

CITIZENS

# Radio Call Book Magazine






and TECHNICAL REVIEW

SPRING  
EDITION

50¢



SERVICE - REPAIR - ENGINEERING

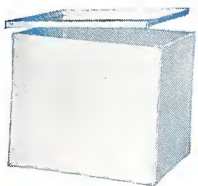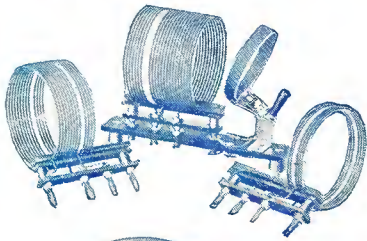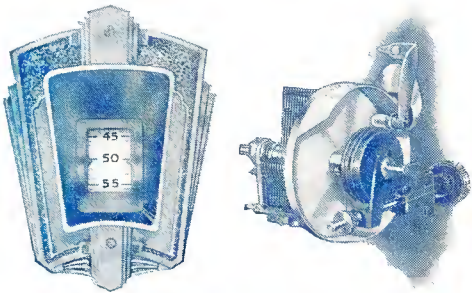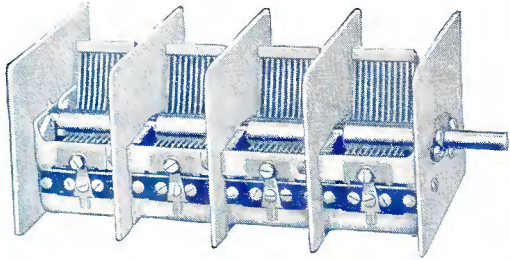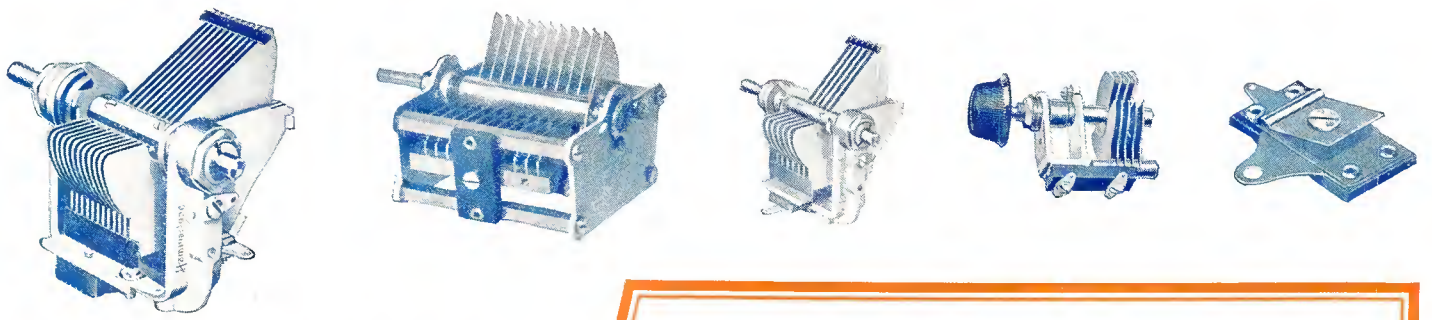

# SUCCESS

to the **SERVICE MAN**

**As Good Tools Help to Make a Good Mechanic. Good Parts are Essential to Efficient Service Work**

**E**VERY service man knows how much his work is simplified and his reputation sustained by parts he can rely on. "Cheapness" in anything is the most expensive in the long run.

In making replacements, remember *Hammarlund reliability*.

Since radio began, Hammarlund has been condenser headquarters. Later came coils, dials, chokes, shields, couplings and the famous "HiQ" Custom-Built Receivers—*all leaders in their field.*

Not by chance has Hammarlund leadership been maintained—but by the power of better *engineering*, better *manufacturing* and better *values*.

Will you give us the opportunity to assist you? We shall welcome it.

Send 25c for HiQ-31 Manual. A Mint of Helpful Information



**HAMMARLUND MFG. CO.**  
424-438 West 33rd Street  
New York, N. Y.

MAIL  
COUPON  
for  
Data

For Better Radio  
**Hammarlund**  
PRECISION  
PRODUCTS

HAMMARLUND MFG. COMPANY,  
Dept. CB-7,  
124-438 W. 33rd St., New York.  
Please send me free literature on Hammarlund Parts. If HiQ-31 Manual is wanted check here  and enclose 25c (cash or stamps).

Name \_\_\_\_\_


Address \_\_\_\_\_

# AMERTRAN POWER AMPLIFIERS

TYPE PA (Series 80) AmerTran Amplifiers provide an economical means of obtaining quality reproduction of sound in large volumes. The large sizes have sufficient output to operate three or four dynamic loud speakers at full volume, or they may be used to distribute audio-frequency power to numerous magnetic loud speakers or head phones. For home use there are smaller models.

Easily installed, fool-proof, so compact they are easily handled with no danger of damage, these complete amplifiers are assembled from parts of the same high quality as those AmerTran units which have won the distinction of being considered the "Standard of Excellence for Audio Reproduction."

**Type PA,  
Series 80**

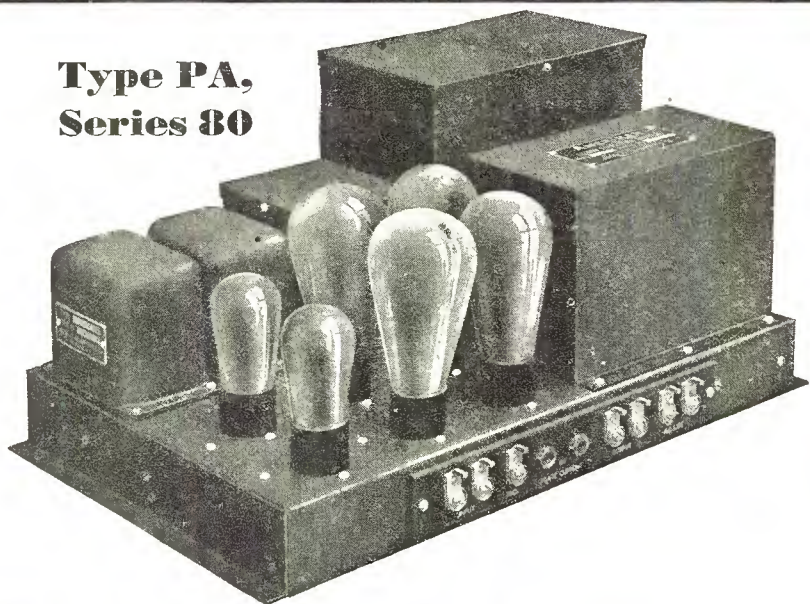

## AmerTran Sound Systems

Complete AmerTran sound systems of the rack and panel type are now available for every application where flawless reproduction is required—in schools, apartments, concert halls, amusement parks, hotels, clubs, and large private homes.

Although of standard design, the interchangeable panel construction permits of many varied combinations to fit any requirement. They are assembled to satisfy the customer's exact specifications—and delivery can be made promptly.


These AmerTran Sound Systems represent the best that modern engineering genius and skilled workmanship can produce with finest quality materials.
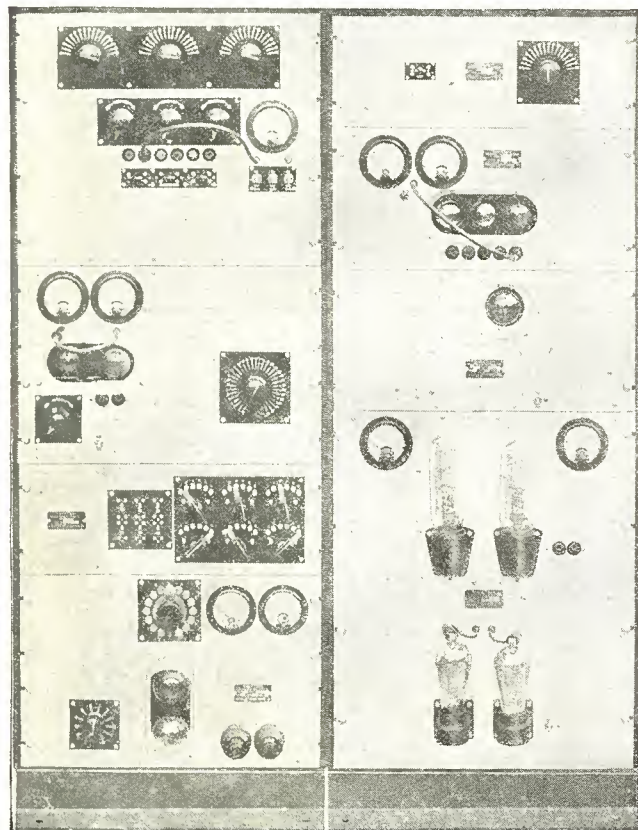
### Other AmerTran Products

Audio-Frequency Transformers  
Transmitting Equipment  
Power Amplifiers  
Filter Chokes



Power-Supply Transformers  
Parallel-Feed Chokes  
Sound Systems  
Power Blocks



American Transformer Company  
178 Emmet Street, Newark, N. J.

R. C. B. 1-31

Please send me your general catalog describing AmerTran audio parts and power amplifiers.

Name .....  
Street & No. ....  
Town..... State.....

**AMERICAN  
TRANSFORMER COMPANY**  
178 EMMET STREET  
NEWARK, N. J.

*Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review*

# More Power per Dolla

- Compare PAM amplifiers with any others or test them side by side with others in any unbiased properly equipped laboratory. The result is always the same. PAM amplifiers will give you the most actual measured power per dollar.

- In addition you will also find a better frequency characteristic, higher efficiency with less hum and lower operating temperature. Many invisible refinements such as condensers with an expected operating life of twenty five years, fuse protection, output terminals that are not alive with high voltage direct current, etc. are a part of each PAM.

- All of which means you receive more of what you want and less of what you do not want in a PAM amplifier.

- As a buyer, if you consider these statements, you cannot purchase other than a PAM for any amplifier installation if you desire the most value for your dollar.

- Send for bulletin C.C.B. 8 entitled "More Power per Dollar" which describes latest Samson Amplifiers.

Main Office;  
Canton, Mass.

**Samson Electric Co.**

MANUFACTURERS SINCE 1882


MEMBER  
**RMA**

Factories; Canton and  
Watertown, Mass.

# BIG PAY JOBS

*open*

## for Every Radio Trained Man

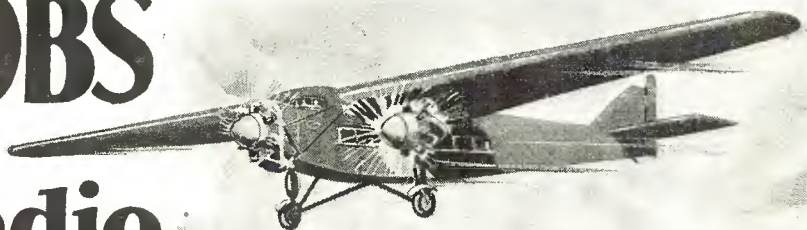

Don't spend your life slaving away in some dull, hopeless job! Don't be satisfied to work for a mere \$20 or \$30 a week. Let me show you how to make **real money in Radio**—the fastest-growing, biggest money-making game on earth.

**Thousands of Jobs Paying \$60, \$70 to \$200 a Week**

Jobs as Designer, Inspector and Tester paying \$3,000 to \$10,000 a year—as Radio Salesman and in Service and Installation Work, at \$45 to \$100 a week—as Operator or Manager of a Broadcasting Station, at \$1,800 to \$5,000 a year—as Wireless Operator on a Ship or Airplane, as a Talking Picture or Sound Expert—Thousands of jobs paying \$60 and up to \$200 a week!

## Learn Without Lessons *in* 60 Days

Coyne is NOT a Correspondence School. We don't teach you from books or lessons. We train you on the greatest outlay of Radio, Television and Sound equipment in any school—on scores of modern Radio Receivers, huge Broadcasting equipment, the very latest newest Television apparatus, Talking Picture and Sound Reproduction equipment, Code Practice equipment, etc. You don't need advanced education or previous experience. We give you **RIGHT HERE IN THE COYNE SHOPS**—all the actual practice and experience you'll need. And because we cut out all useless theory, you graduate as a Practical Radio Expert **IN 60 DAYS' TIME**.



# TELEVISION *and* TALKING PICTURES

And now Television is on the way! Soon there'll be a demand for THOUSANDS of TELEVISION EXPERTS! The man who learns Television now can make a FORTUNE in this great new field. Get in on the ground-floor of this amazing new Radio development! Come to COYNE and learn Television on the very latest, newest Television equipment.

Talking Pictures and Public Address Systems offer thousands of golden opportunities to the Trained Radio Man. Here is a great new Radio field just beginning to grow! Prepare NOW for these wonderful opportunities! Learn Radio Sound Work at COYNE on actual TALKING PICTURE and SOUND REPRODUCTION equipment.



## No Books - No Lessons All Practical Work at Coyne

No Books! No Lessons! ALL ACTUAL, PRACTICAL WORK. You build radio sets, install and service them. You actually operate great Broadcasting equipment. You construct Television Receiving Sets and actually transmit your own Television programs over our modern Television equipment. You work on real Talking Picture machines and Sound equipment. You learn Wireless Operating on actual Code Practice apparatus. We don't waste time on useless theory. We give you just the practical training you'll need—in 8 short, pleasant weeks.

## EARN as You LEARN

Don't worry about a job! You get Free Employment Service for Life. And don't let lack of money stop you. If you need part-time work while at school to help pay expenses, we'll gladly help you get it. Coyne is 31 years old! Coyne Training is tested—proven beyond all doubt. You can find out everything absolutely free. Just mail coupon for my big free book!

**RADIO DIVISION COYNE ELECTRICAL SCHOOL**  
 H. C. LEWIS, President Founded 1899  
 500 S. Paulina St. Dept. 11-5A, Chicago, Ill.

H. C. LEWIS, President


**Radio Division, Coyne Electrical School**  
 500 S. Paulina St., Dept. 11-5A, Chicago, Ill.

Send me your Big Free Radio Book and all details of your Special Introductory Offer. This does not obligate me in any way.

Name .....

Address .....


City ..... State .....

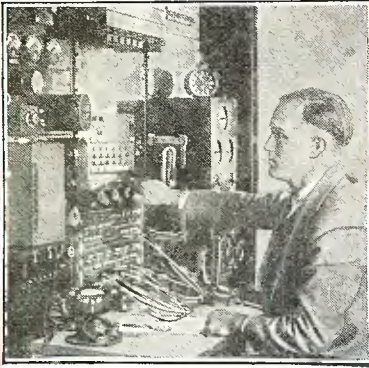

Broadcasting Stations offer fascinating jobs paying from \$1,800 to \$5,000 a year.



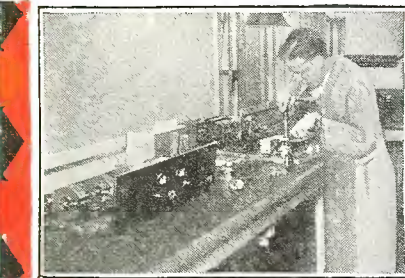
Operating on board ship gives you world-wide travel without expense and a salary of \$85 to \$200 a month besides.



Spare time set servicing is paying N. R. I. men \$200 to \$1,000 a year for their spare time. Earnings begin almost at once after enrolling.



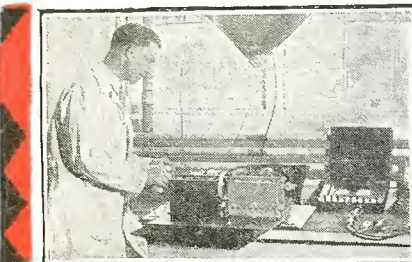Commercial Land Stations are being opened very rapidly in our leading cities. Trans-Oceanic telephony offers many attractive jobs.



Radio factories employ thousands. Salaries for well trained men range from \$1,800 to \$5,000 a year.

# You're Wanted

## Take your pick of these fine **Big Pay** Radio Jobs

You have seen how the men and young men who got into the automobile, motion picture and other industries when they were started had the first chance at the key jobs—are now the \$5,000, \$10,000 and \$15,000 a year men. Radio offers you the same chance that made men rich in those businesses. Its growth has already made men independent and will make many more wealthy in the future. Its amazing growth can put you ahead too. Don't pass up this opportunity for a good job and future financial independence.

### Hundreds of \$50 to \$100 a week jobs Opening Every Year

Radio needs more trained men badly. Why slave your life away for \$25 to \$40 a week in a no-future job when you can get ready in a short time for Radio where the good jobs pay \$50, \$60, \$75 and \$100 a week? And many of these jobs can quickly lead to \$150 to \$200 a week. Hundreds of fine jobs are opening every year for men with the right training—the kind of training I'll give you.

### I Am Doubling and Tripling Salaries

Where you find big growth you always find many big opportunities. I am doubling and tripling the salaries of many men every year. After training with me only a short time they are able to make \$1,000 to \$3,000 a year more than they were getting before. Figure

out for yourself what an increase like this would mean to you—the many things that mean so much in happiness and comfort that you could buy with an additional \$1,000 to \$3,000 a year.

### Many Make \$10 to \$25 a week Extra Almost at Once

The day you start I'll show you how to do ten jobs common in most every neighborhood that you can do in your spare time. I'll show you how to repair and service all makes of sets and do many other jobs all through my course. I'll give you the plans and ideas that are making \$200 to \$1,000 for my students while they are taking my course. G. W. Page, 107 Raleigh Apts., Nashville, Tenn., writes: "I made \$935 in my spare time while taking your course."

### You Have Many Jobs to Choose From

Broadcasting stations use engineers, operators, station managers. Radio manufacturers continually need testers, inspectors, foremen, engineers, service men, buyers and managers. Shipping companies use hundreds of operators and give them world-wide travel with practically no expense and a good salary besides. There are hundreds of opportunities for you to have a spare time or full time Radio business of your own. I'll show you how to start one with practically no capital. My book tells you of other opportunities. Be sure to get it at once.



### \$400 a Month

"I spent fifteen years as traveling salesman and was making good money but could see the opportunities in Radio. Believe me I am not sorry, for I have made more money than ever before. I have made more than \$400 each month and it really was your course that brought me to this. I can't say too much for your school."

J. G. Dahlstead,  
1484 South 15th St.,  
Salt Lake City, Utah.



### \$800 in Spare Time

"Money could not pay for what I got out of your course. I did not know a single thing about Radio before I enrolled, but I have made \$800 in my spare time although my work keeps me away from home from 6:00 A. M. to 7:00 P. M. Every word I ever read about your course I have found true."

Milton I. Leiby, Jr.,  
Topton, Pa.



### Seldom Under \$100 a week

"My earnings in Radio are many times greater than I ever expected them to be. In November I made \$577, December \$645, January \$465. My earnings seldom fall under \$100 a week. I say the N. R. I. course is thorough and complete. You give a man more for his money than anybody else."

E. E. Winborne,  
1267 W. 48th St., Norfolk, Va.

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# for a **Big Pay** Radio Job



**I will train you AT HOME**  
**free book gives facts and proof**

**I Will Train you at Home in Your Spare Time**

Hold your job. There is no need for you to leave home. I will train you quickly and inexpensively during your spare time. You don't have to be a high school graduate. My course is written in a clear, interesting style that most anyone can grasp. I'll give you practical experience under my 50-50 method of training—one-half from lesson books and one-half from practical experiments. When you graduate you won't have to take any kind of a job to get experience—you will be trained and experienced ready to take your place beside men who have been in the field for years.

**Television and Talking Movies Included**

My course not only gives you a thorough training in Radio—all you need to know to get and hold a good job—but also your choice without extra charge, of any one of these special courses: Television, Aircraft Radio, Broadcasting, Commercial and Ship Radio Stations, Sound Pictures and Public Address Systems, and advanced Radio Servicing and Merchandising. You won't be a "one job" man when you finish my course. You'll know how to handle a job in any one of Radio's 20 different branches of opportunity.



**Salary Three Times Larger**

"Before I completed your course I went to work for a Radio dealer. Now I am assistant Service Manager of the Sparks-Withington Company. My salary is three times what it was before taking your course. I could not have obtained this position without it. I owe my success to N. R. I. training."

H. A. Wilmoth,  
 Sparks-Withington Co.,  
 Jackson, Mich.

**Lifetime Employment Service to All Graduates**

When you finish my course you won't be turned loose to shift for yourself. Then is when I will step in and help you find a job through my Employment Department. This Employment Service is free of extra charge both to you and the employer. My Employment Department is getting three times as many calls for graduates this year as last year.

**Your Money Back if Not Satisfied**

You do not risk a penny when you enroll with me. I will give you an agreement in writing, legal and binding upon the institute, to refund every penny of your money upon completing my course if you are not satisfied with my Lessons and Instruction Service. The resources of the N. R. I., Pioneer and World's Largest Home-Study Radio, training organization stands back of this agreement.

**Find Out What Radio Offers You—Get My Book at Once**



One copy of my valuable book "Rich Rewards in Radio" is free to anyone interested in making more money. It tells you where the good jobs are, what they pay, how you can quickly and easily fit yourself to get one. The coupon below will bring you a copy. Send it at once. Your request does not obligate you in any way. Act NOW.

**J. E. SMITH, President**  
 Dept. IAE  
 National Radio Institute  
 Washington, D. C.



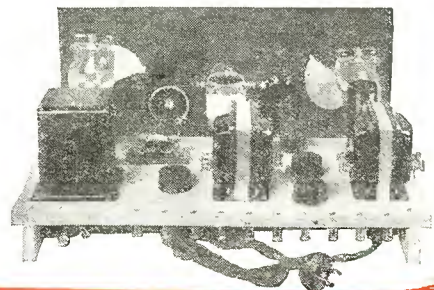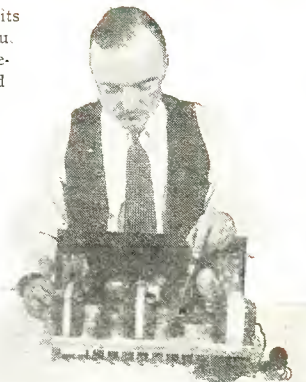**I give You 8 Big Outfits of Radio parts for a home Experimental Laboratory**

You can build over 100 circuits with the outfits I give you. You learn from actual experience about A.C. Screen Grid Circuits, push-pull amplification and the other features in modern sets. You work out with your hands the principals, diagrams and circuits you learn from my lesson books. You get as much practical experience under this unequalled method of home training, in a few months, as the average fellow gets in two to four years in the field.



**Clip and mail NOW for FREE INFORMATION**

**J. E. SMITH, President**  
 National Radio Institute, Dept. IAE  
 16th & U Streets, N. W., Washington, D. C.

Dear Mr. Smith:—Send me "Rich Rewards in Radio." Tell me more about Radio's opportunities for good jobs and quick promotion; also about your practical method of Home training. I understand this request does not obligate me and that no agent will call on me.

Name.....

Address.....

City.....State.....

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# Citizens Radio Call Book Magazine

## AND TECHNICAL REVIEW

(Copyright, 1931)  
Established 1921

C. O. STIMPSON, President  
H. ANHEISER, Treasurer  
F. A. HILL, Editor  
RICHARD K. PEW, Technical Editor

Executive Offices:  
508 So. Dearborn St., Chicago, Ill.  
Member Audit Bureau of Circulations

Advertising Representatives:

Chicago—A. B. Mills, 508 S. Dearborn  
Phone Wabash 1901  
New York—(Branch Office) 154 W. 42nd St.  
Room 1125, Wisconsin 7-5681 and Wisconsin 7-1429

JANUARY, 1931

Published January, March, September, November

Vol. 12, No. 1

### Contents This Issue

#### BROADCAST

Chain Distribution .....	12
U. S. Broadcasting Stations.....	13-20
Consolidated Broadcast List....	21
Broadcasting Stations by Fre- quencies .....	22
U. S. Broadcast Stations by States .....	23
Foreign Broadcast Stations.....	23-25
Short Wave and Visual Broad- cast Stations .....	25
Mileage Chart .....	26-27
Handy Receiver Log.....	28

#### PICTORIAL RADIO

Quick Test for Receiver Trou- ble .....	29
Reviving Faded Engraving.....	29
Cake Pan for Power Supply Mounting .....	29
Soap Model of Station WFAA	29
Increasing Regeneration of 224	30
Mike and Amplifier Hears Gas Knock .....	30
Raising Voltage of Power Sup- ply .....	30
Don't Tip Electrolytic Con- densers .....	30
Antenna Substituter is Port- able .....	30

#### FEATURE ARTICLES

Power Amplifier Measure- ments .....	31-32
A Page of Interesting Pictures	33
Scott 1931 All-Wave Super....	34-35

Field Strength Effect on Re- ceivers .....	36-37
Design Data on H. F. L.'s "Lit- tle Giant" Super.....	38-39
W9XF Short Wave Transmit- ter at WENR.....	40
By E. H. Gager	
Lincoln D. C. 8 for Use with Breather Battery .....	41
Distortion and Cross-Talk Re- duced .....	42-43
Silver 714 Custom Built Super	44
Westinghouse Remote Control	45
Short Wave and Broadcast on A. C. Conqueror.....	46

#### SERVICE and REPAIR SECTION

Factory Schematic Index.....	47
Aligning R. F. and I. F. Stages in Radiola Supers.....	47-49
Circuit for Adding Pick-Up to Westinghouse Receivers ....	49
Increasing Utility of D. C. Me- ters .....	50-51
By Jesse Marsten	
Service Data on the New Ma- jestic 50 Chassis.....	52-53
Locating Internal Noises in Re- ceivers .....	54-55
By F. L. Sprayberry	

#### RESPONSE CURVE SECTION

Receiver Response Data.....	56
General Motors 120.....	57
Crosley 53-54 .....	57
General Electric Model H-31..	58

Radiola 80 Super.....	58
Amrad Model 84.....	59
Graybar 700 Super.....	59
Kennedy Model 42.....	60
Audiola 31 Super.....	60
Columbia Model 100.....	61
Silver 36-A Super.....	61
Atwater-Kent 72 Super.....	62
Zenith Model ZE-70 Jr.....	62
Sentinel 106 Super.....	63
Stromberg-Carlson Model 10..	63

#### SERVICE and REPAIR SCHEMATICS

Edison R6, R7.....	64
Victor R35, R39, RE57.....	65
Crosley 53 and 54.....	66
Bosch Model 58.....	67
Apex 31 (U. S. Radio).....	68
Silver 36-A Super.....	69
Amrad Model 84.....	70
Radiola 44 .....	71
Westinghouse WR4 .....	72
Radiette F 14.....	73
Stewart Warner R-100.....	73
Kennedy Model 10.....	73

#### RADIO ENGINEERING

Speakers and Theater Sound Reproduction .....	74-75-76
By Louis Malter	

#### MISCELLANEOUS

New Products for the Trade....	86
Annual Questionnaire .....	106
Blueprint Page .....	111



# Announcing the SCOTT

# ALL-WAVE


**IN WHICH SCOTT OUTDOES SCOTT IN POWER, SELECTIVITY AND TONE + + + +**

THOSE who know Scott World Record Receivers will find it difficult to believe that a better receiver could be built. And such would not have been possible, had the Scott Laboratories not developed an ingeniously new type of intermediate transformer. But they *did*, and results so greatly exceed any present day idea of radio performance, that even imagination cannot conceive the wonders of which this receiver is capable. Scott again challenges the industry to any kind of competitive test.


In the new Scott intermediate transformer—the heart of the new Scott twelve tube screen grid All-Wave Superheterodyne—the primary winding is completely isolated and shielded from the secondary. Coupling between the two is achieved in a way that permits the vacuum tube to function as it never has before. Tremendous amplification is obtained—far more than is possible with the orthodox coupling transformer. And the amplification is automatically controlled and regulated to absolute precision, making the receiver equally sensitive over the whole wave band! See the sensitivity curve reproduced herein. It is the flattest sensitivity curve yet plotted by Citizens Radio Call Book Laboratory. At the same time, *selectivity* is given an entirely new meaning. Practically speaking, there are no conditions under which the new Scott All-Wave Superheterodyne will not give absolute, precise 10 Kilocycle separation between 200 and 550 meters. And without sacrifice in tone! The entire musical scale is covered fully, roundly and perfectly. See the Scott *selectivity* curve, illustrated on this page, and elsewhere in this issue. Check it! Compare it!

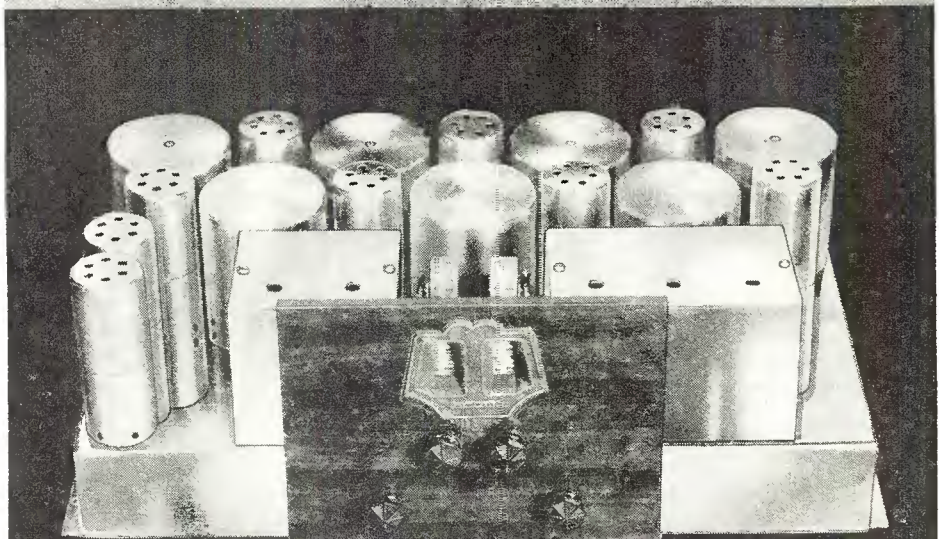**International Range**

There is no limit to the range of the new Scott All-Wave Superheterodyne. With this receiver, the whole world awaits the dial, for it tunes everything between 20 and 550 meters and brings all stations in with more volume than can be used. Think of it! Short wave reception—foreign broadcasts at the mere flick of a dial—from




# SUPERHETERODYNE

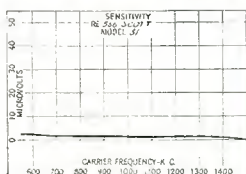

This curve shows the Scott All-Wave to be equally sensitive between 600 and 1400 K.C.

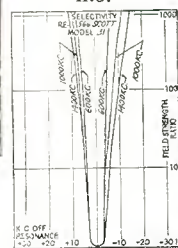This curve shows the Scott All-Wave to be equally selective between 600 and 1400 K.C.



Both charts were made in the Engineering Laboratory of the Citizens Radio Call Book.

the same receiver that brings you your local programs. The Scott All-Wave is the only self-contained universal receiver in existence today—and it costs less than many receivers that operate only between 200 and 550 meters.

**All-Metal Chassis**

The performance of this great new-day receiver is not its only distinguishing feature.

Its construction is equally distinctive. The chassis is heavy pressed steel—heavily chrome-plated and polished. Shields are likewise chromed and polished. A more beautiful, more rugged mechanical construction has never been seen in the entire radio industry. And every chassis is custom-built and custom-tested in the Scott Laboratory.

Full particulars of the new Scott All-Wave Superheterodyne will be gladly furnished. Simply sign and clip the coupon from this announcement and mail at once. It will bring you the most interesting radio story ever told.

## MAIL this COUPON

**SCOTT TRANSFORMER CO., 4450 RAVENSWOOD AVE., CBI, CHICAGO, ILL.**

Sole Representative for New Zealand: CHAS. BEGG & CO., Ltd., 21 Princess St., Dunedin, N. Z.  
Sole Representative for Uruguay: ARMANDO I. LOPEZ, Chile 388 Cerro, Montevideo, Uruguay

SCOTT TRANSFORMER CO. CBI  
4450 Ravenswood Ave., Chicago.

Send me full particulars of the new Scott All-Wave Superheterodyne.

NAME .....

STREET .....

TOWN ..... STATE .....

Be sure to read every page of it

# SEND FOR BIG FREE CATALOG

Going Big!

You are not fully equipped without our 40 page Catalog


## THE NEW MELORAD

Cathedral Tone

MANTLE SET


TRIPLE SCREEN-GRID  
TONE CONTROL  
MATCHED DYNAMIC  
SPEAKER

Dealers and Servicemen!

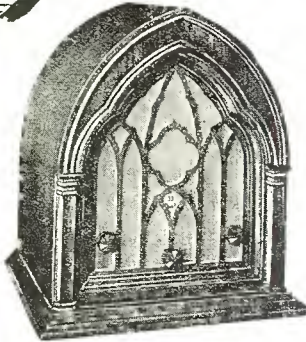


Housed in this gorgeous walnut Gothic Cabinet 16 1/2" high, 14 1/2" wide and 10 1/4" deep. Only

**\$26<sup>95</sup> | \$24<sup>50</sup>**

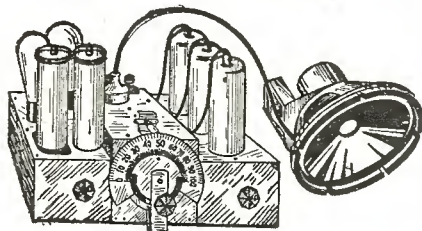

Chassis uses 3-224, 1-245 and 1-280 tubes and is equipped with matched dynamic speaker. For chassis and speaker. Tubes, \$2.50 extra.

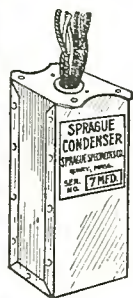Be prepared to meet the great demand for this popular radio set during the holiday season. Equals the performance of any console receiver and yet you can sell it for less than \$75.00 completely installed and still double your investment. Order your sample to-day and avoid the last-minute rush.



### REPLACEMENT Condenser Blocks

- Peerless Courier, as illustrated, ea. \$1.75  
A K 37 ..... 4.80  
Majestic B ..... 2.95  
Victor R32 ..... 3.25  
R C A 18, 33 and 51 1.50  
R C A 17 ..... 4.95  
R C A 41 ..... 4.25  
R C A 60, 62 ..... 5.95  
Zenith 11E ..... 3.25  
Brandes B15 ..... 2.95  
Kolster 6H ..... 2.95  
Kolster K21 ..... 2.50  
Kolster K43 ..... 3.25  
Kolster K22, 20, 42 3.25

### Voltage Dividers, Fixed Resistances and GRID Suppressors


Ward-Leonard, Aerovox, Ohmite and Hy-watt wire wound resistances from 33 to 250,000 Ohms for all standard sets at 20 to 50c each. Full description in our catalog.


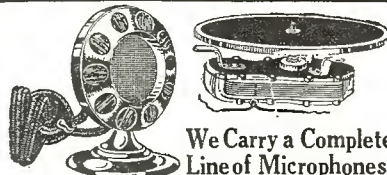
### Centralab, Frost, Yaxley, Clarostat, Bradley-ohm, Carter and Electrad Variable Volume Controls and Potentiometers

All sizes from 2 to 500,000 ohms carried in stock for replacements in all standard sets. Prices from 20 to 45c each. ALSO Wire Wound and Carbon pigtail resistances from 10 ohms to 5 megohms at \$1.50 per dozen.

FOR PRICES GET OUR CATALOG  
MAIL YOUR ORDER TO




### We Carry a Complete Line of Microphones, Turntables, Pick-ups and Amplifiers for Public Address Systems and Theatres.

Universal Baby Mike. A real microphone, single button, with covers and 25 ft. of cable. List, \$7.50. Our Price, \$4.50.

### Carryola Synchronous Motor

Complete with turn-table. Silent, sturdy and compact, only 1 1/4" thick. No brushes. Only \$4.25.

### Bosch Power Amplifier

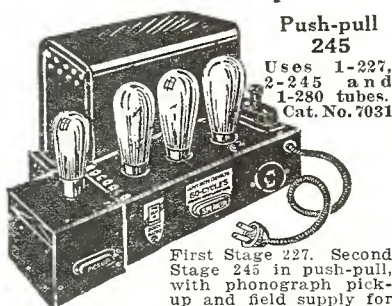


Push-pull 245  
Uses 1-227, 2-245 and 1-280 tubes. Cat. No. 7031  
First Stage 227. Second Stage 245 in push-pull, with phonograph pick-up and field supply for 2500 ohm D. C. dynamic speaker with or without input transformer (specify which). Also furnishes filament and plate voltage for 224, 227 tubes. Can be used to convert any battery set into an up-to-date A. C. receiver with 245 push-pull audio.

OUR NET PRICE, \$19.50

### Power Transformers For all Standard Sets Carried in Stock

Model illustrated is for A. C. Dayton Navigator and other sets using 224, 227, 245 and 280 tubes, \$3.85.


VARIABLE LINE VOLTAGE → 105V. 115 120V.

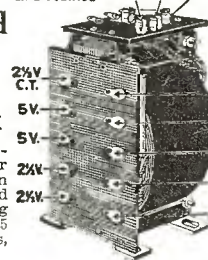

- |                       |         |
|-----------------------|---------|
| Freshman Q            | \$ 6.75 |
| Freshman QD           | 7.85    |
| Philco sets           | 3.75    |
| Zenith 33, 35         | 3.25    |
| Radiola 44, 46        | 4.95    |
| RCA Double Choke      | .95     |
| AK40-42 Power Pack    | 11.50   |
| AK46 Power Pack       | 15.00   |
| Sonora B33            | 4.75    |
| RCA Audio             | .55     |
| Earl 21, 22           | 2.25    |
| Radiola 60, 62        | 5.95    |
| Kolster K20           | 2.25    |
| Stromberg-Carlson 642 | 3.95    |
| Step down 220 to 110V | 3.95    |
| Kolster 6H            | 7.50    |
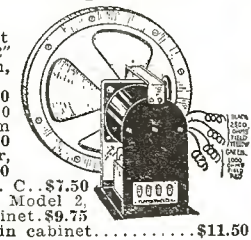
### Dynamic Speakers

- Peerless Giant Auditorium, 12" Diaphragm, 110 V., A. C. \$14.50  
D. C. with 1000 and 2500 ohm fields .. \$10.00  
Peerless Courier, 7" D. C. \$7.50  
Baldwin, 9", A. C. \$7.50  
Temple A. C., Model 2, in Walnut Cabinet. \$9.75  
Peerless 17A, in cabinet..... \$11.50



TERMS:—20% with order, balance C.O.D. 2% discount allowed for full remittance with order only.

# Federated Purchaser

114 Reade Street

New York, N. Y.

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review


# Here's the Very Set That Did It—the New *Lincoln D.C. 8-Super*

**“Too Good to Be True”  
But It's True—**

that marvelous Test Report in this issue of the Call Book—so far surpassing others as to defy belief. To see, for once, how *genuine* 10 KC selectivity looks in an engineering test—turn to page 41; and notice too, the beautiful tone-quality and sensitivity curves of this new D.C. Lincoln!

**Self-Contained Power  
—No A.C. Line Interference**


Crystal-clear long-distance reception, free from the cracks, growls and sputter of A.C. line interference and fluctuations—that's the gift of the new Lincoln DC-8. And since it uses the new low-amperage 2 volt D.C. tubes (filament supply operates from oxygen in the air—no acids—no charging) you can assemble it in a console with *self-contained power* and forget it for a year. Now, indeed, there's real reward in a D.C. set!

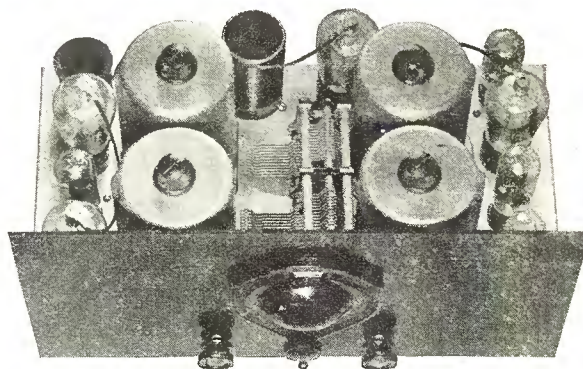

**GET THE AMATEUR PHONE BAND  
(80 Meters)—By Just Throwing a Switch!**

There's a new principle entirely in this marvelous new D.C. Lincoln Super—without changing a coil, just by snapping a switch on the panel, we have tuned in at the Lincoln laboratory hundreds of amateur phone stations, including all nine districts of the U. S. ! It's uncanny—having the 80 meter phone band spread over 60 degrees of the dial, with all the hum-free D.C. clearness—then flipping the switch back and finding yourself again with the 90 broadcast channels laid out before you like so many tracks in a great railroad stations! Just standard broadcast parts, too—no short-wave coils to fool with—and oh, what a difference it makes in listening, to have the very set that gave those marvelous performance curves!

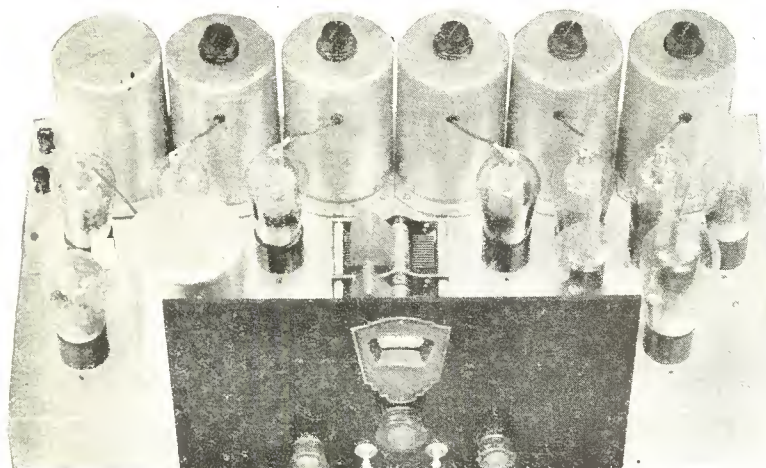**LABORATORY BUILT CHASSIS (Less Tubes) LIST PRICE \$80.00**



Write for full descriptive matter and special discounts to distributors at once. Dept. C12

## *Lincoln De Luxe 31*

*Utilizing Six Screen Grid Tubes in the most powerful, selective receiver known today*

Excerpts from letters received this week:

*Detroit, Mich.* . . . We are located on a main street car line, also within 3 miles of WWJ, the Detroit News, and are picking up Mexico City with this station in operation. Have also picked up KFI and KPO as early as 8:55 P.M. Eastern Standard time. Your machine is nothing short of a wonder. Shamrock, Texas . . . I have verified reception from KXO, El Centro, Cal., with only 100 watts output, get WGY with WFAA on air 10 KC away; get WEAF, WJZ, WFRB; WBZ with KDKA on air; KXO, KJR, and plenty of Mexican stations and some with only 100 watts. Also get Cuban stations and Canadian stations.

*Lynn, Mass.* . . . Your set arrived November 14th in good condition and is set up and running fine. Very much pleased with performance and workmanship. It certainly beats everything in radio. Near center of city in noisy locality, set brings in stations with fine volume and clarity in daytime never before listenable on any other set I have heard. Tone quality fine, separation of stations perfect. Look for some more orders from me very soon.

*Cincinnati, Ohio.* . . . I have a Lincoln Deluxe "31" for the family and think it absolutely the best I ever heard of all makes.


*Oklahoma City, Okla.* . . . Your new chassis and power pack received recently and certainly works fine. Have logged stations from all four corners of the United States and more.

**LINCOLN RADIO CORPORATION**  
**329 SOUTH WOOD ST. - CHICAGO - ILLINOIS**

*Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review*

# WANT TO MAKE A SUCCESS?
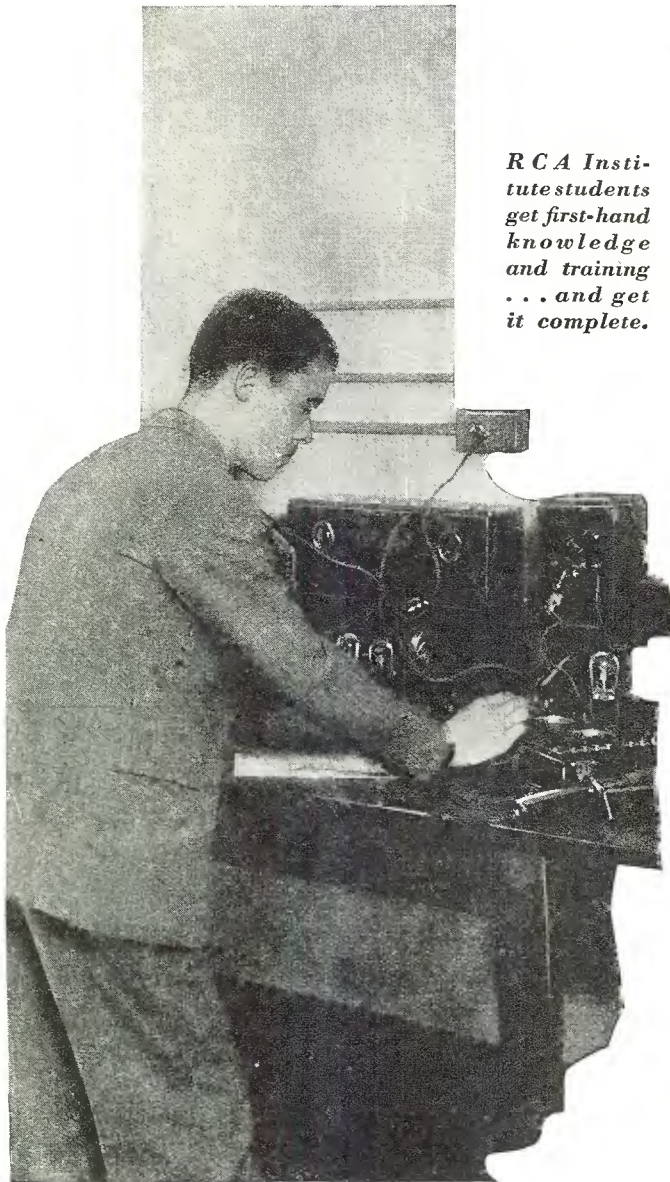
## Study radio in your spare time at home



*RCA Institute students get first-hand knowledge and training . . . and get it complete.*

**A**RE you satisfied with the position you now hold? Do you feel that you're worth more money? Are you pleased with yourself, your work, your associates . . . and your future? What does next year hold for you . . . and the year after that?

Are you content to merely plod along through the best years of your life . . . or do you want to get into far pleasanter work . . . meet more interesting people . . . and hold a well paid position?

The ambitious man ties his future to an industry that's developing rapidly . . . that's going *up and up!* Your life lies before you . . . will it be a losing game or a profitable adventure? . . . Will you GROW with a GROWING BUSINESS or will you waste your life and opportunities in an industry that is already fighting a losing battle?

If you are looking for a REAL opportunity . . . if you want to make the most of your life . . . to grasp the success that should be yours, *then we say to you, "Study Radio."*

Everyone knows that Radio is the fastest growing industry in the world today . . . countless opportunities are waiting for men who have the training and ability to grasp them. Where have you heard of any business that has developed as fast as this? Radio needs *trained* men and needs them NOW! *Think of the future Radio offers you!*

You can easily obtain the training you need under the direction of RCA Institutes, a division of Radio Corporation of America, which thoroughly trains men in every branch of radio and also assists them in obtaining employment. You learn radio by actual experience on the very latest types of radio equipment. You study under the direction of nationally known experts. You can learn all about radio servicing and selling, ship operating, shore station operating, radio telephony and telegraphy, and airplane radio equipment . . . also instruction in sound motion picture installation, maintenance and repair!

### *Study at Home in Your Spare Time*

The RCA Institutes complete Home Laboratory Training Course gives you all you need to know about radio. The lessons are of absorbing interest . . . easy to learn. You rapidly progress, step by step . . . and you receive absolutely free the complete RCA Institutes Laboratory Equipment, a modern outlay of apparatus furnished to every student . . . enabling you to easily solve radio problems. This is the way for you to acquire, in your spare time, the commercial knowledge and ability that command good pay.

### *Home Training Course By America's oldest and foremost Radio training organization*

This home training course and free laboratory equipment are backed by more than 20 years' experience. A signed agreement by RCA Institutes assures you of absolute satisfaction . . . furthermore, if after taking this course you are not satisfied in every way, your money will promptly be returned to you.

### *Read this free book*

Everything you want to know about Radio . . . Describes in detail the home training that has placed thousands of men in good paying positions. Forty fascinating pages of pictures and text all about radio.

RCA INSTITUTES, Inc.  
Dept. BC-1  
75 Varick St., New York, N. Y.

Gentlemen: Please send me your big FREE 40-page book which tells about the many opportunities in Radio and about your famous laboratory method of radio instruction at home.



**Mail this  
coupon  
NOW . . .  
start on the  
road to suc-  
cess in radio  
T O D A Y !**

Name \_\_\_\_\_

Address \_\_\_\_\_


Occupation \_\_\_\_\_

*Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review*

# READ HOW YOU CAN
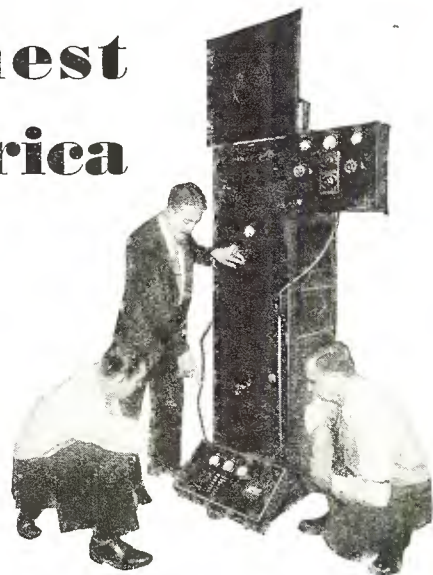
## Study radio in the finest equipped schools in America

In order to make it easy for you to study radio, RCA Institutes has opened six completely equipped schools throughout the country . . . at New York, Chicago, Boston, Baltimore, Philadelphia and Newark, N. J. Each of these six schools has the very last word in radio equipment. They all offer exactly the same training in day or evening classes . . . you study under the personal direction of RCA experts. In this way you learn at the very heart of radio itself, because you study under the direction of RCA . . . the great corporation that sets the standards for the entire radio industry. The very progress of radio is measured by the achievements of the famous engineers in the great research laboratories of the Radio Corporation of America.



*You get commercial training that prepares you for success in radio.*

### Only training course sponsored by Radio Corporation of America

Graduates of these schools are thoroughly posted in all the very latest developments, the newest inventions and greatest discoveries in radio, because they study in the finest equipped schools in America.


That's what RCA Institutes does for you . . . that's the kind of training you want . . . the practical, thorough knowledge that you need for success in radio.

### Opportunities for Trained Men

Graduates frequently obtain positions shortly after graduation. Every graduate receives the thorough training that gives him the knowledge and the confidence to hold a good paying position.
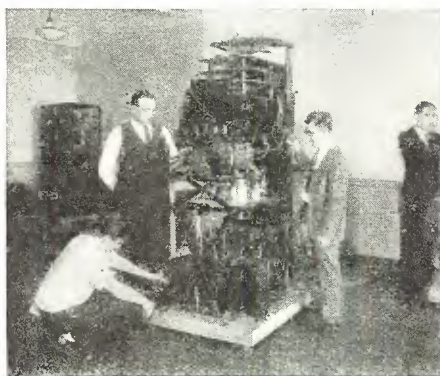
### Come in today . . . See for yourself!

Step into the nearest school and then you will know why it is that thousands of men have acquired the training that has enabled them to occupy well paid positions in radio. Meet the instructors, talk to the students, examine the equipment . . . convince yourself . . . See what radio can offer you, and what RCA Institutes can DO for you. We will be glad to meet you . . . glad to explain everything . . . to show you everything . . . without the slightest obligation on your part! Come in today and get a copy of our free book, or send for it by mail. See what our course has done for others and what it can do for you!



#### BOARD OF MANAGERS OF RCA INSTITUTES, Inc.

The names of these men are known throughout the world as the greatest names in radio. Their experience will guide you in your training

Chairman of the Board  
**GENERAL JAMES G. HARBORD**  
Chairman of the Board  
Radio Corporation of America

President  
**RUDOLPH L. DUNCAN**

Vice-President  
**F. R. BRISTOW**

**WILLIAM BROWN**  
Vice-President and General Counsel  
Radio Corporation of America

**W. A. WINTERBOTTOM**  
Vice-President  
RCA Communications, Inc.

**CHARLES J. PANNILL**  
Vice-President  
Radiomarine Corporation of America

**GEORGE S. DE SOUSA**  
Treasurer, Radio Corporation of America

**E. A. NICHOLAS**  
President, E. A. NICHOLAS, Inc.

**A. E. REOCH**  
Vice-President, RCA Photophone, Inc.

**CHARLES HORN**  
General Engineer  
National Broadcasting Company

Send this coupon to the school most convenient for you to attend.

## RCA INSTITUTES, INC.

A division of Radio Corporation of America

RCA Institutes, Inc., operates resident schools, giving day and evening classroom instruction in the following cities. Mail the coupon to or call at the institute most convenient to you.

- 222 North Bank Drive, Chicago
- 75 Varick Street, New York
- 899 Boylston Street, Boston
- 1211 Chestnut Street, Philadelphia
- 560 Broad Street, Newark, N. J.
- 1215 N. Charles Street, Baltimore

RCA INSTITUTES, Inc.  
Dept. BC-1

Please send me catalog describing your resident school (classroom) instruction.

Name.....

Address.....

Occupation.....



Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# Distribution of Broadcast Chains by Cities

City	Chain	Kilo-cycles	City	Chain	Kilo-cycles	City	Chain	Kilo-cycles
Akron, Ohio			Hartford, Conn.			Portland, Ore.		
WADC ..... Columbia	1320	WTIC ..... National	1060	KGW ..... National	620			
WFJC ..... National	1450	Hopkinsville, Ky.		KOIN ..... Columbia	940			
Asheville, N. C.		WFIW ..... Columbia	940	Providence, R. I.				
WWNC ..... Columbia	570	Hot Springs, Ark.		WJAR ..... National	890			
Atlanta, Ga.		KTHS ..... National	1040	WEAN ..... Columbia	780			
WGST ..... Columbia	890	Houston, Texas		Raleigh, N. C.				
WSB ..... National	740	KPRC ..... National	920	WPTF ..... National	680			
Atlantic City, N. J.		KTRH ..... Columbia	1120	Richmond, Va.				
WPG ..... Columbia	1100	Indianapolis, Ind.		WRVA ..... National	1110			
Baltimore, Md.		WPBM ..... Columbia	1230	Roanoke, Va.				
WBAL ..... National	1060	Jackson, Miss.		WDBJ ..... Columbia	930			
WCAO ..... Columbia	600	WJDX ..... National	1270	Rochester, N. Y.				
Bangor, Me.		WJAX ..... National	900	WHAM ..... National	1150			
WLBS ..... Columbia	620	Kansas City, Mo.		WHEC ..... Columbia	1440			
Bay City, Mich.		KMBC ..... Columbia	950	Salt Lake City, Utah				
WBCM ..... Columbia	1410	WDAF ..... National	610	KSL ..... National	1130			
Birmingham, Ala.		Lawrence, Kan.		KDYL ..... Columbia	1290			
WAPI ..... National	1140	WREN ..... National	1220	San Diego, Calif.				
WBRC ..... Columbia	930	Lincoln, Neb.		KFSD ..... National	600			
Boston, Mass.		KFAB ..... National	770	San Antonio, Texas				
WEEL ..... National	590	Little Rock, Ark.		WOAI ..... National	1190			
WBZA ..... National	990	KLRA ..... Columbia	1390	KTSA ..... Columbia	1290			
WNAC ..... Columbia	1230	London, Can.		San Francisco, Calif.				
Buffalo, N. Y.		CJGC ..... Columbia	910	KGO ..... National	790			
WBEN ..... National	900	Los Angeles, Calif.		KPO ..... National	680			
WKBW ..... Columbia	1480	KECA ..... National	1430	KFRC ..... Columbia	610			
WMAK ..... Columbia	900	KFI ..... National	640	Savannah, Ga.				
Charlotte, N. C.		KHJ ..... Columbia	900	WTOC ..... Columbia	1260			
WBT ..... National	1080	Louisville, Ky.		Schenectady, N. Y.				
Chattanooga, Tenn.		WHAS ..... National	820	WGY ..... National	790			
WDOD ..... Columbia	1280	Memphis, Tenn.		Seattle, Wash.				
Chicago, Ill.		WMC ..... National	780	KOL ..... Columbia	1270			
WGN ..... National	720	WREC ..... Columbia	600	KOMO ..... National	920			
WLIB ..... National	720	Miami, Fla.		Sioux City, Iowa				
WENR ..... National	870	WIOD ..... National	1300	KSCJ ..... Columbia	1330			
WLS ..... National	870	WQAM ..... Columbia	560	Spokane, Wash.				
KYW ..... National	1020	Milwaukee, Wis.		KHO ..... National	590			
KFKX ..... National	1020	WTMJ ..... National	620	KFPY ..... Columbia	1340			
WCFL ..... National	970	WISN ..... Columbia	1120	Springfield, Mass.				
WBO ..... National	560	Minneapolis, Minn.		WBZ ..... National	990			
WMAQ ..... Columbia	670	WCCO ..... Columbia	810	St. Louis, Mo.				
WBBM ..... Columbia	770	WRHM ..... Columbia	1250	KSD ..... National	550			
WJDD ..... Columbia	1130	Montreal, Can.		KVK ..... National	1350			
Cincinnati, Ohio		CKAC ..... Columbia	730	KMOX ..... Columbia	1090			
WLW ..... National	700	Nashville, Tenn.		St. Paul, Minn.				
WSAI ..... National	1330	WSM ..... National	650	KSTP ..... National	1460			
WKRC ..... Columbia	550	WLAC ..... Columbia	1470	Superior, Wis.				
Clearwater, Fla.		New Haven, Conn.		WEBC ..... National	1290			
WFLA ..... National	620	WDRG ..... Columbia	1330	Syracuse, N. Y.				
WSUN ..... National	620	New Orleans, La.		WFBL ..... Columbia	1360			
Cleveland, Ohio		WSMB ..... National	1320	Tacoma, Wash.				
WTAM ..... National	1070	WDSU ..... Columbia	1250	KVI ..... Columbia	760			
WHK ..... Columbia	1390	New York, N. Y.		Tallmadge, Ohio				
Columbus, Ohio		WEAF ..... National	660	WADC ..... Columbia	1320			
WAIU ..... Columbia	640	WJZ ..... National	760	Tampa, Fla.				
WCAH ..... Columbia	1430	WABC ..... Columbia	860	WDAE ..... Columbia	1220			
Council Bluffs, Iowa		Norfolk, Va.		Toledo, Ohio				
KOIL ..... Columbia	1260	WTAR ..... Columbia	780	WSPD ..... Columbia	1340			
Covington, Ky.		Oil City, Pa.		Toronto, Can.				
WCKY ..... National	1490	WLBW ..... Columbia	1260	CKGW ..... National	690			
Dallas, Texas		Oklahoma City, Okla.		CFRB ..... Columbia	960			
WFAA ..... National	800	WKY ..... National	900	Topeka, Kan.				
KRLD ..... Columbia	1040	KFJF ..... Columbia	1480	WIBW ..... Columbia	580			
WRR ..... Columbia	1280	Omaha, Neb.		Tulsa, Okla.				
Davenport, Iowa		WOW ..... National	590	KVOO ..... National	1140			
WOC ..... National	1000	Orlando, Fla.		Washington, D. C.				
Denver, Colo.		WDBO ..... Columbia	1120	WRC ..... National	950			
KLZ ..... Columbia	560	Philadelphia, Pa.		WMAL ..... Columbia	630			
KOA ..... National	830	WFI ..... National	560	Waterloo, Ia.				
Des Moines, Iowa		WLIT ..... National	560	WMT ..... Columbia	600			
WHO ..... National	1000	WCAU ..... Columbia	1170	Wichita, Kan.				
Detroit, Mich.		WFAN ..... Columbia	610	KFH ..... Columbia	1300			
WWJ ..... National	920	Phoenix, Ariz.		Worcester, Mass.				
WJR ..... National	750	KTAR ..... National	620	WTAG ..... National	580			
WXYZ ..... Columbia	1240	Pittsburgh, Pa.		Yankton, S. Dak.				
Fargo, N. Dak.		WCAE ..... National	1220	WNAX ..... Columbia	570			
WDAY ..... Columbia	940	KDKA ..... National	980	Youngstown, Ohio				
Ft. Wayne, Ind.		WJAS ..... Columbia	1290	WKBN ..... Columbia	570			
WOWO ..... Columbia	1160	Portland, Me.						
Ft. Worth, Texas		WCSH ..... National	940					
WBAP ..... National	800							
Harrisburg, Pa.								
WHP ..... Columbia	1430							

# American Broadcasting Stations

Station assignments shown in the following pages were made by the Federal Radio Commission. This list is revised from issue to issue and is therefore up-to-the-minute. Initials such as E, C, M, and P denote Eastern, Central, Mountain and Pacific time.

## KBPS

1420 kc, Portland, Ore., Benson Polytechnic School, 100 w, P.

## KBTM

1200 kc, Paragould, Ark., Beard's Temple of Music, 100 w, C.

## KCRC

1370 kc, Enid, Okla., Champlin Refining Co., 100 w, C.

## KCRJ

1310 kc, Jerome, Ariz., C. C. Robinson, 100 w.

## KDB

1500 kc, Santa Barbara, Calif., D. Faulding, 100 w, P.

## KDFN

1210 kc, Casper, Wyo. D. L. Hathaway, 100 w, P.

## KDKA

980 kc, Pittsburgh, Pa., Westinghouse E. & M. Co., 50,000 w, E.

## KDLR

1210 kc, Devils Lake, N. D., KDLR, Inc., 100 w.

## KDYL

1290 kc, Salt Lake City, Utah, Intermountain Broadcasting Corp., 1000 w, M, "On the Air, Goes Everywhere."

## KECA

1430 kc, Los Angeles, Calif., Pacific Development Radio Co., 1000 w, P.

## KELW

780 kc, Burbank, Calif., Earl L. White, 500 w, P, "The White Spot of the San Fernando Valley."

## KEX

1180 kc, Portland, Ore., Western Broadcasting Co., 5000 w, P, "A Public Service Necessity."

## KFAB

770 kc, Lincoln, Neb., KFAB Broadcasting Co., 5,000 w, C, "Home Sweet Home."

## KFBB

1280 kc, Great Falls, Mont., Buttrey Broadcast, Inc., 1000 w, M.

## KFBK

1310 kc, Sacramento, Calif., James McClatchy Co., 100 w, P.

## KFBL

1370 kc, Everett, Wash., Leese Bros., 50 w, P, "The Voice of Puget Sound."

## KFDM

560 kc, Beaumont, Tex., Magnolia Petroleum Co., 500 w, C, "Kall for Dependable Magnolene."

## KFDY

550 kc, Brookings, S. D., State College, 500 w, C.

## KFEL

920 kc, Denver, Colo., Eugene P. O'Fallon, Inc., 500 w, M, "The Argonaut Station."

## KFEQ

680 kc, St. Joseph, Mo., Scroggin & Co., 2500 w, C.

## KFGQ

1310 kc, Boone, Iowa, Boone Biblical College, 100 w, C.

## KFH

1300 kc, Wichita, Kan., Radio Station KFH Co., 1000 w, C, "Kansas' Finest Hotel, in the Very Heart of God's Country."

## KFI

640 kc, Los Angeles, Calif., Earl C. Anthony, Inc., 5000 w, P, "National Institution."

## KFIO

1120 kc, Spokane, Wash., Spokane Broadcasting Corp., 100 w, P.

## KFIU

1310 kc, Juneau, Alaska, Alaska Elec. Light & Power Co., 10 w.

## KFIZ

1420 kc, Fond du Lac, Wis., Reporter Printing Co., 100 w, C.

## KFJB

1200 kc, Marshalltown, Iowa, Marshall Electric Co., 100 w, C, "Marshalltown, the Heart of Iowa."

## KFJF

1480 kc, Oklahoma City, Okla., National Radio Mfg. Co., 5000 w, C, "Radio Headquarters of Oklahoma."

## KFJI

1370 kc, Astoria, Ore., KFJI Broadcasters, Inc., 100 w, P.

## KFJM

1370 kc, Grand Forks, N. D., University of North Dakota, 100 w, C.

## KFJR

1300 kc, Portland, Ore., Ashley C. Dixon & Son, 500 w, P.

## KFJY

1310 kc, Ft. Dodge, Iowa, C. S. Tunwal, 100 w, C.

## KFJZ

1370 kc, Ft. Worth, Texas, Henry Clay Meacham, 100 w, C.

## KFKA

880 kc, Greeley, Colo., Mid-Western Radio Corp., 500 w, M. Shared.

## KFKB

1050 kc, Milford, Kan., KFKB Brdcstg. Assn., 5000 w, C, "The Sunshine Station in the Heart of the Nation."

## KFKU

1220 kc, Lawrence, Kan., University of Kansas, 500 w, C, "Up at Lawrence on the Kaw."

## KFKX

See under KYW.

## KFLV

1410 kc, Rockford, Ill., Rockford Broadcasters, Inc., 500 w, C.

## KFLX

1370 kc, Galveston, Texas, Geo. Roy Clough, 100 w, C.

## KFMX

1250 kc, Northfield, Minn., Carleton College, 1000 w, C.

## KFNF

890 kc, Shenandoah, Iowa, Henry Field Seed Co., 500 w, C, "Known for Neighborly Folks."

## KFOR

1210 kc, Lincoln, Neb., Howard A. Shuman, 100 w, C.

## KFOX

1250 kc, Long Beach, Calif., Nichols & Warriner, Inc., 1000 w, P, "Where Your Ship Comes In."

## KFPL

1310 kc, Dublin, Texas, C. C. Baxter, 100 w, C, "Baxter's Place."

## KFPM

1310 kc, Greenville, Texas, The New Furniture Co., 15 w, C, "Biggest Little Ten Watts on the Air."

## KFPW

1340 kc, Ft. Smith, Ark., John Brown Schools, 50 w, C.

## KFPY

1340 kc, Spokane, Wash., Symons Broadcasting Co., 1000 w, P.

## KFQD

1230 kc, Anchorage, Alaska, Anchorage Radio Club, 100 w.

## KFQU

1420 kc, Holy City, Calif., W. E. Riker, 100 w, P.

## KFQW

1420 kc, Seattle, Wash., KFQW, Inc., 100 w, P, "Gateway to Alaska and the Orient."

## KFRC

610 kc, San Francisco, Calif., Don Lee, Inc., 1000 w, P.

## KFRU

630 kc, Columbia, Mo., Stephens College, 500 w, C, "Where Friendliness Is Broadcast Daily."

## KFSD

600 kc, San Diego, Calif., Airfan Radio Corp., 500 w, P.

## KFSG

1120 kc, Los Angeles, Calif., Echo Park Evan. Assn., 500 w, P, "The Church of the Air."

## KFUL

1290 kc, Galveston, Texas, W. H. Ford, 500 w, C, "The City of Perpetual Sunshine."

## KFUM

1270 kc, Colorado Springs, Colo., W. D. Corley, 1000 w, M, "Known for Unsurpassed Mountain Scenery."

## KFUO

550 kc, St. Louis, Mo., Concordia Theological Seminary, 500 w, C, "The Gospel Voice."

## KFUP

1310 kc, Denver, Colo., Fitzsimmons General Hospital, 100 w, M.

## KFVD

1000 kc, Culver City, Calif., Los Angeles Broadcasting Co., 250 w, P.

## KFVS

1210 kc, Cape Girardeau, Mo., Hirsch Battery & Radio Co., 100 w, C, "The City of Opportunity."

## KFWB

950 kc, Hollywood, Calif., Warner Bros. Broadcasting Corp., 1000 w, P.

## KFWF

1200 kc, St. Louis, Mo., St. Louis Truth Center, Inc., 100 w.

## KFWI

930 kc, San Francisco, Calif., Radio Entertainments, Inc., 500 w, P.

## KFXD

1420 kc, Nampa, Idaho, Service Radio Co., 50 w, M.

## KFXF

920 kc, Denver, Colo., Colorado Radio Co., 500 w, M, "The Voice of Denver."

## KFXJ

1310 kc, Edgewater, Colo., Western Slope Broadcasting Co., 50 w, M, "America's Scenic Center."

## KFXM

1210 kc, San Bernardino, Calif., Lee Bros. Broadcasting Co., 100 w, P, "The Voice of the Orange Empire."

## KFXR

1310 kc, Oklahoma City, Okla., Exchange Avenue Baptist Church, 100 w, C.

## KFXY

1420 kc, Flagstaff, Ariz., Mary M. Costigan, 100 w, M.

## KFYO

1420 kl, Abilene, Texas, Kirksey Bros., 100 w, C, "Brecknridge, the Dynamo of West Texas."

**KFYR**

550 kc, Bismarck, N. D., Meyer Broadcasting Co., 1000 w, C.

**KGA**

1470 kc, Spokane, Wash., Northwest Broadcasting System, Inc., 5000 w, P.

**KGAR**

1370 kc, Tucson, Ariz., Tucson Motor Service Co., 100 w, M, "Way Out on the Desert."

**KGB**

1330 kc, San Diego, Calif., Pickwick Broadcasting Corp., 250 w, P, "Music for the Sick."

**KGBU**

900 kc, Ketchikan, Alaska, Alaska Radio & Service Co., 500 w.

**KGBX**

1310 kc, St. Joseph, Mo., KGBX, Inc., 100 w.

**KGBZ**

930 kc, York, Nebr., Geo. R. Miller, 500 w, C, "The Swine and Poultry Station."

**KGCA**

1270 kc, Decorah, Iowa, Chas. W. Greenley, 50 w, C.

**KGCR**

1210 kc, Watertown, S. D., Cutler's Radio Broadcasting Service, Inc., 100 w.

**KGCU**

1200 kc, Mandan, N. D., Mandan Radio Association, 100 w, M, "The Voice of the West."

**KGCC**

1310 kc, Wolf Point, Mont., First State Bank of Vida, 100 w, M.

**KGDA**

1370 kc, Mitchell, S. D., Mitchell Broadcasting Corp., 100 w, M.

**KGDE**

1200 kc, Fergus Falls, Minn., Jaren Drug Co., 100 w, C.

**KGDM**

1100 kc, Stockton, Calif., E. F. Pepper, 250 w.

**KGDY**

1200 kc, Huron, S. D., Loesch & Wright, 15 w, C.

**KGEF**

1300 kc, Los Angeles, Calif., Trinity Methodist Church, 1000 w, P.

**KGEK**

1200 kc, Yuma, Colo., Beehler Elec. Equip. Co., 50 w, M, Shared.

**KGER**

1360 kc, Long Beach, Calif., C. Merwin Dobyns, 1000 w, P, "The Service Club of the Air."

**KGEW**

1200 kc, Ft. Morgan, Colo., City of Ft. Morgan, 100 w, P.

**KGEZ**

1310 kc, Kalispell, Mont., Chamber of Commerce, 100 w, M, "Located in the Switzerland of America—The Beautiful Flathead Valley."

**KGFF**

1420 kc, Alva, Okla., D. R. Wallace, 100 w, C.

**KGFG**

1370 kc, Oklahoma City, Okla., Oklahoma Broadcasting Co. Inc., 100 w, C, "The Whole Gospel to the Whole World."

**KGFI**

1500 kc, Corpus Christi, Texas, Eagle Broadcasting Co., 100 w, C, "The Voice of West Texas."

**KGFI**

1200 kc, Los Angeles, Calif., Ben S. McGlashan, 100 w, P, "Keeps Good Folks Joyful"

**KGFK**

1500 kc, Moorhead, Minn., Red River Broadcasting Co. Inc., 50 w, C.

**KGFL**

1370 kc, Raton, N. Mex., W. E. Whitmore, 50 w, M.

**KGFW**

1310 kc, Ravenna, Neb., Sothman & McConnell, 50 w.

**KGFX**

580 kc, Pierre, S. D., Dana McNeil, 200 w, C.

**KGGC**

1420 kc, San Francisco, Calif., Golden Gate Broadcasting Co., 100 w, P.

**KGGF**

1010 kc, South Coffeyville, Okla., Powell & Platz, 500 w.

**KGGM**

1230 kc, Albuquerque, N. Mex., New Mexico Broadcasting Co., 250 w.

**KGHF**

1320 kc, Pueblo, Colo., Ritchie & Finch, 250 w, M.

**KGHI**

1200 kc, Little Rock, Ark., Berean Bible Class, 100 w.

**KGHL**

950 kc, Billings, Mont., Northwestern Auto Supply Co., 1000 w, M.

**KGIQ**

1320 kc, Twin Falls, Idaho, Radio Broadcasting Corp., 250 w, M.

**KGIR**

1360 kc, Butte, Mont., KGIR, Inc., 500 w, M.

**KGIW**

1420 kc, Trinidad, Colo., Leonard E. Wilson, 100 w, M.

**KGIX**

1420 kc, Las Vegas, Nev., J. M. Heaton, 100 w.

**KGIZ**

1500 kc, Grant City, Mo., Grant City Park Corp., 50 w, C.

**KGJF**

890 kc, Little Rock, Ark., First Church of the Nazarene, 250 w.

**KGKB**

1500 kc, Brownwood, Tex., Eagle Publ. Co., 100 w, C.

**KGKL**

1370 kc, San Angelo, Tex., KGKL, Inc., 100 w, C.

**KGKO**

570 kc, Wichita Falls, Tex., Wichita Falls Broadcasting Co., 250 w, C.

**KGKX**

1420 kc, Sandpoint, Idaho, C. E. Twiss and F. H. McCann, 100 w, P.

**KGKY**

1500 kc, Scottsbluff, Nebr., Hilliard Co., Inc., 100 w, C.

**KGMB**

1320 kc, Honolulu, Hawaii, Honolulu Broadcasting Co., 500 w, P.

**KGMP**

1210 kc, Elk City, Okla., Bryant Radio & Elec. Co., 100 w, C.

**KGNF**

1430 kc, North Platte, Nebr., H. L. Spencer, 500 w, M.

**KGNO**

1210 kc, Dodge City, Kans., Dodge City Broadcasting Co. Inc., M.

**KGO**

790 kc, San Francisco, Calif., National Broadcasting Co. Inc., 7500 w, P.

**KGRS**

1410 kc, Amarillo, Texas, Gish Radio Service, 1000 w, C, Shared.

**KGU**

940 kc, Honolulu, Hawaii, Marion Mulrony, Advertising Publ. Co., 1000 w, "In the Land of Sunshine, the Future Playground of America."

**KGW**

620 kc, Portland, Ore., Oregonian Pub. Co., 1000 w, P, "Keep Growing Wiser."

**KGW**

1200 kc, Lacey, Wash., St. Martins College, 10 w, P, "Out Where the Cedars Meet the Sea."

**KHJ**

900 kc, Los Angeles, Calif., Don Lee, Inc., 1000 w, P, "Kindness, Happiness, Joy."

**KHQ**

590 kc, Spokane, Wash., Louis Wasmer, Inc., 1000 w, P, "In the Friendly City."

**KICK**

1420 kc, Red Oak, Iowa, Red Oak Radio Corp., 100 w.

**KID**

1320 kc, Idaho Falls, Ida., KID Broadcasting Co., 250 w, M.

**KIDO**

1250 kc, Boise, Idaho, Boise Broadcasting Station, 1000 w, P.

**KIT**

1310 kc, Yakima, Wash., C. E. Haymond, 50 w, P.

**KJBS**

1070 kc, San Francisco, Calif., Julius Brunton & Sons Co., 100 w, P, "The Voice of the Storage Battery."

**KJR**

970 kc, Seattle, Wash., Northwest Broadcasting System, Inc., 5000 w, P.

**KLCN**

1290 kc, Blytheville, Ark., C. L. Lintzenich, 50 w, C.

**KLO**

1400 kc, Ogden, Utah, Peery Building Co., 500 w, M.

**KLPM**

1420 kc, Minot, N. D., John B. Cooley, 100 w, C.

**KLRA**

1390 kc, Little Rock, Ark., Arkansas Broadcasting Co., 1000 w.

**KLS**

1440 kc, Oakland, Calif., Warner Bros., 250 w, P, "The City of Golden Opportunity."

**KLX**

880 kc, Oakland, Calif., Tribune Pub. Co., 500 w, P, "Where Rail and Water Meet."

**KLZ**

560 kc, Denver, Colo., Reynolds Radio Co., Inc., 1000 w, M, "The Pioneer Station of the West."

**KMA**

930 kc, Shenandoah, Iowa, May Seed & Nursery Co., 500 w, C, "Keeps Millions Advised."

**KMAC**

1370 kc, San Antonio, Texas, W. W. McAllister, 100 w, C, "Radio Sam at San Antonio."

**KMBC**

950 kc, Kansas City, Mo., Midland Broadcasting Co., 1000 w, C, "Kansas City's Most Powerful Public Service Broadcasting Station."

**KMCS**

1120 kc, Inglewood, Calif., Dalton's, Inc., 500 w, P.

**KMED**

1310 kc, Medford, Ore., Mrs. W. J. Virgin, 50 w, P, "See Crater Lake."

**KMJ**

1210 kc, Fresno, Calif., J. McClatchy Co., 100 w, P.

**KMLB**

1200 kc, Monroe, La., J. C. Liner, 50 w, C.

**KMMJ**

740 kc, Clay Center, Neb., The M. M. Johnson Co., 1000 w, C, The Old Trusty Station."

**KMO**

860 kc, Tacoma, Wash., KMO, Inc., 500 w, P.

**KMOX**

1090 kc, St. Louis, Mo., Voice of St. Louis, Inc., 50,000 w, C.

**KMPC**

710 kc, Beverly Hills, Calif., R. S. Macmillan, 500 w, P.

**KMTR**

570 kc, Los Angeles, Calif., KMTR Radio Corp., 500 w, P, "Your Friend in Hollywood."

**KNX**

1050 kc, Hollywood, Calif., Western Broadcast Co., 5000 w, P, "The Voice of Hollywood."



**KOA**

830kc, Denver, Colo., National Broadcasting Co. Inc., 12,500 w, M.

**KOAC**

550 kc, Corvallis, Ore., Oregon State Agricultural College, 1000 w, P, "Science for Service."

**KOB**

1180 kc, State College, N. M., N. M. College of Agri. & Mech. Arts, 20,000 w, M, "The Sunshine State of America."

**KOCW**

1400 kc, Chickasha, Okla., Oklahoma College for Women, 250 w, C.

**KOH**

1380 kc, Reno, Nevada, Jay Peters, Inc., 500 w.

**KOIL**

1260 kc, Council Bluffs, Iowa, Mona Motor Oil Co., 1000 w, C, "The Hilltop Studio."

**KOIN**

940 kc, Portland, Ore., KOIN, Inc., 1000 w, P, "The Station of the Hour."

**KOL**

1270 kc, Seattle, Wash., Seattle Broadcasting Co., 1000 w, P.

**KOMO**

920 kc, Seattle, Wash., Fisher's Blend Station, Inc., 1000 w, P.

**KONO**

1370 kc, San Antonio, Tex., Mission Broadcasting Co., 100 w, C.

**KOOS**

1370 kc, Marshfield, Ore., H. H. Hanseth, Inc., 100 w, P.

**KORE**

1420 kc, Eugene, Ore., Eugene Broadcast Station, 100 w, P.

**KOY**

1390 kc, Phoenix, Ariz., Nielsen Radio & Sporting Goods Co., 500 w, M, "Kind Friends Come Back."

**KPCB**

650 kc, Seattle, Wash., Westcoast Broadcasting Co., 100 w, P. Shared.

**KPJM**

1500 kc, Prescott, Ariz., Miller & Klahn, 100 w, M.

**KPO**

680 kc, San Francisco, Calif., Hale Bros. & The Chronicle, 5000 w, P, "The City of the Golden Gate."

**KPOF**

880 kc, Denver, Colo., Pillar of Fire, Inc., 500 w, M.

**KPPC**

1210 kc, Pasadena, Calif., Pasadena Presbyterian Church, 50 w, P.

**KPQ**

1500 kc, Wenatchee, Wash., Westcoast Broadcasting Co., 50 w, P.

**KPRC**

920 kc, Houston, Texas, Houston Printing Co., 1000 w, C, "Kotton Port Rail Center."

**KPSN**

1360 kc, Pasadena, Calif., Pasadena Star-News, 1000 w, P.

**KQV**

1380 kc, Pittsburgh, Pa., Doubleday-Hill Elec. Co., 500 w, E, "The Smoky City Station."

**KQW**

1010 kc, San Jose, Calif., Pacific Agric. Foundation, 500 w, P, "For God and Country."

**KRE**

1370 kc, Berkeley, Calif., First Congregational Church, 100 w, P.

**KREG**

1500 kc, Santa Ana, Calif., Pacific-Western Broadcasting Federation, 100 w, P.

**KRGV**

1260 kc, Harlingen, Texas, KRGV, Inc., 500 w.

**KRLD**

1040 kc, Dallas, Texas, KRLD, Inc., 10,000 w, C, "Down Where the Blue Bonnets Grow."

**KRMD**

1310 kc, Shreveport, La., Robert M. Dean, 50 w, C.

**KROW**

930 kc, Oakland, Calif., Educational Broadcasting Corp., 500 w, M.

**KRSC**

1120 kc, Seattle, Wash., Radio Sales Corp., 50 w, P.

**KSAC**

580 kc, Manhattan, Kan., Kansas State Agricultural College, 500 w, C.

**KSCJ**

1330 kc, Sioux City, Iowa, Perkins Bros. Co., 1000 w, C.

**KSD**

550 kc, St. Louis, Mo., Pulitzer Pub. Co., 500 w, C.

**KSEI**

900 kc, Pocatello, Idaho, KSEI Broadcasting Assn., 250 w, M, "Kummunity Southeast Idaho."

**KSL**

1130 kc, Salt Lake City, Utah, Radio Service Corp., 5000 w, M, "The Voice of the Intermountain Empire."

**KSMR**

1200 kc, Santa Maria, Calif., Santa Maria Radio Co., 100 w, P, "The Valley of Gardens."

**KSO**

1380 kc, Clarinda, Iowa, Berry Seed Co., 500 w, C, "Keep Serving Others."

**KSOO**

1110 kc, Sioux Falls, S. D., Sioux Falls Broadcasting Assn., 2000 w, C.

**KSTP**

1460 kc, St. Paul, Minn., National Battery Broadcasting Co., 10,000 w, C.

**KTAB**

560 kc, San Francisco, Calif., Associated Broadcasters, 1000 w, P, "Knowledge, Truth and Beauty."

**KTAP**

1420 kc, San Antonio, Texas, Alamo Broadcasting Co., 100 w, C, "The World's Biggest Little Station."

**KTAR**

620 kc, Phoenix, Ariz., KTAR Broadcasting Co., 500 w, M, "Phoenix, Where Winter Never Comes."

**KTAT**

1240 kc, Ft. Worth, Tex., S. A. T. Broadcasting Co., 1000 w, C.

**KTBI**

1300 kc, Los Angeles, Calif., Bible Institute of Los Angeles, 1000 w, P.

**KTBR**

1300 kc, Portland, Ore., M. E. Brown, 500 w, P.

**KTBS**

1450 kc, Shreveport, La., Tri-State Broadcasting Co., 1000 w, E.

**KTHS**

1040 kc, Hot Springs, Ark., Chamber of Commerce, 10,000 w, C, "Kum to Hot Springs."

**KTLC**

1310 kc, Houston, Tex., Houston Broadcasting Co., 100 w, C.

**KTM**

780 kc, Los Angeles, Calif., Pickwick Broadcasting Corp., 500 w, P, "The Station with a Smile."

**KTNT**

1170 kc, Muscatine, Iowa, Norman Baker, 5000 w, C, "The Voice of the Iowa Farmers' Union."

**KTRH**

1120 kc, Houston, Tex., Rice Hotel, 500 w, C.

**KTSA**

1290 kc, San Antonio, Texas, Lone Star Broadcasting Co., 1000 w, C.

**KTSL**

1310 kc, Shreveport, La., Houseman Sheet Metal Works, Inc., 100 w, C.

**KTSM**

1310 kc, El Paso, Tex., W. S. Bledsoe and W. T. Blackwell, 100 w, C.

**KTW**

1270 kc, Seattle, Wash., First Presbyterian Church, 1000 w, P.

**KUJ**

1500 kc, Longview, Wash., Paul R. Heitmeyer, Inc., 100 w, P.

**KUOA**

1390 kc, Fayetteville, Ark., University of Arkansas, 1000 w, C.

**KUSD**

890 kc, Vermilion, S. Dak., University of South Dakota, 500 w, C.

**KUT**

1500 kc, Austin, Tex., Rice Hotel, 100 w, C.

**KVI**

760 kc, Tacoma, Wash., Puget Sound Radio Broadcasting Co., 1000 w, P, "Puget Sound Station."

**KVL**

1370 kc, Seattle, Wash., KVL, Inc., 100 w, P.

**KVOA**

1260 kc, Tucson, Ariz., R. M. Riculfi, 500 w.

**KVOO**

1140 kc, Tulsa, Okla., Southwestern Sales Corp., 5000 w, C, "The Voice of Oklahoma."

**KVOS**

1200 kc, Bellingham, Wash., KVOS, Inc., 100 w, M.

**KWCR**

1310 kc, Cedar Rapids, Iowa, Harry F. Paar, 100 w, C.

**KWEA**

1210 kc, Shreveport, La., Hello World Broadcasting Corp., 100 w, C.

**KWG**

1200 kc, Stockton, Calif., Portable Wireless Tel. Co., 100 w, P.

**KWJJ**

1060 kc, Portland, Ore., KWJJ Broadcasting Co., Inc., 500 w, P, "The Voice from Broadway."

**KWK**

1350 kc, St. Louis, Mo., Greater St. Louis Broadcasting Corp., 1000 w, C.

**KWKC**

1370 kc, Kansas City, Mo., Wilson Duncan Broadcasting Co., 100 w.

**KWKH**

850 kc, Shreveport, La., Hello World Broadcasting Corp., 10,000 w, C.

**KWLC**

1270 kc, Decorah, Iowa, Luther College, 100 w, C.

**KWSC**

1220 kc, Pullman, Wash., State College of Washington, 1000 w, P, "The Voice of the Cougars."

**KWWG**

1260 kc, Brownsville, Texas, Brownsville Herald Publishing Co., 500 w, C, "Good Night, World."

**KXA**

570 kc, Seattle, Wash., American Radio Tel. Co., 500 w, P.

**KXL**

1420 kc, Portland, Ore., KXL Broadcasters, Inc., 100 w, P, "The Voice of Portland."

**KXO**

1500 kc, El Centro, Calif., Irey & Bowles, 100 w, P.

**KXRO**

1310 kc, Aberdeen, Wash., KXRO, Inc., 75 w, P.

**KXYZ**

1420 kc, Houston, Texas, Harris County Broadcasting Co., 100 w, C.

**KYA**

1230 kc, San Francisco, Calif., Pacific Broadcasting Corp., 1000 w, P.

**KYW**

1020 kc, Chicago, Ill., Westinghouse E. & M. Co., 10,000 w, C.

**KZM**

1370 kc, Hayward, Calif., Leon P. Tenney, 100 w, P.

**NAA**

690 kc, 434.5 m. United States Navy Department, Washington, D. C., 1000 w, "Where the Time Signals Originate," E.

**WAAF**

920 kc, Chicago, Ill., Drivers Journal Pub. Co., 500 w daytime, C.

**WAAM**

1250 kc, Newark, N. J., WAAM, Inc., 1000 w, E, "Sunshine Station."

**WAAT**

940 kc, Jersey City, N. J., Bremer Broadcasting Corp., 300 w, E.

**WAAW**

660 kc, Omaha, Neb., Omaha Grain Exchange, 500 w daytime, C, "Pioneer Market Station of the West."

**WABC**

860 kc, New York City, N. Y., Atlantic Broadcasting Corp., 5000 w, E.

**WABI**

1200 kc, Bangor, Maine, Pine Tree Broadcasting Co., 100 w, E, "The Pine Tree Wave."

**WABO**

See under WHEC.

**WABZ**

1200 kc, New Orleans, La., Coliseum Place Baptist Church, 100 w, C.

**WACO**

1240 kc, Waco, Tex., Central Texas Broadcasting Co., Inc., 1000 w, C.

**WADC**

1320 kc, Tallmadge, Ohio, Allen T. Simmons, 1000 w, E, "Watch Akron Develop Commercially."

**WAIU**

640 kc, Columbus, Ohio, American Insurance Union, 500 w, E, "The Radio Voice of the American Insurance Union."

**WALR**

1210 kc, Zanesville, O., Roy W. Waller, 100 w, E.

**WAPI**

1140 kc, Birmingham, Ala., Alabama Polytechnic Institute, 5000 w, C.

**WASH**

1270 kc, Grand Rapids, Mich., WASH Broadcasting Corp., 500 w, C.

**WAWZ**

1350 kc, New York, N. Y., Pillar of Fire, 250 w, E, "The Voice of the Heart of New York."

**WBAA**

1400 kc, Lafayette, Ind., Purdue University, 500 w, C.

**WBAK**

1430 kc, Harrisburg, Pa., Pennsylvania State Police, 500 w, E, "The Voice of Pennsylvania."

**WBAL**

1060 kc, Baltimore, Md., Consolidated Gas, Elec. Co., 10,000 w, E, "The Station of Good Music."

**WBAP**

800 kc, Ft. Worth, Tex., Carter Publications, Inc., 10,000 w, C.

**WBAX**

1210 kc, Wilkes-Barre, Pa., John H. Stenger, Jr., 100 w, E, "In Wyoming Valley, Home of the Anthracite."

**WBBC**

1400 kc, Brooklyn, N. Y., Brooklyn Broadcasting Corp., 500 w.

**WBBL**

1210 kc, Richmond, Va., Grace Covenant Presbyterian Church, 100 w, E, "Richmond, the Gateway North and South."

**WBBM**

770 kc, Chicago, Ill., Atliss Co., Inc., 25,000 w, C.

**WBBR**

1300 kc, Brooklyn, N. Y., People's Pulpit Association, 1000 w, E, "Watch Tower."

**WBBZ**

1200 kc, Ponca City, Okla., C. L. Carrell, 100 w, C.

**WBCM**

1410 kc, Bay City, Mich., James E. Davidson, 500 w, E, "Where the Summer Trail Begins."

**WBCN**

See under WENR.

**WBEN**

900 kc, Buffalo, N. Y., Buffalo Evening News, 1000 w, E.

**WBGF**

1370 kc, Glens Falls, N. Y., W. Parker & N. Metcalf, 50 w, E.

**WBIG**

1440 kc, Greensboro, N. C., North Carolina Broadcasting Co., 500 w, E.

**WBIS**

See under WNAC.

**WBMS**

1450 kc, Hackensack, N. J., WBMS Broadcasting Corp., 250 w.

**WBOQ**

See under WABC.

**WBOW**

1310 kc, Terre Haute, Ind., Banks of Wabash Broadcasting Assn., 100 w, C, "On the Banks of the Wabash."

**WBRC**

930 kc, Birmingham, Ala., Birmingham Broadcasting Co., 500 w, C, "The Biggest Little Station in the World."

**WBRE**

1310 kc, Wilkes-Barre, Pa., Louis G. Baltimore, 500 w, E.

**WBSO**

920 kc, Needham, Mass., Babson's Statistical Org., Inc., 250 w, E.

**WBT**

1080 kc, Charlotte, N. C., Station WBT, Inc., 5000 w, E, shared, "The Queen City of the South."

**WBTM**

1370 kc, Danville, Va., Clarke Elec. Co., 100 w, E.

**WBZ**

990 kc, Springfield, Mass., Westinghouse E. & M. Co., 15,000 w, E, "The Broadcasting Station of New England."

**WBZA**

990 kc, Boston, Mass., Westinghouse E. & M. Co., 500 w, E.

**WCAC**

600 kc, Storrs, Conn., Connecticut Agricultural College, 250 w, E, "Voice from the Nutmeg State."

**WCAD**

1220 kc, Canton, N. Y., St. Lawrence University, 500 w, E, "The Voice of the North Country."

**WCAE**

1220 kc, Pittsburgh, Pa., Kaufman & Baer Co., 1000 w, E, "Where Prosperity Begins."

**WCAH**

1430 kc, Columbus, Ohio, Commercial-Radio Service Co., 500 w, E.

**WCAJ**

590 kc, Lincoln, Neb., Nebraska Wesleyan University, 500 w, C.

**WCAL**

1250 kc, Northfield, Minn., St. Olaf College, 1000 w, C, "The College on the Hill."

**WCAM**

1280 kc, Camden, N. J., City of Camden, 500 w, E.

**WCAO**

600 kc, Baltimore, Md., Monumental Radio, Inc., 250 w, E, "The Gateway of the South."

**WCAP**

1280 kc, Asbury Park, N. J., Radio Industries Broadcast Co., 500 w, E.

**WCAT**

1200 kc, Rapid City, S. D., South Dakota State School of Mines, 100 w, M.

**WCAU**

1170 kc, Philadelphia, Pa., Universal Broadcasting Co., 10,000 w, E, "Where Cheer Awaits U."

**WCAX**

1200 kc, Burlington, Vt., University of Vermont, 100 w, E.

**WCAZ**

1070 kc, Carthage, Ill., Superior Broadcasting Co., 50 w.

**WCBA**

1440 kc, Allentown, Pa., B. B. Musselman, 250 w, E.

**WCBD**

1080 kc, Zion, Ill., Wilbur Glen Voliva, 5000 w, C.

**WCBM**

1370 kc, Baltimore, Md., Baltimore Broadcasting Corp., 100 w, E.

**WCBS**

1210 kc, Springfield, Ill., Dewing & Meester, 100 w, C.

**WCCO**

810 kc, Minneapolis, Minn., Northwestern Broadcasting Inc., 7500 w, C, "Service to the Northwest."

**WCDA**

1350 kc, New York, N. Y., Italian Educational Broadcasting Co., 250 w, E.

**WCFL**

970 kc, Chicago, Ill., Chicago Federation of Labor, 1500 w, C, "The Voice of Labor."

**WCGU**

1400 kc, Brooklyn, N. Y., U. S. Broadcasting Corp., 500 w, E.

**WCHI**

1490 kc, Chicago, Ill., People's Pulpit Association, 500 w, C, "The Watch Tower—Radio WORD."

**WCKY**

1490 kc, Covington, Ky., L. B. Wilson, 500 w, E.

**WCLB**

1500 kc, Long Beach, N. Y., Arthur Faske, 100 w, E.

**WCLO**

1200 kc, Janesville, Wis., WCLO Radio Corp., 100 w, C.

**WCLS**

1310 kc, Joliet, Ill., WCLS, Inc., 100 w, C.

**WCMA**

1400 kc, Culver, Ind., General Broadcasting Co., 500 w, C, "The Voice of Culver."

**WCOA**

1340 kc, Pensacola, Fla., City of Pensacola, 500 w, E, "Wonderful City of Advantages."

**WCOC**

880 kc, Meridian, Miss., Mississippi Broadcasting Co., 500 w, C.

**WCOD**

1200 kc, Harrisburg, Pa., N. R. Hoffman Co., 100 w, E.

**WCOH**

1210 kc, Yonkers, N. Y., Westchester Broadcasting Corp., 100 w, E.

**WCRW**

1210 kc, Chicago, Ill., Clinton R. White, 100 w, C.

**WCSC**

1360 kc, Charleston, S. C., Jordan & Burk, 500 w, E.

**WCSH**

940 kc, Portland, Me., Congress Square Hotel Co., 1000 kc, E, "The Voice From Sunrise Land."

**WDAE**

1220 kc, Tampa, Fla., Tampa Publishing Co., 1000 w, E, "WDAE, the Voice of the Times at Tampa."

**WDAF**

610 kc, Kansas City, Mo., Kansas City Star Co., 1000 w, C, "Enemies of Sleep."

**WDAG**

1410 kc, Amarillo, Texas, National Radio & Broadcasting Corp., 250 w, C, "Where Dollars Always Grow."

**WDAH**

1310 kc, El Paso, Texas, Eagle Broadcasting Co., 100 w, M.

**WDAY**

940 kc, Fargo, N. D., WDAY, Inc., 1000 w, C.

**WDBJ**

930 kc, Roanoke, Va., Richardson-Wayland Elec. Corp., 250 w, E, "The Magic City."

**WDBO**

1120 kc, Orlando, Fla., Orlando Broadcasting Co., 1000 w, E, "Down Where the Oranges Grow."

**WDEL**

1120 kc, Wilmington, Del., WDEL, Inc., 250 w, E, "First City of the First State."

**WDGY**

1180 kc, Minneapolis, Minn., Dr. Geo. W. Young, 1000 w, C.

**WDIX**

1500 kc, Tupelo, Miss., Blair & Anderson, 100 w, C.

**WDOD**

1280 kc, Chattanooga, Tenn., WDOD Broadcasting Co., Inc., 1000 w, C.

**WDRC**

1330 kc, New Haven, Conn., Doolittle Radio Corp., 500 w, E.

**WDSU**

1250 kc, New Orleans, La., Jos. H. Uhalt, 1000 w, C.

**WDWF**

1210 kc, Providence, R. I., Dutée W. Flint and The Lincoln Studios, 100 w, E.

**WDZ**

1070 kc, Tuseola, Ill., James L. Bush, 100 w.

**WEAF**

660 kc, New York, N. Y., National Broadcasting Co., Inc., 50,000 w, E.

**WEAI**

1270 kc, Ithaca, N. Y., Cornell Univ., 1000 w, E.

**WEAN**

780 kc, Providence, R. I., Shepard Broadcasting Service, 250 w, E, "We Entertain a Nation."

**WEAO**

570 kc, Columbus, Ohio, Ohio State University, 750 w, E.

**WEBC**

1290 kc, Superior, Wis., Head of The Lakes Broadcasting Co., 1000 w, C.

**WEBQ**

1210 kc, Harrisburg, Ill., First Trust & Savings Bank, 100 w, C.

**WEBR**

1310 kc, Buffalo, N. Y., Howell Broadcasting Co., 100 w, E, "We Extend Buffalo's Regards."

**WEDC**

1210 kc, Chicago, Ill., Emil Denmark, Inc., 100 w.

**WEDH**

1420 kc, Erie, Pa., Erie Dispatch-Herald, 30 w, E.

**WEEI**

590 kc, Boston, Mass., Edison Elec. Illum. Co., 1000 w, E, "The Friendly Voice."

**WEHC**

1200 kc, Emory, Va., Emory and Henry College, 100 w, E.

**WEHS**

1420 kc, Evanston, Ill., WEHS, Inc., 100 w, C.

**WELK**

1370 kc, Philadelphia, Pa., WELK Broadcasting Station, Inc., 100 w, E.

**WELL**

1420 kc, Battle Creek, Mich., Enquirer-News Co., 50 w, E.

**WENR**

870 kc, Chicago, Ill., Great Lakes Radio Broadcasting Co., 50,000 w, C, "Voice of Service."

**WEPS**

See under WORC.

**WEVD**

1300 kc, New York, N. Y., Debs Memorial Radio Fund, 500 w, E.

**WEW**

760 kc, St. Louis, Mo., St. Louis University, 1000 w, C.

**WEXL**

1310 kc, Royal Oak, Mich., Royal Oak Broadcasting Co., 50 w, E.

**WFAA**

800 kc, Dallas, Texas, Dallas News and Journal, 50,000 w, C, "Working for All Alike."

**WFAN**

610 kc, Philadelphia, Pa., Keystone Broadcasting Co., Inc., 500 w, E.

**WFBC**

1200 kc, Knoxville, Tenn., First Baptist Church, 50 w, E.

**WFBE**

1200 kc, Cincinnati, Ohio, WFBE, Inc., 100 w, E.

**WFBG**

1310 kc, Altoona, Pa., William F. Gable Co., 100 w, E, "The Original Gateway to the West and We Wish You All the Very Best."

**WFBM**

1360 kc, Syracuse, N. Y., The Onondaga Co., Inc., 1000 w, E, "When Feeling Blue, Listen."

**WFBP**

1230 kc, Indianapolis, Ind., Indianapolis Power & Light Co., 1000 w, C.

**WFBT**

1270 kc, Baltimore, Md., Baltimore Radio Show, Inc., 250 w, E, "Home of the Star Spangled Banner."

**WFDL**

1310 kc, Flint, Mich., Frank D. Fallain, 100 w, E.

**WFDV**

1370 kc, Rome, Ga., Dolies Goings, 100 w, E.

**WFDW**

1420 kc, Talladega, Ala., R. C. Hammett, 100 w, C.

**WFI**

560 kc, Philadelphia, Pa., Strawbridge & Clothier, 500 w, E, "Key City of Industry."

**WFIW**

940 kc, Hopkinsville, Ky., WFIW, Inc., 1000 w, C.

**WFJC**

1450 kc, Akron, Ohio, WGAR Broadcasting Co., 500 w, E.

**WFLA**

620 kc, Clearwater, Fla., Clearwater Chamber of Commerce and St. Petersburg Chamber of Commerce, 1000 w, E, "Inviting the World to the Springtime City."

**WGAL**

1310 kc, Lancaster, Pa., WGAL, Inc., 100 w, E, "World's Gardens at Lancaster."

**WGBB**

1210 kc, Freeport, N. Y., Harry H. Carman, 100 w, E, "The Voice of the Sunrise Trail."

**WGBC**

1430 kc, Memphis, Tenn., Memphis Broadcasting Co., 500 w, C. Shared.

**WGBF**

630 kc, Evansville, Ind., Evansville on the Air, Inc., 500 w, E, "Gateway to the South."

**WGBI**

880 kc, Scranton, Pa., Scranton Broadcasters, Inc., 250 w, E.

**WGBS**

600 kc, New York, N. Y., General Broadcasting System, Inc., 500 w, E.

**WGCM**

1210 kc, Gulfport, Miss., Great Southern Land Co., Inc., 100 w, C.

**WGCP**

1250 kc, Newark, N. J., May Radio Broadcast Corp., 250 w.

**WGES**

1360 kc, Chicago, Ill., Oak Leaves Broadcasting Corp., 500 w, C, "World's Greatest Entertainment Service."

**WGH**

1310 kc, Newport News, Va., Hampton Roads Broadcasting Corp., Inc., 100 w, E.

**WGL**

1370 kc, Ft. Wayne, Ind., Allen-Wayne Co., 100 w, C.

**WGMS**

See under WLB.

**WGN**

720 kc, Chicago, Ill., Tribune Co., 25,000 w, C.

**WGR**

550 kc, Buffalo, N. Y., Buffalo Broadcasting Corp., 1000 w, E.

**WGST**

890 kc, Atlanta, Ga., Georgia School of Technology, 250 w, E, "The Southern School with the National Reputation."

**WGY**

790 kc, Schenectady, N. Y., General Electric Co., 50,000 w.

**WHA**

940 kc, Madison, Wis., University of Wisconsin, 750 w, C.

**WHAD**

1120 kc, Milwaukee, Wis., Marquette University, 250 w, C.

**WHAM**

1150 kc, Rochester, N. Y., Stromberg-Carlson Tel. Mfg. Co., 5000 w, E.

**WHAP**

1300 kc, New York, N. Y., Defenders of Truth Society, Inc., 1000 w, E.

**WHAS**

820 kc, Louisville, Ky., The Courier Journal Co. & Louisville Times Co., 11,000 w, C.

**WHAT**

1310 kc, Philadelphia, Pa., Independence Broadcasting Co., 100 w, E.

**WHAZ**

1300 kc, Troy, N. Y., Rensselaer Polytechnic Institute, 500 w, E.

**WHB**

860 kc, Kansas City, Mo., WHB Broadcasting Co., 500 w, C.

**WHBC**

1200 kc, Canton, Ohio, St. John's Catholic Church, 10 w, E.

**WHBD**

1370 kc, Mt. Orab, Ohio, F. P. Moler, 100 w, E, "Ohio's Highest Point."

**WHBF**

1210 kc, Rock Island, Ill., Beardsley Specialty Co., 100 w, C.

**WHBL**

1410 kc, Sheboygan, Wis., Press Pub. Co., 500 w, C.

**WHBQ**

1370 kc, Memphis, Tenn., Station WHBQ, Inc., 100 w, C.

**WHBU**

1210 kc, Anderson, Ind., Citizens Bank, 100 w, C, "First Hoosier Bank on the Air."

**WHBY**

1200 kc, Green Bay, Wis., St. Norbert's College, 100 w, C.

**WHDF**

1370 kc, Calumet, Mich., Upper Michigan Brdcstg. Co., 100 w, C.

**WHDH**

830 kc, Boston, Mass., Matheson Radio Co., Inc., 1000 w, E.

**WHDI**

1180 kc, Minneapolis, Minn., Wm. Hood Dunwoody Ind. Inst., 500 w, C.

**WHDL**

1420 kc, Tupper Lake, N. Y., Tupper Lake Broadcasting Corp., 10 w, E.

**WHEC**

1440 kc, Rochester, N. Y., Hickson Electric Co., Inc., 500 w, E.

**WHFC**

1420 kc, Cicero, Ill., Triangle Broadcasters, 100 w, C.

**WHIS**

1420 kc, Bluefield, W. Va., Daily Telegraph Printing Co., 100 w, E.

**WHK**

1390 kc, Cleveland, Ohio, Radio Air Service Corp., 1000 w, E, "Cleveland's Pioneer Station."

**WHN**

1010 kc, New York, N. Y., Marcus Loew Booking Review, 250 w, E, "Voice of the Great White Way."

**WHO**

1000 kc, Des Moines, Iowa, Central Broadcasting Co., 5000 w, C.

**WHOM**

1450 kc, Jersey City, N. J., New Jersey Broadcasting Corp., 250 w, E.

**WHP**

1430 kc, Harrisburg, Pa., Pennsylvania Broadcasting Co., 500 w, E.

**WIAS**

1420 kc, Ottumwa, Iowa, Poling Electric Co., 100 w, C.

**WIBA**

1280 kc, Madison, Wis., Capital Times Co., 500 w, C.

**WIBG**

930 kc, Elkins Park, Pa., St. Paul's Church, 50 w, E.

**WIBM**

1370 kc, Jackson, Mich., WIBM, Inc., 100 w.

**WIBO**

560 kc, Chicago, Ill., Nelson Bros. Bond & Mortgage Co., 1000 w, C.

**WIBR**

1420 kc, Steubenville, Ohio, G. W. Robinson, 50 w, E, "Where Investments Bring Results."

**WIBU**

1210 kc, Poynette, Wis., W. C. Forrest, 100 w, C.

**WIBW**

580 kc, Topeka, Kan., Topeka Broadcasting Assn., Inc., 1000 w, C, "Topeka—Where Investment Brings Wealth."

**WIBX**

1200 kc, Utica, N. Y., WIBX, Inc., 100 w, E.

**WICC**

1190 kc, Bridgeport, Conn., Bridgeport Broadcasting Station, Inc., 500 w, E, "The Industrial Capital of Connecticut."

**WIL**

1200 kc, St. Louis, Mo., Missouri Broadcasting Co., 100 w, C, "A Wave Length Ahead."

**WILL**

890 kc, Urbana, Ill., University of Illinois, 250 w, C.

**WILM**

1420 kc, Wilmington, Del., Delaware Broadcasting Co., Inc., 100 w, E.

**WIOD**

1300 kc, Miami, Fla., Isle of Dreams Broadcasting Co., 1000 w, E, "Wonderful Isle of Dreams."

**WIP**

610 kc, Philadelphia, Pa., Gimbel Bros., Inc., 500 w, E, "Watch Its Progress."

**WIS**

1010 kc, Columbia, S. C., George T. Barnes, Inc., 500 w, E.

**WISJ**

560 kc, South Madison, Wis., Wisconsin State Journal Broadcasting Co., 500 w, C.

**WISN**

1120 kc, Milwaukee, Wis., Evening Wisconsin Co., 250 w, C.

**WJAC**

1310 kc, Johnstown, Pa., Johnstown Automobile Co., 100 w, E, "The Voice of the Friendly City."

**WJAG**

1060 kc, Norfolk, Neb., Norfolk Daily News, 1000 w, C, "Home of the Printer's Devil."

**WJAK**

1310 kc, Marion, Ind., Marion Brdst. Co., 50 w.

**WJAR**

890 kc, Providence, R. I., The Outlet Co., 250 w, E, "The Southern Gateway of New England."

**WJAS**

1290 kc, Pittsburgh, Pa., Pittsburgh Radio Supply House, 1000 w, E.

**WJAX**

900 kc, Jacksonville, Fla., City of Jacksonville, 1000 w, E, "WJAX—W for Wonderful, JAX for Jacksonville."

**WJAY**

610 kc, Cleveland, Ohio, Cleveland Radio Broadcasting Corp., 500 w, E.

**WJAZ**

1490 kc, Chicago, Ill., Zenith Radio Corp., 5000 w, C.

**WJBC**

1200 kc, LaSalle, Ill., Kaskaskia Broadcasting Co., 100 w, C.

**WJBI**

1210 kc, Red Bank, N. J., Monmouth Broadcasting Co., 100 w, E.

**WJBK**

1370 kc, Highland Park, Mich., J. F. Hopkins, 50 w, C.

**WJBL**

1200 kc, Decatur, Ill., Commodore Broadcasting Co., 100 w, C.

**WJBO**

1420 kc, New Orleans, La., Valdemar Jensen, 100 w, C.

**WJBT**

See under WBBM.

**WJBU**

1210 kc, Lewisburg, Pa., Bucknell University, 100 w, E, "In the Heart of the Keystone State."

**WJBW**

1200 kc, New Orleans, La., C. Carlsen, Jr., 30 w, C, "The Serve You Broadcasting Station at New Orleans."

**WJBY**

1210 kc, Gadsden, Ala., Gadsden Broadcasting Co., 50 w, C.

**WJDJ**

1270 kc, Jackson, Miss., Lamar Life Ins. Co., 1000 w, C.

**WJJD**

1130 kc, Chicago, Ill., Loyal Order of Moose, 20,000 w, C, "Every Child Is Entitled to a High School Education and a Trade."

**WJKS**

1360 kc, Gary, Ind., Johnson-Kennedy Radio Corp., 1000 w, C.

**WJR**

750 kc, Detroit, Mich., The Goodwill Station, Inc., 5000 w, E.

**WJSV**

1460 kc, Alexandria, Va., Independent Publishing Co., 10,000 w.

**WJW**

1210 kc, Mansfield, Ohio, Mansfield Broadcasting Association, 100 w, E.

**WJZ**

760 kc, New York City, N. Y., National Broadcasting Co., 30,000 w, E.

**WKAQ**

890 kc, San Juan, Porto Rico, Radio Corp. of Porto Rico, 500 w, E, "Porto Rico, The Island of Enchantment in the Caribbean Sea."

**WKAR**

1040 kc, East Lansing, Mich., Michigan State College, 1000 w, E.

**WKAV**

1310 kc, Laconia, N. H., Laconia Radio Club, 100 w, E, "The Voice of the Winnepesaukee Lake Region."

**WKBB**

1310 kc, Joliet, Ill., Sanders Bros., 100 w, C.

**WKBC**

1310 kc, Birmingham, Ala., R. B. Broyles Furniture Co., 100 w, C.

**WKBF**

1400 kc, Indianapolis, Ind., Indianapolis Broadcasting Corp., 500 w, C, "We Keep Building Friendships."

**WKBH**

1380 kc, LaCrosse, Wis., WKBH, Inc., 1000 w, C.

**WKBI**

1420 kc, Chicago, Ill., Fred L. Schoenwolf, 100 w, C.

**WKBN**

570 kc, Youngstown, Ohio, W. P. Williamson, Jr., 500 w, E.

**WKBO**

1450 kc, Jersey City, N. J., Camith Corp., 250 w, E.

**WKBQ**

1350 kc, New York, N. Y., Standard Cahill Co., Inc., 250 w, E.

**WKBS**

1310 kc, Galesburg, Ill., Permil N. Nelson, 100 w, C.

**WKBV**

1500 kc, Connersville, Ind., Knox Battery & Electric Co., 100 w, C.

**WKBW**

1480 kc, Buffalo, N. Y., WKBW, Inc., 5000 w, E.

**WKBZ**

1500 kc, Ludington, Mich., K. L. Ashbacker, 50 w.

**WKJC**

1200 kc, Lancaster, Pa., Kirk Johnson & Co., 100 w, E.

**WKRC**

550 kc, Cincinnati, Ohio, WKRC, Inc., 1000 w, E, "WKRC, K—Kodel, R—Radio, C—Corporation."

**WKY**

900 kc, Oklahoma City, Okla., WKY Radiophone Co., 1000 w, C.

**WKZO**

590 kc, Berrien Springs, Mich., WKZO, Inc., 1000 w, C, "The Radio Lighthouse."

**WLAC**

1470 kc, Nashville, Tenn., Life & Casualty Ins. Co., 5000 w, C, "The Thrift Station."

**WLAP**

1200 kc, Louisville, Ky., American Broadcasting Corp. of Kentucky, 100 w, C.

**WLB**

1250 kc, Minneapolis, Minn., University of Minnesota, 1000 w, C.

**WLBC**

1310 kc, Muncie, Ind., Donald A. Burton, 50 w.

**WLBK**

1420 kc, Kansas City, Kan., WLBK Broadcasting Co., 100 w, C, "Where Listeners Become Friends."

**WLBG**

1200 kc, Petersburg, Va., Robert Allen Gamble, 100 w, E.

**WLBL**

900 kc, Stevens Point, Wis., Wisconsin Department of Markets, 2000 w, daytime, C, "Wisconsin. Land of Beautiful Lakes."

**WLBW**

1260 kc, Oil City, Pa., Radio-Wire Program Corp., 500 w, E.

**WLBX**

1500 kc, Long Island City, N. Y., John N. Brahy, 100 w.

**WLBZ**

620 kc, Bangor, Me., Maine Broadcasting Co., 500 w, E.

**WLCI**

1210 kc, Ithaca, N. Y., Lutheran Assn. of Ithaca, 50 w, E.

**WLEX**

1410 kc, Lexington, Mass., Lexington Air Station, 500 w, E.

**WLEY**

1370 kc, Lexington, Mass., Lexington Air Station, 100 w, E.

**WLIB**

See under WGN.

**WLIT**

560 kc, Philadelphia, Pa., Lit Brothers, 500 w, E, "The Quaker City Siren."

**WLOE**

1500 kc, Boston, Mass., Boston Broadcasting Co., 100 w.

**WLS**

870 kc, Chicago, Ill., Agricultural Broadcasting Co., 5000 w, C.

**WLSI**

See under WDFW.

**WLTH**

1400 kc, Brooklyn, N. Y., Voice of Brooklyn, Inc., 500 w, E.

**WLVA**

1370 kc, Lynchburg, Va., Lynchburg Broadcasting Corp., 100 w, E.

**WLW**

700 kc, Cincinnati, Ohio, Crosley Radio Corp., 50,000 w, E.

**WLWL**

1100 kc, New York, N. Y., Missionary Society of St. Paul, 5000 w, E.

**WMAC**

See under WSYR.

**WMAF**

1410 kc, So. Dartmouth, Mass., Round Hills Radio Corp., 500 w, E.

**WMAK**

1040 kc, Buffalo, N. Y., WMAK Broadcasting System, 1000 w, E.

**WMAL**

630 kc, Washington, D. C., M. A. Leese Co., 250 w, E.

**WMAQ**

670 kc, Chicago, Ill., WMAQ Inc., 5000 w, C.

**WMAZ**

890 kc, Macon, Ga., Macon Junior Chamber of Commerce, 250 w, E, shared, "Watch Mercer Attain Zenith."

**WMBA**

1500 kc, Newport, R. I., LeRoy Joseph Beebe, 100 w, E.

**WMBC**

1420 kc, Detroit, Mich., Michigan Broadcasting Co., Inc., 100 w, E.

**WMBD**

1440 kc, Peoria Heights, Ill., Peoria Heights Radio Laboratory, 500 w.

**WMBF**

See under WIOD.

**WMBG**

1210 kc, Richmond, Va., Havens & Martin, Inc., 100 w, E, "The Daytime Station."

**WMBH**

1420 kc, Joplin, Mo., Edwin Dudley Aber, 100 w, C, "Where Memories Bring Happiness."

**WMBI**

1080 kc, Chicago, Ill., Moody Bible Institute Radio Station, 5000 w, C, shared, "The West Point of Christian Service."

**WMBJ**

1500 kc, Wilkensburg, Pa., Rev. John W. Sproul, 100 w, E.

**WMBO**

1310 kc, Auburn, N. Y., Radio Service Laboratories, 100 w, E.

**WMBQ**

1500 kc, Brooklyn, N. Y., Paul J. Gollhofer, 100 w.

**WMBR**

1370 kc, Tampa, Fla., F. J. Reynolds, 100 w, E, "WMBR, Everything for Radio at Tampa, Fla."

**WMC**

780 kc, Memphis, Tenn., Memphis Commercial Appeal, Inc., 500 w, C, "WMC, Memphis, Down in Dixie."

**WMCA**

570 kc, New York, N. Y., Knickerbocker Broadcasting Co., Inc., 500 w, E, "Where the White Way Begins."

**WMMN**

890 kc, Fairmont, W. Va., Holt Rome Novelty Co., 250 w, E.

**WMPC**

1500 kc, Lapeer, Mich., First Methodist Protestant Church, 100 w, E, "Where Many Preach Christ."

**WMRJ**

1210 kc, Jamaica, N. Y., Peter J. Prinz, 10 w, E, "The Gateway of the Sunrise Trail."

**WMSG**

1350 kc, New York, N. Y., Madison Square Garden Broadcast Co., 250 w, E.

**WMT**

600 kc, Waterloo, Iowa, Waterloo Broadcasting Co., 500 w, C.

**WNAC**

1230 kc, Boston, Mass., The Shepard Broadcasting Service, 1000 w, E.

**WNAD**

1010 kc, Norman, Okla., University of Oklahoma, 500 w, C, "The Voice of Soonerland."

**WNAX**

570 kc, Yankton, S. Dak., Gurney Seed & Nursery Co., 1000 w, C.

**WNBK**

1500 kc, Binghamton, N. Y., Howitt-Wood Radio Co., 100 w, E, "The Voice of the Triple Cities."

**WNBH**

1310 kc, New Bedford, Mass., New Bedford Broadcasting Co., 100 w, E, shared, "The Gateway to Cape Cod."

**WNBO**

1200 kc, Silver Haven, Pa., J. B. Spriggs, 100 w, E.

**WNBR**

1430 kc, Memphis, Tenn., Memphis Broadcasting Co., 500 w, C.

**WNBW**

1200 kc, Carbondale, Pa., Home Cut Glass & China Co., 10 w, E.

**WNBX**

1200 kc, Springfield, Vt., First Congregational Church Corp., 10 w, E.

**WNBZ**

1290 kc, Saranac Lake, N. Y., Smith & Mace, 50 w, E.

**WNJ**

1450 kc, Newark, N. J., Radio Investment Co., 250 w, E, "The Voice of Newark."

**WNOX**

560 kc, Knoxville, Tenn., Sterchi Bros., 1000 w, C, "Smoky Mountain Station."

**WNYC**

570 kc, New York, N. Y., Department of Plant & Structures, 500 w, E, "Municipal Broadcasting Station of the City of New York."

**WOAI**

1190 kc, San Antonio, Texas, Southern Equipment Co., 50,000 w, C, "The Winter Playground of America."

**WOAN**

See WREC.

**WOAX**

1280 kc, Trenton, N. J., WOAX, Inc., 500 w, E, "Trenton Makes, the World Takes."

**WOBT**

1310 kc, Union City, Tenn., Titsworth's Radio & Music Shop, 100 w, C.

**WOBU**

580 kc, Charleston, W. Va., WOBU, Inc., 250 w, E.

**WOC**

1000 kc, Davenport, Iowa, Central Broadcasting Co., 5000 w, C.

**WOCL**

1210 kc, Jamestown, N. Y., A. E. Newton, 25 w, E.

**WODA**

1250 kc, Paterson, N. J., Richard E. O'Dea, 1000 w, E, "The Voice of the Silk City."

**WODX**

1410 kc, Mobile, Ala., Mobile Brdcastg. Corp., 500 w, C.

**WOI**

640 kc, Ames, Iowa, Iowa State College, 5000 w, C.

**WOKO**

1440 kc, Poughkeepsie, N. Y., Hudson Valley Broadcasting Corp., 500 w, E.

**WOL**

1310 kc, Washington, D. C., American Broadcasting Co., 100 w, E.

**WOMT**

1210 kc, Manitowoc, Wis., Francis M. Kadow, 100 w.

**WOOD**

1270 kc, Grand Rapids, Mich., Walter B. Stiles, Inc., 500 w, C, "The Voice of the Whispering Pines."

**WOPI**

1500 kc, Bristol, Tenn., Radiophone Broadcasting Co., 100 w, E.

**WOQ**

1300 kc, Kansas City, Mo., Unity School of Christianity, 1000 w, C.

**WOR**

710 kc, Newark, N. J., J. Bamberger Broadcasting Service, Inc., 5000 w, E.

**WORC**

1200 kc, Worcester, Mass., A. F. Kleindienst, 100 w, E.

**WOS**

630 kc, Jefferson City, Mo., State Marketing Bureau, 500 w, C, "Watch Our State."

**WOV**

1130 kc, New York, N. Y., International Broadcasting Corp., 1000 w, E.

**WOW**

590 kc, Omaha, Neb., Woodmen of the World, 1000 w, C, "The Omaha Station."

**WOWO**

1160 kc, Ft. Wayne, Ind., Main Auto Supply Co., 10,000 w, C.

**WPAD**

1420 kc, Paducah, Ky., Paducah Broadcasting Co., 100 w, C.

**WPAP**

See under WQAO.

**WPAW**

1210 kc, Pawtucket, R. I., Shartenberg & Robinson, 100 w, E, "The City of Diversified Industries."

**WPCC**

560 kc, Chicago, Ill., North Shore Congregational Church, 500 w, C.

**WPCH**

810 kc, New York, N. Y., Eastern Broadcasters, Inc., 500 w, E.

**WPEN**

1500 kc, Philadelphia, Pa., Wm. Penn Broadcasting Co., 100 w, E, "First Wireless School in America."

**WPG**

1100 kc, Atlantic City, N. J., WPG Broadcasting Corp., 5000 w, E.

**WPOE**

1370 kc, Patchogue, N. Y., Nassau Broadcasting Corp., 100 w, E.

**WPOR**

See under WTAR.

**WPSC**

1230 kc, State College, Pa., Pennsylvania State College, 500 w, day, E, "The Voice of the Nittany Lion."

**WPTF**

680 kc, Raleigh, N. C., Durham Life Insurance Co., 1,000 w, E.

**WQAM**

560 kc, Miami, Fla., Miami Broadcasting Co., 1000 w, E.

**WQAN**

880 kc, Scranton, Pa., Scranton Times, 250 w, E.

**WQAO**

1010 kc, New York, N. Y., Calvary Baptist Church, 250 w, E.

**WQBC**

1360 kc, Vicksburg, Miss., Delta Broadcasting Co., 300 w, C.

**WQDM**

1370 kc, St. Albans, Vt., A. J. St. Antoine, 5 w, E.

**WQDX**

1210 kc, Thomasville, Ga., Stevens Luke, 50 w, E.

**WRAF**

1200 kc, La Porte, Ind., Chas. Middleton, 100 w, C.

**WRAK**

1370 kc, Williamsport, Pa., C. R. Cummins, 50 w, E.

**WRAW**

1310 kc, Reading, Pa., Reading Broadcasting Co., 50 w, E, "The Schuylkill Valley Echo."

**WRAX**

1020 kc, Philadelphia, Pa., WRAX Broadcasting Co., 250 w, E.

**WRBI**

1310 kc, Tifton, Ga., Kent's Furniture & Music Store, 20 w, E.

**WRBJ**

1370 kc, Hattiesburg, Miss., Woodruff Furniture Co., 10 w, C.

**WRBL**

1200 kc, Columbus, Ga., David Parmer, 50 w, E.

**WRBQ**

1210 kc, Greenville, Miss., J. Pat Scully, 250 w, C.

**WRBT**

1370 kc, Wilmington, N. C., Wilmington Radio Association, 100 w, E.

**WRBX**

1410 kc, Roanoke, Va., Richmond Development Corp., 250 w, E.

**WRC**

950 kc, Washington, D. C., National Broadcasting Co., 500 w, E, "The Voice of the Capital."

**WRDO**

1370 kc, Augusta, Me., Albert S. Woodman, 100 w, E.

**WRDW**

1500 kc, Augusta, Ga., Davenport's Musicove, Inc., 100 w, E.

**WREC**

600 kc, Memphis, Tenn., WREC, Inc., 500 w.

**WREN**

1220 kc, Lawrence, Kan., Jenny Wren Co., 1000 w, C.

**WRHM**

1250 kc, Minneapolis, Minn., Minnesota Broadcasting Corp., 1000 w, C, "Welcome Rosedale Hospital, Minneapolis."

**WRJN**

1370 kc, Racine, Wis., Racine Broadcasting Corp., 100 w, C.

**WRNY**

1010 kc, New York, N. Y., Aviation Radio Station, 250 w, E.

**WROL**

1310 kc, Knoxville, Tenn., Stuart Broadcasting Corp., 100 w, C.

**WRR**

1280 kc, Dallas, Texas, City of Dallas, 500 w, C.

**WRUF**

830 kc, Gainesville, Fla., University of Florida, 5000 w, E.

**WRVA**

1110 kc, Richmond, Va., Larus Bros. & Co., Inc., 5000 w, E, "Carry Me Back to Old Virginny."

**WSAI**

1330 kc, Cincinnati, Ohio, Crosley Radio Corp., 500 w, E, "The Gateway to Dixie."

**WSAJ**

1310 kc, Grove City, Pa., Grove City College, 100 w, E.

**WSAN**

1440 kc, Allentown, Pa., Allentown Call Pub. Co., 250 w, E, "We Serve Allentown Nationality."

**WSAR**

1450 kc, Fall River, Mass., Doughty & Welch Electrical Co., Inc., 250 w, E.

**WSAZ**

580 kc, Huntington, W. Va., WSAZ, Inc., 250 w, E.

**WSB**

740 kc, Atlanta, Ga., Atlanta Journal Co., 5000 w, E, "The Voice of the South."

**WSBC**

1210 kc, Chicago, Ill., World Battery Co., 100 w, C.

**WSBT**

1230 kc, South Bend, Ind., South Bend Tribune, 500 w, C.

**WSDA**

See under WSGH.

**WSEN**

1210 kc, Columbus, Ohio, Columbus Broadcasting Corp., 100 w, E.

**WSFA**

1410 kc, Montgomery, Ala., Montgomery Brdstg. Co., 500 w, C.

**WSGH**

1400 kc, Brooklyn, N. Y., Paramount Broadcasting Corp., 500 w.

**WSIX**

1210 kc, Springfield, Tenn., 638 Tire & Vulcanizing Co., 100 w, C.

**WSJS**

1310 kc, Winston-Salem, N. C., The Journal Co., 100 w, E.

**WSM**

650 kc, Nashville, Tenn., National Life & Accident Ins. Co., 5000 w, C, "We Shield Millions."

**WSMB**

1320 kc, New Orleans, La., Saenger Theaters, Inc., & Maison Blanche Co., 500 w, C, "America's Most Interesting City."

**WSMK**

1380 kc, Dayton, Ohio, Stanley M. Krohn, Jr., 200 w, C, "The Home of Aviation."

**WSOC**

1210 kc, Gastonia, N. C., A. J. Kirby Music Co., 100 w, E.

**WSPA**

1420 kc, Spartanburg, S. C., 100 w, E, "The Voice of South Carolina."

**WSPD**

1340 kc, Toledo, Ohio, Toledo Broadcasting Co., 500 w, E.

**WSSH**

1410 kc, Boston, Mass., Tremont Temple Baptist Church, 500 w, E, "Stranger's Sunday Home."

**WSUI**

880 kc, Iowa City, Iowa, State Univ. of Iowa, 500 w, C, "The Old Gold Studio."

**WSUN**

See under WFLA.

**WSVS**

1370 kc, Buffalo, N. Y., Seneca Vocational High School, 50 w, E, "Watch Seneca Vocational School."

**WSYR**

570 kc, Syracuse, N. Y., Clive B. Meredith, 250 w, E.

**WTAD**

1440 kc, Quincy, Ill., Illinois Stock Medicine Broadcasting Corp., 500 w.

**WTAG**

580 kc, Worcester, Mass., Worcester Telegram Pub. Co., Inc., 250 w, E, "The Voice From the Heart of the Commonwealth."

**WTAM**

1070 kc, Cleveland, Ohio, National Broadcasting Co., 50,000 w, E, "The Voice from the Storage Battery."

**WTAQ**

1330 kc, Eau Claire, Wis., Gillette Rubber Co., 1000 w, C.

**WTAR**

780 kc, Norfolk, Va., WTAR Radio Corp., 500 w, E.

**WTAW**

1120 kc, College Station, Texas, Agri. & Mech. College of Texas, 500 w, C.

**WTAX**

1210 kc, Springfield, Ill., WTAX, Inc., 100 w.

**WTBO**

1420 kc, Cumberland, Md., Associated Brdstg. Corp., 100 w, E.

**WTEL**

1310 kc, Philadelphia, Pa., Foulkrod Radio Eng. Co., 50 w, E.

**WTFI**

1450 kc, Toccoa, Ga., Toccoa Falls Institute, 500 w, E.

**WTIC**

1060 kc, Hartford, Conn., Travelers Broadcasting Service Corp., 50,000 w, E, "The Insurance City."

**WTMJ**

620 kc, Milwaukee, Wis., Milwaukee Journal, 1000 w, C.

**WTNT**

1470 kc, Nashville, Tenn., Tenn. Pub. Co., 5000 w, C.

**WTOC**

1260 kc, Savannah, Ga., Savannah Broadcasting Corp., 500 w, E.

**WWAE**

1200 kc, Hammond, Ind., Hammond - Calumet Broadcasting Corp., 100 w.

**WWJ**

920 kc, Detroit, Mich., Evening News Assn., 1000 w, E.

**WWL**

850 kc, New Orleans, La., Loyola University, 5000 w, C.

**WWNC**

570 kc, Asheville, N. C., Citizens Broadcasting Co., 1000 w, E.

**WWRL**

1500 kc, Woodside, N. Y., Long Island Broadcasting Corp., 100 W.

**WWVA**

1160 kc, Wheeling, W. Va., West Virginia Broadcasting Corp., 5000 w, E.

**WXYZ**

1240 kc, Detroit, Mich., Kunsy Trendle Broadcasting Co., 1000 w, E.

# Consolidated Broadcast List

Call	Town	Call	Town	Call	Town	Call	Town		
KRPS	Portland, Ore.	KICK	Red Oak, Ia.	WBAA	Lafayette, Ind.	WIAD	Milwaukee, Wis.	WMC	Memphis, Tenn.
KBTM	Paragould, Ark.	KID	Idaho Falls, Idaho	WBAB	Harrisburg, Pa.	WIAM	Rochester, N. Y.	WMCA	New York, N. Y.
KCRG	Enid, Okla.	KIDO	Boise, Idaho	WBAL	Baltimore, Md.	WIAP	New York, N. Y.	WMFN	Fairmont, W. Va.
KCRJ	Jerome, Ariz.	KIT	Yakima, Wash.	WBAP	Fort Worth, Tex.	WIAS	Louisville, Ky.	WMPC	Lapeer, Mich.
KDB	Santa Barbara, Calif.	KJBS	San Francisco, Calif.	WBAX	Wilkes-Barre, Pa.	WHAT	Philadelphia, Pa.	WMRJ	Jamaica, N. Y.
KDKN	Casper, Wyo.	KJR	Seattle, Wash.	WBBC	Brooklyn, N. Y.	WHAZ	Troy, N. Y.	WMSG	New York, N. Y.
KDKA	Pittsburgh, Pa.	KLCN	Blytheville, Ark.	WBBL	Richmond, Va.	WHB	Kansas City, Mo.	WMT	Waterloo, Ia.
KDLR	DeVils Lake, N. D.	KLO	Ogden, Utah	WBHM	Chicago, Ill.	WHBC	Canton, Ohio	WNAC	Boston, Mass.
KDYI	Salt Lake City, Utah	KLPM	Minot, N. D.	WBRR	Brooklyn, N. Y.	WHBD	Mt. Orab, Ohio	WNAN	Norman, Okla.
KECA	Los Angeles, Calif.	KLRA	Little Rock, Ark.	WBZZ	Ponca City, Okla.	WHBF	Rock Island, Ill.	WNAX	Yankton, S. D.
KEFV	Burbank, Calif.	KLS	Oakland, Calif.	WBZM	Bay City, Mich.	WHBO	Memphis, Tenn.	WNBF	Biinghamton, N. Y.
KEKX	Portland, Ore.	KLX	Oakland, Calif.	WBZV	Chicago, Ill.	WHBT	Anderson, Ind.	WNBH	New Bedford, Mass.
KEFV	Lincoln, Neb.	KLZ	Denver, Colo.	WBZT	Buffalo, N. Y.	WHBY	Green Bay, Wis.	WNBW	Silver Haven, Pa.
KEFB	Great Falls, Mont.	KMA	Shenandoah, Ia.	WBZG	Glens Falls, N. Y.	WHDF	Calumet, Mich.	WNBZ	Charlottesville, Va.
KFRK	Sacramento, Calif.	KMAC	San Antonio, Tex.	WBZJ	Greensboro, N. C.	WHDD	Boston, Mass.	WNBZ	Springfield, Vt.
KFBH	Ivercreech, Wash.	KMBC	Kansas City, Mo.	WBZL	Boston, Mass.	WHDI	Minneapolis, Minn.	WNBZ	Saranac Lake, N. Y.
KFDM	Beaumont, Tex.	KMCS	Inglewood, Calif.	WBZM	Hackensack, N. J.	WHDL	Tupper Lake, N. Y.	WNJ	Newark, N. J.
KFDY	Brookings, S. D.	KMED	Medford, Calif.	WBZV	Terre Haute, Ind.	WHDC	Rochester, N. Y.	WNXX	Knoxville, Tenn.
KFBI	Denver, Colo.	KMFB	Fresno, Calif.	WBZC	Birmingham, Ala.	WHDF	Cicero, Ill.	WNXX	New York, N. Y.
KFBO	St. Joseph, Mo.	KMLB	Monroe, La.	WBRE	Wilkes-Barre, Pa.	WHK	Cleveland, Ohio	WOAI	San Antonio, Tex.
KFOR	Boonville, Mo.	KMMJ	Clay Center, Neb.	WBSSO	Needham, Mass.	WHN	New York, N. Y.	WOAN	Memphis, Tenn.
KFH	Wichita, Kans.	KMO	Tacoma, Wash.	WBTT	Chicago, Ill.	WHO	Des Moines, Iowa	WOAX	Trenton, N. J.
KFI	Los Angeles, Calif.	KMON	St. Louis, Mo.	WBTM	Danville, Va.	WHOM	Jersey City, N. J.	WOBU	Union City, Tenn.
KFIO	Spokane, Wash.	KMPK	Beverly Hills, Calif.	WBZA	Boston, Mass.	WHPP	Harrisburg, Pa.	WOBU	Union City, Tenn.
KFTU	Juneau, Alaska	KMTR	Los Angeles, Calif.	WCAC	Storrs, Conn.	WIAS	Ottumwa, Ia.	WOC	Davenport, Ia.
KFTZ	Fond du Lac, Wis.	KNN	Hollywood, Calif.	WCAD	Canton, N. Y.	WIBA	Madison, Wis.	WOCI	Jamestown, N. Y.
KFJB	Marshalltown, Iowa	KOA	Denver, Colo.	WCAG	Pittsburgh, Pa.	WIBG	Elkins Park, Pa.	WODA	Paterson, N. J.
KFTF	Oklahoma City, Okla.	KOAC	Corvallis, Ore.	WCALH	Columbus, Ohio	WIBM	Jackson, Mich.	WODX	Mobile, Ala.
KFTH	Astoria, Ore.	KOB	State College, N. M.	WCAL	Lincoln, Neb.	WIBR	Chicago, Ill.	WOI	Ames, Ia.
KFJM	Grand Forks, N. D.	KOCW	Chickasha, Okla.	WCAL	Northfield, Minn.	WIBS	St. Louis, Mo.	WOI	Poughkeepsie, N. Y.
KFRF	Portland, Ore.	KOH	Reno, Nev.	WCAM	Camden, N. J.	WIBT	St. Louis, Mo.	WOI	Washington, D. C.
KFRV	Fort Dodge, Ia.	KOH	Columbus, Miss.	WCAN	Camden, N. J.	WIBT	Poyntette, Wis.	WOMT	Manitowoc, Wis.
KFLZ	Fort Worth, Tex.	KOIN	Portland, Ore.	WCAN	Baltimore, Md.	WIBW	Topeka, Kans.	WOOD	Grand Rapids, Mich.
KFKA	Greely, Colo.	KOL	Seattle, Wash.	WCAP	Asbury Park, N. J.	WIBX	Utica, N. Y.	WOPI	Bristol, Tenn.
KPKB	Milford, Kans.	KOMO	Seattle, Wash.	WCAT	Rapid City, S. D.	WICC	Bridgeport, Conn.	WOQ	Kansas City, Mo.
KPKU	Lawrence, Kans.	KONO	San Antonio, Tex.	WCAU	Philadelphia, Pa.	WII	St. Louis, Mo.	WOR	Newark, N. J.
KPKX	Chicago, Ill.	KOOS	Marshfield, Ore.	WCAX	Burlington, Vt.	WILL	Irthana, Ill.	WORC	Worcester, Mass.
KPLA	Rockford, Ill.	KORE	Eugene, Ore.	WCAY	Carthage, Ill.	WILM	Wilmington, Del.	WORS	Jefferson City, Mo.
KPLX	Galveston, Tex.	KOY	Phoenix, Ariz.	WCBA	Allentown, Pa.	WIOD	Miami, Fla.	WOW	New York, N. Y.
KPMN	Northfield, Minn.	KPCB	Seattle, Wash.	WCBD	Zion, Ill.	WIOP	Philadelphia, Pa.	WOWO	Ft. Wayne, Ind.
KPNF	Shenandoah, Ia.	KPCM	Prescott, Ariz.	WCBM	Baltimore, Md.	WISJ	Columbia, S. C.	WPAD	Paducah, Ky.
KFOR	Lincoln, Neb.	KPJM	San Francisco, Calif.	WCBS	Springfield, Ill.	WISN	Milwaukee, Wis.	WPAP	New York, N. Y.
KFOG	Long Beach, Calif.	KPOF	Denver, Colo.	WCBO	Minneapolis, Minn.	WJAC	Johnstown, Pa.	WPAP	Pawtucket, R. I.
KPPL	Dublin, Tex.	KPPC	Pasadena, Calif.	WCDA	New York, N. Y.	WJAG	Norfolk, Neb.	WPCC	Chicago, Ill.
KPFM	Greenville, Tex.	KPO	Wenatchee, Wash.	WCDF	Chicago, Ill.	WJAK	Marion, Ind.	WPEN	New York, N. Y.
KPFW	Ft. Smith, Ark.	KPRC	Houston, Tex.	WCGU	Brooklyn, N. Y.	WJAR	Providence, R. I.	WPHN	Philadelphia, Pa.
KPTV	Spokane, Wash.	KPSN	Pasadena, Calif.	WCHD	Chicago, Ill.	WJAX	Pittsburgh, Pa.	WPI	Atlantic City, N. J.
KFOD	Anchorage, Alaska	KQV	Pittsburgh, Pa.	WCKY	Covington, Ky.	WJAX	Jacksonville, Fla.	WPK	Patchogue, N. Y.
KFOU	Holy City, Calif.	KQW	San Jose, Calif.	WCLB	Long Beach, N. Y.	WJAY	Cleveland, Ohio	WPK	Norfolk, Va.
KFOV	Seattle, Wash.	KRE	Berkeley, Calif.	WCLO	Janesville, Wis.	WJAZ	Chicago, Ill.	WPSC	State College, Pa.
KFRC	San Francisco, Calif.	KREG	Santa Ana, Calif.	WCMA	Culver, Ind.	WJBC	La Salle, Ill.	WPTF	Raleigh, N. C.
KFRH	Columbia, Mo.	KRGV	Harlingen, Tex.	WCOA	Pensacola, Fla.	WJBI	Red Bank, N. J.	WOAM	Miami, Fla.
KFSD	San Diego, Calif.	KRLD	Dallas, Tex.	WCOE	Meridian, Miss.	WJBK	Highland Park, Mich.	WOAN	Scranton, Pa.
KFSG	Los Angeles, Calif.	KRMD	Shreveport, La.	WCOG	Harrisburg, Pa.	WJBL	Decatur, Ill.	WOAO	New York, N. Y.
KFUL	Galveston, Tex.	KRNB	Oakland, Calif.	WCOH	Yonkers, N. Y.	WJBO	New Orleans, La.	WBOC	Vicksburg, Miss.
KFUM	Colorado Spgs., Colo.	KRSC	Seattle, Wash.	WCRW	Chicago, Ill.	WJBT	Chicago, Ill.	WODM	St. Albans, Vt.
KFUO	St. Louis, Mo.	KSAC	Manhattan, Kans.	WCSC	Charleston, S. O.	WJBT	Lewisburg, Pa.	WOFX	Thomasville, Ga.
KFTP	Denver, Colo.	KSGJ	Sioux City, Ia.	WCST	Portland, Me.	WJBR	New Orleans, La.	WRAF	La Porte, Ind.
KFVD	Culver City, Calif.	KSP	St. Louis, Mo.	WDAE	Tampa, Fla.	WJBR	Decatur, Ill.	WRAC	Williamsport, Pa.
KFVS	Cape Girardeau, Mo.	KSEI	Pocatello, Idaho	WDAF	Kansas City, Mo.	WJBS	Gary, Ind.	WRAX	Philadelphia, Pa.
KFWB	Highland, Calif.	KSL	Salt Lake City, Utah	WDAG	Amarillo, Tex.	WJCS	Detroit, Mich.	WRBI	Tifton, Ga.
KFWP	St. Louis, Mo.	KSMR	Santa Maria, Calif.	WDAL	El Paso, Tex.	WJVS	Alexandria, Va.	WRBI	Hattiesburg, Miss.
KFWT	San Francisco, Calif.	KSOO	Sioux Falls, S. D.	WDAY	Fargo, N. D.	WJW	Mansfield, Ohio	WRBI	Columbus, Ga.
KFXD	Nampa, Idaho	KSTP	St. Paul, Minn.	WDBJ	Roanoke, Va.	WJZ	New York, N. Y.	WRBK	Washington, Miss.
KFXE	Denver, Colo.	KTAB	San Francisco, Calif.	WDBO	Orlando, Fla.	WJZ	New York, N. Y.	WRBT	Washington, N. C.
KFXJ	Edgewater, Colo.	KTAH	San Antonio, Tex.	WDDI	Wilmington, Del.	WKAQ	San Juan, P. R.	WRBX	Roanoke, Va.
KFXM	San Bernardino, Calif.	KTAF	San Antonio, Tex.	WDGY	Minneapolis, Minn.	WKBQ	Buffalo, N. Y.	WRC	Washington, D. C.
KFXR	Oklahoma City, Okla.	KTAR	Phoenix, Ariz.	WDGP	Tulpe, Miss.	WKBQ	New York, N. Y.	WRDO	Augusta, Me.
KFXZ	Flagstaff, Ariz.	KTAT	Ft. Worth, Tex.	WDOD	Clinton, Tenn.	WKBK	Chicago, Ill.	WRDW	Augusta, Ga.
KFYR	Bismarck, N. D.	KTBH	Los Angeles, Calif.	WDRC	New Haven, Conn.	WKBK	Chicago, Ill.	WRFB	Memphis, Tenn.
KGA	Spokane, Wash.	KTBH	Portland, Ore.	WDSU	New Orleans, La.	WKBF	Indianapolis, Ind.	WRFB	Lawrence, Kans.
KGAR	Tucson, Ariz.	KTPS	Shreveport, La.	WDWF	Providence, R. I.	WKBH	La Crosse, Wis.	WRHM	Minneapolis, Minn.
KGB	San Diego, Calif.	KTHS	Hot Springs, Ark.	WEAF	New York, N. Y.	WKBK	Chicago, Ill.	WRNY	New York, N. Y.
KGBU	Ketchikan, Alaska	KTLG	Houston, Tex.	WEAL	Ithaca, N. Y.	WKBK	Chicago, Ill.	WROL	Knoxville, Tenn.
KGBX	St. Joseph, Mo.	KTM	Los Angeles, Calif.	WEAN	Providence, R. I.	WKBK	Chicago, Ill.	WRR	Dallas, Tex.
KGFZ	York, Neb.	KTNB	Nashville, Tenn.	WEAT	Providence, R. I.	WKBK	Chicago, Ill.	WRUP	Gainesville, Fla.
KGGC	Decorah, Ia.	KTRH	Houston, Tex.	WEAV	Providence, R. I.	WKBK	Chicago, Ill.	WRVA	Richmond, Va.
KGGT	Mandan, N. D.	KTSA	San Antonio, Tex.	WEBC	Superior, Wis.	WKBK	Chicago, Ill.	WSAI	Cincinnati, Ohio
KGCX	Wolf Point, Mont.	KTSL	Shreveport, La.	WEBO	Harrisburg, Ill.	WKBK	Chicago, Ill.	WSAJ	Grove City, Pa.
KGDA	Mitchell, S. D.	KTSM	El Paso, Tex.	WEBR	Buffalo, N. Y.	WKBK	Chicago, Ill.	WSA	Allentown, Pa.
KGDE	Fergus Falls, Minn.	KTWW	Seattle, Wash.	WEDC	Chicago, Ill.	WKBK	Chicago, Ill.	WSAR	Fall River, Mass.
KGDM	Stockton, Calif.	KUJ	Longview, Wash.	WEDH	Erie, Pa.	WKBK	Chicago, Ill.	WSAZ	Huntington, W. Va.
KGDY	Huron, S. D.	KUOA	Fayetteville, Ark.	WEEL	Boston, Mass.	WKBK	Chicago, Ill.	WSB	Atlanta, Ga.
KGEF	Los Angeles, Calif.	KUSD	Vermillion, S. D.	WEHC	Emory, Va.	WKBK	Chicago, Ill.	WSBC	Chicago, Ill.
KGFK	Yuma, Colo.	KUT	Austin, Tex.	WEHS	Evanston, Ill.	WKBK	Chicago, Ill.	WSBT	South Bend, Ind.
KGFR	Long Beach, Calif.	KVI	Tacoma, Wash.	WEIK	Philadelphia, Pa.	WKBK	Chicago, Ill.	WSDA	Brooklyn, N. Y.
KGFV	Fort Morgan, Colo.	KVT	Seattle, Wash.	WEIL	Philadelphia, Pa.	WKBK	Chicago, Ill.	WSEN	Columbus, Ohio
KGFZ	Kalispell, Mont.	KWA	Tucson, Ariz.	WELB	Battle Creek, Mich.	WKBK	Chicago, Ill.	WSPN	Montgomery, Ala.
KGFF	Alva, Okla.	KWOO	Tulsa, Okla.	WENR	Chicago, Ill.	WKBK	Chicago, Ill.	WSGH	Brooklyn, N. Y.
KGFG	Oklahoma City, Okla.	KVOS	Bellingham, Wash.	WEPS	Worcester, Mass.	WKBK	Chicago, Ill.	WSLX	Springfield, Tenn.
KGFI	Corpus Christi, Tex.	KWCR	Cedar Rapids, Ia.	WEVD	New York, N. Y.	WKBK	Chicago, Ill.	WSJS	Winston-Salem, N. C.
KGFP	Los Angeles, Calif.	KWEA	Shreveport, La.	WEW	St. Louis, Mo.	WKBK	Chicago, Ill.	WSM	Nashville, Tenn.
KGFL	Itaton, N. M.	KWEG	Stockton, Calif.	WEXL	Royal Oak, Mich.	WKBK	Chicago, Ill.	WSMB	New Orleans, La.
KGFV	Ravena, Neb.	KWGG	Portland, Ore.	WFAN	Dallas, Tex.	WKBK	Chicago, Ill.	WSMK	Dayton, Ohio
KGFX	Pierre, S. D.	KWJJ	Portland, Ore.	WFBC	Phoenixville, Pa.	WKBK	Chicago, Ill.	WSOC	Gastonia, N. C.
KGGC	San Francisco, Cal.	KWK	St. Louis, Mo.	WFBC	Knoxville, Tenn.	WKBK	Chicago, Ill.	WSPA	Spokane, W. Va.
KGGF	So. Coffeyville, Okla.	KWKC	Kansas City, Mo.	WFBE	Cincinnati, Ohio	WKBK	Chicago, Ill.	WSTB	Toledo, Ohio
KGGM	Albuquerque, N. M.	KWKK	Shreveport, La.	WFBI	Indianapolis, Ind.	WKBK	Chicago, Ill.	WSWB	Boston, Mass.
KGHI	Pueblo, Colo.	KWLV	Decorah, Ia.	WFBO	Albany, Pa.	WKBK	Chicago, Ill.	WSTQ	Manitowish, Wis.
KGHL	Billings, Mont.	KWVG	Fergus Falls, Wash.	WFBR	Baltimore, Md.	WKBK	Chicago, Ill.	WSTP	Iowa City, Ia.
KGIR	Twin Falls, Idaho	KXNA	Seattle, Wash.	WFDD	Flint, Mich.	WKBK	Chicago, Ill.	WSUN	Clearwater, Fla.
KGIW	Trinidad, Colo.	KXL	Portland, Ore.	WFDV	Rome, Ga.	WKBK	Chicago, Ill.	WSVS	Buffalo, N. Y.
KGLX	Las Vegas, Nev.	KXO	El Centro, Calif.	WFDW	Tallahassee, Fla.	WKBK	Chicago, Ill.	WSYR	Syracuse, N. Y.
KGLZ	Grant City, Mo.	KXRO	Aberdeen, Wash.	WFTI	Philadelphia, Pa.	WKBK	Chicago, Ill.	WTAD	Quincy, Ill.
KGJF	Little Rock, Ark.	KXYZ	Houston, Tex.	WFTL	Fort Lauderdale, Fla.	WKBK	Chicago, Ill.	WTAG	Worcester, Mass.
KGKB	Brownwood, Tex.	KYA	San Francisco, Calif.	WFLA	Lakeland, Fla.	WKBK	Chicago, Ill.	WTAM	Cleveland, Ohio
KGKL	San Angelo, Tex.	KYW	Chicago, Ill.	WFLC	Akron, Ohio	WKBK	Chicago, Ill.	WTAN	Washington, D. C.
KGKO	Wichita Falls, Tex.	KZM	Hayward, Calif.	WFLD	Chicago, Ill.	WKBK	Chicago, Ill.	WTAP	Norfolk, Va.
KGKN	Sandpoint, Idaho	WAAP	Chicago, Ill.	WGBB	Freeport, N. Y.	WKBK	Chicago, Ill.	WTAW	College Station, Tex.
KGKY	Scottsbluff, Neb.	WAAM	Newark, N. J.	WGBC	Memphis, Tenn.	WKBK	Chicago, Ill.	WTAX	Springfield, Ill.
KGMB	Honolulu, Hawaii	WAAP	Jersey City, N. J.	WGFB	Evansville, Ind.	WKBK	Chicago, Ill.	WTBO	Cumberland, Md.
KGMP	Elk City, Okla.	WAAY	Omaha, Neb.	WGFI	Scranton, Pa.	WKBK	Chicago, Ill.	WTFL	Philadelphia, Pa.
KGNF	North Platte, Neb.	WABC	New York City, N. Y.	WGFS	New York, N. Y.	WKBK	Chicago, Ill.	WTFI	Toccoa, Ga.
KGNO	Dodge City, Kans.	WABT	Bangor, Me.	WGFP	Newark, N. J.	WKBK	Chicago, Ill.	WTIC	Hartford, Conn.
KGO	San Francisco, Calif.	WABO	Rochester, N. Y.	WGFS	Chicago, Ill.	WKBK	Chicago, Ill.	WTIM	Milwaukee, Wis.
KGRS	Amarillo, Tex.	WABZ	New Orleans, La.	WGH	Newport News, Va.	WKBK	Chicago, Ill.	WTMD	Nashville, Tenn.
KGW	Honolulu, T. H.	WACO	Waco, Tex.	WGL	Fort Wayne, Ind.	WKBK	Chicago, Ill.	WTOT	Savannah, Ga.
KGW	Portland, Ore.	WADC	Tallmadge, Ohio	WGM	Minneapolis, Minn.	WKBK	Chicago, Ill.	WVAE	Hammoud, Ind.
KGW	Accy, Wash.	WADL	Columbus, Ohio	WGN	Chicago, Ill.	WKBK	Chicago, Ill.	WWJ	Detroit, Mich.
KH	Los Angeles, Calif.	WALR	Zanesville, Ohio	WGR	Buffalo, N. Y.	WKBK	Chicago, Ill.	WWN	New Orleans, La.
KIQ	Spokane, Wash.	WASB	Birmingham, Ala.	WGT	Atlanta, Ga.	WKBK	Chicago, Ill.	WWNB	Woodside, N. C.
		WASH	Grand Rapids, Mich.	WGY	Schenectady, N. Y.	WKBK	Chicago, Ill.	WWVA	Hutchinson, W. Va.
		WAWZ	New York, N. Y.	WHA	Madison, Wis.	WKBK	Chicago, Ill.	WXXZ	Detroit, Mich.

# U. S. Broadcasting Stations by Frequencies

**550 Kilocycles, 545.1 Meters:**  
KOAC, WGR, WKRC, KFUO, KSD, KFDY, KFYR.

**560 Kilocycles, 535.4 Meters:**  
WLIT, WFL, KFDM, WNOX, KTAB, KLZ, WIBO, WPCC, WQAM, WISJ.

**570 Kilocycles, 526.0 Meters:**  
WNYC, WMCA, WSYR, WMAC, WKBN, WWNC, KGKO, WNAX, KXA, KMTR, WEAO

**580 Kilocycles, 516.9 Meters—Canadian Shared:**  
WTAG, WOBW, WSAZ, KGFX, KSAC, WIBW

**590 Kilocycles, 508.2 Meters:**  
WEEI, WCAJ, WOW, KHQ, WKZO.

**600 Kilocycles, 499.7 Meters—Canadian Shared:**  
WCAO, WREC, WOAN, KFSD, WCAC, WMT, WGBS

**610 Kilocycles, 491.5 Meters:**  
WFAN, WIP, WDAF, KFRC, WJAY

**620 Kilocycles, 483.6 Meters:**  
WLBZ, WTMJ, KGW, WFLA, WSUN, KTAR

**630 Kilocycles, 475.9 Meters—Canadian Shared:**  
WMAL, WOS, KFUR, WGBF

**640 Kilocycles, 468.5 Meters:**  
WAIU, KFI, WOI

**650 Kilocycles, 461.3 Meters:**  
WSM, KPCB.

**660 Kilocycles, 454.3 Meters:**  
WEAF, WAAW

**670 Kilocycles, 447.5 Meters:**  
WMAQ

**680 Kilocycles, 440.9 Meters:**  
WPTF, KPO, KFEQ

**690 Kilocycles, 434.5 Meters—Canadian Wave:**

**700 Kilocycles, 428.3 Meters:**  
WLW

**710 Kilocycles, 422.3 Meters:**  
WOR, KMPC

**720 Kilocycles, 416.4 Meters:**  
WGN, WLIB

**730 Kilocycles, 410.7 Meters—Canadian Wave:**

**740 Kilocycles, 405.2 Meters:**  
WSB, KMMJ

**750 Kilocycles, 399.8 Meters:**  
WJR

**760 Kilocycles, 394.5 Meters:**  
WJZ, WEW, KVI

**770 Kilocycles, 389.4 Meters:**  
KFAB, WBBM, WJBT

**780 Kilocycles, 384.4 Meters—Canadian Shared:**  
WTAR, WPOR, KELW, KTM, WMC, WEAN

**790 Kilocycles, 379.5 Meters:**  
WGY, KGO

**800 Kilocycles, 374.8 Meters:**  
WBAP, WFAA

**810 Kilocycles, 370.2 Meters:**  
WPCH, WCCO

**820 Kilocycles, 365.6 Meters:**  
WHAS

**830 Kilocycles, 361.2 Meters:**  
KOA, WHDI, WRUF

**840 Kilocycles, 356.9 Meters—Canadian Wave:**

**850 Kilocycles, 352.7 Meters:**  
KWKH, WWL

**860 Kilocycles, 348.6 Meters:**  
WBOQ, WABC, KMO, WHB

**870 Kilocycles, 344.6 Meters:**  
WLS, WENR, WBCN

**880 Kilocycles, 340.7 Meters—Canadian Shared:**  
WQAN, WGBI, WCOC, KLX, KPOF, KFKA, WSUI

**890 Kilocycles, 336.9 Meters—Canadian Shared:**  
WJAR, WMMN, WMAZ, WGST, KGJF, WILL, KUSD, KFNE, WKAQ

**900 Kilocycles, 331.1 Meters:**  
WKY, WLBL, KHJ, KSEI, KGBU, WJAX, WBNB

**910 Kilocycles, 329.5 Meters—Canadian Wave:**

**920 Kilocycles, 325.9 Meters:**  
WVJ, KPRC, WAAF, WBSO, KOMO, KFXF, KFEL

**930 Kilocycles, 322.4 Meters—Canadian Shared:**  
WIBG, WDBJ, WBRC, KGBZ, KMA, KFWI, KROW

**940 Kilocycles, 319 Meters:**  
WCSH, WFIW, KOIN, KGU, WHA, WDAY, WAAT

**950 Kilocycles, 315.6 Meters:**  
WRC, KMBC, KFWR, KGHL

**960 Kilocycles, 312.3 Meters—Canadian Wave:**

**970 Kilocycles, 309.1 Meters:**  
KJR, WCFL

**980 Kilocycles, 305.9 Meters:**  
KDKA

**990 Kilocycles, 302.8 Meters:**  
WBZ, WBZA

**1000 Kilocycles, 299.8 Meters:**  
WHO, WOC, KFVD

**1010 Kilocycles, 296.9 Meters—Canadian Shared:**  
WQAO, WPAP, WHN, WRNY, KGGF, WNAD, KQW, WIS

**1020 Kilocycles, 293.9 Meters:**  
KYW, KFKX, WRAX

**1030 Kilocycles, 291.1 Meters—Canadian Wave:**

**1040 Kilocycles, 288.3 Meters:**  
WKAR, KTHS, KRLD, WMAK

**1050 Kilocycles, 285.5 Meters:**  
KNX, KFKB

**1060 Kilocycles, 282.8 Meters:**  
WBAL, WJAG, KWJJ, WTIC

**1070 Kilocycles, 280.2 Meters:**  
WTAM, WCAZ, WDW, KJBS

**1080 Kilocycles, 277.6 Meters:**  
WBT, WCBF, WMBI

**1090 Kilocycles, 275.1 Meters:**  
KMOX

**1100 Kilocycles, 272.6 Meters:**  
WPG, WLWL, KGDM

**1110 Kilocycles, 270.1 Meters:**  
WRVA, KSOO

**1120 Kilocycles, 267.7 Meters—Canadian Shared:**  
WTAW, WISN, WHAD, KFSG, KRSC, WDEL, WDBO, KFIO, KTRH, KMSC

**1130 Kilocycles, 265.3 Meters:**  
WOV, KSL, WJJD

**1140 Kilocycles, 263.0 Meters:**  
WAPI, KVOO

**1150 Kilocycles, 260.7 Meters:**  
WHAM

**1160 Kilocycles, 258.5 Meters:**  
WVVA, WOWO

**1170 Kilocycles, 256.3 Meters:**  
WCAU, KTNT

**1180 Kilocycles, 254.1 Meters:**  
KEX, KOB, WHDI, WDGY

**1190 Kilocycles, 252.0 Meters:**  
WICC, WOAI

**1200 Kilocycles, 249.9 Meters—Canadian Shared:**  
WABI, WNBX, WORC, WIBX, WHBC, WLAP, WLBG, WNBO, WKJC, WNBW, WABZ, WJBW, WBBZ, WFBC, WRBL, KGCW, WJBC, WJBL, WVAE, WRAF, KFJB, WCAT, KGDY, KFWF, KGDE, WCLO, WHBY, KSMR, WIL, KVOS, KGY, KGEK, KGEW, KGHL, WCAV, WCOD, WFBE, KBTM, WEHC, WEPS, KMLB, KGJJ, KWG

**1210 Kilocycles, 247.8 Meters—Canadian Shared:**  
WJBI, WGBB, WCOH, WOCL, WLCI, WPAW, WDFE, WLSI, WJW, WBAX, WJBU, WMBG, WSIX, WJBY, WRBO, WGCM, KWEA, KDLR, KGCR, KFOR, WHBU, KFVS, WBEQ, WQDX, WCRW, WEDC, WCBW, WTAX, WHBF, WDMT, WSBG, KDFN, KMJ, KFXM, KPPC, WALR, WBBL, WMRJ, KGMP, KGNO, WSEN, WSOC, WIBU.

**1220 Kilocycles, 245.6 Meters:**  
WCAD, WCAE, WREN, KFKU, WDAE, KWSC

**1230 Kilocycles, 243.8 Meters:**  
WNAC, WBIS, WPSC, WSBT, WFBM, KFQD, KYA, KGGM

**1240 Kilocycles, 241.8 Meters:**  
WACO, KTAT, WXYZ.

**1250 Kilocycles, 239.9 Meters:**  
WGCP, WODA, WAAM, WLB, WGMS, WRHM, KFMX, WCAL, KIDO, KFOX, WDSU

**1260 Kilocycles, 238.0 Meters:**  
WLBW, KWWG, KRGV, KOIL, KVOA, WTOC

**1270 Kilocycles, 236.1 Meters:**  
WEAI, WASH, WOOD, KWLC, KGCA, KTW, KOL, KFUM, WFBR, WJDX

**1280 Kilocycles, 234.2 Meters:**  
WCAM, WCAP, WOAX, WDOD, WRR, KFBB, WIBA

**1290 Kilocycles, 232.4 Meters:**  
WNBZ, WJAS, KTSB, KFUL, KLCN, KDYL, WEBC

**1300 Kilocycles, 230.6 Meters:**  
WBBR, WHAP, WEVD, WHAZ, KFH, KGEF, KTBI, KFJR, KTBR, WIOD, WMBF, WOQ

**1310 Kilocycles, 228.9 Meters:**  
WKAV, WEBR, WNBH, VOL, WGH, WFDG, WHAT, WFBG, WRAW, WGAL, WSAJ, WBRB, WKBC, WGBT, KRMD, KFPM, WDAH, KFEL, KFJR, WKBS, WRBI, WCLS, WKBB, KWCR, KFJY, KFGO, WBOV, WJAK, WLBC, KTSB, KFUP, KFXT, KFBK, KGEZ, KMED, KTSB, KGCX, WJAC, WJSJ, KXRO, KGFU, KFIU, KGBX, KIT, WMBO, KCRJ, KTLG, WEXL, WROL, WTEL.

**1320 Kilocycles, 227.1 Meters:**  
WADC, WSMB, KID, KGIQ, KGHF, KGMB

**1330 Kilocycles, 225.4 Meters:**  
WDRG, WTAQ, KSCJ, WSAI, KGB

**1340 Kilocycles, 223.7 Meters:**  
KFPW, WCOA, KFPY, WSPD

**1350 Kilocycles, 222.1 Meters:**  
WMSG, WCDL, WKBQ, KWK, WAWZ.

**1360 Kilocycles, 220.4 Meters:**  
WQBC, WJKS, WGES, KGIR, KGER, KPSN, WFBL, WCSC.

**1370 Kilocycles, 218.8 Meters:**  
WSVS, WCBM, WHBD, WJKB, WIBM, WRBK, WELK, WHBQ, WRBT, KGGF, KFJZ, KGKL, KFLX, KGDA, KZM, KRE, WPOE, KFBL, KWKC, WRIN, KGAR, KVL, KFIL, KGFL, WHDF, KOOS, WGL, KFJM, KCRG, WMBR, WRBJ, WLEY, WBGF, WBTM, WFDV, WLVA, WQDM, WRDO, KONO, KMAC

**1380 Kilocycles, 217.3 Meters:**  
KQV, KSO, WKBH, WSMK, KOH

**1390 Kilocycles, 215.7 Meters:**  
WHK, KLRA, KUOA, KOY

**1400 Kilocycles, 214.2 Meters:**  
WCGU, WSGH, WSDA, WLTH, WBBC, WCMA, WKBF, KOCW, WBAA, KLO

**1410 Kilocycles, 212.6 Meters:**  
KGRS, W DAG, KFLV, WHBL, WBCM, WODX, WSFA, WLEX, WSSH, WMAF, WRBX.

**1420 Kilocycles, 211.1 Meters:**  
WTBO, WKBI, WJBR, WEDH, WMBG, KCFE, WHIS, KTAP, KFYO, KICK, WIAS, KGGG, WLBF, WMBH, KFIZ, KORE, WILM, KGIW, KGGX, KPOW, KLPAL, KXL, WHDL, WHFC, WEHS, KFOU, KFXD, KGIX, WJBO, WELL, WFDW, WPAD, WSPA, KBPS, KFNX, KXYZ

**1430 Kilocycles, 209.7 Meters:**  
WHP, WCAH, WGBC, WNRB, WBAK, KECA, KGNF

**1440 Kilocycles, 208.2 Meters:**  
WHCC, WABO, WOKO, WCBA, WTAD, WMBD, KLS, WSN, WBIG

**1450 Kilocycles, 206.8 Meters:**  
WBMS, WNJ, WKBO, WSAR, WFJC, WTFI, KTBS, WHOM

**1460 Kilocycles, 205.4 Meters:**  
WJSV, KSTP

**1470 Kilocycles, 204.0 Meters:**  
KGA, WTNT, WLAC

**1480 Kilocycles, 202.6 Meters:**  
KFJF, WKBW

**1490 Kilocycles, 201.6 Meters:**  
WCKY, WJAZ, WCHI

**1500 Kilocycles, 199.9 Meters:**  
WMBA, WLOE, WNBZ, WMBQ, WLBX, WWRL, WKBZ, WMPG, WOPF, WPNB, KGBK, WKBV, KPJM, KDB, KUJ, KGFY, WMBJ, KREG, WCLB, WRDW, KGIZ, KGKY, KPQ, KUT, WDIX, KXO, KGFK.



# U. S. Broadcasting Stations Listed by States

<b>ALABAMA</b> Birmingham, WBRC, WKBO. WAPI Gadsden, WIBY Mobile, WODX Montgomery, WSFA Talladega, WFDW	<b>ALASKA</b> Anchorage, KPQD Juneau, KFIU Ketchikan, KGBU	<b>ARIZONA</b> Flagstaff, KFXV Jerome, KGRJ Phoenix, KTAR, KOY Prescott, KPJM Tucson, KGAR, KVQA	<b>ARKANSAS</b> Fayetteville, KLON Fayetteville, KUOA Fort Smith, KEPW Hot Springs, KTHS Little Rock, KLRA, KGHI, KGJF Paragould, KBTM	<b>CALIFORNIA</b> Berkeley, KRE Berkeley Hills, KMPC Burbank, KFIW Culver City, KFVD El Centro, KXO Fresno, KMI Hayward, KZM Hollywood, KNX, KFWB Holy City, KFOH Inglewood, KMCS Long Beach, KFQX, KGER Los Angeles, KFI, KFSG, KGEF, KGEI, KILI, KTHI, KCCA, KMTR, KTM Oakland, KLS, KIX, KROW Pasadena, KPCC, KPSS Sacramento, KPRB San Bernardino, KFXM San Diego, KFSD, KGB San Francisco, KFRC, KPWI, KJBS, KPQ, KGGG, KYA, KGO, KTAB San Jose, KQW Santa Ana, KREG Santa Barbara, KDB Santa Maria, KSMR Stockton, KGDH, KWG	<b>COLORADO</b> Colorado Springs, KFUM Denver, KFEL, KFUP, KFXX, KOA, KPQF, KLZ Edgewater, KFNJ Fort Morgan, KGEW Greeley, KFRX Pueblo, KGBF Trinidad, KGIW Yuma, KGEK	<b>CONNECTICUT</b> Bridgeport, WICO Hartford, WTIC New Haven, WDRO Storrs, WCAO	<b>DELAWARE</b> Wilmington, WDEL, WILM	<b>DISTRICT OF COLUMBIA</b> Washington, NAA, WMAL, WRC, WOL	<b>FLORIDA</b> Clearwater, WFLA, WSNW Gainesville, WRUF Jacksonville, WJAX Miami, WIOD, WMBF, WQAM Orlando, WDBO Pensacola, WCOA Tampa, WDAE, WMBR	<b>GEORGIA</b> Atlanta, WGST, WSB Augusta, WRDW Columbus, WRBL Macon, WMAZ Rome, WFDY Savannah, WTOO Thomasville, WQDX Tifton, WRBI Toccoa, WTFI	<b>HAWAII</b> Honolulu, KGU, KGMB	<b>IDAHO</b> Boise, KIDO Idaho Falls, KID Nampa, KFXD Pocatello, KSEI Sandpoint, KGIKX Twin Falls, KGIQ	<b>ILLINOIS</b> Carthage, WCAZ	Chicago, KYW, WAAF, WCFL, WCRW, WEDC, WENR, WGES, WKBI, WPCO, WGN, WMAQ, WMBL, WBBM, WSBC, WBCN, WIBO, WJAZ, WJBT, WJLB, WLS, WKFX, WJXD, WCIH Cicero, WIFC Decatur, WJBL Evanston, WEHS Galesburg, WKBS Harrisburg, WBEQ Joliet, WCLS, WKBB La Salle, WJBC Peoria Heights, WMBD Quincy, WTAQ Rockford, KPLV Rock Island, WIFB Springfield, WCBS, WTAX Tuscola, WIZ Urbana, WLL Zion, WGBD	<b>INDIANA</b> Anderson, WHRU Connersville, WKBV Culver, WCMA Evansville, WGRF Fort Wayne, WGL, WWOV Gary, WJKS Hammond, WYAB Indianapolis, WFBM, WKBF Lafayette, WBA La Porte, WRAF Marion, WIAK Muncie, WLBO South Bend, WSBT Terre Haute, WBOW	<b>IOWA</b> Ames, WOI Boone, KPQO Cedar Rapids, KWOB Clarinda, KSO Council Bluffs, KOIL Davenport, WOC Decorah, KGCA, KWLO Des Moines, WHO, Ft. Dodge, KFIY Iowa City, WSIU Marshalltown, KFJB Muscatine, KTNT Ottumwa, WIAS Red Oak, KICK Shenandoah, KENE, KMA Sioux City, KSCJ Waterloo, WMT	<b>KANSAS</b> Dodge City, KGNO Kansas City, WLBF Lawrence, KPKU, WREN Manhattan, KSAC Milford, KPKE Topeka, WIBW Wichita, KFH	<b>KENTUCKY</b> Covington, WCKY Hopkinsville, WETW Louisville, WHAS, WLAP Paducah, WPAD	<b>LOUISIANA</b> Cedar Grove, KGGH Monroe, KMLB New Orleans, WVAR, WCRE, WJBO, WIBW, WSMB, WVL, WDSU Shreveport, KTSL, KWEA, KRMD, KTBS, KWKH	<b>MAINE</b> Augusta, WRDO Bangor, WABI, WLEZ Portland, WCSH	<b>MARYLAND</b> Baltimore, WCAO, WCBM, WBAL, WFB Cumberland, WTBO	<b>MASSACHUSETTS</b> Boston, WBZA, WVEI, WNAC, WSSH, WBIS, WHDH, WLOE Fall River, WSAR Lexington, WLEX, WLEY Needham, WBOS New Bedford, WNRH So. Dartmouth, WMAF Springfield, WBZ Worcester, WTAG, WORC, WEPS	<b>MICHIGAN</b> Battle Creek, WELL Bay City, WBCM Berrien Springs, WKZO Calumet, WHDF Detroit, WMBC, WWJ, WJR, WXYZ	East Lansing, WKAR Flint, WFDF Grand Rapids, WASH, WOOD Highland Park, WSEK Jackson, WIBM Lapeer, WMPQ Ludington, WKBZ Royal Oak, WEXL	<b>MINNESOTA</b> Anoka, WCCO Fergus Falls, KGDE Minneapolis, WDCY, WHDL, WLB, WRHM, WOCO, WGIS Moorhead, KGFK Northfield, KFMX, WCAL St. Paul, KSTP	<b>MISSISSIPPI</b> Greenville, WRBQ Gulfport, WGMG Hattiesburg, WRBJ Jackson, WLD Meridian, WCOO Tupelo, WDX Vicksburg, WQBO	<b>MISSOURI</b> Cape Girardeau, KFVS Columbia, KFRL Grant City, KGIZ Jefferson City, WOS Joplin, WMBH Kansas City, KWKC, WDAF, WOQ, WBB, KMBC St. Joseph, KGEK, KFEQ St. Louis, KFWE, KSD, KWIK, WVEW, WIL, KMIX, KFUO	<b>MONTANA</b> Billings, KGHL Butte, KGIR Great Falls, KFBE Kalispell, KGEZ Wolf Point, KGCO	<b>NEBRASKA</b> Clay Center, KMMJ Lincoln, KFAB, KFOR, WOAJ Norfolk, WJAG North Platte, KGNF Omaha, WAAY, WOW Ravenna, KGEW Scottsbluff, KGKY York, KGBZ	<b>NEVADA</b> Las Vegas, KGIX Reno, KOH	<b>NEW HAMPSHIRE</b> Laconia, WKAV	<b>NEW JERSEY</b> Asbury Park, WCAP Atlantic City, WPG Camden, WCAM Hackensack, WEMS Jersey City, WAAT, WKBO, WHOM Newark, WAAM, WGCP, WNJ, WOR Paterson, WODA Red Bank, WBEI Trenton, WOAX	<b>NEW MEXICO</b> Albuquerque, KGGM Raton, KGFL State College, KOB	<b>NEW YORK</b> Auburn, WMBO Binghamton, WNEF Brooklyn, WBB, WLTH, WSDA, WMBQ, WSGH, WBBR, WCGU Buffalo, WKBV, WBBR, WBYV, WSVS, WMAK Canton, WCAD Freeport, WGRB Glens Falls, WBGF Ithaca, WLOI, WEAJ Jamaica, WMRJ Jamestown, WOCL Long Beach, WCLR Long Island City, WLBS New York, WHN, WJZ, WKRO, WJCA, WMSG, WNYC, WPCB, WRNY, WARC, WOW, WQAO, WLWL, WBOG, WDA, WFAE, WBYD, WGBS, WHAP, WPAF, WAJZ Poughkeepsie, WPOE Poughkeepsie, WOKO Rochester, WHAM, WHEC Saranac Lake, WNEZ Schenectady, WGY	Syracuse, WFBL, WSYR, WMAC Tupper Lake, WHDL Troy, WHAZ Utica, WIBX Woodbaven, WEVD Yonkers, WWRL Yonkers, WCOH	<b>NORTH CAROLINA</b> Asheville, WUNC Charlotte, WPT Gastonia, WSOC Greensboro, WBIG Raleigh, WPTF Wilmington, WRBT Winston-Salem, WSJS	<b>NORTH DAKOTA</b> Bismarck, KFRZ Devils Lake, KDLR Fargo, WDAY Grand Forks, KFJM Mandan, KGO Minot, KLPM	<b>OHIO</b> Akron, WEJC Canton, WHBC Cincinnati, WKRO, WSAI, WLV, WFBE Cleveland, WHK, WJAY, WTAM Columbus, WAIU, WCAH, WLAO, WSEN Dayton, WSAK Mansfield, WJW Middletown, WSRQ Mt. Orab, WHBD Steubenville, WBR Tallmadge, WADO Toledo, WSPD Youngstown, WKBN Zanesville, WALR	<b>OKLAHOMA</b> Alva, KGEF Chickasha, KOCW Elk City, KGPW Elk City, KCRC Norman, WNAD Oklahoma City, KFJF, KFJR, KGOB, KGGF, WKY Ponca City, WBBZ Sallisaw, KGEY, KGGF Tulsa, KVOO	<b>OREGON</b> Astoria, KFJI Corvallis, KOAO Eugene, KORE Marsfield, KOOS Medford, KMED Portland, KBK, KOIN, KFJR, KGW, KTRB, KWJJ, KXL, KPB, KVOO	<b>PENNSYLVANIA</b> Allentown, WGBA, WSN Altoona, WBBG Carbondale, WNBW Elkins Park, WIBG Erie, WEDH Frankford, WFKD Grove City, WSAJ Harrisburg, WCOD, WBAK, WHP Johnstown, WJAC Lancaster, WGAL, WKJC Le Moyne, WHP Lewisburg, WJBU Oil City, WLEW Pittsburgh, WCAU, WFI, WLP, WLIT, WRAX, WPN, WFN, WELK, WHT, WTEL, WSDA, WJAS, KDKA Reading, WRAW Scranton, WGBI, WQAN, Silver Haven, WNBO State College, WPSO Wilkes-Barre, WBAX, WBRE Wilkes-Barre, WBBJ Williamsport, WRBK	<b>PORTO RICO</b> San Juan, WKAQ	<b>RHODE ISLAND</b> Cranston, WDWL Newport, WJBA Pawtucket, WPAW Providence, WEAN, WJAR, WDWL	<b>SOUTH CAROLINA</b> Charleston, WCSC Columbia, WIS Spartanburg, WSPA	<b>SOUTH DAKOTA</b> Brookings, KFDY, KGCR	Huron, KGDY Mitchell, KGDA Pierre, KGEF Rapid City, WCAT Sioux Falls, KSOO Vermillion, KUSD Watertown, KGCR Yankton, WNAX	<b>TENNESSEE</b> Bristol, WOPF Cbatanooga, WODD Knoxville, WFBC, WNOX, WROL Memphis, WGRG, WHBO, WMC, WNBR, WOAN, WREC Nashville, WLAC, WSM, WNTN Springfield, WSIX Union City, WOBT	<b>TEXAS</b> Ableene, KFYO Amarillo, KGRS, WDAG Austin, KUT Beaumont, KFDM Brownsville, KKWG Brownwood, KGBK College Station, WTAW Corpus Christi, KGFI Dallas, KRLD, WFAA, WRR Dublin, KFIJ El Paso, WDAI, KTSM Fort Worth, KFIZ, WBAP, KAT Galveston, KPLN, KFUL Greenville, KTFM Harlingen, KRGV Houston, KPRC, KTLG, KTRH, KXYZ San Angelo, KGFI, KGKL San Antonio, KTAP, KTXA, WOAI, KONO Waco, WACO, KMCC Wichita Falls, KGKO	<b>UTAH</b> Ogden, KLO Salt Lake City, KDYL, KSL	<b>VERMONT</b> Burlington, WCAX St. Albans, WQDM Springfield, WNBX	<b>VIRGINIA</b> Alexandria, WJVS Arlington, NAA Danville, WBTM Emory, WEHC Lynchburg, WLVA Newport News, WGH Norfolk, WTAJ, WFOR Peterborough, WJHG Richmond, WBBJ, WMBG, WRYA Roanoke, WDBJ, WRBX	<b>WASHINGTON</b> Aberdeen, KXRO Bellingham, KYOS Erie, KFBL Everett, KFYI Lacey, KGY Longview, KJY Pulman, KWSC Seattle, KOL, KFOW, KPO, KJR, KOMO, KPGB, KRSC, KTW, KVL, KXA Spokane, KFIO, KFPY, KGA, KHQ Tacoma, KMO, KVI Wenatchee, KPQ Yakima, KIT	<b>WEST VIRGINIA</b> Bluefield, WHBS Charleston, WBOB Fairmont, WMMN Huntington, WSAZ Wheeling, WVA WISCONSIN Bau Claire, WTAQ Fond Du Lac, KFIZ Green Bay, WBBY Janesville, WCLO La Crosse, WKRH Madison, WIA, WIBA Manitowish, WJMT Menasha, WTMJ Milwaukee, WHDH, WISN, WTMJ Poyntelle, WIRU Racine, WRIN Sheboygan, WHBL South Madison, WISJ Stevens Point, WLBI Superior, WBEQ	<b>WYOMING</b> Casper, KDFN
---	---	---	--	---	--	---	---	--	---	---	--------------------------------------	---	-----------------------------------	---	---	---	--	---	---	---	---	---	--	---	---	---	--	---	--	---	---------------------------------------	--	---	---	---	--	--	---	---	---	--	-------------------------------------	---	---	--	--	---	---	--	---	--	--	--	--------------------------------

## FOREIGN BROADCAST STATIONS

Call	Meters	Call	Meters	Call	Meters
<b>ARGENTINA</b>					
LP1 Buenos Aires	476	L87 Buenos Aires	229.2	2KY Sydney	280
LP3 Buenos Aires	545	L88 Buenos Aires	243.8	2UW Sydney	267
LP4 Buenos Aires	448	L89 Buenos Aires	215.8	6WF Perth	435
LP5 Buenos Aires	209.8	L92 La Plata	438	63L Perth	297
LP6 Buenos Aires	509	L93 Rosario	275.3	58L Adelaide	412
LR1 Buenos Aires	380	L94 Mendoza	380	5DN Adelaide	313
LR2 Buenos Aires	344.8	L95 Parana	240	5KA Adelaide	250
LR3 Buenos Aires	315.8	LT6 Mar Del Plata	212.7	5AD Adelaide	229
LR4 Buenos Aires	309	LT8 La Plata	450	4QG Brisbane	394.5
LR5 Buenos Aires	361.5	LV5 Rosario	218.9	4BC Brisbane	233
LR6 Buenos Aires	330			4BK Brisbane	217
LR7 Buenos Aires	400	<b>AUSTRALIA</b>		48K Rockhampton	322
LR8 Buenos Aires	261	7ZL Hobart	516	4GR Toowoomba	294
LR9 Buenos Aires	291.2	3AR Hobart	337	7IA Lannecton	273
LS1 Buenos Aires	425	7HO Melbourne	484	2MK Rathurst	260
LS2 Buenos Aires	252.1	3LO Melbourne	375	4CH Charleville	256
LS3 Buenos Aires	236.2	3FZ Melbourne	322	4MK Mackay	252
LS4 Buenos Aires	270.4	3DB Melbourne	255	2NC Newcastle	241
LS5 Buenos Aires	280.5	2B Sydney	451	2HD Newcastle	212
LS6 Buenos Aires	220.4	2FC Sydney	350	4RO Newcastle	238
		2GB Sydney	316	3WR Wangaratta	238
		2UE Sydney	293	3TR Trafalgar	234

Call	Meters
3BA	Ballarat 231
2AY	Albury 227
3AX	Carlton 222
3KZ	Lismore 224
3GL	Geelong 214
3BO	Bendigo 207
2MV	Moss Vale 205.4
2GN	Goulburn 201.3
2MO	Gunnedah 200
2CA	Canberra 285

AUSTRIA

Graz	352
Innsbruck	283
Innsbruck	218
Klagenfurt	453
Linz	246
Vienna	517

BELGIUM

ON4ED	Anvers 250
ON4GT	Bruxells 260
ON4RB	Bruxells 508.5
ON4RC	Bruxells 215
ON4FO	Bruxells 589.4
ON4CE	Chatelineau 220
ON4FG	Dampreny 210
ON4RG	Gand 275
ON4RW	Liège 280
ON4BQ	Marchienne-Docherie 290
ON4EX	Orchomont 225
ON4CF	Verriers 215

BOLIVIA

La Paz	175
La Paz	300

BRAZIL

PRAM	Amparo 470
PRAH	Bahia 445
PRAN	Curytiba 340
PRAZ	Franca 270
PRAJ	Juiz de Fora 350
PRAY	Mogy das Cruzes 300
PRAD	Pelotas 326
PRAG	Porto Alegre 275
PRAF	Recem, Para 350
PRAP	Recife 400
PRAI	Ribeirao Preto 280
PRAA	Rio de Janeiro 400
PRAE	Rio de Janeiro 320
PRAC	Rio de Janeiro 350
PRAK	Bio de Janeiro 260
PRAF	Rio de Janeiro 220
PRAS	Santos 338
PRAE	Sao Paulo 398
PRAR	Sao Paulo 298
	Campinas 256

BRITISH COLONIES

TAW	Hamilton, Bermuda 545
ZWV	Victoria Peak, Hong Kong 350
7LO	Narobi 90
1SE	Singapore 350

BRITISH INDIA

VTUB	Bombay 357.1
VTC	Calcutta 370.4
VCA	Calcutta 370.8
VPB	Colombo 480
VUR	Rangoon 398

CANAL ZONE

NBA	Panama 355
-----	------------

CANADA

CKX	Brandon 556
CFNC	Calgary 435
CFJC	Calgary 435
CHCA	Calgary 435
CFAC	Calgary 435
CHCK	Charlottetown 313
CFYQ	Charlottetown 313
CFPO	Chatham 246
CHVK	Chilliwack 246
CFMC	Coquitlam 246
CFRW	Fleming 500
CFNB	Fredericton 246
CHMA	Edmonton 517
CKUA	Edmonton 517
CFCA	Edmonton 323
CNRE	Edmonton 323
CHNS	Halifax 323
CHRH	Halifax 323
CHCS	Hamilton 341
CIDL	Hamilton 341
CKOC	Hamilton 341
CFCH	Iroquois Falls 500
CFJC	Kamloops 268
CFRC	Kingston 323
CFRE	King, York Co. 313
CNFX	King, York Co. 323
CFQC	Leffbridge 268
CFGC	London 330
CNRL	London 330
CNRA	Moncton 476
CKPR	Midland 323
CFCF	Montreal 291
CKAC	Montreal 411
CFYC	Montreal 411
CNBM	Montreal 411
CFRM	Moose Jaw 500
CHVC	Pilot Butte 313
CFLC	Prescott 297
CKPC	Preston 246
CKCO	Ottawa 500
CNRO	Ottawa 500
CFQC	Quebec 341
CKYJ	Quebec 341
CKVY	Quebec 341
CNRO	Quebec 341
CNRD	Red Deer 357
CKLD	Red Deer 357
CHCT	Regina 313
CFCK	Regina 313
CHBR	Regina 313
CNRR	Regina 313
CFQC	Saskatoon 330
CNRS	Saskatoon 330
CFOR	Sea Island 327
CFRO	St. John 246
CNRS	Summerside 268
CFCB	Sydney 341
CNRT	Toronto 357
CFCA	Toronto 357
CKOW	Toronto 357
CKGW	Toronto 435
CFBC	Toronto 435
CFRC	Toronto 435
CKCL	Toronto 517
CKNC	Toronto 517

Call	Meters
CFCL	Toronto 517
CNRY	Vancouver 411
CKCD	Vancouver 411
CHLS	Vancouver 411
CKFC	Vancouver 411
CKMO	Vancouver 411
CKWK	Vancouver 411
CFCT	Victoria 476
CKCR	Waterloo 297
CKY	Winnipeg 385
CNRW	Winnipeg 385
CKYI	Wentzville 323
CFJX	Yorkton 476

CHILE

CMAO	Antofagasta
	Asuncion 345
CMAI	Concepcion 320
CMAJ	Santiago 280
CMAE	Santiago 498
CMAF	Santiago 365
CMAH	Santiago 400
CMAI	Tacna 550
CMAK	Temuco 245
	Valparaiso 400

CHINA

COHB	Harbin 445
COMK	Mukden 425
	Shanghai 342
XGAH	Shanghai 328
XOL	Tientsin 480
GEC	Tientsin 280

COSTA RICA

NRH	Heredia 306
TIC	Sau Jose 340

CUBA

CMHD	Caibarien 325
CMJC	Camaguey 227
CMJA	Camaguey 225
CMHF	Camajuani 200
CMGE	Cardenas 218
CMJB	Ciego de Avila 234
CMJD	Ciego de Avila 193
CMHA	Cienfuegos 260
CMHE	Cifuentes 345
CMGA	Colou 360
CMCG	Guanabacoa 244.7
CMCT	Guanabacoa 201.6
CMAA	Guanajay 275
CMBH	Havana 201.6
CMBP	Havana 201.6
CMBL	Havana 201.6
CMCM	Havana 201.6
CMBE	Havana 213.4
CMBY	Havana 213.4
CMBI	Havana 213.4
CMBA	Havana 222.9
CMCD	Havana 222.9
CMCS	Havana 222.9
CMCF	Havana 222.9
CMCU	Havana 222.9
CMGR	Havana 233.4
CMRJ	Havana 233.4
CMCY	Havana 223
CMGE	Havana 233.4
CMBM	Havana 233.4
CMCW	Havana 244.7
CMCA	Havana 244.7
CMBX	Havana 233
CMCE	Havana 233
CMCR	Havana 244.7
CMQ	Havana 244.7
CMCN	Havana 244.7
CMBC	Havana 263.3
CMBT	Havana 280.3
CMCB	Havana 280.3
CMCC	Havana 280
CMCZ	Havana 296.8
CMBD	Havana 313.8
CMCK	Havana 313.8
CMCQ	Havana 314
CMX	Havana 333.1
CMCF	Havana 333.1
CMC	Havana 245.8
CMBS	Havana 379.5
CMK	Havana 410.8
CMW	Havana 510
CMRN	Las Pinos 213.4
CMCO	Marianao 244.7
CMBK	Marianao 233
CMFM	Marianao 233
CMBN	Marianao 296.8
CMBY	Marianao 213
CMCF	Matanzas 286
CMGC	Matanzas 286
CMGD	Matanzas 263
CMGB	Matanzas 263
CMAE	Pinar del Rio 240
CMRE	Beparto Poey 213.4
CMIB	Sagua la Grande 200
CMHE	Santa Clara 210
CMHI	Santa Clara 270
CMKA	Santiago de Cuba 205
CMKB	Santiago de Cuba 250
CMKC	Santiago de Cuba 231
CMKD	Santiago de Cuba 273
CMBG	Santiago de las Vegas 280
CHMC	Tunucio 379

CZECHOSLOVAKIA

OKR	Bratislava 279
OKB	Brno 342
	Kosice 293
	Moravska-Ostrava 263
OKP	Praha 487
	Praha 250

DANZIG

Danzig	453
--------	-----

DENMARK

Kalundborg	1153.8
Kobenhavn	281
Soro	1153.8

DOMINICAN REPUBLIC

HIX	Santo Domingo 448
-----	-------------------

DUTCH EAST INDIES

PFC	Batavia 220.7
PLE	Bandoeng 31.86
PLB	Bandoeng 15.93
	Bandoeng 310
PLF	Malabar 17
	Surabaya 140

EGYPT

SRE	Cairo 255
-----	-----------

Call	Meters
	<b>ESTONIA</b>
Tallinn	401
Tartu	285
	<b>FINLAND</b>
OFA	Helsinki 221
OFC	Jakobstad 291
OFB	Lahti, Suomi 1796
OFD	Pori 218
OFE	Tampere 453
OFG	Turku 246
OFH	Viipturi 291

FRANCE

PTT	Bordeaux-Lafayette 304.3
	Ecole Supérieure 447
	Grenoble 328.2
	Lille 265.5
	Limoges 293.6
	Lyon La-Doua 465.8
	Marseille 315.3
	Montpellier 286
	Petit Parisien 326
	Radio-Agen 311.5
	Radio-Beziers 212
	Radio Juan-les-Pins 248
	Radio L. L. 265.1
	Radio Lyon 238.8
	Radio-Mont-de-Marsan 400
	Radio-Montpellier 250.1
	Radio-Nimes 240
	Radio Normandie 213.5
	Radio-Paris 1724
	Radio-Sud-Ouest 237.2
	Radio Toulouse 232.7
	Eiffel 1444
	Radio Vitus 309
	Rennes 22
	Strasbourg 345.2
	Toulouse-Pyrenees 255.3

FRENCH COLONIES

SDB	Algiers 363.7
SKR	Constantine 42.8
	Haiphong 320
	Radio S. Denis, Reunion 500
TUA	Tunis 1450

GERMANY

Aachen	453
Augsburg	560
Berlin I	419
Berlin II	284
Bremen	319
Breslau	325
Dresden	319
Flensburg	319
Frankfurt	390
Freiburg	569
Gleitwitz	253
Hamburg	372
Hanover	560
Kaiserslautern	270
Kassel	546
Kiel	246
Koln	227
Konigsberg	276
Konigswusterhausen	1635
Langenberg	473
Leipzig	259
Magdeburg	283
Muncheberg	533
Munster	234
Nordeich	1630
Nurnberg	239
Stettin	283
Stuttgart	360
Zeeseen	1635

GREAT BRITAIN

2BD	Aberdeen 301
2BE	Belfast 242
6BM	Bournemouth 288.5
2LS	Bradford 288.5
5WA	Cardiff 310
5GB	Daventry 479
5XX	Daventry 1553
2DE	Dundee 288.5
2EH	Edinburgh 288.5
5SC	Glasgow 399
6RH	Hull 288.5
2LS	Leeds-Bradford 288.5
6LV	Liverpool 356
2LO	London 356
2LY	Manchester 377
5NO	Newcastle 261
5PY	Plymouth 288.5
6ST	Sheffield 288.5
6ST	Stoke-on-Trent 288.5
5SX	Swansea 288.5

HAITI

HHK	Port au Prince 326
-----	--------------------

GUATEMALA

TGW	Guatemala 525
-----	---------------

HOLLAND

HDO	Bloemendaal 245.9
	Hilversum 1071
	Hilversum 298
	Huizen 1875
	Scheveningen 1071

HUNGARY

	Lakihegy 550
--	--------------

ICELAND

	Akureyri 192
	Reykjavik 192

IRISH FREE STATE

6CK	Cork 225
2BN	Dublin 413

ITALY

IRO	Bolzano 445.9
IGE	Genoa 385.1
IMI	Milan 500.8
INA	Naples 331.4
	Palermo 209.8
IRO	Rome 441.1
ITO	Torino 275.2
	Trieste 256.4

JAPAN

JOAK	Dairen 395
JOEK	Hiroshima 353
JOJK	Kanazawa 423
JOKE	Kobe 366
JOJK	Kumamoto 380
JOEK	Nagoya 370
JOEK	Osaka 400
JOJK	Sapporo 361
JOHK	Sendai 390
JOAK	Tokyo 345

Table of international radio call letters and frequencies. Columns include Call, Meters, and Country. Countries listed include Yugoslavia, Latvia, Lithuania, Mexico, Monaco, Morocco, New Zealand, Norway, Peru, Philippines Islands, Poland, Portugal, Roumania, Salvador, Spain, Sweden, Switzerland, Turkey, Union of Soviet Socialist Republics, Uruguay, and Venezuela.

SHORT WAVE RELAY BROADCASTING STATIONS

Table of short wave relay broadcasting stations. Columns include Call, Owner, Kilocycles, Meters, and Kilocycles. Stations are categorized by United States and Foreign locations.

VISUAL BROADCASTING STATIONS

Table of visual broadcasting stations. Columns include Call, Kilocycles, Meters, and Owner. Lists various stations and their respective frequencies and owners.

AIR-LINE DISTANCES IN STATUTE MILES


FROM/TO	Albuquerque, N. Mex.	Atlanta, Ga.	Baltimore, Md.	Boise, Idaho	Boston, Mass.	Brownsville, Tex.	Buffalo, N. Y.	Chicago, Ill.	Cincinnati, Ohio	Cleveland, Ohio	Denver, Colo.	Des Moines, Iowa	Detroit, Mich.	El Paso, Tex.	Fargo, N. Dak.	Fort Worth, Tex.	Galveston, Tex.	Hastings, Nebr.	Hot Springs, Ark.	Houghton, Mich.	Jacksonville, Fla.	Kansas City, Mo.	Los Angeles, Calif.	Louisville, Ky.	Memphis, Tenn.
Albuquerque, N. Mex.	1273	1273	1670	774	1967	838	1577	1126	1248	1417	332	833	1360	228	968	561	803	588	773	1252	1492	717	663	1174	938
Atlanta, Ga.	1273	1273	575	1830	933	960	695	583	368	550	1208	738	595	1293	1112	750	688	901	498	947	286	675	1935	317	335
Baltimore, Md.	1670	575	1670	2055	358	1525	273	603	423	305	1239	913	398	1750	1143	1239	1245	1154	964	808	2098	962	2313	498	792
Boise, Idaho	774	1830	2055	774	2266	1610	1872	1453	1663	1754	637	1155	1671	969	975	1263	1538	934	1384	1367	2098	1158	663	1623	1506
Boston, Mass.	1967	933	358	2266	1967	1881	398	849	737	550	1766	1159	613	2067	1304	1574	1598	1415	1302	922	1015	1250	2590	823	1133
Brownsville, Tex.	838	960	1525	1610	1881	1881	1575	1234	1184	1402	1047	1102	1398	682	1445	471	287	1013	650	1543	1025	923	1370	1093	777
Buffalo, N. Y.	1577	695	273	1872	398	1575	695	454	392	175	1368	762	216	1690	923	1221	1239	1019	956	560	880	862	2195	463	802
Chicago, Ill.	1126	583	603	1453	849	1234	454	454	249	307	918	310	236	1249	571	820	954	566	585	367	861	413	1741	268	481
Cincinnati, Ohio	1248	368	423	1663	737	1184	392	249	218	218	1090	509	234	1333	818	839	897	742	569	589	628	541	1892	92	410
Cleveland, Ohio	1417	550	305	1754	550	1402	175	307	218	218	1223	617	94	1521	838	1046	1116	871	787	518	768	700	2044	309	627
Denver, Colo.	332	1208	1505	637	1766	1047	1368	918	1090	1223	607	1153	554	642	642	643	925	353	749	970	1468	555	828	1035	878
Des Moines, Iowa	833	738	913	1155	1159	1102	762	310	509	617	607	545	980	397	745	640	851	256	488	458	1024	180	1433	477	485
Detroit, Mich.	1360	595	398	1671	613	1398	218	236	234	94	1153	545	1475	745	745	1018	1111	800	761	427	832	643	1976	315	621
El Paso, Tex.	228	1293	1750	969	2067	682	1690	1249	1333	1521	554	980	1475	1161	1161	543	723	757	302	1422	1481	836	702	1253	978
Fargo, N. Dak.	968	1112	1143	975	1304	1445	923	571	818	838	642	397	745	1161	1161	973	1218	440	875	393	1400	548	1436	818	832
Fort Worth, Tex.	561	750	1239	1263	1574	471	1221	820	839	1046	643	640	1018	543	973	943	799	544	273	1093	943	460	1212	751	448
Galveston, Tex.	803	688	1245	1538	1598	287	1289	954	897	1116	925	851	1111	723	1218	283	677	226	326	633	799	677	1423	807	492
Hastings, Nebr.	588	901	1154	934	1415	1013	1019	566	742	871	353	256	800	757	440	544	808	513	666	901	1178	226	1177	693	591
Hot Springs, Ark.	773	498	964	1384	1302	650	956	585	569	787	749	488	761	802	875	273	375	513	901	901	1178	326	1437	480	176
Houghton, Mich.	1252	947	808	1367	922	1543	560	367	589	518	970	458	427	1422	393	1093	1277	666	901	901	1216	633	1787	636	830
Jacksonville, Fla.	1492	286	682	2098	1015	1025	880	861	628	768	1468	1024	832	1481	1400	943	799	1178	728	1216	943	460	1212	751	448
Kansas City, Mo.	717	635	962	1158	1250	923	862	413	541	700	555	180	643	836	548	460	677	226	326	633	799	677	1423	807	492
Los Angeles, Calif.	663	1935	2313	663	2590	1370	2195	1741	1892	2044	828	1433	1976	702	1426	1212	1423	1177	1437	1787	2070	1117	910	1550	1483
Louisville, Ky.	1174	317	498	1623	823	1093	483	268	92	309	1035	477	315	1253	818	751	807	693	480	636	1178	226	1177	693	591
Memphis, Tenn.	938	335	792	1506	1133	777	887	831	708	922	878	485	621	978	882	448	492	591	176	830	1216	633	1787	636	830
Miami, Fla.	1492	286	682	2098	1015	1025	880	861	628	768	1468	1024	832	1481	1400	943	799	1178	728	1216	943	460	1212	751	448
Minneapolis, Minn.	980	905	1140	1125	1258	923	862	413	541	700	555	180	643	836	548	460	677	226	326	633	799	677	1423	807	492
Missoula, Mont.	895	1790	1947	232	2124	1706	1740	1348	1578	1640	670	1074	1552	1115	819	1312	1595	891	1385	208	2070	1117	910	1550	1483
Nashville, Tenn.	1117	218	597	1631	941	952	626	394	239	456	1018	523	468	1169	900	643	666	697	370	760	502	472	1777	153	195
New Orleans, La.	1030	427	1001	1713	1359	536	1087	831	708	922	1079	825	938	986	1221	470	288	870	358	1187	511	678	1675	623	358
New York, N. Y.	1810	747	170	2153	188	1695	291	711	568	404	1628	1023	483	1902	1213	1398	1415	1275	1125	849	838	1097	2446	650	953
Norfolk, Va.	1696	507	167	2137	467	1465	435	696	474	429	1562	983	522	1755	1258	1226	1195	1216	955	946	548	1009	2352	528	778
Oklahoma, Okla.	518	753	1173	1138	1490	659	1117	689	755	946	503	469	905	578	786	188	456	357	260	926	988	293	1182	675	422
Omaha, Nebr.	718	815	1026	1044	1280	1061	883	432	620	738	485	122	666	875	390	590	828	135	490	547	1098	165	1312	579	529
Philadelphia, Pa.	1748	663	90	2113	268	1614	278	664	501	343	1575	972	444	1834	1186	1324	1335	1222	1051	827	758	1037	2388	580	878
Phoenix, Ariz.	330	1592	2002	733	2295	1023	1904	1451	1578	1745	585	1154	1685	347	1225	858	1065	901	1094	1550	1800	1045	357	1512	1264
Pittsburgh, Pa.	1498	520	194	1863	478	1424	178	411	258	115	1320	718	208	1592	952	1097	1140	967	825	630	703	784	2135	345	660
Portland, Me.	2015	1022	446	2282	100	1961	438	892	802	603	1803	1197	657	2126	1313	1642	1678	1454	1371	924	1113	1300	2631	892	1205
Portland, Ore.	1107	2172	2367	340	2553	1944	2167	1765	1987	2063	985	1479	1975	1286	1248	1612	1885	1271	1733	1638	2442	1397	825	1953	1852
Richmond, Va.	1628	470	128	2060	471	1428	375	618	399	353	1488	905	445	1695	1180	1170	1154	1142	897	870	953	937	2283	457	722
St. Louis, Mo.	938	467	731	1389	1036	975	662	259	308	490	793	270	452	1033	658	568	697	455	325	591	755	238	1585	242	242
Salt Lake City, Utah	483	1580	1858	292	2099	1317	1701	1260	1450	1567	372	952	1490	689	865	977	1249	708	1116	1242	1840	922	577	1400	1250
San Francisco, Calif.	893	2133	2451	516	2696	1675	2298	1855	2037	2163	946	1547	2087	993	1447	1454	1693	1297	1648	1833	2375	1500	345	1983	1800
Schenectady, N. Y.	1823	840	278	2120	150	1770	249	702	605	408	1618	1012	467	1930	1157	1445	1487	1267	1175	776	960	1107	2445	1945	1010
Seattle, Wash.	1178	2180	2341	405	2508	2015	2130	1743	1974	2035	1020	1470	1945	1373	1206	1658	1938	1288	1759	1588	2450	1505	956	1945	1867
Shreveport, La.	764	548	1064	1433	1410	510	1080	725	688	904	799	624	891	752	1002	209	233	615	142	1043	733	326	1420	598	279
Spokane, Wash.	1028	1960	2110	290	2279	1852	1900	1514	1746	1804	827	1243	1715	1238	976	1470	1753	1061	1552	1360	2239	1286	939	1720	1652
Springfield, Mass.	1889	863	282	219																					

AIR-LINE DISTANCES IN STATUTE MILES


FROM/TO	Miami, Fla.	Minneapolis, Minn.	Missoula, Mont.	Nashville, Tenn.	New Orleans, La.	New York, N. Y.	Norfolk, Va.	Oklahoma, Okla.	Omaha, Nebr.	Philadelphia, Pa.	Phoenix, Ariz.	Pittsburgh, Pa.	Portland, Me.	Portland, Ore.	Richmond, Va.	St. Louis, Mo.	Salt Lake City, Utah	San Francisco, Calif.	Schenectady, N. Y.	Seattle, Wash.	Shreveport, La.	Spokane, Wash.	Springfield, Mass.	Vermillion, S. Dak.	Washington, D. C.
Albuquerque, N. Mex.	1710	980	895	1117	1030	1810	1696	518	718	1748	330	1498	2015	1107	1628	938	483	893	1823	1178	764	1028	1889	742	1648
Atlanta, Ga.	610	905	1790	218	427	747	507	753	815	663	1592	520	1022	2172	470	467	1580	2133	840	2180	548	1960	863	917	542
Baltimore, Md.	958	948	1947	597	1001	170	167	1173	1026	90	2202	194	446	2367	128	731	1858	2451	278	2341	1064	2110	282	1083	33
Boise, Idaho	2368	1140	252	1631	1713	2153	2137	1138	1044	2113	733	1863	2282	349	2060	1389	292	516	2120	405	1433	290	2196	973	2045
Boston, Mass.	1258	1125	2124	941	1359	188	467	1490	1280	268	2295	478	100	2553	471	1036	2099	2696	150	2508	1410	2279	79	1314	392
Brownsville, Tex.	1100	1335	1706	952	536	1695	1465	659	1061	1614	1023	1424	1961	1944	1428	975	1317	1675	1770	2015	510	1852	1805	1161	1493
Buffalo, N. Y.	1184	733	1740	626	1087	291	435	1117	883	278	1904	178	438	2167	375	662	1701	2298	249	2130	1080	1900	325	916	290
Chicago, Ill.	1190	356	1348	394	831	711	696	689	432	664	1451	411	892	1765	618	250	1260	1855	702	1743	725	1514	774	479	594
Cincinnati, Ohio	957	603	1578	239	708	568	474	755	620	501	1578	238	802	1987	399	308	1450	2037	605	1974	688	1746	659	694	403
Cleveland, Ohio	1088	632	1640	456	922	404	429	946	738	343	1745	115	603	2063	353	490	1567	2163	408	2035	904	1804	473	785	303
Denver, Colo.	1732	699	670	1018	1079	1628	1562	503	485	1575	585	1320	1803	985	1488	793	372	946	1618	1020	799	827	1692	468	1490
Des Moines, Iowa	1338	235	1074	523	825	1023	983	469	122	972	1154	718	1197	1479	905	270	952	1547	1012	1470	624	1243	1085	187	895
Detroit, Mich.	1156	542	1552	468	938	483	522	905	666	444	1685	208	657	1975	445	452	1490	2087	467	1945	891	1715	540	705	397
El Paso, Tex.	1662	1156	1115	1169	986	1902	1755	578	875	1834	347	1592	2126	1286	1695	1033	689	993	1930	1373	752	1238	1990	920	1726
Fargo, N. Dak.	1721	219	819	900	1221	1213	1258	786	390	1186	1225	932	1312	1248	1180	658	865	1447	1157	1206	1002	976	1240	284	1141
Fort Worth, Tex.	1150	870	1312	643	470	1398	1226	188	590	1324	858	1097	1642	1612	1170	568	977	1454	1445	1658	209	1470	1495	689	1210
Galveston, Tex.	941	1087	1595	666	288	1415	1195	456	828	1335	1065	1140	1678	1885	1154	697	1249	1693	1487	1938	233	1753	1524	938	1214
Hastings, Nebr.	1468	399	891	697	870	1275	1216	357	135	1222	901	967	1454	1217	1142	455	708	1297	1267	1288	615	1061	1340	167	1139
Hot Springs, Ark.	983	722	1385	370	358	1125	955	260	490	1051	1094	825	1371	1733	897	325	1116	1648	1175	1759	142	1552	1224	605	936
Houghton, Mich.	1345	272	1208	760	1187	849	946	926	547	827	1550	630	924	1638	870	591	1242	1833	776	1588	1043	1360	860	510	813
Jacksonville, Fla.	328	1192	2070	502	511	838	548	988	1098	758	1800	703	1113	2442	953	755	1840	2375	960	2450	733	2239	957	1203	647
Kansas City, Mo.	1247	413	1117	472	678	1097	1009	293	165	1037	1045	784	1300	1397	937	238	922	1500	1107	1505	326	1286	1173	280	943
Los Angeles, Calif.	2355	1522	910	1777	1675	2446	2352	1182	1312	2388	357	2135	2631	825	2283	1585	577	345	2445	956	1420	939	2515	1291	2295
Louisville, Ky.	923	605	1550	153	623	650	528	675	579	580	1512	345	892	1953	457	242	1400	1983	695	1945	598	1720	745	663	473
Memphis, Tenn.	878	700	1483	195	358	953	778	422	529	878	1264	660	1205	1852	722	242	1250	1800	1010	1867	279	1652	1055	642	763
Miami, Fla.	1516	2359	821	681	681	1095	802	1233	1402	1023	1998	1014	1357	2716	831	1067	2098	2603	1229	2740	950	2528	1210	1510	927
Minneapolis, Minn.	1516	1010	1010	695	1050	1019	1047	692	291	985	1279	745	1445	1435	968	464	988	1585	975	1403	859	1173	1056	238	936
Missoula, Mont.	2359	1010	1582	1733	1733	2030	2045	1162	978	1997	932	1754	2133	430	1967	1331	435	762	1978	395	1457	170	2060	887	1940
Nashville, Tenn.	821	695	1582	470	470	758	586	602	604	683	1445	472	1015	1970	526	253	1390	1958	820	1973	470	1752	863	704	567
New Orleans, La.	681	1050	1733	470	470	1173	932	575	845	1090	1318	923	1445	2063	899	599	1433	1923	1259	2098	280	1898	1287	960	968
New York, N. Y.	1095	1019	2030	758	1173	2142	2027	843	1032	2079	2142	313	277	2455	287	873	1972	2568	142	2419	1230	2190	120	1189	204
Norfolk, Va.	802	1047	2045	586	932	293	1186	1095	220	2079	1829	316	565	2458	79	771	1925	2510	426	2440	1037	2211	411	1166	145
Oklahoma, Okla.	1233	692	1162	602	575	1324	1186	405	405	1256	1829	316	565	2458	79	456	862	1386	1354	1523	297	1324	1412	502	1150
Omaha, Nebr.	1402	291	978	604	845	1144	1095	405	1094	1094	1032	837	1318	1373	1020	352	833	1425	1133	1372	617	1149	1205	115	1012
Philadelphia, Pa.	1023	985	1997	683	1090	83	220	1256	1094	1094	2079	254	360	2419	205	808	1923	2518	205	2388	1153	2159	201	1143	122
Phoenix, Ariz.	1998	1279	932	1445	1318	2142	2027	843	1032	2079	1829	313	277	2455	287	1270	504	652	2152	1112	1067	1020	2220	1043	1980
Pittsburgh, Pa.	1014	745	1754	472	923	313	316	1013	837	254	1829	316	565	2458	79	561	1670	2264	350	2145	939	1918	400	891	188
Portland, Me.	1357	1145	2133	1015	1445	277	565	1550	1318	360	2345	545	545	2563	565	1094	2127	2725	197	2513	1484	2285	159	1345	480
Portland, Ore.	2716	1435	430	1970	2063	2455	2458	1488	1373	2419	1007	2174	2563	2381	2381	1723	636	536	2405	143	1783	295	2488	1293	2360
Richmond, Va.	831	968	1967	526	899	287	79	1122	1020	205	1960	242	565	2381	2381	699	1850	2436	406	2362	985	2133	407	1089	96
St. Louis, Mo.	1067	464	1331	253	599	873	771	456	352	808	1270	561	1094	1723	699	466	1158	1738	898	1722	466	1500	958	450	710
Salt Lake City, Utah	2098	988	435	1390	1433	1972	1925	862	833	1923	504	1670	2127	636	1850	1158	582	592	1950	697	1155	548	2027	785	1845
San Francisco, Calif.	2603	1585	762	1958	1923	2568	2510	1386	1425	2518	652	2264	2725	536	2436	1738	582	592	2548	680	1655	730	2625	1383	2437
Schenectady, N. Y.	1229	975	1978	820	1259	142	426	1354	1133	205	2152	350	197	2405	406	989	1950	2548	2363	2363	1290	2139	86	1165	313
Seattle, Wash.	2740	1403	395	1973	2098	2419	2440	1523	1372	2388	1112	2145	2513	143	2362	1722	697	680	2363	2363	1820	229	2445	1282	2335
Shreveport, La.	950	859	1457	470	280	1230	1037	297	617	1153	1067	939	1484	1783	985	466	1155	1655	1290	1820	466	1500	958	450	710
Spokane, Wash.	2528	1173	170	1752	1898	2190	2211	1324	1149	2159	1020	1918	2285	295	2133	1500	548	730	2139</						

KC	Meters	STATIONS	DIALS		KC	Meters	STATIONS	DIALS	
			1	2				1	2
1500	199.9				1020	293.9			
1490	201.2				1010	296.9			
1480	202.6				1000	299.8			
1470	204.0				990	302.8			
1460	205.4				980	305.9			
1450	206.8				970	309.1			
1440	208.2				960	312.3			
1430	209.7				950	315.6			
1420	211.1				940	319.0			
1410	212.6				930	322.4			
1400	214.2				920	325.9			
1390	215.7				910	329.5			
1380	217.3				900	333.1			
1370	218.8				890	336.9			
1360	220.4				880	340.7			
1350	222.1				870	344.6			
1340	223.7				860	348.6			
1330	225.4				850	352.7			
1320	227.1				840	356.9			
1310	228.9				830	361.2			
1300	230.6				820	365.6			
1290	232.4				810	370.2			
1280	234.2				800	374.8			
1270	236.1				790	379.5			
1260	238.0				780	384.4			
1250	239.9				770	389.4			
1240	241.8				760	394.5			
1230	243.8				750	399.8			
1220	245.8				740	405.2			
1210	247.8				730	410.7			
1200	249.9				720	416.4			
1190	252.0				710	422.3			
1180	254.1				700	428.3			
1170	256.3				690	434.5			
1160	258.5				680	440.9			
1150	260.7				670	447.5			
1140	263.0				660	454.3			
1130	265.3				650	461.3			
1120	267.7				640	468.5			
1110	270.1				630	475.9			
1100	272.6				620	483.6			
1090	275.1				610	491.5			
1080	277.6				600	499.7			
1070	280.2				590	508.2			
1060	282.8				580	516.9			
1050	285.5				570	526.0			
1040	288.3				560	535.4			
1030	291.1				550	545.1			

# PICTORIAL RADIO

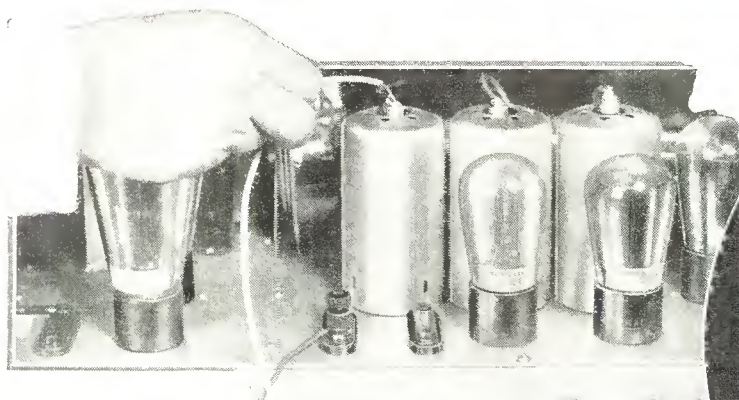

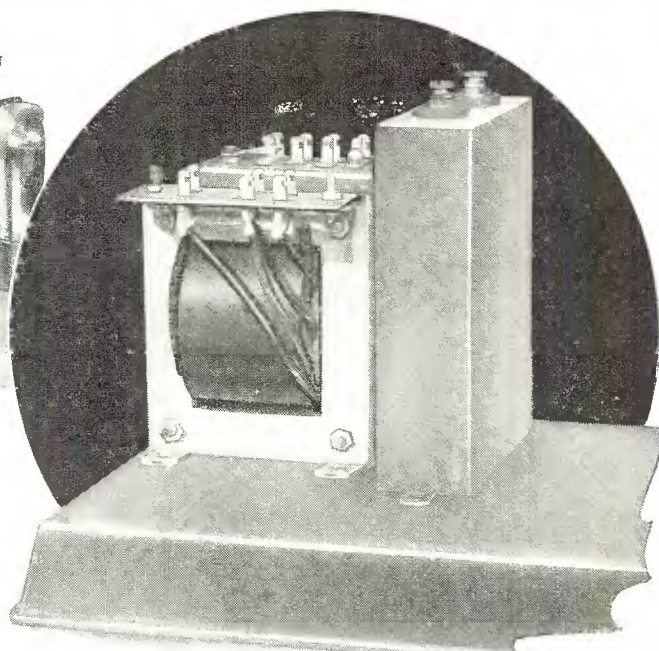
A quick test to determine location of trouble when receiver signals are weak, or the set dead, is to remove the antenna lead, and alternately tap it on the last r. f., second r. f. and then first r. f. Increased signal at any position will indicate trouble is ahead of that stage




The dime store again comes in handy. An aluminum cake pan (you can get 'em in all sizes and shapes) can be used as a mounting for a power supply, as shown in the picture. Underneath all resistors, small condensers, etc., may be mounted



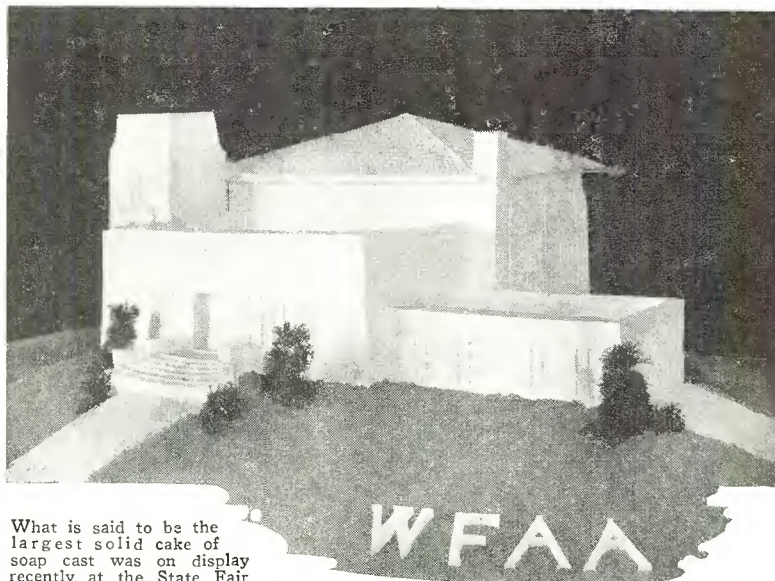
Engravers' wax may be used when it is desired to revive lettering or figures on instrument panels. Simply scrape out the old lettering with a fine pointed instrument, and refill the engraving cavities with the wax. The photograph shows how



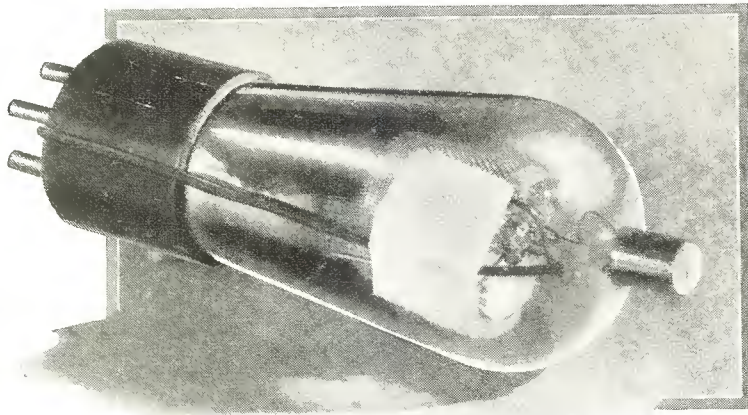What is said to be the largest solid cake of soap cast was on display recently at the State Fair of Texas, the handiwork of 15 year old Mike Owen, Jr. More than 7000 pounds of soap were used. It is a replica of station WFAA owned by the Dallas News




Hark ye DX hounds! How to increase (for fishing purposes) the sensitivity of your screen grid receiver. Run a very fine wire from the plate terminal up the side of the tube to within a short distance of the cap. Glue it down with tape. The proximity of the wire to the cap will govern the amount of regeneration increase of that 224 tube. This scheme is only good when used on a receiver having either cathode or screen volume control

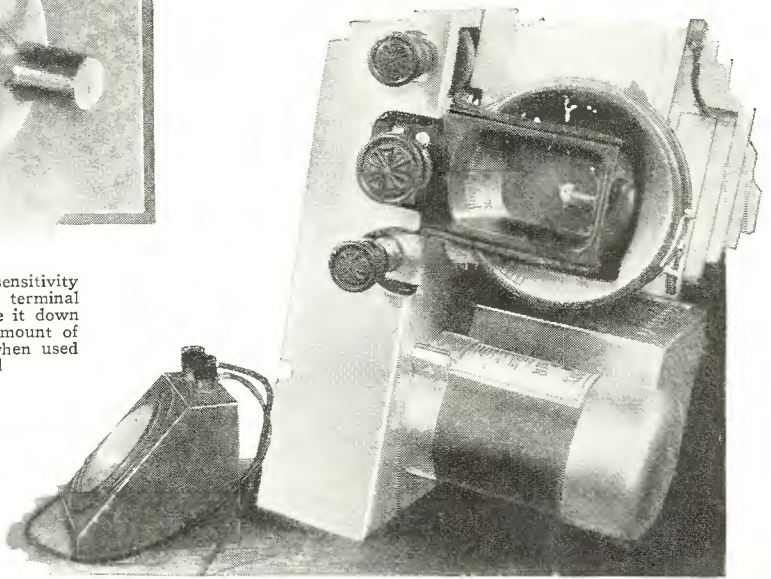


If a receiver hums when it is being tested, do not always blame the set, especially if it's tipped up as the one in the photograph. The cause of the hum is the electrolyte running off the elements of the electrolytic condenser and reducing its filtering capacity



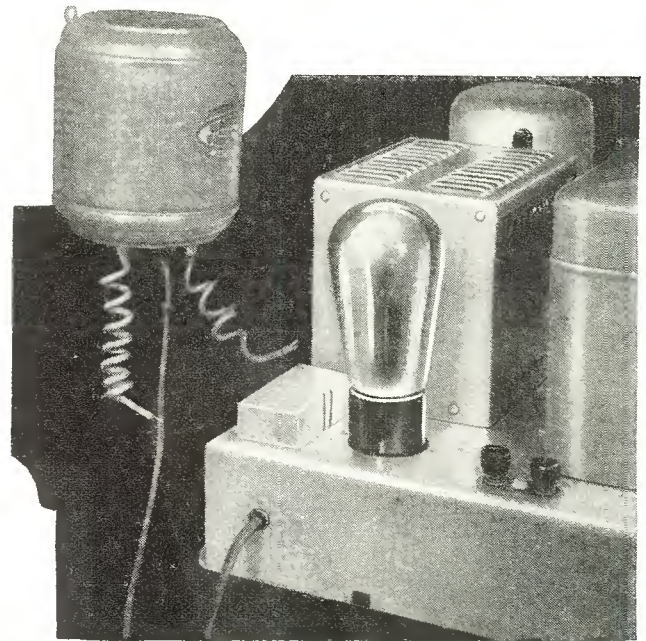Microphone and vacuum tubes, magnifying sounds a hundred fold, have been combined with other delicate instruments to form an electrical ear to detect the faintest whisper of a knock and yet remain deaf to other engine noises. The apparatus was developed by researchers of the Atlantic Refining Co.



In many receivers it is not always necessary to use an antenna. Sometimes the ground wire can be used. One manufacturer has designed what is known as the "ground-tenna," the device pictured at the left in this photograph, which may be installed inside the console of a receiver and which will give satisfactory operation over average distances. The two coiled wires go to antenna and ground binding posts of the receiver, while the straight wire goes to the ground connection. In the event an antenna compensator is used on the receiver it will probably be necessary to vary it because of the change in input conditions. Device made by Western Coil and Electrical Company

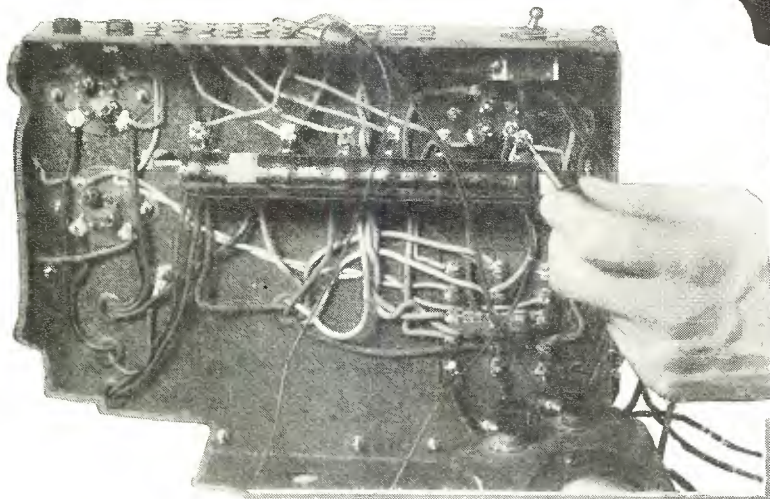

In some 280 power supplies no condenser is provided at the input end of the choke. On a 250 volt supply the voltage may be raised by as much as 60 volts by the addition of a 2 mfd. condenser from filament to plate of the rectifier. When replacing condensers in power supplies it may pay the service man to watch for jobs without input condensers



# Power Amplifier Measurements

(PART I)

**I**N presenting the electrical fidelity response curves on these pages it is well to outline the conditions of measurement and from what these conditions were derived.

The logical method of measuring the electrical fidelity of an audio frequency amplifier is from a standpoint of maximum undistorted output. At the time, however, a suitable harmonic analyzer was not available, making it necessary to run the measurements under other conditions. If the amplifiers were perfect it would make no difference at what power level they were measured as long as the selected level did not exceed maximum undistorted output. Unfortunately, all amplifiers are not perfect

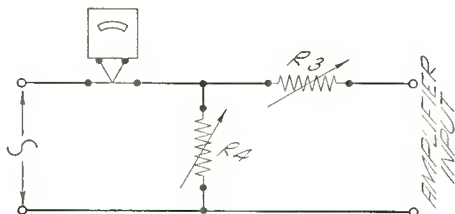


Figure 1

and therefore it would be unfair to measure a single 250 at the same power level as 250's in push-pull.

To determine the most satisfactory method of measurement a number of experimental measurements were made under varying conditions, results analyzed and the following procedure decided upon: The constant input-variable output method seemed most satisfactory. Value of power output selected as standard was one-third rated undistorted power output of the output tubes. When used in push-pull the Western Electric rating of three times the power output of a single tube was used. Since the constant input-variable output method was used the standard would only hold good for the reference level

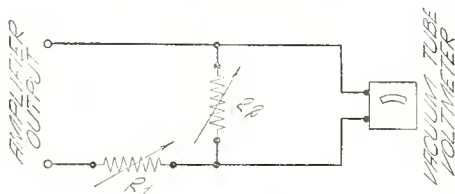


Figure 2

of 400 cps. (cycles per second). At this point of power output it is not likely any amplifier would be so designed that it would be operating in an overloaded condition, also there would be sufficient voltage input to cause the


*On account of the number of amplifiers to be measured and their division into two or more classes, it has become necessary to present this article in two parts. The remaining amplifiers will be treated in the March issue of this magazine.—Editor.*

preceding tubes to be operating at a satisfactory point of grid swing. Also by this method a 245, 250 or push-pull combination of any tube may be measured on an equal basis. The input and output impedances were held to the manufacturer's rated value. The loads were purely resistive.

In Figure 1 is illustrated the input circuit and in Figure 2 the output circuit. All component measurement instruments were in the secondary standards classification and very carefully calibrated against primary standards. The tubes used in all amplifiers were of average transconductance and selected within very narrow limits. The temperature rise figures were as measured with the thermometer in contact with transformer case, the amplifier being in open non-circulating air and of four or more hours duration. Amplifiers were warmed up under full voltage for a period of three hours before measurements were made. Overall gain as given in decibels is as measured at the given a.c. line voltage. This should be noted as in some amplifiers the plate voltage will change with slight changes in line voltage and in some cases a material change in gain will occur.

\* \* \*

### Amer-Tran Model 86

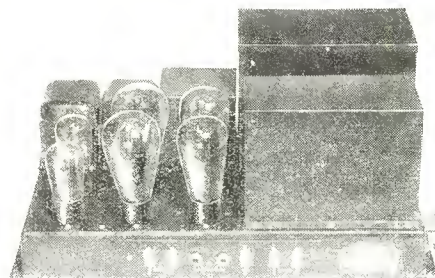

Amer-Tran model 86. Method of measurement: Constant input, variable output.


Output impedance load . 500 ohms  
Input impedance load . 500 ohms

Line voltage ..... 115 volts  
Line current ..... 1.5 amps  
Max. temperature rise.... 17.5 deg. F.  
Following values are as measured at 400 cycles per second:  
Output power level..... 4.65 watts  
Hum level: More than 46 Db. below the reference level.  
Gain ..... 70. Db.


### Tubes Used

1 a.f. .... UY 227  
2 a.f. .... UY 227  
P. P. .... UX 250  
P. P. .... UX 250  
Rectifier .... UX 281  
Rectifier .... UX 281

### Amer-Tran Response Curve

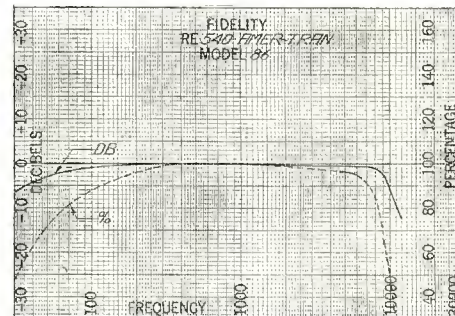

### Samson PAM 39

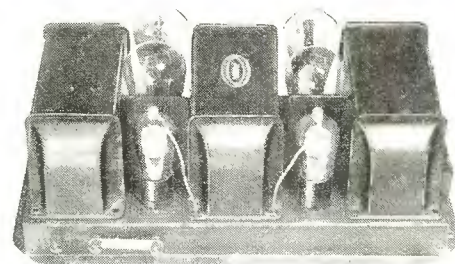

Samson PAM 39. Method of measurement: Constant input, variable output.


Output impedance load..... 500 ohms  
Input impedance load..... 5000 ohms  
Line voltage ..... 113.5 volts  
Line current ..... 1.2 amps  
Max. temperature rise.... 19.5 deg. F.  
The following values are as measured at 400 cycles per second:

Output power level..... 4.65 watts  
Hum level, 4.7 per cent.... 26.3 Db.  
Gain ..... 57.12 Db.


### Tubes Used

1 a.f. .... UY 224  
2 a.f. .... UY 224  
P. P. .... UX 250  
P. P. .... UX 250  
Rectifier .... UX 281  
Rectifier .... UX 281

**Samson Response Curve**

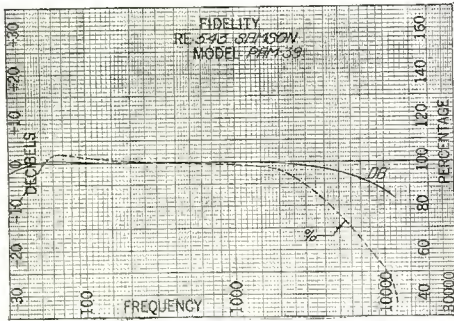

**Rauland Model 53-A**

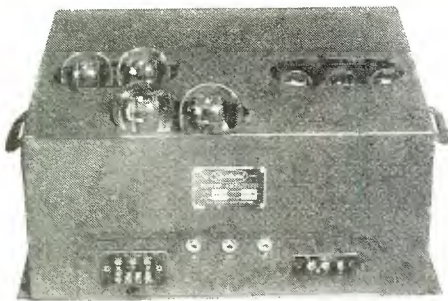

Rauland model 53-A. Method of measurement: Constant input, variable output.

Output impedance load...8000 ohms  
 Input impedance load...4000 ohms  
 Line voltage ..... 112 volts  
 Line current ..... 1.5 amps  
 Max. temperature rise.... 11. deg.F.


The following values are as measured at 400 cycles per second:

Output power level..... 4.65 watts  
 Hum level, 2.98 per cent.. 30.5 Db.  
 Gain ..... 68.13 Db.


**Tubes Used**

- 1 a.f. .... UY 227
- 1 P. P. .... UX 112-A
- 1 P. P. .... UX 112-A
- 2 P. P. .... UX 250
- 2 P. P. .... UX 250
- Rectifier ..... UX 281
- Rectifier ..... UX 281

**Rauland Response Curve**

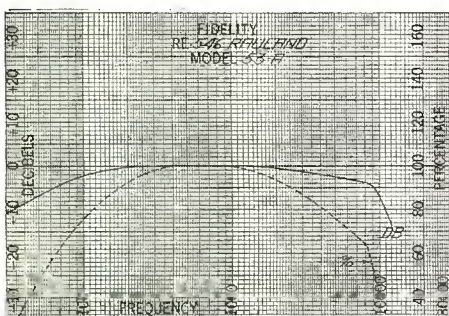

**Electrad Model C-250**

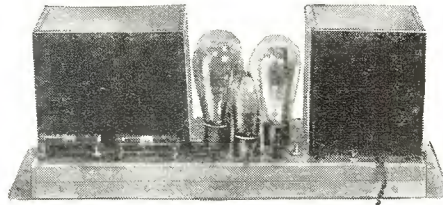

Electrad model C-250. Method of measurement: Constant input, variable output.

Output impedance load...4000 ohms  
 Input impedance load...8000 ohms  
 Line voltage ..... 114 volts  
 Line current ..... 1.63 amps  
 Max. temperature rise.... 19. deg.F.


Following values are as measured at 400 cycles per second:

Output power level..... 4.65 watts  
 With tone control set at treble: Hum level, more than 46 Db. below the reference level.  
 Gain ..... 53.53 Db.

**Tubes Used**

- 1 a.f. .... UY 224
- P. P. .... UX 250
- P. P. .... UX 250
- Rectifier ..... UX 281
- Rectifier ..... UX 281

**Electrad Response, Treble**

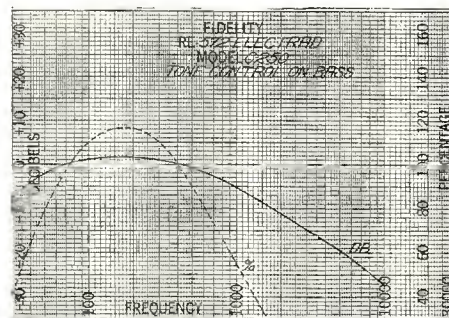


Electrad model C-250. Method of measurement: Constant input, variable output.

Output impedance load...4000 ohms  
 Input impedance load...8000 ohms  
 Line voltage ..... 114 volts  
 Line current ..... 1.63 amps  
 Max. temperature rise.... 19. deg.F.


Following values measured at 400 cycles per second:

Output power level..... 4.65 watts  
 Hum level, more than 46 Db. below the reference level.  
 Gain ..... 50.64 Db.

**Electrad Response, Bass**

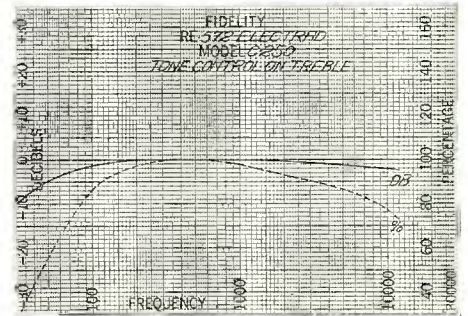

**Thordarson Model 3715**

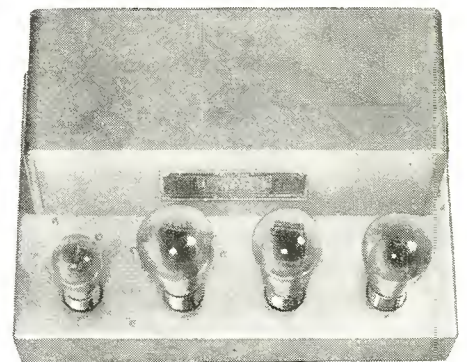

Thordarson model 3715. Method of measurement: Constant input, variable output.

Output impedance load...1800 ohms  
 Input impedance load...8000 ohms  
 Line voltage ..... 115 volts  
 Line current ..... .77 amps.  
 Max. temperature rise.... 17. deg.F.


The following values are as measured at 400 cycles per second:

Output power level..... 1.55 watts  
 Hum level, more than 46 Db. below the reference level.  
 Gain ..... 42.29 Db.

**Tubes Used**

- 1 a.f. .... UY 227
- 2 a.f. .... UX 250
- Rectifier ..... UX 281

**Thordarson Response Curve**

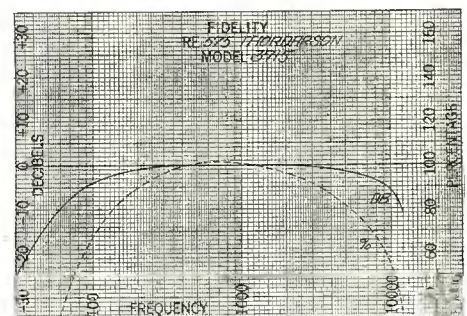

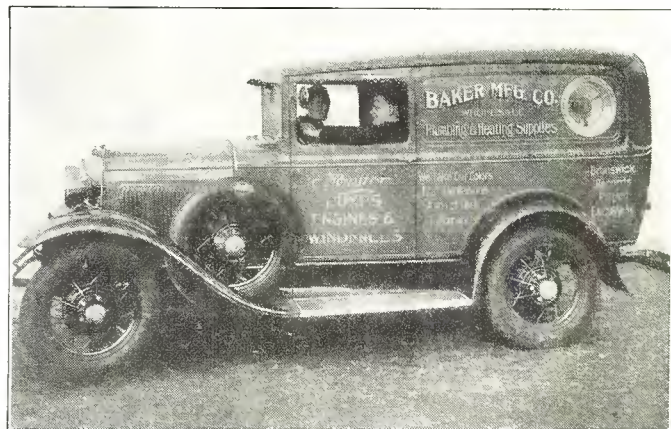
# A Page of Interesting Pictures




This is the new home of KDKA at Saxonburg, Pa., the transmitter being housed in the attractive building shown here


The Baker Mfg. Co., wholesale plumbing and heating supplies, covers the Oklahoma oil fields and finds that musical entertainment comes in handy not only on the trips but while the car is parked at the leases. The Radio Laboratories, 1511 Walnut St., Kansas City, Mo., made the installation and supplied the photograph at the right



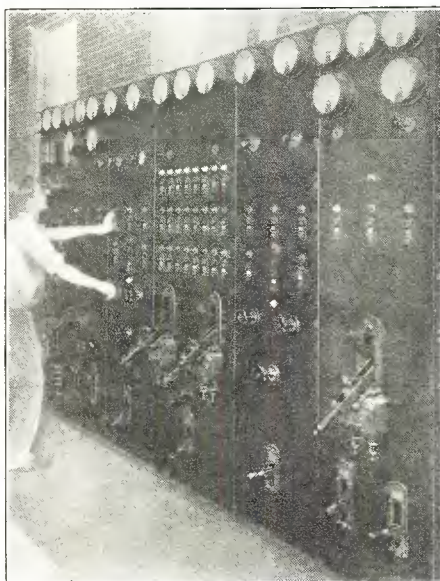
Painted yellow and black to reduce flying hazards these poles are used for the antenna installation at KDKA. The transmitter house shown in the preceding photograph may be seen in the background of this picture



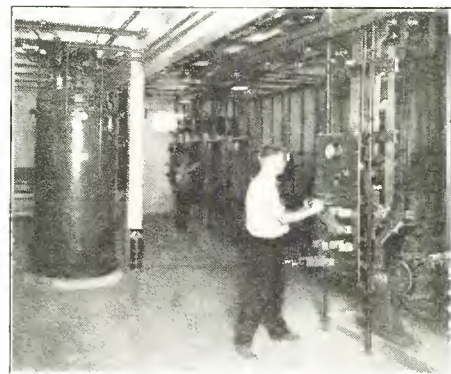This photograph shows one of the power panels at the New KDKA transmitting station. Another section of the power equipment installed in the basement may be seen in the photograph at the right



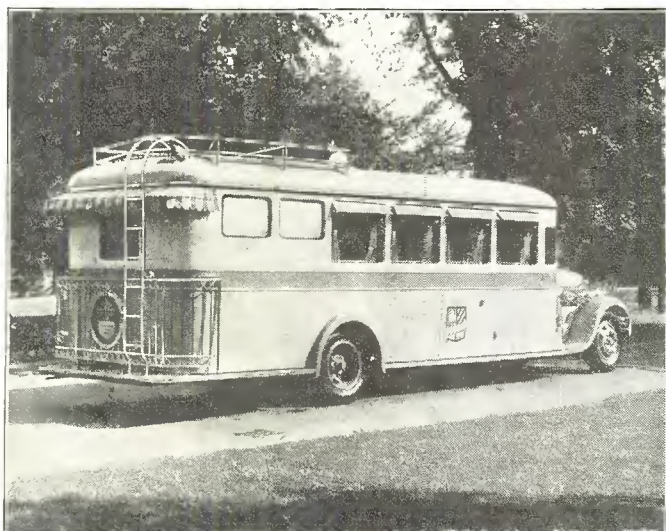In this photograph is shown part of the power equipment used in the KDKA transmitter, this installation being made in the basement of the transmitter house. This sub-station generates sufficient power to meet the lighting requirements of a city of 25,000 inhabitants. The present power of the new transmitter is 50,000 watts



To provide entertainment on long trips a Delco automotive radio has been installed in the de luxe motor coach, Bonne Entente II, owned by General Motors of Canada, Ltd., and used by company officials for making business tours



Installed in locker compartments above the seats the Delco standard set is easily accessible for tuning. This photo shows the interior view of the Bonne Entente II used by GM executives while travelling in Canada. The receiver has automatic volume control to compensate for variations in signal strength

# Scott 1931 All-Wave Superheterodyne

DESCRIBED on this page is the Scott 1931 All-wave receiver using the superheterodyne circuits, and covering both the broadcast and short wave bands. The front view of the chassis is found in Figure 1; a close-up of the rear chassis in Figure 2; the separate power supply in Figure 3 and the schematic for the power supply in Figure 4. Response curves covering sensitivity, selectivity and fidelity as recently taken in our laboratory, are shown in Figures 5, 6 and 7, respectively, while the electrical connections of the super are shown in the drawing in Figure 8.

## From 15 to 545 Meters

The receiver covers a frequency range of from 20,000 kc. to 550 kc. Six sets of coils are required to cover this range, there being two coils to each set. Coil ranges are as indicated: 15-21 meters; 21-31 meters; 31-51 meters; 51-105 meters, and 105-200 meters. The broadcast set is from 200 to 545 meters. Each set of coils overlaps so there are no dead spots between bands.

The antenna coil for the broadcast band is tapped at 2, 8 and 15 turns and coupled very loosely to the first r.f. stage. On short waves the antenna is connected to ground through a concentrated high inductance. This inductance is mounted on the three gang condenser cover and has a wire with a grid clip soldered to it. To tune on short waves,

remove grid clip leading from first r.f. coil and place grid clip from concentrated inductance on first r.f. tube; then connect antenna to binding post on

circuit of this stage also has the oscillator signal, this latter being at a 470 kc. difference from incoming frequency. The mixer is biased to operate as a plate rectification detector, the stage using a 224 screen grid.

## Intermediate Stage

Three stages of intermediate frequency, tuned to 470 kc., and inductively coupled make use of the 224 tubes. Coupling from stage to stage is by a very small number of turns of wire, to hold a sharp peak on all the intermediate frequency grid circuits which are tuned by

a fixed and a very small variable condenser. The amount of gain per stage can be varied by moving the plate coupling coils up or down the grid coil. It is not recommended that changes be made in this coupling since it was originally set in the laboratory for best operation.

The second detector, using a 227, is a power detector, used to prevent overloading on strong signals. Instead of the single 227 first audio this job has two of these tubes arranged in push-pull, also to prevent overload and feeding through transformer coupling to the grids of the 245 tubes in push-pull, these tubes being located in the power supply unit.

Connected to the receiver chassis by a cable is the power supply unit whose schematic diagram is shown in Figure 4. A fuse is provided inside the amplifier base to protect the apparatus from damage due to a shorted circuit or tubes. A five prong socket in the front of the power supply is furnished to supply energy for the speaker field and

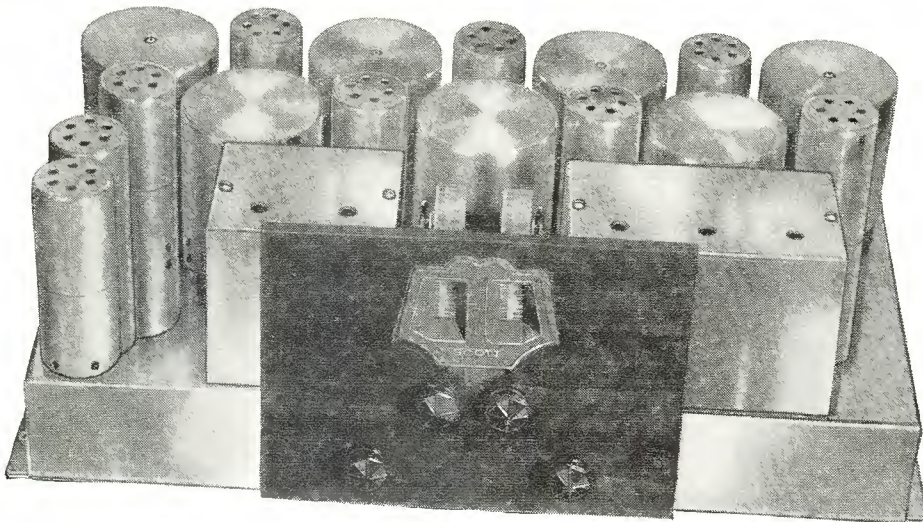


Fig. 1. Here is shown the front view of the chassis of the Scott 1931 All-Wave super recently measured in our laboratory

side of three gang condenser cover. The plug-in coils make the other changes that are necessary when they are plugged in their proper sockets.

## Oscillator Coupling

Examination of the circuit will show the oscillator is coupled to the lower end of the grid coil of the first detector, or mixing tube. These circuits are

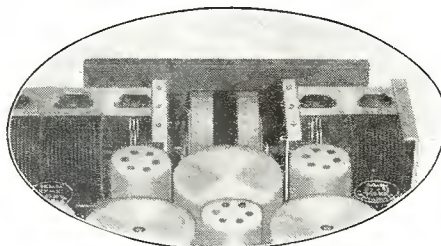


Fig. 2. A close-up view of the rear of the chassis, showing plug-in coils to the left and right of the two tube shields, and also special condenser sections for covering the higher frequencies

coupled inductively for the broadcast band, and capacitatively coupled on the short wave band. Grid circuit tuning is used, a 227 being employed. There are no other connections to make in the oscillator circuit other than plug in the proper oscillator coil (the one with four prongs) when changing to short wave operation, as all the short wave condensers are changed when coils are plugged into socket.

The first detector, or mixer, is tuned by one of the three gang sections to the incoming signal frequency. The grid

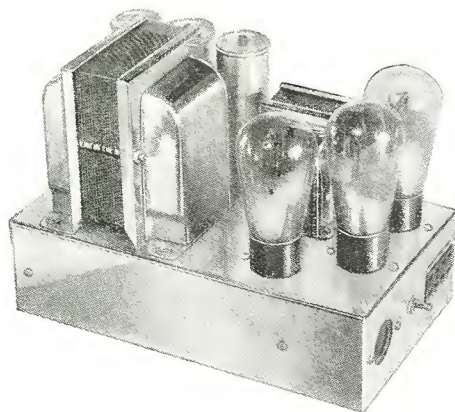


Fig. 3. The power supply used with the receiver described on this page is illustrated in this photograph

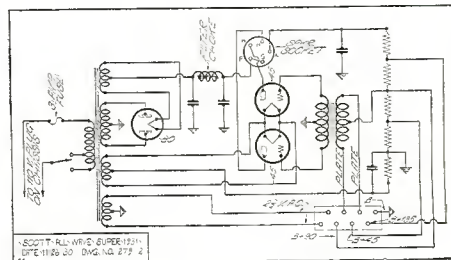


Fig. 4. Schematic diagram of the power supply of the Scott 1931 receiver

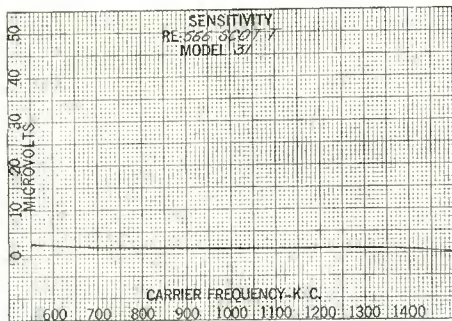


Fig. 5. Sensitivity curve

output transformer which is located in the speaker base. The speaker has a five prong socket plug to fit this socket. The speaker field winding acts as the filter choke in the power unit. The rectifier used in the power supply is the conventional 280.

A comprehensive set of instructions for operating and servicing the receiver has been prepared for the Scott receiver by the engineers of the maker, from which excerpts will be made later in this article.

**Two Dial Control**

Two dials are used in tuning the present model, this being particularly desirable on the higher frequencies. Dials are marked in kilocycles for the broadcast band, and in numbers for the logging on the short wave bands. The dial to the left (see Figure 1) tunes the oscillator circuit and the right one the antenna input stage and the first detector. The oscillator dial will be at the frequency of the incoming signal, although the r.f. dial at the right may be as much as 10 kc. off. In tuning, harmonics may occur if the two dials are not kept together.

At the left in Figure 1 is a knob that switches from local to distant input conditions. It has three positions, low, medium and loud signal; all the way to the left is low, center is medium, and all the way to the right for loudest reception. On the right of the panel is the volume control knob operating a combined on-off switch and variable

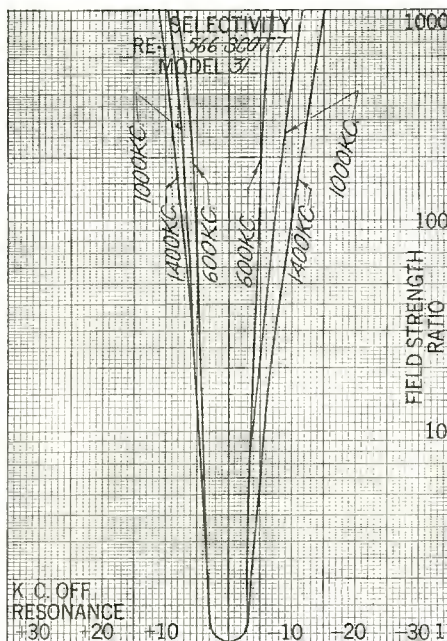


Fig. 6. Selectivity curve

resistor. Turn the knob to the right to start up the set.

Instructions for operating the receiver on short waves state: remove the oscillator can (the one to the left, facing the front of the set, in the row nearest the panel). Remove the r.f. can (the one to the right, facing the set, in the row nearest the panel). Pull out the r.f. and oscillator coils and plug in the r.f. and oscillator coils to cover the short wave band desired. Be sure both coils have the same markings on top.

Now remove the cap from the screen grid tube in the r.f. stage, which is the second tube on the right hand side closest to the front panel, and place the screen grid cap coming from the choke coil on the large condenser shield on the screen grid tube. Remove the antenna from the antenna post on the rear of the chassis, and connect it into the antenna post on the large condenser shield.

The cans are left off when using the receiver for tuning in short waves. The receiver is tuned in the same manner

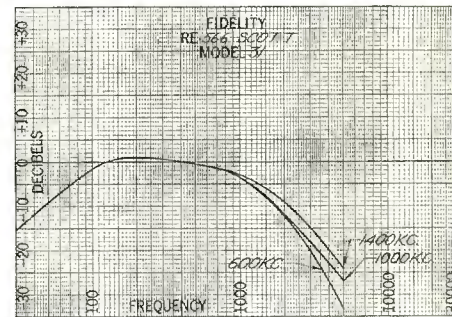


Fig. 7. Fidelity curve

as when tuning on the broadcast band, except that the kilocycle markings on the dials are ignored and the numbers used instead. Dials will track together pretty well except in a few places, but even there the two will only be a few numbers apart.

The three binding posts in the rear of the chassis are for the use of a magnetic pickup. Terminal 1 is connected to the cathode of the second detector, terminal 2 is connected to the C bias resistor and condenser, while the third terminal is connected to ground.

Each receiver is carefully balanced at the factory and it should not be necessary to immediately rebalance it. When necessary it may be rebalanced as follows: Carefully tune in a station about 700 kc. Starting with the first i.f. stage turn the small balancing condenser to the right and left until maximum signal strength is obtained. Do this with each stage in turn. To balance the r.f. start with the balancing condenser next to the dial in the large condenser can. This is the antenna stage. Turn the condenser to right and left until maximum signal is obtained. Next to this stage is the r.f. where the same procedure is followed. The last condenser is for the short wave and will not have to be balanced. If the oscillator does not line up to kilocycle markings, turn the small condenser (to the left of the small condenser can) down to lower dial readings, and up to raise the dial reading. To change the reading on the r.f. follow the same procedure.

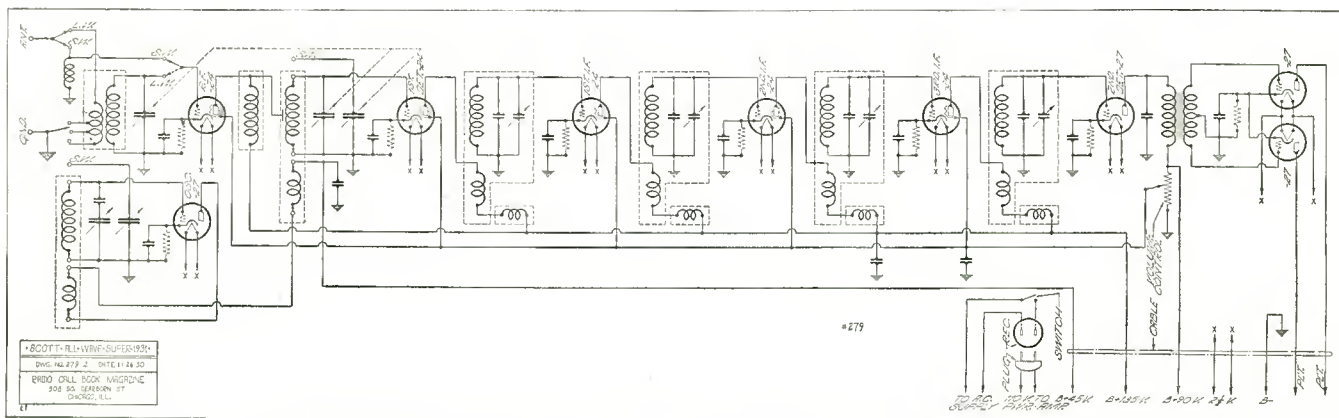


Fig. 8. In this diagram will be found the electrical connections for the Scott 1931 All-Wave receiver

# Field Strength Effect on Receivers

SINCE the use of field intensity measurements has become the accepted index to the performance of a broadcasting station, it should be of interest to the listener and station owner alike to be familiar with the method by which such measurements are taken and the interpretation of such measurements in terms of their effect on receiver performance.

Fig. 2 shows a map made from field intensity measurements made with apparatus such as shown in Fig. 3. Fig. 3 is the circuit diagram of a typical field intensity measurement set, which consists essentially of a superheterodyne receiver of a more or less conventional type, with a beat oscillator, operating about 500 cycles from the peak frequency of the intermediate amplifier of the receiver, added. This receiver uses a loop antenna with the midpoint grounded and a known resistance added in the center of the loop. A carefully

*We are indebted to Messrs. Doolittle and Falknor, Chicago, for the preparation of the maps accompanying this article, since the field strength plotting shown thereon represents recent measurements taken covering one of the broadcasting stations in the Middle West.—Editor.*

shielded local oscillator is also used, and can be tuned to frequencies in the broadcast band by means of a condenser. A sensitive volume indicator is coupled to the output of the receiver so that the intensity of the beat note, resulting from a received signal, and the beat note resulting from the local oscillator can be compared for relative intensity.

## How It's Done

Signals are measured by tuning in the desired station and swinging the loop to a point where maximum deflection is secured, on the volume indicator. With the loop again swung to a position where the received signal falls to zero and the local oscillator put into operation, in zero beat with the signal of the station in operation, the attenuator is adjusted until the deflection on the volume indicator is the same for both the local oscillator and the received signal. If the current supplied to the attenuator is now read and the attenuator loss noted, the current flowing through the loop resistor can be easily calculated. Knowing this current and the resistance in series with the loop their product will give the voltage actually introduced into the loop from the radio station under observation. If this value is divided by the effective height of the loop antenna the signal intensity in

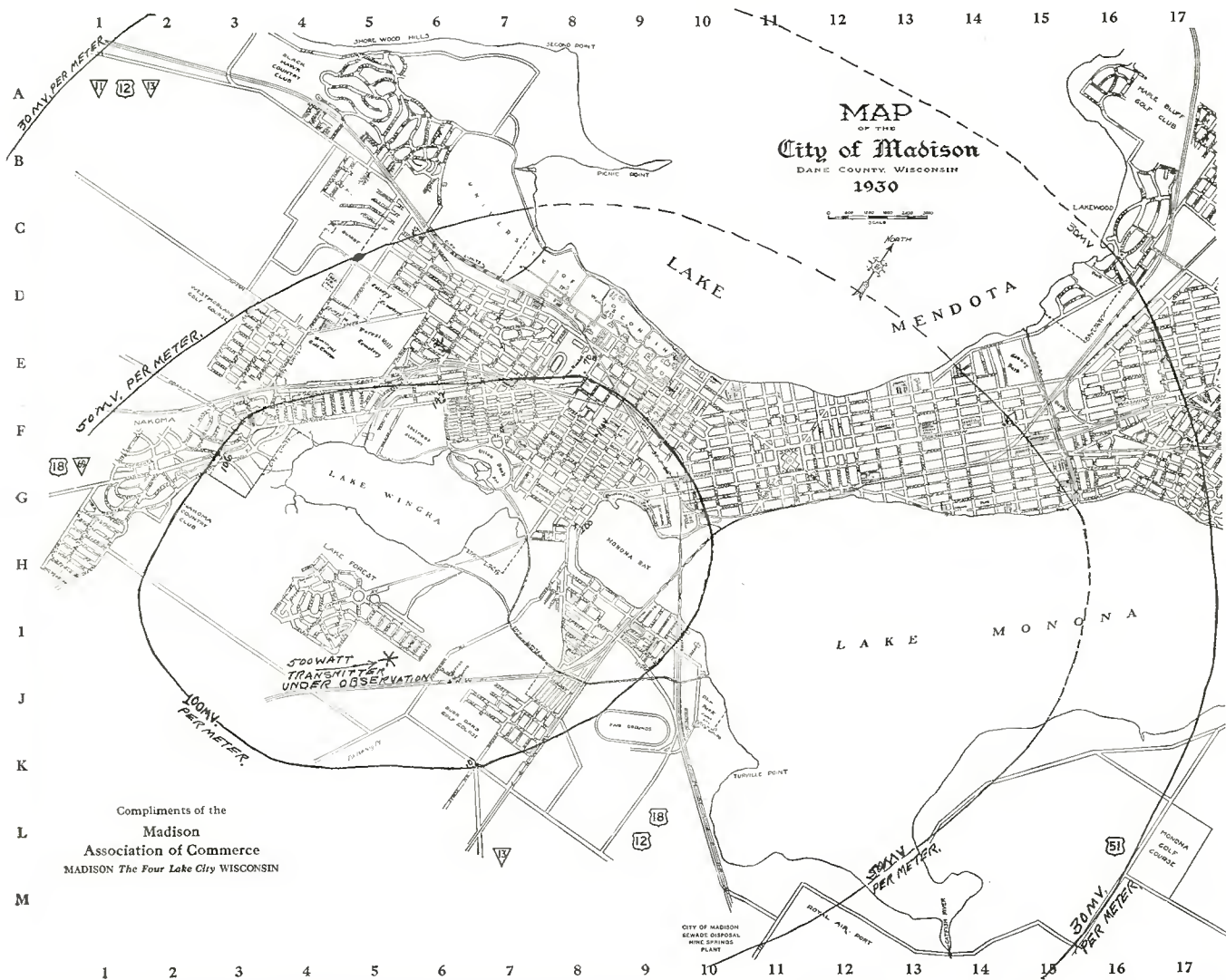


Fig. 1. This map shows the field strength of a local station, measurements being made to determine to what extent the thickly populated area would be affected by a strong field strength

terms of millivolts or microvolts per meter is the result.

**Show Grades of Service**

A map such as shown in Figs. 1 and 2 are prepared by connecting all points, having the same field intensity. Such lines show the relative grades of service to be expected, at various distances from a transmitter and also show the various degrees of interference that may be expected on signals from other stations due to the characteristics of the receiving set.

Fig. 2 shows that transmission from the station, from which these maps were made, is quite uniform in all directions, although some obstruction has caused a slight decrease in transmission to the South and Southeast. It further shows that for rural communities very good reception can be expected beyond the confines of the survey, for rural communities the lowest dependable signal being about 1 millivolt per meter. This map also shows that since the 30 millivolt circle falls in a thickly populated area, it is quite possible that a considerable territory will be covered with a signal intensity in excess of 50 millivolts per meter above which level considerable interference will be experienced on all receivers, when tuned to stations near the one under measurement, while on receivers of the older types modulating of the signals of all stations by the local station will be experienced.

**Serious Effects**

In order to determine to what extent the thickly populated area would be effected, the map of Fig. 1 was made. This map shows that the major portion of the town will be seriously effected by cross talk when a receiver is tuned to a station less than 20 kc. away from the local station, while few receivers will be able to receive signals separated by 10 kc. or less from the frequency of the local station.

Several types of interference may be expected from the local station in a case such as shown on Fig. 1. On very old receivers with little if any shielding of

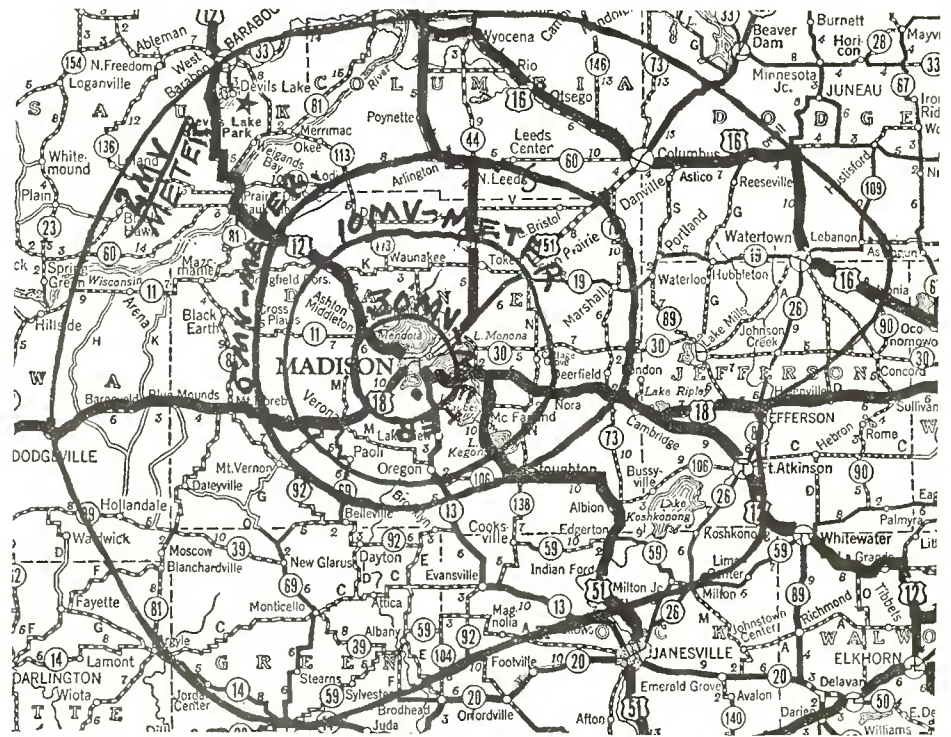


Fig. 2. The field strength map shown here was made from measurements taken with apparatus whose simplified schematic diagram is shown in Figure 3

radio circuits, cross talk on all stations will occur due to the fact that sufficient voltage induced by the local station will always be present on the grid of the detector tube to cause the local station to be heard regardless of where the receiver is tuned.

On other types of receivers where shielding is satisfactory but the antenna system is poorly tuned or not tuned at all the local station will be heard only when the receiver is tuned to it or any other station. This is due to the fact that the signal applied to the grid of the first tube in the receiver by the local station is of such a high value that the first tube acts as a detector and all received signals are modulated by the local station.

On receivers having the antenna system sharply tuned it will be found that all but stations differing less than 15 or 20 kc. from the local station will be received satisfactorily. On receivers of

this type the interference is due to the fact that the side bands from both the local station and the station that is desired to be received, overlap the resonance curve of the receiver.

In a territory where the field intensity of the local station is much in excess of 100 millivolts per meter bad cross talk can be expected on almost all types of receivers except where at least some pre-tuning is done before any signal reaches the grid of a tune. With this type of receiver it is possible to attenuate the local station sufficiently so that the voltage at the grid of the first tube will be too low to cause modulation of all other radio signals.

In cases where extreme local interference is experienced from causes indicated by the field intensity maps shown here, it is usually possible to reduce such interference by reducing the length of the antenna used on the re-

(Continued on page 83)

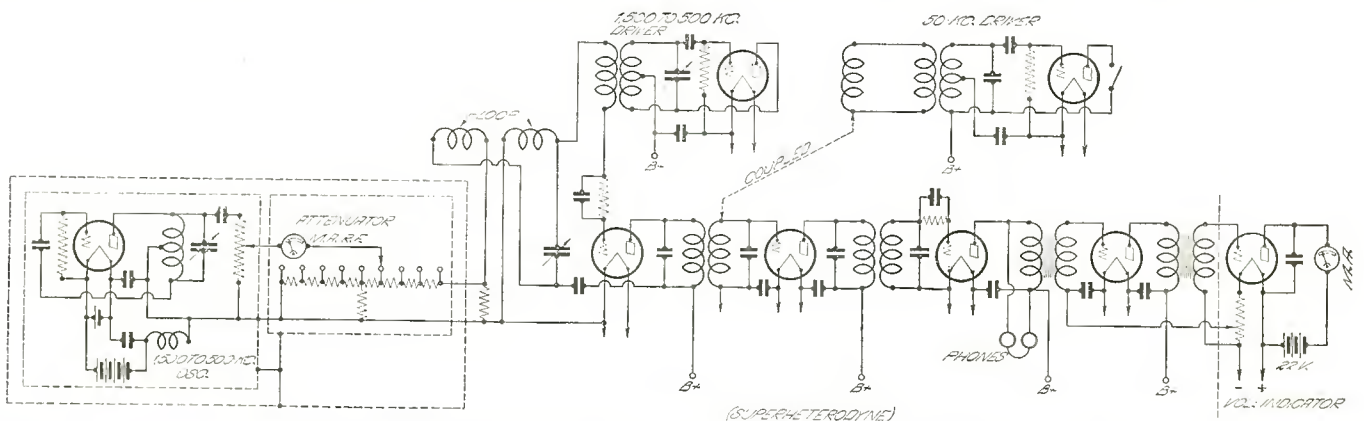


Fig. 3. The field strength equipment, described and photographed in our November issue, uses the simple schematic shown in the above drawing

# Design Data on H. F. L.'s "Little Giant"

By E. K. OXNER\*


THE recent advent of numerous commercial superheterodynes as broadcast receivers has greatly increased the popular interest in receivers of this fundamental type. Great differences exist among the various adaptations of this familiar circuit and this article deals with the characteristics of some of the important components of a super which is about to appear on the market.

The great number of stations and the closeness of their allocation has made mandatory the use of at least three circuits at broadcast frequency ahead of the mixer or first detector tube to prevent carrier modulation and other undesired responses, particularly in view of the fact that the frequency 175 kc. has been almost universally adopted as the center of the intermediate amplifier transmission band.

The 3 r.f. circuits, as they are familiarly called, are in themselves conventional in construction; care is taken that the r.f. amplification is substantially the same over the entire broadcast spectrum. Numerous methods of coupling the oscillator circuit to the third of these r.f. circuits are available, and offer little choice as to results; one of the most common methods (that of coupling through the mutual inductance of the two tuning coils when properly related physically) serves to minimize the difficulties of single dial operation or a close approach thereto.

Many schemes, both mechanical and electrical, have been propounded, to

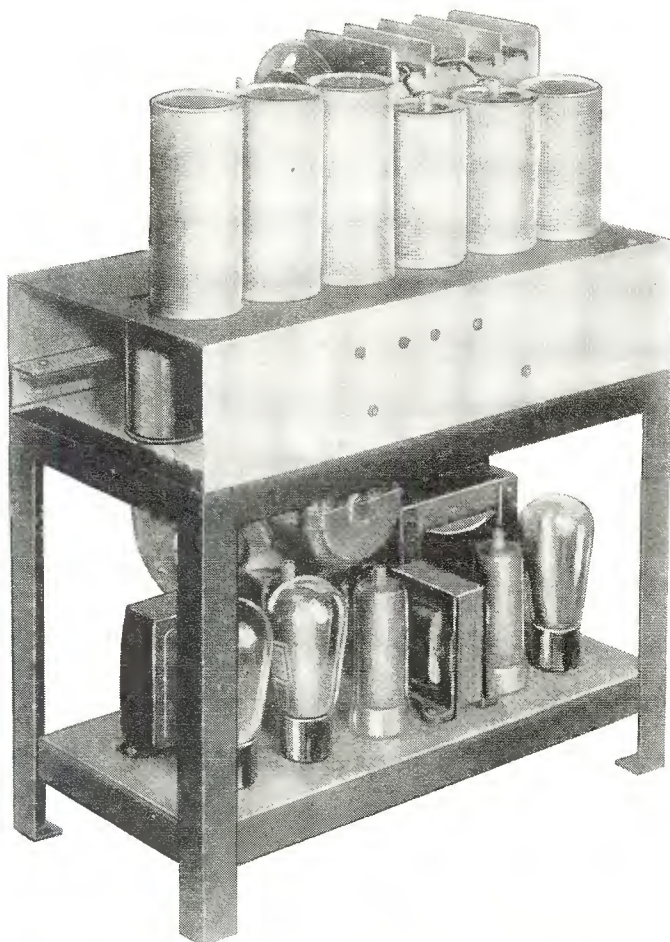\*Chief engineer, High Frequency Laboratories, Chicago.






This illustrates the rear chassis view of the "Little Giant" super made by the High Frequency Laboratories and described in the accompanying article


provide a close approach to single dial tuning, with circuits differing by 175 kc. for maximum output and therefore operating over spectra of different widths. The mechanical methods have not been widely used commercially; a series condenser network has come into general use and is fairly satisfactory. Its main objectionable feature is that, theoretically, it offers only an "approach" to real single dial tuning, if the latter be defined as to require that the "difference" frequency of the two circuits be always, and exactly, the intermediate frequency.

A method which provides this exact tuning required, and which further simplifies the construction of the receiver circuits as well as their adjustment in the field, is that involving the use of a special plate shape for the oscillator tuning condenser. Cost of testing has heretofore prevented its use, but gang condensers are now available with such special plates in one section. The necessity for holding correct inductance values for all tuning coils is of the same order as with the series condenser method.


Fig. 1 indicates the capacity curve of the r.f. tuning condensers of such a gang unit. Fig. 3 shows the actual tuning curve of such units when associated with coils of the correct inductance and with proper allowance for minimum capacity, including trimmer, socket, coil, wiring and the tube, itself. To reproduce this curve exactly in the oscillator circuit requires that for any stated dial setting, the oscillator generate a frequency 175 kc. higher than that of the r.f. circuits. Thus the tuning curve of the oscillator circuit is obviously that of the r.f. circuits except that the frequency scale is shifted.

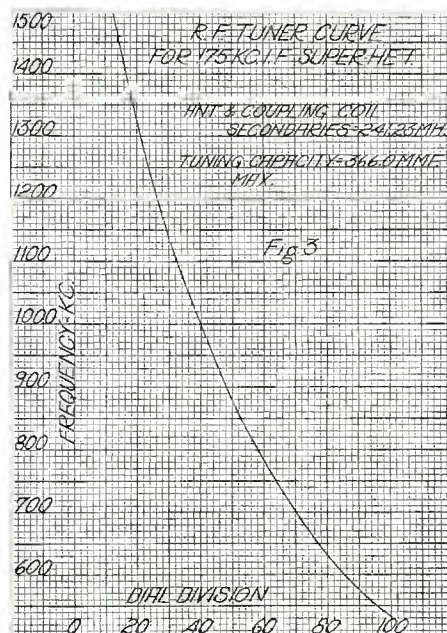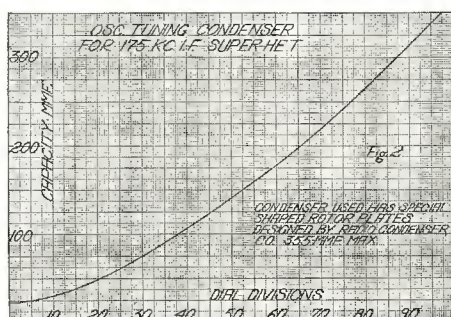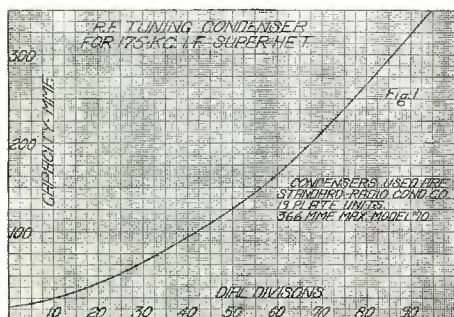




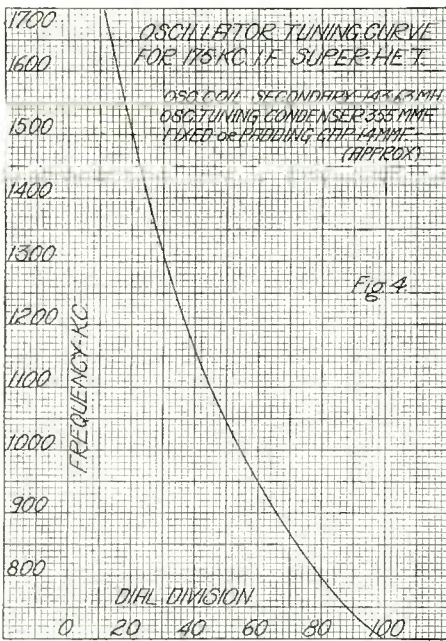

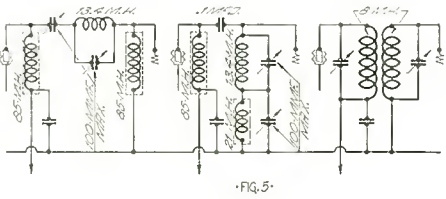Numerous values of oscillator circuit inductance can be used, as well as any sufficient value of minimum circuit capacity which will be encountered in other parts of the circuit. For this work, an inductance value as indicated on Figure 4 was chosen, together with



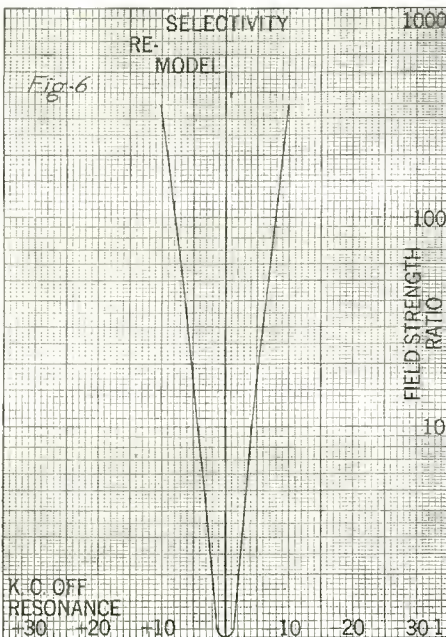
a total minimum capacity of 50 mmf. of which varying amounts are to be inserted by means of the trimmer. This total reserve is sufficient to cover practically any arrangement of parts, etc., in any super. Figures 2 and 4 show the condenser and tuning curves, respectively,




tively, of the oscillator circuit used in this receiver. The mathematical treatment of this problem was performed by Dr. E. D. Koepfing of the Radio Condenser Co., who supply the condensers used.

It should be noted that with such a tuning system, a check in the field, at any time, on the phasing of a receiver may be done in the same manner as with any multi stage r.f. set, merely by deflecting the slotted plates of the condensers at any dial setting, as compared to the extremely judicious balance between the values of *two* trimmers, which is required in the case of the series condenser system.

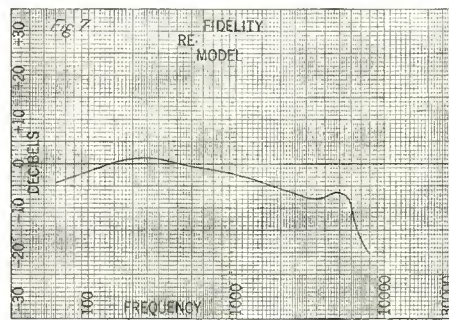The intermediate amplifier, the "Heart of the Super," is again, in this




case, the Hopkins Band Rejector, with a considerable improvement in control of band shape and width. The performance curves of this system, which has been in use for nearly a year, have previously been published, as well as explanatory articles outlining the means of suppressing interfering signals. Figure 5 shows the diagram of the newest Hopkins circuit, with all constants given. Tubes are operated at the voltage ratings specified by the manufacturers. Among other improvements,

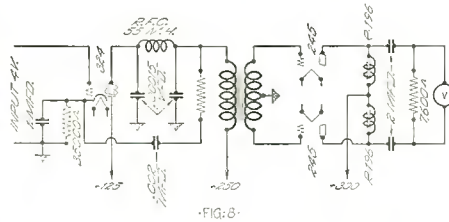


this type amplifier contains adjustments which may be used to alter band width at the base of the curve (near the minimum input level) without affecting band width under the heavier input voltages. This is unique, and offers the great advantage that the amplifier as a whole does not "break down" or, in effect, widen its transmission band when confronted with an extremely high input signal voltage. Figure 6 is a typical result of an extreme adjustment, greatly favored by some fans who want the greatest possible selectivity. This curve is for the i.f. amplifier alone and does not include r.f. selection.

This receiver employs, for its audio

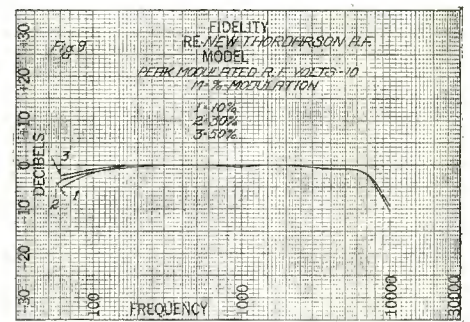


channel, an entirely new development in the well known dynamic speaker, as well as a remarkable improvement in the audio transformer used in its single audio stage, coupling a screen grid power detector directly to the output tubes. Figures 7 and 8 show, respectively, the operating conditions and the performance characteristic of the only such a.f. transformer available when development work was started on the components of this new super. This older system has been used extensively in a very large number of sets, whose output quality was accepted as par excellence. Comparison of Figure 9, showing the performance of the newly developed a.f. channel, will indicate immediately the remarkable improvement in response

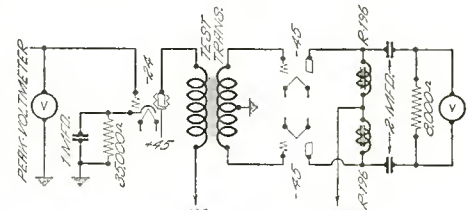


which has been attained. Figure 10 shows the circuit conditions under which this new transformer was operated when the graph of Figure 9 was secured. The transformer curves and data are due to the Thordarson Electric Mfg. Co., of Chicago, whose laboratories investigated and developed the units used, at the request of the High Frequency Laboratories.

Figure 11 shows the performance curve of the new dynamic speaker used in this super. This graph represents actual sound pressure output, as measured in the laboratories of one of the foremost radio manufacturers. The response

(Continued on page 81)

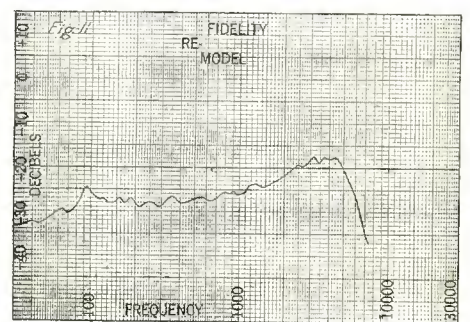

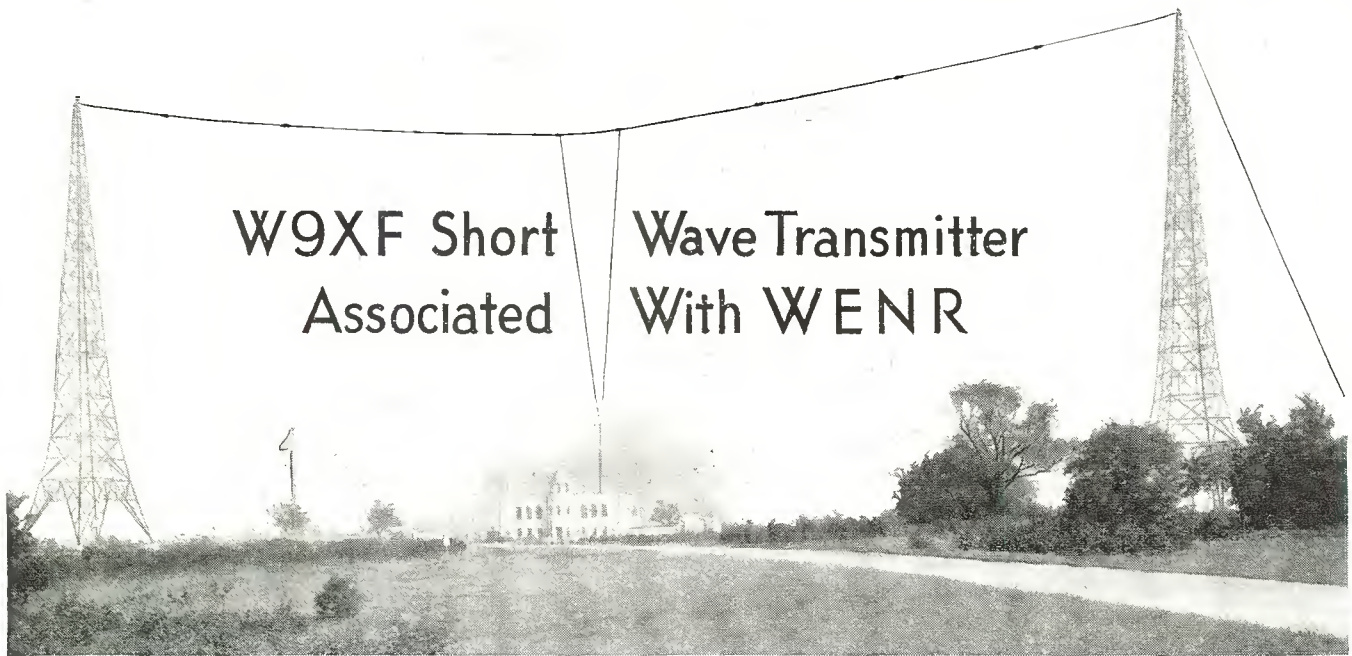

## W9XF Short Wave Transmitter Associated With WENR

**T**HE call letters W9XF were first used when the 50,000 watt transmitter for WENR was installed early in March, 1928. The preliminary test of this high powered transmitter made W9XF well known throughout the United States and many foreign countries. Therefore, when the Great Lakes Broadcasting Company was granted a license for a short wave transmitter, it was proper that the call letters W9XF should be assigned to this station.

### For Delay Work

This station operates under an experimental license granted for the purpose of experimenting in the transmission of

\*Chief engineer, Great Lakes Broadcasting Co.—Stations WENR, W9XF, W9XR.

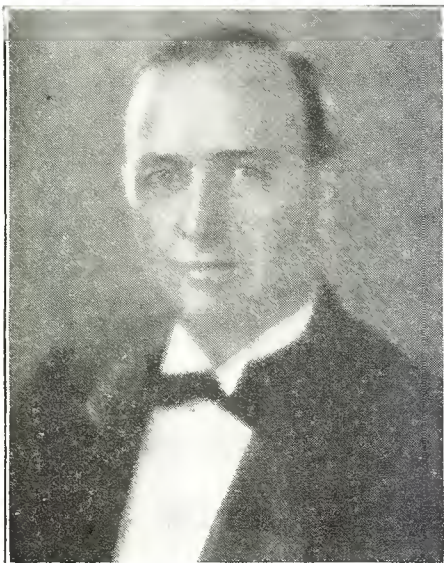


Fig. 1. E. H. Gager, chief engineer of the Great Lakes Broadcasting Co., operating stations WENR, W9XF and W9XR

By E. H. GAGER\*

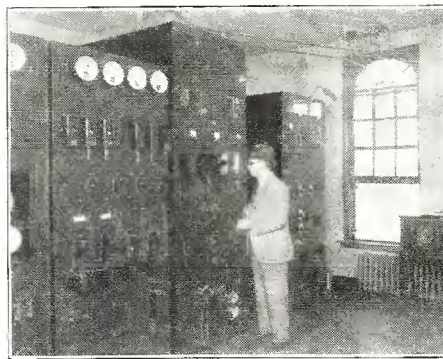


Fig. 2. Built by their own engineers, this photo shows the short wave relay equipment at WENR, where Mr. Gager is seen inspecting a part of the "works"

programs to foreign countries for re-broadcast in those countries. Its use for domestic broadcasting is not permitted. All of the programs of WENR are transmitted by W9XF. Reports have been received from every part of the civilized world, but the transmission seems to be particularly good toward the southwest. Japan, Australia and New Zealand are the countries best served by this transmitter. On one occasion, a two-hour program was successfully rebroadcast by 3YA, Christchurch, New Zealand. According to the reports of the New Zealand Broadcasting Company, not a word of the entire program was missed and the quality throughout the entire broadcast maintained a very high standard.

The transmitter has a rated power of 5,000 watts in the antenna, with approximately 85 per cent modulation. Two, UV-207 twenty kilowatt, water cooled tubes are used in the final stage.

The frequency of the transmitter is controlled by a 1,505 kilocycle quartz crystal. The frequency is multiplied by two stages of multiplication to the operating frequency of 6,020 kilocycles. The antenna is located approximately 600 feet from the transmitter building and is fed by a two-wire transmission line mounted on fifteen-foot poles. This transmission line passes directly under the antenna of the 50,000-watt transmitter.

### Mysterious Signals

Shortly after W9XF was put in service, we began to receive complaints

(Continued on page 82)



Fig. 3. Here we have a high power tube, a peanut receiving tube, and a high power organist. Rating of the tube is 100 kw, that of the peanut tube probably in milliwatts, while the rating of Irma Glen, WENR's organist, is very high according to countless thousands of her listeners

# Lincoln DC 8 De- signed for Use With New Breather Battery

**Latest Super Also Tunes Over  
80-Meter Band Without Coil  
Change**

PRIOR to the development of the a.c. type receiver, radio equipment as a whole depended upon battery operation. The general outline of equipments required d.c. operated tubes, requiring a heavy drain on the filament supply, the power of which was furnished by a storage battery and the plate supply of a dry battery type or of the storage type. Due to the heavy drain on the plate supply, "B" batteries would not last long and the "A" supply, or, storage battery required constant charging; and, in the country districts where power lines are not available, batteries had to be carried miles back and forth at regular periods.

With the advent of the a.e. receiver, the storage battery type of receiver with all its inconvenience of charging and acid, went into the discard and manufacturers throughout the country concentrated on the design of equipment to be powered by the 110 volt a.c. line

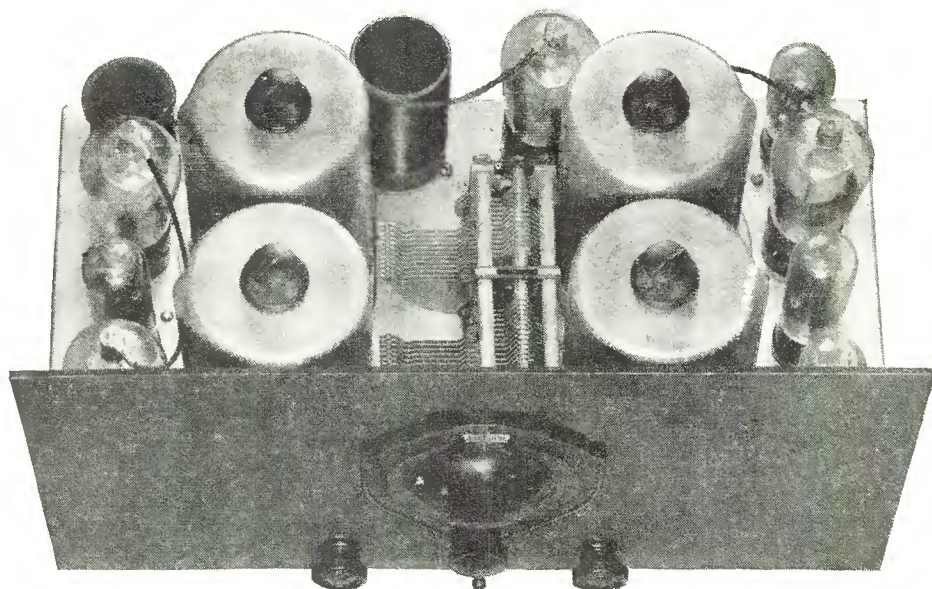


Fig. 1. From this photo may be seen the compactness of the Lincoln D-C 8 described in the accompanying text

current. By this program, thousands of homes in the outlying farm districts, were forced to use the antiquated storage battery equipment, due to the fact they could not purchase the more up-to-date radio receiver.

This created a great hardship on thousands of homes in view of the fact that the outlying districts must depend more or less upon reception from stations some distance away, and they, of all people, should have equipment capable of high amplification and modern design which radio has given the masses of people in the congested districts.

Due to recent developments in the last year, all of the detrimental features of the previous battery type receiver have been wiped out. In the design of the Lincoln DC-8 receiver, it is now possible to have consistent operation for a period of a year without any attention whatever to power equipment—

(Continued on page 81)

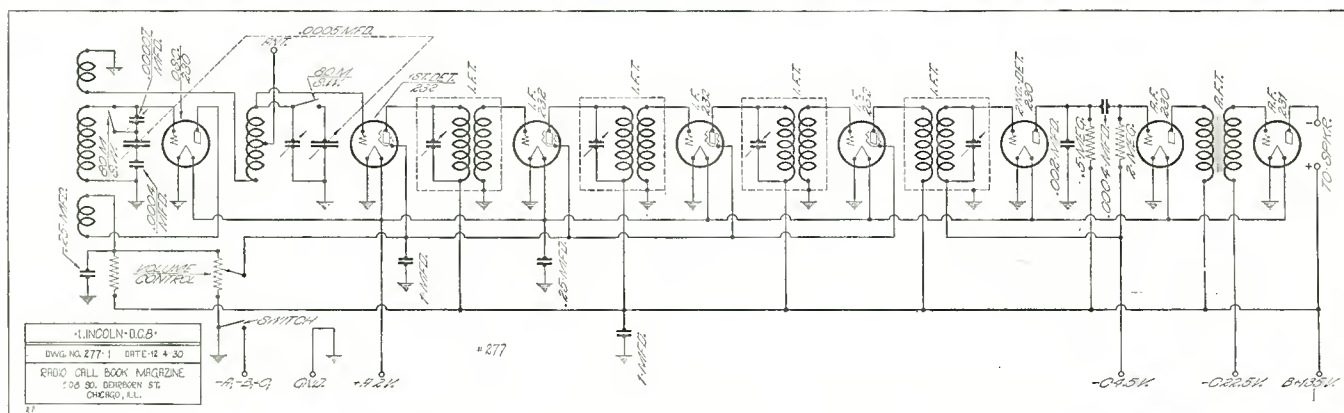
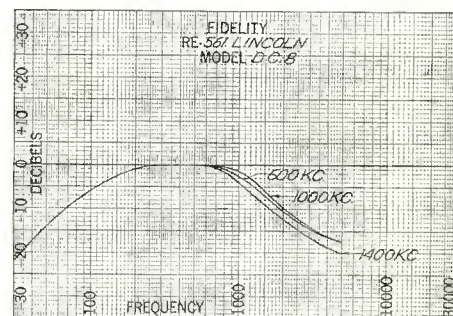
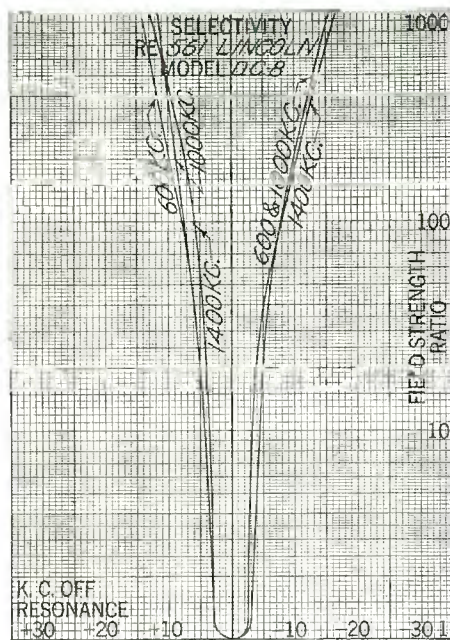
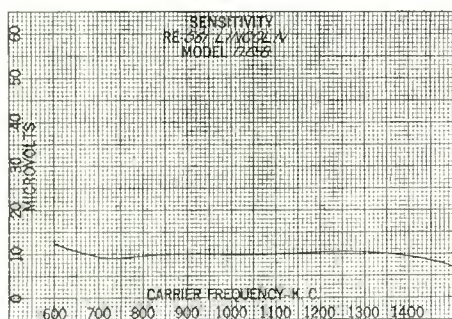


Fig. 2. Electrical details of the Lincoln D-C 8 may be learned by consulting the above schematic

# Distortion and Cross-Talk Reduced

**D**ESIGNED to reduce distortion due to: (1) non-linearity between input and output voltages in an r.f. amplifier, (2) cross-talk effects, and (3) hum in a.c. receivers due to low frequency modulation of the carrier, in control and screen grid circuits, two new screen grid tubes, the 550 and 551 were described by Stuart Ballantine, of the Boonton Research Corporation at the November meeting of the Rochester section of the Institute of Radio Engineers. Numbers of these tubes have been produced by Arcturus, Raytheon and Grigsby-Grunow companies who co-operated with the Boonton Research Corporation in manufacturing studies. Receiver tests in the field were made through the co-operation of the engineers of the Radio Frequency Laboratories.

Basis for the above is found in Contributions from the Radio Frequency Laboratories, No. 22, "Reduction of distortion and cross-talk in radio receivers by means of variable- $\mu$  tetrodes," by Stuart Ballantine and H. A. Snow, Boonton Research Corporation, Boonton, N. J., dated October, 1930.


From this paper we learn the cause of the first and second effects enumerated above is the increase in the high order curvature of the tube characteristic in relation to the effects of the first order, which increases as the applied r.f. voltages are increased. Reduction of these effects has been achieved in the new tubes by shaping the plate current-grid voltage characteristic so as to minimize the higher order curvature over an extended range of control grid voltage.

An abbreviated digest of interesting portions of the paper is given here:

## Common Bias Control

A graphical method of applying the data for a unit stage to the prediction of the performance, control characteristics, overload and selection of control grid graduation in an amplifier comprising several stages is shown in Fig-

**Fig. 2. Control analysis for graduated bias control; stage 3 uncontrolled; stages 1 and 2 controlled by common bias. Other conditions identical with Fig. 1**

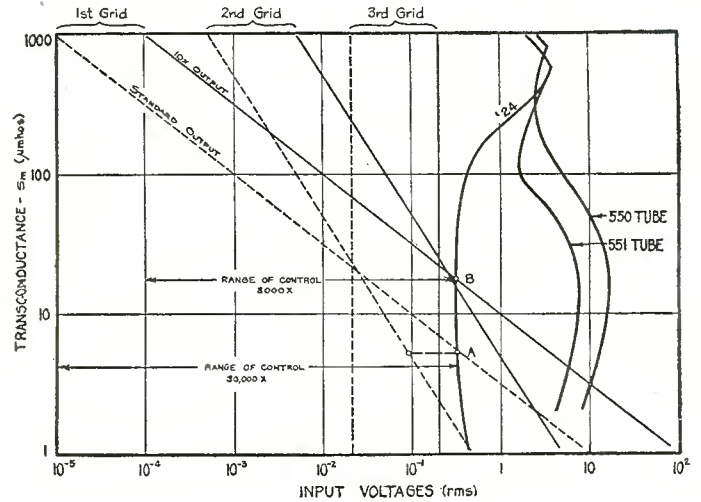

ure 1, where grid bias values do not appear explicitly but are represented by corresponding values of transconductance of the tube plotted as ordinates. This figure represents the case of com-


*Due to a shortage of space it has been necessary to considerably abridge the material in the paper by Messrs. Ballantine and Snow. However, we trust all the salient features have been retained. Engineers desiring the full paper will no doubt be supplied with copies upon application to the Boonton Research Corporation at Boonton, N. J. —Editor.*

At the grid of the third stage, for example, when the bias has been adjusted so the transconductance has been decreased from 1000 to 100 micromhos the voltage will have been increased ten times to preserve constant input to the detector; in the second stage the voltage will have been increased 100 times for standard output, and in the last stage to 1000 times, and so forth. It will be seen that overload occurs first in the third stage and limits the range of distortionless control. At standard output overload at the third stage occurs when transconductance equals 60 and input voltage is .05 volts, range of control being 5000 times. For ten times standard output, overload in the third stage occurs when transconductance is 250 and input voltage of  $9 \times 10^{-4}$  volts, a range of control of only 90 times. The unsuitability of this method of control (common grid bias) when high voltage detectors are to be operated with 224 tetrodes is thus apparent.

## Graduated Bias Control

The advantage of a graduated bias control, in which the third stage is not controlled, and the first and second stages are controlled by a common bias is brought out in Figure 2, the other conditions here being identical with those in Figure 1.

In the case of standard output the first stage overloads first at point A for 6 micromhos and input voltage of .3 volt, a range of control of 30,000 times. At ten times output, overload is reached simultaneously in the first two stages at point B. Since the modulation-distortion curve is vertical in this region the maximum input voltage for 20 per cent distortion is about the same for ten times as for normal output. This is enormously greater than in the case of the common bias illustrated in Figure 1 where the range was only 90 times.

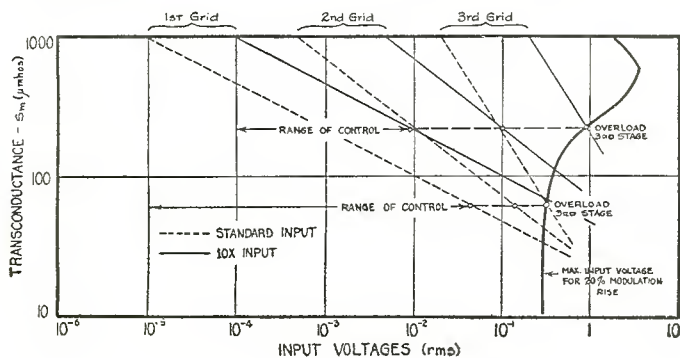

**Fig. 1. Control analysis. Diagram of input voltages in 3 stage amplifier employing 2A tetrodes controlled by common grid bias in all stages**

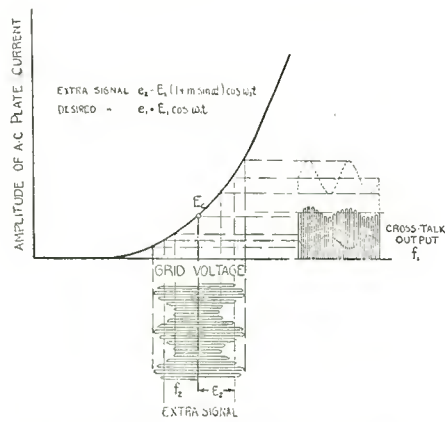


Fig. 3. Illustrating the production of Class B cross-talk. Heavy curve represents the relation between amplitude of plate current of desired signal frequency and grid bias with the desired signal impressed on the grid

It will be seen that the best graduation of bias depends in general upon the level of voltage at which the detector is to operate, and upon the distortion contour of the tube. A further graduation of bias between stages 1 and 2 generally results in additional improvement.

It should be noted the representation of the stage input voltages in the diagram by straight lines assumes the transconductance is independent of the voltage. In the range of voltages over which the input-output relations are non-linear this is not strictly true, and curved lines would be required in a perfectly accurate representation.

**Cross-Talk**

The term cross-talk is employed here to designate that species of interference which originates in r.f. amplifier tubes by modulation between two or more signals. These modulation effects depend upon the higher-order curvature parameters of the tube and are to that extent related to the problem of dis-

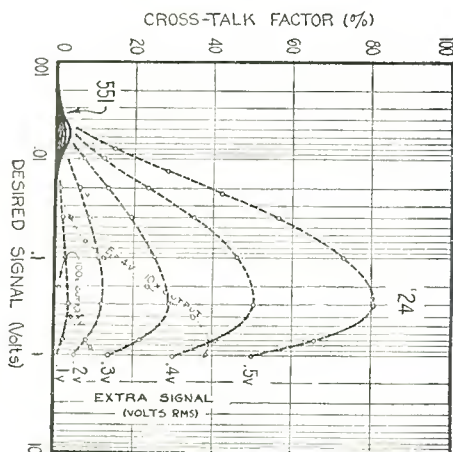


Fig. 4. Experimental curves showing cross-talk production in 24 and 551 tetrodes. Constant output maintained, corresponding to .001 volt desired signal at -3 volt bias

tortion. Any improvement effected in a tube to reduce distortion will also reduce a large part of the cross-talk.

For our present purposes we shall distinguish between two main classes of cross-talk.

In the first class (Class A) are included effects due to beating between two signals whose frequencies differ from each other and from that to which the receiver is tuned.

In the second class (Class B) is included cross-talk heard in circumstances of the following type: The receiver is tuned to a desired signal; a second signal, called the extra signal, of different frequency, is also present at the grid of the first tube. We shall also suppose the selectivity of the receiver and the frequency difference between the signals are such as to exclude the possibility of the extra signal being heard by simple interference in the ab-

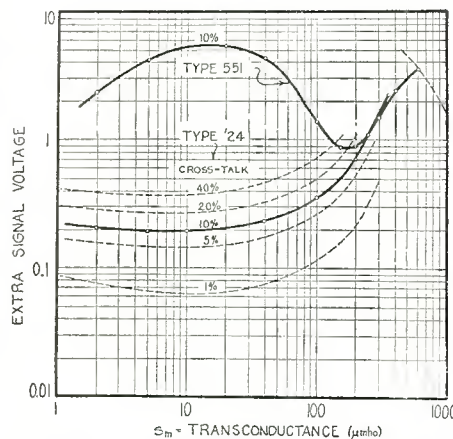


Fig. 5. Diagram showing relation between the transconductance produced by grid bias variation, and maximum voltage of interfering signal for various percentages of cross-talk

sence of the desired signal. If the desired signal he modulated both signals are heard simultaneously, if unmodulated the extra signal is heard.

The mathematical theory can be developed along the lines of the following physical picture. Figure 3 represents the relation between the amplitude of the r.f. output current of the tube and the grid bias with the desired signal (Fig. 4) impressed on the grid. This relation is derivable from the input-output data and in general is non-linear. We shall now regard the extra signal (Fig. 5) as varying the grid voltage about the point  $E_c$  which represents the grid bias. In order that the output of the tube shall be audible after detection it should be of the modulated signal type.

Figure 4 shows the relation between the cross-talk factor for an average 224 tetrode (dotted curves) and the new type 551 tetrode (solid curves) and the input voltage at a fixed voltage output

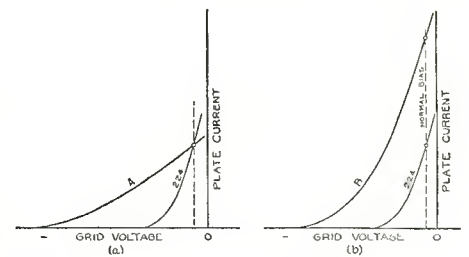


Fig. 6. Showing (a) decreasing transconductance and (b) increasing plate current accompanying attempts to decrease distortion by decreasing the mu-factor

level, and for several fixed values of extra signal. The modulations of the two signals were the same, 30 per cent. The output level was such that 1000 microvolts were required at normal bias (-3v;  $S_m = 1000$  micromhos) to produce it. A sufficient attenuation between this stage and the one following it was used to avoid any cross-talk effects in the second stage. The desired signal frequency was 1000 kc. and that of the extra signal was 900 kc. This frequency difference was not critical at the value employed, but was sufficient to preclude interference on the one hand and combination cross-talk of Class A on the other. Both desired and extra signals were applied directly to the grid of the tube.

**Cross-Talk Analysis**

For cross-talk analysis in a multi-stage amplifier we have employed a graphical method similar to that used for distortion and analysis which was shown in Figures 2 and 3. This is based on the fact that the cross-talk is approximately independent of the desired signal voltage. The basis of the method is a contour curve for the tube which shows the relation between the extra signal voltage which has to be applied to the grid to attain a given percentage of cross-talk and the operating point on the characteristic, as represented by the transconductance at the point. A typical set of such contours is shown in Figure 5.

The reduction of cross-talk at higher desired signal voltages which has been achieved in the 551 tube will be seen to be considerable. At  $S_m = 2.5$  micromhos, for example, the ratio of extra signal voltage for 10 per cent cross-talk amounts to about 23 to 1. This means

(Continued on page 80)

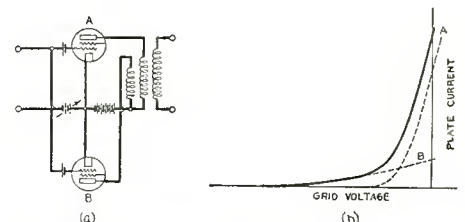


Fig. 7. Method of decreasing distortion and cross-talk

# Silver 714 A. C. Superheterodyne

**M** EASUREMENT and schematic details of the Silver-Marshall 714 a.c. custom built superheterodyne will be found here. Electrical connections of the tuner will be found in the drawing at the bottom of this page, while the three response curves are also shown. The front view of the chassis is shown in Figure 1, while the power supply schematic is shown in Figure 3.

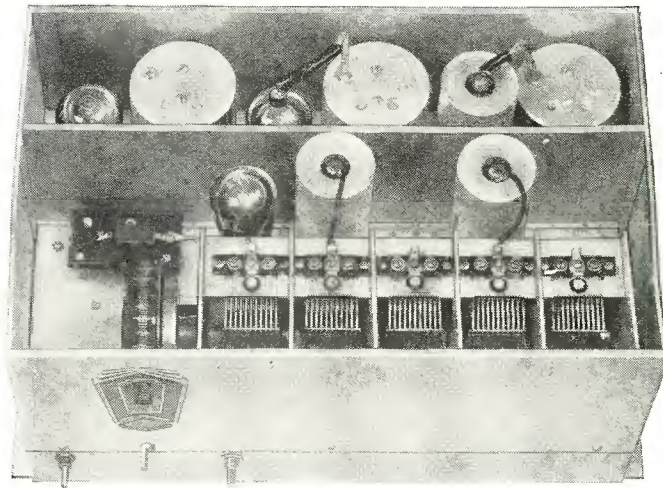


Fig. 1. This photograph shows the front top view of the Silver-Marshall 714 a.c. tuner, which, with its amplifier, was measured in the laboratory of this magazine. Curves are shown on this page

A band pass stage preceding the first 224 r.f. and another stage following it, feed into the first detector, these two stages using four of the five sections in the 5 gang condenser. The fifth section is used by the oscillator.

### Sensitivity Very Good

Judging from the response curve measurement made on this receiver in the laboratory it is the most sensitive and selective that has yet been measured by our engineers. Those who have been following the curves appearing in each issue will be interested in these findings.

Measurements were made with the dummy antenna consisting of 20 uh,

200 mmf and 25 ohms. The output impedance load was adjusted to 4000 ohms and coupled capacitively to the plates of the 245 output tubes. Receiver was phased at the factory value and the volume control turned on full. Line voltage 115, current .98 amperes.





Transconductance of the tubes was: 1 r.f. 1140; mixer 1120; detector 1030; 1 i.f. 1250; 2 i.f. 1200; 1 a.f. 1000; P.P. 1940; P.P. 1980 and oscillator 1000 micromhos.

In the following tables will be seen the interference ratios and the band width of the 714:

### Interference Ratio


Resonance	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.....	.....	.....	.....
1000 kc.....	.....	.....	.....
1400 kc.....	.....	.....	.....
	Minus 10	Minus 20	Minus 30
600 kc.....	.....	.....	.....
1000 kc.....	.....	.....	.....
1400 kc.....	.....	.....	.....

(Continued on page 83)

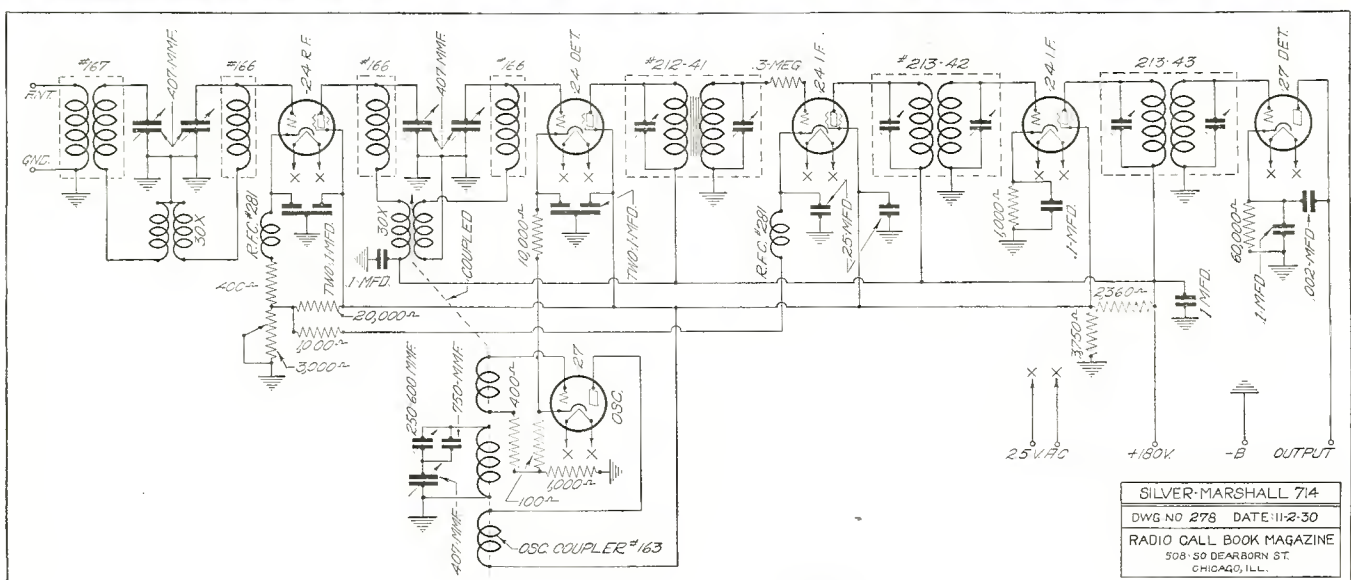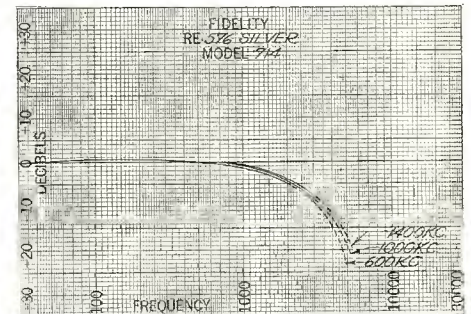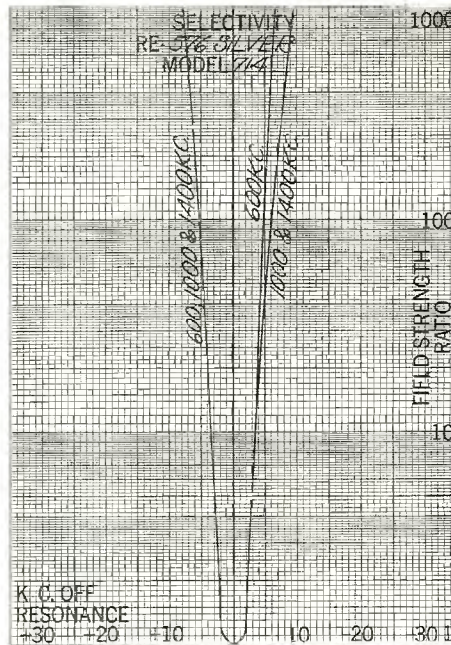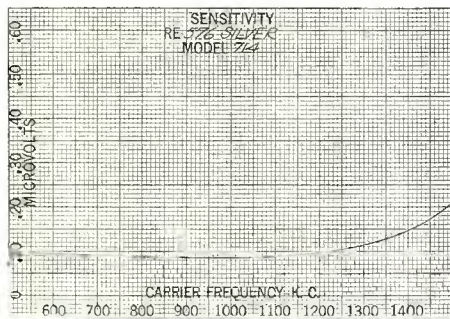

SILVER-MARSHALL 714  
 DWG NO 278 DATE 11-2-30  
 RADIO CALL BOOK MAGAZINE  
 508 - 50 DEARBORN ST.  
 CHICAGO, ILL.

# Westinghouse Remote Control Unit

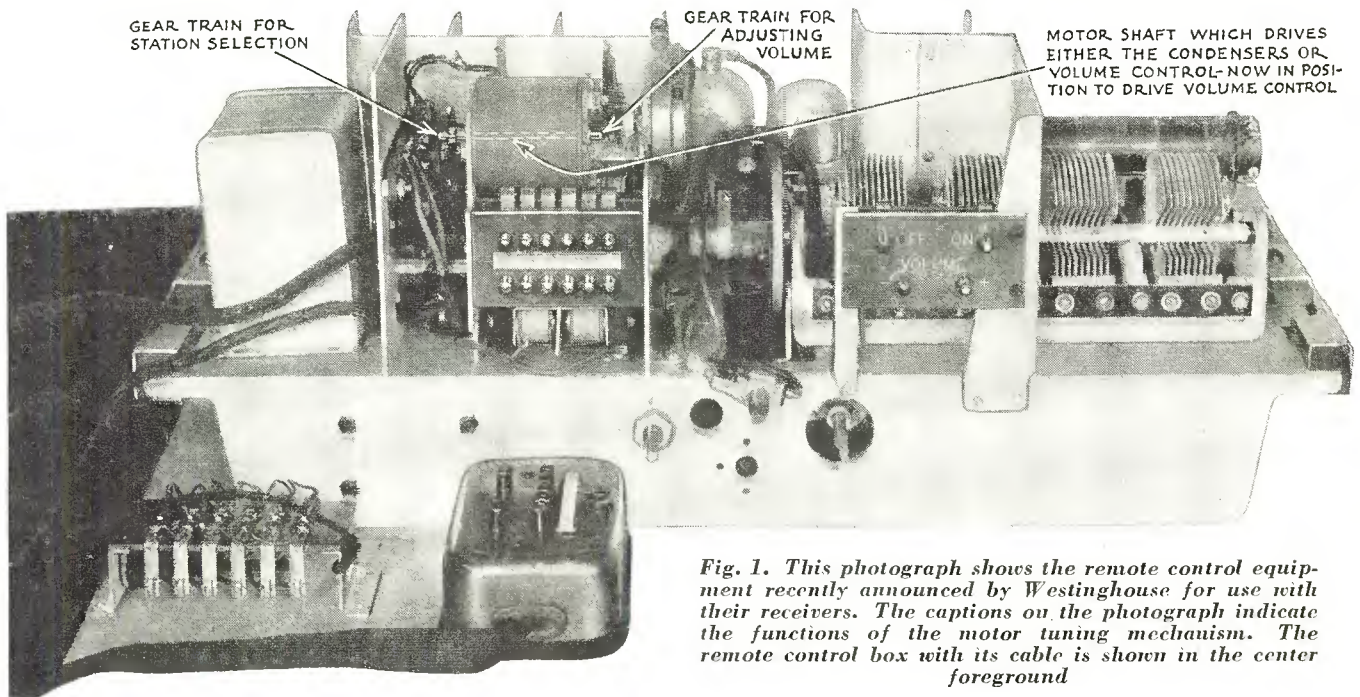

*Fig. 1. This photograph shows the remote control equipment recently announced by Westinghouse for use with their receivers. The captions on the photograph indicate the functions of the motor tuning mechanism. The remote control box with its cable is shown in the center foreground*

**E**MBODYING the most advanced engineering developments known to radio science, the new remote control equipment of the Westinghouse radio receiver brings increased pleasure into radio reception.

## Motor Does Trick

An electric motor which automatically turns condensers to the right position makes it possible for listeners to tune in the desired stations simply by pressing a button.

The heart of the remote control is a row of buttons on the front of the cabinet to the left of the illuminated dial. The buttons are pressed in and the desired stations are tuned in, after which the set is ready to be operated from the remote control box.

## Tune From Chair

The listener may retire to the comforts of any easy chair or to any other place where the remote control box has been located. Through the simple operation of corresponding press buttons the listener may tune in the desired stations just as accurately as though he were manually operating the receiver.

A feature of the Westinghouse remote control equipment is that a flat cord is used to connect the control box with the receiver. This flat cord has the advantages of being more flexible and durable than a round one and at the same time may be laid under a carpet out of sight.

## Fractional Degree Accuracy


From a mechanical standpoint the station selector contacts which control the rotation of the motor are actuated

by a series of cams. Accuracy within a fraction of a degree is obtained because when the condensers are rotated to the desired point the electrical contact is broken and the motor driven gear engaging the gear train which drives the condensers is disengaged.

The regular method of manual tuning is available as the remote control does not interfere with the ordinary operation of the receiver.

It will be observed by referring to the photograph in Figure 1, that the remote control box has a series of six buttons, by means of which as many stations may be automatically tuned in. Besides that by placing one finger on one of the two buttons at the left of the box in the photograph, and another finger on the other, it is possible to rock the tuning back and forth in search of any station that is not allocated to the six positions.

On the little panel at the right of the chassis in Figure 1 will be found four push buttons. The two at the top control the stopping and starting of the receiver itself, while the two buttons at the bottom control the volume.

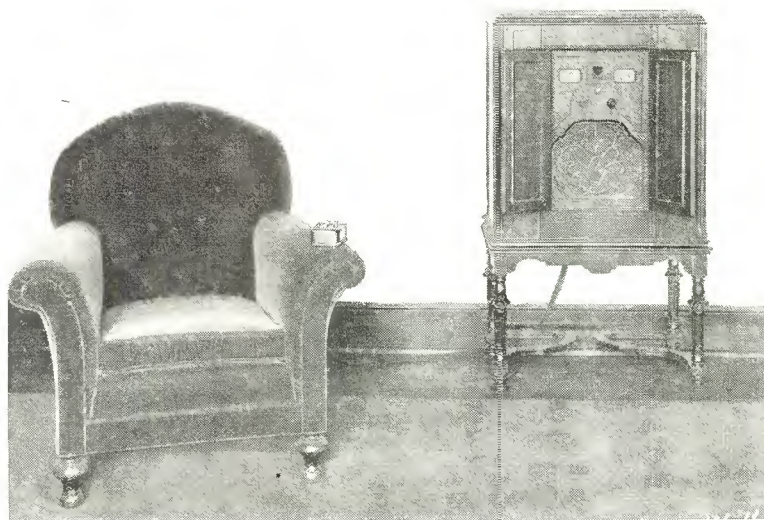

*Fig. 2. This picture shows a view of one of the Westinghouse receivers with the remote control device placed in it, and the remote control box located at the arm of a chair, from where it may be operated by the user. Push buttons are also installed on the panel of the receiver so that tuning can be done from that position too. The new device does not in any way interfere with the normal manual tuning*

# S.W. and Broadcast on A.C. Conqueror

RECENTLY designed by engineers of the Insuline Corporation of America, the A. C. Conqueror, model 47, illustrated photographically on this page, covers both the short wave and broadcast bands from 17 to 600 meters, by the employment of six plug-in coils. Ranges of these coils will be found at the end of this article.

The schematic diagram of the receiver is shown in Figure 2, while the front top view of the A.C. Conqueror is found in Figure 1.

It will be observed the antenna input stage is of the tuned type, the primary coil being variable, this input feeding to a screen grid 224. The bias for this stage is derived from the voltage drop across the resistor between cathode and ground. The plate circuit of the 224 is not tuned, but the secondary circuit of the detector is tuned, and in addition has the regenerative coupling coil which is controlled by the throttle condenser, or regeneration condenser.

### Careful Bypassing

One of the features worthy of mention is the care with which all the circuits are bypassed or choked, to eliminate common coupling. The screen

voltage on the 224 passes through a resistor from the 180 volt feeder, and the plate supply for the 224 passes through another resistor in the 180 volt line, the latter being bypassed with a 2 mfd condenser. Thus the common coupling between screen and plate of

is employed.

### Double Tuning Control

Tuning of the first r.f. and the detector circuits is by double control, the left hand drum (in Figure 1) tuning the r.f. stage, and the right hand drum tuning the detector. The center knob connected to the condenser in the center is for the regeneration control. The knob at the extreme left is for variation of the coupling between the antenna coil and the secondary. An on-off switch is provided at the right. Good shielding is provided in each of the stages so that capacity effects are not to be expected. With a well filtered power supply the receiver functions without hum, regeneration control is smooth and the individual coil ranges generous as to coverage.

### Coil Range

The first of the plug-in coils covers from 17-23 meters; the second from 27-45 meters; the third from 40-80 meters; fourth from 75 to 150 meters; fifth from 145 to 300 meters (lower half of the broadcast band) and the last coil covering from 295 to 600 meters which is the upper half of the broadcast wavelength section.

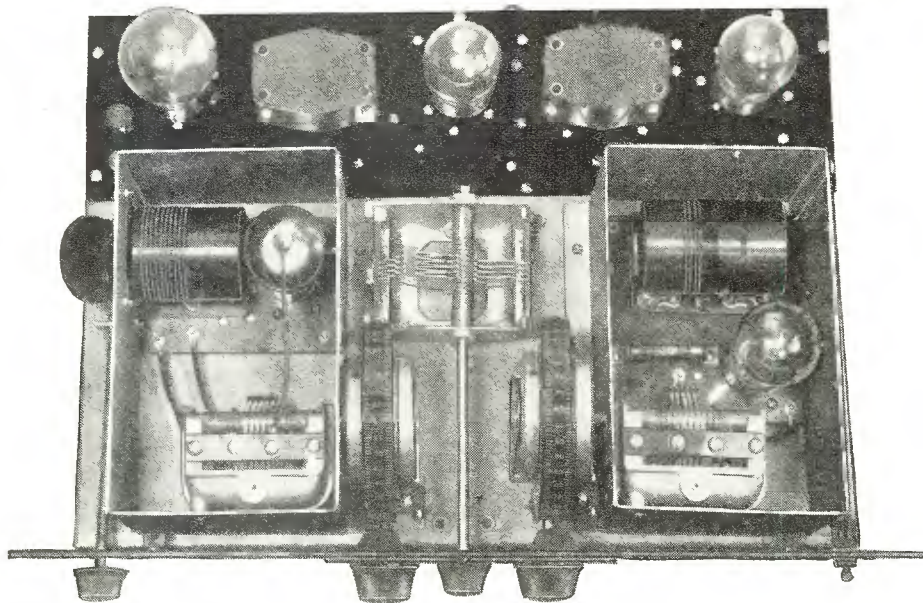


Fig. 1. This photograph shows the top of the new A.C. Conqueror, model 47, recently designed by the Insuline Corporation of America

the 224 is eliminated. It will also be seen that the plate circuit of the detector, where a 227 is used, is also fed through a separate resistor in the 180 line to further obviate common coupling. The same practice is employed in the first and second audio stages. Resistance coupling is used between the first and second audio stages, transformer coupling being used for the power output stage where a 245 tube

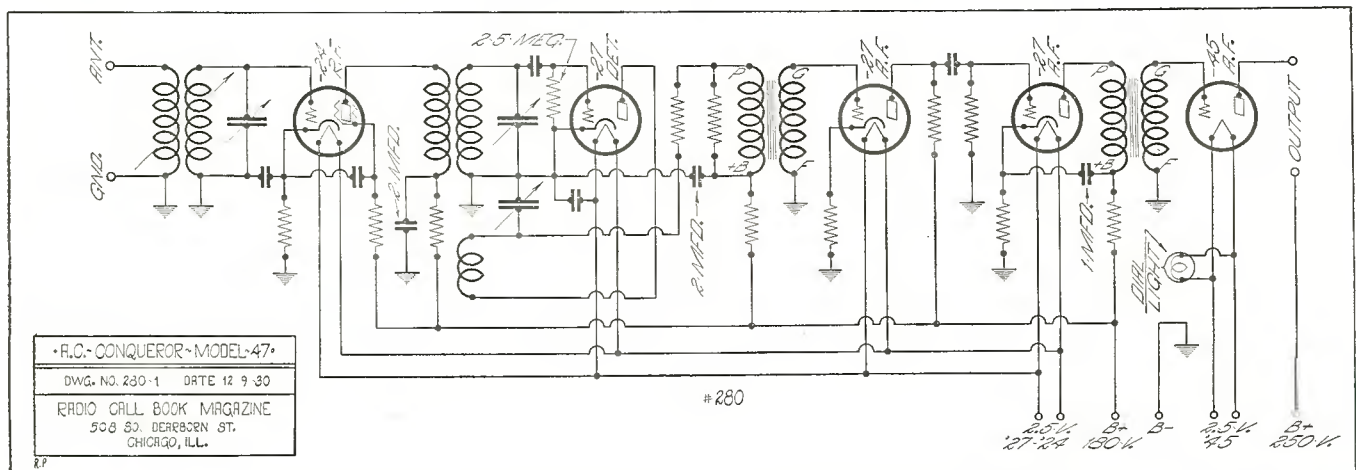


Fig. 2. In this illustration will be found the schematic diagram of the receiver described on this page. Any well filtered power supply with the voltages indicated may be used if desired





# Aligning RF and IF in Radiola Supers

## FACTORY SCHEMATIC INDEX

Name	Model	Vol.	No.	Month	Year	Page	SR. No.
A. C. Dayton	Navigator	10	4	Nov.	1929	94	24
Acme Mfg. Co.	AC7	10	10	March	1929	92	3
Acme Mfg. Co.	AC4	10	2	March	1929	93	4
All-American Mohawk	90	11	4	Nov.	1930	80	74
All-American Mohawk	6	10	2	March	1929	94	1
All-American Mohawk	8	10	2	March	1929	93	2
American Bosch	28-29	10	4	Nov.	1929	91	21
Amrad	70	10	4	Nov.	1929	92	22
Amrad	81	11	1	March	1930	81	44
Amrad	84	12	1	Jan.	1931	70	106
Apex	48	11	4	Nov.	1930	79	80
Apex (U. S. Radio)	31	12	1	Jan.	1931	68	108
Atwater Kent	38	11	1	Jan.	1930	72	28
Atwater-Kent (cap.)	55, 55-C	11	3	Sept.	1930	82	51
Atwater-Kent (Ind.)	55, 55-C	11	3	Sept.	1930	82	52
Audiola	31	11	4	Nov.	1930	79	79
Balkett	A	10	3	Sept.	1929	85	12
Bosch	43	11	4	Nov.	1930	81	73
Bosch	48	12	1	Jan.	1931	67	109
Bosch Auto	80	11	4	Nov.	1930	82	94
Bremer-Tully	7-70	10	3	Sept.	1929	83	10
Bremer-Tully	81-82	11	4	Nov.	1930	80	75
Brunswick	3KRO	10	4	Nov.	1929	93	23
Brunswick	815	10	4	Nov.	1930	76	86
Brunswick	814	11	4	Nov.	1930	81	71
Colonial	81AC	11	1	Jan.	1930	73	99
Colonial	33 AC	11	4	Nov.	1930	74	61
Crosley	Roamto	11	3	Sept.	1930	71	67
Crosley	408, 418, 428, 828	11	3	Sept.	1930	79	57
Crosley	608 Gembox	10	2	March	1929	95	5
Crosley	705 Showbox	10	2	March	1929	96	6
Crosley	Jewelbox 704B	11	2	March	1930	78	41
Crosley	57	11	4	Nov.	1930	69	83
Crosley	53, 54, 57	12	1	Jan.	1931	66	103
DayFan	5080	10	3	Sept.	1929	84	11
DeLoe Auto. Radio		11	3	Sept.	1930	70	66
Edison	R4, R5, C4	11	3	Sept.	1930	69	49
Edison	R4, R5, C4	11	4	Nov.	1930	77	49
Edison	R6, R7	12	1	Jan.	1931	64	99
Erla	DuoConcerto	11	1	Jan.	1930	77	33
Fada	7AC	10	3	Sept.	1929	86	13
Fada	35-35Z	10	4	Nov.	1930	78	70
Federal	11	10	4	Nov.	1929	89	19
Freed-Eisemann	NR80	10	4	Nov.	1929	90	20
Freshman	2-N-12	10	3	Sept.	1929	87	14
General Motors		11	3	Sept.	1930	69	68
General Motors		11	4	Nov.	1930	82	68
Giffman Bros.	100	11	1	Jan.	1930	76	32
Graybar Electric Co.	600	11	2	March	1930	79	79
Grebe	7AC	10	4	Nov.	1929	87	47
Grebe	AH1	11	4	Nov.	1930	75	96
Gullbransen	Nine-in-Line	11	2	March	1930	77	40
Howard	S.G.A.	11	3	Sept.	1930	72	56
Howard	8	10	3	Sept.	1929	89	16
Kellogg	523-528	11	4	Nov.	1930	73	77
Kennedy, Colin B.	20	11	2	March	1930	75	48
Kennedy, Colin B.	26	11	4	Nov.	1930	71	81
Kennedy, Colin B.	10	12	1	Jan.	1931	73	38
King Mfg. Co.	J	11	1	Jan.	1930	75	31
Kolster	4	10	3	Sept.	1929	81	8
Kolster	21-23	11	2	March	1930	82	45
Kolster	K-43	11	4	Nov.	1930	70	72
Kyleston	70	11	4	Nov.	1930	78	65
Majestic	90B	10	3	Sept.	1929	80	19
Majestic	130-A	11	4	Nov.	1930	89	55
Majestic	50	12	1	Jan.	1931	68	84
Philco	86-82	10	4	Nov.	1929	96	26
Philco	95	11	3	Sept.	1930	78	60
Radiette	F14	12	1	Jan.	1931	73	104
RCA	60	11	1	Jan.	1930	74	30
RCA	66	11	3	Sept.	1930	81	64
RCA	44	12	1	Jan.	1931	71	102
Silver	36A	12	1	Jan.	1931	69	107
Silver-Marshall	30B	11	3	Sept.	1930	73	53
Silver-Marshall	30	11	1	Jan.	1930	79	35
Silver-Marshall	35-A	11	4	Nov.	1930	72	82
Single	9	11	1	Jan.	1930	71	27
Single (Continental)	R-20	11	2	March	1930	83	46
Sonora	5R	10	4	Nov.	1929	95	25
Sparton	ACS9	10	3	Sept.	1929	82	9
Sparton	589	11	3	Sept.	1930	76	63
Splindorf	E175	11	1	Jan.	1930	80	36
Stemite	261	10	3	Sept.	1929	88	15
Stemite	70-80-95	11	4	Nov.	1930	81	76
Stewart-Warner	930	11	3	Sept.	1930	74	62
Stewart-Warner	Series 900	11	1	Jan.	1930	78	34
Stewart-Warner	R100	12	1	Jan.	1931	73	85
Stromberg-Carlson	846	11	3	Sept.	1930	75	54

SO much interest has been shown by service men in seeking data covering servicing of the recently announced superheterodynes under the Radiola, G. E., Westinghouse and Graybar banners, that it is felt desirable to quote here at length the alignment procedure covering the r.f. and i.f. stages of these 175 kc. superheterodynes.

### All Super Chassis Alike

The following instructions are excerpts from the service manual on the Westinghouse WR-5, and as such will apply to all the Radiola, General Electric and Graybar superheterodynes. The General Radio type 360 oscillators mentioned in the instructions are those originally built to R. C. A. specifications for their service organizations.

"Five adjustable condensers are provided for the lining up of the r.f. circuits and shifting the oscillator frequency so it will be at a 175 kc. difference from the incoming r.f. signal throughout the tuning range of the set. Poor quality, insensitivity and possible inoperation of the receiver may be caused by these condensers being out of adjustment.

"If other adjustments have not been tampered with (the intermediate tuning and gang-condenser line-up condensers) the following procedure may be used for adjusting these condensers:

### R. F. Alignment

"(a) Procure an r.f. oscillator giving a modulated signal at exactly 1400 kc. and 600 kc. The General Radio Co., types 320 or 360 after calibration by G. R. Co., will be suitable. A non-metallic screwdriver 1/4-in. in diameter is also necessary.

"(b) An output indicator is necessary. This may be a current squared galvanometer connected to the secondary of the output transformer instead of the cone coil of the reproducer

Stromberg-Carlson	635-636	10	4	Nov.	1929	88	18
Stromberg-Carlson	12-14	11	4	Nov.	1930	67	23
T. C. A. Clarion	50	11	4	Nov.	1930	79	78
Temple	8-60	11	2	March	1930	74	37
Transitone Auto Radio		11	4	Nov.	1930	80	69
U. S. Radio & Television		11	2	March	1930	76	39
Victor	R32, RE45, R52	11	3	Sept.	1930	77	61
Victor	R35, R39, RE57	12	1	Jan.	1931	65	101
Westinghouse	WR-5	11	4	Nov.	1930	66	92
Westinghouse	WR-4	12	1	Jan.	1931	72	107
Zenith	52	11	2	March	1930	80	43
Zenith	70	11	4	Nov.	1930	56	97

unit, an 0.5 millimeter connected in series with the plate supply to the second detector (lead No. 1) or the output devices included in the General Radio oscillators. In the type 320 the meter leads should be connected in the second detector plate circuit and in the type 360 across the cone coil connections of the loudspeaker. The cone coil may remain in place or be disconnected, satisfactory results being obtained in either case.

“(c) Locate the 600 kc. trimming condenser, and turn the adjusting screw until it is about  $\frac{3}{4}$  of the way in. Set the “Local-Distant” switch at “Distant.”

“(d) Set oscillator in operation at exactly 1400 kc. Place the set in operation and tune in the signal. Make sure the receiver is properly grounded and has an average antenna. Adjust the volume control until a reading is obtained in the output meter. While making adjustments regulate the volume control so that an excessive reading is not obtained. Then adjust the selector knob until the scale reads 1400 kc. Now adjust the oscillator, 1st detector r.f. and link circuit trimming condensers in the order given until maximum output is obtained.

“(e) Set the oscillator at exactly 600 kc. Tune in the signal on the set and adjust the 600 kc. oscillator trimming condenser, for maximum output while rocking the gang condenser back and forth. The dial scale should read exactly 600 kc. If it does not read 600 kc. loosen the screws that hold the scale and slip it until it reads  $\frac{1}{2}$  the error from 600 kc. on the opposite side of

600 kc. For example, if the scale reads 620 kc. at maximum output set the scale at 590 kc. Another example would be if the scale read 580 kc. to set it at 610 kc.

“(f) Shift the oscillator frequency to 1400 kc. and set the selector scale at exactly 1400 kc. Now adjust the four trimming condensers in the order given under (d) until maximum output is obtained.

“(g) Place the oscillator again in operation at 600 kc. and tune in the signal with the receiver. If adjustments have been properly made, the signal will be received at maximum output when the scale reads exactly 600 kc. If not, then the operations given under (e) and (f) must be again repeated.

“With this adjustment so that the scale is exactly at 600 and 1400 all other dial readings will be correct within very close limits.

### Adjustment of I. F. Tuning Condensers

“Two screen-grid intermediate frequency amplifier stages are used in this set. Three transformers are necessary for coupling these two stages. Both the primary and secondary of each transformer is accurately tuned to 175 kc. and the correct functioning of the receiver is dependent on the proper alignment of the i.f. stages.

“The first i.f. transformer (the one in the copper container) has its two windings very loosely coupled, this condition being further accentuated by having copper shield placed between each winding, which makes possible very sharp tuning of this first i.f. stage

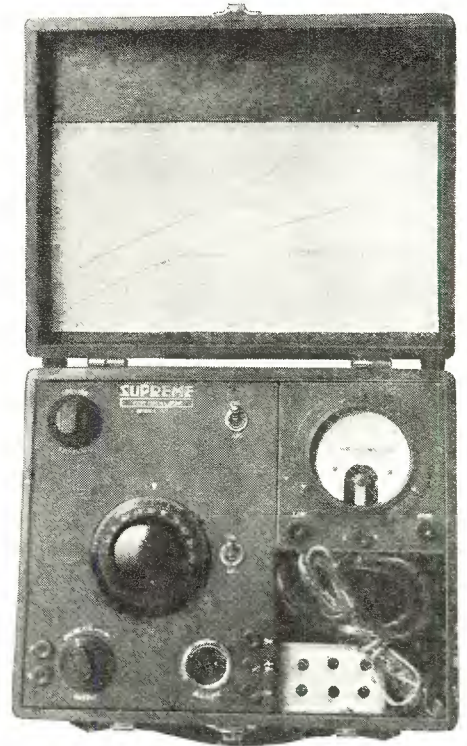


Fig. 2. Above is illustrated the recently announced model 70 made by the Supreme Instruments Corp., of Greenwood, Miss.

unless the “Local Distant” switch is in the local position and resistance is artificially added to the circuits. The other two transformers have their winding closely coupled (overcoupled) so that a broad top effect is obtained in the tuning curve. The reason for discussing the i.f. curve is that this type of coupling has a bearing on the method to be used for lining up the i.f. transformers. The second and third transformers being over-coupled, their tuning condensers are adjusted until a plus or minus equal frequency shift of the i.f. oscillator frequency will give the same output, and a flat top effect is obtained on the tuning curve. This is not the adjustment of the condensers that will give a maximum output and is a different procedure from that used in previous superheterodyne receivers. The first transformer being closely coupled the tuning condensers are adjusted for maximum output.

### Detailed Procedure

“A detailed procedure for making these adjustments follows:

“A modulated r.f. oscillator giving a signal at 175 kc. and having a vernier condenser for shifting this frequency from 171 kc. to 179 kc. is necessary for aligning the i.f. stages of this set. The General Radio Co.’s type 360 oscillator gives this frequency variation, but calibration of these secondary points must be made on instruments purchased prior to June 1, 1930. On these earlier models and on the older General Radio type 320 oscillators to which the 175 kc. frequency has been added, the General

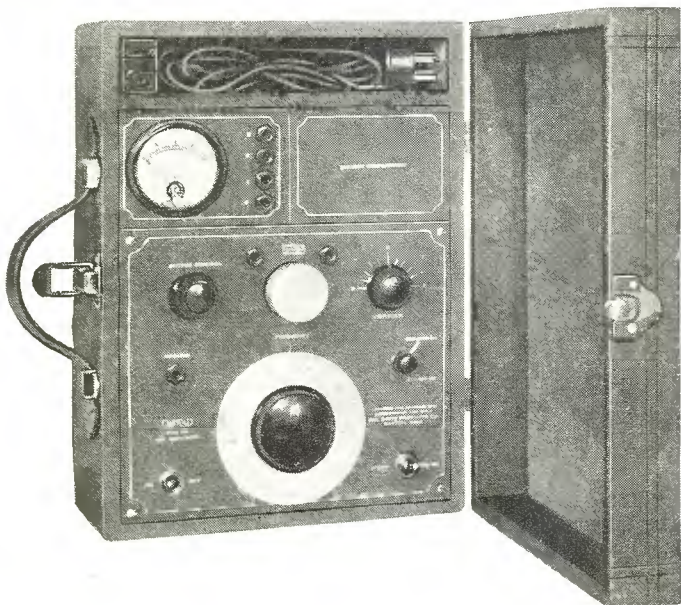


Fig. 1. This is one of the test oscillators designed by the Radio Products Co., of Dayton, Ohio, for use by service men in making alignment checks on receivers both t.r.f. and superheterodyne. It is known as the model 180

Radio Co. will add such calibrations, together with a 600 kc. and 1400 kc. calibration at a nominal cost.

"A nonmetallic screwdriver  $\frac{1}{4}$  inch in diameter is also necessary for making these adjustments. With the necessary equipment at hand, proceed as follows:

"(a) Place the set in such a position that access to all mechanism is obtained.

"Place the receiver in normal operation with the volume control at minimum and then remove the oscillator tube. (Socket No. 2.) Make sure a good ground connection has been made.

"(b) Connect output meter in circuit. The meter leads of the type 320 oscillator should be connected in series with lead No. 1 of the s.p.u. terminal strip.

"The type 360 output meter should be substituted for the cone coil of the reproducer unit and the switch on the oscillator set at 'Dynamic.'

"(c) Place the oscillator in operation at 175 kc. and connect the coupling lead to the control grid connection of the second i.f. tube. (Socket No. 4.) If excessive output is obtained, disconnect the coupling lead from the oscillator and place it a short distance away, but in such a position that will cause an indication in the output meter without causing the needle to go beyond the scale.

"(d) Adjust the secondary and then the primary of the third i.f. transformer until a maximum reading is obtained in the output meter. After obtaining maximum output we know the two windings are closely adjusted to the same frequency. Now they must be readjusted until a flat top effect is obtained in the tuning curve. The flat portion should be at least 5 kc. in width. The method of doing this is to shift the oscillator frequency back and forth from 171 kc. to 179 kc. and noting, when the condensers are adjusted, that no appreciable change in output reading is obtained from 172.5 kc. to 177.5 kc. Also the drop in output should be the same at 171 kc. and 179 kc. This indicates that the flat top is centered at 175 kc. The usual method to obtain this characteristic is, after adjusting to maximum output to adjust the capacity of the secondary condenser until the flat top effect is obtained. It will probably not be centered at 175 kc. It is, however, easy to shift its center point by increasing each condenser slightly to shift it to a lower frequency or decreasing both condensers slightly to increase its frequency. To make this adjustment the first time will be somewhat difficult, but after a little experience it is equally as easy as other superheterodyne adjustments.


"(e) After adjusting the third i.f. transformer, shift the coupling lead to the control grid connection of the 1st i.f. tube and place it at a greater distance from the oscillator. Then advance the volume control to maximum. If necessary, reduce this coupling to an even greater extent so that too great an indication is not obtained in the output meter.

"(f) Now adjust the secondary and primary condensers until a maximum output is obtained. Then readjust in the same manner as with the third transformer until a flat top effect is obtained. This may not be quite as broad as the third transformer.

"(g) If the 'Local Distant' switch is not already so adjusted, place it in the 'Distant' position. Then shift the coupling lead to the control grid connection of the first detector. (Socket No. 3.) Now adjust the volume control until the meter reading is not excessive and then adjust the secondary and primary of the 1st i.f. transformer condensers until maximum output is obtained. This transformer tunes very sharply and no further adjustments are necessary.

"This completes the i.f. tuning adjustments and when so made, the set will perform at maximum efficiency."

### Adding Pickup Unit to the WR5

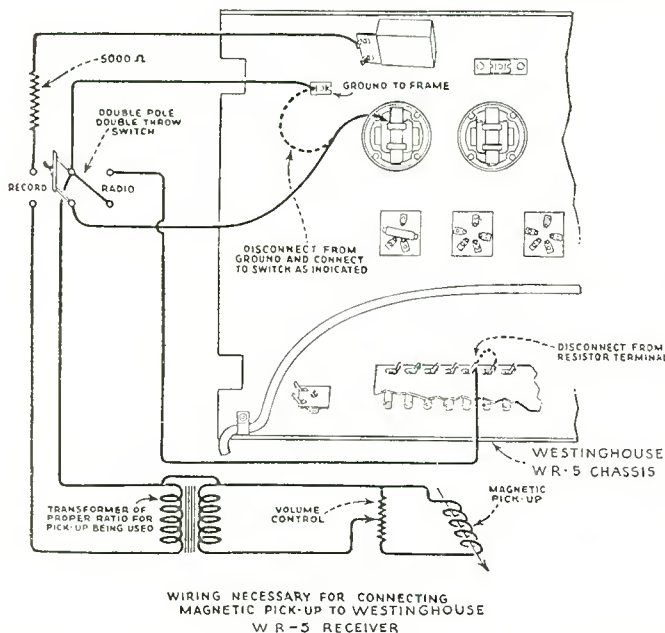

Numerous requests have been made of our editorial department for data on the wiring changes necessary to provide for the employment of a magnetic type pickup on the Westinghouse WR-5 superheterodynes. This data has just been made available to us by the Westinghouse interests and the drawing at the left embodies the changes recommended by the makers of the receiver

voted to the following: measuring instruments, resistance units, oscillators, tube testers, vacuum tube voltmeters, capacity tests, inductance tests, audio and output systems. The information given the service man is concise and complete; the volume well worth more than its price.

Mr. Rider will be remembered as the author of "Mathematics of Radio," "Radio Trouble Shooter's Manual," "Sound Pictures and Trouble Shooter's Manual," etc.

### Stewart-Warner Service

HERE'S an interesting letter from David C. Dodge, of the Stewart-Warner Sales Co., 1344 Broadway, Denver, Colo., which covers service methods:

"Permit me to brag a little. Less than one-half of 1 per cent of the model 100 series Stewart-Warner radios sold in this territory have required service.

"Inasmuch as we are wholesalers only, we feel we would be taking business away from our dealers if we maintained an extensive service department. Therefore we work only on Stewart-Warner sets, and our testing equipment is of the usual type: tube tester, set tester for continuity also containing ohmmeter, oscillator, etc."

### Practical Testing Systems

A COMPREHENSIVE review of the practical testing systems available to the service men, and bearing the title given above, has recently been received by our editorial department. It is the work of John F. Rider, well known

writer of radio textbooks, and is published by the Radio Treatise Co., Inc., 1440 Broadway, New York. The volume lists at one dollar.

A glance at the contents will readily show the scope of the book, which is well illustrated schematically throughout. Among the chapters are those de-

# Increasing the Utility of D. C. Meters

By JESSE MARSTEN\*

THE business of servicing a radio set or any speech equipment is a matter of determining the causes for a non-operative or poorly operative condition. Where the question is not a matter of fundamental design or construction, or an adjustment of a variable circuit element, such as a trimming condenser, the service problem resolves itself essentially into a determination of defective tubes or incorrect voltages.

A set delivering the proper voltages to the terminals for which they are intended would generally indicate continuity of circuits and satisfactory operating conditions—with a few exceptions, such as shorted variable condensers. Consequently a first determination of operating voltages at the tube terminals would give the major clues to the source of trouble. For example an open bias resistor or secondary of an r.f. or a.f. transformer will show up as absence of bias on the tube. An open primary would be evidenced by absence of voltage on the plates of tubes. Wrong values of bias resistor or voltage divider resistors would be shown by incorrect bias or plate voltages. Shorted filter condensers would result in no voltages being delivered from the power pack, and so on. By the same token current measurements may likewise be used as indices of satisfactory operating conditions, particularly so as regards the condition of the tubes. Thus plate current measurement under conditions recommended by the tube manufacturers will show the presence or absence of sufficient electron emission for satisfactory results.

Such a wide range of voltages and current are encountered in normal practice, that, in the absence of a multiplicity of meters or an elaborate test set, considerable difficulty would be experienced in making such tests.

For example, the d.c. currents in an average receiver vary from less than 1 milliampere to over 100 milliamperes, and the voltages from 1½ volts to 400 volts. In special receivers and speech equipment this range is considerably greater, currents going as high as 250 milliamperes, and voltages to 1000 volts.

### A Universal Meter

A test meter which has come into almost universal use is the 0-1 milliammeter, or 0-1.5 millimeter. By itself it has a limited degree of usefulness as a measuring instrument. But its sphere of utility may be considerably enlarged by the addition of suitable resistors of proper value, and the application of some elementary principles of electricity.

Its range as an ammeter can be increased to cover all ranges normally


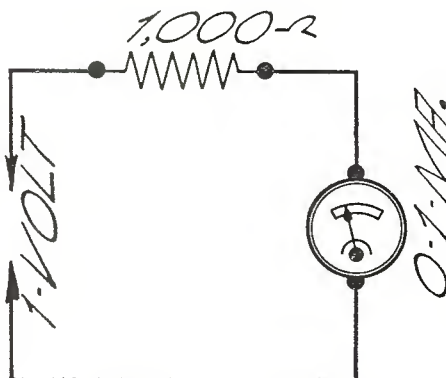


FIG:2

met in practice, and it may also be used as a voltmeter up to 1000 volts or more if necessary. The reason for this is that direct current ammeters and voltmeters are essentially the same from the point of view of construction. A voltmeter is really an ammeter calibrated to read volts. The two instruments differ only in their manner of being connected in the circuit to be measured, ammeters being connected in series with the circuit in which current is to be measured, voltmeters being connected in parallel with the circuit to be measured.

Fig. 1 shows a milliammeter (A) connected in series with a line, and a similar milliammeter in series with a resistor R connected across or in parallel with the line. Instrument A measures the total load current, for example, the plate current of a tube. Instrument B measures the current flowing through the resistor R and itself, the current

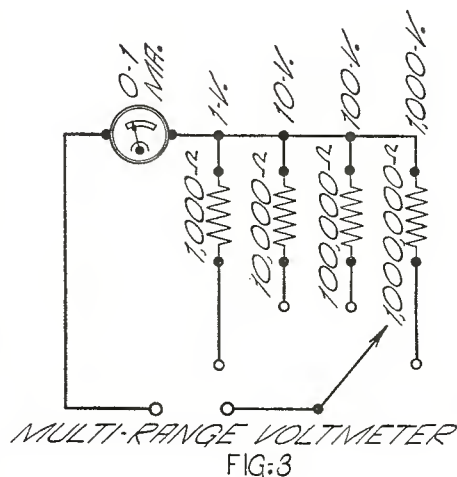

MULTI-RANGE VOLTMETER  
FIG:3

being supplied by the source of voltage E. According to Ohm's law

$$E = IR \text{ or } I = \frac{E}{R}$$

If R is kept constant, the current through ammeter B will be proportional to the voltage. Therefore, it is possible to calibrate the milliammeter B in volts.

To take a specific case, in Fig. 2 we have a 0-1 milliammeter with a resistance of 1,000 ohms in series. Assuming the resistance of the ammeter to be negligible, if a source of voltage is applied to the two terminals A B, sufficient to cause a current of 1 m.a. to flow through the system this voltage will be given by

$$E = IR = 1 \text{ ma.} \times 1000 \frac{1}{1000} \times 1000 = 1 \text{ volt}$$

With this external resistance of 1000 ohms, called a multiplier, the meter will measure a maximum voltage of 1 volt. Higher voltages may be measured by increasing the value of the multiplier resistance. To determine the value of multiplier resistance R required to convert a milliammeter having a maximum reading I, into a voltmeter to read a maximum voltage V, use the following formula:

$$R = \frac{1000 \times V}{I}$$

To illustrate: It is desired to convert a 0-1.5 milliammeter into a voltmeter to read up to 750 volts. V = 750 volts, I = 1.5.

$$R = \frac{1000 \times 750}{1.5} = 500,000 \text{ ohms}$$

A wide range of voltages can be covered by using a number of multipliers with a switching arrangement each cov-

\*Chief Engineer, International Resistance Company.

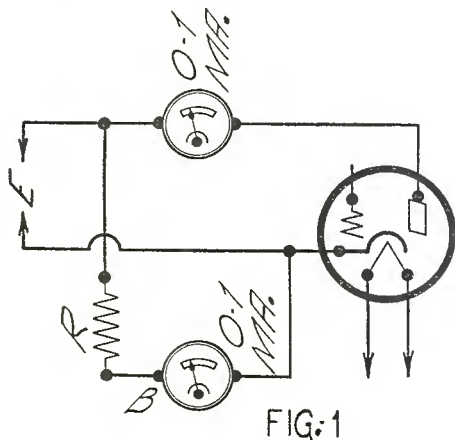


FIG:1

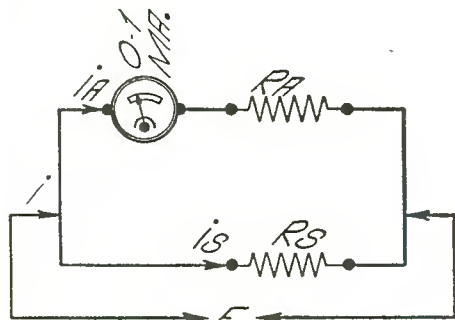


FIG. 4

ering a different range. Thus Fig. 3 shows a 0-1 milliammeter with suitable resistors for converting it into a multi-range voltmeter reading 0-1, 0-10, 0-100, 0-1000 volts.

**Increasing Voltmeter Range**

Where a voltmeter of a given range is available it is possible to increase the range by simple extension of the foregoing principles. It is necessary, however, to know the resistance of the voltmeter. This may be marked on the face of the meter or the resistance per volt may be marked on the meter. If the latter is the case the total resistance will be given by the product of the maximum reading of the voltmeter and the resistance per volt. Thus, if the resistance per volt is 1000 ohms and the voltmeter is a 0-100 meter, the total resistance is 100,000 ohms.

Suppose it is desired to increase the range of a voltmeter 0-V volts having a resistance  $R_v$ , by a factor  $n$ , i. e., we want the meter to read  $nV$  volts. The multiplier  $R_m$  required will be given by the formula:

$$R_m = (N-1) R_v$$

To illustrate: We have a voltmeter reading 0-100 volts, having a resistance of 1000 ohms per volt, and it is desired to increase its range to read 500 volts. The total resistance of the voltmeter  $R_v$  is  $100 \times 1000 = 100,000$  volts. It is desired to increase its range 5 times  $500 = 5 \times 100$ ; therefore  $N = 5$ . The multiplier resistance required is therefore—

$$R_m = (N-1) R_v = (5-1) \times 100,000 = 400,000 \text{ ohms}$$

**Increasing Milliammeter Range**

To enable a milliammeter to read higher currents than that for which it is designed it is necessary to use shunt resistors rather than series, as shown in Fig. 4. A measurable portion of the total current to be measured flows through the meter and the balance flows through the shunt. By properly choosing the shunt resistor  $R_s$  a simple proportionality factor may be obtained relating to the total current to the measured current.

In Fig. 4 let  $R_a$  = resistance of ammeter

let  $R_s$  = resistance of shunt

let  $E$  = voltage applied

across meter and shunt

let  $i_a$  = current through ammeter

let  $i_s$  = current through shunt

let  $I$  = total current =  $i_a + i_s$

let  $N$  = factor by which ammeter range is to be increased, i. e.,  $1 = Ni_a$

Then the following relations are true

$$i = i_a + i_s$$

$$i = Ni_a$$


$$e = iaRa$$

$$e = i_s R_s$$

From these four relations by simple arithmetic the following formula can be deduced:

$$R_s = \frac{R_a}{N-1}$$

which gives the value of the shunt re-

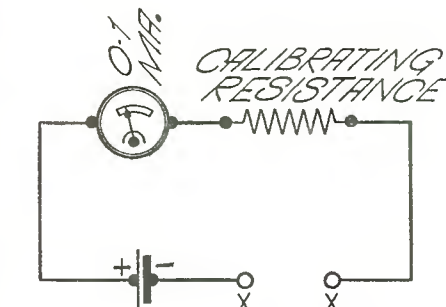

FUNDAMENTAL CIRCUIT OF OHMMETER

FIG. 5

sistor required to increase an ammeter range by a factor  $N$ .

To illustrate: Suppose we have a 0-1 milliammeter whose resistance  $R_a$  is 30 ohms, and we desire to increase its range 10 times ( $n = 10$ ); i. e., we want it to read up to 10 ma. The shunt resistor required will be given by

$$R_s = \frac{R_a}{n-1} = \frac{30}{10-1} = \frac{30}{9} = 3\frac{1}{3} \text{ ohms}$$

**Converting Milliammeter Into Ohmmeter**

The conversion of a milliammeter into an ohmmeter is a direct application of Ohm's law, which is

$$I = \frac{E}{R}$$

$R$  is the circuit resistance

$E$  is the voltage drop across the resistor

$I$  is the current through the resistor

If this current is measured by an ammeter, and the voltage  $E$  is kept constant, the current  $i$  will be inversely proportional to the resistance in the circuit, and for given conditions it would therefore be possible to calibrate the ammeter in ohms.

The circuit commonly employed in this conversion is shown in Fig. 5. A battery of definite voltage is used in series with a resistance  $R$ , called a calibrating resistance, in series with a 0-1 milliammeter. The unknown resistor  $R_x$  is connected to the terminals  $X$ . This calibrating resistance  $R$  must be chosen with reference to the battery voltage  $E$ , so that when a short circuit is applied across  $X$  the meter reads maximum current, 1 milliampere. Thus suppose we use a  $4\frac{1}{2}$  volt battery as the source of voltage. With the terminals  $X$  short circuited,  $R$  must be 4,500 ohms in order that the maximum current 1 ma. be the current flowing

$$I = \frac{E}{R} = \frac{4.5}{4,500} = 1 \text{ ma.}$$

In other words whenever the current reads 1 ma. with this arrangement, we know that the circuit connected to terminals  $X$  has zero resistance, or is short circuited. Suppose a resistance of value 4,500 ohms is now connected across terminals  $X$ . The current registered by the milliammeter will be given by


$$I = \frac{E}{R + R_x} = \frac{4.5}{4,500 + 4,500} = \frac{4.5}{9000} = 0.5 \text{ ma.}$$

and whenever this meter reads 0.5 ma. with this arrangement we know that the circuit or resistor connected across terminals  $X$  has a resistance of 4,500 ohms.

In the same way every reading on the milliammeter will correspond to some definite resistance, and for a given battery voltage and calibrating resistance the meter can be calibrated in ohms. The range and scale may be modified, by altering the values of battery voltage and calibrating resistance. Increasing the voltage and calibrating resistance increases the value of the maximum resistance that can be measured.

The last figure shows typical 0-1 ma. scales converted into direct reading ohmmeters. A single scale is made for a voltage of 1.5 and a calibrating

(Continued on page 80)

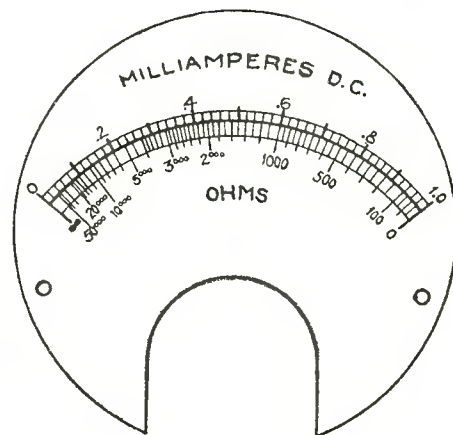

# Service Data on the New

REPRESENTING as it does a departure from the circuits employed in previous receivers of that name, the Majestic chassis model 50 (used in model 52 receivers), photographed on this page, is a superheterodyne using 175 kc. intermediate frequency amplification. The diagram in Figure 4 gives all the electrical connections of the receiver and its power supply; Figure 1 shows the rear of the chassis, indicating position of the i.f. aligning condensers, and the aligning condenser for the oscillator tracking; Figure 2 is a bottom view of the chassis, showing position of the antenna alignment condenser, and the oscillator alignment screw. The table of average operating tube voltages is shown in Figure 3.

Perhaps the most important data on servicing this receiver is the information covering the alignment procedure. The model 50 chassis being a superheterodyne, employs a somewhat different procedure of alignment from previous Majestic models.

Oscillator alignment condenser is accessible from the bottom side of the chassis, and is located next to the end of the gang condenser on which the cable drive is mounted. See Fig. 2.

Second antenna alignment is accessible from the bottom side of the chassis and is located through the center hole of the chassis bottom. See Fig. 2.

First antenna alignment (compensating) condenser is accessible from the back side of the chassis, slightly upward and to the right of the antenna and ground binding posts. See Figure 1.

The oscillator tracking condenser is accessible from rear side of the chassis through a hole in the r.f. base assembly just to the right of the power transformer. See Fig. 1. The i.f. alignment

positions are also indicated in this photograph.

## Alignment Procedure

Tune in at approximately 1280 kc. and align oscillator and antenna circuits.

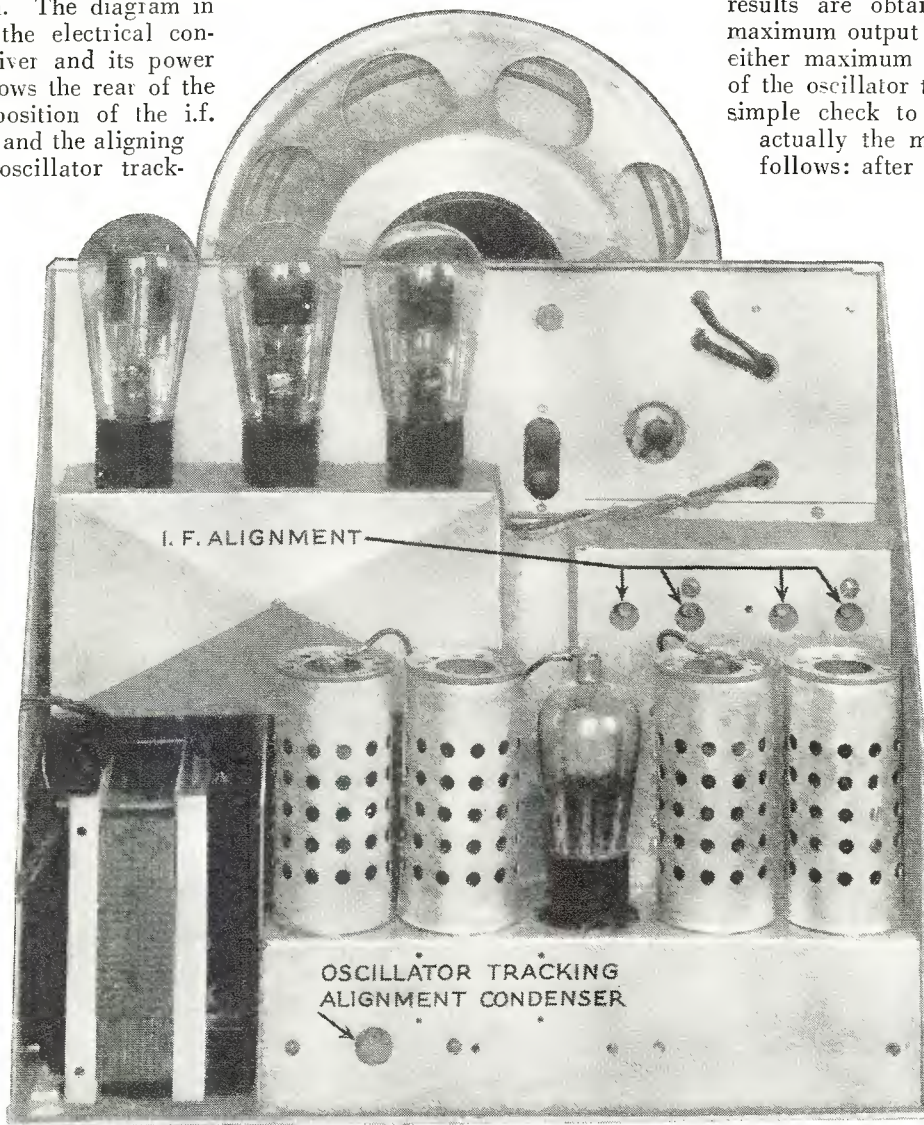


Fig. 1. This photograph of the new Majestic 50 chassis shows the position of the antenna compensating condenser, the four i.f. alignment positions and the oscillator tracking alignment condenser

Tune in at approximately 600 kc. and adjust the oscillator tracking condenser on chassis while rotating the tuning knob slightly back and forth until the maximum signal strength is noted on the output meter.

Next set main tuning dial to exactly 1500 kc. and tune in 1500 kc. signal with oscillator alignment condenser.

Retune antenna alignment condenser.

The dial setting should be checked by tuning in a broadcast station with a known frequency higher than 1000

kc. Slip the dial strip to the correct setting with respect to the index of the dial escutcheon.

Carefully test receiver for sensitivity and selectivity, and if necessary the entire operation outlined previously should be repeated until satisfactory results are obtained. In some cases maximum output may appear to fall at either maximum or minimum capacity of the oscillator tracking condenser. A simple check to determine if this is actually the maximum output is as follows: after obtaining the best setting

of the tracking condenser, try a slight readjustment of the second antenna alignment condenser. If this readjustment results in only a slight improvement, the oscillator tracking condenser is satisfactorily adjusted.

## I. F. Alignment

For intermediate frequency alignment, connect the output of the i.f. oscillator to the grid of the first detector. Tune oscillator at 175 kc. and align the first detector plate circuit, intermediate frequency grid circuit, intermediate frequency plate circuit and the second detector grid circuit to this frequency. This alignment should be done with great caution, inasmuch as it materially affects the entire selectivity of the receiver.


If the intermediate frequency circuits are so far out of alignment that no signal can be heard, it may be necessary to put the oscillator output on the grid of the i.f. tube and roughly align the second half of the i.f. stage first, and then proceed as above indicated. The four aligning condensers are located on the rear of the chassis about midway down on the right side (see Fig. 1). From left to right, facing the rear of the chassis, these positions are: first detector plate; i.f. grid; i.f. plate; second detector grid.

# Majestic Model 50 Chassis

A small compensating condenser is provided to adjust the reflected capacity of the antenna. Adjustment of this condenser is possible through the hole in the rear of the chassis (to the right and above the antenna-ground binding posts in Figure 1). When the installation of the receiver is complete, a station between 1000 and 1400 kc. should be tuned in; volume control set for low volume, and the antenna compensator adjusted until maximum volume is secured. Further adjustment of this condenser is not necessary unless the length or position of the antenna is changed.

The volume control consists of two

Fig. 2. Here are shown the antenna alignment (second) position, and the position of the oscillator alignment screw, both of which are mentioned in the text covering the alignment procedure

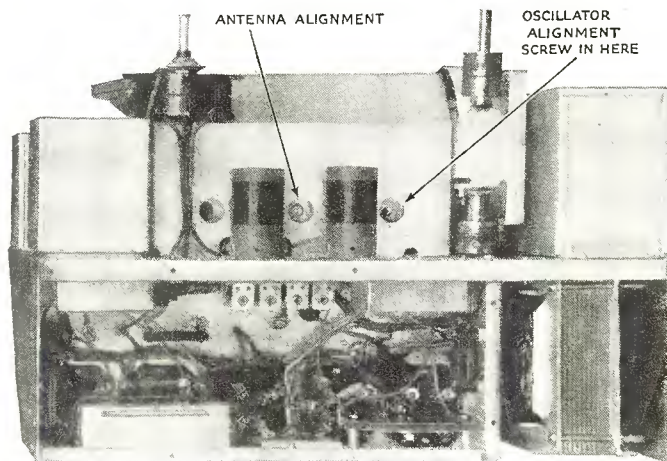

## Majestic Model 50 Chassis

Tube Type	Position in Set	A Volts	B Volts	C Volts	Cathode Volts	Screen Volts	Normal Plate M. A.	Plate M. A. Grid Test	Change
224	1 R.F.	2.35	180	3	3	90	3.	---	---
227	Osc.	2.35	90	---	---	---	3.	---	---
224	1 Det.	2.35	180	8	8	90	.8	---	---
224	1 I.F.	2.35	256	3	3	90	4	---	---
227	2 Det.	2.35	225	20	20	---	.5	---	---
245	P.P.	2.35	250	1.75*	---	---	25	---	---
245	P.P.	2.35	250	1.75*	---	---	25	---	---
280	Rect.	4.8	358	---	---	---	40	---	---

Line voltage 115. Volume control maximum.

\*On analyzer 245 grids may read 1.75 volts. If so, to get true reading measure with voltmeter from filaments to ground. This should be 37.5 volts.

According to the Majestic manual on this receiver, under no conditions should an attempt be made to use a ground connection on the antenna binding post. Be certain that the antenna and ground wires are connected to their respective binding posts and that they have been passed through hole in the back of the cabinet as indicated by label.

In territories where the a.c. line voltage is excessive, it is desirable that a voltage control be used. This may be secured from the Majestic distributor and should be used in every case where the line voltage exceeds 113 volts. This voltage regulator has three outlets marked 110, 120 and 130. The receiver plug should be inserted in the proper outlet, as determined by the service man's investigation of the line voltage. If the voltage regulator is not used where line voltage is excessive, rated normal tube life will be reduced.

elements, a 645-ohm potentiometer and a 10,000-ohm rheostat; the latter connected to antenna to ground and varying the signal input from antenna; the former controlling the bias voltage for the r.f. and first detector tubes. Both controls are operated simultaneously by the same shaft.

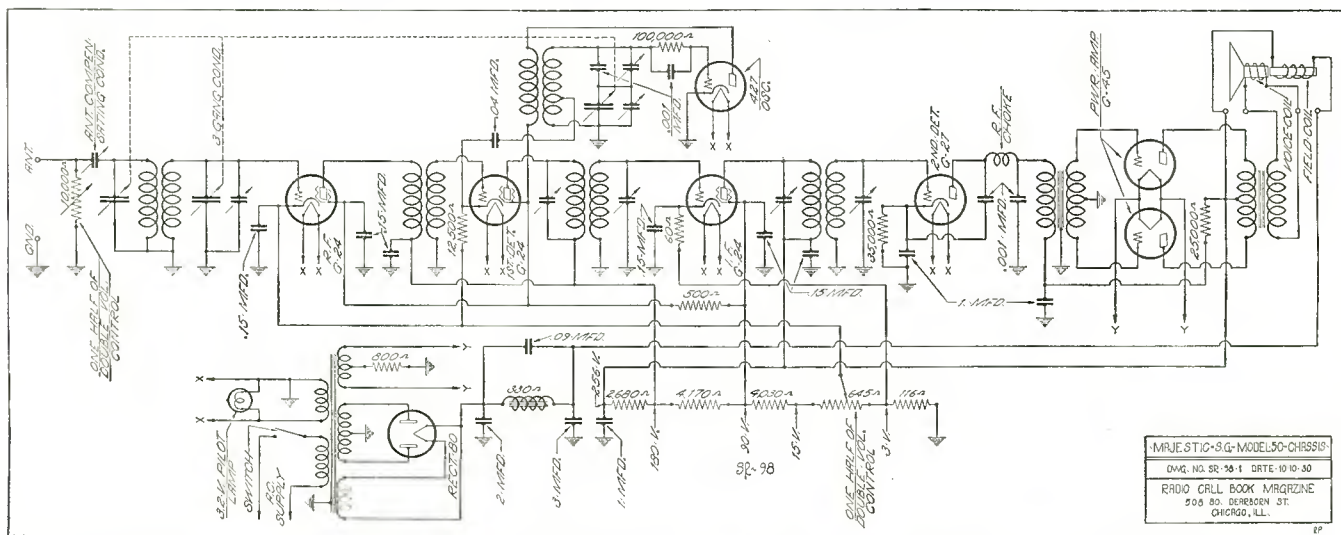


Fig. 4. The electrical details of the circuit employed in the Majestic model 50 chassis are given in this drawing

# Locating Internal Noises in Receivers

By F. L. SPRAYBERRY\*

**I**NTERNAL noise in a receiving set is a real problem to the average serviceman. Usually he can locate ordinary defects in a receiver such as grounded circuits, burnt out by-pass condensers and defective resistors. But it takes a real expert to locate and overcome the elusive internal noises that are often encountered.

The purpose of this article is to help the serviceman locate and overcome these difficult problems.

Radio receivers are very sensitive devices and once noise gets into the receiver it is amplified and passed on to the speaker in the same way speech and music are passed on. Some of these noises originate outside the receiver and some originate inside. All noises cannot be eliminated or reduced, but a great many can. The causes of noises arising in the receiver are so numerous that it would be futile to attempt to describe each one separately. These noises may be due to poor design, poor construction or defective parts. Fortunately, there are certain noises which can be classified into a few major groups.

## Mechanical and Electrical Noises

Under these two broad general classifications of noise in a receiver, we have first a noise which reaches the ear by way of the loudspeaker which is the amplified impulse through the regular amplifying system. Second, there are noises which reach the ear directly without being transmitted electrically through the receiver. These latter noises are frequently as troublesome a source of disturbance as the former. As typical examples of the first class we have intermittent opening and closing of contacts in a circuit. This may be in the form of a defective connection or a defective condition of one or more of the parts used in the receiver.

As examples of the mechanical noises, we have noise due to vibration of the laminations in a power transformer or rattles in a cabinet door caused by vibration. Some mechanical noises are heard even though the speaker is disconnected or a resistance network substituted for the speaker. A simple check can be made to determine whether the disturbing noise comes from the speaker or not. Substitute a 4,000 to 8,000-ohm resistor for the speaker. While the resistor may not match the speaker output exactly it will place enough load on

*The last word has not been written in servicing radio sets, nor is it likely to ever be written. With thousands upon thousands of service men in this country it is only natural that each man should develop his own method of servicing. However, here is an interesting and factful story, written by a man who is a radio service specialist. Perhaps in his article you will find short cuts that will save you time and money, or else lead the way to changes in your methods of servicing.*

—Editor.

the apparatus under test to show whether or not the noises are of a mechanical nature. If the noise is still present it does not come from the speaker and must be traced in the set. This test, of course, is not applicable where the noise, although not coming through the speaker, is caused by speaker vibration affecting some part of the receiver, for example, rattling cabinet doors due to excessive output from the speaker. Here the serviceman must use his judgment in applying the tests.

Noises may further be classified according to the nature of the noise as follows:

Scratching noises, clicks, crashes, rattles and grating noises, generally due to poor construction or defective parts.

Whistling, generally due to regeneration, poor tubes and oscillation.

Ringling noises, gradually increasing in intensity. These are called microphonic noises—sometimes due to poor design—defective parts—defective tubes or too much volume.

Hum—generally due to poor construction—defective parts, faulty design or poor tubes.

In servicing a noisy receiver, the first thing to do is to determine whether the noise comes from outside or inside the receiver. In the case of a battery set this can generally be definitely determined by disconnecting the aerial from the set. If the noise disappears it shows that it comes from the outside and that

the set is O. K. If the noise still persists, however, the indications are that it originates in the set and it becomes a matter of diagnosing the trouble in the manner outlined in this article.

In the case of electric sets this test is not conclusive. If disconnecting the antenna causes the noise to stop, its source is generally external to the receiver. If noise is still present, it may still come in from the outside through the power line and get into the receiver by way of the power pack.

Every serviceman should carry with him a line filter of simple design that can be quickly and easily connected to the line of the ordinary a.c. set to filter out line noises. Figure 1 shows an arrangement which has been used successfully for this purpose.

If the noise is appreciably reduced after connecting the filter between line and receiver, it indicates that the noise originates outside the set and comes in on the line. If the noise is still present it will be reasonable to assume that its source is in the receiver and it can be eliminated.

## Irregular Noises

Under this heading come all sorts of crackles, scratchings, gratings, hissing and frying noises. The first three types are most frequently due to poor contacts. These arise from various causes. The most important are poor soldering and poor contact between tube prongs and socket spring contacts. Poor soldering may result in a loose and therefore intermittent contact which is readily detected and observed by moving the lead to see if it is loose. The presence of a large amount of resin around a soldered joint is always a sure indication of a poor joint. The continuity tester to be described later will help greatly in locating high resistance contacts. The presence of a green substance at a joint is a definite sign of corrosion and indicates a likely source of noise. The only thing to do in a case of this sort is to re-solder the joints properly. A poorly soldered joint is a source of noise in any circuit, power pack, audio or radio, since it causes irregular variations of current.

In battery sets such irregular noises arise due to poor contact at the battery terminals. To avoid corrosion in storage battery terminals, it is best to use vaseline on the terminals. Weak batteries are also frequent sources of sputtering and crackling noises. The storage battery should be kept in condition by

\*Radio Service Specialist, National Radio Institute.



keeping it filled with distilled water and not allowing the voltage to fall below 1.8 volts. Frequently, it is a single cell in a battery that is the source of trouble, shown by a drop in voltage of the battery when it is operating under load. This is especially true of the storage battery. A hydrometer test may show correct gravity but a voltage test will show up a defective cell even if it has correct gravity if the voltage test is made while the battery is under load.

**Tube and Tube Contacts**

Special attention should be paid to these because they are often a source of

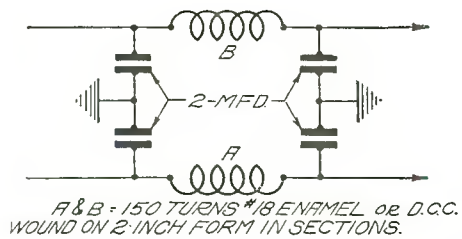


Fig. 1. This portable filter is suggested by the author to filter out line noises and should prove valuable to the service man

noise. A gassy tube indicated by a blue haze in the tube when working, causes irregular changes in plate current, thereby producing noise. The best remedy for this is to use a new tube even though the old tube may show correct operating characteristics. However, the abnormal condition causing the blue haze in the old tube has more than likely ruined it.

Loose elements in tubes will cause noise. Tapping the tube with your finger will sometimes show up a loose element. A slight ringing noise may be produced on tapping the tubes but this is normal. If tapping a particular tube results in crackling or sputtering, examine the tube socket contacts and examine the prongs of the tubes.

Defective socket springs are another source of noise. Socket spring contacts are made of phosphor, bronze or nickel silver. Such contacts are designed so that they exert pressure against the tube prongs. These springs may make good contact at the start and then later on develop poor contact for various reasons. Heat from a soldering iron may cause the spring to lose its "temper" and continual pushing and pulling the tube out of its socket may result in pushing the socket spring so far away that it does not make contact with tube prongs. Or the contact may be intermittent and we have another source of noise. Socket contacts and tube prongs should be cleaned if corrosion has formed or if they are dirty. Sand paper tube prongs and scrape socket prongs with a small pen knife. Bend the socket prong with a pair of small nose pliers

so that it will make good contact with the tube prong.

**Volume Control**

If a scratching noise is heard on any station as the volume control is rotated throughout its range, the noise is due to the volume control and may be in the form of a defective resistance winding or poor contact between the rotating arm and the resistance winding. There may be an oxidized contact. Poor mechanical contact may be made by the contact arm being bent away from the winding. It can be bent with a small pair of pliers so that it makes firm contact. A dirty winding or an oxidized winding should be cleaned. First use sandpaper lightly and then apply cigarette lighter fluid to the winding by means of a small tooth brush.

**Defective Insulation**

Sputtering, hissing and frying noises are frequently caused by poor insulation. If a breakdown occurs between two points, noise in the receiver results. Poor insulation in a power transformer may cause flash-overs and sparks. A frequent offender is the bakelite terminal strip which generally carries all the metal terminals. The presence of soldering flux and acid results in leakage between terminals and consequent noise. The terminal strip should be thoroughly cleaned and dried. If there is leakage due to the breakdown of the insulating material, parts of the strip have most likely been carbonized or charred. This may be scraped away with a knife. Dirt between posts at high potentials causes the same trouble and should be removed in a similar manner. Power transformers, choke coils, and filter condensers are the worst offenders in this respect since they are in the high voltage circuits. The rectifier tube socket should also be carefully examined for signs of leakage.

Failure of wire insulation may be caused mechanically. For example, if a high voltage wire is caught under a metal clamp or another wire which is tightened by a screw, the insulation may be broken though to such an extent that there will be mechanical strain and the wire may ground intermittently. Examination of the wiring will show up these causes of noise trouble.

Variable condensers are often a source of noise. The plates may touch as the rotor is rotated and produce a clicking noise. Fine particles of dust between condenser plates will also cause noise and it is often very hard definitely to trace noises to the variable condensers. One should always clean the condenser plates of noisy receivers carefully. This is accomplished by drawing ordinary smoking pipe cleaners between separate plates of both rotor stator plates.

**Noise Due to Feed Back**

Much has been written in regard to feed back oscillations. We do not intend to go into this subject too deeply here as most servicemen are familiar with the general procedure to be followed in correcting for undesirable regeneration.

When a set oscillates at radio frequencies, the characteristic squeal or whistle is heard. The pitch of this whistle, going up and down in scale as the variable condenser is rotated from one end of the dial to the other. In general, if we are servicing a neutrodyne set this means that the receiver must be reneutralized. This same condition may also be caused by an unbalanced condition of the main tuning condensers in tuned t. r. f. receivers.

Servicemen have their own particular methods for neutralizing. One solution is offered here. Carry in your service kit, drinking straws which you can obtain at most candy shops or drug stores. Place a portion of one of the straws on one of the tube's filament prongs then insert it in the socket in which the tube operates. It is the usual practice to begin at the tube preceding the detector

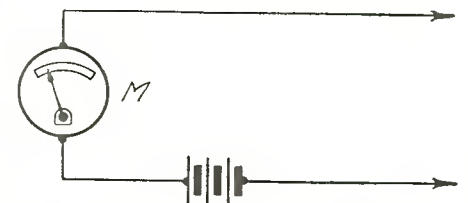


Fig. 2. A simple continuity tester is illustrated in this drawing. It consists of a voltmeter in series with a 4.5 volt C battery, and a set of test leads

and work back toward the antenna stage. A broadcast or modulated oscillator signal at about 1300 kilocycles is tuned in on the receiver. Due to the tube's filament being unlighted, it will not amplify and you can adjust the neutralizing capacity for that stage. A correct adjustment will be made when minimum signal is heard in the loud speaker or when a minimum deflection is obtained on an output meter.

The balancing condensers are adjusted in the same manner. An insulated screwdriver or hexagon wrench is used in balancing these condensers depending on the type of receiver in question. If the oscillation is in the radio frequency stages, the following may be the cause:

I. Absence of a good ground on a receiver or imperfect grounding which in most cases increases the tendency to regeneration and oscillation. This applies to the main ground connection and other various parts of the circuit which are supposed to be grounded.

II. Too much gain or amplification  
(Continued on page 77)

# Receiver Response Curve Section

**T**HOSE interested in the response curves appearing in this issue will find on this page a brief summary of the equipment, conditions of measurement, and a description of the meaning of sensitivity, selectivity and electrical fidelity.

The photograph shown here represents the apparatus used in making the measurements in our laboratory. As a rule only the latest models of receivers are measured for publication in this magazine.

## Equipment Used

Equipment used in the response measurements conforms to specifications of the I. R. E. and the R. M. A. standardization committee. Such apparatus for the most part is manufactured by The General Radio Co. All test frequencies are determined by zero beat of a crystal controlled dynatron oscillator. Volt meters and microvoltmeters are periodically checked against calibrated standards for accuracy of adjustment.


## Conditions of Measurement

All measurements are made in the manner outlined by the Institute of Radio Engineers Standardization Committee and published in detail in the 1929 Year Book of that organization. The individual conditions of measurements pertaining to each receiver will be found in the article accompanying each family of curves.
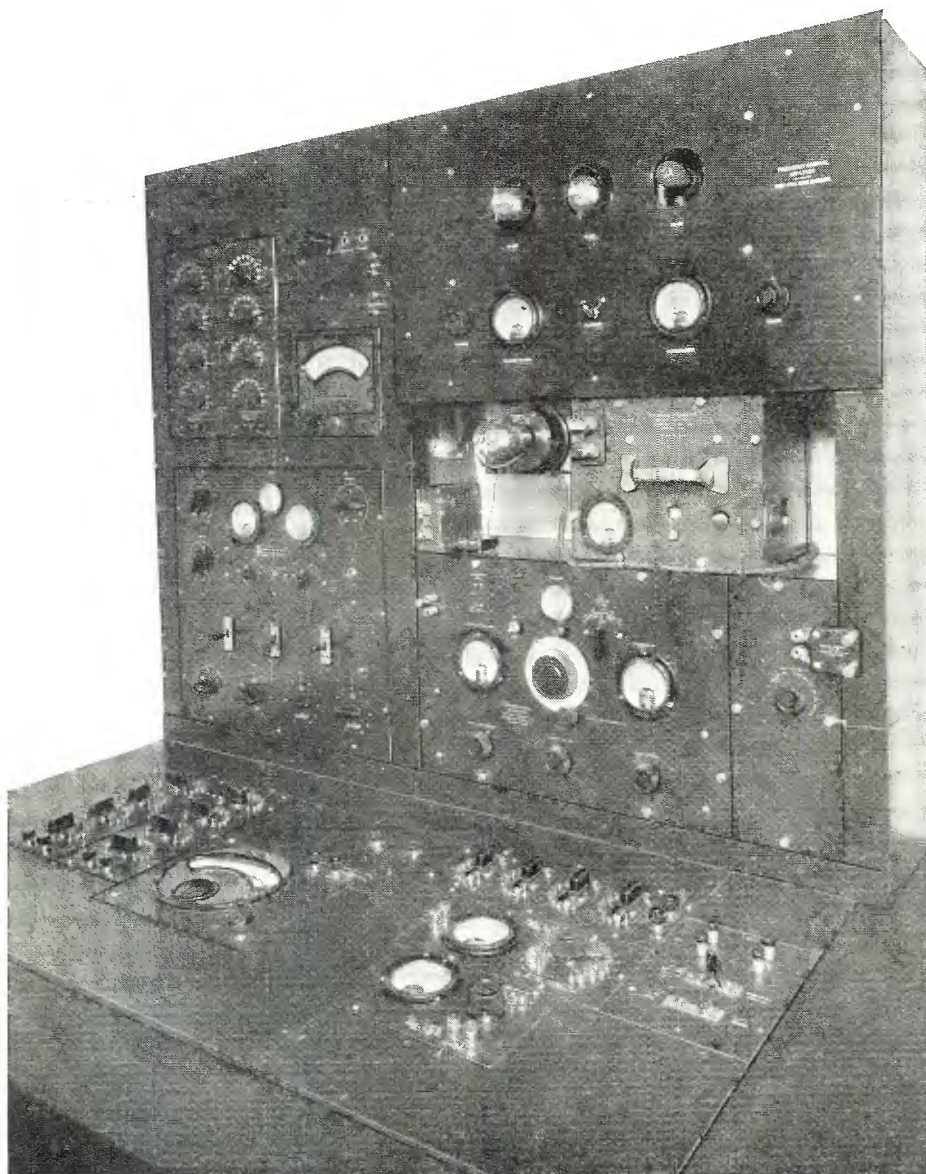
## Sensitivity

Sensitivity curves show sensitivity in microvolts input plotted against carrier frequency in kilocycles.

Interpretation of this curve follows: A station will cause standard speaker output (.05 watts) when it has a local



field strength equal to the microvolts divided by four indicated on the curve directly above the frequency of the station. To find the sensitivity of the receiver in microvolts per meter (based on a four-meter antenna), divide any point on the curve in microvolts by four. This sensitivity is measured at 30 per cent modulation.

## Selectivity

Selectivity curves are plotted in field strength ratios vertically and frequency horizontally. Field strength ratios are determined by the input in microvolts required to obtain standard speaker output at the various frequencies off resonance, divided by the input required to give standard speaker output at resonance. The curves may be analyzed as follows: Resonance is the vertical zero line. A station on any frequency off resonance will cause equal

volume interference when its vertical line intersects the curve of the station desired. The point of intersection indicates a field strength ratio greater than resonance which produces equal volume interference. For general purposes the selectivity of the receiver is the number of kilocycles between the sides of the curve at any specified carrier frequency and field strength ratio.

## Electrical Fidelity

Electrical fidelity of a receiver is the loss or gain in faithfulness with which the audio component of the carrier frequency passes through the receiver. The measurements are made with a constant r.f. input voltage required to give standard speaker output when 400 cycles per second, 30 per cent modulation, is used. The r.f. input is main-

tained and the various test modulation frequencies varied. The ratio of the output at the modulation frequency of 400 cycles to the output at the other modulation frequencies (30 to 5000 cps) is calculated in decibels and plotted as loss or gain as the case may be from 400 cps. These measurements do not take into consideration the frequency response curves of the speaker used.

Since curves of all receivers are taken under the same conditions, it may be said that such curves serve as a yardstick by means of which various receivers of the same class may be compared. This means supers may be compared against supers, or tuned r.f. rated against tuned r.f. It is obvious that comparisons between the super and the tuned r.f. are hardly fair because of their circuit differences.

# The General Motors Model 120-A



**G**ENERAL MOTORS model 120-A measured in our laboratory on November 17, yielded the curves shown on this page. Serial number of the chassis 64637A. Output impedance was adjusted to 4000 ohms, coupled capacitatively to the plates of the 245 tubes. Standard output of .05 watts was maintained. The dummy antenna employed consisted of 20 uh, 200 mmf and 25 ohms. Phasing frequency at which alignment made was 1400 kc. Volume control turned on full. No oscillation indicated nor hum level measurable.

Mutual conductance of the tubes used in these measurements is shown as follows: 1 r.f. 1015; 2 r.f. 960; 3 r.f.

1030; detector 1050; 1 a.f. 940; p.p. 1730 and 1860 micromhos.


The dotted line in the fidelity chart was taken with the tone control turned to the bass position.

In the two tables below are shown:

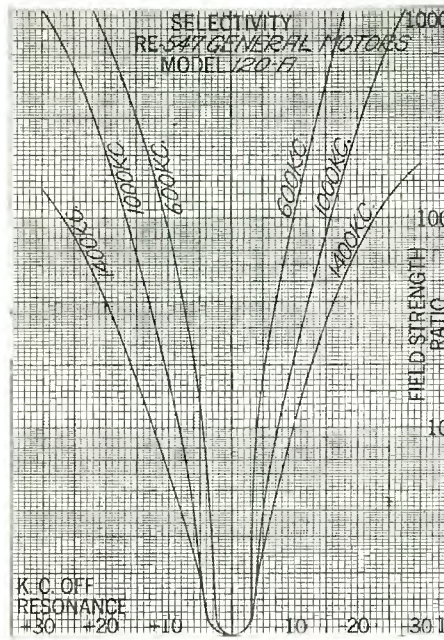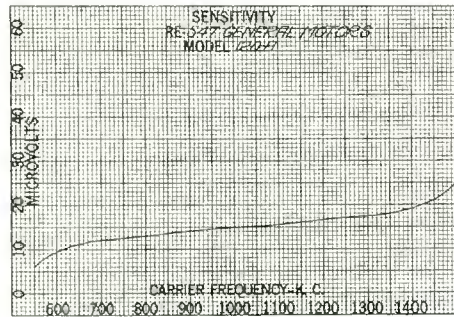

Resonance	Interference Ratio		
	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.....	80.7	608.0	1800
1000 kc.....	17.05	205.0	977
1400 kc.....	5.02	38.3	138.4
	Minus 10	Minus 20	Minus 30
600 kc.....	103.0	14.5	-----
1000 kc.....	22.7	261.0	1317.0
1400 kc.....	6.3	70.7	181.0

Times field strength	Band Widths		
	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	8.5	16.0	18.0
100	20.5	32.7	49.7
1000	40.0	58.0	-----

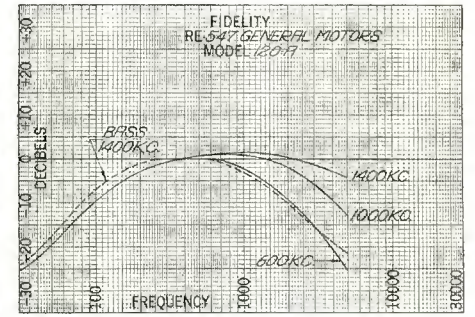



# Crosley Radio Model No. 54

**A**FAMILY of curves taken on one of the midgets made by Crosley, the model 54 whose schematic diagram and service data appears elsewhere in this issue, is illustrated on this page, measurements having been taken November 11.

Output impedance was adjusted to 4000 ohms and coupled capacitatively to the plate of the single 245 output tube. The output was maintained at .05 watts. Input to the set was through a dummy consisting of 20 uh, 200 mmf and 25 ohms. The receiver was phased at a frequency of 1100 kc. The volume control was turned to maximum. No oscillation noted, nor hum level measurable.


The mutual conductance of the tubes used in this measurement is shown here: 1 r.f. 1140; 2 r.f. 1070; detector 1170 and output tube 1970 micromhos.

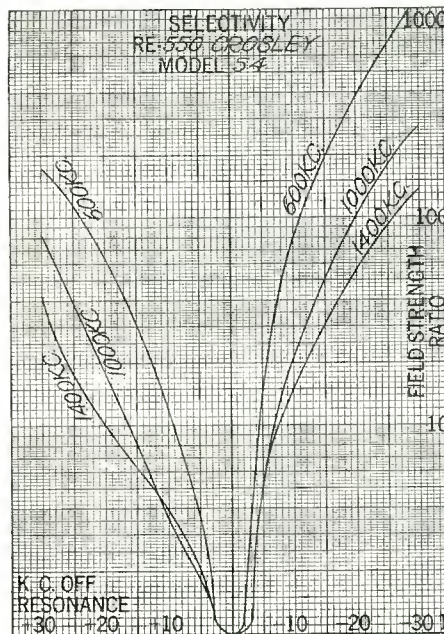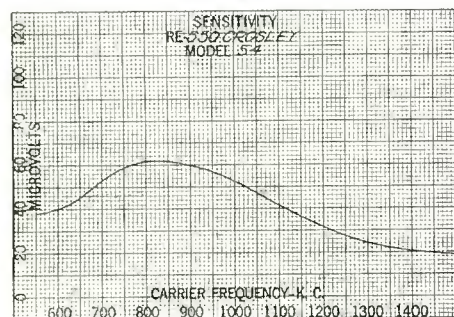Interference ratios and the band widths are indicated in the tables shown:



Resonance	Interference Ratio		
	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.....	9.62	61.2	172.0
1000 kc.....	3.44	18.4	81.6
1400 kc.....	4.18	9.83	42.2
	Minus 10	Minus 20	Minus 30
600 kc.....	75.7	374.0	1205.0
1000 kc.....	21.0	100.8	274.0
1400 kc.....	15.1	55.2	136.0

Times field strength	Band Widths		
	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	14.0	23.5	27.5
100	35.0	-----	-----
1000	-----	-----	-----

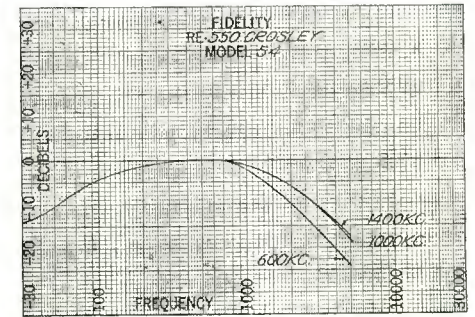

# General Electric Model No. H-31

**M**EASUREMENTS on one of the superheterodynes marketed under the General Electric banner, the model H-31 have been recently completed and the three curves derived therefrom given at the bottom of this article.

An output impedance load of 4000 ohms was maintained, this being coupled capacitatively to the plates of the 245 output tubes. Standard output was .05 watts. The dummy antenna used was the standard having 20 uh, 200 mmf and 25 ohms. No change was made in the phasing frequency since this value was set in the factory. Volume control was turned full on. No measurements could be made covering either the hum level or oscillation.

Tubes have a mutual conductance as

indicated in this paragraph were used on the measurements: 1 r.f. 940; 1 i.f. 1020; 2 i.f. 900; 1 detector 1000; 2 detector 1030; oscillator 1300; p.p. 1850 and p.p. 1850 micromhos.

In the two tables following may be found the interference ratios and the band widths as taken from the curves




on selectivity.

### Interference Ratio

Resonance	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.	900	-----	-----
1000 kc.	900	-----	-----
1400 kc.	900	-----	-----
	Minus 10 Minus 20 Minus 30		
600 kc.	-----	-----	-----
1000 kc.	-----	-----	-----
1400 kc.	-----	-----	-----

### Band Widths

Times field strength	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	7.9	7.9	7.9
100	12.4	12.5	12.4
1000	17.9	17.9	17.9

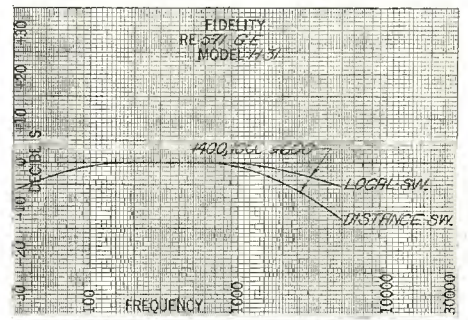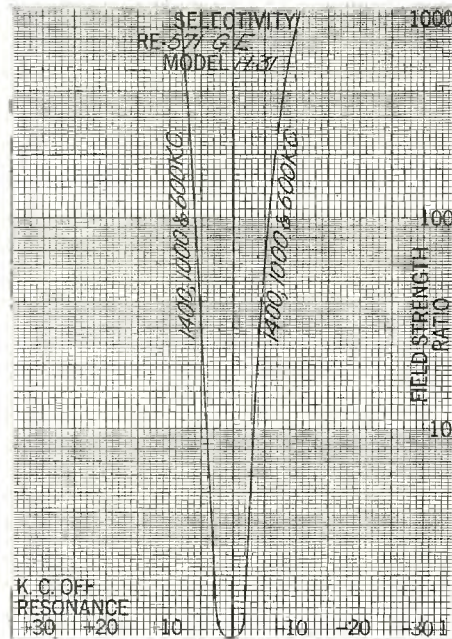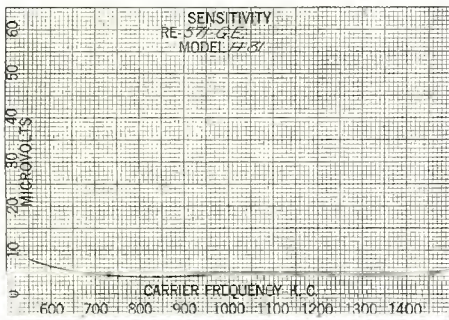

# Radiola Superheterodyne Model 80

**U**SING the 175 kilocycle intermediate frequency stages and known as the bell-wether of this type of superheterodyne in commercial production, the model 80 selling under the name of Radiola, has recently been measured in our laboratory, and the response curves of this model taken.

As customary the output impedance load was adjusted to 4000 ohms and coupled capacitatively to the plates of the 245 tubes. The standard output of .05 watts was maintained, the antenna input being from the standard dummy, consisting of 20 uh, 200 mmf and 25 ohms. The phasing frequency set in line production was maintained. Volume control turned on full. No hum or os-

cillation found.

Mutual conductance of the tubes used in this measurement is shown by the following values: 1 r.f. 940; 1 i.f. 1020; 2 i.f. 900; oscillator 1300; 1 detector 1000; 2 detector 1030; p-p




1850 and p.p 1850 micromhos.

### Interference Ratio

Resonance	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.	900	-----	-----
1000 kc.	900	-----	-----
1400 kc.	900	-----	-----
	Minus 10 Minus 20 Minus 30		
1000 kc.	-----	-----	-----
600 kc.	-----	-----	-----
1400 kc.	-----	-----	-----

### Band Widths

Times field strength	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	8.0	8.0	8.0
100	12.5	12.5	12.5
1000	18.0	18.0	18.0

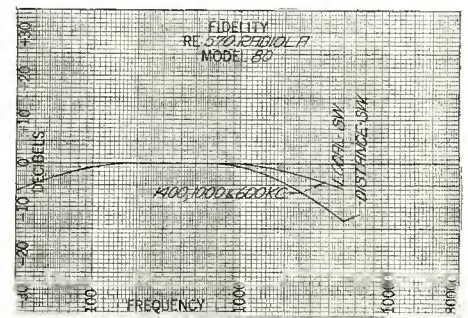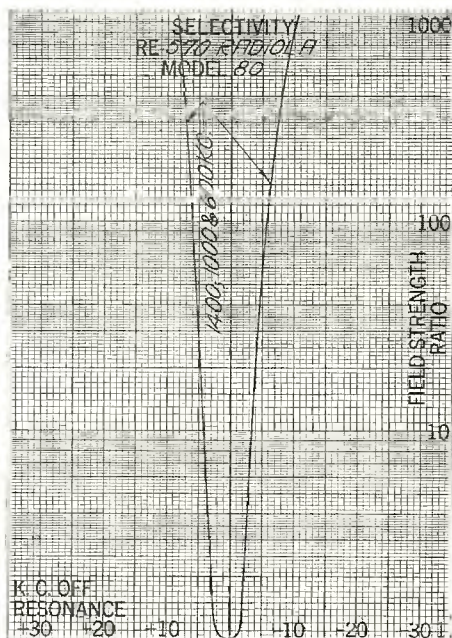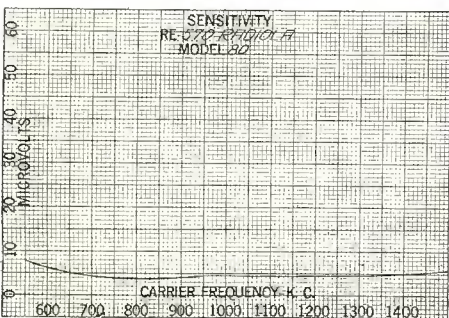

# Amrad Receiver Model No. 84



RECENT measurements made on one of the Amrad chassis, model 84, shows the curves resulting in the three graphs with this article.

The output impedance load was adjusted to 4000 ohms and coupled capacitatively to the plates of the 245 tubes. Standard output of .05 watts was maintained on all measurements. The dummy antenna was the standard containing 20 uh, 200 mmf and 25 ohms. The receiver was phased at 1400 kilocycles and the volume control turned on full. Neither hum nor oscillation was found.

The mutual conductance of the tubes used in this measurement follows: 1

r.f. 1140; 2 r.f. 1240; 3 r.f. 1170; detector 1120; 1 a.f. 1040; p.p. 1920 and 1970 micromhos.

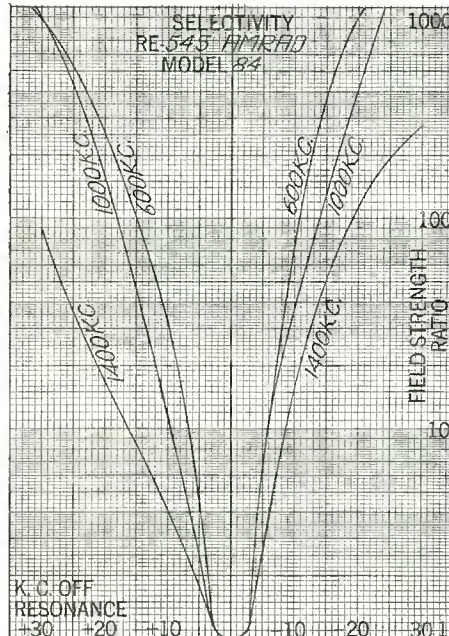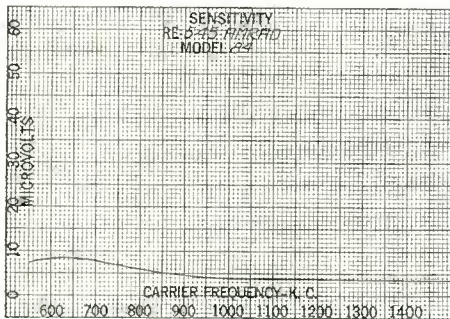Based on the curves of selectivity the interference ratios and the band widths are derived below:




**Interference Ratio**

Resonance	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
1000 kc.	11.5	160.0	380.0
600 kc.	33.0	250.0	380.0
1400 kc.	4.0	17.0	38.0
	Minus 10 Minus 20 Minus 30		
600 kc.	6.5	900.0	-----
1000 kc.	6.5	410.0	-----
1400 kc.	2.6	112.0	270.0

**Band Widths**

Times field strength	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	12.5	15.5	25.0
100	25.7	32.0	-----
1000	52.5	55.0	-----

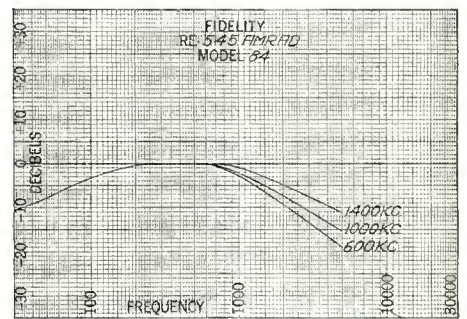

# Graybar Superheterodyne, No. 700

THREE of the response curves covering the superheterodyne marketed under the Graybar name and known as model 700 are shown here.



As usual the output impedance load was adjusted to 4000 ohms. Coupling to the plates of the 215 output tubes was capacitive. The standard output for receivers, .05 watts, was maintained on all measurements. Antenna input was through the dummy consisting of 20 uh, 200 mmf and 25 ohms. Phasing frequency was checked at the value set at the factory, and the volume control turned on maximum. No hum nor oscillation was present.

Mutual conductance of the tubes used in this set-up is indicated in the follow-

ing values: 1 r.f. 940; 1 i.f. 1020; 2 i.f. 900; detector 1000; p.p. 1850; p.p 1850; 2 detector 1030 and oscillator 1300 micromhos.

In the two tables following will be found the interference ratios and the

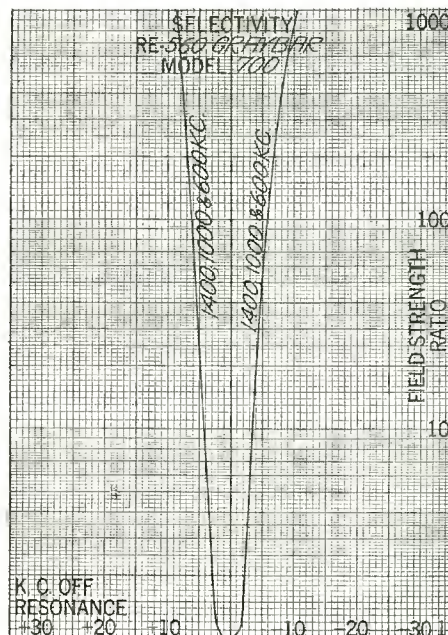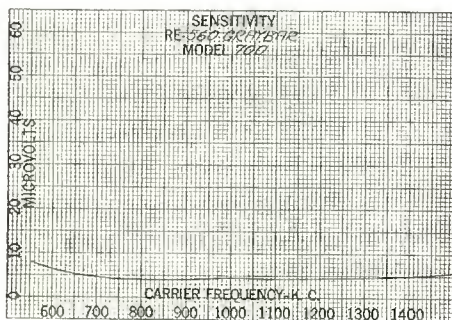band widths as taken from the selectivity curves:




**Interference Ratio**

Resonance	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.	900	-----	-----
1000 kc.	900	-----	-----
1400 kc.	900	-----	-----
	Minus 10 Minus 20 Minus 30		
600 kc.	-----	-----	-----
1000 kc.	-----	-----	-----
1400 kc.	-----	-----	-----

**Band Widths**

Times field strength	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	8.1	8.1	8.1
100	12.6	12.6	12.6
1000	18.1	18.1	18.1

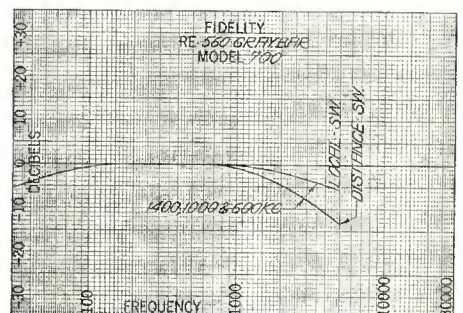

# Kennedy Radio Model No. 42



**A**MONG the midget receivers recently measured in our laboratory is the Colin B. Kennedy model 42 whose response curves are shown on this page.

Output impedance load was adjusted for 4000 ohms, coupled capacitatively to the output power stage plate. Standard output of .05 watts was maintained. Antenna input was through the dummy containing 20 uh, 200 mmf and 25 ohms. Phasing frequency set at the factory was maintained and the volume control turned on full. No oscillation and no hum level was found.

Mutual conductance of the tubes used in this measurement is indicated in the following values: 1 r.f. 980; 2 r.f.

1030; detector 1040; 1 a.f. 1020, and power output stage 1920 micromhos.

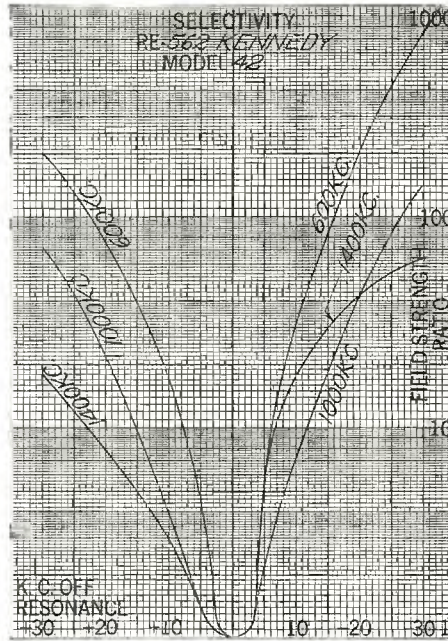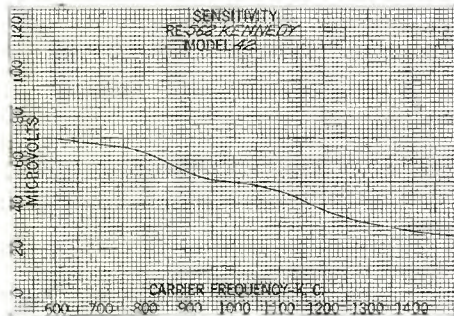In the two tables following will be found the interference ratios and the band widths, this data being secured from the selectivity curves:



**Interference Ratio**


Resonance	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.	17.00	75.0	200.0
1000 kc.	3.90	22.0	71.0
1400 kc.	2.95	7.8	18.0

Resonance	Kilocycles off resonance		
	Minus 10	Minus 20	Minus 30
600 kc.	30.0	205.0	750.0
1000 kc.	7.2	42.0	140.0
1400 kc.	17.5	42.0	63.0

**Band Widths**

Times field strength	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	13.7	27.0	30.0
100	38.5	---	---
1000	---	---	---

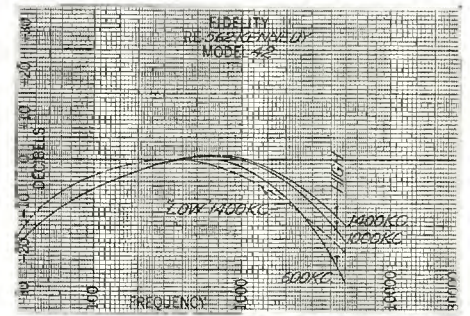



# Audiola Super Model No. 31

**M**EASUREMENTS have been completed on the Audiola model 31 superheterodyne and its response curves are shown on this page. Input for the measurements was through the standard dummy antenna consisting of 20 uh, 200 mmf and 25 ohms. The output impedance was maintained at 4000 ohms and coupled capacitatively to the plates of the 245 output tubes. The receiver was phased at 1400 and 600 kilocycles and the volume control turned on full. Line voltage measured 110 volts and current .9 amperes.

Transconductance of the tubes used in the measurement on this model is in-

dicated: 1 r.f. 1030; mixer 1080; detector 1100; 1 i.f. 1050; 2 i.f. 1020; P.P. 1940; P.P. 1970 and oscillator 1080 micromhos.

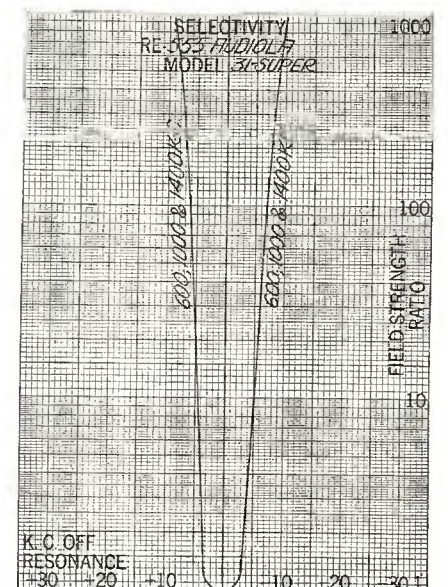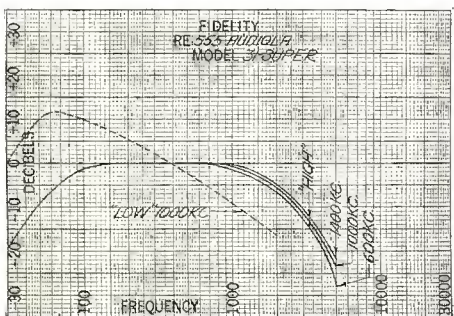In the two tables will be found the interference ratios and the band widths:



**Interference Ratio**


Resonance	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.	1300	---	---
1000 kc.	1300	---	---
1400 kc.	1300	---	---

Resonance	Kilocycles off resonance		
	Minus 10	Minus 20	Minus 30
600 kc.	900.0	---	---
1000 kc.	900.0	---	---
1400 kc.	900.0	---	---

**Band Widths**

Times field strength	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	9.5	9.5	9.5
100	13.0	13.0	13.0
1000	19.5	19.5	19.5

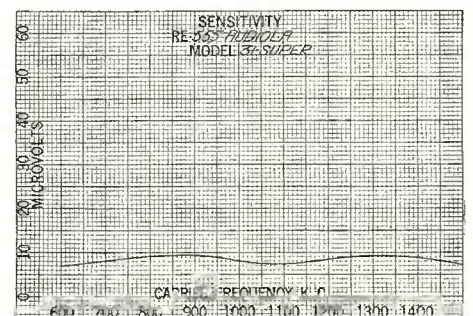

# Silver Super Model No. 36-A

**R**ESPONSE curves of the Silver superheterodyne model 36-A are shown on this page. Schematic circuit of the receiver and service data appears elsewhere in this section.

Dummy antenna used consisted of 20 uh, 200 mmf and 25 ohms. Output impedance was adjusted to 4000 ohms, coupled capacitatively to the plates of the 245 tubes in the output stage. The receiver was phased at the factory setting and the volume control turned to maximum. Line voltage 110 volts and current .95 amperes. Standard output of .05 watts was used in the measurements.




Transconductance of the tubes used indicated as follows: 1 r.f. 1120; mixer

1080; detector 1250; 1 i.f. 1140; 2 i.f. 1040; P.P. 1940; P.P. 1980; oscillator 1000 micromhos.

Interference ratios and band widths are shown in the two tables:

Resonance	Interference Ratio		
	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.	900	-----	-----
1000 kc.	900	-----	-----
1400 kc.	900	-----	-----
	Minus 10	Minus 20	Minus 30
600 kc.	-----	-----	-----
1000 kc.	-----	-----	-----
1400 kc.	-----	-----	-----

Times field strength	Band Widths		
	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	8.5	8.5	8.5
100	12.0	12.0	12.0
1000	18.5	18.5	18.5

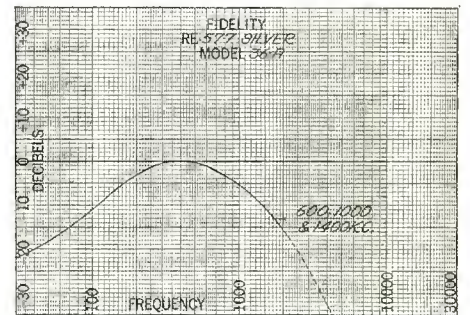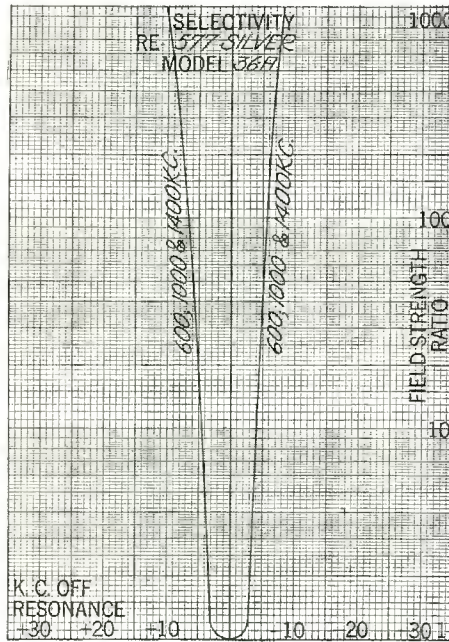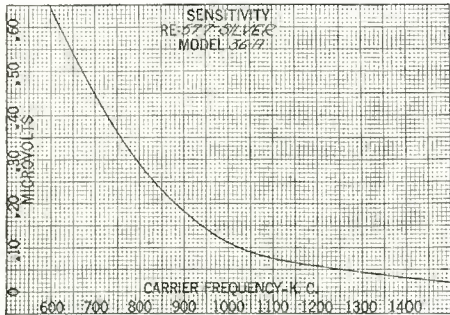

# Columbia Radio Model No. 100

**M**ODEL 100 Columbia, used by the Columbia Phonograph Co., is another chassis recently passing through our measurement laboratory. The response curves for this receiver are shown in this article.

Output impedance load was adjusted at 4000 ohms and coupled capacitatively to the plates of the 245 output tubes. Power output was maintained at the standard value of .05 watts. The customary antenna dummy was one with 20 uh, 200 mmf and 25 ohms. The receiver was phased at 1400 kc. and the volume control turned to maximum. Neither hum nor oscillation was encountered.

The tubes used in these measurements




had the mutual conductance values indicated: 1 r.f. 1140; 2 r.f. 1240; 3 r.f. 1170; detector 1120; 1 a.f. 1040; p.p. 1920 and p.p. 1920 micromhos.

Interference ratios and band widths, taken from the selectivity curves, are

set forth in the two tables following:

Resonance	Interference Ratio		
	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc.	32.0	255.0	-----
1000 kc.	11.5	165.0	870.0
1400 kc.	3.3	18.0	83.0
	Minus 10	Minus 20	Minus 30
600 kc.	60.0	840.0	-----
1000 kc.	36.0	410.0	-----
1400 kc.	14.5	112.0	280.0

Times field strength	Band Widths		
	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10	12.0	15.5	30.5
100	27.0	31.7	-----
1000	48.5	55.0	-----

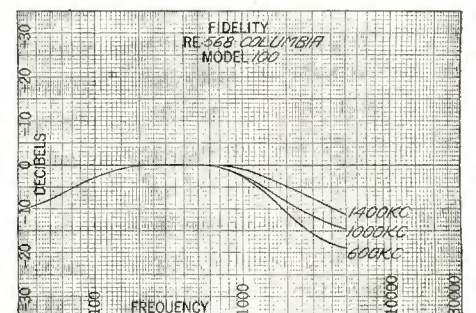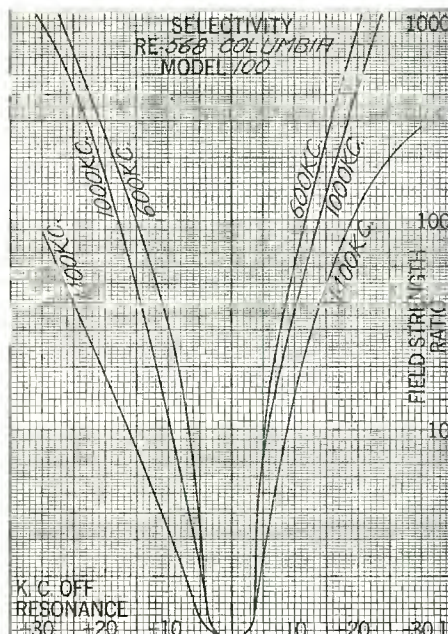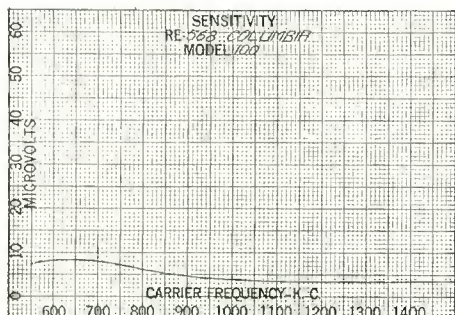

# Atwater-Kent Model 72 Super

**A**TWATER-KENT'S superheterodyne, known as their model 72, has been recently measured in our laboratory and the curves derived are presented on this page. In reading the sensitivity curves, readers should note that microvolts are plotted from 0 to 6, a period being placed between the numeral and the cipher.

Dummy antenna used consisted of 20 uh, 200 mmf and 25 ohms. Output impedance was maintained at 4000 ohms, coupled capacitatively to the output plates. The factory phasing frequency was maintained and the volume control turned to maximum setting. Line voltage 115, current .82 amperes.




Transconductance of the tubes used:

Mixer, 1140; detector, 1000; 1 i.f. 1080; 2 i.f. 1040; 1 a.f. 1000; P.P. 1940; P.P. 1980, and oscillator, 1030 micromhos.

Interference ratios and band widths are shown in these tables:

Resonance	Interference Ratio		
	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc. ....	75.0	-----	-----
1000 kc. ....	-----	-----	-----
1400 kc. ....	275.0	-----	-----
	Minus 10	Minus 20	Minus 30
600 kc. ....	-----	-----	-----
1000 kc. ....	450.0	-----	-----
1400 kc. ....	210.0	-----	-----

Times field strength	Band Widths		
	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10 -----	9.5	9.2	9.2
100 -----	17.7	14.0	14.5
1000 -----	28.0	21.0	27.0

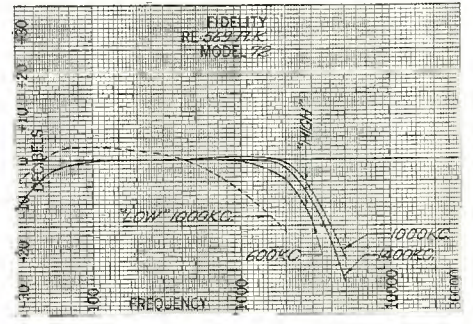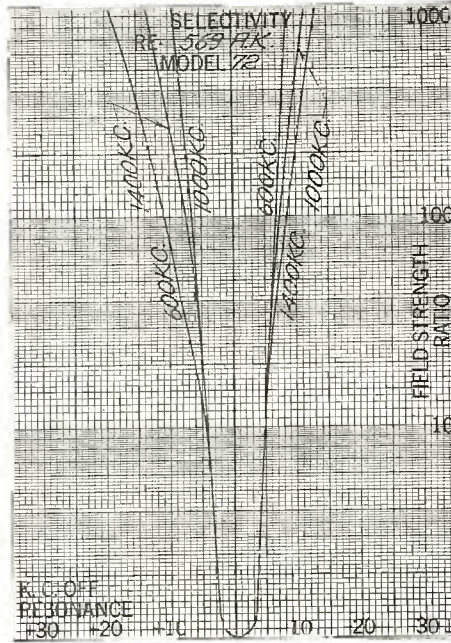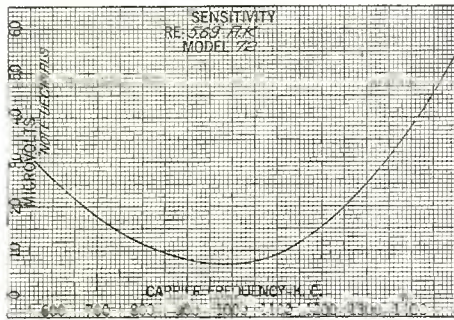

# Zenith Radio Model ZE-70 Jr.

**R**ESPONSE curves have been taken on the Zenith model ZE-70 Jr., and are illustrated on this page. R.f. input to the receiver was through the standard dummy consisting of 20 uh, 200 mmf and 25 ohms. Output impedance was kept at 4000 ohms, coupled capacitatively to the plates of the 245 output tubes. The receiver was phased at 1400 kc. and the volume control turned to maximum. Line voltage 115 volts, current .85 amperes.




Transconductance of the tubes used in the measurement are indicated: 1 r.f. 1080; 2 r.f. 1040; 3 r.f. 970; detector

970; 1 a.f. 950; P.P. 1980 and P.P. 1940 micromhos.

In the two tables below will be found the interference ratios and the band widths taken from the selectivity curves:

Resonance	Interference Ratio		
	Kilocycles off resonance		
	Plus 10	Plus 20	Plus 30
600 kc. ....	112.0	900	-----
1000 kc. ....	58.0	550.0	-----
1400 kc. ....	5.3	31.0	142.0
	Minus 10	Minus 20	Minus 30
600 kc. ....	240.0	-----	-----
1000 kc. ....	24.0	550.0	-----
1400 kc. ....	5.9	46.0	285.0

Times field strength	Band Widths		
	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10 -----	8.8	13.8	26.0
100 -----	17.5	25.5	51.5
1000 -----	34.5	47.5	-----

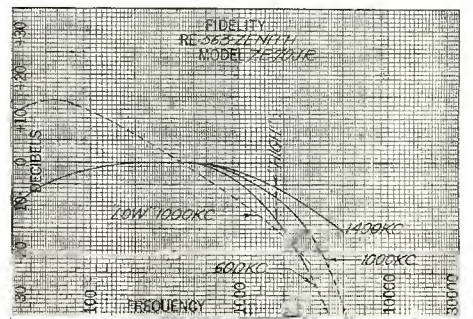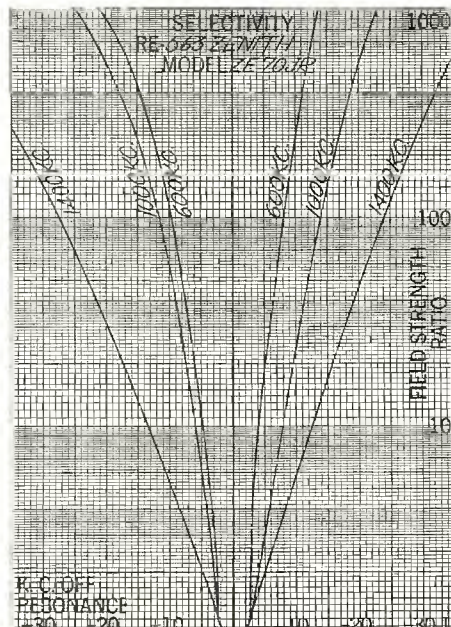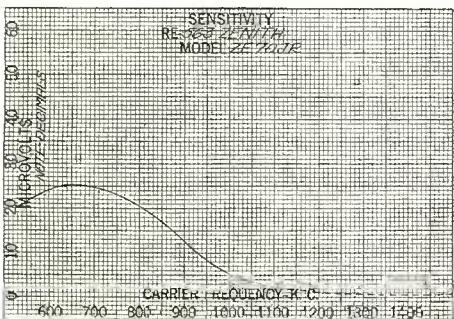



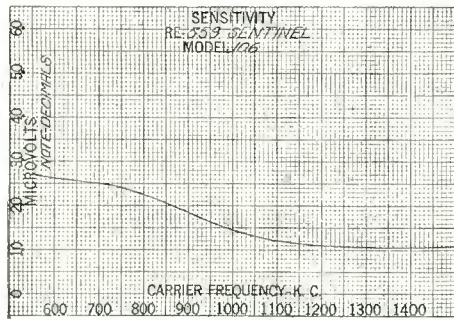
# Sentinel Super Model 106


**S**ENTINEL'S model 106 super-heterodyne has recently passed through our measurement laboratory and its curves are shown on this page. The dummy antenna used consisted of 20 uh, 200 mmf and 25 ohms. Output impedance was maintained at 4000 ohms, coupled capacitatively to the plates of the 245 output tubes. Factory phasing frequency was maintained and the volume control turned on full. Line voltage 110 volts, current .72 ampercs.

Transconductance of the tubes used in this measurement: 1 r.f. 980; mixer 1080; detector 950; 1 i.f. 1040; P.P. 1980; P.P. 1940 and oscillator 1180




micromhos.

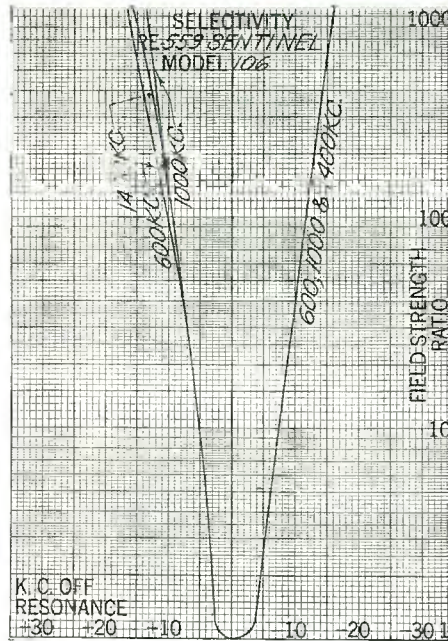In the two tables here shown will be found the interference ratios and the band widths:



Resonance	Interference Ratio		
	Plus 10	Plus 20	Plus 30
600 kc....	95.0	-----	-----
1000 kc....	140.0	-----	-----
1400 kc....	140.0	-----	-----
Resonance	Interference Ratio		
	Minus 10	Minus 20	Minus 30
600 kc....	37.0	-----	-----
1000 kc....	37.0	-----	-----
1400 kc....	37.0	-----	-----

Times field strength	Band Widths		
	Kilocycles wide		
10	600 kc.	1000 kc.	1400 kc.
100	12.5	12.5	12.5
1000	21.7	21.0	21.7
1000	32.0	29.5	32.5

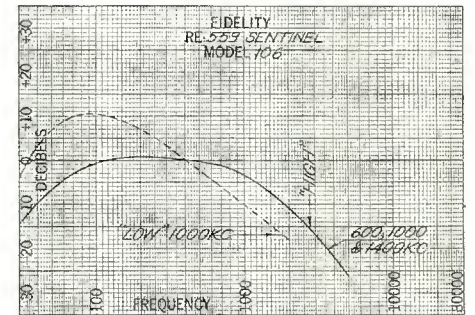

# Stromberg-Carlson Model 10



**M**EASUREMENTS of the sensitivity and fidelity of the Stromberg-Carlson model 10 receiver have been completed and the curves are shown on this page.

Input was through the standard dummy consisting of 20 uh, 200 mmf and 25 ohms. Output impedance was maintained at 4000 ohms coupled capacitatively to the plates of the 245 tubes. The receiver was phased at factory kc setting and the volume control turned to maximum. Line voltage 115 volts, current .9 ampercs.

Transconductance of the tubes used in the measurements is indicated by the


following values: 1 r.f. 1060; 2 r.f. 920; 3 r.f. 840; detector 990; p.p. 1620; p.p. 1660 micromhos.

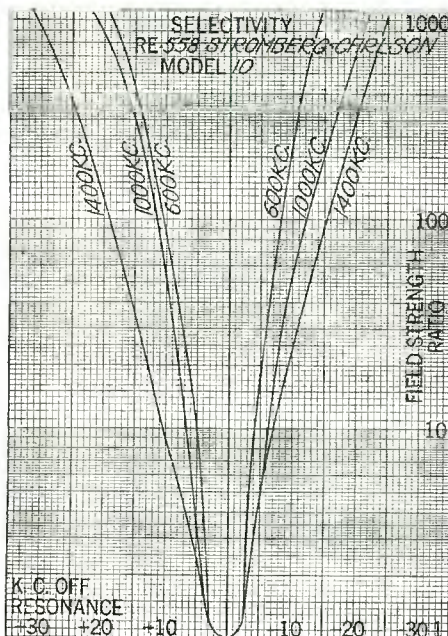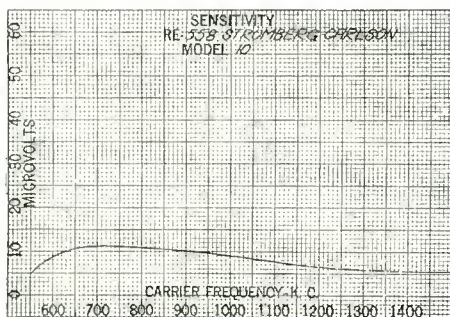In the two tables following will be found the interference ratios and the band widths:



Resonance	Interference Ratio		
	Plus 10	Plus 20	Plus 30
600 kc....	85.0	-----	-----
1000 kc....	52.0	780.0	-----
1400 kc....	9.0	125.0	-----
Resonance	Interference Ratio		
	Minus 10	Minus 20	Minus 30
600 kc....	230.0	-----	-----
1000 kc....	54.0	620	-----
1400 kc....	24.0	300	-----

Times field strength	Band Widths		
	Kilocycles wide		
10	600 kc.	1000 kc.	1400 kc.
100	9.0	13.0	17.5
1000	19.0	23.5	34.5
1000	34.0	44.0	56.0

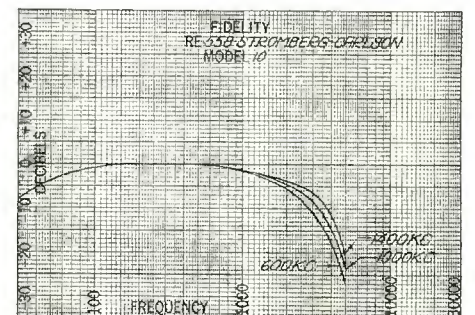

# Edison Models R-6 and R-7

**R**ESPONSE curves of the Edison models R6, R7 have been published previously, appearing on page 64 of the November issue of this magazine. In that number it was stated the schematic would be found elsewhere in that issue. However, this was in error, since the schematic published on page 77 was that of the Edison models R4, R5, C4, in no way related to the schematic of the R6, R7 shown on this page.

As will be seen from the schematic in Figure 2 these models are the screen grid type as contrasted with the 227's in the previous models. Tube operating values are shown in the chart in Figure 1.

A socket reading analysis chart covering r.f., detector, a.f. and rectifier stages is included in the Edison service manual, from which some of the more interesting servicing aids are taken.

In the case of the first r.f. socket no reading on filament voltage which should be 2.2 volts with the fuse in the 115-volt position indicates: open filament lead to socket; open filament of secondary; shorted filament secondary; open circuit in either connecting cable or six-prong connector. Low reading of filament voltage indicates: low line voltage; incorrect location of primary fuse; shorted turns in filament secondary; shorted turns in primary of power transformer; short circuit in filament wiring. High filament reading indicates: high line voltage; incorrect location of primary fuse.

Normal plate voltage is 190 volts. No reading indicates open plate lead; open cathode lead; grounded first or second r.f. plate lead; open first and

second r.f. plate isolating resistor; shorted first and second r.f. plate by-pass condenser; open low frequency or high frequency primary of 4th r.f. coil; "A" choke open or grounded; B choke

field winding; B choke shorted; grounded high voltage secondary; one lead to 280 socket open; shorted turns in high voltage secondary; one side of high voltage secondary open; shorted

Edison Models R6 and R7

Tube Type	Position in Set	A Volts	B Volts	C Volts	Cathode Volts	Screen Volts	Normal Plate M. A.	Plate M. A. Grid Test	Change
224	1 R. F.	2.2	190	---	2.5	80	3.5	6.0	2.5
224	2 R. F.	2.2	190	---	2.5	80	3.5	6.0	2.5
224	3 R. F.	2.2	190	---	2.5	80	3.5	6.0	2.5
227	Det.	2.2	---	*	---	---	---	---	---
227	1 A. F.	2.2	40	.5-2.5	±3.0	---	1.1	1.4	.3
227	2 A. F.	2.2	115	.5	6.0	---	3.8	4.8	1.0
245	P. P.	2.48	260	46	---	---	31.0	36.0	5.0
245	P. P.	2.48	260	46	---	---	31.0	36.0	5.0
280	Rect.	4.85	---	---	---	---	48.0	---	---

Line voltage, on 115-volt tap. Volume control.  
\*Grid volts 8-10 on strong signal.

Fig. 1. In this table may be found the tube operating voltages for the Edison model illustrated schematically on this page

grounded; open r.f. voltage divider, located in power unit; shorted filter condenser section; grounded rectifier filament winding; open radio-phono switch contacts; open or short circuit in either connecting cable or six-prong connector.

Low reading indicates: low line voltage; incorrect location primary fuse; low emission rectifier tube; grounded 3rd r.f. plate lead; shorted 3rd r.f. plate by-pass condenser; shorted speaker

filter condenser section; short circuit between 3rd r.f. filter condenser and automatic volume control by-pass condenser; open 1 a.f. bias resistor; low potential end of screen grid voltage divider open (located in a.f. filter unit), shorted turns in primary of power transformer. High reading indicates: high line voltage; incorrect location primary fuse; shorted 1 r.f. screen grid by-pass condenser; shorted 2 a.f. plate by-pass condenser.

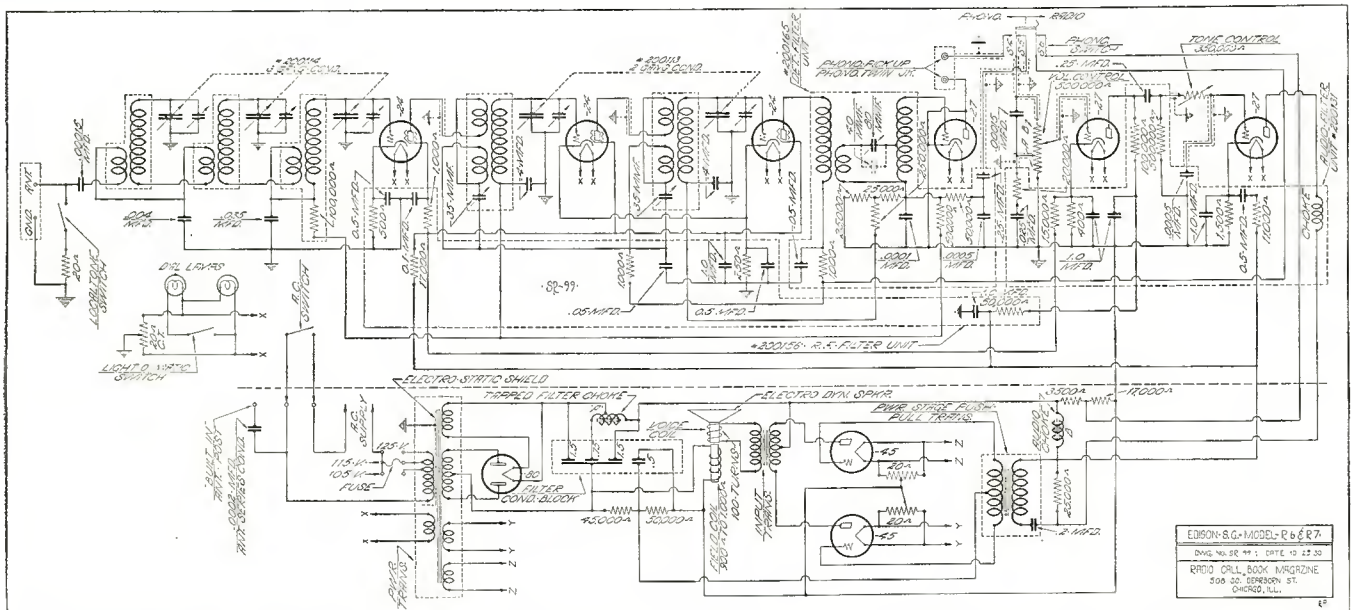


Fig. 2. The schematic diagram of the Edison models R6 and R7 including the power supply is shown in this diagram

# Victor Models R 35, R 39, RE57

**K** NOWN as the "micro-synchronous" model and using four stages of tuned r.f. with screen grid tubes, the Victor models R35, R39 and RE57 are illustrated schematically on this page in Fig. 2 with a table of tube operating values shown in the table in Fig. 1.

An interesting point in the Victor service manual covers installation of the receiver in a room so the receiver faces the length of the room rather than its breadth; also a space of at least four inches be allowed between the back of the cabinet and the wall. Best acoustic results will be obtained if these suggestions are followed.

Under general tests it is indicated that excessive hum may be caused by: faulty 224 in detector socket (at least one 224 out of the four will be found that will give minimum hum in the detector socket); faulty 280 or 227; unbalance in plate currents of the two 245's. (Try new 245 in one socket, then in another); wire or terminal grounded to chassis, or open circuit in any of the various ground connections to chassis; open or shorted center tap resistor in amplifier unit; short or partial short in one of the resistors mounted on the under side of the resistor board; shorted or open condenser in condenser bank or faulty connection to condenser bank; defective 280 socket, one plate not making contact; faulty connection to tapped section of filter reactor.

Microphonic howl may be caused by: defective tube in detector or first audio tube sockets; speaker not properly felt

insulated from baffle on front of the cabinet. (Raise the amplifier-speaker unit to gain access to the felt and re-adjust the felt properly, making sure the rim of the speaker is tight against the felt); loose metal parts such as screws, shields, etc., or an improperly centered cone may set up a howl or

coils or tubes, too much unshielded exposure of the green lead between the control grid of the 224 and coil; open circuit in any of the .1 mfd by-pass condensers, or poor ground (loose rivet) in any of these condensers; ungrounded shield on shielded lead of the radio chassis.

## Victor Models R35, R39 and RE57

Tube Type	Position in Set	A Volts	B Volts	C Volts	Cathode Volts	Screen Volts	Normal Plate M. A.	M. A. Grid Test	Change
224	1 R. F.	2.15	172	2.5	---	80	2.5	5.0	2.5
224	2 R. F.	2.15	172	2.5	---	80	2.5	5.0	2.5
224	3 R. F.	2.15	172	2.5	---	80	2.5	5.0	2.5
224	Det.	2.15	75	---	8	2.5	---	---	---
227	1 A. F.	2.15	55	0	---	---	1.5	1.8	.3
245	P. P.	2.25	185	36	---	---	19.0	22.0	3.0
245	P. P.	2.25	185	36	---	---	19.0	22.0	3.0
280	Rect.	4.8	---	---	---	---	36	---	---

Line voltage 112, on 120 tap. Volume control maximum.

Fig. 1. The tube operating values shown in this chart for the Victor R35, R39 and R57 are those taken with a Jewell analyzer, the manual indicating socket analysis together with possible causes of trouble

mechanical rattle, depending upon the nature of the fault; on the home recording model an open circuit in either of the resistors on the microphone reactor may cause a howl.

Oscillation in the set characterized by a generally unstable condition while tuning, may be caused by: Ungrounded or poorly grounded chassis; removal of shielding from any of the condensers,

Under excessive noise the following causes are listed: intermittent short or high resistance in any of the soldered joints, or in the power switch connections; loose or defective pilot lamp, or pilot lamp socket; shorted plates in one or more of the tuning condensers; faulty power or audio transformer; intermittent short on filter or by-pass condensers.

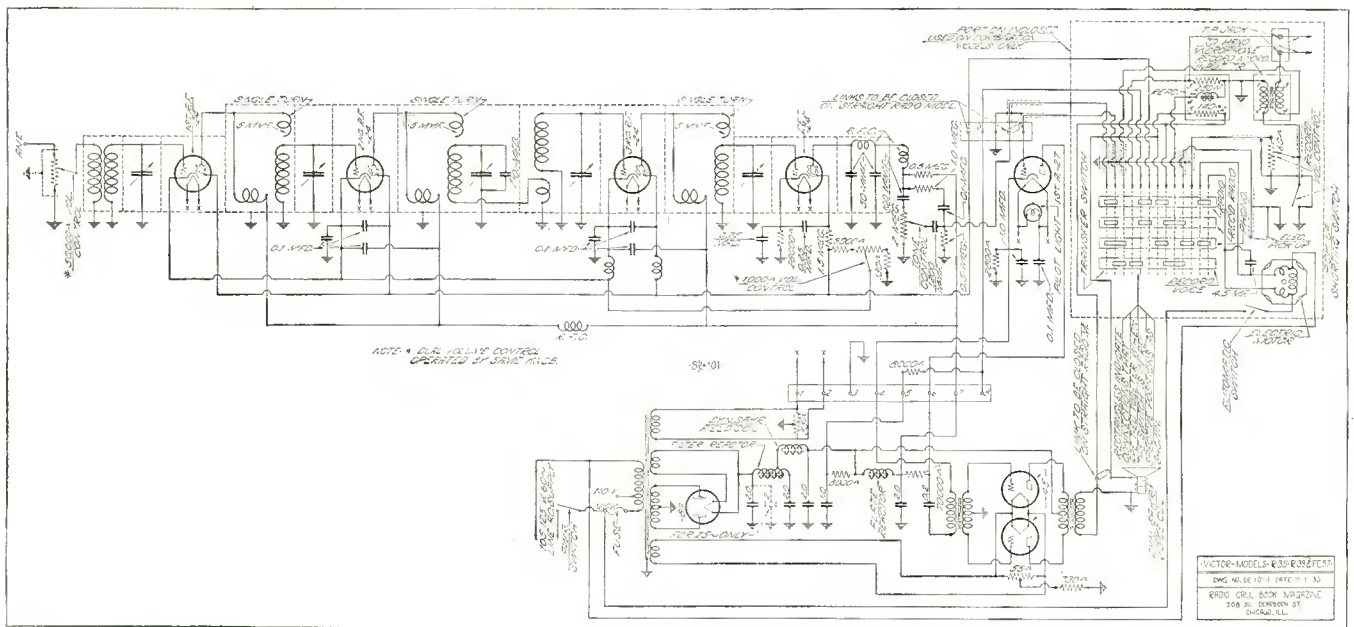


Fig. 2. The schematic diagram of the Victor models described on this page is shown in this illustration together with its power supply



# Bosch Receiver Model No. 58

**S**ERVICE data on the model 58, made by the American Bosch Magneto Corp., is shown on this page, the tube table in Figure 1 and the schematic of the receiver and power supply in Figure 2. The model 60 is practically the same as the 58 except it has an automatic volume control, a mute switch and a larger speaker.

Under service complaints in the Bosch manual are to be found a number of suggestions worth repeating since they cover the most common complaints. Weak or poor reception from distant stations might be caused by inefficient antenna, open or grounded antenna; poor or broken ground connection; defective tubes; condensers not aligned mechanically; condensers not aligned electrically; defective coil or connections; low or incorrect socket voltages; rectifier tube defective. Referring to the trimming condenser, if a peak or point of loudest reception cannot be secured by adjusting the trimmer condenser, look for an open antenna lead-in, grounded antenna, or shorted lightning arrester. A defect in the receiver or a wrongly connected local-distance cable may produce the same effect.

Poor tone quality might be caused by a defective power tube; unmatched power tubes; lack of C bias; incorrect voltages. Rattles and vibration may be caused by a speaker out of adjustment. Make sure the wires from the voice coil are not lying against the diaphragm. Also make sure the vibration is not caused by loose parts, such as the chassis holding bolts, etc.

Noise level is treated of in the manual since it covers a condition that is hard to explain to the lay user of a radio set. Noise level is the term ap-

plied to the amount of static and interference noise heard with the receiver turned on fully but not tuned to a station signal. If the noise level is high it is obvious that a weak or distant station will not be heard above the interference. The noise level is higher in summer, due to natural static, and is higher in congested districts or near trolley lines because of man-made inter-

ference. Experience with receivers for automobile use has shown that a very considerable difference in reception may occur in a very short distance. In general, reception is better in thinly populated or suburban districts than in congested sections.

A loose connection anywhere in the receiver or accessories may produce noisy reception. Check the antenna and

## Bosch Model 58

Tube Type	Position in Set	A Volts	B Volts	C Volts	Cathode Volts	Screen Volts	Normal Plate M. A.	Plate Grid Test	M. A. Change
224	1 R.F.	2.2	170	2.2	---	75.	3.0	---	---
224	2 R.F.	2.2	170	2.2	---	75.	3.0	---	---
224	3 R.F.	2.2	170	2.2	---	75.	3.0	---	---
224	Det.	2.2	30*	1.5	---	10.*	.1*	---	---
227	1 A.F.	2.2	150	8.0	---	---	5.0	---	---
245	P.P.	2.4	250	50	---	---	30.	---	---
245	P.P.	2.4	250	50	---	---	30.	---	---
280	Rect.	5.0	---	---	---	---	---	---	---

Line voltage 115. Volume control maximum.

\*Approximate, since measured through high resistance.

Fig. 1. The table of tube characteristics as given in the Bosch manual covering model 58 may be seen above. Values marked with an asterisk are approximate since measurements are made through a high resistance

ference. In some locations, therefore, reception of distant, or in some cases even semi-distant stations, may be impossible due to the high noise level.

A word or two about location seems proper. Local conditions have a decided effect upon reception. For this reason identical receivers will perform differently when installed in various different locations in the same town or

ground system, also the speaker cord.

The house lighting system should be checked for loose connections, defective switches or sockets. Jarring the cabinet will frequently indicate if the loose connection is in the receiver. Noise caused by turning the selector control is generally caused by condenser plates touching, or particles of metal between the plates.

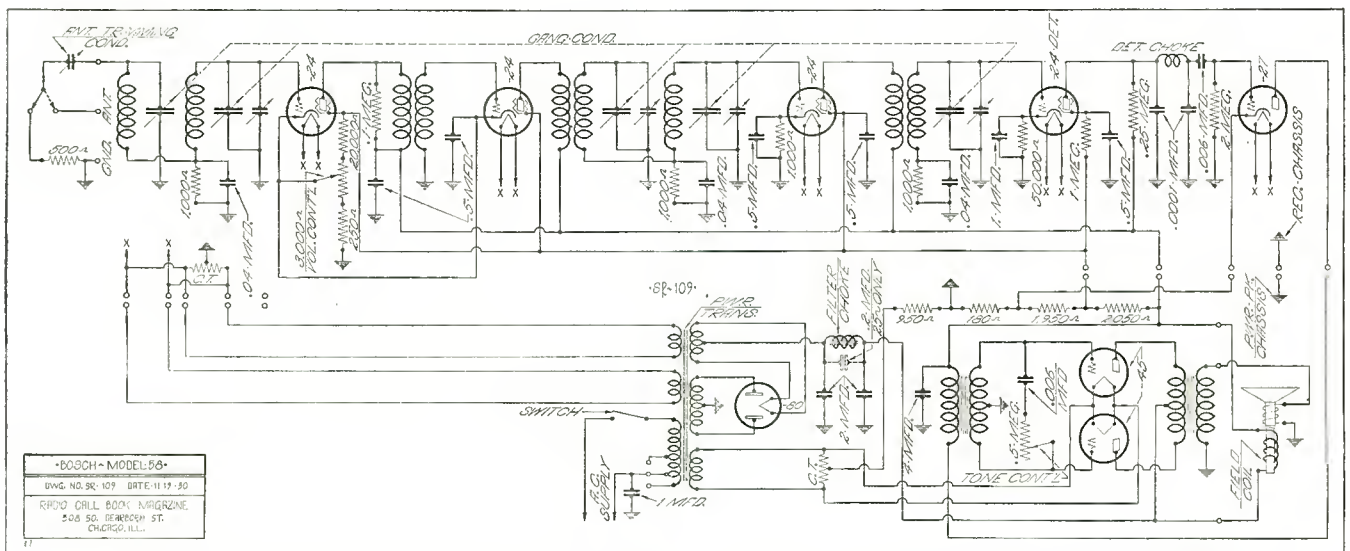


Fig. 2. The receiver and power supply of the Bosch model 58 is found in the schematic drawing above





# Amrad Receiver Model 84

**I**N the schematic diagram at the bottom of this page will be found the electrical connections for the Amrad model 84 receiver. A table of the tube operating values will be found in Figure 1, these values being taken from the voltage limits table shown in the Amrad service manual from which extracts have been made.

### How Voltages Derived

An examination of the circuit diagram in Figure 2 will show that the return plate circuit from the speaker field is connected directly to the r.f. and first audio plates and through a 100,000 ohm resistor to the detector plate. Thus, practically the same voltage is applied to the r.f. and first audio plates while a somewhat lower voltage is applied to the detector plate. The appropriate positive voltage for the screen grid of the detector tube is applied through a 1 megohm resistor connected to the positive plate circuit return from the speaker field.

Below the first audio tube on the circuit diagram a branch of this positive plate circuit passes down through a string of resistors, 2500, 1100, 330 ohms and thence to ground (chassis). These resistors supply potential to the r.f. screen grids and the first audio emitter. The circuit to the r.f. screen grids runs from the junction of the 2500 and 1100 ohm resistors through a 10,000 ohm (20,000 ohm in later chassis) to the tubes. The emitter of the first a.f. tube is connected to the junction between the 330 and 1100 ohm resistors. Emitters of the r.f. tubes are grounded to chassis through proper resistors shown. Emitter of the detector is biased to ground with a 20,000 ohm resistor.

### Output Grid Bias

Grids of the output tubes are biased with approximately 360 ohms from center tap of the filament resistor to ground. Biasing of the first a.f. tube is accomplished by the resistor between the emitter and ground.

### Volume Control

In the grid circuit of the first a.f. tube is a variable coupling resistor

taining the emitters at positive potentials with respect to chassis and partially, when grid current is flowing, by the drop due to the grid current in the 60,000 ohm resistor in the detector grid circuit. This latter drop due to grid current is the basis of the automatic volume control. A signal strong enough to cause grid current to flow in this circuit automatically increases the negative bias on the grids of the r.f. and

### Amrad Model 84

Tube Type	Position in Set	A Volts	B Volts	C Volts	Cathode Volts	Screen Volts	Normal Plate M. A.	Plate M. A. Grid Test	Change
224	1 R.F.	2.3	170	2.5	---	60.	---	---	---
224	2 R.F.	2.3	170	2.5	---	60.	---	---	---
224	3 R.F.	2.3	170	2.5	---	60.	---	---	---
224	Det.	2.3	95	4.0	---	35.	---	---	---
227	1 A.F.	2.3	130	8.0	---	---	---	---	---
245	P.P.	2.3	220	40.	---	---	---	---	---
245	P.P.	2.3	220	40.	---	---	---	---	---
280	Rect.	4.6	250	---	---	---	---	---	---

Line voltage 117. Volume control maximum.

Fig. 1. Tube operating values in the above table are derived with speaker connected and line voltage of 117, with fuse in high position. Measure plate and grid voltages with a high resistance d.c. voltmeter (600 ohms or more per volt) from plate or grid contact to emitter contact, except for the grid voltage of the first a.f. tube which should be measured from emitter to chassis

which is used as a manual volume control. Since it follows the detector in the circuit, it controls the volume both of the radio signals and of the phonograph reproduction through the phonograph terminals.

### R.F. and Detector Bias

The biasing of the r.f. and detector tubes is partially accomplished by main-

detector tubes. This decreases the amplification in the r.f. and detector stages.

### Local-Distance Switch

In addition to the manual volume control and automatic volume control, a local-distance switch is provided for adapting the receiver to the reception of powerful signals from nearby stations.

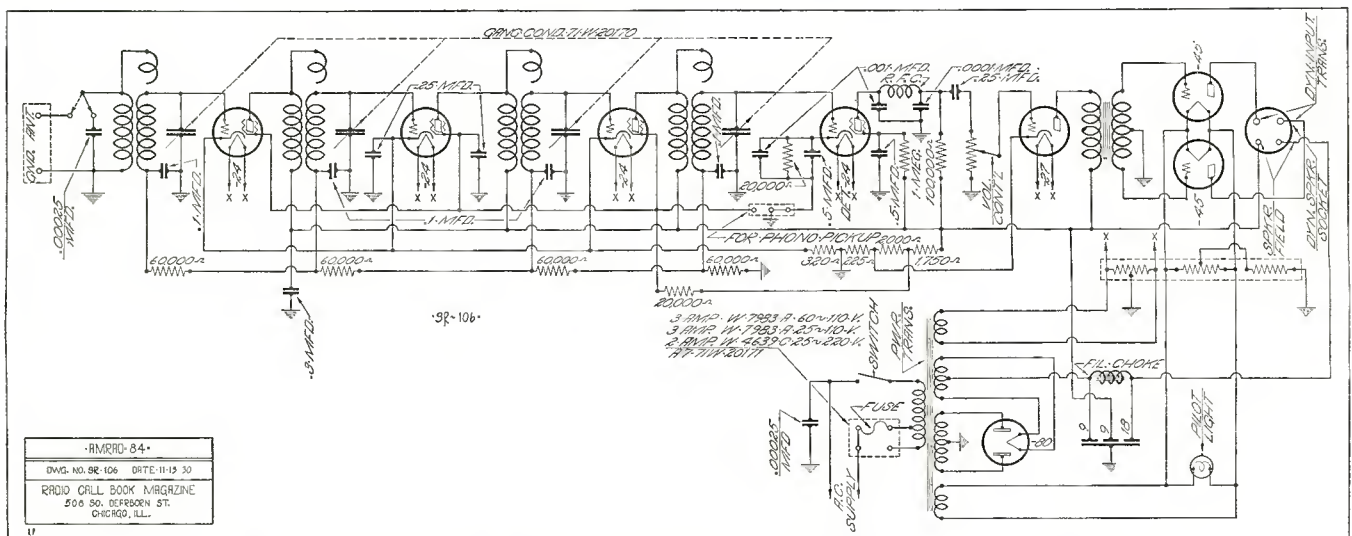


Fig. 2. The schematic diagram of the Amrad model 84 is shown in this drawing



# Radiola Receiver Model 44

**P**ROBABLY on account of the great numbers of these receivers in service in the field, our information department has been besieged with requests for information covering the Radiola 44 receiver. Tube operating values in Figure 1 and the schematic of the receiver and power supply in Figure 2 will be of interest, together with such other important service data as can be abridged from the manual for that model.

### Excessive Hum

Excessive hum during operation of the receiver may be due to: external pickup. Throw switch to local position and see if hum disappears; a.c. input plug reversed, try reversing its position; open center tap resistance in socket power unit; shorted bypass and filter condensers, generally accompanied by inoperation; low emission 280 rectifier; defective dynamic if used; open resistance unit, usually accompanied by inoperation; if the .25 and 1.75 mfd tapped connections of the receiver 1 mfd bypass condenser are reversed a loud hum may be present; hum may also be caused by the speaker being out of center, check on this condition by releasing the center screw so that the cone can find its own center, and then tighten the center screw.

### Oscillation

Oscillation through any part of the tuning range may be attributable to shields not properly in place, or not making contact with base on account of dirt; shield over antenna lead to local-distant switch not grounded or properly covering the leads; defective r.f. filter in detector plate circuit; there are two filters, one of which is shunted by two condensers in the plate circuit of the detector, oscillating occurring if the filters are defective or the condens-

ers go open; contact clips between shield and condenser shaft broken or not making good contact; open bypass condenser; defective 224 tube.

### Service Hints

A brief resume of the service data chart shown in the Radiola 44 manual follows:

No signals: defective operating switch, defective volume control; defective r.f. transformer; defective coupling reactor; defective bypass condenser; defective socket power unit.

fective audio system; open grid in any stage.

Uncontrolled oscillation: shields not in place, or making good contact; tube shields not in place; defective r.f. filter.

Tubes fail to light: no a.c. line voltage; operating switch not on; defective a.c. input cord; defective power transformer.

### Antenna Installations

Covering special antenna installations for noisy locations, it is noted: Erect as

## Radiola Model 44

Tube Type	Position in Set	A Volts	B Volts	C Volts	Cathode Volts	Screen Volts	Normal	Plate	Grid	Change
							M. A.	M. A.	M. A.	M. A.
224	1 R.F.	2.35	164	1.5	1.5	45.0	3.8	2.3	1.5	1.5
224	2 R.F.	2.35	164	1.5	1.5	45.0	3.8	2.3	1.5	1.5
224	Det.	2.35	100	6.0	7.0	50.0	.8	.7	.1	.1
245	A.F.	250	230	6.0	---	---	34.	---	---	---
280	Rect.	5.0	260	---	---	---	---	---	---	---

Line voltage 120, set on 120 tap. Volume control maximum.

Fig. 1. The voltages shown in the above table are those for the Radiola 44, data being values derived through the use of a Jewell analyzer

Weak signals: local-distant switch not on distant position; lineup condensers not adjusted properly; defective main tuning condensers; defective parts in receiver assembly; defective parts in socket power unit; low line voltage.

Poor quality: defective coupling reactor, condenser or resistor in coupling circuit; defective output condenser or choke; local-distant switch not properly operated.

Audio howl: receiver oscillating; de-

long and as high an antenna as possible and then couple it to the antenna lead of the receiver through a small coupling condenser. This condenser with a 200 foot antenna should be about .0003 mfd and smaller with larger antennas. The effect of the long antenna is to increase the pickup to a point where it will be proportionately higher than the noise level. The series condenser then reduces the effective antenna capacity and limits the input energy to the receiver.

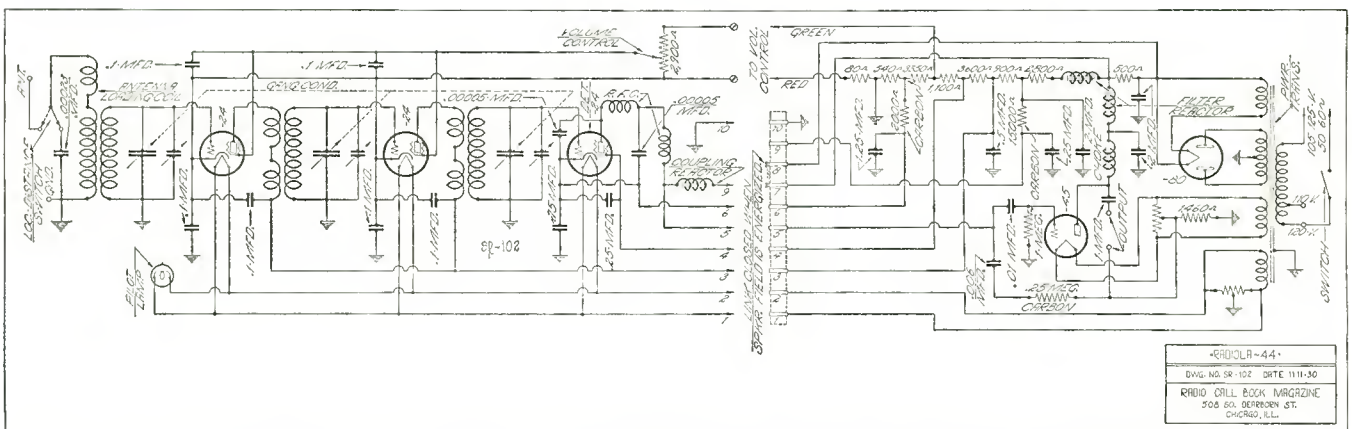


Fig. 2. The schematic of the receiver and its power unit is shown above for the Radiola 44

# Westinghouse Model WR-4

ON this page are given the tube operating values and the schematic diagram of the Westinghouse WR-4 receiver, a seven-tube tuned r.f. model whose response curves appeared on page 65 of the November issue of this magazine.

Examining the circuit in Figure 2, antenna and ground are connected to each side of a 50,000-ohm potentiometer, the moving contact of the potentiometer connected to one side of the primary of the first r.f. transformer, the other side connected to ground. The action of the potentiometer is one-half the action of the volume control (the other half being in the 50,000-ohm potentiometer across the 12,000-ohm resistor, the movable arm connected to terminal 3 shown in the schematic).

The secondary of the r.f. transformer is connected to grid circuit of the first 224 which is tuned by the first unit of the gang condenser. The plate circuit of this tube contains a high impedance coil inside the grid coil of the second r.f. transformer. This plate coil is of the proper impedance to match the 224 and is at right angles to the grid coil in which it is located. This is done so that the inductive coupling between these circuits is at a minimum. A single turn at one end of the grid coil is connected to the 224 and provides capacitive coupling between the circuits. The reason for using capacitive coupling instead of inductive is that the primaries of the r.f. transformer resonate at about 350 kc. with receiver capacitance and tend to increase the sensitivity at the low end of the range. Capacitive coupling has less reactance to high frequencies than to low frequencies, thereby increasing the effective coupling at the high frequency end. A combination of the two gives about equal gain throughout the tuning range.

The following two r.f. circuits function in the same manner as the one already described. The screen grid voltage of these three 224's is varied by means of the second section of the volume control. This action occurring simultaneously with the variation of input voltage to the first tube gives a positive control of volume without distortion.

The detector circuit functions as a biased-grid power detector, operating at a high plate voltage so that an out-

the 245 tubes. Hence impedance coupling is used; one-half of a tapped reactor being in the plate circuit of the detector. This reactor is of quite high impedance and functions as an auto-transformer. Two coupling condensers are used to pass the a.c. component of the detector output to the grids of the 245 tubes. Two high resistance units are used so that the proper grid bias may be impressed on these tubes.

The output of the 245 tubes is coupled to the cone coil of the dynamic

## Westinghouse Model WR4

Tube Type	Position in Set	A Volts	B Volts	C Volts	Cathode Volts	Screen Volts	Normal Plate M. A.	Plate Grid Test	M. A. Change
224	1 R.F.	2.3	160	2.5	---	85	3.0	---	---
224	2 R.F.	2.3	155	2.5	---	85	3.5	---	---
224	3 R.F.	2.3	155	2.5	---	75	3.5	---	---
224	Det.	2.3	225	7.5	---	55	.5	---	---
245	P.P.	2.3	200	1.0*	---	---	25.0	---	---
245	P.P.	2.3	200	1.0*	---	---	25.0	---	---
280	Rect.	4.6	---	---	---	---	---	---	---

Line voltage 120. Volume control maximum.

\*Not true reading due to resistor in circuit.

Fig. 1. The tube voltage values shown in this table are taken from the tables shown in the service manual covering the Westinghouse WR-4 receiver

put sufficient to swing the two 245 tubes to maximum output is obtained. The detector tube is operated at 250 volts plate potential and 10 volts negative bias. It will be noted that the bias reading of 1 volt for the grids of the 245's as shown in the tube operating table is the result of making this reading through a high resistance.

As the 224 detector must work into a high impedance, transformer coupling would not be suitable for coupling into

through a center-tapped primary, step-down transformer.

A full wave rectifying circuit using a 280 provides the d.c. voltages necessary for the plate and grid supply of all tubes and also for the dynamic field supply. The filter circuit is of the type employed in the superheterodyne models, except that a .1 mfd condenser is used to bypass any high frequency ripple that may be present in the rectified output.


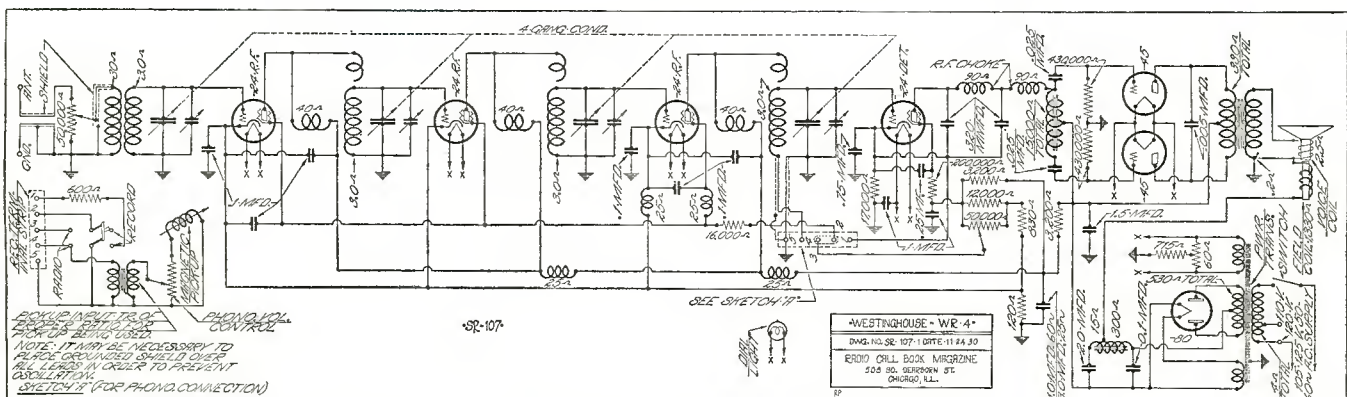


Fig. 2. The drawing here shows the electrical connections of the receiver and power supply of the Westinghouse WR-4 receiver

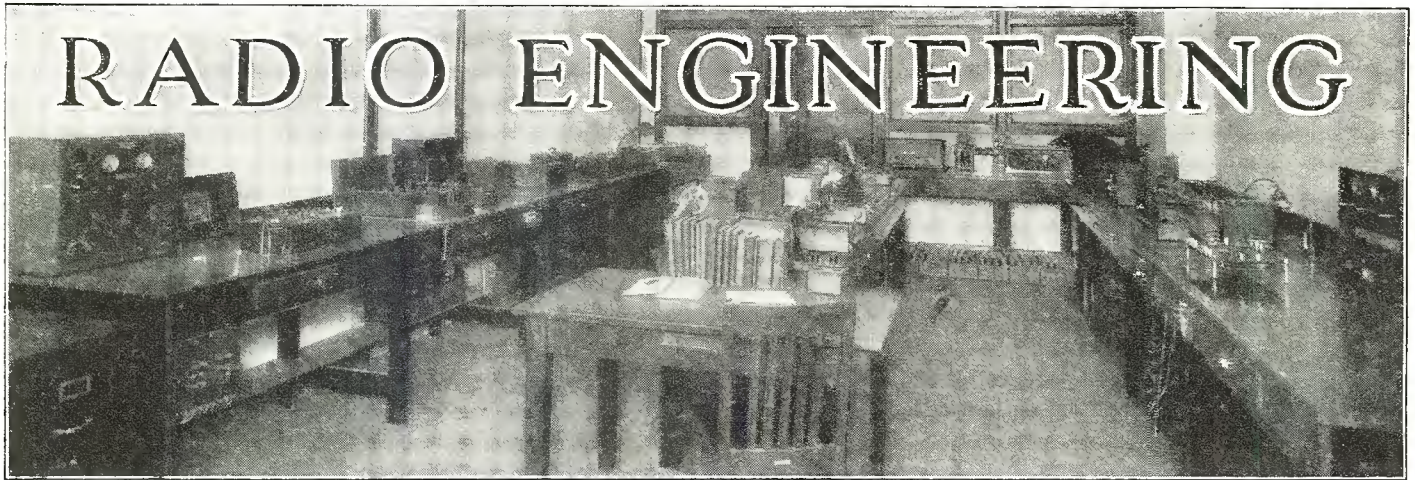



## Speakers and Theater Sound Reproduction

By LOUIS MALTER\*

**T**HE ultimate goal in theater reproduction of sound motion pictures is the complete simulation in each part of the theater of the sound originally impinging upon the pickup microphone. This goal is at present far from having been achieved, one of the weakest links in the chain between sound striking the microphone and the sound impinging upon the ear of the auditor being the loudspeaker.

At the present time the two chief types of loudspeakers in use in theaters are the cone speaker with directional baffle and the horn type speaker.

In the following discussion the elements which measure the satisfactoriness of a loudspeaker, and the influence of these elements on the reproduction obtained from the two types of loudspeakers mentioned above will be considered. The results of certain measurements will be used to explain the quality of reproduction obtained with each type of loudspeaker in theaters.

### Elements Determining Loudspeaker Performance

The extent to which a loudspeaker can deliver satisfactory reproduction is measured by five factors, which may be classified in order of importance as follows:

1. Frequency range.
2. Uniformity of response.
3. Radiation distribution characteristics.

If the pressure at a great distance from the speaker is measured at various angles with the normal to the mouth of the speaker a continuous curve is obtained. If the intensity along the normal is set equal to unity the curve ob-


*Mr. Malter's paper reproduced on these pages, is reprinted from the Journal of the Society of Motion Picture Engineers, Vol. XIV, Number 6, 1930, pp. 611-622.*

*It is particularly interesting to those desiring to keep pace with developments in the theater sound reproduction field.—Editor.*

tained is defined as the radiation distribution characteristics for the particular frequency at which the measurement is obtained. The family of curves showing the radiation distribution characteristics throughout the frequency range is a measure of the quality of reproduction at various angles to the normal. The ideal characteristic is that in which the intensity is uniform for all frequencies throughout the angle defined by the entire audience in a theater at the center of the speaker mouth and which then falls off to zero very sharply outside this angle.

#### 4. Efficiency.

The absolute efficiency of a loud-

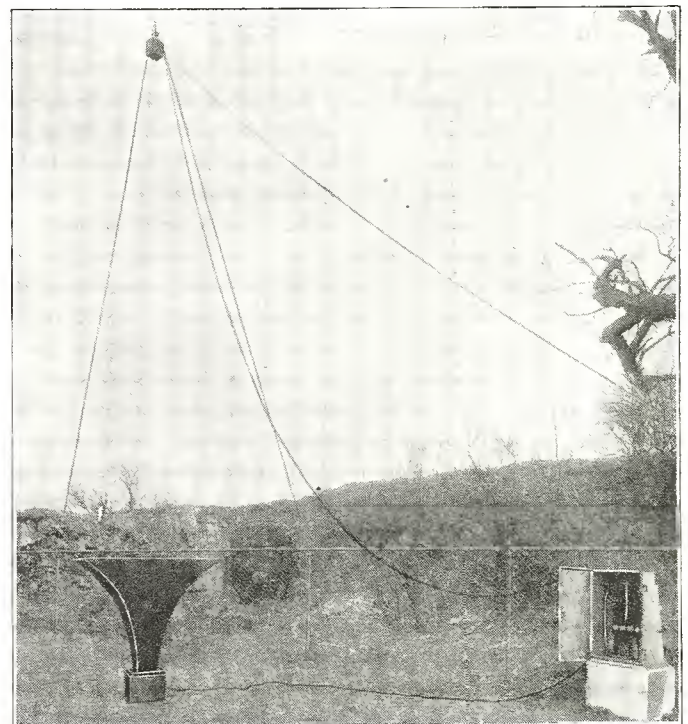

*Fig. 2. This photograph shows a set-up to determine frequency response characteristics of the speaker for higher frequencies*

\*RCA Photophone, Inc., New York.

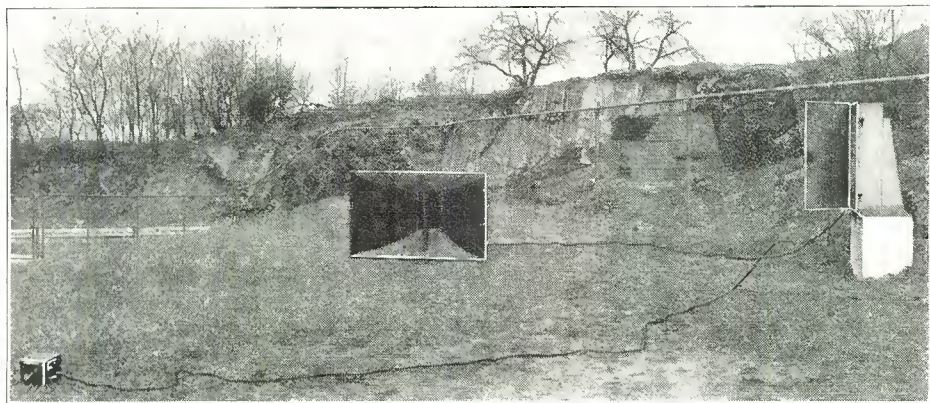


Fig. 3. Here is shown a setup to determine frequency response characteristics for lower frequencies

speaker is defined as the ratio of the total acoustic power radiated by the loudspeaker to the total acoustic power radiated by an ideal loudspeaker if fed from the same electrical source.

#### 5. Input power capacity.

The input power capacity of a loudspeaker is measured by the value of  $\frac{e^2}{4r}$

where  $e$  is the maximum open circuit voltage which can be impressed upon the loudspeaker terminals without producing noticeable distortion, and  $r$  is a resistance equal in magnitude to the impedance to which the speaker is designed to be connected.

### Loudspeaker Measurements

In order to obtain an accurate and absolute comparison between the performance of the "directional baffle type" loudspeaker and the horn type loudspeaker, frequency response characteristics of the most widely used type of directional baffle type loudspeaker and of the most widely used type of horn loudspeaker were obtained in the following way.

Each loudspeaker was placed on the ground out of doors pointing directly upward and at a sufficiently great distance from buildings so that reflections from these did not affect the results obtained. A condenser microphone was suspended directly above the center of the loudspeaker mouth at a distance of 20 feet. (See Fig. 2.) The condenser microphone was connected to a sound amplifier. The entire sound measuring equipment was corrected electrically so as to possess a uniform over-all frequency characteristic.

The frequency-response characteristics obtained in this manner are correct down to a frequency at which the radiation distribution characteristic of the speaker becomes so broad that sufficient sound is reflected from the ground to interfere with the radiation shooting straight up. In order to obtain the frequency characteristic for the lower frequencies, the speaker is placed along the ground with its mouth pointed to-

wards the condenser microphone, which is placed close to the ground and at a distance of 20 feet from the speaker mouth. (See Fig. 3.) In this case the phase difference at the microphone between the direct radiation and that reflected from the ground is negligibly small at low frequencies so that the actual low frequency characteristic is obtained. This low frequency characteristic, however, must be divided by two due to reflection from the ground. (The assumption of practically complete reflection from the ground has been checked by experiment.) The fact that over a certain region (300 to 500 cycles) both methods yield the identical result is a further check on the composite method.

Fig. 4 is a photograph of the beat-frequency oscillator and high quality amplifier used in making the measurements. These were set up indoors and leads run out to the speaker and the bullet amplifier associated with the condenser microphone. The recording mechanism shown permits of a rapid and accurate frequency response characteristic being taken in a few moments. A complete description of a similar sound pressure recording mechanism has been previously published.<sup>1</sup>

### Discussion of Experimental Results

The frequency response characteristics obtained are shown in Fig. 5. In order to enable a fair comparison to be made between the frequency characteristics of the two types of speakers the two frequency response curves have been so placed as approximately to overlap in the center of the range, *i. e.*, between 300 and 800 cycles. This has necessitated raising the curve of the directional baffle type loudspeaker. (See later discussion under "Efficiency.") A careful study of these curves enables us to make a competent comparison between the two types of speakers as regards frequency range, uniformity of response, and efficiency.

<sup>1</sup>Wolff and Ringel: "Loudspeaker Testing Methods," Proc. Inst. Radio Eng. (May, 1927).

**Frequency Range and Uniformity of Response.**—It is immediately evident that the frequency range of the directional baffle type speaker is greater at both the low and high ends of the scale. The cut-off frequencies of the directional baffle type speaker are about 35 cycles and 6000 cycles at the low and high ends, respectively, whereas those of the horn type speaker are about 125 cycles and 5000 cycles, respectively. Thus at the lower end of the frequency scale the directional baffle type speaker has a half octave frequency range than the horn type and about 1/5 octave more at the higher end.

As regards uniformity of response the directional baffle type of speaker obviously has the advantage. Between 300 and 5000 cycles the response of the directional baffle type is slightly more irregular, but between these limits the variations in the response of the horn type are greater. Below 300 cycles, however, the horn type speaker is appreciably less responsive than the directional baffle type. As will be seen below, this deficiency in low frequency response in the horn type speaker is a serious defect.

**Efficiency.**—In order to enable a fair comparison to be made between the frequency response characteristics of the two types of speakers, the response characteristics of the two types of speakers, the response curve of the directional baffle type speaker was raised 7 decibels. In order to determine the relative average efficiencies of the two types of speakers the curve for the directional baffle type speaker was placed at its proper level, and the average response between its cut-off limits (90 and 6000 cycles) determined by means of a planimeter. The result obtained is 15.6 decibels. The average response of the horn type loudspeaker for the same input power and between the same limits is 13.3 decibels. The average straight-ahead response of the horn type loudspeaker is thus 2.7 decibels greater than that of the directional baffle type loudspeaker, for the same power input. This corresponds to a power efficiency ratio of 1.9 to 1.0. This difference corresponds to between 1 and 2 steps on the average gain control and is consequently of minor importance.

**Radiation Distribution Characteristics.**—The radiation distribution characteristics of both types of speakers as now used are sufficiently good to yield satisfactory results. The distribution characteristics are fairly uniform through angles of about 20 degrees to each side of the normal to the mouth opening. In the average size of theater this is sufficient. In wider and larger houses, two or more speakers may be used, thus securing good directional characteristics as well as permitting an increase in the total amount of radiation as required by the larger size of the house.

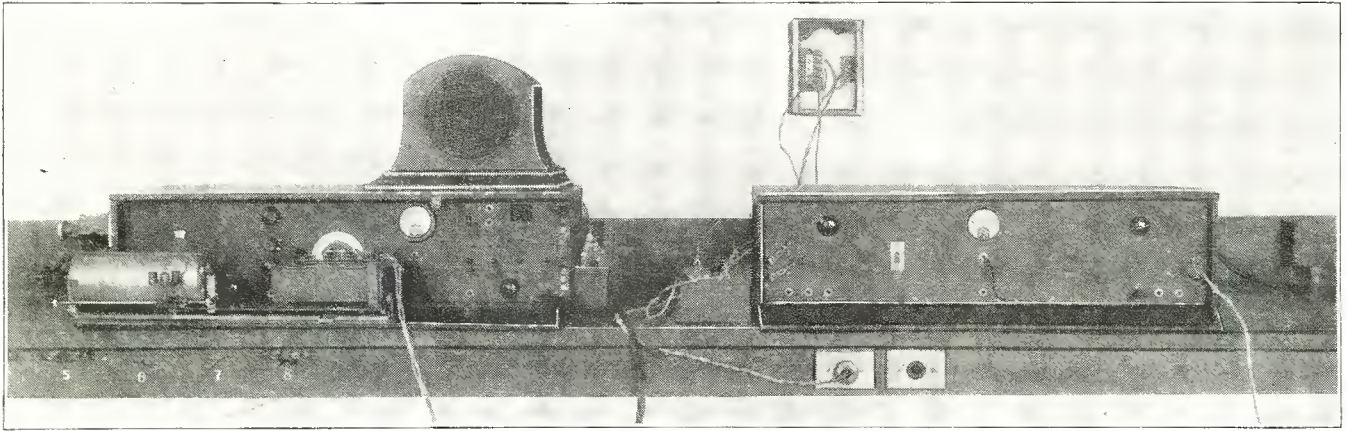


Fig. 4. This photograph shows the beat frequency oscillator and high quality amplifier used in making the measurements

**Input Power Capacity.**—No accurate measurements were made with respect to this quantity. However, it has been our observation that similar houses require the same number of speakers of either type for satisfactory sound reproduction. This indicates that, in view of the somewhat greater efficiency of the horn type speaker, the directional baffle type speaker has the edge in respect to input power capacity. This is what might be expected from the fact that the radiating surface of the directional baffle type speaker, *i. e.*, a cone, is much sturdier than the fragile metal diaphragm of the horn type speaker.

#### Results in Theaters

It is exceedingly interesting to compare the results obtained with both types of speakers on listening tests in theaters and see to what extent these results are explainable on the basis of the measurements described above.

Comparisons of this sort must be made separately for both speech and music.

If, in the reproduction of speech, we fix our attention upon the *understandability* only, we find that each of the loudspeakers is equally good. However, although speech on each of these speakers is equally understandable, the reproduction on the directional baffle type speaker is far more *natural* than on the horn type speaker. Reproduction on the horn type speaker has an unnatural quality. All voices sound very much alike whether of the same or opposite sex. Looking away from the screen makes it sometimes difficult to distinguish the sex, except from the context. Male voices, particularly, sound too high pitched and unnatural.

These results are easily explainable on the basis of the obtained frequency characteristics. It is well known that the elimination of all frequencies below 300 cycles and above 4000 cycles exerts a negligible effect upon the understandability of speech. Since, on the whole, the response of the two speakers between these limits is the same, we would expect the understandability to be the

same. This is what is actually observed.

However, the characteristic frequencies of the speaking voice lie below 300 cycles. They center around 125 cycles for the male voice and around 250 cycles for the female voice. It is these "fundamental" frequencies which give to each speaking voice its individuality and distinctiveness. A lack or deficiency of the frequencies below 300 cycles will rob the voice of these characteristics. This accounts for the superiority in naturalness of speech reproduction on the directional baffle type loudspeaker. The response of the directional baffle type speaker, between 100 and 300 cycles, is considerably greater than that of the horn type speaker between the same limits. This is particularly true below 140 cycles. Around 100 cycles the difference in response is around 12 decibels.

The reproduction of music is also adversely affected by the deficiency in the response below 300 cycles. Music reproduced on a horn type speaker lacks the fullness and depth apparent in the reproduction by the directional baffle type speaker. The complete reproduction of the lower register instruments is impossible on the horn type speaker. The result is that music loses its real quality and retains merely its melody. This is particularly true for music of a symphonic nature.

In a recent paper<sup>2</sup> certain statements


are made in a discussion of horn and cone (or baffle) type speakers. The cone (or baffle) type speakers referred to in that paper are of a type wherein cones are set in a flat baffle, a type which is much less widely used than the directional baffle type speakers. Some of the claims made for the horn type loudspeaker are not borne out by our experiments. Thus it is claimed that the horn type loudspeaker and flat baffle type of loudspeaker are equally satisfactory as regards frequency characteristics. This may be true in theory but tests of actual devices as used in commercial practice show that the upper and lower cut-off frequencies of the flat baffle type of loudspeaker, which coincide approximately with those of the directional baffle type using the same cone, are much more widely separated than those of the horn type loudspeakers.

In addition the claim for power efficiency ratio of the horn type speaker to flat baffle type of 10 to 1 refers to a single cone in a flat baffle. In practice cones are never used this way in theaters, being either used in multiple on a flat baffle or, as is commonly the case, being set in a directional baffle. Either of these setups results in a

<sup>2</sup>Blattner and Bostwick: "Loudspeakers for Use in Theaters," J. Soc. Mot. Pic. Eng. XIV (Feb., 1930), No. 2, p. 151.

(Continued on page 82)

Fig. 5. This graph shows the relative frequency response characteristics of the two speakers, the dotted line being the horn type, and the solid line the directional baffle type

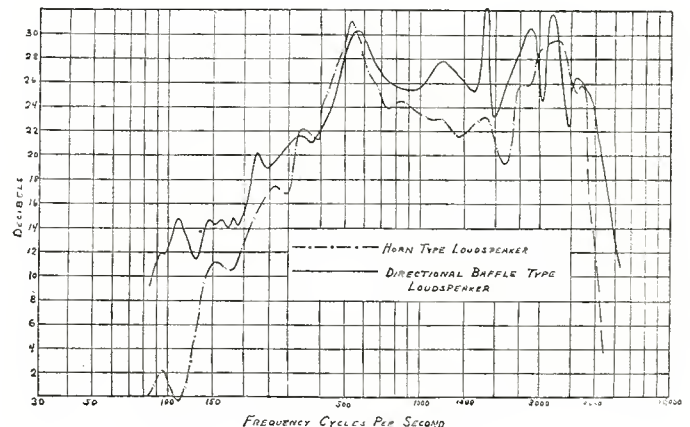

## WRIGHT-DECOSTER REPRODUCERS

*It is truly the outstanding "speaker of the year"*

The tonal quality, clarity and volume on distance is exceptional. All of the fine qualities of WRIGHT-DE COSTERS theatre reproducers, which are being used all over the world, are combined in the home models.

*The Speaker  
of the Year*



*Model 217 Jr.  
Chassis*

### For Tone and Volume on Distance

Those who are looking for the best reproducer for their receiving set, invariably choose the WRIGHT-DECOSTER. You can have the Junior Model in either a beautiful table or console cabinet, or we can furnish a Junior chassis which will match any receiving set perfectly.

*Write for complete information and  
address of nearest sales office*

**WRIGHT-DECOSTER, INC., 2215 University Avenue, St. Paul, Minn.**

Export Dept., M. SIMONS & SON, 25 Warren Street, New York. Cable Address, Simonrice, New York



**Model A  
PHONOGRAPH AND RADIO SPEAKER  
COMBINATION**

This superb creation, which is used in the lobbies of some of the largest and most beautiful theatres in the country, is an ideal reproducer for the home. In addition to being a beautiful piece of furniture, it will reproduce everything from a talking voice to a full symphony orchestra with such precision and fidelity as only a WRIGHT-DECOSTER REPRODUCER can.

### Locating Internal Noises in Receivers

*(Continued from page 55)*

will also cause excessive regeneration or oscillation, even though the set is neutralized. The better the shielding in a set, the more amplification we can get out of it and still have the set stable. But there is a definite limit to this amplification. Now if there are any conditions which tend to increase this amplification, feedback and oscillations will occur with resultant noise. One of the causes of this is excessive plate voltage and in case of screen grid tubes—excessive screen grid voltage.

III. One important object of shielding is to prevent coupling from one coil to another. Manufactured receivers are supposed to have satisfactory shielding. Trouble frequently arises when the shields are not securely in place. Shields may not be properly grounded. The shielding should, therefore, be examined to make sure it makes perfect contact.

IV. Open by-pass condensers. Plate by-pass condensers are employed for the purpose of eliminating the coupling which is always present in the plate supply. If by-pass condensers of any sort become defective or short circuited, they are likely to cause noise.

By-pass condensers are connected across grid bias resistances. If these by-pass condensers are open, oscillation will result. Condensers suspected of producing noise should be thoroughly checked with a d.c. potential of from 200 to 500 volts. Connect the condenser across any d.c. potential lying between the above values and then short circuit its terminals. If not defective, a spark will be produced. This applies only to by-pass condensers having a capacity of above .25 mfd.

#### A. F. Regeneration Noises

Under this we will consider motor boating as well as other possible sources of noise.

The following noises are frequently encountered in audio frequency systems:

1. Coupling between speaker leads and detector grid circuits. If the speaker, a.c. line or plate leads are near any part of the detector grid circuit, they may cause squealing. The remedy is obvious. Keep all leads as far away from the detector grid circuit as possible.

2. An open plate circuit in the detector will cause a howling noise. Tracing back over the plate circuit will of course establish the fault.

3. Open grid circuits will cause squealing noises. Open grid circuits may be caused by open secondaries of audio transformers, open grid bias batteries, open grid bias resistors, or open grid return connections. This condition is generally indicated by an absence of grid bias on the audio frequency tubes.

4. If the trouble is due to motor boating, it manifests itself by a steady "put put" sound resembling a motor boat in action. This is due to a low oscillatory feedback in the eliminator or power pack circuit. To eliminate this, connect large by-pass condensers across each of the voltage dividers to ground. By-pass condensers of about two microfarad capacity can be connected between the plate circuit and filament circuit to reduce motor boating.

#### Noises Due to Tube Howling


Microphonic tubes often cause a ringing sound in the loudspeaker gradually increasing in intensity, which is generally caused by the vibration of the tube elements in the detector or audio frequency stages. This vibration causes the plate current to change very rapidly and the change in plate current is transmitted through the set resulting in the ringing sound. It is usually sound waves coming from the speaker that set the tube into vibration.

Special heavy weights can sometimes be placed on micro-

*Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review*

# THE NEW DAYRAD SELF-BIASING TUBE CHECKER

(Type L)

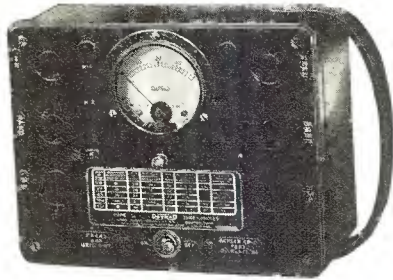

A revelation in tube checking methods; a long step forward in the interest of dealer and service man; an instrument which adds to servicing efficiency and insures greater customer satisfaction.

Checks all tubes for "End of Life"—  
Finds open and short circuits—  
Tests both 280 Plates separately—  
Shows up noisy tubes—  
Locates the "Duds"—

Yet the net price  
to dealers is  
but

**\$27.60**


## DayRad Type 180 Test Oscillator

The many models of Super Heterodyne radio now in use makes necessary the aligning of Intermediate Frequency stages.

This Oscillator is equipped with an Output meter for visualizing adjustments, is also a Broadcast Frequency Oscillator, and is the universal instrument for aligning, ganging, neutralizing and other functions. Accuracy is assured; sensitivity and selectivity in the greatest degree are secured.

Dealers'  
Net Price

**\$57.50**

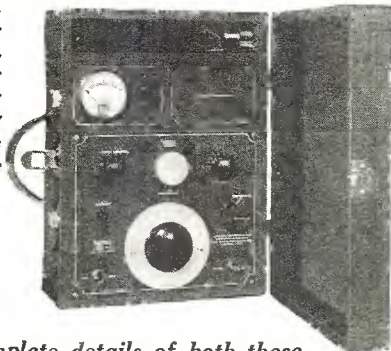

Send for complete details of both these instruments, and ask for any other information you may need. We are always glad to co-operate.

**The Radio Products Company**

5th & Norwood

Dept. K

Dayton, Ohio

phonic tubes to prevent them from vibrating. An application of several turns of friction tape around the top of a tube will sometimes reduce a microphonic condition.

In most cases it is best to rearrange the tubes until you find one that is not microphonic. In the modern receiver, microphonics are rarely encountered and are most always due to a defective tube.

### Further Notes on Mechanical Noises

1. Sputtering, snapping noises—these noises are caused by electric sparks due to the breakdown of insulation in some part of the circuit. They can be heard even with the loudspeaker disconnected and are invariably due to defective insulation either on wires or the terminal strip. Where this occurs, separating the wires or cleaning terminal strips is the only remedy. A visual inspection while the set is operating will reveal where the breakdown occurs.

2. If there are any loose parts in the receiver such as loose screws and nuts, these parts may be set into vibration when the loudspeaker is in operation. Noises thus developed are clicking, rattling, metallic noises. The remedy, of course, is to tighten up these parts.

3. If the power transformer vibrates or hums excessively, tighten the clamps which hold the transformer core. If the windings are loose, wedge them by means of bakelite or dry wood spacers.

### Speaker Noises

These noises are mechanical in origin and consist of rattles, clicks and scratches. In most cases the defect can be established by visual inspection. The two main types of speakers in use are the magnetic and dynamic. Most troubles will be found to be in dynamics, as more dynamics than magnetics are in use.

In the case of a magnetic speaker, we generally have more moving parts, such as springs, driving pins, and more soldered connections. There are always two or three soldered connections on a magnetic speaker and they are likely to develop noise. Connections should be examined carefully and the cone and driving pin moved back and forth to see that the driving pin does not slip through the solder.

The most common trouble in dynamic speakers is caused by the voice coil dragging against pole piece. This produces scratching and distorted sounds and is easily recognized. Some dynamic speakers have an adjusting screw attached to the center of the electromagnet, which in turn is mechanically connected to the voice coil of the speaker by means of a bakelite strip which is called the spider. By adjusting the screw that is attached to the pole piece, the position of the voice coil can be varied in relation to the pole piece. This screw should be adjusted until the voice coil does not touch the pole piece at any point. A thin piece of paper inserted between pole piece and voice coil can be used to gauge the distance between the two.

Sometimes dust and foreign particles get between the pole piece and the voice coil and these in turn cause certain noises. One effective way of removing these is to use a blower from an ordinary vacuum cleaner. Before using the blower, however, turn it on to be sure that no dirt is in the pipe. Then allow the full force of air to blow between the voice coil and pole piece, moving the diaphragm up and down at the same time with your hand. This generally removes all dust from this point.


Examine the cone both at the voice coil and outer edge. If it is torn or uncemented, use ambroid cement, which can be obtained from most speaker manufacturers. If the leather strip or chamois skin is hard in spots, rub it with your fingers on each side until it becomes soft and pliable.

### Tracing Noise

The best instrument which can be employed as an indicator of noise is a good speaker or headset, because, in the last



# Ferranti Amplifying Equipment

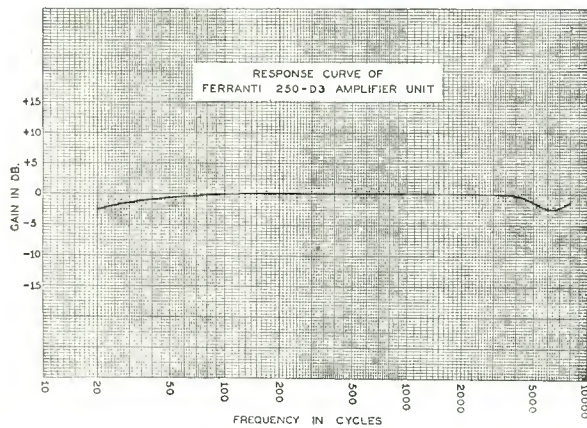

**O**F COURSE, you want an amplifier with a good curve and here it is. But you will also want simplicity in operation and reliability in service and these three requirements are salient features of the new Ferranti D3 equipment.


It is sound judgment to buy for the future as well as the present and in buying Ferranti equipment you insure yourself against necessity for future changes when better accessories are available requiring flattest possible curves for best results.

The above curve of a 250 D3 unit shows remarkable fidelity of reproduction because its greatest loss between 20 and 8000 cycles is less than 3 db. It sets a mark far above usual standards.


The 250 D3 units are equipped with push-pull transformers having primary windings perfectly balanced as regards both resistance and impedance.

Ferranti audio transformers are used in laboratories for inductance standards.

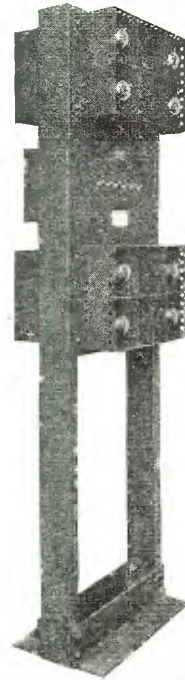Information regarding amplifiers and special transformers sent on request.



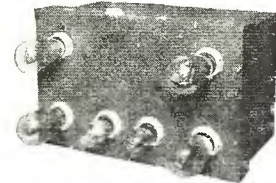(Above)  
250-D3  
DOUBLE  
Channel  
Amplifier  
Unit



(Left)  
250-D3  
SINGLE  
Amplifier  
for home  
and other  
uses

New and Exclusive  
Features



Amplifying Unit

- (1) Unusually high amplification . . . completely fills largest auditoriums.
- (2) High efficiency.
- (3) Low hum.
- (4) No overheating . . . temperature rise never exceeds 25 degrees centigrade.
- (5) No compound of any kind used in power section.
- (6) Electrolytic condensers and dry type transformers and chokes.
- (7) No distortion . . . wide frequency range . . . clarity and timbre on BOTH voice and music.
- (8) Top and bottom units interchangeable without changes in wiring.
- (9) Single or double channel, with any specified input or output impedance.

## FERRANTI, INC., 130 W. 42nd St., Desk 31, New York, N. Y.

analysis, what you hear is what counts. It is of the utmost importance, however, that the speaker or headset be in good mechanical condition.

The most frequent sources of noise are varying resistors, intermittent contacts or shorts. An ohmmeter and continuity tester are frequently of great assistance in detecting these. Intermittent contacts can be quickly established by using the continuity tester shown schematically in Fig. 2. This consists of a voltmeter connected in series with a 4½-volt C battery. When the two test leads are connected across the terminals of the resistor or the apparatus under test it will read less than 4½ volts.

If the meter needle flickers between certain values it indicates a varying resistance and that part of the circuit should be most carefully checked.

In checking the condition of resistors do not bear down on the resistance but pull up with your test leads. This will serve to strain the connection and if an intermittent contact is being made it will show up when making this test.

### Stage by Stage Elimination

If it is determined that the noise is internal it is necessary to locate the particular circuit which is causing the trouble, namely, whether it is in the audio or radio frequency system, the detector or power pack and in which particular stage the trouble arises. The best method to follow here is the stage by stage elimination process. In this method one stage is added at a time and observation made when the noise comes in. All tubes should be kept in operation. This method of test assumes that the aerial and ground system is in perfect mechanical condition and that it is not itself a source of noise.

Assume now that the noise is internal. Therefore, disconnect the aerial and ground. The noise should still be present. Then, short circuit the grid or grids of the output tubes. This immediately disconnects all tubes ahead of the output tube or

tubes. If noise is still present, it means that the source of trouble is in the output stage or in the voltage supply or the speaker and these should be examined carefully.

If noise is not present, the output stage and voltage supply for these tubes is O. K. Now add the first audio frequency stage by disconnecting the short on the grid of the output tubes. Short circuit the grid of the first r.f. tube. If noise comes in now it is in the first audio frequency stage or voltage supply to this stage. These circuits should be critically examined. If noise is still absent, both these stages and their associated voltage supplies are O. K. Next, remove the short circuit from the first audio frequency stage and short circuit the detector grid. Proceed this way until the source of trouble is definitely located in a particular circuit. Knowing the circuit in which the trouble is present, it is a simple matter to make corrections. When each radio frequency stage is checked and the grid of each radio frequency stage is shorted, rotate the variable condenser to see whether this introduces noise. Frequently, the variable condenser plates may short at some point and cause noise. This test should be made with each radio frequency stage shorted so as to determine which particular variable condenser is causing the trouble if any.

### Visual Inspection

Keen visual inspection is one of the simplest and most effective means available for the serviceman's use in locating ordinary sources of noise. In this method. No instruments, other than the serviceman's eyes, are needed but he must exercise his powers of observation. A visual examination of the wiring of the set will show connections which are loose or unsoldered, soldered joints which are corroded or resinous, insulation which is punctured or mechanically injured, tube socket prongs which are bent and make imperfect contact and so on. The possible sources of trouble causing noise which can be detected by the observant eye are many. One of the

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# The Condenser that repairs itself

**THE MERSHON ELECTROLYTIC CONDENSER** cannot be injured by high voltage surges. It provides a high resistance path dissipating surges and protecting its associate equipment from damage. It is self-healing and actually improves with use.

That is one reason why **MERSHON ELECTROLYTICS** are more economical and last longer than other types of filter condensers. Because of these advantages, thousands of servicemen now specify **MERSHON ELECTROLYTIC CONDENSERS** as standard equipment in power packs which they build or repair.

**MERSHON CONDENSERS** are now sold by over forty leading radio parts distributors in the United States. If your regular distributor cannot supply your requirements, write the factory for a list of companies which stock all the standard sizes of **MERSHON CONDENSERS**.





**The Booklet**

**"Puncture-Proof Filter Condensers"**  
contains a complete story of the Merphon.  
Send for a **FREE COPY** Today and Learn  
How to Eliminate Condenser Trouble

## THE AMRAD CORPORATION

155 E. Ohio St.

Chicago, Ill.

# Use a REESONATOR




Now Only \$3.95

The Reesonator is only recommended for sets having an untuned antenna or floating tube, such as: Atwater Kent models, 30, 32, 35, 37, 38, 48, and 49. Radiola models, 16, 17, 18, 33, 51, and 333. Crosley Bandbox and Jewelbox and most models in Victor, Temple, Silver-Marshall, General Electric, Westinghouse, Apex radios, and many others.

### for SHARP TUNING DISTANCE and POWER

**NO**—the Reesonator is not new—it is an instrument which has been on the market for over three years and we have over 40,000 satisfied customers throughout the United States, Canada; in fact, the Reesonator is in use throughout the entire world. Its principle is used in most high powered, modern sets of today. The Reesonator will increase the selectivity and power of your machine to the equivalent of two extra tubes. The Reesonator will enable you to play distant stations with dance volume, that were barely audible without it. It is connected across aerial and ground wires, and can be done by anyone without tools in a minute.
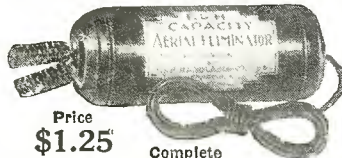
## F. & H. Aerial Eliminator Each Instrument Tested on Actual 1000 Mile Reception



Price \$1.25 Complete

this type of aerial will be used practically entirely in the future. Installed in a minute's time by anyone. Return in three days if not satisfied.

8,000 dealers handle our line. DEALERS! Over 80 leading jobbers carry this line; or order samples direct.

**ITEMS SHIPPED POSTPAID**

Name.....

Address.....

City..... State.....

Inclosed find ( ) check ( ) M.O. for \$.....

( ) or send C.O.D. items checked, under three-day trial money back guarantee.

( ) REESONATOR

( ) F. & H. Capacity Aerial Eliminator.

( ) Literature ( ) Dealers' proposition.

**F. & H. Radio Laboratories** Dept. Fargo North Dakota

first steps to be taken by the serviceman therefore, is to examine critically the wiring and construction to see what defects can be found.

## Increasing the Utility of D. C. Meters

(Continued from page 51)

resistance of 1500 ohms. This same scale may be used for other values of voltage and calibrating resistance by using the multiplying factors shown in the table.

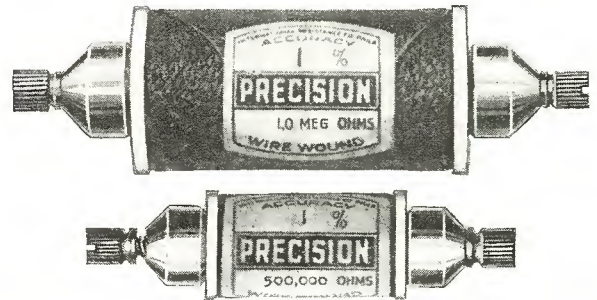


Fig. 7. Here are shown two of the different types of precision units used in the applications mentioned by the author

It is of course essential in all these arrangements that resistors having a high precision be employed in order that the accuracy of the meter be maintained. Figure 7 shows some of the different types of precision units which have been used in such applications.

## New Tubes Reduce Distortion and Cross-Talk

(Continued from page 43)

that with a given extra signal voltage the cross-talk for the 551 will be only 1/500th that of the 24 type.

Figures 5 and 4 bring out the important fact that for reduction of cross-talk, attention must be paid to the tube parameters at large transconductance (low negative bias) whereas in the case of distortion, the control diagrams Figures 2 and 3 show that their proper adjustment at lower values of  $S_m$  is of more importance.

Briefly the 551 tube not only renders unnecessary the use of double pre-selectors for reduction of image response but in most circumstances is considerably more efficacious in reducing cross-talk. Over a large range of signal voltages the cross-talk of the 551 is of the order of 1/100th to 1/500th that of the ordinary 224 tube. In order to obtain this same improvement with 224 tubes by means of a preselector comprising a chain of resonant circuits of normal selectivity with an extra signal 20 kc. from the desired signal, at least three tuned circuits would be required.

Figure 6 shows the grid-plate transfer characteristic of an ordinary tetrode of the 24 variety. To raise the input voltage at which distortion appears the design could be changed so as to decrease the mu-factor of the tube, thus spreading out the range of grid voltages and obtaining a characteristic of the type shown at A. This however, entails a sacrifice in transconductance and amplification at the initial bias if the plate current at this point is adjusted to the same value. If the transconductance at the initial bias is to be maintained at the same value instead, then an increase in plate current must be tolerated as shown by the characteristic B.

A way out of this difficulty is shown in Figure 7. The amplifier stage in 7-a comprises two tubes in parallel. Of these tubes (A) is of the high-mu type and B is of the low-mu type. The high-mu tube A yields high amplification but can

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

handle only small input voltages; the low-mu tube B yields low amplification but can handle high input voltages. In combination the two tubes complement each other to produce a characteristic of the desired type, 7-b, solid line.

**How It's Done**

For reasons of economy it is desired to incorporate this principle in a single tube structure. One way of accomplishing this is where the control grid is divided into two sections which are mounted with a gap between them. At low negative biases the entire cathode is operative and the tube has about the same characteristics it would have if the gap were not present; as the grid bias increases negatively the electron current through the upper and lower parts of the control grid are cut off, leaving a low-mu control through the gap. At these bias voltages the tube acts as if the upper and lower sections of the control grid were formed of solid metal and controlled the current through the gap in the ordinary manner. Gaps may also be placed at the ends of the cathode instead of in the middle.

**Design Data on H.F.L. "Little Giant"**

*(Continued from page 39)*

curve shown approximates the ideal toward which all speakers strive, and, when supplied from an adequate audio channel, provides a marked increase in fidelity.

The accompanying photograph indicates the constructional features of the whole receiver, and its one piece construction, including the speaker. The space at the right side of the tuning dial accommodates the remote control mechanism—not shown in photograph—which, in two distinct types, permits selection of 6 stations or complete remote tuning of any station which could be tuned by hand at the set dial.

Complete performance curves of the entire receiver, and its wiring diagram, will be shown in forthcoming issues, together with other notes and data on components which may be of interest.

*(To preserve uniformity, the curves, etc., accompanying this article have been drawn on our standard paper.—Editor.)*

**Lincoln DC-8 Designed For Use With New Breather Battery**


*(Continued from page 41)*

thanks to the development of the 2 volt low drain tubes which are now available, and the National Carbon Co. "breather" A battery. To those living in d.c. districts, 25 cycle districts, and the outlying districts where no power lines are available, the Lincoln DC-8 will be a great boon. The highly engineered features in this equipment should make possible extreme selectivity, coupled with high amplification and sensitivity. The "A" supply gives consistent service for one year without charging or inconvenience, being vitalized by oxygen taken from the air, and the low 16 mill ampere drain on the "B" supply makes possible the use of dry "B" batteries.

Another very desirable feature of the Lincoln DC-8 design is the elimination of interference coming over the a.c. line; being absolutely independent from this source.

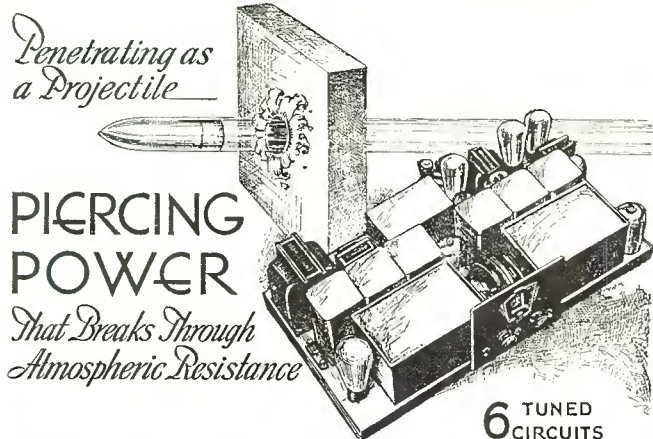**General Design**

The design of the Lincoln DC-8 incorporates every known development of Lincoln equipment. Assembled on a cadmium steel base 8 1/2 x 15 inches, it is small enough to be mounted in an automobile if desired. There are four Lincoln high gain intermediate transformers of the tunable type. The tubes required are four of the 32 type 2 volt screen grids; three 30 type and one 31 amplifier. Mounted in the rear are spaced wound antenna and oscillator coils of the plug-in variety, convenient for the experimenter to use any high frequency



**GETS YOUR STATION**

**S**ENSITIVITY and selectivity—twin essentials of any well designed radio—have always been overwhelmingly evident in "HiQ" Custom-Built Receivers.

While producers of factory-built radios are now spending fortunes to tell the public about "four or five-tuned circuits," "HiQ" owners have enjoyed SIX tuned circuits for the past two years.

This is just another example of how FAR AHEAD OF THE FIELD custom-designing always is.


If you really appreciate fine radio—radio with ability to do all you demand of it, and to do it so much better than you thought was possible—just tune in with the new Hammarlund "HiQ-31."

It has the power and selectivity of an accurately aimed projectile—the sensitivity that breaks through atmospheric obstacles and gets your station—tone that beggars description—and beauty of finish that would delight a Swiss watch maker.

A.C. and D.C. models, complete ready to install (less tubes) \$146.00 upward—or factory-wired units easily assembled by you or your custom-radio builder.

Mail coupon for the 48-page "HiQ-31" Manual, giving all details.

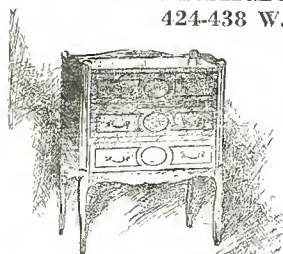**HAMMARLUND-ROBERTS, INC.**  
424-438 W. 33rd Street, New York



**THE CHALET**

One of ten specially selected consoles and phonograph combinations with acoustical characteristics matching the superb "HiQ-31" Amplifier

Custom-Built Radio  
by **HAMMARLUND**

HAMMARLUND-ROBERTS, Inc.  
Dept. CB-1, 424-438 W. 33rd St., New York, N.Y.  
Enclosed 25c (stamps or coin) for "HiQ-31" Manual.  
Name \_\_\_\_\_  
Address \_\_\_\_\_

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

The  
revolutionary  
**I.C.A.**  
Conqueror  
Short Wave Set  
gets them all!



Here is the short-wave set that stands head and shoulders above anything at its low price and is the equal of any short-wave set at any price.

The I. C. A. Conqueror is of unique and superior design, the work of I. C. A. engineers in collaboration with a foremost ship-to-shore short-wave expert. The coils are a masterpiece of scientific design and precision manufacture.


But the performance of the I. C. A. Conqueror is the thing that counts. How far will it reach? Half way round the world—no set can go farther. How about selectivity? Simple tuning gives absolute hair-line separation. Ease of operation? The most inexperienced tuner gets foreign stations at the first try.

The I. C. A. Conqueror uses a 224 screen grid in the R. F., one 227 (A. C. model) detector and two 227's and one 245 in the special transformer-resistance-transformer type audio. The Conqueror is also to be had in Battery Model. For broadcast-band reception, special coils are supplied.

Dealers, professional set builders and service-men can make real money assembling and selling the I. C. A. Conqueror. Easy to make part- or full-time profits. Order from jobber or mail order house. If they can't supply, send direct. List price of set \$65 (either A. C. or Battery Model)—Net \$39. A. C. Power Pack list price \$34.50—Net \$19.75. Send for catalog and full information free on request.

INSULINE CORP. of America, 78-80 Cortlandt St., New York  
Send for 1931 Catalog of Radio and Television Apparatus

THE NEW "EXPLORER"  
SHORT WAVE

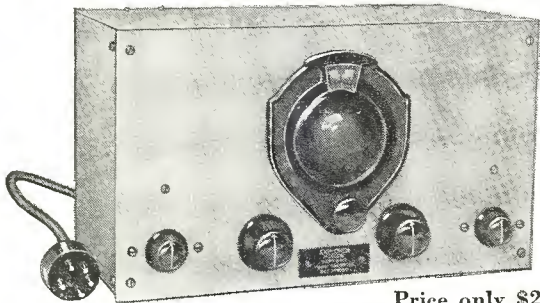

Price only \$24.50

**PLUGLESS POWER CONVERTER**  
A sensational advance in short wave reception

**AUTOMATIC BAND SELECTION.** No plug-in coils! Wave-length range 15 to 160 meters; automatic band selector changes wave-length bands by the turn of a knob. **POWER RECEPTION.** The EXPLORER itself uses two tubes, greatly amplifying distant signals. Used with your broadcast receiver, it makes possible reception of stations all over the world with real loud-speaker volume. The EXPLORER, designed on entirely new principles, is the last word

in short-wave radio construction. Full size; thoroughly shielded; subpanel construction; removable chassis is enclosed in beautiful satin-finish aluminum cabinet; large vernier dial; extra vernier tuning condenser with effective ratio of 200 to 1 gives ease of tuning even with weakest stations. Results obtained are unsurpassed by regular short wave receivers; and elimination of plug-in coils makes the EXPLORER the most convenient of all short wave receiving apparatus.

Price only \$24.50. Fully guaranteed. Models for every receiver, including all superheterodynes. Order now! Sent C.O.D. on receipt of \$2 or prepaid on receipt of price in full. State make and model of receiver, and whether A.C. or D.C. Foreign, price \$25.50, remit in full with order.

Send for Free Literature

**RIM RADIO MFG. COMPANY**

693 Grand Street

Brooklyn, N. Y., U. S. A.

short-wave coils he desires to experiment with. Controls on the front panel are simple to operate, the volume control being of the screen grid voltage regulation type and is of wire wound construction. The phone tip jacks are conveniently located in rear of chassis together with antenna and ground binding posts.

**80 Meter Band**

Working on entirely new principles, the Lincoln DC-8, by simply throwing a switch, will tune the interesting 80 meter amateur phone band, covering 60 degrees on the dial as easily as broadcast, utilizing only the standard broadcast parts throughout. Due to the pure d.c. current utilized, the amateur phone band comes in clear as there is no 60 cycle modulation.

The compact size of chassis allows assembly in small con- The antenna requirements are only from 15 to 20 feet long sole with heavy motor type speaker and battery equipment. and can be easily located in any living-room.

**Speaker and Theater Sound Reproduction**

(Continued from page 76)

marked increase of efficiency. A comparison of a horn type speaker with a single cone is thus not representative of the relative characteristics of standard apparatus.

The radiation resistance characteristic shown for a horn type loudspeaker with a 50 cycle cut-off is not typical of the horns employed in practice. The construction of a horn with so low a cut-off is very expensive and the size of the horn would probably be such as to make it large for the average theater. Aside from these considerations, the smooth cut-off shown is attainable only with an infinitely long horn, that is, attainable only with the unattainable. The frequency characteristic of a finite horn always exhibits horn resonances such as those which appear on the actual horn characteristic given in Fig. 5. In addition, as has been shown above, considerations of efficiency favor the horn type of loudspeaker only to a slight extent.

**Conclusions**

The above results can now be summarized as follows: In power handling capacity the two speakers are about the same. In efficiency the horn type speaker is somewhat superior. The directional characteristics of both types are satisfactory. As regards frequency response characteristics, the directional baffle type speaker is markedly superior to the horn type in the reproduction of both speech and music. On the basis of these factors it appears quite conclusively that for theater reproduction, of the commercial devices in use at the present time, the directional baffle type loudspeaker yields more satisfactory results.

**W9XF Short Wave Transmitter**

(Continued from page 40)

that WENR, operating on 870 kilocycles, could be heard on 800 and on 940 kilocycles. As this could not be attributed to any harmonic of the 870 kilocycle frequency, the cause was somewhat of a mystery. Upon investigation, we found that this condition existed only when the 870 kilocycle and 6,020 kilocycle transmitters were in operation simultaneously. Furthermore, that unless both stations were transmitting the same program, no intelligible modulation could be detected.

Manifestly, this phenomenon was caused by a combination of the two frequencies. The sixth harmonic of 870 kilocycles is 5,220 kilocycles. The combination of this frequency with the 6,020 kilocycle frequency, produced a beat frequency of 800 kilocycles. This 800 kilocycle radiation was picked up by the grid leads of the main power amplifier on the fifty kilowatt set and broadcast, but of course, very little power was radiated at this frequency.


The eighth harmonic of 870 kilocycles, is 6,960 kilocycles.

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

Here's the Oscillator You Have Been Waiting For

The Jewell Portable Test Oscillator

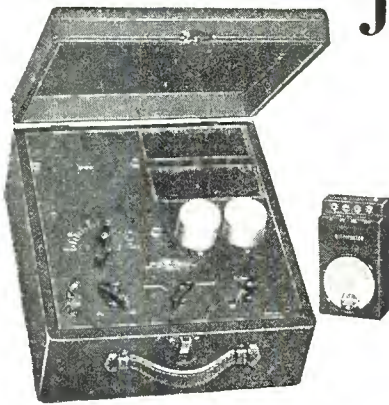A Necessary Instrument for Adjusting All Receivers



Radio frequency circuits, whether in a tuned radio frequency or super-heterodyne receiver, must be accurately adjusted to obtain the greatest sensitivity and selectivity. To make these adjustments accurately and quickly, a test oscillator of special design is required. No makeshift, cheaply built oscillator can be used for checking modern high gain receivers.

The Jewell Pattern 560 Portable Test Oscillator is designed and built to meet the needs of radio servicemen. Simplicity of operation, hair-line accuracy, and assured reliability are the cardinal features of this portable test oscillator. Each feature has been achieved by incorporating constructional details which actual service tests have proved absolutely necessary.

Features of the Jewell Portable Test Oscillator

SELF-CONTAINED BATTERIES

The Jewell Test Oscillator is convenient to use because it operates from self-contained batteries. Services both A.C. and D.C. sets. Accurate adjustments cannot be made with A.C. operated oscillators that feed energy back to the receiver through light lines.

LEAK-PROOF INTERLOCK SHIELDING

Every part of the Jewell Test Oscillator is enclosed by a combination aluminum and copper interlocking shield. An oscillator with less shielding is worthless.

BROADCAST AND INTERMEDIATE BANDS

The Jewell Pattern 560 Portable Test Oscillator covers the broadcast band from 550 to 1500 K.C. and the intermediate frequency band from 125 to 185 K.C. Jewell Test Oscillator is adequate for testing every super-heterodyne receiver built today, and provides for future design in that it covers the entire band from 125 to 185 K.C.

NEW '30 TYPE TUBES

Two tubes are used; one a radio frequency oscillator and a second to generate audio frequency notes. Shielded tube compartments are of ample size for the '30 type tubes with present small glass envelope or with the new larger standard size envelope.

OUTPUT METER

The Jewell Test Oscillator may be had with or without Jewell Pattern 559 Portable Output Meter. The meter is carried in a pocket provided in the oscillator case. In use, it is placed near the output circuit of the receiver eliminating long leads and preventing any possible coupling to the oscillator.

EASY TO OPERATE

You do not have to study the instruction book to use the Jewell Test Oscillator. A wiring diagram and set of calibration charts are carried in the oscillator cover where they can never be mislaid.

- Pattern 560 Test Oscillator, complete with tubes, batteries and output meter. List Price ..... \$97.00 Dealers' Price ..... 72.75
- Pattern 560 Test Oscillator without output meter. List Price ..... 82.00 Dealers' Price ..... 61.50
- Pattern 559 Output Meter only: List Price ..... \$15.00 Dealers' Price ..... 11.25

Send for Bulletin

describing the Pattern 560 Portable Test Oscillator.



Jewell Electrical Instrument Co.  
1642-G Walnut Street, Chicago, Ill.

30 YEARS MAKING GOOD INSTRUMENTS



Grids Were Shielded

The combination of this frequency with 6,020, results in 940 kilocycles. This frequency we found to be causing trouble on the grid circuits of the intermediate power amplifier of the fifty kilowatt set. The power radiated on this frequency seemed to be much lower than the 800 kilocycle radiation and caused less trouble than the other, due to the fact that 940 kilocycles is a regional channel.

The obvious remedy for the trouble was to shield the grid circuits, or trap out the stray frequencies. Neither of these methods was easy to accomplish with such a high powered transmitter. The shielding method was finally adopted and proved to be perfectly satisfactory.

It is probable that this trouble would not have been detected were it not for the fact that both stations were transmitting the same program. Undoubtedly, there would have been a heterodyne caused on both the 800 and 940 kilocycle channels but the source of the interfering carrier would not have been known. It is possible that some of the stray heterodynes heard in the broadcast band originate from similar causes. The interfering transmitters need not be located in the same building, as we found that the 6,020 kilocycle power was delivered from the antenna 600 feet away. With the antenna disconnected, the transmitter and transmission line could be operated without interfering with the 870 kilocycle transmitter. The building which houses both transmitters has a double copper screen enclosing all four sides, ceiling and floor of the transmitter room. Therefore, it is possible that a short wave transmitter located some distance away from a broadcast station, may be causing interference within the broadcast band.


Silver 714 A.C. Superheterodyne

(Continued from page 44)

Band Widths

Times field strength	Kilocycles wide		
	600 kc.	1000 kc.	1400 kc.
10 .....	7.0	7.0	7.0
100 .....	10.0	11.2	11.2
1000 .....	14.5	17.5	17.5

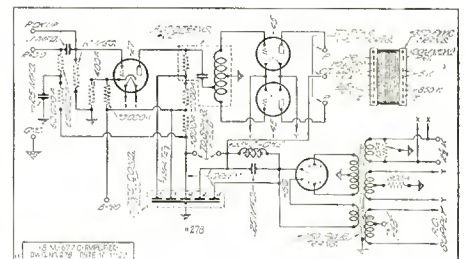It will be noticed that the fidelity curves (electrical fidelity) are shown in solid lines covering a portion of the range, the solid lines indicating measured values, while the dotted lines indicate projected values.




The power supply schematic is shown in the drawing. The first audio, the two 245 tubes in push-pull and the 280 rectifier are placed in the power supply unit which is connected to the 714 tuner by means of a cable.

Field Strength Effect on Receivers

(Continued from page 37)

ceiver. This is due to the fact that not only is the received signal from the local station reduced, but it is made necessary at the same time to operate the receiver with the volume control turned near maximum. This is an advantage because

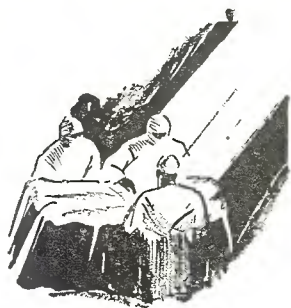when  
Death  
gambles  
with  
control . . . . .



The white robed surgeon never dares to lose control. Slovenly technique may spell death. Every phase of the building of a CENTRALAB resistance must be under control for smooth noiseless performance.

. . . and twenty million CENTRALAB controls have already been sold.

**Dealers and Servicemen**

SEND 25c for new VOLUME CONTROL GUIDE showing how to service most old and new sets with a handful of CENTRALAB controls.

**Centralab**

**CENTRAL RADIO LABORATORIES**


Dept. 726-J, 26 Keefe Ave.

Milwaukee, Wis.

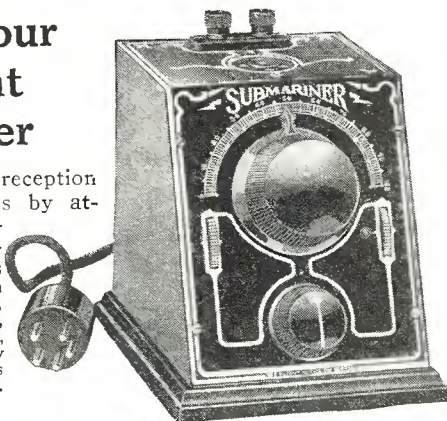**SHORT WAVE**

With Your  
Present  
Receiver

EXPERIENCE reception on short waves by attaching a "Submariner" to your present receiver. Users of "Submariners" in U. S. hear England, Holland, Germany, South America, Mexico, Australia and many other distant countries broadcasting music, etc.



**THE SUBMARINER**

Is the pioneer short wave adapter which has been sold in every country in the world since 1926. Since that time, it has been improved greatly and has always been far ahead of any other adapter. It is a quality product, and equal in performance to any short wave receiver. Remember we do not make only one adapter and

say it will operate on every set, but we have many different models which are designed for each make of set. For instance our model JATY, 19-50 meters, at \$22.50, or our JIATY, interchangeable coil, 13-145 meters, at \$27.50, will give extraordinary results, equal to any short wave Super-Heterodyne receiver, when attached to the

**New Screen Grid Super-Heterodyne Receivers**

Of course, we have a model designed for your receiver and the price range is \$17.50 to \$27.50.

**ORDER TO-DAY.** Will be sent postpaid upon receipt of price or C.O.D. if \$1.00 accompanies order. Foreign—Cash with order.

**J-M-P MANUFACTURING CO., INC.**

3437 Fond du Lac Ave.

Milwaukee, Wis., U. S. A.

on most sets the volume control operates by increasing the grid bias on the rf. amplifier tubes for low volume. Under this condition of high bias on rf. amplifier tubes they are approaching a condition where their detection efficiency is high and since this efficiency increases as the volume control is turned towards the low side it can be seen that the higher the volume control can be turned to give the desired signal strength, the less the local station will interfere with the reception of weaker stations.

**General Motors Midget Out**


USING four 224 screen grids, a 245 and a 280 rectifier, the "Little General" has just been put on the market by General Motors Radio at Dayton, Ohio. Three r.f.

stages and a power detector comprise the screen grid employment.

Addition of this model brings the total number of General Motors sets up to nine. The "Little General" has a tone selector, four tuned circuits, and a dual volume control. All screen

grid tubes are shielded as are gang condenser sections.

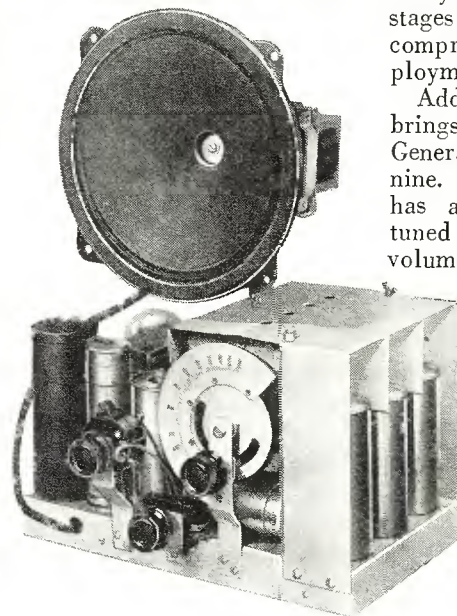A photograph of the chassis is shown here. Response curves will probably appear in a later edition of this magazine. Speaker used is of the dynamic type.




**Filmophone Radio Announced**

AND now comes the last word in home entertainment, consisting of home talkies, home movies, the radio and the phonograph in one combination instrument, according to a release by the Bell and Howell Co., Chicago, covering their recently announced Filmophone.

A Bell and Howell Filmo movie projector, utilizing the regular 16 mm. home movie size film, is used for the pictures and a Howard chassis is the basis for the radio feature.

A phonograph motor is so arranged that the turntable can be operated at either the standard speed for ordinary phonograph records, or at 33 1/3 revolutions per minute when the records for the sound pictures are played.

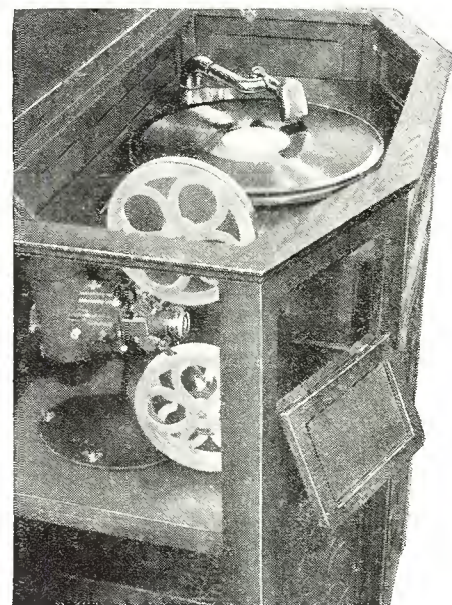The flexibility of the new combination is such that talkies and also



(Continued on page 87)



# Now You Can Have Seventy Stations in Twenty Minutes!

## S-M 714 Superheterodyne Tuner

The 714 Superheterodyne Tuner is the finest piece of radio equipment it is possible to produce today—just as the famous Sargent-Rayment 710 was the “boss of the air” in its day. A stock model in the Silver-Marshall Main Laboratory at Chicago brought in clearly and distinctly, and at room volume, *ninety-three* stations, one after the other, including Cuba, Mexico City, and every station on the west coast that was on the air! Over a period of a month you should be able to log every station in the call book that is within reason.

The 714's excellence isn't an accident—it is the result of two years of painstaking development in the great S-M Laboratories under McMurdo Silver's personal supervision. It contains eleven tuned circuits (over twice as many as the most expensive t. f. sets): two, in a dual-selector, precede the first '24 r. f. tube, two are between the r. f. and '24 first detector, and one is in the '27 oscillator circuit. It uses a factory-aligned and tested 443 screen-grid i. f. amplifier, having in itself six tuned circuits. Imagine, if you can, adding six more tuned circuits to the 710 or 712—and all six tuned to a single frequency!

Tubes required: 4—'24's, 2—'27's.



Price (tuner only), completely factory-wired, tested and RCA licensed, less tubes.....\$87.50 List

Component parts total.....\$76.50 List

The 714 Superheterodyne Tuner can be used with any standard audio amplifier but operates at its maximum with the S-M 677B. It is a combination two-stage amplifier and power supply. It furnishes the necessary heater and plate supply for the 714 and takes its power from any 105-120 volt, 50-60 cycle source. Tubes required: 1—'27, 2—'45's, 1—'80.

Price, completely factory-wired, tested and licensed, less tubes.....\$82.50 List

Component parts total.....\$68.50 List

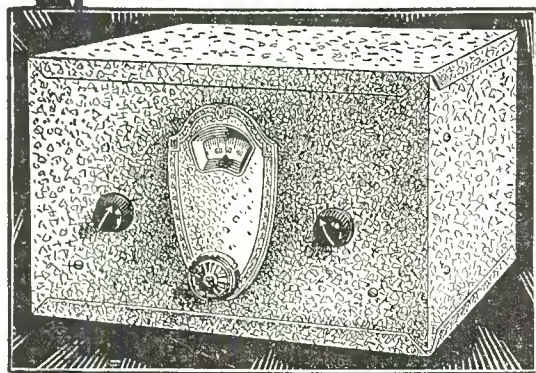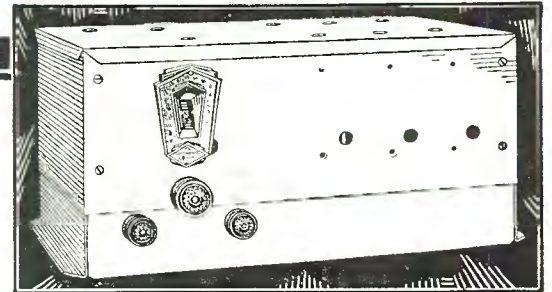

## Foreign Programs in Your Home

The S-M 738 Converter turns any broadcast receiver into a short-wave superheterodyne with a range of from two to ten thousand miles, for to every bit of the sensitivity and selectivity of your broadcast set, is added the power of *three more tubes!*

There is nothing that the most expensive commercial short-wave receiver will do, in the way of distance, that the 738 will not duplicate and beat—and at one-third the cost. Under favorable weather and local receiving conditions, it will bring in every American short-wave broadcaster and the principal foreign stations.

It is built in a beautiful black crystalline case with a hammered silver dial—entirely at home in the finest living-room.

The wired model can be hooked up in three minutes—you merely remove the antenna lead from the broadcast receiver and connect it to the antenna post of the converter; then run two leads from the 738 to the antenna and ground posts of the broadcast set—and tune it in. A switch can be easily arranged to throw the set from long to short waves at will.

It tunes by a single dial (which tunes the oscillator circuit) and an auxiliary midget condenser. It will give, in addition to short-wave broadcasting, phone and i.c.w. where there is any carrier modulation at all. Included in the list price are eight coils (four pairs) which cover the wave length range of from 18 to 206 meters.

Tubes required: 1—'24, 1—'26, 1—'27.

Price, completely factory-wired, tested and RCA licensed, less only tubes.....\$69.50 List

Component parts total.....\$59.50 List

## Get Your Free Copy of the S-M General Parts Catalog

Check the coupon for your copy of the SILVER-MARSHALL 1931 GENERAL PARTS CATALOG. The Radiobuilder, Silver-Marshall's official publication, tells the latest news of the great S-M laboratories. Fill in the coupon for a sample copy.

**SILVER-MARSHALL, Inc.**  
6413 West 65th Street • Chicago, U. S. A.

Silver-Marshall, Inc., 6413 W. 65th St., Chicago, U. S. A.  
 .....Send me, free, your NEW 1931 CATALOG with sample copy of the RADIOBUILDER. Also Data Sheets as follows: (Enclose 2c for each Data Sheet desired.)  
 .....No. 25. 714 Screen-Grid Superhet Tuner.  
 .....No. 23. 738 Short-Wave Superhet Converter.  
 Name.....  
 Address.....


# NEW PRODUCTS FOR THE TRADE

## New Weston Circuit Tester

At the right is to be seen the model 563 d.c. circuit tester, just announced by the Weston Electrical Instrument Corp., of Newark, N. J.

This model is for checking resistance values and continuity of circuit during the process of manufacture, and for service and installation work on many types of electrical apparatus.

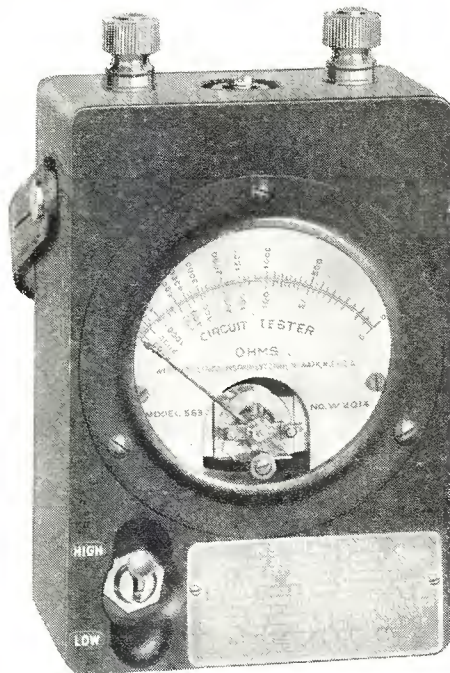Accurate within 2 per cent, the 563 is compact, self-contained and portable. It uses a Weston 301, 3¼-inch diameter meter with two resistance ranges, 5,000 and 50,000 ohms, a 1.5-volt flashlight cell, a leather strap carrying handle, and a pair of 30-inch leads with test prods.



## Kellogg Hand Microphone

Among the several new products designed for broadcasting, home recording, experimenting and amateur work, recently announced by the Kellogg Switchboard and Supply Co. of Chicago, is the No. 29 hand microphone illustrated at the right. It is only 6½ inches in length, and weighs about 10 ounces. Despite its small size, it is sturdily constructed and reproduces throughout the musical scale with fidelity.

Engineers of the company have also designed a modulation transformer to be used with the hand microphone, the transformer having input for either single or double button microphones, the output of the transformer being matched to the input impedance of standard amplifying tubes on the market.


The microphone may be used in standard broadcasting, public address systems, amateur work, or in home recording wherever a reliable, sensitive and inexpensive "mike" is required.


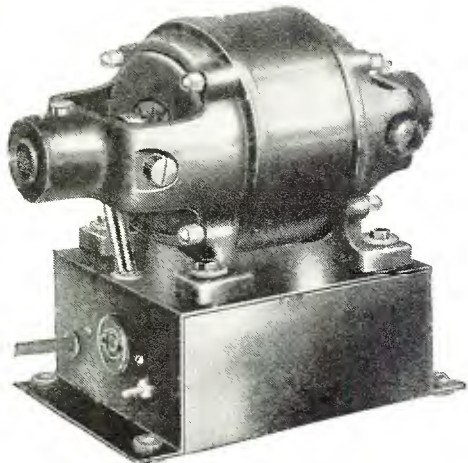
## Janette Rotary Converter

The Janette Manufacturing Co., of Chicago, announces their new type CA-20-F rotary converter shown in the photograph at the left.


This unit has a capacity of 110 watts, sufficient for the majority of a.c. sets now on the market. It is a quiet, dynamically balanced unit which will operate an a.c. set without ripple or hum. It is available for 32, 115 or 230 volts d.c. The unit is complete with filter, cord, plug and d.c. receptacle.


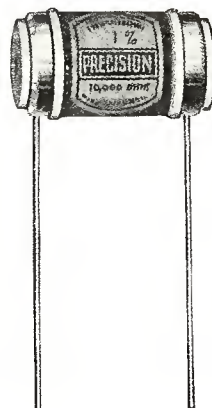
## International Wire Wound Resistor

Shown at the left is an illustration of the precision wire wound resistor recently placed on the market by the International Resistance Co., of Philadelphia, Pa. The moulded end contacts are to prevent open contacts, a trouble formerly occurring in the spot soldered or spot welded joints.

The pigtail connections make for ease in assembly. These resistors have numerous other unique features that are explained in the new catalogue recently published, which will be sent on request by writing the service department of the company at 2006 Chestnut St., in Philadelphia.





(Continued from page 84)

movies without sound can be projected. The pictures may also be shown with radio or phonograph musical accompaniments not synchronized with the film. Of course the radio or phonograph are available each by itself if desired.

A large number of home talkies subjects can now be secured from photographic dealers. Among these are the always amusing "Felix, the Cat" cartoons, as well as numerous other entertaining and instructional features.

### Chromatrope Uses Two Speakers

**I**LLUSTRATED in this article is the Chromatrope recently announced by the Oxford Radio Corporation of Chicago, which makes use of two speakers, both dynamics. In the photograph the upper speaker is most efficient on the higher frequencies while the lower speaker is most effective in the rendition of the lower frequencies. The designers place the two speakers, one above another, in a console eighteen inches in depth to provide a longer air column, enabling the low note speaker to reach low fundamentals which might otherwise be difficult.

Included in the receiver is a tone balancer consisting of an




audio choke, two condensers and a variable resistor. The variation of the resistance raises or lowers the amplitude of the low frequency response, but does not affect the high frequencies, the response from the speaker being very pleasing.

In the photograph it will be seen the tuner portion of the set is on the top shelf, and the amplifier and power supply located on the bottom shelf. The receiver is a licensed tuner, using three 224 screen grids, two 227's, two 245's and two 280's making a total of nine tubes. A local-distance switch is used, as well as a volume control.

### G-M Photoelectric Relay

**T**HE G-M Laboratories, Inc., Chicago, have recently completed the development of a compact photoelectric relay and light source for application to many industrial and commercial operations. It is known as type G-M No. 1281 (Continued on page 88)

GET  
the  
new

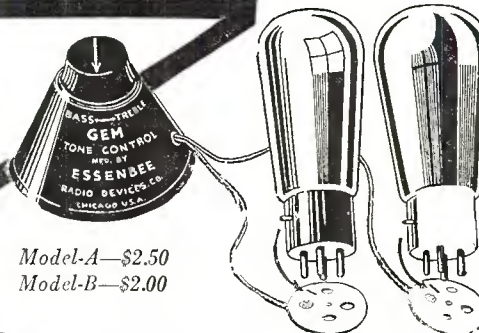

Model-A—\$2.50  
Model-B—\$2.00

GEM ■ TONE CONTROL

PLACE ADAPTERS  
UNDER POWER TUBES

#### Superior to All—Least in Price

By attaching a Gem Tone Control to any A. C. Radio Receiving Set you can get just the right tone you may desire—brilliant, bright, mellow, or deep. It brings your radio right up-to-date at little expense. MODEL A is a portable device encased in a beautiful walnut bakelite case and may be placed anywhere on or away from the radio. MODEL B is made for panel mounting and can be installed in the radio cabinet itself, for it has a shaft long enough to take a 3/8" panel. It has an arrow walnut knob to match the cabinet. If your dealer cannot furnish you with a Gem Tone Control, fill in the coupon below and we will be glad to forward the desired model to you.

#### ESSENBEE RADIO DEVICES CO.

732 Mather Street, Chicago, Illinois.

Enclosed find my payment of \$\_\_\_\_\_ for Model \_\_\_\_\_ Gem Tone Control.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

## The Latest Data on the Construction and Repair of Radio Receivers


### Radio Construction Library

3 Volumes, 6x9, 993 Pages, 561 Illustrations

**W**RITTEN by two widely known radio engineers these three books cover every phase of building, repairing and "trouble-shooting" on modern receiving sets. This practical Library includes: **PRACTICAL RADIO**—The fundamental principles of radio, presented in an understandable manner. Illustrated with working diagrams. **PRACTICAL RADIO CONSTRUCTION AND REPAIR**—Methods of locating trouble and reception faults and making workmanlike repairs. **RADIO RECEIVING TUBES**—Principles underlying the operation of all vacuum tubes and their use in reception, remote control and precision measurements.
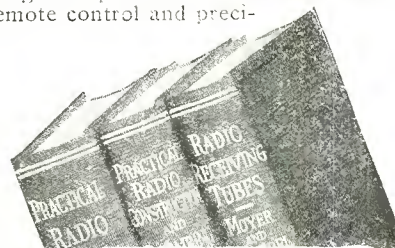
#### 10 Days FREE Examination

Examining these books free for ten days. You will find them invaluable as a home study course and as a reference in the daily radio problems which you meet in your work. Simply fill in the coupon and the books will be sent to you postage prepaid; there is nothing to pay if they do not prove satisfactory.




### FREE EXAMINATION COUPON

McGraw-Hill Book Company, Inc. 370 Seventh Avenue, New York  
Send me the new RADIO CONSTRUCTION LIBRARY, three volumes, for 10 days' free examination. If satisfactory I will send \$1.50 in ten days, and \$2.00 a month until \$7.50 has been paid. If not wanted I will return the books.

Name.....  
Home Address.....  
City and State.....  
Position.....  
Name of Company.....RCB-1-31

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

(Continued from page 87)

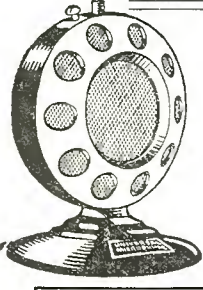

## BROADCAST

### Your Own Voice Over Your Radio

Possibilities for home entertainment practically unlimited! Everyone thinks of a new and novel use for BABY MIKE. Your hearers get same thrill as if they listened to you direct from a radio station. Worth many times its price in entertainment!

Send for Our **NEWEST CATALOG.** Largest Assortment and Biggest Bargains in **RADIO SETS and PARTS.** All Merchandise at Wholesale

Price Only **\$750**


**S. HAMMER RADIO CO.** 142 Liberty Street, New York  
Tel. Hitchcock 1152—Dept. C

and is essentially an electric switch controlled by means of a beam of light. Any interruption of this light beam operates the switch which can control any electrical devices desired.

The application of this unit is meeting with wide acceptance for counting parts on conveyors, inspecting work on presses, operating safety devices, timing of operations. In operation the light from the upper lens is reflected from the remotely placed mirror to the lower lens, where it is received by the photo-electric cell. Any interruption of this beam of light by any object causes the relay contacts to close, thereby operating a counter, power switch, signal or other device. The Visitron protoelectric cell single stage amplifier, light source and other essential parts are completely enclosed in a drawn steel case. Installation of the unit is quite simple since it is only necessary to connect the unit to a 110 volts 60 cycle line.
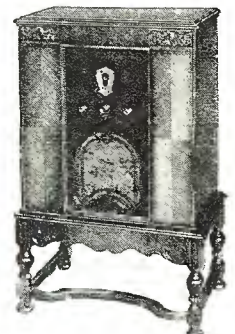
### Commonwealth Announces Models

THE Commonwealth Radio Mfg. Co., of Chicago, announces an attractive line of superheterodynes, consisting of three models, model 91 a low boy, model 92 a high boy, and model 93 a phonograph combination. The chassis is compact in design, the power pack being integral with the tuner. Tubes used are four 224, two 227, two 245 and one 280. Output of the receiver is handled by the new Trimm, Jr., stadium speaker. Tone control is also included. The cabinets are designed along the latest vogue, stressing a simple beauty that pleases all.



This same concern announces a new line of 6 tube receivers bordering on

the midget class but with a little more advanced design. Unusual sensitivity and selectivity are the two features of this chassis. The tubes are four 224, one 245 and one 280. New type "Litz" bank-wound coils are employed. The Utah midget dynamic speaker is perfectly matched to this chassis and renders good tone. The line consists of model 13 mantle cabinet, model 14 Taboret console, model 51 low boy console and model

53 phonograph combination. Model 13 and 14 are shown in the illustrations.



### Polymet In Sound Field

THE entry of this important firm into the sound equipment field has been expected for some time. Widely known throughout the electrical and radio industries, Polymet products are now destined to become important factors in the newer field of sound.

The actual entry of this company has been preceded by many months of exhaustive research. Polymet is well equipped to manufacture such parts. Plants of the company, each under the exclusive direction of a specialized engineer insuring strict adherence to standards, fabricate all the elements entering into the construction of these items. The Polymet plant at Winsted, Conn., makes the copper, enameled and insulated wire. The Easton, Pa., plant fabricates the coils, solenoids, chokes and transformers. The main plant, in New

(Continued on page 89)

# SAVE UP TO 80% on Radio TUBES

A set of our Super Tubes will make your set work like new. Every tube tested and fully guaranteed for six months in any receiver.

GUARANTEED 6 MONTHS


List Price	Our Price	List Price	Our Price	List Price	Our Price
201A..... \$1.25	\$0.59	112..... \$2.25	\$0.99	281..... \$7.25	\$1.95
226..... 1.75	.69	280..... 1.90	.99	250..... 11.00	1.95
171A..... 2.25	.69	199UX.. 2.50	.99	210..... 9.00	1.95
227..... 2.20	.69	199UV.. 2.75	.99	401..... 4.50	1.95
200A..... 3.50	.75	120..... 2.50	1.59	"B" Eliminator tube, 125 mil. 4.50	2.45
245..... 2.00	.85	484..... 3.25	1.59		
224..... 3.30	.99	182..... 3.50	1.69		

Get a whole new set of guaranteed, first quality tubes. WE PAY POSTAGE. Don't wait. Send today. RONWYN RADIO CORP., 1413 S. Michigan Ave., Dept. 51, Chicago, Ill.

# RESISTORS

## ... GET THIS GUIDE TODAY

If you have not received one of our new Resistor Replacement Guides, be sure to send in for it now. Service men and amateur operators agree it is the most helpful radio book ever offered. This handy little Guide shows clearly and concisely not only how to locate cause of trouble in radio sets, but it also shows the proper types and values of resistors to use in the various types of radio receivers. List—50c each



**International Resistance Co.**  
2006 Chestnut Street, Philadelphia, Pa.

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

(Continued from page 83)

York, is entirely devoted to the manufacture of condensers and resistors.

Besides parts manufacture, Polymet also assembles complete amplifiers suitable for sound work of every sort. It is the contention of Polymet engineers that the expense of breakdowns and repair work can largely be avoided by incorporating related transformers, condensers, resistances, etc., in products, rather than attempting to get good results from "stranger" products.

### Mayo Replacement Parts


**T**HE Mayo Laboratories, pioneers in replacement parts manufacturing, located at 280 East 137th Street, New York City, have allied with a complete service engineering department which at present is handling service for most of the distributors and large radio sales organizations in the United States.

This department conducts a free information bureau to service men in regards to servicing radio sets, public address equipment and electrical and radio measuring equipment, and has prepared a new and complete catalogue (No. 18) which contains a complete list of condenser blocks, transformers and resistors for the standard sets.

Mayo Laboratories, who have recently added to their extensive equipment additional coil winding machinery, resistance winders and condenser equipment for both paper and electrolytic condensers, can take care of either production runs on any article or the necessary one at a time that some service men need.
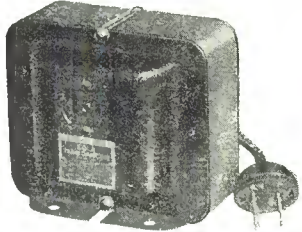
### Sola Voltage Compensator

**R**ECENTLY designed by the Sola Corporation of Chicago, to reduce high line voltages and increase low line voltages, the Sola voltage compensator is illustrated in the accompanying photograph.



Characteristics of the compensator are: capacity 100 watts, input 95 to 135 volts (60 cycle only), output .9 amperes at 110 volts; weight 7¼ lbs., height 3¼ inches, width 4 inches, depth 3½ inches. The standard compensator will only serve sets up to and including 120 watts.

According to the designers the principle followed in securing automatic regulation lies in the ingenious design of the core. Portion "A" of the core functions as a standard step-up auto transformer when line voltage drops below a predetermined limit. This action builds up the normal voltage at this point. Arm "C" of core functions slightly under the saturation knee of the iron permeability. When line voltages rise the increase in saturation of arm "C" forces a greater portion of the flux through the higher reluctance path "B," thereby an auxiliary coil of opposite polarity counteracts the excessive voltage, delivering a corrected and steady flow of current.

### Simplimus Home Recorder

**A**NNOUNCEMENT has just been made by Simplimus, Inc., of Boston, Mass., of the Simplimus Recorder designed for making of records in the home either from radio programs, from the voice itself. Home recording blank records are also available.

(Continued on page 90)



Model 245-A

## SET and TUBE TESTER


**\$12** NET TO DEALER *At Your Jobbers . . . If*  
 \$20 LIST *Ordered direct remittance*  
*must accompany order*

**N**OW equipped with the new Readrite D.C. Meters. More than ever it remains the outstanding value in servicing testers. Covers practically 100% all field work. Simple to use. Easy to carry. Checks all voltages at sockets, also line voltage. Tests all tubes in general use. A complete tester.

Beautiful baked enamel finish. Rugged. Compact. Accurate. Complete instructions.

*Other new Readrite items include Direct Reading Ohmmeters; A.C. Connection Counter Tube Tester; Tube Short-Tester, etc.*

*Catalog of Complete Line Upon Request*

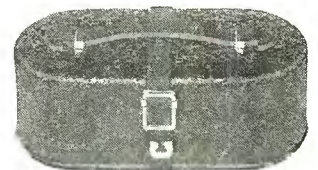



## READRITE METER WORKS

Established 1904

10 College Avenue

Bluffton, Ohio

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

Announcing

## A NEW CATALOG FOR SERVICE MEN

Build up service business by making guaranteed repairs!

The use of Polymet Quality Products makes this possible. Use the same Condensers, Resistors, Transformers, Chokes as adopted as standard by practically all leading manufacturers.

✦ ✦ ✦

The New 1931 Service Men's Parts Catalog is Ready

Ask for it on your letter-head, or send your card. A copy, together with liberal discount schedule, will be sent by return mail.

PRODUCTS

**POLYMET MANUFACTURING CORP.**  
 World's Largest Manufacturer of Radio Essentials  
 829 E. 134th Street, N. Y. City

# POLYMET


(Continued from page 89)

The equipment consists of the hand microphone, input control stage and the recorder. The input control stage can be plugged into any d.c. or a.c. receiver and the equipment is ready for recording or for playing back a record already made. All equipment comes with full instructions and diagrams.
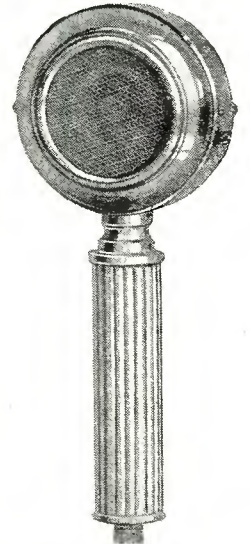
### Ellis Two Button Hand Mike

SHOWN in the illustration is the model 12-N two button hand microphone made by the Ellis Electrical Laboratory of Chicago. It has just been placed on the market and makes use of the Ellis adjustable buttons of the same type as employed in regular broadcast type units.

This hand microphone is especially recommended for home recording devices, industrial and home talking picture machines, portable public address outfits and in general wherever it is not convenient to use a regular spring mounted microphone. Each unit is carefully made and individually tested. Size 6½ inches long, head 2 7/16 inches in diameter, 1½ inches thick.



In addition to the above item Ellis also makes a line of demountable spring suspension microphones together with other necessary accessories for speech work.


### New Amperites Marketed

ACCORDING to advices from the Amperite Corporation of New York, two new Amperite models have been announced. One is the 6-30 to handle the new 2 volt tubes such as the UX 230 and UX 232 on 6 volts, and the other Amperite 6-31 to handle the 231 type tube on 6 volts.

The Amperites just mentioned are connected exactly the same as the battery type resistors, in series with one of the filament leads. The designers state that by replacing the ¼ ampere tubes with the new tubes and the Amperites here listed the storage battery will last four times as long, a point which might be of interest to the users of storage batteries.
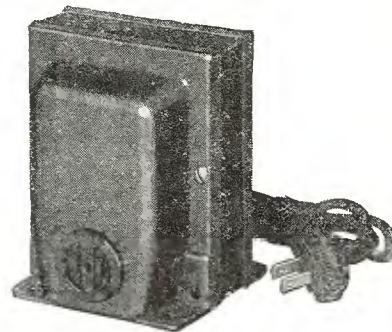
### Acme Step-Down Transformers

SHOWN in this illustration is the Midget, 50 watt Acme step-down transformer made by the Acme Electric and Manufacturing Co., of Cleveland, Ohio. This is a transformer, which with the Standard, 150, 250 and 350 watt types, find their principal application in the export field where the voltage supply ranges from 200 to 240 volts, with 50 or 60 cycles.



Acme transformers are liberally designed and the coils are especially impregnated to meet conditions in the export field.

Care is taken to give each transformer a high voltage insulation breakdown test at ten times the working voltage, as well as an induced voltage test at twice the normal working voltage.

(Continued on page 91)

### Servicemen and Dealers!

Here Is Your Chance to Make More Money

Cash in on this new device when servicing sets —one demonstration sells the wonder

### FILTERMATIC

Entirely automatic, no bothersome tuning, improves tone —reduces static, brings in distance, increases volume, prolongs life of tubes, separates stations.

FOR ALL RADIOS. POST PAID—ONLY \$1.00


Send Cash or P. O. Money Order. Satisfaction Guaranteed or Money Refunded

SERVICE MEN AND DEALERS WRITE FOR OUR ATTRACTIVE OFFER

Filtermatic Mfg. Co. (Dept.) 4458 Frankford Ave., R.C. Philadelphia, Penna.



### Build Your Own Capacity Bridge

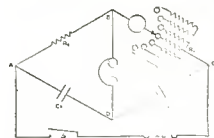

We manufacture wire-wound resistors of any value from 0.01 to 10,000,000 ohms, having negligible inductance and distributed capacity and calibrated to an accuracy of 1%. Their use is highly

recommended for Laboratory Standards, High Voltage Regulators, Telephone Equipment, Television Amplifiers, Grid and Plate Resistors, Electrical Apparatus, and Test Equipment, etc. Send today for your copy of an article reprinted from September QST telling how to build a capacity bridge. Address Dept. S.



Super Akra-Ohm wire-wound Resistors are recommended for the construction of an inexpensive capacity bridge in September QST. The following Super Akra-Ohm Resistors, Type GM, were used:

	Each
1— 100 Ohm..	\$1.25
1— 300 Ohm..	1.25
2— 1,000 Ohm..	1.25
1— 3,000 Ohm..	1.25
1— 10,000 Ohm..	1.50
1— 30,000 Ohm..	1.50
1—100,000 Ohm..	2.00

**Shallcross Mfg. Company**  
 ACCURATE HIGH RESISTANCE WIRE WOUND RESISTORS  
 ELECTRICAL SPECIALTIES  
 700 PARKER AVENUE  
 COLLINGSWORTH, Pa.

If you are interested in building your own Wheatstone bridge, special resistors are available

(Continued from page 90)

ages, doubling the frequency. Each transformer is furnished with eight feet of cord and plug.

In this illustration is shown the Clara-Tone antenna tuning device marketed by the Essenbee Radio Devices Co., of Chicago.




In some types of receivers, especially those employing an periodic primary, reception may be improved by inserting in the antenna circuit an external tuning arrangement.
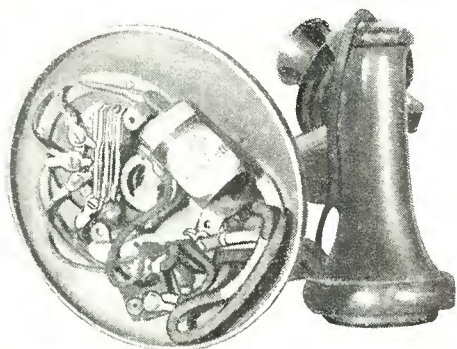
### Cures Dialing Interference

**T**OBE Deutschmann Corporation of Canton, Mass., announce a new Filterette especially designed for use in the automatic telephone equipment for elimination of dialing interference. The Filterette is shown in the illustration accompanying this article.

Anyone with a screwdriver can install the Filterette in the




telephone stand base by merely removing three screws and the base. The Filterette has two flexible leads that fit under terminals described in the instructions that accompany the device.

### Filtermatic Loading Coil

**D**ESIGNED to either increase the effective primary inductance by placing it in series with the antenna, or reduce the effective inductance by placing it in parallel with the primary circuit, the Filtermatic has been announced by the Filtermatic Manufacturing Co., of Philadelphia, Pa. The device is easy to install since it is merely placed either across the antenna and ground terminals of your receiver, or in series with the antenna lead and the antenna terminal. Both methods of connection should be tested to secure the best form for a particular receiver.

(Continued on page 92)

## IT'S EASY TO IDENTIFY 1931 TUBES

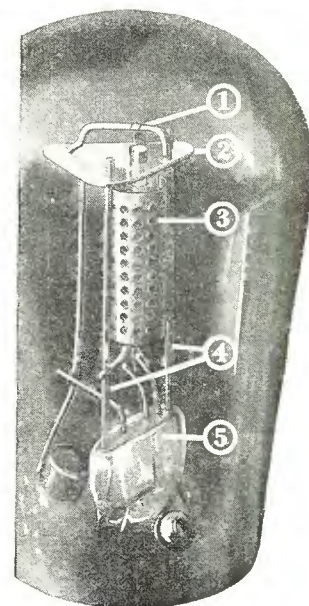

①

### Positive Characteristics

TUBES must do more than light, or ride on testimonials. From factory to ultimate socket, they must provide definite electrical characteristics precisely matched to radio set requirements at all times.

And that is the function of ultra-sturdy De Forest construction.

1. Nickel support wires of twice the normal diameter.
2. Heavy, accurately punched mica spacer positively positioning elements at top.
3. Perforated metal plate in place of wire mesh.
4. Heavier side supports providing ample rigidity four ways.
5. Special tempered glass press produced a unique De Forest automatic units, accurately mounting support wires.

These and other advanced features, found in fresh De Forest Audions—tubes produced a month or two ahead of sale—insure the 1931 performance of the 1931 radio set.

*de Forest*  
AUDIONS  
RADIO TUBES




DE FOREST RADIO CO.  
PASSAIC, N. J.

After all, there's no substitute for 25 years' experience



# GEORGE W. WALKER SUPER-CONVERTER

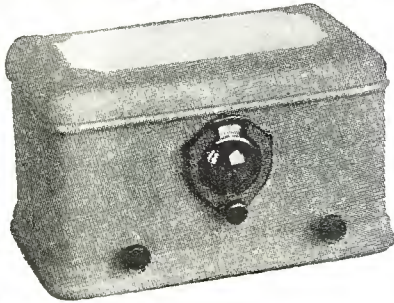

(Model No. 4)

Convert Your Present Radio Receiver into a Short-Wave Super-Heterodyne

Listen to Foreign Programs With Pleasing Volume

## WALKER SUPER-CONVERTER FEATURES

Four A.C. Tubes, including Screen Grid and No. 180 Rectifier. All A.C. operated.

### Truly Single Dial Tuning

No changing of coils for the popular Short-Wave Band. Adaptable for use with either battery or A.C. receivers. Attractive in appearance with its neat and compact two-toned moire finished metal cabinet, which measures but 7"x7"x12" long.

The Walker Converter represents the result of several years of experience in the design of Short-Wave equipment.


Each device tested in actual operation at the factory, insuring uniform efficiency in performance.

COMPLETELY WIRED AND ASSEMBLED (Less Tubes)

**\$65.00**
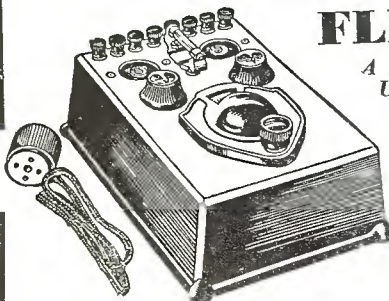
## FLEXI-UNIT

A Flexible Radio Device of Unlimited Application—



Showing No. '01 Adapter

Efficient reception of the entire wave band of 15 to 550 meters. Can be used with either A.C. or Battery receivers, or as an individual single tube receiver for short or long waves. Serves many purposes. Indestructible! Simple to operate—and inexpensive.

Write for Free Literature—Liberal Discounts to Dealers and Service Men

One of America's Pioneer Radio Manufacturers

**THE WORKRITE RADIO CORP.** 1810 E. 30th St. Cleveland, Ohio


Short-Wave Receiver, Short-Wave Adapter, Regular Broadcast Tuner, R.F. Pre-Amplifier (Booster), Radio "Experimental" Unit, Oscillator and Wave-trap. USE THIS UNIT AHEAD OF YOUR SHORT-WAVE TUNER AS A R.F. BOOSTER.

Should your List Price dealer be unable to serve you promptly—Mail your order direct to factory. Including Coils

- No. '01 Adapter Plug (Battery) ..... \$2.00
- No. '27 Detector Plug (A.C. Set) ..... 2.50
- No. '27 R.F. Adapter Plug (A.C. Set) ..... 3.00
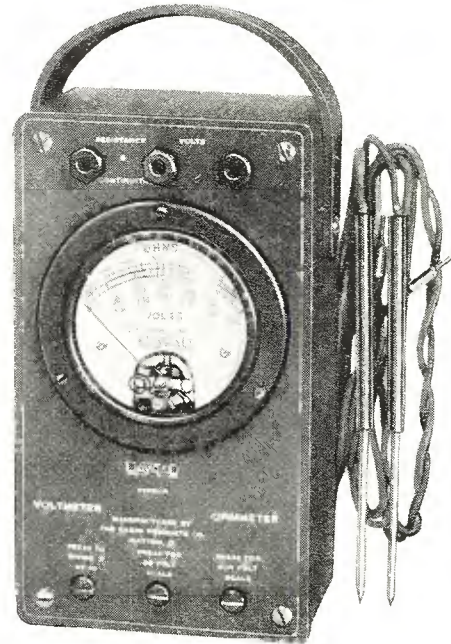
## Dayrad Voltmeter-Ohmmeter

A COMPLETE self-contained combination voltmeter and ohmmeter for service work has been announced by the Radio Products Co., of Dayton, Ohio, and is shown in the photo accompanying this description.




The type R shown here is equipped with genuine D'Arsonval movement meter. There are two direct reading resistance ranges, and three voltage ranges. A 4½ volt C battery is self-contained, furnishing power for the continuity and resistance test.

Two other products made by the same company are the type 180 test oscillator especially desir-


able for alignment work on the new superheterodynes, and the type 8-180 test panel.
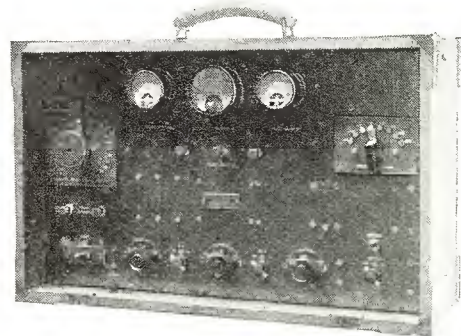
## Jenkins and Adair Equipment

BELOW may be seen the type B portable amplifier made by Jenkins and Adair, Inc., of Chicago, designed and built especially for broadcast station pickup work. It consists of a three stage amplifier using standard tubes to-



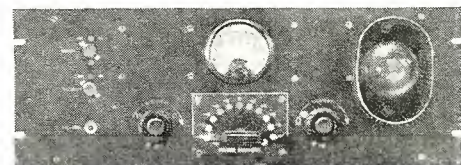gether with a built in level indicator. The two position input normally for either carbon microphones or condenser transmitters, can also be built to accommodate wire lines or phonograph pickup if desired. The input circuit switch, in addition to its normal duty, controls a relay in the output circuit which prevents clicks from going out on the line.



The smaller illustration shows the type C (calibrated) level indicator panel. The circuit is simple and the components rugged. A special input transformer suitably tapped with its associated switch and control points, together with a High Mu

(Continued on page 93)

**KOLSTER**  
245 Power Amplifier with Matched Dynamic Speaker.

The Amplifier has 2 stages, using the 227 in the first and two 245 tubes in the push-pull stage with a 280 rectifier. For 115 volt, 60 cycle a.c. current.

List \$98.00  
(Less tubes) Our Price \$24.50  
with speaker (less tubes)

**WRITE FOR OUR BARGAIN BULLETIN**

Chuck full of Bargains on Standard Merchandise and Replacement Parts.

**To-Day Free**

**STUYVESANT ELECTRIC CO., INC.**  
53 WALKER ST. NEW YORK.


## DEALERS—SERVICEMEN!

We are headquarters for JEWELL and WESTON Testers, Set Analyzers and Meters.

LOWEST WHOLESALE PRICES  
Mail Orders Promptly Filled

**SUN RADIO COMPANY** 64 Vesey Street New York City

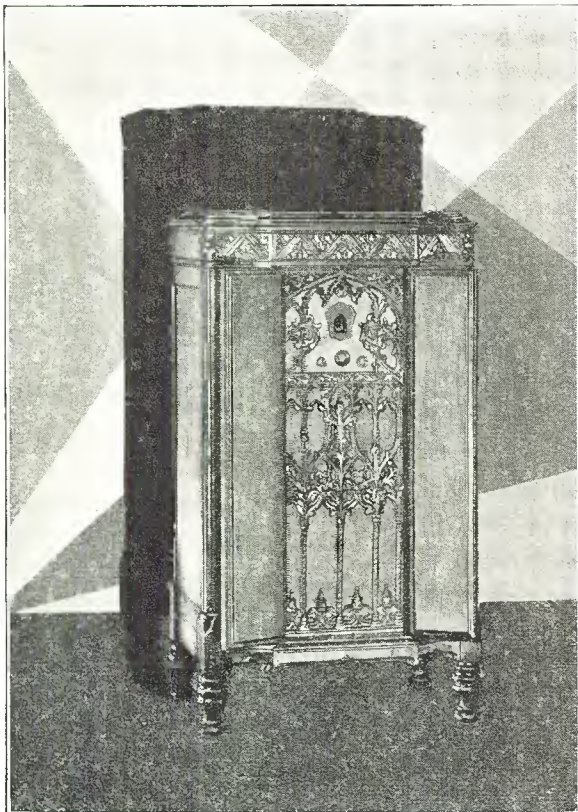Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review



## OXFORD CHROMATROPE

### BRINGS IN THE MISSING MUSIC

A NEW DEFINITION OF TONE—"The complete range of audible sound, with the correct relative intensities of bass, intermediate and treble."

*Frank Reichmann*

By means of two powerful electro-dynamic speakers, a "tuned" theatre amplifier, and an acoustical cabinet design, the OXFORD CHROMATROPE satisfies and demonstrates the above definition for the first time.

The OXFORD CHROMATROPE sets a new standard of sound recreation. It reproduces the lowest drum note, the highest violin note, the lowest and highest overtones of every musical instrument or sound, all in the correct balance. Here is complete music for the first time, exquisitely sweet or magnificent and tremendous, as the mood suits you, but always superatively colorful.

*Hear, own and enjoy one of these famous, new, scientific sound re-creators.*

Manufactured by

### OXFORD RADIO CORPORATION

2035 West Pershing Place

Chicago, U. S. A.

tube and proper filter circuit constitutes the assembly. Level is shown on a special level indicator (Weston). The range in readings is from minus 10 to plus 8 Db. in steps of 2 Db., covering the requirements for all regular broadcasting and recording work.

### Portable Electric Ear

THE world's first portable "electric ear" to separate the various sounds of a whirring electric motor was demonstrated publicly for the first time recently at the Westinghouse Research Laboratories by J. P. Foltz, who developed it.

So compact that it fits into an ordinary suitcase, this new



"electric ear" can easily be taken to whatever sound may be under observation.

Entirely self-actuated, it can be carried to waterwheel generators in a lonely power station in the wilds of Alaska, to motors in an automobile factory around Detroit, to motors in a ship at sea or submarine far below the surface.

This "electric ear" consists of a microphone, an amplifier of several stages to raise the energy level, a filter circuit which permits only one frequency at a time to pass, a meter for

reading amplitudes, and some batteries to furnish power. The complete equipment weighs about sixty pounds and is independent of any outside current supply.

The microphone may be of either the electro-dynamic or condenser type. It is connected to the sound analyzer by a wire and plug. By turning certain knobs and dials, sensitivities on the "selector" from one to 10,000 are possible. Frequency ranges from 60 to 7,000 cycles can be obtained.

In line with the studies of various cities in an attempt to reduce the objectionable noise which, it is said, are gradually making nervous wrecks of the human race, the first step is to analyze the noise and find the parts which make it up.

"Noise is a queer phenomenon," said Mr. Foltz. "It is usually made up of various smaller noises and is seldom found in the pure state.

"When an apple is dropped on a wooden floor, the 'thud' which 'strikes' the human ear is made up of a great number of sounds having no more resemblance to the 'thud' than flour, milk, baking powder, butter and eggs have to a finished cake.


"When the apple hits the floor, the impact starts a series of complex 'broadcasts' which in physics are represented by waves, called sound waves. *It is entirely possible to 'produce' silence by two sound waves which fit into each other much like the teeth of two saw blades.*

"In a somewhat different application, it is also hoped that in the future this new portable 'electric ear' may be used as an advance fault finder for airplane motors and propellers. So much more sensitive than the human ear, it is anticipated that it will hear loose wrist-pins, piston-rings, main bearings, warped or split propellers long before they are loud enough—and consequently dangerous—to be heard by the human ear.

*(Continued on page 94)*

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review
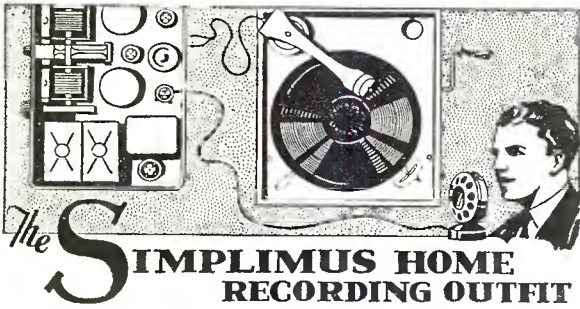
## Servicemens Opportunity to Make Money!



HOME RECORDING HAS TAKEN THE COUNTRY BY STORM and every wide-awake service man and radio dealer should have a sample kit of the SIMPLIMUS RECORDER on hand, to show every phonograph and radio set owner.

The SIMPLIMUS RECORDER makes radio programs, voice records and own home talkies and can be operated from any radio set. A single demonstration is usually sufficient to sell the average individual.

The complete SIMPLIMUS HOME RECORDING OUTFIT includes Hand Microphone, Input Control Stage and Recorder and any radio set or phonograph turntable can be used. List price \$50.00. DEALER'S NET PRICE.....**\$29.50**

Home Recording Double Face Record Blanks (Standard six-inch pre-grooved blanks). Four (4) blanks for List Price 95c. NET PRICE.....**.86c**  
 Package of eight (8) Recording and Reproducing Needles. List Price 25c. NET PRICE.....**.23c**

**Servicemen and Dealers!** Write or wire for exclusive territory proposition. Here's a chance to use a new product to help build up your sales and profit. An all year seller!

Be the First to Show the Latest Order the SIMPLIMUS HOME RECORDER TODAY!

I am enclosing  check or  money order for Sample Kit of the Simplimus Home Recorder.

Name.....  
 Address.....  
 City..... State.....  
 Occupation.....

**SIMPLIMUS, INC.** 67 CHURCH STREET BOSTON, MASS.

It is not unlikely that when developed this apparatus will be made part of airplane's required inspection before flight.


"This future 'electric ear' could be incorporated in an airplane's dashboard so that a bad motor part or propeller blade developing during flight would instantly show up as a red light to warn the pilot of prospective trouble. Then, with the cards on the table, the pilot would be able to decide whether he could safely cross the Rockies, the Alleghenies, or parts of the Atlantic Ocean without landing at the nearest airport to have the trouble remedied.

"Of course, these are only hopes at present and we will probably need considerable time to develop them. Once on a commercial basis, however, they give promise of a more enjoyable life on the earth and a safer life in the air."

While this equipment gives great promise, it is not yet in commercial production.
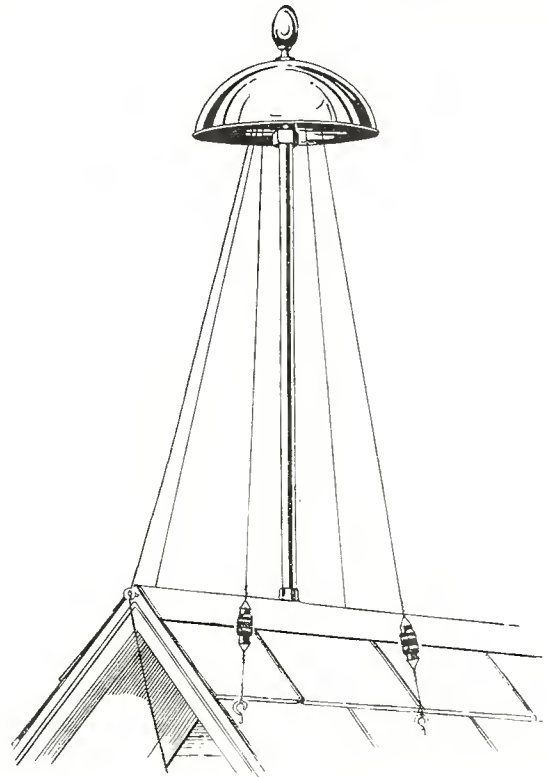
## Airway Super Aerial

A recent product announced by the Airway Super Aerial Mfg. Co., of Fort Wayne, Indiana, is the one illustrated above.




It is strongly built and properly insulated. It has copper alloy dome, tinned copper wire, and glass insulators.
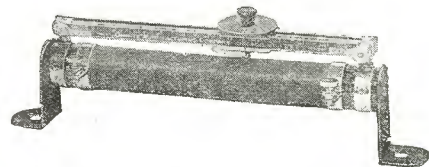
## New Ohmite Product

ILLUSTRATED below is one of the new products announced by the Ohmite Manufacturing Co., of Chicago.

It is a slide wire rheostat-potentiometer. Mounting legs are provided for each end. Details of the new item may be



had by writing the manufacturers at 636 North Albany Avenue.

## Setbuilders Attention! RADIO PARTS-KITS-TUBES

Largest Assortment in the U. S. A.

Everything for Receiving and Transmitting

Big Discounts to Setbuilders on Parts, Kits, Tubes, etc.

Northwest Wholesale Distributors of U. S. Apex, Gloritone, and Automobile Sets

**WEDEL COMPANY, Inc.** SEATTLE, WASH. Established 1888

## PHOTOELECTRIC CELLS

By Dr. Norman R. Campbell and Dorothy Ritchie

Research Staff, General Electric Co., Wembley, England. A complete, practical treatise. Illustrated.....\$4.50

## TELEVISION

By Sydney A. Moseley and H. J. Barton Chapple

History, latest theories and developments. Illustrated.....\$2.50

**ISAAC PITMAN & SONS, 2 West 45th Street, New York**

We carry complete line replacement parts for

EARL, FREED-EISEMANN, FREED and FRESHMAN RECEIVERS

Send for Catalogue

AK 37 replacement blocks, 90 day guarantee.....\$3.75  
 Carbon metallized resistors (mfd. by DURHAM) 20 values in stock, per dozen.....\$1.00  
 Freshman Q power transformers (for 1-280, 1-226, 1-227, 1-171, 1-222 or 224) (can be used in midget sets).....\$3.25  
 Tip jacks, each.....\$0.04

**FREED SALES SERVICE CO.**  
 16c Hudson Street New York City



### New Transmitting Condenser


A NEW product in the transmitting line has been announced by the Air-Way Condenser Co., of Brooklyn, N. Y., which is marketing an intermediate transmitting condenser to meet the need for a condenser for low power installations where weight and space are essential factors.

The condensers are made entirely of aluminum, which accounts for a weight of 3½ ounces for the 50 mmf size and 8 ounces for the highest capacity manufactured, which is 150 mmf. The space occupied by the latter is 2¾ by 5 inches.

Among some of the features used are rigid phosphor bronze spring, extension shaft which permits ganging, three post supports for the end plates. If desired single hole mount can be supplied at slight extra cost, as well as brackets for base mounting. The voltage breakdown rating is 1500 volts.
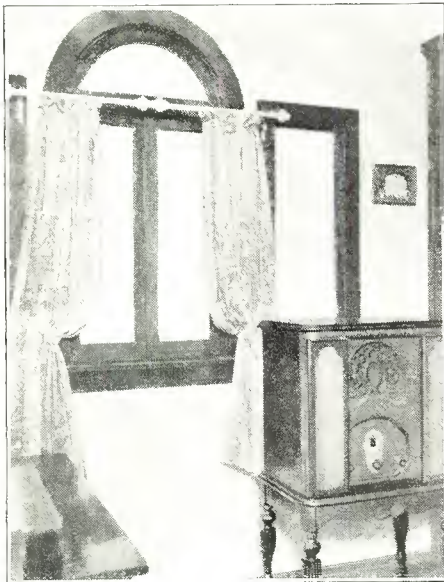
### Placement of Set in Room

MANY service men overlook the fact that in many cases reception may be improved by the proper installation of the receiver in the customer's room. In the photograph shown may be seen one of the methods of installation.



In the upper picture the console is placed near the window, about four inches from the wall. The principal reason for this setting, is the fact that in certain locations best results are secured when the set is located near a window, particularly in the homes where metal lath is used in the walls.

### TUBES—TUBES—TUBES

For Replacements—All Standard and Special Types

[ *Jobbers—Dealers and Servicemen* ]  
Write us your requirements! Greater profits. Special job lots always available.

KUCKER RADIO & ELEC. CO. 67 Cortlandt St. New York, N. Y.

# N

## A PERFECT TUBE TESTER

*The First Tube Tester Which Indicates Directly Normal Wear and Noisy Tubes*



- Applies Correct D.C. Plate and Grid Volts.
- Applies Correct Filament Volts.
- Indicates Directly, Dynamic Mutual Conductance and Plate Current.
- Tests All Tubes Including the New 2-Volt Type.

THE AC-47 Radio Tube Tester is the first jobbers' and dealers' type tester to be placed on the market operating from 110 volt A.C. line, which actually applies D.C. TO THE PLATE, and at the same time, delivers the correct amount of D.C. GRID BIAS.

In all other types of tube testers now on the market, Raw A.C. is applied to the plate, and the tube is made to act as its own rectifier. It is impossible to get an accurate check of any tube unless D.C. is applied to the plate.

In the AC-47 Radio Tube Tester, all the voltages are standardized and are absolutely INDEPENDENT OF LINE VOLTAGE FLUCTUATIONS.

MUTUAL CONDUCTANCE is the most important determining constant of the excellence of any radio tube, and the AC-47 is the first to be placed on the market, which actually indicates this constant DIRECTLY ON A METER.

----- Detach and mail this coupon -----

**THE HICKOK ELECTRICAL INSTRUMENT CO.**  
Cleveland, Ohio

Am interested in the following items: AC-47 Radio Tube Tester. Check  SG-4600 Radio Set Tester. Check  Ohm-Capacity Meter. Check

Name.....

Address.....

City.....

State.....

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# RADIO SERVICE SCHEMATICS



THE editorial staff of the CITIZENS RADIO CALL BOOK MAGAZINE has prepared the most complete *Service Manual* ever published—which is yours for the price of the “Call Book” alone.

*Over one hundred Schematic Wiring Diagrams of Popular Factory Built Radio Receivers and Power Supplies, carefully drawn by our own expert drafting force, are contained in this BIG NEW SERVICE MANUAL.*

RECEIVER RESPONSE CURVES, showing sensitivity, selectivity and fidelity characteristics, prepared in our own laboratory as specified by the IRE and RMA are given, showing such popular brands as RCA, Majestic, Atwater Kent, Crosley, Silver, Sparton, Stewart-Warner, Brunswick and others.

*Laboratory and workshop formulas are shown in simplified form to aid the Service Man and Engineer*

The regular annual subscription price to the “Call Book” is \$2.00. . . . We offer you . . . .  
**ONE FULL YEAR’S SUBSCRIPTION AND THIS COMPLETE SERVICE MANUAL for only \$2.00**

*If you are already a subscriber, we will extend your subscription for a year.*

*Fill in the Coupon,  
 Enclose \$2.00 and  
 get your “Call Book” for  
 one whole year  
 and  
 this BIG HANDY  
 SERVICE MANUAL  
 as a premium*

**CITIZENS RADIO SERVICE BUREAU**

508 South Dearborn Street, Chicago, Ill.

Gentlemen:

Please find enclosed \$2.00 (Foreign \$2.25), for which kindly enter my subscription for One Full Year to CITIZENS RADIO CALL BOOK MAGAZINE and TECHNICAL REVIEW. It is understood that I am to receive ABSOLUTELY FREE, a copy of “Radio Service Schematics.” Start my subscription with  January 1931  March 1931  Sept. 1931  Nov. 1931.

NAME.....

STREET & NO.....

CITY..... STATE.....

*Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review*

## LOWEST PRICES--1-DAY SERVICE

The rapid growth of our mail-order department is a tribute to our desire to give you the best values in standard radio parts and accessories at the lowest prices.

To those living in the Eastern United States, our service can not be equalled and our slogan "You get it sooner from us" is not an idle boast. A trial order will convince you.

GET OUR CATALOG--IT'S FREE!

# CAMERADIO

C. R. O.  
430 WOOD ST.  
at Diamond St.  
PITTSBURGH PA.

## Study RADIO in CANADA

CANADA'S PIONEER COLLEGE, endorsed by leading radio manufacturers offer DAY, EVENING, HOME STUDY and SPECIAL TRADE COURSES with free scholarships and trip to Toronto (all expenses paid). Write today for free booklet.

Radio College of Canada, Limited  
310 Yonge St. Toronto




30 DAYS' FREE TRIAL  
FACTORY TO YOU. SAVE 1/3 to 1/2

Latest 1931 Super-SCREEN GRID!


TONE CONTROL and latest features of costliest sets. Send for Special Offer.

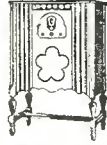**MIRACO** MIDWEST RADIO CORP.  
11th Successful Year  
831-HJ Miraco Dept. Cincinnati, Ohio



\$49.89  
less tubes

## WARD ELECTRIC IRONS for PERFECT SOLDERING

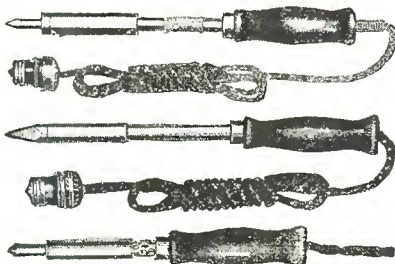

No. 600—3/8" Tip—110V  
—135W .....\$7.50

No. 168—5/8" Tip—110V  
—100W .....\$2.80

WARD RADIO JR.—3/8"  
Tip—110V—100W .....\$2.50

THE WARD RADIO JR. IRON is only 10" in length and is designed especially for radio work. All irons are fully guaranteed and approved by the Underwriters Laboratories. Tips are tinned ready for use and are easily interchangeable. Irons maintain an even temperature while in operation and the handle always remains cool. They are especially designed for greater efficiency and long life under heaviest working conditions.

### HEAVY IRONS FOR SPECIAL WORK

-----MAIL COUPON NOW!-----

WARD MANUFACTURING COMPANY  
Dept. F-3, 1161 Milton Avenue, Chicago, Ill.

I enclose M. O. for \$..... Please send postpaid Iron No. ....

Send C.O.D. Iron No. ....

Send Special Dealers Proposition.

Name.....

Address.....

City..... State.....

# RADIO'S Latest and Greatest

Get This 168 Page Catalog

EVERYTHING AT LOWEST WHOLESALE PRICES!

At no time since the science of RADIO startled the world have you been able to secure such astounding values as the new Allied catalog brings you. If you contemplate buying either a complete set or any single article of radio equipment, it will mean money in your pocket to have this 1931 book of wonderful radio values before you.

All the 1931 marvels of Radioland . . . 1931 Screen Grid, Tone Control, A. C. Humless All-Electric Sets, Mantel Sets, Public Address, Phono-Combinations, Dynamic Speakers, Beautiful Consoles . . . as well as battery operated sets. Also the brand new Slot Machine Radio . . . a big money-maker for restaurants, hotels, stores and public places.

Our buying power alone brings you these amazing values. With resources of over three million dollars, we maintain an enviable position in the buying market. You reap the benefit.

Get This Free Bargain Book Today!

**ALLIED RADIO CORPORATION**  
711 W. Lake St. Dept. C-2 Chicago, Ill.

## The MARS Powerful SUPER-MIDGET

\$55.70 List



Model 13

The Big Sensation of the Year

No other midget performs like the MARS. A real distance getter. A coast to coast receiver of exceptional quality. For daytime reception. Plenty of "wallop." Six tubes! 4 Screen grid! Super-dynamic speaker. Tone Control! "Litz" Coils! L-W Audio! R.C. Condensers. A real radio—not an imitation. Made to sell to the "tough" customer.

ONLY FEW TERRITORIES OPEN

Dealers, Service Men—WRITE!

Dealers and service men everywhere are making real money handling the MARS Super-Midget. Customers buy on first demonstration. For quick sales and lasting satisfaction, turn to the MARS. Exclusive territories are going fast. Write or wire for profit-making proposition.



Model 14 \$65.70 List

COMMONWEALTH RADIO MFG. CO.  
853 West Harrison Street Chicago, Illinois

## NUBOR FLASHES

We have so many good items at such attractive prices in Standard Radio Parts, that even a full page advertisement could not do them justice, therefore send for our Big 16 page catalog and pick the winners.

**NUBOR WHOLESALE** Dept. C, 14-B Warren St. NEW YORK, NEW YORK

## SERVICE MEN AND DEALERS

GET THESE BARGAIN SPECIALS!

- |   |  |
|---|--|
| 7 St. Copper Aerial Wire 15c. Lots of 50 .....\$7.15                            | Silk Parallel Lamp Cord, 500 ft. spools in white, brown, gold.....\$2.50   |
| 7/22 Heavy Copper Aerial Wire 28c. Lots of 50 .....\$12.50                      | Fixed Pigtail Resistors, Asst. ohms, per doz. ....\$96c  |
| A. K. Mod. 37 sets Replace Block.\$3.75   | Majestic B Replace Block, guaranteed, each .....\$2.65   |
| Filt. Cond. 1 mfd. 450 D.C.....32c  | Bryant A. C. Toggle Switch for battery and electric sets approved, while they last, ea. 19c. Lots of 10.....\$1.70 |
| Filt. Cond. .5 mfd. 450 D.C.....25c   |  |
| Fixture Wire, stranded, S. C. C. 1,000 ft. spools in white and brown.....\$3.20 |  |
- Send 20% with order, balance C. O. D. Deduct 2% for full remittance.  
LEIMAN RADIO COMPANY, 58 WARREN STREET, NEW YORK, N. Y.

# CLAR-A-TONE

Gives Volume—Reception and Tone Your Radio Never Produced Before



  
\$1.95  
Postpaid

## Money Back Guarantee

Pure, clear tone—greater volume—interference cut out instantly! Attach Clar-A-Tone to your set and enjoy tone you never thought your radio could produce.

Thousands of owners say Clar-A-Tone is amazingly ingenious. And radio engineers will tell you what a fine technical accomplishment it is.

Regular price, \$2.50—but now as special introductory offer, we will ship you a Clar-A-Tone direct for only \$1.95. Mail the coupon below with check or money-order, or currency. No C.O.D.'s. Money back any time within 10 days if you're not satisfied. Simple installation instructions complete on box.

**ESSEN BEE RADIO DEVICES CO.**

732 Mather Street, Chicago, Illinois.

Enclosed find my payment of \$1.95 for Clar-A-Tone, sent postpaid.

Name.....

Address.....


City..... State.....

A Big Special—While They Last

## \$110.00 PHOTOPHONE



12-inch Dynamic **SPEAKERS**

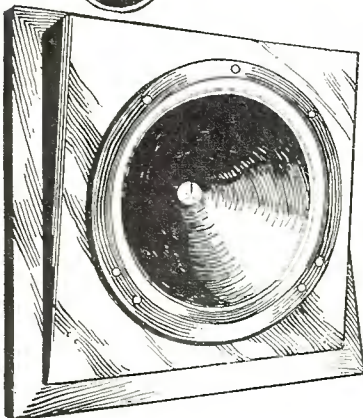

Brand New in original cases. Only limited number — order today **\$15**

Never before was such an astounding value offered. Every carnival owner, motion picture house, theater, church, fair, American Legion Post, club, sound engineers and radio experimenters will want one.

12-inch Dynamic. Field Supply, 110 volts D. C.; Field Resistance, 1000 Ohms; Voice Coil, 8 Ohms; Mounting, Steel angle frame. For adaptation to A. C. operation, \$6.50 additional.

**M. & H. SPORTING GOODS CO.**  
512 Market St., Philadelphia

Terms: 25% with order; balance C.O.D. or Sight Draft.  
SPECIFY EXPRESS OR FREIGHT


## Announcing a new— BROWNING-DRAKE Screen-Grid RADIO

This new receiver will surpass the sales of the Browning-Drake Kit—and remember they outsold every other kit.

Service Men—Set Builders—Dealers! Write Today for New Proposition

**BROWNING-DRAKE CORP.**, 224 Calvary St., Waltham, Mass.

# For TESTS ON SUPERHETS

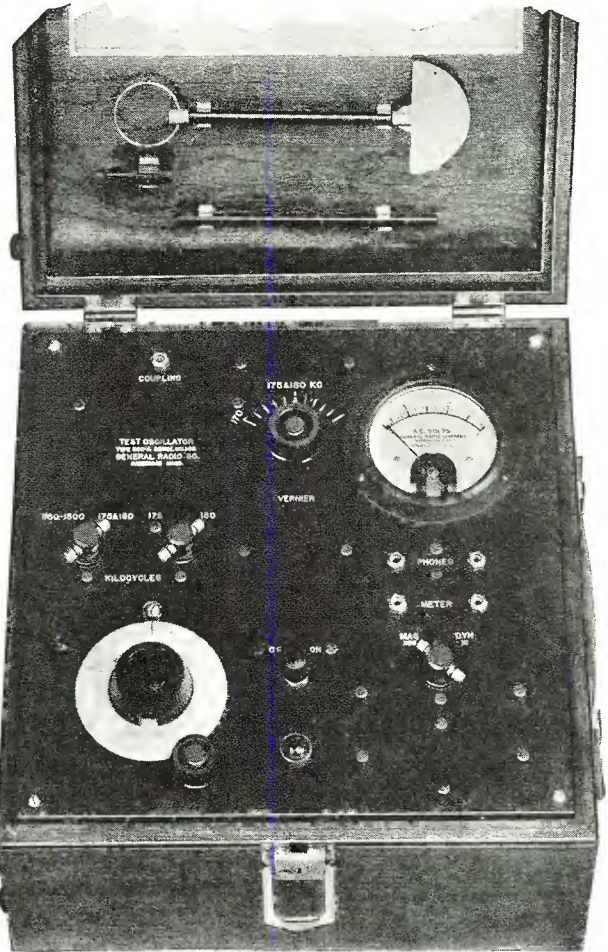

## The Type 360-A Test Oscillator

is the result of more than two years of experience with the design and manufacture of test oscillators for servicing Radiola superheterodyne receivers. Several hundred instruments are already in use and the list is growing as other manufacturers go into production on superhets.

### Note the Following Features:

- (a) Modulated signals are available at 175 kc., 180 kc., and any frequency in the broadcast band.
- (b) The 180-kc. channel is calibrated at five 1-kc. intervals on either side for aligning band-pass filters.
- (c) The 500-kc. to 1500-kc. tuning control is calibrated throughout the band.
- (d) Test tools and a copper-oxide-rectifier output meter are included as regular equipment.


Get the facts before you buy a test oscillator. Send for a copy of Bulletin 932-C1.

**GENERAL RADIO COMPANY**  
Offices, Laboratories, Factory  
**CAMBRIDGE A, MASSACHUSETTS**

Pacific Coast Warehouse: 274 Brannan Street, San Francisco

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# FREE!

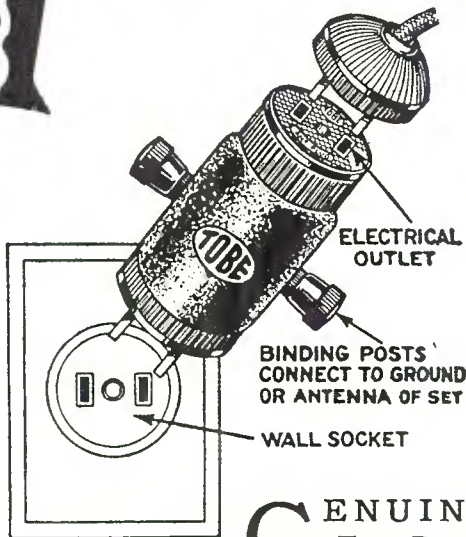

## GENUINE Tobe Four Purpose Light Socket Aerial

FREE with one year's subscription to Citizens Radio Call Book—Radio's Greatest Magazine.

This device saves the cost and bother of installing an aerial, lightning arrester or ground and at the same time permits the use of an electrical outlet. Just plug in your electric lamp or electric radio set as you now do to baseboard receptacle or lamp socket. Over all dimensions 2 1/4" x 2 1/2".

Static minimized—construction of plug prevents excessive pickup of static—increased selectivity—improves tone quality. Tuning is sharpened—your set will tune much more sharply when you use a Tobe Aerial, than when you use an outside aerial. Each aerial guaranteed for two years, unconditionally. Full instructions showing many combinations accompany each aerial.

**Send This Coupon Today!**

CITIZENS RADIO SERVICE BUREAU  
508 So. Dearborn Street, Chicago, Ill.

Here is my \$2.00 (Foreign \$2.25), for which please send me a Tobe Four-Purpose Light Socket Aerial FREE and enter my subscription for the Citizens Radio Call Book Magazine for one year starting with

March 1931  Sept. 1931  Nov. 1931  Jan. 1932

Name.....

Street & Number.....

City..... State.....

BACK NUMBERS AVAILABLE 50c



Licensed Under  
Loftin-White and  
R.C.A. Patents

**ELECTRAD C-250 AMPLIFIER**  
Provides 10.35 watts undistorted output with input volts .3. Utilizes one 224, two 250 and two 281 tubes. Completely assembled only.

## High Quality AMPLIFICATION At Low Cost!

With the New **ELECTRAD LOFTIN-WHITE**  
Direct-Coupled **AMPLIFIERS**

**E**NGINEERS have long awaited the perfected advantages of the revolutionary Loftin-White *direct-coupled* system in an amplifier of high output and wide general adaptability.

The Electrad C-250 Amplifier is the answer. The C-250 (illustrated above) and its companions, the A-250 and the A-245 provide the notably high quality output, general stability, low initial cost and operating economies for which this system is noted.


These Amplifiers are *perfected* products of typical Electrad high quality and offer a range of power suitable for present-day needs.

They are readily adaptable to all usual requirements of sound amplification from microphones, phonograph pickups, radio tuners,—in fact, for all types of amplification of audio frequencies.



**ELECTRAD A-250  
AMPLIFIER**

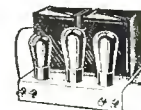Provides 4.6 watts undistorted output. Utilizes one 224, one 250 and one 281 tube. Completely assembled only.



**ELECTRAD A-245  
AMPLIFIER**

Provides 1.6 watts undistorted output with one 224, one 245 and one 280 tube. Completely assembled or in kit form.

Mail Coupon for Circular containing detailed information about Electrad Amplifiers.

ELECTRAD, INC., Dept. CB-1  
175 Varick St., New York, N. Y.  
Please send technical information about ELECTRAD Amplifiers.  
 Check here for literature on complete Electrad line.

Name.....

175 Varick St., New York, N.Y.

**ELECTRAD**  
INC.

Address.....

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# Astonishing ~ RADIO VALUES

Up-to-the-minute offerings at lowest wholesale prices. Includes newest Tone Control, Screen Grid Superheterodyne, Radio-Phonograph combinations, short wave receivers, automobile radios, Public address. Attractive walnut consoles and latest accessories, parts and kits. Don't buy until you see our big catalog.



Headquarters for TELEVISION Apparatus and SHORT-WAVE Equipment

S-M, NATIONAL, I.C.A., THORDARSON, JEWELL and READRITE. We also carry a Complete Line of Radio Parts. Prompt Deliveries—Lowest Wholesale Prices.

Send for **FREE** Complete Catalog

**Western Radio Mfg. Co.**  
The Big Friendly Radio House  
128 W. Lake St. CHICAGO ILL.

## REPAIR PARTS

Complete Line of the Following:  
CENTRALAB—CARTER—YAXLEY  
VOLUME CONTROLS  
MERSHON and BASSETT CONDENSERS  
THORDARSON TRANSFORMERS  
ELECTRAD RESISTORS—ALL TYPES  
Order Your Requirements from Us Today  
Prompt Delivery!

**RADIO PARTS COMPANY, INC.**  
313 West State Street, Milwaukee, Wis.



### No More Stolen Microphones

with the ELLIS 'Demountable'



The Ellis DEMOUNTABLE Microphone provides an easy method of removing and replacing the unit. When not in use the microphone unit can be placed in the pocket and carried to a place safe from theft or exposure to the elements. List price \$85.00. Other Models \$25.00, \$45.00, \$75.00 list. New two-button Hand Microphone now ready.

Write for complete details

**ELLIS ELECTRICAL LABORATORY**

Sales Corporation

337 WEST MADISON ST. Chicago, Illinois  
EXPORT "SIMONS," 25 WARREN ST., NEW YORK. CABLE "SIMONTRICE"



**HARRY C. MOIR**  
PRES. & GEN. MGR.  
THE MARRIOTT GROUP



The Morrison is the World's Tallest Hotel—46 Stories High.

Nearest Hotel in the City to stores, Offices, Theatres and Railroad Stations.

A Guest at the Morrison enjoys all the luxuries that only a hotel of premier standing can offer. Yet rates are remarkably low—\$2.50 up—because sub-rentals pay all the ground rent. The saving is passed on to guests.

Every room in the Morrison Hotel is an outside room, with bath, circulating ice water, bed-head reading lamp and Servidor. A housekeeper is stationed on each floor.

## CHICAGO'S MORRISON HOTEL

Corner Madison and Clark Streets

**2500 Rooms \$2.50 Up**



A SMART HOTEL in America's Smartest Resort

**The St. Charles**

On the Boardwalk Atlantic City, N. J.

The St. Charles will appeal to your personal comfort—your stay will be made a pleasant one and you will feel better physically. The tang of ozone makes you fit! Concerts and Recitals. American and European Plan. Perfect Service. Booklet.

Wire COLLECT for Reservations

Recently Completed and the Outstanding Success of the City

## The Belvedere Hotel

48th Street, West of Broadway, New York City  
TIMES SQUARE'S FINEST HOTEL

Large single rooms with private tub and shower—\$3.00, \$3.50 and \$4.00—Bath \$5.00  
Large double room, twin beds—\$6.00  
Special weekly rates

Within convenient walking distance to important business centers and theatres. Ideal transit facilities. 450 rooms, 450 baths. . . . Every room an outside room—with two large windows . . . and a dandy little serving pantry in each room. . . . Moderately priced restaurant featuring a peerless cuisine.

**CURTIS A. HALE, Managing Director**  
Illustrated booklet free on request

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# Send for New 1931

Radio and Electrical  
Wholesale Trade Catalog

→ IT IS FREE ←

Royal-Eastern's New 1931 General Wholesale Trade Catalog has been compiled to place before you a most comprehensive line of high-grade nationally advertised merchandise, at lowest wholesale prices.

Every worth-while radio, electrical and sporting goods item is featured at lowest wholesale prices. Being the largest radio and electrical mail order house in the East, we can serve you best. *We buy no seconds. We have no job lots.* Only fresh and clean products in original factory cartons.

Same day shipping service—and, Royal-Eastern never substitutes.

With our large warehouses and a background of thirty-three years of service to the trade, we are in a position to render the same service to you as has been our custom in the past.

Official authorized headquarters for New Hammarlund HiQ31, Silver-Marshall and Pilot Products.

### Best Credit Rating!

#### OUR BANKING AFFILIATIONS AND DEPOSITORIES

The National City Bank of New York, N. Y.  
Irving Trust Co., New York, N. Y.  
Brooklyn National Bank, Brooklyn, N. Y.  
Bank of Manhattan, Long Island City, N. Y.  
Huguenot Trust Co., New Rochelle, N. Y.

33 Years  
Service to  
the Trade

Send for Catalog  
Today!  
IT'S FREE!

33 Years  
Service to  
the Trade

## Royal-Eastern Electrical Supply Company

16-18 W. 22nd St. (Dept. X), New York, N. Y.

Branch Warehouses:

Brooklyn, N. Y. Long Island City, N. Y.  
New Rochelle, N. Y.

## WELLSTON GOLD TEST AERIAL

**Gets  
Greater  
Distance**

*Reduces  
Static and  
Hum!*

The  
World's  
Smallest  
Aerial  
2½ by 5 inches  
in Size



### IMPROVES RADIO RECEPTION

This NEW-IMPROVED WELLSTON GOLD TEST AERIAL eliminates both outside and inside aeri-als. One of the greatest innovations since radio itself, this new improved model follows closely upon the success attained by the original WELLSTON GOLD TEST AERIAL which at present is giving satisfactory service to thousands of radio owners throughout the country. It brings in distant stations with crystal clear tone quality and greater volume—gives selectivity without distortion and helps to eliminate overlapping of stations.

#### IT WILL NEVER WEAR OUT

Made of emerald green genuine Condensite, the WELLSTON GOLD TEST AERIAL is of the filtered type endorsed by radio engineers and has a capacity equivalent to 54 ft. of best grade aerial wire strung 50 ft. high in the air. It is absolutely non-directional, non-corrosive and guaranteed never to wear out. It does away with all lightning hazards and because it does not connect into a light socket, all AC hum and line noise is eliminated.

#### Easy to Install

It is a simple matter to install the WELLSTON GOLD TEST AERIAL—even a child can do it in a minute's time. No extra tools are needed. Place it anywhere—inside or on the back of the radio cabinet. Once installed no further attention is required.

For Sale by Leading Radio Dealers

Price **\$2.50** (Retail)

The WELLSTON RADIO CORP., Dept. 110, St. Louis, Mo.

#### Jobbers—Dealers Wanted Everywhere!


We have an unusual money-making proposition to offer Jobbers and Dealers on this new and improved type of aerial. Exclusive territory open. Complete dealer service—circulars, window displays, counter cards, coupled with a strong national advertising campaign. Write at once for full information, including SPECIAL LARGE DISCOUNTS, Price List, Etc.

## Improved BRAXTON-KING

(Model C-5)

Five  
Screen Grid  
Tubes

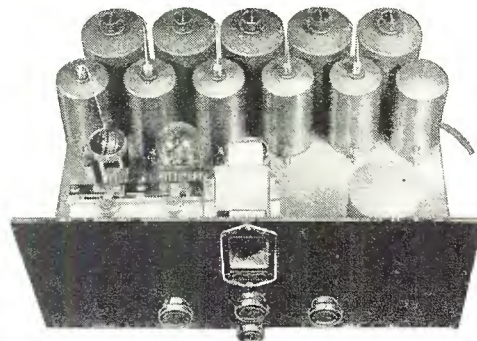Five Tunable  
Intermediate  
Transformers



A. C. SCREEN GRID  
SUPERHETERODYNE TUNER **\$89.50**

INCORPORATING all the advantages of our previous Model C tuner, the new Model C-5 includes numerous efficient improvements such as heavier shielding throughout, automatic antenna compensation and other detailed changes that give even greater amplification and selectivity. This Model may be used in connection with any two stage amplifier.

Set  
Builders!

Write for  
Information  
and  
Discounts

MISSISSIPPI VALLEY RADIO COMPANY  
5650 Delmar Blvd., St. Louis, Mo.

Please rush complete data on Braxton-King Model C-5 Tuner and Model-D Amplifier.

Name.....  
Address.....  
City..... State.....

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# Make a PROFIT from Every Service Call

When tubes blow... filter equipment foils... tone quality suffers... install AMPERITE. Automatically regulates line voltage fluctuations, up and down, between 100 and 140 volts to exact requirements.

Easily installed in 5 minutes without chassis changes. Satisfies customers... reduces free service... pays you a profit. A type for every electric radio.



**AMPERITE Corporation**  
501 BROADWAY NEW YORK

## AMPERITE

Self-Adjusting  
LINE VOLTAGE CONTROL

Ask your dealer or write us giving set name and model. Address Dept. CB-1




# Hotel Dixie

42<sup>d</sup>-43<sup>d</sup> Streets West of Broadway

A New and Better Hotel for Times Square

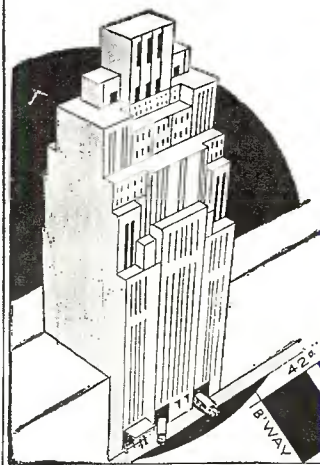Not alone new in construction and equipment, but new in conception of service and comfort to its guests. Directed by S. Gregory Taylor, who has made such enviable successes of the Hotels Montclair and Buckingham.



**Single Rooms**

with tub and shower

**\$3, \$4 and \$5**

**Double Rooms**

with tub and shower

**\$4, \$5 and \$6**

A few terraced rooms and suites, exceptionally large closets, on an attractive monthly basis.

**RADIO IN EVERY ROOM**

Entrances on 42nd and 43rd Sts.

## CENTRAL UNION BUS TERMINAL

LOCATED IN THE DIXIE HOTEL BUS CONNECTIONS FOR ALL POINTS IN THE UNITED STATES

Radiorc AEROVOX Tascos Webster's Forest  
Samson & Dubilier Westinghouse  
ELECTRAD Unipower  
Graybar Kolster's Sorensen  
Worm Electric Powerizer Flechtheim Jewell

**EXTRA EXTRA**

**American SALES COMPANY**  
18-21 Warren Street NEW YORK CITY

Guaranteed Merchandise  
ORDERS SHIPPED  
SAME DAY RECEIVED

Take Advantage  
REAL MONEY  
MAKERS

Radio and Electrical Wholesale  
BARGAIN BULLETIN NO. 66

DEALERS! WHOLESALERS!

**!!WRITE NOW!!**

New Wholesale Catalog No. 66 full of real low prices on: Condensers, Transformers, Speakers, and other numerous items including replacement parts.

AMERICAN SALES CO. C-21 WARREN STREET, NEW YORK CITY

# WE MOVE!

## OUR PRICES HIT NEW LOWS!

To save the cost of trucking to our new quarters of over 15,000 sq. ft., our new Bargain Bulletin No. 66 contains the lowest prices yet! . . . it is on the press now—a card will put you on our list . . .

SEND FOR FREE CATALOG JUST OUT

**COAST TO COAST RADIO CORPORATION**

HEADQUARTERS  
ALL RADIO REPLACEMENT PARTS

142-C LIBERTY ST. NEW YORK CITY

# RADIO PARTS CATALOG

Every dealer and service man should have a copy of our parts catalog. A complete line of standard parts are listed along with replacement parts at lowest prices.

SEND FOR YOUR COPY

We specialize in  
PUBLIC ADDRESS AND TESTING EQUIPMENT

# SILMAN

COMPANY

614-620 GRANT STREET PITTSBURGH, PA.

**"SOUTH of the MASON-DIXON LINE"**  
is but another way of saying  
"Hospitality"!

# HOTEL LUDY

South Carolina Ave. at the Boardwalk

Atlantic City's Newest Centrally Located Fireproof Hotel is South of the Mason-Dixon Line.

Its rates are as pleasing as its hospitality.

\$5 up Daily, American Plan, \$30 up Weekly; \$2.50 up Daily, European Plan

Fireproof Garage Attached  
R. B. LUDY, M. D.

# The HOTEL LUDY

ATLANTIC CITY, N.J.



# FREE!!

**with a year's subscrip-  
tion to the  
Citizens Radio Call  
Book Magazine**



The Famous WARD needs no introduction. Heating Elements will not burn out; either A. C. or D. C., 110-115 volts draws 100 watts. Six feet of heater cord, standard 2-piece separable plug, ebony finish handle, brass plated barrel, 3/8-in. diamond-shaped tip, temperature 500 degrees maintained, handle remains cool. Handle insulated against possible short. A genuine high-grade electric iron. Lava rock core approved and listed as standard by Underwriters' Laboratories.

**A most useful household article.  
Can be used to solder anything  
that requires soldering**

Send in the coupon below and receive the iron absolutely free with a year's subscription to the Citizens Radio Call Book Magazine. Hurry—this offer is limited—mail coupon today.

***Iron Is Guaranteed by Manufacturer for  
One Year—Hurry—This Offer  
Is Limited***

**Citizens Radio Service Bureau  
508 So. Dearborn Street, Chicago, Ill.**

Here's my \$2.00 (Foreign \$2.25), for which please send me a Ward Electric Soldering Iron free and enter my subscription for the Citizens Radio Call Book Magazine for one year starting with

March 1931  Sept. 1931  Nov. 1931  Jan. 1932

Name.....

Street and Number.....

City.....State.....

Back Numbers Available 50c

## Radio Handbook



Each of these Association-developed plans is a big money-maker. Set owners everywhere want their sets modernized, freed from static, made to operate electrically, and want all their rooms wired for radio. Learn to render these services and you can easily make \$3 an hour spare time, to say nothing of the money you can make repairing, building sets and selling supplies. Our members are cleaning up! You can do the same.

### Join the Radio Training Association of America

A membership in the Association will give you the training you need to render these services—enable you to earn \$25 and up a week spare time; start you in a business without capital—prepare you for the \$3,000 to \$10,000 big-pay positions—give you the privilege of buying supplies at wholesale.

To a limited number, we will give Special Memberships that may not—need not—cost you a cent. Write for details and free Radio Handbook.

**RADIO TRAINING ASSOCIATION OF AMERICA**  
4513 Ravenswood Avenue Dept. RCB-1 CHICAGO, ILLINOIS

**1931  
LOWEST  
WHOLESALE  
PRICES!**

# FREE

# RADIO CATALOG

**T**HIS big catalog—rich from cover to cover with astounding radio bargains—is yours for the asking. It contains all the newest and latest in radio receivers, accessories, parts and kits. Screen Grid, A. C., Humless, all-electric sets—also battery-operated sets and direct-current sets. No radio need is overlooked. Everything in this big book is available at wholesale prices, and many items are spotlighted as specials at truly astounding prices.

To be without this book is to miss your greatest buying opportunity in radio. Every page points the way to money saving. Never before have such startling values been offered—made possible by our tremendous buying power and low cost of operation. Quick deliveries and expert co-operation are assured on all orders. Send for your copy of this catalog today. See for yourself the many unusual values we are offering.

**Get This Free Bargain Book Today!**

**Chicago Salvage Stock Store**  
509 S. State St. Dept. 552 Chicago

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

**SET BUILDERS  
SERVICEMEN  
DEALERS  
AGENTS**

**Send for FREE  
Complete Catalog**

**BALTIMORE  
RADIO CORP.**  
47-C MURRAY ST.  
NEW YORK. N.Y.

## GUARANTEED RADIO SERVICE

*Repairing—Testing—Designing and Electrifying*

WE are completely equipped to repair and test any make Receiver or Power Device. Our high class workmanship, together with modern testing equipment, enables us to rapidly locate the defects involved in your receiver in a scientific manner. *All work is guaranteed* and our charges are no more than paid for inferior workmanship.

**DEALERS, JOBBERS AND MANUFACTURERS—Let us give you an estimate for repairing and servicing all your defective radio apparatus. Our prices are low and the workmanship is of the highest class obtainable.**

**RADIO SERVICE LABORATORIES, Inc.**  
440 So. Dearborn St. Phone Harrison 2870 Chicago, Ill.

## RADIO BARGAINS

World Wide Short Wave Receivers. Receive from 14 to 550 Meters. Price 6.45  
 Low Power Transmitter adaptable for phone or code. With plug-in coils... \$14.75  
 Auto Radio—Uses 3 224, 2 227 tubes and 1 245 Power Tube, single dial, tremendous volume. Compact. Fits any car. We guarantee this set to perform better than sets selling up to \$150. 20.00  
 B Eliminator, Bone Dry, with 280 tube, 180 volts, will operate up to 10 tube set, fully guaranteed. 6.75  
 AC—A B C Power Packs. 8.75  
 Tubes: 1X type, 30-day replacement guarantee. No. 210, \$2.25; No. 230, \$2.35; No. 281, \$1.85; No. 243, \$1.25; No. 224, \$1.25; No. 227, 75c; No. 226, 65c; No. 171, 75c.

WRITE FOR CATALOGUE  
 Chas. Hoodwin Co., 4240 Lincoln Ave., Dept. A-4, Chicago

## HOTEL AUDITORIUM

Opposite Cleveland's  
**\$15,000,000**  
 Public Auditorium

300 Clean Modern Rooms  
 Each with bath  
**\$2.00 \$2.50 \$3.00**

NO PARKING WORRIES  
 HERE

2 Garages at the Hotel  
 W. H. Byron, Manager  
 East 6th at St. Clair Ave.  
**CLEVELAND**

**AIREX  
RADIO BUYERS' GUIDE**

WORLD WIDE SERVICE

Dealers  
 Servicemen  
 Write for Catalog  
**THE AIREX CO.**  
 67 Cortlandt St.  
 New York N. Y.

## RADIO BOOKS

By JOHN F. RIDER  
 Write for descriptive literature  
**RADIO TREATISE CO., INC.**  
 1440 BROADWAY NEW YORK CITY

## Trained Radio Operators Needed!

Radio operating offers you a pleasant and steady job with good pay. Plenty of opportunities for travel and advancement. You can qualify in a short time in our new and well equipped school under expert instructors.

Write for free booklet "Opportunities in Radio"  
**WEST SIDE YMCA RADIO SCHOOL**  
 Established 1910 110 West 64th Street, New York City

STATEMENT OF THE OWNERSHIP, MANAGEMENT, CIRCULATION, ETC., REQUIRED BY THE ACT OF CONGRESS OF AUGUST 24, 1912

OF CITIZENS RADIO CALL BOOK MAGAZINE AND TECHNICAL REVIEW, published four times yearly at Chicago, Illinois, for October 1, 1930. State of Illinois, County of Cook, ss.

Before me, a notary public in and for the state and county aforesaid, personally appeared Chas. O. Stimpson, who, having been duly sworn according to law, deposes and says that he is the Publisher of the CITIZENS RADIO CALL BOOK MAGAZINE AND TECHNICAL REVIEW and that the following is, to the best of his knowledge and belief, a true statement of the ownership, management (and if a daily paper, the circulation), etc., of the aforesaid publication for the date shown in the above caption, required by the Act of August 24, 1912, embodied in section 411, Postal Laws and Regulations, printed on the reverse of this form, to wit:

1. That the names and addresses of the publisher, editor, managing editor, and business managers are: Publisher, Chas. O. Stimpson, Chicago, Ill.; Editor and Managing Editor, Fred A. Hill, Chicago, Ill.; Business Manager, H. Anheiser, Chicago, Ill.
2. That the owner is (if owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding one per cent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a firm, company, or other unincorporated concern, its name and address, as well as those of each individual member, must be given): Citizens Radio Service Bureau, Chicago, Ill.; Chas. O. Stimpson, Chicago, Ill.; H. Anheiser, Chicago, Ill.; F. A. Hill, Chicago, Ill.
3. That the known bondholders, mortgagees, and other security holders owning or holding 1 per cent or more of total amount of bonds, mortgages, or other securities are (if there are none, so state): There are none.
4. That the two paragraphs next above, giving the names of the owners, stockholders, and security holders, if any, contain not only the list of stockholders and security holders as they appear upon the books of the company but also, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, is given; also that the said two paragraphs contain statements embracing affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner; and this affiant has no reason to believe that any other person, association, or corporation has any interest direct or indirect in the said stock, bonds, or other securities than as so stated by him.
5. That the average number of copies of each issue of this publication sold or distributed, through the mails or otherwise, to paid subscribers during the six months preceding the date shown above is (this information is required from daily publications only).

CHAS. O. STIMPSON, Publisher.  
 Sworn to and subscribed before me this 6th day of October, 1930.  
 ANTON O. LANDES, Notary Public.  
 (My commission expires April 25, 1934.)

# At Last, Homecrafters!

## Here's a Publication Devoted Entirely to Your Needs!



### EVERY TOPIC COVERED

- |                 |                   |
|-----------------|-------------------|
| Woodworking     | Beadwork          |
| Wood-finishing  | Paper-craft       |
| Glass-working   | Toys              |
| Lathe Work      | Wrought Iron Work |
| Model Making    | Archery           |
| Weaving         | Photography       |
| Pewter Work     | Sculpture         |
| Copper Work     | Oil Painting      |
| Jewelry Working | Etching           |
| Leather Work    | Clocks            |

### How you've wished

for such a magazine—you men who delight in making things at home! How you've longed for a magazine devoted entirely to homecraft subjects.

### And here it is—

a 96 page, large-size magazine which deals with every homecraft interest. Covers each subject thoroughly. Profusely illustrated with large photographs and large-scale working drawings. Full instructions for the complete job. No guessing about design or detail and no blue-prints to buy.

### Edited by Men Who Know

—the leaders in each field of homecraft work. New, original designs. Short-cuts in getting unusual results. Above all, every point made clear.

For the man who has had little experience, as well as for the veteran. Not only *telling* how, but *showing* how to make each article. Results that will truly surprise your family and friends.

### Every Subject Treated

Whatever your interest, you'll find it represented here. Covers the whole range of homecraft subjects thoroughly. The year's issue forms a valuable library for constant reference. You'll treasure this magazine. It will be a guide and inspiration to you every day of the year.

### Thousands Have Subscribed

No magazine ever made such rapid advances in circulation. Congratulations come from every side. To see the magazine is to want it for your daily use. Nothing like it ever published before. The one magazine the home craftsman needs. It is his "bible."

### Don't Miss an Issue

Send in your subscription *now*. A single idea from a single issue will be worth far more than the subscription price. And each issue will delight and surprise you. You'll say it's the very best investment you ever made. Moreover, your money back if you are not more than pleased with this most unusual magazine.

## Special Offer

The regular price of Popular Homecraft is 35c single copy at your news-dealer or from us, \$2.00 a year (6 issues), \$3.50 for two years (12 issues). For a limited time only, we will give you a six months' subscription (3 issues) for \$1.00. Attach coupon to remittance. Mail today.

### MAIL THIS COUPON

POPULAR HOMECRAFT  
754 N. Michigan Ave., Chicago, Ill.

Enclosed is \$.....for which send me Popular Homecraft for.....

Name.....

Street.....

Town.....State.....

**POPULAR HOMECRAFT**  
754 N. Michigan Ave. Chicago, Ill.

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# ANNUAL QUEST ONNA RE



Every year the Citizens Radio Call Book Magazine and Technical Review asks its readers a number of questions calculated to show preference of these readers for certain types of editorial matter to appear in future issues.

During the past three years the content of this magazine has been selected in accord with wishes of the majority of readers returning the questionnaires.

We would like a widespread expression on this year's questions so that all classes of readers may be fully represented. Remember, its your book and this is your opportunity of indicating your choice of subjects.

Please fill in the form below, tear out along the dotted line and mail to:

## Citizens Radio Call Book Magazine and Technical Review 508 South Dearborn St., Chicago



1. In your work, which components give you the most trouble? .....Condensers .....Resistors .....Transformers .....Tubes.
  2. What portion of your work is devoted to tube replacements? .....10% .....25% .....50% .....75%.
  3. What tubes do you recommend? .....
  4. Are you part owner, or employed in a radio store? .....Part owner .....Employee.
  5. What factory receivers do you recommend? .....
  6. Do you wish additional curves on receivers other than the present sensitivity, selectivity and fidelity measurements in our magazine? .....Yes .....No.
  7. What service test equipment do you use? .....
  8. Would you consider your service work during this season as profitable? .....Yes .....No.
  9. Does a complete file of all factory schematics materially help in your work? ..... Yes .....No.
  10. Do you service receivers of more than one make? .....Yes .....No.
  11. Have you found the response curves as published by us a help in your sales work? .....Yes .....No.
  12. Where do you secure your replacement parts? .....Mfr. .....Distributor. .....Elsewhere.
  13. Do you still derive pleasure or profit from experimenting with circuit combinations? .....Yes .....No.
  14. Would you prefer receiving each issue of this magazine by mail or from the newsstand? .....Mail .....Newsstand.
- Please check your occupation in the classes shown:

- |   |                              |
|---|------------------------------|
| .....Radio distributor  | .....Dealer service man      |
| .....Radio dealer   | .....Independent service man |
| .....Miscellaneous dealer (such as electrical, music, hardware and automotive radio outlet) | .....Technician              |
|   | .....Experimenter            |

Name.....

Address.....

City..... State.....

Q1931

*Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review*

# MAYO

**For SERVICE MEN  
REPLACEMENT  
TRANSFORMERS, CONDENSERS  
RESISTANCES**

SEND FOR NEW CATALOG—THE MOST COMPLETE EVER PUBLISHED

**MAYO PARTS ARE GUARANTEED FOR SIX (6) MONTHS**

We will repair any defective condenser block, replacing the blown section with guaranteed high voltage condensers, making a flat charge of \$3.00 for any block.

Mayo replacement parts *are not* made from surplus or job lot material. Every part used is manufactured in our own plant.

**MAYO LABORATORIES, Inc.**


*Factory and Office*

280 East 137th Street

New York City



## POWER AMPLIFIERS

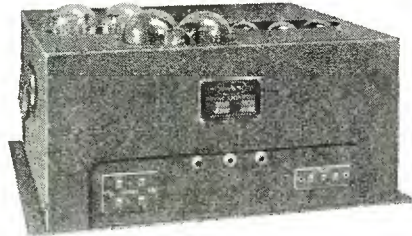

*A Dependable and Powerful Amplifier for Every Sound System Purpose*

The technical merit of Rauland Amplifiers has been proved by thorough independent tests, as well as by actual service. A report on a recent test appears in this issue. This test was made on a stock model by the Laboratory of Citizens Radio Call Book. The results again demonstrate the extraordinary quality of Rauland Amplifiers.

In addition to their high quality in power and fidelity, Rauland Amplifiers are **DEPENDABLE**. They are made by the originators of the famous Rauland-Lyric and All American audio transformer. Behind their design is many years specialization in the science of audio amplification.

**MODERATE IN PRICE**

*[ We welcome the opportunity to supply full technical information. Our staff of expert engineers is eager to help in any sound problem. Write for catalog,—now. ]*

**THE RAULAND CORPORATION**

3341 Belmont Avenue

Chicago, Illinois


# What's NEW in RADIC ?

**H**OW would you like to be posted on the new things and new developments in radio, just as soon as they come out? How would you like to receive mail from the country's leading radio manufacturers, wholesale radio mail order houses and publishers in the radio industry? How would you like to have access to the most complete radio data files ever compiled, containing all the important facts in every phase of radio progress? How would you like to receive regularly, catalogs, folders, circulars, price lists, bulletins, samples galore, etc., keeping you in close touch with the happenings in the radio industry for an entire year? This is only part of our complete service to you.

Would you like to locate a manufacturer of a certain product? Would you like to know the name of a jobber near you handling some particular item you may be interested in? Let us solve these questions for you.

No live radio dealer, fan, amateur, experimenter or professional can afford to be without our comprehensive service. Our business is the nerve center of the radio industry, reaching out everywhere, collecting data from every available source, maintaining the most complete service of its kind in the world.

**This Handy Practical Portfolio FREE!**

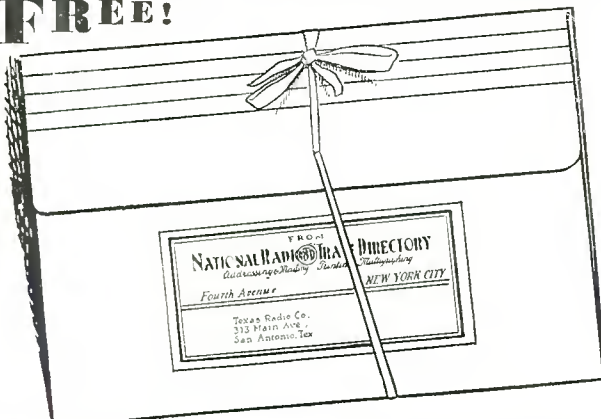

Every subscriber to our service receives a 10 by 12-inch accordion portfolio made of a durable material, in which to save the valuable data we send you.

You will realize that the amount we spend for postage alone does not cover the charge for our service. The \$1 subscription fee barely pays the necessary expenses entailed in mailing.

**all for \$1**

A subscription to our service will actually save you many times the small cost of \$1.00.

If there is any additional information you may require before subscribing, write for further details.

**Just Pin Dollar Bill to this form, fill in and Mail at once!**

Date.....

**NATIONAL RADIO TRADE DIRECTORY,**  
303 Fourth Avenue, New York. Dept. C

Gentlemen:

Enclosed please find \$1.00 for one year's subscription to your "Big Mail" and "Radio" Information Service. It is understood that you are to put my name on your stencil list to receive mailings, including catalogs, bulletins, price lists, samples, etc. I am also to receive free a 10 by 12 inch accordion portfolio.

NAME.....


ADDRESS.....

CITY..... STATE.....

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review
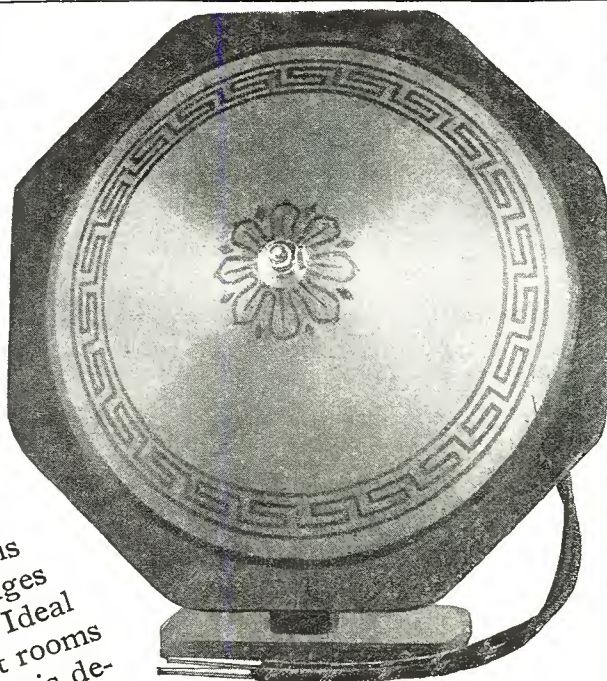
# FREE!

YOU can enjoy the perfect re-  
production and the unusual  
convenience of this Midget Cone  
Speaker **absolutely free**. Manu-  
factured by one of the largest  
manufacturers in the country, this  
speaker has innumerable advantages  
in portability and perfect tone. Ideal  
for apartment use, or in different rooms  
of the house, the Midget Speaker is de-  
lighting thousands who are now using it.



One of these speakers may be yours for  
the cost of the "Call Book" alone,  
by just filling in the coupon be-  
low for one year's subscription to  
the Citizens Radio Call Book  
Magazine. Because the supply is  
**limited**, do not delay in sending  
in your order today!

From  
Elizabeth, N. J.:  
"I received the Mid-  
get speaker today.  
It's great and I am  
well pleased."  
Richard Ogden.

From Ocean Breeze, Cal.,  
W. P. McGuide writes: "I  
received your Midget  
Speaker and sure was sur-  
prised by its performance.  
I play all distant stations  
just as good as any speaker  
I've had, and it performs  
dandy." . . .

The regular annual subscription price  
of the "Call Book" is \$2.00 a year.  
You can get this MIDGET CONE  
SPEAKER ABSOLUTELY FREE  
and the "Call Book" mailed to you  
for a year postpaid, for only \$2.00.

**Mail This Coupon Today!**


CITIZENS RADIO SERVICE BUREAU  
508 S. Dearborn St., Chicago, Ill.

Here's my \$2.00 (Foreign \$2.25), for which please send me CITIZENS  
RADIO CALL BOOK MAGAZINE for one year, beginning  Septem-  
ber, 1930;  November, 1930;  January, 1931;  March, 1931. This sub-  
scription entitles me to a FREE MIDGET LOUD SPEAKER.

Name (Print Plainly).....


Street Address.....

City.....

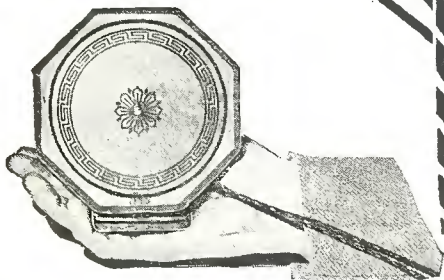

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# RADIO AMATEUR CALL BOOK

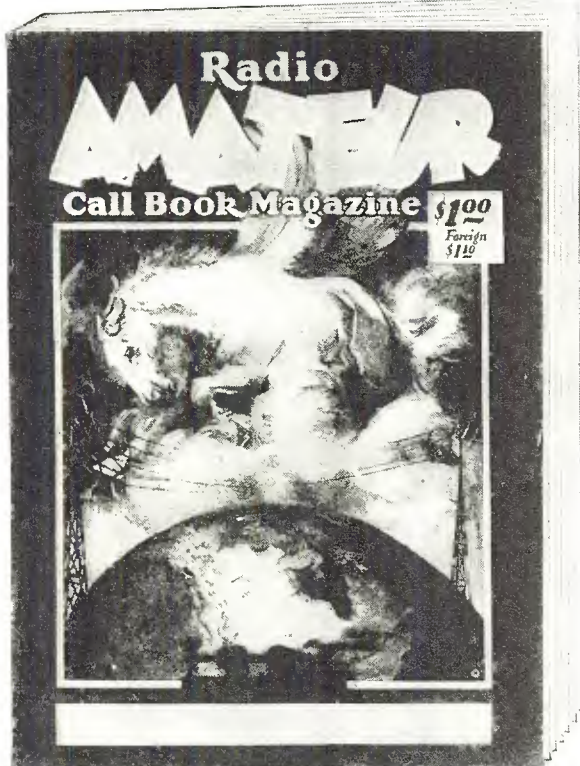

Buy Your Copy at the Following Stores:—

- |  |   |
|--|---|
| <p><b>ARIZONA</b><br/>Nielsen Radio &amp; Sporting Goods Co., 621 N. Central Ave., Phoenix, Arizona.</p> <p><b>CALIFORNIA</b><br/>Inter-City Radio Stores Co., 405 American Ave., Long Beach, Calif.<br/>Natic Book Store, 104 W. 1st St., P.O. Box 417, Los Angeles, Calif.<br/>Radio Manufacturers' Supply Co., 1000 S. Broadway, Los Angeles, Calif.<br/>Radio Supply Co., 912 S. Broadway, Los Angeles, Calif.<br/>Nichol News Co., Modesto, Calif.<br/>Hammond Radio School, 3020 Champion St., Oakland, Calif.<br/>E. A. Gardner &amp; Co., 899 Main St., Riverside, Calif.<br/>I. S. Cohen's Sons, 1025 Market St., San Francisco, Calif.<br/>Geo. W. Mesher, 2949 Sacramento St., San Francisco, Calif.<br/>Offenbach Electric Co., 1452 Market St., San Francisco, Calif.<br/>Warner Brothers, 428 Market St., San Francisco, Calif.</p> <p><b>CONNECTICUT</b><br/>American Radio Relay League, Hartford, Conn.<br/>Hatty &amp; Young, Inc., 119 Ann St., Hartford, Conn.</p> <p><b>DISTRICT OF COLUMBIA</b><br/>Okay Radio Co., 417 11th St., N. W., Washington, D. C.</p> <p><b>ILLINOIS</b><br/>Chicago Radio Apparatus Co., 415 S. Dearborn St., Chicago, Ill.<br/>Goldman's Book Store, 424 S. Dearborn St., Chicago, Ill.<br/>Newark Elec. Co., 226 W. Madison St., Chicago, Ill.<br/>Western News Co., 17-29 E. Austin Ave., Chicago, Ill.<br/>Peoria News Stand, 500 Main St., Peoria, Ill.</p> <p><b>INDIANA</b><br/>Kruse-Radio, Inc., 33 W. Ohio St., Indianapolis, Ind.</p> <p><b>MASSACHUSETTS</b><br/>Tremont Elec. Supply Co., Inc., 228 Tremont St., Boston, Mass.</p> <p><b>MICHIGAN</b><br/>S. S. Kresge Co., Store 1185, 1403 Woodward Ave., Detroit, Mich.<br/>Radio Speculatives Co., 175 E. Jefferson Ave., Detroit, Mich.</p> <p><b>MINNESOTA</b><br/>Findley Elec. Co., Inc., 111 S. 6th St., Minneapolis, Minn.<br/>E. P. Johnson, Waseca, Minn.</p> | <p><b>MISSOURI</b><br/>Birnstein-Applebee Co., 1408 McGee St., Kansas City, Mo.<br/>E. B. MacDowell, 3145 Karnes Blvd., Kansas City, Mo.<br/>Foster Company, 410 Washington Ave., St. Louis, Mo.</p> <p><b>NEW YORK</b><br/>Fort Orange Radio Dist. Corp., 117 N. Pearl St., Albany, N. Y.<br/>McCarthy Bros. &amp; Ford, 75-79 W. Mohawk St., Buffalo, N. Y.<br/>Blau, The Radio Man, Inc., 89 Cortlandt St., New York, N. Y.<br/>J. H. Bunnell &amp; Co., 215 Fulton St., New York, N. Y.<br/>Win. Egert, 179 Greenwich St., New York, N. Y.<br/>Leeds Radio Co., 45 Vesey St., New York, N. Y.<br/>Suu Radio Co., 64 Vesey St., New York, N. Y.<br/>Roy C. Stage, Montgomery &amp; Burt Sts., Syracuse, N. Y.</p> <p><b>OHIO</b><br/>Bergman Tool &amp; Radio Co., 628 Prospect Ave., Cleveland, O.<br/>S. S. Kresge Co., Store 1153, 97 N. High St., Columbus, O.<br/>Kladag Radio Labs., Kline Bldg., Kent, O.</p> <p><b>OREGON</b><br/>Rich's Cigar Store, 6th &amp; Washington Sts., Portland, Ore.<br/>Stubbs Electric Co., Portland, Ore.<br/>Spokane Radio Co., Inc., 528 First Ave., Spokane, Wash.</p> <p><b>PENNSYLVANIA</b><br/>Hall's, 218 Chestnut St., Harrisburg, Pa.<br/>M. &amp; H. Sporting Goods Co., 512 Market St., Philadelphia, Pa.<br/>C. S. Wertsner &amp; Son, 50 N. 13th St., Philadelphia, Pa.<br/>Eugene G. Wile, 10 S. 10th St., Philadelphia, Pa.<br/>Cameradio Co., 430 Wood St., Pittsburgh, Pa.</p> <p><b>TEXAS</b><br/>Fort Worth Radio Supply Co., 104 E. 10th St., Fort Worth, Tex.</p> <p><b>VERMONT</b><br/>Wheeler's Pharmacy, Inc., 27-31 Main St., Springfield, Vt.</p> <p><b>WASHINGTON</b><br/>Spokane Radio Co., 528 1st St., Spokane, Wash.<br/>Wedel Company, 520 Second Ave., Seattle, Wash.</p> <p><b>WISCONSIN</b><br/>Radio Parts Co., 309 State St., Milwaukee, Wis.</p> |
|--|---|

THERE'S MONEY FOR YOU IN

# RADIO



Wonderful opportunity for ambitious men to win success in this fast-growing profession

THE Radio industry is expanding so rapidly that trained men are at a premium. There is a constant, urgent demand for operators—factory superintendents—engineers—service men—designers—salesmen.

There is no better way for you to succeed in this fascinating business than to study the Radio Course of the International Correspondence Schools. This course is new and complete. It was written by practical authorities in this field. It is endorsed by leading radio experts and radio manufacturers.

Quincy J. Workman, of Scranton, Penna., writes that he has "nearly doubled his salary" since he took up the I. C. S. Radio Course. He is now manager of the Radio Department in a large store.

This same course enabled John M. Paynter, of the U. S. Lighthouse Service, Charleston, S. C., to get a position as Radio Operator and Ship's Electrician. Scores of other men in radio factories, laboratories and stores report similar progress.

You, too, can get in on the ground floor if you act quickly. But don't delay too long. Mark and mail the coupon today and let us tell you all about the I. C. S. Radio Course and what it can do for you.

### Mail the Coupon for Free Booklet

INTERNATIONAL CORRESPONDENCE SCHOOLS, Box 8318-E, Scranton, Pa.  
Without cost or obligation, please tell me all about the  
NEW RADIO COURSE

Name \_\_\_\_\_

Street Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

If you reside in Canada, send this coupon to the International Correspondence Schools Canadian, Ltd., Montreal, Canada

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# Index to Advertisers

<b>A</b>		<b>G</b>		<b>P</b>	
Airex Company, The.....	104	General Radio Company.....	98	Pitman & Sons, Isaac.....	94
Allied Radio Corporation.....	97			Polymet Mfg. Corp.....	90
American Sales Company.....	102	<b>H</b>		Popular Homecraft.....	105
American Transformer Co.....	1	Hammarlund Mfg. Co...Second Cover			
Amperite Corporation.....	102	Hammarlund-Roberts, Inc.....	81	<b>R</b>	
Amrad Corporation, The.....	80	Hammer, S.....	88	RCA Institutes, Inc.....	10-11
Audiola Radio Company.....		Hickok Electrical Instrument Co.....	95	Radio Amateur Call Book, Inc.....	109
.....Fourth Cover		High Frequency Laboratories.....	112	Radio College of Canada, Ltd.....	97
Auditorium Hotel.....	104	Hoodwin Co., Chas.....	104	Radio Parts Company, Inc.....	100
<b>B</b>		<b>I</b>		Radio Products Co., The.....	78
Baltimore Radio Co.....	104	Insuline Corp. of America.....	82	Radio Service Lab., Inc.....	104
Belvedere Hotel, The.....	100	International Correspondence		Radio Training Association of	
Browning-Drake Corp.....	98	Schools.....	109	America.....	103
<b>C</b>		International Resistance Co.....	88	Radio Treatise Co., Inc.....	104
Cameradio Co.....	97	<b>J</b>		Rauland Corp., The.....	107
Central Radio Laboratories.....	84	J. M. P. Mfg. Company, Inc.....	84	Readrite Meter Works.....	89
Chicago Salvage Stock Stores.....	103	Jewell Electrical Instrument Co.....	83	Rim Radio Mfg. Co.....	82
Citizens Radio Service Bureau		<b>K</b>		Ronwyn Radio Corp.....	88
(Blue Prints).....	111	Kucker Radio & Elec. Co.....	95	Royal-Eastern Electrical Supply	
Citizens Radio Service Bureau		<b>L</b>		Co.....	101
(Subscription Offers).....		Leiman Radio Co.....	97	<b>S</b>	
.....96-99-103-108		Lincoln Radio Corp.....	9	Samson Electric Co.....	2
Commonwealth Radio Mfg. Co.....	97	Ludy, The Hotel.....	102	Scott Transformer Co.....	7
Coast to Coast Radio Corp.....	102	<b>M</b>		Shallcross Mfg. Co.....	90
Coyne Electrical School.....	3	M. & H. Sporting Goods Co.....	98	Silman Company.....	102
<b>D</b>		Mayo Laboratories, Inc.....	107	Silver-Marshall, Inc.....	85
DeForest Radio Co.....	91	McGraw-Hill Book Company,		Simplimus, Inc.....	94
Dixie, Hotel.....	102	Inc.....	87	St. Charles Hotel.....	100
<b>E</b>		Midwest Radio Corporation.....	97	Stuyvesant Electric Co., Inc.....	92
Electrad, Inc.....	99	Mississippi Valley Radio Co.....	101	Sun Radio Co.....	92
Ellis Electrical Laboratory.....	100	Morrison Hotel.....	100	<b>W</b>	
Essenbee Radio Devices Co.....	87-98	<b>N</b>		Ward Mfg. Company.....	97
<b>F</b>		National Radio Institute.....	4-5	Wedel Company, Inc.....	94
F. & H. Radio Laboratories.....	80	National Radio Trade Directory.....	107	Wellston Radio Corp.....	101
Federated Purchaser.....	8	Nubor Wholesalers.....	97	West Side Y. M. C. A. Radio	
Ferranti, Inc.....	79	<b>O</b>		School.....	104
Filtermatic Mfg. Co.....	90	Oxford Radio Corp.....	93	Western Radio Mfg. Co.....	100
Freed Sales Service Co.....	94			Weston Electrical Instrument	
				Corp.....	Third Cover
				Workrite Radio Corp., The.....	92
				Wright-DeCoster, Inc.....	77



# CALL BOOK BLUE PRINTS

For Service Men, Set Builders and Experimenters

**A**CCURATE, clear and dependable drawings of nearly every known circuit. This, and our one day mailing, makes us the leader in Radio Blueprint Service.

## Factory Built Receiver Schematics

*Drawings listed below are intended for Service purposes only. If the schematic you desire is not shown here, write us for it.*

No. SR24 A. D. Dayton Navigator.....	\$0.50	No. SR96 Grebe Synchrophase AII-1.....	\$0.50
No. SR3 Acme AC7.....	.50	No. SR17 Grebe 7AC.....	.50
No. SR4 Acme AC4.....	.50	No. SR59 Grebe SK-4.....	.50
No. SR1 All-American Mohawk 6.....	.50	No. SR40 Gulbransen Nine-in-Line.....	.50
No. SR2 All-American Mohawk 8.....	.50	No. SR16 Howard Green Diamond 8.....	.50
No. SR174 All-American Mohawk 96.....	.50	No. SR56 Howard SG. A.....	.50
No. SR21 American-Bosch 28 and 29.....	.50	No. SR118 Jesse French Jr. "G".....	.50
No. SR73 American-Bosch 48.....	.50	No. SR77 Kellogg 525.....	.50
No. SR22 Amrad 70 A. C.....	.50	No. SR98 Kennedy 10.....	.50
No. SR44 Amrad 81.....	.50	No. SR48 Kennedy 20.....	.50
No. SR106 Amrad 84.....	.50	No. SR81 Kennedy 26.....	.50
No. SR80 Apex 48 Chassis.....	.50	No. SR81 King Model J.....	.50
No. SR108 Apex Series 31.....	.50	No. SR8 Kolster K20; K22; K25 and K27.....	.50
No. SR28 Atwater-Kent 38.....	.50	No. SR45 Kolster K21; K23; K24 and K28.....	.50
No. SR51 Atwater-Kent 55 & 55C (Cap. Coupled).....	.50	No. SR72 Kolster K43.....	.50
No. SR52 Atwater-Kent 55 & 55C (Inductive Coupled).....	.50	No. SR65 Kyelectron 70.....	.50
No. SR114 Atwater-Kent 66.....	.50	No. SR88 Majestic Super "Classics" 50.....	.50
No. SR79 Audiolia 31.....	.50	No. SR7 Majestic (Grigsby-Grunow) 70.....	.50
No. SR111 Audiolia Super 1931.....	.50	No. SR55 Majestic (Grigsby-Grunow) 90B.....	.50
No. SR112 Audiolia Junior.....	.50	No. SR84 Majestic (Grigsby-Grunow) 130-A.....	.50
No. SR12 Balkeit A.....	.50	No. SR26 Philco 86-82.....	.50
No. SR94 Bosch Auto Radio 80.....	.50	No. SR60 Philco 95.....	.50
No. SR109 Bosch 58.....	.50	No. SR104 Radiette F-14.....	.50
No. SR117 Bosch 60.....	.50	No. SR102 RCA 44.....	.50
No. SR10 Brenner-Tully 7-70.....	.50	No. SR30 RCA 60.....	.50
No. SR75 Brenner-Tully 81 & 82.....	.50	No. SR64 RCA 66.....	.50
No. SR23 Brunswick 3KRO.....	.50	No. SR92 RCA 80.....	.50
No. SR71 Brunswick S-14.....	.50	No. SR107 RCA 48.....	.50
No. SR86 Brunswick 15, 22, 32, 42.....	.50	No. SR115 Sentinel 11; 15; 16; 12 and 12K.....	.50
No. SR78 Clarion 50.....	.50	No. SR35 Silver-Marshall 30.....	.50
No. SR29 Colonial 31AC.....	.50	No. SR53 Silver-Marshall 30-B.....	.50
No. SR95 Colonial 33 & 34 A. C.....	.50	No. SR82 Silver-Marshall 35-A.....	.50
No. SR47 Columbia (Chicago) SGS.....	.50	No. SR105 Silver Super 36-A.....	.50
No. SR103 Crosley 53 & 54.....	.50	No. SR27 Sledge (Continental) 9.....	.50
No. SR5 Crosley 608 Gembox.....	.50	No. SR46 Sledge (Continental) R-20.....	.50
No. SR6 Crosley 705 Showbox.....	.50	No. SR25 Sonora Delux 5R.....	.50
No. SR41 Crosley Jewelbox 704B.....	.50	No. SR91 Sparton 600; 610 & 620.....	.50
No. SR57 Crosley 40S, 41S, 42S & 82S.....	.50	No. SR9 Sparton ACS9.....	.50
No. SR67 Crosley "Roamie" (Auto Radio).....	.50	No. SR58 Sparton 931.....	.50
No. SR83 Crosley 77.....	.50	No. SR63 Sparton 589.....	.50
No. SR11 DayFan 5080.....	.50	No. SR36 Spitzdorf F-175.....	.50
No. SR66 Delco Auto Radio.....	.50	No. SR45 Steinite 261.....	.50
No. SR87 Delco Police Short Wave Receiver 3003.....	.50	No. SR76 Steinite 70, 80, 95.....	.50
No. SR99 Edison R6 & R7.....	.50	No. SR34 Stewart-Warner 900.....	.50
No. SR49 Edison R4, R5, C4.....	.50	No. SR62 Stewart-Warner 950.....	.50
No. SR33 Erla DuoConcerto R-2.....	.50	No. SR85 Stewart-Warner R-100A, B & E.....	.50
No. SR50 Eveready Series 50.....	.50	No. SR93 Stromberg-Carlson 12 & 14.....	.50
No. SR13 Fada 7AC.....	.50	No. SR18 Stromberg-Carlson 635 & 636.....	.50
No. SR70 Fada 35 & 35Z.....	.50	No. SR54 Stromberg-Carlson 846.....	.50
No. SR19 Federal II.....	.50	No. SR97 Temple S-60, S-80 & S-90.....	.50
No. SR20 Freed-Eisemann NR-80.....	.50	No. SR69 Transitone Auto Radio.....	.50
No. SR14 Freshman 2-N-12.....	.50	No. SR39 U. S. Radio & Television 37.....	.50
No. SR92 General Electric II-31.....	.50	No. SR119 Vitatone 54 (Zaney-Gill Corp.).....	.50
No. SR107 General Electric T-41.....	.50	No. SR101 Victor Micro-Synchronous R-35; R-39 & RE-57.....	.50
No. SR68 General Motors A.....	.50	No. SR61 Victor R-32, RE45 & R52.....	.50
No. SR32 Gillfillan 100.....	.50	No. SR92 Westinghouse WR-5.....	.50
No. SR12 Graybar 600.....	.50	No. SR107 Westinghouse WR-4.....	.50
No. SR62 Graybar 700.....	.50	No. SR97 Zenith 71; 72; 73 & 77.....	.50
No. SR107 Graybar 67S.....	.50	No. SR43 Zenith 52.....	.50

## Public Address Systems

No. SR100 Amer-Tran PA-86.....	\$0.50	No. SR88 Webster (Racine, Wis.) A37-50.....	\$0.50
No. SR90 Silver-Marshall 692.....	.50	No. SR89 Webster (Chicago) DII-250.....	.50

## Kit Receiver Blueprints

Full sized blueprints are available of any circuit ever published in the Call Book. Space permits listing only a few of the more popular ones. Write us if the desired print is not shown here.

No. 14 Browning-Drake 4 Tube Receiver Using Audio Frequency Amplification.....	\$1.00	No. 123 World's Record Super Ten & Power Pack (6 drawings).....	\$1.00
No. 32 Scott "World's Record" Super Eight.....	1.00	No. 147 Custom-built Model Madison-Moore International One-Spot A. C. Sub-panel Job (6 drawings).....	1.00
No. 56 Improved Browning-Drake.....	1.00	No. 167 Scott World's Record SG Nine "Power Pack Operated" (4 drawings).....	1.00
No. 68 Improved Remler 45 K. C. Super-heterodyne Receiver (5 drawings).....	1.00	No. 179 Lincoln S-80 One-Spot Super—(3 drawings).....	1.00
No. 73 Magnaformer Super-heterodyne Receiver (5 drawings).....	1.00	No. 231 Custom-built Model World's Record Shield Grid A. C. 10 (4 drawings).....	1.00
No. 99 Magnaformer 9-S A. C. (5 drawings).....	1.00	No. 246 Pilot Super-Wasp Short Wave Receiver (3 drawings).....	1.00

## Graphic Wiring Diagrams

No. 101 World's Record Economy Super 8.....	\$0.60	No. 213 Junior 4 Tube Receiver.....	\$0.10
No. 174 Sargent-Rayment Seven Receiver.....	.50	No. 221 Modulated Oscillator.....	.60
No. 195 Junior 2 Tube Receiver.....	.10	No. 236 S-M 722 A. C. Screen Grid Receiver.....	.60
No. 196 Aero A. C. Short Wave Converter.....	.60	No. 237 S-M 735 Short Wave Receiver, A. C.....	.60
No. 202 Silver-Marshall 730 Four Tube Receiver.....	.60	No. 244 S-M S. G. A. C. 712 Rec. (to be used with 677 Power Pack).....	.60
		No. 245 S-M 677 Power Pack (to be used with 712 Receiver).....	.60

## Schematic Wiring Diagrams Primarily for Service Work


No. 174a Sargent-Rayment Seven Receiver.....	\$0.50	No. 238a Lincoln S-40 Screen Grid A. C. Super.....	\$0.50
No. 187a Citizens Special Short Wave Receiver.....	.50	No. 239a C. R. Lantz "Seven Seas" Console Receiver.....	.50
No. 213a Magnaformer 1929 A. C. Super.....	.50	No. 244a S-M S. G. A. C. 712 Rec. (to be used with 677 Power Pack).....	.50
No. 221a Modulated Oscillator.....	.50	No. 245a S-M Power Pack (to be used with 712 Receiver).....	.50
No. 223a Silver-Marshall 720 A. C. Shield Grid Six.....	.50	No. 249a Hammarlund-Roberts Hi-O 30.....	.50
No. 225a Hollister A. C. Super Eight.....	.50	No. 254a Lincoln DeLuxe Ten A. C. S. G. Receiver.....	.50
No. 234a HPL Mastertone Receiver, A. C.....	.50	No. 255a Silver-Marshall 722 S. G. D. C. Receiver.....	.50
No. 236a S-M 722 A. C. Screen Grid Receiver.....	.50	No. 260a Lincoln DeLuxe 31.....	.50
No. 237a S-M 735 Short Wave A. C. Receiver.....	.50	No. 270a Silver-Marshall 738.....	.50

Any of the above blue prints will be sent postpaid by return mail upon receipt of the proper amount. C. O. D. orders not accepted.

**CITIZENS RADIO SERVICE BUREAU** 508 SOUTH DEARBORN STREET 7TH FLOOR—CHICAGO, ILLINOIS

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

**NEW  
IN  
EVERY  
WAY**

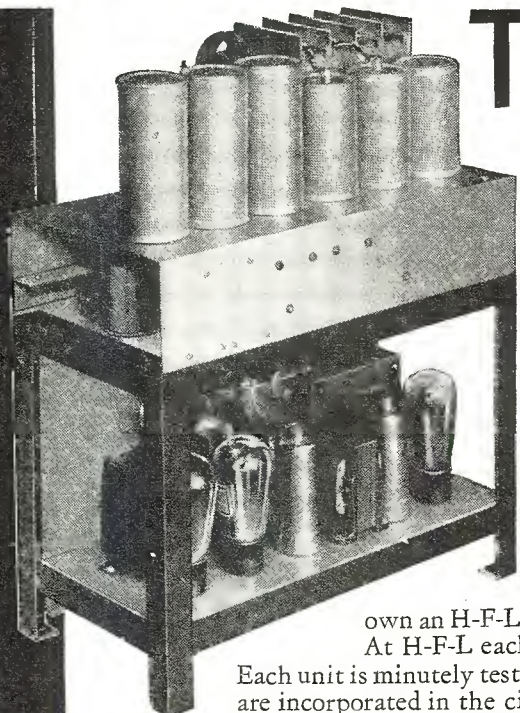

# The Difference is in the Making!

## The Advantage is Yours the H-F-L Way

The fine things are always hand made. This is especially true in radio. The art advances so fast, that huge factory-set-ups for mass manufacture cannot keep pace. Only a few may ever

own an H-F-L—such quality receivers cannot be built in quantity. At H-F-L each receiver is hand made to the precision of a watch.

Each unit is minutely tested before inclusion in the set. The latest discoveries are incorporated in the circuits. The most advanced designs are followed in the arrangement of the chassis. Thus, your H-F-L receiver gives you all that radio has to offer. Buy H-F-L in these great expectations—you will not be disappointed!

# THE LITTLE GIANT MASTERTONE

## MAKES ITS FIRST BOW TO FAME IN THE FIELD OF FINE RADIO

**HOPKINS BAND REJECTOR SYSTEM**  
Entirely new! New in circuit arrangement—new in chassis design. America's outstanding builders of fine radio now produce a supremely fine low-priced superheterodyne receiver for everybody. A real sensation is this set. It challenges all comparison. Quick as a flash, it falls into tune with the station selected. With microscopic fineness, it accepts that signal to the exclusion of everything else in the air. Even background noises cannot creep in. With bounding power, it reaches to the outposts of the world in its reception range. With enrapturing tone, it transports you to new heights of musical enjoyment. New miracles of this wizard-like art are brought to produce an entirely new superlative performance. Yet, all this you get at surprisingly low cost. No more to spend than for ordinary radio!

### Sensational New Circuit!

To combine 10-kilocycle selectivity with beautiful tone quality has been the dream of every radio engineer. But, not until the perfection of the Hopkins Band Rejection System was this possible. Now in the Mastertone this is accomplished. Far away stations, on bands adjacent to powerful locals, are brought in with clarity, volume and full strength. No compromising of tonal reproduction by side band clipping. Tune to the station desired and all the energy in that channel is accepted and reproduced. All adjacent stations are entirely avoided. Reception is *precise*,

**WORLD WIDE RECEPTION POWER**  
*definite*, unhampered! The Hopkins Band Rejector System is exclusive with H-F-L and is found in no other receivers.

### Extreme Selectivity

The full value of screen grid tubes brought to perfection. Reach out to the far corners of the earth for unforced, clear-as-a-bell reception. The sensitivity is greater than 1 micro-volt per meter—all over the dial. This sensational circuit arrangement always provides the reliable 10-kilocycle separation at all volumes—high or low, at all wave lengths, on local or far distant stations.

### Single-Unit Chassis

A cascaded, one-unit chassis of great ruggedness. Built like a skyscraper of steel and aluminum. The dynamic speaker is integral with the chassis. All delicate parts enclosed and protected from accidental injury. All units securely anchored so that after years of use it still functions perfectly. Very compact, measuring only 21 inches high, 16 inches wide and 8 inches deep. Ideal for use in console or for inbuilding in the wall.

### Beautiful Console Model


This wonder receiver is now available in a modern, walnut console in striking design. Neat, compact, but a fitting companion to the finest furnishings the home might have. And, best of all, it comes at

**SINGLE UNIT CHASSIS**  
a price lower than the market has ever offered. Here we have a complete, ultra powerful, beautiful tone superheterodyne receiver at a cost even less than must be paid for an ordinary trf set when secured through the usual channels.
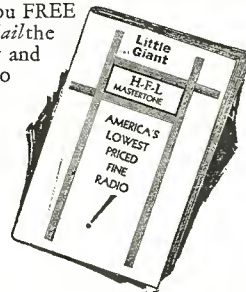
### Write for Whole Story

Learn how you can test this record-breaking, sensational new receiver and see and hear for yourself. Know the amazing price. Find out about the great new circuit embodied in it. Hear the enthusiastic praise of those who have already tuned it! All this will be brought to you in a little Brochure which will be sent to you FREE on request. Mail the Coupon now and soon begin to enjoy radio in all its possibilities.

**DEALERS:**  
Write for Special H-F-L Franchise.



**HIGH FREQUENCY LABORATORIES**  
Dept. B241, 3900 No. Claremont Ave.  
CHICAGO

High Frequency Laboratories, Dept. B241,  
3900 No. Claremont Ave., Chicago, Ill.

Without cost or obligation to me, please send me a copy of your new Brochure describing the New Little Giant Mastertone and your liberal selling policy.

Name.....  
Address.....  
City.....State.....

**AMERICA'S LOWEST PRICED FINE RADIO**  
**H-F-L « MASTERTONE »**  
**A Super-Heterodyne**  
**WITH THE HOPKINS BAND REJECTOR SYSTEM**

Tell 'Em You Saw It in the Citizens Radio Call Book Magazine and Technical Review

# IT PAYS TO BUY WESTONS



## MODEL 565

Model 565 is practically a radio service laboratory—the most complete test set designed for radio servicing. (Includes R. F. Oscillator).

### Service Scope of Model 565

Model 565 makes the required tests on every modern radio receiver. This includes D. C. sets with reversed filaments; Power Transformers; A. C. line and all heater voltages; Battery voltages and currents; Resistance and Continuity of Circuits; Condensers; Speaker-coil currents. R. F. Oscillator permits tests independent of broadcast signals. Model 565 checks every type tube—A.C., D.C., Pentode and both plates of Rectifier at the same time; all filament, heater, cathode voltages; bias, control grid and plate voltages; plate and screen currents;—operating directly from any 50-60 cycle 90-135 volt A.C. line.

### Equipment of Model 565

8 range A.C. VOLT-AM-MILLIAMMETER controlled by 9 point Bi-polar switch; 12 range D.C. VOLT-OHMMETER controlled by 23 point Bi-polar switch with index markings; 3 range D.C. MILLIAMMETER controlled by 3-way toggle switch; DIRECT READING OHM-METER; R.F. OSCILLATOR; CONDENSER METER; POLARITY REVERSING SWITCH;  $4\frac{1}{2}$  volt self-contained BATTERY; and for external tests, BINDING POSTS for all ranges, and LEADS.

To cooperate with those temporarily affected by the current business recession, Weston makes it possible to obtain the best in radio service equipment on a convenient payment plan. Write for details.

WRITE FOR CIRCULAR H H

**WESTON ELECTRICAL INSTRUMENT CORPORATION**  
574 Frelinghuysen Avenue



## MODEL 566


A two meter test set—inexpensive, light, convenient, and rapid in operation—designed for radio servicing in the home.

### Service Scope of Model 566

Model 566 checks all type tubes under same conditions as exists when in the radio set. Checks all model radio sets. Checks Transformers; Line voltage; filament or heater current and voltages; cathode, bias and control grid voltages; plate current and voltage; screen currents; both plates of full-wave rectifier tubes; battery voltages; resistance and continuity of circuits; condensers and speaker-coil currents.

### Equipment of Model 566

9 range A.C. VOLT-AM-MILLIAMMETER controlled by dial switch; 10 range D.C. VOLT-OHM-MILLIAMMETER controlled by 23 point Bi-polar switch with index markings; DIRECT READING OHMMETER; CONDENSER METER; OUTPUT METER (Rect. type); POLARITY REVERSING SWITCH;  $4\frac{1}{2}$  volt self-contained BATTERY; and for external tests, BINDING POSTS for all ranges, and LEADS.

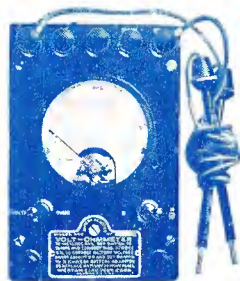

**MODEL 564**—Model 564 is a compact inexpensive VOLT-OHMMETER for voltage and resistance measurements and continuity tests.

Used in radio repair shops, factories, and laboratories.

### Description of Model 564

Model 564 has 6 D.C. ranges—600/300 30 3 volts (all 1000 ohms per volt) and 0-100,000, 0-10,000 ohms; a  $4\frac{1}{2}$  volt "C" battery and 30-inch test cables with prods. All ranges are brought to binding posts. 2 toggle switches permit change from voltmeter to ohmmeter, and from 100,000 to 10,000 ohm range. Size:  $5\frac{1}{2}$  x  $3\frac{3}{8}$  x  $2\frac{1}{8}$  inches. Weight (complete): 2.3 lbs.

# AUDIOLA


KNOWN FOR ITS TONE

**9** YEARS' EXPERIENCE IN MAKING FINE RADIO RECEIVERS IS THE FOUNDATION FOR AUDIOLA'S NEW

*Genuine Screen Grid*

**SUPERHETERODYNE**

Licensed by R. C. A.

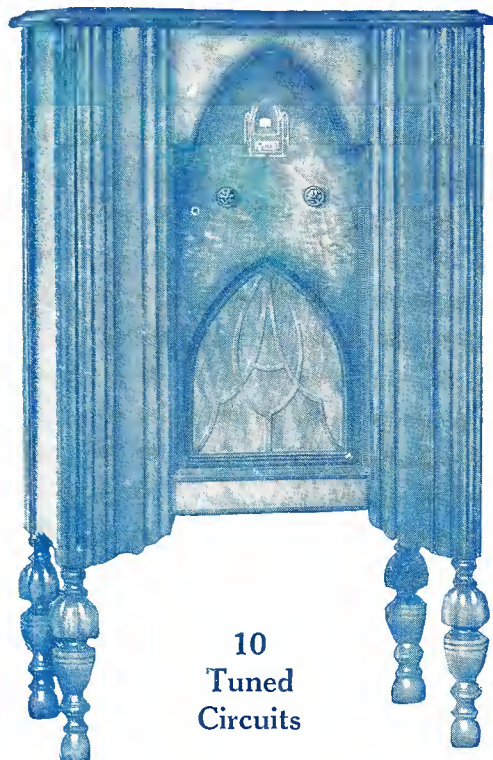

10  
Tuned  
Circuits

DEALERS are finding every day the immense advantage in selling a radio receiver that satisfies all requirements as to sensitivity and selectivity and fidelity.

In the past the dealer has had no method of predicting the performance of his receiver line. Today he has a yardstick by means of which all sets may be measured and can devote his energies to selling that receiver secure in the knowledge that the measured performance will be maintained.

Response curves on the AUDIOLA SUPERHETERODYNE have recently been taken and the results are shown in the Response Curve Section of this magazine. Dealers are urged to acquaint themselves with these curves.

Note particularly the sensitivity and selectivity curves; the former to learn the ability of the receiver to pick up distant signals; the latter to discriminate between two stations on the air. Selectivity is more important than ever on the eve of super power recently authorized for many of the better known broadcasting stations. Fidelity curves give an idea of the faithfulness with which the desirable frequencies in the musical range are expressed in the speaker.

*A receiver that fulfills every expectation—that checks with the yardstick of radio, will be the BEST SELLER for 1931*

**Priced from \$107 Up**

*Write Us Today for Our Special Dealer's Proposition!*

## AUDIOLA RADIO CO.

430 SOUTH GREEN STREET

CHICAGO, ILLINOIS

**9 YEARS OF SUCCESSFUL RADIO MANUFACTURING**