

# HAM TIPS



A PUBLICATION OF THE TUBE DEPARTMENT · RCA · HARRISON, N. J.

Volume XI, No. 1

Spring, 1951

## Compact 2-Meter Civil-Defense Transmitter Employs RCA Miniatures and Popular 2E26

By

George D. Hanchett, Jr., W2YM\*

When the FCC reserved sections of the two-meter and other bands for Civil-Defense operations in the event of war, public-spirited amateurs recognized the need for compact mobile and fixed-station equipment. In order to help fill this need, the transmitter described in this article was designed and constructed. This versatile two-meter transmitter meets the requirements of extreme reliability, minimum stand-by power consumption, ease of adjustment, and portability. It may be operated either from a 117-volt ac line or from a 6-volt storage battery; this transmitter provides an output of approximately 10 watts.

AS SHOWN in the schematic diagram on pg. 4, a 6AK6 is employed as a crystal oscillator-tripler stage. Starting with an 8-Mc crystal, this stage provides a 24-Mc signal to the second 6AK6 which triples to 72 megacycles. A 5763 miniature beam-power amplifier is used as a doubler and a 2E26 operates as the final amplifier at 144 megacycles. For maximum power efficiency, a 1635 is used as a class B modulator. A 6N7-GT may be employed to obtain the same modulator output, but the 1635 has the advantage of requiring less heater power and a lower zero-signal plate current. The first audio amplifier utilizes one half of

\*RCA Tube Dept., Harrison, N. J.

Fig. 1. A compact Civil-Defense transmitter for fixed-station or mobile operation.



a 12AU7 as a grounded-grid stage to obtain a good match to the carbon microphone, and also to provide a convenient source of voltage for the microphone.

### Meter Circuit

Metering the grid circuits of the frequency multipliers and the final amplifier, and the plate circuits of both the final amplifier and the class B modulator is accomplished by means of an external test meter. This arrangement permits the use of a single meter for adjusting all of the transmitters in a Civil-Defense network.\*

As shown in Fig. 2, the test-meter circuit consists of a 0-1 ma meter, a two-section six-position switch, and two resistors. Connection of the test meter to the transmitter is made by means of a cable and plug.

When the meter switch is set to any one of the first three positions shown in Table I, the meter and the 910-ohm resistor, in series, are connected across a 10-ohm shunt ( $R_{22}$  for position 4, or  $R_{23}$  for position 5) to indicate the final-amplifier or modulator plate current, respectively. The meter deflection is proportional to the flow of grid current.

In positions 4 and 5 of the meter switch, the meter and the 910-ohm resistor, in series, are connected across a 10-ohm shunt ( $R_{22}$  for position 4, or  $R_{23}$  for position 5) to indicate the final-amplifier or modulator plate current, respectively. The test meter is connected between ground and a 1N34 rectifier in the antenna-coupling circuit in position 6 of the meter switch.

### Construction

The transmitter is constructed on a 7 by 11 by 2-inch chassis; it is so arranged that the rf section is on one side of the chassis (refer to Fig. 3) and the modulator and power plugs on the other side. Separating these two sections, on the underside of the chassis, is a strip of aluminum to which a resistor board is fastened. All of the resistors, with the exception of the 5763 grid resistor,  $R_{10}$ , are mounted on this board. Such mechanical support of the resistors provides the necessary ruggedness for mobile operation.

By-passing in the frequency multipliers and the final amplifier is accomplished with single- and dual-section ceramic capacitors. The metering leads are brought to an octal meter jack for con-

\*Each unmetred transmitter may be monitored during transmission by a pair of headphones connected to monitor jack  $J_5$  in the antenna-coupling circuit.

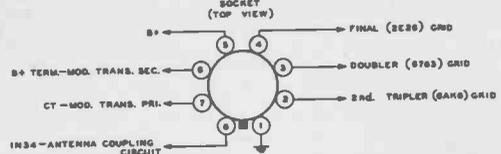
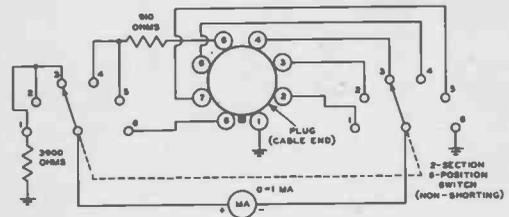


Fig. 2. Test-meter circuit.

Table I — Test-Meter Calibration Data

Switch Position	Indication	Full-scale Deflection
1	2nd tripler (6AK6) grid current	5 ma
2	Doubler (5763) grid current	5 ma
3	Final (2E26) grid current	5 ma
4	Final (2E26) plate current	100 ma
5	Class B mod. plate current	100 ma
6	RF power output	15 watts

nection to the external test meter. Transformer  $T_1$  is a standard RCA TV sound if unit, 206K1, and  $L_1$  is a stagger-tuned video if coil, 202L1.

The arrangement of the components in the output tank circuit is shown in Fig. 5. The bracket for this tank circuit is made from a 4 by 5-inch piece of aluminum. The output link coil is connected to a coaxial relay so that in the non-energized position, the antenna will be connected to the associated receiver.

### Adjustment

The tuning of the transmitter is a simple process. With only the two 6AK6's in place, connect the transmitter to the 300-volt supply. Connect the test meter to the unit and set the selector switch to the second tripler-grid position. Vary the inductance of  $L_1$  to obtain oscillation, and then adjust the primary and secondary of  $T_1$  for maximum meter deflection. The grid current of the second 6AK6 should be approximately 2 ma.

Insert the 5763 into the transmitter and adjust  $L_2$  to resonance as indicated by maximum 5763 grid current when the test meter is set in position 2. At resonance the grid current of the 5763 should be approximately 1 ma. Adjust-

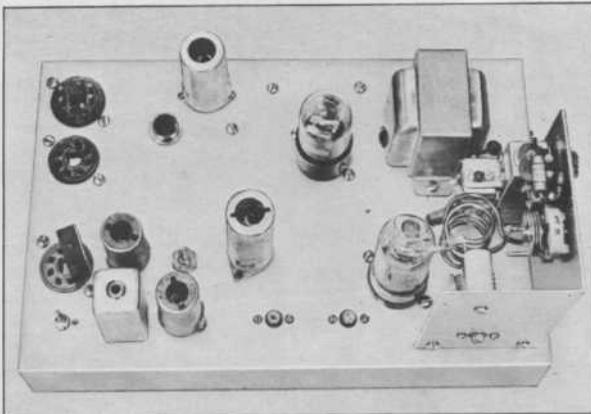


Fig. 3. Top view of the transmitter.

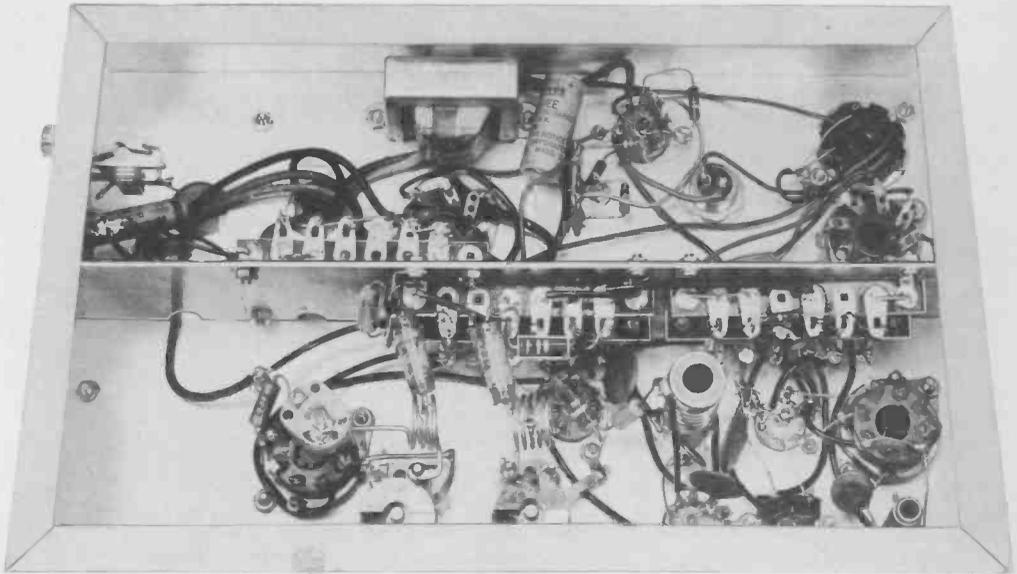


Fig. 4. Bottom view of the transmitter. The resistor board provides the necessary mechanical support for mobile operation.

ment of  $L_2$  should be made as rapidly as possible, so that the 5763 plate circuit (which will probably not be in resonance) does not draw excessive current for a sustained period.

Switch the test meter to the 2E26 grid position (3) and plug in the 2E26. To protect the 2E26 during the initial tune-up, disconnect the series screen resistor,  $R_{16}$ , from the plate supply. Then adjust  $C_{14}$  and  $C_{15}$  for maximum grid current in the 2E26; the 2E26 grid current should be approximately 1.5 to 2.0 ma.

At this point in the initial tuning procedure, the final amplifier should be neutralized as follows: rotate  $C_{20}$  through its entire range and observe the downward kick of the test meter (switch set in position 3, the 2E26 grid-current position). Then adjust neutralizing capacitor  $C_7$  until the downward deflection of the meter needle is minimized when  $C_{20}$  is rotated through its range. Reconnect the screen-grid resistor to the plate supply and set the meter selector switch to the 2E26 plate-current position (4). Capacitor  $C_{20}$  should then be adjusted for resonance.

After these adjustments have been made, connect the antenna to the transmitter and set the test meter switch to the output position (6). Capacitor  $C_{21}$  should be adjusted for maximum output. When a 52-ohm coax cable is used, a meter reading of approximately 0.4 ma indicates 10 watts of rf power. Finally, readjust  $L_1$ ,  $T_1$ ,  $C_{14}$ ,  $C_{15}$ , and  $C_{20}$  for maximum power output.

The 1635 class B modulator tube and the 12AU7 speech-amplifier tube should then be plugged in and the microphone connected to the transmitter.

#### AC Power Supply


The power supply for ac operation is shown to the right of the transmitter unit in Fig. 1; the schematic diagram for this supply is shown in Fig. 7. This supply is constructed on a 5 by 10 by 3-inch chassis. It employs a conventional full-wave rectifier and filter circuit, plus a selenium rectifier which supplies 6 volts dc for relay operation. The relay shown in Fig. 7 is a control

relay which simultaneously grounds the center tap of the high-voltage winding of the power transformer and applies energizing voltage to the antenna relay when the microphone switch is closed.

#### Genemotor Power Supply

For mobile and emergency operation, the power unit shown in the upper left-hand corner of Fig. 1 should be connected to the octal chassis

Fig. 5. Closeup view of the tank circuit.

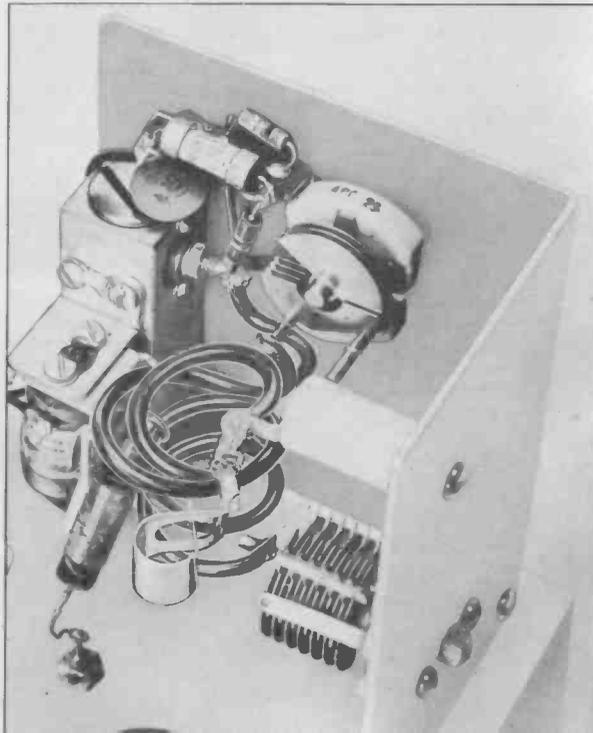

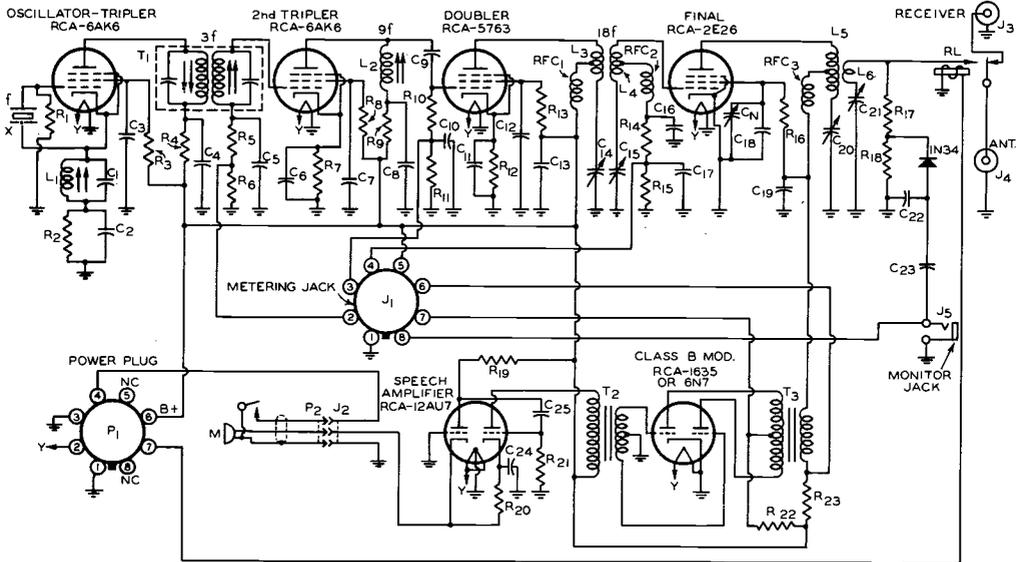


Fig. 6. Schematic diagram of the transmitter.

connector P<sub>1</sub>, located on the transmitter. This supply employs a Genemotor which operates from a 6-volt storage battery to provide a plate voltage of 300 volts. The output of the Genemotor is filtered with a single 4- $\mu$ f capacitor. A control relay is also included in this supply as shown in the schematic diagram, Fig. 8. When the microphone switch is pressed, this relay connects the ungrounded input terminal of the Genemotor to the "hot" side of the storage battery, and simultaneously applies energizing voltage to the antenna relay. A 5 by 9½ by 2-inch chassis is required for the construction of this power supply.

#### Installation Notes (Mobile Operation)

For mobile operation, the transmitter and the Genemotor supply should be fastened securely to a shock-mounted support. A piece of ¾-inch plywood and four shock mounts will serve as a simple vibration-proof mounting.

Connection to the car battery should be made through a heavy conductor to minimize voltage drop. If the transmitter is installed in the trunk of the car, a No. 4 flexible cable is recommended; a No. 6 conductor is adequate if the length is four feet or less.

Check the polarity of the auto battery and de-

termine the polarity of the grounded terminal. As shown in Fig. 8, the negative input terminal of the Genemotor is grounded. If the positive terminal on the battery is grounded, reverse the input connections to the Genemotor.

Since the details of the mobile installation will vary with the type of vehicle and also with individual preferences, the control circuit for the application of heater voltage has not been included in the dc supply. Heater voltage should be controlled by means of a 6-volt, SPST relay with ¼-inch contacts connected in series with the "A hot" input terminal of the Genemotor supply and the ungrounded battery terminal. Energizing voltage to the coil of this relay may be controlled by a SPST toggle switch located at the operating position.

#### Operation

With the ac power supply connected to P<sub>1</sub>, heater voltage will be applied to the tubes in the transmitter when the power supply switch is turned on. Closing the microphone push-to-talk switch will simultaneously apply plate voltage to the transmitter tubes and cause the antenna-transfer relay to operate, regardless of the power supply employed.

Table II — Currents and Voltages for Normal Operation\*

Meter Indication	Oscillator Tripler (6AK6)	Second Tripler (6AK6)	Doubler (5763)	Final (2E26)	AF Amp (½ 12AU7)	Driver (½ 12AU7)	Modulator (1635)
E <sub>b</sub> (v)	275	265	300	300	300	300	300
I <sub>b</sub> (ma)	12	15	35	60	4	7	6 (min.) 40 (max.)
I <sub>c2</sub> (ma)	2.3	3.0	2.5	5.0	—	—	
E <sub>c2</sub> (v)	195	165	250	200	—	—	—
I <sub>c1</sub> (ma)	0.7	2	0.9	1.6	—	—	—
E <sub>k</sub> (v)	12	20	1.5	0	4	11	0

\* For  $\pi$  output of 10 watts.

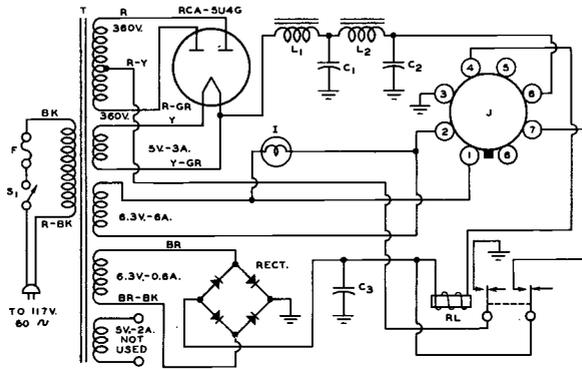


Fig. 7. Schematic diagram of the power supply for the fixed-station installation.

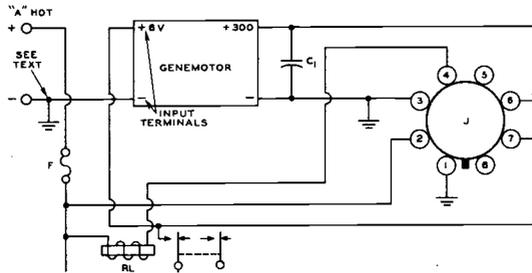


Fig. 8. Schematic diagram of Genemotor power supply for the mobile installation.

**Transmitter**

- C<sub>1</sub> 100  $\mu$ f.
- C<sub>2</sub> 0.005  $\mu$ f, disc ceramic.
- C<sub>3</sub> Twin 0.004  $\mu$ f, disc ceramic.
- C<sub>4</sub> 0.005  $\mu$ f, disc ceramic.
- C<sub>5</sub> Twin 0.004  $\mu$ f, disc ceramic.
- C<sub>6</sub> 0.005  $\mu$ f, disc ceramic.
- C<sub>7</sub> 10  $\mu$ f.
- C<sub>8</sub> 0.005  $\mu$ f, disc ceramic.
- C<sub>9</sub> 10  $\mu$ f.
- C<sub>10</sub> 0.005  $\mu$ f, disc ceramic.
- C<sub>11</sub>, C<sub>12</sub> Twin 0.004  $\mu$ f, disc ceramic.
- C<sub>13</sub> 0.005  $\mu$ f, disc ceramic.
- C<sub>14</sub> 25  $\mu$ f, air padding.
- C<sub>15</sub> 25  $\mu$ f, air padding.
- C<sub>16</sub> 100  $\mu$ f.
- C<sub>17</sub> 0.005  $\mu$ f, disc ceramic.
- C<sub>18</sub> 47  $\mu$ f.
- C<sub>19</sub> 470  $\mu$ f, feed-through type.
- C<sub>20</sub> 25  $\mu$ f, air padding.
- C<sub>21</sub> 25  $\mu$ f, air padding.
- C<sub>22</sub> 0.005  $\mu$ f, disc ceramic.
- C<sub>23</sub> 0.01  $\mu$ f, 400 wv.
- C<sub>24</sub> 25  $\mu$ f, 25 wv, electrolytic.
- C<sub>25</sub> 0.005  $\mu$ f, disc ceramic.
- C<sub>N</sub> 4-30  $\mu$ f, ceramic.
- J<sub>1</sub> 8-pin octal socket.
- J<sub>2</sub> Amphenol connector PC2F.
- J<sub>3</sub> Coaxial connector type N } part of coax relay Rt.
- J<sub>4</sub> Coaxial connector type N }
- J<sub>5</sub> Phone jack.
- L<sub>1</sub> RCA 202L1, TV picture if coil.
- L<sub>2</sub> 5 turns 14E on 1/2-in. diam, spaced to fill winding space of 11/16 in. on National XR50 form.
- L<sub>3</sub> 5 turns 14E on 1/2-in. diam; space between turns equal to wire diam.
- L<sub>4</sub> 3 turns 14E on 1/2-in. diam; space between turns equal to wire diam.
- L<sub>5</sub> 3 turns 10E on 3/4-in. diam; spaced to occupy 1/2 in.
- L<sub>6</sub> Single turn 10E on 1-in. diam.
- M Carbon microphone with "push-to-talk" switch.
- P<sub>1</sub> 8-pin octal plug.
- P<sub>2</sub> Amphenol connector MC2M.
- R<sub>1</sub> 100,000 ohms, 1/2 watt.
- R<sub>2</sub> 1,000 ohms, 1/2 watt.
- R<sub>3</sub> 47,000 ohms, 1/2 watt.
- R<sub>4</sub> 1,000 ohms, 1/2 watt.
- R<sub>5</sub> 33,000 ohms, 1/2 watt.

- R<sub>6</sub> 1,000 ohms, 1/2 watt.
- R<sub>7</sub> 1,000 ohms, 1/2 watt.
- R<sub>8</sub> 47,000 ohms, 1/2 watt.
- R<sub>9</sub> 1,000 ohms, 1/2 watt.
- R<sub>10</sub> 82,000 ohms, 1 watt.
- R<sub>11</sub> 1,000 ohms, 1/2 watt.
- R<sub>12</sub> 68 ohms, 1/2 watt.
- R<sub>13</sub> 22,000 ohms, 1 watt.
- R<sub>14</sub> 33,000 ohms, 1 watt.
- R<sub>15</sub> 1,000 ohms, 1/2 watt.
- R<sub>16</sub> 20,000 ohms, 1 watt.
- R<sub>17</sub> 15,000 ohms, 1/2 watt.
- R<sub>18</sub> 10,000 ohms, 1/2 watt.
- R<sub>19</sub> 47,000 ohms, 1/2 watt.
- R<sub>20</sub> 1,000 ohms, 1/2 watt.
- R<sub>21</sub> 470,000 ohms, 1/2 watt.
- R<sub>22</sub>, R<sub>23</sub> 10 ohms, 1/2 watt.

RFC<sub>1</sub> } 40-in. length of 32E wound  
 RFC<sub>2</sub> } on 1/4-in. diam. form.  
 RFC<sub>3</sub> }

Rt. Advance 8500, 6-volt type or equivalent.

- T<sub>1</sub> RCA 206K1, TV sound if transformer.
- T<sub>2</sub> Thordarson T20D76 or equivalent.
- T<sub>3</sub> Thordarson T21M52 or equivalent.

**AC Power Supply**

- C<sub>1</sub> 40  $\mu$ f, 450 wv, electrolytic.
- C<sub>2</sub> 80  $\mu$ f, 450 wv, electrolytic.
- C<sub>3</sub> 3,000  $\mu$ f, 15 wv, electrolytic.
- F 5-ampere fuse.
- I 6-v, 150-ma pilot lamp.
- J 8-contact octal socket.
- L<sub>1</sub> Choke, 3 henrys at 225 ma, Peerless C-315-X or equivalent.
- L<sub>2</sub> Choke, 5 henrys at 200 ma, Stancor C-1646 or equivalent.
- RL Relay, 6v (dc), Advance 500 or equivalent.
- RECT Selenium rectifier, 600 ma, 25v, Federal 1017.
- S<sub>1</sub> SPST Toggle Switch.
- T Power transformer, RCA 201T8.

**Genemotor Power Supply**

- C<sub>1</sub> 4  $\mu$ f, 450 wv, electrolytic.
- F 30-ampere fuse.
- G Carter Genemotor 325-A or equivalent: input 6v, 21 amp; output 300v, 250 ma.
- J 8-contact octal socket.
- RL Relay, 6v(dc), Advance 500.



siderably less than the positive voltage between the final-amplifier cathode and ground; therefore, the net potential at the top of the grid-bias resistor is positive.

This voltage is applied to the control-grid of the 6AQ5 through isolating resistor  $R_2$ , but the low resistance of the positive 6AQ5 grid and the high resistance of the isolating resistor cause a relatively large voltage drop; hence the grid of the 6AQ5 is slightly positive. The combined effects of slightly positive bias on the control-grid, and the substantial positive voltage on the screen-grid reduce the dc plate resistance of the 6AQ5 to a low value. The plate of the 6AQ5, being tied to the final-amplifier screen grid, puts a heavier load on the screen-grid dropping resistor  $R_4$  than does the screen grid of the final amplifier; therefore, the voltage on this screen is greatly reduced when the key is in the up position. In fact, it is reduced below the cathode voltage, and this, plus the negative bias applied between cathode and the control-grid, serves to cut off the final-amplifier plate current. The overall effect is that the screen-grid of the final amplifier is protected and the rf signal is interrupted.

### Circuit Details

Note the location of the grid and plate meters

in the circuit. This arrangement provides the least amount of interaction without having the plate-current meter in the high-voltage circuit. As connected, milliammeter  $M_2$  indicates the sum of the plate and screen currents. The grid meter,  $M_1$ , indicates the dc grid current. (As previously mentioned, grid current continues to flow when the key is up.) The grid current is practically the same when the key is down.

The values for the three added resistors ( $R_2$ ,  $R_3$ , and  $R_5$ ) are given in the schematic diagram; actual values are not critical. Resistor  $R_2$  is simply an isolating resistor to keep rf off the 6AQ5 control-grid. Resistor  $R_5$  is a key-click suppressor. Resistor  $R_3$  applies positive voltage to the final cathode and 6AQ5 screen-grid; its value may be halved or doubled for experimental trials. Resistor  $R_4$  is the screen-grid dropping resistor.

A 6AQ5 keying tube is satisfactory for an 807 or 829-B. If one or two 813's are used in the final rf amplifier, a 6V6-GT or 6F6-G should be substituted for the 6AQ5. The actual resistance and power rating of  $R_3$  will vary with the plate-supply voltage.

It is good practice to short out the secondary of the modulation transformer when a phone transmitter is keyed. Switch  $S_1$  is included in the circuit for this purpose.

## TVI BIBLIOGRAPHY (Part II)

A comprehensive listing of articles on TVI and related topics. Although the articles appearing in the non-amateur publications contain only brief mention of the amateur and TVI, they have been included to supply the advanced amateur with a complete set of references. A few important articles on interference from sources other than amateur transmitters as well as some editorials have been listed. Radio amateur groups will find the editorial articles valuable references for discussions. Note that the articles are listed in chronological order; this has been done to facilitate retrospection, and to permit easy cross reference to TV reception techniques and improvements.

1949

- "Cure Your TVI in Three Easy Lessons," by P. S. Rand, *W1DBM, CQ*, May 1949, pg 20.  
 "TVI Patterns," *QST*, May 1949, pg 43.  
 "Minimizing Television Interference," by P. S. Rand, *Electronics*, June 1949, pg 70.  
 "Shielding Experiments and TVI," by M. Seybold, *W2RY1, CQ*, June 1949, pg 31.  
 "TVI Tips," *QST*, June 1949, pg. 44.  
 "Useful Tool for TVI Reduction," by W1FTX, *QST*, July 1949, pg 69.  
 "TVI Tips," *QST*, July 1949, pg 64.  
 "Lazy Linear," *GE Ham News*, July-Aug. 1949, pg 1.  
 "TVI Tips," *QST*, Aug. 1949, pg 45.  
 "The Service Technician and TV Interference," by H. S. Brier, *W9EGQ, Radio & Television News*, August 1949, pg 32.  
 "TVI Reduction—Western Style," by C. E. Murdock, *W6OMC, QST*, Aug. 1949, pg 44.  
 "Adjusting the Antenna Coupler and Harmonic Filter," by G. Grammer, *W1DF, QST*, Aug. 1949, pg 32.  
 "Household Radio Interference Elimination," by J. W. Teegarden, *Radio & Television News*, Sept. 1949, pg 34.  
 "Winning Three Falls from Gorgeous George," by W. I. Orr, *W6SAL, CQ*, Sept. 1949, pg 29.  
 "Shielding Against TVI," by P. S. Rand, *W1DBM, Radio & Television News*, Sept. 1949, pg 57.  
 "TVI Tips," *QST*, Oct. 1949, pg 55.  
 "ARRL's New TVI Film" (editorial), *QST*, Oct. 1949, pg 9.  
 "TVI Can be Cured" (booklet), by W2UOL, Eldico of New York, Inc. (Douglaston, L. I.).  
 "TVI-Free Rig for 10," by M. Seybold, *W2RY1, CQ*, Oct. 1949, pg 11; Nov. 1949, pg 23.  
 "Harmonic Reduction in a 500-watt All-Band Rig," by D. H. Mix, *W1TS, QST*, Nov. 1949, pg 21.

- "The Regenerative Wavemeter," by G. Grammer, *W1DF, QST*, Nov. 1949, pg 29.  
 "Harmoniker," *GE Ham News*, Nov.-Dec. 1949, pg 1.  
 "TV Interference from Incandescent Lamps," by D. G. Fink, *Electronics*, Dec. 1949, pg 132.  
 "TVI on 160 Meters?," by P. S. Rand, *W1DBM, CQ*, Dec. 1949, pg 11.  
 "TVI . . . a challenge to the future of ham radio!," Collins Radio Co., *CQ*, Dec. 1949, pg 10.  
 "Half-Wave Filters," *QST*, Dec. 1949, pg. 36.  
 "The Design of Low-Pass Filters," by M. Seybold, *W2RY1, QST*, Dec. 1949, pg 18; "Feed-Back," (errata), *QST*, Jan. 1950, pg 21.

1950

- "A High-Attenuation Filter for Harmonic Suppression," by A. M. Pichitino, *W3NJE, QST*, Jan. 1950, pg 11.  
 "TVI and the Serviceman," by John F. Rider, *Successful Servicing* (John F. Rider Publisher, Inc., N. Y., N. Y.), Jan. 1950, pg 5.  
 "Practical Filters for Minimizing TV Interference," *Tele-Tech*, Jan. 1950, pg 28.  
 "Eliminating Broadcast Interference Caused by TV Receivers," by J. Najork, *W2HNN, Radio & Television News*, Jan. 1950, pg 52.  
 "TV Interference Problems," by W. L. Kiser, *Radio-Electronics*, Jan. 1950, pg 36.  
 "ZC8PM Licks TVI," by P. Miller, *ZC8PM/W2AIS, CQ*, Jan. 1950, pg 22.  
 "One Solution," by R. M. Ryan, *W7GWA, CQ*, Feb. 1950, pg 26.  
 "Eliminating TVI with Low-Pass Filters," Part I, by G. Grammer, *W1DF, QST*, Feb. 1950, pg 19.  
 Re: "Half-Wave Filters," *QST*, Feb. 1950, pg 34.  
 "RMA Withdraws Film," *QST*, Feb. 1950, pg 26.  
 "TV Interference Problems," by W. L. Kiser, *QST*, Feb. 1950, pg 44.

## TVI BIBLIOGRAPHY (Continued)

- "TVI Tips—Junk-Box TVI Checker," *QST*, March 1950, pg 54.
- "TVI-Proofing the Command Transmitter," by S. J. Lanzalotti, *CQ*, March 1950, pg 18.
- "A TVI Filter for Coaxial Transmission Lines," by J. Forrest, *Radio & Television News*, March 1950, pg 61.
- "Simulating TV Interference Patterns," by E. G. Louis, *Radio & Television News*, March 1950, pg 49.
- "Eliminating TVI with Low-Pass Filters," Part II, by G. Grammer, *W1DF, QST*, March 1950, pg 20.
- "A Note on Capacitive Interstage Coupling," *GE Ham News*, March-April 1950, pg 6.
- "Sweeping the Spectrum" (notes on the Harmoniker), *GE Ham News*, March-April 1950, pg 7.
- "Eliminating TVI with Low-Pass Filters," Part III, by G. Grammer, *W1DF, QST*, April 1950, pg 23.
- "Eliminating TVI on Ten Meters," by S. Kupferman, *W2GVT, CQ*, May 1950, pg 18.
- "A Low-Cost TVI Filter," by C. A. Dene, *W3CPC, QST*, May 1950, pg 16.
- "Tailor Made' Antenna Couplers," by G. Grammer, *W1DF, QST*, May 1950, pg 19.
- "Latest Techniques for the Elimination of Ham TVI," by P. S. Rand, *W1DBM, CQ*, June 1950, pg 9.
- "Modifying the BC-459 for TVI-Free 40-Meter Operation," by H. S. Brier, *W9EGQ, CQ*, June 1950, pg 27.
- "TVI" (editorial), *Service*, June 1950, pg 19.
- "TV Interference Problems," by D. Lerner, *Radio & Television News*, July 1950, pg 62.
- "TVI . . . Causes and Remedies," by I. Kamen, *Service*, Aug. 1950, pg 20.
- "TVI Tips—High-Pass Filters," *QST*, Aug. 1950, pg 46.
- "Design and Application of High-Pass Filters," by M. Seybold, *W2RYI, RCA HAM TIPS*, Fall 1950.
- "TV Interference from Horizontal Deflection Circuits," by D. Lerner & J. Howell, *Radio & Television News*, Sept. 1950, pg 50.
- "TVI . . . Causes and Remedies," (part II) by I. Kamen, *Service*, Oct. 1950, pg 32.
- "Television Interference on Broadcast Receivers," by M. Mandl, *Radio-Electronics*, Oct. 1950, pg 22.
- "Shielding for TVI Reduction," by W. E. Cheshire, *W8UPC, QST*, Oct. 1950, pg 118.
- "TVI-Proofing the ARC-5 VHF Transmitter," by O. W. H. Johnson, *W2ZYX, QST*, Nov. 1950, pg 50.
- "Getting Rid of TVI for Improved Video," by R. F. Scott, *Radio-Electronics*, Nov. 1950, pg 30.
- "High-Pass Filters for TV Receivers," by C. F. Bane, *W6WB, Tecnews* (Electric Supply Co., Oakland, Calif.), Nov. 1950.
- "Television Interference from FM Receivers," by S. D. Uslan, *Successful Servicing*, (John F. Rider Publisher, Inc., N. Y., N. Y.), Nov. 1950, pg 1.
- "Simple Experimental Shielding," by J. W. Weber, *W9BDS, QST*, Dec. 1950, pg 66.
- "TVI Tips—Harmonic Separators," *QST*, Dec. 1950, pg 30.
- "Pursuit and Elimination of Parasitics," by W. I. Orr, *W6SAI, CQ*, Dec. 1950, pg 24.
- "TV Installation Techniques," by S. L. Marshall (John F. Rider Publisher, Inc., N. Y., N. Y.), 1950, pages 210-223.

Devices and arrangements shown or described herein may use patents of RCA or others. Information contained herein is furnished without responsibility by RCA for its use and without prejudice to RCA's patent rights.



From your local  
RCA distributor,  
headquarters for RCA  
receiving and  
power tubes.

RCA HAM TIPS  
is published by the  
RCA Tube Dept.,  
Harrison, N. J.  
It is available  
free of charge  
from RCA Distributors

Joseph Pastor, Jr.,  
Editor W2KCN

If undeliverable for any reason, notify  
sender, stating reason, on Form 3547,  
postage for which is guaranteed.

WHEN MAILING  
PLACE POSTAGE HERE