

it eliminates the need for an extra terminal brought out from the center point of the filament or the need of using a shunt potentiometer such as is used in A. C. receivers across the filament, that system of connection has been adopted as standard in using a "C" battery in amplifier circuits employing D. C. tubes.

The negative terminal of the filament is therefore taken as the "reference point" in D. C. tube circuits and the recommended "C" bias resistor for a given filament plate voltage that is required when the positive terminal of the "C" bat-

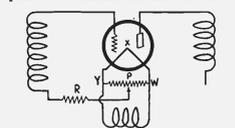


Fig. 18

tery is connected to the negative terminal of the tube to take advantage of the difference in potential between that point and the center point of the filament.

When a CX-371A is used as an A. C. tube, however, with the filament current being supplied by the winding of a transformer which provides A. C. current for the filament, it is necessary because of the reversals in current flow which makes each filament terminal alternately positive and negative, to take the center point of the filament as a reference point. The means usually adopted to do this is to use either a center tap on the filament winding or to use a center tapped resistor across the filament of the tube. The center tap resistance method is usually used as being the most efficient and simpler method, and is shown in Fig. 18.

It is easily seen that while the points "W" and "Y" of the filament shown in Fig. 18 alternately become positive and negative as the current flow reverses, the average value at "X" lies between the two at any time and provides the best reference point.

In selecting the proper value of grid bias voltage and the proper value of resistance to use to obtain that voltage, the fact that point "X" is positive with respect to the negative terminal of the filament must be taken into consideration. The correct voltage to use in cases where a D. C. tube such as the CX-112A, CX-371A or CX-310 is used

as an A. C. tube is equal to the normal grid bias voltage recommended for any given value of plate voltage (with the positive terminal of the "C" battery con-

Tube Type	Plate Voltage	Plate Current	D. C. Operation Connected to A		A. C. Operation Grid Return to Center Tap	
			Grid Voltage	Resistor (ohms)	Grid Voltage	Resistor (ohms)
CX-112A	90	5.5	-4.5	820	-7.0	1270
	135	7.0	-9.0	1280	-11.5	1650
	180	10	-13.5	1350	-16.0	1600
CX-371A	90	10.0	-16.5	1650	-19.0	1900
	135	16	-27.0	1700	-29.5	1850
	177	18	-33.0	1850	-35.5	1970
CX-310	180	20	-40.5	2000	-43.0	2150
	250	12.0	-18	1500	-20	1700
	350	20.0	-35	1750	-37.5	1900
CX-350	250	28			-45	1600
	350	45			-63	1400
	450	85			-90	1250
CX-326	90	3.5			-6.0	1700
	135	6.0			-10.0	1500
	180				-15.5	1600

* With battery operated tubes it is seldom convenient to use a resistor carrying the current of one tube to provide "C" bias. The resistor size then depends upon the number of tubes in the set, etc., and in general is lower than the value shown here.

Fig. 19

nected with the negative terminal of the filament for D. C. operation) equal to one-half of the rated filament voltage of the tube.

In the case of the CX-112A and CX-371A, the proper grid bias for A. C. operation is equal to the normal value for D. C. operation plus an additional 2.5 volts. In the case of the CX-310 whose filament is rated at 7.5 volts, the proper grid bias is equal to the normal value for D. C. operation plus an additional 3.75 volts.

In the case of the CX-326, and CX-350, the grid bias values listed

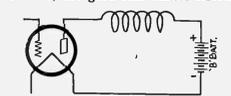


Fig. 20

in the tables of recommended grid bias are given for A. C. operation because those tubes are specially designed for A. C. use and the values recommended are given for A. C. operation with the center point of the filament taken as the reference point.

The table shown in Fig. 19 will prove helpful in eliminating any misunderstanding as to the proper value of grid bias to use when using power tubes either as D. C.

tubes or A. C. tubes. In using this table it must be kept in mind that the values of resistors given are those to be used when the resistor is used to supply the grid bias for a single tube. If a single resistor is to be used to supply the grid bias for more than one tube under similar conditions of plate voltage and current, the values of the resistors will be proportionately lower, i. e., one-half the value given for two tubes, one-third for three tubes, etc.

Before proceeding with instructions on the proper method to use in calculating the correct value of resistance required for the grid bias resistor under different con-



Fig. 21

ditions of plate voltage and number of tubes used, it will be helpful to correct an erroneous impression regarding the flow of current in the voltage divider of a power supply unit which is furnishing current to the plate circuit of a receiver.

The simplest type of receiver plate circuit and power supply is that shown in Fig. 20, in which a "B" battery is used as the source of plate current. There is no difficulty in tracing the path of the current in this circuit. The current flows in a complete circuit consisting of the battery, the conducting path between the plate and the filament and whatever coils or other apparatus may be placed in the plate circuit.

If it is necessary to use a voltage lower than the total voltage of the "B" battery as is the case when 90 volts are required for a CX-301A and a 135- or 180-volt "B" battery block is used as the source of current, all that is necessary to do is to tap off at the desired terminal of the battery as shown in Fig. 21. The current for that particular circuit, then, is furnished by that portion of the battery between the 90-volt terminal and the negative terminal of the battery.

If, however, no taps are provided on the battery, it is possible to use a voltage divider to provide the necessary 90 volts for that particular circuit. The path of the current in the plate circuit of the tube in such a case is as shown in Fig. 22 by the heavy lines. It is readily

seen that the portion "R1" of the voltage divider does not carry any of the current of the plate circuit of the tube but only the "waste current" due to the connection of the total resistance of "R1" and "R2" across the battery. Since "R1" carries only the waste cur-

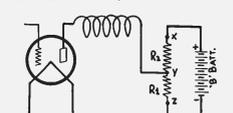


Fig. 22

rent resulting from the connection of the full resistance of "R1" and "R2" across the battery, while "R2" carries both the waste current mentioned and the plate current, it is readily seen that section "R2" must be designed to carry the heavier load. This load depends on the voltage difference between points "X" and "Y" and is found by subtracting the voltage obtained at that tap as measured by a high resistance voltmeter between the "B" terminal and voltage tap, from the total output voltage tap, measured in the same way between the "B" terminal and the positive terminal of the "B" battery.

In this particular instance with a total voltage of 180 volts and the tap at 90 volts, the difference be-

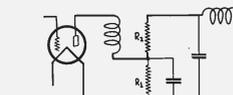


Fig. 23

tween the 90-volt tap and the highest "B" battery voltage, is 90 volts. However, if the total output voltage of a power supply unit were to have a tap at the next highest tap is 70 volts, so that the current carrying capacity required in resistor "R1" is 4.83 watts. The total current flowing in section "R2" is 49 milliamperes and the difference in that section it would be necessary to multiply the current drawn which we will assume is 16 milliamperes for four CX-326 tubes the voltage difference between the tap and the high point or 410 volts this will give a value of 0.16 amperes times 410 volts or 6 watts.

For safe operation, a resistor should be selected for that section

which is conservatively rated at at least twice that value.

The equivalent power supply and plate circuit combination usually shown is shown in Fig. 23, with the rectifier and filter circuit substituted in place of the battery.

Here again it will be noticed that the current in the plate circuit flows through the resistor "R2" and not through resistor "R1" which again brings out the fact that it is the upper section of the voltage divider which bears the greatest load and must be designed accordingly to carry it. Many of the voltage divider failures in units which are built up of individual resistor sections are due to the failure of some experimenters to grasp the idea that the upper sections of the voltage divider are the ones which carry the load and also that the voltage which should be used in making the calculations to determine the current carrying capacity of the section should be the difference in voltage between the tap and the high voltage end of the rectifier output.

It must also be kept in mind that in many cases the upper sections also carry the load of the other taps in addition to the load of the high voltage taps. In the case shown in Fig. 24 for instance, section "R1" carries not only the 20 milliamperes that goes to the 180-volt section but also the current which goes to the other taps, so

particular section, by the voltage drop between the terminals of the section.

While the rating in watts of the section used can be held down to about twice the value thus determined, it is good practice to use a resistor having several times the

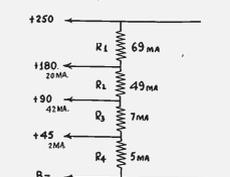


Fig. 24

rating of the calculated figure since the use of a very conservative rating with plenty of safety factor results in a unit which will operate continuously for practically unlimited periods without showing any signs of heating.

The various types of circuits used to provide the necessary grid bias in A. C. tube circuits and the calculation of the proper grid bias resistors to use will be discussed in detail in the next issue of the Research Worker.

AEROVOX WINDS PATENT SUIT

In an opinion handed down November 5, 1928 by the Honorable Judge John C. Knox of the United States District Court for the Southern District of New York, the patent claims upon which the Dubilier Condenser Corporation based its suit against the Aerovox Wireless Corporation, for alleged infringement of Dubilier patents on mica condensers, were held invalid and a decision was rendered in favor of the Aerovox Wireless Corp.

In reviewing the facts in the case, Judge Knox found that the patent claims contained in the Dubilier patent No. 1,497,095 on which Dubilier brought suit for infringement were not valid and that the patent claims in the Horton patent No. 1,572,604, owned by Dubilier and on which Dubilier also brought suit for infringement, were not infringed by the construction of the Aerovox condensers. The opinion goes on to state at length why the patent claims on which Dubilier brought suit represent nothing worthy of monopoly protection.