



condensers have the same capacity, and therefore the same reactance, it is obvious that the voltage will be 100 volts across each of the three condensers. This indicates that the voltage divides equally among the various condensers, provided they have the same capacity.

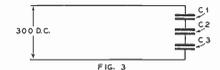


FIG. 3

Now let us take the case of unequal capacities, as shown in Fig. 2. Assume again that the source of voltage is 300 volts a.c. 60 cycles and that we have connected across this voltage one 1 mfd. condenser and one 2 mfd. condenser. The reactance of the 1 mfd. condenser as indicated above is 2600 ohms. By reference to the chart it will be found that a 2 mfd. condenser has one-half the reactance or 1300 ohms. This makes a total reactance of the two in series 3900 ohms. The current through the circuit will therefore be the voltage 300 volts divided by the total reactance 3900 ohms which gives a total of .077 amperes.

The voltage across the condensers will again as in the foregoing example be equal to the reactance of the condenser multiplied by the current. In the case of the 1 mfd. condenser this gives us 2600 x .077 or 200 volts. In the case of the 2 mfd. condenser we have 1300 multiplied by .077 or 100 volts. Note in this case that the voltage division is unequal and that the larger capacity has the lower voltage across it.

The above example indicates what happens when condensers are connected in series on a.c. When condensers are connected in series to a source of d.c. voltage the results are, however, entirely different.

In the case of direct current circuits the division of voltage bears no direct relation to the capacities of the condensers connected in series. In the case of series sections on d.c. the voltage across any one section depends entirely upon the insulation resistance of the condenser.

Let us work through a few examples for series sections on d.c., for in this way we can show most clearly the difference between series sections on d.c., and series sections on a.c. Suppose we have three sections connected in series on d.c. as shown in Fig. 3 in which the three sections are marked C1, C2, and C3. In the case of d.c. operation we must take into consideration the insulation resistance of the condensers. Assume that the three condensers connected in series for this first example have the following characteristics:

UNIT	CAPACITY	INSULATION RESISTANCE
C-1	1 mfd.	1000 megohms
C-2	1 "	1000 "
C-3	1 "	1000 "

When these three series condensers are connected across d.c. the condensers immediately take a charge but after the initial charging current, the current drawn from the d.c. source will be determined by the insulation resistance of the three sections in series. In this case the insulation resistance of the three sections in series is 3000 megohms. The current through the circuit will therefore be

$$I = \frac{E}{R}$$

$$I = \frac{300}{3000 \times 10^6}$$

$$I = 0.1 \times 10^{-6} \text{ amperes}$$

Therefore, the current is 0.1 microamperes.

The voltage across any one section is equal to the insulation resistance of the section multiplied by the current. Since in this example the sections have the same insulation resistance the voltage across each section is equal to the insulation resistance 1000 megohms multiplied by the current 0.1 microamperes. This gives

$$E = IR$$

$$= 0.1 \times 10^{-6} \times 1000 \times 10^6$$

$$= 100 \text{ volts}$$

Therefore, in an example of the type given each section will have 100 volts across it, and the voltage will divide equally.

However, in the manufacture of paper condensers the procedure is to check the capacity to be sure that it is within tolerance and to then check the insulation resistance to make certain that it is above a certain minimum value. For example a 1 mfd. condenser might have an insulation resistance of 1000 megohms or it might, as an example have an insulation resistance of 2000 megohms. Both condensers would be considered entirely satisfactory. Suppose, however, we connected three condensers in series which have the following characteristics.

UNIT	CAPACITY	INSULATION RESISTANCE
C-1	1 mfd.	1000 megohms
C-2	1 "	1500 "
C-3	1 "	2000 "

In such a combination the total insulation resistance would be 4500 megohms, and if the voltage was 300 volts d.c. the current would be

$$I = \frac{300}{4500 \times 10^6} = 0.0667 \times 10^{-6} \text{ amp.}$$

The voltages across the individual sections will again be equal to the total current drawn from the d.c. source will be determined by the insulation resistance. This gives the following values for the voltages across the sections.

UNIT	VOLTAGE
C-1	66.7 volts
C-2	100 volts
C-3	133.3 volts

It will be noted from the above that while, quite naturally, the total voltage adds up to 300 volts the voltage does not uniformly divide between the various sections due to the fact that the sections have unequal resistances.

Because of the above problem, and the fact that the voltage division may be even more unequal, unless proper care is exercised, it is desirable always to use condensers rated at the proper voltage, rather than for the user to make up a bank out of several individual condensers. If, however, several condensers are used in series, then the precaution should be taken to connect across them a group of resistors as shown Fig. 4. These resistors should have values as low as can be tolerated in the circuit.

These resistors should have values considerably lower than the probable insulation resistances of the condensers. In fact, in the case of paper condensers it will generally be possible in ordinary circuits to use a bank of resistors to give a current drain of 1 microampere. This current, small, is still much greater than the leakage current of the condensers, and the resistor will therefore serve to equalize the voltages.

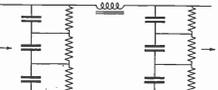


FIG. 4

As a typical example, in the case of a 1000 volt circuit the total value of the shunt resistance connected across the circuit will be 1 megohm, and the bank would consist of as many individual resistors (all equal in value) as there are condensers in series. For two condensers in

series there would be two one-half megohm resistors; for three condensers in series there would be used 3 resistors in the order of 330,000 ohms each.

By using such an arrangement, the voltage will divide evenly and thereby greatly reduce the possibility of any condenser failures.

In a future issue of the Research

Worker we will carry this discussion forward further with particular reference to the types of condensers especially designed for high voltage circuits.

Some Useful Data on A. F. Characteristics

The tables given below contain considerable information useful to workers in the field of audio engineering. One table indicates various important points in the frequency spectrum from 16 cycles up to 32,768 cycles. The other table indicates the peak audio frequency power developed by various musical instruments, played very loudly. These values for the maximum audio frequency output of musical instruments may be compared with the output of a violin played very softly which is 4 micro-watts.

NOTE	CYCLES PER SECOND	PIPE ORGAN	REMARKS
C ⁹	32,768		Beyond limit of audibility for average person.
C ⁷	16,384		Telephone silent with 40 volts on receiver terminals.
	10,000		Considered ideal upper limit for perfect transmission of speech and music.
C ⁶	8,192	3/4 in.	5,000
	5,000		Highest note on fifteenth stop.
C ⁵	3,096		Considered as satisfactory upper limit for high quality transmission of speech and music.
E ⁵	2,560		Highest note of pianoforte.
G ⁴	3,072		Approximate resonant point of ear cavity.
	3,000		Considered as satisfactory upper limit for good quality transmission of speech.
C ⁴	2,048		Maximum sensitivity of ear.
	2,000		Mean speech frequency from articulation standpoint.
	1,500		Representative frequency telephone currents.
A ²	850		Orchestral tuning. See note below.
A ^{1 1/2}	800		Considered as satisfactory lower limit for good quality transmission of speech.
E ^{1 1/2}	600		Considered as satisfactory lower limit of high quality transmission of speech and music.
	600	8 ft.	Lower note of man's average voice.
	426 2/3		Lowest note of 'cello.
C ¹	256		Lowest note of average church organ.
	200	16 ft.	Considered ideal lower limit for perfect transmission of speech and music.
	128		Lowest note of pianoforte.
	80		Lowest audible sound. Longest pipe in largest organ.
	64		
	60		
	32		
	30		
	27		
	25		
	16	32 ft.	

PEAK POWER OF MUSICAL INSTRUMENTS

INSTRUMENT	PEAK POWER, WATTS
(Fortissimo Playing)	
Heavy Orchestra	70
Large Bass Drum	25
Pipe Organ	13
Snare Drum	12
Cymbals	10
Trombone	6
Piano	0.4
Trumpet	0.3
Bass Saxophone	0.3
Bass Tuba	0.2
Bass Viol	0.16
Piccolo	0.08
Flute	0.06
Clarinet	0.05
French Horn	0.05
Triangle	0.05

Notes of the "Gamut"	C	D	E	F	G	A	B	C
Vibration frequencies proportional to	1	9/8	5/4	4/3	3/2	5/3	15/8	2
Intervals between successive notes	9/8	10/9	16/15	9/8	10/9	9/8	16/15	

NOTE: Nearest note is indicated. Scale based on Middle C⁴ (Physical Pitch)=256 cycles.