

Radio Editors of magazines and newspapers are hereby given permission to reprint in whole or in part, with proper credit to the Aerovox Corporation, the contents of this issue of the Aerovox Research Worker.

The AEROVOX

Research Worker

The Aerovox Research Worker is a monthly house organ of the Aerovox Corporation. It is published to bring to the Radio Experimenter and Engineer authoritative, first hand information on condensers and resistances for radio work.

VOL. 11, NO. 10

OCTOBER, 1939

50c per year in U.S.A.
60c per year in Canada

Television Receivers

PART 3

By the Engineering Department, Aerovox Corporation


I.F.-AMPLIFIERS

THE circuits of the picture-i.f. amplifiers may look quite unfamiliar to servicemen and others who have worked only with ordinary broadcast receivers. The i.f.-amplifier in a television receiver consists of two distinct amplifiers: the sound-i.f. amplifier and the picture-i.f. amplifier. They are preceded by a network which serves to separate the two signals.

When a.v.c. is used in the picture-i.f. amplifier as well as in the sound amplifier it may then be a separate a.v.c. system, or, the a.v.c. system of the sound-i.f. amplifier may control some of the picture-i.f. stages while the other stages are manually controlled. In the smaller and less expensive receivers, the picture-i.f. amplifier has no a.v.c. and the manual sensitivity control is called "contrast control".

THE SOUND-I.F. AMPLIFIER

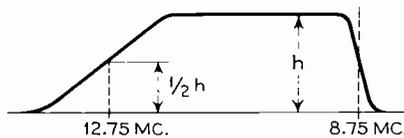There is practically nothing new in the sound-i.f. amplifier. It is of the usual construction employing double-tuned circuits which are deliberately made rather broad so as to make the tuning less critical and to insure good quality. The RMA standard frequency for the sound-i.f. amplifier is 8.25 mc.



In some cases this frequency may be changed again to 455 kc. making this part of the receiver a double super-heterodyne.

Those who make their own television receivers might use an existing all-wave set for the sound reception by tuning it to 8.25 mc. and coupling it to the first detector of the television receiver. If this is done, care should be taken not to feed the signal from one converter into the next; there should be at least one 8.25 mc. amplifier stage in between. In general, the use of the double super is not advised. Such a circuit is subject to complications due to the interaction of the two oscillators; the results are numerous birdies and "ghost signals". Only extreme care in the shielding and design of the oscillators will prevent this difficulty.

The alignment of the sound i.f. amplifier should not offer any difficulties to those who are familiar with present-day alignment procedure.

THE PICTURE-I.F. AMPLIFIER

It was explained in Part I that the picture carrier or "video"-carrier has been modulated normally at the transmitter and then has a part of one sideband removed. The radiated signal then consists of the carrier, a double-sideband for the lower "video-frequencies" and a single-sideband for the higher video-frequencies. If such a signal were passed by the i.f.-amplifier unchanged and rectified, the lower video-frequencies would arrive twice as strong as the higher ones. Therefore, the i.f. response curve is to have a special shape which corrects this trouble. The RMA standard curve is shown in Figure 1. Note that the high-frequency end of the curve is sloping and that the carrier falls at a point where the response is one-half of the peak value. The two sidebands of the lower video-frequencies and the carrier have been cut so that their combined effect is equal to that of the single-sideband at the higher frequencies.

At the low-frequency end of the i.f. response curve a sharp cut-off is desirable because the sound-carrier of 8.25 mc. must not pass through the picture channel and yet the sidebands down to 8.75 mc., which represent the highest video-frequencies (fine detail in the picture), should be passed. The

AEROVOX PRODUCTS ARE BUILT BETTER

wide-band amplifier must generally be supplied with special trap circuits to keep the sound-carrier out of the picture-channel.

Taking the 50-56 mc. channel as an example, the picture-carrier is at 51.25 mc., the sound-carrier at 55.75 mc. After beating these carriers with the oscillator (64 mc.), these become 12.75 and 8.25 mc. respectively. The sound-carrier of the lower channel, 44-50 mc. is at 49.75 mc. which becomes 14.25 mc. in the i.f.-amplifier. This carrier may sometimes become troublesome and many receivers include trap circuits in the picture-i.f. amplifier to eliminate it.

The picture-i.f. amplifier generally consists of several stages; some are straight band-pass stages while some band-pass stages each have one trap circuit added.

BAND-PASS AMPLIFIER STAGES

Each amplifier stage consists of an amplifier tube plus a network coupling it to the next tube. For reasons which shall become clear later, the amplifier tube must be one of the high-mutual-conductance type such as the 1851, 1852, 1853, 1231 or 1232. The coupling circuit provides the band-pass properties. Some engineers prefer to use the filter theory for calculating and designing the circuit. The result is usually a configuration which is totally unlike the familiar coupling circuits. One may also employ the customary over-coupled circuits. Overcouple them still more to make them broad enough and connect resistors across them to lower the double peaks. This type of circuit can be shown to be equivalent to a T-network or Pi-network such as the filter theory would provide.

The following is a brief review of the behavior of overcoupled circuits with design equations included. Those who are not mathematically inclined may skip the equations and still derive a comprehensive understanding of coupled circuits.

Assume two tuned circuits, individually tuned to the same frequency and coupled inductively. Let one of the circuits, the primary, be excited from a suitable generator, such as an amplifier tube (see Figure 2). Due to the inductive coupling, the current in the coil L_1 will induce an e.m.f. in the secondary (L_2). The magnitude of this e.m.f. is

$$E_2 = -j\omega MI_1 \quad (1)$$

and it lags 90 degrees behind the primary current. This e.m.f. will cause a current to flow in the secondary and

when the secondary is tuned to the signal frequency, the impedance of the secondary is a pure resistance. The secondary current, I_2 , is therefore in phase with the induced e.m.f., E_2 .

$$I_2 = \frac{E_2}{R_2} \quad (2)$$

This secondary current again induces an e.m.f. into the primary which is opposite in phase to the primary current. The net result of the presence of the secondary is the same as if a resistance had been added to the primary circuit. The magnitude of this resistance is

$$\frac{(\omega M)^2}{R_2} \quad (3)$$

If the secondary had not been tuned to the frequency of the signal, but had too much inductance, the secondary current would have lagged behind the induced e.m.f. in the secondary and the e.m.f. induced in the primary would then be the same as if a resistance and a capacitive reactance had been added to the primary. Similarly, had the secondary had too much capacitive reactance, it would have reflected back on the primary as a resistance and an inductive reactance. The magnitude of this "coupled impedance" is


$$\frac{(\omega M)^2}{Z_2} \quad (4)$$

Therefore we see that a correctly tuned secondary does not alter the tuning of the primary but a detuned secondary has the effect of detuning the primary in the opposite direction.

The coupling between two inductances is indicated by a coefficient k . When all the magnetic flux of the primary circuit is linked with all of the magnetic flux of the secondary, then k equals unity or the coupling is 100%. In general

$$k = \frac{M}{\sqrt{L_1 L_2}} \quad (5)$$

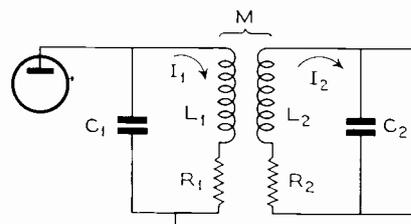Let us gradually increase the coupling in the circuit of Figure 2 by increasing the value of M (the mutual inductance) and let us observe the effect on the shape of the resonance curve as it would be seen on an oscillograph and wobbulator. The circuits are still individually tuned to the same frequency.



$$Q_1 = \frac{\omega L_1}{R_1} \quad Q_2 = \frac{\omega L_2}{R_2}$$

$$Z_2 = \sqrt{R_2^2 + \left(\omega L_2 - \frac{1}{\omega C_2}\right)^2}$$

$$\omega = 2\pi f$$

Fig. 2

When M is very small and we have very loose coupling, the voltage across the secondary condenser has a single peak and is very sharp. This condition is known as "insufficient coupling" because the voltage across the secondary condenser is not as high as it might be.

When the coupling is now further increased, the height of the resonance curve grows until we come to a condition called "critical coupling". At this point, maximum energy is transferred from primary to secondary and it is the point of maximum response where there is still a single peak. At critical coupling

$$\omega M = \sqrt{R_1 R_2} \quad (6)$$

The coupling still can be increased but the response at resonance does not increase any more. The curve now becomes double peaked; one peak is below and one above the resonant frequency. The peaks have moved farther apart when the coupling is made tighter; they become higher when the coils have a high Q (have little resistance) and lower when the Q is low.

$$Q = \frac{2\pi f L}{R} \quad (7)$$

In the application of the double-peaked response curve for picture i.f. amplifiers, the peaks must first be brought far enough apart and then they must be lowered by making the circuits less efficient (placing resistance in series or in parallel with them) until, at a critical value of Q , the response curve is nearly flat.


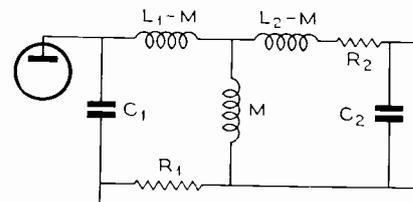


Fig. 3

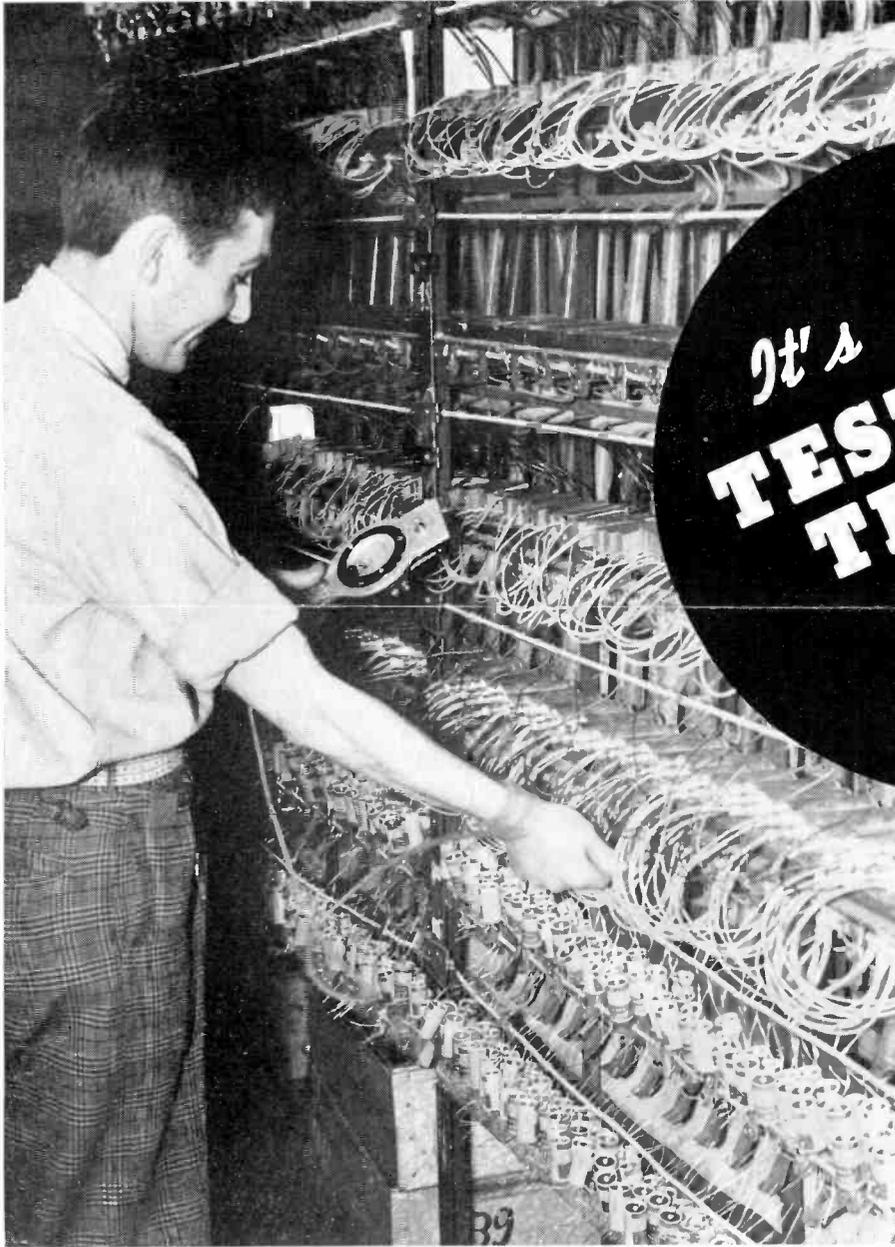

It's
**TEST...
 TEST...
 TEST...**

in building
QUALITY
into every
AEROVOX
CONDENSER

● **THERE** are no class distinctions among AEROVOX condensers when it comes to routine factory inspection and test. The ten-dollar X-mitting condenser and the ten-cent by-pass tubular are treated alike in safeguarding the good name of AEROVOX.


So it is no idle boast that every AEROVOX condenser is individually tested. It would be quicker and cheaper to make percentage tests or even spot tests, whereby units selected at random might answer for the quality and dependability of the entire run.

But AEROVOX, with an experience second to none

in the mass-production of quality condensers, prefers to test each unit individually. Only in this way can your assemblies or your service jobs be safeguarded against the chance of defective or sub-standard condensers. Please remember this point.

See Our New Catalog...

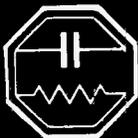The 1939-40 Edition is ready to aid you in selecting just the right condensers for any job you may be handling. Ask your local jobber for a copy—or write us direct. It contains more pages, more items, more listings, more choice, than ever before. Simply indispensable!



AEROVOX CORPORATION

New Bedford, Mass.



Sales Offices in All Principal Cities