



AEROVOX
BUILT BETTER
CONDENSERS AND RESISTORS



counted. If some other number is counted, the multivibrator is not locked-in on the correct submultiple of the control frequency but on a frequency found by dividing the control frequency by the number of "carrier spaces" in the series of harmonics:

$$f = \frac{F}{n+1}$$

Where:
 f = multivibrator frequency,
 F = control oscillator frequency,
 n = number of multivibrator harmonics counted between adjacent control frequency harmonics ($n+1$ is the number of spaces between the harmonics.)

If the frequency of synchronization is incorrect, the setting of the variable resistor in the multivibrator must be changed.

Adjustments made to the variable resistor should result in abrupt changes of the multivibrator frequency, the harmonics abruptly changing their total number. If instead there is a smooth variation in frequency, the multivibrator is out of control and operating independently, and the control voltage must be increased. In the absence of control, it will also be noticed that the multivibrator harmonics are rough and wavering in character.

When the proper number of points are counted between the control frequency harmonics, a test may be made for positiveness of control by rotating the frequency-synchronization control back and forth over a small arc. This should cause no frequency change, and is a good test for the appropriate control voltage level.

When the control voltage is of the proper value, it will be possible to switch the multivibrator on and off repeatedly without disturbing its controlled frequency.

A Convenient Method for Referencing Second-Order Frequency Standards: See "The Interval," L. M. Hull & J. K. Clapp. Proc. I.R.E., February 1951.

Beg Pardon...

If, due to our irregular and lagging publication dates, we have caused you to write and inquire; or, if we've given you the impression you've been given any issues of the AEROVOX RESEARCH WORKER, we're sorry.

Due to certain circumstances beyond the editors' control, publication dates have necessarily lagged.

Although this is the November 1940 issue, we expect to catch up within the next month, after which the AEROVOX RESEARCH WORKER will appear quite regularly — the month it is dated.

In the meantime, please bear with us a little while longer.



Look for the Red Sticker!

Keep your eye peeled for the familiar yellow-and-black Aerovox cartons and spot those with the red sticker across the front. Ask to see those new items... Here's how our "flagging" system works:


1. Vivid red label extends around one end of carton. Displays "New Item" signal. Sides indicate list price, since such item is not as yet listed in catalog.

2. Other end of carton remains as usual, with Catalog Number, rating, capacity. If you are going to order more of his item, be sure to jot down the data taken off the red sticker.

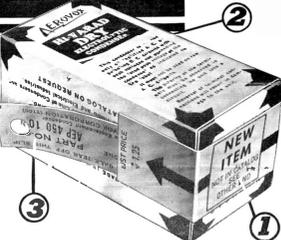3. Label includes tear-off re-order ticket on side. When item is sold, your jobber tears off this ticket and places it on his order hook or in the drawer, as a reminder to re-order this item and have it in stock for your convenience.

Recent Aerovox NEW ITEMS...

Plain electrolytic. Wide applications. Voltage in various sizes. Capacities — conventional, low-voltage. Special "three lead" type. I.F.E.C. section (see lead) I.F.R. type. Ultra-miniature oil filled miniature tubular in brass case. Ultra-miniature paper condensers for heavy duty. High voltage, high grade types for cathode-ray tubes.



● Hardly a month passes but that Aerovox introduces some *new type* or *new value* or *new size* of condenser, in step with the rapid strides of the radio art and practice. And unless such new items are promptly brought to your attention, there is the ever-present danger that you may not profit from this Aerovox alacrity to your up-to-the-minute requirements.

And so we now *flag* those new items so you won't miss them. Yes! Each new-item carton carries a *vivid red label* on front and sides (see above). Those new items on your jobber's shelves simply won't be overlooked. The list price of the still uncatalogued item appears on the label. A tear-off re-order ticket insures the continued stocking of the new item by your jobber.

Be sure to take advantage of these new and latest condenser types in your work. By so doing you too can keep ahead of the radio parade.

Watch the Jobber's Shelves!

● Look for those red-label Aerovox cartons. You can pick out the new items without a struggle. Ask your jobber to show you those new items. Use them in your work. Ask for latest catalog—or write us direct.

AEROVOX CORPORATION

New Bedford, Mass.

Sales Offices in All Principal Cities



Radio Editors of magazines and newspapers are hereby given permission to reprint in whole or in part, with proper credit to the Aerovox Corporation, the contents of this issue of the Aerovox Research Worker.



The Aerovox Research Worker is a monthly house organ of the Aerovox Corporation. It is published to bring to the Radio Experimenter and Engineer authoritative, first-hand information on condensers and resistances for radio work.

VOL. 12, NO. 11

NOVEMBER, 1940

50c per year in U.S.A.
60c per year in Canada

Theory and Operation of Multivibrators

By the Engineering Department, Aerovox Corporation

THE multivibrator is a unique form of relaxation oscillator first described in 1919 by H. Abraham and E. Bloch. The circuit was comparatively obscure for a number of years and has only lately become very well known for its part in measurements of radio frequencies, although J. K. Clapp proposed it for that present peculiar application as early as 1927.

As an oscillator, operated alone, the multivibrator is notoriously unstable. Its frequency is altered considerably by the slightest shifts in operating voltages or circuit values and its output-voltage wave form is characteristically ragged. Accordingly, it has little practical worth as an independent frequency generator.

However, the device has another noteworthy property which well adapts it to certain applications as we shall see later. It may readily be stabilized by injecting a small voltage of proper magnitude into its circuit from another stable oscillator. In the controlled state the stability and frequency accuracy of the multivibrator reach the same order as those properties of the controlling oscillator, and the emitted frequency becomes independent of small shifts in circuit values.

It is not required that the control oscillator frequency coincide with the fundamental frequency of the multivibrator circuit in order to obtain synchronization. The controlling frequency may be a harmonic or sub-harmonic. Multivibrators have been

controlled experimentally by frequencies 40 to 50 times higher than their natural frequencies. In common present applications, the controlling frequency is harmonically related to the multivibrator fundamental (and generally held to a ratio of 10-to-1 for best results), so that the multivibrator presents the practical appearance of subdividing the control frequency. And it is in this role of frequency divider that the device enjoys its present wide acquaintance.

While frequency multiplication may be carried out simply by choosing the multivibrator fundamental equal to an integral multiple of the control frequency, this function is somewhat more satisfactorily performed by conventional multiplier circuits (doublers, triplers, quadruplers, etc.). However, it is interesting to note that harmonic frequencies may be obtained directly from the harmonically-controlled multivibrator. Even in the controlled state the multivibrator output voltage is rich in harmonics spaced equal to the multivibrator fundamental, several harmonics of this being readily located with a sensitive detector. This harmonic series may extend far beyond the control frequency, subdividing spaces established by harmonics of the latter. Thus, when a 10-ke. multivibrator is controlled by a 100-ke. standard frequency oscillator in a modern frequency measuring assembly, prolific 10-ke. harmonics are provided to sub-divide equally the space between any two adjacent 100-ke. harmonics.

While frequency multiplication may be carried out simply by choosing the multivibrator fundamental equal to an integral multiple of the control frequency, this function is somewhat more satisfactorily performed by conventional multiplier circuits (doublers, triplers, quadruplers, etc.). However, it is interesting to note that harmonic frequencies may be obtained directly from the harmonically-controlled multivibrator. Even in the controlled state the multivibrator output voltage is rich in harmonics spaced equal to the multivibrator fundamental, several harmonics of this being readily located with a sensitive detector. This harmonic series may extend far beyond the control frequency, subdividing spaces established by harmonics of the latter. Thus, when a 10-ke. multivibrator is controlled by a 100-ke. standard frequency oscillator in a modern frequency measuring assembly, prolific 10-ke. harmonics are provided to sub-divide equally the space between any two adjacent 100-ke. harmonics.

Aside from its radio-frequency applications, the harmonically-controlled multivibrator makes it possible to obtain precisely-known low frequencies from a stabilized higher-frequency oscillator. Thus, standard low frequencies extending down into the audio-frequency spectrum may be obtained from a satisfactory radio-frequency oscillator.

THE MULTIVIBRATOR CIRCUIT

The multivibrator circuit differs from other relaxation oscillators in its particular use of two triodes in cascade, yet resembles others in the absence of any inductance in the frequency-determining circuits, other than the small amount encountered as a circuit stray. It is entirely a resistance-capacitance oscillator.

The conventional multivibrator circuit of Figure 1 is seen to be essentially that of a two-stage triode resistance-coupled amplifier with the exception that the output circuit is coupled back to the input through a feedback condenser C₁, the interstage coupling condenser; C₂ the plate-circuit by-pass condenser usually encountered in resistance-coupled amplifier circuits. The tubes A and B are identical in type and may be any suitable triodes. However, space may be conserved and replacement simplified by employing twin triodes 106-G, 116-G, 8-A, 8-C, 8-G, 656, 678-G, 6N7, 6N7-G, 6S7, 6Z7-G, 12C7, 19, 53, or 79.

AEROVOX PRODUCTS ARE BUILT BETTER

Printed in U. S. A.

Copyright 1940 by Aerovox Corporation

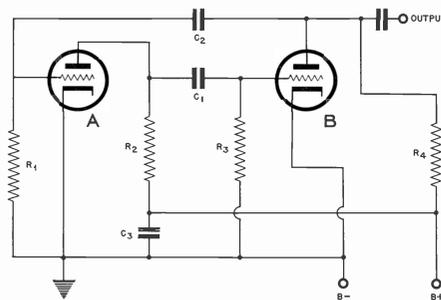


Fig. 1

For any pair of identical fixed coupling condensers, the value of grid resistors required for a desired multivibrator frequency may be calculated by multiplying the sum of the capacitances in farads by the reciprocal of the frequency in cycles per second:

$$(3) \quad R_g = \frac{1}{f} (C_1 + C_2)$$

If, as above, the capacitances are chosen equal:

$$(4) \quad R_g = \frac{2C}{f}$$

The value of grid resistor may also be determined from the equation:

$$(5) \quad R_g = \frac{K}{f}$$

Where:

$$K = \frac{500}{\text{in this case } \begin{cases} R_g = \text{grid resistance in ohms,} \\ C = \text{capacitance in mfd's.,} \\ f = \text{frequency in kilocycles.} \end{cases}}$$

If we neglect the presence of tubes, the multivibrator circuit is observed to be aperiodic. It is the function of one tube to sustain in that circuit periodic current variations of irregular wave form when excited by the other tube which provides the phase relation necessary to maintain the oscillations.

Because the fundamental frequency of oscillation is determined by the relaxation-oscillator time constant of the circuit, it is largely dependent upon the values of the coupling condensers, C_1 and C_2 , and the grid resistors, R_1 and R_2 . While there is no simple formula whereby the exact frequency of the combination may be calculated, a close approximation may be made from the following equation which takes into consideration the capacitances and resistances mentioned:

$$(1) \quad F = \frac{1000}{R_1 C_2 + R_2 C_1}$$

Where:

$$\begin{cases} F = \text{frequency in kilocycles,} \\ C = \text{capacitance in mfd's., and} \\ R = \text{resistance in ohms.} \end{cases}$$

For circuit simplification it is usual to choose C_1 equal to C_2 and R_1 equal to R_2 , whereupon equation (1) becomes:

$$(2) \quad F = \frac{1000}{2RC} = \frac{500}{RC}$$

setting of the variable member being equal to the value indicated by equations (3), (4) or (5).

A practical example of 10-kc. multivibrator employed in several of the low-priced frequency standards now available to amateurs, servicemen, and others employs the two triodes of a 6N7 tube. In this circuit, C_1 and C_2 are each of 0.002 mfd. capacitance. R_1 and R_2 are each 2500 ohms, R_3 is 30,000 ohms, and R_4 composed of a 20,000-ohm fixed resistor connected in series with a 15,000-ohm rheostat (frequency control). The plate-circuit bypass condenser, C_3 is omitted. The fundamental frequency may be varied between approximately 8,000 and 12,000 kilocycles with the variable grid resistor.

SYNCHRONIZATION

Control of the multivibrator is effected by injecting an alternating voltage of suitable frequency and magnitude into the circuit, as previously described. The control voltage might be applied to the grid of tube A (Figure 1) through a sliding tap on the resistor R_1 . The correct voltage for satisfactory synchronization might then be obtained experimentally by varying the position of this tap.

Better stability is obtained, however, when the control voltage is injected into the multivibrator plate circuit, preferably being developed across a common plate-circuit resistor as shown in Figure 2. R_5 is the common resistor interposed in the B+ line. The plate circuit of the control oscillator (or amplifier) receives its operating potential from one end of this resistor, while the multivibrator circuit is connected to the adjustable tap in order that the proper amount of control voltage may be selected.

When the circuit values are fixed, the frequency emitted by the multivibrator progresses in distinct steps (jumping abruptly from one to the

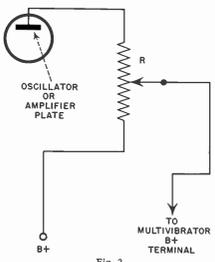


Fig. 2

T
D

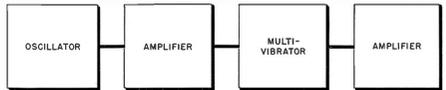


Fig. 3

best synchronization, it will be noted that the multivibrator fundamental should be set somewhat lower than the desired controlled frequency.

In order to isolate the control oscillator from multivibrator circuit disturbances, it is recommended that one or more untuned, resistance-coupled *tetrode* or *pentode* amplifier stages be inserted between the oscillator multivibrator, as indicated in Figure 3. A similar isolating amplifier is shown following the multivibrator to protect the latter from output-circuit disturbances. This last amplifier may be highly biased to accentuate the higher harmonics that are extremely useful for radio-frequency measurements.

Action of the injected control voltage is not the same for even and odd frequency ratios. If the multivibrator circuit is symmetrical, wave symmetry tends to restrict positive control to the even ratios. Hull and Clapp⁷ has suggested circuit asymmetry for stable operation and positive control with both even and odd ratios. There are a number of ways of arriving at satisfactory asymmetry but the most pleasing is perhaps their system of making the plate resistor R_4 (see Figure 1) ten to fifty times larger than R_3 . Preserving this ratio, the plate resistance should be kept low for ease in selecting the operating frequency.

There is an optimum value of control voltage for the best synchronization and this is slightly more than the minimum value required for frequency "stepping" to the desired fundamental. When the multivibrator is satisfactorily controlled, the variable synchronizing resistor may be varied over a small arc of rotation without encountering adjacent frequency steps. While it will be found possible to keep the multivibrator "locked" on steps other than the particular frequency for which it was designed, it is recommended that operation be restricted to that frequency most closely approximated by the C values.

PRACTICAL CONSIDERATIONS

For the most reliable operation, C_1 and C_2 should be first-grade mica condensers (whenever the capacitance permits) obtained as near as possible to the values arrived at by calculation. They should be mounted below the instrument chassis away from the heat of tubes and close to their points of connection.

As far as practicable the triodes should be matched in characteristics, and, if possible, such points may be particularly as regards inter-electrode

capacitances. Certainly there must be no wide tube differences, if performance with matched circuit values is expected.

The various resistors should be of not less than 2-watt rating for the output of the receiving triodes operated at 250 volts, or less, plate potential. The variable resistor used as a frequency-synchronization control should be a regulation wire-wound type of the best quality and must have a maximum value not exceeding 50 percent of the total resistance calculated for the leg in which it is inserted.

The plate power supply should incorporate voltage regulation for greatest stability of the multivibrator control oscillator-amplifier. The current requirement of multivibrator arrangements, such as described in the foregoing paragraphs, is relatively low so that simple voltage regulator circuits should be adequate.

For most positive control, the oscillator-multivibrator frequency ratio should not be carried beyond 10-to-1 in a single multivibrator stage.

Switching operations in the multivibrator stage should not be accomplished in such a manner as to place a varying load on the control oscillator (if plate-supply voltage regulation is not used). Since such variations will react unfavorably on the oscillator frequency. The multivibrator may be switched by short-circuiting a switch connected between one triode grid and ground, thus leaving the plate current undisturbed.

PRACTICAL ADJUSTMENT

One of the most satisfactory methods of checking the multivibrator frequency consists in tuning through a series of its harmonics with a calibrated radio receiver. As near the frequency of the control oscillator as possible, the additional harmonics being brought into adjacent harmonics of the control oscillator are counted to determine the frequency of the multivibrator.

Assume, for example, a 10-kc. multivibrator controlled by a 100-kc. standard frequency oscillator. With the multivibrator switched off, any two adjacent harmonics of 100 kc. are located on the receiver dial and their positions noted. The multivibrator is then switched on, whereupon its harmonics will appear as equally-spaced, middle signals between the 100-kc. harmonics. If the multivibrator frequency is exactly 10 kc. as intended, the "middle" signals may be

(Continued next page)

CHART A

C (MFD.)	Grid Resistance (in Ohms)			
	100 Kc.	15 Kc.	1 Kc.	0.1 Kc.
.001	5000	50,000	500,000	
.002	2500	25,000	250,000	
.003	1666	16,666	166,666	
.004	1250	12,500	125,000	
.005	1000	10,000	100,000	
.006	833	8,333	83,333	
.007	714	7,142	71,428	
.008	625	6,250	62,500	
.009	555	5,555	55,555	
.01	5000	50,000	500,000	
.02	2500	25,000	250,000	
.03	1666	16,666	166,666	
.04	1250	12,500	125,000	
.05	1000	10,000	100,000	
.06	833	8,333	83,333	
.07	714	7,142	71,428	
.08	625	6,250	62,500	
.09	555	5,555	55,555	
1.0	5000	50,000	500,000	
2.0	2500	25,000	250,000	
3	1666	16,666	166,666	
4	1250	12,500	125,000	
5	1000	10,000	100,000	
6	833	8,333	83,333	
7	714	7,142	71,428	
8	625	6,250	62,500	
9	555	5,555	55,555	
10	5000	50,000	500,000	
2.0	2500	25,000	250,000	

Listings have been omitted where resistance values are at such high or low extremes that positive adjustment of the circuit be-