

ICD 08559

# MODERN ELECTRONICS™

SEPTEMBER 1986 \$1.95  
CANADA \$2.50

THE MAGAZINE FOR ELECTRONICS & COMPUTER ENTHUSIASTS


- Two-Band Stereo LED Power Meter
- Upgrading Radio Shack's Color Computer

*Complete Construction Plans:*

- Electronic Dice
- Experimenter's Aviation-Band Receiver

*Also:*

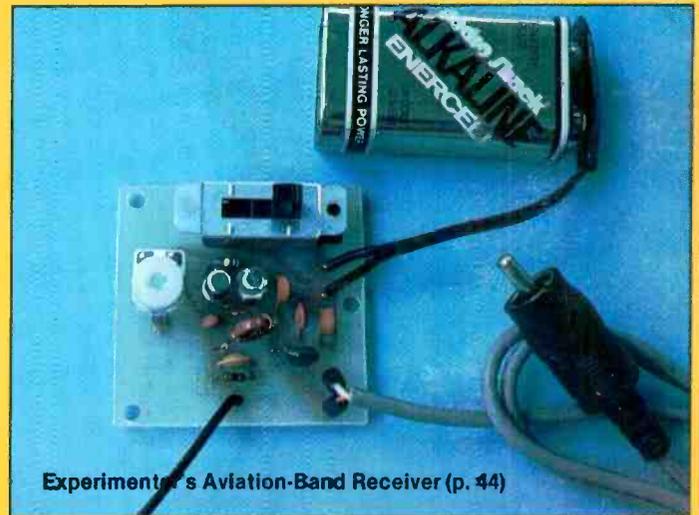
- All About Audio Circuits
- New Electronic Products Coming Up



Experimenter's Aviation-Band Receiver (p. 44)



Electronic Dice for Board Games (p. 52)

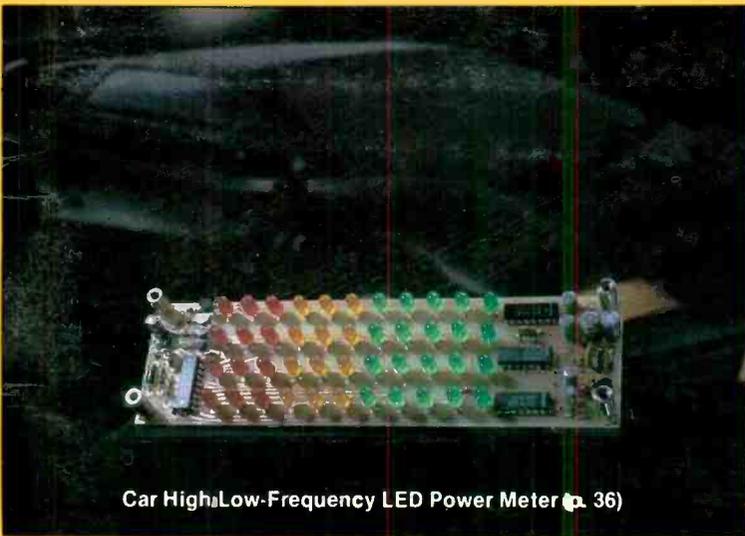

Car High/Low-Frequency LED Power Meter (p. 36)

Plus: Forrest Mims on Piezoelectric Buzzers ● Eric Grevstad previews Epson and AMQ Compatibles, Personal Publisher ● Don Lancaster answers readers' questions ● Glenn Hauser reports from the Caribbean ● New Technical Books ● Electronic & Computer News ... and more.



# New GPS Series: Tek sets the pace with SmartCursors™ and push-button ease.

Work faster, smarter, with two new general purpose scopes from Tektronix. The four-channel, 100 MHz 2246 and 2245 set the new, fast pace for measurements at the bench or in the field. They're easy to use and afford, by design.

**On top: the 2246 with exclusive integrated push-button measurements.** Measurements are accessed through easy, pop-up menus and implemented at the touch of a button. Measure peak volts, peak-to-peak,  $\pm$  peak, dc volts and gated volts with new hands-off convenience and on-screen readout of values.

SmartCursors™ track voltmeter measurements in the 2246 and visually indicate where ground and trigger levels are located. Or use cursors in the manual mode for immediate, effortless measurement of waveform parameters.

**Both scopes build on performance you haven't seen at the bandwidth or prices.** Lab grade features include sweep speeds to 2 ns/div. Vertical sensitivity of 2 mV/div at full bandwidth for

Features	2246	2245
Bandwidth	100 MHz	100 MHz
No. of Channels	4	4
Scale Factor Readout	Yes	Yes
SmartCursors™	Yes	No
Volts Cursors	Yes	No
Time Cursors	Yes	No
Voltmeter	Yes	No
Vertical Sensitivity	2 mV/div	2 mV/div
Max. Sweep Speed	2 ns/div	2 ns/div
Vert/Hor Accuracy	2%	2%
Trigger Modes	Auto Level, Auto, Norm, TV Field, TV Line, Single Sweep	
Trigger Level Readout	Yes	No
Weight	6.1 kg	6.1 kg
Warranty	3-year on parts and labor including CRT	


low-level signal capture. Plus trigger sensitivity to 0.25 div at 50 MHz, to 0.5 div at 150 MHz.

Accuracy is excellent: 2% at vertical, 2% at horizontal. And four-channel capability includes two channels optimized for logic signals.

**Best of all, high performance comes with unmatched convenience.** You can see it and feel it — in the

responsive controls and simple front-panel design, in extensive on-screen scale factor readouts, and in simplified trigger operation that includes Tek's Auto Level mode for automatic triggering on any signal.

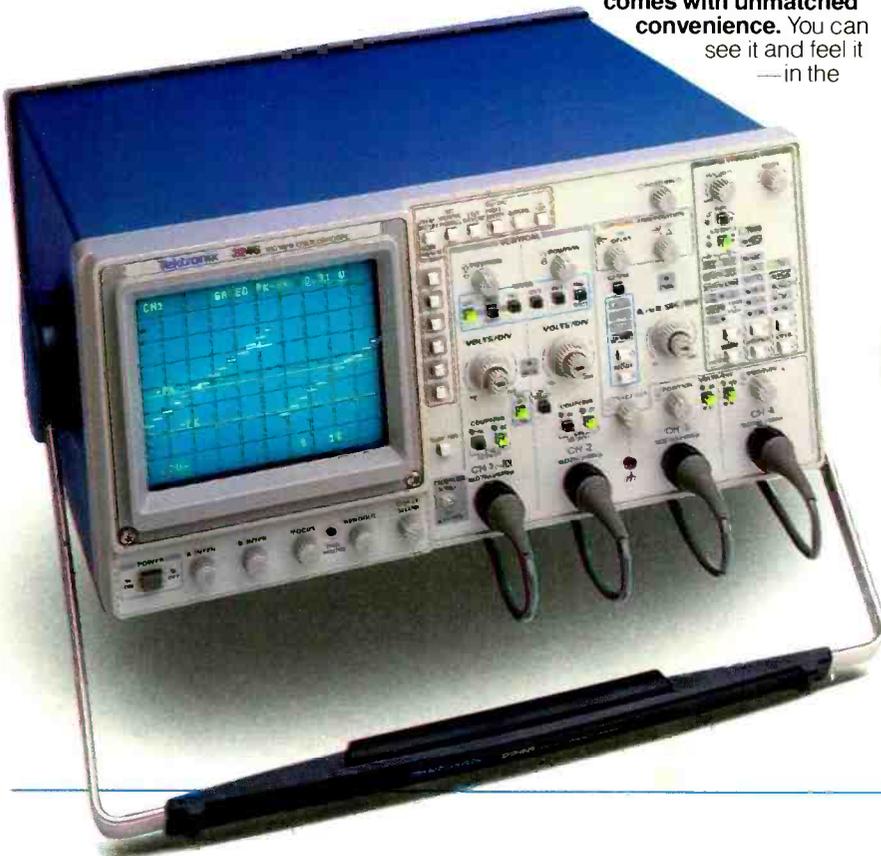**Contact the Tektronix office or sales representative nearest you for complete details.** Each scope is backed by Tek's three-year warranty, plus excellent documentation, training programs and outstanding service support — worldwide.




Featuring four channels, flexible triggering, extensive CRT readouts and push-button ease of use, the new Tek 2246 (left) and 2245 (above) bring high-quality, low-cost analysis to diverse applications in digital design, field service and manufacturing.

CIRCLE 78 ON FREE INFORMATION CARD

**Tektronix**  
COMMITTED TO EXCELLENCE
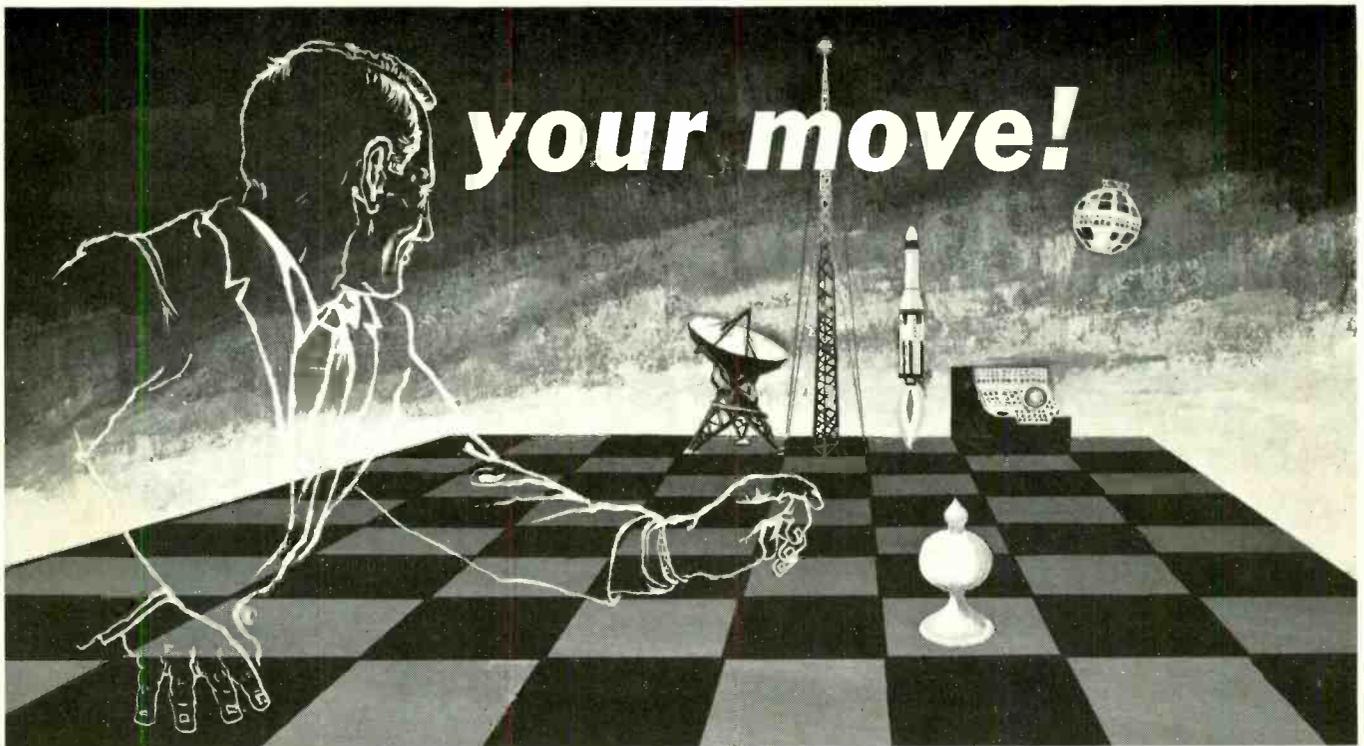
# Where's Your **ELECTRONICS** Career Headed?



## The Move You Make Today Can Shape Your Future

Yes it's your move. Whether on a chess board or in your career, you should plan each move carefully. In **electronics**, you can *move ahead* faster and further with a

## **B. S. DEGREE**

Put professional knowledge and a COLLEGE DEGREE in your electronics career. Earn your degree through independent study at home, with Grantham College of Engineering. No commuting to class. Study at your own pace, while continuing your present job.

The accredited Grantham non-traditional degree program is intended for mature, fully employed workers who want to upgrade their careers . . . and who can successfully study electronics and supporting subjects through

### **INDEPENDENT STUDY, AT HOME**

Free Details Available from:

**Grantham College of Engineering**  
10570 Humbolt Street  
Los Alamitos, California 90720

### **Independent Home Study Can Prepare You**

Study materials, carefully written by the Grantham staff for independent study at home, are supplied by the College, and your technical questions related to those materials and the lesson tests are promptly answered by the Grantham teaching staff.

### **Recognition and Quality Assurance**

Grantham College of Engineering is accredited by the Accrediting Commission of the National Home Study Council.

All lessons and other study materials, as well as communications between the college and students, are in the English language. However, we have students in many foreign countries; about 80% of our students live in the United States of America.

**Grantham College of Engineering** M-9-86  
10570 Humbolt Street, Los Alamitos, CA 90720

Please mail me your free catalog which explains your B.S. Degree independent-study program.

Name \_\_\_\_\_ Age \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

SEPTEMBER 1986

VOLUME 3, NUMBER 9

## FEATURES

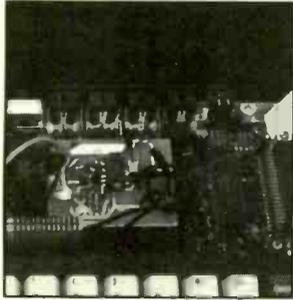


24

- 16 Solid-State Audio Circuits, Part 1**  
The basic transistor and IC circuits used in audio equipment. *By Joseph J. Carr*
- 24 Upgrading a Radio Shack "Bare Bones" Color Computer**  
Add 64K RAM, Extended BASIC and 64-column video output to CoCo. *By John Richardson*
- 32 Consumer Electronics Showcase**  
Latest product offerings to dealers for the second half of 1986 showcased at a major trade show. *By William Sommerwerck*
- 36 Two-Band Stereo LED Power Meter**  
Visually monitor your car stereo system's high- and low-frequency output power. *By Ross Ortman*
- 44 An Experimenter's Aviation-Band Receiver**  
Tunes in on airport and airborne radio activity. *By Dan Becker*
- 48 Using the Operational Transconductance Amplifier**  
Discover this often-disregarded op-amp. *By C.R. Fischer*
- 52 Electronic Dice**  
Project makes playing board games more fun. *By Bill Owen*



32

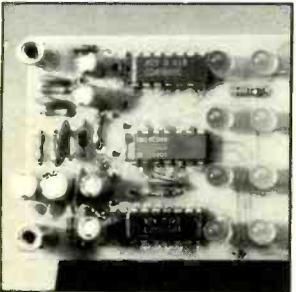

36



52

- ## COLUMNS
- 60 Electronics Notebook**  
Piezoelectric Buzzers. *By Forrest M. Mims III*
  - 66 Hardware Hacker**  
Author answers readers' questions. *By Don Lancaster*
  - 72 PC Papers**  
First Impressions: Epson and AMQ Compatibles; Personal Publisher. *By Eric Grevstad*
  - 76 Communications**  
Report from the Caribbean. *By Glenn Hauser*

## DEPARTMENTS

- 4 Editorial**  
*By Art Salsberg*
- 5 Letters**
- 6 Modern Electronics News**
- 12 New Products**
- 84 Books & Literature**
- 94 Advertisers Index**

## EDITORIAL STAFF

**Art Salsberg**  
Editor-in-Chief

**Alexander W. Burawa**  
Managing Editor

**Dorothy Kehrwieler**  
Production Manager

**Elizabeth Ryan**  
Art Director

**Barbara Scully**  
Artist

**Pat Le Blanc**  
**Florence Martin**  
Phototypographers

**Hal Keith**  
Illustrator

**Bruce Morgan**  
Photographer

**Joseph Desposito, Leonard Feldman,**  
**Eric Grevstad, Glenn Hauser,**  
**Don Lancaster, Forrest Mims III,**  
**Stan Prentiss**  
Contributing Editors

## BUSINESS STAFF

**Richard A. Ross**  
Publisher

**Art Salsberg**  
Associate Publisher

**Dorothy Kehrwieler**  
General Manager

**Frank V. Fuzia**  
Controller

**Arlene Caggiano**  
Accounting

**Cheryl Chomicki**  
Subscriber Services

## SALES OFFICES

**Modern Electronics**  
76 North Broadway  
Hicksville, NY 11801  
(516) 681-2922

Eastern Advertising Representative  
**Herb Pressman**  
76 North Broadway  
Hicksville, NY 11801  
(516) 681-2922

Midwest & West Advertising Representative  
**Market/Media Associates**  
1150 Wilmette Ave.  
Wilmette, IL 60091  
(312) 251-2541  
**Ted Rickard**  
**Kevin Sullivan**

Offices: 76 North Broadway, Hicksville, NY 11801. Telephone: (516) 681-2922. Modern Electronics (ISSN 0748-9889) is published monthly by Modern Electronics, Inc. Application to mail at second class rates pending at Hicksville, NY and other points. Subscription prices (payable in US Dollars only): Domestic - one year \$16.97, two years \$31.00, three years \$45.00; Canada/Mexico - one year \$19.00, two years \$35.00, three years \$51.00; Foreign - one year \$21.00, two years \$39.00, three years \$57.00. Foreign Air Mail - one year \$74.00, two years \$145.00, three years \$216.00.

Entire contents copyright 1986 by Modern Electronics, Inc. Modern Electronics or Modern Electronics, Inc. assumes no responsibility for unsolicited manuscripts. Allow six weeks for delivery of first issue and for change of address. Printed in the United States of America. Postmaster: Please send change of address notice to Modern Electronics, Inc., 76 North Broadway, Hicksville, NY 11801.



# Power to the Product!

## Low cost B&K-PRECISION DC power supplies with high cost features

**NEW**



**Model 1630 (3 amp) \$225**  
**Model 1610 (1 amp) \$150**

Now you can have the power you need, wherever you need it, at a surprisingly low cost.

These new B&K-PRECISION power sources each give you control up to 30 volts DC with fully adjustable current limiting. Other features include:

- Excellent regulation and low-ripple characteristics
- Dual meters monitor voltage and current simultaneously
- Two current ranges
- Fine and coarse voltage controls
- Isolated output
- Protected against reverse polarity external voltages
- Two identical supplies can be connected in series or parallel
- Can be used as a constant voltage or constant current source

Compare prices, features and performance, and you'll agree that the 1610 and 1630 power supplies are revolutionary.

Available for immediate delivery at your local B&K-PRECISION distributor. For additional information or the name of your local distributor contact B&K-PRECISION.

**BK PRECISION**  
**DYNASCAN**  
**CORPORATION**

6460 West Cortland Street  
Chicago, Illinois 60635 • 312/889-9087

International Sales: 6460 W. Cortland St., Chicago, IL 60635  
Canadian Sales: Atlas Electronics, Ontario  
South and Central American Sales:  
Empire Exporters, Plainview, NY 11803

CIRCLE 84 ON FREE INFORMATION CARD

# EDITORIAL

## Surging Back

You can't always count a product out when it loses favor. For a brief time, stereo hi-fi components seemed to have lost their appeal to some extent. In 1984, for example, factory sales dropped some 28 percent in dollars. We all heard that video was usurping its steady growth position, that personal computers had captured everyone's interest in its place, and so on. But as soon as the compact disc and player fired consumer interest, separate audio component sales surged back.

Some electronic products have "died," resurged, and then lost their appeal for one reason or another. CB radio is an example. Others showed enormous promise, such as videodisc players, going toe to toe with competing systems—in this case, videocassette recorders—only to lose out in the sales numbers game. Will it have another day? Then there are products that display cyclical appeal, such as personal computers. These machines had a relatively bad year in 1985, though the word "relatively" has to be underscored when talking about unit sales that exceeded four-million (down about one-million from the previous year).

Cordless telephones were "hot" in 1983 and 1984, the latter year peaking at 6.3-million units sold to dealers. Sales dipped appreciably to 4-million units in '85, though better designs that used dual frequencies and security codes were introduced to spur sales. So far, however, they haven't reached their previous popularity level.

Audio tape recorders are taking a back seat to CD players in the hearts and minds of people nowadays. But looming in the background, probably scheduled for 1987 introduction, is digital audio tape (DAT), which promises sound quality that approaches that of a laser-generated CD disc system, while adding recording capability. So here's a product that could, indeed, surge back.

Will cheap computers enjoy a resurrection? With low-cost IBM clones in abundance today and a greater awareness on the part of the public concerning what inexpensive computers can—and cannot—do, it's doubtful. Even Commodore International, which moved about 2¼-million computers last year, is facing financial troubles. Low-cost computers

declined by one-third last year on a world-wide basis. Nevertheless, Commodore has introduced an upgraded model C-64 with a graphics video environment—icons, mouse, pull-down menus—to stem the tide. Will this lead to a resurgence? Time will tell.

Household penetration is an indication, too, as to how popular a product is and how much play there is in sales potential. For home computers, 15% penetration is the estimate. So it's still a business/professional-oriented world for computers. Even VCRs, as popular as they are and as low as their selling prices have become today, were only in about 30% of U.S. homes by the end of 1985. At that juncture, it's interesting to note that 64.7% of *Modern Electronics* readers owned VCRs. Sony tried to bolster Beta-format sales by introducing hi-fi stereo sound, only to be matched by a similar development by VHS makers, so a resurgence there is unlikely. Now 8-mm and VHS-C camcorders are jockeying for position.

Will breadboarding of circuits slide away due to the rising star, computer-aided design (CAD)? More and more professional design engineers now sit in front of a computer workstation to design circuits instead of going to the breadboard/solder iron route, so it's possible. Prototypes will eventually have to be breadboarded, though. On second thought, this might be done directly on a pc board whose foil pattern was generated by computer.

It's rare to find a product that lost favor bouncing back unless some special advance calls for this to happen. Amateur radio, for example, does not exhibit growth in this country. But if the Morse Code test requirement was lifted, as it has been in many other countries, burgeoning equipment sales will surely follow.

Meanwhile, we'll all watch the moves that manufacturers make in enhancing older technology to capture our imagination as well as new technology that's implemented in a way that induces us to upgrade whatever we own.

*Art Salsberg*



**ANTI-STATIC SEATING.** With electronic devices and computer susceptible to damage by electrostatic discharges, anything that can be done to minimize this problem is welcome. Uniroyal's recently introduced anti-static NaugaStat U<sup>®</sup> upholstery fabric is an interesting step in this direction. The special grade of vinyl-coated material is said to help control static generated by chair and operator movement. According to the company, the new material has the capacity to dissipate a 5,000-volt charge in less than two seconds when using a suitable grounding path.

**ROBOT SAFETY STANDARD.** The first American National Standard for industrial robots has been approved by ANSI, establishing guidelines for construction, installation, and use of robots to safeguard people who work with them. There have been few robot-related accidents to date, but as the U.S. robot population increases from about 20,000 to an expected 75,000-100,000 in the next decade, proper safety procedures will be essential. Robot shipments in 1985 rose 33 percent to about \$443 million.

**ELECTRONIC CAR NAVIGATION.** An automotive navigation system concept is not new. There have been a host of developments, all very expensive; all depending on external assistance schemes such as satellite transmissions and road induction loops. Now, however, a European company, the largest supplier of automobile dashboard instrumentation, might change all this. The company, VDO Adolph Schindling, has developed a \$400 navigation system that employs the earth's natural magnetic field as a guidance reference point. Called Citypilot, the system is said to provide guidance accuracy to within 3 percent of the distance traveled. A light pen is used by the driver on a bar-coded map to plot the journey, which is inputted to an onboard microcomputer that displays distance and location information on a liquid-crystal display.

**THE OLDEST MICROCOMPUTER?** In a contest held by the Computer Museum located in Boston, Mass., the Kenbak-1 8-bit micro built in 1971 won. The designer, John Blankenbaker, said that about 40 machines were sold to schools with 256 bytes of memory, a 1-MHz clock and a serial memory organization. It only provided 1000 instructions per second, so was really an educational machine--not one that could be used, even if expanded, for applications programs. The MITS Altair 8800 was really the landmark computer, though, using a CPU that could address a lot of memory and a bus structure, the Altair bus, eventually dubbed the S-100, coupled with BASIC created by Bill Gates who later formed Microsoft.

**VHS/8-mm COMBO VCR.** Samsung Electronics created a storm at the Summer Consumer Electronics Show when it showed a prototype dual VCR deck that had VHS and 8-mm provisions on board, permitting dubbing from one to the other. The rub, to the Motion Picture Association of America (MPAA) was unauthorized copying prospects.

# SHOCK ABSORBER.



## **RCA's Power Safe surge suppressors absorb voltage surges before your customers' electronics get damaged.**

Now you can help your customers protect their expensive electronic equipment from sudden shock with two new surge suppressors from RCA.

The Power Safe (SK406) protects TVs, computers, microwaves and more by absorbing transient voltage surges resulting from nearby lightning strikes, load switching and other causes before the surge hits the equipment. Handsomely designed and easy to install, this handy six-outlet strip simply plugs into any grounded wall outlet.

The Power Safe Plus (SKF406) protects every way the Power Safe does, plus it filters out electronic noise interference. The suppressor's high-frequency bi-directional filter senses, absorbs, and dissipates noise interference before it can reach the equipment.

Together, they have the potential to become powerful profit builders for you.

To learn more about this shock-absorbing team, see your RCA Distributor. Or contact RCA Distributor and Special Products Division, Deptford, NJ 08096-2088.

**RCA** Distributor and  
Special Products Division

*NRI Trains You At Home—As You Build*

# GET THE KNOW-HOW TO SERVICE EVERY COMPUTER ON THIS PAGE...AND MORE.



IBM is a Registered Trademark of International Business Machines Corporation.

Epson is a Registered Trademark of Epson America, Inc.

Apple and the Apple logo are Registered Trademarks of Apple Computer, Inc.

Compaq is a Registered Trademark of COMPAQ Computer Corporation.

© 1985 AT & T Technologies, Inc.

# Your Own IBM-Compatible Computer

## Learn the Basics the NRI Way—and Earn Good Money Troubleshooting Any Brand of Computer

The biggest growth in jobs between now and 1995, according to Department of Labor estimates, will occur in the computer service and repair business, where demand for trained technicians will actually *double*.

You can cash in on this opportunity—either as a full-time corporate technician or an independent serviceperson—once you've learned all the basics of computers the NRI way. NRI's practical combination of "reason-why" theory and "hands-on" building skills starts you with the fundamentals of electronics, then guides you through advanced electronic circuitry and on into computer electronics. You also learn to program in BASIC and machine language, the essential languages for troubleshooting and repair.

### Total Computer Systems Training, Only From NRI

No computer stands alone. . . it's part of a total system. To successfully service and repair computers, you have to understand computer *systems*. And only NRI includes a complete computer system as part of your training, preparing you for the real world of computer servicing.

You start with the step-by-step assembly of the highly rated, IBM PC compatible Sanyo 550 Series computer. You install and troubleshoot the "intelligent" keyboard. Then you assemble the power supply,



install the disk drive and extra memory that gives you a powerful! 256K RAM system. Finally, you interface the high-resolution monitor and dot-matrix printer and begin to use the \$1,000 worth of software that's included. You're learning about, working with, servicing and troubleshooting an entire computer system—monitor, keyboard, computer, disk drive, power supply, and printer—all the essentials you'll meet every day as a computer service professional.

### No Experience Needed, NRI Builds It In

This is the kind of practical, hands-on experience that makes you uniquely prepared, with the skills and confidence you need for success. You learn at your own convenience in your own home. No classroom pressures, no night school, no need to quit your present job until you're ready to make your move. Your training is backed up by your personal NRI instructor and the NRI technical staff, ready to answer your questions and help you when you need it. You get it all from NRI!

#### Your NRI

- course includes the
- IBM PC compatible Sanyo computer with memory expansion to 256K RAM
- high-resolution monitor
- double-density/double-sided disk drive
- "intelligent" keyboard
- dot-matrix printer with near-letter-quality mode
- NRI Discovery Lab<sup>®</sup> to teach circuit design and operations
- digital multimeter
- logic probe
- spreadsheet, word processing software—and more.

### 100-Page Free Catalog Tells More

Send the postage-paid reply card today for NRI's big 100-page color catalog on NRI's electronics training, which gives you all the facts about NRI courses in Microcomputers, Robotics, Digital Electronics Servicing, Data Communications, TV/ Audio/ Video Servicing, and other growing high-tech career fields. If the reply card is missing, write to the address below.

**NRI** SCHOOLS

McGraw-Hill Continuing Education Center  
3939 Wisconsin Avenue  
Washington, DC 20016




We'll Give You Tomorrow.

For more information on products described, please circle the appropriate number on the Free Information Card bound into this issue or write to the manufacturer.
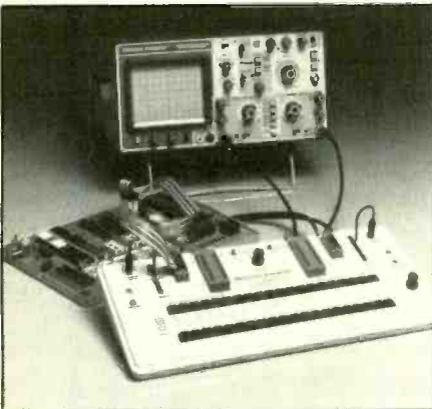
## Component Tester Accessory

Beckman's new Scopemate 2 oscilloscope IC and component tester accessory offers both in- and out-of-circuit test capabilities. It can be used with all types of analog, digital and hybrid components. The accessory compares a suspect device against a known good one, eliminating tedious pin-by-pin and contact-by-contact testing.




Connected to any dual-trace X-Y oscilloscope, Scopemate 2 tests for shorts opens, diode action and leakage by applying up to 14 volts rms at 300 mA to compare unpowered devices. It displays both good and bad signatures of the component being tested. Results are displayed as a graphic waveform, rather than in a numeric format that requires interpretation. Major differences in component signatures indicate a malfunction in the device being tested.

Supplied are an operators manual, two scope interconnect cables, four banana-to-clip leads, four banana-to-ground leads, 20- and 40-pin extension test cables and a plug-in power transformer. Scopemate 2 measures 14.5" x 7" x 1.5" and weighs 3.1 lbs. \$395.

CIRCLE 1 ON FREE INFORMATION CARD

## Power & Control Amplifiers

Technics has a pair of premium-

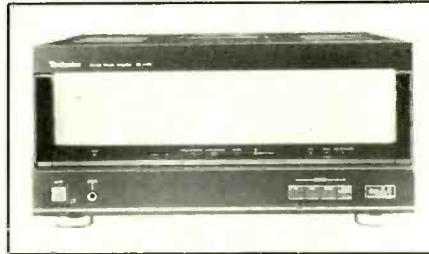

quality stereo products built around new class-AA circuitry. The Model SE-A100 stereo power amplifier develops 170 watts/channel into 8 ohms, 20 Hz to 20 kHz, at 0.0007% THD. Separate transformers in each current drive amplifier and a third transformer for the left and right channel voltage control amplifiers are said to help eliminate interchannel interference through the power supply. Two large power meters give readings from 0.0001 watt to 300 watts. \$1,500.

Class-AA technology in the Model SU-A200 control amplifier's phono equalizer and output circuit provide a rated S/N of 80 dB for MM and 73 dB for MC cartridges at 0.0008% distortion, 20 Hz to 20 kHz. Eight audio inputs are supplemented by one set of VCR input/output jacks, front and rear audio outputs and a video monitor output. CD signals can bypass the filter circuits and go directly to the volume control. A background video function allows the user to listen to one source while viewing another. \$1,000.

CIRCLE 2 ON FREE INFORMATION CARD

## Floppy-Based Handheld Computer

Sharp's new Model PC-1600 handheld computer features storage on 2.5" disks with an optional micro-floppy drive. The tiny computer features the first fiber-optic interface to be used in a handheld. A Z80A-like proprietary microprocessor is about 2.5 times faster than that used in Sharp's PC-1500 computer. The PC-1600 is software compatible with the PC-1500 and accommodates many of the peripherals designed for the PC-1500.



Featured are: 16K of RAM (expandable to 80K); a 4-line by 26-character LCD display; the fiber-optic interface; an analog input; an RS-232C serial interface; separate alphabetic keyboard and numeric keypad; a 60-pin I/O bus; and BASIC interpreter in ROM. Options include the microfloppy drive with 128K capacity; a 4-color pen plotter/cassette interface and a 32K RAM module. The computer measures 8"L x 3.5"W and weighs less than 1 lb. \$345.

CIRCLE 3 ON FREE INFORMATION CARD

## Deluxe Handheld Scanner

Regency's new Model HX1500 handheld programmable scanner provides a 55-channel capacity, 11 popular bands and selectable chan-



nel banks. Designed to compete in versatility with basestation units, it is claimed to offer more channel capacity than any other scanner on the market. Band coverage includes 10-meter Amateur; vhf low; vhf AM; vhf/AM Aircraft; Space Research; vhf Amateur; vhf high; Federal and Government Land Mobile; uhf Amateur; uhf; and uhf-T.

A sealed rubber keypad beeps when keys are pressed, and an LCD window displays the frequency entered and flashes messages that aid in programming. Channels can be grouped into any of four banks for fast scanning and easy access. A top-mounted control allows the user to activate the scan mode without removing the scanner from his belt. Included are dual scan speeds, priority channel, scan delay, search, direct channel access, earphone, flexible antenna and diecast aluminum chassis. \$369.95.

CIRCLE 6 ON FREE INFORMATION CARD

### *Tiny 8-mm Camcorder*

Claimed to be the world's smallest 8-mm camcorder, Olympus's 3.3-lb. Model VX-801 provides a 6× power zoom lens with auto focus, auto exposure and automatic white balance; dubbing and editing capabilities; and the ability to record from other video sources. An f1.2 lens and CCD image sensor allow recording under ambient lighting down to 10 lux.

Up to two hours of recording time is possible on a single cassette. Auto focus can be manually overridden, and two programmed white balance positions can override automatic white balance. Focus lock permits the user to pan, zoom in or out of a scene, and maintain sharp focus on one stationary object. A macro setting is provided for close-up shooting. The zoom lens has a 9-to-54-mm focal length range.

A flying erase head provides smooth transitions between scenes and other editing effects. An insert button makes editing from another




video player as easy as pressing a button. Two rotating heads in the FM recording system produce hi-fi monaural sound. The built-in electronic viewfinder can be adjusted to satisfy individual vision. Supplied are a unidirectional microphone, an ac adapter/charger and a 2-hour rechargeable battery pack.

CIRCLE 7 ON FREE INFORMATION CARD
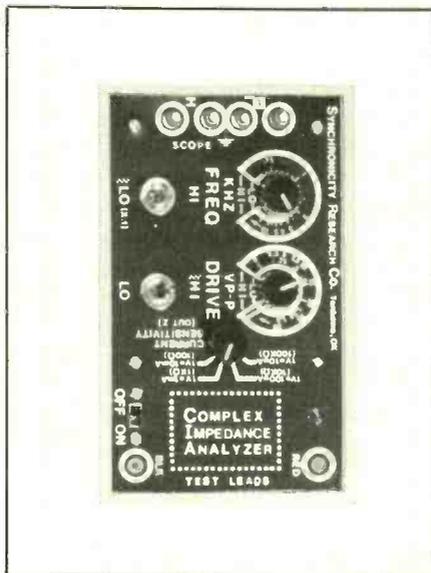
### *Complex Impedance Analyzer*

An advanced component analyzer that retrofits to an ordinary oscilloscope to display the E-I signature of components under test has been announced by Synchronicity Research (Tonkawa, OK). Called the Complex Impedance Analyzer, it uses a triangular instead of the usual sine wave test signal. Test signal frequency can be varied up to 10 kHz, its amplitude up to 30 volts peak-to-peak.

In addition to providing improved semiconductor tests, the instrument's triangle wave and wide frequency range are said to make it pos-



sible for the CIA to perform accurate inductance and capacitance measurements from less than 2 mH to beyond 200 H and from less than 100 pF to beyond 20 μF. The impedance of complex networks and transducers can also be measured. The CIA is battery powered for convenient field-service use, but it can also be used on a testbench.

CIRCLE 88 ON FREE INFORMATION CARD

### *Soldering Station*

OK Industries introduced a new soldering station with recessed temperature-selection switches that allows you to choose between 650, 750 and 850 degrees F. soldering temperatures without having to change tips. The tri-temperature Model SA-10's zero voltage heater power switching, low leakage and fast heat-up and recovery time features make this an ideal tool for a broad range of soldering applications.



The tri-temperature station uses J-type thermocouple sensing to provide stable and accurate temperature repeatability within ± 5 degrees Fahrenheit. The CMOS-safe plug-in soldering iron features a comfortable, cool grip and a non-burn cord. It includes the soldering station with switches and indicators, soldering iron, long-life tip and tip cleaning sponge. Both 117- and 230-volt ac models are available, each with 24-volt, 48-watt handpieces.


CIRCLE 83 ON FREE INFORMATION CARD

### *Portable Motion Detector*

The Model 870 "Infralert" from Eltec Instruments is a portable passive infrared sensor that is claimed to use
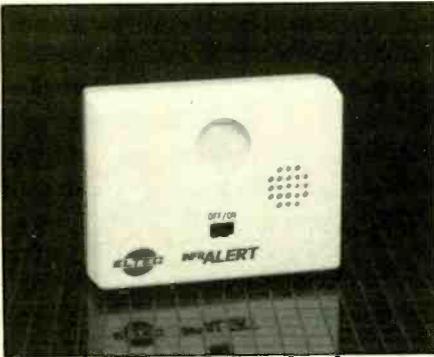
## NEW PRODUCTS ...

the same technology as that used in state-of-the-art intruder alarms. Its alarm tone automatically sounds when a person or object moves into its line of sight. Infralert can be used to monitor temporarily restricted or hazardous areas, merchandise cases, display windows, doors and windows, stairways, gunracks, swimming pools, etc.



The device is powered for up to a year by a single 9-volt battery. It uses fixed-focus optics that give it a narrow field of view that is less likely to interfere with normal room activities than is possible with wide-field-of-view systems. Its built-in delay circuit gives you time to arm the system and leave the protected area without tripping the alarm.

CIRCLE 16 ON FREE INFORMATION CARD

### *In-Dash CD Player/Receiver*

Panasonic Auto Products' Model CQ-E800 15-step random-access programmable CD player with digital AM/FM-stereo receiver consists of one unit that fits into the dashes of most American-made cars and a support electronics unit that goes under a seat. A special suspension system protects the player's miniaturized laser pickup against vibrations and jolts. Features include a skip key and scan, pause, on-track repeat and automatic loading functions.

The preamplifier has volume, fader, balance, bass and treble controls, plus output terminals for connection to a booster amplifier. The tuner section offers scan and seek functions and instant access to 12 FM and 6 AM stations that the user stores in



memory. An LCD window displays recalled station and frequency (tuner mode) and elapsed time, selection in play and CD selections stored in memory (CD mode).

Electrical noise is handled by Impulse Noise Quieting (INQ) circuitry. An automatic FM Optimizer (FMO) helps improve FM reception in weak signal areas. \$699.95.

CIRCLE 17 ON FREE INFORMATION CARD

### *GPIB Tool Kit*

Integrating an IBM PC into a GPIB instrument system has been simplified with Tektronix's new GPIB tool kit. The GPIB Users Resource Utility package, known as GURU, consists interface board with self-test/diagnostics, a shielded GPIB cable, tutorial manual and software support, including a test procedure generator and subroutines library.

GURU's manual provides instructions on how to use the IBM PC and compatibles to control instrumentation via the GPIB and includes programs and a user resource library of applications programs. GURU provides a software tool that allows you to generate a program that executes a prescribed test sequence without having to write code. All you need know are the details of the task to be per-

formed and follow the instructions and answer menu questions, with GURU generating the required routine.

You can call any of the 16 BASIC subroutines that allow you to focus on the problem rather than the bus. These interactive subroutines include instrumentation selection and setup, range and tolerance tests, waveform acquisition and storage, and waveform graphs and statistics. Each subroutine performs a regular check for errors. \$600.

CIRCLE 18 ON FREE INFORMATION CARD

### *Satellite TV Systems Troubleshooter/Tester*

Satellite Test Equipment Co.'s (Scottsdale, AZ) new Model ET-15 satellite troubleshooter and test set is reported to allow a user with minimal technical background to troubleshoot a satellite TV system in 15 minutes or less. The microprocessor-controlled test set produces all signals required at 15 GHz (K band), 4 GHz (C band), and most single and block frequencies.

The ET-15 tests LNAs, LNBs, downconverters, polarizers, TV receivers and monitors, any satellite receiver, cables and splitters. Among its features are a signal-strength meter with a peaking function for setting up antenna dishes and a continuity tester






for checking motor drives and sending devices. It also features an external video input that accepts a camera, VCR or computer signal. \$799.
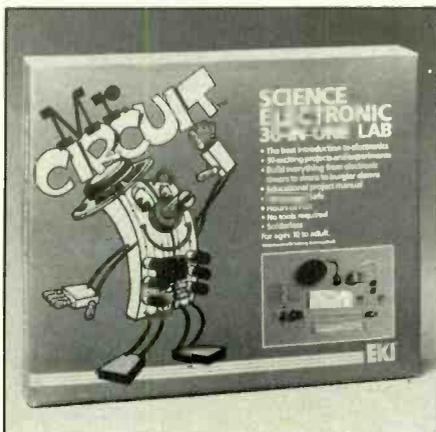
### Electronics Education Lab


The Mr. Circuit 30-in-One Lab from Electronic Kits International is the first in a series of learn-by-doing electronics education kits. It allows people who are interested in learning about electronics to have fun while quickly assembling a variety of relatively simple projects. There are 30



different projects in all, ranging from fun devices like and electronic canary to practical devices like an ultrasonic pest repeller. Some projects can even serve as test instruments, like the diode and transistor checkers and an audio generator. Projects are assembled on a solderless breadboarding socket, using reusable supplied components and wires. Everything needed to assemble the projects, except a 9-volt transistor battery, are supplied in the kit.

(Continued on page 96)

# Free Famous hi-tech catalog

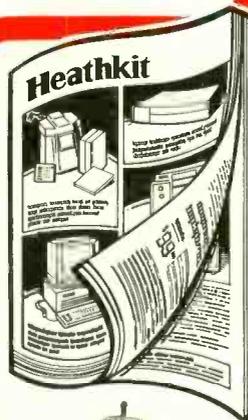

**A very special computer & electronics guide that shows you what the exciting world of kitbuilding can do for you.**

Challenge. Knowledge. Achievement. Enjoyment. All of these things are yours when you build a Heathkit high-quality product. Our colorful, informative catalog reflects the years of experience and technological expertise that make these things happen for you.



HERO® 2000 Educational Robot and Courseware  
IBM-PC Compatible Expandable Computers

Amateur Radio Terminal Node Controller

Precision Test Instruments

Electronic Keyless Doorlock

In our catalog you'll find over 450 interesting and useful items – from computer hardware and software to robots and test instruments, and from home security systems to color tv's and amateur radio equipment.

But what makes Heath Company unique is that we offer you the confi-

dence and pride that you can only get by building a state-of-the-art product yourself. And you're backed by our promise, "We won't let you fail."

The Heathkit Catalog is a simple – and FREE – first step toward this excellent opportunity.

**Send NOW for your FREE Heathkit Catalog**



**Yes!** I want to see what kitbuilding can do for me. Please send me the latest Heathkit Catalog Free.

Send to: Heath Company, Dept. 079-452  
Benton Harbor, Michigan 49022

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

Zip \_\_\_\_\_

**Heathkit**

Heath Company

A subsidiary of Zenith Electronics Corporation

CL-787R1

# Solid-State Audio Circuits

## Part 1

By Joseph J. Carr

Audio circuits are among the most interesting of linear circuits with which to experiment. They are excellent as weekend and one-evening projects for electronics hobbyists and experimenters. Part of the reason for their popularity is that they are so useful to so many people; another is that they are generally well-behaved and, thus, can easily be built with low-cost components.

In this first installment of our two-part article, we discuss the basic circuits used in modern audio-amplifying equipment and explore both discrete transistor and integrated-circuit (IC) audio amplifier circuits. The information contained here will lay the groundwork for the more detailed discussions of circuits, built around actual components, that will appear in next month's conclusion.

### Transistor Biasing

One of the most important factors in understanding solid-state audio circuits is the methods used to achieve proper biasing of transistors. Figure 1 shows several of the most common methods. These circuits, or variations of them, are used in most discrete and IC audio circuits.

Figure 1A shows the simplest—and most practical—biasing scheme. Fixed base-current bias is established by current flow from the emitter-base junction of the transistor through  $R1$  to the supply voltage. The amount of bias is dependent on the value of  $R1$  and the supply voltage. The primary disadvantage of this bias arrangement is that it provides no means of automatically limiting collector current. Hence,

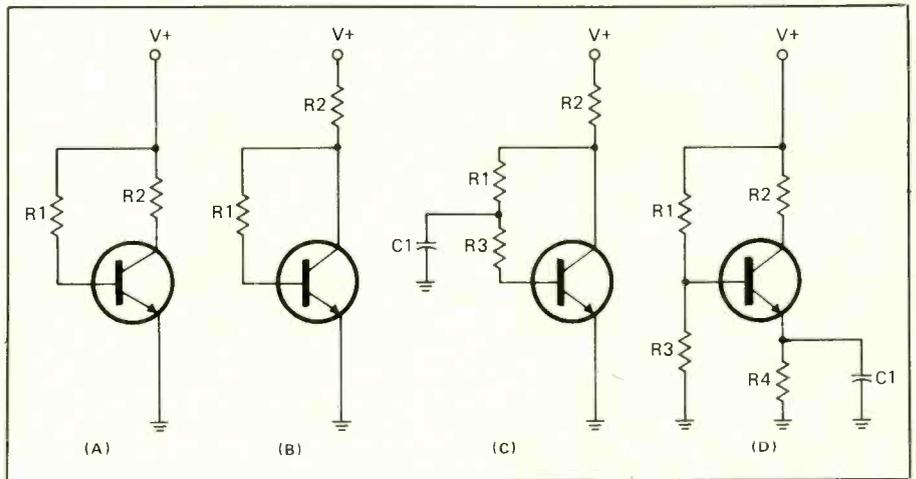


Fig. 1. Several of the most common methods for biasing transistors.

fixed base-current biasing yields circuits that can be unstable.

Another simple form of self-bias, shown in Fig. 1B, is called collector feedback. Because  $R1$  is connected to the transistor side of load resistor  $R2$ , any change in collector current will cause a proportional but opposite change in transistor bias. For example, if collector current increases because of a temperature increase, the voltage at the collector decreases (becomes less positive). In turn, this reduces the current through the emitter-base junction and  $R1$  circuit. Although this bias system does provide a degree of stabilization, it also introduces degeneration caused by feedback of any ac signal voltage developed across the load resistor.

Collector-feedback with ac bypassing is the same as in Fig. 1B, except that an electrolytic capacitor has been added to filter out (bypass) variations.

Combination fixed and self-bias (Fig. 1D) provides both good stabilization and minimum degeneration. Fixed emitter-base bias is developed by the  $R1/R3$  voltage divider. Usual-

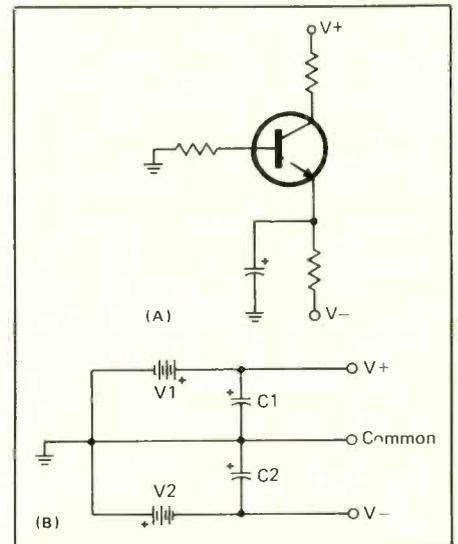


Fig. 2. An amplifier biased for dual-polarity power supply operation (A) and a typical dual-polarity power supply (B).

ly, the value of  $R3$  is substantially less than that of  $R1$ . Resistor  $R4$  stabilizes the transistor. For example, if emitter-to-collector current increases because of an increase of temperature, the voltage drop across  $R3$  also increases. This places a more-positive voltage on the emitter,

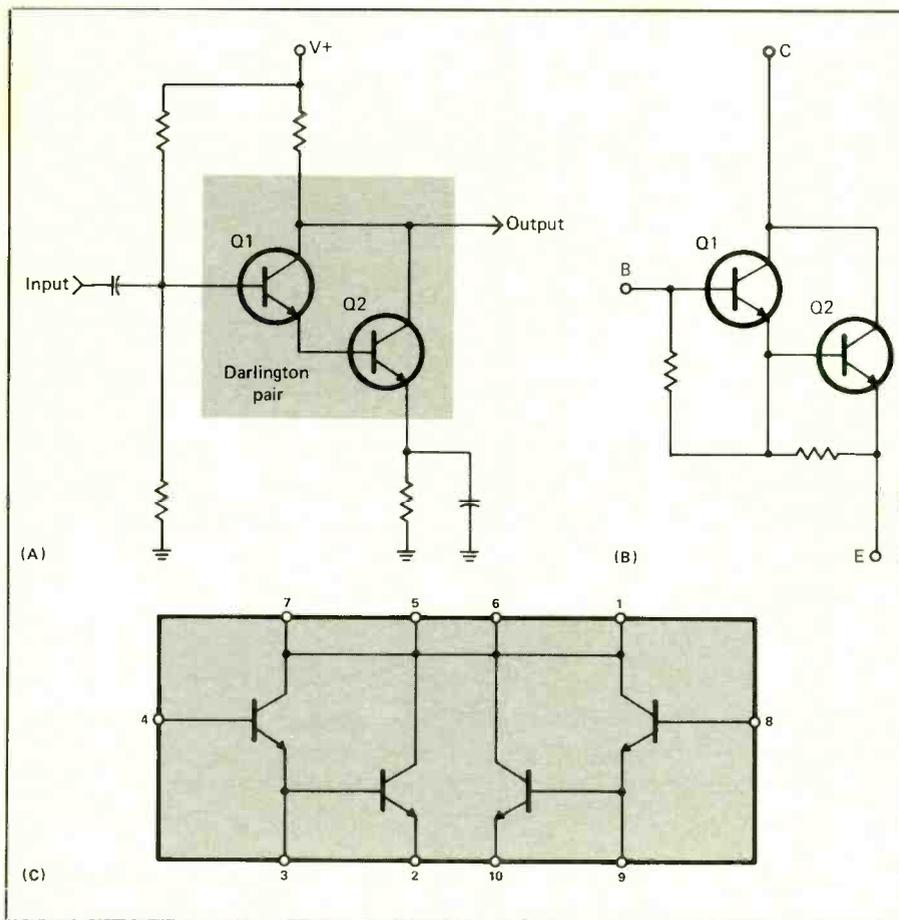


Fig. 3. A Darlington amplifier configuration built around two discrete transistors (A). Though the Darlington arrangement contains two separate transistors, when wired together as shown, the two can be treated as one transistor with single base, emitter and collector leads (B). Matched dual-Darlington transistor pairs are also available in convenient IC package form (C).

ing used more often in solid-state audio applications is the Darlington amplifier—also called the Darlington pair, or the “super-beta” transistor (when both transistors are inside the same package). An example of this configuration is shown in Fig. 3A. Notice that the collectors of the two transistors are tied together. Also note that the emitter of the input transistor is tied directly to the base of the output transistor. This arrangement produces higher current gain and a much higher range of input impedance than is possible with single bipolar transistors. Beta gain is  $H_{fe} = H_{fe}(Q1) \times H_{fe}(Q2)$ .

If the transistors are identical, overall beta gain is the square of the beta gain of any one transistor. You can see why this configuration is called “super-beta” by a simple example. Suppose two transistors with a beta of, say, 100 are connected in a Darlington configuration as in Fig. 3A. Overall beta of this combination is  $100 \times 100 = 10,000$ .

Although discrete transistors can be connected in the Darlington circuit, several manufacturers offer Darlington-configured transistors in one package, or integrated-circuit Darlington amplifiers. Figure 3A shows the internal circuit of a Darlington transistor. Most often, the device is a power amplifier in which Q1 is a driver transistor and Q2 is an output power transistor. One common Darlington pair in hi-fi amplifiers uses a 2N3053 for Q1 and a 2N3055 for Q2.

Figure 3C shows an IC dual-Darlington amplifier. This particular device is the RCA CA3036. There are also operational amplifiers and special-purpose ICs on the market that use a Darlington amplifier as the input circuit.

### Audio Power Amplifiers

There are several basic designs for audio power amplifiers. For pur-

which reduces the forward bias on this transistor. The capacitor bypasses ac variations around the emitter resistor to prevent degeneration. The value of R4 usually is five to ten times less than that of R3.

The dual-supply method (Fig. 2A) is a not so universally recognized biasing circuit as some of the others, but is being used more and more in modern circuits. It can be identified by the fact that the ground (or common) is not returned to the positive or negative side of the dc power supply. (The Fig. 2B circuit represents the kind of dc power supply used: two voltages, one positive to ground and the other negative to ground). Instead, in most applications, the

ground, usually the chassis or a printed wiring board ground bus, “floats” at the electrical mid-point of the two supplies. In most cases, the two voltages are equal; in others, V- and V+ are different.

Increased output voltage swing is one of the advantages of the dual supply circuit, regardless of whether discrete transistors or integrated circuits are used. Another advantage is improved thermal stability. This can mean a lot in an amplifier that has marginal heat sinking or that is used inside a closed cabinet. A third advantage is that these circuits tend to be less sensitive to hum pick-up caused by power supply ripple.

Another type of circuit that is be-

poses of discussion let us turn to the Fig. 4 circuit. This basic audio amplifier chain has been used in a lot of equipment over the years. There are three stages shown: preamplifier, driver and power amplifier. The preamplifier builds up the voltage level of the input signal. The driver raises the power level of the amplified signal sufficiently to drive the output power amplifier stage. The output power amplifier, of course, develops the power to drive the loudspeaker.

In Fig. 4B is shown a simple circuit used in many car and home radios, though rarely in high fidelity applications. This single-ended class-A amplifier uses a choke or autotransformer for output impedance matching. It has several disadvantages. For one thing, as a class-A amplifier, the output collector current flows 100 percent of the time, even when there is no input signal. As a result, a lot of heat is generated. In some cases, a 3- to 5-watt fuse resistor ("fusistor") is placed in series with the transistor to protect the circuit if excess heat causes  $Q1$  to blow. Another disadvantage is that fidelity is not too good unless feedback is provided. Though the fusistor provides a small amount of beneficial degenerative feedback, additional feedback must be provided in most cases.

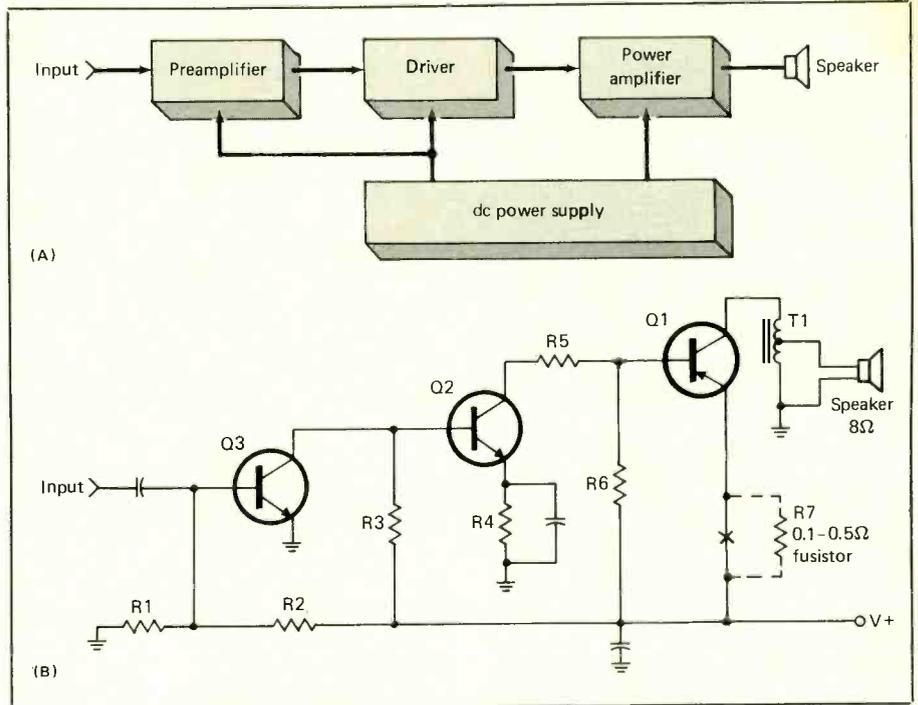


Fig. 4. A typical audio-amplifier chain contains preamplifier, driver amplifier and power amplifier stages, all powered by a common power supply. This arrangement is shown in block diagram form in (A), while (B) shows the schematic equivalent sans power supply.

Two basic kinds of feedback circuits are normally used in audio circuits. One is called the "second collector-to-first emitter" system (Fig. 5A). With correct values of components, this circuit can make a relatively mediocre amplifier sound like a more expensive one. Figure 5B shows the second widely used feed-

back system, dubbed the "second emitter-to first base" system. This circuit often employs only one resistor to supply feedback signals.

The push-pull circuit is widely preferred over other types for both power handling ability and overall fidelity. Figure 6 shows the standard transistor push-pull circuit that has

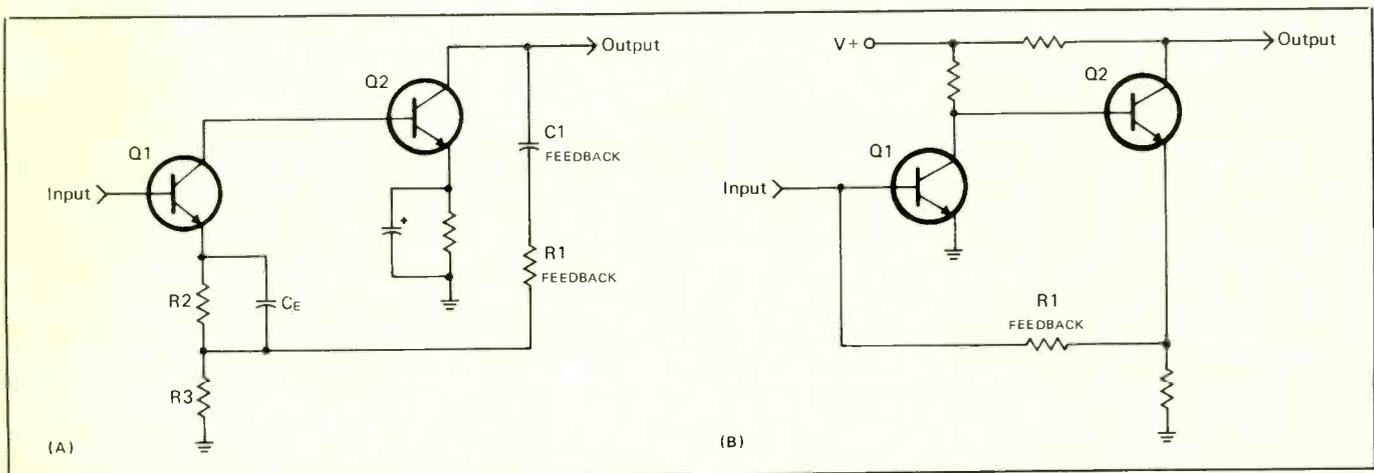


Fig. 5. The two basic kinds of feedback circuits normally used in audio circuits: second collector to first emitter (A) and second emitter to first base (B).

# EXPAND YOUR CAREER HORIZONS...



*The CIE Microprocessor Trainer helps you to learn how circuits with microprocessors function in computers.*

## START WITH CIE.

Microprocessor Technology. Satellite Communications. Robotics. Wherever you want to go in electronics... start first with CIE.

Why CIE? Because we're the leader in teaching electronics through independent study. Consider this. We teach over 25,000 students from all over the United States and in over 70 foreign countries. And we've been doing it for over 50 years, helping thousands of men and women get started in electronics careers.

We offer flexible training to meet your needs. You can start at the beginner level or, if you already know something about electronics, you may want to start at a higher level. But wherever you start, you can go as far as you like. You can even earn your Associate in Applied Science Degree in Electronics.

Let us get you started today. Just call toll-free 1-800-321-2155 (in Ohio, 1-800-362-2105) or mail in

**CIRCLE NO. 171 ON FREE INFORMATION CARD**

the handy reply coupon or card below to:  
Cleveland Institute of Electronics,  
1776 East 17th Street, Cleveland, Ohio 44114.

### CIE

**World Headquarters**

**Cleveland Institute of Electronics, Inc.**  
1776 East 17th Street • Cleveland, Ohio 44114

Please send your independent study catalog.  
For your convenience, CIE will try to have a representative contact you — there is no obligation.

Print Name \_\_\_\_\_

Address \_\_\_\_\_ Apt. \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Age \_\_\_\_\_ Area Code/Phone No. \_\_\_\_\_

Check box for G.I. Bill bulletin on Educational Benefits

Veteran  Active Duty **MAIL TODAY!**

Just call toll-free 1-800-321-2155 (in Ohio, 1-800-362-2105)

MO-64

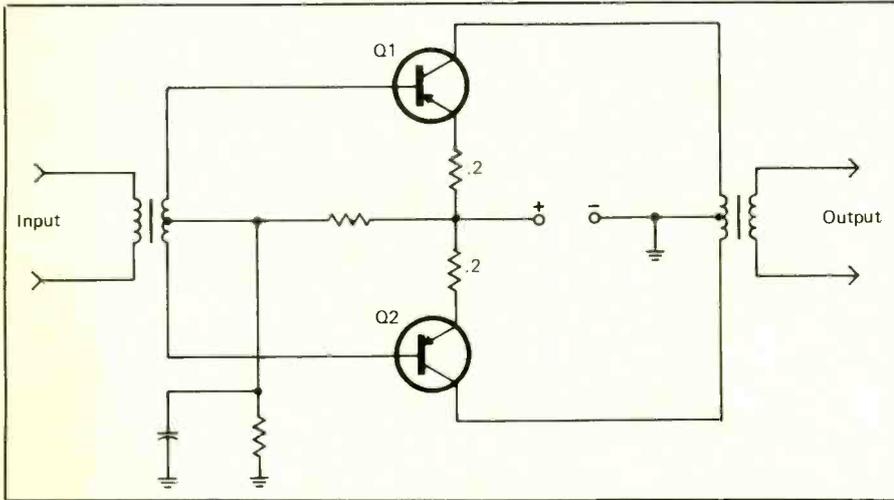


Fig. 6. A typical push-pull amplifier stage with transformer input and output. Note that this arrangement requires a dual-polarity power supply.

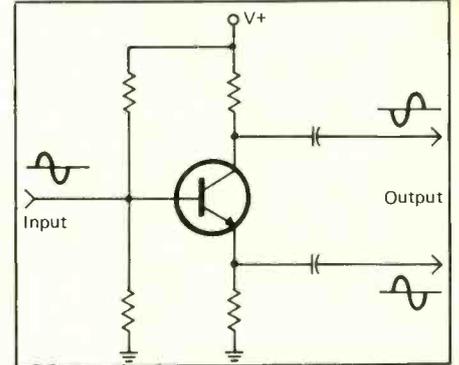


Fig. 8. A transistor phase inverter is one possible replacement for the interstage (input) transformer needed for the opposite-polarity driving signals for the two halves of the push-pull amplifier circuit.

been used in almost every audio application, from \$5 portable radios to relatively high-priced, medium-grade radios and stereos. It is, however, a lot less cost-efficient when compared with other circuits of more recent design.

Another breed of push-pull amplifier is shown in Fig. 7. Often called the "split-secondary, totem-pole" circuit, this one is used in many domestic and (especially) imported radios. The series connection of the output transistors and split-

secondary interstage transformer *T1* are the two identifying features of this type of circuit.

One thing that all push-pull amplifiers have in common is the necessity of phase-splitting the input signal to provide two new signals 180 degrees out-of-phase to drive the two halves of the push-pull circuit. In older designs, this was accomplished with either a center-tapped transformer (Fig. 6) or a split-secondary interstage transformer (Fig. 7). In many modern circuits, however, the inter-

stage transformer is replaced by another means to split the input signal.

The transistor phase inverter is one possible replacement for the interstage transformer. These circuits (Fig. 8) have one driving signal taken from the collector, the other from the emitter of the transistor. Another method of providing drive signals of opposite polarity is to use an IC pre-amplifier that has both inverted and noninverted output terminals. Such ICs provide wideband, push-pull outputs from a common input signal. An example is shown in Fig. 9. This particular circuit is based on the RCA CA3020 IC preamp.

Designers have other methods of accomplishing phase inversion that is often more economical than either of the other methods. These methods are also used in IC and hybrid audio power amplifiers, and are called "complementary-symmetry" and "quasicomplementary" amplifiers. Complementary-symmetry methods, shown in simplified form in Fig. 10, take advantage of the fact that pnp and npn bipolar transistors require signals of opposite polarity to perform the same basic function. Notice that the speaker, minus output transformer, is connected to the midpoint of the two series-connected

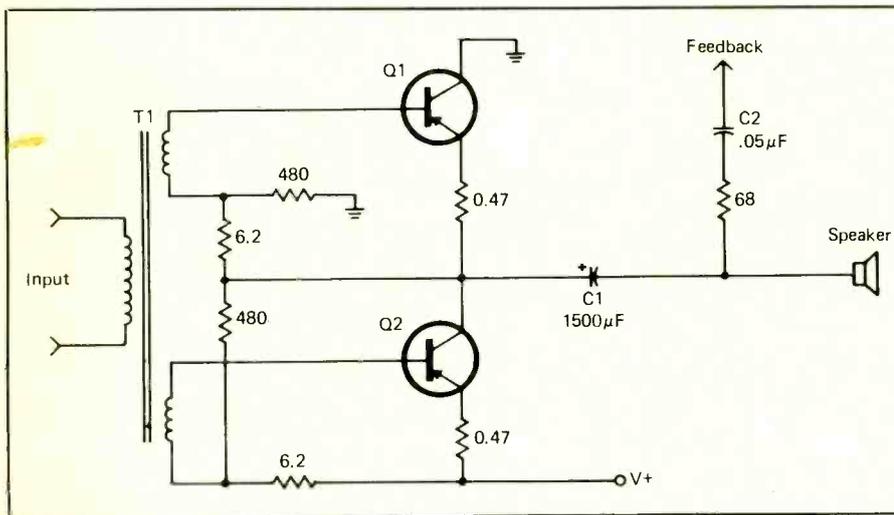


Fig. 7. The split-secondary totem-pole amplifier is similar to the conventional push-pull amplifier, except that it has no output transformer and can operate with a single-polarity power supply.

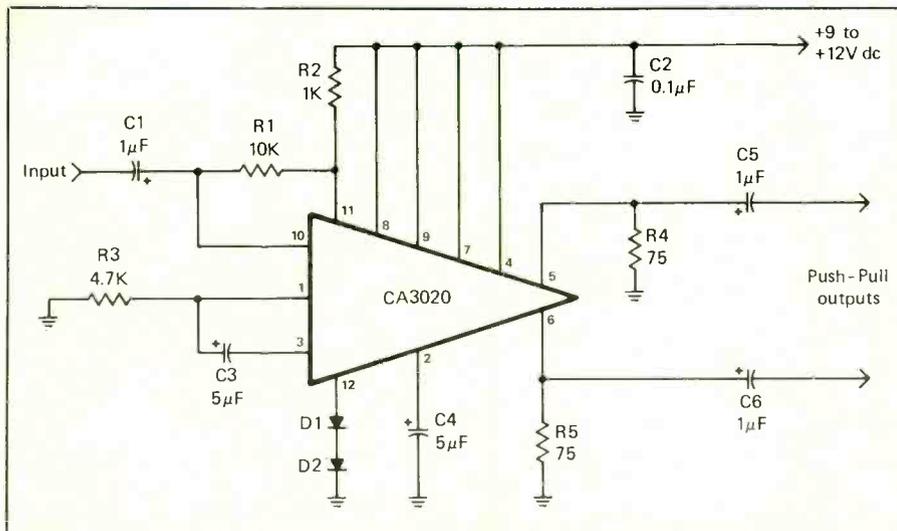


Fig. 9. An IC amplifier that has inverted and noninverted output terminals offers another way of obtaining phase-inverted signals for push-pull operation.

pairs of transistors for low- and medium-power complementary circuits. It is even relatively easy to find matched pairs for medium-power (a few watts) applications. But at higher power, the problem is greater. This has led to an interesting modification of the complementary-symmetry circuit, called the quasicomplementary circuit shown in Fig. 11. This circuit uses a "totem-pole" output in which the same type of npn or pnp transistors are in series with each other, and complementary driver stage  $Q1/Q2$ . It is fairly easy to find the medium-power complementary drivers and matched (identical) output transistors required for this type of circuit.

### Coming Next Month

This concludes our primer on the general theory of transistor and IC audio amplifiers. In next month's concluding part of this article, we will discuss the details of audio pre-amplifier and tone-control circuits built around actual commonly available components. **ME**

power transistors. Versions of this circuit that use a single asymmetrical dc power supply usually employ a capacitor to block dc from the speaker circuit. (The voltage at point "A" is usually  $V+ / 2$ ). Dual-polarity circuits do not require the capacitor.

Complementary-symmetry amplifier circuits have at least one major disadvantage: It is difficult to locate matching pnp and npn transistors. Manufacturer "spec" sheets reveal that there are only a few types that can be paired for complementary

service at any given output power level. As the amplifier's power level increases, the number of available types decreases dramatically. The problem becomes even more acute when selecting service replacements for these transistors.

It is relatively easy to find matched

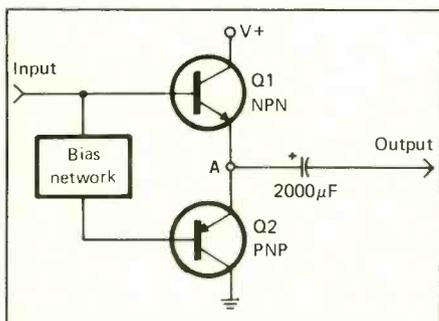


Fig. 10. An economical way of obtaining phase inversion is with the so-called "complementary-symmetry" circuit that uses npn and pnp transistors. Versions of this circuit that use a single asymmetrical power supply usually have a capacitor that prevents dc from getting to the speaker.

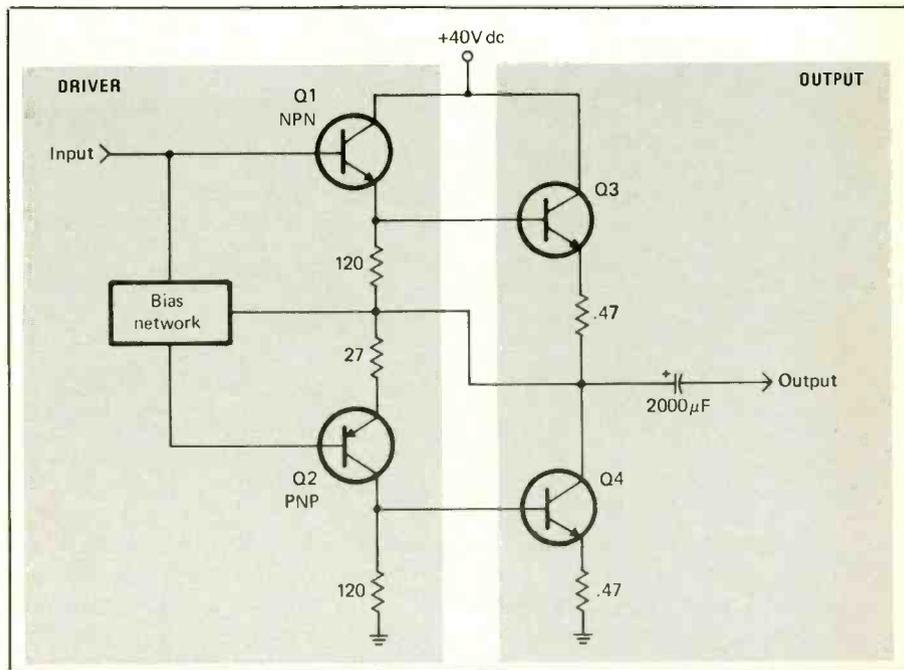


Fig. 11. The "quasicomplementary" circuit uses the same type of npn and pnp transistors in a totem-pole arrangement and a complementary driver stage consisting of  $Q1$  and  $Q2$ .

# Upgrading a Radio Shack “Bare Bones” Color Computer

*How to add 64K RAM, Extended BASIC and 64-column video output to CoCo*

By John Richardson

One of the hottest selling holiday-season products last year was Radio Shack's “bare bones” Color Computer II, featuring 16K of memory (RAM) and Standard BASIC. Priced at only \$88 they sold like ice pops in July, but many buyers soon discovered that its 16K RAM and “standard” version of BASIC doesn't do very much. Well, here's how to inexpensively upgrade it to run *World Class* word processing and telecommunications software—stuff that puts to shame a lot of the mega-buck software being sold for even “business computers.”

Basically, all it takes is less than \$50 and an evening's effort to upgrade the CoCo II to a high-performance computer having both 64K RAM and a video monitor output capable of displaying 64 columns, rather than the CoCo's normal 32 column TV display. With these one-evening retrofits you can then run *MikeyTerm*, a public domain modem program, and *Telewriter-64*, an under-\$70 word processor that's easier to use, much easier to learn, and even more powerful than *WordStar* (it can transmit any printer control codes), and it can directly save its files in ASCII or binary.

Unlike most modern telecommunications software that requires considerable time and effort to learn to



use, and which requires frequent reference to the documentation if not used every day, *MikeyTerm* operates from a single menu. Even more important, it features *dynamic buffer control*, which in plain English means the user can instantly select and save parts of the incoming text because it takes only one key to open/close the receive buffer, which is later dumped to mass storage.

Upgrading the 16K CoCo II is a lot like making over Cinderella from a “Plain Jane” into a princess because most of what's needed is already there. The only extras required for high-performance word processing and telecommunications is a video output for a conventional composite


monochrome or color monitor, and sufficient RAM to store many pages of the text—preferably 64KB. Also, if you want to get into sophisticated programming you'll need Extended BASIC—an enhanced version of the BASIC used in the higher priced versions of the CoCo II.
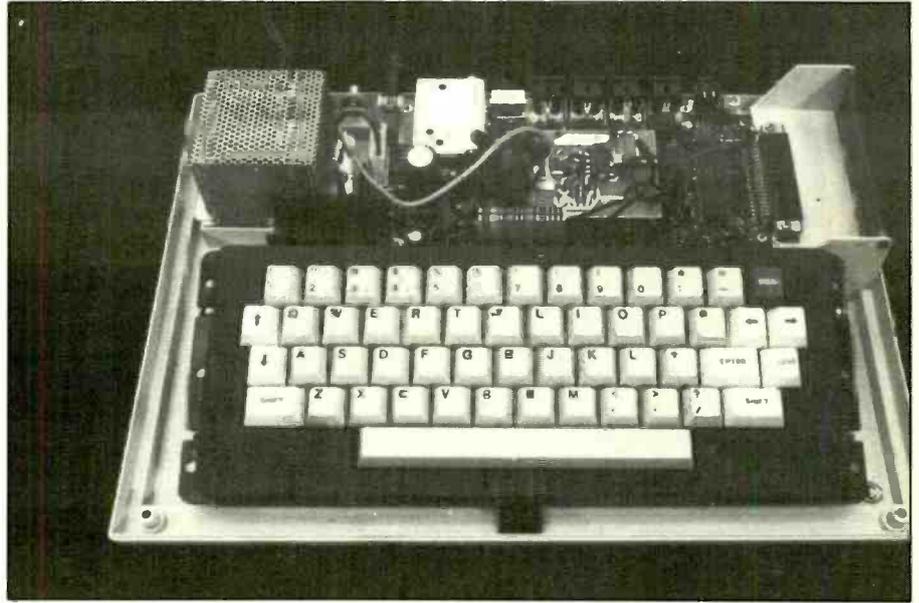
## *Built For Factory Upgrades*

From the introduction of the original CoCo—what enthusiasts call the CoCo I—Radio Shack intended the 16K computer to have its RAM and BASIC upgraded by its own service stations, so sockets and jumpers were built into the motherboard for just about every integrated circuit



One of six screws that must be loosened to open the cabinet is hidden under the label that warns against opening the case. To get at it, push the tip of a Phillips screwdriver through the label.



With the top off, you have access to CoCo's entire interior.

and the RAM address programming. In the upgrades we'll shortly describe, you will simply utilize the sockets that Radio Shack provided for its own use. The only thing Radio Shack would not do was install a composite video output to go along with the TV output, so in later versions of the CoCo they actually made it more difficult—almost *impossible*—to retrofit a conventional video monitor output; but you will easily get around this mine field.

### The Monitor Problem

Since the CoCo was designed to use a conventional color TV as a monitor, its output was an rf signal on either TV channel 3 or 4 (user selected). Unfortunately, the bandwidth of a TV set can *cleanly* resolve only 30 to 40 characters per line. Since "standard" business correspondence is usually considered to be 64 characters per line, the aftermarket word processor Telewriter-64 needed a monitor capable of greater than the CoCo's 32 columns. This required a conventional video monitor, which was provided by a \$30 aftermarket retrofit video monitor adapter. To

do the above, one simply removed the existing *video display generator* (VDG) IC from its socket, plugged in the retrofit video adapter, and then installed the VDG in a socket on the video adapter. It was that easy. But for whatever the reason, Radio Shack eliminated the VDG's socket in later CoCo models, making it necessary for the modifier to either unsolder the 40-pin VDG or solder the video adapter's wires directly to the

VDG's pins. Either way, it could result in damage if the person wasn't experienced in miniature assembly.

But regardless of how hard a manufacturer tries to restrict the user to his products, aftermarket vendors will find a way to get around the roadblocks, and that's just what happened in the case of the video drive. One of the original vendors of retrofit video monitor adapters simply equipped their adapter with mini-



To remove the keyboard, lift it straight up and gently flip it back to the rear.


clips that the user hooks over the appropriate VDG terminals (and three motherboard locations). While the retrofit might appear at first glance to be a rat's nest of wires, the mini-clips avoid soldering to the VDG's pins. Although the clips move, they are firmly locked in place and, most important, the thing works—though you won't believe it when you first complete the retrofit. Actually, it is easier and safer to install the new kind of mini-clip video adapter.

### ***Making The Retrofits***

The first step in upgrading a 16K CoCo II is to open the case and remove the keyboard so that you can get at the RAM and VDG. Just moving the keyboard out of the way isn't sufficient; it must be removed to avoid possible damage. To open the cabinet you first loosen the six screws on the underside. You will actually see only five screws because the sixth is concealed under the small black label that says the warranty is voided if the cabinet is opened. Simply push a Phillips screwdriver through the label to get at the screw. Note: (The factory knows you have opened the cabinet if the label is broken.) Since the screws are two different lengths, mark which holes get the short screws and which the long ones. Actually, a better way to handle the screws is to simply loosen them and then place a strip of tape over their holes so they won't fall out.

Holding the cabinet together by hand, flip the computer right-side up, then gently lift the top of the cabinet straight up and off. The top comes off very easily: don't pry or bend the edges if it's stuck. If you can't get the top off, the problem is most likely a screw that isn't fully released, or a missed screw.

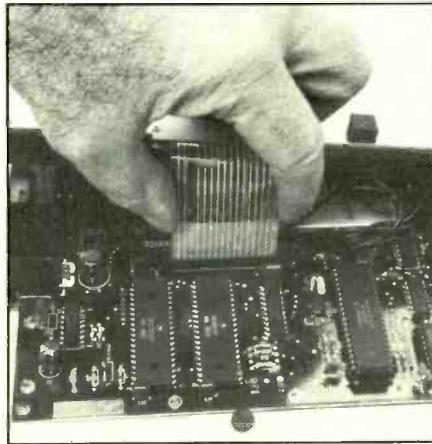Next, remove the keyboard, taking care not to damage its plastic connecting cable. Do it this way. Lift the keyboard clear of its mounting posts and flip it backwards, placing



*Do not grip the keyboard's ribbon cable as shown to unplug it from the motherboard; it might be damaged. Instead, grip it on both sides between thumb and forefinger and lift straight out.*


it gently on the motherboard. You will see that the keyboard connects to the motherboard through a wide plastic strip having silver-color conductors. It will appear that the ribbon is permanently attached to its motherboard connector, but it's not. The small black block on the mother-

board that secures the ribbon is really a socket.


With thumb and forefinger, grasp both sides of the ribbon directly above the motherboard connector and gently rock the ribbon from edge to edge while applying a slight pulling force. The ribbon will work loose and come out of its connector. Don't rush the job and pull too hard: gentle persuasion will get the ribbon free without damage. (Don't bother to mark the ribbon because it can go back only one way.) When the ribbon is free, lift the keyboard straight out and set it safely aside, making certain you don't lose the small black rubber washers that fit on the posts under the keyboard. You now have access to the entire motherboard.
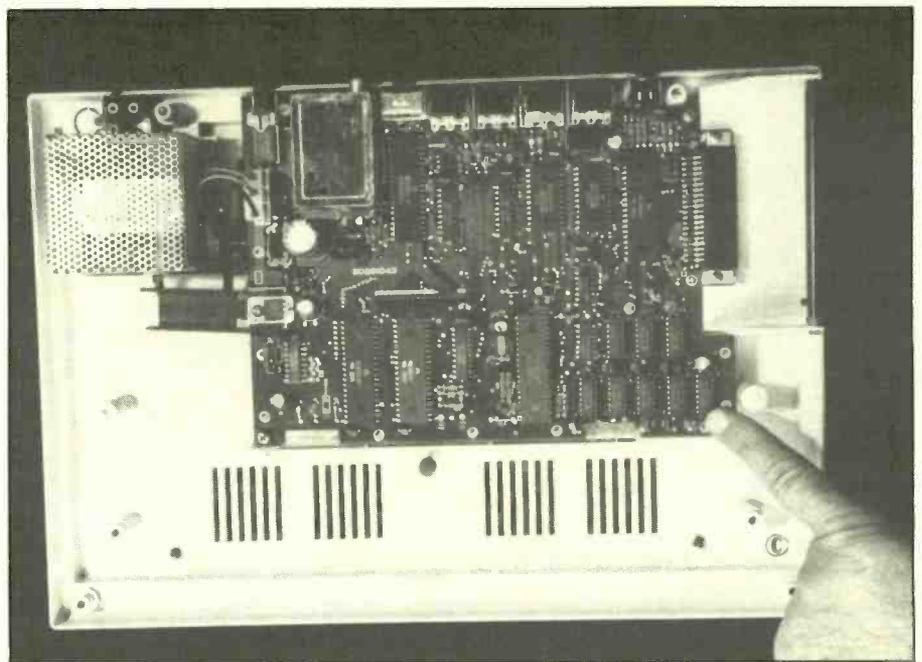
### ***More Memory***

Make the memory upgrade first. There have been several different versions and configurations of the CoCO since its introduction, but whether it has 4K, 16K, 32K or 64K of RAM it uses eight socketed RAM chips to provide the rated memory.



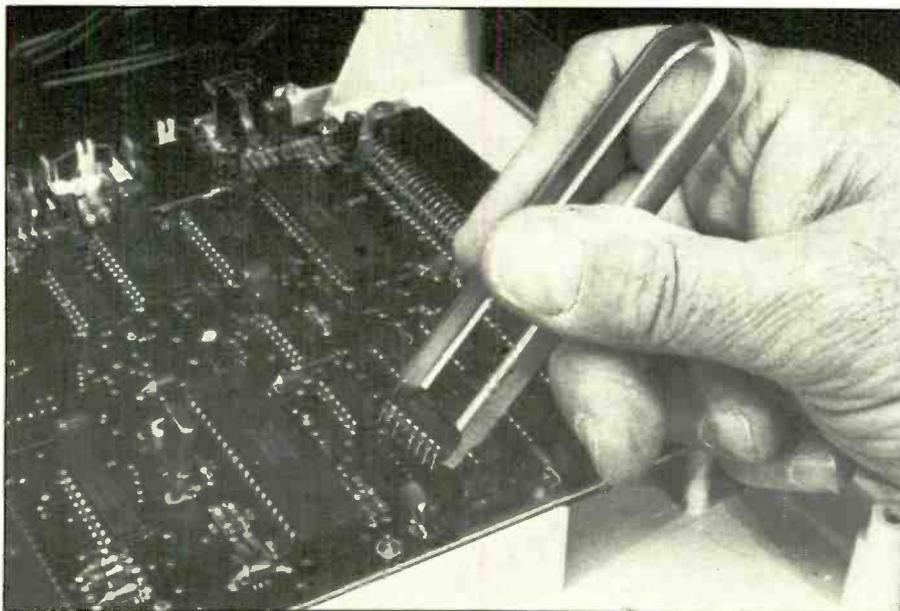*Eight socketed memory ICs are in the lower-right of the motherboard. Remove the factory-installed 16K chips and replace them with 64K chips.*



*Use an extracting tool to remove the 16K RAM chips.*

In earlier models of the CoCo, it was necessary to remove a metal shield and cut some capacitors to upgrade RAM to 64K. Neither is necessary in the new version. There is no shield over the memory chips: you simply replace the existing memory chips with 4164s—the same inexpensive

64K chips used in the IBM PC—and short-circuit two solder mini-pads from the top of the motherboard.

Several variations of the 4164 are sold for the IBM PC, and they might not even be identified as a 4164. The rule is: if the chips are sold as 64K RAMs for the IBM PC or the Color

Computer they can be used. Generally available “IBM substitutes” are the 4564N-20 and 4164P, which presently sell for as little as 99 cents apiece. It makes no sense to spend more than \$30 for a set of eight “official” 64K CoCo chips.


### ***Only A Swap***

First step in memory upgrade is to simply swap new chips for the old. Since the ICs are sensitive to static electricity, make certain you are grounded through a ground strap (attached to the metal clip of your watchband) or a grounding bracelet. After you're grounded, remove all eight original 16K memory chips using some kind of extraction device. Don't try to flip the chips out of their sockets using a screwdriver unless you have had experience doing it because a little too much force can damage the socket, and then you're in for a lifetime of intermittent glitches. Make certain the pins of the new ICs are straight—use needlenose pliers if it's necessary to straighten them—and snap the chips into their sockets, making sure the notch at one end of the chip corresponds to the position of the notch of the original IC (they all face the same way) and that no pins fold under as you push the chips home.

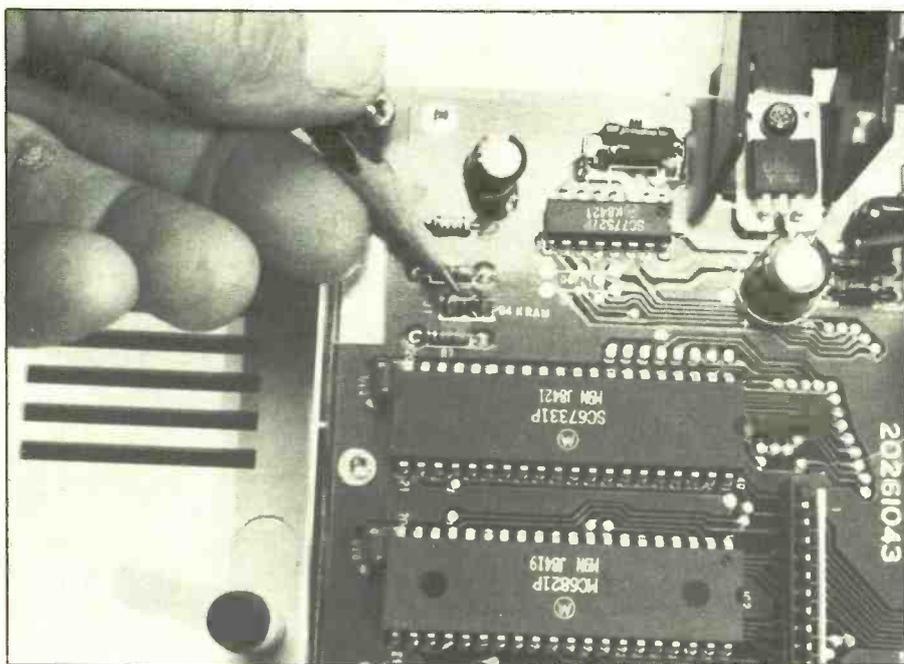
### ***Programming for 64K***

After all eight memory ICs are installed, locate the two small solder pads at the upper-left corner of the motherboard labeled “64K RAM.” Simply soldering a jumper across the solder pads programs the CoCo for 64K. Install the jumper from the top of the board; don't attempt to remove the motherboard from the cabinet for this operation.


Using a very small pencil soldering iron tip, melt the solder in one hole and slip in the end of a short length of pretinned #20 or #22 solid, bare wire. Form the wire into a small ¼" loop, position the free end over the



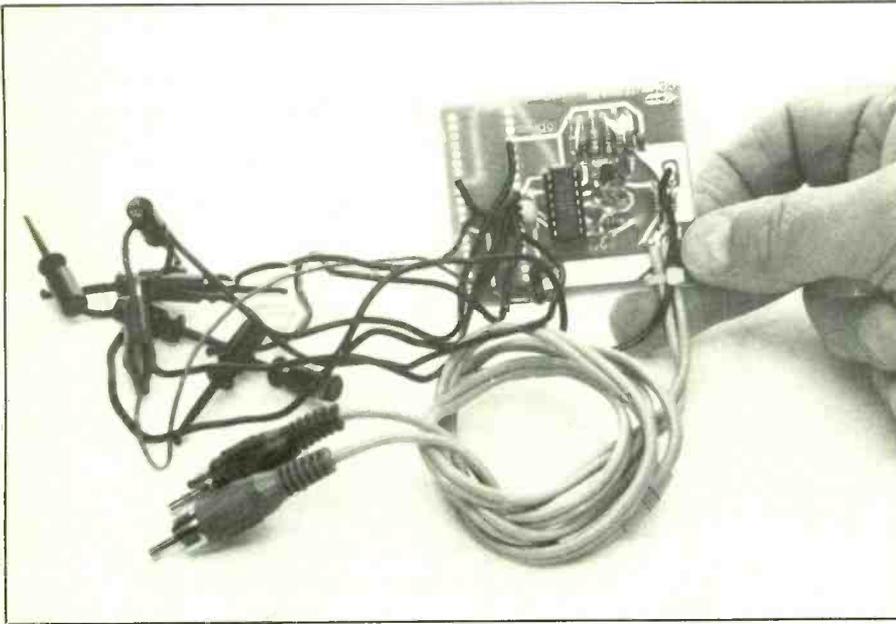*Program the CoCo to address 64K of RAM by soldering a wire across the two “64K” solder pads located at the upper-left of the motherboard.*



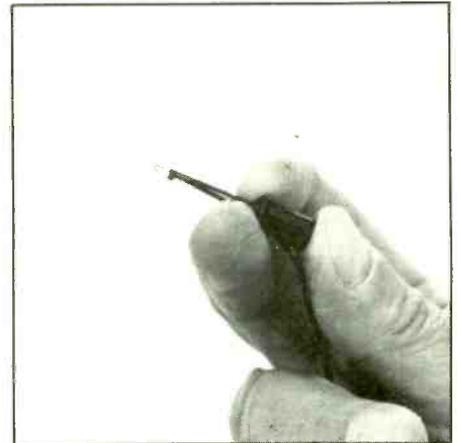*Interconnects from the small commercially available video adapter board connect to the CoCo via wires terminated in mini-clips. The two cables terminated in phono plugs are the new video and sound outputs.*



*The display board's mini-clips provide a secure connection when the spring-loaded "body" is released.*

second solder pad, heat the pad and force the pretinned free end of the wire into the hole. That's it!

### ***Enhanced Basic***

If you think you will want Enhanced BASIC, install the Enhanced BASIC retrofit ROM now—before the video adapter is installed—because it's possible the video adapter will get in the way if you try to do it later. You can purchase the Enhanced BASIC upgrade ROM from Radio Shack or any of several vendors that sell parts for the CoCo. (Since the price is the same, get it the most convenient way.) Simply snap the Enhanced BASIC upgrade ROM into the matching empty socket in the top-right of the motherboard. You can't miss it because it's the only empty socket. Just make certain the notched end of the ROM faces the rear of the motherboard.


### ***Installing The Video Adapter***

There are several kinds of video monitor adapters floating around from CoCo aftermarket vendors; for

ease of installation we recommend the Universal Video Plus, the one shown in the photographs here. To install the Universal Video Plus

adapter simply match its clip leads to the VDG. On the adapter are a set of 40 holes corresponding to the VDG's terminals. Seven holes have clip leads. Just match the seven and connect the remaining clips to the locations specified in the instructions supplied with the adapter.

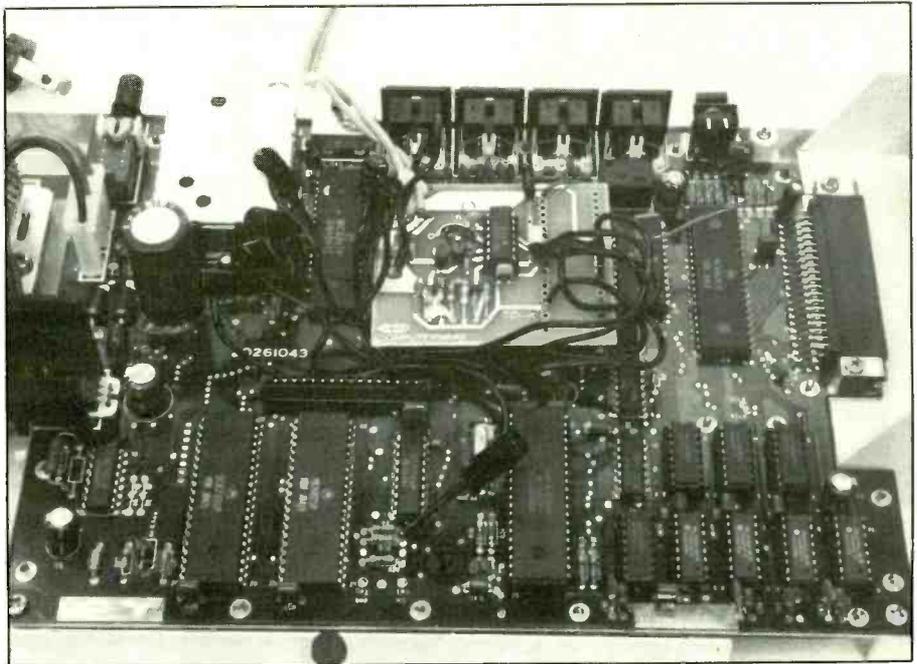The adapter is secured to the top of a large IC by a piece of double-



*The video adapter mounts on top of an IC with double-sided tape (supplied with kit). Installing the adapter with holes to the right lets you tuck most of excess wire lengths under the board's front edge.*

sided tape. It's very sticky and you get just one shot to secure the adapter. To make certain the adapter does not interfere with reinstalling the keyboard, position it so its left edge is adjacent to the VDG, and as far to the rear of the motherboard as possible. In this location the adapter drops down on an IC and sticks in place.

The adapter provides separate audio and video outputs at standard phone connectors. If you have no need for the sound output, you can cut off its shielded cable at the adapter. While you could notch out the cabinet and let the video (and audio) cables simply hang free, the wire is actually too short to reach a monitor's rear input jack. Thus, it will require a female-male extension, which isn't all that easy to locate.

Instead, we suggest you install a standard phono jack ( $\frac{1}{4}$ " mounting hole) in the bottom of the cabinet about  $\frac{3}{4}$ " to the right of the power switch (an open area inside the cabinet), cut off the existing video connector, and connect the video output cable to the phono jack using the most direct cable routing (cut off the excess cable). If you also want the audio output, there is room in the same area for a second phono jack.


The video adapter has a small trimmer potentiometer, which is the output level control that must be adjusted after the keyboard is installed.

---
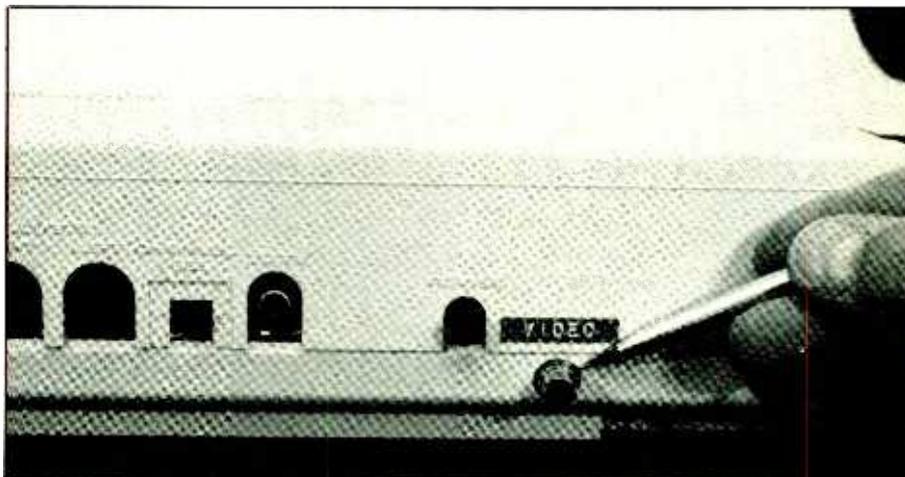
### More Video

---

The video adapter's output is either color or monochrome, but not both simultaneously. It is supplied set for monochrome. If you want to use a color monitor, cut the small wire jumper on the adapter's printed circuit board. If you want to have the option of color *or* monochrome, cut the jumper and connect each lead to a miniature slide or toggle—*not* momentary action pushbutton—switch. Install the switch on the cabinet wherever you would like to have it.



*Instead of bringing the video cable through the cabinet, you can install a phono jack on the CoCo's cabinet to the right of the power switch and connect the cable to this. If you are using the audio option, do the same for its cable. Label jack(s) for easy identification.*

Both the video and rf outputs are simultaneously active, meaning you can use both a composite monitor and a TV monitor at the same time; or at the very worst, you can use either without having to connect or disconnect cables. Of course, if you are displaying 60 or 80 characters on the composite monitor, it will barely be legible on an ordinary TV monitor.

---

### Install the Keyboard

---

To install the keyboard, rest it on its back toward the rear of the motherboard (the same position it was in when you removed it). Then slide the ribbon straight down into its connector. It will be a tight fit, so don't push too hard or you might bend or damage the plastic. Grab both sides of the ribbon about  $\frac{1}{2}$ " back from the end and, if necessary, rock the ribbon from side to side as you gently push down. Once the ribbon slides in it's connected, even if it appears to be just slightly seated. (The ribbon does not go very far into the socket, about  $\frac{1}{8}$ ", so if it seems to be seated it probably is.)

Install the rubber washers back on the posts and flip the keyboard forward onto the posts. Finally, make

your checks and adjustments before closing the case.

---


### Checkout

---

Connect a composite monitor to CoCo's video output and fire up the computer. Adjust the small trimmer potentiometer on the video adapter for a decent screen display. Check that all the keyboard keys work. If not, *turn off the power* and check the seating of the keyboard cable. You might get some strange color box patterns when the computer is first turned on, but if the computer seems to work okay just forget them.

When you're certain all the retrofits are working, adjust the video trimmer for best picture. Write a small BASIC program to fill the screen with characters and then adjust the video trimmer for maximum screen brightness coincident with minimum blooming of the individual characters. Also, fiddle with the monitor's own brightness and contrast controls, interacting them with the adapter's trimmer.

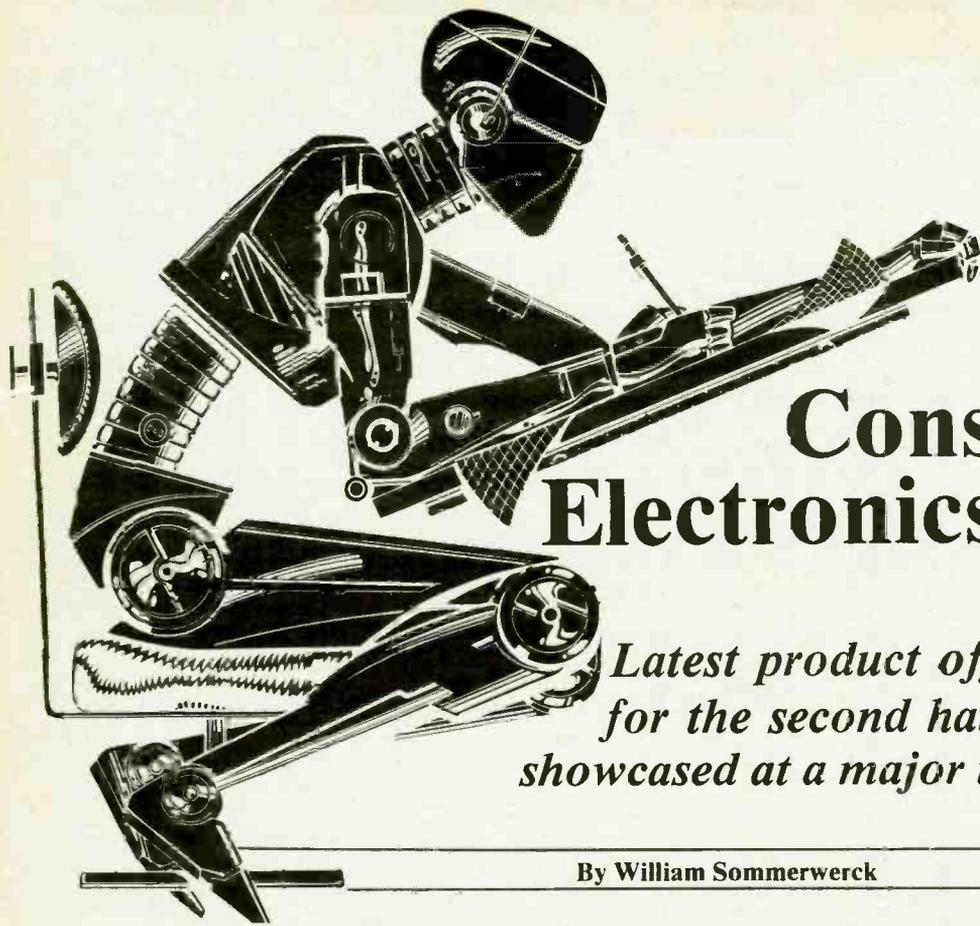Then reassemble the cabinet when you're satisfied with the video adapter's adjustment. Your new 64K video-output CoCo is now ready to use as a powerful computer. **ME**



# Consumer Electronics Showcase

*Latest product offerings to dealers  
for the second half of 1986 are  
showcased at a major trade show*

---

By William Sommerwerck


---

**C**elebrating its 20th year in electronics show biz, the past Summer Consumer Electronics Show was bigger than ever. With more than 1,400 exhibitors spread out over about 725,000 square feet, the whole spectrum of current and com-

ing up consumer electronics products could be seen if one had the time and energy to pursue it fully. Here are some products that were especially interesting because they were innovative, high quality or struck my fancy as I wended my way around the exhibits.

**Acoustic Research**, after an absence of nearly 15 years, again has a line of electronics, including pre-amp, tuner, CD player, power amp, integrated amps and receivers, most of which sport single-system remote control. AR is also going after the Bose "RoomMate" market, with its "powered pARTner," a portable speaker/amp with separate woofer and tweeter, and a hefty 15-watt output.

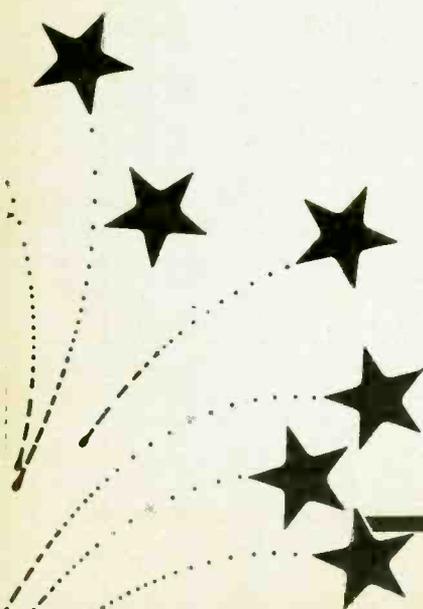**Atari** finally released its 7800 video game system and a selection of interesting games. The 7800 system is claimed to have the highest resolution of any home computer or video game, and will also play regular 2600 cartridges. Atari says it'll support the 7800 with more titles. Guess the company believes there's still a spark of life left in this entertainment electronics area.




**Casio's** new SK-1 keyboard can record any sound, which is then "played back, looped, or changed, using any of 13 different sound envelopes." So what, you say? That's been available on professional synthesizers for several years. Yes, but the SK-1 costs only \$130. The company also introduced a \$120 scientific pocket portable computer with 65 sci functions and BASIC and Assembly languages.



**Cincinnati Microwave** claims its new StarCast C-band system minimizes "sparklies," those bursts of microwave noise in a video display. CMC did extensive research to characterize the threshold and peak levels of r-f noise, using this to distinguish the noise from the signal, lopping off the former.

**Final Technology** finally showed a working version of its Laser Turntable. This is the long-dreamed-of machine that plays conventional LP's with a beam of light; nothing touches the disk. I was one of the few journalists invited to hear the unit, and I can verify that it works. It will not be available for at least another four months . . . at an estimated \$2,500.


**Commodore** introduced a remodeled Commodore 64 computer, the 64C. It features a new hardware/software system that provides graphics-based operation with a "point and click" icon interface for under \$250. They say that the new operating system and applications on disk can be purchased separately for \$59.95 by current Commodore 64 owners. The new mouse or joystick-controlled machine uses a 6510A CPU that's said to be compatible with the old C-64 computer and can, thus, use older software packages.

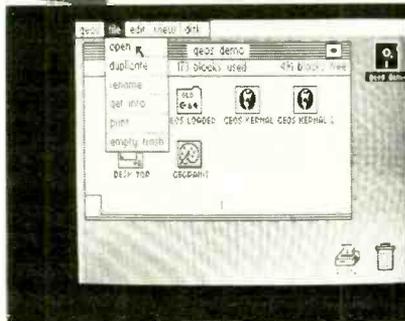

**Future Communications's** "Phasecom" TVRO antennas are flat. Using phased-array principles, they can be mounted on a roof or the side of a house. Prices range from \$421 to \$1200.

**Interstate Voice Products** displayed its module that attaches to a cellular phone to provide voice operation without having to touch the phone or take your eyes off the road.

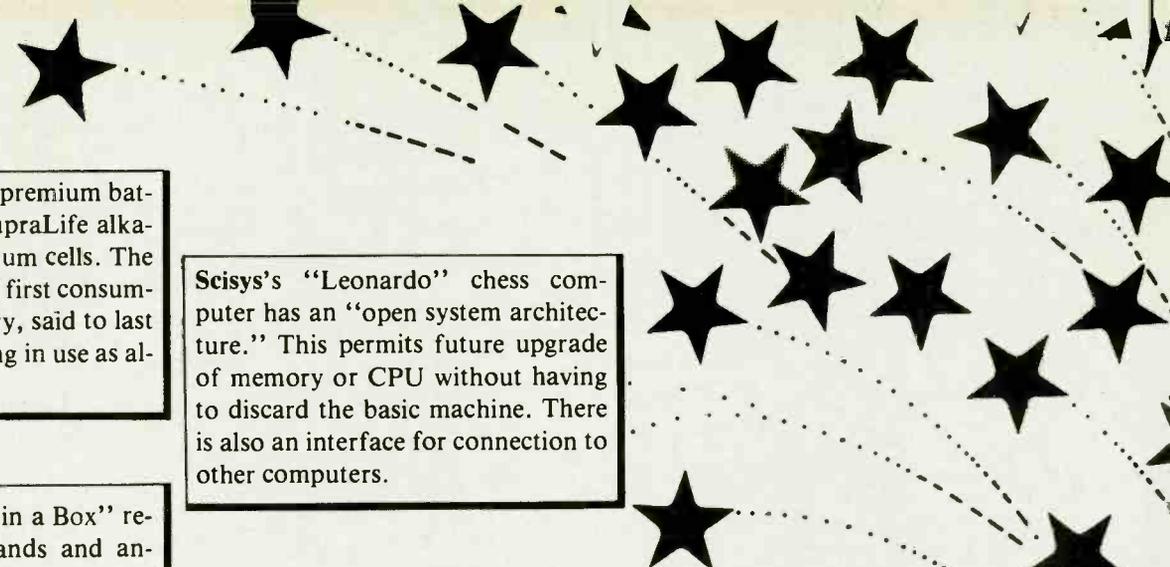**JVC**, among others, has responded to the challenge of 8-mm camcorders with an upgrade of VHS camcorders that include 60-minute recording time (twice as much as previously) and HQ video circuits to improve picture quality. The system uses a VHS-C mini-cassette that's played back on home VHS videocassette decks with the use of a special adapter.



**Kodak** has entered the premium battery market with its SupraLife alkaline and UltraLife lithium cells. The latter appears to be the first consumer 9-volt lithium battery, said to last more than 200% as long in use as alkaline types do.

**Mastervoice's** "Butler in a Box" recognizes vocal commands and answers in a human-sounding synthesized voice. It controls lights and appliances (via BSR X-10 protocol), answers the phone, and communicates with (or is controlled by) a computer through an RS-232C port. It can query an intruder, and if it doesn't recognize the voice, turn on lights and sound the alarm. This barely scratches the surface; you need a demonstration to appreciate this brilliant piece of design.

**Polaroid** (in cooperation with Toshiba) has a freeze-frame recorder that permits any single video frame to be recorded on their new Spectra film, or most 35-mm color negative or transparency films. Special circuits double the number of scanning lines for a more pleasing picture.

**Scisys's** "Leonardo" chess computer has an "open system architecture." This permits future upgrade of memory or CPU without having to discard the basic machine. There is also an interface for connection to other computers.

**Sega's** "MasterSystem" video game appears to incorporate the same graphics chips used in its current arcade games. Software comes in two forms: the Sega Card (which resembles an electrified credit card, and can hold up to 32K), and the Mega Cartridge (with four times that capacity). I was more impressed with Sega's hardware and game selections than with Nintendo's Entertainment System introduced last year.

**Seiko's** LVD-302 LCD pocket color TV has a screen that measures only 2" diagonally. But with 74,000 picture elements, it produced the least coarse display of any I've seen. The LC elements now change state quickly, with virtually no streaking of moving objects. The color picture displayed was clean and highly saturated.

**Sony** has a water-tight casing for its popular 8-mm "HandyCam." The portable video recorder even includes a waterproof microphone!

**Toshiba's** DX-7 is the first VCR with a digital frame store. Any selected frame can be converted from analog to digital and held in 144K of RAM. This permits stable, noiseless slow motion and freeze-frame. The deluxe VHS deck includes the usual high-end features, such as Hi-Fi sound and HQ video. The company also demonstrated a digital noninterlaced TV monitor that provides 525 lines in 1/60th second.

**Video Interface Technology's** Video Vitalizer is a sophisticated digital pattern and effects generator. Up to 120 effects are possible, depending on how many ROMs you're willing to buy. There isn't enough room to list all the features, let alone explain them. Prices run from \$549 to \$1031, depending on the number of effects and accessories.


**Yamaha's** new DSP-1 Digital Sound Field Processor is said to be able to recreate the acoustic "personality" of many music environments. Forty eight preset acoustic environments are stored digitally to give a user a choice of listening to music in an intimate jazz club or a 1,000-seat auditorium, according to the company. Dolby Surround sound field is included in the new unit, which is the popular sound imaging technique used in many movie theatres.

# Radio Shack Parts Place™

'87 CATALOG AVAILABLE—COME GET YOUR FREE COPY!

184 Full-Color Pages ■ Hundreds of New Items and New Low Prices ■ Not Sent by Mail

## (1) Breadboard It

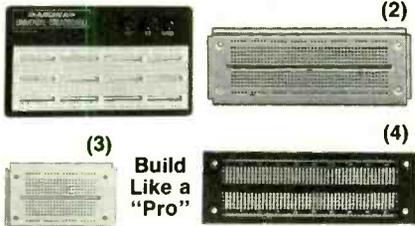

- (1) **Universal.** Our best! Breadboard is mounted on a 7 x 4" "stay-put" steel base with rubber feet, 640 plug-in points, 3 binding posts. #276-169, 19.95
- (2) **Modular Breadboard Socket.** 2 buses, 550 indexed connection points. Snap together for more complex designs. 2 1/8 x 6" #276-174 ..... 11.95
- (3) **Modular Breadboard Socket.** Smaller version of Fig. 2. 2 1/8 x 3 5/8" #276-175 ..... 6.95
- (4) **Matching PC Board.** Same layout as sockets for easy circuit transfer. #276-170 ..... 2.69

## Easy-to-Use Soundmakers



- (11) **Electronic Chime.** IC/speaker combo produces a "ding-dong" sound. 12 VDC. #273-071 ..... 6.95
- (12) **2-Tone Piezo Buzzer.** Really gets attention! Operates 8 to 16 VDC. #273-070 ..... 8.95
- (13) **PC-Mount Piezo Buzzer.** Loud, yet consumes only 12 milliamperes at 12 VDC. #273-065 ..... 2.49

## Resistor Kit Bargains



- (14) **1/4-Watt, 5% tolerance.** 100-piece set includes 13 popular standard values ranging from 10 ohms to one megohm. #271-308 ..... 2.79
- (15) **Precision Metal-Film.** 1/4-watt, 1% tolerance. 50 piece set includes 12 popular standard values ranging from 10 ohms to one megohm. #271-309 ..... 2.49

## Hobby Motor Bargains




- (18) **High Torque.** 8300 maximum RPM, operates 1.5 to 3 VDC. Approximately 1 1/2" long by 1 5/16" dia. #273-223 ..... 79¢
- (19) **With Brass Pulley.** Built-in noise filter. Operates 3 1/2 to 9 VDC. #273-229 ..... Pkg. of 2/1.49

## Attention-Getting LEDs



- (20) **Super-Bright Red LED.** A real breakthrough! Outputs 300 mcd at 20 mA yet runs cool. Point-source type in a clear epoxy T-1 3/4 package. #276-066 ..... 99¢
- (21) **CQX21 Blinking LED.** Combines MOS driver IC and red LED in a T-1 3/4 package. #276-036, 1.19

## Books by Forrest Mims

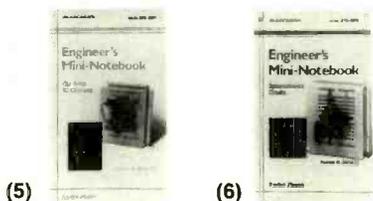


- **Easy-to-Read Schematics**
- **Parts in Stock at Radio Shack**
- (5) **Op Amp Mini-Notebook.** Learn as you build! 48 pages contain over 40 clever circuits using popular op amps such as the 741. #276-5011 ..... 1.49
- (6) **Optoelectronics Mini-Notebook.** 48 pages. Features a great introductory section on optical components. Projects range from a simple LED circuit to lightwave transmitter/receiver circuits. #276-5012 ..... 1.49

## Voice Synthesizer Team

- Add Voice to Your Computer**
- (7) **SPO256-AL2 Speech Synthesizer IC.** MOS/LSI device is easy to interface with most computers. With data. 28-pin DIP. #276-1784 ..... 12.95
- (8) **CTS256-AL2 Text-to-Speech IC.** Translates ASCII characters into control data for Fig. 7. With data. 40-pin DIP. #276-1786 ..... 16.95

## Fiber-Optics Components

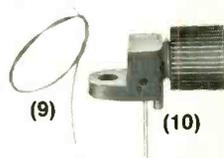- (9) **Optical Fiber Cable.** 3-meter length of high-quality optical cable is ideal for experiments. #276-228 ..... 5.99
- (10) **Emitter/Detector Set.** Use to send analog or digital signals through fiber optic cable. With data. #276-225 ..... 4.99



## Hi-Q Ceramic Discs




pF	VDC	Cat. No.	2-Pack	µF	VDC	Cat. No.	2-Pack
4.7	50	272-120	.39	.001	500	272-126	.49
47	50	272-121	.39	.0047	500	272-130	.49
100	50	272-123	.39	.01	500	272-131	.49
220	50	272-124	.39	.047	50	272-134	.49
470	50	272-125	.39	1	50	272-135	.49
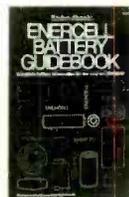
## Battery Guidebook

Helps You Select The Right Battery

Learn how batteries work, how to recharge and test them, and how to choose the best values. Includes complete technical data on all ENERCELL® batteries. 160 pages. #62-1396 ..... 1.99



## Tantalum Capacitors



- High Capacity in A Small Package
- IC Pin Spacing
- 20% Tolerance

µF	WVDC	Cat. No.	Each	µF	WVDC	Cat. No.	Each
0.1	35	272-1432	.49	2.2	35	272-1435	.59
0.47	35	272-1433	.49	10	16	272-1436	.69
1.0	35	272-1434	.49	22	16	272-1437	.89

## Low-Cost Panel Switches



- (16) **Submini Toggles.** 3 A at 125 VAC. 1/4" mtg. hole. SPST. 275-612 ..... 1.69 SPDT. 275-613 ..... 1.79 DPDT. 275-614 ..... 2.19 DPDT Center-Off. 275-620 ..... 2.29
- (17) **Submini SPST Momentary.** Rated 0.5 amp at 125 VAC. Normally open. 1 1/2 x 1/4" Includes one red, one black. 3/8" mtg. hole. 275-1571 ..... Set of 2/1.69

## Digital Logic Probe



**NEW!**

The fast way to test TTL, LS and CMOS digital circuits. Color-coded LEDs indicate high, low or pulsed logic states (up to 10 MHz). Simultaneous tone output frees your eyes for faster testing. 36" leads with clips provide power from circuit under test. With instructions. #22-303 ..... 16.95

## Digital Logic Pulser



**NEW!**


Together, the pulser and probe make an effective diagnostic team for testing today's digital circuits. Produces single 5 µs pulse or a continuous 5 Hz pulse train at the push of a button. Features overload protection and low output impedance. With instructions. #22-304 ..... 17.95

## 21-Range Digital VOM

Cut 37%

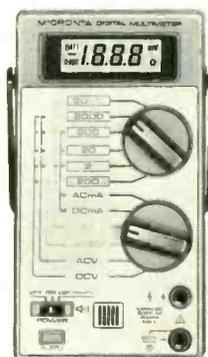**SUPER SAVER!** Reg. 59.95 **3788**

Accuracy, ease of use and famous Microcronta® quality at 33% off! Features big LCD display, "beep" continuity test mode, ohms zero-adjust button, diode-check mode. Measures to 1000 volts DC, 500 volts AC, AC/DC current to 200 mA. Resistance to 20 megohms. 6 3/8 x 3 1/2 x 1 3/8". With owner's manual and probes. Requires 2 "AA" batteries. #22-191, Sale 37.88



Over 1000 items in stock: Binding posts, Books, Breadboards, Buzzers, Capacitors, Chokes, Clips, Coax, Connectors, Fuses, Hardware, ICs, Jacks, Knobs, Lamps, Multitesters, PC Boards, Plugs, Rectifiers, Relays, Resistors, Switches, Tools, Transformers, Transistors, Wire, Zeners, more!

**Radio Shack®**  
A DIVISION OF TANDY CORPORATION

Prices apply at participating Radio Shack stores and dealers

# Two-Band Stereo LED Power Meter

*Lets you visually monitor your car stereo system's high- and low- frequency output power*

By Ross Ortman


**M**any modern car-stereo amplifiers are so powerful that they can put your normally rugged speakers in jeopardy of burning up. A stereo power meter like the dual-band one described here provides an excellent means for guarding against this type of hazard.

The Two-Band Stereo Power Meter offers an unusual bargraph-like display. Unlike most power meters that provide a single display for each channel, this project has two per channel. Input signals are split into high- and low-frequency groups that are separately monitored for each channel. This allows you to keep an eye out for dangers to your woofers and mid-range drivers/tweeters separately, making displayed data much more meaningful.

All power information is displayed in four attractive horizontal "bargraphs" made up of discrete LEDs. The LEDs are of different colors, with green at the low-power end, yellow in the medium-power middle range and red in the high-power "danger" end. Consequently, not only is the Power Meter a practical device, it is also a very attractive high-tech addition to your vehicle.
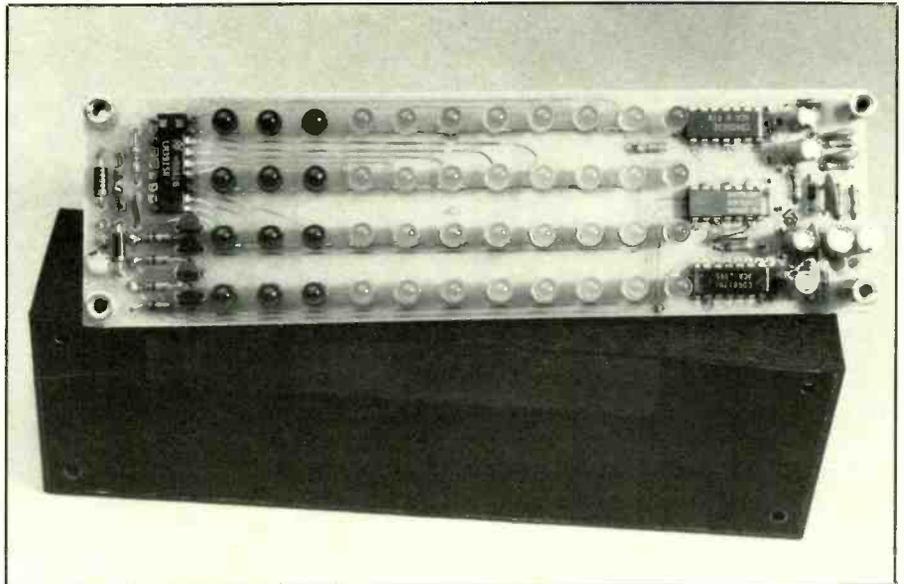
## About the Circuit

As shown in the block diagram in Fig. 1, the Power Meter consists of three main sections. The first is the input filter, which separates the left



and right outputs from an amplifier into high- and low-frequency groups, with a crossover frequency of about 3 kHz.

Second in the chain is the multiplexing circuit. This circuit's oscillator, operating at about 380 Hz, is used to clock a 4017 decade counter/divider that supplies 10 decoded outputs, four of which are used to sequentially pass the filter outputs to the display driver and turn on its corresponding row of light-emitting diodes. A 4066 quad bilateral switch selects the filter output dictated by the counter/divider.

Outputs from the bilateral switches are sent to the display circuit, which is the third section. This circuit consists of four rows of LEDs, an LM3915 bar/dot driver and

switching transistors that selectively supply power to individual rows of LEDs. The LEDs display the amplitude of the signal delivered to the Power Meter, as filtered and switched by the preceding sections, in a bargraph-like display format.

Now that you have an idea of system architecture, refer to the schematic diagram in Fig. 2. Power for the circuit is supplied by the electrical system of the vehicle in which the project is used. It is protected against transients and incorrect power connection by *D1*, *D2*, *C1* and *C13*.

Inputs to the project are ac coupled through *C2* and *C3*. This allows the Power Meter to be used with floating ground and high-power car stereo systems that usually have a dc component in their outputs. Separ-

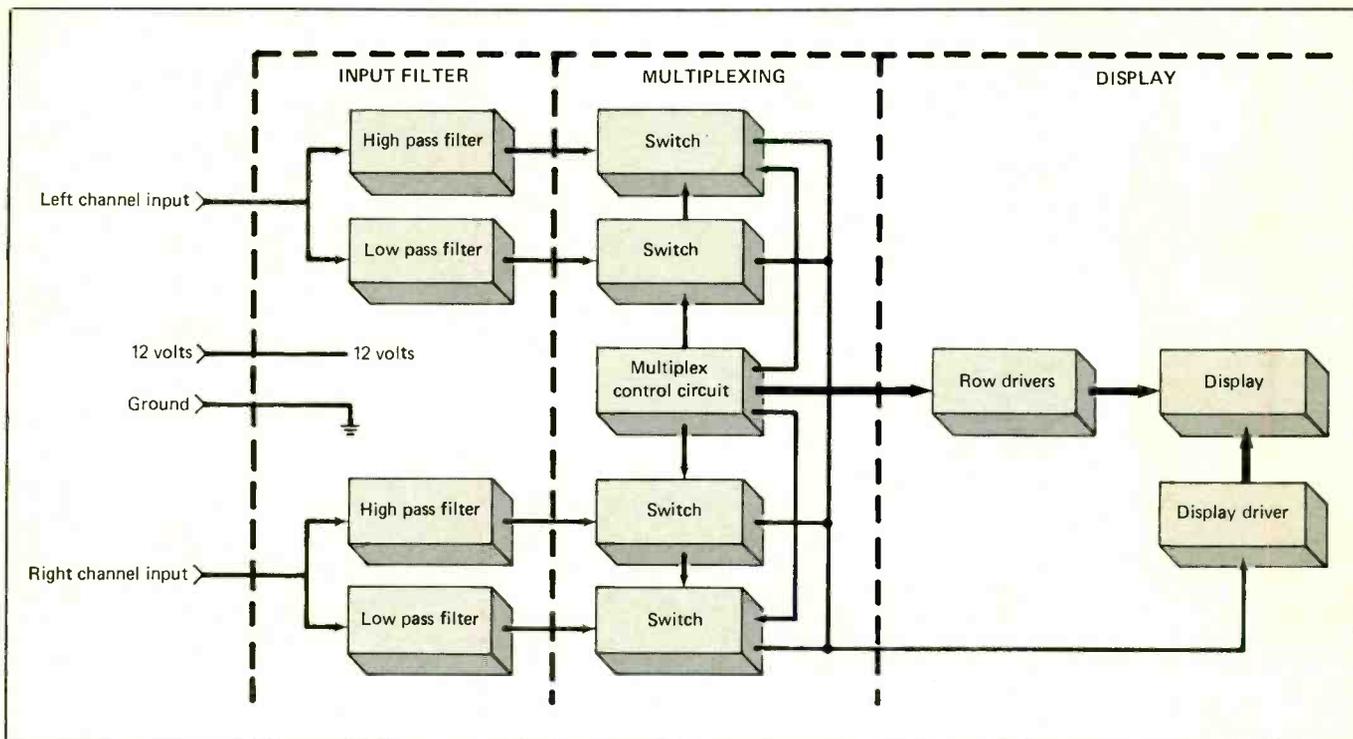


Fig. 1. Stereo Power Meter consists of an input filter, a multiplexer and a decoder/driver/display system.

ate low- and high-pass filters are provided for each channel: *C4/R3* for the high- and *R1/C6/R5* for the low-pass filters in the left channel and *C5/R4* for the high- and *R2/C7/R6* for the low-pass filters in the right channel.

Once the inputs are filtered, *D3* through *D6* rectify them and store their relative amplitudes in *C8* through *C11*. Individual level adjustments for each channel are provided by *R7* through *R10*. At the wiper of each of these controls is a calibrated dc voltage that is relative to the level of the power present at the inputs of each channel.

Since the input power is separated into two separate frequency bands, the amount of high- and low-frequency power in the left channel are the dc voltages at *R7* and *R9*, respectively. In the right channel, the appropriate controls are *R8* and *R9*, respectively.

Sections A and B of *IC2*, along with *R11* and *C12* make up a 380-Hz oscillator. Decade counter/divider

*IC3* provides a sequential set of four pulses that are used to control the multiplexing. The multiplexing circuit is used to scan the four filtered voltage levels and display their amplitudes on their respective rows of LEDs. It does this by selecting each filter output in sequence and turning on the transistors for each respective row of LEDs. Using this scheme, only one row of LEDs is on at any given instant in time. However, because of the high-speed scan rate, all rows appear to be on simultaneously.

There are separate power-level bargraph driver/display circuits for the high- and low-frequency bands for each channel. These are *Q1* with *LED2* through *LED11* and *Q3* with *LED24* through *LED33* arrangements, respectively, for the left channel. The right-channel arrangements are *Q2* with *LED13* through *LED22* and *Q4* with *LED35* through *LED44*. Not part of the actual power-measuring section of the project are *LED1*, *LED12*, *LED23* and *LED34*, which serve as power indica-

tors that come on whenever dc power is applied to the circuit from the vehicle's electrical system, even if no input signal is present.

Quad bilateral switch *IC1* passes each filter's output to the input of bargraph display driver *IC4*. This IC then turns on from one to ten LEDs of the selected row. The number of LEDs that come on indicate the relative input power level.

### Construction

You can build the Power Meter using any wiring technique that suits you. However, printed-circuit wiring is recommended to provide stability and safety in the harsh automotive environment. No matter where you decide to mount the Power Meter—in an overhead console or under the dashboard—make sure to house it in some type of enclosure to protect the circuit from accidental shorting to any exposed metal in the vehicle. An enclosure also provides a more readable and attractive display.

A double-sided printed-circuit

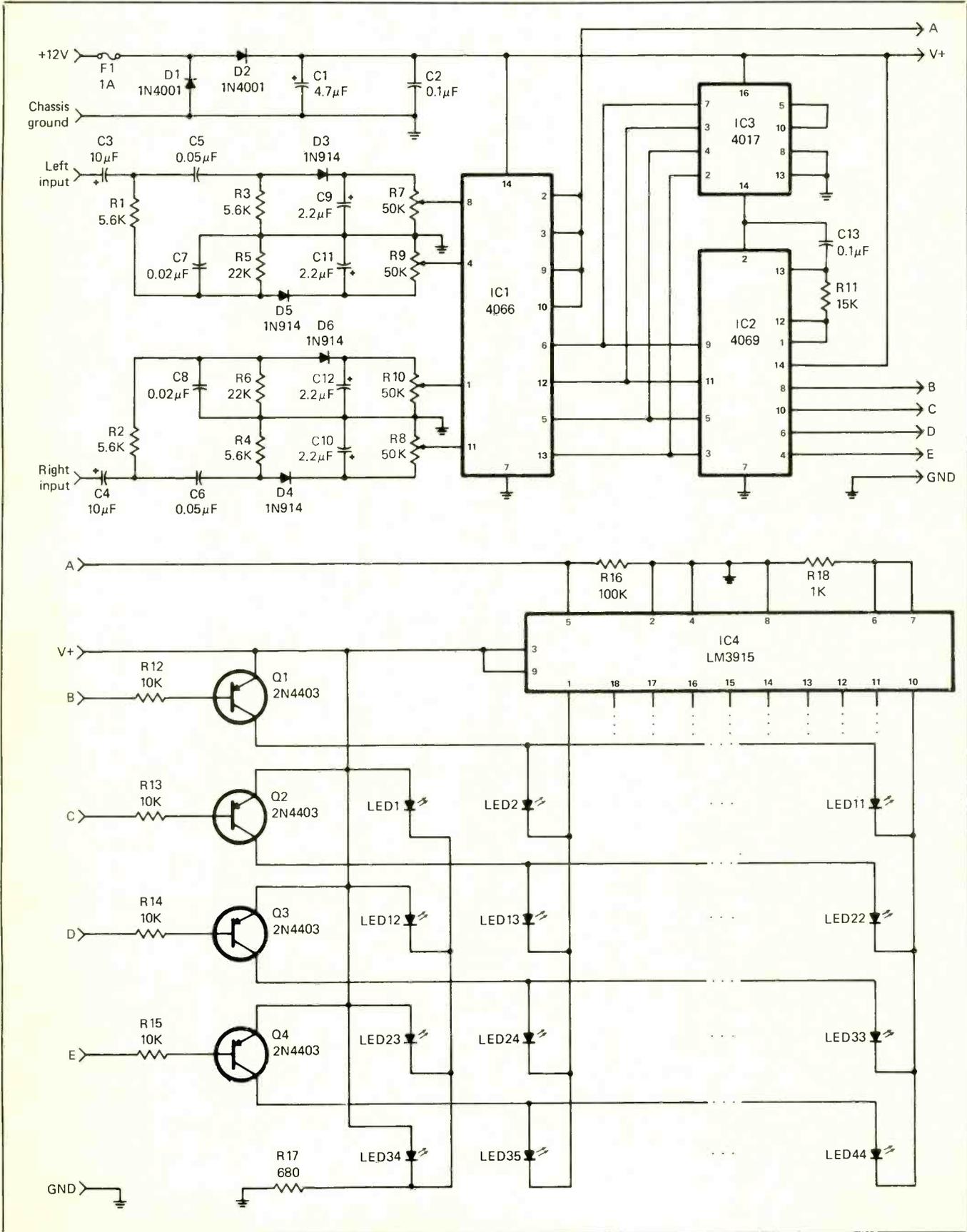


Fig. 2. Separate high- and low-frequency "bar" displays consist of 10 LEDs in each channel bar, plus one LED in each bar that comes on when dc power is applied. Only four LEDs are shown for each channel.

## PARTS LIST

### Semiconductors

D1,D2—1N4001 rectifier diode  
 D3 thru D6—1N4148 signal diode  
 IC1—4066 quad bilateral switch  
 IC2—4069 hex inverter  
 IC3—4017 decade counter/divider  
 IC4—LM3915 bar/dot driver  
 LED1 thru LED4—0.2" light-emitting diode (20 green; 12 yellow; 12 red—see text)

Q1 thru Q4—2N4403 transistor

### Capacitors

C1—4.7- $\mu$ F, 16-volt electrolytic  
 C2,C13—0.1- $\mu$ F disc  
 C3,C4—10- $\mu$ F, 35-volt electrolytic  
 C5,C6—0.05- $\mu$ F disc  
 C7,C8—0.02- $\mu$ F disc  
 C9 thru C12—2.2- $\mu$ F, 25-volt electrolytic

### Resistors (1/4-watt, 5% tolerance)

R1 thru R4—5,600 ohms  
 R5,R6—22,000 ohms  
 R11—15,000 ohms  
 R12 thru R15—10,000 ohms  
 R16—100,000 ohms  
 R17—680 ohms  
 R18—1,000 ohms  
 R7 thru R10—50,000-ohm vertical-mount trimmer potentiometer

### Miscellaneous

F1—1-ampere fast-blow fuse  
 Printed-circuit board; suitable enclosure (see text); power cable with in-line fuse holder; two-conductor zip cord; 1/2" spacers (4); machine hardware; hookup wire; solder, etc.

Note: A double-sided pc board with plated-through holes is available for \$17.95 plus \$1.50 P&H from: Dakota Digital, R.R. 1, Box 83, Canisota, SD 57012.

board was used for wiring the Power Meter's circuit in the prototype shown in the lead photo. You can fabricate this board, using the Fig. 3 actual-size etching-and-drilling artwork. Alternatively, you can pur-

chase a ready-to-wire pc board with plated-through holes from the source given in the Note at the end of the Parts List.

Bear in mind that with a home-made double-sided board, all component leads and pins that contact the foil pattern on top and bottom must be soldered to the pads on *both* sides of the board. This means that if you wish to use sockets for the ICs, some of whose pins contact pads on both the top and bottom, you will have to use all-metal Molex Soldercons instead of the usual sockets. If you use the plated-through commercial board, however, you can use standard IC sockets. Capillary action will assure that all junctions on top and bottom of the board will be securely soldered if you solder on only the bottom of the board.

Referring to Fig. 4, begin wiring the board by installing and soldering into place the resistors. Follow with the diodes, making sure to properly orient them. Then proceed to the transistors. Bend the center base leads of the transistors slightly toward the flat of the case. Holding the board in the orientation shown in Fig. 4, install each transistor with the flat facing the top of the board. The bent-forward base lead in each case plugs into the offset hole in the solder-pad pattern. Adjust the height of the transistors to about 1/4" from the surface of the board and solder the leads to the pads. Use heat judiciously to avoid damaging the transistors.

Now install and solder into place the capacitors, making sure that the polarized electrolytics are properly oriented. You have the option of installing the ICs directly on the board, with their pins soldered to the foil patterns (on both sides if your board is homemade) or via sockets or Soldercons.

The most difficult step in assembly is installation of the LEDs because of the repetitive nature of the operation and the fact that all LEDs in each row and column must be carefully

aligned and of uniform height to provide a balanced display. Keep firmly in mind that the cathodes in all cases go into the holes nearer the bottom edge when the board is oriented as shown in Fig. 4. There are two ways to identify the cathode lead: the lead near the slight flat in the case lip and the widened lead near the bottom of the case.

A good way to assure uniform LED height is to push the LED leads down until the widened portion of the cathode leads just touch the top of the board. Solder only the cathode leads of all 44 LEDs to the pads. Each horizontal "bar" in the display consists of green, yellow and red LEDs. The first five LEDs in each bar (e.g. LED1 through LED5 in the topmost bar) are green, the next three are yellow and the final three are red.

If you prepare an alignment template for the LED matrix, a lot of time can be saved in positioning the LEDs to make a symmetrical display. The template is made from heavy cardboard stock like Bainbridge board or thin but rigid plastic like 1/8"-thick Plexiglass cut to 5" long by 2" wide. Cut out and paste the actual-size template shown in Fig. 5 to the cardboard or plastic template blank. If you prefer not to cut up the page, place the blank behind Fig. 5, centering it in the outline, and pierce with a pin or needle at the center of each circle. Then remove the blank.

Drill an 1/16" or 3/16" hole through the center of each hole outline (or through each marked point). You should have a total of 44 holes arranged in a symmetrically balanced matrix. Place the template over the LEDs. Adjust the positioning of the LEDs so that their domes fit into all 44 holes. With the LEDs in place, position the template so that it is parallel with the top edge of the board. Check to make sure that all LEDs are at a uniform height. If any are not, reflow the solder and adjust as necessary. Then solder the cathode leads

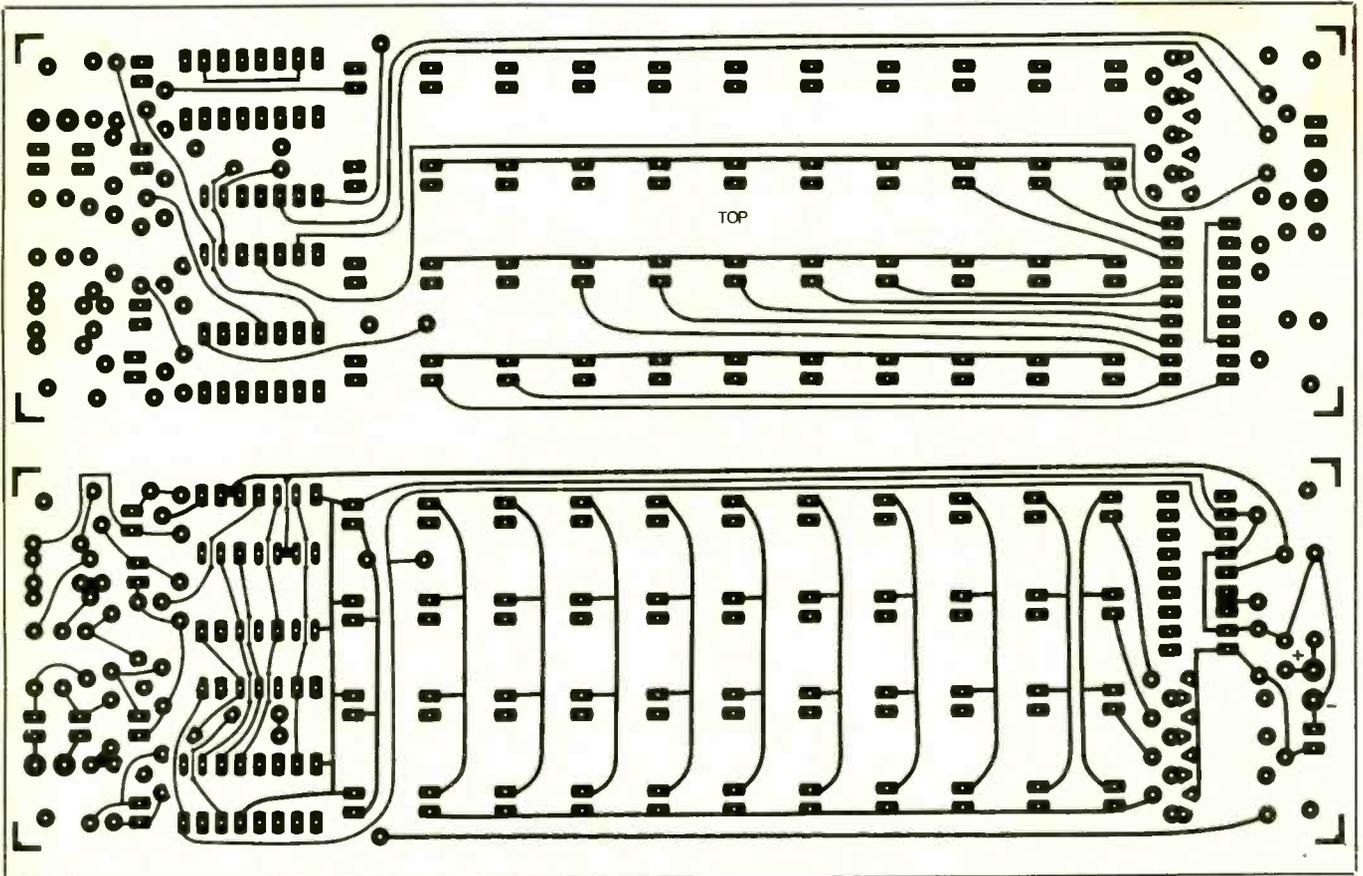


Fig. 3. Actual-size etching-and-drilling guides for top and bottom of double-sided printed-circuit board.

of first the top row of LEDs to the solder pads. Repeat for the second, third and fourth rows. Use heat sparingly to prevent damaging the LEDs.

Remove the template and discard it if you have no further need for it.

If you plan to make more Power Meters, store the template away for later use.

You can, of course, arrange the LEDs without the aid of a template. In this case, you will have to perform

the entire operation by eye. Needless to say, this can be a very time-consuming operation.

Referring back to Fig. 4, install the R7 through R10 trimmer controls on

(Continued on page 90)

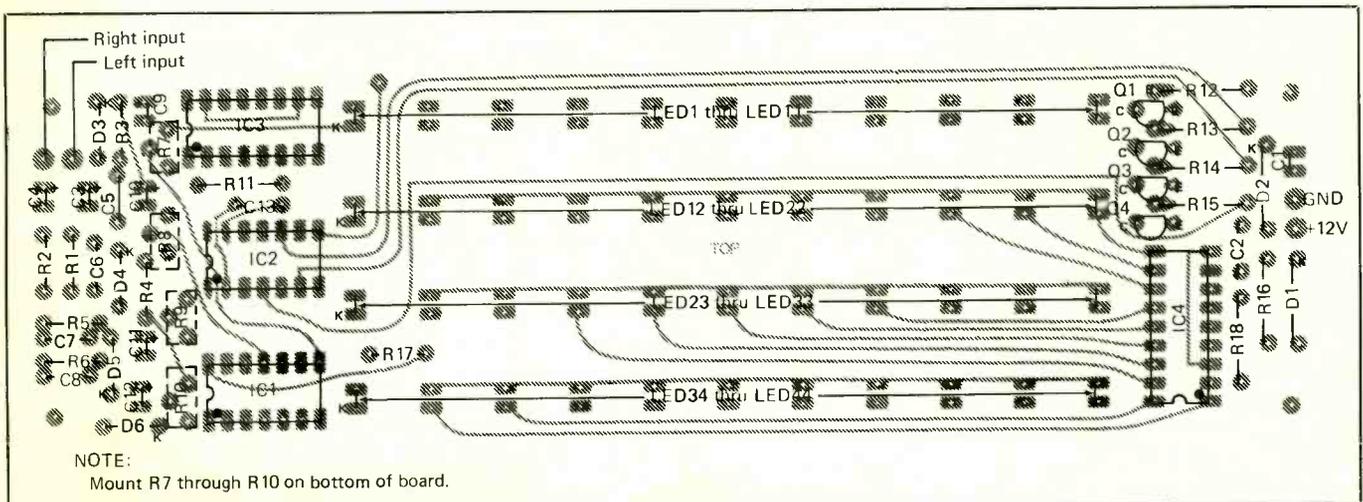


Fig. 4. Placement/orientation wiring diagram.




152K *Lowest Price In The USA!* 152K

# Computer System Sale

• Students • Word Processing • Home • Business

**152K System \$379\***  
(130XE System)

EDUCATE WITH ATARI

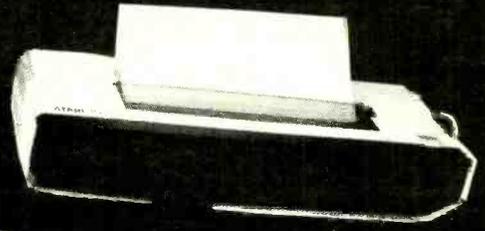

**Limited Time**  
**FREE Software w/ System Purchase\***  
Home Filing Mgr., Star Raiders,  
Music Composer, Defender

LOOK AT ALL YOU GET FOR ONLY **\$379**  
LIMITED QUANTITIES  
SYSTEM PRICE

- ① Atari 130XE 152K Computer
  - ② Atari 1050 127K Disk Drive
  - ③ Atari 1027 Letter Quality 20 CPS Printer
- Super Atari Word Processor  
Atari BASIC Tutorial Manual

All connecting cables & T.V. interface included.  
☆ Monitors sold separately.

LIST PRICE	INDIVIDUAL SALE PRICE
\$249.00	\$134 <sup>95</sup>
299.00	159 <sup>95</sup>
299.00	159 <sup>95</sup>
59.95	49 <sup>95</sup>
16.95	7 <sup>95</sup>
<b>\$923.90</b>	<b>\$512.75</b>

**SAVE OVER \$100**  
ALL 5 ONLY  
**\$379<sup>00</sup>**  
SYSTEM SALE PRICE

**TOTALS**

**CALL FOR 1027 PRINTER REPLACEMENT OPTIONS**

\* Free software subject to substitution for other titles

### Other Accessories

	List	Sale	
☆ 12" Hi Resolution Green Screen Monitor	\$199.00	\$79.95	Add \$9.95 for Connection Cables
☆ 13" Hi Resolution Color Monitor	\$399.00	\$139.95	Add \$10 for UPS

**15 DAY FREE TRIAL.** We give you 15 days to try out this ATAR COMPUTER SYSTEM!! If it doesn't meet your expectations, just send it back to us prepaid and we will refund your purchase price!! **90 DAY IMMEDIATE REPLACEMENT WARRANTY.** If any of the ATARI COMPUTER SYSTEM equipment or programs fail due to faulty workmanship or material within 90 days of purchase we will replace it IMMEDIATELY with no service charge!

**Best Prices • Over 1000 Programs and 500 Accessories Available • Best Service**  
**• One Day Express Mail • Programming Knowledge • Technical Support**

**Add \$25.00 for shipping and handling!!** Enclose Cashiers Check, Money Order or Personal Check. Allow 14 days for delivery. 2 to 7 days for phone orders. 1 day express mail! We accept Visa and MasterCard. Add \$25 if Air Mail. C.O.E. on phone orders only. Add \$50 for CANADA, PUERTO RICO, HAWAII, ALASKA, APO-FPO orders.

**COMPUTER DIRECT**  
*We Love Our Customers*  
22292 N. Pepper Rd., Barrington, Ill. 60010  
**312/382-5050 to order**

# An Experimenter's Aviation-Band Receiver

*Low-cost project lets you tune in on airport and airborne radio activity*


By Dan Becker

If you live within 20 miles of a busy airport, you have an opportunity to tune in on some exciting radio activity. With the Experimenter's Aviation Band Receiver to be described, you can listen to aircraft and tower communications in the 118-to-135.95-MHz band assigned to aviation activities, including the 121.5-MHz world-wide emergency channel.

Channels are divided into increments of 50 kHz each, with each assigned to a different type of service. Some channels are used by air traffic controllers who continuously give course and altitude instructions to pilots aloft. Other channels are used while an airplane is on the ground. These service channels carry maintenance, fuel status, weather (including wind speed and direction and temperature aloft) and personal requests by pilots enroute. Much of what you can hear is routine, but in times of emergency, you can get first-hand information before the news media report it.
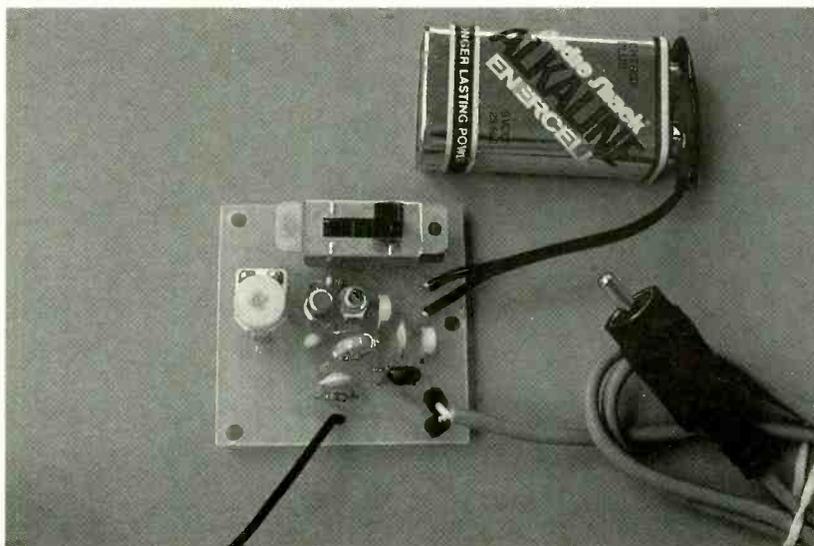
## About the Circuit

Shown in Fig. 1 is the complete schematic diagram of the Experimenter's Aviation Band Receiver. It is built around a single transistor, identified as *Q1*, which operates as both an r-f amplifier and a detector. The output of this transistor is coupled to an ex-



ternal audio amplifier via a coaxial (shielded) audio cable. Almost any epitaxial transistor rated for vhf service will work in this circuit.


Because aviation communication is via amplitude-modulated (AM) signals, the value of the dc collector current of *Q1* can be made to vary in direct proportion to these signals. This requires an input signal amplitude of greater than 10 millivolts. In addition, any variation in the dc collector current must be extracted and amplified.

Two functions are performed by the Aviation Band Receiver. One is its operation as a Hartley oscillator

in which the approximately 120-MHz operating signal frequency is governed by *T1*, *C2* and *C3*. This greatly amplifies the microvolt-level signals that appear at the antenna and feeds them back to the base of *Q1* with an amplitude greater than the 10-mV minimum level needed by the circuit for proper operation.

In the second function, any variation in the dc collector current will appear as a variation in the emitter-collector voltage, measured at the collector side of *R4*. It is here that the audio information is extracted and sent off to the audio amplifier.

Capacitors *C1*, *C4*, *C6* and *C7* by-

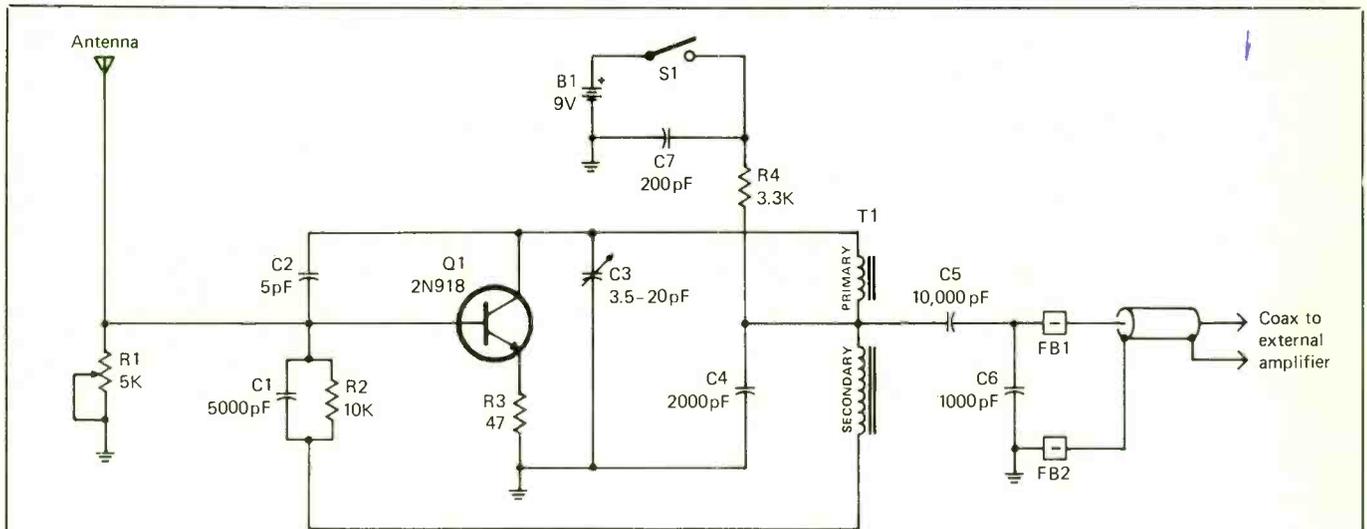

### PARTS LIST

#### Semiconductors

Q1—2N918 npn transistor

#### Capacitors

C1—5,000-pF ceramic disc

C2—5-pF, high-Q ceramic disc

C3—3.5-to-20-pF trimmer

C4, C7—2,000-pF ceramic disc

C5—10,000-pF Mylar

C6—1,000-pF disc

Resistors ( $\frac{1}{8}$ -watt, 5% tolerance)

R2—10,000 ohms

R3—47 ohms

R4—3,300 ohms

R1—5,000-ohm trimmer potentiometer

#### Miscellaneous

B1—9-volt battery

FB1, FB2—Vhf ferrite bead

S1—Spst slide or toggle switch

T1—Hand-wound transformer

Printed-circuit board; suitable en-

closure; T-25-0 powdered-iron toroid core and 30-gauge enameled wire for T1; 1-meter length of hookup wire for antenna; connector for B1; coaxial audio cable; machine hardware; hookup wire; solder; etc.

Note: A kit of all parts including pc board, all components and audio cable (but not enclosure) is available for \$8.95 plus \$1.00 S&H from: Dan Becker, 101 Highland Dr., Chapel Hill, NC 27514.

Fig. 1. Complete schematic diagram of Experimenter's Aviation Band Receiver.

pass radio frequencies. Potentiometer *R1* and resistors *R2*, *R3* and *R4* establish a quiescent dc collector current of approximately 1 mA. In addition, regenerative control *R1* permits the gain to be adjusted to establish oscillation and *C3* permits fine tuning of the operating frequency. Ferrite beads *FB1* and *FB2* in series with the audio output help isolate the audio cable from r-f signals. The antenna is made from a 1-meter or shorter length of hookup wire.

Power for the circuit is supplied by ordinary 9-volt battery *B1*. It is applied to the circuit via spst switch *S1*.

### Construction

The very simple circuit of the Experi-

If you elect pc construction, wire the board exactly as shown in the components-placement and orientation diagram given in Fig. 3. (You can also use Fig. 3 as a rough guide to component layout if you use perf-board construction.) When wiring experimenter's Aviation Bank Receiver is readily assembled on a 2" × 2" piece of perforated board, using appropriate soldering hardware. Alternatively, you can fabricate a printed-circuit board using the actual-size etching-and-drilling guide shown in Fig. 2. A third alternative is to assemble the circuit on a ready-to-wire pc board supplied in the kit of parts from the source given in the Note following the Parts List.

the board, be sure to keep all lead lengths as short as possible.

All components for this project, except *T1*, are readily available from parts suppliers ready for installation. The only component you are not likely to find is the transformer, which you must wind yourself. This is not difficult. All you need are a powdered-iron toroid core (see Parts List) and some 30-gauge enameled wire. Begin by winding four turns of the wire onto the core to make the primary. Without cutting the wire, form a 2" loop and continue winding eight more turns to make the secondary winding. Wind all turns in the same direction.

When all turns have been wound

on the toroid core, cut the loop and the ends of the wire so that there are four equal-length leads. Carefully scrape away the enamel from all four leads for a distance of about  $\frac{1}{2}$ ". Then lightly tin with solder the exposed metal of each lead. Inspect the solder. If there are any gaps or the solder has blobbed instead of evenly coating the leads, you missed some of the enamel while scraping. Rescrape any lead that appears to be suspicious and retin.

Install and solder into place first *S1* and then the transformer as shown in Fig. 3. Then install the resistors and capacitors. When you install transistor *Q1*, adjust its height above the board's surface to  $\frac{3}{16}$ ". Then wire the battery connector to the appropriate pads. Keep the battery connector's leads to just a few inches in length and arrange them as far away from the rest of the circuit as possible.

If your coaxial audio cable has phono plugs at both ends, snip off one from either end. Then remove 1" of outer insulation from the cut end. Be careful to avoid cutting through the shield conductors as you do this. Depending on whether the shield is braided or spirally wound, separate the fine conductors so that they can be twisted into a tight bundle. Then strip  $\frac{1}{4}$ " of insulation from the inner conductor. Very lightly tin with solder the inner conductor and tightly twisted shield wires. Exercise care soldering to avoid melting the insulation and causing a short circuit.

Slip a ferrite bead over the cable's shield wires and the inner conductor. Then install and solder into place the two conductors in the appropriate holes in the board.

Prepare a suitably sized metal enclosure to accommodate the circuit board by drilling three mounting holes for 6-32 machine hardware. Use the board itself as a template for determining where to drill the holes. Then cut a slot for *S1*'s toggle, drill

access holes for *R1* and *C3*, and drill small holes through which the antenna lead and audio cable are to exit the box. Make sure the hole for the antenna wire is exactly in line with the antenna hole on the pc board. Line the antenna and audio cable holes with rubber grommets to protect the wire and cable from chafing and shorting out against the metal box.

Mount the board in place with spacers and 6-32 machine hardware. You can mount *B1* either with a standard metal battery clip fastened to the box with machine hardware or with double-sided foam tape to any wall where it will not interfere with the circuit board.

### Adjustment and Use

Set trimmer control *R1* to about three-quarters of its travel clockwise and trimmer capacitor *C3* to approximately minimum capacitance. Place the circuit board on a table near an audio amplifier and plug the Aviation Band Receiver's audio cable into the amplifier's auxiliary (AUX) or microphone (MIC) input jack. Position the project's antenna up and away from the circuit board. Use a thumb tack to hold it against a wall.

Plug a 9-volt transistor battery into the battery connector and turn on the project and the amplifier. Set the

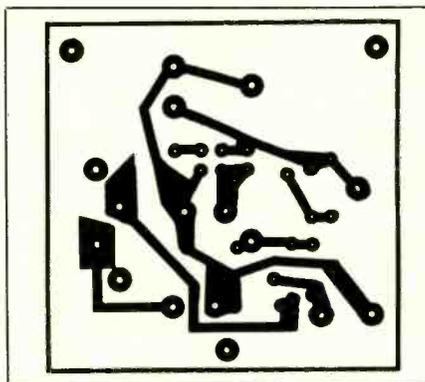


Fig. 2. Actual-size etching-and-drilling guide for receiver's printed-circuit board.

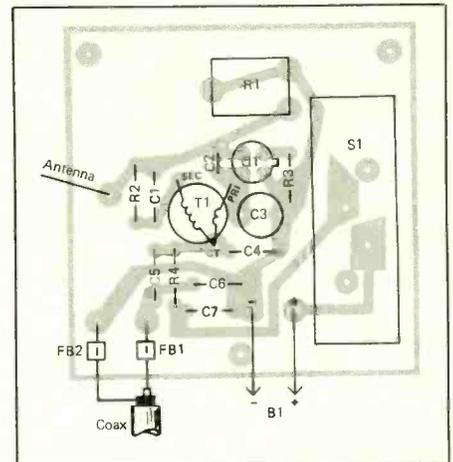


Fig. 3. Components-placement/orientation diagram.

amplifier's volume control about half-way up and the tone controls for minimum treble to reduce the hiss from the oscillator.

Adjust the setting of *R1* until you hear a distinct hissing sound coming from the amplifier's speaker(s). This hiss indicates that the circuit is oscillating. In addition, you can vary the settings of both *R1* and *C3* to tune in different segments of the Aviation Band.

### In closing

If you are an avid listener, you will likely want to keep your Experimenter's Aviation Band Receiver on at all times. Therefore, you might consider building a dedicated audio amplifier and separate ac-operated power supply to use instead of the battery for continuous monitoring. You can find projects for these options in past issues of *Modern Electronics*. You can also use an amplifier module with its own battery power supply and speaker for portable operation. In this case, you will undoubtedly want to equip your receiver with a transfer jack that will switch back in the *B1* battery supply when ac power is removed when operating in the portable mode. Happy listening.

ME

# NEW! Lower Price Scanners

Communications Electronics,<sup>™</sup> the world's largest distributor of radio scanners, introduces new lower prices to celebrate our 15th anniversary.

## Regency<sup>®</sup> MX7000-GP

List price \$699.95/CE price \$469.95  
**10-Band, 20 Channel • Crystallless • AC/DC**  
Frequency range: 25-550 MHz. continuous coverage and 800 MHz. to 1.3 GHz. continuous coverage. The Regency MX7000 scanner lets you monitor Military, Space Satellites, Government, Railroad, Justice Department, State Department, Fish & Game, Immigration, Marine, Police and Fire Departments, Broadcast Studio Transmitter Links, Aeronautical AM band, Aero Navigation, Paramedics, Amateur Radio, plus thousands of other radio frequencies most scanners can't pick up. The Regency MX7000 is the perfect scanner to receive the exciting 1.2 GHz. amateur radio band.

## Regency<sup>®</sup> Z60-GP

List price \$299.95/CE price \$179.95/SPECIAL  
**8-Band, 60 Channel • No-crystal scanner**  
Bands: 30-50, 88-108, 118-136, 144-174, 440-512 MHz. The Regency Z60 covers all the public service bands plus aircraft and FM music for a total of eight bands. The Z60 also features an alarm clock and priority control as well as AC/DC operation. Order today.

## Regency<sup>®</sup> Z45-GP

List price \$259.95/CE price \$159.95/SPECIAL  
**7-Band, 45 Channel • No-crystal scanner**  
Bands: 30-50, 118-136, 144-174, 440-512 MHz. The Regency Z45 is very similar to the Z60 model listed above however it does not have the commercial FM broadcast band. The Z45, now at a special price from Communications Electronics.

## Regency<sup>®</sup> RH250B-GP

List price \$659.00/CE price \$329.95/SPECIAL  
**10 Channel • 25 Watt Transceiver • Priority**  
The Regency RH250B is a ten-channel VHF land mobile transceiver designed to cover any frequency between 150 to 162 MHz. Since this radio is synthesized, no expensive crystals are needed to store up to ten frequencies without battery backup. All radios come with CTCSS tone and scanning capabilities. A monitor and night/day switch is also standard. This transceiver even has a priority function. The RH250 makes an ideal radio for any police or fire department volunteer because of its low cost and high performance. A 60 Watt VHF 150-162 MHz. version called the RH600B is available for \$454.95. A UHF 15 watt version of this radio called the RU150 is also available and covers 450-482 MHz. but the cost is \$449.95.

## NEW! Bearcat<sup>®</sup> 50XL-GP

List price \$199.95/CE price \$114.95/SPECIAL  
**10-Band, 10 Channel • Handheld scanner**  
Bands: 29.7-54, 136-174, 406-512 MHz. The Uniden Bearcat 50XL is an economical, hand-held scanner with 10 channels covering ten frequency bands. It features a keyboard lock switch to prevent accidental entry and more. Also order part # BP50 which is a rechargeable battery pack for \$14.95, a plug-in wall charger, part # AD100 for \$14.95, a carrying case part # VC001 for \$14.95 and also order optional cigarette lighter cable part # PS001 for \$14.95.



## NEW! Scanner Frequency Listings

The new Fox scanner frequency directories will help you find all the action your scanner can listen to. These new listings include police, fire, ambulances & rescue squads, local government, private police agencies, hospitals, emergency medical channels, news media, forestry radio service, railroads, weather stations, radio common carriers, AT&T mobile telephone, utility companies, general mobile radio service, marine radio service, taxi cab companies, tow truck companies, trucking companies, business repeaters, business radio (simplex) federal government, funeral directors, veterinarians, buses, aircraft, space satellites, amateur radio, broadcasters and more. Fox frequency listings feature call letter cross reference as well as alphabetical listing by licensee name, police codes and signals. All Fox directories are \$14.95 each plus \$3.00 shipping. State of Alaska-RL019-1; State of Arizona-RL025-1; Baltimore, MD-Washington, DC-RL024-1; Buffalo, NY/Erie, PA-RL009-2; Chicago, IL-RL014-1; Cincinnati/Dayton, OH-RL006-2; Cleveland, OH-RL017-1; Columbus, OH-RL003-2; Dallas/Ft. Worth, TX-RL013-1; Denver/Colorado Springs, CO-RL027-1; Detroit, MI/Windsor, ON-RL008-3; Fort Wayne, IN/Lima, OH-RL001-1; Hawaii/Guam-RL015-1; Houston, TX-RL023-1; Indianapolis, IN-RL022-1; Kansas City, MO/KS-RL011-2; Long Island, NY-RL026-1; Los Angeles, CA-RL016-1; Louisville/Lexington, KY-RL007-1; Milwaukee, WI/Waukegan, IL-RL021-1; Minneapolis/St. Paul, MN-RL010-2; Nevada/E. Central CA-RL028-1; Oklahoma City/Lawton, OK-RL005-2; Orlando/Daytona Beach, FL-RL012-1; Pittsburgh, PA/Wheeling, WV-RL029-1; Rochester/Syracuse, NY-RL020-1; San Diego, CA-RL018-1; Tampa/St. Petersburg, FL-RL004-2; Toledo, OH-RL002-3. New editions are being added monthly. For an area not shown above call Fox at 800-543-7892. In Ohio call 800-621-2513.

## NEW! Regency<sup>®</sup> HX1500-GP

List price \$369.95/CE price \$239.95  
**11-Band, 55 Channel • Handheld/Portable**  
**Search • Lockout • Priority • Bank Select**  
**Sidelit liquid crystal display • EAROM Memory**  
**Direct Channel Access Feature • Scan delay**  
Bands: 29-54, 118-136, 144-174, 406-420, 440-512 MHz. The new handheld Regency HX1500 scanner is fully keyboard programmable for the ultimate in versatility. You can scan up to 55 channels at the same time including the AM aircraft band. The LCD display is even sidelit for night use. Includes belt clip, flexible antenna and earphone. Operates on 8 1.2 Volt rechargeable Ni-cad batteries (not included). Be sure to order batteries and battery charger from accessory list in this ad.

## Bearcat<sup>®</sup> 100XL-GP

List price \$349.95/CE price \$203.95/SPECIAL  
**9-Band, 16 Channel • Priority • Scan Delay**  
**Search • Limit • Hold • Lockout • AC/DC**  
Frequency range: 30-50, 118-174, 406-512 MHz. The world's first no-crystal handheld scanner now has a LCD channel display with backlight for low light use and aircraft band coverage at the same low price. Size is 1 1/2" x 7 1/2" x 2 1/2". The Bearcat 100XL has wide frequency coverage that includes all public service bands (Low, High, UHF and "T" bands), the AM aircraft band, the 2-meter and 70 cm. amateur bands, plus military and federal government frequencies. Wow...what a scanner! Included in our low CE price is a sturdy carrying case, earphone, battery charger/AC adapter, six AA Ni-cad batteries and flexible antenna. Order your scanner now.

## Bearcat<sup>®</sup> 210XW-GP

List price \$339.95/CE price \$209.95/SPECIAL  
**8-Band, 20 Channel • No-crystal scanner**  
**Automatic Weather • Search/Scan • AC/DC**  
Frequency range: 30-50, 136-174, 406-512 MHz. The new Bearcat 210XW is an advanced third generation scanner with great performance at a low CE price.


## NEW! Bearcat<sup>®</sup> 145XL-GP

List price \$179.95/CE price \$102.95/SPECIAL  
**10 Band, 16 channel • AC/DC • Instant Weather**  
Frequency range: 29-54, 136-174, 420-512 MHz. The Bearcat 145XL makes a great first scanner. Its low cost and high performance lets you hear all the action with the touch of a key. Order your scanner from CE today.


## TEST ANY SCANNER

Test any scanner purchased from Communications Electronics<sup>™</sup> for 31 days before you decide to keep it. If for any reason you are not completely satisfied, return it in original condition with all parts in 31 days, for a prompt refund (less shipping/handling charges and rebate credits).

Regency  
MX7000

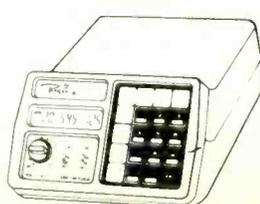

Regency  
HX1500

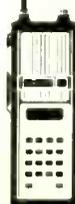

## NEW! Bearcat<sup>®</sup> 800XLT-GP

List price \$499.95/CE price \$317.95  
**12-Band, 40 Channel • No-crystal scanner**  
**Priority control • Search/Scan • AC/DC**  
Bands: 29-54, 118-174, 406-512, 806-912 MHz. The Uniden 800XLT receives 40 channels in two banks. Scans 15 channels per second. Size 9 1/4" x 4 1/2" x 1 1/2".

## OTHER RADIOS AND ACCESSORIES

Panasonic RF-2600-GP Shortwave receiver..... \$179.95  
RD95-GP Uniden Remote mount Radar Detector..... \$128.95  
RD55-GP Uniden Visor mount Radar Detector..... \$98.95  
RD9-GP Uniden "Passport" size Radar Detector..... \$199.95  
BC-WA-GP Bearcat Weather Alert..... \$49.95  
DX1000-GP Bearcat shortwave receiver SALE..... \$349.95  
PC22-GP Uniden remote mount CB transceiver..... \$99.95  
PC55-GP Uniden mobile mount CB transceiver..... \$59.95  
R1060-GP Regency 10 channel scanner SALE..... \$92.95  
MX3000-GP Regency 30 channel scanner..... \$229.95  
XL156-GP Regency 10 channel scanner..... \$139.95  
UC102-GP Regency VHF 2 ch. 1 Watt transceiver..... \$124.95  
P1405-GP Regency 5 amp regulated power supply..... \$69.95  
P1412-GP Regency 12 amp reg. power supply..... \$164.95  
MA256-GP Drop-in charger for HX1200 & HX1500..... \$84.95  
MA518-GP Wall charger for HX1500 scanner..... \$14.95  
MA516-GP Carrying case for HX1500 scanner..... \$14.95  
MA257-GP Cigarette lighter cord for HX12/1500..... \$19.95  
MA917-GP Ni-Cad battery pack for HX1200..... \$34.95  
SMMX7000-GP Svc. man. for MX7000 & MX5000..... \$19.95  
SMMX3000-GP Service man. for Regency MX3000..... \$19.95  
B-4-GP 1.2 V AAA Ni-Cad batteries (set of four)..... \$9.95  
B-8-GP 1.2 V AA Ni-Cad batteries (set of eight)..... \$17.95  
FB-E-GP Frequency Directory for Eastern U.S.A..... \$14.95  
FB-W-GP Frequency Directory for Western U.S.A..... \$14.95  
ASD-GP Air Scan Directory..... \$14.95  
SRF-GP Survival Radio Frequency Directory..... \$14.95  
TSG-GP "Top Secret" Registry of U.S. Govt. Freq..... \$14.95  
TIC-GP Techniques for Intercepting Comm..... \$14.95  
RRF-GP Railroad frequency directory..... \$14.95  
CIE-GP Covert/Intelligent, Elect. Eavesdropping..... \$14.95  
A60-GP Magnet mount mobile scanner antenna..... \$35.95  
A70-GP Base station scanner antenna..... \$35.95  
USAMM-GP Mag mount VHF/UHF ant. w/ 12' cable..... \$39.95  
USAK-GP 3/4" hole mount VHF/UHF ant. w/ 17' cable..... \$35.95  
USATLM-GP Trunk lip mount VHF/UHF antenna..... \$35.95  
Add \$3.00 shipping for all accessories ordered at the same time. Add \$12.00 shipping per shortwave receiver. Add \$7.00 shipping per scanner and \$3.00 per antenna.

## BUY WITH CONFIDENCE

To get the fastest delivery from CE of any scanner, send or phone your order directly to our Scanner Distribution Center<sup>™</sup>. Michigan residents please add 4% sales tax or supply your tax I.D. number. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability, acceptance and verification. All sales on accessories are final. Prices, terms and specifications are subject to change without notice. All prices are in U.S. dollars. Out of stock items will be placed on backorder automatically unless CE is instructed differently. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. Shipments are F.O.B. Ann Arbor, Michigan. No COD's. Most products that we sell have a manufacturer's warranty. Free copies of warranties on these products are available prior to purchase by writing to CE. Non-certified checks require bank clearance. Not responsible for typographical errors.

Mail orders to: Communications Electronics<sup>™</sup>, Box 1045, Ann Arbor, Michigan 48106 U.S.A. Add \$7.00 per scanner for R.P.S./U.P.S. ground shipping and handling in the continental U.S.A. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping charges are three times continental U.S. rates. If you have a Discover, Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-USA-SCAN. In Canada, order toll-free by calling 800-221-3475. WUI Telex anytime, dial 671-0155. If you are outside the U.S. or in Michigan dial 313-973-8888. Order today. Scanner Distribution Center<sup>™</sup> and CE logos are trademarks of Communications Electronics Inc.

‡ Bearcat is a registered trademark of Uniden Corporation.  
† Regency is a registered trademark of Regency Electronics Inc. AD #070286-GP

Copyright © 1986 Communications Electronics Inc.

For credit card orders call  
**1-800-USA-SCAN**

**COMMUNICATIONS  
ELECTRONICS INC.**

**Consumer Products Division**

P.O. Box 1045 □ Ann Arbor, Michigan 48106-1045 U.S.A.  
Call 800-USA-SCAN or outside U.S.A. 313-973-8888

# Using the Operational Transconductance Amplifier

*Discover the advantages of working with this often-disregarded member of the op-amp family*

By C.R. Fischer

**H**undreds of uses for the common operational amplifier have been paraded through pages of books and magazine articles during the past 20 years. Strangely, though, several other devices in the op-amp family have been virtually ignored during the same period. One of the lesser-known close cousins of the op amp is the operational transconductance amplifier, or OTA. This nifty little device has attributes that are difficult to duplicate by other means.

Among the OTA's functions is a unique biasing input that allows the device to be used as a voltage- or current-controlled resistor or switch. This feature makes it invaluable for varying parameters in such analog circuits as waveform generators, amplitude and frequency modulators, electronic musical instruments, etc. While the operational transconductance amplifier resembles a typical operational amplifier at first glance, there are some essential differences that cannot be ignored if you expect it to operate properly. In this article, we will cover these differences, show you some basic circuits to get you started experimenting, and talk about some of the OTAs currently on the market.

## Defining the OTA

For purposes of comparison, Fig. 1 shows the pinouts of the ordinary

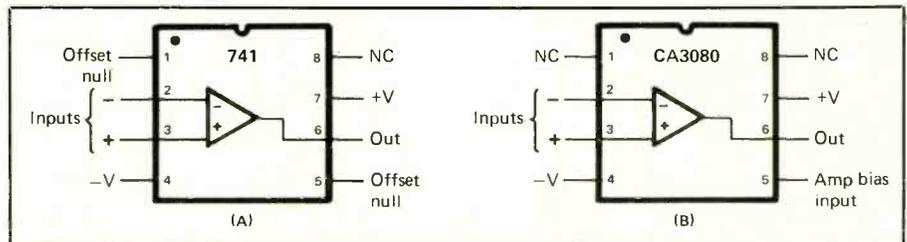


Fig. 1. Pinouts of the ordinary 741 op amp (left) and CA3080 operational transconductance amplifier (right). Though both appear to be identical, note that the 741 has offset null, while the CA3080 has a bias input.


741 op amp and the CA3080 operational transconductance amplifier. The two devices appear to be identical at first glance, but if you look closely, you will notice that the CA3080 has an amplifier bias input at pin 5. This input provides a means for varying the conductance (reciprocal of resistance) of the CA3080 OTA by varying the current flowing into this pin. With no current, there is no output whatsoever, while an input current of about 1.5 mA produces maximum gain.

Pin 5 is 0.7 volt above the negative supply potential, and input current

must be limited to less than 2 mA to avoid damaging the IC. Note also that the CA3080 requires a dual-polarity power supply that delivers no more than +18 and -18 volts. To remain on the safe side, you should limit power supply potential to +15 and -15 volts.

Two other idiosyncrasies of the OTA are the input and output structures. The inputs are capable of handling only very-low-level signals, ranging from 10 to 40 mV in the case of the CA3080. Applying a higher-level input causes severe distortion in the output signal, though some new-

Fig. 2. A simple single-chip voltage controlled amplifier, or vca.

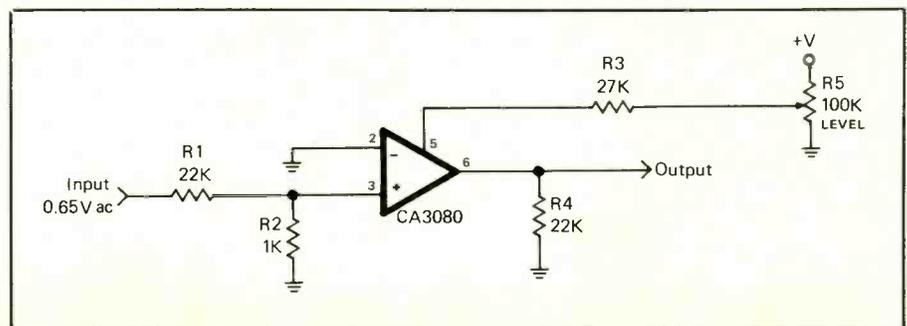

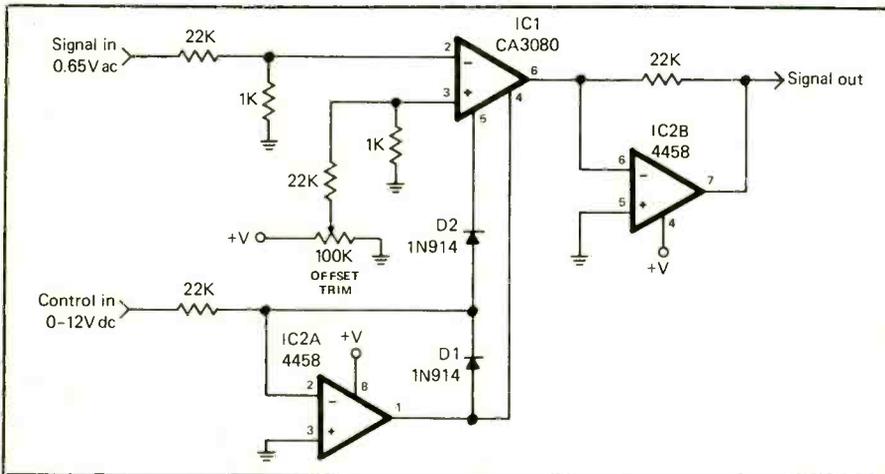


Fig. 3. Improved voltage-controlled amplifier uses ordinary operational amplifiers as a voltage-controlled circuit source and an output buffer.

er chips have been designed to safely handle higher-level inputs.

Another way the OTA differs from conventional op amps is that it has a current output with an impedance in the tens of megohms. If this is a disadvantage in a given application, you can simply follow the OTA with an ordinary op amp, which then serves as an output buffer.

A load resistor to ground can convert the output current back to a voltage. Since the value of this resistance controls the voltage gain, the OTA gives control of this parameter with a single component.

In essence, there are three ways to control the output level of the OTA. You can vary the input signal voltage level, the load resistance, and the control current. In most cases, the


first two would be fixed and only the control current would be varied.

### OTA Applications

A very simple voltage-controlled amplifier, or vca, is shown in Fig. 2. The  $R1/R2$  input attenuator has been set for a 0.6-volt ac input signal. Current to the bias output of the OTA is limited by  $R3$ ,  $R4$  is the output load, and  $R5$  provides a variable control voltage. With the value shown for  $R5$ , the circuit's gain range is from 0 to 1 (unity).

If an envelope generator is used with the Fig. 2 circuit, this vca can be used to reproduce the attack and decay feature of a musical instrument. In fact, this type of circuit will work in any application where resistance must be changed and manual control

Fig. 4. Using an operational transconductance amplifier as an analog switch to gate high-level signals from digital logic.

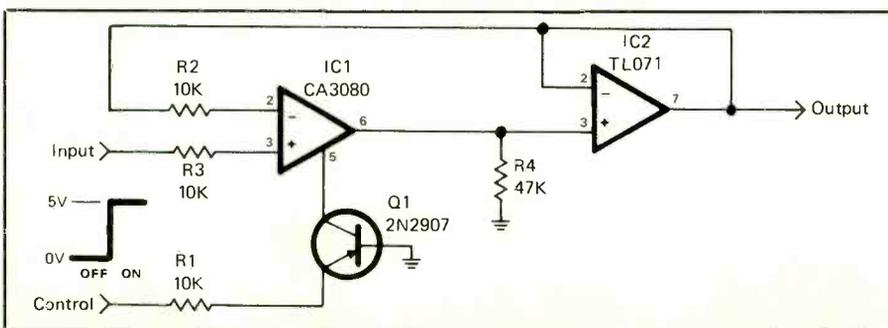

is impractical or impossible. Remote controls, amplitude modulators and computer control of analog circuits (use a D/A converter) are a few representative examples.

Though the Fig. 2 circuit can be used as is, performance can be improved by using the circuit shown in Fig. 3 (adapted from a similar vca in Walter Jung's *IC Op Amp Cookbook*). Directly driving the IC1 CA3080 OTA is the IC2A voltage-controlled current source. This design eliminates the need for a current-limiting resistor and references the control voltage to ground instead of to  $-14.3$  volts.

Serving as a buffer for IC1, IC2B gives the improved vca a reasonably low output impedance whose output level is set by  $Rf$ . The OFFSET TRIM control in the CA3080's input circuit is used to null any undesired offset voltage that can cause an audible "pop" when the control voltage is rapidly changed. In some cases, control may not be necessary if pin 2 is grounded.

A vca is usually modulated with a changing voltage, but there is no reason why it cannot be gated so that it functions as an analog switch. This opens a whole new range of applications that allow you to remotely turn on and off signals. Chips like the 4016 and 4066 are inexpensive and easy to find. However, since they are limited to a 15-volt signal range and require a switching signal that equals the supply voltage in amplitude, you might find it more convenient to use an OTA instead of these devices.

Figure 4 shows an OTA configured as an analog switch. Transistor Q1 switches the input on and off with a low-level signal. In selecting  $R1$ , scale its value at a rate of 2,000 ohms per volt on the control line. With the correct value, you can control the switch with 5-volt TTL or higher-voltage CMOS logic.

Figure 5 shows a very common use for the analog switch. This sample/hold circuit "samples" a voltage at

its input when triggered and continues to "hold" that level until another command is issued. When the control line goes high, the *IC1* OTA acts as a closed switch and charges *C1* until the input and output voltages are equal. With the line low, the "switch" opens so that the voltage is stored in *C1*. To prevent leakage currents from introducing errors, use a low input bias operational amplifier like the CA3140 or LM351 for *IC2* and polyester or polystyrene capacitor for *C1*.

There are quite a few uses for the sample/hold circuit in electronics. For example, it can be used to create a random music box, as shown in Fig. 6. Here *IC3* is a simple voltage-controlled oscillator (vco) that acts as a tone source and serves as an input for the Fig. 5 sample/hold circuit. Trigger generator *IC4* can be varied from 0.5 Hz to beyond 10 kHz. The sample/hold circuit picks voltages off the triangle-wave output of *IC3* and feeds them back to the vco to give the familiar Hollywood "computer language" sound used in motion pictures and TV shows. You are likely to find this neat little toy quickly appropriated by your children, however.

You may have noticed that the circuits in Figs. 4 and 5 lack the input attenuators that were necessary in the vca circuits. This is possible because here the 10-to-40-mV level applies the difference between the - and + inputs. Since one of the vca's inputs in Figs. 2 and 3 was grounded, the other input had to be near ground potential. In a switching circuit, however, when the switch is open, no signal can get through. Also, distortion is meaningless. When the switch is closed, the output buffer sends the input signal back to the remaining input. With both inputs at the same level, distortion is not a problem.

### Some Available OTAs

In this article, we showed representative circuits built around RCA's

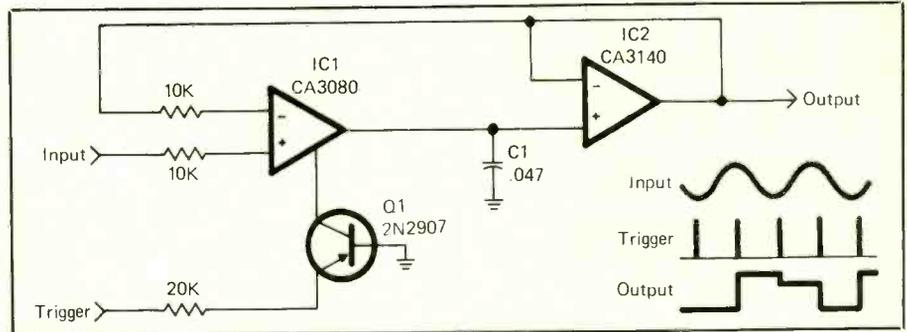


Fig. 5. A typical OTA sample/hold circuit.

CA3080 because this OTA is readily available and inexpensive to purchase. It costs about \$1.00 from mail-order suppliers. RCA (Solid State Div., P.O. Box 3200, Somerville, NJ 08876) has been marketing the CA3080 since 1971. It is still used in new designs today. It may suffer from a severely limited input level that compromises its signal-to-noise ratio, but the CA3080 is still useful where this is not an important consideration. Note, too, that RCA also manufactures the CA3280, a dual version of the CA3080.


National Semiconductor's (2900 Semiconductor Dr., Santa Clara, CA 95051) very interesting and versatile LM13600 dual OTA has several features not found elsewhere. Among these are linearizing diodes

that reduce signal distortion and an internal buffer for each OTA. Because the buffers are not internally wired, you can substitute an external buffer if desired. National's applications booklet for the LM13600 has a variety of circuits for the experimenter, including a stereo volume control, voltage-controlled filters (vcfs), and a two-chip sine-wave vco with a range of 5 Hz to 50 kHz, the last at less than 1% distortion.

Since audio signal processing and electronic music make up a significant portion of the OTA market, it should come as no surprise that manufacturers have designed ICs especially for audio applications. While these devices are much more expensive than the CA3080, their im-

(Continued on page 83) ◆

Fig. 6. Adding these two IC circuits and a few other parts to the sample/hold circuit in Fig. 5 produces an entertaining random music machine.

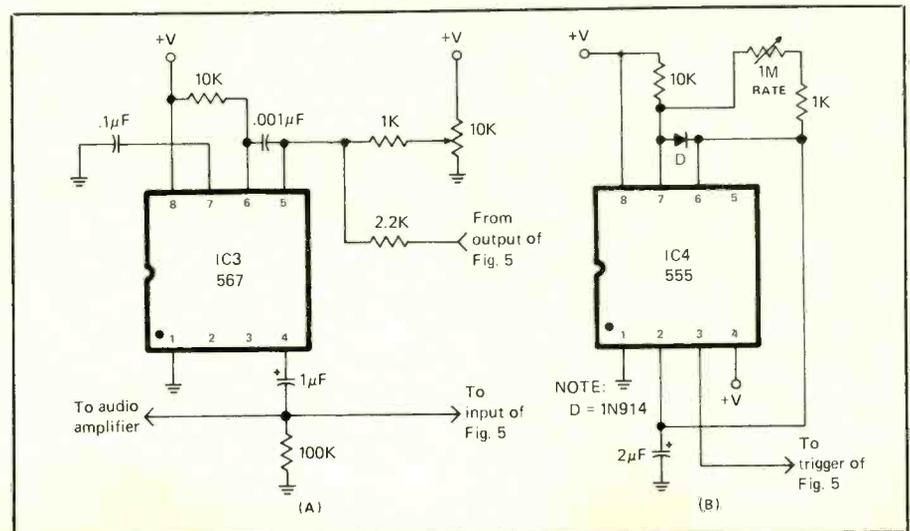

\* \*

# 2 CENTS PLAIN

\* \*

That's about all it costs subscribers for each page of editorial matter in **MODERN ELECTRONICS** . . . every month. No charge for informative advertisers' messages. Or for free information requested on our bound-in postpaid Free Information Service card.

**A bargain?** You bet! **MODERN ELECTRONICS** is a veritable one-stop source of "hard" information for enthusiasts whose interests spread across the entire spectrum of electronics and computers for work and play. The latest technical information and news written by a galaxy of authoritative writers—Forrest Mims on "Experimenting," Don Lancaster on "Hardware Hacking," Stan Prentiss on "Video," Len Feldman on "Audio," Glenn Hauser on "Communications," and Eric Grevstad on "Personal Computers," to name a few authors who share their specialized experiences with readers every month.

**This neat package** keeps everyone abreast of the important developments in electronics and computers. From new devices and circuits to useful construction projects to evaluations of the latest products. Both "how to do" and "how it works" information increases your technical competence every page of the way. Two cents a shot. And hands-on product evaluations make you a wiser buyer, whether it's on a test instrument or a video recorder. So whether you're a service technician, an engineer, a budding one in a technical career path, or an active electronics enthusiast, **MODERN ELECTRONICS** will serve you well. Subscribe and be sure to get every information-packed issue delivered to you every month. It's important reading you can't afford to miss!

Just fill out the coupon and mail with your check, money order or credit-card information (Visa or MasterCard) to enter your subscription. Do it today to ensure earliest delivery!

-----

## MODERN ELECTRONICS

76 North Broadway, Hicksville, NY 11801

Please send me Modern Electronics for  3 Years  2 Years  1 Year


Name \_\_\_\_\_  
 Street \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_ Zip \_\_\_\_\_

Charge My Order To: Payment Enclosed \$ \_\_\_\_\_

MasterCard      3 Years (36 issues) . . . . . \$45.00   
                                  2 Years (24 issues) . . . . . \$31.00   
 VISA                    1 Year (12 issues) . . . . . \$16.97

Account Number  
 [ ] [ ] [ ] [ ]

To preserve your copies of

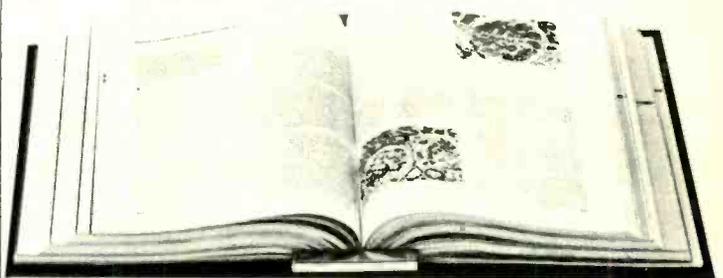

A choice of handsome and durable library cases-or binders-for your copies of **MODERN ELECTRONICS**. Both styles bound in green library fabric stamped in gold leaf.

**Cases:** Each case holds 12 issues.  
 Price per case \$7.95; three for \$21.95;  
 six for \$39.95 postpaid.

**Binders:** Each binder holds 12 issues.  
 Issues open flat. Price per binder \$9.95;  
 three for \$27.95; six for \$52.95 postpaid.

*(Canadian and foreign requests should also include an additional \$2.50 per item for shipping costs.)*


-----  
**To: Jesse Jones Industries (Since 1843)**  
**P.O. Box 5120, Dept. MOD, Philadelphia, PA 19141**

I enclose my check or money order for \$ \_\_\_\_\_.  
 Please send me \_\_\_\_\_ MODERN ELECTRONICS

Files.       Binders.



*(Please Print)*

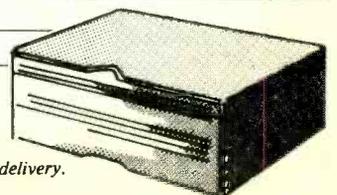Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_  
 State \_\_\_\_\_  
 Zip \_\_\_\_\_



*Please allow approximately 4 weeks for delivery.*

# Electronic Dice

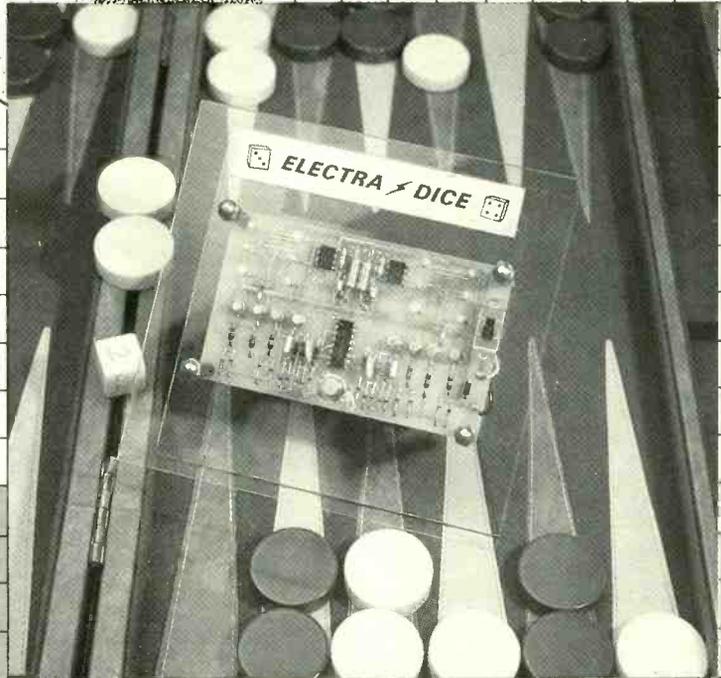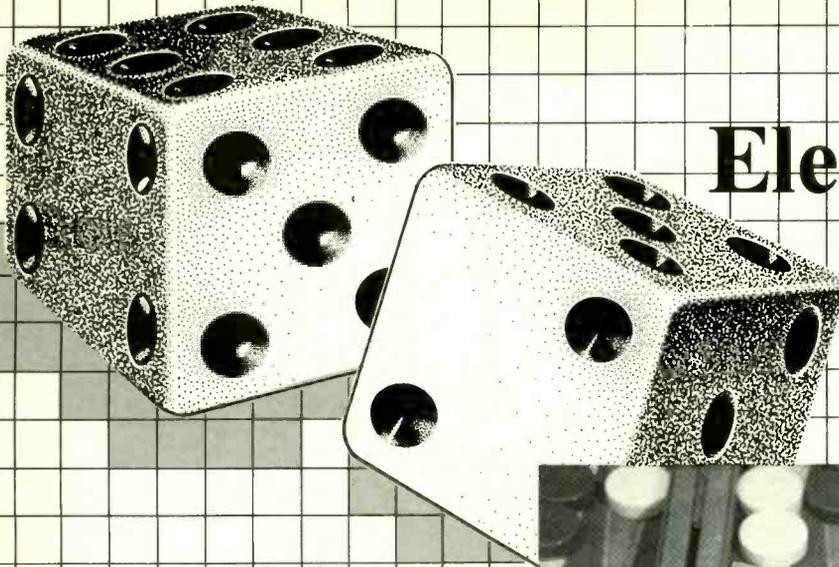

*Visible circuit with LEDs makes playing board games more fun than with traditional cubes and assures players of true "rolls"*

By Bill Owen

Almost everyone likes playing board games in which the action turns on the roll of dice. The old way of playing such games with actual dice cubes may not be unexciting, but "Electra Dice" described here can make the playing more fascinating as players press a button and watch light-emitting di-

odes flicker until they stop rolling to present the numbers of the roll.

The fascination goes beyond just flickering of some LEDs. Unlike most projects that are hidden inside utility boxes, you sandwich Electra Dice between two layers of clear Plexiglass so that players can view the circuitry as well as the "roll" of the electronic dice. Moreover, having the numbers generated electronically gives one a sense of confidence in the trueness of a roll.

The project costs only about five times what you would pay for ordinary dice cubes. And it is convenient to use because it runs on a standard 9-volt battery.

## *About the Circuit*

Shown in Fig. 1 is the overall schematic diagram of Electra Dice. It consists of two identical halves that form the two "dice." Each die consists of seven LEDs that randomly

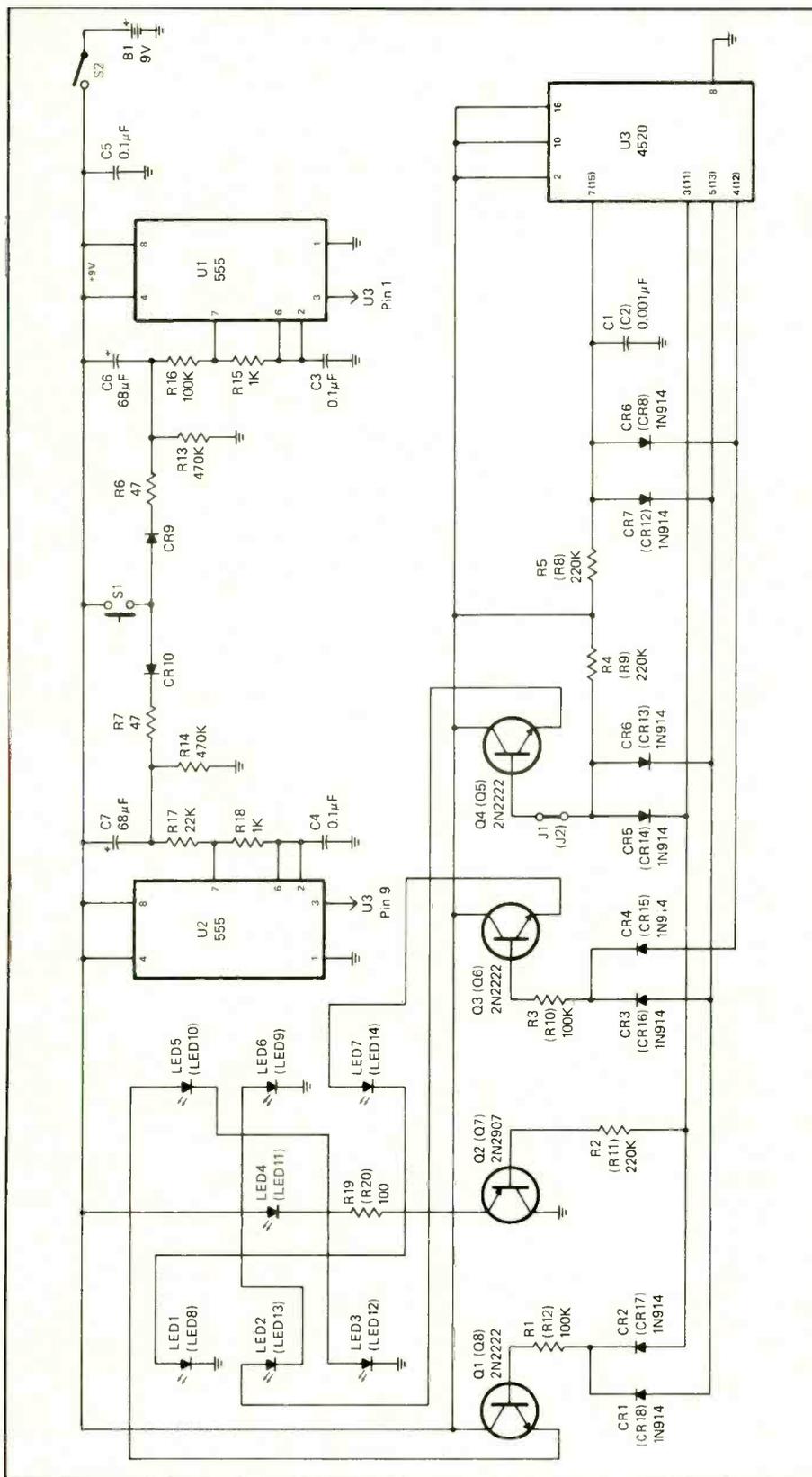


Fig. 1. Though project has two dice display circuits, only one die's driver/LED system is shown. Remaining circuitry is mirror-image of LED1-LED7/Q1-Q4 circuitry. Completing circuitry is indicated by numbers in parentheses.

**PARTS LIST**

**Semiconductors**  
 CR1 thru CR18—1N914 switching diode  
 LED1 thru LED14—3-mm red light-emitting diode

Q1, Q3, Q4, Q5, Q6, Q8—2N2222 npn transistor  
 Q2, Q7—2N2907 pnp transistor  
 U1, U2—555 timer  
 U3—4520 dual decade counter

**Capacitors**  
 C1, C2—0.001- $\mu$ F disc  
 C3, C4, C5—0.1- $\mu$ F disc  
 C6, C7—68- $\mu$ F, 16-volt tantalum

**Resistors** (1/4-watt, 5% tolerance)  
 R1, R3, R10, R12, R16—100,000 ohms  
 R2, R4, R5, R8, R9, R11, R17—220,000 ohms  
 R6, R7—47 ohms  
 R13, R14—470,000 ohms  
 R15, R18—1,000 ohms  
 R19, R20—100 ohms

**Miscellaneous**  
 B1—9-volt transistor battery  
 SW1—Spst pushbutton switch  
 SW2—Spst slide switch

Printed-circuit board; 1/8"-thick Plexiglass panels (2); 4-40  $\times$  2 1/4" machine hardware; IC sockets or Molex Soldercons (optional—see text); battery clip for B1; double-sided foam tape; hookup wire; solder; etc.

**Note:** The following items are available from NRG Electronics, P.O. Box 24138, Ft. Lauderdale, FL 33307: P.C. board and all electronic components for \$14.95; drilled Plexiglass panels with hardware and label for \$4.95. Add \$2.00 S&H per order. Florida residents, please add 5% sales tax.

light to form the usual 1 through 6 dots that appear on conventional dice. Though traditional dice cubes have a maximum of six dots on the highest number face, the Electra Dice has seven LEDs. This gives the same effect that you would have if you were playing with conventional dice when you roll a 1, 3 or 5. It makes the display appear balanced, with the odd dot in the center, rather than off to one side.

After closing power switch SW2, the action begins when ROLL push-

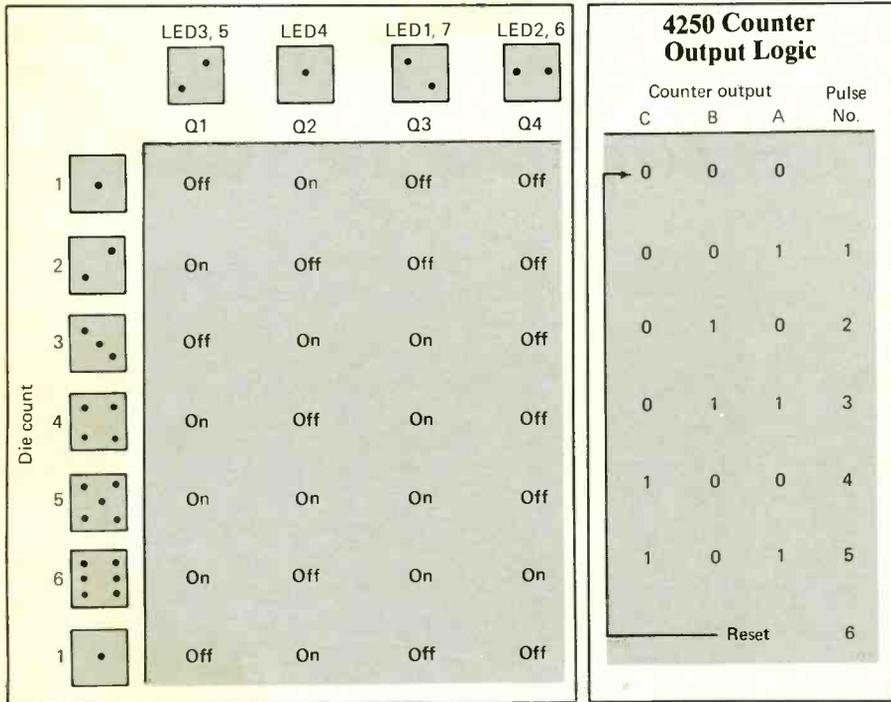


Fig. 2. Conditions for each driver transistor for specific die counts.

button switch *SW1* is momentarily pressed and released. Separate 555 timer ICs *U1* and *U2* then begin counting down. During the count-down periods, which are different for the two timer circuits, counter *U3* continuously rolls the LED "dice." When the two timer stages reach the end of their countdown cycles, the dice stop rolling and the LED dice displays "freeze." At this point, the left and right dies will separately display a number between the usual 1 and 6.

Light-emitting diodes *LED1* through *LED7* make up the left die. *LED8* through *LED14* the right die. Because the project consists of mirror-image circuitry, only the portion for the left die is shown in Fig. 1. The portions that make up the right die are indicated by the numbers in parentheses.

During a roll, the LEDs are continuously and repeatedly sequenced from 1 through 6. Examining the six different die counts in Fig. 2 makes it clear that only four different combinations of LEDs are required. There-

fore, *LED1/LED7*, *LED2/LED6* and *LED3/LED5* are connected in series pairs so that both LEDs in each pair light simultaneously when the circuitry decodes their specific sequences. Transistors *Q1* through *Q4* electronically switch on and off the LED pairs. (This same action occurs in the second half of the circuit, with *Q5* through *Q8* controlling *LED8* through *LED14*.)

Figure 2 shows the manner in which these four driver transistors can be switched on to derive the six die counts. Note that *Q2*, a pnp transistor, is different from the other three driver transistors in that a high at its base input turns off and a low turns on the transistor. The other transistors are all npn devices.

Unfortunately, there does not exist a ready-made electronic circuit or IC that will produce the high and low inputs to the transistors to properly sequence them. However, a standard digital counter IC's outputs can be used either directly or in combination to do the job.

Shown in the Counter Output Lo-

gic Table are the highs and lows present at the outputs of the 4520 counter IC (*U3* in the project) as pulses are fed into the clock input. In this circuit, a pulse is a transition from high to low and back to high. The 4520 is a dual binary counter. Its four outputs are capable of counting from zero to 15 (for a total count of 16). Because the 4520 is a dual binary counter, it is a natural as the sequencing device for a project in which two dies are required, as is the case with the Electra Dice because all we need is the one integrated circuit.

To display the six die counts with seven LEDs, the four transistors must receive six unique input combinations. To achieve this, the counter is rigged to reset back to zero after the sixth pulse is counted. Only three counter outputs are required to provide the six unique inputs required. These are the A, B and C outputs from the 4520, which are added together using diodes or connected directly, as in the case of *Q2*, to the bases of the driver transistors.

Digital circuit design is usually the result of logical expressions written to satisfy specific requirements. The designer works from the desired outputs—such as the die patterns in Electra Dice—back to the available outputs from the counter IC. Transistors and diodes permit logical expressions to be carried out electronically. A logical expression can be formulated for each desired result. Because the seven LEDs can be controlled by four transistors, a logical expression is needed for each transistor in terms of the A, B and C counter outputs. The expressions with their electronic equivalents are shown in Fig. 3.

Using a pnp transistor for *Q2* satisfies the requirement for a low at output A of counter *U3* for *LED4* to light when a 1, 3 or 5 is rolled. The OR expression as in "A OR B" finds its electronic equivalent in two diodes that connect together at the base, allowing a transistor to turn on

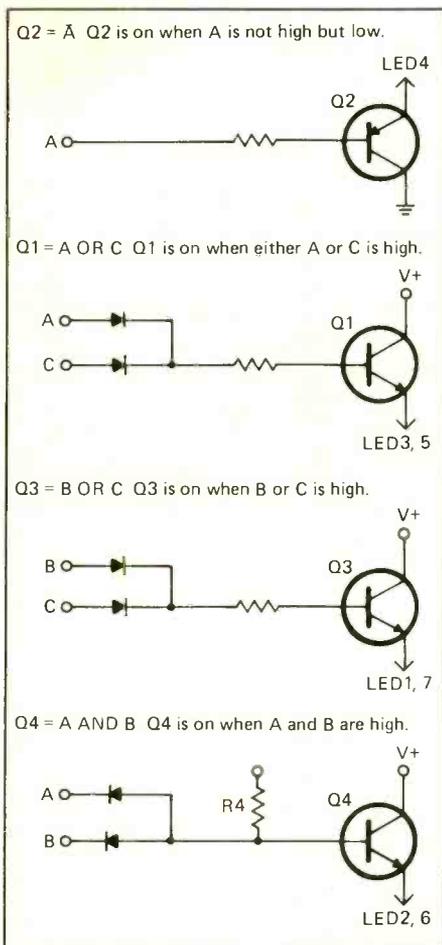


Fig. 3. The logic expressions and electronic equivalents for each driver transistor.

from either input. The AND expression follows from the fact that Q4 will be turned on by R4 only if A AND C are high simultaneously.

As mentioned above, U3 must be reset after the sixth pulse. Otherwise, it would count right on up to 16 and cause problems with counts coming out of turn. The sixth pulse causes the B and C outputs to both go high. This condition is detected and used to reset the counter. If either the B or the C output is low, the reset input is also low. However, when both B and C are high, the counter automatically resets to zero.

### Construction

There is nothing particularly critical with regard to circuit layout. For

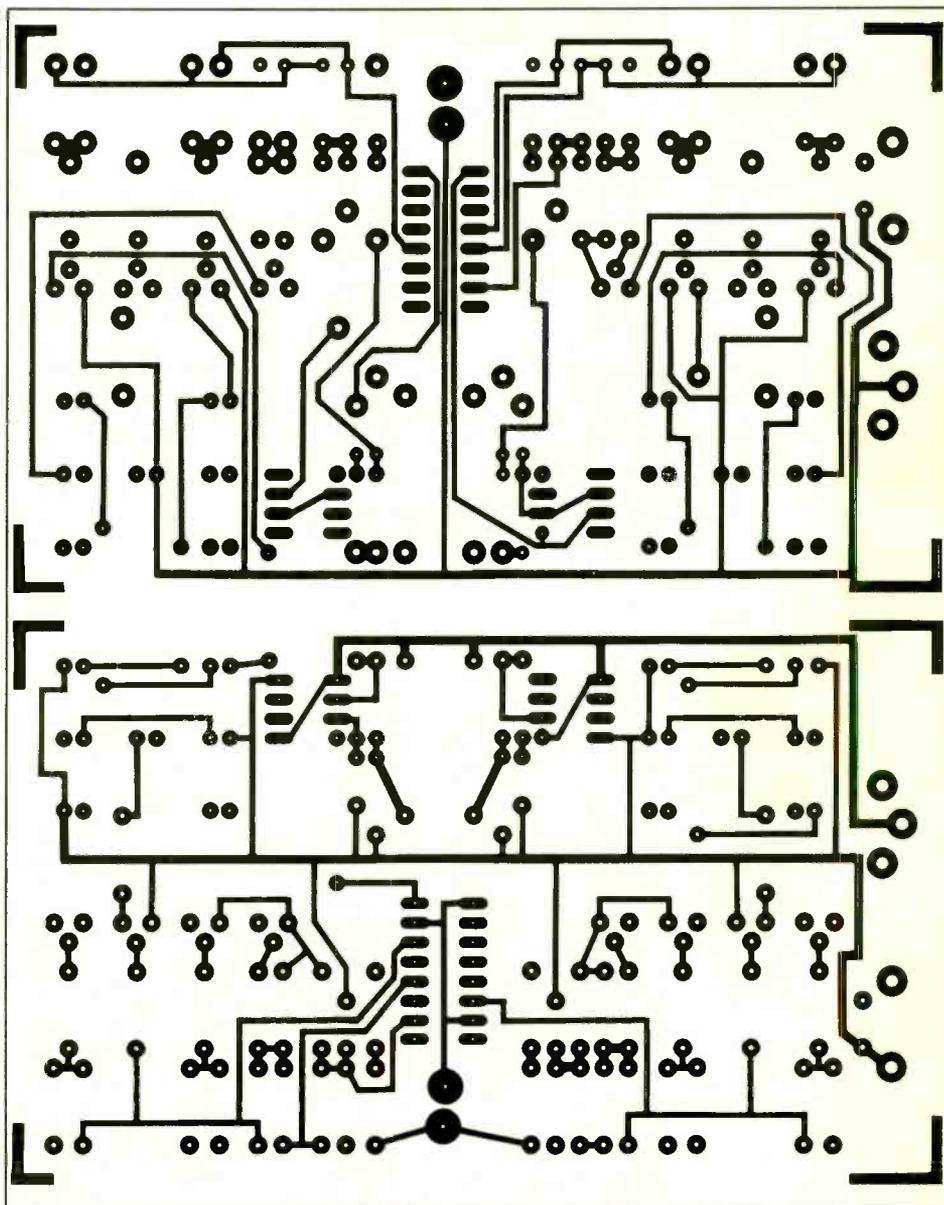


Fig. 4. Actual-size etching-and-drilling guides for both sides of printed-circuit board.

convenience, though, printed-circuit board construction is recommended. You can fabricate this double-sided pc board, using the actual-size etching-and-drilling guides in Fig. 4. If you do, make sure that both guides are properly registered on the pc blank during exposure. When installing components on a homemade double-sided pc board, solder all leads that contact the top and bottom traces on both sides of the board. Additionally, it is necessary

to solder short lengths of solid hook-up wire or component leads in the holes that bridge conductors on both sides of the board.

If you prefer not to etch and drill your own board, you can purchase a kit of parts that contains a ready-to-wire pc board from the source given in the Note at the end of the Parts List. The board in this kit has plated-through holes that eliminate the need for having to solder on both sides.

Referring to Fig. 5, begin wiring

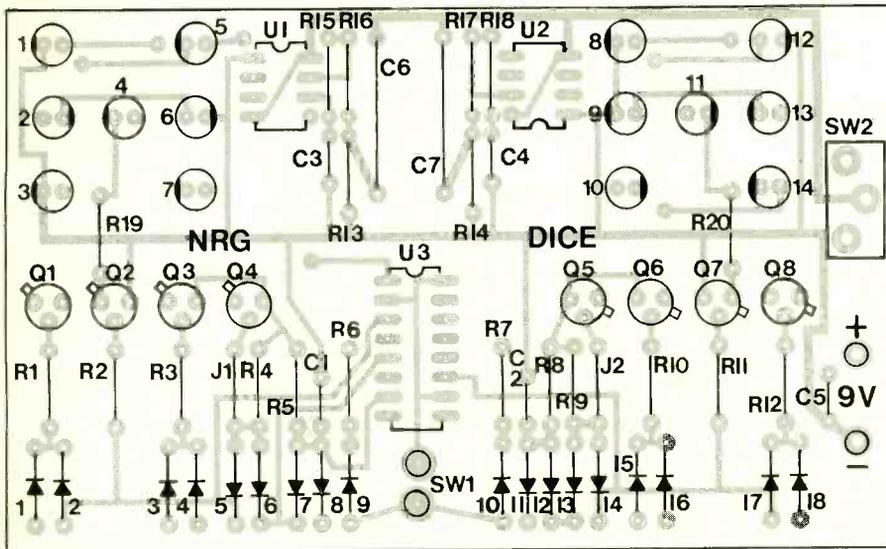


Fig. 5. Components placement/orientation diagram for pc board.

the board by installing and soldering into place the diodes at the locations indicated by numbers only along the bottom of the board when held in the orientation shown. Make sure you properly orient these and all other polarized and indexed components—tantalum capacitors, LEDs, transistors and ICs—before soldering their leads or pins to the board's copper pads.

After installing the diodes, proceed with the resistors, insulated jumper wires (in the locations indicated by J1 and J2) and capacitors. Next, install the ICs. You can install these directly on the board or via optional sockets that make it easier to troubleshoot the circuit and replace a defective IC if this should become necessary. Use sockets only if the plated-through board is used. You can not use sockets with a homemade board because they do not provide access to solder the pins to the required pads on the top of the board. Instead, use Molex Soldercons that do give soldering access.

Practice safe handling procedures for the 4520 CMOS decade counter IC. One way to ensure against damaging this IC with static electricity is to make sure that your hand is the

only thing that touches it once it is removed from its protective carrier and that you hold the board in your other hand as you plug it into the holes in the board, the socket or the Molex Soldercons.

Install the transistors, making sure their emitter, base and collector leads plug into the appropriate holes and that they stand approximately  $\frac{1}{4}$ " above the surface of the board. Install the 2N2907 transistors in the Q2 and Q7 locations and the 2N2222 transistors in all other locations. Note that the tabs pointing to the transistors' emitters point upward and slightly to the left for Q1 through Q4 and downward and slightly to the right for Q5 through Q8 as shown in Fig. 5.

Now install the LEDs in the locations indicated by numbers only in the upper-left and upper-right. Make sure that the cathode leads plug into the holes indicated by the flats in the case outlines. Let the LEDs stand a uniform  $\frac{3}{4}$ " above the surface of the board. You might want to slip  $\frac{3}{4}$ " lengths of small-diameter plastic tubing over each anode lead before plugging the LEDs into the board. The tubing serves two purposes—one is to give a uniform height, the

other to provide insulation to prevent the LED leads from shorting to each other.

Bear in mind that light-emitting diodes are heat sensitive and are easily damaged by excessive soldering heat. Therefore, it is a good idea to use small heat sinks or the jaws of longnose pliers to absorb the heat as you solder each lead to its copper pad on the board. When all LEDs have been soldered into place, arrange them in symmetrical patterns.

Solder the leads of the battery clip to the labeled 9V pads on the right side of the board. The red clip lead goes to the hole labeled with the + sign, the black lead to the hole labeled with the - sign.

Prepare two 2" lengths of hookup wire by stripping  $\frac{1}{4}$ " of insulation from both ends. If you use stranded wire, tightly twist together all fine strands of wire at each end and sparingly tin with solder. Solder one end of each wire to the pads labeled SW1. Then install slide switch SW2 directly on the board.

Cut two sheets of  $\frac{1}{8}$ "-thick Plexiglass to 6"  $\times$  5 $\frac{3}{4}$ ". Drill four  $\frac{1}{8}$ " holes through both sheets for mounting the circuit-board assembly centered in the area. Drill a fifth hole for pushbutton switch SW1 in the top panel. Place a  $\frac{1}{2}$ "  $\times$   $\frac{3}{4}$ " strip of double-sided foam tape exactly in the center of the bottom panel for mounting the 9-volt battery.

Mount SW1 in its hole in the top panel. Solder the free ends of the two hookup wires to the lugs of SW1. Then use 1" spacers and 4-40  $\times$   $\frac{3}{4}$ " machine hardware to sandwich together the circuit board and Plexiglass panels. When you are finished, there should be eight spacers, two at each corner, separating the circuit board from each Plexiglass panel.

Press the battery into the foam tape and clip the connector onto its terminals. Reach under the top Plexiglass panel and flip SW2 to on. The LEDs should immediately begin flashing and eventually stop at a roll


pattern. Press and release *ROLL* switch *SW1*; the LEDs should again flash until they stop at a roll pattern. Press and release *SW1* several more times to assure that the circuit is operating properly. If everything appears to be okay, Electra Dice is ready to be put into service.

If the project is not working properly, turn off the power and remove the clip from the battery. Before suspecting a bad component, carefully check all connections to determine if you missed soldering one. Also check for cold-soldered joints, re-soldering any that are suspicious. If this does not clear up the problem, carefully check the polarization and orientation of all diodes, transistors, LEDs, ICs and the two tantalum capacitors.

Whenever Electra Dice is not being used for playing games, always turn off its power. Though the circuit itself does not draw much current, the LEDs do. Note, too, that mounting power switch *SW2* directly on the board instead of on the top

panel makes it almost impossible for *SW2* to be toggled on by accident.

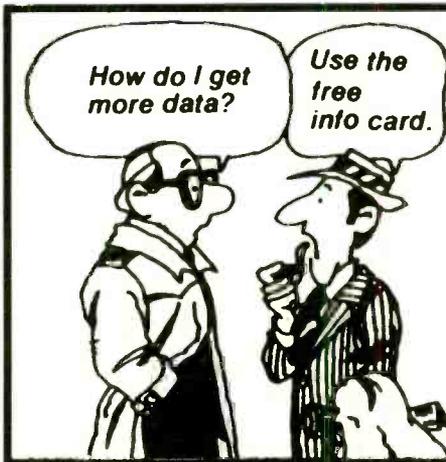
To play with Electra Dice, all you do is turn on the power and press and release the *ROLL* switch. Then sit back and watch the flickering of the LEDs gradually come to a halt.



### Free Product Information

Readers can obtain free information on products advertised by certain companies, as well as for some editorially mentioned products. Simply circle the appropriate number printed below an advertisement onto the Modern Electronics "Free Information Service" card bound into this issue. After filling in your name and address, just mail the postpaid card. Your request will be forwarded directly to the advertiser with a mailing label prepared by our reader-service department to ensure speedy response.

## GET THE WORD ON SWL RECEIVERS

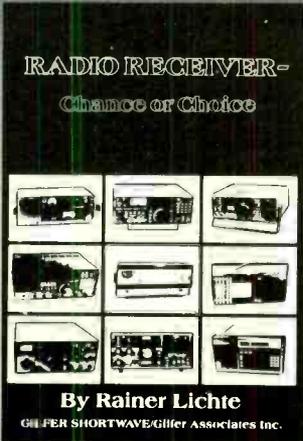

Find out how they *really* perform with this comprehensive new book by famous radio engineer, Rainer Lichte. He puts all the popular SWL receivers through real-life tests and gives you the actual results (so you have something besides manufacturer's specs. to judge by). Covers Panasonic, Sony, Yaesu, Kenwood, Drake, Eska, Hitachi, Grundig, Phillips, JVC, Dymek, ITT, ICOM, Bearcat, and more (explains the mysteries of tech. specs., too). 256pp of *straight* info. Send \$18.50 (+ \$2 Shipping and Handling) to:

**POPULAR COMMUNICATIONS**  
76 N. Broadway, Hicksville, NY 11801

CIRCLE 87 ON FREE INFORMATION CARD

Say You Saw It In Modern Electronics

# SURPRISE!

You don't have to be a licensed ham to join ARRL and receive **QST** every month.



Join the over 10,000 radio enthusiasts who are unlicensed ARRL ASSOCIATE MEMBERS, and receive **QST** every month. It's jam-packed with articles and columns on ham-DX, VHF-UHF, "Making Waves" — for young hams, radio clubs, emergency communications, antennas and simple build-it yourself projects up through the cutting edge of communications technology. We hope to have *you* as a member!

### MEMBERSHIP APPLICATION

Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ Prov./State \_\_\_\_\_ PC/Zip \_\_\_\_\_

- Yes! Sign me up as an ARRL member. Send me 12 big issues of **QST** and my membership certificate. Enclosed is \$25 (\$33 outside of the US).
- Please send me information on how to become a licensed radio amateur.



Expires \_\_\_\_\_  
Bank. No. \_\_\_\_\_ Expires \_\_\_\_\_

**The American Radio Relay League**  
225 Main St. Newington, CT. 06111 USA ME

CIRCLE 94 ON FREE INFORMATION CARD

## Piezoelectric Buzzers

By Forrest M. Mims III

**Piezoelectric sound** sources have been available for more than 20 years. In the mid-1960's, Mallory introduced the Son-alert™, a piezoelectric sound source installed in a plastic housing with a built-in driver circuit. Today numerous kinds of self-contained piezoelectric buzzers, as they are often called, are readily available from many sources. Radio Shack's catalog, for example, describes piezoelectric buzzers that produce continuous, pulsing, dual, and chime sounds.

Consumer and industrial applications for piezoelectric buzzers abound. They are used in wrist and pendant watches, alarm clocks, calculators, microwave ovens, telephones, smoke alarms, geiger counters, automobiles, and in many other consumer appliances and industrial equipment. Because piezoelectric buzzers and elements are inexpensive, easy to use, and highly reliable, they are particularly popular with experimenters.

### Piezoelectric Buzzer Design

Piezoelectricity literally means pressure electricity. It is the phenomenon wherein a voltage is produced when pressure is applied to certain crystals. Conversely, piezoelectric crystals change their shape in response to an applied voltage. Crystals of quartz, tourmaline, and Rochelle salt exhibit piezoelectric properties. Though its piezoelectric effect is weak, quartz is the most important of these crystals. It is used to make highly reliable and reproducible mechanical oscillators whose frequency varies only slightly with changes in temperature. Such crystals provide frequency standards and highly stable oscillators for digital clocks and watches, television receivers, radio transmitters, and so forth.

Rochelle salt crystals have long been used to make high-impedance crystal earphones and microphones. Development of high-intensity piezoelectric buzzers and related devices awaited the development of a family of manmade ferroelectric ceramics having excellent piezoelectric properties. Among the best developed of these is zirconate titanate.

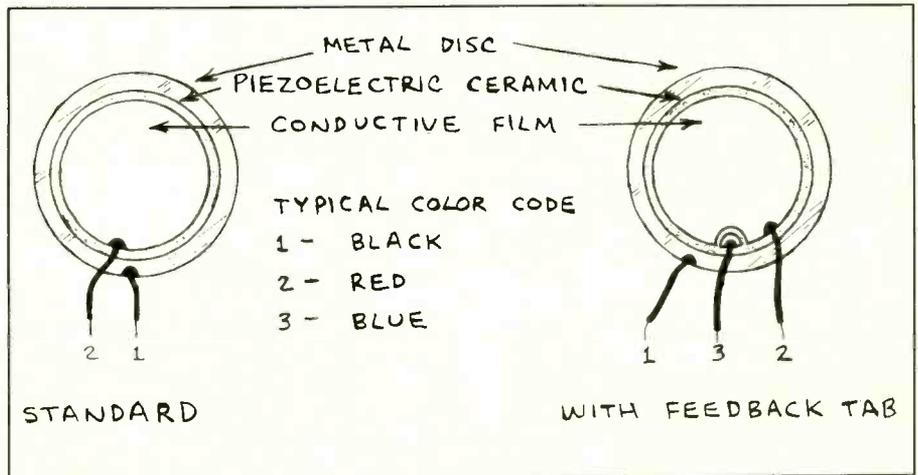


Fig. 1. Details of typical piezoelectric buzzer elements.

Figure 1 shows two typical piezoelectric sound generator elements. Most such elements have a diameter ranging from 25 to 40 mm and a preferred or resonant frequency of from 2 kHz to 7 kHz. The elements are formed by bonding a disc of piezoelectric ceramic to a larger disc of flexible metal. Electrical contact to the disc is provided through the metal disc and a conductive film applied to the opposite side of the ceramic disc. When a voltage is applied across the two electrical contacts, the diameter of the ceramic disc expands. This motion is transformed into a movement perpendicular to the plane of the disc by the spring-like action of the metal disc. The direction of motion of the disc is dependent on the polarity of the applied signal.

Note that one of the discs in Fig. 1 is equipped with a third terminal called the feedback tab. This tab is a separated portion of the metalized coating on the surface of the ceramic material. When an oscillating signal is applied across the other two terminals, a voltage appears at this tab that can be used to stabilize the frequency of the oscillator circuit. More about this later.

A circular disc will tend to vibrate at a preferred frequency called the mechanically-resonant frequency. A dramatic illustration of the resonance of a piezoelectric buzzer element can be arranged by connecting the element to a variable frequency signal generator, either a com-

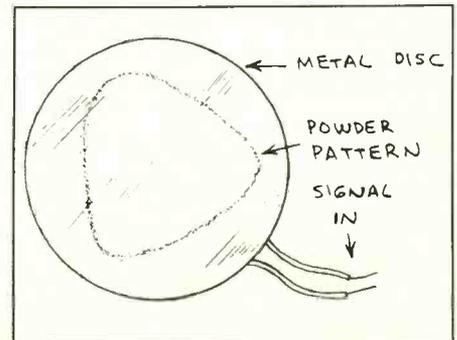


Fig. 2. Nodal pattern of an oscillating piezoelectric buzzer element.

mercial unit or one of the circuits that follows. The element is then placed with its metal side up on a soft surface (a few layers of tissue paper works well), and some light, dry powder such as sugar or an artificial sweetener is then poured on the center of the metal disc. A signal is then applied, and its frequency is swept across the audio spectrum.

The powder may vibrate slightly when the signal is applied. At a particular frequency, the powder will become considerably more agitated. Much of the powder will vibrate off the surface of the disc, leaving behind a nearly circular pattern outlining the disc's nodal region, the position of minimum vibration. Figure 2 shows a typical powder pattern that results when a resonant signal is applied to a real disc.

Knowing the nodal pattern of a piezoelectric element is important, for mechanical attachment to the disc can be made in the nodal region without impairing the sound producing abilities of the disc. Figure 3 shows the nodal mount configuration along with other methods of mounting a piezoelectric disc. Though the mounting method can greatly affect both the mechanical resonance of the disc and its sound amplitude, the mounting procedure need not be so precise as suggested by Fig. 3. For instance, a disc can be cemented to a rigid surface with a flexible sealant such as silicone adhesive. If the surface to which the disc is cemented is itself acoustically resonant, the sound level may be further amplified. This effect occurs when piezoelectric discs are cemented to the inside of musical greeting cards since the paper from which the cards are made adds to the resonant area of the disc along.

### Operating Precautions

Recall that the operation of piezoelectric devices is reversible. A dramatic demonstration of this can be made by connecting a neon glow lamp to the terminals of a piezoelectric sound generator element. When the element is struck by a hard object, the resulting piezoelectric voltage will be high enough to flash the lamp. Several hundred volts or more can be produced in this manner. Therefore, to protect the driver circuitry, it may be necessary to connect a blocking diode across a piezoelectric element that might be subjected to mechanical shock or vibration.

It is important to avoid connecting a dc source across a piezoelectric buzzer element. Apparently this may depolarize the ceramic material, thereby greatly reducing or even eliminating its piezoelectric properties.

Finally, when experimenting with piezoelectric buzzers, remember that these devices can produce exceptionally loud, shrill sounds. Sound pressure levels in excess of 100 dB are easily possible. Sound levels this high can be very uncomfortable and can produce long-lasting headaches. Therefore, it is important to use

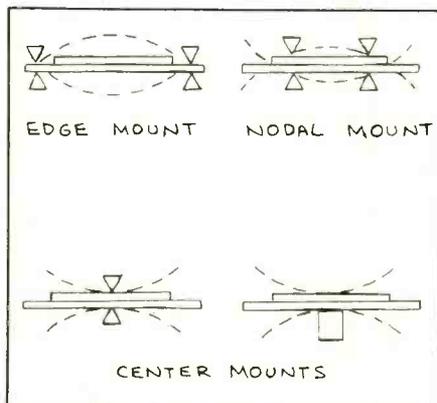


Fig. 3. Mounting arrangements for piezoelectric buzzer elements.

ear protectors when working with piezoelectric buzzers at close range. I used COM-FIT™ multi-purpose earplugs (North Consumer Products, P.O. Box 7500, Cerritos, CA 90701) while experimenting with the circuits described below. These earplugs have an attenuation of around 35 to 40 dB over the frequency range at which most piezoelectric buzzers operate (2 to 4 kHz). Before I purchased these earplugs, I stuffed wads of cotton or facial tissue in my ears. While this helped, the professional earplugs work much better.

If other people are present in or near the area in which you plan to experiment with a piezoelectric buzzer, you can muffle the sound of the buzzer somewhat by placing some modeling clay over the sound output aperture. Of course this method will not work if you are experimenting with piezoelectric elements and do-it-yourself driver circuits such as those described below.

### Buzzer Drivers

A piezoelectric buzzer consists of a self-contained piezoelectric disc element and a miniaturized oscillator-driver circuit. Many different kinds of buzzers are available, most of which can be operated by connection to a suitable power supply. Figure 4 shows how to vary the volume of a piezoelectric buzzer by means of a series-connected potentiometer. Considering the very loud sound emitted by many

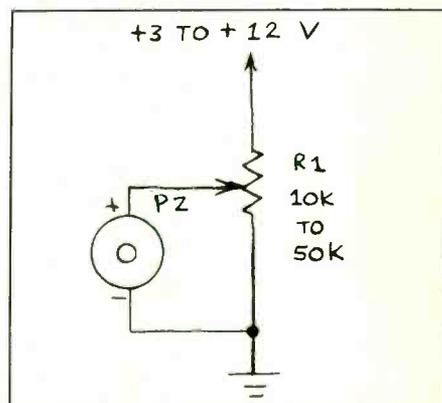


Fig. 4. Controlling the volume of a piezoelectric buzzer.

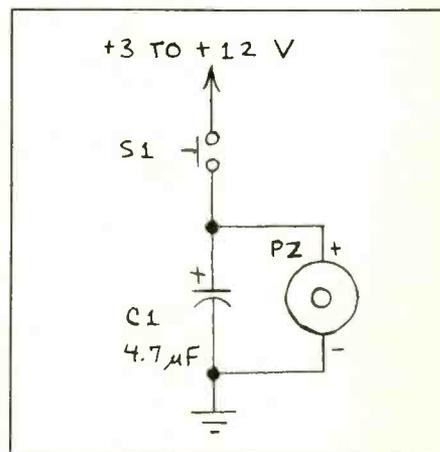


Fig. 5. Achieving a bell-like sound from a piezoelectric buzzer.

such buzzers, this simple arrangement can become very handy.

Piezoelectric buzzers that produce chime and bell-like sounds are available from Radio Shack and other sources. Alternatively, you can simulate such sounds by connecting a capacitor across a buzzer as shown in Fig. 5. When push-button *S1* is briefly pressed, the buzzer emits a tone and *C1* is instantly charged to the supply voltage. When *S1* is released, *C1* continues to power the buzzer for a brief time. During this interval, the volume of the tone from the buzzer drops markedly, thereby simulating the sound of a bell or chime. The resultant effect can be modified by trying different capacitor values.

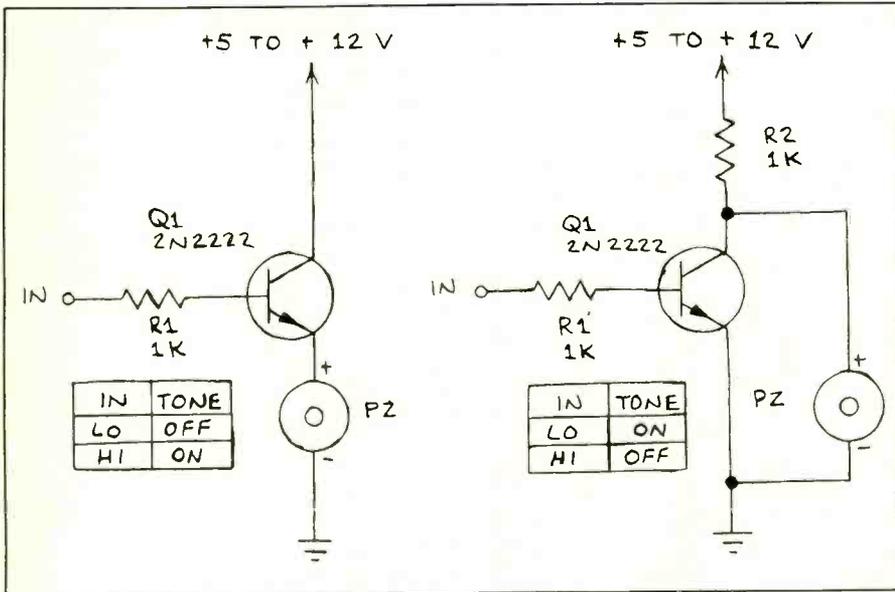


Fig. 6. Piezoelectric buzzer logic interfaces.

Piezoelectric buzzers can be easily actuated by logic circuits. Figure 6 shows two simple interfaces. One circuit preserves the logical status of the input signal; the other inverts the logical status of the input. Many different npn switching transistors can be used for *Q1*. Resistor *R1* can range in value from 1k to 10k or more. Supply voltage should not exceed the maximum allowable for the piezoelectric buzzer.

## Element Drivers

Piezoelectric buzzer elements are considerably smaller than factory-assembled buzzers that include driver circuits. For this reason it's often advantageous to use unmounted buzzer elements when space is at a premium. Fortunately, buzzer element driver circuits can be very simple, particularly since the elements can also function as capacitors and feedback elements.

## Fixed-Frequency Driver

Figure 7 shows a single-transistor oscillator designed to drive a three-terminal buzzer element at a fixed frequency. The element I used in a test version of this circuit, a No. PKM11-6A from muRata

Corporation of America (1148 Franklin Rd., SE, Marietta, GA 30067), operated at a frequency of 6772 Hz. A similar element is also available from Radio Shack (Catalog No. 273-064). Since oscillation frequency of this circuit is controlled by the dimensions of the element's feedback tab, the circuit is remarkably stable. For instance, adding or subtracting 100k to or from *R1* changed only the shape of the circuit's waveform, without affecting its frequency. Moreover, the frequency of oscillation is relatively independent of the supply voltage.

## Variable-Frequency Drivers

Variable-frequency piezoelectric element drivers may or may not use a three-element piezo device with a feedback tab. In either case, though the element emits sound across the audio spectrum, it will produce the loudest sound when driven at its acoustically resonant frequency.

Figure 8 shows a single-transistor buzzer element driver designed for variable-frequency operation. The circuit is a modified Hartley oscillator, a single-stage amplifier with positive feedback provided by a center-tapped inductor. Though the inductor can be made by wrapping magnet wire around an air or

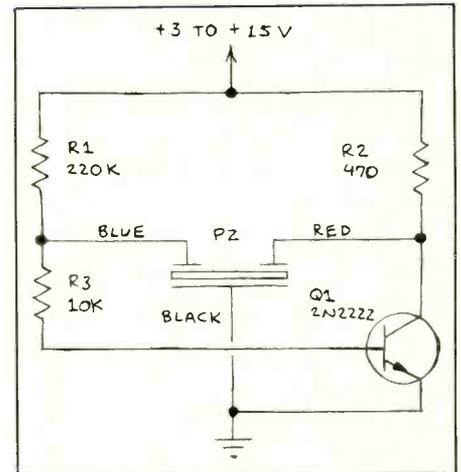


Fig. 7. Single-transistor piezoelectric buzzer element driver.

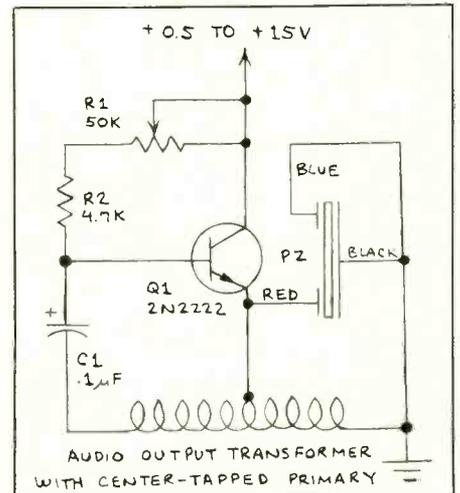


Fig. 8. Hartley oscillator piezoelectric buzzer element driver.

ferrite core, an easier solution is to employ the primary side of a center-tapped audio-output transformer such as Radio Shack's Catalog No. 273-1380. This inexpensive transformer has 1,000-ohm center-tapped primary and 8-ohm secondary windings.

Oscillation frequency of the circuit in Fig. 8 can be altered by means of *R1* (*C1* also controls the frequency). The most unique aspect of the circuit is the fact it can be powered by a 0.5-volt supply. Therefore, a single high-efficiency silicon solar cell will power the circuit. Of

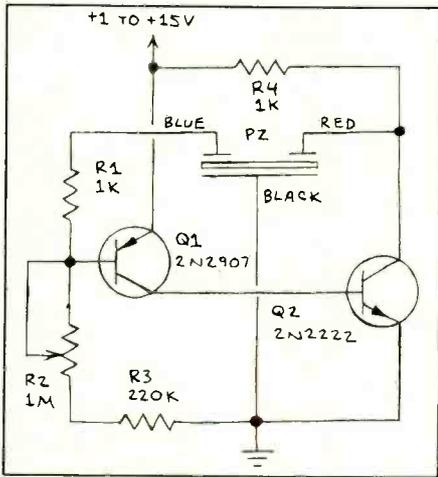


Fig. 9. Adjustable-frequency piezoelectric buzzer element driver.

course, sound level will not be as high as at higher supply voltages. Both *Q1* and the buzzer element require more than 0.5 volt for proper operation, which is supplied by the autotransformer action of *T1*. When current through the transformer is interrupted during each cycle of oscillation, a voltage is generated in the transformer's winding by the collapsing magnetic field. This voltage supplies the boost necessary to operate the circuit.

Figure 9 shows a simple two-transistor driver in which a buzzer element does double duty as a capacitor. Oscillation frequency of the circuit is controlled by *R2*. As long as polarity is preserved, many different transistors can be substituted for *Q1* and *Q2*. Note that this circuit will operate, albeit at a reduced sound level, when the supply voltage is as little as 1 volt.

Figure 10 shows a simple variable-frequency unijunction transistor driver. As in the Fig. 9 circuit, the Fig. 10 circuit's buzzer element does double duty as a timing capacitor. In operation, the buzzer element's terminals are charged through *R1*, which controls oscillation frequency, and *R2*. When the charge on the element reaches the switching threshold, the UJT switches on and discharges the voltage on the element through *R4*. The alternating charge/discharge cycle causes the buzzer element to emit an audible tone.

Figure 11 shows a single-chip CMOS variable-frequency buzzer element driver adapted from one published in a Gulton Industries' application note. Notice how the three pairs of gates in the 4049 are connected in parallel to permit higher drive current. Though the frequency of this circuit can be altered by means of *R2*, because of the feedback tab connection, the circuit will lock onto the buzzer element's resonant frequency when that point is reached in *R2*'s adjustment. For example, the breadboard version of the circuit I built operated over a range from about 200 Hz to 7 kHz. When *R2* was adjusted, the frequency changed in abrupt steps rather than gradually. When the resonant frequency of the buzzer element was reached (about 7 kHz in the test circuit), the circuit no longer responded to changes in *R2*'s value. Instead, it oscillated at the buzzer element's natural resonant frequency.

Figure 12 shows a simple variable-frequency driver designed around a 555 timer chip. This circuit doesn't use the

feedback tab of the buzzer element (in the event one is included). Therefore, the frequency of oscillation is continuously variable by means of *R1*. By increasing the value of *C1* to 0.47  $\mu$ F, the circuit will produce a metronome-like pock . . . pock . . . pock sequence.

### Experimenting with Piezoelectric Buzzers

Though piezoelectric buzzers are intended for use as miniature speakers and warning devices, they can also be used to perform a number of interesting experiments. Figure 13 shows how to demonstrate the ability of a three-terminal buzzer element to function as an audio-frequency filter. A signal generator inputs a variable-frequency waveform to the red lead of a buzzer element. An oscilloscope connected to the blue feedback lead will display the signal that propagates through the piezoelectric ceramic.

I used a No. PKM11-6AO element in the arrangement shown in Fig. 13. This element has a resonance peak at about 7 kHz. The arrangement in Fig. 13 indicated peaks at 2.3, 7.0, 18, 27 and 45 kHz.

Keep in mind that there is no electronic connection between the signal generator and the scope. The signal applied to the buzzer element generates an acoustical pressure wave that travels through the ceramic to the feedback electrode where an output voltage then appears. This is the principle behind ceramic filters, surface-acoustic wave devices and piezoelectric transformers and isolators.

If you don't have access to a signal generator and scope, you can demonstrate these principles with the help of the driver circuit in Fig. 12. Simply connect the anode lead of a LED to the buzzer element's feedback tab. Connect the cathode lead of the LED to ground. When power is applied to the circuit, the voltage appearing at the feedback tab will be adequate to forward bias the LED and cause it to glow dimly. For best results, use a high-efficiency red LED and try different oscillation frequencies.

Piezoelectric buzzers can be used in many experiments that demonstrate the principles of sound. For example, place a

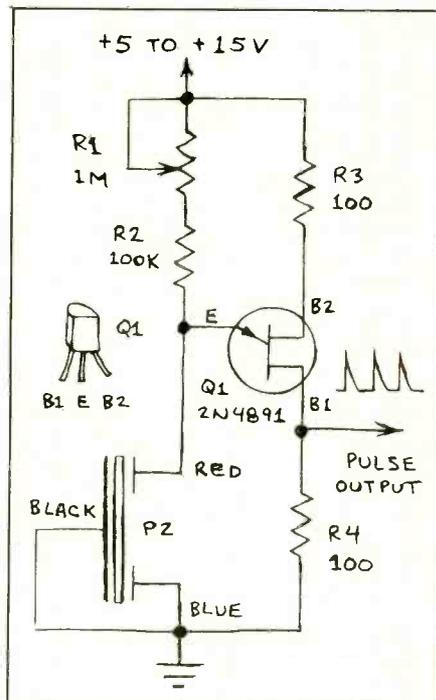


Fig. 10. Unijunction transistor piezoelectric buzzer element driver.

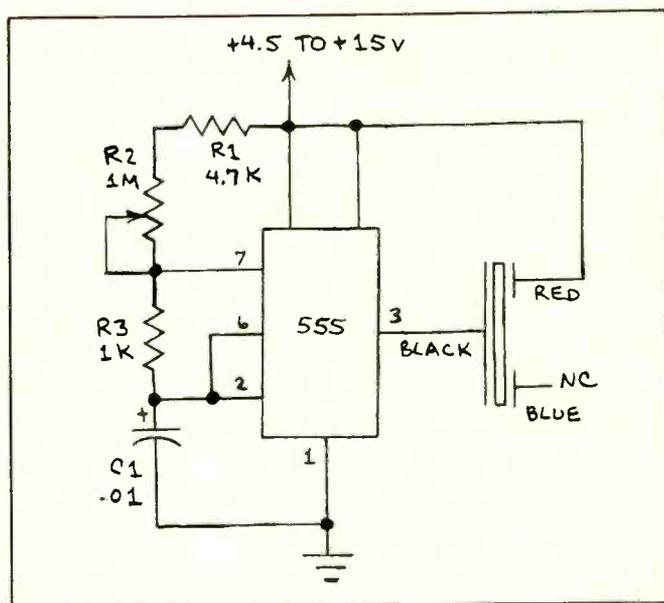
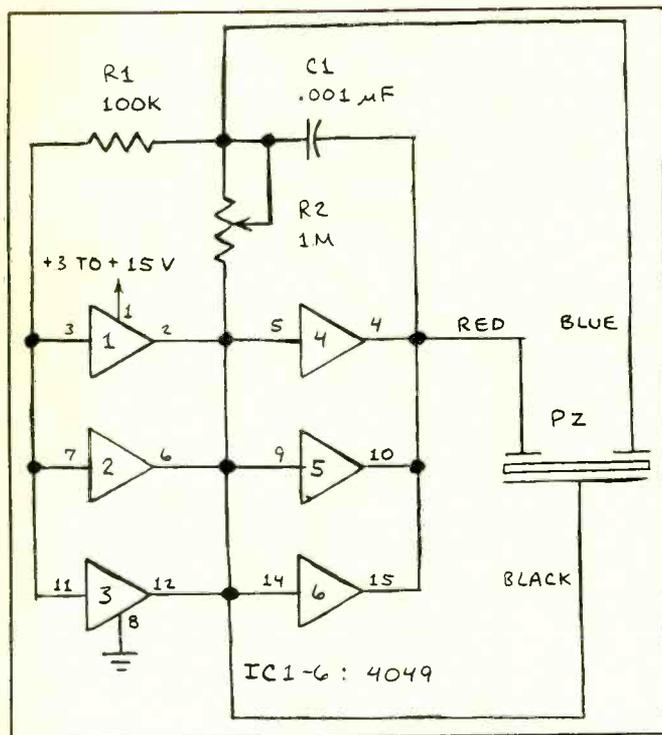


Fig. 12. Piezoelectric buzzer element driver built around 555 timer.

Fig. 11. Hex-inverter piezoelectric buzzer element driver.

buzzer somewhere in a room and then walk through different portions of the room. You will notice that the sound of the buzzer will be dramatically different in various parts of the room. Merely moving your head an inch or so may make a major difference in the volume of the sound level. This phenomenon occurs because of stable standing waves set up by the fixed-frequency tone from the buzzer. Highly localized areas of constructive and destructive interference cause the sharp variations in sound level. This experiment works best in small rooms with little or no sound-absorbing matter such as curtains, carpets and upholstered furniture.

The preceding experiment can be made much more interesting if you have access to a sound level meter. I used a Realistic sound level meter from Radio Shack to measure the sound pressure level from a fixed-frequency buzzer placed in a corner of my office. You can also use the simple (and uncalibrated) do-it-yourself sound-level meter described in the October 1985 installment of this column. The fluctuations in the sound level sometimes ex-

ceeded 20 dB when the meter was moved a small fraction of an inch. With the help of the calibrated meter, it was easy to detect sound being reflected from flat surfaces like filing cabinets and a wall.

Still another experiment I have tried is to launch a piezoelectric buzzer in a model rocket. The buzzer was activated just prior to launch and its sound recorded with a small recorder. The recording was later connected to a frequency meter and the frequency of the tone measured at intervals. The frequency of a sound source is shifted with respect to an observer if there is relative motion between the two. This is the well known Doppler shift. Knowing the shift in frequency, it was then possible to calculate the velocity of the rocket. Indeed, a teenage member of

the rocket club I then sponsored did just that for a science fair project. Incidentally, a piezoelectric buzzer forms a handy tracking beacon for a model rocket that parachutes into tall grass.

Finally, it seems prudent to again remind you that the sound from piezoelectric buzzers can sometimes be excruciatingly uncomfortable. Persons working with operating buzzers may be exposed to potentially harmful levels in excess of 100 dB. Therefore, it is very important to wear ear protectors when working with these miniature but potent sound sources. I did just that while preparing this column and am happy to report my head is clear. Some previous unprotected sessions with piezoelectric buzzers gave me headaches and left me feeling dizzy. **ME**

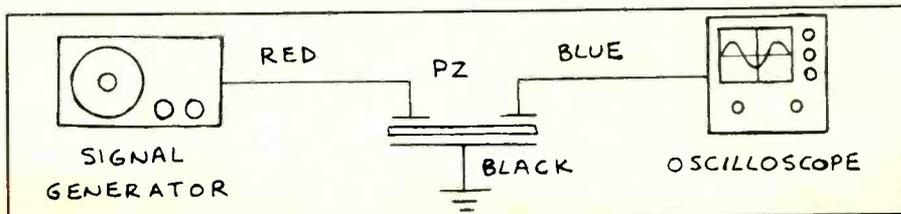


Fig. 13. Using a piezoelectric buzzer element as an audio signal filter.

**NEW** **\$395<sup>00</sup>** **128K Apple** **\$395<sup>00</sup>**  
**Compatible Computer**

The moment you buy it the Laser 128 computer is compatible with virtually all software for the Apple® II, Apple® IIe, and Apple® IIc. All the equipment is here. Plus the Laser 128 gives you the features Apple® forgot.

- 5 1/4" Disk Drive • Additional Disk Drive Interface • Serial Printer Interface
- Parallel Printer Interface • Modem Interface • RGB 80 Column Color Interface
- Mouse Interface • Hi-Res Graphics • 32K Rom • 128K RAM • Expansion Slot for Apple® Peripheral cards • Battery Pack Interface • Numeric Keypad
- Limited time only • Programable Function keys • Carrying Handle

**\* Free Magic Window Iie Professional Word processor (\$149.95 Value)** \*with Laser 128 Purchase



Comparably priced  
 Apple® Iie  
 system  
**\$1500.00**

Comparably priced  
 Commodore® 128  
 system  
**\$850.00**

- Home
- Business
- Students
- 90 Day Warranty
- 15 Day Free Trial

This is the best computer buy in the U.S.A. You get the complete Laser 128 computer with all the features shown. Plus for a limited time only, you get the Professional Magic Window Iie Wordprocessor all for only \$395.00. We have tested this machine with over 500 software titles from our comprehensive catalog and the Laser 128 runs them all perfectly. (it even runs Appleworks®) This is a must buy for new and old computer buyers. List \$648.95. **Sale \$395.00.**

	List	Sale	Accessories	List	Sale
Centronics cable (for Centronics Printer)	\$ 29.95	\$ 19.95	2nd Disk Drive	\$299.95	\$129.95
Serial Cable (for Modem hookup)	\$ 34.95	\$ 19.95	Professional Analog Joystick	\$ 39.95	\$ 19.95
9" 80 Column Hi-Res Green Monitor	\$199.00	\$ 59.95	RGB cable (RGB Monitor hookup)	\$ 24.95	\$ 19.95

Apple and Commodore are registered trademarks of Apple Computer Inc. and Commodore Business Machines Inc. respectively

Add \$10.00 for shipping, handling, and insurance. Illinois residents please add 6 1/4 % sales tax. Add 20.00 for CANADA, PUERTO RICO, HAWAII, ALASKA, APO-FPO orders. All orders must be in U.S. Dollars. WE DO NOT EXPORT TO OTHER COUNTRIES EXCEPT CANADA. Enclose Cashier Check, Money Order or Personal Check. Allow 14 days for delivery, 2 to 7 days for phone orders, 1 day express mail. Prices & Availability subject to change without notice.  
**VISA — MASTER CARD — C.O.D.** C.O.D. on phone orders only.

**Computer Direct**  
 We Love Our Customers  
 22292 N. Pepper Rd., Barrington, Illinois 60010  
**312/382-5244 to order**

## Using Double-Layer Capacitors; Computer Power Interface, Underground Radio Technology

By Don Lancaster

**How Big** is a one-Farad capacitor? Would you believe less than a cubic inch? Conventional wisdom and poorly done cartoons notwithstanding, a new capacitor technology is now available that crams incredible capacitance values into very small volumes. As Fig. 1 shows, these are called double-layer capacitors. They are both reasonably priced and available from distributor stock. For instance, a 1.0-Farad, 5-volt *NEC* # FZ0H105Z is available from *Mouser Electronics* for \$4.59 each (part 551-1.0Z05).

Being a brand new and "hacker friendly" part, there's lots of exciting new possibilities here. But there are also some definite use limits and restrictions.

One major use for double-layer capacitors is as power backup for CMOS memory chips. The capacitor can fake memory nonvolatility during a short power outage. Unlike most batteries, these devices can be cycled indefinitely, have at least a 10-year life, can easily be soldered in place, are not polarized, usually cannot leak or explode, and readily indicate their charge.

Back to the basics. A traditional capacitor consists of two conductors separated by an insulator. When a current is routed through a capacitor, a charge will build up and will be stored. The amount of the charge depends on the current and how long the current is applied.

The charge also depends on the surface area of the conductors, the spacing between conductors, and a property of the insulator material known as the dielectric constant.

Capacitors have many electronic uses, ranging from storing dc in power supplies; coupling/bypassing ac signals; resonating coils for frequency selection; and for integrating precision waveforms.

The storage size of a capacitor is measured in Farads. A 1-Farad charge will supply a current of 1 ampere for 1 second. Most capacitors have traditionally been much smaller than this, and are measured in microfarads ( $\mu\text{F}$ ) or picofarads (pF) instead of Farads.

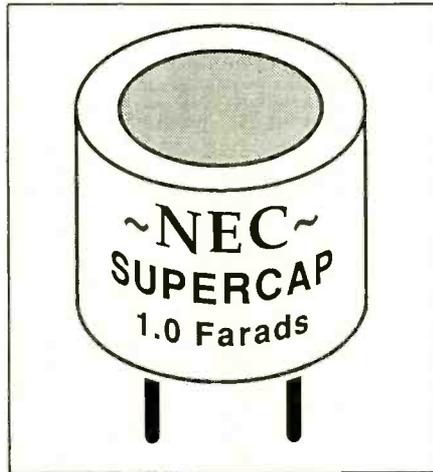


Fig. 1. A 1.0-Farad capacitor!

For instance, if you hold two fingernails one fingernail apart, you will have created the equivalent of a 1-pF capacitor. Among other difficulties, there are not nearly enough people in the world to build a 1-F capacitor by this method.

Some ways to get more capacitance are to increase the plate area, to decrease the spacing between the plates, and to raise the dielectric constant. All of these techniques have been used in combination to create the various capacitor families available today.

For example, ceramic capacitors use special insulators with a dielectric constant of 8000 or more. Electrolytic capacitors build up an extremely thin insulating oxide film. They also increase the conductor surface area by etching. Sometimes a double etch is used where big pits are first added to the original surface, and when this is done, small pits are added to the big pits.

But the double-layer capacitor goes far beyond what traditional capacitors are able to do. It uses a fundamentally different principle, first discovered by Helmholtz over a century ago. It turns out that if you have a boundary between a solid and a liquid, a double layer of charge builds up at the surface between the two. To build a useful double-layer capacitor, you use a solid plate, a liquid electrolyte and a second solid plate. To prevent the two solid plates from touching, you place

a porous, insulating separator between the two. The separator allows ions in the electrolyte to move back and forth as charge is accumulated, but prevents any direct short-circuit between plates.

The solid plates used for today's double-layer capacitors are made from activated charcoal which has an incredible surface area, since it is made up of countless tiny particles. A gram of activated charcoal may have a surface area equal to one-quarter of a football field! And therein lies the secret to extreme capacitance values in a very small package.

In exchange for the extreme capacity in a very small space, there are some definite tradeoffs. The breakdown voltage of the electrolyte used in today's double-layer capacitors is only 1.2 volts. To get a useful +5-volt dc working voltage, six capacitors are placed in series inside the package.

Instead of directly building a 1-F capacitor, there are really 36 farads of capacitance in the package, since six series connected capacitors each yield a 1-F series equivalent capacitance.

So, you *must* be careful to never exceed the recommended working voltage of a double-layer capacitor.

In addition, these are not precision components, since activated charcoal itself is not a very precise material. Tolerances are in the -20% to +80% range. Also, charge is inherently an "undense" way of storing energy, compared to chemical conversions. Large single-layer capacitors are simply not in the same energy storage league as batteries, and I don't think you will ever see the day when you start a lawnmower with a double-layer capacitor.

So, while double-layer capacitors are incredibly better than regular capacitors for storing bunches of charge in a small volume, they are not nearly as good as a battery when mucho dense energy storage is required.

Finally, charcoal is not a very good conductor, and conductive elastomers are also used in the construction that are only moderately conductive. Thus, a double-layer capacitor is *not* a low-impedance device and can *not* be rapidly charged or discharged.

One interesting side effect here is that the inherently limited charge and discharge rates of a double-layer capacitor give automatic short-circuit protection. Some batteries, especially Ni-Cds, instead tend to get downright violent when you short them.

Several manufacturing options are available that trade off maximum possible charge and discharge currents against cost and size. The smallest and cheapest versions are intended for long-time, low-current memory backup uses.

Let me know what interesting uses you can come up with for this exciting, yet imperfect, new hacker component.

### OK. How did you do it?

If there's one thing I can't resist, it's a good hack, especially if it lies well beyond the far side of "disgustingly elegant." Check the capacitor lettering in Fig. 1. Note that we not only have isometric lettering, but the lettering is also correctly wrapped around a cylinder! This was quickly and easily "drawn" with the stock and standard Apple Writer word processor, as were *all* parts of *all* figures in this column. Oh, yes, I did add a short little custom text routing of my own that I'll be happy to share with you. The same routine also lets you set text in a helix or an inwardly closing spiral.

Write or call for you free copy.

### How can I Control AC Power With a Personal Computer?

There are two problems involved in controlling high-power ac loads with a personal computer or microprocessor parallel port. The first is that the weak port signals must somehow be *amplified* to make them "strong enough" to control a high power load. The second hassle is that there is a very deadly shock hazard involved with ac power control, which means that some sort of *safety isolation* is an absolute must.

While you could use a relay driver IC and a relay, the usual way to handle 110-volt ac high-power interface today is to connect a phototriac optoisolator to a triac power control device. Figure 2 shows details.

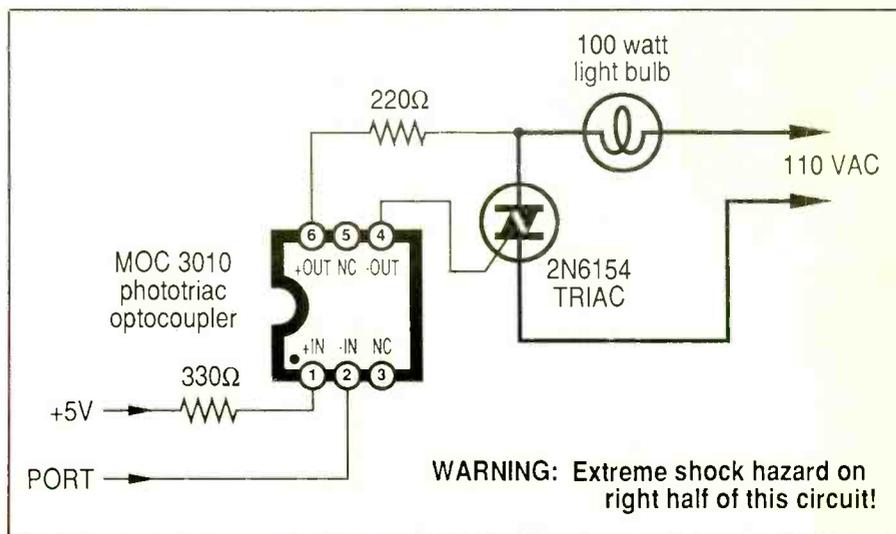


Fig. 2. A 110-volt ac power control interface for a personal computer.

The triac optoisolator consists of a light-emitting diode that drives a photo-sensitive ac power control device called a phototriac. When the LED lights, the phototriac turns and activates the main high-power triac to switch the load.

Because only a light beam connects the input to the output, you get total safety isolation. The "amplification" you need comes from both the internal phototriac and the main power triac.

There are some important details you have to be aware of when you use this circuit. First and foremost, note that there is a deadly shock hazard anywhere to the right of the triac optoisolator; so use extreme caution when working on *any* circuit of this type.

The power triac will switch on or off most any ac load, such as lamps, motors, heaters, or whatever. A minimum load must always be provided for proper operation, say 7 watts or so. The maximum load depends on the triac and the size of the heat sink you use.

One classic handbook for triac power control is the *SCR Manual* from *General Electric*. My issue is sort of dated, so it may have a new name and a new price by now. Cost should be around \$5.

You also *must* use a phototriac optoisolator, rated at least 200 volts for 110-volt ac operation, or 400 volts for

220-volt ac operation. Note that the other types of optocouplers will instantly self-destruct if you try to use them for ac power control. The *Motorola* MOC 3010 is often a good choice and costs slightly over a dollar.

I have also shown the inputs to this circuit connected "backwards" from some other circuits you may have seen. There is a very important reason for this. Most parallel ports on microprocessor systems are much better at sinking current to ground than they are at sourcing current from a positive voltage.

With this circuit, the output port either sinks current to ground, activating the phototriac optoisolator and powering the load, or doing nothing and not delivering power to the load. Connected "backwards," the optoisolator is much better matched to the parallel computer port and will work much more reliably.

One little gotcha with this "backwards" connection: Your port will now be active low, so a zero at the port will *activate* the load. Your software must, of course, recognize this fact, and write zeros to the port locations when you want to power the load.

Note that a machine-language command of EOR #\$FF will automatically convert all of the ones in a word to zeros and vice versa. From BASIC, an XX =

# HARDWARE HACKER...

(255 - XX) will also convert all ones in a word to zeros or vice versa. Details vary with the application, of course.

Typical cost of one channel of power control should be under \$3, unless you are using a very large triac.

More info on microcomputer power interface appears in my *Micro Cookbook*, Volume II (SAMS #21829).

## Is There an Easier Way?

Well, if you want to pay a little more, you can cut the parts count to one. Figure 3 shows how to use a Crydom D2W202F solid-state relay by *International Rectifier* and do all of your power control with a single part. *Newark Electronics* sells them for \$7.95 in singles as stock #81F4904.

The circuit is still the same as before, since the resistors, triac and optocoupler are all inside the package. Also as before, the + input goes to the microcomputer's +5-volt supply line, and the - pin goes to the port output. A zero turns on the load, a one turns it off.

The device is good for 2 amperes and might be pushed a little further with some sort of clip-on heat sink. Around 220 watts of light bulbs, or possibly a quarter-horsepower motor can be controlled. Note that a severe shock hazard exists on the power side of this circuit.

## What About Proportional Control?

If you have a proportional control interface, you not only can turn on/off motors, heaters, and lamps, but you can control their brightness, temperature, or speed as well.

It turns out that the Fig. 2 and 3 circuits can also be used for proportional control, but the software gets more complicated. And you have to be aware of exactly what you are up to.

First, the load you use *must* respond to voltage in a proportional manner. Incandescent lamps will, but fluorescent lamps will not. Most heaters or soldering irons will respond proportionally and present no problems.

Universal type motors (those with brushes) will alter speed with changing

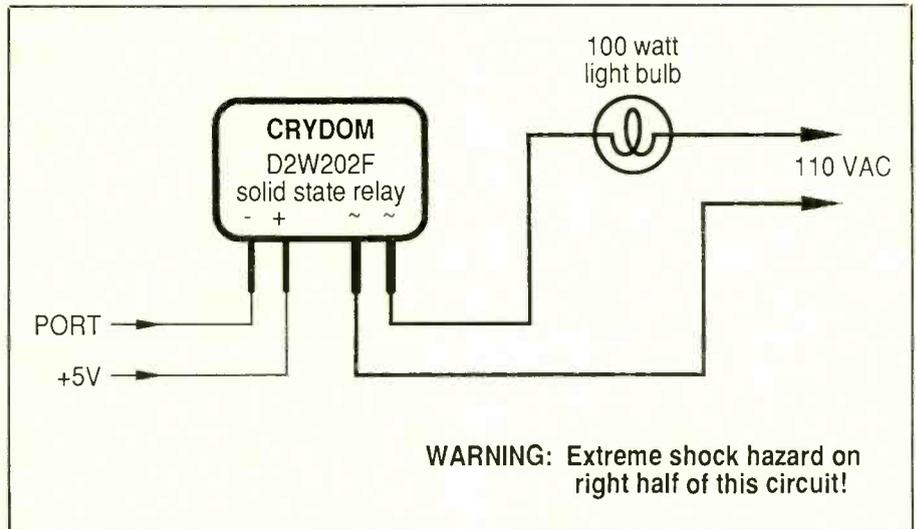


Fig. 3. A simpler but more costly power interface option.

voltage, but the more common ac induction motor can destroy itself if you try voltage control. Even when you control the speed of a universal motor by varying its voltage, you may get very limited torque. There are fancier techniques involving feedback that can be used to get around this problem.

So, your initial experiments at proportional power control are best done with incandescent lamps, heaters, etc.

The trick to proportional power control is to deliver a turn-on pulse that is precisely delayed from each ac-line half cycle. Figure 4 shows details.

If turn-on occurs very early in each ac half-cycle, nearly all the power will appear across the load. If turn-on takes place in mid-cycle, around half of the power gets to the load. Should the turn-on occur very late in the cycle, only a small amount of power gets to the load. Finally, with no turn-on pulse at all, the load gets no power and stays off.

Your computer must somehow sense the beginning of each half line cycle. This can be done with a line-derived interrupt signal or by routing something similar to an input port. The software inside the computer or microcontroller then will

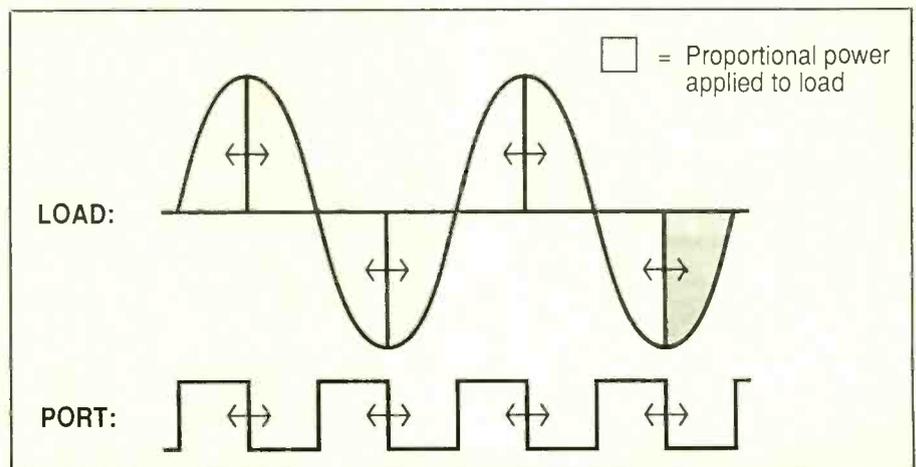


Fig. 4. Proportional power control requires precise timing.

## NAMES AND NUMBERS

**General Electric**  
Electronics Park Bldg. 7  
Syracuse, NY 13221  
(800) 626-2001

**Motorola Semiconductor**  
Box 20912  
Phoenix, AZ 85036  
(602) 244-6900

**Newark Electronics**  
228 East Lake Street  
Chicago, IL 60640  
(312) 941-7200

**International Rectifier**  
1521 E. Grand Avenue  
El Segundo, CA 90245  
(213) 322-4987

**Mouser Electronics**  
Box 9003  
Lakeside, CA 92040  
(619) 449-2222

**Howard W. SAMS**  
4300 West 62 Street  
Indianapolis, IN 46206  
(800) 428-SAMS

**Natl. Speleological Society**  
Cave Avenue  
Huntsville, AL 35810  
(205) 852-1300

**NEC Electronics**  
401 Ellis Street  
Mountain View, CA 94043  
(415) 960-6000

**Speleonics**  
Box 5283  
Bloomington, IN 47402  
(812) 335-7305

automatically convert a speed, brightness, or temperature value to the proper turn-on delay.

The timing is such that machine-language code *must* be used, particularly if you are controlling more than a few loads with the same computer. The precision and linearity of your outputs can be greatly improved by using some sort of feedback. This, of course, ups your system complexity.

You should be able to use a computer the size of an Apple IIe to control something like 32 theater lights to 32 brightness levels. This would make a very interesting programming project.

A totally different way to handle proportional control is with those *BSR* power modules sold by *Radio Shack* and others. These are fairly easy to interface to most computers, besides offering remote-control options.

### Is There any more Information on Underground Radio Technology?

I've found another most interesting publication on underground technology. This beauty covers such things as underground radio communications and position measurement, ultrasonic and laser ranging, self-climbing ladders and

even automatic spare-lamp switchers. All hands-on and real-world with full schematics, parts lists, the whole bit.

It's called *Speleonics* and is published quarterly (four times a year).

Included in each issue are a dozen how-to articles and a subscriber list of others interested in similar underground tools, concepts, and techniques. Price is — better sit down for this one — a dollar per issue or \$4 per year!

Should you want information on caving and speleology in general, you can instead contact the *National Speleological Society* and they can put you in touch with individual local cavers and an NSS grotto or two in your area. **ME**


### NEED HELP?

Phone or write your **Hardware Hacker** questions directly to:

**Don Lancaster**  
**Synergetics**  
Box 809  
Thatcher, AZ 85552  
(602) 428-4073

**SAVE MONEY!**

**CALL  
FREE**

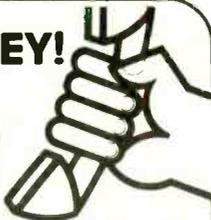

**1-800-237-3063**

7 A.M. TO 5 P.M. MON-THURS  
(IN CONTINENTAL U.S. EXCEPT FL)

**FOR ALL YOUR  
CRYSTAL  
NEEDS!**

General Communication  
Industry • Marine VHF  
Amateur • Scanners  
CB Standard & Special  
Microprocessor

**GET YOUR FREE  
1986 CATALOG**



SINCE  
1965



Call or write:  
**JAN CRYSTALS**  
P.O. Box 06017  
Fort Myers, FL  
33906-6017  
**(813) 936-2397**

### Get into Telecommunications BE AN INSTALLATION AND REPAIR SPECIALIST

TRAIN AT HOME IN SPARE TIME... NO PREVIOUS EXPERIENCE NEEDED. Skilled telecommunication installers and repairers work on all kinds of telephone, telegraph, radio, TV and satellite systems. And in the near future many more will be needed to maintain systems responsible for electronic mail, computer tie-ins and remote utility reading.

TOP PAY...INTERESTING WORK. Experienced "telecom" installers and repairers make good money, and since most belong to a union, they enjoy great benefits as well.

HOME-STUDY COURSE SHOWS YOU WHAT TO DO, HOW TO DO IT. Now you can learn the basics of installation and repair at home in spare time. Hands-on lessons cover everything from installing systems and routing messages to troubleshooting and repairs.

No need to quit job or school. Easy home-study course shows you step by step...lets you learn by doing with the tools in your hands. Program includes manuals and lessons, plus tool kit to use while training and on the job. Get free facts. No salesman will visit you. **Mail Coupon Today.**



**School of Telecommunications** #3206  
925 Oak Street, Dept. DL086  
Scranton, PA 18508

Rush me free facts on how I can learn telecommunications installation and repair at home in spare time.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Apt. \_\_\_\_\_  
City/State/Zip \_\_\_\_\_

## First Impressions: Epson and AMQ Compatibles, Personal Publisher

By Eric Grevstad

I don't think I've reviewed a plain, unabashed PC clone since the NCR PC4 in 1984, back when IBM compatibility was still uncommon and the reviewer's toolkit consisted of 1-2-3 and Flight Simulator. Nowadays that acid-test twosome doesn't scare anyone. You can buy PC-compatible BIOS (basic input/output system) chips on any street corner in New York—well, maybe not in the low-tech neighborhoods on the West Side, but you know what I mean—and the industry's moved on to 80286 processors, micro-floppy drives, and Enhanced Graphics Adapters.


But it's good to get back to basics, to see the old 8088 CPU percolating along at its old 4.77-MHz clock rate. This month's micros are from two companies (a global titan and a near unknown) in two categories (desktop and transportable), but they have one thing in common. Each costs a third as much as the IBM and Compaq machines I would have compared them to in 1984.

On the other hand, the old clock can seem kind of slow for today's newest applications. Did someone say "desktop publishing"? Read on, and let's get on with the reviews . . .
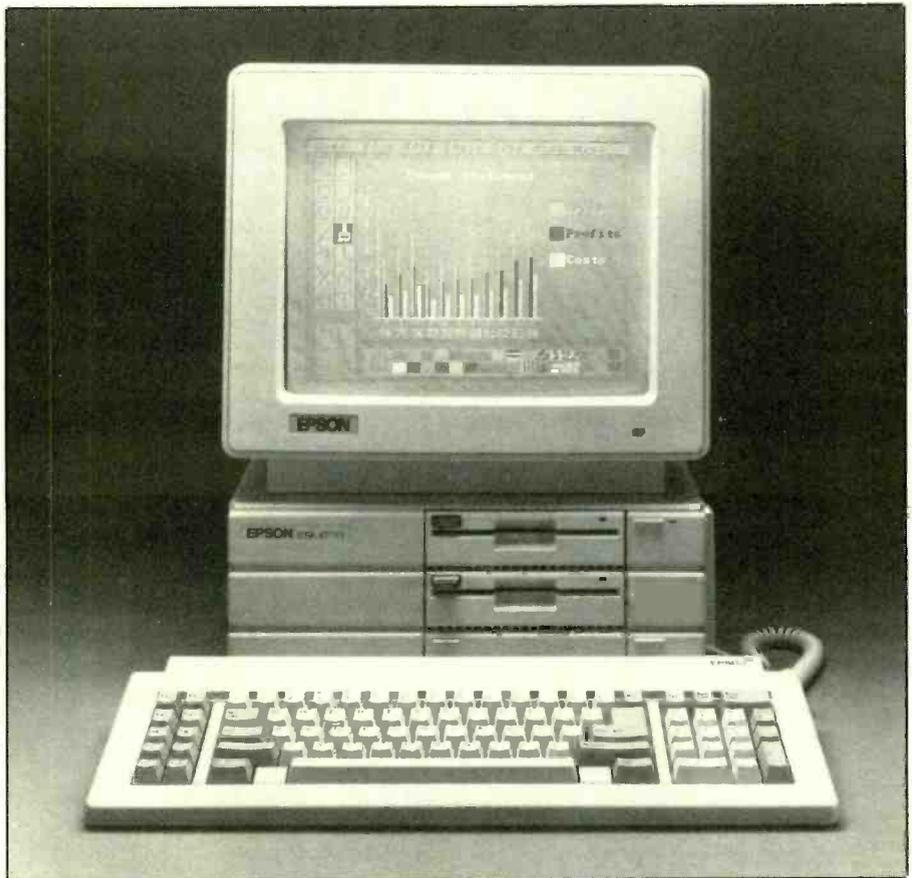
### Epson's Compact Cube

Setting aside the mail-order specials, there are three brand-name entries in the low-cost desktop race: the Tandy 1000 (U.S.), Leading Edge D (Korea), and Epson's Equity I (Japan). The Epson is the most conventional clone of the three. It's the only one that makes novices buy and install a video board—but has some appealing features. For one thing, it's only \$995 with 256K and one disk drive (\$1,295 with two drives, \$1,895 with one floppy and a 20-megabyte hard disk).

The Equity system unit is a trim 15 inches square by six inches high; there are too many ugly lines and cosmetic plastic latches for my taste, but at least it doesn't hog your desk. Its space efficiency is even more impressive when you pop the top: the motherboard fits under the drives, with nothing but blank metal beneath the



Epson's Equity I: compact, compatible, nothing to write home about.

three full-length expansion slots (they're on a small platform plugged into a motherboard bus, in an example of the Epson's modular architecture).

You'll have only two slots free after installing a video card, but a piggyback RAM card (\$169) lets you upgrade to 512K without using one. (Going to 640K requires a slot, but at least parallel and serial ports are standard.) Epson's monochrome text card (\$129) looks homely even by text-card standards, bristling with capacitors by way of meeting radio interference rules and producing faintly wobbly characters on the 12-inch green monitor (\$149), but the Equity accepted all my non-Epson boards: my Quadboard to reach 640K, my Tecmar graphics adapter for video games, and my All Sales Final Mail-Order Mostly Hercules-Compatible Graphics Card,

which lit constellations of pixels behind Microsoft Word just as it does in my Tandy 1200.

There are several convenient touches, from a power socket for your monitor to DIP switches mounted up front instead of under the hood—little doors conceal the switches, reset button, power switch, and keyboard connector. The keyboard is first-class, once PC owners adapt to its AT-style layout (giant shift, Ctrl, and Enter keys, but the backslash where backspace should be and no separate Enter key for the keypad).

While the Epson ran all the software I tried, it's worth checking out the supplied GW-BASIC and MS-DOS 2.11 disks. Beginners will appreciate several menu routines that make tricky FORMAT or MODE syntax or Epson printer setup as easy as pressing the arrow and

Enter keys; experts will like Executive Systems' XTREE, a helpful directory sorter for running programs or flagging groups of files for DOS operations.

Once you add memory, a monitor, and a video card, the Equity I isn't the cheapest compatible around; once you've grappled off its top cover and sprung loose its flimsy back panel, you'll think it's not the sturdiest, either. It works well, but I'd say the Tandy 1000 offers superior economy and the Leading Edge better standard equipment.

### *Watch Out, Compaq*

Compaq could get away with high prices when both IBM compatibility and suitcase transportability were scarce, but they'd better stop congratulating themselves on making the Fortune 500 and have a sale. The papers are full of stories about business buyers' new willingness to try bargain brands, and AMQ Computer Corp. is gunning for Compaq with a "Made in U.S.A." flag in one hand and a one-year warranty in the other.

The AMQ line is built around an 8088-based luggable with 9-inch monochrome display, parallel and serial ports, a keyboard that latches (with some twiddling) onto the system to form the bottom of the suitcase, and sliding doors to conceal the cooling fan and power switch.

That's nothing you won't find in the original 1983 Compaq, but check the extras—a cubbyhole to stash the power cord, an RGB port for an external monitor, and 704K on the motherboard (Lotus 1-2-3 Release 1A can use the extra 64K, though I don't know what else can). Then check the size—15 by 18 by 8.5 inches, like the new Compaq Portable II instead of the bulkier Compaq Portable. Then check the price—\$1,395 with two 360K floppy disks, \$1,995 with a 10 MB hard disk, \$2,195 with 20 MB.

The 24-pound, two-disk AMQ I tested was noticeably easier to haul around than a standard Compaq, ran all the software I gave it, and even carried four or five disks in its little slot beside the screen. There were minor complaints: I didn't mind the function keys horizontally

above the regular keys, but wished AMQ hadn't left the backslash between the shift and Z keys (the Alt key was a trifle sticky, too).

The keyboard was balky about re-treating into its lair when I packed up. The standard text/graphics display isn't too sharp (AMQ promises Hercules-compatible monochrome graphics as a factory-installed option). It's a bad choice for first-time buyers—no DOS is supplied, and the manual is dreadful.


Still, the affordable AMQ impressed me enough to outshine the top-of-the-line AT 286: the same machine, with one of its four expansion slots taken by a 20 MB hard-disk controller and another (really two) stuffed with Phoenix Computer Products' Pfaster286 board. This mighty kludge packs an 8-MHz 80286 chip, two megabytes of RAM (for a 2.7-MB system total), and its own AT-compatible BIOS. Like the turbo boards I tested last February (p. 84), it gives you, in effect, two computers controlled by a keyboard toggle—type PFAST to activate the 80286, PSLOW to return to the PC side.

At \$3,995, the AT 286 definitely undercuts Compaq's 80286 Portable II, and its colossal memory allows great gimmicks like a one-megabyte RAM drive with caching to cut down on disk access. But for all its speed it didn't strike me as a fully integrated AT compatible (there's a lot of rigamarole with different startup batch files for each processor; Word 3.0 wouldn't run on the 80286, the the Norton Utilities rated the slow side at 0.8 times PC performance).

Besides I doubt that many people need both hotel-room computing and blazing performance. Given a traveling job and enough cash to buy an 80286 Compaq, I'd buy an AMQ—but I'd buy one of the 8088 models, and use the money left over to buy a desktop AT clone for the office.
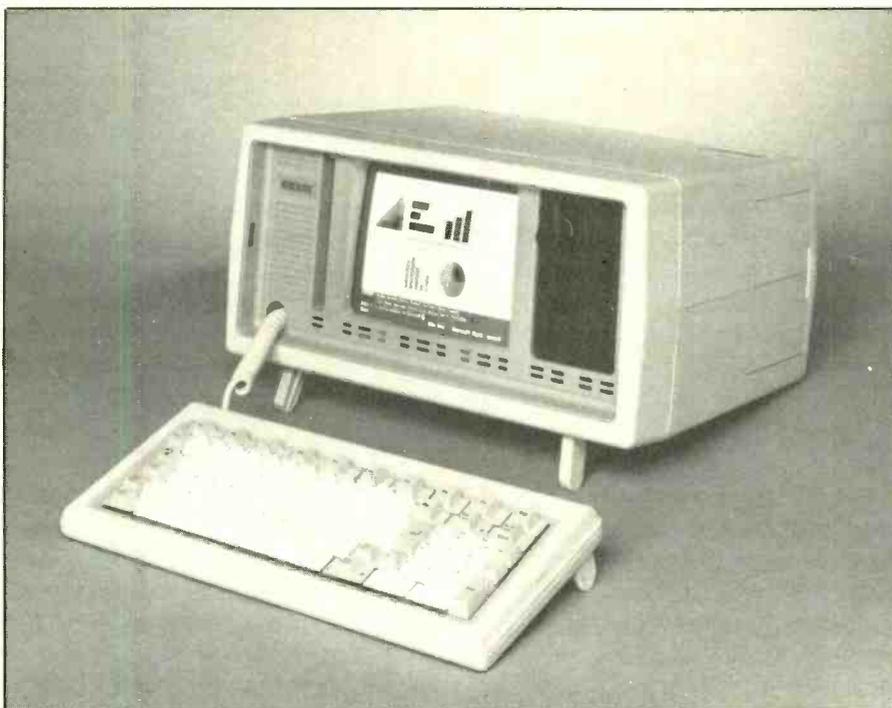
### *Creeping Into Journalism*

Desktop publishing may be the current catch phrase, but it's not the next Visi-Calc. For many users, it can actually decrease productivity—you'll spend hours lining up columns and rotating graphics,



*AMQ goes head to head with Compaq.*

## Names and Addresses

**AMQ Computer**  
1901 So. Bascomb Ave.  
Suite 340  
Campbell, CA 95008  
408-559-0781

**Epson America Inc.**  
2780 Lomita Blvd.  
Torrance, CA 90505  
213-539-9140

**T/Maker Graphics**  
2115 Landings Dr.  
Mountain View, CA 94043  
415-962-0195

when a quick, simple memo might suffice. But if you truly need to put out announcements or newsletters, there's now a reasonably priced package for the PC that's a fine illustration of the concept's pros and cons. T/Maker's ClickArt Personal Publisher (\$185) mixes text and clip art so nicely you'll play with it for days. It's also such a strain on the 8088—despite requiring 512K and preferably a hard disk—that you'll miss your deadline while waiting for word wrap.

Personal Publisher can't handle a long document or annual report, but for one- or two-page productions it's a terrific implementation of Macintosh concepts (including working without a mouse better than any other Mac imitation I've seen.) Each page is composed of layered "transparencies" for text and graphics, respectively, each with a cut-and-paste clipboard; you'll have to save your text to disk while loading and picking clip art, but MacPaint-style icons make choosing, moving, and erasing art and drawing lines and boxes easy.

Text comes in one to three columns and a number of familiar Macintosh fonts, though type size choices are limited. Putting ingredients together, with "PictureWrap" to arrange text around graphics and zoom-out previews to offset the IBM color card's quarter-page screen display (the sharper Hercules card shows half a page), is remarkable "Gee, it really works" fun.


## The PC Papers Paper

### Mayor Battles Aliens

CITY HALL -- Mayor Jeanne McKay's first weeks in office were preoccupied with the invasion of large lizard creatures from space, but the Democratic party regular told reporters she anticipates a return to debate on town water and zoning issues as soon as the aliens agree to vacate the Andrews property west of Route 116.

"Basically, the Council and I agree that the attack of the Sauroid storm troopers takes precedence over the Middle School bond issue and other matters raised in my campaign," the mayor said at a press conference yesterday. "The governor and United Nations have been very attentive to our reports on the lizard situation, and we're still optimistic that a peaceful settlement can be reached while the majority of the city's population remains."

### Back to School

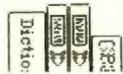

Is your son or daughter ready to hit

## GOOD NEWS AND BAD NEWS


strategies parents can use to make the end of summer vacation less of a traumatic time or experience for your youngsters as this term begins.

"Children are more willing to leave for classes when they know a warm, supportive home environment will

be waiting when they return," Kelly points out. "Selling the house and moving to a different neighborhood during school hours is an extremely negative activity and an unpleasant surprise when the child comes home. If you must suddenly leave town in the middle of a school day, at least leave a note or forwarding address."
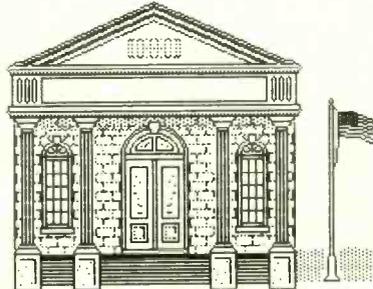
### Sample Printout Scandal

KEENE, NH -- Eric Grevstad, contributing editor for *Modern Electronics* magazine, confessed today to using graphic images having no relation to his text in the preparation of a sample ClickArt Personal



*It's not the New York Times, but ClickArt Personal Publisher brings newsletter layout to the dot-matrix owner.*

It also makes Microsoft's sluggish Windows look like a rocket ship. On 8088 systems, Personal Publisher's word processor can take half a minute to close up a line of text after deleting a few words; changing type size or column layout, you'll stare at the "please wait" wristwatch icon for so long it should be a sundial. After giving the print command, go see a movie; printing a "final-quality" page on an Epson LQ-1000 took half an hour. (The product was late coming to

market and the laser driver options, \$150 each for HP's LaserJet and Apple's LaserWriter, didn't come in time for review; there'll also be various font and picture disks for \$49.95.)

Personal Publisher needs a bit more development and an AT or faster machine before it challenges Mac publishing products, but it has gorgeous potential for the future. Usually I argue that the 8088 is just fine, but I may join the crowd awaiting the 80386 after all. **ME**

# COMPUTING POWER

## FROM FLOPPY DISK SERVICES

XT-turbo systems




PRICES AND SPECS SUBJECT TO CHANGE WITHOUT NOTICE.

Floppy Disk Services has been supplying storage systems to the hobby and professional computer community for 7 years now. You can buy with confidence from a supplier that is in for the long haul. Whether you need advice or technical help, our staff is here to serve you.

The 'Service' in Floppy Disk Services stands for the confidence you'll have in dealing with us. We do not make you wait when a problem comes up. We will be there to help, and more importantly support and guide you. In the unlikely event we cannot answer your questions, a staff member will return a call to you in a timely and professional manner with the answer.

Warranty is a term that sometimes is taken for granted. At Floppy Disk Services, we support one of the strongest warranty policies in the business. Our policy is to replace any equipment found to be defective in any way during the warranty period. It's as simple as that! No waiting for the merchandise to be sent back to the factory. If we find a problem, (other than abuse), we simply ship a new unit back to you.

The XT-clone system pictured above is our Super System VII XT clone. It contains a turbo processor, a 20mb hard disk formatted RLL to 31mb, 640K RAM, two 360K floppies, 1 AT 1.2 mb drive, mono amber monitor, par port, ser port, clock and AT type keyboard! You might expect to pay thousands for this system, but Floppy Disk Services, inc. will supply it ready to run with a 1 year warranty. Call for latest quotes on your custom system needs...

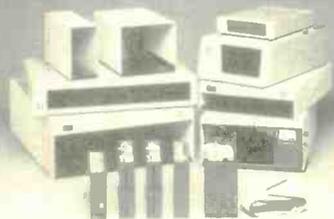

Complete line of drive enclosures

**800-223-0306**

CALL FOR FREE CATALOG

Dealer Inquiries Invited



39 Everett Dr., Bldg. D Lawrenceville, NJ 08648  
(609) 799-4440



## Report from the Caribbean

By Glenn Hauser

We're on the move again, visiting six islands during one week this summer. Our objective was not only to monitor and record, but also to visit almost every broadcasting facility on the islands. We came away with a vivid set of visual impressions, preserved in scores of color slides, several hours of recordings, and a notebook full of loggings and notes from interviewing station personnel.

Antigua, home of the BBC and Deutsche Welle Caribbean Relay Station, was our first stop. North American listeners of the BBC owe a great debt to this facility, which provides clearer and more reliable signals than are possible direct from Britain. If you've heard BBC on 11775 in the morning, 6175 in the evening, or 9510 late at night, this is the source of those transmissions.

The site is roughly in the center of the island, just north of a settlement called Sea View Farm. Five large red and white towers arranged in an arc support a network of curtain antennas, the interior towers holding up different curtains on each side. Power demands of the four 250-kW transmitters exceed what the public utility can supply, so each depends on its own diesel generator, as big as a locomotive. They're across the lawn from the transmitter building, where the four senders (each made up of three units) are arranged in a row in a long hall open to the outside. During our visit, in the middle of the afternoon, all were off the air, as is normal during the daytime until 4 pm AST (2000 UTC), so we stuck our head inside one of them and marveled at the size of the huge copper coils, which must be removed by hand when band changes are required. Our cordial host was the engineer in charge, Chris Clemens, who also showed us inside the 65° air-conditioned hut next to the recently installed satellite dish. Not only could we listen in on the feed from London to Antigua, but also a different circuit for Ascension, where we had previously served. Ascension is a much more isolated island, in the South Atlantic, but the fishing is great!



Many satellite dish owners would like to know how to tune in the BBC that way, avoiding the pitfalls of shortwave reception, but Mr. Clemens said this would be impractical without specially-designed equipment, since the audio from London is split into two separate parts, and then recombined for a higher-fidelity signal. Deutsche Welle opted for a different system to accomplish the same end, which on paper was superior to the BBC design, but in practice produces inferior audio.

We also visited the high-frequency receiving site, about 5 miles east. Much of the equipment had been torn out, and more was to follow, as there is no longer any need for it with the advent of satellite-feeding. It was sad to see large holes in the racks, a bank of twelve professional playback recorders going unused, but at least some shortwave receivers were still tuned to 15070 as backup. Barring total failure of the satellite, the only time HF feeds are needed is twice a year for a few days, during a few minutes after sunrise, when there is a solar transit outage. The receiving site has a "pipeline" to Europe, thanks to its rhombic arrays; but it will be mothballed. It occurred to us that with a bit of modification, it could be turned into a relay transmitter site for some other broadcaster . . .

Antigua is also the home of four medium-wave stations, three of which are often heard in North America. The Voice

of America relay is near the northern tip of the island near the airport and next to a US Naval base; a three-tower array broadcasts on 1580 kHz only four hours a night, in English at 0000-0400 UTC (although the carrier goes on an hour earlier for warmup and trouble-shooting, if necessary). The transmitter is an old army portable unit, which has previously seen duty in other parts of the world. There are rumors that VOA will be upgrading this facility as part of its worldwide expansion program.

ZDK, "Magic Radio" is the private commercial outlet, which on 1100 kHz is frequently heard along the east coast of North America as far as Newfoundland, especially around sunset. Its regular audience extends over much of the Caribbean, with a pop music format. Present studios are in a bright blue building near the outdoor market in St. Johns, the country's capital. Within a year, a new building of its own will be ready further east. The transmitter is north of the city, linked by low-power FM on 99.0 MHz.

Caribbean Radio Lighthouse operates on 1165 kHz from the southwestern part of the Island, near Jolly Beach. This conservative Baptist evangelical station also penetrates into North America, thanks to its split frequency. It's deeply involved in indoctrinating the children of this and neighboring islands, through a bible study course by radio. Among all the preachers, who are carefully selected and required not to overdo the solicitation, there is also a classical music program Mon.-Fri. at 9:30-9:55 pm. The organization is also resuming plans to put on another station in Grenada, now that the Marxist government is gone.

Montserrat. We hopped over to this "emerald isle" for a day—it's much more mountainous and scenic than Antigua, and the roads are much better. The major outlet here is Radio Antilles, "The Big RA," broadcasting from a seaside site at the southern end of the island. Though publicized as 200,000 watts on 930 kHz, the transmitter actually runs 135 kW, but the exaggeration comes from a directional pattern toward the south with a two-tower antenna. Its news

coverage is highly regarded, and the main program during the daytime is "Caribbean Togetherness."

Since last September, RA has been relaying the Voice of America at 8 pm-midnight. Manager Kristian Knaack, who was kind enough to talk with us for over an hour when we dropped in, is very pleased with this arrangement, since it makes for an increase in quality of listenership to compensate for a decline in quantity during those hours. He also feels that Radio Canada International's audience in the Caribbean has increased 1000% since it began relays on RA, nightly at 7-7:30 pm. He was surprised to hear that this visitor out of nowhere was a regular broadcaster on his station, each Sunday on the RCI relay. VOA, RCI (and Deutsche Welle for relays on shortwave) were picked up from a high-frequency receiving site at St. George's, not far from the studios in the capital, Plymouth—and the audio quality shows on 930. But by now, a line feed should be in operation for VOA, and also for RCI, which first feeds its audio to Washington. Herr Knaack has also produced and written a 25-program series for Caribbean listeners, "The Long War on the Short Waves."

He has a new competitor in Montserrat in the form of "Gem Radio," a partly-American-owned FM station which started in May, 1985. Like RA, it wants to reach as many other islands as possible, either through its 177 kW ERP station near Plymouth on 94.4 MHz, or a network of FM translators it plans, the first of which is already operating from the other side of Montserrat, and thus receivable in Antigua. The 100-watt stereo signal on 93.8 MHz reaches there surprisingly well. ZGM relies on music and news programming from the Satellite Music Network and Satellite News Network; U.S. offices are in Milwaukee.

*Anguilla.* Our next stop was St. Maarten, but day trips out to other islands, starting with nearby Anguilla, are of more radio interest. The Caribbean Beacon, another U.S.-owned evangelical station, is found in the southeastern part of the island, in a gleaming white building

with dark peach colored trim, certainly the nicest facility of all the AM & FM stations we visited. A new modular 50-kW transmitter is the first thing the visitor

sees, behind glass, upon walking in. If anything goes wrong, it can usually stay on the air by bypassing the problem through a backup module. It and the old



**Two things a technician shouldn't be without ...**

**#1. The Telephone**

**#2. The NEW MCM Electronics Catalog**

Your telephone is a very important part of your business. It saves you time ... it helps you run your business smoothly and efficiently ... it's dependable ... and it's convenient.

Like your telephone, the new MCM Catalog offers you many of the same advantages.

With our wide selection of product lines, you'll save time looking for parts. Our fast, friendly and dependable service will help you operate smoothly, and you'll like our low prices.

Convenient too! Our nationwide toll free numbers make us as close as that other important business tool — your telephone!

Call today for your FREE copy of the latest MCM Catalog. No obligation to buy!

**Catalog #12 Now Available**

**Call TOLL-FREE 1-800-543-4330**

**(In Ohio call 1-800-762-4315)**

**(In Alaska or Hawaii 1-800-858-1849)**



**MCM ELECTRONICS**

*A PREMIER Company*

858 E. Congress Park Drive  
Centerville, OH 45459

Source No. ME-15

CIRCLE 8 ON FREE INFORMATION CARD

# Montserrat




## ZGM FM 94

**Order  
Back Issues of  
MODERN  
ELECTRONICS**

## Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Earn up to  
\$30 an hour  
and more!

Learn at home in spare time.  
No previous experience needed!

No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radio-telephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications. Radio-TV, Microwave, Computers, Radar, Avionics and more! You don't need a college degree to qualify, but you do need an FCC License.

**No Need to Quit Your Job or Go To School**  
This proven course is easy, fast and low cost! **GUARANTEED PASS** - You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

**COMMAND PRODUCTIONS**  
FCC LICENSE TRAINING, Dept. 220  
P.O. Box 2223, San Francisco, CA 94126

Please rush **FREE** details immediately!

NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

15-kW transmitter feed a single tower on two separate frequencies, 1610 and 690 kHz, respectively. They were programmed in parallel at the time, but by now 690 should have been turned over to Family Radio (well-known on shortwave as WYFR), fed by satellite.

Thanks to the clear frequency of 1610, The Caribbean Beacon is heard nightly in North America, and frequently all over the world. The engineer said he had even been able to pull in 1610 during the daytime in Miami. The other 15-kW transmitter, no longer used, will be turned over to the Anguillan government's station, Radio Anguilla. That should greatly increase its coverage, except it may abandon the "split" channel of 1505 for an "even" one. That's the likely fate of the few remaining Caribbean splits, thanks to digital receivers which skip past frequencies ending in -5.

We suggest you not delay in DXing these stations, if you haven't already. With a good selective receiver, sensitive antenna, and a little help from the aurora over a darkness path, the following can be heard in North America: 535 Grenada, 555 St. Kitts, 595 Dominica, 705 St. Vincent, 825 St. Kitts, 885 Montserrat, 1165 Antigua, 1505 Anguilla.

*St. Eustatius*, one of the Netherlands Antilles, has had a radio station since May 1985, but due to a daytime-only schedule, no DX listeners had heard it. Radio Statia (the common name of the island, pronounced STAY-shuh), PJE3, operates 1 kW on 1120 kHz at 1000-2230


UTC. It doesn't have to sign off at sunset, but prefers to, unless a demand arises for evening broadcasts. If this schedule remains, the only remote chance for North Americans to hear it will be at sign-on and sign-off when the sun is lowest; although sunrise and sunset times vary little in the tropics, keep in mind that during December there'll be more darkness to the north.

*Saba* was our final, and most enjoyable stop. This smallest of the Netherlands Antilles is also the most vertical—a volcanic peak jutting out of the ocean. Practically every home on the island (pop. 1000) has a terrific panoramic view of the sea, as they are perched on the slope. An "impossible" road connects the airport on one side of the island to The Bottom on the other side, home of the Voice of Saba, PJF1, 1410 kHz. This small station began more than a decade ago on 1445 and 1435 kHz, but after it moved to 1410 it disappeared from the *World Radio TV Handbook* and from the consciousness of DX listeners.

Its affable owner, Max Nicholson, is also acting governor of the island when the governor is away. PJF1 also has a studio in the more populous St. Maarten, on Front Street in Philipsburg. Not only is it a remote studio, but it serves as the relay point (by FM) from the studio on Saba to the transmitter on the other side of Saba! The carrier stays on all night, though programming is limited to 1000-2330 UTC (Sundays from 1700). We suggested that it would be helpful to distant listeners if a continuous ID tape could be played during the "off" period; and since Mr. Nicholson showed us the pairs of crystals he still has for 1445 and 1435, how about a special DX test on one of the old frequencies? However, time was running out, since a brand-new 5-kW transmitter was to be installed by the end of June, and it could not accept the old crystals. Perhaps the old transmitter will remain as a standby.

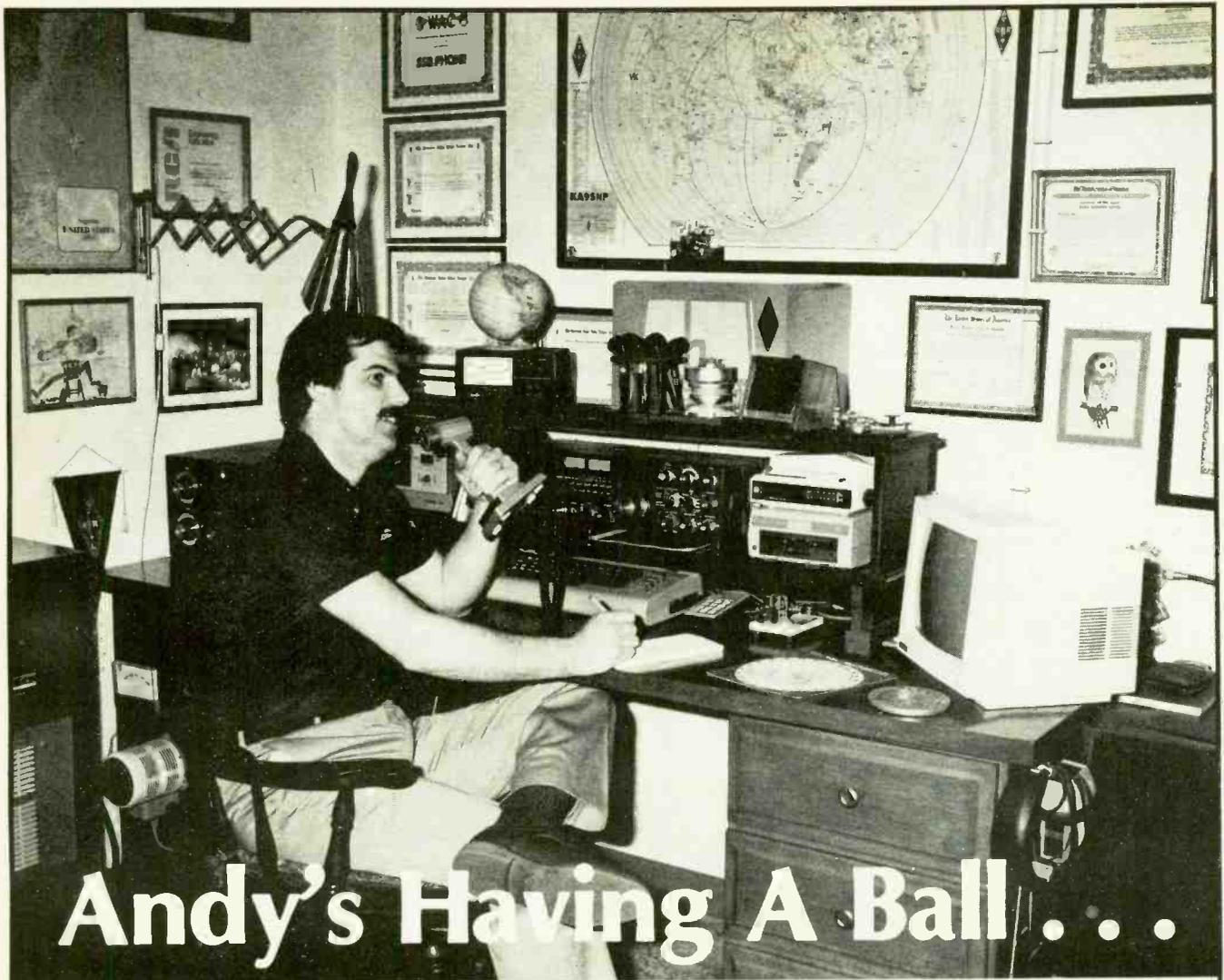One sure way to hear the Voice of Saba is to visit the island; our half-day visit was all too short. Saba is beautiful, unspoiled, and away from it all, though easily accessible through St. Maarten. **ME**





# Andy's Having A Ball . . .

## and you can too!

Andy is a Ham Radio operator and he's having the time of his life talking to new and old friends in this country and around the world.

You can do it too! Join Andy as he communicates with the world. Enjoy the many unique and exclusive amateur bands . . . the millions of frequencies that Hams are allowed to use. Choose the frequency and time of day that are just right to talk to anywhere you wish. Only Amateur Radio operators get this kind of freedom of choice. And if it's friends you're looking to meet and talk

with, Amateur Radio is the hobby for you. The world is waiting for you.

If you'd like to be part of the fun . . . if you'd like to feel the excitement . . . we can help you. We've got all the information you'll need to get your Ham license. Let us help you join more than a million other Hams around the world and here at home. Who are we? We're the American Radio Relay League, a non-profit representative organization of Amateur Radio operators.

For information on becoming a Ham operator  
circle number 110 on the reader service card or write to:

**AMERICAN RADIO RELAY LEAGUE**

Dept CQ, 225 Main Street  
Newington, Conn. 06111.

## Transconductance Amp

(from page 50)

proved noise and distortion levels make them useable in professional high-end consumer gear. Solid State Microtechnology (2070-B Walsh Ave., Santa Clara, CA 95050) makes several ICs in this category, including the SSM 2024 quad OTA and SSM 2014 vca with a dynamic range of 118 dB and 0.01% distortion!

Curtis Electromusic Specialties (distributed by PAIA Electronics, 1020 W. Wilshire Blvd., Oklahoma City, OK 73116) makes a series of OTA-based chips for audio/musical uses. These include the CEM 3330 and CEM 3360 vcas.

### In Closing

From the foregoing, you can see that the operational transconductance amplifier is a highly versatile—though a bit anonymous—op-amp-like device. Hopefully, you will introduce it to your catalog of exciting ICs with which to experiment and to use in practical circuits.

## NEW FROM DON LANCASTER

### HANDS-ON BOOKS

CMOS Cookbook	14.50
TTL Cookbook	12.50
TV Typewriter Cookbook	12.50
Active Filter Cookbook	14.50
Micro Cookbook vol I	15.50
Micro Cookbook vol II	15.50
Enhancing your Apple vol I	15.50
Enhancing your Apple vol II	15.50
Applewriter Cookbook	19.50
Apple Assembly Cookbook	21.50
Incredible Secret Money Machine	7.50

### UNLOCKED SOFTWARE

Absolute Reset IIe & IIc	19.50
Applewriter Toolkit (Dos 3.3e)	39.50
Applewriter Toolkit (ProDOS)	39.50
Both Applewriter Toolkits	59.50
Applewriter/Laserwriter Utilities	49.50
Laserwriter Demo Pack	FREE
Apple Ram Card Disassembly Script	24.50
Enhance vol I Companion Disk	19.50
Enhance vol II Companion Disk	19.50
Assembly CB Companion Disk	19.50
Applewriter CB Companion Disk	24.50
Classic Cell Animation Demo	12.50

FREE VOICE HELPLINE

VISA/MC

## SYNERGETICS

Box 809-ME  
Thatcher, AZ 85552  
(602) 428-4073

CIRCLE 56 ON FREE INFORMATION CARD

# LISTEN UP!

Here's what you've been looking for—an all new hard-hitting monthly magazine which gives a unique insider's view of what's really going on in the world of communications. POPCOMM is your primary source of information—bigger and better than any communications magazine, with exciting coverage of scanners, shortwave broadcast & utility stations, spy stations, pirate and clandestine broadcasters, RTTY monitoring, survivalist communications systems, FCC news, wiretapping and bugging, scrambling/unscrambling, surveillance/undercover communications, satellite & cable TV, sophisticated telephones, & more. What you've been looking for all along! Take advantage of substantial savings over the newsstand price by subscribing now. Don't miss out on even one single issue of POPULAR COMMUNICATIONS—order your subscription now.

## Twelve Issues \$16

## POPULAR COMMUNICATIONS

76 N Broadway, Hicksville, NY 11801

Yes! The NEW POPULAR COMMUNICATIONS is just the magazine I've been looking for. Start sending it to me now! I understand that I may cancel at any time for any reason, and receive a full refund on my unused subscription.

Paid by:  Check  Money Order  MasterCard  Visa  
My account number is


Name \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_  
Canada/Mexico—one year \$18.00; two years \$33.00, three years \$48.00; Foreign—one year \$20.00, two years \$37.00; three years \$54.00; Foreign Air Mail—one year \$73.00, two years \$143.00, three years \$213.00.

USE  
YOUR  
FREE  
INFORMATION  
CARD

## HOT!!

Turn Your Computer Into A

## DIGITAL STORAGE OSCILLOSCOPE

And More With The  
**MB230 WORKSHOP**



OSCILLOSCOPE

**\$129.95**  
(C64 Version)



INTERFACE UNIT

The MB230 is designed for use with your home or personal computer. It is a complete Electronic Instrument and Electro-Mechanical Workshop which contains Interface Unit, D.C. Motors, Gears, Sensors, Construction Components, Disk Based Software and instructions for 50 sample projects.

Included are:

- Digital Storage Oscilloscope
- Digital Voltmeter
- Digital Speech & Sound (Record/Playback)
- A/D-D/A Conversion
- D.C. Motor Control (Var. Speed)
- Infrared Control
- Motors, Gears, Generators
- Motorized Mechanical Robotics
- Cars, Cranes, Toys, Etc.



VOLTMETER



MOTOR AND GEARS

The heart of the MB230 Workshop is the B100 Interface Unit which connects to all types of sensors and is able to control lights, motors, relays and other external devices. The MB230 manual contains suggestions and instructions for many advanced projects such as antenna positioning and relay control.

Available for the following computers:

Commodore 64 (\$129.95), Apple 2+, 2E (\$159.95),

Atari 800 (\$139.95).

Coming soon for IBM, Amiga, Atari 520ST.

To order or for more information call toll free 1-800-824-2549. Cashier's check, Money order, VISA, or Mastercard orders accepted.

Order now to avoid delay!

ALL ORDERS SHIPPED UPS BLUE AT NO EXTRA CHARGE

**MULTIBOTICS, INC.** 2561 South 1560 West  
Woods Cross, Utah 84087

CIRCLE 26 ON FREE INFORMATION CARD

# ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR  
**B.S.E.E.  
DEGREE**

**THROUGH HOME STUDY**

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

**COOK'S INSTITUTE  
OF ELECTRONICS ENGINEERING**



347 RAYMOND ROAD  
P.O. BOX 20345  
JACKSON, MISSISSIPPI 39209

CIRCLE 42 ON FREE INFORMATION CARD

## SUPER LONG PLAY TAPE RECORDERS

10 Hour Model — \$95.00\*  
14 Hour Model — \$159.00\*

Modified Panasonic Slimline, high quality, AC-DC Recorders provide 5 or 7 continuous hours of quality recording & playback on each side of cassette for a total of 10 or 14 hours depending on model. Built-in features include • Voice level control, • Digital counter, etc. TDK DC 180 Cassette Furnished.



### PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up. **\$24.50\***



**VOX VOICE ACTIVATED CONTROL SWITCH**  
Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike. **\$24.95\***



\* Add for ship & hdg. Phone Adapter & Vox \$1.50 ea. Recorders \$4.00 ea. Cal. Res. add tax. Mail order. VISA, MIC, COD's OK. Money Back Guarantee. Free data avail., Dealer Inquiries invited. Free data. ©  
**AMC SALES, Dept. 9335 Lubec**  
St., Box 928, Downey, CA  
(213) 90241 Phone  
869-8519

CIRCLE 49 ON FREE INFORMATION CARD

# BOOKS

**The New Sound of Stereo, By Ivan Berger & Hans Fantel. (New American Library, Soft cover. 265 pages. \$12.95.)**

Though this book is meant to serve as a guide to buying and using the latest in hi-fi equipment, you will not find page after page of information about current makes and models. This would limit the book's usefulness, since the models would be quickly obsolete. Rather, the authors, both of whom are long-time experts in the hi-fi/stereo field, wisely concentrated on the relatively unchanging principles right through to digital audio gear.

Following a brief background on audio, the book introduces the "system" concept and how to build a component system suitable to one's needs. Actual listening to sound—which is the reason why one buys a hi-fi system in the first place—is emphasized. Much of the book also focuses on the various elements that make up a system: speakers, turntables, tuners, tape decks, etc. To provide maximum detail coverage, the majority of these topics are discussed in more than one chapter, such as "A Sense of Power" and "A Sense of Control" under amplifiers, and the turntable, cartridge and tonearm under "Phonographs." Right up to date, the book covers compact-disc and digital technology, sound-enhancement devices, and portable and car stereo equipment.

Lots of how-it-works information is given, along with pros and cons, helpful advice, drawings and photos. Technical information, consisting mainly of curves that depict power, frequency response, sensitivity, etc., is also given.

An Appendix, titled "When Things Go Wrong," provides a nice touch. It gives sage advice on keeping a system operating and determining when ailing gear needs a repair shop.

*New Sound of Stereo* is highly recommended for anyone interested in understanding the underlying workings of hi-fi components and what additional functions featured in top-of-the-line, costlier models actually do. Coupled with the text's lucid writing, the book will make you a more judicious buyer.

**Enercell Battery Guidebook (Radio Shack. Soft cover. 156 pages. \$1.99.)**

If you use or specify batteries for electronic products and projects (and that in-

cludes just about everyone), this information-packed book reveals most of what you could ever wish to know about batteries. It describes in full technical detail the entire line of Radio Shack's "Enercell" batteries, including common carbon-zinc, all types of "high-energy," alkaline, mercury- and silver-oxide, lithium and rechargeable nickel-cadmium cells and batteries. Though the information is specifically for Radio Shack's Enercell line, almost all of it is also applicable to other manufacturers products.

Opening chapters deal with definitions of the various types of cells available, factors that influence battery performance, selecting the right cell or battery for a given application, recharging cells, etc. Then more than 100 pages is devoted to technical listings. Contained in each listing are a dimensioned drawing of the cell or battery, a table of technical specifications, and in many cases one or more graphed characteristics curves. Provided information includes cell or battery type, suggested current range, terminal voltage at full charge, rated capacity, average weight and volume, etc. A shortcoming is omitting listing of competitive brand numbers—Duracell *et al*—but the price paid for this is made up for by the very low cost of the book.

**Maintenance and Repair of Video Cassette Recorders by Matthew Mandl. (Prentice-Hall, Inc. Hard cover. 245 pages. \$24.95.)**

This book describes how to maintain the mechanical and repair the electronic portions of VCRs. Initial chapters, written to be understood by even readers with no background in electronics, lay the groundwork that leads up to electronic trouble-shooting procedures. Included here are sections on routine maintenance of the mechanical portions of VCR transports, as well as information on the basic VCR signals and systems and the most common problems found in both VHS and Beta VCRs.

Comprehensive descriptions of the VHS and Beta systems are handled in separate chapters. Then comes a run-down on the various test instruments needed to conduct a troubleshooting session. The remainder of the book is devoted to repair procedures and includes instructions on tuning and aligning cir-

cuits, isolating and replacing defective parts, pinpointing common VCR troubles, and miscellaneous VCR-related factors. A chapter on Test Equipment covers the use of pattern generators, oscilloscope use with display examples and the vectorscope for adjusting color.

Many schematics and other illustrations support the text, which serve as a strong foundation in understanding how VCRs work, as well as servicing them.

**Apple IIc, an Intelligent Guide by Fred Blechman. (CBS Computer Books. Soft cover. 270 pages. \$17.95.)**

The marketing thrust of the Apple IIc computer is toward users who run and use commercial software. Accordingly, if you want to program, the supplied documentation is woefully inadequate. Moreover, even if the Apple IIc user is familiar with BASIC programming, some Apple IIc peculiarities present an obstacle. This book fills the information hole for programming applications.

The guide starts at square one and successively builds from there, showing you how to create and customize programs on the IIc. Most of the text is given over to fairly in-depth discussions of BASIC programming techniques, with particular emphasis on Apple IIc color and graphics programming.

There are a couple of bonuses, too. One is the helpful information given on printers, modems, disk drives and other non-Apple peripherals that can be added to the IIc relatively easily and inexpensively. The other is an entire chapter containing reviews of 24 commercial software packages that run on Apple II series computers, including the IIc.

**NEW LITERATURE**

**Video Products Catalog.** Nearly 200 video accessories and installation hardware are listed and described in RCA's new 42-page, color catalog. New in this edition is a section on camcorder accessories. Other product lines described include cases for VCRs and cameras, tripods and camera mounts, blank videocassette tapes, and more. For a copy of the 1986 RCA Video Accessories catalog, write to: RCA Sales Promotion Services, Deptford, NJ 08096.

**Parts & Equipment Catalog.** Listed in Fordham Radio's new 164-page Summer '86 catalog are almost 2000 brand-name products ranging from test instruments to tools to video and audio equipment. Other categories include CCTV monitors and equipment; PA equipment; audio accessories; car stereos; CB transceivers; telephones; and more. All items listed are fully described, illustrated and include

specifications, applications and pricing information. For a free copy, write to: Fordham Radio 260ME Motor Pkway., Hauppauge, NY 11788.

**Terrestrial Interference Filter Catalog.** Filters designed to cure terrestrial interference (TI) in TVRO Earth stations are described in the Filters For Suppressing Microwave Terrestrial Interference cata-

**ELENCO PRODUCTS AT DISCOUNT PRICES!**



**20 MHz DUAL TRACE OSCILLOSCOPE**  
**\$336** MO-1251



**35 MHz DUAL TRACE OSCILLOSCOPE**  
**\$545** MO-1252

Top quality scopes at a very reasonable price. Contains all the desirable features. Elenco's 2 year guarantee assures you of continuous service. Two 1x, 10x probes, diagrams and manual included. Write for specifications.

**MULTI METER with CAPACITANCE and transistor tester**  
**\$65** Model CM-1500  
Reads Volts, Ohms, Current, Capacitors Transistors & Diodes

**TRUE RMS 4 1/2 DIGIT MULTIMETER**  
**\$135** Model M-7000  
.05% DC Accuracy  
1% Resistance with Freq. Counter & Deluxe Case

**3 1/2 DIGIT MULTIMETER**  
**\$25** Model M-1600  
1% DC Accuracy  
1% Resistance  
Reads 10A DC

**GF-8016 Function Generator with Freq. Counter**  
**\$219**  
• Sine, Square, Triangle.  
• Pulse, Ramp, .2 to 2 MHz  
• Frequency .1 thru 10 MHz  
GF 8015 without Freq. Meter \$169

**NEW POWER BLOX**  
The Power Supply For Breadboarding  
**\$1495** **\$995**  
Now a Power Supply for your Bread Blocks. Snaps in to existing units. Fully regulated and short circuit protected.  
12V @ .3A, 5V @ 1A, .5V @ .5A  
\$22.95 for Both, Power Blox & Breadboard

**Triple Power Supply XP-660**  
**\$14950**  
0-20V @ 1A  
0-20V @ 1A  
5V @ 5A  
Fully Regulated, Short Circuit Protected with 2 Limit Cont. 3 Separate Supplies.

**3 Amp Power Supply XP-650**  
**\$11950**  
0-40V @ 1.5A  
0-20V @ 3A  
Fully regulated, short circuit protected current limit control

**DIGITAL LCR METER**  
Model LC-1800  
Measures: Inductors Capacitors, Resistors  
**\$148**  
Inductors 1µH to 200 H  
Capacitor 1Pf to 200µf  
Resistor .01Ω to 20M Ω  
Ranges 6 Ind, 7 cap, 7 res

C&S SALES, 8744 W. North Ter. Niles, IL 60648 800-292-7711 (312) 459-9040  
15 DAY MONEY BACK GUARANTEE ASK FOR CATALOG  
2 Year Limited Guarantee! Add 5% for Postage (\$10 max.), IL Res., 7% Tax

CIRCLE 91 ON FREE INFORMATION CARD

## ELECTRONIC COMPONENTS



**FREE CATALOG**

Manufacturers of Quality  
Electronic Components

Serving the Nation from Texas and California

- BATTERY HOLDERS & CLIPS • COILS
- CAPACITORS • CONNECTORS • FUSES
- JACKS • KNOBS • LAMPS • PLUGS
- MICROPHONES • POTENTIOMETERS
- RELAYS • RESISTORS • SWITCHES
- TRANSFORMERS • SPEAKERS • LEDS
- SEMICONDUCTORS • RF COILS

OVER 16,000 DIFFERENT ITEMS IN STOCK!  
CATALOGS MAILED OUTSIDE USA SEND \$2.00

**MOUSER ELECTRONICS**  
2401 HWY 287 NORTH MANSFIELD, TX 76063  
PHONE 817-483-4422

CIRCLE 43 ON FREE INFORMATION CARD

## cable tv

### DESCRAMBLER PARTS

We stock the exact parts, PC Board and A.C. Adaptor for an article published in Radio Electronics Magazine (Feb., 1984) on building your own CABLE TV DESCRAMBLER.

**#701 PARTS PACKAGE ..... \$29.95**

Includes all the original resistors, capacitors, diodes, transistors, integrated circuits, coils and IF transformers.

**#702 PC BOARD ..... \$12.95**

Original etched & drilled silk-screened PC Board used in the article.

**#704 AC ADAPTOR ..... \$12.95**

(14 volts DC @ 285MA)

**Both #701 & #702 ..... \$39.00**

**#701, 702 & 704 ..... \$49.00**

**FREE!!** Reprint of Radio Electronics Article on Building Your Own Cable TV Descrambler with any purchase.

Add \$2.50 Shipping & Handling  
\$4.50 for Canadian Orders

**ORDER TOLL FREE**

1-800-227-8529

Visa, MasterCard or C.O.D.

**J & W ELECTRONICS, INC.**

P.O. Box 800Z  
Mansfield, MA 02048

CIRCLE 10 ON FREE INFORMATION CARD

log from Microwave Filter Co. Included are filters designed to cure destructive and nondestructive interference and diagrams tell you where to place the filters in a TVRO system. Among the items described in full detail are an Installer's Kit for diagnosing and curing nondestructive TI in 70-MHz i-f receivers and a Sky Doc Kit that deals with both destructive and nondestructive TI. For a free copy of catalog TVRO/85, write to: Linda DeCoursey, Microwave Filter Co., Inc., 6743 Kinne St., East Syracuse, NY 13057.

**Instrument & Accessories Catalog.** A full-color short-form catalog that lists a complete range of bench test instruments is now available from O.K. Industries. The 22-page catalog contains complete descriptions, specifications and photos of: function/pulse/sweep generators, frequency and universal counters, digital multimeters, a mini-oscilloscope, thermometers, probes and pulsers, plus such accessories as thermocouples, test-lead kits, carrying cases, a bench rack, test clips, etc. For a free copy of the "Bench Test Instrument" catalog write to: O.K. Industries, Inc., Electronics Division, 3455 Conner St., Bronx, NY 10475.

**Darlington Transistor Catalog.** A 48-page catalog that describes single- and dual-Darlington power transistor modules is available from Semikron Inc. It contains electrical, mechanical and thermal specifications and data and includes circuit diagrams, dimension drawings and performance curves. For a copy of the Transipack catalog, write to: Martha T. Varney, The Gurrier Co., One Park Ave., P.O. Box 788, Hampton, NH 03842.

**Stepper Motor Catalog.** Comprehensive performance specifications for its stepper motors and controls are contained in the new full-size, looseleaf-binder-punched 40-page catalog just released by Bodine Electric Co. Test data on the company's high-accuracy 1.8 stepper motors and companion line of application matched L/R modular controls are given. Included is information on Bodine's new encased translator and indexer controls with resonance compensation that minimize mid-frequency resonances and extend usable speed/torque motor range. Also included are a new 8-ampere open chassis translator and inexpensive damping modules. For a free copy of

Catalog No. ST-2, write to: Bodine Electric Co., 2500 W. Bradley Pl., Chicago, IL 60618.

**R-f Instruments Catalog.** Bird's new 60-page R-f Instruments catalog lists and describes the company's Thruline and directional wattmeters, coaxial load resistors and attenuators, calorimeters and r-f components. A Tech-Data section is provided. For a free copy of Catalog No. GC-85, write to: Bird Electronic Corp., 30303 Aurora Rd., Cleveland (Solon), OH 44139.

**Ceramic Capacitors Catalog.** A 24-page catalog from Cera-Mite Corp. provides comprehensive information about selection and use of a wide variety of ceramic capacitors. Included are sectional drawings that illustrate construction features and curves that illustrate capacitance change versus frequency and temperature and capacitance decrease versus dc voltage bias. Described and defined are ceramic-disc, heavy-duty and feed-through capacitors. The catalog provides such data as marking information, lead style specifications, packaging, performance, general application notes, military and aerospace qualifications and diagrams of typical applications. For a free copy, write to: Cera-Mite Corp., 123 6 Ave., Grafton, WI 53024.

**Test & Measurement Peripherals Catalog.** Rapid Systems' new newspaper-format catalog contains specifications on that company's digital and enhanced digital oscilloscope, spectrum analyzer, data logger and data acquisition peripherals for Apple, Commodore and IBM personal computers. Also included are a complete description of the company's Digital Signal Processing Lab Course, applications and comparison charts and a distributor list. For a free copy, write to: Rapid Systems Inc., 755 N. Northlake Way, Seattle, WA 98103.

**IC/Transistor Selector Guide.** A quick-reference selection guide that describes configurable gate arrays, linear ICs, bipolar LSI memory devices, digital ICs and small-signal transistors is available from Raytheon. The 96-page guide gives product descriptions and specifications and cross-reference charts. For a copy of the Product Selection Guide, write on company letterhead to: Marketing Communications Dept., Raytheon Semiconductor, 350 Ellis St., Mountain View, CA 94039.

MASTER THE NEW ELECTRONICS WITH MCGRAW-HILL'S

# Contemporary Electronics Series

The fast, easy and low cost way to meet the challenges of today's electronic innovations. A unique learning series that's as innovative as the circuitry it explains, as fascinating as the experiments you build and explore.


From digital logic to the latest 32-bit microprocessor, the McGraw-Hill Contemporary Electronics Series puts you into the electronic picture one easy step at a time. Fifteen unique Concept Modules, sent to you one every 4-6 weeks, give you a handle on subjects like optoelectronics, robotics, integrated circuits, lasers, fiber optics and more.

Each Concept Module goes right to the heart of the matter. You waste no time on extraneous material or outdated history. It's a fast, efficient, and lively learning experience... a non-traditional approach to the most modern of subject matter.

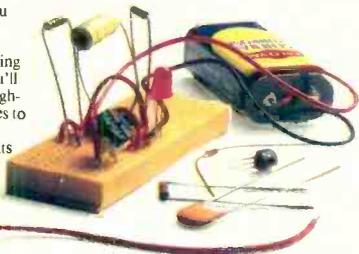
### Unique Interactive Instruction

With each module, you receive a McGraw-Hill Action Audio Cassette. Each tape is a dynamic discussion that drives home the key facts about the subject. Your learning

With your first module, you get this solderless breadboarding system. You'll use it throughout the series to build electronic circuits and bring concepts to life.



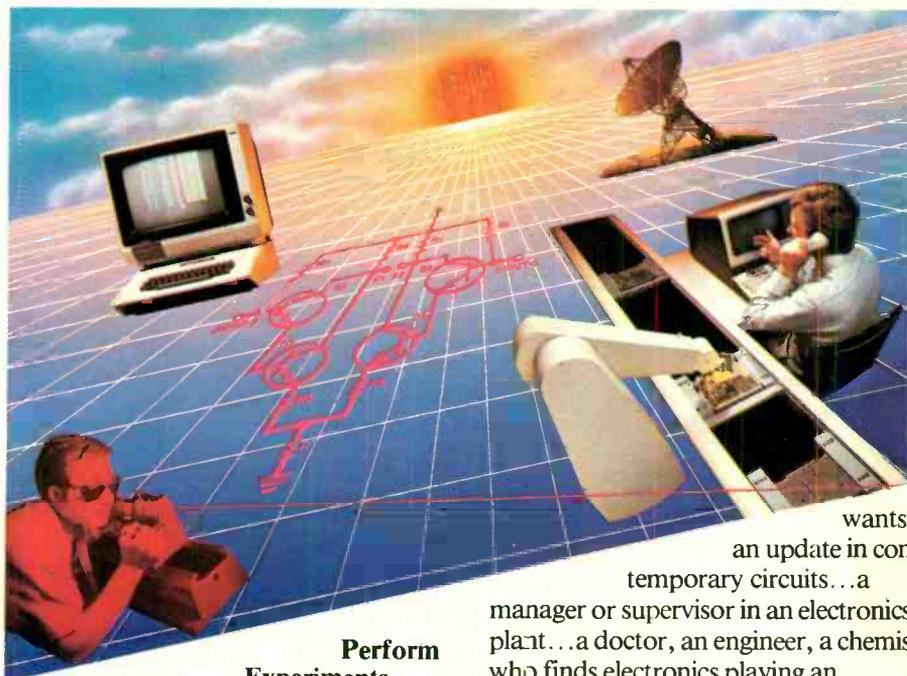experience is reinforced through interaction with vividly illustrated text, audio cassettes, and actual electronic experiments. Indexed binders preserve backup material, notes, and tapes for convenient referral.



wants an update in con-

temporary circuits... a

manager or supervisor in an electronics plant... a doctor, an engineer, a chemist who finds electronics playing an increasingly important role in your work. It's even for electronics engineers or technicians who feel their training needs freshening up. It's the quickest,

most convenient, probably least expensive way to do it. And the only one that gives you hands-on experience.

### Perform Experiments in Contemporary Electronics

Throughout your series, laboratory experiments reinforce every significant point. This essential experience... dynamic, hands-on demonstrations of theory in practice... will help you master principles that apply all the way up to tomorrow's latest VLSI (Very Large Scale Integrated) circuitry.

In your very first module, you'll use integrated circuits to build a digital oscillator, verifying its operation with a light emitting diode (LED). You'll learn to identify passive and active components, understand concepts common to all electronic circuits.

### For Anyone Interested in Electronics

The Contemporary Electronics Series is designed for anyone from hobbyist to professional. It's for you if you're looking for new fields of interest... if you're a teacher who



### 15-Day No-Risk Trial

To order your first module without risk, send the postage-paid card today. Examine it for 15 days under the terms of the order form and see how the Contemporary Electronics Series gets you into today's electronics. If card has been used, write us for ordering information.



McGraw-Hill  
Continuing Education Center  
3939 Wisconsin Ave.  
Washington, D.C. 20016

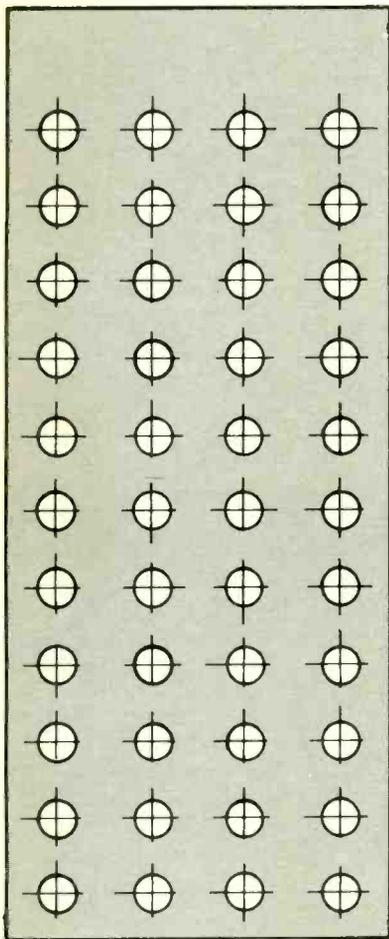


Fig. 5. Actual-size alignment template for LED installation.

the *bottom* of the board. Then prepare a two-conductor zip cord by removing  $\frac{1}{4}$ " of insulation from the conductors at both ends. Tightly twist together the wires in each conductor and tin with solder. Make these cords as long as needed to route between your amplifier and the Power Meter after final installation in your vehicle. Solder one end of this cable to the pads labeled LEFT INPUT and RIGHT INPUT from the bottom side of the board.

Next, connect the red +12-volt and black ground power leads to the pads labeled +12V and GND on the bottom right side of the board. Make these leads long enough to reach the vehicle electrical system's ground and any point that is at +12 volts when the ignition is on and is off

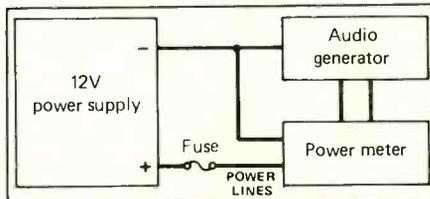


Fig. 6. Test setup for calibration.

when the ignition is off. The +12-volt wire should have an in-line fuse holder in it. Install a 1-ampere fast-blow fuse in the holder.

Any enclosure large enough to accommodate the circuit board and that has one panel that can be replaced with a clear or tinted panel can be used to house the project. An ideal size would have internal dimensions of  $7\frac{1}{4}$ "  $\times$   $2\frac{1}{4}$ "  $\times$   $1\frac{1}{2}$ ". You can make such an enclosure from  $\frac{1}{8}$ "-thick Plexiglass or  $\frac{1}{4}$ "-thick plywood, or you can modify an existing plastic or metal chassis to suit your needs. Just be sure to make one  $7\frac{1}{4}$ "  $\times$   $2\frac{1}{4}$ " panel from bronze or neutral-gray tinted transparent plastic to provide good contrast in relatively bright light for easy viewing of the display. Whichever material you use, paint all inside surfaces of the enclosure, except the faceplate, flat black to cut down on reflections.

Mask from view the left and right portions of the circuit board not in the LED matrix area. This can easily be done by applying black electrical tape or black paint to the appropriate areas on the inside surface of the faceplate.

Mount the circuit board inside the enclosure with four sets of  $\frac{1}{2}$ " spacers and 4-40  $\times$   $\frac{3}{4}$ " machine screws, nuts and lockwashers to the faceplate. The lockwashers between the nuts and circuit board are important because they prevent the hardware from working loose due to vibration from the road.

Because the display consists of LEDs whose different colors are self-explanatory, there is no need to label the faceplate. However, if you wish

to give your project a more professional appearance, you can apply legends to the outside surface of the faceplate. Typical legends include LEFT LOW FREQUENCY, RIGHT LOW FREQUENCY, LEFT HIGH FREQUENCY and RIGHT HIGH FREQUENCY to the left of the individual bargraphs in the blanked-out areas. Under the bottom bargraph, you can bracket each color grouping and letter LOW POWER, MEDIUM POWER and HIGH POWER legends in the appropriate areas and then run vertical lines to separate the color groups.

All lettering should be done with a white dry-transfer lettering kit applied directly to the front surface of the faceplate. Since this type of lettering is very fragile, you should place an additional  $\frac{1}{8}$ " thickness of clear Plexiglass over the entire faceplate to protect the lettering. In this event, use 1"-long screws for mounting the board.

### Checkout and Calibration

Referring to Fig. 6, connect the Power Meter's dc power leads to a 12-volt dc source. The first column of LEDs at the left (farthest from the transistors) should immediately light, indicating that power has been applied to the project. All other LEDs in the display should be off.

Apply an input signal from an audio signal generator or other audio source between the LEFT INPUT channel lead and the negative power-supply lead. Turn up the sound until the LEDs in the top and/or third row of the display begin to light. The row(s) of LEDs that turn on will depend on the frequency or frequencies delivered to the Power Meter's input.

If you are using an audio signal generator, sweep the frequency control from the low to the high end of the audio spectrum while observing the LED display. The LEDs in the top and third rows come on at frequencies above and below about 3 kHz, respectively.

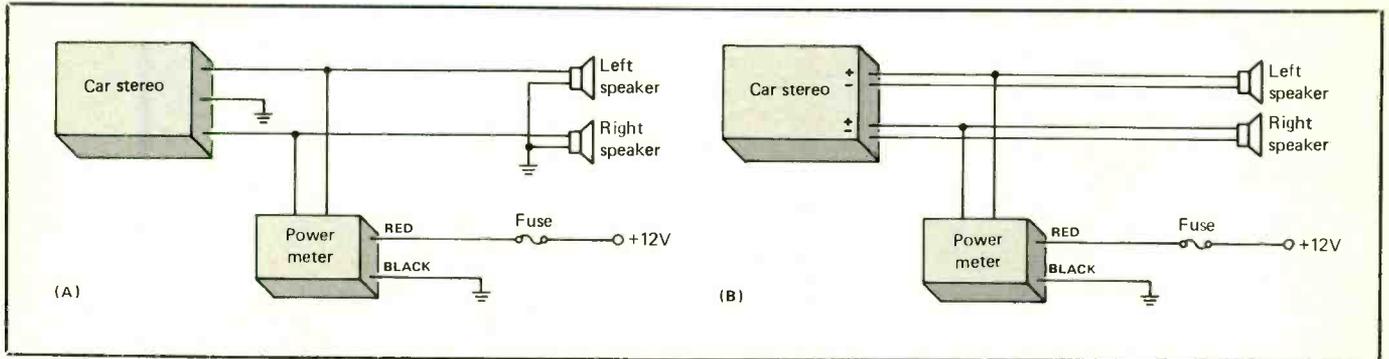


Fig. 7. Power Meter can be connected into conventional grounded (A) and floating ground (B) systems.

Disconnect the signal generator from the LEFT INPUT and connect it to the RIGHT INPUT. Repeat the above test, this time observing that the second and bottom rows of LEDs light when the signal is swept from the high to the low frequencies, respectively.

If everything checks out okay connect the Power Meter to the audio amplifier and electrical system in your vehicle. Refer to Fig. 7 for details. Determine whether your system has a conventional chassis ground or has a floating ground and use the hookup arrangement that applies to your installation. Do not perform final installation until calibration is done.

You can calibrate the Power Meter in either of two ways. One way is to tune to an FM station and turn up the volume control until the sound just begins to distort and then back off until the distortion just disappears. Then adjust the R7 through R10 trimmers until just the first red LED (third from the right) in each column comes on. If you are using a mono signal source, perform these adjustments separately for each channel. To make calibration as accurate as possible, set all tone and equalizer controls for a flat frequency response before you adjust the trimmer controls.

(Note: Always set the trimmer controls so that the *first* red LED in

each bargraph display comes on with average signal levels. Do *not* set the controls so that all red LEDs come on with average signal levels. If you do, there will be no way you can tell from looking at the display when dangerous power levels and transient high-power peaks are being delivered to your speakers.)

For the second, much more accurate calibration procedure, make a calibration tape on a home cassette recorder. Record a minute or two each of 400-Hz and 5-kHz tones on both stereo tracks simultaneously. Play the tape back on your car stereo system while monitoring the output of your amplifier with an oscilloscope. If you have a 2- or more channel scope, you can observe both amplifier channels simultaneously. Otherwise, you must work on each channel separately. Turn up the volume to the point just before clipping of the signal appears on the scope's screen and adjust the trimmer controls so that the first red LED in each of the respective bands comes on. Keep these tests as short as possible to avoid damaging your speakers, your amplifier and your ears!

If you want to use the Power Meter only as a visual display, accurate calibration is not necessary. Simply adjust the controls so that the first of red LEDs come on at your normal highest listening level.

During final installation, mount the Power Meter in a location where the display will be easy to view but not where it will interfere with the driver or passengers or will pose a hazard in an emergency situation. After you install the Power Meter in its final location, route all wiring to and from it so that it is not visible and will not be damaged.

ME

148 PAGES  
100'S OF NEW  
PRODUCTS

GET IT NOW!



More pages, more products and it's hot off the press! Get the new 1986/7 DICK SMITH ELECTRONICS Catalog and find anything for the electronics enthusiast. The data section alone is worth the price of admission. Send for your copy today.

Please reserve my copy of the 1986 Dick Smith Catalog. I enclose \$1 to cover shipping.

Name .....

Address .....

City .....

Zip .....

69H




DICK SMITH ELECTRONICS INC.  
P.O. Box 2249 Redwood City CA 94063  
EVERYTHING FOR THE ELECTRONICS ENTHUSIAST!


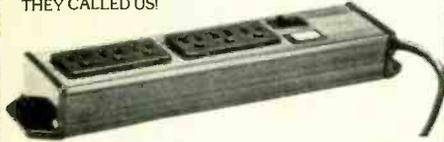
### Advanced Surge Protector/Filter !! SURGE PROTECTION !!

Do you want the best protection available at the best price with a lifetime warranty? The U.S. NAVY, AT&T, U.S. ARMY, NASA, and the Colorado state school system did so THEY CALLED US!



**ZAPSTAR S-6 SURGE PROTECTOR/FILTER**  
**\$59.95**

- \* Six Grounded Outlets
- \* Light to Indicate Protection is in Effect
- \* Dual Stage EMI/RFI Filtering
- \* On/Off Power Control Rocker Switch
- \* 15 Amp Circuit Breaker
- \* Full Three Mode Surge Protection

#### ZAPSTAR S-6 - SPECIFICATIONS

<b>RESPONSE TIME:</b>	Under 1 Nanosecond
<b>CLAMPING VOLTAGE:</b>	151 Volts
<b>DISSIPATION CAPABILITY:</b>	100 Joules (1,000,000 Watt 100 Microsecond)
<b>FILTER ATTENUATION:</b>	-55 DB (1-1000 MHZ)

So it's no wonder that the people with the most to protect call us for protection.  
Call Toll Free

## 1-800-624-8189

In Florida, call (305) 722-7770.

Why settle for less?

Manufactured by:  
SEVERTS-ZORMAN ENGINEERING, INC.  
Ft. Lauderdale, FL



CIRCLE 85 ON FREE INFORMATION CARD

**SPEAKER CATALOG**

1001 bargains in electronics. Save up to 50% call toll free 1-800-346-2433 for ordering only. Order by VISA/MC/AMX. No COD's. Missouri, Alaska, Hawaii call 1-816-842-5092, or write McGee Radio, 1901 McGee St., K.C., MO 64108. Postage for catalog \$1.00.

### PICKS UP A WHISPER 50 FEET AWAY!

The model WAT-50 miniature FM transmitter uses a 4-stage circuit NOT to be confused with a simple wireless microphone. Simply snap the unit on top of a 9V battery and you can hear every sound in an entire house up to 1 mile away! Use with any FM radio. Tunes to any frequency from 70mhz - 130mhz. Easy to assemble kit includes all parts and instructions. Only 29.98 tax incl.



The **WIRELESS TELEPHONE TRANSMITTER** model WTT-20 is only about the size of a dime, yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Completely automatic. Uses power from the telephone line itself - never needs a battery! Up to 1/4 mile range. Tunes from 70mhz - 130mhz. Easy to assemble kit includes all parts and instructions. Only \$29.98 tax incl.

Call or send MO, VISA, MC for immediate delivery. Single kit orders include \$1.50 S&H. FREE SHIPPING on orders of 2 or more. All orders shipped by U.S. Mail. COD add \$4.00. Personal checks allow 21 days.

**DECO INDUSTRIES**  
BOX 607, BEDFORD HILLS, NY 10507  
914-232-2827

CIRCLE 80 ON FREE INFORMATION CARD

# MODERN ELECTRONICS MART

**Classified Commercial Rates:** 90¢ per word, 15-word minimum (\$13.50) prepaid. (Word count includes name and address, ZIP code and abbreviation each count as one word; P.O. Box number and telephone number count as two words each.) Indicate free category heading. A special heading is available for a \$6 surcharge. *First word only is set boldface caps* at no charge. Add 20% for additional boldface words.

**Mart Display Rates:** 1" x 1 col., \$120; 2" x 1 col., \$230; 3" x 1 col., \$330. Prepayment discount 5% for 6 issues; 10% for 12 issues prepaid at once.

(All advertisers with PO Box addresses must supply permanent address and telephone number. Copy is subject to publisher approval.)

**Mailing Information:** Copy must be received by the publisher by the 20th of the third month preceding the cover date. Send Advertising material with check or money order to: Modern Electronics, Classified Department, 76 N. Broadway, Hicksville, NY 11801.

## VIDEO

**SATELLITE DESCRAMBLING.** Latest methods of digital scrambling of the audio in satellite television transmissions. Covers sampling rates, pseudo-random data generation, and decoding. \$10.95; Design manual for constructing **PARABOLIC SATELLITE DISH ANTENNAS.** \$9.95. **CABLETRONICS,** Box 30502, Bethesda, MD 20814.

**PROJECTION TV . . .** Convert your TV to project 7 Foot picture . . . Results comparable to \$2,500 projectors . . . Total cost less than \$30.00 . . . Plans and 8" Lens \$21.95 . . . Illustrated information **FREE.** Macrocoma-MA Washington Crossing, Pennsylvania 18977. Creditcard orders 24 hours (215) 736-3979. Dealer Inquiries, (215) 736-2880.

**DISCOUNT CATV** Converters/Decoders and Video Accessories. Free information. Easy View, P.O. Box 221C, Arlington Heights, Illinois 60006. (312) 952-8504. Ask for Rudy Valentine.

**CABLE TV DESCRABLERS.** All brands available. "WE WON'T BE UNDER-SOLD." Dealer inquiries welcome. We ship C.O.D.'S. For catalog send \$3.00 to Consumer Video Corp., P.O. Box 913, Clifton Park, NY 12065. (518) 783-5636 M-F 9am-5pm EST.

**SATELLITE systems.** Catalog of 600+ discount name brand components \$2.00 (refundable) **MICROTRONICS,** Box 2517, Covina, CA 91722.

**UNSCRAMBLE** satellite signals the easy way. Parts available from Radio Shack. Send \$19.95 for plans & catalog, board & plans \$39.95, Kits from \$99.95. Vidio Research, PO Box 2, Kingsport, TN 37662.

**CABLE TV Secrets** - the outlaw publication the Cable Companies tried to Ban. HBO, Movie Channel, Showtime, Descramblers, Converters, etc. Suppliers list included. \$8.95. Cable Facts, Box 711-ME, Pataskala, OH 43062.

**WORLDS** best channel 3 notch filter. \$19.95. (Dealer inquiries invited). Crosley(G), Box 840, Champlain, N.Y. 12919.

**CABLE and SUBSCRIPTION TV** secret manual. Build your own **DESCRAMBLERS,** converters. Instructions, schematics for sine wave inband/outband gated sync SSAVI (HBO, Showtime, Cinemax, UHF, etc.). Send \$8.95 to **CABLETRONICS,** Box 30502ME, Bethesda, MD 20814.

**UNIVERSAL CRT Adapter.** Guaranteed to work with All CRT Testers. Test/Clean/Restore All B/W, Color/Scope/Projection CRT's. Chargecards, COD's. \$59.95 1-800-331-9658. Dandy Electronics, 2323 Gibson, Muskogee, OK 74403.

## ELECTRONICS

**FM TRANSMITTER KIT,** matchbox size, super sound sensitivity, adjustable frequency/gain. Board, parts, educational instructions, \$19.95. Pershing Technical, P.O. Box 1951, Fort Worth, Texas 76101.

**PICTURE** Flyer lists quality electronic surplus at low prices. Since 1970. Send for the last 3 issues. Star-Tronics, Box 683, McMinnville, OR 97128.

**TEKTRONIX** Clearance Sale on 530-540-550-580 series lab scopes. Prices start at \$100: Tek 547 dual-trace 50 MHz delayed—sweep incl. plug-in \$320 plus \$20 U.P.S. Free list. Sheldon M. Rubin, 117 W. Ridge St., Rye Brook, NY 10573 (914) 937-2535.

**TOROID** cores. Iron Powder and Ferrite. Ferrite beads. Ferrite rods. Free catalog and winding chart. Palomar Engineers, Box 455, Escondido, CA 92025. (619) 747-3343.

**SPECTRUM** Analyzer/Receiver Kits \$60. Send SASE for details. Science Workshop, Box 393ME, Bethpage, N.Y. 11714.


**TRIACS** - Prime RCA 100% tested. T4700D (400V 15A) . . . 10/\$7.50. T2700D (400V 6A) . . . 10/\$5.00. Shipping \$1.00. Use MC/VISA & Order Toll Free 800-821-5226 Extension 426. JIM RHODES, Inc.

**SPECTACULAR STROBE LIGHT CHASERS,** Stroboscopic Devices, High Voltage Supplies, Rare Scientific Items, Plans, Kits. Free Catalog. **ALLEGRO ELECTRONIC SYSTEMS,** #3 Mine Mountain, Cornwall Bridge, CT 06754.

**LOWEST POSSIBLE PRICES ANYWHERE!** FULL WARRANTY - Most Audio Brands!! C.D.'s - Car Products - Computers (Hardware - Software) - Most Video Brands!! **ELECTRIFIED DISCOUNTERS,** 996 Orange Ave., P.O. Box 151, West Haven, CT 06516, MC/VISA (203) 937-0106.

\$\$\$\$ Super Savings on electronic parts, components, supplies and computer accessories. Free 40-page catalog for SASE. Get on our mailing list. BCD ELECTRO, P.O. Box 830119, Richardson, TX 75083 or call 214-690-1102.

# ELECTRONIC SURPLUS COMPONENTS & GOOD STUFF
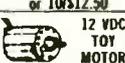
<b>MACHINE PIN SOCKET</b>  <b>22 PIN GOLD PLATED SOCKET</b> 5 Pcs. \$1.75 Stk. #CS-22M	<b>CIRCUIT BOARD BONANZA</b>  Sound generator boards removed from electronic pin-ball games. Contains oscillators, control circuits & 2 watt audio amp. Experimenter's dream!! \$2 ea - 10/12.50 w/schematics <b>5V &amp; 12V REGULATOR BOARD</b> Regulator board containing 5V & 12V to 220 regulators, fuses, bridges, caps & I/O connectors. Size 2"x4" w/heatinks. REG-512 ..... \$3.50 <b>RECTIFIER BOARD</b> Contains (4) 10 Amp bridges, (3) large filter caps, & I/O conn. Size 4.5" x 8" BRDG-4 ..... \$2.50 ea or 10/\$12.50 <b>LINEAR &amp; CMOS BONANZA</b> Circuit board removed from SINGER electronic calculators. Has 20 linear & CMOS IC's & a wealth of other parts. BD-20 ..... \$2.50 ea or 10/\$12.50  12 VDC TOY MOTOR Stk. #MO-12 ..... 2/\$1.00	<b>SURPLUS LASERS</b> <b>LASER-80</b> Frequency Case Price 40 MHZ HC18 ..... \$1.25 60 MHZ HC18 ..... \$1.25 10 MHZ HC18 ..... \$1.25 10 7MHZ HC18 ..... \$7.75 14 318MHZ HC18 \$1.25	<b>CRYSTALS</b>  Frequency Case Price 40 MHZ HC18 ..... \$1.25 60 MHZ HC18 ..... \$1.25 10 MHZ HC18 ..... \$1.25 10 7MHZ HC18 ..... \$7.75 14 318MHZ HC18 \$1.25	<b>VOLTAGE REGULATORS</b> 7805 5V 1.5amp 7812 12v 1.5amp 7824 24v 1.5amp 7905 5v 1.5amp 7905 5v 1.5 amp 7912 12v 1.5 amp <b>\$4.3 EACH</b>	<b>VOLKES MODEM</b> <b>300 BAUD</b> <b>\$24.95</b>	<b>AT CRYSTAL</b> <b>18 MEG</b> <b>\$3.50</b>	<b>ELECTRONIC PIEZO DEEP BUZZER</b> Special - 2/\$1.00 7/8" Diameter element on pleasing mounting. Originally used in Radio Shack telephone as the ring. Stk. #PZ-78 ..... \$7.75	<b>COMMODORE PRINTER/PLOTTER FITS ALL MODELS</b> <b>\$49.95</b>	<b>BUILD YOUR OWN EPROM ERASER</b> <b>115VAC BLACK LIGHT (ULTRA VIOLET)</b> 115 volt ultra violet light, with lamp, ballast and in-line cord switch. Just build enclosure to finish. Stk. #EPE-125 ..... \$12.50 <b>TI COMPUTER FLOPPY DRIVE CABLES</b> <b>SINGLE FLOPPY DRIVE CABLE</b> Cable is 15" long with 34 pin card edge & 34 pin header conn. CFS-15 ..... \$2.00 ea or 10/\$14 <b>DUAL FLOPPY CABLE</b> Cable is 34" long w/34 pin edge connectors. CFS-30 ..... \$4.00 ea or 10/\$25 <b>POWER SUPPLY MFG. BY GENERAL INSTR.</b> Input: 110VAC Output: +5VDC @ 5Amps +12VDC @ 2.5Amps -12VDC @ 3Amps PS-120 ..... \$19.95 Used in some Commodore comp. <b>WALL PLUG ADAPTERS</b> 6VDC @ 300ma \$1.75 or 10/\$12.50 <b>ISOLATION TRANSFORMER</b> 117VAC 117VAC @ 125VAC Mtg. by Signal Trans \$3.00 each - 10/\$20.00 <b>RIGHT ANGLE HEADERS</b> 40 pin ..... \$4.00 34 pin ..... \$5.00 10 pin ..... \$2.25 <b>TRANSFORMERS</b> STK.# P/N Secondary Price (VAC) (VAC) TN-6 3 117 6.3 @ 300ma ..... \$1.25 TN-12 117 12 @ 400ma ..... \$1.35 TN-24A 117 24 @ 200ma ..... \$1.25 TN-24B 117 24ct. @ 3.6 Amp ..... \$3.50																																																																																																																														
<b>ROCKER SWITCH</b> 16 Amp On/Off Used in Xerox 820 Computers \$7.75	Full Wave Bridge <b>GAMP-300V</b> 2/\$1.00	<b>IC BARGAINS</b> L300 ..... \$1.15 L3122 ..... \$4.2 L3240 ..... \$8.00 L301 ..... \$1.15 L3124 ..... \$1.40 L3241 ..... \$8.00 L302 ..... \$1.15 L3125 ..... \$3.30 L3242 ..... \$8.00 L303 ..... \$1.15 L3126 ..... \$4.40 L3243 ..... \$8.00 L304 ..... \$1.15 L3127 ..... \$4.40 L3244 ..... \$8.00 L305 ..... \$1.15 L3133 ..... \$2.75 L3245 ..... \$8.00 L306 ..... \$1.15 L3134 ..... \$2.75 L3251 ..... \$4.45 L309 ..... \$1.15 L3139 ..... \$3.30 L3253 ..... \$4.40 L310 ..... \$1.15 L3145 ..... \$5.5 L3257 ..... \$4.45 L311 ..... \$1.15 L3151 ..... \$4.40 L3258 ..... \$4.40 L312 ..... \$2.25 L3153 ..... \$3.30 L3260 ..... \$11.00 L313 ..... \$3.30 L3154 ..... \$4.40 L3262 ..... \$4.40 L314 ..... \$2.25 L3154 ..... \$7.75 L3266 ..... \$3.30 L315 ..... \$3.30 L3156 ..... \$4.40 L3273 ..... \$7.75 L320 ..... \$1.15 L3157 ..... \$3.30 L3279 ..... \$3.30 L321 ..... \$1.10 L3158 ..... \$4.40 L3280 ..... \$8.00 L327 ..... \$2.25 L3160 ..... \$5.50 L3290 ..... \$4.45 L328 ..... \$2.25 L3161 ..... \$4.40 L3293 ..... \$7.75 L332 ..... \$2.25 L3161 ..... \$4.40 L3293 ..... \$7.75 L333 ..... \$2.25 L3162 ..... \$6.60 L3298 ..... \$4.45 L337 ..... \$3.30 L3163 ..... \$7.75 L3299 ..... \$15.00 L338 ..... \$2.25 L3164 ..... \$5.50 L3322 ..... \$2.50 L340 ..... \$2.25 L3165 ..... \$8.00 L3323 ..... \$2.25 L342 ..... \$3.30 L3166 ..... \$7.75 L3364 ..... \$8.00 L351 ..... \$2.20 L3169 ..... \$11.00 L3366 ..... \$4.40 L354 ..... \$2.25 L3174 ..... \$3.30 L3367 ..... \$4.40 L355 ..... \$2.20 L3175 ..... \$3.30 L3368 ..... \$3.30 L373 ..... \$3.30 L3181 ..... \$1.25 L3373 ..... \$5.50 L374 ..... \$2.25 L3191 ..... \$8.00 L3374 ..... \$7.75 L385 ..... \$4.45 L3192 ..... \$7.70 L3375 ..... \$3.25 L386 ..... \$1.19 L3193 ..... \$7.74 L3377 ..... \$3.30 L389 ..... \$5.50 L3194 ..... \$6.60 L3378 ..... \$4.40 L3107 ..... \$2.28 L3195 ..... \$9.00 L3380 ..... \$8.00 L3109 ..... \$2.20 L3196 ..... \$7.70 L3383 ..... \$7.75 L3112 ..... \$3.30 L3197 ..... \$7.75 L3399 ..... \$11.00 L3122 ..... \$3.35 L3221 ..... \$5.50 L3670 ..... \$1.24	<b>HEAT-SHRINK TUBING</b> <b>100'</b> 5/8" = \$15.00 3/8" = \$10.00	<b>COMPUTER RUBBER FEET</b> <b>4/\$2.00</b>	<b>NEC 3500 40 CPS SERIAL PRINTER "REBUILT" PRINTER</b> <b>\$550</b>	<b>ULTRAVIOLET TUBES GOOD FOR EPROM ERASERS</b> 110 VAC \$2.25 ea. - 10/\$15.00	<b>POWER SUPPLY</b> General purpose compact power supply. 3 outputs: +5V @ 1 Amp. & +12V @ 1 Amp. & +24V @ 1 Amp. Power Transistors mounted on a heat sink. 2"x4" w/transformer. Stk. #PS-3P ..... \$4.49	<b>WATER CABLE CONVERTER</b> Model No. TC-1M Converter. Both Mid-Band & VHF frequencies. Has built in power supply. Units are new & in working cond. Stk. #TC-1M ..... \$9.95	<b>1000 PRECISE RESISTOR ASS'T ALL SIZES &amp; VALUES</b> Stk. #RES-1000 ..... \$3.00 <b>9 conductor Spectrastrip with red marker strip.</b> 250' per roll. WRIB-9 stranded wire. WRIB-9 ..... \$10/roll <b>20 conductor spectrastrip with red marker stripe.</b> 100' per roll. 28ga. stranded wire. WRIB-20 ..... \$30/roll. or WRIB-20 ..... \$25/roll <b>CPM DISK For V20 CHIP</b> \$3.75 <b>DISKETTE LOOSE LEAF HOLDER</b> Vinyl Diskette Holder Holds 2-5/4" diskettes. Has 3 hole punch to mount in standard loose leaf folder. Stk. #VIN-5 ..... 10/\$2.50 For standard 8 1/2"x11																																																																																																																														
<b>RIGHT ANGLE TOGGLE SPDT 10/\$3.00</b>	<b>SNAP ACTION SWITCH</b>  <b>MICRO-SWITCH ASS'T OF 10</b> \$2.50 Stk. #SO-10M	<b>NEW! MILTON BRADLEY XFMR.</b> Input: 120VAC Output: 12VAC CT @ 1.7AMP UL Approved Stk. #TN4243-33 \$4.95	<b>6845 VIDEO CHIP</b> <b>\$4.50</b>	<b>EPROM</b> 2716 ..... \$2.00 2532 ..... \$2.75 2732 ..... \$2.25 2764 ..... \$2.75 27128 ..... \$4.50	<b>COMPUTER GRADE CAPACITORS</b> Ass't of 10 Stk. #CC-10 ..... \$2.50	<b>COMPUTER CHESS GAME</b>  <b>MILTON BRADLEY CHESS GAME</b> Electronic circuit board removed from famous toy maker's game. Board has 6502 processor, 74LS series IC's, buzzer & many other useful components. Boards are complete and un-damaged. MB part #7924243001. BD-792 ..... \$3.95 ea. 10/\$24	<b>RIBBON CABLE</b>  9 conductor Spectrastrip with red marker strip. 250' per roll. WRIB-9 stranded wire. WRIB-9 ..... \$10/roll 20 conductor spectrastrip with red marker stripe. 100' per roll. 28ga. stranded wire. WRIB-20 ..... \$30/roll. or WRIB-20 ..... \$25/roll	<b>OUTDOOR SPEAKER HORN</b> Stk. #Spr-60 ..... \$6.95	<b>XEROX 1810 CPM BOOT DISK</b> \$3.75 <b>PLASTIC ENCLOSURE</b> 2"x3"x4" ..... \$1.75 <b>STANDARD 6' 3 PRONG LINE CORD</b> \$4.00 #CRD 6 <b>DIABLO TYPE 30 POWER SUPPLIES</b> 115VE 8amps \$15.00 <b>ALTOS 8000 COMP.</b> \$250 <b>100 PC ASSORTMENT RF COILS</b> \$3.50 <b>COILED CORD BONANZA</b> 4 conductor coiled cord. Black vinyl jacket. Extends to 6 ft. No connectors on either end. Stk. #CC-000 ..... 3/\$1.00 4 conductor coiled cord. Black vinyl jacket. Extends to 6 ft. Phone connector on one end and no connector on the other. Stk. #CC-020 ..... 2/\$1.00 4 conductor coiled cord. Grey vinyl jacket. Extends to 6 ft. Used as keyboard cable. Phone jack to 5 pin din connector. Stk. #CC-100 ..... \$4.00																																																																																																																														
<b>COMPUTER POWER CORDS</b> BD-20 ..... \$2.50 ea or 10/\$12.50 \$1.75 EA - 10/\$12.50	<b>GIANT CAPACITOR ASSORTMENT</b> 500 PCS. \$9.95	<b>COMPUTER CHESS GAME</b> \$1.75	<b>SPECIAL TRANSISTOR SALE STK. #T-500</b> 500 PC 2N2222 Un-Marked - \$3.50	<b>EDGE CONNECTORS</b> ALL ARE 1.56" SPACING. 22/44 EDGE CONNECTOR  \$2.00 31/62 Connector for IBM PC Board. 1" spacing ..... \$2.50	<b>8-PIN HEADER STRIP</b> Stk. #HDR-8 \$1.5 EACH	<b>HOOK-UP WIRE ASS'T</b> 6 SPOOTS OF 50' - \$3.00 #WIR-30H	<b>SMALL COMPUTER QUALITY CAPS</b> CERAMIC NONVOLATILE CAPS. FOR ALL TYPES OF COMPUTER APPLICATIONS. ULTRA STABLE PART # NFB. VOLTS COST CMO-103 -.01 50 -10 CMO-473 -.047 50 -11 CMO-104 -.1 50 -12	<b>12 VAC @ 250ma TRANSFORMER</b> TN12A \$11.50	<b>WIRE TEST PROBE WIRE</b> 18 Gauge rubber coated. Red, black, white or blue. .... 100'/\$13 <b>HOOK-UP WIRE</b> 24 Gauge standard cond. 22 Gauge solid conductor, your choice 100'/\$2 WIRE WRAP WIRE 30 Gauge solid cond. Choice of colors. Wlr-30 ..... 100'/\$2.50																																																																																																																														
<b>ELECTRONIC COMPONENT BONANZA</b>																																																																																																																																							
<table border="1"> <thead> <tr> <th>STOCK#</th> <th>DESCRIPTION</th> <th>PRICE</th> </tr> </thead> <tbody> <tr><td>Res20</td><td>Power res. assort. 20pcs</td><td>\$2.29</td></tr> <tr><td>Res100</td><td>Precision res. assort. 1% &amp; 2% types 100 pcs.</td><td>\$2.59</td></tr> <tr><td>Res1000</td><td>Res assort. 1000pcs. All sizes &amp; values</td><td>\$3.25</td></tr> <tr><td>Rel100p</td><td>100 miniature trim pots. pc mount</td><td>\$4.79</td></tr> <tr><td>Res25p</td><td>25 tv and radio pots. Good selection</td><td>\$2.79</td></tr> <tr><td>Res25g</td><td>25 ganged pots. Hard to find types</td><td>\$3.25</td></tr> <tr><td>Ch35</td><td>Miniature choke coils. 35pcs. many values</td><td>\$2.79</td></tr> <tr><td>Ch15</td><td>Slug tuned if coils. 15 pcs.</td><td>\$2.29</td></tr> <tr><td>Ch20</td><td>Open wound tuning coils. 20pcs.</td><td>\$2.29</td></tr> <tr><td>Ch10</td><td>Transimr style choke. 60mh. 10 pcs.</td><td>\$2.29</td></tr> <tr><td>Cp100</td><td>100pc. electrolytic assort. Great values</td><td>\$3.37</td></tr> <tr><td>Cp100d</td><td>Ceramic disc caps. 100pcs. great values</td><td>\$2.59</td></tr> <tr><td>Cp25hv</td><td>High voltage disc caps. 1Kv min. 25 pcs.</td><td>\$2.79</td></tr> <tr><td>Cp25p</td><td>25pcs. polystyrene caps. high stability</td><td>\$1.79</td></tr> <tr><td>Cp685</td><td>Nichicon 6800mf @50v. 12 pcs.</td><td>\$2.75</td></tr> <tr><td>*Cp316</td><td>Meppco 3000mf @16v. low est 12 pcs.</td><td>\$3.75</td></tr> <tr><td>Cp12s</td><td>Mallory low est switching caps. 10pcs.</td><td>\$3.75</td></tr> <tr><td>Cp100ma</td><td>100 mylar bypass &amp; coupling caps. Axial</td><td>\$3.75</td></tr> <tr><td>Cp100mr</td><td>100 mylar bypass &amp; coupling caps. Radial</td><td>\$4.25</td></tr> <tr><td>Cp25t</td><td>Tantalum assortment. 25pcs.</td><td>\$3.55</td></tr> <tr><td>Cp25dm</td><td>25pc. dipped mica cap. assortment</td><td>\$2.79</td></tr> <tr><td>Cp13cg</td><td>Mallory computer grade caps. 13pcs.</td><td>\$4.79</td></tr> <tr><td>Dh100g</td><td>100 germanium diodes. in34 etc.</td><td>\$2.25</td></tr> <tr><td>Dh100s</td><td>100 silicon diodes. in4148 types, etc.</td><td>\$2.25</td></tr> <tr><td>Dh15p</td><td>15pcs. power diodes 2 amps &amp; above</td><td>\$2.75</td></tr> <tr><td>Q50m</td><td>50 Magnavox tv replacement transistors</td><td>\$3.79</td></tr> <tr><td>Q100a</td><td>100 small signal transistors. Pnp &amp; npn</td><td>\$4.79</td></tr> <tr><td>Q150r</td><td>150 rt transistors. Metal can, unmarked</td><td>\$1.79</td></tr> <tr><td>Q10p</td><td>T0 220 power transistors. 10pcs. pnp &amp; npn</td><td>\$2.29</td></tr> <tr><td>F3</td><td>6 inline fuse holder w/3amp fuse, 3 pcs</td><td>\$2.99</td></tr> <tr><td>Ch10</td><td>10 airpax circuit breakers. 3 to 25amps</td><td>\$4.49</td></tr> <tr><td>Cn30dm</td><td>30pc. moxlex connector &amp; socket assortment</td><td>\$3.49</td></tr> <tr><td>Bs25</td><td>25pc. barrier strip assort. 2 to 20 connects</td><td>\$2.55</td></tr> <tr><td>Wr100</td><td>100' connecting &amp; hook-up wire. All gauges</td><td>\$2.25</td></tr> <tr><td>Xo3</td><td>3 pcs. speaker crossover networks</td><td>\$1.59</td></tr> <tr><td>Sp2</td><td>Pair of 6x9 car speakers</td><td>\$4.79</td></tr> <tr><td>Rel10</td><td>10pc. relay assortment. Ac &amp; dc types</td><td>\$3.79</td></tr> <tr><td>Jk25</td><td>25pc. audio jack &amp; connector assort.</td><td>\$2.59</td></tr> <tr><td>Sw25</td><td>Slide switch assortment. many sizes. 25 pcs.</td><td>\$2.59</td></tr> <tr><td>Sk16</td><td>100pcs. 16 pin IC sock. Staggered pins</td><td>\$2.25</td></tr> <tr><td>Sk14</td><td>100 pcs. 14 pin IC sock. Staggered pins</td><td>\$2.25</td></tr> </tbody> </table>	STOCK#	DESCRIPTION	PRICE	Res20	Power res. assort. 20pcs	\$2.29	Res100	Precision res. assort. 1% & 2% types 100 pcs.	\$2.59	Res1000	Res assort. 1000pcs. All sizes & values	\$3.25	Rel100p	100 miniature trim pots. pc mount	\$4.79	Res25p	25 tv and radio pots. Good selection	\$2.79	Res25g	25 ganged pots. Hard to find types	\$3.25	Ch35	Miniature choke coils. 35pcs. many values	\$2.79	Ch15	Slug tuned if coils. 15 pcs.	\$2.29	Ch20	Open wound tuning coils. 20pcs.	\$2.29	Ch10	Transimr style choke. 60mh. 10 pcs.	\$2.29	Cp100	100pc. electrolytic assort. Great values	\$3.37	Cp100d	Ceramic disc caps. 100pcs. great values	\$2.59	Cp25hv	High voltage disc caps. 1Kv min. 25 pcs.	\$2.79	Cp25p	25pcs. polystyrene caps. high stability	\$1.79	Cp685	Nichicon 6800mf @50v. 12 pcs.	\$2.75	*Cp316	Meppco 3000mf @16v. low est 12 pcs.	\$3.75	Cp12s	Mallory low est switching caps. 10pcs.	\$3.75	Cp100ma	100 mylar bypass & coupling caps. Axial	\$3.75	Cp100mr	100 mylar bypass & coupling caps. Radial	\$4.25	Cp25t	Tantalum assortment. 25pcs.	\$3.55	Cp25dm	25pc. dipped mica cap. assortment	\$2.79	Cp13cg	Mallory computer grade caps. 13pcs.	\$4.79	Dh100g	100 germanium diodes. in34 etc.	\$2.25	Dh100s	100 silicon diodes. in4148 types, etc.	\$2.25	Dh15p	15pcs. power diodes 2 amps & above	\$2.75	Q50m	50 Magnavox tv replacement transistors	\$3.79	Q100a	100 small signal transistors. Pnp & npn	\$4.79	Q150r	150 rt transistors. Metal can, unmarked	\$1.79	Q10p	T0 220 power transistors. 10pcs. pnp & npn	\$2.29	F3	6 inline fuse holder w/3amp fuse, 3 pcs	\$2.99	Ch10	10 airpax circuit breakers. 3 to 25amps	\$4.49	Cn30dm	30pc. moxlex connector & socket assortment	\$3.49	Bs25	25pc. barrier strip assort. 2 to 20 connects	\$2.55	Wr100	100' connecting & hook-up wire. All gauges	\$2.25	Xo3	3 pcs. speaker crossover networks	\$1.59	Sp2	Pair of 6x9 car speakers	\$4.79	Rel10	10pc. relay assortment. Ac & dc types	\$3.79	Jk25	25pc. audio jack & connector assort.	\$2.59	Sw25	Slide switch assortment. many sizes. 25 pcs.	\$2.59	Sk16	100pcs. 16 pin IC sock. Staggered pins	\$2.25	Sk14	100 pcs. 14 pin IC sock. Staggered pins	\$2.25	<b>COMPUTER CHESS GAME</b> \$1.75 <b>DISKETTE LOOSE LEAF HOLDER</b> Vinyl Diskette Holder Holds 2-5/4" diskettes. Has 3 hole punch to mount in standard loose leaf folder. Stk. #VIN-5 ..... 10/\$2.50 For standard 8 1/2"x11	<b>31/62 Connector for IBM PC Board. 1" spacing</b> \$2.50	<b>4" COOLING FAN</b> 120 VAC NEW Stk. # FN-4 - \$6.50	<b>MAGNETS</b> 2" Bar Magnet with Tape On One Side 2/\$1.00	<b>POWER SUPPLY</b> 5V @ 35 AMP \$45.00	<b>12 VOLT MINIATURE PC BOARD RELAY</b>  SPOT #REL-12Y \$1.25	<b>TV-GAME SWITCH</b> \$6.5 EACH OR 10/\$4.25	<b>RADIO SHACK BROKEN BOARDS TRS-80 MOD III</b> 5/\$10.00	<b>TOCOM 55 PLUS CABLE TV CONVERTER</b> 55 CHANNEL CONVERTER Mainboard - \$7.50 Power supp. - \$4.50 No Return & Long Delivery on These Cable Converters, Best Buy!
STOCK#	DESCRIPTION	PRICE																																																																																																																																					
Res20	Power res. assort. 20pcs	\$2.29																																																																																																																																					
Res100	Precision res. assort. 1% & 2% types 100 pcs.	\$2.59																																																																																																																																					
Res1000	Res assort. 1000pcs. All sizes & values	\$3.25																																																																																																																																					
Rel100p	100 miniature trim pots. pc mount	\$4.79																																																																																																																																					
Res25p	25 tv and radio pots. Good selection	\$2.79																																																																																																																																					
Res25g	25 ganged pots. Hard to find types	\$3.25																																																																																																																																					
Ch35	Miniature choke coils. 35pcs. many values	\$2.79																																																																																																																																					
Ch15	Slug tuned if coils. 15 pcs.	\$2.29																																																																																																																																					
Ch20	Open wound tuning coils. 20pcs.	\$2.29																																																																																																																																					
Ch10	Transimr style choke. 60mh. 10 pcs.	\$2.29																																																																																																																																					
Cp100	100pc. electrolytic assort. Great values	\$3.37																																																																																																																																					
Cp100d	Ceramic disc caps. 100pcs. great values	\$2.59																																																																																																																																					
Cp25hv	High voltage disc caps. 1Kv min. 25 pcs.	\$2.79																																																																																																																																					
Cp25p	25pcs. polystyrene caps. high stability	\$1.79																																																																																																																																					
Cp685	Nichicon 6800mf @50v. 12 pcs.	\$2.75																																																																																																																																					
*Cp316	Meppco 3000mf @16v. low est 12 pcs.	\$3.75																																																																																																																																					
Cp12s	Mallory low est switching caps. 10pcs.	\$3.75																																																																																																																																					
Cp100ma	100 mylar bypass & coupling caps. Axial	\$3.75																																																																																																																																					
Cp100mr	100 mylar bypass & coupling caps. Radial	\$4.25																																																																																																																																					
Cp25t	Tantalum assortment. 25pcs.	\$3.55																																																																																																																																					
Cp25dm	25pc. dipped mica cap. assortment	\$2.79																																																																																																																																					
Cp13cg	Mallory computer grade caps. 13pcs.	\$4.79																																																																																																																																					
Dh100g	100 germanium diodes. in34 etc.	\$2.25																																																																																																																																					
Dh100s	100 silicon diodes. in4148 types, etc.	\$2.25																																																																																																																																					
Dh15p	15pcs. power diodes 2 amps & above	\$2.75																																																																																																																																					
Q50m	50 Magnavox tv replacement transistors	\$3.79																																																																																																																																					
Q100a	100 small signal transistors. Pnp & npn	\$4.79																																																																																																																																					
Q150r	150 rt transistors. Metal can, unmarked	\$1.79																																																																																																																																					
Q10p	T0 220 power transistors. 10pcs. pnp & npn	\$2.29																																																																																																																																					
F3	6 inline fuse holder w/3amp fuse, 3 pcs	\$2.99																																																																																																																																					
Ch10	10 airpax circuit breakers. 3 to 25amps	\$4.49																																																																																																																																					
Cn30dm	30pc. moxlex connector & socket assortment	\$3.49																																																																																																																																					
Bs25	25pc. barrier strip assort. 2 to 20 connects	\$2.55																																																																																																																																					
Wr100	100' connecting & hook-up wire. All gauges	\$2.25																																																																																																																																					
Xo3	3 pcs. speaker crossover networks	\$1.59																																																																																																																																					
Sp2	Pair of 6x9 car speakers	\$4.79																																																																																																																																					
Rel10	10pc. relay assortment. Ac & dc types	\$3.79																																																																																																																																					
Jk25	25pc. audio jack & connector assort.	\$2.59																																																																																																																																					
Sw25	Slide switch assortment. many sizes. 25 pcs.	\$2.59																																																																																																																																					
Sk16	100pcs. 16 pin IC sock. Staggered pins	\$2.25																																																																																																																																					
Sk14	100 pcs. 14 pin IC sock. Staggered pins	\$2.25																																																																																																																																					

**LOLIR ELECTRONICS**  
 13933 NO. CENTRAL #212  
 DALLAS, TX 75243

214-234-8032  
 214-234-8091  
 214-234-8105

TERMS: Check or Money Order. COD's Add \$1.90. TX Res. add 6% Tax. Please add \$3.50 shipping. All out of stock items will be refunded.

CIRCLE 65 ON FREE INFORMATION CARD





# COMB

Authorized Liquidator

## FLOPPY DISKS



- 100% certified error free!
- 5 1/4" double sided, double density.
- Meets ANSI Standards!
- As low as 59¢ each!
- Manufacturer's Limited Lifetime Warranty.

We are able to offer these top quality disks at **BELOW dealer cost** because of a big savings on a huge quantity purchase from the maker. These disks are compatible with most IBM, Apple®, Commodore, and many other personal computers.

Includes protective jackets, write protect tabs, adhesive use labels. Stock up NOW!

### 20 DISK PACKAGE:

Mfr. List: ~~\$71.98~~ **\$19**  
Liquidation Price . . . . .  
Item H-1493-3475-001 Ship, handling: \$3.00

### 100 DISK PACKAGE:

Mfr. List: ~~\$359.90~~ **\$59**  
Liquidation Price . . . . .  
Item H-1493-3475-019 Ship, handling: \$7.00

Credit card customers can order by phone,  
24 hours a day,  
7 days a week.



**Toll-Free: 1-800-328-0609**

Your check is welcome!  
No delays in orders paid by check.

Sales outside the 48 contiguous states are subject to special conditions. Please call or write to inquire.

C.O.M.B. Direct Marketing Corp. Item H-1493  
1405 N. Xenium Lane/Minneapolis, MN 55441-4494

Send the following items. (Minnesota residents add 6% sales tax. Sorry, no C.O.D. orders.)

Send 20 Disk Package(s) Item H-1493-3475-001 at \$19 each plus \$3 each for shipping, handling per package.

Send 100 Disk Package(s) Item H-1493-3475-019 at \$59 each plus \$7 each for shipping, handling per package.

My check or money order is enclosed. (No delays in processing orders paid by check, thanks to TeleCheck.)  
Charge:  VISA®  MasterCard®  American Express®

Acct. No. \_\_\_\_\_ Exp. \_\_\_\_\_

PLEASE PRINT CLEARLY

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ ZIP \_\_\_\_\_

Phone (\_\_\_\_) \_\_\_\_\_

Sign Here \_\_\_\_\_

# COMB

Direct Marketing Corp.

Authorized Liquidator

1405 N. Xenium Lane  
Minneapolis, Minnesota 55441-4494


## NEW PRODUCTS . . . (from page 15)

Four basic lessons are included in the educational material. These include basic atomic theory and electron flow; how to use the solderless breadboarding socket; component identification and schematic symbols; and how to read the resistor color code.

CIRCLE 28 ON FREE INFORMATION CARD
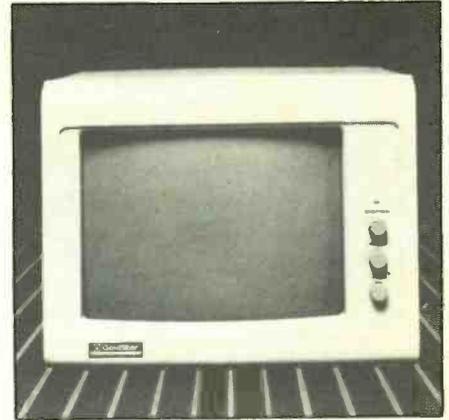
### High-Resolution VDM

Goldstar's new Model MBH-2003 12" amber-screen video display monitor is said to provide a 1100-line resolution at screen center, displaying 25 lines of up to 132 text characters per line. The high-resolution monitor features an anti-glare screen and a cabinet to match the IBM PC. Input to the VDM is composite video,



which makes it compatible with any computer that has a composite output. Additional features include power, brightness and contrast controls. The MBH-2003 measures 13.8"W x 12.6"H x 10.9"D. \$185.

CIRCLE 9 ON FREE INFORMATION CARD



### FAX Converter/Printer

New from Universal Electronics Inc. (Columbus, OH) is the Model DES M-800 facsimile converter that allows the user to capture quality photos and graphics using a dot-matrix printer. The microprocessor-controlled converter connects to the audio output of any good AM or FM communications or satellite receiver. The audio is then converted into graphics data that is printed out on most Epson parallel dot-matrix printers. Print size is 8" wide by as long as needed with a 1:1 aspect ratio. Photos are reproduced in 16 levels of gray.

To use the M-800, one simply tunes the receiver for maximum FAX signal level on the product's "tune" indicator and then selects the appropriate speed. The M-800 then automatically synchronizes and starts printing the picture with a resolution up to 120 dpi, 180 to 220 line pitch. Printing can be left to right or right to left at the user's option, in negative or positive format. An FM mode allows printing of all satellite transmitted weather facsimile, marine facsimile and worldwide news photo services. \$599.

CIRCLE 48 ON FREE INFORMATION CARD

# COMPUTERS AT WHOLESALE

## SMARTTEAM MODEM



103/212A-Operates at 300 BAUD and 1200 BAUD  
 •BELL 103 and 212A compatible  
 •HAYES compatible  
 •Auto answer, dial and redial  
 •External speaker for monitoring calls  
 •AC adapter supplied  
 Uses RS 232-C Connector.

No. 91990 ..... **\$165<sup>00</sup>**

## COLOR GRAPHICS BOARD

RGB and Composite Port, Light Pen interface, Graphics 320 x 200 (color), 640 x 200 (BW), Text 25 x 80. FCC Approved.

No. 92280 ..... **\$69<sup>00</sup>**

## MULTI I/O CARD

Built-in Floppy Controller that can drive 2 floppy drives. Two RS 232 serial adapters, Timer Port, Parallel printer port, joystick adapter. FCC Approved.

No. 96770 ..... **\$88<sup>00</sup>**

## BASIC TURBO SYSTEM

COMPARE OUR BASIC SYSTEM TO OTHERS & SAVE!



### OURS

- 8mhz "super" Mother Board
- 256K of memory installed
- Mother Board expandable to 1024K
- 150-watt power supply
- Deluxe keyboard with large return key
- Full warranty on all products
- Built-in clock & game I/O port
- MS-DOS and GW-Basic, fully licensed

### THEIRS

- Slower 4.77mhz Mother Board
- No memory included
- Only 256K capacity Mother Board
- Less powerful 135-watt power supply
- Standard keyboard with inconvenient small return key
- Not included
- Not included

### INCLUDES:

- Super-fast 8mhz Mother Board, Expandable to 1024K with 256K Installed
- Built-in Clock and Game I/O Port
- 150-Watt Power Supply
- IBM® AT-Looklike Case with Key Lock
- MS-DOS and GW Basic
- IBM® -Style Keyboard with Large Return Key
- FCC Approval
- Manual and System Packing Box

No. 99111 ..... **\$438<sup>00</sup>**

CIRCLE 39 ON FREE INFORMATION CARD

## KEYBOARDS



K150M—AT-look-alike keyboard, made exclusively for XT's, with enlarged return key, cap lock & num lock. FCC Approved.

No. 99020 ..... **\$59<sup>00</sup>**  
 K-134—features separate numerical & cursor pads/ function keys along top, LED cap lock & num lock. FCC Approved.  
 No. 51515 ..... **\$76<sup>00</sup>**

## MAGNAVOX COLOR MONITOR



•RGB High resolution •13" diagonal •640 dots/H-240 lines/V-2000 characters •80 column •FCC Approved.

No. 97890 ..... **\$298<sup>00</sup>**

## POWER OUTLET STRIP




6 outlets with 15 amp surge protector & 6' cord. Protect your computer investment!

No. 90140 ..... **\$9<sup>95</sup>**

## SATELLITE T.V.

## IMPORT SPECIALS

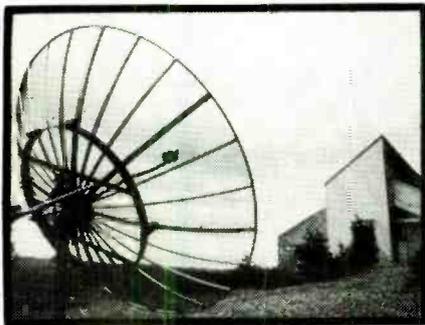

SYSTEM "AA"  
**PORTABLE SATELLITE SYSTEM**  
 ONLY 15 MINUTES SET-UP TIME!

INCLUDES:

- 5 ft. Aztec spun aluminum antenna w/patio mount
- Brand-name receiver
- 100° LNA
- Feedhorn
- 100 ft. hook-up cable

Antenna can be hung on wall for storage!  
**COMPLETE SYSTEM**

ONLY **\$377<sup>00</sup>**  
 SAVE OVER \$600!!!

SPCL09

## MULTI-NAIL DRIVER



4-in-1 nail driver includes 4 sockets — nail driver, screwdriver, socket wrench and nail puller  
 Nationally Advertised at \$4.99.

92180 ..... **\$125**  
 "AS SEEN ON TV"

## TRAVEL ALARM



LCD travel alarm clock mounted in a snap-up wallet for use on the road!

Suggested Retail \$12.99.  
 94020 ..... **\$230**

## STROSEM 6"x9" CAR SPEAKERS



Hi-energy 3-way speaker pair with 40-oz. magnet for rear deck mounting.

Suggested Retail \$50.00/pr.  
 23010 ..... **\$775** pair

## CAR STEREO EQUALIZERS



Slim-design car stereo equalizers with built-in power booster, LED power indicators, fader, and 100-200 watts maximum power output.  
 Suggested Retail \$70.00

22330 ..... 7 band ..... **\$985**  
 22350 ..... 10 band ..... **\$1225**

Telko

## EXPENSE TABULATOR

NEW INNOVATION

Calculates and records expenses while you travel! Features 16 expense categories, detachable thermal printer, full-function memory, and expense error correction key.  
 Nationally Advertised at \$129.95.

96910 ..... **\$59<sup>00</sup>**

SANYO

## SOLAR CALCULATOR



Solar-powered wallet-type calculator never needs batteries. features LCD display, independent memory, and includes wallet.

Suggested Retail \$16.95.  
 11230S ..... **\$325**



# THE WHOLESALE OUTLET

1 INTERSTATE AVENUE, DEPT. ME, ALBANY NEW YORK 12205

CALL TOLL FREE: 1-800-344-4387 (NON-NYS) ALL OTHER CALLS AND NYS 518-459-7883. CALL FOR CATALOG WITH HUNDREDS OF PRODUCTS! ALL ORDERS SHIPPED FOB ALBANY. CUSTOMER PAYS FREIGHT AND HANDLING. ALL OTHER ORDERS SHIPPED UPS COD (CASH, MONEY-ORDERS OR CASHIER'S CHECK ONLY). MINIMUM ORDER \$25. PRICES SUBJECT TO CHANGE WITHOUT NOTICE. WE ARE NOT RESPONSIBLE FOR TYPOGRAPHICAL ERRORS. SOME ITEMS NOT AS PICTURED.

CIRCLE 40 ON FREE INFORMATION CARD



# SCOPE 3½ DIGIT LCD MINI-METER WITH THE MAXI-SPECS

Small enough to fit in your shirt pocket

**ONLY \$29.95**  
Model DVM-630

Model CC-30 Deluxe  
Zippered Carrying Case \$4.50

- 0.5% DC accuracy
- 6 Functions, 19 Ranges
  - DC Voltage, 0.1 mV to 1000 V
  - DC Current, 0.1 uA to 2A
  - Resistance, 0.1 ohm to 2 M ohm
  - Diode Test
  - Battery Test
- Measures approx. 5 x 2¼ x 7/8 in.
- 300 hour battery life
- Automatic zero adjust
- Low battery indication
- Test leads included



## SCOPE HAND-HELD DIGITAL CAPACITANCE and MULTIMETERS

- 0.5% DC Accuracy
- Highest Quality
- Highest Performance
- Lowest Prices



**Model DCM-602**  
**\$69.95**

**3½ Digit Capacitance Meter**  
8 ranges with full scale values to 2000 uF  
**FEATURES** • Broad test range - 1 pF to 2000 uF • LSI circuit provides high reliability and durability • Lower power consumption • Crystal time base  
• Protected from charged capacitors  
• Frequency range - 800 Hz to 8 Hz

**Model DVM-634**  
**\$48.75**

7 functions, 32 ranges.  
Transistor measurement included.

### 3½ Digital Multimeters

**FEATURES** • DC Voltage 100 uV - 1000 V • AC Voltage 100 uV - 750 V • AC/DC Current 200 uA - 10 Amps • Resistance 20 Megohms • Capacitance (DVM 636/638) 1 pF - 20 uF  
• Overload Protection • Auto-decimal LCD readout • Polarity indication • 300 hour battery life with 9V transistor battery • Low battery indication

**Model DVM-638**  
**\$79.95**

11 functions, 38 ranges.  
Includes logic level detector, audible visual continuity, capacitance and conductance measurement.

**Model DVM-636**  
**\$62.75**

8 functions, 37 ranges.  
Capacitance measurement included.

ASK FOR FREE CATALOG.  
Money orders, checks accepted. C.O.D.'s require 25% deposit.



# Fordham

260 Motor Parkway, Hauppauge, NY 11788

Toll Free  
**800-645-9518**  
In NY State **800-832-1446**

CIRCLE 63 ON FREE INFORMATION CARD

### Service & Shipping Charge Schedule Continental U.S.A.

FOR ORDERS	ADD
\$25-\$100	\$4.50
\$101-\$250	\$6.00
\$251-\$500	\$8.00
\$501-\$750	\$10.50
\$751-\$1,000	\$12.50
\$1,001-\$1,500	\$16.50
\$1,501-\$2,000	\$20.00
\$2,001 and Up	\$25.00