

MARCH, 1963

35 CENTS



# RF REPORTER

including **Electronic Servicing**

## SPECIAL ISSUE

# TEST

# EQUIPMENT

Special 8-page Book Section

A Key to  
Test-Equipment Circuits

Alignment Equipment  
for Stereo FM


•  
Ringing Checks  
for Sweep Coils

You Can Service  
Transistors With a VOM

•  
Industry Uses  
Unique Test Equipment

IA 26 1104 1266  
WM. M. DAVIS  
RAC. & TV SERV.  
118 RIVERSIDE AVE.  
CANNON CITY, COLO.

# POWERMATE

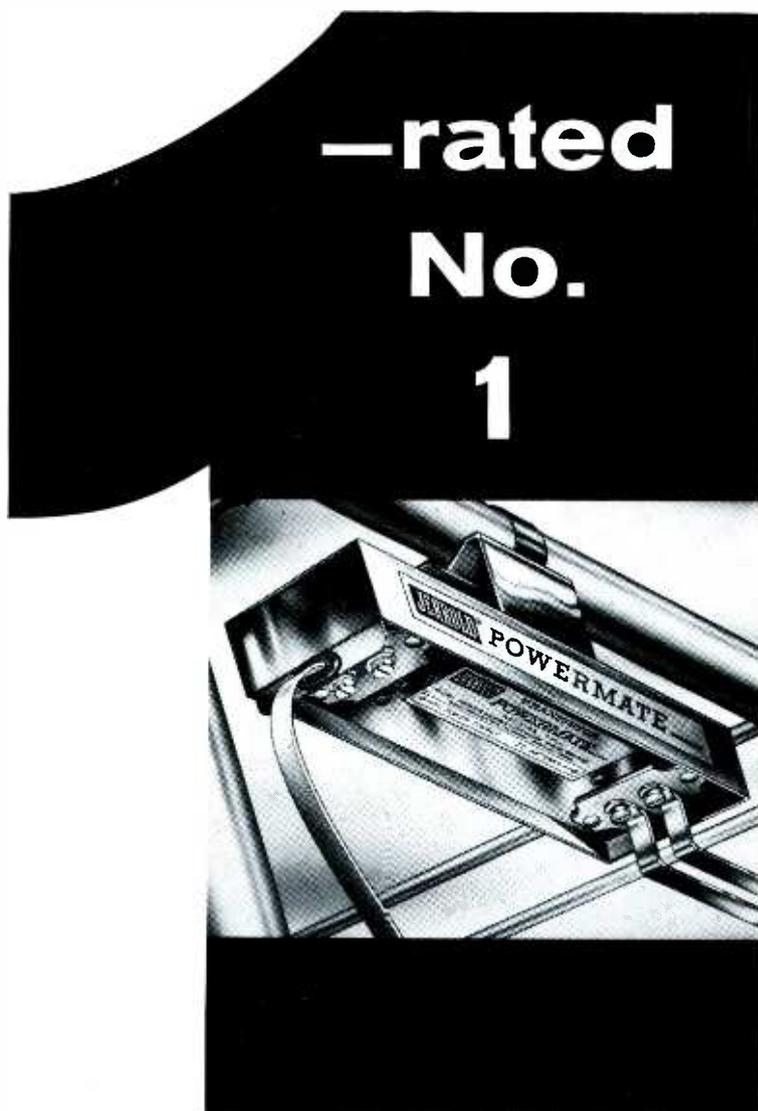

## ...the unquestioned leader in antenna-mounting preamplifiers

"Improved" models of other TV/FM antenna amplifiers may come and go, but Jerrold POWERMATE remains the one to beat.

Only POWERMATE delivers consistent high gain on both high and low bands—no "hills and valleys" to cause smearing and ghosting. And only POWERMATE offers the over-all reliability that cuts call-backs to the bone. Service-


men and viewers, even in deepest fringe areas, agree that POWERMATE outperforms them all . . . more customer satisfaction, more profit for you.

Are you getting your share of this POWERMATE-hungry market? See your Jerrold distributor today, or write Jerrold Electronics, Distributor Sales Division, Philadelphia 32, Pa.



A subsidiary of THE JERROLD CORPORATION

# A KEY TO

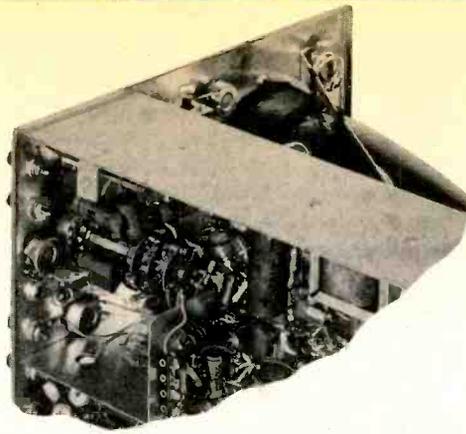

# TEST EQUIPMENT CIRCUITS

Increase your understanding of instrument operation.

Service technicians depend for their livelihood on their understanding of electronic circuits, and on their ability to repair them. And yet, surprisingly few servicemen have a really concrete knowledge of what's inside

the test instruments they use every day. Not too many of them realize how much easier it would be to use test equipment if only they understood it more completely. In this special book section, you'll learn what is

actually happening inside various test apparatus when you take a measurement, look at a waveform, or feed a signal into an ailing set.

### Circuits Are Simple

At first glance, most test instruments appear to contain either a maze of complex wiring, or a printed board with numerous components mounted in neat, but confusing, rows. An analysis of the wiring diagram may only add to your uncertainty, since it appears different from anything you've seen in a television or radio schematic. But, take a second glance at the diagram. You'll notice it contains the same components you work with every day, and you'll soon find they're connected into circuits that are not nearly so complex as they may seem. To prove this point, consider that a television set contains several times as many parts as your voltmeter or scope, and its schematic is even more complicated than that of the test instrument—if you look at the entire schematic at once. However, when you analyze a TV set, you concern yourself with only one portion at a time; this method will work just as well with test-equipment schematics.

One feature of instrument diagrams seems to offer a stumbling block: Connections through multisection switches can be difficult to trace if you're not familiar with them, especially when the schematic shows the switch set at

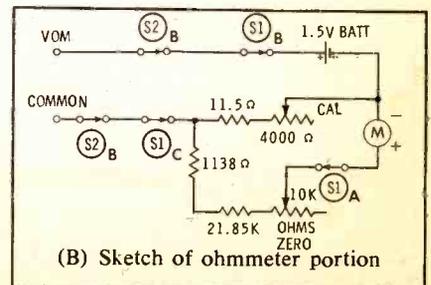
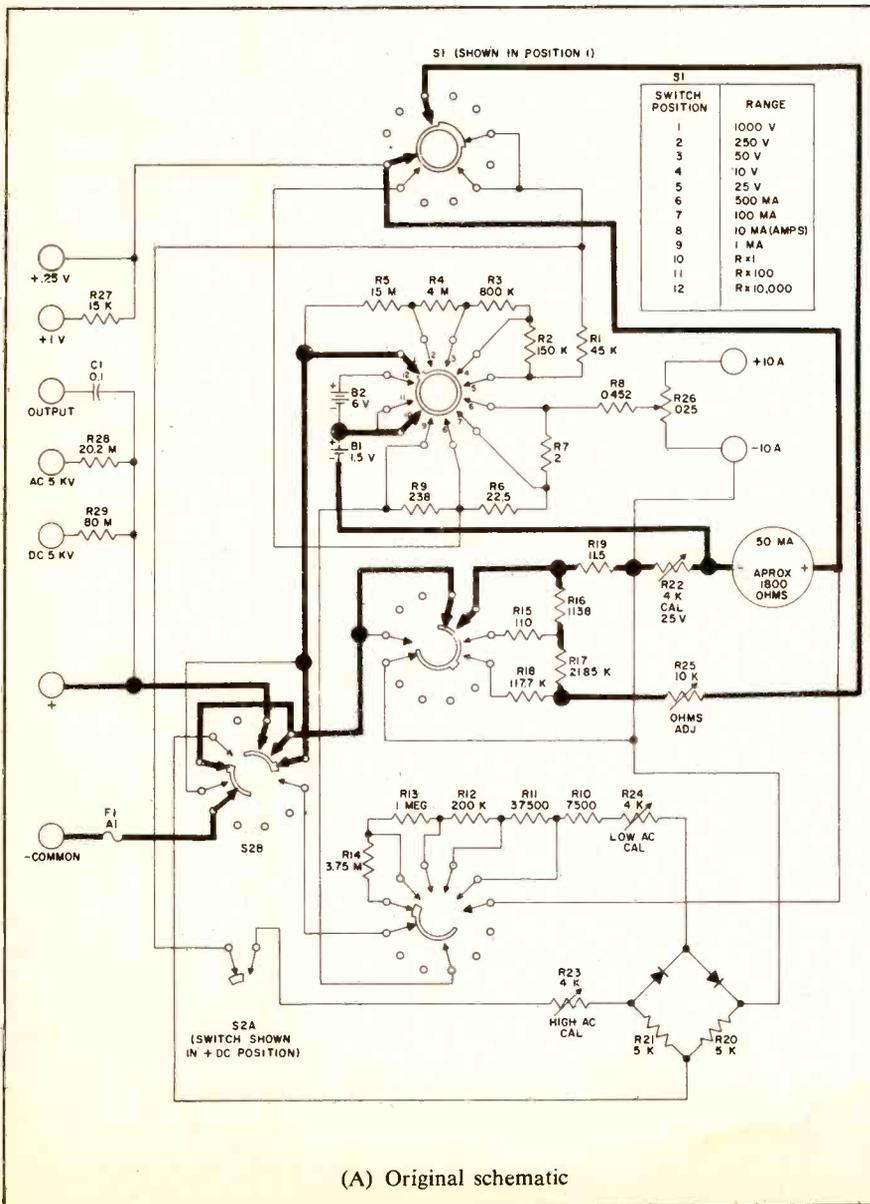


Fig. 1. Technique of "extracting" simplified schematic for easier understanding.

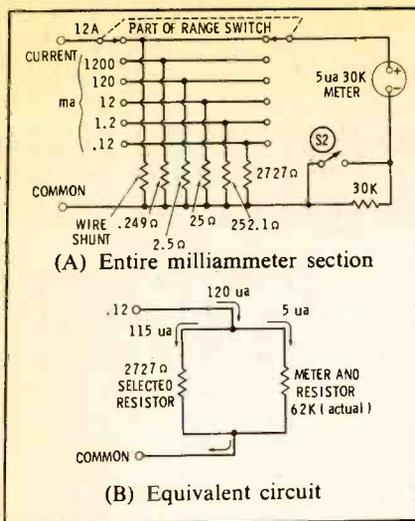


Fig. 2. Current-measuring circuits consist of meter with resistive shunts.

some position other than for the function in which you are interested. But there is a technique that can be utilized to overcome this problem—that of “lifting out” a portion of the schematic and sketching it in simplified form. This will be done with many of the schematic diagrams shown throughout this text, and you’ll be able to see how it’s done. Essentially, it involves lightly marking the switch on the original schematic as if the switch were in the desired position, ignoring the actual setting shown. Tracing connections is thus greatly simplified, and any section of the circuit (for example, the ohmmeter portion) can be sketched in simple form. This technique is demonstrated in Fig. 1; a normal VOM schematic is shown in Fig. 1A, with the  $R \times 1$  ohmmeter portion marked by heavier lines. Fig. 1B shows the simplified sketch which can then be made for a fuller understanding of the circuit.

With these “tricks” in mind, let’s turn to actual equipment, and learn exactly what makes each type of unit “tick.” The most-used instruments on the technician’s service bench are the

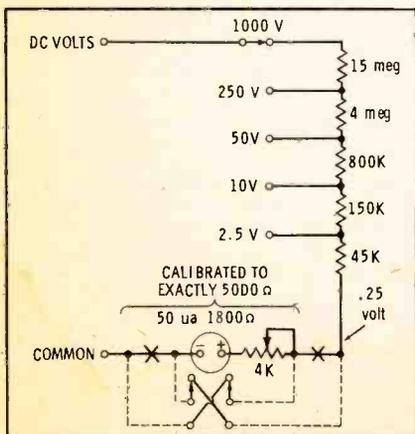


Fig. 3. Common DC voltmeter section is characterized by series-resistor chain.

VOM, VTVM, scope, and signal generator. We’ll examine the circuits commonly found in each, and learn how they function. This information can be put to practical use through a better understanding of how to use the instruments more effectively and how to determine the cause of any malfunction.

### The VOM

The volt-ohm-milliammeter centers around a simple current meter, utilizing series and parallel resistances to permit measuring voltage and checking resistance in addition to the basic function of measuring current. To understand the VOM, you should understand the meter movement, because every other circuit component is chosen carefully to complement this “heart” of the instrument.

#### The Meter

The sensitivity of the entire VOM depends on the meter. Two factors involved in rating meter movements are the amount of current required to drive the pointer to full scale, and the resistance of the coil. The less current that is required to bring its pointer to full scale, the greater is the sensitivity of the meter. The coil resistance depends on the size of the coil wire and the number of turns needed for the required sensitivity. Most meters used in VOM’s are 100-ua and 200-ua units with 800- or 1000-ohm coils; less expensive instruments use 1-ma meters, while more sensitive ones incorporate meters as sensitive as 5 ua.

The characteristics of the meter coil determine the sensitivity of the finished VOM. The almost universal sensitivity for VOM’s is 20,000 ohms per volt, but there are instruments ranging from 1,000 to 200,000 ohms per volt.

#### DC Milliammeter

From the schematic of a typical

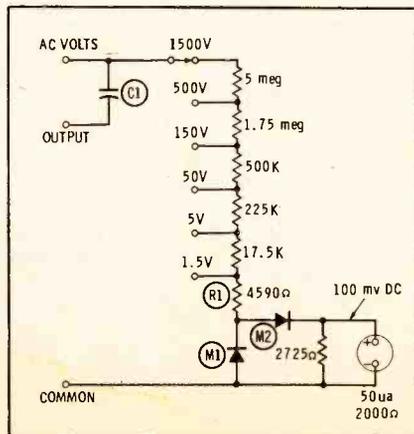


Fig. 4. Rectifiers are used in every AC voltmeter — sometimes they’re tubes.

200,000 ohms-per-volt meter, you can extract a sketch of the milliammeter section (like Fig. 2A) from which you can easily analyze the action of the circuit.

Fig. 2B is a further simplification that shows how the shunt resistor increases the current range of the basic meter movement, for measuring greater amounts of current. As the value of the shunt resistor is decreased, more of the current applied at the terminals is shunted around the meter. If the instrument of Fig. 2B is placed in a circuit carrying 120 ua, only 5 ua will flow through the meter, and 115 ua will go through the shunt resistor. The amount of resistance is carefully picked to calibrate the circuit for exactly the current range desired.

The circuit in Fig. 2A incorporates a feature that can be found in several recent VOM’s: Switch S2 is connected to remove the series resistor from the meter circuit. When the series resistor is thus bypassed, the meter-circuit resistance is reduced to only that of the meter. As a result, the entire circuit requires only half as much current to drive the meter to full deflection, so each scale reading must be divided by 2; thus, the .12-ma (120-ua) scale actually reads .06 ma, or 60 ua.

One other point to notice: For the 12-amp scale, a wire shunt is used. This is a carefully selected piece of low-resistance wire, for it must pass almost the full 12 amps of current. (Only 5 ua can pass through the meter, leaving 11.999995 amps to pass through the shunt.)

#### DC Voltmeter

In Fig. 3, a 50-ua, 1800-ohm meter movement is being used in a VOM to measure DC voltage. A voltmeter, probably the simplest of circuits to understand, always consists of dropping resistors (multipliers) in series with the meter movement. The multiplier resistors can be considered in either of two ways: They can be looked on as dividers that reduce the voltage to the correct amount for the meter, or they can be thought of as current-limiting resistors to lower the current so it is just enough to drive the meter to full scale. Whichever way you prefer to think of them, the multiplier resistors in a voltmeter are always in series with the meter. This is opposite to the arrangement used with current meters, which invariably have the resistances in parallel with the meter movement.

Some VOM’s incorporate a reversing switch for the DC voltmeter, to make it unnecessary to reverse the test

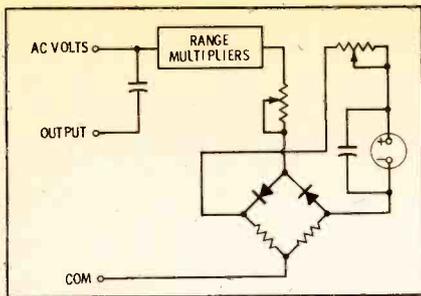


Fig. 5. Bridge-type AC rectifier is a bit more sensitive than half-wave type.

leads when measuring certain voltages. When it is included, the switch is usually placed in the metering circuit as shown in Fig. 3.

#### AC Voltmeter

To measure AC voltages with the ordinary DC meter movement, it is necessary to rectify the input voltage. Fig. 4 shows a typical AC voltmeter, using a 50- $\mu$ a, 2000-ohm meter with semiconductor rectifiers M1 and M2. In a number of VOM's, M1 and M2 are a single dual-diode unit. The multiplier resistors are almost the same as with the DC ranges; the only difference is in the values, which must be changed to compensate for the addition of the meter rectifiers. This means the meter sensitivity can't be used directly in calculating the values for multiplier resistors, because the internal resistances and rectifying effects of M1 and M2 must also be considered. This difference is also corrected for, in many VOM's, by a special scale on the meter face for AC volts.

Careful analysis of the circuit in Fig. 4 will help explain one of the precautions which you must ordinarily observe when measuring signal voltages in certain electronic circuits. For example, if you were to measure the audio voltage at the plate of an output stage, the DC voltage present would also have considerable effect on the meter indication, because a positive DC voltage can pass through rectifier M2 and cause a reading on the meter. The result might be a fairly high indication, even though audio voltage might actually be almost non-existent.

Such readings can lead to confusing results. To eliminate this error, you can try making a second measurement with the test leads reversed, and accepting only the lesser reading of the two. This precaution is sometimes unnecessary, because a number of AC voltmeters include a blocking capacitor (such as C1 in Fig. 4) for measuring AC in the presence of DC. In

most instruments, the capacitor is connected to a jack called OUTPUT because it is used primarily in testing audio output stages. Very often, the scale card of the meter is provided with an extra scale — usually calibrated in decibels — to facilitate output readings and allow for the difference in accuracy introduced by adding the capacitor to the divider network.

Fig. 5 shows a slightly different AC voltmeter. In this circuit, the rectifier unit is wired into a bridge network. This arrangement, being full-wave, is somewhat more sensitive than the system shown in Fig. 4. One noteworthy difference about this circuit concerns the erroneous readings that may occur in DC-carrying circuits. In the circuit of Fig. 5, reversing the test leads will have little effect in correcting the error. Therefore, it is necessary to use the "output" function when DC is present in the circuit being tested.

#### Ohmmeter

Resistance can be measured relatively easily; it is necessary only to apply a known voltage to the unknown resistance, measure the resulting current, and use Ohm's law to compute the resistance. All three steps can be handled automatically by the circuit in Fig. 6.

A 1½-volt battery is used as the voltage source for the R x 1 scale. To set the meter for testing, the ZERO ADJUST potentiometer is set for a full-scale reading with the unknown resistance at zero ohms (leads shorted together). This means the scale card will read from right to left for increasing values of resistance. Practically all VOM's are designed this way, and are thus called *right-hand-zero* ohmmeters. As the unknown resistance increases, less current flows in the meter, and the pointer indicates a higher resistance value on the scale card.

The highest range of this particular ohmmeter (R x 10K) is powered by 7½ volts — usually four 1½-volt flashlight cells in series with the single cell used for lower ranges. Switching to the highest range also connects the measuring circuit to a different point on the divider network. All the resistors in the network are carefully chosen so that, once the meter has been "zeroed" (remember, this is at full scale), a zero reading will occur at every setting of the range switch when the test leads are shorted together. In this type of ohmmeter, when

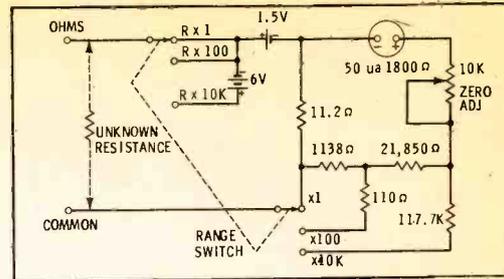


Fig. 6. Ohmmeter section of VOM changes dividers, voltages with range.

you find it fails to "zero" on one range or another, you can blame slight variations in the resistors which make up the divider network. (Of course, this assumes the batteries are fresh.) However, this slight shift can be taken care of by resetting the ZERO ADJ potentiometer, and will have little effect on resistance readings.

#### The VTVM

It has been truthfully said that a VTVM is merely a glorified VOM. However, this "glorification" is not without good cause. One of the assets of the vacuum-tube voltmeter is its input impedance, which is constant for all its ranges and very high in value—10 megohms is common, compared with 20,000 ohms per volt for most VOM's. This means that, on its 500-volt scale, a VOM would have an input impedance of 10 megohms—comparable to the impedance of a VTVM; but, on the 10-volt scale the VOM would have an input impedance of only 200K ohms (which would load down some high-impedance circuits), while the VTVM still would maintain its 10-megohm input impedance.

The VTVM also has other advantages. The use of a vacuum tube makes it possible to incorporate a relatively inexpensive meter movement, yet obtain instrument sensitivity far exceed-

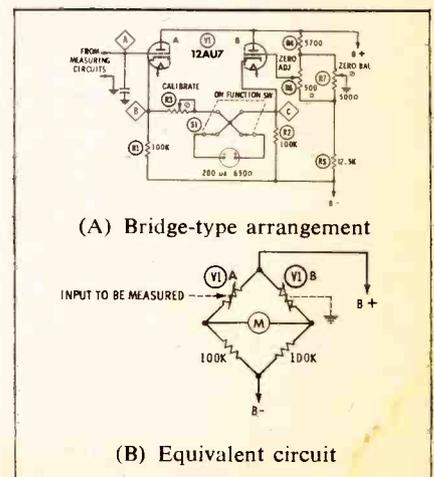


Fig. 7. Metering circuit for VTVM uses vacuum tube to increase sensitivity.

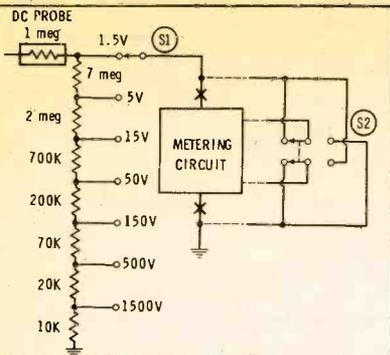


Fig. 8. DC section of VTVM is similar to its counterpart in the usual VOM.

ing that of the VOM. Also, it permits easy conversion of the ohmmeter scale into a *left-hand-zero* type, making it more consistent with the rest of the scale card. Much higher ohmmeter ranges can be used, because of the increased sensitivity of the metering circuit.

#### The Metering Circuit

The main difference between the VTVM and VOM is in the metering circuit. Most modern VTVM's use a bridge circuit like that shown in Fig. 7, with a vacuum tube as two "legs" of the bridge. The meter itself is connected between the cathodes, which represent the balance points for the bridge, as shown in Fig. 7B; the tubes then represent variable resistances in the two upper legs of the bridge. One tube maintains balance in the bridge when the input is zero; the other "senses" the value of any input voltage and unbalances the circuit, causing an indication on the meter.

Let's examine the circuit a bit more closely. First, the input: The voltage from the measuring circuits (multipliers, range switch, etc.) is developed between the grid of V1A and ground; therefore, it is actually applied between the grids of the two tubes, since

the grid of V1B is returned to ground through R6 and the slider of R7. Thus, a positive voltage at point A will cause greater conduction in V1A and reduce conduction in V1B, causing point B to become more positive and point C to become more negative. The meter indicates this change by an up-scale movement of the pointer. If a negative voltage is applied to point A, point C becomes more positive (from increased conduction in V1B) and point B becomes more negative. The result is a downscale swing of the needle, unless polarity switch S1 is changed to cause the meter to read upscale.

When the value of the applied voltage is known, R3 can be adjusted until the current through the meter is just enough to make the pointer fall at the proper marking on the scale card, thus calibrating the instrument.

If the input voltages are not applied at just the right "point" in the bridge, the positive and negative swings will not be symmetrical—that is, a 10-volt positive swing will not unbalance the bridge exactly the same amount as a 10-volt negative swing. The ZERO BAL potentiometer allows for adjusting this balance to suit the tube characteristics.

It is also necessary to establish an equilibrium within the bridge, for it must be exactly balanced so no indication will be passed on to the meter when point A is tied to ground or no voltage is being applied. For this purpose, the ZERO ADJ potentiometer is provided; it will be found on the front panel of most VTVM's, where the operator can adjust it easily.

Certain of the above functions are handled somewhat differently in various VTVM's, but you'll find that most follow the same general design pattern. Remember, a circuit such as that in Fig. 7 does not depend on an extremely sensitive meter movement for its sensitivity. In the VTVM whose metering circuit is shown in Fig. 7, a 200-ua, 650-ohm meter is used, although the input impedance of the VTVM is 10 megohms. This demonstrates a basic fact about a VTVM: its input impedance depends essentially on the divider networks used at the input of the instrument, and has little to do with the sensitivity of the basic meter movement.

#### DC Voltmeter

There is a simple method of analyzing the voltmeter section of a VTVM: merely think of it as a VOM, and consider the vacuum-tube metering circuit as a simple meter. For an example, look at Fig. 8. The input multiplier consists of resistors totaling 10 megohms; various points in this di-

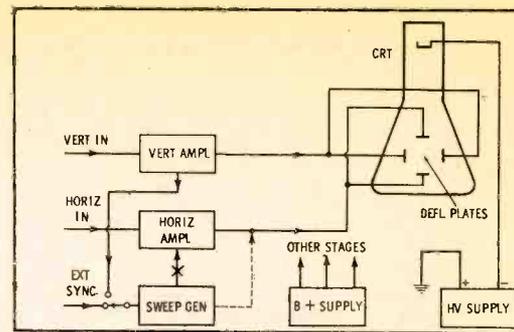


Fig. 10. Basic diagram of oscilloscope includes the functions most necessary.

vider chain are connected to the metering circuit to derive the various ranges. Since the metering circuit in this case (the grid circuit of V1A—Fig. 7) has almost an infinite impedance, it has little effect on the divider network, or on the input impedance of the instrument.

The DC probe contains a 1-meg resistor, as do most of those used with modern VTVM's. The resistor helps isolate the VTVM tube stages from the circuit being tested—particularly on the lowest range, where the 1-meg resistor is the only isolation between the measured circuit and the grid of V1A. This resistor also makes the overall input impedance of the VTVM 11 megohms on all DC ranges.

Note the similarity between the circuit of Fig. 8 and that in Fig. 3. The metering circuit in Fig. 8 performs the same functions as the meter and the calibration potentiometer of Fig. 3.

In Fig. 8, you'll also notice an extra switch, S2. This is a polarity-reversal switch of a type used in some VTVM's, which "flips" the input connections to the entire metering circuit instead of changing just the meter connections as is done in some instruments.

#### AC Voltmeter

There are several types of AC voltmeters used in different models of VTVM's: ordinary AC voltmeters, for measuring rms values of power-line and audio voltages; peak-reading voltmeters, which indicate the peak value of any AC waveform; peak-to-peak voltmeters, that can measure complex waveforms such as those found in television sets; and special amplified voltmeters, usually for measuring very small audio or other rms voltages.

The most common of these—the *rms voltmeter*—is found in both VOM's and VTVM's; a typical circuit is shown in Fig. 9A. You'll notice its similarity to the AC voltmeter in Fig. 4; the function of the VTVM metering circuit is the same as in the DC voltmeter just discussed.

You'll notice two divider networks. Since the shunting effect of rectifier

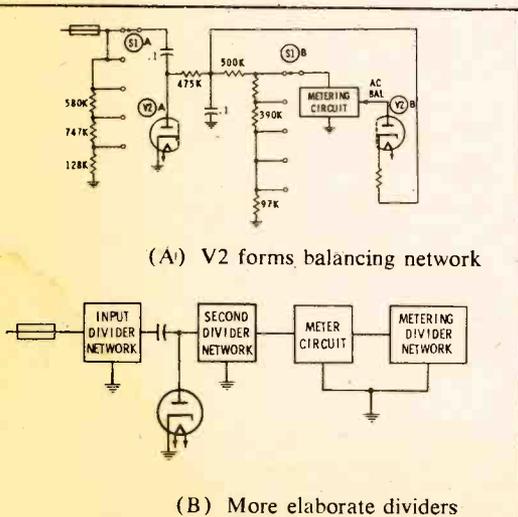


Fig. 9. Special circuit arrangement for AC voltmeter in one popular VTVM.

V2A will vary with the voltage impressed across it, allowance must be made for this before the rectified voltage is fed to the metering circuit. The resistive network associated with switch S1 (both sections) takes care of this.

Rectifier V2B feeds a portion of the rectified voltage back to the metering circuit to balance the entire network so it will correctly read both positive and negative excursions of the input AC voltage. This matters little with sine waves, but when the rms (effective) value of an odd-shaped waveform is being measured, it is important that the circuit be effectively balanced.

A more elaborate variation of the AC voltmeter is shown in Fig. 9B, in block form. In this system, three divider networks are incorporated in the measuring circuits; the input divider, the rectifier-compensating network, and a divider network associated with the metering circuit itself. The additional divider merely permits more precise design of the measuring circuit to cover each range more accurately.

#### Peak-Reading VTVM

In the rms-type meter, the "effective" voltage of a sine wave is only .707 times the peak value, and this is what the instrument measures. To measure peak (and peak-to-peak) voltages, a voltage-doubler rectifier—often a bridge-type—is normally used, along with a filter circuit having a long time constant. The values of the filter components are chosen so the capacitor hardly has time to start discharging before the next half-cycle recharges it. Thus, the reading indicates more nearly the actual peak of the input signal.

In peak-reading VTVM's, the rms scale is merely calculated from the fact that the rms value of a sine wave is exactly .707 times the peak value. Therefore, as a rule, the rms scales are accurate only when a sine wave voltage is being measured. Remember, this applies only to VTVM's that are designed for peak or peak-to-peak measurements.

#### Current Measurement

Very few VTVM's make any provision for measuring current. When they do, their current-measuring circuits are exactly the same as those used in VOM's, and the bridge circuit is not used. The meters used in VTVM's, as explained before, are seldom as sensitive as those used in VOM's, since this sensitivity is not needed. For this reason, VTVM's are not likely to be capable of measuring very low currents—a slight limitation on their usefulness.

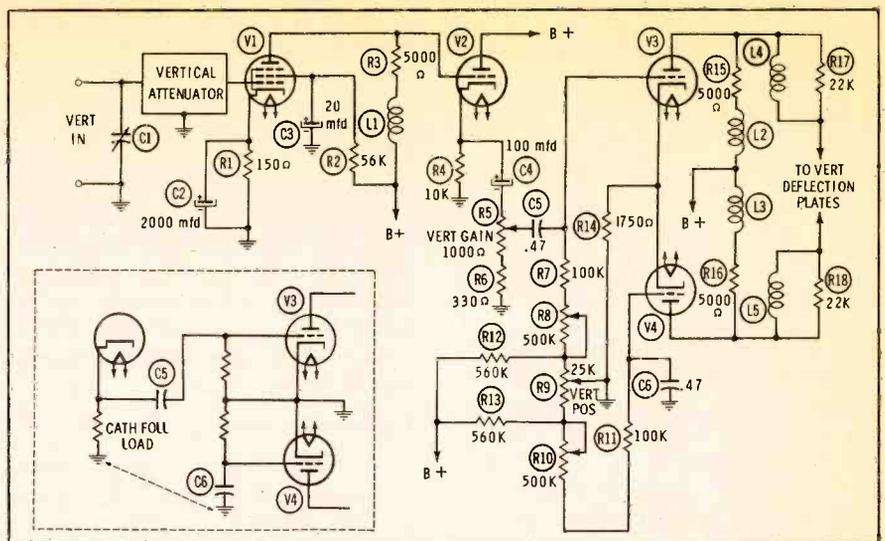


Fig. 11. Vertical amplifier is signal-handling section of the oscilloscope.

### Oscilloscopes

Next to the VOM and VTVM, the oscilloscope is undoubtedly the most indispensable troubleshooting instrument for the practical serviceman. With it, he can actually look at the most complex waveforms traced by the continually alternating signal voltages in electronic circuits. To perform this feat, every oscilloscope—even the simplest—must have certain functions. A glance over Fig. 10 will show you the basic sections that every oscilloscope must contain. Each section may be as elaborate or as simple as the application calls for, but the key stages are still the same.

#### Vertical Amplifiers

Differences you will find in vertical amplifiers will generally concern the input-attenuator arrangement, the amount of amplification, the bandwidth, and the point of sync takeoff. A typical vertical amplifier is shown schematically in Fig. 11.

The first significant feature you'll notice is the fact that the output is push-pull and one output tube connects to each deflection plate of the CRT. Most modern scopes use this arrangement, as it permits the use of tubes which consume little power, while still driving large-screen scope tubes. Single-ended output stages are still used occasionally, but they're not very common.

The push-pull output stage shown in Fig. 11 is unusual in its own right,

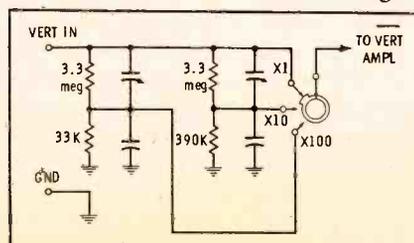
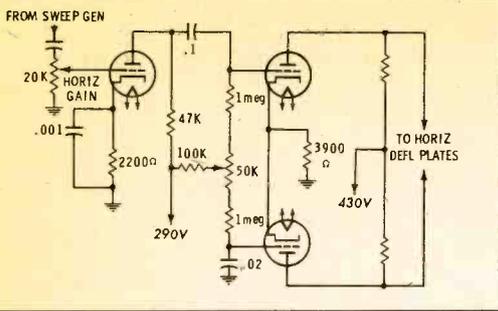


Fig. 12. Vertical attenuator network.

because of the uncommon driving arrangement—usually found only in scopes. Cathode follower V2 is used as the driver tube. C4 couples the signal to the VERTICAL GAIN control R5; the impedance of the capacitor is so low that the cathode-follower signal load effectively consists of R5 and R6 paralleling R4. Capacitor C5 feeds the signal to the grid of V3. But how is the push-pull signal developed and made to drive V3 and V4 on alternate cycles? The insert of Fig. 11 shows the simplified equivalent push-pull circuit. Since C6 grounds the grid of R4 for signal voltages, the cathode-follower load is connected to both grids—one end to V3, and the other to V4. Thus, when the signal waveform is positive-going, V3 conducts; on the negative excursion, V4 conducts. In this way, the tubes act in push-pull, without the conventional phase-splitters, phase inverters, or driver transformers commonly associated with push-pull operation.

You'll also notice that V3 and V4 are connected directly to the deflection plates; no coupling capacitor is used. This means that the deflection plates operate at the same potential as the output-tube plates, and that varying the average plate voltage of either output tube will alter the DC voltage on that one deflection plate, thus offering an easy means of positioning the beam vertically.

In the circuit of Fig. 11, this beam positioning is done by changing the tube bias; control R9 is the adjustable part of a voltage divider which balances the bias voltage between the grids. Moving the control slider toward V3 will place its grid nearer ground potential, applying more of the cathode bias to the grid. Meanwhile, the V4 grid becomes slightly more positive because of its connection to B+ through R13. Conduction

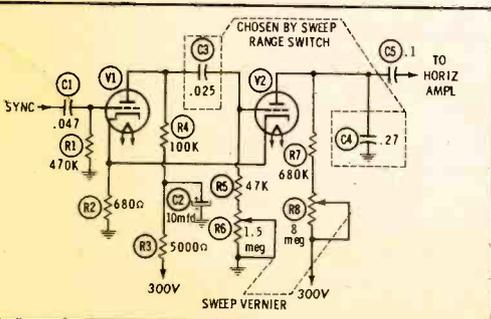


**Fig. 13. Horizontal amplifier doesn't incorporate bandwidth-widening parts.** in V3 decreases, while current through V4 increases. The plate of V3 becomes more positive, and so does the corresponding deflection plate—thus attracting the electron beam in the CRT. The plate of V4 becomes less positive, aiding the action and allowing the beam to move toward the opposite deflection plate more easily.

To summarize the action of the output stage: The average position of the CRT beam depends on the bias of the output tubes, and this beam positioning is controlled by R9. The instantaneous movement of the CRT beam in step with the signal is accomplished by the push-pull action of the output stages, caused by the signal being fed to the output grids from the cathode follower.

The input attenuator limits the input signal to a level that will not overload the first amplifier stage. It usually consists of a resistive divider network like that shown in Fig. 12. The capacitors, which prevent favoring certain frequencies, are present only in compensated attenuators. In more elaborate instruments, attenuators of even greater complexity are common.

The gain of the vertical amplifier section is developed mostly in the input amplifier. However, the bandwidth of the instrument is dependent on the bandpass of all the amplifiers. V1 in Fig. 11 uses choke L1 for high-frequency peaking, and high-value cathode-bypass capacitor C2 to prevent low-frequency degeneration. DC coupling to the cathode follower prevents any frequency-response problem there.



**Fig. 14. Multivibrator-type sweep generator uses cathode coupling system.**

In the output stage, both series and shunt peaking coils are used to flatten the overall response of the vertical amplifier section. Resistors R15, R16, R17, and R18 serve to dampen any self-resonant characteristics of the peaking coils.

If a single-ended output stage is used, one deflection plate is grounded. Operation is then somewhat similar to the push-pull action described in the insert of Fig. 11, with the ground connection serving as a signal-coupling device.

### Horizontal Amplifiers


In many scopes, the horizontal amplifier system is an exact replica of the vertical amplifier, having equivalent sensitivity and bandwidth. In most service scopes this extra gain and response is unnecessary, and the horizontal section has only enough gain to fill the CRT screen with the drive signal from the sweep generator. Some, however, include extra gain so the trace can be expanded for close inspection of some portion of the display.

Fig. 13 shows one of the more common horizontal amplifiers. It is quite similar to the vertical amplifier shown in Fig. 11, except it has less gain, and the bandwidth is more limited. The same push-pull configuration—so common in modern scopes—is used in this amplifier. However, you'll notice the absence of frequency-compensating devices in this amplifier—a clue that bandwidth is not considered important for the horizontal sweep system of this scope.

### Sweep Generators

To sweep the CRT beam from side to side, a linear-sawtooth generator is incorporated in every scope. It may be called the sawtooth oscillator, sweep generator, sweep multivibrator, time-base generator, or one of countless other names based on the circuit configuration. The function is always the same: to sweep the CRT beam across the face of the CRT in a linear fashion, and then bring it quickly back across the screen to begin another trace. In a few older scopes, blocking oscillators are used, but nowadays the multivibrator is the more common circuit.

Two types of multivibrators are in general use—the cross-coupled and cathode-coupled circuits. The latter arrangement, using a common cathode resistor to couple the two sections of the multivibrator, is probably a little more prevalent than the plate-to-grid type. A typical cathode-coupled multivibrator is shown in Fig. 14. This circuit is a free-running sawtooth os-

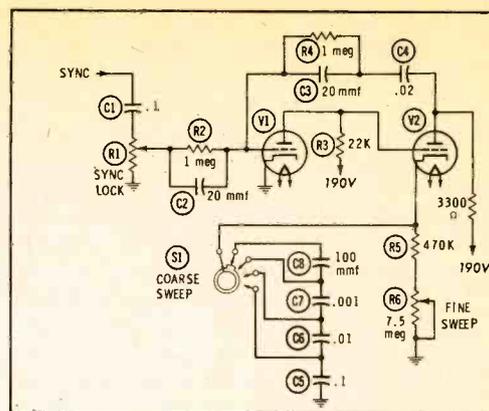


**Fig. 15. Frequency-determining parts in cathode of cross-coupled oscillator.**

illator, but can be controlled by a synchronizing signal applied through C1. Feedback is provided primarily by cathode resistor R2, which is common to both stages; however, oscillation is also dependent on the coupling provided by capacitor C3.

The frequency of the circuit in Fig. 14 depends on the time constants formed by C3, R5, and R6 in the grid circuit of V2, and by C4, R7, and R8 in the plate circuit. The main frequency selector is a switch that connects alternate values of capacitors in place of C3 and C4, while a dual-control potentiometer (R6 and R8) serves for "fine tuning." Ranges of sweep frequencies vary with scope application; some sweep only up to 40 or 50 kc, while others provide sweep frequencies as high as 1 mc.

A variation of the cross-coupled multivibrator is shown in Fig. 15. The main frequency-controlling components are connected to the cathode of V2; S1 chooses one of the frequency-determining capacitors, and R6 functions as a vernier tuning control. Also note the DC coupling between the plate of V1 and the grid of V2. This multivibrator can be controlled by a sync signal coupled to the grid of V1 through C1.

The main frequency-selecting switch of most scopes almost invariably includes a position which applies a portion of the AC line voltage to the input of the horizontal amplifier; this permits sweeping the CRT with a

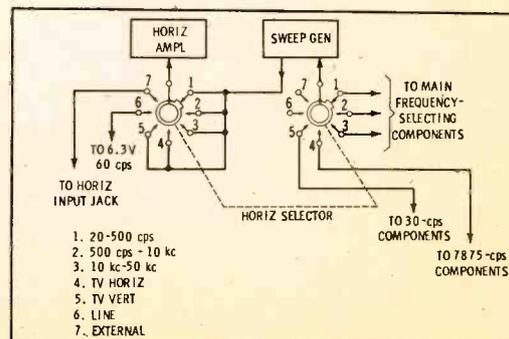

**Fig. 16. Horizontal frequency selector.**

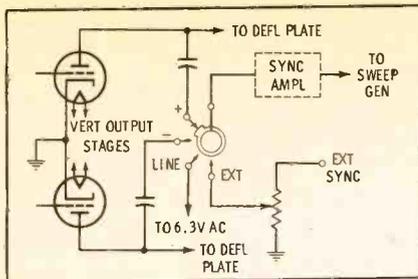


Fig. 17. Sync circuit of typical scope.

60-cps sine-wave trace (useful in certain applications). Other auxiliary positions of the frequency-selector switch provide fixed-tuned TV horizontal and vertical sweep rates; these are usually preset to show waveforms of two or three horizontal lines or vertical frames. Also, the same switch is ordinarily used to connect the horizontal amplifier to the HORIZONTAL INPUT jack on the panel. Fig. 16 depicts a typical frequency-selector switch, and shows schematically the connection made in each position.

#### Sync Section

Quite a few scopes don't actually have a sync "section," although practically all of them have provisions for synchronizing the trace, so the waveform display will stand still horizontally. Most common is the system shown in Fig. 17 or a similar variation of it.

For the + and - positions of the switch, a sample of the input signal is taken from the plate of each output stage. If the signal is predominantly positive-going, best sync is obtained if the switch is set at the + position; if the signal is mostly negative the - position provides best sync. "Line" sync makes it easy to stabilize patterns that are exact multiples or sub-multiples of the line frequency—60 cps. An amplitude control is generally used with external sync, since too much synchronizing voltage can sometimes distort the scope's horizontal sweep.

In many scopes of more elaborate design, a sync amplifier is included, as shown by dotted lines in Fig. 17. When this stage is used, the sync-amplitude control is usually placed in the amplifier grid circuit, thus affecting all sync signals—both internal and external.

#### Auxiliary Circuits

There are a number of circuits, in some scopes, that are not absolutely necessary to the main function of the instrument. These circuits make operation of the instrument easier in many instances; in other cases, they adapt the unit to special applications; sometimes they make it easier to interpret

the traces. Among these auxiliary circuits are retrace blanking, Z-axis modulation, triggered sweep, polarity reversal, variable-bandwidth switching, and various calibrating devices.

*Retrace blanking* simply consists of a negative pulse, derived within the instrument, that is applied to the grid of the CRT during the time when the trace is "snapping back" to begin a new line. In some scopes, the opposite "tack" is taken; the CRT is biased past cutoff and is "unblanked" during sweep time. Fig. 18A shows a waveform with a retrace line visible, while Fig. 18B shows the effects of retrace blanking.

*Z-axis modulation* has limited use in service work. It is simply a connection, usually on the front panel, by which a signal can be applied to the grid of the CRT to decrease or blank the intensity during negative portions of the Z-axis signal.

*A triggered sweep*, useful for analysis of certain pulse waveforms, is found most frequently on industrial scopes. In these instruments, the sweep generator is not free-running, but depends on an external stimulus or trigger. As a rule, it must be triggered for each excursion of the sweep, but some can be set to run for a definite number of cycles after each triggering pulse. In all models, the trigger pulse is applied in essentially the same manner as the sync signal in ordinary scopes.

*Polarity reversal* is merely a way of turning the trace upside down so positive-going pulses (such as television sync pulses) point downward, whereas they might normally point upward. This can be done rather easily by providing a switch to reverse the polarity of the signal just before it is fed to the push-pull output stage. With some scopes, this is done by switching the push-pull input from the cathode (as in Fig. 11) to the plate, which must have a suitable plate-load resistor.

A compromise between bandwidth and sensitivity must often be reached in scope design. To get around this, a few scopes offer two *bandwidths*, chosen by a switch on the front panel.

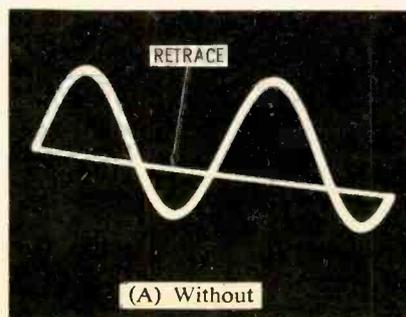


Fig. 18. Effects of retrace blanking.

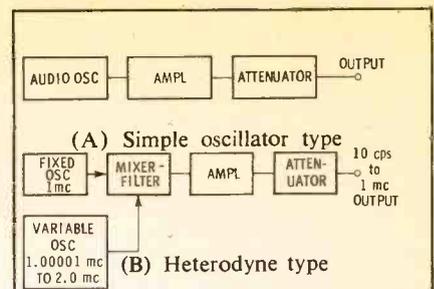


Fig. 19. Two types of audio generator.

The wide-band position sacrifices some sensitivity; but when measurements must be made that demand high sensitivity, the switch can be set for narrower bandwidth and higher gain. The change is accomplished within the instrument merely by removing the effects of some of the peaking components and changing operating voltages of certain tubes.

There are a number of *calibrating* devices and methods. Basically, they all consist of a predetermined voltage that can be applied to the vertical amplifier. The vertical gain control is then set to obtain a certain arbitrary vertical trace size; thereafter, that amount of deflection represents the same value as the calibrating voltage. In most scopes, the markings on the vertical-attenuator switch then represent decimal multipliers for the original calibrating voltage.

The calibrating voltage is usually taken from the filament circuit via a resistive divider which sets the exact voltage—commonly 1 volt. In many scopes, a calibrated graticule aids in reading peak-to-peak signal voltages with the scope; the calibration is simpler and more "automatic."

#### Signal Generators

Signal injection is recognized as a quick, logical method of localizing trouble in all sorts of electronic circuits. But, as in other phases of service work, the application of any troubleshooting plan is only as thorough as your understanding of the tool—in this case, the signal generator.

There are a number of general types: simple harmonic (noise) generators, audio generators, RF gener-

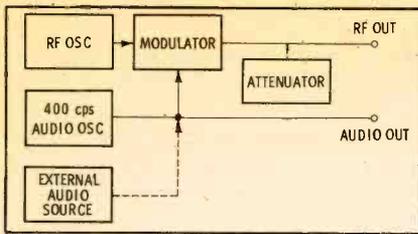


Fig. 20. Service-type signal generator.

ators, modulated RF generators, and special pulse (and pulsed-RF) generators. The simplest of these—the noise generator—consists of a circuit that can produce sharp pulses at some frequency in the audio spectrum. The fundamental frequency can be used for signal injection in audio equipment, while the high harmonic content of the pulsed signal makes its output useful also in RF and IF stages. For example, a 1000-cps harmonic generator can produce a usable signal for troubleshooting IF stages and RF amplifiers at more than 1000 times the fundamental frequency. This is because of the sharp nature of the pulses; the sharper the leading edge and the flatter the top of each pulse, the higher is the harmonic content of the signal.

#### Audio Generators

For testing audio circuits, two general types of instruments have been developed (Fig. 19). The first, shown in Fig. 19A, consists of a simple oscillator that produces an audio sine wave, an amplifier to raise the signal-voltage level, and an attenuator system. The oscillator can be a phase-shift type, a multivibrator, a blocking oscillator, or any other type capable of producing an audio sine wave. The amplifier increases the signal level sufficiently to permit injection directly into high-level output stages—usually 5 or 10 volts rms. The attenuator may be a carefully calibrated divider network that permits choosing the exact amount of signal—millivolts or volts—for a specific purpose; but in less expensive generators, the attenuator may be only a potentiometer.

Fig. 19B shows a different type of generator, more elaborate than the one shown in Fig. 19A; it is called a *beat-frequency* audio generator. In this in-

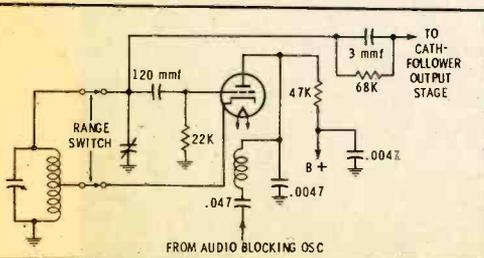


Fig. 21. Hartley oscillator that can be amplitude modulated with audio tone.

strument, the signal from a variable oscillator (controlled by the frequency dial) is mixed with the output of a fixed oscillator; the resulting beat-frequency signal is amplified and fed to the output network. The advantages of this system are greater accuracy of the audio output frequency, greater stability, and a wider range of available frequencies.

#### RF Generators

The "old standby" of radio and television servicing is the RF generator, usually equipped with an internal audio oscillator so a choice of three output signals—pure RF, modulated RF, or audio only—can be provided. This makes for versatility in application, because the instrument can be used for all sections of radios and television sets—provided the range of RF frequencies is sufficient. Some signal generators make provision for modulating their RF signal with the output from an external audio generator, further increasing the versatility.

Fig. 20 shows the essential portions of a service-type signal generator, with certain more elaborate features added in dashed lines. The oscillator is similar to those found in other RF devices; more often than not, it is a Hartley type. In many instruments, the modulation actually takes place in the RF oscillator tube—at the screen grid, at the plate, or at both. The attenuator shown can be anything from a simple potentiometer to a complex bolometer arrangement used for measuring microvolts of output signal.

The Hartley oscillator shown in Fig. 21 is typical of those found in service generators, although other variations are used. The signal-takeoff point for this circuit, however, is somewhat different from most; the output signal is taken directly from the tuned tank (at the grid connection) rather than from the plate circuit of the tube. This is done to permit use of an inexpensive triode tube and still allow the plate circuit to be connected to the modulating signal without affecting the tuned tank.

To prevent interaction between the tuned tank and the load connected to the instrument, a cathode follower is inserted between the oscillator and the output attenuator system.

If the oscillator tube is a pentode (or a pentagrid type), the circuit can be connected as shown in Fig. 22. In this arrangement, the output is taken from the plate of the tube, while modulation takes place at the screen grid. Thus, the oscillator section controls the plate current at an RF frequency, while at the same time the screen grid

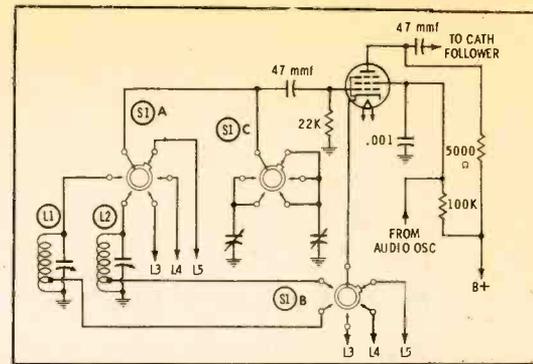


Fig. 22. Bandswitching signal generator with screen-modulated oscillator.

varies the plate current at an audio rate. The result of these actions is a modulated RF signal fed to the cathode follower, and thence to the output system.

A common attenuator arrangement is shown in Fig. 23. It is essentially a rather simple configuration, but is effective in preventing leak-through of RF signal to the output jack. In use, the COARSE control is set for enough output signal (with the FINE control fully clockwise) to fulfill the needs of the job being done. Then the FINE control couples out only as much of the signal as is needed for each step of the signal-injection or alignment procedure.

#### Conclusion

The circuits in this section are typical of those found in the most-used bench instruments in the ordinary service shop—the VOM, VTVM, scope, and signal generator. Each circuit has alternate arrangements which may vary from instrument to instrument. You'll find, however, that every instrument in each group *must* perform certain operations, and it is these operations you have learned about in the preceding pages. If you understand the functions described, and the circuits used to perform them, you'll have no difficulty in understanding whatever brand and model of instrument you own. Also, when you understand what's going on inside your test equipment, you'll not only be better able to use each instrument for its basic purposes, but you'll find you can develop many additional uses. Then your instruments will truly be what they're intended to be—the tools of a professional serviceman. ▲


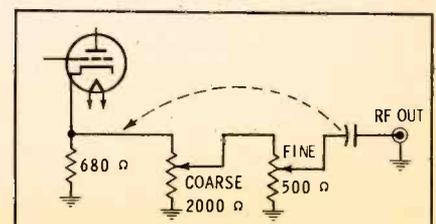


Fig. 23. Common RF output attenuator.

Prices effective January 1, 1963

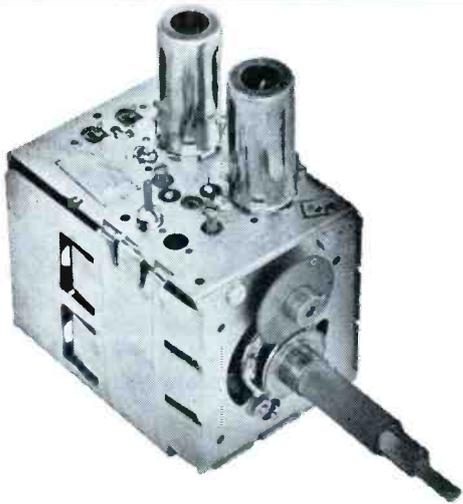Tarzian offers  
**FAST, DEPENDABLE  
TUNER REPAIR  
SERVICE (ALL  
MAKES)**



It just makes sense that a manufacturer of tuners should be better-qualified, better-equipped to offer the most dependable tuner repair and overhaul service.

Sarkes Tarzian, Inc. pioneer in the tuner business, maintains two complete, well-equipped Factory Service Centers—assisted by Engineering personnel—and staffed by specialized technicians who handle **ONLY** tuner repairs on **ALL** makes and models.

Tarzian-made tuners received one day will be repaired and shipped out the next. Allow a little more time for service on other than Tarzian-made tuners.

Tarzian offers a 12-month guarantee against defective workmanship and parts failure due to normal usage. And, compare our cost of \$9.50 and \$15 for UV combinations. There is absolutely no additional, hidden charge, for **ANY** parts except tubes. You pay shipping costs. Replacements on tuners beyond practical repair are available at low cost.

Ⓢ Tarzian-made tuners are identified by this stamping. When inquiring about service on other tuners, always give TV make, chassis and Model number. All tuners repaired on approved, open accounts. Check with your local distributor for Sarkes Tarzian replacement tuners, replacement parts, or repair service.

 **SARKES TARZIAN, INC.**  
*Bloomington, Indiana*

MANUFACTURERS OF TUNERS . . . SEMICONDUCTORS . . . AIR TRIMMERS . . . FM RADIOS . . . AM/FM RADIOS . . . AUDIO TAPE . . . BROADCAST EQUIPMENT

**ONLY**  
**\$9.50**  
**INCLUDING**

**ALL PARTS**  
(except tubes)  
**and LABOR**

**24-HOUR SERVICE**  
**1-YEAR WARRANTY**

**TWO SERVICE CENTERS  
TO SERVE YOU BETTER**

**See your distributor, or use the  
address nearest you for fast fac-  
tory repair service**

537 South Walnut St.  
Bloomington, Indiana  
Tel: 332-6055

10654 Magnolia Blvd.  
North Hollywood, Calif.  
Tel: 769-2720

# The **HIDDEN 600\*** wrote these **6 SUCCESS STORIES...** **Service Technicians supply the happy endings!**

Capacitor success stories are no novelty at Sprague. The "Hidden 600", Sprague's behind-the-scenes staff of 600 experienced researchers, have authored scores of them! And customers add new chapters every day. But none has proved more popular than the 6 best sellers shown here. Developed by the largest research organization in the capacitor industry, these 6 assure happy endings to service technicians' problems.

## 1 **DIFILM® BLACK BEAUTY® MOLDED TUBULAR CAPACITORS**



The world's most humidity-resistant molded capacitors. Dual dielectric—polyester film and special capacitor tissue—combines best features of both. Exclusive HCX® solid impregnant produces rock-hard section—nothing to leak. Tough case of non-flammable phenolic—cannot be damaged in handling.

## 2 **DIFILM® ORANGE DROP® DIPPED TUBULAR CAPACITORS**



Especially made for exact, original replacement of radial-lead tubulars. Dual dielectric combines the best features of both polyester film and special capacitor tissue. Exclusive HCX® solid impregnant—no oil to leak, no wax to drip. Double dipped in bright orange epoxy resin to beat heat and humidity.

## 3 **TWIST-LOK® ELECTROLYTIC CAPACITORS**



The most dependable capacitors of their type. Built to "take it" under torrid 185°F (85°C) temperatures—in crowded TV chassis, sizzling auto radios, portable and ac-dc table radios, radio-phono combinations, etc. Hermetically sealed in aluminum cases for exceptionally long life. Withstand high surge voltages. Ideal for high ripple selenium rectifier circuits.

## 4 **ATOM® ELECTROLYTIC CAPACITORS**



The smallest dependable electrolytics designed for 85°C operation in voltages to 450 WVDC. Small enough to fit anywhere, work anywhere. Low leakage and long shelf life. Will withstand high temperatures, high ripple currents, high surge voltages. Metal case construction with Kraft insulating sleeve.

## 5 **LITTL-LYTIC® ELECTROLYTIC CAPACITORS**



Ultra-tiny size for use in transistorized equipment. High degree of reliability at reasonable price. All-welded construction—no pressure joints to cause "open" circuits. Withstand temperatures to 85°C (185°F). Hermetically sealed. Extremely low leakage current. Designed for long shelf life—particularly important in sets used only part of the year.

## 6 **CERA-MITE® CERAMIC CAPACITORS**



Tiny, tough, dependable in practically every application. Low self-inductance of silvered flat-plate design gives improved by-pass action in TV r-f circuits. Higher self-resonant frequency than tubular ceramics or micas. Tough moisture-proof coating. Designed for 85°C operation.

\*The "Hidden 600" are Sprague's 600 experienced researchers who staff the largest research organization in the electronic component industry and who back up the efforts of some 8,500 Sprague employees in 16 plants strategically located throughout the United States.

Handy Hanging Wall Catalog C-457 gives complete service part listings. Ask your Sprague Distributor for a copy, or write Sprague Products Company, 105 Marshall Street, North Adams, Massachusetts.

**SPRAGUE®**  
 THE MARK OF RELIABILITY

**publisher**  
Howard W. Sams

**general manager**  
Mal Parks, Jr.

**editor**  
Verne M. Ray

**managing editor**  
Forest H. Belt

**asst. managing editor**  
Thomas A. Lesh

**associate editors**  
George F. Corne, Jr.  
Fred G. Biesecker

**consulting editors**  
William E. Burke  
Joe A. Groves  
C. P. Oliphant

**production manager**  
Robert N. Rippy

**circulation fulfillment**  
Fat Tidd, Mgr.  
Katherine Krise, Ass't.  
Cara La Von Willard, Ass't.

**art directors**  
Dick Lovell  
Robert W. Reed

**advertising & editorial assistants**  
Ruth E. Bastin  
Georgeanna Caldwell  
Paula Haffner  
Elie Rother

**photography**  
Paul Cornelius, Jr.

**advertising sales offices**  
John Grace, advertising sales manager

**midwestern**  
Hugh Wallace  
PF REPORTER

4300 West 62nd Street,  
Indianapolis 6, Ind.  
AXminster 1-3100

**eastern**  
Charles Horner  
Howard W. Sams & Co., Inc.  
3 West 57th Street,  
New York, N. Y.  
MUrray Hill 3-6350

**western**  
The Maurice A. Kimball Co., Inc.  
2550 Beverly Blvd., Los Angeles 57, Calif.  
DUnkirk 8-6178; and 580 Market Street,  
Room 400, San Francisco 4, Calif. EXbrook 2-3365

**Address all correspondence to**  
PF REPORTER, 4300 W. 62nd Street,  
Indianapolis 6, Indiana



# PF REPORTER

including **Electronic Servicing**

VOLUME 13, No. 3      **CONTENTS**      MARCH, 1963

<b>A Key to Test-Equipment Circuits</b>		<b>3</b>
Special 8-page Book Section— Knowing what's inside your instruments will help you make better use of them.		
<b>Letters to the Editor</b>		<b>14</b>
<b>The Electronic Scanner</b>		<b>20</b>
<b>Symfact: Video Output (Contrast Control at Plate)</b>		<b>27</b>
See what happens to voltages and waveforms when troubles occur.		
<b>Ringin' Checks for Sweep Coils</b>	<i>Allan F. Kinckiner</i>	<b>30</b>
Shop Talk—Specific directions on using a scope to test inductances.		
<b>Alignment Equipment for Stereo FM</b>	<i>Fred G. Biesecker</i>	<b>32</b>
Proper multiplex adjustments are possible only with new generators built for the purpose.		
<b>Skope Skills</b>		<b>34</b>
How's your proficiency in using the front-panel controls?		
<b>Industry Uses Unique Test Equipment</b>	<i>Joseph A. Risse</i>	<b>36</b>
Servicing Industrial Electronics—Specialized devices make complex tests at production-line speeds.		
<b>Test Equipment Guide for Shops</b>		<b>38</b>
<b>Getting More From Your Test Equipment</b>	<i>Robert G. Middleton</i>	<b>42</b>
Basic shop instruments have untapped resources you can exploit.		
<b>You Can Service Transistors With a VOM</b>	<i>George F. Corne, Jr.</i>	<b>48</b>
Current, voltage, and resistance can be measured more accurately than you may have realized.		
<b>Notes on Test Equipment</b>	<i>Forest H. Belt</i>	<b>60</b>
Lab reports on the Seco Model 250A Transistor and Tunnel Diode Tester, and on the B & K Model 850 Color Analyst.		
<b>Keeping Your Test Equipment Modern</b>	<i>Ernest Tricomi</i>	<b>74</b>
Dollar and Sense Servicing—Set up a wise policy for buying additional and replacement instruments.		
<b>The Troubleshooter</b>		<b>78</b>
<b>Product Report</b>		<b>95</b>
<b>Free Catalog &amp; Literature Service</b>		<b>98</b>
<b>Monthly Index</b>	<b>on free literature card</b>	

## ABOUT THE COVER

Test equipment is a major factor in a technician's productive capacity, and an important item in his budget; so he needs to keep posted on its availability and proper use. Therefore, we're again presenting a special issue devoted entirely to test instruments for the service shop.



Copyright © 1963 by Howard W. Sams & Co., Inc. PF REPORTER is a trademark of Howard W. Sams & Co., Inc. No part of PF REPORTER may be reproduced without written permission. No patent liability is assumed with respect to use of information herein. Acceptance of advertising does not in any manner signify the products, policies and services so advertised have been approved, endorsed or recommended by this magazine.

Subscription Prices: 1 year—\$4.00, 2 years—\$7.00, 3 years—\$9.00, in the U.S.A., its possessions and Canada.

All other foreign countries: 1 year—\$5.00, 2 years—\$9.00, 3 years—\$12.00. Single copy 35¢; back copies 50¢

Indexed in Lectrodex.  
Printed by the Waldemar Press Div.  
of Howard W. Sams & Co., Inc.



# PRODUCTS FOR MODERN LIVING



**ATR PLUG-IN TYPE PORTABLE INVERTERS\***

**MODELS**  
 6-RMF (6 volts) 60 to 80 watts. Shipping weight 12 lbs. DEALER NET PRICE \$33.00  
 12T-RME (12 volts) 90 to 125 watts. Shipping weight 12 lbs. DEALER NET PRICE \$33.00  
 \*Additional Models Available

A. C. HOUSEHOLD ELECTRICITY Anywhere in your own car, boat or plane

Operates Standard A.C.  
 • Record Players  
 • Dictating Machines  
 • Small Radios  
 • Electric Shavers  
 • Heating Pads, etc.  
 In your own car or boat!



**ATR "A" BATTERY ELIMINATOR**

For Demonstrating and Testing Auto Radios—TRANSISTOR or VIBRATOR OPERATED!

Designed for testing D.C. Electrical Apparatus on Regular A.C. Lines—Equipped with Full-Wave Dry Disc-Type Rectifier, assuring noiseless, interference-free operation and extreme long life and reliability.

**MAY ALSO BE USED AS A BATTERY CHARGER**  
 MODEL 610C-ELIF . . . 6 volts at 10 amps. or 12 volts at 6 amps. Shipping weight 22 lbs. DEALER NET PRICE \$49.95  
 MODEL 620C-ELIT . . . 6 volts at 20 amps. or 12 volts at 10 amps. Shipping weight 33 lbs. DEALER NET PRICE \$66.95

---

**AUTO-RADIO VIBRATORS**


By every test ATR Auto-Radio Vibrators are best! and feature Ceramic Stack Spacers, Instant Starting, Large Oversized Tungsten Contacts, Perforated Reed, plus Highest Precision Construction and Workmanship and Quiet Operation!

There is an ATR VIBRATOR for every make of car!

Ask your distributor for ATR's Low Priced type 1400, 6 volt 4-prong Vibrator; and 1843, 12 volt 3-prong; or 1840, 12 volt 4-prong Vibrator. **THE WORLD'S FINEST!**



---

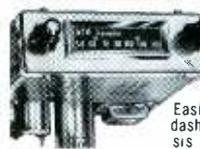

**ATR UNIVERSAL KARADIO**

**MODEL 600 SERIES**

Easily installed in-dash or under-dash. Amplifier power-supply chassis may be separated from tuner chassis for easy servicing. Utilizes 6-tube superheterodyne circuit (2 dual-purpose tubes). Supplied with separate 5" x 7" speaker. Neutral gray-tan baked enamel finish. Overall size 4" deep x 6 1/2" wide x 2" high. Tuner Chassis; with Amplifier Chassis, 2 3/8" deep x 6 1/2" wide x 3 3/8" high. Shipping weight 7 lbs. WILL OUT-PERFORM MOST SETS!

Model 612—12 Volt, Dealers Net Price \$31.96  
 Model 606—6 Volt, Dealers Net Price 31.96

Airplane Style Overhead Mounting under Cab Roof

**NO PRINTED CIRCUITRY**

---

**ATR TRUCK KARADIO**


Excellent Tone, Volume, and Sensitivity!

Compact, yet powerful. Fits all trucks, station wagons, most cars and boats. Just drill a 3/8 inch hole in roof and suspend the one-piece unit (aerial, chassis and speaker) in minutes. Watertight mounting assembly holds antenna upright. Yoke-type bracket lets you tilt radio to any angle.

Extra-sensitive radio has 6 tubes (2 double-purpose), over-size Alnico 5 PM speaker for full, rich tone. Big, easy-to-read illuminated dial. Fingertip tuning control. Volume and tone controls. 33-in. stainless steel antenna. Neutral gray-tan enameled metal cabinet. 7 x 6 1/2 x 4 in. high over-all. Shipping weight 10 1/2 lbs.

Model TR-1279—12 A for 12V Dealer Net Price \$41.96  
 Model TR-1279—6 A for 6V Dealer Net Price \$41.96

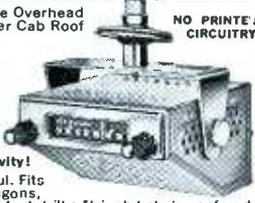See Your Electronic Parts Distributor Write Factory For Free Literature



**ATR ELECTRONICS, INC.**  
 Formerly: American Television & Radio Co.  
 Quality Products Since 1931  
 ST. PAUL 1, MINNESOTA—U.S.A.

## LETTERS TO THE EDITOR

REPORTER excellent reading and very informative. They help universally, without regard to the origin of the set. Keep those magazines coming!

CHRIS KNIGHT

Perth, Australia

*We've always wondered—being on the underside, do you ever have trouble with tubes falling out of their sockets? Seriously, we "up over" inhabitants are always pleased to hear from our counterparts living "down under."—Ed.*

Dear Editor:

I'd like to get a copy of the "Fusible-Resistor Guide" that appeared in the December, 1962 issue, without having to tear it out. I've kept all issues of PF REPORTER since January 1954; I consider them a valuable reference library. Ten of the issues have been slightly chewed by our beagle pup, but they are still usable.

JERRY BIGGER

Kansas City, Kan.

*Your pup has unmistakably fine tastes, Jerry. A reprint of the "Fusible-Resistor Guide," on durable card stock, is available free to any PF REPORTER reader who wishes to carry it in his tube caddy.—Ed.*

Dear Editor:

In sets which have the dual-diode AFC rectifiers soldered into the printed board. I make a practice of soldering the pins from old tube sockets into the board. Then, whenever I have to replace the diode later, it is a simple matter of plugging the unit in.

SAYREVILLE ELECTRONICS

Sayreville, N. J.

*This might save some time if you will be servicing the set year after year, or if you replace them quite often.—Ed.*

Dear Editor:

I'd like to see an article, with illustrations, on repairing and adjusting levers, switches, and springs on the clocks in clock radios.

FRED H. ITO

Walnut Grove, Calif.

*Just watch future issues, Fred. An article on this subject is in the works.—Ed.*

Dear Editor:

I had an interesting experience recently. I spent all morning battling a remote control unit, with little success. At noon, when I went home for lunch, my October issue of PF REPORTER had arrived; so, I looked through it while I ate. Lo and behold, in the Troubleshooter section was "Restless Remote," discussing the same chassis on which I'd been working. When I got back to the shop, I spent only minutes in locating the trouble. This is not the first time PF REPORTER has pulled me out of a sticky service situation, but it surely was the most timely.

GILBERT CLEMONS

Georgetown, Del.

*Not everyone gets instant troubleshooting for their dessert—just PF REPORTER readers. Be sure to watch our future menus.—Ed.*

Dear Editor:

I wonder if you could put a note in PF REPORTER to see if I can find a job as a TV repairman? I'm a Seventh-Day Adventist, and would have to be off every Sabbath. I'm 42, am an electronics-school graduate, and have 12 years' experience.

H. A. DODSON

202 Holly Ave.  
 Charleston Heights, S. C.

*Anyone have an opening for a southern gentleman?—Ed.*

Dear Editor:

In the article "Unusual Faults in Filament Circuits" (January, 1963), Fig. 5 shows a special method of obtaining DC filament voltage for hum-free operation. My friends and I have examined this diagram and cannot figure out how the circuit works. Would you examine it, and if the wiring is correct, please explain how it works?

LAWRENCE W. HUDSON

Flushing, N. Y.

*The schematic is correct. A detailed explanation of voltage-doubler circuits appeared in the article "Debugging B+" (September, 1962). Operation of the filament string can be understood very simply if you consider that a DC voltage (with respect to ground) appears at the junction between the two rectifiers. (Note that the AC line is not returned to ground.) Any circuit connected at this point will receive the voltage—approximately 130 volts DC—developed here. In this case, that circuit is the filament string.—Ed.*

Dear Editor:

I'd like to point out that on page 41 of the December issue, capacitor C2 in Fig. 4 is shown as a resistor. The text refers to a capacitor. Which is correct?

HENRY GONDER

West Hollywood, Fla.

*The text has it stated correctly. Capacitor C2 across the ringing coil was inadvertently drawn as a resistor.—Ed.*

Dear Editor:

Thought it's about time I put in a few words from "down under." Having serviced sets in England, Europe, and Australia. I've come to the conclusion we have the same troubles as you encounter in the U.S.A. I find the articles in PF



**TUBE TESTER 88, \$69.50 NET**—locates all tube faults quickly, accurately with patented Seco grid circuit test that checks tubes 11 ways—also cathode emission test.  
**DELUXE POWER SUPPLY RPS-5, \$69.50 NET**—transistorized zener-regulated circuit maintains constant voltage over wide load fluctuation without overshoot—up to 30 V DC and 150 ma.  
**REGULATED TRANSISTORIZED SUPPLY RPS-2, \$26.95 NET**—constant voltage—adjustable 0-25 V. Bias tap—0-100 ma.

**TRANSMITTER TESTER 510B, \$48.95 NET**—reads both positive and negative modulation peaks on 0-120% scale—also RF output in 0-5 watts and 0-400 ma. For Handy-Talkies too!  
**REGULATED TRANSISTORIZED SUPPLY RPS-4, \$36.95 NET**—constant voltage—meter ranges 0-1.5, 0-15 and 0-30 V DC—reads load in 0-30 and 0-150 ma. Taps for simultaneous biasing.

**TRANSISTOR AND TUNNEL DIODE ANALYZER 250, \$74.50 NET**—complete transistor lab in one compact unit—even has VOM! Analyzes semi-conductors in or out of circuit—no set-up data needed.  
**ANTENNA TESTER 520A, \$49.95 NET**—reads Forward Power and Reflected Power directly in watts! Antenna efficiency reads in: SWR from 1:1 to 8:1, per cent, or GOOD-POOR. For 50 ohm coax.

## New Look in Test Equipment



The look is bold, professional, functional. Handsome black cases, lustrous brushed aluminum panels, wide easy-to-read meters—"matched set" appearance and quality. It comes to you now from Seco. See the "New Look" display of Seco test equipment at your electronic distributor's and at the May Parts Show in Chicago. Look for the red velvet!

**SECO ELECTRONICS, INC.**

1221 South Clover Drive,  
 Minneapolis 20, Minnesota  
 Subsidiary of Di-Acro Corpora-  
 tion, Lake City, Minnesota

Be  
a hero  
at home



**GET G-E APPLIANCES WITH THE PURCHASE OF G-E RECEIVING TUBES**

Your G-E Receiving Tube Distributor is giving away goodies for the home with the purchase of G-E tubes. You can get General Electric Appliances . . . Automatic Toasters, Can Openers, Coffeemakers, Toothbrushes . . . designed to make you a hero with the whole family.



**AUTOMATIC TOOTHBRUSH**

Most effective toothbrush ever designed, and even children will like to use it. Kit includes cordless handle, four personal snap-in brushes and automatic recharging holder. When you buy G-E tubes, ask for ETR-3536.



**AUTOMATIC CAN OPENER**

Opens cans in a jiffy without cranking and twisting. Safe and easy to use . . . no sharp edges. Magnet automatically removes the cutout lid. Mounts on wall in seconds. Yours with the purchase of G-E tubes. Ask for ETR-3537.



**AUTOMATIC COFFEEMAKER**

Makes 3 to 9 delicious cups of coffee. No watching or timing necessary. Just put in the coffee and water, set the control for strength and the coffeemaker does the rest. Take it home with your G-E tubes. Ask for ETR-3538.



**AUTOMATIC REFLECTOR TOASTER**

Toasts both sides at once by reflected heat. Any kind of bread will fit . . . so will frozen waffles, pancakes, cheese sandwiches. Shuts itself off automatically. You can get it with the purchase of G-E tubes. Ask for ETR-3539.

Another accent on value from G-E **ELECTRONICS** Distributors

OR  
 be your own  
 [sneaky] hero  
 down at the  
 shop

**GET A GENERAL ELECTRIC PLASTIC  
 TOOL CASE**

Your G-E Distributor will (quietly) slip you one of these handy tool cases made of high-impact polystyrene that resists oil, grease, battery acid . . . won't warp, rust or rot. Lids overlap the base to shed water. Equipped with 2 and 3-tier cantilever trays. Red-orange and grey in three sizes.



**ETR-3517 . . .** Size 18¼" x 9½" x 9½". Yours with the purchase of G-E tubes



**ETR-3280 . . .**  
 Size 15¾" x 8" x 8¼"  
 Get it with G-E tubes



**ETR-3516 . . .**  
 Size 14" x 6" x 5½"  
 Buy G-E tubes and it's yours


*Progress Is Our Most Important Product*

**GENERAL  ELECTRIC**



This program is available at the option of your local distributor.

## BUSS Sub-Miniature PIGTAIL TRON FUSES

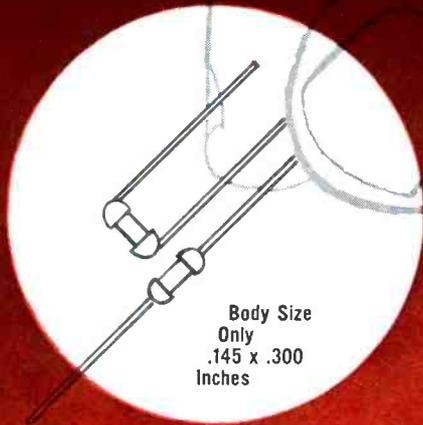

Body Size  
Only  
.145 x .300  
Inches


Tron fuses are so small they can be used as an integral part of circuit—to protect miniaturized devices—or gigantic multi-circuit electronic devices, without sacrifice of space.

They are hermetically sealed for potting without danger of sealing material affecting operation and have high resistance to shock or vibration. Operate without exterior venting. May be teamed with other components in replaceable unit.
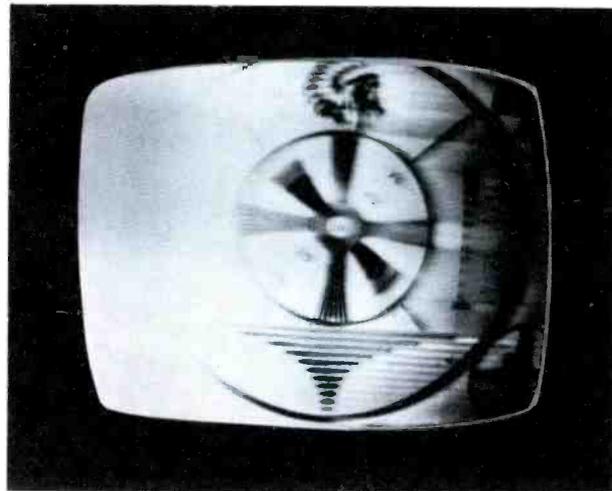
# BUSS

Write for BUSS  
Bulletin SFB.


BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis 7, Mo.



Extreme smearing and apparent overloading are strong clues to the nature of this fault, pointing to a video or IF-stage trouble. The symptoms appear considerably different from those of AGC overload, so you can discount the possibility of the defect being in an AGC-controlled stage. The "whited-out" half of the screen is characteristic of IF regeneration or oscillation, and the ringing points to a stage near the video detector. (A hand brought near the tube in the faulty stage determined positively which one it was. One voltage measurement revealed a bias resistor which had increased considerably in value.)

—From Howard W. Sams "Photofact Guide to TV Troubles"

## BUSS : the complete line of fuses ...

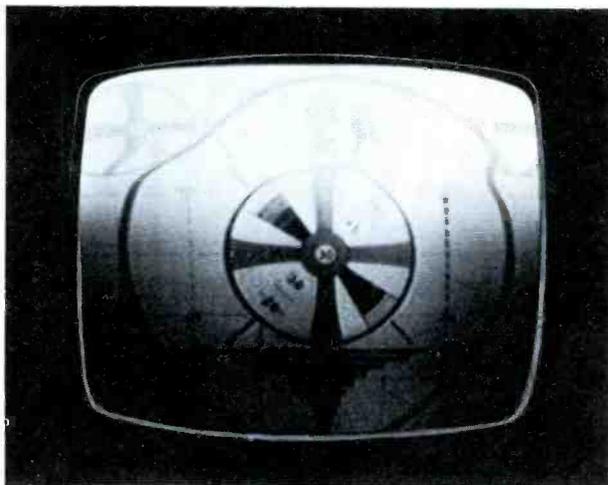

Here's a condition which, on first glance, could indicate trouble in any of several stages. The most prominent symptom is the horizontal pulling at the top. However, look more closely: Poor interlace indicates that the fault is also affecting vertical sync to some extent. A 60-cps hum mingled with some snow in the picture indicates the trouble is probably connected in some way with the earlier stages of the receiver—because the high gain of these circuits tends to magnify even slight faults. (The trouble was traced to an open resistor connecting the AGC line to the grid of the first IF tube.)

—From Howard W. Sams "Photofact Guide to TV Troubles"

## Let BUSS Fuses Help Protect Your PROFITS

To make sure BUSS fuses will operate as intended under all service conditions, each and every BUSS fuse is individually tested in a sensitive electronic device.

This is your assurance that when you sell or install BUSS fuses, you are safeguarded against complaints, call-backs and adjustments that might result from faulty fuses and eat away your profit.


It is just good business  
to sell fuses the BUSS way.

# BUSS

Write for BUSS  
Bulletin SFB.

BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis 7, Mo.
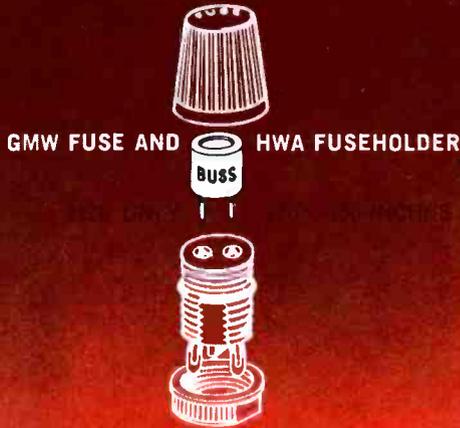
## BUSS Sub-Miniature FUSE-HOLDER COMBINATION



A light weight, protective device for space-tight applications in multiple circuit apparatus. Fuse has transparent window for visual inspection of element. Fuse may be mounted alone or used in holder on printed circuit boards.

HWA holder can also be panel mounted with or without use of knob. Knob makes holder water proof for front of panel.

# BUSS

For full details write for BUSS bulletin SFB


BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis 7, Mo.



This symptom offers a number of clues which can help pinpoint the location of the faulty component. For example, heavy snow means the front-end circuits must be amplifying; indeed, the sparkle and the heavy, coarse snow are indicative of operation at full gain, as when AGC bias is lost. In this set, only the first IF and the RF amplifier are AGC-controlled. The slight ringing helps eliminate the RF amplifier from suspicion, since this symptom is seldom caused by this section. Thus, the field is narrowed down to the first IF stage. (The trouble was a shorted capacitor in the grid circuit, altering AGC voltage and stage tuning.)

—From Howard W. Sams "Photofact Guide to TV Troubles"


.... of unquestioned high quality

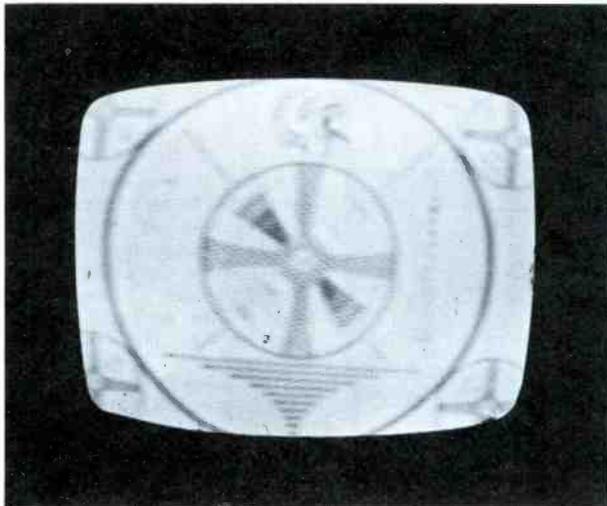

This picture is faded and washed out, but not snowy—indicating considerably reduced gain in the video amplifier or in one of the later IF stages. (Snow is missing because the faulty stage is not amplifying noise developed in the front end.) The video in the background, even though washed out, shows noticeable variations in shading instead of a dull, flat tone; this fact points more conclusively to a middle- or last-IF fault than to trouble after the video detector. (Voltage measurements on the second and third IF stages revealed a plate-supply resistor greatly increased in value.)

—From Howard W. Sams "Photofact Guide to TV Troubles"
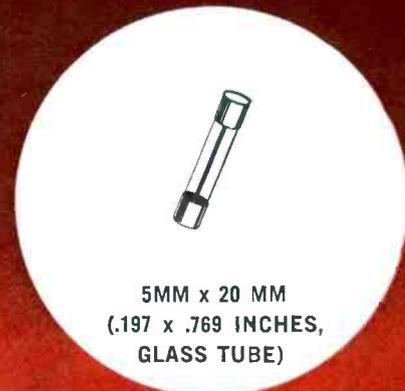
## BUSS MINIATURE FUSES Made To Foreign Standards



5MM x 20 MM  
(.197 x .769 INCHES,  
GLASS TUBE)

Designed for protection of miniaturized circuits or equipment. Commonly used in equipment of foreign make.


# BUSS

Write for BUSS  
Bulletin SFB.


BUSSMANN MFG. DIVISION, McGraw-Edison Co., St. Louis 7, Mo.
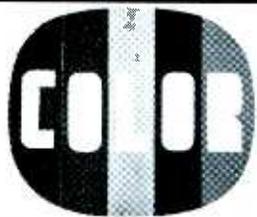
# 4 ways to increase your income

RCA Institutes, Inc. offers these four comprehensive home study courses especially designed to help build your income immediately!



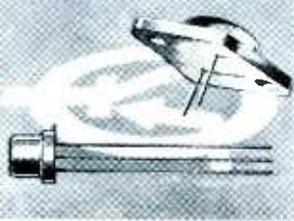**COLOR TV** Add Color TV Servicing to your skills with this up-to-the-minute home training course and take advantage of the growing profit potential in this area! Train under the direction of RCA...experts in Color TV.



**TRANSISTORS** You get the necessary background for semiconductor technology including characteristics of tunnel diodes, rectifiers and other solid state devices. Transistor trainer also available.



**AUTOMATION ELECTRONICS** Trains you for the many applications of automation electronics in industry and government including Photoelectronics, Digital Computer Techniques, Synchros and Servomechanisms, Automatic Control Systems, and many more!



**MOBILE COMMUNICATIONS** Trains you to service and maintain 2-way radio communications on land, sea, and air! Gives you the technical foundation for space communications!

Take advantage of RCA's Liberal Tuition Plan. You only pay for lessons you order; and have no long-term obligations. Licensed by New York State Education Department. Approved for Veterans.

## RCA INSTITUTES, INC.

A Service of Radio Corporation of America  
350 West Fourth Street, New York 14, N. Y.



The Most Trusted Name in Electronics

SEND THIS COUPON NOW FOR COMPLETE FREE INFORMATION

RCA INSTITUTES, INC. Home Study School, Dept. PF-33  
350 West Fourth Street, N. Y. 14, N. Y.


Without obligation, rush me free information on the following RCA Home Training Course: COLOR TV TRANSISTORS MOBILE COMMUNICATIONS AUTOMATION ELECTRONICS

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

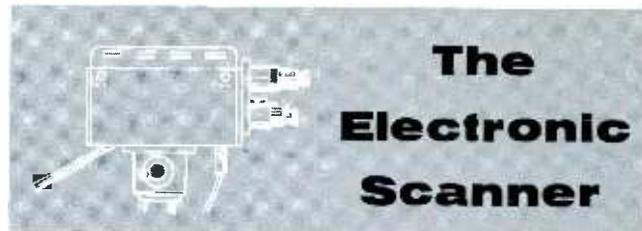**CANADIANS**—Take advantage of these same RCA courses at no additional cost. No postage. No customs. No delay. Send coupon to: RCA Victor Company, Ltd., 5581 Royalmount Ave., Montreal 9, Quebec.



## The Electronic Scanner

### Visual Call System



Depicted in the photo is one of two new "Videocentri" CCTV systems now being manufactured by Industrial TV Utilities. This system, primarily for use in apartment buildings, includes a master 8" monitor screen in the lobby and a private monitor screen in each individual apartment. When a visitor enters the lobby to call on a tenant, he presses the appropriate call button; the apartment monitor then shows a picture of the visitor. If desired, conversation between the two parties can be held through the audio system. To prevent tenant "snooping," the apartment monitor cannot be set to view the lobby area without a call-button signal from the lobby. A similar system for commercial and industrial applications is also available. Both types of systems are being marketed through service dealers.

### Novar Production

Sylvania's tube division has begun manufacturing a number of novar receiving tubes for use in television receivers. Included are: 6GJ5, 12GJ5, 6GT5, 12GT5, 17GT5, and 6JB6—all horizontal output amplifiers; 6BH3, 17BH3, 22BH3, 6DW4, and 17BS3—dampers; and 5BC3—a low-voltage rectifier. Sylvania is developing additional novar types for future release.

### Long Live the King



Mr. A. A. Ward, president of Altec Lansing, and Mr. H. S. Morris, vice president of the firm, are shown congratulating Milton G. Thomas, Southeastern Regional Sales Manager, on his winning a recent nationwide sales campaign. The mock coronation ceremony, proclaiming Mr. Thomas "King Mike I," highlighted the company's recent annual sales meeting held at the Riviera Hotel, Palm Springs, California.

### Fishin' Time's A-Comin'



A free fishing rod or reel is being offered by Permactel with the purchase of 288 rolls of plastic electrical tape. The purchaser has a choice of either a Wright-McGill "Grainger" spinning rod or a Garcia-Mitchell spinning reel. The offer, which expires April 15, 1963, applies to the purchase of 29D, 29L, 295D, or 295L plastic tapes.


### Instant Credit

Mr. Harry R. Ashley, president of EICO Electronic Instrument Co., Inc., recently announced his firm has joined the "Uni-card" Credit Plan. Now, any Uni-card holder can purchase EICO electronic equipment—hi-fi and test instruments, for example—from any authorized EICO dealer, without a down payment.
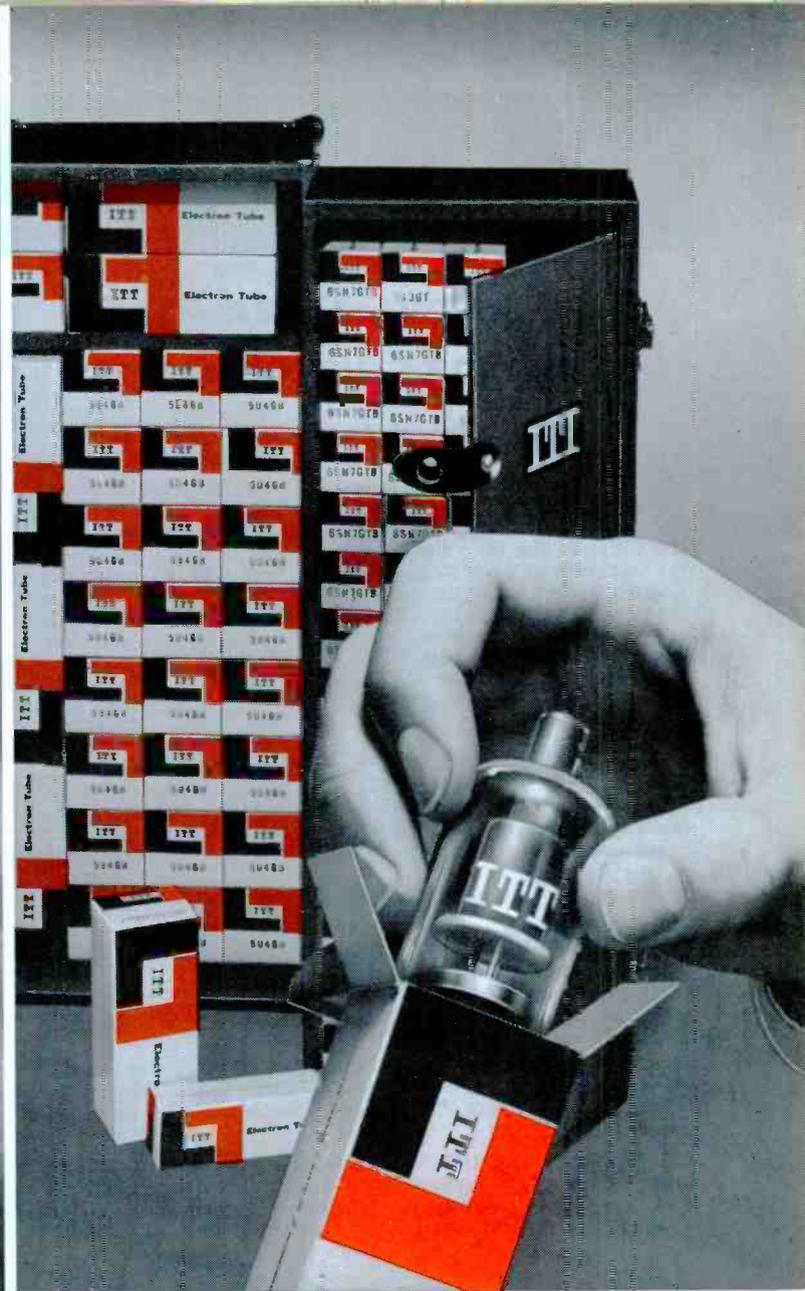
### Go-Togethers



Service technicians will find, for a limited time, a free 3-oz. (caddy-size) can of "Trol-Aid" packaged with every large, economy-size can of "Tun-O-Lube" tuner cleaner. Chemtronics, manufacturer of these products, is offering the special purchase to acquaint technicians with the new 16-oz. can of "Tun-O-Lube."



## ITT batteries...and ITT tubes...give you first-line quality ...and extra profit margin

ITT batteries—penlites, C, D, and 9-volt miniatures — now offer the same “extra value” and acceptance already experienced with fast-moving ITT Receiving Tubes.

ITT can provide this “extra value” of finest quality at higher profit margins in each of its lines because ITT products are on call from 154 factories and laboratories in 24 countries. If you are selling ITT tubes and batteries, you can compete with anyone in the world

... on quality, on price, and on acceptance. Brands without these worldwide resources are finding it tougher than ever.

Make sure *you* have this *value* leadership in *your* service market. Stock ITT tubes and batteries—the only worldwide lines with such a world-famous name.

ITT Distributor Products Division, International Telephone and Telegraph Corporation, Box 99, Lodi, New Jersey.

# SENCORE

## SIMPLIFIES COLOR SERVICING

### NEW! CA122

### COLOR CIRCUIT ANALYZER

A simple approach to a complex problem

Here is an instrument that is designed to eliminate the guesswork in color TV servicing. A complete analyzer that provides all required test patterns and signals for testing from the tuner to the tri-color tube. Additional analyzing signals for injection at each stage including audio, video and sync, brings to life a truly portable and practical TV analyzer for on the spot service; virtually obsoleting other analyzers with the advent of color. Sencore's simplified approach requires no knowledge of I, Q, R-Y, B-Y, G-Y or other hard to remember formulas. The CA122 generates every signal normally received from the TV station plus convergence and color test patterns.

The CA122 offers more for less money:

**TEN STANDARD COLOR BARS:** The type and phase that is fast becoming the standard of the industry. Crystal controlled keyed bars, (RCA type) as explained in most service literature, offer a complete gamut of colors for every color circuit test.

**WHITE DOTS:** New stabilized dots, a must for convergence, are created by new Sencore counting circuits.

**CROSS HATCH PATTERN:** A basic requirement for fast CRT convergence.

**VERTICAL AND HORIZONTAL BARS:** An added feature to speed up convergence, not found on many other color generators.

**SHADING BARS:** Determines the ability of the video amplifier to produce shades (Y Signal) and to make color temperature adjustments. An important feature missing on other generators.

**COLOR GUN INTERRUPTOR:** For fast purity and convergence checks without upsetting color controls. Insures proper operation of tri-color guns, preventing wasted time in trouble shooting circuits when CRT is at fault.



A must for color . . .

a money maker for black and white TV servicing

**ANALYZING SIGNALS:** RF and IF signals modulated with any of the above patterns for injection into grid circuits from antenna to detector. IF attenuator is pre-set for minimum signal for each IF stage to produce pattern on CRT thus providing a check on individual stage gain. Sync and video, plus or minus from 0 to 30 volts peak to peak, have separate peak to peak calibrated controls for quick checks on all video and sync circuits. Crystal controlled 4.5 mc and 900 cycles audio simplify trouble shooting of audio circuits.

**NEW ILLUMINATED PATTERN INDICATOR:** A Sencore first, offering a rotating color film that exhibits the actual color patterns as they appear on color TV receivers. Locks in with pattern selector control.

You'll pay more for other color generators only.

Dealer Net . . . . . **187.50**

### NEW! PS120 PROFESSIONAL WIDE BAND OSCILLOSCOPE

A portable wide band 3 inch oscilloscope for fast, on-the-spot testing. An all new simplified design brings new meaning to the word portability . . . it's as easy to operate and carry as a VTVM. Though compact in size, the PS120 is powerful in performance: Vertical amplifier frequency response of 4 MC flat, only 3 DB down at 7.5 MC and usable to 12 MC, equips the technician for every color servicing job and the engineer with a scope for field and production line testing. AC coupled, with a low frequency response of 20 cycles insure accurate low frequency measurements without vertical bounce. Sensitive single band vertical amplifier; sensitivity of .035 volts RMS for one inch deflection saves band switching and guessing. Horizontal sweep frequency range of 15 cycles to 150 KC and sync range from 15 cycles to 8 MC (usable to 12 MC) results in positive "locking" on all signals. New exclusive Sencore features are direct reading peak-to-peak volts — no interpretation; dual controls to simplify tuning; lead compartment to conceal test leads, jacks and seldom used switches. Rear tilt adjustment angles scope "just right" for easy viewing on bench or production line.

Size: 7" w x 9"h x 11 1/4" d. Weight: 12 lbs.

Dealer Net . . . . . **124.50**  
(with low cap. probe)

Kit . . . . . **74.50**



A must for servicing color TV in the home . . . lowest priced broad band scope. All hand wired — all American made

# SENCORE

SIMPLIFIES SWEEP CIRCUIT TROUBLE SHOOTING

## SS117 SWEEP CIRCUIT ANALYZER For Color and Monochrome Testing

A professional trouble shooter that helps you methodically walk the trouble out of "tough-dog" sweep circuits in monochrome and color receivers. The SS117 provides a positive but simple push button test on all circuits indicated in the block diagrams. These time-consuming circuits are checked step-by-step with tried and proven signal injection and substitution methods. All checks can be made from the top of the chassis or from under the chassis when it is removed from the cabinet.

TV horizontal oscillator check is made by substituting a universal oscillator known to be good. Horizontal output check consists of a cathode current and screen voltage test. The TV horizontal yoke is checked by substituting a universal yoke from the SS117 and viewing brightness or restoration of 2nd anode voltage. Horizontal flyback is checked dynamically in circuit by measuring the power transfer to the yoke when TV is turned on. TV horizontal sync can be used to control the SS117 horizontal oscillator, providing a positive check on sync from the video amplifier to the TV oscillator. Vertical circuits are tested by simple signal injection from vertical yoke to oscillator for full height on CRT. The SS117 with the CA122 Color Analyzer provides a complete TV analyzer for virtually every stage in monochrome or color receivers.


External checks for AC, DC, peak to peak voltage readings and DC current in the upper right hand corner save using a separate VTVM. Accurate 2nd anode measurements up to 30,000 volts are made with a sensitive 300 microamp meter and the attached high voltage probe. AC outlets, all steel construction and mirror in the cover makes every servicing job easier.

Size: 10 1/4" x 9 1/4" x 3 1/2". Wt. 10 lbs.

Dealer Net. . . . . 89.50



The SS117 checks them all

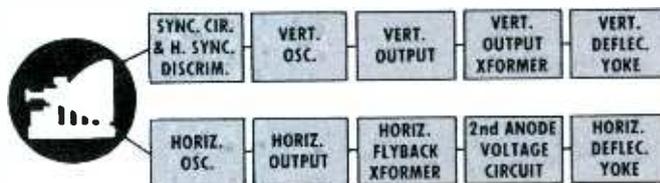

FREE—A 33 RPM half hour permanent record packed with every unit explains each test.

## FOR FASTER MORE ACCURATE TUBE TESTING TC114 MIGHTY MITE TUBE CHECKER

This is the famous Mighty Mite, acclaimed by over 25,000 servicemen, maintenance men and engineers as "the best they've ever used." A complete tube tester that is smaller than a portable typewriter yet finds tubes that testers costing hundreds of dollars miss, thus selling more tubes and reducing call backs. A real money maker for the serviceman and a trusty companion for engineers, maintenance men and experimenters. The Mighty Mite has been acclaimed from coast to coast as the real answer for the man on the go. Even though the Mighty Mite weighs less than 8 pounds, new circuitry by Sencore enables you to use a meter to check grid leakage as high as 100 megohms and gas conditions that cause as little as one half microamp of grid current to flow. Thus, too, it checks for cathode current at operating levels and shorts or leakage up to 120,000 ohms between all elements. And it does all this by merely setting four controls labeled A, B, C, & D with new type easy grip knobs. Check these plus Sencore features... Meter glows in dark for easy reading behind TV set... The new Mighty Mite has large size Speedy-Setup Tube Chart inside of cover—cuts setup time for even faster servicing. New stick proof D' Arsonval meter will not burn out even with shorted tube... Rugged, all steel carrying case and easy grip handle.

The improved Mighty Mite will test virtually every radio and TV tube that you encounter, nearly 2000 in all, including foreign, five star, auto radio tubes plus the new Compactrons, Novars, Nuvistors and 10 pin tubes. Has larger, easy-to-read type set-up booklet for faster testing.

Size: 10 1/4" x 9 1/4" x 3 1/2". Weight: 8 lbs.

Dealer Net. . . . . 74.50

## TM116 TUBE TESTER MODERNIZING PANEL

New tube adapter for testing Compactrons, Novars, Nuvistors and 10 pin tubes in any tube tester except cardomatic types. Plugs into octal socket of your tube tester enabling you to test these new tubes in the same manner

Fast, Accurate . . .  
never lets  
you down

A must for color

that your tester checks  
conventional tubes. Tube set-up  
chart included with each adapter.  
Dealer Net. . . . . 24.95





## WHAT ELSE DOES PHILCO PUT IN THE CARTON?

When you pick up the box, you expect to find a receiving or CR tube in it. Naturally.

But when the name PHILCO is on the carton, you get something more . . . at no extra cost to you. In every Philco carton there is an important extra . . . a bonus that you can't see but is even more valuable to you!

What is it? . . . it's *A SATISFIED CUSTOMER!*

The name "Philco" has enjoyed prestige and respect in parts and accessories for over 33 years. Now, it has added resources and stability with another famous name . . . "Ford". Together they stand for products that assure your confidence and dependability . . . now, even more than ever before.

When you use Philco tubes, your customer knows you are delivering the best.

**Use the Tubes That Mean "Satisfied Customers"**

**PHILCO Star Bright 20/20 Picture Tubes and PHILCO Receiving Tubes**

A complete line of all types for all makes and models of television and radio receivers, manufactured under exacting quality standards, thoroughly tested and inspected.



**DEPEND ON YOUR  
PHILCO DISTRIBUTOR . . .**

your one-stop-shopping center for quality picture tubes and receiving tubes for Philco or ANY OTHER MAKE.

**PARTS & SERVICE OPERATIONS**

**PHILCO**<sup>®</sup>

A SUBSIDIARY OF *Ford Motor Company*

Exquisite Collection  
of Fabulous



**LANVIN**  
PARIS PERFUMES

- Arpege
- My Sin
- Scandal

Here is a sweetheart gift that does double duty. Three famous Lanvin fragrances packaged expressly for Philco. The deluxe hinged lid package doubles as an attractive jewel box after the perfumes have been used.

Your Complimentary Gift with the purchase of **99** Philco Receiving Tubes\*




AD-4093

ARPEGE

MY SIN

SCANDAL

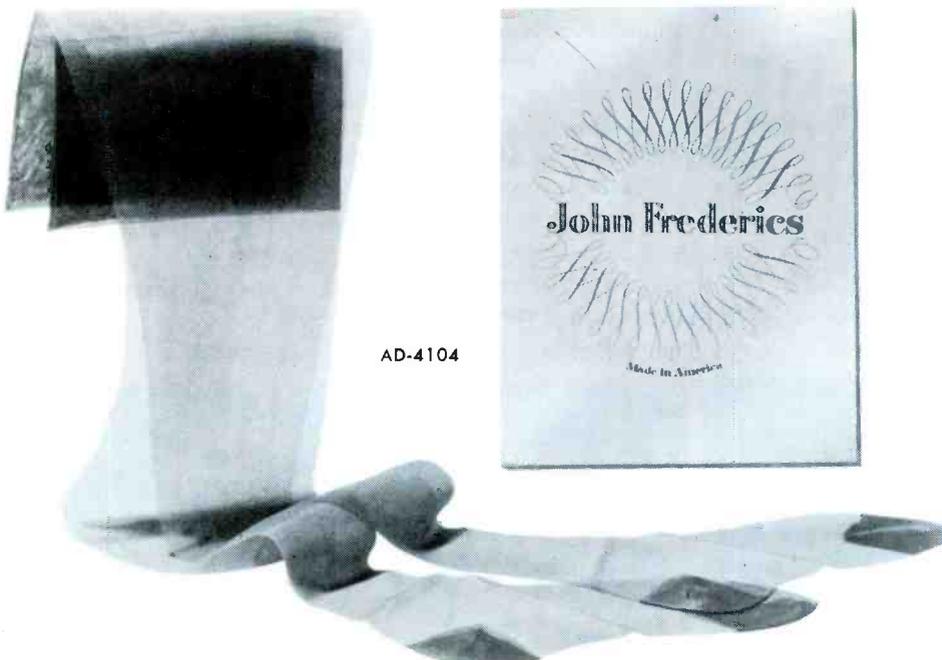**Gifts from your Philco Distributor  
for all of YOUR Own GIFT Occasions**



AD-4104

**Famous  
John Frederics  
Seamless Runless  
Hosiery—3 Pairs**

Fine, ultra sheer nylon hosiery that WILL NOT RUN UNDER NORMAL WEAR. Regular \$4.95 value. Nationally-famous JOHN FREDERICS brand that every woman recognizes. Latest fashion shade, all sizes. Packaged 3 pairs to a box.

Your Complimentary Gift with the purchase of **66** Philco Receiving Tubes\*

\*Or any Combination of CR Tubes and Receiving Tubes. One Philco Star Bright 20/20 CR Tube equivalent to 25 Receiving Tubes.

**DON'T DELAY—See Your Philco Distributor Today—Offer Limited!**

# DESIGNED FOR COLOR TV

## WINEGARD COLORTRON ANTENNAS

4 gold anodized models from \$24<sup>95</sup>

\*Pat. Nos. U.S. 2,700,105; 2,955,289 • Canada 511,984 • Others Pending.

### AVAILABLE WITH REVOLUTIONARY NUVISTOR COLORTRON AMPLIFIER...



Now, through continuous Winegard research, a new, improved Electro-Lens yagi has been developed—the New WINEGARD COLORTRON—PERFECT ANTENNA FOR COLOR TV!

Colortrons have a flat frequency response (plus or minus ½ DB across any 6 MC channel), no “suck-outs” or “roll-off” on end of bands . . . accurate 300 ohm match (VSWR 1.5 to 1 or better) . . . unilobe directivity for maximum ghost and interference rejection. They deliver today’s finest color reception, give a new picture quality to black and white. Colortrons are the only outside antennas that carry a WRITTEN FACTORY GUARANTEE OF PERFORMANCE.

And Colortrons are built to last. High tensile aluminum tubing for rigidity and stability, insulators with triple moisture barrier, GOLD ANODIZED for complete corrosion-proofing.

There are 4 Colortron models to cover every reception need, from suburbs to distant fringe areas . . . \$24.95 to \$64.95 list.

New Winegard Colortron twin-nuvistor amplifier perfectly matches Colortron antennas. Gives added gain and sensitivity on both color and black and white. Ultra-low noise, high

gain Colortron Nuvistor Amplifier can easily drive 6 or more TV sets.

With revolutionary twin-nuvistor circuit, Colortron amplifiers can handle up to 400,000 micro-volts of signal without overloading. *This is 20 times better than any single transistor amplifier.* The Colortron Amplifier will bring the weakest signals up out of the snow, yet strong local TV & FM signals will not overload it. A special life saver circuit gives the two nuvistors a life of 5 to 8 years.

This amplifier is completely trouble free and the finest performing antenna amplifier you can own.

Completely weather sealed, nothing is exposed to corrode and cause trouble . . . has all AC power supply with 2 set coupler. (Model No. AP-220N, \$39.95 list). Twin transistor model also available up to 80,000 micro-volts input. *New type circuit protects transistor from static electricity built up in lightning flashes.* (Model No. AP-220T, \$39.95 list).


Colortron Amplifier can be added to any good TV antenna for sharper, clearer TV reception.

Ask your distributor or write for technical bulletin.

World's most powerful TV antenna




MODEL C-44  
GOLD ANODIZED \$64.95

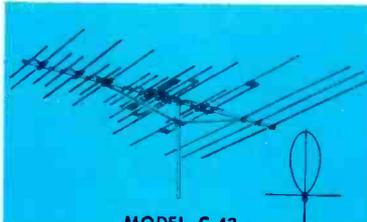

MODEL C-43  
GOLD ANODIZED \$51.90



MODEL C-42  
GOLD ANODIZED \$34.95

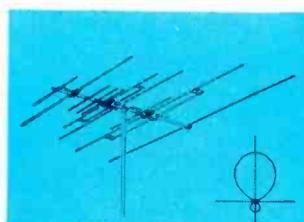

MODEL C-41  
GOLD ANODIZED \$24.95








# Winegard

There's an extra bonus of quality and performance in every Winegard product.  
ANTENNA SYSTEMS

3009-3A Kirkwood • Burlington, Iowa



Contrast Control at Plate

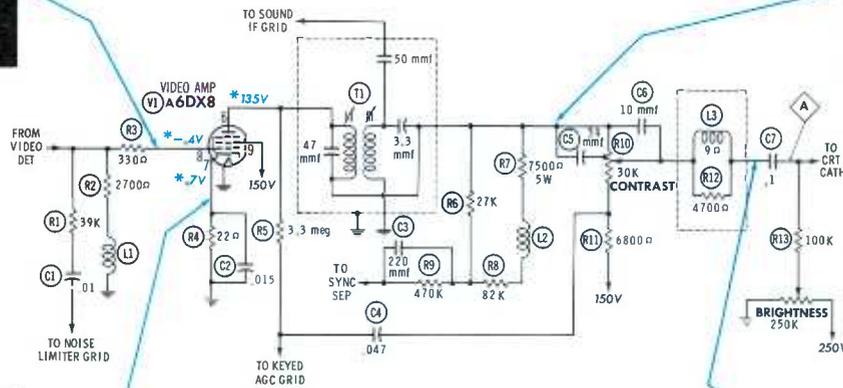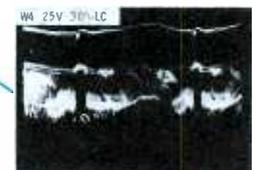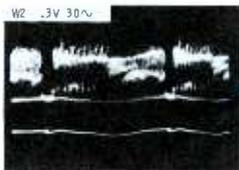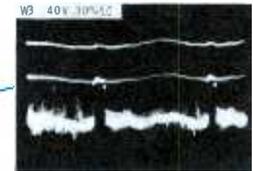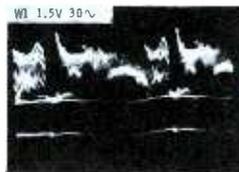

DC VOLTAGES taken with VTVM, on inactive channel; antenna terminals shorted. \* Means voltage varies with conditions — see "Variations."

WAVEFORMS taken with wide-band scope; controls set for 25-volt p-p video to CRT. Low-cap probe (LC) used where direct probe distorts signal.

### Normal Operation

Pentode section of 6DX8 functions in single video output stage. Detector load is DC-coupled to grid circuit, and input signal determines grid bias of V1A. Type of circuit shown here has constant gain regardless of contrast-control setting. Control doesn't change operating voltages on tube; it merely taps off wanted amount of signal to be fed to CRT cathode. (Principle of operation is similar to that of many volume-control circuits.) Plate circuit of V1A has three different parallel paths to B+ voltage sources: R7-L2 in series, R6-R8 in series, and R10-R11 in series. As a result, plate voltage is little affected by any one open component. Sync signal to separator is taken off via voltage divider (R6-R8) in plate circuit. AGC takeoff is from two different points; R5 provides a DC voltage for keying-tube grid, while a video signal for this grid is coupled via C4. Correct operation of AGC is dependent on both these inputs; therefore, almost all troubles in video output stage will upset AGC action to some degree. As a result, bias on AGC-controlled stages may be upset enough to create RF-IF signal distortion that aggravates trouble symptoms.

### Operating Variations

**PIN 6** With station signal present, voltage increases from 135 to 145 volts. Adjusting AGC control for more gain through front-end stages causes proportional increase in W3 amplitude; DC plate voltage also increases, since average conduction of V1A is reduced.

**PIN 7** Very little change in DC voltage results from applying signal or adjusting contrast control.

**PIN 8** DC voltage shifts from -.4 volts to -1 volt when signal is present; remains close to this value at all moderate or strong input-signal levels. Rotating AGC control causes larger shift in voltage here; maximum setting without overload is -3 volts, and minimum (which results in weak picture and unstable sync) is -.1 volt.




CRT used in this set is a "low-drive" type; 25-volt video signal applied to cathode is sufficient for normal contrast. W4 amplitude varies from 8 to 40 volts with adjustment of contrast control.

### SYMPTOM 1

## Insufficient Video

No Snow;  
Normal Sound

**R11 Open**

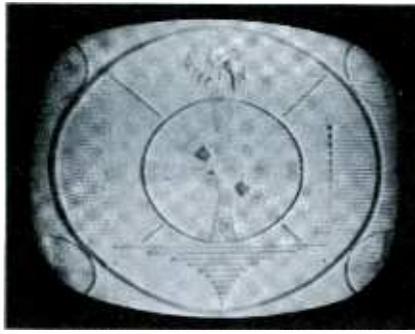


### Symptom Analysis


Picture has “washed-out” appearance. Absence of snow, and good sound, suggest front-end stages are probably not at fault. Contrast adjustment causes only minor change in picture; AGC control is operative, but adjustment doesn’t clear trouble. Overload doesn’t occur as usual at maximum setting.



Waveform Analysis

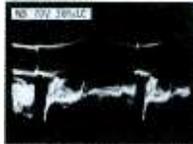

Voltage and Component Analysis

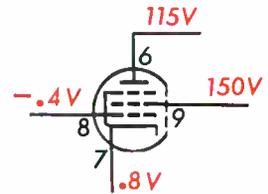

W1 is lower in amplitude than normal—only .8 volts at an AGC setting that would normally yield 1.5 volts—but it is passing through front end without distortion. W3 is also properly shaped, but measures 20 volts (a 50% drop from normal). W4 offers good clue to trouble spot, for its amplitude won’t change with contrast adjustment. However, a slight change in frequency response does occur when control is set to minimum. These indications call for further checking in and around contrast-control circuit.

Biggest clue to trouble is plate voltage. With R11 open, one of parallel B+ paths to plate of V1A is broken, and plate voltage drops to 115 volts. Voltages on grid and cathode stay within normal limits. DC-voltage decrease is passed to AGC grid via R5, but signal input to same point via C4 increases because open R11 prevents voltage division. Net result is that AGC circuit receives false impression of strong station signal, and overbiases RF-IF stages. If C4 or bottom of R10 were to open, AGC would cut off front end.

### SYMPTOM 2

## Overloaded Video

Buzz in Sound

**R7 Open**



### Symptom Analysis


Problem looks like typical AGC overload trouble, with picture tearing, and loud buzz in sound. Adjusting contrast control for lower video-signal input to CRT cathode changes contrast of picture on screen only slightly. Rotating AGC control to its minimum position will affect picture, but won’t cure fault.



Waveform Analysis



Voltage and Component Analysis

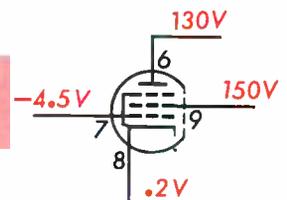

Excessive (10-volt) amplitude of W1 is big clue that RF-IF stages are running at high gain. Undistorted shape of this waveform, coupled with fact the AGC control is operative, is a clue that trouble isn’t caused by AGC circuit alone. W3 is much too high in amplitude, shows compressed sync pulses, and thus ties trouble to video amplifier. Gain of stage has actually decreased—grid signal is amplified 15 times, rather than normal 25 or 30 times. Excessive RF-IF gain is consequence of defective signal fed to AGC system.


High negative voltage on grid of V1A is due to excessive signal amplitude; W1 is so strong that negative peaks drive V1A into cutoff, accounting for flattened positive peaks of W3. With high average bias, tube presents abnormally high resistance from plate to ground. Since lowest-resistance branch of plate load is open, total plate-to-source resistance is also higher than normal. Ratio between these resistances stays nearly constant; thus, plate voltage is deceptively close to normal. High-wattage R7 is among first suspects.

**SYMPTOM 3**

**No Video**

No Audio;  
No Snow

**R4 Open**

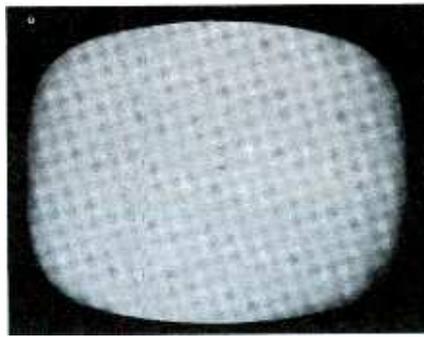


**Symptom Analysis**


Raster is present, but no video or audio. Slight buzz can be heard in sound at high volume setting. Rotation of AGC control to maximum position reveals weak, garbled station audio and increased buzz; this proves tuner oscillator is working. Weak audio could be capacitively coupled through dead video stage.



**Waveform Analysis**

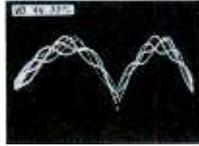

**Voltage and Component Analysis**

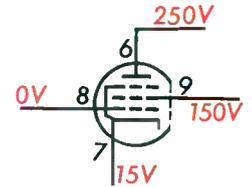

No video, but only random circuit noise, is present in W1 and W3. Trouble could be caused by defect in AGC circuit cutting off RF and IF stages. Clamping AGC fails to produce picture on CRT; but causes normal W1 to appear at grid of V1A, proving fault involves AGC, and indicating a check on the video amplifier is in order. Injection of signal to grid of V1A fails to give any indication on CRT screen. This case demonstrates that trouble is difficult to isolate to video stage without taking AGC into account.


Full 250-volt B+ on plate of V1A indicates tube is not passing plate current. Voltage on the grid is zero, which would permit tube to conduct heavily under normal conditions. Screen is receiving normal supply voltage, so cathode-return path must be open. 15-volt reading on cathode further confirms cathode circuit is causing tube cutoff. If tube conduction were developing this high drop across cathode resistor, plate voltage would be drastically reduced—not high. If R4 merely increased value, weak picture might appear.

**SYMPTOM 4**

**No Raster**

High Voltage and  
Sound Normal

**C7 Shorted**

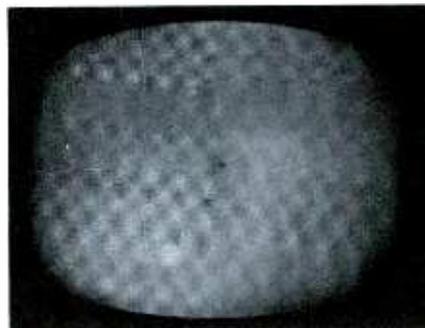

**Symptom Analysis**

High voltage is present, and picture-tube checker shows CRT to be good; so trouble is probably in circuitry associated with CRT gun—probably wrong operating voltage on some element. Station audio is good in volume and clarity, almost ruling out defective front end or AGC, and most video troubles.



**Waveform Analysis**




**Voltage and Component Analysis**

**NO  
VOLTAGE  
CLUES**

Symptoms noted during home call focus attention directly on CRT signal and bias circuitry. Normal appearance of W3 further confirms that video output and previous stages are operating normally. Scope check of W4 during rotation of contrast control shows amplitude variations, proving control is doing its job. Normal W3 and W4, even with C7 shorted, could be misleading in one sense, but a valuable clue in another—they further tie trouble to wrong DC operating voltage on grid or cathode of picture tube.

No meaningful voltage change takes place on any element of V1A. Voltage reading on cathode of CRT (point A) reveals 145 volts. (Normal cathode voltage on this "low-drive" CRT is 30 to 35 volts, variable with brightness control.) Only feasible way a voltage this high could reach cathode is via shorted C7. Leakage in C7 will lower brightness-control range, but defect must become very bad before customer will complain. He'll call much quicker if C7 opens; video will be very weak, giving appearance of defective CRT.

# RINGING CHECKS FOR SWEEP COILS

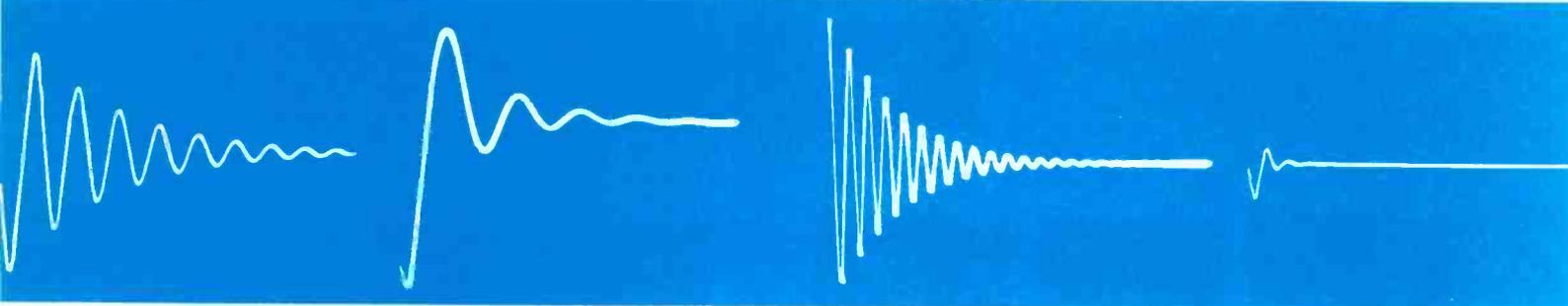

A large number of different defects are capable of causing a partial or complete loss of raster and high voltage, so the serviceman generally shifts his mental apparatus into high gear whenever he is confronted with this complaint. Defects can range from simple short or open connections to complex malfunctioning of entire circuits. Componentwise, trouble may be caused by anything from a "two-


bit" resistor or capacitor to a transformer costing as much as twenty dollars.

In an overwhelming majority of raster and high voltage troubles, routine voltmeter and scope readings—coupled with tube changing and component checking or substituting—will reveal the source of trouble. In the remainder of cases, where these procedures give indefinite results, the inductances in the circuit (yoke, flyback, and width coil) become suspect. Resistance checks of their windings often fail to disclose faults, so a better means of checking these parts is needed.


ated by the latest 114° horizontal sweep components.

This indication of Q is far more useful than any DC test for spotting slight defects in coils. For practical purposes, it is not necessary to make an exact measurement of Q; a comparison with a known good coil of a similar type furnishes sufficient evidence to spot trouble. However, a numerical understanding of the Q factor will help explain why the ringing test is useful.


Q is actually the ratio between

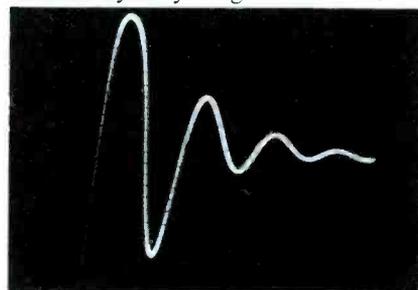

(A) Low-Q, iron-core

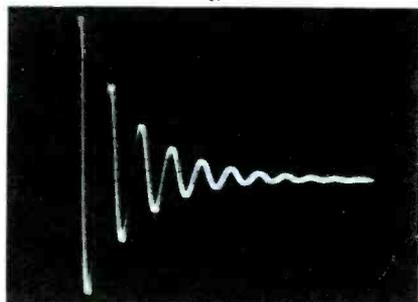

(B) Medium-Q, ferrite-core

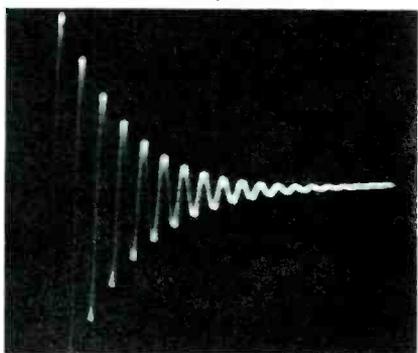

(C) High-Q, ferrite or air core

Fig. 1. Typical coil ringing patterns.

## Coil Ringing Characteristics

One reliable means of determining the efficiency of an inductive component is to examine the damped wave train generated when the inductor is excited by a sharp pulse. The sudden change in applied voltage sets off several cycles of oscillation or "ringing" that can be scoped as shown in Fig. 1. The number of ringing cycles and the rate of their decay are determined by the efficiency or Q of the coil. Low-Q inductors, such as audio or vertical output transformers and other laminated iron-core types, ring as in Fig. 1A. Units with powdered-iron or ferrite cores, like those in horizontal deflection circuits, produce more cycles of ringing (Fig. 1B)—showing that such inductances have considerably higher efficiency or Q factors. A very high-Q coil will ring in the manner shown in Fig. 1C; although this pattern was obtained from an air-core choke wound in special fashion with Litz wire, it is not much different from the waveforms gener-



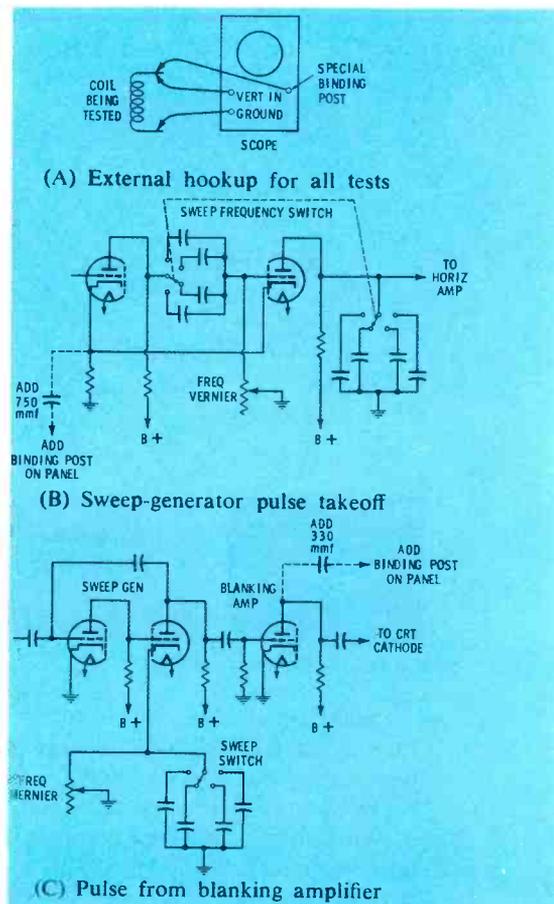



Fig. 2. Connections for obtaining pulse from scope for ringing tests.

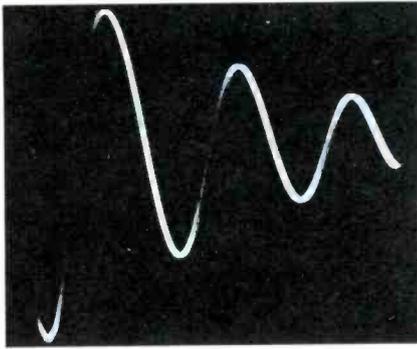

(A) 10 kc—too few cycles shown

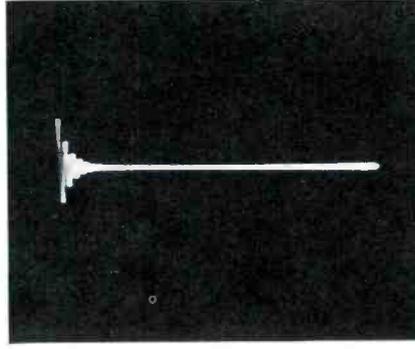

(B) 300 cps—dies out too fast

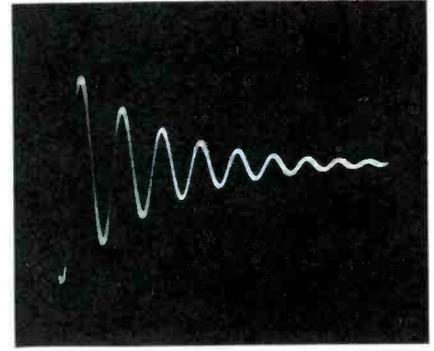

(C) 2600 cps—close to ideal

Fig. 3. Proper scope-sweep frequency is a "must" for good check of flyback.

a coil's inductive reactance and its AC resistance—the higher the ratio, the greater the Q. Shorted turns and similar defects increase the AC resistance by absorbing power in the defective winding; therefore, the Q is lowered. It should be noted that the AC resistance behaves differently from the DC resistance. In a DC ohmmeter check, a few shorted turns merely lower the apparent resistance — sometimes by such a small amount that the fault goes undetected.

The relative effect on AC and DC resistance is clearly shown by the following example. In one specific type of deflection yoke, the

vertical windings normally have an inductance of 44.3 millihenries. Special measurements in a 1-kc bridge circuit indicate a Q of 4 and an AC resistance of 69 ohms, whereas the indicated DC resistance is 60 ohms. With a short between turns of the vertical winding, one yoke of this type was found to have an inductance of 38.6 millihenries, a Q of 2.7, and an AC resistance of 90 ohms, even though the DC resistance was still almost exactly 60 ohms. This trouble could have been discovered quickly, without computations, by someone who was experienced in using a scope for ringing checks.

### Test-Pulse Source

Many servicemen receive the suggestion of ringing checks with more than a little skepticism. "Where," they want to know, "do I get the pulse needed to generate the ringing?" Actually, it is seldom necessary to look any farther than the scope itself.

Many models of scopes have usable pulses already present at panel jacks bearing such diverse names as Z AXIS, HORIZ IN, NEG GATE, and SAWTOOTH. The presence of such signals is generally not revealed by connecting the scope's

• Please turn to page 87


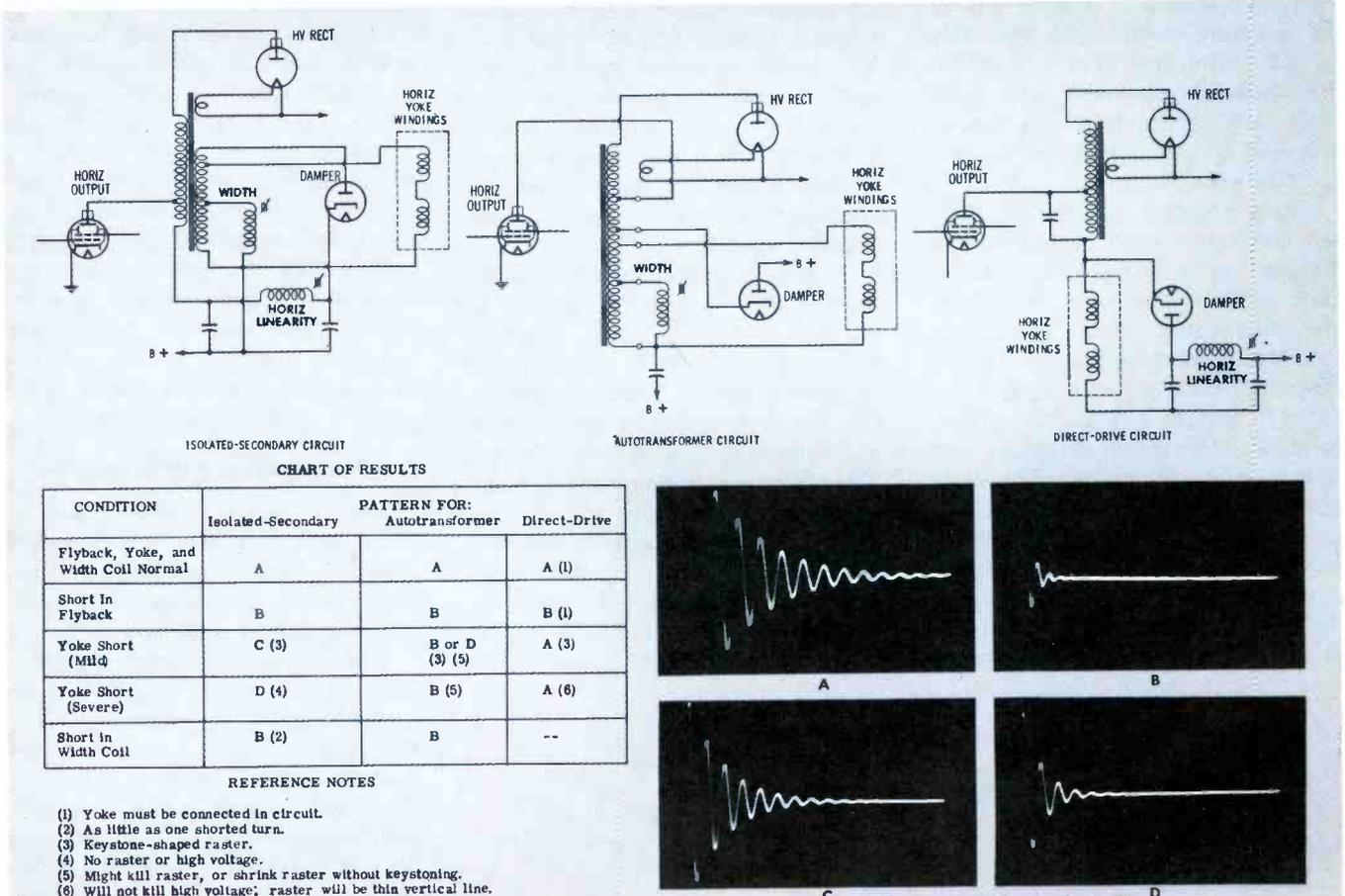


Fig. 4. Ringing tests in horizontal sweep circuits characteristically give these results.

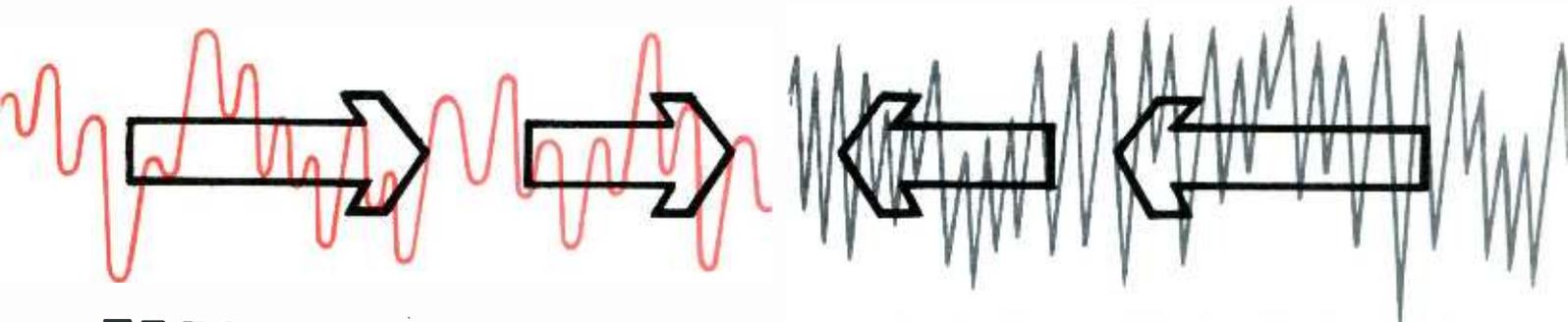

# ALIGNMENT EQUIPMENT FOR STEREO FM

What you need and how to use it.  
by Fred G. Biesecker

It has been almost two years since the Federal Communications Commission (FCC) held the press conference announcing a new medium in broadcasting—stereo FM. The long-awaited stereo standards were described, and approval was granted to begin stereo-FM broadcasting as soon as equipment could be installed. Now there are nearly 300 FM stations broadcasting stereo, and many more are contemplating the idea.

Many servicemen have been wondering what's happened to stereo FM — why don't they hear more about it? The answer is: There's a steady build-up of interest among the listening public, but the only service technicians who are "in" on this quiet development are those who have accumulated the know-how and special equipment to handle multiplex receivers.

These receiver or adapter units are much less complicated than a TV set, even though the circuits may seem unfamiliar. The usual multiplex section of an FM receiver consists of an amplifier or two, a frequency doubler or a locked oscillator, several tuned coils, transformers, capacitors, resistors, and sometimes trap circuits. The main difference between these circuits and those with which you're already familiar is in the special signal that must be handled, bringing about the need for specialized test instruments. If you have this equipment,

and understand its use, you should find servicing stereo FM both easy and interesting.

## Characteristics of the Signal

The stereo-FM signal contains all the information needed to enable multiplex receivers to reproduce the original stereo program. In addition, the stereo signal is compatible; that is, it provides an FM signal for listeners who have only ordinary FM receivers that are not equipped for stereo.

Although the stereo-FM signal is similar in many ways to the monophonic FM signal, it cannot be transmitted over as long a distance without deterioration of stereo quality; the stereo signal has only one-half to two-thirds the coverage range of a monophonic signal. Therefore, it is necessary that receiving equipment be in peak operating condition to produce acceptable results.

The compatible signal used by monophonic receivers is the sum of the left and right stereo channels ( $L + R$ ). The FCC specifies that the signal should frequency-modulate the station carrier the same as an ordinary monophonic signal. The difference between the left and right stereo channels ( $L - R$ ) amplitude-modulates a 38-kc subcarrier; the latter is then suppressed, leaving only its upper and lower sidebands (23 to 53 kc) to modulate the main carrier. The

two signals,  $L + R$  and  $L - R$ , are interleaved at the transmitter, frequency-modulating the station carrier at 90% modulation, or  $\pm 67$  kc deviation from center frequency.

Fig. 1 shows the composite stereo FM signal as it is put together at the transmitter, with the  $L + R$  and  $L - R$  signals shown in their respective portions of the channel spectrum. Located between the  $L + R$  and  $L - R$  signals is a 19-kc signal known as the pilot carrier. This signal is used to synchronize the  $L - R$  demodulator in the receiver, to keep the phase of the resulting signals precisely the same as in the transmitter. This 19-kc pilot carrier must be transmitted with an accuracy of  $\pm 2$  cps, according to FCC requirements. The 67-kc carrier signal—indicated at the right in Fig. 1—is known as the SCA (Subsidiary Communications Authorization) subcarrier. It is authorized by the FCC for use by some stations to transmit special program information, such as background music or a similar service. It can operate simultaneously with either mono- or stereo-FM programs.

## Prealignment Information

Fig. 2 shows a block diagram of a typical stereo-FM multiplex adapter. Let's go through it, especially noting the tuned circuits and how they affect operation.

The composite stereo signal is coupled to input amplifier V1A through C1. At the output of V1A, the signal is split; a portion is applied to cathode follower V1B, and then sent through a low-pass filter composed of L1, C2, and C3. This filter network eliminates all except the  $L + R$  signal (below 15 kc), which is applied to the separation

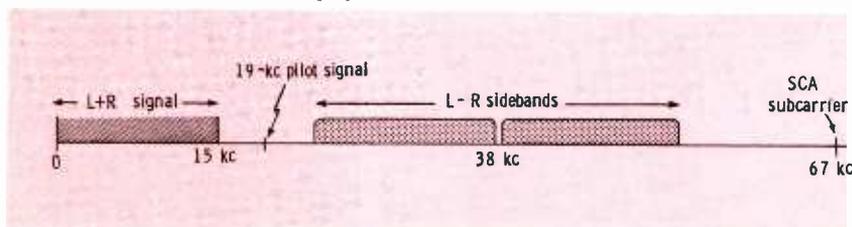


Fig. 1. Composite stereo FM signal is made up of several different parts.

control for insertion into the matrixing circuit.

The above-15 kc portion of the signal from V1A is applied to the grid of V2A. The L - R sidebands, the pilot carrier, and any SCA signals are amplified and fed through a bandpass filter composed of C5, C6, and L2. The filter passes the L - R signal and works in conjunction with another filter — R1, L3, and C7—to eliminate any SCA information. Notice that L2 and L3 are tunable; they must be adjusted during alignment to pass a maximum of the 23- to 53-kc energy while eliminating the 67-kc signal.

From the plate of V2A, the 19-kc pilot carrier is applied to tuned transformer T1, to synchronize a keyed Hartley oscillator — V2B. The 38-kc output of V2B is coupled through transformer T2 and inserted at the demodulator network to recover the L - R signal from the 23- to 53-kc sidebands. The demodulator consists of balanced diodes X1 and X2. Diode X1 develops the L - R signal directly, while diode X2 inverts it—resulting in an R - L signal. The two are sent to the matrix network for mixing with the L + R signal, thus reclaiming the left and right signals in their original form. Then, following a de-emphasis network, the signals are coupled to their respective left- and right-channel amplifiers.

#### The Front End

Before alignment of a stereo FM multiplex adapter is attempted, it is important that the FM receiver section be properly aligned. Since the information contained in the stereo signal extends to 53 kc, the IF bandwidth must be at least 150 kc to accommodate the entire signal, and a 200-kc bandwidth is preferred to allow for any slight mistuning or drift.

The response of the FM detector in the receiver or tuner must be linear over a frequency range from 50 cps to 53 kc. If it isn't, one of several results might occur. First, attenuation or loss of the L - R signal might cause inadequate stereo separation. Second, a nonlinear response can induce a phase shift between the sidebands, causing unwanted modulation and resulting

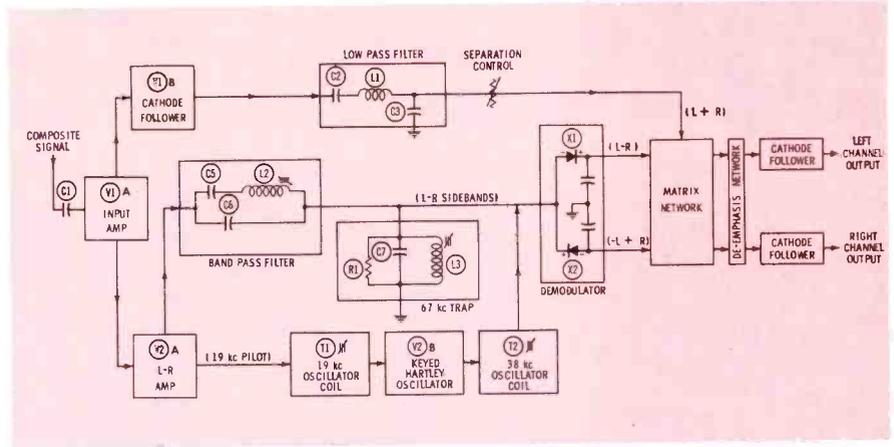


Fig. 2. Adapter reinserts 38-kc subcarrier and matrixes L + R with L - R.

in distortion as well as poor channel separation; these effects are especially noticeable at higher frequencies. Third, a nonlinear detector can result in a phase shift between the pilot carrier and the L - R sidebands, causing improper reinsertion of the subcarrier; this, too, would result in distortion and a loss of channel separation.

#### The Multiplex Section

Stereo-FM equipment that is in need of multiplex adjustment often provides significant clues. For example, a fluttering 400-cps tone is a good indication that alignment of the 38-kc oscillator (if this system is used) is necessary; this trouble can sometimes be taken care of simply by adjusting the oscillator

slug until the tone is no longer heard.

Insufficient channel separation can also be caused by a misaligned 38-kc oscillator. But, before making adjustments for this reason, be sure the local station is transmitting stereo.

Low "whistle" tones heard during a stereo broadcast indicate interference from the 67-kc SCA subcarrier beating with the second harmonic of the 38-kc signal. There are three possible cures for this interference. First, try retuning the FM dial for minimum interference; then, if it is still objectionable, adjust the 67-kc trap in the multiplex circuitry. If this doesn't help, it may be necessary to realign not

• Please turn to page 92


CHART I—Features of Stereo FM Signal Generators

Manufacturer	Model	Built-In RF Generator	Stereo Signal Output	Modulation Indicator Meter	Crystal-Controlled 19 kc	SCA Facilities	Built-In Audio Oscillator	List Price	In Kit Form
Calbest	MX625SG	Preset 88-90 mc	0-1V rms	Yes	Fixed	Input Jack	No	\$495.00	No
Fisher	300	Preset 100 mc (97-103 mc)	0-6V p-p	Yes	Phase Adj'ble	Input Jack	1000 and 1200 cps	\$495.00	No
Hickok	725	Variable 92-104 mc	0-4V p-p	No	Phase Adj'ble	Built-In 67-kc Sub-carrier	400 and 1200 cps	\$495.00	No
Karg	MX-1G	None	0-10V p-p	No	Fixed	None	No	\$250.00	Yes
Precision Apparatus	E-490	None	0-12V p-p	No	Phase Adj'ble	None	No	\$229.00	Yes
RCA	WR-51A	100 mc	0-10V p-p	No	Phase Adj'ble	67-kc Sub-carrier	400 and 1000 cps		No
H. H. Scott	830	None	0-5V rms	No	Phase Adj'ble	None	No		
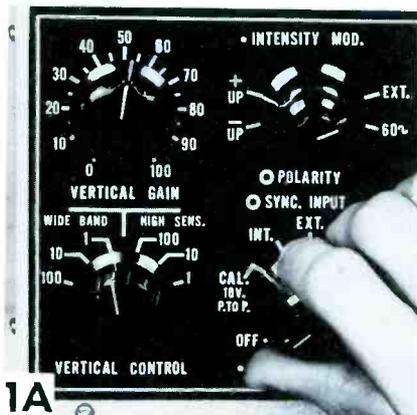
# SCOPE SKILLS

The oscilloscope is a jack of all trades; it can serve as a signal tracer, distortion analyzer, AC voltmeter, frequency meter, alignment indicator, and test-signal source, among other things. The key to making full use of its versatility is deft and intelligent operation of the many panel controls. Most technicians have learned at least the rudiments of scope operation—setting up the brightness, focus, and positioning controls, and bringing at least an approximation of the correct signal waveform into view. For those who are having difficulty in progressing past this point, the hints on these pages should open the door to the many advantages of operating a scope like a “pro.”

**1** Many scope users—even experienced ones—don’t obtain maximum benefit from waveform analysis because they don’t have a keen awareness of the relation between vertical gain settings and peak-to-peak voltage readings. Yet, exact amplitude measurements are just as important as waveshape analysis in the diagnosis of signal faults. The most common method of checking waveform ampli-



1A




1B

tudes is by comparison with a test signal of known peak-to-peak voltage. Most service scopes have some type of built-in calibrating signal, fed to the CRT either internally (by a CAL switch—photo 1A) or from a panel jack via the vertical input terminal (photo 1B).

**2** With this signal applied, the vertical-gain vernier control is adjusted until the waveform extends

some specific number of divisions on a scale or graticule placed in front of the CRT. (If a sine wave is used, reducing the horizontal gain will make it easier to set up the calibration.) Now, if the vertical gain is left untouched, the sizes of all other waveforms will indicate their amplitudes, relative to that of the calibrating signal. For waveforms too high to fit on the screen, all you need to do is switch the vertical attenuator to a higher position, and multiply the measured voltage by the attenuation factor.

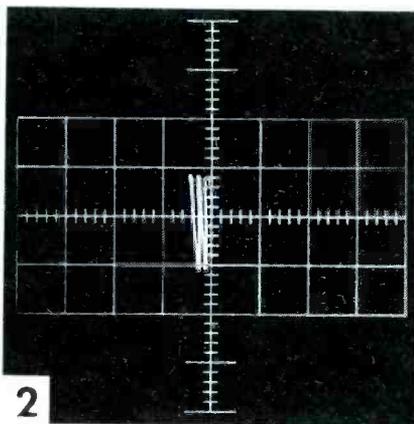**3** Once the vertical-gain vernier setting has been “frozen” by calibration, waveform height can be adjusted only with the decade attenuator; thus, it will naturally vary over a wide range. However, usable waveforms can be obtained without con-




2




3

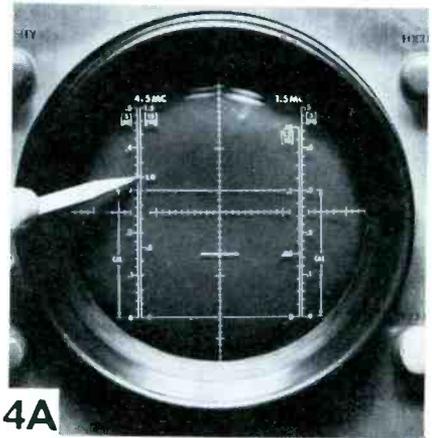stant recalibration, if the scope is set up so that nearly all patterns will be between 0.4” and 4” in height. One popular calibration standard makes 1 volt peak to peak equal to



4A

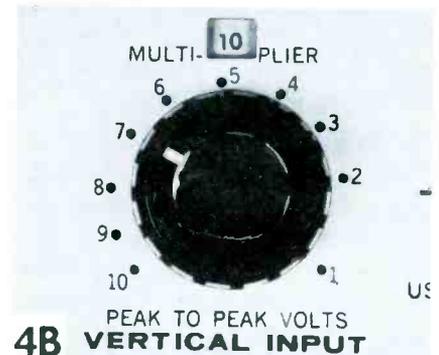

4B

1” deflection on the x1 range; then this range is most suitable for viewing signals of between 0.4 and 4 volts peak to peak. At the same time, effective spans of the x10 and x100 ranges are 4-40 and 40-400 volts.


You’ll occasionally want to change the fine adjustment to expand or reduce waveform height for a better view. To avoid losing calibration, why not mark the vertical dial with the correct position?

**4** There’s a trend afoot to provide “direct readout” of vertical gain settings in peak-to-peak voltage values, instead of the arbitrary decade multipliers and 0-to-100 vernier log-


ging scales which have long been conventional for scopes. One recently introduced model has voltage values marked on the CRT graticule (photo 4A); although the preliminary calibration procedure is basically similar to that used on other scopes, the numerical scale simplifies the process by making it unnecessary to count squares on an unmarked scale. Another approach (photo 4B) is to set the unknown waveform to a prescribed height on the CRT screen, and then read the peak-to-peak voltage directly from the control dial (multiplying the vernier setting by the factor that appears in the small window).




5A

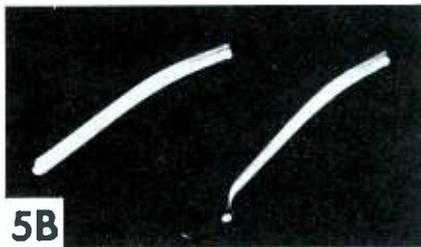

5B

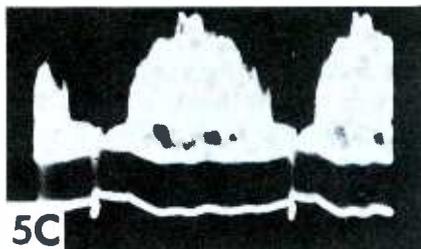


5C

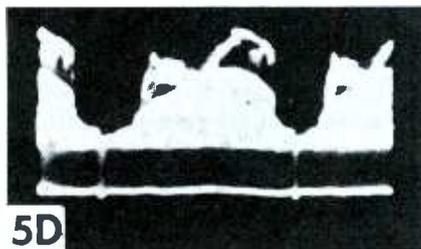

5D

5 Touching the direct probe of a scope to a circuit is the same thing as placing a 20- to 100-mmF capacitor across it. This shunt capacitance can throw sensitive sweep oscillators off frequency and decrease the amplitude of video waveforms at high-impedance points. Adding a low-capacitance probe reduces the capacitive loading caused by the scope to a small proportion (typically 1/10) of the original amount; but at the same time, the signal reaching the scope terminals is only 1/10 of that picked up by the probe.

At most TV test points, signal

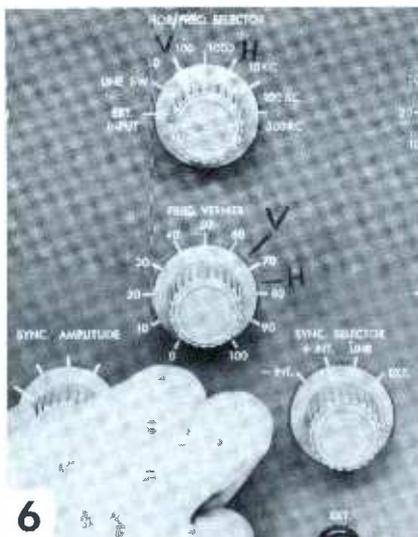

6

strength still is ample to produce a clear pattern; the vertical amplifier is simply operated at higher gain. In critical circuits the user is rewarded by more accurate waveforms. For example, photo 5A shows the modified sawtooth waveform at the plate of a vertical multivibrator, as viewed with a low-capacitance probe. Use of a direct probe (photo 5B) greatly attenuates the negative spikes in this waveform, and also tends to induce vertical rolling.

The direct probe has an advantage over the low-cap probe, however, in viewing weak signals and ripple waveforms under 1 volt peak to peak. To use a low-cap probe in such cases, the scope has to be operated at close to maximum gain, and is subject to stray pickup of hum and hash. Photo 5C shows the cathode waveform of a video output tube (this happens to be W2 in this month's *Symfact*) as it would appear if taken with a low-cap probe; notice the waviness due to hum. By use of a direct probe, the scope can be operated at the next higher attenuator setting, with the improved results shown in photo 5D.


6 Practically all scoping done in TV work requires setting the scope's sweep oscillator at either 30 or 7875 cps, to display two cycles of either vertical or horizontal sync or sweep signals. (Viewing only one cycle isn't recommended, since retrace is likely to occur at a critical point.) Even if the sweep switch has special "V" and "H" settings to aid in locating these important frequencies, the sweep vernier has to be adjusted critically to "tune in" a signal. If the scope has a sync-amplitude control, applying a moderate amount of sync at first will help in location of the proper vernier setting; but the less sync is used, the less chance there is of distorting the sweep trace.

Solidly locking in a waveform can be one of the most difficult aspects of scope operation. The source of the sync, as well as its amplitude, affects

stability. Many scopes now provide a choice of negative or positive polarity for internal sync, since many waveforms respond much better to one than to the other.

Since internal sync is derived from the signal in the scope's vertical amplifier, a change in the vertical-gain setting may alter the sync strength. This tends to let the sweep oscillator drift off frequency, especially if you are depending too heavily on sync to stabilize the pattern. For easier lock-in of signals at 7875 cps, try switching to external sync and running a clip lead from the panel SYNC jack to the general vicinity of the set's high-voltage cage. Direct attachment to yoke-lead insulation is not recommended because the induced sync signal may have an amplitude of several hundred volts. For 30-cps waveforms, LINE sync may work better than internal sync. Careful attention to your sync sources will minimize the annoyance of readjusting the sweep vernier every time you switch back and forth from 30 cps to 7875 cps.

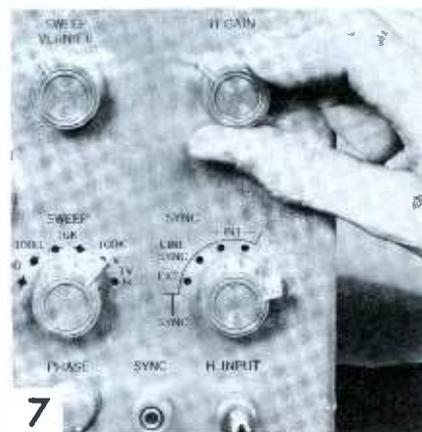7 Alignment setups, in conjunction with a sweep generator, bring into play a group of scope controls that are ignored in all other service work. The alignment generator takes over the job of horizontally deflecting the scope trace, to make sure this trace will be perfectly synchronized with the frequency-modulated generator-output signal; therefore, the scope's sweep generator has to be



7

disabled. In some scopes, the sweep-selector switch has an OFF or EXT position; in others, switch contacts operated by the sync control render the scope's sweep and sync controls ineffective. The horizontal gain control adjusts the length of the trace line produced by the input from the generator, and the vertical gain controls affect the height of the response curve.

The PHASING control is effective only when the horizontal plates of the scope CRT are being driven by an internal 60-cps sine-wave signal (line sweep); therefore, this control is inactive in a normal alignment setup. ▲



cially designed relay in series with the high voltage provides high sensitivity to breakdown. The test voltage—from 0 to 2000 volts rms—may be applied to as many as 11 devices, either sequentially or simultaneously, for periods of 2 to 120 seconds.

### Digital Voltmeter

Digital instruments of high accuracy are being used in industry for both manual and automatic measurements. A typical example is the voltmeter shown in Fig. 3.

The particular advantage of a digital voltmeter is that it makes high-precision readings possible. The range covered is from 9.999 to 999.9 volts, with an average measuring time of 1 second. The measured voltage is displayed in a row of four 1"-high numerals.

In a digital voltmeter (DVM), the unknown voltage is applied to one side of an electronic balance detector. At the same time, precise voltage increments are added by the DVM to the other side of the detector until the two voltages are equal. The voltage value added by the DVM to balance the unknown is displayed as its readout.

The DVM measurement technique is called the potentiometric or comparison method, in which a second voltage is developed to equal the unknown. As is shown in the functional diagram of Fig. 4, the potentiometric voltage is taken from a voltage divider connected to a very stable source known as the reference voltage or working reference. Programmed stepping switches vary the voltage-divider setting until the potentiometric voltage is equal to the unknown input voltage; at the same time, they operate the digital readout. The voltage-comparison amplifier informs the programming circuits of the relative amplitude of the unknown input and potentiometric voltage to each step of the switches. A polarity-reversing switch for the reference voltage permits measuring both positive and negative inputs. The range switch varies the setting of an input attenuator so voltages greater than the reference voltage can be measured. Range changing may also be accomplished by choosing a differ-



Fig. 2. Hi-Pot tester locates breakdowns in insulation between conductors.

ent reference-voltage value, generally changing to 1 volt or 100 volts.

### Taut-Band Meter Movements

In meters designed for portable use in industry, a unique meter-movement construction is often employed — taut-band suspension. A basic movement in which this suspension is utilized is shown in Fig. 5. Instead of spiral springs, as in d'Arsonval movements, two metal strips (given a partial twist and held taut by tension springs) serve as springs to hold the pointer against the zero stop. The advantages of this relatively new suspension method include:

1. Elimination of bearings (and thus bearing friction).
2. Relative immunity to vibration and shock.
3. Reduced maintenance because of fewer moving parts.



Fig. 3. Digital voltmeter generates voltage to compare with unknown.

4. Increased sensitivity, up to several hundred percent over jewel-and-bearing instruments.

In the figure, the relative size of the taut band has been exaggerated in order to show the construction of the movement more clearly. Actual taut bands are only 0.005" wide and 0.0005" thick.

### Recording Instruments

Recording instruments are used in industry where it is desired to have a permanent, continuous record of information such as voltage, current, pressure, humidity, flash points, rpm, etc. Any quantity

• Please turn to page 83


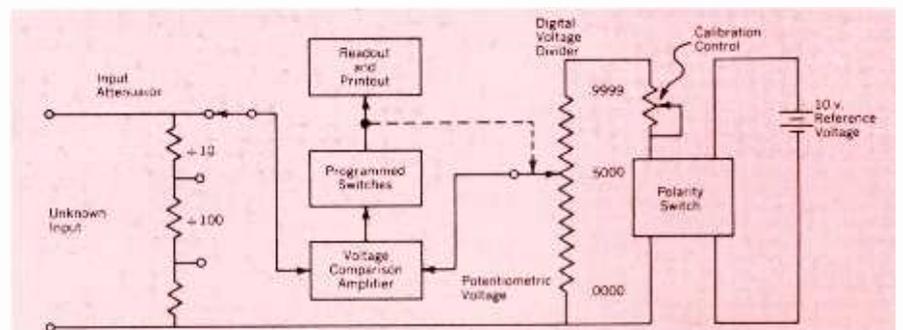


Fig. 4. Programmed switches set up voltage balance and digital readout.

# TEST EQUIPMENT

## *Guide*

# FOR SHOPS

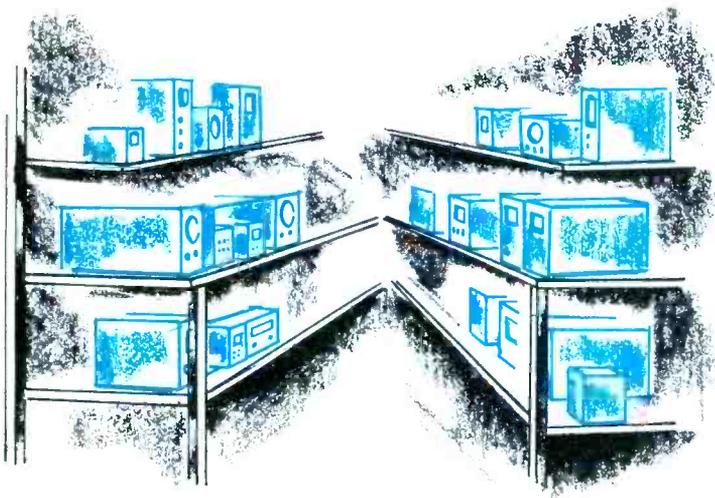


To keep up with the advancing electronics field, many new and helpful items of test equipment have been developed. The serviceman is faced with the problem of choosing the right instruments to cope with the variety of faulty electronic devices he encounters each day. Purchasing every new piece of test equipment that becomes available is impractical and unnecessary. Each serviceman must weigh his own needs and purchase only those items that can help him make a profit. For example, it would be impractical to purchase a color-bar generator for a shop that repairs only transistor radios. If an instrument is going to remain on a shelf and collect dust, it serves no useful purpose and is an unwise investment. But the

serviceman should keep an open mind in considering unfamiliar new types of test equipment, because they may offer him an opportunity to increase his efficiency. Likewise, he should not hesitate to replace obsolete or worn-out equipment, which can waste valuable time by giving false readings or even failing to work when needed.

From a recent survey of service shops, it was found that the VOM, VTVM, oscilloscope, and tube tester are still considered basic instruments. The chart below shows additional test equipment that will prove helpful for various types of service work. It is divided into categories in case you want to concentrate on one or more specialized fields.


Test Equipment	VOM	VTVM	Oscilloscope	Tube Checker	CRT Tester	Transistor Checker	Signal Generator	Sweep Generator	Harmonic Generator	Signal Tracer	Capacitor Checker	Substitution Boxes	Yoke-Flyback Tester	AC Wattmeter	Frequency Meter	Modulation Monitor	Field Strength Meter	Dummy Load	Isolation Transformer	DC Power Supply	Special Circuit Analyzers	
B-W TV	◆	◆	◆	◆	◆	◆	◆	◆			◆	◆	◆	◆			◆				◆	
Color TV	◆	◆	Wide Band	◆	◆		Bar Dot	◆			◆	◆	◆	◆			◆				◆	
AC-DC Radio	◆	◆	◆	◆			◆		◆	◆	◆	◆							◆			
Xstr Sets	◆	◆	◆	◆		◆	◆		◆	◆	◆	◆									◆	◆
Hi-Fi	◆	AC Type	◆	◆		◆	Stereo Audio	FM	◆	◆	◆	◆									◆	
Auto Radio	◆	◆	◆	◆		◆	◆		◆	◆	◆	◆									◆	
CB	◆	◆	◆	◆		◆	◆			◆	◆	◆			◆	AM	◆	◆		◆	◆	
2-way	◆	◆	◆	◆		◆	◆			◆	◆	◆			◆	AM FM	◆	◆		◆	◆	

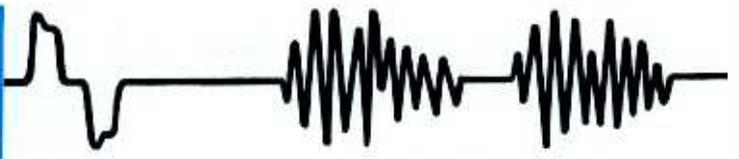

## Tips for Technicians


Mallory Distributor Products Company  
 P.O. Box 1558, Indianapolis 6, Indiana  
 a division of P. R. Mallory & Co. Inc.
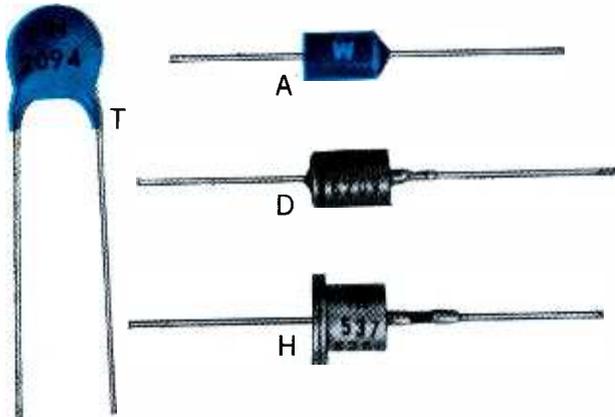
### Time for a new look at silicon rectifiers



SILICON RECTIFIERS—750 ma @ +50°C

PRV	T	A	D	H
50	1N2090	A50	D50	1N536
100	1N2091	A100	D100	1N537
200	1N2092	1N2069	1N3193	1N538
300	1N2093	A300	D300	1N539
400	1N2094	1N2070	1N3194	1N540
500	1N2095	A400	D400	1N1095
600	1N2096	1N2071	1N3195	1N1096

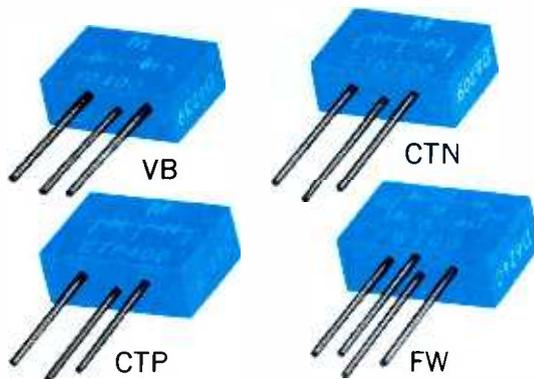

PACKAGED RECTIFIER CIRCUITS

PRV	750 ma @ +50°C			1.5 amp @ +50°C FW
	VB	CTN	CTP	
50	VB50	CTN50	CTP50	FW50
100	VB100	CTN100	CTP100	FW100
200	VB200	CTN200	CTP200	FW200
300	VB300	CTN300	CTP300	FW300
400	VB400	CTN400	CTP400	FW400
500	VB500	CTN500	CTP500	FW500
600	VB600	CTN600	CTP600	FW600

The silicon rectifier industry moves at such a rapid pace that you may not be aware of some recent developments.

Take *hermetic sealing* for example. Many technicians feel that the "top hat" rectifier is the only safe one to use . . . probably because it's the original MIL type (1N536, etc.). This is the Mallory "H" type. It's a fine rectifier and we sell thousands of 'em. If you really *need* hermetic sealing, you should check the Mallory "D" series. It's smaller than the "H" and actually has *better characteristics* at a *lower price*.

But are you sure you really *need* hermetic sealing? The Mallory "A" series (axial leads) and "T" series (parallel leads) actually withstand *four times* the humidity cycling of the MIL test. They're both epoxy encapsulated and are available in all ratings up to 600 PRV at lower cost than either the "D" or "H". You shouldn't confuse the Mallory "A" or "T" rectifiers with those made by other people, though. No kidding, we use a *superior* encapsulating system. If you need *quality*, you'll be ahead with Mallory.

So, whenever you need 750 ma from 50 to 600 PRV, decide on the style and price that fit your requirements. Your Mallory Distributor has *exactly* the right rectifier for you.

**Multi-rectifier circuits.** Instead of hooking up a number of rectifiers to make a doubler, full-wave center-tap or full-wave bridge, you can now get Mallory *pre-packaged circuits*. Cost is less than that of separate rectifiers. And convenience and reliability are far greater, because you have fewer solder connections to make, fewer parts to stock and handle. We make them in ratings up to 600 PRV.

**Reliability.** Lots of people think "reliability" applies only to military electronics. But Mallory doesn't think so. We think the service technician needs reliable components, too. We'd like to say our silicon rectifiers were 99.99% reliable. But we can't. In order to quote 99.99%, one must have a *failure somewhere*. The fact is, that during 1962 we didn't have a *single failure*. Saying 100% reliability sounds like bragging . . . so we won't say it.

You might be interested to know that every single Mallory silicon rectifier gets a complete electrical check at *full* temperature and *full* load THREE SEPARATE TIMES. Time consuming? You bet! But there is absolutely no question about quality.


Mallory Silicon Rectifiers are available through your Franchised Mallory Distributor . . . see him for other Mallory products, too . . . batteries, capacitors, controls, switches, resistors and vibrators. In fact, see him for *all* of your electronic requirements.

**WE RECOMMEND  
RAYTHEON TUBES**

**RAYTHEON**



**GUARANTEED BY  
GOOD HOUSEKEEPING**

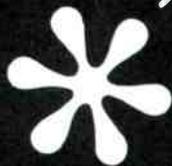

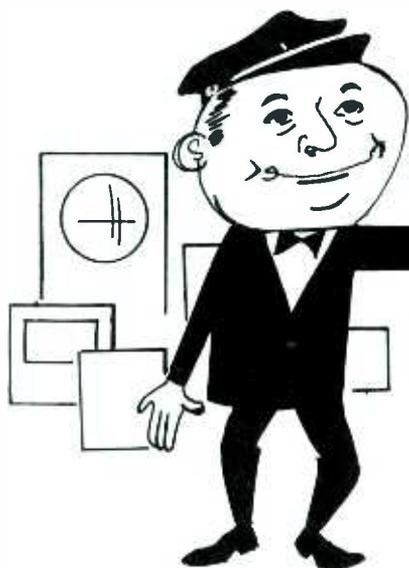
# Bring 'em back for more

This business-builder makes real sense—the new customer-catching Good Housekeeping Seal decal for service dealers who replace with Raytheon receiving and picture tubes. It's yours—part of Raytheon's 1963 "Deal with the Seal," created to help boost your profits and enhance your own fine service reputation.

**We're using full-page advertising in Good Housekeeping magazine** to tell more than 5 million families how the Good Housekeeping Seal guarantees performance and quality of all Raytheon tubes. We're re-





# Getting MORE from

# your TEST EQUIPMENT



Keep looking for new ways to utilize what you now have.

by Robert G. Middleton

Experienced technicians have learned that basic test instruments—such as the VOM, VTVM, oscilloscope, and signal generator—can do many more jobs than are usually expected of them. To develop these additional methods of using test equipment requires a basic understanding of the workings of each instrument, and a certain amount of imagination.

Unusual ways to use test apparatus are illustrated by the following examples, which are all practical techniques you can use in everyday service work. They demonstrate the type of thinking involved in making better use of your basic instruments.

### VOM as AC Ammeter

When tracing power-supply shorts, some technicians choose the technique of monitoring the line-current demand of the receiver while disconnecting various power-supply branches. This is a useful method, because when the shorted branch is disconnected, the current decreases sharply. If the excessive current is due to a defect in the power transformer, “unloading” it will leave the input current unaffected. A burned-out tube in a series-string receiver will cause the meter pointer to leap, quiver, and fall back to zero when the receiver is first turned on. The momentary reading occurs because the B+ filters charge up through the semiconductor rectifiers; there is no heater drain, nor is any current drawn from the power supply.

The initial surge in a normal TV receiver is from 5 to 15 amperes.

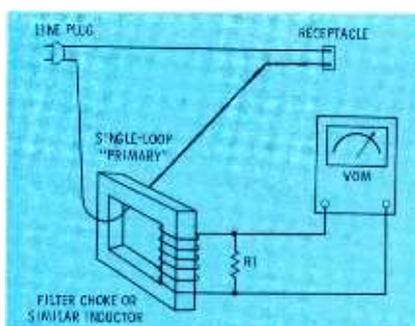


Fig. 1. Line splitter adapts VOM to measure AC current on voltage ranges.

The ammeter will then drop quickly to a reading of 0.5 to 1 amp, and creep up until the raster is about to appear. Then, as the horizontal system swings into operation, the ammeter reading will rapidly climb to the normal operating value.

Very few service-type VOM's have a built-in AC ammeter function, but some manufacturers build adapters or accessories for this purpose. In fact, it is a simple matter to make up your own adapter, as shown in Fig. 1. The *line splitter* is a short length of AC cord, interconnecting a standard AC plug and receptacle. One of the wires in the line splitter is run through the core window of the current transformer (any small iron-cored inductor). The male end of the splitter is plugged into the female receptacle.

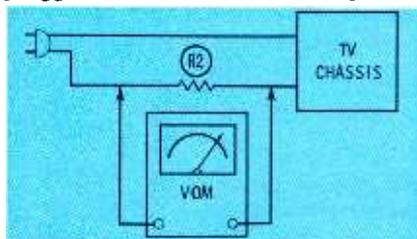


Fig. 2. Use current through R2 as a reference for calibrating line splitter.

R1 is a calibrating resistor, and its value will be selected during the initial calibration. Of course, the adapter should be enclosed in a small box, for the sake of neatness and to keep the position of the single-turn primary fixed.

To calibrate your adapter, use the reference setup shown in Fig. 2. The VOM is set to the AC-voltmeter function—usually on the lowest range, unless the inductor you are using as a current transformer has a rather large inductance. R2 is a power resistor having a low value, such as 1 or 2 ohms. After the chassis has warmed up, and is drawing steady current from the line, measure the AC voltage drop across R2 and calculate the current from Ohm's Law:  $I = E/R$ . Do not remove the resistor from the power line.

Plug in the current adapter, and connect the VOM to the adapter output. Now, select a value for R1 (in the adapter) which causes the VOM to read 1 volt for each ampere in the line. For instance, if the chassis is drawing 2.25 amperes, select a value for R1 which makes the VOM read 2.25 volts. Then, the AC voltage scale can be used to read AC amps. If the inductor does not give enough output voltage, simply utilize a choke with more turns. Small filter chokes with high inductance are best and usually will provide ample output to “trim down” with the shunt resistor. Or, you may even find that a two-turn primary suits the characteristics better than a one-turn primary. In any case, do not omit R1 from the adapter, or transients that oc-

cur when the line splitter is connected or disconnected might cause arcing between layers of the inductor secondary. The resistor serves not only to calibrate the readings, but also to protect the inductor.

#### VTVM as RF Voltmeter

Most VTVM's have an RF probe, or such a probe can be obtained from the manufacturer. Vacuum-tube diode probes will withstand considerable input voltage without being damaged, while semiconductor types are somewhat limited in this latter respect. Since nothing is ahead of the RF probe, signal frequencies up to 100 mc and sometimes 250 mc can be applied. If the lowest full-scale range of the meter is .5 volt, or thereabout, as little as .01 volt (10 mv) rms will be readable on the scale, and the instrument can be used as a high-frequency signal tracer.


You can make a quick check for local-oscillator operation in a TV set by touching the RF probe to a floating tube shield placed over the oscillator tube. Furthermore, the IF signal can be traced through the IF strip. You should measure about 0.1 volt at the first IF grid, if the set is receiving a fairly strong signal. In normal operation, a greater signal voltage is measured at each successive plate and grid terminal. Of course, the probe tends to detune the IF circuits, so the readings are only relative; but this procedure will enable you to isolate the trouble area, in case the signal is being stopped or attenuated somewhere.

If you suddenly get a very high reading when testing at an IF terminal, detuning has caused oscillation. Disregard this reading, and simply proceed to the next grid or plate terminal.

Beginners are sometimes confused when the VTVM shows a reading as the probe is moved about in the air; but the unconnected probe tip is only picking up stray fields. To avoid errors from this source, make it a practice to short the probe tip to the ground lead when zeroing the meter.

The short ground lead provided with an RF probe should always be used, because a long ground lead (Fig. 3) develops excessive reactance at higher frequencies. This will cause the RF reading to be low. To prove this fact, first ob-

*Put your TV Tuner Troubles*

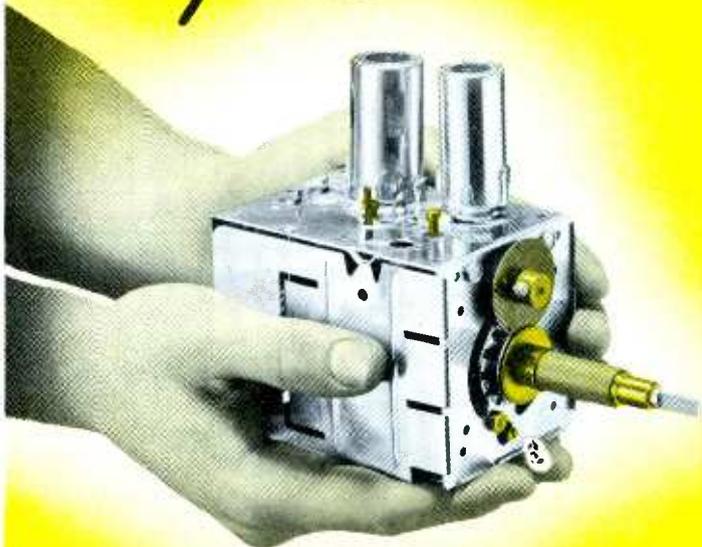

*in Skilled Hands*

# CASTLE

## TV TUNER SERVICE CENTERS

### 1. Compare the Quality

What price quality? We could "just repair" your tuner for less than \$9.95 . . . but, the little extra you pay for a Castle Overhaul buys a lot of quality. And don't forget the "Big Bonus" you get on a UV combination . . . a double portion of Castle quality for the same price.

**And remember . . . in over a decade of service in this specialized field, there has been no increase in the Castle Overhaul charge of \$9.95.**

Castle replaces all defective parts, (tubes and major parts are extra at net prices) and then aligns your tuner to the exact, original specifications.

Simply send us your defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint.

**ONE PRICE**

**9<sup>95</sup>**

**ALL MAKES**

**VHF TUNERS  
UHF TUNERS  
UV COMBINATIONS\***

\*UV combination tuner must be of one piece construction. Separate UHF and VHF tuners with cord or gear drives must be dismantled and the defective unit sent in.

90 Day Warranty

Send for **FREE Mailing Kit** and complete details.

*See map for Castle Center Serving You*



Pioneers in TV  Tuner Overhauling

**CASTLE TV TUNER SERVICE, INC.**

5701 N. Western Ave., Chicago 45, Illinois

653 S. Palisade Ave., Cliffside Park, New Jersey

In Canada: 136 Main St., Toronto 13, Ontario

**THE INDUSTRY'S  
ONLY COMPLETE  
"LOOK-ALIKE" LINE  
OF BOTH NEEDLES  
AND CARTRIDGES!**



150 Exact  
Replacement  
Cartridges

300 Exact  
Replacement  
Needles

Speeds your phono service . . . assures consistent high quality and complete compatibility of needles and cartridges. Inventory and handling costs are cut to the bone. And the industry's greatest array of sales tools — cross-reference catalogs, wall charts, displays and merchandisers — is available to suit your requirements. Ask your E-V distributor, or send coupon for profitable details, today.

**Electro-Voice**

ELECTRO-VOICE, INC., Dept. 337R  
Buchanan, Michigan  
Please send my free needle and cartridge catalogs plus name of nearest distributor.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

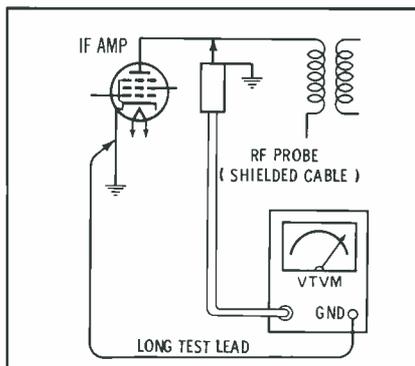


Fig. 3. Long test lead is poorer RF ground than outer conductor of cable.

serve the signal-voltage reading with both ground leads connected. Then, disconnect the short ground lead, forcing the RF signal to return via the long test lead. The scale reading will take a nose dive.

### Sensitizing Your Capacitance Bridge

Most capacitance bridges use an electron-ray tube as a null indicator. There are probably times when you have wished the null indication were more sensitive, so you could adjust the bridge with greater accuracy. It's easy to sensitize the null indication by using your scope in place of the electron-ray tube. Connect the vertical-input lead of the scope to the electron-ray tube input terminal of the bridge, and the ground lead to the bridge's "common" bus.

A 60-cps sine-wave pattern will appear on the scope screen. As the bridge approaches a balanced condition, the amplitude of the pattern will drop sharply and become very small at the well-defined balance point. At the same time, the "eye" indicator will be changing its pattern very slowly.

### Scope as P-P Voltmeter

Interpreting wave shapes is one thing, and measuring waveform amplitudes is another. We sometimes tend to neglect peak-to-peak voltage measurements in service work, and this is unfortunate, since amplitude is just as important as shape—sometimes even more so. In other words, a signal-circuit fault may result in a large change of signal amplitude with little or no change in waveshape. If we fail to measure the peak-to-peak voltage, we miss the boat. It does take a little time to calibrate a scope for peak-to-peak measurements, but it is time well spent. Let's summarize

the basic facts about peak-to-peak voltage measurements:

1. As depicted in Fig. 4, the vertical attenuator in most modern scopes has a "step" switch and a fine control. With the calibrating voltage applied, note what settings of both controls are necessary for a reference deflection (usually of 1" or 2").
2. After making these settings, use only the step attenuator to provide patterns of usable height; if you change the setting of the fine control, the basic calibration is lost.
3. The step attenuator (Fig. 5) is a decade, or decimal, device. In other words, the pattern height is increased or decreased by a factor of 10 when you switch to an adjacent position. This makes it simple to keep track of the vertical sensitivity for whatever pattern height was chosen for calibration.

An example will help clarify these steps. Suppose the calibration voltage is 1 volt peak to peak, and you adjust the vertical gain control for a 1" deflection on the scope graticule. Then, as long as the attenuator (step) switch remains at the 1 position, 1" will represent 1 volt of input signal; thus, a 3" pattern will be caused by a 3-volt signal. If the attenuator switch is changed to 100, each 1" of deflection automatically represents 100 volts; a 3" pattern would indicate the presence of a 300-volt peak-to-peak signal.

The same technique will apply no matter what calibrating voltage


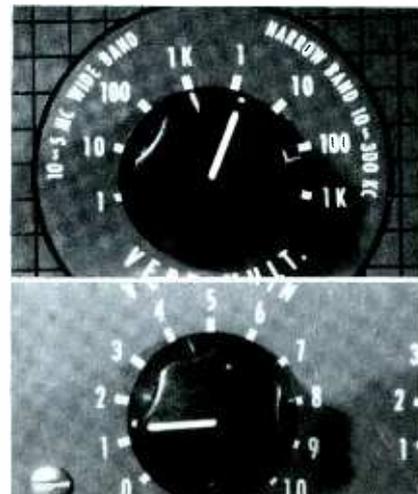


Fig. 4. Scope vertical gain is adjustable by step switch and fine control.

See Only the Scale You Want... in the Exact Range You Want

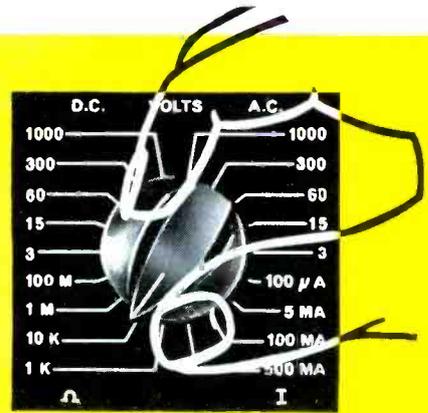just set the range switch  
and the correct scale appears  
**AUTOMATICALLY**



in the new **B&K**  
**VOM and VTVM**

## V O M A T I C 360

### AUTOMATIC VOLT-OHM MILLIAMMETER

WITH  
BURN-OUT PROOF  
METER

Greatly simplifies your VOM use. Individual full-size scale for each range—and only one scale visible at any one time, automatically. Once you set the range switch, it is impossible to read the wrong scale. Reading in the range you want is amazingly easy—and direct. No reading difficulties, no multiplying, no errors.

**Sensitivity** 20,000 ohms per volt DC; 5000 ohms per volt AC. **Accuracy** ±3% DC; ±5% AC; (full scale). **DC Volts** in 6 ranges 0-6000. **AC Volts** in 6 ranges 0-6000. **AF (Output)** in 4 ranges 0-300 volts. **DC Current** in 5 ranges 0-10 amps. **Resistance** in 4 ranges 0-100 megohms. Supplemental ranges also provided on external overlay meter scales. Meter protected against extreme overload and burn-out. Polarity reversing switch. Automatic ohms-adjust control. Mirrored scale. Complete with 1½-volt and 9-volt batteries, test leads, and easy-viewing stand.

Net, \$5995



## DYNAMATIC 375

### AUTOMATIC VACUUM-TUBE VOLTMETER

Once you set the range switch, you automatically see only the scale you want and read the exact answer directly. Saves time, eliminates calculation, avoids errors. Individual full-size direct-reading scale for each range. Simplifies true reading of peak-to-peak voltages of complex wave forms in video, sync and deflection circuits, pulse circuits, radar systems, etc. Includes DC current ranges, too.

**Accuracy** ±3% full scale AC and DC. **Sensitive** 100 microampere meter movement. **DC Volts** in 7 ranges 0-1500. **AC Volts (rms)** in 7 ranges 0-1500. **AC Volts (peak-to-peak)** in 7 ranges 0-1500. **DC Current** in 3 ranges 0-500 ma. **Ohms** in 7 ranges 0-1000 megohms. Utilizes single DA-AC ohms probe and anti-parallax mirror. Swivel stand converts to carry-handle. Includes 1½ volt battery. Operates on 117 volts 50-60 cycle AC.

Net. \$8995

Ask Your B&K Distributor  
for Demonstration, or  
Write for Catalog AP20-R



**B & K MANUFACTURING CO.**

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.

Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.

you use—2 volts could be set up as a 2" deflection. Also, some scope graticules are marked in divisions other than inches. If so, these divisions can be used the same as described for inches: one division can represent 1 volt, and so on.

Normal peak-to-peak voltages at key check points are specified on most receiver service diagrams. Don't overlook this valuable troubleshooting aid—there are many circuit faults which can't be pinpointed by ordinary DC voltage and resistance measurements, but can be located quickly by checking

signal amplitudes with a scope.

### Signal Generator for Gain Tests

A signal or marker generator is an indispensable adjunct to the foregoing instruments. Tests may show that RF and IF stages are operating, but the signal level still is suspiciously weak. In such cases, a gain measurement of each stage is in order. Proceed as follows:

1. Connect a VOM or VTVM at the detector output.
2. Apply the generator output—at a frequency in the middle of the IF band—to the grid

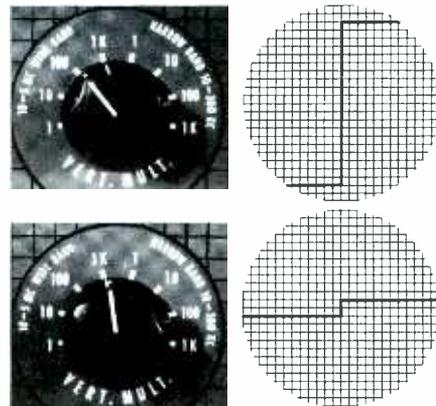


Fig. 5. Effect on waveform when attenuator is switched to higher position.

of the suspected stage, and then to the following grid. (Clamp the AGC line in this test; also keep the signal level low, so it won't overload the set.)

3. The ratio of the voltmeter readings is the approximate stage gain. In Fig. 6, for example, if the voltmeter readings are 2.5 volts and .25 volt, the stage gain is 10.

The generator should have a blocking capacitor in series with the output lead to prevent disturbing the DC grid bias; a 250-mmf capacitor is satisfactory. The VTVM should be set to measure DC volts. As a general guide, a stage gain of about 10 is normal for low values of AGC clamping voltage. High AGC bias will reduce the measured gain in normal operation, but will not block the controlled tubes because they generally are remote-cutoff types.

In summary, basic test instruments will give much greater benefits if full advantage is taken of their capabilities. It is a fact that many tests and measurements commonly considered to be in the province of elaborate and expensive instruments can be made with basic test equipment, provided you know how to use it. ▲


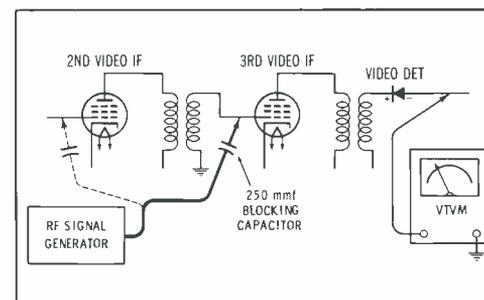


Fig. 6. Test setup to check IF stage gain with signal generator and VTVM.

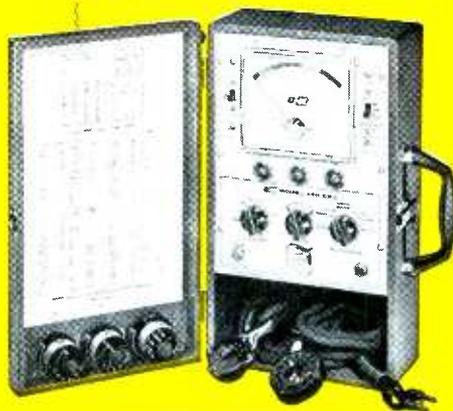**SAVE CUSTOMERS MAKE MONEY**

THE INDUSTRY'S STANDARD  
Most Widely Used Today  
by Professional Servicemen



FAMOUS DELUXE

**B&K**

**CRT 440**



For Black & White and Color

"Most valuable and useful" . . . "Wouldn't be without it" . . . "Pays for itself over and over again" . . . servicemen say. Quickly checks and corrects television picture tube troubles in a few minutes right in the home without removing tube from set. Gives new life to weak or inoperative tubes. Checks for leakage, shorts, open circuits and emission. Removes inter-element shorts and leakage. Repairs open circuits and low emission. Restores emission and brightness. Life Test checks gas content and predicts remaining useful life of picture tube. Makes new tube sales easier. Completely self-contained. Rich leatherette-covered carry-case. Net, \$74.95

#### TESTS AND REJUVENATES

all picture tubes at correct filament voltage from 1 to 12 volts

#### TESTS AND REJUVENATES

110° tubes and the new 19" and 23" tubes

#### TESTS AND REJUVENATES

color picture tubes. Checks each gun of color tube separately

#### UP-DATE YOUR B&K CRT WITH THESE ACCESSORIES

Subscribe to New Picture Tube Information Service

**Model C40 Adapter.** For use with previous Models 400 and 350 CRT's—to test and rejuvenate TV color picture tubes and 6.3 volt 110° picture tubes. Net, \$9.95

**Model CR48 Adapter.** For use with previous Models 400 and 350 CRT's—to test and rejuvenate 110° picture tubes with 2.34, 2.68, and 8.4 volt filaments. Net, \$4.95

See Your B & K Distributor, or Write for Catalog AP20-R

**B & K MANUFACTURING CO.**  
Division of DYNASCAN CORPORATION  
1801 W. BELLE PLAINE AVE. CHICAGO 13, ILL.  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 253 Broadway, N.Y. 7, U.S.A.





*...leave sooner—get there faster!*



*It's there in hours...and costs you less!*

	Buses Daily	Running Time	20 lbs.	30 lbs.	40 lbs.*
BOSTON NEW YORK	20	5 hrs. 15 min.	\$1.80	\$2.10	\$2.35
LOUISVILLE NASHVILLE	13	4 hrs. 10 min.	1.70	2.00	2.35
MIAMI DAYTONA BEACH	18	5 hrs. 30 min.	1.90	2.15	2.45
LOS ANGELES SAN FRANCISCO	28	9 hrs. 20 min.	2.10	2.45	2.80
CHICAGO INDIANAPOLIS	10	4 hrs. 15 min.	1.70	2.00	2.30

\*Other low rates up to 100 lbs.

Save time! Save money! Ease those inventory control problems too! Ship via Greyhound Package Express! Packages go everywhere Greyhound goes, on regular Greyhound buses. Very often they arrive the same day shipped. Ship nationwide, anytime... twenty-four hours a day, seven days a week, weekends and holidays. Ship C.O.D., Collect, Prepaid, or open a charge account. Insist on Greyhound Package Express. **It's there in hours... and costs you less.**

**GREYHOUND PACKAGE EXPRESS**, Dept. 52-P  
140 S. Dearborn St., Chicago 3, Illinois

Please send, without cost or obligation, complete information on Greyhound Package Express service... including rates and routes.

NAME \_\_\_\_\_ TITLE \_\_\_\_\_

COMPANY \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ PHONE \_\_\_\_\_

**CALL YOUR LOCAL GREYHOUND BUS TERMINAL  
OR MAIL THIS CONVENIENT COUPON TODAY**






QUICKER SERVICING  
by George F. Corne, Jr.


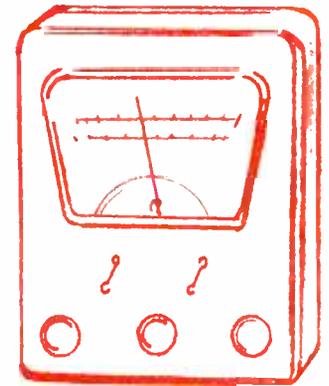
# you **Can** service transistors with a **VOM**



Many servicemen have perfectly good VOM's in their shops doing nothing but sitting and collecting dust on the shelf; others may be using their VOM's now and then, but only on tube radios and TV sets. Most technicians really haven't given much thought to using a VOM for servicing transistorized equipment. They usually prefer to use a VTVM for transistor work simply because they feel their VOM can't do the job as well, or that it might "load" transistor circuits enough to affect their operation. If you have similar impressions about the VOM, you may be missing some of its features that can be put to good use on transistorized sets.

One of these features in particular—current-measuring capability—is certainly applicable to transistor-radio repair. Don't forget, the transistor is a current-operated de-

vice, and current readings are very helpful (sometimes even necessary) in checking and troubleshooting transistor radios. Most vacuum-tube voltmeters don't have this feature, and you must use a separate milliammeter to check current in a receiver. There are special test instruments designed especially for transistor work, most of which come equipped with a current meter—but so do VOM's.

### Voltage Measurements

The majority of VOM's, especially newer ones, have a sensitivity rating of 20,000 ohms per volt (ohms/volt). This means that when the range switch is set to read 1 volt full scale, the shunt resistance connected to the circuit under test will be 20K; on the 2.5-volt range, the resistance will be 2.5 times 20K, or 50K. The shunt resistance increases proportion-

ately as the voltage range is increased. The accuracy of the voltage reading obtained will generally increase, since less circuit loading will occur.

A VOM with a sensitivity of at least 20K ohms/volt *can* be used to measure transistor-radio voltages, with suitable accuracy. Circuits that use transistors have low impedance and are less likely to be upset by the low shunt resistance of the VOM than, for example, the high-impedance grid circuit of a vacuum-tube oscillator. (A VOM with an ohms/volt rating *lower* than 20K may tend to load circuits an undue amount, affect their operation, and cause inaccurate voltage readings. For this reason, it shouldn't be used for transistor servicing.)

### Ranges

The best VOM's for transistor work are those in which the lowest DC voltage range is only 1 or 2.5 volts, full scale. (Many newer instruments have even lower voltage scales especially intended for transistor measurements, so keep this in mind if you're thinking of buying one.) A meter with a range this low is useful for measuring the low bias voltage between the base and the emitter of a transistor. This bias voltage is normally just a few tenths of a volt, and reading it becomes a guessing game on a higher voltage scale—say the 10-volt scale, for instance.

On the other hand, in case your present VOM doesn't have a 1- or 2.5-volt range, don't worry about it; you can still measure the bias voltages mentioned above, merely by adopting a different method. Using the chassis as ground, meas-


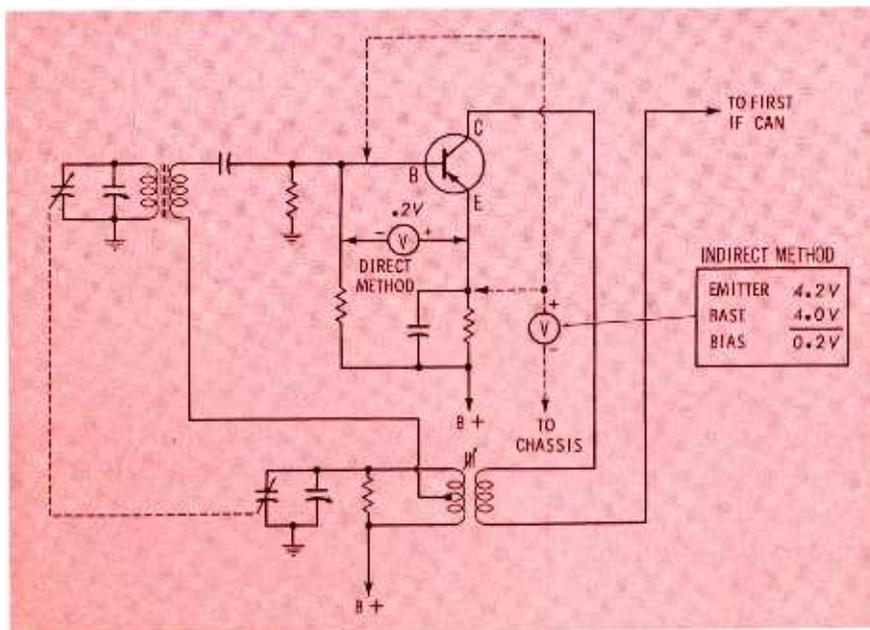


Fig. 1. Two methods to measure base-to-emitter voltage in transistor stage.

# NEW

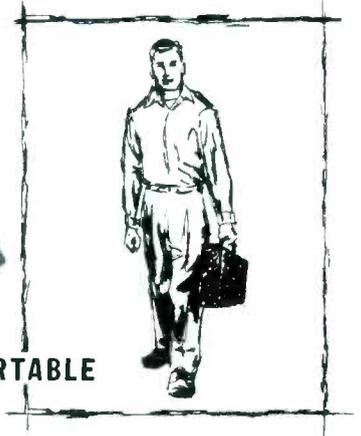

**FEWER CONTROLS**  
**VERSATILE**  
**CONTROLLED REJUVENATION**




**PORTABLE**

*Designed by*  
**VYTANT ALEKS**

**Easy to Use!**

## GC-CRT TESTER and REJUVENATOR

### FOR COLOR and Black and White!

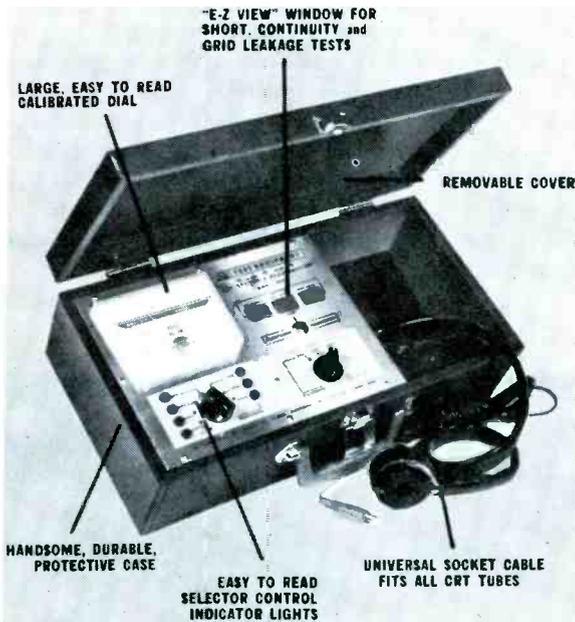

"E-Z VIEW" WINDOW FOR SHORT, CONTINUITY and GRID LEAKAGE TESTS

LARGE, EASY TO READ CALIBRATED DIAL

REMOVABLE COVER

HANDSOME, DURABLE, PROTECTIVE CASE

EASY TO READ SELECTOR CONTROL INDICATOR LIGHTS

UNIVERSAL SOCKET CABLE FITS ALL CRT TUBES

Just off the GC Production lines . . . designed for the serviceman to answer his specific need, simply and practically. The GC CRT Tester and Rejuvenator brings you, in addition to conventional testing, a unique DYNAMIC EMISSION test together with an effective CONTROLLED SHOT REACTIVATION circuit.

**CATHODE EMISSION TEST** is a GC first. A high voltage pulse applied to the 2nd anode of the CRT provides more accurate tube condition. Provisions for bias cut-off test.

**LIFE TEST** to predict the remaining useful life of the picture tube. **CONTROLLED DC shot REACTIVATION** cleans cathode surface for normal emission provided by 3 levels of reactivation intensity. Indicator light safeguards against overdose and tube damage.

**ADAPTABLE TO ALL 110° PICTURE TUBES** with special filament voltage, as well as the newest 19" and 23" Tubes (23EP4). **CHECKS SHORTS, FILAMENT CONTINUITY, GRID LEAKAGE** with "E-Z View" neon window indicator. Easy . . . positive.

**TESTS, REACTIVATES ALL COLOR CRT TUBES**, each gun separately including the newest "small button" Diheptal RCA unit.

**100% SELF CONTAINED** in handsome, protective carrying case. **ACCESSORY COMPARTMENT** contains power cord . . . a single combination socket cable to accommodate ANY CRT.

**PLUS** easy to read wide angle, calibrated meter and selector control indicator lights clearly indicate test functioning.

**No. 36-616 CRT TESTER AND REJUVENATOR** Net 69.95

**FREE** Send for new catalog of complete line of GC Test Equipment. Write Dept. 44, GC Electronics, 400 S. Wyman, Rockford, Ill.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_



## GC ELECTRONICS CO.

DIVISION OF TEXTRON ELECTRONICS, INC., 400 So. WYMAN STREET, ROCKFORD, ILLINOIS, USA





**3 SPEAKERS CAN NOW REPLACE 16**

# simply say **Delco**

These three new Delco Radio 8-10-ohm replacement speakers permit you to cut 16 numbers from your inventory. They can replace all units in current General Motors cars and many competitive makes. They

install easily and quickly, take a "tip jack," "blade," or solder connection. Excellent for home hi-fi and TV sets, too! Speak up for the latest in replacement speakers. Call your United Delco supplier today.

**THREE NEW SPEAKERS, ALL WITH SLOTTED MOUNTING HOLES**

Number	Size	Magnet Wt.	Mounting
6126	6 x 9"	1.6 oz.	front/rear
6127	4 x 10"	1.6 oz.	front/rear
6128	6" round	2.5 oz.	rear-seat

**SPECIAL**

**UNIVERSAL 8-10-OHM  
6 x 9" REAR SPEAKER PACKAGE**  
Contains all materials necessary for rear-seat speaker installation: Speaker, Grill, Wiring, Switch. Part No. 6122.

**Delco Radio** Automotive Radio Service Parts and Electro-Mechanical Devices are distributed nationally through **United Delco**

DELCO RADIO, Division of General Motors, Kokomo, Indiana



*most* **RELIABLE**  
**TRANSISTOR**  
*antenna* **AMPLIFIER**



**WINEGARD'S**  
**RED HEAD**


Red Head is one transistor amplifier that does what it's supposed to do . . . boosts those weak signals right out of the snow, gives brighter contrast to your pictures without trouble and call-backs.

Red Head has a lightning-protected circuit—no transistor burnout due to lightning flashes, static precipitation or power line surges. Built-in high pass filter rejects interference from Citizen's Band, hams, etc. Unlike other transistor amplifiers, it can't cause smear or graininess in picture from phase distortion . . . has linear frequency response, no suck-outs or roll-offs at end of bands. You get clear, bright picture detail on color and black and white.

OTHER ADVANTAGES OF WINEGARD'S RED HEAD—has newest type four-lead transistor . . . is AC powered, no corrosion at terminals, no polarity problems—has built-in 2-set coupler in power supply—mounts easily on antenna, mast or wall—powerful enough to drive 6 sets, can be remotod up to 1500 feet using 300 ohm twin lead or ladder line. New eye-catching bright red amplifier housing—gives lasting product identity.

Red Head is your *best* transistor antenna amplifier buy. Try a few and see for yourself. Write for technical data or ask your Winegard distributor.

There's a Winegard Quality Antenna for Every Reception Need

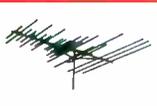 COLORTRON AMPLIFIER \$39.95	 COLORTRON ANTENNA Model C-44—Gold Anodized \$64.95	 COLORTRON ANTENNA Model C-43—Gold Anodized \$51.90	 COLORTRON ANTENNA Model C-42—Gold Anodized \$34.95	 COLORTRON ANTENNA Model C-41—Gold Anodized \$24.95
---	---	---	---	---

YOU GET AN EXTRA BONUS OF QUALITY AND VALUE FROM WINEGARD



**Winegard** ANTENNA SYSTEMS

3009-38 Kirkwood • Burlington, Iowa

for change in its operation due to circuit loading. This was true for the other circuits in the receiver, too.

**Current Measurements**


The current-measuring feature of a VOM also makes the instrument valuable in transistor repair work. Not only can you check to see that the total current drawn by the radio is within limits (good callback insurance after a repair job is complete), but you can also use current readings to check the operation of each transistor stage—as you'll see presently.

The total current drawn by a transistor radio varies from one receiver to another, of course, as does the amount required by a single stage. The RF and IF stages draw considerably less current than the driver and output stages—particularly if the output is wired in push-pull. For this reason, it's well to have some idea what values of current you might expect to find in individual transistor stages. Here are some typical values: RF and IF stages normally draw from .5 to 1.5 ma; driver stages from 1.5 to 3.5 ma; output stages, 5 ma or more, depending on the setting of the volume control. Let's take a closer look at a typical six-transistor radio, especially noting the current distribution throughout the stages.


Under idling conditions—no input signal, and volume control set to minimum—the total current measures 10.2 ma. The current distribution for each stage is as follows: converter, .5 ma; first IF amplifier, 1.4 ma; second IF amplifier, 1.2 ma; driver, 1.6 ma; push-pull output stage, 5.5 ma. Again, these current values are for no-signal conditions. Tuning in a station and rotating the volume control for a normal listening level, we see the *total* current drawn by the radio zoom to 35 or 40 ma, and at maximum volume, 60 to 70 ma. The majority of this current is drawn by the class-B driver and output stages.

The actual measurement of the current through an individual transistor stage can be accomplished by several different methods. One way is to measure the voltage drop across the emitter resistor (or col-

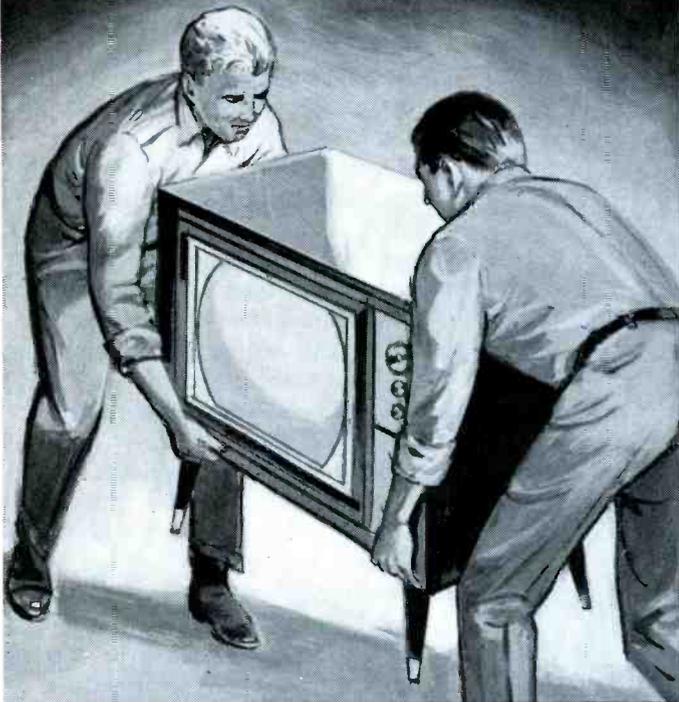It used to take 2 men to pull  
a color TV set into the shop...



BUT NO MORE

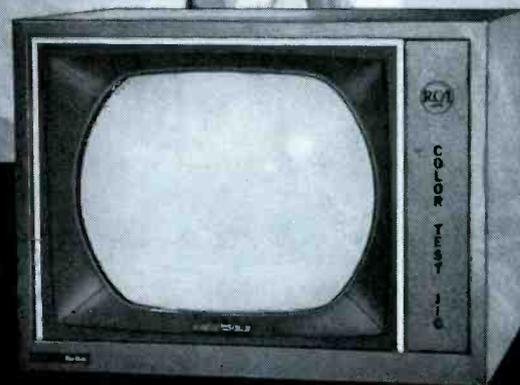

## RCA COLOR TV TEST JIG

Cuts your manhours on Color-TV home service calls

Here is a real "must" for anyone servicing or planning to service color TV sets.

No longer must you send two men to a customer's home to pull in his entire color set. Now, one man can simply remove the chassis and bring it back to your shop for testing, troubleshooting and alignment in your RCA Color TV Test Jig.

Look at some of the extra advantages built into this money-saving unit:

- **Minimizes costly damage claims.** Pulling chassis eliminates possibility of scratching or damaging a customer's cabinet when transporting it to and from his home.
- **Saves time.** Eliminates need to reconverge a customer's set when chassis is returned. Convergence control panel on Test Jig provides static and dynamic convergence for CTC-10, CTC-11 and CTC-12 chassis.
- **Versatile.** Can be used with CTC-4, 5, 7, 9, 10, 11 and 12 chassis.
- **Safe.** Supplied with factory-installed safety glass and kine mask.
- **Complete components kit,** supplied with unit, provides all necessary service components and instructions for installing RCA Color Picture Tube.
- **Professional appearance.** Finish matches that of your other RCA test instruments.

The RCA Color TV Test Jig is available through your Authorized RCA Parts and Accessories Distributor. See him this week to find out how this versatile instrument can help you capitalize on the growing Color TV servicing market.

For information on where you may obtain the RCA Color Test Jig, and for additional specifications, fill out and mail the coupon below.

RCA PARTS AND ACCESSORIES, CAMDEN, N. J.



The Most Trusted Name in Electronics

RCA Parts and Accessories  
P.O. Box 654, Camden, New Jersey

Please send me full specifications on the RCA Color TV Test Jig, and the name of the nearest distributor where I may obtain it.

Name \_\_\_\_\_

Company or Service Shop \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Available from all authorized ARCO distributors



# Arcolytic®

## 1401 Values...The largest selection of exact replacement twist-mount & tubular electrolytics

■ 99.99% high purity aluminum foil electrolytics at no extra cost! ■ Choose from stock any single, dual, triple or quadruple capacitance - voltage combination for replacement in television, radio, and other electronic equipment ■ Made to withstand high ripple and high surge voltages ■ Designed for 85°C high temperature operation ■ Greater shelf and operating life because only premium grade ingredients are used ■ Built and tested to meet EIA Specification RS-154 ■ Individually packaged with mounting plates for your convenience ■ Unconditionally Guaranteed.

# ARCO

ELECTROLYTIC DIVISION  
electronics inc.

Community Drive, Great Neck, New York • HUnter 7-0500

Branches:  
Dallas 7  
Los Angeles 35

lector resistor, if the stage has one), and then calculate the current by Ohm's law; you might find this to be the easiest way. Another method is to disconnect the emitter circuit and insert the current meter. You can do this without removing any of the components in the circuit, by merely cutting the printed foil (or circuit) going to the emitter, and connecting the meter across the open conductor.

A third method (which is also one of the quickest means of locating a defective transistor stage) involves connecting the meter to monitor the *total* current drawn by the radio. Then, one transistor at a time can be checked by shorting the base to the emitter while watching the meter for a change in current. The total value of current drawn by the radio will decrease a small amount when this test is performed, *if* the transistor is working; removal of the bias voltage stops current flow through the transistor. Make sure you check any stage that doesn't cause a change in current when this test is performed—it is probably inoperative. Caution: *Do not* short any element of a transistor to chassis as you might do in tube circuits—grid to ground, for example—because, in some circuits this action could cause excessive current and ruin the transistor.

### Resistance Measurements

For all general purposes, the ohmmeter section of a VOM operates in the same manner as that of many VTVM's. When using an ohmmeter in transistorized circuitry, you should guard against possible damage to the transistors. Many ohmmeters are capable of delivering enough voltage and current to ruin low-power transistors—those used as RF and IF amplifiers, for example. For this reason, it's best to follow two simple rules governing resistance measurements when semiconductors are present:

### Test Voltage

First, before you use the instrument, measure the voltage that is available at the ohmmeter's test leads. Most ohmmeters are powered by a single 1.5-volt dry cell, or two cells connected in series for a total of 3 volts. But, there are instruments that use higher voltages

**FINEST  
MONEY-MAKER  
FOR  
Professional  
Servicemen**

# Multiple-Socket Speed with Gm Accuracy

**PLUS OBSOLESCENCE PROTECTION**

**TESTS**  
All TV and Radio Tubes  
—Old and New

**TESTS**  
Nuvistors and Novars

**TESTS**  
European Hi-Fi Tubes,  
Voltage Regulators, and  
Most Industrial Types

**TESTS**  
the New 10-Pin Tubes

**TESTS**  
for True Dynamic  
Mutual Conductance (Gm)

**TESTS**  
New 12-Pin  
Compactrons



## Model 700 DYNA-QUIK DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER

See your B&K Distributor  
or Write for Catalog AP20-R

### TESTS BOTH OLD AND NEW TUBE TYPES—SELLS MORE TUBES PER CALL

All over the nation, thousands of professional servicemen rely on the "700". Once you use it, you'll be as enthusiastic as they are. *Everyday use has proved its speed . . . its accuracy . . . its efficiency.* This up-to-date, obsolescence-proof tube tester is designed for maximum use *today and tomorrow.* Provides multiple-socket section to quick-check most of the TV and radio tube types the *true dynamic mutual conductance way—plus* simplified switch section to check new tube types in Dyna-Quik emission circuit. Also includes provision for future new sockets.

Makes test under set-operating conditions. Checks each section of multi-section tubes separately. Checks for *all* shorts, grid emission, leakage and gas. Makes quick "life" test. Exclusive *adjustable* grid emission test provides *sensitivity to over 100 megohms.*

Makes complete tube test in seconds. Checks average set in a few minutes. Discovers weak tubes that need replacement. *Satisfies more customers. Sells more tubes. Saves call-backs. Insures your reputation. Pays for itself over and over again.* Net, \$169<sup>95</sup>

### Time-Saving, Money-Making Instruments Used by Professional Servicemen Everywhere



Model 960 Transistor  
Radio Analyst



Model 360 V O Matic  
Automatic VOM



Model 375 Dynamatic  
Automatic VTVM



Model 1076  
Television Analyst



Model 440 CRT  
Rejuvenator Tester

**NEW TUBE INFORMATION SERVICE**  
Available every 3 months, on subscription,  
for all B&K Dyna-Quik Tube Testers



**B & K MANUFACTURING CO.**

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.

Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.

on certain positions of the range switch. One unit uses 1.5 volts for the R x 1 and R x 100 ranges, and 7.5 volts for the R x 10K range. A few have as much as 15 to 30 volts available at the test leads. So, if you haven't already done so, rotate the selector switch on your meter to each resistance range and check the output voltage with a separate voltmeter. This way, you'll know how much voltage is available.

If more than 3 volts are present at your meter leads, on any range, you'd do well to check the voltage

rating of the transistors before you connect the test leads. The voltage rating of a transistor varies with the type, of course, as does the breakdown voltage between the base, emitter, and collector elements. Usually, transistor manuals list the breakdown voltage from the collector to the other two elements, but breakdown voltage isn't normally given for the base to the emitter. As a rule of thumb, don't apply to the *collector* of a transistor a DC test voltage that exceeds the supply voltage of the receiver, and don't apply a DC test voltage

from the emitter to the base of a transistor in excess of 3 volts. Generally, the 1.5 volts found in modern ohmmeters should be safe enough.

In passing, we might caution against the use of component checkers—a resistance-capacitance checker, for example—to measure the resistance of a transistor. Most of these instruments use bridge circuits, with a fairly high test voltage (AC in some)—enough to damage a transistor.

#### Test Current

The second rule to remember involves the current available from the ohmmeter's test leads. When measuring the resistance of circuits containing low-power transistors (or when checking the transistor out of circuit), use a high resistance scale—at least R x 100. Maximum current flows from the meter test leads when the range switch is in the R x 1 position. In this position, an excessive amount of current might be drawn by a transistor with low-resistance diodes—enough to ruin it, and quick. The R x 1 scale may be used to check high-power output transistors, for they are capable of handling the higher current available from the meter (often several hundred milliamperes).

#### Summary

The VOM is a versatile instrument for use in servicing transistor radios. In addition to having features to measure current, voltage, and resistance, (all needed for transistor troubleshooting) it is usually portable and ready for instant use, needing no external power.

If you will equip it with a few special probes for transistor servicing (alligator clips and needle-point tips, in particular) and keep it as a permanent test instrument on your transistor servicing bench, you'll find each repair job a bit easier; and your VTVM will be free for other applications.

#### Handful of Testers

The unit pictured, Heath Co.'s Model IM-20 *Handy Lab*, has quite a few instruments packed into its 52½ cubic inches—a DC voltmeter, a resistance and capaci-



- Tests TV and Radio Tubes —both old and new
- Tests all Novars
- Tests Nuvistors, 10-pin Tubes, and 12-pin Compactrons
- Tests Voltage Regulators, Thyratrons, Auto Radio Hybrid Tubes, European Hi-Fi Tubes, and Many Industrial Types

## B&K PROFESSIONAL QUALITY AT LOW COST

### Model 600 Compact Portable Dyna-Quik Makes Tube Testing Quick, Accurate, Profitable!

It's amazing how quickly you can accurately check out tubes on every call—sell more replacements, and make more money—with this up-to-date, low-cost professional quality tube tester.

Checks for all shorts, grid emission, leakage, and gas. Checks each section of multi-section tubes separately. Checks tube capability under simulated load conditions. Rejects bad tubes, not good tubes. Quickly reveals tube condition, saves customers, stops call backs, increases servicing profit.

Exclusive adjustable grid emission test. Sensitivity to over 100 megohms. Phosphor-bronze socket contacts.

Complete tube listing in handy reference index.  
Handsome, sturdy leatherette-covered carry-case.

Size 8½" x 11" x 4½". Net, \$74.95



QUICK, DIRECT, ERROR-FREE  
READINGS WITHOUT MULTIPLYING

Model 375  
VTVM  
Net, \$89.95

Model 360  
V O Matic  
Net, \$59.95



See Your B&K  
Distributor  
or Write for  
Catalog  
AP20-R



**B & K MANUFACTURING CO.**

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 79, Ont.

Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.

# NOW EVERYONE CAN QUICKLY Set up and Service Color TV



**1 PATTERN DISPLAY STANDARD**  
Shows correct pattern in window viewer for visual guide

**2 PATTERN SELECTOR**  
Produces each pattern individually for quick, easy convergence

**3 AUTOMATIC DECONVERGENCE**  
Simplifies static and dynamic convergence. No digging into set

**4 COLOR SELECTOR**  
Produces each color one at a time for accurate color set-up

**5 COLOR GUN KILLER**  
Automatically enables the technician to actuate any combination of the 3 guns

**6 DEMODULATOR ALIGNMENT**  
Makes alignment extremely simple, without going into the color set

## New! **B&K** Model 850 **COLOR GENERATOR**

*Most Complete, Most Versatile, Portable Instrument for Use in the Home and in the Shop  
Makes Color TV Set-up and Service Easier, Faster than ever!*

Now every service technician can be ready to set-up and service color TV with amazing new ease and speed! New advanced design simplifies the entire operation, saves time and work in every installation. Eliminates difficult steps in digging into the color TV set. Gives you new confidence in handling color.

**Produces Patterns, Burst, and Colors Individually**—Provides dot pattern, crosshatch, vertical lines, horizontal lines, burst signal, and individual colors—one at a time—on the TV color set—for fastest, easiest check. Unique window-viewer on front of the instrument panel shows you each pattern as it should be—gives you an exclusive display standard to use as a sure guide for quick, visual comparison.

**Provides Accurate, Individual Color Display**—Produces Green, Cyan, Blue, B-Y, Q, Magenta, R-Y, Red, I, Yellow, and Burst—one at a time. All colors are crystal-controlled and are produced by a precision delay-line for maximum accuracy. Each color is individually switch-selected—no chance of error.

**Provides Accurate NTSC-Type Signal**—Color phase angles are maintained in accordance with NTSC specifications.

**Makes Convergence and Linearity Adjustments Easy**—Highly stable crystal-controlled system with

vertical and horizontal sync pulses, assures the ultimate in line and dot stability.

**Simplifies Demodulator Alignment**—The type of color display produced by this instrument provides the ultimate in simplicity for precise demodulator alignment.

**Provides Automatic Deconvergence**—Eliminates the necessity for continual static convergence adjustments. The instrument automatically deconverges a white into a color dot trio without digging into the color set to mis-adjust the convergence magnets. It also deconverges a white horizontal or vertical line into red, green and blue parallel lines. This greatly simplifies dynamic convergence adjustments.

**Provides Exclusive Color Gun Killer**—Front-panel switch control makes it easy to disable any combination of the three color guns. Eliminates continuous adjustment of the background or screen controls, or connection of a shorting clip inside the receiver. The switch also selects the individual grids of the color tube and connects to a front-panel jack to simplify demodulator alignment.

**Provides Switch-Selected R.F. Signals**—Factory-tuned, for channels 3, 4, and 5—for open channel use in your area.

Model 850 also includes other features that make it invaluable for home and shop use. Net, **\$199<sup>95</sup>**

See Your B&K Distributor  
or Write for Catalog AP20-R




**B & K MANUFACTURING CO.**

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.


Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.

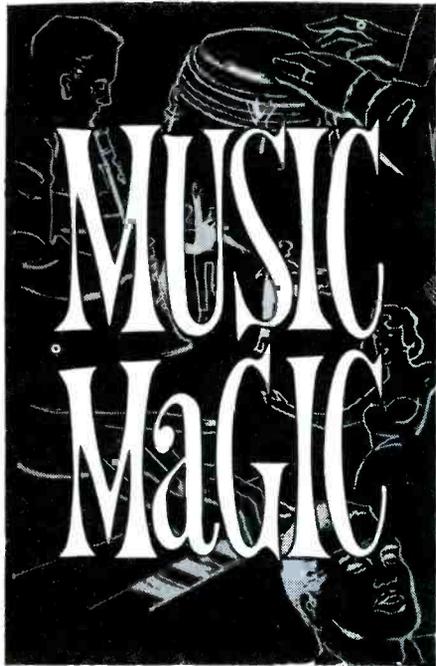Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.



# Utah Sorcerer

SPEAKER SYSTEM

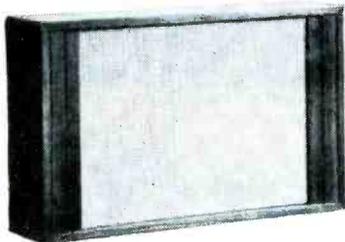

with a flick of the wrist...

and like Magic, your room fills with bewitching, beguiling sound which could only come from Utah's Sorcerer. Only the magic of Utah's electronic ingenuity produces the big, the full, distortion-less sound from such a compact, complete speaker cabinet.

- Styling—fits Early American through Modern decor.
- Components—Two Utah Speakers, an 8" Woofer, 5" Tweeter.
- Cabinet—Hand-rubbed, oiled walnut veneer, applied to 1/2" plywood, a standard for fine furniture.
- Location—Wall, bookshelf, floor, table-top.
- Dimensions—20" in length, 12" high, 5" deep.
- Power rating—12 watts.
- Uses—Hi-Fi or Stereo, as extension speakers for record player, radio or TV.

MODEL SH-4W—Finished Walnut Veneer



HUNTINGTON, INDIANA



tance substitution box, an AC indicator, a continuity tester, and an AF and RF signal generator.

The DC voltmeter is built around a 1-ma meter movement, and the input sensitivity of the instrument is 1000 ohms per volt. It has four ranges—15, 50, 150, and 500 volts DC—with an accuracy of  $\pm 10\%$ .

The resistance-substitution section contains five values (100, 1000, 10K, 100K, and 1 meg); all are rated at 1 watt, with 5% tolerance. The capacitor portion of the Handy Lab consists of five 400-volt capacitors: .001, .005, .02, .1, and 8 mfd; the latter is an electrolytic unit.

An NE-51 neon lamp is incorporated as the AC indicator, and a #49 pilot lamp works in conjunction with a pair of penlight cells to form a continuity checker—effective for circuits with resistance less than 50 ohms.

Two transistors are wired into Hartley oscillator circuits—one operating at approximately 1000 cps and the other between 450 kc and 700 kc. The 450-kc RF output can be modulated by the 1000-cps audio tone, providing a modulated RF test signal.

The several functions of the Model IM-20, coupled with its small size, make it a handy device for the service caddy. It can be used in a number of servicing situations in the home: for locating open filaments by continuity or voltage tests; for measuring B+ and other DC voltages in the set; for checking resistors and capacitors by substitution; for checking the effectiveness of most electrolytics; and for signal injection to help isolate faulty stages. ▲

# BUZIT TRANSISTORIZED SIGNAL TRACER

FOR ONLY \$8.10 DEALER NET WITH BATTERIES



USED FOR TROUBLE SHOOTING

- A.F. CIRCUITS • I.F. CIRCUITS
- R.F. CIRCUITS • CONTINUITY CHECKS • SPEAKERS, ETC.

EXCELLENT FOR TRANSISTOR RADIOS BECAUSE BUZIT USES ONLY A 3 VOLT POWER SUPPLY

ASK YOUR ELECTRONIC PARTS DISTRIBUTOR FOR MODEL NO. **BZ-1**

Manufactured by **WORKMAN Electronic PRODUCTS, INC.** SARASOTA, FLORIDA


## New BERN'S Perfect Pin Crimper

### Picture-Tube Repair Tool

Also for—5U4, 6SN7, 6BQ6, etc.

Eliminates that hard soldering job

only \$1.25 each

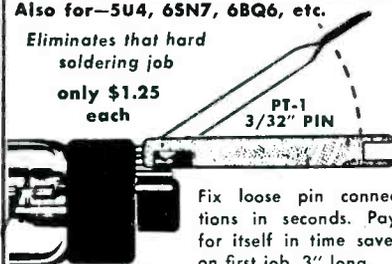

Fix loose pin connections in seconds. Pays for itself in time saved on first job. 3" long.

Patented Intermittent operation of picture tubes due to defective solder connections easily corrected. Provides solid electrical connections, can also be used as channel-selector wrench and screwdriver. Pin keeps its original form. A 3-in-1 tool.

### 3 MODELS ELIMINATE SOLDERING

Makes Solid Electrical Connections Phono Pin-Plug Crimper

Slip wire in "pin plug," insert in tool, and squeeze... job is done.



C-rings 1c ea.

Use end of tool to push on Cring for ground connection.

Ant. plugs, hi-fi, multiple plugs, public address, radio and TV tubes, radar, speakers, and loop connections. Many, many more uses.

Model LC-3 for 5/32" pin diameter

At your parts distributor or write us

**BERN'S**

Mfg. Co. 9853 Chalmers, Detroit 13, Mich.

*Every RCA Victor New Vista® TV uses  
Space Age Sealed Circuitry... extra  
dependable easy-to-service circuits that are...*

# more precise

*than old-fashioned all hand-wired circuitry!*



Old-fashioned all hand-wired Circuitry



Precision Crafted RCA  
Space Age Sealed Circuitry

Let your own TV  
service records  
prove the   
dependability  
of RCA Victor  
New Vista® TV

SEE WALT DISNEY'S "WONDERFUL WORLD OF COLOR" SUNDAYS, NBC-TV NETWORK



The Most Trusted Name in Electronics

TMK (s)®

March, 1963/PF REPORTER 59

# CHEK-IT CIRCUIT TESTER

FOR ONLY **\$1.49** DEALER NET  
LESS BATTERIES

**BATTERY OPERATED  
TESTS WITH POWER OFF**



MADE IN  
U.S.A.


- CONTINUITY • FUSES • SWITCHES
- CHIMES • APPLIANCES • MOTORS
- BUZZERS • PUSH BUTTONS
- AUTO IGNITION and VOLTAGE REGULATORS, ETC.

ASK YOUR ELECTRONIC  
PARTS DISTRIBUTOR FOR

**W MODEL NO. BZ5**

Manufactured by  
**WORKMAN Electronic PRODUCTS, INC.**  
SARASOTA, FLORIDA
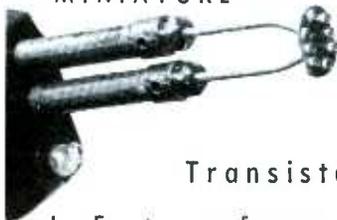
## DeSod System PRINTED CIRCUIT DESOLDERING TOOLS FAST • EASY • QUICK CHANGE MINIATURE



Transistor


I. F. transformers

Removed and replaced in one minute with no damage to transformer or printed board.

Tools available for most multi-contact components of printed boards. DeSod tools fit your present solder gun.

Available from your local distributor.

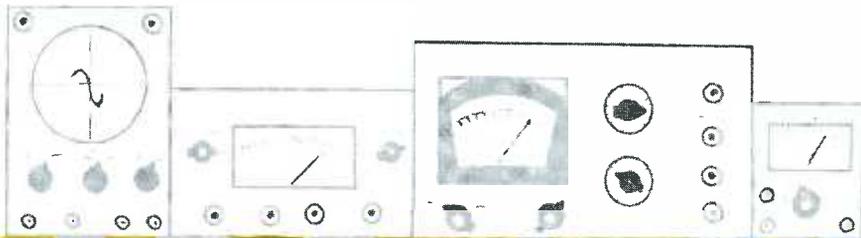**EVERSOLE INDUSTRIES**  
2121 W. State St.  
Fremont, Ohio



# NOTES ON TEST EQUIPMENT

by **Forest H. Belt**

## Picture-Window Color

A rather novel idea has been incorporated in the Model 850 *Color Analyst* (Fig. 1) designed and built by the B & K Division of Dynascan Corp. A window in the panel of the instrument displays the hue and the design of the color test pattern that should be seen on the color-set screen. No matter what pattern is selected — color or convergence signals—it appears in the window of the Model 850 exactly as it should appear on the receiver CRT, making comparison easy.

Specifications are:

1. *Power Required* — 117 volts AC, 60 cps, 36 watts.
2. *RF Output*—Channel 3, 4, or 5 selected by rear-panel switch; unmodulated sound carrier displaced 4.5 mc from the video carrier.
3. *Video Patterns* — Convergence signals consisting of 300 dots, 10 vertical lines, 14 horizontal lines, or crosshatch of 10 vertical and 14 horizontal lines; video available at panel jack, with polarity and amplitude controlled by a panel potentiometer.
4. *Color Signals* — Burst, yellow, I, red, R-Y, magenta, Q, B-Y, blue, cyan, and green; signal phases all correspond to those on the NTSC color-phase wheel.
5. *Controls and Terminals* — four rotary switches: PATTERN, COLOR, POWER, and GUN KILLER; two slide switches: COLOR SYNC-NORMAL and CHANNEL (on rear panel); pin jacks: HORIZONTAL, VIDEO, DEMODULATOR, and GROUND; permanently attached CRT cable, deconvergence cable, and RF cable.
6. *Other Features* — Metal mirror in cover; rear compartment for storing leads and cables; window on front panel, indicating pattern being generated; carrying handle for portability.
7. *Size, Weight, Price* — 9" x 12¾" x 9"; 13 lbs; \$199.95.

The Model 850 is a color-signal generator for use with any color TV receiver. It will provide all the signals normally needed for chroma-circuit adjustments, demodulator phasing, and convergence. The signal can be applied to the antenna terminals of the TV set,

or else connected at the output of the video detector, since both RF and video outputs are provided from the Model 850. The VIDEO control on the front panel of the instrument makes it possible to produce either positive-going or negative-going video signals, for injection at any point in the video amplifiers of a receiver.

An examination of the block diagram in Fig. 2 will point out some of the features of this instrument. In many sections, it is similar to other color generators; for example, the dot-bar section uses the blocking-oscillator frequency dividing arrangement that is extremely popular in modern instruments because of the excellent stability. The 31.5-kc divider, however, is a multivibrator.

The Model 850 is one of the first such instruments to make extensive use of transistors—four in all. Most of them are used as pulse shapers in the various circuits.

The operation of the Model 850 is as follows: The 189-kc master oscillator controls all actions. When the PATTERN switch is set for one of the convergence patterns, the divider oscillators reduce the frequency of the pulses to form horizontal sync from the 15.75-kc divider, vertical sync from the 60-cps divider,



Fig. 1. Window of this color-bar unit shows color pattern to aid servicing.

# New TRANSISTOR RADIO ANALYST

makes it Easy and Profitable to Service all Transistor Radios



Model 960

TRANSISTOR RADIO ANALYST

with Exclusive *DYNA-TRACE*  
Single-Point Probe—and Built-in  
Metered Power Supply and VTVM


Complete Transistor Radio  
Service Shop in One Instrument

Signal-Generator, Power Supply, Milliammeter, VTVM, Battery Tester, Ohmmeter, and Both In-Circuit and Out-of-Circuit Transistor Tester—All in One

Also Speeds Servicing of Tube-Type Radios

Check all circuits - Pinpoint any trouble ... in minutes

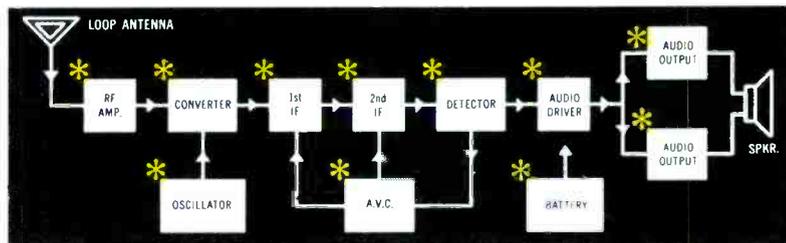Now you can profit from transistor radio servicing! This amazing new B&K "960" ANALYST gives you *everything* in one complete easy-to-use instrument. Makes transistor radio servicing *quick and easy*. Nothing else is needed except the transistor radios themselves waiting to be serviced. Brings you new customers for service, parts, and batteries. Makes this new business *yours*.



#### EASILY TROUBLE-SHOOT ANY STAGE BY UNIQUE POINT-TO-POINT SIGNAL INJECTION

The ANALYST gives you a complete signal-generating source for point-to-point signal injection. Easily enables you to trouble-shoot any transistor radio—check all circuits stage-by-stage—isolate and pinpoint the exact trouble in minutes.

Supplies modulated signals, with adjustable control, to check r.f., i.f., converter, and detector. Supplies audio signal to check audio driver and audio output. Provides unmodulated signal to test local oscillator. Provides separate audio low-impedance output for signal injection into loudspeaker voice coils to check speaker performance.

#### BUILT-IN METERED POWER SUPPLY FOR EASY SERVICING

Makes it easy to operate radio under test, while you inject your own signals. Provides from 1 to 12 volts in 1½ volt steps. Supplies all bias taps that may be required.

#### SIMPLIFIES IN-CIRCUIT TRANSISTOR TEST WITH NEW DYNA-TRACE SINGLE-POINT PROBE

Unique single-point probe needs only the one contact to transistor under test. No longer are three wires required to connect to emitter, base, and collector. Gives fast, positive meter indication. Saves time. Makes trouble-shooting simple and easy.

#### BUILT-IN VTVM

Includes high-input-impedance vacuum-tube voltmeter, which is so necessary for transistor radio servicing.

#### TESTS ALL TRANSISTORS OUT-OF-CIRCUIT

Meter has "Good-Bad" scale for *both* leakage and beta. Also has direct-reading Beta scale, calibrated 0-150. Assures quick, accurate test. Also automatically determines whether transistor is NPN or PNP. Meter is protected against accidental overload and burn-out.

Model 960. Net, \$99<sup>95</sup>

Solve Every Service Problem and Profit with a Modern B&K Service Shop. See Your B&K Distributor or Write for Catalog AP20-R



**B & K MANUFACTURING CO.**

Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.  
Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.  
Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.



**WITH UTICA  
CB TRANSCEIVERS**

**T & C II  
TRANSCEIVER**

New dual conversion 6 channel crystal controlled transceiver with tunable receiver for all CB channels. S meter and signal strength output indicator, external crystal socket, auxiliary speaker terminal and universal power supply. Deluxe chrome cabinet. List Price **199.95**



**TOWN & COUNTRY  
MC-27 TRANSCEIVER**

Dual conversion 6 channel crystal controlled. Exceptional sensitivity and selectivity. Double Gated Noise Suppression circuit, AVC with improved squelch circuit. Universal power supply. Deluxe chrome cabinet. List Price **179.50**



**CB ANTENNAS**

**GIZMOTCHY** 2 in 1 Vertical-Horizontal Beam Antenna for hi-efficiency and greater distance base station performance. List Price . . . . . **\$5.95**

**BUDDY WHIP** 96 inch fibre glass mobile antenna. Can be adjusted to any position from driver's seat. List Price **\$24.50**

**UTICA**

COMMUNICATIONS CORP., Dept. PF-3  
2917 W. IRVING PARK RD., CHICAGO 18, ILLINOIS

Sold thru leading Parts Distributors

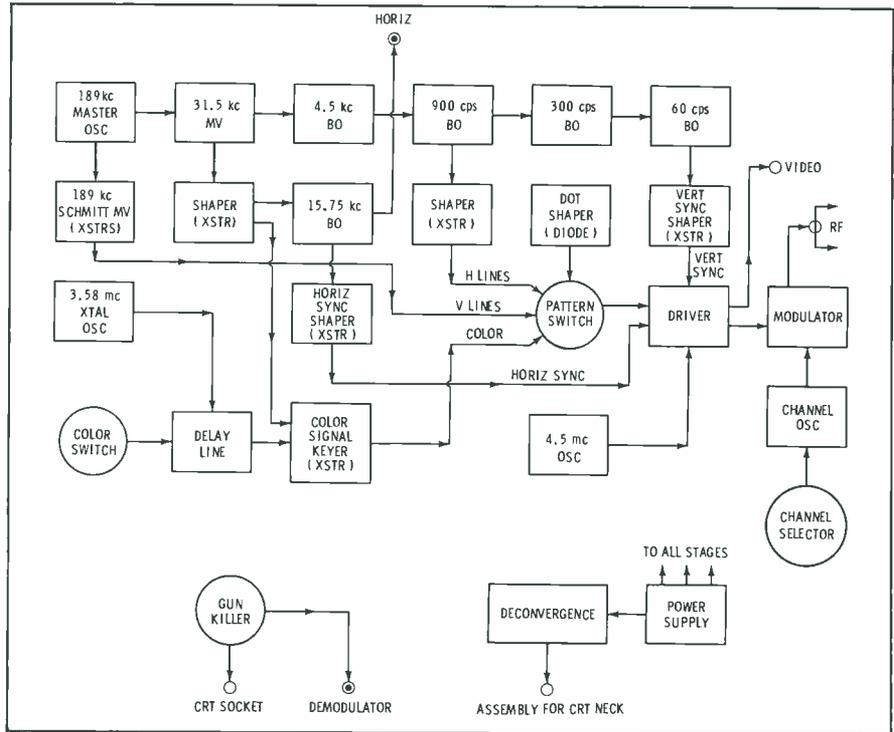


Fig. 2. Gun-disabling section of Model 850 is separate from rest of instrument.

and horizontal convergence lines from the 900-cps divider; vertical convergence lines are taken directly from the 189-kc master oscillator. The sync signals are fed to the driver stage to be mixed with the rest of the composite video signal. The pulses for convergence lines are coupled to the pattern switch, which selects the pulses to be sent to the driver stage. For dots, a diode arrangement clips out the lines from a basic crosshatch pattern, leaving only the crossover points, and forming approximately 300 dots for the video signal.

When the PATTERN switch is set for color patterns, the color circuits are coupled to the driver stage. A pulse from the 31.5-kc multivibrator serves to key the color signal in such a way as to form a "bar" in the center of the color screen. This bar contains no color information, resulting in the display shown in Fig. 3—a dark bar in the center with color on both sides.

The different colors are developed in

a delay line which alters the phase of the 3.58-mc chroma signal in accordance with NTSC standards. The COLOR switch picks off signals at specific points on the delay line for the color keyer, which then sends the chroma signal to the driver tube for mixing with the sync signals.

A three-channel RF oscillator permits the choice of channel 3, 4, or 5. The RF signal is fed to a modulator where the video and/or chroma signals are impressed on the carrier, and the modulated RF signal is coupled to the RF output cable. A VIDEO jack at the output of the driver stage permits direct injection of the signal into the receiver video stages, if this form of connection is desired. In case the user may need to adjust 4.5-mc traps, a signal from a crystal-controlled 4.5-mc oscillator is provided. It is fed into the driver stage, where it beats against the carrier signal in the modulator and produces a sound carrier. There is no audio modulation.

**PRECISION TUNER SERVICE**  
P. O. BOX 272      1200 S. WALNUT ST.  
BLOOMINGTON, IND.      EDISON 99653

**7.50**  
V or U  
**COMBO PLUS POSTAGE**  
9.95

**6 MONTH WARRANTY**

All Types T.V. Tuners Cleaned, Repaired and Aligned to Factory Specifications. Same day in shop service on most Tuners. Price Includes Minor Parts, Major Parts at Cost Price. We use Original Parts if possible. State Make Model and Enclose all Parts and Tubes. Pack Well and Insure.  
**ALSO HAVE LARGE STOCK OF EXCHANGE TUNERS, WRITE FOR TYPES AND PRICES.**

DISTRIBUTOR DIVISION/1963

# service components



resistors  
potentiometers  
switches



## CLAROSTAT

PHONE: (AREA CODE 603) 742-1120 • TWX: 603-742-2038

# GUIDE TO PROFITS

Quality components are the first, and basic step, in profitable servicing. For resistors, potentiometers and switches always refer to the brand-new 1963 Clarostat Service Components Catalog now available from your Clarostat distributor, or write . . .

# CLAROSTAT

MFG. CO. INC., DOVER, NEW HAMPSHIRE



# New Business Opportunity For Independent Servicemen



Mr. A. D. Mayo Orlando, Florida



Mr. J. Blumenthal Detroit, Michigan



Mr. A. Smeland Camden, New Jersey



Mr. H. Seiden Albany, New York



Mr. M. Goldweber Cleveland, Ohio



Mr. J. Errico Trenton, New Jersey

## Join These Former Servicemen Who Now Own Successful Lafayette Associate Stores

You can join the 65 former servicemen who now know the true independence and security that comes from owning your own business. As a franchised Lafayette Radio Electronics Associate, you benefit from more than 40 years experience selling hi-fi components, citizen band radios, recorders, science and electronics kits, tools, hobby supplies, TV repair equipment and all the other things that make this the fastest-growing industry in the country. You'll have your own exclusive marketing area and the same guidance and advertising support that has helped many men such as you (some with little or no business experience) become successful business leaders. If you have a basic knowledge of radio, television or electronics, and you're willing to invest from \$10,000 to \$30,000 to get the things you've always wanted out of life, mail the coupon today for further information.

**Lafayette Radio Electronics Corporation**  
111 Jericho Turnpike, Syosset, L. I., New York

PF-33

**Mr. Robert Laub**

Please send me full information on how I can own my own profitable business.  
I understand there is no obligation.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_


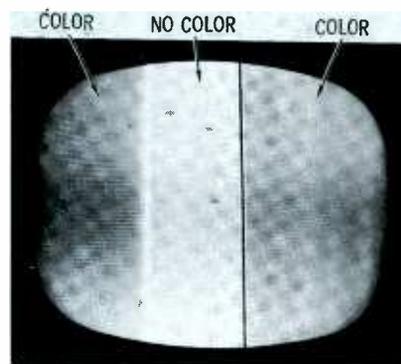


Fig. 3. Bar pattern of color generator.

The gun-killer section is independent of the other circuits in the instrument. It is connected to the receiver by an adapter socket that plugs into the base of the color CRT and accommodates the regular CRT socket. The industry hasn't standardized on labeling of switches used in instruments of this type, so various labels may indicate either the gun or guns that are disabled or the gun or guns left on. The GUN KILLER switch on the Model 850 follows the practice of indicating which guns are on. The guns are disabled by the time-honored method of shunting a 100K resistor to ground from the CRT grids. Positions are provided to leave any single gun operating, or any combination of two guns.

A unique feature of the Model 850 is the deconvergence attachment. In operation, an electromagnet is clamped on the neck of the CRT and positioned between the red and blue convergence coils. By rotating the POWER switch to the "deconverge" position, you send DC current through the deconvergence coil and thus displace the dots on the color screen. In this way, the dots can be deconverged for inspection at any time during normal convergence procedures.

Using the Model 850 on one of our lab receivers proved its usefulness, especially for demodulator-phase adjustments. The gun-killer circuit provides a jack for connecting a scope to check demodulator adjustments, or they can be monitored by watching the screen of the color CRT. Color-generator instruction manuals often differ from one another in the technique recommended for adjusting phase in the demodulators. The booklet included with the Model 850 suggests the "null" method. This consists of feeding the R-Y signal into the receiver, disabling the red and green guns (GUN KILLER switch in the "blue" position), and checking for a uniform dark screen. You see, if the phasing adjustments are correct, no R-Y color signal should appear on the blue CRT gun, and it should be cut off. Then, since the red and green guns are disabled, the portions of the screen where color normally appears (Fig. 3) should look the same as the dark section. To check the other demodulator adjustment, feed the B-Y signal to the set, disable the blue and green guns (turn the GUN KILLER to "red"), and tune for a null — a dark

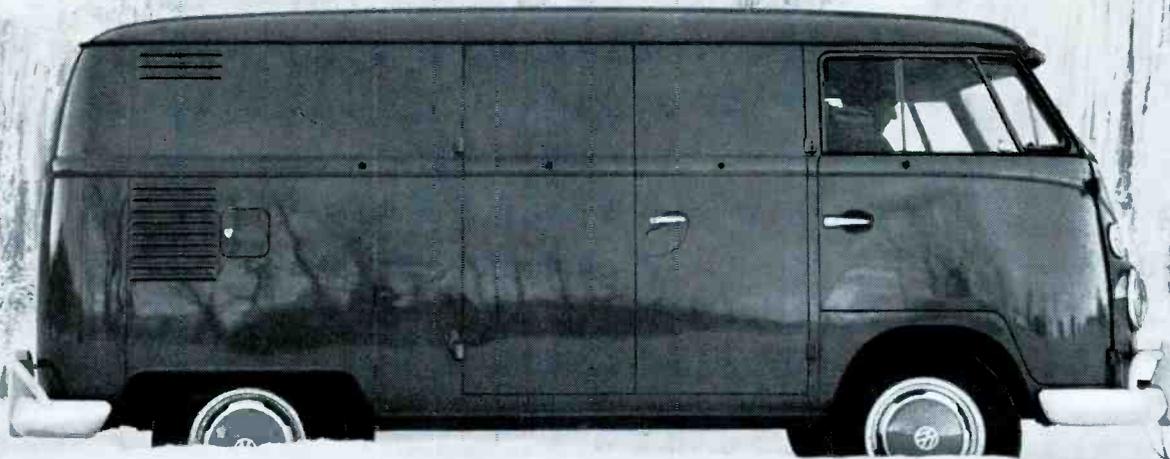

©1963 VOLKSWAGEN OF AMERICA, INC.

## How to succeed in snow business.

It's easy. Get a truck with:

- (a) An air-cooled engine in back.
- (b) The initials VW in front.

And there you are: a roaring success in the snow.

The weight of the Volkswagen engine sits directly over the drive wheels.

So you go, while others grunt.

(For years people have put sandbags in sedan trunks for the same reason.)

Eight inches of snow is considered tractable for a VW. It plows through mud, sand and slush just as easily. Fully loaded.

(Fully loaded means 1830 lbs. Nearly twice the load of regular trucks.)

And once you get through the drifts, you'll also get 20 to 30 mpg.

And a truck that will never freeze up. Or boil over, either.

So how would you rather be pushed?

By an engine in the rear?  
Or by your friends?






**ATLAS  
SOUND  
EC-10**  
ALL-NEW  
PAGING SPEAKER

**Breakthrough**  
IN DESIGN — MATERIALS — PERFORMANCE

Every way you look at it, the American-made Atlas Sound EC-10 is 100% NEW. For its size and price, this compact, weather-proof speaker is a powerhouse of crisp, articulate sound for a wide variety of applications. Ideal where space, weight and appearance are a factor. Small in dimensions, but a giant in performance. Low in price, but high in value.

Molded of Implex\* — a new, tough, all-weather acrylic plastic — the horn and throat sections assure vibration-free and resonance-free output from its acoustically-clean lines. Rugged corrosion-proof die castings provide extra strength where needed. Overall the handsome beige-and-brown colors blend with any decor. • Also new is the magnetic circuit. Engineered around a new highly efficient ceramic magnet, the design confines the flux concentration to the voice coil gap area, thus increasing conversion efficiency. • The diaphragm assembly is a departure, too! It's reinforced phenolic, bonded to the voice coil in one piece, and self-aligning. • The adjustable bracket is different, too! Of tough steel, its clever design makes mounting simple and secure.

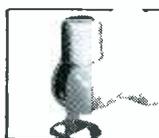The Atlas Sound EC-10 paging speaker is worth listening to — and hear this — the list price is only ..... **\$23<sup>75</sup>**



**ATLAS SOUND T-4 TRANSFORMER**  
For multiple speaker installations, Atlas Sound T-4 weatherproof line matching transformer is specially designed for the EC-10. You mount it on the speaker with just a single screw. **\$6.25 List**

Specifications: Power 6 watts; Standard Impedance 8 ohms (available 45 ohms); Length Overall 6 3/8"; Bell Diameter 6 1/4"; Weight 2 lbs.

\*t.m. Rohm and Haas

Write for full details and latest catalog.

**ATLAS SOUND** Division of American Trading and Production Corporation  
1419-51 39th Street, Brooklyn 18, N. Y. • In Canada: Atlas Radio Corp. Ltd., Toronto

**R** FOR "DOCTORS OF SERVICING"



**Where there's  
a contact...  
or a relay...**

**Service with Contact Shield! Protective! Corrective!** It not only cleans and safeguards contacts better on TV, radio, and hi-fi sets; on all relay-operated electrical equipment, regular protective maintenance with this versatile cleaner prevents sticky relays—while corrective servicing unsticks them... **in seconds.** Promotes greater conductivity, keeps relays working smoother, longer. Contact Shield—the professional service man's cleaner.

**APPLICATIONS INCLUDE:**

- Bowling Alley Automatic Pin Spotters
- Vending Machines
- Slot Machines
- IBM Computers and other data processing equipment
- Industrial Equipment using relays, such as welding machines, etc.
- Pinball Machines
- Telephone Switchboards

For handy guidebook to better servicing, write Channel Master Corp., Ellenville, N.Y.

screen all the way across. If both tests show a "nulled" screen, the phasing adjustments are okay.

The instruction manual is very thorough in describing color alignment setups for all major color television chassis, and goes into considerable detail on various other phases of color-TV servicing with the Color Analyst.

### Semiconductor Analyzer

One of the more recent entries in the semiconductor-tester field is the Seco Model 250 *Transistor and Tunnel Diode Analyzer* (Fig. 4). This unit can perform comprehensive tests on both low and high power transistors, as well as on tunnel diodes, zener diodes, and ordinary germanium diodes.

1. *Power Required* — 117 volts AC, 60 cps, 11 watts; available also in battery-powered model using three 1.5-volt flashlight cells.
2. *Transistor Tests* — both signal and power types, NPN or PNP, and triode types; tests quality,  $I_{cbo}$ ,  $I_{ceo}$ , and DC beta; special circuit for balancing out  $I_{ceo}$  during gain tests; quality can be checked with transistor in circuit or out.
3. *Diode Tests*—Signal or power types, zeners, tunnel (Esaki) diodes; forward and reverse current; checks negative resistance in tunnel diodes.
4. *DC Voltmeter*—Three ranges, from 0 to 1, 10, and 100 volts DC; sensitivity 5000 ohms per volt.
5. *DC Milliammeter* — Three ranges, from 0 to .2, 10, and 100 ma.
6. *Ohmmeter* — One range, with 150 ohms center, 5000 ohms highest readable scale mark.
7. *Signal Generator* — Uses any good transistor plugged into test socket; audio frequency on fundamentals; RF-IF signals on harmonics.
8. *Panel Meter* — 3 1/2" face size; sensitivity 200 ua; scales: from 0 to 200 and 0 to 10 for reading microamps.



Fig. 4. Unit can test many different kinds and types of semiconductor units.

# WHY... SERVICE COLOR TV ?

**WHY WAIT?  
YOU CAN MAKE  
MONEY NOW!**

**...IF YOU'RE EQUIPPED - AND  
A WIDE BAND SCOPE IS A MUST**



**OVER 750,000 SETS IN 1963**  
**65% OF NBC PROGRAMMING\*  
IN COLOR**  
**LOWER PRICED 70° SETS TO BE  
INTRODUCED IN 1963**  
**1,500,000 ALREADY IN USE**


\*PRIME TIME

This Hickok-quality, full 5", wide-band scope - factory assembled, wired and calibrated can put you in color TV service... for less than \$200.00.

- Rise time—less than 0.08  $\mu$ sec.
- AC response—5 cycles to 4.5 MC within 3 db
- Vertical sensitivity—40 MV RMS/inch
- 5 times horizontal sweep expansion
- Sharp, bright (1600 volts anode potential)  
Trace with full astigmatic correction  
and, of course, it's...



THE COMPLETE COLOR LINE

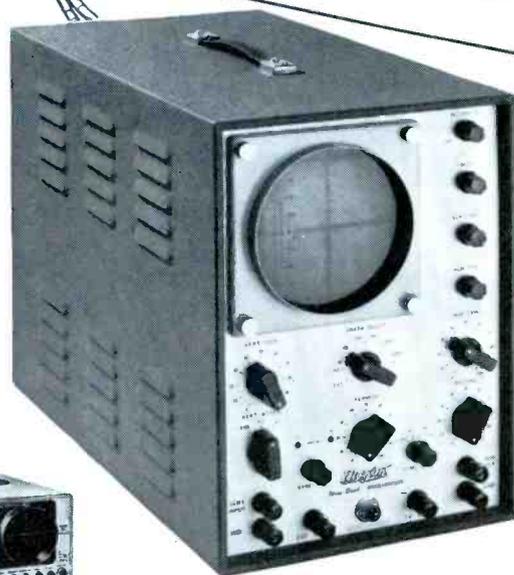

MODEL 615



MODEL 656XC



MODEL 660



MODEL 661



MODEL 675A

THE **HICKOK**

**ELECTRICAL INSTRUMENT CO.**  
10566 DUPONT AVENUE • CLEVELAND 8, OHIO

**PLANET**



TYPE L . . . for long, long years of service life ask your distributor for PLANET LYTICAPS, the universal replacement type electrolytic capacitor. Available in a wide range of capacities in voltages from three to five hundred. The Planet listing carries many of the newer values required for adequate servicing of both TV and industrial electronic equipment. Planet LYTICAPS are called out on the blueprints of many blue chip equipment manufacturers because their engineers found that LYTICAPS are truly "Engineered for Quality".

Write today for complete information

**PLANET SALES CORPORATION**  
 225 Belleville Avenue Bloomfield, New Jersey

**TRANSISTORIZED CHARGER**  
 MADE IN U.S.A.

**FOR WINTER-WEAK BATTERIES**



- MODEL NO. BC-6 FOR 6 VOLT
- MODEL NO. BC-12 FOR 12 VOLT

ONLY **\$280** DLR. NET

AT YOUR ELECTRONIC DISTRIBUTOR

MANUFACTURED BY **WORKMAN Electronic PRODUCTS, INC.**  
 SARASOTA, FLORIDA

**KARG**



**FM Stereo Multiplex Signal Generator**

Produces the FCC specified composite Stereo Multiplex signal.

Production alignment and testing of Stereo Adaptors, Tuners and Receivers.

Servicing and alignment of Tuners and Adaptors.

- Model MX-1G cabinet \$250.
- Model MX-1G rack \$255.

**SAVE \$100. Build your own Precision MX-1G Generator**  
 —kit \$150.

Send complete data and specs.

For prepaid shipment in U.S.A., send check or money order to: **KARG LABORATORIES**  
 162 ELY AVENUE, S. NORWALK, CONN.

milliamps, volts, and beta; 0 to infinity for ohms; I<sub>ceo</sub>, I<sub>cbo</sub>, and diode quality; meter movement protected from overload by internal diode.


9. Controls and Terminals—three potentiometers: FEEDBACK, A and B (for test-circuit adjustments); two rotary switches: TYPE SELECTOR and FUNCTION SELECTOR; slide POWER switch; momentary contact CANCEL button for I<sub>ceo</sub>; ten banana jacks: two for OHMS and DIODE tests, three for DC voltmeter, and one each for COMMON, MA, AF, RF-IF, and B<sub>2</sub> connection for tetrode transistors; two transistor sockets; three built-in test leads for transistors.

10. Size, Weight, and Price—10" x 7 3/4" x 4 1/2"; 4 1/2 lbs; \$86.50 AC-powered, \$74.50 battery-operated.


The Model 250A offers a number of functions in addition to its basic purpose of testing semiconductors. For example, it can be used as a harmonic generator for signal injection into RF, IF, or audio stages of radio receivers. To operate the unit in this fashion, it is necessary only to insert a good transistor in the test socket and adjust the instrument for a dynamic test of the transistor. When the transistor is oscillating in the test circuit, a pair of test leads plugged into the jacks on the panel will connect the oscillator signal to the set under test.

This signal-generator function is possible because of the manner in which the 250A tests transistors—by measuring their efficiency in an oscillatory circuit. With the feedback control set just high enough for oscillation, the transistor usually generates an approximate sine wave; this signal is excellent for audio tests. When the control is advanced further, the waveform begins to resemble a square wave, and is much richer in harmonics; this is the signal to use for RF and IF signal injection.

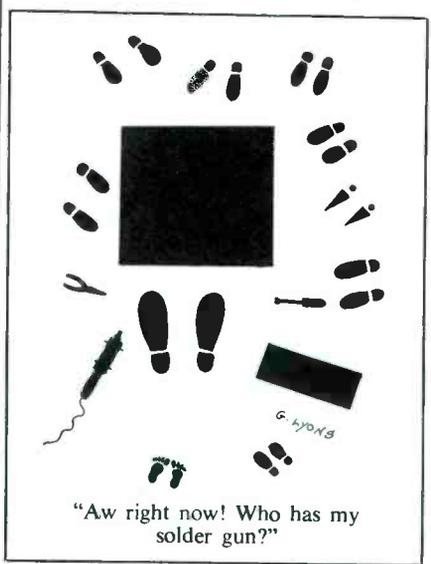Also included in the Model 250A are circuits for operating the unit as a VOM. Ranges are provided which will permit most or all of the measurements that must be made in the average tran-



"Aw right now! Who has my solder gun?"

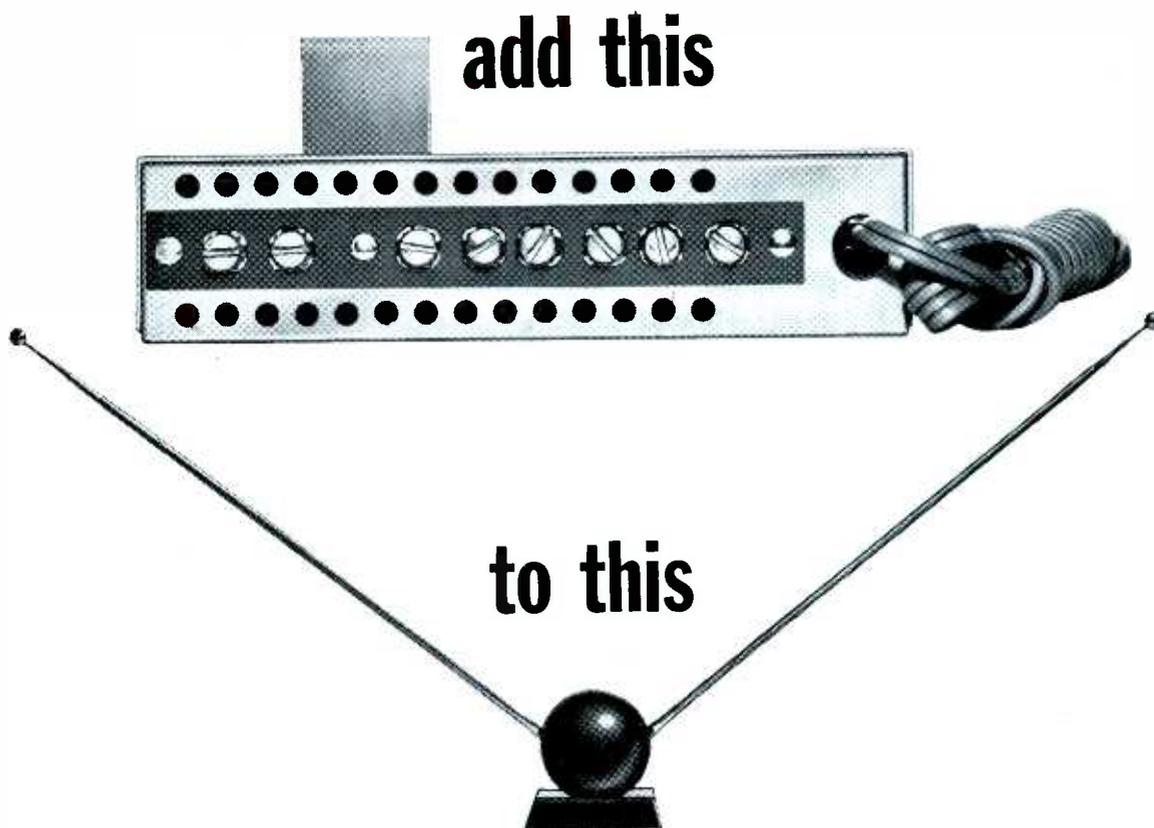

you'll be amazed at the improved performance

## BLONDER-TONGUE B-24c INDOOR BOOSTER

Some people think a booster is only for use with outdoor antennas. Not so. In many cases, the new Blonder-Tongue B-24c indoor TV FM booster produces a dramatic improvement in reception when used with an indoor antenna. Simply add it to any garden variety indoor antenna, and you get up to 12 db gain in signal strength—enough to turn your indoor antenna into a powerful antenna system. The Blonder-Tongue B-24c is easy to install anywhere in the home—patented, stripless screws eliminate the need to cut and twist twin lead. It can be used to amplify signals from any indoor or outdoor antenna. It's an excellent solution where your customers

can not or do not want to utilize an outdoor antenna. Hook up a B-24c and show your customers how much sharper and clearer it makes the picture. Tell them of the extra TV or FM sets they can operate from single indoor antennas—up to 4. You've got a profitable sale.

In very difficult reception areas an outdoor antenna is necessary because it delivers a better signal-to-noise ratio than an indoor antenna. In that case you still can use a B-24c indoor booster, or any one of the indoor or outdoor boosters in the Blonder-Tongue line. Blonder-Tongue boosters perform best. Try them today.

engineered and manufactured by

**BLONDER-TONGUE**  
9 Alling St., Newark, N. J.


Canadian Division: Benco Television Assoc., Ltd., Toronto, Ontario  
home TV accessories • closed circuit TV • community TV • UHF converters • master TV

Howard W. Sams 1962

**ONLY  
PUBLICATION  
OF ITS KIND!**
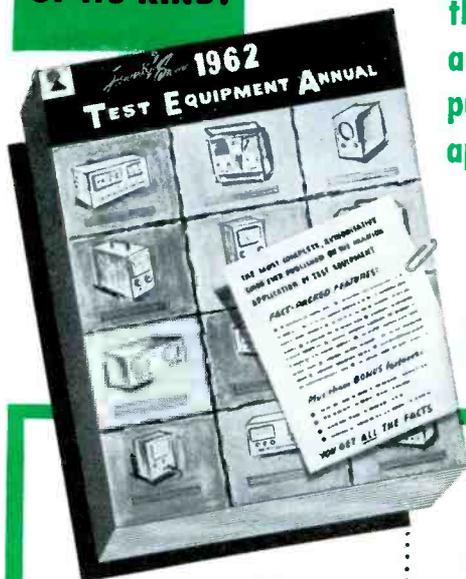
# Test Equipment Annual

the most complete,  
authoritative guide ever  
published on the practical  
application of test equipment



Only  
**\$1.50**

132 Pages  
Over 100 Illustrations  
the most useful, practical, time-saving information on test equipment ever to appear in a single volume!

## UNIQUE BUSINESS SECTION

Here's the money-saving information you need to help you buy and use test equipment to best advantage:

- Prorating Your Equipment for Tax Deductions
- When Should You Buy New Equipment
- Kit or Factory-Wired—How to Decide
- He Owns a TV Shop—On Wheels!

### SPECIAL! TEST EQUIPMENT BUYER'S GUIDE

Lists complete specifications for virtually every instrument available through parts distributors—especially planned to help you choose just the instruments you need in your work. Instruments are listed by category with informative tips preceding each group.

HERE'S YOUR TEST EQUIPMENT  
BUYING GUIDE IN ONE  
CONVENIENT VOLUME!

## FACT-PACKED FEATURES!

So easy to understand—here's the help you need to increase your servicing know-how... here are the latest techniques developed by the experts for your benefit.

### Partial List of Contents:

- How to Get More Mileage From Your VOM and VTVM
- How to Interpret Tube Tester Readings
- Using a Scope Effectively
- Circuit Analyzers Cut Troubleshooting Time
- Choosing Your Color TV Equipment
- Making Two-Way Transmitter Measurements
- Using Component Testers and Substitutors to Advantage
- The Versatility of Pulse Generators
- Using and Understanding Probes
- Radiation Detection and Measurements
- Transistor Testers—What They Do and How They Do It.

**DON'T MISS THE 1962 TEST EQUIPMENT ANNUAL**—it's packed with lab-proved test equipment information and latest servicing techniques to make your work easier, more profitable!

**ORDER YOUR COPY TODAY**

ONLY

**\$1.50**

**HOWARD W. SAMS & CO., INC.**

Order from your local parts distributor, or mail to Howard W. Sams & Co., Inc. Dept. 363  
1720 E. 38th St., Indianapolis 6, Ind.

Please send me \_\_\_\_\_ copy(ies) of "Test Equipment Annual"  
My (check) (money-order) for \$ \_\_\_\_\_ enclosed.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

(outside U.S.A. priced slightly higher)

## Bonus 16-PAGE BOOK SECTION

Gives you all the facts you need to take the guesswork out of using signal generators—written by Bob Middleton, the dean of test equipment authorities.

**YOU GET ALL THE FACTS!**

sistor receiver — volts, milliamps, and ohms.

An interesting feature of the Model 250A is the thoroughness of its transistor analysis. First, the suspected component can be checked—in or out of the circuit — for quality. If the in-circuit dynamic test is inconclusive for any reason, the transistor can be removed from its circuit and plugged into a test socket (or connected to the built-in clip leads). Next, the leakage between the collector and base (I<sub>cb0</sub>) is tested with the emitter open. The scales on the instrument reveal whether the leakage is abnormal for the type of transistor being analyzed (power or signal type). Then, the emitter-collector leakage (I<sub>ce0</sub>) is measured with the base "floating." Again, scales on the panel meter indicate if the reading is acceptable.

Lastly, DC beta — the gain of the transistor — can be measured. Before this reading is taken, a special arrangement permits adjusting the test circuit to "ignore" the I<sub>ce0</sub> of the transistor, which otherwise might upset an accurate beta evaluation. After the I<sub>ce0</sub> CANCEL control is adjusted, beta can be read directly from the meter scale.

In addition to the usual tests for transistors, forward and backward resistances between the various elements can be measured with the Model 250A, utilizing the ohmmeter section. The same test setup is used to check the forward and reverse current in signal and power diodes. Scales on the meter are labeled with normal readings.

Tunnel diodes have a very special characteristic, and require special testing techniques. When a very minute voltage is applied to a normal tunnel diode, current begins to flow. Many of them start conducting with only a few microvolts. Fig. 5 shows a graph of voltage versus current in a typical tunnel diode. As the applied voltage increases, the current rises proportionately—up to a point. The voltage soon reaches a value (known as the *peak* point—typically 55 to 65 mv) at which the current stops rising; as the voltage continues to increase beyond this point, the current begins dropping off. Finally, at a few hundred millivolts, the current decreases to a minimum, at what is called the *valley* point. As the voltage increases

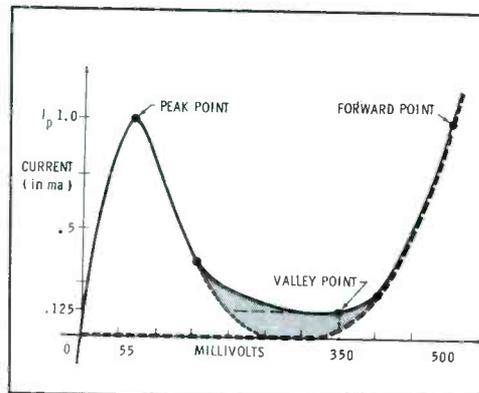


Fig. 5. E and I curve of tunnel diode.

# What's the difference in loudspeakers that makes Quam so special?

All loudspeakers look pretty much alike, and may even sound pretty much alike—yet Quam speakers are different—in a way that's very important to you who use them!

the  
difference  
lies  
in  
**PERFORMANCE  
RELIABILITY**

When it's a Quam speaker—you install it and forget it. Quam speakers are built to give long, trouble-free performance.

Quam's factory is a manufacturing plant, not merely an assembly shop. By making our own speaker parts, we can guarantee the quality of the materials that go into them. Our voice coils are centered precisely; each and every speaker is thoroughly tested; the product you get meets the standards we have insisted on for almost forty years.

Quam Quality Line speakers are enameled in gold—and while the color has no effect on performance characteristics, it symbolizes the quality and reliability that's built into every Quam speaker.

ASK FOR

# QUAM

**THE QUALITY LINE—  
for all your speaker needs**

QUAM-  
NICHOLS  
COMPANY

234 East Marquette Road  
Chicago 37, Illinois

# NEED TRANSFORMERS? YOU NAME IT . . . MERIT MAKES IT

- Power
  - Rectifier
  - Vibrator
  - Step-up, Step-down
  - Photo Flash
  - Isolation
  - Driver
  - Modulation
  - Audio Output
  - Vertical Output
  - Filter Choke
  - Tube to Line
  - Constant Voltage Line
  - Transistor
- . . . and others

# JOB CALL FOR COILS? YOU NAME IT . . . MERIT MAKES IT

Horizontal Output, Deflection Yoke, Width and Linearity, Antenna, Oscillator, Peaking, Interstage, Ratio Detector, Quadrature, IF Transformer

. . . and others

## SEE MERIT'S COMPLETE LINE OF QUALITY COMPONENTS IN THE NEW MERIT CATALOG AND REPLACEMENT GUIDE

Contains 19,492 easy to find manufacturer's part numbers to Merit equivalents. Merit's **exact replacements** mean fewer callbacks, ease of installation, plus **TOTAL SERVICE VERSATILITY**.

# YOU NAME IT . . . MERIT MAKES IT

# MERIT

## COIL AND TRANSFORMER CORPORATION

MERIT PLAZA

HOLLYWOOD, FLORIDA



Fig. 6. Cover converts to carrying case.

even further, the current again rises, eventually reaching a practical maximum—known as the *forward* point. Beyond this, the diode could be damaged. The forward-point current has the same value as the current at the peak point.

In the graph the peak point of 1 ma is reached at an applied voltage of 55 mv, the valley point of 125 ua is at 350 mv, and the forward point (again 1 ma) occurs at approximately 500 mv. The region where the current *decreases* with *increased* voltage — an apparent violation of Ohm's law — is known as the *negative resistance* region. This characteristic is important to the operation of tunnel diodes, and should be checked with the 250A.

Zener diodes can be checked on the Analyzer, too. The same test procedures that apply to tunnel diodes are used for testing zeners. The key to the tests is the voltage and current at which the zener *begins* to conduct; beyond that point, the current merely rises as the voltage increases.

The instruction manual included with the Analyzer gives detailed information about each test the unit performs. In addition, a chart of popular transistor types indicates normal gain readings and dissipation ratings. A chart of tunnel diodes lists test connections for a number of popular types, and indicates normal peak and valley currents.

The cover of the Model 250A is unusual. A condensed chart of test procedures is included on a card in the cover of the instrument. When folded back, the cover holds the procedure chart in view for easy reference; when in place — as shown in Fig. 6 — it forms a handgrip for carrying the unit. ▲

### now in our lab . . .

We're analyzing these test instruments for future "Notes" columns.

Electro Model EC-3 Power Supply  
G-C Model 36-590 CB Tester  
Hickok Model 725 Stereo Generator  
Heath Model IO-10 DC Scope  
Jackson Model 800 Color Generator  
Perma-Power Model 1A89  
Door-Opener Tester

# Find it and Fix it in 1/2 the time!

EASILY SOLVES "TOUGH DOGS"... INTERMITTENTS... ANY TV TROUBLE



MODEL  
1076

TELEVISION  
BLACK & WHITE AND COLOR

# ANALYST

**By Easy Point-to-Point Signal Injection, You see the Trouble on the TV Screen and Correct it—Twice as Fast and Easy!**


Simplified technique stops lost hours never recovered on "tough dogs", intermittents, and general TV troubleshooting. This one instrument, with its complete, accurate diagnosis, enables any serviceman to cut servicing time in half... service more TV sets in less time... satisfy more customers... and make more money.

With the Analyst, you inject your own TV signals at any time, at any point, while you watch the generated test pattern on the picture tube of the television set itself. This makes it quick and easy to isolate, pinpoint, and correct TV trouble in any stage throughout the video, audio, r.f., i.f., sync and sweep sections of black & white and color television sets—including intermittents. No external scope or waveform interpretation is needed. Checks any and all circuits—solves any performance problem. Gives you today's most valuable instrument in TV servicing—proved by thousands of professional servicemen everywhere.


Available on Budget Terms. As low as \$30.00 down.

Net, \$32995

## SIMPLIFIES COLOR TV SERVICING, TOO

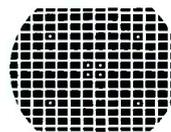

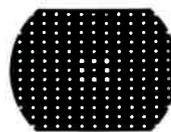Enables you to troubleshoot and signal trace color circuits in color TV sets, or facilitate installation.



Generates white dot, crosshatch and color bar patterns on the TV screen for color TV convergence adjustments.



Generates full color rainbow display and color bar pattern to test color sync circuits, check range of hue control, align color demodulators. Demonstrates to customers correct color values.

## Time-Saving, Money-Making Instruments Used by Professional Servicemen Everywhere



Model 960 Transistor Radio Analyst



Model 360 V O Matic Automatic VOM



Model 375 Dynamatic Automatic VTVM



Model 700 Dyna-Quik Tube Tester



Model 440 CRT Rejuvenator Tester

See Your B&K Distributor  
or Write for Catalog AP20-R



**B & K MANUFACTURING CO.**



Division of DYNASCAN CORPORATION

1801 W. BELLE PLAINE AVE. • CHICAGO 13, ILL.

Canada: Atlas Radio Corp., 50 Wingold, Toronto 19, Ont.

Export: Empire Exporters, 253 Broadway, New York 7, U.S.A.

# Keeping your Test Equipment MODERN

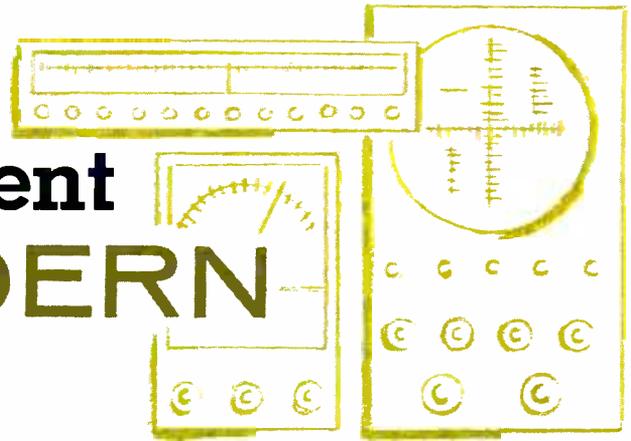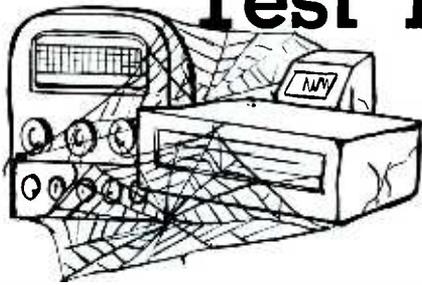

by Ernest Tricomi

A man walked into his psychiatrist's office. On his head was perched an owl. The owl spoke first. "Doc," it said, "how do I get this thing off my feet?"

Which illustrates very clearly that things are not always what they appear to be at first glance. Like the cost of test equipment. A good test instrument might carry a price tag that seems rather high to you; but when you consider how much time it can save you in the customer's home or at your service bench, it's easy to realize its cost is outweighed by the savings that result from doing jobs in less time.

Suppose you're called to a customer's home to repair a television set. Your minimum charge is \$5.00 for the first half-hour, and \$5.00 per hour thereafter. Now, if you had a little genie by your side to aid in diagnosis, pointing out a weak tube here, a leaky capacitor there, or a source of future trouble somewhere else, it might result in saving of a full ten minutes in the course of the call. If you make six or seven such calls a day, that extra ten minutes could easily amount to time enough for still another call that day!

The same idea applies in the shop. Suppose you pay your technicians \$2.40 per hour. If a man loses *only five minutes* of each hour, from lack of proper equipment, it can cost you a considerable amount—as shown in Table I.

## New Equipment—Which Types?

New test instruments are introduced every month. The trend is to combine three and four different functions in one instrument whenever it is practical. Multipurpose instruments save money on the

Table 1—Cost of Lost Time

No. of Men	Cost Per Day	Approximate Cost Per Year (240 days)
1	1.80	384.00
5	8.00	1920.00

original investment, as well as saving time in actual test procedures. Most of the new equipment is also portable so it can be carried into the customer's home or used at the service bench.

The test instruments you should have depends on what types of equipment you service. For example, if you service mostly transistor radios, you need a transistor tester more than you need a scope; and if you specialize in two-way gear, you'll find a frequency meter more helpful than a sweep-circuit analyzer.

Look over your present equipment. What modern features are missing in the instruments you have now? Can you think of other features which would make servicing faster and more convenient for you? When you've analyzed these factors, make a list of special functions you need in your work, and then decide which instruments should be replaced to fulfill these needs.

## How Much to Buy?

A shop owner could easily become test-equipment poor if he went out and bought everything that came down the pike. You need to decide how much of your total income you should reinvest in updating your test equipment, and then spend this money judiciously.

An average shop may have a total of about \$2500 invested in test equipment, according to a recent survey. If you consider obsolescence and use, four or five years is a good economic life for test equipment. This means you should spend \$500 or \$600 per year to keep modern, dependable instruments available. According to Table I, saving just five minutes of each working hour will result in a cash saving of more than half that amount. So, again you see it pays to have modern test equipment.

You can budget a portion of your total service income for test equipment purchases. The percent-


Table II—Test Equipment Budget

Investment in TE	On Eqpt. Per Yr.	Gross Income	Approx. Portion
2,500	500	7,500 10,000	7% 5%
	750	7,500 10,000	10% 7%
5,000	1,000	15,000 25,000	7% 4%
	1,500	15,000 25,000	10% 6%

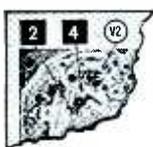
# why take hours to troubleshoot when PHOTOFACT® does it for you in minutes!

IF YOU'RE NOT NOW A PHOTOFACT LIBRARY OWNER, YOU'RE  
MORE THAN PAYING FOR IT IN THE TIME YOU LOSE


HERE ARE JUST A FEW OF THE DOZENS OF WAYS PHOTOFACT SAVES YOU TIME



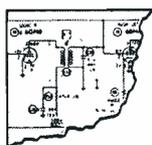**CircuitTrace®** saves countless hours of foil tracing time. This exclusive Sams system pin-points junctions and test points on schematic and printed board.



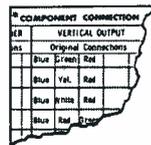
**Famous Standard Notation Schematic** saves valuable hours—always uniform, accurate, complete for every model.




**Exact Terminal Connections** are indicated—no need for trial-and-error methods—a real time-saving feature.



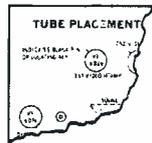
**Field Servicing Notes** spell out locations of adjustments for speedy "in home" servicing. Saves time spent in hunting for hidden adjustments.



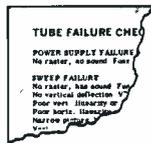
**Tube Location Guide** enables you to locate and replace proper tubes in seconds—a big time-saver on most repair jobs.



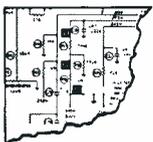**Tube Failure Check Charts** spell out probable tubes responsible for failure—no need to waste time studying circuitry.



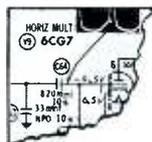**Clear Parts Symbols** with values and associated information are shown plainly on the schematic—no time wasted in cross-reference "look-up."



**Waveform** actual photos are shown on schematic for quick comparison of patterns on your scope. No time wasted in guesswork.



**Unique Alignment System** eliminates guessing; you get complete instructions with response curves, how to connect test equipment, proper adjustment sequence.




**Full Photo Coverage** of the actual equipment makes identification of all components and wiring easy—you can see everything.




**Terminal Identification** saves you time; transformer and coil terminals quickly identified by color code or basing diagram shown on schematic.



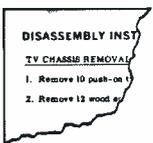
**Auto Radio Removal** instructions show you step-by-step procedure for removal of even the most complicated models—a big time-saver.



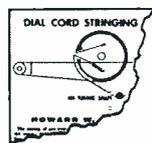**Disassembly Instructions**, step-by-step, help you remove difficult chassis, sub-chassis, and assemblies in minutes.



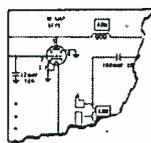**Dial Cord Stringing** instructions save you up to an hour or more of time and headaches on a single job.



**Alternate Tuner Data**—separate schematics, alignment data and parts lists are provided—no time wasted interpreting various tuner versions.

OWN THE TIME-SAVING, PROFIT-MAKING PHOTOFACT LIBRARY

FREE  
FILE  
CABINETS

THIS EASY-BUY WAY

The PHOTOFACT Library more than pays for itself from the first day you put it into your shop. It gives you instant time-saving help on more than 52,000 listings of TV, radio, hi-fi and other home-entertainment equipment—virtually any model made since 1946. You can own a PHOTOFACT Library this special Easy-Buy way:

- NO INTEREST
- NO CARRYING CHARGES
- ONLY \$10 DOWN
- UP TO 30 MONTHS TO PAY

You get FREE file cabinets with your PHOTOFACT Library—so you have all you need for time-saving, money-making service work right at your fingertips. Get the full PHOTOFACT Library details today.

You'll find dozens of other invaluable time-saving features in PHOTOFACT. Own the complete Library—so you can put your hands instantly on all the quick help you need for any job on your bench! Start a Standing Order Subscription today—keep up with current model output! See your Sams Distributor for full details or send coupon now.

SEND  
COUPON

HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc., Dept. 7-C3  
4300 W. 62nd St., Indianapolis 6, Indiana

- Send full information on Easy-Buy Plan  
 Enter my Photofact Standing Order Subscription

My Distributor is: \_\_\_\_\_

Shop Name \_\_\_\_\_

Attn. \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



**NEW-ATTRACTIVELY  
LOW PRICED**  
from  
*Swing-O-Lite*

**COMPLETELY ASSEMBLED BUT  
LESS EXPENSIVE THAN A KIT**

American ingenuity can beat foreign competition—and we give quality and service besides. Compare our prices with any similar lamp.

**INCANDESCENT  
ALL-PURPOSE LAMP**



- 45" Arm Reach
- All Metal Construction
- Air-Vented Shade

• Complete Flexibility  
... Yet Stays Put in  
Any Position

MODEL BB45C  
SUGGESTED RETAIL

**\$14<sup>50</sup>**

Less Bulb

Choice of P, C  
or W Mounts  
Colors: Brown,  
Tan, Grey

**FLUORESCENT  
MAGNIFIER-LAMP**



- 45" Arm Reach
- Complete Flexibility
- All Metal Construction


• 5" diameter Magnifying  
Glass Lens with a  
Powerful 13" Focus  
• Counter Balanced

MODEL BBM-9  
SUGGESTED RETAIL

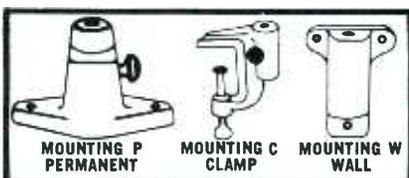**\$30<sup>75</sup>**

Less Bulb

Choice of P, C  
or W Mounts  
Colors: Brown,  
Tan, Grey



MOUNTING P  
PERMANENT

MOUNTING C  
CLAMP

MOUNTING W  
WALL

*Swing-O-Lite* INC.  
13 MOONACHIE ROAD HACKENSACK, N. J.

age will depend on your gross volume, and can be figured according to the chart in Table II. For example, suppose your investment in test equipment is \$2500, and its average useful life is five years. This means you should budget approximately \$500 each year for test-equipment replacement. Now, if your gross income from service labor is \$10,000, you will be laying aside about 5% of your gross income for keeping your test equipment modern.

**Depreciation Helps, Too**

Be sure to use whatever tax advantages result from the purchase of new equipment. The revision in depreciation methods made recently by the Internal Revenue Service is designed to encourage businessmen to spend money for modernization. Thus, it is now more attractive than ever to invest in up-to-date test equipment.

If you can prove to the satisfaction of your IRS office that any item of your test equipment becomes obsolete after only three years, you may depreciate one third of its value each year, for tax purposes. This can result in some very substantial tax savings, which will help pay for the cost of modernization.

**Finding Information**

To keep well informed of current trends in test-equipment design, you may want to look carefully through the pages of your trade magazines. For example, in this very issue you'll find several pages of fact-filled advertisements intended specifically to provide full information on the instruments being offered. Our regular test-

equipment features (such as *Notes on Test Equipment*) are written to help you "size up" each instrument or group of instruments, and determine which ones fit your requirements.

Another helpful source of information is literature from test equipment manufacturers and other sources. This information will point out the "what" and "where" of using test equipment profitably.

**Review Your Needs**

Sit down some quiet evening and look over your shop and equipment with the question in your mind, "What test instrument could have improved my time and accuracy in each recent job?" This will help you pinpoint the type of equipment you will find most useful. After you have selected the broad type of instrument you need, shop for it as carefully as you would for a new car or a new location. Keep in mind its utility, convenience, appearance, and quality, as well as its price. Your local electronic parts distributor can often help you considerably in making a wise choice.

The success of your service business depends on your skill in swiftly and surely diagnosing whatever ills may befall electronic products. The secret is no secret at all—it's the judicious choice and expert use of good, dependable test equipment. If you haven't already done so, review your test-equipment rack now and determine what you need to bring your own shop up to date in testing instruments. Next — plan carefully, along the lines pointed out in this article, how much money you should spend on keeping your equipment modern. Then, do it! ▲

**TV TUNERS** \* REBUILT OR EXCHANGED  
ALL TYPES

**\$9.95** including all parts and labor  
(except broken wafers—billed at cost)

- Normally shipped same day received
- 90 day full guarantee
- U/V combinations \$17.95

FREE—If Mailing carton sent to you on request

Phone REpublic 3-9189  
**L. A. TUNER EXCHANGE**  
4611 West Jefferson Blvd.  
Los Angeles 16, California

RCA—PIONEER OF COLOR TV—BRINGS YOU

ALL YOU  
NEED FOR

# COLOR-TV SERVICING



WR-64A



WO-91A



WR-69A



WR-70A



WR-99A

## RCA Color-Bar/Dot/ Crosshatch Generator

Low-cost, lightweight, portable instrument that provides all essential Color-TV test patterns. Simple to operate: only 3 controls. RF output leads connect directly to antenna terminals of receiver; no external sync leads required. Crystal-controlled signals assure rock-steady patterns, free from "jitter" and "crawl." Extra-wide-range chroma control. Generates:

- **Color-bar pattern:** ten bars of color, including R-Y, B-Y, G-Y, I and Q signals spaced at 30° phase intervals for checking phase and matrixing, and for automatic frequency and phase alignment. Permits accurate alignment of the "X" and "Z" demodulators which are used extensively in RCA Victor and many other makes of color TV receivers
- **Crosshatch pattern:** a grid-like pattern of thin sharp lines for adjusting vertical and horizontal linearity, raster size, and overscan
- **Dot pattern:** a pattern of small sized dots facilitating accurate color convergence adjustments

\$189.50\* with output cables.

## RCA 5-Inch Oscilloscope for Color-TV

A wideband scope excellent for checking colorburst signals and general troubleshooting of wideband color circuits and other electronic equipment. Multi-scale calibrated graph screen makes measurement of peak-to-peak voltage as easy as with a VTVM.

- New 2-stage sync separator assures stable horizontal sweep lock-in on composite TV signals
  - Dual bandwidth: 4.5 Mc at 0.053 volt rms/in. sensitivity. 1.5 Mc at 0.018 volt rms/in. sensitivity
  - Continuously adjustable sweep frequency range: 10 cps to 100 Kc
  - 3-to-1 voltage-calibrated, frequency-compensated step attenuator for "V" amplifier
  - Simplified, semi-automatic voltage calibration for simultaneous voltage measurement and wave-shape display
  - Vertical-polarity reversal switch for "upright" or "inverted" trace display
- \$249.50\*, including direct/low capacitance probe and cable, ground cable, and insulated clip.

## RCA Television FM Sweep Generator

Specifically designed for visual alignment and troubleshooting of color and black-and-white TV receivers, and FM receivers. The RCA WR-69A has pre-set switch positions for all VHF TV channels, FM broadcast band, and TV video, chrominance, and IF frequencies. The WR-69A has these important features:

- IF/Video output frequency continuously tunable from 50 Kc to 50 Mc
  - Sweep-frequency bandwidth continuously adjustable from 50 Kc to 20 Mc on IF/Video and FM; 12 Mc on TV channels
  - Output level—0.1 volt or more
  - Attenuation range: TV channels, 60 db IF/Video, 70 db FM, 60 db
  - Return-trace blanking
  - Two adjustable bias voltages on front panel
- \$295.00\* including all necessary cables.

## RCA RF/VF/IF Marker Adder

Designed for use with a marker generator (such as RCA's WR-99A) and a sweep generator (such as RCA's WR-69A), this instrument is used for RF, IF, and VF sweep alignment in both color and black-and-white TV receivers. In visual alignment techniques, it eliminates distortion of sweep response pattern. Important features:

- Choice of four different marker shapes provided by front panel switch for different types of sweep-response curves and for positive and negative sweep traces
- Provides very high-Q markers of high-amplitude and narrow bandwidth
- Complete front panel control of marker shape, marker amplitude, marker polarity, sweep amplitude, and sweep-trace polarity

\$74.50\* complete with cables.

## RCA Crystal-Calibrated Marker Generator

Supplies a fundamental frequency RF carrier of crystal accuracy for aligning and troubleshooting color and B&W TV receivers, FM receivers and other electronic equipment in the 19-260 Mc range. Combines functions of multiple-marker generator, re-broadcast transmitter, and heterodyne frequency meter.

- Highly stable output
  - May be calibrated at 240 separate crystal check points—accurate calibration provided at 1-Mc and 10-Mc intervals
  - Matched-impedance pad-type attenuator and double shielding of the oscillator provide effective attenuation of all frequencies
  - Most-used IF and RF frequencies are specially indicated on the dial scale
  - Sound and picture carrier markers available simultaneously
- \$242.50\* complete with output cable and phone tip.

RCA ELECTRON TUBE DIVISION, Harrison, N. J.




The Most Trusted Name in Electronics

\*User Price (Optional)




# TRANSCCEPTOR

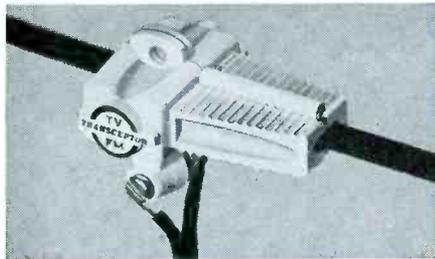


## THE ONLY INDUCTIVE SET COUPLER



slide apart

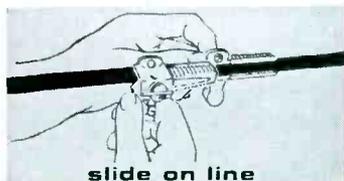

slide on line

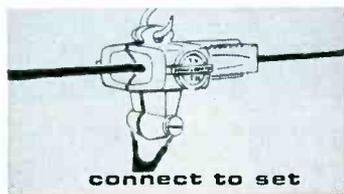

connect to set

## ANYONE CAN INSTALL IN SECONDS


Any number and combination of TV and FM sets can be run off one antenna with foolproof, simple, rugged TRANSCCEPTOR. Because it uses electromagnetic pickup, TRANSCCEPTOR simply snaps on main antenna line without tools, stripping, splicing or soldering. Line is not cut, signal loss is minimized, set-to-set isolation is improved (12 db).

Impedance is matched automatically. Uses standard 300-ohm flat line. Operates up to 20 sets without amplification in normal signal areas. Easy to sell, easy for customer to use, TRANSCCEPTOR is guaranteed for life of the set.

As an inexpensive impulse purchase, accessory sales builder, or give-away on larger purchases—you'll build sales and profits with TRANSCCEPTOR.

**AEROGAP CORPORATION**  
1880 VINE STREET HO 6-7385  
LOS ANGELES 28, CALIFORNIA

**\$2<sup>98</sup>** RETAIL

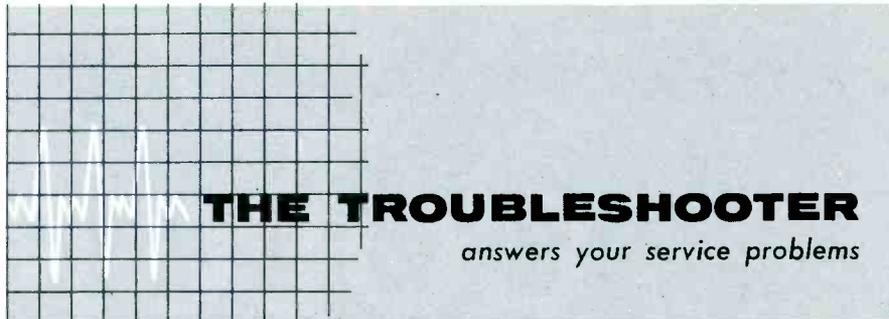

# THE TROUBLESHOOTER

answers your service problems

## Sweep-Alignment Touchup

In sweep alignment of video IF's, I have a difficult time figuring out how to position markers correctly on the scope trace during the final overall check. For instance, take the stagger-

tuned set I aligned today. All the various slugs seemed to peak normally, using a marker generator and VTVM; but when I checked the results with a scope, the 45.75-mc marker was too far down on one side of the curve. I thought it would be boosted higher by


## COLOR COUNTERMEASURES

Symptoms and service tips from actual shop experience

Chassis: Zenith 27KC20, 29JC20

Symptoms: Intermittent focus.

Tip: This trouble is generally caused by nothing more than misadjusted controls in the horizontal circuits—the horizontal efficiency coil and high-voltage potentiometer. The symptom will be further aggravated if the CRT controls happen to be set too high, so check them first and readjust if necessary; it's a good idea to keep the screen controls at the lowest possible level consistent with proper gray-scale tracking. Next, adjust the high voltage, output current, and regulator current as described in the service information. All these adjustments can usually be made without pulling the chassis.

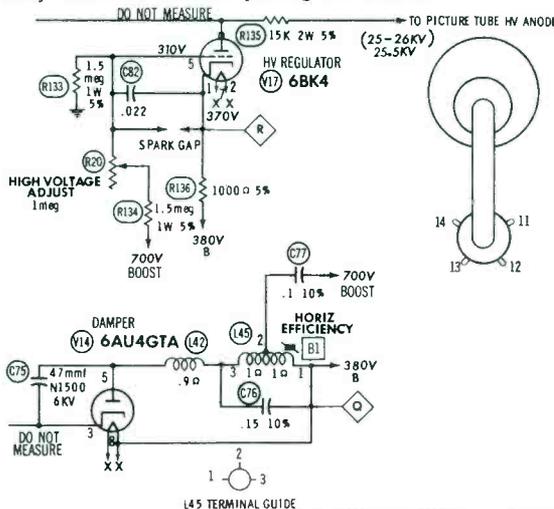

TUNER
RENU TUNER
TUNER

T. V.

# TUNER REPAIR

**\$6<sup>95</sup>** VHF or UHF

(U/V COMBINATION \$13.50)

**POSITIVELY NO EXTRAS**

MAIL ORDER ONLY

## RE-NU INC.


Compare the low price of this service... and remember that all work is performed by skilled technicians using equipment designed exclusively for tuner repair.

**ALL MAKES—\$6.95** for single tuner (\$13.50 for U/V combination) 6 months warranty.

Tuner must be complete and accompanied by all damaged parts. Give full details of complaint and channels used. Send with correct type, tested tubes. Remove all accessories; motors, brackets, knobs, etc.

Either prepay repair charge plus \$1.00 for return postage, insurance and handling on each unit; or request C.O.D. shipment at the repair charge plus \$1.50 each unit.

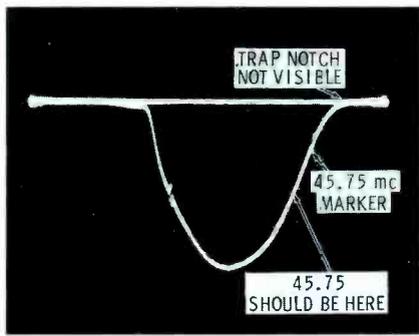**2403 W. Ardmore Ave.**  
**Chicago 45, Illinois**



adjustment of a coil tuned to 45.5 mc, but turning this slug only distorted the shape of the trace. By adjusting more than one slug, I finally obtained a fairly good curve.

I was also unable to make the 47.25-mc trap notch show up at first.

CARLTON G. MEANS

Troy, W.Va.

*You'll frequently find it necessary to readjust more than one coil during the final touchup, since there is a certain amount of interaction between the various IF tuned circuits. Even though all the coils seemed to peak normally, aging of a set can cause some peaks to become lower and broader than in a new set; therefore, you may find it necessary to take steps such as you describe.*

*The initial step-by-step adjustments occasionally result in a curve which has the correct shape, but which is shifted in frequency so that none of the markers fall at the proper points. This doesn't happen often; but if it does, here's a remedy: Using an accurate marker as a reference, "move" the entire curve under it (by slightly turning every coil in the same direction) until the marker rests at the desired point.*

*When the curve winds up distorted, as you describe, try turning each slug slightly and noting which portion of the curve is most affected. By thus locating the coil that must be tuned for each specific change, you can generally "shape up" the response curve with a minimum of "twiddling."*

### On the Level

I can't measure DC voltages accurately with my direct-coupled scope (an EICO Model 460), although the waveform displays seem to be okay. At a point where I measure, say, 200 volts with a VTVM, the DC scope indicates only 110 volts—judging from the change in position of the trace on the calibrated scope screen. I've rechecked the calibration, and have checked all tubes, voltages, and resistances, but nothing seems to help.

CHARLES BEY

Richmond, Va.

*Your scope's calibrating waveform may be in error. In the Model 460, this is a 60-cps sine-wave signal (0.4 volt peak to*

## NEWEST RCA SENIOR VOLTOHMYST® NOW AVAILABLE AS A KIT FOR ONLY \$57.95\*

### NEW!

0.5-volt full-scale DC range for more accurate measurements of low voltages used in transistor circuits.

### EXTRA!

Pre-assembled, factory tested probe (WG-299D) is included with every kit.

**SAVE MONEY** with this kit version of the RCA WV-98C, the newest improved model of the popular RCA SENIOR VOLTOHMYST. Even with its added features for extra versatility, this new kit still costs less than prior models.

This rugged precision instrument measures **AC voltages** (0.2 to 4200 volts peak-to-peak and 0.1 to 1500 volts rms); **DC voltages** (0.005 to 1500

volts DC); and **resistances** (0.2 ohms to 1000 megohms). Accurate to  $\pm 3\%$  full-scale on both AC and DC ( $\pm 5\%$  on the 1.5 and 5-volt AC ranges). Less than 1% tracking error.

Scales are separately color-coded to differentiate peak-to-peak and rms voltage readings. Its big meter, 6½ inches wide—electronically protected against burnout—is one of the most readable ever designed into a VTVM.

### RCA WV-98C

**\$57.95\***  
KIT

**\$79.50\***  
WIRED

For more information, ask your Authorized RCA Test Equipment Distributor.

\*User Price (Optional)

RCA ELECTRON TUBE DIVISION, HARRISON, N. J.



THE MOST TRUSTED NAME IN ELECTRONICS

IT PAYS TO USE AEROVOX!

First-rate quality just doesn't happen by chance... you have to work at it. This is just as true in the design and manufacture of capacitors as it is in radio-TV-electronics servicing. You know from experience that you simply cannot expect repeat business unless you have built up a reputation based on dependability and honest service. If you're particular about your service and your profits... be particular about the capacitors you use. Take ceramic capacitors, for example. Aerovox offers you a complete line of rugged, dependable and proven top-quality ceramic capacitors in every case style for your every replacement need. See your Aerovox Distributor for a wide selection of disk types for by-pass coupling, general purpose, hi-voltage and temperature compensating applications. Yes, he stocks cartwheels, standoffs and feedthrus in all sizes and values, too. And for real "plus" profits be sure to ask your Aerovox Distributor about disk ceramic kits AK-200 and AK-201HS. Remember, it pays to use Aerovox!



TUBULAR



FEED-THRU



STAND-OFF




HI-VOLTAGE  
CARTWHEELS



PLATE  
ASSEMBLIES




KITS

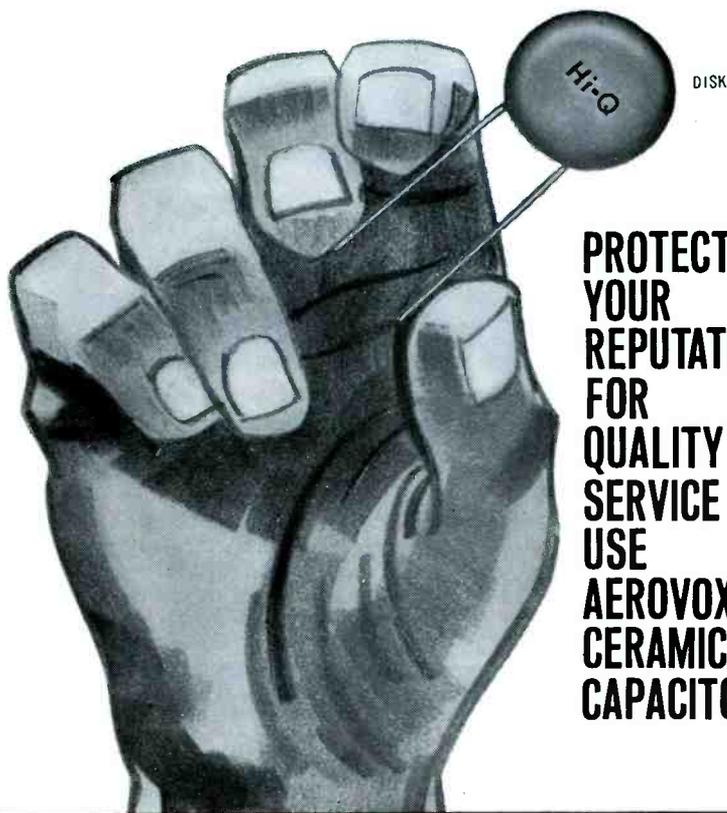

**PROTECT  
YOUR  
REPUTATION  
FOR  
QUALITY  
SERVICE...  
USE  
AEROVOX  
CERAMIC  
CAPACITORS**



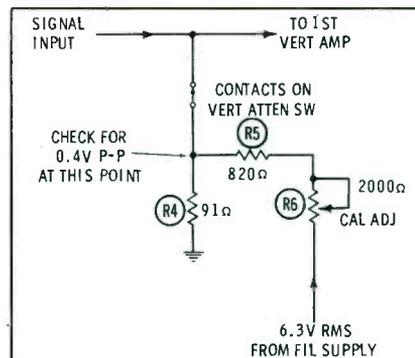**AEROVOX CORPORATION**  
DISTRIBUTOR DIVISION, NEW BEDFORD, MASS.  
Technical Leadership—Manufacturing Excellence



peak) which is injected into the vertical amplifier when the vertical attenuator is switched to the CAL position. (Calibration is accomplished by adjusting the vertical-gain vernier control so the waveform extends 4 divisions on the screen scale, thus making each division equal to 0.1 volt on the x1 position of the vertical attenuator.) The calibrating signal passes through all stages of the vertical amplifier, except the input attenuator network; therefore, it would be affected just the same as any other signal if there were trouble in the amplifier, and calibration should not be upset.

Since the entire amplifier (three push-pull stages) is DC-coupled, the amount of vertical deflection caused by a DC voltage shift should be the same as for an equivalent swing of instantaneous AC voltage. Therefore, any trouble that might cause nonlinear response to different amounts of DC-voltage change would also cause waveform distortion. If all DC voltages read too low, the calibrating signal is probably too strong. On the schematic, note that it is derived from the filament voltage via R4, R5, and R6. Check the voltage at the junction of R4 and R5 with a sensitive VTVM that gives peak-to-peak AC readings. If the voltage is more than 0.4 volt peak to peak, try resetting R6; if this fails to solve the problem, carefully check the values of R4 and R5.

If the trouble is not in the calibrating-voltage source, the next most likely spot is the vertical input attenuator. To help in isolating a fault here, check to see if the incorrect readings occur on all attenuator-switch settings, or on only one or two ranges.

#### Blister on the Trace

I have a kit-type scope which operates normally except that a small area on the trace bulges upward. This spot is about 1/2" wide, and rises about 1/16" above the normal trace level. It appears once, near the center of the screen, when the sweep controls are set for 60 cps; at higher sweep frequencies, several of the bulges are seen. The symptom is unaffected by shorting either the vertical or horizontal input terminal to ground, or by switching to 60-cps line sweep. When I apply the calibrating signal from the front-panel test jack to the vertical input, the "bump" slightly

distorts the calibrating waveform, which is normally sinusoidal.

JAMES B. CORUM

Upham, N. Dak.

Since the symptom is a vertical deflection of the CRT trace line, it's most logical to look first in the vertical amplifier for the cause. The action of the sweep controls is positive proof you're dealing with a 60-cps interfering signal of some sort, probably hum or a "glitch" from the power supply.

Try substituting all tubes in the vertical-amplifier section, since one of them may have heater-cathode leakage. If this doesn't help, attempt to isolate the trouble by grounding the grid of each tube in turn. (Do this only briefly, to protect the circuits in case the grid normally runs at a high positive potential.) If the "blister" disappears, the interference is being introduced somewhere prior to the point being checked. Be sure all wiring is dressed exactly as specified, especially near the input circuits.

It's remotely possible that trouble within the CRT itself could cause this form of base-line distortion; so, if all else fails, try a new 5U1.

### Meter Protection

I recently burned out the movement of my 20,000-ohms-per-volt VOM. When I replace it, I'd like to put a fuse in series with the new movement. What would be the proper size to use?


While I'm working on the meter, I would also like to bring two leads out from the movement to an extra set of jacks, so the sensitive movement may be used with other pieces of equipment around the shop. Would this harm the calibration of the meter?

JOHN DAVIS

Brooklyn, N.Y.

A good rule of thumb for calculating a suitable fuse rating is to multiply by ten the current needed to drive the meter to full scale. Most meter movements are rugged enough to survive a considerably higher overload than ten times the rated full-scale current. I've actually seen some meter movements of 50-microampere sensitivity being protected by a 1/200-amp instrument fuse; in this case, the fuse won't blow until the overload amounts to a hundred times the normal full-scale current.

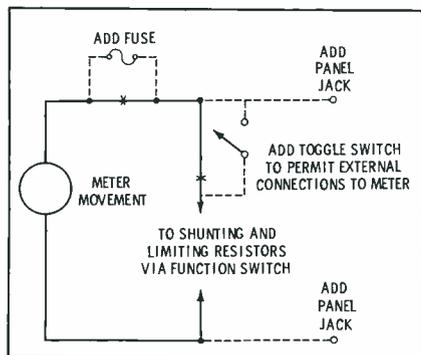Using the meter movement with other equipment will not harm the calibration,



# Checklist for buying a full-power CB 2-way radio

look for these features:

**TRANSMITTER POWER** — For longest transmission range possible, choose a 5 watt unit, the maximum authorized power input for Class D CB radios.

**SENSITIVITY** — A greater sensitivity rating indicates a better ability to reproduce weak signals. Look for a sensitivity rating below 1 microvolt to capture signals transmitted many miles away.

**SELECTIVITY** — A radio's ability to reject interference from channels not tuned in, is largely determined by the type of circuit used: superregenerative, superheterodyne or dual-conversion superheterodyne. The latter circuit, the dual-conversion superheterodyne, is acknowledged by experts to be the best circuitry for clearest reception. Says Len Buckwalter, noted communications author, in *Electronics Illustrated* May 1962. "... Look for the dual-conversion feature if you wish to get top receiver performance."

**CRYSTAL-CONTROLLED CHANNELS** — Fixed crystal controls assure accurate, fast communications contact. They enable users to switch quickly from one channel to another to contact different persons, to find a channel that isn't busy. It is best to choose a CB unit with multiple crystal-controlled channels for an efficient, flexible 2-way radio system.

**POWER SUPPLY** — A power supply should be an integrated part of a CB radio. Since full-power CB radios are most often used in vehicles and base stations, a CB radio's power supply should be able

to operate from both 12-volt auto battery and 110-volt AC line.

**AUTOMATIC SQUELCH** — This automatically eliminates annoying background noise when a CB radio is on 'standby' (not transmitting and ready to receive any radio calls). Thus, hisses, crackles and other noises can't distract workers, drivers, etc.

**AUTOMATIC NOISE LIMITER** — An effective automatic noise limiter is necessary, especially in heavily populated areas, to shut out extraneous interferences such as ignition noise. Makes messages more intelligible.

**RELIABILITY** — CB radios must withstand vibration and shock which occurs during mobile use. Solid-state components—transistors and diodes—are less susceptible to damage than fragile tubes.

**PORTABILITY** — Some full-power CB radios may be used in the field as portable units when equipped with a portable case-battery accessory. These units are generally lightweight, compactly designed and offer greater operating flexibility.

**INSTALLATION** — Compact CB radios with simple mounting provisions don't steal leg room in vehicles, lower installation and maintenance costs.

Cadre Industries has two 5-watt models that rate high in every category. Each is supplied with a press-to-talk microphone, set of matched channel crystals, universal mounting bracket and AC & DC cords.



### Cadre '510'

All-Transistor, 5-Watt, 5-Channel, plus all-channel manual Tuner, \$209.95



### Cadre '515'

All-Transistor, 5-Watt, 5-Channel, \$194.50

See your Cadre distributor for a demonstration, or for more details, write:  
**CADRE INDUSTRIES CORP.** □ COMMERCIAL PRODUCTS DIVISION □ ENDICOTT, NEW YORK □ AREA CODE 607, 748-3373  
 Canada: Tri-Tel Assoc., Ltd., 81 Sheppard Ave. West, Willowdale, Ont. Export: Morhan Exporting Corp., 485 Broadway, New York 13, N. Y.

# What's A Marker Adder?

This is a question heard often these days. Marker adders are growing in popularity, but a number of servicemen still don't understand them.

A marker adder is an instrument that will add a marker signal to a sweep-alignment response curve without distorting the curve. More than that: It can develop a marker as large or as small as is desired, can place that marker anywhere on the curve (even in deep trap notches), and will not affect the shape of the alignment curve at all. It does this by the simple expedient of adding the marker after the sweep curve is developed on the scope screen. Let's see how it is done.


The figures show two ways of marking the sweep alignment curve. In the method that omits the marker adder, the marker and sweep generators are connected to send the signals into the receiver simultaneously. The marker signal is mixed with the sweep signal in the receiver circuits. If a fairly strong marker is desired—especially in checking the frequency of trap notches—the marker-generator output must be increased, often resulting in overloading of the receiver circuits and severe distortion of the response curve seen on the scope screen.

When the marker adder is used, only the sweep-generator signal is fed to the receiver;

thus, it can be adjusted to avoid overloading. The receiver response curve is not fed directly to the scope; it is sent, instead, into the marker adder. Meanwhile, a sample of the sweep-generator signal is fed into the marker adder, and there mixed with the marker-generator signal. Since the sweep-signal sample is the same as that being fed to the receiver, the sample signal—with the marker now added—can be superimposed on the response curve coming from the receiver. Both signals are applied to the scope in the normal manner, resulting in a scope display that resembles the usual curve.

The marker size can be controlled by adjusting the amount of signal fed in from the marker generator, but the shape of the response curve is totally unaffected because the marker signal doesn't even enter the receiver. Special circuits in the marker adder allow you to set the width of the marker, as well as its height, making it more visible on the "skirts" of a response curve.

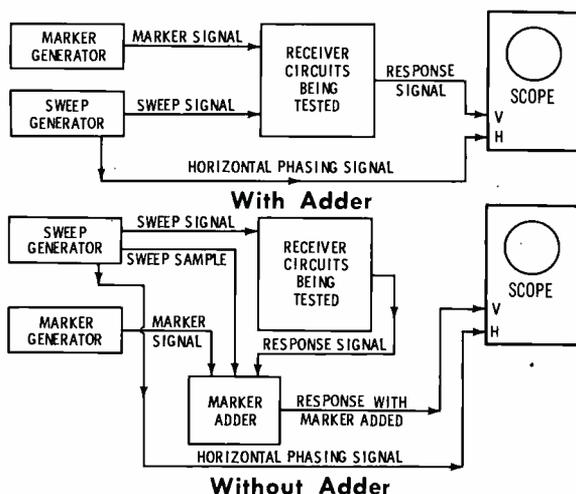In a few recent sweep generators, a marker-adder circuit is built right into the instrument. This arrangement operates in the same manner, except fewer connections are required. In either form, a marker adder is a very helpful instrument on the alignment bench.



provided the movement is not connected to more than one circuit at a time. Be sure to wire the fuse between the jacks and the movement.

## Chroma Sweep

I'm looking for a TV alignment generator with which I can perform a complete video and chroma alignment of a color TV set. Will any instrument do the job, or must it be a special type?

CARR TV

South Boston, Mass.

Any good-quality alignment generator can be used for adjusting the RF, video IF, and sound IF stages in a color receiver. However, chroma-bandpass alignment, as pointed out in the recent article "Color Alignment Setups" (June, 1962), requires a sweep generator that will reach well below 3 mc. The minimum center frequency can be higher than 3 mc, if the sweep width is sufficient to cover the desired range. For example, a 4-mc center frequency, with a sweep width of at least 3 mc on each side, will actually result in a signal reaching from 1 mc to 7 mc. Generally speaking, such signals are obtainable with mechanically-swept instruments; but the electronic-sweep types seldom develop sufficient sweep width at low center frequencies.


## Ohms Up


I have a problem with my VTVM (schematic enclosed), and hope you can help me with it. The instrument works perfectly except that all ohmmeter readings are 10% high. I've checked the battery, the resistances, the tube, and the test leads; and they all seem okay to me. Can you suggest a remedy?

ROBERT C. MILLER

Bethlehem, Conn.

Since the unit works normally on AC and DC voltmeter readings, the meter movement must be satisfactory; therefore, you must decide which ohmmeter components could affect all resistance readings. Try sketching just the ohmmeter section (the special 8-page Book Section in the front of this issue tells you how), and you'll see that R11 and the OHMS ADJUST control are the only components common to every ohmmeter range. Chances are that R11 has increased in value. Be sure to use a replacement with a value tolerance of 1%, to insure accuracy.

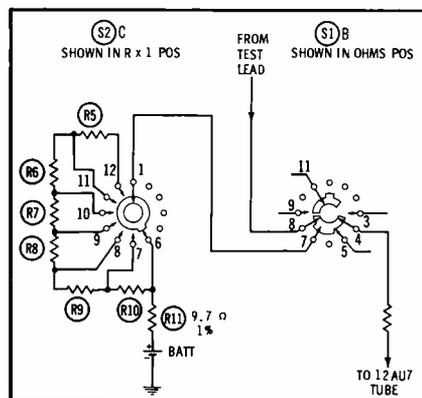

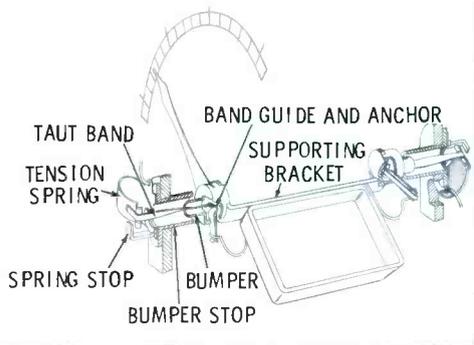

**Fig. 5.** Taut-band suspension is used in many industrial meter movements.

which can be converted to an electrical signal may be displayed by a strip chart or graphic recorder. These recording instruments employ a pen which is fastened to a movement similar to that used in a standard meter. The pen is held against a chart or graph which either rotates or moves from a roll. As the chart moves, variations in the electrical input signal to the recorder cause the pen stylus to move or vibrate, drawing a graph of the signal on the chart.

Graphic recorders are also utilized to compare one variable function with another: For example, to indicate stress versus strain, speed versus torque, temperature versus pressure, response of an antenna versus rotation, etc. These instruments are sometimes used as a control element, automatically initiating action to return a system to its normal operating conditions in case an input exceeds or falls below a required value. In these applications, the instrument is known as a recorder-controller. A front panel view of a recorder-controller, with a circular chart, is shown in Fig. 6.


A variety of accessories make graphic recorders adaptable to



# Coming in the APRIL Issue
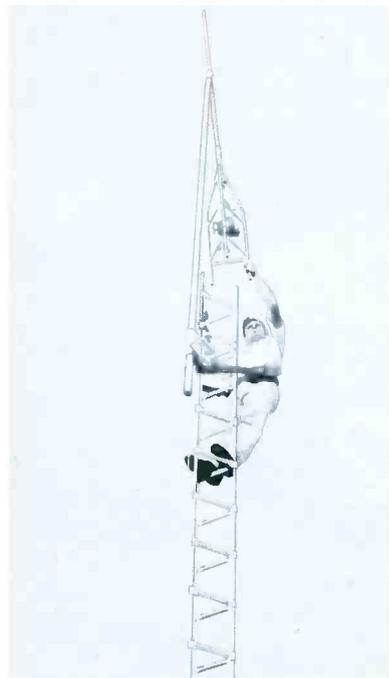
## Special Antenna Section:

- ★ **Spotting Antenna Failures Quickly**  
Sure-fire methods make servicing a snap!
- ★ **Sizing Up Antennas**  
How modern designs increase their effectiveness.
- ★ **Installing Communications Antennas**  
Plans and practices to prevent problems.
- ★ **How to Strip and Solder Cables**  
Actual photos of the correct techniques.



Plus Plenty of Other Servicing Features . . .

- Know Your '63 Color Circuits (Sweep and HV Systems)
- Symfact—Covering Full-Wave Silicon Doublers
- Radar Maintenance Is Easy
- Stock Guide for TV Tubes
- Troubleshooter

and more!

### Get Free Premium Books With Subscription

Enter my subscription to PF REPORTER and send me free book(s) checked.

3 Years \$9.00     2 Years \$7.00     1 Year \$4.00

The Troubleshooter's Handbook  
 Servicing Industrial Electronics  
 Servicing TV from Tuner to Picture Tube } Check one for each year you subscribe

Bill Me     Remittance Enclosed     Extend Present Subscription

Take this coupon to your distributor, or mail to:

**Howard W. Sams & Co., Inc.**

4300 W. 62nd St., Indianapolis 6, Ind.

Name \_\_\_\_\_

Firm \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Please Check Your Business Classification

- Independent Radio, TV Serviceman
- Owner, Mgr.
- Retailer with Service Department
- Service Mgr.
- Industrial Electronics Service
- Employee
- Other (Specify occupation and title)



**1**  
Genuine, fresh Little Devil® resistors (on "Tally Tape" or in Cabinet Assortments)



**2**  
**3 WAYS TO MAKE SURE IT STAYS FIXED**

You're always safe, always sure with any of these three quality replacements. Why be otherwise? Repair jobs that boomerang cost you hard-earned profit. Little Devil® resistors come in 1/10, 1/4, 1/2, 1, and 2 watts from 2.7 ohms to 22 Megs . . . AB Pots from 50 ohms to 5 Megs in several shaft lengths and styles . . . gold-bonded diodes in ninety 1N types off the shelf.

Call your distributor for the latest Ohmite Stock Catalog 30.

Be right with


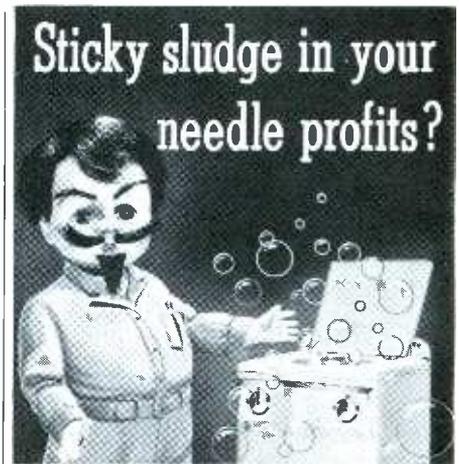


**Fig. 6.** Recorder-controller both indicates and corrects system deviations.

many uses. For example: linear amplifiers permit recording of very low-level signals; special transducers convert physical phenomena to electrical signals; and servo amplifiers are used to supply a feedback signal to control a manufacturing process.
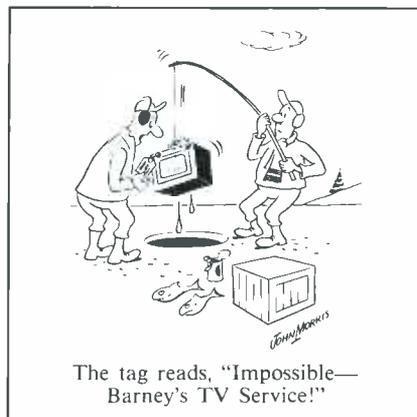
### Electronic Quality Control

As the trend in U.S. industry continues toward automated production, the need increases for rapid means of testing, monitoring, or controlling the quality of products being produced or processed. This need has brought about a variety of electronic devices to aid inspection and control people in keeping up with faster production rates. Some of these devices test finished items on either a regular or random sampling basis, with no feedback or error signal returning to control the manufacturing processes. Other test and monitoring devices act automatically, when a flaw or drop-off in quality is detected, to control the production tolerances. In many cases, the necessary corrections are made before even a single item reaches a beyond-tolerance state. In other systems, defective items are automati-



## USE DUOTONE FOR FAST SUCCESS

Needle replacement problems go down the drain when you use Duotone needles. Genuine diamond, synthetic sapphire and osmium tipped. No phonograph can be considered completely serviced if its worn needle is not replaced. Most of your customers don't know that worn needles ruin their records. Tell them. Remember Duotone is a name they know and trust.



You'll be bubbling with increased sales.

**DUOTONE**  
COMPANY, INC. KEYPORT, N.J.

**PROFESSIONAL technicians**

use *Dave Rice's*

**OFFICIAL ORDER BOOKS**

for every **TV-RADIO service** call

This is the businesslike approach to service record keeping. TriPLICATE forms serve as order form, invoice and office record, with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10. In stock at your distributor.

\*\*\*\*

**FREE**

Write for your free folder describing Dave Rice's OFFICIAL ORDER BOOKS, including an actual size sample copy of the handy order form.



**ELECTRONIC PUBLISHING CO., INC.**  
133 N. JEFFERSON ST.  
CHICAGO 6, ILLINOIS

cally rejected as the production process, fully corrected, continues at full capacity.

**Robotester**

Shown in Fig. 7 is a device capable of performing a great variety of automatic troubleshooting or testing functions, either in the production and assembly of components and equipment, or in preventive and corrective maintenance. It's called a *Robotester*.

The basic *Robotester* can perform up to 20 separate circuit tests through sockets on the side panel, at a rate exceeding 60 per minute. The device is adaptable to many types of tests. For example, it can test or measure voltage, current, resistance, inductance, capacitance, frequency, impedance, temperature, and flow rate. The *Robotester's* testing sequence is set up on a punched or perforated tape. For each test, the instrument can indicate acceptance, rejection, or deviation from a required standard. When a rejection occurs, an alarm may signal an attendant who can remove or correct the rejected item.

Optional or accessory units for the *Robotester* include a unit known as a *Robotroller* which will insert a variety of additional test conditions. One or more multiplier units, added to the *Robotester*, can increase the possible tests to 1000 or more. Automatic printers are another optional addition; such printers can automatically record all the data provided by the *Robotester*, permitting later analysis of passed

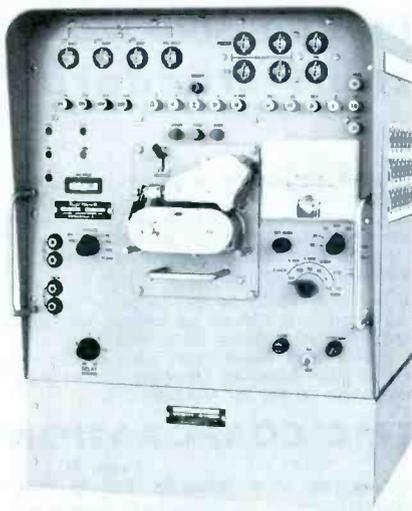


Fig. 7. *Robotester* automatically performs tests programmed on a tape.

**Mercury** offers you the **GREATEST VALUE**  
in **TUBE TESTERS**

**TOP QUALITY • SPEED • ACCURACY • LOW PRICES**  
*...sell more tubes—earn more money*

a true **DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER**  
for only **\$79.95** Net



**Model 1000**  
**MUTUAL CONDUCTANCE TUBE TESTER**

- Tests for true dynamic mutual conductance (Gm)
- Tests for shorts and leakage between any tube elements
- Tests for gas and grid emission ... sensitivity over 100 megohms
- Tests picture tubes

Here, for the first time is a true dynamic mutual conductance tube tester to sell for less than a hundred dollars... in fact it bears a price tag of only \$79.95... truly, one of the greatest values in test equipment to come your way in a long time.

Size: 14x9½x4¾"

**Model 1100 TUBE TESTER**  
*... an outstanding tester—yet amazingly low in price!*



- Tests for shorts and leakage
- Tests for dynamic cathode emission
- Tests for grid leakage
- Tests for gas content

**\$39.50** Net Size: only 10¼x8¼x3¼"

Here is the answer to technicians who seek a dependable, professional performing tube tester at a minimum cost. The Model 1100 has a range of operation that will outperform many, more expensive testers. It boasts an exclusive meter bridge circuit, found only in more expensive testers. Conveniently compact in size—a whale of a money-maker.

**ALL MERCURY Tube Testers have these features:**

- Also test the new tube types including Novars, Nuvistors, Compactrons, new 10-pin tubes as well as battery type tubes, auto radio hybrid tubes, voltage regulators, foreign and hi-fi tubes, thyratrons and most industrial tube types.
- Check each section of multi-section tubes separately
- Handsome, two-tone long lasting etched aluminum panel
- Housed in sturdy carrying case with handsome leatherette finish.

**Model 1200**  
**MUTUAL CONDUCTANCE TUBE TESTER**

- Tests for true dynamic mutual conductance (Gm)
- Tests for shorts and leakage between any tube elements
- Tests for gas and grid emission ... sensitivity over 100 megohms

**\$119.95** Net

Here is a deluxe dynamic mutual conductance tube tester with a unique push-button set-up method that can be compared with the ease of selecting a record on a juke box. Push buttons provide complete flexibility in accommodating all present and new tube types and basing arrangements. The Model 1200 is the most versatile tube tester available today.

**Deluxe**  
**Dynamic Mutual Conductance Tube Tester with FAST PUSH BUTTON SETTINGS**



**TREMENDOUS VALUE!**

- Also tests black and white and color picture tubes.
- Also tests transistors.
- Also tests batteries under load

Size: 18¼x10¾x4¾"

See your electronics parts distributor or write for complete Mercury catalog

**Mercury** **ELECTRONICS CORPORATION**  
manufacturers of quality electronic products

111 Roosevelt Avenue, Mineola, New York

EXPORT: EMEC Inc., 127 Grace St., Plainview, N. Y.

and rejected items.

### Digital Data Logger

A simplified block diagram of a typical data-logging system is shown in Fig. 8. The data logger can automatically make and record two measurements per second in automatic testing of devices such as missiles, and in reliability and quality-control work. In this system, several inputs (such as voltage and resistance) are sequentially scanned and measured. In addition, their values are displayed on digital indicating instruments and, at the same time, recorded for a permanent record. The input channels are connected to the input scanner, which is a transistorized unit consisting essentially of selector switches. Up to 100 channels are scanned automatically and transferred to the indicating instrument and the data printer and recorder. The scanner also displays the input-channel number while supplying this number to the data recorder which prints it alongside the data for that channel. From the digital-data recording system, an "end-of-recording" signal tells the input

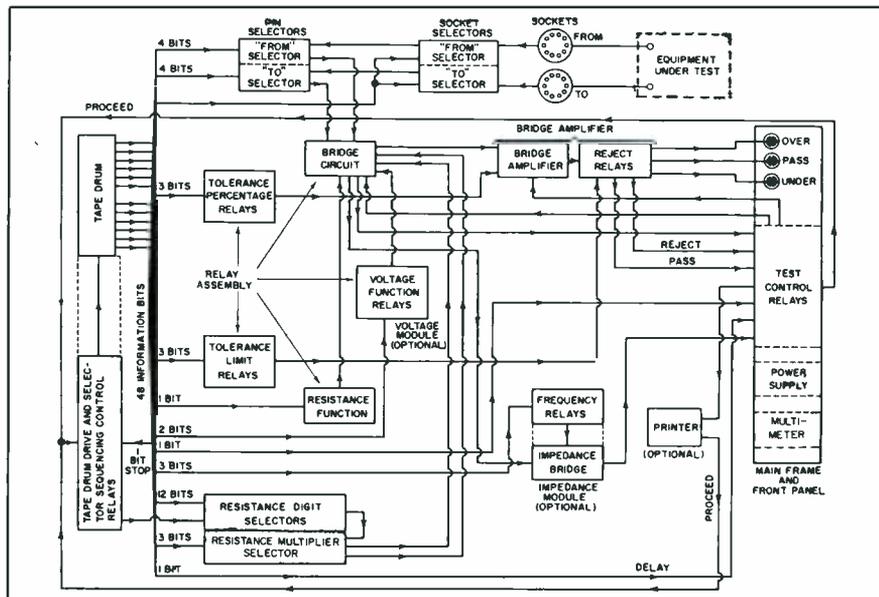


Fig. 8. Data-logging system automatically makes and records measurements.

scanner when to step to the next input.

### Conclusion

If some special testing function is needed by an electronic system in industry, rest assured there is some instrument that can do it—with production-line speed and efficiency. The variety of special instruments in industrial electronics

seems almost endless, and their complexity is sometimes great enough that special test equipment is required to service them. However, any electronics technician working alone in industry generally handles only a small number of different types of instruments; thus, he can become as familiar with them as with service scopes and generators. ▲

**ARE YOU CASHING-IN ON THE PROFITABLE 2-WAY RADIO SERVICE BUSINESS?**

- ★ Motorola will train you for this rewarding, elite profession
- ★ Send for our FREE EVALUATION EXAM. Prove to yourself that you are ready to learn FM 2-way radio servicing.

Opportunities in 2-way radio servicing are virtually unlimited. Just one of the hundreds of successful Motorola Service Stations writes, "we would be pleased to interview any graduate of your school that has received some training in 2-way radio maintenance. We are an established firm, 10 years old, with a promise of expansion governed by our ability to obtain competent technicians." Get all the facts today. There is no obligation and no salesman will call.

**MOTOROLA TRAINING INSTITUTE**  
4545 West Augusta Blvd. • Chicago 51, Illinois • Dept. ACX39

Send me FREE entrance exam.  
 Send full details on Home Study Course on FM 2-way Radio Servicing  
 Send me details on how you can help me prepare for an FCC License.

Name \_\_\_\_\_ Occupation \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**Acme Electric**  
**VOLTAGE ADJUSTORS**

**a quick, inexpensive way to correct off-standard voltage**

TV sets, hi-fi's and other electronic equipment operate best when voltage holds closely to the normal 115-120 volts for which they were designed. Over-voltage and/or under-voltage affects the performance of the tubes and the life expectancy of all other components. Why fight an off-standard voltage condition? Correct it with an Acme Electric T-8394M Voltage Adjustor.

Corrects voltage over a range from 95 to 125 volts to normal 115/120 volts, simply by turning a regulating switch. Includes voltmeter which indicates output voltage; cord and plug and plug-in receptacle. Tell your supply dealer you want the Acme Electric T-8394M 300 watt, Voltage Adjustor. No other so compact, complete, practical, inexpensive. Write for Bulletin 091.

**ACME ELECTRIC CORPORATION**  
943 Water St. SAA 3581-2033 Cuba, N. Y.  
In Canada: Acme Electric Corp. Ltd., 50 Northline Rd., Toronto Ont.

**Acme Electric**

## Ringling Checks

(Continued from page 31)


own vertical input lead to the special jack, because the pulse is likely to be derived from the horizontal sweep generator, and ordinarily occurs during retrace of the CRT beam. However, the serviceman can readily check for special pulse signals by using another scope to check all panel terminals of his own scope. A pulse from the horizontal sweep generator makes an excellent test signal because it offers a wide choice of ringing frequencies and automatically synchronizes the ringing waveform with the scope sweep.

If a suitable pulse is found, it can be connected directly to the coil under test, as shown in Fig. 2A. A sawtooth-wave output from the scope can also be utilized by adding a small capacitor (approximately 100 mmf) in series with the lead from the special jack to the coil.

In case the scope provides no ready-made pulse source, there are several other instruments that can supply a signal; one is the square-wave generator used in many shops for checking audio amplifiers. But instead of using an external source such as this, it's easier in the long run to modify a scope so it always has a ringing pulse "on tap." This can be done by simply adding one little capacitor within the scope and connecting it to an insulated binding post on the panel.

The arrangement of the binding post is left to the individual serviceman's discretion. He can either add one more post to the scope panel or convert some post to a ringing-pulse connection.

The internal capacitor hookup depends on the type of horizontal sweep circuit used in the scope. Fig. 2B shows the proper connection for scopes that use a cathode-coupled multivibrator as a horizontal sweep generator. Scopes using the Selzer-Anthony horizontal sweep circuit should be wired as shown in Fig. 2C, to minimize loading of the multivibrator. I have tried to show enough of both these common circuits so that little difficulty should be had by any serviceman in making the ringing-pulse modification. Generally, all he will need to do is to get out the wiring sche-

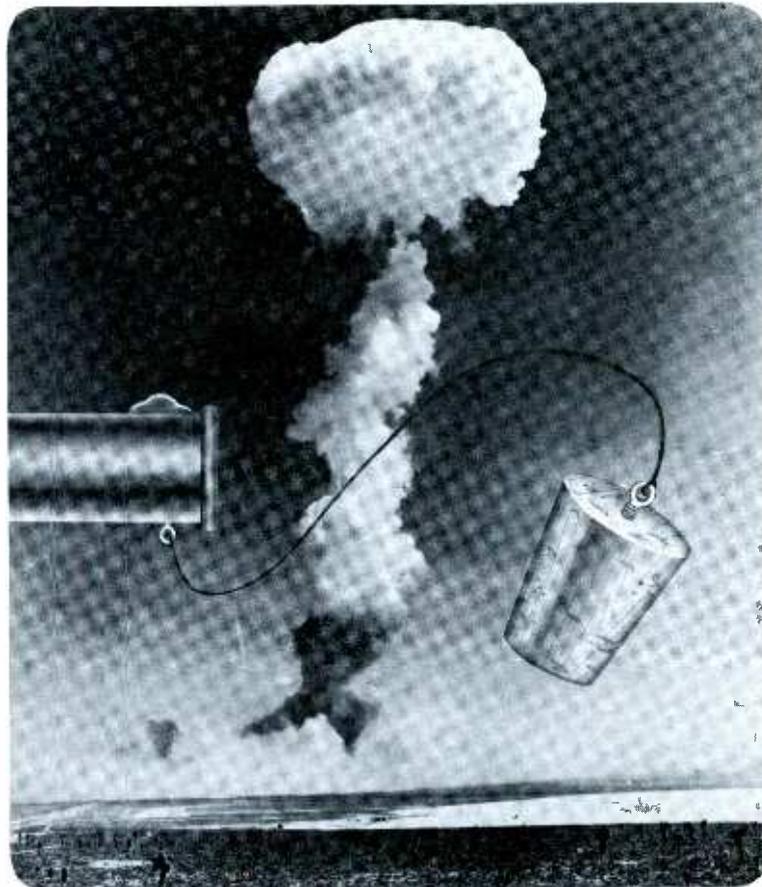

## full-range SOUND

Popgun or atomic blast . . . There's a Precision PA amplifier to handle any sound requirement, large or small. Realistically power-rated, you can select a unit to provide uniform coverage on every job.

You can count, too, on Precision's reputation for quality . . . dependable design that means versatility and operating simplicity throughout the entire line.

Write for Popular PA and Professional Sound Catalogs.



**MODEL 10PA**  
Low end of a popular line of PA equipment ranging up to 100 watts of audio output.



**MODEL G5M**  
Deluxe preamplifier, mixer, equalizer from Precision's professional sound group.



**MODEL 25MPA**  
All-transistor 25 watt mobile PA amplifier featuring low current drain from 12 volt car battery.

*Grommes*  
**PRECISION ELECTRONICS, INC.**  
9101 KING STREET • FRANKLIN PARK, ILL.

matic of his scope and match it with Fig. 2B or 2C, correlating tube functions and sweep controls.

### Sweep Frequency for Testing

It is very important that the correct scope-sweep frequency be used in making a ringing check. I have observed that the natural resonant frequency of a ringing-test setup including a horizontal deflection component is usually around 30 kc. If ringing at this frequency is examined with a 10-kc scope sweep, only the first three cycles of the damped wave will be visible, as

in Fig. 3A; if the scope trace is swept at only 300 cps, the ringing cycles quickly decay and appear bunched at the start of the trace (Fig. 3B). Obviously, neither of these sweep frequencies is appropriate for checking horizontal deflection components.

While using either of the test setups in Figs. 2B and 2C to check yokes or flybacks, I have found that a sweep frequency of approximately 2600 cps presents a wave train that just barely decays to an insignificant amplitude across the full width of the trace (Fig. 3C).

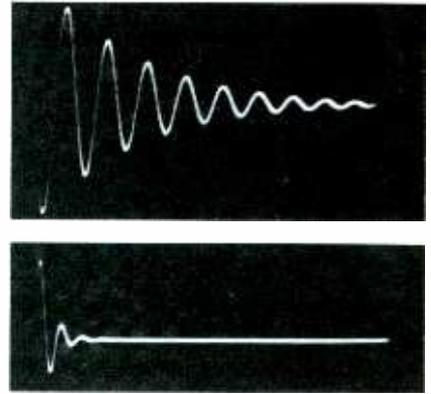


Fig. 5. Out-of-circuit tests of good and bad flybacks give these results.


Locating this approximate sweep frequency is fairly simple: Scope the horizontal drive signal in a properly operating TV receiver, and adjust the scope's sweep-frequency switch and vernier frequency control so that six cycles of horizontal drive occupy one trace. Make a mental or written note of these control settings for future usage.

### Horizontal-Circuit Tests

One major advantage of the ringing test is that the entire horizontal deflection circuit, or at least most of the inductances in the circuit, can be checked with one test. In this initial check, it is not necessary to disconnect anything—not even the high-voltage rectifier. Merely attach both the vertical-input lead and the pulse lead of the scope to the plate lead of the horizontal output tube, and attach the scope ground lead to the receiver chassis or B minus. Standardize on using this hookup for all types of deflection circuits—straight transformer, autotransformer, or direct drive.

Fig. 4 tabulates the results typically obtained in these three common deflection circuits at a test frequency of 2600 cps. Note that different defects sometimes give nearly identical test results; however, the exact defect can be found by making further tests. For example, a shorted flyback and a shorted width coil usually produce quite similar ringing traces. If a check of the entire circuit indicates that either of these windings is possibly defective, it is a simple matter to pinpoint the offending part by merely disconnecting the width coil. If trace B remains, the width coil is apparently not the offender. Next, any capacitor that shunts a wind-

*"good enough"*

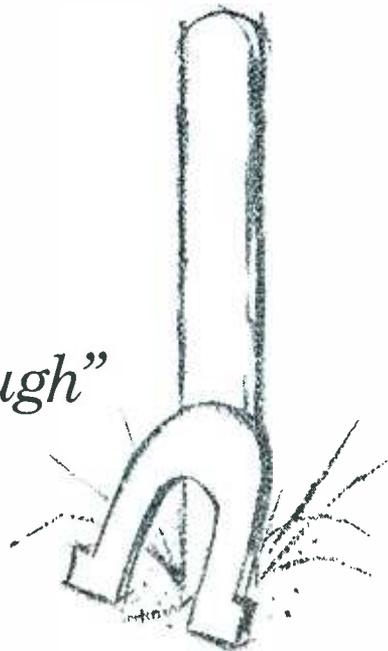

*is not enough at Stancor*



We will never be content to rest on our laurels. Even though proof of customer satisfaction is expressed for Stancor products by our position of leadership in the marketplace—our Product Development Program is working every day to make our product not merely the best available . . . but the best possible.

Check our brand-new Admiral, Philco and Silvertone replacements. You'll find:  
 • Complete, detailed, self-sufficient instruction sheets • Slotted mounting brackets for easier installation • Longer leads for greater versatility and convenience • Improved insulation to minimize corona.


These features are all part of Stancor's program to give you replacement transformers that are better than Original parts with servicing simplicity built right in . . . because good enough is *not* enough for Stancor's customers.

**STANCOR**  
 ELECTRONICS, INC.  
 3501 W. ADDISON • CHICAGO 18, ILL.


ing of the flyback should be disconnected, and finally the yoke itself should be taken out of the circuit. If any of these operations results in a normal trace, the last part disconnected is at fault. If trace B remains, there is scarcely any doubt left that the flyback is defective.
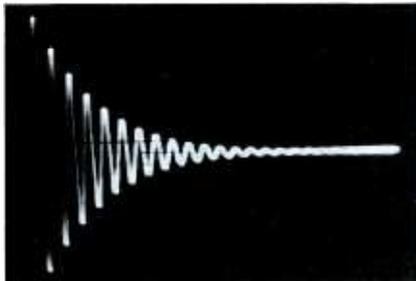
### Checking Components Separately

"Out-of-circuit" checks of individual components are equally simple, if standardized hookups and specific scope-sweep frequencies are consistently used. For flybacks, the condition of all windings can be determined by connecting the scope across the winding considered to be the transformer's "primary." That is, attach both the pulse-supply lead and the vertical-input lead to the plate wire of the horizontal output tube (not the high-voltage rectifier plate connection), and clip the scope's ground lead to the other end of this winding. On autotransformers, ground the bottom terminal. A representative trace obtained from a good flyback, using a sweep frequency of 2600 cps, is shown in Fig. 5A. Either a single-turn short or a high-resistance leakage within any winding, as well as shorts between separate windings, will show



(A) Normal for 44-mh yoke

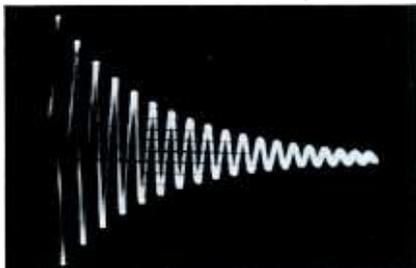

(B) Normal for 9-mh yoke



(C) Defective—any type

Fig. 6. Yoke ringing patterns.

CHECKS AND REJUVENATES ALL PICTURE TUBES  
WITHOUT ADAPTORS OR ACCIDENTAL TUBE DAMAGE



the all NEW

Featuring Automatic Controlled Rejuvenation

# SENCORE

## CR125 CATHODE RAY TUBE TESTER

From SENCORE, designers of the famous Mighty Mite Tube Tester and other valuable time savers, comes another industry best. An all new method of testing and rejuvenating picture tubes. Although the method is new, the tests performed are standard, correlating directly with set-up information from the RCA and GE manuals.

Check these outstanding features and you will see why this money making instrument belongs on top of your purchasing list for both monochrome and color TV testing.

**Checks all picture tubes thoroughly and carefully;** checks for inter-element shorts, cathode emission, control grid cut-off capabilities, gas, and life test.

**Automatic controlled rejuvenation.** A Sencore first, preventing the operator from over-rejuvenating or damaging a tube. An RC timing circuit controls the rejuvenation time thus applying just the right amount of voltage for a regulated interval. With the flick of a switch, the RC timer converts to a capacity type welder for welding open cathodes. New rejuvenation or welding voltage can be re-applied only when the rejuvenate button is released and depressed again.

**Uses DC on all tests.** Unlike other CRT testers that use straight AC, the CR125 uses well filtered DC on all tests. This enables Sencore to use standard recommended checks and to provide a more accurate check on control grid capabilities. This is very important in color.

**No interpretation chart.** Two "easy view" neon lights clearly indicate shorts between any element. A chart is included for interpretation of shorts, if desirable. This chart is not necessary for normal testing on the CR125.

**No adaptor sockets.** One neat test cable with all six sockets for testing any CRT. No messy adaptors, reference charts or up-dating is required. The Sencore CR125 is the only tester with both color sockets. (Some have no color sockets, others have only the older type color socket.)

**No draggy leads.** A neat, oversized compartment, in the lower portion of the CR125 allows you to neatly "tuck away" the cable and line cord after each check in the home.



All six sockets, including latest color socket, on one neat cable.

**SENCORE, INC.**

426 S. WESTGATE DRIVE  
ADDISON, ILLINOIS

### SPECIAL INTRODUCTORY OFFER WORTH \$5.00

Most SENCORE products are sold by recommendation. So that you will be first in your area to buy and recommend the CR125, this coupon is worth \$5.00 on the purchase of the CR125 when presented to your parts distributor.

Why not save \$5.00 now?

Herb Bowden  
President

# TWICE

## THE performance



### TRANSISTORIZED "FREQ" METER

### NEW! UP TO 48 AM/FM CHANNEL OPTION



TYPE 5890B

True versatility is now achieved by permitting up to 48 rf/af channels. (With optional case). Rugged and lightweight, the basic meter weighs but 8 pounds and is ideally suited for such functions as: carrier frequency error indication, relative transmitter field strength, modulation deviation measurement, receiver rf alignment generator, aural monitoring of modulated signal, and a host of others.

#### FEATURES

- 24 r-f/i-f channels and an audio signal in one, pint-sized package. (48 channels optional).
- 25 to 470 Mc spectrum plus i-f channels in the 100 kc to 100 Mc range.
- Defies obsolescence—permits addition of new channels.
- Signal generator output for receiver servicing.
- Checks adjacent- or split-channel gear with excellent precision.
- Compact, transistorized, life-long battery powered—requires no AC connection.

ONLY \$435 Basic 24 channel unit  
(Furnished with one rf crystal)  
Additional 24 channel add-on unit  
Price less crystals

\$199

## FAIRCHILD

ROU MONT LABORATORIES  
DIVISIONS OF FAIRCHILD CAMERA AND INSTRUMENT CORPORATION  
750 Bloomfield Avenue, Clifton, New Jersey

up as in Fig. 5B. Results of this test are practically identical in nearly all flybacks, even those as dissimilar as the so-called "Flying Saucer" and the heavy, complex-cored types used in early receivers.


To check the horizontal windings of a yoke, attach the pulse and vertical-input leads of the scope to one end of the windings, and ground the other end. Again, use a 2600-cps sweep. Resultant traces will vary somewhat, depending upon the inductance of the windings. A high-inductance winding (44 mh) presents the rather fast-decaying trace in Fig. 6A, while a low-inductance (9-mh) yoke produces greater ringing (Fig. 6B). Only slight ringing, as pictured in Fig. 6C, indicates a defective yoke.

Defective linearity coils will not show up in the "entire-circuit" check, except in some very rare designs. A defect is easy to recognize, however, by merely adjusting the core. A good linearity coil will have an effect on raster linearity, width, or brightness, whereas a defective linearity coil will have no effect—regardless of how much its inductance is varied.

There may be times when a serviceman might want to give this coil a separate ringing test. It can be done, but the scope frequency is different from that used with other horizontal coils. The scope sweep should be set to approximately 4000 cps—recognized by locking in four cycles of horizontal drive from



(A) Normal for 2.5-mh coil

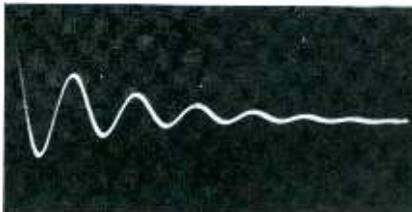

(B) Normal for 20-mh coil



(C) Short—either type of coil

Fig. 7. Linearity-coil ringing.

### YOUR INSURANCE POLICY

ALL G.A.M. FIXED STATION ANTENNAS (UHF) & (VHF) ARE INSURED UP TO \$250.00 AGAINST LIGHTNING OR WIND STORM AT NO COST TO YOU!

### G.A.M.'s FIRST AGAIN!

Simply fill out G.A.M.'s form and send to us when you buy Model TG-5-S or any G.A.M. Fixed Station and we'll send you your policy FREE! Up to \$250.00 protection for cost of labor for the re-installing, or replacing, or repairing antenna only in the event that antenna shall have been damaged or destroyed by lightning or windstorm. Offer good in U.S.A. and CANADA

### TG-5-S FIXED STATION

- HEAVY DUTY CONSTRUCTION
- THREE HALF WAVE ELEMENTS
- SWR LESS THAN 1.5:1
- MAKES 20 WATTS SOUND LIKE 60 WATTS

\$95.00 LIST

WRITE FOR INFORMATION  
ON SPRINGS, MOBILE AND  
FIXED STATION HIGH GAIN  
ANTENNAS (VHF & UHF).

SEE YOUR DISTRIBUTOR OR WRITE G.A.M. DIRECT  
**G.A.M. Electronics** inc.  
138 Lincoln St., Manchester, N. H.

Save time  
& increase  
efficiency...

Be modern  
& completely  
up-to-date...



Operate Test Equipment, TV, Radio,  
Soldering Irons, Power Tools, etc.  
110 Volt, 60 Cycle A.C. Power  
from your Battery, with a

## terado POWER INVERTER

[60 cycle frequency stable within 1/2 cycle, in spite of changing input voltage or load.]

Now your truck can be a repair shop on wheels! Terado power inverters provide the needed 60 cycle, 10 volt power for operating television and radio sets, signal generators, tube testers, vacuum tube voltmeters, oscilloscopes, soldering irons, drills and other uses. Models from 15 to 600 watts.

See your electronics parts jobber, or write:

**terado CORPORATION**  
1073 Raymond Avenue  
St. Paul 8, Minnesota  
In Canada, Atlas Radio Corp. Ltd. — Toronto, Ont.

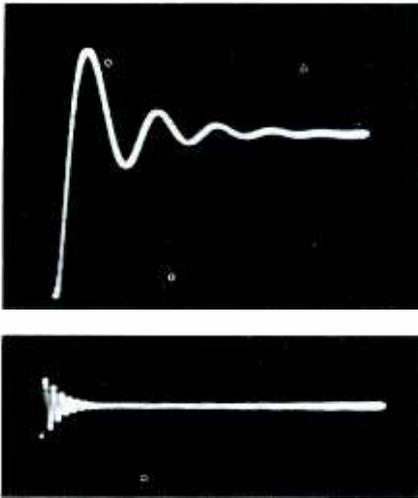


Fig. 8. Good and bad vertical output transformers—scope frequency 800 cps.

an operating receiver. Apply the test leads across the full winding on tapped units, or across the largest winding on multiple-wound units. Resultant traces for typical coils are shown in Fig. 7.


#### Vertical Sweep Coils

For vertical deflection components, use a hookup like Fig. 2A across the largest winding of the component (primary of output transformer, or secondary of blocking-oscillator transformer); use a sweep frequency of 800 cps. As mentioned earlier, these iron-core units do not have a very high Q; therefore, even a good unit will ring for only a few cycles. Nevertheless, the difference between normal and abnormal patterns is still obvious, as demonstrated in Fig. 8.
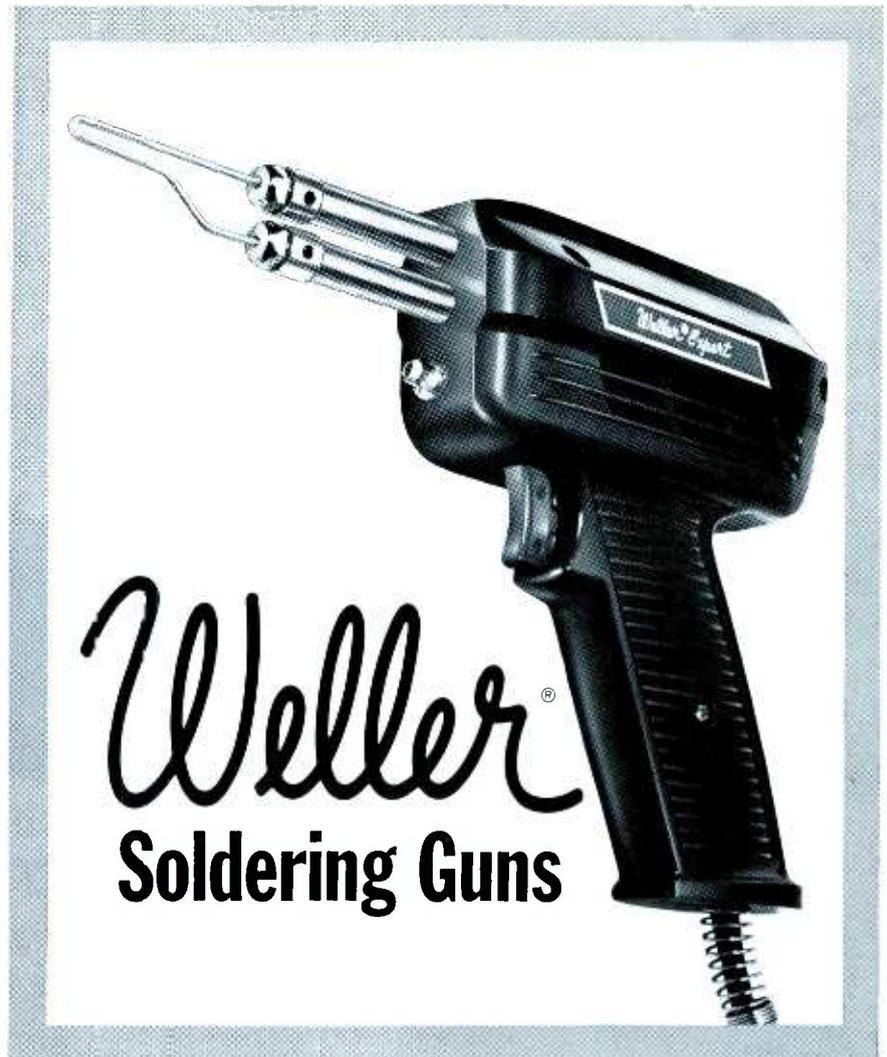
#### Choice of Frequency

The frequency of the shock-excited oscillations in a ringing test depends not only on the characteristics of the coil being tested, but also on the shunt capacitance introduced by the scope connections. Since test conditions may vary to a considerable degree, some servicemen may find it necessary to use scope-sweep frequencies somewhat different from those which have been mentioned.

The easiest method of finding the proper frequencies for your scope would be to make ringing tests on a number of known good coils at various sweep rates, and standardize on the frequencies at which the damped wave trains appear similar to the ones illustrated in this article. ▲



OVER  
5 MILLION  
SOLD

ALL MODELS  
DUAL HEAT

YOUR  
BEST BUY

**2 soldering temperatures.** An original Weller feature that provides 2 trigger positions, lets you switch instantly to high or low heat to suit the job.

**Prevents damage to critical components.** You use low heat when working with heat-sensitive components.

**Tip lasts longer.** Dual Heat enables you to prolong tip life by using high heat only when necessary.

**Gives full, constant heat.** Wiping action of tip nuts eliminates contact resistance, oxidation.

**Solders in seconds.** No waiting. Saves time and current.

**No danger from an idling hot tool.** Heat is instantly "on" or instantly "off".

**Spotlight illuminates work.** Eliminates shadows.

**Comfortable in use.** Pistol grip fits hand naturally, remains cool.

Weller Dual Heat Soldering Guns are available in many models with ratings from 100/140 to 240/325 watts. Also supplied in plastic-case kits with accessories. All Weller Guns are guaranteed 1 year.

At your Electronic Parts Distributor

WELLER ELECTRIC CORP., 601 STONE'S CROSSING RD., EASTON, PA.

## Stereo FM

(Continued from page 33)  
only the multiplex section, but also the RF tuner and IF's for a symmetrical wide-band response.

### Alignment Equipment

If misalignment is responsible for improper operation of the stereo FM multiplex unit, make sure you have the proper test equipment. You'll need a stereo signal generator, an oscilloscope, and an AC VTVM. You may need an audio oscillator, too, depending on which


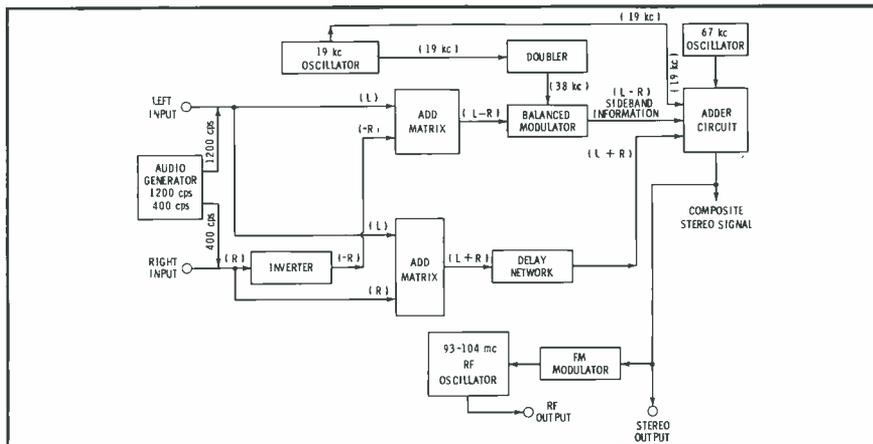


Fig. 3. Multiplex generator produces all essentials of stereo-FM signal.

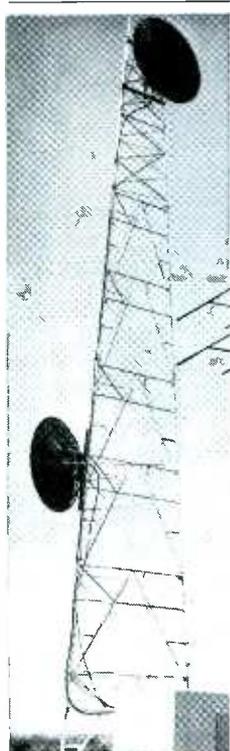

*The most Famous Name in  
**TOWERS of ALL KINDS!***

**Here are the advantages you get  
when you insist on ROHN TOWERS**

**LARGEST FULL RANGE OF TOWERS**—you can get anything from home TV and amateur radio towers to heavy-duty communication and micro-wave towers. Included are 170 foot self-supporting towers, 1,000 foot guyed towers, and "fold-over" towers. Regardless of your needs, ROHN can supply it.


**UNQUESTIONED LEADERSHIP IN DESIGN AND MANUFACTURE**—you get the latest in advanced tower engineering. All communication towers are engineered to EIA specifications, and are proved by thousands of installations. No other manufacturer can surpass the quality and fine reputation of ROHN.

**QUALITY MATERIALS AND WORKMANSHIP**—Only highest quality steel is used which fully meets the specifications for the job. ROHN towers are hot-dipped galvanized **after fabrication**—a feature ROHN pioneered!

**SERVICE WHEREVER YOU WANT IT**—ROHN representatives are world-wide. Complete erection service for communication systems, broadcasting, micro-wave, and other needs is available; also competent engineering service to help you.

**Settle for the BEST in TOWERS**—ROHN—today the world's largest, exclusive manufacturer of towers of all kinds!

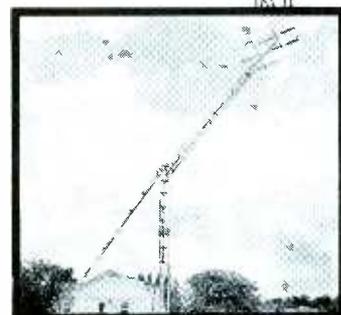*For your needs, contact your local ROHN salesman, distributor or dealer; or write direct for information.*



SEND THE HANDY COUPON INDICATING YOUR NEEDS

**ROHN**  
Manufacturing  
Company  
BOX 2000  
PEORIA, ILLINOIS

ROHN Manufacturing Company  
Box 2000  
Peoria, Illinois

Send me complete literature on the following ROHN Products:

<input type="checkbox"/> Home TV Towers	<input type="checkbox"/> Amateur Towers
<input type="checkbox"/> Communication Towers	<input type="checkbox"/> AM-FM Broadcasting Towers
<input type="checkbox"/> Micro-Wave Towers	<input type="checkbox"/> Government

Name \_\_\_\_\_  
Firm \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

stereo generator you use.

Basically, there are several types of stereo-FM signal generators available. One type has no internal RF generator, and must be coupled directly to the multiplex section; others are RF types that can feed a signal into the stereo receiver's antenna terminals. Some generators have built-in audio oscillators, while others require an external audio generator as an accessory. The functions of all types are similar, once the equipment is set up for operation.

Fig. 3 shows a typical stereo-FM signal generator. Let's analyze the block diagram, to see where and how the alignment signals are developed.

The left-channel audio (L) and the right-channel audio (R) information are combined in the add matrix networks. However, before being applied to the L - R matrix circuit, the right-channel audio information is inverted in phase so proper mixing will take place. The output of the L - R add matrix is fed into a balanced modulator along with an internally generated 38-kc signal. The balanced modulator suppresses the 38-kc subcarrier, and the output contains only the L - R sidebands. This information is sent to another adder circuit for mixing with the L + R signal and the 19-kc pilot carrier.

The L + R signal must pass through a delay circuit so it will arrive at the adder exactly in phase with the L - R sideband information. To insure that the sideband information recovered at the receiver will maintain a proper phase relationship with the L + R signal, the generator provides a 19-kc subcarrier for the 38-kc reinsertion-

signal oscillator to "lock in" upon.

Provisions are made in some generators for supplying the adder circuit with a 67-kc signal for use in aligning the receiver traps that attenuate SCA interference. Some instruments include a 67-kc oscillator, while others provide only a jack where the SCA signal can be injected. The 67-kc signal, the 19-kc signal, and the L - R sideband information can usually be switched on and off, for testing multiplex units under various signal conditions.

From the adder circuit, the composite stereo signal is coupled to the stereo output jack. The unit being discussed also incorporates an RF generator having a tunable frequency range from 92 to 104 mc. With this type of generator, you can simulate an actual stereo-FM broadcast, with the output being coupled loosely or directly to the antenna terminals of a stereo-FM receiver; if desired, a stereo tape or phono recording can be used for program material, instead of the internal audio oscillators.

To show the variety of facilities included in stereo-FM signal generators, Chart I lists several key specifications for most of the service-type units now available.

### Alignment Setups

The detector output level of the FM receiver is very important. Multiplex circuits may require anywhere from .2 volts to 2 volts rms for normal operation, and the stereo signal generator must be set for an output level sufficient to "drive" them. Distortion and motor-boating can be caused by insufficient signal voltage at the multiplex input, since the 19-kc pilot signal may be too weak to synchronize the demodulator system. On the other hand, too much signal voltage can cause distortion, poor separation, and spurious responses. To determine the correct level (if you don't already know), you can use your scope to observe the detector output of the receiver, while it is tuned to a station broadcasting stereo. Then connect the leads from the multiplex generator to the scope and adjust the signal level for the same approximate peak-to-peak deflection.

For aligning the 19-kc oscillator

## For Big Profits Doing This...



### ...Use These:

Whether it's hi-fi in the home, or CB in car, boat, truck, or taxi, custom installation jobs jump into the big-profit category when you deliver high quality at low cost.


And especially with EICO kits, which average 40% less than our own, low, wired prices. Wire 'em up yourself and pocket the difference—with your customer's blessing, because if you build the components yourself, it's custom-made all the way through!

But kit or wired, EICO's all-out, no-compromise engineering, EICO's strikingly dramatic beauty, and EICO's fantastically low prices provide all the ingredients necessary for big profits on custom jobs. To put it simply: *You Profit from EICO Excellence.*



Deluxe Citizens Band Transceivers

	Kit	Wired
# 770: 117 VAC only	\$79.95	\$109.95
# 771: 117 VAC and 6 VDC	89.95	119.95
# 772: 117 VAC and 12 VDC	89.95	119.95

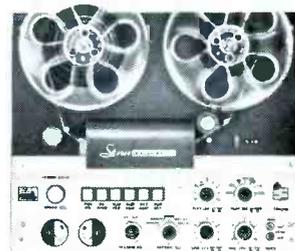


NEW TRANSISTORIZED  
STEREO/MONO 4-TRACK  
TAPE DECK RP100

Semikit \$299.95	Wired \$399.95
Luggage-type Carrying Case \$29.95	
Standard 19-inch Rack Mount \$9.95	



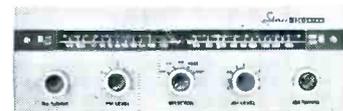STEREO FM MULTIPLEX TUNER ST97  
Semi-Kit \$99.95      Wired \$149.95  
Includes metal cover and FET.



FM/AM STEREO TUNER ST96  
Kit \$89.95      Wired \$129.95  
Includes metal cover and FET.




70-WATT INTEGRATED  
STEREO AMPLIFIER ST70  
Kit \$99.95      Wired \$149.95  
Includes metal cover and FET.

40-WATT INTEGRATED  
STEREO AMPLIFIER ST40  
Kit \$79.95      Wired \$129.95  
Includes metal cover and FET.

Rely on EICO Excellence for your test equipment too:



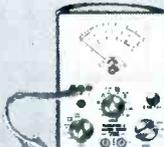AC VTVM &  
AMPLIFIER  
#250  
Kit \$49.95  
Wired \$79.95



TRANSISTOR  
AND CIRCUIT  
TESTER #680  
Kit \$25.95  
Wired \$39.95



IN-CIRCUIT  
CAPACITOR  
TESTER #955  
Kit \$19.95  
Wired \$39.95

**EICO**

ADD 5% IN THE WEST

For complete catalog of over 106 EICO kits and wired units—hi-fi, test equipment, citizens radio, ham gear—plus name of nearest distributor, write to dept PF-3 EICO ELECTRONIC INSTRUMENT CO., INC., 3300 Northern Blvd., L.I.C. 1, N.Y. Export Dept., Roburn Agencies Inc., 431 Greenwich Street, New York 13, N. Y.

See Us at IRE Booth #3101

# NEW SAMS BOOKS

## Electronics Math Simplified, Vol. 2

By Alan Andrews. Progresses from Vol. 1; new advanced sections on algebra and trigonometry; circuit and component data calculations, Boolean algebra, and mechanics. Emphasizes the practical uses of math in electronics; includes numerous examples and practical exercises; appendix has log and trig tables. An excellent self-study guide, well-suited also for school textbook use. Very helpful to anyone studying for 1st- and 2nd-Class Licenses. \$4.95 224 pages; 5 1/2 x 8 1/2". Order MAT-2, only. . . . \$4.95  
Electronics Math Simplified, order MAT-1 . . . \$4.95

**101 Ways to Use Your Color TV Test Equipment**  
By Robert G. Middleton. Written in the time-tested formula acclaimed by thousands of TV technicians. Shows you practically how to use test equipment to diagnose color TV circuit troubles quickly and easily. Describes proper equipment hookups, how to evaluate test results, how to check instruments; includes time-saving techniques. 144 pages; \$2.50 5 1/2 x 8 1/2". Order TEM-9, only. . . . \$2.50

## Basic Electronic Series: Radio Circuits

By Capt. T. M. Adams, U.S.N. Fifth volume in a series using unique 4-color diagrams to show visually the voltage and current actions and signal paths in basic electronic circuits, during each and every moment of operation. This volume explains how oscillator, amplifier, detector and rectifier circuits are combined to form all the basic types of radio receiver circuits. Superior to any previous texts. \$2.95 160 pages; 5 1/2 x 8 1/2". Order BER-1, only. . . . \$2.95  
Previous 4 vols. in slipcase—Save \$1.85! Order BEL-40, only. . . . \$9.95

## CB Radio Servicing Guide

By Leo G. Sands. Only complete book on the subject! This easy-to-understand guide describes typical CB sets and installations, including design and operation of all modern CB transmitter, receiver and power supply circuits; gives detailed procedures for tuning up, testing, troubleshooting; explains FCC regulations regarding operation and servicing. Includes valuable chapters for the professional technician. 160 \$2.95 pages; 5 1/2 x 8 1/2". Order CRS-1, only. . . . \$2.95

## Transistor Radio Servicing Manuals

Just out! 4 timely volumes (17, 18, 19, 20) in a single money-saving vinyl-wrapped package. PHOTOFAC<sup>®</sup> coverage of 224 popular transistor radio models: Admiral, Airline, Aladdin,

Americana, Arvin, Baylor, Bulova, Channel Master, Columbia, Continental, Coronado, Crest, Emerson, Fuji Denki, Futura, GE, Harpers, Hitachi, Hoffman, Kowa, Lafayette, MMA, Matsushita, Motorola, Norelco, Olympic, Panasonic, Philco, Plata, RCA, Realistic, Realtone, Riviera, Roscon, Sampson, Seminole, Sharp, Silverstone, Sony, Standard, Supreme, Sylvania, Toshiba, Trans-American, Trans-ette, Travler, Tru-tone, Webcor, Westclox, Westinghouse, Yaou, Zenith. \$9.95 Vols. 17, 18, 19, 20 ordered individually, each. \$2.95  
PHOTOFAC<sup>®</sup> coverage of 224 popular transistor radio models: Admiral, Airline, Aladdin, Americana, Arvin, Baylor, Bulova, Channel Master, Columbia, Continental, Coronado, Crest, Emerson, Fuji Denki, Futura, GE, Harpers, Hitachi, Hoffman, Kowa, Lafayette, MMA, Matsushita, Motorola, Norelco, Olympic, Panasonic, Philco, Plata, RCA, Realistic, Realtone, Riviera, Roscon, Sampson, Seminole, Sharp, Silverstone, Sony, Standard, Supreme, Sylvania, Toshiba, Trans-American, Trans-ette, Travler, Tru-tone, Webcor, Westclox, Westinghouse, Yaou, Zenith. \$9.95 Vols. 17, 18, 19, 20 ordered individually, each. \$2.95

## Ham Antenna Construction Projects

By J. A. Stanley, WØBV. Shows you all you need to know to custom-build your own antenna. Describes "basic" horizontal dipole and V-beam designs, vertical jobs for best low-angle radiation and DX'ing, trap types, multi-element beams and single-side-band units, UHF, and even indoor styles. Gives step-by-step instructions for installing, tuning up, testing, getting most from transmitter power. \$2.95 160 pages; 5 1/2 x 8 1/2". Order HAJ-1, only. . . . \$2.95

## ABC's of Lasers and Masers

By Allen Lytel. The first easily understandable coverage of this fascinating subject. Explains how these special semiconductors are used in micro-wave and light-frequency radiation applications. Describes dramatic aspects of Laser technology, in which a radiating beam is used as a surgical knife, welding torch, heat ray, etc. Provides an understanding of Laser theory and its significance. 96 pages; \$1.95 5 1/2 x 8 1/2". Order LAL-1, only. . . . \$1.95

## Citizens Band Radio Manual, Vol. 3

PHOTOFAC<sup>®</sup> coverage of 38 late-model CB transceivers: Cadre, Capital, Citi-Fone, Eico, Globe, Gonset, Hallcrafters, Heath, ITT, Lafayette, LaSalle, Magnavox, Philmore, Poly-Comm, Vocaline, Webcor. Includes section on test equipment requirements for CB servicing. 160 pages; 8 1/2 x 11". \$2.95 Order CB-3, only. . . . \$2.95

## HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. No. C-33 4300 W. 62nd Street, Indianapolis 6, Ind.

Send me the following books:  
 MAT-2  TEM-9  BEL-40  TSM-51  LAL-1  
 MAT-1  BER-1  CRS-1  HAJ-1  CB-3

\$\_\_\_\_\_ enclosed.  Send FREE Booklist

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

coil, simply disable all L and R signals in (or to) the generator, and be sure no 67-kc signal is present; thus, you'll end up with only the 19-kc portion of the composite stereo signal. Connect the generator to the input of the multiplex circuitry—or, if it is an RF type, to the receiver-antenna terminals. Hook the scope (or AC VTVM) at some convenient point between the demodulator and the coil to be adjusted. The 19-kc signal source can also be used to align the 38-kc coil or transformer. Once the scope has been set for two cycles of 19-kc signal, a four-cycle display will appear when the 38-kc doubler is in proper adjustment.

For checking and aligning the separation between the left and right channels, the ideal setup can be accomplished by using the signal generator to feed the composite signal to the input of the adapter, and connecting a two-channel scope to the left and right outputs. The same effect can be had by using two AC VTVM's in place of the scope. By this arrangement, you can monitor both channels without switching leads. However, you can get excellent results by using a single scope or AC VTVM connected to one channel at a time; it just takes longer to complete the job.

Another alignment technique involves using both the horizontal input and vertical input circuits of your scope. Connect the horizontal input of the scope to an accurate 38-kc signal, and connect the vertical input to the 38-kc test point on the adapter. With the scope set for external sync, adjust the 19-kc oscillator coil until a circular pattern is observed on the scope screen. The 38-kc doubler coils or transformers can be peaked with this same setup.

## Conclusion

Stereo-FM alignment isn't complicated, as you can see from the foregoing; neither is the test equipment difficult to understand. And when you become familiar with the instruments and techniques of stereo alignment, spread the word among your audio and hi-fi customers who are in range of stereo broadcasts. You'll be surprised how your stereo business will pick up!



# INJECTORALL

THE NEEDLE DOES THE JOB!

**TUNER CLEANER AND LUBRICANT**  
with...  
**INJECTOR NEEDLE**

The leak-proof steel Injectorall Needle lubricates where you need it... you can reach hard-to-get at Wafers without pulling Tuners apart, or even removing Chassis.

The BEST CLEANER on the market today!

**INJECTORALL CO.** Brooklyn 14, New York


## Miniature I. F. TRANSFORMERS OSCILLATOR COILS and LOOP ANTENNAS

for Transistor Sets

GENERAL REPLACEMENTS FOR IMPORTED and DOMESTIC SETS

Size 3/8" x 3/8"  
PART NO. OPERATION  
455-A1 INPUT  
455-A2 INTERSTAGE  
455-A3 OUTPUT  
455-OA OSCILLATOR

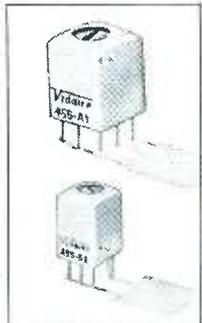Size 1/4" x 1/4"  
PART NO. OPERATION  
455-B1 INPUT  
455-B2 INTERSTAGE  
455-B3 OUTPUT  
455-OB OSCILLATOR



Packaged in Plastic See-Thru box in display carton with instruction

MODEL LA-14  
FOR USE WITH 148 MMFD. TUNING CONDENSER  
SIZE 1 1/8 x 1/8



MODEL LA-21  
FOR USE WITH 211 MMFD. TUNING CONDENSER — SIZE 2-5/16 x 11/16

MODEL LA-36  
FOR USE WITH 365 MMFD. TUNING CONDENSER — SIZE 2-13/16 x 11/16

Packaged in plastic bag on display card

**Vidatronics ELECTRONICS MFG. CORP.**  
365 BABYLON TPKE. — ROOSEVELT, N. Y.

# PRODUCT report

For further information on any of the following items, circle the associated number on the Catalog & Literature Card.

## Ceramic Microphone (51X)



A compact, high-output microphone, the **Euphonics Model C47 "Hot Head,"** is designed for Citizens-band, amateur, marine, and other communications applications. The unit has an average output level of -48 db, and a frequency range of 300-4000 cps. Other features include a DPDT push-to-talk switch, and a high-impact case. The unit will operate over a temperature range of 0° to 200° F. List price of the microphone is \$16.00.

## Contact Cleaner (52X)




A new spray solution, "Contact Kleen," can be used to restore smooth action to relays, controls, switches, attenuators, thermostats, and prongs. The cleaner is available from **Chemtronics** in an 8-oz. aerosol spray can, equipped with a stainless steel spray-extension tube. The price for each can is \$1.49.

## Nuvistor (53X)



Another addition to the growing nuvistor line — the **13CW4** — is similar to its companion types **2CW4** and **6CW4**, except for a 13.5-volt, 60-ma heater. This high- $\mu$  **RCA** unit was designed for use as a grounded-cathode RF amplifier in multiple-antenna systems and in antenna-booster amplifiers.

## Broadband Antenna (54X)

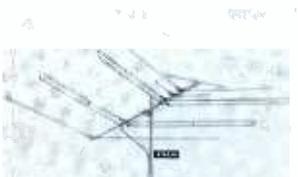

Providing a gain of at least 10.5 db within the high TV band, and 8.5 db within the low band, the **TACO Model C-33 "Color Guard"** is a broadband antenna designed for color-TV reception. The elements are manufactured of a chrome-aluminum alloy with a corrosion-proof golden conductive coating, and are designed for high mechanical strength to resist ice and wind loading. The antenna has a list price of \$17.95.


## Sweep Oscillator (55X)

The "Sona-Sweep" **1141-A** beat-frequency sweep oscillator, designed for testing and aligning ultrasonic amplifiers, is a recent development of **Kay Electric**. The unit covers frequencies from 20 cps to 200 kc, with sweep widths of 0 to 2 kc and 100 cps to 20 kc; the sweep rate can be manually varied from 5 to 25 cps, or locked at 30 cps. Crystal-controlled markers of 50, 100, and 200 kc, which may be used simultaneously or separately, are also available. The sweep output is a sawtooth, synchronized by the sweeping oscillator, and has an amplitude of approximately 7 volts.

Communications, mobile radio...

# A First Class FCC License

...or Your Money Back!

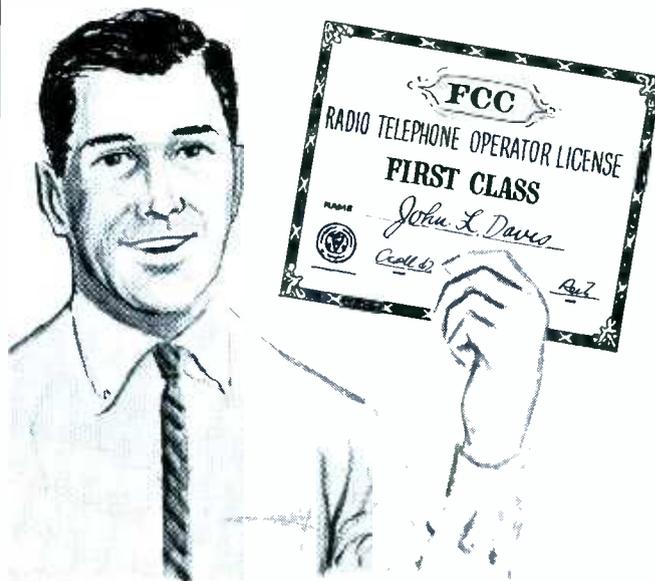

Your key to future success in electronics is a First-Class FCC License. It will permit you to operate and maintain transmitting equipment used in aviation, broadcasting, marine, microwave, mobile communications, or Citizens-Band. Cleveland Institute home study is the ideal way to get your FCC License. Here's why:

Our training programs will *quickly* prepare you for a First-Class Commercial Radio Telephone License with a Radar Endorsement. Should you fail to pass the FCC examination after completing your course, you will get a *full refund* of all tuition payments. You get an FCC License . . . or your money back!

You owe it to yourself, your family, your future to get the complete details on our "proven effective" Cleveland Institute home study. Just send the coupon below TODAY. There's no obligation.


### MAIL COUPON TODAY FOR FREE CATALOG

#### Cleveland Institute of Electronics

1776 E. 17th St., Dept. PF-4  
Cleveland 14, Ohio

Please send FREE Career Information prepared to help me get ahead in Electronics, without further obligation.

#### How to Succeed in Electronics

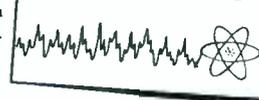

#### CHECK AREA OF MOST INTEREST -

- |   |  |
|---|--|
| <input type="checkbox"/> Electronics Technology | <input type="checkbox"/> First-Class FCC License   |
| <input type="checkbox"/> Industrial Electronics | <input type="checkbox"/> Electronic Communications |
| <input type="checkbox"/> Broadcast Engineering  | <input type="checkbox"/> _____ other _____         |

Your present occupation \_\_\_\_\_

Name \_\_\_\_\_ (please print) Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Accredited Member National Home Study Council

PRODUCT  
NEWS from EPL

# Only 37¢ per watt output DC Power Supply

Unbeatable Performance and Price



D-612T ... \$59<sup>95</sup>

► **Look at these exclusive features...**

- Lowest price per watt output.
- Full 10 ampere rating on V-12 volt range.
- Surplus power on 0-16 volt range.
- Full year warranty.
- Superior filtering over entire output.
- Large, easy-to-read plastic meters.
- Heavy overload capacity.

► **Compare with others...**

Brand	Voltage Output	Ampere Cont.	Output Interm.	Meters	Price/Watt Output**	Warranty	Terminals
EPL	0-8	10	20*	Large, clear plastic	.37	1 Year	Insulated binding posts
	0-16	10	20*				
A	6	10		Metal	.69	90 Days	Stud and wing nuts
	12	6					
C	0-8	10	20	Metal	.62	90 Days	Stud and wing nuts
	0-16	6	12				
E	0-8	10	20	Metal	.50	90 Days	Insulated binding posts
	0-16	6	10				
M	0-8	10	20	Metal	.62	1 Year	Stud and wing nuts
	0-16	6	14				
P	0-8	10	20	Metal	.68	90 Days	Metal binding posts
	0-16	6	12				

\*Best of all for operating signal seekers! \*\*Based on maximum continuous ratings.

**17 Others from 6 to 125 VDC from \$19.95 up**

Stocked at Your Electronic Distributor

**FREE NEW CATALOG PS-562 on complete line**



**ELECTRO PRODUCTS  
LABORATORIES**

6125-T Howard, Chicago 48 (Niles), Ill.

Phone: 647-6125

Canada: Atlas Radio Ltd., Toronto

Since 1936...Pioneers in Low Voltage DC Power Supplies

## Universal Replacement Knobs (56X)

A kit of two-part TV and radio tuning knobs, Colman stock number 1179, contains 12 knob heads and 48 stems that can be assembled into more than 2700 different replacement knobs. The new heads are color-matched to existing universal two-part knobs, and will fit all stems presently in use. The kit has a list price of \$15.56.




## Record Cleaner (57X)

A chemically-treated sponge, useful for removing grit and dirt from phonograph records, is being offered by **Fidelitone**. Periodic use of the sponge to clean the playing surface of records will keep them free from dust and lint; this helps to reduce wear on both the stylus and the record. The "Foam-Coat" sponge is packaged in a plastic box and is priced at 69¢.


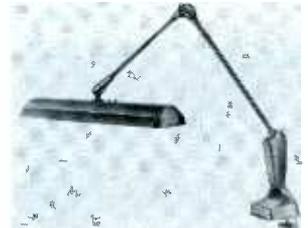
## Desk Lamp (58X)

This new fluorescent desk lamp, available in either neutral brown or office grey, is made by **Acme**. Designated as the Model 404G, the unit comes with either a standard 26" arm or an extra-long 33" arm. A double-bolt clamp holds the wide base securely to a desk or table; a pad on the clamp prevents damage to the furniture. The lamp may also be secured to the desk with screws, to provide a permanent installation.



## Scratch Remover (59X)

Technicians looking for a compound to remove fine scratches and abrasions from plastic material will be interested in "Surefire." Developed by **Wilco**, this nonflammable, nonabrasive compound can be used to remove scratch marks from any type of plastic—picture-tube safety shields and plastic cabinets, for example. "Surefire" will not scratch plastic surfaces, and is harmless to hands and skin.



## CB Microphone (60X)

The Model 356C microphone, for Citizens-band use, being marketed by **Turner**, has a frequency range of 80-7000 cps and an output of -53 db. The microphone, complete with a 5' coiled cord, comes wired for push-to-talk operation. A hanger button and a dash bracket are included. List price is \$12.50.



## Electric Antenna (61X)

No clips or springs are necessary with the **Tenna "C-Bam"** power-driven AM/FM/CB auto antenna, a pushbutton-operated unit that extends to 55" and retracts to 9½". Its collapsibility reduces chances of damage from low garage doors, washracks, and vandalism. The "C-Bam" is top-loaded and can be installed in most conventional locations on a vehicle. Any 12-volt battery will power the unit.

### Miniature Microphone (62X)



A rugged miniature microphone, the **Shure Model CA5A**, weighs only  $\frac{3}{4}$  of a gram. The tiny size of this high-impedance unit (1" x .250" x .100") makes it ideal for use in hearing aids, small head-worn microphones, hand-held transmitters, pocket tape recorders, and dictating machines. It has a frequency range of 50 to 5000 cps, and an output level of -73 db.

### Transistorized Tape Recorder (63X)



A new transistorized portable tape recorder, weighing only 5½ lbs., and able to provide two hours of playing time, is available from **Citroen**. The Model 660 comes equipped with leather carrying case, remote-control microphone, earphone, batteries, telephone pick-up, reel of tape, and take-up reel. The recorder has a list price of \$149.50.

### Tool Chest (64X)



Tools and parts are easily moved from one working area to another with the **Owatonna Model 105** rolling tool chest. Constructed of 18-gauge steel with a blue baked-enamel finish, the chest has three drawers plus a lower storage compartment. The front casters are equipped with locking toe brakes. An AC outlet attachment, to provide a source of power for test equipment and other tools, is available at

extra cost; also, a matching two- or six-drawer service chest may be purchased if extra drawer space is required.

### Speaker Enclosure (65X)



For use as a supplementary speaker system, the **Mercury Model CH-2 "Challenger"** is a slim enclosure with dimensions of 18" x 12" x 3½". It contains two 6" x 9" speakers and a 4" tweeter, a crossover network, and a side-panel knob that can be used to adjust the sound-output level. Available

in a walnut finish, with a user price of \$29.75, the unit has a peak power capacity of 15 watts.

### Receiving Tubes (66X)



Two new tubes, the 6HA5/-EC900 RF triode amplifier and the 6GJ7/ECF801 oscillator-mixer for use in UHF and VHF television tuners, were recently announced by **AmpereX**. When incorporated in future sets using the popular 6EH7 and 6EJ7 in a two-stage IF system, these new types will improve set sensitivity considerably. Both tubes feature frame-grid construction.

### Stereo/Mono Needle (67X)

A new kind of needle, capable of playing stereo records on a monophonic changer, has been added to the **Jensen** line. This offers the hi-fi fan an opportunity to start his stereo collection, even though he doesn't yet have a stereo phonograph. The needle is specially designed to "give" when it encounters the "hills and dales" found only in stereo records, thus avoiding damage to cartridge or record.

## ANOTHER SERVICE-PROVED PRECISION INSTRUMENT

### NEW MODEL CR-60 PICTURE TUBE TESTER AND REJUVENATOR. HEATER VOLTAGE CONTINUOUSLY VARIABLE FROM 1.5 TO 12V INDEPENDENT OF LINE VOLTAGE VARIATIONS




At last a picture-tube tester that can't become obsolete! Operating on the proven true "Beam-Current" circuit method, the CR-60 is a time and labor saver that pays for itself many times over. Tests and rejuvenates all picture tubes — black & white (110°, 114°, low G2) and color (each gun separately). Renews tube life. checks and repairs shorts, leakage, opens and low emission. Determines need for booster and predicts probable tube life. Portable, leatherette-covered case. See your PRECISION distributor or write. Net only \$64.95. This and all other PRECISION PRODUCTS are guaranteed for one full year

**PRECISION APPARATUS CO., INC.**

SUBSIDIARY OF PACOTRONICS, INC. 70-31 84th ST., GLENDALE, NEW YORK

## ANOTHER SERVICE-PROVED
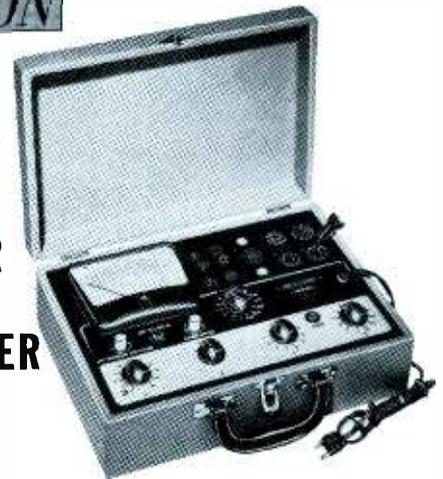
### PRECISION INSTRUMENT MODEL 650 GRID CIRCUIT ANALYZER TUBE TESTER AND MEGOHMMETER



Tests most tubes including 10-pin miniatures, 12-pin Compactrons, 5- and 7-pin Nuvisitors, Novars, octals, picture tubes (with optional adapter AD-65) and a wide variety of foreign and industrial types. Indicates gas currents as low as 1 ua. Checks for intermittent shorts, gas content, grid emission, leakages (sensitivity over 100 megohms). Special megohmmeter circuitry for measurement of condenser leakage, continuity and leakage of printed circuitry. Complete in leatherette-covered case. See your PRECISION distributor or write today for a complete catalog. Net only \$69.95. AD-65 Adapter: Net only \$5.95. This and all other PRECISION PRODUCTS are guaranteed for one full year

**PRECISION APPARATUS CO., INC.**

SUBSIDIARY OF PACOTRONICS, INC. 70-31 84th ST., GLENDALE, NEW YORK

March, 1963

Acme Electric Corp. 86  
 Aerogap Corp. 78  
 Aerovox Corp. 80  
 Arco Electronics, Inc. 54  
 Atlas Sound Corp. 66  
 ATR Electronics, Inc. 14  
 B & K Mfg. Co.—Div. of  
 Dynascan Corp. 45, 46, 55, 56, 57, 61, 73  
 Berns Mfg. Co., Inc., The 58  
 Blonder-Tongue Labs 69  
 Bussmann Mfg. Div. 18-19  
 Cadre Industries 81  
 Castle TV Tuner Service 43  
 Champion DeArment Tool Company 50  
 Channel Master Corp. 66  
 Clarostat Mfg. Co., Inc. 63  
 Cleveland Institute of Electronics 95  
 Delco Radio Div. (GMC) 51  
 DeSod Div. of Eversole Industries 60  
 DuMont, Allen B. Labs 90  
 Duetone Co., Inc. 84  
 EICO Electronic Instrument Co., Inc. 93  
 Electronic Publishing Co., Inc. 84  
 Electro Products Labs 96  
 Electro-Voice, Inc. 44  
 GAM Electronics, Inc. 90  
 GC Electronics Co. 49  
 General Electric Co.  
 Receiving Tube Dept. 16-17  
 Greyhound Corp. 47  
 Hickok Electrical Instrument Co. 67  
 Injectorall Co. 94  
 ITT Distributor Products Div. 21  
 Jackson Electrical Instrument Co. 98  
 Jerrold Electronics Corp. 2nd Cover  
 Karg Laboratories 68  
 Lafayette Radio Electronics Corp. 64  
 L. A. Tuner Exchange 76  
 Littelfuse, Inc. 4th Cover  
 Mallory, P. R. & Co., Inc. 39  
 Mercury Electronics Corp. 85  
 Merit Coil & Transformer Corp. 72  
 Motorola Training Institute 86  
 Ohmite Mfg. Co. 84  
 Precision Apparatus Co., Inc. 97  
 Philco Corp. 24-25  
 Planet Sales Corp. 68  
 Precision Electronics, Inc. 87  
 Precision Tuner Service 62  
 Quam-Nichols Co. 71  
 Raytheon Co. 40-41  
 RCA Electron Tube Div.  
 (Electronic Instrument Section) 77, 79  
 (Receiving & Picture Tubes) 3rd Cover  
 RCA Institutes, Inc. 20  
 RCA Parts & Accessories Div. 53  
 RCA Sales Corp. 59  
 RE-NU, Inc. 76  
 Rohn Mfg. Co. 92  
 Sams, Howard W. & Co., Inc. 70, 75, 94  
 Sarkes Tarzian, Inc. 11  
 Seco Electronics, Inc. 15  
 SENCORE, Inc. 22, 23, 89  
 Sprague Products Co. 12  
 Stancor Electronics, Inc. 88  
 Swing-O-Lite, Inc. 76  
 Terado Co. 90  
 Triplett Electrical Instrument Co. 1-2  
 Utah Electronics Corp. 58  
 Utica Communications Corp. 62  
 Vidaire Electronics Mfg. Co. 94  
 Volkswagen of America, Inc. 65  
 Weller Electric Corp. 91  
 Western TV Tuner Rebuilders 50  
 Workman Electronic Products, Inc. 58, 60, 68  
 Winegard Co. 26, 52

ANTENNAS & ACCESSORIES

- 1X. **ANTENNA-CRAFT**—Brochure on anodized aluminum UHF antennas, Models SA-1483 (channels 14-83) and SA-7083 (channels 70-83), guaranteed for black-and-white or color reception.  
 4X. **GAM**—Specifications on miniaturized TG-2-R VHF mobile antenna—mounts on top of vehicle or in other restricted spaces. See ad page 90.  
 5X. **JFD**—Brochures on LPV log-periodic TV antennas and *Transitenna*; also bulletins and catalogs showing entire line of TV-FM indoor and outdoor antennas and accessories.  
 6X. **WARD PRODUCTS**—Catalog 614 listing full replacement line of auto-radio and mobile communications antennas and accessories.  
 7X. **WINEGARD**—Complete technical data, schematic, and service tips on new "Red-Head" transistorized antenna preamplifier. See ads pages 26, 52.

AUDIO & HI-FI

- 8X. **ATLAS SOUND, Div. of American Trading & Production Corp.**—Catalog and specification sheet describing new Model EC-10 paging speaker and T-4 line-matching transformers. See ad page 66.  
 9X. **CBS LABORATORIES**—Information on STR-100 test record for professional audio technicians.  
 10X. **EICO**—New 32-page catalog of kits and wired equipment: stereo and monophonic hi-fi, test equipment, Citizens-band transceivers, ham gear, and transistor radios. Also "Stereo Hi-Fi Guide" and "Short Course for Novice License." See ad page 93.  
 11X. **FISHER**—40-page booklet giving authoritative answers to most frequently asked questions on stereo hi-fi; also list of available equipment.  
 12X. **HARMAN-KARDON**—Brochure on new line of mobile, portable, and general-purpose public address equipment.  
 13X. **OAKTRON**—8-page catalog of speakers, enclosures, wall and ceiling baffles, line transformers, auto rear-seat speaker kits, and accessories.  
 14X. **QUALITONE**—"Needle Wall Chart" cross-reference of cartridge numbers and replacement needles.  
 15X. **QUAM-NICHOLS**—Detailed information on full-fidelity hi-fi loudspeakers. See ad page 71.  
 17X. **SONOTONE**—Specification sheet on Model WR8-BH "New Sonotone Sound" wide-range hi-fi speaker.  
 18X. **UTAH**—Conversion data to allow using constant-voltage line transformers in constant-impedance systems; catalog sheet on baffles and line transformers. See ad page 58.

COMPONENTS

- 19X. **BUSSMANN**—Information on new GBB fast-opening fuse for protecting solid-state devices, such as semiconductor rectifiers. See ad page 18-19.  
 20X. **CENTRALAB**—6-page booklet describing "Fastatch" II replacement control system, and FRK-100 dealer kit.  
 22X. **LITTELFUSE**—Form L-562 showing prices and specifications on complete line of fuses, fuse holders, and merchandising aids. See ad 4th cover.  
 23X. **SPRAGUE**—Chart C-457 (designed to hang on wall) showing all popular TV/radio/hi-fi replacement components. See ad page 12.  
 24X. **SWITCHCRAFT**—Specifications on new *NF-Lite* and *Littlet-Lite* miniature illuminated push-button switches.

SERVICE AIDS

- 25X. **CASTLE**—Leaflet describing fast over-

haul service on television tuners of all makes and models; also illustrated lists of universal and original-equipment tuners. See ad page 43.

- 26X. **ELECTRONIC CHEMICAL**—Catalog and brochure listing electronic-chemical line, including formula EC-44 for cleaning and lubricating contacts.  
 27X. **GC ELECTRONICS**—48-page new-products supplement FR-62-S for general catalog FR-62; lists replacement antennas, test equipment, and service aids. See ad page 49.  
 28X. **PRECISION TUNER**—Information on repair and alignment service for any TV tuner. See ad page 62.  
 29X. **STANDARD KOLLSMAN**—Catalog sheet on UHF converters.

SPECIAL EQUIPMENT & SERVICES

- 30X. **ACME**—Specifications and applications for control-type magnetic amplifiers with capacities from 5-1000 watts and voltage ranges from 24-160 volts. See ad page 82.  
 31X. **ATR**—Literature on 1963 *Karadions*, including tube-equipped and transistorized versions. All sets available as "universal" or "customized." See ad page 14.  
 32X. **GREYHOUND**—Complete information on Greyhound Package Express, including rates and routes. See ad page 47.  
 33X. **TERADO**—Catalog sheet 5999 describing complete line of converters, battery chargers, and relays. See ad page 90.  
 34X. **VOLKSWAGEN**—60-page illustrated booklet, "The Owner's Viewpoint," describing how various business enterprises use VW trucks; complete specifications on truck line. See ad page 65.

TECHNICAL PUBLICATIONS

- 35X. **CLEVELAND INSTITUTE OF ELECTRONICS**—"Pocket Electronics Data Guides" with conversion factors, formulas, tables, and color codes. Also, folder "Choose Your Career In Electronics" describing home-study electronics training programs, including FCC-license preparation. See ad page 95.  
 36X. **HOWARD W. SAMS**—Literature describing all current publications on radio, TV, communications, audio/hi-fi, and industrial electronics, including Fall-Winter 1962 Book Catalog and descriptive flyer on 1962 *Test Equipment Annual*. See ads pages 70, 75, 94.

TEST EQUIPMENT

- 37X. **B & K**—Catalog AP20-R, giving data and information on Model 850 *Color Analyst*, Model 960 *Transistor Radio Analyst*, Model 1076 *Television Analyst*, *Dynamac* 375 VTVM, *V-O-Matic* 360, Model 625 *Dyna-Tester*, Models 600 and 700 *Dyna-Quik* tube testers, Model 420 and 440 CRT Tester-Reactivators, and Model 1070 *Dyna-Sweep* Circuit Analyzer. See ads pages 45, 46, 55, 56, 57, 61, 73.  
 38X. **HICKOK**—Information about specifications of new Model 677 Wide Band Oscilloscope; also "Scope Facts." See ad page 67.  
 39X. **KARG**—Data sheet and instruction booklet for MX-1G Stereo Multiplex Signal Generator; also "Alignment and Adjustment of Stereo FM Tuners And Adapters." See ad page 68.  
 40X. **MERCURY**—8-page catalog of tube testers, component substitutors, CRT tester, and other service test equipment. See ad page 85.  
 42X. **SECO**—Complete information on three new 0-30 volt power supplies, all featuring transistor-regulated voltage. See ad page 15.  
 43X. **SENCORE**—Brochure answering questions about SENCORE color test equipment. See ads pages 22-23, 89.  
 44X. **TRIPLETT**—Catalog 44-T containing specifications of new test equipment. See ad pages 1-2.

TOOLS

- 45X. **BERNS**—Data on 3-in-1 picture tube repair tools, on *Audio Pin-Plug Crimper* that lets you make pin-plug and ground connections for shielded cable without soldering, and on ION adjustable "beam bender." See ad page 58.  
 46X. **EVERSOLE**—Description and price list of *DeSod* desoldering tools for use on printed-circuit boards, including new tip for compactron sockets. See ad page 60.  
 47X. **XCELITE**—Bulletin P562 describing "Service Master" 99SM and other electronics service kits containing interchangeable handles, nutdriver and screwdriver blades, pliers, and wrenches.



TUBES & TRANSISTORS

- 48X. **ADMIRAL**—Wall-chart "Picture Tube Substitution Guide" for tube sizes ranging from 7" to 27".  
 49X. **AMPEREX**—33-page catalog with numerical index, descriptions, and basic specifications on tube line.  
 50X. **SYLVANIA**—Specifications and characteristics of NPN large-signal silicon epitaxial mesa transistors.



JACKSON MODEL 648					JACKSON MODEL 658				
Tube Type	Fil. D.	E.	Plate Test	Tube Type	Sec.	Heater H-K	Circuit P-G	Plate Grid Test	Heater Current
6DL4	6.3 A125	AC47	42V	6DL4	T	6.4J 125	ac47 25R	6WY*	
6FM7*	6.3 C6	AC79	19XZ	6FM7*	T	6.4K C6	ac78 15Q	10XY*	
		Nor-S switch in S position			T	" C5	ac90 17R	70VY*	
		CS AC89	35VW						
6FY7*	6.3 AC5	AC29	43VW	6FY7*	T	6.4L C5	ac29 20R	70VY*	
		AC6 AC79	59XZ		T	" C6	ac78 20Q	10XY*	
		Nor-S switch in S position							
6HE5*	6.3 AC3	B124	31W	6HE5*	P	6.4L C3	B124 24Q	85VY*	
8106	Set line to 80% mark 12.6 A125	C349	28V	8106	P	13.6M 125	c349 30R	25VY*	
JACKSON MODEL 598									
Tube Type	A.	B.	C.	Fil. Cont.	D.	E.	F.	G.	
6DL4	6.3	4Y2	3679	5	8	1		55	
8106	Set line to 75% mark 12.6	4	8	5	1	7	2	44	

# LET RCA PUT YOU IN THE COLOR PICTURE

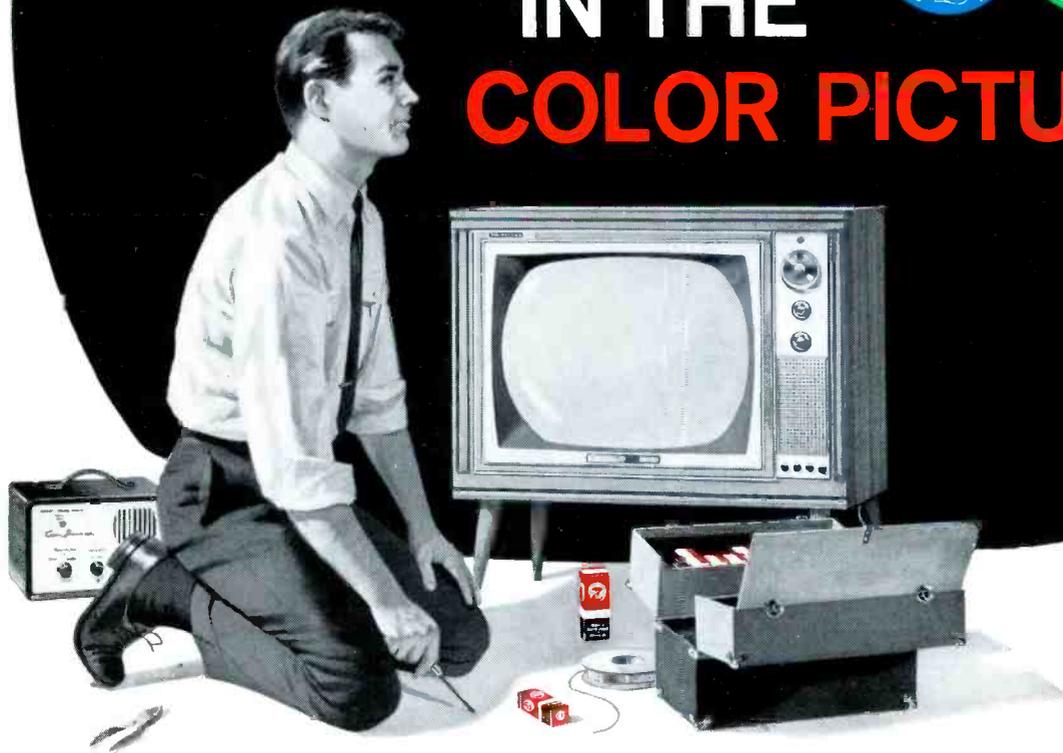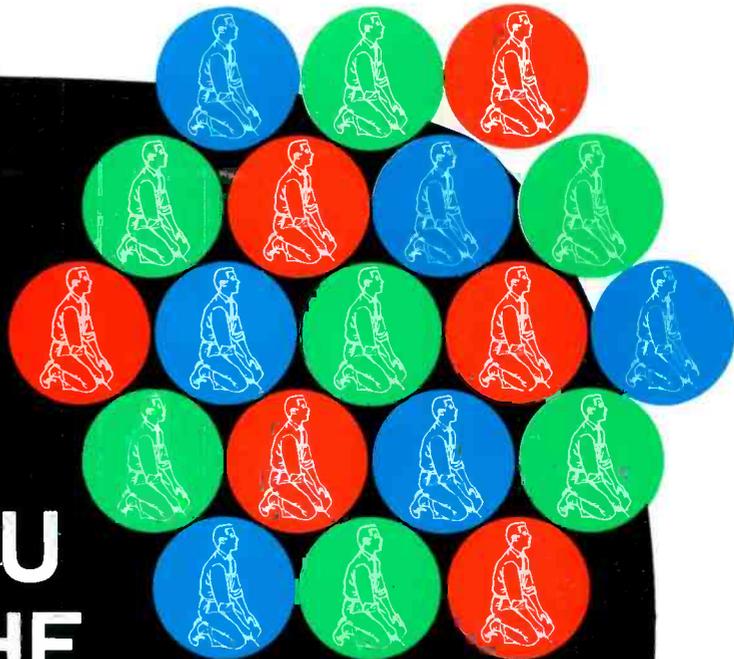

## Get the All-New RCA Institutes Color TV Home Study Course **FREE** with Your Purchases of Dependable RCA Receiving Tubes

Make no mistake about it: the future of electronic servicing is in Color TV! ... And here's how RCA—pioneer of the compatible Color TV system in use today—can put you in the color picture.

The RCA Electron Tube Division offers you the RCA Institutes brand-new, completely up-dated Color TV Home Study Course FREE with your purchases of RCA entertainment receiving tubes. This practical course, filled with the latest up-to-the-minute information, will help equip you to troubleshoot and repair all modern color receivers regardless of brand.

Because Color TV is already such big business (approaching \$300 million a year), this course can start making money for you as soon as you complete it—and for many years to come. Don't miss this major opportunity for a more profitable future. Ask your participating Authorized RCA Tube Distributor for full details right away.

### WHAT YOU GET

**4 Study Groups, 8 Graded Lessons.** This is an all-new course, never before offered. Covers the most modern Color TV circuits. Even if you've taken a previous color course you'll still benefit from this one.

**Handsome, durable 3-ring binder** to keep all lessons and examinations in a permanent reference file.

**RCA Institutes Color TV Graduation Certificate** on completion of course—plus all regular RCA Institutes educational services to students. Graded examinations on every lesson.



The Most Trusted Name in Television

RCA ELECTRON TUBE DIVISION, HARRISON, N. J.

# FASTER THAN A SHORT CIRCUIT



## SUB-MINIATURE MICROFUSES

and microfuse holders  
for internal connection  
and panel mounting.

1/500 AMP. thru 5 AMPS.

@ 125 volts. Will  
interrupt 10,000 AMPS.  
DC short circuit.



## 8AG INSTRUMENT FUSES

1/500 AMP. thru 5 AMPS.

For instrument and meter protection, Littelfuse  
pioneered the design and  
development of reliable fast-acting fuses.

# LITTELFUSE

Des Plaines, Illinois