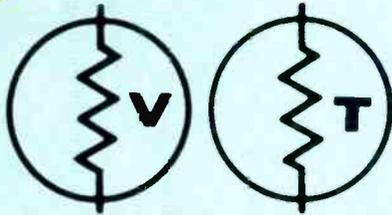





Electronic Servicing

TESTING and CIRCUIT OPERATION of:




Varistors and Thermistors,
page 14

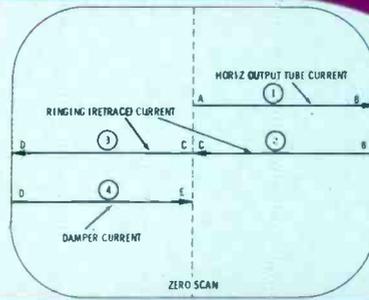

Horizontal Sweep,
page 36

Auto Cassette Drive Systems,
page 44

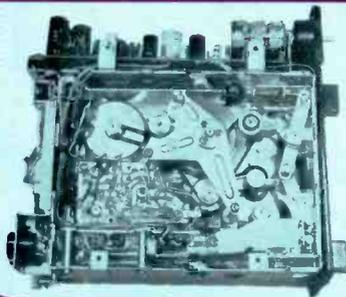

TV Varactor-Equipped Tuners,
page 26



SOURCE GUIDE TO IMPORTED PRODUCTS, page 50

EST-0010 N 10 1971 48
NORMAN C. RIEDEL
9111 SHEA AVE.
GREEN BAY WISC 54303

“I put a radio in a racing car for a Yellow Pages customer!”

“I don't think he turns it on when he's racing, but I guess he uses his racer around town,” says Stephen Nyikos, owner of Ra-dis-co, Inc., Indianapolis Indiana. “He found me in the Yellow Pages, where a lot of my customers do. I've been advertising with the Yellow Pages for about thirty years now, and it sure pays off. It's a constant reminder to past customers, and it's a great way to get new customers. I advertise in three local



directories, and I take full advantage of the multiple listings. So no matter where a customer looks for me, he's bound to find me.”

Let the Yellow Pages do your talking. People will listen.



An effective way to build business.

Electronic Servicing

in this issue...

SERVICING TECHNIQUES (GENERAL)

14 Varistors and Thermistors—Operation and Testing—How these voltage- and temperature-sensitive resistors function and typical circuitry they are used in, plus practical methods for testing them (Troubleshooter/Carl Babcoke).

COLOR TV

26 Varactor Tuners—Operation and Servicing—How RCA's and Sylvania's switchless VHF and UHF tuners function, plus general servicing techniques (Bruce Anderson/ES Contributing Author).

SHOP MANAGEMENT

32 Business Management Checklist—A listing and discussion of the prime elements of the seven major areas of management skills. See how your management IQ measures up (Better Management Guides/Robert G. Amick).

TELEVISION

36 Horizontal Sweep—Operation and Troubleshooting—First of a two-part series which explains in detail how horizontal scan is produced and provides general and specific troubleshooting procedures (Shop Talk/Carl Babcoke).

AUTO ELECTRONICS

44 Auto Casette Players—Drive Systems and Related Common Troubles—Thorough but concise descriptions of the drive and eject mechanisms, and causes and cures of the most frequently encountered troubles (Carr Electronics/Joseph J. Carr).

GUIDES

50 Source Guide To Imported Consumer Electronic Products—A cross reference of brand names to importers, distributors and/or manufacturers. Over 650 brand names of foreign-made sets are listed in this updated and expanded edition of an ES annual feature.

DEPARTMENTS

Electronic Scanner	4	Audio Systems Report	42
Symcure	10	Product Report	64
Service Bulletin	12	Catalog and Literature	66
Test Equipment Report	22	The Marketplace	70
		Advertisers' Index	70

Second class postage paid at Kansas City, Mo. and additional mailing offices. Published monthly by INTERTEC PUBLISHING CORP., 1014 Wyandotte St., Kansas City, Mo. 64105. Vol. 21, No. 11. Subscription rate \$5 per year in U.S., its possessions and Canada; other countries \$6 per year.

Copyright, 1971, Howard W. Sams & Co., Inc. All rights Reserved. Material may not be reproduced or photocopied in any form without written permission of publisher.

EDITORIAL
GEO. H. SEFEROVICH, Director
J. W. PHIPPS, Managing Editor
CARL BABCOKE, Technical Editor
BARBARA L. BORDERS, Editorial Assistant
DUDLEY ROSE, Art Director

CONTRIBUTING AUTHORS

Bruce Anderson
Joseph J. Carr

TECHNICAL CONSULTANT

JOE A. GROVES

EDITORIAL ADVISORY BOARD

LES NELSON, Chairman
Howard W. Sams & Co., Indianapolis

CIRCULATION

EVELYN ROGERS, Manager

ADVERTISING SALES

Kansas City, Missouri 64105
Tele: 913/888-4664
E. P. LANGAN, Director
R. JACK HANCOCK, Manager
JAKE STOCKWELL
MIKE KREITER
JOAN HIRES, Production

REGIONAL ADVERTISING SALES OFFICES

Indianapolis, Indiana 46280

ROY HENRY
2469 E. 98th St.
Tele: 317/846-7026

New York, New York 10019

CHARLES C. HORNER
3 W. 57th St.
Tele: 212/688-6350

Los Angeles, California 90005

JOHN D. GILLIES
3600 Wilshire Blvd., Suite 1510
Tele: 213/383-1552

London W. C. 2, England

JOHN ASHCRAFT & CO.
12 Bear Street
Leicester Square
Tele: 930-0525

Amsterdam C. Holland

JOHN ASHCRAFT & CO.
W.J.M. Sanders, Mgr.
for Benelux & Germany
Herengracht 365
Tele: 020-240908

Tokyo, Japan

INTERNATIONAL MEDIA
REPRESENTATIVES LTD.
1, Shiba-Kotohiracho, Minatoku
Tele: 502-0656



ELECTRONIC SERVICING (with which is combined PF Reporter) is published monthly by Intertec Publishing Corp., 1014 Wyandotte Street, Kansas City, Missouri 64105.

Subscription Prices: 1 year—\$5.00, 2 years—\$8.00, 3 years—\$10.00, in the U.S.A., its possessions and Canada.

All other foreign countries: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00. Single copy 75¢; back copies \$1.

Adjustment necessitated by subscription termination at single-copy rate.



Robert E. Hertel, Publisher

Intertec Publishing Corp.
Subsidiary of Howard W. Sams & Co., Inc.

Breakthrough!

The new B & K Precision 1440 General Purpose Oscilloscope breaks through with laboratory performance at a Service Technician price.

And it comes with an exclusive feature: the CALI-BRAIN system of measuring waveform voltages. Only B & K scopes have CALI-BRAIN—a real advance in TV test equipment.

Use this scope for troubleshooting in the latest Transistor & IC equipment. It has 10 MHz frequency response, 35n Sec rise time and high sensitivity. A choice of AC or DC coupled vertical amplifier for complete testing flexibility. And sweep rates from 5 Hz to 500 kHz, two TV sweep rates synchronized with built-in automatic TV sync separator. Use the 1440 as a vectorscope for color TV testing or as a general purpose instrument for TV-radio/audio testing.

The B & K Precision 1440 breaks through with greater capability, reliable, all-solid-state design, CALI-BRAIN voltage measuring. And it gives you an ease of operation you will have to see to believe... So break through to higher servicing profits today!

About the Cali-Brain® System

The CALI-BRAIN voltage measuring system increases your efficiency because it lets you examine any waveform and measure its peak-to-peak voltage without changing your test set-up. Now you can confirm the manufacturer's service data exactly—checking out typical waveforms and peak-to-peak voltage readings at various test points.

Cali-Brain® in Action

Use CALI-BRAIN when you want to measure peak-to-peak voltage of the waveform displayed on the scope screen. Here's what happens when the CALI-BRAIN switch is activated:


- The horizontal sweep collapses and the waveform under examination appears as a straight vertical line.
- A numerical indicator in the CRT bezel lights up to show the full scale voltage (including decimal point) corresponding to the Vertical Attenuator setting.



B & K Precision Model 1440
\$299⁹⁵
Probe Included

- A graduated scale on the graticule overlay is illuminated on either side of the scope screen. The scale corresponds to the full scale voltage indicator in the bezel.
- The vertical waveform line on the CRT moves to either side of the screen, to align itself with the illuminated scale.

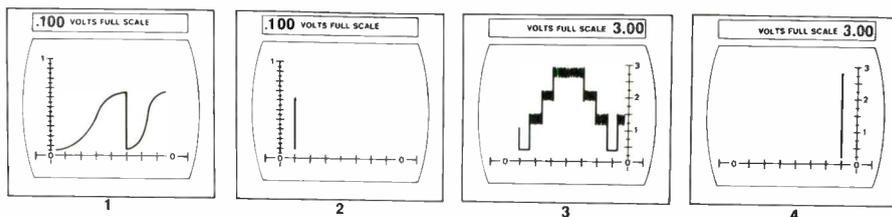The entire CALI-BRAIN action is automatic—and takes less than a second. After you have read waveform voltage, you deactivate CALI-BRAIN system with a single switch, and the waveform is again displayed. One probe and one test instrument—lets you concentrate on trouble shooting, not the test equipment!



To read peak-to-peak voltages utilizing Cali-Brain, note the full scale voltage reading in the bezel above the screen (fig. 1—.100 volts full scale) (fig. 3—3.00 volts full scale). Pull out the Cali-Brain knob and you will notice that the 1st waveform in fig. 2. reads .067 volts P-P and the second waveform in fig. 4. reads 2.95 volts P-P.

See your local distributor or write us for more information



Product of
DYNASCAN CORPORATION
1801 W. Belle Plaine • Chicago, Illinois 60613

Circle 5 on literature card

Motorola Initiates Inspection And Service Modification Of One Portable Color TV To Correct Possible Shock Hazard

Motorola has announced an inspection and modification program for one newly introduced 19-inch portable color TV model which, under certain conditions, could present a possible shock hazard. About 3,000 units are involved, with most believed to be in wholesale distributor and dealer inventory.

Owners of Motorola model WP581HW were urged by the company to immediately disconnect this color TV model and to phone the retailer from whom the product was purchased. Owners also can call the nearest Motorola distributor, whose name and location is listed in the guarantee booklet.

Or, consumers owning the model WP581HW may call collect to the headquarters of Motorola's consumer products division. The phone number is Area Code 312-451-1000. Callers should ask for

Ed Gaiden, national service manager, who will arrange for assistance in the inspection and modification of this product.

Motorola servicers, located throughout the country, will make the necessary inspection and modifications of the set. The model number "WP-581HW" can be located on the back cover of the set just under the picture tube bell, a "bulge" in the back of the cabinet. After the set has been modified and safety inspected, a large red letter "S" will be added to the model number.

Edward P. Reavey, Jr., Motorola vice president and divisional general manager, said that the task of locating any WP581HW models which have passed into consumer hands will be greatly aided by a program setup as part of the Motorola consumer satisfaction program. The safety modification program was placed into operation immediately upon discovery of the possible shock hazard. The company has a field force tracing WP-581HW models through distributor, retailer and consumer channels.

Shumavon Elected President of NATESA

Leo Shumavon, Dorchester, Mass., was elected president of the National Alliance of Television & Electronic Service Associations (NATESA), at the Association's 26th annual convention, at Hot Springs, Ark., in August. Shumavon succeeds LeRoy Ragsdale, Fort Smith, Ark.

Other officials elected included: Harold Eales, Oklahoma City, vice president; Stanley Brohn, Rouge, La., secretary-general; and Tom Easum, Memphis, Tenn., re-elected treasurer.

Frank Moch, Chicago, Ill., was reappointed executive director of the Association.

GE To End Radio Production

General Electric Company will curtail radio production by 1972, according to a report in a recent issue of *Home Furnishings Daily*.

GE, reportedly the last remaining major U.S. company manufacturing radios, presently produces radios in its Utica, New York plant.

System Developed To Provide Stereo Music Over Existing CATV Lines

A system to supply stereo music to CATV subscribers has been announced by Tape-Athon Corp. of Inglewood, California.


Initial plans, according to David Anthony, president of Tape-Athon, call for use of a signal splitter on the incoming TV line at the subscribers' residence and feeding the multiplex stereo music signal to any FM radio, FM receiver or FM hi-fi set in the home. A decoder, installed at the receiver, would unscramble the signal and permit the subscriber to select any of a number of music channels.

(Continued on page 6)

TRUE TRIGGERED SWEEP OSCILLOSCOPE/VECTORSCOPE

MODEL TO-50

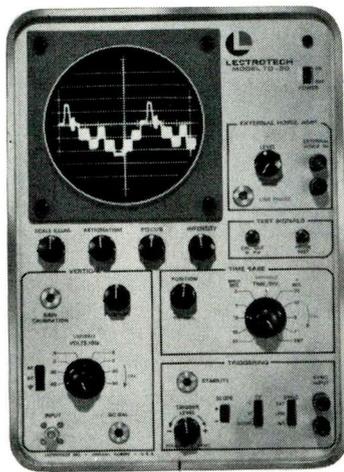- DC to 10 mhz frequency response
- .02 volt sensitivity
- Calibrated vertical attenuator
- Calibrated time base
- Supplied with combination direct/locap probe
- 5 X magnifier
- Automatic triggering mode
- 5" flat face tube edge-lit graticule




One Year Warranty \$ **339⁵⁰**
All American Made **NET**



See your distributor or write Dept. E-11
LECTROTECH, INC.
4529 N. Kedzie Ave., Chicago, Illinois 60625

Circle 6 on literature card

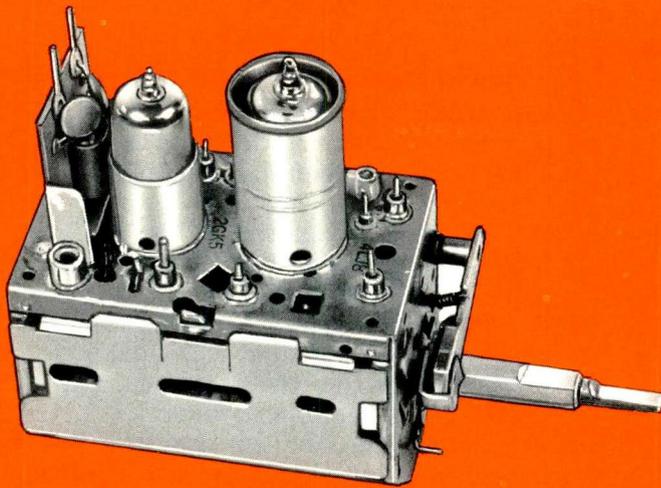

\$9⁷⁵

TUNER SERVICE CORPORATION

PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS AT ONE PRICE.

TUNER REPAIR

VHF Or UHF Any Type \$9.75.
UHF/VHF Combo \$15.00.

In this price all parts are included. Tubes, transistors, diodes, and nuvistors are charged at cost.

Fast efficient service at our 4 conveniently located service centers.

1 year guarantee backed up by the largest tuner manufacturer in the U.S.—SARKES TARZIAN INC.

All tuners are cleaned inside and out, repaired, realigned and air tested.

TUNER REPLACEMENT

Replacement Tuner \$9.75.

This price buys you a complete new tuner built specifically by SARKES TARZIAN INC. for this purpose.

The price is the same for every type of universal replacement tuner.

Specify heater type

Parallel 6.3V
Series 450 mA
Series 600 mA

All shafts have the same length of 12".

Characteristics are:

Memory Fine Tuning
UHF Plug In
Universal Mounting
Hi-Gain Lo-Noise

If you prefer we'll customize this tuner for you. The price will be \$18.25. Send in original tuner for comparison purposes to our office in INDIANAPOLIS, INDIANA.



TUNER SERVICE CORPORATION

FACTORY-SUPERVISED TUNER SERVICE

MIDWEST	817 N. PENNSYLVANIA ST., Indianapolis, Indiana	TEL: 317-632-3493
EAST	547-49 TONNELE AVE., Jersey City, New Jersey	TEL: 201-792-3730
SOUTH	938 GORDON ST., S. W., Atlanta, Georgia	TEL: 404-758-2232
SOUTH-EAST	1505 CYPRESS ST., TAMPA, FLA. 33606	TEL: 813-253-0324
WEST	SARKES TARZIAN, Inc. TUNER SERVICE DIVISION 10654 MAGNOLIA BLVD., North Hollywood, California	TEL: 213-769-2720

Circle 7 on literature card

**Sharper, brilliant
Jitter-Free intensity or
pulse markers!**




SMG-39 LECTROTECH sweeper marker generator

A precision sweeper with quality and features found only in high priced laboratory instruments. The SMG-39 utilizes post injection markers for fast, accurate alignment of any television receiver when used with any standard oscilloscope. The SMG-39 provides all needed bias' and linear sweeping signals for accurate alignment. Unique marker display enables accurate marker positioning for superior receiver alignment. VFO facility provides any additional marker from 39 MHz to 49 MHz for protection from future obsolescence, may also be used for spot alignment.


Exclusives

- Jitter-Free Intensity or Pulse Markers • VFO Variable Marker
- 4 Bias Supplies including — 67 Volts


Marker Options

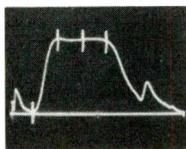

Pulse Vertical
(Overall Chroma).

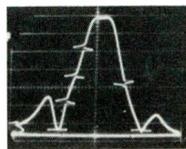

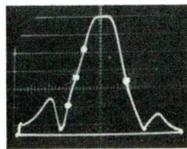Pulse Horizontal
(Typical I.F.
response).



Intensity
(Typical I.F.
response).

Benefits

- Clean, bright Jitter-Free pulse markers
- All markers of equal amplitude regardless of position on response curve.
- Adjustable marker amplitude
- Marker location accurately determined with brilliant pulse or intensity markers (a must in AFT alignment)
- All signals have blanking included for zero base line

FULL TWO YEAR PARTS WARRANTY

SMG-39

Solid state, glass epoxy circuit boards.
Complete with all cables. NET **33950**



See your distributor or write Dept. E-11
LECTROTECH, INC.

4529 N. Kedzie Ave., Chicago, Illinois 60625
Circle 8 on literature card

(Continued from page 4)

Adams Named President Of RCA Service Company

Appointment of Robert F. Adams as President of the RCA Service Company has been announced by Edgar H. Griffiths, Executive Vice President, Services, RCA.

Mr. Adams succeeds Mr. Griffiths, who has been President of the RCA Service Company for the past three years.

In his new post, Mr. Adams will direct the overall activities of the RCA service unit, which, among other services, installs and services RCA consumer electronic products.

Before his new appointment, Mr. Adams had been division vice president, Technical Products Service, RCA Service Company, since February, 1967. He joined the RCA Service Company in March 1948, and subsequently served in a series of management assignments in the consumer and commercial areas.

GE Receives NEA "Special Recognition Award"

General Electric's Television Receiver Products Department has been cited "for unselfish efforts in upgrading the Electronic Industry by supporting the National Electronic Service Conference, and much appreciated co-operation with the Country's Service Associations," by the National Electronic Associations (NEA) Inc.

The Special Recognition Award was announced at the NEA Annual Convention in Portland, Oregon, by Norris Browne, President, National Electronic Associations, Inc. Of the 24 awards made, two went to electronic companies. The awards are presented annually to individuals, organizations or firms that have provided outstanding service to the servicing industry as a whole.

Mr. Browne presented the Special Recognition Award to W. H. "Dutch" Meyer, national product service manager, Television Receiver Products Department, during the National Electronic Service Conference Meeting in Hot Springs, Arkansas, August 25th.

Improved service and product serviceability are two target areas of the television department. "Quality and reliable service is a joint responsibility of the manufacturer and the servicing industry," said Mr. Meyer. "Our aim is to take our experience and knowledge, couple it with that of the television service industry and establish systems which work."

"We are grateful to the servicing industry," Meyer said, "for its cooperation and guidance, and to the National Electronic Associations for this award. It will be a source of continuous encouragement for us. We look forward to continuing our relationship and work with the independent electronic service dealers and their associations."

This year, GE television has been working closely with the Virginia Electronics Association (VEA) of Tidewater, Virginia, an affiliate of the

(Continued on page 8)


only a BUSS fuseholder could have so many quality features squeezed into such a small package

Space Saver!



Space-saving size: projects only one inch behind panel, only 1-25/32 inches overall length

Space Saver!

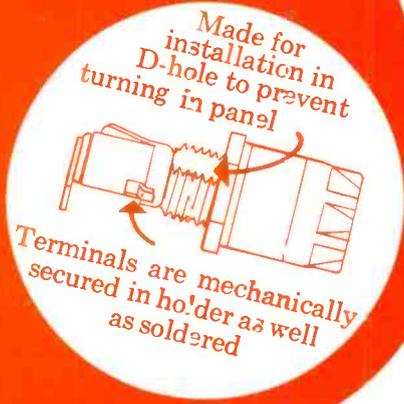

Made for installation in D-hole to prevent turning in panel
Terminals are mechanically secured in holder as well as soldered




Easy-grip bayonet-type knob - sturdy compression spring assures good contact
Knob grips fuse so that fuse is withdrawn when knob is removed

BUSS



HTA

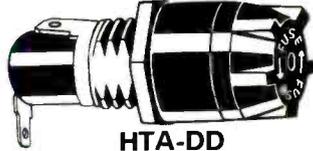

HTA-DD



HTA-HH



Knob has break-out hole to allow use of test probe



Solder Terminals (HTA)

FUSEHOLDERS

FOR 1/4 x 1/4 INCH FUSES

Rated for 15 amps at any voltage up to 250

Dielectrically capable of withstanding 1500 volts A.C. between terminals and between terminals and panel




3/16" Quick-Connect Terminals (HTA-DD)



1/4" Quick-Connect Terminals (HTA-HH)

For more information on the HTA Fuseholder and the complete BUSS QUALITY line of small dimension fuses, fuseholders, and fuse-blocks, write for BUSS Bulletin SFB.

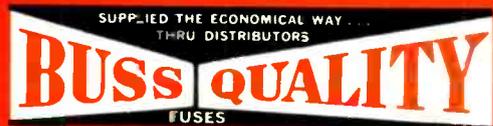BUSSMANN MFG. DIVISION,
McGraw-Edison Co., St. Louis, Mo. 63107



(Continued from page 6)

National Alliance of Television & Electronic Service Associations (NATESA). Several VEA members serve on an independent servicer panel and conduct pre-production serviceability inspections on television receivers. The nationally adopted National Electronics Associations (NEA) Serviceability Rating Form, a weighed, quantitative, measurement, is the prime evaluation tool.

General Electric television also has made moves in availability of replacement parts and communications. They are expanding their network of franchised independent parts distributors and are running tests on a new credit policy out of the Chesapeake regional parts center as well as toll-free telephone ordering systems in the Southeast.

A Guaranteed Active Parts (GAP) program also is in operation. A parts distributor and television service company can participate by stocking recommended parts which the Company guarantees they will sell. General Electric will buy the parts back if they don't.

In addition, each of the Company's districts has implemented direct-mail communication with television servicers. The goal is to get the General Electric "Television Service News" in the hands of every television company and servicer who regularly services television sets. The "Television Service News" is a free quarterly publication which provides data on parts outlets, tech-

nical publications, training and new products and tells whom to contact in any given area for assistance.

According to Meyer, these programs are "just the beginning."

Bank Interest Rates Charged Independent Business On Rise According to NFIB

Bank interest rates reported currently being paid by independent business firms continued a relaxed upward push in August, according to data compiled from the continuous field survey of the National Federation of Independent Business (NFIB).

The national average in September reportedly was 7.97 percent, up from 7.91 percent the previous month. The rate of increase apparently was dampened by the reverse trend in the Pacific Coast States which showed the average interest rate dropping from 8.56 percent the previous month to 8.4 percent, according to the NFIB.

This reportedly is not only the lowest rate shown this year in this block of states, but is also the first time in some 36 months that the average interest rate has shown a decline. In the west-south-central states centered around Texas, the average rate showed a slight gain from 7.77 percent to 7.9 percent.

The biggest increases reportedly were in the New England and mountain states. In the former, the movement upward was from 7.63 percent to 7.9 percent, and in the latter from 8.14 percent to 8.7 percent.

There reportedly appears to be some correlation between the average bank interest rate as reported by the survey respondents and the demand for bank loans. Nationally, 33 percent of the respondents report making bank loans, which is the same percentage as the previous month, but up from the 31 percent negotiating loans at mid-year. In the Pacific states where the average interest rate is shown on a downward trend, only 29 percent report that they have currently taken out loans, compared with 27 percent at midyear.

In New England, 37 percent report taking out loans as compared to 30 percent at midyear, and in the mountain states, 35 percent reported loan activity, compared to a midyear average of 32 percent.

The survey results also show variations in respect to vocations. Independent retailers, wholesalers, service firms and construction firms all show a current bank interest rate of a flat 8 percent. This reflects a slight increase for all but the construction field, in which a decline of one tenth of one percent is indicated. ▲

Change of Address

To receive Electronic Servicing at your new address, send an address label from a recent issue and your new address to:

Electronic Servicing, Circulation Dept.
1014 Wyandotte St., Kansas City, Mo. 64105

Put it to Work!

NEW AND ONLY
FROM EICO-
THE INDUSTRY'S
LOWEST-PRICED
PROFESSIONAL
FET-VM.

Model 239
\$39.95
KIT



Use the battery powered Solid State EICO 239 on your bench or in the field. Check semiconductor and vacuum tube circuits. 11 Megohm DC input impedance. Read AC rms and DC voltages in seven steps from 1 to 1000 volts on large 4 1/2" meter. Measure and read peak-to-peak AC to 2800 volts. Check resistance from 0.2Ω to 1000MΩ on seven ranges. Provides a total of 28 useful ranges on 12 accurate scales. Automatic battery check. Includes exclusive DC/AC ohms Uniprobe™. Factory Assembled, \$59.95.

FREE 32 PAGE EICO CATALOG


For latest catalog on EICO Test Instruments, Stereo, EICOCRAFT Projects, Environmental Lighting, Burglar/Fire Alarm Systems, and name of nearest EICO Distributor, check Reader Service Card or send 25¢ for First Class mail service.

EICO, 283 Malta Street, Brooklyn, N.Y. 11207



Circle 10 on literature card

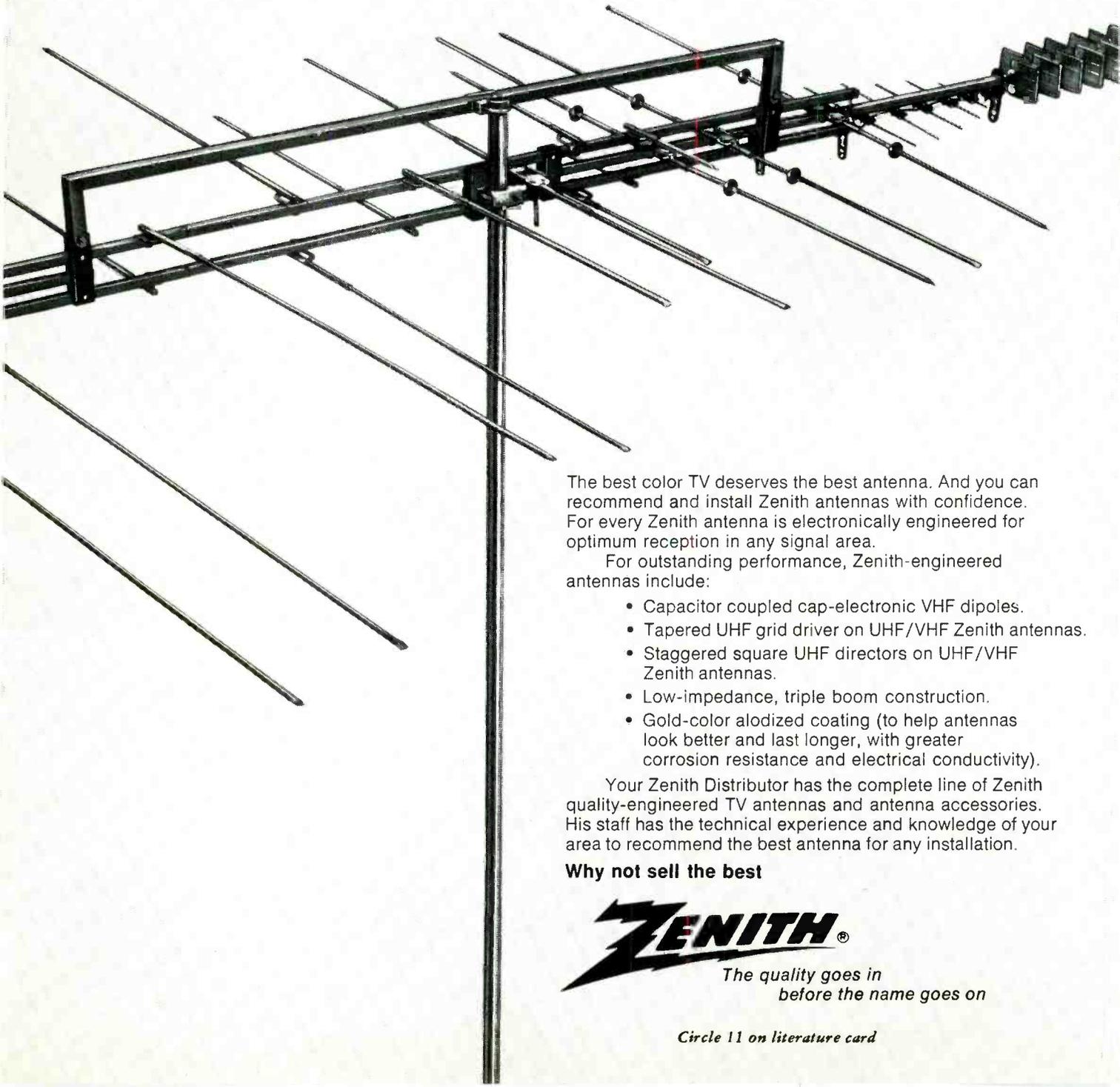Engineered for outstanding reception— Zenith outdoor antennas for Color TV!



The best color TV deserves the best antenna. And you can recommend and install Zenith antennas with confidence. For every Zenith antenna is electronically engineered for optimum reception in any signal area.

For outstanding performance, Zenith-engineered antennas include:

- Capacitor coupled cap-electronic VHF dipoles.
- Tapered UHF grid driver on UHF/VHF Zenith antennas.
- Staggered square UHF directors on UHF/VHF Zenith antennas.
- Low-impedance, triple boom construction.
- Gold-color alodized coating (to help antennas look better and last longer, with greater corrosion resistance and electrical conductivity).

Your Zenith Distributor has the complete line of Zenith quality-engineered TV antennas and antenna accessories. His staff has the technical experience and knowledge of your area to recommend the best antenna for any installation.


Why not sell the best

ZENITH®

*The quality goes in
before the name goes on*


Circle 11 on literature card

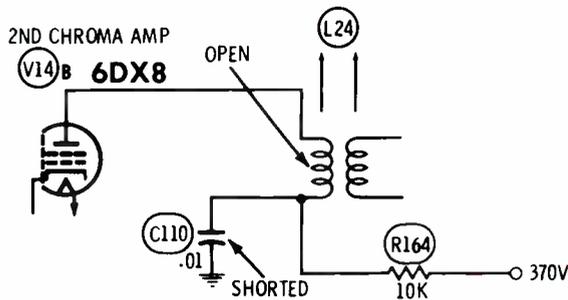Chassis—Motorola TS914
PHOTOFACT folder—798-2




Symptom—no color; no plate voltage on pin 6 of V14
Cure—check for open transformer L24 or shorted C110 and burned R164

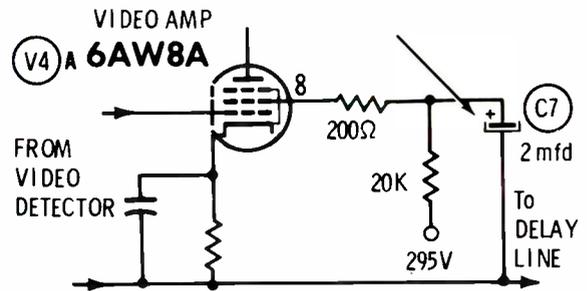Chassis—Sears 562.10130
PHOTOFACT folder—806-3




Symptom—smeared picture and poor vertical locking
Cure—test C7 by replacement; the value is not critical

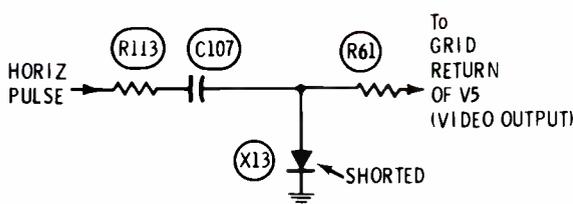Chassis—Sylvania DO6-1
PHOTOFACT folder—922-3




Symptom—black, vertical bars on left side of screen
Cure—check diode X13 and replace, if shorted

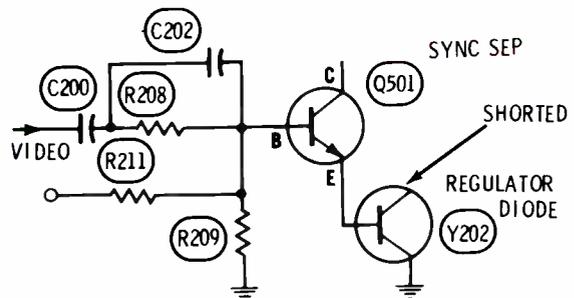Chassis—General Electric C-1
PHOTOFACT folder—1100-2




Symptom—no vertical or horizontal locking
Cure—check diode Y202 and replace, if shorted

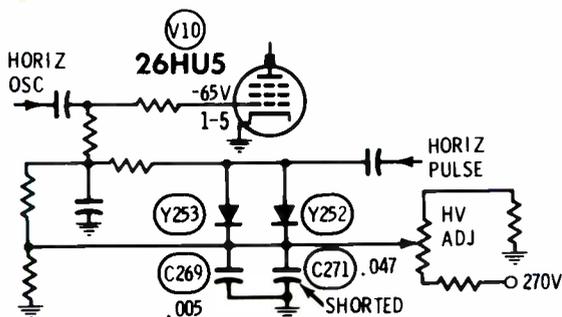Chassis—General Electric C-1
PHOTOFACT folder—1100-2




Symptom—dim raster; reduced high voltage
Cure—check C271 and replace, if shorted

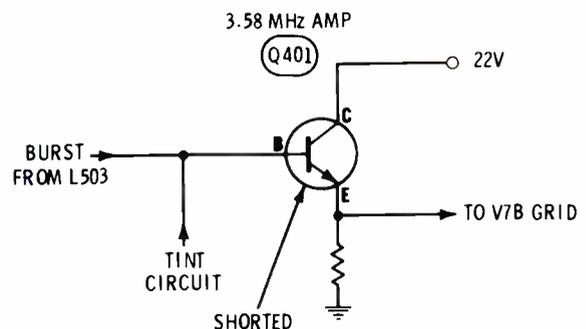Chassis—General Electric C-1
PHOTOFACT folder—1100-2



Symptom—missing or weak color
Cure—check transistor Q401 and replace, if shorted

TV TUNER SERVICE

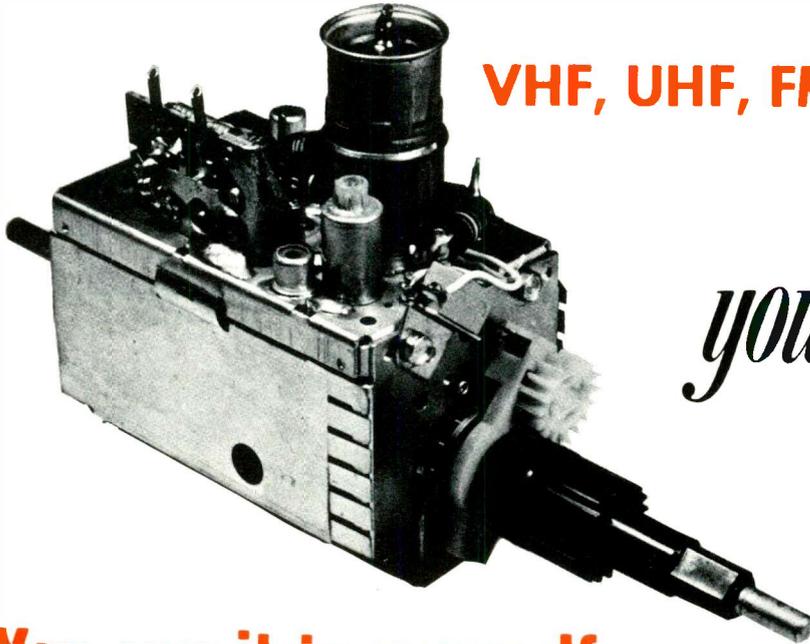

VHF, UHF, FM or IF-Subchassis. . .
 . . . All Makes

you get...


Fast 8 hr. Service!

You owe it to yourself

1 YEAR GUARANTEE

to try P.T.S. We are the fastest growing, oldest and now the largest tuner service company in the world. Here is what you get:

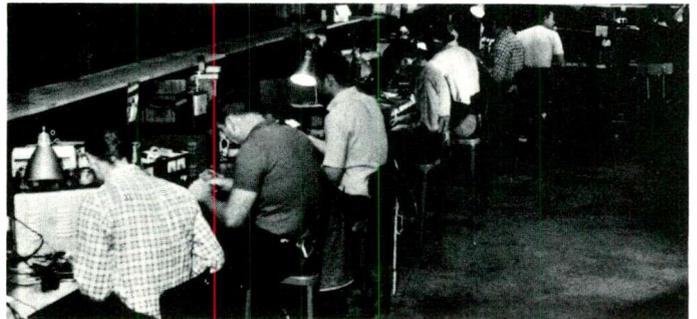1. Fastest Service — 8 hr. — in and out the same day. Overnight transit to one of our six plants, for parts, tuners or IF-modules.
2. All tuners cleaned inside and out, repaired, realigned and air tested.
3. On IF-modules all stages checked, all traps set with high calibre test equipment.
4. Fine Quality! Your customers are satisfied and you are not bothered with returning your units for rework!
5. Lower Cost! Up to \$5.50 less than other tuner companies!
6. Friendly, helpful personalized service!



FIRST TO OFFER 365-DAY GUARANTEE!
 COLOR—BLACK & WHITE—TRANSISTOR TUNERS—ALL MAKES
 GUARANTEED COLOR ALIGNMENT—NO ADDITIONAL CHARGE

We offer you finer, faster...

VHF-UHF-FM	\$ 9.95
UV-COMBO	\$16.95
IF-MODULE	\$12.50

Major Parts charged at Net Price

CUSTOMIZED REPLACEMENTS AVAILABLE
 FOR \$12.95 UP (NEW OR REBUILT)

Precision
Tuner Service



LIKE TO DO IT YOURSELF?

PTS makes all tuner parts available to you.
 Send one dollar (redeemable) for our
TUNER REPLACEMENT GUIDE AND PARTS CATALOG

- 60 pages of top information
- Blow-up of all tuners
- Largest exact tuner replacement guide
- Antenna Coil Replacement Guide
- Multi-fit Replacement Tuner Shaft Guide

For fastest service, send faulty unit with tubes, shields and all broken parts to:

PTS ELECTRONICS, INC.

HOME OFFICE—P. O. Box 272—Bloomington, Ind. 47401	Tel. 812/824-9331
EAST—P. O. Box 3189—Springfield, Mass. 01103	Tel. 413/734-2737
WEST COAST—P. O. Box 41354—Sacramento, Calif. 95841	Tel. 916/482-6220
MOUNTAIN—P. O. Box 4145—Denver, Colo. 80204	Tel. 303/244-2819
SOUTHWEST—P. O. Box 7332—Longview, Tex. 75601	Tel. 214/753-4334
SOUTHEAST—P. O. Box 6771—Jacksonville, Fla. 32205	Tel. 904/389-9952

Circle 12 on literature card

servicebulletin

a digest of info from manufacturers


New high-voltage regulator tube Magnavox T958 and T962 color TV chassis

The new 6EN4 high-voltage regulator tube is used in all productions of the T958 chassis and has been used in some of the T962 chassis.

Magnavox recommends the 6EN4 as replacement for the 6BK4/6EL4 type. However, the 6BK4/6EL4 cannot be used in any chassis designed for the newer 6EN4 tube, because the grid is brought out to a different pin. The grid of the 6BK4 is pin 5; pin 6 is used for the grid for the 6EN4. If a 6BK4/6EL4 is installed in a chassis designed for the 6EN4, the high-voltage hold-down circuit will limit the high voltage to 18KV.

Replace VDR when transistor is replaced Zenith 4B25C19 or 19CC19 TV chassis

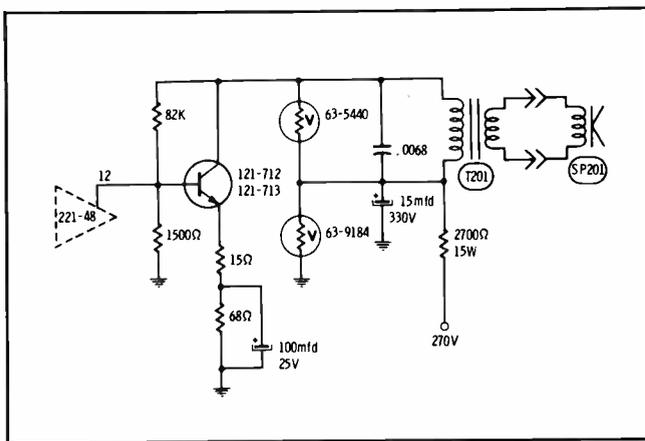If replacement of the audio output transistor is necessary, Zenith recommends that the varistor (VDR) which is in parallel with the primary of the audio-output transformer should be replaced at the same time. The transistor part number is 121-712 or 121-713, and the part number of the varistor is 63-5440.



Do not service the receiver without a speaker or a load resistor connected across the speaker output leads, because the output transistor and the varistor can be damaged by the high peak voltages which can result.

Circuit change to prevent repeated failure of power supply diodes General Electric KE color TV chassis


General Electric KE color TV chassis

Add a .001-mfd 1KV capacitor (furnished by GE with the diode) in parallel with both CR109 and CR110 power supply diodes when the diodes are replaced.

These capacitors help protect the diodes against line-voltage transients.

Design of audio-output transistors changed Zenith late-production color TV chassis

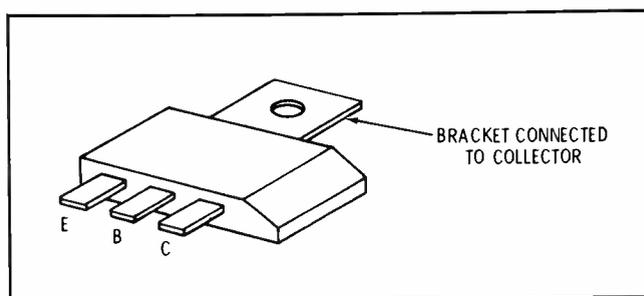
The original-equipment, matched-pair audio-output transistors used in these chassis have clips which press the transistors against an aluminum shield, for better heat dissipation.



Replacement transistors, Zenith part number 964-27986, have an adequate heat sink that is part of the transistor and is connected internally to the collector. These extruded flat brackets, projecting from the tops of replacement transistors, should NOT be clipped to the aluminum shield, because this would short the collector circuit.

Excessive brightness RCA CTC40, CTC44 or CTC47 color TV chassis

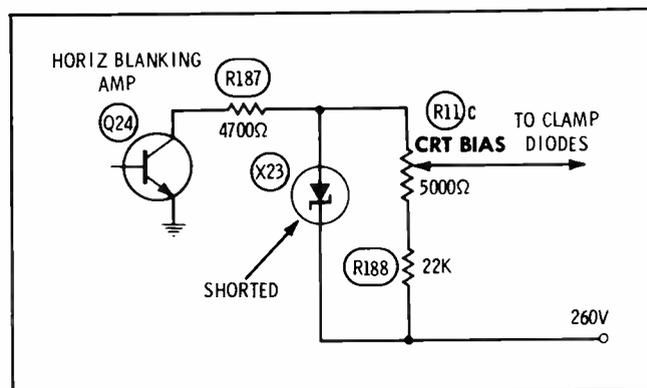Excessive brightness symptoms, such as retrace lines or screen too bright when brightness and screen controls are turned down completely, might be caused by leakage or a short in zener diode CR712 (X23 in PHOTOFAC T Folder 1111-3).



An ohmmeter test of the zener diode should be sufficient to detect such leakage. ▲

8 top guides to expert servicing— from Sams



Hi-Fi Stereo Servicing Guide

by ROBERT G. MIDDLETON. A complete guide to effective servicing of a-m tuners, fm tuners, stereo-multiplex units, and audio amplifiers (all components, except record players and tape recorders). Includes hi-fi speaker system installations, trouble localization, and overall system evaluation. Also gives testing methods for verifying performance.

Order 20785, only \$3.95

Record Changer Servicing Guide

by ROBERT G. MIDDLETON. Presents the general principles of record changer design, followed by a detailed analysis of the working parts of changer mechanisms. Explains adjustment and lubrication procedures, diagnostic techniques for operating troubles, and the corrective measures required to remedy them. This is a thoroughly practical guide.

Order 20730, only \$3.95

Radio Receiver Servicing Guide

by ROBERT G. MIDDLETON. Presents the professional technician's approach. Covers troubleshooting and repair of a-m radio receivers, both solid-state and tube type. Methods for quick localization of troubles in any circuit are explained in detail, along with the proper use of test equipment. Includes a fascinating final chapter on the restoration of antique radio receivers.

Order 20790, only \$3.95

Tape Recorder Servicing Guide

by ROBERT G. MIDDLETON. Tells how to repair tape recorders profitably. Thoroughly explains the principles and characteristics of magnetic recorder circuitry, describing the various components and systems. Provides full instructions on preventative maintenance, adjustments, and proper solutions to tape transport, recording, and reproduction troubles.

Order 20748, only \$3.95

Color TV Servicing Guide

by ROBERT G. MIDDLETON. Shows how to apply fast troubleshooting techniques to color-TV repair using the famous Middleton system based on analysis of trouble symptoms illustrated by actual full-color picture tube photos. Clearly-written text explains possible trouble causes and diagnostic procedures. Final chapter explains in detail how to use color-bar generator.

Order 20358, only \$4.25

Transistor Color-TV Servicing Guide

by ROBERT G. MIDDLETON. Clearly explains the basics of the various circuits used in transistor color-TV receivers, including the most recent developments. Shows how to apply proper troubleshooting procedures based on analysis of trouble symptoms. Includes a wealth of circuit diagrams, charts, and picture tube and waveform photographs.

Order 20693, only \$4.50

Transistor-TV Servicing Guide

by ROBERT G. MIDDLETON. Second edition. Updated to provide full information on latest circuitry and many additional new test procedures. Clearly explains general transistor circuitry and servicing techniques and then proceeds through the receiver, section by section, describing various picture and or sound trouble symptoms and their remedies.

Order 20696, only \$3.95

TV Servicing Guide

by LESLIE D. DEANE and CALVIN C. YOUNG, JR. This is the famous guide used by more than 100,000 service technicians. Shows you how to apply quick troubleshooting procedures based on analysis of trouble symptoms illustrated by picture tube photos. Fully explains possible causes for each trouble symptom and then details proper diagnostic and repair procedures.

Order 20361, only \$3.25

HOWARD W. SAMS & CO., INC.

Order from your Electronic Parts Distributor, or mail to Howard W. Sams & Co., Inc., Dept. ES-111 4300 W. 62nd St., Indianapolis, Ind. 46268.

Send books checked at right. \$_____ enclosed. (Please add sales tax where applicable.)

Send FREE 1972 Sams Book Catalog

Name _____

Address _____

City _____ State _____ Zip _____

- | | |
|--------------------------------|--------------------------------|
| <input type="checkbox"/> 20785 | <input type="checkbox"/> 20358 |
| <input type="checkbox"/> 20730 | <input type="checkbox"/> 20693 |
| <input type="checkbox"/> 20790 | <input type="checkbox"/> 20696 |
| <input type="checkbox"/> 20748 | <input type="checkbox"/> 20361 |



HOWARD W. SAMS & CO., INC.

Circle 13 on literature card

Varistors and Thermistors—Operation and Testing

by Carl Babcoke

Conventional resistors can be tested with an ohmmeter, because their values are not significantly changed by reasonable variations of applied voltages or their operating temperatures.

Other, less conventional types of resistors, such as varistors (VDR) and thermistors, are not so easily measured, because they are designed so that their values change a predictable amount when the internal temperature or the voltage applied to them is varied. A varistor is a type of resistor which is designed to change resistance when the applied voltage is changed. A thermistor is a type of resistor whose resistance varies with temperature. The symbols for varistors and thermistors are shown in Fig. 1.

Characteristics Of Varistors

Ordinary resistors have linear characteristics. If the voltage which is applied to such a resistor is doubled, the current is doubled. Application of 10 times the original voltage also causes the current to increase 10 times.

By comparison, doubling the voltage applied to a varistor, which is a nonlinear device, might cause 8 times the original current flow. To say this another way: the higher the applied voltage, the lower the resistance of a varistor. A varistor attempts to maintain a constant voltage across itself.

Testing Varistors

Varistors are manufactured in many different wattages, shapes and resistances. However, a detailed study of just one type should provide us with enough information to

guide our troubleshooting tests.

A varistor which often is teamed with a thermistor in many degaussing circuits was measured in the ELECTRONIC SERVICING laboratory. Factory ratings of the varistor were 8 volts at 15 milliamps: no resistance was specified.

Ohmmeter readings

The resistance of the varistor as read on the ohmmeter function of a VTVM depended on the scale used, because the voltage applied to the varistor was different in each case. The readings obtained are shown in Table 1, along with the voltages applied to the varistor by the VTVM on different ohmmeter scales.

According to Ohm's law, this varistor should have measured 530 ohms at 8 volts (a voltage level a VOM or VTVM cannot supply). An ohmmeter test of a varistor obviously cannot give accurate readings. And, because the characteristics of the varistor are nonlinear, the ohmmeter reading cannot be multiplied by a conversion factor to achieve better accuracy.

However, a nearly equal reading between a new varistor of the same ratings and the suspected one should serve as proof the varistor is not defective, if there are no visible signs of damage.

Voltage vs current tests

Because the varistor was rated in volts and milliamps, a graph of voltage and current seemed the best way to display these relationships, as shown in Fig. 2B. The curve on the graph appears to be exponential, and would have become more steep if the voltage had been increased.

During routine servicing, the cur-

rent through the varistor should be checked only at the **rated** voltage. One measurement is sufficient, unless you are not certain it is a varistor. In that event, the current should be measured at several levels of applied voltage, to determine if the response is linear (normal resistor) or exponential (varistor).

A graph of resistance readings

Resistance readings made with the rated voltages applied are not very practical. However, computation by Ohm's law can give us a graph of resistance readings from the voltage and current values graphed in Fig. 2. A graph produced by such computations is shown in Fig. 3.

Varistors are voltage regulators

Because an increase of voltage causes the resistance of a varistor to decrease, a varistor can be used in a voltage divider circuit as a voltage regulator. The percentage of regulation is not so high as that obtained with zener diodes, but a varistor can withstand arcs or other temporary overloads without damage.

Fig. 4 shows the voltage regulator circuit and a graph of the voltages obtained when the supply voltage was varied.

Varistor Circuits That Rectify

Under certain conditions, a varistor can be substituted for a diode in a rectifier circuit, and a positive or negative DC voltage produced.

Varistors will not rectify sine or other symmetrical waves

Fig. 5A shows the schematic of a shunt rectifier circuit. Polarity of the DC voltage at the output is **positive**, although rectifier current

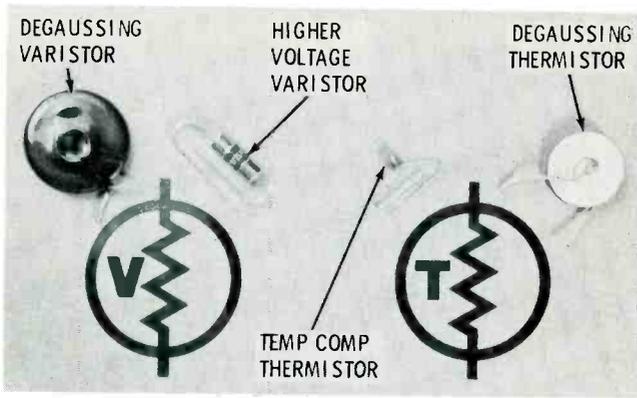


Fig. 1 Examples of varistors and thermistors and their symbols.

Table 1

X10 scale	about 10K	1.5 volts
X100 scale	10K	1.4 volts
X1000 scale	14K	.9 volt
X10K scale	20K	.26 volt

Fig. 2 One way of testing varistors is by the voltage-current method. A) Circuit used to test varistors by voltage and current. B) Parabolic graph obtained when the applied voltage and resulting current are plotted.


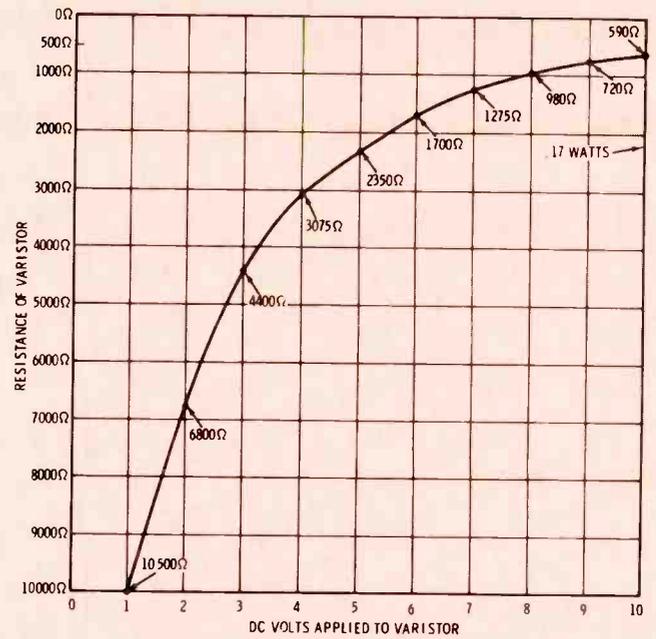
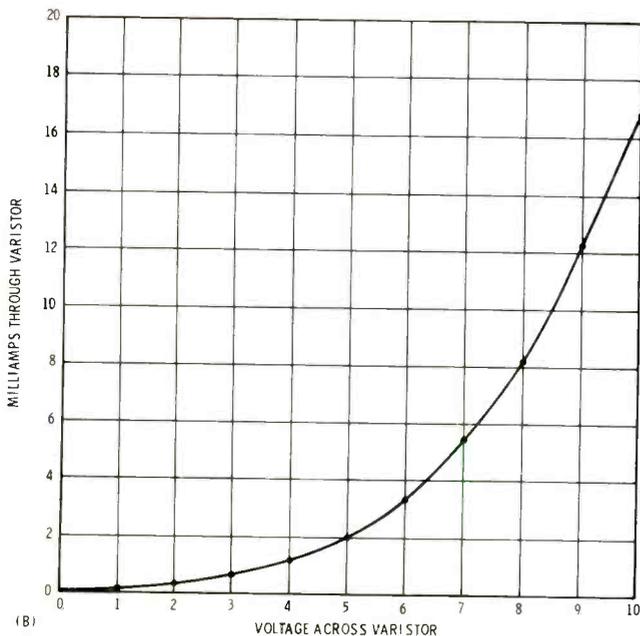
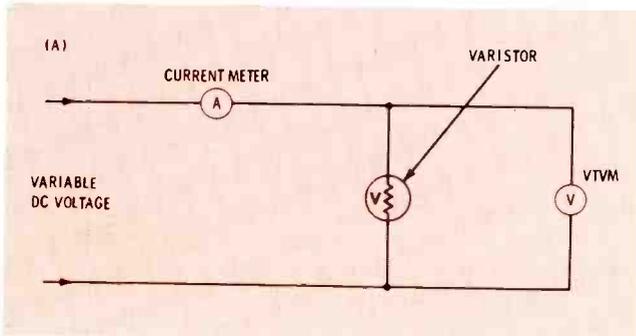
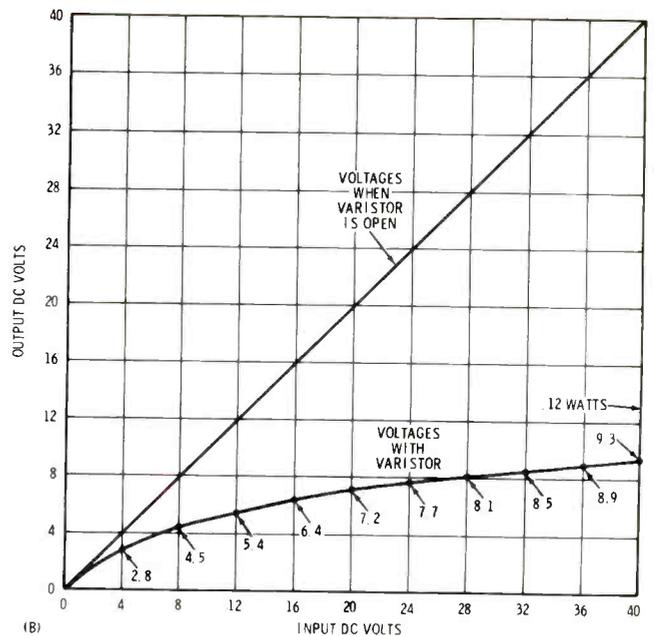


Fig. 3 A graph of applied voltage versus resistance can be computed by Ohm's law, using the values in Fig. 2.

Fig. 4 Because a varistor attempts to maintain a constant voltage across itself, it is a type of voltage regulator.

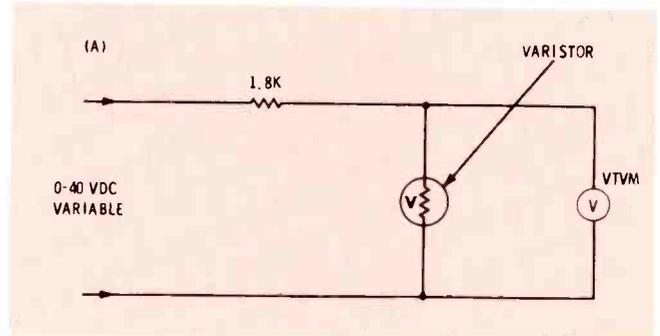

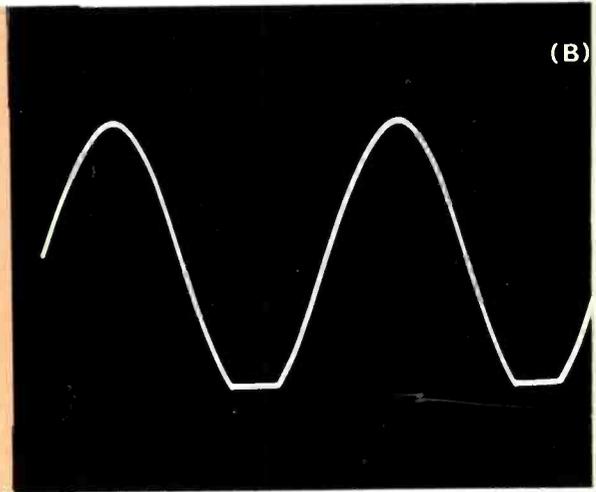
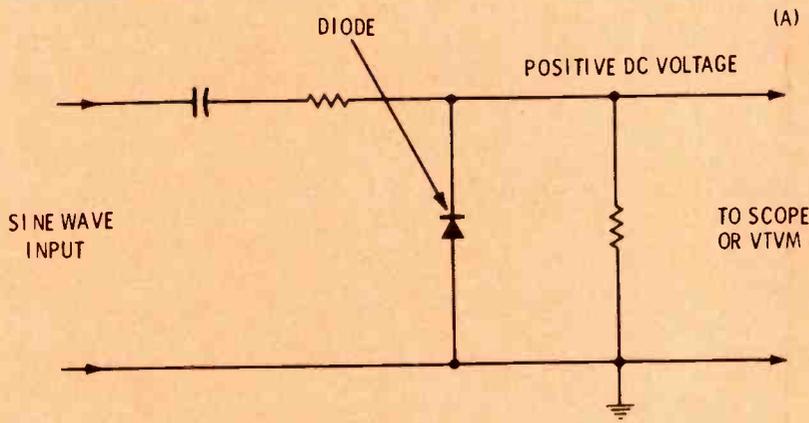


Fig. 5 Proof that a rectifier circuit in which the diode conducts during the negative-going peak of the waveform produces positive voltage. A) Circuit used for waveform and voltage measurements. B) Scope waveform showing that, because of the clipped negative peak, diode current during the negative peak produced positive DC voltage.

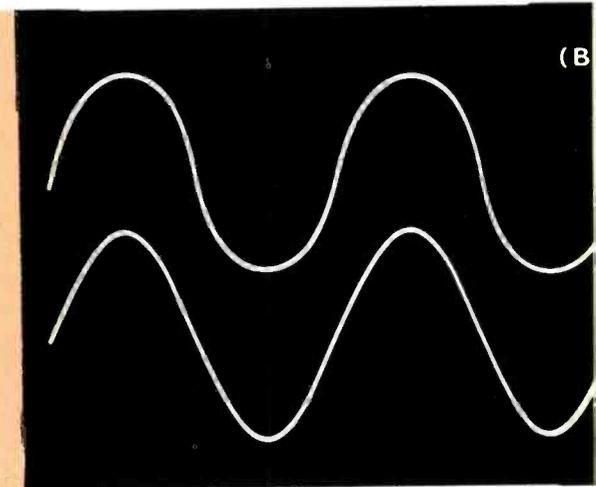
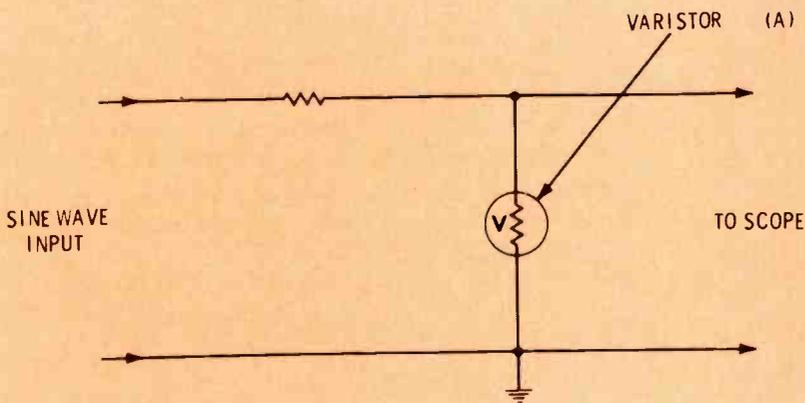


Fig. 6 A varistor passes the same amount of current whether the applied voltage is positive or negative, provided the amplitude of the applied voltage is the same. A) Circuit of a sine wave applied to a varistor. B) Bottom waveform is the input sine wave for comparison; both the positive and negative peaks of the top waveform have been rounded by varistor current. The existence of identical positive and negative alterations prove that a varistor has no diode characteristics.

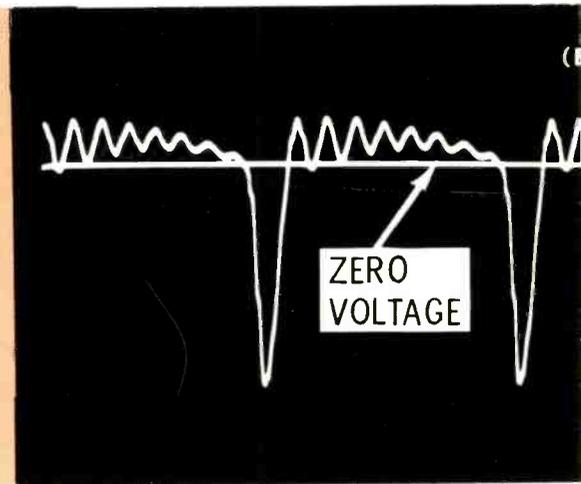
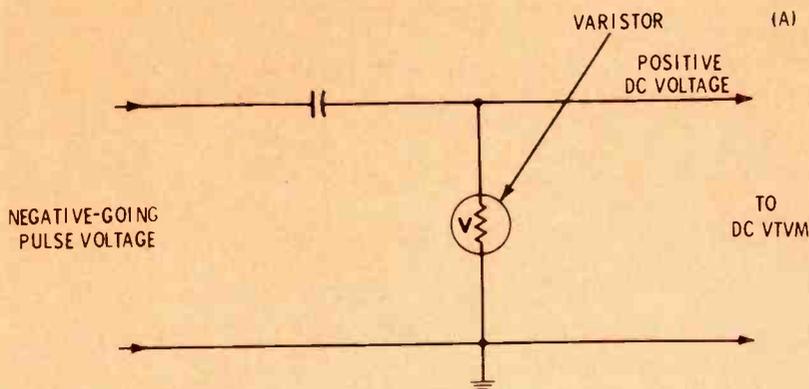


Fig. 7 DC voltage can be obtained from varistors, if the applied waveform is non-symmetrical. A) Circuit which produced the waveforms and DC voltages. B) Scope waveform of the input signal, showing the true zero voltage line. The negative-going voltage is greater than the positive-going.

occurs at the tip of the **negative** peak, as shown in Fig. 5B by the clipping of the lower tip.

We can conclude, therefore, that any similar rectifier circuit which mainly draws current from the negative tip of the input waveform will produce a positive voltage (and vice-versa). Let's sidestep this conclusion for a time and examine another characteristic of varistors.

A varistor operated in the circuit shown in Fig. 6A did **not** produce any DC voltage. The waveform across the varistor exhibited equal rounding of both the positive and negative peaks, as shown in Fig. 6B. Substitution of a coupling capacitor for the series resistor produced no DC voltage; however, the waveform tilted somewhat, the amount depending on the value of the capacitor. These experiments prove that the current through the varistor is the same for negative as for positive voltages. In other words, a varistor has no diode characteristics, and will not rectify a sine wave or any other **symmetrical** waveform.

Varistor will rectify pulses

The circuit shown in Fig. 7A is the same as that in Fig. 6A, except that the resistor in Fig. 6A was removed and a capacitor substituted. When the 24-volt PP, negative-going pulse shown in Fig. 7B was applied to the circuit, a +3.7 volts was produced at the output.

"Rectification" produced a DC voltage in this example because the input waveform was not symmetrical. We cross-switched the leads to the varistor, but the output voltage remained positive. However, when a positive-going input pulse was substituted, the output voltage was negative.

These results are proof that pulses can be "rectified" by a varistor, but further facts are needed to explain why it is true.

Across the top of the negative-going waveform shown in Fig. 7B is a line which indicates true zero voltage in a capacitance-coupled circuit. The photograph is a double exposure: first, a normal waveform picture was made when the scope was adjusted for AC input (through a coupling capacitor). Next, the scope probe was disconnected from

the rectifier circuit, and a second exposure was made on the same film, to show the true zero-voltage line.

Any varistor draws the same amount of current regardless of whether the pulse is positive or negative, provided the shape and PP amplitude are identical. When the input to the circuit was the waveform shown in Fig. 7B, the varistor drew current from both positive and negative peaks. However, because the waveform is not symmetrical—there is much more voltage below the zero-voltage line than above—the positive voltage developed by the negative-going varistor current is dominant over the lesser negative voltage produced by the smaller positive peak. The net output is a small amount of positive voltage. By way of comparison, a diode, substituted for the varistor, produced +17 volts when connected in one polarity and -2.3 volts when the connections were reversed.

Color TV Circuits Which Use A Varistor For "Rectification"

A circuit which should be familiar to many technicians is shown in Fig. 8. It is part of the vertical sweep circuit used in many RCA color receivers. (The first of these varistor-equipped circuits was introduced in 1963).

The function of the circuit is to change automatically the bias of the vertical output tube, to compensate for any small drift in the height. It is, in effect, a one-tube AGC circuit.

The varistor rectifies the huge non-symmetrical pulse coming from the plate of the vertical-output tube, producing an output of -30 volts. This negative voltage is filtered by R133 and C95 and applied to the grid of the output tube. A slightly larger positive voltage from the height control is added to the same grid. The net result is a positive voltage on the grid; however, because the cathode is even more positive, the tube normally is still held below cutoff until the application of a drive signal from the oscillator.

With this circuit arrangement, if the output tube weakens, for example, the reduction of the PP amplitude of the positive-going plate pulse causes the varistor to produce less negative voltage; consequently, the voltage on the grid of the output tube becomes more positive and the effects of the weakened tube are partially cancelled out.

The -30 volts produced by the varistor cannot be measured on a chassis that is operating normally, because it is usually cancelled out by the positive voltage from the height control. The DC voltage at


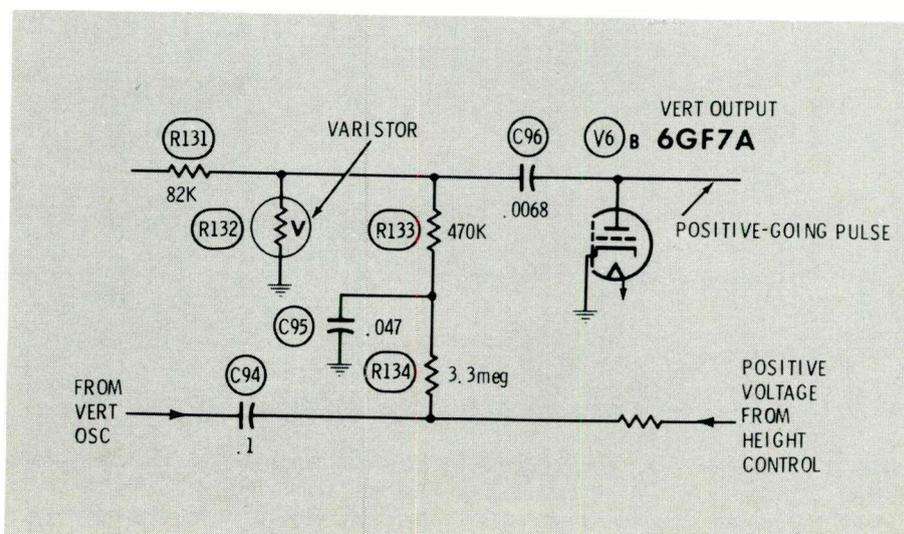


Fig. 8 Schematic of part of the vertical-output stage in the RCA CTC38A color TV chassis. The varistor "rectifies" the positive-going pulse from the plate of the output tube, producing a negative voltage, the amplitude of which varies with the amplitude of the pulse. This variable negative voltage changes the grid voltage of the output tube, to partially cancel any change in height.

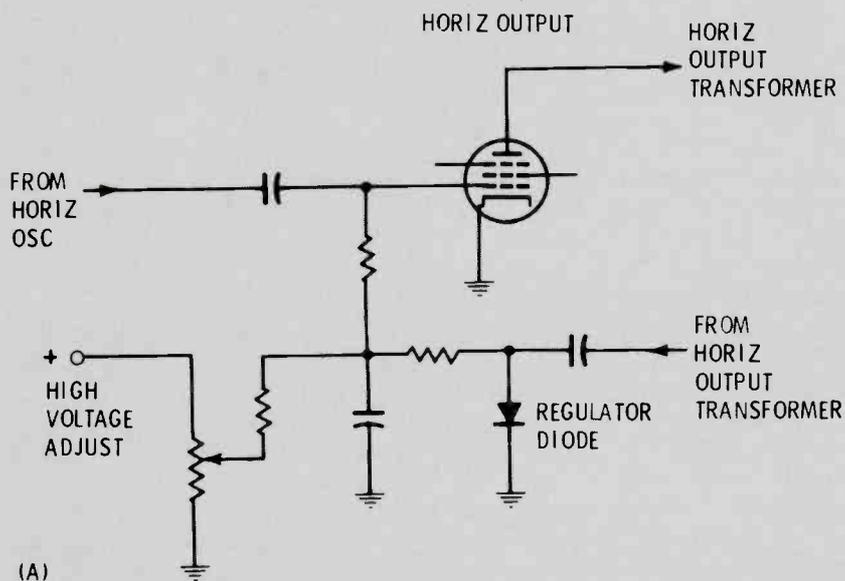

the varistor will be less positive than that found at the grid.

If you doubt that the varistor actually produces a negative voltage, just disconnect R133 from C96 and ground the loose end of R133. Then measure the voltage at the varistor. It will be negative.

An open varistor in this circuit would significantly increase the height. If you suspect that the varistor is defective, remove it and substitute a fixed resistor of about 470K. There will be no automatic height control, but the sweep should be normal otherwise.

Varistors Used in High-Voltage Regulator Circuits

Conventional high-voltage regulator circuits which vary the grid bias of the horizontal-output tube to regulate the sweep power and high voltage use a silicon diode to rectify the horizontal pulse, as shown in Fig. 9A. The negative voltage thus obtained was usually "balanced" by a positive voltage from the high-voltage adjustment control. The resultant voltage is connected to the "low" end of the grid resistor of the horizontal-output tube.

If the high voltage and pulses from the high-voltage transformer increase, the conduction of the diode also increases, producing a negative voltage, which, applied to the grid, reduces the maximum plate current of the horizontal-output tube. In this manner, the horizontal sweep power and high voltage are reduced to almost the same level that existed before the increase.

We might also call this a one-tube AGC circuit; however, the primary objective is to regulate the current (power), not the gain of the tube.

Many later chassis designs have substituted a varistor for the diode, as shown in Fig. 9B. Operation is the same except that a higher pulse is needed to produce the same amount of negative voltage. Because of the difference in pulse amplitude required, you should not substitute a varistor in a circuit originally designed for a diode, or vice versa.

Varistors are usually stable and dependable. For example, varistors are nearly immune to damage from high-voltage arcs or other transient voltages which would destroy a diode. Undoubtedly, this accounts

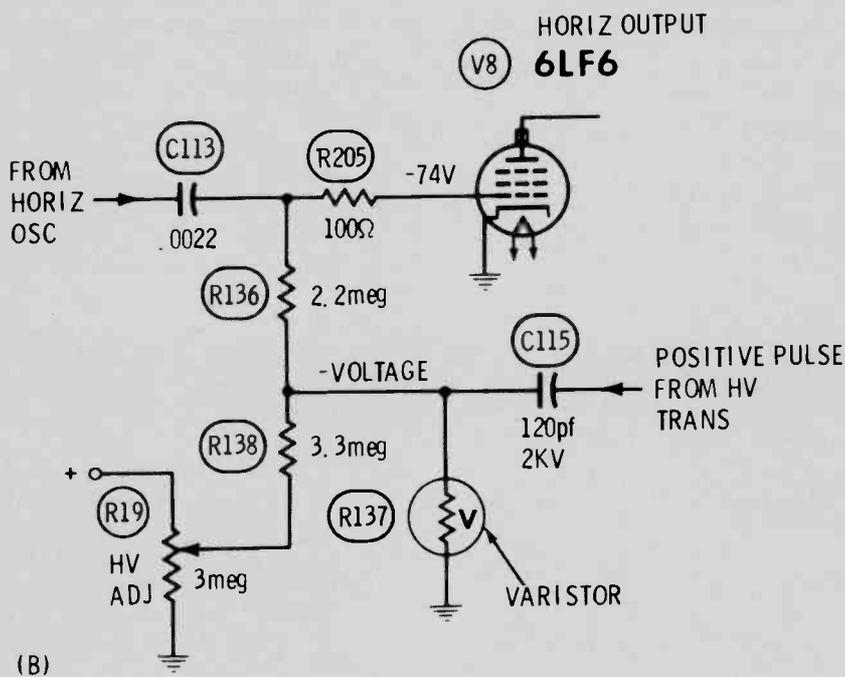


Fig. 9 A) Conventional, grid-type, high-voltage regulator system employs silicon diode. B) Schematic of the high-voltage regulator circuit in the Zenith 12A10C15 color TV chassis. The varistor "rectifies" the positive-going pulse obtained from a winding on the high-voltage transformer, producing a negative voltage which normally varies according to the amplitude of the pulse. Because voltage from the high-voltage control cancels part of the negative voltage, changes in the negative voltage become larger in proportion when the pulse increases only slightly. It also determines the maximum plate current in the output tube, which, in turn, determines the amount of width and high voltage.

Pick a present with RCA...

When you purchase RCA entertainment receiving and picture tubes from your participating RCA Distributor



15 gifts for you and your family

- | | | |
|--|------------------------------------|------------------------------------|
| 1. Bulova Digital Electric Alarm Clock | 6. Baby's Busy Box | Tiny Town Nurse Set |
| 2. Love-Me-Baby Doll | 7. Mirro-Matic Buffet Server-Fryer | Dip-A-Flower Maker |
| 3. Mighty Tonka Crane | 8. Drag Stripper Boys Bike | Easel Peg Chest |
| 4. Paint by the Number Set | (Not Shown) | Skittle Pins |
| 5. Tiny Tonka Cars | Tiny Town Doctor Set | Atlas Train Set |
| | | Mini Miss Girls Drag Stripper Bike |

Play Santa Claus with your choice of 15 name-brand high quality gifts for yourself, your home, your children, just in time for the holiday gift-giving season!

See your participating RCA tube distributor for full details. RCA/Electronic Components/Harrison, N. J. 07029



RCA



New Heathkit Digital Multimeter... lab precision for only 229.95!*

- 3½ digits for 100 uV resolution on 200 mV range, 1 V on 1000 V
- 10 voltage ranges (5 AC, 5 DC)
- 10 current ranges (5 AC, 5 DC)
- 6 resistance ranges to 20 megohm
- Furnished, assembled DC calibrator permits 0.2% accuracy DCV (can be lab calibrated to 0.1%)

A breakthrough in instrumentation! The new Heathkit IM-102 brings you a true Digital Multimeter (circuitry and readout) meeting lab-quality specs for about half the price of comparable wired DMMs. The unit accurately measures AC and DC voltages and currents, and resistance, with no need to change probes or switch meter for changes in DC polarity. It automatically displays positive or negative DC voltage and current, indicating correct amplitude and polarity. Five overlapping ranges measure voltage from 100 uV to 1000 V on DC (either polarity); 5 ranges cover 100 uV to 500 V on AC; 10 ranges measure 100 nA to 2 A on AC or DC; and 6 ranges measure resistance from 0.1 ohm to 20 megohms. Input impedance is approx. 1000 megohms on 2 V range (10 megohms on higher ranges), with overload protection on all ranges. Decimal point automatically placed with range selection. Overrange indicated by front panel light. A preassembled precision DC calibrator is furnished. And an internal circuit plus a unique transfer method provides accurate AC voltage calibration. Other deluxe features included at this low price are: all solid-state design with cold cathode readout tubes and a "memory" circuit to assure stable, non-blinking operation; detachable 3-wire line cord (no batteries needed); dual primary power transformer; isolated floating ground; aluminum cabinet with die-cast zinc front panel and tinted window. Standard banana jack connectors and test leads included. Kit assembles in about 10 hours. For lab spec. performance at half the cost...order your IM-102 today!

Kit IM-102, 9 lbs. 229.95*

Kit ID-1041, 30 kV high-voltage probe, 1 lb. 6.95*



**FREE
1972
Heathkit
Catalog.
Over
300 kits!**

HEATH COMPANY, Dept. 25-11
Benton Harbor, Michigan 49022

- Please send FREE Heathkit Catalog.
 Enclosed is \$_____, plus shipping.
 Please send model(s)_____

Name _____
 Address _____
 City _____ State _____ Zip _____

Prices & specifications subject to change without notice.
 *Mail order prices; F.O.B. factory. TE-251

HEATHKIT
Schlumberger

Circle 15 on literature card

for their increased use in circuits in which a diode previously has been used.

Testing Thermistors


The resistance of a thermistor changes according to the internal temperature. The resistance of most of those used in TV or stereo products decreases when the temperature is increased (negative temperature coefficient).

Although thermistors in fragile glass "beads" are used in electronic thermometers, the thermistors found in home entertainment products are usually more rugged and their performance less critical. Therefore, a satisfactory test of a thermistor can be obtained by merely checking, at two or three easily duplicated temperatures, the resistance as measured on an ohmmeter.

For example, one small thermistor is factory rated at 270 ohms @ 25 degrees Centigrade (77 degrees Fahrenheit) and 39.7 ohms @ 75 degrees Centigrade (167 degrees Fahrenheit). (To change Centigrade readings to Fahrenheit, multiply by 9/5 and add 32.) At a room temperature of approximately 73 degrees Fahrenheit, the resistance measured 250 ohms. When the thermistor was squeezed between two fingers for about a minute, the resistance decreased to 190 ohms. A small soldering iron was touched to the leads of the thermistor and the resistance slowly decreased to 24 ohms. At this time, the thermistor was uncomfortably hot to the touch.

Another large thermistor, designed for surge duty in series with the primary of the power transformer in a color receiver, was tested in a similar fashion. Room temperature produced a resistance reading of 76 ohms, finger heat reduced the reading to 60 ohms, and heating the leads with a soldering iron decreased the resistance to 1.6 ohms, which is approximately the "hot" resistance obtained in normal use.

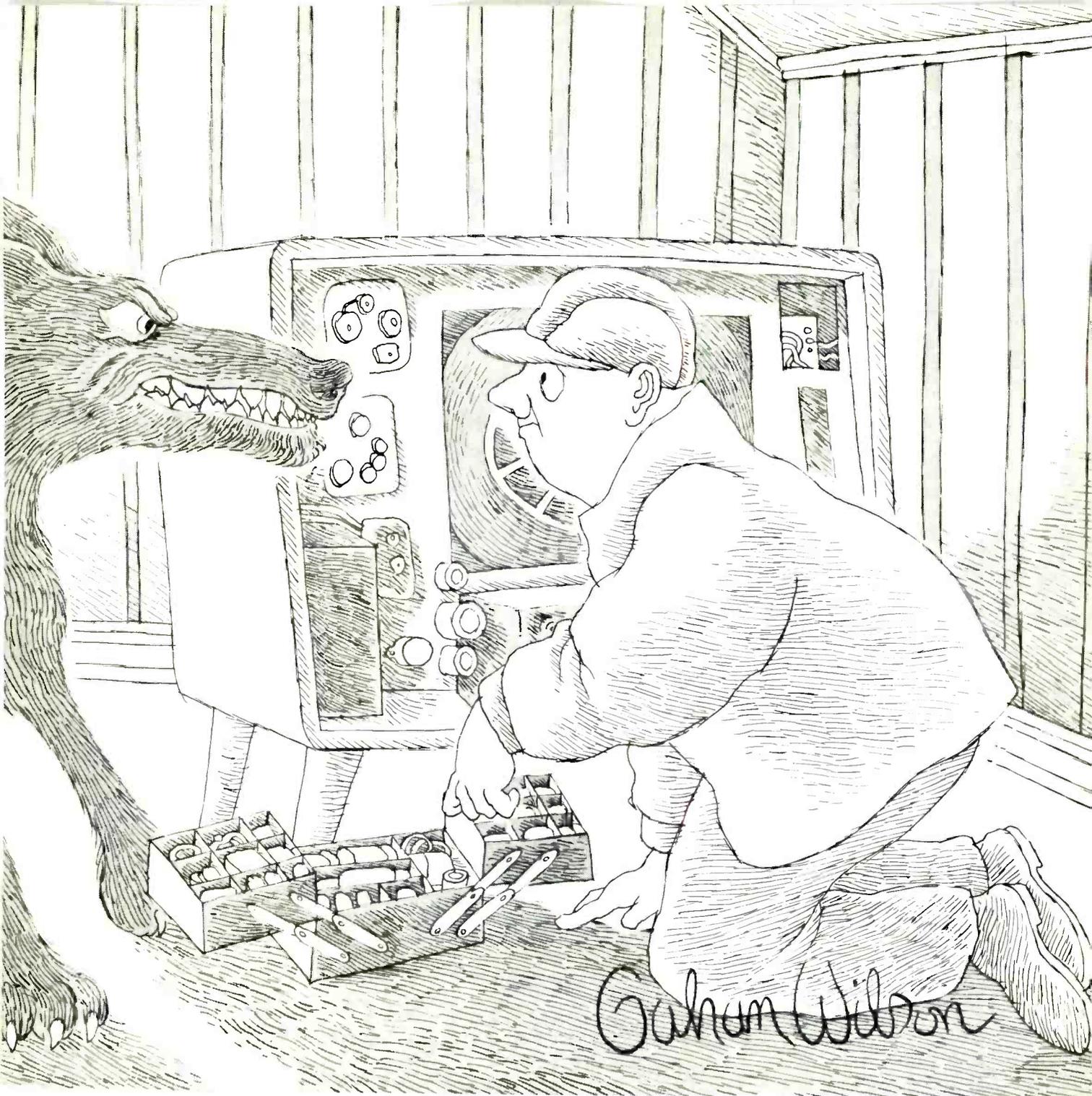The recommended ohmmeter tests using these three easily obtained temperatures are sufficiently accurate for evaluating the condition of thermistors used in television and stereo receivers. ▲



When you're in a hurry, it's nice to know GTE Sylvania has the parts.

Only 26 tubes and ECG solid-state components will solve practically all of your vertical and horizontal replacement problems.

And they're all available from your Sylvania distributor.

Because tubes are tubes, we can't promise to reduce the number you'll have to carry. But, with the Sylvania line, chances are your distributor will have the tube you need when you need it.

In semiconductors, the story is different. Just 124 ECG solid-state devices including transistors, diodes and integrated circuits will replace over 41,000 different types. In the vertical and horizontal sections alone,

only 6 ECG solid-state devices will take care of almost every job.

And they save a lot of space in your tube caddy. When your distributor is stocked with Sylvania receiving tubes and ECG semiconductors you'll have the parts you need. And you'll get them fast.

It's like having a complete warehouse built into your telephone.

And that should take some of the dog work out of your job.

GTE SYLVANIA

Circle 16 on literature card

GREAT VALUE! FROM
WORKMAN *Electronic*
 SARASOTA, FLORIDA PRODUCTS, INC.



NEW LARGE BUTTON, SAFE DIRECTION VALVE WITH EASY TUBE EXTENSION INSERTION.
NEW 8 PACKS OF 6 OZ. AEROSOL CHEMICALS WITH BOX OF 5 PRECISION TOOLS.
NEW ULTRA WISSH FORMULA FOR COLOR TV TUNERS. SAFE FOR ALL PLASTICS.

- MODEL SC6A-8 ULTRA WISSH with box of 5 precision screwdrivers
- MODEL HL6-8 LUBRITE with box of 5 precision nut drivers
- MODEL HG6A-8 MIRACLE BATH with box of 5 precision wrenches


\$8.88 PER BOX
 Dealer Net



TOOL KIT WITH EVERY 8 PACK

Circle 17 on literature card

TELEMATIC TRANSVERTER

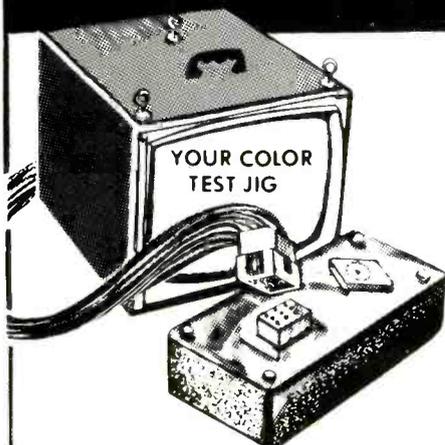

NOW!
Service Solid State Color Television
 with your own color test jig and Telematic's plug-in Transverter.

1995
 NET

Ask your distributor for information



TELEMATIC DIV., UXL CORP.
 2245 PITKIN AVE., BKLYN., N.Y. 11207

Also available a complete line of solid state yoke adaptors and cables. Buy the Transverter, and make a solid state Color Test Jig.

- Plug-in for transistor TV
- Un-plug for tube TV

Circle 18 on literature card

test equipment report

CRT Tester/Rejuvenator

A new cathode ray tube tester/rejuvenator, for checking color and b-w CRT's without removing them from the chassis, has been introduced by Leader Instruments Corp.

Model LCT-910 compares color gun emission and grid cutoff characteristics, and rejuvenates the picture tube to proper emission and brightness along with the ability to "super rejuvenate" for added tube life, according to the manufacturer. It reportedly also repairs shorts, opens and leakage between elements and will predict useful tube life via meter readings.



Other features include: continuously adjustable element voltages, for "as needed settings"; automatic rejuvenator rate control; RC timer; 0 to 40-volt heater potentials available; 117 VAC, 60-Hz operation; 4½-inch scaled meter.

The LCT-910 reportedly is self-contained in a high-impact, grained vinyl carrying case with handle. The case has 8 rubber bumpers for vertical or horizontal use.


The unit is supplied with plug-in sockets to facilitate test procedures. Size is 13 inches x 8½ inches x 5 inches and weight is approximately 12 pounds.

Price is \$129.50.

Circle 50 on literature card

25-MHz Bandwidth Oscilloscope

A new wide-band oscilloscope,

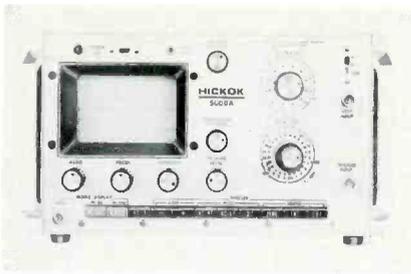

with a vertical bandwidth from DC to 25 MHz (-3 dB point), has been introduced by the Hickok Company.

Model 5000A reportedly has a built-in vertical delay line which provides 50 nanoseconds of display prior to the triggering point on the input waveform.

Specifications include: 3-percent calibrated vertical sensitivities from 10 millivolts to 50 volts per division in 1, 2, 5 sequence; input impedance of 1 megohm, 30 picofarads; overload protection up to 600 volts (300 volts for sensitive ranges); rise time of 14 nanoseconds; sweep speed from 50 nanoseconds to 2 seconds per division in a 3-percent calibrated 1, 2, 5 sequence.

The 5000A measures 6 $\frac{7}{8}$ inches x 11 $\frac{1}{4}$ inches x 19 inches and weighs 24 pounds.


The price is \$595.00.

Circle 51 on literature card

Direct-Reading Capacitance Meter

A direct-reading, portable, battery operated instrument capable of measuring capacitors with values from 2 pf to .1mf has been developed by Lateur Engineering Co.

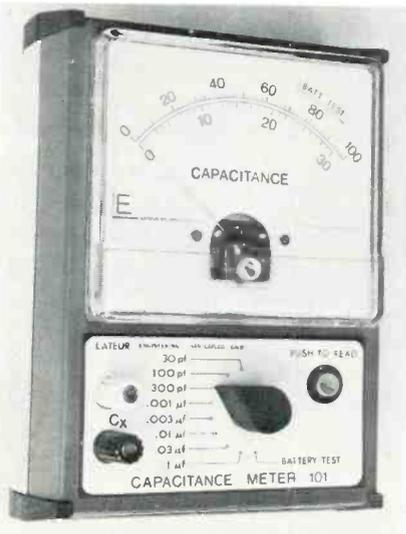Capacitance is determined by switching the unit through each of



eight ranges until a reading is indicated on the meter.

Model 101 is 5 inches x 7 inches x 2 inches and weighs 1 $\frac{3}{4}$ pounds. Price of the unit is \$94.50.

Circle 52 on literature card

Adapter Converts VOM To Transistor/Diode Tester

An adapter which reportedly converts any VOM into an in- or out-of-circuit transistor and diode tester has been announced by Coletronics.

Model TRA-1 Adapter reportedly permits measurement and/or detection of shorts, leakage, opens



and beta of both high- and low-power PNP and NPN transistors, and open and shorts and forward and reverse currents of diodes. A switching system reportedly eliminates the need for transferring of leads during front-to-back resistance measurements of diodes.

(Continued on page 24)

FOR THE MONEY

- Discounted to provide you with a higher profit margin.
- Proven quality for better customer satisfaction.
- A complete range of popular service types readily available.

In every important way, IEC Servicemaster is number one. For complete details, contact your IEC representative today, or International Electronics Sales Corporation, Melville, N. Y. 11746. (516) 694-7700.

IEC SERVICEMASTER
INTERNATIONAL ELECTRONICS SALES CORPORATION

Circle 19 on literature card

(Continued from page 23)

The two leads of the VOM are plugged into their respective jacks on the front panel of the adapter. The results of tests are read directly from the meter of the VOM. The transistor to be tested is either plugged into a socket on the front of the adapter or three color-coded leads protruding from the front of the adapter are connected to the respective elements of the transistor or diode.

The unit operates from two "AA" batteries, which are included with it. Price is \$15.95.

Circle 53 on literature card

Wheatstone Fault Location Bridge

A new Wheatstone bridge, Model 2103, that can be used for DC resistance measurements and also for finding faults in multi-conductor cables, has been introduced by the Special Instruments & Machinery Co.

Resistances from 0.09 ohms to 110K ohms reportedly can be measured with an accuracy of 0.5%, in six ranges. Shorts between conductors and ground faults in cables with low or high resistance, as well as common ground faults of all conductors and differences between conductors can be detected and



measured with the bridge, according to the manufacturer.

The 2103 bridge is supplied with a galvanometer, battery and two cables. It has an 11-inch circular dual scale with sub-divisions from 0.9 to 11 for resistance readings and from 0 to 55 percent for fault localization.

Model 2103 weighs 2.5 pounds, and sells for \$180.00. A carrying case with cable compartment is available for \$18.00.

Circle 54 on literature card

Digital VOM

A 3½-digit digital VOM which can be used as a portable test in-




strument or can be panel-rack-mounted is being marketed by Triplet Corp.

Model 8035 features: a chopper-stabilized amplifier which provides a high input resistance of 10 megohms on all AC and DC ranges; drift-free stability circuitry; 7-bar fluorescent tube display with wide-angle viewing window; ± 1 percent, ± 2 percent, ± 25 percent accuracy on the DC voltage, AC voltage and ohmmeter ranges, respectively; frequency compensated on AC voltage range; Automatic Polarity display; 100-percent over-range (1999 counts) and out-of-range display blanking, preventing any erroneous reading. The instrument also is capable of precision measurements of AC or DC current.

The compact digital VOM weighs 4½ pounds and is 3½ inches by 8⅛ inches x 10 inches.

The readout display of Model

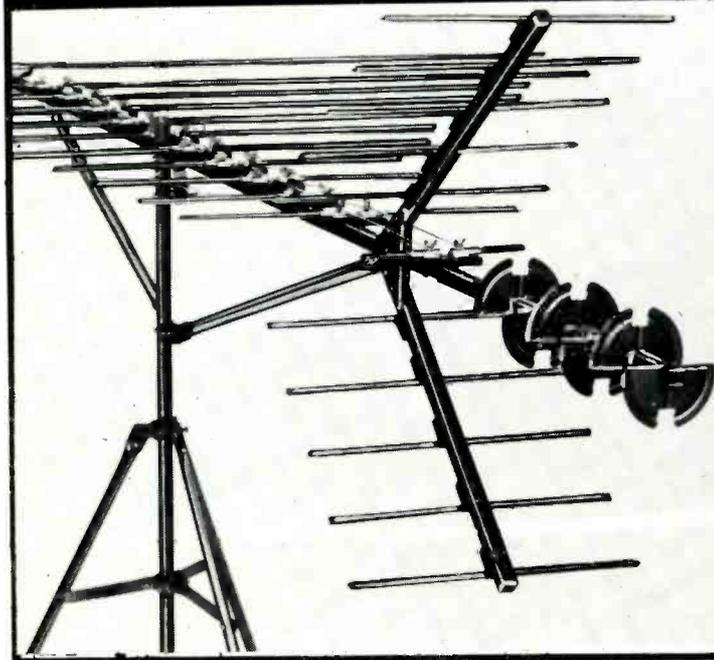RMS "STAR-TRACK"™ Antennas are breaking all sales records!



The most Advanced Space-Age VHF/UHF/FM Color Antennas ever introduced!...

- Similar design to Antennas used in Space Program.
- "Corner Reflector Driven Disc Director Array" for total UHF coverage!
- "Multiple Tuned, Cut-to-Channel VHF Elements" for total VHF-FM coverage!
- Maximum construction features for long dependable life!
- Exclusively features Reynolds Aluminum "COLORWELD" durable baked enamel Gold finish!
- Each Antenna includes famous RMS model SP-332 VHF/UHF Splitter for Single Down-Lead economical installation!
- "STAR-TRACK's" are licensed under U.S. Patent No. 3,440,658.

Write for FREE "Star-Track" Catalog -

RMS ELECTRONICS, INC.

50 Antin Place, Bronx, N.Y. 10462 • Tel. (212) 892-6700

Circle 20 on literature card

8035 consists of four plug-in, type-seven bar fluorescent display tubes; a movable decimal point; and plus/minus autopolarity symbols. A green circularly polarized window reportedly provides maximum light transmission from the display tubes while minimizing internal reflection caused by ambient light. The plug-in type readout tubes can be easily removed when maintenance is required, according to the manufacturer.

Front panel controls of the compact test instrument include a DC offset adjust and power switch, located on the lower left portion of the front panel; two input terminals, marked "Input" and "Com", which are used for all measurements; two function selector push-button switches marked DC-Ω, for DC and ohms, and the other marked AC, for AC voltage and current measurements. The range selector panel, in the upper right portion of the 8035, is suitably labeled voltage, current and ohms. A single, molded polarized plug is used for current input terminal connection.

All the electronic circuitry of the Model 8035 DVOM is designed for easy serviceability, and is mounted on one circuit board which is supported by the side panels, according to the manufacturer. The metal case of lightweight aluminum reportedly also has good electrical shielding characteristics, which permit the unit to be operated in high-noise areas.

A unique cord rack located on the rear of the digital tester provides cord storage when the instrument is being transported or not in use and also takes up cord slack when the instrument is in use.

DC Voltage Ranges are: 0-.1, 1.0, 10, 100 and 1000 VDC. Accuracy is ±.1 percent reading (RDG), ±1 Digit. Full-scale step response is 1 second nominal.

AC Voltage Ranges are: 0-.1, 1.0, 10, 100, 1000 VAC. Basic accuracy is ±.2 percent reading (RDG), ±1 digit. Full-scale response is 3 seconds.

Ohmmeter Ranges are: 100, 1K, 10K, 100K, 1 megohms and 10 megohms. Basic accuracy is ±.25 percent reading (RDG), ±1 digit.

Current AC & DC Ranges are: 100 μA, 1mA, 10mA, 100mA and 1000mA.

Basic accuracy is **DC:** ±.2 percent reading, ±1 digit.

AC: ±.5 percent reading, ±1 digit.

Full-scale response is DC, 1 second; AC, 3 seconds.

The basic measuring circuit of the new Triplet test instrument consists of a 100-millivolt, 3½-digit DC voltmeter which utilizes dual-slope integration and a chopper-stabilized amplifier to provide accuracy, long-term stability and high-input impedance, according to the manufacturer. All ranges and functions are converted to a DC

level for measurement by this circuit. All ranges are fuse protected to prevent damage from overloading.

Any measurement which produces an indication which is out of range of the unit (more than 1999 counts) will cause the three least significant digits to blank. This feature prevents erroneous readings.

The price of the Model 8035 DVOM is \$385.00. It comes equipped with test probe, two alligator clips, instruction manual and warranty. ▲

Circle 55 on literature card



CHANNELLOCK

Gives You More In Hand Tools Including

TOUGHNESS

That Stands Up
To Tough Jobs
Year After Year

You'll take pride—as do we—in the beautiful finish and fine craftsmanship of your CHANNELLOCK tools. But even more, you'll like their durability, their toughness in hard service year after year. The skilled forging of beautiful, tough, hard working hand tools has been our only business at CHANNELLOCK since 1886. Best of all, you pay no premium price for CHANNELLOCK quality. LIKE TO SEE THE ENTIRE LINE? Send for our catalog . . . yours for the asking.

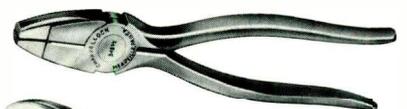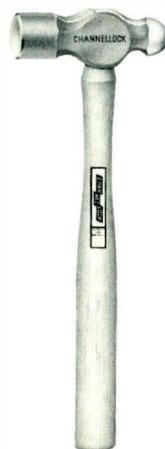

TOOLS BY
CHAN-NEL-LOCK

MEADVILLE, PA. 16335

Circle 21 on literature card

Varactor tuners—operation and servicing

by Bruce Anderson/ES Contributing Author

A look at RCA's and Sylvania's mechanicalless VHF and UHF tuners.

■ One of the more important developments in television receivers in the past couple of years is the varactor tuner. Because it is still relatively costly, compared to a standard VHF tuner, it isn't likely to take the industry by storm in the near future—no more than the transistor has completely replaced the vacuum tube. Nevertheless, at least two major US manufacturers, Sylvania and RCA, and one Canadian manufacturer, Electrohome, have introduced it in their top-of-the-line instruments.

Design and Servicing Features of the Varactor Tuner

The outstanding feature of the

varactor tuner is the absence of any mechanical tuning devices within the tuner. While this may not seem particularly spectacular, the advantages to be gained are very real.

Design advantages

From the design standpoint, the bulk of the tuner can be reduced; its life expectancy is much greater because there are no moving parts; there is no deterioration of switch contacts because there are none in the tuner (although a switch might be used externally to control it); and there is no need to locate the tuner so that its shaft can extend through the front panel of the cabinet. And, there are no reasons why this tuner can't be placed right on the circuit board along with the rest of the receiver section.

Servicing advantages

From the servicing aspect, the

absence of the wafer switches, or turret contacts, removes the need for tuner cleaning, which always has been a time-consuming job. And, because there are no internal switches, the remaining components inside the shield are more accessible than their counterparts in a standard tuner.

The RCA version, which is the only varactor tuner we have had an opportunity to work with, can be removed from the cabinet and replaced in less than five minutes. The UHF and VHF tuners are mounted on a single metal base, and the whole assembly is attached with one screw. There are three coaxial cables to unplug, and one six-pin plug to pull—no knobs, shafts, drum indicators, etc., to fight.

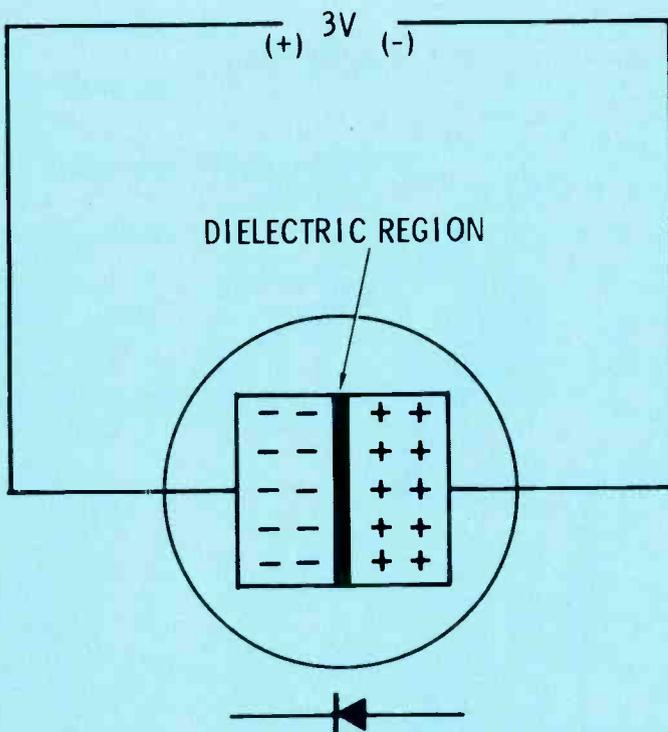


Fig. 1 Varactor diode with moderate reverse bias.

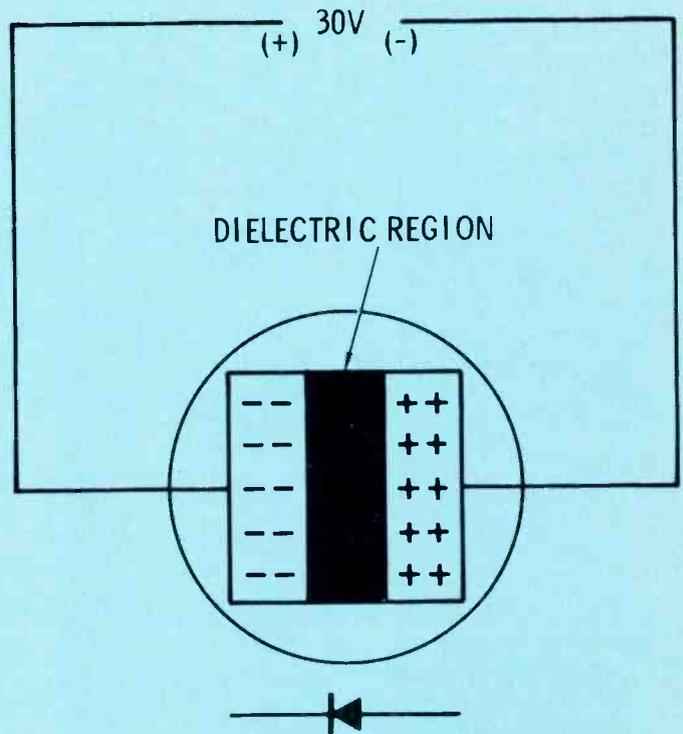


Fig. 2 Varactor diode with high reverse bias.

Varactors and Switching Diodes

In many ways, a varactor VHF television tuner is more similar to a radio tuner with bandswitching than it is to a conventional TV tuner. The bandswitching is used to select electronically either the high band or the low band; within each band, tuning is continuous. The actual tuning is accomplished by varying the capacitance of the resonant circuits; but the conventional variable capacitor has been replaced by an electronic device called a **varactor**, a word coined from **variable reactor**.

How a varactor functions

In essence, a varactor is simply a reverse-biased, solid-state diode. Most "garden variety" diodes will exhibit the characteristic, although diodes used for this purpose are specially designed, for optimum operation.

Fig. 1 illustrates the conditions within a solid-state diode when it is reverse biased by a moderate voltage—perhaps 3 or 4 volts. Because the N-type cathode material is connected to a positive source, the free electrons are attracted away from the PN junction. Likewise, the negative potential applied to the P-type anode attracts the holes (positive current carriers) away from the junction. Thus there are three distinct regions within the semiconductor material: 1) Near the cathode terminal there are many negative current carriers; 2) near the anode terminal there are many positive current carriers; and 3) near the junction of N and P material there are no carriers at all.

The effect of the conditions within the diode are similar to those within an ordinary capacitor. Because the regions of the material which are rich in current carriers are separated by a region which has no current, we have, in effect, two conductors separated by a dielectric.

Varying the capacitance of a varactor

Fig. 2 illustrates the effect of increasing the reverse bias on the diode. Because the attraction of the

carriers to the voltage sources is greater, the region around the junction, which becomes an insulator, is enlarged. In effect, the distance between the two capacitor "plates" has been increased, and the capacitance is less.

The amount of capacitance obtainable from a diode is relatively small. The capacitance produced by applying a very small reverse bias to the diode used as a varactor is somewhat less than 50 picofarads. With as much as 40 or 50 volts of reverse bias applied, the capacitance decreases to only 2 or 3 picofarads. In one tuner presently in use, the capacitance of the varactors increases from 5 picofarads with 20 volts of bias applied, to about 25 picofarads with 5 volts. In this same tuner, the range of the control, or tuning, voltage is from about 4 volts to about 20 volts. This 5:1 capacitance range is adequate to tune a resonant circuit across either the low band or the high band of the VHF television spectrum.

Bandswitching with diodes

Because of several design factors, it is simpler to switch the varactor tuner from low band to high band than it is to tune it continuously from channel 2 to channel 13. To accomplish this switching, the designers again rely on diodes, but here they are used as switches rather than variable capacitors.

Fig. 3 illustrates the general circuit configuration used for switching. When the switching diode is forward biased by applying to its anode a positive voltage from the band switch, it effectively connects the lower end of L1 to RF ground by way of C1, and the resonant circuit consists of L1 and the varactor diode. If the inductance of L1 is roughly .05 microhenrys, the varactor can tune the circuit across the high-band TV channels. (For convenience, the stray capacitance of the circuit has been ignored. Because the capacitances of C1, C2,

and C3 are so large, they do not affect the tuning.)

If the supply voltage for Q1 is switched through L2, rather than through the bandswitch diode, the diode is cut off by the positive voltage supplied to its cathode, C1 is effectively disconnected from L1, and L2 is connected in series with L1. If the inductance of L2 is about 0.74 microhenry, the total inductance is about .8 microhenry, and the varactor can tune the circuit across the lower VHF band. (Again, the effects of stray capacitance have been ignored.)

The VHF Tuner

Although the Sylvania and the RCA VHF tuners are different in many details, their general configurations are so similar that the RCA diagram in Fig. 4 can be used to illustrate both.

Each uses a MOSFET RF amplifier, a cascode mixer and a transistor local oscillator. These three active circuits are very similar to their counterparts in a conventional tuner—only the method of tuning them is basically different.

Both tuners use four distinct tuner circuits: 1) The RF input circuit matches the 75-ohm output impedance of the balun and IF trap to the gate of the FET and also tunes the gate circuit to the desired channel. To get the desired impedance match, the tuned circuit must also act as an autotransformer, which makes the bandswitching a little complicated. Both tuners use two bandswitching diodes in this circuit (CR1 and CR2). A single varactor, CR11, is used for tuning. 2) The RF output circuit tunes the drain of the MOSFET, Q1. The resonant circuit consists of a varactor and two inductances, which are in series for low band. The bandswitching diode takes one inductor out of the circuit for high-band operation. 3) The mixer input is tuned by a pair of inductors (L12 and L13) and a varactor (CR13).

Again, for high-band operation, a bandswitching diode removes one inductor. The Sylvania tuner uses a transformer to couple the MOSFET output to the mixer input; RCA depends on mutual inductance of the bandswitching diode leads in high band and an inductance common to both circuits in low band. 4) The local oscillator, Q4, is tuned about the same way in both tuners, and once again tuning is accomplished by a varactor (CR14) connected across a pair of series inductors, one of which can be disconnected by the bandswitching diode.

Both of these tuners are unlike conventional tuners in that the output of the UHF tuner, which is at the IF frequency, is injected at the base of the Cascode mixer, Q2 and Q3, rather than into the VHF RF amplifier. Because the "front end" of the VHF tuner isn't used during UHF reception, it is possible for VHF reception to be snowy or completely absent, while UHF reception is normal. In conventional tuners, this symptom almost always indicates a faulty VHF balun or antenna system.

In RCA sets employing the new tuner, it is possible to plug the IF input cable (link cable) into the output jack of the UHF tuner and obtain reasonably good UHF reception. This can be a useful in-home troubleshooting technique.

The method of switching the diodes is a bit different in the RCA and Sylvania tuners. RCA does it by applying positive voltage to the anodes of the switching diodes, to turn them on, and by feeding positive voltage to the cathodes when they are to be turned off (for high and low bands, respectively). Sylvania uses positive voltage to the anodes to turn them on for high band, but simply removes this voltage for low-band operation.

The UHF Tuner

There also are many similarities in the UHF tuners. (Again, the RCA circuit is used for illustrations; see Fig. 5.)

Both the RCA and the Sylvania tuners use an RF amplifier with forward AGC, and both have an IF amplifier. These two stages of amplification make it unnecessary to use the RF amplifier of the VHF

tuner as an IF amplifier during UHF reception, and this is the reason for the additional amplifiers in the UHF tuner. Without them, the design of the VHF tuner would have been much more difficult.

There are four resonant circuits tuned by varactors in each of these tuners: RF amplifier input, RF amplifier output, mixer input and local oscillator. Because the UHF band covers only about one octave (as opposed to about two octaves in the VHF band) bandswitching is not required. Mixing takes place in a diode, just as in a conventional UHF tuner, and the IF amplifier is a straightforward, common-base circuit.

A unique feature of the RCA UHF tuner is the ceramic substrate which forms the "chassis" of the tuner and also "contains" the tuned-line inductors, plus some of the capacitors. The substrate is a slab of alumina silicate, which is similar to the material from which chinaware is made. The material is specially compounded to be very durable and also to have high heat conductivity, along with very high electrical resistance. After firing, conductors, resistors, and small capacitors (actually two conductors close together) are printed or plated on the surface, and the discrete components are then soldered to the exposed conductors.

Tuner Control

Frequency selection using a varactor tuner requires two functions: bandswitching and varactor biasing. Sylvania elected to use pushbuttons for these purposes, while RCA chose a motor-driven rotary switch. In Canada, RCA Limited is marketing both types of control systems, the pushbutton variety, for local-control receivers, and the motor-driven-rotary switch version, for remote-control sets.

Regardless of the physical characteristics of the control system, the electronics are similar. In all cases the switches apply the appropriate voltage to the bandswitching diodes


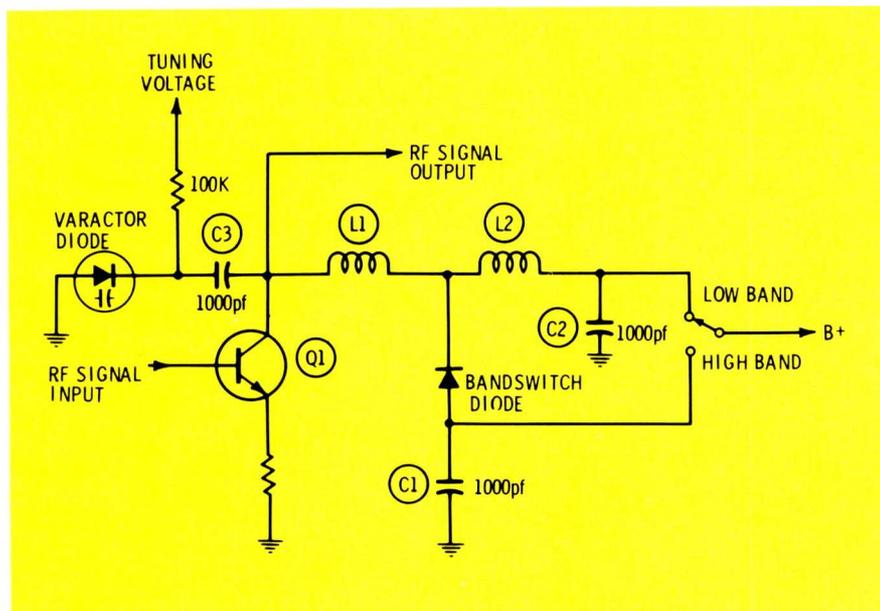


Fig. 3 Representative RF amplifier with bandswitching and varactor tuning.

Fig. 4 The RCA KRK 155 varactor VHF tuner. (Courtesy RCA Technical Services)

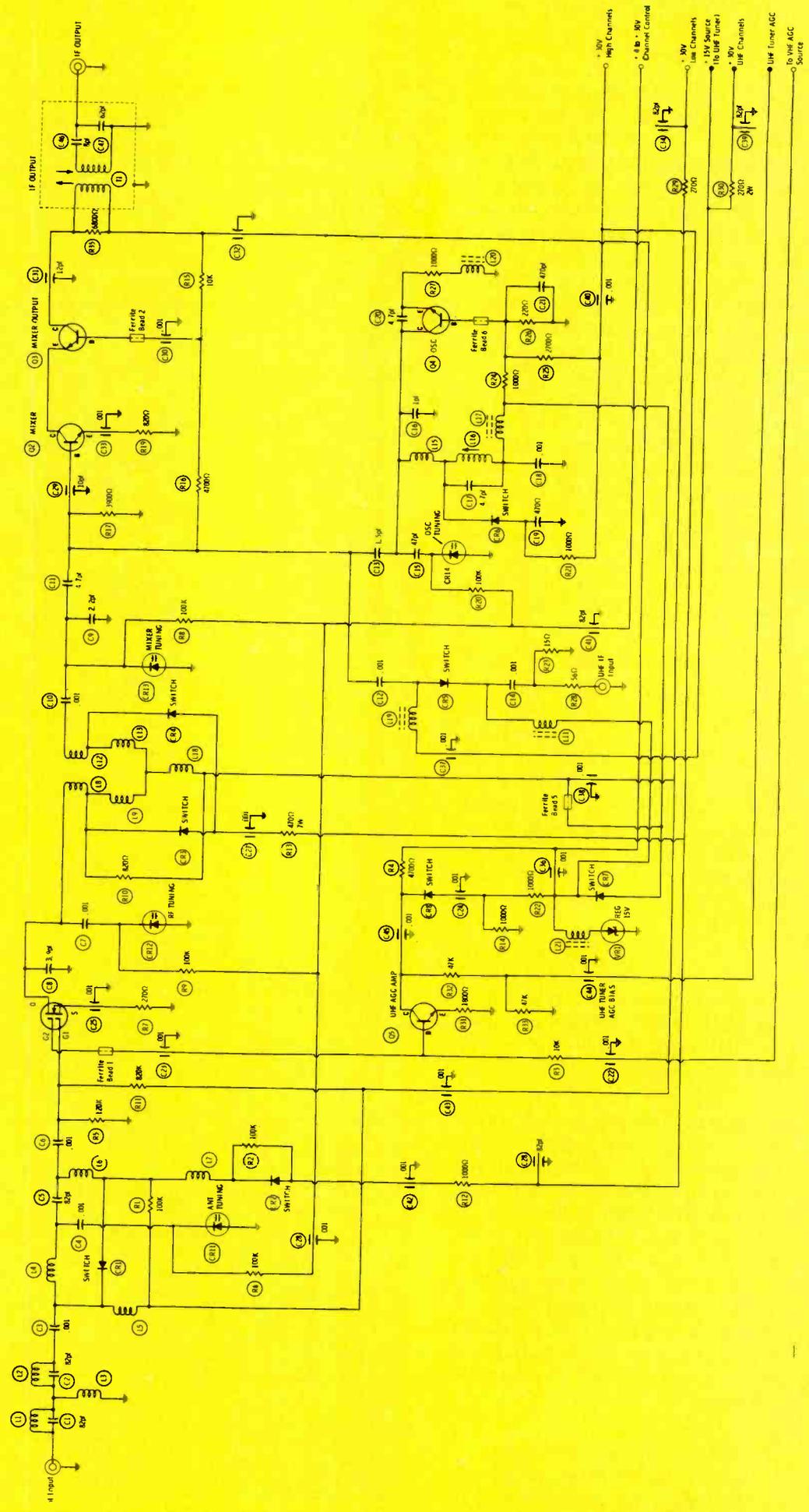

of the VHF and also control the B+ supply to the UHF tuner and to the VHF local oscillator and RF amplifier, which are turned off during UHF operation. A second set of contacts on each pushbutton (or position of the rotary switch) connects a potentiometer wiper to all the varactors. There is a separate potentiometer for each channel. Sylvania has eleven potentiometers, which can be set to receive any eleven channels, either UHF or VHF. RCA has twenty channel "pots", with twelve for VHF and eight for UHF; however, a simple wiring change allows either two, three, or five of the VHF channels to be changed over to UHF. The RCA Canadian pushbutton version has a pot for each VHF channel and four which may be tuned to any frequency in the UHF band.

AGC and AFT

Because the UHF tuner is equipped with amplifiers, both it and the VHF tuner require automatic gain control (AGC). In both the RCA and Sylvania VHF tuners, reverse bias is used (which means that a less positive bias voltage reduces the gain). In the UHF tuners, forward bias is used (that is, more positive bias reduces the gain).


In the RCA receiver, the VHF tuner bias is inverted by a circuit in the VHF tuner and supplied to the UHF tuner. Sylvania supplies the UHF tuner separate bias voltage from the chassis.

Because these tuners are tuned by a voltage, the source of this voltage must be well regulated. An approximate 25-volt change in voltage tunes the UHF tuner across all 70 channels; a 0.1-volt drift in the supply voltage to the tuning potentiometers would cause nearly a 2-MHz change in tuning. Because of this, extremely good regulators are used, and AFC voltage is added to this, to hold the tuners on frequency.

Servicing Considerations

The techniques for servicing varactor tuners are very similar to

Fig. 5 The RCA KRK 160 varactor UHF tuner. (Courtesy RCA Technical Services)

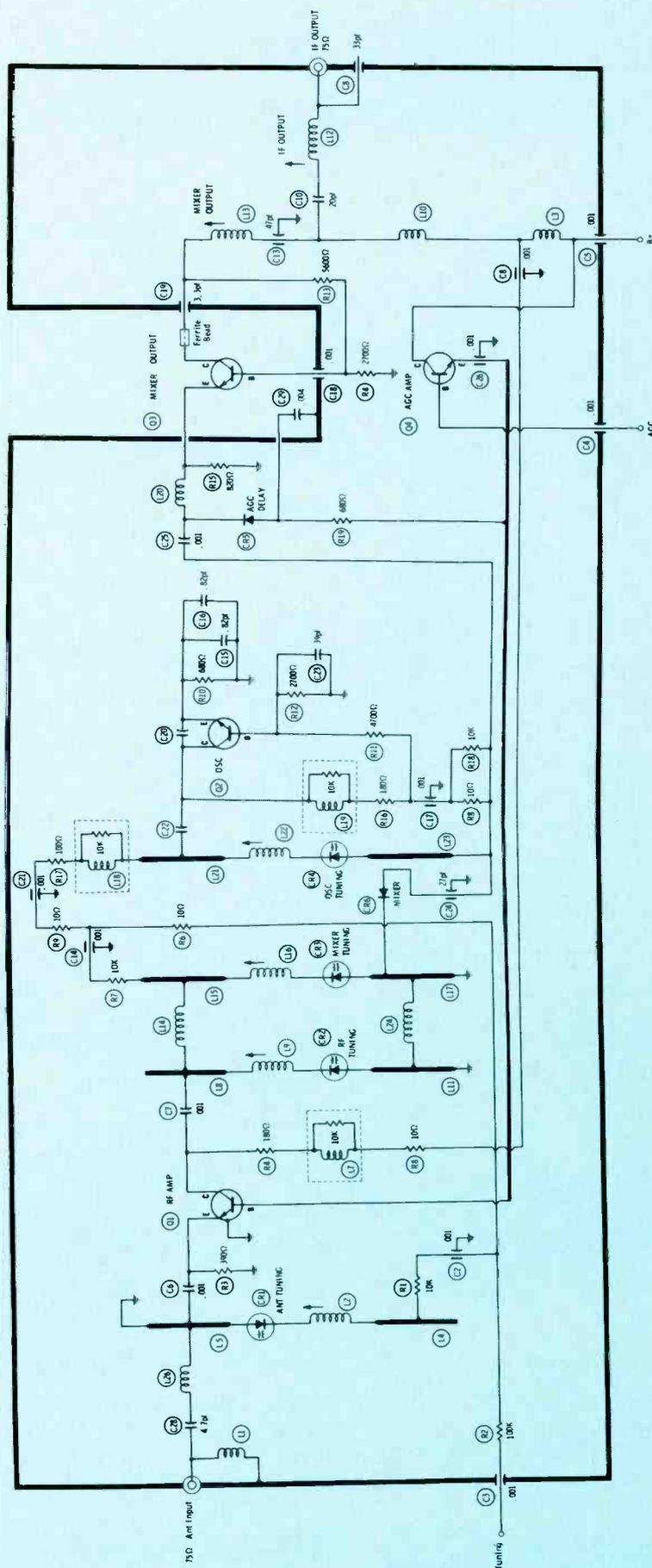

those used for conventional tuners, insofar as the amplifier and mixer stages are concerned. There are, however, a lot of other problems which can occur because of the voltage-controlled tuning.

First, it is very important that the regulation of the tuning voltage remains optimum. If there is a tendency of the tuner frequency to drift, it is likely that the tuning voltage also is drifting. If drifting frequency is the problem, check the voltage regulation.

The possibility of a varactor diode opening or shorting is relatively remote, but it can happen. The varactor and bandswitching diodes can be checked in the conventional man-

ner with an ohmmeter. However, because the capacitance-versus-voltage curves for varactors are not very uniform, replacing a single varactor will cause misalignment of the tuner. The varactors are supplied in **matched sets** and have to be replaced that way.

Bandswitching diodes are not so critical, and a single diode can be replaced without tuner alignment.

A shorted varactor will completely disable the tuner. If it opens, low gain with increased noise might result. If a local-oscillator varactor opens, the oscillator will swing completely off frequency, and there will be, of course, no reception.


If a bandswitching diode shorts, operation of the tuner will be normal whenever it is set up to operate in the mode in which that particular diode normally is saturated. For example, if an RF amplifier input diode, which normally is saturated during high-VHF-band operation, becomes shorted, operation will be normal for channels 7 through 13, because the diode would have been conducting (shorted) anyway. Nor will it cause any problems with UHF reception, because the RF amplifier of the VHF normally is disabled during UHF reception.

Summary



The signal processing functions of the varactor tuner are essentially the same as those in a conventional tuner. Only the method of tuning is changed.

So far, there are only two major entries in this field, and both systems are basically similar. No doubt, other manufacturers will introduce their own versions of varactor tuners, but it is likely that their operation also will be similar to that of the RCA and the Sylvania tuners.

In general, servicing varactor tuners is not particularly difficult; it is actually simpler in one respect—there is no switch to contend with. If you have been in the habit of repairing your tuners, you shouldn't really worry about this new type. If you send them to a jobber, as many service shops do, these jobbers can do just as good a job on varactor tuners as they have done in the past on conventional tuners. ▲

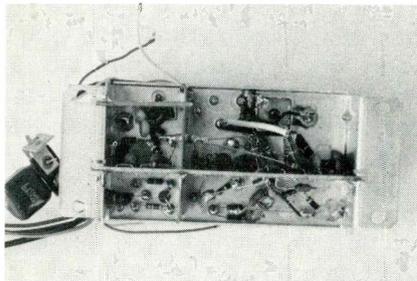

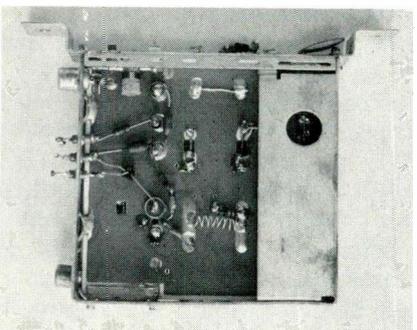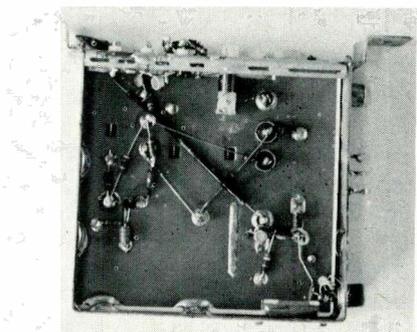Bottom view of the RCA VHF tuner. (Courtesy RCA Technical Services)



Obverse and reverse views of the RCA UHF tuner. (Courtesy RCA Technical Services)


FAST

COMPLETE SERVICE ON ALL MAKES OF TV TUNERS

Maximum Time In Shop 24 Hrs.

(Warranty: One Full Year)

(WE SHIP C.O.D.)
YOU PAY SHIPPING
\$9.95

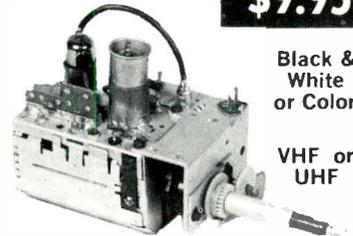

Black & White or Color

VHF or UHF

UV Combo's \$16.50

Price includes all labor and parts except Tubes, Diodes & Transistors. If combo tuner needs only one unit repaired, disassemble and ship only defective unit. Otherwise there will be a charge for a combo tuner. When sending tuners for repair, remove mounting brackets, knobs, indicator dials, remote fine tuning arrangements and remote control drive units.

WE UNCONDITIONALLY GUARANTEE All Tuners FOR ONE FULL YEAR



All tuners are serviced by EXPERTLY TRAINED TECHNICIANS with years of experience in this specialized field. All tuners are ALIGNED TO MANUFACTURER'S SPECIFICATION on crystal controlled equipment and air checked on monitor before shipping to assure that tuner is operating properly.

**GEM CITY
TUNER SERVICE**

Box 6G Dabel Station
1621 Mardon Drive
Dayton, Ohio 45420

Circle 22 on literature card

Business management checklist

Check your own management IQ

Management of a small business generally is tougher than managing an industrial giant, for a number of reasons.

For one thing, the industrial giant usually has considerably greater resources—its own assets and its reserve line of credit. For another, its affairs will be guarded and controlled by a staff of specialists—each responsible for only one area, or a part of one area, of the firm's activities. The *real* management is mostly concerned with directing, organizing, and coordinating the specialists. With its resources and its specialists, the big business isn't jeopardized by common garden-variety mistakes. It takes a real champion goof to put the giant under.

Small businessmen, by comparison, are often both the front office and back shop of their businesses. They are both chief executive and chief bottle-washer. Both of these jobs demand time and skill. But, too often, time spent managing is classed as "overhead", while time spent "doing the business" is classed as profit-making. This concept turns management into a neglected stepchild.

Good managers may have some inborn traits, but there are also a lot of good ones who've acquired the traits they need, and learned the skills they lacked without getting closer to a formal classroom than the local public library. Some of the traits they value are:

- Curiosity—to wonder about the hows and whys of problems.
- Stubbornness—to pursue answers to the hows and whys until they're in the bag.
- Inventiveness—the ability to devise your own solution when no other can be found.
- Adaptability—the ability to keep up with the times and conditions, instead of trying to keep things the way they were.
- Personality—the ability to be an individual and to respect the individuality of others.

Most important, you need the ability to think straight and reduce matters to their absolute basic terms. I heard (or read) a discussion by members of *Operations Research*, a business consulting operation, in which this recent technology/philosophy was described in terms of what it might have been able to do for the buggy-whip and harness manufacturers when they were shut down by development of the automobile. These

gentlemen, having decided they were in the buggy-whip and harness-making business and that there was no more market for whips and harness, quietly shut their doors and went out of business.

The boys from *Operations Research* would have clarified their basic premise for them. They weren't in the buggy-whip and harness-making business—they *really* were in the *transportation business*. Some determined searching in that wider field might have turned up new opportunities which fitted their experience, skills and plant capabilities. Transportation was then, and still is, a rapidly changing but still-growing field. But, ideally, a skillful manager would have foreseen the end of "natural" motive power (bone, muscle and horseshoes) and would have began plans to convert his company's efforts to another area. The steamboat, railroad and their ancestor, the stationary engine, had shown what was coming.

So, that leads to the one thing every good manager has—a firm, clear idea of what business he's in, why he's in it, what he expects to do with it and where he expects it to take him. There it is—goals and objectives, the heart of any philosophy of management. After that comes planning, procedures and methods directed at achieving the goals and objectives.

Maybe this little quiz about the seven major areas of management, gathered from a number of sources, will help you check your management interests and abilities, and measure your own management effectiveness. It may show you the weak spots in your own management skills.

What Kind Of A Planner Are You?

- Have you a long-range plan for the growth of your business?
- Have you plans to cover actions to be taken when the most dangerous or most likely emergencies strike?

Real management calls for constructive change. That means change as the result of planning, not change forced on you by a crisis or dictated by circumstances. Changes leading to growth, not directed at just holding on. You're in a business that features change—new chassis designs every year, new concepts and applications at a rapid pace. You have to plan to be ready for them, and plan to get the most out of them.

Emergency planning is a must. A financial crisis should find you with plans to carry you through. Pre-plan your search for credit, if a loan is needed. Know where you'll go for that loan (and why). Have that lender, at least, aware of your past record for good management and credit handling. Have your plan ready to present to him, to show him a serious, business-like borrower at his deskfront.

Don't forget this: No small business is ever more secure than the health of its owner-manager. Planning should include what's to be done to protect your business if you're ill or disabled. An extended absence can destroy the value of your business when you need it most. Who among your employees can be groomed to take over? (Before he's needed, of course—that's part of planning.) If you haven't any employees, can you get someone in to handle your business for the duration of the emergency? If you can't, you'll probably have to sell out—and a defunct business isn't worth as much as a going one.

Do your plans include a budget?

A short-term plan stating your goals in budgetary terms is a good idea. Keeping it short-term gives you control of current operations through your budget. Setting down your objectives in your budget gives you something definite to shoot for. Frequent comparisons between plan and result shows you what adjustments you must make to achieve those goals.

How About Organization? Personnel Skills? Efficiency Of Equipment and Shop Layout?

- If you have help, do you delegate as much as you can so that you have time for planning and other management duties?
- Do your employees have adequate supervision?
- Is one of your employees prepared and designated to take over in your absence?
- Do you maintain the personnel records required by law, union contracts and your own personnel policies?
- Do you review job performance periodically to determine each man's job competency and proper compensation level?

Delegating authority and work doesn't just set you free to manage. It also develops your employees, expands their capabilities and keeps them busy. Supervision is part of the training function, as well as keeping the work flowing and minimizing time-wasting. Control is at the heart of management, and record-keeping is essential to effective control. Periodic reviews are the fairest way of determining who gets raises, and the most objective way of dealing with job performance problems.

Are your fixtures and equipment adequate and up-to-date?

Are your stock areas as close as possible to the bench they serve?

Time spent waiting to use a piece of test equipment can take the profit out of a job. Maybe you need more than one of that item, or something to replace it on certain types of jobs. Does every man you have in the shop have adequate bench space, test equipment and tools? Crowding isn't a money saver, either. Just as waiting time eats up profit, so does walking time to a basement-stockroom, or one clear at the back of the building. Three or four steps should be the average. Shop layout can be an important profit-saver, and should be part of your growth and improvement plans.

How About Inventory Control and Purchasing?

- Is your parts inventory organized and controlled?
- Do you keep complete stock count, purchasing and sales records for it?
- Do you have a "never-out" list for staple items, to be sure you're really never out of them?
- Do you keep close checks on slow-moving, or high-cost items and those nearing obsolescence?
- Do you have adequate safeguards against theft, breakage, shortages and other inventory shrinkage?
- Do you keep separate records of those items in your shop which belong to others?

An organized inventory saves expensive time when a part is needed. You have what you need, know where to find it and can get it quickly. It also shortens the time required to make the stock-control count you should be taking periodically. Controlled inventory avoids excessive stocks of items that are rarely used, involve large investments, or are facing early obsolescence. Inventory shrinkage—by theft, breakage and items not delivered as ordered—eat into *your* share of the business. You *must* keep that leak plugged.

Records of consignment goods (those which belong to others) is the beginning of control for these items. Aside from questions of legal responsibility for them while they're in your possession, you need to know what you have, what's to be done with them, when, and who owns them. If you have parts or merchandise on consignment, you might be using them on a trial basis or to meet a temporary need. Once the need or trial period is past, you should either purchase or return them. Records keep you on top, or ahead of, the problems that consignment deals bring up.

- Do you issue purchase orders in writing?
- Do you follow up your orders, to see that goods are being received as ordered, in correct quantities and on time?
- Do you take advantage of available discounts—trade, quantity or cash—and include them on your written orders?

Written orders avoid most arguments, and quickly end the others. They show what you ordered and give you your own record to compare with what's delivered. Your written purchase order can also specify whatever special conditions must be met—delivery dates, times and shipment methods, for example. Checking deliveries is the one way you can be certain that you get what you ordered, in good condition, and get what you're being charged for.

Discounts are added incentives to good management. There are some businesses which earn cash discounts almost equal to their operating profits. You can't earn money any easier than the discount you receive for paying cash with your order, or for paying ahead of time. Mark that down as "profit derived directly from good management." That's where it belongs.

How Are You At Advertising, Promotion and Customer Relations?

- Do you plan promotional activities?
- Do you have an advertising program, geared to your market, your kind of business and your planned objectives?
- Do you try to assess the performance of your advertising or promotions in the light of those factors?
- Do you add value to your service by projecting an image of your business that your customers respect?
- Do you develop customer confidence in your judgment and your readiness to assure their satisfaction?
- Do you, and your people, see each customer as an individual or just as "one of the crowd"?

Knowing objectives, reducing them to basics, really pays off here. You have to decide what "image" you want. You must know what you have to sell that is *special*, in very specific terms. Not "better service", but, "Better service *because . . .*" You promote, and advertise, the "Because . . .".

One aspect of promotion you should always pay attention to: Your replacement customers. Your old ones die off, move away, retire, lose interest or give in to the push of your competitors. This attraction shouldn't sink you, and it won't, if you keep getting replacements lined up for your "old reliables".

Accounting and Finance

- Do you have an accurate, complete bookkeeping system that is balanced and summarized each month?
- Do you keep careful records of cash outlays for parts, supplies and services?
- Do you deposit each day's cash receipts in the bank without delay?
- Do you have a petty cash fund, limit its use to small amounts, and hold it to what's needed for short

periods of, say, two weeks or so?

- Do you avoid frequently drawing checks payable to "Cash"?
- Do you avoid signing your checks in advance?
- Do you watch over your liabilities with the same care you give your assets?

Keeping records of cash expenditures takes little time, and it's far more reliable than memory. A check stub or small cash ticket is all that's needed. Without such records, your expenses can get out of control. Books, properly kept and summarized at regular intervals, keep you informed about which way your business is headed and give you time to correct faults while they're small.

Holding cash in the shop overnight is bad business, and it's even worse to start making cash payments out of your cash receipts. Daily bank deposits prevent both from getting started. A petty cash fund avoids check-writing for small items and keeps your overnight cash-holding to a minimum. Pre-signed checks are invitations to dishonesty — whether among your staff or outsiders. **Cash is your most vulnerable asset.** It deserves your most determined efforts to protect and conserve it.

Watching your liabilities is another important way to protect your investment in your business. Not just to keep liabilities to a level you can handle, but to make sure that the liabilities you pay on are really *yours*. That means checking statements from your suppliers against your own records, to avoid overcharges, paying someone else's bill, or paying for merchandise you didn't order. You need records and well-established procedures to substantiate your claims.

How Do You Stand On Insurance, Tax and Legal Understanding?

- Do you have an insurance program, handled by a knowledgeable and conscientious insurance agent, to protect you from casualty losses?
- Does it cover your business properly?
- Are you getting the most protection for your premium dollar?

It is possible to become an expert about your insurance needs, but you don't have to, if you rely on a conscientious, knowledgeable and reliable agent. You periodically should review your protection and your loss exposures with him—to cover changes in values, to cover changes in your business properties or changes in your operations and procedures. Additional hazards, new coverage requirements, added risks, special exclusions might be involved in some of the changes you make, so keep your agent informed. Let him help

you get the most for your money through proper use of deductibles, planning coverages for expansion according to need and/or means, and careful shopping for the best policies.

- Do you file your required tax reports on time?
- Have you someone who's responsible for this, and do you check to make sure it's taken care of?
- Have you any way of checking to make sure that you're not overpaying your taxes?

Unless you keep a tax calendar, or have someone do it for you, you risk being late filing returns and reports required by law. That can cost you penalties and interest. An occasional tax "check-up" by an expert is a good idea, to be sure you're not paying more than you should. He can save you more than his fee for such services.

- Do you know your legal obligations to your customers, suppliers, neighbors and local government?
- Do you have access to a good attorney who can advise you about these matters and represent you if serious legal problems arise?

Following are some of the things you should understand in a general way, as they apply to you and the way you do business:

- Your local zoning regulations, regulations about signs, licenses, advertising and business practices.
- You should have a fair idea of your legal rights and obligations in your dealings with customers, suppliers and others with whom you have business relationships.
- You should have a fair smattering of knowledge of contracts—oral and written.

You need to know these things to stay out of difficulties. You needn't have more than a basic knowledge to guide your decisions, with an attorney available to handle trouble or resolve the complex questions.

Some Miscellaneous Points

- Do you belong to a local, regional or national trade organization?
- Do you take an active part in its programs for progressive legislation, industry standards, professional upgrading?

There's strength in good industry or trade association memberships. Some associations help with educational matters, others with sound licensing and certification programs, or still others provide a forum for exchange of ideas and business data. If yours doesn't, it will only do so when its members demand that it serve them. It will only hear your demand if you belong.

If association membership isn't practical, or if there's no association for you to join, you can work for the changes on your own. Or take the lead, and get your colleagues to help you form an association that's geared to your needs.

- Speaking of upgrading, how about your own efforts?
- Do you regularly read the technical bulletins, promotional aids and trade papers and magazines available to you?
- Do you participate in the programs they offer?

Upgrading yourself calls for a constantly expanding knowledge of the products, techniques, concepts and applications which represent the "state of the art". It also calls for improving your skills at running your business. To ignore either one is to invite disaster—you can't survive unless you keep up technically, nor can you survive if you fall behind as a manager.

Summary

There they are, the seven major areas of management skills: Planning; organization; inventory control and purchasing; advertising; promotion and human relations; financial control; relationships with legal and governmental institutions; and, for lack of a better name, business citizenship.

They should give you this kind of picture of a good manager:

- He knows what he wants and what he must do to accomplish it.
- He has, or gets, information to guide his plans and decisions.
- He is rarely unprepared for developments in his operations, because he has either made those developments happen or has planned for their occurrence. When he acts, it is for a purpose he has defined and for reasons he knows.

One thing you'll never hear a good manager say is: "The way things were going, I had to do something!" ▲

Horizontal sweep— operation and troubleshooting

This first of two parts explains how horizontal scan is achieved and provides general troubleshooting tips. Part 2 will provide specific troubleshooting techniques.

Horizontal Sweep Is Produced By Current

Currents through the coils of deflection yokes generate magnetic fields which move the electron beam in a picture tube to produce a raster. Voltages are of secondary importance.

General Requirements For Correct Horizontal Deflection

Without any horizontal deflection of the electron beam in the picture tube, the raster would consist of one vertical line located at the center of the screen. There is

no current in the horizontal yoke coils when the beam is at the center of the screen, a condition which occurs twice during each horizontal cycle—once during trace time and once during retrace.

Direct current of **positive** polarity flowing through the yoke deflects the electron beam to the **right** of center. Direct current of **negative** polarity flowing through the yoke deflects the electron beam to the **left** of the zero-current center of the screen.

Horizontal deflection is accomplished in four separate operations.

The locations where these four basic steps take place on the screen of the picture tube are shown in Fig. 1A.

Current through the horizontal coils in the deflection yoke should be large enough to move the picture tube beam the full width of the screen. Theoretically, the current waveform should have a perfect sawtooth shape. In practice, this ideal waveform is compromised somewhat, although the basic sawtooth shape always can be seen in a normally operating receiver. To compensate for excessive scan at

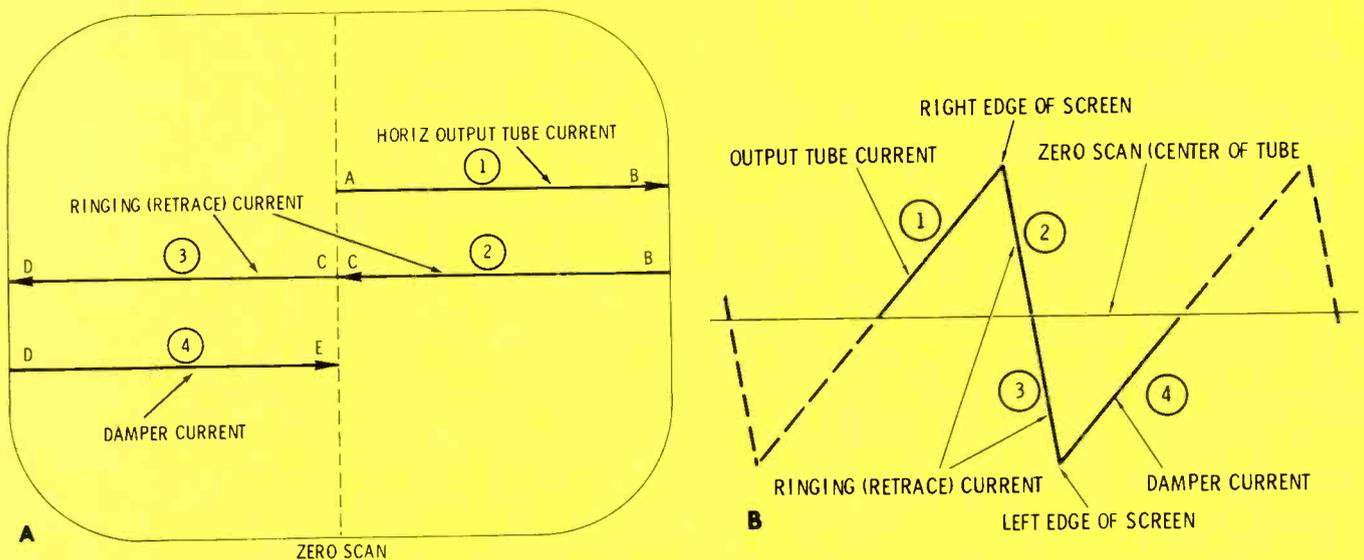


Fig. 1 Locations where the four steps of horizontal deflection occur on the screen of the picture tube, and also where they are located on the waveform of yoke current. This information can help technicians correlate visual symptoms with the area of the circuit where the defect is most likely to be. A) Power to scan from the center of the picture tube screen (point A) to the right edge (point B) is supplied by plate current of the horizontal-output tube. Current from

ringing of the yoke circuit moves the electron beam, in two separate steps, to the left side of the screen (point D). Current from damper rectification moves the beam from the left edge (point D) to the zero-current center of the picture tube screen (point E). These four steps constitute one cycle of horizontal scan. B) The same four steps of horizontal deflection as they relate to the waveform of yoke current.

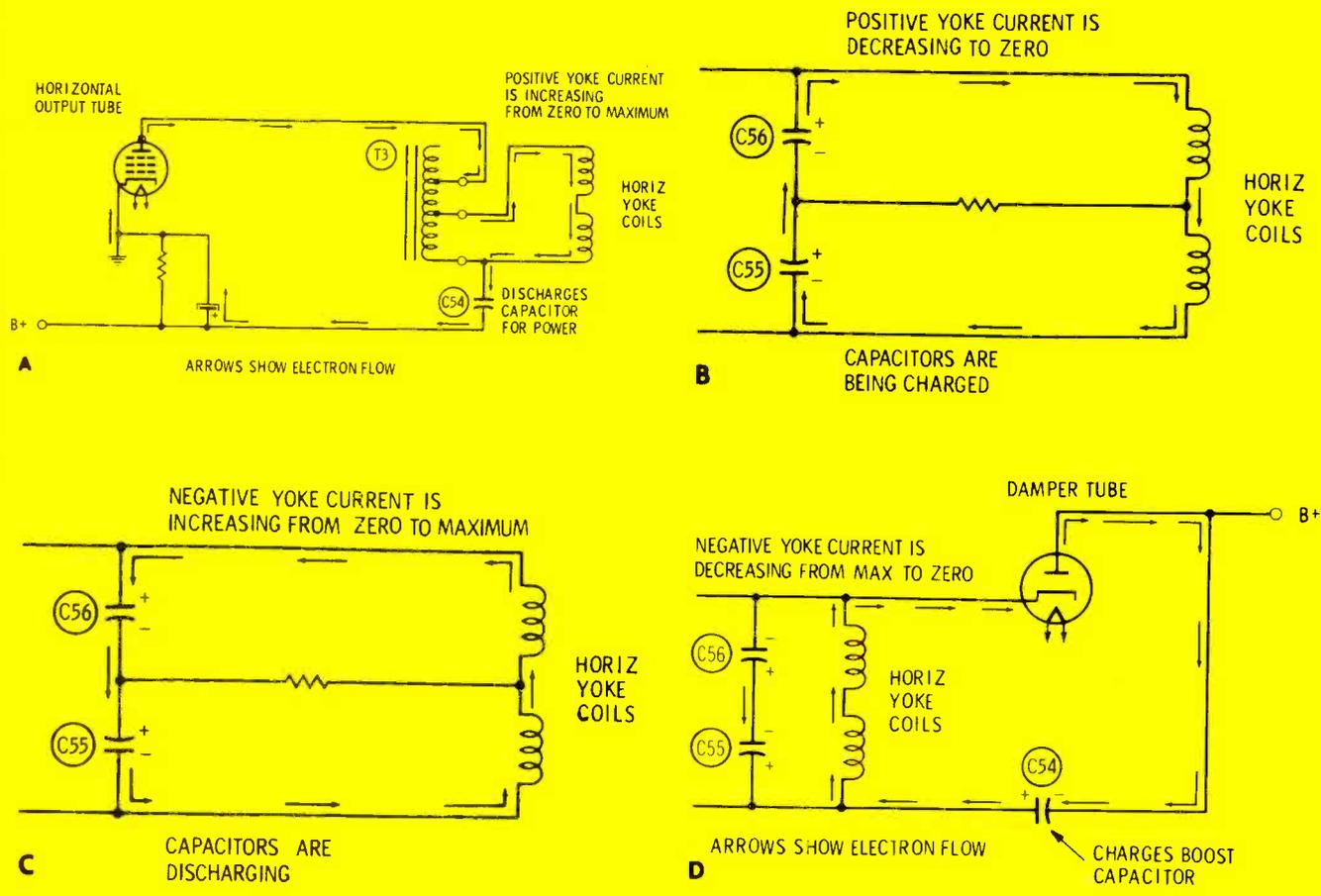


Fig. 2 Simplified schematics show electron current through the yoke, and any other parts directly involved, during the four steps of horizontal deflection. It is assumed that deflection has been operating normally long enough to charge C54, and the beam is at the horizontal center of the picture tube screen, at which point no current is flowing through the yoke. A) Gradually increasing plate current through the horizontal output tube moves the electron beam of the picture tube from the point of no deflection at the center to the extreme right edge of the screen. The yoke capacitors have no effect on the yoke current, because ringing is damped by the load and the slow rate of change of the tube current. When the drive waveform at the grid of the output tube starts down the trailing edge of the sawtooth, the current through the output tube is stopped abruptly. This is the end of step 1. B) The sudden cessation of tube current shock excites the main tuned circuit (yoke coils, C55 and C56) into ringing at the unloaded frequency of approximately 75 KHz. The polarity of the yoke current at this time is positive, the same as that previously supplied by the output tube; however, it is becoming less positive because C55 and C56 are being charged. Yoke current rapidly decreases to zero, and the beam is returned to the center of the screen. Because the damper cathode is positive relative to the plate, the damper cannot conduct. During the small interval at the center of the screen, when the yoke current is

zero, the yoke capacitors are fully charged with positive voltage—which produces the large positive-going pulse that is rectified to supply the high voltage for the CRT anode. This is the end of step 2. Both this action and the similar ringing step which follows proceed very rapidly; they are the complete retrace. C) Ringing continues, and the capacitors discharge back into the yoke coils. The polarity of the yoke current reverses (becomes negative) and gradually increases until the beam is moved to the extreme left edge of the picture tube screen. The damper cathode gradually becomes less positive and nearer conduction during this time. This is the end of step 3. D) A negative-going voltage pulse starts to form as the ringing attempts to continue, but this pulse causes the cathode of the damper tube to become negative relative to the plate, and the damper conducts. This conduction continues for about 1/3 to 1/2 of the total deflection time; both the damper and the yoke currents gradually decrease as the ringing is damped out and the beam is moved to the center of the picture tube. Because the damper current loads the tuned circuit the yoke capacitors have little effect on the yoke current. Damper conduction (rectification) also replenishes the charge in C54, because the voltage previously stored in the capacitor was used during Step 1 by the horizontal output tube. This is the end of step 4, and the end of one cycle of horizontal deflection.

the edges of picture tubes which use wide-angle deflection, the waveform often is curved at each end. Because of such variations, the most accurate method of judging linearity is by visual observation of the

crosshatch pattern displayed on the screen.

Yoke current can be viewed easily by adding a low-value resistor (.5 to 5 ohms) in series with the yoke, and connecting the scope

leads across the resistor. **(Warning:** Because the yoke is connected to B-boost voltage, the scope will be several hundred volts more positive than chassis ground.)

Fig. 1B shows the points where


Circuit "Ringing"

A capacitor accepts a charge when it is connected to a source of voltage. This charge is obtained gradually. A charged capacitor will discharge into a resistor, a coil or another capacitor. This, too, is a gradual process.


Voltage applied to an inductor produces current, but the current increase is gradual and not instantaneous. If the supply voltage is disconnected, the current flows in the same direction but at a decreasing rate until the energy is dissipated. An inductor will discharge into a resistor, capacitor or another inductor. If no external component is connected to an inductor when the supply voltage ceases, the inductor will discharge into the stray capacitance of its own windings.

A capacitive reactance (capacitor) and an inductive reactance (coil), connected in parallel become a tuned circuit, which transfers energy from one reactance to the other until circuit losses drain the power to zero. This is often called "ringing", or damped oscillation.

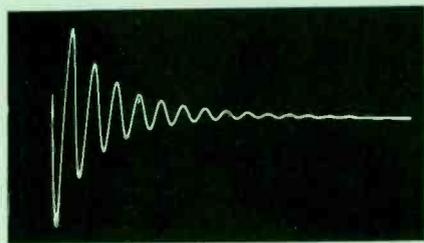
The following analysis of the action of a tuned circuit is confined to coil current and capacitor voltage, because these two are the most important factors in the deflection circuits of television receivers.



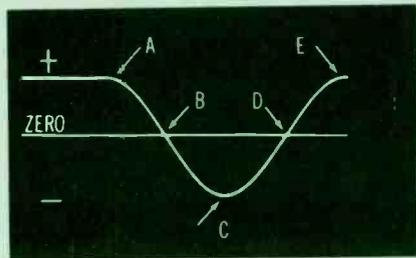
A DC supply voltage was connected to a tuned circuit long enough for the current to reach maximum. When the power supply was suddenly disconnected the damped wavetrain of sine waves shown here was produced. The first 1/4 cycle is not displayed on the scope screen because the vertical amplifier section of this particular triggered-sweep scope is not equipped with a delay line.



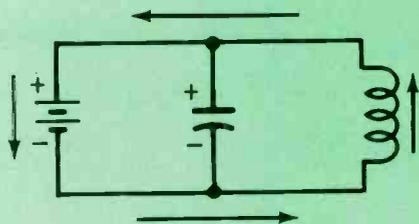
Shows the power supply voltage and the first cycle of the sine wave of coil current. Beginning and ending points of each 1/4 cycle are indicated by letters.



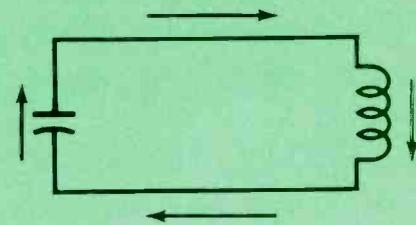
A battery was the source of the maximum "positive" coil current. The small battery voltage also appeared across the capacitor.



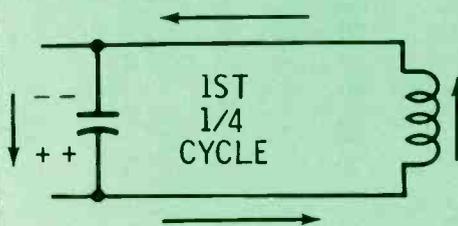
The capacitor voltage (source) was zero, and the "negative" coil current was maximum at point "C".



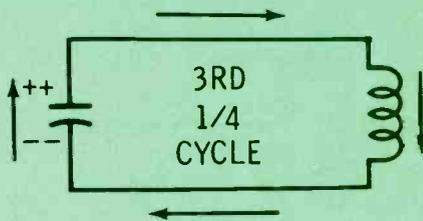When the battery was disconnected, "positive" coil current flowed from the coil (source of power) into the capacitor and charged it with a negative voltage. The coil current gradually decreased in step with the increase in capacitor voltage. This action is shown between points "A" and "B" in Photo 2.



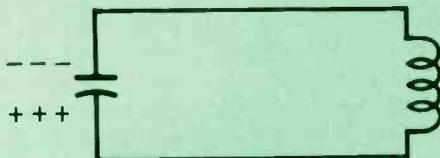
"Negative" coil current (source) decreased as it charged the capacitor with positive voltage. Points "C" to "D" in Photo 2.




The coil current was zero at point "B" in Photo 2, and the negative voltage across the capacitor was nearly 50 times larger than the original battery voltage.



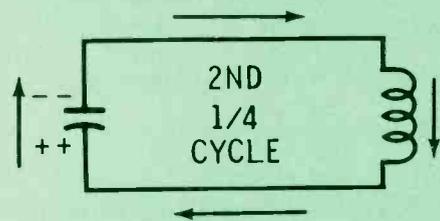The coil "negative" current (source) reached zero, and the capacitor was charged to maximum positive voltage at point "D" in Photo 2.



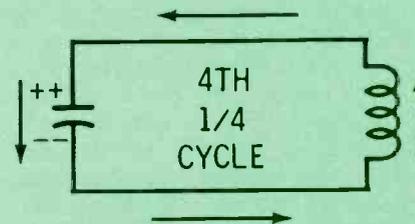The negative capacitor voltage (source) discharged back into the coil and caused "negative" coil current. This corresponds to the waveform portion "B" to "C" in Photo 2.



Positive voltage from the capacitor (source) flowed into the coil producing an increasing "positive" coil current. This action is between points "D" and "E" in Photo 2. The capacitor voltage was zero and the "positive" coil current maximum at point "E".

Succeeding cycles of "ringing" occur in the same way as described for this first cycle, except that the amplitude of each succeeding cycle becomes smaller because of power losses imposed by the circuit.

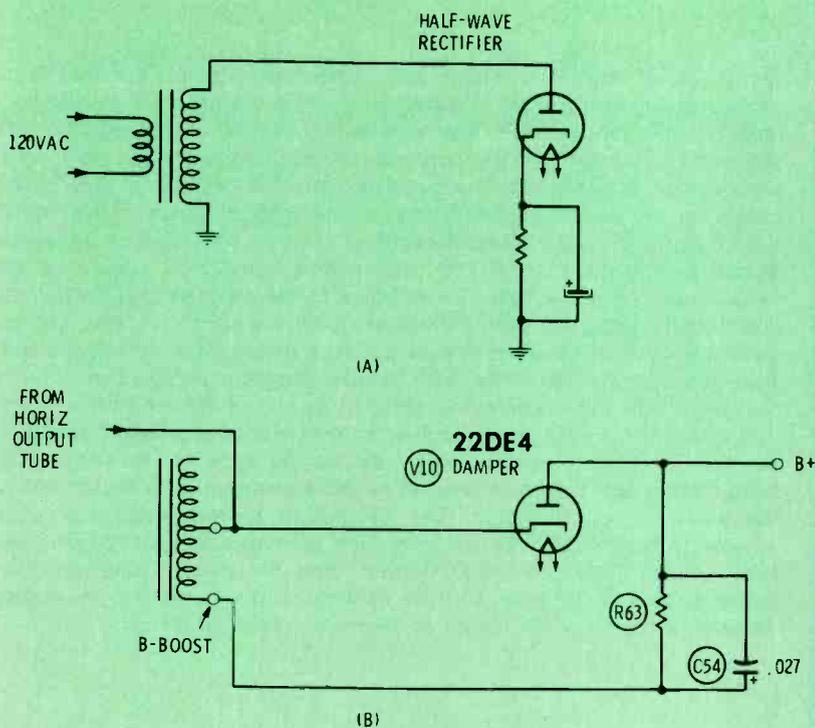


Fig. 3 Dampener action is exactly the same as that in a series, peak-reading rectifier circuit. A) Schematic of a conventional, series, half-wave, peak-reading rectifier circuit. The larger the capacitance of the peak-reading filter capacitor, the shorter the period of time during which tube current flows. B) Schematic of a typical damper circuit is the same as that of the previous rectifier circuit, except that it is inverted and is connected to B+ instead of ground. The size of the B-boost capacitor (peak-reading capacitor) determines the linearity of the left half of the raster.

the four steps of horizontal deflection occur on the sawtooth waveform of yoke current.

The four steps of horizontal deflection are illustrated and explained in Fig. 2.

Dampener Tube Operation

Operation of the damper tube circuit seemingly is different and more complicated than that of most other circuits. This false impression is due, in part, to the way the circuit is drawn on most schematics. Actually the damper functions much like a half-wave rectifier. Fig. 3A shows the schematic of a simple rectifier circuit, which is nearly identical to the typical damper circuit shown in Fig. 3B.

Conduction of the damper tube occurs whenever the cathode becomes more negative than the plate. Capacitor C54 is charged during

conduction. Because this stored voltage keeps the cathode positive relative to the plate, further conduction cannot occur until the normal oscillation, or ringing, voltage of the horizontal deflection system swings negatively enough to exceed this stored voltage.

The voltage developed by damper conduction is called B-boost. Because it is added in series, it increases the supply voltage which is applied to the plate of the output tube. Thus, power which would otherwise be lost is changed into deflection power.

The capacitance and leakage of the B-boost capacitor are critical for correct deflection. Horizontal-linearity, or horizontal-efficiency, tuned circuits are often inserted between B-boost and the supply voltage, in place of the simple capacitor described here.

Waveforms Produced By Horizontal Deflection Systems

Each scope waveform taken from horizontal deflection circuits contributes some information. Several such waveforms, which have the same phase, are shown in Fig. 4. These verify the theory of horizontal sweep operation given previously. (The waveforms in Fig. 4 are from a Sears 456/528.51912 b-w television chassis, the schematic of the horizontal deflection circuit of which is shown in Fig. 5.)

Grid drive for the horizontal output tube (Fig. 4, W1)

The first important voltage waveform is that of the horizontal oscillator signal at the control grid of the output tube. This waveform is subject to considerable variation from model to model. Some chassis require a rounded sawtooth with a pulse at the bottom, while others require a more linear sawtooth without a pulse. The purpose of the pulse, when required, is to cut off the output tube current more rapidly.

The top of the sawtooth at the grid of the output tube in the Sears chassis is rounded more than that in some chassis, apparently to reduce excessive scan at the extreme right edge of the picture. This improves the linearity on the right side.

The sawtooth grid waveform in all chassis has a small, flattened area on the top of the waveform, because the grid current drawn by the output tube clips the voltage. If the normal flat spot is missing, no current is being drawn by the output grid.

Cathode current (Fig. 4, W6)

Many color receivers produce a sawtooth of horizontal output cathode current that has less ringing than the amount seen here. In any event, the tube should not be continuously drawing current. Current should flow for slightly more than 50 percent of the time. After you have observed the waveform produced by the output tube cathode current in a number of different receivers, you will know what is normal and what is not, and can use the waveform to diagnose many horizontal defects.

Yoke current (Fig. 4, W8)

Not many occasions demand that we view the waveform of yoke cur-

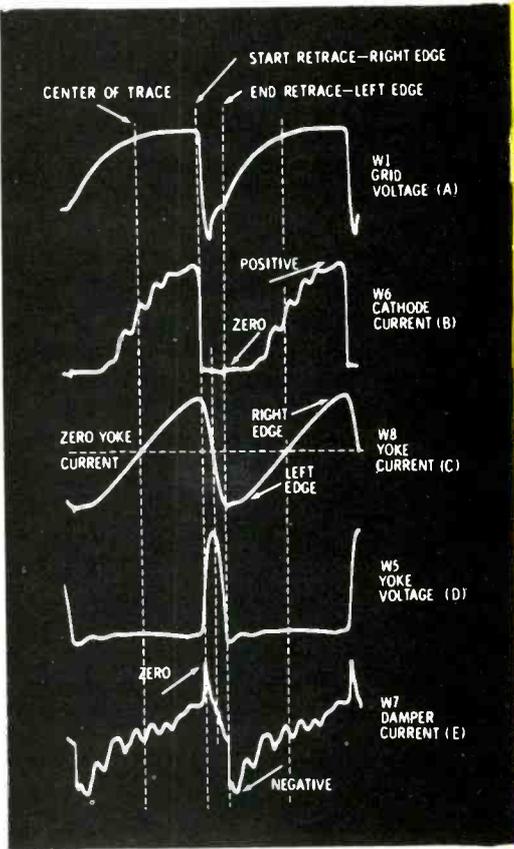


Fig. 4 These important voltage and current waveforms from the Sears chassis (schematic in next illustration) illustrate the phase (time) relationships of the various deflection actions. A) The downward edge of the sawtooth at the grid of the horizontal output tube causes a very rapid cessation of tube current. The cutoff of current is so fast the line barely shows on the waveform. Reduction of high voltage occurs if this line is tilted, which indicates slower shutoff of current. B) Cutoff of horizontal output tube current starts the ringing which produces retrace of the beam. Notice that the tube current stops at the exact instant the retrace starts (trailing edge of yoke current sawtooth waveform). C) Zero damper current occurs at the same time as cutoff of output tube current (the start of retrace). D) The tip of the pulse of yoke voltage occurs at the center of retrace, which is the only action revealed by any of the waveforms at that particular time. E) Maximum damper current (negative polarity) occurs at the end of retrace, represented by the trailing edge of the sawtooth of yoke current and the tip of a small negative-going pulse at the bottom of the yoke voltage waveform. The decreasing damper current is small enough to be cancelled by the increasing current of the horizontal output tube at the center of the trace. Current from the output tube increases (positive polarity of yoke current) enough to overcome the decreasing damper current near the center of the trace (center of picture).

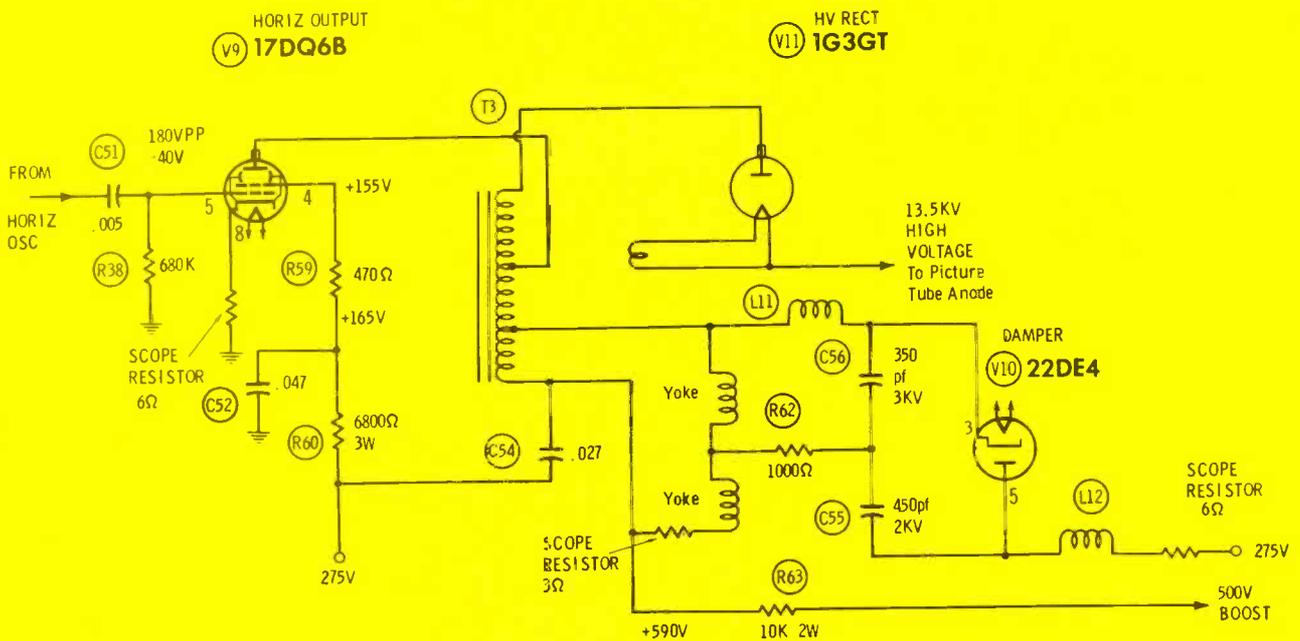


Fig. 5 Complete schematic of the horizontal sweep and high-voltage section of the Sears 456/528.51912 b-w television chassis. Normal DC voltages for this one individual chassis are included. Waveforms will be added next month, to illustrate a detailed discussion about troubleshooting the horizontal sweep sections of television receivers.

rent. If there is a raster, the condition of the sweep can be determined by viewing it. The normal shape of the yoke current waveform is an approximate sawtooth, and it is included here to show the time relationship between yoke current, which is the final product, and the other voltages and currents.

Yoke voltage (Fig. 4, W5)

The yoke voltage waveform, and other pulse voltages taken from the horizontal output transformer for AGC, blanking or other uses, is the one normally associated with horizontal deflection. However, the yoke pulse is **not** the force which causes yoke current, and, consequently, has only limited value for trouble analysis. Beyond a certain point, some conclusions based on this waveform alone will be misleading. Next month, we shall give specific examples for your guidance.

Damper current (Fig. 4, W7)

Damper current is another waveform which is seldom analyzed. The characteristic of damper current that

surprised me the most the first time I saw it was the long duration of current. I had assumed incorrectly that the damper tube conducted once on the first negative ringing pulse, and that was the end of damper conduction.


The damper current waveform **appears** to indicate zero current at the start of trace (left side of the screen), followed by increasing current toward the right side. However, this interpretation is wrong. The current at the start of the trace at the left edge is **maximum negative**. Remember, as stated previously, negative yoke current is necessary for any kind of deflection on the left side of the screen. For example, during retrace from the center to the left edge of the screen, the current with the beam at the center is zero, gradually becomes more negative, reaching maximum negative at the extreme left edge. Deflection from the left edge to the center of the screen begins with maximum negative current (from the damper tube) at the left edge, and gradually decreases to zero at the center.

General Troubleshooting Tips

To help with troubleshooting, remember that damper circuit conditions are mainly responsible for the left side of the picture. For example: A weak damper tube will stretch the extreme left side of the picture.

The horizontal output tube contributes scan for the right side of the picture.

Some interdependency exists between the sequence of steps in horizontal deflection, and this can cause some blurring of the symptoms. For example, a weak horizontal output tube would be expected to give the primary symptom of narrow width on the right side of the picture. However, cutoff of the abnormally low plate current reduces the amplitude of the yoke ringing during retrace. This reduced ringing generates a smaller pulse of voltage, which, in turn, produces less damper conduction, and, consequently, reduced scan on the left side of the screen. The final result is a picture that is narrowed on **both** sides. ▲

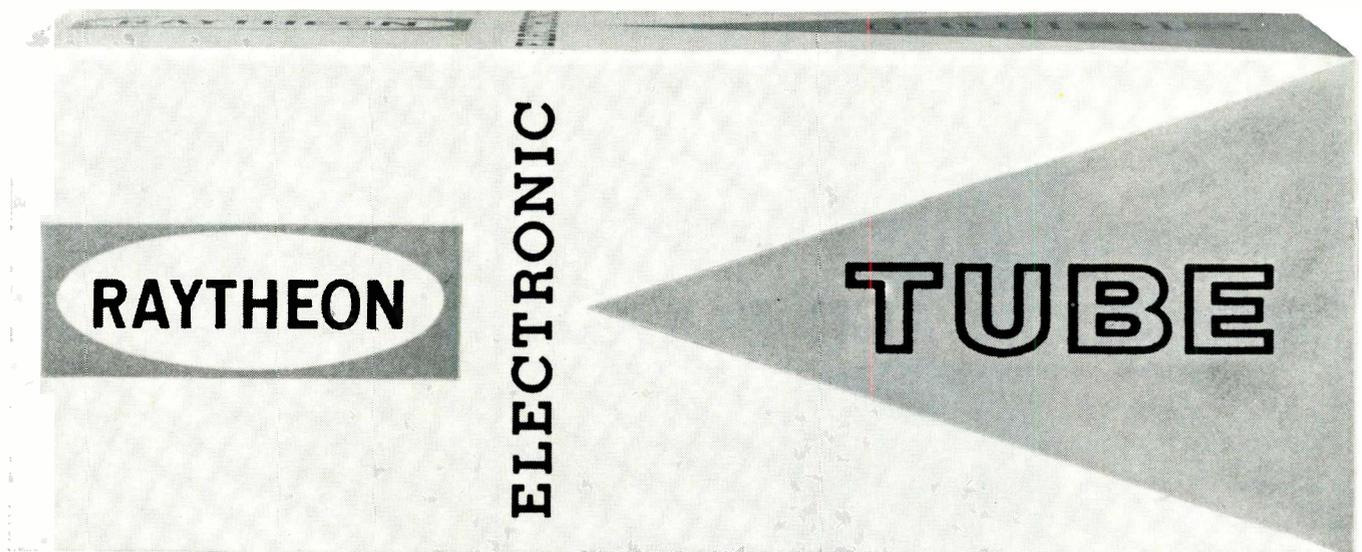

your silent partner

You and our tubes make a great team. Great because it's a close sales partnership. So close that you, the independent serviceman, are our only outlet.

We don't compete with service trucks. Or captive business. That's helped you make us the largest independent tube supplier in the business.

Together we've come a long way.

You've found it's good business to do business with us.

And because your business is good, ours is.

Let's keep it growing together.


Circle 23 on literature card

Stereo Microphone Mixer

The Model M688 stereo microphone mixer, which reportedly is designed to deliver high-quality performance when used with stereo tape recorders without built-in mixing capabilities, has been introduced by Shure Brothers Inc.

The M688 reportedly accepts four high- or low-impedance microphones through four inputs, plus a stereo auxiliary high-level input, each with its own volume control. Three microphone inputs have front-panel switches for left- or right-channel output. The fourth microphone input has a pan control which reportedly allows this input to be directed to the left channel, the right channel, or anywhere in between.

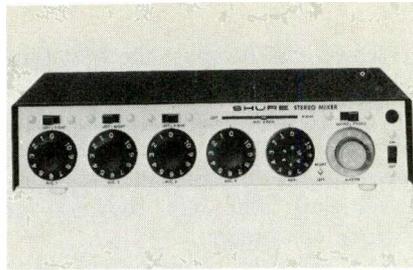The M688 can also be used in audio-visual and multi-media presentations in which a stereo music source is used, or for stereo sound



reinforcement applications.

The unit is equipped with a stereo high-level, high-impedance output plus a left-plus-right (mono) microphone level output (high or low impedance), according to the manufacturer.

Model M688 sells for \$114.00.

Circle 70 on literature card

12-Inch Loudspeakers

The Model 9, a 12-inch, two-element, dual-cone speaker, and the Model 10, a three-element, coaxial speaker, have been introduced by Jensen Sound Laboratories.


Specifications include:

Nominal size—12 inches for both
Power rating—20 watts for both
Frequency range—25-15,000 Hz for Model 9; and 25-18,000 Hz for Model 10

Impedance—8 ohms for both
Crossover—6,000 Hz, mechanical crossover, for Model 9; 4,000 Hz for Model 10

Balance control—Model 10, high frequency; none on Model 9


Woofers resonance—30 Hz for both

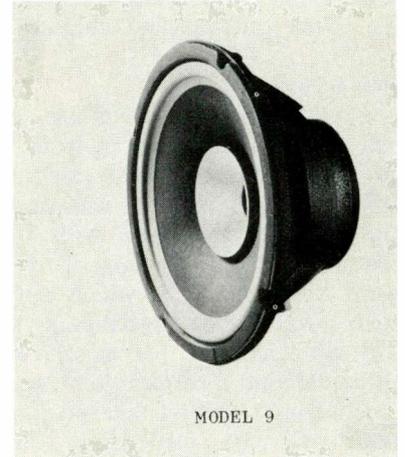

MODEL 9

Dimensions—12 $\frac{3}{8}$ inches x 5 $\frac{3}{4}$ inches for both

Connections—Push-type binding posts for both

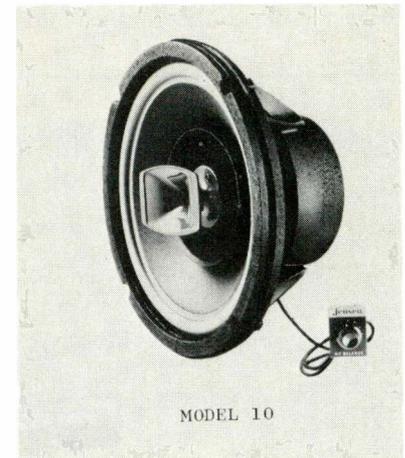

MODEL 10

Weight—8 $\frac{1}{2}$ pounds for Model 9, and 10 pounds for Model 10. Model 9 sells for \$30.00, and Model 10 sells for \$45.00.

Circle 71 on literature card

Stylus Cleaner


Duotone Company announces the availability of Microlux Stylus Cleaner.

The stylus cleaner is a chemical known as Formula ML-365, which is applied to the stylus with a brush. It cleans the stylus and acts as a deterrent to further accumulation of dirt. The Microlux application does not harm the stylus, its mounting or the records, and it acts

NOW... ONE PERMA-POWER BRITENER SOLVES BOTH KINDS OF COLOR TV PICTURE PROBLEMS...

NEW **COLOR BRITE** HAS BOTH...
ISOLATION AND BOOST!

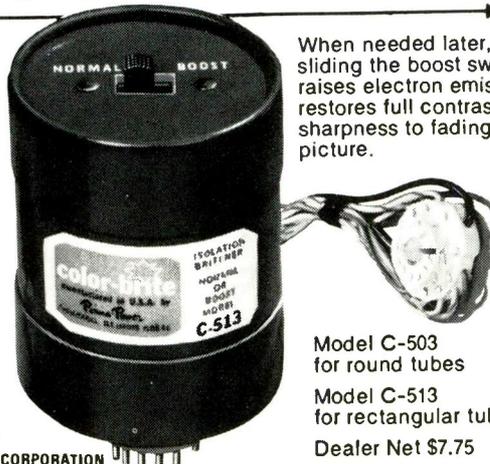This efficient new Britener corrects for cathode-to-filament shorts causing loss of black and white video drive... isolates the short, restores the black and white information necessary for color picture quality.



When needed later, sliding the boost switch raises electron emission, restores full contrast and sharpness to fading picture.

Model C-503 for round tubes

Model C-513 for rectangular tubes


Dealer Net \$7.75

Perma Power

PERMA POWER DIVISION OF CHAMBERLAIN MANUFACTURING CORPORATION

5740 North Tripp Avenue, Chicago, Illinois 60646 (312) 539-7171

Circle 24 on literature card

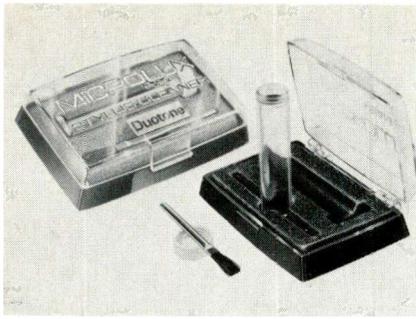

as an antistatic, according to the manufacturer. It reportedly is equally effective with diamond or sapphire stylus.

The Microlux stylus cleaner sells for \$2.50.

Circle 72 on literature card

X-R Series Metal Cassette

A new metal cassette which reportedly eliminates static charge problems developed by plastic cassettes has been introduced by Auricord Div. of Scovill.

Static charge problems are reduced because the metal cassette is a ground, draining off any static charges. The metal housing reportedly insures dimensional stability and contains two machined bearing tape guides for tape location and low internal friction. Temperature and humidity do not affect the stability of the metal cassette, and decreased flutter and wow are provided, according to the manufacturer.



The metal cassette will fit any standard cassette machine, and is offered in PRO 60-, 90-, or 120-minute lengths.

The X-R PRO 60 sells for \$3.95.

Circle 73 on literature card

Statement of Ownership, Management and Circulation, Act of August 12, 1970; Section 3685, Title 39, United States Code).


1. Title of Publication: Electronic Servicing
2. Date of Filing: September 27, 1971.
3. Frequency of Issue: Monthly
4. Location of known office of publication (Street, city, county, state, zip code): 1014 Wyandotte St., Kansas City, Jackson County, Missouri 64105.
5. Location of the headquarters or general business offices of the publishers (not printers): 1014 Wyandotte St., Kansas City, Jackson County, Missouri 64105.
6. Names and addresses of publisher, editor, and managing editor: Publisher, Robert E. Hertel, 1014 Wyandotte St., Kansas City, Missouri 64105; Editor, George H. Seferovich, 1014 Wyandotte St., Kansas City, Missouri 64105; Managing editor, J. W. Phipps, 1014 Wyandotte St., Kansas City, Missouri 64105.
7. Owner (if owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the names and addresses of the individual owners must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual must be given.) Howard W. Sams & Co., Inc.—a wholly owned subsidiary of International Telephone and Telegraph Corporation, 320 Park Ave., New York, New York 10022.

8. Known bondholders, mortgages, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages or other securities (if there are none, so state): None.
9. Paragraphs 7 and 8 include, in cases where the stockholders or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner. Names and addresses of individuals who are stockholders of a corporation which itself is a stockholder or holder of bonds, mortgages or other securities of the publishing corporation have been included in paragraphs 7 and 8 when the interests of such individuals are equivalent to 1 percent or more of the total amount of the stock or securities of the publishing corporation.
10. This item must be completed for all publications except those which do not carry advertising other than the publisher's own and which are named in sections 132.231, 132.232, and 132.233, postal manual (Sections 4355a, 435b, and 4356 of Title 39, United States Code).

	Average No. Copies Each Issue During Preceding 12 Months	Single Issue Nearest To Filing Date
A. Total No. Copies Printed (Net Press Run)	61,426	65,415
B. Paid Circulation		
1. Sales through dealers and carriers, street vendors and counter sales..	6,544	5,323
2. Mail Subscriptions..	48,835	52,946
C. Total Paid Circulation..	55,379	58,269
D. Free Distribution (including samples) by Mail, Carrier or Other Means	1,422	650
E. Total Distribution (sum of C and D)	56,801	58,919
F. Office Use, Left-Over, Unaccounted, Spoiled after Printing	4,625	6,496
G. Total (sum of E & F—should equal net press run shown in A)	61,426	65,415

I certify that the statements made by me above are correct. (Signature of editor, publisher, business manager, or owner).

ROBERT E. HERTEL

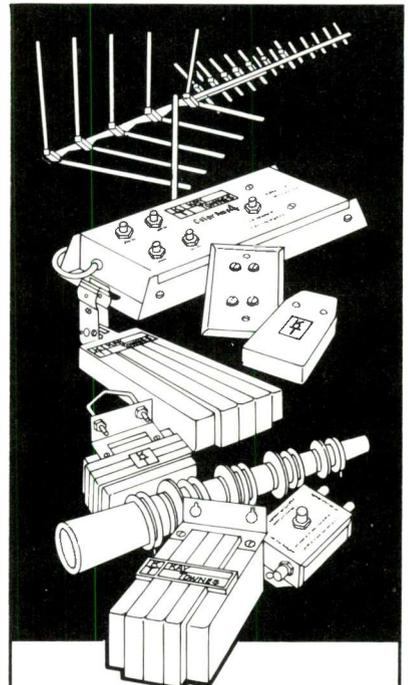

From Antennas to Wall Outlets KAY-TOWNES Makes Everything!

One supplier, one distributor can give you a complete line of high quality systems and components for better TV pictures and brighter sales pictures!

You can sell a complete line of

- All-Channel TV and FM Antennas
- Area Special Antennas for your location
- Hi-Carbon Golden Masts... telescoping or straight lengths
- Distribution Amplifiers and Systems
- Antenna Mounted Amplifiers and Couplers
- All related equipment including: Splitters, Couplers, Mixers, Wall-Taps and Drop-Taps.

Every Kay-Townes product is field tested, performance proved... and designed and manufactured in the U.S.A.

WRITE NOW FOR OUR COMPLETELY NEW MATV AND ANTENNA CATALOGS!

KAY-TOWNES

P.O. Box 593
Rome, Georgia 30161
Phone: (404) 235-0141

Circle 25 on literature card

by Joseph J. Carr/ES Auto Electronics Editor

Auto Cassette Players-- Drive Systems and Related Common Troubles

This month, we will look at the basic systems in auto cassette players, as well as some of the problems which are common to most, if not all, brands. We will bypass the audio amplifiers and motorspeed regulator circuits, because these are similar to circuits of similar function in four- and eight-track machines, which were covered in the January, 1971, issue of ES. In fact, some Japanese manufacturers use the same audio printed-circuit board in cassettes as that which they use in eight-track units.

The Cassette

A typical cassette is shown in Fig. 1. The player's capstan shaft fits through the bottom front lip of the cassette, in a position directly behind the tape. The pinch roller of the player fits through the front slot, to rest on the capstan, with the tape sandwiched between them.

The backside of the cassette is shown in Fig. 2. The two knock-outs, one on each side of the rear apron, prevent accidentally recording over recorded information which

you wish to retain. The knock-out is removed after a side has been recorded, as shown in Fig. 2. Most machines which can record have a lever that presses against the knock-out. If the little piece of plastic is missing, the lever will slide forward to prevent the record button from being activated.

This feature is often the source of the type of complaints for which "fixing the customer" will prove more successful than attempting to find a trouble in the set. Such a situation popped up recently in my shop. A fellow purchased a cassette recorder/playback machine with which is supplied a "sampler" cassette. These tapes usually have some type of music on one side and are blank on the other. The proud owner was trying to record on the pre-recorded side of his sampler.

The Player

A typical automotive-type cassette playback unit is shown in Fig. 3. This particular machine is the Craig Model 3501. The indicator lamp to the left of the loading slot

lights whenever a cassette is playing. The red lamp to the right of the slot turns on only after the cassette has finished playing. The play lamp will extinguish when the stop lamp comes on. The three center push buttons are, left to right rewind, manual eject, and fast forward. The other controls are tone, balance, and volume.

The drive system

The drive systems of most automotive cassette players fall into one of two basic categories: belt driven or idler driven. Both types use a drive belt between the motor pulley and the flywheel. The system we are calling belt driven, however, also uses either the same belt or an additional belt to drive the take-up spindle. Such a player, the Automatic Radio Model ACS-6000, is shown in Fig. 4. The undercarriage of the Craig 3501, which uses idler wheels to drive the take-up mechanism, is shown in Fig. 5. Notice that the idler style of player seems less complicated than the drive belt design. It isn't.

Fig. 6 is a side-view drawing of

Fig. 1 A typical cassette (top and front view).

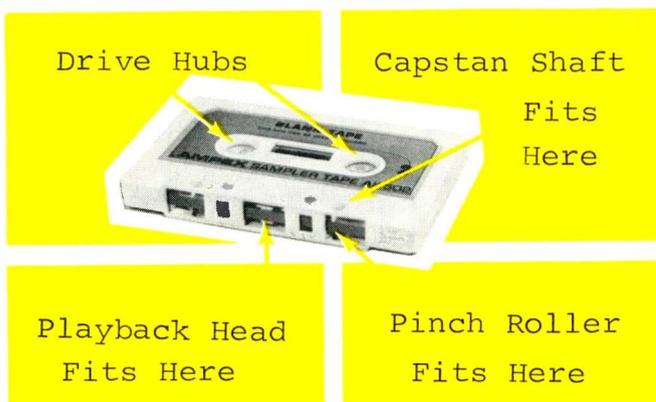


Fig. 2 Rear view of typical cassette, with anti-record notches pointed out.



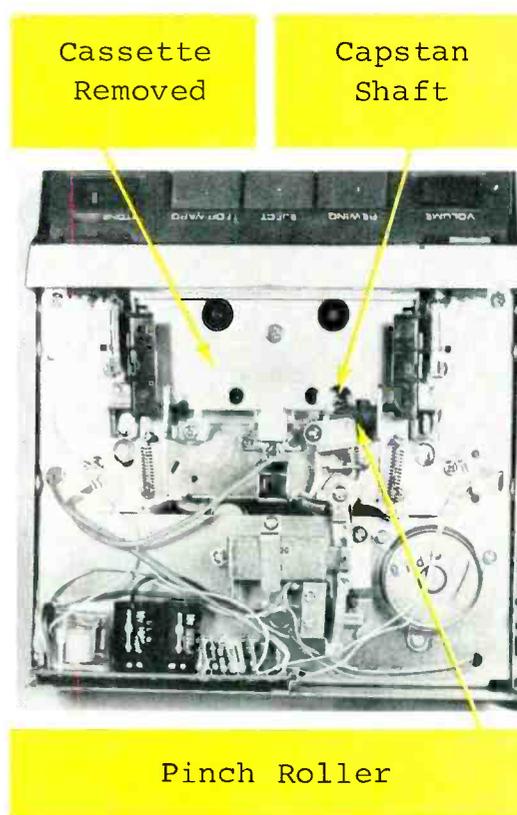
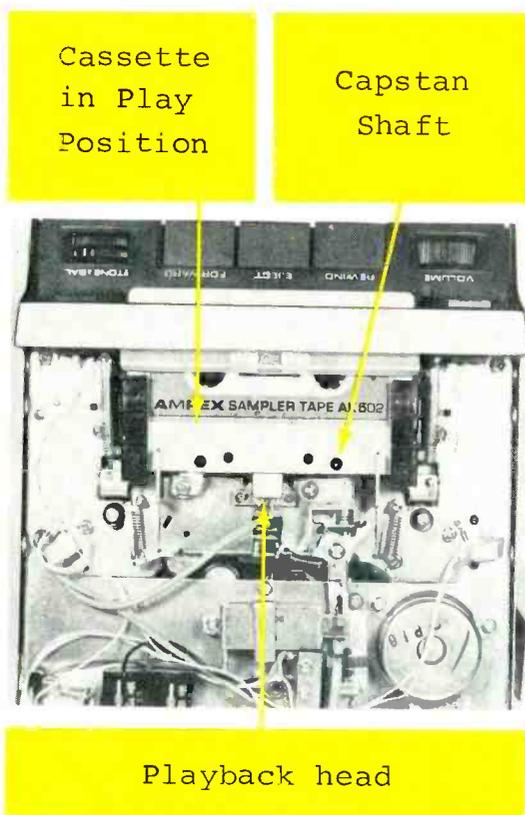
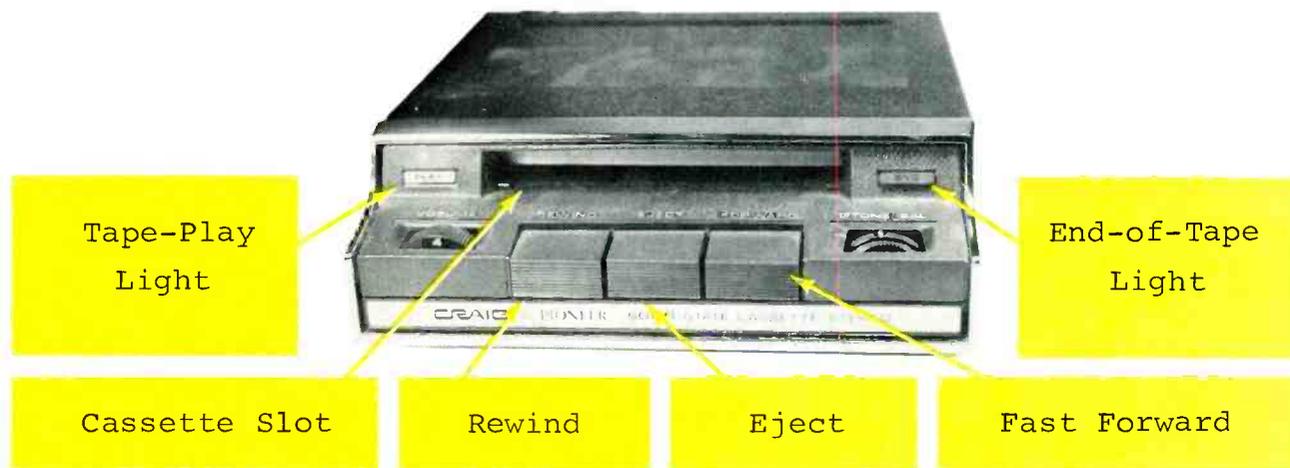


Fig. 3 A typical automotive cassette-type tape player, Craig Model 3501. A) Front view. B) Top view, with cassette in position to play. C) Top view, with cassette removed.

the capstan and flywheel assembly used in most cassette players. (The relative spacing is somewhat exaggerated, for illustration purposes. The capstan and bearing, for example, make a much closer fit.) The capstan shaft is attached and concentric to the flywheel. It fits through the chassis or cassette carriage via a sleeve bearing and flange. The rubber pinch roller is mounted to the top side of the chassis and presses against the cap-

stan. Pressure is generally supplied by a tension spring. This pressure is usually adjustable either by anchoring one end of the spring in one of several chassis holes or by turning a cam-screw assembly. The flywheel usually has two grooves for drive belts. The larger of the two is usually the motor belt.

In belt-driven take-up systems, there is usually a pulley and drive shaft assembly connected to the flywheel via a rubber belt. The drive

shaft rotates against a rubber tire on the rim of the take-up spindle. This is frequently a trouble point and will be discussed in greater detail later.

Fig. 7 shows the top view of a popular make of cassette player. The two black circular objects are the take-up reel (left) and the supply reel (right). The tape spindles and the motor-drive mechanism are mounted on a movable platform. When not in use, this platform is at

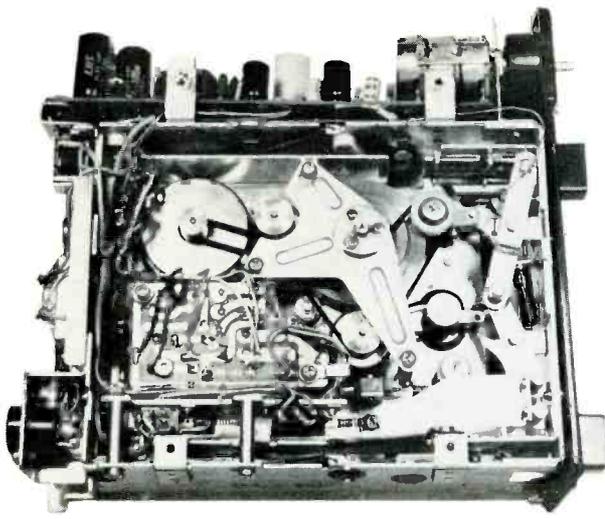


Fig. 4 Bottom view of Automatic Radio Model ACS-6000 cassette tape player, which used a belt-drive system between motor and flywheel and take-up sprocket.

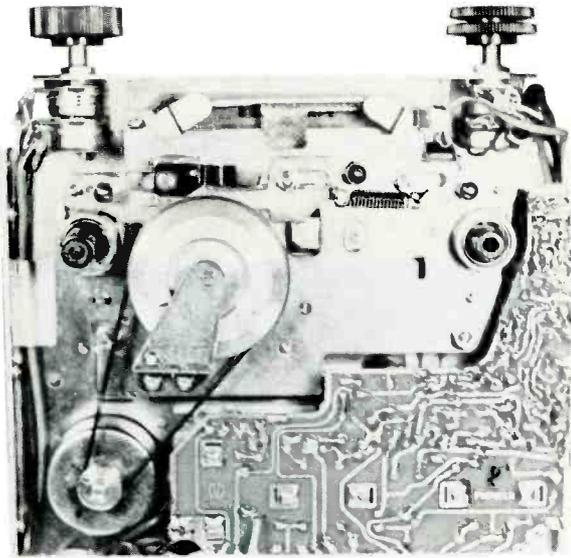


Fig. 5 Bottom view of Craig Model 3501 cassette tape player, which employs a belt between the motor pulley and the flywheel, but uses idler wheels to drive the take-up sprocket.

rest at the bottom of the machine. The cassette strikes two tape guide locks when it is inserted into the machine. This releases the mechanism and forces the platform up into the play position. When the cassette and the platform are both in position, several things occur simultaneously: 1) The power switch closes, energizing the circuits; 2) the pinch roller presses against the capstan shaft; 3) the spindles engage the two reel sprockets inside the cassette; and 4) a lock shaft on the platform engages the lock bar on the chassis. (This lock bar is mechanically coupled to the automatic eject solenoid.)

The automatic eject system

An automatic eject system, a feature found on most automotive cassette players, turns the machine off and ejects the cassette when a side has finished playing. This is done to prevent the tape leader from being torn off the supply reel at the end of play. (It is glued to the reel and is not an endless loop like the eight-track cartridge.) An electromechanical sensor tells the eject amplifier when the supply spindle has stopped turning. There are significant differences among the several popular types of sensors.

A version of one of the most popular sensors is shown in Fig.


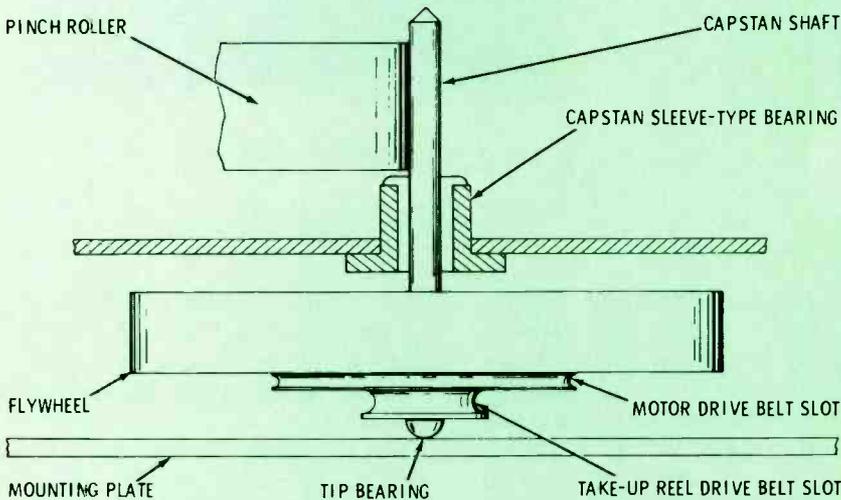


Fig. 6 Side-view drawing of capstan and flywheel assembly used in most automotive cassette tape players.

Drive Platform

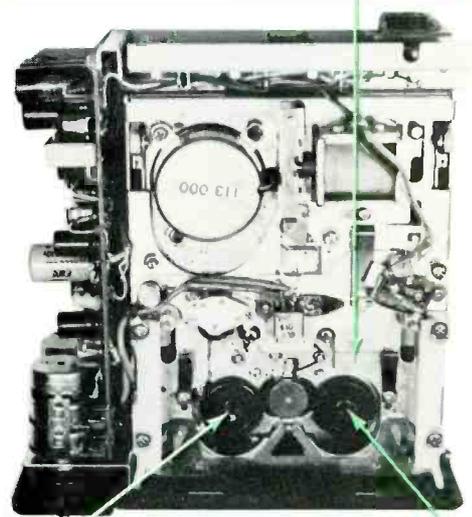

Take-up Reel

Supply Reel

Fig. 7 Top view of Automatic Radio Model ACS-6000 cassette tape player.

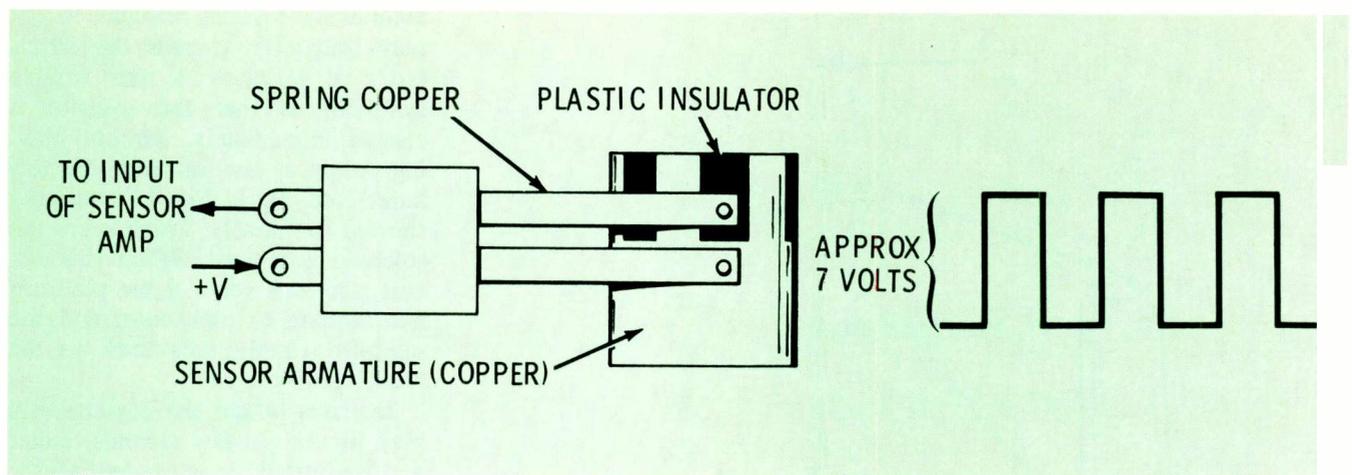


Fig. 8 A) Drawing of cartridge-stop sensor mechanism used in many cassette tape players. B) Rectangular pulse, produced by sensor mechanism, drives sensor amplifier.

8. The sensor armature is a cylindrical device which is attached concentrically to the supply spindle shaft. The bottom half of the armature is solid copper; the top half, however, consists of equal-size bands of copper and plastic insulator. The switch section of the sensor consists of two strips of spring copper resting on each of the two halves of the armature. The armature rotates whenever the supply spindle rotates. One of the switch leaves is connected to a positive voltage source, and the other is connected to the input of the sensor amplifier. This arrangement supplies a rectangular pulse of approximately 7 volts amplitude to the amplifier. Because the frequency output of most sensors is about 1 Hz, it might be impossible to view the pulse on an oscilloscope. This is one case where a conventional VTVM might be better for viewing a waveform than a scope.

Another sensor system is shown in Fig. 9. In this case the switch is two pieces of spring conductor which alternately "make and break" as a square-shaped cam rotates with the supply spindle. The output of this sensor is also a low-frequency rectangular pulse. Adjustment is accomplished by varying the position of the support block so that the contacts open on the high points of the cam and close on the flat portions.

Some cassette players use a magnetic sensor, such as that shown in Fig. 10. These sensors usually consist of two electromagnetic coils positioned above and below an interrupter disc. This disc is driven

by the supply spindle. The disc's rim is cut out so that metal alternately shields then exposes the two coils to each other. In this way, it alternately interrupts then restores the magnetic flux path between the two coils. A DC bias is supplied to one coil making it an electromagnet. This "shaded" induction produces a rectangular pulse across the leads of the opposite coil.

At least one brand of player uses an interrupter disc made of alternate sections of ferrite and powdered brass. The powdered iron of the ferrite sections will reinforce the flux density while the brass attenuates the flux. This produces the varying magnetic field necessary for transformer action.

Fig. 11 shows a typical cassette-stop/eject amplifier circuit. Pulses from the sensor are impressed on the base of the input transistor, Q1. Because Q1 is an NPN device, positive excursions of the input waveform cause an increase in collector-to-emitter current. This current also flows through resistor R2, developing across it an in-phase rectangular pulse of voltage. These pulses are coupled by capacitor C1 to a half-wave voltage doubler. The output of the doubler is used to charge a relatively large-value capacitor, C2. The charge on C2 forward biases NPN transistor Q2. The discharge path for C2 is through the transistor base-emitter junction and the two bias resistors. This discharge path has a time constant of 8 to 30 seconds, depending on the particular design. The forward biased condition of Q2 reduces the voltage at point A to almost zero. This pre-

vents Q3 from conducting, because its bias network is effectively shorted.

When the sensor stops rotating, the pulses cease. Because it is the nature of a capacitor to respond to voltage **changes**, instead of to an absolute DC level, the position of the sensor switch when the reel stops is unimportant. What is important is that the pulses have ceased. With nothing passing through the voltage doubler to keep C2 charged, it slowly discharges at a rate determined by the time constant (RC). When the voltage across C2 has dropped to the proper level, Q2 is cut off. Because there no longer is any collector current flowing through Q2, the voltage at point A returns to the "normal" level, which is sufficient to forward bias transistor Q3. The suddenly increased collector-to-emitter current in Q3 is sufficient to energize the eject solenoid, K1. This solenoid is coupled to the lock bar. When it moves out of the way, the cassette platform drops down to the "rest" position, and the cassette is forced out of the loading door. A closer view of this mechanism is shown in Fig. 12. The solenoid plunger pulls the lock bar up and releases the lock shaft, which is mounted to the movable cassette platform. When the lock shaft is released, gravity, assisted by a pair of power springs, returns the platform to the rest position.

Common Troubles and Their Causes

A very common complaint about

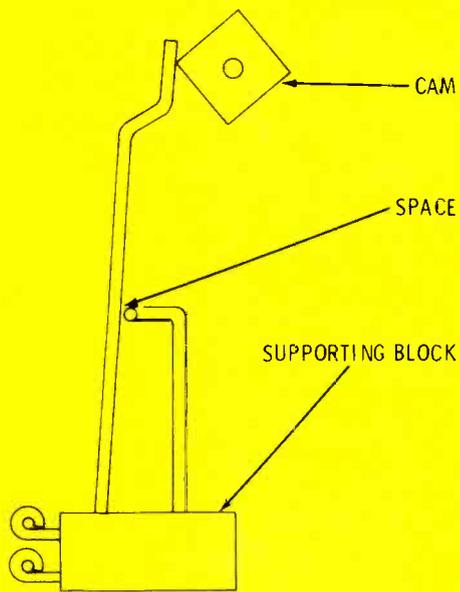


Fig. 9 Drawing of cam-type of cassette-stop sensor mechanism.

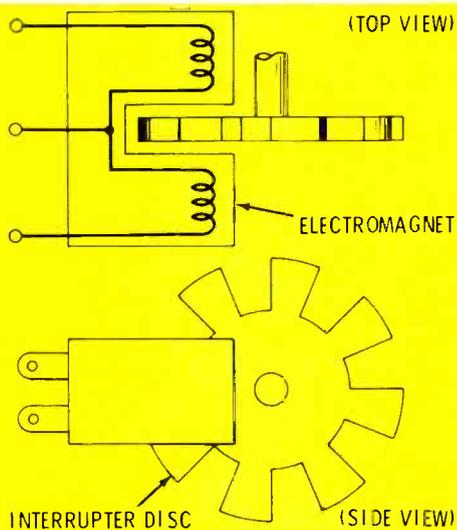



Fig. 10 Top- and side-view drawings of interrupter-disc-type of cassette-stop sensor.

automotive cassette machine is: "It plays only a few seconds, then drops out". A variation of this trouble symptom is that the cassette is ejected immediately, without playing, even a few seconds. In this latter case, Q3 in Fig. 11 is usually shorted completely, which keeps the solenoid energized. When this occurs, the lock shaft of the platform has nothing to lock onto, and the platform simply falls back to the "rest" position.

In cases where the cassette will play for only a few seconds, either a misadjusted or corroded sensor switch usually is the cause. It is best to replace both the sensor armature and switch leaves, if neither cleaning nor adjustment will restore proper functioning. Don't waste time troubleshooting the sense amplifier, until you have checked out the sensor switch and armature. I have found literally hundreds of defective sensors, but only a few defective sensor amplifiers.

The take-up spindle problem mentioned earlier is another common defect. A rubber belt drives the pulley drive shaft assembly, as shown in Fig. 13. The top edge of the drive shaft rubs directly against a rubber tire on the rim of the take-up spindle. If tension at this

Fig. 11 Typical cassette-stop / eject amplifier, which controls current to the eject solenoid, K1. Input to the amplifier section is the pulses from the sensor mechanism. See text for details of operation.

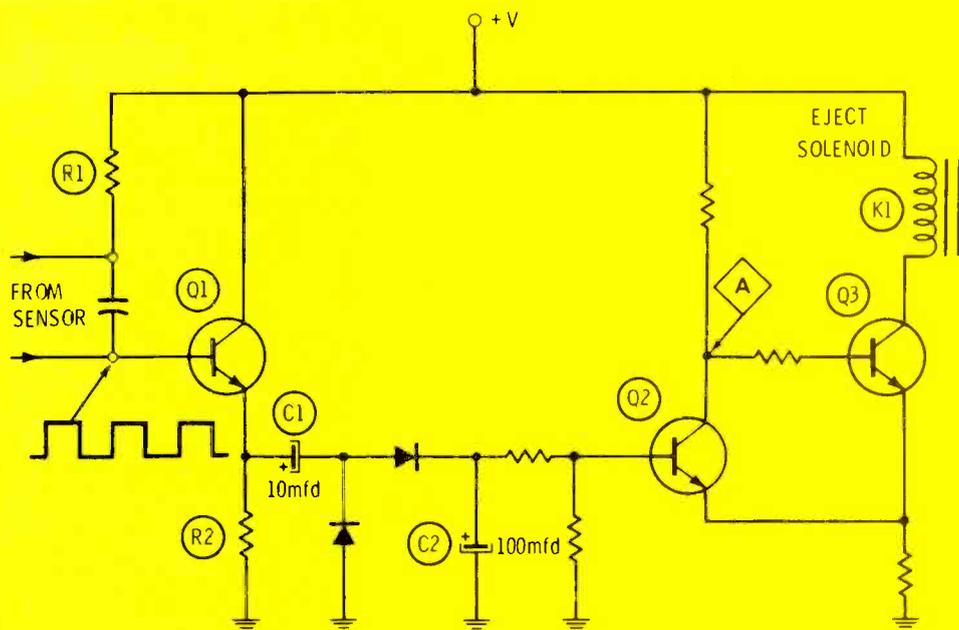

point is too great, or if the unit has been used a lot, the drive shaft will tend to undercut the rubber tire (Fig. 3B). This might have been prevented if the top edge of the drive shaft were higher than, or on the same level as, the top edge of the rubber tire. In any event, the rubber tire should be replaced if it shows any signs of such undercutting.

If the tire is severely undercut, the drive shaft will not make sufficient contact with it. This causes the take-up spindle to cease turning. The pinch roller and capstan, however, continue feeding tape. With the take-up reel not absorbing the slack, tape will begin feeding outside the cassette, into the pinch roller mechanism, and will wrap around the capstan shaft, eventually breaking. Multiple breaks are not uncommon.

Whether or not the tape actually breaks, I usually dispose of it. Most of the tape that spilled out of the cassette will be creased, twisted and otherwise damaged. A wrinkled tape is of little consequence when used in an eight-track unit, unless an extensive length of tape is damaged. Cassette players, however, have a small diameter capstan. Also, the top of the capstan is close to the top edge of the tape. A wrinkled

tape tends to ride up and down on the capstan. It is only a matter of time before the tape spills over the top of the capstan and into the mechanism once again.

Another cause of tape spill and breakage is a bent capstan shaft, which will tend to wobble against the pinch roller. There seems to be some doubt as to whether a bent shaft causes the sleeve bearing to wear out or whether a worn out sleeve bearing will allow the shaft to bend. In any event, it is true that they both are usually found together. It is a good idea, therefore, to replace both.

Tape spill, by the way, is a leading complaint about automotive cassette machines. It is so common, and the results are so drastic, that it is considered poor bench procedure to operate one of these units without first removing the covers to examine the take-up reel. Immediately after inserting the cassette (this turns on the machine), take a quick look at the take-up reel. If it fails to turn, immediately eject the cassette. Failure to do this quick enough can cause irreparable damage to the cassette. If the cassette just happens to be your test tape, you, or someone who is likely to yell very loudly, will have paid between four and twenty dollars for it. ▲

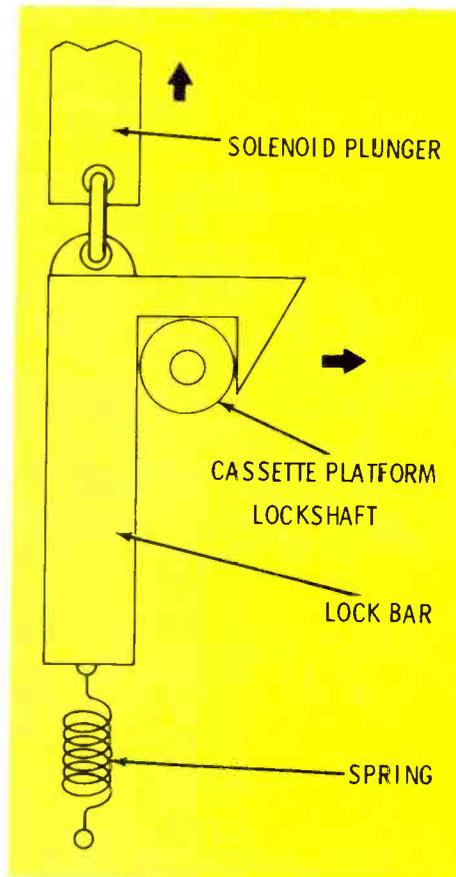


Fig. 12 Drawing of lock mechanism which holds cassette platform in play position until cassette-stop/eject amplifier energizes eject solenoid K1. Lock bar is then pulled up by solenoid plunger and cassette platform drops to "rest" position, forcing cassette out slot in front of player.

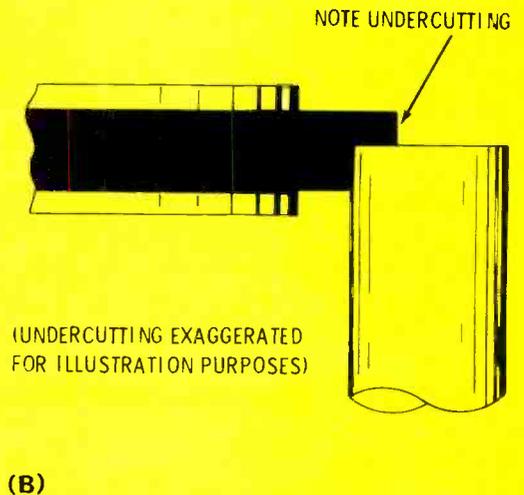
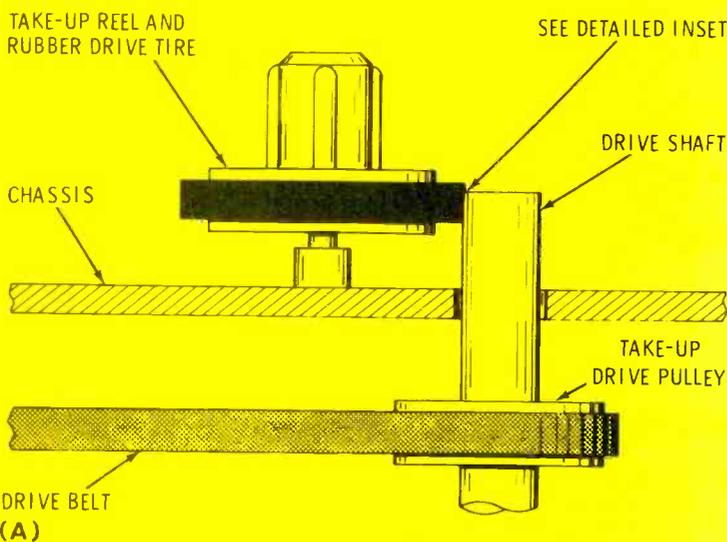


Fig. 13 A) Side-view drawing of take-up spindle drive mechanism. B) Enlarged view of drive shaft and rubber tire on take-up reel, showing undercutting of tire by shaft, caused by improper alignment and/or wear.

Source Guide To Imported Consumer Electronic Products

This guide correlates the brand name of an imported consumer electronic product with the manufacturer, importer and/or the distributor of that product and indicates whether or not that brand name is or has been covered in Howard W. Sams specialized series of transistor radio, auto radio and tape recorder manuals (TSM, AR and TR series) or in PHOTOFAC.

The number following each brand name indicates the most likely source from which service information and/or parts may be obtained, or to which a set may be sent for repair service. Before shipping a set, it is best to write the company indicated to determine if repair service is available, and if it is, what the company rules are concerning shipment of the set.

To provide continuous updating of this source guide, the editors of ELECTRONIC SERVICING would appreciate receiving from readers other brand names that are being used but do not appear here. If the manufacturer, importer and/or distributor is known, please include it. If it is not known, we will attempt to trace it and publish the information in ELECTRONIC SERVICING.

Complete

Manufacturer/Importer/Distributor list beginning on page 58

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
ACME	251	yes
AFCO	3	no
AGS	406	no
AITC	201	no
AKAI	4	no
AMC (Aimcee)	11	yes
AMD	483	yes
APF	5	no
Adell	8	no
Adonis	6	no
Advanco	10	no
Aimor	2, 45	no
Aircastle	399	yes
Aircorder	347	no
Airline	280	yes
Aiwa	12	yes
Aiwa (Milovac)	375	yes
Akai (Camart)	60	no
Akai (Roberts)	353	no
Alaron	41	yes
Alfred	64	no
Alliance	14	yes
Allied	16	yes
Alpha	299	yes
Alps	18	no
Ambassador	17	yes
Amertone	19	no
Amico	130	no
Ampex	22	yes
Angel	26	no
Annabel	41	no
Apolec	2	yes
Aristo	24	no
Aristocrat	37	yes
Aristo-Tone	24	no
Arrow	26	no
Astrex	460	no
Astrotone	231	yes
Audio-Lite	91	no
Audio Magnetics	33	no
Audio/Stereo	283	yes
Audion	34	no
Audiopak	32	no
Audiotape	32	no
Audiovox	35	yes
Audition	481	no

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Aud-I-Tone	206	yes	Cameo	28	yes	Crown (Industrial Suppliers)	196	yes
August Moon	148	no	Candle	61	yes	Crowncorder	90	no
Automatic	36	yes	Capehart	63	yes	Curtis-Mathes	92	yes
Auto Music	323	no	Capri (Nason)	291	no	Daltone	95	no
Auto-Sonic	258	yes	Capri (Toepfer)	432	no	Data Packaging	96	no
Aztec	39	no	Captain	487	no	Dec	94	no
BASF	40	no	Car Pal	35	no	Decca	97	yes
BSR (U.S.A.)	42	yes	Car Tapes	65	no	Dejay	98	no
B&K	41A	yes	Catalina	478A	yes	Delmonico	99	yes
Barkleigh	43	no	Cathy	306	no	Demco	79A	yes
Baron	50	no	Channel	70	no	Dempa	100	no
Baylor	468	yes	Channel Master	71	yes	Denon	301	no
Belaic	146	no	Chemicon	300	no	Denon (Sheraton)	379	no
Belair (Hamway)	177	no	Chinon	366	no	Dia	308, 309	no
Belair (Mason)	261	no	Cipher	268	yes	Dimension	427	no
Belair (Toko)	436	no	Citation	179	no	Dokorder (Pengo)	332	no
Belair (Toyo)	445, 446	no	Clairtone	75	yes	Dokorder (Wilson)	479	no
Belaire	146	no	Claricon	482, 483	yes	Dolphin	102	no
Belcor	44	no	Clarion	482, 483	yes	Domino	308, 309	no
Belcorder	177	no	Clark	77	yes	Doral	164	no
Bell & Howell	46	yes	Clasonic	76	no	Dorset	430	no
Benjamin	48	yes	Coach	101	no	Douglas	394	yes
Big Ben	438	no	Color Volt	392	no	Drexel	103	yes
Bigston	230	no	Columbia	79	yes	Dual	462	yes
Billion	373	no	Commodore	80	yes	Durpoint	104	yes
Birch	424	yes	Communica	439	no	Dyn	105	yes
Blaupunkt	52	yes	Concertone	81	yes	Dyn-Sonic	105	no
Boeing	50	no	Concertone (Monarch)	278	yes	Dynakits	106	no
Boman	57	no	Concord	82	yes	Dynatronics	197	yes
Bowman	57	yes	Constant	62	no	Dynavox	107	yes
Bozak	120	no	Consul	156	no	Ebner	136	no
Bradford	168	yes	Consul Delux	160	no	Echo	225	no
Brand 5	354	no	Contelcee	85	no	Echo Radio	108	no
Bravo	350	no	Continental	57	yes	Edital	120	no
Brenell	136	no	Coral	86	no	Eico	109	yes
Brightone	1	no	Coronado	154A	yes	Eicocraft	109	no
Broadmoor	55	yes	Coronet	26	yes	Eiwa	110	no
Browni	72	no	Cortina	109	yes	Eiwacorder	110	no
Bulova	56	yes	Corvair	453	yes	Elac	48	no
Bush	451	no	Corvette	272	yes	Eldorado	78	no
CBC	72	no	Country	222	no	Electra	111	no
CEC	74	no	Courier	86A	yes	Electro	112	yes
CONION	83	no	Craig	88	yes	Electro-Brand	112	yes
Caisonic	344	no	Crest	432	yes	Electrohome	113	yes
Califco	58	yes	Crest-Line	62	no	Electrohome	281	yes
			Crown	90	yes	Electro-Home	281	yes
						Electro-Phonic	281	yes
						Electro-Wipe	104	no

Source guide, continued . . .

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Elgin	118	yes	Galaxy	29	no	ISCO	196	yes
Elite	119	no	Garrard	159	yes	ITC (Ikegami)	193	no
Embassy	121	no	Gaytone	177	no	ITC (Int'l Transistor)	201	no
Emerald	203	no	Geloso	20	yes	ITT	192	yes
Emi	48	no	Gema	29	no	Ideal	199	no
Emud	99	yes	General	451	yes	Imperial	194	yes
Empire	448	no	Gibbs	57	yes	Imperial Delux	194	no
Empire	124	no	Gibson Girl	354	no	Impex	195	no
Encore	59	no	Gidget	36	no	Inland	197	yes
Engineers	356	no	Global	164	yes	Inmont-Cass/8	69, 70	no
Englishtown	399	yes	Globe	155	yes	Intermart	198	no
Epicure	126	no	Goer	166	no	Intersonic	202	no
Espo	128	no	Goer 8	70	no	Invico	67	no
Essex	237, 238	yes	Golden Shield	165	yes	Invicta	447	yes
Estey	129	no	Goodmans of England	119	no	Irish	203	no
Ever-Play	171	yes	Goodway	166	no	JFD	205	yes
E-Z Splice	104	no	Gotham	167	yes	JIL	208	no
Fabulloyds	238	no	Granada	146	no	JJJ	206	no
Faircrest	139	yes	Grand Prix	72	no	JVC (Delmonico)	99	yes
Fairfax	132	no	Gregory	169	yes	Jade	350	no
Fairmont	133	yes	Grenadier	123	no	Jaguar	293	yes
Fairmont	134	yes	Grundig	170	yes	Japarc	209	no
Falcon Sergeant G-2	116	no	Gusdorf	172	no	Jensen	210	no
Fanon	135	yes	Guy Barry	134	yes	Jeolco	211	no
Fantavox	257	no	HTV	175	no	Juli-corder	437	no
Fanuc	153	no	Halco	174	no	Juliette	441	yes
Facom	153	no	Hammarlund	114	yes	Juli-phone	437	yes
Federal	138	yes	Harlie	178	no	KCK	212	no
Fen-Tone	136	no	Harman-Kardon	179	yes	KLH	213	yes
Ferrograph	120	yes	Harp	145	no	Katone	216	no
Fidela	288, 289	no	Hatsune	181	no	Kaysons	218	no
Fidelity	356	no	Hemisphere	359	yes	Kensington	430	no
Fix Tuned	142	no	Heritage	182	no	Kent	219	yes
Fleetwood	455	yes	Hi-Delity	335	yes	Kenwood	220	yes
Foster	144	no	Highsky	204	no	Kenwood (Trio)	456	yes
Four Star	143	no	Highwave (Delmonico)	99	yes	Keystone	31	no
Fuji	147	no	Highwave (Marvel)	260	yes	Kilts	101	no
Fujiden	151	no	Hinode	183	no	Kitaron	223	no
Fujion	149	no	Hit	182	no	Kits	224	no
Fuji Ricoh	150	no	Hitachi	186	yes	Kleen-Sweep	104	no
Fujitsu	153	no	Hiwave	261	no	Knight	16	yes
Fujitsu Ltd.	152, 153	no	Hokuyo Musen	189	no	Kodam	225	no
Funia	154	no	Honey Tone	29	yes	Koronette	141	no
GC	155	no	Hosho	82	yes	Korting	5	yes
GRT	157	no	J. B. Hunter	17	no	Koss	226	no
GW	158	no	IEM	191	no	Koss-Acoustech	226	no

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Koss/Rek-O-Kut	226	no	Mars	256	no	Muskat	47	no
Kowa	227	yes	Martel	258	no	NAC	290	no
Koyo	228	yes	Marvel	251	yes	NACO	310	no
Kron	194	no	Mascot	356	yes	NAL	311	no
Kroy (York)	491, 492	yes	Master Control	483	no	NDK	302	no
Kuba	337	yes	Masterwork	263	yes	NGK	286	no
Kupi-Tone	478	no	Masterwork (Columbia)	79	yes	NIKKA	73	no
Kyocera	229	no	Matsushita	264	yes	NTK	286	no
LIC	241	no	Maxell	184	no	Nakamichi	288, 289	no
L.W.E.	7	no	Mayfair	27	yes	Nanaola	443	no
Lafayette	231	yes	Mecca	259	no	Nassau	423	no
Lamie	415	no	Medallion	272	yes	National	327	yes
Lark	59	no	Megatone	6	no	Nec (Kanamatsu)	214	yes
Leader	232	no	Melodian	221	no	Nec (Nippon)	303	yes
Leak	127	yes	Mercury	266	no	Nemco	287	no
Lear Jet Stereo 8	233	yes	Mercury (Pax)	330	yes	Net	294	no
Le-bo	234	no	Message Minder	53	no	Newell	2	no
Levtron	468	no	Metex	308, 309	no	Nichicon	297	no
Lexington	341	yes	Metro	269	no	Nitto	307	no
Liberty	235	yes	Mexko	342	no	Nivico (Delmonico)	99	yes
Lion	236	no	Micro	271	no	Nobility	295	no
Little Pal	251	no	Microsonic	344	no	Nocturne	179	no
Lloyd's	238	yes	Midland	272	yes	Nordmende	406	yes
Loben	433	no	Miharu	273	no	Norelco	312	yes
Longines Symphonette	239	yes	Mikado	274	no	North American	310	yes
Lord Barkleigh	43	no	Milovac	375	yes	Novel	147	no
Loyal	240	no	Mingon	415	no	NuVox	313	no
Lucky	241	no	Mini-Swinger	424	no	OKI	68	yes
Lulu	329	no	Miny	310, 259	no	OMGS	310	yes
Luxtone	242	no	Miracord	48	yes	Ocean	173	no
Lynn	243	no	Miradon	337	no	Ocean & Transonic	454	no
McIntosh	120	yes	Mirandette	15	no	Olson	318	yes
MGA	275	yes	Mitsubishi	275	yes	Olympic	319	yes
MYM	245	no	Mitsumi	276	no	Omron	321	no
Macrosonic	490	no	Miyakawa	277	no	Onkyo	325	no
Magatone	308, 309	no	Mody-Kit	54	no	Oral	322	no
Magnatone	129	yes	Monacor	278	yes	Orion	324	yes
Magnecord	425	yes	Monarch	278	yes	Orion (Fried Trading)	146	yes
Magnifique	356	no	Monarch (BSR)	42	yes	Ortofon	120	no
Magnus	249	no	Mondo	279	no	Oscar	93	no
Major	250	no	Moore	314	no	Pacific	326	no
Majorette	250	yes	Morse	281	yes	Panasonic	327	yes
Mallory	250A	yes	Mortone	203	no	Panger	427	no
Mantone	251	no	Muntz Stereo-Pak	283	yes	Paros	204	no
Marantz	252	yes	Murata	284	no	Patronic	328	no
Mar-Lin	253, 254	no	Musicolor	285	no			

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Pax	330	no	Rota	352	no	Singer	390	yes
Peerless	331	yes	Rotacorp	352	no	Skandia	391	no
Pencorder	341	no	Rotel	355	no	Skyfon	320	no
Penneys-Penncrest	333	yes	Roxy	315	no	Skymaster	295	no
Perfection	334	no	Royal	250	yes	Solo-phone	389	no
Perpetuum-Ebner	120	yes	Rozinante	357	no	Sonics	393	no
Pet	365	no	Rutherford	92	yes	Sonoco	395	no
Petely	335	no	St. Mortiz	251	no	Sonoramic	354	no
Peter Pan	424	no	SD	413	no	Sony/Superscope (Recorders)	410	yes
Petite	406	yes	SMK	388	no	Sony	397	yes
Phoenix	59	no	Saba	358	yes	Sound	304	yes
Phonola	425	yes	Samac	372	no	Sound N Color	109	no
Pianola	57	no	Sampson	200	yes	Soundesign	349	yes
Pickering	338	no	Sandhurst	6	no	Sovereign	379	no
Pioneer	339	no	Sandhurst	6	no	Spica	408	yes
Plata (Dyn)	105	yes	San-ei Instrument	360	no	Spico	398	no
Plata (Kaysons)	218	yes	Sankoh	362	no	Spinola	400	no
Playtape	89	no	Sanrin	363	no	Sportmaster	401	yes
Poly-Planer	247	no	Sansui	367, 368	yes	Squealer	71	no
Poly-Sonic	247	no	Sanyo	369	no	Stanbrooke	430	no
President	331	no	Satellite	49	yes	Standard	402	yes
Princeton	25	no	Saxony	450	yes	Stanford	404	no
Qatron	343	no	Scene	166	no	Stanton	120	no
Quickmount	247	no	Scene Tuner	69, 70	no	Starfire	255	no
Radiant	344	no	Scotch	244	no	Star-Lite	262	yes
Radiomaster	345	no	Scott	370	yes	Startone	190	no
Raleigh	218	yes	Seavox	146	no	Stellar	30	no
Ranger	427	yes	Seeburg	371	yes	Stereo-Dyn	105	no
Realistic	16	yes	Selecto	104	no	Stereo Dynetic	389	no
Realtone	349	yes	Seminole	364	yes	Stereo-Magic	405	no
Record-Matic	104	no	Sentry	31	no	Stereomatic	6	no
Recoton	350	no	Setico	376	no	Sterling	406	yes
Regency	350A	yes	Shamrock	203	no	Stewart	243	yes
Rembrandt Antennas	13	yes	Shannon	101	no	Sublime	347	no
Rhapsody	41	yes	Sharp	377	yes	Summit	408	no
Rising	188	no	Sharpe	378	no	Sun Bird (Katoh)	215	no
Rivera	292	no	Sharpe (Elpa)	120	no	Sun Bird	208	no
Roberts	353	yes	Sheraton	379	yes	Sun Glass	20	no
Roberts Ross	431	no	Sherwood	380	yes	Sunny-vox	386	no
Robette	180	no	Shibaden	383	yes	Sunsonic (Sankei)	361	no
Robin	261	yes	Shimadzu	384	no	Sunsonic	407	no
Robins	354	yes	Shin-ei	385	no	Suora	103	no
Robyn	354A	yes	Shin-Shirasuna	387	no	Super Dynamic	413	no
Rolecor	355	no	Shure	389	no	Superex	409	yes
Romar	340	no	Silver	387	yes	Supersonic	399	yes
Ross	356	yes				Supre-Macy	246	yes

Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage	Brand Name	Manufacturer, Importer and/or Distributor	Sams Coverage
Sylvano	23	no	Tonecrest	270	yes	Viscount	84	yes
Symphonette	239	yes	Tonemaster (Broadmoor)	55	yes	Vision	468	yes
Synchronex	344	no	Tonemaster (TAC)	451	yes	Vista	88	yes
TDK	413	no	Tonex	59	no	Voca	469	no
TDK Cassette	413	no	Toshiba	442	yes	Vornado (Automatic)	36	no
TMK	447	no	Toshiba (Trans World)	453	yes	Vornado	470	yes
TWI	455	no	Toshri	137	no	Wald	471	no
Tact (Fried)	146	no	Townley	125	no	Waltham (Int'l Importers)	200	no
Tact (Hamway)	177	no	Trancel	453	yes	Waltham	472	no
Taico	414	no	Transcriber	452	no	Watts	120	no
Takt	416	no	Transette	272	yes	Wealth (Funia)	154	no
Tamradio	417	no	Transicorder	305	yes	Wealth (Toyomenka)	447	no
Tamura	418	no	Transonic	453	yes	Weather Ear	121	no
Tandberg	419	yes	Transworld	115	no	Weltron	475	yes
Taya	444	no	Trio	456	no	Webcor	474	yes
Teac (Teac)	420, 420A	yes	Triumph	458	yes	Westinghouse	476	yes
Teaberry	419A	yes	Tropicana	45	no	Wharfedale	478	no
Technicorder	317	no	Troubador	123	no	Wilco	369	yes
Tel	427	no	Truetone	477	yes	Wilson	480	no
Telecon	421	yes	Tussah	459	no	Windsor	481	no
Telefunken	422	yes	Twin XX Twenty	247	no	Winston	447	yes
Tele-Tone	424	yes	USAC	463	no	Winston	477	yes
Telex	425	yes	Uher	258	yes	Wollensak	244	yes
Telex-Phonola	425	yes	Ultra-82	467	no	XAM	374	no
Telmar	426	yes	Unelco	460	no	YAOU	162	yes
Telmar (Martel)	258	yes	Unicord	20	no	Yamaha	485	no
Tempest	38	no	Unidyne	389	no	Yamatake-Honeywell	487	no
Ten (Fujitsu)	152, 153	yes	Unimetrics	231	no	Yaskawa	489	no
Ten (Sanyo)	369	yes	Union	461	no	Ye	486	no
Ten Brand	35	no	Unisphere	389	no	Yec	493	no
Tenna	427	yes	United Audio	462	no	Yew	490	no
Tennac	428	no	Valencia	208	no	York	492	yes
Tennamatic	427	no	Valient	464	yes	York (N.Y. Transistor)	296	yes
Tenphonic	429	no	Vantage	131	yes	Zenon	494	no
Thorens	120	yes	Velk	465	no			
Three-Star	291	no	Venice	316	no			
Tobi-Sonic	27	no	Versatek	121	no			
Toho	438	no	Vesper	434	yes			
Tokai	434, 435	yes	Viking	425	yes			
Toko	436	no	Vikoa	467	no			

**Complete
Manufacturer/Importer/Distributor list
beginning on page 58**

Manufacturer/Importer/Distributor List

1. A&A Trading Co.
23 E. 26th St.
New York, N.Y.
2. ABC Import & Export
47 W. 30th St.
New York, N.Y.
3. AFCO Electronics, Inc.
P.O. Box 973
Oakland, Calif. 94604
4. AKAI America, Ltd.
2139 E. Bell Amo Blvd.
Compton, Calif. 90020
5. APF Electronics, Inc.
515 Madison Ave.
New York, N.Y. 10022
6. A&S Trading Co.
124 W. 30th St.
New York, N.Y. 10001
7. Acoustron Corp.
2418 Bartlett
Houston, Tex. 77006
8. Adell International, Inc.
43700 Adell Blvd.
Novi, Mich. 48050
10. Advance Transistor Co.
1225 Broadway
New York, N.Y.
11. Amcrest Corp.
1440 Broadway
New York, N.Y. 10018
12. Aiwa International Corp.
One E. Wacker Dr.
Chicago, Ill. 60611
13. All Channel Products, Corp.
47-75 48th St.
Woodside, N.Y.
14. Alliance Mfg. Co., Ltd.
Lake Park Blvd.
Alliance, Ohio
15. Allied Impex Corp.
300 Park Ave. S.
New York, N.Y.
16. Allied Radio Shack
2617 W. 7th St.
Ft. Worth, Tex. 76107
17. Allied Stores Purchasing
401 Fifth Ave.
New York, N.Y. 10016
18. Alps Electric Co., Ltd.
c/o Kanamatsu-Gosho (USA),
Inc.
One Whitehall St.
New York, N.Y. 10004
19. Amerex Trading Co.
417 Fifth Ave.
New York, N.Y.
20. American Geloso Electronics,
Inc.
251 Park Ave. S.
New York, N.Y. 10010
21. American Sankyo Corp.
149 Fifth Ave.
New York, N.Y. 10004
22. Ampex Corp.
Landmeyer Rd.
Elk Grove Village, Ill. 60007
23. Apex Repair Center
1141 Broadway
New York, N.Y.
24. Aristo-Tone Electronics
240 Fifth Ave.
New York, N.Y. 10001
25. Arlans Dept. Stores, Inc.
393 Seventh Ave.
New York, N.Y. 10001
26. Arrow Trading Co.
Seven W. 26th St.
New York, N.Y.
27. Artic Import Co.
(Bee Electronics)
(Mayfair Electronics Corp.)
666 W. Kinzie St.
Chicago, Ill.
29. Associated Importers
34 Dore St.
San Francisco, Calif.
30. Astra Trading Co.
175 Fifth Ave.
New York, N.Y. 10010
32. Audio Devices, Inc.
235 E. 42nd St.
New York, N.Y.
33. Audio Magnetics Corp.
14600 S. Broadway
Gardena, Calif. 90247
34. Audion Corp.
200 Fifth Ave.
New York, N.Y.
35. Audiovox Corp.
300 Denton Ave.
New Hyde Park, N.Y. 11040
36. Automatic Radio Sales
Two Main St.
Melrose, Mass. 02176
37. Automotive Associates
551 Fifth Ave.
New York, N.Y. 10017
38. Azad International
22 W. 27th St.
New York, N.Y.
39. Aztec Sound Corp.
2140 S. Lipan St.
Denver, Colo.
40. BASF Systems, Inc.
Crosby Dr.
Bedford, Mass. 01730
41. B&B Import & Export Co.
15755 Wyoming Ave.
Detroit, Mich. 48238
- 41A. B & K Dynascan Corp.
1801 W. Belle Plaine Ave.
Chicago, Ill. 60613
42. B.S.R. (USA), Ltd.
Route 33
Blauvelt, N.Y. 10913
43. Barker Stores
815 Hutchinson River Parkway
Bronx, N.Y. 10465
44. Belcor Corp.
457 Chancellor Ave.
Newark, N.J.
45. Bell Electronics
1180 Broadway
New York, N.Y. 10009
46. Bell & Howell Co.
7235 N. Linder Ave.
Skokie, Ill. 60076
47. Bel-Mar, Inc.
1942 N.E. 151st St.
N. Miami Beach, Fla. 33160
48. Benjamin Electronic Sound Co.
40 Smith St.
Farmingdale, Long Island, N.Y.
11736
49. Best of Tokyo
11 W. 42nd St.
New York, N.Y.
50. Boeing Electronics Co., Ltd.
1-9, Ryocho Sakata City
Yamagata, Japan
52. Robert Bosch Corp.
2800 S. 25th Ave.
Broadview, Ill. 60153
53. Boston Worldwide
148 State St.
Boston, Mass.
54. Bowman Electronics
155 E. First Ave.
Roselle, N.J.
55. Broadmoor Industry, Ltd.
530 Santa Rosa Dr.
Des Plaines, Ill. 60018
56. Bulova Watch Co.
630 Fifth Ave.
New York, N.Y. 10020
57. California Auto Radio, Inc.
9426 Stewart & Gary Rd.
Downey, Calif.
58. California Trading Co.
P.O. Box 3164
Torrance, Calif.
59. Caltrade Mfg. & Trading Co.
360 Ninth St.
San Francisco, Calif. 94103
60. Camart Products
Repair Center
1845 Broadway
New York, N.Y.
61. Candle America, Inc.
1457 Venice Blvd.
Los Angeles, Calif. 90006
62. Canton-Son, Inc.
12 W. 27th St.
New York, N.Y.
63. Capehart Corp.
770 Lexington Ave.
New York, N.Y. 10021
64. Capin Mercantile Corp.
109 Nelson Ave.
Nogales, Ariz. 85621
65. Car Tapes, Inc.
320 W. Ohio St.
Chicago, Ill. 60610
66. Cardinal Electronics
5069 Broadway
New York, N.Y.
67. Challenge Corp.
150 Fifth Ave.
New York, N.Y.
68. Chancellor Electronics, Inc.
457 Chancellor Ave.
Newark, N.J. 07112
69. Channel Marketing, Inc.
26 Springdale Rd.
Cherry Hill, N.J. 08034
70. Channel Marketing, Inc.
342 Madison Ave.
New York, N.Y.
71. Channel Master
Ellenville, N.Y. 12428
72. Charles Brown & Co.
1170 Broadway
New York, N.Y. 10001
73. Chiyoda Electronic Co., Ltd.
3-9, Soto Kanda 3-chome,
Chiyoda-ku
Tokyo, Japan
74. Chuo Denki Co., Ltd.
1767 Aza Higashidaira,
Higashi Matsuyama
Saitama, Japan
75. Clairtone Electronic Corp.
100 Ronson Dr.
Rexdale, Ontario, Canada
76. Clarion Shoji Co., Ltd. (USA)
2306 Cotner Ave.
Los Angeles, Calif. 90064
77. David Clark Co., Inc.
360 Franklin St.
Worcester, Mass. 01604
78. A. Cohen & Sons, Inc.
27 W. 23rd St.
New York, N.Y. 10010
79. Columbia Records Corp.
51 W. 52nd St.
New York, N.Y. 10019
- 79A. Command Electronics, Inc.
11830 Shaver Rd.
Schoolcraft, Mich. 49087
80. Commodore Import Corp.
507 Flushing Ave.
Brooklyn, N.Y. 11205
81. Concertone, Inc.
7035 Laurel Canyon Blvd.
N. Hollywood, Calif. 91605
82. Concord Electronics Corp.
1935 Arnacost Ave.
W. Los Angeles, Calif. 90025
83. Coney Onkyo Co., Ltd.
1-23, Iwaya Kita-machi 5-chome,
Nada-ku
Kobe, Japan
84. Consolidated Merchandising
Corp.
59-50 Queens Midtown Expwy,
Maspeth, N.Y. 11378

85. Continental Telephone Answering Devices
17 W. 46th St.
New York, N.Y.
86. Coral Audio Corp.
8-9, Soto-Kanda 3-chome,
Chiyoda-ku
Tokyo, Japan
- 86A. Courier Communications, Inc.
100 Hoffman Pl.
Hillside, N.J. 07205
87. Craig Panorama, Inc.
2302 E. 15th St.
Los Angeles, Calif. 90021
88. Craig Corp.
921 W. Artesia Blvd.
Compton, Calif. 90220
89. Craigstan Corp.
1115 Broadway
New York, N.Y.
90. Crown Radio Corp.
228 E. Harris Ave.
S. San Francisco, Calif. 94080
91. Curtis-Electro Lighting, Inc.
1536 S. Paulina St.
Chicago, Ill. 60608
92. Curtis-Mathes Sales Co.
P.O. Box 151
Athens, Tex. 75751
93. Daishin Electric Industry Co., Ltd.
2-5, Ohmori-minami, Chta-ku
Tokyo, Japan
94. Daiwa, Ltd.
1, Nihonbashi, Edobashi
2-chome, Chuo-ku
Tokyo, Japan
95. Dalamai & Sons
107 Franklin
New York, N.Y. 10002
96. Data Packaging Corp.
205 Broadway
Cambridge, Mass. 02139
97. MCA Dist. Corp.
445 Park Ave.
New York, N.Y. 10022
98. Dejay Industries
90 N. Washington St.
Boston, Mass.
99. Delmonico International
50-35 56th Rd.
Maspeth, L. I., N.Y. 11378
100. Delta International, Ltd.
P.O. Box 1946
Grand Junction, Colo.
101. Dictotape, Inc.
9090 Krier Place
Brooklyn, N.Y. 11236
102. Dolphin Sansho, Ltd.
11-13, Shimoigusa 5-chome,
Suginami-ku
Tokyo, Japan
103. Drexel Radio Corp.
P.O. Box 15156
New Orleans, La.
104. Duotone Co., Inc.
6875 SW 81st St.
Miami, Fla. 33143
105. Dyn Assoc. Importers, Inc.
270 W. 22nd St.
Hialeah, Fla. 33010
106. Dynaco, Inc.
3060 Jefferson St.
Philadelphia, Pa. 19121
107. Dynavox Electronics Corp.
40-05 21st St.
Long Island City, N.Y. 11101
108. Echo Tsushin Kogyo Co., Ltd.
29-9, Shimo Sueyoshi 1-chome,
Tsurumi-ku
Yokohama, Japan
109. Eico Electronic Instrument Co., Inc.
283 Malta St.
Brooklyn, N.Y. 11207
110. Eiwa Sangyo Co., Ltd.
6-11, Nishi Shinbashi 2-chome,
Minato-ku
Tokyo, Japan
111. Electra Radio Corp.
30 W. 23rd St.
New York, N.Y.
112. Electro-Brand, Inc.
210-220 W. Chestnut
Chicago, Ill. 60610
113. Electrohome, Ltd.
809 Wellington St. N.
Kitchener, Ontario, Canada
114. Electronic Assistance Corp.
20 Bridge Ave.
Red Bank, N.J. 07701
115. Electronic Industries, Inc.
901 Daniel St.
Kenner, La. 70062
116. Electronic Research & Development, Ltd.
6th Floor, Shiozaki Bldg. 7,
Hirakawa-cho, 2-chome,
Chiyoda-ku
Tokyo, Japan
118. Elgin National Industries, Inc.
50-35 56th Rd.
Maspeth, N.Y. 11378
119. Elite Electronics
195 E. Central Ave.
Farmingdale, N.Y. 11735
120. Elpa Marketing Industries, Inc.
Thorens & Atlantic Ave.
Garden City Park, N.Y. 11040
121. Embassy
5330 E. 38th St.
Indianapolis, Ind. 46218
123. Empire Scientific Corp.
1055 Stewart Ave.
Garden City, N.Y. 11530
124. Empire Ultrasonics, Ltd.
1199 Broadway
New York, N.Y. 10001
125. The Englishtown Corp.
42 Broadway
New York, N.Y. 10004
126. Epicure Products, Inc.
185 Somerville Ave.
Somerville, Mass. 02143
127. Ercona Corp.
432 Park Ave. S.
New York, N.Y. 10016
128. Espo Engineering Corp.
5334 W. 65th St.
Chicago, Ill. 60638
129. The Estey Co., Div. of Electro-Learner Corp.
Ziegler St.
Harmony, Pa.
130. Exhibit Sales Co.
South Third St.
Philadelphia, Pa. 19106
131. Fairfax Dist. Co., Inc.
1328 New York Ave. N.W.
Washington, D.C.
132. Fairfax Industries, Inc.
165 Ward St.
Paterson, N.J. 07505
133. Fairmont Electronics, Inc.
55 W. 39th St.
Suite 506
New York, N.Y. 10018
134. Fairmont Electronics
12 Crescent St.
Holyoke, Mass.
135. Fanon Electronic Industry
100 Hoffman Pl.
Hillside, N.J. 07205
135. Fen Tone International
106 Fifth Ave.
New York, N.Y. 10011
137. Fedco, Inc.
P.O. Box 2605
Terminal Annex
Los Angeles, Calif. 90054
138. Federal Transistor Co., Inc.
519 S. Broadway
Los Angeles, Calif. 90013
139. J.M. Fields
111 8th Ave.
New York, N.Y.
141. Fisher Sonic Co., Inc.
405 44th St.
Brooklyn, N.Y.
142. Fix Tune Solid State Electronics
One W. 30th St.
New York, N.Y. 10001
143. Fortune Star Products
1207 Broadway
New York, N.Y. 10001
144. Foster Electric Co., Ltd.
230 N. Michigan Ave.
Chicago, Ill. 60601
145. L. K. Franklin Co.
8412 S. Olympic Blvd.
Beverly Hills, Calif.
146. Fried Trading Co.
425 Bedford Ave.
Brooklyn, N.Y. 11211
147. Fuji Electrochemical Co., Ltd.
437 Fifth Ave.
New York, N.Y. 10016
148. Fuji Electronics Co., Ltd.
Mikko Mita Bldg., 26-4
Takanawa
1-chome, Minato-ku
Tokyo, Japan
149. Fuji Onkyo Co., Ltd.
15-13 Shimomaruko 1-chome,
Ohta-ku
Tokyo, Japan
150. Fuji Ricoh Co., Ltd.
1046-2 Ikebukuro Toshima-ku
Tokyo, Japan
151. Fujiden International Corp., Hase Bldg., 25, Bingomachi 3-chome,
Higashi-ku
Osaka, Japan
152. Fujitsu California, Inc.
16410 S. Figueroa St.
Gardena, Calif. 90247
153. Fujitsu, Ltd.
680 Fifth Ave.
New York, N.Y. 10019
154. Funai Electric Co., Ltd.
3004 W. Logan Blvd.
Chicago, Ill. 60647
- 154A. Gamble-Skogmo, Inc.
P.O. Box 458
Minneapolis, Minn. 55440
155. GC Electronics Co.
400 S. Wyman St.
Rockford, Ill. 61101
156. GCL Mercantile Corp.
36 Utter Ave.
Hawthorne, N.J. 07507
157. GRT Corp.
1286 N. Lawrence Station Rd.
Sunnyvale, Calif. 94086
158. GW Electronics, Inc.
1647-4 S. Sepulveda Blvd.
Torrance, Calif.
159. Garrard, Div. of British Industries Co.
Westbury, N.Y. 11590
160. General Consolidated
87 Dell Gen Ave.
Lodi, N.J.
161. The General Corp., Chicago
500 Fullerton Parkway
Chicago, Ill. 60614
162. General Corp.
Master Apartment
310 Riverside Dr.
New York, N.Y. 10025
164. Global Import & Export
858 W. Flagler St.
Miami, Fla. 33139
165. Golden Shield Corp.
56 Harvester Ave.
Batavia, N.Y.
166. Goodway, Inc.
11401 Roosevelt Blvd.
Philadelphia, Pa.
167. Gotham Electronics, Inc.
170 Michael Dr.
Syosset, N.Y. 11791
168. W. T. Grant Co.
1441 Broadway
New York, N.Y. 10018
169. Gregory Amplifier Corp.
3650 Dyra Ave.
Bronx, N.Y.
170. Grundig Electronic Sales
355 Lexington Ave.
New York, N.Y. 10017

Manufacturer / Importer / Distributor List continued . . .

- | | | | |
|--|---|---|---|
| 171. Gulton Industries
212 Durham Ave.
Metuchen, N.J. | 196. Industrial Suppliers
755 Folsom St.
San Francisco, Calif. 94107 | 219. Kent Overseas, Inc.
38 W. 33rd St.
New York, N.Y. | 241. Lucky International
1155 Broadway
New York, N.Y. 10010 |
| 172. Gusdorf & Sons, Inc.
6900 Manchester Ave.
St. Louis, Mo. 63143 | 197. Inland Dynatronics, Inc.
10 Horizon Blvd.
S. Hackensack, N.J. 07606 | 220. Kenwood Corp.
69-41 Calamus Ave.
Woodside, N.Y. | 242. Luxor International
39 W. 29th St.
New York, N.Y. |
| 173. Hachiyo Electric Sound Co., Inc.
3-6, Higashigaoka 2-chome,
Meguro-ku
Tokyo, Japan | 198. Intermart Corp.
147 W. 42nd St.
New York, N.Y. | 221. Keystone Electronics Corp.
11, Hirakawacho 1-chome,
Chiyoda-ku
Tokyo, Japan | 243. Lynn Stewart Co.
439 E. Illinois St.
Chicago, Ill. 60611 |
| 174. Halen Associates
25 Fifth Ave.
New York, N.Y. 10003 | 199. International Distributors, Inc.
1178 Pope St.
Memphis, Tenn. 38102 | 222. King Korn Marketing Div.
of Fullview Industries, Inc.
6001 N. Clark St.
Chicago, Ill. 60626 | 244. 3M Company Mincom Div.
3M Center
St. Paul, Minn. 55101 |
| 175. Hamamatsu TV Co., Ltd.
c/o Kinsho-Mataichi Corp.
80 Pine St.
New York, N.Y. 10005 | 201. International Transistor
1206 S. Maple
Los Angeles, Calif. | 223. Kitaron Electric Co., Ltd.
1-13, Arakawa 1-chome,
Arakawa-ku
Tokyo, Japan | 245. MYM Trans-World Corp.
1165 Broadway
New York, N.Y. |
| 177. Hamway Import Co.
40 W. 29th St.
New York, N.Y. 10001 | 202. Intersonic Corp.
P.O. Box 215
Rockaway, N.J. 07866 | 224. Kits Industries, Inc.
729 Ceres Ave.
Los Angeles, Calif. 90021 | 246. Macy's Dept. Store
Herald Square
New York, N.Y. 10001 |
| 178. Harlie Transistor Products
393 Sagamore Ave.
Mineola, L.I., N.Y. | 203. Irish Tape Div. Morhan
National Sales Co., Inc.
458 Broadway
New York, N.Y. 10013 | 225. Kodama Chemical Industry
Co., Ltd.
7-3, Soto Kanda 6-chome,
Chiyoda-ku
Tokyo, Japan | 247. The Magitron Co., Div. Era
Acoustics Corp.
311 E. Park St.
Moonachie, N.J. 07074 |
| 179. Harman-Kardon, Inc.
55 Ames Court
Plainview, N.Y. 11803 | 204. Izumi Co., Ltd.
9-13, 1-chome, Meauro Honcho,
Meauro-ku
Tokyo, Japan | 226. Koss Electronics, Inc.
2227 N. 31st St.
Milwaukee, Wisc. 53208 | 249. Magnus Organ Corp.
1600 W. Edgar Rd.
Linden, N.J. 07036 |
| 180. Haskel Howard Co.
21 Hazelton Rd.
Yonkers, N.Y. | 205. JFD Electronics Corp.
62nd St. at 15th Ave.
Brooklyn, N.Y. | 227. Kowa American Corp.
276 Fifth Ave.
New York, N.Y. | 250. Major Electronics Corp.
649 39th St.
Brooklyn, N.Y. |
| 181. Matsune Electric Industrial
Co., Ltd.
Yatsurugi, Twakura-cho,
Niwa-gun
Aichi, Japan | 206. J.J.J. Merchandise
15 W. 26th St.
New York, N.Y. 10010 | 228. Koyo International, Inc. of
America
330 Madison Ave.
New York, N.Y. 10017 | 250A. P. R. Mallory & Co., Inc.
3029 E. Washington St.
Indianapolis, Ind. 46206 |
| 182. Heritage International Trading
Co.
1330 Stuyvesant Ave.
Union, N.J. 07083 | 208. Japan Industry, Ltd.
Kawazu Bldg., 4 Kitayacho,
Shibuya-ku
Tokyo, Japan | 229. Kyocera International, Inc.
510 S. Mathilda Ave.
Sunnyvale, Calif. 94086 | 251. Manhattan Novelty Co.
263 Canal St.
New York, N.Y. 10013 |
| 183. Hinode Electric Works
13, Kamiyama-cho, Kita-ku
Osaka, Japan | 209. Jappac Co., Ltd.
21-21, Joban 9-chome, Urawi-shi
Saitama, Japan | 230. Kyokuyo Electric Co., Ltd.
605, Oazo Idogi Ageo
Saitama, Japan | 252. Marantz Co., Inc.
8150 Vineland Ave.
Sun Valley, Calif. 91352 |
| 186. Hitachi Sales Corp. of America
48-50 34th St.
Long Island City, N.Y. 11101 | 210. Jensen Mfg. Div. The Muter Co.
5655 W. 73rd St.
Chicago, Ill. 60638 | 231. Lafayette Radio & Electronics
111 Jericho Turnpike
Syosset, L.I., N.Y. 11791 | 253. Mar-Lin Radio Corp.
45 W. 27th St.
New York, N.Y. |
| 188. Hokuyo Musen Kogyo Co., Ltd.
6, Shikishima-cho 4-chome,
Johto-ku
Osaka, Japan | 211. Jeolco (USA), Inc.
477 Riverside Ave.
Medford, Mass. 02155 | 232. Leader Instrument Corp.
24-20 Jackson Ave.
Long Island City, N.Y. 11101 | 254. Mar-Lin West, Ltd.
1515 Santee St.
Los Angeles, Calif. 90015 |
| 189. Hokuyo Musen Co., Ltd.
80-26 138th St.
Kew Gardens, N.Y. | 212. KCK Co., Ltd.
528 W. Wellington Ave.
Chicago, Ill. 60657 | 233. Lear Jet Stereo, Inc.
13131 Lyndon Ave.
Detroit, Michigan 48227 | 255. Mar-Lin Enterprises
1472 Broadway
New York, N.Y. |
| 190. Hotta Clock & Watch Co., Ltd.
23-12, Ueno 5-chome, Taito-ku
Tokyo, Japan | 213. KLH Research and Development
Corp.
30 Cross St.
Cambridge, Mass. 02139 | 234. Le-bo Products Co., Inc.
71-08 51st Ave.
Woodside, N.Y. 11377 | 256. Mars Radio Corp.
79, Hanazonocho, Shinjuku-ku
Tokyo, Japan |
| 191. IEM
187, Kominato-cho 3-chome,
Naka-ku
Yokohama, Japan | 214. Kanematsu New York
One Whitehall St.
New York, N.Y. | 235. Liberty Trading Co., Ltd.
Nippon Bldg., 8, Ohtemachi
2-chome
Chiyoda-ku
Tokyo, Japan | 257. Marshall Field & Co.
111 N. State St.
Chicago, Ill. 60690 |
| 192. ITT Distributor Products
250 Broadway
New York, N.Y. | 215. Katoh Co., Ltd.
Oaawa Bldg., 2-13, Motohama-
cho,
Naka-ku
Yokohama, Japan | 236. Lion Electronics Corp.
194 S. 8th St.
Brooklyn, N.Y. | 258. Martel Electronic Sales
2356 S. Cotner Ave.
Los Angeles, Calif. 90064 |
| 193. Ikegami Electronics Industries,
Inc. of New York
35-27 31st St.
Long Island City, N.Y. 11106 | 216. Katone Corp.
37 W. 28th St.
New York, N.Y. | 238. Lloyd's Electronics of
California, Inc.
18601 S. Susana Rd.
Compton, Calif. 90221 | 259. Maruwa Electronic & Chemical
Co., Ltd.
1-18, Nishiura-cho, Higashi-ku
Nagoya, Japan |
| 194. Imperial Import Co.
1199 Broadway
New York, N.Y. 10001 | 217. Kay Jewelers
1328 New York Ave., NW
Washington, D.C. 20005 | 239. Longines Symphonette
200 Myrtle Ave.
Larchmont, L.I., N.Y. | 260. Marvel International
30 E. 42nd St.
New York, N.Y. |
| 195. Impex Electronics
213 S. Robertson Blvd.
Beverly Hills, Calif. | 218. Kaysons International, Ltd.
6500 Flotilla St.
Los Angeles, Calif. 90022 | 240. Loyal Sangyo Co., Ltd.
28-1, Sekiguchi 1-chome,
Bunkyo-ku
Tokyo, Japan | 261. Mason Camera Corp.
1141 Broadway
New York, N.Y. 10001 |

263. Masterwork Audio Products
1080 Graffle Rd.
Hawthorne, N.J. 07506
264. Matsushita Electric Corp. of America
200 Park Ave.
New York, N.Y. 10017
265. M.E. Parts & Repair
43-30 24th St.
Long Island City, N.Y.
266. Mercury Record Corp.
315 E. Wacker Dr.
Chicago, Ill. 60601
267. Metasco
401 Fifth Ave.
New York, N.Y. 10016
268. Metric TV Parts
Repair Center
65 Lexington Ave.
Passaic, N.J.
269. Metro of California
4861 Santa Monica
Los Angeles, Calif. 90029
270. Metro Wholesale Corp.
53 W. 43rd St.
New York, N.Y. 10036
271. Micro Seiki Co., Ltd.
19, Fujimicho, Itabashi-ku
Tokyo, Japan
272. Midland International Corp.
P.O. Box 1903
N. Kansas City, Mo. 64141
273. Miharu Shoji Co., Ltd.
P.O. Box 4
Ellenville, N.Y. 12428
274. Mikado Electronics Corp.
34 Dore St.
San Francisco, Calif.
275. Mitsubishi International Corp.
7045 N. Ridgeway Ave.
Lincolnwood, Ill. 60601
276. Mitsumi Electronics Corp.
One Lefrak City Plaza
Flushing, N.Y. 11368
277. Miyakawa Shoko Co., Ltd.
13-1, Higashi Azabu 1-chome,
Minato-ku
Tokyo, Japan
278. Monarch Electronics Corp.
7035 Laurel Canyon Blvd.
N. Hollywood, Calif. 91605
279. Mondo Electronic Corp.
19-3, Kami-Ochiai 1-chome,
Shinjuku-ku
Tokyo, Japan
280. Montgomery Ward
619 W. Chicago Ave.
Chicago, Ill. 60607
281. Morse Electro Products Corp.
101-10 Foster Ave.
Brooklyn, N.Y. 11236
283. Muntz Stereo Corp. of America
7715 Densmore Ave.
Van Nuys, Calif. 91406
284. Murata Corp. of America
Two Westchester Plaza
Elmsford, N.Y. 10523
285. Musicolor Products Visionics,
Inc.
4332 Artesia Ave.
Fullerton, Calif. 92633
286. NGK Spark Plugs (USA), Inc.
12511 Beatrice St.
Los Angeles, Calif. 90066
287. Nagata Electric Mfg. Co., Ltd.
240, Hanakawaminamino-cho
Nishiyodogawa-ku
Osaka, Japan
288. Nakamichi Research, Inc.
153, Suzukicho 1-chome,
Kodaira
Tokyo, Japan
289. Nakamichi Research (USA), Inc.
130 Woodbury Rd.
Woodbury, N.Y. 11797
290. Nakayama Denshi Co., Ltd.
13-5, Nishimagome, 2-chome,
Ohta-ku
Tokyo, Japan
291. Nason Trading Co.
230 Fifth Ave.
New York, N.Y.
292. National Electronics
38-20 S.E. 8th
Miami, Fla.
293. National Silver Co.
241 Fifth Ave.
New York, N.Y.
294. Net Electronics
8315 E. Firestone Blvd.
Downey, Calif. 90241
295. New York Merchandise Co.
32 W. 23rd St.
New York, N.Y. 10010
296. New York Transistor Co.
New Jersey
297. Nichicon Capacitor, Ltd.
3941 N. Pine Grove Ave.
Chicago, Ill. 60613
298. Nichimen Co.
60 Broad St.
New York, N.Y.
299. Nippon Alpha Electric Co., Ltd.
200 Park Ave.
New York, N.Y. 10017
300. Nippon Chemical Condenser
Co., Ltd.
86-16 60th Ave.
Rego Park, N.Y. 11373
301. Nippon Columbia Corp. of
America
Six E. 43rd St.
New York, N.Y. 10017
302. Nippon Densan Co., Ltd.
Morita Bldg., 15, Shibanihskubo,
Hiroomachi, Minato-ku
Tokyo, Japan
303. Nippon Electric New York, Inc.
200 Park Ave.
New York, N.Y. 10017
304. Nippon Sound Co., Ltd.
5-12, Shinsayama 1-chome,
Sayama City
Saitama, Japan
305. Nippon Sound Equipment Co.,
Ltd.
55-1, Kamiishihara 3-chome,
Chofu
Tokyo, Japan
306. Nissho Electronic Corp.
225, Hirano Babacho, Higashi
Sumiyoshi-ku
Osaka, Japan
307. Nitto Gramophone Co., Ltd.
5, Higashi Irlfuneco,
Nishinari-ku
Osaka, Japan
308. Noam Electronics Corp.
60 W. 45th St.
New York, N.Y. 10036
309. Noam Electronics Corp.
118-21 Queens Blvd.
Forest Hills, N.Y. 11375
310. North American Foreign
Trading Co.
1115 Broadway
New York, N.Y. 10010
311. North American Leisure Corp.
1776 Broadway
New York, N.Y. 10019
312. North American Phillips Co., Inc.
100 E. 42nd St.
New York, N.Y. 10017
313. NuVox Electronics
150 Fifth Ave.
New York, N.Y. 10011
314. OTC International (Chicago),
Inc.
205 W. Wacker Drive
Chicago, Ill. 60606
315. Ofuna Electronics Industry,
Co., Ltd.
526, Kamikashio-cho, Totsuka-ku
Yokohama, Japan
316. Oikawa Kogeisho Co., Ltd.
9-9, Minamidai 5-chome,
Nakano-ku
Tokyo, Japan
317. Oki Electric Industry Co., Ltd.
202 E. 44th St.
New York, N.Y. 10017
318. Olson Electronics, Inc.
260 S. Forge St.
Akron, Ohio 44308
319. Olympic International, Ltd.
89-89 Union Turnpike
Ellendale, N.Y. 11227
320. Omiya Electric Co., Ltd.
866, Sakaemachi 3-chome,
Funabashi City,
Chiba, Japan
321. Omron R & D, Inc.
440 E. Middlefield Rd.
Mountainview, Calif. 94040
322. Oral Denki Kogyo Co., Ltd.
Ginza Midori Bldg., 11-9, Ginza
5-chome, Chuo-ku
Tokyo, Japan
323. Original Industries Corp.
529 Jericho Turnpike
Mineola, N.Y. 11501
324. Orion Electric Co.
1170 Broadway
New York, N.Y.
325. Osaka Onkyo Co., Ltd.
43-23 Colden St.
Apt. 25D
Flushing, N.Y. 11355
326. Pacific Import Co.
37 W. 23rd St.
New York, N.Y.
327. Panasonic Repair
43-20 24th St.
Long Island City, N.Y.
328. Patson Trading Co., Inc.
1199 Broadway
New York, N.Y. 10001
329. J. J. Paulson Associates
24 Brooklyn Ave.
Freeport, N.Y. 11520
330. Pax, Ltd.
5125 Church St.
Skokie, Ill. 60076
331. Peerless Telerad, Inc.
37-15 61st St.
Woodside, N.Y. 11377
332. Pengo Traders
234 Fifth Ave.
New York, N.Y.
333. J. C. Penney Co., Inc.
1301 Ave. of the Americas
New York, N.Y. 10019
334. Perfect Sound Mfg. Co., Ltd.
5-16, Ginza 6-chome, Chuo-ku
Tokyo, Japan
335. Petely Enterprises
441 Lexington Ave.
New York, N.Y.
337. Phillips Audio, Inc.
29-28 41st Ave.
Long Island City, N.Y. 11101
338. Pickering and Co., Inc.
101 Sunnyside Blvd.
Plainview, N.Y. 11803
339. U.S. Pioneer Electronics Corp.
178 Commerce Rd.
Carlstadt, N.J. 07072
340. D. Plough Distributing Co.
P.O. Box 2266
Memphis, Tenn. 38102
341. Ponder & Best, Inc.
11201 W. Pico Blvd.
Los Angeles, Calif. 90064
342. Puchi Properties, Inc.
405 Grand Ave.
Nogales, Ariz.
343. Qatron Corp.
12000 Old Georgetown Rd.
Rockville, Md. 20852
344. Radiant Corp.
8220 N. Austin Ave.
Morton Grove, Ill. 60053
345. Radiomaster, Inc.
1314 Blondell Ave.
Bronx, N.Y. 10461
347. Ramson Trading Co.
1185 Broadway
New York, N.Y. 10001
349. Realtone Electronics Corp.
34 Exchange Place
Jersey City, N.J. 07302
350. Recoton Corp.
46-23 Crane St.
Long Island City, N.Y. 11101

Manufacturer / Importer / Distributor List continued . . .

- 350A. Regency Electronics, Inc.
7900 Pendleton Pike
Indianapolis, Ind. 46206
352. Risui Corp.
3-2, Hongo 3-chome, Bunkyo-ku
Tokyo, Japan
353. Roberts Div./Rheem Mfg. Co.
5922 Bowcroft Ave.
Los Angeles, Calif. 90016
354. Robins Industries Corp.
15-58 127th St.
Flushing, N.Y. 11356
- 354A. Robyn Co.
P.O. Box 478
Rockford, Mich. 49341
355. Roland Electronics Co., Ltd.
36-8, Ohkayama 1-chome,
Meguro-ku
Tokyo, Japan
356. Ross Electronics
2834 S. Lock St.
Chicago, Ill. 60608
357. Rozinante, Inc.
878 Wing St.
Plymouth, Mich. 48170
358. Saba Corp. Service Dept.
724 N. 7th St.
Allentown, Pa. 18102
359. The Sampson Co.
2244 S. Western Ave.
Chicago, Ill. 60608
360. San-ei Instrument Co., Ltd.
Canterbury House, Apt. D-15
15 Canterbury Rd.
Great Neck, N.Y. 11021
361. Sankei Manufacturing Co., Ltd.
21-3, Shimomaru 4-chome,
Ohta-ku
Tokyo, Japan
362. Sankoh Electric Co., Ltd.
25-11, Nishi Ochiai 1-chome,
Shinjuku-ku
Tokyo, Japan
363. Sanrin Electric Co., Ltd.
1-152, Kashiwagi 1-chome,
Shinjuku-ku
Tokyo, Japan
364. Sans & Streiffe, Inc.
8400 Brookfield Ave.
Brookfield, Ill. 60513
365. Sanshin Electric Co., Ltd.
35-20, Koenji Minami 5-chome,
Suginami-ku
Tokyo, Japan
366. Sanshin Optical Co., Ltd.
21-17, Takashima 1-chome, Suwa
Nagano, Japan
367. Sansui Electronics Corp.
2301 S. Grand Ave.
Los Angeles, Calif. 90007
368. Sansui Electronics Corp.
32-17 61st St.
Woodside, N.Y. 11377
369. Sanyo Electric, Inc.
1200 W. Walnut St.
Compton, Calif. 90220
370. H. H. Scott
111 Powder Mill Rd.
Maynard, Mass. 01754
371. Seeburg Corp.
1500 N. Dayton St.
Chicago, Ill. 60622
372. Seidai Manufacturing Co., Ltd.
Oaza-kudo, Koga-machi, Kasuya-
gun
Fukuoka, Japan
373. Sekii Industry Co., Ltd.
11-11, Kuramae 3-chome, Taito-
ku
Tokyo, Japan
374. Selectron Internationl Co., Inc.
55 Veteran Blvd.
Carlstadt, N.J. 07072
375. Milovac International Co., Inc.
4215 W. 45th St.
Chicago, Ill.
376. Setico Import Co.
2321 Liberty St.
Jacksonville, Fla.
377. Sharp Electronics Corp.
10 Keystone Plaza
Paramus, N.J. 07652
378. Sharpe Instruments Div. of
Scintrex, Inc.
Amherst Industrial Park
Tonawanda (Buffalo), N.Y. 14150
379. Sheraton Electronics Co., Inc.
401 Broadway
New York, N.Y.
380. Sherwood Electronic Labora-
tories, Inc.
4300 N. California Ave.
Chicago, Ill. 60618
383. Shibaden Corp. of America
58-25 Brooklyn Queens Expwy.
Woodside, N.Y. 11377
384. Shimadzu Seisakusho, Ltd.
c/o Ataka America, Inc.
633 Third Ave.
New York, N.Y. 10017
385. Shin-ei Electric Co., Ltd.
6-8, Tagara 4-chome, Nerima-ku
Tokyo, Japan
386. Shinkyo Co., Ltd.
3, Kanda Kaji-cho 3-chome,
Chiyoda-ku
Tokyo, Japan
387. Shin-Shirasuna Electric Corp.
521 Fifth Ave.
New York, N.Y. 10017
388. Showa Musen Kogyo Co., Ltd.
c/o Kanematsu-Gosho (USA),
Inc.
One Whitehall St.
New York, N.Y. 10004
389. Shure Brothers, Inc.
222 Hartrey Ave.
Evanston, Ill. 60204
390. Singer Consumer Products
30 Rockefeller Plaza
Room 622B
New York, N.Y. 10020
391. Skandia Electronics Corp.
4260, Nyo-i-Gemba, Kusunoki-cho,
Kita-ku
Nagoya, Japan
392. Sola Electric Div. of Sola
Basic Industries
1717 Busse Rd.
Elk Grove Village, Ill. 60007
393. Sonics Corp.
2, Kojimachi 3-chome, Chiyoda-
ku
Tokyo, Japan
394. Son Lee Electronics
1227 Broadway
New York, N.Y.
395. Sonorac Co., Ltd.
1-10, Shimomeguro 1-chome,
Meguro-ku
Tokyo, Japan
397. Sony Corp. of America
47-47 Van Dam St.
Long Island City, N.Y. 11101
398. Spico Electronics
Div. of Spirling Products
Henrietta St. & Duffy Ave.
Hicksville, N.Y. 11802
399. Spiegel, Inc.
1061 W. 35th St.
Chicago, Ill. 60609
400. Spinola International Corp.
315 Fifth Ave.
New York, N.Y. 10016
401. Sportmaster Radio
2570 Devon Ave.
Des Plaines, Ill.
402. Standard Radio Corp.
60-09 39th Ave.
Woodside, N.Y. 11377
404. Stanford International
569 Laurel St.
San Carlos, Calif. 94070
405. Stereo Magic Div. Eastern
Specialties Corp.
Five Richard Dr. W.
Mt. Arlington, N.J. 07856
406. Sterling Hi Fidelity, Inc.
22-20 40th Ave.
Long Island City, N.Y. 11101
407. Sunsonic Corp.
10-5, Ginza 4-chome, Chuo-ku
Tokyo, Japan
408. Summit International
1140 Broadway
New York, N.Y. 10001
409. Superex Electronics
4 Radford Place
Yonkers, N.Y.
410. Superscope, Inc.
8150 Vineland Ave.
Sun Valley, Calif. 91352
413. TDK Electronics Corp.
23-73 48th St.
Long Island City, N.Y. 11101
414. Taisei Co., Ltd.
Kyodo Bldg., 6, Takaracho
3-chome,
Chuo-ku
Tokyo, Japan
415. Taiyo Koki Co., Ltd.
427, Oaza Iida, Ohmiya
Saitama, Japan
416. Takt Denki New York
1170 Broadway
New York, N.Y. 10001
417. Tamradio Co., Ltd.
241-20 Northern Blvd.
Douglaston, N.Y. 11363
418. Tamura Electric Works, Ltd.
427 Fifth Ave.
New York, N.Y. 10016
419. Tandberg of America
Eight Third Ave.
Pelham, N.Y. 10803
- 419A. Teaberry Electronics Corp.
3401 Shadeland Ave.
Indianapolis, Ind. 46226
420. Teac Corp. of America
2000 Colorado Ave.
Santa Monica, Calif. 90404
- 420A. Teac (Repair)
404 Jericho Turnpike
Syosset, N.Y.
421. Telecon Corp.
4-6, Osaki 5-chome,
Shinagawa-ku
Tokyo, Japan
422. Telefunken Sales Corp.
S. St./Roosevelt Field
Garden City, L.I., N.Y. 11530
423. Telephone Dynamics Corp.
1333 Newbridge Rd.
North Bellmore, N.Y. 11710
424. Tele-Tone Co., Inc.
444 S. 9th Ave.
Mount Vernon, N.Y.
425. Telex/Waters Conley Co., Inc.
9600 Aldrich Ave. S.
Minneapolis, Minn. 55420
426. Telmar
2339 S. Cotner Ave.
Los Angeles, Calif. 90064
427. Tenna Corp.
19201 Cranwood Parkway
Warrens Heights, Ohio
44128
428. Tennac Antennas
P.O. Box 1005
Burlington, Iowa 52601
429. Tensho Electric Ind. Co., Ltd.
Electronics Div.
3-3, Koyama 1-chome,
Shinagawa-ku
Tokyo, Japan
430. Terra International
Three E. 28th St.
New York, N.Y. 10016

431. J. H. Thal Associates
200 Fifth Ave.
New York, N.Y.
432. Alfred Toepfer
One Broadway
New York, N.Y. 10004
433. Toho Boeki Kaisha, Ltd.
7-14, Uchikanda 2-chome,
Chiyoda-ku
Tokyo, Japan
434. Tokai Corp. of America
500 Fifth Ave.
New York, N.Y. 10036
435. Tokai Communication Apparatus Corp.
816, Nakahara, Shizuoka City,
Shizuoka, Japan
436. Toko New York, Inc.
350 Fifth Ave.
New York, N.Y. 10001
437. Tokyo Rokuon Kogyo Corp.
17-11, Daita 4-chome,
Setagaya-ku
Tokyo, Japan
438. Tokyo Sansei (N.Y.), Inc.
1170 Broadway
New York, N.Y. 10001
439. Tokyo Wireless Corp.
33-37, Tokumaru 3-chome,
Itabashi-ku
Tokyo, Japan
440. Topp Electronics, Inc.
4201 N.W. 77th Ave.
Miami, Fla. 33166
441. Topp Import & Export, Inc.
40 Whelan Rd.
E. Rutherford, N.J.
442. Toshiba America, Inc.
Warehouse-Service Center
41-06 Delong St.
Flushing, N.Y. 11355
443. Toshiba Audio Industrial Co., Ltd.
c/o Toshiba America, Inc.
477 Madison Ave.
New York, N.Y. 10022
444. Toshiba Denshionkyo Co., Ltd.
Third Wako Bldg., 12-1, Shiba
Nishikubo, Akefune-cho, Minato-ku
Tokyo, Japan
445. Toyo Radio Co., Ltd.
9-12, Osaki 2-chome,
Shinagawa-ku
Tokyo, Japan
446. Toyo Radio Corp. of America
1842B S.W. 169th St.
Gardena, Calif. 90247
447. Toyomenka, Inc.
Two Broadway
New York, N.Y.
448. Trade Distributors, Inc.
1199 Broadway
New York, N.Y. 10001
449. Trade Unlimited
75-03 Main St.
Flushing, N.Y.
450. Trans-Aire Electronics Corp.
393 Sagamore Ave.
Mineola, N.Y.
451. Trans America Electronics Co., Inc.
6479 N. Avondale
Chicago, Ill. 60631
452. Transcriber Co., Inc.
P.O. Box 478
Attleboro, Mass. 02703
453. Transistor World Corp.
52 Broadway
New York, N.Y. 10004
454. Transocean Electronics, Inc.
Tojo Bldg., 14 Shinjuku
4-chome,
Shinjuku-ku
Tokyo, Japan
455. Transworld Industrial Corp.
5204 Hudson Ave.
W. New York, N.J.
456. Trio Corp.
212 Fifth Ave.
New York, N.Y.
457. Trio Corp.
(Kenwood Electronics, Inc.)
15711 S. Broadway
Gardena, Calif. 90247
458. Triumph/General Time Corp.
599 S. Wheeling Rd.
Wheeling, Ill. 60090
459. Tussah Corp.
1412 Broadway
New York, N.Y. 10018
460. Unelco Electronics Corp.
322 N. Eutaw St.
Baltimore, Md. 21201
461. Union Co., Ltd.
22-31, Kamisueyoshi 5-chome,
Tsurumi-ku
Yokohama, Japan
462. United Audio Products, Inc.
1205 S. Columbus Ave.
Mount Vernon, N.Y. 10553
463. United States Antenna Corp.
P.O. Box 46462
Cleveland, Ohio 44146
464. Valiant Radio Corp.
380 Second Ave.
New York, N.Y.
465. Velk Electric Corp.
33-14, Zenukuji 3-chome,
Suginami
Tokyo, Japan
466. Vendome Enterprises
212 Fifth Ave.
New York, N.Y.
467. Vikoa, Inc.
400 Ninth Ave.
Hoboken, N.J. 07030
468. Vision Electronics, Inc.
1116 E. Houston St.
San Antonio, Tex. 78206
469. Voca Dictating Machine
274 Madison Ave.
New York, N.Y.
470. Vornado, Inc.
174 Passaic St.
Garfield, N.J. 07026
471. Wald Sound
11131 Dora St.
Sun Valley, California 91352
472. Waltham Electronics, Ltd.
Toyokawa Bldg., 12-13, Ginza
8-chome, Chuo-ku
Tokyo, Japan
473. Webcor Div. of Consolidated Merchandising Co.
59-50 Queens Midtown Expwy.
Maspeth, N.Y. 11378
474. Weltron Co., Inc.
514 E. Peabody
P.O. Box 217
Durham, N.C. 27702
475. Westinghouse Electric
Route 27 Vineard Rd.
Edison, N.J. 08817
476. Western Auto Supply
2107 Grand Ave.
Kansas City, Mo. 64108
477. Wharfedale, Div. of British Industrial Co.
Westbury, N.Y. 11590
- 478A. White Stores, Inc.
Wichita Falls, Tex. 60639
479. Whitehall Overseas Corp.
1140 Broadway
New York, N.Y.
480. Wilson Import Co.
1157 Broadway
New York, N.Y. 10029
481. Windsor Industries, Inc.
88 Third Ave.
Brooklyn, N.Y. 11217
482. F.W. Woolworth
233 Broadway
New York, N.Y. 10010
483. World Mark Electronics
663 Dowd Ave.
Elizabeth, N.J.
484. World Mart, Inc.
201 N.W. 21st St.
Miami, Fla. 33127
485. Yamaha International Corp.
7733 Telegraph Rd.
Montebello, Calif. 90054
486. Yamano Electric Mfg. Co., Ltd.
12-27, Iwats 3-chome, Higashi
Osaka City,
Osaka, Japan
487. Yamatake-Honeywell Co., Ltd.
c/o Honeywell, Inc.
24-30 Skillman Ave.
Long Island City, N.Y. 11101
488. Yashima Electric Industrial Co., Ltd.
314, Kamifuda, Chofu
Tokyo, Japan
489. Yaskawa Electric America, Inc.
100 Bliss Dr.
Oak Brook, Ill. 60521
490. Yewtec Corp.
1995 Palmer Ave.
Larchmont, N.Y. 10538
491. Yokohama LPG Trading Co., Ltd.
80, Onocho 5-chome, Naka-ku
Yokohama, Japan
492. York Radio Corp.
15 Empire St.
S. Hackensack, N.J. 07606
493. Yutaka Electric Mfg. Co., Ltd.
c/o Marubeni-Iida (America), Inc.
938 Merchandise Mart
Chicago, Ill. 60654
494. Zenon Corp.
12-4, Takanawa 1-chome,
Minato-ku
Tokyo, Japan

productreport

for further information on any of the following items, circle the associated number on the reader service card.

Rosin-Core Solder

A new rosin-core solder reportedly formulated for service technicians has been introduced by Chemtronics, Inc.

The rosin-core flux is predetermined, to provide the correct



amount of flux, and in direct ratio to the size of the solder strand, according to the manufacturer. The rosin residue, after soldering, reportedly is non-corrosive, non-conductive, non-hygroscopic, and is fungus resistant.

The solder is available in dispenser tube and in 1-pound bulk reel. The dispenser tube contains 110 inches of .062 (1/16)-inch diameter solder with 60/40 tin-lead alloy.



One pound reels are available with either 40/60, 50/50 or 60/40 composition tin-lead alloy ratios and with various diameters.

The dispenser tube sells for \$.39, and prices of the 1-pound spools start at \$1.87.

Circle 60 on literature card

Soldering Iron With Automatic Heat Control

A soldering instrument with a control system mounted directly



within the instrument handle has been introduced by Edsyn, Inc.

The Loner electronic control reportedly automatically maintains thermal balance during each soldering cycle, matching termination load with preset temperature settings. The unit will "idle" at 9 watts or will match any soldering load up to 50 watts, according to the manufacturer.

The handle is constructed of transparent polycarbonate, to allow viewing of internal workings. Adjustment of temperature reportedly is accomplished by turning the control knob.

The Loner weighs 4 ounces and sells for \$35.00.


Circle 61 on literature card

Scanning Receiver

A new scanning monitor receiver, the Bearcat III, which reportedly features interchangeable plug-in RF modules to cover any two of the three public safety/business bands (high, low and UHF), or single band, has been introduced by Electra Corp.

Placement of up to eight plug-in crystals in a crystal socket automatically determines the band of operation for each channel when two bands are used. With two-band operation, any combination of eight channels in the two bands can be monitored.

Features reportedly include: band

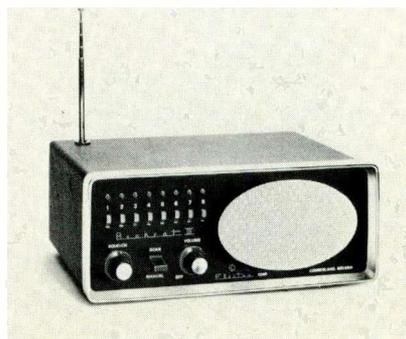

coverage without frequency spread limits; quartz crystal IF filters; solid-state LED channel-indicator lights; built-in 3 inch x 5 inch front-mounted speakers; improved squelch control; faster scan; sharper selectivity; external speaker jack; integrated circuitry, and non-sliding feet.

The Bearcat III measures 3½ inches x 9 inches x 6 inches. Front controls are: channel switches, squelch, volume/on/off and combined manual/scan/channel-select switch.

Bearcat III is made in six models, with installed RF modules, mobile-mounting bracket and cords for 115 VAC and 12 VDC, according to the manufacturer.

Bearcat III is priced from \$139.95 to \$159.95.

Circle 62 on literature card

Semiconductor Replacements

Twenty-two new types have been added to the ECG line of replacement semiconductors offered by GTE Sylvania, Inc.

The new types are described as linear integrated circuits; all ceramic high-voltage rectifiers; high-voltage silicon and selenium triplers; and silicon and germanium transistors and diodes. All reportedly are intended as replacement parts for use in home entertainment equipment.

Functionally, the added types include: NPN silicon power transistors, for use in television vertical and horizontal deflection sections, an NPN "Darlington" amplifier, for audio preamplifiers; a plastic NPN power transistor, for use in audio and video amplifiers; damper diodes; audio power amplifiers; a general-purpose silicon diode, for detection, switching, and gating applications; and a matched pair of silicon diodes for FM detection, AFT, stereo multiplex and horizontal AFC functions.

The new rectifiers are high-voltage types which feature all-ceramic construction. Each is furnished with a pair of step-down, clip-in adapters, for use in equipment requiring clip-in installations. ▲

Circle 63 on literature card

For more information about above products use reader service card

JOIN

The Photofact®-of-the-Month Club


BUILD YOUR OWN UP-TO-THE-MINUTE SERVICE DATA LIBRARY

HERE'S HOW IT WORKS:

- Each month a sturdy, sealed P.O.M. carton will be delivered to you by your local Photofact distributor.
- This P.O.M. carton contains 6 Photofact sets in handy, ready-to-file folders. These 6 sets include the latest and most reliable service data on at least 50 new chassis—color TV receivers, black and white TV receivers, AM and FM radios, hi-fi's, stereos and record changers.
- Your P.O.M. carton also contains a bonus package of *Advance Schematics*—preliminary schematics on the very latest color, black and white chassis to fill your immediate servicing needs. (At a later date you'll receive a complete Photofact set on each of these)

- You will also receive a monthly service bulletin, *Photofact Servicer* offering inside troubleshooting advice and timely additional information.
- And, as a special feature, each P.O.M. carton contains 6 valuable certificates which you can save and redeem for a free metal file cabinet. (One-drawer model is free with 60 certificates—Four-drawer model requires only 144 certificates and \$21.95)

The special advantage of subscription membership in the P.O.M. Club is measured in dollars and cents! You save \$54.00 each year over the individually purchased set price (regular price per set is \$3.00). Members receive this entire service package each month for just \$13.50 per month! Can you afford not to take advantage of this tremendous savings on the complete service data so vitally important in your industry?

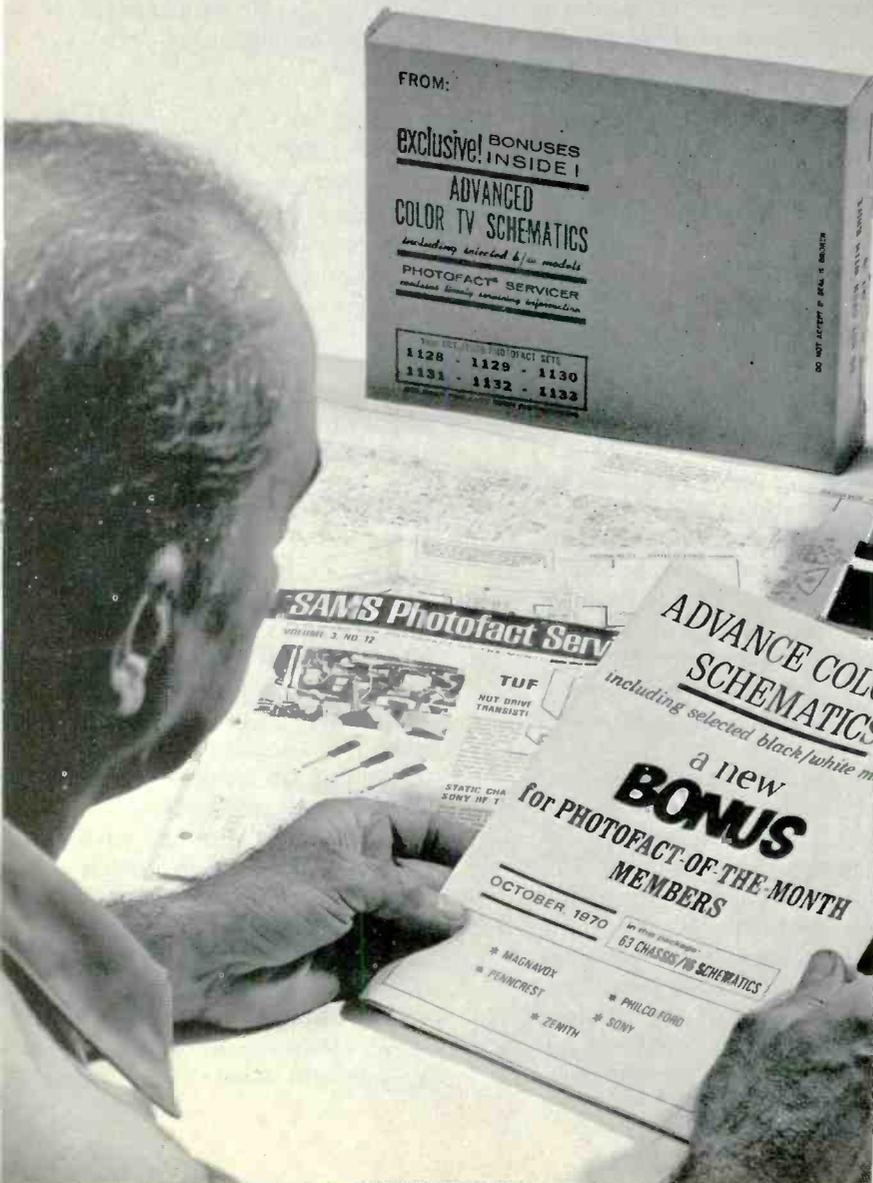


HOWARD W. SAMS & CO., INC.
 4300 West 62nd St. • Indianapolis, Ind. 46268

Please enroll me as a new member of the Photofact-of-the-Month Club. I agree to pay \$13.50 per month for my membership and understand my subscription will begin with the 6 current Photofact Sets, to be delivered by my local Sams Distributor. ES-1X1

NAME _____
 BUSINESS NAME _____
 ADDRESS _____
 CITY _____
 STATE _____ ZIP _____
 My Local Sams Distributor Is _____

COLOR TV CONTROLS

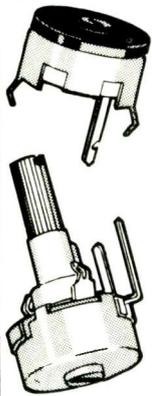

FOR
AUDIO
FOCUS
COLOR
SENSITIVITY
BRIGHTNESS
HORIZ. FREQ.
A.G.C. DELAY
CONVERGENCE
VERT. CENTER
HORIZ. CENTER
VERT. LINEARITY

105 EXACT REPLACEMENTS



RCA · ZENITH
SILVERTONE
ADMIRAL Etc.


ASK FOR FREE CROSS
REFERENCE No. X67

MANUFACTURED FOR THE OEM
MARKET, NOW AVAILABLE FOR
REPLACEMENT PARTS

WORKMAN *Electronic*
PRODUCTS, INC.
P.O. BOX 3828 SARASOTA, FLORIDA 33578

Circle 27 on literature card

REBUILD YOUR OWN PICTURE TUBES?

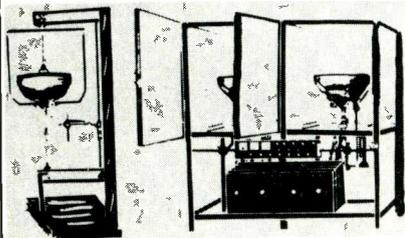

With Lakeside Industries precision equipment, you can rebuild any picture tube!

EASY TO OPERATE

Requires only 4 x 8 ft. of space.

Rebuilds either black and white or color, regardless of tube size.

Amazing low operational costs.

Offers excellent additional income to your present business.

For complete details on how you can become part of this increasing industry, write direct or mail this coupon.

LAKESIDE INDUSTRIES

5234 N. Clark St.
Chicago, Ill. 60640
Phone: 312-271-3399

- Free demonstration appointment
 Send me more information

Name
Address
City State

Circle 28 on literature card

catalogs literature

ANTENNAS

100. *Vikoa, Inc.* — is making available a 64-page, illustrated catalog covering their line of wire and cables and IDS-MATV equipment. Hardware, accessories, connectors and fittings and an index also are included.

101. *Jerrold Electronics Corp.* — Catalog S, titled "Systems and Products for TV Distribution," lists specifications of this manufacturer's complete line of antenna distribution products, including antennas and accessories, head-end equipment, distribution equipment and components, and installation aids.

AUDIO

102. *Bell P/A Products Corp.* — new 6-page catalog gives detailed specifications and descriptions of the company's broad line of commercial sound components and special purpose sound system products.

103. *GC Electronics* — has made available a 52-page, two-color catalog, (FR-71-A) featuring 350 items for the music listener and hobbyist. Included in the booklet are a variety of TV antenna installations, acoustic-suspension loudspeaker systems, speaker switching devices, stereo headphones, microphones and accessories.

104. *Jensen Manufacturing Div.* — has issued an 8-page catalog, No. 1090-E, which describes applications of 167 individual speaker models. Special automotive, communications, intercom and weathermaster speakers, plus a complete line of electronic musical instrument loudspeakers are featured.

AUTO ELECTRONICS

105. *Littelfuse, Inc.* — has released a new 32-page, 1971 automotive replacement fuse guide for passenger autos, sports cars, trucks, and taxi cabs. Fuse descriptions and circuits they protect are included.

CABLE

106. *Columbia Electronic Cables* — has published a 92-page wire, cable, and cord-set catalog No. CEC-MC-571 which includes technical data concerning comparison charts of different types of insulating materials, copper wire specifications, estimating charts, and ampere ratings.

CAPACITORS

107. *Cornell-Dubilier Electronics* — has issued an 80-page cross-reference, 1972 catalog for location of single, dual, triple, and quadruple section replacement electrolytics.

COILS

108. *J. W. Miller Co.* — announces a new 92-page radio and TV replacement coil cross reference guide for known domestic and foreign color and black and white TV sets, home and car radios. Over 22,000 replacement coils for 327 manufacturers names reportedly are listed.

COMPONENTS

109. *Arco/LDP div. of Loral Corp.* — has published a new cross-reference guide and price book for its miniature aluminum electrolytic capacitors. The four-page publication includes specifications for the Arco/LDP line of Miniature Arcolytics, cross-references them by part number with similar products of other capacitor manufacturers.

110. *Essex International, Inc.* — announces their 24-page SC-5 RBM Standard Controls Catalog listing over 450 electrical/electronic relays and contactors.

111. *General Electric Tube Department* — has released a new 52-page Entertainment Semiconductor Almanac, No. ETRM-4311F. The almanac contains approximately 20,000 cross references from JEDEC, or OEM part numbers to GE parts numbers for universal replacement semiconductors, selenium rectifiers for color TV, dual diodes, and quartz crystals.*
112. *Loral Distributor Products* —has made available a 24-page electrolytic capacitor replacement guide. The catalog features replacement products by the original manufacturers part number.
113. *Precision Tuner Service* — announces a new tuner parts catalog, including a cross reference list of antenna coils and shafts for all makes of tuners.*
114. *RCA Distributor Products* —introduces a 72-page "SK Series Top-Of-The-Line Replacement Guide" (SPG-202L) which cross-references over 20,000 semiconductor device numbers. In addition a Solid State Quick Selection Replacement Chart (1L1367) listing 79 entertainment SK-Series devices is included. Price of this catalog is \$35.
115. *RCA/Solid-State Division* — announces a revised edition of the Power Transistor Directory, which reflects new product programs, as well as new product data. All product matrices have been updated to include the latest commercial types as well as preliminary data on developmental types, including RCA power transistors, both silicon and germanium. The Index of Types has been expanded to include DT types as well as JEDEC (2N-Series) types and RCA 40-K series types. Copies are \$40.*
116. *Semitronics Corp.* — has a new, revised "Transistor
- Rectifier, and Diode Interchangeability Guide" containing a list of over 100 basic types of semiconductors that can be used as substitutes for over 12,000 types. Include 25 cents to cover handling and postage.
117. *Sprague Products Co.*—has announced a 40-page manual which lists original part numbers for each manufacturer, followed by ratings, recommended Sprague capacitor replacements, and list prices. More than 2,500 electrolytic capacitors are included.
118. *Stancor Products*—pocket-size, 108-page "Stancor Color and Monochrome Television Parts Replacement Guide" provides the TV technician with transformer and deflection component part-to-part cross reference replacement data for over 14,000 original parts.
119. *Sylvania Electric Products, Inc.* — a 73-page guide which provides replacement considerations, specifications and drawings of Sylvania semiconductor devices plus a listing of over 35,000 JEDEC types and manufacturers' part numbers. Copies are \$1.00.*
120. *Workman Electronic Products, Inc.*—has released a 32-page, pocket-size cross reference listing for color TV controls. 105 Workman part numbers are listed in numerical order with specifications and illustrations of the part.*

PICTURE TUBES

121. *General Electric* — a 12-page, 4-color, illustrated "Picture Tube Guidebook", Brochure No. ETRO-5372, provides a reference source for information about GE color picture tube replacements and tube interchangeability.*
122. *GTE Sylvania, Inc.* — has published an interchangeability guide listing 191 commonly used color TV

TV TECH AID

Takes you right to the source of the trouble... without guesswork and wasted time!

You receive each month OVER 40 ACTUAL CAUSES AND CURES OF COLOR AND B-W TV TROUBLE SYMPTOMS . . .

reported by leading TV manufacturers, technicians and field reps . . . each presented in a concise, brief format, including a clearly marked schematic diagram of the associated circuitry . . . no wading through unnecessary details!

You also receive timely and complete information about CIRCUIT MODIFICATIONS AND OTHER VALUABLE SERVICE DATA relating to both new and existing TV models.

Start or expand your own file of causes and cures with TV TECH AID . . . arranged so you can file them by make and model, by trouble symptom or use your own system!

SUBSCRIBE or RENEW NOW!

only \$7.95 per year (12 issues)
(that's less than 67¢ per month!)

NEW!

Over 400 Causes and Cures of Recurring Troubles in major-brand Black-and-White TV

All in one large, easy-to-use issue
All for only **\$5.95** . . . Less than 1½¢ per tip . . . each of which can save you hours of valuable troubleshooting time!

TV TECH AID
P.O. BOX 603
KINGS PARK, N.Y. 11754
ENCLOSED IS A CHECK OR MONEY ORDER FOR \$
PLEASE SEND:
<input type="checkbox"/> 1971—12 ISSUES—\$7.95
<input type="checkbox"/> 1970—BOOK FORM—\$5.95
<input type="checkbox"/> 1969—12 ISSUES—\$4.95
<input type="checkbox"/> 1971 B-W BOOK—\$5.95
<input type="checkbox"/> 1972—12 issues—\$7.95
TO:
NAME
ADDRESS
CITY
STATE ZIP.....

Circle 29 on literature card

FREE CATALOG

HARD-TO-FIND PRECISION TOOLS

Lists more than 1700 items—pliers, tweezers, wire strippers, vacuum systems, relay tools, optical equipment, tool kits and cases. Also includes four pages of useful "Tool Tips" to aid in tool selection.



JENSEN TOOLS and ALLOYS
4117 N. 44th Street, Phoenix, Arizona 85018

Circle 31 on literature card

INCREASE PROFIT — SATISFY CUSTOMER

NOW PERFECT COLOR T.V. with
TERADO VOLTAGE ADJUSTERS



CORRECTS HIGH OR LOW
VOLTAGE TO NORMAL CAP. 300 to 500 watts

SATURN (shown) Model 50-172 Dealer Net \$18.77
POLARIS (w/o meter) Model 50-204 Dealer Net \$12.24
SEE YOUR ELECTRONIC PARTS JOBBER, OR WRITE

terado CORPORATION
1053 Raymond Ave., St. Paul, Minn. 55108

Circle 32 on literature card

YEATS appliance dollies

MOST VERSATILE color TV TRUCK DEVELOPED!

NO LIFTING
ROLLS UP & DOWN STAIRS

DeLuxe Model No. 14
\$89.50
ORDER YOURS TODAY!
FREE illustrated brochure

Yeats Appliance Dolly Sales Co.
1301 W. FOND DU LAC AVE.
MILWAUKEE, WIS. 53205

Circle 33 on literature card

NOW A ONE STOP SHOPPING CENTER FOR YOUR AUTO RADIO AND 8 TRACK STEREO PARTS: AT FACTORY DISCOUNTS

WE ARE AUTHORIZED PARTS
DISTRIBUTORS FOR:

DELCO	PANASONIC
BENDIX	KRACO
MOTOROLA	PHILIPS
LEAR JET	BELLE WOOD
TENNA	WARD
METRA	QUICKMOUNT
AUTOMATIC	AC SPEEDO
ONGUARD	CRAIG
MEMOREX	VERITAS
INLAND	CHAPMAN CARLOCK
DYNATRONICS	EV GAME

STEREO LOCK MOUNTS

AND MANY OTHERS

Send Your Order With Part Number
and Description of The Part To

Laran Electronics, Inc.

Dept. ES, 3768 Boston Road
Bronx, N. Y. 10469

Circle 34 on literature card

picture tubes which can be replaced with 19 GTE Sylvania Color Bright 85® types.*

MISCELLANEOUS

123. *Allied Radio Shack's*—new 132-page, 1972 Electronic Parts & Accessories catalog reportedly lists thousands of hard-to-find electronic items. Exclusive Allied, Realistic, and Radio Shack brand products are listed, as well as the complete line of Knight-Kit and Science Fair Kits.

SEMICONDUCTORS

124. *General Electric Tube Products Dept.* — announces the availability of their revised, 60-page, 1971 edition of the Entertainment Semiconductor Almanac. The Almanac reportedly provides approximately 24,000 cross-references from JEDEC, or OEM part numbers to GE part numbers for universal replacement semi-conductors, selenium rectifiers for color TV, dual diodes and quartz crystals.*

125. *GTE Sylvania, Inc.* — announces a revised semiconductor guide which reportedly gives replacement information for more than 41,000 solid-state devices. The 73-page catalog, ECG 212D, provides characteristics and outline drawings of the 124 components in the Sylvania ECG semiconductor line. The catalog is \$1.00.*

SERVICE AIDS

126. *Kester Solder* — has released an 8-page brochure presenting the company's full line of soldering products. Presented are: "44" resin core solder, acid-core solder, solid-wire, bar solder, TV-radio solder, and Metal Mender.

127. *Chemtronics*—announces a new 12-page, 1971-1972 catalog of products, including: tuner sprays, circuit coolers, insulating sprays, contact and control sprays,

lubricants, tape head and record cleaners/accessories, cartridge tape head cleaners and conditioners, electronic glues and cements, solder, and spray paints.

TV ACCESSORIES

128. *Telematic* — introduces a 14-page catalog featuring CRT brighteners and reference charts, a complete line of test jig accessories and a cross reference of color set manufacturers to Telematic Adapters and convergence loads.

TECHNICAL PUBLICATIONS

129. *Howard W. Sams & Co., Inc.* — literature describes popular and informative publications on radio and television servicing, communications, audio, hi-fi industrial electronics, including their 1971 catalog of technical books about every phase of electronics.*

130. *Sencore, Inc.* — Speed Aligner Workshop Manual, Form No. 576P, provides 20 pages of detailed, step-by-step procedures for operation and application of Sencore Model SM158 Speed Aligner sweep-marker generator.

131. *Sylvania Electric Products, Inc., Sylvania Electronic Components Div.* — has published the 14th edition of their technical manual, which includes mechanical and electrical ratings for receiving tubes, television picture tubes and solid-state devices. Price of this manual is \$1.90.*

132. *Tab Books* — has released their Spring, 1971 catalog describing over 170 current and forthcoming books. The 20-page catalog covers: schematic/servicing manuals, broadcasting; basic technology; CATV; electric motors; electronic engineering; computer technology; reference; television, radio and electronics servicing; audio and hi-fi stereo; hobby and experiment; amateur ra-

dio; test instruments; appliance repair, and transistor technology.*

TEST EQUIPMENT

133. *Dynascan Corp.* — announces a new 24-page 2-color catalog of B&K Precision Test Equipment. A total of 21 instruments are reportedly presented; from a Mutual Conductance Tube Tester to a new DC to 10 MHz Triggered Sweep Oscilloscope.
134. *Eico* — has released a 32-page, 1971 catalog which features 12 new products in their test equipment line, plus a 7-page listing of authorized Eico dealers.*
135. *Information Terminals* — has introduced a new brochure featuring the M-100 Tension Monitor, the M-200 Torque Tester and the M-300 Head and Guide Gage.
136. *Leader Instruments Corp.* — announces the 1971 Catalog of Leader Test Equipment. Test equipment included is the LBO-301 portable triggered-sweep oscilloscope, LSW-330 new solid-state post injection sweep/marker generator, and the LCG-384 mini-portable, solid-state battery operated color-bar generator.
137. *Lectrotech, Inc.* — announces the 1972 catalog, "Precision Test Instruments for the Professional Technician". It contains specifications and prices on sweep marker generators, oscilloscopes, vectorscopes, color bar generators and other test equipment.
138. *Mercury Electronics Corp.* — 14-page catalog provides technical specifications and prices of this manufacturer's line of Mercury and Jackson test equipment, self-service tube testers, testers, test equipment kits and indoor TV antennas.
139. *Tektronix, Inc.* — has announced a 4-page brochure describing the 54 Series oscilloscope manufactured by

Tektronix English subsidiary, Teletipment.

140. *Triplett Corp.* — announces a 6-page, two-color brochure featuring four new portable, battery-operated, FET Volt-Ohm-Milliameters and accessories.
141. *Triplett Corp.* — Bulletin No. 51570, a 2-page technical bulletin which provides the specifications and price of Triplett's new Model 602VOM.

TOOLS

142. *Chapman Manufacturing Co.* — offers a pamphlet containing their line of tools and tool kits. Kit No. 6320, the Midget Ratchet is featured along with other available tool kits.
143. *General Electric Industrial Heating* — a new two-page brochure describing a desolder tool which facilitates solder removal from electronic components on printed circuit boards, and permits the liquid solder to collect in a catcher under the tool's tip.
144. *Ideal Industries* — introduces a 2-page, 4-color brochure announcing their new Heat Gun. Performance characteristics applications, operating features, specifications and ordering information reportedly are included.
145. *Janel, Inc.* — announces a three-color catalog on precision hand tools used primarily in miniature and micro-miniature electronic assembly and production applications.
146. *Jensen Tools and Alloys* — has announced a new catalog No. 470, "Tools for Electronic Assembly and Precision Mechanics." The 72-page handbook-size catalog contains over 1,700 individually available items.*
147. *Xcelite, Inc.* — Bulletin N770 describes this company's three new socket wrench and ratchet screw-driver sets.

*Check "Index to Advertisers" for additional information. ▲

NEW ENDECO Desoldering Kits

MODEL
300-K
KIT
SHOWN



All you need to handle almost any desoldering and resoldering job!

Kit 300K includes the famous Endeco pencil desoldering iron Model 300, six different size tips (.038 to .090) for any job, tip cleaning tool, and metal stand for iron . . . all in a handy lifetime steel storage box. \$19.90 net. Model 300K-3 with a 3-wire cord \$20.90. Also a similar kit for military users. Kit 100K with large Endeco iron (Model 100A) is \$27.40, and 3-wire Kit 100AD-3 \$28.40.

SEE YOUR DISTRIBUTOR OR WRITE



**ENTERPRISE
DEVELOPMENT
CORPORATION**

5127 E. 65th St., Indianapolis, Ind. 46220
Circle 35 on literature card

REPLACEMENT PARTS & ACCESSORIES WELTRON'S GOT 'EM! DO YOU?

plugs & jacks * stereo switches *
universal replacement antennas &
bases * volt meters * cables * mi-
crophones * power supplies * auto
stereo accessories * high precision
motors * synchronous motors *
shaded 4-pole motors *

**COMPLETE CATALOG AVAILABLE.
CALL YOUR DISTRIBUTOR NOW!**

**Weltron[®]
COMPANY, INC.**

514 EAST PEABODY STREET, DURHAM, N.C. 27702
919-682-0333

Circle 36 on literature card

NEW!


UPDATED
MODEL from
HC-8A



"IN-CIRCUIT"

**CURRENT CHECKER
FOR B&W AND COLOR SETS**

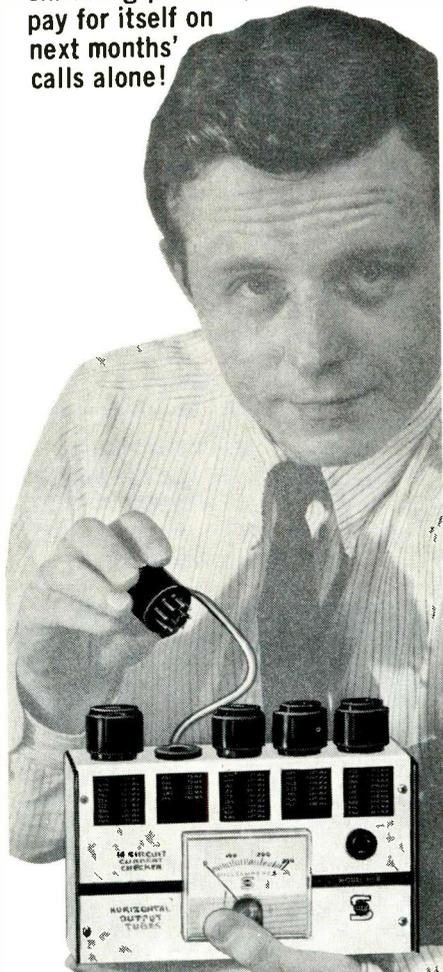Eliminates most common cause of "callbacks" (unstable focus, shrinking pictures, etc.)! Should pay for itself on next months' calls alone!



AIDS IN TROUBLE SHOOTING

There's just nothing like the HC-8A. Tune horizontal drive and linearity for "dip"—and in seconds—you've got best possible focus, width and stability at minimum cathode current. Makes convergence adjustments faster, easier—longer lasting!

Especially useful on color TV where a slight misadjustment of horizontal linearity or efficiency coils drives cathode currents sky high! 5 pre-wired sockets for all popular horizontal output tubes lets you plug into circuit fast—no clipping or unsoldering of leads!

ONLY
\$45.00
NET

See Your Distributor or Order Direct



**SECO
ELECTRONICS CORP.**

1001 Second St. So. • Hopkins, Minn. 55343

Circle 37 on literature card

**advertisers'
index**

American Telephone & Telegraph Co.	1
B & K Manufacturing Co.	3
Bussmann Mfg. Div. McGraw Edison Co.	7
Channelock, Inc.	25
Eico Electronic Instrument Co., Inc.	8
Enterprise Development Corp. ..	69
GTE Sylvania—Consumer Renewal	21
Gem City Tuner	31
General Electric Tube Products	Cover 4
Heath Company	20
International Electronics Corp. .	23
Jensen Tools and Alloys	68
Kay Townes Antenna Company	43
Lakeside Industries	66
Laran Electronics Inc.	68
Lectrotech, Inc.	4, 6
Perma Power Div. of Chamberlain Mfg.	42
Precision Tuner Service	11
RCA Electronic Components Cover 2, Cover 3, 19	
RMS Electronics, Inc.	24
The Raytheon Company	41
Howard W. Sams & Co., Inc. ..	13
Seco	70
TV Tech Aid	67
TeleMatic Div., UXL Corp.	22
Terado Corporation	68
Tuner Service Corporation	5
Weltron Co., Inc.	69
Workman Electronic Products, Inc.	22, 66
Yeats Appliance Dolly Sales Co.	68
Zenith Radio Corporation	9

WILD DISCOUNTS

National brand TV test equipment.

Write for details.

P. O. Box 42
Greenvale, N.Y. 11548

The MARKETPLACE

This classified section is available to electronic technicians and owners or managers of service shops who have for sale surplus supplies and equipment or who are seeking employment or recruiting employees.

Advertising Rates
in the Classified
Section are:

- 25 cents per word (minimum \$3.00)
- "Blind" ads \$2.00 additional
- All letters capitalized—35 cents per word

Each ad insertion must be accompanied by a check for the full cost of the ad.

Deadline for acceptance is 30 days prior to the date of the issue in which the ad is to be published.

This classified section is not open to the regular paid product advertising of manufacturers.

EQUIPMENT FOR SALE

For Sale: C-G3 Lab grade frequency counter with converters, mint condition, very reasonable. John Perkovich, Route 1, Cascade, Wisc. 53011. 9-71-1t

CRT Picture Tube Rebuilder—used 3 months. Accessories included, cost \$4000 sell \$1500. Ray Davidson, 508 New York Avenue, Huntington, N.Y. 11743. 11-71-1t

POSITION WANTED

Seeking employment in Montana as TV Technician or in parts. Have recent diploma from NRI. Harvey Kreiman, 922 8th. Ave. Helena, Mt. 59601. 11-71-1t

ELECTRONIC SERVICING . . .
the country's only magazine
devoted 100% to the
ELECTRONIC SERVICING
industry . . .

Now—Just 3 RCA Hi-Lite “V” Type Color Picture Tubes Replace **185** Types



Replaces **92** types

18VABP22	19HCP22/	490ASB22
18VACP22	19HKP22	490BAB22
18VADP22	19HFP22	490BCB22
18VAHP22	19HJP22	490BDB22
18VAJP22	19HKP22	490BGB22
18VAQP22	19HQP22	490BHB22
18VARP22	19HRP22	490BRB22
18VASP22	19HXP22	490CB22
18VATP22	19JBP22	490CHB22
18VBAP22	19JDP22	490CUB22
18VBCP22	19JHP22	490DB22
19EXP22	19JKP22	490EB22
19EXP22/	19JNP22	490EB22A
19GVP22	19JQP22	490FB22
19EYP22	19JYP22	490GB22
19EYP22/	19JZP22	490HB22
19GWP22	19KEP22	490JB22
19FMP22	19KFP22	490JB22A
19FXP22	490AB22	490KB22
19GLP22	490ACB22	490KB22A
19GSP22	490ADB22	490LB22
19GVP22	490AEB22	490MB22
19GVP22/	490AFB22	490NB22
19EXP22	490AGB22	490RB22
19GWP22	490AHB22	490SB22
19GWP22/	490AHB22A	490TB22
19EYP22	490AJB22	490UB22
19GXP22	490AJB22A	490VB22
19GYP22	490AKB22	490WB22
19GZP22	490ALB22	490XB22
19HBP22	490AMB22	490YB22
19HCP22	490ANB22	490ZB22
	490ARB22	

Replaces **22** types

19VABP22	21FJP22A/
19VACP22	21GVP22
21AXP22	21FKP22
21AXP22A	21GUP22
21AXP22A/	21GUP22/
21AXP22	21FBP22A
21CYP22	21GVP22
21CYP22A	21GVP22/
21FBP22	21FJP22A
21FBP22A	21GXP22
21FBP22A/	21GYP22
21GUP22	21GZP22
21FJP22	21HAP22
21FJP22A	

Replaces **71** types

23VACP22	25AEP22	25BRP22
23VADP22	25AFP22	25BSP22
23VAHP22	26AGP22	25BVP22
23VALP22	25AJP22	25BWP22
23VAMP22	25ANP22	25BXP22
23VANP22	25AP22	25BZP22
23VAQP22	25AP22A	25CBP22
23VARP22	25AP22A/	25CP22
23VASP22	25XP22	25CP22A
23VATP22	25AQP22	25FP22
23VAUP22	25ASP22	25FP22A
23VAWP22	25AWP22	25GP22
23VAXP22	25AXP22	25GP22A
23VAYP22	25AZP22	25RP22
23VAZP22	25BAP22	25SP22
23VBAP22	25BCP22	25VP22
23VBCP22	25BDP22	25WP22
23VBDP22	25BFP22	25XP22
23VBEP22	25BGP22	25XP22/
23VGBP22	25BHP22	25AP22A
23VBHP22	25BJP22	25YP22
23VBJP22	25BMP22	25YP22/
23VBRP22	25BP22	25BP22A
25ABP22	25BP22A	25ZP22
25ADP22	25BP22A/	
	25YP22	

Here's the way to save yourself time, give your customers faster service and improve your profit. Stock these three RCA Hi-Lite color picture tubes and have immediate replacements for the fastest moving industry types — 185 of them.

RCA Hi-Lite types are all new, made to OEM specifications and contain the newest RCA manufacturing technology, including Perma-Chrome and the latest X-ray attenuating glass.

It adds up to a big plus for you. Order these three RCA Hi-Lite tubes, and other types you may need, from your RCA Distributor. He also has the complete RCA Interchangeability Guide, available free of charge.

RCA | Electronic Components | Harrison, N.J. 07029

RCA Electronic Components

THE ELECTRIC GIFTS

WITH GENERAL ELECTRIC TUBES



12 great gifts . . .
calculated to
please you

Save the gift point coupons you'll receive with each General Electric tube purchase from your participating distributor . . . and earn your great electric gifts.

- 1. GE Styling Comb, 282 Gift Points
- 2. GE Tape Recorder, 543 Gift Points
- 3. GE Marble Clock, 265 Gift Points
- 4. GE Youth Phono, 459 Gift Points
- 5. GE Portable Vacuum Cleaner, 564 Gift Points
- 6. GE Toast-R-Oven™, 608 Gift Points
- 7. GE Porta-Color® Television (reception simulated), 4331 Gift Points
- 8. Black & Decker® Drill Set, 412 Gift Points
- 9. Dremel Electric Shoe Polisher, 640 Gift Points
- 10. Brothers® Electric Pencil Sharpener, 260 Gift Points
- 11. Brothers® Calculator, 4728 Gift Points
- 12. Automatic Putting Set, 260 Gift Points

Tube Products Department, Owensboro, Ky.

GENERAL ELECTRIC