



Electronic Servicing



Color-TV Test Jigs

What's available
and how to use
them, page 14


Horizontal sweep and
high voltage, page 40

Interference in TV, page 50

Transistor testing, page 58

Servicing German car
radios, page 22

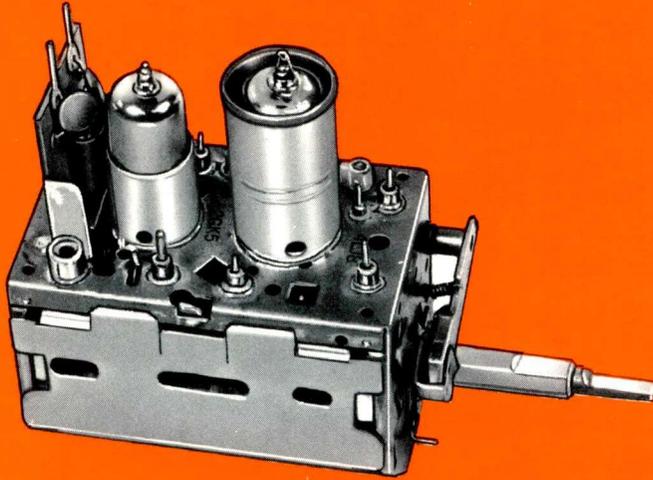LSI-3070 N 10 1972
NORMAN C RIEDEL
9111 SHEA AVE
GREEN BAY WISC 54303



\$975

TUNER SERVICE CORPORATION

PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS AT ONE PRICE.

TUNER REPAIR

VHF Or UHF Any Type \$9.75.
UHF/VHF Combo \$15.00.

In this price all parts are included. Tubes, transistors, diodes, and nuvistors are charged at cost.

Fast efficient service at our 4 conveniently located service centers.

1 year guarantee backed up by the largest tuner manufacturer in the U.S.—SARKES TARZIAN INC.

All tuners are cleaned inside and out, repaired, realigned and air tested.

TUNER REPLACEMENT

Replacement Tuner \$9.75.

This price buys you a complete new tuner built specifically by SARKES TARZIAN INC. for this purpose.

The price is the same for every type of universal replacement tuner.

Specify heater type

Parallel 6.3V
Series 450 mA
Series 600 mA

All shafts have the same length of 12".

Characteristics are:

Memory Fine Tuning
UHF Plug In
Universal Mounting
Hi-Gain Lo-Noise

If you prefer we'll customize this tuner for you. The price will be \$18.25. Send in original tuner for comparison purposes to our office in INDIANAPOLIS, INDIANA.



TUNER SERVICE CORPORATION

FACTORY-SUPERVISED TUNER SERVICE

MIDWEST	817 N. PENNSYLVANIA ST., Indianapolis, Indiana	TEL: 317-632-3493
EAST	547-49 TONNELE AVE., Jersey City, New Jersey <small>(Home Office) Highway 1 & 9</small>	TEL: 201-792-3730
SOUTH	938 GORDON ST., S. W., Atlanta, Georgia	TEL: 404-758-2232
SOUTH-EAST	1505 CYPRESS ST., TAMPA, FLA. 33606	TEL: 813-253-0324
WEST	SARKES TARZIAN, Inc. TUNER SERVICE DIVISION 10654 MAGNOLIA BLVD., North Hollywood, California	TEL: 213-769-2720

Circle 1 on literature card

Leader outduals them all!

LBO-505 DUAL CHANNEL/ DUAL TRACE SOLID STATE OSCILLOSCOPE

MODEL LBO-505 \$559.95

Price Includes:
2 LPB-8X Direct Lo/Cap Probes
2 Terminal Adapters — BPX
1 Set of Test Leads



The more you see... the more you believe.

Accuracy! Performance! Exclusive, Leader-developed features! That's what makes the LBO-505 the Number One Dual Channel/Dual Trace Scope. You get triggered and automatic sweep. AC or DC coupling per channel. 15MHz bandwidth. Maximum horizontal speed of 0.1 microseconds/cm (10X magnification). 10MVp-p/cm vertical sensitivity. Separate or simultaneous display in sweep mode of channels 1 and 2, alternating, chopped, added algebraically and vector (X-Y). The triggered sweep range extends from 1 μ s/cm to 0.5s/cm, calibrated in 17 steps. Scale illumination is continuous with front panel control.

How can you use the LBO-505 most efficiently? You'll find more ways than you can think of ... at first. It makes troubleshooting a breeze! Compare 2 signals simultaneously — input and output, for color, monochrome, audio and much more. Check gain, loss, distortion, phase shift, frequency ... you name it. Do your own thing. The LBO-505 belongs on every bench and in every lab. Feature-for-feature, price-for-price, job-for-job ... it outduals them all!

Send for new catalog. See your distributor.

Leader

INSTRUMENTS CORP.

37-27 Twenty-Seventh Street
Long Island City, New York 11101
(212) 729-7410

Circle 4 on literature card

Electronic Servicing

TEST EQUIPMENT

14 Color-TV Test Jigs—This general discussion about the primary function of a test jig and how it is used to perform that function, plus a look at the characteristics and specifications of the three major brands currently available, should put you on the right track to choosing the one which is right for you (**Notes On Test Equipment/ES Technical Staff**).

AUTO ELECTRONICS

22 Servicing German-Made Auto Radios—ES's auto electronics consultant takes a look at the major "problems" normally associated with servicing European auto radios—how to interpret European schematics, the availability of service literature, component identification and replacement and the most significant differences of circuitry (**Carr Electronics/Joseph J. Carr**).

COLOR TV

40 Horizontal Sweep And High Voltage In Color TV, Part 2—The horizontal-output, high-voltage, damper and focus circuitry are analyzed in this part of a three-part series which examines the functions of circuits and components, and the symptoms and causes of typical related defects and how to isolate them (**Shop Talk/Carl Babcoke**).

TELEVISION (GENERAL)

50 Externally-Generated Interference In TV—Methods for quickly determining whether the interference is externally generated and, if so, where it is entering the receiver and how it can be eliminated or reduced (**Bruce Anderson/ES Contributing Author**).

SERVICING TECHNIQUES (GENERAL)

58 The Terminology of Transistor Testing—A review of the characteristics commonly analyzed by technicians to determine the condition of transistors. Also included are related test setups (**Forest H. Belt**).

GUIDES

67 Supplement to 1972 Sams PHOTOFACT Annual Index (January thru March)—A complete listing of new models of entertainment electronic products covered in PHOTOFACT since the 1972 PHOTOFACT Annual Index was published in December.

DEPARTMENTS

Electronic Scanner	4	Audio Systems Report	55
Symcure	8	Antenna Systems Report	56
Service Bulletin	10	Product Report	62
Test Equipment Report	34	Catalog & Literature	63
Book Review	48	Advertisers' Index	65
Service Training		The Marketplace	66
Schedule	49		

Second class postage paid at Kansas City, Mo. and additional mailing offices. Published monthly by INTERTEC PUBLISHING CORP., 1014 Wyandotte St., Kansas City, Mo. 64105. Vol., 22, No. 4. Subscription rate \$6 per year in U.S., its possessions and Canada; other countries \$7 per year.

Copyright, 1972, Howard W. Sams & Co., Inc. All rights Reserved. Material may not be reproduced or photocopied in any form without written permission of publisher.

EDITORIAL

GEO. H. SEFEROVICH, Director
J. W. PHIPPS, Managing Editor
CARL BABCOKE, Associate Editor
BARBARA L. BORDERS, Editorial Assistant
DUDLEY ROSE, Art Director

CONTRIBUTING AUTHORS

Bruce Anderson
Joseph J. Carr

TECHNICAL CONSULTANT

JOE A. GROVES

EDITORIAL ADVISORY BOARD

LES NELSON, Chairman
Howard W. Sams & Co., Indianapolis

CIRCULATION

EVELYN ROGERS, Manager

ADVERTISING SALES

Kansas City, Missouri 64105
Tele: 913/888-4664

E. P. LANGAN, Director
R. JACK HANCOCK, Manager
JAKE STOCKWELL
MIKE KREITER
JOAN HIRES, Production

REGIONAL ADVERTISING SALES OFFICES

Indianapolis, Indiana 46280
ROY HENRY
2469 E. 98th St.
Tele: 317/846-7026

New York, New York 10019

CHARLES C. HORNER
3 W. 57th St.
Tele: 212/688-6350

Los Angeles, California 90005

JOHN D. GILLIES
3600 Wilshire Blvd., Suite 1510
Tele: 213/383-1552

London W. C. 2, England

JOHN ASHCRAFT & CO.
12 Bear Street
Leicester Square
Tele: 930-0525

Amsterdam C. Holland

JOHN ASHCRAFT & CO.
W.J.M. Sanders, Mgr.
for Benelux & Germany
Herengracht 365
Tele: 020-240908

Tokyo, Japan

INTERNATIONAL MEDIA
REPRESENTATIVES LTD.
1, Shiba-Kotohiracho, Minatoku
Tele: 502-0656



ELECTRONIC SERVICING (with which is combined PF Reporter) is published monthly by Intertec Publishing Corp., 1014 Wyandotte Street, Kansas City, Missouri 64105.

Subscription Prices: 1 year—\$6.00, 2 years—\$10.00, 3 years—\$13.00, in the U.S.A., its possessions and Canada.

All other foreign countries: 1 year—\$7.00, 2 years—\$12.00, 3 years—\$16.00. Single copy 75c; back copies \$1.

Adjustment necessitated by subscription termination at single copy rate.



Robert E. Hertel, Publisher

Intertec Publishing Corp.
Subsidiary of Howard W. Sams & Co., Inc.

SERVICE

technicians know that Color TV repair demands more time and effort. That's why Sprague strives to simplify Color TV capacitor selection.

COLOR

TV capacitors by Sprague come in the exact ratings required to meet the exacting requirements of Color TV.

TV

service becomes more demanding as Color TV keeps expanding. That's why exact capacitor ratings are important. They help you to restore original set performance.

EASIER

selection of replacement capacitors for Color TV is assured when you look to the broad Sprague line. You'll get the capacitor you need—when you need it—every time.

Just off the press! See your Sprague Distributor for a free copy of our new 40-page K-110 Twist-Lok[®] and Print-Lok[®] Capacitor Replacement Manual, or write to: Sprague Products Company, 105 Marshall St., North Adams, Mass. 01247

THE BROAD-LINE PRODUCER OF ELECTRONIC PARTS

Circle 5 on literature card



electronic scanner

news of the industry

Increased use of integrated circuits (IC) by Japanese manufacturers of color TV receivers was reported recently in **Home Furnishings Daily**. According to the report, Tokyo Shibaura Electric Co., which manufactures and markets home entertainment electronic products in this country under the name "Toshiba," will include IC-equipped color TV's in the line it exports to the U.S. this year. Also, Sony reportedly will employ more IC's in their Trinitron color receivers. Mitsubishi, which sells color TV in this country under the MGA label, is another Japanese manufacturer who has introduced IC equipped color chassis. However, a spokesman for Mitsubishi said that the manufacturer has not yet decided whether the new color TV's will be included in the MGA line marketed in this country this year. The IC-equipped units are already on the market in Japan.

Canada's largest retailer reportedly will establish its own TV and appliance repair organization within the next two years. Eaton, which sells through its own department stores and through catalogs and about 300 other outlets in Canada, will expand its present servicing operation to include consumer electronic units not purchased from it.

Television receiver sales during the next quarter century will exceed 370 million sets, according to a recent prediction by Barton Kruezer, RCA executive vice president, consumer electronics. Kruezer also predicts that by the end of the next quarter century annual sales of television receivers will be in excess of 17 million sets, and annual sales of black-and-white television receivers during the next 25 years probably will remain above 5 million.

A possible shock hazard exists in early runs of three Zenith 12-inch black-and-white television receivers, models C1335, C1340 and T2616, according to the manufacturer. The condition, an incorrectly secured antenna-assembly cover, was discovered during engineering tests. Zenith officials said that the company had had no reports of failures of these models which already have been sold and has no reason to believe that any failure has been experienced. However, the company notified Zenith distributors and dealers to hold, for modification, inventories of the models and to notify purchasers of the sets that a modification of the set was needed and would be performed by Zenith distributors and dealers, at Zenith's expense.

Daily television viewing is steadily increasing, according to Norman E. Cash, president, Television Bureau of Advertising. Cash reports that the latest Nielsen figures reveal that average daily home TV viewing in 1971 topped six hours for the first time (6 hours 2 minutes in 1971 compared to 5 hours 56 minutes in 1970). This reportedly was the ninth consecutive year of increased home TV viewing.

Teledyne Service Company has acquired nine of the former RCA Service-America facilities, according to a recent report in **Home Furnishings Daily**. Teledyne Service, the servicing arm of Teledyne Packard Bell, California-based manufacturer of color TV, reportedly purchased three each of the Service-America facilities in Philadelphia, San Francisco and Miami. This boosts

(Continued on page 6)

What do RCA SK series devices have that other replacements don't?




SOLID-STATE HARDWARE

- 10 sockets for transistors and IC's
- 15 heat sinks from TO-18 to TO-3 package styles



QUALITY PRODUCT

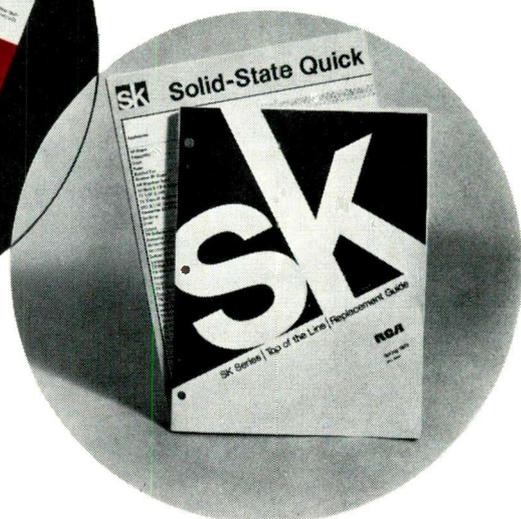- Top-of-the-line quality
- Meet-or-beat specs
- 23 new types
- Now 120 SKs replace more than 46,000 devices



INFORMATION SUPPORT

- Accurate • Comprehensive
- New SK Replacement Guide
- New SK Wall Chart
- Transistor Tape/Slide Educational Shows
- Manuals

All three make up the RCA Solid-State System — a product and back-up approach to a replacement line of devices with the professional technician and service dealers' needs in mind. You put the elements together — and they work. Product is top-of-the-line. Literature is accurate and comprehensive, and hardware helps in your day-to-day servicing.

Remember, RCA's Solid-State System is based on premium product — more than 120 different devices (including 23 brand new ones) that can replace more than 46,000 units, both foreign and domestic. They cover the full range of replacement needs — from small signal types, integrated circuits, insulated gate and junction type FET's,

to the newest silicon audio 100-watt output types.

Designed especially for replacement use, RCA SK units are backed by electrical characteristics that make them comparable to or better than original devices. There are no cast-offs or factory seconds.

All units and the types they replace are cross-referenced in the RCA Replacement Guide, SPG-202M. There's a Quick-Selection Wall Chart, too, 1L1367A, and new Audio-Visual service aids. These spell the industry's finest informational backup for replacements — all SK, all available from your RCA Distributor. See him today for your copies.

RCA Electronic Components | Harrison | N.J. 07029.

RCA Electronic Components

the total number of Teledyne Service operations nationally to more than 100. Teledyne Service Company reportedly does not limit its servicing to Teledyne Packard Bell products. Five other former ServiceAmerica facilities remain up for sale; J.C. Penney Company reportedly is negotiating the purchase of these.

General Electric has introduced an all-solid-state color-TV receiver. The new 16-inch portable model receiver is equipped with a completely solid-state chassis which used the same "easy-service" design concept as the Company's recently announced all-solid-state 19-inch black-and-white line. Don Johnstone, general manager of General Electric's Television Department, said the new chassis is "the forerunner of a new generation of solid-state General Electric televisions to be introduced this year."

Sylvania recently introduced the first 17-inch color television receivers manufactured by the domestic television industry. A Sylvania spokesman said the 17-inch receiver "would become increasingly popular as 18-inch sets are phased out of production."

Hitachi's carry-in color-TV warranty covers transistors for five years; all other parts, including the picture tube, are covered for two years, and service labor during the first year of the warranty is free. Hitachi, which recently announced its first 19-inch color receiver, presently offers 13 all-solid-state color receivers.

PTS Electronics, Inc., authorized by RCA to repair in-warranty RCA tuners at no charge. PTS Electronics, Inc., Indiana-base tuner repair operation, with six locations throughout the country, recently was authorized by RCA to at no charge repair any RCA tuner in warranty. Dealers and service shops may send defective in-warranty RCA tuners directly to PTS, prepaid and with a completed return-material tag. PTS will repair and return the tuner prepaid the same day it is received, at no charge to the dealer. RCA warranties reportedly cover b-w TV tuners for 90 days and color-TV tuners for one year. PTS recently moved their Southeast location from Miami to Jacksonville, Florida. Other locations include Bloomington, Indiana; Springfield, Massachusetts; Longview, Texas; Denver, Colorado; and Sacramento, California.

52.6 per cent of U.S. households now have color television, according to recent National Broadcasting Company estimates. The total U.S. homes with color-TV receivers reportedly is now about 32.9 million.

Wage/price controls will continue indefinitely, according to a statement contained in the Council of Economic Advisers, (CEA) annual economic report to Congress. The statement, reportedly written personally by CEA Chairman, Herbert Stein, said that "speculation (that) the administration will abandon controls prematurely—out of fatigue, ideological aversion or other causes—is groundless. Having embarked on this course, the Administration has no intention of departing from it in circumstances where it would risk either resumption of inflation or the need to reimpose the controls". Service companies and servicing dealers reportedly are bound by the restrictions of Phase 2, regardless of their volume of business. When in doubt about wage and/or price restrictions, servicers should check with their local Internal Revenue Service office.

Motorola has discontinued offering portable and table radio, portable phonograph and portable tape players. The reason given by Motorola for bowing out of this segment of the entertainment electronic market is that it has become "increasingly difficult to gain the profit return" required to continue offering these "personal electronics."

1971 sales of color television receivers to dealers were 28.2 per cent above those of 1970, according to entertainment electronic sales statistics recently released by the Marketing Services Department of the Electronic Industries Association (EIA). Monochrome TV sales increased 11.9 per cent during the same period. Also up over 1970 levels were sales of home (+38 per cent) and auto radio (+29.9 per cent). □

For all types of $\frac{1}{4} \times 1\frac{1}{4}$ " fuses and fuseholders:

BUSS YOUR ONE SOURCE

Normal Blowing Fuses

AGC GLH MTH
From $\frac{1}{500}$ to 30
amps, for 32V, 125V,
or 250V

Time Delay Fuses


MDL MDX
From $\frac{1}{100}$ to 30 amps,
for 32V, 125V, or 250V

Visual Indicating Fuse

GBA (Red Indicating
Pin)
From $\frac{3}{4}$ to 5 amps,
125V




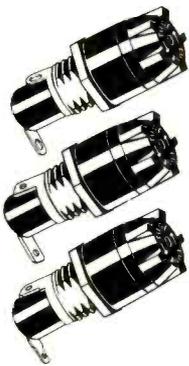Space-Saver
—projects only one
inch behind panel



HTA (Solder
Terminals)
HTA-HH ($\frac{1}{4}$ "
Quick-Connect
Terminals)
HTA-DD ($\frac{3}{16}$ "
Quick-Connect
Terminals)

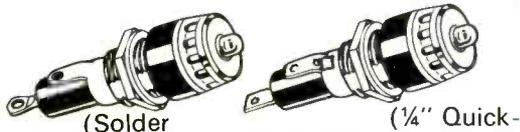HKP (Solder Terminals) **HKP-HH** ($\frac{1}{4}$ " Quick-Connect Terminals)
The Fuseholder for All-Purpose Applications



HLD (Solder Terminals) **HLD-HH** ($\frac{1}{4}$ " Quick-Connect Terminals)
Visual Indicating Fuseholder



HKL (Octagon Knob) **HKL-X** (Flat-Sided Knob)
Lamp Indicating Fuseholder

FUSEHOLDERS

All Have These Features in Common • Rated for 15 amps at 250 volts • Dielectrically capable of withstanding 1500 volts a.c. between terminals and between terminals and panel • Bayonet-type knob grips fuse so that fuse is withdrawn when knob is removed; strong compression spring assures good contact •

Made for installation in D-hole to prevent turning in panel • Terminals are mechanically secured as well as soldered in holder

This is only a sampling — use the coupon below to get a full description of the complete BUSS line of fuses and mounting hardware.

BUSSMANN MFG. DIVISION, McGraw-Edison Co.
St. Louis, Missouri 63107

ES-472

Name _____

Title _____

Company _____

Address _____


City _____

State _____

Zip _____




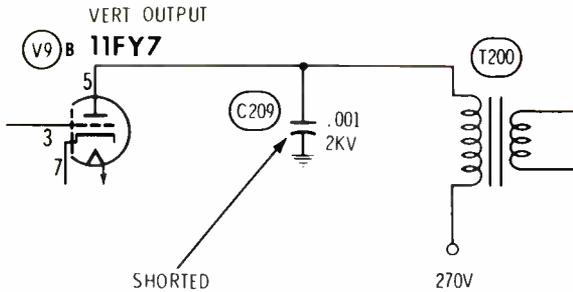Chassis—General Electric H-3 b-w
PHOTOFACT—1094-1




Symptom—No vertical sweep
Cure—Check for a shorted C209

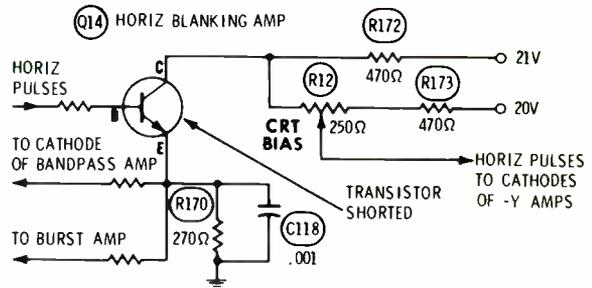Chassis—Sylvania D12 or D13
PHOTOFACT—1045-2 or 1021-2




Symptom—Dim raster; weak color; poor color locking
Cure—Check for leakage in blanker transistor Q14

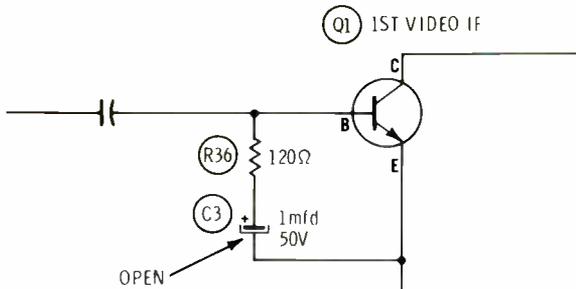Chassis—Sylvania D12 or D13
PHOTOFACT—1045-2 or 1021-2




Symptom—Audio motorboat; IF oscillation; AGC overload
Cure—Check for an open C3

Chassis—Airline GEN8147A
PHOTOFACT—886-1

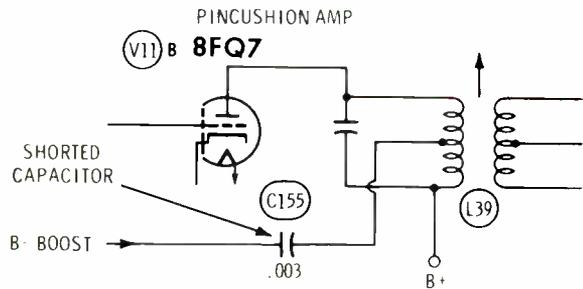


Symptom—No high voltage
Cure—Check C155 and replace, if leaking or shorted

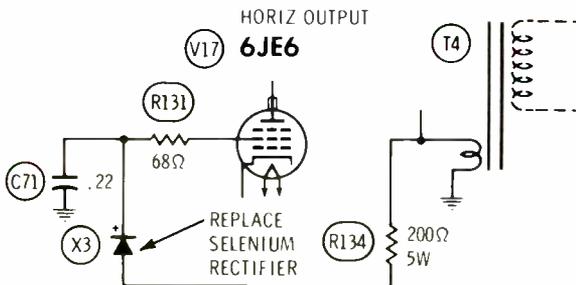Chassis—Sethcell-Carlson U800
PHOTOFACT—715-3




Symptom—Narrow width; poor focus; easy to bloom picture
Cure—Replace selenium rectifier X3

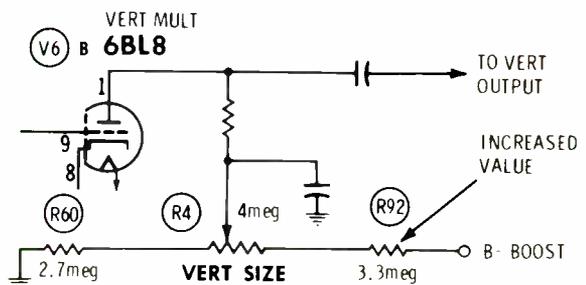Chassis—Motorola ZDTS-589 b-w
PHOTOFACT—803-3



Symptom—Insufficient height
Cure—Check R92 and replace, if value above 3.3 megohms

TV TUNER SERVICE

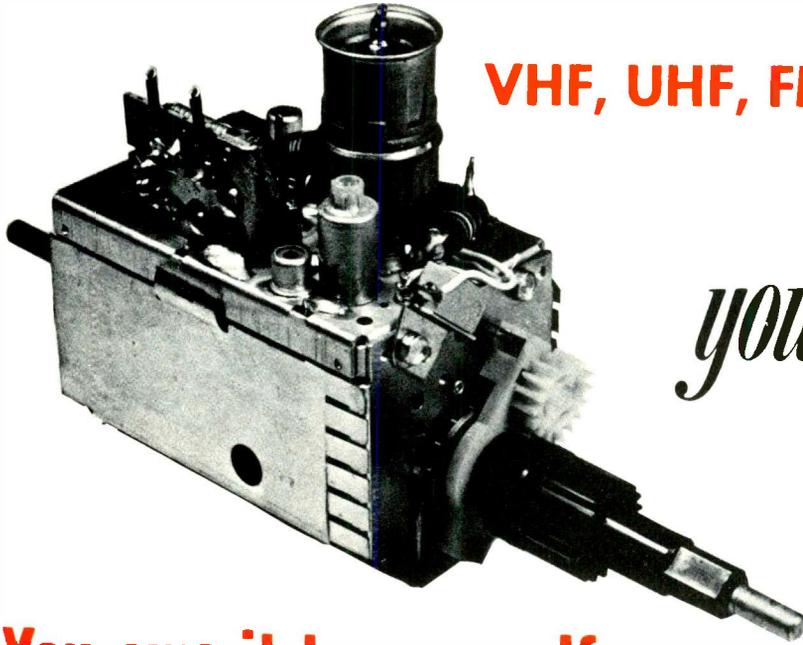

VHF, UHF, FM or IF-Subchassis. . .
 . . . All Makes


you get...

Fast 8 hr. Service!

You owe it to yourself

to try P.T.S. We are the fastest growing, oldest and now the largest tuner service company in the world. Here is what you get:

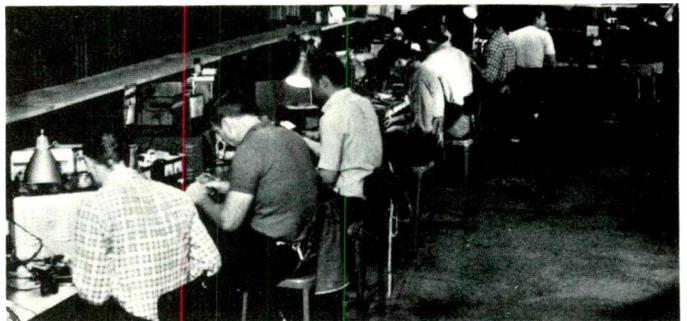1. Fastest Service — 8 hr. — in and out the same day. Overnight transit to one of our six plants, for parts, tuners or IF-modules.
2. All tuners cleaned inside and out, repaired, realigned and air tested.
3. On IF-modules all stages checked, all traps set with high calibre test equipment.
4. Fine Quality! Your customers are satisfied and you are not bothered with returning your units for rework!
5. Lower Cost! Up to \$5.50 less than other tuner companies!
6. Friendly, helpful personalized service!



1 YEAR GUARANTEE

We offer you finer, faster...

**Precision
 Tuner Service**



FIRST TO OFFER 365-DAY GUARANTEE!
 COLOR—BLACK & WHITE—TRANSISTOR TUNERS—ALL MAKES
 GUARANTEED COLOR ALIGNMENT—NO ADDITIONAL CHARGE

VHF-UHF-FM	\$ 9.95
UV-COMBO	\$16.95
IF-MODULE	\$12.50

Major Parts charged at Net Price

CUSTOMIZED REPLACEMENTS AVAILABLE
 FOR \$12.95 UP (NEW OR REBUILT)

LIKE TO DO IT YOURSELF?

PTS makes all tuner parts available to you.

Send one dollar (redeemable) for our

TUNER REPLACEMENT GUIDE AND PARTS CATALOG

- 60 pages of top information
- Blow-up of all tuners
- Largest exact tuner replacement guide
- Antenna Coil Replacement Guide
- Multi-fit Replacement Tuner Shaft Guide

For fastest service, send faulty unit with tubes, shields and all broken parts to:

PTS ELECTRONICS, INC.

HOME OFFICE—P. O. Box 272—Bloomington, Ind. 47401	Tel. 812/824-9331
EAST—P. O. Box 3189—Springfield, Mass. 01103	Tel. 413/734-2737
WEST COAST—P. O. Box 41354—Sacramento, Calif. 95841	Tel. 916/482-6220
MOUNTAIN—P. O. Box 4145—Denver, Colo. 80204	Tel. 303/244-2815
SOUTHWEST—P. O. Box 7332—Longview, Tex. 75601	Tel. 214/753-4334
SOUTHEAST—P. O. Box 6771—Jacksonville, Fla. 32205	Tel. 904/389-9952

Circle 8 on literature card

To service Color TV you need:

1. vectorscope
2. color bar generator

and you can't use one without the other!



portable



for home or shop

One Year Warranty

only the V7 gives you both

- The only complete one unit color vectorscope/color-bar generator available anywhere!
- Completely portable for servicing color TV in the home . . . no need to bring set to the shop!
- The only one with detailed instructions on color circuit alignment and color adjustment. And, additional instructions are available as new sets are introduced!
- Recommended by leading TV manufacturers!
- Proven performance . . . over 4 years of use in field and shop by thousands of technicians . . . no other vectorscope manufacturer can make this claim!

V7

- Checks and aligns demodulators to any angle.
- Checks and aligns bandpass-amplifier circuit.
- Pinpoints troubles to a specific color circuit.

Exclusive Features: Self-Calibrating—adjust timing circuit without external test equipment, Dial-A-Line—adjust horizontal line to any width from 1 to 4. Plus: All Crosshatch, Dots, and Color Patterns; Voltage Regulated; Fully Enclosed Cable Compartment. Free copy of Wayne Lemon's Book, "Color TV Servicing Simplified with Vectorscope," Net **18950**

Remember . . . V7—the complete one

See your distributor or write Dept. ES-4
LECTROTECH, INC.
 5810 N. Western Ave., Chicago, ILL. 60659

Circle 9 on literature card

Addition of an AGC control Magnavox T946 chassis


An AGC control has been added to the Magnavox late-production T946 chassis. This control replaces fixed resistor R50, which was used previously.

Adjust the AGC control for minimum snow on the weakest available channel, then monitor the picture produced by the strongest signal, to make certain there is no overload. If necessary, adjust the AGC control to just beyond the point at which overload is eliminated.

Install an AGC control, Magnavox part number 220217-5, in early-production T946 chassis, if any difficulty with weak-signal snow or strong-signal overload is experienced.

Adjacent-channel interference Motorola TS599 b-w chassis

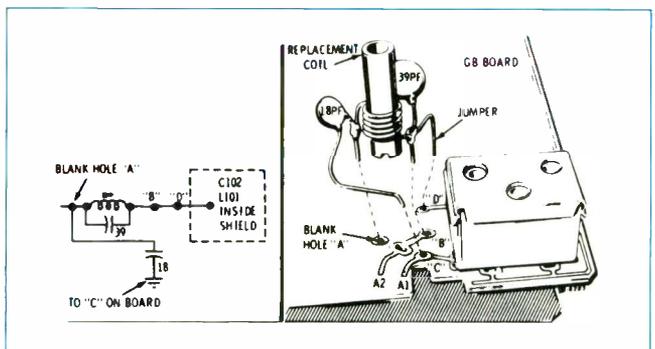Adjacent-channel interference from the video carrier of a higher-channel television station can be reduced by the addition of a 39.75M-Hz trap,



Motorola part number 24P65175A09.

Remove the original coil (L100) and install the replacement trap, as shown in the drawing. This trap has been pretuned at the factory and should require no further adjustment. If some interference persists, carefully fine tune the desired channel, then tune the trap for minimum interference.

Interaction of ACC and color-killer adjustments Magnavox T952 color TV chassis

Interaction between the ACC and color-killer adjustment might cause loss of color or incorrect color-killer action. The factory recommends the following sequence of adjustments:

- Preset the color control to maximum CW, and the ACC control (R196) to fully CCW, as viewed from the component side of the board. A screwdriver is required to adjust the ACC

(Continued on page 12)

Best values

Here are really high-capacity, low-voltage capacitors at great competitive prices.


MTA, MTV—From 1 microfarad to 1000 microfarads. Tubular aluminum units that are fully molded in moistureproof polypropylene plastic. All-welded construction. MTA axial lead and MTV single-ended lead capacitors are perfect for printed-circuit applications. MTV's also feature molded standoffs for good solder flow and board washing.

SX Polystyrene Capacitors—Available in 130 ratings from 5 picofarads to .47 microfarads depending

upon voltage... with the utmost stability. Exceptionally high insulation resistance, greater than 100,000 megohms... low power factor less than .05%. Temperature coefficient $-150 \text{ ppm}/^\circ\text{C} \pm 60 \text{ ppm}/^\circ\text{C}$... in ratings of 63, 160, and 600 WVDC.

And you can get all you need right now... from a few to production quantities.

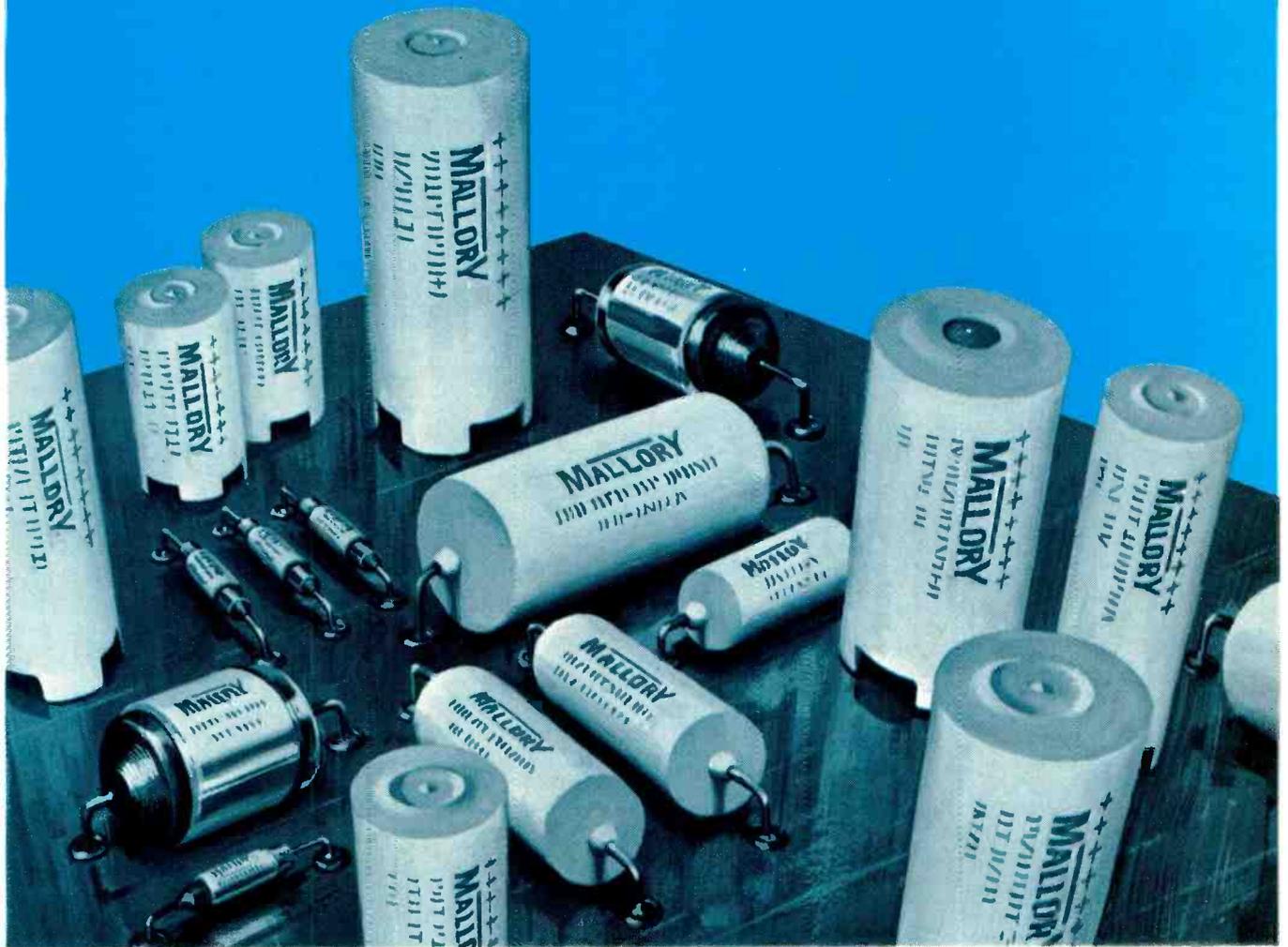But if you want high-value capacitors, we have them, too. In fact, we can supply just about any kind you need. Call your Mallory distributor today!



MALLORY

MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC.

Box 1284, Indianapolis, Indiana 46206; Telephone: 317-636-5353

Batteries Capacitors Controls • CRIME ALERT® • DURATAPE® • Recorders • Resistors • Semiconductors • SONALERT® • Switches • Timers

Circle 10 on literature card



TV TUNER SUBBERTM



Transistorized Test Unit substitutes the tuner in defective TV Receiver to prove whether original tuner is good or bad.

Completely self-contained and battery operated.

Requires only two connections (antenna and i.f. cable)
Comes complete with extension cables.

Substitutes the VHF tuner and tests the UHF tuner.

Provides signal to simplify testing of tuner, i.f. system and AGC system.

Use on the bench, or in the home; in most cases without removing tuner or chassis from cabinet.

Complete kit **\$22.95**

Factory wired **\$29.95**

Add \$1.00 shipping and handling on prepaid orders. We will ship C.O.D.

CASTLE TV TUNER SERVICE

5701 N. Western Ave., Chicago, Ill. 60645 • Ph. 312-561-6354

Circle 11 on literature card



FOR TIGHT SPOTS!

CHAPMAN

**Midget RATCHET SET
plus ADAPTERS**

**18°
Working
Arc**

**POST
PAID**

Seventeen different interchangeable adapters with a screwdriver attachment and extension, plus the world's mightiest MIDGET RATCHET in a compact 4" x 6" steel case. The strength of this twenty tooth stainless steel ratchet far exceeds torque standards set by military specifications. Requiring only an 18° working arc, reverse action is obtained by simply turning the ratchet over. Kit includes 12 Allen Hex Adapters from .050" to 5/16", 2 popular Philips sizes (#1 and #2), 2 Slotted Head sizes (1/4" and 3/8"), plus a 1/4" Square Drive for use with standard sockets.

Only \$12.95

Send Check
or Money Order

**POCKET SIZE
NO. 6320 KIT**



Send Check
or Money Order to ...

THE CHAPMAN MANUFACTURING COMPANY

DURHAM, CONNECTICUT 06422 Dept. ES-4

Circle 12 on literature card

(Continued from page 10)

control, which is mounted near the service switch.

- Turn the channel selector to an unused channel.
- Rotate the color-killer control in the direction which produces colored snow. Reverse the rotation to just past the point at which the colored snow is eliminated.
- Tune in the weakest station signal that has color and rotate the ACC control CW until color just disappears. Reverse the rotation (CCW) about 1/8 turn beyond the point where the color reappears.
- Check the color performance on all available channels, to be sure color is obtained on each channel.

Modification to minimize tube failures


Zenith 12CB12X and 16DB12X TV chassis

Late-production runs of these two Zenith chassis include an additional diode which should minimize one type of tube failure.

The function of diode SE201 is to supply to the series heater string a voltage of about 1/2 the level of the line voltage. SE201 supplies a half-wave, unfiltered, negative DC voltage to the tube heaters, without the heat a dropping resistor would create.

However, if the SE201 diode shorts, the full line voltage is applied to the tube heaters. This can cause an abnormal number of tube failures.

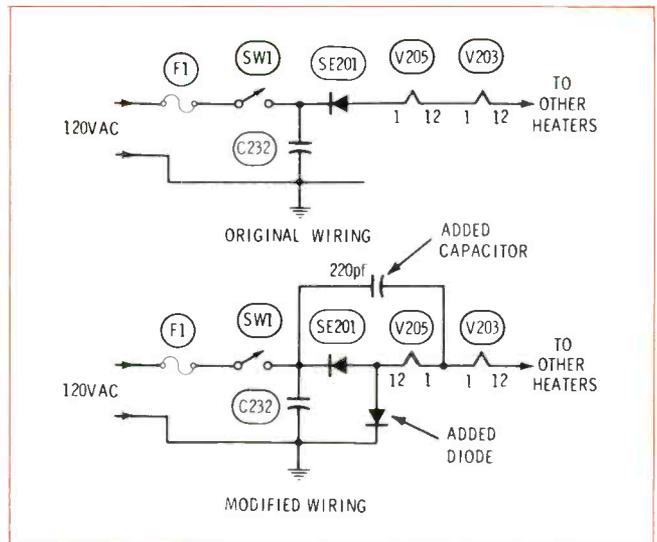The polarity of the added diode is such that the diode does not conduct when SE201 is not defective. If SE201 shorts after the other diode has been added, the full line voltage is applied to the added diode. The resultant overload would cause fuse F1



to blow and remove all power from the receiver. Although repairs are necessary before the receiver can be operated, the tubes are protected against overload.

A 220-pf, ceramic capacitor also has been added, to minimize "diode radiation"-type hum bars. To speed installation of the capacitor, the heater wiring of V205 is reversed. □



Our ECG 102A transistor replaces...

To Be Replaced	ECG Replacement	To Be Replaced	ECG Replacement
11B33	102A	MA393E	102A
11B54	102A	MA393G	102A
11B55	102A	MA393R	102A
11B56	102A	MA815	102A
11B75	102A	MA881	102A
11B75C			
11B77	102A	MA882	102A
11B77B	102A	MA883	102A
11B77C	102A	MA884	102A
11B156	102A	MA885	102A
	102A	MA886	102A
11B156C			
11B171	102A	MA887	102A
11B172	102A	MA888	102A
11B175	102A	MA889	102A
11B176	102A	MA890	102A
	102A	MA891	102A
11B178			
11B186	102A	MA892	102A
11B187	102A	MA893	102A
11B263	102A	MA894	102A
11B270	102A	MA895	102A
		MA896	102A

and hundreds more.

The 102A is only one big part of our very small line.

Just 124 Sylvania ECG semiconductor parts will replace over 41,000 manufacturer's part numbers and JEDEC types.

Our new ECG semiconductor replacement guide makes it easy for you to find out exactly which one of ours is the one you need.

With our guide and our 124 replacements, you can service practically any solid-state entertainment product on the market.

No more lugging sets back to the shop because you couldn't carry all the parts you needed.

With Sylvania's 124 semiconductors you can handle almost all of your repair jobs right in your customer's home.

Stock up on Sylvania ECG semiconductors now.


It's just another small thing from GTE Sylvania that can take a big load off your back.

Sylvania Electronic Components,
Waltham, Mass. 02154

GTE SYLVANIA

Color-TV Test Jigs

by the ES technical staff

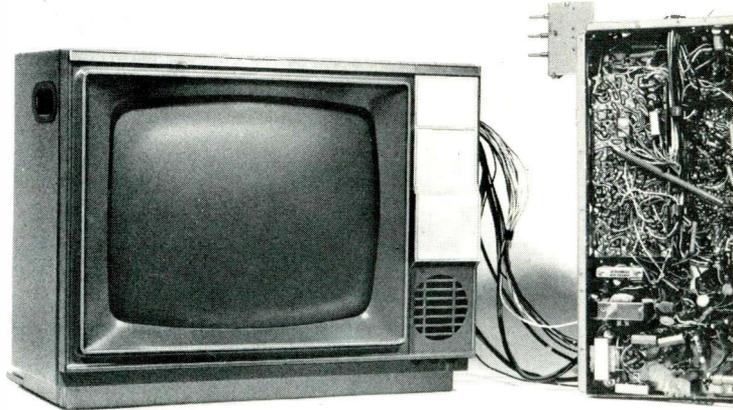

■ Basically, a color-TV test jig consists of a color picture tube and/or the convergence and yoke assemblies and other CRT-related circuitry, cables and sockets required to physically connect and electronically match a substitute picture tube to a particular color TV chassis.

The primary purpose of a color-TV test jig is to perform as an acceptable substitute for the picture tube normally used with a chassis. The major reasons for such substitution are:

- To eliminate the need for bringing into the shop the complete receiver. Instead, when in-shop servicing of the main chassis is required, the chassis and tuner assembly can be removed from the cabinet, brought to the shop and connected to the color-TV test jig, and the bulky, heavy and easily-damaged cabinet and color CRT can be left in the home.
- Rapid determination of whether a visual trouble symptom is caused by a defect in the chassis or whether it is caused by a defective picture tube. If the color-TV test jig is portable, this determination can be made in the home, providing the customer first-hand proof of the source of the defect, and, if the picture tube is defective and the policy of the shop permits in-home replacement of picture tubes, it can

eliminate the need for in-shop servicing.

Adapting The Color-TV Test Jig To A Chassis

As implied previously, to acceptably perform as a substitute for the picture tube regularly used in a color-TV chassis, the test picture tube must be matched both physically and electrically to the chassis. Because of the physical and electrical differences which exist among the many makes and models of color-TV receivers in use today and those which will be produced in the future, adaptation of a test jig to a majority of these receivers requires a variety of different cables, sockets, plugs and matching devices, commonly referred to as "adapters."

The major differences of designs for which adapters usually are provided are:

- **CRT base**—This essentially is a "physical" match of the chassis CRT socket to the base plug of the picture tube in the test jig, to insure that the various elements of the substitute picture tube receive the correct operating voltages and/or signals.
- **Convergence**—In test jigs equipped with dynamic convergence circuitry and adjustments, this involves a "physical" match of the convergence socket of the color-TV chassis

to the socket of the extension cable of the test-jig convergence board. In test jigs with only a static, or center, convergence assembly and no dynamic circuitry adjustments, this involves plugging into the convergence socket of the color-TV chassis a small assembly which electrically simulates the load normally imposed on the sweep circuit by the dynamic convergence circuitry.

- **Yoke**—This can involve both electrical and physical matching. Physically, the yoke socket of the color-TV chassis must be adapted to the plug of the test-jig yoke. The electrical match relates to the inductances of the coils of the test-jig yoke, which must approximate those of the coils of the TV chassis. If they do not, ringing, insufficient or excessive width and/or height, or some other form of abnormal raster might be produced. For example, if an old RCA CTC9 color-TV chassis is connected to a new RCA test jig, the set will operate normally except that the raster will be slightly too wide and the height reduced.

These small discrepancies in raster size are of no consequence in most cases. A bench technician should have no difficulty evaluating the performance of a chassis/jig combination with

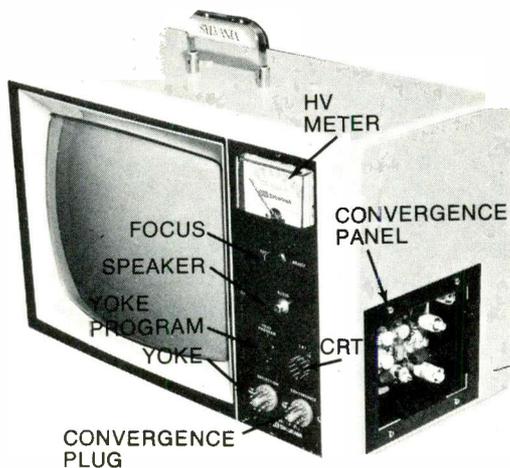


Fig. 1 Diagonal view of the GTE-Sylvania Model CK1500X Chek-A-Color Jig, showing the locations of the yoke-programmer plug and other components.

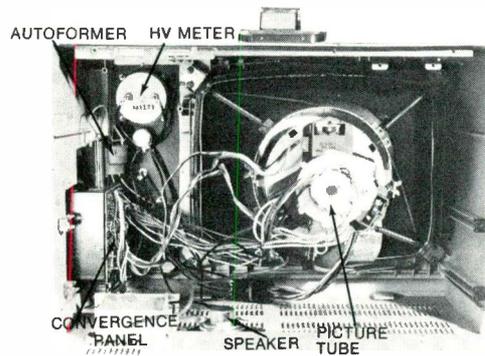


Fig. 2 Rear view of the Sylvania jig, showing the interior details.

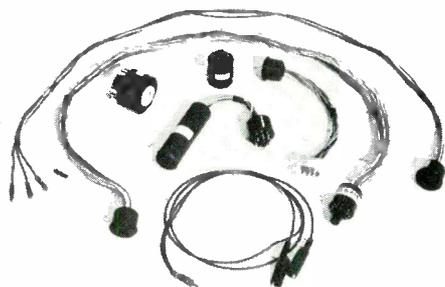


Fig. 4 Examples of the extension cables, plugs and adapters which are available from Sylvania distributors.

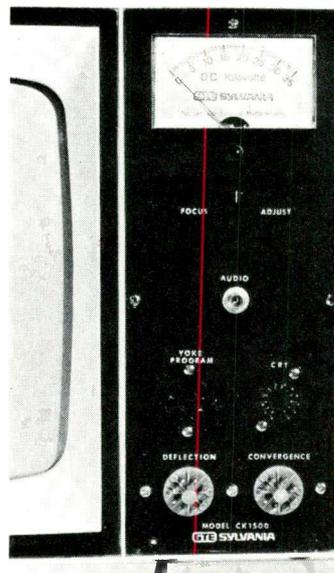


Fig. 3 A close-up view of the Sylvania test-jig panel with controls.

GTE-Sylvania Model CK1500X Chek-A-Color Jig

Cabinet: Made of two-toned plastic; apparently originally designed for a portable color receiver. Included are: a handle; a plastic back; a panel on side, for convergence board; a panel on front, for high-voltage meter, and plugs for yoke, yoke programmer, convergence, CRT base and speaker.

Picture tube: A 15-inch color-picture tube is furnished. A 4M-ohm resistor, which is wired in series with the anode lead, provides protection against damage by internal arcs.

Focus: Built-in source. A fixed amount of focus voltage for low-focus-voltage tube is provided by multiplier resistor assembly of high-voltage meter wiring.

High voltage meter: A built-in, high-voltage meter measures up to 35KV, in 500-volt increments.

Speaker: A 5-inch speaker is mounted on bottom of cabinet. A cable, with plug and clips, for connection between speaker jack on front panel and chassis, is supplied.

Center convergence: Components required for purity and four center-convergence adjustments are mounted on neck of CRT.

Dynamic convergence: A convergence board, accessible through a recess in side of cabinet, permits dynamic convergence, if needed.

Yoke matching: Switching of yoke coils by means of "yoke programmer" plugs plus an internal autotransformer gives a choice of

10 horizontal and 2 vertical yoke inductances, including those needed for hybrid and solid-state chassis.

Accessory cables, loads, and plugs: 6 "yoke programmer" plugs are furnished with the jig. 60 cables and plugs are available. A booklet which lists correct cables and plugs for use with each brand and chassis of receiver is included with jig. Prices of adapters and plugs range from \$1.00 to \$6.00.

Size and weight: GTE-Sylvania Model CK1500X Chek-A-Color Jig is 20½ inches x 14 inches x 16 inches, weighs 33 pounds.

Price: GTE-Sylvania Model CK1500X Chek-A-Color jig is priced at \$239.15, and is available from distributors of Sylvania tubes and TV receivers.

GTE-Sylvania Model CK1500 Chek-A-Color Jig

Similar to Model CK1500X, except it does not have some of the deluxe features, such as the high-voltage meter, yoke autotransformer and speaker, and only one yoke-programmer plug is included. The price is \$172.50.

Kits are available individually, at extra cost, to add the features of the CK1500X jig. Kits and prices are: K501 speaker kit, \$6.90; K502 high-voltage meter kit, \$33.90; K503 solid-state yoke transformer, with 5 yoke-programmer plugs, \$25.85.

slightly mismatched yoke-coil inductances, if the home-call technician relates to him the width, height and vertical linearity produced by the yoke normally used with the chassis.

Some makes of test jigs actually provide a method of matching the inductances of the test-jig yoke coils to those of the coils of the yoke normally used with the chassis.

• **Focus voltage**—A test jig equipped with a picture tube which requires a focus potential of 4.7K or 5K volts will not produce a raster when operated by a chassis normally equipped with a picture tube which requires a much lower focus potential. To match up such a chassis/jig combination, either an external power source will be required to supply the high focus potential required by the test jig or the test jig will have to be supplied with an adjustable divider assembly for dropping down part of the chassis high voltage, for application to the focus element of the test-jig picture tube.

If a test jig has no "built-in" provision for matching the focus potentials of chassis and jig, a circuit for supplying the correct focus potential can be built from the special high-megohm resistor assembly and focus control which in some chassis are used to develop the focus potential from the high-voltage supply.

Application Notes

Recently, three different makes of color-TV test jigs were used and analyzed in the ES lab. The features, specifications and photos of these test jigs are listed and shown separately here.

During the use of the test jigs, the following application notes were made:

Jig-to-chassis grounding

Normally, the chassis and picture tube of a color-TV receiver are grounded together by a metal cabinet, which is common to both, or the chassis presses down against a flat, conductive ribbon which is connected to the metallic mask of the picture tube.

The chassis and picture tube must be grounded together because a voltage charge will develop on any ungrounded metallic surfaces near the face or bell of the picture tube and, when the potential is sufficient, will arc over to the nearest grounded surfaces—which could be a human hand on a control knob. Such arcs can be dangerous as well as annoying.

Because the "automatic" grounding which exists between chassis and picture tube when both are installed in the cabinet does not exist when the chassis is connected to the picture tube of a test jig, separate grounding connections between the two must be made.

All three of the test jigs used in the ES lab were equipped with a ground cable and clip for connection to the TV chassis. Be sure the mask and aquadag of the test-jig picture tube and the receiver chassis are connected together, to prevent a difference of potential between them.

Use of the test jig with a "hot-chassis" TV

One side of the input power line of some color-TV receivers is connected electrically to the chassis. To reduce the possibility of electric shock to anyone who touches them, these hot-chassis receivers are equipped with blocking filters in the antenna leads, plastic chassis mounts, fishpaper, plastic shafts for controls external to the cabinet, and a variety of other insulating devices.

However, when the "hot" chassis is removed from the cabinet, few of the previously described insulating devices are operative or effective. Consequently, when the chassis is removed from the cabinet and connected to a test jig, the chassis should be operated from an isolation transformer. (Do **not** use an autotransformer; the secondary of an autotransformer is not isolated and, consequently, does not provide the required protection.)

Degaussing

Because degaussing of the picture tube of the test jig seldom is needed unless the jig is moved, and because the variety of degaussing circuits used in color-TV receivers makes it impractical to design a test jig which will operate from all or most of them, most commercially-built color-TV test jigs are not equipped with degaussing systems.

Most automatic degaussing circuits used in TV receivers can be disconnected from the internal degaussing coils and the receiver operated without damaging either the degaussing circuit or any other receiver circuitry. The only exceptions which we are aware of are those automatic degaussing systems equipped with a thermally-operated switch. A jumper should be connected across the switch, to substitute for the coil.

If you are uncertain whether a particular chassis can be operated without damage while connected to a test jig, check the operating instructions provided with the test jig.

Use of extension cables

The use of an extension cable between the base of the picture tube in the test jig and the picture-tube socket of the chassis can cause unacceptable smearing of the fine detail in the picture. This is the only extension cable which noticeably changes the size or quality of the picture. Even an 18-inch extension cable with cardboard spacers separating the grid and cathode wires will significantly reduce the detail in the picture.

This reduction of picture detail is of no consequence when analyzing many color-TV trouble symptoms; however, if the complaint involves the sharpness or quality of the color of the picture, it can make the analysis more difficult or, in extreme cases, impossible.

If possible, position the TV chassis and the test jig so that no extensions are required between the two. For example, the test jig could be positioned facing the rear of the bench, with a mirror

Fig. 5 Diagonal view of the RCA Mark III color-TV test jig. The optional high-voltage meter should be mounted above the convergence board.

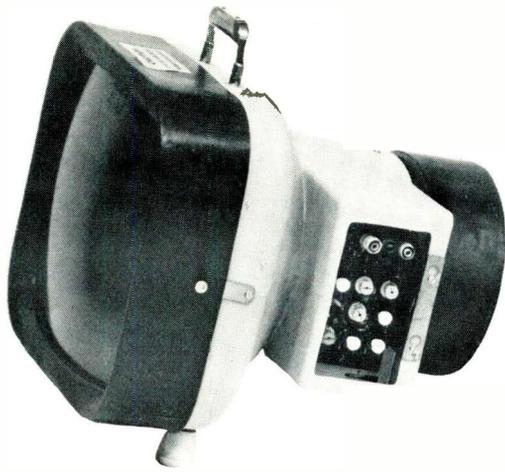


Fig. 6 Rear view of the Mark III shows the CRT, yoke and convergence plugs, which are accessible.



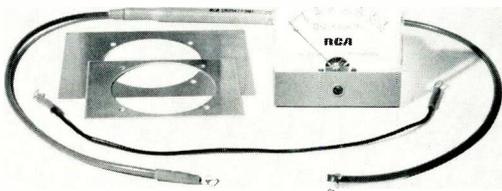
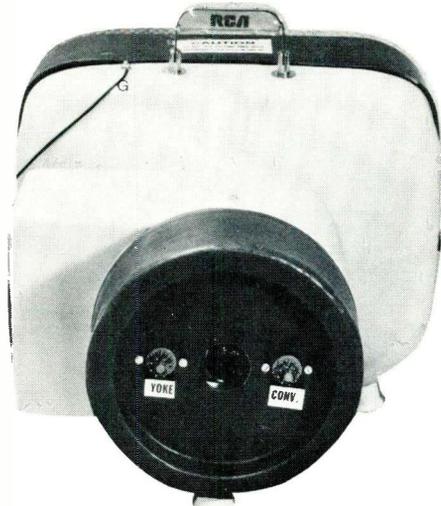


Fig. 8 The optional 10J110 high-voltage meter kit, which can be installed in the Mark II and the Mark III jigs.

A

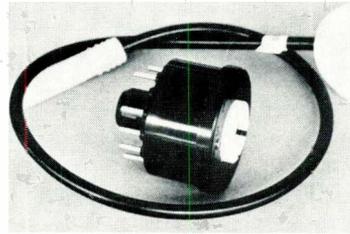

B

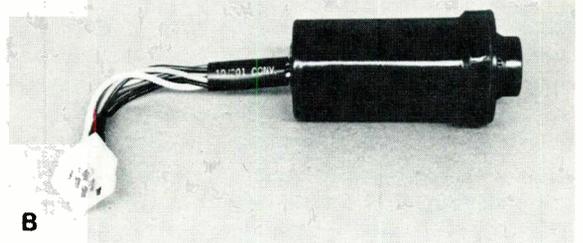

C



Fig. 7 A, B & C Examples of the extension cables, adapters and kits which are available from RCA distributors.

providing a reflected view of the picture tube screen, and the chassis positioned at the front of the bench, so that it not only is as close as possible to the test jig but is more accessible to the technician. The only inconvenience involved in such an arrangement would be remembering that the mirror image is the reverse of that of the view it is reflecting, or left is right and right is left.

Diagnostic Limitations

The designs of commercially-built test jigs necessarily bypass, short out, open up or in some

other manner incapacitate or provide a substitute for one or more picture-tube related circuits. Consequently, any defects in such circuits might be "covered up" by the test jig.

For example, the chassis of color-TV receivers equipped with rectangular picture tubes include pincushion-correction circuits. Because these pincushion-correction circuits usually are shorted across by the test jig, any trouble symptoms caused by defects in them would be effectively eliminated by the test jig.

Also, if the chassis circuit

which produces the focus voltage for a picture tube which uses a relatively low voltage is replaced by a source built into the test jig or some other source external to the chassis, any defects existing in the chassis focus circuit (and the related trouble symptoms) will be effectively eliminated.

Determine which chassis circuits and/or functions are incapacitated or substituted by the test jig you use, so that you can be alert to any related defects and trouble symptoms which might be "covered up."

RCA Mark II and Mark III Color-TV Test Jigs

Cabinet, Mark II: Made of plastic; resembles that of a table-model receiver. No handle. A degaussing coil, with a plug to fit RCA chassis, is supplied.

Cabinet, Mark III: Two-piece, form-fitting plastic, with handle. Hooks can be added, if desired, for suspension of the unit from a ceiling.

Picture tube: Not furnished. A 19-inch color-picture tube which uses high-voltage focus (about 4.7KV) is required, and is available from RCA distributors for \$64.50.

Focus: Approximately 4.7KV is required from the chassis under test. An external source must be used with chassis equipped with picture tubes which use lower focus voltage.

High-voltage meter: A meter kit, RCA stock 10J110, for installation in either the Mark II or Mark III, is available for \$26.19.

Speaker: No speaker included. The Mark II cabinet has space on the inside of the front panel where one can be installed.

Center convergence: A complete convergence system around the neck of the picture tube is included.

Dynamic convergence: Convergence panel is recessed in the side of Mark III cabinet, where it is accessible for adjustments. Convergence board in Mark II cabinet is mounted to top, near back.

Yoke matching: Both jigs are available with either tube or solid-state yoke and convergence components. A solid-state yoke can be used to replace the tube-type yoke when servicing solid-state chassis.

Accessory cables, loads and plugs: A variety of adapters, cables, and plugs are available at prices ranging between \$1.26 and \$7.56. Three kits in "tool boxes", for Admiral, Magnavox and Zenith, are available, in addition to dozens of ICTJ-standard individual adapters. Adapters are listed by model, with explanatory notes, in the book: "RCA Industry Compatible Test-Jig Cross Reference". A kit of 8 cables, including one for automatic degaussing, is furnished with each Mark II jig. A kit of 7 cables is furnished with each Mark III jig. Size: Mark III is 17½ inches x 16½ inches x 17¾ inches.

Price: Mark II or Mark III is available, in either tube or solid-state version, for \$115.50, less picture tube, from distributors of RCA parts, tubes and accessories.

Summary

The two major advantages which can be realized from the use of a color-TV test jig—elimination of the need for bringing into the shop the receiver cabinet and picture tube, and being able to quickly determine whether or not a trouble symptom is caused by the picture tube—alone make it a valuable servicing aid, either in the home or on the bench.

Adaptation of a color-TV test jig to a particular chassis involves both physical and electrical matching. In most cases, the adapters provided with the test jig or which are available

from the manufacturer of the jig reduce adaptation to merely selecting the correct cable, socket and/or plug.

If a particular adapter is needed and unavailable from the manufacturer of the test jig you are using, it is probable that an adapter designed for the application can be obtained from the adapter line of another brand of test jig, and used with yours. At least one test-jig manufacturer offers adapters which can be used with other makes of test jigs.

Adapters can be fabricated by a technician, but it can be time

consuming, and such home-built adapters too often become more of a source of trouble than the chassis the technician is servicing. When a commercially-built adapter is available, even from the manufacturer of another make of test jig, buy it, and spend your time servicing TVs, not your own home-built test-jig adapters.

Color-TV test jigs are safe to use, provided the grounding and other related precautions previously outlined are heeded, including the use of an isolation transformer when servicing "hot" chassis.

(Continued on Page 20)

Cable Description	Test Jig 10J102 & 10J103 See note 1	Test Jig 11A1015-A See note 1
Picture Tube Socket Adapter	Not Required	Not Required
Picture Tube Socket Extension Cable	13B113	13B111
Deflection Yoke Adapter	10J220	10J118 and 10J220
Deflection Yoke Extension Cable	221X1	Not Required
Convergence Adapter	10J221	10J221
Convergence Extension Cable	221X1	221X1
Automatic Degausser Adapter	10J304	
Automatic Degausser Extension Cable	10J111	[Defeat Degausser Coil Circuit with Jumper]
High Voltage Extension Cable	13A100	13A100

Notes:

1 It may be desirable to obtain better convergence. This can be accomplished by removing the red lead with white tracer from Convergence Board Terminal "H" (Junction of GRN, RED/WHT and WHT leads) and connect to Terminal "F" (Junction of R-813 and GRN lead). After completion of tests, return wiring to its original position.

Zenith (cont'd)		Manuf. Page No.	Chassis	Models	Manuf. Page No.
Chassis	Models				
			20Y1C48 (cont'd)	Y4523H1/R1/R1, Y4525M1/M4, Y4528H1, Y4531DE1, Y4533M1, Y4537M1, Y4539H1/R1/R1, Y4541W1, Y4543P1, Y4545H1, Y4547M1, Y8530M1, Y8548H1, Y8558M1, Y8559M1, Y8568DE1 (Combination)	53
16Z8C50 (cont'd)	Z4514M07/M08, Z4515H07/H08, Z4516W07/W08, Z4517M07/M08, Z4518DE07/DE08/P07/P08, Z4519P07/P07, Z4520M07, Z4524H07, Z4526M07, Z4528H07, Z4532DE07/P07, Z4533W07, Z4535M07, Z4538DE07/P07, Z620B07	80			
20X1C36	T2962W, T2974W, T2976H, T2978W, X4541W, X4543DE, X4545H, X6541W, X6543DE, X6545H/X, X6577M, X6549H, T2912M, T2961R/W, T2963W, T2965H, T2967M, T2968M, X4204L, X4206W, X4210R/W, X4214W, X4218M, X4222W, X4224H, X4226M, X4228H, X4240W, X4242M, X4246H, X4257DE, X4501Y, X4500W, X4511W, X4514R/W, X4518R/W, X4519W	53	20Y1C48 or 20Y1C50	GA50-34R/R2/W/W2, GA50-36W/W1, GA50-40W/W1, GA50-42H/R1, GA50-44M/W1, S2951R6/R7/W6/W7, S2959R6/W6, T2952L6, T2953W2/W6/W7, T2956W6, T2958P6/W6, T2960M6, T2969W6, T2971M6, T2972H6, T2973W6, T2979W6, T2991DE6/P6, Y4202Y6, Y4204W6, Y4207W6, Y4216W6, Y4502W6/W7/W8/W9, Y4507W6, Y4514R6/R7/R8/R9/W6/W7/W8/W9, Y4515W6/W7/W8/W9, Y4518DE6/DE7/DE8/DE9/P6/P7/P8/P9, Y4517M6/W7, Y4518W6, Y4519P6/W6, Y4520M6, Y4523H6/H8/R6/R8, Y4526M6/M8, Y4528H6/H8, Y4532DE6/DE8/P6/P8, Y4533W6/W8, Y4537M6/M8, Y4539H6/H8/R6/R8, Y4541W6, Y4543DE6/P6, Y4545H6, Y4547M6, Y8530M6, Y8548H6, Y8558M6, Y8559M6, Y8568DE6 (Combination Model), GA50-37W, GA50-41W, GA50-43H, GA50-45M, Y6207W6, Y6507W6, Y6519P6/W6, Y6520M6, Y6523H6/R6, Y6541W6, Y6545H6, Y6547M6, Y6549H6, Y6543DE6/P6, Y6550M6, Y6560M6, Y6565M6, Y6570DE6 (Combination Models)	53
20X1C38	X4520W, X4525M, X4528H, X4531DE, X4533W, X4535W, X4537M, X4539H/R, X4547M, X6206W, X6218M, X6222W, X6226M, X6240W, X6242M, X6246H, X6247DE, X6501/W, X6520W, X8220M, X8240W, X8260H, X8280M (Combination)	53			
20Y1C48	S2959R1/W1, S2990W3, T2955W3/W5, T2956W1, T2959W1, T2971M1, T2972H1, T2973W1, T2975W1, Y4202Y6, Y4204W6, Y4217W7/W8, Y4502W2/W3, Y4507W1, Y4514R3/W3, Y4516R3/W3, Y4517M3, Y4518W1, Y4519W5, Y4520M5, Y4522W1/W4	53	20Z1C37	T2930L6, Y3905Y2, Y3905Y6, Y3910W6, Y5918H6	53

Fig. 9 Examples of the detailed listings in the RCA test-jig cross-reference book.

Fig. 10 The Tele-Matic Econo-Jig, which can be carried, placed on a bench or hung from the ceiling.



Fig. 12 The components and accessories shown here are furnished with the TeleMatic Econo-Jig.



Fig. 11 Examples of the loads, adapters and extension cables which are available from TeleMatic distributors.

TO USE TELEMATIC YOKE ADAPTORS WITH JIGS LISTED BELOW:

EQUIP JIGS FROM	WITH MATCH CORD
MOTOROLA (KT-120) RCA 70° (11A1015)	MODEL MC-77
MAGNAVOX (701264)	MODEL MC-78
ZENITH (12 pin Molex) SUPERIOR (CJ-1900)	MODEL MC-79
ZENITH (8 IN-LINE MOLEX CONNECTOR)	MODEL MC-8

Fig. 13 Typical listing of adapters available from TeleMatic for other brands of jigs and the extensions and adapters needed for each brand and model of receiver.

ADMIRAL
YA11 CD51 25 Series
YA11 CD55 D11 Series
YA11 CD52 G11 Series
YA12 CD55 G12 Series
YA12 CD52 G13 Series H12 Series, K15 Series
YA12 CD58 H10 Series

TeleMatic Model EJ190 Econo-Jig

Cabinet: Shipped unassembled, the cabinet consists of two metal side panels, a top panel of metal reinforced with plywood, a wood bottom, a perforated fiberboard back, and a plastic mask which serves as the front panel. Captive nuts imbedded in the wood make assembly easy. Metal panels are finished in imitation walnut grain. Also furnished are: rubber feet, a handle and three eye-bolts, for ceiling mounting.

Picture tube: Not furnished. None available from TeleMatic. Any standard 19-inch color tube can be used.

Focus: Supplied by the TV chassis. Because the majority of color-TV chassis are equipped with picture tubes which use about 4.7KV of focus voltage, this type of picture tube should be selected for use in the EJ190 test jig. And, because a chassis which supplies a focus voltage of less than 800 volts probably would not produce a raster on this type of picture tube, a focus supply which is fed via special resistors from the high-voltage supply will be required, if you want to operate a low-voltage-focus chassis with the jig.

High-voltage meter: No provision is made for a built-in meter.

Speaker: No provision is made for a built-in speaker.

Center convergence: Components to be mounted on the neck of the picture tube, for center convergence and purity adjustments, are supplied with the jig.

Dynamic convergence: No provision is made for dynamic convergence; however, TeleMatic offers "convergence load" adapters which plug into the chassis and provide a load to the sweep circuits which is similar to that normally provided by the convergence system. TeleMatic states that dynamic convergence usually is not essential for proper test jig operation, and that testing is much faster without dynamic convergence.

Yoke matching: The yoke supplied with the jig matches most tube-equipped TV chassis. Their plug-in "Match-A-Yoke" adapter compensates for all but solid-state yoke differences. TeleMatic offers a "Solid-State Transverter" adapter which matches any solid-state chassis to any jig equipped with a tube-type yoke.

Accessory cables, loads and plugs: About 32 extension cables, loads, and adapter plugs, for most brands and models of color receivers, are available from TeleMatic. Also, "match cords" are available, to convert other brands of test jigs to the use of TeleMatic cables and plugs.

Size: Econo-Jig Model EJ190 is 18¾ inches x 15¾ inches x 18¾ inches.

Price: Econo-Jig Model EJ190 sells for \$49.95, with the leads and components shown in the photo here. The Match-A-Yoke unit is \$6.95, and the improved Solid-State Transverter is \$24.95. Any of these items can be obtained from distributors who sell TeleMatic products.

now **9** midget driver sets



*for double duty on dozens
of popular screws and nuts*



Three new assortments have joined Xcelite's family of "Compact Convertibles." Each an Xcelite "original." Nowhere will you find such a variety of sizes and types in a midget set, for driving slotted, Phillips, Allen, Scrulox®, hex, and clutch head screws. And hex nuts.

All of professional quality, precision made of finest materials. All doing "double duty" with torque amplifier handle that slips over color-coded midget tools for longer reach, greater driving power. Each easily identifiable on the bench or in the service kit thru Xcelite's exclusive, optically clear, plastic "show case" that closes securely with positive snap-lock.

nationwide availability through local distributors

NEW!

PS130
3 slot tip, 2 Phillips
screwdrivers, 5 nutdrivers

PS140
4 slot tip, 3 Phillips screwdrivers, 3 nutdrivers

PS6
3 slot tip, 3 Phillips screwdrivers

PLUS PS88, PS120, PS7, PS89, PS44
and PS-TR-1 with varying selections
of screwdrivers and nutdrivers.

REQUEST
FREE CATALOG.



XCELITE, INC., 18 Bank St., Orchard Park, N. Y. 14127
In Canada contact Charles W. Pointon, Ltd.

Circle 14 on literature card

Fig. 14 The Match-A-Yoke by TeleMatic makes small changes in the matching of the test jig yoke and the chassis, to reduce ringing and possible insufficient or excessive picture size.




Fig. 15 Matching of a test jig with standard yoke to a solid-state chassis is accomplished by TeleMatic with their improved Transverter adapter.

(Continued from Page 18)

Because a color-TV test jig incapacitates and/or provides a substitute for some of the picture-tube-related circuitry in the color-TV chassis, you should study carefully the application notes which are provided with the test jig, to familiarize yourself with exactly which chassis circuitry does not function when the test jig is connected. Remember, defects in such circuitry usually are effectively "covered up" by the test jig.

A color-TV test jig is a useful test instrument and, in the opinion of the ES technical staff,

should be purchased and used by all TV shops which service color TV's. But, as with all test instruments, the general design, operation, applications and limitations should be clearly understood by the technician before he uses it. Having read this article, you should now be in a position to select the test jig that best suits your situation, and, after carefully reading the application notes which accompany it, proficiently use it and realize from that use the ultimate advantage of any practical test instrument—quicker, more profitable servicing. □

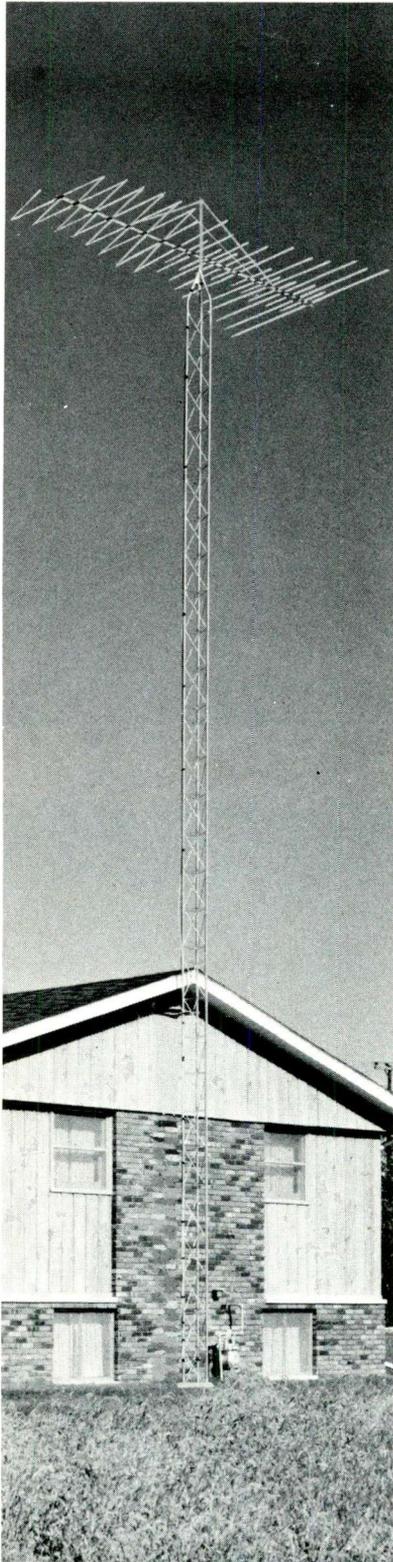

Do you have ONE SOURCE of SUPPLY for any TOWER or accessory you might need?

Do you have one source of supply for any tower or accessory you might need? ROHN manufactures a complete line of towers of every style and type for every need . . . Home, Commercial or Industrial. A complete line of accessories is also available for every type tower or antenna installation.

Almost a Quarter-Century of experience and ROHN developed mass production techniques with the latest electronic equipment means the highest quality product at the lowest possible price. Hot Dip Galvanizing of all towers and accessories gives long life and attractiveness to its products.

Here's what this means to you . . .

- ONE SOURCE OF SUPPLY —
Hundreds of items from one dependable source.
- CUSTOMER SATISFACTION
- FAST DELIVERY

See your Distributor or write:

ROHN **MANUFACTURING**
P.O. BOX 2000 / PEORIA, ILL. 61601

Please send your catalog:

DIVISION OF



Name _____
Co. Name _____
Address _____
City _____
State _____ Zip _____

For complete
Information —
MAIL THIS
COUPON TODAY!



Circle 15 on literature card

Servicing German-made auto radios

Why Service German Auto Radios?

Because there is an extremely large number of German-made car radios in use, and they do need occasional repair, a shop willing to take them on might corner this segment of the local market.

With authorized repair stations for Blaupunkt and Becker auto radios so few and far between, it is possible that your local import car dealers are having to ship defective units to either the importer's service facility or a distant authorized independent repair shop. The shop in which this writer services auto electronics receives German car radios by mail or by United Parcel Service from dealers over a hundred miles away. When we told one local Mercedes-Benz parts manager that we could handle his in-warranty Becker repairs (as well as the more lucrative out-of-warranty repairs) he became so overjoyed that it looked for a moment like he was going to prostrate himself and kiss the ground we walked on.

Service Literature

One possible reason many technicians hesitate to service German car radios is that they believe that service manuals for these sets are not available. This is not true. Howard W. Sams has given for many years at least some coverage to the more popular German car radios. Also, the two major importers, Becker and Blaupunkt (Robert Bosch Corporation), have been most generous with their respective service manuals. I know of several shops which have requested manuals from these two companies and were surprised at the volume of material sent and the speed of the reply. Although there technically is a charge for the manuals,

they frequently come through either without an invoice or with an invoice marked "no charge".

Another reason many technicians, particularly older ones, hesitate to service German-made car radios is that in the "old days" the service manuals were written only in German and used European schematic symbols. Some of the modern manuals, however, are printed in English and use symbols which are standard in the United States. The modern manuals which are printed in German have one line or an entire paragraph in German

followed by a translation in English, French, and Spanish.

A glossary of German words commonly used in car radio service manuals is given in Table 1. Although most of the manuals covering the radios you will be servicing will be either all-English or German with an English translation, keep the glossary handy for the one out of ten manuals which is all-German.

One other source of service manuals, by the way, is the customer. Some German manufacturers pack at least a short-form manual with the warranty papers

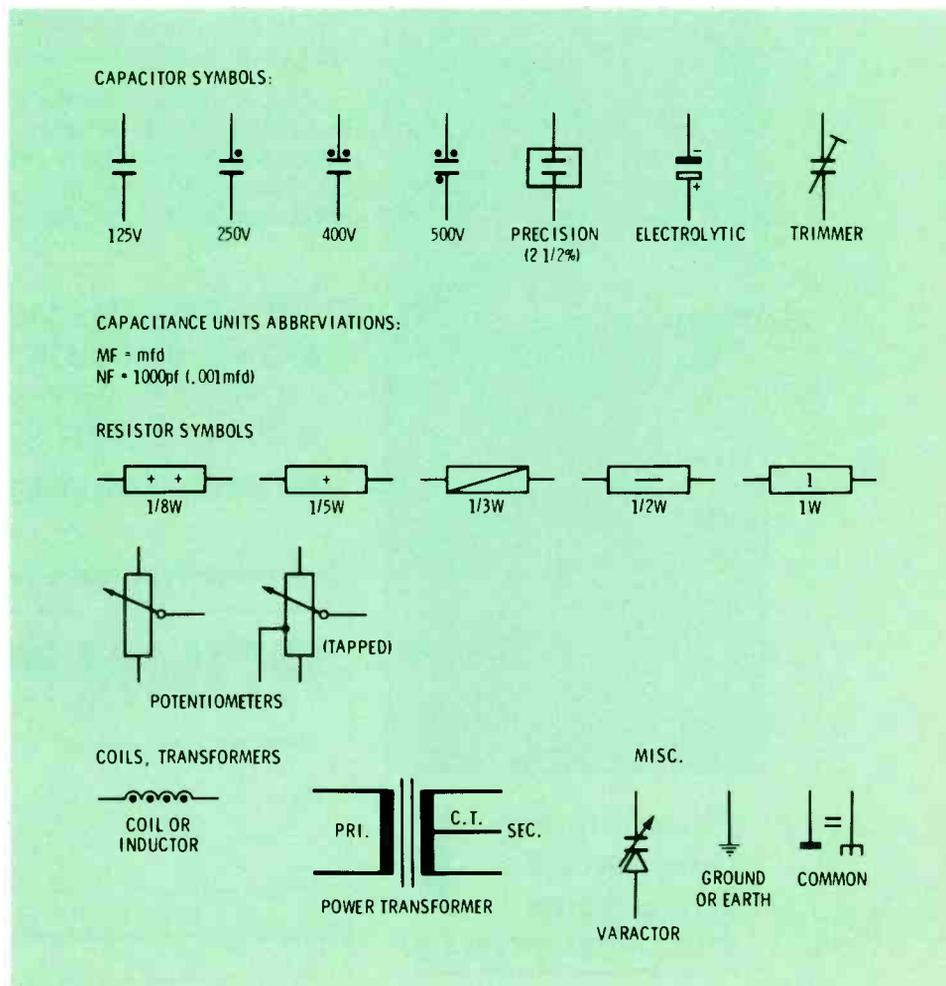


Fig. 1 Electronic component and other symbols used on most European schematic diagrams.

The big difference in TV Alignment instruments: Ours Works.

The B & K Model 415 Sweep/Marker Generator not only works, but it makes alignment jobs faster and more accurate.

Why? Because it eliminates the need for a separate marker generator, sweep generator, marker adder, and bias supply. You get it all in one compact instrument.

And it's so easy to use. The IF and chroma bandpasses are simulated on the front panel for constant reference. Lights tell you which of the crystal-controlled markers are in use and where they should be located. And the exclusive marker tilt feature lets you place the markers either horizontally or vertically, so you can always identify their exact positions.

Put the B & K Model 415 Sweep/Marker Generator to work for you.

Ask your distributor for complete details.



Product of
DYNASCAN CORPORATION
1801 W. Belle Plaine
Chicago, Illinois 60613



Model 415:
\$399.95

Circle 16 on literature card

that accompany each new radio. Frequently, you will also find a print of the schematic folded up inside one of the radio's cover plates. (The Germans rarely resort to that obnoxious practice of glueing the schematic to the radio.)

Schematic Symbols

Fig. 1 shows some of the more common schematic symbols used by the Germans. Although there will be any number of variations in use from maker to maker, those in Fig. 1 are relatively universal. Notice that the capacitor symbols show the voltage rating with a series of dots. One dot means 250 VDC, two dots indicate 400 VDC, and three dots mean that the rating is 500 VDC. Precision capacitors are indicated by a box around the normal capacitor symbol. The symbol for an electrolytic is only slightly different from our equivalent symbol.

The wattage ratings of resistors are also indicated by codes. The progression of wattage ratings is somewhat different from that used in the United States. We use one-quarter watt, one-half watt, one watt, etc. The Germans use one-eighth watt, one-fifth watt, one-third watt, one-half watt, one watt, etc.

These ratings codes allow a non-German technician to determine the rating without having to read a German-language spare-parts list (Ersatzreilliste).

When replacing one of the resistors with an odd wattage rating, use the next higher standard U.S. value. A one-fifth watt, for example, can be replaced with a one-half watt U.S. resistor.

Exact German resistance values, on the other hand, can be a problem to locate. A typical German resistor might have a value of 30K instead of the U.S. standard value of 27K or 33K. In the United States we have a "tolerance overlap" system in effect to compute the standard progression of values. If a German resistor needs replacement, use the closest standard U.S. value. For example, let's again use the German 30K value. 30,000 ohms

German	English
Kundendienstchrift	Service manual
Schaltbild	Schematic
Ersatzreilliste	Spare parts list
Abgleichpunkt	Alignment point
Lautsprecher	Loudspeaker
ZF	IF (intermediate frequency)
Masse	Ground
Spannungen	Voltage
Oszillator	Oscillator
Gemessen	Signal
Bedruckte Platten	Printed-circuit board (PCB)
ZF-Platte	IF PCB
Widerstande	Resistor
Einstellregler	Adjuster
Transformatoren	Transformer
Transistoren	Transistor
Bandfilter or ZF-Filter	IF transformer
Spulen	Coils or inductors
Kondensatoren	Capacitors
Kunstfoilen	Plastic film capacitor
Kondensatoren	capacitor
Keramik Kondensatoren	Ceramic capacitor
Elektroly-Kondensatoren	Electrolytic capacitor

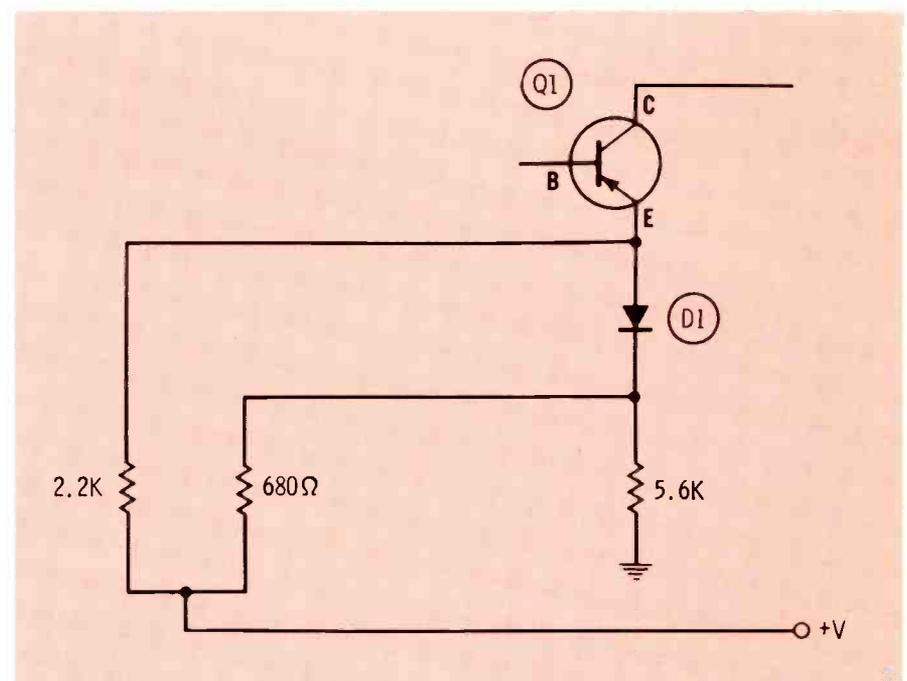



Fig. 2 Semiconductor diodes are used frequently to stabilize the bias of the front ends of German car radios.

plus or minus ten percent (3000 ohms) gives a range of 27,000 ohms to 33,000 ohms. It is likely that either a 27K or 33K with a ten per cent tolerance will fall within that range.

Fig. 1 also shows the standard European method of depicting an iron-core transformer. The

windings are shown as black solid bars instead of as coils. In some schematics it appears that the thickness of the secondary bar (relative to the primary) indicates the relative current capacity, while the length indicates the relative voltage rating. This does not, however, give absolute val-

THE MONEY TREE

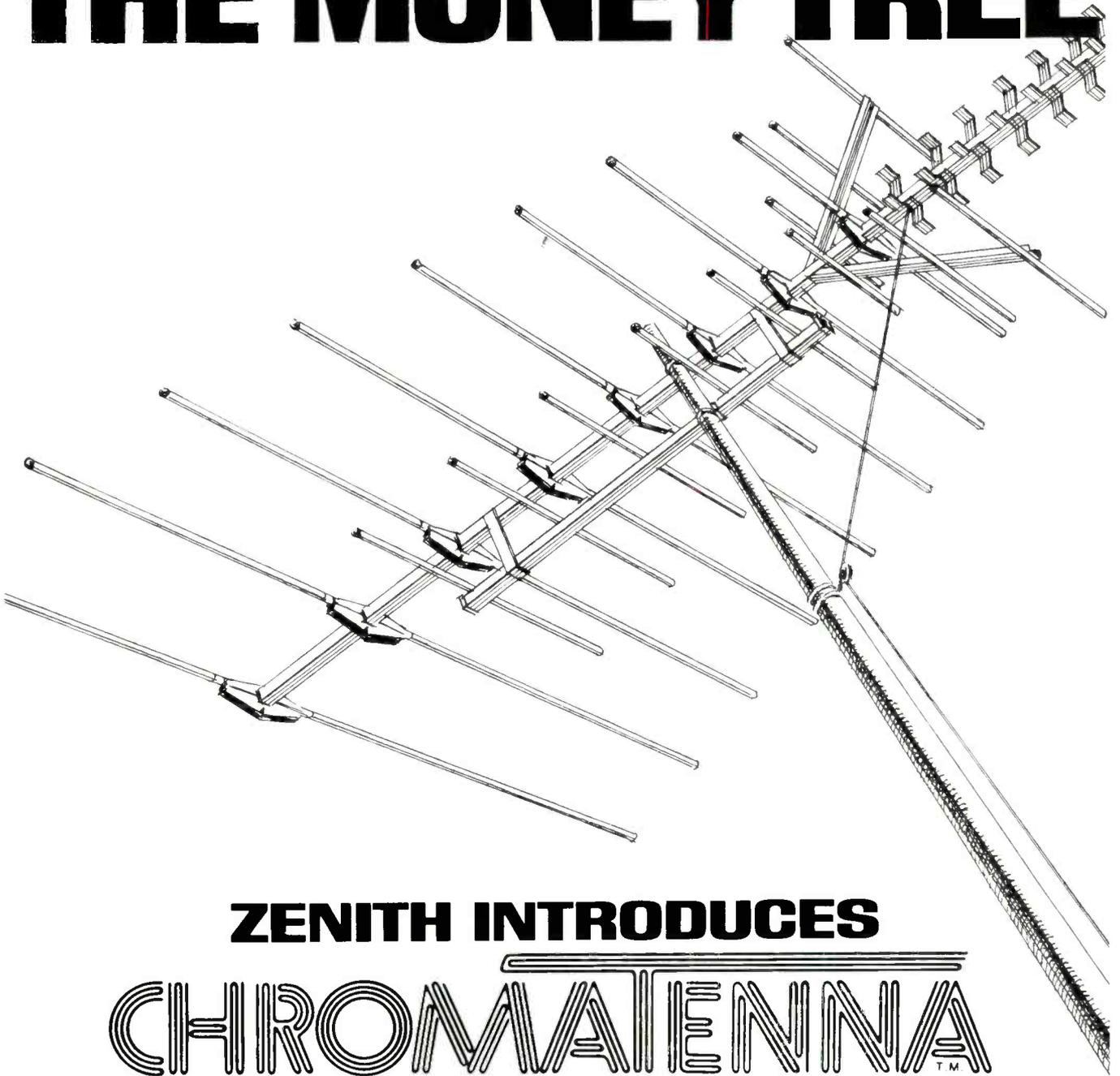

ZENITH INTRODUCES CHROMATENNATM ANTENNAS

**A whole new line of antennas from Zenith
built to deliver a peak picture...and peak profits for you.**

Zenith's new Chromatenna line incorporates all the electronic knowledge and "know how" of Zenith engineering. 20 different antennas, for color and black & white TV, meet every reception condition. Result: a *superb picture* for your area.

The new line includes 7 antennas for VHF/UHF/FM, 5 for VHF/FM and 8 for UHF/FM. And a complete line of antenna accessories.

The sales skills that helped make Zenith a sales leader have been used to put together a complete merchandising

package. Convenient Display Rack. Display Header. Wall Banner. Presentation Catalog. Ad Mats. Result: more antenna sales, *peak profits* for you.

Ask your Zenith Distributor for full information about the new Chromatenna line.



*The quality goes in
before the name goes on*

Circle 17 on literature card

ues. The idea is best illustrated by example.

Suppose a transformer had a secondary that was designed to step up the voltage. This requires that the current capacity of the secondary be scaled down in the same proportion as the secondary voltage is scaled up. The diagram would show the bar representing the secondary winding as being longer and thinner than the bar representing the primary winding. For a filament transformer, the secondary bar would appear shorter (lower voltage) and thicker (higher current) than the primary. These indications are not always in use, but the author has seen them often enough to believe that they are true.

RF Band Identification

One of the first things that you will notice about some European car radios is the strange markings on the dial scale. The customer might complain that the FM band is dead. OK, let's get down to finding out why. Only... which pushbutton is for the FM band? There might be as many as five pushbuttons marked "L", "M", "K", "U" and possibly "Q". The band designations represented by these letters are shown

in Table 2. The two bands of interest in the United States, AM and FM, will be marked "M" (medium wave) for AM and either "U" or "UKW" for FM. "U" simply means "VHF" or "Ultrakurzwellen" (ultra short waves).

The other bands frequently found on German car radios are "L" (long wave) and "K" (kurzwaben or short wave). The existence of a long wave band doesn't indicate a peculiar European penchant for monitoring aviation beacons and maritime CW traffic. In Europe, there is a very active broadcast band situated in the 150K to 300K-Hz segment of the radio spectrum. In fact, a lot of returning Americans claim that "L" was their favorite band because of the superior reception it offered. The "K" shortwave band will be a small segment of the spectrum between 2 and 10 or possibly 12M-Hz.

"Q" usually designates an outboard accessory such as a cassette tape player or a multiband short-wave converter. In sets of recent design the "Q" pushbutton operates the cassette player by switching the audio leads of the receiver from internal to an external jack. It also might turn on power to the cassette deck. European-made radios encountered in the U.S. with either "L"

or "K" bands are probably export models.

Some of the older sets made exclusively for the European market have an FM band that is slightly different from ours. These sets will tune from around 85M-Hz to 100M-Hz. You will pick up channel 5 TV audio on the low end of the dial while the upper portion of our FM band will be missing.

If you encounter one of the German car radios with a tuning dial marked in wavelength instead of frequency, you can convert the dial readings, for calibration purposes, by using the equations given in Table 2. It once was standard practice in Europe to use wavelength. Some of the older designs of European-made radios have been brought into the U.S. For example, you might encounter one on which the AM radio dial scale is marked from 594 (or 600) to 181 meters. The FM dial will be marked 3.43 to 2.78 meters.

On most modern domestic production and on all U.S. model export sets the dial is marked according to frequency.

Circuit Differences

One difference worthy of note is the widespread use of semi-

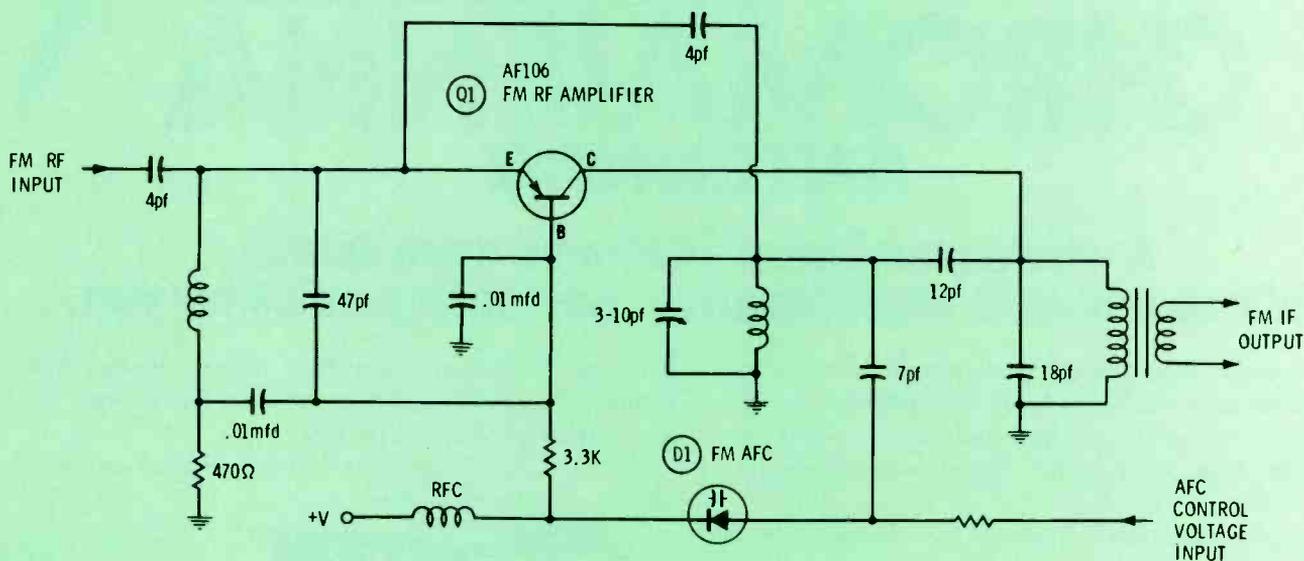


Fig. 3 The use of a single converter transistor, as shown here, in the FM front-end of a Becker Europa MU (AM/FM) receiver, is probably one reason that most German auto radios have lower sensitivity than their American-built counterparts.

conductor diodes to stabilize the bias on the front-end transistors. This type of circuit is shown in Fig. 2. The thermal coefficient of a semiconductor diode used for this purpose is such that the bias of the stage will tend to remain stable over a wide range of ambient temperatures.

This characteristic in the past has led to certain rather interesting service problems. In one older AM Blaupunkt, for example, a frequent complaint was that the radio would change stations as the customer depressed the automobile's accelerator! Because this was before the days of varactor diode tuning, and on the AM band to boot, many technicians would at first tend to disbelieve the customer. Once he road tested the car, however, he would become a believer. These radios would actually shift frequency several dozen kilohertz as the car accelerated from a stand-still to 30 or 40 miles per hour.

The cure was a new diode and a voltage check of the regulator in the car. When I encounter one of these sets, I place a Zener diode across the internal B+ line, to prevent a possible callback. Then, if the problem re-occurs the customer will hold us responsible even if he has failed to have a VW automotive electrician

Table 2

Labels Commonly Used On The Bandswitch And Pushbuttons Of German Car Radios

LABEL	MEANING
L	Longwave (150-290 KHz)
M	Medium Wave (515-1640 KHz) AM Broadcast band
U	Ultra Short wave (VHF) 87-108 MHz
UKW	"Ultra Kurz Waben" Same as "U"
K	Shortwave usually a band between 2 and 10 MHz

WAVELENGTH CALIBRATED DIALS

Some older European car radios had dial scales calibrated by wavelength rather than frequency. The unit is the meter.

Examples:

AM Broadcast 594-181 Meters

FM Broadcast 3.43-2.78 Meters

For conversion to frequency use the formulas:

$$F \text{ KHz} = \frac{300,000}{\lambda \text{ (meters)}} \quad \text{or} \quad F \text{ MHz} = \frac{300}{\lambda \text{ (meters)}}$$

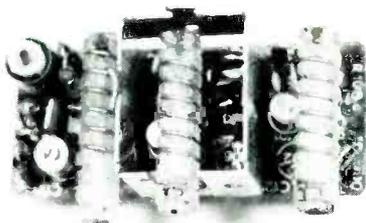


Fig. 4 The FM tuner subassembly of a Blaupunkt Model '3670 Frankfurt auto radio. Comparing the sizes of the two small, type TO-18 transistors and the rest of the circuit board will put into perspective the relatively small size of the subassembly.

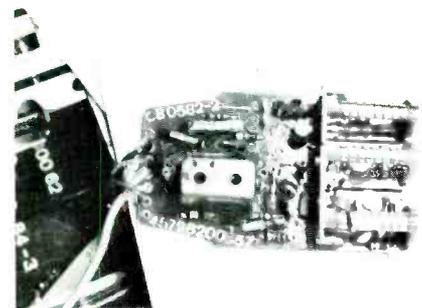


Fig. 5 The FM tuner subassembly of a Blaupunkt "Emden III" export model receiver. This subassembly is slightly larger than that in Fig. 4 because the 1st FM IF transformer is mounted on it.

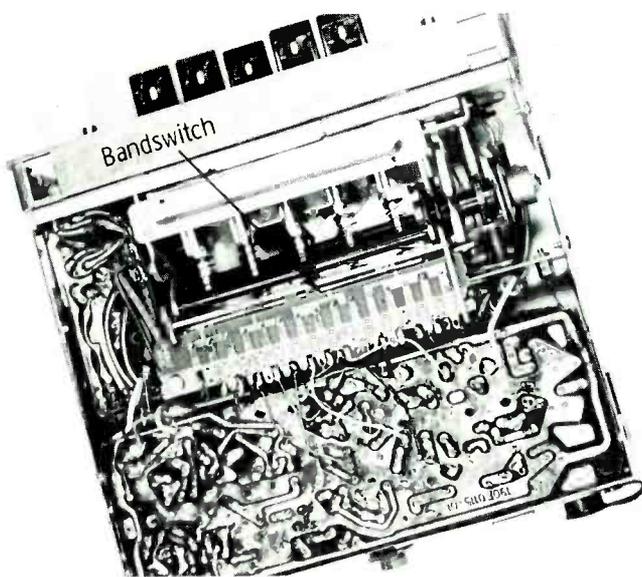


Fig. 6 Bottom view of the Becker Europa AM/FM receiver showing the bandswitch and the main printed-circuit board.

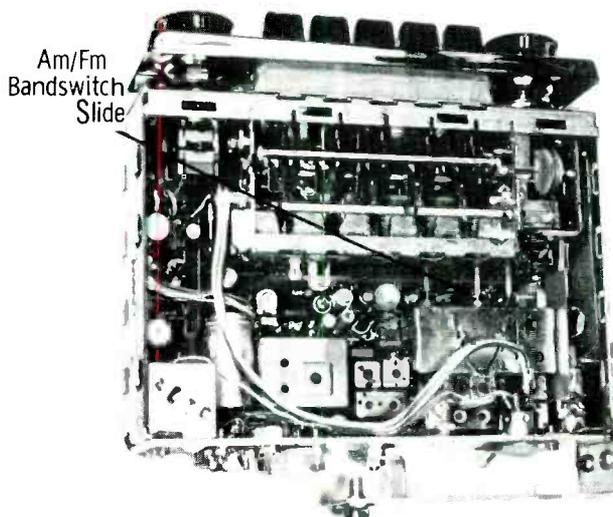


Fig. 7 The AM/FM bandswitch of the Blaupunkt '3670 series Frankfurt receivers has been the chief cause of "dead" or intermittent-operation complaints.

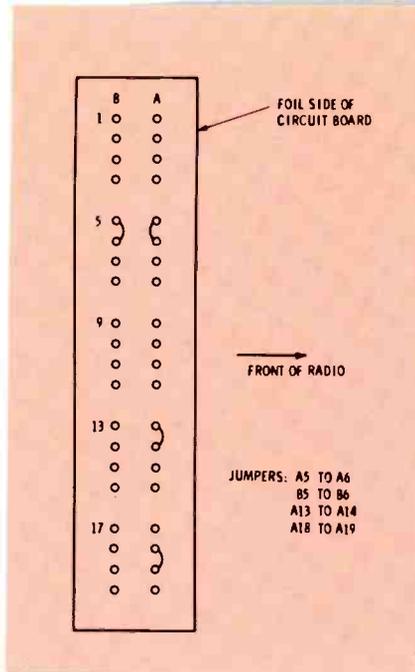


Fig. 8 Illustrated here is the factory-recommended modification of the band-switch board of Blaupunkt Frankfurt receivers.

check out the voltage regulator (there are cures for THAT too . . . no warranty unless the customer provides a bill from a VW dealer showing that the regulator has been checked and is okay).

In most American car FM radios, the tuner is equipped with separate oscillator and mixer transistors. Most German designs, however, use a single converter transistor in the FM front end. This probably is the reason why most German-built auto radios have lower sensitivity than American radios.

A typical German FM converter stage is shown in Fig. 3. This particular circuit is from a Becker Europa MU. ("Europa" is the model, and "MU" indicates that it is an AM/FM set). The actual circuit is not too unusual except that it isn't used extensively in this country. It is basically a common-base Colpitts oscillator with the signal from the RF amplifier injected at the emitter terminal.

Two typical German FM tuner subassemblies are shown in Fig. 4 and 5. The tiny tuner in Fig. 4 is from a Blaupunkt model '3670 "Frankfurt (U.S.)". The transistors on the circuit board give an indication of the small size of this tuner. They are not TO-5 types but instead are the much smaller TO-18 types. Note that the oscillator coil in the center is shielded

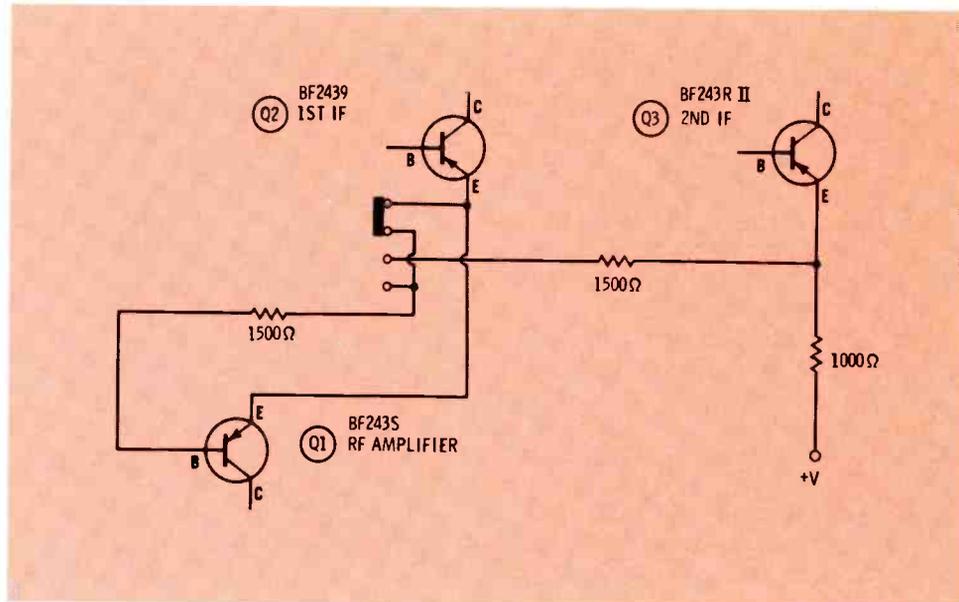


Fig. 9 The bias and AGC voltage for the RF amplifier stage of the Blaupunkt Frankfurt receiver is developed in the emitter circuits of the 1st and 2nd AM IF amplifiers. See text for related trouble.

from the other circuits.

The slightly larger tuner in Fig. 5 is from a Blaupunkt "Emden III", an overseas delivery model. One reason for the larger size of this tuner is that the 1st FM IF transformer is mounted on the same printed-circuit board.

The same types of trouble which occur in domestic auto radios also occur in German car radios. Common defects include defective RF amplifier and converter transistors and AFC diodes. As is also true of American radios, resistors and capacitors are not particularly common sources of trouble. There seems to be fewer defective solder joints in most German models. This does not mean that there is no chance of finding a workmanship defect in a German car radio. They have their quality-control problems, too.

One of the biggest problems in German car radios is the bandswitches. With all of those bands, the Germans frequently resort to some complex switching circuits. The bandswitch in the Becker Europa MU (stereo) is shown in Fig. 6. The part showing in the photograph is only one section of the total bandswitch mechanism. It is a good idea to clean the bandswitch on every German radio which is brought in for service.

The '3670 series of Frankfurt

(U.S.) sets by Blaupunkt are installed by many VW dealers. Historically, these radios have exhibited a problem with the AM/FM switch. A common complaint is that the radio is either dead or intermittent on AM but operates normally on FM. A too-quick reading of these symptoms might lead you to believe that the auto antenna is open intermittently when it actually isn't. The stator element of the AM/FM bandswitch is a printed-circuit board rather than a manual assembly.

When this complaint is encountered, set the radio to AM and gently rock from side to side the moving slide on the bandswitch. (The location of this slide is shown in Fig. 7. It is directly behind the Permeability Tuning Mechanism (PTM) and in front of the FM tuner housing.) If this causes the radio to operate, even momentarily, it will be necessary to clean the switch and perform the following Blaupunkt-recommended circuit modification: As illustrated in Fig. 8, cause solder to flow across terminals A5 to A6, B5 to B6, A13 to A14, and A18 to A19. The view in Fig. 8 is from the printed side of the board.

European designers have used some unusual AGC and bias circuits in their car radios. A typical arrangement is the Blaupunkt Frankfurt circuit shown in Fig. 9. Notice that the bias and AGC for

NOW you can measure resistors accurately **IN CIRCUIT!** in solid state devices



FE20 HI-LO
with hi-voltage probe and large
six-inch meter
\$129.50




FE21 HI-LO
with 4 1/2-inch
meter **\$99.50**

WITH THE NEW HI-LO FIELD EFFECT MULTIMETERS


USES ONLY .08 VOLTS TO POWER OHMMETER TO PREVENT TRANSISTORS FROM CONDUCTING AND UPSETTING READINGS

Look at these extra features to see why the Hi-Lo meter belongs on your want list:

- Unbelievable specifications of 15 megohm input impedance on DC and 12 megohms on AC
- Laboratory accuracy of 1.5 percent on DC and 3 percent on AC
- 9 DC voltage ranges from as low as .1 volts full scale to 1000 volts
- 3 hi-voltage ranges of 3 KV, 10 KV and 30 KV
- 9 DC zero center ranges from .05 volts to 500 volts . . . a must for delicate transistor bias measurements
- 7 resistance ranges from 1000 ohms full scale to 1000 megohms
- 9 DC current ranges from 100 microamps to 1 amp
- Automatic built-in battery test . . . never a worry about rundown batteries, just push the switches under the meter and read.
- Standard .6 amp fuse to protect the ohms and milliamps scales if voltage or overload is accidentally applied. No more need to return the meter to factory for repair . . . just replace the fuse.
- Special probe with 100K isolation resistor in probe to prevent AC pickup or to prevent loading oscillator circuits. Leave in normal position for most tests.

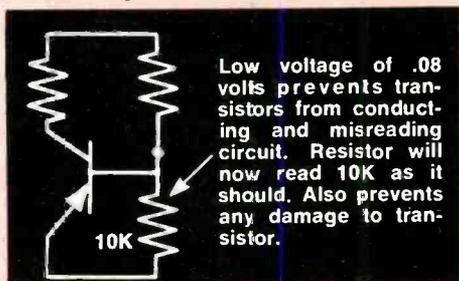

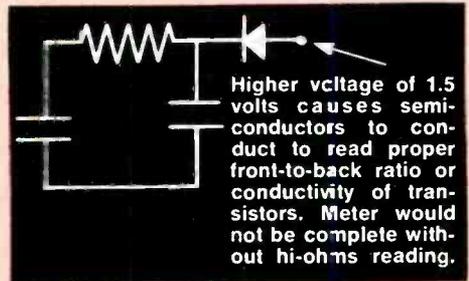Here is why you should have both Hi and Lo battery voltages for correct in-circuit resistance measurements in solid state circuits:



SENCORE INC. 3200 Sencore Drive • Sioux Falls, South Dakota 57107

Circle 18 on literature card

the RF amplifier is developed by the emitter circuits of the 1st and 2nd AM IF amplifiers. (Multiple AM IF amplifiers are common in European sets.)

Excessive leakage current in Q3 in Fig. 9 can cut off the RF amplifier, Q1. The hiss produced in such a case sounds like that produced by a bad RF amplifier transistor. Consequently, when the RF amplifier in these radios is cut off, check the IF amplifiers.

Because a lot of relatively well-to-do folks drive new Mercedes-Benz automobiles, it seems only natural for the Mercedes-Benz radio supplier, Becker, to offer an AM/FM/stereo FM car radio. Becker chose the Motorola integrated-circuit stereo decoder as the means for converting the Europa series radios to stereos. It was something of a surprise to lift the Becker stereo printed-circuit board and find a Motorola MC1304. (In some cases, this chip can be purchased through Motorola Semiconductor Products distributors for less than its available for through Becker, MAPI, Delco, etc.)

The Becker people have added a composite preamplifier (Fig. 10) of their own in the MC1304 external circuitry. A photo of the actual board is shown in Fig. 11. Although it might appear to be a bit difficult to troubleshoot, it really is relatively simple. Becker has mounted the printed-circuit board on hinges so that it can be swung up into the vertical position. The leads attached to the board are long enough to permit this.

All but the least expensive German AM manual car radios use externally-mounted transistors which have a size and shape much like our TO-66 package transistors. An example of these, shown mounted on a Blaupunkt Emden III, can be seen in Fig. 12. These transistors are located behind the radio mounting bezel. In other models they are found on the rear chassis panel.

Some models of the units produced by both major German companies use an external audio power-amplifier chassis. This package will mount either to the firewall of the car or can be sus-

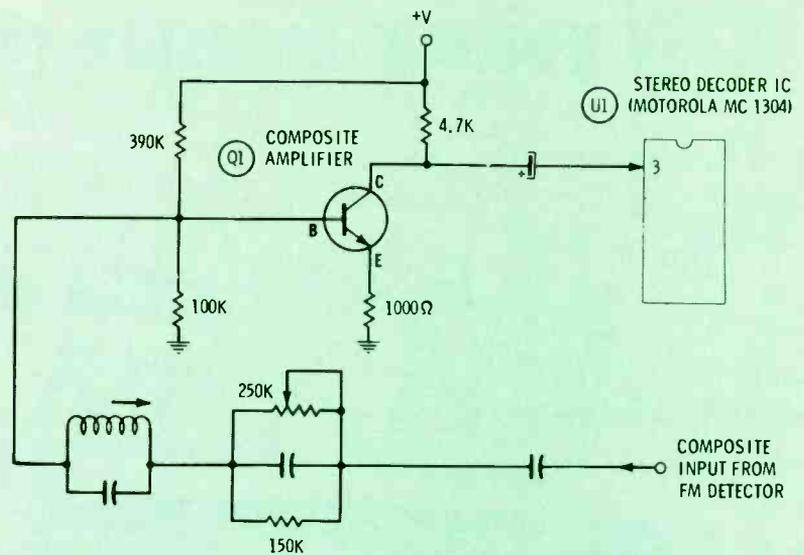


Fig. 10 The Becker Europa series of auto radios have been converted to stereo by use of a Motorola integrated-circuit stereo decoder. Becker has added to the external circuitry of the IC decoder their own composite preamplifier, the circuitry of which is shown here. See text for details.

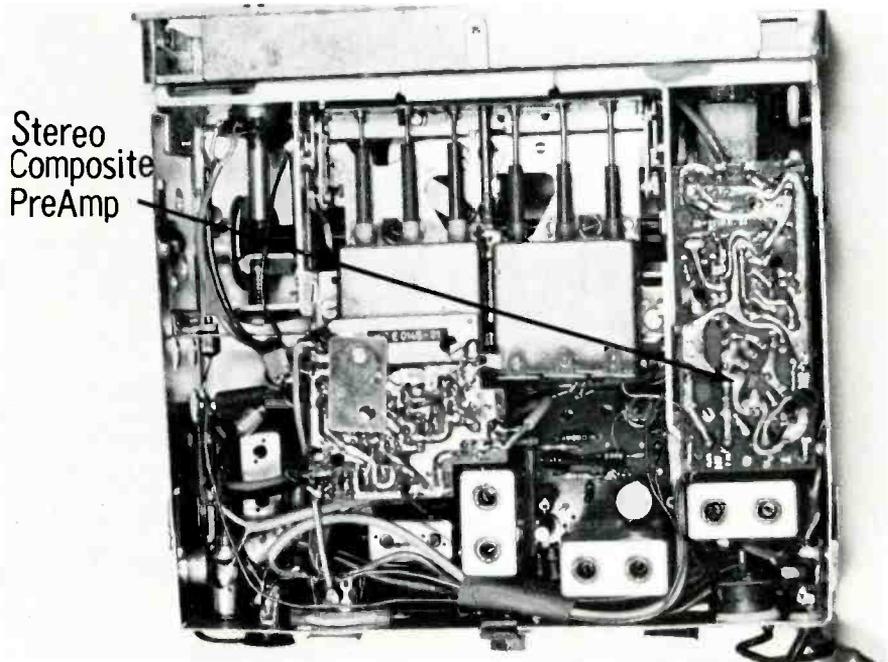



Fig. 11 Bottom view of Becker Europa auto radio with stereo composite amplifier printed-circuit board pointed out.

ended on stiff brackets beneath the radio.

In certain of the now obsolete hybrid designs, it was common to find an outboard package containing a solid-state, push-pull audio amplifier and a solid-state, DC-to-DC high-voltage converter. These tube-type sets can be identified by the three type TF

80/30 power transistors along one side of the outboard package. Push-pull audio stages are a rarely violated rule in German designs. In American sets, however, they are the exception.

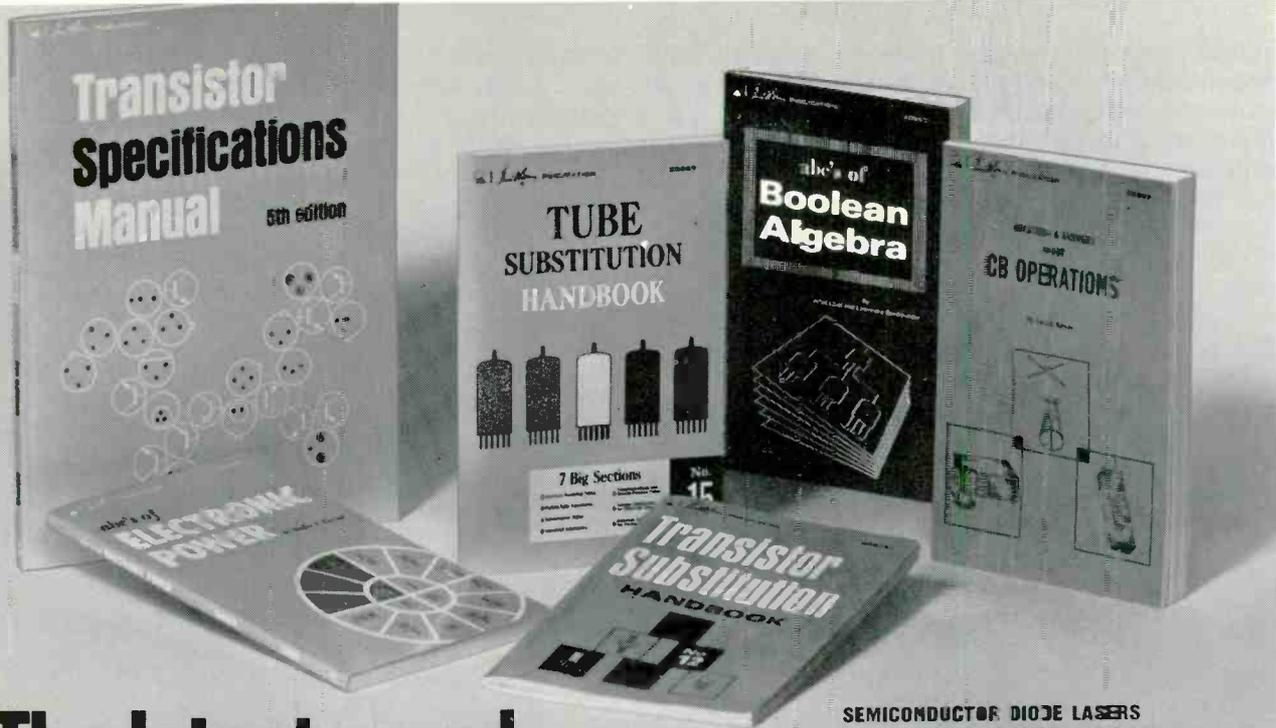Try to use only original replacements for these transistors. The problems encountered in trying to use American TO-3 or



The latest word on Electronics!

Sams presents 9 brand new or completely revised books...invaluable working aids for anyone in electronics.

TRANSISTOR SPECIFICATIONS MANUAL 5th Edition

by the Howard W. Sams Engineering Staff
160 fact-packed pages of electrical and physical data for nearly 10,000 transistor types. Lists electrical and physical parameters, essential facts for servicing, and manufacturers of each type. All EIA-registered TO outlines are shown and dimensioned drawings are provided for nonstandard cases.
No. 20883 \$4.50

ABC's OF ELECTRONIC POWER

by Rufus P. Turner
A clear explanation of electronic power and how to measure it, each point clearly illustrated by worked-out examples. No step in the mathematical solution is omitted. Covers: fundamentals, dc power measurement, ac power measurement, rf power measurement.
No. 20884 \$3.50

TUBE SUBSTITUTION HANDBOOK 15th Edition

by the Howard W. Sams Engineering Staff
The most complete, up-to-date direct tube substitution guide you can use. Includes over 12,000 substitutions for receiving and picture tubes. Easy to use. Sections cover: cross reference of all American receiving tubes, picture tubes and recommended substitutions, cross reference of subminiature tubes, industrial substitutions for receiving tubes, communications and special-purpose tube substitutions, cross reference of American and foreign tubes.
No. 20889 \$1.75

TRANSISTOR SUBSTITUTION HANDBOOK 12th Edition

by the Howard W. Sams Engineering Staff
Here is the answer if you can't get an exact replacement for a failed transistor. Using computers, the Sams Engineering Staff made over a billion comparisons of electrical and physical parameters of all transistors. The over 100,000 substitutions that can be safely and satisfactorily made are listed here in easy-to-find order.
No. 20899 \$2.25

ABC's OF BOOLEAN ALGEBRA 3rd Edition

by Allan Lytel and Lawrence Buckmaster
A knowledge of Boolean algebra, the algebra of logic, is essential for anyone wishing to understand the logical functions of computer circuitry. This text introduces and explains symbolic logic and shows, with simple block diagrams and examples, the relation between language and switches, and the principles of logical design. It shows how to write logical expressions, expand and simplify them, and how to use relays and switches in circuits.
No. 20867 \$3.50

QUESTIONS AND ANSWERS ABOUT CB OPERATION 2nd Edition

by Leo G. Sands
A quick and handy reference source of information about CB radio; its classes and uses, licensing and FCC rules, operating procedures, selection of CB equipment, and installation of transceivers and antennas in mobile and fixed-station locations. As valuable for anyone who works with CB radio as it is for electronics engineers and technicians.
No. 20893 \$2.95

SEMICONDUCTOR DIODE LASERS


by Ralph W. Campbell & Forest M. Mims
This introduction to the rapidly expanding use of the injection laser shows how the science progressed from ruby rods to its present compact, highly efficient, and economical form of the semiconductor diode laser. It gives information on construction methods, circuits, conventional and infrared photographs, power requirements, power output, practical uses, and future possibilities.
No. 20887 \$5.95 (tentative)

SOLID STATE SERVICING

by William Sloop
Easy-to-understand, practical service information to aid the service technician in repairing any solid state electronic equipment used in black and white TV, color TV, and radio circuitry. Includes troubleshooting hints and procedures.
No. 20888 \$4.95 (tentative)

RADIO AMATEUR OPERATING HANDBOOK

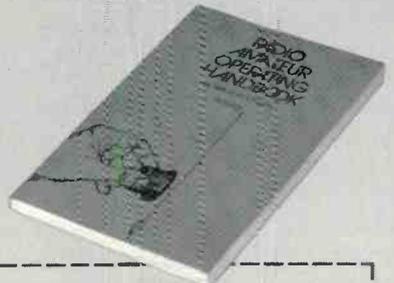by Marshall Lincoln, W7DQS
While it is not a technical book on electronics, this book is a practical single-source working guide for hams. It covers all facets of on-the-air operating activities as well as the building, testing, and modifying of equipment. It is particularly intended to improve the ham's operating methods and techniques in radio communication.
No. 24028 \$4.95



HOWARD W. SAMS & CO., INC.

ES 042

- | | |
|--------------------------------|--------------------------------|
| <input type="checkbox"/> 20883 | <input type="checkbox"/> 20893 |
| <input type="checkbox"/> 20884 | <input type="checkbox"/> 20887 |
| <input type="checkbox"/> 20889 | <input type="checkbox"/> 20888 |
| <input type="checkbox"/> 20899 | <input type="checkbox"/> 24028 |
| <input type="checkbox"/> 20967 | |

Order from your Electronics Parts Distributor, or mail to Howard W. Sams & Co., Inc., 4300 West 62nd Street, Indianapolis, Indiana 46268.

Send books checked at right, \$_____ enclosed. Please include sales tax where applicable. Canadian prices slightly higher.

Send Free 1972 Sams Book Catalog.

Name _____

Address _____

City _____

State _____

Zip _____

TO-36 transistors in the limited space offered in the typical German car radio make them impractical. Some of the universal replacement guides optimistically offer one of their numbers that are electrically identical. The identity, however, is electrical only.

If you encounter one of the older tube-type classic Becker "Mexico" models, you probably will find a significant lack of sensitivity. This might be caused by a faulty "antenna" section of the bandswitch (see Fig. 13). This switch is not located on the master bandswitch assembly but instead is a small, leaf-spring-powered unit located close to the antenna input jack. It is operated by a long bar connected to the master switch slide.

If cleaning and retensioning of the leaf spring do not cure the problem, it might be necessary to order a new switch from Becker. (Addresses for both Becker and Blaupunkt can be found in the latest edition of your Sams Annual PHOTOFACT Index and in the Source Guide to Imported Sets published annually in the November issue of ES.) The usual reason these switches fail is a loss of tension in the spring. When this occurs, you can see daylight through the point where the contacts are supposed to come together. If you have a supply of surplus Delco Wonder Bar parts, try using the spring from either the Wonder Bar start switch or the solenoid recocking switch. I have found from experience that many of the springs from older Delco switches will fit perfectly into the space occupied by the spring in the Becker antenna switch.

German composite AM and FM IF amplifiers at first examination might appear complex and difficult to service. A typical Blaupunkt circuit is shown in Fig. 14. It is the coupling between two IF stages. Although it is the reason for the excellent selectivity figures for which these radios have a justified reputation, it can be somewhat difficult to troubleshoot. One problem is the extreme small size of those coils. (I once heard an electronics in-

structor say that solid state is fine but do not expect too high a degree of set miniaturization. His pre-1960 reason was that no one could find a way to miniaturize the henry and the watt. The Germans and the Japanese have obviously never got the message because they have succeeded in miniaturizing the henry, and,

judging from recent Hi-Fi advertising, the watt is on it's way down.)

Although not yet typical, the audio stage shown in Fig. 15 offers evidence that the Germans soon might be making extensive use of integrated circuitry. It is the preamplifier stage from one channel in the Becker Europa

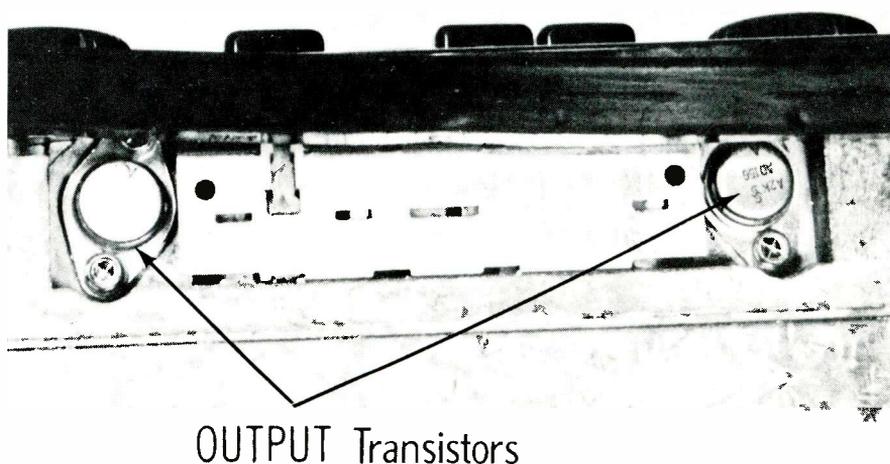


Fig. 12 Bottom view of Blaupunkt Emden III showing externally-mounted output transistors, a feature of all but the least expensive German AM manual auto radios.

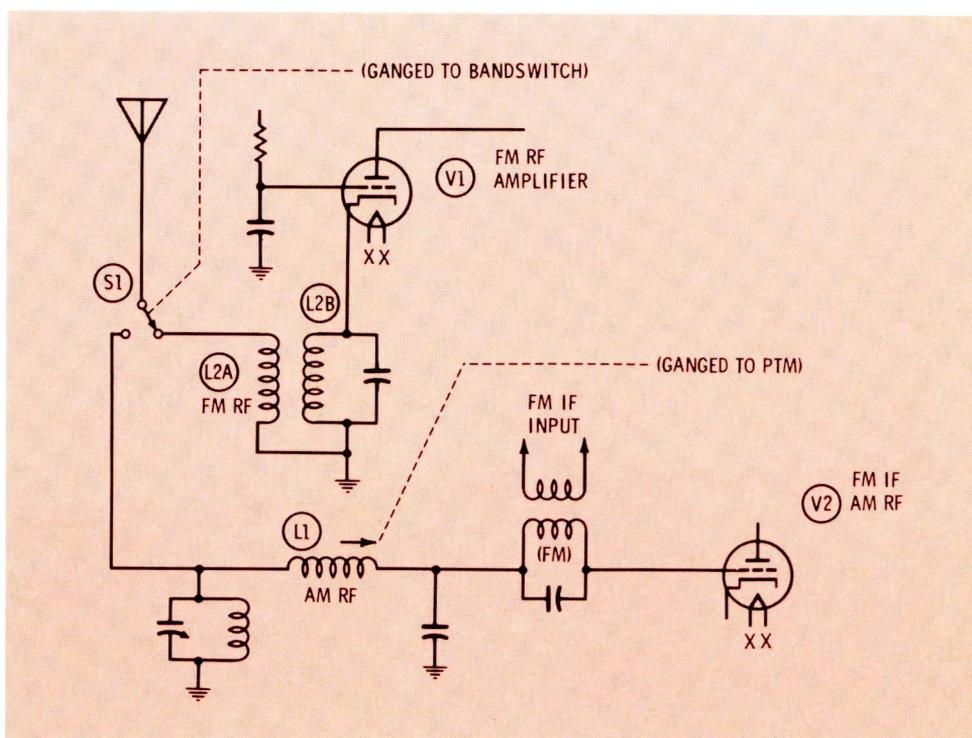


Fig. 13 Leaf-spring-powered antenna switch, shown here, which is ganged to the bandswitch, is one source of reduced sensitivity in the older, tube-type Becker "Mexico" model receivers.

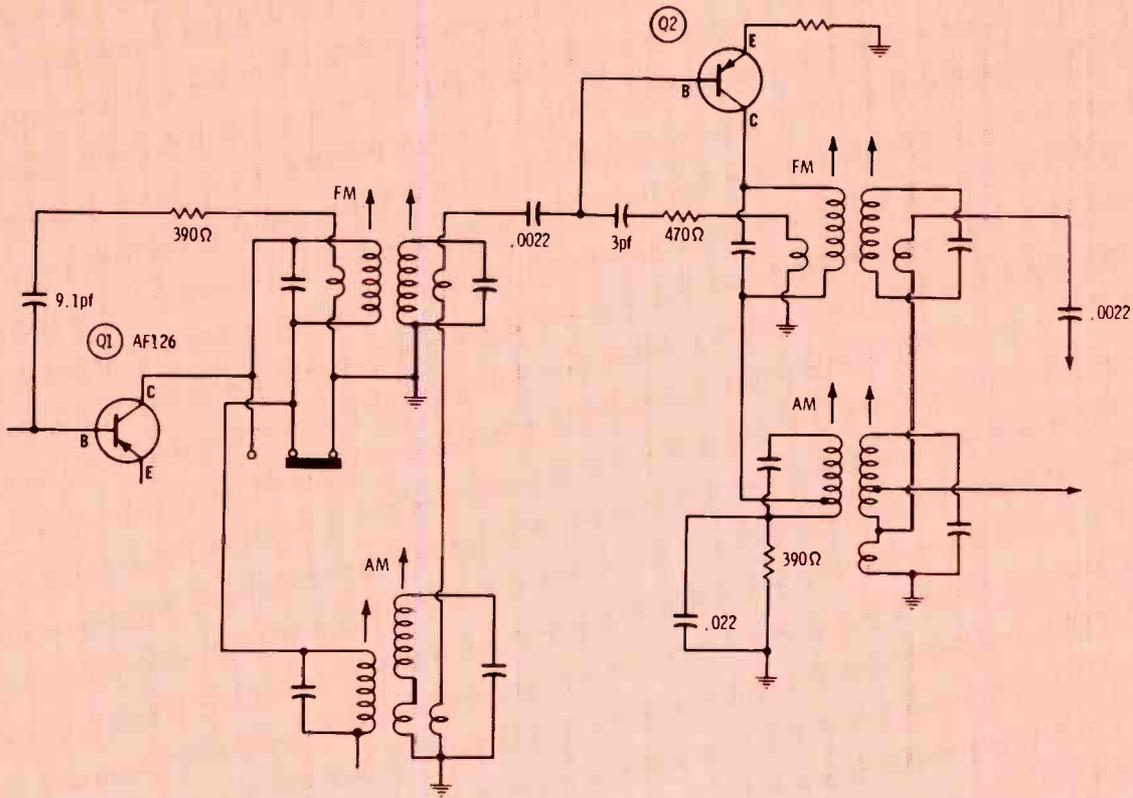


Fig. 14 Complex coupling between two IF stages of a composite AM/FM IF amplifier, shown here, is a typical Blaupunkt design.

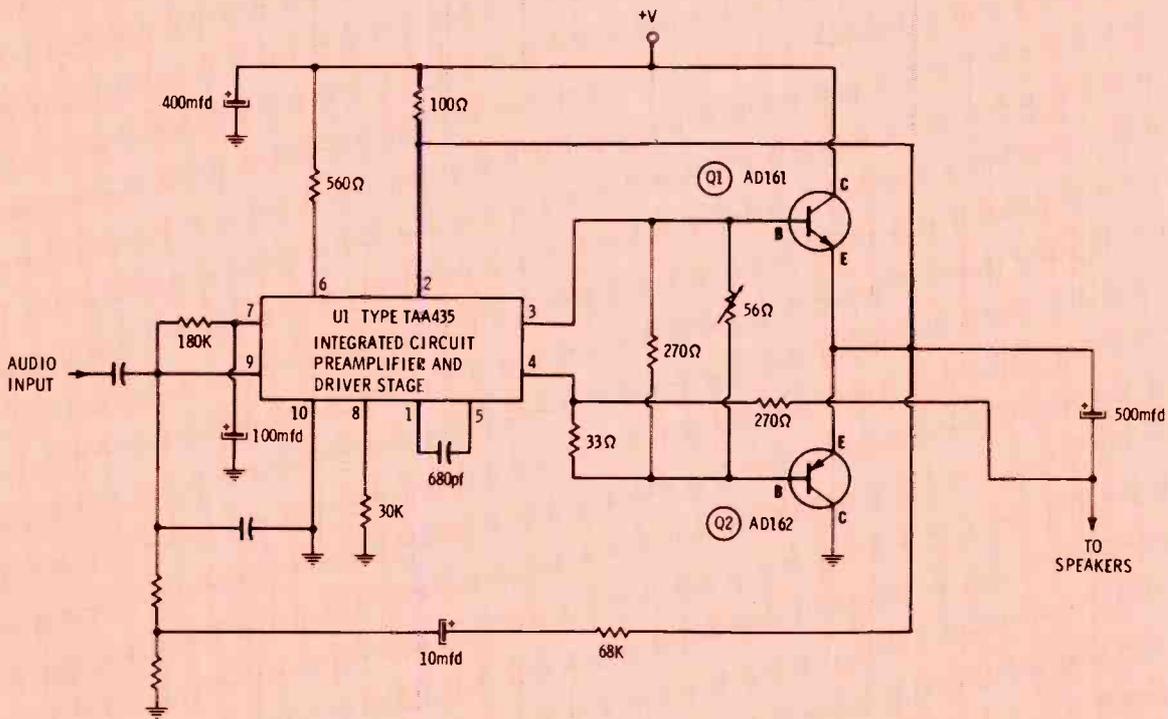


Fig. 15 Use of IC's by German auto-radio manufacturers is evidenced by the IC-equipped audio preamplifier and driver section of the Becker Europa MU stereo auto radio.

WORKMAN
Subsidiary of IPM TECHNOLOGY INC.
BOX 3828 SARASOTA, FLA. 33578

Electronic
PRODUCTS, INC.

OEM and REPLACEMENT
MANUFACTURERS OF

**FAIL
SAFE**
IN
MOLDED
BLACK
PHENOLIC
CASE

**CIRCUIT
BREAKERS**

14 Models
FA1 to FA7
& FAD Dual
BREAKER



FREE BUTTON EXTENSION
IN PACKAGE

FREE VEST POCKET
CROSS REFERENCE

ASK FOR BOOKLET # X53

RECOGNIZED UNDER THE
COMPONENT PROGRAM OF
UNDERWRITERS' LABORATORIES, INC.

Circle 20 on literature card

**MERCURY
TUNER
SERVICE** offers a
new money- and time-
saving approach to tuner
repair . . .

- All major parts replaced AT COST!
- 1N82 UHF diode replaced AT NO COST!
- Return POSTAGE PAID!
- Extra-fast service!

All tuners completely overhauled and aligned to manufacturers' specifications . . . then "air checked" on Mercury's VISION-VIEW MONITOR.

VHF . . . only \$9.50

UHF . . . only \$8.50

VHF/UHF . . . only \$14.50

Save an additional \$1.00

by sending this ad with tuner NOW!

B-WorCOLOR

Tube or

Transistor

**MERCURY
TUNER
SERVICE**

DEPT. "C", 49 McClellan St.
Bronx, N.Y. 10452,
Phone (212) 293-9060

Circle 21 on literature card

MU stereo receiver. The type TAA435 IC takes the place of the several preamplifier and driver components needed to make a decent complementary-symmetry audio amplifier stage.

The output transistors in Fig. 15 are more difficult to find than the replacement catalogs indicate. The type AD162 is available while the AD161 is somewhat harder to find. Many of the universal replacement catalogs list a silicon NPN unit for the AD161 replacement. Although the silicon might operate satisfactorily in a single-ended stage, it can cause distortion in the complementary configuration unless a silicon replacement for the PNP transistor can also be located.

These transistors can be ordered under original type number from several sources. First, try the manufacturers of the radio being repaired. Both Becker and Blaupunkt use this pair. Also, try a distributor that handles parts for the O.E.M. Chrysler radios made by Philips, Ltd., of Canada. The 1969-1970 model Philips radios used the AD161 and AD162 transistors.

Give It Some Consideration

Well, there you have a brief look at German car radio servicing.

If there is stiff competition among auto radio shops in your area, you can get an edge over the others by offering import dealers total service. If you can handle O.E.M. Bendix and MAPI (Motorola) warranties as well as the next guy, what is the difference to the local VW dealer? If, on the other hand, you are the only guy that can also handle his Becker and Blaupunkt work, he will probably shoot all of his business your way.

Warranty and retail repairs to the German brands give you a better shot at VW, Porsche, Mercedes-Benz, Volvo, Saab, and Audi dealers. Keep life simple for the parts managers of the auto dealers and they will reciprocate by giving you a lot of business. □

test equipment report


Features and/or specifications listed are obtained from manufacturers' reports. For more information about any product listed, circle the associated number on the reader service card in this issue.

Transistor Curve Tracer

Product: Model 101 curve tracer
Manufacturer: Testline Instruments

Function and/or Application: Checks transistors in- and out-of-circuit.

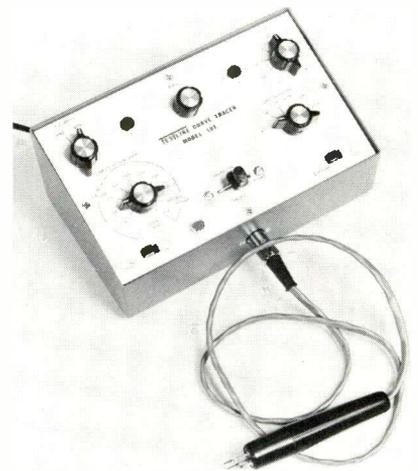Features: Plugs into any conventional oscilloscope for displaying curves. Two styles of probes for in-circuit checking of transistors of any configuration. In-circuit checking of high-voltage, focus rectifiers and FET's can be made. Two transistor sockets for testing and matching transistors out-of-circuit. NPN or PNP displays, in- or out-of-circuit; germanium or



silicon transistors checked; FET or bi-polar transistors checked. FET curves displayed for enhancement or depletion mode. Zener diode displays from a few microamps to 100 mA.

Specifications: Base current: 1 μ A per step to 1000 μ A per step in nine ranges. Gate voltage: 250 mV per step to 1000 mV per step in three discrete ranges. Collector voltage: 0 to 80 V; 0 to 100 mA, dependent on dissipation resistors. Load resistance: 470 ohms to 47K ohms. Power re-

quirements: 115 VAC; 60 cycle, 1/2 amp.

Price: Model 101 sells for \$150.00.

Circle 50 on literature card

CRT Auto Tracker

Product: CR161 auto-tracker

Manufacturer: Sencore, Inc.

Function and/or Application: Automatic checking of color CRT gun tracking.

Features: Computer memory circuits store CRT information during emission checks, color guns are automatically compared to each other for a 1:5 to 1



ratio by pushing a Automatic Tracking button. Results can be read as "Good" or "Bad." The CR161 tests the standard three-gun color CRT as well as the "single-gun" Trinitron and black and white. Filament voltage setting, gun balance setting, shorts test, shorts removal, emission check, and three rejuvenation positions are covered with a single switch. The CR161 is housed in a brushed steel and vinyl-clad carrying case with setup book included.

Specifications: N/A

Price: The CR161 sells for \$140.00.

Circle 51 on literature card

Dual-Trace Triggered-Sweep Scope

Product: Model IO-105 dual trace triggered-sweep DC-15 MHz oscilloscope

Manufacturer: Heath Co.

Function and/or Application: The IO-105 provides dual-trace, triggered-sweep display

Features: Switch selected AC or DC coupling permits triggering at a given point or at a pre-

(Continued on page 36)

HOPPING ALL OVER TOWN FOR REPLACEMENT PARTS . . .


Just hop to

STANCOR...

for all your **exact** monochrome and color TV replacement needs.

Stancor Products offer a complete line of flybacks, yokes, vertical outputs, audio outputs, power width and larity controls for all major manufacturers.

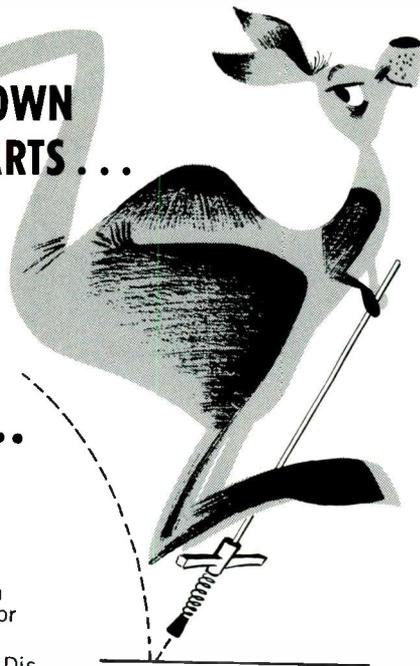Stocked by over 1,000 Service Part Distributors. Back up stock—Chicago, Dallas, Los Angeles, Hackensack and Atlanta.



ESSEX INTERNATIONAL, INC.

ESSEX CONTROLS DIVISION • STANCOR PRODUCTS • 3501 W. ADDISON ST. • CHICAGO, ILL. 60618

Circle 22 on literature card

Quick-Servicing Info About COLOR TV, B-W TV, and STEREO

TV TECH AID

Takes you right to the source of the trouble without guess work and wasted time. In each monthly issue you receive over

40 actual causes and cures of color and B&W TV trouble symptoms. You also receive timely and complete information about circuit modifications and other valuable service data.

- Place your 1972 subscription now. All new. 12 Issues \$7.95
- Get these valuable back issues while they last **At Reduced Rates**



SEND YOUR CHECK OR MONEY ORDER TO:

TV TECH AID

P. O. Box 603
Kings Park
N.Y. 11754

- 1969-12 Issues \$4.95
- 1970-Book Form \$5.95
- 1971 B&W Book \$5.95
- 1971 12 Issues \$7.95
- 1972 All New 12 Issues \$7.95

Name.....
 Address.....
 City.....
 State.....Zip.....

Circle 23 on literature card


ARROW AUTOMATIC STAPLE GUNS

CUT WIRE & CABLE INSTALLATION COSTS

... without cutting into insulation!

SAFE! Grooved Guide positions wire for proper staple envelopment! Grooved Driving Blade stops staple at right depth of penetration to prevent cutting into wire or cable insulation!

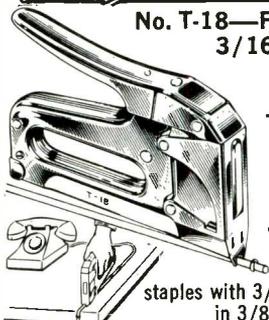
No. T-18—Fits wires up to 3/16" in diameter.



BELL, TELEPHONE, THERMOSTAT, INTERCOM, BURGLAR ALARM and other low voltage wiring.

Uses T-18 staples with 3/16" round crown in 3/8" leg length only.

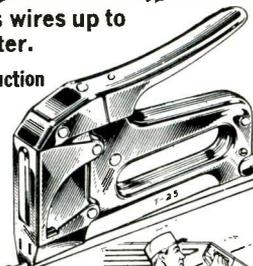No. T-25—Fits wires up to 1/4" in diameter.




Same basic construction and fastens same wires as No. T-18.

Also used for **RADIANT HEAT WIRE**

Uses T-25 staples with 1/4" round crown in 9/32", 3/8", 7/16" and 9/16" leg lengths.

T-18 and T-25 staples also available in Monel and with beige, brown and ivory finish at extra cost.

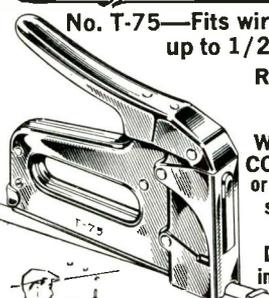No. T-75—Fits wires and cables up to 1/2" in diameter.



RADIANT HEAT CABLE, UF CABLE, WIRE CONDUIT COPPER TUBING or any non-metallic sheathed cable.

Also used as **DRIVE RINGS** in stringing wires.

Uses T-75 staples with 1/2" flat crown in 9/16", 5/8" and 7/8" leg lengths.

Arrow Automatic Staple Guns save 70% in time and effort on every type of wire or cable fastening job. Arrow staples are specially designed with divergent-pointed legs for easier driving and rosin-coated for greater holding power! All-steel construction and high-carbon hardened steel working parts are your assurance of maximum long-life service and trouble-free performance.

Ask your Electrical Supply Dealer or write for further details.

ARROW FASTENER COMPANY INC
Saddle Brook, New Jersey 07663
"Pioneers and Pacesetters
For Almost A Half Century"

Circle 24 on literature card

(Continued from page 35)

lected DC level; positive and negative slope triggering is also switch selectable. Other features: rear panel sweep gate output delivers a 3.5 volt pulse in sync with sweep for special applications; TTL-compatible external blanking input; 8 x 10 cm rectangular flat-face CRT with standard camera mount on bezel; removable side panels for accessibility; 15-inch depth.



Specifications: X-Y capability permits each input to be displayed as a function of the other; Channel 1 controls the Y axis and Channel 2 controls the X axis. Both inputs are balanced for less than 5 per cent phase shift to 50 KHz. An 18-position time base switch in a 1, 2, 5 sequence gives sweep rates from 100 msec/cm to 0.2 usec/cm. DC-15 MHz bandwidth and 24 nsec rise time permits analysis of high frequency and sharp-front waveforms. Full bandwidth is provided from 20 V/cm to 50 mV/cm.

Price: The IO-105 scope sells for \$399.95

Circle 52 on literature card

Digital Multimeter

Product: Model 3300A 3-1/2 digit multimeter

Manufacturer: Hickok

Function and/or Application: Measures AC and DC voltages

Features: The 3300A can operate for 24 hours from an internal nickel cadmium battery; the battery is good for 1000 recharges minimum. Cyclopedia case and shock-mounted components allow accurate measurements over a wide range of environmental conditions. The 3-1/2 digit display is non-blinking. Automatic

zeroing circuit adjusts for zero before every reading. Decimal point is automatically positioned and polarity is automatically displayed.

Specifications: Ranges are: **5 AC voltage ranges**, from 100 millivolts to 1 kilovolt; maximum resolution is 100 microvolts; accuracy is 0.5 per cent of reading ± 1 digit. Bandwidth for AC measurements is to 100KHz. **5 DC voltage ranges**, from 100 millivolts to 1 kilovolt; maximum resolution is 100 microvolts; accuracy is 0.1 per cent of reading ± 1 digit. **5 AC current ranges**, for 100 microamperes to 1 ampere; maximum resolution is 100 nanoamperes; accuracy is 0.5 per cent of reading ± 1 digit. **5 DC current ranges**, for 100 microamperes to



1 ampere; maximum resolution is 100 nanoamperes; accuracy is 0.2 per cent of reading ± 1 digit. **7 resistance ranges**, for 100 ohms to 100 megohms; maximum resolution is 100 milliohms; accuracy is 0.3 per cent of range ± 1 digit. The 3300A measures 8 inches X 5 7/8 inches X 4 inches, and weights 6 pounds.

Price: Model 3300A sells for \$435.00.

Circle 53 on literature card

Frequency Counter


Product: Model IB-1101 100M-Hz frequency counter

Manufacturer: Heath Co.

Function and/or Application: Frequency measurements from 1 Hz to over 100 MHz.

Features: Input circuit accepts input levels from less than 50 mV

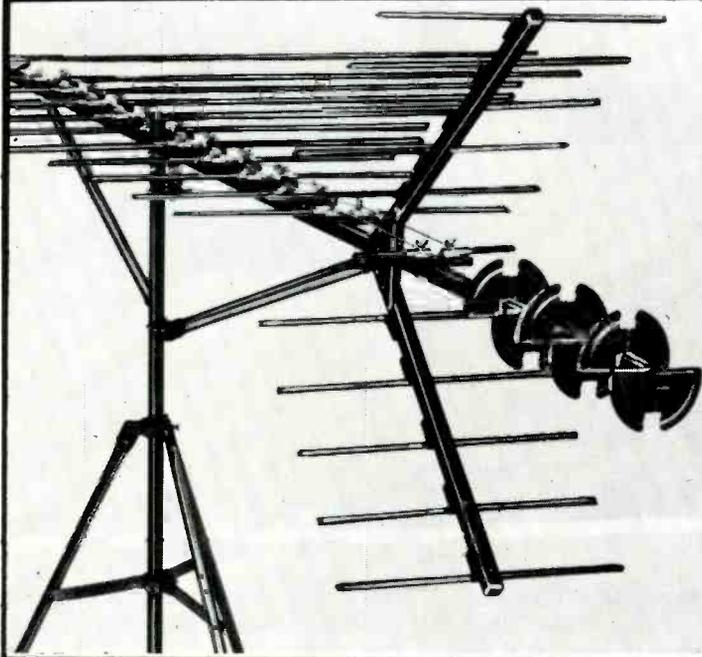RMS "STAR-TRACK"™ Antennas are breaking all sales records!



The most Advanced Space-Age VHF/UHF/FM Color Antennas ever introduced!...

- Similar design to Antennas used in Space Program.
- "Corner Reflector Driven Disc Director Array" for total UHF coverage!
- "Multiple Tuned, Cut-to-Channel VHF Elements" for total VHF-FM coverage!
- Maximum construction features for long dependable life!
- Exclusively features Reynolds Aluminum "COLORWELD" durable baked enamel Gold finish!
- Each Antenna includes famous RMS model SP-332 VHF/UHF Splitter for Single Down-Lead economical installation!
- "STAR-TRACK's" are licensed under U.S. Patent No. 3,440,658.

Write for FREE "Star-Track" Catalog -

RMS ELECTRONICS, INC.

50 Antin Place, Bronx, N.Y. 10462 • Tel. (212) 892-6700

Circle 25 on literature card

to more than 200 V, depending on frequency. Overrange circuitry can expand five-digit readouts to eight-digit capabilities. The decimal point is automatically placed with range selection, while front-panel lights indicate MHz, KHz, overrange and gating. A one megohm input impedance and low input capacitance reduce the chance of circuit over-

Dual-Trace Triggered Oscilloscope

Product: Model 553P 5-inch scope

Manufacturer: Kikusui Electronics Corp.

Function and/or Application: Measurement and waveform monitoring applications

Features: Single gun 5-inch flat faced CRT with helical PDA operating at 3000V. The dual-trace system displays either channel separately, alternates between channels or choppers between channels, all solid-state circuitry.

Specifications: The 553P that

contains a vertical differential DC amplifier that produces a bandwidth of DC to 10MHz, with a voltage accuracy of ± 3 per cent. Model 553P measures $8\frac{1}{8}$ inches X $11\frac{1}{8}$ inches X $18\frac{1}{8}$ inches and weighs 24 pounds.

Price: Model 553P sells for \$538.00.

Circle 55 on literature card

For more information about above products use reader service card




loading. The 26 digital IC's and five color-cathode readout tubes plug into individual sockets. A built-in variable-level signal source permits initial sensitivity setup, a conventional AM radio can be used as time-base oscillator adjustment standard.

Specifications: N/A

Price: The IB-1101 sells for \$269.95.


Circle 54 on literature card

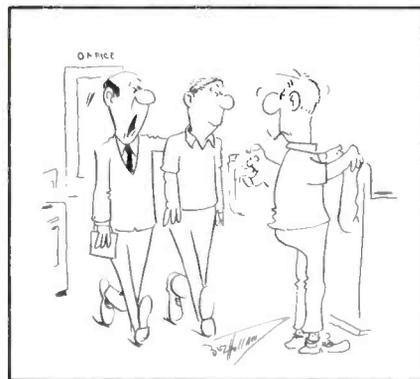

"Pheany, take 5 minutes out and show the new man here all you know about the repair department."

shop talk

With Carl Babcoke
ES Associate Editor

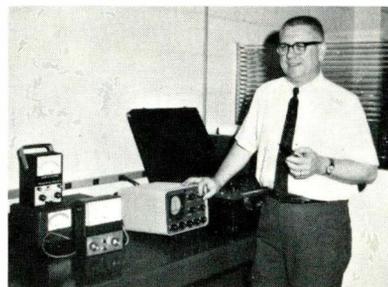

Horizontal sweep and high voltage in color TV, Part 2

Second of a three-part series which analyzes the functions of circuits and individual components, and the symptom and causes of typical defects, and proven techniques for quickly isolating them.

Part 1 of this series described how the horizontal AFC and horizontal oscillator circuits of a typical tube-type color TV receiver, RCA CTC7AA functioned together to produce a signal with the correct phase, frequency, shape and amplitude required to properly drive the horizontal-output stage. Included also were analyses of the function of each component in the horizontal AFC and oscillator circuits and how defects typical of each affect the characteristics of the drive signal.

In this second part of the series, the functions of the horizontal sweep and high-voltage sections will be analyzed, by examining how each component, when operating correctly, contributes to the function(s) of the section or stage in which it is electrically located and, when defective, adversely affects that function.

A complete schematic diagram of the circuitry analyzed is given in Fig. 6.

• **R123 (16K-ohm, 7-watt resistor)**—Reduces the 395-volt supply to the level required by the screen grid of the 6DQ5. An increase of the resistance of R123 reduces the screen voltage, width and high voltage in the same way that leakage in C78 does. (See Line "H" in Table 3.) A reduction of the resistance of R123 increases the screen voltage, width and high voltage, and also increases the 6DQ5 dissipation above the maximum rating, which, in turn, reduces the life of the tube.

• **C78 (.1m-fd capacitor)**—Bypasses the screen grid of the 6DQ5, to prevent degeneration and loss of gain produced by the tube. The value is not very critical; however, a capacitance of less than .01m-fd reduces the width and high voltage. A capacitance of less than .0005m-fd black out the raster and eliminates the high voltage. Not all TV receivers lose their raster when the screen-grid bypass capacitor opens, but most exhibit some loss of width.

Severe leakage of 10K ohms or less across C78 is necessary to significantly reduce the width.

• **6DQ5, the horizontal-output tube**—The symptoms produced by a defective 6DQ5 widely vary according to the exact defect and the extent of the defect. The voltage readings produced by two 6DQ5 tubes which had

different amounts of reduced emission are shown on Lines "B" and "C" in Table 2. Figure 7A shows the slight reduction in width and the compression along the right edge of the picture which were produced by the weak tube the readings of which are given on Line "B" in Table 2.

A 6DQ5 tube which was too weak to produce a raster produced at the damper the waveform shown in Fig. 7B.

A typical cause of repeated burn-outs of the 6DQ5 output tube is shown in Fig. 8. It is a tiny crack around a rivet where the printed circuit for the heater of the oscillator tube is soldered to a lance on the chassis. For a permanent repair, resolder the joint, and also add wires between all of the grounds on the horizontal-oscillator board.

• **T5, the horizontal-output/high-voltage transformer**—An impedance-matching transformer which supplies sweep current to the yoke, and horizontal pulses to the rectifiers and the convergence circuit.

Open or shorted turns in the windings which are connected to the output, damper or rectifier tubes usually eliminate the high voltage (and with it, the raster).

An open in the winding which is connected to the convergence circuits would cause inadequate horizontal dynamic convergence action. Shorted turns in these

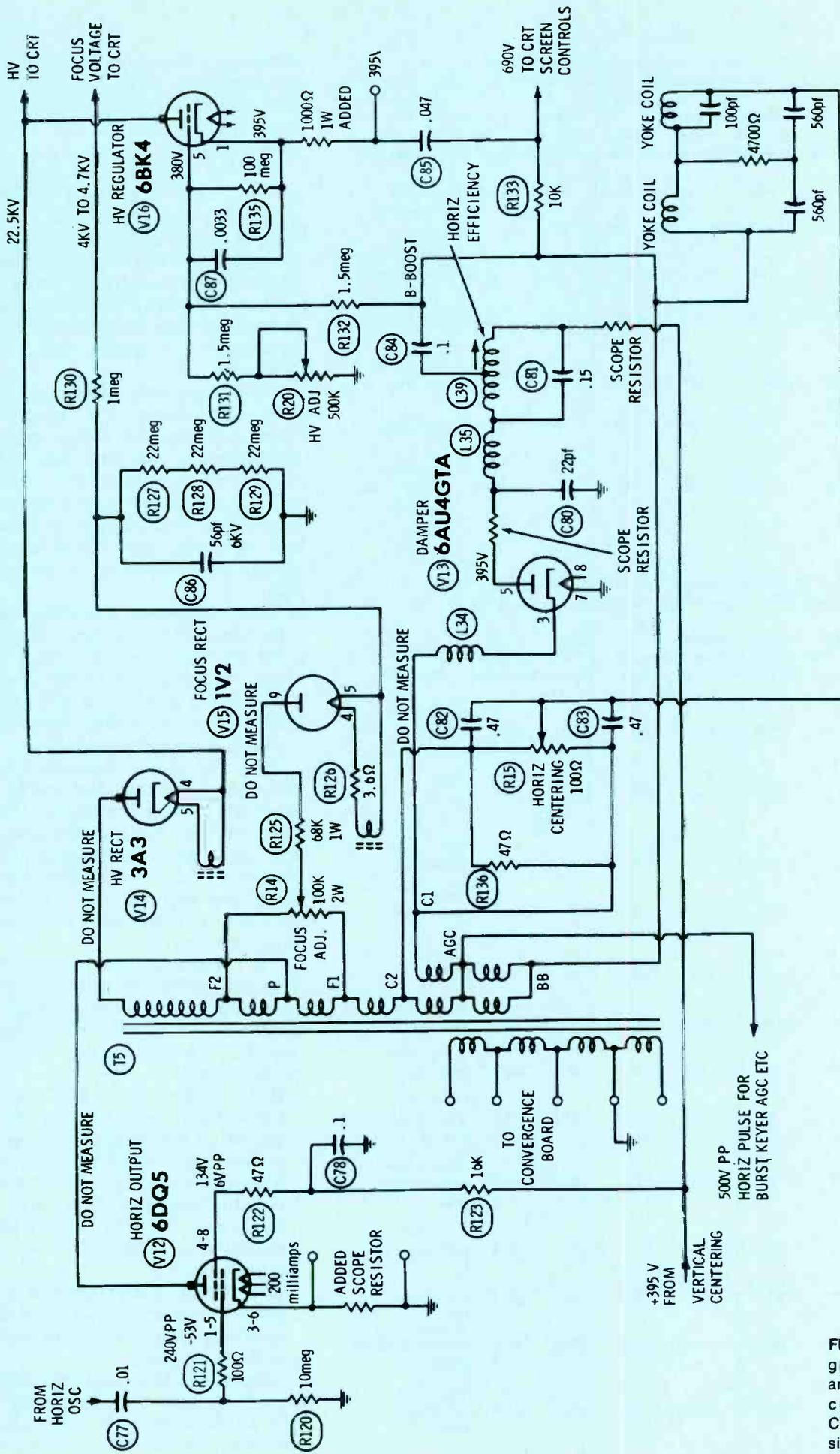


Fig. 6 Schematic diagram of the sweep and high-voltage circuits of the RCA CTC7AA color television chassis.

Table 2
 Voltages And Currents Produced At Key Points By Various
 Degrees Of Failure Of The Horizontal-Output And Damper Tubes

Defect or condition	6DQ5 DC grid voltage	6DQ5 cathode milliamps	6DQ5 screen voltage	B-boost voltage	6BK4 cathode milliamps	High voltage kilovolts	Remarks
(A) Normal	-53	200	134	740	.80	22.5	Normal crosshatch
(B) 6DQ5 slightly weak	-53	160	180	690	.00	20.0	1" narrow each side
(C) 6DQ5 very weak	-53	60	275	510	.00	00.0	No raster—see Fig. 7B
(D) 6AU4 slightly weak	-53	180	145	710	.00	24.0	Stretched on left—
(E) 6AU4 very weak	-53	40	85	350	.00	00.0	No raster—
(F) 6AU4 dead	-53	15	75	00	.00	00.0	No raster—output tube is cooler

Table 3
 Comparison Of Normal Voltages And Currents At Key Test Points
 In CTC7AA Chassis And Those Produced By Typical Defects

Defect or condition	6DQ5 DC grid voltage	6DQ5 cathode milliamps	6DQ5 screen voltage	B-boost voltage	6BK4 cathode milliamps	High voltage kilovolts	Remarks
(A) Normal operation	-53	200	134	740	.80	22.5	normal crosshatch
(B) Normal brightness down	-53	200	134	745	1.20	22.7	black raster
(C) Normal high brightness	-53	200	134	715	.10	21.9	near blooming
(F) Insufficient drive	-44	210	145	740	.60	22.7	Fig. 6 1" narrow each side
(G) R120 open	-56	175	140	730	.50	23.0	little vis-change
(H) Low screen voltage	-53	150	105	740	.10	22.0	½" narrow each side
(I) C81 shorted	-53	215	142	735	.40	22.0	1" narrow on left
(J) Open yoke	-53	70	84	820	.70	6.5	no raster—waveform in Fig. 12
(K) No regulation	-53	200	132	790	.00	25.0	size changed with brightness
(L) C84 boost cap leaking	-53	185	140	690	.00	20.0	1" narrow each side
(M) Horiz out of lock	-48	210	140	745	.90	22.7	out of lock
(N) Osc dead—no drive	0	600+	110	300	.00	00.0	no raster—damper & 6DQ5 bright red
(O) R20 HV control open	-52	215	150	600	1.80	10.0	narrow on left & poor focus

windings (or certain shorts in the convergence wiring) reduce the width and the high voltage; however, such shorts do not eliminate the raster.

Shorted turns in any winding of T5, except those used for convergence, increase the plate current of the 6DQ5 tube, causing it to operate with a glowing red plate. This overload usually quickly destroys the tube. A gassy high-voltage or focus rectifier produces the same red-plate symptom.

Other receivers which employ pincushion-correction circuits have side-pincushion-correction transformers with some windings connected in parallel with those of T5. Shorted turns (or an excessive DC current through the control winding) can cause a red output plate and loss of high voltage.

• **R14 (100K-ohm, 2-watt potentiometer)**—This control adjusts the amount of focus voltage by varying the amplitude of pulses which are applied to the plate of the focus rectifier from the sweep transformer windings.

Many of these controls have developed burned and carbonized resistance elements. This carbonization has shorted across the windings of T5, to which the control is connected, and eliminated the high voltage. This defect also causes the 6DQ5 plate to glow a dull red.

To measure the resistance, remove the control from the circuit. Any reading below 100K is sufficient reason for replacement. A 2-watt-rated control must be used.

• **R125 (68K-ohm, 1-watt resistor)**—This resistor has been added to late-production runs, to limit the current which flows through the focus control during high-voltage arcs. Add a resistor to any CTC7AA-equipped models which do not already have it.

• **C86 (56-pf, 6-KV ceramic capacitor)**—The input (or peak-reading) capacitor for the focus rectifier circuit.

Leakage in this capacitor causes poor focus. A shorted capacitor eliminates both the focus voltage and the raster, although



What happens when male can meets female can?

It's far more than love at first sight... it's a whole new way to use professional chemicals. In terms of convenience. And savings.

Because now, you can take it with you. "It" being the profit-making power of Chemtronics TUN-O-WASH, TUN-O-FOAM and TUN-O-BRITE. **The great "space war"**

With all the tubes and parts a serviceman has to carry, he's often at a loss for space to fit in a large can of chemicals as well. Even knowing he can often make \$5.00 to \$10.00+ more per call.* And when he wants to do an extra-thorough job, de-



gunking with a degreaser before using a cleaner/lubricant, the problem's even worse. Until now.

The world's finest chemicals are now the world's most portable

With a Chemtronics Transfer Kit, you can carry all you need in a shirt-pocket. With the refillable "Slim-Jim" cans in each Transfer Kit (each can, no bigger than the kind you fill a butane lighter from), you can carry a complete tuner service kit in your pocket. And still save money on the "economy-size" cans you re-fill from.

Proof? Ounce-for-ounce, transfer kits can save you up to 25% or more on the world's favorite electronic average prices charged by 100 servicemen surveyed for chemical "tuner tuneup"

AND THE SINGLE CAN

tronic chemicals. And you get two "Slim-Jim" refillable cans that make them a breeze to take along.

It's the kind of idea only a serviceman would think of. It's simple—no special gadgets. Just half a minute, and the "Slim-Jim" is refilled with enough to service six to ten tuners (and the large cans are still in the shop for bench use!).

Why wait? It's at your local distributor's now

"Sex and the Single Can;" more popularly known as the Chemtronics Transfer Kit, comes in three varieties, to meet the needs of knowledgeable technicians:

TCK-1 Double-Degreaser
Two 24 oz. TUN-O-WASH, Two "Slim-Jim" Transfer Cans
TCK-2 Degreaser & Polisher/Lubricant

One each of Bench Size TUN-O-WASH and TUN-O-BRITE, Two "Slim-Jim" Transfer Cans

TCK-3 Degreaser & Cleaner/Lubricant

One each of Bench Size TUN-O-WASH and TUN-O-FOAM, Two "Slim-Jim" Transfer Cans



A PROFIT STORY FOR SERVICEMEN

If you want to make more profits, while you save money, stop by and pick one up today!

CHEMTRONICS INC.
1250 Ralph Avenue
Brooklyn, N.Y. 11236



Circle 26 on literature card

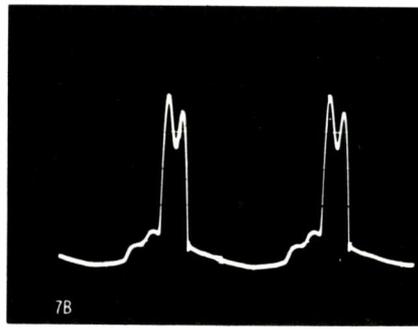
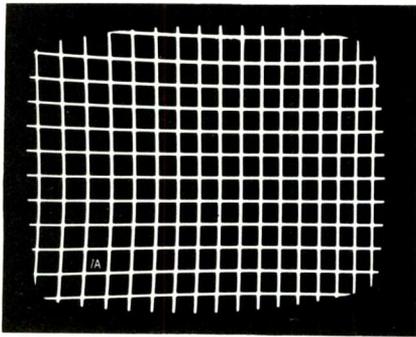


Fig. 7 Crosshatch pattern displayed on the CRT and the yoke waveform produced by two different degrees of weakness of the horizontal-output tube. (A) A moderately weak 6DQ5 narrowed the picture about 1 inch, mostly on the right edge, and slightly reduced the brightness. (B) A 6DQ5 which was too weak to permit high voltage or a raster produced this 900 volt p-p waveform at the cathode of the damper tube.

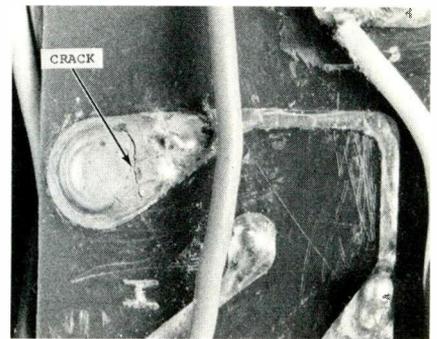


Fig. 8 This intermittently-open ground point of the heater supply to the horizontal oscillator caused the horizontal-output tubes to fail before the defect was found. We suggest that all the grounds on the board be connected together by insulated wire.

the high voltage remains.

If the capacitor opens, the focus voltage will be reduced, and even maximum CW adjustment of the FOCUS control will not produce acceptable focus.

• **R127, R128 and R129 (22M-ohm carbon resistors)**—These resistors stabilize the DC voltage which is applied to the focus electrode of the CRT. Without these resistors as bleeders, the focus electrode would be "floating", and might become too positive because of current flow inside the CRT. Such a possible, but rare, condition would cut off the focus rectifier tube and thereby make the FOCUS control inoperative.

The tolerances of these bleeder resistors are not critical.

• **R130 (1M-ohm, carbon-type resistor)**—Limits the current which might flow back through the focus circuit during arcs inside the CRT. The value is not critical.

• **R15 (100-ohm potentiometer)**—The horizontal-centering control. Centering is accomplished by a small amount of DC which is forced through the horizontal-yoke windings.

A DC voltage is developed across R15 and the paralleled windings of T5 because they are in the path of DC current flow between the damper tube (and the B+ supply) and the plate of the 6DQ5.

When the centering control is adjusted to the electrical center, a bridge circuit—consisting of

the windings of T5 from "AGC" to "C2" and "AGC" to "C1", plus the two halves of R15—is in balance and no DC flows through the yoke coils. At this point, the picture is centered as though there were no centering circuit.

When R15 is turned in one direction away from dead center, a "positive" current flows through the yoke, and the picture is moved to the right. The farther R15 is turned in this direction the more current flows, and the more the picture is moved to the right.

When R15 is turned away from dead-center in the other direction a "negative" current flows through the yoke, moving the picture to the left. The farther R15 is turned in this direction, the more "negative" current flows through the yoke coils, and the farther the picture is moved to the left.

Thus, movement of the picture about one inch either side of dead center is possible.

If the picture cannot be centered properly, R15 probably is open near one end terminal. The control should be removed from the circuit, for an ohmmeter test.

• **C82 and C83 (.47-mfd capacitors)**—These capacitors remove from R15 the AC voltage which would be produced by the sawtooth of yoke current if they were missing. Such an AC voltage drop would quickly burn up R15.

• **L34 and L35, anti-parasitic RF choke**—Their precise function is not clear. However, incorrect

inductance of these two chokes in some receivers have caused narrow, rounded, black vertical bars on the extreme left side of the raster.

Because the coils are not wound over a resistor, an open circuit in either choke will eliminate all horizontal sweep and high voltage.

• **C80 (22-pf ceramic capacitor)**—Operates in conjunction with L35. The waveform produced by a scope with width expanded X5 and connected in parallel with L35 is shown in Fig. 9. A short circuit in this capacitor would blow the 3/4-amp fuse.

• **L39, the HORIZ EFFICIENCY coil**—With C81 and C84, this coil tunes the entire sweep system to produce an impedance of sufficient value to minimize current and heating in the 6DQ5 horizontal-output tube. It is wrong to call this a "horizontal-linearity" coil, because the linearity is changed very little by adjustment of this coil. Because this efficiency circuit requires special consideration during troubleshooting, it will be discussed more fully in the next installment, which will outline specific troubleshooting procedures.

• **C81 (.15-mfd paper- or mylar-type capacitor)**—Tunes L39. The waveshape in Fig. 10 shows that the "Q" is insufficient to produce a sine wave. Line "I" of Table 3 shows the effect of a shorted C81.

• **6AU4, the damper tube**—The function of this tube is to rectify the negative-going portion of the sine-wave ringing voltage which is produced by the cessation of yoke current. The current produced by this rectification is the “negative” yoke current which produces deflection from the extreme left side of the screen back to the center.

This rectification also acts as a brake, to damp out the ringing after its usefulness is over.

The DC voltage produced as a side-effect of the rectification is added to the power supply voltage to increase the plate voltage applied to the 6DQ5.

Damper action effects the width and linearity of the left half of the screen and the amount of high voltage. The waveforms produced at various points in the damper circuit are shown in Fig. 10.

• **C84 (.1-mfd paper- or mylar-type capacitor)**—The B-boost bypass capacitor. It is the input, or peak-reading, filter capacitor for the damper circuit.

An open C84 eliminates the high voltage and, consequently, the raster. The best clue to an open C84 is the huge, distorted waveform of 700 volts p-p found on the B-boost line. This waveform and the normal 110-volt p-p rounded-parabola waveform are shown in Fig. 11.

Significant leakage in C84 narrows the picture. A leakage of 4.7K ohms reduced the width about 1 inch at each edge of the picture (see Line “L” in Table 3).

A shorted C84 eliminated the high voltage.

The exact capacitance of C84 is not very critical, although the width and high voltage are reduced if the capacitance is less than .02 mfd.

• **The two horizontal coils in the deflection yoke**—These coils magnetically deflect the beams of the CRT.

Any unbalance in the current through the coils or any difference in the number of turns will cause a trapezoidal raster (wider at the top than at the bottom, or vice-versa).

An open in either coil stops all horizontal deflection and usually eliminates the high voltage and, consequently, the raster. The waveform picked up by positioning the scope probe near a yoke wire when a yoke coil is open is shown in Fig. 12. The width of the pulse is wider than normal (more damper conduction and higher boost voltage) and the amplitude is reduced (less high voltage). Line “J” in Table 3 shows the voltages that were produced by an open yoke.

Excessive leakage or an open in either of the two 560-pf capacitors which are inside the yoke cover, or even a serious unbalance in the coils, will cause the 4.7K-ohm balancing resistor to overheat and possibly be destroyed. If one of the capacitors shorts and the balancing resistor burns open, the picture will be slightly wider. If one of the ca-

pacitors opens and the resistor burns open, the picture will be slightly narrow. If either capacitor shorts and the value of the resistor is reduced by overheating, the picture becomes trapezoidal. If either capacitor opens and the resistance is reduced because of overheating, the picture becomes slightly narrow and exhibits yoke ringing. If both capacitors short, the high voltage and, consequently, the raster, are eliminated.

The 100-pf capacitor which parallels the “hot” yoke coil is used to balance the high frequencies so that each coil receives the same. If this capacitor shorts, the picture will be trapezoidal and the high voltage reduced. If the capacitor opens, the scanning lines on the left edge of the picture will exhibit some ringing.

• **6BK4, DC-shunt-type, high-**

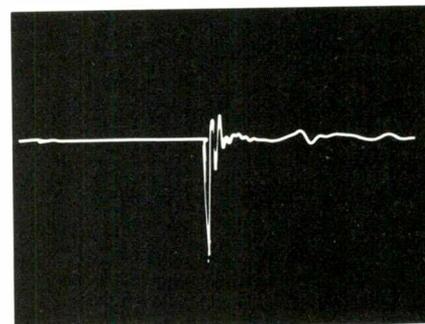


Fig. 9 A sudden decrease in damper current triggered this short damped-wave-train, because of the resonant circuit consisting of L35 and C80 in Fig. 6. The scope sweep was increased X5, to widen the waveform.

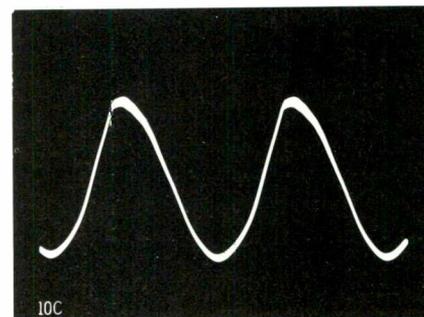
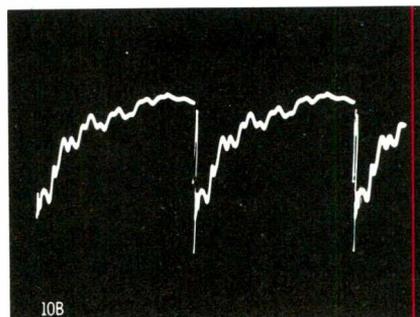
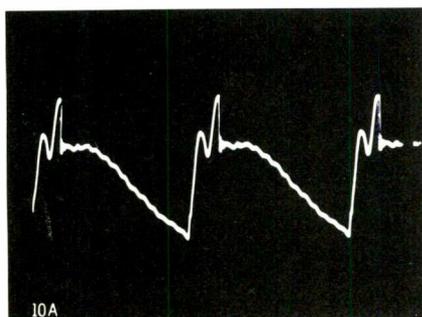


Fig. 10 Waveforms observed at various points in the damper circuit. (A) Waveform of the damper current through a temporary “scope” resistor which was connected between B+ and the junction of L39 and C81 in Fig. 6. (B) Waveform of the damper current through a “scope” resistor connected between the plate of the

damper and L35. The polarity of this and the waveform in (A) are opposite because C84, the boost capacitor, is connected to the midpoint of L35. (C) Waveform produced when the scope was connected in parallel with C81. It is almost a sine wave, but with some of the pulse remaining.

voltage regulator—The width, horizontal linearity and high voltage are regulated by maintaining a constant high-voltage current through the rectifier tube. The manufacturer establishes the maximum beam current for the CRT according to each chassis, and any portion of the high-voltage current which is not being used by the picture tube should flow through the regulator tube. For example, the maximum regulator current specified in the service data for the CTC7AA chassis is 1.2 milliamps. If the CRT draws .8 milliamp, the 6BK4 should draw .4 milliamp. If the CRT draws 1.2 milliamps, the 6BK4 should have zero conduction. If the brightness control is turned to black out the raster, the 6BK4 should draw 1.2 milliamps. (These amounts apply only to the CTC7AA chassis; later models are rated at 1.4 milliamps.)

In fact, the best way of obtaining valuable information about regulator action is to monitor the regulator current while you adjust the brightness control.

Measurement of the regulator current with the picture tube blacked out is more informative than is measurement of the high voltage using a high-voltage probe and meter. However, the best, and recommended, method is to measure **both**.

For example, consider the case of a receiver which has a very efficient horizontal sweep circuit, and which is operated on a line

voltage of 125 volts. If the high voltage is reduced to the specified amount by adjustment of the HV ADJ control, the regulator current might be 1.9 to 2.0 milliamps. This, of course, exceeds the ratings, and will shorten the lifespan of the regulator tube. If both the high voltage and the regulator current had been measured and analyzed, the line voltage could have been reduced, or the value of the screen resistor of the horizontal-output tube increased, or both. Then both the high voltage and the regulator current could have been brought within tolerance.

At the other extreme, assume that the receiver has a weak horizontal-output stage, is operated on low line voltage, or has an open input filter capacitor which reduces the B+ voltage, or is subject to all three conditions at once. If the HV ADJ control is adjusted for the rated high voltage, the regulator tube might be drawing only .2 milliamp, even when the screen is black. These conditions permit a CRT gun current of only .2 milliamp before regulation is lost and poor focus and narrow width are encountered.

Or, think about the case of the opinionated customer who insisted that the picture was brighter before you worked on the receiver. How do you prove to yourself **and** the customer that the receiver does indeed have maximum brightness? Just monitor the regulator current while you adjust the brightness control

from the point which produces a black raster to that which produces maximum brightness. If the regulator current is normal when the picture is blacked out (say .8 to 1.1 milliamps for older models or 1.2 to 1.4 milliamps for newer ones), and the current decreases smoothly when the brightness is increased, it proves that the brightness level at which the regulator current almost is zero is the true maximum brightness. Any attempt to increase the brightness above this point probably would cause blooming and defocussing.

Incidentally, the amount of high voltage has only a slight effect on the brightness. If the high voltage is increased or decreased 2KV and all other voltages remain the same, the difference in the brightness is just barely perceptible. Remember, most receiver conditions which increase the high voltage also increase the B-boost (and the boosted-boost), which is the source of the CRT screen voltages. Higher screen voltages on the guns of the CRT cause more conduction and more brightness. This increase in screen voltage, not high voltage is responsible for most of the change in brightness when the high voltage is changed with the HV ADJ control. Small changes in DC voltage to the screen grids, control grids or cathodes affect the brightness level far more than do larger changes in high voltages. Don't try to guess the amount of high voltage, **measure it!**

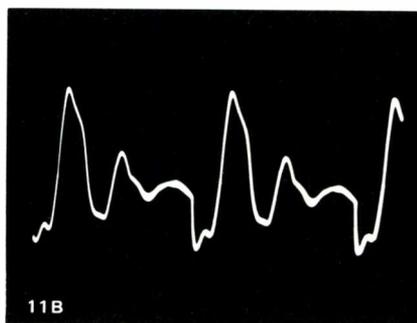
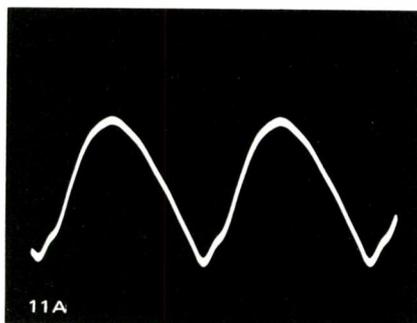


Fig. 11 Waveforms observed between terminal "BB" of T5 (Fig. 6) and ground, with different conditions of C84. (A) Normal waveshape is a slightly-distorted parabola of 110 volts p-p. (B) When C84 is open, this huge 700 volts p-p waveform is produced.

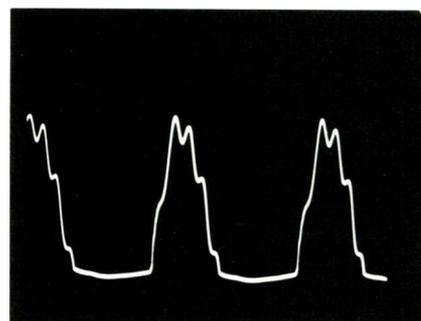


Fig. 12 Waveform produced by an open yoke winding. The scope probe was held near the yoke wire. The wider-than-normal pulse produces more b-boost voltage (from rectification by the damper) and the lower-than-normal amplitude eliminates the high voltage.

- **Resistor in cathode circuit of high-voltage regulator**—Later-model RCA's include a 1000-ohm resistor in the cathode circuit of the 6BK4. One milliamp of cathode current produces a 1-volt drop across the resistor. By measuring this voltage, you can determine the value of the regulator current without the difficulty of opening the circuit to insert a current meter. (Add a 1000-ohm resistor to any early-model CTC7AA chassis you service.)

If you should discover that one of these 1000-ohm resistors in the cathode circuit of the 6BK4 is badly burned because of overload, be sure to replace the regulator tube. It is almost certain to be shorted.

Excessive regulator current caused by a leaky capacitor or incorrect bias on the regulator tube usually is not sufficient to destroy the resistor. However, check it anyway.

- **C87 (.0033-mfd paper- or mylar-type capacitor)**—This capacitor slows down the response time of the regulator, to avoid "hunting", and also bypasses stray horizontal pulses, which might upset regulator action.

A leakage of 330K in parallel with C87 increased the regulator current (during operation with a picture of normal brightness) from .5 milliamp to 1.2 milliamps. Brightness decreased, focus blurred and the width narrowed on the left side of the screen.

- **R131 and R132 (1.5M-ohm, 5-per cent, 2-watt resistors)**—These resistors mainly determine the grid-to-ground voltage applied to the regulator tube. R20, the HV ADJ control, is in series with R131, to provide a vernier adjustment of the grid voltage. The cathode voltage of the regulator tube is clamped by connection, through the 1000-ohm resistor, to the 395-volt supply. As the B-boost voltage increases and decreases in step with any change in the high-voltage rectifier current, the grid of the

6BK4 receives slightly more than 50 per cent of the change in B-boost voltage.

In practice, the values of resistors which normally are in the megohms usually increase, if they change at all. If the value of R131 increases, the regulator tube draws more current. If the value of R132 increases, the regulator draws less current.

The values of R131, R132 and R20 are very critical because a bias of about -14 volts cuts off a


6 BK4. Notice Lines "K" and "O" in Table 3.

In Part 3

This completes the analysis of the function of the stages, sections and individual components of the horizontal sweep and high voltage system of a typical tube-type color TV receiver.

In the final installment of this series, part 3, specific troubleshooting tips and procedures will be presented. □

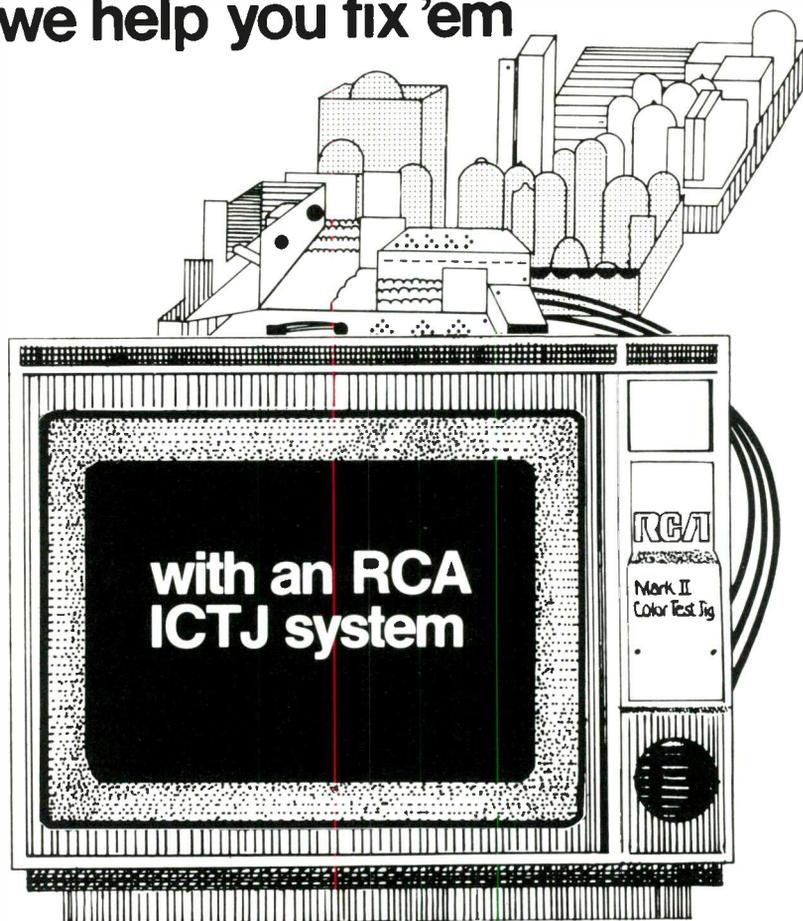As fast as you get 'em we help you fix 'em



Sound like the TV serviceman's dream? It is. RCA's industry compatible test jig is a complete testing system that lets you service more than 90% of all color TV console chassis on the market—and updates you as new ones come along.

Here's how: The RCA ICTJ system includes the test jig itself (in bench or portable models), your choice of 102 adaptors and cables, plus a handy cross-reference manual that specifies the right adaptors for each set. But most important, as the new models need service, you'll be kept up to date with new inserts for the manual and any necessary new adaptors will be made available. So whatever's coming, you'll be ready.

See your RCA Parts and Accessories distributor today for full information.

Parts and Accessories, Deptford, New Jersey 08096

Circle 27 on literature card

RCA

Sources of 12FR8 Tubes

We have a 12FR8 tube, also other older type tubes such as 80's, 78's and 24's. Anyone interested please contact us.

Gibson Radio & TV Service
110 Clark Ave.
Punxsutawney, Pa. 15767

We have about 50 12FR8 tubes. Will sell them for \$5.00 each, include postage.

Marmax Sales
3815 NW 35th Ave.
Miami, Fla. 33142

We have carried the FR8-2 solid-state replacement for the 12FR8 for over 3 years. We have a large stock on hand. The units, unlike imitations, compensate for the 12FR8 heater which is wired in the output transistor bias network in Bendix auto radios. The net price is \$6.30 each.

We also stock the DV8-1 solid-state replacement for the 12DV8. Net price is \$4.50.

Figart's Radio Supply Co.
6320 Commodore Sloat Dr.
Los Angeles, Calif. 90048

We are making a 12FR8 solid-state tube and have been selling same for the past eighteen months. The net price of the tube is \$4.00 each in any quantity. Orders may be addressed to:

Mark Electronics, Inc.
2315½ Artesia Blvd.
Redondo Beach, Calif. 90278

bookreview

Transistor Specifications Manual (5th Edition, Catalog No. 20883)

Author: The Howard W. Sams Engineering Staff

Publisher: Howard W. Sams & Co., Inc.

Size: 8 5/16 X 10 3/4, 160 pages

Price: Softcover, \$4.50.

This large, easy-to-use manual provides the electrical and physical characteristics needed to select the most suitable replacements for both recent and older designs of transistors.

The manual is divided into three principal sections: specifications, outlines and lead identification.


The specifications section lists essential electrical characteristics, including design polarity, leakage (I_{CBO}) gain (hFE), and minimum frequency response plus maximum design limits such as element voltages, collector current, power and temperature. Also included for each transistor are code numbers which, when cross-referenced to the other two major sections, give the manufacturer and indicate the lead and terminal arrangement and which outline illustrates the physical characteristics.

This edition includes a special specifications section for RF power transistors, which, in addition to the other characteristics listed previously, gives the G_{PE} , P_{OUT} , frequency limitations, V_{CC} and the efficiency.

The outlines section illustrates the physical shape of each transistor and gives all pertinent physical dimensions.

The lead and terminal section identifies the collector, emitter and base elements.

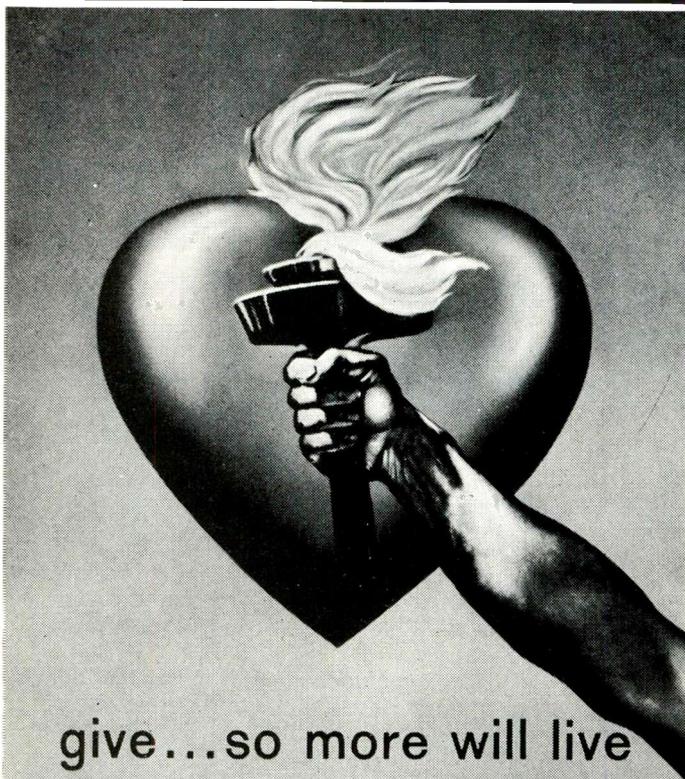Contents: Key to Transistor Specifications—Transistor Specifications—Key to RF Power Transistors—RF Power Transistor Specifications—Registered Transistor Outlines—Transistor Outlines—Lead and Terminal Identification—Key to Manufacturers. □



give...so more will live
HEART FUND

**If it's about servicing consumer
electronic products, you'll find it in
ELECTRONIC SERVICING**

service training

SCHEDULE

Manufacturers, distributors, electronic technical schools and service associations are invited to use this column to announce their electronic training activities which are open to all electronic technicians. Information about the training session(s) or seminar(s) should be mailed to the following address at least 60 days in advance of the first scheduled date: Service Training Schedule, ELECTRONIC SERVICING, 1014 Wyandotte St., Kansas City, Mo. 64105. Include: a brief description of the course; the duration of each session; the location, time and date; the cost, if any; and any other pertinent information.

Wollensak

Course content: Wollensak technical service experts will cover the servicing of Wollensak open reel and cassette recorders and the cassette duplicating system in 21 U.S. cities in 1972.

Sponsor: Wollensak/3M Audiovisual Products

Duration: 1-day sessions

Fee: Registration fee is \$37.50.

Dates and Locations:

San Antonio, Texas, May 9; Denver, Colo., May 11; Cincinnati, Ohio, May 23; Cleveland, Ohio, May 25.

Magnavox


Sponsor: Magnavox Service Training Center

Duration: Weekly and 2-day sessions

Dates and Locations: See schedule below.

Course content: No. 102, Colorimetry and Color TV Setup, 1-day; Course No. 203, Deluxe Color TV Chassis Circuit Analysis and Troubleshooting, 2-days; Course No. 204, Solid-State Color TV Circuit Analysis and Troubleshooting, 2-days; Course No. 511, Magnavox Color Remote-Control Systems, 2-days; Course No. 202, Color Television Alignment, 1-day; Course No. 130, Solid-State Components—Their Operation and Application in Solid-State Radios, 2-days; Course No. 302, Solid-State Television Circuitry

3 Instruments in One!

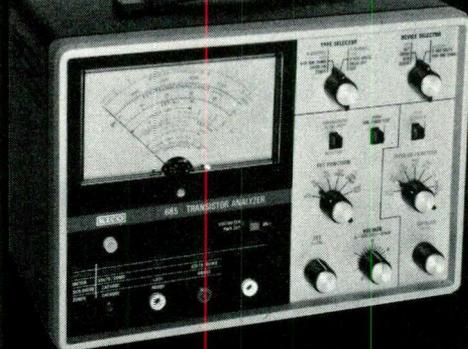

**NEW EICO
TRANSISTOR
ANALYZER**

**Model 685
\$99.95
KIT**

FACTORY WIRED \$149.95

Nobody but Eico makes the troubleshooting of solid state equipment so quick, easy, versatile and precise for the professional electronics technician and engineer—and at such low cost!

- Dynamically tests transistors in and out of circuit.
- Performs the 4 basic tests on all types of FETs including pinch-off.
- Performs the 3 basic tests on all types of bipolar transistors.
- Tests for true transconductance and AC Beta, in and out of circuit.
- Tests all types of diodes and measures zener voltage.
- Tests SCRs, TRIACs, and UJTs.
- Incorporates easy-to-use DC Voltmeter and Ohmmeter.
- 50 uA taut band meter movement.

FREE 32 PAGE EICO CATALOG

For latest catalog on EICO Test Instruments, Stereo, EICOCRAFT Projects, Environmental Lighting, Burglar/Fire Alarm Systems, and name of nearest EICO Distributor, check Reader Service Card.

EICO, 283 Malta Street, Brooklyn, N.Y. 11207



Circle 29 on literature card

and Service Techniques, 2-days; Course 140, Magnavox Tape Recorders, 2-days; Course No. 160, Magnavox Record Changers, 2-days.

Courses 130, 140, 160, 203, 204, 302 and 511 are 2-day programs. Only registrations for both will be accepted.

For further information contact:
Magnavox Service Training Center
2131 Bueter Rd.
Fort Wayne, Ind. 46803

	New York	Atlanta	Cleveland	Chicago	Dallas	Los Angeles	San Francisco
Apr. 6	202	202	202	202	202	202	202
Apr. 10 Apr. 11	130	130	130	130	130	130	130
Apr. 12 Apr. 13	302	302	302	302	302	302	302
Apr. 17	120	120	120	120	120	120	120
Apr. 18 Apr. 19	203	203	203	203	203	203	203
Apr. 20	202	202	202	202	202	202	202
Apr. 24 Apr. 25	511	511	511	511	511	511	511
Apr. 26 Apr. 27	204	204	204	204	204	204	204
May 1 May 2	130	130	130	130	130	130	130
May 3 May 4	140	140	140	140	140	140	140

Externally Generated Interference In TV

How to determine where the interfering signal is entering and how to eliminate or reduce it. by Bruce Anderson/ES Contributing Author

■ When we stop to consider all the sources of electromagnetic radiation in existence today, we wonder why there aren't more instances of interference than there are. Nevertheless, it is small consolation to the occasional victim to learn that he is one of a very small group—he simply wants the problem solved.

Eliminating interference seldom is an easy task. The television designers have taken a lot of pains to make their products immune to most interference, and the FCC has all sorts of restrictions which remove most of the possible causes. This means that there is seldom a "standard fix" for an interference problem. There are, however, some standard approaches to the problem, and these are the subject of this discussion.

Some Practical Considerations

Because the interference is probably a local problem, immediately hauling the set off to the shop seldom accomplishes anything. This seems obvious, but we know of an instance where a combination was brought in, not once, but twice, to get rid of interference in the audio. Because the source of the interference was about one block from the home, and sixty blocks from the shop, very little was accomplished. Once the exact nature of the problem was determined, the fix required about forty-five minutes to install—in the home.

In some instances, it will be necessary to remove the receiver to the shop to do the work, but this should not be done until it has been determined what fix is required. Even when the required procedure is known, it often is simpler to finish the job on the

spot. This does not mean that your customer should expect the job to be done for the price of a service call. On the contrary, the fact that you have to "bring your shop into the home" demands that you charge regular shop rates, perhaps more. The customer should be told this before you begin.

Interference in the Audio

Interfering conversations in the audio are most often encountered in combination receivers which use the amplifiers of the radio/record player for TV sound.

The first step is to prove that the interfering signal is actually being injected into the audio system. This can be done by switching the function selector to the record-player position and observing whether or not the interference is still present.

Starting from the switch, disable each stage of the audio amplifier by shorting the emitter to the base, until the interference is eliminated. When you locate the stage which eliminates the problem, bypass the base to the emitter with a small capacitor. Usually, a capacitance of 100 to 1000 pfd will be sufficient.

Fig. 1 illustrates the cause and fix for this problem. The basic problem here is that, although the input impedance of a solid-state audio amplifier might be low at audio frequencies, it might be relatively high for RF signals. Quite often a large capacitor will effectively function as an inductor at RF, or the copper pattern of the printed circuit will act as an antenna. The leads of the capacitor which you install also can have enough impedance at RF to cause trouble, so keep them as short as possible, and

locate the capacitor as close to the transistor leads as you can.

Interference in the IF Amplifier

More often, a spurious signal will find its way into the IF amplifiers of the TV receiver. Again, the first step is to prove that this is the case.

To determine that the IF strip is the point of entry, disable the tuner and see if the interference persists. If it does, it is probably that the interference is entering one of the IF amplifiers.

It is unlikely that a video amplifier is picking up the unwanted signal, because the gain of the video amplifiers is relatively small. However, to be certain that the problem is not in the video system, disable the video detector and observe whether or not the interference persists.

There are several ways to eliminate the tuner output. Disconnecting the coaxial cable which conducts the tuner output to the IF-amplifier input is the easiest method in many cases. Disconnecting B+ from the tuner is another. If tubes are used in the tuner, removing them is the easiest method.

There is a possibility that the action of the AGC system can be misleading if the interference persists when the tuner is disabled. Disabling the tuners causes the AGC circuit of the receiver to drive the IF amplifiers to maximum gain. This, in turn, might cause the IF strip to pick up interference which would not be noticeable if the amplifier were operating at its normal gain. To avoid this trap, measure the IF AGC bias under normal operating conditions on the weakest channel, and then inject this amount of fixed bias when the

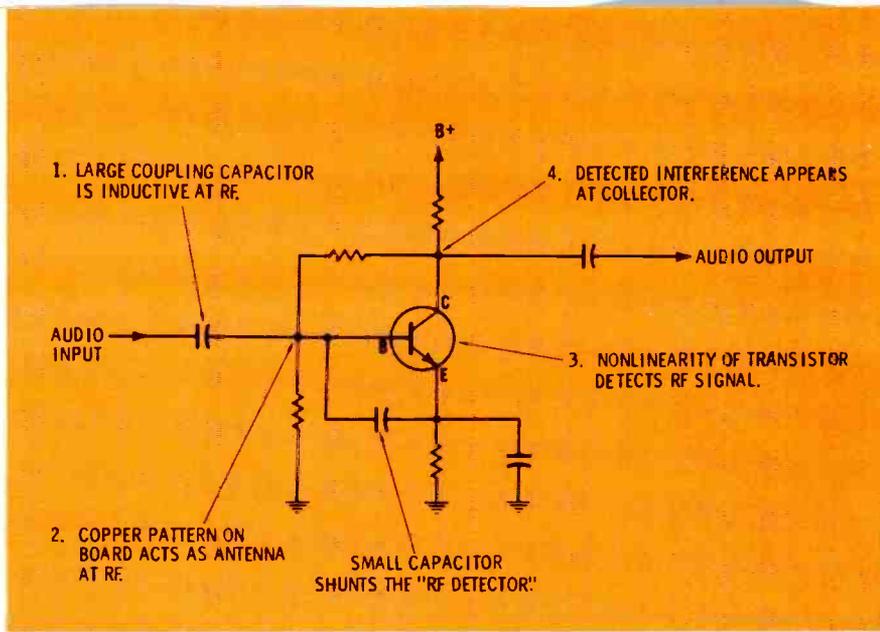


Fig. 1 How an audio amplifier can become a "crystal radio".

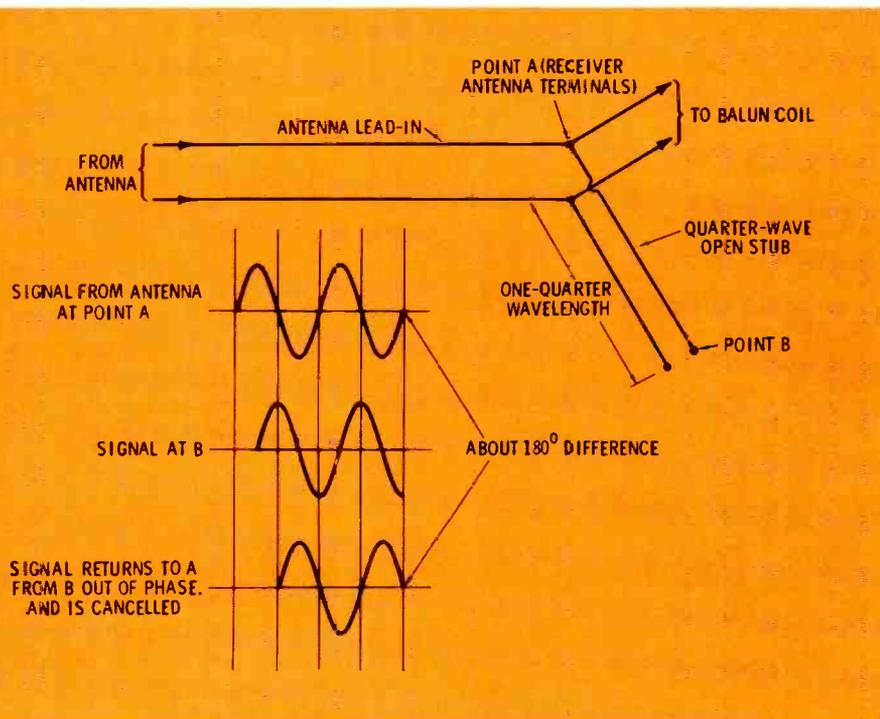


Fig. 2 Construction and operation of a quarter-wave, open-stub trap.

tuner is disabled. If the unwanted signal is still present, you can be assured that it really is entering one of the IF amplifiers.

Shielding is the simplest way of getting rid of IF interference, and a piece of ordinary aluminum foil is an excellent shielding material. If the IF amplifiers are transistors, there is very little heat dissipation, and a close-fitting piece of foil may be formed over the IF strip. Naturally, the foil must be securely grounded to the chassis, and it must not come in contact with any points

of the circuit which have voltage on them.

Do not use paper as an insulating material between the foil and the circuit elements. Even though there is practically no heat generated by a transistorized IF amplifier under normal conditions, a failure in the future might produce enough heat to ignite the paper. It is better to fabricate some metal supports for the aluminum shield. A few lengths of solid-copper wire, about 14- to 16-gauge, can be soldered to the chassis or to

ground points on a printed-circuit board. These will support the foil away from the circuitry, and also can serve as convenient ground connections for the shield.

If the IF amplifier uses tubes, the circuit is usually less susceptible to interference in the first place, particularly if the tubes are shielded. If the shields are missing, they should be replaced, of course. If there were no shields originally, it usually is no problem to install some. It probably will be necessary to ground any added shields. This can be done with a short length of ground braid soldered to the shield and the chassis, or to a ground point on the circuit board. Installation of additional tube shields might make it necessary to realign the IF amplifier, because the shields can detune the circuits.

Shielding the under side of the IF strip might also be necessary. This looks like a tough job at first, but actually it is simpler than shielding the top. Just shield the whole bottom of the cabinet. A flat piece of window screen is handiest for this job. (Aluminum foil obstructs the ventilation holes in the bottom of the cabinet.) Cut the screen to the right size, stretch it tightly across the cabinet bottom and fasten it with a few thumb tacks. When the chassis is installed, it will make contact with the screen all around its perimeter.

Shielding the entire inner surface of the cabinet can be effective, but it is quite a chore, and unless it is done carefully, it won't be very effective. The sides of the cabinet are easy to shield,

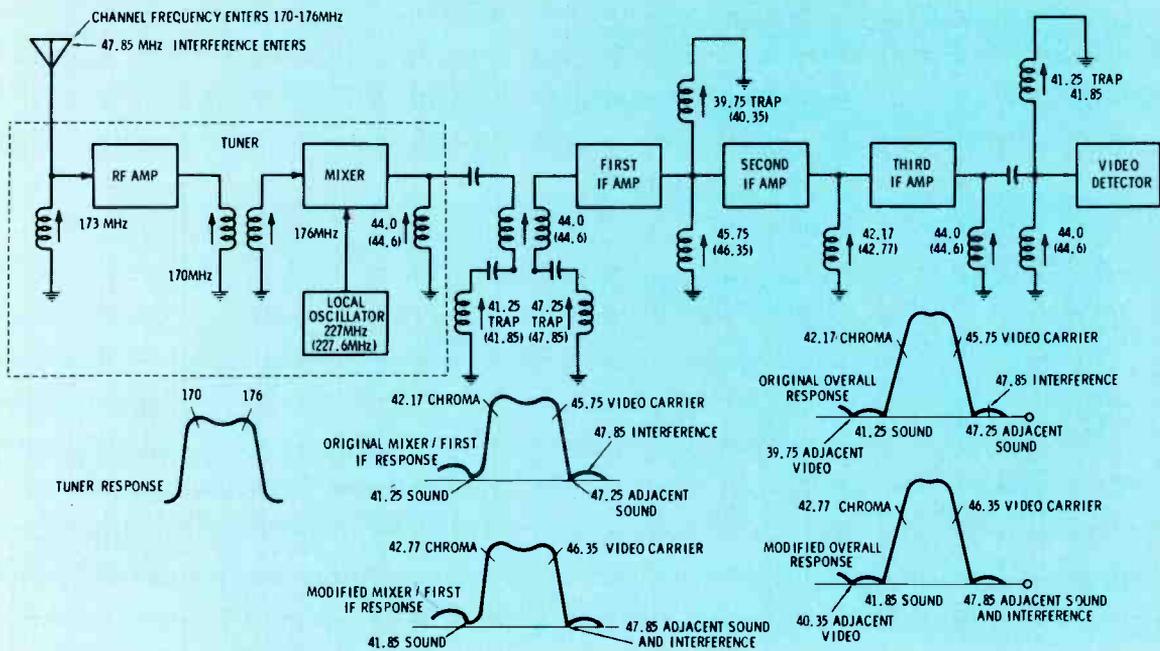


Fig. 3 Effect on interference of realigning the IF amplifiers and retuning the local oscillator. New frequencies are shown in parentheses.

Table

Frequencies listed here illustrate how to realign the video IF's to trap out interference in or near the IF passband. In this example the interfering signal has a frequency of 47.85 MHz.

Old Frequency	New Frequency	Marker Point
47.25 MHz	47.85 MHz	Adjacent-channel trap
47.75 MHz	46.35 MHz	Video IF carrier
42.17 MHz	42.77 MHz	Chroma subcarrier
41.25 MHz	41.85 MHz	Sound trap
39.75 MHz	40.35 MHz	Adjacent-channel trap

but the front (if it is not metallic) and the back can be difficult.

Tuner Interference

By far, the part of the receiver which is most susceptible to interference is the tuner. There are several reasons for this: (1) Smaller interfering signals will be objectionable, because of the relatively high gain of the tuner; (2) most interference "rides" into

the receiver right along with the broadcast signals, making shielding ineffective; (3) because of the local oscillator, a spurious signal having any frequency which can mix with either the broadcast frequency, the local-oscillator frequency, their sum, and perhaps their harmonics, can produce energy at the IF frequency.

Shielding the tuner is fairly

simple, and although it might not solve the problem, it is a good place to start. If you prefer to know whether shielding will do the trick without trying it, disconnect the tuner input cable and clamp the AGC bias as described before. If the interference still is present, shielding probably will be effective.

Another quick method which can be used to determine if shielding the tuner will help, is to disconnect the antenna lead-in, wrap the tuner in paper towels, then wrap aluminum foil around the towels and ground the foil at one or more points.

Assuming that the unwanted signal is entering through the antenna input, attempt to improve the ratio of the signal level between the TV signal and the interfering signal. Increasing the level of the TV signal with a more sensitive antenna or one with better directivity is always a good approach. Sometimes, relocating the antenna to a place which is naturally shielded from the interference will solve the problem.

The use of shielded lead-in often can eliminate or reduce interference. If you try this, extend the shielding all the way to the balun, not just to the back of

the cabinet, and ground the shield. In some instances, the results might be better with the shield ungrounded, so try it both ways. If the receiver has a "hot chassis," make the RF ground connection with a capacitor which has at least a 500-volt rating and a value of about 1000 pfd.

Some receivers have a built in 72-ohm coaxial antenna terminal. If this is the case, a coaxial lead-in might be the simple solution.

When the interference is from an FM station, a simple trap often is effective. These are marketed by several companies, and should be available from your local parts distributor.

If the exact FM trap you require is not available, and you know the frequency of the interference, you can sometimes obtain acceptable results from a "home-made" trap. This trap is properly called an "open quarter-wave stub" and its construction and operation are illustrated in Fig. 2.

As a signal passes down a lead-in, its phase continuously changes, going through 360 degrees as it travels a full wavelength, or 90 degrees in one-fourth wavelength. If the signal encounters an open end (or a short for that matter), it is reflected back along the line. If the signal travels one-fourth wavelength to an open, it has been shifted 90 degrees before it is reflected back. By the time it reaches the original starting point, it is shifted another 90 degrees, so that the reflected signal is exactly out of phase with the original signal at that point. The sum of these two signals, therefore, is zero.

To make a trap, cut a piece of lead-in which is slightly more than one-fourth as long as the wavelength of the frequency to be trapped.

Calculating the exact length is

laborious, because the velocity of a signal in a lead-in is involved, but dividing 180 feet by the frequency in MHz is accurate enough.

Connect one end of the stub to the antenna terminals, along with the lead-in, and start cutting off the other end, a quarter-inch at a time, until the interference is eliminated or reduced to an acceptable level.

Aligning Out Interference

Although it is seldom mentioned, there is really nothing "sacred" about the marker frequencies specified for alignment of IF amplifiers in a TV receiver. As shown in Fig. 3, the receiver local oscillator is tuned 45.75MHz above the video carrier of the channel to be received. Then the IF stages are stagger-tuned to provide bandpass for the TV signal. The precise frequency of each of the video IF circuits is seldom specified, since only the overall response is of prime importance.

As an example, suppose that there is a 47.85MHz interfering signal in an area. While this is outside the normal passband of the IF strip, it can still produce enough output at the video detector to cause interference patterns on the CRT. But, if this signal could be made to fall exactly in the trap frequency of the adjacent-channel sound trap, normally 47.25 MHz, the trap would attenuate it below the level at which it becomes troublesome.

Impossible? Not at all. Just get out the alignment data for the chassis and add 0.6 MHz—the difference between the adjacent-channel sound trap and the frequency of the interfering signal—to all the alignment check frequencies. It is best to write down all of them as shown in the accompanying table, to avoid confusion. Then realign the receiver to these new frequencies.

Alternatively, the receiver

TeleMatic

PROFESSIONAL COLOR TV SERVICE EQUIPMENT

ECONO JIG

Color Test Jig



\$49.95 Net
less tube

- Complete with all components and cables.
- Durable metal cabinet.
- Professional equipment for rapid servicing.

ADAPT-ALLS

Yoke Convergence Adaptors



- To service all sets with any test jig.
- FREE: Write for cross-reference listing thousands of sets.

TRANSVERTERS

Service Solid State TV




- On any make test jig with simple plug-in Transverter.

MOLEX CUSTOM CABLE KIT

Make all combinations of Molex Cables

CR-596 contains:

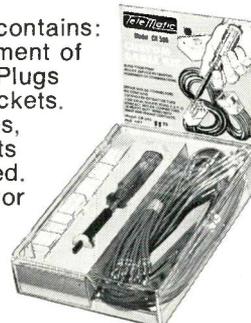- Assortment of Molex Plugs and sockets.
- 18 wires, contacts attached.
- Extractor tool.



Send for our Free Catalog

TELEMATIC DIV., UXL CORP.
2245 PITKIN AVE., BKLYN., N.Y. 11207

Circle 30 on literature card



ONE FOR THE MONEY

- Discounted to provide you with a higher profit margin.
- Proven quality for better customer satisfaction.
- A complete range of service types for radio, TV, hi-fi, foreign and industrial electronics.

In every important way, International Servicemaster is number one. For complete details, contact your International representative today, or International Electronics Sales Corporation, 10 Daniel Street, Farmingdale, New York 11735, (516) 293-1500.

International
International Electronics Sales Corp.
div. of International Components Corp.
Circle 31 on literature card

could be aligned "low"—video IF carrier at 44.75 MHz, chroma subcarrier at 41.17 MHz, etc.—to provide more separation between the TV signal and the interference.

The same procedure can be used to trap out an interfering frequency which is below that of the IF's. For example, an interfering 40.15M-Hz signal can be attenuated by shifting up the whole IF tuning so that the 39.25M-Hz trap is set to 40.15M-Hz. In this case, 0.8M-Hz would be added to each of the original IF alignment frequencies.

Even if the interfering signal is within the normal TV IF passband, realignment might be effective. You may be able to "slip" a 42M-Hz signal over into the 41.25M-Hz trap (if it is amplitude modulated), or a 46.5M-Hz radiation can be shifted over into the 47.25-MHz trap. Generally, all the tuned circuits in the IF strip can be tuned at least 1M-Hz in either direction from their nominal frequencies, and some can be retuned much farther.

Another scheme which can be used in some instances is to retune only one trap to the interfering frequency. The 39.75M-Hz trap is not necessary for normal operation unless the next higher channel is occupied. It usually can be tuned across three or four MHz, allowing it to tune out anything from 38.25 to 41.25M-Hz. The 47.25M-Hz trap can sometimes be used the same way, but it might be necessary to "touch up" the rest of the strip to obtain the specified bandpass.

Summary

Eliminating interference can be one of the toughest jobs encountered in television servicing. Because of this, many technicians prefer to leave all but the simplest of these problems to someone else, and unless he is something of a diplomat, this is often a wise decision.

For those who are willing to

tackle the interference problems, there are some basic rules to follow, some technical and some not. We feel that the following are vital:

1. Before doing anything, explain to the customer that he has a serious difficulty; that your time is worth a certain amount and that you might have to spend several hours finding and curing the problem; that you will have to do some (perhaps all) of the troubleshooting and repair in his home; and that you cannot guarantee satisfactory results. (Remember, doctors, lawyers, dentists, and ministers don't guarantee success.)

2. Find out where the interfering signal is entering the receiver. This is done by signal tracing, much the same technique used in day-to-day receiver servicing.

3. Signals entering the audio system are usually removed by shunt capacitors which are large enough to attenuate RF but small enough that they do not seriously affect the quality of sound reproduction.

4. Signals entering the IF strip are best handled by shielding. This might involve simply laying a piece of screen wire beneath the chassis; but you might have to shield the entire IF amplifier.

5. Shielding the tuner might solve the problem, but usually signals enter the tuner by way of the antenna input. Try a better antenna, relocating the antenna, shielding the lead-in, or trapping at the receiver antenna terminals.

6. Only if there is no other solution, realign the receiver IF amplifiers so that the interfering signal is outside the passband or in one of the traps of the receiver. Most IF's can be shifted a megahertz or more in either direction without changing the quality of the picture or sound an unacceptable amount. Sometimes a single trap can be retuned to "take out" the unwanted signal. □

audio systems report

Features and/or specifications listed are obtained from manufacturers' reports. For more information about any product listed, circle the associated number on the reader service card in this issue.


Five-Channel Mixer/Power Amplifier

Product: Power amplifier

Manufacturer: Altec, Inc.

Function and/or Application: To mix and amplify audio signals from separate power sources.

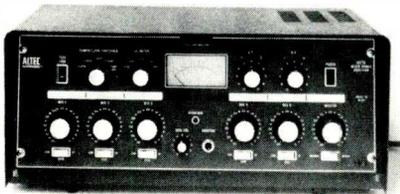Features: Designed for installation in churches, schools, hotels, theatres, convention halls, ball parks, recording studios, etc. Built-in test oscillator for system level adjustments, set-up and testing; five mixing inputs with



controls, visual overload indicators; circuit breaker for amplifier protection. The 1607A has a 600 ohm line level link between the mixer/line amplifier and power amplifier input.

Specifications: 75 watts rms power from either AC or DC power source. Low noise mixing circuits for switchable input gain giving it flexibility for the varying types of audio.

Price: Model 1607A sells for \$648.00.

Circle 60 on literature card

DC Tape Player Motors

Product: Tape player motors

Manufacturer: Weltron Co.

Function and/or Application: Motors for cartridge players

Features: Motors have been designed for use in many cartridge players including: Toshiba, Bowman, AudioVox, Pioneer, Panasonic, Times, Electro, Muscat. Electra, Westbury, Pianola, Craig, Kraco, Weltron and others. In the selection are universal



motors, universal motors less shields, motors with shields, and motor-and-shield brackets.

Specifications: The 12-volt DC replacement motors operate at 2000 to 3000 rpm. Voltage and direction vary according to model.

Price: The price of the tape player motors are from \$9.40 to \$10.75.

Circle 61 on literature card

Line-Matching Transformer

Product: Model A97A line matching transformer

Manufacturer: Shure Brothers, Inc.

Function and/or Application: Transformer matches low-impedance microphones to medium impedance tape recorders.



Features: The A97A improves the overall audio input signal and permits the use of very long cables without loss of high frequency and without hum and noise pickup. The Shure A15 series of attenuators, equalizers, and filters can be used with A97A for further improved performance.

Specifications: Model A97A measures 2 1/2 inches X 3/4 inches.

Price: The A97A sells for \$21.00.


Circle 62 on literature card

**For more information
about above products
use reader service card**

NEW! UPDATED MODEL HC-8A from 

"IN-CIRCUIT" CURRENT CHECKER FOR B&W AND COLOR SETS

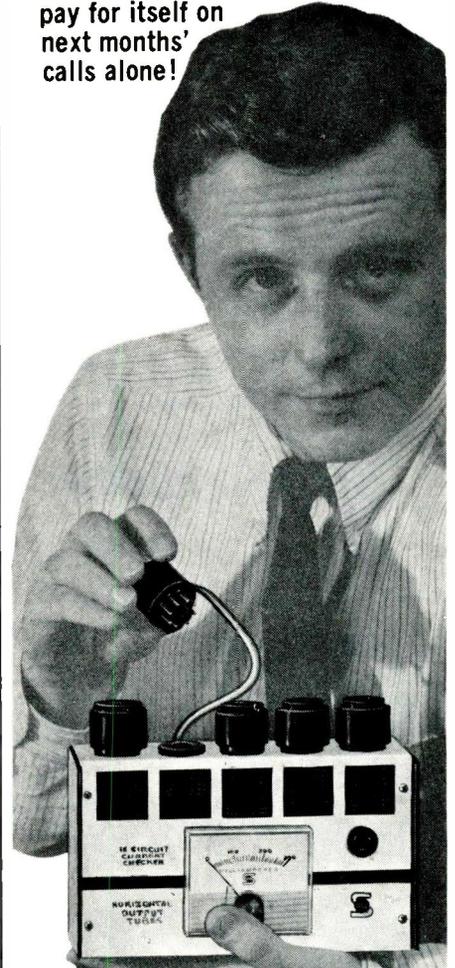Eliminates most common cause of "callbacks" (unstable focus, shrinking pictures, etc.)! Should pay for itself on next months' calls alone!



AIDS IN TROUBLE SHOOTING

There's just nothing like the HC-8A. Tune horizontal drive and linearity for "dip"—and in seconds—you've got best possible focus, width and stability at minimum cathode current. Makes convergence adjustments faster, easier—longer lasting!

Especially useful on color TV where a slight misadjustment of horizontal linearity or efficiency coils drives cathode currents sky high! 5 pre-wired sockets for all popular horizontal output tubes lets you plug into circuit fast—no clip-^{ONLY} \$45^{NET} ping or unsoldering of leads!

See Your Distributor or Order Direct

 **SECO ELECTRONICS CORP.**
1001 Second St. So. • Hopkins, Minn. 55343

Circle 32 on literature card

KEEP 'EM QUIET...

and CLEAN 'EM, TOO ...
with **QUIETROLE**



When you use Quietrole, you can be sure of clean, quiet operation, because you are using the number one cleaning and lubricating spray pack available. Safe for any set, color, or black and white. Absolutely no harmful aftereffects of any type.

In bottles too, if you prefer.

QUIETROLE . . . the choice of better servicemen everywhere.




Product of

QUIETROLE
COMPANY

Spartanburg, South Carolina

Circle 33 on literature card

Save Time on PC Board Repairs!

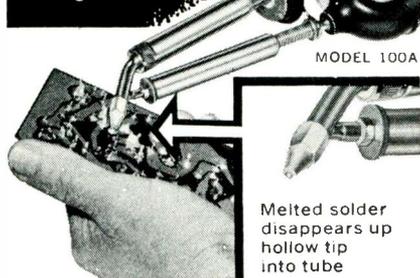

MODEL 100A

Melted solder disappears up hollow tip into tube

The ENDECO Desoldering Iron Removes Soldered Components in seconds . . . without damage!

Endeco melts solder, then removes it by vacuum • Leaves terminals and mounting holes clean • Resolders too • One-hand operation • Temperature controlled for continuous use • Ideal for use with shrinkable tubing • 4 tip sizes • Quickly pays for itself in time saved • Only \$18.75 net.

SMALLER SIZE AVAILABLE. SEE YOUR DISTRIBUTOR OR WRITE:



ENTERPRISE
DEVELOPMENT
CORPORATION

5127 E. 65th • Indianapolis, Ind. 46220

Circle 34 on literature card

antenna systems report

Features and/or specifications listed are obtained from manufacturers' reports. For more information about any product listed, circle the associated number on the reader service card in this issue.

Antenna Mounting Kit



Product: BSAK base station mounting kit

Manufacturer: Larsen Electronics

Function and/or Application: Adapt vehicular units for base station use

Features: Kit includes hardware for mounting to any tower or mast, ground plane rods and complete tools and instructions. Unit accommodates either the 150 or 450 MHz bands.

areas where channels are broadcast from different directions. Multiple single channel antennas can be combined into a single downlead to the TV set and also can be used to combine a single channel antenna with a broad band antenna. In many cases, the couplers eliminate the need for an antenna rotator. The Yagi couplers are encased in weather-proof housings, complete with straps and thumbscrews for mast mounting. The YC-75 includes F

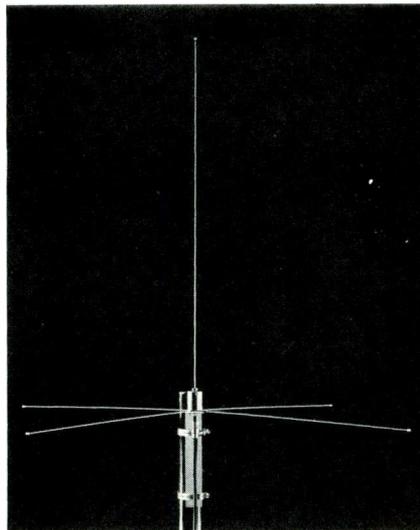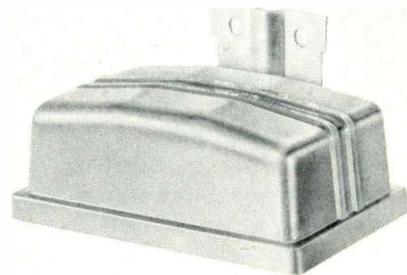

Specifications: Gain approaches the 3 or 5 dB mark for the 150 MHz and 450 MHz models when used in mobile service. Weight is less than one pound with next to zero wind load.

Price: The BSAK kit sells for \$24.50.

Circle 70 on literature card

Antenna Couplers

Product: Yagi antenna couplers for home and commercial MATV system.

Manufacturer: Jerrold Electronics

Function and/or Application: Combining output of two antennas into a single lead-in.

Features: The YC-300 is used in

connectors, weather boots and an extension tool.

Specifications: The YC-300 series is used for 300 ohm twinlead installations. The YC-75 series is used for 75 ohm coaxial systems. 300 and 75 ohm models are available for each VHF channel, 2 to 13; there is a 75 ohm model for FM. Two paths are provided for TV signals; one passes a specific TV channel with a minimum of loss, 2.0 dB, but attenuates all other channels, 20 dB. The other path attenuates the channel to which it is tuned by about 10 dB, passing all other channels with only about 1 dB attenuation.

Price: The YC-300 and YC-75 couplers sell for \$11.65 each.

Circle 71 on literature card

FM Receiver-Modulator


Product: Weathermod FM receiver-modulator for weather broadcasts

Manufacturer: Catel Corp.

Function and/or Application: FM applications in coaxial cable systems.

Features: The Weathermod combines a VHF-FM receiver and an FM modulator to add weather broadcasts to CATV and MATV system. The usual 162.55 MHz or 162.40 MHz can be converted to any frequency in the FM band from 88 to 108 MHz. Audio output

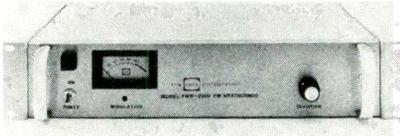is provided to add the broadcasts to the aural frequency of a CATV weather channel. Input jacks facilitate the addition of a microphone or music source to the system. The Weathermod is solid-state, using silicon transistors, integrated circuits and FET field effect transistors.



Specifications: Sensitivity is 0.5 uV for 20 dB quieting and adjacent channel rejection is 80 dB. Stability is 0.005 per cent with the use of crystal-controlled circuitry. Output is 45 dB, continuously variable, and the spurious beats are 60 dB below the output level. The Weathermod is designed for 117 volts AC operation and requires 3 1/2 inch of vertical space in a standard 19-inch relay rack.

Price: The Weathermod sells for \$695.00.

Circle 72 on literature card

Adjustable P-Clips

Product: N/A

Manufacturer: Electrovert, Inc.

Function and/or Application: Bundles and secures cable and/or wire. Applications include: cables, bundles of wires, components, pipes and tubing where a clamp, strain-relief or strap is required.

Features: P-clips in nine sizes to fit bundle diameters from 1/8 inch through 2 inches. The P-clips are molded of virgin nylon for service indoors and outdoors. The clips are lightweight, abrasion resistant, tough, have high tensile strength, resilience and minimum absorption rate with chemical resistance to common solvents, alkalies, dilute acids, oils and grease.

Specifications: N/A

Price: The price of the adjustable P-clips start at \$2.75.

Circle 73 on literature card

Put the first team on the bench

Heathkit "Profit-Makers" pay-off in price and performance

NEW IB-1102 120 MHz FREQUENCY COUNTER;

Another Heathkit first! An eight-digit counter with illuminated overrange, gating, kHz and MHz indicators. Preassembled temperature compensated clock assures overall accuracy. High-impedance, low-capacitance (FET) input circuit presents minimum loading. Automatic triggering level permits "hands-off" operation. Sensitivity is 50 mV to 100 MHz, 125 mV above 100 MHz. The 1102 will accept inputs up to 120 V rms from 1 Hz to 150 Hz, 50 V at 4 MHz, and 3 V at 120 MHz. Stability is ± 1 ppm from $+10^\circ$ to $+40^\circ$ C, and aging rate is less than ± 1 ppm per year. Other features include ECL circuitry, 1 Hz resolution without switching time base, 120/240 VAC operation, portable case with bail handle and detachable line cord. Assemble yours in an easy 15 hours.

Kit IB-1102, 12 lbs. 349.95*

349.95*



IM-102 DIGITAL MULTIMETER;

Measures AC and DC voltage, current, and resistance, with automatic switching for DC polarity. Five overlapping ranges show voltage from 100uV to 1000V on DC; 5 ranges cover 100uV to 500V on AC; 10 ranges measure 100nA to 2A, AC or DC; 6 resistance ranges cover 0.1 ohm to 20 megohms. Input impedance is 1,000 megohms on the 2V range, 10 megohms on higher ranges, with overload protection on all. 3 1/2 digits for 100uV resolution on 200mV range, 1V on 1000V. Automatic decimal point. Panel light indicates over-range. DC calibrator, furnished assembled, and unique transfer method allow calibration to 0.2%. Unit can be lab calibrated to 0.1%. Kit includes standard banana jack connectors complete with test leads. Assembles in approximately 15 hours. For lab spec performance on a budget...order your IM-102 today!

Kit IM-102, 9 lbs. 229.95*

Kit ID-1041, high-voltage probe accessory, 1 lb. ... 6.95*

229.95*



IO-103 5" TRIGGERED SWEEP SCOPE;

Maximum flexibility in a general purpose scope, at a price to fit any budget... the new Heathkit IO-103 is a tech's dream come true! Big 6x10 cm screen with lighted graticule for easy, accurate measurements. DC-10 MHz ± 3 dB response with less than 50 ns rise time on vertical channel. Horizontal expansion gives x2 magnification $\pm 5\%$ for a 50 ns/cm sweep rate. Triggered sweep, too, with selection of either normal or automatic modes. Other features are switch controlled AC-DC coupling; provision for external triggering signals and horizontal deflection signal; front-mounted connectors for vertical inputs and 1V peak-to-peak signal for checking calibration; 120/240 VAC operation. Put this budget-minder to work for you now.

Kit IO-103, 37 lbs. 229.95*

229.95*



Free — Your 1972 Heathkit Catalog with the world's largest selection of instrument kits.

HEATH COMPANY, Dept. 25-4
Benton Harbor, Michigan 49022

Enclosed is \$ _____, plus shipping.

Please send model(s) _____

Please send FREE Heathkit Catalog.

Name _____

Address _____

City _____

State _____

Zip _____

Prices & specifications subject to change without notice.

*Mail order prices; F.O.B. factory.

TE-260

Circle 35 on literature card

The Terminology of Transistor Testing

A review of the terms applied to the qualities and quantities commonly measured to determine the condition of transistors. Associated test setups are also included.

by Forest H. Belt

We've had transistors more than twenty years. In that time, most of us have picked up transistor jargon. Most of us talk freely about leakage and beta and gain. Some of us even know what "bipolar" means, although it took the FET to bring significance to the word.

But awhile back I had the chance to quiz a large group of technicians. Included in what I asked were some transistor terms. The number of those who didn't really understand the terms surprised me. They could use them, but only a small percentage knew exactly what they meant.

For example, all the technicians quizzed knew what leakage is. But barely more than half knew the alphabet symbols for the various kinds of transistor leakage. Only one out of three knew which kind of leakage most affects transistor operation.

They all knew about JFETs and

IGFETs. Yet, only a few recognized the peculiarities that make testing FETs so different. And none could tell me what I_{BSS} is. That's no calamity in itself, but it can hinder those technicians when they service equipment which uses FETs.

Here's the point: Transistor testing has a language of its own. Fortunately, you don't need to learn the dozens of engineering parameters. Instruments that technicians buy test only the few parameters that are important for servicing. Learn those fairly well, and you're set for transistors of any kind.

Design Features

Polarity

You might already know the basic language of transistor testing. One term is **polarity**. It signifies whether a bipolar transistor is NPN or PNP, or whether a FET is N-channel or P-channel. Set up the tester wrong and you'll get no reading or, at best, a wrong one.

Some instruments have a chart with polarities listed. But new transistor types are introduced every month. Charts are outdated quickly. Consequently, it is better to refer to the diagram of the equipment you're servicing. Fig. 1 shows the schematic symbols for popular transistors.

Elements

Be familiar with transistor **elements**. Ordinary (bipolar) transistors have a collector, base, and emitter. The base is the control element. Its material determines the polarity in which operating voltage are applied. However, the polarity arrow is in the emitter element of the schematic symbol.

The JFET has drain, source, and gate elements. The gate is the control element. Electrons usually flow through the channel from source to drain, but they can flow the other way too. The polarity of the channel material determines the polarity of bias applied to the gate.

The symbol for a junction FET (JFET), also shown in Fig. 1, has the "polarity" arrow in the gate element. The arrow points in-

Fig. 1 Schematic diagram symbols of the available types of transistors. The arrows on the elements of the symbols indicate the polarity of the design of the transistor and, consequently, the polarity of the bias voltage required for normal, or forward-bias, operation. For normal operation, the voltage applied to the gate of the N-channel JFET should be positive, and that applied to the P-channel type should be negative. Normal bias voltage applied to the gate of the N-channel enhancement-type MOSFET should be positive and that applied to the gate of the P-channel unit should be negative. The depletion type of MOSFET's operate with voltages of either polarity applied to the gate.

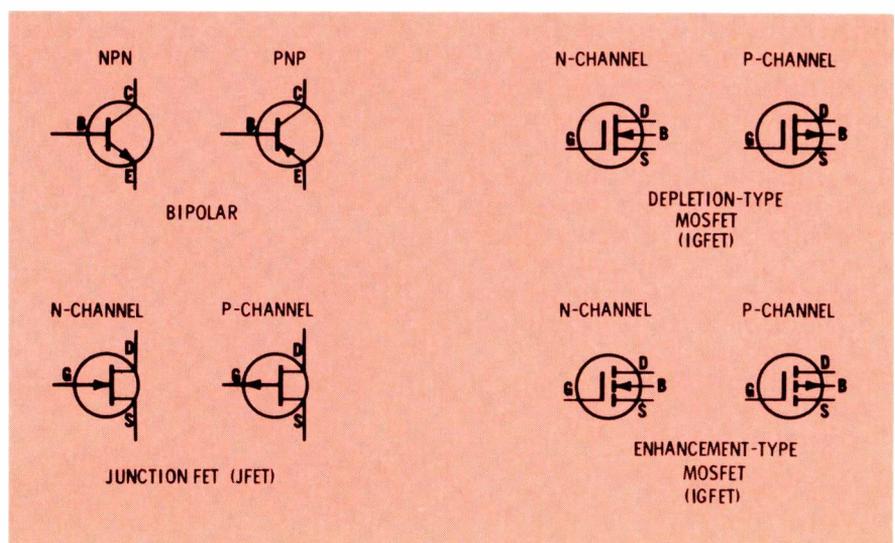


Table 1
Bipolar Transistor Ratings

	Voltage (max)	Current (max)	Power (max)
Small-Signal	50V	50mA	2W (?)
Low-Power	100V	1 A	10-20W
High-Power	above 100V	several amps	over 25W

Table 2
Typical Values Of I_{CBO}

Size	Germanium	Silicon
Small-Signal	0-5 μ A	0-2 μ A
Low-Power	up to 50 μ A	0-5 μ A
High-Power	up to 1000 μ A	up to 500 μ A

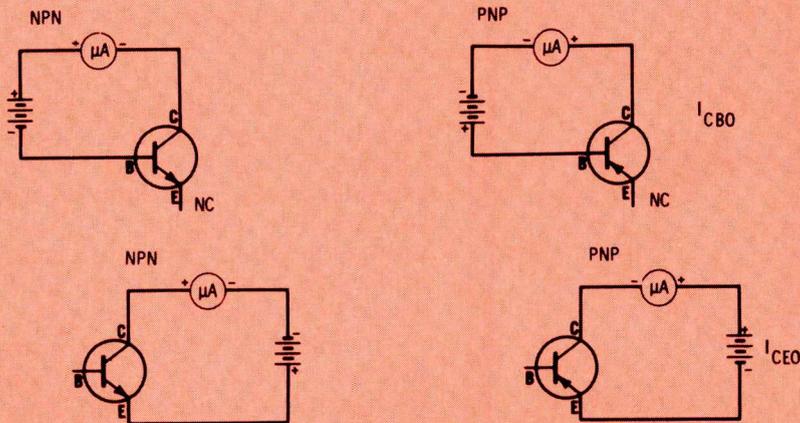


Table 3
Typical Values
Of DC Beta

Transistor	Beta
Small-Signal	2-50
Low-Power	10-100
High-Power	50-500

Fig. 2 Test setups for measuring the leakage of bipolar transistors. The setup for measuring I_{CES} (not shown) is the same as that for measuring I_{CEO} except that the base lead is connected to the emitter lead instead of "floating."

ward, toward the channel, to indicate an N-channel JFET. It points outward, away from the channel, for a P-channel.

Insulated-gate FETs (IGFET's) are available in two modes: depletion and enhancement. With an IGFET, the polarity of the bias voltage for the gate depends on this mode of operation as well as on the substrate or channel material. The caption of Fig. 1 explains the bias polarities for the types shown.

One kind of IGFET not shown has two gates. Both gates control the flow of electrons through the channel. In use, one gate is for DC control of the overall gain; the signal is applied to the other gate. For testing, the two gates are usually tied together, because if either one is bad, the transistor is useless.

Physical and electrical size

Transistors fall into three categories of size. Table 1 gives some general idea of the operating limits within these groupings. RF and IF transistors, and a few used in audio preamplifiers, are considered small-signal transistors.

Audio amplifiers, a very few RF transistors, and low-power output transistors fall into the second group. Audio output, current-switching, and a few powerful RF transistors belong in the third group. Remember these categories. You'll encounter them again and again.

Types Of Measurements

Testing any transistor involves two sets of measurements: a group of tests for leakage, and another group for gain. When you know these two qualities of any transistor, you know whether it will operate satisfactorily. These are the qualities transistor testers measure for you.

Leakage

When you talk about transistor leakage, the terms sound like you're reciting the alphabet. Leakage is a measure of backward, or reverse, current between two transistor elements. The capital letter "I" represents current. The letters for the elements are printed inferior (like c and b). If the inferior letters are capitals, leakage is DC; if lower

case, AC. Thus, DC leakage between collector and base is I_{CB} .

The operating condition of the remaining element during the test is denoted by a third inferior letter. Collector-base leakage in a bipolar transistor is measured with the emitter open. So the inferior capital letter o is added. When you see I_{CBO} , you know it means collector-base leakage current measured with the emitter open, or floating.

Fig. 2A shows the setup for measuring I_{CBO} in NPN and PNP bipolar transistors. The base and collector are biased opposite to their normal forward operating polarities. Silicon transistors should have no more than 1 or 2 microamps of leakage; germaniums can have 3, 4, or even 5 microamps and still operate properly. Table 2 lists typical limits of leakage.


You should easily figure out now that I_{CEO} indicates collector-emitter leakage, measured with the base open. Fig. 2B shows this test setup in which the collector and emitter are reverse biased, and the base has no connection. This type of leakage can be sev-

NOW... ONE PERMA-POWER BRITENER SOLVES
BOTH KINDS OF COLOR TV PICTURE PROBLEMS...

NEW COLOR BRITE HAS BOTH...

ISOLATION AND BOOST!

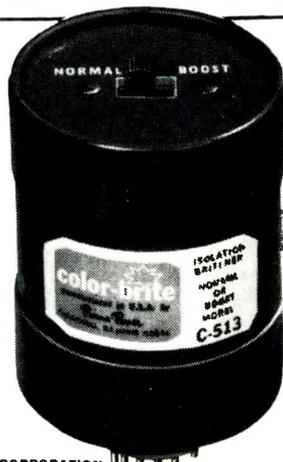This efficient new Britener corrects for cathode-to-filament shorts causing loss of black and white video drive . . . isolates the short, restores the black and white information necessary for color picture quality.



When needed later, sliding the boost switch raises electron emission, restores full contrast and sharpness to fading picture.



Model C-503
for round tubes
Model C-513
for rectangular tubes
Dealer Net \$7.75



PERMA POWER DIVISION OF
CHAMBERLAIN MANUFACTURING CORPORATION

5740 North Tripp Avenue, Chicago, Illinois 60646 (312) 539-7171

Circle 36 on literature card

eral microamps, even a milliamp or more in some power germaniums.

Not all testers have a configuration for measuring I_{CEO} . But it is handy for power transistors. The normal I_{CBO} of some is so high that it's difficult to tell when one is defective. The I_{CEO} test is more revealing.

One tester has an I_{CES} test. It's the same as measuring I_{CEO} except the base is shorted to the emitter. The amount of I_{CES} for any transistor should be less than its I_{CEO} . If not, the transistor is defective.

If you make all three leakage measurements, they should shape up like this: The I_{CES} must be lower than I_{CEO} , and the I_{CBO} must be lowest of all. Any other relationship reveals a faulty transistor.

Field-effect transistors (FET's) have their own letter symbols for leakage, but they're formed the same as those for bipolar transistors.

I_{GSS} is the most common FET leakage measurement. That's leakage from gate to source, with the drain element shorted to

source. The test setups are diagrammed in Fig. 3. A tiny bit of leakage is permissible in a junction FET. However, even slight leakage between gate and channel of an insulated-gate FET (IG-FET or MOSFET) makes the transistor not usable.

Testers that check FETs usually include a test labeled I_{DSS} . It's not leakage. It stands for current between drain and source when the gate is shorted to source for zero bias. It is sometimes called zero-bias drain current. Its greatest usefulness is in matching up two or more FETs. It reveals the conductance of their channels.

Gain

Once a transistor has passed its leakage tests, the next thing you measure is gain—the amount of amplification. The word for gain in bipolar transistors is **beta**.

Most testers measure DC beta. It's a ratio of collector current to base current. You may see it abbreviated H_{FE} in some transistor manuals. For all practical purposes in the testers you're likely

to buy for servicing, DC beta is about the same as AC beta. Only at RF and high audio frequencies is there a significant difference in the two figures, and the accuracy required for these applications is found usually only in lab instruments.

There are at least two steps in the measurement of beta. The first, a calibrate step, is necessary because most transistors have at least a slight leakage. A few testers have two such steps. To calibrate most testers, you turn the function knob (or push a button) to "BETA CAL" or "BETA SET" and then adjust the meter needle to full scale or to a special "calibrate" line. Do it the way the manufacturer's instructions say to. This first step (or first two) compensates for whatever leakage exists in the transistor. Beta wouldn't be accurate otherwise.

The second (or third) step is to switch to "READ BETA." The meter needle comes to rest somewhere on the scale. You read the value of beta directly.

There might be more than one scale on the meter face. If so the beta switch usually has high/low positions or X1 or X10 multipliers. Use the appropriate scale and/or multiplier.

Ranges of DC beta for bipolar transistors are listed in Table 3. Remember these figures are obtained by dividing the base-current change into the collector-current change. Specific values depend on bias level as well as on the individual transistor.

Instruments that test AC beta show figures in the same range as for DC beta. However, the lower-case letters are used in the inferior part of symbols which relate to AC. The symbol for AC beta is H_{fe} . That's how you tell which kind of beta is being measured.

Measuring the gain of FET's is a whole different ball game. They are not **current**-controlled. The current flowing in their channels is affected by the **voltage** on the gate. Therefore, gain is reported in terms of **mutual conductance**, as in tubes. The abbreviation or symbol is G_m .

The unit of measure is a **mho**. Measured this way, the gain figure is always fractional. The

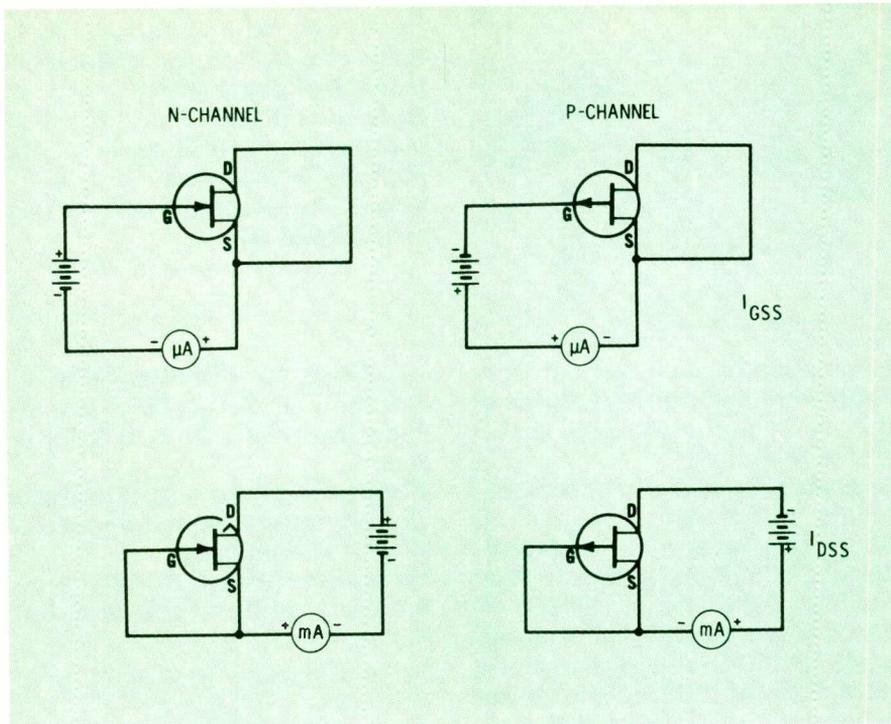


Fig. 3 Test setups for measuring the leakage (I_{GSS}) and drain current (I_{DSS}) of JFET's of both polarities. The same qualities of IGFET's are measured in the same way except that the base (substrate, or B) should be connected to the source during the tests.

practice, therefore, is to show G_m in millionths of a mho, or **micromhos**. Sometimes it's abbreviated mho or MHO.

The figure of G_m is arrived at by dividing a specific change in source-to-drain current by the change in gate voltage needed to achieve it.

For example, suppose a FET is letting 50 milliamps of source-drain current (I_{DS}) through its channel, with 5 volts bias between source and gate (V_{GS}). When bias is changed to 7 volts, source-drain current drops off to 10 milliamps. That's an I_{DS} change of 40 milliamps for a V_{GS} change of 2 volts. (Remember, it's the **change** you're interested in here.) Dividing 0.040 by 2, gain or G_m of this FET computes to 0.02 mhos, or 20,000 micromhos.

You calibrate the FET tester with a given set of operating conditions. You use a " G_m CAL" or " G_m SET" knob. Then you switch to "READ" and see where the new conditions make the needle pointer stop on the FET gain scale. If the meter has more than one G_m scale, use the one that corresponds to the function-knob position.

Diodes

You can check diodes with the leakage section of your transistor tester. Just set up for measuring ICBO and connect the diode to the collector and base test leads.

Connecting the diode across one polarity of voltage should produce high leakage in one direction and none in the other. If leakage is indicated in both directions, the diode is shorted or leaky. If no leakage is produced in either direction, the diode is open.

Curve Tracers

These instruments are relatively new to the transistor-testing field. So far only two have been introduced specifically for technicians, but at least one more is scheduled to be introduced soon.

The terminology defined previously also is used with curve tracers. Additionally, a curve tracer can display on your scope a whole family of I_B/I_C or V_G/I_D curves. There are special terms: "signature pattern," V_{ce} , avalanche point, and so on. But they are another story, which will be discussed later, when curve tracers are more popular. □

NOW A ONE STOP SHOPPING CENTER FOR YOUR AUTO RADIO AND 8 TRACK STEREO PARTS: AT FACTORY DISCOUNTS

WE ARE AUTHORIZED PARTS DISTRIBUTORS FOR:

DELCO	PANASONIC
BENDIX	KRACO
MOTOROLA	PHILIPS
LEAR JET	BELLE WOOD
TENNA	WARD
METRA	QUICKMOUNT
AUTOMATIC	AC SPEEDO
ONGUARD	CRAIG
MEMOREX	VERITAS
INLAND	CHAPMAN CARLOCK
DYNATRONICS	EV GAME
	STEREO LOCK MOUNTS

AND MANY OTHERS

Send Your Order With Part Number and Description of The Part To

Laran Electronics, Inc.

Dept. ES, 3768 Boston Road
Bronx, N. Y. 10469

Circle 37 on literature card

Clean low voltage contacts with



CO CONTACT CLEANER



It removes minute particles by evaporating them away. Perfect for watt-hour meters, recording instruments, calibration. Great for computer heads, precision test equipment, relays, switches. High purity

- Leaves no residue
- Degreases • Penetrates
- Harmless to plastic
- No flash or fire point.

FOR NAME OF YOUR NEAREST AUTHORIZED DISTRIBUTOR WRITE

CRC Chemicals
Electrical Products
Dresher, Pa. 19025
Division of C. J. Webb, Inc.

Circle 38 on literature card

productreport

Features and/or specifications listed are obtained from manufacturers' reports. For more information about any product listed, circle the associated number on the reader service card in this issue.

Sockets For Radio And TV

Product: Replacement sockets for various applications

Manufacturer: Workman Electronic Products

Function and/or Application: N/A

Features: Included are: octal sockets, novar sockets, printed-circuit sockets, tube sockets and miniature sockets in laminated and molded models; seven, nine and twelve pin plug sockets with



Nuvistor, transistor, silicon rectifier, crystal and general purpose sockets. High-voltage cups, sockets and lids to fit the high-voltage cups together with needed socket components such as mica collector and nylon screw insulators, power transistor mounting kits and sockets also have been added.

Specifications: N/A

Price: Prices of the replacement sockets start from \$.34 to \$2.93.

Circle 80 on literature card

Replacement Components

Product: SOLID-TUBE replacements

Manufacturer: Electronic Devices, Inc.

Function and/or Application: Replacements for color TV components

Features: Cool operating temperature, fast starting, longer voltage life, the prevention of circuit and socket damage and



elimination of one potential x-ray source are among the features of the solid-state SOLID-TUBES and renewal parts.

Specifications: The four replacements for vacuum tubes are: R-3A3 high voltage rectifier (45KV-5mA), \$9.95; R-3AT2 high voltage rectifier (45KV 5mA), \$9.95; R-2AV2 focus rectifier (9KV-5mA), \$4.45 and R-DW4 damper diode (6KV 250mA), \$6.95. The six renewal parts are: R-36M solid-state tripler (30KV 2.5mA), \$29.95; R-48M solid-state quadrupler (32KV 2.5mA), \$29.95; R-12C SOLID-STICK high-voltage rectifier (45KV 5mA), \$9.95; R-158 silicon focus rectifier cartridge (8KV 5mA), \$3.55; S-168 selenium focus rectifier cartridge (16.8KV 1mA), \$2.45 and S-1208 selenium boost diode cartridge (800V 2mA), \$1.60.

Circle 81 on literature card

Electronic Service Bag

Product: Tool bag for electronic personnel.

Manufacturer: K. Leather Products, Inc.

Function and/or Application: Bag for carrying tools, parts, meters and various electronic equipment.



Features: Lower section of bag has three sliding trays with divided compartments for parts and components. Bag can be equipped with an outside pouch for carrying service manuals,

books and paper. The tool bag is made of cowhide and is available in black or ginger color.

Specifications: The tool bag measures 17 inches X 11 1/2 inches X 5 1/4 inches.

Price: The electronic service bag sells for \$45.00.

Circle 82 on literature card


Dolly for Moving TV's

Product: TELE-CASTER TV dolly

Manufacturer: Becker & Fuhrmann

Function and/or Application: Permit movement by one man of TV and the cabinets

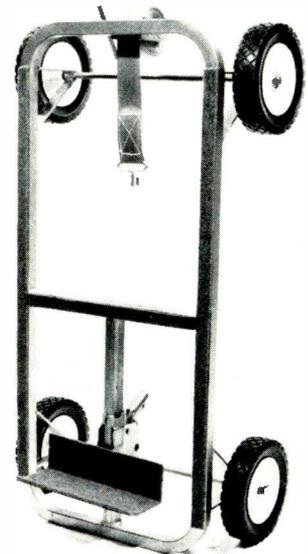Features: Four 8-inch steel wheels, rubber tires and ball



bearings permit easy movement up or down stairs or into a truck. The dolly can remain strapped to the cabinet during transportation.

Specifications: N/A

Price: The TELE-CASTER TV dolly sells for \$79.50.

Circle 83 on literature card

Moving?

Send your new address to:
ELECTRONIC SERVICING

Circulation

1014 Wyandotte St.
Kansas City, Missouri 64105

catalogs literature

Circle appropriate number on Reader Service Card.

ANTENNAS

100. *Blonder-Tongue, Inc.*—announces a booklet presenting the basic facts necessary to understand MATV systems. A Glossary of Terms is included for further understanding.
101. *Gavin Electronics, Inc.*—has introduced new full color literature for its Colorfinder outdoor color TV antenna line. The 6-page brochure describes all seven Gavin Colorfinder models. Featured are antennas with a reception range from metro to deep fringe.
102. *Jerrold Electronics Corp.*—Catalog S, titled "Systems and Products for TV Distribution," lists specifications of this manufacturer's complete line of antenna distribution products, including antennas and accessories, head-end equipment, distribution equipment and components, and installation aids.

AUDIO

103. *Arista Enterprises, Inc.*—announces their 58-page needle and cartridge catalog. The needle cross reference reportedly has up-to-date cross references of all major needle marketers, in addition to cross reference sections of phonograph manufacturers' needle and cartridge numbers.
104. *GC Electronics*—an updated line of exact replacement rubber drives and belts is detailed in the new Walsco cross-reference catalog. Included are a variety of phono and recorder drive wheels and pulleys, pinch rollers, round rubber belts, square cross-section rubber belts, spring belts and fabric drive belts, felt pressure pads, phono mounting "E"

and "C" clips in an assortment kit, motor mounting grommets, changer switches, and a kit of assorted phono drives and belts.

105. *G-V Controls*—Bulletin No. 4007 announces specifications, applications, line drawings, photographs and ordering information for the self dialing "hot-line" telephone unit.
106. *Jensen Manufacturing Div.*—has issued an 8-page catalog, No. 1090-E, which describes applications of 167 individual speaker models. Special automotive, communications, intercom and weathermaster speakers, plus a complete line of electronic musical instrument loudspeakers are featured.
107. *Shure Brothers*—has published a new catalog describing their line of microphone and circuitry products for broadcasting, recording, motion pictures, and professional sound reinforcement. Included are illustrations and technical specifications.

AUTO ELECTRONICS

108. *Littelfuse, Inc.*—has released a new 32-page, 1971 automotive replacement fuse guide for passenger autos, sports cars, trucks, and taxi cabs. Fuse descriptions and circuits they protect are included.
109. *Nortronics Co., Inc.*—announces a revised brochure describing the Model 5800 replacement head for a reported 90 per cent of all 8-track auto and home stereo players. A listing of players is offered by more than 70 different manufacturers in terms of model number or head part number.


CAPACITORS

110. *Cornell-Dubilier Electronics*—has issued an 80-page cross-reference, 1972 catalog for location of single, dual, triple, and quadruple section replacement electrolytics.
111. *Loral Distributor Products*—has made available a 24-

NOW SOLVED...

A tough problem* that has been with us since long before the transistor was invented!

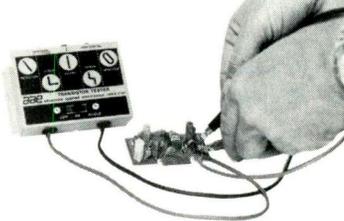*A way to check transistors, capacitors and resistors without unsoldering them from the circuit.



Saves time and tells you more than the old hazardous way of unsoldering components from the circuit. Connect the transistor tester to your scope and get rapid readings on transistors, diodes, capacitors, and resistors. Symbol on face of tester shows scope pattern for each good component.

\$29.95 Postage Paid

Send check or money order (no C.O.D.) to:

aae

advanced applied electronics
1000 South Main Street
Council Bluffs, Iowa 51501
712/328-8625

Circle 39 on literature card

page electrolytic capacitor replacement guide. The catalog features replacement products by the original manufacturers part number.

112. *Sprague Products Co.*—has announced a 40-page manual which lists original part numbers for each manufacturer, followed by ratings, recommended Sprague capacitor replacements, and list prices. More than 2,500 electrolytic capacitors are included.

COMPONENTS

113. *Bulow International*—announces a new parts list for spare-parts and replacement parts for several major European radio and electronics manufacturers. Components, transistors, diodes and mechanical parts are included.
114. *P. R. Mallory & Co., Inc.*—introduces a 64-page general catalog containing approximately 10,000 items. Included in the catalog are

batteries, capacitors, controls, resistors, semiconductors, switchers, and timers plus security systems, cassette recorders and cassette recording tapes.

115. *Precision Tuner Service*—announces a new tuner parts catalog, including a cross reference list of antenna coils and shafts for all makes of tuners.
116. *Workman Electronic Products, Inc.*—has released a 68-page 1972 catalog of replacement components for radio and television. Included are resistors, fusing devices, circuit breakers, sockets, convergence controls, electronic chemicals, audio cables, adapters for hi-fi and cassette type recorders battery holders and prototype kit components.

CONTROLS & SWITCHES

117. *Centralab Dist. Products*—introduces a chart which covers all Fastatch II rotary and push-pull action line switches. Diagrams are illustrated for each switch plus photographs for quick reference guide to replacement push-pull line switches.

KITS

118. *Heath Co.*—announces their 1972 Heathkit catalog, reportedly featuring over 350 kit projects. Projects for the home, the car, and workshop are included.

MARINE ELECTRONICS

119. *Raytheon Co.*—introduces the Webster antennas and seven new antennas designed for use with standard and single sideband marine radio-telephone and citizens band radios. The Webster antennas for VHF/FM radio are offered in 3 dB, 6 dB, and 9 dB models.

SECURITY ELECTRONICS

120. *Mountain West Alarm Supply Co.*—a 64-page catalog describes and offers over 350 intrusion and fire alarm products. Six-pages of Application Notes for alarm equipment also is included.

SEMICONDUCTORS

121. *Electronic Devices, Inc.*—announces a 4-page catalog on solid-state replacement and renewal parts for color TV receivers including solid-tubes, cartridges and multipliers. Solid-state solid-tube high-voltage rectifiers, focus rectifiers and damper diodes, silicon and selenium focus cartridges, diagrams showing dimensional drawings and socket connections for solid-tube solid-state replacements of vacuum tubes with maximum ratings for pulse rectifier service is also included.
122. *GTE Sylvania, Inc.*—introduces a 73-page illustrated catalog which provides information for more than 41,000 semiconductor devices, and outline drawings of the 124 components in the ECG semiconductor line. A complete alphanumeric cross-reference by type number is contained in the guide.
123. *General Electric Tube Products Dept.*—announces the 80-page ETRM 4311H, 1972 Entertainment Semiconductor Almanac. 33,000 cross references from JEDEC, or OEM part numbers, to GE part numbers for universal replacement semiconductors, selenium rectifiers for color TV, dual diodes and quartz crystals, are included.
124. *Motorola*—announces release of the HEP HMA-07 semiconductor cross-reference guide and catalog. Replacements are reportedly listed for over 30,000 semiconductor device numbers. A product catalog plus 168 new hobby, dealer and industrial M.R.O. devices are also included.
125. *RCA Distributor Products*—introduces a 72-page "SK Series Top-Of-The-Line Replacement Guide" (SPG-202L) which cross-references over 20,000 semiconductor device numbers. In addition a Solid State Quick Selection Replacement Chart (1L1367) listing 79

entertainment SK-Series devices is included.

126. *Semitronics Corp.*—has a new, revised "Transistor Rectifier, and Diode Interchangeability Guide" containing a list of over 100 basic types of semiconductors that can be used as substitutes for over 12,000 types.
127. *Sylvania Electric Products, Inc.*—a 73-page guide which provides replacement considerations, specifications and drawings of Sylvania semiconductor devices plus a listing of over 35,000 JEDEC types and manufacturers' part numbers.

SERVICE AIDS

128. *Chemtronics*—announces a new 12-page, 1971-1972 catalog of products, including: tuner sprays, circuit coolers, insulating sprays, contact and control sprays, lubricants, tape head cleaners and conditioners, electronic glues and cements, solder, and spray paints.
129. *Kester Solder*—has released an 8-page brochure presenting the company's full line of soldering products. Presented are: "44" resin core solder, acid-core solder, solid-wire, bar solder, TV-radio solder and Metal Mender.
130. *M. P. Odell Co.*—a new 12-page booklet entitled "The Whys and Hows of Cleaning Electronic Equipment" reviews some of the effects of dirt and air pollution on electronic equipment performance together with cleaning methods and systems.

SOLID-STATE

131. *Electronic Devices, Inc.*—offers a replacement guide on tubes and parts replaced by the EDI solid-state replacement components for color TV.
132. *International Rectifier*—64-page volume, JD-451, has been revised and lists information on diodes, zeners, capacitors, rectifiers and SCR's. There are a reported 4000 new transistor listings.

Specifications, characteristics, tables and wall charts are also included.

TECHNICAL PUBLICATIONS

133. *Howard W. Sams & Co., Inc.*—announces publication of a new 96-page 1972 Technical and Scientific Book Catalog. Described are over 800 hardbound and softbound books which cover “do-it-yourself” titles from the Audel Division, amateur radio publications, audio visual materials, instructor’s guides and student workbooks. Titles range from “ABC’s of Air Conditioning” to *Writer’s and Editor’s Technical Stylebook*”.
134. *Sencore, Inc.*—Speed Aligner Workshop Manual, Form No. 576P, provides 20 pages of detailed, step-by-step procedures for operation and application for Sencore Model SM 158 Speed Aligner sweep-marker generator.
135. *Sylvania Electric Products, Inc., Sylvania Electronic Components Div.*—has published the 14th edition of their technical manual, which includes mechanical and electrical ratings for receiving tubes, television picture tubes and solid-state devices.
136. *Tab Books*—has released their Spring 1972 catalog describing over 170 current and forthcoming books. The 20-page catalog covers: schematic/servicing manuals, broadcasting; basic technology; CATV; electric motors; electronic engineering; computer technology; reference; television, radio and electronics servicing; audio and hi-fi stereo; hobby and experiment; amateur radio; test instruments; appliance repair, and transistor technology.

TEST EQUIPMENT

137. *Dynascan Corp.*—announces a new 24-page 2-color catalog of B&K Precision Test Equipment. A total of 21 instruments are reportedly presented; from a Mutual

Conductance Tube Tester to a new DC to 10 MHz Triggered Sweep Oscilloscope.

138. *Eico*—has released a 32-page, 1972 catalog which features 12 new products in their test equipment line, plus a 7-page listing of authorized Eico dealers.
139. *Information Terminals*—has introduced a new brochure featuring the M-100 Tension Monitor, the M-200 Torque Tester and the M-300 Head and Guide Gage.
140. *Leader Instruments Corp.*—announces the 1972 Catalog of Leader Test Equipment. Test equipment included is the LBO-301 portable triggered-sweep oscilloscope, LSW-300 new solid-state post injection sweep/marker generator, and the LCG-384 miniportable, solid-state battery operated color-bar generator.
141. *Lectrotech, Inc.*—announces the 1972 catalog. “Precision Test Instruments for the Professional Technician”. It contains specifications and prices on sweep marker generator, oscilloscopes, vectorscopes, color bar generators and other test equipment.
142. *Tektronix, Inc.*—a 14-page test equipment booklet if available presenting the Telequipment line of oscilloscopes and a curve tracer. Single-trace, dual-trace, and dual-beam scopes are discussed. Also listed are Field Engineering offices where technical assistance may be obtained.
143. *Testline Instruments*—has issued a brochure for their new Model 101 Curve Tracer for checking transistors in- and out-of-circuit. All features, specifications, applications and warranty information are included.
144. *Speco Components Specialists, Inc.*—announces their 43-page, 1972 catalog of VOM multimeters and meters for TV technicians. Individual features and specifications for each instrument are included.

(Continued on page 66)

advertisers' index

Advance Applied Electronics Co.	63
Arrow Fastener Co. Inc.	36
B & K Division, Dynascan Corporation	23
Bussmann Mfg. Div. McGraw Edison Co.	7
CRC Electrical	61
Castle Television Tuner Service, Inc.	12, 66
Chapman Manufacturing	12
Chemtronics	43
Eico Electronic Instrument Co., Inc. ..	49
Enterprise Development Corp.	56
Essex International, Inc.	35
Heath Company	57
International Electronic Sales Corp. ..	54
Laran Electronics	61
Leader Instruments Corp.	1
Lectrotech, Inc.	10
Littelfuse, Inc.	Cover 4
Mallory Distributor Products Co.	11
Mercury Tuner Service	34
Precision Tuner Service	9
Perma Power	60
Quietrole Company	56
RCA Electronic Components ..	Cover 3, 5
RCA Parts & Accessories	47
RMS Electronics, Inc.	39
Rohn Manufacturing Co.	21
Howard W. Sams & Co., Inc.	31
Seco Electronics Corp.	55
Sencore Inc.	29
Sprague Products Company	3
GTE Sylvania Elec. Components	13
TV Tech Aid	35
Telematic Div. of UXL Corp.	53
Tuner Service Corporation	Cover 2
Workman Electronic Products, Inc. ...	34
Xcelite, Inc.	20
Zenith Radio Corporation	25

The Tuner People




OVERHAUL SERVICE — All makes VHF or UHF tuner (1960 or later) **\$9.95**
Overhaul includes parts, except tubes and transistors.
Dismantle tandem UHF and VHF tuners
Remove all accessories.

CUSTOM EXCHANGE REPLACEMENTS
When our inspection reveals tuner is unfit for overhaul, we offer a custom replacement (Replacements are new or rebuilt.)

EXACT REPLACEMENTS
Castle replacements made to fit exactly
Purchase outright . . . no exchange **\$15.95**

UNIVERSAL REPLACEMENTS
Prefer to do it yourself?

STOCK No.	HEATERS	SHAFT		I.F. Snd.	PRICE
		Min.*	Max.*		
CR6P	Parallel 6.3v	1 3/4"	3"	41.25	8.95
CR7S	Series 600mA	1 3/4"	3"	41.25	9.50
CR9S	Series 450mA	1 3/4"	3"	41.25	9.50
CR6XL	Parallel 6.3v	2 1/2"	12"	41.25	10.45
CR7XL	Series 600mA	2 1/2"	12"	41.25	11.00
CR9XL	Series 450mA	2 1/2"	12"	41.25	11.00

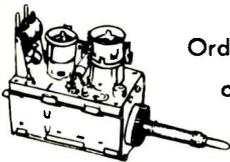

Order Now . . .
or write for more
information.

CASTLE TV TUNER

MAIN PLANT: • Ph. 312-561-6354
5701 N. Western Ave., Chicago, Ill. 60645

EAST: • Ph. 212-846-5300
130-07 89th Rd., Richmond Hill, N.Y. 11418

Circle 44 on literature card

TOOLS

145. *Chapman Manufacturing Co.*—offers a pamphlet containing their line of tools and tool kits. Kit No. 6320, the Midget Ratchet is featured along with other available tool kits.

146. *Jensen Tools and Alloys*—has announced a new catalog No. 470, "Tools for Electronic Assembly and Precision Mechanics." The

72-page handbook-size catalog contains over 1,700 individually available items.

147. *Janel, Inc.*—announces a three-color catalog on precision hand tools used primarily in miniature and micro-miniature electronic assembly and production applications.

148. *Xcelite, Inc.*—Bulletin N770 describes this company's three new socket wrench and ratchet screwdriver sets.

TRANSFORMERS/COILS

149. *J.W. Miller Co.*—announces a new 92-page radio and TV replacement coil cross reference guide for known domestic and foreign color and black-and-white TV sets, home and car radios. Over 22,000 replacement coils for 327 manufacturers names reportedly are listed.

TUNER REPAIR

150. *PTS Electronics, Inc.*—62-page catalog with over 600 exact-replacement tuners are listed under their original manufacturer number for ease of exchange. A replacement guide for antenna coils and shafts is also provided.

TV ACCESSORIES

151. *Telematic*—introduces a 14-page catalog featuring CRT brighteners and reference charts, a complete line of test jig accessories and a cross reference of color set manufacturers to Telematic Adapters and convergence loads.

TV PICTURE TUBES

152. *GTE Sylvania*—50-page brochure which describes characteristics of over 900 television picture tubes, plus data on interchangeability information and tips on installation and handling of TV picture tubes.

153. *GTE Sylvania, Inc.*—has published an interchangeability guide listing 191 commonly used color TV picture tubes which can be replaced with 19 GTE Sylvania Color Bright 85® □

The MARKETPLACE

This classified section is available to electronic technicians and owners or managers of service shops who have for sale surplus supplies and equipment or who are seeking employment or recruiting employees.

Advertising Rates
in the Classified
Section are:

• 25 cents per word
(minimum \$3.00)

• "Blind" ads \$2.00
additional

• All letters capitalized—
35 cents per word

Each ad insertion must be accompanied by a check for the full cost of the ad.

Deadline for acceptance is 30 days prior to the date of the issue in which the ad is to be published.

This classified section is not open to the regular paid product advertising of manufacturers.

FOR SALE

Obsolete radio and TV tubes. For free price list and types available send stamped, self addressed envelope to Delux Electronics, 156 Robert St., Westport, Mass. 02790 4-72-1t

FOR SALE:

- HEAT GUNS**, Used, Good Cond.
 - 5amp-200°/300° F., 8amp-250°/350° F., 10amp-300°/500° F.
New price; \$47.50, Our price; \$12.50 plus postage.
 - 14amp-500°/750° F., 20amp-750°/1000° F.,
New price; \$57.50, Our price; \$16.50 plus postage.
 - POLARAD MULTIBAND SPECTRUM ANALYZERS**, Mod. SA-84 Freq. 10MC to 40.88GC. Excellent cond. Calibrated.
New price; \$6,930.00, Our price; \$1,250.00. post. pre-pd.
 - TEKTRONIX TYPE C-A DUAL-TRACE PLUG-INS**, Excellent cond. Calibrated.
New price; \$460.00, Our price; \$200.00. post. pre-pd.
 - FLUKE POWER SUPPLIES**, Mod. 407D.
 - Main output voltage; 0-55VDC
 - Main output current; 0-300ma
 - Bias output; 0 to -250VDC
 - AC outputs (2) 6.3v at 5amps
Brand new units in original cartons.
New price; \$450.00, Our price; 250.00. post. pre-pd.
 - PORTABLE WHEATSTONE BRIDGE & DECADE BOXES**, L&N Mod. 5340A 0.1ohms to 11.5 Meg ohms. New cond. With Galvanometer.
New price; \$292.00, Our price; \$85.00. plus postage.
- Many other items in stock. Rentals also available.
Complete listing of Equip. available upon request.
We also maintain a complete Calibration & Repair facility for Test Equipment; Write for information.
IMTRONIX INC. 305 N. Broadway, Fresno, Calif. 93701 ph. (209)485-2741
For Sale—Perfect condition—Sweep Circuit Analyzer, Sencore Model SS137, \$45.00. Prepaid. Send check to Walter L. Rochow, 19 Canterbury Rd, Asheville, N.C. 28805. 4-72-1t
For Sale: Sams Photofacts. For information call 1-203-423-6937 after 6pm or write Paul Barbeau, R.R. #1, Storrs, Conn. 06268. 4-72-1t

EQUIPMENT WANTED

RCA WR99A crystal-calibrated TV marker generator. Michael Brady, 461 N. Harper Ave., Los Angeles, Calif. 90048 4-72-1t

"WANTED, CRT rebuilding plant, only new, write: A. Icaza, P.O. Box 806, New York, NY 10459" 4-72-1t

SAMS PHOTOFACT

Supplement to 1972 ANNUAL INDEX

Covers PHOTOFACT Set Numbers 1218 thru 1235 and Specialized Volumes AR-109 thru AR-116, CB-37, CB-38, MHF-21 thru MHF-23, TR-90 thru TR-95, TSM-129 thru TSM-131 Released.

JANUARY thru MARCH 1972

This Supplement is your Index to new models covered by PHOTOFACT since December 1971. For model coverage prior to this date see the 1972 PHOTOFACT Annual Index. Use this Supplement with the Annual Index—together they are your complete Index to PHOTOFACT coverage of over 88,000 models.



A		B		C		D		E		F		G		H	
Set No.	Folder No.	Set No.	Folder No.	Set No.	Folder No.	Set No.	Folder No.	Set No.	Folder No.	Set No.	Folder No.	Set No.	Folder No.	Set No.	Folder No.
ADmiral		ALLIANCE		CATALINA		DUMONT-Cont.		EMERSON-Cont.		GENERAL ELECTRIC-Cont.					
Admiral Corp.-National Service Div., P.O. Box 845, Bloomington, Illinois 61701		The Alliance Mfg. Co., Inc. 22790 Lake Park Blvd. Alliance, Ohio 44601		White Stores, Inc. Wichita Falls, Texas 60639		Ch. 30K18-1B 1224-POM		Ch. 30K17-1A 1218-POM		WM201HGR-4/202HYV-4 (Ch. H-4) 1223-2					
Chassis K16-1A/-2A 1218-POM		C-225 (Antenna Rotator) 1211-SED		Ch. 122-752F 1229-2		Ch. 32K18-1B 1224-POM		Ch. 30K18-1A 1218-POM		WM205HW-4/206HWD-4 (Ch. H-4) 1223-2					
Chassis K1663-33 (Similar to Chassis) 1204-1		ALLIED		Ch. 122-2815A 1234		Ch. 120976A (PCB1211-4) 1102-1		Ch. 31K18-1A 1218-POM		WM225HW-4 (Ch. H-4) 1223-2					
Chassis 1K70-B (Runs thru 16) (PCB1211-4) 1083-1		Allied Radio Shack 2617 West Seventh Street Fort Worth, Texas 76107		Ch. 122-2820A 1234-1		Ch. 120984A (PCB1211-4) 1102-1		Ch. 32K1673-32 1218-POM		WM257NWD-2 (Ch. N-2) 1219-1					
Chassis 1K8-1A/-2A 1218-POM		14A50502 MHF-22		Ch. 122-2845A 1234-1				Ch. 32K1686-4 1218-POM		WM264CWD-2 (Ch. C-2) 1231-2					
Chassis 1K1697-9/-10 (Similar to Chassis) 1204-1		1450 (14A50502) MHF-22		Ch. 122-2850A 1234-1				Ch. 32K1687-2 1218-POM		WM270CWD-2 (Ch. C-2) 1231-2					
Chassis 12K2084-6 1218-POM		ALLIS CHALMERS (See Auto Radio Listing)		Ch. 122-2855A 1234-1						WM274CWD-2 (Ch. C-2) 1231-2					
Chassis 12K2086-2 1218-POM		AMBASSADOR (Also See Recorder Listing)		Ch. 122-2865A 1234-1						WM277CWD-2 (Ch. C-2) 1231-2					
Chassis 12K2088-1, -2 1218-POM		Allied Purchasing Corp. 401 Fifth Avenue New York, N. Y. 10016		Ch. 122-2865A 1234-1						WM279CCT-2/279CEA-2 (Ch. C-2) 1231-2					
Chassis 13K2089-1 1218-POM		AM7112WD (Late Prod.) 1225-1		Ch. 122-2885A 1234-1						WM381CWD-2/382CWD-2/385CWD-2 (Ch. C-2) 1231-2					
Chassis 15K1673-33 1218-POM		AM7116WD 1229-1		Ch. 122-2890A 1234-1						Ch. C-2 1231-2					
Chassis 15K1680-1 1218-POM		AMPEX (See Auto Radio and Recorder Listings)								Ch. CP1-1, -6, -7, -8, -11, -12, -13 1219-5, 1221-4					
Chassis 15K1687-1, -2 1218-POM		ARVIN (Also See Recorder Listing)								Ch. H-4 1223-2					
Chassis 15K1697-9/-10 (Similar to Chassis) 1068-1		Arvin Industries Inc. 1531 Thirteenth Street Columbus, Indiana 47201								Ch. L-2 1231-2					
Chassis 15K1700-1 1218-POM		30R56-12 (Ch. 1.0071) 1212-4								Ch. N-2 1219-1					
Chassis 15K1700-2 1218-POM		40R56-12 (Ch. 1.0071) 1212-4								Ch. PA40-1, -2, -3, -4 1219-5, 1221-4					
Chassis 15K1700-3 1218-POM		80M35-11 (Ch. 1.00791) 1230-4								Ch. R-1 1220-2					
Chassis 15K1700-4 1218-POM		80M35-16 (Ch. 1.00791) 1230-4								Ch. T-6 1218-POM					
Chassis 15K1700-5 1218-POM		Ch. 1.00711 1212-4								Ch. TU240-8, -9, -10, -11, -12, -13 1221-4					
Chassis 15K1700-6 1218-POM		Ch. 1.00721 1212-4								Ch. TU540-1, -11 1219-5					
Chassis 15K1700-7 1218-POM		Ch. 1.00791 1230-4								Ch. W-1 1221-1					
Chassis 15K1700-8 1218-POM		ASTRO LINE (See Auto Radio Listing)													
Chassis 15K1700-9 1218-POM		BENNETT													
Chassis 15K1700-10 1218-POM		Bennett Laboratories, Inc. 5800 Christie Avenue Emeryville, California 94608 (Address Change)													
Chassis 15K1700-11 1218-POM		BLONDER-TONGUE													
Chassis 15K1700-12 1218-POM		Blonder-Tongue Laboratories 9 Alling Street Newark 2, New Jersey													
Chassis 15K1700-13 1218-POM		DA-4Y (1425) (TV Distribution Amp) 1232-SED													
Chassis 15K1700-14 1218-POM		Suburban 4542 (UHF/VHF Amp) 1232-SED													
Chassis 15K1700-15 1218-POM		BOMAN ASTROSONIX (See Auto Radio and Recorder Listings)													
Chassis 15K1700-16 1218-POM		Caravelle CB-38													
Chassis 15K1700-17 1218-POM		CCT-3 CB-37													
Chassis 15K1700-18 1218-POM		CONRIG CB-38													
Chassis 15K1700-19 1218-POM		CRAIG (See Recorder Listing)													
Chassis 15K1700-20 1218-POM		CROWN RADIO (See Recorder Listing)													
Chassis 15K1700-21 1218-POM		CURTIS MATHES													
Chassis 15K1700-22 1218-POM		Curtis Mathes Mfg. Co. P.O. Box 5610 Dallas, Texas 75222													
Chassis 15K1700-23 1218-POM		Ch. 47-2 1230-5													
Chassis 15K1700-24 1218-POM		DELCO (See Auto Radio and Recorder Listings)													
Chassis 15K1700-25 1218-POM		DODGE (See Auto Radio Listing)													
Chassis 15K1700-26 1218-POM		DUMONT													
Chassis 15K1700-27 1218-POM		DuMont Radio & Television 14th & Coles Streets Jersey City, N. J. 07302													
Chassis 15K1700-28 1218-POM		19DP01 (Ch. 30K18-1B) 1224-POM													
Chassis 15K1700-29 1218-POM		19DP02W (Ch. 31K18-1B) 1224-POM													
Chassis 15K1700-30 1218-POM		25DC04W/06S/07M (Ch. 12K16-1) 1224-POM													
Chassis 15K1700-31 1218-POM		59T01WN (Ch. 120976A) (PCB1211-4) 1102-1													
Chassis 15K1700-32 1218-POM		59T02WN (Ch. 120984A) (PCB1211-4) 1102-1													
Chassis 15K1700-33 1218-POM															

NOTE: * Denotes Television Receiver. * Denotes Color Television Receiver. AOR Denotes Available On Request. AR Denotes Auto Radio Series Volume. CB Denotes CB Radio Series Volume. HTP Denotes Home Tape Player Series Volume. MHF Denotes Modular Hi-Fi Series Volume. PCB Denotes Production Change Bulletin. POM Denotes Bonus Schematic in Photofact-of-the-Month Package—Unavailable After Month of Issue. SED Denotes Special Equipment Data. TR Denotes Tape Recorder Series Volume. TSM Denotes Transistor Radio Series Volume.

K

KAY-TOWNES
 Key-Townes Antenna
 Chapter
 Turner Chapel Road
 Rome, Georgia 30161

AB-4000/4100 (VHF/FM) 1225-SED
 AB-4200 (VHF/UHF-FM) 1225-SED
 Distribution Amp. 1224-SED
 AB-4400 (VHF/UHF) 1224-SED
 Distribution Amp. 1223-SED
 AB-4700 (VHF/UHF/FM) 1223-SED
 Distribution Amp. 1223-SED
 AB-4800 (VHF/FM) 1223-SED
 Distribution Amp. 1223-SED
 AB-4900 (VHF/FM) 1223-SED
 Amp. 1225-SED
 AB-5000 (VHF/UHF/FM) 1225-SED
 AB-5100 (Antenna-Mounted) 1225-SED
 Amp. 1224-SED
 AB-5200 (VHF/UHF/FM) 1225-SED
 Amp. 1225-SED
 AB-5300 (VHF/UHF/FM) 1229-SED
 Amp. 1229-SED
 AB-5400 (VHF/UHF/FM) 1229-SED
 Distribution Amp. 1229-SED
 AB-5800 (VHF/UHF/FM) 1229-SED
 Distribution Amp. 1229-SED
 AB-6000 (VHF/FM) 1223-SED
 Mounted Amp. 1223-SED
 AB-6100/6200/6300 (VHF/FM Amp) 1229-SED
 AB-7100 (VHF Amp) 1225-SED
 AB-7200 (UHF Amp) 1228-SED
 AB-7800 (VHF/UHF/FM) 1228-SED
 Amp. 1228-SED
 AB-8000 (VHF/FM Antenna) 1223-SED
 Mounted Amp. 1223-SED
 AB-8200 (VHF/UHF/FM) 1223-SED
 Antenna Mounted
 AB-8700 (VHF/FM Amp) 1228-SED
 AB-8800 (VHF/FM Amp) 1228-SED
 AB-9100 (VHF Distribution) 1226-SED
 Amp. 1226-SED
 AB-9400 (VHF/UHF/FM) 1226-SED
 Distribution Amp. 1226-SED

L

LAFAYETTE
 Lafayette Radio Electronics
 111 Jericho Turnpike
 Syosset, L.I. New York 11791

Dyna-Cam 3A (99-31940L) CB-37
 Dyna-Cam 12a (99-32484) CB-38
 HB-23A (99-32351WX) CB-38
 LR-100 (99-02214WX) MHF-23
 Telstar 558-25 (99-32377WX) CB-37
 99-02214WX MHF-23
 99-31940L CB-37
 99-32351WX CB-38
 99-32377WX CB-37
 99-32484 CB-38

LLOYD'S
 (See Recorder Listing)

M

MACK TRUCK
 (See Auto Radio Listing)

MAGNAVOX
 (Also See Recorder Listing)
 The Magnavox Company
 Buena Road
 Fort Wayne, Indiana 46803

1P9822 MHF-21
 1R1707 1212-5
 1R1729 1229-5
 1R1736 1216-5
 Chassis A510-02-AA, BA (Similar to Chassis) 923-5
 Chassis A511-01-BA (Similar to Page 57) MHF-21
 Chassis A512-01-AA MHF-21
 Chassis A512-02-AA (Similar to Page 5) MHF-21
 Chassis 1952-06 1218-POM
 Series 1218-POM
 Chassis 1952-10 1218-POM
 Series 1218-POM
 Chassis 1952-11 1218-POM
 Series 1218-POM
 Chassis 1952-12 1218-POM
 Series 1218-POM
 Chassis 1952-13 1218-POM
 Series 1218-POM
 Chassis 1957-01-AA, BA, CA, DA, EA, FA 1218-POM
 Chassis 1957-02-AA, BA, CA, DA, EA, FA 1218-POM
 Chassis 1960 Series 1230-POM

MEDALLION
 (See Auto Radio and Recorder Listings)

MERCURY
 (See Auto Radio and Recorder Listings)

MGA
 Mitsubishi International Corp.
 7045 North Ridgeway Ave.
 Lincolnwood, Illinois 60465

BB-090 1218-POM
 BB-130 1222-2
 BB-131 1218-POM
 CH-121 1218-POM
 CH-141 1218-POM
 CH-160 1218-POM
 CH-190/191 1218-POM
 CS-165 1218-POM
 CS-195 1218-POM

MIDLAND
 (Also See Recorder Listing)
 Midland International Corp.
 For CB Models
 Midland Communications Co.
 P.O. Box 19032
 Kansas City, Mo. 64141
 For All Other Models
 P.O. Box 1903
 Kansas City, Mo. 64141

13-868 CB-37
 13-874 CB-38
 15-1128 1232-1

MORSE ELECTRO PRODUCTS
 (Also See Recorder Listing)
 Morse Electro Products Corp.
 101-10 Foster Avenue
 Brooklyn, New York 11236

T-9 TSM-131
 T-16 TSM-130
 T-17 TSM-131
 T-107 TSM-131
 T-108 MHF-23
 T-109 MHF-23
 T-100 MHF-21
 Ch. 744 MHF-21
 Ch. 263 (Similar to Chassis) 1207-3
 Ch. 31H 1222-4
 Ch. 41, 43 1224-4
 Ch. 103 1217-4
 Ch. 76K 1214-4
 Ch. 77K 1221-5

MOTOROLA
 (Also See Auto Radio and Recorder Listings)
 Motorola, Inc.
 9401 Grand Avenue
 Franklin Park, Ill. 60131

BP309PH (Ch. C12T5-465T) 1091-2
 BP318HW (Ch. E12T5-465T) 1091-2
 BP403HW (Ch. C12T5-465T) 1091-2
 BP416HW (Ch. C12T5-465T) 1091-2
 BP419HW (Ch. C12T5-465T) 1091-2
 BP422HW (Ch. C12T5-465T) 1091-2
 BP1001HW (Ch. C12T5-465T) 1091-2

N

NORELCO
 (See Recorder Listing)

OLDSMOBILE
 (See Auto Radio and Recorder Listings)

OLYMPIC
 Olympic Int'l. Ltd.
 Service Dept.
 85-99 Turnpike
 Glendale, N.Y. 11227

6P71 1221-2
 6P94 1219-2

OPTEL
 (See Auto Radio Listing)

P

PACKARD BELL
 (Also See Recorder Listing)
 Teledyne Packard Bell
 Kansas City, Mo. 64141
 12333 West Olympic Blvd.
 Los Angeles, Calif. 90064

RPC-234 (Ch. 18HF6) 1215-4
 RPC-238 (Ch. 18HF6) 1215-4
 RPC-252 (Ch. 18HF7) 1215-4
 RPC-311/312/314 (Ch. 36HF2) 1204-4
 RPC-313 (Ch. 36HF2) 1204-4
 RPC-344/346/348 (Ch. 18HF6) 1215-4
 RPC-352 (Ch. 18HF7) 1215-4
 RPCT-344/346 (Ch. 18HF6, TPAK-25) For Radio Ch. 1215-4
 For Tape Player (Similar to Page 80) MTP-1
 RPS-09 (Ch. 18HF7) 1215-4
 RPS-105/107 (Ch. 36HF2) (Similar to Chassis) 1204-4
 RTS-115 (Ch. 36HF2, TRA-1A) For Radio Chassis 1204-4
 Ch. 744 MHF-21
 Ch. 263 (Similar to Chassis) 1207-3
 Ch. 31H 1222-4
 Ch. 41, 43 1224-4
 Ch. 103 1217-4
 Ch. 76K 1214-4
 Ch. 77K 1221-5

PANASONIC
 (Also See Auto Radio and Recorder Listings)
 Matsushita Electric Corp. of America
 Panasonic Service & Parts Div.
 10-16 44th Drive
 Long Island City, N.Y. 11101

CT-392, C 1218-POM
 CT-394, C 1218-POM
 CT-395VR 1230-POM
 CT-991P (Late Prod.) 1228-2
 RE-6451, C 1211-5
 RE-700, C 1217-4
 RS-8205, C MHF-23
 SG-635 1228-2
 TR-003, C 1224-POM
 TR-005, C 1224-POM
 TR-425B, C 1231-5
 TR-465R 1230-POM
 TR-522 1230-POM
 TR-539 1224-POM

PEARCE-SIMPSON
 Pearce-Simpson Inc.
 4701 N.W. 77th Ave.
 Miami, Florida 33152

Cougar 23 CB-38

PENNEY-PENNCREST
 (Also See Recorder Listing)
 J. C. Penney Co., Inc.
 1301 Lincolnway of America
 New York, N.Y. 10019

CR201 (TV Remote Control Unit) 1225-2A
 CT202 (TV Remote Control Unit) 1225-2A
 685-4874/4828 1230-POM
 2341 1230-POM
 2852 1230-POM
 2853 1225-2
 2855, A 1223-3
 2856 1218-POM
 2857 1230-POM
 2861/62/63 1221-3
 2871, A 1218-POM
 2872 1230-POM
 2885A (PCB 1229-4) 1130-2
 2886 1224-2
 2887, A 1218-1
 3840 TSM-129
 3850 TSM-130
 4356A/57A/58A 1226-1
 4392A 1226-1
 4396A 1224-5
 6825, A MHF-21

PHILCO-FORD
 Philco-Ford Corporation
 Tigra & 'C' Streets
 Philadelphia, Pa. 19134

8522AWH (Ch. 20P24) (PCB-1211-4) 1148-1
 8532AWA (Ch. 20P24) (PCB-1211-4) 1148-1
 *C7301AWA (Ch. 225T80) 1235-2
 *C7320AWA (Ch. 225T80) 1235-2
 *C7340AWA (Ch. 225T80) 1235-2
 *C7345AWA (Ch. 225T80) 1235-2
 *C7360AFW/61AMA (Ch. 225T80) 1235-2
 *C7382APC, AMD (Ch. 225T80) 1235-2
 *C7370AWA/72ALP (Ch. 225T80) 1235-2
 *C7382ALK (Ch. 215T91P) 1235-2
 *C8180AWA/82ALK (TV Ch. Only 225T81) 1235-2
 *C9440AWA (Ch. 225T80) 1235-2
 *C9450AWA/52APC (Ch. 225T80) 1235-2
 H540UWA (Ch. U1505T) 1232-5
 H572UDK (Ch. U1505T) 1232-5
 Ch. U1505T 1232-5
 Ch. 20P24 (Run 7) (PCB 1211-4) 1148-1
 Ch. 215T91P 1235-2
 Ch. 225T80/81 1235-2

PIONEER
 U.S. Pioneer Electronics Corporation
 178 Commerce Road
 Carlstadt, New Jersey 07072

SX-440 MHF-22
 SX-990 MHF-21

PLYMOUTH
 (See Auto Radio Listing)

PONTIAC
 (See Auto Radio and Recorder Listings)

R

RCA
 RCA Sales Corporation
 600 North Sherman Drive
 Indianapolis, Indiana 46201

AP191W (Ch. KC517E) (PCB 1216-4) 1061-1
 AP301W (Ch. KC517A) (PCB 1232-4) 1115-2
 AQ098E (Ch. KC517E) 1224-4
 AQ122W (Ch. KC518BA) 1227-2
 AQ127E (Ch. KC518BA) 1227-2
 AQ186F, WEN (Ch. KC517E, R, AB) (PCB 1216-4) 1061-1
 AQ191W (Ch. KC517E, P, AA) (PCB 1216-4) 1061-1
 AQ194W (Ch. KC517E, P, AA) (PCB 1216-4) 1061-1
 AQ198WEN/200W (Ch. KC5172D, E) (Similar to Chassis) 1198-3
 AQ201WEN (Ch. KC5174H, L, M) (PCB 1232-4) 1115-2
 AQ325E, H (Ch. CTC51B) (Similar to Chassis) 1209-3
 EQ446EEN (Ch. CTC52A) (Similar to Chassis) 1211-3
 EQ484EEN (Ch. CTC55XT) (Similar to Chassis) 1203-2
 EQ475W (Ch. CTC59XA) 1212-POM
 EQ475WR (Ch. CTC59XB) 1212-POM
 EQ485W (Ch. CTC50XR) 1226-2
 EQ505W/5631 (Ch. CTC50XR) 1226-2
 HP908L/910D, S (Ch. CTC39XP, RC, 1239D, RS-253F) For TV Chassis 1126-3
 For Radio/Amp. Chassis (Similar to) 1169-6
 JPI92W (Ch. KC5171T, AC) (PCB 1216-4) 1061-1
 RYM694E TSM-130
 R25476D 1217-5
 V51001W (Ch. RS-265D) 1207-4
 V51200W (See Page 75) MHF-20
 VZ303P (Ch. RS-270B) 1208-4
 Ch. CTC50XR 1226-2
 Ch. CTC51B (Similar to Chassis) 1209-3
 Ch. CTC55XT (Similar to Chassis) 1203-2
 Ch. CTC59XA, XB 1212-POM
 Ch. CTC59XB, Y, Z, E, F, P, R, T (PCB 1216-4) 1061-1
 Ch. KC5173K, L, N, P 1061-1
 Ch. KC5174H, L, M (PCB 1232-4) 1115-2
 Ch. KC5176X 1224-4
 Ch. KC5180A 1227-2
 Ch. RC-3008A 1224-1A

RANGER
 (See Auto Radio and Recorder Listings)

RAYMER
 Raymer Electronics, Inc.
 14660 Raymer Street
 Van Nuys, California 91405

LTS-1 (Speaker Line Tester) 1217-SED
 795 (10 Watt Amplifier) 1217-SED

REALISTIC
 (Also See Recorder Listing)
 Allison Radio Shack Corporation
 2727 West 7th Street
 Fort Worth, Texas 76107

TRC-100B (21-134) CB-38
 TRC-100C (21-134) CB-38

REGENCY
 Regency Electronics, Inc.
 7900 Pendleton Pike
 Indianapolis, Indiana 46226

CB-291 CB-37
 Sprint-23 (CB-291) CB-37

ROBERTS
 (See Recorder Listing)

ROBYN COMPANY
 P.O. Box 478
 Rockford, Michigan 49341

TR-123C CB-38

S

SAAB
 (See Auto Radio Listing)

SANYO
 Sanyo Electric Inc.
 1200 West Walnut Street

Set No.	Folder No.	Model No.
ZENITH—Cont.		
★C910W8 (Ch. 18CC29)	1225-3	
★C914W8 (Ch. 18CC30)	1225-3	
★C4025W5 (Ch. 19CC19)	1215-3	
(Similar to Chassis)		
★C4030W5 (Ch. 19CC19)	1215-3	
(Similar to Chassis)		
★C4730X (Ch. 25CC25)	1212-POM	
★C4787P/88DE/89P (Ch. 25CC35)	1212-POM	
★C5722W1 (Ch. 14CC16)	1233-3	
★C5722W7 (Ch. 14CC16Z)	1233-3	
★C6030W4 (Ch. 19CC19, S-86335) (Similar to Chassis)	1215-3	
★C6730X, X11 (Ch. 25CC25)	1212-POM	
★C6787P/88DE (Ch. 25CC35)	1212-POM	
★C8775P (TV Ch. Only 25CC55)	1212-POM	
Royal 7312 (Ch. 23-1, 24-1)	TSM-131	
R7312 (Ch. 23-1, 24-1)	TSM-131	
★S-87861 (TV Remote Control Unit)	1233-3A	
★S-87941 (TV Remote Control Unit)	1233-3A	
★T2616W, W1, W2, W3 (Ch. 12CB12X)	1212-POM	
★T2824W1, W3 (Ch. 14CC14)	1233-3	
★T2824W7, W9 (Ch. 14CC14Z)	1233-3	
★T2828W1, W3 (Ch. 14CC16)	1233-3	
★T2828W8 (Ch. 14CC16Z)	1233-3	
★T2833W8 (Ch. 18CC30)	1225-3	
★T2836W5 (Ch. 19CC19) (Similar to Chassis)	1215-3	
★Ch. 12CB12X	1212-POM	
★Ch. 14CC14, Z/15, Z/16, Z	1233-3	
★Ch. 18CC29/30	1225-3	
★Ch. 19CC20	1230-POM	
Ch. 23-1	TSM-131	
Ch. 24-1	TSM-131	
★Ch. 25CC25	1212-POM	
★Ch. 25CC55	1212-POM	

Set No.	Folder No.	Model No.
CARTAPE Car Tapes Inc. 9180 Kelvin Ave. Chatsworth, California 91311		
CT-8900	AR-116	
CHANNEL MASTER Channel Master Corp. Ellenville, N.Y. 12428		
6203	AR-116	
6204	AR-113	
CHEVROLET United Delco Distributors		
118PB72	AR-115	
21AFM1	AR-109	
21AP81	AR-110	
21AP8K1	AR-110	
21AT411	AR-112	
21BFM1	AR-114	
21BF81	AR-113	
21BFP2 (See Page 61)	AR-113	
21BFPK1	AR-113	
21BFPK2 (See Page 61)	AR-113	
21BP81	AR-112	
21BP8T1	AR-115	
21HP8K1	AR-112	
21TP81	AR-110	
21TT411	AR-112	
21XP81	AR-115	
7305841	AR-110	
7313971	AR-112	
7932241	AR-112	
7314211	AR-114	
7930061	AR-115	
7930161	AR-115	
7932411	AR-112	
7932611	AR-109	
7932911	AR-112	
7933011	AR-113	
7933501	AR-110	
7933641	AR-112	
7935021	AR-112	
7936011	AR-113	
7936181	AR-115	
7936601	AR-112	
CHRYSLER Chrysler Corp. P.O. Box 1118 Detroit Michigan 48231		
288FW1	AR-109	
2884759 (8BBJ, 18BJ)	AR-89	
3501164 (288FW1) (1972 Prod.)	AR-109	
DELCO United Delco Distributors		
208CT11	AR-115	
7937400	AR-115	
DODGE (Also See MoPar) Chrysler Corp. P.O. Box 1118 Detroit, Mich. 48231		
10P2010	AR-109	
3420889 (10P2010)	AR-109	
3501157	AR-109	
FO-MO-CO (See Ford, Lincoln, Mercury) FORD Ford Motor Co. Dearborn, Mich.		
D28A-18810 (Similar to Page 51)	AR-59	
D2HA-18810 (Similar to Page 51)	AR-51	
18TF	AR-115	
D28T/BT/BTW (Similar to Page 51)	AR-59	
GENERAL MOTORS CORP. (GMC) United Delco Distributors		
26TRMP1	AR-110	
26TT411	AR-112	
26TTC1P	AR-110	
7305516	AR-110	
7308166	AR-112	
7931766	AR-110	
HITACHI Hitachi Sales Corporation of America 48-50 34th Street Long Island City, N.Y. 11101		
CS-1000IC	AR-111	
TRQ-206	AR-116	
INTERNATIONAL International Harvester Co. 180 N. Michigan Avenue Chicago, Illinois 60601		
18T1H	AR-110	

Set No.	Folder No.	Model No.
J		
JOHN DEERE		
1AR4231	AR-110	
18TJD	AR-113	
75MJJD	AR-110	
M		
MACK TRUCK		
117AMT	AR-112	
2045X28	AR-108	
MEDALLION Medallion Automotive Products Company P.O. Box 1903 Kansas City, Missouri 64141		
65-500	AR-116	
MERCURY Ford Motor Co. Dearborn, Mich.		
DORJ-19A241A	AR-109	
1CP2033	AR-109	
MOTOROLA Motorola, Inc. 9401 West Grand Ave. Franklin Park, Ill. 60131		
87185	AR-116	
TM2005	AR-111	
TM7185	AR-116	
75MFT	AR-109	
10P3598	AR-109	
Ch. TD138J	AR-116	
O		
OLDSMOBILE United Delco Distributors		
23AFM1	AR-112	
23AFP1	AR-115	
23AT411	AR-112	
23BFM1	AR-110	
23BFP1	AR-114	
23BP81	AR-115	
7935013	AR-115	
7935023	AR-115	
7935033	AR-110	
7937413	AR-112	
7938303	AR-115	
7938313	AR-114	
OPEL United Delco Distributors		
24LP81	AR-114	
24PP81	AR-112	
7312234	AR-112	
7930254	AR-114	
P		
PANASONIC Matsushita Elec. Corp. of America Panasonic Service & Parts Div. 10-16 44th Drive Long Island City, N.Y. 11101		
CX-351E	AR-111	
CX-830E	AR-111	
PLYMOUTH (Also See MoPar) Chrysler Corp. P.O. Box 1118 Detroit, Mich. 48231		
3501157	AR-109	
PONTIAC United Delco Distributors		
12BFM2	AR-115	
21AFM1	AR-113	
21AP81	AR-114	
21AP8K1	AR-114	
21XFMT1	AR-115	
22AFM1	AR-113	
22AP81	AR-114	
22AP8K1	AR-114	
22AT411	AR-112	
22BFM1, 2	AR-112	
22BFM2	AR-115	
22BFP1	AR-109	
22BFP2 (See Page 99)	AR-109	
22BFPK1	AR-109	
22BFPK2 (See Page 99)	AR-109	
22BP8K2	AR-115	
22BT411	AR-112	
22T8P1	AR-114	
22FFM1	AR-113	
22FP81	AR-114	
22FT411	AR-112	
22GFA1	AR-113	
22GP81	AR-114	
22PG8K1	AR-114	
22XT411	AR-112	
7307302	AR-114	
7307332	AR-114	
7307702	AR-112	
7312332	AR-113	
7312892	AR-114	
7312912	AR-114	
7313522	AR-114	
7313542	AR-113	
7313552	AR-114	
7930022	AR-109	
7930032	AR-112	
7930202	AR-115	
7930212	AR-115	

Set No.	Folder No.	Model No.
PONTIAC—Cont.		
7930252	AR-115	
7930492	AR-112	
7930542	AR-113	
7933241	AR-114	
7933261	AR-113	
7933501	AR-114	
7934782	AR-112	
7936191	AR-115	
7936232	AR-112	
R		
RANGER Ranger Auto Radio 19201 Cranwood Parkway Warrensville Heights, Ohio 44128		
R-71-T	AR-111	
S		
SAAB Saab, Inc. 100 Waterfront New Haven, Conn.		
OB5A, OB5AA, OB5AB	AR-113	
OB5A99	AR-113	
185A	AR-113	
185A99	AR-113	
9F85A, 9F85AB	AR-110	
9F85A99	AR-110	
SIMCA Chrysler Corporation P.O. Box 1118 Detroit, Michigan 48231		
1851, 1851B	AR-114	
T		
TENNA Tenna Corporation 19201 Cranwood Parkway Warrensville Heights, Ohio 44128		
TC-80-T	AR-116	
TC-82-T	AR-111	
TOYOTA Toyota Motor Sales U.S.A., Inc. 2055 West 190th Street Torrance, Calif. 90501		
CR-12ZFT	AR-114	
CX-161FTB	AR-114	
CX-165FTB	AR-115	
RT-60LFT	AR-114	
86120-20090 (CR-12ZFT)	AR-114	
86120-22040 (RT-60LFT)	AR-115	
86260-14010 (CX-165FTB)	AR-114	
86260-20011 (CX-161FTB)	AR-114	
TRIUMPH British Leyland Motors Inc. 600 Willow Tree Road Leonia N.J. 07605		
08TR, 08TRA, B	AR-110	
18TR	AR-110	
9F8TR	AR-113	
TRUSTONE Western Auto Supply Co. 2107 Grand Avenue Kansas City, Missouri 64108		
ITC7004A-07	AR-111	
MIC7003A-17	AR-116	
4DC7003	AR-116	
4DC7004	AR-111	
V		
VOLVO Volvo Distributors, Inc. Volvo Drive Rockleigh, New Jersey		
08VO, 08VOC, D	AR-109	
18VO, 18VOC, D	AR-109	
9F8VO, 9F8VOC, D	AR-112	
W		
WARDS-RIVERSIDE Montgomery Ward & Co. 619 Chicago Avenue Chicago, Illinois 60607		
ZCX-16753A, B, C, D	AR-116	
61-16753J	AR-116	
WELTRON Weltron Company Inc. 514 East Peabody Street Durham, North Carolina 27702		
717, 718	AR-111	
WHEEL HORSE Wheel Horse 515 West Ireland Road South Bend, Indiana 46614		
18TWH	AR-114	

Set No.	Folder No.	Model No.
RECORDERS AND TAPE PLAYERS		
A		
AMBASSADOR Allied Purchasing Corp. 401 Fifth Avenue New York, N.Y. 10016		
2V960	TR-95	
AMPEX Ampex Consumer Equipment Division 2201 Lunt Avenue Elk Grove Village, Illinois 60007		
Micro 9A (Similar to Page 5)	TR-81	
Micro 40	AR-111	
Micro 44	AR-109	
761	TR-95	
767	TR-95	
1461	TR-95	
1467	TR-95	
ARVIN Arvin Industries, Inc. 1531 Thirteenth Street Columbus, Indiana 47201		
40L31-19 (Ch. 1.48701, 1.48702)	TR-92	
Ch. 1.48701/702	TR-92	
B		
BOMAN ASTROSONIX Boman Astrosonix Div. of California Auto Radio Inc. 9426 Stewart & Gray Road Downey, California 90241		
BM-907	AR-116	
BM-910	AR-111	
SP-90	AR-116	
BUICK United Delco Distributors		
148PB72	AR-114	
24AT411	AR-112	
24BP81	AR-114	
24BT411	AR-112	
7307554	AR-112	
7930134	AR-114	
7935374	AR-112	
C		
CADILLAC United Delco Distributors		
15CFM73	AR-114	
25CFM11, 2	AR-114	
25CT411	AR-112	
7930495	AR-112	
7937005	AR-114	
CARTAPE Car Tapes Inc. 9180 Kelvin Ave. Chatsworth, California 91311		
CT-8900	AR-116	
CHANNEL MASTER Channel Master Corp. Ellenville, N.Y. 12428		
6201	TSM-129	
6202	TSM-131	
6203	AR-116	
6204	AR-113	
6205	TSM-130	
6208	TSM-130	
CHEVROLET United Delco Distributors		
118PB72	AR-115	
21AT411	AR-112	
21BP81	AR-115	
21TF411	AR-112	
21XP81	AR-115	
7313971	AR-112	
7930061	AR-115	
7930161	AR-115	
7936181	AR-115	
7936601	AR-112	
CRAIG Craig Corp. 2302 East 15th Street Los Angeles, California 90021		
2606	TR-90	
CROWN RADIO Crown Radio Corp. 228 E. Harris Ave. South San Francisco, Calif. 94080		
CTR-320W	TR-93	
CTR-8750	TR-94	
D		
DELCO United Delco Distributors		
208CT11	AR-115	
7937400	AR-115	

Set No.	Folder No.	Model No.
E		
ELECTROPHONIC Electrophonic Corp. of America 101-10 Foster Avenue Brooklyn, New York 11236		
T-9	TSM-131	
T-16	TSM-130	
T-17	TSM-131	
G		
GENERAL MOTORS CORP. (GMC) United Delco Distributors		
26TT411	AR-112	
7308166	AR-116	
H		
HITACHI Hitachi Sales Corporation of America 48-50 34th Street Long Island City, N.Y. 11101		
CS-1000IC	AR-111	
TRQ-206	AR-116	
TRQ-2325	TR-95	
TRQ-250, E, R, W	TR-91	
TRQ-260 (A), (W)	TR-92	
TRQ-280 (A), (E), (W)		

Set No.	Folder No.
O	
OLDSMOBILE United Delco Distributors	
23AT411	AR-112
7937413	AR-112

Set No.	Folder No.
P	
PACKARD BELL Teledyne Packard Bell Electronics 12333 West Olympic Blvd. Los Angeles, Calif. 90064	
TRD-120 (Similar to Page 34)	TR-73

Set No.	Folder No.
PANASONIC Matsushita Electric Corp. of America Panasonic Service & Parts Div. 10-16 44th Drive Long Island City, N.Y. 11101	
CX-351EU	AR-111
CX-830EU	AR-111
RQ-209DAS	TR-90
RQ-222AS	TR-95
RQ-226S	TR-94
RQ-236S	TR-93
RS-256UAS	TR-95

Set No.	Folder No.
PENNEY'S-PENNCREST J. C. Penney Co., Inc. 1301 Avenue of the Americas New York, N.Y. 10019	
3840	TSM-129
3850	TSM-130
6232,6233 (Similar to Page 136)	TR-18

Set No.	Folder No.
PONTIAC United Delco Distributors	
128FM12	AR-115
21XFMT1	AR-115
22AT411	AR-112
228FM11	AR-115
228T411	AR-112
22FT411	AR-112
22XT411	AR-112
7307702	AR-112
7930252	AR-115
7930492	AR-112
7934782	AR-112
7936191	AR-115
7936232	AR-112

Set No.	Folder No.
R	
RANGER Ranger Radio 19201 Cranwood Parkway Warrensville Heights, Ohio 44128	
R-71-T	AR-111

Set No.	Folder No.
REALISTIC Allied Radio Shack Corporation 2727 West 7th Street Fort Worth, Texas 76107	
TR-8 (14-912)	TR-91
TR-8A (14-912A)	TR-91
14-912, A	TR-91

Set No.	Folder No.
ROBERTS Rheem Manufacturing Co. Califone-Roberts Div. 6050 West Jefferson Blvd. Los Angeles, Calif. 90016	
525	TR-93
530	TR-93

Set No.	Folder No.
S	
SHARP Sharp Electronics Corp. 10 Keystone Place Paramus, N. J. 07652	
RD-426U	TR-92

Set No.	Folder No.
SONY Superscope, Inc. 8150 Vineland Ave. Sun Valley, Calif. 91353	
TC-100 (Serial #258,171 and Later (USA) #309,101 and Later (Canada))	TR-90
TC-160	TR-93
TC-650	TR-94

Set No.	Folder No.
SONY-Cont.	
TC-651 (Similar to Page 65)	TR-94
TC-707C (Similar to Page 65)	TR-94
TC-2200	TR-93

Set No.	Folder No.
SYLVANIA GTE Sylvania Inc. 700 Efficent Street Batavia, New York 14021	
CT150 (Ch. TC4)	TR-94
Ch. TC4	TR-94

Set No.	Folder No.
SYMPHONIC Symphonic Radio & Electronic Corp. Foot of John Street Lowell, Massachusetts 01852	
AT-115	TR-90
CR-142	TR-90

Set No.	Folder No.
T	
TENNA Tenna Corporation 19201 Cranwood Parkway Warrensville Heights, Ohio 44128	
TC-80-T	AR-116
TC-82-T	AR-111

Set No.	Folder No.
TOYOTA Toyota Motor Sales U.S.A., Inc. 2055 West 190th Street Torrence, Calif. 90501	
CX-161FTB	AR-114
CX-165FTB	AR-114
86260-14010 (CX-165FTB)	AR-114
86260-20011 (CX-161FTB)	AR-114

Set No.	Folder No.
TRUETONE Western Auto Supply Co. 2107 Grand Avenue Kansas City, Mo. 64108	
ITC7004A-07	AR-111
MIC7003A-17	AR-116
4DC7003	AR-116
4DC7004	AR-111

Set No.	Folder No.
W	
WARDS (AIRLINE-RIVERSIDE) Montgomery Ward & Co. 619 Chicago Avenue Chicago, Illinois 60607	
GEN-3930A	TR-95
GEN-6211A	TSM-129
ZCX-16753A, B, C, D	AR-116
61-16753	AR-116
62-6211	TSM-129
62-3930	TR-95

Set No.	Folder No.
WELTRON Weltron Company Inc. 514 East Peabody Street Durham, North Carolina 27702	
WFMX-104	TSM-129
717,718	AR-111
2001	TSM-131

Set No.	Folder No.
WOLLENSAK 3M Company Revere-Mincom Div. 2501 Hudson Rd. St. Paul, Minnesota 55119	
6150 (Lots A, B)	TR-93
6154 (Lots A, B)	TR-93
6250	TR-91
6350	TR-91
6360	TR-91
6364	TR-91

Set No.	Folder No.
Y	
YORK York Radio Corp. 15 Empire Blvd. So. Hackensack, N. J. 07606	
CTR-12	TR-95

JOIN THE PHOTOFACT®-OF-THE-MONTH CLUB

BUILD YOUR OWN UP-TO-THE-MINUTE SERVICE DATA LIBRARY

HERE'S HOW IT WORKS:

- Each month a sturdy, sealed P.O.M. carton will be delivered to you by your local Photofact distributor.
- This P.O.M. carton contains 6 Photofact sets in handy, ready-to-file folders. These 6 sets include the latest and most reliable service data on at least 50 new chassis—color TV receivers, black and white TV receivers, AM and FM radios, hi-fi's, stereos and record changers.
- Your P.O.M. carton also contains a bonus package of *Advance Schematics*—preliminary schematics on the very latest color, black and white chassis to fill your immediate servicing needs. (At a later date you'll receive a complete Photofact set on each of these)

- You will also receive a monthly service bulletin, *Photofact Servicer* offering inside troubleshooting advice and timely additional information.
- And, as a special feature, each P.O.M. carton contains 6 valuable certificates which you can save and redeem for a free metal file cabinet. (One-drawer model is free with 60 certificates—Four-drawer model requires only 144 certificates and \$21.95)

The special advantage of subscription membership in the P.O.M. Club is measured in dollars and cents! You save \$54.00 each year over the individually purchased set price (regular price per set is \$3.00). Members receive this entire service package each month for just \$13.50 per month! Can you afford not to take advantage of this tremendous savings on the complete service data so vitally important in your industry?



ASK YOUR SAMS DISTRIBUTOR
TO SIGN YOU UP TODAY!

HOWARD W. SAMS & CO., INC.
4300 WEST 62nd ST. • INDIANAPOLIS, INDIANA 46268

Now—Just 3 RCA Hi-Lite "V" Type Color Picture Tubes Replace ~~185~~¹⁹⁵ Types



Replaces 98 19" types

18VABP22	19HCP22/	490ASB22
18VACP22	19HKP22	490ASB22A
18VADP22	19HFP22	490BAB22
18VAHP22	19HJP22	490BCB22
18VAJP22	19HKP22	490BDB22
18VAQP22	19HQP22	490GB22
18VARP22	19HRP22	490HBB22
18VASP22	19HXP22	490BRB22
18VATP22	19JBP22	490CAB22
18VBAP22	19JDP22	490CB22
18VBCP22	19JHP22	490CHB22
18VBHP22	19JKP22	490CUB22
19EXP22	19JNP22	490DB22
19EXP22/	19JQP22	490DB22A
19GVP22	19JYP22	490EB22
19EYP22	19JZP22	490EB22A
19EYP22/	19KEP22	490FB22
19GWP22	19KFP22	490GB22
19FMP22	490AB22	490HB22
19FXP22	490ACB22	490JB22
19GLP22	490ADB22	490JB22A
19GSP22	490AEB22	490KB22
19GVP22	490AFB22	490KB22A
19GVP22/	490AGB22	490LB22
19EXP22	490AHB22	490MB22
19GWP22	490AHB22A	490NB22
19GWP22/	490AJB22	490RB22
19EYP22	490AJB22A	490SB22
19GXP22	490AKB22	490TB22
19GYP22	490AKP22A	490UB22
19GZP22	490ALB22	490VB22
19HBP22	490AMB22	490WB22
19HCP22	490AMB22A	490XB22
	490ANB22	490YB22
	490ARB22	490ZB22

Replaces 22 21" types

19VABP22	21FJP22A/
19VACP22	21GVP22
21AXP22	21FKP22
21AXP22A	21GUP22
21AXP22A/	21GUP22/
21AXP22	21FBP22A
21CYP22	21GVP22
21CYP22A	21GVP22/
21FBP22	21FJP22A
21FBP22A	21GXP22
21FBP22A/	21GYP22
21GUP22	21GZP22
21FJP22	21HAP22
21FJP22A	

Replaces 75 25" types

23EGP22	25ABP22	25BP22A/
23EGP22A	25ADP22	25YP22
23VABP22	25AEP22	25BRP22
23VACP22	25AFP22	25BSP22
23VADP22	25AGP22	25BVP22
23VAHP22	25AJP22	25BWP22
23VALP22	25ANP22	25BXP22
23VAMP22	25AP22	25BZP22
23VANP22	25AP22A	25CBP22
23VAQP22	25AP22A/	25CP22
23VARP22	25XP22	25CP22A
23VASP22	25AQP22	25FP22
23VATP22	25ASP22	25FP22A
23VAUP22	25AWP22	25GP22
23VAWP22	25AXP22	25GP22A
23VAXP22	25AZP22	25RP22
23VAYP22	25BAP22	25SP22
23VAZP22	25BCP22	25VP22
23VBAP22	25BDP22	25WP22
23VBCP22	25BFP22	25XP22
23VBDP22	25BGP22	25XP22/
23VBEP22	25BHP22	25AP22A
23VBGP22	25BJP22	25YP22
23VBHP22	25BMP22	25YP22/
23VBJP22	25BP22	25BP22A
23VBRP22	25BP22A	25ZP22
23VBT22		


Stock these three RCA Hi-Lite color picture tubes and have immediate replacements for the fastest moving industry types—195 of them. It's the way to save yourself time, give your customers faster service, improve profits.

RCA Hi-Lite types are all new, made to OEM specifications and contain the newest RCA manufacturing technology, including Perma-Chrome and the latest X-ray attenuating glass.

Order these three RCA Hi-Lite tubes, and other types you may need, from your RCA Distributor. He also has the complete RCA Interchangeability Guide, available free of charge.

RCA | Electronic Components | Harrison, N.J. 07029

RCA Electronic Components

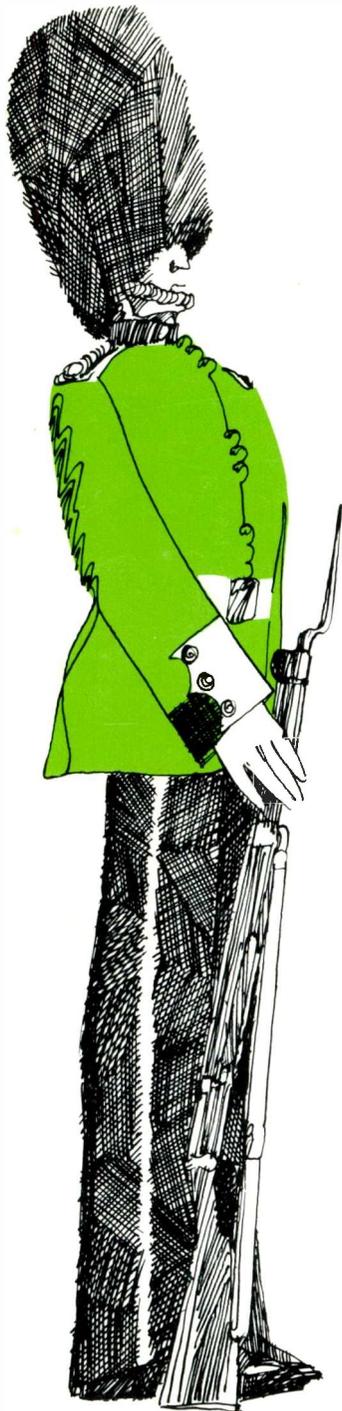

24 hour watch



Everyday. All over the world. On millions of television sets, our sentry stands. The new Littelfuse Circuit Breaker. Meeting industry's new safety requirements of SE-O insulating materials, our breaker is demanded by virtually all set manufacturers. It's the perfect replacement part too!

Contact your nearest Littelfuse source. He'll show you the 19 available models with a variety of packaging choices.

24 hour watch. All over the world. It's a big assignment. But the Littelfuse Sentry is one of television's brightest stars.

Recognized under the components program of Underwriters Laboratory, Inc.

LITTELFUSE

Littelfuse, Inc. Subsidiary of Tracor, Inc.
800 E. Northwest Highway, Des Plaines, Ill. 60016

Circle 3 on literature card