

The how-to magazine of electronics...

AN INTERTEC PUBLICATION

ELECTRONICTM

Service & Technology

OCTOBER 1987/\$2.25

Measuring VCR tension and torque • Ruling out static

Unusual waveform/function generator circuits

VCR test and alignment procedures



Easier Testing. By Comparison.

*Scopemate 2™ With Your Scope Or Ours,
Still The Best Price Solution
For Good/Bad IC and Component Testing.*

Now you can economically test all types of analog, digital and hybrid components—including resistors, capacitors, diodes and ICs with up to 40 pins—using a simple X-Y oscilloscope. In the field or on the bench, in-circuit or out-of-circuit. Without tedious pin-by-pin or contact-by-contact testing.

It's made possible by Scopemate 2™ from Beckman Industrial. All it does is plot voltage vs. current. Just a lot easier. A lot faster.

Scopemate 2 compares components known to be good with those to be tested, giving you a very accurate and fast way to identify bad devices. The voltage vs. current plot from a known good device is compared to the device under test. In fact, since there's no complex numerical test data to interpret, Scopemate 2 is ideal for less experienced personnel.

And, at \$395 it doesn't take too long to figure that Scopemate 2 may pay for itself in saved testing time. Real soon. Scopemate 2 comes with a simple yet comprehensive operator's manual, a complete set of leads, interconnect cables and plug-in transformer.

Although Scopemate 2 will work with just about any X-Y oscilloscope,



9020 20MHz Delayed Sweep Oscilloscope \$499.00

Vertical Accuracy: $\pm 3\%$
Time-based accuracy: $\pm 3\%$
Input Impedance: 1M ohm
35pF (2%)
Input Max. Voltage: 400V
(DC + pos. peak AC)
Sweep Delay Ranges:
10, 1.0, 1ms; 10, 1.0, 1 μ s
Mode: Normal, search, delay

Beckman Industrial Circuitmate™ Model 9020 offers capabilities seldom found on other scopes costing less than \$500.

Proven capabilities such as **delayed sweep** for easy bandwidth analysis, zoom-in for short-duration events, a variable holdoff function for a stable display of non-periodic signals—even beam finding to

Scopemate 2™ IC/Component Tester \$395.00

Test Method: Direct Visual Comparison (known good vs. device under test)

Test Sockets/Interface: 20 and 40-pin ZIF IC sockets, banana jacks

Power: 120 or 220VAC, 50/60Hz, 5VA max. (specify)

Circuit Test Voltage/Current: 14VAC RMS (voltage, approx.); 300 μ A AC RMS (current, approx.)

Pin Test selection: Push-button switch per pin

locate and return trace to view regardless of control settings. And switchable X1/X10 probes give you more sensitivity for low frequency measurements, less circuit loading for high frequency measurements.

For real value, combine the 9020 and Scopemate 2 for performance and flexibility unmatched by systems costing \$1,500 or more. For less than \$900.

Both Scopemate 2 and our Circuitmate Model 9020 illustrate a simple commitment by Beckman Industrial—to provide service test instruments that meet your needs. Whether through advanced technology or value oriented applications of proven technology, Beckman Industrial gives you the right features at the right price, with service test instruments built to rigorous standards of quality and reliability.

Visit your Beckman Industrial distributor today and find out how the ruggedly reliable Scopemate 2 and the 9020 Oscilloscope can meet your needs. And why they offer the best value around. By comparison.



*In Service
Instruments,
We're The One.*

Beckman Industrial™

Beckman Industrial Corporation, Instrumentation Products Division
A Subsidiary of Emerson Electric Company
3883 Ruffin Road, San Diego, CA 92123 1898
(619) 495 3200 • FAX (619) 268 0172 • T.L.X. 249051

© 1987 Beckman Industrial Corporation

Circle (1) on Reply Card



NEW TEK. PURE & SIMPLE.



Now, the perfect measure of economy plus performance in a low-cost, 50 MHz scope backed by a 3-year warranty. The new 2225 exemplifies Tek quality at its pure and simple, affordable best. It's the easy, economical answer to your professional scope needs at bench and field sites, on the manufacturing floor and in the classroom.

Two-channel, single time-base Tek basics enhanced by features of much more expensive scopes. Plus outstanding ease of use.

You get 500 $\mu\text{V}/\text{div}$ vertical sensitivity for low-level signals. Horizontal alternate sweep magnifications of X5, X10 and X50 for time measurement accuracy. New front-panel Z-axis input. HF and LF Reject trigger filtering to stabilize noisy-signal displays. Plus

| | |
|----------------------|--|
| Bandwidth | 50 MHz |
| Vertical Sensitivity | 500 $\mu\text{V}/\text{div}$ |
| Waveform Expansion | X5, X10, X50 Alternate Magnifications |
| Maximum Sweep Speed | 5 ns/div |
| Trigger Modes | Peak-to-Peak Auto, Norm, TV Field, TV Line, Single Sweep |
| Trigger Couplings | AC, DC, HF Reject, LF Reject |
| Weight | 6.6 kg/14.6 lb |
| Warranty | 3-year on parts and labor, including CRT |

\$995

TV Line and Field triggering. All in a compact, portable package.

Two heavy-duty Tek 10X modular probes with a new ruggedized probe tip are included.

Scope. Probes. 3-year warranty. 30-day free trial. One free call gets it all!

Call Tek direct to order, obtain literature or get the name of your nearest Tek representative or distributor. Technical personnel can answer your questions and expedite delivery. Direct orders include probes, operator's manual, 30-day free trial on approved credit and factory-trained service worldwide. Everything that says genuine Tek!

Call Tek direct:
1-800-426-2200
In Oregon, call collect:
627-9000



Circle (3) on Reply Card

Tektronix
COMMITTED TO EXCELLENCE

6 Test your electronics knowledge

By Sam Wilson, CET
This month's quiz tests your knowledge of circuits and power supplies, with a bonus question for radio buffs.

10 The dissipation factor...an explanation

By D. Joseph Frazier
This answer to the April 1987 "Report from the test lab" explains the function of the dissipation factor of a capacitor.

16 VCR test and alignment procedures


By G. McGinty, CET
Just following the steps for testing and aligning VCRs takes time, but getting together the necessary equipment and learning the symptoms and waveforms can speed up the process.

26 Ruling out static

By Dixon Gleeson
Although a lot of electronics servicing professionals think of static as simply an irritant, it can degrade or even destroy static-sensitive components. Yet following just three rules can protect expensive components both in the field and in the shop.



page 16
A basic test-equipment setup for VCR testing and alignment can be stored on a roll-away cart for convenience. (This photo and cover courtesy of Leader Instruments.)

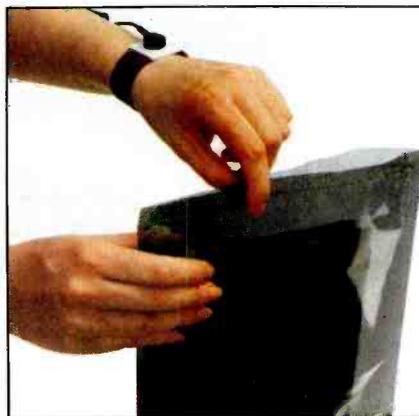

page 26
Static shielding bags and static dissipative kits can protect sensitive electronic components from ESD damage.

Departments:

- 4 Editorial
- 8 News
- 12 Technology
- 15 Photofact
- 25 Literature
- 31 Profax
- 39 Books
- 58 Products
- 60 Computer Corner
- 62 Video Corner
- 64 Audio Corner
- 65 Readers' Exchange
- 68 Advertisers' Index

42 Measuring tape tension and torque in VCRs

By Wayne Graham
The mechanical systems that drive VCR tape cause most VCR failures. To diagnose which component is causing the problem, the technician needs to know the difference between tension and torque, and how to measure both.

45 Unusual waveform/function generator circuits

By Joseph J. Carr, MSEE, CET
Although you might be familiar with the common waveforms, internal circuits generate more unusual waveforms too. Knowing these can help you service complex electronics more effectively.

52 What do you know about electronics — a new zener diode


By Sam Wilson, CET
Many bipolar transistors behave strangely when connected into the circuit backwards. The author discusses light-emitting diodes, which produce a zener diode characteristic on a curve tracer, and also introduces some do-it-yourself dimmers and decade boxes.

ARM YOURSELF AGAINST STATIC



WITH NTE'S PATENTED FIELD SERVICE KIT.

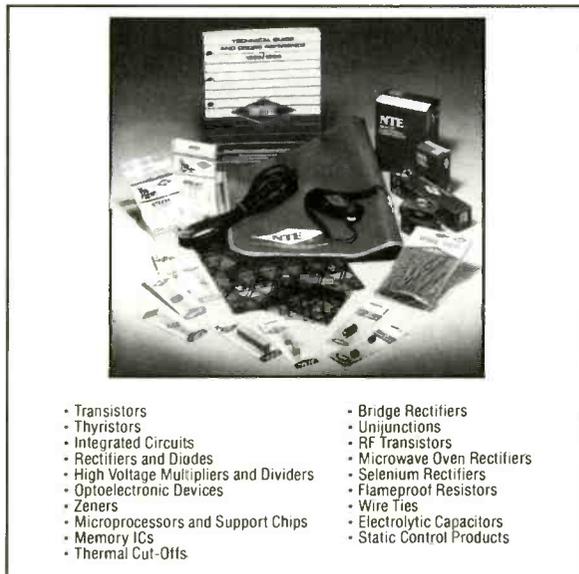LOOK FOR THE FULL LINE OF QUALITY NTE
REPLACEMENT PARTS AND PRODUCTS:



- Transistors
- Thyristors
- Integrated Circuits
- Rectifiers and Diodes
- High Voltage Multipliers and Dividers
- Optoelectronic Devices
- Zeners
- Microprocessors and Support Chips
- Memory ICs
- Thermal Cut-Offs
- Bridge Rectifiers
- Unijunctions
- RF Transistors
- Microwave Oven Rectifiers
- Selenium Rectifiers
- Flameproof Resistors
- Wire Ties
- Electrolytic Capacitors
- Static Control Products

Static electricity is a real hazard to sensitive electronic equipment. Now you can protect valuable components in the field and in the plant with NTE's new Field Service Kit.

Our Kit includes everything you need to keep your equipment free of static — a 24" x 24" table top work mat, wrist strap with 8' coil cord, 15' clip-on grounding line and anti-static component storage bags. Both the wrist strap cord and grounding cord contain integral current limiting resistors.

Unlike other kits currently on the market, NTE's patented* three-

layer construction produces controlled static drain, eliminating the danger of sparking and the chance of additional component failure during the repair operation. The static-dissipative, vinyl work surface is durable and its bright green color enhances visibility. The entire Kit folds down into a compact unit and comes with its own zip-close bag.

Look for NTE's new Field Service Kit and our other static control products — including our anti-static foam, for shipping and storing equipment, and separately packaged wrist straps — at your local NTE distributor.

*Patent issued November 8, 1983.
U.S. Patent No. 4,414,260.



NTE ELECTRONICS, INC.

44 FARRAND STREET • BLOOMFIELD, NEW JERSEY 07003
(Outside N.J.) 1-800-631-1250 • (N.J. only) 1-800-624-2624

For more information or the name of your local distributor, call or write NTE.

Circle (4) on Reply Card

The "smart" home of the future

Wouldn't it be nice if you could dial a phone, say from where you work, from the movies or a restaurant or even from out of town, and be connected with your home. No, I don't mean *someone* at your home, I mean with a central control and sensing unit that would let you turn lights on and off, reset the temperature setting on your thermostat, turn on your VCR to record a program that you forgot you wanted to watch, check to see if you in fact left an iron turned on (and turn it off if you did), or

check the outside and inside temperatures.

Sound far-fetched? It does to me too, but considering the advanced state of today's electronic technology and some things that are going on in the electronics industry, it just might become possible sooner than any of us think.

The most recent issue of the EIA/CEG Newsletter features an article called "Interest grows in home automation as CEG begins to draft standard." The report is quoted here:

There is a new American home on the horizon—one that is efficient, secure and very smart. It is the fully automated intelligent home. Although "smart" systems—automated controls for heating, air conditioning, lighting and security—have been used in office buildings for years, this technology has not been available for the family home. The EIA's Consumer Electronics Group is developing industry-wide standards that will soon make the dream of the intelligent home a reality.

According to Group Vice President Thomas P. Friel: "To understand the system, one should think of a home as a network of highways. Its 'roads' are the power

and telephones, infrared remotes and coaxial cables. Although all are now capable of carrying commands and information throughout the home, the roads are not yet connected. The EIA standards will join all of these into a network through which commands can be issued for various home functions."

With the growing interest in the development of a standard for a remote-controlled home system, CEG envisions this system utilizing power lines, twisted wire pairs, coaxial cables and infrared wire to control audio/video, lighting, major appliances and security systems with the push of a button.

If you find it hard to imagine the idea of a home full of electrical and electronic devices that can be programmed in advance to come on and off on a set schedule, and can then be reprogrammed remotely using the buttons of a touch-tone phone, try to picture the reaction you'd get if you tried to describe a modern home to someone at the turn of the century whose home had just been wired for a few electric lights. He would no doubt find it impossible to conceive of pictures being received from a distance, even from space, or news reports received instantaneously as they happen on the other side of the globe.

And imagine if you tried to convince him that in the future

he would be able to cook food in minutes without heat, or if you tried to describe what he would be able to do with the telephone and a personal computer.

This central bus proposed by the EIA Consumer Electronics Group, along with the electronics technology already in place, should serve to keep the consumer electronics revolution rolling for a long time to come. But we all know that the technology will continue to advance at a rapid pace in the meantime, making the possibilities even more incredible.

It's an exciting time to be involved with electronics and should prove to be interesting for consumers as well as rewarding for servicing professionals.



Portable Problem Solver

Ultra-compact Digital Storage Oscilloscope-Multimeter.

Easily carried in a tool kit or attache case—powered by batteries or supplied ac adaptor—this 2-in-1 lightweight is always ready for hand-held action.

Multi-function, 200-kHz DSO.

Just flip the switch from DMM to SCOPE and the performance of a professional Digital Storage Oscilloscope is at your fingertips. Lets you capture and analyze single-shot and very slow phenomena. Stores up to three waveforms, and has such top-of-the-line features as auto-ranging time base setting, pre-trigger, roll mode, and on-screen readout of setting conditions. Low-power indicator

alerts you when batteries need recharging, while a separate back-up system protects memory.

Full-function, 3½-digit DMM.

Precise measurement of ac/dc voltage, current and resistance is easy to see on the large, high-contrast, display. Automatically selects range which provides greatest accuracy and resolution.

Perfect for many applications.

LCD-100 is a unique combination instrument that can confirm that its DMM is measuring a desired signal. Better by far than a DMM alone... more useful in the field than any benchtop DSO in this bandwidth, LCD-100 is ideal for servic-

ing a broad range of electromechanical, electrical and electronic systems.

Call toll-free
1-800-645-5104
 In NY State
(516) 231-6900

Ask for an evaluation unit, our latest Catalog, more information, or the name of your "Select" Leader Distributor.

For professionals
 who know
 the
 difference.






380 Oser Avenue, Hauppauge, New York 11788
 Regional Offices:
 Chicago, Dallas, Los Angeles, Boston, Atlanta
 In Canada call Omnitrax Ltd. (416) 828-6221

For Information Circle (36) on Reply Card
 For Demonstration Circle (37) on Reply Card

Test your electronics knowledge

By Sam Wilson, CET

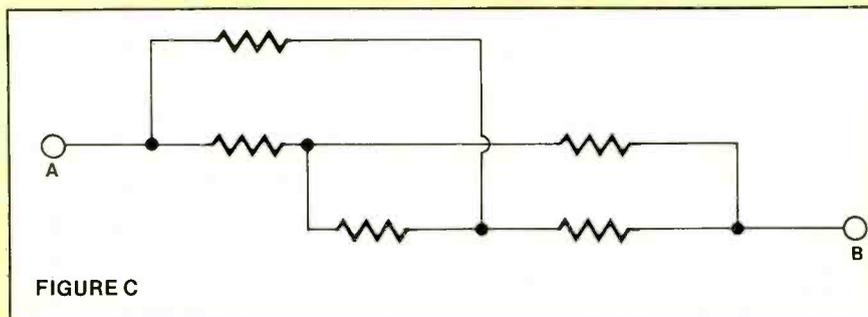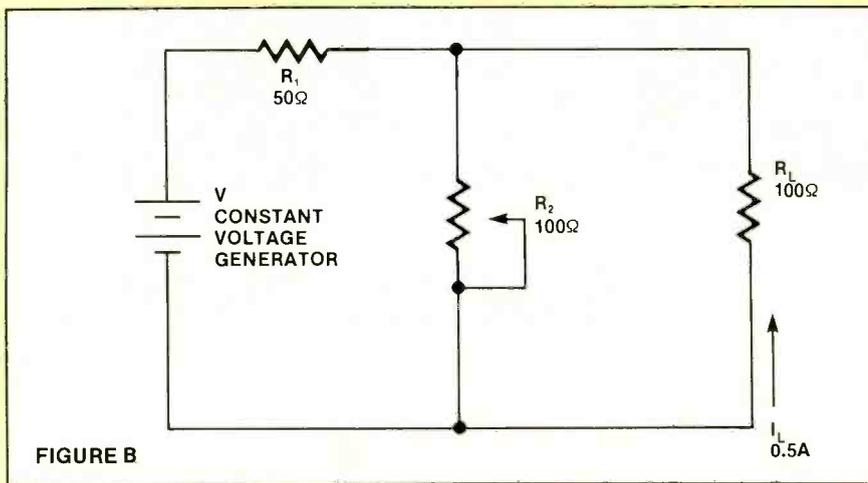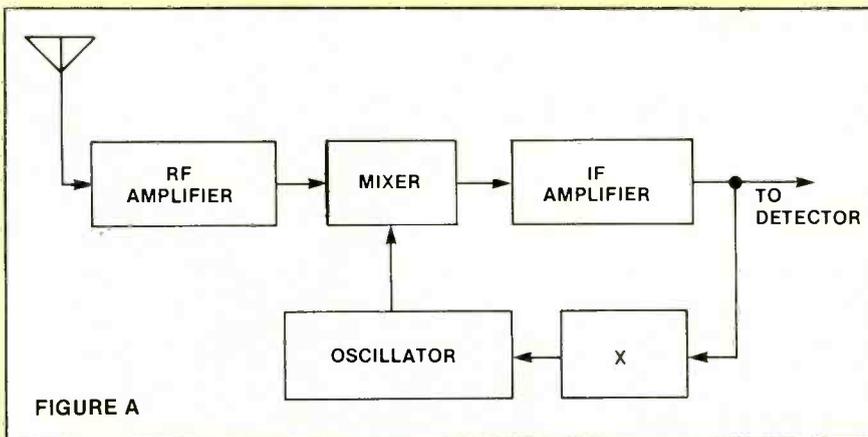

- The vertical antennas used with AM broadcast transmitters are
 - quarter-wavelength.
 - half-wavelength.
 - one-wavelength.
- The resonant frequency of a certain series-tuned L-C circuit is adjusted by moving the turns of the coil farther apart or closer together. To lower the resonant frequency, you should move the turns
 - closer together.
 - farther apart.
- Which of the following circuits might be found in the block marked x in Figure A?
 - BFO
 - AGC amplifier
 - discriminator
 - wideband amplifier
- What is the highest number that can be counted with five J-K flip flops?
 - 32
 - 16
 - 24
 - 31
- Consider the simple circuit in Figure B. With R_2 adjusted to 100Ω , the current through R_L is $0.5A$. To maintain $0.5A$ through R_L , you would have to
 - increase the resistance of R_2 if the resistance of R_L decreases.
 - increase the resistance of R_2 if the resistance of R_L increases.
- Each resistor in the circuit of Figure C is 10Ω . The resistance between A and B is _____.
- What is the name of the power supply system that converts dc to ac?
- Which of the following is true for a power supply?
 - A lower percent regulation is better than a higher percent regulation.
 - A higher percent regulation is better than a lower percent regulation.

9. Which of the following is true for a power supply?

- A.) It is better to have a low ripple factor.
- B.) It is better to have a high ripple factor.

10. To increase the brightness of the lamp in the circuit of Figure D, move the wiper of R

- A.) toward point A.
- B.) toward point B.

BONUS QUESTION - 10 points:
Who was the first person to transmit a coded message by radio waves?

- A.) Morse
- B.) Marconi
- C.) Tesla
- D.) Edison

Answers are on page 40

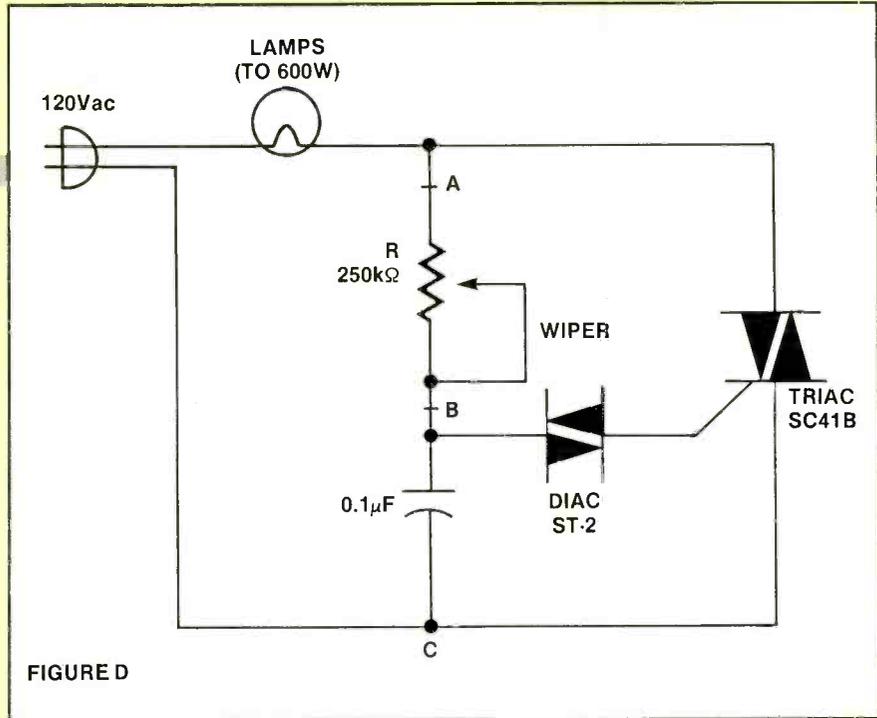


FIGURE D

NEW RUGGEDIZED SCOPE PROBES

Just a phone call away.

\$35 P6103

50 MHz 10x
Compensation Range
15 to 35 pF

\$58 P6109

150 MHz 10x
Compensation Range
18 to 22 pF


These new passive voltage probes can be used with any oscilloscopes having matching compensation ranges.

Screw in tips mean easy repair, no downtime.

To order call toll free **1-800-426-2200**

In Oregon, call collect (503) 627-9000.

VISA and MasterCharge accepted.

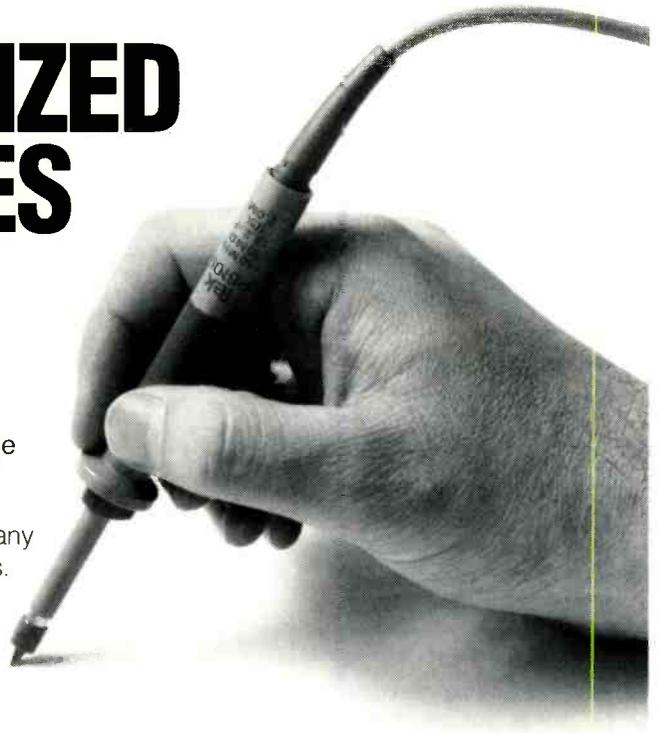

Tektronix
COMMITTED TO EXCELLENCE

CEG announces U.S. Skill Olympics winners

Six winners have been chosen in the Electronic Products Servicing Contest, one of 38 skill contests held during the Vocational Industrial Clubs of America (VICA) 23rd annual U.S. Skill Olympics. The contest, sponsored by the Consumer Electronics Group (CEG), tested problem-solving, soldering and desoldering skills and knowledge of safety problems.

The six winners, listed below, were awarded free subscriptions to *ES&T* magazine.

NARDA and NESDA discuss joint association

Exploratory discussions on possible future joint ventures were held August 13 by members of NARDA/NASD (the National Association of Retail Dealers of America and the National Association of Service Dealers) and NESDA/ISCET (the National Electronics Sales & Service Dealers Association and the International Society of Certified Electronics Technicians). The four members who attended the session were Dorothy Cichetti, president of NESDA, Jim Parks, chairman of ISCET, Kent Crawford, president of NASD, and David McKalip, secretary of NARDA. The discussions may eventually lead to a consolidated international association to serve the sales and service industry.



The six winners of the Electronic Products Servicing contest at the U.S. Skill Olympics were, left to right: postsecondary winners Mike King, 3rd place; Henrik Moller, 2nd place; and Dean Johnson, 1st place; and secondary winners Michael Belew, 1st place; William Lee, 2nd place; and Ady Little, 3rd place.

The how-to magazine of electronics

ELECTRONIC

Servicing & Technology

Editorial, advertising and circulation correspondence should be addressed to: P.O. Box 12901, Overland Park, KS 66212-9981 (a suburb of Kansas City, MO); (913) 888-4664. Home office fax: 913-888-7243; Home office telex: 42-4156 INTERTEC OLPK

EDITORIAL

Nils Conrad Persson, *Editor*
 Carl Babcoke, *Consumer Servicing Consultant*
 Tom Cook, *Senior Managing Editor*
 Alisa Carter, *Associate Editor*
 Joy Culver, *Editorial Assistant*
 Darryll Fortune, *Editorial Assistant*
 Darren Sextro, *Editorial Assistant*

CONSULTING EDITORS

Homer L. Davidson, *TV Servicing Consultant*
 Christopher H. Fenton, *Circuit Fabrication Consultant*
 Victor Meeldijk, *Components Consultant*
 Kirk G. Vistain, *Audio Consultant*
 Sam Wilson, *Electronics Theory Consultant*

ART

Kevin Callahan, *Art Director*
 Tim Lynch, *Graphic Designer*

BUSINESS

Cameron Bishop, *Group Vice President*
 Eric Jacobson, *Publisher*
 Greg Garrison, *Sales Manager*
 Stephanie Fagan, *Promotions Manager*
 Kelly Hawthorne, *Promotions Coordinator*
 Dee Unger, *Advertising Supervisor*
 Julie Chilson, *Advertising Coordinator*

ADVERTISING

Regional advertising sales offices are listed in classified pages.

ADMINISTRATION

R. J. Hancock, *President*
 Doug Riemer, *Circulation Vice President*
 Jo Ann DeSmet, *Fulfillment Manager*
 Janey Powell, *Circulation Manager*
 Dee Manies, *Reader Correspondent*



Member, Audit Bureau of Circulation



Member, American Business Press



Member, Electronic Servicing Dealers Association

ELECTRONIC SERVICING & TECHNOLOGY is the "how-to" magazine for technicians who service consumer electronics equipment. This includes service technicians, field service personnel and avid servicing enthusiasts, who repair and maintain audio, video, computer and other consumer electronics equipment.

SUBSCRIPTION PRICES: one year \$18, two years \$30 in the USA and its possessions. Foreign countries: one year \$22, two years \$34. Single copy price \$2.25; back copies \$3.00. Adjustment necessitated by subscription termination to single copy rate. Allow 6 to 8 weeks for new subscriptions.

PHOTOCOPY RIGHTS: Permission to photocopy for internal or personal use is granted by Intertec Publishing Corp. for libraries and others registered with Copyright Clearance Center (CCC), provided the base fee of \$2 per copy of article is paid directly to CCC, 21 Congress St., Salem, MA 01970. Special requests should be addressed to Eric Jacobson, publisher. ISSN 0278-9922 \$2.00 + 0.00



©1987 All rights reserved.

Now electronics technicians can get into VCR Servicing quickly and easily

Learn professional VCR servicing at home or in your shop with exclusive videotaped demonstrations

Today, there are more than 10 million VCRs in use, with people standing in line to have them serviced. You can bring this profitable business into your shop with NRI professional training in VCR servicing. This top-level training supports the industry's claim that the best technicians today are those who service VCRs.

Integrated Three-Way Self-Teaching Program


In one integrated program, NRI gives you a study guide, 9 instructional units, 2 hours of video training tapes accompanied by a 32-page workbook that pulls it all together. At home or in your shop, you'll cover all the basic concepts of video recording, mechanical and electronic systems analyses, and the latest troubleshooting techniques. Your workbook and instructional units also contain an abundance of diagrams, data, and supplementary material that makes them valuable additions to your servicing library.

The "How-To" Videotape

Your NRI Action Videocassette uses every modern communications technique to make learning fast and easy. You'll enjoy expert lectures and see animation and video graphics that make every point crystal-clear. You'll follow the camera eye into the heart of the VCR as step-by-step servicing techniques are shown. Both electronic and mechanical troubleshooting are covered . . . including everything from complete replacement and adjustment of the recording heads to diagnosing micro-processor control faults.

Plus Training On All The New Video Systems

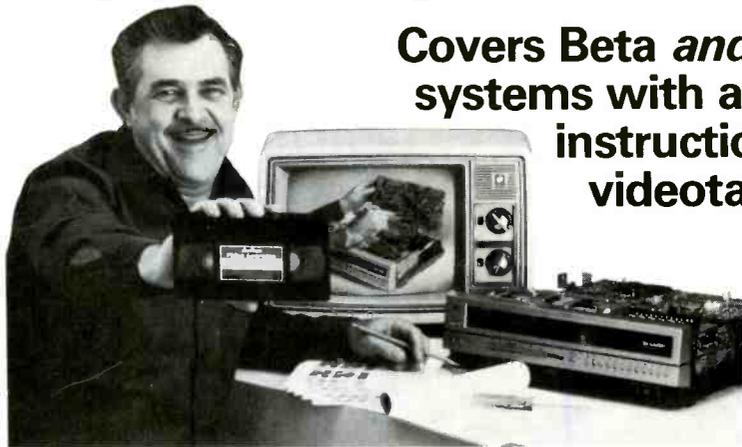Although your course concentrates on VCRs covering Beta, VHS, and 3/4" U-Matic commercial VCRs, NRI also brings you up to speed in other key areas. You'll get training in capacitance and optical video disc players, projection TV, and video cameras. All are included to make you the complete video technician. There's even an optional final examination for NRI's VCR Professional Certificate.



Covers Beta and VHS systems with actual instruction on videotape.

The Best Professional Training

This exclusive self-study course has been developed by the professionals at NRI. NRI has trained more television technicians than any other electronics school! In fact, NRI has consistently led the way in developing troubleshooting techniques for servicing virtually every piece of home entertainment equipment as it appears in the marketplace.

Satisfaction Guaranteed . . . 15-Day No-Risk Examination

Send today for the new NRI Self-Study Course in VCR Servicing for

Professionals. Examine it for 15 full days, look over the lessons, sample the videotape. If you're not fully satisfied that this is the kind of training you and your people need to get into the profitable VCR servicing business, return it for a prompt and full refund, including postage. Act now, and start adding new business to your business.

Special Introductory Offer

This complete VCR training course with two hour videotape is being offered for a limited time only, on orders received from this ad, at our low introductory price of \$179.95. Save \$20 by acting now!

NRI Training For Professionals
McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Washington, DC 20016

YES! Get me started in profitable VCR servicing. Rush me my NRI self-study course in VCR Servicing for Professionals. I understand I may return it for a full refund within 15 days if not completely satisfied.

PLEASE SPECIFY TAPE FORMAT DESIRED VHS BETA

Name (please print) _____

Company _____

Street _____

City/State/Zip _____

Enclosed is my check money order for \$179.95 (D.C. residents add 6% tax) Make check payable to NRI

Charge to VISA MasterCard _____

Interbank Number _____

Card Number _____ Expiration Date _____

Signature _____

(required for credit card sales)



NRI Training For Professionals
McGraw-Hill Continuing
Education Center
3939 Wisconsin Avenue
Washington, DC 20016

2630-107

Report from the test lab

The dissipation factor...

an explanation

In the last "Report from the Test Lab" (April 1987) the author evaluated the American Reliance AR-460-D LCR meter and asked the question, "What is a dissipation factor?" He pointed out that the meter being tested measures dissipation factor, but this parameter was not thoroughly discussed in the material provided with the meter.

D. Joseph Frazier, strategic marketing manager for American Reliance, provides the following explanation.

An ideal capacitor or inductor would store but not dissipate energy—energy out would be equal to energy in. However, in the real world capacitors and inductors do have losses.

The first type of loss in a capacitor is associated with the dielectric material. The dielectric losses may be represented by a *parallel model* expressed as a perfect, lossless capacitor (C_p) in parallel with a resistor (R_p) that represents the dielectric resistance. (See Figure 1.)

In this model, the dissipation factor may be expressed as:

$$D = 1 / (F \times C_p \times R_p)$$

where F represents the frequency of the applied voltage, and C_p and R_p represent the values of capacitance and resistance measured at frequency F .

The second type of loss is associated with the resistance of the conductors and plates. The resistance losses may be represented by the *series model*, which is represented as a perfect, lossless capacitor (C_s) in series with a resistor (R_s) that represents the resistance in the plates and conductors. (See Figure 2.)

In this model, the dissipation factor may be expressed as:

$$D = F \times C_s \times R_s$$

where F again represents the frequency of the applied voltage, and

C_s and R_s represent the values of capacitance and resistance measured at frequency F .

Because the capacitor's dielectric material is not a perfect insulator, a current will flow between the two plates. This current is referred to as the *leakage current* and causes some of the stored energy to be lost as heat. Also, because the conductors are not perfect, they possess a certain resistance, which also causes heat (IR) losses during charge and discharge cycles. Both these losses considered together are the capacitor's *dissipation factor*.

It is important to note here that excessive leakage currents will cause errors in capacitance measurements. Therefore, it is good practice to test a capacitor for excessive leakage *before* attempting a capacitance measurement.

It may be clearly seen in the dissipation factor formula that the dissipation factor is inversely related to the leakage current.

The inductor's energy loss that we are concerned with is caused by the resistance inherent in the wire forming the inductor. This may be shown as the inductance L_s in series with the resistance R_s . (See Figure 3.)

However, the resistance of an inductor is rarely specified. Instead, a quality factor, Q , is commonly used:

$$Q = (F \times L) / R$$

where F represents the frequency of the applied voltage, L is the inductive reactance at frequency F and R is the resistance. Obviously, Q is therefore frequency dependent.

During periods of current flow, the resistance develops heat due to IR losses. This is the loss defined by the quality factor, Q .

Q is related to the dissipation factor by:

$$D = 1 / Q$$

It is easily seen, then, that the higher the Q (or lower the dissipation factor) the better an inductor's quality is.



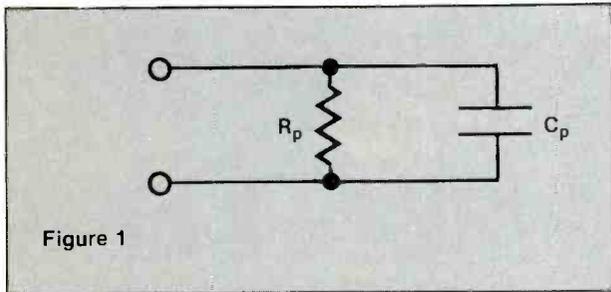


Figure 1

Figure 1. One energy loss that occurs in capacitors is associated with the dielectric material. The dielectric losses may be represented by a parallel model expressed as a perfect, lossless capacitor (C_p) in parallel with a resistor (R_p) representing the dielectric resistance. Leakage current caused by the imperfect dielectric material will cause heat loss and errors in capacitance measurements. A leakage resistance of $100M\Omega$ or more is considered large, and $1M\Omega$ or less will cause excessive leakage current.

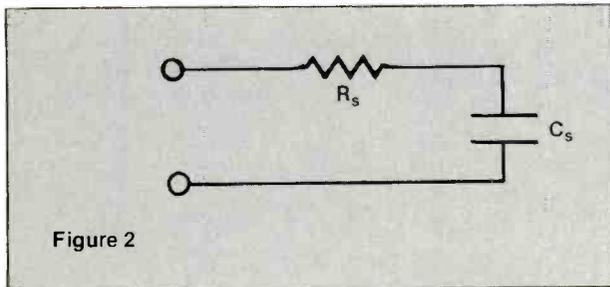


Figure 2

Figure 2. Capacitor energy loss is also caused by the capacitor's conductors and plates. These losses may be represented by a series model, with a perfect, lossless capacitor (C_s) in series with a resistor (R_s) representing this resistance.

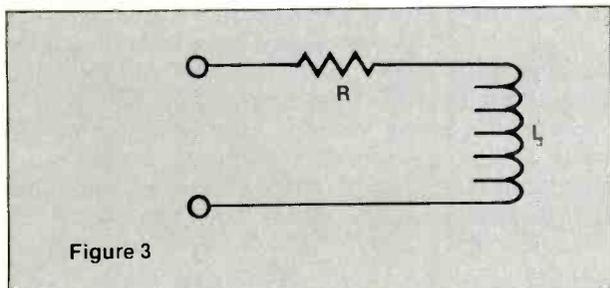


Figure 3

Figure 3. Energy loss in an inductor is primarily caused by the resistance inherent in the wire forming the inductor. This loss may be shown as the inductance L_s in series with the resistance R_s .

BS&T

OK
Electronics
Division



How Easy is it to put 1 GHz at your fingertips? Or in your tool kit? Or in your attaché?

AS EASY AS THE
OK ELECTRONICS MODEL 512,
HAND HELD FREQUENCY COUNTER

The 200MHz frequency counter coupled with the Mode 514 prescaler allows you to extend the range to 1GHz. The counter has an 8 digit LED display, operates with a nine volt battery, has two BNC inputs and the counter/prescaler package costs less than \$275.⁰⁰



AFFORDABLE
EXCELLENCE




OK
Industries
Inc.



4 Executive Plaza, Yonkers, New York 10701 USA
Telex 125091 OK NY. Te ex 23235E OK NY UR
Phone (514) 967-6800
Fax (914) 959-6650

Circle (7) on Reply Card

Total remote control

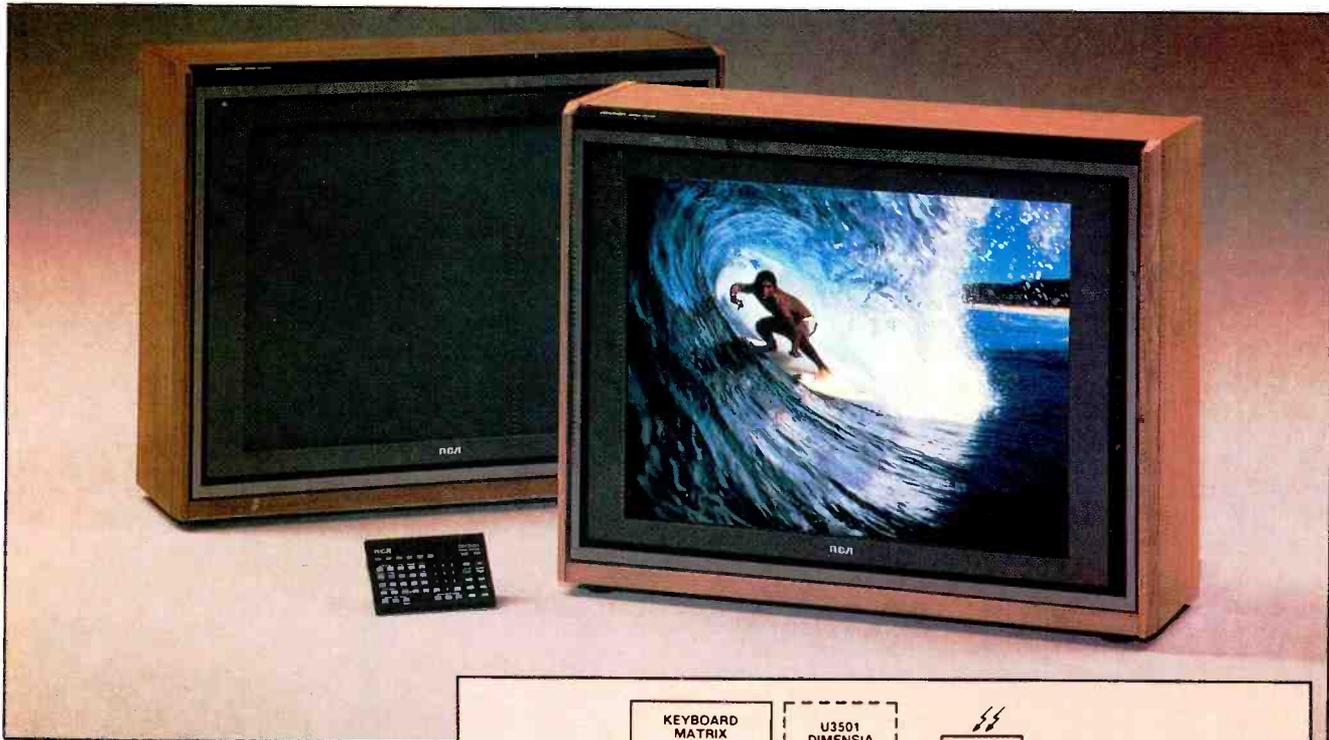


RCA has developed a new unitized chassis system that offers remote control of virtually every picture and sound adjustment, including broadcast stereo sound, alarm and sleep tuners and on-screen tuning.

The control system is a pushbutton operated, memory-equipped digital system with on-screen menus and prompts. The system controls channel and function selection and all video and audio settings, including brightness, sharpness, contrast, color, tint, volume, balance, bass and treble.

Both the tuning system control and MTS broadcast stereo circuits are an integral part of the circuit board. The tuner assembly is a single in-line package (SIP) circuit board soldered directly to the chassis circuit board.

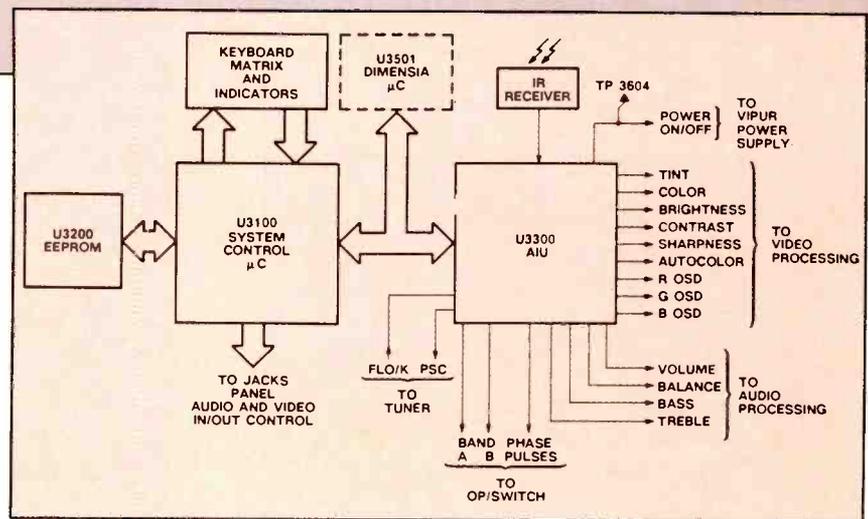The on-screen tuning features multicolored on-screen displays that give information about operating status and also serve as visual guides that assist in selecting and operating the receiver's functions. The tuner can receive 147 non-scrambled cable and standard



broadcast channels. Some models have an electronic RF switch for choosing between two antenna inputs.

To improve serviceability, RCA kept more than 80% of the circuits identical or almost identical to those used in previous RCA unitized chassis. Of the remaining circuits that are different, most are employed in the MTS audio and the system control sections.

RCA also eliminated cabinet screws on the bottom, top and sides of the cabinet, and simplified removal of the chassis to two hold-

down screws and six connectors. The bench setup for full operation with a test jig (including speakers) requires only the connection of the HV anode, kine drive, yoke and front-panel assembly. The company included extra-long cables and wires to eliminate the need for service extension cables and made the ac power cord detachable. Finally, the company included an EIA multiport connector on the back of the TV for checking composite video/audio without removing the cabinet back.

ES&T

Photofact

These Photofact folders for TV receivers and other equipment have been released by Howard W. Sams & Co. since the last report in ES&T.

TELEVISION RECEIVERS:

| | |
|--|--------|
| EMERSON MS198R, MS198RA | 2525-1 |
| GENERAL ELECTRIC 8-1445 (CH. RS-A) | 2528-1 |
| HITACHI CT1376 | 2528-2 |
| PANASONIC CTH-2530/39/60R/69R, PC-26N60R | 2523-1 |
| PANASONIC CTH-2053R, CTJ-2042R/53R | 2527-1 |
| PANASONIC CTH-2600R (CH. NMX-GXLCN) | 2529-1 |
| SEARS 564.42450550/51/52 | 2523-2 |
| SEARS 564.40351650/51 | 2525-2 |
| SEARS 564.48101650, 564.48201650 | 2526-2 |
| SYLVANIA RAF146SL01 | 2526-1 |
| TOSHIBA CX2676, CX2886C/96C, CZ2696 | 2524-2 |
| TOSHIBA CX2006 (CH. TAC8530) | 2527-2 |
| VIDEO CONCEPTS AH1000 (CH. ECC-2801) | 2529-2 |
| MONITOR: | |
| LEADING EDGE 7BM613074G | 2524-1 |

M



M is for...

More selection. Our catalog has an unbeatable line-up of parts and products in stock ready for immediate shipment.

Many new products — over 9000 total items in this new edition.

Money — that's what you'll save with our competitive pricing.

Most important of all — M is for MCM.

No other company can offer you such convenience, selection and fast, friendly service. Check out our new catalog. It's yours **FREE** with no obligation to buy.

Call **TODAY** for your **FREE** copy!


1-800-543-4330

1-800-762-4315

(Ohio)

1-800-858-1849

(Alaska/Hawaii)

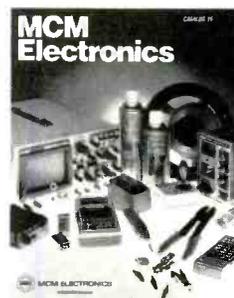


MCM ELECTRONICS

858 E. CONGRESS PARK DR.
CENTERVILLE, OH 45459

A PREMIER Company

SOURCE NO. ES-26

Circle (8) on Reply Card

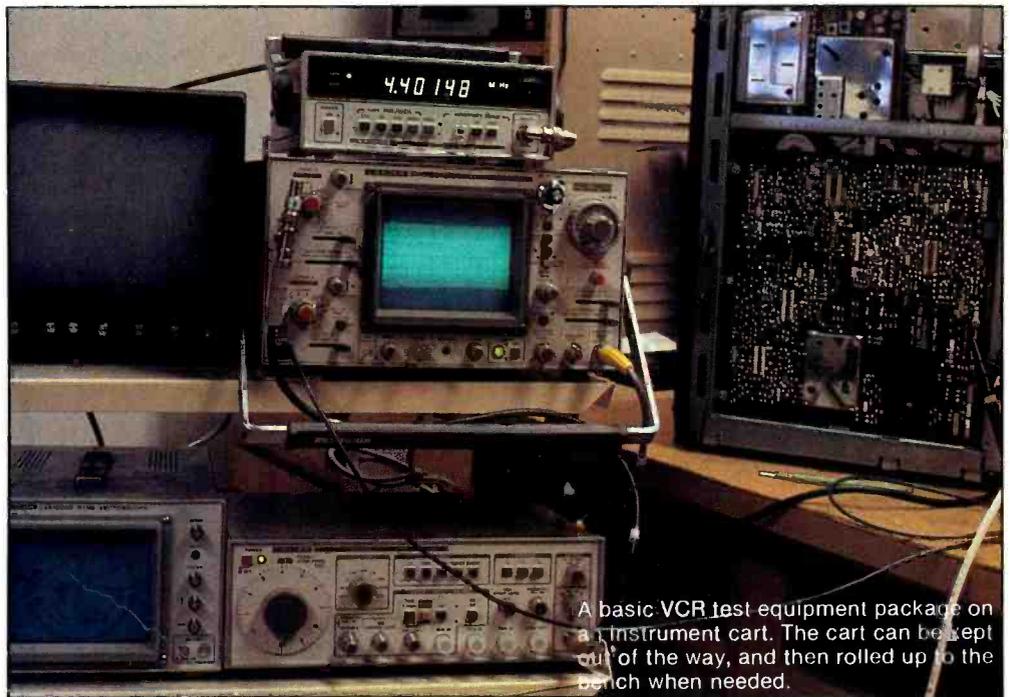

A basic VCR test equipment package on an instrument cart. The cart can be kept out of the way, and then rolled up to the bench when needed.

Test and alignment procedures for VCRs are sometimes time consuming because you have to follow a specific procedure for each model. Just following the steps takes time, as does the search for test points, adjusting points and so on. And I guess we've all had the experience with an adjustment procedure that just doesn't work. It might have been a slip in translation or a procedure borrowed from an earlier model.

This article deals with some basic ways to do alignment checks; some are routine, others are not. The idea is to make things easier, follow procedures that will apply to all models and get maximum help from your test equipment.

Basic setup

The photograph above shows the basic VCR test equipment package on an instrument cart that can be kept out of the way and rolled up to the bench when needed. The heart of the setup is a 35MHz, dual-channel, delayed-sweep scope. The scope, a Leader LBO-324L, has recently been upgraded to 40MHz bandwidth. A frequency counter sits atop the scope and is normally connected to the CH-1 output of the scope. This permits the CH-1 amplifier in the scope to act as a counter pre-amp, and cuts down on the number of test probes in use. The system remains flexible – if you want to do a camera check, you can transfer counter in-

put to the subcarrier output jack for the pattern generator. (See "TV Camera Test Bench – A Setup to Speed Checks and Adjustments" in the April 1986 issue of *ES&T*.)

Just below the scope is a 10MHz function generator (Leader LFG-1310), a very versatile instrument used in one of the methods described for FM modulator deviation adjustments described later. The video monitor is a 9-inch Panasonic black and white with external sync, underscan and pulse cross. It's ideal for camera work, but useful for many VCR checks as well.

The pattern generator produces the standard NTSC color bars in the form shown in practically all VCR service manuals – split-field bars that conform to EIA standard RS-189A. This generator produces other patterns that are extremely

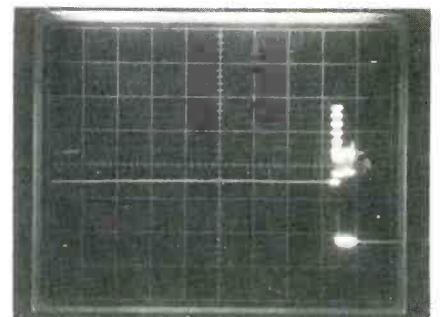


Figure 1. It's easier to check CH-1 and CH-2 if you used delayed sweep with highlighted B time base adjusted to straddle the head-switching transition.

VCR test and alignment procedures

By G. McGinty, CET

useful, such as the window pattern (used in this article to adjust luminance FM deviation), modulated staircase and a video sweep, complete with sync blanking and burst.

Video head switching

Many alignment procedures have been dropped in VCRs because of improvements in design and in component tolerances. Head-switching adjustment remains, however. The reason is that the timing of mechanical events, such as when the video heads slam into tape and when the 60Hz feedback pulse is generated, are determined by mechanical tolerances and are trimmed electronically. Head-switching should be checked every time the heads have been replaced or even if the machine has had a few years of service. To set playback head switching, you need an alignment cassette. These have

been available from the VCR manufacturers, but some produced by independent manufacturers such as Astigmatics have shown up. A dual-channel scope is also necessary. Delayed sweep is not a necessity, but it sure makes things easier.



To do the job you have to search out one internal signal—the head-switching signal, a 30Hz square wave produced on the servo board. Sometimes it's called head switching, sometimes FF (flip flop) or something similar. This signal does a number of things, such as turning on the pre-amp for the head in contact with tape, letting system control know that the scanner is spinning, etc. It can be found on a servo board TP but also in the PB pre-amps and system control.

Find and monitor the head-switching square wave with a 10:1 probe on scope CH-2. And trigger

from CH-2—that's essential. You're monitoring PB video output on CH-1, so video out of the VCR is connected to the CH-1 input with a BNC tee. Terminate the tee, if this is the last stop, or route the cable to the input of the video monitor and terminate there.

Play back the section of the alignment cassette recommended for head switching (usually staircase). Check CH-2 for a stable 30Hz square wave and CH-1 for video amplitude of sufficient amplitude for observation (2cm).

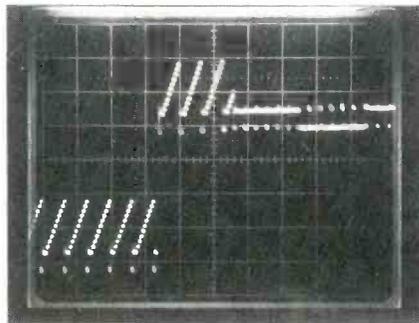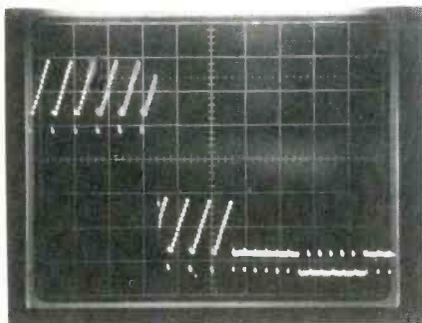I use delayed sweep because you can look at the time span ahead of the head-switching signal. To do this, highlight the A trace with A intensified by B to straddle the time zone of the next switching transition (see Figure 1). Here the scope is triggered by the positive-going edge of the switching square wave (scope slope switch set to +).



A

B

Figure 2. The head-switching signal added to PB output video makes the correct switch location easy to see.

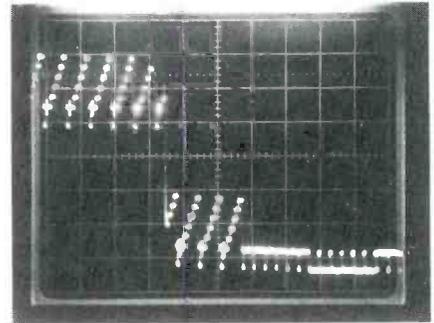


Figure 3. A head-switching adjustment made in the record mode makes the servo follow the accuracy of the alignment cassette.

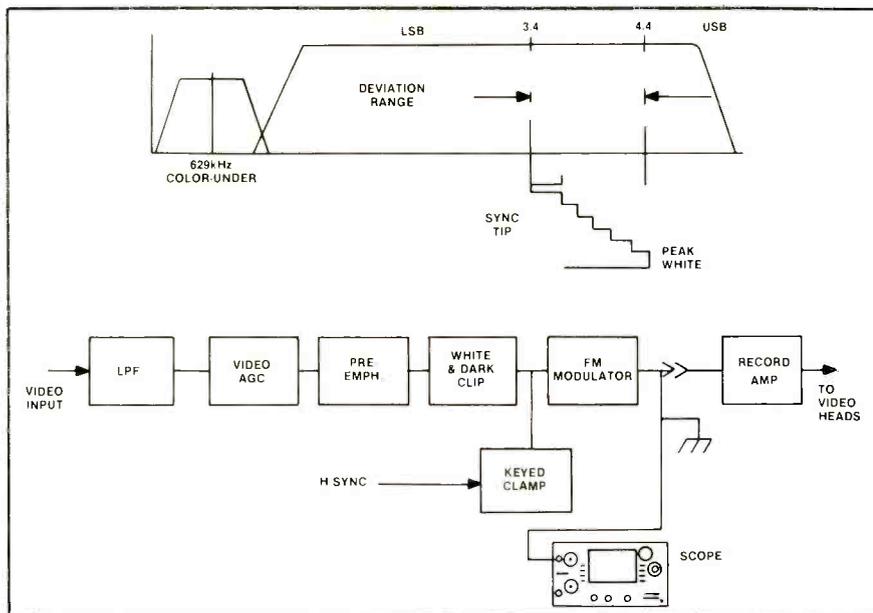


Figure 4. The basic luminance FM processing and deviation range.

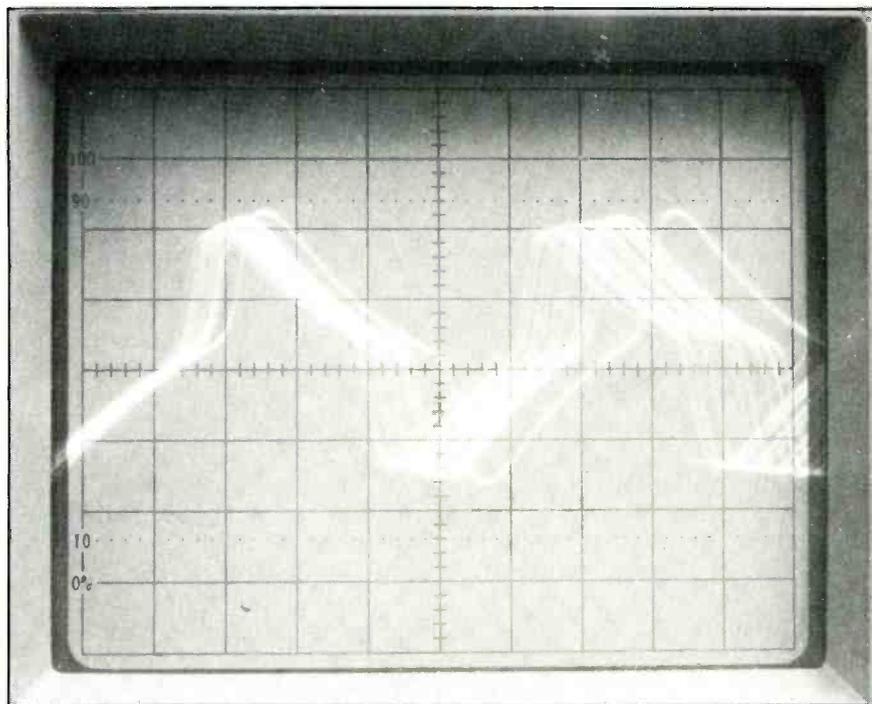


Figure 5. FM modulator output for the color-bar signal shows several discrete periods. (Waveshape is typical.)

The A time base is at 2ms/cm, and the B time base is at 0.1ms/cm, enough to see about 16 horizontal lines that straddle the switching point. The delay pot on the scope is set to make the highlighted B time base straddle the switching excursion as shown. To make the adjustment, switch the VERT MODE switch on the

scope to ADD and set the H DISPLAY to show the B time base (see Figure 2A). Now you see the sum of both waves, and the negative excursion of the head-switching signal shows up as an abrupt step in the video waveform.

The VHS spec calls for the switch to occur 6.5 H lines ahead of V sync. The step makes this very easy to see. V sync is that wide, negative-going pulse with five narrow positive-going slots, the serrations. V blanking starts three lines earlier and contains six of the leading, narrow equalizing pulses.

To the left of V blanking are three horizontal lines of active video plus that half line. That's what the adjustment is made to do. I try one of the two head-switching adjustments by trial and error to find the right one for the switch excursion I'm looking at. Remember, there are two for standard play (2-hour) and another two for extended play (6-hour). You also need an EP alignment cassette for the latter.

To look at the switching point for the other head, simply push the slope polarity button on the scope (see Figure 2B). Now the scope is triggering on the negative head-switching excursion and we're looking at the positive-going step. This time, adjust the remaining delay pot, again for the switching step to occur 6.5 lines ahead of V sync. The waveform looks a little different this time. Note that half line of active video before the start of V blanking. This line denotes the end of field one and the beginning of field two. (The start of field one shows a full line of video before V blanking, as shown in A of the figure.) This time, the adjustment is made for three full lines of video before that half line that occurs before blanking for a full 6.5 lines before sync. In both cases, the adjustment is very easy to see, thanks to the use of delayed sweep and the use of the ADD mode.

When you complete the PB head-switching adjustment using an alignment cassette, you have made the VCR switch video heads at precisely the right time, based

on track location for the recording of V sync—a job we expect the VCR manufacturers to do correctly and under controlled lab conditions. There is more to this adjustment, however. After PB the record servo is adjusted to lay down V sync in exactly the same place, in effect imitating the alignment cassette. The adjustment is called REC PHASE or something like it, and is made in the REC mode with a work cassette. Otherwise, the setup and adjustment is exactly the same. Figure 3 shows the record-mode adjustment using the 5-step staircase produced by the pattern generator.

Luminance modulator

I recently had to replace the IC chip that processes the input luminance signal for recording purposes. I was somewhat frustrated by an alignment procedure for the FM modulator that just didn't work, so I began looking for

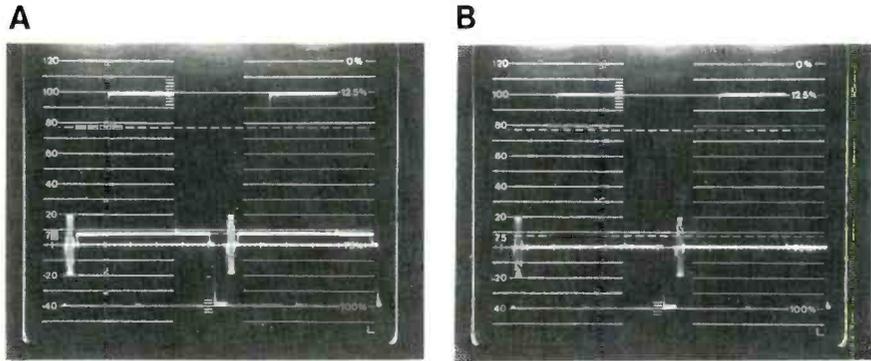



Figure 6. The window signal shown on a waveform monitor: 6A is with setup; 6B is with setup reduced to zero.



Figure 7. This generator permits front-panel adjustment of sync, setup, burst, luminance and chrominance amplitudes. Setup can be reduced to zero.

CIE Cleveland Institute of Electronics

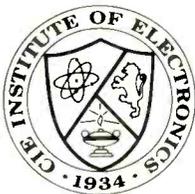Accredited Member National Home Study Council



CIE is the world's largest independent study electronics school. We offer ten courses covering basic electronics to advanced digital and microprocessor technology. An Associate in Applied Science in Electronics Engineering Technology is also offered.

Study at home — no classes. Programs accredited and eligible for VA benefits.

CIE Cleveland Institute of Electronics
1776 East 17th St., Cleveland, Ohio 44114
YES! I want to get started. Send me my CIE school catalog including details about the Associate Degree program.

Print Name _____
Address _____ Apt. _____
City _____ State _____ Zip _____
Age _____ Area Code/Phone No. _____

Check box for G.I. Bulletin on Educational Benefits
 Veteran Active Duty **MAIL TODAY!**

AES-27

Circle (9) on Reply Card

Acu-Min® Precision Miniature Tools for Industry

Precision Miniature Tools

For Electronics Professionals Worldwide

- ➔ Slotted Screwdrivers
- ➔ Cross Recess Drivers
- ➔ English Hex Drivers
- ➔ Metric Hex Drivers
- ➔ Open End Wrenches
- ➔ Socket/Nut Drivers
- ➔ Spline Drivers
- ➔ Tweezers



PLUS An all new line-up of high quality Precision Measuring Tools, including micrometers, calipers, dial indicators, scribes and more.

1-800-223-9036
Sales & Customer Service
401-885-0911
in Rhode Island and Alaska

Over 400 Precision Products
in our NEW Catalog.
Call now for your copy.

Moody Tools, Inc.
42-60 Crompton Avenue
East Greenwich, RI 02818

Circle (10) on Reply Card

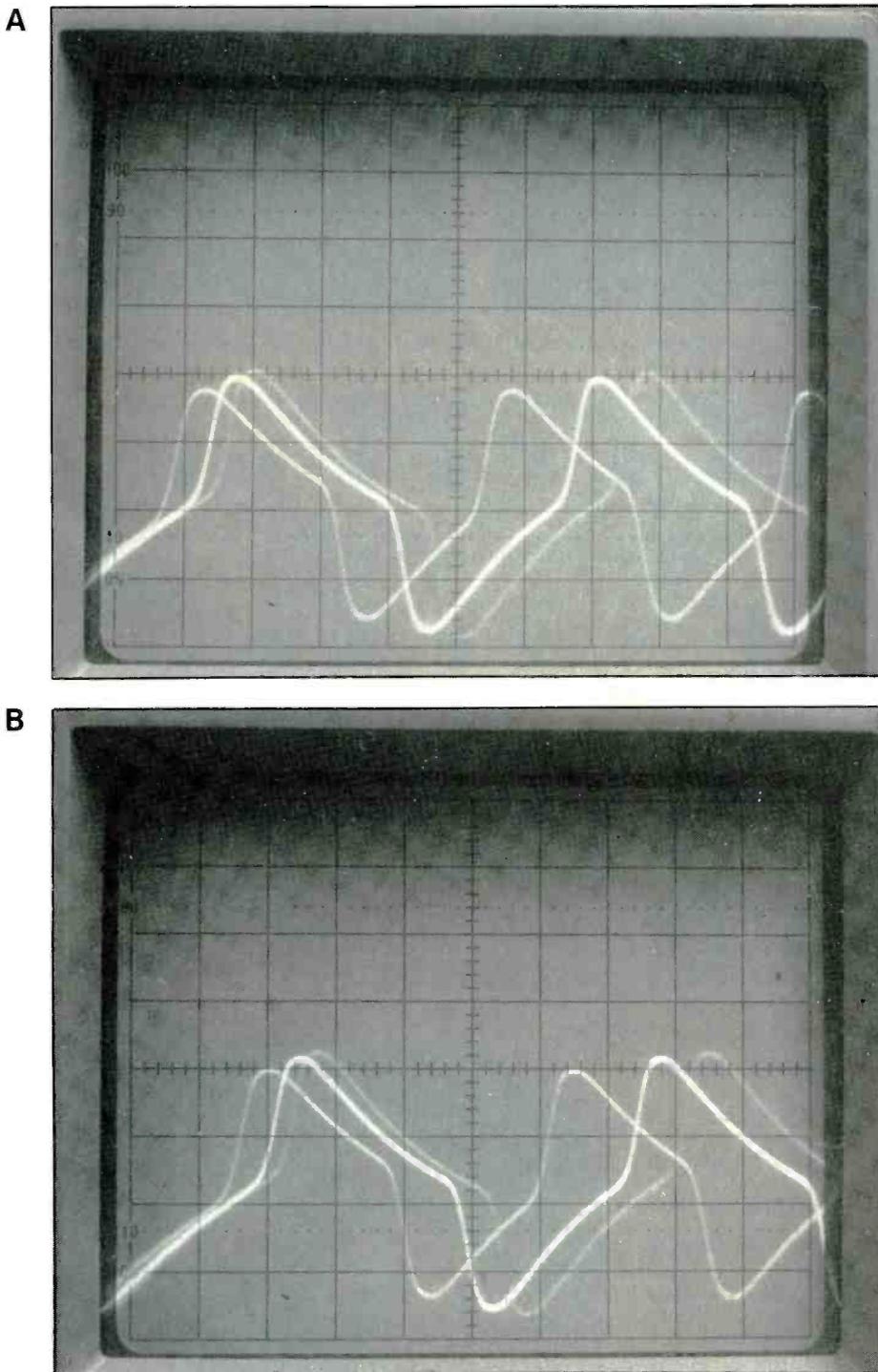


Figure 8. These three waves represent sync-tip frequency (longest period), black (brightest wave) and peak white (shortest period).

alternatives and, hopefully, universal ways of doing it. The following are two simple alternatives to the factory procedure.

Following Y-AGC and the white and black clip adjustments, the FM modulator must be set up to cover the correct deviation range for the

full video excursion from sync tip to peak white. Figure 4 shows the deviation range, FM sidebands and color-under slot for the VHS system. The picture shows a drop-off in upper sidebands that really tells the story of the high frequency limits of what the playback process does. Farther into the tape, both upper and lower FM sidebands are present.

Many schemes are in use for setting the deviation range, that is, the frequencies at which the FM modulator works at the signal limits of sync tip and peak white. It was easy for older VCRs that used a diode clamp circuit to clamp sync tip to an adjustable dc voltage at the input to the modulator. Just remove the signal and the modulator runs at the sync tip frequency. All you need is a frequency counter.

However, most systems now use a *keyed* clamp. In the absence of input video, the dc voltage input to the FM modulator is just about meaningless. Thus, the adjustment procedure must be done with a normal signal applied. Existing factory procedures often involve elaborate substitutions or heterodyne techniques that involve complex in-circuit connections. I looked for a scheme that requires only one observation point in the VCR, the output of the FM modulator or the input to the Y record amp.

Why not period?

This technique requires a scope with an accurate time base capable of measuring the *period* of the signal in the range of 200ns to 300ns ($0.5\mu\text{S}/\text{cm}$ with a X10 magnifier yields 50ns/cm, just right). The idea is to measure the period of the FM wave out of the modulator for both sync tip and peak white video levels.

Figure 5 shows the output of the FM modulator on a typical VHS VCR when standard color bars are applied as the input signal. The scope is synced internally on the signal being observed with a 50ns/cm time base. You can see that FM is taking place because there are a number of signals with differing periods—one for each

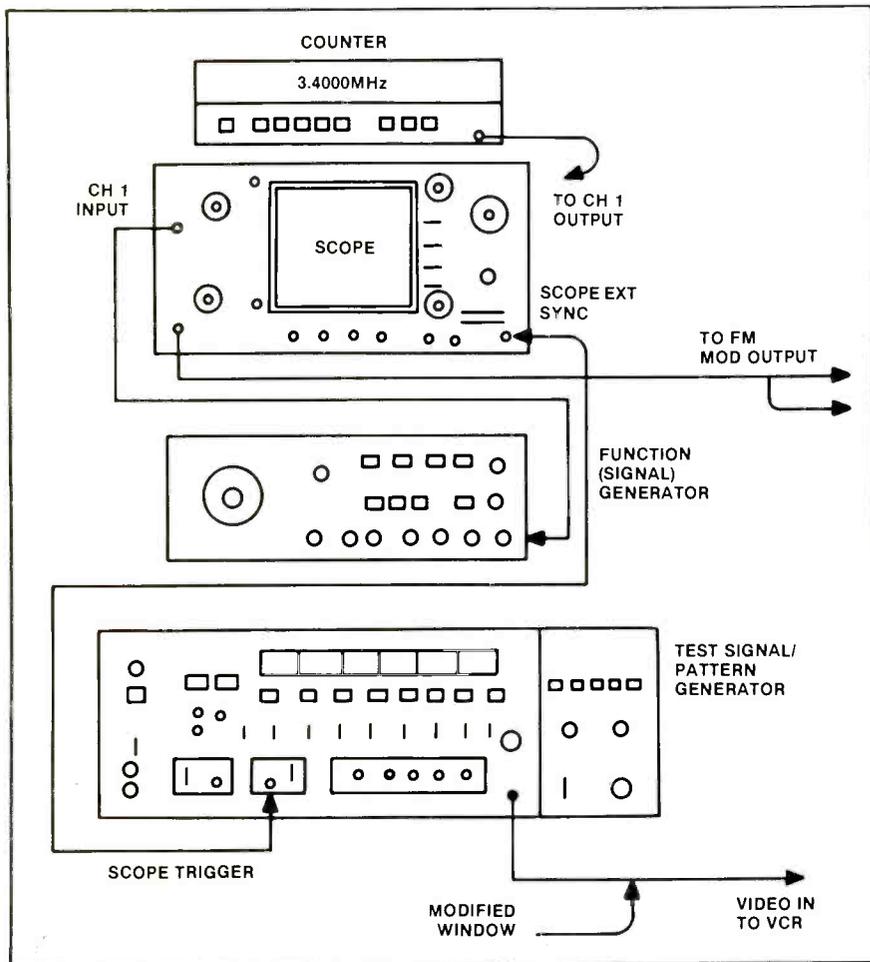


Figure 9. System hookup for the heterodyne method of deviation adjustment.

luminance step in the color-bar waveform as well as steps for blanking, setup and sync tip: too many signals of which to make sense. What's needed is the simplest signal you can devise—one that has a minimum number of levels and still represents typical video so clamp circuits and others continue to work normally.


The solution is the window signal. It normally has only four levels: peak white, sync tip, blanking and setup. The window signal is a good, simple video signal. The center half of the picture is white, the rest black, yielding a 50% average picture level. Figure 6A shows the 2H waveform for the standard window signal taken on a waveform monitor. The black level is as shown at 7.5% (7.5IRE) and peak white is at 100% (100IRE on the scale at the left). If you apply this signal to a VCR, the FM modula-

tor operates at four discrete frequencies.

To make the situation even simpler, that 7.5% setup can be eliminated, leaving only three discrete frequencies. Figure 6B shows the window waveform with setup reduced to zero and luminance reset to bring it back to 100%. Fortunately, this generator permits these adjustments from the front panel (see Figure 7). With SETUP turned fully CCW, it goes to zero and "black" is the same as the blanking level (as it was originally intended to be).

When the modified window signal is applied, the FM modulator works at only three frequencies: sync tip, blanking and peak white, as shown in Figure 8A. The traces are not equally bright. The modulator operates at the sync tip frequency for the shortest period of time so its wave is the dimmest.

ELENCO PRODUCTS AT DISCOUNT PRICES!

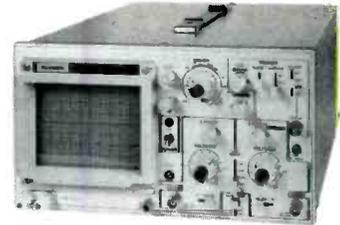

20 MHz Dual Trace Oscilloscope \$359.95 MO-1251

Two 1x, 10x 100 MHz probes, diagrams and manual included. Write for specs.
35 MHz \$499.95 MO-1252



GF-8016 Function Generator with freq. counter


\$239.95

Sine, Square, Triangle
Pulse, Ramp, .2 to 2 MHz
Frequency .1 thru 10 MHz

GF-8015 without freq. meter \$179

Triple Power Supply XP-660

0-20V @ 1A
0-20V @ 1A
5V @ 5A

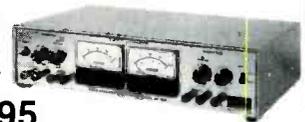

\$159.95

Fully regulated, short circuit protected
with 2 limit cont. 3 separate supplies

3 Amp Power Supply XP-650

0-40V @ 1.5A
0-20V @ 3A



\$129.95

Fully regulated, short circuit protected
current limit control

Color Convergence Generator



SG-200

\$69.95

Finest in the industry
10 rock steady patterns

Multimeter with Capacitance and Transistor Tester

Model CM-1500A
with case

\$64.95

Reads volts, ohms, current,
capacitors, transistors, diodes



Digital LCR Meter **\$148.95**



Model LC-1800

Measures: Inductors
Capacitors, Resistors
Inductors 1uH to 200H
Capacitor .1pF to 200uF
Resistor .01 Ohms to 20M Ohms
Ranges 6 Ind, 7 cap, 7 res

C + S Sales, Inc., 1245 Rosewood
Dr., Deerfield, IL 60015. 800-
292-7711. 312-459-9040. ASK
FOR CATALOG. Add 5% P&H
(\$10 max. per item) IL Res.,
add 7% sales tax



Circle (11) on Reply Card

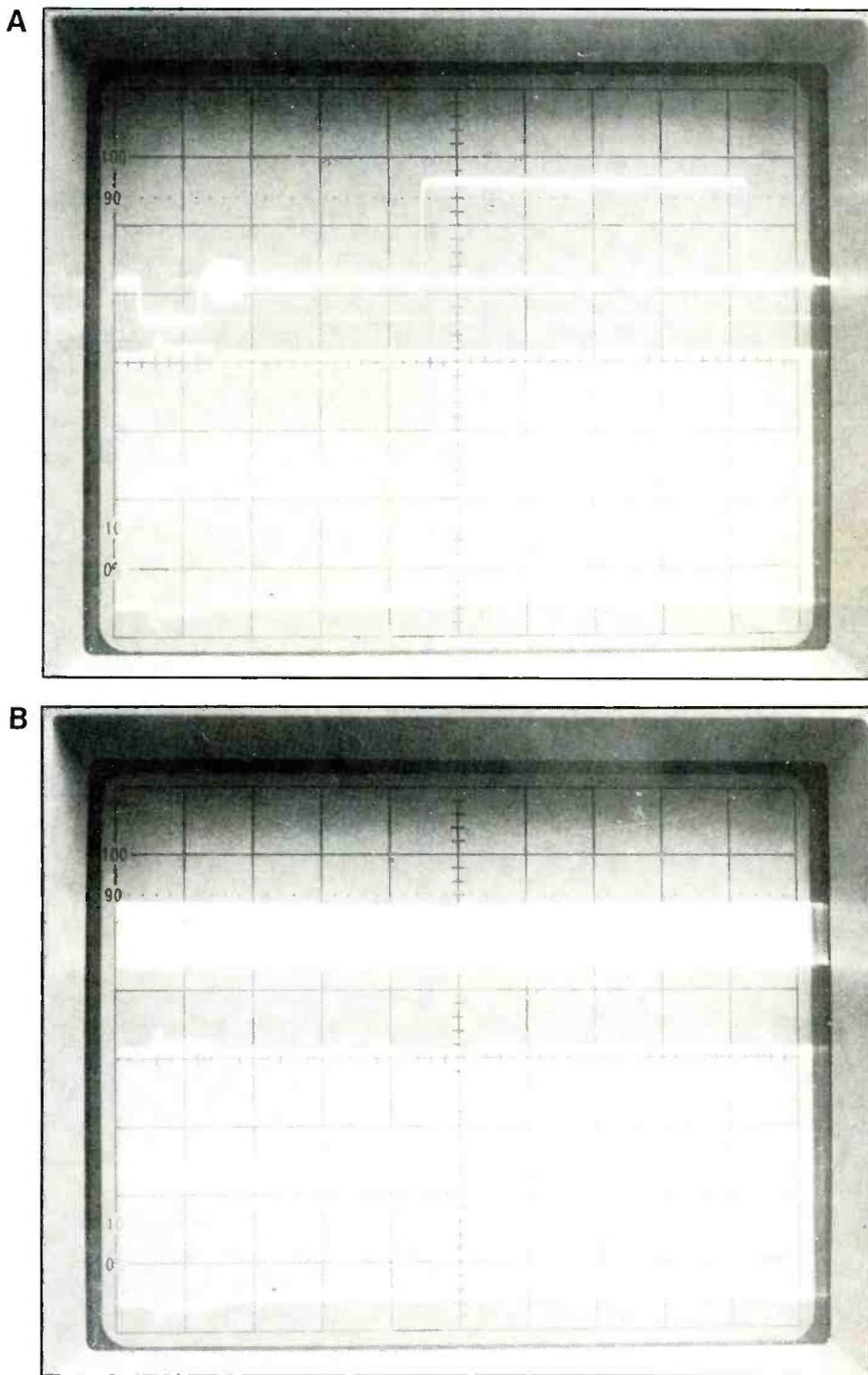


Figure 10. Heterodyne waveforms: 10A shows the window waveform, on top, and the modulator output, on bottom; 10B shows the CW signal, on top, and the modulator output, on bottom.

The modulator spends most time at black so its wave is the brightest, but we'll ignore the blanking period. We are interested in the lowest frequency (sync tip) with the longest period and in the highest frequency (peak white) with the shortest period.

Frequency vs. period

| | Frequency | Period (1/f) |
|------------|-----------|-----------------|
| Sync tip | 3.4MHz | 294ns |
| Peak white | 4.4MHz | 227ns |

In Figure 8A, centering has been adjusted to put the longest (and dimmest) wave peak at the second graticule line from the left with the peak on the horizontal graticule line with the minor graduations. Counting to the next peak of this longest and dimmest wave, you'll see 5.8cm. This multiplied by 50ns/cm yields 290ns—close enough. If you are making adjustments at sync tip frequency, set your oscilloscope for 5.8 divisions.

Figure 8B shows scope centering reset to look at the shortest (highest frequency) wave. This time there are 4.5 divisions for 255ns, close enough to 227, which will allow adjustment of *deviation* (usually AGC gain) for a period of 4.5 divisions.

Heterodyne method

The method I prefer doesn't require the tedium of measuring period, but the indication takes some getting used to and is almost impossible to photograph. The setup is as shown in Figure 9. The scope must be triggered externally from the H DRIVE SCOPE TRIGGER signal provided by the generator, and I'll use the modified window again. The output of the VCR FM modulator is monitored on CH-2 of the scope. To start with, put generator video on CH-1. Figure 10 shows both waveforms in the ALT mode. I reset the time base (out of calibration) so one line occupies the width of the screen. Make a mental note of those parts of the display taken up for sync tip and peak white. You can also spot these on the modulator waveform, because modulator output is seldom equal at all frequencies.

Next, output of the signal generator is applied to CH-1 where you can also accurately monitor frequency with the frequency counter connected to CH-1 output. Scope gains should be set for about four divisions of the FM modulator

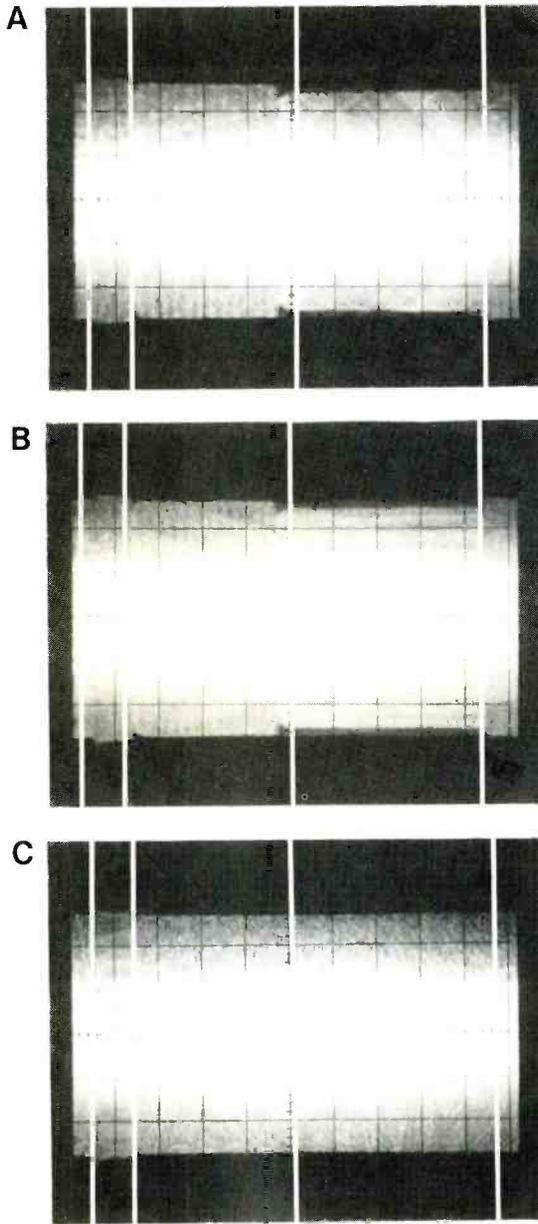


Figure 11. Heterodyne waveforms show zero beat at peak white (11B) and sync tip (11C). If the generator is set midway between, as in 11A, you just get a jumble of signal.

signal and two divisions of the generator signal.

The VERT MODE switch on the scope is then set to ADD. This will allow you to see a zero beat between the CW signal from the generator and the output of the modulator. Figure 11A shows what it looks like when the generator is set midway between the correct sync tip and peak white frequencies—just a jumble of signal. With the generator set to 4.4MHz and deviation set correctly in the VCR, a zero beat occurs in that part of the waveform where you noted that peak white resides (refer back to Figure 10).

The zero beat appears when all the lines in the peak white zone of the waveform flatten out and become a bunch of horizontal parallel lines (see Figure 11B). This is much easier to see on the

TENTEL® MAKES IT EASY TO DIAGNOSE VCR MECHANICS

Award winning Tentelometer tape tension gauge for proper interchange and tape handling. One gauge for Beta, VHS and U-Matic.

T2-H7-UM **\$295**

Torque gauge NEW from Tentel to save you money— Universal and accurate for Beta and VHS— 0 to 600 gm cm. Take-up, FF and Rew torques.

TQ608 **\$139**

Head protrusion and eccentricity gauge to determine the amount of wear remaining on the VCR heads; safe, easy, measures in microns.

HPG-1 **\$479**

Spindle height and elevator latch and alignment gauge to diagnose cassette binding and edge damage problems. Finds problems not detected by any other method.

TSH-V4 **\$395**

Tentel manufactures a complete line of gauges for U-matic, 1" Type "C", Betacam and other recorders, too. If you've suffered the frustration of having a master tape ruined, or if you are responsible for maintaining and repairing VCRs— There's no faster, easier method to test the various mechanics that make VCRs work properly. Call our technical engineering dept. for details—ask about the combo discount for all 4 gauges. We've been helping customers for years and want to help you too—your satisfaction is guaranteed.

TENTEL® CORP. 1506 Dell Ave.
Campbell, CA 95008

(408) 379-1881
800 538-6894 (Not in CA)

Circle (12) on Reply Card

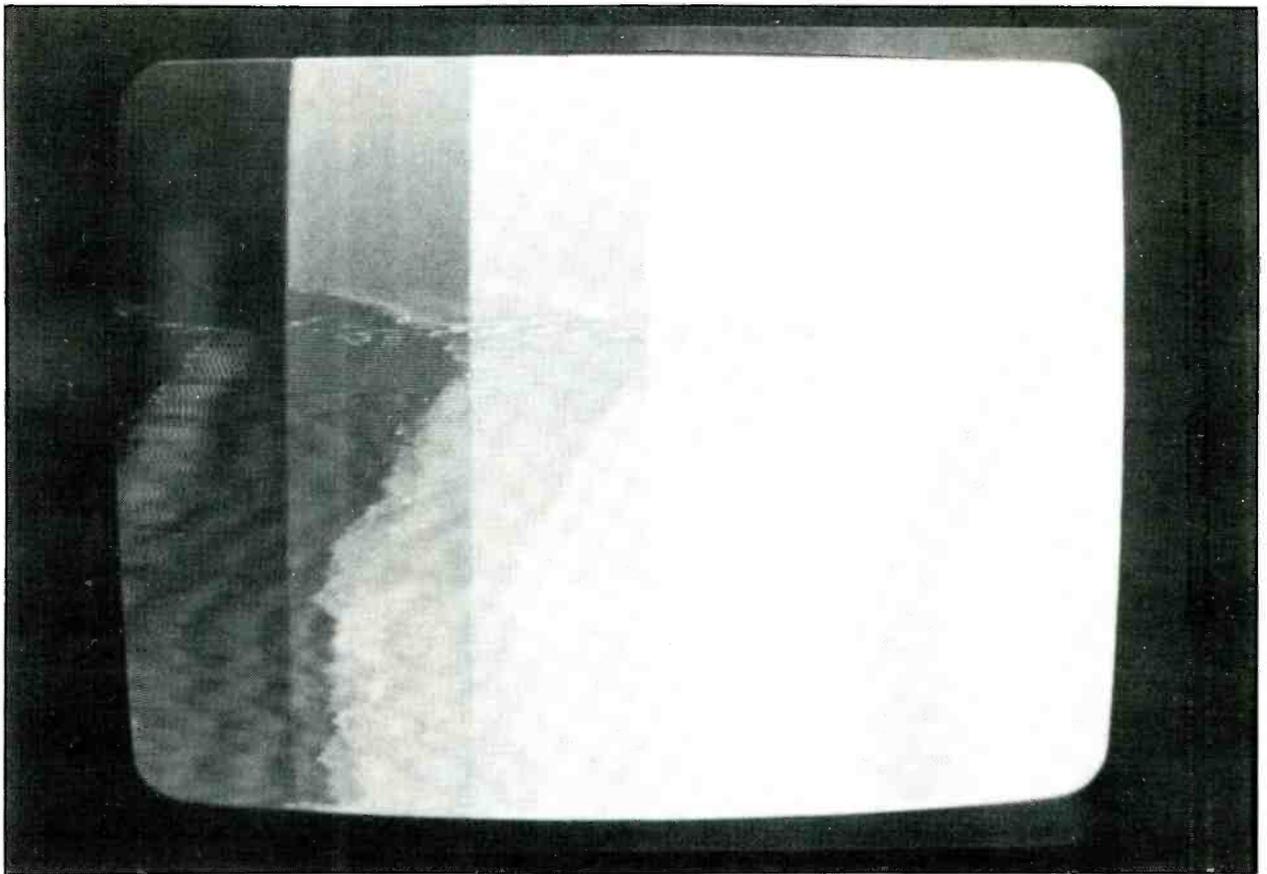


Figure 12. This symptom is caused by bad relay contacts in the relay that selects PB output from SP or EP video heads.

scope than it is to photograph because the patterns change and move due to drift, and the exposure time dictated by the camera causes the picture to blur.

Set the generator to 3.4MHz and set the sync tip adjustment for an indication of zero beat at the sync tip area (see Figure 11C). Although this method involves an indication that is somewhat difficult to recognize, it requires only one simple connection to the VCR and makes use of the accuracy of the frequency counter.

A common problem bonus

The VCR with the modulator fault had two problems. The second problem is very common and often intermittent. I had my film camera set up, so I took the picture of Figure 12. This problem has nothing to do with test equipment use, but it represents a symptom that can be recognized on sight and might save you a lot of time and trouble. The symptom looks like mistracking and is often

confused with it. A beat appears in the picture.

In the standard play mode, the clue to the problem is that clear band of picture at the top. This problem is caused by bad contact on the relay in the video head circuit that selects the standard-play or extended-play heads. The relay does so by shorting out the unused heads for either mode.

However, bad contacts make the shorting action ineffective and both heads pick up signal. What you see is a beat between the signal picked up by both SP and EP heads. The EP heads are mounted to slam into tape later than the SP heads, so they don't contribute anything until the SP heads have been working for part of their swipe. Before the EP heads hit tape, the picture is clear. The EP picture has an opposite symptom; the bottom of the picture is clear. The remedy is always the same—replace the relay. This is easy on some models, a bear on others.

ES&T_{inc}

Literature

Video test notes

Leader Instruments is offering a series of application notes designed to augment available technical information in the application of video test equipment. The "Teleproduction Test" notes explain basic concepts and routine test procedures and offer shortcuts to complex VCR and video camera alignment procedures.

The first three issues are primers in the use of the waveform monitor. The fourth issue starts a similar series on the basic aspects of the vector scope - what it shows and how it is used to evaluate color performance and in-phase matching of several video sources.

The fifth and sixth issues will discuss the basic operation of the vectorscope, showing how checks are made and how the vectorscope serves to bring a multicamera system into the proper phase relationship for flawless operation.

Circle (125) on Reply Card

RF design guide

Multiplex Technology is offering an illustrated, 4-page brochure for installers to use as a guide when designing RF systems. The guide offers seven steps that take the installer from setting the picture quality objective to the final system layout. A system worksheet is included for the installer to figure attenuation losses and quantities of components required.

The guide discusses when to use splitters or taps and covers system losses in various types of cable and components and at various frequencies. The guide also give three diagrammed examples of RF systems using an RF amplifier.

Circle (126) on Reply Card

Parts and tool brochure

A new line of parts, tools and service aids for audio and videotape equipment is described in an 18-page brochure now available from the distributors and special markets division of *Philips ECG*.

The fully illustrated brochure contains information on audiotape and VCR test cassettes, tape repair kits and precision adjustment tools for VHS and Beta VCRs, lubricants and cleaning materials for audio and video equipment, opto sensing devices, replacement belts and head assemblies for VCR units.

The replacement parts section lists cross-references by equipment manufacturers' model number for belt kits and video heads and includes comprehensive cross-reference charts by part numbers, for individual belts, heads and sensing devices.


Circle (127) on Reply Card



Matsushita Services Company

Panasonic Technics Quasar

Training Materials

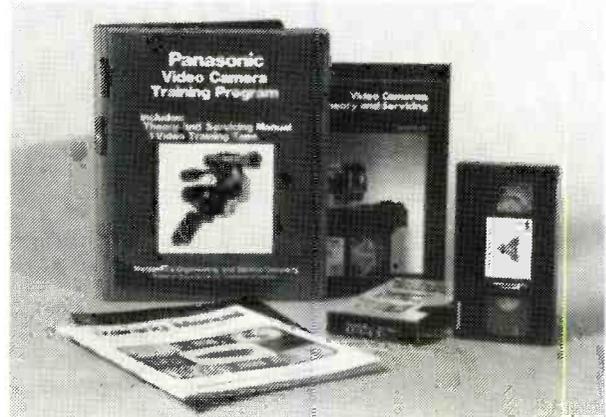

Introducing two new additions to our growing videotape library; TT-A08 "The Basics of Compact Disc" and TT-V43 "What is a CCD VHS Movie".

The TT-A08 is an overview of the complex Compact Disc audio system, while the TT-V43 describes the Charge Coupled Device and its application to color camcorder technology. These tapes are available for the price of \$32.95 each (\$29.95 each plus 10% shipping and handling).

To order these new releases, or to receive a free catalog listing all of our training materials, mail the coupon below to:

Matsushita Services Company
ESD/Publications 2B-6
50 Meadowland Parkway
Secaucus, N.J. 07094

Please send me the following:

- TT-A08 "The Basics of Compact Disc"
- TT-V43 "What is a CCD VHS Movie?"
- Free Training Materials Catalog

My check for \$ _____ is enclosed.

SHIP TO:

Name _____

Company _____

Address _____

City _____ State _____ Zip _____

Please allow 4-6 weeks for delivery. N.J. residents please add \$1.80 N.J. state sales tax.

Circle (13) on Reply Card

Ruling out static

Three basic rules of static protection will protect not only static-sensitive equipment, but also your reputation

By Dixon Gleeson

This article was adapted from the article "Ruling Out Static," which was originally published in the September 1986 issue of Microservice Management magazine.

Cost of device failure in the computer industry

| Point of failure detection | Economic cost | Intangible cost |
|----------------------------|--|--|
| Device level | Device cost, if not returned to vendor, plus test costs. | Back orders Production delays Investment in surplus inventory and storage to cover failed devices. |
| Board level | \$15 | Production slowdown Lower yields Employee frustration |
| System level | \$150 | Late shipments Disrupted production schedule |
| In the field | \$1,500 | Loss of customer goodwill Detrimental effect on market — present and future |

Not too many years ago, static was simply an irritant around the house—a zap from the doorknob on a cold, dry night, a strange force field in front of the TV screen that acted like a magnet for dust and made cleaning difficult, or something that made your hair stand on end after you combed it.

Then electronics manufacturers began to realize that static electricity was more than an irritant. It was causing millions of dollars in damage to their sensitive parts. New microminiature devices were being destroyed or degraded by voltage levels of static so low that no one even noticed. Static became known as the silent killer.

Components that were catastrophically damaged would simply cease to function and were normally caught by outgoing inspection. However, the parts that were only degraded by static, the walking wounded, usually eluded detection and made it to the field. Once there, they often would operate erratically or fail prematurely.

The result was a marked increase in service problems, such as early field failures, intermittent and difficult-to-diagnose problems, more DOA (dead on arrival) boards and larger spare inventories. Service costs grew dramatically.

Many companies eventually discovered that it's a worthwhile investment for service technicians, spares storage and handling, and repair facilities to use the same static-control processes used in manufacturing.

The static control solution

If you are going to avoid electrostatic discharge damage, your organization must operate under the same three rules for static control recognized throughout the electronics industry.

- *Rule 1:* Handle static-sensitive devices only at a static-safeguarded work area.

Gleeson is market development manager of the Static Control Division of 3M, Austin, TX.



- *Rule 2:* Transport static-sensitive devices only in static-shielding packages.

- *Rule 3:* Make certain that your suppliers follow rules 1 and 2.

Inside the servicing facility

First, rule 1 involves protecting static-sensitive devices at permanently installed work stations, and requires two steps:

1. Remove static charge from conductors (including people) by grounding.
2. Neutralize static charge on non-conductors with ionized air.

The static control products commonly used to accomplish these two tasks are now widely accepted: static-dissipating table mats and floor mats, conductive wrist bands and ground cords for personnel, and ionized air blowers for controlling static on the non-conductors in the area (polystyrene coffee cups, vinyl work-order holders and cellophane cigarette wrappers). Such a system is quite effective if installed properly, audited regularly and explained accurately to the users.

Rule 2 is also fairly simple. While sensitive electronics are being handled by a properly grounded worker at a work station that is safeguarded as outlined above, they are protected from static damage. However, whenever those parts must be removed from that work station and might be handled by ungrounded personnel, they should first be put into some type of static-shielding package. A static-shielding package is defined as one that protects its contents from all three potential static problems: triboelectric charges (charges generated by friction), electrostatic discharge (current) and electrostatic fields (voltage).

Many types of packaging on the market today claim to be static-protective. However, it is impor-

tant that you not confuse static-protective with static-shielding. Not all such packages protect against all three static threats. Let's take a moment to examine why this is so important.

- *Triboelectric charges.* Any time two surfaces come into contact and then separate, one surface will gain electrons and the other will give them up, so that both surfaces become charged. Such frictional charging is termed triboelectric. Because components naturally shift around inside a package during handling and transport, it is important that the material used as the inner layer of the container prevents triboelectric charging caused by this movement.

- *Electrostatic discharge.* A true static-shielding package will also prevent the penetration of a static discharge or spark. Because such a discharge is really a tiny arc of electric current from one charged object to another or to ground, it can be blocked by including an adequate dielectric or insulating layer in the protective package.

- *Electrostatic fields.* The majority of electronic devices used today are field-sensitive. That is, they operate by virtue of changes in voltage. As such, they are also sensitive to damage from electrostatic fields. Therefore, a true static-shielding package must not allow the penetration of such fields. This requires that the package include a highly conductive layer that can act as a Faraday Cage around the contents.

An important point to remember about static-protective packaging: Many bag manufacturers produce what they call a transparent antistatic bag, usually tinted pink or blue. Although such bags do have a low level of surface conductivity because of a chemical additive that draws moisture from the air to the bag's surface, they are not nearly conductive enough to offer shielding against electrostatic fields. In

fact, when the air is dry and the potential for static generation is the highest, such antistatic bags are at their weakest.

To reiterate rule 2: Any time a sensitive component or assembly must be removed from a static-safeguarded work area, it should first be packaged in a static-shielding container, and should not be removed from that container by anyone who is not properly grounded or at another protected work station.

Rule 3 is easy to understand and applies equally to a manufacturing or a service situation. Make sure your suppliers of sensitive devices follow rules one and two. You should not have to inherit the liability for damaged or degraded parts from vendors.

Even though static control is important in the plant and has been shown to provide tremendous returns on the manufacturer's investment, it is more critical and cost-effective in the field.

In the field service environment

As mentioned at the beginning of this article, there are two types of damage caused by static: complete destruction and degradation. Catastrophic failures, although expensive, can be detected before the parts leave the plant. However, degraded or weakened devices can make it past quality control and usually find their way into customers' hands before they fail. Then this costly and troublesome problem falls to the technician.

Computer industry estimates indicate that correcting a static-caused defect in an individual component costs a company only the value of that part if the defect is noticed at the device level. However, if the defect is not discovered until after the device has been mounted on a PC board, that cost rises to about \$15 because of

quality-control time, extra handling and rework.

If the faulty part is not found until after it has become part of finished assembly, the cost is then estimated to be about \$150. If it doesn't show up until the component is in the customer's hands and then results in a service call, the total cost for the company averages about \$1,500. (See the table on page 26.)

Because it is estimated that about 90% of all static damage results in weakened devices and latent failures rather than immediate, catastrophic failures, it is obvious that most damaged devices will fall into this last, most expensive category.

It is absolutely essential that static control be brought into the field. It really is a similar process

to that described for the plant.

Rule 1: Field service technicians' work sites are never permanent, because the technicians must move about. However, it is still possible to have a properly static-safeguarded work station anywhere. Technicians should carry in their tool kit a portable, static-dissipative field service kit.

These kits consist of a lightweight, foldable mat of static-dissipating material, a wrist band for the technician to wear and grounding cords and clips to connect both components together and to ground. The foldable kit fits into a standard tool case or pouch, and should be the first item removed on a service call.

The mat is unfolded and connected to ground by the cord provided. The wrist band is slipped on and

also connected to ground. The mat offers a static-free area you can lay sensitive parts on, and the wrist band and cord prevent charges from building up on the technician's body. (It should be noted here that the technician's practice of touching the equipment frame occasionally to drain static from the body is not an adequate procedure. As soon as the frame is let go, body movements are enough to build up additional new charges that can damage components.)

Aside from the portability, the only way this field work site now differs from a permanent static-safeguarded work station in a plant is that it does not include an ionized air blower to neutralize the static charge on nonconductors. Because it would be impractical to carry the type of ionizer used to-


CIRCUIT TRANSPORT CASES

Physical and static protection for valuable circuit boards.

Put tough protection around your expensive circuits during transit and storage with economical "Fortress" cases from Atrix. These double-wall units guard against static, RF and EMI, as well as mechanical stress.

- Rugged layered construction — ABS plastic over aluminum
- Sizes to suit various circuit boards — 24 models from 12 x 14 to 18 x 24 inches, all 8-inches wide, custom sizes also available
- Supplied with static dissipative Z-fold foam packing and tie-down straps
- Flush handle, sealable latches, stackable in any combination of sizes, with case-to-case grounding

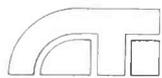
Call the Atrix Easy-Order 800 Number for fast service.



ATRIX, INC 14221 Ewing Avenue South Burnsville, MN 55337

(612) 894-6154 1-800-222-6154 FAX (612) 894-6256 Telex 9102400139

Circle (35) on Reply Card

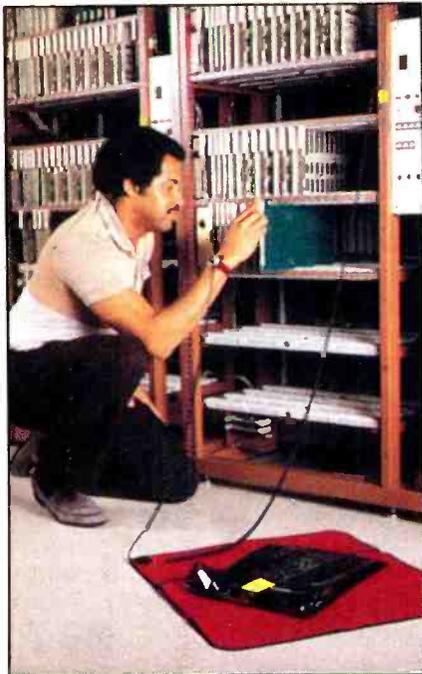

Static-dissipative service kits provide a static-safeguarded work area for a service technician on site.



Some static-shielding bags provide total protection against static charges and also offer greater security for the contents with a new single-track closure mechanism.

day to each job site, it is doubly important for the technician to remember to keep such things as nylon windbreakers, common plastics and vinyl work-order folders from the sensitive components.

Rule 2: All sensitive spare parts being stored or handled by service technicians in the field should already have been packaged in static-shielding bags or containers. If they were properly static-protected during manufacture and have been stored in static-shielding packaging since they left assembly, then DOA rates should be minimal.

It is then the technicians' responsibility to make sure they wear a grounded wrist strap before unpacking the spare. The final important step is to repack the faulty board in a static-shielding container so that it will suffer no additional damage during the return trip to be repaired.

Rule 3: Every service organization should insist that its suppliers adhere to rules one and two.

Static control products

Quite a few products are uniquely adapted to fulfill the static control needs of servicing technicians. Some of these are general products that also have wide application in manufacturing, but others have been developed specifically for field service.

Rule 1 products: The basic rule 1 product has already been described—the portable, static-dissipative kit, consisting of a static-free work surface, a conductive wrist band and a ground cord system to connect the components together to ground.

Rule 2 products: The most common static-shielding container, even in field service, is the transparent static-shielding bag. (This transparency is, of course, an important feature for field service, because it allows a technician to verify the contents of the package without opening it up and exposing them to static.)

STOP YOU'VE TRIED THE REST - NOW TRY THE BEST!

THE MOST COMPLETE ONE STOP CATALOG IN THE INDUSTRY
DRASTIC DISCOUNT ON NAME BRANDS
QUALITY PRODUCTS & SERVICE YOU CAN COUNT ON

KENWOOD

150 MHz 60 MHz
100 MHz 40 MHz
70 MHz 20 MHz

STORAGE SCOPES!

NEW



Industrial Quality Power Supplies

BK PRECISION

20 MHz DUAL TRACE

MODEL 2120

Reg. \$470.00

OUR PRICE \$395.00

- Includes Probes
- TV V & TV H
- Single or Dual Trace Operation



NOTE WE STOCK ENTIRE LINES OF KENWOOD, B&K, BECKMAN, VIZ, HITACHI & FLUKE TEST EQUIPMENT
CALL US TOLL FREE FOR DISCOUNT PRICES

CABLE CONVERTERS



MODEL MR-702

72 Ch Wireless Remote Control

\$73.99 ea.

10-up \$69.99 ea.

BOGEN



P.A. AMPLIFIER

CALL FOR YOUR DISCOUNT PRICES ON ALL BOGEN AMPLIFIERS & INTERCOMS IN STOCK

ALSO STOCKED

| | |
|------------------------|------------------|
| Antennas | Chemicals |
| Antenna Amps & Preamps | Semiconductors |
| Video Accessories | Flybacks |
| VCR Tires | Triplers |
| VCR Belts | Tools |
| VCR Rollers & Idlers | Soldering Equip. |
| VCR Heads | Background Sound |
| VCR Tools | Speakers |
| Tubes | Intercoms |

CALL TOLL FREE FOR OUR NEW 1988 CATALOG

R. N. J. ELECTRONICS, INC.

805 ALBANY AVENUE • P.O. BOX 528
LINDENHURST, NEW YORK 11757

800-645-5833

Ask For Free Catalog

516-226-2700

PHONE ORDERS WELCOME
VISA, MC & COD'S ACCEPTED
ADD 5% Shipping (\$10 Maximum)

Circle (14) on Reply Card



A typical static-protected work station includes mats, wrist straps and an ionized air blower.

However, packaging has actually gotten quite a bit more sophisticated in the past few years.

- The standard static-shielding bag has been modified to include a layer of cushioning antistatic bubblepack, thus affording the contents physical protection as well as static protection.


- A recloseable feature is also now available to keep the bags more securely closed and to keep the components cleaner.

- A static-shielding bubblepack material has been introduced that can be used to wrap oddly shaped components. It also offers both physical and static protection.

Although static control can save time and money, it can also save something even more important – a reputation as a quality service organization.



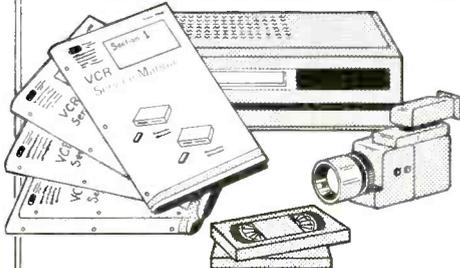Increase Your Servicing Potential ... by subscribing to our VCR and CAMERA SERVICE LITERATURE



With it, you will be able to repair any covered **Magnavox**, **Sylvania**, or **Philco** VCR or Camera.

These annual subscriptions feature all product releases for each year and are convenient, clear and concise. Our manuals are some of the best in the industry! Included are:

- Product Summaries
- Adjustment Procedures
- Printed Circuit Board Diagrams
- Block Diagrams
- Schematic Diagrams

In addition, you will receive supplements as new product versions are added, giving you up-to-date servicing information. You will also receive Video Systems Bulletins covering current, "hot" information and special servicing tips.

| VCR Annual Product Releases For: | Price: | Camera Annual Product Releases For: | Price: |
|----------------------------------|---------------|-------------------------------------|---------------|
| 1984 | \$50.00 | 1985 | \$25.00 |
| 1985 | \$60.00 | 1986 | \$25.00 |
| 1986 | \$60.00 | 1987 | \$30.00 |
| 1987 | \$70.00 | 1988 | Subscribe now |
| 1988 | Subscribe now | | |

Payment is required with order (U.S. Funds) You may use VISA or MasterCard

To place your subscription order, or for more information, call: 615/475-0400 or write: **N.A.P. Consumer Electronics Corp., Product Services, Literature Order Dept., P.O. Box 555, Old Andrew Johnson Hwy., Jefferson City, TN 37760**

PHILIPS



VHS Head Cleaning Cassette

- ★ Compatible with all VHS type VCR's
- ★ Maintains Peak Performance for any VHS Video Recorder or Player
- ★ High Quality Dry Cleaning
- ★ Thoroughly Cleans Heads in 15 Seconds
- ★ Cleans up to 100 Times



SBC103AC01
Video Cleaning
Cassette for VHS

- Remittance Enclosed for _____ Tape(s) at \$12.95 each.
- Send information on other Philips Universal Accessories

Name _____ Sub Total \$ _____
 Address _____ Tax \$ _____
 City _____ State _____ Zip _____ Ship. & Hdl. \$ 3.00
 Total Amt. \$ _____

8 a.m.-5 p.m. Phone # () _____

VISA, MasterCard, American Express or C.O.D.:
Call Toll-Free 1-800-255-5122 (In Tenn. 1-800-824-2567)

Check or Money Order, (No Cash Accepted) Mail Form to:
N.A.P. Consumer Electronics Corp., Accessories Marketing Dept.,
P.O. Box 1597, Greeneville, Tenn. 37744-1597

Prices subject to change without notice. Availability subject to change at time of purchase

© 1987 N.A.P. Consumer Electronics Corp.

Circle (34) on Reply Card

Books

Understanding Electricity and Electronics Principles; Understanding Electricity and Electronics Circuits; revised by David L. Heiserman; Howard W. Sams & Company, 256 pages and 328 pages respectively, \$14.95 each.

These two books cover some basic areas of electronics principles and circuits. "Understanding Electricity and Electronics Principles" discusses basic principles, using ample illustrations and highlighting important concepts. Summaries and self-quizzes help the reader see what he's learned. "Understanding Electricity and Electronics Circuits" covers the building blocks for all electronic equipment, from basic electrical principles to the control of electricity by using transformers. Principles and applications are presented at an easy-to-learn pace.

Published by Howard W. Sams, 4300 W. 62nd St., Indianapolis, IN 46268; 317-298-5400.

ABCs of Electronics, 4th Edition; by Farl Jacob Waters; Howard W. Sams & Company, 200 pages, \$12.95.

This completely revised tutorial on the fundamentals of electronics includes a new chapter on computer basics. The book provides a quick introduction to such electronics concepts as atoms, electrons and magnetic forces, along with basic electronic components and their applications. Other topics covered include impedance, electron tubes, solid-state physics, transistors, integrated and digital circuits, basic amplifier circuits, operational amplifiers and radio frequency production.

Published by Howard W. Sams, 4300 W. 62nd St., Indianapolis, IN 46268; 317-298-5400.

Encapsulation of Electronic Devices and Components (Electrical Engineering and Electronics Series, Volume 36), by Edward R. Salmon; Marcel Dekker, 240 pages, \$59.75 (U.S. and Canada), \$71.50 (all other countries) hardbound.

Before encapsulating an electronic device or component, two important decisions must be made: which material and which method to use. The solid advice of a materials chemist, someone who can clarify the trade-offs in any encapsulation choice, is needed at this point. Anyone responsible for selecting the material and means to protect any electronic device will find that this book progresses

logically through the various classes of materials, providing descriptions, advantages and limitations, application methods for each material, and lists of names and addresses of suppliers. To avoid communication problems, basic definitions, terms and symbols, and guidelines used throughout the industry are included.

Published by Marcel Dekker, Inc., 270 Madison Ave., New York, N.Y. 10016; 212-696-9000.



SAVE and SAVE again on all your OK Electronics products from Joseph Electronics

Buy any OK Test Instrument featured in this ad at a super saving price and receive a Joseph Electronics coupon entitling you to a **10%** discount on ALL your OK product needs purchased from us for the rest of 1987! Choose from an array of Solder and Desoldering equipment, Wire Wrapping, PC Boards and accessories, I.C. and component handling tools, production aids, wire wrapping equipment, hand tools, wire and cable, enclosures, fans, racks and of course, Electronic Test Equipment and Test Probes.

HURRY! QUANTITIES LIMITED AT SALE PRICES



COUNTERS

| Model | Description | Reg. | Special |
|-------|-------------------|--------|---------------|
| 510 | 200 MHz Bench | 385.00 | 339.00 |
| 512 | 200 MHz Hand-Held | 149.00 | 129.00 |
| 515 | 600 MHz Bench | 365.00 | 319.00 |



GENERATORS

| Model | Description | Reg. | Special |
|-------|----------------------|--------|---------------|
| 202 | 200 kHz Function | 239.00 | 215.00 |
| 203 | 2 MHz Function | 289.00 | 259.00 |
| 204 | 5 MHz Pulse | 299.00 | 269.00 |
| 205 | 5 MHz Function | 555.00 | 499.00 |
| 206 | 5 MHz Sweep/Function | 995.00 | 895.00 |
| 207 | 5 MHz Pulse/Function | 995.00 | 895.00 |



OSCILLOSCOPE

| Model | Description | Reg. | Special |
|-------|-------------------|--------|---------------|
| 1010 | 10 MHz Mini Scope | 395.00 | 349.00 |



DMM's

| Model | Description | Reg. | Special |
|-------|-------------------------|--------|---------------|
| 601 | 3.5 Digit LCD 1% Acc. | 225.00 | 199.00 |
| 603 | 3.5 Digit LED .25% Acc. | 195.00 | 169.00 |
| 604 | 3.5 Digit LCD .25% Acc. | 215.00 | 189.00 |

Joseph electronics

**CALL: 1-800-323-5925
(in Illinois 312-297-4200)**

Visa • Mastercard • Discover • Phone orders welcomed. Order handling charges
Value: \$0-999 \$1000-2499 \$2500-up
Add: \$10.00 \$15.00 \$20.00
Open account to rated companies.

8830 N. MILWAUKEE, NILES, IL 60648, DEPT. F

Illinois residents add 7% tax.

Circle (15) on Reply Card

ANSWERS to the QUIZ

1. A.) They are Marconi quarter-wave antennas.
2. A.) Moving the turns closer together increases the inductance. The equation for resonant frequency is

$$f = \frac{1}{2\pi\sqrt{LC}}$$

Making L larger lowers the value of f.

3. C.) A discriminator is used to sense any shift in the carrier frequency. In the I-F stage of an AM receiver, the carrier is usually at 455kHz. It is assumed that a shift in the carrier frequency must be due to a drift in the oscillator frequency.

4. D.) Five flip flops can make 32 counts. Zero is one of the counts, so the highest number counted is 31.

5. B.) If R_L increases, the resistance of the parallel branch also increases. Because the voltage is constant, the corresponding increase in circuit resistance causes a decrease in circuit current and a corresponding decrease in the current through R_L . To get the current through R_L back up to 0.5A, you have to increase the resistance of R_2 more than R_L increased. That raises the resistance of the parallel branch so that the voltage across that branch is sufficient to get 0.5A through R_L . The graph in Figure E shows values of R_2 for corresponding values of R_L . It is based upon the equation

$$R_2 = \frac{25R_L}{75 - 0.5R_L}$$

which, in turn, assumes that V, R_1 and I_L are constant.

6. 10Ω. The circuit in Figure C is another example of a balanced Wheatstone bridge. (You'll have to redraw the circuit to see that.) No current flows through the center leg, so it can be removed. That leaves the circuit shown in Figure

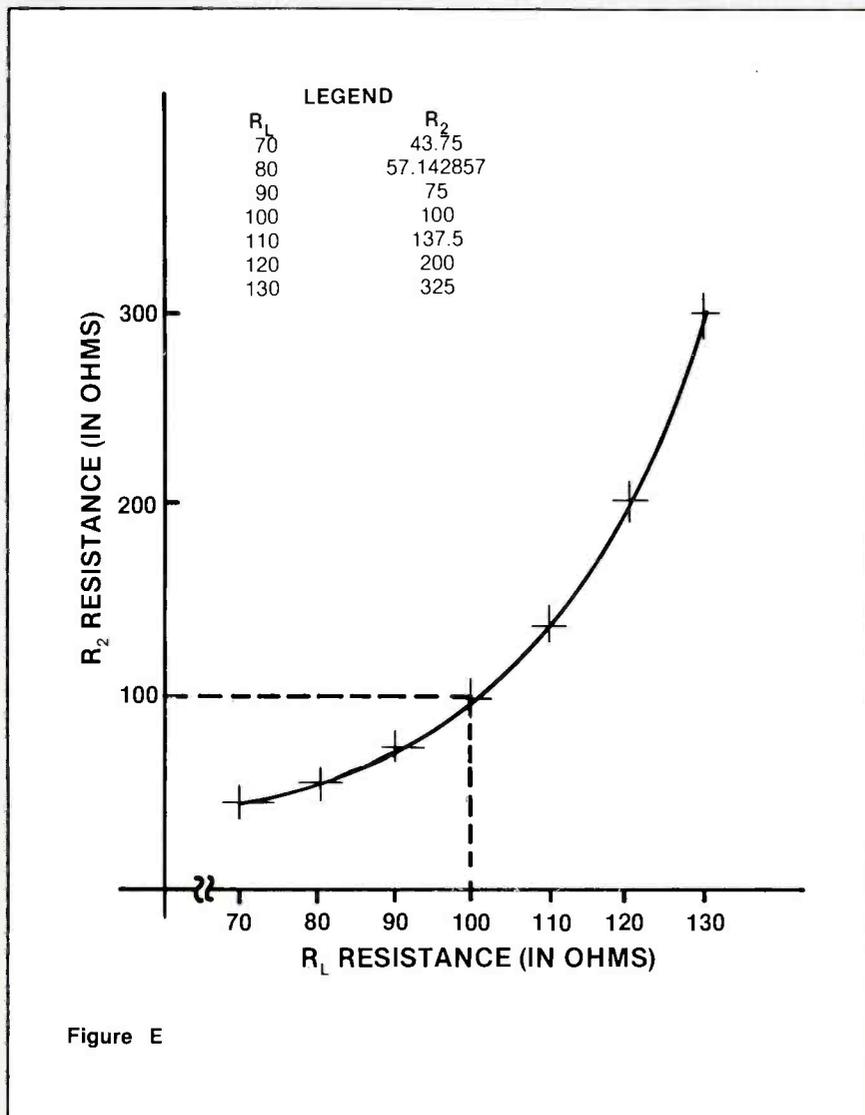


Figure E

F and a resistance of 10Ω .

7. Inverter. Do not confuse this power supply circuit with a converter, a circuit that converts one value of dc to a higher value of dc.

8. A.) The equation for percent regulation is:

$$\% \text{ regulation} = \left(\frac{\text{no load } V - \text{full load } V}{\text{full load } V} \right) 100$$

In a perfect (ideal) supply the no load and full load voltages would be equal, and there would be zero percent regulation.

9. A.) Ripple factor = $\sqrt{\frac{I_{\text{rms}}}{I_{\text{dc}}} - 1}$


where I_{rms} is the effective voltage of the output voltage and I_{dc} is the average value of the output voltage. For a perfect power supply, where $I_{\text{rms}} = I_{\text{dc}}$, the ripple factor is zero.

10. A.) With the wiper of the variable resistor at A, there is no phase difference between the voltage across the triac and the input gate voltage. The triac will start conducting at the start of each half cycle, and the brightness of the lamp will be maximum.

ANSWER TO BONUS QUESTION:

D.) Thomas Edison was really the first. I know this will be hard to take if you are a Tesla fan, but it's true!

ES&T

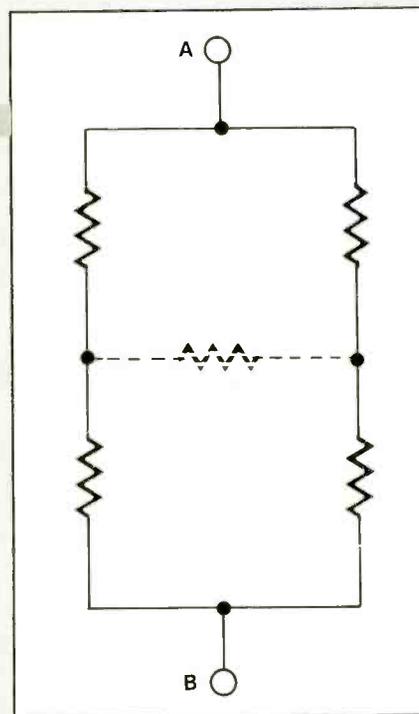

VCR Maintenance and Repair on Video Tape

There is no other tape like ours on the market. This VHS tape is loaded with one hour and forty-seven minutes of expert information. This new tape takes you step-by-step through four different VCRs and shows you the similarities and differences of each.

The only hand tool required is a Phillips head screwdriver. That's right! There is no test equipment or special tools required. Also, you need no special schooling to perform the simple tasks on our video.


Save time and money

After viewing this program you will be able to do the most common repair jobs on all VCRs. To save time and money on your VCR repairs order your own VHS VCR tape NOW! Simply call:

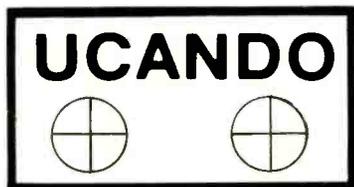(513) 548-6113 or
1-800-323-0826 (Ohio only)

and have your Master Card or Visa ready.

The tape is only \$29.95 + 3.00 (postage and handling). Please allow 6-8 weeks for delivery.



VCR EDUCATIONAL PRODUCTS
P.O. BOX 386
GREENVILLE, OHIO 45331

Circle (16) on Reply Card

MODULAR PROBES FOR SALE

For All Oscilloscopes
To 300MHz
X1 to X100
Attenuation

*Pictured
Accessories
Included*



INSTANT REPAIR

Probe tip, Head, BNC and Cable all screw into place easily and quickly.

TEST PROBES, INC. TPI

Your Probe Specialists

Coline U.S. Sales & Stocking Source P.O. Box 2113, La Jolla, CA 92038 (619) 535-9292

COMPARE PRICE — COMPARE PERFORMANCE

| Model | Attenuation | Bandwidth | Price |
|----------|-------------------|------------------------|----------------|
| M12SW | X1-X10 Switchable | X1-10MHz X10-250MHz | \$72.00 |
| M12X10 | X10 | 250MHz | 62.00 |
| M12X10AP | X10 with Readout | 250MHz | 68.00 |
| M15X100 | X100 | 250MHz | 79.00 |
| M15X10HF | X10 | 300MHz | 79.00 |
| M12X1 | X1 | 30MHz | 38.00 |

Circle (17) on Reply Card

October 1987 *Electronic Servicing & Technology* 41

Measuring tape tension and torque in VCRs

By Wayne Graham

VCRs are complex devices from an electronics standpoint, but they also contain complex mechanical systems for driving the tape. It is these mechanical systems that cause the majority of VCR failures. Proper diagnosis of problems with VCR mechanical components such as clutches, brakes, belts, pinch rollers, solenoids and motors requires a good comprehension of the terms *torque* and *tension*. Many service technicians treat these terms almost equally, but in fact they are quite different, although they are related.

Tension

Tension is simply the pull force exerted and is expressed in units of grams, ounces, pounds or, for the really scientific, newtons. The few purists and Ph.D.s among us are concerned with the terms grams of force vs. grams of mass, or pounds of force vs. pounds of mass. Suffice it to say that here on earth, the rest of us can merely use the terms grams or ounces and we'll all know what we mean. (The purists will be the ones talking about newtons.) Useful conversion factors are:

28.35 grams = 1 ounce
16 ounces = 1 pound
453 grams = 1 pound
1,000 grams = 1 kilogram

and to allow us to communicate with the purists:

102 grams = 1 newton

It is easy to simulate tension—just hang a weight on a string or

piece of magnetic tape and the value of the weight equals the amount of tension in the string or tape. (See Figure 1.)

Torque

Torque is a little more complex than tension. Torque is a rotational force; it is the result of a force (tension) acting at a point some distance from a center of rotation. (See Figure 2.) Torque is therefore a computed value.

Torque is equal to the tension multiplied by the perpendicular distance between the axis of rotation and the applied force (for tape transports this is equal to the radius of the tape pack):

$$\text{torque} = \text{tension} \times \text{radius}$$

Torque is a function of both the force applied and the distance to this force, so the units of torque are:

g-cm (gram-centimeters),
in-oz (inch-ounces), and
ft-lb (foot-pounds).

Other convenient conversion factors are:

72g-cm = 1in-oz,
192in-oz = 1ft-lb,
1152g-cm = 1in-lb.

Relating this to a VCR, the torque (in gram-centimeters) exerted by a reel is equal to the tape tension (in grams) multiplied by the radius of the tape reel (in centimeters). Remember that the radius equals the diameter divided by two.

$$\begin{aligned}\text{Torque} &= \text{tension} \times \text{radius} \\ \text{Radius} &= \text{diameter} \div 2 \\ 2.54\text{cm} &= 1\text{in}\end{aligned}$$

Measuring tension and torque

Let's compare some of the common methods used for measuring torques and tensions in VCRs:

1. The hope-and-pray method
2. The tension cassette
2. The spring (fish) scale
4. The Tentelometer tension gauge
5. The dial-torque gauge

1.) The *hope-and-pray* method is by far the easiest but the least effective. Spray some oil or clean with a Q-tip and hope and pray it keeps working—no tools or gauges required. This method is not recommended for building a large base of satisfied customers.

2.) *Tension cassettes* look like actual tape cassettes but have a meter built in. They are available from a number of VCR manufacturers. Although they are configured like a standard cassette, they are not interchangeable from one brand of VCR to another. Because they work by measuring the torque (tension times radius) exerted by the holdback reel inside the cassette, as the tape guidance system between the cassette and video head changes, different torques are required for providing the proper tape tension going into the scanning video heads.

Keep in mind that consistency in tape tension going into the video heads is required between VCRs to maintain interchangeability from one machine to another. Care must also be taken to keep tension cassettes properly calibrated,

Graham is general manager of Tentel, Campbell, CA.

because a faulty tension cassette would cause VCRs with proper tension to be "corrected" to a faulty tension.

Because service technicians are usually working on malfunctioning machines, chances are good that the tape inside a tension cassette will become damaged and will require replacement. After tape

replacement, it is recommended that the readings be checked against another new tension cassette to make certain that the rebuilt gauge is reading correctly. This procedure would automatically double your tension cassette investment, and tension cassettes are not available for all brands and models of VCRs.

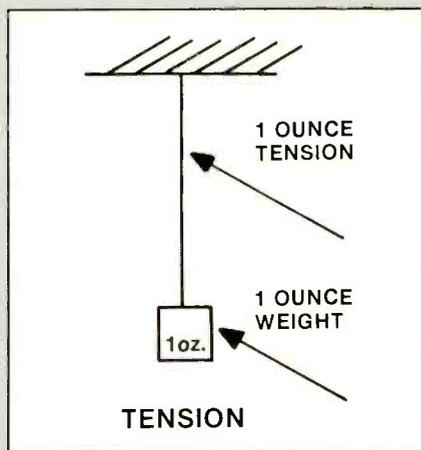


Figure 1. Tension is just the pull force exerted and can be simulated by hanging a weight from a piece of string. The tension is the same value as the weight.

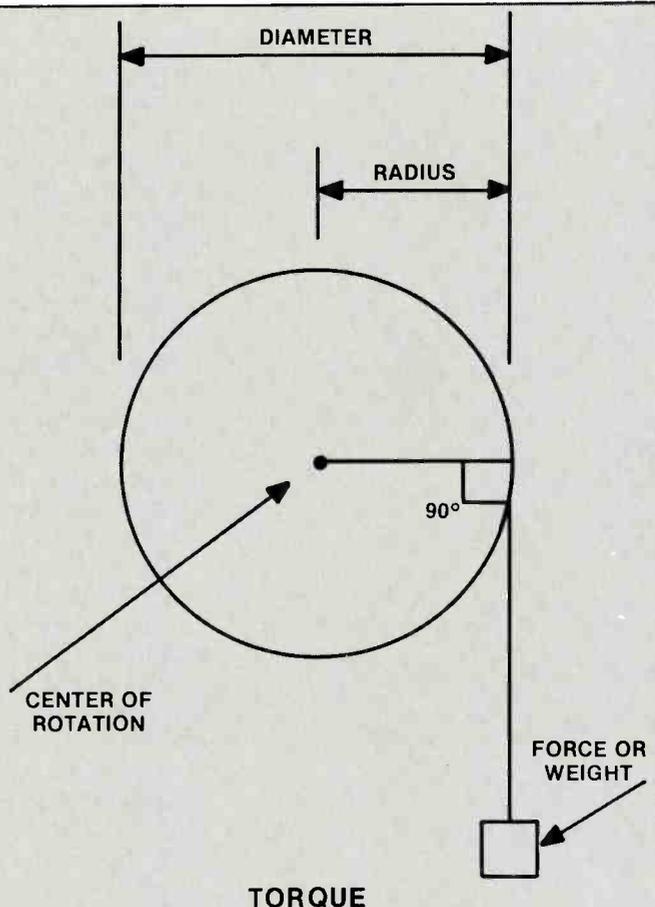


Figure 2. Torque is a rotational force, the result of a force acting at a point some distance from the center of rotation. The value of the torque is the tension multiplied by the radius.

3.) *Spring scales*, sometimes called *fish scales* because they are similar to the scales used to weigh fish, can be used to pull on tape. For measuring supply holdback tension, a reel (obtained by taking apart a cassette) is placed onto the supply spindle, the tape is threaded out into the machine, simulating the tape path during PLAY, and the back tension is determined by measuring the tension exerted on the tape by the holdback torque of the supply reel.

It is usually necessary to remove at least one side of the VCR to gain access to the tape so that you can connect the spring scale to the tape's end. The tape and spring scale must be pulled smoothly and at the approximate tape speed that the tape would encounter during normal play. The various sensors on the machine would have to be "fooled" to allow the VCR to go into the play mode or into other modes where torques or tensions need to be measured.

4.) The *Tentelometer* tape tension gauge consists of three tiny probes that protrude from one side of a small case. The case contains a meter scale and pointer that provides readings in grams and ounces of tension. The gauge provides a method of measuring the supply holdback tension by sliding the probes of the gauge over the tape while the VCR is moving the tape. VCRs can move tape smoothly and at the correct speed quite easily, so these variables are removed from the measurement.

Calibration can easily be checked in the field, allowing service technicians to be confident of their readings. Because the tension measurement is made out in the tape path next to the inlet idler (on a VHS), the correct specification is the same on all VHS recorders. Measuring a specification of $\pm 30g$ (25g to 35g) will assure proper back tension for skewing interchange.

The device can also be used for checking the functioning of the holdback tension servo. By comparing the holdback tension on a

full supply reel to that of a nearly empty reel, the device tells you that the servo requires adjustment if the readings change by more than five grams. The Tentelometer is referenced in many of the factory service manuals, including Panasonic, GE, Gold Star and Hitachi, but will work on any brand of VCR.

5.) The *dial torque gauge* is an excellent, fast method of determining the torques (usually in gram-centimeters) exerted by both the supply spindle and the take-up spindle during the various modes of the VCR. These desired torques are specified in both the clockwise and counter-clockwise direction for fast-forward, rewind and stop modes.

Torques are also associated with take-up during play as well as between modes such as "play to stop" and "stop to play." In all, there are approximately eleven torques that could contribute to tape damage or an inoperable VCR and should be checked with a dial torque gauge. Dial torque gauges are available from the individual VCR manufacturers and from independent suppliers. All units measure directly in gram-centimeters.

No matter how you do it, there are mechanical measurements that should be made when servicing a VCR. Problems with supply back-tension can cause tape damage or hooking (flagging) tape-interchange problems. Problems with fast forward or rewind can cause slow FF or REW times, tape cinching (tight pack), edge damage and subsequent tape destruction. Problems with various take-up torques can cause tape destruction because the tape is not drawn back into the cassette and is crinkled in the cassette door when the tape is ejected.

With the proliferation of low cost VCRs, it is imperative that the service technician choose a fast, reliable, repeatable, field verifiable method of performing the various mechanical tests. To do otherwise is to invite problems and complaints.

ES&T

Unusual waveform/ function generator circuits

By Joseph J. Carr, MSEE, CET

Many different types of electronic equipment use internal circuits that generate waveforms. Most readers are familiar with ordinary sine wave and square wave generator circuits, so in this article we are going to deal with sine/cosine generators, sawtooth generators and pulse generators. Because these circuits are based on an electronic circuit called an integrator, let's look first at the elementary Miller integrator circuit.

Integrators

Integration is a mathematical process used frequently in electronic instrumentation circuits. Although the details of integration are from calculus and are thus beyond the scope of this article, you need to know a few details about integration on at least a descriptive level. Figure 1 demonstrates some of these principles. Keep in mind one fact: The *integral* of a curve (the result of integration) is the area under the curve.

Consider Figure 1A. In this case, a dc voltage is turned on at time T_1 and turned off at time T_2 . Between T_1 and T_2 the voltage remains constant at V_1 . The mathematical "curve" represented by voltage V is simple because $V = V_1$ at all times. The integral of this curve is the area under the curve, which for this simple case is merely the product of the base and height of the rectangle: $V_1 \times (T_2 - T_1)$. If the signal of Figure 1A is applied to an integrator, the output of the integrator will initially be zero and will rise at a constant rate from T_1 until T_2 , reaching a value dependent upon the values of V_1 and $(T_2 - T_1)$.

Figure 1B shows a practical example from medical electronics.

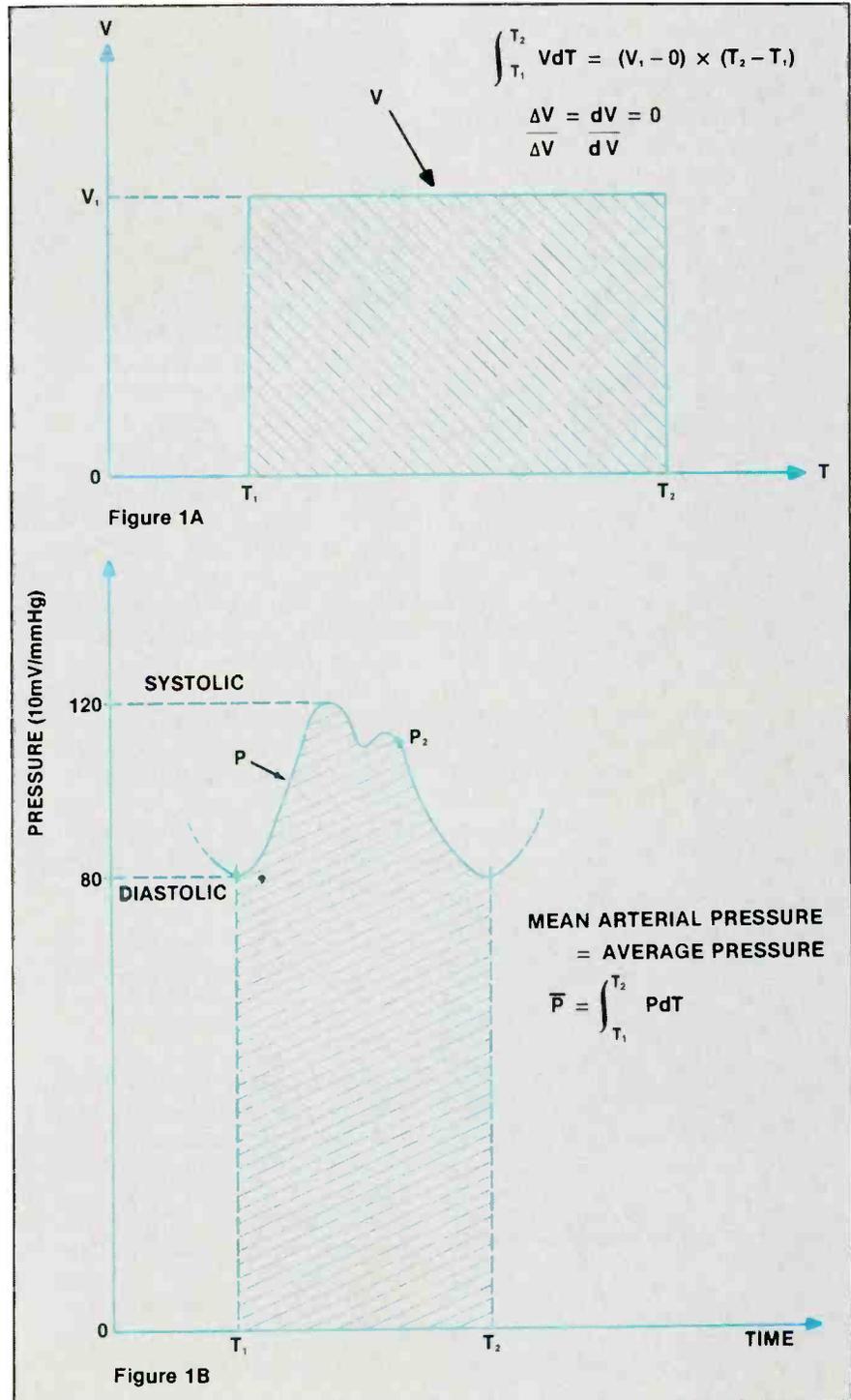


Figure 1. The integral of a curve that's described by a mathematical formula is equal to (for the simple curve in 1A) the product of its base times the height. A practical use of integration is in medical electronics. Figure 1B shows how mean arterial pressure is calculated by integrating instantaneous arterial pressure over one cardiac cycle.

Arterial blood pressure monitors represent blood pressure with a voltage. In modern devices, the voltage analog of pressure is usually 10 millivolts per millimeter of mercury (10mV/mmHg) of pressure. Thus, for the case shown, a systolic pressure of 120mmHg is represented by 1,200mV, while the 80mmHg diastolic pressure is represented by 800mV.

Doctors, especially in intensive care units, sometimes want the mean arterial pressure (MAP). The MAP is the time average of the blood pressure waveform (P) over one cardiac cycle (that is, between two beats of the heart, as represented by points T₁ and T₂). If we apply the pressure voltage waveform to an integrator, the output of the integrator will be the MAP.

The simplest form of integrator is the resistor capacitor (RC) network shown in Figure 2. In this circuit, the output voltage changes as the charge caused by I₁ accumulates in the capacitor. The rate of increase in V_o is dependent on the input voltage and the values of R and C. If you recognize the circuit as a low-pass filter (LPF), or as a part of a vertical integrator from TV sets, you are correct. The integrator also functions as an LPF with a roll-off of -6dB/octave above the -3dB knee frequency (1/6.28 RC).

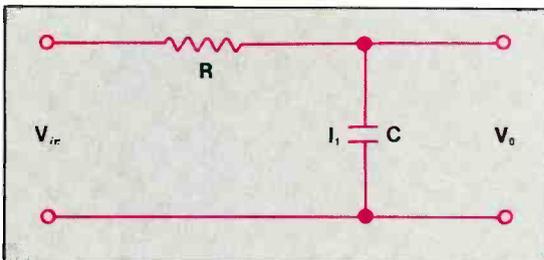


Figure 2. A simple form of integrator is the RC circuit, where the charge on the capacitor is proportional to the total amount of current that has flowed in the circuit.

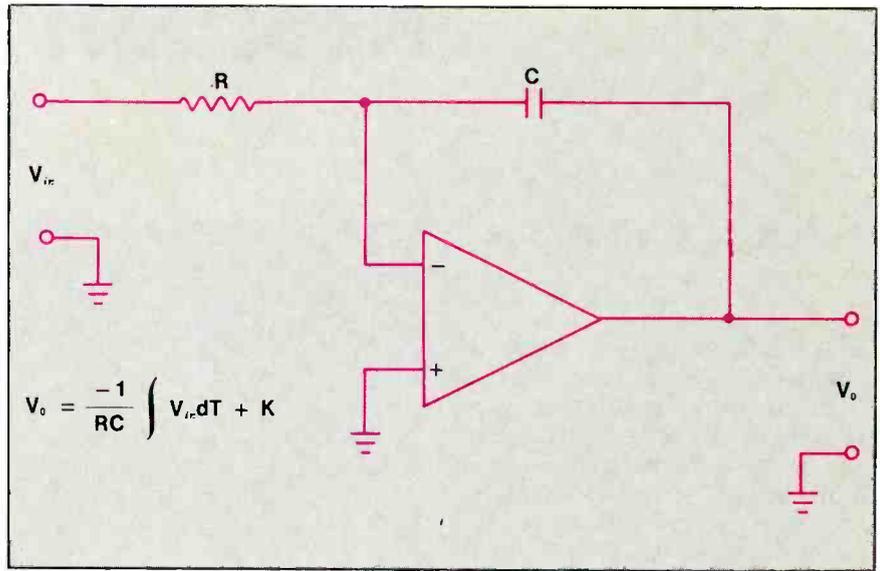


Figure 3. A Miller integrator is basically an op-amp inverting follower with the feedback resistor (R₂) replaced with a capacitor.

The electronic *Miller integrator* circuit is shown in Figure 3. The active element is an operational amplifier that has a capacitor in the feedback network. This circuit basically is the inverting follower with the feedback resistor (R₂) replaced by a capacitor. The gain of this circuit is -1/RC. Keep in mind that with small values of R and C, this gain can be extremely high, resulting in problems for the designer. Consider an example: What is the gain of an inverting integrator in which R = 10kΩ, and C = 100pF?

$$\begin{aligned} \text{Gain} &= -1/RC \\ &= -1/(10,000\Omega \times [100 \times 10^{-12}\text{F}]) \\ &= -1/0.000001 \\ &= -1,000,000 \end{aligned}$$

With a gain of 1,000,000, we find that a small error or dc offset at the input will result in a very large error at the output. For example, suppose we have a 1Vp-p sine wave that has a 10mV dc offset (not very much). This dc offset will be integrated with a gain of 1,000,000 so the 10mV becomes

$$10\text{mV} \times 1,000,000 = 10,000\text{V.}$$

Of course, the output of the op-amp is limited to about 10V or 12V, so the output will saturate quickly. The normal offset of a 741

will saturate the output of such an integrator so fast you'll think it's shorted. In general, the rule of thumb is to make the time-constant of the RC network long (about 5×) relative to the period of the input signal.

Figure 4 shows some common electronic signals at the input and output of an electronic integrator. In each case, the upper trace is the input and the lower trace is the output. For the case of the sine wave shown in Figure 4A, the output is phase-shifted 90° to become a cosine wave. Thus, the output is in quadrature with respect to the input signal.

The integrator action on square waves is shown in Figure 4B. Because the amplitude of a square wave is constant, the integrator output will rise at a constant rate until the square wave drops low again. At that time, the slope of the output waveform changes and starts decreasing. Thus, the integrator makes a triangle waveform out of a square wave. Incidentally, this technique is used by function generators to form triangle waveforms.

A practical integrator

Almost all textbooks on linear integrated circuits or operational amplifiers, including mine, show the circuit of Figure 3. However,

Discover How The World's Only 100% Automatic, Dynamic, & Portable LC Analyzer Gives You Total Confidence In Your Cap/Coil Testing . . . Call 1-800-843-3338 Today!

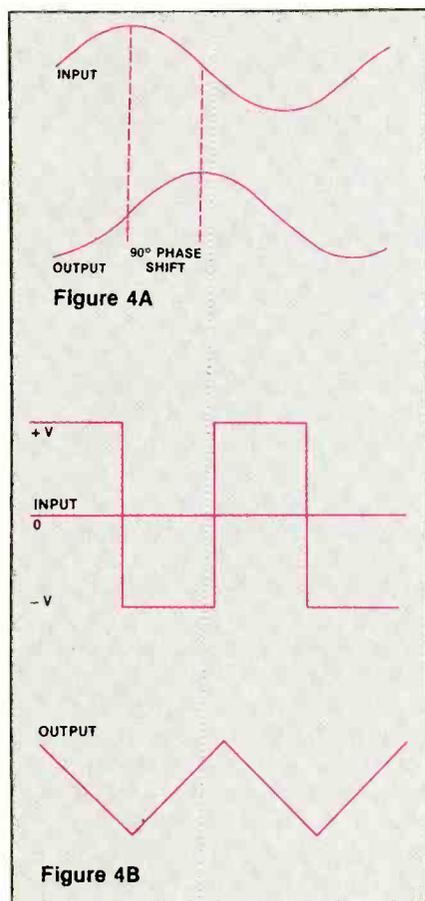


Figure 4. The effect of an integrator is the same regardless of the input waveform: The output waveform is proportional to the area under the curve of the input waveform. The apparent effect, however, will differ greatly with different waveforms. In Figure 4A, a sinusoidal waveform will be phase shifted by 90°, while in Figure 4B, a square wave will be turned into a triangular waveform.

with real operational amplifiers it doesn't work. Unfortunately, some articles and books don't tell you what the problem is or how to deal with it.

The principal problem in practical integrators is that the dc offset voltage normally present at the output of real operational amplifiers will charge capacitor C_1 , and thereby soon saturate the op-amp. The output voltage will start rising immediately after turn-on, and soon it will be off the scale. If you have a signal applied to V_{in} , the output will show that signal with a constantly increasing dc offset potential.

One tactic used to cancel the effects of offset is to use an opera-

New



LC77 AUTO-Z™
Automatic Capacitor and Inductor Analyzer
Double Patented \$1,895

IEEE - 488

The first cap/coil analyzer guaranteed to reliably test anywhere, without calculations, look-up tables, or error — 100% automatically so you're confident of your accuracy.

Do you want to eliminate doubt from your cap/coil testing? The LC77 AUTO-Z tests all key parameters with results *anyone* can understand. Automatic good/bad results eliminate the guesswork for error-free analysis. Touch-sensitive keypad and one-two-three setup makes your AUTO-Z the easiest and fastest LC analyzer on the market.

Are you frustrated trying to test the new high-tech caps/coils used in modern electronics? Only the LC77 AUTO-Z allows you to test them all. Test capacitors from 1 pf to 20 farads, with leakage tests to 1000 V and ESR to 2000 ohms for locating failures other testers miss. Inductor value from 1 uh to 20 H and a patented ringing test for dependable, error-free coil testing every time.

Do you need the freedom of a battery-operated portable LC meter? The LC77 is 100% battery portable for use in the field or factory. The full power and potential of the LC77 AUTO-Z is packed into a light-weight, portable package. The AUTO-Z puts the complicated electronics on the inside for ease of operation on the outside.

Do you want maximum efficiency with a bus compatible LC testing system? Your LC77 AUTO-Z is IEEE 488 compatible for automated cap/coil analysis for data collection, incoming inspection, and quality assurance tests.

Be satisfied that you can meet all the challenges new technology brings. Call WATS Free 1-800-843-3338 today and tell your Area Sales Engineer you want to "try before you buy" with Sencore's exclusive 10 Day Self Demo.

AUTO-Z is a trademark of Sencore, Inc.

WATS Free 1-800-843-3338 In Canada WATS Free 1-800-851-8866



SENCORE

Means Success In Electronic Servicing

3200 Sencore Drive, Sioux Falls, South Dakota 57107

Call Collect 605-339-0100 In SD & AK

Circle (18) on Reply Card

October 1987 *Electronic Servicing & Technology* 47

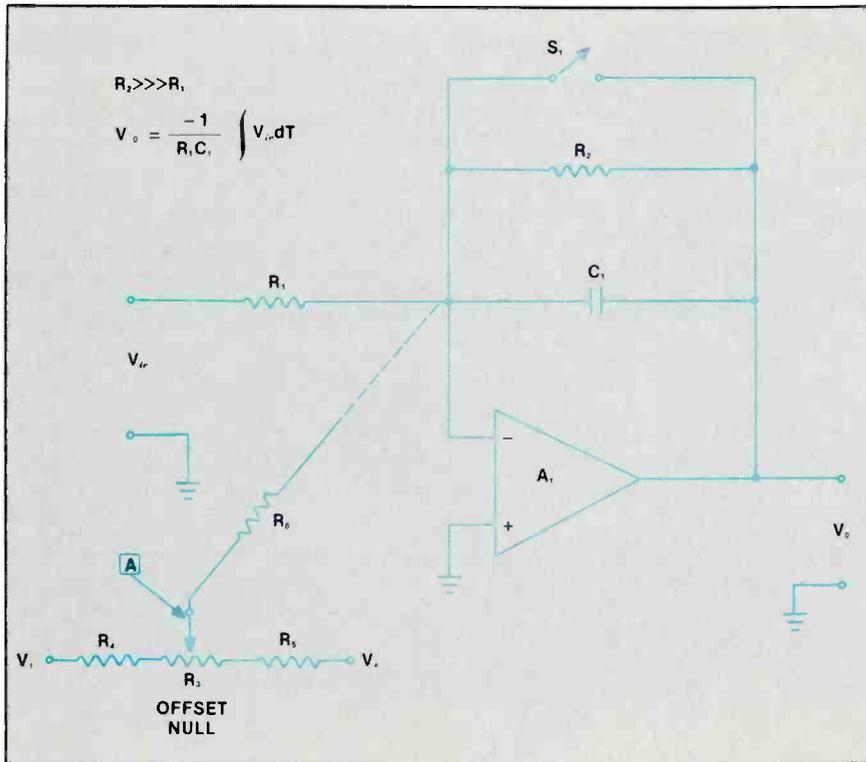


Figure 5. This drawing shows two ways to construct a practical Miller integrator. One is to connect a resistor across the integrator capacitor in order to keep the dc from building up. (R_2 must be much larger than R_1 .) Or, as shown by the arrow marked A and described in the text, you can use an offset null potentiometer.

good selection (see Figure 5). Devices of the 741 family, however, are practically useless for integrator service.

Another tactic is to connect a resistor across the integrator capacitor to keep the dc from building up. This tactic is especially useful for integrators that see periodic input signals. The rule of thumb is to make the shunt resistor (R_2) much larger than R_1 . In the test case, I used a 470k Ω input resistor and an 18M Ω shunt resistor, which worked quite nicely.

Finally, you may also have to use an offset null potentiometer in some circuits. In my test case, with 400Hz sine, square and triangle wave input signals, the potentiometer was not needed. Other cases, however, may require a counter offset provided by R_3 . Although the values of the resistors in this network are dependent upon the application, most of the time a 5k Ω value for R_3 and 10k Ω and 27k Ω values for R_4 and R_5 will suffice. Make R_6 equal to R_1 for starters—it can be increased or decreased as needed after the circuit is tested.

To adjust the potentiometer, short the input of the integrator (making $V_{in} = 0$). Adjust R_3 for a

tional amplifier that has a very low offset potential and no input bias current (or very little). For low-cost applications, the CA-3140 BiMOS op-amp (which uses MOSFET input transistors) is a

$$R_3 \gg R_2$$

$$R_1 = R_4$$

$$T = \frac{2V_1 R_3 C_1}{V_-}$$

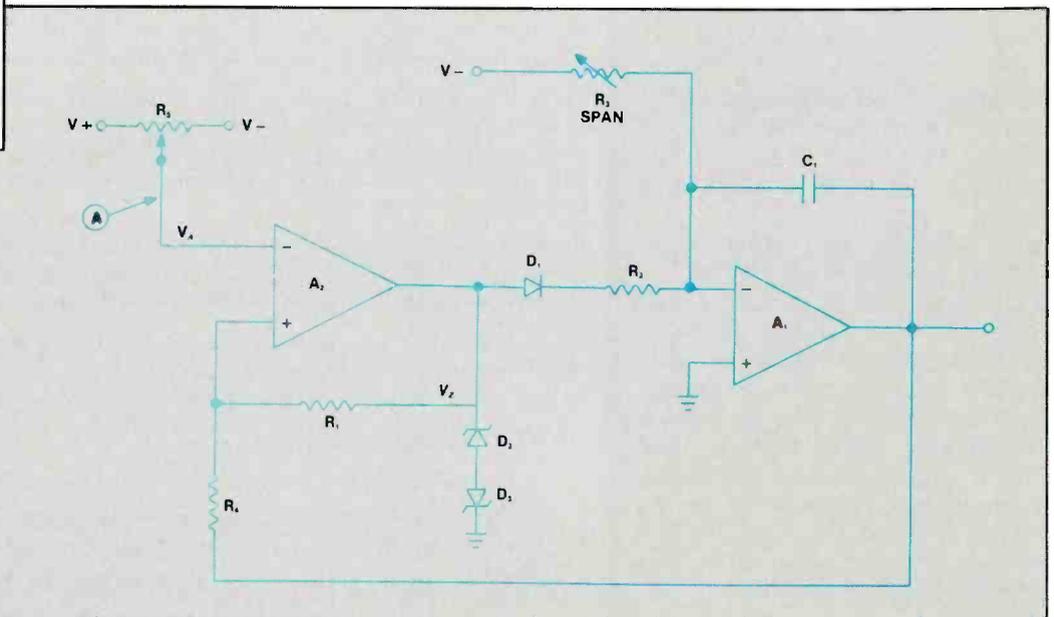


Figure 6. This circuit will produce the classic sawtooth waveform.

Analyze defective waveforms faster, more accurately, and more confidently — every time or your money back

potential of 0V at point A. Momentarily close S_1 to force the output voltage to zero. If the output voltage rises to either positive or negative values after S_1 is opened, adjust R_3 to cause the rate of increase to slow down to zero. Again close S_1 and see if the output voltage changes. Repeat the procedure until the output voltage remains at zero following every closing of S_1 .

In normal operation, switch S_1 is used to reset the integrator after it performs an operation. It is used in some instruments where a value is calculated, but it only occasionally is needed in cases where an integrator sees a periodic signal with no dc offset component.

A sawtooth generator circuit

Figure 6 was derived from a circuit given in a classic op-amp book. The ramp generator circuit is the integrator formed with A_1 , C_1 and R_3 (being driven by V_-). The output voltage ramps up until it reaches the threshold of comparator A_2 . That comparator uses positive feedback and a reference voltage V_{ref} provided by a potentiometer. The trip threshold is $V_{ref} + V_1$ (which is set to 0.7V greater than the zener voltage of D_1/D_2 , assuming that these diodes are identical).

When the output voltage hits the threshold voltage, the comparator output snaps positive and forward biases diode D_3 . If resistor R_2 is much less than R_3 , then C_1 will discharge very rapidly, resulting in the classical sawtooth wave-shape. The reset time, T_2 , will be much shorter than the period, T_1 , if R_2 is much less than R_3 .

Another means of generating a sawtooth waveform is to use a special function generator chip, such as the Exar XR-2206, which is available from Jim-Pak and others. Although in another circuit the XR-2206 will generate sine, square wave and triangle waveforms, in the circuit of Figure 7A the chip generates a sawtooth and a short duty-factor pulse.

The frequency of this sawtooth generator circuit is set by resistors R_1 and R_2 , plus capacitor C_2 .



with the SC61 Waveform Analyzer
Patented \$2,995

If you value your precious time, you will really want to check out what the exclusively patented SC61 Waveform Analyzer can do for you. 10 times faster, 10 times more accurate, with zero chance of error.

End frustrating fiddling with confusing controls. Exclusive ultra solid ECL balanced noise cancelling sync amplifiers, simplified controls, and bright blue dual trace CRT help you measure signals to 100 MHz easier than ever.


Accurately and confidently measure waveforms from a tiny 5 mV all the way to a whopping 3,000 V without hesitation with patented 3,000 VPP input protection — eliminates expensive "front end" repairs and costly equipment downtime.

Make only one circuit connection and push one button for each circuit parameter test: You can instantly read out DC volts, peak-to-peak volts and frequency 100% automatically with digital speed and accuracy. It's a real troubleshooting confidence builder.

Confidently analyze complex waveforms fast and easily. Exclusive Delta measurements let you intensify any waveform portion. Analyze glitches, interference signals, rise or fall times or voltage equivalents between levels; direct in frequency or microseconds.

Speed your digital logic circuit testing. Analyzing troublesome divide and multiply stages is quicker and error free — no time-consuming graticule counting or calculations. Simply connect one test lead to any test point, push a button, for test of your choice, for ERROR FREE results.

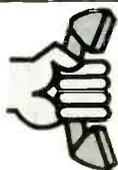To see what the SC61 can do for your troubleshooting personal productivity and analyzing confidence, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

SENCORE

3200 Sencore Drive
Sioux Falls, SD 57107
605-339-0100 In SD Only

*innovatively designed
with your time in mind.*

Circle (19) on Reply Card

October 1987 *Electronic Servicing & Technology* 49

Figure 7A

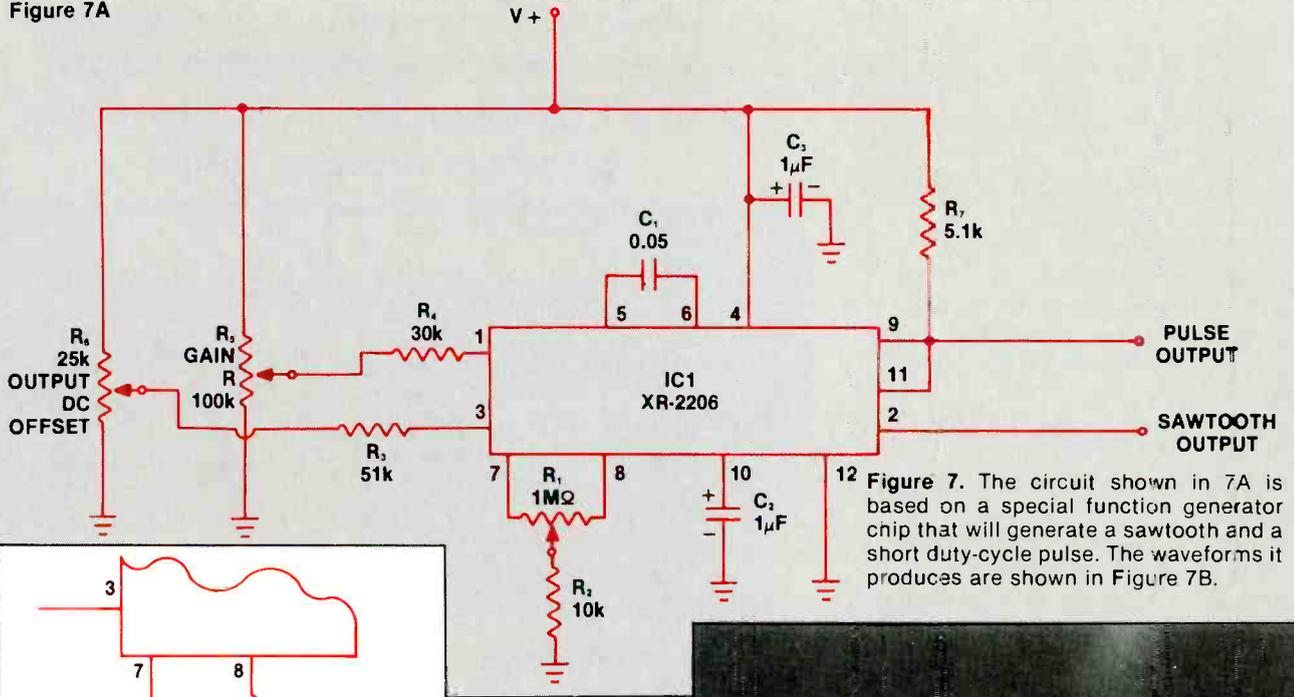


Figure 7. The circuit shown in 7A is based on a special function generator chip that will generate a sawtooth and a short duty-cycle pulse. The waveforms it produces are shown in Figure 7B.


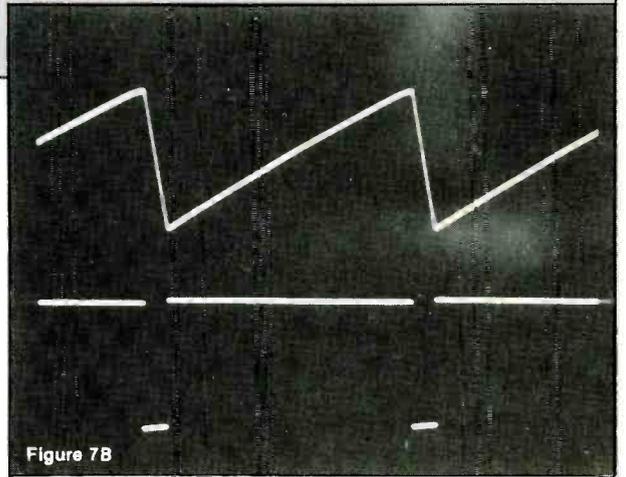
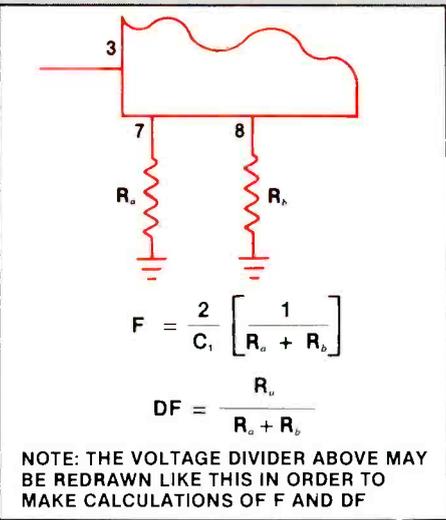


Figure 7B

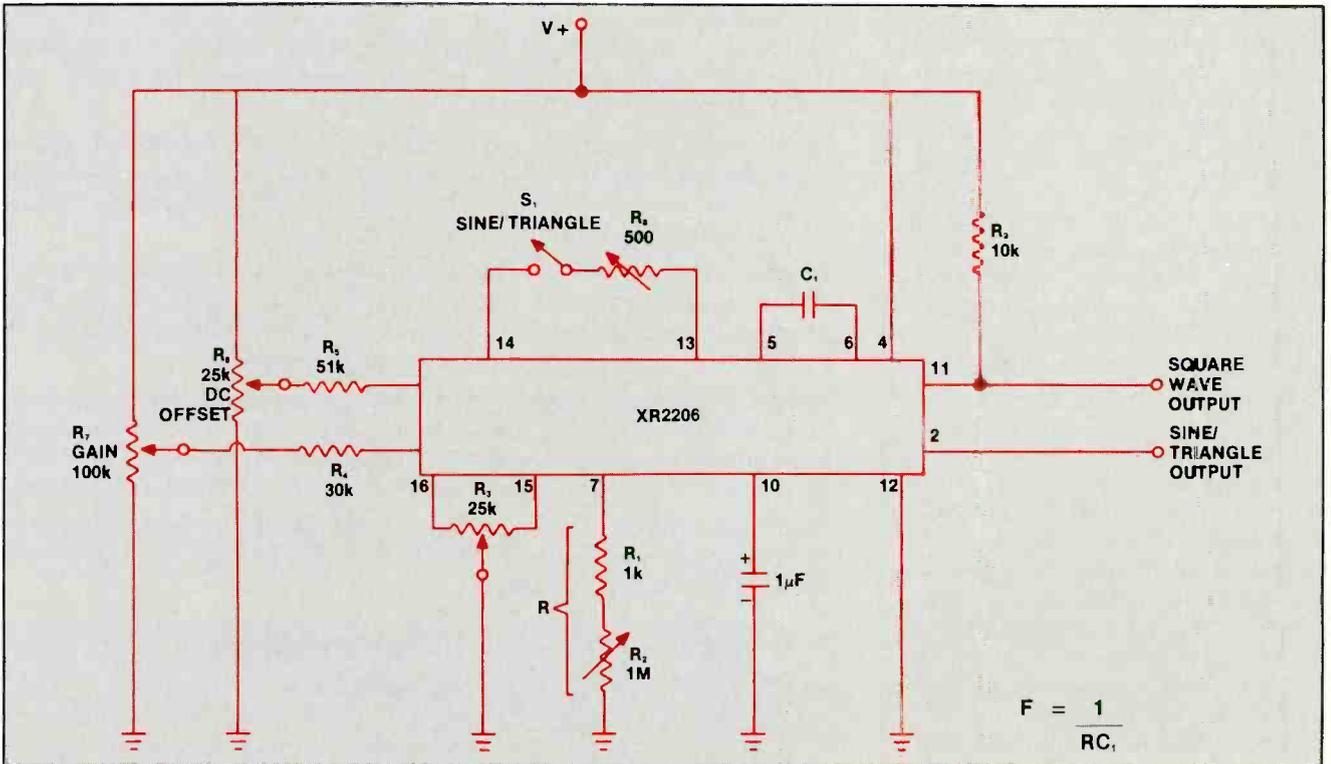

$$F = \frac{1}{RC_1}$$

Figure 8. The same special function generator chip connected here will produce a square wave and a sine/triangle output.

Call 1-800-843-3338 today
to start thoroughly analyzing
and pinpointing any trouble in any
TV-RF distribution system,
automatically to FCC specifications . . .

$$F = \frac{2}{C_1} \times \frac{1}{(R_1 + R_2)}$$

Where F is in hertz, C₁ is in farads, R₁ and R₂ are in ohms.

The duty factor (DF) is found from:

$$DF = \frac{R_1}{(R_1 + R_2)}$$

Jim-Pak makes a circuit-board "function generator" kit for less than \$20. The kit creates the sine wave, square wave and triangle wave signals. It can be easily modified for sawtooth applications. The sawtooth and pulse output waveforms of Figure 7A are shown in Figure 7B.

The same Exar XR2206 device can also be used for generating sine wave and square wave signals. Figure 8 is the circuit for this application. Switch S₁ determines whether the signal at Pin 2 is a sine wave or triangle waveform. This circuit is similar, but not identical, to the function generator circuit. The operating frequency is:

$$F = 1/R C_1$$

Where:

F is in hertz

R is in ohms, and is the sum of R₁ + R₂

C is in farads

The amplitude and dc offset of the output waveform is adjusted using trimmer potentiometers R₆ and R₇.

Waveform generators are the building blocks of complex electronic equipment such as televisions, personal computers and oscilloscopes. If a technician wants to understand these devices well enough to service them effectively, he must understand these signal forming circuits.

ES&T

New



IEEE - 488

with the All New
FS74 CHANNELIZER SR™ TV-RF Signal Analyzer
Patents Pending \$3495

Does your success in servicing RF distribution systems depend on locating problems quickly and accurately? If so, here's why your all new Sencore FS74 CHANNELIZER SR. will mean success for you . . .

Quickly tune in all TV/FM channels from 5 MHz to 890 MHz. Exclusive all channel, microprocessor-controlled digital tuner checks every standard and cable channel with better than FCC accuracy to fully analyze any system.

Exclusive 5 microvolt sensitivity to bring in even weak signals. Autoranged attenuator automatically selects the best sensitivity for simplifying your VHF, UHF, or FM signal measurements like never before possible.

Automatic hassle-free S/N ratio, A/V ratio, and hum level tests. Exclusive on-channel signal-to-noise ratio test eliminates time-consuming signal comparison and chart reading. Exclusive audio-to-video ratio test measures directly in dB for easy comparison to specifications.

Exclusive checks for ghosts, co-channel interference, line reflections, and other signal quality checks. Portable 4 MHz wideband battery-operated monitor lets you finally check the quality of your cable or MATV system and stop annoying callbacks.

Built-in autoranging AC/DC volt/ohmmeter makes troubleshooting a snap. Exclusive all-weather design holds tighter than FCC specifications from -4°F to +104°F. Truly portable, field-tested tough for dependable ease of use.

Begin successfully locating TV-RF signal problems more quickly and accurately than ever before possible, with the new FS74 CHANNELIZER SR. Call WATS Free 1-800-843-3338 today for a free Product Guide or an industry exclusive "Try before you buy" 15 Day Self Demo.

"CHANNELIZER SR." is a trademark of Sencore, Inc.



WATS Free 1-800-843-3338 In Canada WATS Free 1-800-851-8866

SENCORE

Means Success In Electronic Servicing

3200 Sencore Drive, Sioux Falls, South Dakota 57107

Call Collect 605-339-0100 In SD & AK

Circle (20) on Reply Card

What do you know about electronics?

A new zener diode

By Sam Wilson, CET

In a previous article I discussed the strange behavior of a transistor that amplified when its emitter and collector were interchanged in an amplifier circuit. Since that article was written, I've learned that many types of bipolar transistors behave that way.

Transistors may be fabricated with the emitter-base-collector (EBC) leads arranged in that order. However, the ECB configuration is also used. It wouldn't be hard to make a wrong turn and get one reversed in a circuit. The point

is that the transistor would work, but the gain would be greatly reduced. That would give the false indication that there is something else wrong in the circuit.

What I want to discuss now is the strange behavior of light-emitting diodes. They produce a zener diode characteristic on a curve tracer. At the present time I have a young man trying to design a regulated power supply using this reverse-current characteristic. If he comes up with a useful design, I'll put it in a future article.

Let me explain—before I get a boxcar full of letters—that I know the readers of this magazine are too highly organized to get a transistor or LED in the circuit backwards. But I also know of places that start students into the field by having them replace defective components. Students are often well organized too, but they lack experience.

Build your dimmer

The light dimmer (Figure D) in this month's "Test Your Elec-

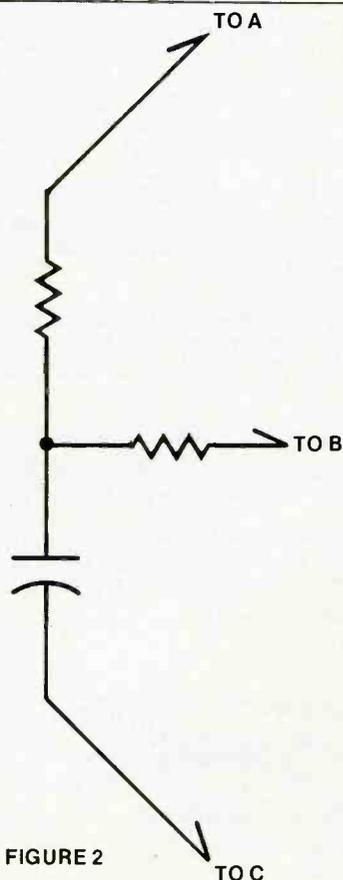


FIGURE 2

THIS PORTION OF AREA UNDER SINE WAVE IS REMOVED. LOWER RMS VALUE RESULTS.

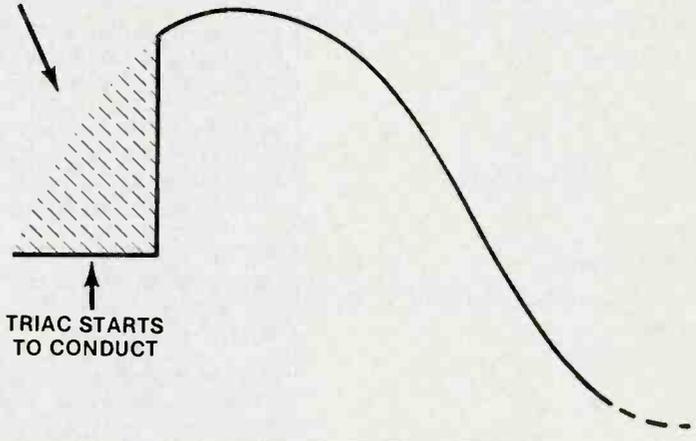


FIGURE 1

0 TO 10M Ω 0 TO 1M Ω 0 TO 100k Ω 0 TO 10k Ω 0 TO 1k Ω 0 TO 100 Ω

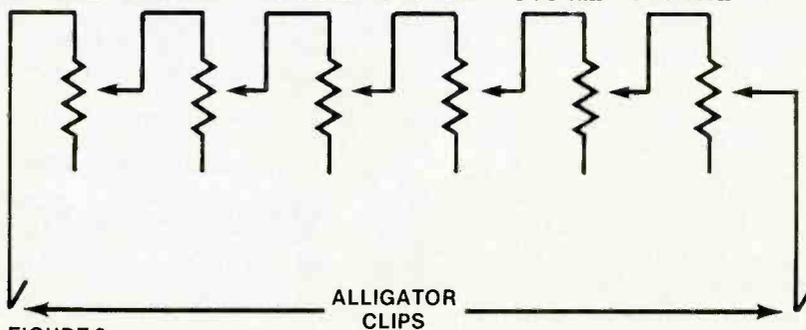


FIGURE 3

ALLIGATOR CLIPS

Walk "Tough Dog" Troubles Out Of Any TV & VCR In Half The Time . . . Guaranteed!



with the exclusive, patented
VA62 Universal Video Analyzer™ . . . \$3,495

Would you like to . . .

Reduce your analyzing time? Isolate any problem to one stage in any TV or VCR in minutes, without breaking a circuit connection, using the tried and proven signal substitution method of troubleshooting.

Cut costly callbacks and increase customer referrals by completely performance testing TVs and VCRs before they leave your shop? Own the only analyzer that equips you to check all standard and cable channels with digital accuracy. Check complete, RF, IF, video and chroma response of any chassis in minutes without taking the back off the receiver or removing chassis, plus set traps dynamically and easily right on the CRT.

Reduce costly inventory from stocking yokes, flybacks, and other coils and transformers for substitution only, with the patented Ringing Test? Run dynamic proof positive test on any yoke, flyback, and integrated high voltage transformer.

Protect your future by servicing VCRs for your customers before they go to your competition? Walk out "tough dog" troubles in any VCR chrominance or luminance circuit to isolate problems in minutes. Have proof positive tests of the video record/play heads before you replace the entire mechanism.

Have one piece of test equipment that doesn't need replacing every time technology changes? Be able to service Stereo TVs & VCRs profitably, and get in on the ground floor of this growing market with exclusive phase-locked accessories.

Find out how the VA62 Universal Video analyzer will make servicing easier and more profitable in your shop? Call WATS Free 1-800-843-3338 and ask your area Sales Engineer for a "Try before you buy" 10 Day Self Demo or a full color brochure and join the many servicers already on the road to more profitable servicing with the VA62.

Universal Video Analyzer is a trademark of Sencore, Inc.



WATS Free 1-800-843-3338 In Canada WATS Free 1-800-851-8866

SENCORE

Means Success In Electronic Servicing

3200 Sencore Drive, Sioux Falls, South Dakota 57107

Call Collect 605-339-0100 In SD & AK

Circle (21) on Reply Card

October 1987 *Electronic Servicing & Technology* 53

tronics Knowledge" quiz really works with the values shown. However, the range of control is limited.

The R-C circuit produces a lagging phase shift at point B. The greater the phase shift, the greater the delay in turning on the lamp for each half cycle.

A typical lamp current is shown in Figure 1. The greater the delay – and shaded area – the lower the rms value. If you decide to build one to cut glare, add the circuit shown in Figure 2. It will increase the range of brightness.

The circuit was given in an applications manual that was distributed by General Electric many years ago. It still works very well. It is *not* for motors or any other inductive load. Also, it will *not* work with fluorescent lights.

Another type of decade

In the next few issues I'm going to include some basic test equipment that you can make. You can't buy these. I don't think manufacturers could make and distribute them at a reasonable price.

Decade boxes are useful for temporarily substituting resistor and capacitor values into circuits. Another type of resistor substitution box is shown in Figure 3. Use variable resistors that are linear and have a relatively high power rating.

I didn't go to the trouble of trying to mark resistance values on the unit. I set the desired resistance with an ohmmeter.

Six color code brands

Without looking at Table 1, what is the value of a resistor that has

the following six bands of color (in the order given):

brown-red-brown-black-brown-red

From Table 1, note that the *fifth* band tells the tolerance (1% in the

example) and the *sixth* band tells the temperature coefficient (TC).

Don't get fooled by this resistor color code. The answer is:

$$121\Omega, \pm 1\%, \pm 50\text{ppm}/^\circ\text{C}$$

The designation ppm/ $^\circ\text{C}$ means parts per million per degree Celsius. For the example, a change of 1°C would result in a resistance change of 50 parts for every million parts of resistance.


The standard values for 1% and 2% resistances are given in Table 2. Note that they are given to three places and a multiplier. The 5% and 10% resistances are given to two places and a multiplier. The resistor given in the example is a standard value.

When to multiply, when to divide

Over the years of working with technicians and students, there is one complaint that I've heard more than any other: "I'm not good at mathematics." (There are two variations: "I never was good at mathematics," and "I'll never be good at mathematics.")

I'm convinced that there is no such thing as a special talent for
Continued on page 57

Table 1.
Resistor color codes

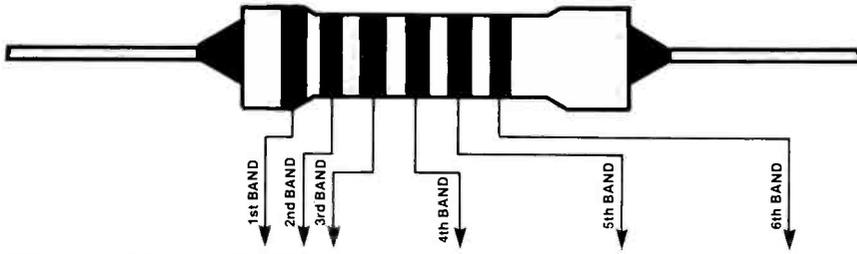

| Color | 1st, 2nd, 3rd significant figure | Multiplier | Tolerance | TC |
|--------|----------------------------------|------------|-------------|-----------------------------------|
| Black | 0 | 1 | | |
| Brown | 1 | 10 | $\pm 1\%$ | |
| Red | 2 | 10^2 | $\pm 2\%$ | $\pm 50\text{ppm}/^\circ\text{C}$ |
| Orange | 3 | 10^3 | | |
| Yellow | 4 | 10^4 | | |
| Green | 5 | 10^5 | $\pm 0.5\%$ | $\pm 25\text{ppm}/^\circ\text{C}$ |
| Blue | 6 | 10^6 | | |
| Violet | 7 | 10^7 | | |
| Grey | 8 | 10^8 | | |
| White | 9 | 10^9 | | |
| Silver | | 10^{-1} | | |
| Gold | | 10^{-2} | $\pm 5\%$ | |

Table 2.
Standard values for 1% and 2% resistors

| $\pm 2\%$ | $\pm 1\%$ | $\pm 5\%$ |
|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|-----------|
| 1.00 | 1.00 | 1.78 | 1.78 | 3.16 | 3.16 | 5.62 | 5.62 | 1.0 |
| | 1.02 | | 1.82 | | 3.24 | | 5.76 | 1.1 |
| 1.05 | 1.05 | 1.87 | 1.87 | 3.32 | 3.32 | 5.96 | 5.90 | 1.2 |
| | 1.07 | | 1.91 | | 3.40 | | 6.04 | 1.3 |
| 1.10 | 1.10 | 1.96 | 1.96 | 3.48 | 3.48 | 6.19 | 6.19 | 1.5 |
| | 1.13 | | 2.00 | | 3.57 | | 6.34 | 1.6 |
| 1.15 | 1.15 | 2.05 | 2.05 | 3.65 | 3.65 | 6.49 | 6.49 | 1.8 |
| | 1.18 | | 2.10 | | 3.74 | | 6.65 | 2.0 |
| 1.21 | 1.21 | 2.15 | 2.15 | 3.83 | 3.83 | 6.81 | 6.81 | 2.2 |
| | 1.24 | | 2.21 | | 3.92 | | 6.98 | 2.4 |
| 1.27 | 1.27 | 2.26 | 2.26 | 4.02 | 4.02 | 7.15 | 7.15 | 2.7 |
| | 1.30 | | 2.32 | | 4.12 | | 7.32 | 3.0 |
| 1.33 | 1.33 | 1.33 | 2.37 | 2.37 | 4.22 | 7.50 | 7.50 | 3.3 |
| | 1.37 | | 2.43 | | 4.32 | | 7.68 | 3.6 |
| 1.40 | 1.40 | 2.49 | 2.49 | 4.42 | 4.42 | 7.87 | 7.87 | 3.9 |
| | 1.43 | | 2.55 | | 4.53 | | 8.06 | 4.3 |
| 1.47 | 1.47 | 2.61 | 2.61 | 4.64 | 4.64 | 8.25 | 8.25 | 4.7 |
| | 1.50 | | 2.67 | | 4.75 | | 8.45 | 5.1 |
| 1.54 | 1.54 | 2.74 | 2.74 | 4.87 | 4.87 | 8.66 | 8.66 | 5.6 |
| | 1.58 | | 2.80 | | 4.99 | | 8.87 | 6.2 |
| 1.62 | 1.62 | 2.87 | 2.87 | 5.11 | 5.11 | 9.09 | 9.09 | 6.8 |
| | 1.65 | | 2.94 | | 5.23 | | 9.31 | 7.5 |
| 1.69 | 1.69 | 3.01 | 3.01 | 5.36 | 5.36 | 9.53 | 9.53 | 8.2 |
| | 1.74 | | 3.00 | | 5.49 | | 9.76 | 9.1 |

Continued from page 54

math. That myth is the basis for such statements as "You really have to be born with the gift of math." Actually, people with that so-called gift were given a positive attitude when they were young and were taught the simple rules necessary for working problems.

If you got off to a wrong start, and you're not yet 100 years old, you can still acquire a math skill. First, you get a positive attitude by saying to yourself—ten times—"If Sam Wilson can do it, anyone in the world can do it." Then you set out to learn the 30 or 40 basic laws and a few good tricks of the trade. The example I'm giving here is how to know if you multiply or divide to get an answer.

Problem: How many nanoamperes (nA) are there in 270 microamperes (270 μ A)?

Solution: Table 3 shows some basic relationships between units. Remember that you can multiply anything by the number 1 without

| | | |
|-------------|---|------------------|
| 1 unit | = | 1,000 milliunits |
| 1 milliunit | = | 1,000 microunits |
| 1 microunit | = | 1,000 nanounits |
| 1 nanounit | = | 1,000 picounits |

changing its value.

From this table you pick what you want and what you got. Then, you make one or more fractions that are equal to 1. Make the fractions in such a way that the units you *have* will cancel and the units you *want* don't cancel. Remember, if two things are equal, dividing one by the other always gives a value of one, and you can multiply by one without changing the value of a number.

In the sample problem we *want* nanounits and we *have* microunits. So, make a fraction:

$$\frac{1,000 \text{ nanounits}}{1 \text{ microunit}} = 1$$

$$270\mu\text{A} \times \frac{1,000\text{nA}}{1\mu\text{A}} = 270,000\text{nA}$$

Note that the microunits cancel and all you have left is nanounits. In some problems you may have to make two or more fractions. Keep going until you have cancelled out all of the undesired units.

Problem: Convert 660 picoamperes (660pA) to microamperes (μ A).

Solution:

$$\begin{aligned} 660\text{pA} &\times \frac{1\text{nA}}{1,000\text{pA}} \times \frac{1\mu\text{A}}{1,000\text{nA}} \\ &= 660 \times \frac{1}{1,000} \times \frac{1}{1,000} \mu\text{A} \\ &= 0.000660\mu\text{A} \end{aligned}$$

To get the answer, divide by 1,000, then divide by 1,000 again. There are 0.000660 μ A in 660pA.

As with anything else that is new, this procedure seems clumsy



Plug in!

To the NESDA system.

YOUR BUSINESS is in the world's fastest changing industry. If you're not careful, you could find your business in the dark.

But, you don't have to stay there.

Through a system of local, state, and regional groups, the **National Electronics Sales & Service Dealers Assn. (NESDA)** keeps members up-to-date with the fast pace of advancing technology while offering:

- ◆ Managerial and technical training.
- ◆ Business contacts.
- ◆ Technical and management certification.
- ◆ Information on new products.
- ◆ Legislative activities that affect the industry.

Don't be left in the dark. Let the NESDA system work **FOR YOU!**

For more information and an application, write to:
NESDA, 2708 W. Berry St., Ft. Worth, TX 76109; Ph (817) 921-9061

Name _____

Bus. Name _____

Address _____

State _____ Zip _____ Phone _____

Member of State Local Assn. _____




FOR ALL YOUR:

- **SOLDERING/DESOLDERING**
- **REPAIR/REWORK**

NEEDS . . .


Solder Dispensing


Gold Plating Preparation

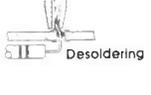
Desoldering


Routing


Circuit Removal


Coating Removal


Circuit Replaced


SMD Replacement


Resistive Tweezing


Conductive Tweezing


Wire Stripping


SMD Removal

CALL FOR YOUR LOCAL A.P.E. DISTRIBUTOR:

AUTOMATED PRODUCTION EQUIPMENT CORPORATION
 142 Peconic Avenue • Medford, N.Y. 11763
 516-654-1197 • TWX: 510-228-2120

Circle (22) on Reply Card

at first. However, once you use it a few times you get to believe in it because it eliminates the possibility of mistakes. Here are some additional examples.

Problem: There are 2.54cm in an inch. How many inches are there in 153cm?

Solution:

$$153\text{cm} \times \frac{1 \text{ inch}}{2.54\text{cm}} = 60.2+ \text{ inches}$$

Problem: How many inches are there in a meter? (Note: 1 meter = 1,000cm)

Solution: You are looking for *inches per meter*. The word *per* always means to divide.

$$\frac{\text{inches}}{\text{meter}} \times \frac{1\text{m}}{2.54\text{cm}} \times \frac{100\text{cm}}{1\text{m}} = 39.37 \frac{\text{inches}}{\text{meter}}$$

The fall of E

When you first learned Ohm's law, it may have been in the form $I = E/R$. The letter I means the intensity of current and E stands for electromotive force (emf).

When students progress from Ohm's law to more advanced work, they get into trouble if they cancel units as shown in the previous section. It would seem that when you get done cancelling units, you should end up with force to represent voltage.

The trouble is that voltage is a unit of *work*—not force. In science the word *work* is simply translated as force times distance. The voltage of a battery, for example, is the amount of work required to move a unit negative charge (one coulomb) from its positive terminal to its negative terminal.

If you've been reading your technical materials and looking into company catalogs, you must have noticed that E is now very rarely used to represent voltage. The reason, of course, is that you shouldn't use the term *electromotive force* to represent a unit of *work*. Besides, the units won't cancel when you are doing advanced math problems.


ES&T

Products

Anti-static cleaner

The Zero-Charge anti-static cleaner from *Tech Spray* is a topically applied solution that cleans work areas, mats and computer workstations while also controlling static. The cleaner is non-toxic, non-staining, non-flammable and chloride-free. It can be applied by spraying or wiping to control static charge generation on fabrics, acrylics, laminates and other surfaces.

Circle (75) on Reply Card

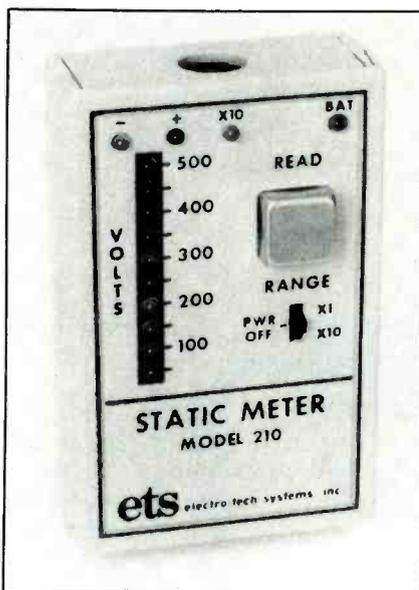

Electrostatic instrumentation

The model 210 electrostatic field meter from *Electro-Tech Systems* uses an array of 12 solid-state light-emitting diodes to detect and indicate the magnitude and polarity of electrostatic fields. Four different colors indicate the relative levels and polarity of the detected field. It has two user-selectable ranges that set measurements sensitivity at $\pm 500\text{V}$ or $\pm 5000\text{V}$ full scale. Its circuits provide for automatic overscale and low-battery indication.

Circle (76) on Reply Card

Digital power and VSWR meter

The *Coline TPI* meter displays true rms power and VSWR on a 0.5-inch digital readout. Frequency coverage is continuous from dc

to 1,500MHz without the need for plug-in elements. The meter measures power to 100W CW or 200W with 50% duty cycle. Resolution is 100mW. VSWR differences of 0.1 are detected and displayed over a range of 1:00-99:1. The meter operates up to a year on an internal 9V battery.

Circle (77) on Reply Card

Copper desoldering braid

A line of flux-impregnated copper braid, available in four sizes, is available from *M.M. Newman Corporation*. Kwik-Wik is a pure copper braid that is flux-impregnated to absorb solder by capillary action when touched by a hot soldering iron tip. The braid comes packaged on spools in 5-foot lengths in four sizes: thin (0.03-inch), small (0.06-inch), medium (0.08-inch) and wide (0.01-inch).

Circle (78) on Reply Card

Test and measurement lab test

Rapid Systems has introduced the R200 series personal computer-based instrumentation lab courses. The course allows immediate hands-on application of the 500-page course text, which accompanies a variety of hardware packages priced from \$999 to \$2,995. The courses teach the skills needed to operate PC-based instruments and covers the theory necessary for understanding the acquisition and use of digitized data. Course topics include: elements of computer systems, assembly and high-level programming languages, data acquisition, instrument tools, instruments, data links and buses, operating systems, applications and experiments. Hardware includes an oscilloscope, a spectrum analyzer and a data-acquisition peripheral.

Circle (79) on Reply Card

Probe assemblies

Hirschmann has introduced Kleps probe assemblies with standard 250mm (10-inch) plug-in leads. These assemblies will allow the user to attach to any 25² or round posts. Other connections or lead lengths can be ordered.

Circle (80) on Reply Card

Soldering iron control unit


The model S-4 control unit from *Sibex* is designed to convert any soldering iron into an adjustable-temperature soldering station. The unit works with any 110Vac-powered iron up to 100W in size. Solid-state circuitry produces a spike-free, adjustable dc voltage and minimizes the possibility of damaging critical components.

Circle (81) on Reply Card

Printer cleaner

3M has added two new filters to the service vacuum cleaner. The unit's high-capacity filtration system now has three filters for a variety of specialized applications. In addition to the toner/dirt filter, the unit now has a fine-particle filter for cleaning laser printers that use toners in the 0.3 to 0.5 micron range, plus a dust/dirt filter for general cleaning that traps dust and larger particles.

Circle (82) on Reply Card

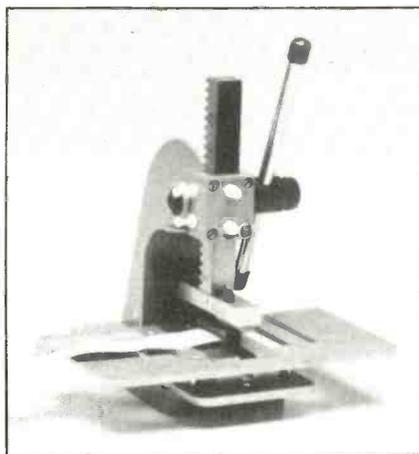

IDC manual press

The *PanaVise* IDC bench assembly press is capable of low-volume mass termination of various IDC connectors on flat (ribbon) cable. The 1/4-ton manual press has cartridge-style interchangeable base plates (no tools required) and accommodates a broad range of IDCs, including female socket transition connectors, card edge connectors, standard DIP plugs and D-sub. An interchangeable base plate terminates up to 64-pin IDCs.

Circle (83) on Reply Card

Degreaser

Lectra-Clean cleaner and degreaser from *CRC Chemicals* removes grease, oil, wax, dirt, moisture and other foreign substances that can cause leakage, excessive resistance and hazardous operation of electrical equipment. The degreaser is non-flammable, non-conducting, does not stain and is non-corrosive to metals.

Circle (84) on Reply Card

Modem/ac line protector

The P208 modem/ac line protector from *MCG Electronics* protects both ac power lines and modem I/O ports from transients caused by lightning, disk drives and switching surges. The unit is a solid-state, plug-in protector that offers 1ns response time and has heavy-duty protection components for use in industrial applications. It plugs into a local 120Vac, 15A outlet.

Continued on page 61

ATTENTION! ELECTRONICS TECHNICIANS



EARN YOUR
**B.S.E.E.
DEGREE**
THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

COOK'S INSTITUTE OF ELECTRONICS ENGINEERING

 347 RAYMOND ROAD
P.O. BOX 20345
JACKSON, MISSISSIPPI 39209

Circle (23) on Reply Card

Portable Variac®

AUTOTRANSFORMERS & VOLTAGE REGULATORS

Does The Job Right!



Advanced design and "hi-rel" performance make Variac portables the logical choice. Each portable Auto-transformer is fully enclosed, has overload protection and generates output from 0 to 117% above line, efficiently. With Voltmeter, Wattmeter or Ammeter, you can choose from 2 or 3 wire versions in 120V, 5 to 18A models and in 240V, 2 to 8A units. The portable Voltage Regulators have

1KVA capacity and 115V ratings with custom units also available. Want smooth, fast response without distortion? Specify Variac to do the job right. Send for details.

You'll Think They're Custom Built!

TECHNIPOWER®

A *Denril* COMPANY

P.O. Box 222, Commerce Park, Danbury, Conn. 06810
Tel. (203) 748-7001 TWX: 710-456-9280
SEE US AT WESCON '87 Booth 1430

Circle (33) on Reply Card

Read-only memories

This installment of *Computer Corner* begins a 4-part series on non-volatile memories. Part 2 will cover programmable ROMs, Part 3 will cover erasable ROMs, and Part 4 will discuss accessing the different types of read-only memory.

Most technicians are already familiar with read/write memories (RAM), and will recall that those Random Access Memories are volatile—the data and/or programs they store are lost as soon as power is turned off.

For applications where the program will be reused over and over and should be available at all times, you need a non-volatile memory. Non-volatile semiconductor memories range from the ordinary read-only memory (ROM) that, once manufactured, cannot be reprogrammed, to read mostly memories (RMM) that can be erased and reprogrammed thousands of times.

Non-volatile memories can be classified into several different categories, depending on their semiconductor technology, internal structure, programming and erasing method, and electrical characteristics.

Read-only memory

The ordinary read-only memory consists of an IC that is mask-programmed at the factory during the manufacturing process. ROM chips feature either MOSFETs or BJTs. The ROM's storage locations (addresses) are written into—programmed—by the manufacturer according to the customer's specifications. In other words, the designer of the computer or microprocessor-based equipment that will use the ROM tells the IC manufacturer what data and/or programs are to be stored in the memory chip.

A suitable mask (photographic template of the integrated circuit) is then made, and the chip is programmed during the last phase of fabrication. ROMs are generally used in large production runs because the IC manufacturer charges thousands of dollars for the initial mask.

Once manufactured, read-only memories cannot have their contents changed—new information cannot be written into them. Therefore, they are used for long-term storage of information that is not intended to change during the operation of a system. For example, ROMs can permanently store the data, monitor program and subroutines that make up the operating system of a computer, as well as the language interpreter (such as BASIC) that translates computer language instructions into binary code that the computer can understand. This built-in program storage makes it possible to use some computers, such as the Commodore 64, immediately after they're turned on, compared to the majority of computers whose operating system and language interpreter must first be loaded from disk before they can be used.

Note—Programs stored in ROM are referred to as *firmware* because they are not subject to change; programs stored in RAM are called *software* because they can easily be altered. *ROM packs* (program cartridges) used to run video games on a home computer are another good example of firmware; the cartridges simply contain a ROM IC mounted on a small printed circuit board.

ROM applications

ROMs are used to store tables of data that do not change, such as logarithmic and trigonometric “look-up” tables that contain values of logs, sines, cosines and more in calculators. They are also used to store code conversion tables (for example, binary to BCD conversion), and can be used as *character generators* for video display on CRT screens; in this application, the ROM stores the binary codes that represent the dot patterns for each alphanumeric or graphic character.

In summary, a ROM is a memory that cannot be written into but can be read from as often as desired. Next month we'll cover PROMs—user-programmable ROMs.

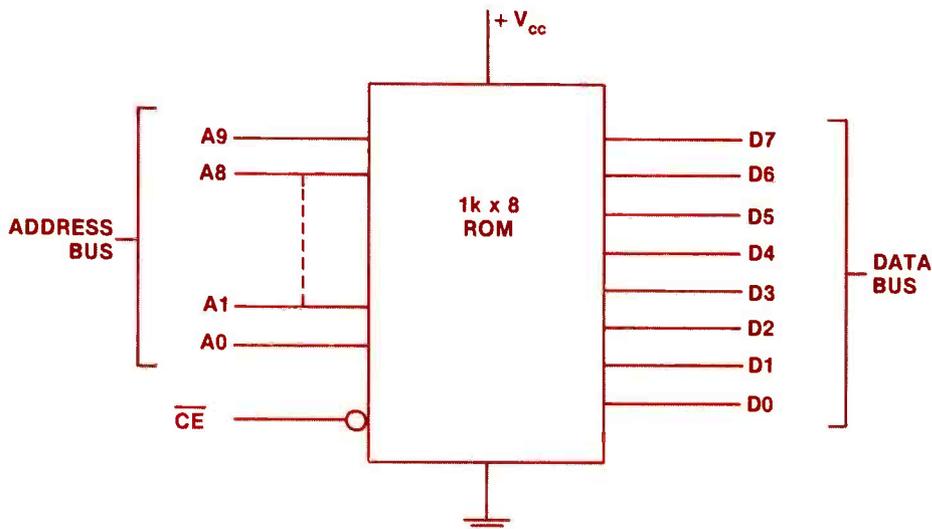


Figure 1. An ordinary ROM can be read from but cannot be written to. A 1k x 8 ROM can store 1024 data words because of its 10 address lines (A9 through A0). The data words are eight bits wide because the IC has eight data pins (D7 through D0).

Products

Continued from page 59

Clamp voltage is 200V peak initial, 300J minimum, $\pm 200V$ peak.

Circle (85) on Reply Card


Digital Probes

Two logic probes (20MHz and 50MHz) and a pulser probe are now being marketed by *Mercer Electronics*, division of *Simpson Electric Company*.

Models 9604 (20MHz) and 9605 (50MHz) logic probes have a slim, compact design that makes them easy to use in densely populated PC boards. Levels and pulses can be viewed from two front-mounted LEDs and stored as desired. Two additional LEDs in the base of the unit display any improper connection or over-voltage applications.

The Pulser model 9606 is multi-functional. In the pulse mode, it can inject $50\mu s$ pulses into a logic circuit without isolating ICs. It has a sync input permitting use of an external synchronizing signal.

Circle (86) on Reply Card

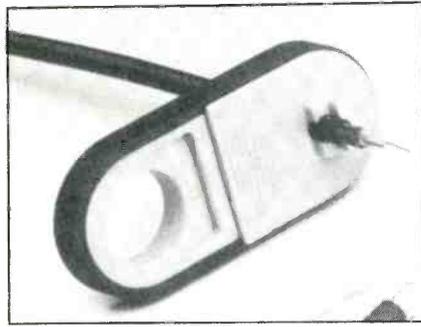

Coax wire stripper

Paladin Corporation's Toggle coaxial wire stripper uses a *toggle* blade system to strip braid and dielectric off coax cable in any number of strip configurations for any type of coax connectors. Toggle is available in sizes suited for cables from RG58 up to RG8/11. Custom sizes can be accommodated upon request.

Circle (87) on Reply Card

PC monitor tester

The MONTEST-D4 PC monitor tester from *Network Technologies* tests monochrome, CGA, EGA and high-resolution monitors. The

device can be used to align, converge and color balance. It is battery powered for portable operation, and generates four patterns—color bars, cross hatch, full raster and windows. It also controls colors, intensity and reverse video.

Circle (88) on Reply Card

Static-dissipative grounding kit

The static dissipative grounding kit from *Contact East* reduces sparking and shorting damages. The resistance to ground is greater than $10^6\Omega$ and less than $10^9\Omega$. It is designed to remove static charges from the service engineer and to provide a static-free surface during field repair of PC boards. The kit includes a 24"x24" static-dissipative work mat with two pockets; one medium and one large wrist band; and a ground-cord assembly, model 3051. It folds to an 8"x12" unit.

Circle (89) on Reply Card

ES&T

NESDA Computer Group

COMPUTER SALES AND SERVICE DEALERS
WORKING TOGETHER



- Service training.
- Assistance in selecting in-house equipment and software.
- Specialized software for service management.

- Factory contacts for service literature and parts.
- Involvement in a stable and productive national trade association.

FOR MORE INFORMATION SEND BUSINESS CARD TO:
NESDA COMPUTER GROUP, 2708 WEST BERRY STREET
FORT WORTH, TEXAS 76109; PHONE (817) 921-9061

PSP

Service Software System
only \$495.00
all this for one low price!

- Tracking through complete repair cycle...
- Billing (automatically tabulates interest)...
- Aged Receivables...
- Manages & tracks Technician's workload...
- Assigns information to Warranty forms...
- Handles Consignment or Rental of parts & equipment...
- Generates: Receipts, Inventory Control Sheets, Status Reports, Authorization Slips, Daily Repair Reports, etc....
- And more!!

For any IBM Compatible from PC to AT.
Minimum: 10 meg-hard disk & 256K RAM

PSP, 3840 S. Palo Verde, #204, Tucson, AZ 85714
(602) 889-8888

Circle (25) on Reply Card

The VCR mechanical-state switch

In a modern VCR, a lot goes on mechanically that you might not ordinarily think about. Let's contrast the mechanics of a VHS VCR with an audio cassette deck. In an audio cassette deck, you insert the tape (there might be a loading motor in one of the modern audio cassette decks), close the door, press the PLAY button and it goes. The pressure pad on the tape cassette provides the proper pressure to hold the tape against the stationary play head as the tape is drawn across the head by the capstan. The take-up motor turns the take-up reel to wind the tape.

In a videocassette recorder, a lot more happens, and it all has to be in precise synchronization. Take a front-loading VHS VCR, for example the GE 1VCR4012. Within the loading mechanism there are three switches: an UP switch, a DOWN switch and an IN switch. Table 1 shows the possible combinations of open and closed positions of these switches and the action that takes place as a result of each combination.

Table 1.
Switch positions

| | Cassette unloaded | Loading/unloading | Cassette loaded |
|-------------|-------------------|-------------------|-----------------|
| IN Switch | open | closed | open |
| UP Switch | closed | open | open |
| DOWN Switch | open | open | closed |

When a cassette is inserted into the VCR, it physically causes the UP switch to open. Further insertion closes the IN switch. This combination of switch conditions is sensed by the system-control microprocessor, which in turn puts

out a signal that turns on the cassette loading-motor drive system so that the motor runs in the loading direction. After the cassette is loaded, the DOWN switch closes. Again, this signal is sensed by the microprocessor, which in turn puts out a signal that turns the motor off.

One of the important features of a VCR is the mechanical-state switch. This switch serves as the interface between the mechanical and the electrical portions of the VCR. The switch monitors the position of the tape transport system and sends it to the system-control microprocessors. When an operation mode is selected, the system-control stages (microprocessors) tell the loading motor to turn in either the load or the unload direction.

Movement of the loading motor governs the operational timing of all mechanical modes. In other words, the action of the loading motor through belts, pulleys, gears and rods changes the mechanical configuration of the tape transport mechanism. The mechanical-state switch is also linked to the loading motor so that it moves as the loading motor moves. Therefore, as the loading motor drives the tape transport mechanism into the mechanical configuration, the mechanical-state switch monitors those configurations as they occur.


There are two types of mechanical-state switches you may find in a VCR: a slide type of switch and a rotary type. The particular type of tape transport mechanism determines which type of state switch is used. A 5-position, slide-type switch is shown in Figure 1, while an 8-position, rotary mechanical-state switch is shown in Figure 2. Even though they are physically different, both switches perform the same function in a similar manner.

A simplified schematic of the slide type of mechanical-state switch and its connections to the system control stages is shown in Figure 2. The five contacts of the switch are converted to three data lines by a diode matrix before being sent to the system-control stages.

The switch is shown in the STOP position. Should the PLAY key be pressed at this time, the loading motor will

| | POSITION (3) | POSITION (2) | POSITION (1) |
|------------|--------------|--------------|--------------|
| PLAY (P) | L | H | L |
| PAUSE (P) | L | H | H |
| REV (P) | H | L | L |
| STOP (P) | H | L | H |
| FF/REW (P) | H | H | L |

Figure 1. Information from this 5-position, slide-type switch is converted to three data lines by a diode matrix before being sent to the system-control stages.

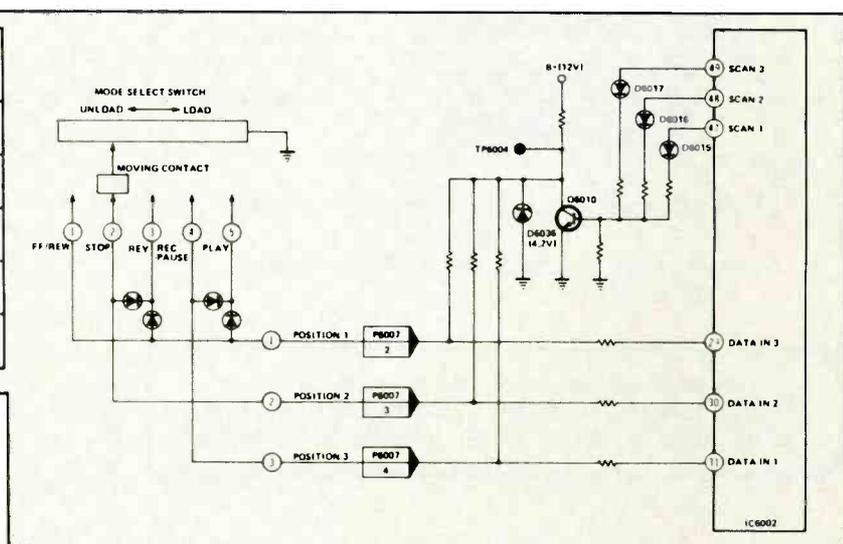

begin to move in the load direction. Between position 2 and position 3, the loading posts will move, loading the tape. At the same time, as the contact inside the mechanical-state switch reaches position 3, the loading posts are caught by the V stoppers and the posts can move no further because of the construction of the cam gear.

Loading-motor movement continues, however, and during the period that the mechanical-state switch advances through positions 4 and 5, the pressure roller, tension post and other parts of the mechanism are moved to suitable positions for the playback operation. When position 5 is reached by the mechanical-state switch, the data (L,H,L) sent to the microprocessor (IC 6002) causes the loading motor to stop.

The rotary mechanical-state switch is an 8-position device. The intelligence from this switch is also delivered to the system-control microprocessor by three data lines.

As we said at the outset, there's a lot going on in a VCR mechanically. An understanding of the role of the mechanical-state switch will help you understand how the VCR operates and what is supposed to be going on at any time. This will help you diagnose and correct problems when the unit malfunctions.

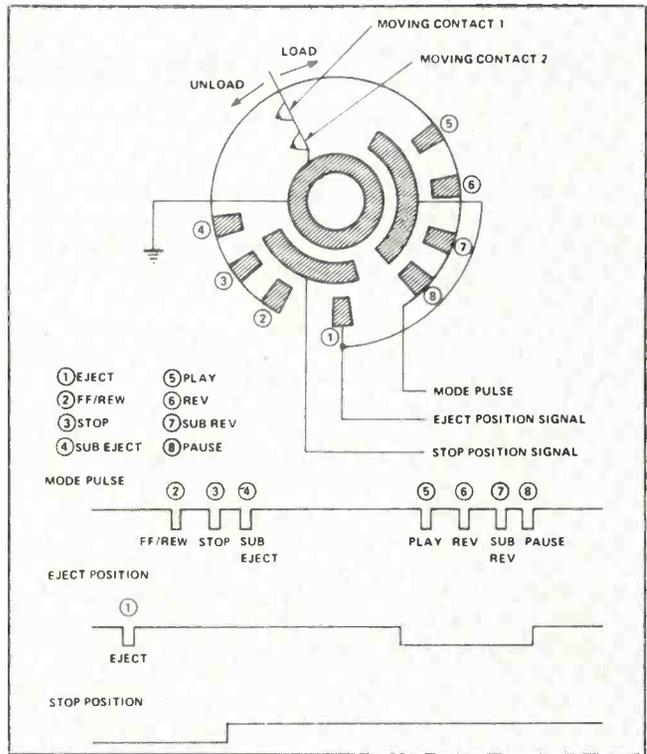


Figure 2. This rotary-type switch has eight positions.

ES&T

**Technicians,
Get Serious
About Your
Profession**



Being a certified electronics technician lets people know that you are a professional in your field. It tells them that you are serious about your work and can perform up to CET standards.

Now you can order the "Study Guide for the Associate-Level CET Test" from the International Society of Certified Electronics Technicians. It includes material covering the most often missed questions on the Associate CET exam. 8½" x 11", paperback, 60 pages.

For More Information Contact:

IS CET, 2708 W. Berry, Fort Worth, TX 76109; (817) 921-9101


NAME _____
ADDRESS _____
CITY _____ STATE _____
ZIP _____
_____ copies @ \$5 (+ \$1 postage.)

_____ send material about IS CET and becoming certified.

ELECTRONIC WAREHOUSE CORP.

- Over 20,000 Electronic Items in stock
- TOLL-FREE "800" Phones
- 24 hour hot line automatic order taker
- Same day order processing & shipping
- VISA & MASTER CARD accepted

SPECIAL OCTOBER FEATURE

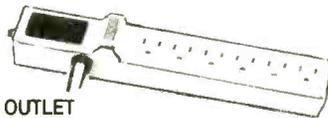

**6 OUTLET
SURGE-PROTECTED STRIP** with circuit breaker, on/off switch and 6' 3-wire cord.
only **\$9.95** each

ATTENTION VCR REPAIRERS:

We stock 155 different VCR belt Kits, 47 different Video Heads, and 119 VCR Clutch Tire replacements, in addition to complete Idler Assemblies, Loading Gears, Sensing Lamps, and the most comprehensive Service Data inventory available anywhere!

Call or write for our latest 144 page money-saving catalog of values, and don't forget... We'll beat any advertised price on Leader and B&K Test Equipment...Call us after you have shopped around and we'll prove it.




TOLL FREE
(800) 221-0424

(718) 375-2700
New York State
dealers call collect

**1910 CONEY ISLAND AVENUE
BROOKLYN, NEW YORK 11230**

Circle (26) on Reply Card

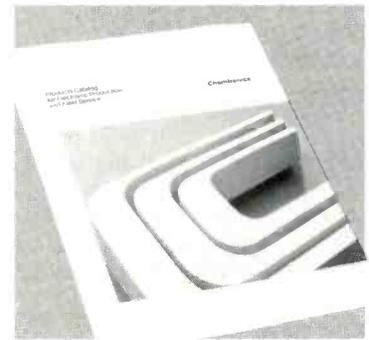

CHEMICAL SOLUTIONS

FREE CHEMTRONICS CATALOG!

Comprehensive new source for over 200 products used in electronic manufacturing and field service. Precision cleaning agents, flux removers, bulk solvents, circuit refrigerants, precision dusters, non-residual wipers, foam swabs, premoistened pads/swabs, antistatic compounds, conformal coatings, lubricants, adhesives, desoldering braids, rosin core solder and solder masking agents. Complete with technical specifications and application guide.



Chemtronics Inc.
681 Old Willets Path
Hauppauge, N.Y. 11788
516-582-3322

Circle (27) on Reply Card

Component interactions

Ever since video and audio tied the knot, the number of components and interconnections in the typical "home entertainment system" (remember when it used to be called just a stereo or TV?) has multiplied. As in any family, there are occasional spats.

As video and audio have become more complicated, people find it hard to keep up, and many a service call can result. Knowing the fundamentals might reduce the number of these nuisance problems. Not only that, but much trouble these days is *synergistic* in nature, meaning it only occurs when the entire system is hooked up.

Component placement

Let's start with the most egregious example of erroneous placement, the glass-doored stereo rack. This was surely developed by a marketing type turned interior decorator. It looks nice, keeps dust off the units, but shortens their lives. Then you can buy new ones.

The key drawback is heat build-up. The inside of a typical rack can easily run 20° or 30° above ambient after an hour or two of operation. The resultant thermal cycling is a common cause of component failure, particularly in the output section.

Even though the manufacturer usually makes a perfunctory attempt to ventilate through cutouts in the back, the only thing that will even come close to working is a fan, which I haven't seen in anything except professional 19-inch rack cabinets. Leaving the front door open would help, but most people don't. The natural tendency is to keep a door closed. Otherwise, why have a door at all?

What's a user to do? First of all, put the amplifier at the top of the stack. It generates the most heat. Granted, there will still be a phono above it, but this is the best we can do and still keep it convenient. Second, leave the door open when the system is powered up. Unless it's structurally necessary, leave the back off the rack. This improves airflow and accessibility.

Acoustic feedback

I've lost count of how many times a customer has called me up to complain that his phono sounds distorted whenever he turns it up loud. But of course, his friend, who has exactly the same stereo system, has no such problem. After some interrogation, we usually find that the phonograph is sitting on top of one of his speakers.

The name of the phenomenon is *acoustic feedback*. The musical material being played causes the speaker cabinet to vibrate, which in turn makes the tone-arm rattle, which becomes part of the music signal going back to the amp. Here we have both necessities for an oscillator: positive feedback and lots of gain. Setting the volume high enough creates a positive feedback loop, causing distortion, howling, and perhaps a blown speaker driver or amp.

Keep the turntable well away from the speakers, preferably on a wall-mounted shelf, which makes it less susceptible to vibration. Even small amounts of acoustic feedback, perhaps too weak to result in oscillation, can muddy the bass.

Impurity on TV

Ever know someone who's just had his TV repaired and

finds a misplaced blob of color on the screen? He brings it back. You degauss it. It looks A-OK on the bench.

Two hours later the blob has returned. After some questioning, you discover that he has a pair of 18-inch Altec Lansings right next to the set. Of course, he won't believe you when you tell him to put some space between the speakers and the TV. After all, the other TVs in his house have built-in speakers, and they don't have a problem!

This is where patience comes in handy. The speakers built into most TVs are puny, low-fi devices, with magnets that would be shamed by those little daisies people use to hold notes to the refrigerator. The few sets that do have good speakers usually also have magnetic shielding. High-fidelity systems don't.

Micropollution

Thanks to microprocessors, most home entertainment equipment doubles as a small RF noise generator. To prove it, use a portable AM radio to "sniff" around a VCR or late model hi-fi receiver. You'll probably get an earful of noise across most of the band. This radio garbage can cause some strange interactions. When you detect unusual interference in a home entertainment system, try changing the relative positions of various pieces of equipment.

One egregious example of poor positioning is setting a VCR on top of a TV, just above the flyback. Maybe 15.734kHz isn't really RF, but large doses of it do some strange things to the CMOS microprocessors in the typical VCR. Clocks keep bad time, function buttons work erratically. Sometimes even the video output is polluted.

Snakes out back

The spaghetti behind most audio/video systems makes the snake house at the Brookfield Zoo look underpopulated. Shields notwithstanding, every inch of that stuff is radiating a magnetic field. The best we can do is try to position cables so their interactions will be as benign as possible. Two electromagnetic characteristics work in our favor. First, cables that cross each other at right angles interact little. Second, magnetic flux falls off as the square of distance, which means that doubling the space between cables quarters the interaction.

Avoid long, parallel runs of cable, and don't mix low- and high-amplitude signal carriers in the same bundle. A good example of the worst possible setup is a parallel run of phono cable and ac power cord. Second worst would be to run the phono and speaker cables together. Not only do the signal amplitudes differ greatly, but a potential feedback path is established whenever input and output cables run together.

Remember that cables fail more often than the equipment they connect, and always suspect them first if you have an intermittent signal problem. Also, a few years of experience have taught me that if there's a dead channel and a Y connector in the same system, the Y connector is usually the culprit. I don't know why.

Any of you with good component-interaction stories ought to send them to me, care of *ES&T*. The best ones will make it into the column, and you'll have the satisfaction of seeing your name in print and helping your fellow technicians at the same time.



Readers' Exchange

No requests for Readers' Exchange items will be accepted without a full, verifiable name, address AND phone number. This information is necessary for ES&T files. Phone numbers will not be published, if so requested. Any requests received without this information will be returned. Editor.

Editor's note: Readers' Exchange items are published in the order they are received. We are happy to offer this service at no charge to you, our readers, but ask that:

- Items are typed (or legibly written).
- Your name, address and telephone number are included on the same page as your item (envelopes and contents may become separated); using your peel-off label is a good idea.
- You limit any item to no more than three units.

Please understand that **ES&T** is in production six weeks to two months ahead of publication date. Requests received in October will probably be published in the December issue. If time is of the essence or if you absolutely must get your request published, we suggest that you consider a classified ad.

Wanted:

Schematic for Maxima AM/FM/cassette car radio, model CSC 671; readout frequency chip, part no. D1708 G 011-8344 EK007. Pay any fair price. John H. Hayden, Route 6 Box 1427, Danville, VA 24541.

Service manual or wiring diagram for Lafayette transistor stereo amplifier, LA-125T. E. Cardona, Cardona Radio Music Shop, Apeninos 633, Puerto Nuevo, Puerto Rico, 00920.

SMK11 3½-inch B&W televisions, model TPS 5050, made for or by Symphonic Electronic Corporation of Lowell, MA. Need not be in working condition but must be complete. Also need the power supply or adaptor, AC30 (in Sams 1060-3). State price. Cleo Zarella, 937 Center St., Brockton, MA 02402.

Sams for VCR, MHF, TR, TSM, CB, CC, CD, CP, CMT, CSCS, SD. Rigo Palacios, 210 E. Anderson Ave., Round Rock, TX 78664.

Back issues of Radio & TV Retailing magazine; old radio knobs (especially wooden Zenith knobs); picture tubes—21FDP4, 21EAP4, 3KP4, 7JP4, 10LP4; old radio and TV advertising items. Doug Heimstead, 1349 Hillcrest Drive, Fridley, MN 55432; 612-571-1387.

Heathkit 11-5230 CRT tester and rejuvenator. Will buy or trade B&K model 177 meter. Alex Minelli, 718 Michigan St., Hibbing, MN 55746.

Deflection yoke no. TLY5503F for Quasar, chassis no. TS968, new or good condition. Armando, Claude's TV, Radio Shack, 3 Third St., Newport, VT 05855; 802-334-7074.

CRT board no. CTG for Quasar model WU94651D chassis TS962N. Paul Davis, P.O. Box 615, Manasquan, NJ 08736; 201-974-2180.

Schematic/service manual or operator's manuals: Cimron (Lear-Siegler) DMM, model 7630; Orion VTVM, model V-100M; Redco frequency counter, model RFC-250; Dumont scope, type 301-A; Radio Specialty FM deviation meter, type 1163-60-3. Will buy original, pay for copies or copy and return. Donald H. Nash, 1444 Palaski St., Port Charlotte, FL 33952; 813-629-3934.

I have a 1967 Lafayette model LR1000T stereo receiver with a faulty 6-position selector. Lafayette has gone out of business. Does anyone have information on Lafayette or the selector? Wayne Holmquist, 42 Woodway Drive, Shrewsbury, MA 01545.


Schematic for Panasonic table model AM-FM radio, model RS836S. Don Buck, 1005 S. Main, Wheaton, IL 60187; 312-979-3651 by day or 312-665-5714 evenings.

Learn how to repair VCRs...

Read

Video Corner

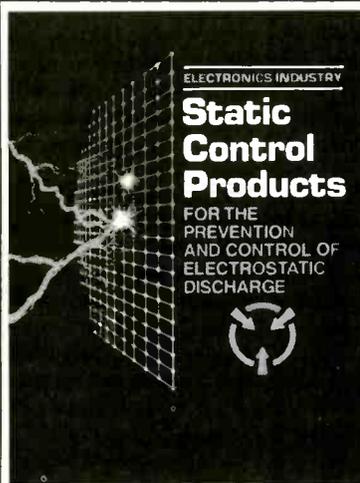each month
in **ELECTRONIC**
Servicing & Technology



COMPLETE INVENTORY OF "NAME BRAND" PRODUCTS FOR:

- * Assembly/Repair Stations
- * Q/A, Q/C Test Stations
- * Field Service Operations
- * Product Packaging & Storage
- **Fast, Dependable Delivery**
- **"Free" Applications Assistance**
- **Complete Support Facilities**
- **Competitive Pricing**

Gregory Thomas, Inc. is your "One Stop" source for static control products for the Electronics, Aerospace, Medical, Telephone, & Service Industries. Our reputation for superior products, service, and applications assistance is your assurance that your needs will be supplied with the highest quality products available, at very competitive prices, fast delivery, and full support. For all of your ESD Control Requirements, **"Call GTI before you buy!"**

GT INC. **GREGORY THOMAS INCORPORATED**
"STATIC CONTROL SPECIALISTS"
834 N. Highland Ave. • Aurora, Illinois 60506
312-859-3007 800-782-8422 (Outside IL)

MEMBER: NEDA EOS/ESD ASSOC. ASNE

Circle (28) on Reply Card

October 1987 **Electronic Servicing & Technology** 65

Grundig Majestic chassis, model 2320U radio. Must be complete, no speakers, but does not have to operate. *J.E. Humphrey, 8233 S. Figueroa St., Los Angeles, CA 90003.*

Sencore CG25 color bar generator; service manual for 65W Scott stereo amplifier, model 458A; service manual for 19-inch color TV, RCA model JC 950W, CTC 88B chassis. *George Demaris, 7387 Pershing Ave., Orlando, FL 32822-5743; 305-227-3746.*

Manual or copy of manual for Fairchild digital multimeter, model 7050. *C.E. Garrison, Rt. 6 Box 48, Warrenton, VA 22186.*

Schematic service manual or copy for Brenmar model 1500 single-sideband radio-telephone. Will pay. *N. Young, 214 East Robertson St., Brandon, FL 33511.*

Schematic for Hallcrafters S214. Also need CRT boards for Sony 4-203, 5-303, 5-305 and 5-307 micro TVs, plus a dead Sony KV5000 for parts. *Allan V. Eisenhour, 9 Rachel Carson Lane, Centerville, MA 02632; 617-775-4289.*

Owner's and/or service manual for Eico 902 audio analyzer. Eico 250 ac VTVM and amplifier. Sencore TR-139 transistor tester. Sencore Handy "53" and HP 400 EL ac voltmeter. Also need a solid-state wow and flutter meter, 2-channel ac millivoltmeter. Price must be reasonable. *Jim Pann, AV Electronic Services, 11886 San Pablo Ave., El Cerrito, CA 94530; 415-233-2900.*

Old tubes; service data for radio receivers built before 1950; audio wattmeter. 100W; Sencore SG-165 AM/FM stereo analyzer; grid-dip oscillator. *Donald G. Harris, 3332 N. 57 Ave., Phoenix, AZ 85031; 602-247-7020.*

Schematic diagram for a Quadraflex reference 240R AM/FM stereo receiver; Executone PA amplifier, model PBK 625. Will buy or make copy and return. *Andrew Y. Horeczko, 1600 W. 22nd St., San Pedro, CA 90732.*

Tektronix storage scope, type 564, whole or just the CRT #154-410, T5640-200. Please state price. *Kenny Yu, 934 Clement St., San Francisco, CA 94118; 415-387-0759.*

B&K #1000, #1076, Hickok #760 scanners and any (Flying Spot) equipment; any technical manuals. *D. Test, P.O. Box 9064, Newark, NJ 07104.*

Complete convergence assembly for Sylvania TV model CX 2174 W. *Willard Wiles, 728 E. Kingsley Ave., Panama, CA 91767; 714-622-0363.*

NRI Discovery Lab. *William P. Jarvis, 1214 Fifth Ave., Beaver Falls, PA 15010; 412-846-7735.*

Schematics for Mura-Phones models 711 and 801. Will pay \$25 for schematics. *Vitale's Electronics, RD6 Box 303, Newton, NJ 07860; 201-383-5565.*

Flyback transformer for Broadmoor TV, model 3513, part #09270776M or TCF-11. *George Saylor, 2319 Parrish St., Philadelphia, PA 19130.*

For Sale:

A.B. Dick mimeograph machine with manual, \$35; textbooks, service manuals, radio and TV parts, 700 new standard brand tubes, 85% off list price. Send large s.a.s.e. for list. *M. Seligsohn, 1455 55th St., Brooklyn, NY 11219.*

Sencore LC53 Z meter, excellent condition (less than 50 hours of use), \$600. *E. Benham, 1011 Alam Ave., Auburn, AL 36830; 205-826-4100 ext. 71 by day or 205-821-6642 evenings.*

Sams Photofact 4-drawer file cabinet full of folders starting at 1000-2000, plus several CB, TR, TSM, AR, \$300 takes all; Sencore VA-48, like new, \$750; Sencore CR-143, like new, \$150; Sencore TRC4, like new, \$40; H.P. 4260A universal bridge, \$150; B&K model 606 tube tester, \$75. *Harley W. Jansen, 1600 1st Ave., Marion, IA 52302; 319-377-3141.*

ECG transistor , 50¢ each; GC Magnameter, \$45; direct probe for scope, \$10; Beckman DM73 digital meter, \$25; Heathkit signal tracer, \$10. *John Toth, 2786 71st St. CT W, Bradenton, FL 34209; 813-795-2786.*

Western Electric 12B transmission measuring set, \$20; Atwater Kent Radio "Service Manual and Parts List," 1928-1929, \$15; Sams Auto Radio

PRB... OFFERS A COMPLETE SELECTION OF:

- VCR REPLACEMENT BELTS
- VIDEO CLUTCH TIRES

PROJECTOR-RECORDER BELT has the Replacement Belts and Video Clutch Tires you want. PLUS...

- Our new and improved MEASUR-A-BELT GUIDE helps you find the PRB Replacement Belt you need...fast.
- There's no need to disassemble and assemble your VCR clutch drive... just snap off the old... then snap on the new PRB tire.

PRB has the belts and tires you need...and the system that helps you find your replacement belts and clutch tires easily and fast for a profitable return on every sale.

PRB Belts... Made in the U.S.A.

For more information call toll free...

National 1-800-558-9572

In Wisconsin 1-800-242-9553

Business Number 1-414-473-2151

TLX 4994411 PRB USA

In Canada call collect: 1-613-225-5003.

FAX: 414/473-4727



PROJECTOR-RECORDER BELT CORP.
P.O. Box 176 Whitewater, Wisconsin 53190

Circle (29) on Reply Card

Electrodyn is rebuilding the world of Electronics

Tuner Rebuilding

- 24-hour Turnaround
- One-year Limited Warranty

TVRO Equipment Repair

- 72-hour Turnaround
- 90-day Limited Warranty

VCR Repair

- 72-hour Turnaround
- 90-day Limited Warranty

Module Repair

- 72-hour Turnaround
- One-year Limited Warranty
(see price list for exceptions)

Most Makes & Models

*Turnaround time is dependent upon parts availability

ELECTRODYN, INC.

917 S. Rogers St.
Bloomington, IN 47401
(812) 334-1023

Circle (24) on Reply Card

ATTENTION TECHNICIANS

- ★ JOB OPENINGS
- ★ MONTHLY TECHNICAL TRAINING PROGRAM
- ★ BUSINESS MANAGEMENT TRAINING
- ★ LOW COST INSURANCE
- ★ CERTIFICATION
- ★ TECHNICAL SEMINARS

All of this in a nonprofit international association for technicians

FIND OUT MORE:



604 N. Jackson St.
Greencastle, IN 46135

Manual AR1, 1949, \$10; Majestic Service Manual, 1929, \$10; Sams manuals, \$2.50 each, send s.a.s.e. for list. Shipping in U.S. included. *Donald H. Nash, 1444 Pulaski St., Port Charlotte, FL 33952; 813-629-3934.*

B&K model 466 picture tube checker and rejuvenator. Have all adapter sockets plus SP-66 main adapter for other sockets. Mint condition, barely used, must sell. \$150. *Gordon Lane, 239 Jacksonian Drive, Hermitage, TN 37076; 615-889-6195. no collect calls please.*

Sylvania CK3000 test jig, works great, all original adapters and some extra, \$250. *J.R. Hinely, P.O. Box 119, Rincon, GA 31326.*

Back issues of PF Reporter, ES&T, Radio Electronics, Electronic World and others. Send s.a.s.e. for list. *Clark Trissell, 3530 Pawnee St., Lincoln, NE 68506.*

Sencore SC-61 waveform analyzer, VA-62 video analyzer, TF-46 portable super cricket, PR-57 powerite, all for \$4,150; B&K 1077B TV analyst, \$200; B&K 466 CRT tester/rejuvenator, \$75. All in excellent condition, shipping not included. *Walt Wasyluk, Tokos TV Repair, 74368 Maricopa Drive, 29 Palms, CA 92277; 619-367-7418/9677.*

Heathkit CRT tester and rejuvenator, \$50; color/dot generator, \$50; HV 1V to 400V power supply, \$75; 1V to 15V power supply, \$20; RLC bridge, \$20; signal tracer, \$20; DMM, \$35; VTVM, \$10; component tracer, \$75; HV 40kV probe, \$15; HV 30kV probe, \$5. *C.A. Peterson, 2720 Q St., Vancouver, WA 98683; 206-694-2068.*

Instruction manuals for: signal generators (Precision series E-200-C, 1947; E-200, 1940; E-400 (sweep), 1954; and Eico 360 TV-FM (sweep), 1949;) B&K 465 set-up charts (1966, 1977); 1959 Doss Pioneer 250 horizontal sweep Quantalyst; and more. \$5 each plus COD shipping or \$50 plus shipping for all. Send s.a.s.e. for complete list. *David Lehmann, RR 2 Box 104, Mansfield, MO 65704; 417-924-3350.*

Navy signal generator (small port.) AN/USM-27B, \$50 or best offer; Mite-SCM Co. teleprinters, contact chatter tester by AECO, EPC100026, \$50; govt. T/MS, \$15 each—what are you looking for? *D. Test, P.O. Box 9064, Newark, NJ 07104.*

Power Mate power supplies, model PX-EE-28V, 115V input, 28V at 18A output, \$25 plus shipping. *Ron Baublitz, P.O. Box 37, Ellicott City, MD 21043-0037; 301-465-9453.*

Diehl Mark V analyst. New in box, with manual, never used. \$500 or trade for TV test equipment. *B&M Appliance, Geo. McNaught Jr., Star Rt. #1, Box 38, Crescent City, FL 32012; 904-698-1529.*

B&K sweep generator analyst, tube tester, make offer. RCA color jig and much more. Send s.a.s.e. for list. *ALCO 4132 W. Lincoln Ave., Cypress, CA 90630; 714-527-9060.*

Hickok Cardmatic model 123R tube checker. Will also exchange for items listed under wanted column. *Donald G. Harris, 3332 N. 57th Ave., Phoenix, AZ 85031; 602-247-7020.*

600 new standard brand tubes, 90% off list price; radio and TV parts; service manuals; text books. Send large s.a.s.e. for list. *M. Seligsohn, 1455 55th St., Brooklyn, NY 11219.*

Tested and working RCA modules for CTC-70 and CTC-85 chassis. \$1 above dud value. Send s.a.s.e. for list. *G. Stuart Electronics, 503 Sunnyside Lane, Hopkins, MN 55343.*

Selected Sams, numbers 63 through 665, plus AR-22, AR-25, AR-30 and TR-31. Total 61. \$45.75. *William J. Maida, 274 W. Sabal Palm Place, Longwood, FL 32779.*

Will make copies of diagrams, service manuals for all types of B&W or color TVs, radios, stereos, parts, etc. Send s.a.s.e. and list your needs. *Ray's TV Sales & Service, 1308 St. Louis, Gonzales, TX 78629; 512-672-2113.*

Simpson 260 series 6p overload protected VOM, in good shape, \$50. *T.W. Benson, 204 Riverside Ave., Tallahassee, AL 36078; 205-283-4266.*

Almost every issue of PF Reporters from No. 1 through present (under ES&T name): old Sams Photofacts; RCA Institute courses on radio, TV, color TV, transistors, etc. *Richard E. Bishop, 212 Taconic Road, Greenwich, CT 06831; 203-869-0422.*



Classified

Advertising rates in the Classified Section are 85 cents per word, each insertion, and must be accompanied by payment to insure publications. Each initial or abbreviation counts a full word. Minimum classified charge is \$20.00. For ads on which replies are sent to us for forwarding (blind ads), there is an additional charge of \$30.00 per insertion to cover department number, processing of replies, and mailing costs. Classified columns are not open to advertising of any products regularly produced by manufacturers unless used and no longer owned by the manufacturer or distributor.

FOR SALE

AUTOMOBILE RADIO and tape replacement parts. Delco, Chrysler, Phico-Ford, Motorola, Panasonic and many others. Large inventory. *Laran Electronics, Inc., 3768 Boston Road, Bronx, NY 10469. (212) 881-9600. National (800) 223-8314, NY State (800) 446-4430.* 1-85-tfn

VCR REPAIR SOLUTIONS FOR VHS MODELS. Volume I—150 Symptoms and cures—\$11.95. Volume II—\$11.95. All 300, \$19.95. *Eagle Electronics, 52053 Locks Lane, Granger, IN 46530.* 7-87-6t

TV/VCR "Tuff Tips" listed by mfg. and model. 1st edition—200 TV/VCR tips \$10.95, 2nd edition—200 TV/VCR tips \$10.95, both editions \$19.95. For TV tips only—1st or 2nd edition \$5.95, both editions \$10.95. For VCR tips only—1st or 2nd edition \$6.95, both editions \$12.95. *TECH CURES, 4825 Fredericksburg Road, San Antonio, Texas 78229.* 10-87-1t

"THE WORKBENCH COMPANION"—Over 200 pages of Tough Dogs and troubleshooting notes from 20 years in the business. Partial contents: Symcure Index 1970-1987, Radio Elec. Clinic 1969-1987, ETD Index ColorFax 1969-1982, Testing HV Diodes, Int. Flybacks, Zenors, etc. Important note on capacitors and much more. Price: \$29.95 + \$2.50 shipping and handling. *FARRELL ELECTRONICS, Hi-Teck, Larry Gribbin, Chief Engineer, 127 Providence Avenue, SOUTH PORTLAND, MAINE 04106.* 10-87-3t

T.V. SALES & SERVICE. Well established business located northern Virginia. Owner retiring and will help with financing. Call 703-972-7027 after 7:00 p.m. EST. 6-85-tfn

TV TOUGH DOGS: 300 symptoms and cures. Send \$7.95 to DAVIS TV, 11772 Old Fashion Way, Garden Grove, CA 92640. 10-87-tfn

TV/VCR FAILURE HISTORIES—Multiple cures for most problem areas. Send \$6.95 with mfg. and model number to **TECH CURES, 4825 Fredericksburg Road, San Antonio, Texas 78229.** Money will be refunded with free sample, if model is not on database. 10-87-1t

VCR CROSS-REFERENCE LISTINGS for the following electronically similar manufacturers: RCA, Sharp, Sylvania, Panasonic, Quasar, Magnavox, Philco, Hitachi and J.C. Penney. Each \$13.95, any 2 or more \$10.95 each. **TECH CURES, 4825 Fredericksburg Road, San Antonio, Texas 78229.** 10-87-1t

SENCORE SC61 Dual Trace Scope and Sencore VA48 Video Analyzer. Each comes with leads and manuals. Excellent condition. Plus much more! Asking \$2800.00. (312) 289-0056. 10-87-2t

SERVICE MANUALS. Large Shop has 18 yr. collection of duplicates. All original manufacturer. All new. Audio \$1.00, video \$5.00. Send SASE for list. *Tape Recorder Clinic, 4850 E. Speedway, Tucson, Arizona 85712.* 11-86-tfn

EDUCATION

CABLE TV TRAINING—Training in Cable Television Technology. Learn construction, installation, and maintenance. *Cable Correspondence Courses, Inc., P.O. Box 1319, St. Charles, MO 63302.* 7-87-tfn

HELP WANTED

VIDEO/AUDIO technician needed. Top pay and benefits for well trained and experienced technicians who are expert with consumer TV and audio equipment. Training by manufacturers such as: Sony, Hitachi, RCA, Panasonic, etc. are necessary for job experience. Write or call: **Atlantic Electronics, Inc., 1232 NE 26th St., Ft. Lauderdale, FL 33305, 305-564-8274 (10 AM to 6:30 PM).** Ask for Dave or Joe. 06-86-tfn

CAMERA-VIDEO Technicians needed. Top pay and benefits for well trained and experienced technicians who are expert with consumer and/or industrial cameras and VCR's. Training by manufacturers such as Sony, Hitachi, Panasonic, etc., are necessary for job experience. Come to sunny Florida and enjoy your work & leisure time. Write or call **ATLANTIC ELECTRONICS INC., 1232 NE 26th St., Ft. Lauderdale, FL 33305. (305) 564-8274 10 AM to 6:30 PM.** Ask for Dave or Joe. 8-85-tfn

BUSINESS OPPORTUNITIES

NORTH SHORE OF MASSACHUSETTS. Established appliance, TV, and VCR repair service with new and used sales opportunity. Real estate package available. Call for details (617) 281-1006 days. 8-87-4t

ELECTRONIC REPAIR, inventory & equipment. 11 years at same location. Small recreational town in Idaho. Owner wishes to retire. \$15,000. 208-756-2916, Box 488, Salmon, ID. 83467. 9-87-2t

"SHAMROCK TV" in San Diego, Calif.; Established 20 years—great location. Owner retiring. Call (weekdays) 619-488-8282. 10-87-1t

SERVICES

CREDIT REPAIR, Business and Commercial Loans Brokered. Free details. *Commercial Financial Group, P.O. Box 920957, Dept. 241, Houston, Texas 77292-0957.* 10-87-1t

Advertisers' Index

| | Page Number | Reader Service Number | Advertiser Hotline |
|--|-------------|-----------------------|--------------------|
| Atrix, Inc. | 28 | 35 | 800/222-6154 |
| Automated Production Equipment Corp. | 57 | 22 | 516/654-1197 |
| Beckman Industrial Corp. | IFC | 1 | 619/495-3200 |
| C + S Sales | 21 | 11 | 800/292-7711 |
| Chemtronics, Inc. | 63 | 27 | 800/645-5244 |
| Cleveland Institute of Electronics | 19 | 9 | 800/321-2155 |
| Computer Service Center | 61 | 25 | 602/889-8888 |
| Cooks Inst. Elec. Engrg. | 59 | 23 | 601/371-1351 |
| Dandy Mfg. Co. | 68 | 30 | 800/331-9658 |
| Electrobyn Corp. | 66 | 24 | 812/334-1023 |
| Electronics Warehouse Corp. | 63 | 26 | 800/221-0424 |
| ETA | 66 | | |
| Gregory Thomas, Inc. | 65 | 28 | 800/STA-TIC2 |
| Isacet | 63 | | 817/921-9101 |
| Joseph Electronics | 39 | 15 | |
| Laguardia Enterprises | 68 | 32 | 714/579-1276 |
| Leader Instrument Corp. | 5 | 36,37 | 514/337-9500 |
| Matsushita Services Co. (Publications Div.) | 25 | 13 | |
| MCM Electronics | 15 | 8 | 800/543-4330 |
| Moody Tools | 19 | 10 | 800/223-9036 |
| NAP Consumer Electronics (Technical Publications Div.) | 30 | 34 | 615/475-0400 |
| NESDA | 57,61 | | 817/921-9061 |
| NRI Schools - Electronics Division | 9 | | 202/244-1600 |
| NTE Electronics, Inc. | 3 | 4 | 800/631-1250 |
| OK Industries, Inc. | 11 | 7 | 800/523-0667 |
| Projector Recorder Belt Corp. | 66 | 29 | 800/558-9572 |
| PTS Corp. | IFC | 2 | 812/824-9331 |
| RNJ Electronics, Inc. | 29 | 14 | 800/645-5833 |
| Sencore, Inc. | 47,49,51,53 | 18,19,20,21 | 800/843-3338 |
| Sperry Tech, Inc. | 68 | 31 | 800/228-4338 |
| Technipower/A Penril Co. | 59 | 33 | 203/748-7001 |
| Tektronix, Inc. | 1A,1B,1,7 | 3,6 | 800/433-2323 |
| Tentel | 23 | 12 | 800/538-6894 |
| Test Probes, Inc. | 41 | 17 | 619/535-9292 |
| U-Can-Do VCR Educational Products Co. | 41 | 16 | 513/548-6113 |
| Zenith | BC | | |

ADVERTISING SALES OFFICES

ELECTRONIC

Servicing & Technology

ALL U.S. TERRITORIES

Greg Garrison, Sales Manager

P.O. Box 12901

Overland Park, KS 66212

Phone: (913) 888-4664

Fax: (913) 888-7243

Telex: 42-4156 INTERTEC OLPK

NORWOOD, AUSTRALIA

Hastwell, Williamson, Rouse PTY. LTD.

P.O. Box 419

Norwood, S.A. 5067

Phone: 332-3322

Telex AA 87113

LONDON, ENGLAND

Nicholas McGeachin

Roseleigh House, New Street

Deddington, Oxford OX5 4SP

Phone: (0869) 38794

Telefax: (0869) 38040

Telex: 837469 BES G

TOKYO, JAPAN

Haruki Hirayama,

EMS, Inc.

Sagami Bldg., 4-2-21, Shinjuku,

Shinjuku-ku, Tokyo 160, Japan

(03) 350-5666

Telex: 2322520 EMSINCPJ

Cable: EMSINCPERIOD

SAVE TIME

For fast, accurate service, please remove the Peel-Off Label (which is used to address your magazine) and affix it to the Reader Service Card, the Address Change Card, or to any correspondence you send us regarding your subscription.



"Tech's Guide To Pricing"
updated new 5th edition... a framework for setting rates that apply to Hi-Tech products... a formula that guarantees SUCCESS!
Call Toll Free for details
1-800-228-4338 B/S CST

Circle (31) on Reply Card

ELECTRONIC SERVICING & TECHNOLOGY Volume 7, No. 10 (USPS 462-050) is published monthly by Intertec Publishing Corp., 9221 Quivira Road, P.O. Box 12901, Overland Park, KS 66212. Second Class Postage paid at Shawnee Mission, KS, and additional mailing offices. POSTMASTER: Send address changes to ELECTRONIC SERVICING & TECHNOLOGY, P.O. Box 12952, Overland Park, KS 66212-9981.

A MUST FOR THE TV TECHNICIAN

UNIVERSAL CRT ADAPTER- Don't buy another socket for your CRT Tester! Join 10,000 satisfied buyers & WIN the Socket War! GUARANTEED to fit your tester. Test/clean/restore ALL Color, B/W, Projection. \$63.95ppd w/Setup book, Visa, MC, COD.

1-800-331-9658
DANDY MFG. CO.
2323 Gibson, Muskogee, Oklahoma 74403



Circle (30) on Reply Card

HAND REMOTE REPAIR
LA GUARDIA ENT.
5882 Rich Hill Way
Yorba Linda, CA 92686
(714) 579-1276



90 Day Warranty
New Battery Included

- Call for pricing
- 24 hr. turnaround time
- Return freight pre-paid

Circle (32) on Reply Card

New from PTS

How to make top VCR profits with no investment and no headaches.

Now you can immediately offer complete VCR remanufacturing service to your customers.

All makes. All models.

Any VCR VHS, Beta. You name it. Send it to your authorized PTS Servicenter and you'll get complete remanufacturing service.

Fast turnaround. Dependable service.

Your customer wants it fixed now. PTS has the world's largest VCR parts inventory. Fully equipped test positions are manned by factory trained technicians.

You get (and give your customers) fast, guaranteed service.

Famous PTS quality backed by a 90 day PTS warranty.

Every remanufactured VCR gets:

- Complete, thorough cleaning with special PTS approved nonabrasive chemicals and cleaning materials.
- Demagnetization of all metal parts and heads.
- Lubrication of all mechanical parts.
- Tape guide alignment.
- Head and tracking alignment.
- Latest manufacturer's updates, defective and worn parts replaced.
- Historically high failure parts automatically replaced regardless of condition.
- Complete electronic tests and checks.
- Air test and burn-in.
- PTS' 3 stage quality test and spec performance guarantee.

All services backed by PTS' exclusive full 90 day parts and labor limited warranty.

Guaranteed price guarantees your profit.

One low, flat rate includes parts and labor.

\$64^{.95*}


Suggested retail \$89.95.

*Repair price excludes VCR heads, motors, baskets, and cosmetics. These items billed at cost subject to dealer approval. Minimum bench charge of \$24.95 may apply.

Mutilated units and/or previously reworked units by technicians outside of PTS will be subject to a \$24.95 surcharge. PTS reserves the right to return any units with repair costs in excess of unit replacement value.

Get in on the nation's premier VCR profit program. Try PTS' VCR remanufacturing today.

PTS Corporation™

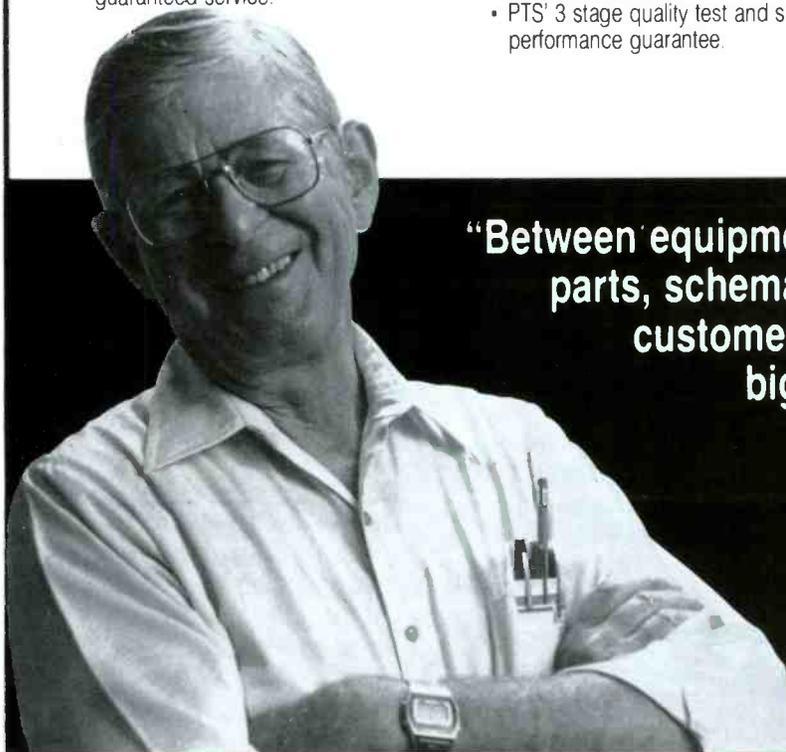

“Between equipment costs, training, parts, schematics, and impatient customers, VCR repair was one big headache. With PTS I'm making the same profit with no investment and no headaches. Thanks PTS.”

For more information or the Servicenter nearest you contact PTS Customer Service at (812) 824-9331.

Circle (2) on Reply Card

www.americanradiohistory.com

Zenith remanufactured and reconditioned
replacement modules and sub-assemblies
factory-fresh
from Exchange Counters
throughout the U.S.

There's no sense risking
an exchange anywhere else!



One of the easiest, fastest, and surest ways for you to preserve the pedigree of the Zenith products you service and maintain is with genuine Zenith replacement parts.

And at no time is this more critical than when you replace the more sophisticated components like modules, tuners, channel selectors and sub-assemblies.

Your participating Zenith parts distributor will supply you with a replacement remanufactured, reconditioned and serviced for reliability by Zenith people as dedicated and knowledgeable as those who made the original.

Equally important, the replacement module or sub-assembly you receive in exchange from your Zenith parts distributor will most likely incorporate Zenith factory modifications, if any, in effect at the time of remanufacture.

And nowhere else but in a participating Zenith parts distributor's Exchange Program can you get assurance that a replacement incorporates a Zenith factory up-date if one exists!

ZENITH
®

The quality goes in before the name goes on.®

That's why you should start taking advantage of your Zenith parts distributor's R&R Exchange Program now.

We'll help you locate the Zenith R&R Exchange Counters in your area if you'll write on your company letterhead with your complete address element and Zip Code.

Chances are there's an Exchange Counter for Zenith factory-fresh replacement modules and sub-assemblies closer than you realize.

Write, if you don't know, and we'll tell you where it is! There's no sense risking an exchange for a Zenith replacement anywhere else!