

Popular Electronics®


WORLD'S LARGEST SELLING ELECTRONICS MAGAZINE SEPTEMBER 1981/\$1

For Home Safety: A Toxic Gas Alarm

For Realistic Music: An Audio Peak Extender

For Better Circuits: VMOS Power Devices

New Ways to Use 8080 Microprocessors

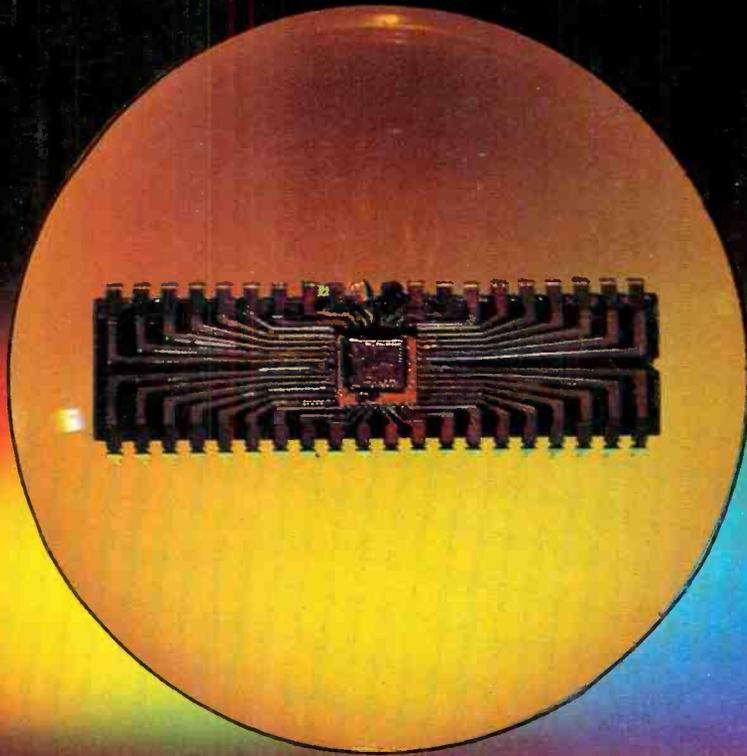


able
Computer
303092 DRK 6450M091 141D DEC83
L. DARRKELL JR
6450 MYRTLEWOOD DR
CUPERTINO CA 95014
09

Reddy Chirra improves his vision with an Apple.

Reddy is an optical engineer who's used to working for big companies and using big mainframes.


But when he started his own consulting business, he soon learned how costly mainframe time can be. So he bought himself a 48K Apple II Personal Computer.

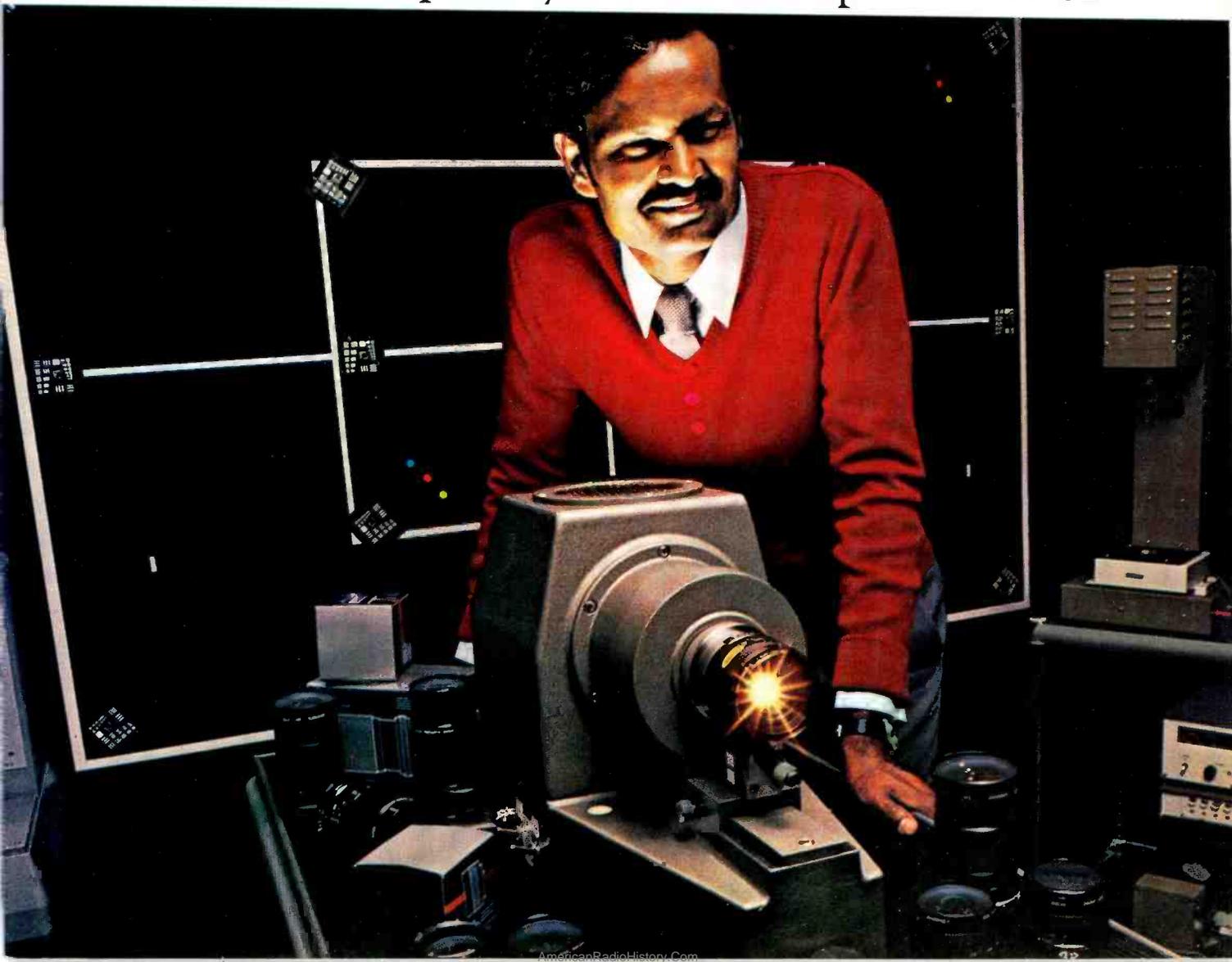And, like thousands of other engineers and scientists, quickly learned the pleasures of



cutting down on shared time
own tamper-proof data base.

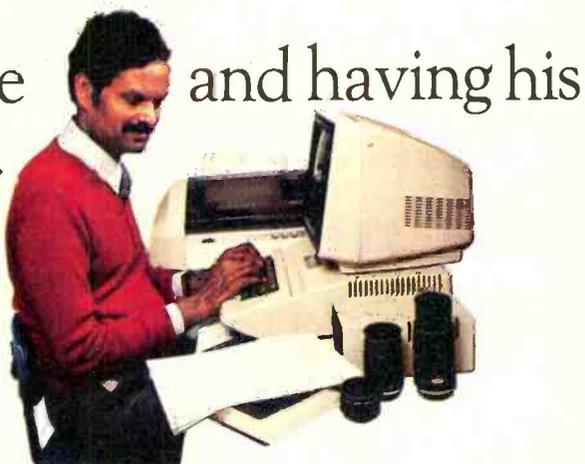His Apple can handle
formulas with up to 80 vari-
ables and test parameters on
250 different optical glasses.



He can even use BASIC, FORTRAN,
Pascal and Assembly languages.

And Apple's HI-RES graphics come in
handy for design.

Reddy looked at other microcomputers, but
chose Apple for its in-depth documentation,
reliability and expandability.

You can get up to 64K RAM in an Apple II.
Up to 128K RAM in our new Apple III. And
there's a whole family of compatible peripherals,
including an IEEE-488 bus for laboratory
instrument control.

Visit your authorized Apple dealer to find
out how far an Apple can go with scientific/
technical applications.


It'll change the way you see things.

The personal computer.  **apple**

Popular Electronics®

WORLD'S LARGEST-SELLING ELECTRONICS MAGAZINE

Protect Your Stereo System

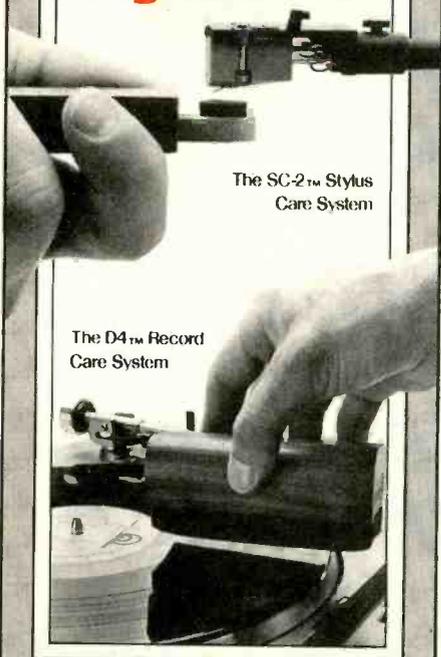

The SC-2™ Stylus Care System

The D4™ Record Care System

and Maintain Its Sound



For a free copy of our "Guide to Record Care" write to Discwasher.

discwasher®

PRODUCTS TO CARE FOR YOUR MUSIC

1407 North Providence Road,
Columbia, MO 65201 USA

A DIVISION OF JENSEN an ESMARK Company

CIRCLE 23 ON READER SERVICE CARD

Feature Articles

DESIGNING WITH THE 8080 μ PROCESSOR / Randy Carlstrom	57
<i>Part I: The Basic System</i>	
THE VMOS POWER FET / Gary McClellan	61
<i>How it can be used to simplify circuits and reduce cost.</i>	
SUCCESSFUL SOLDERING / John D. Borneman	67
<i>Tips on materials, tools, and techniques.</i>	
SIMPLE DISPLAY AND OPERATING PROGRAM FOR THE EXPANDED ELF / Jack Dollhausen	84
<i>Permits easy machine-language input to an 1802-based system.</i>	

Construction Articles

PEAK UNLIMITER AUDIO DYNAMIC RANGE PROCESSOR / John Sutton	75
<i>Extends compressed peaks in recorded music.</i>	
AN ALARM FOR TOXIC GASES / Cass Lewart	79
<i>Detects low concentrations of dangerous air pollutants.</i>	
SINGLE-LED ANALOG METER / David Leithauser	81
<i>Complete LED changes "color" with input voltage.</i>	

Equipment Reviews

BANG & OLUFSEN BEOGRAM MODEL 8000 TURNTABLE	21
SAMPO MODEL 9519 19" COLOR TV RECEIVER	27
SENCORE MODEL SC60 WIDEBANDER DUAL TRACE OSCILLOSCOPE	31
APPLE II PLUS PERSONAL COMPUTER SYSTEM	39

Columns

ENTERTAINMENT ELECTRONICS / Ivan Berger	14
<i>Video Accessories from the Camera Store.</i>	
COMPUTER BITS / Carl Warren	45
<i>High-End Systems (for Low-End Buyers).</i>	
COMPUTER SOURCES / Leslie Solomon	47
HOBBY SCENE / John J. McVeigh	83
SOLID-STATE DEVELOPMENTS / Forrest M. Mims	86
<i>The Billion Transistor Chip?</i>	
EXPERIMENTER'S CORNER / Forrest M. Mims	90
<i>Experimenting with an Air Pressure Switch.</i>	
DX LISTENING / Glenn Hauser	96
<i>Strikes Disrupt International Broadcasting.</i>	
PROJECT OF THE MONTH / Forrest M. Mims	104
<i>Precision CMOS Clock Generator.</i>	


Departments

EDITORIAL / Art Salsberg	4
LETTERS	8
NEW PRODUCTS	10
TIPS AND TECHNIQUES	98
ELECTRONICS LIBRARY	99
NEW LITERATURE	100
OPERATION ASSIST	102
ADVERTISERS INDEX	121
PERSONAL ELECTRONICS NEWS	122

COVER PHOTO BY FRED BURRELL: Copyright © 1981

COPYRIGHT © 1981 BY ZIFF-DAVIS PUBLISHING COMPANY. All rights reserved. Popular Electronics (ISSN 0032-4485) September 1981, Volume 19, Number 9. Published monthly by Ziff-Davis Publishing Co., at One Park Ave., New York, NY 10016. Richard P. Friese, President; Selwyn Taubman, Treasurer; Bertram A. Abrams, Secretary. One year subscription rate for U.S. and Possessions, \$15.00; Canada, \$20.00; all other countries, \$23.00 (cash orders only, payable in U.S. currency). Second Class Postage Paid at New York, N.Y. 10016 and at additional mailing offices. Authorized as second class mail by the Post Office Dept., Ottawa, Canada, and for payment of postage in cash. POPULAR ELECTRONICS including ELECTRONICS WORLD, Trade Mark Registered. Indexed in the Reader's Guide to Periodical Literature. Ziff-Davis also publishes Boating, Car and Driver, Cycle, Flying, Popular Photography, Skiing, Stereo Review, Electronic Experimenter's Handbook, and Tape Recording & Buying Guide. Forms 3579 and all Subscription Correspondence: POPULAR ELECTRONICS, Circulation Dept., P.O. Box 2774, Boulder, CO 80302. Please allow at least eight weeks for change of address, enclosing, if possible, an address label from a recent issue. Permissions. Material in this publication may not be reproduced in any form without permission. Requests for permission should be directed to John Babcock, Rights and Permissions, Ziff-Davis Publishing Co., One Park Ave., New York, NY 10016.

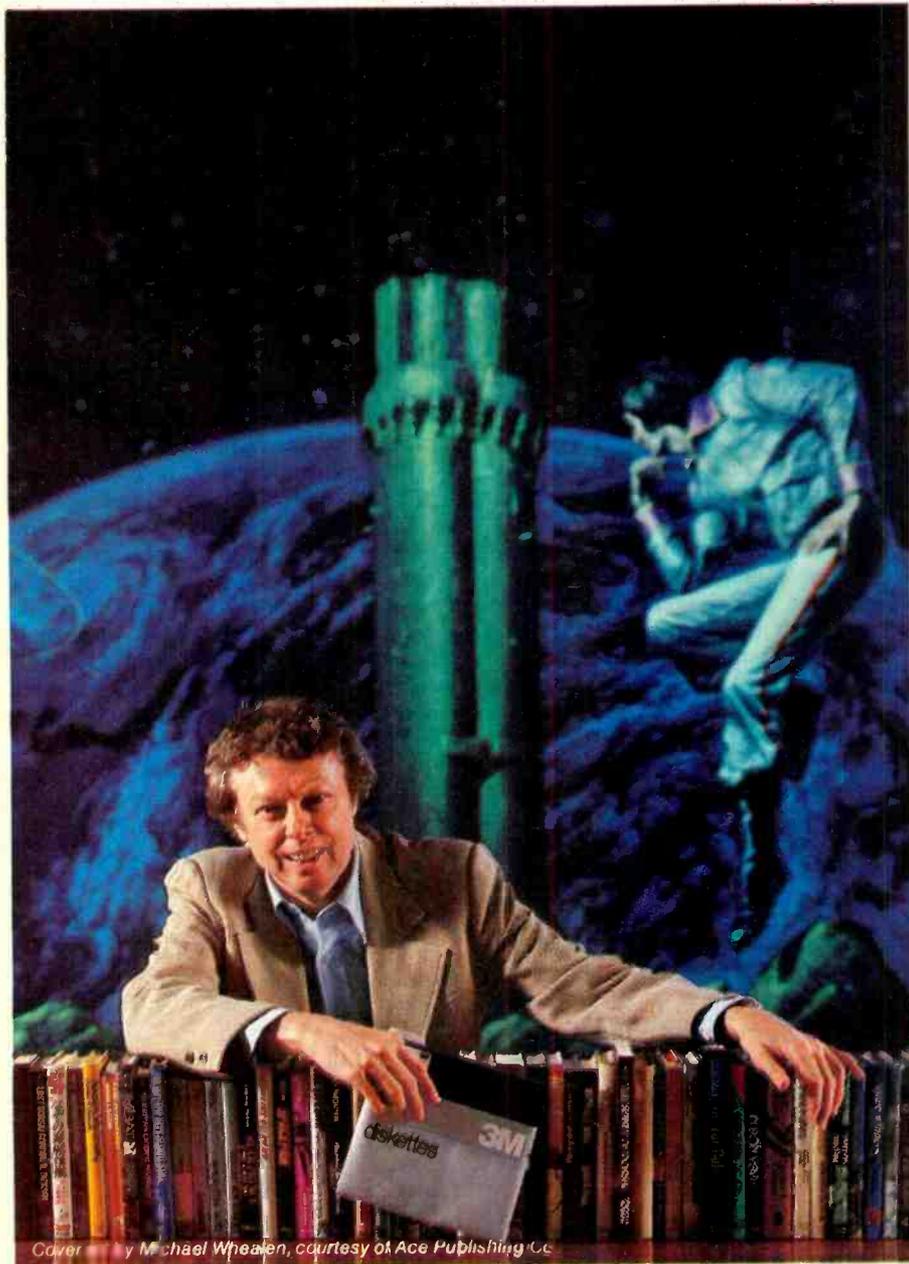"My computer helped me write The Final Encyclopedia. I wouldn't trust anything less than Scotch® Brand Diskettes to make a long story short."



**Gordon R. Dickson,
Science Fiction Author,
Minneapolis, Minnesota**

Gordon Dickson: a small businessman whose product is his own imagination. He's written more than 40 novels and 150 short stories; his newest work is *The Final Encyclopedia*. He uses his personal computer and word processing software to maximize his production. All his words—his product—are stored on diskettes. He calls up sentences and paragraphs on demand, and gets more rewrite out of the time available. So he depends on Scotch diskettes to save himself production time.

Dependable Scotch media can work just as hard for you. Each Scotch diskette is tested before it leaves our factory, and certified error-free. So you can expect it to perform exactly right.

Scotch 8" and 5¼" diskettes are compatible with computer/diskette systems like TRS-80, Apple, PET, Wang and many others. Get them from your local 3M distributor. For the one nearest you, call toll-free: 800/328-1300. (In Minnesota, call collect: 612/736-9625.) Ask for the Data Recording Products Division. In Canada, contact 3M Canada, Inc., Ontario.

**If it's worth remembering,
it's worth Scotch
Data Recording Products.**



3M Hears You...

3M



EDITORIAL

COMPUTER LITERACY

"... an essential outcome of contemporary education is computer literacy."—*Mathematics Teacher*, May '78.

More than three years after the above statement was published, the outcome is not as positive as one might wish, though some progress has been made toward the goal. Attitudinally, few people today seriously question the need for computer literacy in the upcoming generation of adults in the U.S. And more and more computers are being purchased by educational institutions for student-related activities as well as for nonteaching purposes. But only 15 percent of all U.S. public schools use computers for the foregoing activities, according to a recent survey by the National Institute of Education.

Before great strides can be made to develop computer literacy through school programs, there must be satisfactory answers to a series of questions. Where does the money come from? For equipment. For software and related computer material. For development of effective curricula. For teacher training.

We know that government funding for educational material is harder to come by than in the past. Certainly, a bad taste remains from the halcyon days of easy federal and state money for educa-

tion. Much of the equipment bought then now gathers dust in storerooms. We cannot allow this to happen again, of course. Nonetheless, to prepare students today for the computerized society they will face in the future will doubtlessly require governmental assistance.

Along these lines, there have been bills in Congress to establish a national commission to study information technology, another to amend Title III of the Elementary and Secondary Education Act of 1965 to establish a National Center for Personal Computers in Education, and a bill to be reintroduced for federal funds to establish an information clearing house to encourage computer use in school systems.

Other countries are addressing the educational challenge to prepare students for a computerized society. France has a government-funded five-year plan started in 1978 to have a microcomputer in each of its 7,200 secondary schools to train teachers and students in the use of one. Japan, too, has embarked on a funded program for developing computer-assisted instruction, though programming in Kanji-Kana is much more complicated than with our alphabetic language.

Interestingly, Seymour Papert, a math

professor at the Massachusetts Institute of Technology, proposes that a child entering school be issued a microcomputer for school and home use. Nice thought, but in an age where even pencils are at a premium, this is unlikely to happen. He also observes that computer teaching to date has been unimaginative and simply mimics traditionally deficient teaching methods. He points out a more innovative method used by the MIT Children's Learning Lab. Here a child is taught a computer language, LOGO, with which he interacts to solve a math problem or learn a new word.

So the problems of adding a fourth "R" to pre-college education are not without challenge. But if we don't embark on developing a computer-literate population in earnest, our economic position will deteriorate as time passes. Furthermore, academically disadvantaged students will fall behind in the new industrial revolution that we're in right now because more affluent students will surely own their own micro just as they own hi-fi stereo components.

Popular Electronics

JOE MESICS
Publisher

ARTHUR P. SALSBERG
Editorial Director

HAROLD A. RODGERS
Executive Editor

LESLIE SOLOMON
Senior Technical Editor

JOHN R. RIGGS
Managing Editor

EDWARD I. BUXBAUM
Art Director

JOHN J. McVEIGH
Technical Editor

DAVID M. WEBER
Features Editor

ANDRE DUZANT
Technical Illustrator

CARMEN ROBLES
Production Editor

JEFF NEWMAN
Editorial Assistant

Contributing Editors

Carl Warren, Stan Prentiss
Glenn Hauser, Julian Hirsch, Forrest Mims

MARIE MAESTRI
Executive Assistant

Editorial and Executive Offices
One Park Avenue
New York, New York 10016
212 725-3500

Publisher
Joe Mesics
212 725-3568

New York Office
Advertising Manager:
Richard Govatski (725-7460)

Eastern Advertising Manager
Bonnie B. Kaiser (725-3580)
Richard B. Eicher (725-3578)

Midwestern Office
Suite 1400, 180 N. Michigan Ave.,
Chicago, IL 60601 (312 346-2600)
Sales: Ted Welch

Western Representative
Norman S. Schindler & Associates, Inc.
7050 Owensmouth Ave., #209
Canoga Park, CA 91303 (213 999-1414)
Sales: Norm Schindler, Jon Marshall

Representation in Japan
James Yagi
Oji Palace Aoyama
6-25, Minami Aoyama, 6 Chome, Minato-Ku
Tokyo, Japan (407-1930/6821, 582-2851)

Ziff-Davis Publishing Company
Richard P. Friese
Albert S. Traina

President
President, Consumer
Magazine Division
Executive Vice President
Senior Vice
Presidents

Furman Hebb
Phillip T. Heffernan
Sidney Holtz
Edward D. Muhlfield
Philip Sine

Vice Presidents

Robert Bavier
Baird Davis
Edgar W. Hopper
George Morrissey

Selwyn Taubman
Bertram A. Abrams

Treasurer
Secretary

Editorial correspondence: POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. Editorial contributions must be accompanied by return postage and will be handled with reasonable care; however, publisher assumes no responsibility for return or safety of manuscripts, art work, or models submitted.

The publisher has no knowledge of any proprietary rights which will be violated by the making or using of any items disclosed in this issue.



Member Audit Bureau
of Circulations



POPULAR ELECTRONICS

"No one else gives you as many functions in a handheld DMM.

Now you can move up to Fluke."

We've got great news for people who've been holding out for a high quality, high performance DMM at a moderate price: Fluke's new nine-function model D 804 is now available at select electronics supply stores.

With a suggested U.S. price of only \$249 and features you won't find in any other handheld DMM, the D 804 is an exceptional value. Here's why.

Logic level and continuity testing: A real time-saver for troubleshooting passive circuits in pcb's, cables, relay panels and the like. The D 804 has a switch-selectable audible tone and visual symbols to indicate continuity or logic levels.

Direct temperature readings in °C: Used with any K-type

thermocouple, the D 804 delivers fully-compensated readings in °C from -20°C to +1265°C, for checking heating and refrigeration systems.


Peak hold feature captures transients: A short-term memory in the D 804 captures and holds the peak reading of a motor starting current.

And more: 0.1% basic dc accuracy, conductance, 26 measurement ranges, battery, safety-designed test leads and a one year parts and labor warranty. A full line of accessories is also available to extend the measurement capabilities of your DMM.

Ask your dealer about the powerful, versatile D 804 and the rest of Fluke's new Series D line of low-cost digital multimeters.



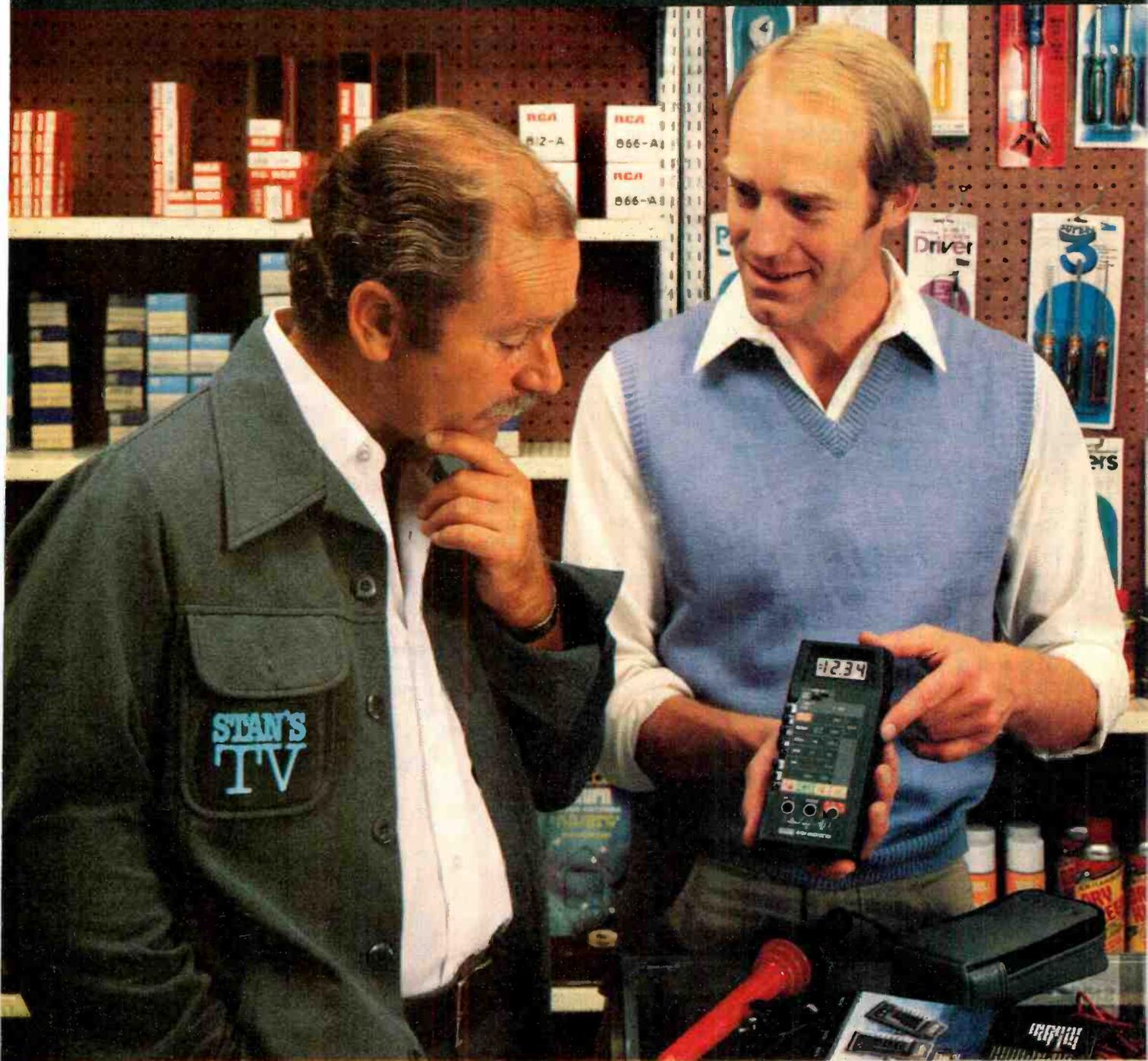From the world leader in DMM's. Now we've designed one for you.



*Suggested U.S. list price
For technical data circle no.
22 ON FREE INFORMATION CARD

If your dealer doesn't carry Series D Multimeters yet, call this number. We'll be happy to tell you who does. 1-800-426-9182

FLUKE[®]

TWELVE STRONG HEATH/ZENITH YOUR

Pick a strong partner


A computer purchase is the beginning of a long term partnership between you and the people you buy from. Your ongoing need for software and accessories requires a partner who will stand by you with a growing line of products. And nowhere will you find a more complete line of hardware, software and accessories than at your Heathkit Electronic Center. Here are twelve strong reasons to make Heath/Zenith your partner.

1. The All-In-One Computer

The heart of the Heath/Zenith line is the stand-alone *89 Computer*. It's a complete system with built-in 5¼-inch floppy disk drive, professional keyboard and keypad, smart video terminal, two Z80 microprocessors, and two RS-232C serial I/O ports. It comes with 16K RAM, expandable to 64K.

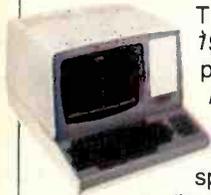2. Peripherals

These include the popular *Heath/Zenith 19 Smart Video Terminal*, loaded with professional features. And the *14 Line Printer*, priced as low as \$495. Other printer brands are on display, including high-speed, typewriter-quality printers.



3. Software

Word processing, includes reliable, easy-to-use Zenith Electronic Typing and powerful, full-featured WORDSTAR.

Small Business Programs, feature General Ledger and Inventory Control.

HUG, Heath Users' Group, offers members a library of over 500 low-cost programs for home, work or play.

4. Programming Languages



For your own custom programs, Microsoft languages are available in BASIC (compiler and interpreter), FORTRAN and COBOL.

5. Operating Systems

Three versatile systems give you the capability to perform your specific tasks.

CP/M by *Digital Research* makes your system compatible with thousands of popular CP/M programs.

UCSD P-System with Pascal is a complete program development and execution environment.

HDOS, Heath Disk Operating System gives you a sophisticated, flexible environment for program construction, storage and editing.

6. Utility Software

Expand the performance range of your computer with a broad selection of utility tools, including the best of *Digital Research* and the complete line of innovative *Softstuff* products.

7. Disk Systems

The 8-inch Heath/Zenith 47 Dual Disk System adds over 2 megabytes of storage to your



89 Computer. Diskettes are standard IBM 3740 format, double-sided, double-density.

The 5¼-inch 87 Dual Disk System adds 200K bytes of storage to your 89. Both disk systems feature read/write protection and easy plug-in adaptability.





8. Self-Study Courses

Learn at your own pace with *Programming Courses* that teach you to write and run your own programs in Assembly, BASIC, Pascal or COBOL.

A course on *Computer Concepts for Small Business* gives you the understanding to evaluate the ways a computer can benefit your business.

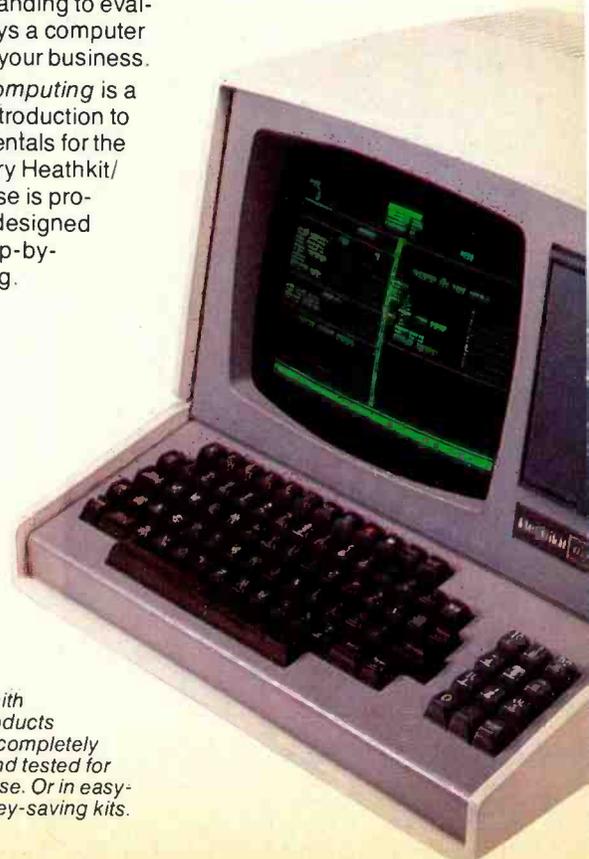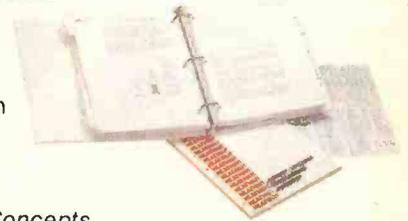Personal Computing is a complete introduction to the fundamentals for the novice. Every Heathkit/Zenith course is professionally designed for easy, step-by-step learning.



All Heath/Zenith Computer Products are available completely assembled and tested for commercial use. Or in easy-to-build, money-saving kits.

REASONS TO MAKE COMPUTER PARTNER

9. Expansion Options

Communicate with the outside world through a *Three-port EIA RS-232C Serial Interface*.

Expand RAM to 64K with easy-to-install *expansion chips*.

10. Accessories



Your Heathkit Electronic Center has the latest in modems, black-and-white and color video monitors, computer furniture and a full line of supplies, accessories, books and parts.

11. Service

No one stands by you like Heath/Zenith.

We help you get your system up and running smoothly. Service is available from trained technicians, over the phone or at one of 56 Heathkit Electronic Centers.



12. Value

Your money buys you more because Heath/Zenith prices are among the industry's most competitive. Make your own comparison and find out how much you can save.

Complete, integrated computer hardware and software, designed to serve you and to grow with you — that's what to look for in a strong partner. And with Heath/Zenith you get it all under one roof.

All at your Heathkit Electronic Center

Pick the store nearest you from the list at right. And stop in today for a demonstration of the Heath/Zenith 89 Computer System. If you can't get to a store, send \$1.00 for the latest Heathkit® Catalog and the new Zenith Data Systems Catalog of assembled commercial computers. Write to Heath Co., Dept. 010-814 Benton Harbor, MI 49022.

Visit Your Heathkit Electronic Center*

where Heath/Zenith Products are displayed, sold and serviced.

- | | | |
|--|--|---|
| PHOENIX, AZ
2727 W. Indian School Rd.
602-279-6247 | MISSION, KS
5960 Lamar Ave.
913-362-4486 | CLEVELAND, OH
28100 Chagrin Blvd.
216-292-7553 |
| ANAHEIM, CA
330 E. Ball Rd.
714-776-9420 | LOUISVILLE, KY
12401 Shelbyville Rd.
502-245-7211 | COLUMBUS, OH
2500 Morse Rd.
614-475-7200 |
| CAMPBELL, CA
2350 S. Bascom Ave.
408-377-8920 | KENNER, LA
1900 Veterans Memorial Hwy.
504-467-6321 | TOLEDO, OH
48 S. Byrne Rd.
419-537-1887 |
| EL CERRITO, CA
6000 Potrero Ave.
415-236-8870 | BALTIMORE, MD
1713 E. Joppa Rd.
301-661-4446 | WOODLAWN, OH
10133 Springfield Pike
513-771-8850 |
| LA MESA, CA
8363 Center Dr.
714-461-0110 | ROCKVILLE, MD
5542 Nicholson Lane
301-881-5420 | OKLAHOMA CITY, OK
2727 Northwest Expressway
405-848-7593 |
| LOS ANGELES, CA
2309 S. Flower St.
213-749-0261 | PEABODY, MA
242 Andover St.
617-531-9330 | FRAZER, PA
630 Lancaster Pike
(Rt. 30)
215-647-5555 |
| POMONA, CA
1555 N. Orange Grove Ave.
714-623-3543 | WELLESLEY, MA
165 Worcester Ave.
617-237-1510 | PHILADELPHIA, PA
6318 Roosevelt Blvd.
215-288-0180 |
| REDWOOD CITY, CA
2001 Middlefield Rd.
415-365-8155 | DETROIT, MI
18645 W. Eight Mile Rd.
313-535-6480 | PITTSBURGH, PA
3482 Wm. Penn Hwy.
412-824-3564 |
| SACRAMENTO, CA
1860 Fulton Ave.
916-486-1575 | E. DETROIT, MI
18149 E. Eight Mile Rd.
313-772-0416 | WARWICK, RI
558 Greenwich Ave.
401-738-5150 |
| WOODLAND HILLS, CA
22504 Ventura Blvd.
213-883-0531 | HOPKINS, MN
101 Shady Oak Rd.
612-938-6371 | DALLAS, TX
2715 Ross Ave.
214-826-4053 |
| DENVER, CO
5940 W. 38th Ave.
303-422-3408 | ST. PAUL, MN
1645 White Bear Ave.
612-778-1211 | HOUSTON, TX
1704 W. Loop N.
713-869-5263 |
| AVON, CT
395 W. Main St. (Rt. 44)
203-678-0323 | BRIDGETON, MO
3794 McKelvey Rd.
314-291-1850 | SAN ANTONIO, TX
7111 Blanco Road
512-341-8876 |
| HIALEAH, FL
4705 W. 16th Ave.
305-823-2280 | OMAHA, NE
9207 Maple St.
402-391-2071 | MIDVALE, UT
58 East 7200 South
801-566-4626 |
| PLANTATION, FL
7173 W. Broward Blvd.
305-791-7300 | ASBURY PARK, NJ
1013 State Hwy. 35
201-775-1231 | ALEXANDRIA, VA
6201 Richmond Hwy.
703-765-5515 |
| TAMPA, FL
4019 W. Hillsborough Ave.
813-886-2541 | FAIR LAWN, NJ
35-07 Broadway (Rt. 4)
201-791-6935 | VIRGINIA BEACH, VA
1055 Independence Blvd.
804-460-0997 |
| ATLANTA, GA
5285 Roswell Rd.
404-252-4341 | AMHERST, NY
3476 Sheridan Dr.
716-835-3090 | SEATTLE, WA
505 8th Ave. N.
206-682-2172 |
| CHICAGO, IL
3462-66 W. Devon Ave.
312-583-3920 | JERICHO, L.I. NY
15 Jericho Turnpike
516-334-8181 | TUKWILA, WA
15439 53rd Ave. S.
206-246-5358 |
| DOWNERS GROVE, IL
224 Ogden Ave.
312-852-1304 | ROCHESTER, NY
937 Jefferson Rd.
716-424-2560 | MILWAUKEE, WI
5215 W. Fond du Lac
414-873-8250 |
| INDIANAPOLIS, IN
2112 E. 62nd St.
317-257-4321 | N. WHITE PLAINS, NY
7 Reservoir Rd.
914-761-7690 | |


Prices and specifications subject to change without notice.

*Units of Veritechnology Electronics Corporation in the U.S.

HEATH/ZENITH

Your strong partner

THERE'S A CROWD
IN YOUR
LIVING ROOM,

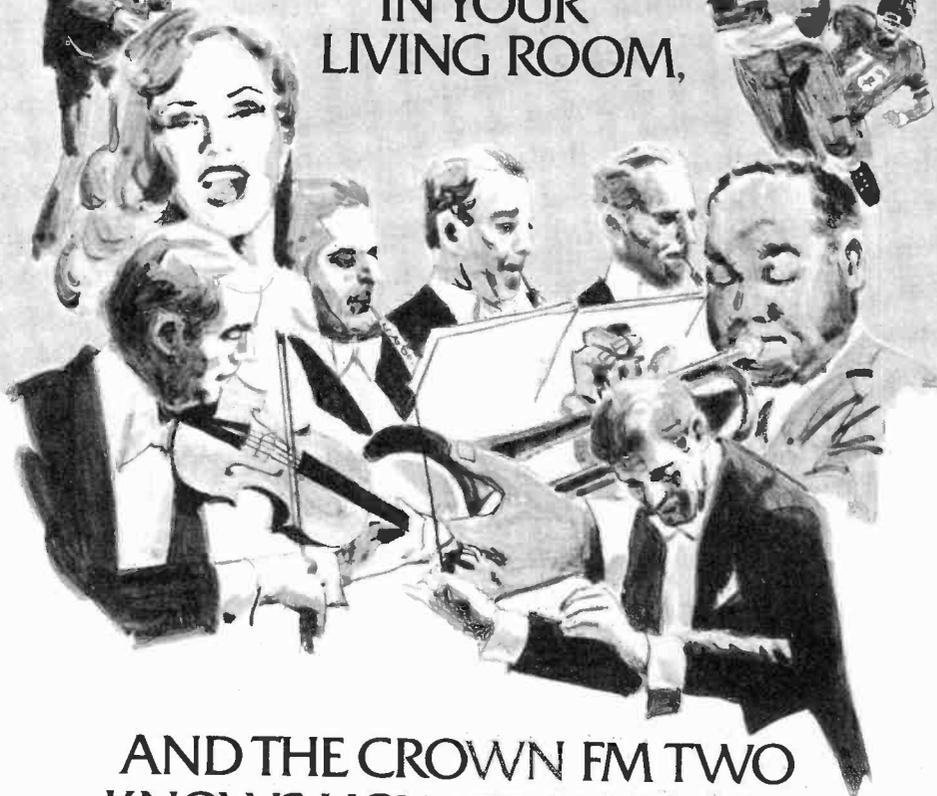

AND THE CROWN FM TWO
KNOWS HOW TO HANDLE IT.



As more FM stations crowd into your listening room, your music enjoyment may be spoiled by confusing combinations of signals caused by RF intermodulation.

The Crown FM TWO has a new cascade J-FET front-end that keeps every signal at its assigned frequency, for clear, undisturbed listening no matter how many FM stations may be on your antenna.

The FM TWO puts more of the latest tuner technology into an attractive, slim-line package. Automatic alignment, pulse-count digital detection, touch-button tuning and six-station memory will all enhance the sonic quality of your system.

THD lower than .05% for bright, bril-

liant reproduction. S/N 80dB for clean output. Stereo separation 60dB @ 1KHz for listening excitement.

But specs are only the beginning. The Crown FM TWO really "listens" better. You can experience that for yourself at your Crown dealer, or ask for a home trial (available at most dealers). Judge carefully how much more real each station sounds with the FM TWO.

Complete information on the FM TWO, on Crown and on other Crown components for home audio systems is in the *Crown Information Package*. Send us the coupon and \$5 and we'll send you the complete package of colorful, fact-filled brochures, reprints of reviews, technical articles by Crown people, price and dealer listings.



CROWN[®]

...WHEN YOU'RE READY FOR REAL!

The Crown Information Package is also available free from your dealer. If you need a list of Crown dealers, use the Reader Service Card number, or call 219/294-5571.

CROWN INTERNATIONAL, Dept. FM
1718 W. Mishawaka Road, Elkhart, Indiana 46517
Here's my \$5 (outside U.S. and Canada, \$8). Send my Crown Information Package, with money-back guarantee.

Name _____

Address _____

City _____ State _____ Zip _____

Phone _____ / _____

CIRCLE NO. 18 ON FREE INFORMATION CARD

AmericanRadioHistory.Com

LETTERS

Motorcycle Headlight Precautions

Anyone planning to build the "Headlight Modulator for Cycle Safety" (June 1981) should be aware of the following restrictions and precautions:

(1) In some states (including Maryland), a headlight modulator is illegal except on emergency vehicles. Check the requirements with your state's motor vehicle authorities.

(2) The U.S. Dept. of Transportation and other agencies have conducted tests whose results indicate that the modulator may confuse others rather than identify the motorcycle.

(3) On all recent-model motorcycles the headlights are turned "on" automatically when the starter is activated. Additional aids to cycle conspicuity are bright headgear and clothing and reflective items either worn or on the bike.
—R. J. Salehar, *Automotive Safety Engineer, Maryland Dept. of Transportation, Glen Burnie, MD.*

Technicolor VCR

In the article "A Buyer's Guide: Video Cassette Recorders" (July 1981), it should have been stated that Technicolor does have a tuner (Model 5112) to go with its video cassette recorder—whose model number, incidentally, is 212. —*Dave Gassner, Technicolor, Inc., Costa Mesa, CA.*

Testing Stress

I read with interest your comments in the "Entertainment Electronics" column in your June issue concerning the alleged findings by Dr. Diamond that digital recordings are "stressful." I thought you might be interested in the results of a clinical test wherein another one of Dr. Diamond's assertions, namely that rock music is harmful to health, was tested. The outcome of the test showed that Dr. Diamond's assertions are based solely on the dubious use of "BK" muscle testing and are erroneous.

Dr. Greenhill gave an excellent review of the poor validity of the "BK" testing approach when he explained its effects on the basis of expectation, suggestion, and just plain poor testing controls. The only likely harm that will come to an individual who listens to digital recordings is that he may enjoy it so much he misses dinner! —*Dr. L.G. Morgan, Morgan Chiropractic Clinic, Nampa, ID.*

POPULAR ELECTRONICS

illegitimate child

Rip-off or spin-off, you've never heard sound like you'll hear from the headphones you can get for only \$5 pictured below. But there's a catch.



It was spawned by Sony. And, it's an entirely new technology. No more cheap paper speakers and heavy magnets. Sound is reproduced with such clarity and power that it will send shivers up and down your spine.

Sony's MDR-3 headphones sell for about \$50, and they've been worth it. Now you can have DAK's for only \$5. We challenge you to take them to your favorite Hi Fi store and compare them to Sony's. But there are 2 things you ought to know.

Thing One. If you can hear a difference, any difference at all, not only can you return them and get your money back, but we'll also give you a free gift for your trouble.

YOU'VE BEEN THERE BEFORE

You may already be familiar with the sound produced by these headphones. If you've ever sat in the very front row during a symphony concert, or right in the middle of a live jazz band, you know the spine tingling thrill of the full rich sound that envelops you.

If you sit even 10 rows back, you lose the feeling. You still listen to the music, but you can't touch or taste the sound.

It's only when you sit right up front that the sound is alive with electricity. It's the same sound you get with Sony's MDR-3s and DAK's \$5 stereophones.

ILLEGITIMATE CHILD

Not recognized by law as a lawful offspring.

The technology is new. Up until the Sony featherweight headphones were introduced, most headphones were simply uncomfortable miniature speaker systems that you wore on your ears.

The Sony breakthrough was made possible by changing the cheap paper speaker cones to mylar diaphragms, and by using the powerful rare earth magnet Samarium to move the diaphragms.

The mylar diaphragms are much more accurate than paper and have a drastically improved dynamic range. The result is a headphone that weighs less than 2 ounces and yet produces 20-20,000hz

sounds better than a theater sized loud speaker system.

Sony fathered the technology for these headphones and obviously has no connection to DAK, but the technological heritage will become vividly apparent when you compare the sound of these marvelous headphones side by side. DAK's come with a full one year limited warranty.

THE CATCH

Thing two. Frankly we are losing our shirts on the headphones, but we're taking a gamble because we want you to try our audio cassettes.

In order to get the \$50 value pair of featherweight headphones for only \$5, we want you to try 10 DAK High Energy, Normal Bias 90 minute cassettes for only \$2.19 each.

DAK's price is less than half the price of the competition, and each cassette comes with a deluxe index insert card, a box and a one year guarantee.

You're very valuable to us in the form of future business. DAK has excited over 80,000 of you valuable customers with special bonuses like the headphones. We find most of you keep buying once you try our cassettes and our prices; and that's a gamble worth taking.

NOT A BAD CATCH

DAK manufactures a cassette that you can really forget about. Great sound, and no problems.

We make mostly industrial cassettes for high speed duplication. We've developed a special jam proof cassette. It uses a spring tension liner within the cassette that guides the tape as it winds.

We coat these liners with a new chemical called Molysulfide which drastically reduces friction within the cassette.

Hi Frequency Protection! As tape moves within the cassette friction causes the build up of static electricity. Static electricity is drastically reduced by the low friction of the Molysulfide and so is its tendency to erase very high frequencies. A very important consider-

ation for often played tapes.

MAXELL 'TAPE' IS BETTER

Yes, honestly, if you own a \$100 cassette deck like a Nakamichi, the frequency responses of Maxell UDXL or TDK SA are slightly superior and you just might be able to hear a difference.

DAK ML has a frequency response that is flat from 40-14,500hz ± 3 db. Virtually all cassette recorders priced under \$600 are flat ± 3 db from 40hz to about 12,500hz, so we have over 2000hz to spare, and you'll probably never notice the difference.

No apology. We feel that we have equaled or exceeded the mechanical reliability of virtually all cassettes and offer one of the best frequency responses in the industry.

TRY DAK ML90 CASSETTES RISK FREE

Try these high energy cassettes and the featherweight headphones in your own home for 30 days. If you aren't 100% satisfied for any reason, return only 9 of the 10 cassettes and the headphones for a courteous refund. The 10th cassette is a gift from DAK for your time.

To order your 10 DAK ML 90 minute high energy cassettes at \$2.19 each and get the headphones for only \$5 with your credit card, call the DAK toll free number below, or send your check for only \$21.90 for the tapes, plus \$5 for the headphones, and \$3 for postage and handling for each group. Order No 9186 (CA residents please add 6% sales tax).

Why not order an extra group of 10 DAK ML90 cassettes. We will add one free ML90 cassette to each additional group you buy and of course you can get a headphone for \$5 with each group.




Call TOLL-FREE(800) 423-2636
In California Call(213) 984-1559
10845 Vanowen St., North Hollywood, CA 91605

NEW PRODUCTS

Additional information on new products covered in this section is available from the manufacturers. Either circle the item's code number on the Free Information Card or write to the manufacturer at the address given.

Hand-Held Computer

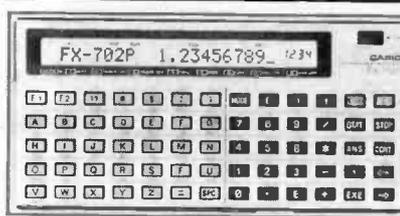


Casio's FX-702P hand-held computer has an alphanumeric keyboard, and uses BASIC as its programming language. It has a memory capacity of 1,680 steps (26 variables). The unit can interface with a printer, and is capable of accepting a ROM package to expand programming capacity. It can also transfer programs directly to a cassette recorder. \$249.95.

CIRCLE NO. 88 ON FREE INFORMATION CARD

Weather Radio Receiver

Radio Shack has announced a new three-channel weather broadcast receiver. Model 12-152 allows instant station selection with a three-position switch. Each position is crystal-tuned to one of the three vhf FM stations used by the NOAA: 162.550, 162.475, or 162.400 MHz. A telescoping antenna is attached. Power is provided by


Subwoofer Kit From Heath

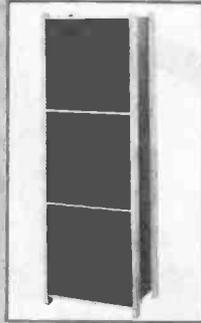

The AS-1320 has an 8-ohm, 15-inch, long-throw driver with 2-inch, four-layer voice coil in a vented enclosure. A 6-inch tuned vent is loaded into the floor. Frequency response is rated as 22 to 500 Hz \pm 3 dB, while overall frequency range is claimed to be 15 to 750 Hz. Amplifier power of at least 30 watts is necessary to ensure adequate listening levels without clipping. The AS-1320 requires either the Heathkit ASA-1320-1 Passive Crossover (\$45), or the Heathkit AD-1702 Electronic Crossover (\$195). Subwoofer measures 64.5" H x 21.5" W x 17" D. A removable panel allows for future expansion to a full-range system. \$300.

CIRCLE NO. 90 ON FREE INFORMATION CARD

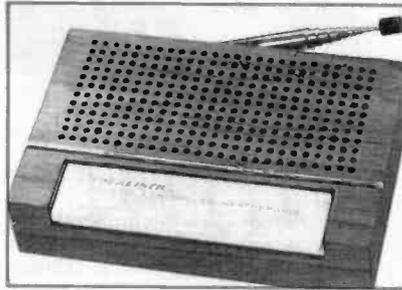a 9-volt battery or an optional ac adapter. With a maximum specified range of 50



miles, the receiver is said to be effective anywhere in the United States. \$24.95.

CIRCLE NO. 91 ON FREE INFORMATION CARD

Audio Cassette Deck




The Model 814 cassette deck from Dual features a Direct Lock and Load system that eliminates the usual door between user and cassette. Also featured are me-

ters that respond to the signal after it has been equalized for recording. An electronic tape-motion sensor stops the transport if a cassette jams or spills. Bias/equalization settings are provided for ferric, ferrichrome, chrome, and metal tape types; and a fifth setting will sense the bias/eq automatically for precoded tapes. \$300.

CIRCLE NO. 92 ON FREE INFORMATION CARD

Linear Tracking Cartridge

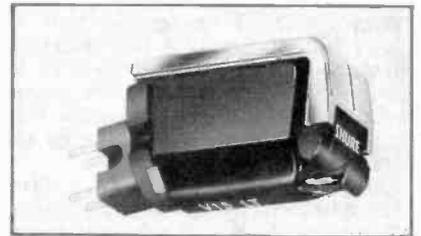

Shure has introduced a version of its V-15 Type IV cartridge designed to fit the Technics SL-Series linear-tracking turntables. The V15 LT has a hyperelliptical stylus and can be used with other linear-tracking or single-pivot tonearms via an adapter. Using a cantilever bearing independently optimized for low and high frequencies, the unit provides a frequency response that extends from 10 to 25,000 Hz, with a channel balance of \pm 2 dB. Output voltage is 4.0 mV per channel for 5 cm/s recorded velocity at 1 kHz; optimum load per channel is 47 k Ω (70 k Ω maximum) in parallel with 200 to 300 pF capacitance. Inductance is 500 mH; dc resistance, 1380 Ω . Net weight, 6 g. \$130.

CIRCLE NO. 93 ON FREE INFORMATION CARD

Portable TV with Built-in VCR



Technicolor Inc. has unveiled a television receiver that is integrated with a VCR.

Called "Video Showcase," the unit measures 18" x 13" x 8 1/2", weighs about 20 lb, and has a 7.7" color picture tube. The VCR uses 1/4" video tape in two-ounce cassettes that play/record for 45 minutes. Tapes can be recorded either with a Technicolor video camera (in the 1/4" format) or with a standard-format camera via an adapter. The VCR has a memory counter, slow-motion, freeze-frame, and sound-dubbing. Another adapter permits tapes in any format to be recorded on or from the Technicolor cassette. Operates from ac or car/boat battery systems. \$1725 with vhf/uhf tuner; \$1595 less tuner.

CIRCLE NO. 89 ON FREE INFORMATION CARD

Combination Pulse/Function Generator

Model 524 from Exact Electronics combines a pulse generator with a function generator in one enclosure. The function generator offers sine, square, and triangle waves with variable symmetry, trigger



Steal One

The Bone Fone was a big success at \$69.95. Can you imagine the success at \$49.95?

This photograph appeared in millions of pages of print promoting the Bone Fone at \$69.95. Will its new price cause a sellout?

It was a hit. The Bone Fone was one of our best-selling products when we introduced it in the fall of 1979.

And like all successful products, it soon made its way into retail stores too. Over 100,000 of the unusual stereo radios were sold and worn by joggers, sports spectators or just plain music lovers. But then the story of the Bone Fone took an unusual twist. But to understand the twist, you first have to understand the Bone Fone.

UNDERSTANDING THE THING

The Bone Fone is an AM/FM radio that drapes around your neck like a scarf. Special speakers, located near your ears, not only play the music but they also vibrate. The vibrations are picked up by your bones. The sound sensation will amaze you and continues to amaze the thousands who wear it today.

A lady in Helena, Montana who bought the unit for her son told us, "It's made a significant contribution to my sanity. No more rock n' roll blasting through the house. The sound goes where my son goes."

A jogger in Rowlett, Texas wrote us, "Amazing separation, fantastic stereo response helps my jogging tremendously. I wasn't really expecting this type of quality through a magazine ad at this price."

One of the most unexpected letters came from a man in Belle Center, Ohio. "You don't have to be young and jog to enjoy Bone Fone. You see, I'm 73 years old. I just sit and listen."

STORY TAKES TWIST

What made the Bone Fone particularly appealing was both its portability and the fact that it did not disturb those nearby. Even more important (and here's where our story takes the twist), it didn't require headphones.

With today's super lightweight headphones, you might think, "So what. Headphones are not a disadvantage." Bone Fone felt that headphones were indeed a disadvantage.

After awhile, headphones feel uncomfortable to the wearer. It's difficult to jog or do any strenuous outside activity with headphones. And finally and most importantly, they are to a

certain extent dangerous because they block out the sounds around you—some of which could be warning you of danger.

PERFECTLY SAFE

With the Bone Fone, not only can you hear beautiful music, but you can hear a car turning a corner or a person shouting. Earphones isolate you from the world around you.

Soon the earphone cassette players started to multiply like rabbits. Prices started to drop, plunging all the way to \$69.95 and putting tremendous pressure on the relatively new Bone Fone stereo.

But the death blow really came when the super small headphones went into major production and manufacturers in Hong Kong started producing a headphone AM/FM radio to sell for only \$49.95. Now the pressure was really on Bone Fone. Sales slowed and the competition was being felt. Where to now?

BIG PROBLEMS APPEAR

Bone Fone Corporation couldn't afford to drop its price. The Bone Fone is built like an expensive AM/FM stereo receiver. It also has an inner sleeve to protect its electronics from moisture and a blue Lycra outer sleeve to give it its distinctive appearance. Bone Fone Corporation was stuck. They couldn't lower their price, and the public was not buying the Bone Fone at \$69.95. Enter JS&A.

JS&A made a large purchase directly from Bone Fone Corporation and can still sell the product to the consumer at the lowest possible price while still making a small but reasonable profit.

In fact, the important role that mail order companies can indeed play is clear from this example. JS&A took most of the current inventory of Bone Fones, and we're ready to offer them at the low price of \$49.95.

TRY IT FOR 30 DAYS

Order a Bone Fone stereo by sending in your check or charging it on your credit card account. When you receive it, try it out. Put it over your shoulders. See how light it feels and how incredible the music sounds. Attach it to your body with its strap. Jog, walk your dog, or

even just plain relax and listen to good music.

Then decide within 30 days if you want to keep it. If you do, you'll own one of the finest ideas in AM/FM stereo radios since the radio became portable. If not, no problem. Return your unit and we'll send you a prompt and courteous refund plus your \$3.00 for postage and handling.

Your unit comes complete with straps for wearing while you jog or run, complete instructions and a 90-day limited warranty. Service should never be required but if it is, Bone Fone and JS&A maintain their own service organization. JS&A is America's premiere electronics mail order company and a champion against the bureaucratic forces of the FTC.

To order, simply send your check for \$49.95 plus \$3.00 for postage and handling per shipment (Illinois residents add 6% sales tax). That's right—no matter how many Bone Fones you order, the cost for postage and handling is only \$3.00. So order enough of them while our supply of units lasts. (We have plenty, so don't worry.) We'll send your Bone Fones complete with batteries, instructions and 90-day limited warranty.

Thanks to the efficiencies of mail order and Bone Fone's problems, JS&A is once again offering a great product at a great new value. Order your genuine Bone Fone stereo at no obligation, today.

JS&A PRODUCTS
THAT THINK®

Dept. PE One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-7000
Call TOLL-FREE 800 228-5000
In Nebraska Call 800 323-6400

©JS&A Group, Inc., 1981


and gate operation, and output levels up to 30 V P-P. Operating from 0.001 Hz to 20 MHz attenuated in 80-dB steps, the frequency/period dial has 10-turn and 3-decade single-turn modes. Also included are variable dc offset, voltage-controlled



frequency input, and sync output. A separate pulse-generator section provides single, double, and delayed pulses over a frequency range from 0.001 Hz to 50 MHz. The period can be adjusted from 20 ns to 1000 s. Pulse width and delay are adjustable from 10 ns to 10 ms. Simultaneous outputs from five connectors give TTL, TTL, ECL, ECL as well as pulse output from the main amplifier. Pulse baseline is set from zero to ± 15 V, with 80 dB of attenuation provided in 10-dB steps. Pulse rise and fall times are rated: 2 ns at the ECL outputs, 7 ns at the TTL outputs, 15 ns or less at the main output. \$1195.

CIRCLE NO. 94 ON FREE INFORMATION CARD

Video Pollution Control

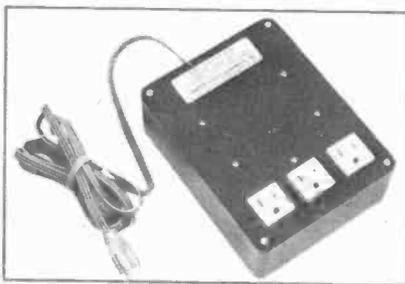

Electronics Specialists has announced a device said to eliminate the video flashes and picture jitter associated with noise

Portable FM Stereo Radio




Weighing less than 1 lb, the Model 7-1000 is General Electric's entry into the portable FM stereo market (it also plays AM). Features include vernier tuning, left and right channel controls, a LED FM stereo indicator, and built-in afc. The headphone cord serves as the antenna, and there is an additional headphone jack. A ferrite magnet with a rated impedance of 32 ohms drives the headphone speakers. Headphone weight is 2 oz. The 7-1000 operates on 3 AA batteries, or on ac with an optional 4.5-V converter. Dimensions are $4\frac{1}{2}''$ H \times $3\frac{1}{4}''$ W \times $1\frac{1}{4}''$ D. \$74.95.

CIRCLE NO. 97 ON FREE INFORMATION CARD

and spikes from power lines, heavy machinery, and lightning. Called the Super Isolator (Model ISO-3), the unit offers 3 dual-balanced pi-filtered ac sockets. Each socket individually handles up to 1 kW. Total capacity is 1875 W. \$94.95. Address: Electronic Specialists, Inc., 171 S. Main St., Natick, MA 01760.

CIRCLE NO. 96 ON FREE INFORMATION CARD

Voice Recognition System

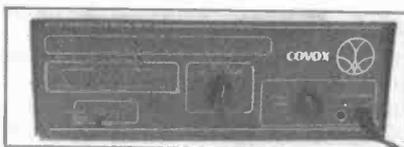

The Covox Model I voice controller is said to be capable of recognizing the spoken phrases, "di", "dah", and long "dah" when voiced in Morse, Binary, or RTTY code. The system, it is claimed, can pick out a human voice in extraneous noise ten times louder than the voice itself. Not a complete speech recognizer, the Model I can be programmed to recognize 16 Morse-encoded words in its stand-alone mode, or can interface with one or more

Sonic Localizer



A signal processor said to improve stereo imaging has been introduced by Phase Linear. The Model 180 Dimensional Sonic Localizer (DSL) is designed for either headphones or loudspeakers, connecting to a preamp or receiver via the tape-monitor loop. The DSL can also operate on a mono signal, producing a synthetic stereo effect. Without the time-delay circuit, THD at 0.5-V output (20 to 20,000 Hz) is 0.009%; IM is 0.004%. Other specifications: S/N, 83 dB up to 0.5-V output; input level, 150 mV rms; input impedance, 20 k Ω ; maximum output voltage, 10 V rms into 10 k Ω . \$149.95.

CIRCLE NO. 98 ON FREE INFORMATION CARD

4 1/2-Digit Hand-Held DMM

Data Precision's new Model 945 is a portable 4 1/2-digit LCD multimeter. It measures dc and ac voltages up to 1000 V dc



and 700 V ac in 5 ranges, both with a resolution of 10 μ V. Resistance, in 6 ranges, is measured from 200 Ω , with 10-M Ω resolution, to 20 M Ω . Five ranges of dc and ac current are measured from 10 nA to 2 A. Basic resistance-measuring accuracy is said to be 0.08%; the claim for dc measurement is 0.015% basic accuracy, while ac is said to be accurate to 0.5%. The Model 945 offers a constant-current source for resistance measurements, permitting a direct display of voltage drop across a load. Powered by a 9-volt battery, the unit weighs 13 oz. \$265.

CIRCLE NO. 95 ON FREE INFORMATION CARD

Lexan-Shell Audio Cassettes

The Loranger Manufacturing Co. has entered the consumer audio cassette tape market with chrome and ferric-oxide formulations packaged in Lexan shells. Marketed under the name, Loran, cost is reported to be \$1 to \$2 higher than current top-of-the-line cassettes. Frequency response for the high-bias tape is given as -11.5 dB at 15.5 Hz and a 0-dB recording level. Without Dolby, dynamic range is 62 dB (S/N 56 dB); with a sensitivity of ± 0.5 dB.

CIRCLE NO. 99 ON FREE INFORMATION CARD



Fresh Air Bubble

Surround your body or your work place with ion-controlled fresh air in America's first bipolar electrostatic home precipitator.

The unit measures only 2" x 4" x 7" and its black appearance will fit into most decor.

There's a danger. And this invisible menace will affect nearly everybody reading this ad.

The danger is pollution—but not the ordinary kind. In fact, ten years ago, we didn't have this new kind of pollution. Let us explain.

Ten years ago, cars didn't have catalytic converters. Today, these catalytic converters "grind up" the car exhaust into particles so small they form micron soot, and micron soot is so fine, it can be easily absorbed into your lungs. Even the EPA has stated, "Because it is so fine, such soot particles stay longer and cause more damage in the respiratory tract."

Ten years ago, homes were able to "breathe" or exchange air between the outdoors and indoors four or five times a day. Today, with our well-insulated energy-conscious buildings our homes literally create and trap pollution that we breathe unwittingly.

OTHER PROBLEMS

There are other problems too. Add the daily soot, dust, smoke and other impurities in the air and you've created pollution problems even worse than they were ten years ago—so bad in fact that environmental groups are especially concerned over this new "time bomb" lurking in our environment.

But American ingenuity hasn't been sitting still. A rash of small devices containing charcoal filters with fans and selling for around \$30 have literally flooded the market. The problem is that these devices only remove particles 5 microns or larger. Today's micron soot is one micron or smaller. Cigarette smoke for example is 2 to 3 microns or smaller.

70,000 UNITS SOLD

In 1978, JS&A introduced the negative ion generator in a national advertising campaign and sold over 70,000 units. It was a device that cleaned the air by electrostatically removing particles even smaller than one micron. Hospital burn centers soon began using commercial versions of the negative ion generator.

Removing sub micron particles from the air was very important, but there was also a surprising second benefit. The unit added negatively charged ions to the air.

We've all felt the effects of negative ions after a thunderstorm. When you take a deep breath, the air smells good and you feel good.


The opposite is true of positive ions which

can be found in polluted environments, air conditioned office buildings and in automobiles. Many scientists believe that positive ions make you feel moody, depressed, irritable and restless. A negative ion generator cancels out the positive ions and fills the air with negative ions.

AN EXPERIMENT

When you blow smoke into an inverted glass bowl and put it over an ion generator, the smoke immediately vanishes. Or if you place the ion generator in an odor-filled room, the room soon smells fresh.

It was these experiments that really convinced the public that the JS&A ion generator was a valuable new home appliance. Soon the market was flooded with competitive ion generators. Many were not as efficient as JS&A's first model. Some emitted very few ions and one actually emitted dangerous levels of ozone. JS&A conducted independent laboratory tests and publicized the results which showed that JS&A's unit was indeed the best.

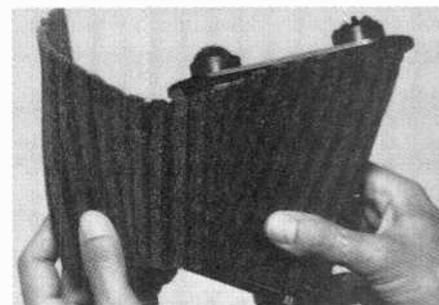

You can easily remove and wash or simply replace the ion filter after it collects the soot. Extra filters are only \$1.00 each and should be replaced or washed once every two months.

That's the history. But like any new technology, there's sure to be improvements. The first ion generator produced negatively charged ions which attached themselves to the pollutants and then fell to the ground. You ended up with clean, fresh air but also dirty rugs and walls.

In winter, the units created electrostatic discharges which can be uncomfortable when touching a door knob or someone else.

CONTROLLED ION ENVIRONMENT

So American scientists created an ion generator using a bipolar emitter which emits a

balanced amount of negative ions to create a controlled ion environment. One emitter produces negative ions and the other controls and shapes those ions to create an ion bubble.

The end result is a unit which leaves just the right amount of negative ions in a large room, attracts the pollution particles and deposits them on a washable collector plate while keeping your floors and walls free of dirt. You're actually placed in a fresh air bubble while you work, sleep or relax and with no uncomfortable electrostatic charge.

I urge you to try the JS&A ion generator in your home or office for 30 days. Put one on your desk or in any smoke-filled room. Notice the refreshing difference in your work environment. Take it home and plug it in next to your bed. Chances are, you'll want to buy another one before our 30-day trial period ends.

SATISFACTION GUARANTEED

But if you are not pleased with your unit for any reason whatsoever, please return it within 30 days and we'll send you a prompt and courteous refund including your \$4.00 postage and handling. JS&A is America's premiere electronics company—a substantial organization that guarantees your satisfaction.

To order, send your check for \$89.95 plus \$4.00 postage and handling (Illinois residents please add 6% sales tax) or credit card buyers may call our toll-free service line below.

We'll send you the JS&A ion generator complete with instructions and a 90-day limited warranty. Then plug it in and leave it run all day and night. The cost to run the unit is only a few cents per day.

The era of the ion generator as a standard household appliance is here. Order the newest and best unit available at no obligation, today.

JS&A PRODUCTS
THAT
THINK®

Dept. PE One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-7000
Call TOLL-FREE 800 228-5000
In Nebraska Call 800 323-6400

©JS&A Group, Inc., 1981

"RATED NO.1 FOR SERVICE & RELIABILITY"
**THIS MONTH'S
 SUPER SPECIALS!**

VIDEO and AUDIO

HOME VIDEO RECORDERS

G.E. VC-1012 VHS Recorder.....	1799
HITACHI VI-8500 VHS Recorder.....	1895
JVC HR-8700 VHS Recorder.....	1799
MAGNAVOX 8310 VHS Recorder.....	1625
PANASONIC PV-1300 VHS Rec.....	1795
PANASONIC PV-1750 VHS Rec.....	1640
Quasar VR-5015 VHS Recorder.....	1595
RCA VET-290 VHS Recorder.....	1750
RCA VET-650 VHS Recorder.....	1895
SANYO VCR-5000 Beta Recorder.....	1725
SONY SL-8000 Beta Recorder.....	1775
SONY SL-8600 Beta Recorder.....	1825
ZENITH VR-9000 Beta Recorder.....	1695

ARCHIVERS

TECHNICS SA-103.....	144.90
TECHNICS SA-203.....	179.90
SANSUI 3702.....	299.90
MARANTZ SR-7100.....	264.90
PIONEER SR-5.....	264.90
SONY STRVX4.....	264.90

PORTABLE VIDEO RECORDERS

AKAI VPS-7350 VHS w/finder.....	11295
JVC HR-2200 VHS w/finder.....	9975
PANASONIC PV-3100 VHS Rec.....	1295
PANASONIC PV-A33P (finder/finder).....	1295
PANASONIC PV-2000 VHS w/finder.....	1875
SONY TR-3000 Beta Recorder.....	1229

VIDEO CAMERAS

HITACHI VCR-8000 Auto Focus.....	1975
JVC GX-88 Camera.....	1695
PANASONIC PK-800 Camera.....	1595
SONY HVC-2200 Camera.....	1985
SONY HC-1850AF Auto Focus.....	1849

VIDEO DISC PLAYERS

MAGNAVOX VH-8000 Laserdisc.....	1599
PIONEER VP-1000 Laserdisc.....	1599
RCA SPT-100 CED Disc Player.....	1399

SONY COLOR TV

KV-1207 (12' Screen).....	1349
KV-1415 (15' Screen).....	1435
KV-1913 (19' Screen).....	1435
KV-1965 (19' Remote).....	1561
KV-2458S (26' Remote).....	1775

*NOTE ALL COLOR TELEVISIONS SHIPPED FREIGHT COLLECT ONLY!

CAR STEREO

PIONEER CASSETTE DECK w/ RADIO

KP-8500.....	124.90
KP-8500.....	141.90
KE-2100.....	174.90
KE-220.....	214.90
KP-4502 (Foreign Cars).....	144.90
KP-8000.....	139.90
KP-9000 (Reg Amp).....	154.90
KP-9500 (Reg Amp).....	174.90
KE-1100.....	209.90

SANYO UP-DARK CASSETTE

FI-C2 (Mini Cassette).....	59.90
FI-C8 (Mini Cassette).....	99.90
FI-C12 (Digital Display).....	114.90
FI-C14 (Cass & Metal Tape).....	147.90
FI-C18 (Digital Tuning).....	164.90

CLARION

PE-483A (w/ Fast Forward).....	79.95
MESUR MP150 Rec. w/ Dolby.....	169.95
PE-751C (Auto Rev).....	224.95
PE-958A (Electronic Tuning).....	289.95
PE-958B (Electronic Tuning).....	179.95
PE-958C (Rec. Tap Or Line).....	109.95
PE-958D (Rec. Tap Or Line).....	109.95

BLAUPUNKT

CR-2010.....	259.90
CR-100.....	124.90
CR-4000.....	259.90
CR-500.....	339.90

MITSUBISHI

MITSUBISHI RX-73 Receiver.....	174.90
MITSUBISHI RX-73 Receiver.....	199.90
MITSUBISHI RX-73 Receiver.....	124.90
MITSUBISHI C2747 (Reg Amp).....	324.90
MITSUBISHI CV-23 (Eq Amp).....	124.90
MITSUBISHI CV-25 (Eq Amp).....	124.90
MITSUBISHI 50-10 (4).....	29.90
MITSUBISHI 50-40CA Coax (4x1).....	64.90
MITSUBISHI 5049TA Trax (4x1).....	69.90

SONY

XR-77 FM/AM CASSETTE*	
XR-70 PREAMP FM/AM CASSETTE*	
XR-60 AMP/1.60 WATTS*	
XR-9 BAND EQUALIZER*	

CONCORD

HPL-101 RECEIVER*	
HPL-112 RECEIVER*	
HPL-120 DIGITAL RECEIVER*	
HPL-305 AMP/RECORD*	
HPL-50 AMP/EQUAL*	

CONCORD AND SONY PRICES TOO LOW TO ADVERTISE PLEASE CALL FOR ADDITIONAL MODEL NUMBERS & PRICES

CAR ACCESSORIES

FOX XK Radar Detector.....	99.50
FOX Visor.....	224.90
FOX Remote.....	109.50
FOX Superfox.....	229.90

FUZZBUSTER (Superfox).....	224.90
FUZZBUSTER I.....	119.90
FUZZBUSTER III.....	109.90
BELL 819 (Superfox).....	184.95

HARADA ANTENNAS ARE AVAILABLE PLEASE CALL FOR MODEL NO. & PRICE QUOTES

BLANK CASSETTES

AUDIO

AMPEX Grand Master I or I C90.....	2.99
BAFF Pro I or C90.....	2.99
FUJI FX I or C90.....	2.99
SCOTCH Highmaster C90 3 Pk.....	3.99
SCOTCH Master I C90.....	3.25
SCOTCH Master II C90 (2 Pk).....	4.49
MEMORISE/HiMag C90.....	2.99
SONY SFC C90.....	3.49
SONY FECP C90.....	3.99
SONY LNS C90.....	1.59
TDK D50 Demagnetizer.....	1.59
TDK DC90.....	1.48
TDK AC90.....	2.45
TDK SC90.....	2.45
TDK MA C90 (Metal).....	6.29
TDK MA C90 (Metal).....	6.29
MAXELL UD1L1 or UD1L R C-90.....	2.49
MAXELL UD1L1 or UD1L R C-90.....	3.29
MAXELL UD C-90.....	1.59
MAXELL UD 35.00.....	5.99
MAXELL WDM-110.....	6.75
MAXELL Cass Demag HE-44.....	6.75

VIDEO

WE CARRY VIDEO TAPES BY: AMPEX, BASF, FUJI, JVC, MAXELL, PANASONIC, MEMorex, TDK, SCOTCH, SONY & RCA.	
ALL BETA L-500.....	11.95
ALL BETA L-750.....	12.95
ALL VHS T-120 (Except HG).....	14.95
MATTEL Intellivision Game.....	279.50
ATARI Video Game CG-2600.....	148.95

SPECIALS

AMPEX T-120-13.95 AMPEX L-500-9.95	
FUJI T-120.....	13.95
SCOTCH T-120 50 Rebate.....	14.95
MAXELL N61-120.....	17.95

WE STOCK B&W & COLOR TV'S, VHS AND BETA VIDEO RECORDERS, AND HOME MOVIES FROM ALL THE MAJOR HOLLYWOOD STUDIOS. SEND FOR FREE CATALOG.

MINIMUM ORDER 12 TAPES 100% GUARANTEED

WE STOCK ALL VIDEO DISC TITLES. CALL OR WRITE FOR A LIST OF PRICES.

HOW TO ORDER BY MAIL: For prompt and courteous shipment, send money order, certified check, cashier's check, MasterCard/Visa (include card number, expiration date and signature). DO NOT SEND CASH Personal and Business checks must clear our bank before processing. Shipping and insurance charge 4% of total order with orders. New York State residents must add 4% sales tax. ALL MERCHANDISE IS BRAND NEW, FACTORY FRESH AND 100% GUARANTEED.

ORDER TOLL FREE: (800)221-8180 or (800)221-8830

NEW YORK CALL: (212) 732-6600

SEND FOR FREE 260 PAGE AUDIO/VIDEO CATALOG

DEPT. PE

23 PARK ROW, NEW YORK, N.Y. 10038

CIRCLE NO. 44 ON FREE INFORMATION CARD

ENTERTAINMENT ELECTRONICS

By Ivan Berger

Video Accessories from the Camera Store

A CAMERA is a camera is a camera. And, therefore, many of the accessories sold at camera stores are useful for video as for photography.

Take tripods. There are some special video models (for example, those combined with video equipment carts); but, for the most part, any good photo (or, better, movie) tripod will provide steadier video pictures. What makes a tripod good? A lot of factors, some of them mutually contradictory. As a case in point, heavy tripods are more stable, but light ones are easier to carry. For video or movie use, the tripod should have a "pan" head, with separate pan (rotate) and tilt adjustments and a handle that extends far enough back to be accessible when your camera is mounted. (Don't use a tripod with a ball-joint head.) It's easier to adjust camera height if your tripod has an adjustable center "elevator" section than if you have to adjust all three legs; but use the legs to get as close as possible to the desired height, so you can minimize elevator extension. That way, the camera has a steadier support.

Make sure, also, that the tripod can stand high enough to put the camera's finder at your eye-level; bending over for a long while is tough on your back. (Most cameras with electronic viewfinders let you aim the finder up, so you can look comfortably down into it when it's at a low angle.)

There are small tripods, too, for low-angle use or for use on table-tops and the like. Most of these are a bit flimsy, but Leica makes a good (and expensive) one, with heavy, cast legs that rotate around the central camera mounting screw to nest flat for carrying. A similar model, sold in Japan by Stutz, is available under some other brand names here. Bolex makes a weirdly jointed camera stand that looks like a praying mantis when unfolded for use; it can be folded to fit a broad variety of situations, and to give a broad enough base to support most home video cameras.

Camera stores sometimes carry shoulder pods or "gunstocks" (most of which look nothing like guns) that can be adjusted to fit most still, cine or video cameras. Since personal fit and comfort are factors here, it pays either to bring your video camera to the store for a fitting or to buy the shoulder pod on a money-back guarantee basis.

work on video cameras. There are attachments for straight and fancy color filtering, for fancy optical effects, for closeups, and to change your lens's focal length.

In video, filters are mainly for special effects. Most cameras have some kind of color balance control, which should at least eliminate the need for conversion filters to match day or indoor light. To get weird colors for special effects, you might be able to use the same controls (it depends on the camera). But you'd be better off with filters, since they give deeper hues and a wider choice of colors, and spare you recalibration of the camera settings when you want things to look normal again.

Filters made for color photography primarily give the effect of changing the color of the light. Though you won't usually need indoor/day conversion filters, you may want to try "FL-D" or "FL-B" filters to reduce the excess green of fluorescent light, mild color-warming filters to take the "chill" off a



Medium-duty tripods such as the Slik M410 provide a steady base for your camera. (The head shown here is actually for a 35-mm camera.)

Filters. Most of the attachments made to fit in front of film camera lenses also

The new Bone Fone appealed to all ages, but not at \$39.95.



Colossal Failure

*The Bone Fone was a great success,
but its little brother laid a big bomb.*

It really flopped. And it was such a flop that we were totally unprepared for it. Here's what happened.

The story actually started out with a product called the Bone Fone, an AM/FM stereo radio that draped around your neck like a scarf. The Bone Fone played stereo music that you actually felt through your bones as well as through your ears. The beautiful effect was hard to describe.

JS&A's earlier advertisements sold the Bone Fone quite well. Soon over 100,000 of them were draped around the necks of music lovers all over the nation and JS&A had a hit. But wait. Our luck was soon to run out.

The AM/FM stereo Bone Fone sold for \$69.95 so it would seem logical that a less expensive unit at \$39.95 that played only AM stations would be a natural winner too. After all, the two speakers on the less expensive Bone Fone were sure to make any AM station sound almost like stereo. Logical, yes, but then some very confident people went a little overboard.

Our ad manager went overboard with a brilliant name for the product—NUTS—the radio for music nuts, sports nuts, news nuts or anybody just nuts enough to wear the thing.

And our product designers went overboard too. Instead of a basic AM radio, they built a unit that was vastly superior to any pocket radio, in fact equal or better than many AM/FM radios. There was an integrated circuit, and a pair of large 3" speakers with big magnets that could really blast out with solid AM music. Remember, the AM unit was not stereo but it seemed that way with its two large speakers.

The sound was so good that even the engineers went overboard adding a tone control and boosting the power the speakers

could take from 0.2 watts to 0.5 watts—all powered by a 6-volt battery system instead of the traditional 3-volt system. Indeed, the unit was built like something the military would design and all put together by one of the best factories in Hong Kong.

Even our purchasing department went bananas and ordered 30,000 of the monsters without testing to see if the product would sell.

Well, if you're sensing that we're about to tell you about a mistake, a gross miscalculation, or even a major disaster, you're right. When we tested the product to see if it would sell, we found out it couldn't. Consumers were buying the stereo Bone Fone at \$69.95 ten to one over the \$39.95 NUTS.

The ad agency was shocked, the product designers and engineers were perplexed, and our purchasing agent was worried. We ended up with 29,940 in stock.

What do you do when everybody goofs? Simple. You lower the price. But from experience we know that even at \$29.95 we're not going to sell out even if we triple our sales. The price had to be dramatic. A real shock. The price had to be so low that a sell-out would be assured. "O.K., \$24.95," said our executive vice president. But she was vetoed. "\$19.95," announced our president. And so it was.

If you realized the value that NUTS represents at \$19.95, you'd buy all you could for gifts this Christmas even though it's months away. But we're sorry, there's a limit: 144 per person or 967 per family. You see, we're anxious to dump the little buggers.

The NUTS comes with a terry cloth sleeve that fits over the unit to make it comfortable to wear for jogging or just plain walking. Take NUTS with you to a sporting event and hear the play by play while still experiencing the

sound of the crowd. A strap firmly secures the NUTS to your body so you can jog or do any physical exercise while the unit stays secure.

If the sleeve gets dirty, don't worry. Just throw it in the washing machine and wash it like a towel. Don't forget, of course, to first remove the radio.

NUTS comes with a 90-day limited warranty but it's built like a battleship so nothing should ever go wrong. But ah, if it does, simply send it to our service-by-mail facility and we'll quickly repair it and have it back pronto.

JS&A is famous for its space-age products since 1971 and its FTC battle since 1979. We're a responsible company that built our reputation on providing service to our customers and fighting off federal bureaucrats.

To order, simply send your check for **\$19.95** plus \$3.00 per order for postage and handling (Illinois residents add 6% sales tax) to the address below or, credit card buyers may call our toll-free order service below. We'll send you your unit complete with instructions and a 90-day limited warranty backed by JS&A's service-by-mail center. (Four AA cell batteries not included.)

If you've ever had a great opportunity to buy a truly great bargain, it's now. But like we said, once we're sold out, that's it. Only 29,940 left. Order yours at no obligation, today.

JS&A PRODUCTS
THAT
THINK®

Dept. PE One JS&A Plaza
Northbrook, Ill. 60062 (312) 564-7000
Call TOLL-FREE 800 228-5000
In Nebraska Call 800 323-6400
©JS&A Group, Inc., 1981

What's new with NRI's home-training program in communications electronics?

Almost everything!

NRI takes you to the edge of technology with state-of-the-art training on microprocessor-based communications equipment.

reflects the latest, state-of-the-art technology...includes up-to-the-minute equipment, experiments, and training techniques. And you learn it all at your convenience, in your own home in your spare time. NRI brings your training to you. No need for night school, classroom pressures, travel expenses, or strict schedules. You're a class of one, learning at your own pace by methods proven with 67 years of experience and over a million and a half other students.

Hands-On Training with Choice of Transceiver or Scanner

That's because NRI training is fully practical training. You not only get the "book learning," but also actual real-world experience through NRI Action Learning techniques. Your hands-on training is built around the advanced 2-meter transceiver that performs as a fixed or mobile station. Its micro-computer controls let you synthesize any frequency in its range, program full or four-channel scanning.

If you wish, you may choose to take your training with the Bearcat 210 scanner receiver. Also microprocessor based, it operates over five bands to give you automatic operation from 32 to 512 MHz.


New Action Audio "Talks" You Through Training

In addition to lessons, experiments, and reference manuals for this

NEW! programmable, microprocessor-based, synthesized five-band scanning monitor receiver



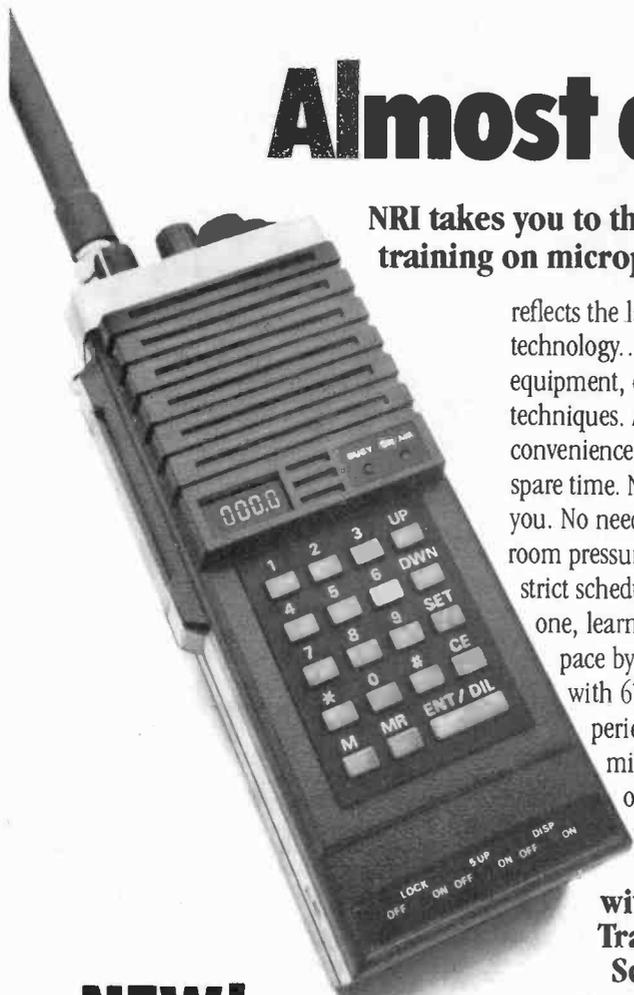high-tech equipment, exclusive NRI Action Audio cassettes reinforce your training. Your NRI instructor leads you step by step through each circuit, explaining




NEW!

hand-held, microprocessor-based 2-meter scanning transceiver

The remarkable world of communications is expanding in quantum leaps! Almost before you can absorb the last one, there's a new advance in technology, a new use for a new miracle of science. And NRI trains you to keep the pace.

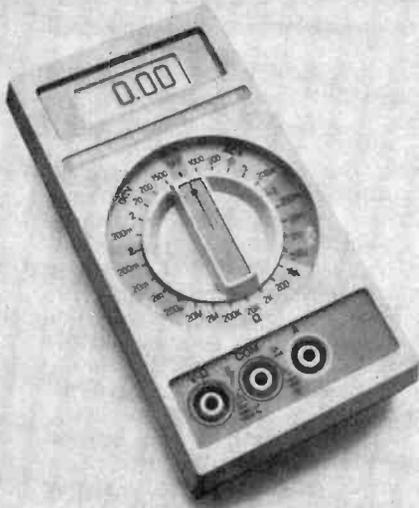Now, NRI's renowned home-study course in Communications Electronics



NEW! fully portable, six-function, 26-scale LCD digital multimeter

its function and interaction with others to make concepts crystal-clear.

Test Instruments Included

Your NRI Communications Electronics course also includes professional test instruments. Use them in the many experiments and demonstrations you perform, then keep them to use in your professional work. You get the Beckman Tech 300 hand-held LCD digital multimeter with six ranges and 26 scales to cover almost every IM-2400 measuring need you'll encounter. You also get the Heathkit UHF frequency counter, indispensable for both bench and field measurements of transmitter output frequency. Both instruments come with NRI Action Audio training backup.

At the heart of your experiment program is the NRI Discovery Lab and the famous NRI Antenna Applications Lab. Using them with your instruments and equipment, you'll perform over 80 separate projects to demonstrate and illuminate the new concepts you learn. Up-to-the-minute experiments cover bipolar and field effect transistors,

op amps, phototransistors, digital logic circuits and power supplies.

New Training in Satellite Communications, Microcomputers, and Digital Electronics

NRI lessons are kept up to date! Latest subjects include the booming field of satellite and data communications and telemetry. You also get training in the key field of microcomputers and digital controls, appearing on more and more communications equipment.

You're Trained in Every Field

Satellite communications is just one of the many fields covered by this complete communications program. You also learn how to install, service, and repair mobile radios; CBs; microwave antenna systems; aircraft and marine radio and navigational electronics; AM, FM and TV broadcast equipment; radar; just about any electronic communications equipment you'll ever run across. You're trained for the good-paying jobs in the secure, high-demand field of today's electronics professionals.

FCC License or Full Refund

NRI stands behind you all the way. Government regulations require

that the servicing of transmission equipment be performed by a technician holding a valid FCC Radio-telephone License. NRI promises that you'll pass your FCC exam and get your license *or your tuition will be refunded in full*. No ifs, ands, or buts ...this money-back agreement is good for a full six months after your graduation. That's how confident we are of the completeness and quality of NRI training.

Free Catalog, No Salesman Will Call


Find out all the facts on this exciting way to get into one of the

NEW! wide-range portable frequency counter with LED digital display



hottest opportunity fields around. Send the postage-paid card for your copy of our free catalog describing NRI Communications Electronics in detail. You'll get lesson plans, equipment specifications, and experiment descriptions plus information on other high-tech courses like Microcomputers, Digital Electronics, TV and Audio Servicing, etc. Send the card today and see what's new with NRI and new for you. If card has been removed, please write to us.

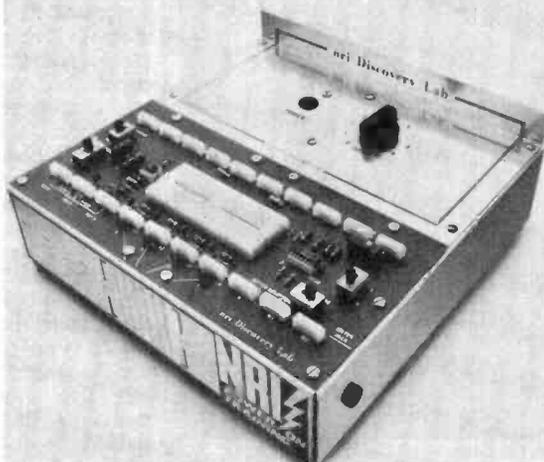NEW! the famous NRI Discovery Lab® now with advanced high technology experiments



NRI Schools
McGraw-Hill Continuing
Education Center
3939 Wisconsin Ave.
Washington, D.C. 20016

We'll give you tomorrow.

grey day, and bluish, "cooling" filters to make a sunny day look overcast or add moonlight effects to daylight shots. Filters made for black-and-white photography are generally of deep, solid colors such as red, blue, yellow, green and orange. Using them on a color camera will usually give bizarre effects, which may, at times, be just what you want.

Polarizing and neutral-density filters are the only ones made for both black-and-white and color film. Polarizers can be used to take the detail-reducing glare off shiny, nonmetallic objects, to shoot

through glass, and so on. They also deepen the blue in the part of the sky 90° from the sun. Although expensive, polarizers can often save the day. They're most useful with electronic-finder cameras, which let you check their effects, and a bit less so with through-the-lens finders, which show their effects somewhat less clearly.

Neutral-density filters are used when the light is too bright for even the smallest lens opening and lowest camera-sensitivity setting, and to let you use a wider lens opening in bright light. A wider

opening reduces depth of field, letting you throw distracting backgrounds out of focus.

Lenses. Some really creative special effects can be achieved with new lens-attachment systems from companies like Cokin (distributed by Minolta), Acme, Ambico, Tiffen and Spiratone though they become tiresome if over-used. These systems are based on holders that attach to your lens, plus a variety of square filters and accessories for many purposes. Available filters include: mist, fog and diffusion filters, color filters with clear centers, and filters that are half colored and half clear. (You could use the colored half to change the color of the sky while leaving the land unaffected, for example.) There are also filter-like attachments that create parallel or concentric multiple images and "vignettors" that frame your picture in a circle, heart, or other shape. Cokin, at least, has holders for lenses with front filter threads up to 82 mm, Spiratone to 77 mm.

Closeup lenses, which attach like filters, can be used to focus on objects closer than your lens's normal near-focusing limit, or into the gap that frequently exists between the far limit of a lens's macro-focusing range (if it has one) and the near limit of its normal focus range. These come in a variety of strengths, and can be stacked, so an assortment of +1, +2 and +3 lenses can be used in any combination up to +6. You'll probably not need more than about a +1, though, especially if your camera has a macro range. There are also split-field closeup lenses that allow you to focus very closely on one half of your image and all the way to infinity on the other half.

Here and there you'll run across wide-angle and telephoto converters designed to fit in front of your camera lens. They're not easy to find, though, especially in sizes to match large video zooms (JVC sells some that may fit competing cameras). Telephoto converters to fit behind the lens are common in still photography, but I know of none to fit the "C" mounts used by most video cameras. If you own a still camera with interchangeable lenses, you can get adapters to fit those lenses onto your C-mount video camera, for really long telephoto shots. (Video lenses rarely get much longer than 75 mm or so, while still camera lenses from 135 to 250 mm are common, and lenses up to 2000 mm are available.) Be sure to use a tripod, with any extreme telephoto lens. Telephotos magnify everything, including camera shake.

One of my favorite accessories is not for cameras but for portable VCRs. If you walk about with a portable hanging from your shoulder, Spiratone's "Postman's Pad" (\$6.95) will make that weight more tolerable than anything else I've tried. Unlike most shoulder pads, its thick, firm, and tapered to match the slope of average shoulders. ♦

THE FUTURE OF TELEVISION IS TODAY WITH DOWNLINK.

Why wait until 1985 just to get three channels of satellite reception when Downlink's D-2X receiver can give you sixty channels of brilliantly clear unedited movies, sporting events, world news and special programming from the many satellites over the North American continent... Now.

The D-2X's modular format and state-of-the-art circuitry allow for sharp, colorful reception of the entire satellite bandwidth (from 3.7-4.2 GHz).

So you can get all sixty channels *plus* the new channels that will be available in the future.

Made from the finest microwave components, the Downlink D-2X receiver features dual-conversion design, permitting multiple receiver installations and phase-lock loop processing which brings living color to your TV.

The complete and easy-to-install Downlink System including the D-2X receiver, low-noise amplifier, Skyview I antenna and cable can be yours for \$3,595.00. So live the future of television now... with Downlink.

For the name of the Downlink dealer nearest you call toll-free 800-641-4645, ext. 214. In Missouri, call 800-492-4892.




For more information, contact:
Downlink, Inc.
30 Park Street
Putnam, Connecticut 06260
(203) 928-7731

CIRCLE NO. 73 ON FREE INFORMATION CARD

Audio Product of the Month

CHOSEN BY THE EDITORS OF POPULAR ELECTRONICS

Bang & Olufsen Beogram 8000

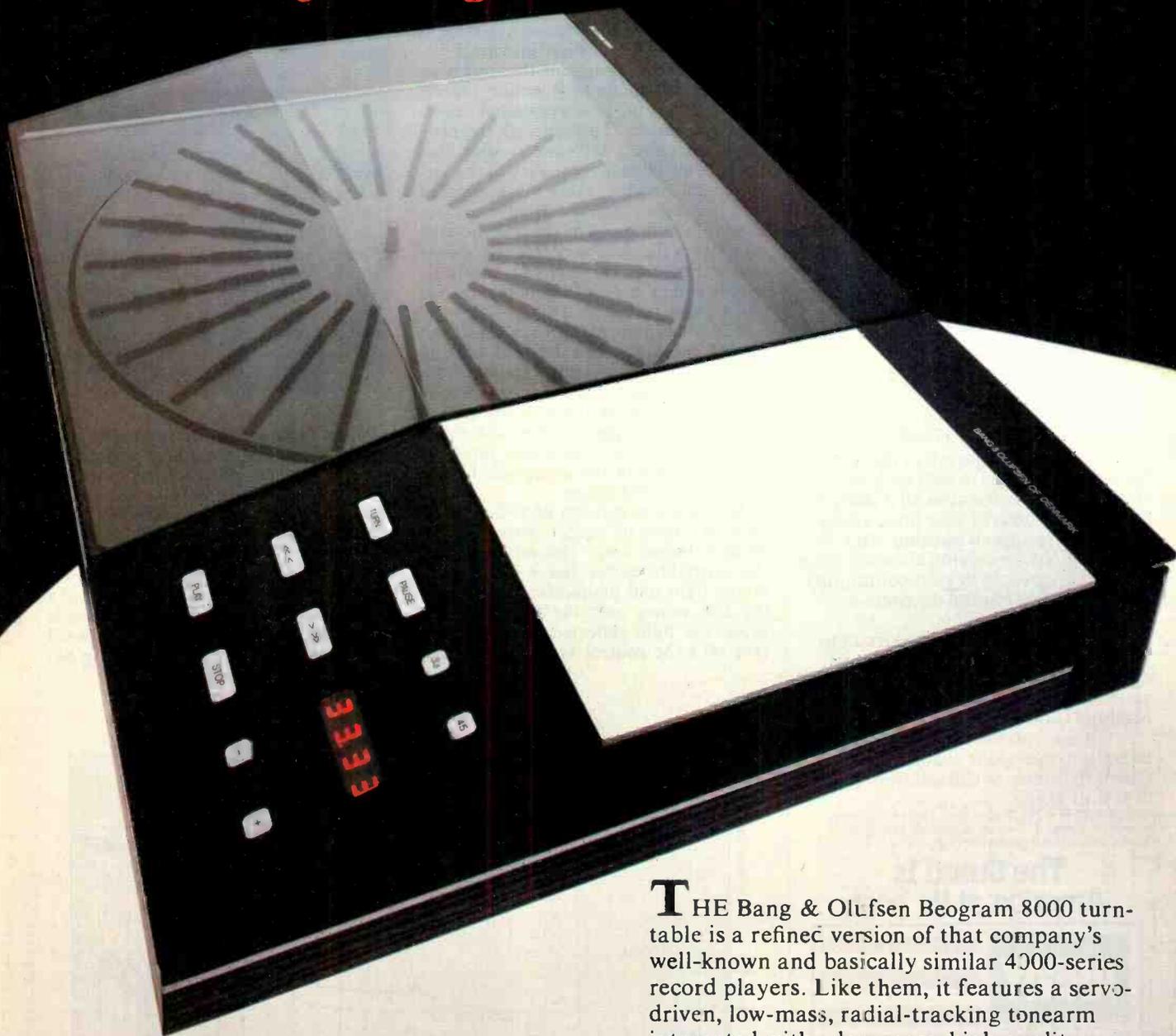

THE Bang & Olufsen Beogram 8000 turntable is a refined version of that company's well-known and basically similar 4000-series record players. Like them, it features a servo-driven, low-mass, radial-tracking tonearm integrated with a low-mass, high-quality magnetic cartridge, completely automatic operation, and foolproof stylus protection.

The B&O Model 8000 differs from its predecessors in that it has a novel direct-drive

GUARDING YOUR ★ MILITARY EXPERIENCE

EXTRA INCOME

If you have experience in any branch of the Armed Forces, you have the chance to earn good extra income while you hold one of the most important jobs in America. In an Army National Guard unit close to home.

Take income. In the Army National Guard, the work you've put into military service can really go to work for you. For instance, if you left as an E-4 with three years experience, you can earn over \$1500 a year. As an E-5 with 6 years experience, over \$1700. And, if you have a critical skill you may also qualify for a cash bonus. To see exactly how far your rank and experience can take you, check out the chart below.

	PER YEAR (Including Annual Training)
E-3 with 2+ years 3+ years	\$1375.68 1427.34
E-4 with 3+ years 4+ years	1519.92 1630.17
E-5 with 4+ years 6+ years	1687.11 1789.80

Plus, a part-time job in the Army National Guard fits in well with your current lifestyle. Because all it takes is two days a month of your time, along with 15 days annual training. And, in the Guard, you're serving close to home, helping the people in your community and state when natural disasters or emergencies occur.

Extra income that's important to you, in a job that's important to your community. It's just one reason to Guard your military experience in the Army National Guard.

To learn about other reasons—from benefits to new skills—contact your local Guard recruiter, or call toll-free 800-638-7600.

*In Hawaii: 737-5255; Puerto Rico: 723-4450; Virgin Islands (St. Croix): 773-6438; Maryland: 728-3388; in Alaska, consult local phone directory.

The Guard is
America at its best.



CIRCLE NO. 53 ON FREE INFORMATION CARD

motor (the 4000-series used belt drive) and a microprocessor control system. It measures about 19 1/4" W × 14 3/4" D × 3 1/2" H with its hinged clear plastic cover lowered and weighs about 20 pounds. It is finished in brushed aluminum and black, with rosewood grain trim. Suggested retail price is \$995.

General Description. The direct-drive motor of the B&O Model 8000 is described by the manufacturer as a "magnetic drive servo-controlled dc motor," with no elaboration. Examination of the motor, with the aluminum platter removed, reveals that the flanged rim of a smaller inner "platter" (the actual rotor) fits into a narrow gap between two large magnetic coil structures. There is no evidence of the complex windings used on many direct-drive motors.

Its appearance suggests that this is an eddy-current motor, not unlike the revolving disc in a conventional home watt-hour meter. Turning with the platter is an optical tachometer disc that supplies a feedback frequency to the servo control circuits, where it is compared to a frequency derived from a quartz crystal oscillator. The microprocessor establishes the necessary frequency division ratios for varying the turntable speeds within ±3% of the nominal 33 1/3 and 45 rpm.

The aluminum platter is a light disc (about 1/8" thick), and the total rotating mass is about 1 3/4 pounds. Instead of the usual rubber mat, the top of the platter has an array of 24 radial black plastic "spokes" that support the record above the metal surface. They also serve an important role in the automatic operation of the record player.

The tonearm consists of two straight parallel tubes of square cross section about 6 inches long. The one closest to the turntable center has a downward-facing light and photocell in its tip. As the arm moves over the rotating turntable, the light reflected from the surface tells the control system whether a

OPERATING CONTROLS:

(All pushbuttons)

TURN: Runs motor while depressed without initiating arm cycle. For use with record cleaning brushes, etc.

PAUSE: Raises arm for temporary interruption of play. After 10 seconds, arm returns to its rest and motor stops but lifting position is held in memory for 30 minutes and arm returns there automatically when PLAY is pressed.

PLAY: Initiates automatic play cycle. Record size and speed are set automatically.

STOP: Terminates playing and shuts off the unit.

33,45: Selects turntable speed for nonstandard records.


+ , - : Varies speed in discrete increments. (Actual speed is shown on a four-digit numerical display.)

<< < , > >> Fast arm movement (slew) controls. Arm lifts and moves slowly on light touch. More pressure speeds up slew speed.

Other Features: 7-pin DIN socket in rear for interface with Model 8000 receiver (for remote switching and control of record player). Stylus force-sliding adjustment on arm tube, calibrated from 0 to 2 grams at intervals of 0.1 gram.


record is present and what size it is. If no record is present, the spoke pattern interrupts the light reflected to the sensor, causing the arm to move to the center until a smaller diameter record (if present) is found, or to eventually return to its rest and shut off the unit. The pickup cannot descend to an empty platter.

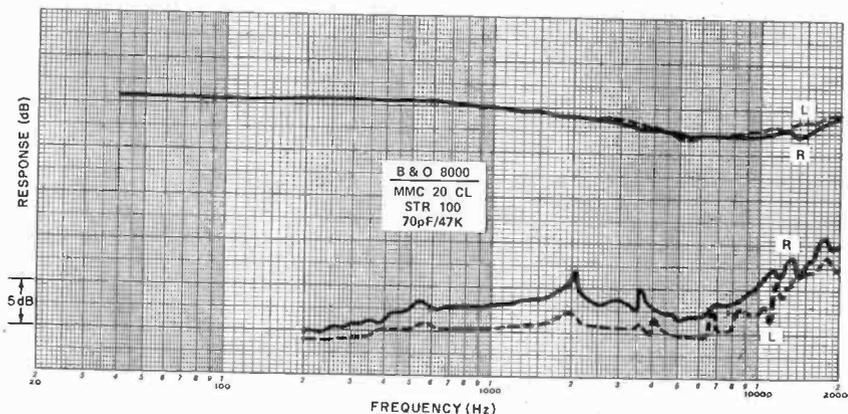When the sensor reaches the edge of a record and the reflected light pattern is interrupted, it continues to move inward by an amount equal to the spacing be-



Frequency response and channel separation of both channels using the CBS STR-100 test record.

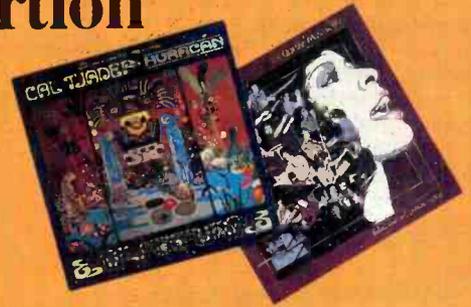When you're ready to "face" the music we have a tip for reduced distortion



Whether you are seeking to reproduce the full dynamic range in the grooves of today's new superdiscs, or simply to obtain maximum listening pleasure from treasured "oldies" in your record collection, you need a phono cartridge that will deliver optimum trackability with minimum distortion.

Because the phono cartridge is the only point of direct contact between the record and your entire stereo system, its role is critical to faithful sound re-creation. That's why upgrading your phono cartridge is the single most significant (and generally least costly) improvement you can make to your stereo system.

To that end Shure now offers the Hyperelliptical Stylus Tip configuration—first introduced on the critically acclaimed V15 Type IV—in a full line of cartridges with a broad range of prices.

The Hyperelliptical Stylus Tip has been called the most significant advance in decades in tip geometry. It has a narrower and more uniform elongated contact area that results in significantly reduced intermodulation and harmonic distortion.


Look over the list at left to see which Shure HE cartridge best matches your tracking force requirements.

Shure has been the top-selling cartridge manufacturer for the past 23 years. For full details on this remarkable line of cartridges write for AL667.

The HE Family: Hyperelliptical-Equipped



V15 Type IV
¾-1¼ grams

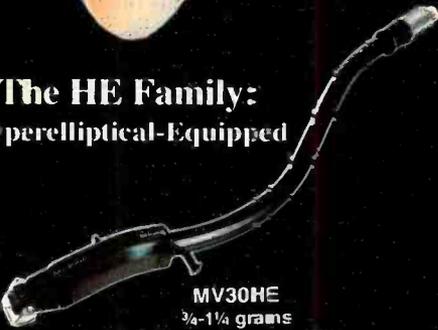

MV30HE
¾-1¼ grams



V15 LT
1¼ grams



V15 Type III-HE
¾-1¼ grams



M97HE
¾-1½ grams



M97HE-AH
(with attached headshell)
¾-1½ grams



M97 LT
1½ grams



M95HE
¾-1½ grams



M75HE Type 2
¾-1½ grams



M75HE-J Type 2
1¼-2½ grams

Go with the leader—Shure.



Shure Brothers Inc., 222 Hartrey Ave., Evanston, IL 60204
In Canada: A. C. Simmonds & Sons Limited
Manufacturers of high fidelity components, microphones,
sound systems and related circuitry.

tween the arm tubes (about 1 inch). Then it stops and lowers the second arm (containing the cartridge) to the record.

The platter always starts at 33 1/3 rpm, but if no record has been found outside of a 10-inch diameter, it automatically changes to 45 rpm. Either speed can be selected at any time by the pushbuttons, however. After the record has been played, the arm returns to its rest position and the motor shuts off. Each time the pickup enters or leaves its rest, the stylus is cleaned of lint by a soft brush.

The cartridge supplied with the Model 8000 is the B&O MMC20CL, the top-of-the-line model. It is a moving-iron cartridge with a single-crystal sapphire cantilever and a diamond stylus having an extended line-contact shape for improved tracing of high-frequency groove modulation. It is designed to track at 1 gram.

Like any other tangential-arm record player, the 8000 is free of skating forces and the need for compensation. As a result, its pickup goes straight up and down when the cueing mechanism is used, and returns to the same groove from which it was raised. The microprocessor of the Model 8000 "remembers" the position on the record from which the cartridge was raised by the PAUSE control and, up to 30 minutes later, can return it to the same spot. (The pickup remains over the record for only about 10 seconds before returning to its rest

position.) Another feature of the Model 8000 is its ability to repeat a record if the PLAY button is touched while it is playing (it finishes the play before repeating, however).

Laboratory Measurements. The B&O MMC20CL cartridge (also available separately with a mounting adapter for conventional arms) had a frequency response flat within +0, -3 dB from 40 to 20,000 Hz with the CBS STR 100 test record, and within +0, -3 dB from 1 to 30 kHz with the JVC 1005 test record (it was down 5 dB at 40 kHz on the latter). The response curve had a broad, shallow dip between 3 and 15 kHz. Channel separation was 20 to 25 dB over most of the audio range and about 15 dB at 50 kHz. The frequency response and crosstalk curves were nearly identical for both channels.

These measurements were made with a cartridge load of 47,000 ohms and 70 picofarads (plus the capacitance of the integral signal cables). Increasing the load capacitance to 440 picofarads had little effect on the frequency response (it actually improved by about 1 dB in the high-frequency range up to 20,000 Hz).

The low effective mass of the arm and cartridge resulted in a relatively high resonance frequency of 12 to 13 Hz, with an amplitude of about 6 dB, falling off to 3 dB at 20 Hz and becoming negligible at higher frequencies. Signal out-

put was about 2.9 millivolts at a 3.54 cm/s velocity. At the rated 1-gram force, the cartridge tracked our high-velocity test records easily, including the 70-micrometer level of the German Hi-Fi #2 test record. The vertical angle of the stylus was 24 degrees.

In subjective tracking tests with the Shure "Audio Obstacle Course" records, the MMC20CL was able to play the entire ERA III record. With the ERA IV record, we heard the beginning of mistracking on the highest level of most of the bands. This is a very severe test, and the cartridge should have no difficulty coping with the levels on almost any commercial record.

Turntable rumble was very low, reading -38 dB in an unweighted measurement and -61 dB with ARLI weighting. The rumble spectrum was mostly at 5 and 14 Hz, with smaller peaks at 40 and 60 Hz. Flutter was 0.05% wrms, and ±0.06% weighted peak (nearly as low as can be measured using test records). Its spectrum had peaks at 3, 10, and 14 Hz, dropping off at higher frequencies.

The turntable speeds were as exact as we could measure at the indicated nominal values, and could be varied over about ±3.3% in steps of either 0.05 or 0.07 rpm, depending on the speed. The automatic cycle times were shorter than on most automatic record players, with 4 seconds required to start playing after the PLAY button was touched, and 6 seconds for the shutdown after play. In the fast (slew) mode, a 12-inch record was covered in 4 seconds. The pause (lift, or cueing) action was perfect, with absolutely no lateral shift during the process, even when we waited for the memory system to take control. Although lift and descent were so rapid as to seem instantaneous, they were gentle and smooth.

In checking the suspension, we found a single transmission response at 30 Hz. The isolation of the Model 8000 was better than any turntable we have measured. Its margin of superiority was 10 to 20 dB over the better units, and 30 to 40 dB better than average.

User Comment. This is a deluxe record player for people who want to listen to records for enjoyment. Hardware-oriented hobbyists who want to change cartridges as new models become available will find the unit frustrating. Its totally integrated design makes such experimentation impossible. The turntable itself is one of the finest we have used; the arm and cartridge rank with the best on any objective basis; and the ergonomics of the entire record player are (in our view) a resounding success. In addition, this turntable is unmatched in immunity to acoustic feedback.

After using the Model 8000 for an extended period, we frankly do not have a single complaint about its performance. Even its high price seems quite reasonable, considering what it does and how well it does it.—*Julian D. Hirsch*

CIRCLE NO. 101 ON FREE INFORMATION CARD

wabash®



Quality, Service and Availability

You can count on all three from Wabash Tape Corporation. Our toll-free number will put you instantly in touch with your local Wabash Distributor . . . and the finest diskettes money can buy!

800-323-9868

Wabash Tape Corporation 2700 Des Plaines Rd., Des Plaines, IL 60018 • 312-298-8585

CIRCLE NO. 68 ON FREE INFORMATION CARD

We've got it all together.



Weller



Weller



Xcelite



Wiss



Nicholson



Boker

**Boker
Crescent
Lufkin
Nicholson
Plumb
Weller, Wiss
Xcelite**



Lufkin



Crescent



Plumb

Take a good look round this ad and you'll agree that "All together" is no exaggeration. Whether you're making or mending, cutting or joining, striking, measuring or stripping, there's a Cooper tool that's just right for the job. Don't take chances on tools. Specify Cooper and get 'em right the first time!

from Cooper The Toolmaker. ^{T.M.}



The Cooper Group

BOKER® CRESCENT® LUFKIN® NICHOLSON® PLUMB® WELLER® WISS® XCELITE®
P.O. Box 728, Apex, North Carolina 27502. Tel: (919) 362-7510 Telex: 57949Z


CIRCLE NO. 12 ON FREE INFORMATION CARD

NOW YOUR BETA MACHINE CAN PERFORM EVEN BETTER THAN WHEN YOU BOUGHT IT.

No matter how well your video cassette recorder has been performing, it's never lived up to its full potential. Because until recently, you couldn't buy High Grade video tape for Beta systems.

With Maxell High Grade Beta tape, you'll finally see what your machine can do. You'll get better color resolution, sharper images and clearer sound.

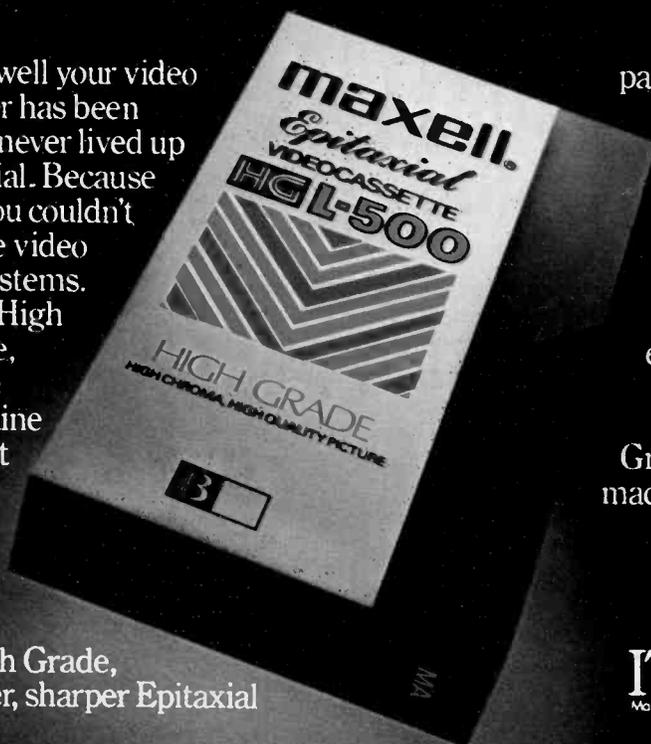To create High Grade, Maxell uses finer, sharper Epitaxial



particles and a unique binding process. The resulting tape not only produces a better picture than ordinary video tape, it's a lot more durable. This drastically reduces video recorder head wear and lets you enjoy a better picture longer.

So if you own a Beta recorder, try Maxell High Grade. You'll discover that the machine you own is even better than the one you bought.

maxell
IT'S WORTH IT.
Maxell Corporation, 60 Oxford Drive, Moonachie, N.J. 07074

CIRCLE NO. 48 ON FREE INFORMATION CARD

Popular Electronics Tests



Screen Picture by Discovision

The Sampo Model 9519 19" Color TV Receiver

THE Sampo Model 9519 is a 19" color receiver with two 5" black and white monitors nested alongside. Packaged in a mahogany veneer wood cabinet $25\frac{3}{4}''W \times 19\frac{1}{16}''D \times 22''H$, it has sensor touch tuning and a 4-inch oval speaker. The unit can be used with an infrared remote control, which has volume up/down, channel select, sound muting, and power on/off. Suggested retail price is \$995.

General Description. The block diagram (Fig. 1) of the main set shows a conventional 4-IC receiver with all luminance, power, outputs and sync functions performed by 28 discrete transistors and a bridge-rectifier diode power supply. The four ICs furnish i-f amplification, agc, automatic fine tuning (aft), FM detection, plus chroma processing and demodulation. A single SCR removes dc operating potential from the 120-V supply, should high voltage rise beyond normal levels. The main dc supply has a 4-transistor power regulator containing the usual sensor and feedback loop. It also offers an additional

transistor, shunted across the power driver and regulator, that will shut down the low-voltage supply if too much current is drawn.

Both auxiliary 5-inch monitors have similar power supplies and (because of their dual receiver/monitor functions) are isolated from the ac line. These medium-resolution monochrome sets are constructed of discrete transistors, three i-f stages, dual i-f/r-f agc adjustments, and varactor tuner elements with voltage U/V switching and broadband dc tuning. There are no audio outputs provided (Fig. 2).

In contrast to the main color set, which has 12-channel tuning, only two channels can be selected manually on the two monitor/receivers; or they can be used to receive a single direct-video input from a camera, video cassette or disc, or other baseband producer. Surprisingly, the auxiliary receivers process a full 4-MHz bandpass versus 3 MHz for the large screen color set. But, because there are no focus controls on the small sets and owing to limitations on tube resolution, the black and white

images aren't exceptionally sharp. Brightness and contrast, however, are adequate.

These minisets can be used with a monochrome surveillance camera and will reproduce a fairly accurate picture. A well-lighted and easily defined scene should be highly visible, but a dimly outlined area will produce a much poorer image. The VC-1001 camera recommended by Sampo for use with the 9519 retails for \$250 and has focus control only. Battery packs are \$75.

Baseband inputs to the monitors may range between 1 and 3+ volts, with negative-going sync. The monitors can be operated on baseband, independent of the main unit.

The tuning system is unusual. The touch of a finger induces a signal that (after its negative portion is clipped) forward biases an npn transistor. This, in turn, lights a sensor lamp and delivers a negative pulse to one end of the appropriate tuning potentiometer. Each individual tuning potentiometer is coupled to the 16-line inverter-buffer of Sensor Touch 1902, and manual bandswitch el-

ements for vhf and uhf selection. With its division ratio preset, the potentiometer delivers the appropriate voltage to the U/V tuners via an emitter follower.

With remote control, however, the scan/select voltages are generated by the infrared transmitter. The optically encoded signal is sensed by a photodiode in the IR receiver whose output is shaped and then routed to a remote-control encoder-decoder. This circuit performs the channel select and maintains the channel voltage in memory.

Remote-control sound is handled somewhat differently. Audio inputs combine through a volume step counter, a muting gate, and a separate volume control via an AND-switch within the processor. The output voltage is dc-controlled, resulting in a low that is inverted and routed to the base of the sound con-

troller. When the set is turned off (but still connected to house current), a memory function maintains volume level. Receiver tuning, however, always reverts to Ch. 1 (channel 2).

Analysis. Multiburst in Fig. 3 shows sloping low- to high-frequency outputs of up to 4 MHz at the single-diode video demodulator, but barely 3 MHz at the picture tube. In Fig. 4, 3.08-to-4.08-MHz chroma is apparent, and there is a very passable response in the lower swept chroma waveform at the picture tube. The vector, however, is somewhat jittery, and yellow-oranges are squeezed toward reds for easy fleshtones. The chroma pattern is not as distinct and symmetrical as it should be, including the jitter, which doesn't show in the final picture on the screen.

Figure 5 is taken from a multiburst through r-f to the picture tube from the No. 1 monitor, and at the camera input with baseband at monitor No. 2. Monitor No. 1 requires some i-f alignment to push the 3.58-MHz multiburst down, but the response is basically good. Camera input shows horizontal sync and blanking as well as some well-defined video modulation.

Comments. The idea of a multi-screen set with surveillance capability could appeal to homeowners and businessmen who are concerned about security. However, a focus potentiometer for the two black-and-white monitors would be a welcome addition to obtain more distinct viewing.

The touch-tuning response is slow, unless you generate a lot of static elec-

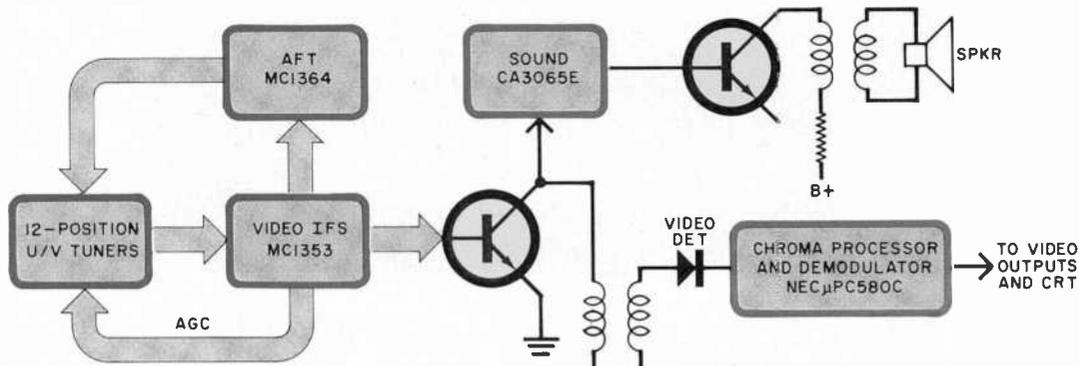


Fig. 1. Simplified block diagram of the main color chassis. Functions are performed by four ICs and 28 discrete transistors.


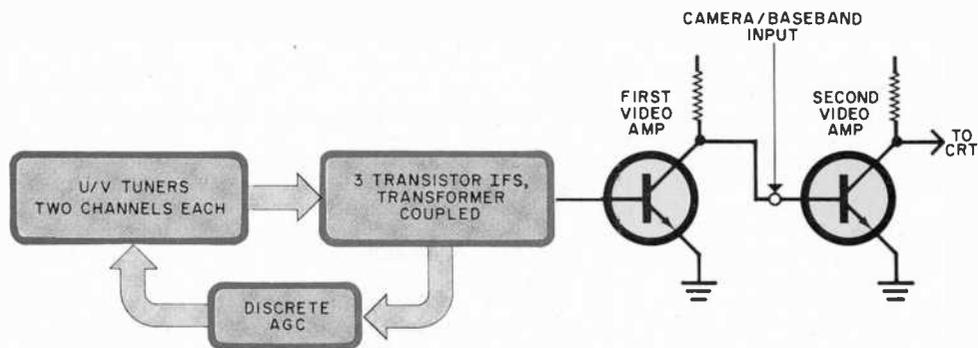


Fig. 2. Simplified block diagram of the chassis for one monitor, using all discrete transistors. The two 5-inch monochrome channels are identical.

Now the stars are within your reach

Movie Stars Concert Stars Sports Stars

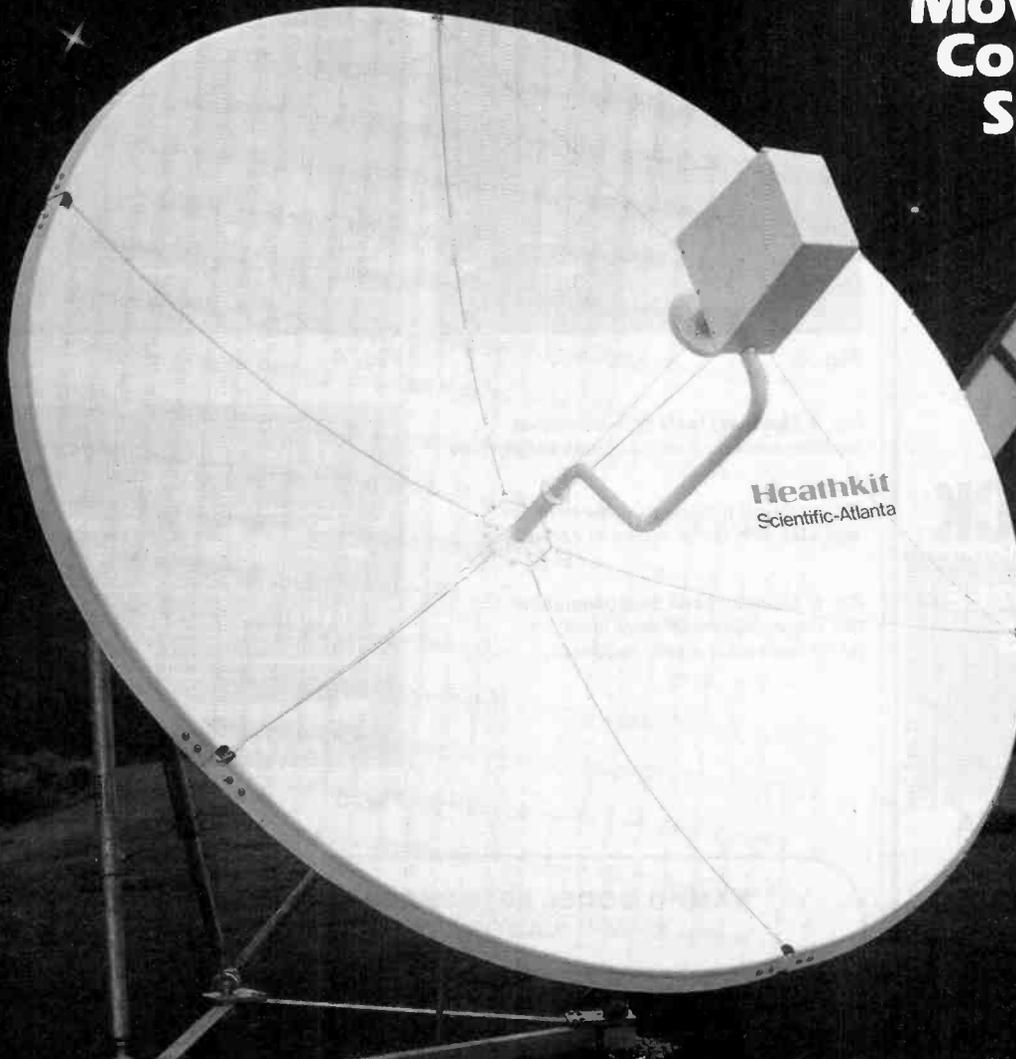

Your favorite stars are coming off the satellites right now in one of the greatest selections of family and adult entertainment ever offered. And now there's a new satellite receiver system that puts it all within your reach - at a price that's within reach.

The new Heathkit Earth Station

It includes a 3-meter Satellite Antenna with a single-axis adjustable mount that lets you direct your antenna to receive signals from the entire satellite arc. It's a heavy-duty, commercial-quality antenna, made by Scientific-Atlanta and designed for long, reliable performance.

Special Low-Noise Amplifier and Down-Converter converts signals to 500 MHz band for transmission on ordinary TV cable.

The Receiver features electronically-synthesized tuning for stable, drift-free reception, and 24 channel selections for a broad variety of programming. It even includes a special Zenith Space Command Remote Control so you can change programs without leaving your easy chair.

Special Earth Foundation Kit anchors your antenna firmly to withstand winds of up to 100 mph.

Unique Site Survey Kit

You can trust Heathkit to do it right. The first step in establishing your station is the purchase of a special Site Survey Kit that includes everything you need to determine a clear line-of-sight to the satellites. So you know your location is correct before you buy the Station.

Easy-to-follow, step-by-step assembly

Like all Heathkit products, the Satellite Earth Station includes a clearly written manual that guides you every step of the way through assembly and installation. And over-the-phone assistance is always available.

For complete details and prices on the Heathkit Earth Station and 400 other electronic kits for home, work or play, send today for the latest free Heathkit Catalog or visit your nearby Heathkit Electronic Center.



Send for free catalog

Write to Heath Co., Dept. 010-816,
Benton Harbor, MI 49022

Visit your Heathkit Store

Heathkit products are displayed, sold and serviced at 56 Heathkit Electronic Centers in the U.S. See your telephone white pages for locations.



Heathkit Electronic Centers are units of Vertechology Electronics Corporation

Viewing of some satellite TV channels may require the customer to obtain permission from, or make payments to, the programming company. The customer is responsible for compliance with all local, state and federal governmental laws and regulations, including but not limited to construction, placement and use. For use only in Continental U.S. This device has not been approved by the Federal Communications Commission. It is not, and may not be, offered for sale or lease, or sold or leased, until the approval of the FCC has been obtained.

Heathkit

CIRCLE NO. 37 ON FREE INFORMATION CARD

WHY K40 BECAME THE LARGEST SELLING CB ANTENNA IN JUST ONE YEAR!

Because

K40™

OFFERS A

MONEY BACK

DOUBLE GUARANTEE

- TRANSMITS FARTHER
- RECEIVES CLEARER

...THAN ANY ANTENNA
IT REPLACES!

*America
can do it
better!*



AN AMERICAN MADE PRODUCT
FROM AN AMERICAN COMPANY.

Call your local CB Dealer



For a FREE demo!

AMERICAN ANTENNA

© Copyright 1979 American Antenna Elgin, Illinois

video

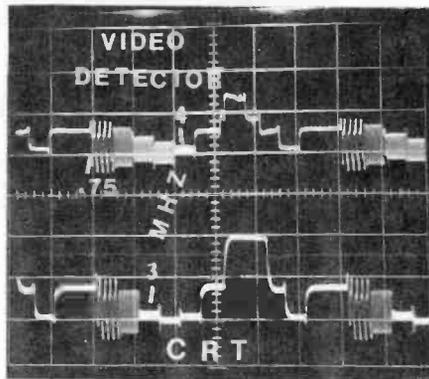


Fig. 3

Fig. 3. Multiburst tests on main-screen receiver showing 3 MHz at cathode ray tube.

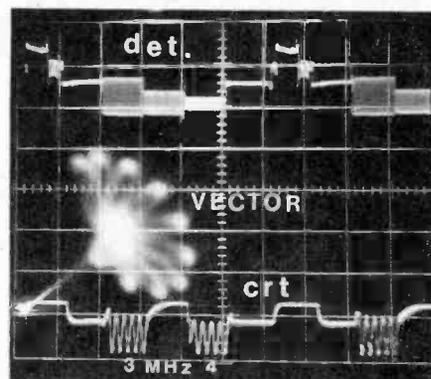


Fig. 4

Fig. 4. Swept chroma at video detector and CRT with vector shape at center.

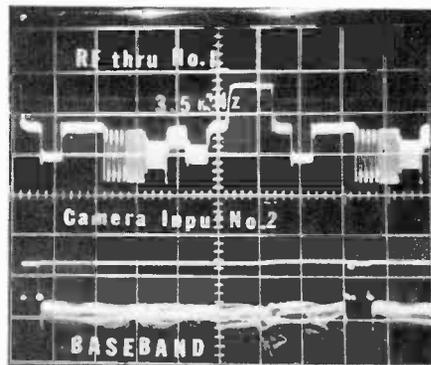


Fig. 5

Fig. 5. Multiburst and baseband at the two 5-inch black-and-white monitors which have a full 4-MHz bandpass.

SAMPO MODEL 9519 THREE-SCREEN RECEIVER LABORATORY DATA

Parameter	Measurement
Tuner/receiver sensitivity (min. signal for snow-free picture):	vhf (Ch. 8): -6 dBmV uhf (Ch. 30): -4 dBmV
Voltage regulation (line varied from 105 to 130 V):	Low voltage: 120-V supply—93.7% 24-V supply—93.9% High voltage: 26-kV supply—90.1%
Luminance bandpass at CRT:	3 MHz
Luminance bandpass at video detector:	4 MHz
S/N at CRT:	40 dB
Horizontal overscan:	15%
Agc signal range:	63 dB
Convergence:	99.9%
Barreling and pincushion effects:	None
CB interference at 60 ft on Chs. 2, 4, 5:	None
Audio bandpass (3 dB down):	130 Hz to 4.1 kHz
Power requirement (3 screens):	123 W
(19" screen only):	107 W

Note: Instruments used in these measurements are: Tektronix/Teletquipment D66, D67A oscilloscopes, Sadelco FS-3D-VU f/s meter, Data Precision 245, 1350, 1750 multimeters; B&K Precision 1248, 1250 color bar generators; Sencore VA48 (modified), CG169 color bar generator and PR 57 power supply; Winegard DX-300 amplifier; and Tektronix, Canon, and Polaroid cameras.

tricity. Wearing crepe-soled shoes, you'll have to wait a number of seconds between channel changes for a new charge to build up. The infrared tuning is wholly satisfactory.

Servicing the monochrome sets could be difficult because they are recessed within the cabinet, and not mounted on

slide rails. For example, it has an almost completely unpluggable chassis. The main 19-inch color receiver's performance is about average among high-end import models. All in all, its conservative design provides a good picture.

— Stan Prentiss

CIRCLE NO. 103 ON FREE INFORMATION CARD

POPULAR ELECTRONICS

MANUFACTURER'S SPECIFICATIONS

CRT

Display area: 8 x 10 cm (rectangular)
Phosphor: P31 (blue)
Accelerating potential: 6 kV
Graticule: built in, 0, 10, 90 and 100% markings

Beam finder

Vertical Amplifier (A and B)

Bandwidth: dc-60 MHz, ± 3 dB, -6 dB at 80 MHz, -12 dB at 100 MHz; ac mode is from 10 Hz to 60 MHz, ± 3 dB

Risetime: 6 nanoseconds

Sensitivity: 5 mV/div to 20 V/div in 12 steps, 1-2-5 sequence with variable vernier; 0.05 V/div to 200 V/div using 39G149 X10 Low Capacitance Probe

Accuracy: $\pm 4\%$ from 20° to 30°C
 $\pm 6\%$ from 0° to 40°C
 10% for A+B, or B-A displays

Input impedance: 10 megohms/ 15 pF using 39G149 probe
 1 megohm/50 pF direct input

Max. input voltage: 2 kV peak-to-peak (dc + peak ac) using the 39G149 probe; 500 V (dc + peak ac) using direct input. Derates with frequency.

Display modes: A, inverted A, B, A & B, A + B, B - A, vector.

Horizontal Deflection

Sweep rate: 100 ms/div to 0.1 μ s/div, 1-2-5 sequence, 19 steps, with variable vernier; special pushbuttons select 2 cycles vertical or horizontal of NTSC composite video.

Accuracy: $\pm 4\%$ typical

X10 magnification: Sweep becomes 10 ms/div to 10 ns/div; accuracy is $\pm 5\%$, except on .1, .2, and .5 μ s/div where it is $\pm 8\%$.

Triggering

Source: channel A, B, ac line, external

Mode: normal, auto, video

Polarity: +, -

Internal trigger sensitivity: ac coupled is 0.5 div of deflection between 10 Hz and 20 MHz; 1 division of deflection from 20 to 60 MHz; 3 divisions of deflection at 100 MHz.

External trigger sensitivity: 100 mV to 40 MHz; triggerable to 100 MHz.

External trigger max input: 500 V (peak ac + dc)

Video trigger sensitivity: 1 division of deflection

Vector (X-Y Mode)

Bandwidth: dc to 5 MHz ± 3 dB

Phase shift: ± 3 degrees, dc to 5 MHz

Input: channel A is Y axis, B is X axis

Sensitivity: same as vertical channels

Z Axis

Beam blanking: 5 V positive

Beam intensification: 5 V negative

Input: dc coupled

Frequency range: dc to 5 MHz

Max. input voltage: 50 V (dc plus peak ac)

Output

Calibration signal: 1 V p-p, 2-kHz square wave

Physical

Weight: 25 pounds

Height: 9.5 in.

Width: 12 in.

Depth: 17 in.

Power Requirements

Normal: 105 to 130 V, 50/60 Hz; 35 W; field adjustable to 210 to 250 V, 50/60 Hz.

Supplied Accessories: two 39G149 X10 Low Capacity Test Probes; one 66K28 Vector Graticule Film; one 48" black test lead.

Optional Accessories: DBA220 X10 Low Level AC Amplifier to increase audio sensitivity by 20 dB; WBA52 Wideband Amplifier to raise 1-to-100-MHz signals by 30 dB; and PL207 r-f Pickup Loop for indirect high-frequency measurement.

There are three controls for each vertical channel—the AC/DC/GND input selector; a 23-position (arranged 1-2-5) VOLTS/DIVISION selector switch with a coaxial vernier, and a VERTICAL POSITION control. Each channel also provides a recessed control for DC BAL. The channel-A position control can be pulled out to invert the channel-A signal only. Because of this, channel A is also provided with a recessed INVERT CAL control. Both vertical channels are provided with a BNC input connector and a banana-type ground connector.

The trigger SOURCE can be selected from CHAN A, CHAN B, AC LINE, or from the EXT input, which is also provided with a BNC input connector. The trigger MODE can be selected from NORM, which shows a trace only when the triggering circuits are fully locked to the input signal, from AUTO, which displays a trace whether the triggering circuits are locked or not, from EXT, which allows external triggering, and from VIDEO, which uses sync separators to lock to video sync pulses. The latter mode works in conjunction with the VIDEO HORIZ and VIDEO VERT pushbuttons to display two or more horizontal lines or video fields.

The trigger LEVEL control can be set to allow triggering on either the positive- or negative-going slope of the displayed waveform, while the trigger POLARITY determines whether the trace starts on the positive or negative transition of the input signal. The TIME-BASE-FREQ selector switch has 19 positions (in a 1-2-5 sequence), from 100 ms/division to .1 μ s/division. The 20th position of this switch, VIDEO PRESET, enables the internal sync separators—there are two, one for the horizontal and one for vertical sync.

Some older scopes use the 60-Hz power-line frequency for viewing video waveforms. With chroma signals, the sync will be unsteady since chroma vertical sync is 59.94 Hz for interlaced signals, and 60.02 Hz for noninterlaced signals. When the X10 expansion switch (mounted coaxially with the HORIZ POS control) is operated, sweep speed becomes 10 ms/div to 10 ns/div. Depressing the VECTOR pushbutton allows X-Y operation with channel A providing the vertical, and channel B the horizontal signal. The vector CRT film overlay is easily applied to the CRT graticule window.

The manual accompanying the SC60 is excellent, and profusely illustrated. Besides a complete discussion of the scope, there is a lengthy section covering applications and maintenance.

Comments. The manufacturer's specifications for the SC60 are shown in the table. The SC60 was checked by the Lockheed Instrumentation Measurement Laboratory (Plainfield, NJ) against standards traceable to the National Bureau of Standards. The Lab issued a certificate testifying that the SC60 met or exceeded its claimed specifications in all respects.

The SC60 was used on a test bench for a few weeks and was found to be excellent. The clarity of the control identifications and the wide spacing between controls made this instrument very easy to use. The traces were bright and sharp, even when displaying fast-risetime, low-frequency signals. Sweep sync was excellent, even at extremes of frequency and amplitude. Of particular value for TV servicing were the two sync separators that allow stable viewing of almost any video signal. —Les Solomon


CIRCLE NO. 104 ON FREE INFORMATION CARD

In a world where sound reaches new levels every day, ADC delivers the ultimate high.

The ultimate high is total control. And an ADC Sound ShaperSM Frequency Equalizer lets you control your sound and custom-tailor your music with the mastery of a pro.

And no better way demonstrates the benefits of an ADC Sound Shaper than taping. Even without a studio environment, you can recreate your personal recordings by changing the frequency response curve of the source material — making the sound more like the original and more agreeable to your ears.

Our complete ADC Sound Shaper IC line* has an equalizer that is right for you and your system. The SS-110 ten-band full octave equalizer, a step up from our SS-1, features LED-lit slide controls and one-way tape dubbing. If you desire even more control, our twelve-band SS-II and top-of-the-line SS-III include two-way tape dubbing and sub-sonic filters. Our SS-III ParagrophicSM with 24 ancillary switches that enable you to control 36 bands per channel combines

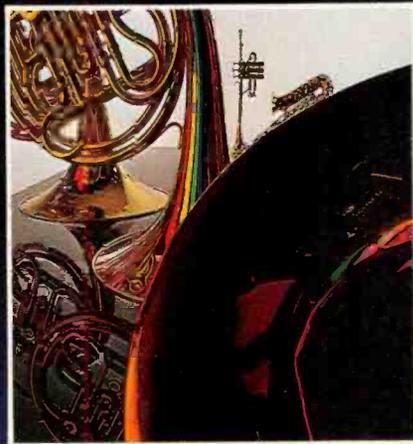

the ease and control of a graphic equalizer with the precision and versatility of a parametric. All at a price you can afford.

All of our equalizers feature LED-lit slide controls allowing for visual

plotting of the equalization curve. And all ADC Sound Shapers embody the outstanding ADC technology that has made us the leaders in the industry.

To really complete your custom-tailored control-ability, our ADC Real Time Spectrum Analyzer is a must. Equipped with its own pink noise generator and calibrated microphone, the SA-1 provides a visual presentation of the changing spectrum through 132 LED displays. So you can actually see proof of the equalized sound you've achieved.

With an ADC Sound Shaper and an ADC Real Time Spectrum Analyzer, you can attain a new level of control. And ultimately, isn't that the musical high you've always wanted?

*Sound Shaper*SM
Frequency Equalizers
and Spectrum Analyzer




ADC
A BSR COMPANY

Sound thinking has moved us even further ahead.

BSR (USA) Ltd., Blauvelt, N.Y. 10913, BSR (Canada) Ltd., Rexdale Ontario

*Sound Shaper is a registered trademark of Audio Dynamics Corporation. *IC indicates new Sound ShaperSM series.

You gotta shop around.

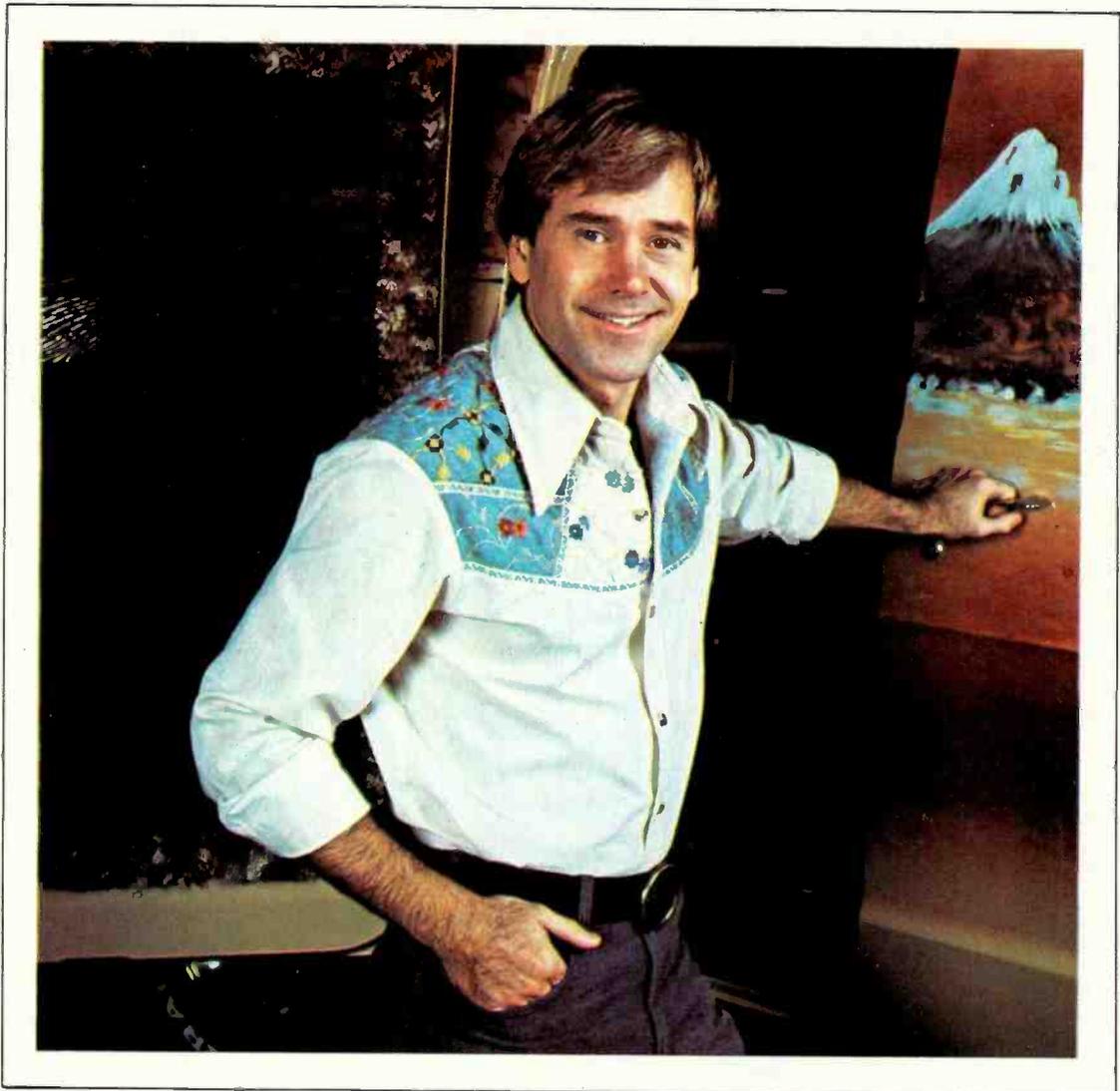

**When you do, you'll probably pick CIE.
You can't afford to settle for
less when it comes to something like
electronics training that could
affect your whole life.**

When you shop around for tires, you look for a bargain. After all, if it's the same brand, better price—why not save money?

Education's different. There's no such thing as "same brand." No two schools are alike. And, once you've made your choice, the training you get stays with you for the rest of your life.

So, shop around for your training. Not for the bargain. For the best. Thorough, professional training to help give you pride and confidence.

* * *

If you talked to some of our graduates, chances are you'd find a lot of them shopped around for their training. They pretty much knew what was available. And they picked CIE as number one.

Why you should shop around yourself.

We hope you'll shop around. Because, frankly, CIE isn't for everyone.

There are other options for the hobbyist. If you're the ambitious type—with serious career goals in electronics—take a close look at what we've planned for you at CIE.

What you should look for first.

Part of what makes electronics so interesting is it's based on scientific discoveries—on ideas! So the first thing to look for is a program that starts with ideas and builds on them!


That's what happens with CIE's Auto-Programmed® Lessons. Each lesson takes one or two principles and helps you master them—before you start using them!

How practical is the training?

This is the next big important question. After all, your career will be built on what you can do—and on how well you do it.

Here are ways some of CIE's troubleshooting programs help you get your "hands-on" training...

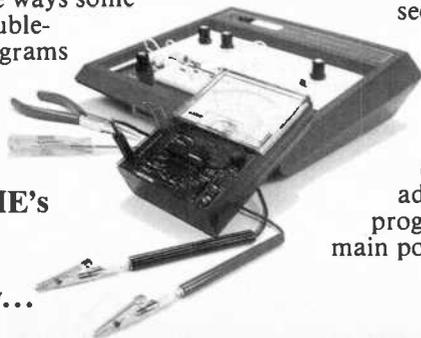With CIE's Personal Training Laboratory...




you learn and review the basics—perform dozens of experiments. Plus, you use a 3-in-1 precision Multimeter to learn testing, checking, analyzing!



When you build your own 5 MHz Triggered-Sweep, Solid-State Oscilloscope you take your first real professional step. You use it as a doctor uses an X-ray machine—to "read" waveform patterns... lock them in... study, understand and interpret them!

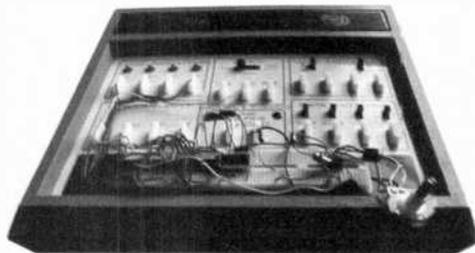When you get your Digital Learning Laboratory you'll be into digital theory—essential training today for anyone



who wants to keep pace with the state of the art of electronics in the eighties. With CIE's Digital Lab, you'll be applying in dozens of fascinating ways the theory you've learned. For example, you'll compare analog and digital devices. You'll learn to make binary to decimal conversions and to work with semiconductor devices and circuits. You'll see how digital equipment is vital in today's exciting, growing fields such as security where digital

theory provides the brains for space-age alarm and protective devices.

Of course, CIE offers even more advanced training programs, too. But the main point is simply this:

All this training takes effort. But you'll enjoy it. And it's a real plus for a troubleshooting career!

Do you prepare for your FCC License?

Avoid regrets later. Check this out before you enroll in any program.

More than half of CIE's courses prepare you for the government-administered FCC License exam. In continuing surveys, nearly 4 out of 5 CIE graduates who take the exam get their Licenses!

Associate Degree

Now, CIE offers an Associate in Applied Science Degree in Electronics Engineering Technology. In fact, all or most of every CIE Career Course is directly creditable towards the Associate Degree.

Shop around...but send for CIE's free school catalog first!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name and date of this magazine. We'll send you a copy of CIE's FREE school catalog—plus a complete package of independent home study information! For your convenience, we'll try to have a representative contact you to answer your questions. Mail the card or coupon—or write:

CIE, 1776 East 17th St.,
Cleveland, OH 44114.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

YES... I'm shopping around for the right kind of career training in electronics troubleshooting — and CIE sounds well worth looking into. Please send me my FREE CIE school catalog — including details about the Associate Degree program — plus my FREE package of home study information!

Print Name _____

Address _____ Apt. _____

City _____

State _____ Zip _____


Age _____ Phone _____ (area code)

Check box for G.I. Bill information:
 Veteran Active Duty

Mail today!

PE44

dbx has been silent too long.

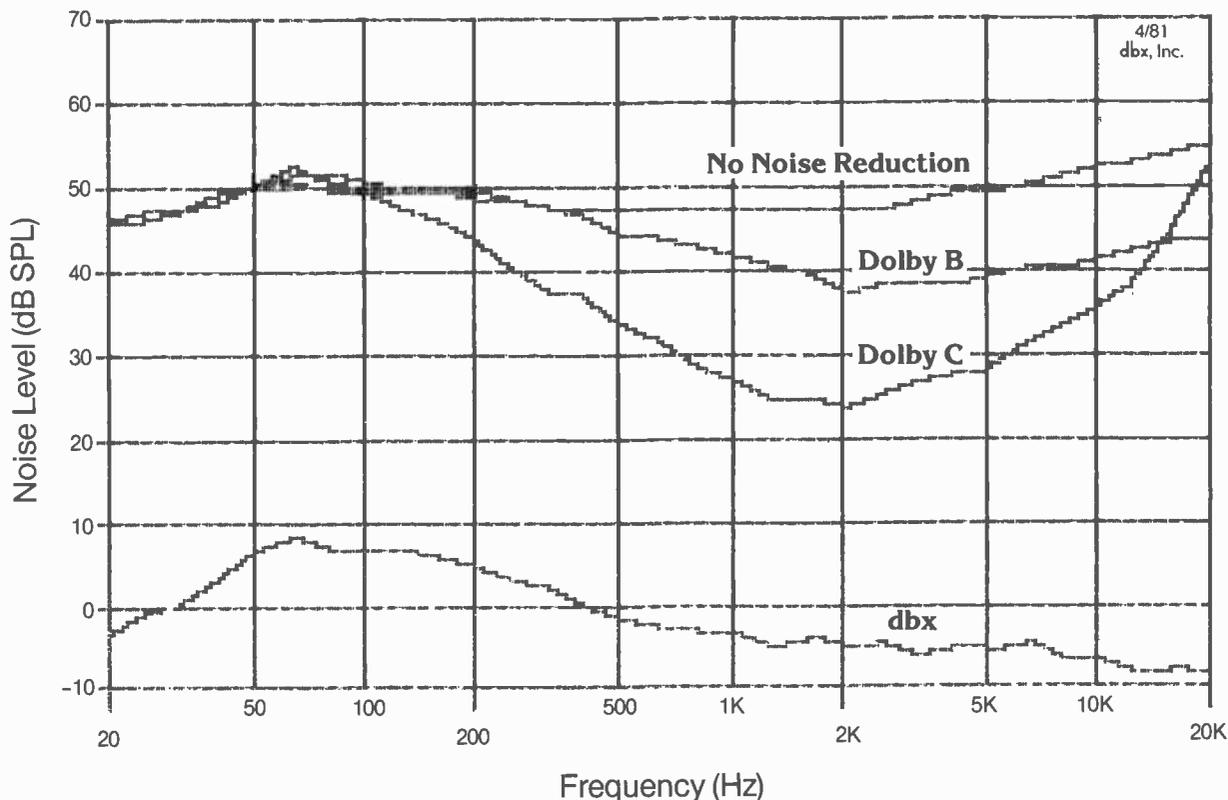

Noise from biased Chromium Dioxide cassette tape, comparing Dolby and dbx noise reduction systems. One third octave analysis. Tape noise level referenced to 200 nWb/m = 110dB SPL.

For years Dolby® has been trying to reduce tape noise.

First came Dolby B. Then Dolby HX. Now there's Dolby C.

At dbx, we think it's time to set the record straight. You see, we've never tried to reduce tape noise. We've never had to.

Because from the beginning, dbx has done what Dolby keeps trying to do: *eliminate* tape noise.

Just compare Dolby's latest attempt with dbx.

Where Dolby C reaches a maximum noise reduction of 20 dB, dbx reaches 50 dB. In a CCIR-weighted noise measurement analysis, Dolby C manages only 18 dB, while dbx achieves 55 dB.

What do these numbers actually mean?

Simply this. When you push the Dolby C button, tape noise decreases. When you push the dbx button, tape noise disappears. (You can perform this test yourself using any blank cassette tape.)

The dbx system reduces tape noise so effectively, that it's beneath the noise floor of even the quietest living rooms. Unlike Dolby C, dbx is effective in more than just the mid-range. It operates across the entire frequency spectrum. There's no low-frequency noise. No high-frequency noise. No noise, period.

No wonder Technics, Onkyo, Yamaha, TEAC and others have designed their newest generation of tape decks with dbx.

There's more to this story, too. With the dbx tape noise reduction system, you're also equipped to play the widely acclaimed dbx Discs, the world's only Full Dynamic Range Records — and the first discs that eliminate record surface noise.

In addition, when digital playback technology finally arrives, dbx is the only system that will faithfully reproduce that sound on tape. You'll even be able to hear the sound of digital in your car, because we've developed a dbx decoding system for car stereo.

So before you rush out to buy a tape deck with Dolby C, we have a suggestion.

Listen to the new tape decks with dbx. Or hear what a dbx Model 222 or 224 can do for your existing system.

At dbx, we've been silent too long.

The fact is, Dolby just reduces noise.


dbx eliminates it.

dbx®

dbx® is a registered trademark of dbx, Inc.
Dolby® is a registered trademark of Dolby Laboratories, Inc.

dbx, Incorporated, 71 Chapel Street, Newton, Mass. 02195 U.S.A.
Tel. (617) 964-3210. Telex 92-2522. Distributed throughout Canada by BSR (Canada) Ltd., Rexdale, Ontario.

Popular Electronics Tests

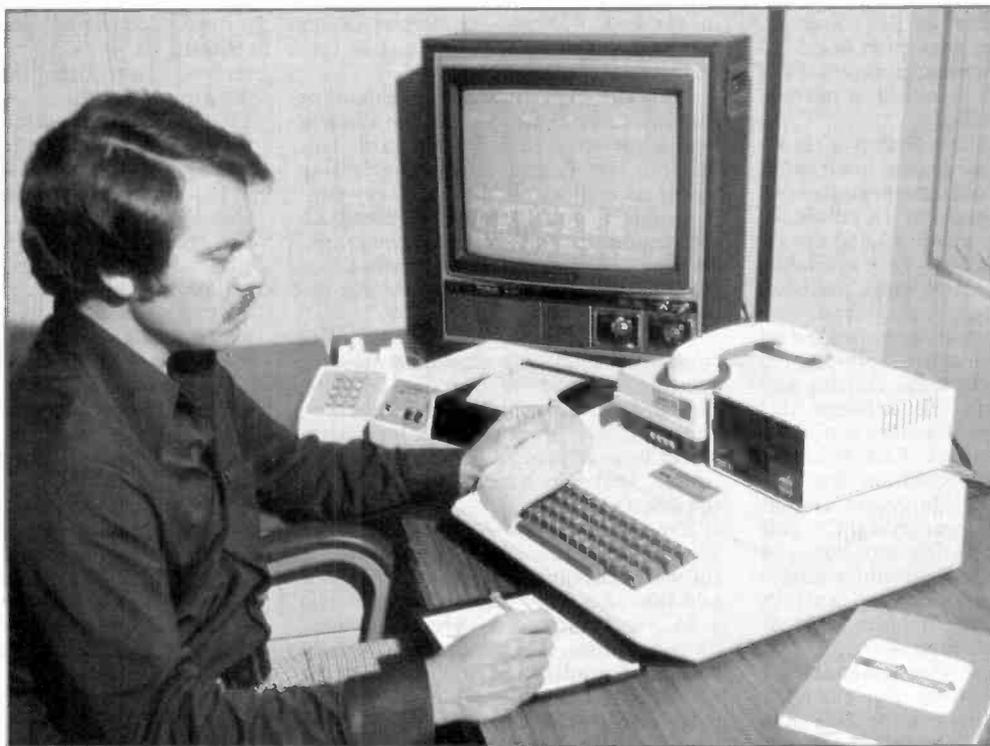

The Apple II Plus Personal Computer System

ALTHOUGH it is not a new entry to the world of personal computers, the Apple II Plus is by far one of the most flexible and powerful machines available. Based on the 6502 microprocessor and an 8-bit bidirectional bus with eight so-called peripheral slots, the system can accommodate a wide range of applications. Essentially, the Apple II Plus is an upgraded version of the Apple II, containing built-in Applesoft and with the Integer BASIC dropped.

As designed, the Apple II Plus can operate with either a conventional TV receiver or a video monitor. When used with the former, the system needs an r-f modulator that meets FCC requirements. Performance is good either way, but the monitor is the best choice when color of very high quality is required.

The computer's enclosure is compact enough to be easily portable, and has a pleasing color. Other accessories, such as the video monitor, disks and printers, are outboard to the main unit. A carrying case, with pockets for cables, is provided for the main-frame section.

A basic Apple II Plus system with 16K bytes of RAM, ROM-resident Ap-

plesoft Extended BASIC, Auto-Start ROM, disassembler, and reference manuals—of which there are many—is priced at \$1330. However, locating a 16K system may be difficult, as Apple has elected to provide only 48K systems (which cost \$1530) to distributors. This has caused retailers some consternation, but, in our opinion, an extra 32K bytes of RAM for \$200 represents a good buy.

The configuration that we used for our evaluation consisted of:

Apple II Plus with 48K RAM and all standard features	\$1,530
Disks II, a 16-sector 5.25-inch single-density floppy with interface and DOS 3.3	645
Second disk drive	525
12-inch monochrome Sanyo monitor	320
Silentype printer with Apple II interface	635
Language System with Apple Pascal	495
SSM Microcomputer Products AIO serial and parallel Apple interface	195
Microsoft RAMcard	195
Z-80 Softcard	349
	<u>\$4,919</u>

In addition to the above, Personal Software has made available: VisiCalc, Visi-dex, Visitrend/Visiplot, and Visiterm. Agent Computer Services provided the Buffered Modem program for testing the viability of communications, and Vista provided the Model-150 40-character keyboard buffer.

General Description. The Apple II Plus consists of a molded, high-impact plastic case that houses the 6502 CPU, a high-efficiency switching power supply with sufficient shielding to avoid EMI and RFI difficulties, a 52-key typewriter-style full-stroke keyboard, cassette recorder input and output jacks, and video display output jack. The system backplane contains eight peripheral slots.

The system keyboard sports 2-key rollover and four special-function keys: CTRL (control), ESC (escape), RESET (used to restart the system), and REPT (repeat—provides automatic repetition of a depressed key). The coding is upper-case ASCII. Lower case is omitted, but can be added by plugging in a PROM with a new character set.

(Continued on page 40)

(Continued from page 39)

The standard display is memory mapped into system RAM and provides three display modes: text, low-resolution graphics, and high-resolution graphics. In the text mode, the display is 960 characters (25 lines \times 40 columns), with each character generated in a 5×7 dot matrix. Upper-case characters, 64 in all, are generated in either a normal, inverse, or flashing mode.

The hallmark of the system is its sophisticated graphics. In the low-resolution mode, 1920 blocks are available (40×48 array) in a total of 16 colors. In the high-resolution mode, 53,760 dot locations (280×192 array) are available, and up to six colors (black, white, red, blue, green, and violet) can be displayed.

Because it is memory mapped, exact locations on screen can be pin-pointed by software to create some exciting and spectacular displays. To enhance this capability, the screen memory is divided into two areas, or pages. This primary/secondary page configuration lets you flip pages in and out to create animation. Moreover, by employing the soft switches of the operating monitor, you can invoke a variety of graphics modes and mixed modes (graphics and text). In addition, the system includes a loud-speaker and joystick controllers.

Numerous well-written manuals are supplied with the system. For example, to get you going, there is the 200-page *Apple II Reference Manual*. This manual provides information on the basic working of the system (including schematics) and supplies such data as important screen addresses and a listing of the ROM monitor. Other manuals explain—in similar detail—Applesoft BASIC, and PASCAL, as well as the use of the DOS.

Our sample system used the language card that bundled PASCAL. Recently, Apple has unbundled the PASCAL portion, offering the upgrade in memory separately. This is probably for compatibility with the Microsoft RAMcard, which was designed to work with existing Apple software and PASCAL.

The Plus II comes equipped with integer ROM-based BASIC and disk-extended Applesoft BASIC. The integer version doesn't support floating-point arithmetic and is like an expanded tiny BASIC. The extended version, however, offers complete BASIC capabilities, including a full set of graphics primitives, and peripheral controller calls such as PDL for paddle. (This function returns the current value from 0 to 255 of the game control specified as the argument. Unfortunately, we didn't have game controls, but are reasonably sure that everything works as advertised.)

The disk subsystem we used, a controller, and two drives, derives power right from the bus, thus reducing the number of wires hanging from the back of the enclosure. The only cable connections run from the controller card to the drives.

In a system of this size, two drives—

all that are generally used—seem to be more than sufficient. However, you can add additional controllers and have as many as six drives. One interesting approach is to add an 8-inch controller and use both the 5.25-inch and 8-inch drives in tandem. Adding the larger drives means that power for them must be taken from external power plugs.

Like the disk system, the Silentye thermal printer works in conjunction with a bus-oriented controller card. This fits into slot-1, and provides operating power as well as all the necessary control signals. The Silentye handles both alphanumerics and graphics. The graphics are presented in a raster format that permits the printing of complete dot-by-dot pictures.

Unfortunately, to get multiple copies from the printer, you must do a multiple printing. This can be overcome by using an SSM AIO serial/parallel card and adding either a dot-matrix or daisy-wheel impact printer. This assumes, of course, that you have an open slot for the interface.

Even though the Apple is designed around the 6502 and is meant to use software developed for that CPU, the addition of a Z-80 microprocessor—via a Microsoft Softcard—greatly extends its capabilities. This, moreover, is done without degrading the functioning of the 6502. The Softcard provides all the features one would expect from a Z-80, including support of the CP/M operating system. However, operation is more complex than it may seem. The Z-80 provides computing power, while the 6502 handles all I/O including operation of the screen display under Z-80 supervision. This arrangement is both speedy and efficient.

Evaluation. The Apple II, almost regardless of configuration, is easy to use. Because of the very carefully written, concise manuals, setting up a system like the one we used is straightforward, and takes only about 30 minutes.

Although not CP/M compatible, the disk operating system (DOS3.3) handles simple jobs extremely well. For example, initializing a disk is done by formatting it via a utility, then writing a Hello program under BASIC. This we found intriguing, as it meant we could be very inventive in our sign-on messages. Furthermore, for turnkey-type operation, our sign-on could be a unique program that interfaces to a larger program or other programs—a menu system, if you will.

When the system is first turned on, the unit begins looking for a disk to load. This is a function of the Auto-Start ROM and can be quite disconcerting at first, especially if you were planning to go into ROMBASIC. To suppress disk operation, simply hold down the RESET key while powering up. Should you power up and want to stop the disk, depressing RESET, will drop you into the ROM-resident language and stop the drives. If RESET is not used, the drives will run

without timing out, which could be a minor problem.

Rumors have circulated concerning the Apple's susceptibility to heat, especially after it has run for long intervals of time. But try as we might, running it for extended periods and deliberately restricting its ventilation, we could induce no heat-related malfunctions, even with the air around the main circuit board at 110°F. We conclude, therefore, that whatever problems the system had in this area have been solved.

Evaluating the system further, we took a program that would link to other files, read and hold tax tables, and update other files. The purpose was to determine whether or not the data would always be accurate as it transferred between files and out to a printer. We set an arbitrary limit of 500 items.

The whole process took about 1 hour and 30 minutes to generate, and another hour and 15 minutes to perform the swaps and sorts. In our test, no data was lost.

Going further, we tried a program that would generate graphics on the screen, using the database already generated. That data was handled with accuracy, but not with dispatch. (However, it must be remembered this is a floppy-based system and speed is not one of its prime virtues.)

Our next test used Personal Software's Visidex, which is designed to take information in any format and return it either on the screen or printer, sorted or unsorted. This program relies on the channel speed of the disk system to display information quickly. Access to a disk record is almost instantaneous. Furthermore, the software package is time-oriented so that records can be related either to system time (date and clock time) or actual time, assuming that you have a real-time clock.

Next, we tested to see if quickly raising and lowering line voltages would damage the rather large database we maintain under Visidex. It did not. Operation was unaffected by line voltages from 75% to 130% of nominal.


One annoying shortcoming was the lack of upper/lower case character set. Even though correctable through purchase of an ROM for about \$65 this omission seems out of place in an otherwise sophisticated system. Furthermore, the location of the arrowed keys is a problem since it is easy to hit one when your goal is the RETURN key. Even worse is the location of the RESET key directly above RETURN. We would have also liked to see some special-function keys, either fixed or user-definable.

Although the backplane design offers flexibility by memory-mapping devices into the system, it does assume that the operator has intimate knowledge of the machine. What would have been nice is a utility program under DOS that would check each slot for a device and determine if it could be properly interfaced. Should the installed card not be of Apple origin or directly supported by Ap-

Radio Shack is America's Parts Place™

No Minimum Order! No Waiting! Low Prices!

Printed Circuit Board Template

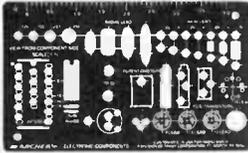

For Fast, Accurate PC Board Designs!


NEW!
3⁹⁵

Superior-quality transparent "cool-blue" stencil with exact-size cut-outs for all commonly used PC components. Simplifies layouts and ends guesswork — your finished boards will have that "pro" look! 276-177 3.95

4" Silicon Solar Cell

NEW!
16⁹⁵

Harness the Sun!

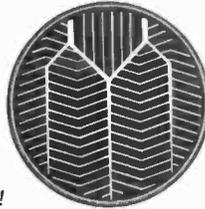


An efficient first-quality cell — use several to power science projects, models, radios, handy-talkies; charge batteries or build into panels, etc. Typical voltage: 0.42. Max. current (short circuit): 2.0A. 276-127 16.95

43-Range, 50,000 Ohms-Per-Volt Multitester With Range Doubler

39⁹⁵

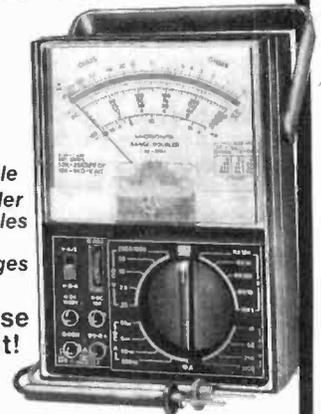
- Big 4 1/4" Mirrored Scale
- Range Doubler Switch Doubles Current and Voltage Ranges



Ready to Use — Not a Kit!

Ideal for home, shop and vehicle electronics testing. Measures: 0 to 1000 volts DC in 12 ranges; 0 to 1000 volts AC in 8 ranges; 0 to 10 amps DC current in 10 ranges; resistance in 5 ranges; Decibels, — 20 to + 62 in 8 ranges. Features diode-protected movement, function switch with "off" position. Accuracy: ± 3% DC, ± 4% AC. Requires "AA" and 9V batteries. 22-204 39.95

Symbols Template

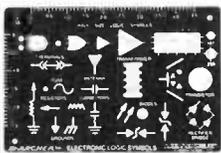

NEW! **2⁹⁵**

The Easy Way to Draw "Pro-Quality" Schematic Diagrams!

A "must" for electronics students, teachers and designers. This durable see-through stencil has all the most-used component and logic symbols, plus two rules. 276-178 2.95

0 to 15VDC Panel Meter



NEW!
8⁹⁵

Precision D'Arsonval Movement

Ideal for automotive projects, battery chargers, power supplies and more. Accuracy: ± 5%, full scale. 2 3/4 x 2 1/4 x 1 1/4" 270-1754 8.95

16K Dynamic RAM




5⁹⁵
New Low Price!

Was \$13.95 in 1981 Catalog

4116. 100% prime! Access time under 250 ns. Ideal for computer memories. 276-2505 Now 5.95

DPST Reed Relay

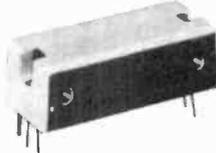

Only **99¢**

Ideal for low-power circuits. Coil: 12VDC, 375-800 ohms. Contacts: 0.5A @ 125 VAC. PC pins on .100" centers. 1 1/8 x 9/16 x 7/16" 275-229 99¢

100k-Ohm Joystick

NEW! **4⁹⁵**

For Video Games, R/C Vehicles and Microcomputers



Twin linear taper controls with a single, removable 1"-long control shaft. Body: 1 7/8" square. With mtg. screws. 271-1705 4.95

Toggle Switch With LED Indicator



NEW! **2⁹⁹**
Rated 5 Amps

SPST for 12-volt DC — perfect for projects or customizing your vehicle. LED in handle lights in "on" position. 275-680 2.99

5-Pin Inline-Type DIN Socket



NEW! **1⁴⁹**

Designed to accept 3 or 5-pin male DIN-type plugs. Built-in strain relief. Solder terminals. 274-006 1.49

Triac-Output Optocoupler



NEW!
High Isolation **2¹⁹**

MOC3010. Ideal for a solid-state AC relay or computer control of real-world functions. Switches up to 125VAC at 100 mA. Isolation: 1 kV, minimum. 6-pin. 276-134 2.19

Op-Amp Output Optocoupler



NEW!
2⁹⁹

1 kV Isolation, Minimum
MOC5010. Ideal for audio projects, audio mixers, more. High linearity. 250 kHz bandwidth. 6-pin. 276-135 2.99

NEW! Ohm's Law "Computer"

49¢
Handy Pocket Guide!



Easy to use — gives you quick answers to Ohm's Law and parallel resistance problems. It'll spoil you! 271-1210 Only 49¢

High-Output Infrared Emitting LED



NEW! **1⁴⁹**

XC880-A. Emits as much energy as three conventional IR LEDs, yet consumes far less current. Good spectral match for photodiodes and transistors. Requires 1.3V at 20 mA. 276-143 1.49


CMOS Timer IC



NEW!
1⁹⁹

7555. CMOS replacement for 555 timer with very low power consumption (80 µA). 100 mA source or sink. 276-1743 1.99

Phase-Locked Loop

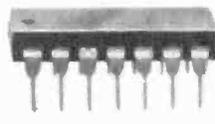


NEW!
1⁵⁹

LM565. Basic building block for FM detectors, freq. synthesizers, SCA and RTTY decoders, and more. 14-pin. 276-1720 1.59

Microwave Diodes

NEW!
1⁹⁹

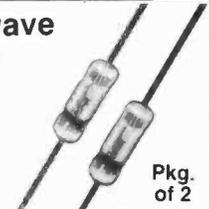

5082-2835. Schottky barrier diodes with low noise figure — ideal for UHF and microwave projects. Why pay more? 276-1124 Pkg. of 2/1.99

NEW 1982 CATALOG AVAILABLE NOW!

Radio Shack

A DIVISION OF TANDY CORPORATION • FORT WORTH, TEXAS 76102
NOW OVER 8000 LOCATIONS WORLDWIDE

ple, its attributes could then be requested and held in a system map file. Application programs could use this file by simply calling the device.

As described, we encountered no problems with heat or, for that matter, bus loading. But we noticed that it does become a tight fit when you start adding cards to the backplane; such is the price of ready portability. And speaking of portability, a card-restraint cage would be a nice touch, even at a slight cost.

Comments. The Apple is one of the most widely supported machines on the personal computer market today, with over 300 companies providing hardware, software or both. Additionally, numerous manufacturers see the machine as a low-cost entry to the high-end graphics marketplace.



Interestingly, though this may be strictly our perception, the audio aspect of the machine has not caught on. But this may be changing. According to some observers, sophisticated voice-output devices will make the machine downright conversational.

As far as we are concerned, the Apple II Plus gets high marks and has no serious shortcomings anywhere. But as capable as this machine is, we aren't convinced that it is ideal for business. We

do believe, however, that it fits well into environments requiring rapid data collection and into graphic arts. In fact, the machine has found a home in numerous

schools that use it for teaching everything from computer science to manufacturing skills. —Carl Warren

CIRCLE NO. 102 ON FREE INFORMATION CARD

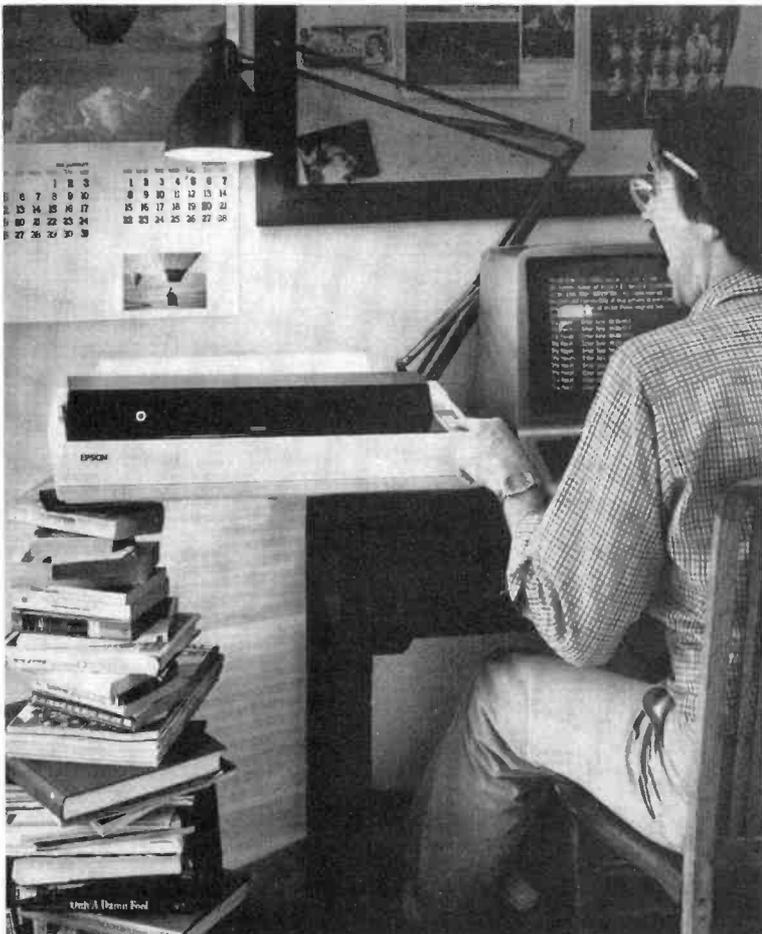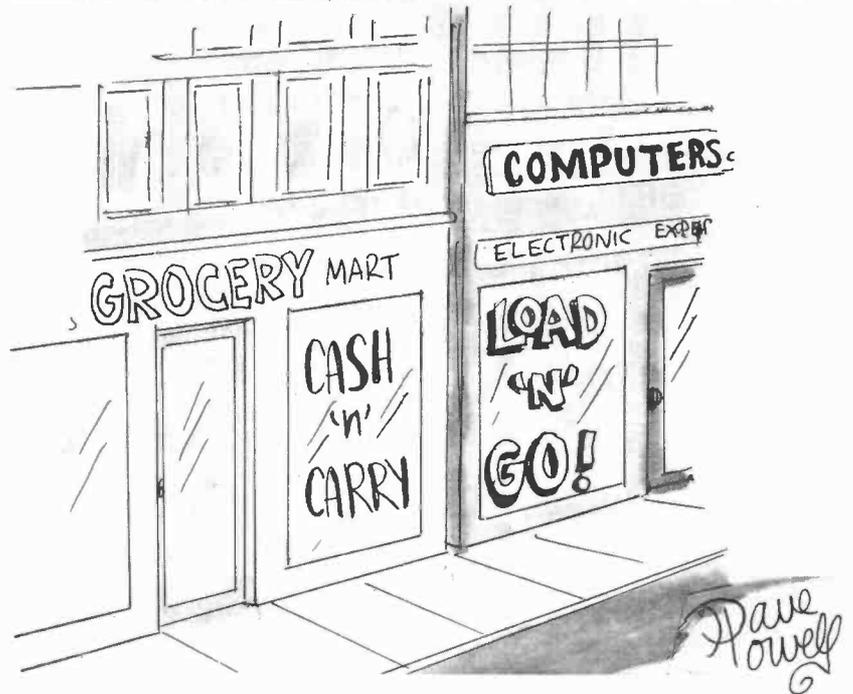

The MX-100. Not just better. Bigger. Epson.

The new Epson MX-100 is a printer that must be seen to be believed.

For starters, we built in absolutely unmatched correspondence quality printing and a high resolution bit-image graphics capability. Then we added the ability to print up to 233 columns of information on 15.5" wide paper to give you the most incredible spread sheets you're ever likely to see. Finally, we topped it all off with *both* a satin-smooth friction feed platen *and* fully adjustable, removable tractors. And the list of standard features goes on and on and on.

Needless to say, the specs on this machine — and especially at under \$1000 — are practically unbelievable. But there's something about the MX-100 that goes far beyond just the specs. Mere words fail us. But when you see an MX-100, you'll know what we mean.

It's not only better... it's bigger.

EPSON
EPSON AMERICA, INC.

3415 Kashiwa Street • Torrance, California 90505
(213) 539-9140

CIRCLE NO. 27 ON FREE INFORMATION CARD


POPULAR ELECTRONICS

ALBIA Electronics


YOUR MAIL-ORDER ELECTRONIC SUPPLY HOUSE!

8 CHANNEL SCOPE MULTIPLEXER, DM-12

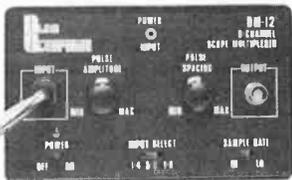Convert your single channel scope into a 4 or 8 channel instrument—just connect the DM-12, 8 channel scope multiplexer to your scope, clip the 8 input probes to the signals you want to view. Simple, easy, fast—can handle logic level TTL signals from DC to 3MHz. Features separate spacing and trace amplitude controls and selectable sampling rate—all to insure easy clear scope display.



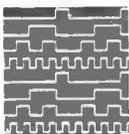Completely assembled and tested! Ready to use!



VIEW 8 CHANNELS AT ONCE!

\$69⁹⁵

- 8 TTL compatible input channels (1 TTL load per channel) can drive 50 Ohm scope cable.
- Maximum full screen amplitude 1.6 Volts adjustable.
- Trace amplitude and spacing controls.
- 4 or 8 channel selector switch.
- 8 color coded input cable, 24" long with insulated alligator clips.
- External 9 VDC power supply included (Model MMAC-2).
- Size 6.25" x 3.75" x 2"
- BNC Output Cable Accessory (Model PSA-2 add \$14.95)

LOW COST CAPACITANCE METER MODULE, DM-8

Connect this high quality low cost Capacitance Meter Module, DM-8 to your digital Volt Meter and turn it into a Digital Capacitance Meter—the Low Cost Way!



Completely assembled and tested! Ready to use!

\$69⁹⁵

- Push to read range (button) from 1pF to 20,000µF
- Zero calibration control
- In one easy to use, self-contained package.
- Battery powered, with "push to read" battery saver circuit (9V batteries not included).
- Size 6.25" x 3.75" x 2"

REGULATED TRIPLE POWER SUPPLY, LOW PRICED!, DM-6

A fully assembled and tested power supply that provides a solid, fully wired triple power supply including fixed 5V @ 1 Amp, 5V to 15V @ 0.5 Amp, and 5V to 15V @ 0.5 Amp—all supplies regulated, short proof. Each supply has short indicator LED. Complete and ready for use in a durable (8" x 6" x 3 1/2") metal case.

\$99⁹⁵



FREE!!
NEW 1981
FALL
CATALOG
Exciting
new products!
Send today!!



ALBIA SATISFACTION WARRANTY:

FOR FAST AND DEPENDABLE DELIVERY SERVICE
IN CT, AK & HI CALL COLLECT (203) 467-5590

CALL TOLL FREE: 1-800-243-6953 9 A.M. to 5 P.M. E.S.T.

WE ACCEPT MASTER CHARGE, VISA AND AMEX CREDIT CARDS

Connecticut Residents add 7 1/2% Sales Tax • Prices shown in U.S. currency only. Foreign orders add 15%.


ALBIA ELECTRONICS INC

44 KENDALL ST. • P.O. BOX 1833 • NEW HAVEN, CT. 06508

CIRCLE NO. 2 ON FREE INFORMATION CARD

AmericanRadioHistory.Com

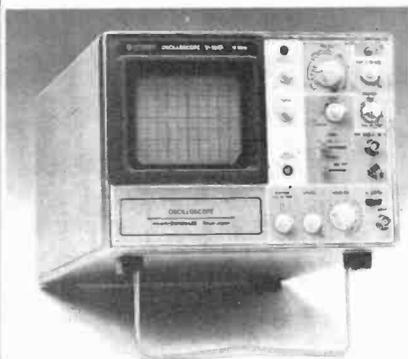HITACHI DC-15MHZ SINGLE-TRACE PORTABLE OSCILLOSCOPE AT THIS LOW, LOW PRICE



- CRT Display area Acceleration potential Intensity modulation 1308UB31 (5-inch, round shape) 8x10div (1 div = 9.5mm) Approx. 2kV Over 5Vp-p
- Vertical deflection Sensitivity and bandwidth 5mV/div—5V/div $\pm 5\%$, DC—15MHz, —3dB 1mV/div—1V/div $\pm 6\%$, DC—5MHz Typ. —3dB (Using x5 amplifier) 24ns Rise time Dynamic range More than 4div at 15MHz Input R and C Direct 1M Ohm, approx. 30pF Maximum input voltage 600Vp-p or 300V (DC + AC peak) Display mode Single-trace DC—500 kHz, 200mV/div X-Y operation Phase difference DC—10kHz 3°

- Horizontal deflection Sweep mode Auto, NORM, TV (+), TV (-)
- TV synchronization TV sync-separator circuit Internal 1 div (V sync-signal) External Over 1 Vp-p (V sync-signal)
- Trigger sensitivity

Frequency	Internal	External
20Hz—2MHz	0.5div	200mV
2—15MHz	1.5div	800mV

- Trigger slope = 0.2µs/div—0.2s/div $\pm 5\%$, 19 calibrated steps
- Sweep time 10 times ($\pm 7\%$)
- Sweep-time magnifier 100ms/div
- Max. sweep rate

- Amplitude calibrator Waveform 1kHz $\pm 10\%$ Typ. Square wave 0.5V $\pm 3\%$ Voltage
- Power requirements 100V (120/220/240V) $\pm 10\%$ 50/60Hz, 40W Approx. 275(W) x 190(H) x 400(D)mm
- Dimensions Approx. 8.5kg
- Weight 0—+40°C
- Ambient operation temperature

MODEL V-151B WITH 2 YEAR MFG. WARRANTY

ONLY **\$499⁹⁵**

WITH FREE DM-12 8 CHANNEL MULTIPLEXER A COMBINED VALUE AT LIST OF \$639.95 YOU SAVE \$140.00

If for any reason, whatsoever, you are not completely satisfied with your purchase, return it within 30 days of purchase date for a full refund— it's as simple as that! Shipping & Handling charges not refundable.

LOW COST HIGH FREQUENCY COUNTER



MODEL NO. DM-7

The Albia Model DM-7, 8 Digit High Frequency Counter is easy to use, switch selectable time base input by a single BNC, nothing to build!

- 5Hz to 550 MHz
- 8 big easy-to-read, 43" high Intensity LED display
- Crystal (± 3 ppm @ 25°) controlled 0.1 or 1.0 sec. gate times
- Convenient benchtop size (7" x 10" x 3") durable attractive case

COMPLETELY ASSEMBLED PRE-CALIBRATED PRE-TESTED

\$149⁹⁵

LOW OHM METER MODULE, DM-10



Measures resistance from 10 milliOhms to 20 Ohms. Now you can measure resistance down to 10 milliOhms with this low cost, easy to use DVM module. Check coil resistance, transformers, relays, chokes, printed circuit board copper paths and ground cables. Special zero balance control nulls out input cable resistance to insure accurate readings. Your DVM has to be set to 2V range during operation.

- Resistance range 10 milliOhms to 20 Ohms
- Zero Calibration control
- Battery powered (push to read battery saver circuit). Requires 1.9 Volt Battery (not included).
- Size 6.25" x 3.75" x 2" (Input cables not included or available)

\$69⁹⁵

FREQUENCY METER MODULE "5Hz to 100MHz", DM-11



Measure frequencies from 5Hz to 100MHz on your digital voltmeter with a resolution of 3 1/2 digits— easy to use— perfect for field service — lab testing — home hobbyist! Connect the DM-11 to your DVM, set the DVM to the 2VDC range, connect a signal to the DM-11 via a BNC cable (not included) and measure the frequency of any source. Hi Lo Range LED's insure fast accurate readings.

- Frequency Range 5Hz to 100MHz
- Input Impedance 1 MegOhm
- Input Sensitivity: < 100Hz < 80mV 100 Hz - 60MHz < 30mV > 60MHz < 70mV
- Size 6.25" x 3.75" x 2"
- External 9V DC power supply included. (Model MMAC-2)
- BNC Input Cable Accessory (Model PSA-2 add \$14.95)

\$69⁹⁵

POSTAGE & HANDLING

ORDERS	ADD
UP TO \$10.00	\$1.95
\$10.01 - \$25.00	3.75
\$25.01 - \$50.00	4.65
\$50.01 - \$100.00	6.45
ORDERS OVER \$100.00 WITHIN UNITED STATES	7.55



FREE ALBIA DESIGNERS TEMPLATE WITH EVERY ORDER RECEIVED

Now you don't have to spend a fortune to enjoy a complete woodworking shop.

The Shopsmith MARK V combines five major power tools into one unique, big-capacity unit.

Whether you're an experienced craftsman, a dedicated hobbyist, or a week-end "do-it-yourselfer," at one time or another, you've probably dreamed of owning a complete woodworking shop. A few hand-held power tools just aren't enough for most projects you'd like to try.

If you purchased the five separate tools woodworkers use most — table saw, vertical drill press, horizontal boring machine, disc sander and lathe — you could expect to pay *at least* a couple of thousand dollars. And even if you had the money, would you have enough space for them?

Save space, save money with the Shopsmith MARK V.

There's one answer that can solve both those problems — the Shopsmith MARK V. This remarkable piece of equipment is a single precision tool that combines all five of the major power tools in one unit that actually takes up less space than a bicycle... and that can be yours for about ONE-THIRD the price of the five separate units!

Outperforms individual tools

The MARK V's unique design not only gives you greater accuracy and more convenience — it allows you to do things you just can't do with other power tools.

This ingenious woodworking system combines a 10" table saw, a 16½" vertical drill press, a horizontal boring machine, a 34" lathe and a 12" disc sander — all powered by *one* rugged variable-speed motor.

After only about an hour's practice, you'll be able to change from one function to another in less than 60 seconds. And you'll be able to perform dozens of sophisticated woodworking operations, including edge sanding, spindle turning, and doweling. We call the MARK V "the tool to start with, the system you grow with," because with optional accessories, you can perform more

specialized operations, like mortising, routing, molding, and many others.

With the Shopsmith MARK V, the skill and accuracy are built right into the machine. It's so simple to operate that even if you're a beginner you'll soon be making your own furniture, cabinets, and gifts. In no time you'll be doing money-saving home repairs and impressive remodeling projects.

Mail the coupon today for your FREE Information Kit.

Find out more about this amazing 5-in-1 tool. Simply mail the coupon below and we'll send you a FREE Information Kit. Your Kit will include a booklet,

"What to Look For When You Buy Power Tools," PLUS all the details on the incredible MARK V. You'll also learn how you can actually use it in your home, for a full 30 days, *without risking a penny!*



1. It's a 10" table saw!



2. It's a 16½" vertical drill press!



3. It's a horizontal boring machine!



4. It's a 34" lathe!



5. It's a 12" disc sander!



Mail this coupon today!



Shopsmith Inc.

The Home Workshop Company
750 Center Drive
Vandalia, Ohio 45377

Dept. 354G



YES! Please send me my FREE Information Kit on the Shopsmith MARK V, including illustrated brochure and "What To Look For When You Buy Power Tools" booklet — PLUS all the details on how I can test-use the MARK V at home, without risk, for 30 days. I understand that this information is FREE and I am under no obligation.

Name _____

Address _____

City _____ State _____ Zip _____

©Shopsmith, Inc. 1981

CIRCLE NO 62 ON FREE INFORMATION CARD

COMPUTER BITS

By Carl Warren

High-End Systems (for Low-End Buyers)

TWO prestigious companies, Xerox and Hewlett-Packard, have added their names in the very-small-business computer field. Both manufacturers have introduced powerful word- and data-processing microcomputer systems featuring the versatile industry-recognized standard operating system, CP/M. Both systems are in the low (less

than \$3,000) to medium (\$10,000) price range.

The principal significance of these developments is that the professional systems approach has entered the world of small systems. For example, the Xerox 820 sports a full-screen display (80 × 24) with reverse video and full-screen mapping, a detachable full-function



The Hewlett-Packard HP-125 microcomputer system supports two RS-232C serial ports and employs two Z-80A microprocessors.

NEW!!! THE ELECTRIC MOUTH*



for S100, Elf II, Apple, TRS-80 Level II*

From \$99.95 kit

Now — teach your computer to talk, dramatically increasing the interaction between you and your machine.

That's right: the ELECTRIC MOUTH actually lets your computer talk! Installed and on-line in just minutes, it's ready for spoken-language use in office, business, industrial and commercial applications, in games, special projects, R&D, education, security devices — there's no end to the ELECTRIC MOUTH's usefulness. Look at these features:

- * Supplied with 143 words/letters/phonemes/numbers, capable of producing hundreds of words and phrases.
- * Expandable on-board up to thousands of words and phrases (just add additional speech ROMs as they become available).
- * Four models, which plug directly into S100, Apple, Elf II and TRS-80 Level II computers.
- * Get it to talk by using either Basic or machine language (very easy to use, complete instructions with examples included).
- * Uses National Semiconductor's "Digitalter" system.
- * Includes on-board audio amplifier and speaker, with provisions for external speakers and amplifier.
- * Adds a new dimension and excitement to programming: lets you modify existing programs and games to add spoken announcements of results, warnings, etc.
- * Installs in just minutes.

Principle of Operation: The ELECTRIC MOUTH stores words in their digital equivalents in ROMs. When words, phrases, and phonemes are desired, they are simply called for by your program and then synthesized into speech. The ELECTRIC MOUTH system requires none of your valuable memory space except for a few addresses if used in memory mapped mode. In most cases, output ports (user selectable) are used.

Spoken Material Included

one	eighteen	ai	dollar	inches	number	ss	c	l
two,	nineteen	cancel	down	is	of	second	d	u
three	twenty	case	equal	h	off	set	e	v
four	thirty	cent	error	kilo	on	space	f	w
five	forty	400hertz tone	feet	left	out	speed	g	x
six	fifty	80hertz tone	flow	less	over	star	h	y
seven	sixty	20ms silence	fuel	lesser	parenthesis	start	i	z
eight	seventy	40ms silence	gallon	limit	percent	stop		
nine	eighty	80ms silence	go	low	please	than	k	
ten	ninety	160ms silence	gram	lower	plus	the	l	
eleven	hundred	320ms silence	great	mark	point	time	m	
twelve	thousand	ceci	greater	meter	pound	try	n	
thirteen	million	check	have	mile	pulses	up	o	
fourteen	zero	oomma	high	multi	rate	volt	p	
fifteen	again	control	higher	minus	re	weight	c	
sixteen	ampere	danger	hour	minute	ready	a	r	
seventeen	and	degree	in	near	right	b	s	

"Elf II" and "The Electric Mouth" are reg. trademarks of Netronics R&D Ltd. "Apple" is a reg. trademark of Apple Computer Inc. "TRS-80 Level II" is a reg. trademark of Tandy Corp.

Continental U.S.A. Credit Card Buyers Outside Connecticut

CALL TOLL FREE 800-243-7428

To Order From Connecticut Or For Technical Assistance, Etc.,

Call (203) 354-9375

NETRONICS R&D LTD. Dept PE

333 Litchfield Road, New Milford, CT 06776

Please send the items checked below:

- S100 "Electric Mouth" kit \$99.95
- Elf II "Electric Mouth" kit \$99.95
- Apple "Electric Mouth" kit \$119.95
- TRS-80 Level II "Electric Mouth" kit \$119.95

Add \$20.00 for wired & tested units. All plus \$3.00 postage & insurance. Conn. res. add sales tax.

Total Enclosed \$ _____

Personal Check Cashier's Check/Money Order

Visa Master Charge (Bank No. _____)

Acct. No. _____

Signature _____ Exp. Date _____

Print _____

Name _____

Address _____

City _____

State _____ Zip _____

keyboard, a choice of 5.25-in. or 8-in. floppy disks, and a full range of CP/M-compatible software. Some very sophisticated communications features are provided, too. Specifically, the 820 supports the 872/873 Communication Server, which provides for *Ethernet* compatibility for future expansion of the machine. Because it is generally agreed that software is the primary ingredient in the success of any computer, Xerox is offering a version of Micropro's WordStar wordprocessing system, Sorcim's Supercalc electronic worksheet, and other CP/M-compatible packages.

The 820 is priced at \$2,995 for CRT, keyboard, 64K bytes of memory, and two 5.25-in single-density floppy disks. Adding the optional 40-cps daisywheel printer (Diablo Model 630) brings the price to \$5,895.

Although Xerox chose not to bundle any software into the basic package, it is offered at standard prices. For example, the word-processing package carries a \$500 price tag regardless of disk size, 8- or 5.25-in. CP/M is an extra \$200.

Hewlett-Packard's HP-125 CP/M system is \$6,960. This is a Z-80-based system with dual 5.25-in. disk drives, two RS-232C communication ports and an integrated 80-cps thermal printer. Unlike Xerox, Hewlett-Packard includes CP/M in the base price, but you should expect to pay extra for additional software. Among the software options offered by HP are: VisiCalc/125, \$200; Word/125, \$500 (a version of WordStar); Graphics/125, \$200 (a version of Personal Software's Visiplot package, designed for creating graphs and doing trend analysis); BASIC 80, \$325; Link/125, \$150; and a CP/M utility package, \$125.

HP, like Xerox, has allowed for communications applications and future growth. Hardware and software provisions have been made to permit the 125 to operate in the company's HP-3000 EDP network or other large mainframe systems.

The HP-125 employs dual Z-80A microprocessors and sports a full 64K bytes of RAM memory. One processor serves the computation requirements of the system, while the other handles the screen/terminal chores.

Xerox and HP have paid close attention to the human engineering needs of the intended user. The 820 and 125 use easy-to-understand menus to guide you in the use of the system(s). Moreover, specific functions such as screen scrolling are assigned individual keys.

Enter IBM. There are more introductions forthcoming, but from more traditional computer manufacturers. The long-awaited IBM entry is imminent, but it will not be based on the S-100 bus, nor will it be greeted with open arms as some "experts" have predicted. As evidenced by the 5110 and 5120, IBM (its position as undisputed leader in new high technology notwithstanding) is unable to offer the level of support required by the small-system user.

The IBM product is believed to be the system that has been under development at the General Systems Division in Boca Raton, FL. The unit reportedly is built around Intel's 8088 microprocessor and will use the operating system designed by Microsoft. This operating system is supposed to be like the CP/M system, and many believe that it may be CP/M 86, rather than the Unix-like Microsoft version. The system supposedly will support up to 256K bytes of RAM and employ dual-tandem double-density (96-tpi) floppy drives.


To support the lowest end of the personal computer spectrum, observers speculate that IBM will offer a stripped-down version for less than \$1,000 when the larger unit is introduced. Interestingly, both IBM systems are based on its 3101 terminal with add-ons.

Whatever the fate of IBM's entries into this market, software incompatibilities will apparently not be a problem.

Sources close to the computer giant say that agreements are in the making for the use of MBASIC, SuperCalc, dBase II, and a variety of other popular software products, including those of Personal Software, but neither IBM nor the suppliers would comment.

From the miniworld, you can probably expect to see low-end (less than \$1,000) entrants from both Digital Equipment and Data General. Whether or not these machines will be CP/M compatible is anyone's guess; right now no one will say.

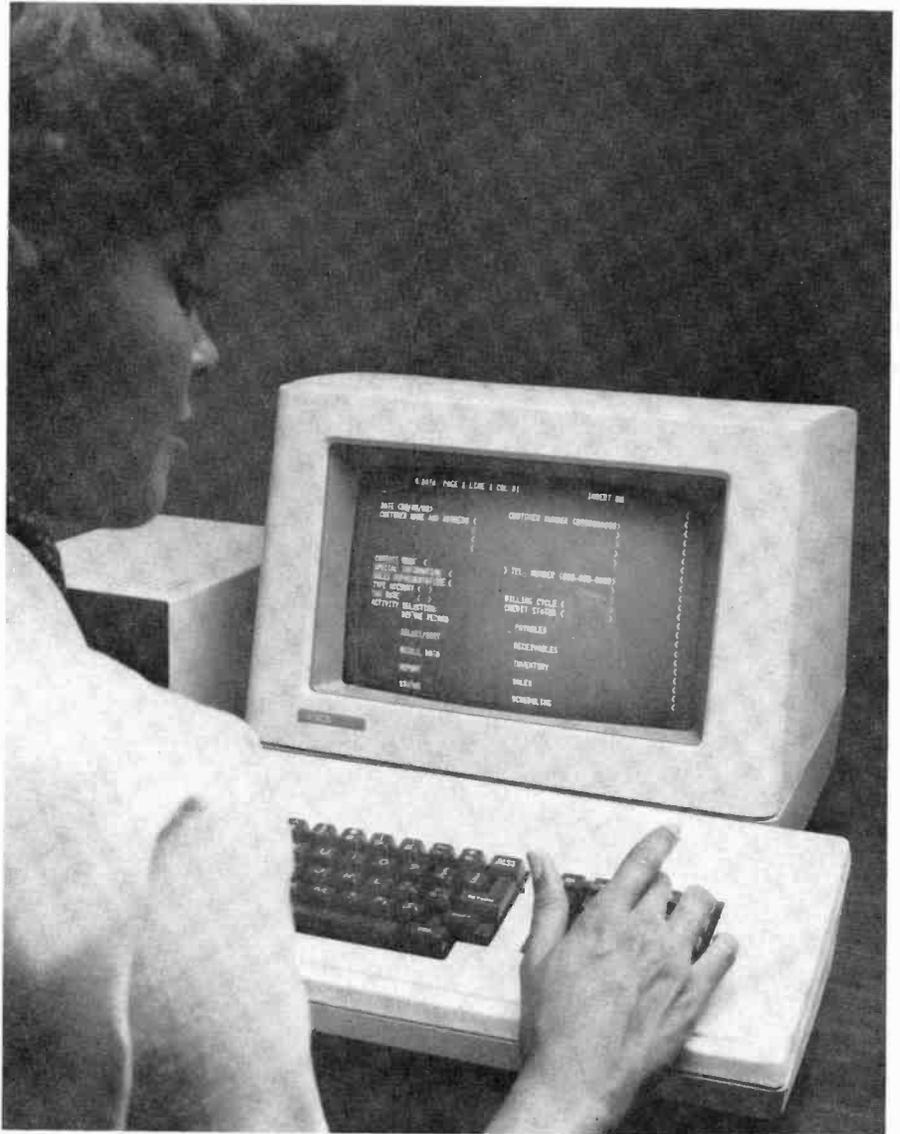Computer Networks. Due to typographical errors three numbers shown in the June, 1981 column are in error. These are 503-641-5510, 503-641-9029 and 817-776-1325. Please do not call these numbers as they are private residences. We apologize for the error. Also, the listing of 915-584-5393 is no longer available.




The Xerox 820 information system includes a Z-80 microprocessor, 64K bytes of RAM, detachable keyboard, and is CP/M compatible.

COMPUTER SOURCES

By Leslie Solomon
Senior Technical Editor

Hardware

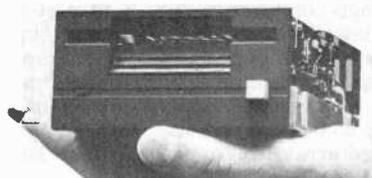3.5" Floppy Disk. The Sony 3.5-inch "Micro Floppydisk Drive" features 437.5K bytes double-density, single-side unformatted and 322.5K bytes formatted. The transfer rate is 500K bits/s,



latency is 50 ms, and access time track-to-track is 15 ms. The drive is 2"H × 4"W × 5.1"D and weighs 1.7 pounds. A special hard-cover diskette is used. Power dissipation is 7.5 watts continuous, 3.3 watts standby. \$400. Diskettes are \$5 each. Address: Sony Data Products Div., 15 Essex Rd., Paramus, NJ 07652 (Tel: 201-368-5000).

Computer Percussion. The Rhythm Box is a computer peripheral that synthesizes the sounds of seven different percussion instruments including bass drum, wood block, snare drum, short cymbals, long cymbals, hand clap, and tom-toms. It is programmed in Level II BASIC or assembly language using a single OUT instruction. It comes with two interface options; Model RBX-T (\$149) for the TRS-80 Model I Level II and the RBX-S (\$179) for other computers, and connects to any standard 9600-baud serial port with RS232 or 20-mA provisions. Address: Newtech Computer Systems, Inc., 230 Clinton St., Brooklyn, NY 11201 (Tel: 212-625-6220).

Single-Board Computer. The CPU-1 is an 8085-based system similar to the Intel 80/04. It operates at 3 MHz, and includes 256 bytes of RAM, 22 I/O lines, serial I/O port, programmable counter/timer, and two sockets for EPROM, expandable on board to 512 bytes of RAM, 44 I/O lines, and two clock timers. The EPROM can be 2708,

2716, 2758, or TMS 2716. It has power-on reset, manual reset and it supports the 8085 interrupt structure. The power supply is on board and only an external transformer is required. It also has a wire-wrap area. \$185. CPU-1A (512 bytes RAM, 44 I/O lines, two timers) is \$220. Address: Pragmatic Designs Inc., 950 Benicia Ave., Sunnyvale, CA 94086 (Tel: 408-736-8670).

6800 Trainer. "Trainer 1" is a two-board computer using a 6808 CPU with 1¼K RAM, provisions for 4K PROM and onboard I/O. It has an 8-digit display, hex keypad, Tbug 2K monitor, and hardware trace. Optional equipment includes KC cassette I/O, parallel I/O, serial (RS232/20 mA) port, crystal-controlled baud rate generator, and expansion cards. Starts at \$349. Address: Omnibyte Corp., 245 W. Roosevelt Rd (1-5), West Chicago, IL 60185 (Tel: 312-231-6880).

Apple Parallel I/O. The APIO allows 8-bit parallel access to Apple II and Apple II Plus systems. The board provides 16 bidirectional data lines, and four handshaking lines for two 8-bit bidirectional interface ports. The direction of the data lines is under software control. On-board PROM operates a printer and makes the board independent of Apple slots. \$109 assembled, \$79 kit. Address: SSM Microcomputer Products Inc., 2190 Paragon Drive, San Jose, CA 95131 (Tel: 408-946-7400).

Tiny BASIC Module. The K-8073 uses the INS8073 CPU with Tiny BASIC, and includes an RS-232 I/O port, cassette port, 8K EPROM, with one slot, 1K RAM, with internal expansion to 8K, STD Bus, Asynchronous Rec/Trans remote controller for single-wire data control and retrieval of 8-bit words from 128 remote slave stations. It has PPI with 24 bi-directional I/O lines, and a real-time clock. Unit is on a 4.5" × 6.5" card and requires 5 volts. \$388. Address: Transwave Corp., RD 1, Box 489, Vanderbilt, PA 15486 (Tel: 412-628-6303).

Color Printer Interface. The CPRINT module allows a Centronics-type parallel port for the TRS-80 Color Computer. Firmware allows all LLIST and PRINT #-2 outputs, a screen-print function can be initiated at any time, line width can be set, graphics in the LPVII can be accessed, page length can be set, and blank lines inserted between pages. The CPRINT module is a fully buffered 8-bit I/O port that can interface with any Model I/III which plug into the printer port. It is compatible with all versions of the Color Computer and requires no extra memory. \$49.95 Address: Micro-Labs, Inc., 902 Pinecrest, Richardson, TX 75080. (Tel: 214-235-0915).

CMOS Computer. The BASYS/1 is an all CMOS computer designed around

the CDP1802 CPU, with up to 2K of RAM and 8K of ROM. It has a flexible I/O circuit. Power requirements are 4 to 6 volts dc at 10 mA. Features include RS-232 or current-loop, parallel I/O, multiplexed I/O that can handle 10 digits and 80 keys, and a ROM monitor. A bus interface is provided. Price ranges from \$175 to \$300 depending on options. Address: Technical Micro Systems, Inc., 366 Cloverdale, Ann Arbor, MI 48105 (Tel: 313-994-0784).

Printers. The Sprinter-20 prints 20 characters wide, optionally sideways or upside down lines, at a normal print speed of 1.5 ips. Up to 5 different character sizes can be selected via ASCII control codes or 140 × n dot matrix in graphics mode. It measures 7.5" W × 5" D × 3" H (\$175). The Sprinter-40 prints 40 characters wide, at a selectable print speed of 2,3, or 4 ips. Wraparound facility permits printing of lines greater than 40 characters. In graphics mode, it has 280 × n dot matrix. It measures 10.5" W × 7.5" D × 4" H (\$295). Interface is parallel, 7-bit ASCII plus Strobe, Busy and Acknowledge, Serial RS-232 to 9600 baud, 1 or 2 stop bits. Address: Alphacom, Inc., 2323 So. Bascom Ave., Campbell, CA 95008 (Tel: 408-249-2152).

Apple Light Pen. The LPS II light pen allows high-resolution (280 × 192) graphics on an Apple II. It is compatible with all languages, and usable in every



screen mode. It provides 60-Hz coordinate generation, and can be installed on the Apple motherboard so no slots are required. \$285. Address: Gibson Labs., Building 10, 406 Orange Blossom, Irvine, CA 92714 (Tel: 714-559-8727).

Ham TRS-80. The "Terminall" converts any TRS-80 into a flexible amateur radio terminal. It contains the necessary interface, audio demodulation, AFSK tone generator and transmitter keying hardware. Plug it into the receiver headphone jack and copy Morse code, with code speed displayed on status line, Baudot, or ASCII. ASCII capability provides upper- and lower-case, control codes, even/odd/no parity, 6/7/8 data bits, 75/110 baud. Software is on cas-

sette or diskette and all you have to do is enter your call sign and time to initiate the program. Text can be typed while receiving or transmitting. Terminal T1 requires Model I with 16K RAM and Level II BASIC. Terminal T3 requires Model III with 16K RAM and Model III BASIC. Address: Macrotronics, Inc., 1125 N. Golden State Blvd., Turlock, CA 95380 (Tel: 209-667-2888 or 634-8888).

Software

Talking Dump. Designed for 6800/6809 SS-50 systems (and soon available for Radio Shack Color Computer), NEWTALK is a completely relocatable utility that does a byte-by-byte memory dump of a selected memory area and prints the output on screen as well as speaking it out through a loudspeaker. \$35 on disk or cassette. Address: Star-Kits, Box 209, Mt. Kisco, NY 10549.

Apple Games. "Three Mile Island" is a quick-response machine language game that simulates TMI in action. It features six full-color displays and auto/

demo and fast/normal modes (\$39.95). "The Best of Muse" includes five games with two three-dimensional maze puzzles, "Tank War," "Music Box," and six mini games. \$64.75. Both require an Apple with disk. Address: MUSE, 330 N. Charles St., Baltimore, MD 21201 (Tel: 301-659-7212).

Medical Software. Medirec is a total medical history and report preparation program for office forms, patient and family history, symptoms, diagnosis, and treatments. It can prepare referral requests, patient history summaries, and referral reports. The diskette records 550 visits (per diskette). Individual records can be recalled, linked and printed either whole or in parts. It also contains a full complement of office routines. It requires a 48K Apple, an 80-column printer, and two disk drives. A Corvus system is also available. \$199.95. Address: Charles Mann & Associates, Micro Software Div., 7594 San Remo Trail, Yucca Valley, CA 92284 (Tel: 714-365-9718).

Color Computer Utilities. The "Color Editor" designed for the Radio Shack Color Computer allows both upper- and lower-case features and will print via the RS232 port. It has change and search commands, and can copy or

move sentences or paragraphs to different locations (\$24.95). The "Color Assembler" is a 6809 type that supports all mnemonics and addressing modes along with standard assembler options and directives. It is a two-pass assembler (\$29.95). The Power Pack plugs into the interface slot and provides up to 6K additional RAM and a 2K monitor. A diagnostic cassette is included (\$159). Address: Computerware, Box 668, 1512 Encinitas Blvd., Encinitas, CA 92024 (Tel: 714-436-3512).

New Language. HI is a general-purpose microlanguage that fits in 3K bytes and features an incremental compiler using selective threaded-code techniques to produce portable ROM-able code. Data declarations allow character, byte, and integer types using upper- and lower-case symbolic names of unlimited length. It has fast integer math supported with decimal, hex, octal, or binary-bases; 14 statements allow multiple statements per line; 11 control structures allow input and timed input conditionals, single, double or multiple branch conditionals, pre- and post-loop testing, and machine-language calls. Five assignment modes provide implied assignment, multiple assignment, multiple equivalence, automatic dynamic type conversion, pointer referencing, indexed arrays, bidimensional files, string

M & M Electronic, Inc.

A Subsidiary of United Products, Inc.
2300 First Avenue
Seattle, Washington 98121
Phone (206) 682-5025

JUST \$4.95
This is just the thing for anyone who can't live without their **DESIGNER SYSTEM FOR BUSINESS PERSONS**.
* Removable disk, 16MB of RAM, 16K of ROM
* Includes all the tools you need to design your own business forms
* Includes all the tools you need to design your own business forms
* Includes all the tools you need to design your own business forms
* Includes all the tools you need to design your own business forms

JUST \$7.98 Each
The perfect way to let your quality show when your family can't see it. All new feature in terms of real value in a package.
* Includes all the tools you need to design your own business forms
* Includes all the tools you need to design your own business forms
* Includes all the tools you need to design your own business forms
* Includes all the tools you need to design your own business forms

Part #	Description	Price
810001	16MB RAM	\$1.50
810002	16K ROM	\$1.50
810003	16MB RAM	\$1.50
810004	16K ROM	\$1.50
810005	16MB RAM	\$1.50
810006	16K ROM	\$1.50
810007	16MB RAM	\$1.50
810008	16K ROM	\$1.50
810009	16MB RAM	\$1.50
810010	16K ROM	\$1.50

INTEGRATED CIRCUITS

Part #	Description	Price
710001	74181	\$1.25
710002	74182	\$1.25
710003	74183	\$1.25
710004	74184	\$1.25
710005	74185	\$1.25
710006	74186	\$1.25
710007	74187	\$1.25
710008	74188	\$1.25
710009	74189	\$1.25
710010	74190	\$1.25

DESIGNER SYSTEM FOR BUSINESS PERSONS

Part #	Description	Price
810001	16MB RAM	\$1.50
810002	16K ROM	\$1.50
810003	16MB RAM	\$1.50
810004	16K ROM	\$1.50
810005	16MB RAM	\$1.50
810006	16K ROM	\$1.50
810007	16MB RAM	\$1.50
810008	16K ROM	\$1.50
810009	16MB RAM	\$1.50
810010	16K ROM	\$1.50

HOW CAN WE SELL THIS STUFF SO CHEAP?
3.579545 MHZ Color Burst Crystal
Perfect for building a time base.
ONLY 50¢ each
10 / \$4.75
Call for larger quantity prices. (#B10003)

SELECTED PARTS

Part #	Description	Price
810001	16MB RAM	\$1.50
810002	16K ROM	\$1.50
810003	16MB RAM	\$1.50
810004	16K ROM	\$1.50
810005	16MB RAM	\$1.50
810006	16K ROM	\$1.50
810007	16MB RAM	\$1.50
810008	16K ROM	\$1.50
810009	16MB RAM	\$1.50
810010	16K ROM	\$1.50

CAPACITORS

Part #	Description	Price
810001	1000PF	\$1.50
810002	2000PF	\$1.50
810003	5000PF	\$1.50
810004	10000PF	\$1.50
810005	20000PF	\$1.50
810006	50000PF	\$1.50
810007	100000PF	\$1.50
810008	200000PF	\$1.50
810009	500000PF	\$1.50
810010	1000000PF	\$1.50

LEDS (DIODES/LED'S)

Part #	Description	Price
710001	74181	\$1.25
710002	74182	\$1.25
710003	74183	\$1.25
710004	74184	\$1.25
710005	74185	\$1.25
710006	74186	\$1.25
710007	74187	\$1.25
710008	74188	\$1.25
710009	74189	\$1.25
710010	74190	\$1.25

ASSORTMENTS

Part #	Description	Price
810001	16MB RAM	\$1.50
810002	16K ROM	\$1.50
810003	16MB RAM	\$1.50
810004	16K ROM	\$1.50
810005	16MB RAM	\$1.50
810006	16K ROM	\$1.50
810007	16MB RAM	\$1.50
810008	16K ROM	\$1.50
810009	16MB RAM	\$1.50
810010	16K ROM	\$1.50

ANQ...FREE GIFTS!
FREE: To the first 100 customers (who meet our terms) we will give a National Semiconductor Credit Card Calculator! Where else can you get a deal like this?
AND: To everyone else, MORE FREE GIFTS! Every package that M & M ships in September will get a Free pack of solder!

CONNECTOR/TERMINAL STRIPS

Part #	Description	Price
810001	16MB RAM	\$1.50
810002	16K ROM	\$1.50
810003	16MB RAM	\$1.50
810004	16K ROM	\$1.50
810005	16MB RAM	\$1.50
810006	16K ROM	\$1.50
810007	16MB RAM	\$1.50
810008	16K ROM	\$1.50
810009	16MB RAM	\$1.50
810010	16K ROM	\$1.50

RESISTORS

Part #	Description	Price
810001	1000PF	\$1.50
810002	2000PF	\$1.50
810003	5000PF	\$1.50
810004	10000PF	\$1.50
810005	20000PF	\$1.50
810006	50000PF	\$1.50
810007	100000PF	\$1.50
810008	200000PF	\$1.50
810009	500000PF	\$1.50
810010	1000000PF	\$1.50

SECRET

Part #	Description	Price
810001	16MB RAM	\$1.50
810002	16K ROM	\$1.50
810003	16MB RAM	\$1.50
810004	16K ROM	\$1.50
810005	16MB RAM	\$1.50
810006	16K ROM	\$1.50
810007	16MB RAM	\$1.50
810008	16K ROM	\$1.50
810009	16MB RAM	\$1.50
810010	16K ROM	\$1.50

RESISTORS

Part #	Description	Price
810001	1000PF	\$1.50
810002	2000PF	\$1.50
810003	5000PF	\$1.50
810004	10000PF	\$1.50
810005	20000PF	\$1.50
810006	50000PF	\$1.50
810007	100000PF	\$1.50
810008	200000PF	\$1.50
810009	500000PF	\$1.50
810010	1000000PF	\$1.50

ANQ...FREE GIFTS!
FREE: To the first 100 customers (who meet our terms) we will give a National Semiconductor Credit Card Calculator! Where else can you get a deal like this?
AND: To everyone else, MORE FREE GIFTS! Every package that M & M ships in September will get a Free pack of solder!

RESISTORS

Part #	Description	Price
810001	1000PF	\$1.50
810002	2000PF	\$1.50
810003	5000PF	\$1.50
810004	10000PF	\$1.50
810005	20000PF	\$1.50
810006	50000PF	\$1.50
810007	100000PF	\$1.50
810008	200000PF	\$1.50
810009	500000PF	\$1.50
810010	1000000PF	\$1.50

RESISTORS

Part #	Description	Price
810001	1000PF	\$1.50
810002	2000PF	\$1.50
810003	5000PF	\$1.50
810004	10000PF	\$1.50
810005	20000PF	\$1.50
810006	50000PF	\$1.50
810007	100000PF	\$1.50
810008	200000PF	\$1.50
810009	500000PF	\$1.50
810010	1000000PF	\$1.50

Into computers? Robotics?
Want to get started?

Take 6 great books for \$2.95

(values to \$94.70)

... and get one FREE!

All the latest info on software, hardware, applications, and theory at savings up to 75%. Plus, discounts on software, games, cassettes, disks ... and more!



Join now and get *How to Build Your Own Working 16-Bit Microcomputer* ... FREE!! (List \$4.95)

7 very good reasons to try The Computer Book Club ...

- **Reduced Member Prices.** Save up to 75% on books sure to increase your know-how
- **Satisfaction Guaranteed.** All books returnable within 10 days without obligation
- **Club News Bulletins.** All about current selections—mains, alternates, extras—plus bonus offers. Comes 10 times a year with dozens of up-to-the minute titles you can pick from
- **"Automatic Order".** Do nothing, and the Main selection will be shipped automatically! But ... if you want an Alternate—or no books at all—we'll follow the instructions you give on the reply form provided with every News Bulletin
- **Continuing Benefits.** Get a Dividend Certificate with every book purchased after fulfilling Membership obligation, and qualify for discounts on many other volumes
- **Extra Bonuses.** Take advantage of added-value promotions, plus special discounts of software, games, and more
- **Exceptional Quality.** All books are first-rate publisher's editions, filled with up-to-the-minute info



THE COMPUTER BOOK CLUB
Blue Ridge Summit, PA 17214

Please accept my Membership in The Computer Book Club and send the 6 volumes circled below, plus a free copy of *How to Build Your Own Working 16-Bit Microcomputer*. I understand the cost of the books selected is \$2.95 (plus shipping/handling). If not satisfied, I may return the books within ten days without obligation and have my Membership cancelled. I agree to purchase 4 or more books at reduced Club prices during the next 12 months, and may resign any time thereafter.

- 841 985 995 1045 1050 1053 1055 1062
1071 1076 1088 1095 1111 1160 1169 1187
1195 1200 1203 1205 1209 1229 1271 1275

Name _____ Phone _____
Address _____
City _____
State _____ Zip _____

(Valid for new members only. Foreign and Canada add 20%. Orders outside U.S. or Canada must be prepaid with international money orders in U.S. dollars. JPEC-981)

truncation, string length and random number operators, and array assignments in load and unload forms. Complete Z80 listing is \$24. **Address:** Systemed, Box 18, Mountain City, TN 37683 (Tel: 615-727-6000).

CP/M Utilities. "Unprotect" provides the original source code for any program that is saved in a protected format. An 8" diskette and CP/M 2.0 or later are required (\$70). "Undelete" restores a file just as it was before the kill or erase command, unless the directory entry has been overwritten. It allows a sector-by-sector inspection with selective restoration of "lost" data (\$45). **Address:** Systemation Inc., Box 75, Richton Park, IL 60471 (Tel: 312-481-2420).

ZX80 Group. Licensed hams using the Sinclair ZX80 or Microace now have a user net on single sideband. Contact Marty Irons, K2MI, 46 Magic Circle Drive, Goshen, NY 10924.

CP/M Unerase Utility. The UN-ERA program can be used to recover one or more ERAsed programs in a CP/M system. When entered, the program will recatalog the file back on the disk directory. It can also work its way through the directory and display each ERAsed file and allow the user to recat-

alog if desired. It also allows printing the user list. It works on both multi- and single-disk systems, and comes on either 5" or 8" diskettes. \$35 plus \$1.50 handling. **Address:** Elliam Associates, 24000 Bessemer St., Woodland Hills, CA 91367.

TRS-80 Users Group. The Computer Information Exchange is a nonprofit national TRS-80 user group that is introducing inexpensive new software for the TRS-80, besides allowing members to purchase hardware items on a group basis. For further information contact Computer Information Exchange, Inc., Box 159, San Luis Rey, CA 92068 (Tel: 714-757-4849).

Information Management. INF080 is an automatic information filing and management system for the TRS-80 Model I and Model III. It creates a virtual dictionary of information that can be quickly located. It supports continuously variable record input length and automatically extends disk files. The cross-referencing has an infinitely long data base, spanning any number of diskettes. Two global commands locate general or specific information over any number of diskettes. It is supplied in object code directly executable from TRSDOS. \$100 on data diskette, \$115

on TRSDOS diskette. **Address:** Bluebird Computer Software, 2267 23rd St., Wyandotte, MI 48192 (Tel: 313-285-4455).

TRS-80 Cross Assembler. These TRS-80-compatible assembler/editors cover the Intel 8048 (ASMB-48), the RCA 1802/1804 (ASMB-18), National COP400 (ASMB-CP4), Zilog Z-8 (ASMB-Z8), Fairchild/Mostek 3870 (ASMB-F8), and the AMI S2000 (ASMB-20). Each assembler shares a common operational structure. With minor exceptions, the assemblers feature instruction mnemonics and syntax as defined by the processor manufacturer. Source files can be saved on tape or disk, and programs must be off-loaded to target processor. Each development system is \$75 on cassette or MOD II diskette and requires a TRS-80 Model I or Model III with 32K RAM. **Address:** Allen Ashley, 395 Sierra Madre Villa, Pasadena, CA 91107 (Tel: 213-793-5748).

Invaders for Color Computer. Color Invaders is an arcade game in color and with sound with 8 levels of play for the TRS-80 Color Computer. It requires 16K and Power Pack. \$19.95. **Address:** Computerware, Box 668, Encinitas, CA 92024 (Tel: 714-436-35112).

PMC PERSONAL COMPUTER
Ideal for small businesses, schools, colleges, homes, etc. Suitable for the experienced, inexperienced, hobbyist, teacher, etc.

ONE YEAR GUARANTEE



SAVE DOLLARS

EG3000 Series

WITH NEW EXTRA KEYS!

ONLY **\$575**
POSTAGE \$20

- 16K user RAM plus extended 12K Microsoft BASIC in ROM
- Fully TRS-80 Level II software compatible
- Huge range of software already available
- Self contained, PSU, UHF modulator, and cassette
- Simply plugs into video monitor or UHF TV
- Full expansion to disks and printer
- Absolutely complete — just fit into mains plug.

SHARP PC121
\$190

COMPUTER POWER THAT ONCE FILLED A ROOM CAN NOW BE CARRIED IN YOUR POCKET!

- Programs in BASIC
- "QWERTY" Alphabetic Keyboard
- 1.9K Random Access Memory
- Long Battery Life.

TV GAME BREAK OUT KIT

Has got to be one of the world's greatest TV games. You really get hooked. Has also 4 other pinball games and lots of options. Good kit for up-grading old amusement games



MINI KIT PCB, sound & vision modulator, memory chip and de code chip. Very simple to construct **\$30.00**
OR PCB **\$6.00** MAIN LSI **\$17.00**

TTL SALE

74LS00 \$0.15	74LS74 \$0.45	74LS365 \$6.75
75LS04 \$0.15	74LS86 \$0.55	74LS373 \$2.20
74LS05 \$0.20	74LS93 \$0.90	Z80A \$5.50
74LS10 \$0.29	74LS157 \$1.20	Z80 \$4.20
74LS32 \$0.35	74LS165 \$1.75	REG. 7805 \$0.90

SOCKETS LOW PROFILE

14 PIN \$0.10	18 PIN \$0.15	24 PIN \$0.25
16 PIN \$0.10	20 PIN \$0.15	40 PIN \$0.30

10V Power Adapter 600ml. **\$6.90** UHF Modulators **\$9.90**

GET YOURSELF A NEW EPSON MX80 & MX70 PRINTER AND SAVE A FORTUNE

Price on application

Interface Cards for Apple, Pet, TRS80, and PMC — RS232 Interface Cards not necessary for parallel.

Full TRS80 **POSTAGE \$20**


ONE YEAR GUARANTEE



COMP PRO MIXER

Professional audio mixer that you can build yourself and save over \$200.

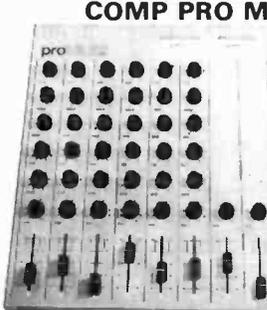Only **\$199** for complete kit.
power supply \$50.00
POSTAGE \$20



ACCESSIT AUDIO ADD-ONS

LOOK! MICROACE/SINCLAIR USERS

8K FLOATING POINT SUPER ROM PACK

WITH NEW MANUAL ONLY **\$35**

MICROACE/SINCLAIR VIDEO UPGRADE KIT

Only runs with NEW ROM (Smooth screen display) ONLY **\$29**

MICROACE/SINCLAIR 16K RAM PLUS EXPANSION BOARD

3 SLOTS WITH EXTRA POWER SUPPLY

16K ONLY **\$149** 4K ONLY **\$110**

MicroAce

A COMPLETE COMPUTER

A new generation of miniature computers

2K Kit ONLY **\$149**
Post and Packing FREE



Sinclair is a Registered Trademark of Sinclair Research Ltd.

MicroAce  Please make checks and money orders payable to **MicroAce** or phone your order quoting **Master Charge, Visa, Diners Club or American Express** number for immediate despatch. Add 6% Tax for Shipments inside California. **MicroAce**, 1348 East Edinger, Santa Ana, California, Zip Code 92705. Telephone: (714) 547 2526

IS YOUR HEART EXERCISING WHEN YOU ARE?



Everyone's talking about the importance of exercise. But how can you tell if it's doing your heart any good?

One way is to monitor your pulse rate. But if you've ever tried to use a pulse meter, you know this is easier said than done. No pulse meter on the market has been able to give you accurate readings conveniently while you exercise.

The crystal breakthrough

The trouble with most pulse meters is that they use an older, temperamental monitoring process. They read blood density through your skin with a projection of infrared light. The slightest movement, light, or pressure can throw them off completely.

The Genesis Exercise Computer overcomes this problem for the first time. It uses a patented crystal which picks up the actual sound waves of your pulse. Much more precise, and movement or light don't interfere.

It's the first truly accurate pulse meter you can conveniently wear while you exercise.

Readings on the run

Strap the compact, 3-ounce Genesis Exercise Computer to your wrist. Program it easily with your minimum, maximum, and resting pulse rates. And go.

Not only will Genesis give you an on-the-mark pulse reading at any second. It'll tell you if you're over or under your preset maximum or minimum.

90% of other pulse monitors force you to stop while taking readings, because movement upsets the computation. Genesis is unique in that it works while you move.

Why is this important? Two reasons. The first has to do with exercise. To strengthen your heart, doctors recommend 20-30 minutes of continuous exercise at 70% to 85% of

your maximum heart rate. This is your "training zone." The Genesis computer tells you how many minutes you've exercised at the right pulse rate and warns you if you're not working hard enough.

The other reason has to do with life itself. The Genesis computer will give an audible warning if you're pushing your heart dangerously. While you exercise—or during a stressful day at the office. If your doctor has warned you about your heart rate, you know right away if things are getting out of hand.

Medical chip

A medically designed micro-processor chip inside the Genesis Exercise Computer makes it smarter than any other pulse meter.

This is why it does much more than units costing 2-3 times as much. Genesis takes your pulse; lets you program your exercise zone simply and quickly; measures your cardiac recovery time, another key to fitness; paces you with a built-in metronome, if you like; and even tells time, in hours and minutes.

Reading your pulse properly isn't as simple as it might seem, because everyone's pulse is erratic. Your heart might have 5 fast beats, followed by 2 slow ones, 1 fast one, 4 slow ones, and so on.

The medical chip and patented Genesis sensor take this into account. Other less expensive devices "hold" an average of beats over a period of time (such as 20 seconds), which often gives distortedly high or low readings. Who wants to know what their pulse was 20

seconds

ago? Instead, Genesis picks up every single beat of your heart and makes the computations instantly.

Program your pulse

Imagine having a direct line to your heart. That's exactly what the Genesis Exercise Computer gives you. It's an important tool for the serious exerciser, the cardiac patient, or anyone who wants to monitor the key indicator of health, fitness, and longevity.

Just program the Genesis Computer to tell you exactly what you need to know about your pulse rate. It's as simple as a digital watch, if not simpler.

Want an idea of how exact it is? In a recent comparison with clinical EKG equipment, it was rated at 94% accuracy that even amazes doctors. Pretty incredible for a device you wear on your wrist.

Only \$159.95, 30 days free.

Units on the market costing \$350 to \$800 don't do nearly as much as the Genesis Exercise Computer. Plus they're awkward to use, and less accurate.

Which makes the low price of Genesis even more amazing. It's only \$159.95. Plus \$2.50 postage and handling.

Better yet, you can try it for 30 days absolutely free. If you're not satisfied, mail it back for a refund, no questions asked. Genesis is factory warranted for one year.

Send your check for \$159.95 plus \$2.50 delivery. Credit card holders: use our toll-free number.

**ORDER TOLL FREE:
(800) 423-6383
SUNSHINE EXPRESS**
4357 Chase Ave.
Los Angeles, CA 90066
In California Call (213) 822-7236



Sensor slips around finger, picks up every heartbeat while you're exercising.

EQUIPMENT AND TRAINING NO OTHER SCHOOL CAN MATCH.

**NTS HOME TRAINING INVITES YOU TO EXPLORE MICROCOMPUTERS,
DIGITAL SYSTEMS AND MORE, WITH STATE-OF-THE-ART EQUIPMENT
YOU ASSEMBLE AND KEEP.**

Without question, microcomputers are the state of the art in electronics. And NTS is the only home study school that enables you to train for this booming field by working with your own production-model microcomputer.

We'll explain the principles of troubleshooting and testing your microcomputer and, best of all, we'll show you how to program it to do what you want.

You'll use a digital multimeter, a digital logic probe and other sophisticated testing gear to learn how to localize problems and solve them.

Send for the full color catalog in the electronics area of your choice—discover *all* the advantages of home study with NTS!

NTS also offers courses in Auto Mechanics, Air Conditioning and Home Appliances. Check card for more information.

1.



We believe that training on production-model equipment, rather than home-made learning devices, makes home study more exciting and relevant. That's why you'll find such gear in most of NTS's electronics programs.

For instance, to learn Color TV Servicing you'll build and keep the 25-inch (diagonal) NTS/HEATH digital color TV.

In Communications Electronics you'll be able to assemble and keep your own NTS/HEATH 2-meter FM transceiver, plus test equipment.

But no matter which program you choose, NTS's Project Method of instruction helps you quickly to acquire practical know-how.

2.






Simulated TV Reception

4.

3.

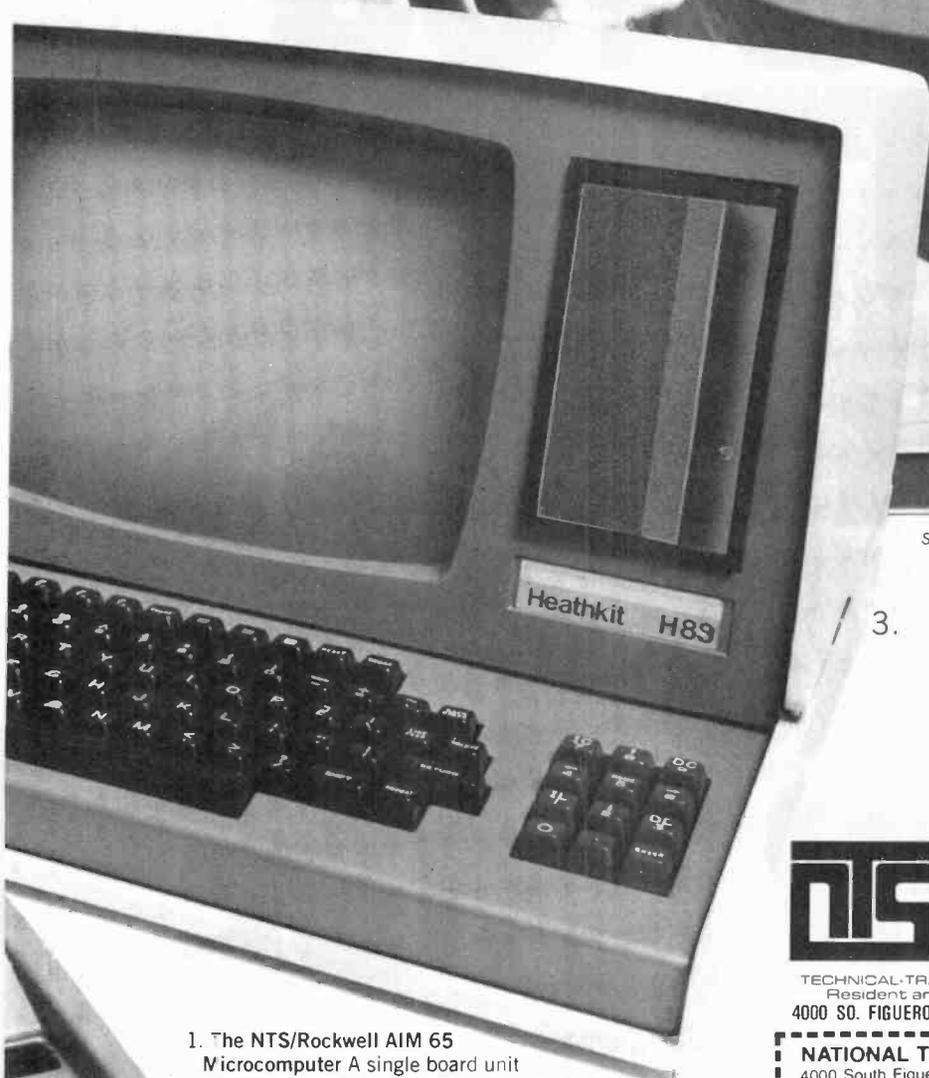

1. The NTS/Rockwell AIM 65 Microcomputer A single board unit with on-board 20 column alphanumeric printer and 20 character display. A 6502-based unit 4K RAM, expandable.
2. The NTS/KIM-1 Microcomputer A single board unit with 6 digit LED display and on-board 24 key hexadecimal calculator-type keyboard. A 6502 based microcomputer with 1K RAM, expandable.
3. The NTS/HEATH H-89 Microcomputer features floppy disk storage, "smart" video terminal, two Z80 micro-processors, 16K RAM memory, expandable to 48K.
4. The NTS/HEATH GR-2001 Digital Color TV (25" diagonal) features specialized AGC-SYNC muting, filtered color and new solid-state high voltage tripler rectifier.

NTS NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 SO. FIGUEROA ST., LOS ANGELES, CA. 90037



NATIONAL TECHNICAL SCHOOLS

4000 South Figueroa Street, Dept. 205-091
Los Angeles, California 90037

Please rush FREE color catalog on course checked below

- | | |
|---|---|
| <input type="checkbox"/> MicroComputers/MicroProcessors | <input type="checkbox"/> Auto Mechanics |
| <input type="checkbox"/> Communications Electronics | <input type="checkbox"/> Air Conditioning |
| <input type="checkbox"/> Digital Electronics | <input type="checkbox"/> Home Appliances |
| <input type="checkbox"/> Industrial Technology | <input type="checkbox"/> Color TV Servicing |

Name _____ Age _____
 Address _____
 Apt. _____ City _____
 State _____ Zip _____

- Check if interested in G.I. information.
 Check if interested ONLY in classroom training in Los Angeles.

WITH SOME TAPE YOU CAN'T TELL YOUR BRASS FROM YOUR OBOE.

When the oxide particles on recording tape aren't of a uniform size and shape, you can end up listening to distortion as well as music. The sounds of different instruments get blurred together, and your music loses its clarity.

At Maxell, every inch of our tape is checked and rechecked to make sure the oxide particles are perfectly uniform. Which means when you listen to music on Maxell tape, every instrument will sound perfectly clear.

So if you can't tell your brass from your oboe, try using our tape.



IT'S WORTH IT.

Maxell Corporation of America, 22 Oxford Drive, Morristown, N.J. 07974

BY RANDY CARLSTROM

DESIGNING WITH THE

8080 MICROPROCESSOR

Part 1: The Basic System

With the widely used 8080 as a model, the basic features of a central processing system are explored

IN ADDITION to its obvious application as the central processing unit (CPU) of a computer system, the microprocessor has found its way into a variety of products ranging from kitchen equipment to sophisticated laboratory data-acquisition systems. The key to this widespread utility is flexibility, which in turn comes from the microprocessor's unique ability to alter its internal logic in response to an external program. Since the response to inputs from the program is extremely rapid—on the order of a few microseconds—the processor can change its electrical configuration practically instantaneously, usually fast enough to convince a human correspondent that it is performing several activities simultaneously.

Given the speed and flexibility of microprocessors, and the fact that they are available at very reasonable prices, it is often economical to use a single processor rather than a great many simpler chips to synthesize logic functions, act as a controller, or the like. To accomplish this, however, it is necessary to understand the architecture of the processor, its needs in terms of support circuitry, how to program it, and how to interface it with the "outside world." Development of the necessary understanding is the goal of this multipart series.

Microprocessors vary in design, with

each design programmable only via its own set of instructions. The unit that will be covered in detail in this series is the 8080. Since this CPU is the grandfather of a growing family of processors, including the Z80, 8048, and 8085, all with a common internal programming language, most of the information will apply to the entire family as well. Instructions not used by the 8080 will not, however, be covered.

The Basic System. Like many processors and logic elements, the 8080 requires a small number of support ICs in order to function. An 8080 along with its support chips is called a *CPU module*.

The program that determines the internal states taken on by the CPU is supplied to it in the form of electrical signals. To generate these signals as required and in the proper order, the program must be stored in some form of "memory" device. These devices represent the binary digits (1, 0) by means of "on-off" switching devices or analogous circuit elements. The binary code in which program instructions are expressed is called *machine language*. Each microprocessor (or microprocessor family) has its own machine language.

Binary instructions or data that are not subject to change can be stored permanently in ROM (read-only memory).

Elements that are variable must be stored in RAM (random-access memory), which can be written, erased, and rewritten by the CPU.

To affect or control devices that interact with the outside world, the processor must deliver signals to them. It does this by means of an I/O (input/output) port. As the name implies, an I/O port can also deliver signals to the CPU from devices that sense external parameters.

Electrical signals representing data, instructions, and addresses (the locations of particular items in memory) pass between the CPU, memory devices, and I/O ports via a set of dedicated lines known collectively as *buses*. A typical bus (Fig. 1) also supplies dc operating power to the elements of the system.

Bus System. There are many versions of the bus system currently used, with the S-100 and SS50 being two of the most common. Although different mechanically, they all contain three major elements: the address bus, the data bus, and the control bus. (Figure 1 does not show the power supply lines and common ground usually carried on the bus system.)

In most systems, there are 16 lines in the address bus, thus enabling 2^{16} or 65,536 (64K) unique addresses. In an 8-bit system, there are 8 lines on the data

bus, allowing 2^8 or 256 data combinations. The control bus carries all system synchronization signals including the "clock" that keeps all CPU module events in step.

Memory. A computer memory is formed from a large array of semiconductor elements, each capable of storing a single binary 1 or 0, organized into groups of *bits* (short for "binary digits") often called *words*. The number of bits in each word is determined by the size of the CPU *registers* (storage locations in-

ternal to the microprocessor) and the number of data lines. A typical RAM arrangement is shown in Fig. 2. A memory word of eight bits is often referred to as a *byte*. Each byte represents one of 2^8 or 256 unique values (0-255). As the 8080 microprocessor uses this memory structure, it is considered a byte-oriented device.

Each memory location contains one word of memory bits, and is identified by a unique number, or *address*, assigned to it. The CPU gains access to the contents of any memory location by

means of its address. A memory word may represent the encoded form of an instruction, or may be data to be processed by the CPU.

The CPU has control of memory in the sense that it can read data and instructions from memory and write data back into memory. Only when the CPU receives a direct memory access (DMA) signal via the control bus does it relinquish control of memory. DMA allows a high-speed device such as a magnetic disk to gain access to memory and control it. As noted earlier, memory that can be read and written or altered is termed read/write memory, or random-access memory (RAM). Memory that can be read, but not altered by writing, is termed read-only memory (ROM).

Input/Output. To the 8080, the outside world may consist of up to 256 input and 256 output devices. These are usually referred to as peripherals, and may include keyboards, printers, displays, etc. Each peripheral communicates with the CPU by exchange of data bytes sent via its associated I/O port and the data bus (Fig. 3). Each peripheral is assigned an address from 0 to 255, much as each memory location is assigned an address. The portion of the I/O system that actually conditions data for input and output is known as the *interface* and generally there is one interface for each peripheral. The use of a port for input or output is done under program control.

Communication between the computer and a peripheral is done in one of two formats—serial or parallel. In parallel data transfer, all eight bits of the data byte are handled simultaneously. This permits rapid movement of data. In serial transfer, data is handled bit-by-bit instead of a byte at a time. This is slower, but has the advantage of using simple hardware (for example, a two-conductor cable or a telephone circuit instead of a multiconductor bus). When two computers exchange data via, say, an intercom line, the parallel data from buses of both computers is converted to serial form and transmitted bit-by-bit down the cable. The IC that performs the conversion from parallel to bit-serial form (and vice versa) belongs to a family of components known as UARTs (Universal Asynchronous Receiver-Transmitter). If used, the UART is part of the computer's I/O interface since it is used for conditioning data for input and output.

There are two basic types of serial communication—RS232 and what is called the 20-mA current loop. Basically, RS232 is a voltage circuit where a logic 0 is a positive voltage, and a logic 1 is a negative voltage. The newest version

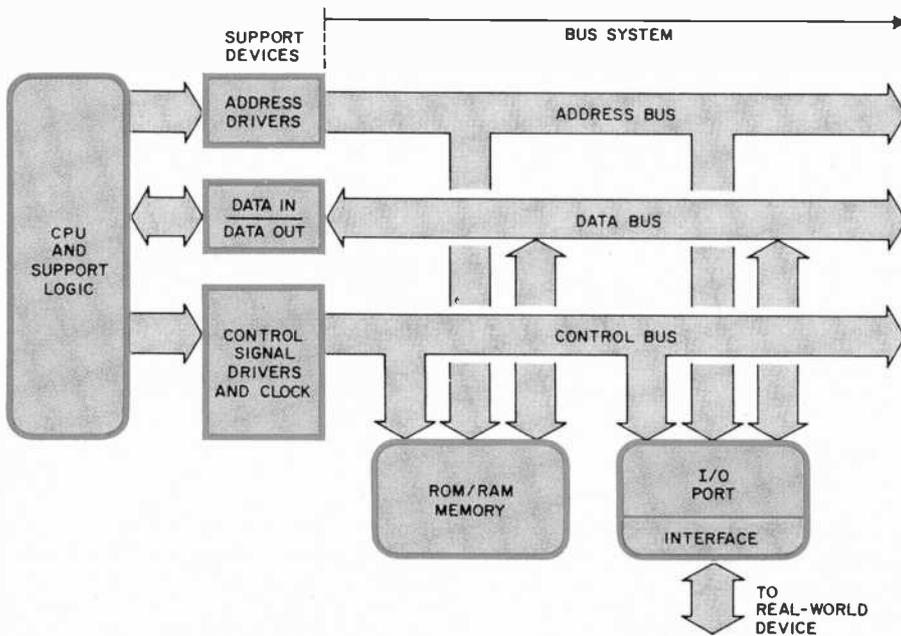


Fig. 1. A typical bus system contains three major elements: address bus, data bus, and control bus.

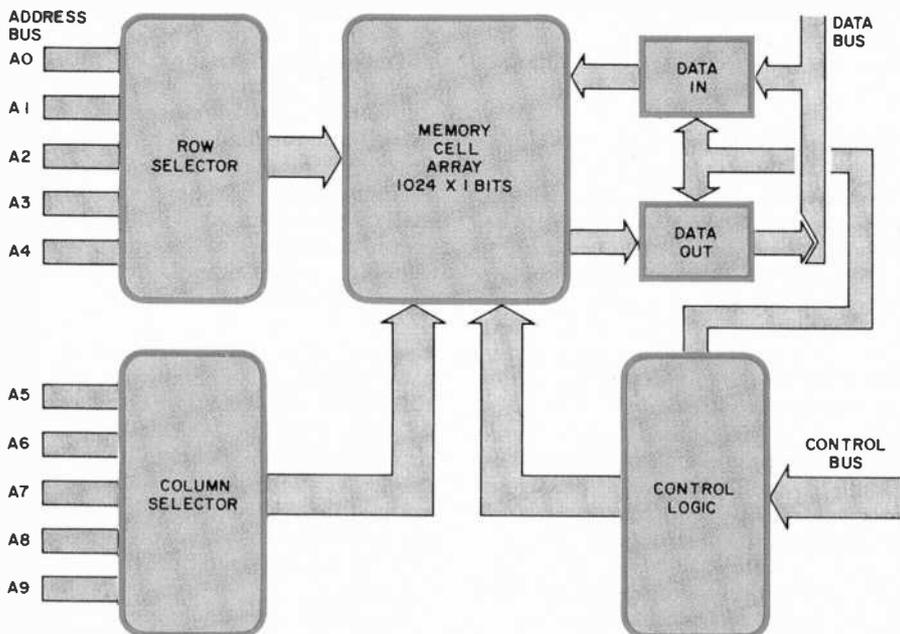


Fig. 2. Arrangement of a 2102 random-access memory. Eight of these are needed for 1024 by 8 bits.

of this voltage interface is RS422—which uses balanced transmission lines and differential current sensing to eliminate noise. The other commonly used serial port is the 20-mA current loop in which a flow of 20 mA in the series circuit produces a logic 1 while an absence of current denotes a logic 0. Both of these serial ports are controlled by a baud rate generator that “clocks” the operational speed of the port. Most peripherals use either the RS232 or 20-mA loops for communication.

Program Interrupt I/O improves the efficiency of CPU operation while data is being transferred to or from a peripheral that is many times slower than the CPU itself. Consider a computer processing large amounts of data, portions of which are to be output to a printer. When the peripheral is ready for data, it

signals the CPU through a program interrupt. When the CPU acknowledges the interrupt, it completes the current instruction being executed in the main program and then automatically branches to a routine that will output the next data byte. After the byte is output to the printer, the CPU returns to where it left off in the main program. The 8080 is capable of handling up to eight interrupts from eight I/O devices using a special instruction of its instruction set. Data input is similarly handled.

Three-State Logic. There can be many peripherals connected to, and communicating along, the same bus lines. Thus, unless some form of “traffic control” is used, confusion can reign. Keeping order is the purpose of the three-state devices, shown in Fig. 4.

Simply, a three-state device can be thought of as an electronic switch connected between each bus line and its associated logic. When the switch is closed, the associated logic can accept or deliver signals to the bus. But, when the switch is open, the bus does not “see” the logic—in effect, the logic does not exist for the bus.

Programming. A program for a computer or processor consists of a sequence of operational instructions stored in memory. Each instruction enables a single elementary operation such as the movement of a data byte, an arithmetic or logical operation on a data byte, or a change in instruction execution sequence. The set of all instructions common to a given CPU is referred to as its *instruction set*. The size of the instruction set is a measure of the CPU’s capabilities. Another such measure is the length of the binary words the CPU can work with. Generally speaking, the larger the instruction set, or word size, the more powerful the CPU. The 8080 (an 8-bit CPU with 72 instructions) is thus more powerful than the 4040 (a 4-bit CPU with 60 instructions). Some microprocessor instruction sets may approach 200 instructions in length.

A program is stored in memory (RAM or ROM) as a sequence of bytes that represent the instructions. The memory address of the next instruction to be executed is held in an internal register of the CPU called the *Program Counter*. Early in the execution phase of each instruction, the program counter is automatically advanced to the address of the next sequential instruction in memory. Thus, program execution proceeds sequentially (i.e. memory location 213 is executed after location 212 is executed, etc.) unless a transfer-of-control, or **BRANCH** instruction (8080 JUMP, CALL, or RETURN) is executed, which causes the program counter to be set to a specified memory address. Program execution would then continue sequentially from this new memory location. The JUMP instruction specifies the address to be jumped to, which can be anywhere in memory. During execution of a JUMP, the CPU replaces the contents of the Program Counter with the address contained in the JUMP instruction.

Subroutines. A special type of jump occurs when the stored program CALLS, or accesses, a subroutine (a program within a program). Usually, a subroutine is a set of instructions that must be executed repeatedly in the course of running the main program. Algorithms that calculate mathematical functions and routines to input or output data to a peripheral device are often programmed as subroutines. The subroutine type of

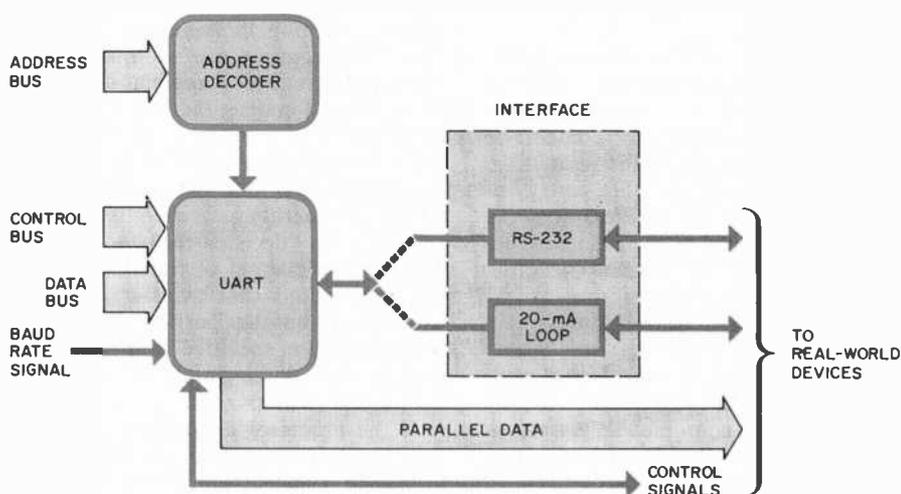


Fig. 3. Each peripheral communicates with the CPU through an associated I/O port and data bus.

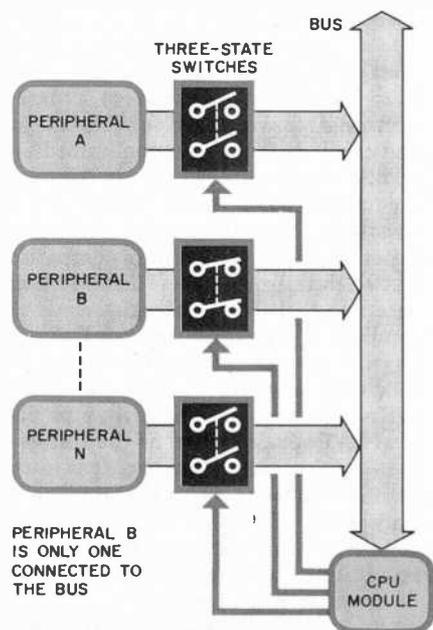


Fig. 4. A three-state device is an electronic switch connected between each bus line and associated logic.

EAST/ WEST MEGA SALES CO

SPECIAL OF THE MONTH!



**EPSON MX-80
PRINTER**
\$469

INTERFACES
IEEE \$55, TRS*80 \$35,
APPLE INTERFACE +
CABLE \$90, RS* 232 \$70



APPLE II PLUS 48K
\$1189



ATARI 800 32K
\$769



**RADIO SHACK
16K Level II Model 3**
\$834

NEC 5510 SPINWRITER	\$2495
INTERTEC SUPERBRAIN	
64K RAM	\$2799
OKIDATA MICROLINE - 83	\$ 769
OKIDATA MICROLINE - 80	\$ 399
APPLE DISK	
w/3.3 DOS Controller	\$ 545
APPLE DISK w/o Controller	\$ 435
BASE II Printer	\$ 599
DIABLO 630	\$2099
w/Tractor Option	\$ 245
HAZELTINE 1420	\$ 799
NORTHSTAR HORIZON 32K QD	\$2975
ATARI 400 16K	\$ 349
RADIO SHACK 64K Model 2	\$3245
ANADEX DP - 9500	\$ 1295
NEC MONITOR	\$ 229
TELEVIDEO 912C	\$ 669
TELEVIDEO 920C	\$ 729
TELEVIDEO 950	\$ 959
ATARI 825 Printer	\$ 619
ATARI 850 Interface	\$ 139
Or both together	\$ 749
ATARI 810 Disk	\$ 449

**TWO WAREHOUSE LOCATIONS
TO ENSURE FAST DELIVERY!**

EAST COAST

1-800-556-7586

12 Meeting Street
Cumberland, RI 02864
1-401-722-1027

WEST COAST

1-800-235-3581

3353 Old Conejo Road
Newbury Park, CA 91320
1-805-499-3678
CA. 1-800-322-1873

MEGA SALES CO

8080 microprocessor

jump requires the CPU to store the contents of the program counter at the time the jump occurs (when the CALL instruction is executed). This enables the processor to resume execution of the main program after the last instruction of the subroutine has been executed.

The processor has a special method of handling subroutines to insure an orderly return to the main program. When the CPU receives a CALL instruction from memory, it advances the Program Counter to the address of the next sequential instruction, and saves the Counter's contents in a special memory area known as the *Stack*. The latter holds the memory address of the instruction to be executed after the subroutine is completed. The processor then loads the address specified in the CALL instruction into its Program Counter. Consequently, the next instruction that is to be executed will be the first step of the subroutine.

Normally the last step of any subroutine is a RETURN instruction. When the processor executes the RETURN instruction, it replaces the current contents of the Program Counter with the address contained on the "top" (last entry) of the Stack. Since this address was the one originally saved by the CALL instruction, the processor will resume execution of the calling (main) program at the point immediately following the original CALL instruction. Note that this operation is very similar to executing a JUMP instruction, the difference being that the JUMP address is contained in the Stack area rather than in the JUMP instruction itself.

A subroutine may CALL another subroutine. This is called "nesting subroutines." If the microprocessor being used has a Stack for storing RETURN addresses, the maximum depth of nesting subroutines is determined solely by the depth of the Stack itself. So if the Stack has space for saving five return addresses, then five levels of subroutines can be accommodated.

Microprocessors have different methods of maintaining their Stack. Some store the RETURN addresses within registers in the processor, but this limits the levels of subroutine nesting. Others, such as the 8080, use a reserved area of RAM for the Stack and maintain a *Stack Pointer* (an internal register of the CPU) which contains the address of the most recent Stack entry; *i.e.*, the Stack Pointer always "points" to the top of the Stack. This type of Stack may be looked upon as a last-in-first-out (LIFO) memory, and allows virtually unlimited subroutine nesting.

Flags. The CPU has a set of flags, or internal flip-flops that are set or cleared (*i.e.*, set to a logic 1 or 0, respectively)


depending upon the results of certain instructions as they are executed. Two flags of the 8080 are: The "Zero Flag," which is set if the accumulator is 0 (actually 00000000 binary), and the "Carry Flag," which may be set when an arithmetic instruction causes the accumulator to overflow (*i.e.*, carry or borrow from an addition or subtraction). In most microprocessors there are other flags besides these. The 8080 has a total of five.

Most processors have instructions available that will store the accumulator and other general-purpose registers and flags on the Stack temporarily. Likewise, there are instructions available to reload the general-purpose registers and flags with data contained on the top of the Stack. This allows the contents of the registers and flags to be saved so that they may be used in another activity, as for example, a subroutine. Just before returning to the main program from a subroutine, the subroutine will restore the registers and flags it used (assuming, of course, that the same registers and flags were saved on the Stack prior to using them in the subroutine).

Let's go over one last concept of a CPU's instruction set, which gives the computer its "decision-making" power. This is a special set of transfer-of-control instructions that transfer program execution to another portion of memory if the condition specified in the instruction is met. An example is the 8080 instruction JUMP-IF-ZERO.

If the processor encounters a conditional transfer-of-control (or "conditional branch") instruction, it checks to see if the specified condition is met. The "condition" is always related to one of the flags. In the case of JUMP-IF-ZERO, program execution is transferred to the JUMP address contained in the instruction in the same manner as the unconditional JUMP if the Zero Flag is set. If the Zero Flag is not set (cleared), program execution assumes its sequential flow and executes the instruction immediately following the JUMP-IF-ZERO. A processor usually has a set of "Compare" instructions, that set and/or clear flags depending upon the result of comparison of two data words (the 8080 can compare two registers, or a register and the contents of a memory location). A conditional branch instruction will often follow a Compare instruction, so that the proper execution path may be chosen (the decision) based on the results of the flags from the Compare. It is in this manner that the CPU makes its "logical decisions." The 8080 also has various conditional calls and conditional returns in addition to the conditional JUMPS in its instruction set. ◇

(To be continued next month)

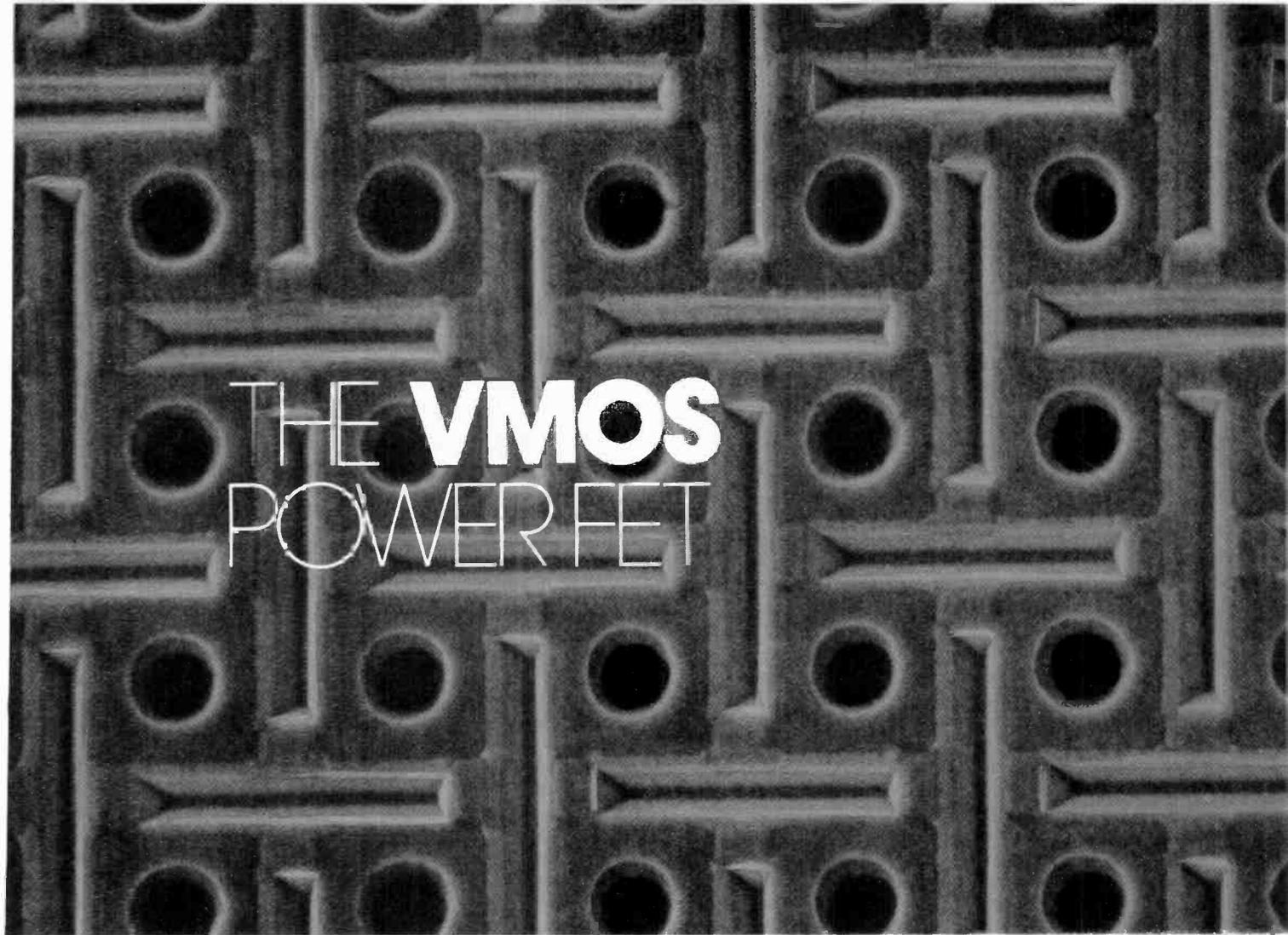

THE VMOS POWER FET

An up-and-coming rival to bipolar devices, VMOS offers advantages in circuit simplicity and improved performance

BY GARY McCLELLAN

VMOS power FETs are being designed into more and more electronic equipment, promising better performance, using less support circuitry, and permitting savings in cost. So far, they have replaced bipolar power transistors in some switching power supplies and audio amplifiers, with applications in power switching and power conversions soon to come.

Compared with its bipolar counterpart, a VMOS power FET has numerous advantages: its input impedance is higher, its bandwidth wider, and its inherent linearity greater. In addition, its temperature coefficient of gain is negative. That is, with a fixed level of drive at its gate, a VMOSFET conducts less and less current as it gets hotter.

Of course, VMOS devices offer a few

tradeoffs to challenge the circuit designer. For one, the gate saturation voltage of the VMOSFET runs somewhat higher than that of an equivalent bipolar device. Second, the relatively high gate capacitance (500-800 pF) means that the input will tend to draw appreciable current at the higher audio frequencies and beyond.

Finally, there is the matter of cost. VMOS devices cost more, but, according to designers, the reductions in support circuitry that they allow can make them in the long run, a better bargain than bipolar.

Typical Applications.

Power Supplies. When the series-pass stage consists of several bipolar devices in parallel, at least two power resistors

per transistor are required to prevent the devices from sharing the load current unequally should their temperatures differ. With the negative temperature coefficient, VMOS devices are free of this "current-hogging" tendency and require no power resistors. Another bonus of VMOS is that very high input impedance, makes the high drive currents that bipolar power transistors would require unnecessary. As a result of this, driver circuits that have lower power ratings and thus are less expensive to fabricate can be used.

Switching power supplies also benefit from VMOS. While many bipolar power transistors—especially the rugged ones—have a bandwidth of 2 or 3 MHz, VMOS devices can operate to 30 MHz and above. Because the VMOS devices

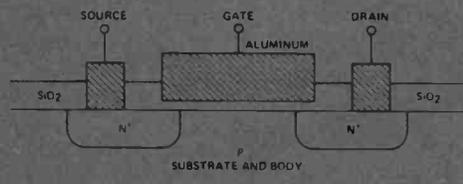


Fig. 1. Cross section of a conventional MOSFET.

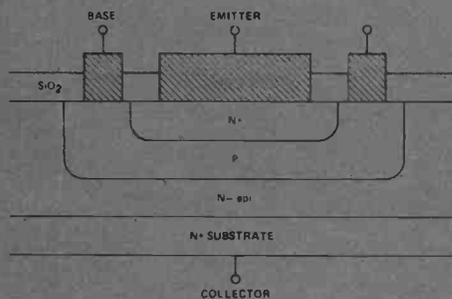


Fig. 2. A double-diffused epitaxial planar transistor.

switch faster, less energy is dissipated in them, and that improves efficiency. The higher switching frequencies made possible—up to 500 kHz as opposed to 100 kHz with bipolars—allow the use of smaller power transformers and output filter capacitors.

Audio Amplifiers are improved by VMOS technology and several commercial products using these devices are available. Here the VMOS devices replace the bipolar power transistors in the output stage. Because of the high-impedance VMOS inputs, less drive power is required by the output stage. That means that the driver stage can use lower-cost, lower-powered components.

Having a more linear operating characteristic, VMOS devices produce inherently less distortion. They are also free of the tendency of bipolar devices to "stick" to the power supply rails, and they come out of saturation faster with no extra drive current required. The result is a "cleaner" power amplifier. Another advantage of VMOS devices in audio amplifiers, is the freedom from "second breakdown," basically a situation in which momentary overvoltage or overcurrent will cause the device to heat up, draw more current, and then heat up some more, until it breaks down.

R-F Amplifier circuits such as those found in transmitters are likely places for VMOS technology. One of the first

applications for the VMOS power FET was in the final amplifier stage of a radio transmitter. The ease with which the devices can be connected in parallel to obtain greater output power, the reduced drive power required, and the wide frequency range make VMOS a natural for transmitter (r-f) applications. At least one VMOS manufacturer claims the devices can tolerate infinite VSWR without destruction! (This corresponds to a situation where the user attempts to transmit without the antenna load connected.) Usually this subjects the output r-f stage to excessive power dissipation. Freedom from second breakdown makes VMOS devices better able to tolerate such abuse.

VMOS is also making inroads in double-balanced mixer circuits, normally a low-power receiver application. Because of their approximately square-law transfer characteristics, VMOS devices deliver more of the desired mixer products and fewer troublesome high-order products, providing more overload margin.

Power-switching applications for VMOS include control of displays, solenoids, and motors. Conventional designs use transistors in most low-power applications and change to SCRs and relays for high power. A good example of a VMOS power switching application lies in display control. At the present time, most display interfacing is done with

inexpensive low-power transistors. If CMOS logic is used, however, it may be necessary to buffer the CMOS signals (which are low current) to the higher current requirements of the driver transistors. With VMOS, no buffering is required; in fact, one CMOS output can drive 100 or more VMOSFETs to the point of saturation!

VMOS can be used to advantage in controlling motors and solenoids, which pose difficulties because of the voltage transients when the current through an inductive load is interrupted. With conventional bipolar transistors, it is necessary to use very high-voltage devices or special networks to suppress the transients. Neither solution is cheap, and suppression networks reduce performance in high-frequency applications. Since VMOS devices are free from second breakdown, and can withstand back emf better, lower voltage FETs can be used and suppression networks simplified. In some low-power circuits, the traditional diode across the motor or solenoid can be removed.

For the area of power control in which SCRs and relays are presently used, VMOS shows promise. Even now, devices to handle high-voltages and high currents are under development. The future will tell whether VMOS will substitute for SCRs and relays, but 450-volt devices are already being advertised.

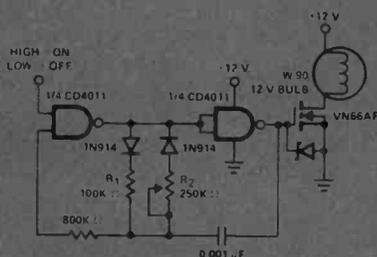


Fig. 5. A simple lamp dimmer circuit.

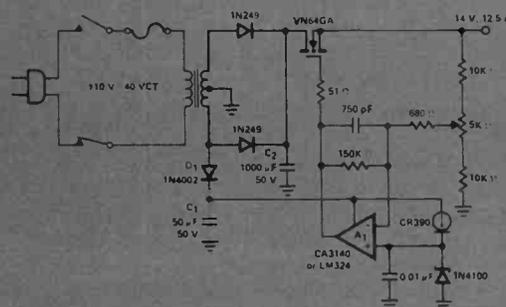


Fig. 6. An automatic battery charger.

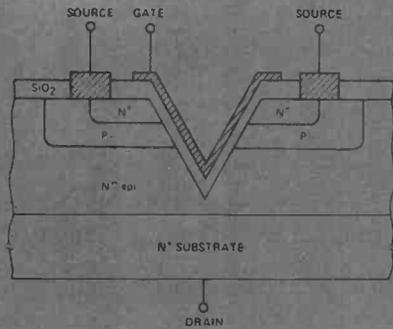


Fig. 3. Cross section of a VMOS channel.

Anatomy of a VMOSFET. Although it would appear that a VMOS power FET would just be a conventional MOSFET on a larger scale, this is not the case. Such a device could be built, but it would be costly and inefficient. Figure 1 shows a cross section of a conventional MOSFET "die," stripped of all nonessentials. Several things prevent this FET from being used effectively for power handling, among them the fact that the current flow is horizontal through the substrate of the device. This is due to the horizontal positions of the drain and source connections, and the relatively great distance between their electrical connections. Both of these cause high resistance—and loss.

As a result of the characteristics of the semiconductor material, current densities are lower when current flows horizontally, and power dissipation is increased. A conventional bipolar power transistor die is shown in Fig. 2. Note that the emitter and collector are in a vertical plane. Because of this arrangement, current densities are higher, and more current can flow between these two points. Since the collector is also the substrate, the die can be thermally bonded to a heat sink for cooling. This is why TO-3 power transistors have the collector connected to the metal case.

The VMOS power FET is a variation on the vertical theme used by conven-

tional power transistors, but it has some key differences. As shown in Fig. 3, four vertical layers are used, with a V-shaped channel etched in the material (which gives the VMOS its name) as the gate connection. A layer of silicon dioxide (SiO_2) insulates the conductive gate channel from the semiconductor materials, and gives the device its high-impedance characteristics. The source connection rests over the n and p materials, and provides the remaining power connection. These are the basics of the fabrication of the VMOS device. In practice, many "V" channels and source connections are paralleled on the die to produce the high current capability.

In use, the drain and gate are biased positive with respect to the source. The insulated gate produces an electric field, which allows the n -type material next to it to permit electrons to travel through the layers from the source to the drain. Increasing the field intensity of the gate (raising its voltage) increases its influence on the n -type material, causing a greater current flow. Conversely, reducing the gate field intensity reduces the source-to-drain current flow.

There are many advantages inherent in this type of construction. Since the substrate forms the drain connection, there is one less connection on the top of the die. As a result, the die can be made smaller. Also, since the drain connection

is so large, saturation resistance can be made very low. This means the completed VMOS power FET can be inexpensive (small die) and handle high power (large drain surface). Another benefit is that each V groove creates two channels, one on each side of the groove, so current density can be doubled. In other words, the VMOS devices can have high sensitivity, with shorter length channels, than conventional MOSFETs. For example, the standard MOSFET needs at least a 5-micrometer channel. VMOS devices, on the other hand, require only about 1.5 micrometers for good results, and shorter V grooves mean less stray capacitance and improved high-frequency performance. The 2N6657 VMOS power FET, for example, switches 1 ampere on or off in 4 nanoseconds. That's 10 to 200 times faster than a bipolar power transistor!

Finally, the VMOS power FET has built-in, high-voltage capabilities. This is because of the n -epi (taxial) layer, which absorbs the depletion region from the pn junction above it, thus acting as a highly effective insulator when the device is turned off. Also, in VMOS construction, the SiO_2 layer under the V groove need withstand only 25% of the gate-drain voltage. (In a conventional MOSFET, the oxide must withstand the entire gate-drain voltage.) Although the point of the V groove can create high

Illustrations courtesy of Siliconix, Inc.

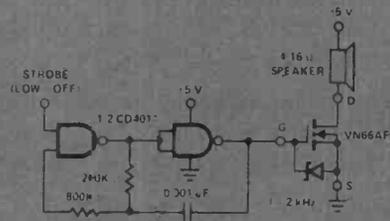


Fig. 4. Circuit for a 2-kHz audio alarm.

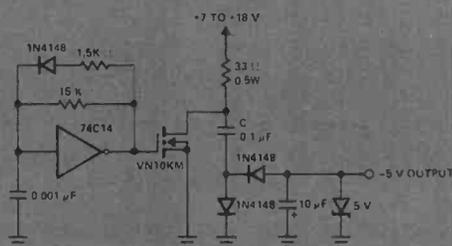


Fig. 7. A "flyback" dc-dc converter.

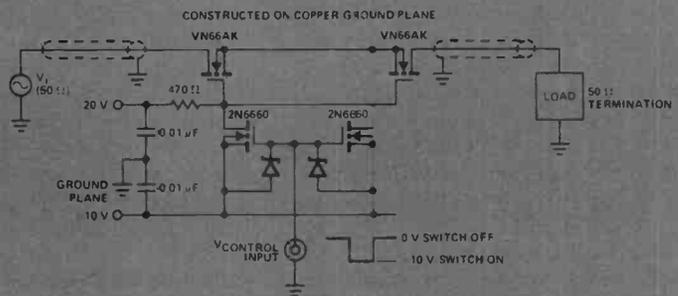


Fig. 8. An $r-i$ switch using VMOS.

electrostatic fields which can break down the oxide layer, work is in progress to solve this problem. One solution is to flatten the point of the V. This should ultimately make available high-voltage devices on a large scale.

Some Simple Circuits. Now that you have a basic familiarity with VMOS devices, let's look at how they can be used in some simple circuits. VMOS devices are now fairly easy to obtain. The VN66AF used in many of these circuits is available nationally through Radio Shack stores. Basically, the circuits run the gamut from simple gadgets where the VMOS power FET simply replaces a conventional power transistor, to a high performance r-f switch where only VMOS will work properly. In all of the circuits, simplicity is apparent, particularly in the drivers for the VMOS devices. This is one of the benefits of high-impedance inputs.

Audio Alarm. A circuit that can be used as a burglar alarm, keyboard beeper, timer alert, or audio tone generator is shown in Fig. 4. The CMOS gate is wired as an oscillator, whose pitch is variable by changing the 200-k Ω resistor, or the 0.001- μ F capacitor. The VMOS power FET is wired as a simple switch that drives the speaker directly. Note a zener diode connected across the gate and source of the VMOS device. This component is internal to the VMOS, and protects the input against overvoltage. A zener is built into most VMOS devices to make them less sensitive to static, so fewer handling precautions are necessary.

The circuit can be built on a small piece of perf board and cemented to the rear of the speaker. If desired, the supply voltage can be raised to 12 V for higher output power. If you want to tinker with the design, you can wire the two unused gates in the CD-4011 for another lower-frequency oscillator. Connect the output of this oscillator to the "strobe" input of the first oscillator. This produces a two-tone "boop-beep" sound similar to some police sirens.

Lamp Dimmer. The problem in dimming conventional incandescent lamps is that more power can be dissipated in the controller than in the lamp! The circuit of Fig. 5 solves this problem using a VMOS and pulse-width modulation. Control R2 changes the duty cycle, or "on time," of the CMOS oscillator. As a result, the on time for the VMOS switch varies along with lamp intensity. Since the VMOS power FET isn't on continuously, it dissipates less power, reducing heat-sink requirements. This circuit can be constructed on perf board, and adapted to many different applications. For example, it should work well con-

trolling low-power dc motors. Freedom from second breakdown, means less chance of damage from back emf or momentary high current. Of course, the maximum ratings of the VMOS device must be observed!

Automatic Battery Charger. The circuit shown in Fig. 6 provides up to 12.5 A at 14 V. As the battery charges and its voltage rises, the circuit automatically reduces the charging current. When the battery is fully charged, the charger cuts off. Thus, a lead-acid storage battery can be maintained fully charged at all times.

allows the op amp to provide more voltage to the VMOS power FET, insuring it will deliver maximum output current. If desired, this project can be built as a battery charger or, with the filter capacitor increased in value, as an adjustable high-current power supply.

"Flyback" DC-DC Converter. With a +7-to-18-volt input, this circuit (Fig. 7) can produce regulated -5 volts. The current output is limited, but should be enough for an op amp or two. The circuit consists of a CMOS oscillator driving a VMOS switch. A full supply voltage square wave appears across the 33-ohm resistor forming the VMOS load, and the negative, or "flyback" transition, is rectified, filtered, and zener regulated to -5 volts. Since the oscillator operates at a high frequency, the filter capacitor can have a small value, yet do a good job. The circuit can be assembled in little space and work with battery-powered op-amp projects.

VMOS R-F Switch. The circuit of Fig. 8 can switch r-f signals in 50 nanoseconds, far faster than any relay (20 to 50 ms typical). Other advantages include 60-dB isolation with a 10-MHz, 20-volt peak-to-peak input, and 1-dB insertion loss. These are impressive features for such a simple circuit.

Basically, the VMOS power FETs are wired as a "T" switch. When the V-control input is 0 volt, the two 2N6660 FETs are biased on, because 10 volts appear between their source and gate. The left 2N6660 turns off both power VMOS devices by pulling their gates to -10 volts. At the same time, the sources of both VMOS devices are pulled low by the right 2N6660. Thus, both VMOS devices are turned off, and the junction between them is grounded to reduce leakage through the switch. Making the V-control input -10 volts turns off the two 2N6660s and the VMOS devices are allowed to turn on because of the 470-ohm pull-up resistor. The input r-f signal passes through the VMOS devices to the output. This simple circuit can be used for many applications where high r-f frequencies are used. A good example would be in a low-power transceiver, or to switch several receivers to one antenna. Build it on a piece of "ground plane" perf board or board covered on one side with copper sheet. This will insure maximum attenuation when the switch is "off."

From this and the other circuits shown above, it is easily seen that VMOS power FETs are not exotic, difficult-to-use devices. On the contrary, they not only offer performance advantages over bipolar devices in many applications, they are often considerably easier to use. \diamond

FOR MORE INFORMATION ON VMOS TECHNOLOGY

The following publications are available from Siliconix, Inc., 2201 Laurelwood Rd., Santa Clara, CA 95054:

Document number	Title
AN79-1	A 500 KHz Switching Inverter for 12 V Systems
AN79-3	Dynamic Input Characteristics of a VMOS Power Switch
AN79-4	Driving VMOS Power FETs
AN79-5	Using the VN64GA High Current, High Power VMOS Power FET
AN79-6	Using VMOS Transistors to Interface from IC Logic to High Power Loads
AN79-7	Applications of the VN10KM VMOS Power FET
AN80-1	A Key to the Advance of Switching Power Supplies
AN80-2	Meet the VMOS FET Model
AN80-3	Ultralinear Broadband Amplifier
AN80-4	Enjoy VHF Power Amplifier Design
AN80-5	An Alternative Power Amplifier Design

Basically, the battery charger is a full-wave rectifier consisting of a pair of 1N249 silicon diodes, filter capacitor C2, and the VMOS series-pass element. The VMOS device is driven by a simple op-amp error amplifier, that compares a portion of the output voltage, via the 5-k Ω potentiometer, with a constant-voltage reference source. The reference consists of a CR390, a 390- μ A current source, and the 1N4100 zener diode. The power for the op amp and reference is derived from a separate source, which produces a slightly higher operating voltage than the main dc source. This

Now in one convenient, workbench guide. . . INSTANT SOLUTIONS TO YOUR ELECTRONIC TROUBLESHOOTING PROBLEMS — FOR ONLY \$2.09!

Imagine! All the valuable nuts-and-bolts instruction you need to slash working time. . .and make more money! For just \$2.09!

That's what you get in WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING by noted electronics authority Robert C. Genn, Jr. This comprehensive source of useful electronics know-how gives you page after page of sensational tips, techniques and shortcuts that can help you take on more jobs. . .finish them faster. . .make better repairs. . .and reduce callbacks!

What's more, WORKBENCH GUIDE shows you how to save money with "home brew" test circuits that do the same job as expensive equipment—at a fraction of the cost!

No gimmicks! No obligation!

You'd normally have to pay \$12.95 to benefit from the wealth of knowledge WORKBENCH GUIDE contains. But you pay only \$2.09! It's our way of introducing you to the Electronics Book Service — the no-risk book club that keeps over 50,000 technicians, troubleshooters and hobbyists informed of the best and most useful books on electronics.

We chose WORKBENCH GUIDE for our introductory offer because it's representative of the many outstanding selections we make available to our members.

Join now as a trial member of the Electronics Book Service and you'll receive your copy of WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING for the low, low price of \$2.09.

Once you have paid for your introductory selection, you are under no obligation to buy any other club offering. That's what makes the Electronics Book Service so unique.

And, even if you never buy another book, you'll still be informed every four weeks of the most useful, valuable new books in the field, available to you at generous savings.

Just look at all the electronics information your \$2.09 will buy!

WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING provides hundreds of sharp ideas and sure-fire techniques for solving even your most difficult troubleshooting problems.

For starters, you get step-by-step instruction in how to build your own test circuits from components you probably have in your junkbox now. They'll help you do everything faster. . .without having to pay for high-priced testing equipment.

Then you discover how to quickly locate all types of malfunctions in electronic equipment. . .and how to correct each problem with minimum inconvenience.

And, you get no mind-boggling explanations. Just straight, easy-to-follow directions for techniques that really work.

WORKBENCH GUIDE is packed with tips and shortcuts that will save you time and money:

- How to use resistors in place of expensive transformers
- How to make a time-saving graph for determining input impedance
- How you can make a simple instrument that measures resistance better, in special cases, than an ohmmeter

- How to construct and use a simple OP AMP tester
 - How to make a device that can determine total harmonic output, as distinct from each frequency of the output
 - How you can knock together a simple, easy-to-use substitute instrument—from components lying around in your shop right now—instead of shelling out big money for a signal generator with metered output
 - How to perform simple, but effective frequency measurements with a scope
- Plus much, much more!

Fully illustrated!

WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING contains over 100 easy-to-follow charts, tables and illustrations to help simplify the techniques and shortcuts you'll be using.

Here are:

- Charts for easy conversion of decibels and voltages
- A table for RF increase vs. percent of modulation
- Conversion factors for areas, volumes and capacitance-to-reactance
- A test set-up for IF amplifier AGC troubleshooting
- A test set-up for testing triacs

WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING is the best source there is for learning how to save time, trouble and big money on instruments and equipment. . .and getting instant answers for up to 99% of the troubleshooting problems you encounter. That makes it a perfect way to introduce you to the Electronics Book Service.


Begin your membership today. Mail this coupon now.

All you need to do to begin your trial membership in the Electronics Book Service is fill out and mail the coupon below. When we receive it, we will ship your copy of WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING at once.

Remember, the Electronics Book Service has no additional book purchase requirements. Once you've paid \$2.09—plus shipping and handling—for WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING, you don't need to purchase any other selections!

Why delay? Mail the coupon below to get your copy of this \$12.95 benchside guide for only \$2.09—and to receive all the benefits of membership in the Electronics Book Service. Fill out and mail your coupon right away.

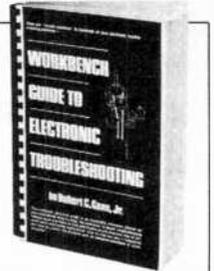Here is the practical and efficient way in which the Electronics Book Service operates.



1. When you enroll as a member, you receive—for only \$2.09 (plus shipping and handling, with tax where applicable)—your copy of WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING. This is the only book you are committed to buy.

2. Thereafter, you are under no obligation to accept any minimum number of selections within any time limit. You can take as many or as few as you wish. And you may resign at any time with no obligation once you have paid for your copy of WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING.

3. On selections you do accept, your membership entitles you to a discount from the publisher's price. This discount is available to members only and provides you with substantial savings.

4. Every four weeks we'll send you a free mailing describing the current selection. If you want the selection, no action is required. It will be shipped to you automatically. If you don't want it, just return the card that is enclosed with the mailing.

5. You have at least 10 days to decide whether or not you want the selection. Return the card so we receive it no later than the date specified. If you don't have 10 days to answer and receive an unwanted selection, return it at our expense.

6. Each mailing also describes a number of alternate or additional selections, also available to you at the special discount price for members.

ABOUT THE AUTHOR

Robert C. Genn is the Director of Engineering at Columbia College in Los Angeles, and President of the Genn Technical Institute. He has been involved in the electronics field for more than 20 years as a Field Engineer, Director of Engineering and Electronics, technician and instructor. Mr. Genn is certified by the California Institute of Technology to teach technicians to troubleshoot, service and repair microwave systems.

ELECTRONICS BOOK SERVICE

Membership Enrollment Center, P.O. Box 42
West Nyack, N.Y. 10995

Please enroll me in the Electronics Book Service on a trial basis. As my introductory selection under this trial membership, send me WORKBENCH GUIDE TO ELECTRONIC TROUBLESHOOTING for only \$2.09 plus shipping and handling, with tax where applicable. I am to receive announcements free of charge and will be entitled to full privileges as a member—without obligation to buy any additional club selections.

Name _____

Address _____

City _____ State _____ Zip _____

Offer limited to new members (U.S. and Canada only). Not available in Hawaii or Quebec.

59-6
96522-8
6651-AB(9)

THANDAR'S COMPLETE PORTABLE TEST BENCH



\$79.95

LCD HAND HELD MULTIMETER

TM354 3½ Digit

● DC Volts : 1mV to 1000V ● AC Volts : 1V to 500V AC rms ● DC current : 1μA to 2A
● Resistance : 1Ω to 2MΩ ● Diode Check
● Basic accuracy : ± (0.75% of reading + 1 digit) ● Battery life : Typically 2000 hours

**2000 hrs
BATTERY
LIFE**



GOLD MEDAL WINNER

\$259

SC110 SINGLE TRACE LOW POWER 2" OSCILLOSCOPE

This truly portable oscilloscope, the only British product to win a Gold Medal at the 1980 Brno Trade Fair, boasts the following specification: ● Bandwidth : DC to 10MHz ● Sensitivity : 10mV/div to 50V/div ● Sweep Speeds : 0.1μsecs/div to 0.5 secs/div ● Power Requirements : 4 to 10V DC from 4 'C' cells or AC adaptor ● Size and weight : 255 x 150 x 40mm; 800gms excl. batteries

FREQUENCY METERS

TF40 8-Digit LCD

● Frequency Range : 10Hz-40MHz (to 400MHz with TP600)
● Sensitivity : 40mV rms ● Timebase accuracy : better than 0.5 ppm ● Battery life : Typically 80 hours

TF200 8-Digit LCD

● Frequency Range : 10Hz-200MHz (to 600MHz with TP600) ● Sensitivity : 10mV rms 20Hz-100MHz, 30mV rms 10Hz-20Hz, 100MHz-200MHz ● Timebase accuracy : better than 0.3 ppm ● Battery life : Typically 200 hours ● \$299 (inc. batts).

PFM200 8-Digit LED Hand Held Meter

● Frequency Range : 20Hz-200MHz (to 600MHz with TP600) ● Sensitivity : Typically 10mV ● Timebase accuracy : better than 2 ppm ● Battery life : Typically 10 hours ● \$99.95

TP600 600MHz Prescaler

● Frequency Range : 40MHz to 600MHz ● Sensitivity : 10mV ● Output : Typically 500mV peak-peak ● \$79



**\$199
inc. batts**

THANDAR SATISFACTION WARRANTY:

If for any reason, whatsoever, you are not completely satisfied with your purchase, return it within 30 days of purchase date for a full refund - it's as simple as that!

TO ORDER CALL TOLL FREE: 800-526-5311
We accept Master Charge or Visa

New Jersey Residents add appropriate Sales Tax. Prices shown in U.S. currency only.

POSTAGE AND HANDLING up to \$100 add \$3. Over \$100 add \$5.

THANDAR ELECTRONICS INC

P.O. Box 8247, Haledon, New Jersey, 07538 Tel: 201-790-3141



**4000 hrs
BATTERY
LIFE**

LCD BENCH MULTIMETERS

**\$199
inc. batts**

TM351 3½ Digit

● DC and AC Volts : 100μV to 1000V (750V AC rms)
● DC and AC current : 100nA to 10A (20A for 10 secs)
● Resistance : 100mΩ to 20MΩ ● Diode check ● Basic accuracy : ± (0.1% of reading + 1 digit) ● Battery life : up to 4000 hours

TM353 3½ Digit

● DC and AC Volts : 100μV to 1000V (750V AC rms) ● DC and AC current : 100nA to 2A
● Resistance : 1Ω to 20MΩ ● Diode check ● Basic accuracy : ± (0.25% of reading + 1 digit) ● Battery life : Typically >3000 hours ● \$159 (inc. batts).

LED MULTIMETERS

DM350 3½ Digit;

34 ranges; 0.1% basic accuracy;



\$99.95

DM235 3½ Digit; 21 ranges; 0.5% basic accuracy; \$69.95

PDM35 3½ Digit; Hand held; 16 ranges; 1% basic accuracy; \$39.95



\$159

PULSE & FUNCTION GENERATORS

TG100 100kHz Function Generator

● Frequency range - 0.1Hz to 100kHz
● Functions : Sine, Square, Triangle and DC from variable 600Ω output ● Output range : 1mV-10V peak-peak ● DC offset range : ±5V ● TTL output ● External sweep : ≥300:1 linear range

STOP PRESS TG102 2MHz Function Generator \$299

TG105 5MHz Pulse Generator

● Period : 200nsec to 200ms (5MHz to 5Hz) ● Pulse width : 100nsec to 100ms ● 50Ω output range : 0.1V-10V ● TTL output ● Sync. output ● Operating modes : run, external trigger, external gate, manual 1-shot or gate ● Complement and square wave ● \$199

SUCCESSFUL SOLDERING


*Helpful tips
on materials, tools,
and techniques*

BY JOHN D. BORNEMAN

IN ELECTRONICS, the basic goal of soldering is to electrically and mechanically join two circuit components. For this connection to be reliable, the solder must adhere to or "wet" the mating surfaces of the components being joined. The wetting of solder to a base metal is similar to the action of water spilled on a smooth surface: if the surface is clean and free of dirt, wax and oils, the water will wet and spread evenly over it; if the surface is waxed, the water balls up.

Most manufacturers of electronic components do a good job of making their products of easily solderable material or providing a clean solderable coating. Copper, copper-clad steel, or nickel-steel are some of the common base metals used in the leads of resistors, capacitors, integrated circuits, etc., and they may be coated with silver, tin, tin-lead, or gold to improve solderability. Greases, oils, dirt, and oxides are the principal sources of contamination that prevent good solder wetting despite the original surface. Also, aging deteriorates the surface and inhibits solder wetting by the formation of oxide films.

Solder Alloys and Fluxes. Technically, soldering is the joining of two parts with a metal alloy having a melting point below 800° F. Various solder alloys include combinations of tin, lead, antimony, silver, indium, and bismuth; however, the most common combination is tin and lead. Tin-lead solders range from pure tin to pure lead and include all proportions in between. For plumbing, alloys of 10% tin and 90% lead (10/

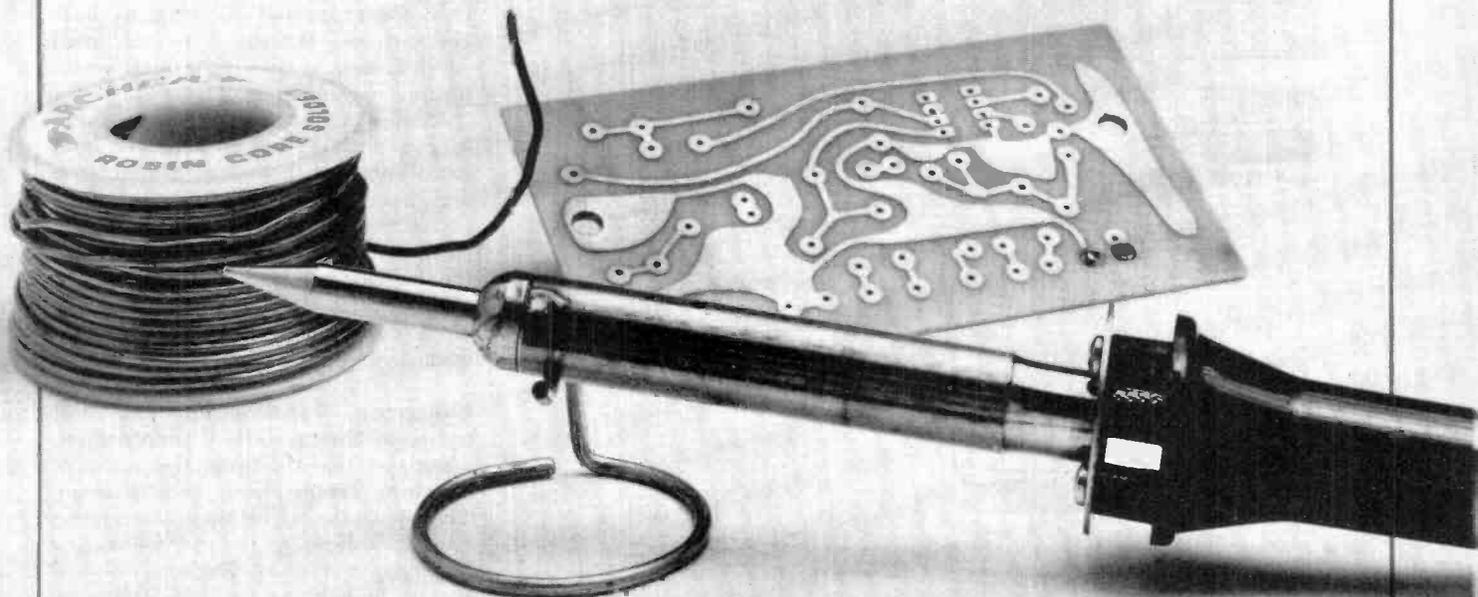

90 solder) are commonly used. In electrical soldering, the alloy mix is usually 60% tin and 40% lead (60/40).

Characteristics of alloys of tin and lead are plotted against temperature in Fig. 1. This graph, referred to as a phase diagram, allows one to see that only a 63/37 alloy has a eutectic point—that is, a single melting point. All other alloys start melting at one temperature, move through a “pasty” or semisolid stage, and then become liquid at a higher temperature. Any physical movement of the components being soldered while the solder is in the “pasty” range will result in a “cold” joint. Such a joint appears grainy and dull, and is mechanically weaker, thus less reliable. Therefore, 63/37 or 60/40 solder is commonly used in electronics since they do not remain long in a “pasty” phase. However, a 50/50 alloy can be used if proper care is taken.

An often-ignored aspect of soldering is the *flux*. The word flux comes from the Latin root “fluere” meaning “to flow.” Soldering flux, which is usually included in the solder as a central core, or separately in liquid or paste form, helps the solder alloy flow around the connection. Flux also cleans the component leads of oxides and films, and allows the solder to wet their surfaces.

Chemically, flux is either acid or rosin based. Always use rosin flux in electronic soldering since the acid may cause corrosion. “Activated” rosin or “RA” flux produces better cleaning and

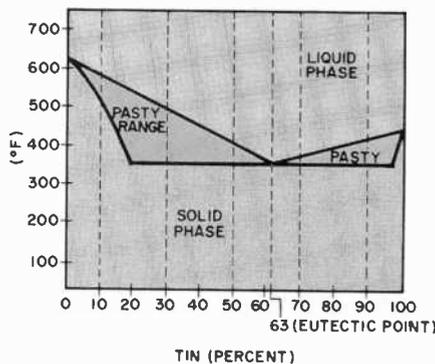


Fig. 1. Melting point, including pasty phase, of alloys of tin and copper.

flowing properties than the popular mildly activated fluxes (RMA), and they are noncorrosive.

Equipment. The tools required to solder electrical connections are: a good soldering iron and a supply of replaceable tips, long-nose pliers for holding parts or bending leads (or as a heat sink for temperature-sensitive components), and desoldering braid (or a suction desoldering tool).

There are basically two types of soldering instruments—the “gun” and the “iron,” although most people use these descriptions interchangeably. In essence, a soldering “gun” is a pistol-shaped device consisting of a transformer forming the bulk of the “gun,” with the secondary winding extending out to

form the replaceable tip. Usually, soldering guns come with high wattages, in most cases too high for use with pc foil patterns. Such guns also generate a high magnetic field around the tip that can de-gauss any magnetically sensitive devices close to it. Using a gun may produce too high a heat on the foil pattern so that the cement that secures the copper foil pattern to the substrate is weakened and the foil separates from the printed circuit board.

The “iron” is often called a “pencil iron” because it resembles a thick pencil that is held in the fingers. These tools feature interchangeable (usually screw-on) tips having various shapes—each for its own purpose. Their wattages are usually low enough to be safely used on pc boards. The latest version of the pencil iron is the low-wattage self-contained rechargeable type that can be used remote from the ac line.

Soldering irons are specified primarily by wattage as shown in the table. Wattage represents the amount of heat capacity available at the iron tip. Irons of all wattages usually run at about the same tip temperature, but a lower-wattage iron will cool faster during soldering. The recommended wattages given in the table are to be used as general guidelines only. Slight variations may give perfectly good performance, depending on the particular soldering situation. A higher-wattage iron is more likely to damage heat-sensitive components. If static-sensitive components are to be soldered, i.e. many MOS devices, be sure the iron has a grounded plug. Soldering irons can produce static voltage spikes that will destroy many integrated circuit components, so a grounded tip is a wise safety measure.

Tips are usually selected by preference. Each type and shape has its place and purpose, but the commonly used pointed, conical type is the most versatile and convenient.

Desoldering equipment is always useful even for experienced solderers. Both braid and suction devices are effective and, again, operator preference is the best guide. If you elect to use a suction desoldering tool, pay close attention to the distance and velocity that the “piston” requires. It is very easy to get a black eye, or have glasses damaged, when using those devices.

Soldering Techniques. The best technique can be outlined simply. First, make sure that the tip of the iron is at operating temperature, and is clean. Then touch the heated tip to the connection, preferably on the part having the larger mass (Fig. 2). The solder should not be brought to the joint until the

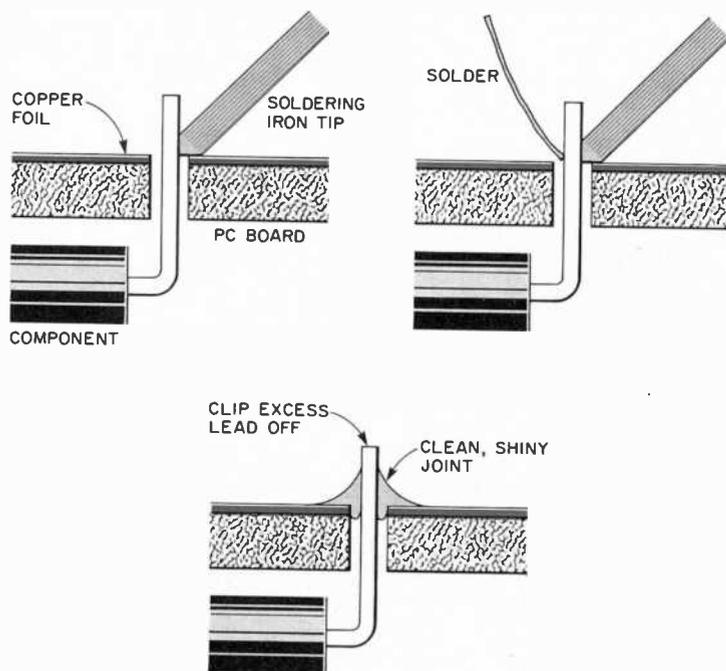


Fig. 2. Steps in soldering. Place heated iron to junction of parts to be soldered (top left) Bring flux-cored solder to the joint after it is hot enough to melt solder (top right) When a smooth-contoured fillet has formed, remove the solder and allow to cool without moving.

IRON WATTAGES FOR DIFFERENT SOLDERING TASKS

Type of Soldering	Recommended Iron Wattage
Light duty: single joints, repair, touch-up, delicate parts such as ICs or fine wires. Mass of parts in connection is small.	25 to 30
Medium duty: multiple joints; many in succession. Mass of parts is intermediate (for example, 1/4-watt resistors or conventional disc capacitors).	60 to 100
Heavy duty: Mass is large, as in wires soldered to steel case or wires to screw heads for ground points.	over 100

metals being joined have become hot enough to melt it. How long this takes is quickly learned after a few trials. The flux-cored solder is then brought to the joint and placed at the junction of the two parts. When the solder has melted and flowed into a smooth-contoured fillet, remove the solder. Keep the tip on the joint for a few seconds, then remove it. Do not disturb the newly made connection until it has had time to solidify. A good solder joint will be shiny (Fig. 3). Disturbing the joint before it has solidified may produce a "cold" joint.

Problem Solving.

To Avoid Cold Joints. Even when you know that the parts should not be moved while the solder joint is cooling, it is sometimes difficult to find enough hands to hold a soldering iron, solder, circuit board, and the part being attached. In this case, a small vise or a surgeon's hemostat may be used to hold the board and parts. If you are using rosin flux in liquid or paste form, another

method is possible. Using long-nose pliers, hold the part to the circuit board. Apply flux to the pieces being soldered and take up the soldering iron. Touch the iron to a length of solder, creating a ball on the tip. Touch the tip to the connection and hold it there until the fillet is formed. This will create a good joint and free your hands to hold the parts.

To Get Good Solder Wetting. Clean the parts well with isopropyl alcohol to remove greases and oils, and use a 10% solution of hydrochloric acid (HCl) to remove the oxides. Fine steel wool may be used on foil patterns to remove oxide films. These chemicals should be available from any drugstore, but remember to ask about any handling precautions before using them. Note that extra liquid flux can also help in soldering contaminated parts.

To Make Solder Flow. Be sure the soldering iron is providing enough heat, with the iron tip on tight and the proper wattage being used. Also be sure enough flux has reached the component leads

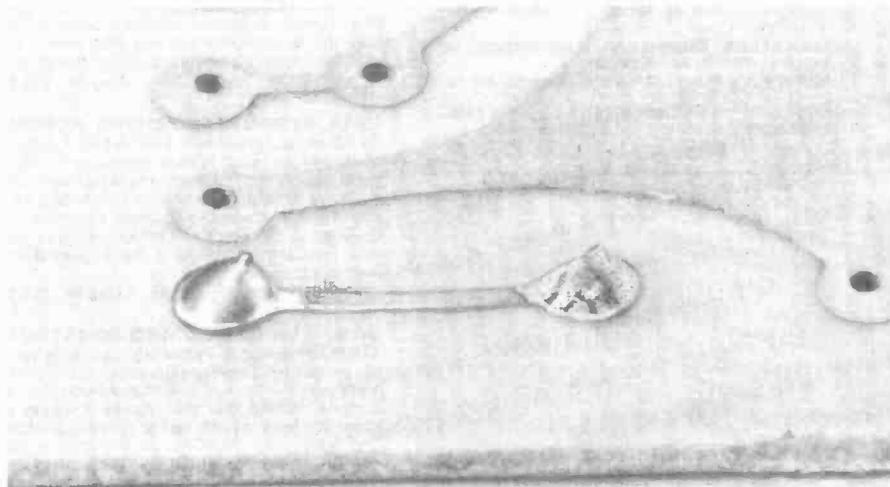


Fig. 3. Photo of two soldered joints. The one at left is shiny indicating a good joint. At right, is a "cold" solder joint.

The world of electronics gee-wizardry



-YOURS FREE.

32-pages of test instruments—from the latest digital multimeters to the famous EICO scopes. Security systems. Automotive and hobbyist products. Kits and assembled. EICO quality. EICO value. For FREE catalog, check reader service card or send 50¢ for first class mail.

EICO® 108 New South Road
Hicksville, N.Y. 11801

CIRCLE NO. 24 ON FREE INFORMATION CARD



Complete Microprocessors line, peripherals & Terminals		
APPLE II PLUS	\$1215.00	Disk 1300K DOS 3.3 w/controller ... \$575.00
48K LANG-SYS		SOROC IQ135 ... 795.00
W/PASCAL	395.00	TI-99/4 ... 399.00
Green Monitor	174.00	Epson MX-80 ... call us
Leedex 100 Mon	139.00	Color Monitor ... call us
iDS 445G	call us	TI-810 ... 1695.00
TI-745	1440.00	80 Column Board ... 299.00

Texas Instruments

Invest. Anal	\$ 42.00	TI-59	\$175.00
Accessories	Call us	TI-55 II	39.95
TI-58C	80.00	Speak & Spell	49.95
PC100C	155.00	TI Programmer	47.95
TI BAII	39.00	MBA	49.95

HEWLETT-PACKARD

System I	call us	HP-41C Mem	
System II	call us	Module	26.00
HP-33C	75.00	HP-41CV	call us
HP-34C	119.00	HP-67	295.00
HP-38C	114.99	HP-97	570.00
HP-41C Prog	189.00	Quad Ram	call us
HP-41C Printer	289.00	Application Pac	call us
HP-41C CRD RDR	169.00		

HP 83, HP 85 and accessory call us for prices

SCM TYPEWRITER SPECIALS


SCM 2200	\$279.00	INTREPID	\$274.00
SCM 2500	289.00	CLASSIC 12	159.00

All units shipped in original cartons with accessories according to manufacturer's specification. Send money orders, personal check 2 weeks to clear. In Illinois add 6% sales tax. Add \$6.95 minimum shipping & handling charges per unit. We ship UPS. Subject to availability. Written warranty for specific products can be obtained free upon request. Above prices are for mail order and prepaid only. Prices and specifications subject to change without notice. Send mail orders.

Nabih's, Inc.

519 DAVIS EVANSTON ILL 60201 TEL 312-869-6144

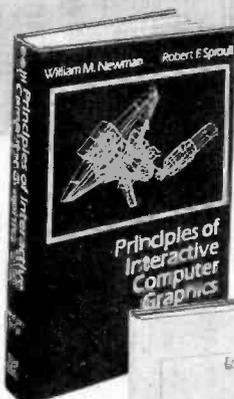BUY ONE of these great professional books when you join the




Principles of Interactive Computer Graphics

THE BYTE BOOK OF PASCAL Edited by Blaise W. Liffick. 340 pp., illus. In this timely book you get up-to-date Byte articles on the subject—from a general introduction to system hardware—from top experts in the field. Includes two versions of a Pascal compiler, one written in BASIC and the other in 8080 assembly language ... a p-code interpreter written in both Pascal and 8080 assembly language ... Pascal vs. COBOL ... a chess-playing program ... an APL interpreter ... and more.

789/673 Pub. Pr., \$29.95 Club Pr., \$22.50



The BYTE Book of Pascal

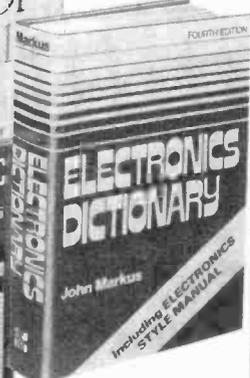

ELECTRONICS DICTIONARY



AUTOMATIC DATA PROCESSING HANDBOOK. Edited by The Diebold Group. 976 pp., 269 illus. Written by a staff of internationally recognized authorities on ADP, this comprehensive handbook explains systems, programming and the languages, communications processes, and the design and installation of today's computers.

168/075 Pub. Pr., \$44.95 Club Pr., \$31.50

SOFTWARE ENGINEERING Edited by Randall W. Jensen and Charles C. Tonies. 580 pp., illus. This book examines all phases of software engineering. It provides an integrated treatment of the true foundations of effective project management and also serves as a dependable guide for designing better programs, implementing them more efficiently, and protecting them from theft or misuse.

788/367 Pub. Pr., \$27.50 Club Pr., \$19.95

THE GIANT HANDBOOK OF COMPUTER PROJECTS By the Editors of 73 Magazine. 504 pp., 217 illus. This book shows you how to build computer equipment from scratch—either as a hobby in itself or as part of another interest such as amateur radio or electronics. The book starts with the fundamental and then covers such projects as computer games, a bionic clock, a computer-controlled thermometer, and much more.

582012-9 Pub. Pr., \$15.95 Club Pr., \$13.50

PRINTED CIRCUITS HANDBOOK. Edited by C. F. Coombs, Jr. 2nd Ed., 634 pp., 595 illus. Covering the subject of printed circuits from the design's idea to final acceptance, this enormously well-received work includes double-sided plated boards through printed boards and also the major variations such as multilayer and flexible circuits.

126/089 Pub. Pr., \$38.50 Club Pr., \$28.95

PRINCIPLES OF DATA BASE SYSTEMS. By Jeffrey D. Ullman. 379 pp., 154 charts and diagrams. This book shows you how to design, assess, query, and protect serial and concurrent databases. It discusses three important data models—the relational, network, and hierarchical—as well as the actual strategies and methods used to store and access records.

582126-5 Pub. Pr., \$21.95 Club Pr., \$17.95

PRINCIPLES OF INTERACTIVE COMPUTER GRAPHICS. By William M. Newman and Robert Sproull. 2nd Ed., 544 pp., illus. Now in a revised, updated Second Edition, this is a volume that has long been THE standard source of information for designers!

463/387 Pub. Pr., \$26.95 Club Pr., \$20.95

DATA STRUCTURES USING PASCAL. By Aaron M. Tenenbaum and Moshe J. Augenstein. 544 pp., illus. With its emphasis on structured design and programming techniques, this definitive work takes you on a trailblazing journey through Pascal. Separate chapters are devoted to the stack, recursion, queues and lists, Pascal list processing, trees, graphs and their applications.

582230-X Pub. Pr., \$23.95 Club Pr., \$18.50

COMPILER DESIGN AND CONSTRUCTION. By Arthur B. Pyster. 357 pp., with sample programs, charts, diagrams, and a comprehensive index. A practical introduction to compiler writing that also shows you how to transform your design into a working product. The book uses PASCAL as the source language—and the IBM 360/370 Assembly Language as the target language—to demonstrate how to build a clearly organized, error-free compiler.

582026-9 Pub. Pr., \$24.50 Club Pr., \$19.95



SOFTWARE ENGINEERING



ELECTRONIC GAMES



COMPUTER CAPACITY

BE SURE TO CONSIDER THESE IMPORTANT TITLES AS WELL—

BIT-SLICE MICROPROCESSOR DESIGN. By J. Mick and J. Brick. 417/814 Pub. Pr., \$18.50 Club Pr., \$14.50

HOW TO DESIGN, BUILD & PROGRAM YOUR OWN WORKING COMPUTER SYSTEM. By R. P. Haviland. 788/987 Pub. Pr., \$14.95 Club Pr., \$12.70

MICROPROCESSORS AND MICROCOMPUTERS: One-Chip Controllers to High-End Systems. By Electronics. 191/417 Pub. Pr., \$24.50 Club Pr., \$18.95

MICROCOMPUTER INTERFACING HANDBOOK: A/D And D/A. By J. J. Carr. 582188-5 Pub. Pr., \$14.95 Club Pr., \$12.70

COMPUTER PERIPHERALS FOR MINICOMPUTERS, MICROPROCESSORS, AND PERSONAL COMPUTERS. By L. C. Hehnstein. 294/518 Pub. Pr., \$19.50 Club Pr., \$15.50


MICROPROCESSORS/MICROCOMPUTERS SYSTEM DESIGN. By Texas Instruments, Inc. 637/58X Pub. Pr., \$24.50 Club Pr., \$19.50

SYNTAX OF PROGRAMMING LANGUAGES: Theory and Practice. By R. C. Backhouse. 582064-1 Pub. Pr., \$25.95 Club Pr., \$19.95

INFORMATION RETRIEVAL SYSTEMS: Characteristics, Testing and Evaluation, 2/e. By F. W. Lancaster. 582000-5 Pub. Pr., \$22.95 Club Pr., \$17.95

ASSEMBLERS, COMPILERS, AND PROGRAM TRANSLATION. By P. Calingaert. 582110-9 Pub. Pr., \$18.95 Club Pr., \$15.95

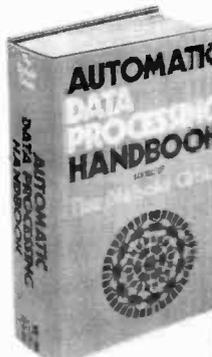HANDBOOK OF MICROCIRCUIT DESIGN AND APPLICATION. By D. F. Stout & M. Kaufman. 617/961 Pub. Pr., \$37.50 Club Pr., \$28.50



AUTOMATIC DATA PROCESSING HANDBOOK



MICROPROCESSOR APPLICATIONS MANUAL



PRINTED CIRCUITS HANDBOOK

and GET ONE FREE (values up to \$60.00) COMPUTER PROFESSIONALS' BOOK CLUB

MICROCOMPUTER INTERFACING By Bruce Artwick. 352pp., 117 illus. In this up-to-date, complete design guide you'll find the detailed descriptions and explanations necessary to enable you to select, build, and interface microcomputer systems to virtually all applications. Advanced interface devices and methods are thoroughly examined and illustrated, with emphasis on design procedures, optimization, performance, and reliability. 789/436 Pub. Pr., \$24.95 Club Pr., \$18.95

COMPUTER CAPACITY. By Melvin J. Strauss. 288 pp., tables and charts. The key purpose of the book is to provide both senior management and DP practitioners with a methodology for identifying and quantifying issues of capacity and demand within the data center without becoming entrapped by language problems. Melvin Strauss tears down the wall and erects a useful structure of thinking, techniques, and communication for DP managers, systems analysts, and cost accounting managers. 582317-9 Pub. Pr., \$24.95 Club Pr., \$18.95

ELECTRONIC GAMES, Design, Programming and Troubleshooting. By W. H. Buchsbaum and R. Mauro. 335 pp., 338 illus. Information you need to design, program, and troubleshoot electronic games is right here in this widely popular hands-on guide. 087/210 Pub. Pr., \$24.50 Club Pr., \$17.50


COMPUTER SYSTEMS ARCHITECTURE. By Jean-Loup Baer. 626 pages, 263 charts, diagrams & tables. A book that takes software and hardware out of their respective pigeonholes... and describes their interaction with the thoroughness of an encyclopedia! You'll find this is a thorough and valuable integration of data processing's "two worlds" and their fascinating relationship. 582208-3 Pub. Pr., \$24.50 Club Pr., \$18.95

COMPUTER DICTIONARY AND HANDBOOK. By Charles and Robert Sippl. 624 pp., illus. This handy reference/guide defines and explains a wide range of computer procedures, products, problems, and applications. Appendixes provide a "state-of-the-art" guide to essential computer concepts. 582079-X Pub. Pr., \$29.95 Club Pr., \$14.95

MICROPROCESSOR PROGRAMMING AND SOFTWARE DEVELOPMENT By F.G. Duncan. 320 pp., with diagrams, tables, and index. For the experienced professional who's a newcomer to microprocessors... this is the introduction to microprocessor programming you've been hoping for! One careful step at a time, the author tracks through his subject with thoroughness and clarity. The detailed discussion is based on four widely used processors—the Motorola 6800, Intel 8080 and 8085, and Zilog Z80. 582069-2 Pub. Pr., \$28.00 Club Pr., \$21.50

ELECTRONICS DICTIONARY. Edited by John Markus. 4th Ed., 768 pp., 1,173 illus. The indispensable standard authority on the meaning of 17,090 terms that make up the language of today's electronics is now available in a revised, updated edition. A model of clarity, conciseness, and authority, it is the best place to look for speedy retrieval of the information you need. 404/313 Pub. Pr., \$29.95 Club Pr., \$22.50

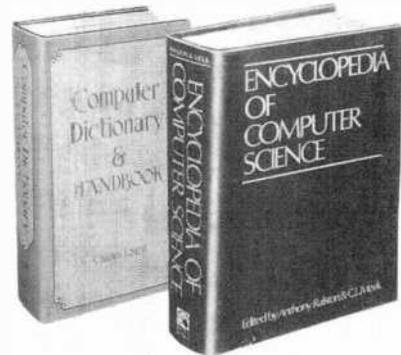MICROPROCESSOR APPLICATIONS MANUAL. By Motorola Semiconductor Products, Inc. 720 pp., illus., 8 1/2 x 11 format. With nuts-and-bolts practicality, this manual by the Motorola people (who should know) gives you detailed applications information on microprocessors and assumes no prior knowledge on your part about MPUs. 435/278 Pub. Pr., \$42.50 Club Pr., \$29.50



ENCYCLOPEDIA OF COMPUTER SCIENCE. Edited by Anthony Ralston and C. L. Meek. 1,500 pp., 60 illus., 100 charts, 7 x 10 format. This first and only in-depth coverage of the entire field of computer science in a single volume is comprehensive and completely up to date. 769/01X Pub. Pr., \$60.00 Club Pr., \$39.95

PROGRAMMING LANGUAGES. By Allen B. Tucker, Jr. 439 pp., illus. Gives you not only the principles of design but the applications of six major programming languages. Shows you their strengths and weaknesses in solving various representative "benchmark" problems. 654/158 Pub. Pr., \$25.95 Club Pr., \$19.50

PERSONAL COMPUTING: Hardware and Software Basics ELECTRONIC BOOK SERIES. 224 pp., 175 illus., outsized 8 1/2 x 11 format Gives you comprehensive guidance to the present state of the art in personal computers—an overall survey of the technology, and methods available to perform various tasks, facts about the work others are doing—and just how they are doing it. 191/603 Pub. Pr., \$23.50 Club Pr., \$19.50

Choose any one of these books at the special club discount, and select any other as your gift Free of Charge when you enroll

Why YOU should join now!

- **BEST BOOKS IN YOUR FIELD**—Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the latest books in your field.
- **BIG SAVINGS**—Build your library and save money too! We guarantee savings of at least 15% off publishers' list prices on every book. Usually 20%, 25% or even higher!

• **BONUS BOOKS**—You will immediately begin to participate in our Bonus Book Plan that allows you savings between 70-80% off the publisher's price of many books.

- **CONVENIENCE**—14 times a year you receive the Club Bulletin FREE, fully describing the Main Selection and alternate selections, together with a dated reply card. If you want the Main Selection, you simply do nothing—it will be shipped automatically. If you want an alternate selection—or no book at all—you simply indicate it on the regular reply card and return it by the date specified. You will have at least 10 days to decide. If, because of late mail delivery of the Bulletin you should receive a book you do not want, just return it at the Club's expense.

As a Club member, you agree only to the purchase of four books (including your first selection) over a two-year period.

SEPTEMBER 1981

Computer Professionals' Book Club

P.O. Box 582, Hightstown, New Jersey 08520

Please enroll me as a member and send me the two books indicated, billing me for my first selection only at the discounted member's price, plus local tax, postage and handling. If not satisfied, I may return the books within 10 days and my membership will be canceled. I agree to purchase a minimum of 3 additional books during the next 2 years as outlined under the club plan described in this ad. Membership in the club is cancellable by me any time after the four book purchase requirement has been fulfilled.

Write Code # of
FREE selection here

Write Code # of
FIRST selection here

Orders from outside the U.S. must be prepaid with international money orders in U.S. dollars

Charge my VISA MASTER CHARGE* Exp. Date _____

Credit Card # _____ *MC Bank # _____

Signature _____

Name _____

Address/Apt. _____

City, State, Zip _____

Corporate Affiliation _____

This order subject to acceptance by McGraw-Hill. All prices subject to change without notice. Offer good only to new members. A postage and handling charge is added to all shipments.

P39537

Shelf Conscious?

Now you can organize your copies of **Popular Electronics**

Now your magazines can be a handsome addition to your decor, well organized, and easy to find, thanks to these durable library-quality cases or binders. They're made of luxury-look leatherette over high-quality binders board. And both styles are custom-designed for this or any magazine you save, with size, color, and imprint selected by the publisher. FREE transfer foil included for marking dates and volumes.

Magazine binders

hold a year's issues on individual snap-in rods, combining them into one volume. \$7.95 each; 3 for \$22.50; 6 for \$42.95. Mixed titles OK for quantity prices.

Open-back cases

store your issues for individual reference. \$6.95 each; 3 for \$19.75; 6 for \$37.50. Mixed titles OK for quantity prices.



Popular Electronics, P.O. Box 5120, Phil., PA 19141

Please send: Cases Binders QUANT. _____

Popular Electronics: _____

(Other): _____

ENCLOSED IS \$ _____ * Add \$1.00 per order for postage & handling. Outside USA add \$2.50 per unit ordered. Send U.S. funds only.

CHARGE (Min. \$10): VISA American Express Master Card

Card # _____ Exp. Date _____

Signature _____

Print Name _____

Address _____

City/State/Zip _____

*Residents of PA add applicable sales tax.


Charge Orders Only: Phone 24 Hrs. TOLL FREE 800-431-2731. NY State Only 800-942-1940.

Just in case.


In case you have a short production run. In case you need good-looking prototypes. In case you need more flexibility or instant availability.

A more realistic price. Or all the above.

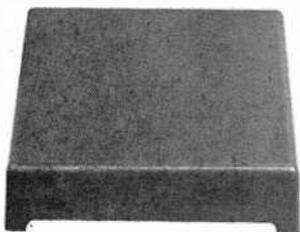
Because you never know when you'll need the right case at the right price, right away, keep us in mind. Or better yet, send for our catalog...just in case



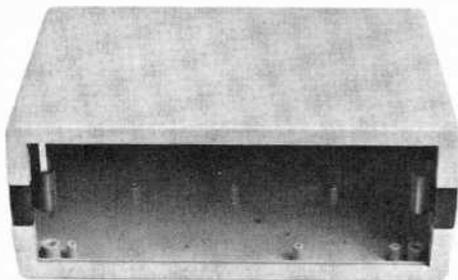DMC Case, 6.75 x 7.5 x 3.25" or 5.5 x 6 x 3"; each includes hardware and aluminum baseplate



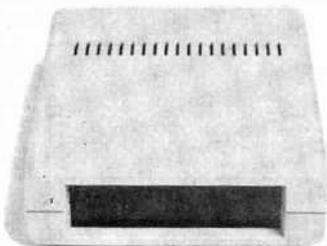Benchtopper Case, 3 x 10 x 7" or 4 x 10 x 7"; each includes hardware and metal front and rear panels



Portable Case, 1.75 x 5.63 x 7.75"; includes hardware, rubber feet, red transparent front panel



Probe Case, 5 x 1 x 0.7"; includes hardware, tip and cable



Handheld Case, 3 x 6 x 1.5"; includes hardware and red transparent front panel

Smarter tools for testing and design.

GLOBAL SPECIALTIES CORPORATION

70 Fulton Terr., New Haven, CT 06509 (203) 624-3103. TWX 710-465-1227
OTHER OFFICES: San Francisco (415) 648-0611. TWX 910-372-7992. Europe: Phone Saffron-Walden 0799-21682. TLX 817477
Canada: Len Finkler Ltd., Downsview, Ontario

Call toll-free for details **1-800-243-6077**

During business hours

Specifications subject to change without notice. © Copyright 1980 Global Specialties Corporation.

soldering

and that it is not necessary to add extra liquid or past flux. Do not keep the iron on the joint or continue adding solder if a connection is not made after two trials. This will only damage the components or the circuit board.

To Solder ICs and Other Small Components. Use only a low-wattage iron and sharp tip to avoid excess heat. Also, use 0.031-inch diameter solder to help control the amount of solder deposited. Provide a heat sink by using long-nose pliers to grasp the lead between the component package and the portion to be soldered.

After completely soldering a pc board, an inspection of the soldered joints is suggested. A toenail clipper can be used to trim any lead ends so they don't protrude too far from the solder. To help in the inspection, a bright spotlight and low-power lens can be used to examine each joint. A sharp tool can clear away dross, solder bridges, or anything that looks suspicious between solder pads, and a toothbrush can be used to clean the solder joint. To make sure that all joints are checked, a drop of red nail polish can be placed on each after inspection. A minute spent checking a board can save an hour of trouble-shooting later on.

Another problem can arise when a plastic capacitor appears to be "soldered" in place, but is not making an electrical connection. This often happens when a small "sleeve" of nonconducting plastic extends from the capacitor body slightly down each lead. The solder will hold the plastic to the pad, but an electrical connection may not result. Use long-nose pliers to break away the unwanted plastic.

Since your fingers may be dirty or oily, handle parts and circuit boards as little as possible. If there is any question of oily spots on a part, clean it using isopropyl alcohol or fine steel wool. If you use steel wool, use lint-free cloth to remove all vestiges of the wool from the parts or board.

To Summarize:

- (1) Use clean new parts and circuit boards.
- (2) Use 60/40 or 50/50 tin-lead alloy solder with an activated rosin core. Liquid or paste rosin flux may be used to improve wetting when necessary.
- (3) Use the proper wattage soldering iron based on the amount of soldering to be done and the type of components being soldered.
- (4) Use the proper soldering sequence—tip to parts, solder to parts—solder away from parts—tip away from parts.
- (5) Use patience.
- (6) Practice.

PEAK UNLIMITER

AUDIO DYNAMIC RANGE PROCESSOR

Increases system gain when passing peaks that may have been limited during the original recording process

BY JOHN SUTTON

LIVE music can easily have a dynamic range exceeding that of current analog recording and playback systems. To "fit" onto an analog tape or disc, this dynamic range must be reduced. Generally, this is accomplished by manipulating the system gain as the signal passes through, making the loud passages softer and the soft passages louder. *Compression* is moderate application of this technique throughout the dynamic range. *Peak limiting* cuts gain radically if the signal exceeds a determined level.

Although this approach works, it sacrifices some of the realism in the reproduction of the program material. But not all of the 30 or so dB of dynamic range subtracted by the compression and limiting process is irretrievably lost. It can be restored by electrical processing complementary to what was done in recording. Most often, the exact nature of the original processing is unknown, making the complementary nature of the restorative action a hit-and-miss proposition. Expansion (the inverse of compression) that is not correct is often unsatisfactory, but the ear is more tolerant of errors in peak unlimiting.

The Peak Unlimiter described in this article "stretches out" what's left of the original peaks to enhance dynamic range. It is low in cost and easy to build and use.

Peak Unlimiting VS. Expansion. Peak unlimiting differs from expansion in that it need not change the system gain as radically to accomplish what it does. This means that attack and release times can generally be faster than in a linear expander without causing audible side effects such as "pumping and breathing." As shown in Figures 1A and 1B, linear expansion may use as much as 20 dB of gain change, while peak unlimiting uses 7.5 dB.

Another advantage of peak unlimiting is that it allows the processor to control each channel independently. Were such an arrangement used in a linear expander, the stereo image of the program material would suffer greatly. Common gain control avoids this, but causes another problem. The effect of synchronized gain change is quite noticeable in music that favors one channel, especially with low-frequency material. To the ear, this may

result in an annoying "swishing" sound that we would like to avoid.

The Peak Unlimiter makes independent gain control work in its favor. Since we're interested in processing short-term peaks with a modest change in gain, attack and release times can be optimized. Audible signal degradation is thereby minimized.

About the Circuit. The Peak Unlimiter, shown schematically in Fig. 2, is designed around two quad BiFET operational amplifiers. The first, *IC1*, performs the actual signal processing, and the other, *IC2*, forms the heart of a gain-change indicator that is common to both audio channels. The signal-processing stages of both channels are identical, so further reference will be made only to the left channel.

Potentiometers *R1A* and *R2* couple a portion of the input signal to capacitor *C1*, which passes ac but blocks any dc level. The signal is applied to the noninverting inputs of *IC1A* and *IC1B* by means of *R4* and *R8*. Diode *D1* rectifies the output of *IC1A*, and capacitor *C2* filters the pulsating dc into a smooth level. This dc level is applied to the gate of FET *Q1* via *R9*

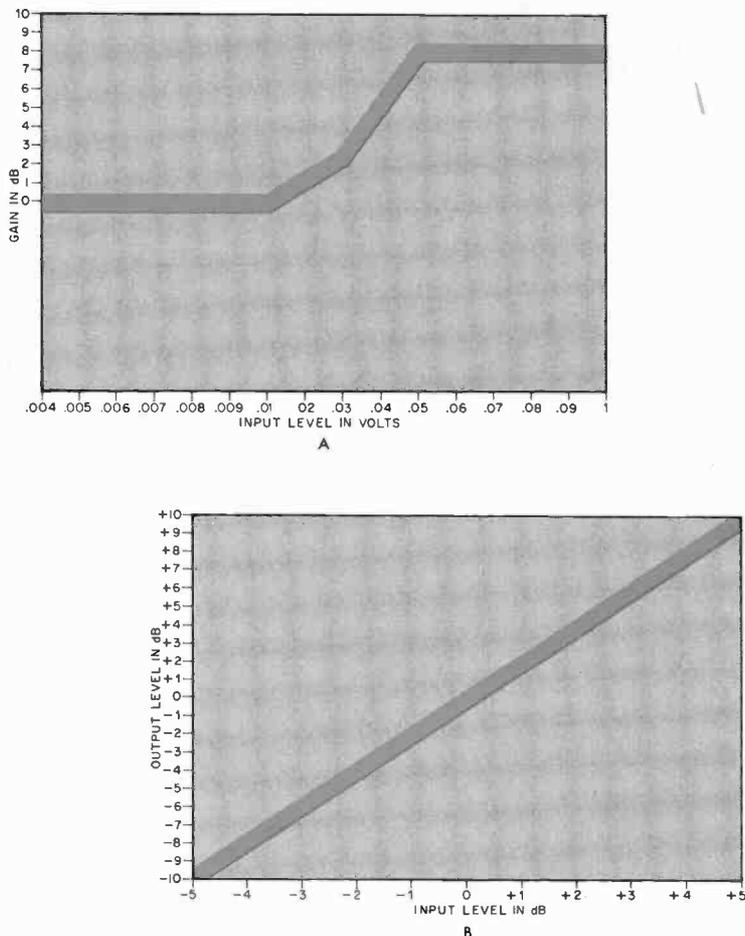


Fig. 1. Peak unlimiting (A) shows a 7.5-dB change, while linear expansion (B) shows a 20-dB variation.

when switch *S1* is in its open position. The time constant associated with this rectifier/filter network has been chosen for optimum project performance. Diode *D1*, a 1N82 germanium type, was carefully chosen for the required dynamic characteristics. Substitution of another diode type may degrade performance.

The drain of *Q1* is connected to the inverting input and feedback resistor of *IC1B*. Its source is grounded. The channel (drain-to-source) resistance of the FET depends on the dc level applied between its gate and source, which in turn depends on the amplitude of the input signal. A large input-signal amplitude results in a large gate-to-source control voltage and, hence, less channel resistance and greater gain. When *S1* is closed, the channel resistance of *Q1* and the gain of stage *IC1B* are constant. No peak unlimiting occurs when the switch is closed.

The output of *IC1B* is routed to jack *J3* by coupling capacitor *C3* and to the input of voltage follower *IC2A*.

Diodes *D3* and *D4* rectify and feed the output of *IC2A* to the inverting and noninverting inputs of differential dc amplifier *IC2B*. Similarly, the output of *IC2C* (the voltage follower in the right-channel portion of the circuit) is rectified and applied to the inputs of *IC2B* by means of *D5* and *D6*. Tricolor emitter *LED1*, which consists of a red LED and a green LED connected back to back and housed in a single package is driven by the output of *IC2B* via current limiter *R23*.

The indicator circuit alerts the user to changes in gain. If the differential dc input voltage is negative, the red section of *LED1* becomes forward biased. In operation, faint red flickers indicate that gain changes of approximately 1.9 dB are taking place. If the differential dc input voltage is positive, the green emitter in *LED1* becomes forward biased. When this happens and the LED flashes green, a gain change of approximately 7.5 dB is taking place.

As is the case with *D1* (and *D2*), the diodes selected for use as *D3* (and

D5) and *D4* (and *D6*) have been specified for their dynamic characteristics. Silicon diode *D4* has a higher conduction threshold than *D3*. This makes possible the desired visual indication of gain changes, because the red section of *LED1* will be firing at lower levels than the green section, which is forward biased only during relatively large changes in gain.

The power supply, shown schematically in Fig. 3, is of fairly conventional design. Transformer *T1* has a fuse-protected primary and a grounded secondary center tap. The outputs of full-wave bridge rectifier *D7* through *D10* are filtered by *C8* and *C10*. Regulators *IC3* and *IC4* generate stable +15- and -15-volt outputs for the rest of the circuit. Capacitors *C9* and *C11* improve the transient response of the IC regulators and ensure low effective power-supply impedances.

Construction. Printed-circuit assembly techniques are recommended in building the Peak Unlimiter. A full-size etching-and drilling-guide for a suitable pc board appears in Fig. 4, and the complementary component-placement guide appears in Fig. 5. Alternative construction techniques such as point-to-point or wrapped-wire assembly can be employed, but care should be taken to avoid ground loops and circuit instability. The use of IC sockets or Molex Soldercons is highly recommended. To ensure close tracking between channels, match *Q1* and *Q2* for their actual values of key parameters— I_{DSS} , V_{GSS} , and g_m .

Observe the polarities and pin basings of electrolytic and tantalum capacitors and of semiconductors. Note particularly that the pin basings of regulators *IC3* and *IC4* differ. The use of a radiation (hum) shield for *T1* is recommended. One can be fashioned by cutting a piece of sheet tin to fit and wrapping it around the body of the transformer. Trimmer potentiometers *R2* and *R11* are not mounted on the pc board: they can be soldered directly to the lugs of dual potentiometer *R1*. Use shielded cable for connections between the input jacks and the dual potentiometer, between the trimmer potentiometers and the circuit board, and between the pc board and the output jacks. Finally, house the project in a metal enclosure.

Initial Adjustment. Patch the Peak Unlimiter into your stereo system at some line-level point, such as a tape-monitor loop, or between the preamplifier outputs and the power-amplifier inputs. The only prelimina-

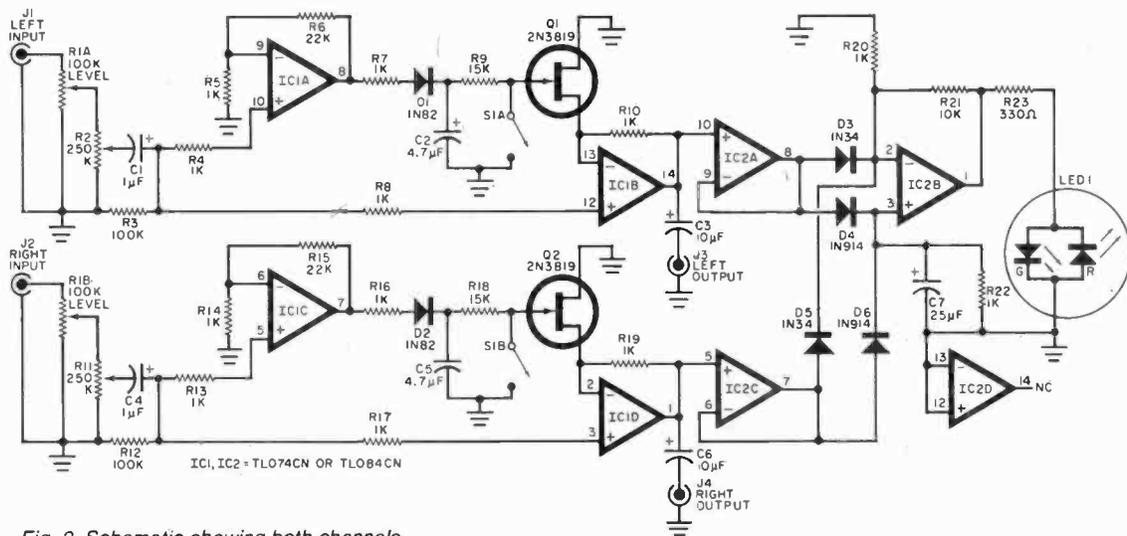


Fig. 2. Schematic showing both channels of the Peak Unlimiter circuit and LED indicator.

PARTS LIST

- C1,C4—1- μ F, 35-V tantalum capacitor
- C2,C5—4.7- μ F, 25-V, radial-lead aluminum electrolytic
- C3,C6—10- μ F, 16-V, axial-lead aluminum electrolytic
- C7—25- μ F, 25-V, axial-lead aluminum electrolytic
- C8,C9,C10,C11—1000- μ F, radial-lead aluminum electrolytic
- D1,D2—1N82 germanium signal diode (see text)
- D3,D5—1N34 germanium signal diode (see text)
- D4,D6—1N914 silicon switching diode (see text)
- D7,D8,D9,D10—1N4002 rectifier
- F1— $\frac{1}{4}$ -ampere fast-blow fuse
- IC1,IC2—TL074CN or TL084CN quad Bi-FET operational amplifier
- IC3—LM340T-15 + 15-volt regulator

- IC4—LM320T-15 — 15-volt regulator
 - J1,J2,J3,J4—RCA phono jack
 - LED1—Tricolor light-emitting diode (Radio Shack 276-035 or equivalent)
 - Q1,Q2—2N3819 n-channel FET (see text)
- The following, unless otherwise specified, are $\frac{1}{4}$ -watt, 5% tolerance, carbon-composition fixed resistors.
- R1—100-k Ω , linear-taper dual potentiometer
 - R2,R11—250-k Ω , linear-taper trimmer potentiometer
 - R3,R12—100 k Ω
 - R4,R5, R7, R8, R10, R13, R14, R16, R17, R19, R20, R22—1 k Ω
 - R6,R15—22 k Ω
 - R9,R18—15 k Ω
 - R21—10 k Ω
 - R23—330 Ω
 - S1—Dpst miniature toggle switch

- T1—35-V, 65-mA, center-tapped transformer (Triad F-227X or equivalent)
- Misc.—Suitable enclosure, printed-circuit or perforated board, standoffs, IC sockets or Molex Soldercons, LED mounting collar, terminal strips, line cord, shielded cable, hookup wire, control knob, suitable hardware, solder, etc.
- Note—The following is available from XEN, Box 2, Scranton, PA 18504: a complete kit of parts (not including enclosure), No. X-1980, for \$59.00 post-paid in the United States. Also available separately are Q1 and Q2, No. XMP-3819, for \$5.00 a matched pair; etched and drilled printed-circuit board, No. X-1980-PCB, for \$11.00; both postpaid in the U.S. Pennsylvania residents, add state sales tax. Allow four to six weeks for delivery. Add 2 weeks for personal check to clear.

ry adjustments that must be made are of trimmer potentiometers *R2* and *R11*. Close switch *S1* so that the peak unlimiting is defeated. Place the MODE switch of the preamplifier in its MONO position, rotate the control knob of the preamplifier's BALANCE potentiometer to its fully left position, and adjust the control knob of the project's front-panel LEVEL control (*R1*) so that the wipers of the dual potentiometer are at the midpoint of their travel. Adjust trimmer potentiometer *R2* so that the signal level at jack *J3* equals that at *J1*. This can be done aurally, by monitoring the loudspeaker output while alternately routing the drive signal through and around the Peak Unlimiter.

A more precise adjustment can be made if you have access to a signal generator and an oscilloscope. Connect the signal generator to a line-level input of the preamplifier and the

probe of the oscilloscope to *J1*. Adjust the generator's output-level control for a 1-volt p-p signal at *J1*. The output frequency of the generator is not critical, but should be approximately 1000 Hz. Then shift the scope probe to *J3* and adjust *R2* for a 1-volt p-p output level.


Next, connect a pair of stereo headphones using clip leads to the "hot" sides of output jacks *J3* and *J4*. Do not make any connection to the common (shell) lead of the headphones.

With the stereo preamplifier still providing a monaural drive signal, adjust *R11* for an output null. If an oscilloscope is being used, connect its probe(s) to the project outputs and set the scope to read differential voltage. Then adjust *R11* for an output null. Note that both channels of the project must be driven by the same signal to make valid adjustments of the trimmer potentiometers.

Now disconnect the clip leads or scope probe(s) and install the cover.

(Continued overleaf)

Fig.3. Power supply provides regulated bipolar 15 volts for op-amp power.

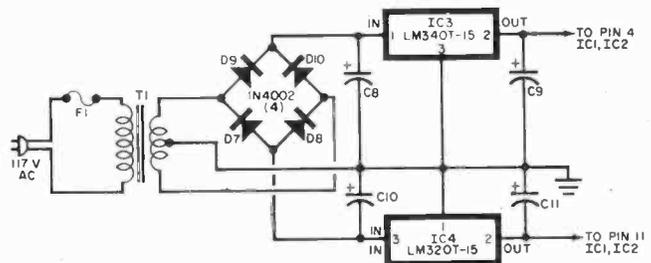

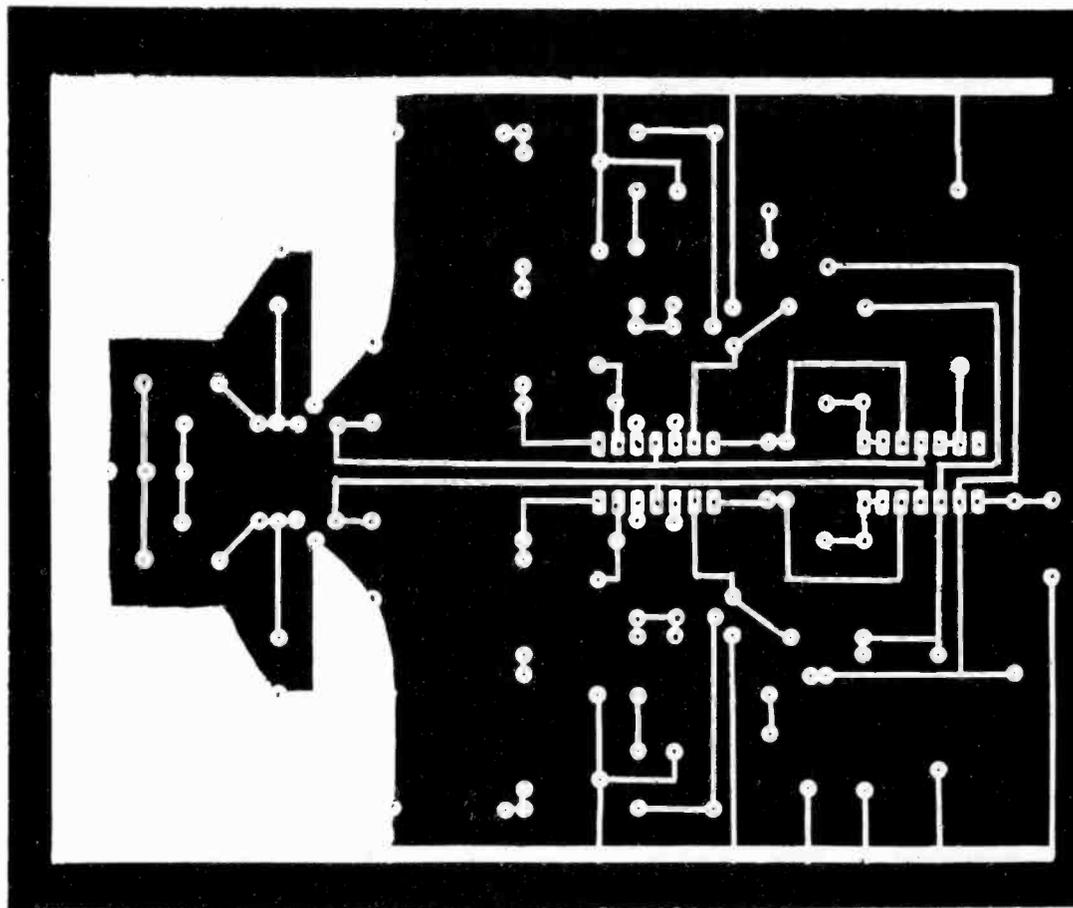


Fig. 4. Etching and drilling guide for pc board.

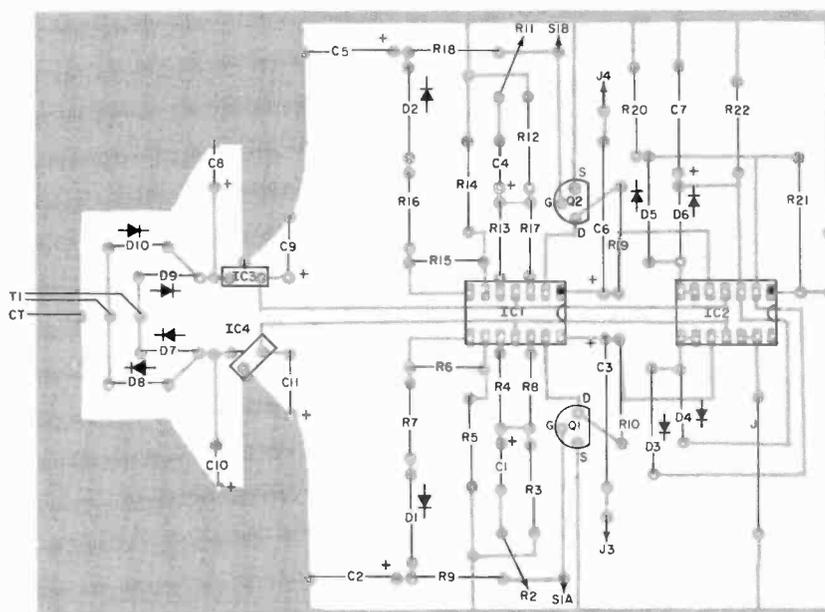


Fig. 5. Component-placement guide for pc board.

Using the Peak Unlimiter. Route audio signals through the project, and monitor the loudspeaker outputs and indicator *LED1*. The author recommends that *LEVEL* control *R1* be adjusted so that, with *S1* in its open position, *LED1* glows red most of the time (except in the absence of input signals) and flashes green on the loudest signal peaks. This recommendation is somewhat arbitrary, however, and your ears should be the final judge. Opening and closing *S1* will allow you to make quick comparison between the processed and unprocessed signal. You might find that the nature of the program material dictates which setting gives the most pleasing results.

An apparent improvement in the program material's signal-to-noise ratio will be realized because of a masking effect introduced by the Peak Unlimiter. Keep in mind that signal peaks are accentuated by several dB, so some caution should be observed, at least at first. If the audio system does not have sufficient headroom, amplifier clipping and damage to the loudspeakers may occur. ♦

AN ALARM FOR TOXIC GASES

Detects oxygen-hungry gases such as carbon monoxide and methane. . . . sounds a warning before dangerous concentrations are reached

BY CASS LEWART

WHEN a lethal fire starts, flame and smoke are not the only killers. Colorless, odorless carbon monoxide gas (CO) has been known to kill or incapacitate people—often far from the fire itself. One factor that makes CO such a stealthy, insidious assassin is its ability to elude conventional smoke detectors. These devices are similarly insensitive to dangerous hydrocarbon gases like methane (CH₄), a toxic compound that is the chief component of natural gas.


The Gas Alarm described here has been designed to sound its warning *before* dangerous levels of poisonous gases accumulate. The Gas Alarm should be considered complementary to, and not a replacement for conventional smoke detectors, as it will *not*

respond to ionized gases generated by fire unless the fire is smoldering in an enclosed area lacking oxygen. This project has the advantage of being self-powered, thus providing portable protection both at home and in hotels or motels when you travel.

The alarm is based on an inexpensive semiconductor sensor whose electrical resistance changes when its active surface is exposed to gases such as carbon monoxide, methane, butane, and alcohol vapors that have a strong affinity for oxygen. (These are known as *reducing gases*.) The sensor element is enclosed in a small capsule and protected by a stainless steel mesh, while a low-power heater activates the sensor element and purifies it after exposure to gas.

Circuit Operation. As shown in Fig. 1, transformer *T1*, fullwave rectifier *RECT1*, resistor *R2*, and filter capacitor *C1* make up the line-powered power supply for 5-volt regulator *IC1*. Resistor *R1*, in conjunction with rectifier *D1*, maintains the charge on the rechargeable cells in *B1*, while diode *D2* allows *B1* to power the circuit in stand-by mode when the line power is interrupted. Under these conditions, *D1* is reverse biased and battery power flows through forward-biased diode *D2* to power the circuit. The regulated output from *IC1* maintains a fixed heater voltage for gas sensor *TGS1* to provide uniform sensitivity. The combination of *R3* and *LED1* forms a power-on indicator.

When gas is present at *TGS1*, the

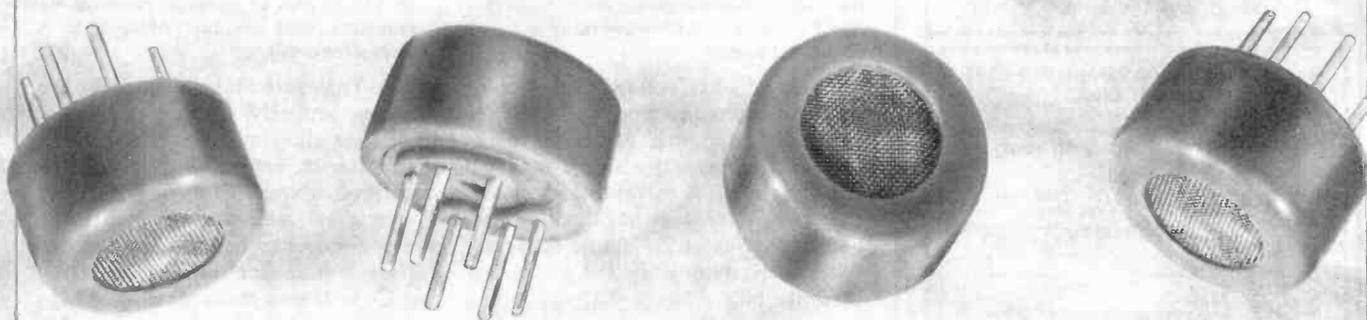

FREE

The newest in home computers, fine stereo components, color TV, HAM radio, precision test equipment, innovative electronics for the home—all in easy-to-build, money-saving kits.

Send today for your **FREE Heathkit® Catalog**



If coupon is missing, write Heath Co., Dept. 010-812 Benton Harbor, MI 49022

Send to: Heath Co., Dept. 010-812 Benton Harbor, MI 49022.

Send my free Heathkit Catalog now. I am not currently receiving your catalog.

Name _____

Address _____

City _____ State _____

CL-724A Zip _____

gas alarm

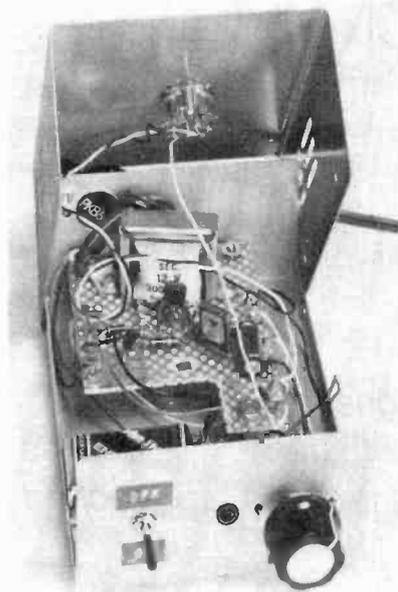


Photo of the author's prototype.

resistance of its sensor element drops, raising the voltage applied across calibration potentiometer *R4*. The rotor of *R4* is connected to the gate of

on perf board or multi-lug terminal strips using point-to-point wiring. Mount the socket for sensor on top of the cabinet for maximum exposure to surrounding air, and mount the alarm on the side or back of the cabinet for best audio output. The six rechargeable cells forming *B1* can be mounted in readily available battery holders.

Adjustment. (1) Plug the Gas Alarm into a 117-volt ac outlet; (2) rotate *CAL* control *R4* fully CCW for minimum resistance between the SCR gate and ground; (3) apply power and allow the sensor to stabilize for 1-2 minutes, then rotate the *CAL* control clockwise till the alarm sounds; (4) rotate *CAL* control CCW till the alarm stops. The alarm is now ready for operation. Test the system by rubbing a drop of alcohol between your fingers, near the sensor. When the alarm sounds, repeat steps two through four.

The rechargeable batteries are trickle charged when the alarm is plugged into an ac outlet, and will be fully charged after approximately 24

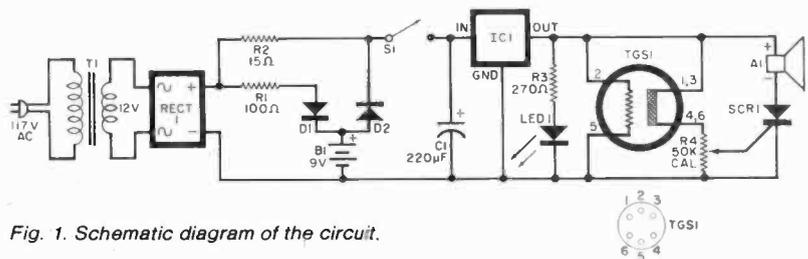


Fig. 1. Schematic diagram of the circuit.

PARTS LIST

- A1—Piezoelectric buzzer (Radio Shack 273-060 or similar)
- B1—Battery (six rechargeable 1.5-V cells)
- C1—220- μ F, 16-V electrolytic
- D1, D2—200-V, 1-A silicon diode
- IC1—5-V regulator (Radio Shack 276-1770 or similar)
- LED1—Red LED (optional)
- R1—100- Ω , 1/2-W resistor
- R2—15- Ω , 1-W resistor
- R3—270- Ω , 1/2-W resistor (optional)
- R4—50-k Ω linear potentiometer
- RECT1—50-V, 1-A full-wave rectifier
- S1—Spst switch

- SCR1—200-V, 6-A SCR (Radio Shack 276-1067 or similar)
- TGS1—Gas sensor (See note)
- T1—12-V, 1-A transformer (Radio Shack 273-1505 or similar)

Misc.—6" x 4" x 2 1/2" enclosure with cover, perf board or terminal strips, etc.
 Note—The following is available from C & R Electronics, Box 217, Holmdel, NJ 07733: Pretested gas sensor, with socket, \$10.95 plus \$1 postage/handling. NJ residents, add 5% tax. Allow 2 to 3 weeks for delivery.

SCR1, and when voltage at that point reaches approximately 0.3 V, *SCR1* turns on, supplying power to alarm *A1*. The piezoelectric alarm specified for *A1* interrupts current flow periodically, so *SCR1* does not latch permanently on. Switch *S1* allows for faster battery charging while the gas sensor is turned off.

Construction. The project will easily fit in a 6" x 4" x 2 1/2" metal cabinet, and all components except the alarm and gas sensor can be mounted

hours. To ensure that the batteries are working properly, unplug the alarm and, after allowing it to stabilize with the batteries, repeat the alcohol test described above. The fully charged AA-size batteries should operate the sensor for over an hour during a power failure. For longer standby operation use C- or D-size rechargeables. These will operate the alarm longer, but also require longer charging time. When the alarm is not in use, open *S1* to protect batteries from discharging through *IC1*. \diamond

SINGLE-LED ANALOG METER

Complete LED changes "color" with input voltage

BY DAVID LEITHAUSER

THERE are many ways that an electronic measuring circuit can display information. Numerical data can be displayed on LED or LCD readouts, analog meters, or similar devices, while on/off indications can be made via a low-cost discrete LED or lamp. Another possibility is to show a changing variable as a series of color variations, taking advantage of a new low-cost, multicolor LED.

This new device consists of a pair of LEDs, one emitting red light and the other green, oppositely polarized and enclosed in a common plastic housing with two electrical leads. Applying current in one direction causes only the forward-biased LED to glow, while the reverse-biased LED remains dark. If the current polarity is rapidly alternated, then the composite LED will glow yellow or greenish red, depending on the duty cycles of the currents in the two directions. This is the operating principle behind the Single

LED Analog Meter. The schematic diagram of the circuit for the meter is shown in Fig. 1.

Circuit Operation. Op amp *IC1A* generates a ramp waveform at point A that drives amplifier *IC1B* via *R4* (*R5* acting as the gain-determining feedback resistor) with the amplified ramp voltage applied to the noninverting input (+) of comparator *IC1C*. The input voltage (referenced to ground) applied to the inverting (-) input is compared with the instantaneous ramp voltage applied to the noninverting input (also referenced to ground). If the input voltage is higher than the ramp voltage, the output of *IC1C* is near ground, and when the input voltage is lower than the instantaneous ramp voltage, the output of *IC1C* is near the level of the positive supply voltage.

The output of *IC1C* is connected to the inverting input of *IC1D* with the

dual-color LED connected like a feedback element in conjunction with current-limiting resistor *R7*. When the output of *IC1C* is positive, the output of *IC1D* is at ground. Thus, current will flow from the output of *IC1C*, through *R7*, and the forward-biased LED to the virtual ground of *IC1D*. This causes that LED to glow. Since the other LED in the package is reverse-biased, it remains dark. When the output of *IC1C* goes to ground, the output of *IC1D* goes high, and current flows the opposite way, causing the now forward-biased LED to glow while the other goes dark.

Thus, contingent on the level of the input signal, the single LED can assume either of two distinct colors, or a combination of the two colors when the input voltage is centered on the ramp voltage.

The builder can decide which of the two colors within the LED can represent the high or low inputs, and ar-

PARTS LIST

- C1—0.01- μ F disc ceramic capacitor
- D1, D2—PTC205, 1-V diode (see text)
- IC1—Quad op amp (Radio Shack 276-1714 or similar, see text)
- LED1—Two-color LED (Radio Shack 276-035)
- R1, R2, R3—10-k Ω , 1/2-W resistor
- R4, R6—330-k Ω , 1/2-W resistor
- R5—1-M Ω , 1/2-W resistor
- R7—See text
- R8, R9—3.3-k Ω , 1/2-W resistor

Note: A pc board (RW-205) is available for \$5.25, plus \$1.25 postage and handling from Danocinths Inc., Box 261, Westland, MI 48185. Michigan residents please add 4% sales tax.

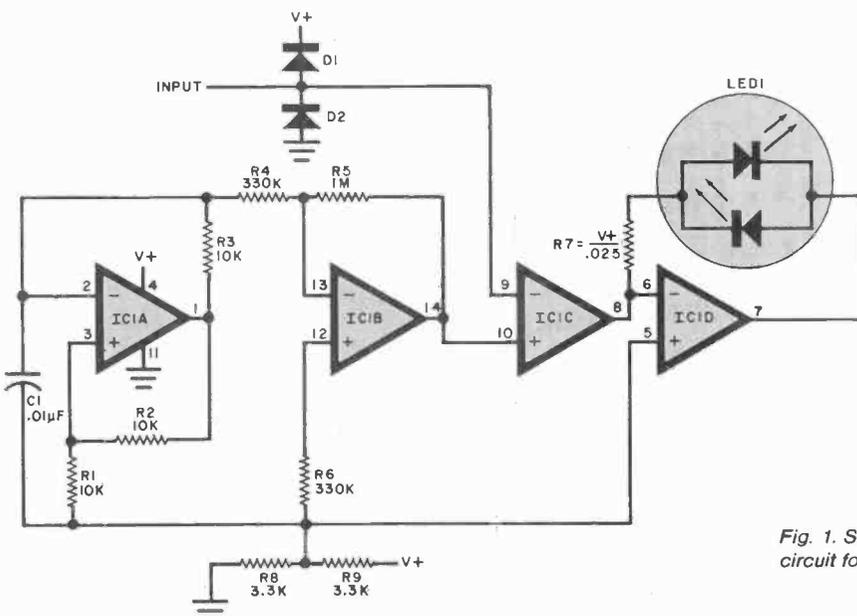


Fig. 1. Schematic diagram of the complete circuit for the LED Analog Meter.

analog meter

range the LED polarity accordingly. (It is suggested that red be used for higher values.) Protection diodes *D1* and *D2* are included to ensure that the input voltage level does not go above the power supply positive voltage or below $-1V$ with respect to ground. If desired, one or more conventional 1N914 or similar silicon diodes can be used in place of the 1-volt diodes specified. Each silicon diode drop is about 0.6 volt, so two in series can provide a limit of about 1.2 volts. Since a single-ended power supply is used, the network of *R8* and *R9* is used to bias the noninverting inputs of the three operational amplifiers

Construction. The circuit can be assembled on a small pc board such as

0.025. For example, with a 9-volt supply, *R7* is $9/0.025$ or 360 ohms (the nearest standard value can be used). Operating power can be any value between 5 and 35 volts dc. If desired, discrete op amps may be used for the four stages.

Applications. The Single LED Analog Meter can be used any place an approximate measurement is to be made. For example, a thermistor can be used to convert temperature to a voltage level that is applied to the input. The LED is then arranged so that a rise in temperature causes the red portion to glow, while lower temperatures keep the green LED lit. The thermistor can be thermally coupled to the output stages of an audio power


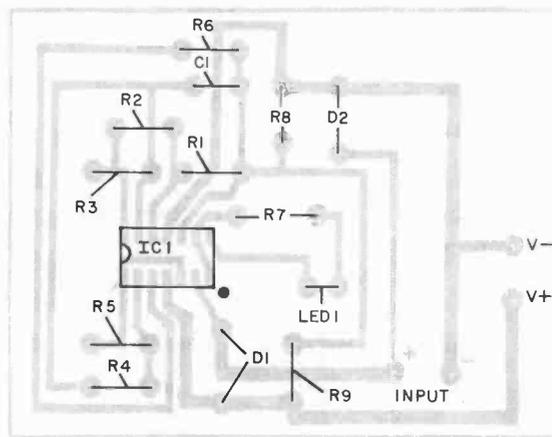


Fig. 2. Full-size etching and drilling guide (above) and component-placement guide (left) for the project's printed-circuit board.

that shown in Fig. 2. Observe the polarity of input protective diodes. A socket may be used for the IC. The polarity of *LED1* is optional.

The value of current-limiting resistor *R7* is determined by dividing the power supply operating voltage by

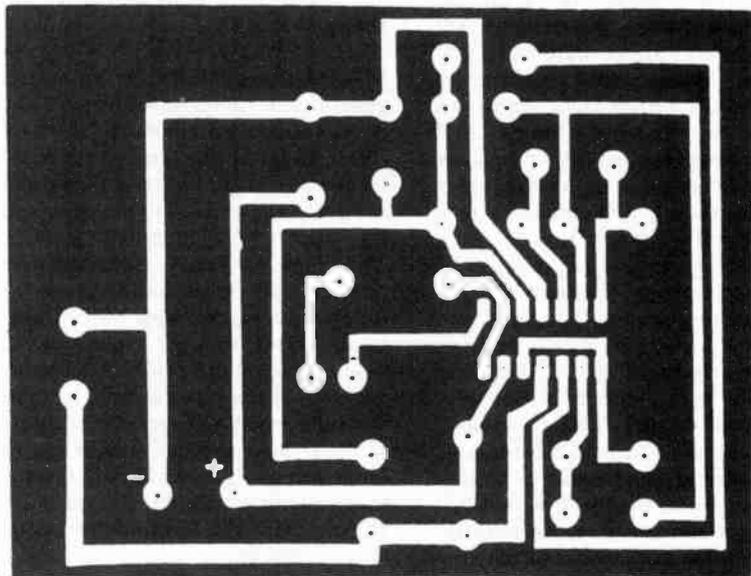amplifier to keep an eye on heat-sink temperature. Or, it can be used for an automotive temperature gauge. The circuit can be used to monitor a high voltage if a suitable voltage divider is used, or monitor a very low voltage if a dc amplifier is used at the input. ◇




18 New Modules: Compact versatile preamps and mixers for every audio application!

These modules are complete in cases and include latest design clip-on edge connectors. Save you time and money and give excellent performance. All modules fully compatible with each other and with ILP power amplifiers and power supplies. Typical performance of all types include frequency response 15 Hz - 50 KHz, distortion typically less than 0.005% (at 1 KHz), and signal/noise ratio better than 80 db. Modules HY6 to HY13 measure $1\frac{1}{4} \times \frac{3}{4} \times 1\frac{1}{4}$ ". HY66 to HY77 measure $3\frac{1}{2} \times \frac{3}{4} \times 1\frac{1}{4}$ ". Complete connection data provided. All modules operate from $\pm 15V$ to $\pm 30V$ maximum. HY67 can only be used with PSU30 power supply unit. For easy mounting we recommend B6 mounting board (for modules HY6 - HY13) @ \$3.75; and B66 (for HY66 - HY77) @ \$4.75. These modules are so reliable they carry a 5-year replacement warranty!

- HY6 Mono PreAmp. Mic/Mag. cartridge/Tuner/Tape/Aux + Volume/Bass/Treble. 10 mA. **\$25.95**
- HY7 Mono Mixer. To mix eight signals into one. 10 mA. **\$19.95**
- HY8 Stereo Mixer. Two channels, each mixing five signals into one. 10 mA. **\$24.95**
- HY9 Stereo Preamp. Two channels mag. cartridge/Mic + Volume. 10 mA. **\$26.95**
- HY11 Mono Mixer. To mix five signals into one + Bass/Treble controls. 10 mA. **\$28.95**
- HY12 Mono Preamp. To mix two signals into one + Bass/Midrange/Treble. 10 mA. **\$26.95**
- HY13 Mono VU Meter. Programmable gain. LED overload driver (meter not included). 10 mA. **\$23.95**
- HY66 Stereo Preamp. Mic/Mag. cartridge/Tape/Tuner/Aux + Volume/Bass/Treble/Balance. 20 mA. **\$48.95**
- HY67 Stereo Headphone Amplifier. Will drive headphones in the range of 4 ohm - 2K ohm. 80 mA. ... **\$49.95**
- HY68 Stereo Mixer. Two channels, each mixing 10 signals into one. 20 mA. **\$31.95**
- HY69 Mono Preamp. Two input channels of mag. cartridge/Mic + Mixing/Volume/Treble/Bass. 20 mA. **\$41.95**
- HY71 Dual Stereo Preamp. Four channels of mag. cartridge/Mic. + Volume. 20 mA. **\$42.95**
- HY73 Guitar Preamp. Two Guitar (Bass/Lead) and Mic + separate Volume/Bass/Treble + Mix. 20 mA. **\$48.95**
- HY74 Stereo Mixer. Two channels, each mixing five signals into one + Treble/Bass. 20 mA. **\$45.95**
- HY75 Stereo Preamp. Two channels, each mixing two signals into one + Bass/Mid-range/Treble. 20 mA. **\$45.95**
- HY77 Stereo VU Meter Driver. Programmable gain/LED overload driver. 20 mA. **\$36.95**

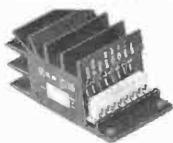AUTOSOUND Power Amp Module INTRODUCTORY PRICE \$29.95



The kind of reliability and performance you have been waiting for in a 12V automotive power amplifier! Use as power booster or drive direct from tape-deck/preamp out. Like all ILP modules, the C15 power booster is encapsulated with integral heatsink, and guaranteed for 5 years. Features include: automatic switch on; selectable input level facility (700 mV or 3V rms); screw-terminal connections; two hole-mount; compact size (4 x 2 x 2"). Output power continuous (typical) 15 watts rms into 4 ohms, freq. response 15 Hz to 30 KHz (-3db), THD 0.1% at 10 watts. Use two for stereo applications.

GLADSTONE 901 Fuhrmann Blvd., Buffalo, NY, 14203.

ELECTRONICS (716) 849-0735
Mail Orders: Check (Certified), or Money

Orders. No C.O.D.'s. Please add 5% shipping.

In Canada: Gladstone Electronics, Toronto, (416) 787-1448

CIRCLE NO. 31 ON FREE INFORMATION CARD


HOBBY SCENE

By John McVeigh, Technical Editor

Checking Diodes

Q. I recently acquired a selection of diodes, and I want to build the AD*ZAP Commercial Killer that was presented in the February 1981 issue. The AD*ZAP receiver employs 1N270 germanium diodes. I know that at least one of my diodes is a 1N270, but I don't know which. Can you tell me how I can find out?—Matt Berent, Baton Rouge, LA

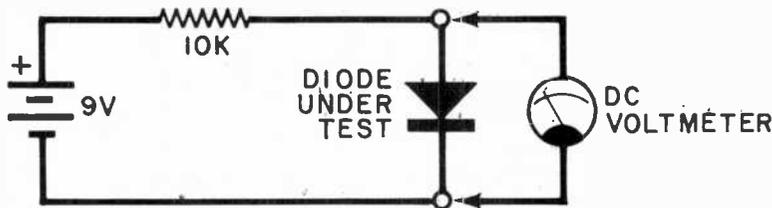A. The simple circuit shown will enable you to distinguish a germanium from a silicon diode. Connect the device to be tested to the circuit as shown so that the



diode will be forward-biased. If you have a lot of diodes to test, build a little test jig that employs binding posts or Fahnestock clips. This will simplify connecting the diodes to the circuit. When the device to be checked is in place, con-

nect the probes of a dc voltmeter across the diode as shown. If the diode is made of germanium, the meter will indicate a voltage drop of approximately 200 mV across the device. If the device under test is made of silicon, the measured voltage will be approximately 600 mV.

Diode action can be verified by reversing the way the diode is connected to the circuit. If the voltage reading is 9 volts, the diode is behaving as an open circuit—as it should under reverse-bias conditions. Note that the circuit will only indicate whether a diode is made of silicon or germanium and whether its junction displays diode action (a simple

good/bad test). However, in the AD*ZAP receiver circuit, the exact germanium diode is not critical. Satisfactory performance should be obtained with any of the common germanium signal diodes (1N34, 1N58, 1N270, etc.).

RFI

Q. In the past, I have built such projects as special-effects units for electronic musical instruments, and have had trouble with interfering radio-frequency signals. Can you give me some tips on how to cut down on this ever-present menace?—Dennis Halsey

A. Radio-frequency interference (RFI) to audio devices is the result of signal rectification. A signal lead or some other conductor acts as an antenna and presents r-f to a semiconductor or some other device which rectifies the signal. (Even a poor solder joint can act as a rectifier.) Once the r-f signal has been rectified, any audio-frequency variations in its envelope can be amplified along with the desired audio signal. To cure RFI, the offending r-f signal must be prevented from reaching the point at which rectification takes place.

There are several tactics that can be employed to achieve this result. The sensitive audio circuit should be housed in a metallic enclosure. Signal cables should have effective shields (many audio ca-

bles are woefully deficient in this respect). Cable shields should be committed to ground at at least one end, but beware of ground loops in high-gain circuits. Keep signal-carrying cables as short as possible.

Inside the project enclosure, use short lead lengths, some of which might have to be shielded. Power-supply buses should be heavily bypassed and should be decoupled with resistors or r-f chokes. Chokes or ferrite beads at high-gain inputs will block the passage of r-f, and bypass capacitors of suitable values will shunt r-f to ground. Capacitor values should be chosen so that their reactances are low at radio frequencies but high at audio frequencies and so that they do not disturb the desired response of the circuit in which they are installed.

An article that appeared in the May 1977 issue of *Stereo Review* describes RFI prevention in audio equipment in some detail. Reprints of the article are available for \$2.00 each (minimum order \$6.00) from *Stereo Review* Reprints, Box 278, Pratt Station, Brooklyn, NY 11205. ◇

New MOSFET POWER AMPLIFIER MODULES



- * State-of-the-art performance
- * Built-in heatsinks
- * Encapsulated circuitry
- * No external parts required
- * Five-year warranty

60, 120 and 240 watt amplifiers utilizing the latest technological advance in audio ... the MOSFET. They provide faster slew rate and complete absence of crossover distortion. They are immune to thermal runaway, increasing long term reliability and eliminating the need for complicated protection circuitry.

Frequency response — 15 Hz — 100 KHz (–3 db). THD (Typical at 1 KHz) — 0.005%. IM (60 Hz and 7 KHz sine wave, 4:1 ratio) — .006%. S/N Ratio (DIN standard) — 100 db. Slew rate — 20 V/uS. Rise time — 3 uS. Input sensitivity/impedance — 500 MV/100k ohm. Output impedance — 4 ohms to infinity. Damping factor — 400.

MOS120 60 watt MOSFET Amplifier (8 ohms) \$ 79.95

MOS200 120 watt MOSFET Amplifier (8 ohms) \$129.95

MOS400 240 watt MOSFET Amplifier (4 ohm). \$199.50

BIPOLAR POWER AMPLIFIER MODULES



- * Built-in heatsinks
- * Five-year warranty

PERFORMANCE SPECIFICATIONS:

Frequency response — 15 Hz — 50 KHz (–3 db). THD (Typical at 1 KHz) — 0.1%. IM Distortion — 0.006%. S/N ratio — 100 db. Slew rate — 15V/uS. Rise time — 5 uS. Input sensitivity/impedance: 500 Mv/100 Kohms. Damping factor — 400. Power rated into 8 ohms (except HY400 rated into 4 ohms).

HY30 (15 watts RMS) \$25.95

HY 60 30 watts RMS) \$29.95

HY120 (60 watts RMS) 59.95

HY200 (120 watts) 79.95

HY400 (240 watts RMS) 99.95

FP480 "Bridges" 2 HY400s for 480 watts RMS ... 20.00

NEW HEAVY DUTY SERIES. With PERMANENT SHORT CIRCUIT PROTECTION. Similar in size, features and performance to bipolar modules.

HD120 (60 watts RMS) \$ 69.95

HD200 (120 watts RMS) 89.95

HD400 (240 watts RMS) 124.95

Rack-Mount Cabinet



\$49.95

Attractive, rugged, professional 19" rack-mount cabinet for easy assembly of your ILP amplifier system. Amplifier modules (2 of) mount on pre-cut back panel. Power supply unit mounts inside chassis. Complete assembly and wiring is a breeze, taking about one hour! Specify which amplifier you will be using: HY120, HY200, HY400, MOS120, MOS200 or MOS400.

Power Supply Units

Circuit boards with all components plus TOROIDAL transformers (except PSU30 and 36). Toroidals are half the size and weight of conventional transformers; and are quieter and more efficient.

PSU50 (± 25V) for 1 or 2 HY50 \$39.95

PSU60 (± 35V) for 1 HY120 51.00

PSU70 (± 35V) for 1 or 2 HY120 64.00

PSU75 (± 45V) for 1 or 2 MOS120 64.00

PSU80 (± 45V) for 1 HY200 65.50

PSU95 (± 45V) for 1 MOS200 72.00

PSU180 (± 45V) for 1 HY400 or 2 HY200 89.50

PSU185 (± 55V) for 1 or 2 MOS200 95.00

PSU36 (± 20V) for 1 or 2 HY30 33.60

PSU30 (± 15V) for combinations of HY6/HY66 series to a maximum of 100 mA or one HY67 22.95

GLADSTONE

Electronics Phone Orders (718) 849-0735

.....
 Gladstone Electronics
 901 Fuhrmann Blvd., Buffalo, NY, 14203
 Name
 Address
 City State Zip
 Charge to () Visa () Mastercard
 Card # Expiry
 Enclosed () check () money order for \$
 Please send

CIRCLE NO. 31 ON FREE INFORMATION CARD

SIMPLE DISPLAY AND OPERATING PROGRAM

BY JACK DOLLHAUSEN

THE simple display and operating system described in this article allows any 1802 user to input machine-language programs, and as a bonus, provide a display readout with any Elf using an 1861 video chip.

The program requires 1K bytes of RAM; 1/2K for display buffer storage, and 1/2K for program and subroutines that do not alter themselves. The I/O commands are compatible with an expanded Elf using an 1861 TV chip. An EF3 flag is required, and this can be supplied by grounding that input through a toggle switch.

The Program. Load the program shown in the Listing starting at M0000. Flip the RUN switch on and enter any two-byte address. The video display will be a column of eight 4-digit addresses with their corresponding data bytes. Set EF3 to logic 0, insert 00 via the INPUT toggle switches and note that when the INPUT switch is turned on, the display scrolls upward through memory. Entering 01 on the switches will produce a down scroll, and 02 will single-step up for each operation of the INPUT switch. To jump the display anywhere in memory, enter 03 and the two-byte address.

Note that the input address is displayed at the bottom of the CRT screen. This is the "active" position, and all operations are performed from this point.

Address an empty memory location (keep in mind that M0200-M03FF is display buffer storage), and make EF3=1. Now with each operation of the INPUT switch, the byte on the toggle switches will be sequentially input into memory. A pointer reminds you that memory is being changed. When finished, return EF3 to logic 0.

To execute a program from any point in memory, set the display to the beginning address of the program to be run and enter 04. The 1861 is disabled by an 04 command, and the machine is running outside the operating program. To return, flip the RUN switch off/on and enter an address. The program you are

INITIALIZATION:

```
0000 F8 01 B1 B2 B3 B8
0006 F8 C9 A1 F8 EA A2
000C F8 81 A3
```

```
000F F8 02 B6 F8 00 A6
0015 F8 00 56
0018 16 96 FB 04
001C 3A 15
```

clear display buffer

```
001E F8 00 B4 F8 25 A4
0024 D4
```

R4 is "main" pgm. ctr.

MAIN PROGRAM:

```
0025 E2 69
0027 37 27 3F 29
002B 6C BE
002D 37 2D 3F 2F
0031 6C AE
0033 37 33
0035 8E FF 07 AE 33 3F
003B 9E FF 01 BE
003F F8 02 B6 F8 00 A6
0045 16
0046 9E 7A D3 9E 7B D3
004C 8E 7A D3 8E 7B D3
0052 16
0053 0E 7A D3 4E 7B D3
0059 86 FB C0 3A 45
005E F8 8B A3 F8 10 D3
```

TV on
ENTER high byte
memory location displayed
ENTER low byte
in RE

RE has top of display
R6 is display buffer pointer
display loop:
R3 is pgm. ctr. for digit
configuration subroutine

one display line
loop for eight lines
display filled

```
0064 3F 64 3E 77
0068 F8 8B A3 F8 8D A6
006E F8 11 D3 2E 6C 5E
0074 1E 30 33
```

ENTER opcode or EF=3
EF3=1, put flag and change
byte
inc display and loop for more

```
0077 F8 8B A3 F8 8D A6
007D F8 12 D3
0080 6C FB 00 3A 87
0085 30 35
```

opcode 00
shift display up

```
0087 6C FB 01 3A 90
008C 2E 2E 30 35
```

opcode 01
shift display down

```
0090 6C FB 02 3A 97
0095 30 33
```

opcode 02
single step display

```
0097 6C FB 03 3A 9E
009C 30 27
```

opcode 03
change display address

```
009E 6C FB 04 3A B3
00A3 61
00A4 2E 9E B0 8E A0
00A9 37 A9
```

opcode 04 (TV off)
run program at :
ENTER high address

```
00AB D0
00AC 00 00 00 00
00B0 00 00 00
```

ENTER low address

R0 is pgm. ctr.

```
00B3 6C FB 05 3A 64
00B8 F8 01 BA F8 EB AA
```

opcode 05 (TV off)
move block of memory

FOR THE EXPANDED ELF

Permits easy machine-language input to an 1802-based system

```

00BE 61 22 EA 37 C1
00C3 3F C3 37 C5
00C7 6C B9
00C9 3F C9 37 CB
00CD 6C A9
00CF 3F CF 37 D1
00D3 6C 1A
00D5 3F D5 37 D7
00D9 6C 2E
00DB 49 5E 1E 89 F3 3A DB
00E2 2A 99 F3 1A 3A DB
00E8 49 5E 30 25
    
```

ENTER beginning add. of data to be moved (high byte)
ENTER (low byte)

ENTER last add. of data to be moved (high byte)
ENTER (low byte)

return for display

TABLE: DIGIT CONFIGURATION

0100	35	2B	2F	39	27	31	41	51
0108	43	45	56	49	3D	4D	20	24
0110	5B	60	66	65	00	00	00	00
0118	00	00	00	00	00	00	00	00
0120	F0	80	C0	80	F0	80	C0	80
0128	80	A0	F0	20	60	20	20	70
0130	10	F0	80	F0	10	F0	90	90
0138	90	F0	10	70	10	F0	80	80
0140	80	F0	80	F0	90	F0	90	F0
0148	10	F0	50	70	50	F0	50	50
0150	50	F0	10	20	40	40	F0	90
0158	F0	90	90	2F	25	25	A5	EF
0160	F8	7C	3E	7C	F8	00	00	00
0168	00	00	AA	00	00	00	00	00
0170	00	00	00	00	00	00	00	00
0178	00	00	00	00	00	00	00	00

SUBROUTINE: DIGIT MAKER

```

0180 D4
0181 39 87
0183 FE FE FE FE
0187 F6 F6 F6 F6
018B A8 08 A8
018E F8 05 A7
0191 48 56
0193 86 FC 08 A6 3B 9D
0199 96 FC 01 B6
019D 27 87 3A 91
01A1 86 FF 27 A6 33 AB
01A7 96 FF 01 B6
01AB 86 FE FE FE FE
01B0 32 B6 FB 80 3A C0
01B6 86 FC 30 A6 3B C0
01BC 96 FC 01 B6
01C0 96 FB 04 3A 80
    
```

Q state identifies hi/lo digit

enter here for single digit
R5 counts 5 lines per digit

SUBROUTINE: TV INTERRUPT

```

01C7 72 70
01C9 C4 22 78 22 52
01CE F8 02 B0 F8 00 A0
01D4 C4 C4 E2 80
01D8 E2 20 A0 E2
01DC 3C D7
01DE 80 E2 20 A0 2F
01E3 34 DE 30 C7
    
```

creating may "eat" the operating program space, so keep the operating program on cassette.

To move a block of memory, address the first memory position to be changed and enter 05. Note that the display blanks. Enter the two-byte beginning address of the data to be moved, and then the two-byte ending address. The display will return when the transfer is complete. Enter a two-byte address to get back in the operating program.

The program uses two subroutines. The TV interrupt routine (M01C7) is a standard 512-byte display for the 1861 chip. The digit maker routine (M0180) provides functions useful in any display requiring hex digits, and has two entry points. If entered at M0181, it will display a digit corresponding to the high or low half byte present in the D register. The main program sets buffer pointer R6 to the position of the upper left corner of the digit in the display, and sets the Q line to specify whether the high or the low digit is to be displayed. Before a D3 is executed, R6, D, and Q must be set and the subroutine leaves R6 pointing to the next digit position in the display. The main program uses the subroutine at M003F-FD to create the display. The routine may also be entered at M018B to produce a symbol or digit of your own design. Following the operations for the pointer at M0068-71 will reveal how this works, and space is provided in the configuration table at M0170-7F.

This program does not alter itself and could be put into ROM. There are, however, three bytes of storage at M01E8-EA which would need to be moved. Putting them at the bottom of the display buffer M03xx will add a line of dancing dots and dashes to the display. Registers R2 and RA point to this storage.


The ability to scan memory and to move stacks makes machine language easier to edit and debug. Keep your loop addresses and X designators straight and you can say almost anything to the 1802 . . . in its own language. ♦

A LOW-BUDGET COURSE IN SOLID STATE CIRCUITS

ED NOLL'S SOLID STATE CIRCUIT FILES VOLUMES I & II provide sensible you-do-it experience with solid-state circuits. Bipolar transistors, field-effect transistors, linear integrated circuits, TTL digital circuits and CMOS integrated circuits are covered. More than 100 basic and advanced circuits. Each circuit is complete, fully explained, and most include suggested procedures for experimentation. All use low-cost, readily available components. Circuits can be constructed quickly on a solderless breadboard. Available from your local electronic distributor.

If you're a student, technician, experimenter, radio amateur, teacher or computer enthusiast, order these invaluable solid-state circuit training programs today.

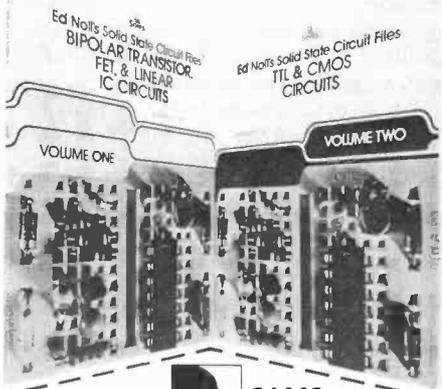VISIT SAM'S AT
WESCON. BOOTH NOS.
1516 & 1518.



Mail to: Howard W. Sams & Co., Inc., 4300 West 62nd St., P.O. Box 7092, Indianapolis, IN 46206.

	Quantity
Volume I—Bipolar Transistor, Fet, & Linear IC Circuits	No. 21753 \$ 7.95
Volume II—TTL & CMOS Circuits	No. 21754 \$ 7.95
Two Volume Set	No. 21752 \$14.50
Amount of order \$ _____	

Add local sales tax where applicable \$ _____

Shipping & handling costs \$ 2.00

Total amount of order \$ _____

Payment Enclosed Check Money Order
 VISA MasterCard Interbank No. _____

Account No. _____ Expiration Date _____

Name (print) _____

Signature _____

Address _____

City _____ State _____ Zip _____

Call toll-free 1-800-428-3696 for the name of your local Sams Book outlet or to order by phone. Offer good in U.S.A. only. Offer expires 1/31/82. AD120

CIRCLE NO. 60 ON FREE INFORMATION CARD

SOLID-STATE DEVELOPMENTS

By Forrest M. Mims

The Billion Transistor Chip?

YOU have probably read about ENIAC, the pioneering electronic digital computer built during World War II. This enormous machine, which filled a room the size of a small house, used 18,000 vacuum tubes, 70,000 resistors, 10,000 capacitors and 7,500 relays and switches. ENIAC weighed 30 tons and consumed 140,000 watts of power.

ENIAC was first operated in November 1945, about the time the average reader of POPULAR ELECTRONICS was born! The Army's Ballistic Research Lab. used the machine from 1946 until it was disassembled in October 1955.

Remarkable advances have been made in computer technology since the power-hungry ENIAC first began making the lights flicker around the University of Pennsylvania, but the basic operating principles of digital computers have not changed much. They still process instructions and data in much the same way they did back in the early 1950's. However, the components and peripherals of today's computers have changed dramatically.

Consider those 18,000 tubes in the old ENIAC: they were the reason ENIAC consumed so much power. There was

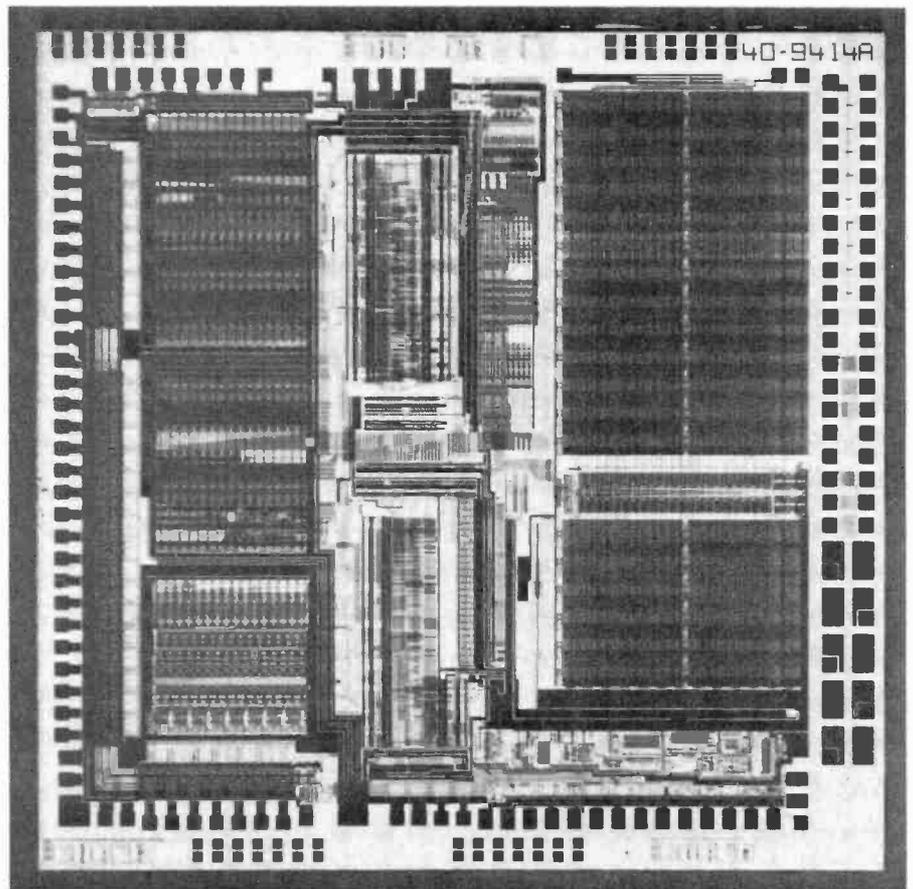


Fig. 1. Photomicrograph of Hewlett-Packard's new CPU containing 450,000 transistors on a single chip.

solid-state developments

even a prediction by one skeptic that the mean time between tube failures would be so brief the computer would operate in short spurts between lengthy delays to find and replace burned-out tubes.

Solid-state switching circuits long ago reduced the power appetite of computers to manageable levels. And, they continue to make possible an amazing degree of miniaturization. Incredible as they are, today's crop of single-chip microcomputers are but a hint of what's to come in the future.

A 450,000-Transistor Microcomputer. One of the latest marvels of miniaturization is the silicon chip whose photomicrograph appears as Fig. 1. This chip, which measures only one-quarter inch on a side, contains 450,000 transistors and functions as the central processing unit of what may be the most powerful 32-bit microcomputer yet developed.

Scientists at Hewlett-Packard's Desktop Computer Division (3404 East Harmony Road, Fort Collins, CO 80525) developed the new CPU chip along with a series of compatible VLSI (very large scale integration) devices containing up to 600,000 transistors per chip. The latter devices include an I/O processor, memory controller, 128K-byte RAM and 528k-byte ROM. Interconnecting these chips provides a complete 32-bit microcomputer.

As significant as the number of transistors per chip is the achievement of interconnections only 1.5 micrometers wide and 1 micrometer apart. To place these tiny dimensions in perspective, a micrometer is twice the wavelength of green light.

The ultranarrow interconnection paths cause current densities too high for the conductors used in ordinary integrated circuits. Therefore, the Hewlett-Packard scientists used tungsten metalization on their chip.

Other VLSI Developments. Hewlett-Packard's new microcomputer was announced at the International Solid-State Circuits Conference (ISSCC) earlier this year. While it is a remarkable

achievement, it may soon be eclipsed by technologies which offer similar component densities, consuming less power.

That's because Hewlett-Packard selected the familiar nMOS process for the new chips. Consequently the CPU chip consumes a hefty seven watts. Other companies in Japan and the United States are thinking in terms of CMOS processes which permit much higher component densities than conventional CMOS while preserving low power-consumption advantage of CMOS.

Bell Laboratories, a relative newcomer in microprocessor technology, has recently developed a 32-bit CMOS microprocessor which incorporates 100,000 transistors on a single chip. While this chip has a fourth the components of the Hewlett-Packard CPU, it consumes only 500 milliwatts.

Another big advantage to CMOS is that differential amplifiers are easily made. This simplifies the inclusion of such on-chip functions as analog-to-digital and digital-to-analog conversion.

What Next? In the mid-1960's, Dr. Gordon Moore of Intel predicted that the number of components integrated onto a single chip would double each year. Figure 2 confirms this prediction and shows that chips containing millions of transistors may possibly be on the horizon.

"Moore's law," as it came to be known, cannot hold forever since it would eventually require devices smaller than their constituent atoms. But look at what is already happening in the big push to make advanced CMOS chips.

Honeywell has just announced a method of forming CMOS chips of sub-micrometer geometry. The firm predicts its new process will permit 250,000 components to be integrated onto a single chip.

Much to the chagrin of the U.S. companies that pioneered integrated circuitry, Japanese firms are making major strides in the development of high-density CMOS. Nippon, for example, makes a CMOS version of the popular 8048 microcomputer. Toshiba and Hitachi


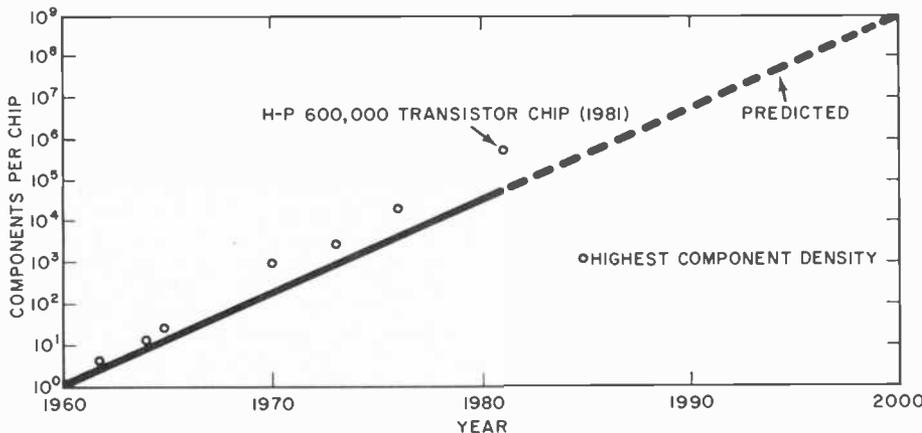


Fig. 2. Maximum number of components per chip from 1960 to the present and projected to the year 2000.

ETCO

CABLE TV CONVERTERS AND OTHER GOOD STUFF!

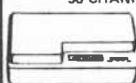SMASHING ALL SALES RECORDS - OUR NEW 30 CHANNEL CABLE TV CONVERTER!



Converts mid & super band cable channels for viewing on your TV set!
No. 346AE047

39⁹⁵

\$34.95 ea / 5

HOT NEW IMPORT! REMOTE CONTROL 30 CHANNEL CABLE TV CONVERTER!



Includes remote TV on-off switch and fine tuning control!
No. 346VA275

89⁹⁵

\$79.95 ea / 5
\$74.95 ea / 10

ETCO MKII WIRELESS - THE ULTIMATE CABLE TV CONVERTER!



Set TV to channel 3 and the hand held remote control does all!
No. 346ZA008

189⁰⁰

VICOR 2000 CONVERTER ELIMINATES PROBLEMS WHEN VIDEOTAPING FROM CABLE TV



Restores your VCR's tape library programming. Restores remote channel control. Enables videotaping of one cable program while watching another.
No. 346VA950

89⁹⁵

UNUSUAL FACTORY SURPLUS MIO-BAND - SUPER-BAND CABLE TV TUNER



Converts cable channels to a common IF frequency. Experimenters - build cable converters, decoders, etc. With schematic No. 346VA342

19⁹⁵

\$17.50 ea / 10

FACTORY SURPLUS UHF TUNERS

4⁹⁵

\$3.95 ea / 10

Brand new production surplus. All solid state. Ideal for experimental work building cable TV converters, etc. No. 346SU099

MINIATURE FM WIRELESS MICROPHONE



Hides in the palm of your hand. Reception on any standard FM radio or receiver.
No. 346VA482

29⁹⁵

\$27.50 ea / 5
\$24.95 ea / 10

QUARTER-MILE WIRELESS MICROPHONE & RECEIVER SYSTEM



FCC approved crystal controlled wireless mike & receiver. All battery operated. Electret wide range response. VU meter.
No. 346VA093

69⁹⁵

\$49.95 ea / 5

FACTORY SURPLUS VHF / UHF "TWIN" VARACTOR TUNERS!



Admiral No. NC 3143 1 BRAND NEW! Ideal for building up existing electronic receiver TV FRONT ENDS! A hard to find item at a sensational price!
No. 346VC308

39⁹⁵

\$34.95 ea / 5

POUMPING! NORELCO ENOLESS LOOP CASSETTES!



4⁹⁵

\$4.49 ea / 10

Impossible to find at any price!
3 minutes - No. 346VA605
6 minutes - No. 346VA606

IN STOCK - THE MURA CORDLESS TELEPHONE SYSTEM!



Answer & originate calls with the wireless handset phone. 600 number recall. Free chargeable. Last number recall. Paging feature. Use with all cordless systems.
No. 346VA274

144⁸⁸

\$129.95 ea / 5

SALE OF QUARTZ BATTERY OPERATED CLOCK MOVEMENTS!



Accuracy of 1 min. / year up to 4 years operation on 1 alkaline C cell. Imported from West Germany. No. 346VA561

9⁹⁵

\$8.95 ea / 6

346VA565 Matching hands \$2.49/set \$1.95/set / 5

20 AMP REGULATED 12VDC POWER SUPPLY!



13.8 vdc no load. 12.5 vdc full load. Easily handles ham station name, auto, SSB, etc. 3000 P.P.P. Brand new. Heavy duty. 110 VAC. No. 346VA394

69⁸⁸

\$59.88 ea / 5

FREE

OUR LATEST 98 PAGE FASCINATING CATALOG is packed in your next order. We'll be glad to send you the catalog number below.

ETCO ELECTRONICS NORTH COUNTRY SHOPPING CENTER PLATTSBURGH, N.Y. 12901

Check with order, please. Visa & MasterCard OK. Inventory, no C.O.D.'s. Add 15% for UPS & Handling (Excess refunded). N.Y. State residents add 7% sales tax. Dealer & Export inquiries invited. Our telephone order desk never closes. Call 1 518 561 8700

CIRCLE NO. 29 ON FREE INFORMATION CARD

solid-state developments

have both developed 4K CMOS memories with ultrafast 18-nanosecond access times. Advanced Japanese research on these and related topics was much in evidence at the ISSCC.

The new generation of high-density ICs will be known as *ultra-large-scale integration* (ULSI). Some of the probable specifications of futuristic ULSI chips were outlined for the ISSCC in a talk by James D. Meindl of Stanford University.

Dr. Meindl predicted we will have chips with from ten million to a billion transistors by the year 2000! According

to his calculations, the size of components can be reduced to 0.25 micrometer. Assuming problems in interconnecting vast numbers of such ultrasmall components can be solved, corresponding increases in chip size provide a good potential for at least 10,000,000 and possibly 100,000,000 transistors per chip. As yet unperfected design techniques and undiscovered technologies may permit billion-transistor chips.


Applications for ULSI. The development of practical ULSI will substantially improve the outlook for such extraor-

dinarily difficult tasks as speech recognition and signature analysis. In the latter category might be chips which will enable precise aircraft or missile identification by detailed processing of radar returns.

Another important application for ULSI will be solid-state memories having the same capacity as some of today's disk memories. Of course, access times will be much faster and physical size much smaller.

Still another major application for ULSI will be entire systems on a single chip. For example, a large mainframe computer might be scaled down to a single ULSI chip. The chip might include all interfacing circuits, several hundred-thousand bits of RAM, several CPUs, onboard analog-to-digital conversion, and other major functions.

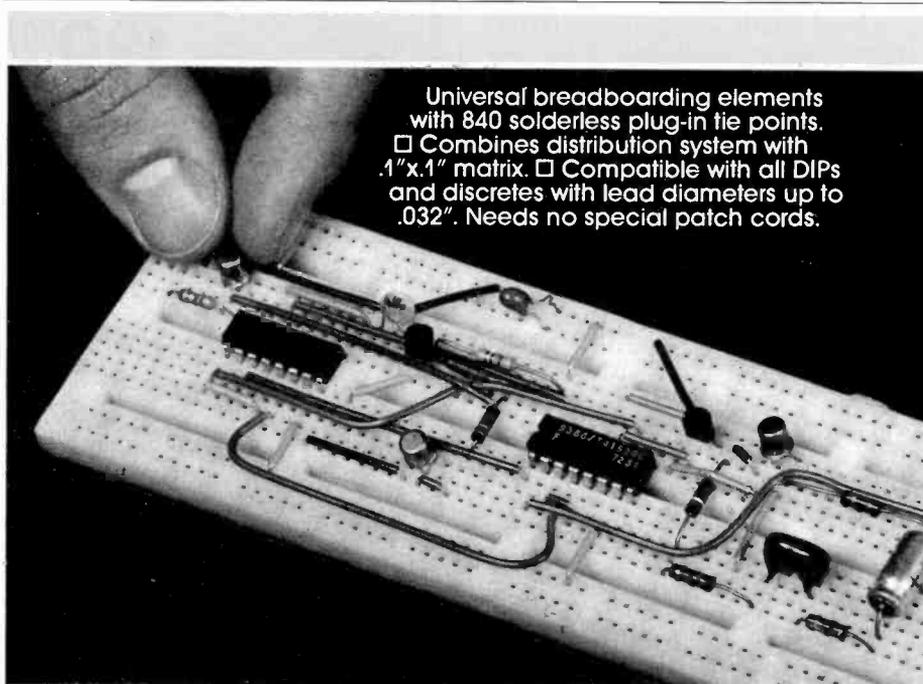These are exciting days indeed for solid-state electronics. I'll keep a close watch on ULSI events and keep you abreast of important developments. In the meantime, if you happen to work for a laboratory or company involved in developing LSI and ULSI chips, please ask your public relations department to put my name on their mailing list.



Universal breadboarding elements with 840 solderless plug-in tie points.
□ Combines distribution system with .1"x.1" matrix. □ Compatible with all DIPs and discretes with lead diameters up to .032". Needs no special patch cords.

Your breadboarding is a super-snap with a solderless A P Super-Strip.


Build a circuit almost as fast as you dream it up. Pull it apart and do another—everything's as good as new.

Our versatile Super-Strip mini-breadboards give you the same top-quality contacts you get in our full-scale ACE All-Circuit Evaluators. Not so "mini," either. You can build circuits with


as many as nine 14-pin DIPs.

Instant-mount backing and quick-removal screws make stacking and racking a snap, too.

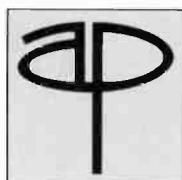Where to buy? Phone (toll-free) 800-321-9668 for the name of your local A P distributor. And ask for our complete A P catalog, The Faster and Easier Book.



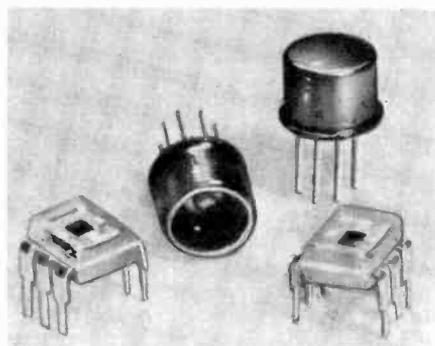A P PRODUCTS INCORPORATED
9450 Pineneedle Drive
P.O. Box 603
Mentor, Ohio 44060
(216) 354-2101
TWX: 810-425-2250
In Europe, contact A P PRODUCTS GmbH
Baumlesweg 21 • D-7031 Weil 1 • W. Germany



Integrated photodetectors with on-chip interfacing made by AEG-Telefunken.

New Photodetector ICs. AEG-Telefunken's Semiconductor Division has announced two highly sensitive integrated photodetectors with on-chip interfacing. The U123P consists of a photodetector, preamplifier, and operational amplifier monolithically integrated on a single chip. It exhibits a 15-dB signal-to-noise ratio when its detector is illuminated by a signal having a power level of only 150 nanowatts.

The U123P requires a single-ended power supply delivering from 4 to 12 volts. Its op-amp output stage provides an open-loop gain of 94 dB. The output of the preamplifier and the input of the op amp are brought out to separate pins to increase the chip's versatility.

AEG-Telefunken's second photodetector IC is designated the U102P. It is similar to the U123P, except that the op-amp output stage has been replaced with a Schmitt trigger. The U102P is supplied in a hermetic 8-lead metal can. For additional information, write AEG-Telefunken Corporation, Route 22, Orr Drive, Somerville, NJ 08876. ◇

PLUG IN to the savings!

Get Stereo Review and Popular Electronics at whopping discounts!

Stereo Review is the music-lover's best friend. Equipment evaluations help you select the best audio gear for your needs. Reviews of important recordings in every category of music help you select the best to build your library at the least cost. Columns by experts help you understand the music industry, the ins and outs of tapes and equipment and the technical side of audio.

Order one or both magazines. Just complete and return the postage-paid order card today!

With this special introductory offer, you can save up to 40% off the full one-year subscription price of **Popular Electronics**...and a big 50% off on a year of **Stereo Review**!

Popular Electronics is the magazine for the serious electronics buff. Its scientific tests by Hirsch-Houck Laboratories help you select audio equipment. Articles help you with electronics experimenting, DX listening, video and personal computing. And the do-it-yourself electronics projects plans are the best anywhere! It's no wonder **Popular Electronics** is the world's largest selling electronics magazine!



EXPERIMENTER'S CORNER

By Forrest M. Mims

Experimenting with an Air Pressure Switch

RECENTLY, I learned that an ultrasensitive air pressure switch is available from Edmund Scientific (101 East Gloucester Pike, Barrington, NJ 08007). I immediately ordered one and have been impressed with its capabilities.

The switch, a Honeywell Model PSF 100A, is actuated (closed) by an air pressure of only 0.02 pounds per square inch (psi). This is equivalent to the pressure of about 0.5 inch of water or a gentle puff of air from a distance of a few inches.

You might be able to purchase the PSF 100A directly from Honeywell. Otherwise, you can buy one from Edmund (Cat. No. 41,623) for \$7.00, plus \$1.30 for postage and handling.

The PSF 100A has two differential control ports—one for low—and the other for high-pressure operation. If one port is at atmospheric pressure (*i.e.*, open), the other will trigger the switch on pressure (high port) or vacuum (low port). If both ports are connected to external gas sources, the switch will close when the pressure difference between the two sources exceeds 0.02 psi.

Fairchild assigns a life of 1,000,000 on-off operations to the PSF 100A. Contact resistance of closed switch is 0.5 ohm.

The major drawback of the switch is its current rating of only 10 milliamperes dc. This means that, in many applications, external buffering is required. We will look at several buffering methods, as well as some practical applications for the PSF 100A shortly. First, let's review some of the applications listed in the Edmund data sheet:

1. Replacement of vane-type flow switches.
2. High-wind detector.
3. Proximity sensor.
4. Counting sensor.
5. Clean-air system pressure-drop detector.
6. Edge sensor.
7. Fan or cooling system failure sensor.
8. Fixed-point temperature detector (in a closed system dependent upon the contraction and expansion of a fixed volume of gas).
9. Respiration rate sensor.

10. Venturi tube sensor.

11. Pressurization sensor for inflatable structures.

These applications in turn suggest others. For example, the high-wind detector idea could be used as a fixed-point air-speed indicator for a model rocket, aircraft, bicycle, or automobile. In each case, the input ports of the sensor require constriction to permit the switch to operate at higher air pressures. Or a higher threshold sensor switch can be used. Honeywell's PSF 100A-3, for example, has a switching threshold of 0.1 psi.

Buffer Circuits for a Pressure Sensor. As long as the current to be switched is less than 10 mA, the PSF 100A needs no buffering. This means the switch can directly actuate LEDs and some solid-state warning devices and alerters. For many applications, however, the rated current capacity of the PSF 100A is insufficient.

Figure 1 shows how to connect a low-current, inexpensive relay to the PSF 100A to increase its switching capability from 10 mA to a full ampere (at 125 volts). Since the relay coil current can safely exceed the 10-mA maximum rating of the PSF 100A's contacts, it is necessary to limit the current flow with an external resistor (R_S). Figure 1 gives the values of R_S for power supplies of both 6 and 9 volts which will allow the relay to pull in without exceeding the 10-mA rating.

I arrived at these values by actual measurements, and you may wish to verify my results. Though the relay coil is specified to have a resistance of 500 ohms, the unit I used actually

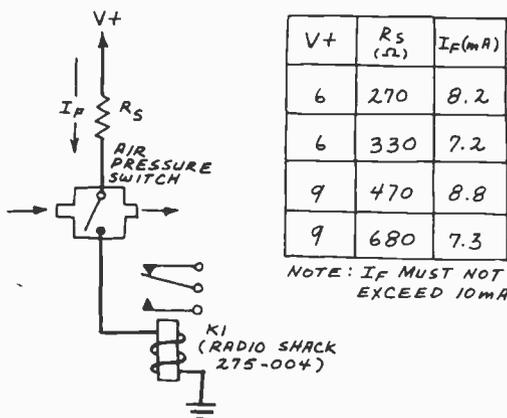


Fig. 1. Using a relay to increase current capacity.

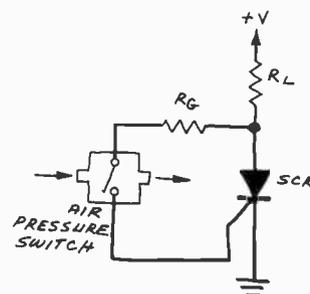


Fig. 2. An air pressure switch can be used to trigger an SCR as shown here.

measured 480 ohms. At 6 volts, this relay pulled in at 5.5 mA and dropped out when the current fell below 4.5 mA. Therefore, the currents given in Fig. 1 provide ample margin for proper operation of the relay.

Figure 2 shows how the PSF 100A can be used to trigger an SCR. The pressure switch is simply inserted in the SCR's gate circuit. Resistor R_G should provide ample SCR gate current while limiting the current through the switch.

Incidentally, remember that a triggered, dc-powered SCR stays on even after the gate signal is removed. Only when the forward current falls below what is termed the minimum required holding current does the SCR turn off. This occurs, of course, when the load is temporarily disconnected. It also occurs on the negative transition of an ac voltage.

Optoisolating the PSF 100A will electrically isolate the

experimenter's corner

sensor from the circuit being controlled. Figure 3 shows how the PSF 100A is connected to the LED portion of a LED-photo transistor optoisolator (also called an optocoupler).

Current-limiting resistor R_S must be selected to limit the current through the LED, and therefore the PSF 100A, to less than 10 mA. The appropriate series resistance can be found with the simple formula: $R_S = (V_F - V_{LED})/I_F$, where V_F is the forward voltage, V_{LED} is the LED forward voltage, and I_F is the desired current in amperes.

GaAs LEDs having a forward voltage from 1.2 to about 1.8 volts are used in most optoisolators. Inserting a typical V_{LED} of 1.5 volts and a desired I_F of 5 mA into our formula gives the following values of R_S for a range of forward voltages:

V_F	R_S
3	300
4	500
5	700
6	900
7	1,100
8	1,300
9	1,500
10	1,700
11	1,900
12	2,100

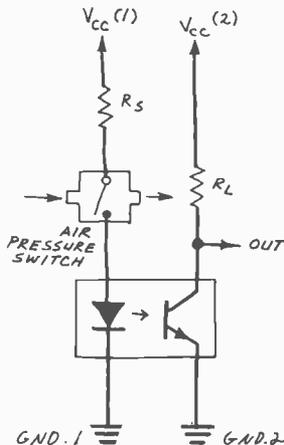


Fig. 3. The air pressure switch can be isolated from the controlled circuit by an optoisolator.

Application Circuits. Having explored the operation of the PSF 100A and seen how its contacts can be buffered, we can now use the switch in practical applications. I've designed three circuits with biomedical applications in mind. Remember that these circuits are merely representative of the ways the PSF 100A can be applied. You can use the same techniques for applications of your own.

Puff/Sip Multi-Channel Controller. Several years ago I read about an electric wheelchair that could be controlled by puffing or sipping on one or more tubes connected to air pressure switches. The same method was used to turn on lights and appliances.

Figure 4 shows one way to implement a "puff/sip" controller. The circuit provides up to five channels of on-off control. More channels can be added by expanding the basic circuit.

The CMOS decade counter (IC2) is a 4017 with self-contained 1-of-10 output decoding. In operation, a clock formed by two NAND gates in IC1 repeatedly cycles IC2 through each of its ten outputs. The five control channels, only one of which is shown in Fig. 4, are provided by adjacent pairs of decoded outputs from IC2.

Channel 1 is controlled by pins 3 and 2 of IC2. At the beginning of a count cycle, pin 3—the lowest order decoded output from IC2—goes high while all other outputs remain low. This turns on Channel 1's ON LED, notifying the operator that the device or appliance controlled by Channel 1 can

FOR ONLY \$129.95 Learn Computing From The Ground Up

Build a Computer kit that grows with you, and can expand to 64k RAM, Microsoft BASIC, Text Editor/Assembler, Word Processor, Floppy Disks and more.

EXPLORER/85

Here's the low cost way to learn the fundamentals of computing, the all-around basics you'll need more and more as you advance in computer skills. For just \$129.95 you get the advanced-design Explorer/85 motherboard, with all the features you need to learn how to write and use programs. And you can grow into a system that is a match for any personal computer on the market. Look at these features: 8085 Central Processing Unit, the microprocessor "heart" of the Explorer/85. (Join the millions who will buy and use the 8080/8085 this year alone!)... Four 8-bit lines 6-bit input/output ports from which you can input and output your programs, as well as control exterior switches, relays, lights, etc. ... a cassette interface that lets you store and reload programs you've learned to write... deluxe 2,000 byte operating system/monitor makes it easy to learn computing in several important ways: • It allows simpler, faster writing and entering of programs • It permits access by you to all parts of the system so you can check on the status of any point in the program • It allows tracing each program step by step, with provision for displaying all the contents of the CPU (registers, flags, etc.) • ... and it does much more!

You get all this in the starting level (Level A) of the Explorer/85 for only \$129.95. Incredible! To use, just plug in your 8VDC power supply and terminal or keyboard/display — if you don't have them, see our special offers below.

Level A computer kit (Terminal Version) ... \$129.95 plus \$3 P&I.*
Level A kit (Hex Keypad/Display Version) ... \$129.95 plus \$3 P&I.*

LEVEL B — This "building block" converts the motherboard into a two-slot S100 bus (industry standard) computer. Now you can plug in any of the hundreds of S100 cards available.

Level B kit ... \$49.95 plus \$2 P&I.*
S100 bus connectors (two required) ... \$4.85 each, postpaid.

LEVEL C — Add still more computing power; this "building block" mounts directly on the motherboard and expands the S100 bus to six slots.

Level C kit ... \$39.95 plus \$2 P&I.*
S100 bus connectors (five required) ... \$4.85 each, postpaid.

LEVEL D — When you reach the point in learning that requires more memory, we offer two choices: either add 4k of a memory directly on the motherboard, or add up to 64k of memory by means of a single S100 card, our famous "JAWS."

Level D kit (CHECK ONE) ... 4k on-board ... \$49.95 plus \$2 P&I.*; 16k S100 "JAWS" ... \$149.95 plus \$2 P&I.*; 32k S100 "JAWS" ... \$199.95 plus \$2 P&I.*; 48k S100 "JAWS" ... \$249.95 plus \$2 P&I.*; 64k S100 "JAWS" ... \$299.95 plus \$2 P&I.*

LEVEL E — An important "building block" that activates the 8k ROM/EPR0M space on the motherboard. Now just plug in our 8k Microsoft BASIC or your own custom programs.

Level E kit ... \$5.95 plus 50¢ P&I.*
Microsoft BASIC — It's the language that allows you to talk English to your computer! It is available three ways: • 8k cassette version of Microsoft BASIC (requires Level B and 12k of RAM minimum; we suggest a 16k S100 "JAWS" — see above) ... \$64.95 postpaid.

8k ROM version of Microsoft BASIC (requires Level B & Level E and 4k RAM; just plug into your Level E sockets. We suggest either the 4k Level D RAM expansion or a 16k S100 "JAWS") ... \$99.95 plus \$2 P&I.*
Disk version of Microsoft BASIC (requires Level B, 32k of RAM, floppy disk controller, 8" floppy disk drive) ... \$329.95 postpaid.

TEXT EDITOR/ASSEMBLER — The editor/assembler is a software tool (a program) designed to simplify the task of writing programs. As your programs become longer and more complex, the assembler can save you many hours of programming time. This software includes an editor program that enters the programs you write, makes changes, and saves the programs on cassettes. The assembler performs the clerical task of translating symbolic code into the computer-readable object code. The editor/assembler program is available either in cassette or a ROM version.

Editor/Assembler (Cassette version; requires Level B) ... \$79.95 plus \$2 P&I.*
Editor/Assembler (ROM version; supplied on an S100 card; requires Level B and 4k RAM (minimum); we suggest either Level D or 16k "JAWS") ... \$99.95 plus \$2 P&I.*

8" FLOPPY DISK — A remarkable "building block." Add our 8" floppy disk when you need faster operation, more convenient program storage, perhaps a business application, and access to the literally thousands of programs and program languages available today. You simply plug them into your Explorer/85 disk system — it accepts all IBM-formatted CP/M programs.

8" Floppy Disk Drive ... \$499.95 plus \$12 P&I.*
Floppy Controller Card ... \$199.95 plus \$2 P&I.*
Disk Drive Cabinet & Power Supply ... \$99.95 plus \$3 P&I.*
Drive Cables (set up for two drives) ... \$25.00 plus \$1.50 P&I.*

CP/M 2.2 Disk Operating System: includes Text Editor/Assembler, dynamic debugger, and other features that give your Explorer/85 access to thousands of existing CP/M-based programs ... \$150.00 postpaid.

NEED A POWER SUPPLY? Consider our AP-1. It can supply all the power you need for a fully expanded Explorer/85 (note: disk drives have their own power supply). Plus the AP-1 fits neatly into the attractive Explorer/85 cabinet (see below).

AP-1 Power Supply kit (8V @ 5 amps) in deluxe steel cabinet ... \$39.95 plus \$2 P&I.*
NEED A TERMINAL? We offer you choices: the least expensive one is our Hex Keypad/Display kit that displays the information on a calculator-type screen. The other choice is our ASCII Keyboard/Computer Terminal kit, that can be used with either



1. Plug in Netronic's Hex Keypad/Display
2. Add Level B in convert in S100
3. Add 4k RAM
4. Plug in Level E here: Microsoft BASIC or Editor/Assembler in ROM
5. Add two S100 boards
6. Add your own custom circuits (prototyping card)
7. Connect terminal

CRT monitor or a TV set (if you have an RF modulator)
Hex Keypad/Display kit ... \$69.95 plus \$2 P&I.*

ASCII Keyboard/Computer Terminal kit featuring a full 128 character set, 8k case, full cursor control, 75 ohm video output, convertible to baudio output, selectable baud rate, RS 232-C or 20 mA I/O, 32 or 64 character by 16 line format ... \$149.95 plus \$3 P&I.*

Steel Cabinet for ASCII Keyboard/Terminal ... \$19.95 plus \$2.50 P&I.*
RF Modulator kit (allows you to use your TV set as a monitor) ... \$6.95 postpaid.

12" Video Monitor (10MHz bandwidth) ... \$139.95 plus \$5 P&I.*
Deluxe Steel Cabinet for the Explorer/85 ... \$49.95 plus \$3 P&I.*
Fan for cabinet ... \$15.00 plus \$1.50 P&I.*

Beginner Pak (Save \$26.00) — You get Level A (Terminal Version) with Monitor Source Listing (\$25 value) AP-1, 5-amp. power supply, Intel 8085 Users Manual ... (Reg. \$199.95) SPECIAL \$169.95 plus \$4 P&I.*

Experimenter Pak (Save \$53.40) — You get Level A (Hex Keypad/Display Version) with Hex Keypad/Display, Intel 8085 User Manual, Level A Hex Monitor Source Listing, and AP-1, 5-amp. power supply ... (Reg. \$279.95) SPECIAL \$218.95 plus \$5 P&I.*

SPECIAL MICROSOFT BASIC PAK (Save \$103.00) — You get Levels A (Terminal Version), B, D (4k RAM), E, 8k Microsoft in ROM, Intel 8085 User Manual, Level A Monitor Source Listing, and AP-1, 5-amp. power supply ... (Reg. \$430.70) SPECIAL \$329.95 plus \$7 P&I.*

Add a Rom-Version Text Editor/Assembler (Requires levels B and D or S100 Memory) ... \$99.95 plus \$2 P&I.*

Starter 8" Disk System — Includes Level A, B floppy disk controller, one CDC 8" disk-drive, two-drive cable, two S100 connectors; just add your own power supplies, cabinets and hardware ... (Reg. \$1085.00) SPECIAL \$999.95 plus \$13 P&I.*

32k Starter System, \$1045.95 plus \$13 P&I.*
48k Starter System, \$1095.95 plus \$13 P&I.*
64k Starter System, \$1145.95 plus \$13 P&I.*

Add to any above Explorer steel cabinet, AP-1 five amp. power supply, Level C with two S100 connectors, disk drive cabinet and power supply, two sub-D connectors for connecting your printer and terminal ... (Reg. \$225.95) SPECIAL \$199.95 plus \$13 P&I.*

Complete 64k System — Wired & Tested ... \$1850.00 plus \$26 P&I.*
Special! Complete Business Software Pak (Save \$925.00) — Includes CP/M 2.2 Microsoft BASIC, General Ledger, Accounts Receivable, Accounts Payable, Payroll Package ... (Reg. \$1325) SPECIAL \$699.95 postpaid.

*P&I stands for "postage & insurance." For Connecticut orders, double this amount.

Continental Credit Card Buyers Outside Connecticut:

TO ORDER
Call Toll Free:
800-243-7428

To Order From Connecticut, or For Technical Assistance, Call (203) 354-9375

CP/M is a reg. trademark of Digital Research

★ (Clip and mail entire ad) ★

SEND ME THE ITEMS CHECKED ABOVE
Total Enclosed (Conn. Residents add sales tax): \$ _____
Paid by:

Personal Check Cashier's Check/Money Order

VISA MASTER CARD (Bank No. _____)
Acct. No. _____ Exp. Date _____


Signature _____
Print Name _____

Address _____
City _____

State _____ Zip _____

NETRONICS Research & Development Ltd.
333 Litchfield Road, New Milford, CT 06776

Fig. 4. A "puff-sip" single-switch, multi-channel controller circuit.

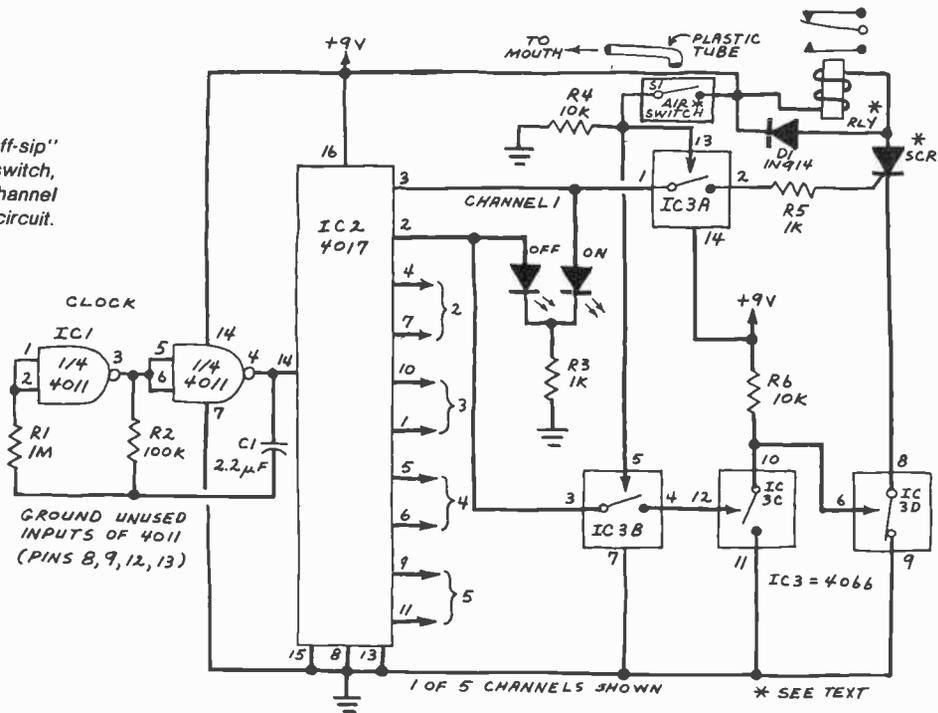

be turned on by puffing or sipping on the plastic tube connected to the circuit's single PSF 100A air switch. Depending upon the value of C1, the operator has up to a second to operate the air switch. If more time is required, the value of C1

can be increased at the expense of slowing down the control cycle.

Whether or not the air switch is closed when Channel 1's ON LED is glowing, the clock eventually advances IC2 to

	74XX	74CXX	74LSXX	74SXX
ZENERS				
500 mw	00 \$.22	\$.37	\$.271	.44
3.0 to 100V	04 .24	.37	.271	.44
1 watt	06 .32	.37	.451	.54
3.0 to 100V	08 .25	.55	.291	.48
Transistors	10 .22	.37	.271	.44
2N697	14 .21	.37	.271	.44
2N1671A	27 .23	-	.291	.45
2N2102	30 .22	.37	.271	.44
2N2222A	37 .36	-	.391	.65
2N2907A	40 .22	.37	.271	.44
2N3055	47 .65	-	.791	.95
2N3904	51 .22	.37	.271	.44
2N3906	54 .22	.37	.271	.44
2N4124	73 .32	.75	.391	.69
2N4126	74 .43	.95	.391	.75
TAKE A 10% DISCOUNT With This Ad!	75 .43	.95	.471	.95
DIODES	76 .32	.75	.391	.75
1N34A	83 .59	1.25	.75	1.50
1N270	85 .75	1.25	1.08	1.50
1N485	86 .43	.75	.391	.72
1N4001	90 .47	.95	.48	-
1N4005	93 .42	.95	.48	-
1N4007	95 .59	.95	.65	-
1N4148	95 .59	.95	.65	-
1N4721	107 .32	1.25	.391	1.50
	121 .35	-	.45	1.10
	123 .53	-	.99	1.25
	125 .45	-	.75	1.50
	132 .89	-	.89	1.50
	151 .59	2.10	.75	1.10
	153 .69	-	.75	1.10
	154 .119	3.75	1.65	1.35
	156 .69	-	.95	1.10
	157 .65	2.50	.75	1.35
	161 .75	1.50	.75	-
	162 .75	-	.99	-
	163 .75	-	.99	-
	165 .75	1.25	.99	-
	174 .79	1.10	.99	1.35
	175 .79	1.10	1.35	1.50
	188 -	-	3.95	3.50
	189 -	-	3.50	3.50
	193 .75	1.50	.99	1.50
	195 .82	1.50	.89	1.50
	221 .110	2.10	1.10	2.00
	240 -	-	1.75	2.25
	241 -	-	1.99	2.25
	242 -	-	1.65	2.25
	244 -	-	1.75	2.25
	245 -	-	1.99	2.45
	279 .72	-	.65	-
	299 -	-	3.75	-
	365 .63	-	.69	-
	366 .63	-	.69	-
	367 .63	-	.69	-
	373 -	2.95	1.75	2.95
	374 -	2.95	1.75	2.95

REGULATORS
LM340TXX or 78XX 85¢ POSITIVE
LM320TXX or 79XX 89¢ NEGATIVE
VIDEO & I.F.
MC1330 \$1.59
MC1349 1.25
MC1350 1.15
MC1358 1.47
ASSOC.
LM380 \$1.45
NE565 1.19
MC1458 .45

SEND FOR FREE CATALOG. WE LIST AND STOCK OVER 2000 TYPES OF I.C.'s, 5000 DIODE TYPES & OVER 3000 TRANSISTOR TYPES. HARD TO FIND OR DISCONTINUED DEVICES - THOUSANDS IN STOCK!! FREE WOODEN NICKEL WITH ORDER.

LINEAR
LM300H \$1.00
LM301N .49
LM307N .49
LM317K 3.95
ua741P .45
ua747N 1.00
NE555V .29

Components Express, Inc.
"Have you kissed your computer lately?"
1380 E. Edinger, Unit CC Santa Ana, CA 92705 (714) 558-3972

BROAD BAND MICROWAVE RECEIVER SYSTEM
1.8GHZ to 2.4 GHZ

only \$295.

With built-in-converter to channel 2, 3, or 4 of any standard TV set.

- 24" Dish
- Feed-Horn Receiver
- Mounting Bracket
- Mounting Clamp
- Instructions
- 300 Ohm to 75 Ohm Adapter
- 750 Ohm to 300 Ohm Adapter
- 60 Feet Coax Cable with Connectors
- 3 Feet Coax Cable with Connectors

RANGE: Line of sight to 250 miles
SCOPE: Will receive within the frequency band from satellites, primary microwave stations, and repeater microwave booster stations
CONTENTS: Completely packaged in 19"x19"x4 1/2" corrugated carton complete with list
WARRANTY: 180 days for all factory defects and electronic failures for normal usage and handling. Defective sub assemblies will be replaced with new or re-manufactured sub assembly on a 48 hour exchange guarantee.
This system is not a kit and requires no additional devices or equipment other than a TV set to place in operation.
Dealer inquiries invited

scorpio electronics
TEL. (714) 754-7545
3198 N AIRPORT LOOP DRIVE COSTA MESA, CALIF 92626
VISA CREDIT CARD ORDERS, PLEASE DIAL... \$10 min.
MASTER-CARD 800 854-7458 ADD \$1.50 FRT.
CARD

decoded output two (pin 2). This turns on Channel 1's OFF LED and notifies the operator that the device or appliance controlled by Channel 1 can be turned off by puffing or sipping on the air switch's tube. Again, whether or not the switch is closed, IC2 continues to advance through the decoded outputs as the clock supplies pulses. If the switch is *not* closed, the controlled device or appliance remains either on or off.

The four transmission gates in a single 4066 analog switch (IC3) provide the necessary control logic for a single channel. If the air switch is closed when Channel 1's ON LED is glowing, IC3A closes, firing the SCR and pulling in the relay.

If the air switch is closed when Channel 1's OFF LED is glowing, IC3B closes. This, in turn, closes IC3C. Switch IC3D is normally in the closed state due to the voltage drop across R6, but when IC3C closes, the control pin (6) of IC3D goes to ground. This opens the current path through the SCR, turning off the SCR and allowing the relay to drop out.

When IC2 advances to the next decoded output, IC3B and IC3C open and IC3D is again closed by the drop across R6. The SCR can then be triggered by a puff or sip the next time Channel 1's ON LED is glowing.

I used a low-current relay (Radio Shack 275-004) in the prototype of the circuit. The SCR can be any low-voltage, economy-grade unit.

Follow the circuit used for Channel 1 to add additional control channels. The PSF 100A in Fig. 4 should be connected to pins 5 and 13 of each additional channel's 4066. This permits one switch to control all channels. Connect the mouth tube to the switch's HIGH port for puff operation or the LOW port for sip operation.

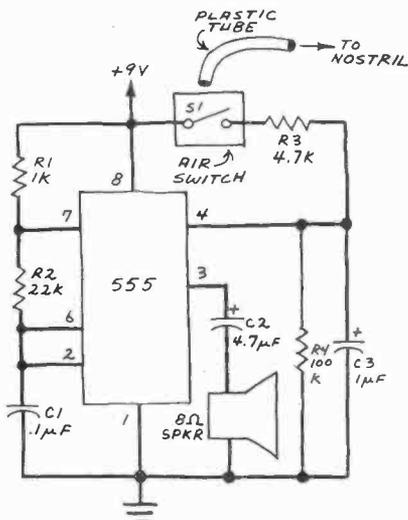


Fig. 5. Respiration indicator provides audible signal.

Caution: Do not exceed the relay's contact ratings. Avoid shock hazards by powering the circuit with a 9-volt battery and carefully insulating connections to the relay's contacts.

Respiration Indicator. The circuit in Fig. 5 provides a brief tone burst each time a person or animal being monitored inhales or exhales. The circuit is a straightforward 555 astable oscillator whose frequency is controlled by C1.

When the PSF 100A air pressure switch, S1, is open, the 555's reset input (pin 4) is held low by R4 and the oscillator is disabled. When S1 is closed, pin 4 of the 555 is made high via R3 and the oscillator is enabled. Simultaneously, C3 is charged through R3 to the battery voltage. When S1 is opened, pin 4 is held high by the charge on C3 until it discharges through R4. The oscillator is then disabled.

The tone frequency of this circuit can be increased (or decreased) by reducing (or increasing) the value of C1. The length of the tone burst can be extended by increasing the value of C3, or the extended tone burst can be eliminated entirely by removing C3. The circuit will continue to provide a tone for each respiration cycle.

I tested the circuit by taping a length of flexible aquarium

the 1981 formula-1™

the antenna specialists co. presents the
latest advance in high-performance antennas for
professional CB communications
... and major support for REACT*


Formula cars and our new Model M-710 Formula-1 share an identical engineering strategy: continually refine a proven basic design with one objective: MAXIMUM POSSIBLE PERFORMANCE.

That's Formula-1—direct descendant of A/S's classic base-loaded mobile police antennas. Born for performance, built to last, Formula-1 is the result of over 25 years of continuous development. Today's new state-of-the-art in mobile CB antennas.



- Precision-wound, water-proof coil. Lifetime burnout guarantee.
- Factory tuned; set-screw ultra-fine tuning.
- Longer whip for more "reach".
- Tapered stainless steel whip minimizes range-robbing wind deflection.
- Anti-static whip ball-tip.
- New quarter-turn quick-disconnect life tested over 2,500 times.
- Easy to install. 17' pre-assembled cable, miniature in-line connector, contour-forming protective mounting gasket, hardware for both roof-top or trunk-lip mounting.
- 5-year limited warranty.

the antenna specialists co.

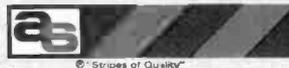

a member of The Allen Group
12435 Euclid Avenue, Cleveland, Ohio 44106
Export: 2200 Shames Drive
Westbury L.I., New York 11590
Canada: A.C. Simmonds & Sons, Ltd.

* Formula-1 contributes more than just performance:

To encourage CB for serious highway communications, we're donating \$1.00 to REACT International for every Formula-1 purchased in 1981. Join REACT. Get involved. Ask your dealer.



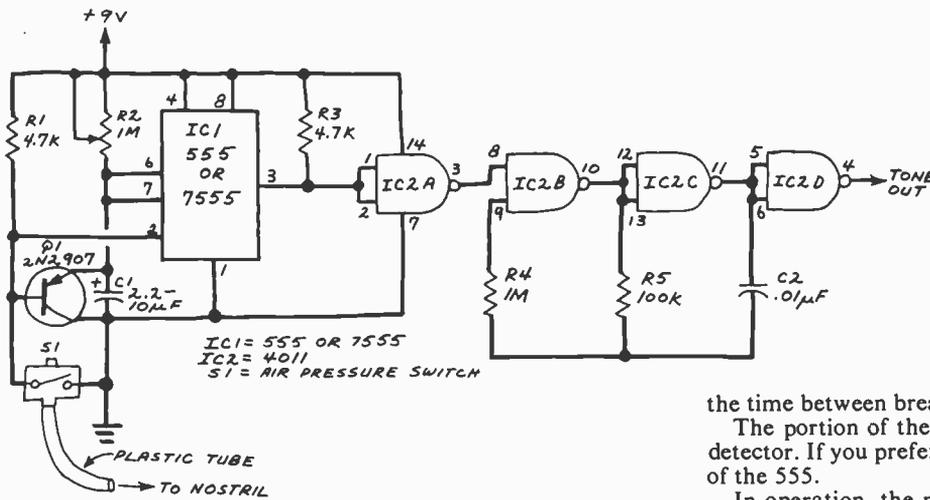


Fig. 6. This circuit monitors respiration and emits a warning tone when time between breaths exceeds a predetermined interval.

tubing under one nostril. When the remaining end of the tubing was attached to the PSF 100A's LOW port, the circuit beeped each time I inhaled. When the tube was connected to the HIGH port, the circuit beeped when I exhaled. Try both operating modes if you build the circuit.

This circuit provides a simple way for recording the breathing rates of animals for study and evaluation. It can also be used with human subjects such as athletes. It should be used with seriously ill patients only under medical supervision. In any case, power the circuit with a 9-volt battery or an isolated line-operated supply to avoid electrical shock.


Respiration Failure Alarm. When used under proper medical supervision, the circuit in Fig. 6 can save a life. It continuously monitors respiration and emits a warning tone when

the time between breaths exceeds a predetermined interval. The portion of the circuit involving IC1 is a missing pulse detector. If you prefer, you can use a 7555, the CMOS version of the 555.

In operation, the missing pulse detector is reset each time S1, a PSF 100A air switch, is closed. Resistor R2 controls the maximum time allowed between reset pulses. If the circuit is not reset before the allowed time expires, pin 3 of the 555 goes low. This actuates an astable oscillator made from IC2B and IC2C. If the 555 is subsequently reset, the oscillator will be disabled. Otherwise the oscillator will provide a continuous warning tone. The frequency of the warning tone can be changed by changing the value of C2.

You can test this circuit by using a length of aquarium tubing as described in the previous section. Be sure to power the circuit with a 9-volt battery or isolated line supply to avoid the possibility of electrical shock. Like any biomedical electronic device, the respiration failure alarm should be used with seriously ill patients only under medical supervision.

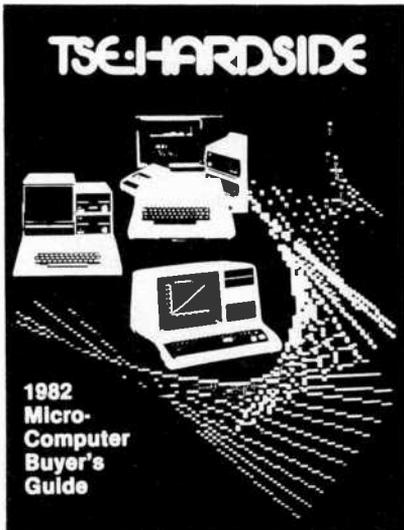THE TSE-HARDSIDE 1982 MICRO-COMPUTER BUYER'S GUIDE



is now available! We've included such valuable information as print samples from each of the printers we carry, feature-by-feature comparisons of Micro-Computer systems in an easy-to-read table format, an informative article on Micros, and pages and pages of complete product descriptions.

We're making this valuable reference available for only \$2.95 (refundable on your next purchase from TSE-HARDSIDE.) Charge customers are welcome to call our toll-free number: 1-800-258-1790 (in NH call 673-5144) THE TSE-HARDSIDE 1982 MICRO-COMPUTER BUYER'S GUIDE will soon arrive at your address via first class mail.

Send to:



Yes! Send me the TSE-HARDSIDE 1982 Micro-Computer Buyer's Guide.

- I've enclosed \$2.95
- Please send only your FREE Price List
- Charge to my credit card
- MasterCard
- Visa

Card No. _____

Interbank No. _____ Exp. Date _____

Signature _____

Name _____

Address _____

City _____

State _____ Zip Code _____

CALCULATOR SAVINGS



HP-32E Scientific	\$42.95
HP-33C Programmable	68.95
HP-34C Adv. Program	114.95
HP-37E Financial	58.95
HP-38C Adv. Financial	114.95
HP-41C Alpha Program	187.95
HP-41CV (Full Memory)	237.95
Card Reader/41	264.95
Printer/41	289.95
Optical Wand/41	92.95
Memory Module/41C	23.95
Quad Memory/41C	76.95
HP-67 Programmable	287.95
HP-97 Desk Program	579.95
HP-85 Desk Computer	2495.00
HP-83 Desk Computer	1695.00
16K Memory Module	99.95

Call for Low Prices on all Calculator and Computer Accessories.

TEXAS INSTRUMENTS

TI-35	\$19.95	TI-59	\$189.95	TI-99/4 Console	\$399.95
TI-55	28.95	PC-100C	159.95	Language Tutor	99.95
TI-57	39.95	Programr	49.95	Speak & Spell	59.95
TI-58C	88.95	TI-5040	67.95	Business Analyst II	39.95

Call for Low Prices on All TI Calculators and Watches

Sharp	PC-1211 Handheld Computer	CALL
	CE-121 Cassette interface	\$49.95
	CE-122 Printer/cassette interface	149.95
	EL-5100 Alphanumeric scientific programmable	69.95
	EL-7001 Miniature typewriter and calculator	99.95
	CT-660E Talking digital alarm clock	59.95
Casio	FX-602P Slim programmable, 512 steps	99.95
	FX-702P Handheld computer	159.95
	FX-3600P Slim programmable, 38 steps	34.95
	M-10 Compact musical keyboard	124.95
	MT-30 Compact musical keyboard	159.95
	W-100 Water sports alarm chrono, 325 feet	34.95
	CA-90 Calculator alarm chrono watch	44.95
Pearlco	S202 Microcassette tape recorder	79.95
	S802 Two-speed, two-hour recorder	99.95
	S801 Olympus' smallest, two-hour	139.95
	X-01 New electronic recorder	199.95
Craig	M100 Language translator	49.95
Olivetti	Praxis 35 Electronic portable typewriter	579.95

For faster delivery use cashier's check or money order. Add shipping: 1% of order (\$3.00 min.). East of Missp Riv. add \$1.50. CA Res add 6%. Subject to availability VISA and MC accepted

ORDER TOLL-FREE 800-421-5188 Information line (213) 633-3282 Outside CA, AK, HI

tam's INCORPORATED
 Tam's Dept. W8
 14932 Garfield Ave.
 Paramount, CA 90723
 (213) 633-3262

CIRCLE NO. 66 ON FREE INFORMATION CARD POPULAR ELECTRONICS

CIRCLE NO. 35 ON FREE INFORMATION CARD

Reader's Comments. The April 1981 installment of this column attracted a number of interesting letters. As you may recall, that column concerned electronic aids for the handicapped. Frank Cuta, an electrical engineer at Battelle North-west Laboratories, wrote that while he appreciated the column, "... the tone of the article tends to appeal to the nonhandicapped person ... It would do a heap of good if you would mention in your next article on this subject that you expect the information to be used by technically inclined handicapped persons as well. It promotes a positive image of handicapped people and their capabilities."

Mr. Cuta, who happens to be blind, is right. I hope his suggestion will encourage both disabled and nondisabled readers to build the projects which appear in this column.

The former chief engineer at a radio station wrote to describe his experiences with a blind operator who was able to operate sophisticated equipment with the help of various LED indicators and a light probe. He also "... used his light probe to 'see' the moon for the first time in his life ... Here's hoping that articles such as Mr. Mims's will stimulate some thoughts on interfacing the world to people who might otherwise sit around all their lives. ..."

This reader had a suggestion of his own: "I've noticed that many elevators now have the floor selector buttons labelled in Braille. The problem is that even though the blind person can select the proper floor, he cannot know for sure which floor the elevator has stopped at. What a place for an annunciator. It could say something as simple as 'third floor' or as elaborate as 'fifth floor: ladies hosiery, lamps, tables and lights.'"

This is an excellent suggestion. I'll be glad to pass along other ideas in future columns. If you wish to make a suggestion, please give permission for its use. Also, clearly print (or type) your name and address. Names will be omitted upon request.



PENNY SALE

Buy 1 Jumbo Pak for \$2.99 and get the 2nd for One Penny.

Order today by calling us on our new toll-free number.

800-343-3086

For orders only.

- 400-PRE-FORMED 1/2 WATTERS, popular values, some 5 & 10% ers. (#6246)
- 35-UPRIGHT ELECTROS. 100%, assorted values & voltages, marked (#3226)
- 75-CABLE TIES, 4" non-slip white plastic, like Ty-wrap. (#5218)
- 50-MINI POTS, pc style, single turn, assorted values. (#3345)
- 150-PC. CAPACITOR SPECIAL, asst. mylars, polys, micas, etc. 100% mat. (#6264)
- 175-1/4 WATT RESISTORS, asst. carbons, carbo-films, some 5%ers. (#5797A)
- 60-POLYSTYRENE CAPS, assorted types, styles & sizes, all good. (#2729)
- SURPRISE PAK Assortment of IC's, caps, pots and parts of every desc. (#6648)
- 175-HALF WATTERS, 100% color coded resistors, asst. values. (#3046)
- 175-MOLEX SOCKETS, "on a strip", make your own pc sockets. (#6255)
- 400-PRE-FORMED 1/4 WATTERS, assorted values, precut for PC appl. (#6622)
- 24-MINI-BULBS, ASST. VOLTAGES & base styles, some colored. (#6757)
- 125-LONG LEAD DISK, prime, marked caps, assorted material. (#2598)
- 50-SLIDE SWITCHES, various shapes, sizes and types (#2726)
- 25-MICRO MINI REED SWITCHES, 1" long, for alarms, relay systems, etc. (#6263)
- 50-THERMISTORS, various types & styles, neg. coefficient, 100% (#4089)
- 200-PRE-FORMED DISCS, caps w/leads for PC use, mixed values. (#2605)
- 50-AXIAL ELECTROS, asst. values, volts, sizes, what a buy! (#3227)
- 100-PLESSY CAPS, ceramic blocks in assorted sizes & values. (#5221)
- 3-WATCH GUTS, 5-function, LED style, assorted sizes, untested (#6287)
- 6-TIME DELAYS, solid state, asst. from 450 mSec to 8 Sec. (#6758)
- 100-PLASTIC TRANSISTORS, untested, to 92, asst. types (#2604)
- 75-TRANSISTOR ELECTROLYTICS, epoxy encapsulated, asst. values. (#2747)
- 20-SLIDE VOLUME CONTROLS, various values & types, for Hi-Fi, etc. (#3057)
- 500-PC-HARDWARE SURPRISE, (approx.) 1 lb. asst. screws, washers, etc. (#6271)
- 100-POWER RESISTORS, 3 to 7 watt power resistors. (#6281)
- 50-2 WATT RESISTORS, assorted carbons, films etc. some 5% ers. (#6238)
- 24-SKINNY TRIM POTS, multi & single turn, asst. values & types. (#6285)
- 40-CRYSTALS, assorted types, some H6/U, some frequency marked. (#6256)
- 20-9V BATTERY CLIPS, snap connector, coded, insulated leads. (#6286)
- 4 HEAVY DUTY LINE CORDS, 2 cond. 6ft. 16 gauge (#6292)
- 200-PRECISION RESISTORS, 1/2 W, assorted wattages 1%, axial (#2428)
- 30-PANEL SWITCHES, assorted rotary, micro, slide, etc. (#6629)
- 20-PAIRS-RCA PLUGS & JACKS, popular for Hi-Fi, speakers, etc. (#6630)
- 4-2N3055 NPN TRANSISTORS, 115 watts, 15 amps, TO-3, 100% mat (#6633)
- 5-LINE CORDS, heavy duty, 18 gauge, 6', molded plug, 2-cond. (#6499)
- 20-2N3055 HOBBY TRANSISTORS, manu. fallout, TO-3, U-test. (#6624)
- 25-PLASTIC POWERS, 25 watt, mpm & mnp, 50-200 w/bco, TO-220. (#6237)
- 150-"4000" RECTIFIERS, IN4000 series, may include; 50 to 1000V. (#2417)
- 30-SCRs & TRIACS, assorted values, 10 Amp TO-220, untested (#6337)
- 60-IN914 SWITCHING DIODES, 4 nsec, axial, glass, untested (#6632)
- 30-INSTRUMENT KNOBS, for half round shafts, some w/pinters. (#6498)
- 35-STEREO INDICATORS, liny red 1.5V bulbs, for Hi-Fi replacement. (#6244)
- 40-EDGE CONNECTORS, asst. 4 & 6 pin, 2-sided, pc leads. (#6364)
- 6-MINI-MOTORS, type RE56, 1.5-6VDC, color-coded wire leads (#6718)
- 25-NE-2 BULBS, neon, for 110 VAC, requires resistor, (not incl.) (#2613)
- 150-METALLIC RESISTORS, mostly 1/2 watters, asst. val. 1-5% tol. (#6280)
- 40-VOLUME CONTROLS, assorted values & types (#6331)
- 25-2N3904 TRANSISTORS, 100% material. (#6370)
- 28ft. COLORED 20 MIL FIBERS, 2' lengths, assorted colors (#6768)
- 125-ONE WATT RESISTORS, 10p names, mostly carbons, some 5%ers. (#3300)
- 200 PC SEMICON SPECIAL, asst. diodes, zeners, etc. untested. (#6284)
- 40-STRAIN RELIEFS, asst. types in various sizes & shapes (#6755)
- 1-UHF TUNER, 3-gang, 300 ohm, direct drive type (#6658)
- 200-TUBULAR CAPS, asst. tubulars, 100mfm to 0.1mf to 600 WDC (#6254)
- 60-MINI LAMP SOCKETS, asst. screw, bayonet, & snap-in's. (#6789)
- 150-SUBMINI IF TRANSFORMERS, asst. transistor radio types (#6259)
- 10-PUSHBUTTON ALARM SWITCHES, spst nc. 1A 125 VAC (#6267)
- 25-DATA ENTRY SWITCHES, asst. 1/2" square keyboard switches (#6627)
- 10-MOTORS MOTORS, asst. size hobby motors, 1-1/2 to 12 volts. (#2551A)
- 150-TERMINAL STRIPS, asst. screw & solder lug types. (#6251)
- 50-TO-5 TRIACS, asst. 50 to 600 PIV, 70% yield, gold plated, 3 leads (#6321)
- 200-HI-QUALITY RESISTORS, 1/8, 1/2, & 1 watters 1% & 5%. (#6627)
- 40-MYLAR UPRIGHT CAPS, asst. epoxy, plastic, polystyrene, etc. (#6634)
- 20-HOBBY LEDS, asst. types & colors, mostly dims. (#6252)
- 12 FT.-FIBER OPTIC RIBBON, 3/8" wide ribbons conduct light (#6770)
- 100-PIN SOCKETS, inline male & female crimp-on connectors. (#6902)
- 100-ASSORTED SPACERS, nylon spacers, washers, grommets, etc. (#6617)

"JOIN THE PAK"
DON'T MISS OUR 25th
ANNIVERSARY CATALOG

POLY PAKS P.O. BOX 942, PE-9
S. LYNNFIELD, MA. 01940

Total Amount of Order \$ _____

INCLUDE SHIPPING AND HANDLING: U.S., ADD \$3; FOREIGN, ADD \$7.
MASS. RES. ADD 5% SALES TAX.

NAME _____

ADDRESS _____

CITY _____

STATE _____ ZIP _____

Enclosed is CHECK MONEY ORDER
Charge my MASTERCARD VISA

ACCT. # _____ EXP. DATE _____

Orders only 800-343-3086 Other calls 1-617-245-3828

ORDERING INSTRUCTIONS • Indicate quantity on line or box near item desired • Complete coupon section • Cut out Ad and mail to Poly Paks, Inc.

■ Send me your FREE catalog

OLYMPIC SALES SINCE 1947 COMPANY

	Retail	Your Cost
HP-85 Microcomputer	3250.00	2595.00
HP-83 Microcomputer	2250.00	1795.00
16K Exp. mem. module	295.00	259.95
Graphics plotter 7225	2450.00	2089.95
Personality mod. for 7225	750.00	579.95
2631B Impact printer, hvy duty	3950.00	3295.95
Opt. 020 for 2631B	150.00	129.95
8 disk drives to choose from		
82902S	1300.00	1149.95
9895A 8" dual drive	6850.00	5950.00
Graphics tablet 9111A	2050.00	1699.95
HP-41CV 2.2K bytes of memory	325.00	259.95
HP-41C Calculator	250.00	188.95
Card reader for 41CV/41C	215.00	168.95
Printer for 41CV/41C	385.00	284.95
Optical wand for 41CV/41C	125.00	97.95
Quad Ram = 4 mem. mods.	95.00	84.95
Memory mod. for 41C		26.95
HP-97 Programmable printer	750.00	579.95
HP-67 Programmable calculator	375.00	297.95
HP-34C Programmable scientific	150.00	117.95
HP-38C Programmable business R/E	150.00	119.95
HP-32E Advanced scientific	55.00	48.95
HP-37E Business management	75.00	58.95

Texas Instruments

	Retail	Your Cost
TI-99/4 Home Computer	5950.00	\$379.95
We carry a large inventory of software, & accessories		
TI-59 Programmable calculator	295.00	199.95
TI-58C Programmable calculator	130.00	93.95
PC 100C Printer/plotter for 59/58	225.00	149.95
NEW! Calculator Watch w/Alarm TI 810-11		
Many features & 1 yr guarantee from TI	29.95	
TI 584-11 Alarm Chron. Dual Time Zone	19.95	

ATARI Computer

	Retail	Your Cost
400 SPECIAL PRICE! 16K	595.00	339.95
No language inc., opt'l basic		54.95
800 16K Computer	1080.00	759.95

ATARI VIDEO TAPES

	Retail	Your Cost
TV GAME	\$225.00	
Minimum 3 tapes/Mixed O.K.		
SONY L500, 2 hr	\$11.89	
L750, 3 hr	14.69	
RCA VK250, 6 hr	13.95	

216 S. Oxford Ave.
Los Angeles, CA 90004
(213) 739-1130

PHONE ORDERS:
TOLL FREE
out of Cal 800-421-8045
in Calif. 800-252-2153
Telex: 67 34 77
Cable: "OLYRAV" LSA

WE HONOR
VISA

apple computer
APPLE COMPUTERS II & III
We are an authorized Apple servicing dealer

16K-32K-48K-128K Graphics tablet
Drive with controller DOS 3.3 and others

80 column cards, VisiCalc and more and more
We have the best prices on Apple computers in America - "CALL US!"

SEIKO (USA) WATCHES - (Limited Current models & MORE! Offer!)
These models guaranteed by Seiko anywhere you wish in USA

	Retail	Your Cost
FJ113 Divers watch, 300 ft; S/S	195.00	79.95
YH006 Ladies quartz LCD, gldtne	295.00	79.95
YH002 Ladies quartz LCD, gldtne	250.00	74.95
YH015 Ladies quartz LCD, gldtne	225.00	69.95
YH003 Ladies quartz LCD, slvrne	215.00	69.95

And many more compare our prices with the nearest Seiko dealer.

casio WATCHES We will beat your own price. Call us for more info.

	Retail	Your Cost
CA 90 Calc/stp/wch w/alarm & more! on Casio	44.95	
CA 901 Calc/stp/wch w/larm all metal watch!	59.95	
W 100 Divers stopwch 300 ft wtr res & more	34.95	
W 150C Divers stopwch 300 ft wtr res S/S case	48.95	
W 150 Divers stopwch 300 ft wtr res all meta	53.95	

MATTEL INTELLIVISION Retail \$325.00 Most animated TV game Y/C: \$239.95

SONY
MANY NEW ITEMS FROM SONY - call for AT DISCOUNTED PRICES! information

AMDEK (Leedex) Quality Monitors

	Retail	Your Cost
100 12" B/W, 12 MHz	179.00	129.95
100-80 12" B/W, metal cab., space for floppy	199.00	159.95
100-G 12" Green, 12 MHz	199.00	159.95
300-G 12" Green, 18 MHz	249.00	189.95
Color I 13" Color, NTSC comp. input, audio amp & speaker	449.00	329.95
Color II 13" Color, RGB input, hi res graphics, speaker	999.00	699.95

All goods subject to availability, this ad supercedes all previous ads; we are not responsible for typographical errors; we will meet or beat any advertised price if our competition has the goods on hand. Minimum shipg & handling \$4.95. All orders subject to verification and acceptance.

Bearcat® 210XL Super Scanner

Look what you get with the Bearcat 210XL. Exciting, new spaceage styling. No-crystal, pushbutton tuning. New, 18 channel, 6-band coverage of over 6000 frequencies. And features like 2 scan speeds, Automatic Squelch, Search, and Lockout. Direct Channel Access. Selective Scan Delay. And much more. There's never been a Scanner like the Bearcat 210XL.

"TAKE IT FROM A
SMART OPERATOR."

Don Adams

**BEARCAT 210XL
SCANNER
\$229.**



THE LOWEST PRICED, FULL-FEATURE, BEARCAT NO-CRYSTAL SCANNER EVER.

Bring home all the real excitement of scanning, and save! Bearcat 160 features a smooth, keyless keyboard for all controls including volume and squelch. Has 5-band, 16 channel coverage. Priority, Selective Scan Delay, Automatic Lockout and Search. And much more. Bearcat is number one in scanning.

"TAKE IT FROM
A SMART
OPERATOR."

Don Adams

\$189.

**BEARCAT 160
SCANNER**



Electra Electra Company
Division of Masco Corp of Indiana

Add \$7.00 per scanner for U.P.S. ground shipping in the continental U.S. Send your cashier's check or money order to our address below or order by phone if you have a Visa or Master Charge card.

**COMMUNICATIONS
ELECTRONICS™**

854 Phoenix □ Box 1002 □ Ann Arbor, Michigan 48106 U.S.A.
Call TOLL-FREE (800) 521-4414 or outside U.S.A. (313) 994-4444

CIRCLE NO. 1 ON FREE INFORMATION CARD

96

DX LISTENING

By Glenn Hauser

Strikes Disrupt International Broadcasting

Radio Canada International was forced off the air in May by labor disputes. Though unable to originate newscasts in any language, RCI was able to continue broadcasting English-language news programs coming from Toronto, which had already been scheduled. RCI did not carry any additional newscasts from Toronto, but played fill music instead.

Kol Israel was also hit by labor difficulties in May. It was forced to substitute fill music for regularly scheduled programs, except the news, which continued as usual. ("Usual" meaning that the news on the 0000, 0100, and 0200 GMT broadcasts was tape-delayed from 2230.)

Radio Andorra faced an even more serious situation at the end of March when its 20-year license expired. The station had been dominated by Spanish and French interests, resulting in little programming which served Andorra itself. The Andorrans wanted it to be a station of their own; it went off the air pending resolution of the conflict.

Radio New Zealand has been struggling to keep its shortwave service going, despite the drawbacks of two antiquated 7½-kW transmitters. Several times over the past few years, it has submitted plans to get new higher-powered transmitters, only to have them turned down by the N.Z. government. The latest proposal is for a site adjoining a naval transmitting facility, with four 50-kW transmitters. If this is also turned down, *Radio New Zealand* threatens to give up shortwave altogether. Not having a big signal means that stronger stations do not respect its frequencies. In late May, the *Voice of America* went on 17860 in the 0000-0400 GMT period; an unidentified utility frequently overcomes 15485; *HCJB* and *Radio Peking* block 11945 after 1130 GMT; and *RNZ's* old 49-meter channel of 6105 can no longer be used because of television-interference complaints near the transmitter site.

Not all the news is bad. The *Voice of Germany*, *Radio Deutsche Welle*, is reportedly expanding its North American service in English to 50-minute programs in September, after several years

during which *DW* considered its North American English-speaking audience worthy of no more than 20 or 30 minute programs. The man to thank is *DW's* new director, Klaus Schütz, though his predecessor, Conrad Ahlers—who died unexpectedly in December—started the move.

New Orleans' new shortwave station, *WRNO*, should be on the air by September if its transmitter and antennas were delivered as planned in late June. Unlike all other U.S. shortwave broadcasting stations, which are either governmental or missionary, *WRNO* will be a commercial rocker. It registered this tentative schedule for September and October: 1830-2100 GMT on 15175; 2100-2300 on 11890; 2300-0200 on 11965; 0200-0700 on 6155. Meanwhile, *Radio Portugal* has started using 6155 for its broadcasts to North America; and the *Austrian Radio* will no doubt object to 6155, which it also uses toward the end of *WRNO's* projected schedule.

Two Pacific Islands which had been difficult-to-impossible to hear in North America burst upon the scene this year. *Radio Kiribati* fired up a single-sideband unit on 16433 kHz, to feed its programs to another island under the same administration, Christmas Island (the one in the Pacific). They picked up an audience in North America, too, in the 0600-0900 time period; the first half of the program is in English (including BBC transcriptions), the second in Gilbertese (or Kiribati).

Radio Cook Islands had at least been on shortwave, usually 5045 kHz, but still faced a considerable challenge until it moved to 11760 kHz, also at 0600 past 0900. During the summer, this frequency happened to be clear after Havana signed off, but this fluke cannot be expected to continue, nor can *Radio Cook Islands* be depended upon to stay on this frequency.

Those still seeking a Pacific DX listening challenge should try for this one: "3RPH," Radio for the Print Handicapped, in Melbourne, Australia, on the unusual frequency of 1705 kHz. Such stations in the U.S. operate on FM sub-carriers, but Australia has taken a different route since its FM broadcasting

POPULAR ELECTRONICS

system is not fully developed. This is a volunteer-operated station with 500 watts, active initially in the local evenings (and heard at 1130 GMT by Arthur Cushen in New Zealand), but planning to expand to 24-hour transmission. Similar stations on nearby frequencies are expected soon in Brisbane, Sydney and Hobart. Now is the time to try for them in North America because, in a few years, this frequency range will be smothered by an expanding domestic AM band.

Two Caribbean islands have new mediumwave stations operated by American interests. The *Voice of America's* English service to the Americas is now available on AM radios, thanks to a 50-kilowatt transmitter on 1580 kHz from Antigua. It could be heard in the U.S. itself before its directional antenna was finished, in the 0000-0400 GMT period. And on Anguilla, Quality Media Corp. has gone on the air with "The Caribbean Beacon" on 690 and 1610 kHz. It's a gospel station, mostly in English, but with Spanish reported at 0300-0330 by Maxfield Greenwood in Maine.

Anti-Castro Cubans in Florida must now feel freer to put clandestine radio stations on the air, since a U.S. attorney refused to prosecute one such operator, much to the chagrin of the FCC. Currently the most reliable and professional anti-Castro station is *Radio Cuba Libre*, which says it is run by the Cuban Christian Democratic Movement. Half-hour broadcasts start at 11 p.m. (ET) on 6989 kHz (announced as 6990), on Thursdays and Sundays.

Ironically, in June, the Senate approved a regulation proposed by Sen. Jesse Helms (R, NC), requiring the *Voice of America* to identify its broadcasts to Cuba as "Radio Cuba Libre." But since "Cita Con Cuba" was dropped several years ago, *VOA* broadcasts in Spanish have been for Latin America in general. This includes those on 1180 kHz from Florida, for which the main target is Cuba.

Radio Quince de Septiembre, the clandestine station opposing the Sandinist government in Nicaragua, operated freely and clearly at 0400 GMT each night on 5565 kHz until the Sandinists apparently decided to jam it in late May. After that, the station and the jammer began playing cat-and-mouse, jumping from one frequency to another in that area, such as 5555 and 5570. Of course, this also disrupts aeronautical communications allocated for this band.

Rádio Nacional, Brasília, provides a pleasant respite from rhetoric and noise, especially on its "Sunday Special" programs at 0200-0300 (GMT Mondays) on 17830 and 15290. Talk and music-oriented specials alternate: scheduled for Aug. 9, Carmen Miranda; Aug. 16, Brazilian Coffee and Its History; Aug. 23, Brazilian Country Music; Aug. 30, History of the Brazilian Republic.

For more background information on broadcasting around the world, tune in Austrian Shortwave Panorama, GMT Mondays at 0434, on 12015 kHz. ◇

SEPTEMBER 1981

THE WEDGE...



...is designed out of a special high-density, open-cell acoustic urethane material for optimum sound absorption and noise reduction in the home, office, and recording studio.

WEDGE products ARE A MUST —

- For the electronics and computer enthusiast to quiet workroom areas.
- For the audiophile, to provide a proper acoustic environment in his sound room.
- For the home hobbyist, to isolate machinery and other unwanted noise problems.
- For the office, as modular office dividers.
- For the recording studio, where portable sound barriers and proper room treatment are essential.

WEDGE products come in a variety of attractive styles, such as our room dividers (shown here), wall paneling, portable sound barriers, and in sheeting, for ease of application anywhere.

For more information and a free brochure contact:

Esotech Inc.

7778 Mitchell Road
Minneapolis, Mn 55344
(612) 934-5790




CIRCLE NO. 21 ON FREE INFORMATION CARD

FREE

McIntosh

STEREO CATALOG and FM DIRECTORY

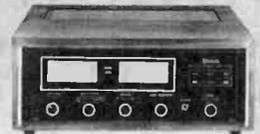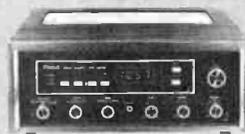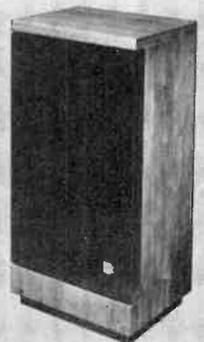Get all the newest and latest information on the new McIntosh catalog. In addition you will receive an FM station directory that covers all of North America.



SEND TODAY!

McIntosh Laboratory, Inc. PE
East Side Station P.O. Box 96
Binghamton, N.Y. 13904

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

If you are in a hurry for your catalog please send the coupon to McIntosh.
For non rush service send the Reader Service Card to the magazine.

CIRCLE NO. 52 ON FREE INFORMATION CARD

PIONEER Car Stereo	
KEX-20	219.99
KE-5100	219.99
KP-7500	186.99
KP-5500	135.99
GM-2 Power Amp	34.99
GM-4 Power Amp	51.99
CD-5 Equalizer	94.99
AD-30 Eq/Amp	94.99

SANYO CAR STEREO	
FT-30	184.99
FT-9	142.99
FTC-16	149.99

JENSEN CAR STEREO	
ALL MODELS IN STOCK CALL FOR THOSE NOT LISTED	
T-415 + EGA 3000	299.99
J-1023 Speakers	84.99/pr
J-1037 Speakers	64.99/pr
J-1065 Speakers	82.99/pr
J-1099 Speakers	48.99/pr
J-1101 Speakers	62.99/pr

CRAIG CAR STEREO	
T-690	214.99
T-619	189.99
R-200	184.99
R-511	149.99

PANASONIC CAR STEREO	
COS-900	341.99
COS-828	266.99
COS-798	242.99
COS-781	222.99
COS-742	199.99
COS-737	184.99
COS-700	177.99

SPECIAL OF THE MONTH
JENSEN R-405 174.99

VIDEO	
Atari CX-2600 Video Game	149.00
TOK T-128 (VHS)	15.49
TOK HG-120 (VHS)	19.99
Maxell T-120 (VHS)	15.49
Fuji T-120 (VHS)	14.99
Sony L750 (Beta)	14.99
Sony L830 (Beta)	16.99
Fuji L500 (Beta)	10.99

MAXELL BLANK TAPES	
UDXL-II C-90	3.39
UDXL-II C-60	2.49
UDXL-I C-90	3.39
UDXL-I C-60	2.49
UD C-90	2.79
UD C-60	1.89
UD 35-1800 Reel	18.49
UD 35-180 Reel	15.29
UD 35-90B Reel	6.79
UD 35-90 Reel	5.49

*TOK BLANK TAPES	
SA C-90	2.99
SA C-60	2.29
AD C-90	2.49
AD C-60	1.79
D C-90	1.69
D C-60	1.29
LX-35-1800 Reel	18.49
LX-35-180 Reel	15.29
LX-35-90B Reel	6.79
LX-35-90 Reel	5.49

WRITE FOR FREE CATALOG
ORDERING INSTRUCTIONS
All merchandise is Factory Fresh with manufacturer's warranty. Send MONEY ORDER or CASHIER'S CHECK for Quick Shipment within 24 Hours. Add Shipping Charges \$4.25. Canada and Puerto Rico add 10% of order. Personal Checks held for 3 weeks.
Customer Service HOT-LINE (212) 683-9088
We carry full lines of SHERWOOD, HARMON-KARDON, NIKKO, SONUS, as well as SONY, MITSUBISHI, CRAIG, and CONCORD car stereos.

Audiomatic Electronics
CALL TOLL-FREE 800-223-2706
In N.Y., Hawaii, Alaska, & Canada Call (212) 686-5500
1263 Broadway, New York, N.Y. 10001

CIRCLE NO. 9 ON FREE INFORMATION CARD

NEW INDOOR ACTIVE ANTENNA

Covers 300 KHz - 30 MHz.
For SWL, BCL, VLF DXers.

Rivals long wires

\$79.95 (+ \$4.00 shipping)



MFJ-1020 NEW INDOOR ACTIVE ANTENNA sits on your desk ready to listen to the world. Rivals, can often exceed, reception of outside long wire. Unique Tuned Active Antenna minimizes intermod, provides RF selectivity, reduces noise outside tuned band. Also use as preselector for external antenna. Covers 300 KHz to 30 MHz in five bands. Adjustable telescoping antenna. Controls: Tune, Band Selector, Gain, On-Off/Bypass. LED. FET, bipolar circuitry. Phono jack for external ant. 6x2x6 inches. 9-12 VDC or 9 V battery for portable use. 110 VAC with optional AC adapter, \$7.95.

Order from MFJ and try it. If not delighted, return within 30 days for refund (less shipping). One year unconditional guarantee. Order yours today. Call toll free 800-647-1800. Charge VISA, MC. Or mail check, money order.

CALL TOLL FREE ... 800-647-1800

MFJ Enterprises, Inc.
BOX 494, MISS. STATE, MS 39762


CIRCLE NO. 51 ON FREE INFORMATION CARD

TIPS & TECHNIQUES

Negative Logic Gates

An experimenter who is accustomed to reading schematics containing positive-logic gate symbols might be confused when a gate symbol with negative-logic inputs turns up. Here's a simple way to

AND GATE WITH NEGATIVE-LOGIC INPUTS

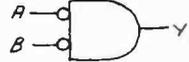


TRUTH TABLE FOR AND GATE WITH POSITIVE-LOGIC INPUTS

A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

TRUTH TABLE FOR AND GATE WITH INPUTS INVERTED

\bar{A}	\bar{B}	Y
1	1	1
1	0	0
0	1	0
0	0	0

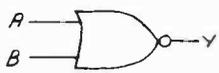TRUTH TABLE FOR NOR GATE WITH POSITIVE-LOGIC INPUTS




decipher those gates. Draw a truth table for the gate, ignoring the inverted inputs, as shown here (see figure). Then invert inputs on the truth table. Determine which type of gate fits this truth table. The truth table with the inverted inputs is that for a NOR gate with positive-logic inputs, which is the actual gate used in such a circuit.—John Fobel, Ontario, CA.

Low-Cost Holders for Soldering Irons

Small clay flower pots (about 4 in. diameter) make good, inexpensive holders for soldering irons. The pot is simply inverted and the iron tip inserted into the drainage hole. Because of its wide base, the holder is very stable; and, since the material is a poor heat conductor, it can be put on a finished table or desk top without causing damage to the finish. Needless to say, the flower pot costs only a fraction of an ordinary soldering-iron holder.—F. Penicka, Mississauga, Ontario, Canada

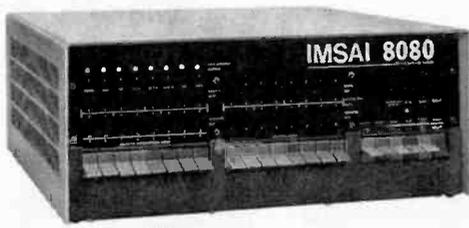Experience The World's Most Versatile Microcomputer



IMSAITM
8080

Kit \$599.00
Assembled \$799.00

- Includes:
- 22-Slot Motherboard with Sockets
 - 28 Amp Power Supply
 - MPU-A 8080 2 Mhz. Processor
 - Programmer's Front Panel

Send Check or Money Order to

IMSAI Computer Division of the Fischer-Freitas Corporation
910 81st Avenue, Bldg. 14 • Oakland, CA 94621
415/635-7615

Imsai is a trademark of the Fischer-Freitas Corporation

CIRCLE NO. 39 ON FREE INFORMATION CARD

ELECTRONICS LIBRARY

TRS-80 BASIC

by Albrecht, Inman & Zamora

This book has been written so that even a beginner can teach himself how to read, write, and program in BASIC on the TRS-80 microcomputer. The "programmed-instruction" format first introduces a topic and follows it with one or more questions, answers for which immediately follow the questions. Review questions at the end of each chapter allow the reader to gauge his progress. Games, graphics, learning tools, and home management applications are given to illustrate programming techniques. Since the book's main thrust is the BASIC language itself, procedures for setting up the TRS-80 and use of a cassette recorder in the system are in separate appendices.

Published by John Wiley & Sons, Inc., 605 Third Ave., New York, NY 10016. Soft cover. 351 pages. \$8.95.

How to Repair CB Radios

by Lawrence E. Schultz

If any of you bodacious CBers are having trouble getting your ears on, here is a straightforward guide to CB troubleshooting and repair. In addition to examples of commercially available equipment, hints are given on how to build your own equipment and accessories. Written from a service technician's point of view, the manual provides a description of the circuitry in both 23- and 40-channel CB radios. Also covered are power supplies, distribution systems, antennas, transmission lines, and single-sideband radios.

Published by McGraw-Hill Book Co., Gregg Div., New York, NY. Soft Cover. 192 pages. \$9.95.

Video/Computers

by Charles J. Sippl & Fred Dahl

Almost every American household contains video and audio terminals—the television set and telephone. These terminals can be interfaced with a number of devices, most importantly, the microcomputer (or computer terminal) and the VCR. If you're interested in imaginative ways to combine this technology, this book may be a good source of ideas. Simple sketches show how things work, and configuration diagrams help you develop your own construction projects. Hardware is listed by manufacturer, with an overview of basic specifications. Published by Prentice-Hall, Inc., Englewood Cliffs, NJ 07632. Hard cover. 246 pages. \$15.95.

Interrelated Integrated Electronics Circuits

by R.M. Mendelson

Here's a book for the project builder. It contains details for building a diversity of interesting electronic projects, including power supplies, amplifiers, passive circuits, test and measurement instruments, and electronic games. All told, there are 25 projects. Among the items you can build are an audio mixer, SSB detector, resistance boxes, portable DMM, battery-powered frequency

counter, electronic dice, and a digital roulette "wheel." Each project is fully described, accompanied by circuit description, schematic diagram, parts list, component-layout diagram, hints on construction, and photo of the finished project. Etching-and-drilling guides for each project are contained in the appendix at the back of the book.

Published by Hayden Book Co., Inc., 50 Essex St., Rochelle Park, NJ 07662. Soft cover. 128 pages. \$6.95.

Hear there and everywhere.



Easy tuning, digital display, professional quality

R-1000

The R-1000 is an amazingly easy-to-operate, high-performance, communications receiver, covering 200 kHz to 30 MHz in 30 bands. This PLL synthesized receiver features a digital frequency display and analog dial, plus a quartz digital clock and timer.

R-1000 FEATURES:

- Covers 200 kHz to 30 MHz continuously.
- 30 bands, each 1 MHz wide.
- Five-digit frequency display with 1-kHz resolution and analog dial with precise gear dial mechanism.
- Built-in 12-hour quartz digital clock with timer to turn on radio for scheduled listening or control a recorder through remote terminal.
- Step attenuator to prevent overload.
- Terminal for external tape recorder.
- Tone control.
- Built-in 4-inch speaker.

- Three IF filters for optimum AM, SSB, CW. 12-kHz and 6-kHz (adaptable to 6-kHz and 2.7-kHz) for AM wide and narrow, and 2.7-kHz filter for high-quality SSB (USB and LSB) and CW reception.
- Dimmer switch to control intensity of S-meter and other panel lights and digital display.
- Effective noise blanker.
- Wire antenna terminals for 200 kHz to 2 MHz and 2 MHz to 30 MHz. Coax terminal for 2 MHz to 30 MHz.
- Voltage selector for 100, 120, 220, and 240 VAC. Also adaptable to operate on 13.8 VDC with optional DCK-1 kit.

OPTIONAL ACCESSORIES:

- SP-100 matching external speaker.
- HS-5 and HS-4 headphones.
- DCK-1 modification kit for 12-VDC operation.



KENWOOD

TRIO-KENWOOD COMMUNICATIONS INC.
1111 WEST WALNUT / COMPTON, CA 90220

NEW LITERATURE

Heathkit Catalog

The new 104-page catalog from Heath includes, in addition to the company's standard kits for amateur radio, stereo, and test equipment, new kits for a 2-meter amplifier, a deluxe antenna tuner, a cordless digital wall clock, and a speedometer/trip log for boats. An educational section includes self-study courses in computer programming, microprocessors, optoelectronics, and hobby electronics. **Address:** Heath Co., Dept. 350-800, Benton Harbor, MI 49022.

PC Drafting Manual and Catalog

Catalog No. 107 from Bishop Graphics describes, in 200 pages, the company's line of pressure-sensitive aids for printed-circuit design and other drafting products. Among methods illustrated are the use of overlay drafting to achieve the accuracy of computer-aided tech-

niques while maintaining the flexibility of manual layout. Also featured are 20,000 printed-circuit drafting aids to create precision pc artwork masters. **Address:** Bishop Graphics, Inc. 5388 Sterling Center Dr., Westlake Village, CA 91359.

Solid-State Replacement Guide

The 1981 RCA SK line of solid-state replacements are listed in a new guide covering 1,300 devices which replace 170,000 domestic and foreign types. Included are transistors, rectifiers, thyristors, integrated circuits, triplers, etc. The 408-page Guide (SPG-202Z) is \$2.25 from RCA distributors or RCA Distributor and Special Products, Box 597, Woodbury, NJ 08096.

US GPO Catalog

The US Government Printing Office has assembled a brochure describing 23 titles of publications on the subjects of radio and electronics. Ranging in price from \$1.90 to \$7.70, the publications cover subjects as diverse as "Basic Electronics" to "Repair of FM Transmitters and Receivers" and "Cathode-Ray Tubes and Their Associated Circuits." The catalog, "Radio and Electronics," can be obtained free from the Superin-

tendent of Documents, Washington, DC 20402.

Miniature Tool Catalog

Catalog C-8010 describes the Moody line of miniature screwdrivers, sockets, hex key wrenches, drills, and taps available in sets and kits. Tools are interchangeable in a solid-locking, chuck-type, knurled handle and are intended for work on models and electronics. **Address:** Moody Tools Inc., 42-60 Crompton Ave., E. Greenwich, RI 02818.

Guide to Loudspeakers

Dahlquist Inc. has published an 8-page brochure called "Hearing and Believing," which describes, in nontechnical language, the theory and proper use of loudspeakers. It discusses such topics as "Spectral Balance," "Imaging," "Dynamic Range," "Driver Blending," and "Practical Hints." **Address:** Dahlquist Inc., 601 Old Willets Path, Hauppauge, NY 11787.

Variable Resistive Devices

"A Guide to Understanding and Specifying Variable Resistive Devices" gives, in 22 pages, performance parameter charts of trimmers and control and pre-

Make up to \$12⁵⁰ an hour

Start your own money making business!

Hundreds of Belsaw trained men have succeeded in this fascinating and highly profitable field... **YOU Can Do It Too!**

Be Your Own Boss!



BE A LOCKSMITH

Never before have money-making opportunities been so great for qualified Locksmiths. Now lucrative regular lock and key business has multiplied a thousandfold as millions seek more protection against zooming crime. Yet there's only one Locksmith for every 17,000 people!

Train FAST at Home - Collect CASH PROFITS Right Away. You're "in business" ready to earn up to \$12.50 an hour a few days after you begin Belsaw's shortcut training. Take advantage of today's unprecedented opportunities in Locksmithing for year-round EXTRA INCOME in spare-time—or fulltime in a high-profit business of your own. Hundreds we've trained have done it. So can YOU! All tools plus professional Key Machine given you with course. These plus practice materials and equipment, plus simple, illustrated lessons, plus expert supervision, plus business-building guidance will enable you to KEEP THE MONEY COMING IN! Ideal for retirement—good jobs too. **SEND FOR EXCITING FACTS—No obligation!** ALL SPECIAL TOOLS AND EQUIPMENT INCLUDED!

PRO KEY MACHINE YOURS TO KEEP!

This Pro Key Machine can absorb add up to 2000 keys to your income and it won't cost you a penny extra with your training. Find out all about it! **RUSH COUPON!**

FREE BOOKLET!

"KEYS TO YOUR FUTURE"

Tells how you quickly train to be your own boss in a profitable sparetime or fulltime business of your own. **Send for your copy today!**

Accredited Member National Home Study Council

10-DAY NO RISK TRIAL!

BELSAW INSTITUTE
1119 Field Bldg.
Kansas City, MO. 64111

There is NO OBLIGATION and NO SALESMAN Will Call—ever!

FREE! BELSAW INSTITUTE
1119 Field Bldg., Kansas City, Mo. 64111
Please rush FREE Book "Keys to your Future."

NAME: _____

ADDRESS: _____

CITY: _____

STATE: _____ ZIP: _____

CLIP AND MAIL COUPON TODAY TO:
POLY PAKS, INC.
P.O. BOX 942, PO-9
S. LYNNFIELD, MA. 01940 (617) 245-3828



FREE!

1981 DISCOUNT ELECTRONICS CATALOG

Over 4.5 Million Satisfied Customers

JOIN THE PAK!

Send for our Free catalog and become a member of our exclusive Pak. Our members receive Poly Paks' exciting catalog several times a year. We offer:

- Penny Sales, Free
- Premiums and Low,
- Low Prices on a wide variety of

Electronic Products such as Computer Peripherals, Integrated Circuits, Speakers, Audio Equipment, Rechargeable Batteries, Solar Products, Semiconductors, and much, much more!

Take advantage of our 25 years as America's foremost Supplier of discount electronics.

RUSH ME YOUR FREE DISCOUNT CATALOG!

NAME: _____

ADDRESS: _____

CITY: _____

STATE: _____ ZIP: _____

CLIP AND MAIL COUPON TODAY TO:
POLY PAKS, INC.
P.O. BOX 942, PO-9
S. LYNNFIELD, MA. 01940 (617) 245-3828

CIRCLE NO. 57 ON FREE INFORMATION CARD

<p>KEY SWITCH</p> <p>S.P.S.T. 125 VOLTS RATED 4 AMPS \$ 3.50 EA.</p>	<p>4PDT PRINTED CIRCUIT 12 VDC</p> <p>14 pin style 3 amp contacts BRAND NEW P.C. Mount \$ 2.75 EA.</p>
<p>COMPUTER GRADE CAP.</p> <p>NEW</p> <p>6,400mfd 60 VDC \$2.50 1 3/8" DIA X 4 1/4" \$2.00 22,000mfd 15 VDC 2" DIA X 2 1/2" HIGH \$2.50 20,000 mfd 25 VOLTS 2" DIA. X 2 1/2" HIGH \$2.00 22,000 mfd 40 VOLTS 2" DIA. X 6" HIGH \$3.00 CLAMPS TO FIT CAPACITORS 50c ea.</p>	<p>SUPER SMALL PHOTO-FLASH</p> <p>170 MFD 330 VOLT 1 1/4" x 7/8" 2 for \$1.50 10 for \$ 7.00</p>
<p>SUB MINI L.E.D.</p> <p>.079" x .098" 20 mA @ 1.75V 10 for \$1.00 200 for \$18.00 400 for \$32.00 1000 for \$70.00</p>	<p>MINI SIZE S/S BUZZERS</p> <p>1 1/2 to 3 volts WITH WIRE LEADS 75¢ each</p> <p>1 1/2 to 3 volts WITH PIN TERMINALS 75¢ each</p> <p>3 to 7 volts WITH PIN TERMINALS 75¢ each</p>
<p>TRANSFORMERS</p> <p>120 volt primaries</p> <p>6 VOLTS at 150 mA \$1.25 12 V.C.T. at 500mA \$2.50 16.5 V. at 3 AMPS \$6.50 18 VOLTS at 1 AMP \$4.50 25.2 VCT at 2.8 AMP \$5.50</p>	<p>PHONE JACK MOLDED PLASTIC NO SWITCH</p> <p>10 FOR \$1.00 100 FOR \$ 8.00 500 FOR \$ 40.00 1000 FOR \$ 70.00</p>
<p>DPDT RELAY 12 VDC</p> <p>AROMAT HL2-P-DC12VDC compact size 10 amp contacts P.C. mount \$ 3.00 each</p>	<p>FLASHER L E D</p> <p>Litronix FRL-4403</p> <p>diffused red led with built in flashing unit 1 1/4 package pulse rate 3Hz @ 20 ma. 2 for \$1.70</p>

ALL ELECTRONICS CORP.

905 S. Vermont Ave.
P.O. BOX 20406
Los Angeles, Calif. 90006
(213) 380-8000
Mon. - Fri. Saturday
9 AM - 5 PM 10 AM - 3 PM
SEND FOR FREE CATALOG

TERMS
• Quantities Limited
• Min. Order \$10.00
• Add \$2.00 Shipping USA
• Calif. Res. Add 6%
• Prompt Shipping

CIRCLE NO. 3 ON FREE INFORMATION CARD

cision potentiometers to help the user choose the best device for his application. A series of schematic diagrams shows how each component is applied in particular circuits. **Address:** Variable Resistive Components Institute, 3451 Church St., Evanston, IL 60203.

CB Antenna Catalog

Featured in a new catalog of CB and scanner antennas from Avanti are two glass-mounted, 1/2-wave units designed for easy mounting on the window or any other smooth surface. Other models include the Moonraker and various base station antennas, plus rotators. **Address:** Avanti Communications, 340 Stewart Ave., Addison, IL 60101.

Mount-Anywhere Sound Cabinets

A 4-page brochure describes two models of the Advantage sound cabinets, featuring Jensen Triax speakers and Advantage Bass Resonator PortHoles. The cabinets are designed to be mounted in any type of vehicle or at home and can also be removed for use out-of-doors. **Address:** Advantage Sound Systems, Inc., Box 970, Jonesboro, AR 72401

Video Production Catalog

A 20-page publication "Video Update" provides information about video production, editing, and use of several new devices in the video field. For example, the Special Effects Keyer adds color titles and graphics to color videotapes during editing. Two devices enable video producers to use an Apple computer as color graphics generator. Request on letterhead, including \$1.50 for postage and handling from: Adwar Video, 100 Fifth Ave., New York, NY 10036.

Assembly Tool Catalog

The Contact East 1981 Catalog offers a guide to over 10,000 products in the areas of hand tools, soldering and desoldering equipment, multimeters, oscilloscopes, anti-static material, test probes, and field service tools. **Address:** Contact East, Inc., Box 160, 7 Cypress Dr., Burlington, MA 01803.

Car Stereo Installation

A 46-page booklet entitled "How to Install a Car Stereo," from Pioneer Electronics, includes sections on wiring, noise problems, speaker mounting, antennas, and power sources. Helpful drawings give installation and dimensional details. Available at Pioneer dealers and from: Pioneer Electronics of America, 1925 E. Dominquez St., Long Beach, CA 90810 with a SASE.

Electronic Instrument Rental

A new 64-page catalog lists over 1,500 electronic test instruments available for monthly rental. Included are oscilloscopes, recorders, logic analyzers, microprocessor test systems, power meters, X-Y plotters, etc. Also computer peripherals such as line printers, ERTs and modems. Delivery is available from eight inventory centers. **Address:** Continental Resources, Inc., 175 Middlesex Turnpike, Bedford, MA 01730.


FCC Regulations on EMI

"The FCC and You" is the title of a booklet published by Sierracin/Power Systems to describe the new FCC regulations governing EMI emissions as they apply to computer devices. Directed primarily toward the computer manufacturer, the rules are of interest to users in that they include topics such as devices affected, what the restrictions are, rule

enforcement and penalties, EMI emission levels, etc. **Address:** Sierracin/Power Systems, 20500 Plummer St., Chatsworth, CA 91311.

Planer Molder Saw

3 Power TOOLS in 1
Feed

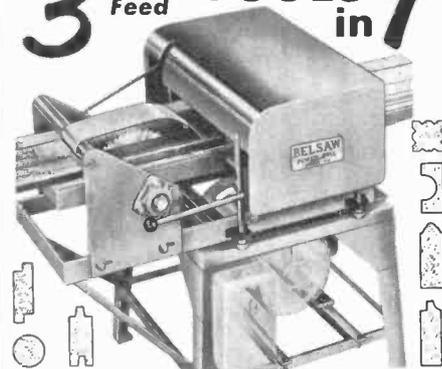

Now you can use this ONE power-feed shop to turn rough lumber into moldings, trim, flooring, furniture —ALL popular patterns. RIP-PLANE-MOLD . . . separately or all at once with a single motor. Low Cost . . . You can own this power tool for only \$50 down.

30-Day FREE Trial! SEND FOR EXCITING FACTS
NO OBLIGATION—NO SALESMAN WILL CALL
RUSH COUPON BELSAW POWER TOOLS CO.
TODAY! 9353 Field Bldg.
Kansas City, Mo. 64111


BELSAW **BELSAW POWER TOOLS**
9353 Field Bldg., Kansas City, Mo. 64111

YES Please send me complete facts about PLANER—MOLDER—SAW and details about 30-day trial offer.

Name _____
Address _____
City _____
State _____ Zip _____

CIRCLE NO. 14 ON FREE INFORMATION CARD

Gnat's Eyebrow, Indeed!

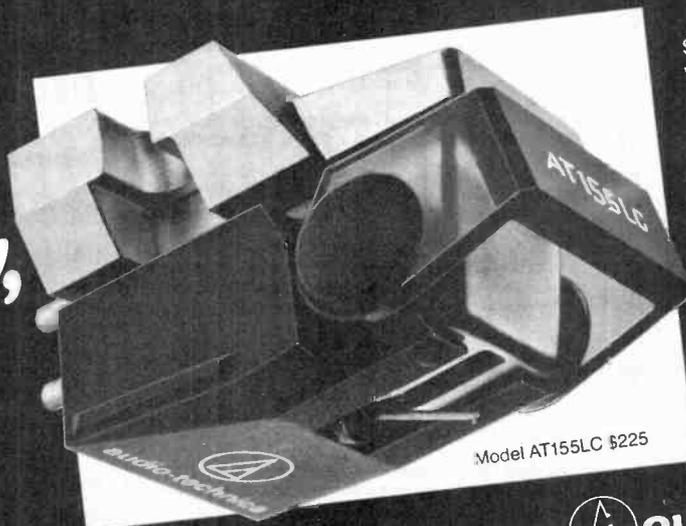


Model AT155LC \$225

Sonic accuracy depends on your stylus. At A-T, we precision shape our best styli with square shanks to micron accuracy (one micron = 0.0000393"). A perfect mounting hole is drilled in the beryllium cantilever by laser. Another laser beam checks each stylus surface for absolute alignment far more accurately than any microscope. All to assure you uncommonly low distortion and dramatic stereo separation... impossible with ordinary round-shank styli. Hear the Audio-Technica difference today!

audio-technica

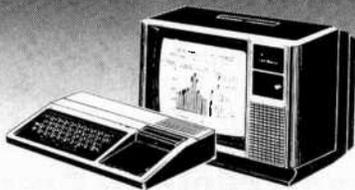**TEXAS INSTRUMENTS
TI-99/4A
HOME COMPUTER**



Whether you're already quite knowledgeable about computers or want to learn how to get started, the TI-99/4 is for you. By simply snapping in one of the many Solid State Software Command Modules either you or just about anybody in your family can use the TI-99/4 because step-by-step instructions are displayed right on the screen.

The TI-99/4 gives you an unmatched combination of features, including:

- Powerful TI-BASIC
- Up to 72K total memory capacity
- **NEW** typewriter keyboard
- 13" color monitor is optional
- Revolutionary TI Solid State Speech Synthesizer is optional

Retail price \$550. Your special BACH Company price **\$499**. Order by September 31, 1981 and get **150.00** worth of TI Software absolutely **FREE!**

ORDER TOLL FREE 800-227-8292

California residents call 415-494-1995. Use VISA, MasterCard, check or money order. Indicate card number and expiration date. Order product no. 54. Add \$4.50 for shipping.

The BACH Company
P.O. Box 51178
Palo Alto, CA 94303



CIRCLE NO. 11 ON FREE INFORMATION CARD

SEE YOUR DEALER TODAY

DEMAND THE ORIGINAL

'Firestik'®

The #1 Helically Wire-Wound and Most Copied Antenna In the World!
27MHz AM/FM/SSB CB
2 METER • MARINE TELEPHONE
LAND MOBILE TELEPHONE
**FIBERGLASS ANTENNAS
AND ACCESSORIES.**

**NEW
CORDLESS
TELEPHONE
ANTENNA**

INCREASES DISTANCE
5 TO 20 TIMES

Dealer & Distributor Inquiries Invited
SEND FOR FREE CATALOG

'Firestik' Antenna Company
2614 East Adams/Phoenix, AZ 85034

Name _____
Street _____
City _____
State _____ Zip _____

Serving the CB and
Communications Market Since 1962.

5-YEAR REPLACEMENT WARRANTY

CIRCLE NO. 30 ON FREE INFORMATION CARD

**OPERATION
ASSIST**

If you need information on outdated or rare equipment—a schematic, parts list, etc.—another reader might be able to assist. Simply send a postcard to Operation Assist, POPULAR ELECTRONICS, 1 Park Ave., New York, NY 10016. For those who can help readers, please respond directly to them. They'll appreciate it. (Only those items regarding equipment not available from normal sources are published.)

Jackson model 112 capacitor tester. Need operating manual, schematic and parts list. Tom Hirsch 846 N. Oliver, Wichita, KS 67208.

Ampeg model B-25 amplifier. Need schematic diagram and any other available information. William McGuire, 162 Brookhaven Ave., Cincinnati, OH 45215.

Knight model 290 FM stereo tuner. Need schematic and service data. R.L. Willard, 111-10th St., New Orleans, LA 70124.

General Electric model FE53JC radio. Need manual and schematic. James Zacher, 121 Hilton Pl., Elgin, IL 60120.

Hallcrafters SX-122 receiver. Need operations manual, schematic and any other available information. Ronald S. Rubin, 1722 Canterbury Circle, Casselberry, FL 32707.

Claricon model 30600 "Privateer" CB. Need schematic and service manual. Joe Chew, Box 2469, Campus Station, Socorro, NM 87801.

Allied star roamer. Need assembly instructions. Tom Pridmore, Box 2095, Melbourne, FL 32901.

Admiral model 394-11B, serial #A308695 radio. Need schematic and dial face. Robert E. Hopkins, 123 W. Marseille Dr., St. Louis, MO 63129.

Precision Apparatus Co., Inc., model E200C signal generator. Need schematic, parts list, and manual. Bill Pechter, 134 Juniper Dr., Freehold, NJ 07728.

Hallcrafters S-85 receiver. Need operating manual and schematic. S.M. VanZant, 166 S. Madera Ave., #63, Kerman, CA 93630.

Kintel model 202BR dc microvoltmeter, serial #2278. Need schematic or manual. Dan Amen, Route 1, Pawnee, OK 74058.

DSI Instruments model #5500 frequency counter. Need schematic. R. Craig Bracken, Rt. Box 84A, Davenport, WA 99122.

Waico Electronics Co., model WA75 transmitter. Need schematic and operating manual. Curtis E. Frazier, 92 West Main St., Rockville, CN 08086.

Sears & Roebuck model 280-626-730 CB/FM radio. Need schematic diagram. Frederick J. Darling, Jr., Box 549, Ayer, MA 01432.

Philco BC221-E frequency meter. Need high band coil, part #22. William J. O'Meara, 807 E. Seminary Ave., Towson, MD 21204.

Hallcrafters model S-40A receiver. Need operation manual, schematic, and service manual. C.H. Nelson, 4712 School, Yorba Linda, CA 92686.

Precision model 10-54 Test Master. Need schematic, operation manual and parts list. B. Robinson, 75-E Nelson Pt. Road, Indian Head, MD 20640.

Tektronix model 511D oscilloscope. Need manual. James A. McCoy, 2734 E. 6th St., Casper, WY 82601.

Realistic DX150 Allied Star Roamer. Need schematic diagram, alignment instructions, and assembly instructions. Tom Pridmore, Box 2095, Melbourne, FL 32901.

Electronics International model 8007 receiver. Need schematic. Andy Anderson, 2250 Cable Ave., Beaumont, TX 77703.



**DON'T
BLAME
THE
SOFTWARE!**

Pat. #4,259,705

Power Line Spikes and Hash often cause memory loss or erratic operation. Often floppies, printer & processor interact!

OUR patented ISOLATORS eliminate equipment interaction AND curb damaging Power Line Spikes, Surges and Hash.

Filtered 3-prong sockets and integral Spike Suppression. 125 VAC, 15 Amp, 1875 W Total - 1 KW per socket.

ISO-1 ISOLATOR. 3 Filtered Sockets; 1000 Amp 8/20 usec Spike Suppressor \$62.95

ISO-4 ISOLATOR. 6 Filtered Sockets; 1000 Amp 8/20 usec Spike Suppressor \$106.95

ISO-3 SUPER-ISOLATOR. 3 DUAL filtered Sockets; 2000 Amp 8/20 usec Spike Suppressor \$94.95

ISO-7 SUPER-ISOLATOR. 5 DUAL filtered Sockets; 2000 Amp 8/20 usec Spike Suppressor \$154.95

MasterCharge, Visa, American Express
TOLL FREE ORDER DESK 1-800-225-4876
(except AK, HI, MA, PR & Canada)

Electronic Specialists, Inc.

171 South Main Street, Natick, MA 01760

Technical & Non-800: 1-617-655-1532

CIRCLE NO. 25 ON FREE INFORMATION CARD

Put Professional Knowledge and a
COLLEGE DEGREE
in your Electronics Career through

**HOME
STUDY**



**Earn Your
DEGREE**

No commuting to class. Study at your own pace, while continuing your present job. Learn from easy-to-understand lessons, with help from your home-study instructors whenever you need it.

In the Grantham electronics program, you first earn your A.S.E.T. degree, and then your B.S.E.T. These degrees are *accredited* by the Accrediting Commission of the National Home Study Council.

Our *free* bulletin gives full details of the home-study program, the degrees awarded, and the requirements for each degree. Write for *Bulletin ET-81*.

Grantham College of Engineering
2500 So. LaCienega Blvd.
Los Angeles, California 90034

operation assist

Precision model 954-G tube tester, serial # 13610. Need current roll chart. Karl Hund, Box 81, Beaverton, MI 48612.

Hickok 110A VTVM. Need manual. Bill Springer, 923 Nelda, Houston, TX 77088.

Tektronix model 533 and RM43 scopes. Need manuals and schematics. A.G. Lowrance, 316 Polk St., Waterloo, IA 50703.

National Semiconductor chip MM58106 digital clock and TV display. Need circuit diagram and information on proper hookup to TV. J. A. Caggianelli, Ashdown Rd., Ballston Lake, NY 12019.

Typograph Corp., model DPM-30 printer. Need service manual. I. Carah, Box 11583, Zephyr Cove, NV 89448.

Tektronix type 512 oscilloscope. Need operating manual and schematic. Al Shor, Box 493, Cardiff, CA 92007.

Monitor Radio model MR-33, serial #7233 receiver. Need schematic, parts list or any available data. Henry J. Hacker, 27 Clarendon Ave., Pikesville, MD 21208.

Galvin BC-611 transceivers. Need any data available. M. Dunn, 45 Livingston Rd., #501, West Hill, Ontario, Canada M1E 1K8.

Ogawa model RS-1 receiver and Harmony model 530 bass amplifier. Need schematics. George Nishimoto, 504 Hoopun St., Hilo, HI 96720.

Concord Electronics Corp., model R-1100 tape deck. Need service information and power transformer. Mike Smith, Box 15337, Sarasota, FL 33579.

Olsen TE-188 r-f signal generator. Need schematic. Hugh Siuda, 512 W. Rand Dr., McHenry, IL 60050.

Allied Radio Corp., Knight model 2-JZ018. Need operating manual and schematic. Mike Dale, 1198 Lock 4 Rd., Gallatin, TN 37066.

Telequipment type S51A servoscope. Need schematic and operation manual. Jack Allen, Woodside Lane, Riverton, NJ 08077.

Ford Industries, Inc., model 1400 phone answering device. Need schematic. Van S. Vangor, Box 346C, Island Falls, Maine 04747.

Dumont type 279 oscillograph. Need schematic and manual. Everett Thompson, R.F.D. #61, La Grange, ME 04453.

Hammurand HZ100 receiver. Need schematic and alignment data. R. McKinnan, Box 1241, San Juan, TX 78589.

Allied model 2515 receiver. Need manual and schematic. Ed Bolin, 7650 Ovaldale St., Charleston, SC 29405.

Hallcrafters model SX-99 receiver. Need operation manual, schematic and service manual. Ross W. Smith, 1816 Abelia Rd., Fallston, MD 21047.

Stromberg-Carlson model AWP8 multi-band receiver. Need owner's manual and operating instructions. Steven A. Davis, Rt. #4, Box 295A, Angola, IN 46703.

RCA Radiola model 44 antique radio. Need tube #45. T. Wright, 4933 Yakima, Pocatello, ID 83204.

Radio City Products Co., Inc., model 664 meter. Need schematic and operating manual. J. Welden Dupre, W5SNK #7 HMS Court, Houma, LA 70360.

Dynaklt model 70 stereo. Need owner's manual. W.M. Breneman, 1000 W. Aaron Dr., #1-1, State College, PA 16801.

Hallcrafters model S-94 civic patrol receiver. Need schematic and service manual. Allen T. Purdy, 17 Dunwoode St., Yonkers, NY 10704.

Hallcrafters SX-100 receiver. Need service data, schematic and alignment procedures. Charles F. Gould, 333 South Fifth Street, Darby, PA 19020.

Itron model 680 frequency counter. Need schematic. W.W. Bell, 1813 Nortonia Rd., Richmond, VA 23229.

DSI Instruments Inc., model 5612 frequency counter. Need schematic, or any information on AM56 Audio Multiplier option for this counter. Gerard Johnson, P.O. Drawer 191, Morgan City, LA 70380.

Video Brain model 101A. Need manual, schematic or any information available. Gary Wojcik, 3916 1/2 N. Kedvale, Chicago, IL 60641.

Phone Mate 9000 answering machine. Need IC chip placement and schematic diagram. J. Ward, Box 5685, Virginia Beach, VA 23455.

Hallcrafters SX 130 receiver. Need schematic and maintenance manual. Mike Kaufman, K6VCI, 107 Sutfield Ave., San Anselmo, CA 94960.

Robosonic Industries model 100 record-er-ophone. Need service data and schematic. Stan Kern, 3 Cinnamon Circle, Apt. 3C, Randallstown, MD 21133.

Sterling model 70-0175 receiver and Bogen series BT-97 Intercom system. Schematic and operation manuals needed.

M. Maynard, 6109 E. Gold Dust Ave., Scotts, AZ 85253.

Tektronix model 555 oscilloscope. Need calibration instructions and schematic for power supply. Roy Kunst, 80 Willow Ave., Hackensack, NJ 07601.

Beston model CTR800 tape recorder radio. Need tape head H7310 and schematic. W.A. Williams, 6020 Lloyd, St. Louis, MO 63110.

Allied Electronics Knight space scanner. Need schematic and operating manual. Douglas Cummings, 1360 N. Celia Way, Layton, UT 84041.

LIVE VIA SATELLITE TV NOW!



- UNDER \$500 DISH ANTENNA
 - FOR ROOF, PORCH, BACKYARD
 - 90 CHANNEL RECEPTION
- JUST PUBLISHED:

8 1/2" by 11" informative book gives a wealth of updated information on • Antennas • Receivers • Low Noise Amplifiers • Sources • Services • Equipment • Manufacturers • Much More

It's Easy ORDER NOW

LIVE VIA SATELLITE, INC.
P.O. Box 2561 Dept. E9

Delray Beach, FL 33444

SEND \$9.95 TODAY.

For first class air mail & handling in U.S. & Canada add \$2.50 U.S. funds. Foreign customers send \$3.50 U.S. Funds. Or call our 24-hour C.O.D. Order Line (305) 845-4447. NOW

Name _____ Zip _____
Address _____

CIRCLE NO. 69 ON FREE INFORMATION CARD

AMAZING DEVICES

(((PHASERS)))

PPF-1 PHASER PAIN FIELD — This device recently developed and patented in our labs is being evaluated by law enforcement agencies for riot and crowd control. It is now available but soon will come under the jurisdiction of weapons and internal machine control making it unavailable to the public. The device is hand-held and looks like a BUCK ROGERS ray gun. It is hazardous if not used with discretion.

PPF-1 PLANS \$15.00

IPG-1 INVISIBLE PAIN FIELD GENERATOR — This amazing, simple hand-held device is about the size of a pack of cigarettes and generates a directional field of moderate to intensive pain in the lower part of the head up to a range of 50'. Device is simple and economical to make.

IPG-1 PLANS \$7.00 IPG-1K ALL PARTS \$39.50

IPG-10 ASSEMBLED & TESTED FOR ANIMAL CONTROL \$49.50

LASERS

RUBY LASER RAY PISTOL — Produces highly intense red beam, capable of burning. A hazardous device. PLANS, PARTS, SOURCES \$15.00

HIGH POWERED CARBON DIOXIDE BURNING AND CUTTING. Complete plans and all parts sources \$15.00

SOLID STATE IR 12 WATTS with built in power supply plans \$8.00 Complete kit with collimator \$74.00

POCKET LASER pulsed, visible red, plans \$7.00 Complete kit \$39.50 Also complete plans and parts sources for RUBY, YAG, NEODYMIUM, HeNe ARGON, DYE, NITROGEN and many more lasers.

SECURITY

SNP-2 SNOOPER PHONE — Dial home or office phone while on vacation activating sensitive mike without phone ringing. Excellent property protection and intrusion device.

SNP2 PLANS \$7.00

SNP2X ALL PARTS \$49.50

SNP20 ASSEMBLED AND TESTED \$99.50

LONG RANGE XMTR PLANS \$7.00

SEE-IN-THE-DARK PLANS \$10.00

DIRECTIONAL SHOTGUN MIKE PLANS \$8.00

SUPER SENSITIVE PARABOLIC MIKE PLANS \$8.00

SOUND & TELEPHONE OPERATED TAPE RECORDER \$7.00

CATALOG ON PLANS, KITS & FINISHED UNITS \$1.00

Send check or money order to

SCIENTIFIC SYSTEMS, Dept. Q1, Box 716


AMHERST, N.H. 03031

CIRCLE NO. 61 ON FREE INFORMATION CARD

SIMPLE SIMON 7+11 PART KITS

MITSUMI UHF TUNER
\$34.95

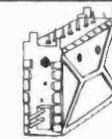Freq. Range UHF 470 - 889 MHz
Channels 14-83 Output Chan 3



1 VT1-SW	Varactor UHF Tuner Model UES-A55F	\$34.95
2 CB1-SW	Printed Circuit Board Pre-Drilled	\$18.95
3 TP2-SW	P.C.B. Potentiometers 1-20K 1-1K & 5-10K OHMS, 7-pieces	\$5.95
4 FR35-SW	Resistor Kit 1/4 W. 5% Carbon Film, 32-pieces	\$4.95
5 PT1-SW	Power Transformer PRI-117VAC, SEC-24VAC, 250MA	\$6.95
6 PP2-SW	Panel Mount Potentiometers & Knobs 1-1KB & 1-5KAT W SW	\$5.95
7 SS*4-SW	IC-5 ea. Diodes 4 ea. Regulators 2 ea. Heat Sink 1 ea.	\$29.95
8 CE8-SW	Electrolytic Capacitor Kit 9 ea.	\$5.95
9 CC13-SW	Ceramic Disk Capacitor Kit 50 W V 33 ea.	\$7.95
10 CT-SW	Variable Ceramic Trimmer Capacitors 5-65PFD, 6 ea.	\$5.95
11 L4-SW	Coil Kit 2 ea. 18MHZ 1 ea. 22MHZ Inductances-prewound and 1 ea. T37-12 Ferrite Toroid Core with 3 H of #26 Wire	\$5.00
12 ICS-SW	1 C. Sockets 1m Inlay 5 ea. 8 Pin, 2 ea. 14 Pin	\$1.95
13 SR SW	Speaker Oval 4x6 & With Prepunched Wood Enclosure	\$14.95
14 MISC-SW	Misc. Parts Kit Includes Hardware, 6 32 & 8 32 Nuts & Bolts, H.U. Wire, Ant. Terms, DPDT ANT SW, Fuse-Fuseholder etc.	\$9.95

When Ordering All Items 1 Thru 14 Total Price \$139.95

ANTENNA & ACCESSORIES

STVA-1-STV	Yagi Antenna 13.5 DB, 75 OHM, CHN 42 Thru 54	\$9.95
STVA-2-STV	Yagi Antenna 13.5 DB, 75 OHM, CHN 20 Thru 26	\$9.95
	Variable Coaxial 75 OHMS Low Loss	\$12 PPF
	F-59 Coaxial Connectors ea.	\$3.95
	MT-1 Special UHF 75-300 OHM Matching Transformer ea.	\$1.45
	A-1 Indoor VHF-UHF Antenna Amplifier with Power Supply 300 OHM IN & OUT, APT 130db gain	\$19.95

Min. Order Amount is \$19.95. Add 10% Shipping and Handling. Over \$40.00 Add 5%.

MAIL ORDERS ONLY

SIMPLE SIMON ELECTRONIC KITS

Ca. orders mail to:
3871 S. Valley View, Suite 12
Las Vegas, Nevada 89103

Other orders mail to:
11850 S. Hawthorne Blvd., Hawthorne,
California 90250, Tel: (213) 675-3347
VISA — MASTERCARD ACCEPTABLE

CIRCLE NO. 70 ON FREE INFORMATION CARD

PROJECT OF THE MONTH

By Forrest M. Mims

Precision CMOS Clock Generator

SEQUENTIAL digital logic circuits require one or more clock pulse generators. Microprocessors often include built-in clock generators. Other sequential circuits may use clocks made from 555 timers, a pair of cross-coupled inverters, or a trio of inverters connected as a ring oscillator.

Intersil makes a general-purpose timer chip which, for a CMOS device, has extraordinary specifications. The chip is the ICM7209, available from some electronics mail order suppliers for about \$4.00.

The ICM7209 is guaranteed to oscillate at frequencies up to 10 MHz, and it can directly drive as many as five TTL gates. With a 5-volt power supply, the chip typically consumes 11 milliamperes and will operate with a minimum of three external components—two capacitors and a quartz crystal (Fig. 1).

The power dissipation of the ICM7209 is directly related to its oscillation frequency. Since the oscillator portion of the chip consumes much less power than its output buffers, power dissipation can be dramatically reduced when the chip is disabled by making pin 3 low. The oscillator portion will continue to operate, but the output buffers will be disabled, thus reducing their current drain.

The crystal can be any quartz crystal having a frequency of oscillation from 10 kHz to 10 MHz, and the circuit can be powered by a supply of 3 to 6 volts. For best results, the crystal should have a load capacitance of 10 pF rather than the usual 30 pF. When C1 and C2 are 18 pF, this provides a typical frequency stability of one part per million (ppm) per one volt change in supply voltage.

Note that the ICM7209 includes two output pins. The divide-by-eight output (pin 6) can be used to obtain many combinations.

While Fig. 1 shows the disable input (pin 3) connected to a switch, disable/enable controls can be easily provided by external logic. Pin 3 can also be connected to either the oscillator IN or OUT pins for some interesting results. For example, when pin 3 is

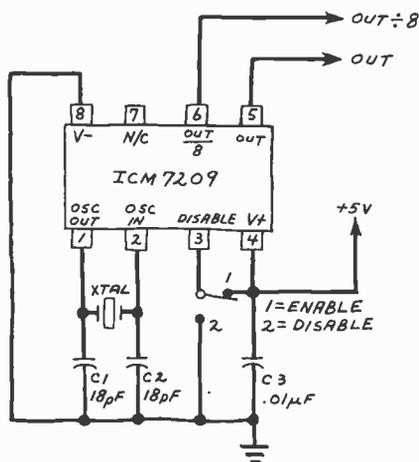


Fig. 1. A clock pulse generator using the ICM7209 chip with just three external components.

connected to pin 2, each of the divide-by-eight pulses appearing at pin 6 are further divided into four separate pulses. This provides a burst output mode not mentioned in the ICM7209's data sheet.

Figure 2 illustrates this chip's operation at its maximum guaranteed frequency of 10 MHz. Intersil claims typical rise and fall times of 10 nanoseconds (25 nanoseconds maximum) as measured from the 0.5-to-2.4-volt output points. These represent TTL logic levels.

As you see in Fig. 2, the circuit in Fig. 1 has a risetime better than 8

nanoseconds and a falltime faster than 7.5 nanoseconds. The pulse width is 50 nanoseconds FWHM (full width, half maximum). Figure 2 was taken directly from the screen of a 100-MHz oscilloscope. I assembled the oscillator on a standard plastic, solderless breadboard with short, point-to-point connection wires.

The ICM7209 provides an excellent solution to the need for a precision clock generator. Though the circuit shown in Fig. 1 isn't tunable, the oscillation frequency can be quickly altered by changing the quartz crystal used. ◇

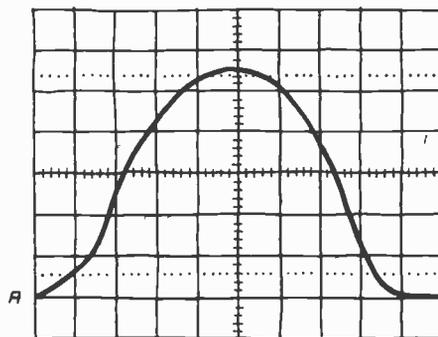


Fig. 2. Output waveform from an ICM7209 with a 10-MHz crystal.

VOLTS/DIV:
A. 1 TIME/DIV: 10 ns
B. _____

DIODES/ZENERS			
QTY			
1N914	100v	10mA	.05
1N4005	600v	1A	.08
1N4007	1000v	1A	.15
1N4148	75v	10ma	.05
1N4733	5.1v	1 W Zener	.25
1N4749	24v	"	.25
1N753A	6.2v	500 mW Zener	.25
1N758A	10v	"	.25
1N759A	12v	"	.25
1N5243	13v	"	.25
1N5244B	14v	"	.25
1N5245B	15v	"	.25
1N5349	12v	3W Zener	.25

SOCKETS/BRIDGES			
QTY			
8-pin	pcb .20	ww	.40
14-pin	pcb .25	ww	.60
16-pin	pcb .30	ww	.70
18-pin	pcb .35	ww	.95
20-pin	pcb .45	ww	1.05
22-pin	pcb .50	ww	1.15
24-pin	pcb .55	ww	1.25
28-pin	pcb .60	ww	1.45
40-pin	pcb .70	ww	1.75
Molex pins .01	To-3 Sockets		.35
2 Amp Bridge	200-prv		1.25
25 Amp Bridge	200-prv		2.25

TRANSISTORS, LEDS, etc.			
QTY			
2N2222M (Metal)	.25	(2N2222 Plastic)	.20
2N2222A	NPN		.35
2N2907A	PNP		.35
2N3906	PNP (Plastic)		.25
2N3904	NPN (Plastic)		.25
2N3054	NPN 4A 90v		.60
2N3055	NPN 15A 60v		.75
TIP125	PNP Darlington		.95
LED	Green Red Clear Yellow		.19
DL747	7 seg 5/8" High com-anode		1.95
DL728B	doub 7 seg 5" com-cathode		2.50
MA6740	doub 7 seg 5" com-cathode		2.50
MAN72	7 seg com-anode (Red)		1.50
MAN3630	7 seg com-anode		1.00
MAN82A	7 seg com-anode (Yellow)		1.50
MAN74	7 seg com-cathode (Red)		1.50

9000 SERIES			
QTY		QTY	
9301	1.95	9322	.65
9309	1.25	9601	.40
9316	.90	9602	.90

C MOS					
QTY		QTY		QTY	
4000	.40	4019	1.15	4041	1.15
4001	.35	4020	1.25	4042	.95
4002	.35	4021	.60	4043	.90
4006	.95	4022	1.25	4044	1.20
4007	.30	4023	.45	4046	1.50
4008	.55	4024	.95	4047	1.50
4009	.75	4025	.45	4048	2.50
4010	.75	4026	2.95	4049	.65
4011	.45	4027	.85	4050	.65
4012	.25	4028	.95	4052	.75
4013	.65	4029	1.00	4053	1.50
4014	.95	4030	.95	4060	2.25
4015	.95	4033	2.50	4066	1.25
4016	.55	4034	3.75	4069/74C04	.45
4017	.95	4035	1.75	4070	.60
4018	.75	4040	1.10	4071	.40
				4072	.50
				MC14409	12.50
				MC14419	4.85
				74C151	2.50

INTEGRATED CIRCUITS UNLIMITED, INC.

7889 Clairemont Mesa Blvd., San Diego, California 92111

Out of State 1-800-854-2211
California 1-800-542-6239

(714) 278-4394

Telex: 697-827
TWX 910-335-1577

Name _____
Street Address _____
City _____ State _____ Zip _____
Phone _____ Charge card # BA MC _____ Exp. Date _____
AE VISA

C.O.D. Will Call UPS Post Net 30 Days P.O. # _____

Add \$2.00 Shipping on all U.S. Orders - \$5.00 Minimum - C.O.D. Orders Accepted - Most Orders Shipped Same Day
Commercial Accounts Invited - California Residents Add 6% Sales Tax - PRICES SUBJECT TO CHANGE WITHOUT NOTICE

24 Hour Phone Service - We Accept American Express/Visa/BankAmericard/Master Card/Barclay Card/Access • 15% Restocking Charge After 10 Days
All Prices in U.S. Dollars - Foreign Orders F.O.B. San Diego

CIRCLE NO. 40 ON FREE INFORMATION CARD

MICROS, RAMS CPUs, E-PROMS	
1771 Disc Controller \$22.50	
8T13	1.50
8T23	2.50
8T24	2.50
8T97	1.50
74S188	4.50
1488	1.75
1489	1.75
1702A	8.50
AM9050/TMS4050	5.00
ICM7207	6.95
ICM7208	13.95
MM5314	6.50
MM5311	6.50
MM5316	6.50
MM5387	4.50
MM5369	3.95
TR1602B	5.95
UPD414/TMS4027	1.50
Z80A	1.00
Z80	9.50
Z80P1 (XA)	9.50
Z802L	1.75
Z107B-4	3.95
2114	4.00
2513 (5V) Up/Lo	9.50
2708	4.95
2716T1	6.95
2716(5V)	9.50
TMS2532/732	22.00
3242	12.50
4116	4.95
6800	9.50
6802	11.50
6820/6520	5.95
6850	7.50
8080	3.95
8085	9.50
8212	2.90
8214	4.95
8216	2.50
8224	4.25
8228	5.95
8251	7.50
8253	9.50
8255	7.50
TMS4044	5.95
ADC0800	22.95

— TTL —					
QTY		QTY		QTY	
7400	.25	7493	.60	74H10	.35
7401	.35	7494	.75	74H11	.45
7402	.35	7495	.60	74H15	.45
7403	.30	7496	.55	74H20	.45
7404	.35	74100	1.75	74H21	.35
7405	.35	74107	.55	74H22	.40
7406	.35	74111	3.00	74H30	.40
7407	.65	74121	.55	74H40	.45
7408	.50	74122	.70	74H50	.40
7409	.35	74123	.70	74H51	.40
7410	.35	74125	.75	74H52	.40
7411	.35	74126	.75	74H53	.45
7412	.35	74132	.75	74H55	.45
7413	.45	74141	.90	74H72	.45
7414	.65	74145	1.35	74H74	1.50
7416	.35	74150	1.15	74H101	.95
7417	.40	74151	.95	74H103	.55
7420	.45	74153	.95	74L00	.60
7426	.35	74154	1.40	74L02	.60
7427	.40	74156	.70	74L03	.35
7430	.40	74157	1.50	74L04	.30
7432	.65	74158	1.50	74L10	.30
7437	.45	74161	1.50	74L20	.75
7438	.50	74163	1.50	74L30	.55
7440	.40	74164	1.50	74L47	1.95
7441	.65	74165	1.70	74L51	.65
7442	.65	74166	1.10	74L55	.85
7443	.75	74175	.75	74L72	.65
7444	.75	74176	1.15	74L73	.70
7445	.75	74177	1.10	74L74	1.95
7446	.75	74180	1.10	74L75	1.05
7447	1.50	74181	2.25	74L85	3.00
7448	1.50	74182	.75	74L93	2.95
7450	.35	74190	1.25	74L123	2.95
7451	.50	74191	1.25	74LS00	.30
7453	.25	74192	1.50	74LS01	.30
7454	.35	74193	1.50	74LS02	.30
7460	.40	74194	.95	74LS03	.30
7470	.35	74195	.95	74LS04	.40
7472	.40	74196	1.75	74LS05	.30
7473	.40	74197	.95	74LS08	.40
7474	.45	74198	1.50	74LS09	.60
7475	.45	74221	1.50	74LS10	.40
7476	.45	74298	1.50	74LS11	.40
7480	.60	74367	1.15	74LS20	.40
7481	.95	75107A	.95	74LS21	.50
7482	.95	75451	.85	74LS22	.45
7483	.75	75452	.85	74LS27	.40
7485	.75	75491	1.50	74LS32	.60
7486	.55	75492	1.50	74LS37	.60
7489	1.95	74H00	.40	74LS38	.65
7490	.75	74H01	.40	74LS40	.70
7491	.60	74H04	.90	74LS42	.75
7492	.50	74H05	.55	74LS47	.95
		74H08	.90	74LS51	.95
				8131	2.75

I ² L, LINEARS, REGULATORS, etc.			
QTY		QTY	
XR2206	3.95	LM320K15	1.65
MCT2(E)	1.25	LM320K24	1.65
8038	4.50	LM320T5(7905)	1.65
LM201	2.00	LM320T12	1.65
LM301	.95	LM320T15	1.65
LM308	1.25	LM323K	4.95
LM309H	1.50	LM324	.85
LM309(340K-5)	1.50	LM337T	2.25
LM310	.85	LM339	.95
LM311 (8-14 Pin)	1.50	7805(340T5)	1.50
LM317T	2.25	LM340T12	1.50
LM318N	1.60	LM340T15	1.50
LM320H6	.89	LM340T18	1.50
LM320H15	.89	LM340T24	1.50
LM320H24	.89	LM340K12	1.50
LM320K5	1.65	LM340K15	1.50
LM320K12	1.65	LM340K18	1.50
		LM340K24	1.50
		LM373	3.95
		LM377	1.95
		78L05	.75
		78L12	.75
		78L15	.75
		78M05	1.95
		LM380(8-14 Pin) 386N	1.19
		LM709(8-14 Pin)	.75
		LM711	.75
		LM723	.75
		LM725	2.95
		LM739	1.95
		LM741(8-14)	.55
		LM747	1.25
		LM1307	1.75
		LM1458	.65
		LM3900	.95
		LM3909	1.50
		NE555	.50
		NE556	1.00
		NE565	1.50
		NE566	1.75
		NE567	1.50
		TA7205	2.95
		76477	2.95
		95H90	9.95
		TL081CP	.75

THIS IS A REPRESENTATIVE LIST OF STOCK ITEMS, OTHER ITEMS AVAILABLE UPON REQUEST. SPECIAL DISCOUNTS ON LARGE ORDERS.

Applektion PP II Printer Card

The PP II parallel printer card for the Apple II computer is designed to allow effective use of your printer which has special functions such as bold and enlarged face print available through the use of escape sequence commands. Since the Apple II does not send escape characters the software on this board does it for you with control characters from the keyboard. One of the main designs of the PP II card is that it contains space enough for 8 independent printer driver programs so new printers are not a problem. The PP II is software compatible with both Apple Basics as well as *CP/M or *Pascal.

*CP/M or Pascal disks providing the appropriate bios patches are available on special request.

PP II printer card (with cable) MX-80 or 737

\$199.95

ARKON ELECTRONICS LTD.

409 Queen St. West
Toronto, Canada M5V 2A5
(416-868-1315)



CIRCLE NO. 8 ON FREE INFORMATION CARD

SAVE!

MONEY • TIME • FREIGHT

- ♪ QUALITY STEREO EQUIPMENT AT LOWEST PRICES.
- ♪ YOUR REQUEST FOR QUOTATION RETURNED SAME DAY.
- ♪ FACTORY SEALED CARTONS—GUARANTEED AND INSURED.
- ♪ SAVE ON NAME BRANDS LIKE:

PIONEER JVC
KENWOOD TEAC
MARANTZ SANSUI
TECHNICS SONY

AND MORE THAN 50 OTHERS
BUY THE MODERN WAY
BY MAIL—FROM



BANK CARDS ACCEPTED
12 East Delaware
Chicago, Illinois 60611
312-664-0020
800-621-8042

CIRCLE NO. 38 ON FREE INFORMATION CARD

This publication is indexed in

THE MAGAZINE INDEX

in COM
microform

... also available
online via
Lockheed's
Dialog Service

For information
write to



INFORMATION ACCESS
CORPORATION

404 Sixth Avenue
Menlo Park, Ca. 94025
(415) 367-7171
800-227-8431

computique computique computique



- 16K, 32K, 48K
- DOS 3.3
- APPLE PLOT
- APPLE PASCAL
- APPLE FORTRAN
- VISICALC
- APPLE WRITER
- GRAPHICS TABLET
- MODEM
- DOW JONES NEWS & QUOTES
- DECISION EVALUATOR
- CONTROLLER (Gen Ledger)
- EPSON
- ELECTRONICS
- DIME
- SILENTYPE
- ANADIX
- SANYO, BW, COLOR, GREENSCREEN
- EXTENDED WARRANTY
- Micro-Courier

AUTHORIZED DEALER AND SERVICE CENTER

Texas Instruments

TI-59 960 PROG	199.95		
PC-100C	169.95		
LCD-PROG NEW	59.95		
TI-3011 NEW	18.95		
TI-355P SCI	22.50		
TI-40 SCI NEW	28.95		
BUS ANAL I	19.95	SPEAK & SPELL READ	59.95
BUS ANAL II	44.95	SPEAK & MATH	59.95
BUS CARD	39.95	TOUCH & TELL NEW	54.95
MBA	54.95	TI-5100 DISPLAY	39.95
INVEST ANALYST	48.95	TI-5101 HAND/PRINT	49.95
TI-54 SCI NEW	39.95	TI-5120 PRINTER	59.95
TI-5511 NEW	44.95	TI-5130 PRINT/DISP	79.95
TI-57 PROG SCI	39.95	TI-5135 PRINT/DISP	79.95
TI-58C PROG CALC	89.95	TI-5142 PRINT/DISP	99.95



Your **hp** HEWLETT PACKARD Headquarters

THE HP-85!

Complete Enhancements,
Peripherals
and Accessories



HP-67	289.95	HP-33E SCI	73.95
HP-97	584.95	HP-37E BUS	59.95
HP-33C SCI	79.95	HP-38E	104.95
HP-34C SCI	114.95	HP-43, 41CV	CALL
HP-38C BUS/RE	119.95	HP-85	CALL
HP-32E SCI	49.95	HP-83	CALL



TOUCH THE FUTURE

ATARI 800 (16K) 789.95
VISICALC AVAILABLE CALL



CHESS CHALLENGER 7 89.95
SENSORY CHESS 129.95



5813 SCI PROGRAMMABLE 34.95
1182A PRINT/DISPLAY 74.95
TALKING CLOCK 79.95
EL-6200 DIG EXEC SEC 89.95



AA-81 DIG/ANALOG ALARM 69.95
VL-TONE MUSICAL INSTRUMENT/CALC 69.95
W100 DEPTH TESTED ALARM CHRONO 39.95
FX7100 SCI CHRONO ALARM CALC 49.95
FX3500 SCI PROGRAMMABLE CALC 39.95

(714) 549-7373
INFORMATION LINE

(800) 432-7068
TOLL FREE (Within CA)

(800) 854-0523
TOLL FREE (Outside CA)

WE WILL MEET OR BEAT ANY COMPETITOR'S ADVERTISED PRICE ON MOST ITEMS IF HE HAS THE MDSE. ON HAND. VISA, MASTERCARD, MONEY ORDER, PERS. CK. (14 WK. DAYS TO CLR.). COD ACCEPTED. MIN. \$4.95 SHIPPING U.S.A. AIR ON REOST. CAL. RES. ADD 6% SALES TX. ALL MDSE. SUBJ. TO AVAIL. PRICES SUBJ. TO CHANGE.

MAIL & PHONE
ORDERS ONLY

3211 SO. HARBOR BLVD.
SANTA ANA, CA 92704
NEWPORT
(714) 549-7373

WRITE
OR CALL
FOR
FREE
CATALOG



PASADENA MID-WILSHIRE
(213) 795-3007 (213) 385-7777
TARZANA LAWDALE
(213) 705-7507 (213) 370-5795
WEST LOS ANGELES BREA
(213) 820-0423 (714) 990-6600

PROFESSIONAL DISCOUNTS

CIRCLE NO. 17 ON FREE INFORMATION CARD

BACK ISSUES AVAILABLE...



If you've missed any of the previously published issues of Popular Electronics Magazine a wide selection is still available. Copies may be ordered for issues published during the past 12 months. In the event a particular issue ordered is out of print your payment will be returned promptly.

Order by mailing \$3.00 per copy (postage & handling included) to Popular Electronics, P.O. Box 278, Pratt Station, Brooklyn, N.Y.

(Outside U.S.A. copies are \$4.00 each.)

Please be sure to enclose payment and identify the specific issues you wish to receive.

DIGI-KEY CORPORATION

In Minn., Ark., Ill. Call 218-681-6474

Capacitors • Real-Time Clock/Calendar • E.F. Johnson • Terminal Strips • T.I. Connectors • Wire Wrapping Supplies • CMOS Rectifiers • Powerwacs • Sams Books • Diamond Tools • Pin/Vac
 AP Products • Batteries • ZNR's • Books • Zenier Diodes • Breadboarding Wire • Buzzers • Vices • Templates • Diodes • S-Types • Drafting Aids • Soldering Supplies • Edge Connectors • IC Socket
 Enclosures • Resistors • Networks • Hardware • Power Supplies • Baby Bins • Thermo-Flux • Jacks • Integrated Circuits • Optoelectronics • Lamps • Millimeter • Edge Connectors • Sockets
 Microprocessors • Smart Latches • Clocks • Logic • PC Layout Supplies • Lithium Batteries • Tantalum Capacitors • Time-Temperature Clock • AD • D/A • Nickel-Cadmium Batteries
 Electrolytic Capacitors • Potentiometers • Car Clocks • Transistors • Home Clock Kits • Tools • Fuse Holders • Boards • Ungar Products • Heat Sinks & Accessories • Solder Wick • AND MORE

INTEGRATED CIRCUITS

7400 TTL	74100 TTL	4000 CMOS	LINEAR
7400	74100	4000	7410
7401	74101	4001	7411
7402	74102	4002	7412
7500	74200	4100	7510

TIME-TEMPERATURE PROGRAMMABLE MODULE



MA1032 Clock
 Digital LCD Clock Module
 • Operates from a single 1.5V Battery
 • 0.1" LCD Display
 Instructions Included in All Orders
 MA1032A ICD Clock Module only \$24.95
 MA1032C Switch for MA1032A \$2.80
 MA1032H Switch for MA1032C, 5 & 8 Buttons \$2.25

RAMANOSK ELECTROLYTIC CAPACITORS

Value	WV	100	150	200	250	300	350	400
1000	100	1.0	1.5	2.0	2.5	3.0	3.5	4.0
1000	150	1.5	2.0	2.5	3.0	3.5	4.0	4.5
1000	200	2.0	2.5	3.0	3.5	4.0	4.5	5.0
1000	250	2.5	3.0	3.5	4.0	4.5	5.0	5.5
1000	300	3.0	3.5	4.0	4.5	5.0	5.5	6.0
1000	350	3.5	4.0	4.5	5.0	5.5	6.0	6.5
1000	400	4.0	4.5	5.0	5.5	6.0	6.5	7.0

NEW! KIT PANASONIC METALLIZED POLYESTER CAPACITORS

Value	WV	100	150	200	250	300	350	400
1000	100	1.0	1.5	2.0	2.5	3.0	3.5	4.0
1000	150	1.5	2.0	2.5	3.0	3.5	4.0	4.5
1000	200	2.0	2.5	3.0	3.5	4.0	4.5	5.0
1000	250	2.5	3.0	3.5	4.0	4.5	5.0	5.5
1000	300	3.0	3.5	4.0	4.5	5.0	5.5	6.0
1000	350	3.5	4.0	4.5	5.0	5.5	6.0	6.5
1000	400	4.0	4.5	5.0	5.5	6.0	6.5	7.0

THE "PROGRAMMABLE" CLOCK MODULES

MA1032 Clock
 Digital LCD Clock Module
 • Operates from a single 1.5V Battery
 • 0.1" LCD Display
 Instructions Included in All Orders
 MA1032A ICD Clock Module only \$24.95
 MA1032C Switch for MA1032A \$2.80
 MA1032H Switch for MA1032C, 5 & 8 Buttons \$2.25

DIGITAL CLOCK BEZEL

MA1032 Clock
 Digital LCD Clock Module
 • Operates from a single 1.5V Battery
 • 0.1" LCD Display
 Instructions Included in All Orders
 MA1032A ICD Clock Module only \$24.95
 MA1032C Switch for MA1032A \$2.80
 MA1032H Switch for MA1032C, 5 & 8 Buttons \$2.25

UNIVERSAL SIZE

MA1032 Clock
 Digital LCD Clock Module
 • Operates from a single 1.5V Battery
 • 0.1" LCD Display
 Instructions Included in All Orders
 MA1032A ICD Clock Module only \$24.95
 MA1032C Switch for MA1032A \$2.80
 MA1032H Switch for MA1032C, 5 & 8 Buttons \$2.25

GOLD PLATED WIRE WRAP

Part No.	Description	Price
MA1032	Digi-Key Programmable Module	1.00
MA1032A	Digi-Key Programmable Module (ICD)	1.00
MA1032C	Digi-Key Programmable Module (Switch)	1.00
MA1032H	Digi-Key Programmable Module (Switch)	1.00

DIGI-CLOCK Kit

MA1032 Clock
 Digital LCD Clock Module
 • Operates from a single 1.5V Battery
 • 0.1" LCD Display
 Instructions Included in All Orders
 MA1032A ICD Clock Module only \$24.95
 MA1032C Switch for MA1032A \$2.80
 MA1032H Switch for MA1032C, 5 & 8 Buttons \$2.25

PANASONIC DISC CAPACITORS

Value	WV	100	150	200	250	300	350	400
1000	100	1.0	1.5	2.0	2.5	3.0	3.5	4.0
1000	150	1.5	2.0	2.5	3.0	3.5	4.0	4.5
1000	200	2.0	2.5	3.0	3.5	4.0	4.5	5.0
1000	250	2.5	3.0	3.5	4.0	4.5	5.0	5.5
1000	300	3.0	3.5	4.0	4.5	5.0	5.5	6.0
1000	350	3.5	4.0	4.5	5.0	5.5	6.0	6.5
1000	400	4.0	4.5	5.0	5.5	6.0	6.5	7.0

SUPER-STRIPS

MA1032 Clock
 Digital LCD Clock Module
 • Operates from a single 1.5V Battery
 • 0.1" LCD Display
 Instructions Included in All Orders
 MA1032A ICD Clock Module only \$24.95
 MA1032C Switch for MA1032A \$2.80
 MA1032H Switch for MA1032C, 5 & 8 Buttons \$2.25

PANASONIC TSW Series

MA1032 Clock
 Digital LCD Clock Module
 • Operates from a single 1.5V Battery
 • 0.1" LCD Display
 Instructions Included in All Orders
 MA1032A ICD Clock Module only \$24.95
 MA1032C Switch for MA1032A \$2.80
 MA1032H Switch for MA1032C, 5 & 8 Buttons \$2.25

PANASONIC RESIN DUAL IN LINE CAPACITORS

Value	WV	100	150	200	250	300	350	400
1000	100	1.0	1.5	2.0	2.5	3.0	3.5	4.0
1000	150	1.5	2.0	2.5	3.0	3.5	4.0	4.5
1000	200	2.0	2.5	3.0	3.5	4.0	4.5	5.0
1000	250	2.5	3.0	3.5	4.0	4.5	5.0	5.5
1000	300	3.0	3.5	4.0	4.5	5.0	5.5	6.0
1000	350	3.5	4.0	4.5	5.0	5.5	6.0	6.5
1000	400	4.0	4.5	5.0	5.5	6.0	6.5	7.0

POWERACE

Part No.	Description	Price
MA1032	Digi-Key Programmable Module	1.00
MA1032A	Digi-Key Programmable Module (ICD)	1.00
MA1032C	Digi-Key Programmable Module (Switch)	1.00
MA1032H	Digi-Key Programmable Module (Switch)	1.00

PANASONIC K1-Series Capacitors

Value	WV	100	150	200	250	300	350	400
1000	100	1.0	1.5	2.0	2.5	3.0	3.5	4.0
1000	150	1.5	2.0	2.5	3.0	3.5	4.0	4.5
1000	200	2.0	2.5	3.0	3.5	4.0	4.5	5.0
1000	250	2.5	3.0	3.5	4.0	4.5	5.0	5.5
1000	300	3.0	3.5	4.0	4.5	5.0	5.5	6.0
1000	350	3.5	4.0	4.5	5.0	5.5	6.0	6.5
1000	400	4.0	4.5	5.0	5.5	6.0	6.5	7.0


NEW! KIT PANASONIC METALLIZED POLYESTER CAPACITORS

Value	WV	100	150	200	250	300	350	400
1000	100	1.0	1.5	2.0	2.5	3.0	3.5	4.0
1000	150	1.5	2.0	2.5	3.0	3.5	4.0	4.5
1000	200	2.0	2.5	3.0	3.5	4.0	4.5	5.0
1000	250	2.5	3.0	3.5	4.0	4.5	5.0	5.5
1000	300	3.0	3.5	4.0	4.5	5.0	5.5	6.0
1000	350	3.5	4.0	4.5	5.0	5.5	6.0	6.5
1000	400	4.0	4.5	5.0	5.5	6.0	6.5	7.0

1740

SN7400N .25	SN7472N .29	SN74156N .79
SN7401N .20	SN7473N .35	SN74157N .69
SN7402N .20	SN7474N .35	SN74160N .89
SN7403N .25	SN7475N .49	SN74161N .89
SN7404N .25	SN7476N .35	SN74162N .89
SN7405N .25	SN7477N 5.00	SN74163N .89
SN7406N .35	SN7480N .50	SN74164N .89
SN7407N .35	SN7482N .50	SN74165N .89
SN7408N .25	SN7483N .69	SN74166N .89
SN7409N .25	SN7485N .35	SN74167N 2.75
SN7410N .25	SN7486N .89	SN74170N 1.95
SN7411N .25	SN7489N 1.75	SN74172N 4.95
SN7412N .35	SN7490N .35	SN74173N 1.39
SN7413N .40	SN7491N .49	SN74174N .99
SN7414N .69	SN7492N .45	SN74175N .89
SN7416N .29	SN7493N .45	SN74176N .79
SN7417N .29	SN7494N .69	SN74177N 1.49
SN7420N .25	SN7495N .69	SN74179N .79
SN7421N .25	SN7496N .69	SN74180N .79
SN7422N .25	SN7497N 3.00	SN74181N 2.25
SN7423N .45	SN74100N 1.40	SN74182N .79
SN7424N .29	SN74108N .89	SN74184N 2.49
SN7425N .29	SN74109N .69	SN74185N 1.29
SN7426N .25	SN74107N .35	SN74190N .79
SN7428N .49	SN74109N .39	SN74191N 1.25
SN7430N .25	SN74116N 1.95	SN74192N .89
SN7432N .25	SN74121N .35	SN74193N .89
SN7433N .25	SN74122N .59	SN74194N .89
SN7438N .40	SN74123N .59	SN74195N .69
SN7439N .25	SN74125N .49	SN74196N .89
SN7440N .20	SN74126N .49	SN74197N .89
SN7441N .89	SN74127N .75	SN74198N 1.49
SN7442N .59	SN74128N .75	SN74199N 1.49
SN7443N 1.10	SN74141N .99	SN74221N .89
SN7444N 1.10	SN74142N 3.25	SN74251N .99
SN7445N .89	SN74143N 3.49	SN74276N 1.95
SN7446N .79	SN74144N 3.49	SN74279N .99
SN7447N .69	SN74145N 1.49	SN74283N 1.25
SN7448N .79	SN74147N 1.95	SN74284N 1.25
SN7450N .20	SN74148N 1.25	SN74285N 3.95
SN7451N .20	SN74150N 1.29	SN74355N .69
SN7452N .20	SN74151N .69	SN74366N .69
SN7454N .20	SN74152N .69	SN74367N .69
SN7459A .25	SN74153N .79	SN74368N .69
SN7460N .20	SN74154N 1.25	SN74390N 1.49
SN7470N .29	SN74155N .75	SN74393N 1.49

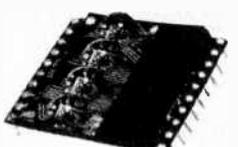
4-Digit 16 Segment Alphanumeric Intelligent Display with Memory, Recorder, Driver



End-stackable, 4-character package. High contrast, 100mi lum, magnified monolithic characters. 64-Character ASCII format. Built-in memory, decoder, multiplex end drivers. Direct access to each digit independently and asynchronously. Five volt logic, TTL compatible. Five volt power supply only. Independent control function. Size: 1" x 1-3/16" H x 225" D.

DL-1416 Alphanumeric Display \$19.95 ea.

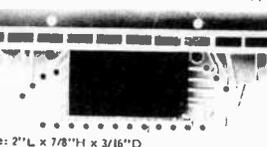10-Segment Bargraph Displays (with On-Board Driver IC-Chip)



Size: 2" L x 7/8" H x 3/16" D

Bar or dot display mode externally selectable by user. Packages are end-stackable for expanded displays. Can be cascaded to 10 arrays (100 bargraph elements). LED current programmable from 2mA to 30mA. Stable internal voltage reference for full scale analog inputs from 1.2 to 12V. Each LED output of driver IC with external access. Size: 2" x 7/8" x 3/16".

NSM3914 Linear Function (10 bars red) 48.95
NSM39146 Linear Function (10 bars green/4 red) 6.95
NSM39147 Logarithmic Function (10 bars red) 2.95
NSM3918 Logarithmic Function (8 pin, 2 yall./2 rd.) 5.95
NSM3918 VU-Meter Function (10 bars red) 5.95
NSM3918 VU-Meter Func. 16 pin./2 yall./2 rd.) 6.95

INTEGRIL

Part No.	Function	Price
7061PI	CMOS Precision Timer	14.95
7065EV/Kit*	3 1/2 Digit A/D (LCD Drive)	24.95
7066VPL	1/2 Digit A/D (LCD Drive)	16.95
7066EV/Kit*	IC, Circuit Board, Display	34.95
7107CPL	3 1/2 Digit A/D (LED Drive)	15.95
7107EV/Kit*	IC, Circuit Board, Display	29.95
7116CPL	3 1/2 Digit A/D LCD Dis. H.L.D.	11.95
7117CPL	3 1/2 Digit A/D LED Dis. H.L.D.	17.95
7201IDR	Low Battery Volt Indicator	2.25
7205IPD	CMOS LED Stopwatch/Timer	12.95
7205EV/Kit*	Stopwatch Chip, XTL	19.95
7206CJPE	Tone Generator	1.95
7206EV/Kit*	Tone Generator Chip, XTL	12.95
7207AIPD	Oscillator Controller	6.50
7207AIPD/Kit*	Freq. Counter Chip, XTL	13.95
7208PI	Seven Decade Counter	3.95
7209IPA	Clock Generator	17.95
7215IPD	4 Func. CMOS Stopwatch CKT	13.95
7215EV/Kit*	4 Func. Stopwatch Chip, XTL	19.95
7216A1J1	8-Digit Up/Down Counter C.A.	32.00
7216C1J1	8-Digit Freq. Counter C.A.	26.95
7216D1P1	8-Digit Freq. Counter C.C.	21.95
7217J1J1	4-Digit LED Up/Down Counter	12.95
7218C1J1	8-Digit Up/Down Counter	11.95
7225A1J1	LCD 4 1/2 Digit Up Counter DRI	10.25
7225A1J1/Kit*	4 1/2 Digit Up Counter DRI	31.95
7285A1J1/Kit*	5 Function Counter Chip, XTL	14.95
7286J1E	CMOS Bin Prog. Timer/Counter	4.95
7287J1E	CMOS Divide-by-256 RC Timer	2.05
7288C1J1	CMOS BCD Prog. Timer/Counter	6.00
7289C1J1	CMOS BCD Prog. Timer/Counter	6.00
7555PI	CMOS 555 Timer (4 pin)	1.45
7556IPD	CMOS 555 Timer (8 pin)	2.20
7611BCPA	CMOS Op Amp Comparator 5MV 2.25	
7612BCPA	CMOS Op Amp Ext. Cmvr. 5MV 2.95	
7613BCPA	CMOS Quad Op Amp Comp. 5MV 3.95	
7613CPE	CMOS Tri Op Amp Comp. 10MV 3.35	
7614ICPD	CMOS Quad Op Amp Comp. 10MV 7.50	
7622CCPD	CMOS Quad Op Amp Comp. 10MV 7.50	
7623CCPD	Voltage Detector	2.95
8038CCPD	Waveform Generator	2.95
8038CPE	Monolithic Logarithmic Amp	21.60
8211C1P	50ppm Acc. Comp. Volt Ref. Diode	2.50
8212C1P	Volt Ref/Indicator	2.95
8213C1P	Volt Ref/Indicator	2.95

74LS

74LS00 .29	74LS92 .75	74LS192 1.15
74LS01 .29	74LS93 .75	74LS193 1.15
74LS02 .35	74LS95 .99	74LS194 1.15
74LS03 .35	74LS96 .99	74LS197 1.19
74LS04 .35	74LS97 1.15	74LS221 1.49
74LS05 .35	74LS98 1.15	74LS222 1.49
74LS06 .35	74LS107 .45	74LS241 1.49
74LS09 .35	74LS108 .45	74LS242 1.49
74LS10 .35	74LS109 .45	74LS244 1.49
74LS12 .35	74LS112 .45	74LS245 1.49
74LS13 .35	74LS113 .45	74LS246 1.49
74LS14 .35	74LS114 .45	74LS248 1.95
74LS15 .35	74LS115 .45	74LS249 1.95
74LS16 .35	74LS116 .45	74LS250 1.95
74LS17 .35	74LS117 .45	74LS251 1.95
74LS18 .35	74LS118 .45	74LS252 1.95
74LS19 .35	74LS119 .45	74LS253 1.95
74LS20 .35	74LS120 .45	74LS254 1.95
74LS21 .35	74LS121 .45	74LS255 1.95
74LS22 .35	74LS122 .45	74LS256 1.95
74LS23 .35	74LS123 .45	74LS257 1.95
74LS24 .35	74LS124 .45	74LS258 1.95
74LS25 .35	74LS125 .45	74LS259 1.95
74LS26 .35	74LS126 .45	74LS260 1.95
74LS27 .35	74LS127 .45	74LS261 1.95
74LS28 .35	74LS128 .45	74LS262 1.95
74LS29 .35	74LS129 .45	74LS263 1.95
74LS30 .35	74LS130 .45	74LS264 1.95
74LS31 .35	74LS131 .45	74LS265 1.95
74LS32 .35	74LS132 .45	74LS266 1.95
74LS33 .35	74LS133 .45	74LS267 1.95
74LS34 .35	74LS134 .45	74LS268 1.95
74LS35 .35	74LS135 .45	74LS269 1.95
74LS36 .35	74LS136 .45	74LS270 1.95
74LS37 .35	74LS137 .45	74LS271 1.95
74LS38 .35	74LS138 .45	74LS272 1.95
74LS39 .35	74LS139 .45	74LS273 1.95
74LS40 .35	74LS140 .45	74LS274 1.95
74LS41 .35	74LS141 .45	74LS275 1.95
74LS42 .35	74LS142 .45	74LS276 1.95
74LS43 .35	74LS143 .45	74LS277 1.95
74LS44 .35	74LS144 .45	74LS278 1.95
74LS45 .35	74LS145 .45	74LS279 1.95
74LS46 .35	74LS146 .45	74LS280 1.95
74LS47 .35	74LS147 .45	74LS281 1.95
74LS48 .35	74LS148 .45	74LS282 1.95
74LS49 .35	74LS149 .45	74LS283 1.95
74LS50 .35	74LS150 .45	74LS284 1.95
74LS51 .35	74LS151 .45	74LS285 1.95
74LS52 .35	74LS152 .45	74LS286 1.95
74LS53 .35	74LS153 .45	74LS287 1.95
74LS54 .35	74LS154 .45	74LS288 1.95
74LS55 .35	74LS155 .45	74LS289 1.95
74LS56 .35	74LS156 .45	74LS290 1.95
74LS57 .35	74LS157 .45	74LS291 1.95
74LS58 .35	74LS158 .45	74LS292 1.95
74LS59 .35	74LS159 .45	74LS293 1.95
74LS60 .35	74LS160 .45	74LS294 1.95
74LS61 .35	74LS161 .45	74LS295 1.95
74LS62 .35	74LS162 .45	74LS296 1.95
74LS63 .35	74LS163 .45	74LS297 1.95
74LS64 .35	74LS164 .45	74LS298 1.95
74LS65 .35	74LS165 .45	74LS299 1.95
74LS66 .35	74LS166 .45	74LS300 1.95
74LS67 .35	74LS167 .45	74LS301 1.95
74LS68 .35	74LS168 .45	74LS302 1.95
74LS69 .35	74LS169 .45	74LS303 1.95

DISCRETE LEDs

XC556 R .200" red	5/31	MV50 .085" red	6/51
XC556G .200" green	4/51	XC209 R .125" red	5/51
XC556Y .200" yellow	4/51	XC209G .125" green	4/51
XC556C .200" clear	4/51	XC209Y .125" yellow	5/51
XC22R .200" red	5/51	XC526 R .185" red	5/51
XC22G .200" green	4/51	XC526G .185" green	5/51
XC22Y .200" yellow	4/51	XC526Y .185" yellow	4/51
MV10B .170" red	4/51	XC526C .185" clear	4/51

Diffused Bi-Color LED

Part No. 199 100+
XC5491 .79 .69

Size: 2.00"(T-t) Red/Green

XC5491 Bi-Color LED, XXTAL 1.8" H, 1.4" W, 1.4" D

RL-2 - \$.39 ea. or 3/51.00

C.A. - Common Anode D.D. - Double Digit

Type	Polarity	Ht	Price
MAN 1	C.A.-red	.270	2.95
MAN 2	5x7 D.M.-red	.300	4.95
MAN 3	C.C.-red	.125	.25
MAN 4	C.C.-green	.300	.99
MAN 5	C.C.-orange	.300	.75
MAN 6	C.C.-red	.300	.75
MAN 7	C.A.-red	.300	.75
MAN 8	C.C.-red	.300	1.25
MAN 9	C.C.-yellow	.300	.49
MAN 10	C.C.-orange	.300	.99
MAN 11	C.C.-orange	.300	.99
MAN 12	C.C.-orange	.300	.99
MAN 13	C.C.-orange	.300	.99
MAN 14	C.C.-orange	.300	.99
MAN 15	C.C.-orange	.300	.99
MAN 16	C.C.-orange	.300	.99
MAN 17	C.C.-orange	.300	.99
MAN 18	C.C.-orange	.300	.99
MAN 19	C.C.-orange	.300	.99
MAN 20	C.C.-orange	.300	.99
MAN 21	C.C.-orange	.300	.99
MAN 22	C.C.-orange	.300	.99
MAN 23	C.C.-orange	.300	.99
MAN 24	C.C.-orange	.300	.99
MAN 25	C.C.-orange	.300	.99
MAN 26	C.C.-orange	.300	.99
MAN 27	C.C.-orange	.300	.99
MAN 28	C.C.-orange	.300	.99
MAN 29	C.C.-orange	.300	.99
MAN 30	C.C.-orange	.300	.99

DISPLAY LEDS

Type	Polarity	Ht	Price
DLG507	C.A.-green	.500	1.25
DL704	C.C.-red	.300	1.25
DL707	C.A.-red	.300	1.25
DL728	C.C.-red	.500	1.49
DL741	C.A.-red	.600	1.25
DL747	C.A.-red	.600	1.49
DL750	C.A.-orange	.600	1.49
DL850	C.C.-orange	.800	1.49
DL338	C.C.-red	.110	.35
FND503	C.C. ± 1	.357	.99
FND507	C.A. (FND503)	.357	.75
FND507	C.A. (FND510)	.500	.99
HDSF3401	C.C.-red	.800	1.50
HDSF3402	C.C.-red ± 1	.800	1.50
HDSF3406	C.C.-red	.800	1.50
5082-7751	C.A., R.H.D.-red	.430	1.25
5082-7752	C.A., R.H.D.-red	.430	1.25
5082-7300	4x7 Numeric (RHD)	.600	22.00
5082-7302	4x7 Numeric (LHD)	.600	22.00
5082-7340	4x7 HxK1 (0-9/A-F)	.600	22.00
4128	Photo Xisistor Opto-Isol.	.69	
LN1-1	Photo Xisistor Opto-Isol.	.69	
MOC3010	Optically Isol. Triacs Driver	1.25	

SOCKETS

Test TEXTOL Sockets

• Nickel Boron Plating
• G.F. PSF Plastic Body
• For testing IC's

Part No.	Pins	Price	Part No.	Pins	Price
214-3339	14 pin	5.95	222-3423	22 pin	9.95
216-3340	16 pin	6.49	224-3346	24 pin	9.75
218-3341	18 pin	7.09	226-3348	26 pin	10.95
220-3342	20 pin	8.49	228-3346	40 pin	12.95

RECEPTACLES

Test TEXTOL Sockets

• Nickel Boron Plating
• G.F. PSF Plastic Body
• Wire Wrap Contacts

Part No.	Pins	Price	Part No.	Pins	Price
214-3592	14 pin	3.75	222-3596	22 pin	12.95
216-3593	16 pin	3.95	224-3597	24 pin	12.75
218-3594	18 pin	4.95	226-3598	26 pin	13.95
220-3595	20 pin	11.95	228-3599	40 pin	15.95

LOW PROFILE (TIN) SOCKETS

1-24	25-49	50-100	
8 pin LP	.17	.16	.15
14 pin LP	.20	.19	.18
16 pin LP	.22	.21	.20
18 pin LP	.29	.28	.27
20 pin LP	.34	.32	.31
22 pin LP	.37	.36	.35
24 pin LP	.38	.37	.36
26 pin LP	.45	.44	.43
36 pin LP	.60	.59	.58
40 pin LP	.63	.62	.61

SOLDERTAIL STANDARD (TIN)

1-24	25-49	50-100	
14 pin ST	.27	.25	.24
16 pin ST	.30	.27	.25
18 pin ST	.35	.32	.3



Clock Modules

12VDC
AUTOMOTIVE/
INSTRUMENT
CLOCK



- APPLICATIONS:
- In-dash auto/clocks
 - After-market auto/clocks
 - Avrc's marine clocks
 - 12VDC oper. instr.
 - Portable/battery powered instruments

Features: Bright 0.3" green display. Internal crystal time-base. ±0.5 sec./day accur. Auto. display brightness control logic. Display color filterable to blue, blue-green, green & yellow. Complete—just add switches and lens.

MA1003 Module (3.05" L x 1.75" H x .90" D) \$16.95

CLOCK MODULES

- MA1023 .7" Red Digital LED Clock Module 8.95
- MA1026 .7" Dig. LED Alarm Clock/Thermometer 18.95
- MA5036 .3" Red Digital LED Clock/Timer 6.95
- MA1002 .5" Red Digital LED Clock & Xformer 9.95
- MA1010 .8" Red Digital LED Clock 7.95
- MA1032 C&A .5" Red Digital LCD Clock 17.95
- MA1043 .3" Green Digital LED Clock 8.95

TRANSFORMERS

- 102-P20 Xformer for MA1023, 1043 & 5036 Mods. 3.49
- 102-P22 Xformer for MA1026 Clock Modules 3.49
- 102-P24 Xformer for MA1010 Clock Modules 3.49



8 OHM SPEAKER

2 1/4" - 8 Ohm - .25 watt
A0201
\$1.25 ea. 2/\$1.95 ea. 10/\$7.95 ea.

BATTERY HOLDER

- Holds 2 ea. C cells
- Aluminum Case
- 5" leads
- H-801-159 \$1.45 each
- 10/\$3.95



BATTERY HOLDER

- Holds 4 ea. C cells
- Plastic case
- 9" leads
- B2721 \$1.49 ea. 10/\$4.25

EPROM Erasing Lamp



- Erases 2708, 2716, 1702A, 5203Q, 5204Q, etc.
- Erases up to 4 chips within 20 minutes.
- Maintains constant exposure distance of one inch.
- Special conductive foam liner eliminates static build-up.
- Inbuilt safety lock to prevent UV exposure.
- Compact - only 7-5/8" x 2-7/8" x 2"
- Complete with holding tray for 4 chips.
- UVS-11E1 Replacement Bulb \$16.95
- UVS-11E \$79.95

JOYSTICKS



- JS-5K 5K Linear Taper Pots \$5.25
- JS-100K 100K Linear Taper Pots \$4.95
- JVC-40 40K (2) Video Controller in case \$4.95

6-Digit Clock Kit



- Bright .300 ht. comm. cathode display
- Uses MS5314 clock chip
- Switches for hours, minutes and hold mode
- Hrs. easily viewable to 20 ft.
- Simulated walnut case
- 115 VAC operation
- 12 or 24 hr. operation
- Incl. all components, case & wall transformer
- Size: 6 1/2" x 3 1/8" x 1 1/4"

JE701 \$19.95

NEW! JE215 Adjustable Dual Power Supply

General Description: The JE215 is a Dual Power Supply with independent adjustable positive and negative output voltages. A separate adjustment for each of the supplies provides the user unlimited applications for IC current voltage requirements. The supply can also be used as a general all-purpose variable power supply.

- FEATURES:
- Adjustable regulated power supplies.
 - Pos. and neg. 1.2VDC to 15VDC.
 - Power Output (each supply): 5VDC @ 500mA, 10VDC @ 750mA, 12VDC @ 500mA, and 15VDC @ 175mA.
 - Two 3-terminal adj. IC regulators with thermal overload protection.
 - Heat sink regulator cooling
 - LED "on" indicator
 - Printed Board Construction
 - 120VAC input
 - Size: 3-1/2" w x 5-1/16" L x 2" H

JE215 Adj. Dual Power Supply Kit (as shown) \$24.95

- JE200 Reg. Power Supply Kit (5VDC, 1 amp) \$14.95
- JE205 Adapter Brd. (for JE200) 5, 9 & 12V. \$12.95
- JE210 Var. Pwr. Sply. Kit, 5-15VDC, to 1.5amp. \$19.95

MICROPROCESSOR COMPONENTS

8080A/8080A SUPPORT DEVICES

- INS5800A CPU 4.95
- 8-Bit Input/Output 3.25
- DP214 Priority Interrupt Control 3.95
- DP216 Bi-Directional Bus Driver 3.49
- DP224 Clock Generator/Driver 3.25
- DP226 Bus Driver 3.49
- DP228 System Controller/Bus Driver 4.95
- DP232 System Controller 5.75
- INS5803 I/O Expander for 8 Series 9.95
- INS5820 Asynchronous Comm. Element 16.95
- DP251 Prog. Comm. I/O (USART) 7.95
- DP253 Prog. Interval Timer 14.95
- DP254 Prog. Peripheral I/O (PPI) 12.95
- DP257 Prog. DMA Control 19.95
- DP259 Prog. Interrupt Control 16.95
- DP272 Prog. CRT Interface 20.95
- DP279 Prog. Keyboard/Display Interface 19.95
- DP303 System Timing Element 6.95
- DP304 8-Bit Bi-Directional Receiver 3.95
- DP305 8-Bit Bi-Directional Receiver 3.95
- DP308 8-Bit Bi-Directional Receiver 3.95
- DP310 Octal Latched Peripheral Driver 5.75
- DP311 Octal Latched Peripheral Driver 5.75

8080/8080 SUPPORT DEVICES

- MC6800 MPU 14.95
- MC6800C MPU with Clock and RAM 14.95
- MC6800A 128-Static RAM 4.95
- MC6801 Peripheral Interf. Adapt. (MC6800) 14.95
- MC6802 Priority Interrupt Controller 14.95
- MC6803 1024-Static ROM (MC6800) 4.95
- MC6804 Asynchronous Comm. Adapter 8.95
- MC6805 Synchronous Serial Data Adapter 8.95
- MC6806 8400bps Digital MODEM 16.95
- MC6807 2400bps Modulator 12.95
- MC6808A Quad-Static Bus Trans. (MC6800) 7.95

MICROPROCESSOR CHIPS

- Z80 (80C1) CPU (1Mx800) 11.95
- Z80A (780-1) CPU (1Mx800-4) (4Mx12) 15.95
- CDP1802 CPU 19.95
- 3801 MPU 11.95
- 1024Q01 ADC CPU: 8-Bit Slice (Com. Temp. Grade) 19.95
- MC5800 MPU w/Clock (8M Bytes Memory) 11.95
- INS5803N-4 CPU: 8-Bit (8MHz) 9.95
- INS5803N-4 CPU: 501 Chip 8-Bit (128 Bytes RAM) 10.95
- INS5804N-4 CPU (256 Bytes RAM) 26.95
- INS5807N CPU: 64 Bytes RAM 26.95
- INS5807N CPU w/Basic Micro Interpreter 29.95
- PR820 CPU 19.95
- TM58900L MPU-16-Bit 49.95

SHIFT REGISTERS

- MM5900H Dual 20-Bit Dynamic 5.00
- MM5900L Dual 20-Bit Static 5.00
- MM5901H Dual 100-Bit Static 5.00
- MM5901L Dual 100-Bit Static 5.00
- MM5902H Dual 64-Bit Accumulator 5.00
- MM5902L Dual 64-Bit Accumulator 5.00
- MM5903H 1024-Bit Dynamic/Accumulator 1.95
- MM5903L 500/512-Bit Dynamic 1.95
- MM5904H Octal 80-Bit 1.95
- MM5904L Octal 80-Bit 1.95
- 250V (100A) 108-Bit Dynamic 3.95
- 251N Hex 42-Bit Static 2.95
- 252V Dual 128-Bit Static 3.95
- 253V 512-Bit Dynamic 2.95
- 254V 512-Bit Dynamic 2.95
- 255V Dual 256-Bit Static 3.95
- 256V Dual 256-Bit Static 3.95
- 382N Quad 80-Bit Static 1.95
- 381PC Fifo (Dual 8) 2.95

DATA ACQUISITION

- AF120-ICN Linear Active Filter 2.95
- AF121-ICJ Touch Tone Low Band Filter 19.95
- AF122-ICJ Touch Tone High Band Filter 19.95
- LW100AH Super Gain Op Amp 1.15
- LM131Z Constant Current Source 1.30
- LM131Z Temperature Transducer 1.40
- LF136N JFET Input Op Amp 1.10
- LF136N Single & Hold Amplifier 1.30
- LM399H Temp. Comp. Prec. Ref. (50ppm/°C) 4.95
- ADC0808LCN 8-Bit A/D Converter (1 LSB) 4.95
- ADC0808LCN 8-Bit D/A Converter (0.78% Lin.) 7.25

DATA ACQUISITION (CONTINUED)

- ALC0808LCN 8-Bit A/D Converter (0.5% Multi) 5.25
- ALC0808LCN 8-Bit A/D Converter (16-Ch. Multi) 10.95
- ADC0808LCN 8-Bit D/A Converter (0.20% Lin.) 8.95
- DAE0808LCN 8-Bit D/A Conv. Micro. Comp. (0.20% Lin.) 8.95
- ADC0808LCN 8-Bit D/A Converter (0.20% Lin.) 8.95

RAM'S

- 1101 256-K Static 3.49
- 1102 512-K Dynamic 16.95
- 1103 1024-K Static 3.49
- 1104 2048-K Static 16.95
- 2101 1024-K Static 3.49
- 2102 2048-K Static 16.95
- 2111 (811) 256-K Static MDS 4.95
- 2112 256-K Static MDS 4.95
- 2114 1024-K Static 950u 3.25
- 2114L 1024-K Static 950u Low Power 3.25
- 2114L 1024-K Static 950u 3.25
- 2114L-7 1024-K Static 950u Low Power 4.95
- 45200 512-K Static 16.95
- 45200 (1111) 512-K Static 200u (M26200N-4) 6.75
- 454 64-K Dynamic 200u 19.95
- 454 (M26200) 64-K Dynamic 200u 19.95
- MM5262 1024-K Dynamic (Fully Decoded) .99
- MM5262 2Kx5 Dynamic 2.95
- MM5262 (2507) 4096-K Dynamic 11.95
- MM5262 (4116) 16Kx1 Dynamic (100ns) (UP148C) 3.49
- MM5262 (2507) 4Kx1 Dynamic (100ns) (UP148C) 3.49
- 2525 64-Bit RAM 16-bit 3.49
- UPD4194 (M402) 4Kx1 Dynamic 16-bit 4.95
- 4Kx1 EPROM 454 4.95
- TMS4005 1024-K Static 9.95

PROMS/EPROMS

- 1102A 2K UV Erasable PROM 6.95
- 8K EPROM 11.95
- 25716 16K EPROM (+5V, -12V) 19.95
- 2716 (1625) 16K 16-Bit EPROM (Single +5V) 8.95
- 2732 (Intel) 32K EPROM 11.95
- 2758 64K EPROM (450ns) (Single +5V) 7.49
- 2764Q 64K EPROM 99.95
- 2764 2048 EPROM 14.95
- 8253 (14538) 32-Kbit PROM (Open Collector) 3.49
- 82515 4096-Bit PROM 14.95
- 82512 (14528) 32-Kbit Tri-State Bipolar PROM 3.49
- 82512 (14528) 4K Dynamic 16-bit 19.95

Over 30 More PROMS Listed in Our Catalog

ROM'S

- 3811 (240) Checker Generator (Upper Case) 9.95
- 3811 (240) Checker Generator (Lower Case) 9.95

NMOS READ ONLY MEMORIES

- MC68678P 128x512 ASCII Shifted w/Greek 12.50
- MC68678P 128x512 ASCII Symbol & Pictures 12.50
- MC68678P 128x512 ASCII Control Char. Gen. 6.95

MICROPROCESSOR MANUALS

- M-280 User Manual 7.50
- M-CDP1802 User Manual 7.50
- M-3500 User Manual 7.50

SPECIAL FUNCTION

- DS8005CN Dual MOS Clock Driver (DMZ) 3.50
- DS8005CN Dual MOS Clock Driver (DMZ) 3.50
- INS1771N-1 Fuzzy Dice Controller 24.95
- INS3601N Communication Chip 6.95
- MM590167N Microprocessor Real Time Clock 6.95
- MM590167N Microprocessor Compatible Clock 11.95
- COM925N 30-50pVAC Fluid Driver (800ns) 3.25
- COM925N Microcontroller with 64-Digit RAM & Direct LED Drive w/Bus Int. 7.49
- COM9N 30-50pVAC Fluid Driver (800ns) 3.25

TELEPHONE/KEYBOARD CHIPS

- AY-54100 Push Button Telephone Dialer 14.95
- AY-54000 Rotary Dialer 14.95
- AY-54000 CMOS Clock Generator 4.50
- AY-54236 Keyboard Encoder (88 keys) 11.95
- HD0805-5 Keyboard Encoder (16 keys) 7.95
- 74C92Z Keyboard Encoder (16 keys) 5.49
- 74C92Z Keyboard Encoder (20 keys) 5.49
- MS51390N Push Button Pulse Dialer 7.95
- MS54099N 16/16-Key Serial Keyboard Encoder 6.95

ELECTRONIC TOY MOTORS

Typical Power Source	Operating Range	TYPICAL CHARACTERISTICS									
		NO LOAD		AT MAXIMUM EFFICIENCY				SMALL TORQUE			
Voltage	Current	RPM	AMP	RPM	AMP	OZ IN	W	%	OZ IN	OZ IN	
DRY CELL	1.5-6.0	3.0	0.20	6-750	0.00	0.260	1.30	57.0	0.97		

.937 O.D. X 1.201 Length MABUCHI RE280 \$.99 each . . . 10/\$7.50 . . . 100/\$50.00

GLOBAL SPECIALTIES


Quick Test Sockets & Bus Strips

EXPERIMENTOR SOCKETS

Model	Length	Width	Center Channel	5 Pin Point Terminals	Bus Strips	Price
EXP48	6.0"	1.0"	n/a	n/a	(4160)	\$ 4.75
EXP300	6.0"	2.1"	3"	94(470)	(280)	\$12.00
EXP325	1.8"	2.1"	3"	22(110)	(210)	\$ 3.50
EXP350	3.6"	2.1"	3"	46(230)	(240)	\$ 6.75
EXP600	6.0"	2.4"	6"	94(470)	(280)	\$14.75
EXP650	3.6"	2.4"	6"	46(230)	(240)	\$ 8.75

\$10.00 Min. Order - U.S. Funds Only. Call. Residents Add 6% Sales Tax. Postage - Add 5% plus \$1 Insurance.

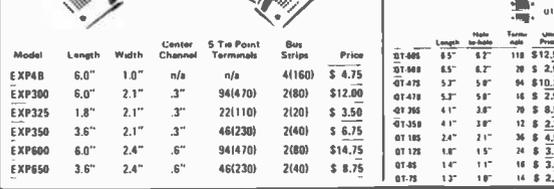Spec Sheets - 25¢. Send 86¢ Postage for your FREE 1982 JAMECO CATALOG.



NEW 1982 CATALOG

Jameco ELECTRONICS

PHONE ORDERS WELCOME (415) 592-8097

MAIL ORDER ELECTRONICS - WORLDWIDE
1355 SHOREWAY ROAD, BELMONT, CA 94002
PRICES SUBJECT TO CHANGE

POWER CORD SALE


Part No.	Input	Output	Price
AC 250	117V/60Hz	12 VAC 250mA	\$3.95
AC 500	117V/60Hz	12 VAC 500mA	\$4.95
AC1000	117V/60Hz	12 VAC 1 amp	\$5.95
AC1700	117V/60Hz	9 VAC 1.7 amp	\$3.95
DC 9200	117V/60Hz	9 VDC 200mA	\$3.25
DC 9000	120V/60Hz	9 VDC 500mA	\$3.95

AC and DC Wall Transformers



Ideal for use with clock, gen. power supplies, any other type of AC or DC application.

CONNECTORS

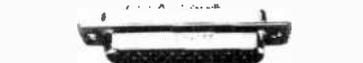

- DB25P D-Subminiature Plug \$2.95
- DB25S D-Subminiature Socket \$3.50
- D20418-2 Screw Lock Hdwr. (2) DB25S/P . . . \$.49
- DB51226 Cover for DB25S/P \$1.75
- Z2144SE P.C. Edge (22/44 Pin) \$2.95
- UG88/U BNC Plug \$1.79
- UG89/U BNC Jack \$3.79
- UG175/U UHF Adapter \$.49
- SO239 UHF Panel Recp. \$1.29
- PL258 UHF Adapter \$1.60
- PL259 UHF Plug \$1.60
- UG260/U BNC Plug \$1.79
- UG1094/U BNC Bulkhead Recp. \$1.29

TRS-80 16K Conversion Kit

Expand your 4K TRS-80 System to 16K. Kit comes complete with: 8 ea. MM5290 (UPD416/4116) 16K Dyn. Rams (*NS) * Documentation for Conversion

TRS-16K2 *150NS \$29.95

TRS-16K4 *250NS \$24.95

JE610 ASCII Encoded Keyboard Kit



The JE610 ASCII Keyboard Kit can be interfaced into any computer system. The kit comes complete with an industrial grade keyboard switch assembly (82-keys), IC's, sockets, connector, electronic components and a double-sided printed wiring board. The keyboard assembly requires +5V @ 150mA and -12V @ 10 mA for operation. Features: 60 keys generate the 126 characters, upper and lower case ASCII set. Fully buffered. Two user-definable keys provided for custom applications. Caps lock for upper-case-only alpha characters. Utilizes a 2376 (40-pin) encoder read-only memory chip. Outputs directly compatible with TTL/DTL or MOS logic arrays. Easy interfacing with a 16-pin dip or 18-pin edge connector. Size: 3 1/2" H x 14 1/2" W x 8 3/4" D

JE610/DTE-AK (After assembled as pictured above) \$124.95

JE610 Kit 82-Key Keyboard, PC Board, & Components (In case) \$ 79.95

K62 82-Key Keyboard (Keyboard only) \$ 34.95

DTE-AK (case only - 3 1/2" H x 14 1/2" W x 8 3/4" D) \$ 49.95

JE212 - Negative 12VDC Adapter Board Kit for JE610 ASCII KEYBOARD KIT (After assembled as pictured above) \$ 99.95

JE600 Hexadecimal Encoder Kit



The JE600 Encoder Keyboard Kit provides two separate hexadecimal digits produced from sequential key entries to allow direct programming for 8-bit microprocessor or 8-bit memory circuits. Three additional keys are provided for user operation without having a bistable output available. The outputs are latched and monitored with 9 LED readouts. Also included is a key entry strobe. Features: Full 8-bit latched output for microprocessor use. Three user-definable keys with one being bistable operation. Debounce circuit provided for all 19 keys. 9 LED readouts to verify entries. Easy interfacing with standard 16-pin IC connector. Only +5VDC required for operation. Size: 3 1/2" H x 8 3/4" W x 8 3/4" D

JE600/DTE-HK (After assembled as pictured above) \$99.95

9-Key Hexadec. Keyboard, PC Board & Cmpnts. (no case) \$59.95

K19 19-Key Keyboard (Keyboard only) \$14.95

DTE-HK (case only - 3 1/2" H x 8 3/4" W x 8 3/4" D) \$44.95

16K Memory 8/\$16.95

4116 300ns

ALL MERCHANDISE 100% GUARANTEED

CALL US FOR VOLUME QUOTES

LS SERIES

74LS00	.25	74LS163	.95
74LS01	.25	74LS164	.95
74LS02	.25	74LS165	.95
74LS03	.25	74LS166	2.40
74LS04	.25	74LS168	1.75
74LS05	.25	74LS169	1.75
74LS08	.25	74LS170	1.75
74LS09	.25	74LS173	.80
74LS10	.25	74LS174	.95
74LS11	.35	74LS175	.95
74LS12	.35	74LS181	2.15
74LS13	.45	74LS189	9.95
74LS14	1.00	74LS190	1.00
74LS15	.35	74LS191	1.00
74LS20	.25	74LS192	.85
74LS21	.35	74LS193	.95
74LS22	.25	74LS194	1.00
74LS26	.35	74LS195	.95
74LS27	.35	74LS196	.85
74LS28	.35	74LS197	.85
74LS30	.25	74LS221	1.20
74LS32	.35	74LS240	1.85
74LS33	.55	74LS241	1.85
74LS37	.55	74LS242	1.85
74LS38	.35	74LS243	1.85
74LS40	.25	74LS244	1.75
74LS42	.55	74LS245	2.85
74LS47	.75	74LS247	.76
74LS48	.75	74LS248	1.25
74LS49	.75	74LS249	.99
74LS51	.25	74LS251	1.30
74LS54	.35	74LS253	.85
74LS55	.35	74LS257	.85
74LS63	1.25	74LS268	.85
74LS73	.45	74LS259	2.85
74LS74	.45	74LS260	.65
74LS75	.50	74LS266	.55
74LS76	.40	74LS273	1.65
74LS78	.50	74LS275	3.35
74LS83	.75	74LS279	.55
74LS85	1.15	74LS280	1.98
74LS86	.40	74LS283	1.00
74LS90	.65	74LS290	1.25
74LS91	.89	74LS293	1.85
74LS92	.70	74LS295	1.05
74LS93	.65	74LS298	1.20
74LS95	.85	74LS352	1.55
74LS96	.95	74LS353	1.55
74LS107	.40	74LS363	1.35
74LS109	.40	74LS365	.95
74LS112	.45	74LS366	.95
74LS113	.45	74LS367	.70
74LS114	.50	74LS368	.70
74LS122	.45	74LS373	1.85
74LS123	.95	74LS374	1.80
74LS124	2.99	74LS377	1.45
74LS125	.95	74LS378	1.18
74LS126	.85	74LS379	1.35
74LS132	.75	74LS385	1.90
74LS136	.55	74LS386	.65
74LS137	.99	74LS390	1.90
74LS138	.75	74LS393	1.90
74LS139	.75	74LS395	1.65
74LS145	1.20	74LS399	1.70
74LS147	2.49	74LS447	.37
74LS148	1.35	74LS490	1.95
74LS151	.75	74LS668	1.69
74LS153	.75	74LS669	1.89
74LS154	2.35	74LS670	2.20
74LS155	1.15	74LS674	9.65
74LS158	.95	74LS682	3.20
74LS157	.75	74LS683	2.40
74LS158	.75	74LS684	2.40
74LS160	.90	74LS685	2.40
74LS161	.95	74LS688	2.40
74LS162	.95	74LS689	2.40

7400 SERIES

7400	.19	74128	.55
7401	.19	74132	.45
7402	.19	74136	.50
7403	.19	74141	.65
7404	.19	74142	2.95
7405	.22	74143	2.95
7406	.22	74144	2.95
7407	.22	74145	.60
7408	.24	74147	1.75
7409	.19	74148	1.20
7410	.19	74150	1.35
7411	.25	74151	.65
7412	.30	74152	.65
7413	.30	74153	.55
7414	.35	74154	1.40
7416	.25	74155	.75
7417	.25	74156	.65
7420	.19	74157	.55
7421	.35	74159	1.65
7422	.29	74160	.85
7423	.29	74161	.70
7425	.29	74162	.85
7426	.29	74163	.85
7427	.29	74164	.85
7428	.45	74165	.85
7430	.19	74166	1.00
7432	.29	74167	1.95
7433	.45	74170	1.65
7437	.29	74172	5.95
7438	.29	74173	.75
7440	.19	74174	.89
7442	.49	74175	.89
7443	.65	74176	.89
7444	.69	74177	.75
7445	.69	74178	1.15
7446	.59	74179	1.75
7447	.69	74180	.75
7448	.69	74181	2.25
7450	.19	74182	.75
7451	.23	74184	2.00
7453	.23	74185	2.00
7454	.23	74186	18.50
7460	.23	74190	.90
7464	.39	74191	1.15
7465	.39	74192	.79
7470	.35	74193	.79
7472	.29	74194	.85
7473	.34	74195	.85
7474	.35	74196	.79
7475	.49	74197	.75
7476	.35	74198	1.35
7480	.59	74199	1.35
7481	1.10	74221	1.35
7482	.95	74246	1.35
7483	.50	74247	1.25
7484	.50	74248	1.85
7485	.65	74249	1.95
7486	.35	74251	.75
7489	4.95	74259	2.25
7490	.35	74265	1.35
7491	.40	74273	1.95
7492	.50	74276	1.25
7493	.49	74279	.75
7494	.55	74283	2.00
7495	.65	74284	3.75
7496	.70	74285	3.75
7497	2.75	74290	.95
74100	1.00	74293	.75
74107	.30	74298	.85
74109	.45	74351	2.25
74110	.45	74365	.65
74111	.55	74366	.65
74116	1.55	74367	.65
74120	1.20	74368	.65
74121	.29	74376	2.20
74122	.45	74390	1.75
74123	.55	74393	1.35
74125	.45	74425	3.15
74126	.45	74426	.85
		74490	2.55

T.V. CIRCUITS

MC1330	1.89
MC1350	1.29
MC1358	1.79
LM380	1.29
LM386	1.50
LM565	.99
LM741	.29
LM1310	2.90
LM1800	2.99
LM1889	2.49

MISC.

8T26	1.69	3242	9.95
8T28	2.49	AY5-1013	3.95
8T95	.99	TR1602	4.95
8T96	.99	IM6-02	7.95
8T97	.99	1771	24.95
8T98	.99	1791	36.95
1488	.99	UPD765	39.95
1489	.99	8272	39.95
DM8131	2.95	1793	49.95

CMOS

74C00	.35	74C373	2.75	4018	.95	4093	.95
74C02	.35	74C374	2.75	4019	.45	4099	1.95
74C04	.35	74C901	.80	4020	.95	14409	8.95
74C08	.35	74C902	.85	4021	1.15	14411	8.95
74C10	.35	74C903	.85	4022	.35	14412	12.95
74C14	1.50	74C905	10.95	4023	.75	14419	2.95
74C20	.35	74C906	.95	4024	.35	4502	.95
74C30	.35	74C907	1.00	4025	.65	4503	.65
74C32	.50	74C908	2.00	4026	.65	4508	1.95
74C42	1.75	74C909	2.75	4027	.80	4510	.95
74C48	2.10	74C910	9.95	4028	.95	4511	.95
74C73	.65	74C911	10.00	4029	.45	4512	.95
74C74	.85	74C912	10.00	4030	.95	4514	1.25
74C83	.80	74C914	1.95	4034	.85	4515	2.25
74C85	1.95	74C915	2.00	4035	.95	4516	1.55
74C86	.95	74C918	2.75	4040	1.25	4518	1.25
74C88	.95	74C920	17.95	4041	.75	4519	1.25
74C89	4.50	74C921	15.95	4042	.85	4520	1.25
74C90	1.75	74C922	5.95	4043	.85	4522	1.25
74C93	1.75	74C923	5.95	4044	.85	4526	1.25
74C95	1.75	74C925	6.75	4046	.95	4527	1.95
74C107	1.00	74C926	7.95	4047	.55	4528	1.25
74C150	.75	74C927	7.95	4049	.55	4531	.95
74C151	.25	74C928	7.95	4050	.55	4531	.95
74C154	.25	74C929	19.95	4051	.95	4532	1.95
74C157	1.75	74C930	19.95	4053	.95	4538	1.95
74C160	2.00	4000	.35	4060	1.45	4539	1.95
74C161	2.00	4001	.35	4066	.75	4543	2.70
74C162	2.00	4002	.25	4068	.40	4555	.95
74C163	2.00	4006	.95	4069	.35	4556	.95
74C164	2.00	4007	.29	4070	.35	4581	1.95
74C165	2.00	4008	.95	4071	.30	4582	1.95
74C173	2.00	4009	.45	4072	.30	4584	.95
74C174	2.25	4010	.45	4073	.30	4585	.95
74C175	2.25	4011	.35	4075	.30	4702	12.95
74C192	2.25	4012	.25	4076	.95	4724	1.50
74C193	2.25	4013	.45	4078	.30	80C07	.95
74C195	2.25	4014	.95	4081	.30	80C95	.85
74C200	2.25	4015	.95	4082	.30	80C96	.95
74C221	2.25	4016	.45	4085	.95	80C97	.95
		4017	1.15	4086	.95	80C98	1.20

DIP SWITCHES

4 position	.85
5 position	.90
6 position	.90
7 position	.95
8 position	.95

TRANSISTORS

PN2222	10/1.00	100/8.99
2N3904	10/1.00	100/8.99
2N3906	10/1.00	100/8.99
2N3055	.79	10/6.99
IN4148		25/1.00
IN4004		10/1.00

CONNECTORS

RS232 MALE	3.25
RS232 FEMALE	3.75
RS232 HOOD	1.25
S-100 ST	3.95
S-100 WW	4.95

LINEAR

LM301V	.34	LM741V	.29
LM308V	.98	LM747	.79
LM309K	1.49	LM748V	.59
LM311	.64	LM1310	2.90
LM317T	1.95	MC1330	1.89
LM317K	3.95	MC1350	1.29
LM318	1.49	MC1358	1.79
LM323K	4.95	LM1414	1.59
LM324	.59	LM1458V	.69
LM337K	3.95	LM1488	1.39
LM339	.99	LM1489	1.39
LM377	2.29	LM1800	2.99
LM380	1.29	LM1889	2.49
LM386V	1.50	LM3900	.98
LM555V	.39	LM3909V	.98
LM556	.69	LM3914	3.95
LM565	.99	LM3915	3.95
LM566V	1.49	LM3916	3.95
LM567V	1.29	75451V	.39
LM723	.49	75452V	.39
LM733	.98	75453V	.39

74S00 SERIES

74S00	.44	74S74
-------	-----	-------

4K STATIC RAMS 8/18.95

2114 LOW POWER 450ns

ALL MERCHANDISE 100% GUARANTEED

CALL US FOR VOLUME QUOTES

8200

8202	45.00
8205	3.50
8212	1.95
8214	3.90
8216	1.85
8224	2.50
8226	1.85
8228	4.95
8237	19.95
8238	4.95
8243	4.50
8250	14.95
8251	5.50
8253	9.85
8253-5	9.85
8255	5.25
8255-5	5.25
8257	9.00
8259	7.00
8272	39.95
8275	29.95
8279	10.50
8279-5	10.50
8282	6.65
8283	6.65
8284	5.80
8286	6.65
8287	6.65
8288	25.00
8289	49.95

6800

6800	6.95
6802	11.95
6809	37.95
6810	4.60
6820	4.95
6821	4.95
6828	9.95
6834	16.95
6840	14.95
6843	42.95
6844	44.95
6845	29.95
6847	15.95
6850	4.75
6852	5.75
6860	10.95
6862	11.95
6871	25.95
6875	6.95
6880	2.95

Z80

Z80	8.95
Z80A	9.95
Z80B	19.95
Z80-PIG	6.50
Z80A-P O	8.60
Z80-CTC	6.50
Z80A-CTC	8.65
Z80-DART	15.25
Z80A-DART	18.75
Z80-DVA	17.50
Z80-DMA	27.50
Z80-SIG/0	23.95
Z80A-S O/0	28.95
Z80-SIG/1	23.95
Z80A-S O/1	28.95
Z80-SIG/2	23.95
Z80A-S O/2	28.95
Z80-SIG/9	17.95
Z80A-S O/9	22.95

SEPTEMBER SPECIALS

4116	150ns	NEC	8 for 19.95
4116	200ns		8 for 17.50

2708		2.99	8 for 2.75ea
2716	Intel and NEC	5.95	8 for 5.50ea
2732	Intel	16.50	8 for 15.95ea
2532	Ti and Hitachi		19.95ea

MPU'S

8035	16.95
8039	19.95
8080A	3.95
8085	12.95
8086	99.95
8088	39.95
8155	11.95
8156	11.95
8185	29.95
8185-2	39.95
8741	39.95
8748	69.95
8755	49.95

6502

6502	6.95
6502A	12.95
6504	6.95
6505	8.95
6520	4.95
6522	9.95
6532	14.95
6551	14.95

IC SOCKETS

1-100 100pcs	
8 pin ST	.13 .11
14 pin ST	.15 .12
16 pin ST	.17 .13
18 pin ST	.20 .18
20 pin ST	.29 .27
22 pin ST	.30 .27
24 pin ST	.30 .27
28 pin ST	.40 .32
40 pin ST	.49 .39

ST = SOLDER TAIL

8 pin WW	.59 .49
14 pin WW	.69 .52
16 pin WW	.69 .58
18 pin WW	.99 .90
20 pin WW	1.09 .98
22 pin WW	1.39 1.28
24 pin WW	1.49 1.35
28 pin WW	1.69 1.49
40 pin WW	1.99 1.80

WW = WIREWRAP

LEDS

Jumbo Red	10/1.00
Jumbo Green	6/1.00
Jumbo Yellow	6/1.00
5082-7760 43°C	.79
MAN74 3°C	.99
MAN72 3°C	.99

DYNAMIC RAMS

4027	(250ns)	2.50	2.00
4116-150	(150ns)	8/21.95	2.65
4116-200	(200ns)	8/19.95	2.35
4116-300	(300ns)	8/16.95	2.00
4164	(200ns)	CALL	CALL

STATIC RAMS

2101	(450ns)	1.95	1.85
2102-1	(450ns)	.89	.85
21L02-1	(LP) (450ns)	1.29	1.15
2111	(450ns)	2.99	2.49
2112	(450ns)	2.99	2.79
2114	(450ns)	8/18.95	2.25
2114L-2	(LP) (200ns)	8/22.95	2.45
2114L-3	(300ns)	8/21.95	2.45
2114L-4	(LP) (450ns)	8/18.95	2.25
4044-4	(450ns)	3.49	3.25
4044-3	(300ns)	3.99	3.75
TMM2016	(200ns)	CALL	CALL
MB6116	(200ns)	CALL	CALL

LP = LOW POWER

LS SPECIALS

LS240	.99	LS245	1.90
LS241	.99	LS373	.99
LS244	.99	SL374	1.75

(Sale Ends September 30, 1981)

EPROMS

1702	256 x 8 (1us)	4.95	4.50
2708	1024 x 8 (450ns)	3.95	3.50
2716	(5v) 2048 x 8 (450ns)	6.95	5.95
2758	(5v) 1024 x 8 (450ns)	9.95	8.95
2716-1	(5v) 2048 x 8 (350ns)	12.95	11.95
TMS2716	2048 x 8 (450ns)	9.95	8.95
TMS2532	(5v) 4096 x 8 (450ns)	21.95	19.95
2732	(5v) 4096 x 8 (450ns)	17.95	16.95

PROMS

74S188	(82S23)	OC	32 x 8	3.95
74S287	(82S129)	TS	256 x 4	4.75
74S288	(82S123)	TS	32 x 8	4.45
74S387	(82S126)	OC	256 x 4	5.75
74S471		TS	256 x 8	9.95
74S472	(82S147)	TS	512 x 8	16.85
74S474	(82S141)	TS	512 x 8	17.85
74S570	(82S130)	OC	512 x 4	7.80
74S571	(82S131)	TS	512 x 4	7.80

JDR MICRODEVICES, INC.

1101 South Winchester Blvd.
San Jose, California 95128
800-538-5000 800-662-6263 (Calif.)
408-247-4852



TERMS: For shipping include \$2.00 for UPS Ground; \$3.00 for UPS Blue Label Air; \$10.00 minimum order. Bay Area Residents add 8 1/2% sales tax. Calif. Residents add 6% sales tax. We reserve the right to limit quantities and substitute manufacturer. Prices subject to change without notice.

MUSICIANS: YOU CAN CREATE YOUR OWN SOUND!

NOW AVAILABLE:

"Electronic Projects for Musicians", revised edition.

By Craig Anderton. The first edition of this book showed thousands of musicians, many with no prior experience in electronics, how to create their own sound by building their own fuzzes, preamps, miniamps, etc. This new edition includes 27 projects, comprising improved/revised versions of most projects from the first book PLUS eight all new projects. There's also a new chapter on how to create pedalboards and multiple effects systems, a chapter on common questions and answers, and extensive use of photographs showing every step of the construction process to make building your own boxes a snap! There's even a soundsheet that demonstrates the sounds of the projects so you can easily decide which ones you'll want to build. All effects give performance that's equal to or better than commercial equivalents, and are designed to a consistent set of specifications to insure compatibility with all types of instruments as well as studio equipment. If you liked the original, you'll love the new version; and if you're just getting started, you couldn't have picked a better time! Foreword by Joe Walsh.

Guitar Player Books; softcover; \$11.95. Available in September.

ALSO AVAILABLE: "Home Recording for Musicians" by Craig Anderton.

Everything you need to know to set up a low cost, high quality studio at home - even includes info on how to build your own mixing console and a soundsheet demonstrating studio techniques. Soft cover; \$9.95. Parts kits available for mixing console project.

GODBOUT

ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

AND, WE HAVE THE PARTS KITS YOU NEED FOR HASSLE-FREE BUILDING!

Sure, you can dig up the parts yourself... but why not let us do the hard work for you? Each kit includes deluxe printed circuit board, all electronic components, potentiometers, instruction sheet, and in most cases, switches and jacks. Here are two of our most popular kits:

Project #8 - Compressor. Increase guitar sustain without fuzz, and add some gain at same time if needed. Also good for keeping levels constant while recording. Line or low level operation; frequency response (any control setting), ± 1 dB, 50 Hz - 20 KHz; headroom, 14V p-p; compression ratio, 10:1 (50 dB change in input level yields 5 dB change in output level). \$22.50.

Project #21 - Phase Shifter. 4 stage phaser includes wide range speed, depth, offset, resonance, and volume controls. Unique "add/subtract" switch provides filter-like effects as well as phasing; resonance control gives penetrating, metallic sound. Also includes true vibrato option (not tremolo). Uses opto-isolators rather than FET voltage control elements for exceptionally low noise (typical S/N ratio, -80 dB unweighted; worst case, -70 dB unweighted) and low distortion operation. Put two in series for even more amazing sounds! \$51.35.

Other kits include Preamp, Ring Modulator, 8 In 1 Out Mixer, Practice Play Along (plugs instrument into hi-fi for playing along with records/FM/tapes), Tube Sound Fuzz, Noise Gate, Active Splitter/Dual Buffer ("Spiffur"), Envelope Follower Adapter, Super Tone Control with on-board mixer, many more. Our MusiKit Flyer gives full details and pricing - write for it today!

Please Note: Unless you are experienced in electronics, we advise purchasing the above book before building any kits. Since we recognize that "do it yourself" may not be for everybody, order the book and look it over; if the building process looks too complex, you may return the book in resalable condition within 10 days for full refund.

TERMS: Call res add tax. Allow 5% shipping; excess refunded. Orders under \$15 add \$2 handling. VISA® and Mastercard® orders (\$25 min) call (415) 562-0836, 24 hrs. Include street address for UPS. More information? Send \$2 cents in stamps for our MusiKit Flyer (US and Canada only) or circle the bingo card number below.

CIRCLE NO. 34 ON FREE INFORMATION CARD

Quest

ELECTRONICS

P.O. Box 44300
Santa Clara, CA 95054

Will call: 2322 Walsh Ave.
(408) 988-1640 TWX 910-338-2139

Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

74LS00 TTL	MOS MEMORY RAM	PROM	MICROPROCESSOR	IC SOCKETS	DISPLAY LEDS																										
74LS00N 29 2101-1 95 2352 19.75 6504 9.95	74LS02N 29 2102-1 95 2708 4.70 6522 5.95	74LS05N 25 2102AM-2L 1.65 2716-1 8.50 6800 6.95	74LS08N 35 2104A-4 4.95 2716-5 Volt 6.50 6802 11.95	74LS10N 35 2107B-4 3.75 62716-5 Volt 48.00 6820 5.95	74LS130N 35 2111-1 3.75 2732 19.75 6836 5.95	74LS14N 1.00 2112-2 3.95 2756 14.00 8080A 3.95	74LS15N 35 2114 3.75 2741A 55.00 8085 12.95	74LS22N 35 2114L 300ns 2.25 2748 55.00 280 9.95	74LS24N 35 2114L 300ns 4.00 2748-8 55.00 280A 11.95	74LS30N 35 4118 200ns 2.95 2755A 55.00 8212 2.90	74LS32N 60 84116 700ns 18.40 NR2523 2.95 8214 3.95	74LS38N 50 MM5262 4.00 NR2523 4.95 8216 2.90	74LS47N 45 MM5280 3.00 NR2526 2.75 8224 3.45	74LS57N 65 MM5320 2.95 NR2529 4.95 8228 4.95	74LS60N 80 MM5330 5.94 NR2531 4.95 8251 6.95	74LS93N .75 PD411D-3 4.00 NR25136 8.75 8253 15.00	74LS95N 1.00 PD411D-4 5.00 NR25137 8.75 8255 5.75	74LS107N 45 PS101L 8.95 DM8577 2.90 8257 10.95	74LS112N 45 4202A 9.95 8223 3.50 8259 14.95	74LS123N 89 7102A 1.50 INTERFACE 1802CP plus 13.95	74LS136N 50 HD165-5 5.95 8091 6.59 1881P 9.50	74LS137N 89 7102A 1.50 ROSE 65 1881P 9.50	74LS155N .78 G1A38500 1 9.95 8097 65 CDP1802C 28.90	74LS157N 1.10 MCM4652514 3.95 8096 65 CDP1881P 7.95	74LS162N 1.10 9368 3.50 8109 1.25	74LS163N 1.10 410D 10.00 8110 4.50	74LS174N 1.15 416 16.00 8113 4.50	74LS190N 1.25 8120 5.50	74LS221N 1.25 416 16.00 8123 3.10	74LS259N 1.00 8124 3.50	74LS367N 89 8125 3.20

RESISTORS * watt 5%
10 per type 03
25 per type 075
100 per type 015
5 per type 012
350 piece pack
1 per type 8 75
1 per type 100
1 per type 05

IC SOCKETS
Solder Tin Low Profile
MAN1 CC 125 39
MAN2 CC 300 39
MAN7 7: CA CC 300 125
DL707 CA 300 100
DL727 728 CA CC 500 160
DL747 750 CA CC 600 95
FAD399 CC 357 70
FAD300 307 CC CA 500 135
FAD303 310 CC CA 500 90
FAD307 807 CC CA 600 225
1 1/2 pin 80
10 pin display 75
18 pin 25 100
24 pin 120
28 pin 150
32 pin 180
36 pin 210
40 pin 240
44 pin 270
48 pin 300
52 pin 330
56 pin 360
60 pin 390
64 pin 420
68 pin 450
72 pin 480
76 pin 510
80 pin 540
84 pin 570
88 pin 600
92 pin 630
96 pin 660
100 pin 690
104 pin 720
108 pin 750
112 pin 780
116 pin 810
120 pin 840
124 pin 870
128 pin 900
132 pin 930
136 pin 960
140 pin 990
144 pin 1020
148 pin 1050
152 pin 1080
156 pin 1110
160 pin 1140
164 pin 1170
168 pin 1200
172 pin 1230
176 pin 1260
180 pin 1290
184 pin 1320
188 pin 1350
192 pin 1380
196 pin 1410
200 pin 1440
204 pin 1470
208 pin 1500
212 pin 1530
216 pin 1560
220 pin 1590
224 pin 1620
228 pin 1650
232 pin 1680
236 pin 1710
240 pin 1740
244 pin 1770
248 pin 1800
252 pin 1830
256 pin 1860
260 pin 1890
264 pin 1920
268 pin 1950
272 pin 1980
276 pin 2010
280 pin 2040
284 pin 2070
288 pin 2100
292 pin 2130
296 pin 2160
300 pin 2190
304 pin 2220
308 pin 2250
312 pin 2280
316 pin 2310
320 pin 2340
324 pin 2370
328 pin 2400
332 pin 2430
336 pin 2460
340 pin 2490
344 pin 2520
348 pin 2550
352 pin 2580
356 pin 2610
360 pin 2640
364 pin 2670
368 pin 2700
372 pin 2730
376 pin 2760
380 pin 2790
384 pin 2820
388 pin 2850
392 pin 2880
396 pin 2910
400 pin 2940
404 pin 2970
408 pin 3000
412 pin 3030
416 pin 3060
420 pin 3090
424 pin 3120
428 pin 3150
432 pin 3180
436 pin 3210
440 pin 3240
444 pin 3270
448 pin 3300
452 pin 3330
456 pin 3360
460 pin 3390
464 pin 3420
468 pin 3450
472 pin 3480
476 pin 3510
480 pin 3540
484 pin 3570
488 pin 3600
492 pin 3630
496 pin 3660
500 pin 3690
504 pin 3720
508 pin 3750
512 pin 3780
516 pin 3810
520 pin 3840
524 pin 3870
528 pin 3900
532 pin 3930
536 pin 3960
540 pin 3990
544 pin 4020
548 pin 4050
552 pin 4080
556 pin 4110
560 pin 4140
564 pin 4170
568 pin 4200
572 pin 4230
576 pin 4260
580 pin 4290
584 pin 4320
588 pin 4350
592 pin 4380
596 pin 4410
600 pin 4440
604 pin 4470
608 pin 4500
612 pin 4530
616 pin 4560
620 pin 4590
624 pin 4620
628 pin 4650
632 pin 4680
636 pin 4710
640 pin 4740
644 pin 4770
648 pin 4800
652 pin 4830
656 pin 4860
660 pin 4890
664 pin 4920
668 pin 4950
672 pin 4980
676 pin 5010
680 pin 5040
684 pin 5070
688 pin 5100
692 pin 5130
696 pin 5160
700 pin 5190
704 pin 5220
708 pin 5250
712 pin 5280
716 pin 5310
720 pin 5340
724 pin 5370
728 pin 5400
732 pin 5430
736 pin 5460
740 pin 5490
744 pin 5520
748 pin 5550
752 pin 5580
756 pin 5610
760 pin 5640
764 pin 5670
768 pin 5700
772 pin 5730
776 pin 5760
780 pin 5790
784 pin 5820
788 pin 5850
792 pin 5880
796 pin 5910
800 pin 5940
804 pin 5970
808 pin 6000
812 pin 6030
816 pin 6060
820 pin 6090
824 pin 6120
828 pin 6150
832 pin 6180
836 pin 6210
840 pin 6240
844 pin 6270
848 pin 6300
852 pin 6330
856 pin 6360
860 pin 6390
864 pin 6420
868 pin 6450
872 pin 6480
876 pin 6510
880 pin 6540
884 pin 6570
888 pin 6600
892 pin 6630
896 pin 6660
900 pin 6690
904 pin 6720
908 pin 6750
912 pin 6780
916 pin 6810
920 pin 6840
924 pin 6870
928 pin 6900
932 pin 6930
936 pin 6960
940 pin 6990
944 pin 7020
948 pin 7050
952 pin 7080
956 pin 7110
960 pin 7140
964 pin 7170
968 pin 7200
972 pin 7230
976 pin 7260
980 pin 7290
984 pin 7320
988 pin 7350
992 pin 7380
996 pin 7410
1000 pin 7440
1004 pin 7470
1008 pin 7500
1012 pin 7530
1016 pin 7560
1020 pin 7590
1024 pin 7620
1028 pin 7650
1032 pin 7680
1036 pin 7710
1040 pin 7740
1044 pin 7770
1048 pin 7800
1052 pin 7830
1056 pin 7860
1060 pin 7890
1064 pin 7920
1068 pin 7950
1072 pin 7980
1076 pin 8010
1080 pin 8040
1084 pin 8070
1088 pin 8100
1092 pin 8130
1096 pin 8160
1100 pin 8190
1104 pin 8220
1108 pin 8250
1112 pin 8280
1116 pin 8310
1120 pin 8340
1124 pin 8370
1128 pin 8400
1132 pin 8430
1136 pin 8460
1140 pin 8490
1144 pin 8520
1148 pin 8550
1152 pin 8580
1156 pin 8610
1160 pin 8640
1164 pin 8670
1168 pin 8700
1172 pin 8730
1176 pin 8760
1180 pin 8790
1184 pin 8820
1188 pin 8850
1192 pin 8880
1196 pin 8910
1200 pin 8940
1204 pin 8970
1208 pin 9000
1212 pin 9030
1216 pin 9060
1220 pin 9090
1224 pin 9120
1228 pin 9150
1232 pin 9180
1236 pin 9210
1240 pin 9240
1244 pin 9270
1248 pin 9300
1252 pin 9330
1256 pin 9360
1260 pin 9390
1264 pin 9420
1268 pin 9450
1272 pin 9480
1276 pin 9510
1280 pin 9540
1284 pin 9570
1288 pin 9600
1292 pin 9630
1296 pin 9660
1300 pin 9690
1304 pin 9720
1308 pin 9750
1312 pin 9780
1316 pin 9810
1320 pin 9840
1324 pin 9870
1328 pin 9900
1332 pin 9930
1336 pin 9960
1340 pin 9990
1344 pin 10020
1348 pin 10050
1352 pin 10080
1356 pin 10110
1360 pin 10140
1364 pin 10170
1368 pin 10200
1372 pin 10230
1376 pin 10260
1380 pin 10290
1384 pin 10320
1388 pin 10350
1392 pin 10380
1396 pin 10410
1400 pin 10440
1404 pin 10470
1408 pin 10500
1412 pin 10530
1416 pin 10560
1420 pin 10590
1424 pin 10620
1428 pin 10650
1432 pin 10680
1436 pin 10710
1440 pin 10740
1444 pin 10770
1448 pin 10800
1452 pin 10830
1456 pin 10860
1460 pin 10890
1464 pin 10920
1468 pin 10950
1472 pin 10980
1476 pin 11010
1480 pin 11040
1484 pin 11070
1488 pin 11100
1492 pin 11130
1496 pin 11160
1500 pin 11190
1504 pin 11220
1508 pin 11250
1512 pin 11280
1516 pin 11310
1520 pin 11340
1524 pin 11370
1528 pin 11400
1532 pin 11430
1536 pin 11460
1540 pin 11490
1544 pin 11520
1548 pin 11550
1552 pin 11580
1556 pin 11610
1560 pin 11640
1564 pin 11670
1568 pin 11700
1572 pin 11730
1576 pin 11760
1580 pin 11790
1584 pin 11820
1588 pin 11850
1592 pin 11880
1596 pin 11910
1600 pin 11940
1604 pin 11970
1608 pin 12000
1612 pin 12030
1616 pin 12060
1620 pin 12090
1624 pin 12120
1628 pin 12150
1632 pin 12180
1636 pin 12210
1640 pin 12240
1644 pin 12270
1648 pin 12300
1652 pin 12330
1656 pin 12360
1660 pin 12390
1664 pin 12420
1668 pin 12450
1672 pin 12480
1676 pin 12510
1680 pin 12540
1684 pin 12570
1688 pin 12600
1692 pin 12630
1696 pin 12660
1700 pin 12690
1704 pin 12720
1708 pin 12750
1712 pin 12780
1716 pin 12810
1720 pin 12840
1724 pin 12870
1728 pin 12900
1732 pin 12930
1736 pin 12960
1740 pin 12990
1744 pin 13020
1748 pin 13050
1752 pin 13080
1756 pin 13110
1760 pin 13140
1764 pin 13170
1768 pin 13200
1772 pin 13230
1776 pin 13260
1780 pin 13290
1784 pin 13320
1788 pin 13350
1792 pin 13380
1796 pin 13410
1800 pin 13440
1804 pin 13470
1808 pin 13500
1812 pin 13530
1816 pin 13560
1820 pin 13590
1824 pin 13620
1828 pin 13650
1832 pin 13680
1836 pin 13710
1840 pin 13740
1844 pin 13770
1848 pin 13800
1852 pin 13830
1856 pin 13860
1860 pin 13890
1864 pin 13920
1868 pin 13950
1872 pin 13980
1876 pin 14010
1880 pin 14040
1884 pin 14070
1888 pin 14100
1892 pin 14130
1896 pin 14160
1900 pin 14190
1904 pin 14220
1908 pin 14250
1912 pin 14280
1916 pin 14310
1920 pin 14340
1924 pin 14370
1928 pin 14400
1932 pin 14430
1936 pin 14460
1940 pin 14490
1944 pin 14520
1948 pin 14550
1952 pin 14580
1956 pin 14610
1960 pin 14640
1964 pin 14670
1968 pin 14700
1972 pin 14730
1976 pin 14760
1980 pin 14790
1984 pin 14820
1988 pin 14850
1992 pin 14880
1996 pin 14910
2000 pin 14940
2004 pin 14970
2008 pin 15000
2012 pin 15030
2016 pin 15060
2020 pin 15090
2024 pin 15120
2028 pin 15150
2032 pin 15180
2036 pin 15210
2040 pin 15240
2044 pin 15270
2048 pin 15300
2052 pin 15330
2056 pin 15360
2060 pin 15390
2064 pin 15420
2068 pin 15450
2072 pin 15480
2076 pin 15510
2080 pin 15540
2084 pin 15570
2088 pin 15600
2092 pin 15630
2096 pin 15660
2100 pin 15690
2104 pin 15720
2108 pin 15750
2112 pin 15780
2116 pin 15810
2120 pin 15840
2124 pin 15870
2128 pin 15900
2132 pin 15930
2136 pin 15960
2140 pin 15990
2144 pin 16020
2148 pin 16050
2152 pin 16080
2156 pin 16110
2160 pin 16140
2164 pin 16170
2168 pin 16200
2172 pin 16230
2176 pin 16260
2180 pin 16290
2184 pin 16320
2188 pin 16350
2192 pin 16380
2196 pin 16410
2200 pin 16440
2204 pin 16470
2208 pin 16500
2212 pin 16530
2216 pin 16560
2220 pin 16590
2224 pin 16620
2228 pin 16650
2232 pin 16680
2236 pin 16710
2240 pin 16740
2244 pin 16770
2248 pin 16800
2252 pin 16830
2256 pin 16860
2260 pin 16890
2264 pin 16920
2268 pin 16950
2272 pin 16980
2276 pin 17010
2280 pin 17040
2284 pin 17070
2288 pin 17100
2292 pin 17130
2296 pin 17160
2300 pin 17190
2304 pin 17220
2308 pin 17250
2312 pin 17280
2316 pin 17310
2320 pin 17340
2324 pin 17370
2328 pin 17400
2332 pin 17430
2336 pin 17460
2340 pin 17490
2344 pin 17520
2348 pin 17550
2352 pin 17580
2356 pin 17610
2360 pin 17640
2364 pin 17670
2368 pin 17700
2372 pin 17730
2376 pin 17760
2380 pin 17790
2384 pin 17820
2388 pin 17850
2392 pin 17880
2396 pin 17910
2400 pin 17940
2404 pin 17970
2408 pin 18000
2412 pin 18030
2416 pin 18060
2420 pin 18090
2424 pin 18120
2428 pin 18150
2432 pin 18180
2436 pin 18210
2440 pin 18240
2444 pin 18270
2448 pin 18300
2452 pin 18330
2456 pin 18360
2460 pin 18390
2464 pin 18420
2468 pin 18450
2472 pin 18480
2476 pin 18510
2480 pin 18540
2484 pin 18570
2488 pin 18600
2492 pin 18630
2496 pin 18660
2500 pin 18690
2504 pin 18720
2508 pin 18750
2512 pin 18780
2516 pin 18810
2520 pin 18840
2524 pin 18870
2528 pin 18900
2532 pin 18930
2536 pin 18960
2540 pin 18990
2544 pin 19020
2548 pin 19050
2552 pin 19080
2556 pin 19110
2560 pin 19140
2564 pin 19170
2568 pin 19200
2572 pin 19230
2576 pin 19260
2580 pin 19290
2584 pin 19320
2588 pin 19350
2592 pin 19380
2596 pin 19410
2600 pin 19440
2604 pin 19470
2608 pin 19500
2612 pin 19530
2616 pin 19560
2620 pin 19590
2624 pin 19620
2628 pin 19650
2632 pin 19680
2636 pin 19710
2640 pin 19740
2644 pin 19770
2648 pin 19800
2652 pin 19830
2656 pin 19860
2660 pin 19890
2664 pin 19920
2668 pin 19950
2672 pin 19980
2676 pin 20010
2680 pin 20040
2684 pin 20070
2688 pin 20100
2692 pin 20130
2696 pin 20160
2700 pin 20190
2704 pin 20220
2708 pin 20250
2712 pin 20280
2716 pin 20310
2720 pin 20340
2724 pin 20370
2728 pin 20400
2732 pin 20430
2736 pin 20460
2740 pin 20490
2744 pin 20520
2748 pin 20550
2752 pin 20580
2756 pin 20610
2760 pin 20640
2764 pin 20670
2768 pin 20700
2772 pin 20730
2776 pin 20760
2780 pin 20790
2784 pin 20820
2788 pin 20850
2792 pin 20880
2796 pin 20910
2800 pin 20940
2804 pin 20970
2808 pin 21000
2812 pin 21030
2816 pin 21060
2820 pin 21090
2824 pin 21120
2828 pin 21150
2832 pin 21180
2836 pin 21210
2840 pin 21240
2844 pin 21270
2848 pin 21300
2852 pin 21330
2856 pin 21360
2860 pin 21390
2864 pin 21420
2868 pin 21450
2872 pin 21480
2876 pin 21510
2880 pin 21540
2884 pin 21570
2888 pin 21600
2892 pin 21630
2896 pin 21660
2900 pin 21690
2904 pin 21720
2908 pin 21750
2912 pin 21780
2916 pin 21810
2920 pin 21840
2924 pin 21870
2928 pin 21

THE MICROCOMPUTER MART

COMPUTER RETAIL STORES

MICROCOMPUTER MART RATE: 1" x 1 Column (1-5/8") \$150. 1-1/2" x 1 Column (1-5/8") \$225.00. 2" x 1 Column (1-5/8") \$300.00. **GENERAL INFORMATION:** Frequency rates available. Payment must accompany copy except credit card—Am. Ex., Diners, MC, VISA (supply Expiration date)—or accredited ad agency insertions. Orders are not acknowledged. They will appear in next available issue after receipt. Closing date: 1st of the 2nd month preceding cover date (for example, April issue closes February 1st). Send order and remittance to MicroComputerMart, POPULAR ELECTRONICS, One Park Avenue, New York, NY 10016. Direct inquiries to (212) 725-3485.

PENNSYLVANIA

DISTRIBUTORS FOR:

- 3M
- Texas Instruments
- Apple
- Ohio Scientific
- Verbatim
- Etc

Call or Write
ERIE COMPUTER COMPANY
 "Since the Beginning"
 2131 W. 8th St., Erie, Penn. 16505
 (814) 454-7652 — Ask for Don Wolfe

NEW HAMPSHIRE

Don't Miss
MICROCOMPUTING
 — the encyclopedia of microcomputing

and
80 microcomputing
 — for the users of the TRS-80*

For subscription information write to:
 Microcomputing Peterborough, NH 03103
 88 Pine Street Attn: Denis
© 1981 by J. J. ... the Nation's Best Deal on a 7" Area Computer

OHIO SCIENTIFIC MICRO-COMPUTERS

A.A. Office
Equipment Company
 2140 American Avenue
 Hayward, CA 94545
 (415) 782-6110

NEW YORK

THE NEC
PERSONAL COMPUTER
 The End of the Compromise

We Have It
 SYNAPSE VIDEO
 P.O. BOX 962 / N.Y., N.Y. 10009
 (212) 860-5776

TEXAS

TEXAS COMPUTER SYSTEMS
Radio Shack
 Authorized Sales Center, OFFERS
LOWEST PRICES on

TRS-80
COMPUTERS

Call TOLL FREE for the BEST PRICES on all
 Radio Shack® Computers and accessories
 • FREE SHIPPING on most items
 • No out of state sales tax charged

NEW—Percom DOUBLE DENSITY for Model I. Twice the disk
 space. Easy to install, no modifications. Copies single density to
 DOUBLE DENSITY to convert existing software. Less than \$200

TOLL FREE 800-351-1473
 Texas Residents 915-597-0673
 TEXAS COMPUTER SYSTEMS
 106 E. 10th, Brady, Tx 76825
 Radio Shack® Authorized Sales Center F701
TM Registered Trademark of Radio Corp.

NEW JERSEY

Floppy Disk Services Inc.
 C.N. 5212
 Princeton, N.J. 08540

Siemens disk drives for your radio shack,
 S-100 or other microcontracted OEM, best
 prices in the country. Complete systems and
 large inventory of spare parts. Direct
 replacement drives for Heath Computers.
DUAL 8 INCH HEATH SYSTEM NOW
AVAILABLE! MOD II drives at half store
prices!

BA-4P Mon-Fri - Mastercard Visa
 Phone orders - 609-771-0374

ILLINOIS

BEST PRICES AVAILABLE
APPLE PRODUCTS
 48K Apple \$1,090. Plus \$20 Shipping
 Call for best deals on Altos
THE COMPUTER ROOM
 2218 Plainfield Rd., Joliet, IL 60435
 For information call: (815) 725-9396
 Certified check for immediate shipment. Personal
 checks delayed for bank clearance. Add \$22.00 for
 major credit (MC/VISA/Amer. Express) MD C.O.D.

MICROFILM EDITIONS AVAILABLE

Copies of POPULAR ELECTRONICS
 Magazine are available on microfilm
 from Xerox University Microfilms, Ann
 Arbor, Michigan; Microfiche from Bell
 & Howell, Micro Photo Division, Woos-
 ter, Ohio.

MICROCOMPUTER MART ORDER FORM

Please Print Clearly or Type Copy in Space Below
 (Indicate position of any illustration in ad & supply B&W photo)

Please refer to heading on this page for rates & ad placement information:

OF INCHES _____ # OF INSERTIONS _____

PAYMENT ENCLOSED \$ _____

CHARGE: You will be billed monthly Amex Diners MC-Interbank # _____

Account # _____ Exp. Date _____

SIGNATURE _____

PRINT NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

RADIO SHACK®

TRS-80™

Computers

Buy Direct From

Pan American Electronics, Inc.



Discounts • Free Shipping
TOLL FREE ORDER NUMBER
 • 800/531-7466 •

Dept. 67 • 1117 Conway Avenue
 Mission, Texas 78572
 Texas & Principle No. 512-581-2765
 Telex Number 767339

NEW Showroom/Warehouse
 2912 N. Main • Ft. Worth, Texas
 Phone (817)625-6333 • Telex 767339

TM Registered Trademark of Radio Corp.

The Original ByteShop®

1415 W. El Camino Real
 Mountain View, CA 94040
 (415) 969-5464

OHIO SCIENTIFIC

Get The Catalog & Our Low Prices
 Data Products Maintenance
 9460 Telsur
 El Monte, CA 91731
 (213) 350-4191 (714) 994-4180

MODEL II



\$459⁰⁰ **DISCOUNT**
 Off List

64K 1 DRIVE \$3440.00

No Taxes on Out of State Shipments

Immediate Shipment On Most Items

TRS-80® DISCOUNT

BUY DIRECT

We carry the full line of TRS-80 Computers. All
 other software, furniture, and accessories at dis-
 count from catalog price. We stock most items
 to assure you fast delivery and save you money.


WRITE FOR A FREE CATALOG

1-800-841-0860 Toll Free Order Entry
MICRO MANAGEMENT SYSTEMS, INC.

DEPT. NO. 12

DOWNTOWN PLAZA SHOPPING CENTER
 115 C SECOND AVE S.W.
 CAIRO, GEORGIA 31728
 GA. & EXPORT PHONE NO (912) 377-7120

MODEL III

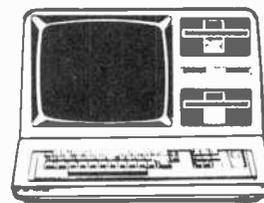

26-1061 4K I..... \$629.00
 26-1062 16K III..... 865.00
 26-1063 32K III
2 Drives, RS232..... 2225.00

Largest Inventory in S.E. U.S.A.

Electronics Classified

CLASSIFIED RATES: Per Word, 15 Word Minimum. **COMMERCIAL:** \$3.00. **EXPAND-AD:** \$4.50. **DISPLAY:** 1" x 2 1/4", \$370.00. 2" x 2 1/4", \$740.00. 3" x 2 1/4", \$1,110.00. **GENERAL INFORMATION:** Frequency rates and prepayment discounts available. Payment must accompany order except credit card—Am. Ex., Diners, MC, VISA (include exp. date)—or accredited ad agency insertions. Copy subject to publisher's approval; must be typewritten or printed. First word set in caps. Advertisers using P.O. Boxes MUST supply permanent address and telephone number. Orders not acknowledged. They will appear in next available issue after receipt. Closing date: 1st of the 2nd month preceding cover date (e.g., Mar. issue closes Jan. 1). Send order & remittance to: Classified Advertising, Popular Electronics Magazine, 1 Park Avenue, New York, NY 10016. Direct inquiries to Rose Lynch, (212) 725-7686.

FOR SALE

FREE! Catalog — LED's, readouts, Poly Paks, Box 942PE Lynnfield, Mass. 01940.

GOVERNMENT and industrial surplus receivers, transmitters, sniperscopes, electronic parts, Picture Catalog 25 cents. Meshna, Nahant, Mass. 01908.

ELECTRONIC PARTS, semiconductors, kits. **FREE FLYER.** Large catalog \$1.00 deposit. **BIGELOW ELECTRONICS,** Bluffton, Ohio 45817.

RADIO—T.V. Tubes — 49 cents each. Send for free catalog. Cornell, 4213 University, San Diego, Calif. 92105.

SAVE UP TO 50% on name brand test equipment. Free catalog and price list. Salen Electronics, Box 82, Skokie, IL 60077.

TELETYPE EQUIPMENT: Copy Military, Press, Weather, Amateur, Commercial Transmissions. Catalog \$1.00. **WEATHER-MAP RECORDERS:** Copy Satellite Photographs, National-Local Weather Maps. Learn How! \$1.00. Atlantic Sales, 3730 Nautilus Ave., Brooklyn, NY 11224. Phone: (212) 372-0349.

SOUND SYNTHESIZER KITS — Surf \$19.95, Wind \$19.95, Wind Chimes \$24.95, Musical Accessories, many more. Catalog free. PAIA Electronics, Box J14359, Oklahoma City, OK 73114.

BUILD AND SAVE. TV EARTH STATION. DETECTIVE ELECTRONICS. TV De-Scramblers, Video Recorders, Color Cameras, advanced Telephone Projects, BROADCAST Electronics. 50 page color catalog of unusual electronic projects AIR MAILED \$3.00; with 3 hour audio cassette dramatization of our catalog \$5.00. Don Britton Enterprises, PO Drawer G, Waikiki, Hawaii 96815.

UNSCRAMBLERS FOR any scanner. Several models available. Free literature. Capri Electronics, 8753T Windom, St. Louis, MO 63114.

UNSCRAMBLERS, seven models available to decode police, ambulance, and fire coded transmissions. Other scanner devices. Tone encoders/decoders. Telephone accessories, etc. Free Catalog. **KRYSTAL KITS,** Box 445, Bentonville, AR 2712. (501) 273-5340.

POLICE/FIRE SCANNERS, crystals, antennas, CBs, Radar Detectors. HPR, Box 19224, Denver, CO 80219.

PRINTED CIRCUIT supplies, chemicals, tools, artwork, plating solutions. Major credit cards. Catalog \$2.00, refundable. **CIRCOLEX,** Box 198, Marcy, NY 13403.

RECONDITIONED TEST EQUIPMENT \$1.00 for catalog. **WALTER'S TEST EQUIPMENT,** 2697 Nickel, San Pablo, CA 94806. (415) 758-1050.

NEW ELECTRONIC PARTS. Continuously stocked. Stamp brings catalog. Daytapo Electronics, 3029 N. Wilshire Ln., Arlington Hts., IL 60004.

ELECTRONIC CATALOG. Over 4,500 items. Parts, & components. Everything needed by the hobbyist or technician. \$2.00 (U.S. funds) \$4.00 Foreign Postage & handling, refundable with first \$15.00 order. T & M Electronics, 472 East Main St., Patchogue, NY 11772. (516) 289-2520.

SPEAKERS SAVE 50%. Build your own speaker system. Write: McGee Radio Electronics, 1901 McGee Street, Kansas City, Missouri 64108.

PRINTED CIRCUIT BOARDS, your artwork. Quick delivery. Reasonable. Atlas Circuits, Box 892, Lincolnton, NC 28092. (704) 735-3943.

CABLE TV DESCRAMBLERS AND CONVERTERS. MICROWAVE ANTENNAS AND DOWN CONVERTERS. Plans and parts. Build or buy. For information send \$2.00. C&D Company, P.O. Box 21, Jenison, MI 49428.

SCRAMBLED TELEVISION—Encoding/Decoding. New publication. Complete theory, circuits. \$9.95. Workshop, Box 393PEJ, Bethpage, NY 11714.

FIBER OPTIC SPECIALS — 100 foot spool of fiber \$3.00 — Experimenter's kit \$6.00 — High Power LED with matched Detector \$10.00 — Data Link construction plans (detailed) \$5.00. Catalog with samples \$1.00. **FIBERTRONICS,** Box 322-A, Primos, PA 19018.

Telephone Listening Device

Record telephone conversations in your office or home. Connects between any cassette or tape recorder and your telephone or telephone LINE. Starts automatically when phone is answered. Records both sides of phone conversation. Stops recorder when phone is hung up. This device is not an answering service.



Each
\$18.95

Qty Disc Avail



Size 2"x3"x1"

Super Powerful Wireless Mic

10 times more powerful than other mics. Transmits up to 1/4 mile to any FM radio. Easy to assemble kit. 15V battery (not incl.)

Call (305) 725-1000 or send \$18.95 + \$1.00 shipping per item to **USI Corp., P.O. Box PE-2052, Melbourne, FL 32901.** COD's accept. For catalog of transmitters, voice scramblers and other specialty items, enclose \$2.00 to **USI Corp.**

CHEMICALS, Apparatus, Project Books, Wide Selection. Catalog send \$1.00 to Pioneer Corp., 14a Hughey Street, Nashua, NH 03060.

TEST EQUIPMENT, new and used. Catalog \$1.00. PTI, Box 8756; White Bear Lake, MN 55110.

QUALITY AUDIO COMPONENTS. Multi-Track Equipment, Programmable Calculators, Accessories. Competitive Pricing! Prompt Delivery! Knowledgeable staff! Service Facility! Credit Cards accepted. **FREE catalog. SOUND IDEAS,** Dept. SR, PO Box 340, Cary, N.C. 27511. 1-800-334-2483 (N.C. 919-467-8462).

UNSCRAMBLE CODED MESSAGES from police, fire and medical channels. Also telephone recording adaptor. Same day service. Satisfaction guaranteed. **Don Nobles Electronics, Inc. Rt. 7, Box 610-A, Hot Springs, AR 71901. (501) 623-6027.**

PCB as low as 15¢ sq-in. **FREE DRILLING.** International Enterprise, 6452 Hazel Circle, Simi Valley, CA 93065.

SUBSCRIPTION TELEVISION EDUCATION MANUAL! Two scrambling decoding systems, theory, circuits. Decoder dealers listed. \$14.95. Microwave Television Manual: **ABEX,** P.O. Box 26601-P5, \$16.25. Kits available. Information package: \$2.00. San Francisco, CA 94126.

TELEVISION DOWNCONVERTERS and decoders \$99.95 up. Details for Stamp. **GW Electronics,** POB 688, Greenwood, IN 46142.

TOP QUALITY SPEAKERS AND KITS. Send \$2.00. Speaker Warehouse, 809 North Route 441, Hollywood, FL 33021.

LOWEST PRICES ELECTRONIC PARTS, confidential catalog free. **KNAPP,** 4750 96th St. N., St. Petersburg, FL 33708.

SATELLITE VISION

SATELLITE VISION

We manufacture the highest spec 3-meter data & video dish in the world 41db gain! We also sell direct. Immediate delivery or you pick up. Complete details including satellite TV information, aiming service and discount schedule. Send \$1.25 for postage & handling to:

TIGER TENNAS
P. O. Box 581
Casselberry, Florida 32707



BUY DIRECT

PICTURE TUBE REBUILDING equipment new and used. **ATOLL TELEVISION,** 6425 Irving Park, Chicago, Illinois 60634.

Satellite TV

FOR THE HOME

Sick of Network TV?

Our receiver lets you get over 75 channels of television directly from earth-orbiting cable TV satellites! HBO, Showtime, super stations, sports and movies worldwide.

We don't just sell information! We Manufacture Hardware!

technical information book and catalog gives you all the facts. Inexpensive dishes, feeds, telemetry software, kits and more. Recommended reading by NASA. The Office of Consumer Affairs and quality companies like Rockwell/Collins. Send \$7.95 today!



From offshore oil rigs, data links to hotels and backyard installations, we wrote the book. Constantly updated, our 94 Page

CALL
24-hrs. C.O.D. Hotline
(305) 339-7800

SPACECOAST

RESEARCH CORPORATION
P.O. Box 442-A, Altamonte Spgs, FL 32701

ROBOT KITS, PARTS, MATERIALS BOOKS. Send \$3 for subscription to catalog and newsletter. **ROBOT MART,** 19 West 34th St., New York, NY 10001.

FREE SPEAKER CATALOG! Woofers, mids, tweeters, hardware, crossovers, grille cloth, plans, kits, information, much more. Discount Prices. Universal Sound, Dept PE, 2253 Ringling Blvd., Sarasota, FL 33577. (813) 953-5363.

SATELLITE TELEVISION... **HOWARD/COLEMAN** boards to build your own receiver. For more information write... **ROBERT COLEMAN,** Rt. 3, Box 58-APE, Travelers Rest, S.C. 29690.

SATELLITE TELEVISION RECEIVERS \$300, dishes \$100, LNA's, downconverters. Catalog \$5.00. **Satellite Systems Development,** Box 184, Milpitas, CA 95035.

DECODE Morse and RTTY signals off the air with our **MORSE-A-WORD** or **RTTY READER.** **MORSE-A-KEYER** keyboard also available. Quality kits or factory wired. Call or write for details. **MICROCRAFT,** Box 513PE, Thiensville, WI 53092. (414) 241-8144.

RF MODULATORS! Special versions for SATELLITE TELEVISION, COMPUTERS, CCTV. Also Monitors, Cameras, Kits. **FREE catalog.** Phone (402) 987-3771. Dealers welcomed. **ATV RESEARCH,** 13-P Broadway, Dakota City, NE 68731.

SPEAKERS in any room. No wiring. Up to 100 watts. For information send \$3.95 to D to R Enterprises, 323 N. Brockway, Palatine, IL 60067.

SUBSCRIPTION TV DECODER KIT \$39.00. Includes parts, manual, and etched board. Manual only \$4.60. **MICROWAVE TV DOWNCONVERTER KIT** \$169.00. Assembled \$220.00. Catalog \$2.00. **J&W Electronics,** P.O. Box 61, Cumberland, RI 02864.

AUDIO FREQUENCY GENERATOR. Digital readout. 15Hz-50KHz. No range switching. Vernier, Sine wave, T.T.L. square. Detailed plans \$7.50. W/O Digital readout \$3.50. P.C.B.'s and parts available. **SCHROEDER ELECTRONICS,** P.O. Box 171, Rolla, MO 65401.

DIGITAL REVERB September 80 issue PE, PCB \$18. Critical IC's \$23. Memory set \$50. SASE for reprint. **Videoart,** Box 10327, Stanford, CA 94305.

MICROWAVE DOWNCONVERTERS BUILT — IN preamp-highest gain. Downconverter board, plans - \$15.00. Power Supply Board, Plans - \$5.00. Antenna Cookbook - \$5.00. All three for \$20.00. **MICRO ENGINEERING,** P.O. Box 17231, Minneapolis, MN 55417.

RF POWER TRANSISTOR - TUBE CATALOG FREE. MRF453/MRF455A/SK1451 - \$14.00; MRF454/SRF2072/MRF2769 - \$17.00; MRF245/MRF247 - \$27.00; 2N4048 - \$6.20; Exclusive Repair Center for PALOMAR PRIDE, etc. Westcom, 1320 Grand, San Marcos, CA 92069. (714) 744-0728.

\$10 ELECTRONIC BUG ZAPPER. 10,000 VOLTS. Plans \$5. Contemporary Concepts, Box 1381, Johnson City, Tennessee 37601.



ELECTRONIC ORGAN KITS
3-4 Manuals

THEATER and CLASSICAL

Refundable Parts
Brochure \$2.00 Catalog \$1.50

Wurlitzer reproductions

DEVTRONIX ORGANS, INC., Dept 20
6101 WAREHOUSE WAY, SACRAMENTO, CA 95826

INEXPENSIVE CABLE TV Descramblers-Converters-Microwave Antennas! Exclusive catalog \$2.00. ACM, Box 3431, Walnut Creek, CA 94598.


SCRAMBLED TELEVISION TUNERS. Wideband UHF tuner converts all UHF to VHF channels. \$28.00 plus \$1.50 postage. Money order only. Quest, Box 1722, Costa Mesa, CA 92627.

PSYCHEDELIC LIGHT DRIVER. 3 channel, 200 watt/channel. Easy build. Kit: \$24.95 plus \$1.50 postage; Plans: \$2.00 SASE. Quest, Box 1722, Costa Mesa, CA 92627.

ALL PURPOSE SHEAR

Cuts metal up to .040" thick, 12" wide; printed circuit laminates up to .093" thick.

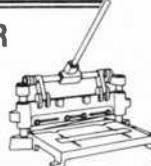Precision fabricated in cast aluminum and hardened tool steel. Accessories available for hole punching, notching, bending and drilling. A versatile tool!



\$280.
F.O.B.
Kepro plant

VISA, MasterCard, American Express cards accepted. Call toll-free 1-800-325-3878 (except in Missouri: 1-314-343-1630)

KEPRO CIRCUIT SYSTEMS, INC.
630 Axminster Dr., Fenton (St. Louis), Mo. 63026

ELECTRONIC BARGAIN! 35 new, guaranteed components, data sheets and 22 project schematics. \$5.00. Dirk, B5 Echols Court, Blacksburg, VA 24060.

AMATEUR MICROWAVE T.V. ANTENNAS. T.V. Receive uninterrupted movies, fully guaranteed. Also in kit form. For information send \$5.00 to: MDS Specialist, P.O. Box 67, Southaven, MS 38671.

ANALOG Delay, Audio, and Music Synthesizer I.C.'s plus more! Free Flyer. PGS Electronics, P.O. Box 735A, Terre Haute, IN 47808.

SHORT WAVE, AMATEUR RECEIVERS, \$50 - \$350. Some brand new. HALL, Rt 3, Box 281A, Staunton, VA 24401. (703) 363-5787. Details for SASE.

PRINTED CIRCUIT BOARDS. We can ship most boards from your artwork in 7 days, or our designers can produce an artwork from your schematic. Precision work, reasonable prices, timely deliveries. Digitronics, P.O. Box 2494, Toledo, Ohio 43606. 419-473-0985.

BALL BROTHERS HI-RES 12" TV Monitors. New. Great with Apple, TRS80 or Ham-TV. \$150.00. Mario Klas, 215 Osceola Ave., Deer Park, NY 11729. (516) 242-2321.

AIM your SATELLITE TELEVISION ANTENNA ACCURATELY using azimuth & elevation data computed for your location ANYWHERE WORLDWIDE. Chart shows which of 44 satellites are within your reception area. You will also receive our 9 page booklet showing future launches, frequencies, formats, antenna/leadline data, list of satellite TV suppliers. \$10.00, COMPUSAT, Cartographic Division, 643 South Route 83, Elmhurst, IL 60126.

GIVE AWAY FREE - ON-TV. Showtime, HBO, microwave MDS, Converter/Decoders, and make money. Information \$5 and SASE. DOT, Box 200E, Chicago Ridge, Illinois 60415.


SATELLITE EARTH STATION - Build your own antenna for less than \$200.00 with materials you can buy local. Complete instructions plus material list. Any handyman can do it. Send today \$7.95 to: YOUNG SATELLITE SYSTEM, P.O. Box 79089P, Fort Worth, TX 76179.

PCB 15¢ sq-in free drilling. Satisfaction guaranteed. INTERNATIONAL ENTERPRISE, 6452 Hazel Circle, Simi Valley, CA 93063.

NEW! Computerized anti-theft device for autos & RV's. Easily installed. Details-send stamp. Professional Mail Service, Box 178, Old Bridge, NJ 08857.

TELEPHONE AND EQUIPMENT CATALOG -- \$2 Refundable. Telcom, 815 East Third, Dept. E, Beardstown, IL 62618.

Enjoy Satellite TV Now

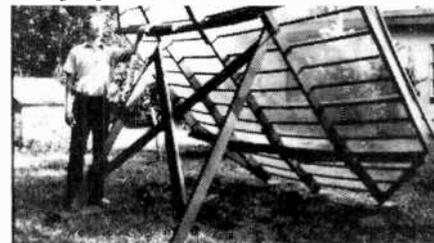

Better than Cable TV—Over 200 TV and radio services. Why waste money? Learn the whole story and build a video system the family can enjoy. No commercials, FREE movies, sports and Vegas shows—worldwide, crystal clear reception connects to any TV set. Big (8 x 11 in.) book loaded with details, photos, kits—

TELLS EVERYTHING! Satisfaction Guaranteed.
Send \$8.95 TODAY! Add \$2.00 for 1st class (air mail) or call our 24 hour C.O.D. rush order line (305) 862-5068.

GLOBAL ELECTRONICS,
P.O. Box 219-K, Maitland, Florida 32751

Resistors 1/4W, 1/2W 5% C.F. 3cea. 1% Metallfilms. IX Sockets, LED's Diodes. Details from, JR INDUSTRIES, 5834-A Swancreek, Toledo, Ohio 43614.

NEW! Computerized anti-theft device for autos & RV's. Easily installed. Details-send stamp. Professional Mail Service, Box 178, Old Bridge, NJ 08857.

REMOTE CONTROL . . . BSR SYSTEM - X-10 plug-in controllers and timers turn lights and appliances on and off via remote modules. Same as Sears, Leviton, Radio Shack. LOWEST PRICES NATIONWIDE - COMPLETE LINE including Telephone Responder Set, Battery Back-up Timer. FREE LITERATURE, PRICE LIST. VISA Master Card. Call: (801) 328-8855. Write: INTERFACE ELECTRONICS, 745 Pacific Avenue, Salt Lake City, Utah 84104.

ATARI SPACE INVADERS IS MORE FUN with the RAPID FIRE Variation. Doesn't LIMIT YOU to FIRING ONLY ONE LASER each time. APPLIES INSTANTLY!! NO MODIFICATION TO YOUR COMPONENTS! NOW SPECIALLY PRICED! \$5.98 COMPLETE. BALIS, Box 522, Brooklyn, NY 11215.

COMPUTER EQUIPMENT

SURPLUS COMPUTER PERIPHERALS: "Selectric" I/O typewriter bargains. World's largest selection. Send 25¢ for bargain-packed flyer. CFR, Box 144, Newton, NH 03858.

INTERACT COMPUTERS — Software, service. Best prices. Send for catalog: MICRO VIDEO, Box 7357, Ann Arbor, Michigan 48107.

SAVE 90% Build Your own Minicomputer. Free Details. Digatek, 2723 West Butler Dr., Suite 20C, Phoenix, AZ 85021.

USED COMPUTER TERMINALS. Printers, Modems, Surplus Electronic parts. Catalog \$1.00. RONDURE COMPANY, THE COMPUTER ROOM, 2522 Butler St., Dallas, TX 75235. (214) 630-4621.

300 LINES/MINUTE! Interface Any Parallel Port To Teletype M40 Printer. Plans \$7, Info \$2. AMD Services, 3815B Wild Rye, San Angelo, TX 76901.

OSBORNE 1 (64K) - \$1400. Atari 800 (16K) - \$742. Free Catalog. GENERAL COMPUTER, Box 345, Melbourne, FL 32901. (305) 777-5400.

SEVEN new unused mini-computer units. EACH includes color or display monitor, keyboard, disc drive, power pack, CPU, Diablo hi-type printer, more. CONSIDER any reasonable offer. CLAREMONT Colleges, 747 N. Dartmouth, Claremont, CA 91711. ATTN: R. Kemmerer.

GOLDCOAST COMPUTER CLUB! Thousands of programs free! Heath, TRS80, Apple FREE DETAILS. Box 181, Bremen, KY 42325.

COMMODORE COMPUTERS. Disk drives, printers. Call for low prices on latest models. 802-658-6908.

C.B. EQUIPMENT

GET MORE CB CHANNELS AND RANGE! Frequency Expanders, boosters, speech processors, how-to-books, plans, modifications. Catalog \$2. CB CITY, Box 31500PE, Phoenix, AZ 85046.

CABLE TV

500 PHILIPS 32 CHANNEL CABLE TV converters and VCR programmers. \$17,800 prepaid to your door. Sample \$48. Birnbom, 3655 Ridgewood, Suite 103, Montreal, Canada H3V 1B4. (phone 514-739-0614). (U.S. inquiries).



39⁹⁵
ADD \$2.50 FOR POSTAGE

30 CHANNEL CABLE TV CONVERTER

ORDER No. 198AE047

ETCO ROUTE 9N,
PLATTSBURGH, N.Y. 12901
Tel.: (518) 561-8700.

FREE!
UNUSUAL 96 PAGE
ELECTRONIC PARTS
& IDEAS CATALOG!

PLANS AND KITS

EXPERIMENTERS! Ten Digital and Audio Circuit Ideas — \$7.00. Free Kit catalog. Wavelength, 7 Bradford Ave., Pittsburgh, PA 15205.

FREE PHONE CALLS made daily by users of this simple electronic device. Report and detailed plans sold for information and education. \$5.00. DISTRIBUTORS MART, Box 333, Modena, NY 12548.

PRINTED CIRCUIT Boards from sketch or artwork. Kit projects. Free details. DANOCINTHS Inc., Dept. PE, Box 261, Westland, MI 48185.


LASERS HANDBOOK with burning, cutting, Ruby Reds, CO's complete plans, books, and parts. Send \$4.00 to: Famco, Dept. PE, Box 1902, Rochester, NH 03867.

GIANT SCREEN TV projection system converts any television into 7-foot picture. Lens & instructions \$14.95. (Dealers welcome). Bell Video, 4616 Belair Rd., Baltimore, MD 21206.

BUILD AN ORCHESTRA THE WE RSI WAY

Preview the world's most advanced Do-It-Yourself Organs, Planos, Synthesizers, Amps, etc. Send \$6.00 for our famous "Sight & Sound" pack.

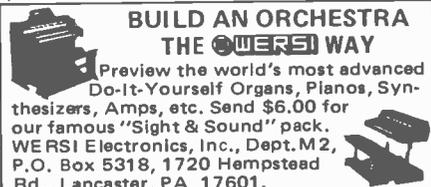WE RSI Electronics, Inc., Dept. M2,
P.O. Box 5318, 1720 Hempstead Rd., Lancaster, PA 17601.



UNIQUE TV DECODER plugs between UHF and VHF tuners on tube or solid-state sets. Plans \$3.95. DECODER ANTENNA receives multi-polarized signals. Plans \$3.95; Antenna Kit \$19.95. Helico, P.O. Box 304, Bridgewater, MA 02324.

GRANT CLOCK KIT Plans \$2.50. Microprocessor Trainer Plans \$5.00. Complete List of Kits and Products FREE. Paccom, 3928 148th N.E., Redmond, WA 98052.

PLANS - Monophonic Organ Synthesizer \$9.50. Kits available upon request. For information, SASE Mad 13, P.O. Box 6742, Concord, California 94524.

ROBOTIC CATALOG-MOTORS, gears, hardware, electronics, \$3.00. Newsletter, \$8.00/yr. MOUDY ELECTRONICS, R.D.2, Box 427-P, Hollidaysburg, PA 16648.

TESLA COIL RESONANT TRANSFORMERS. 50,000V - 5,000,000 volts, 520W - 3,000 kilowatts, Arcs - 100". Illustrated Construction manual includes: 5 Powerful coil plans (Tube, Sparkgap), 25 high-voltage high-frequency experiments, electrical theory, designing procedures, part suppliers. PLUS Nikola Tesla's Historical 100,000,000 volt standing-wave magnifying transmitter. Ball Lightning Production . . . Manual \$15.00. Information color photo \$2.00. B&L Scientific, 215 W. First St., Suite 105-47G, Tustin, CA 92680.

SUBSCRIPTION TELEVISION ON SYSTEMS SINE-WAVE DECODER, 2300 mhz MICROWAVE DOWN-CONVERTER best systems available. Plans \$10.00 each, both \$15.00. NEGATIVE ION GENERATOR, TELEPHONE MEMORY DIALER, Plans \$4.00 each. PCB patterns included. Parts, kits available. For more information, send \$1.00. COLLINS ELECTRONICS, Box 6424, San Bernardino, CA 92412.

RADAR ULTIMATE! Your unit will override reflections of other speed detection radars for 55 MPH indication. Complete plans \$10. D&S Research, P.O. Box 32592, Okla. City, OK 73123.

PROJECTION TV . . . Convert your TV to project 7 Foot picture . . . Results equal to \$2,500 projector . . . Total cost less than \$200.00. PLANS & LENS \$16.00. Illustrated information FREE. Macrocoma, Washington Crossing, Pennsylvania 18977. Credit card orders 24 hours. 215-736-3979.

PHONICS AUDIO KITS. Straightforward design, audiophile specifications and inexpensive! Catalog \$1.00. PHONICS, Box 55311, Indianapolis 46205.

FM STEREO TRANSMITTER KIT. Range up to 1/3 mile, broadcast quality, 30 dB separation, 300 mv input sensitivity. Tunes 88-108 Mhz, highly stable, 50 out. Requires +15V. Complete kit 89.95. MC/VISA (213) 506-0415. Free info, STELLATRON, 4942 Whitsett-205, N. Hollywood, CA 91607.

PROFESSIONAL LIMITER-COMPRESSOR-EXPANDER KITS: Pro specs and features, balanced input, adjustable threshold, slope (1:1 to 100:1), attack and release. Models from \$79 and up. Rack mounting available. Free Info. STELLATRON, 4942, Whitsett-205, N. Hollywood, CA 91607.

VARIABLE POWER SUPPLY DESIGN 5Amp, 5-30V, Technical Manual. \$4.50. Source Consultants, Dept PE-512, 250-2 South Orange, Escondido, California 92025.

ELECTRONIC KITS - Featuring NASA's Powerfactor Controller that saves up to 40% on your electric bill. All kits use highest quality glass boards. Easy to follow instructions, premium grade parts. RODCAR ELECTRONICS, 2720 Biloxi Lane, Mesquite, Texas 75150.

SATELLITE TV SYSTEMS — Where to buy quality at best prices. Send \$2.00, to Cayson Electronics Mfg. Co., 500 Exchange St., Tupelo, MS 38801.

ALARMS

BURGLAR, FIRE, CAR! Finest equipment! Save! Free Catalog, AAS, 186A Oxmoor Road, B'ham, AL 35209.

BURGLAR/FIRE ALARMS. Inexpensive. Install yourself. Send 50¢ for information. Multisystems, Box 80331, Baton Rouge, Louisiana 70898.

HIGH FIDELITY

DIAMOND NEEDLES and Stereo Cartridges at Discount prices for Shure, Pickering, Stanton, Empire, Grado, Audio Technica, Osawa, Satin and ADC. Send for free catalog. LYLE CARTRIDGES, Dept. P, Box 69, Kensington Station, Brooklyn, New York 11218. Toll Free 800-221-0906 9AM - 8PM except Sunday.

WANTED

GOLD, Silver, Platinum, Mercury, Tantalum wanted. Highest prices paid by refinery. Ores assayed. Free circular. Mercury Terminal, Norwood, MA 02062.

TUBES

RADIO & T.V. Tubes — 49 cents each. Send for free Catalog, Cornell, 4213 University, San Diego, Calif. 92105.

TUBES: "Oldies", Latest. Supplies, components, schematics. Catalog Free (stamp appreciated). Steinmetz, 7519-PE Maplewood, Hammond, Ind. 46324.

TUBES-RECEIVING, Industrial and Semiconductors Factory Boxed. Free price sheet including TV, Radio and audio parts list. Transletronic, Inc., 1365 39th St., Brooklyn, New York 11218. Telephone: (212) 633-2800. Toll free: 800-221-5802.

HUGE INVENTORY! Thousands of types. Wholesale prices. FREE CATALOG! ETCO Electronics, DEPT. 290, Plattsburgh, NY 12901.

GOVERNMENT SURPLUS

MANUALS for Govt Surplus radios, test sets, scopes. List \$1.00 (cash). Books, 7218 Roanne Drive, Washington, D.C. 20021.

JEeps — \$58.00!! — CARs — \$35.00!! — 700,000 ITEMS!! — GOVERNMENT SURPLUS!! — Most COMPREHENSIVE DIRECTORY AVAILABLE tells how, where to buy!! — YOUR AREA — \$3. — MONEYBACK GUARANTEE!! — "Surplus Information Services", Department GE-13, Box 99249, San Francisco, California 94109.

BUY DIRECT FROM GOVERNMENT! 500,000 items (including Jeeps) . . . low as 2¢ on dollar! Directory - \$2.00. Disposal, Box 19107-HI, Washington, DC 20036.

INSTRUCTION

UNIVERSITY DEGREES BY MAIL! Bachelors, Masters, Ph.D.'s. Free revealing details. Counseling, Box 317-PE09, Tustin, California 92680.

LEARN WHILE ASLEEP! HYPNOTIZE! Astonishing details, strange catalog free! Autosuggestion, Box 24-ZD, Olympia, Washington 98507.

LEARN ELECTRONIC ORGAN SERVICING at home. Completely revised course covers latest models including digital, LSI's, synthesizers, etc. NILES BRYANT SCHOOL, PO Box 20153, Sacramento, CA 95820.

PASS FCC EXAMS

The Original FCC Tests-Answers exam manual that prepares you at home for FCC First and Second Class Radiotelephone licenses. Newly revised multiple choice exams cover all areas tested on the actual FCC exam. Plus — Self-Study Ability Test. Proven! \$12.85 postpaid. Moneyback Guarantee.

Command Productions P.O. Box 26348-P
Radio Engineering Division San Francisco, CA 94126

MEDICAL ELECTRONICS TECHNOLOGY, home study. Troubleshoot medical instruments. WTI. P.O. Box 124, Pine-dale, CA 93650.

COLLEGE DEGREES BY SPECIAL EVALUATION of EXISTING Credentials & Job Experience. Fast. Inexpensive. (614) 863-1791. Guidance, Box 13151-A9, Columbus, Ohio 43213.

YOU CAN NOW EARN A Bachelor, Master, or Doctoral Degree without leaving home. Courses are under faculty guidance. Kensington University. (P.O. Box 2036-M), 512 E. Wilson, Glendale, CA 91209.

ATTENTION ELECTRONIC TECHNICIANS

Highly Effective Home Study BSEE Degree Program for Experienced Electronic Technicians Our New Advanced Placement Program grants Credit for previous Schooling & Professional Experience. Advance Rapidly! Our 30th Year!
FREE DESCRIPTIVE LITERATURE!
Cook's Institute of Electronics Engineering
DESK 15, P.O. BOX 20345, JACKSON, MS 39209

COLLEGE DEGREES - COURSES - AND DIPLOMAS by mail. Learn how to get an accredited College degree without leaving home. Inquire: Educom Service, 10315-PE, Woodley Ave., #111, Granada Hills, CA 91344.

PERSONALS

MAKE FRIENDS WORLDWIDE through international correspondence, illustrated brochure free. Hermes-Verlag, Box 110660/Z, D-1000 Berlin 11, W. Germany.

CORRESPONDENCE FOR FRIENDSHIP IN PHILIPPINES, MALAYSIA. Free information. AACCC-(PE), Box 1542, Canoga Park, Calif. 91304.

PENFRIENDS — ENGLAND — USA, through correspondence. Send age, interests. Free reply. Harmony, Box 89PE, Brooklyn, New York, 11235.

FOR INVENTORS

PATENT AND DEVELOP your invention. Registered Patent Agent and Licensed Professional Engineer. Send for FREE PATENT INFORMATION every inventor should have. Richard L. Miller, P.E., 3612-E Woolworth Building, New York, NY 10007. (212) 267-5252.

MANUFACTURER SEEKING Patented, Unpatented inventions. Generous royalties. Advantek International, 1100 17th NW, Washington, DC 20036.

INVENTORS Patent your invention. Free initial consultation. We are registered by the U.S. Government. VICTOR J. EVANS & CO., 4637 Eastern Ave., N.E., Washington, DC 20018. Since 1898.

INVENTIONS WANTED

FREE CONSULTATION • NO IDEA TOO SMALL

Disclosure registration Potential cash or royalties from manufacturers seeking new ideas for free information on how to register your ideas. Call or write.

AMERICAN INVENTORS CORP.

59 Interstate Dr. Dept PE
West Springfield, MA 01089 (413) 737-5376
A Free Based Service Company

BUSINESS OPPORTUNITIES

FREE CATALOGS. Repair air conditioning, refrigeration. Tools, supplies, full instructions. Doolin, 2016 Canton, Dallas, Texas 75201.

MECHANICALLY INCLINED individuals desiring ownership of Small Electronics Manufacturing Business — without investment. Write: BUSINESSES, 92-K9 Brighton 11th, Brooklyn, New York 11235.

ATTENTION — T.V. MEN/related fields! HI-PROFIT/LUCRATIVE. YOU can rebuild CRT's for \$3 to \$10 when you own our patented equipment. Lakeside, 4071 Elston, Chicago, IL 60618. (312) 583-6565.

MECHANICALLY INCLINED INDIVIDUALS

Assemble electronic devices in your home. Knowledge, or experience not necessary. Get started in spare time. Above average profits. \$300 - \$600/Wk possible. Sales handled by others. No investment — Write for free details.

ELECTRONIC DEVELOPMENT LAB

Box 1560PE, Pinellas Park, FL 33565

ERASE DEBTS with little-known law — create wealth!! Details FREE — Blueprints, No. EE9, LaGrangeville, NY 12540.

BORROW \$25,000 "OVERNIGHT." Any purpose. Keep indefinitely! Free Report! Success Research, Box 29070-GI, Indianapolis, IN 46229.

FREE BOOK "2042 Unique Proven Enterprises." Fabulous "unknowns," second inflation income. Haylings-M. Carlsbad, CA 92008.

MAILORDER OPPORTUNITY! Start profitable home business without experience or capital. Write for free book, case histories, plus complete details. No obligation. Mail Order Associates, Dept 524, Montvale, NJ 07645.

BORROW \$30,000 without interest! All eligible. Repay anytime. Free details. Infohouse, Box 1004, PE9, New York, NY 10003.

WANT YOUR OWN RADIO STATION? Investment/experience unnecessary. Free information. "Broadcasting", Box 130-A9, Paradise, CA 95969.

SPARE TIME FORTUNE in Vinyl Repair. Huge demand creates exceptional profits. We supply everything. Details free. VIP, 2012 Montrose, Chicago, IL 60618.

\$700 PER MONTH EARNINGS possible filling out income tax forms at home or tax office during tax season. We show you how. Simple, quickly learned. Details mailed free. No salesmen. Hurry. Big demand. Federated Tax, 2012 Montrose, Chicago, IL 60618.

HAVE YOUR OWN BUSINESS! Unlimited growth! No experience necessary! Details \$1.00 to F.L.G.S., 8665 Mission Gorge Road, Bdg. C-1, Santee, CA 92071.

EVERYTHING YOU ALWAYS WANTED TO KNOW but could never find out about the hottest most profitable businesses around. Complete report pinpoints the very best small business opportunities for 1982. Research manuals provide complete details . . . facts . . . figures INCLUDING WHAT YOU CAN EXPECT TO MAKE! For complimentary reports, write: ENTREPRENEUR, 2311 Pontius Ave., Suite E651, L.A., CA 90064.

300% PROFIT on 2500 products. Send \$2.00. REFUNDED. Anthony Cole, River Road, Biddeford, Maine 04005.

PROJECTION TV . . . Make \$200.00+ per evening assembling Projectors . . . Easy . . . Results equal to \$2,500 projectors . . . Your total cost less than \$15.00 — PLANS, LENS & Dealers Information \$14.00 . . . Illustrated information FREE . . . Macrocomax, Washington Crossing, Pennsylvania 18977. Creditcard orders 24 hours 215-736-2880.

AMUSEMENT Centres — Electronic Beat inflation and earn \$40,000+ + in 12 months. Proven facts!! A complete up to date start-up manual on how to start & succeed easily with very little investment. Satisfaction guaranteed. Send only \$7.95 cheque or money order to: = House of Mailorder, One St. Clair Ave.E., Dept E., Toronto Ontario, Canada M4T 2V7.

REPAIRS & SERVICES

TV TUNER REPAIR KIT. Alignment tools & cleaner repair men use. \$7.95 complete instructions. JW Electronics, Box 51B, Bloomington, IN 47402.

REAL ESTATE

BIG . . . NEW . . . FREE FALL CATALOG! Over 2,800 top values coast to coast! UNITED FARM AGENCY, 612-EP West 47th, Kansas City, MO 64112.

RUBBER STAMPS

RUBBER STAMPS, BUSINESS CARDS. Many new products. Catalog. Jackson's, E-100, Brownsville Rd., Mt. Vernon, Ill. 62864.

BOOKS AND MAGAZINES

ELECTRONIC MUSIC and home recording in Polyphony magazine. Advanced applications, interviews, projects, computer music. Sample \$2.00. Subscription (6 issues). \$12.00 US/\$14.00 foreign. POLYPHONY, Box P20305, Okla. City, OK 73156.

LEARN HOW TO FORM, Finance, and operate virtually any type business. Send \$3.00 to: Information, Box 11215N, Fort Worth, Texas 76110.

LOTTERIES make some people millionaires, so can micro-computers. New publication shows how. \$5.00. NEO PUBLISHING, P.O. Box 1368, L.I.C., NY 11101.

FREE CLASSIFIED AD WITH SUBSCRIPTION! Thousands of electronic items for sale or trade each month. Only \$5.00 (in U.S.) to Nuts & Volts, POB 1111-P, Placentia, CAL 92670.

CALCULATOR POWER! Write NOW for free catalogue of calculator related books. Educalc, 27963A Cabot Road, So. Laguna, CA 92677.

EMPLOYMENT OPPORTUNITIES

ELECTRONICS/AVIONICS EMPLOYMENT OPPORTUNITIES. Report on jobs now open. Details FREE. Aviation Employment Information Service, Box 240E, Northport, New York 11768.

JOBS OVERSEAS - Big money fast. \$20,000 to \$50,000 plus per year. Call 716-842-6200, ext. 1740.

NATIONWIDE listings of major companies actively employing ENGINEERS and TECHNICIANS. AVI, Box 264P, Buffalo, NY 14215.

MUSICAL INSTRUMENTS

MUSICAL INSTRUMENTS' HOT LINE! Incredible prices: Amps, PA gear. All instruments. Huge selection. Sam Ash, established 1924. 800-645-3518. NYS: (212) 347-7757.

MOTION PICTURE/VIDEO

VIDEOTAPES - 8MM/16MM MOVIES. TWO 72 page catalogs \$1.00. Both \$1.50. Reelimages, Box 137-PE, Monroe, Connecticut 06468.

VIDEO CASSETTE RENTALS AND SALES. All ratings. BLANK TAPES, VIDEO games, COMPONENTS, BEARCAT Scanners. Write: 20/20 VIDEO, Dept E, Box 60132, Chicago, IL 60660.

AMATEUR RADIO

RADIO AMATEUR CALLBOOKS Directories of Radio Amateurs around the world. Write for FREE catalog. Radio Amateur Callbook, Dept. PE, 925 Sherwood Dr., Lake Bluff, IL 60044.

PLAY YOUR TAPES, records, T.V. on any F.M. radio in your house - wireless - simple hook-up. Satisfaction guaranteed. \$24.95. Port-o-Sound Co., Box 279A, Howard Beach, NY 11414.

DO-IT-YOURSELF

PRINTED CIRCUIT Boards with running water! Technological breakthrough. Precise reproduction. Ideal for beginners. Free info. COVAL, Dept. PE9, 2706 Kirby, Champaign IL 61820.

PATENT INVENTIONS YOURSELF. Free examination 100 page book. Pay \$5.00 later if satisfied. Send name, address: "DO-IT-Yourself Patent Guide-PEY," P.O. Box 2774, Pittsburgh, PA 15230.

SAVE \$\$\$! Satellite Television Manual. Source Catalogue. Dishes, receivers, complete systems. Design, programming. Illustrations, photos. \$4.95. Westcolony, Dept-D, Box 9471, Fresno, CA 93792.

WELDING ALUMINUM? It's easy with the LUMIWELD Process. Designed for "Do-It-Yourselfers". Joins Aluminum to Copper. No special skills or expensive equipment. Money-back guarantee. For details: Send S.A.S.E. Dept. PE, ALUMISMITHS Inc., P.O.B. 517, DeLand, FL 32720. Featured in Pop. Sci. March, 1980.

PROFESSIONAL GIANT SCREEN PROJECTION TV... Don't be fooled by cheap imitations... Build the best!... Simple Construction!... FREE information!... POLI-VISION, 168E Dunmore St., Throop, PA. 18512.

HYPNOTISM

FREE Hypnotism. Self-Hypnosis. Sleep Learning Catalog! Drawer H400, Ruidoso, New Mexico 88345.

MISCELLANEOUS

MPG INCREASED! Bypass Pollution Devices easily. REVERSIBLY!! Free details - Posco GEE9, LaGrangeville, NY 12540.

CHESTER THE CHIP! The "PET" IC! Complete story why he joined the circuits. Care, feeding instructions too. Lots of laughs. Only \$1.99 while supply lasts. Maudko, 524 Montana, Havre, MT 59501.

AUTOMOBILE RE-TUNING For maximized economy. Details free! Techneering, Box 12191DD, Norfolk, VA 23502.

psychology today CASSETTES

PSYCHOLOGY TODAY offers a free catalog which includes a complete up-to-date listing of cassettes available. These tapes feature leading authorities who share their ideas and findings on a wide range of important topics in all areas of the behavioral and social sciences. To obtain the Psychology Today Cassette catalog. FREE-OF-CHARGE, write to: CASSETTE CATALOG, P.O. Box 278, Pratt Station, Brooklyn, N.Y. 11205.

Popular Electronics

ADVERTISERS INDEX

RS no.	ADVERTISER	PAGE no.
2	Albia Electronics	43
3	All Electronics Corp.	100
4	American Antenna	30
5	Antenna Specialists	93
7	AP Products	88
6	Apple Computer	Cover 2, 1
8	Arkon Electronics	108
9	Audiomatic	98
10	Audio-Technica	101
11	Bach Co.	102
13, 14	Belsaw	100, 101
15	BSR (USA) Ltd.	33
	Classified Advertising	118-121
	Cleveland Institute of Electronics, Inc.	34-37
1	Communications Electronics	96
16	Components Express	92
17	Compuque	108
12	Cooper Group	25
18	Crown International	8
19	DAK	9
74	DBX	38
21	Digi-Key Corp.	109
23	Discwasher	2
73	Downlink	20
64	Dynascan	Cover 3
24	EICO	69
76, 77	Electronic Buyers Club	114, 115
25	Electronic Specialists	102
27	Epson	42
28	Escotch	97
29	ETCO	87
30	Firestik	102
22	Fluke	5
31	Gladstone	82, 83
33	Global Specialties	74
34	Godbout Electronics, Bill	116
	Grantham College of Engineering	102
35	Hardside	94
20, 37	Heath Co.	6, 7, 29, 80
38	Illinois Audio	108
39	Imsai	98
40	Integrated Circuits	107
42	Jameco Electronics	110, 111
43	JDR Microdevices	112, 113
44	J&R Music World	14
	JS & A National Sales	11, 13, 15
46	Koss Corp.	Cover 4
69	Live Via Satellite, Inc.	103
47, 48	Maxell	26, 56
51	MFJ Enterprises	98
	Micro Ace	50
	McGraw-Hill	70-73
52	McIntosh Laboratory, Inc.	97
	MICROCOMPUTER MART	117
49	Micro Management Systems	117
71	M & M Electronic Sales	48
	Nabih's	69
53	National Guard, Army	22
	Natl. Technical Schools	52-55
	Netronics, R & D Ltd.	45, 91
	NRI Schools	16-19
55	Olympic Sales	95
	Omega Sales Corp.	60
56, 57	Poly Paks	95, 100
45	Prentice Hall	65
59	Quest Electronics	116
	Radio Shack	41
60	Sams Books	86
61	Scientific Systems	103
	Scorpio	92
62	Shop Smith	44
26	Shure Bros.	23
70	Simple Simon Kits	103
	Sunshine Express	51
50	Tab Books	49
66	Tams	94
	Thandar	66
54	3-M	3
75	Trio-Kenwood	99
68	Wabash Tape	24

CLASSIFIED ADVERTISING ORDER FORM

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (MINIMUM)
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35
36	37	38	39	40
41	42	43	44	45
46	47	48	49	50

Please refer to heading on first page of this section for ad placement information:

COMMERCIAL: \$3.00

OF WORDS _____ # OF INSERTIONS _____

PAYMENT ENCLOSED \$ _____

CHARGE: You will be billed monthly. American Express Diners Visa MasterCharge-Interbank # _____

Account # _____ Exp. Date _____

SIGNATURE _____

PRINT NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

PE-981

ELECTRONICS WORLD®

Personal Electronics News

MUSIC, DANCE, AND OPERA video cassettes have been introduced by Dubs Video Corp. (New York, NY). Called "Kultur," the first releases include artists such as Jascha Heifetz, Marian Anderson, and the Bolshoi Ballet. Future cassettes will continue emphasis on opera, classical music, and dance. Price per cassette is in the range of \$69.95

CLEAN-ROOM REPAIR SERVICE FOR WINCHESTER DRIVES is available at four locations of Shugart Associates: Hudson, MA; Milpitas, CA; Dallas, TX; and Munich, W. Germany. With what it calls its "under-the-bubble" service, Shugart can unseal the drive's media chamber and read/write head assembly and make repairs, using a complete inventory of spare parts. The repair turnaround goal is 30 days maximum.





A UNIFIED APPROACH TO VIDEOTEX STANDARDS has been taken by 26 European countries, members of the European Conference on Posts and Telecommunications. The new basic alpha-mosaic system has a high degree of compatibility with existing British, French and German systems and will be able to receive serial and parallel transmission codes, not requiring a space on the screen when attributes change. Additional features include: sixteen colors, full-screen background color, black foreground color, double-width characters, and underlining. The alpha-mosaic viewdata display system is one of two internationally recognized systems—the other being alpha-geometric. In the former, displays are created from a mosaic of dots, while the latter uses geometric lines, arcs, and circles.

COMPUTER PROGRAMS VIA SHORTWAVE RADIO will be part of an experimental broadcast by Radio Netherlands (Dutch External Service) on Thursday, September 10. The broadcast will include, in English, an introduction to microcomputing and short computer program in three machine-readable formats compatible with Radio Shack's TRS-80, Apple, and Commodore PET computers. If the signal strength is sufficient in the listener's area, the station hopes that the program can be recorded off the air onto cassette tape and played back on a home computer. If the experiment is successful, the idea may be repeated on a regular basis. The broadcast, which will be on the program "Media Network" and last 30 minutes, will be beamed to Eastern North America at 10:47 EDT on 9,490 and 6,165 kHz, and to Western North America at 10:48 PDT on 9,715 and 6,165 kHz. Listeners who hear the broadcast and try the computer program are invited to report their results to: Computer Experiment, Media Network, Radio Netherlands, Box 222, 1200 JG Hilversum, Holland.

A NEW SOLDER FLUX HAS BEEN DEVELOPED to replace natural rosin by Multicore Solders (Westbury, NY). The new material (XERSIN) is claimed to leave residues that are much less corrosive than rosin flux and that need not be removed from a pc board after soldering. Fluxing action, however, is said to be comparable to and compatible with rosin. In addition, fumes resulting from soldering are claimed to contain no aldehydes and are reduced to meet current industry standards.

DOW JONES ADDS WALL STREET NEWS TO COMPUTER SERVICE. In July, the Dow Jones News/Retrieval Service started to deliver transcripts of the half-hour PBS TV program "Wall Street Week," hosted by Louis Rukeyser. Cost to subscribers, who receive business and financial news on command through standard time-sharing terminal or personal computers, is 50 cents per minute during business hours and 25 cents per minute evenings and weekends. Transcripts of the program will be available the Thursday following broadcast, and three previous programs will also be retained in the system.

ROBOTS THAT CAN INTERPRET what they "see" are the subject of a project at the University of Southern California at Los Angeles. Scientists there are preparing computer "brains" for "seeing eye" robots that may soon be performing precision work in military aircraft and space-exploration vehicles. Currently, they are using the robots to perform such image-enhancing tasks as taking the blur out of space exploration photographs, improving the quality of medical x-rays and 3-D brain and body scans, and deciphering fuzzy license plate numbers and other photographic clues for law enforcement.

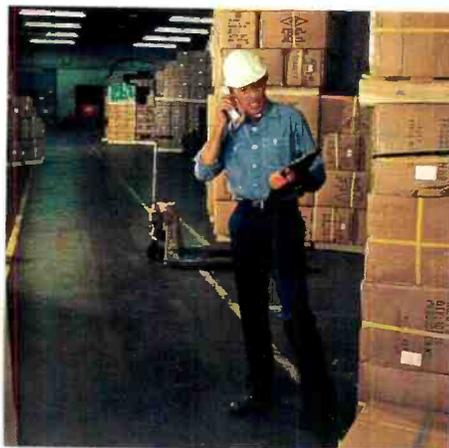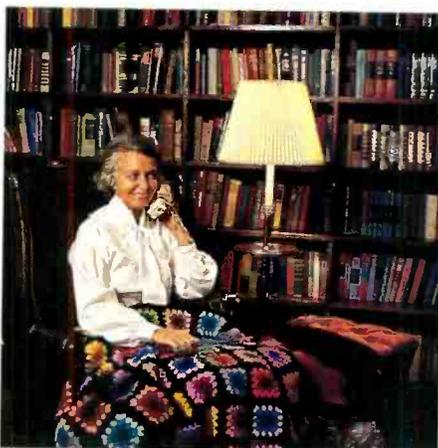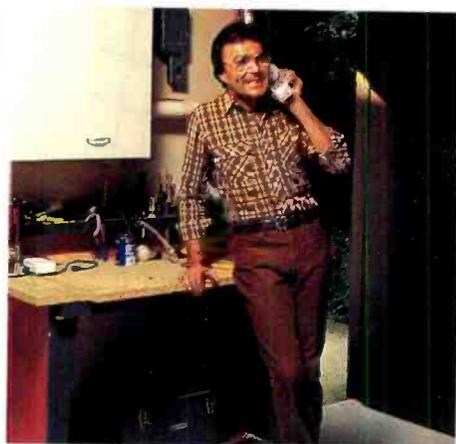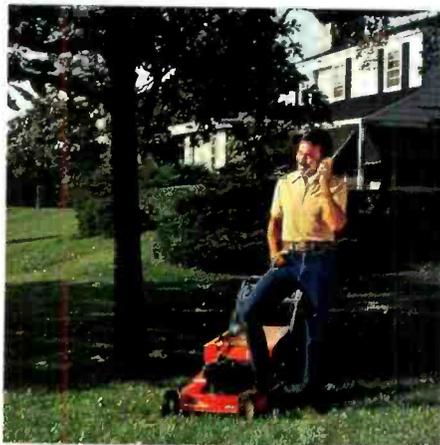

Now—anyone can afford to stay in touch— with the newest Cobraphone...

It goes wherever you go—indoors or out—and makes sure you receive calls you might otherwise miss...

With this new economical Cobraphone cordless extension phone, you can stay in touch for less than \$100.00! And you can use it anywhere in and around your home or even at your neighbors.

Uses for the new Cobraphone are limited only by your imagination: on the patio or at poolside; in the yard, garage, or basement; in the sick-room, by recuperating patients or invalids; in a warehouse or on a construction site. Also use it while watching TV—take calls without leaping up from your favorite chair. Or leave it at your next door neighbor's home, so they can answer your phone while you're away—a great aid to home security!

You'll marvel at the outstanding quality of voice communications on your Cobraphone. That's because Cobra's famous power and quality make sure conversation is "loud and clear" with your Cobraphone—as with Cobra CB radios. And it



features the same full FM duplex system found on all Cobraphones: talk and listen as you would with a conventional phone—no annoying push-to-talk buttons.

The CP-15S installs in seconds: just plug into the nearest AC outlet and phone jack. That's all there is to it!

So visit your favorite retail, department or electronics specialty store today. Ask to see the full Cobraphone line. Then take home your choice and enjoy all your activities—and still be in touch with everyone—anywhere in the world.

Write for free color brochure.


Cobraphone®

Conversation Loud and Clear

Cobra Communications Product Group
DYNASCAN CORPORATION
6460 W. Cortland St. Chicago, Illinois 60635

CIRCLE NO. 64 ON FREE INFORMATION CARD

KOSS FIRE



Finally, there's a speaker that lives up to its promise. The Kossfire dual tweeter loudspeaker system.

It's about time a speaker at a reasonable price lived up to its promise. Not just in the bass and midrange. But in the all-important treble range where power handling really counts. That's why we've designed the Kossfire/210 loudspeaker with not only a 12-inch woofer and a 5-inch midrange, but also with unique dual Kossfire tweeters that double the power handling capability over the high frequency range while virtually eliminating distortion. By placing the Kossfire dual tweeters in the optimum geometric alignment, we've created an ideal horizontal listening plane that's remarkable in its wide and uniform dispersion characteristics. The result is an exciting 4-driver speaker system that won't make you choose between the high road and the low road. And that's a promise!

But then, the Kossfire/210 loudspeaker

has a lot of very promising things going for it. There's a linear phase constant voltage crossover network for seamless transition between drivers. There's a built-in circuit breaker that automatically resets so no fuses are necessary. There's a vertical alignment of woofer, midrange and tweeter array for perfect stereo imaging. And there are separate continuous level controls for midrange and treble response ranges. Not to mention, the Kossfire's beautiful pecan-veneer cabinet.

All in all, these 4-driver Kossfire speakers were created to fill the void between loudspeakers that cost too much and those that promise too much and deliver too little. The superb performance of Kossfire speakers will amaze you. But then, so will their price. And that's a promise!

© 1980 Koss Corp.

KOSS® Stereophones / Loudspeakers / Digital Delay Systems
hearing is believing®

INTERNATIONAL HEADQUARTERS 4129 N. Port Washington Avenue, Milwaukee, Wisconsin 53212 Facilities: Canada, France, Germany, Ireland

CIRCLE NO. 46 ON FREE INFORMATION CARD

AmericanRadioHistory.Com