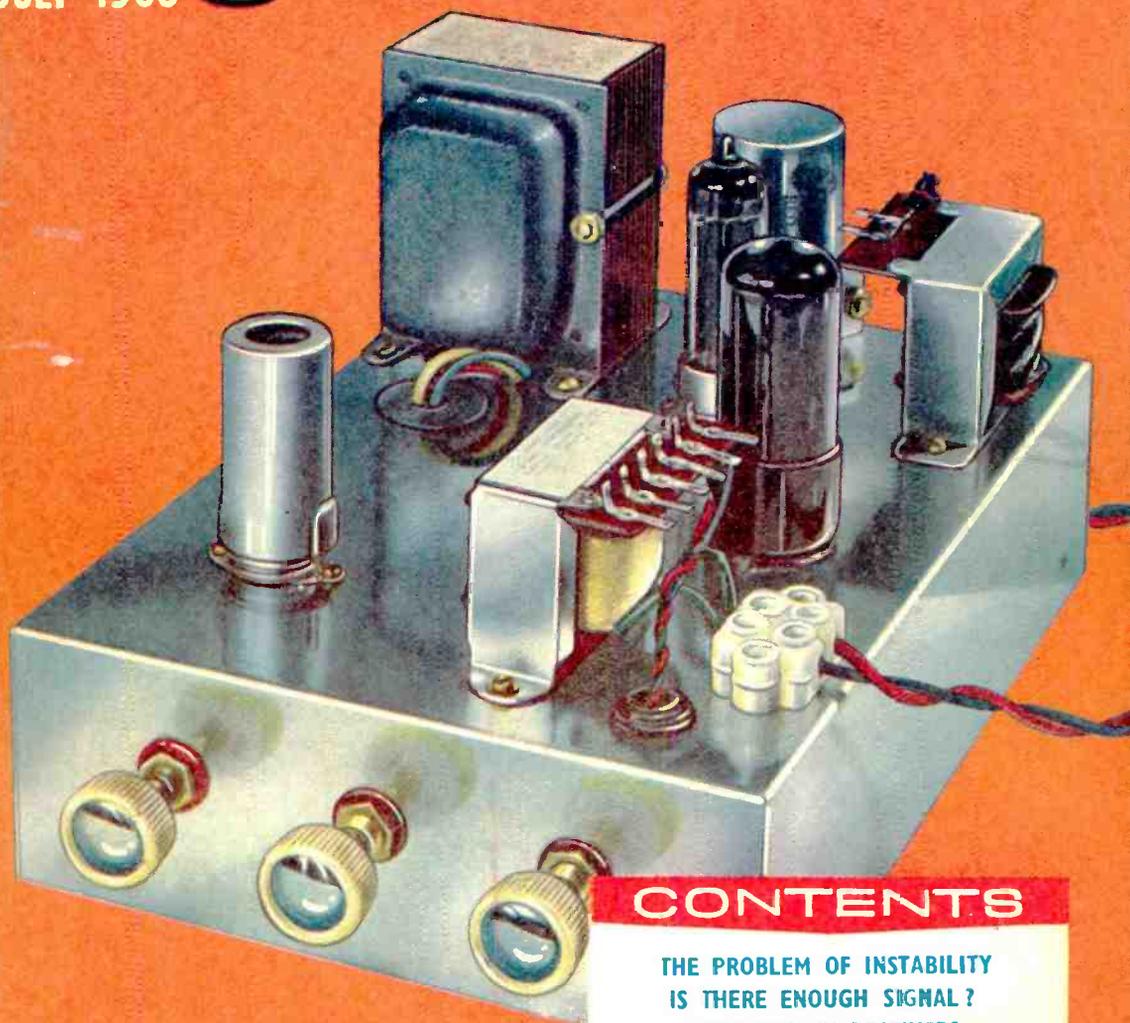


ADD-ON SOUND UNIT

Practical Television ¹⁶

JULY 1960 AND TELEVISION TIMES



CONTENTS

THE PROBLEM OF INSTABILITY
IS THERE ENOUGH SIGNAL?
SERVICING TV RECEIVERS
TWO-BAND PRE-AMP
YOUR PROBLEMS SOLVED
ETC. ETC. ETC.

Introducing

THE NEW **SAPPHIRE** REBUILT TUBE

The Result of Research

**A NEW GUN IN EVERY TUBE—BUY DIRECT FROM THE FACTORY
NOW 18 MONTHS' GUARANTEE**

12 inch £6-0-0

14 inch £6-10-0

15, 16 & 17 inch £7-10-0

£1 REFUNDED ON RECEIPT OF YOUR OLD TUBE
Carriage and insurance 10/6 extra

★ SPECIAL TERMS TO THE TRADE

ELECTRONIC MAINTENANCE SERVICES

*131 St. Ann's Road, Tottenham, London, N.15.
Telephone Stamford Hill 3267, 5555.*

Multi-Purpose VALVE FILAMENT TESTER Model VT4I



- Pocket size
- Battery operated

GIVES INSTANT CHECK OF:

- ★ All TV and Radio Valves and Fuses.
- ★ All pilot lamps.
- ★ Circuit Continuity.
- ★ Built-in 7 and 9 pin valve straighteners.
- ★ Built-in Battery Test.

With this revolutionary instrument you can test all current Valves, Fuses, Continuity and other radio parts. All components tested are shown "good" or "faulty" on panel indicator

Finished in black hammer case with gold front panel. Complete with internal batteries, full instructions, and ready for use

30/-

From your local dealer or if in difficulty order direct

EAGLE PRODUCTS (Dept. P.T.4.)
EAGLE WORKS, COPTIC ST., LONDON, W.C.1.

ERSIN MULTICORE SOLDERS

for a first class joint every time

Ersin Multicore contains 5 cores of extra-active, non-corrosive Ersin Flux. Prevents oxidation and cleans surface oxides.

SIZE 1 CARTON 5/-



HANDYMAN'S CARTON

Suitable for 200 average joints. **60.**

HOME CONSTRUCTORS 2/6 PACK

In addition to the well-known Home Constructors Pack (containing 1 lb. of 18 s.w.g. 60/40 alloys) a similar pack is now available containing 40 lb. of 22 s.w.g. 60/40 alloy especially suitable for printed circuits.



Wherever precision soldering is essential, manufacturers, engineers and handymen rely on MULTICORE. There's a MULTICORE SOLDER just made for the job you have in hand. Here are some of them.

SAVBIT TYPE 1 ALLOY

A specially formulated alloy to reduce the wear of soldering iron bits. Contains 5 cores of non-corrosive Ersin Flux and is ideal for all soldering purposes.



SIZE 1 CARTON 5/-

Available in three specifications

BIB WIRE STRIPPER AND CUTTER

Strips insulation without nicking wire, cuts wire cleanly, splits extruding die. **3/6 each**




MULTICORE SOLDERS LTD.,

MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS. (BOXMOOR 3636)

7-VALVE AM/FM RADIOGRAM CHASSIS

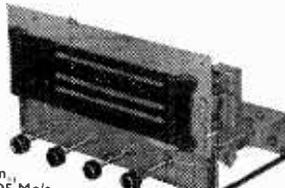Valve Line up:
ECC85, EC81,
EF89, EABC80,
EL84, EM81, E280.



3 wave band and switched gram positions. Med. 200 m.-500 m., Long 1,000 m.-2,000 m., VHF/FM 88-95 Mc/s.
4 Controls. Vol., On-off, Tone, Tuning, Wavechange. P.U., Ae. and E., and speaker sockets. Magic eye tuning. Philips continental tuning insert with permeability tuning on FM, and combined AM/FM IF transformers, 460 Kcs/s and 10.7 Mc/s. Dust core tuning all coils. Latest circuitry, including AVC and Neg. Feedback. 3 watt output. Sensitivity and reproduction of a very high standard. Chassis size 13 1/2 in. x 6 1/2 in. Height 7 1/2 in. Edge illuminated glass dial 1 1/2 in. x 3 1/2 in. Vertical pointer, Horizontal station names, gold on brown background. A.C. 200/250 v. operation.

£13.10.0 Carr. and Ins. 5/-. Complete with 4 knobs walnut or ivory to choice

As previously announced fresh supplies are now being received, but we regret some slight delay may be experienced in fulfilling orders for this popular item.

RE-GUNNED TV TUBES

New Reduced Prices!

And now 12 months' Guarantee!

12in.	£6.00	37in.	£8.10.0
14in.	£7.00	21in.	£10.10.0
15in.	£7.10.0		

All tubes Rebuilt with new Heater Cathode and Gun Assembly—reconditioned virtually as new! Full 6 months' unconditional Guarantee. As used by our own Service Dept. Comprehensive stocks—quick delivery. 10/- part exchange allowance on your old tube.

RECORD PLAYER CABINETS

Contemporary styled, rexine covered cabinet in fawn and brown or mottled red with white polka dot. Size 18 1/2 x 12 1/2 x ht. 8 1/2 in. Fitted with all accessories, including baffle board and anodised metal feet. Space available for all modern amplifiers and auto changers etc. Uncut record player mounting board 14 x 13in. supplied.

£33.3.0



2-valve AMPLIFIER Mk.2

Latest developed circuit giving a higher fidelity response and greater output (2-3 watts) using twin stage valves ECL82 and neg. feedback Tone Control. Complete with knobs etc., wired and tested ready to fit in above cabinet.

ONLY £2.17.8. P. & P. 1/-.

6in. speaker and matching transformer, 22/-, P. & P. 1/6.

SENTROEL RECTIFIERS. E.H.T. Type Fly-back Voltages, K3/252 3 kV., 6/-; K3/40 3.2 kV.; 8/8; K3/45 3.1 kV., 7/3; K3/50 4 kV., 7/9; K3/100 8 kV., 13/6. MAINS TYPES—RM1, 125 v. 60 mA, 4/8; RM2, 125 v. 100 mA, 5/8; RM3, 125 v. 120 mA, 7/8; RM4, 250 v. 250 mA, 16/-; RM4B type 270 mA, 17/6; RM5, 250 v. 300 mA, 21/-.

SPEAKER FRET.—Expanded Bronze anodised metal 8 x 5in., 2/3; 12 x 5in., 3/-; 12 x 12in., 4/6; 12 x 15in., 6/-; 24 x 12in., 9/-, etc. Listed above are only a few items from our very large stock. Send 3d. stamp today for Complete Bargain List.

FULLY GUARANTEED VALVES NEW REDUCED PRICES

1R5, 1T4 7/8	DAF98 9/-	EF80 9/8	PCF92 10/8
185 7/8	DF96 9/-	EF86 13/6	PCL83 12/6
384, 3V4 8/1	DK96 9/-	EF91 8/6	PL81 12/6
5Z4 9/8	DL96 9/-	EL41 10/8	PL82 9/6
6K7 5/6	EABC80 9/8	EL84 9/8	PL83 11/8
6K8 8/6	EM81 9/6	EM81 9/6	PF30 7/6
6Q7 8/8	ECC83 9/6	EY61 10/-	PY81 9/6
6SN7 8/8	ECC84 10/6	EY86 10/-	PY82 7/6
6V8 7/8	ECC80 11/6	EZ80 7/8	PY83 10/8
6X4 7/8	ECP82 11/6	EZ81 7/8	U25 12/6
7C5 9/-	EC81 10/8	MU14 9/8	U191 12/6
7Y4 8/8	ECL80 10/6	PC84 10/6	UCH42 10/8
35L6 9/8	ECL82 11/6	PCF50 10/8	UP41 10/-

Send for List of more Valve Bargains.

SPECIAL PRICE PER SET

1R5, 1T4, 185, 384 or 3V4	£7/8
DK96, DF96, DAF96, DL96	35/-
6K8, 6K7, 6Q7, 6V8, 5Z4 or 6X5	35/-

COAX 80 OHM CABLE. Stand

4in. diam. Low Loss Semi-Air Spaced Aerialax. Top grade cable—not to be confused with inferior types.

SPECIAL REDUCED PRICES
20 yds. 12/6. p. & p. 1/8; 60 yds. 22/6. p. & p. 3/-; 40 yds. 22/6. p. & p. 2/6; All other lengths 8d. per yard.
Coax Plugs 1/-, Sockets 1/-, Complers 1/3, Cable End Sockets 1/8. Outlet Boxes 4/6.

TRANSISTOR 'ONE-WATT' AMPLIFIER


6 v. Battery operated

Latest Push-Pull, 4 Transistor circuit giving full 1 watt output into standard 3 ohms speaker. Good sensitivity and improved freq. response. Neg. feedback. Var. Tone and Volume Controls. Chassis Size 6 1/2 in. x 3 1/2 in. x 1 1/2 in. Current consumption 10 mA quiescent—250 mA at 1 watt. 2 matched GEC GET15 Transistors... 42/- pr. 2 GEC GET3 Transistors... 21/- pr. Driver Trans. 5/8 Output Trans (to 3 ohms)..... 10/8 Complete Kit of Parts incl. circuit etc. less speaker. ONLY 99/6 P. & P. 2/8.

Circuit and instruction booklet 1/6 post free.

VOLUME CONTROLS

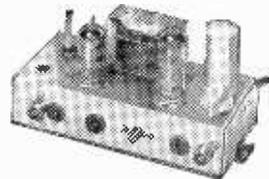10,000 ohms—2 Megohms. All long spindles. Morganite Midget type, 1 1/2 in. diameter. Guar. 1 year. Log or Lin. Ratios. Less Sw. 3/-. D.P. Sw. 4/8, Twin (ganged) controls, 1 meg., 1 meg., 1 meg., less Sw. 8/8 ea.



BAND 3 TV CONVERTER

All channels 7-13 (180-205 Mc/s). Mk. 2 Model. Latest cascade circuit using ECC84 and EF80 valves. 18db gain over standard circuits. Built-in Power Supply 200-250 v. A.C. Size 6 1/2 in. x 3 1/2 in. x 4 in. Simple to fit—only external plug-in connections. Wired and aligned ready to use. Only 79/6, p. & P. 2/8.
B1-B3 changerover Sw. and BBC Aerial Socket fitted and wired, 8/- extra.
Band 3 Aerials. Single Dipole with 4 yds. cable, 13/8, 3 Element Beam, 25/-, 5 Element, 32/6, etc. B1-B5 Crossover Units, 7/6.

RECORD PLAYER BARGAINS

NEW RELEASE by E.M.I.—4-speed Single Player Unit fitted with latest stereo and monaural Xtal cartridge and dual sapphire styli. Auto stop and start. A fidelity unit and bargain buy at only £8.19.6.
BSE—UAS Model.—4-speed autochanger with crystal turnover cartridge, etc., wired for stereo. Bargain £8.19.6.
Garrard—Latest RC121/D/Mk. 2—fitted with GCS Xtal cartridge, plug-in monaural head. Auto/manual selector, etc. The connoisseur's choice for audio perfection. Bargain 10 gns.
Plug-in stereo head GCS/10, £2 extra.
All above are brand new, fully guaranteed models. Carr. and Ins. 4/8.
Comprehensive bargain range of Collaro, BSE and Garrard Units in stock. Send for comprehensive bargain lists.

C.R.T. Heater Isolation Transformers

New Improved types—mains prim. 200/250 v. tapped.

All Isolation Transformers now supplied with alternative no boost plus 25%, and plus 50% boost taps, at no extra charge.
2 v. .. 2A type 12/6 (P. & P. 1/8)
6.3 v. .. 6A .. 12/6 ..
10.5 v. .. 3A .. 12/6 ..
13 v. .. 3A .. 12/6 ..
Other voltages available at some prices.
Small size and tag terminated for easy fitting.

JASON FM TUNER UNITS

(87-105 Mc/s)

Designer-approved kits of parts for these quality and highly popular tuners available as follows:
STANDARD MODEL (FMT)—as previously extensively advertised. COMPLETE KIT, 5 gns. post free. Set of 4 spec. valves, 30/- post free.
LATEST MODEL (FMT2)—attractively presented shelf mounting unit to enclosed Metal Cabinet with Built-in Power Supply. COMPLETE KIT, £7, p. & p. 3/8. Set of 5 spec. valves, 39/6.
NEW JASON COMPREHENSIVE F.M. HANDBOOK, £2/6 post free. 48 hr. Alignment Service, 7/6, p. & p. 3/6.

TYGAN FRET (Murphy pattern) 12 x 12in., 2/-; 12 x 18in., 3/-; 12 x 24in., 4/-, etc.

SPEAKERS P.M. 3 ohm 2 1/2 in. Elac, 18/6. 3 1/2 in. Goodmans, 17/6. 5in. K. & A., 17/8. 6in. Celestion 18/8. 7 x 4in. Goodmans, 18/6. 8in. Rola, 20/-, 5in. Special Cone G'mans, 21/8. 10in. R. & A., 25/-

Terms: O.W.O. or O.O.D. Kindly make cheques, P.O.s etc., payable to T.R.S. Post/Packing up to 4lb. 7d. 1lb. 1/1, 3lb. 1/6, 5lb. 2/-, 10lb. 2/8.

Hours: 9 a.m.—6 p.m. 1 p.m. Wed. Open all day Saturday.

RADIO COMPONENT SPECIALISTS (Est 1946)

70 BRIGSTOCK ROAD, THORNTON HEATH, SURREY (THO 2188)

50 yards Thornton Heath Station.

Buses: 130A, 133, 159, 166 and 190

SPECIALIST IN THE SUPPLY OF NEW VALVES, TRANSISTORS, AND GERMANIUM DIODES

BENTLEY ACOUSTIC CORPORATION LTD.

38 CHALCOT ROAD, CHALK FARM, LONDON, N.W.1.

Telephone: PRIMROSE 9090

EXPRESS POSTAL SERVICE! ALL ORDERS DESPATCHED SAME DAY AS RECEIVED. FOR ONLY 2/6 EXTRA TELEPHONE FOR THAT URGENT ORDER TO BE DESPATCHED IMMEDIATELY BY OUR SPECIAL C.O.D. SERVICE.

OA2	17/6	6C10	9/-	7D6	10/6	25Z4G	9/6	CL33	19/3	ECH3	26/6	HL23DD	PL36	12/-	U339	16/7	X101	33/2
OB2	17/6	6CD6G	36/6	7D8	23/3	25Z5	9/6	CV63	10/6	ECH21	23/3	PL38	26/6	U403	16/7	X109	17/3	
OZ4	5/-	6C6E	9/-	7D7	8/-	25Z6G	10/-	CY1	18/7	ECH35	9/6	HL41	12/6	U404	8/6	XD(1.5)	6/6	
IA3	3/-	6D3	19/11	7R7	12/6	27SU	19/11	CY31	16/7	ECH42	9/-	HL41DD	PL82	7/6	U401	29/10	XFG1	18/-
IA5	6/-	6D6	6/6	7S7	9/6	28D7	7/-	DI	3/-	ECH81	9/-	PL83	9/-	U402	16/7	XYF12	9/6	
IA7GT	12/-	6E5	12/6	7V7	8/6	30C1	8/-	D15	10/6	ECH83	13/11	HL42DD	PL84	£12/8	U403	XYF34	17/6	
IC5	12/6	6F1	26/6	7Y4	7/6	30F5	7/-	D63	5/-	ECL80	9/-	PL820	18/7	U4F42	9/6	XH(1.5)	6/6	
ID5	9/-	6F6G	7/-	7Z4	18/7	30FL1	10/-	D77	4/-	ECL82	10/6	HN309	24/7	PM2B	12/6	UB41	12/-	
ID6	10/6	6F6GTM	8/-	8D2	3/6	30L1	8/-	DAC32	10/6	ECL83	19/3	HVR2	20/-	PM12	6/6	UBC41	8/6	
IHSGT	10/6	6F11	17/3	8D3	4/6	30L15	11/6	DAF91	6/-	EF9	23/3	HVR2A	6/-	PM12M	6/6	UBC81	11/4	
IL4	4/6	6F12	4/6	9B5W	15/3	30P12	7/6	DAF96	8/6	EF22	14/-	KF35	8/6	PM24M	21/3	UBF80	9/-	
ILD5	5/-	6F13	11/6	9D2	4/-	30P16	7/6	DD41	13/11	EF36	6/-	KK32	21/11	PX4	10/6	UBF89	9/6	
ILN5	5/-	6F14	26/6	10C1	12/-	30P11	11/6	DF33	10/6	EF37A	8/-	KL35	8/6	PX25	59/8	UBL21	23/6	
INSGT	10/6	6F15	15/3	10C2	26/6	30P13	12/6	DF66	15/-	EF39	5/6	KLL32	24/7	PY31	16/7	UCB4	14/7	
IRS	6/6	6F16	9/6	10D2	12/-	33A/158M		DF70	15/-	EF40	15/-	KT2	5/-	PY32	11/6	UCB5	9/6	
IS4	9/-	6F17	12/6	10F1	26/6			DF91	4/6	EF41	9/-	KT33C	10/-	PY80	7/6	UCF80	16/7	
IS5	4/6	6F23	10/6	10F9	10/6	35A5	31/3	DF96	8/6	EF42	10/6	KT36	29/10	PY81	8/6	UCH21	23/3	
IT4	4/6	6F32	10/6	10LD3	8/6	35L6GT	9/6	DF97	9/-	EF50(A)	7/-	KT41	12/6	PY82	7/6	UCH42	9/6	
IU5	5/-	6F33	7/6	10LD11		35W4	7/6	DH63	6/6	EF50(E)	5/-	KT44	12/6	PY83	8/6	UCH81	9/6	
2A3	26/6	6G6	6/6		15/11	35Z3	10/6	DH76	5/-	EF54	5/-	KT61	12/6	PZ30	19/11	UCL82	11/6	
2A7	10/6	6H6GT	3/-	10P13	15/-	35Z4GT	6/-	DH77	7/-	EF73	10/6	KT63	7/-	QP21	7/6	UCL83	19/3	
2P	26/6	6I5G	5/-	10P14	19/3	35Z5GT	9/-	DH81	46/5	EF80	7/-	KT66	15/-	QP25	14/6	UF41	9/6	
2X2	4/6	6J5GTG	5/-	11D3	24/7	42	23/3	DH101	28/6	EF85	7/-	KT81	26/6	QS150/15	10/6	UF42	12/6	
3A4	6/6	6J5GTM	6/-	12A6	5/-	43	10/-	DH107	13/11	EF86	10/6	KT88	22/6		10/6	UF80	10/6	
3A5	10/6	6J6	5/6	12AC6	15/3	50C5	12/6	DK32	12/-	EF89	9/-	KTW61	6/6	R12	9/-	UF85	9/-	
3B7	12/6	6J7G	6/-	12AD6	17/3	50C6DG		DK40	21/3	EF91	4/6	KTW62	7/6	R18	14/-	UF86	17/11	
3D6	5/-	6J7GT	10/6	12AE6	13/11		36/6	DK91	6/6	EF92	4/6	KTW63	6/6	R19	19/11	UF89	9/-	
3Q4	7/6	6K7G	5/-	12AH7	8/-	50L6GT	9/6	DK92	9/-	EF97	13/3	KTZ41	8/-	S130	15/-	UL41	9/-	
3Q5GT	9/6	6K7GT	6/-	12AH8	12/6	53KU	19/11	DK96	8/6	EF98	13/3	KTZ63	7/6	SD6	12/-	UL44	26/6	
3S4	7/6	6K8GT	10/6	12AT6	7/6	72	4/6	DL33	9/6	EF183	18/7	L63	6/-	SP4(7)	14/6	UL46	14/6	
3V4	7/6	6K8G	6/6	12AT7	6/-	75	24/7	DL66	17/6	EK32	8/6	MH4(C)	7/6	SP41	3/6	UL84	8/6	
5R4G	17/6	6K25	19/11	12AU6	23/3	77	8/6	DL68	15/-	EL32	5/-	MML4	7/6	SP42	12/6	UM4	17/3	
5U4G	6/6	6L1	23/3	12AU7	6/6	78	6/6	DL82	46/5	EL33	12/6	MMLD6	12/6	SP61	3/6	UM80	15/3	
5V4G	10/6	6L6G	8/-	12AV6	12/8	80	9/-	DL92	7/6	EL34	15/-	M4	8/6	SU25	26/6	UR1C	9/-	
5Y3G	8/-	6L6M	9/6	12AX7	7/6	83	15/-	DL94	7/6	EL38	26/6	MT2/12/18/4	8/6	SU61	9/6	UR1G	19/11	
5Y3GT	6/6	6L7GT	9/6	12BA6	8/-	83V	12/6	DL96	8/6	EL41	9/-	MX40	15/-	T41	23/3	UU6	16/7	
5Z3	12/6	6L18	13/6	12BE6	9/-	85A2	15/-	DM70	7/6	EL42	10/6	N37	19/11	TDD4	12/6	UU8	26/6	
5Z4G	10/6	6L19	23/3	12BH7	21/3	15GB2	15/-	EA50	2/-	EL81	12/6	N78	19/11	TH45	15/-	UU9	7/6	
5Z4GT	10/6	6L3D	8/6	12E1	30/-	161	10/6	EAB30	9/-	EL84	7/6	N108	19/11	TH41	26/6	UY18	18/7	
6A7	26/6	6LD20	15/11	12J5GT	4/6	185BT	33/2	EAC91	4/6	EL85	13/11	N308	20/7	TH233	33/2	UY21	13/11	
6A8G	9/-	6N7	8/-	12J7GT	9/6	185BTA	33/2	EAF42	9/-	EL91	5/-	N339	15/-	TH232	20/-	UY41	7/6	
6A8T	8/-	6P1	19/3	12K5	17/11	304	10/6	EB34	2/6	EL95	10/6	P61	3/6	TP22	15/-	UY85	7/-	
6A8B	9/-	6P25	12/6	12K7GT	5/6	305	10/6	EB41	8/6	EM34	9/6	PACB80		TP25	15/-	VM54B	15/-	
6AC7	4/-	6P28	26/6	12K8GT	14/-	807	7/6	EB91	4/-	EM71	23/3		13/11	TP2620	33/2	VP2(7)	12/6	
6AG5	5/6	6Q7G	6/6	12Q7GT	5/-	956	3/-	EB33	23/3	EM80	9/-	PCC84	8/-	YB86	13/3	V4	15/-	
6AK5	8/-	6Q7GT	11/-	12SA7	8/6	1821	16/7	EB33	5/-	EM81	9/-	PCC85	9/6	U12/14	8/6	VP2B	14/6	
6AL5	4/-	6R7G	10/-	12SC7	8/6	5763	12/6	EB41	8/6	EM84	10/6	PCC88	23/11	U16	10/6	VP4B	23/3	
6AM6	4/6	6SA7GT	8/6	12SG7	7/-	7475	7/6	EB81	8/-	EN31	37/-	PCC89	11/6	U18/20	8/6	VP13C	7/-	
6AQ5	7/6	6SC7	7/6	12SH7	8/6	9002	5/6	EBF80	9/-	EY51	9/-	PCF80	8/-	U22	8/-	VP23	6/6	
6AT6	7/-	6SG7GT	8/-	12SJ7	8/6	AC/PEN		EBF83	13/11	EY83	16/7	PCF82	10/6	U24	29/10	VP41	6/-	
6AU6	10/-	6SH7GT	8/-	12SK7	6/6	5-pin 23/3		EBF89	9/6	EY84	14/-	PCL82	10/6	U25	17/11	VR105	8/-	
6AV6	12/8	6SJ7GT	8/-	12SQ7	11/6	7-pin 15/-		EBL21	23/3	EY86	9/-	PCL83	11/6	U26	10/6	VR150	7/6	
6B7	10/6	6SK7GT	6/-	12SR7	8/6	AC/PEN/P		EBL31	23/3	EZ35	6/-	PCL84	12/6	U31	9/6	VT61A	5/-	
6B8G	4/6	6SL7GT	6/6	12T4	10/6	DD	12/6	ECS2	5/6	EZ40	7/-	PEN4A	12/6	U33	26/6	VT501	5/-	
6B8GT	5/-	6SN7GT	5/6	12Y7	27/10	ACSPEN		ECS4	6/-	EZ41	7/-	PEN4B	26/6	U35	26/6	W61M	26/6	
6BA6	7/6	6S07GT	9/-	18	23/3	EC70	12/6	EZ80	7/-	PEN4D	U37	26/6	U37	26/6	U37	26/6		
6BE6	6/-	6SS7GT	8/-	19A05	10/6	EC92	13/3	EZ81	7/-	PEN25	19/11	U45	9/-	W81M	6/-	OC81	18/-	
6BG6G	23/3	6U4GT	12/6	19B6G		ACSPEN	23/3	EC92	13/3	EZ81	7/-	PEN25	19/11	U45	9/-	W81M	6/-	
6BH6	8/-	6U5G	7/6			AC/JS	23/3	EC92	13/3	EZ81	7/-	PEN25	19/11	U45	9/-	W81M	6/-	
6BQ7A	15/-	6V6G	7/6	19H1	10/-	ATP4	3/-	EC93	8/6	FC4	15/-	PEN40DD	U50	6/6	W729	18/7		
6BR7	15/-	6V6GTG	8/-	20F1	15/3	AZ1	18/7	EC93	8/6	FC4	15/-	PEN40DD	U50	6/6	W729	18/7		
6BS7	25/-	6X4	5/-	20L1	26/6	AZ1	13/11	EC93	8/6	FC13C	26/6	PEN44	26/6	U54	19/11	X31	26/6	
6BW6	8/6	6X5GT	6/-	20P1	26/6	B36	15/-	EC93	8/6	FV4/500		PEN45	19/6	U76	6/-	X41	15/-	
6BX7	7/-	630L2	10/-	20P3	23/3	BL63	7/6	EC93	8/6	FV4/500		PEN45DD	U78	5/-	X61(C)	12/6		
6BW6	8/6	6X5GT	6/-	20P1	26/6	B36	15/-	EC93	8/6	FV4/500		PEN45DD	U78	5/-	X61(C)	12/6		
6BWX	7/-	7A7	12/6	20P5	23/3	C1	12/6	EC94	9/-	GZ30	9/-	PEN383	23/3	U201	16/7	X65	12/6	
6C4	5/-	7B6	21/3	25A6G	10/6	C1C	12/6	EC95	8/6	GZ32	10/-	PEN45DD	U251	14/-	X66	12/6		
6CSG	6/6	7B7	8/6	25L6GT	10/6	CBL1	26/6	EC98	23/11	GZ34	14/-		33/2	U281	19/11	X76M	14/-	
6C6	6/6	7B7	8/6	25U4GT	16/7	CBL31	23/3	EC99	5/6	H63	12/6	PEN/DD	U282	22/7	X78	21/3		
6C8	12/6	7C5	8/-	25Y5	10/6	CCH35	23/3	ECF80	10/6	HABC80			4020	33/2	U301	23/3		
6C9	12/6	7C6	8/-	25Y5G	10/6	CK506	6/6	ECF82	10/6		13/6	PL33	19/3	U329	14/-	X81	46/5	

NEW MULLARD AMPLIFIER BOOK. HOW TO BUILD THE LATEST DESIGNS, 9/3d, post free.

NEW METAL RECTIFIERS—FULLY GUARANTEED. Technical leaflet on Metal Rectifiers free on receipt of S.A.E.

DRM-1B	15/4	RM-1	5/3	WX3	3/6	14A100	27/-	14RA 1-2-8-2	17/6	16RE 2-1-8-1	8/6
DRM-2B	16/2	RM-2	7/6	WX4	3/6	14A124	28/-	14RA 1-2-8-3	21/-	18RA 1-1-8-1	4/6
DRM-3B	23/3	RM-3	9/6	WX6	3/6	14A163	38/-	14RA 2-1-16-1	21/-	18RA 1-1-16-1	6/6
LW7	21/-	RM-4	14/-	14A86	17/6	14B130	35/-	16RC 1-1-16-1	8/6	18RA 1-2-8-1	11/-
RM-0	7/11	RM-5	19/6	14A97	25/-	14B261	11/6	16RD 2-2-8-1	12/-	18RD 2-2-8-1	15/-

VOLUME CONTROLS Standard Can

All with long spindle and double-pole switch, 4/6 each.

10K, 25K, 50K, 100K, 6/6	32 x 32 mid.,
--------------------------	---------------

DOUBLE BEAM "SCOPE"



for D.C. & A.C. APPLICATIONS


Engineered to precision standards, this high-grade instrument is made available at the lowest possible price, incorporating the essential features usually associated with luxury instruments.

This "SCOPE" will appeal particularly to Service Engineers and Amateurs. A high gain, extremely stable differential Y-amplifier (30 mV/C.M.). Provides ample sensitivity with A.C. or D.C. inputs. Especially suitable for measurement of transistor operating conditions where maintenance of D.C. levels is of paramount importance. Push-pull X amplifier; Fly-back suppression; Internal Time-base Scan Waveform available for external use; pulse output available for checking T.V. Line O/P Transformers, etc.; Provision for external X Y/F and CRT Brightness Modulation. A.C. mains 200/250 v. £19.19.6, plus P. & P. 7/8, or 50/- deposit, plus P. & P. 7/8 and 12 monthly payments of 33/4.

FULL 12 MONTHS' GUARANTEE INCLUDING VALVES AND TUBE.

ALIGNMENT ANALYSER TYPE MC12

A.C. mains 200/250V. Provides: "Wobulator" (Swept Frequency) operation, for FM/TV alignment linear frequency sweep up to 12 Mc/s. From 400 kc/s-80 Mc/s. Capacitance Measurement. Two ranges provided 0-80pF and 0-120pF. Special Facility enables true resonant frequency of an tuned ckt. I.F. transformer, etc., to be rapidly determined. Cash price £6.19.6, plus 5/- P. & P. H.P. terms 25/- deposit plus 5/- P. & P. and six monthly payments of 21/6.

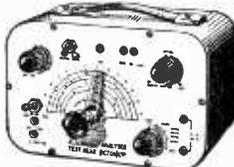

WOLSEY 3-ELEMENT FOLDING DIPOLE


I.T.V. Aerial less mounting bracket for External use, complete with 12 yds. of coaxial cable, 15/-; 4 element, 17/6. P. & P. on above, 3/6.

LINE E.H.T. TRANSFORMER

With built-in line and width control. 14 KV. Scan coil, 90° deflection, on ferrite yokes. Frames O.P. transformer pt. 18 KV. smoothing condenser. Can be used for 14in., 17in. or 21in. tubes. Complete with circuit diagram.

29/6 Plus 4/- P. & P.

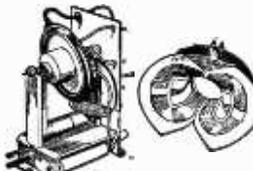Focus Magnet suitable for the above (state tube). 10/- Plus 2/6 P. & P.



F.M. TUNER UNIT

by famous German manufacturer. Coverage 88-100 Mc/s. Complete with MC8S, size 4in. x 2in. x 2in.

25/- P. & P. Circuit Diagram 1/- FREE with Unit.

10.7 Mc/s. I.F. and Discriminator Coil, 4/- pair.

MAINS TRANSFORMERS

All with tapped primaries. 200-250 volts, 0-160, 180, 200 v., 60 ma., 6.3 v. 2 amps., 10/6. 280-0-280 80 ma 6.3 v. 2 amp., 6.3 v. 1 amp., 10/6. 350-0-350 v., 70 ma., 6.3 v. 1 amp., 6.3 v. 2 amp., 10/6. 250-0-250 v., 70 ma., 6.3 v. 2 amp., 10/6. Postage and packing on the above, 3/-.


TRANSISTOR TESTER

For both P.N.P. and N.P.N. transistors incorporating moving coil meter. In metal case, size 4 1/2 x 3 1/2 x 1 1/2 in. Scale marked in gain and leakage. Complete 19/6 Plus 2/6 P. & P. and ready for use.

BUILT POWER SUPPLY UNIT


A.C. Mains 200-250 v. D.C. Output 250 v. at 75 ma., also 6.3 v., 2 amp. heater winding. 21/- Plus 3/6 P. & P.

SIGNAL GENERATORS

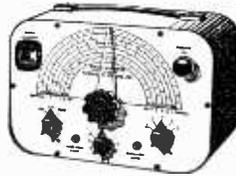


£6.19.6 or 25/- deposit and 6 monthly payments of 21/6. P. & P. 5/- extra. Coverage 100 Kc/s-100 Mc/s on fundamentals and 100 Mc/s to 200 Mc/s on harmonics. Metal case 10in. x 6in. x 5 1/2in., grey hammer finish. Incorporating three miniature valves and Metal Rectifier. A.C. Mains 200/250. Internal Modulation of 400 c.p.s. to a depth of 30%; modulated or unmodulated R.F. output continuously variable. 100 milli-volts, C.W. and mod. switch, variable A.F. output. Incorporating magic-eye as output indicator. Accuracy plus or minus 2%.

Cash £4.19.6 or 25/- deposit and 4 monthly payments of 21/6. Plus Postage and Packing 5/-. Coverage 120 Kc/s-84 Mc/s. Metal case 10in. x 6in. x 4 1/2in. Size of scale, 6in. x 3in. 2 valves and rectifier. A.C. mains 200-250 v. Internal modulation of 400 c.p.s. to a depth of 30% modulated or unmodulated R.F. output continuously variable. 100 milli-volts. C.W. and mod. switch variable A.F. output and moving coil output meter. Grey hammer finished case and white panel. Accuracy plus or minus 2%.

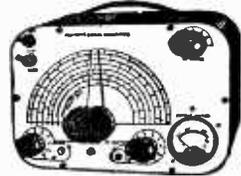

SIGNAL & PATTERN GENERATOR

£6.19.6 P. & P. 5/-

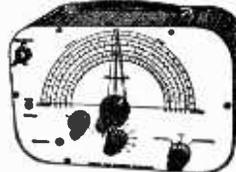


Or 25/- deposit. P. & P. 5/- and 6 monthly payments of 21/6. Coverage 7.6 Mc/s-310 Mc/s. In five bands, all on fundamentals, slow motion tuning audio output. 8 vertical and horizontal bars, logging scale. In grey hammer finished case with carrying handle. Accuracy ± 1% A.C. mains 200-250 v.

CHANNEL TUNER

Will tune to all Band I and Band III stations. BRAND NEW by famous manufacturer. Complete with P.C.C. 84 and P.C.F. 80 valves (in series). I.F. 16-19 or 33-38. Also can be modified as an aerial converter (instructions supplied). Complete with knobs.

22/6 Plus 3/6 P. & P.

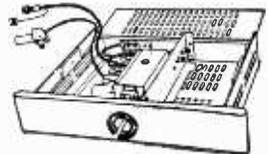

HEATER TRANSFORMER

To suit the above, 200-250 v., 6/- Plus 1/6 P. & P.

8-WATT PUSH-PULL AMPLIFIER

COMPLETE WITH CRYSTAL MIKE AND 8in. LOUDSPEAKER

A.C. mains 200-250 v. Size 10 1/2in. x 6 1/2in. x 2 1/2in. Incorporating 6 valves. H.F. pent., 2 triodes, 2 output pens and rectifier. For use with all makes and type of pick-up and mike. Negative feed back. Two inputs, mike and gram., and controls for same. Separate controls for Bass and Treble lift. Response flat from 40 cycles to 15 Kcs., ± 2 db; 4 db down to 20 Kcs. Output 8 watts at 5% total distortion. Noise level 40 db down all hum. Output transformer tapped for 3 and 15 ohm speech coils. For use with Std. or L.P. records. Plus musical instruments such as Guitars, etc. £4.19.6 Plus 3/6 P. & P. 7/8.


Or 20/- deposit Plus P. & P. 7/8, and 4 monthly payments of 23/-.

RADIO & T.V. COMPONENTS (Acton) LTD.

23 HIGH STREET, ACTON, LONDON, W.3.

All enquiries S.A.E. GOODS NOT DESPATCHED OUTSIDE U.K.

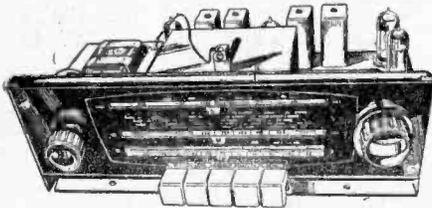BRAND NEW AM/FM (V.H.F.) CHASSIS AT £13.6.8. (P. & P. 10/-)



Why buy a F.M. Tuner at the same price?
Tapped input 220-225 v. and 226-250 v. A.C. ONLY.
Chassis size 15 x 6 1/2 x 5 1/2 in. high. New manufacture.
Dial 1 1/4 x 4 in. in gold and black.
Pick-up Extension Speaker, A.E., E. and Dipole sockets. Five "piano" push buttons—OFF, L.W., M.W., F.M. and Gram. Aligned and tested. With all valves & O.P. Transformer. Tone-control fitted.
Covers 1,000-1,900 M.; 200-500 M.; 88-99 Mc/s.
Valves EZ80 rect., ECH81, EF89, EABC80, EL84, ECC85. Speaker & Cabinet to fit chassis. 47/6.
10 x 6 in. ELLIPTICAL SPEAKER. 20/-

TERMS:—(Chassis) £4.16.8 down—10/- carr.—and 6 Monthly Payments of 30/- or with Cabinet & Speaker £5.9.2 down and 7 Monthly Payments of 32/-.


We are specialists in ITA Converters. Our converters give direct switching ITA to BBC, metal rectifier, co-axial plug. Can be fitted in 5-10 mins. and need no alteration to your set. ALL AREAS. ALL SETS. ALL CHANNELS. 12 months' guarantee (3 months on valves).

"READY TO USE" ITA CONVERTER


Separate gain controls. Valves PCF80 and PC84. Switch positions ITA (1)—ITA (2)—BBC. Bakelite moulded cabinet 8 1/4 x 4 x 6 in. £5.5.0. P. & P. 3/-.



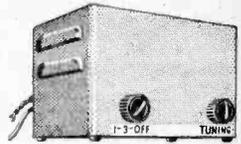For the last 50 ITA Converters of this type (Brand New and Fully Guaranteed) we will accept the "Relow Cost" figure of ONLY 60/- (3/- P. & P.) Reduced from £4.7.6.
Two valves ECH81—grey hammer finish—Switch positions OFF, ITA, BBC. Own Power supply. BUY IT NOW.




60/- (3/- P. & P.)

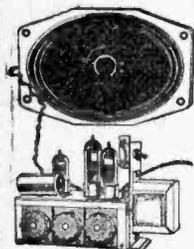

3-VALVE AMPLIFIER (INCL. RECT.) Capable of giving 6 watts. Mains and output transformers. Valves ECC81, EL84 and Rect. 3 Controls, volume, bass and treble. On/Off switch. Fully guaranteed. Chassis size 6 1/2 x 3 x 2 1/2 in.; with 7 x 4 in. elliptical speaker or 6 1/2 in. round (Goodmans); state which.

Only 67/- (P. & P.)

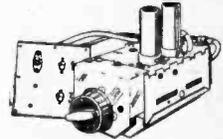THE BRAYHEAD TURRET TUNER. £7.7.0 post free. Complete with booklet and fitting instructions. State set and model No. when ordering.
Converts your 5-channel BBC only set to receive ITA as well.



ITA AERIALS clipping to existing mast 1-2 in. dia. 3-element, 22/-; 5-el., 30/-; 9-el., 50/-; Loft mounting, 3-el., 20/-; 5-el., 28/-; Combined single BBC and 5-el. ITA. 75/- with chimney-lashing; Co-axial cable semi-air-spaced, 7d. yd. or 20 yds., 11/-. Aerial prices carr. paid. Postage on cable 1/-.


50 SILVERED MICA AND CERAMIC CONDENSERS, 10/-, 50 RESISTORS, 5/- ALL NEW.

NEW WAXED TUBULARS. 350 v. or above, 3 of each, 0.001, 0.002, 0.005, 0.01, 0.02, 0.05, 0.1 mF. Total 21 for 4/6, post paid.

STUPENDOUS OFFER! 13-CHANNEL TUNER

L.F. 34-38 Mc/s complete with valves PCF80 and PC84. Removed from chassis but in working order.

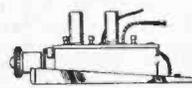15/- (2/6 P. & P.) Knobs 2/6 extra. Some tuners less valves 7/6.



NEW ITA AND BBC TUNER. By well-known manufacturer for superhet TVs with 35-38 Mc/s I.F. For all areas; covers all 13 channels. Switch gives BBC and two ITA selections. Suits G.E.C. sets BT4543, 4544, 5146, 5147, 5543, 5542 and 6641 without alteration. Easily adapted as aerial converter, and instructions can be provided free. Has ITA and BBC co-axial sockets and separate gain controls.
WITH VALVES PCF80 and PC84, 22/6 (P. & P. 3/-). Some without valves at only 12/6 (P. & P. 3/-).

ITA TABLE TOP AERIAL

An ITA table top aerial with amazing performance. The Waisey Hi-Q at 19/6 (2/8 post). Gives good reception up to 20 miles, and has cross-over unit in base with socket for BBC aerial.
Same model but very slightly tarnished for ONLY 12/6 (2/6 post).



GRAMOPHONE AMPLIFIER with 5 in. SPEAKER. On Fabric-covered Baffle 12 1/2 x 8 in. Mains and Output Transformers. Metal Rectifier. ECL82 Valve. Tone and Volume Controls. On/Off switch. Fully Guaranteed. Two Knobs supplied. Ready to play. Useful for Stereo.


ONLY 57/-, post 3/-

PERSPEX UNSCRATCHED. (Post 2/- each or 6 post free.) 12 1/2 x 9 1/2 x 1/2 in. clear. 4/6; 14 1/2 x 11 x 1/2 in. clear. 5/-; 15 x 12 x 1/2 in. tinted. 6/-; (Also 15 x 12 in. slightly scratched at 3/-).

AUTOMATIC RECORD CHANGERS, COLLARO CONQUEST with manual play also. Turnover crystal pick-up, 4-speed, A.C. mains 200-250 v., see illus.

£7.10.0 (5/- P. & P.)

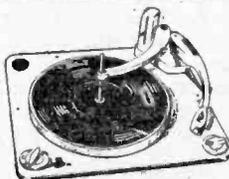B.S.R. 4-speed U.A.S. auto-changer £6.15.0 (5/- carriage).



LISTEN WITHOUT INTERFERENCE

Fully built V.H.F./F.M. set. Wired, aligned and tested. 6 Mullard valves; with mains transformer. 88-98 Mc/s. **ONLY £8.8.0 (4/- carr.)**. Cheap room dipole 10'-, 300 ohm twin feeder, 6d. yd. All with 12 Months guarantee.

Delivery by return. C.O.D. 2/- extra. Terms: Cash with order or one-third down and balance plus 7/6 (up to £7.10.0) in four equal monthly payments. Balance over £7.10.0 add 1/- in £1 and pay in not more than 6 monthly payments. See special terms for A.M.-F.M. chassis. All new goods unless stated. Send 6d. for 16-page catalogue.

GLADSTONE RADIO

3 CHURCH ROAD, BRISTOL 5 and 247 NEW ROAD, PORTSMOUTH

POSTED ORDERS TO CAMBERLEY PLEASE

65A HIGH STREET, CAMBERLEY, SURREY. Tel. 2791 (Camberley closed Sats; Bristol and Portsmouth closed Weds.)



Practical Television



& TELEVISION TIMES

Vol. 10 No. 118

EVERY MONTH

JULY, 1960

Editorial and Advertisement Offices:
PRACTICAL TELEVISION
George Newnes, Ltd., Tower House,
Southampton Street, W.C.2.
© George Newnes Ltd., 1960.

Phone: Temple Bar 4363
Telegrams: Newnes, Rand, London.
Registered at the G.P.O. for transmission by Canadian Magazine Post.

SUBSCRIPTION RATES including postage for one year

Inland - - £1.2.0 per annum
Abroad - - £1.0.6 per annum
Canada - - 19s. per annum

CONTENTS

	Page
Editorial	505
Telenews	506
Two-Band Pre-amp ..	508
Boosting C.R. Tubes ..	510
Servicing TV Receivers ..	513
Instability	517
Is There Enough Signal?..	521
Add-on Sound Unit ..	524
Feeder Cables	527
Underneath the Dipole ..	529
Trade News	531
Letters to the Editor ..	535
Your Problems Solved ..	536

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Television." Such articles should be written on one side of the paper only, and should contain the name and address of the sender, whilst the Editor does not hold himself responsible for the manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to: The Editor, "Practical Television", George Newnes, Ltd., Tower House, Southampton Street, London, W.C.2.

Owing to the rapid progress in the design of radio and television apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent.

Copyright in all drawings, photographs and articles published in "Practical Television" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden.

Trends in Viewing

IT seems that, until a third service begins, the development of television in Great Britain is limited. Several years ago the intelligent observer could have forecast that, once the initial novelty of ITV had disappeared, then tastes in viewing would alter progressively as viewers became more familiar with the programmes transmitted. When ITV first began, as was expected, many viewers watched the programmes in preference to those of the BBC; the novelty of the programmes and the generally more popular style both contributed to this trend. For the BBC, the worst period occurred in late 1957 when, according to the BBC's own figures, their share of the nightly audience dropped below 30 per cent of the total for the first and only time. During the next few months, the viewing figures remained relatively static although periodically the BBC showed slight gains over ITV. However, ITV always regained its position soon after the decline. In recent months, though, a change in these trends has been evident; according to figures produced by TAM (Television Audience Measurement Ltd.) there has been a gradual decline in the popularity of ITV. The proportion of the total audience with multi-channel sets watching the commercial network has fallen from 72 per cent to 66 per cent since September last although, naturally, there are differences from region to region. As might be surmised, those areas in which ITV is a recent introduction still remain, for the most part, loyal to ITV: a particular instance is Ulster TV where the proportion of ITV viewers very soon after the opening reached over 70 per cent although this was not so with Anglia TV where the initial ITV share of the viewing was no more than 55 per cent. Another factor upon which viewing figures partly hinge is the preponderance of industrial areas in the north of England where available leisure hours tend to differ from those in the south of England.

Generally speaking, and leaving aside minor regional differences, the BBC is lately gaining an increasing proportion of the viewing audience. All this has occurred without any evident or specific change of policy and therefore it seems that the slight decline in ITV figures depends to some extent on the standards of their programmes. There have been many complaints that advertisements occupy too much of the programme time and it is interesting to note that the ITA has recently announced that while the daily maximum of 10 per cent will continue, from 12th September, spot advertising will not exceed 7½ minutes in the clock hour, and from 24th December, 7 minutes. The ITV programme policy is being based more and more on regular weekly series: "episoded" serials. Perhaps it is believed that when a regular diet is offered, then viewing becomes a matter of habit rather than choice.

It seems that the BBC's long-established policy of providing well-balanced programmes is now achieving success in areas where ITV is no longer a novelty.

Our next issue, dated August, will be published on July 22nd.



Television Receiving Licences

THE following statement shows the approximate number of Television Receiving Licences in force at the end of April 1960, in respect of television receiving stations situated within the various Postal Regions of England, Wales, Scotland and Northern Ireland.

Region	Total
London Postal	1,822,985
Home Counties	1,427,406
Midland	1,599,203
North Eastern	1,716,602
North Western	1,413,175
South Western	884,213
Wales and Border Counties	635,040
Total England and Wales	9,498,604
Scotland	925,322
Northern Ireland	144,759
Grand Total	10,568,685

Southern Area ITV

FINDINGS of the first complete survey covering the whole of the newly-defined Southern ITV area have been released by TAM. They reveal that there were, at mid-March, 589,000 homes—half the number of homes in the enlarged Southern area—receiving independent television from either the Chillerton Down or the Church Hougham transmitter.

An analysis of ITV homes reveals that the Southern area still has a consistently higher percentage of ITV homes in the ABC socio-economic group than any other ITV area. TAM survey figures for mid-March reveal that 45 per cent of its homes are occupied by people in this class compared with 33 per cent for the whole network.

Results of the survey are published by TAM along with those for London, Midlands, Northern, Scottish, South Wales and the West, and North Eastern ITV areas. In common with the trend in five of these areas, findings for the Southern area show a slight drop in the average size of ITV homes compared with figures for last October. The

average size of ITV homes in the South Wales and the West area, however, remains stationary. TAM adds that these comparisons tend to indicate that ITV ownership is now penetrating further into the smaller families which constitute the bulk of the non-TV population.


Research Chair

THE University College of North Staffordshire accepted last July an offer from Granada TV Network to found a Research Chair in Communication. Dr. Donald Mackay has been appointed to the Chair and took up his appointment in June. He will appoint a team including two medical scientists, one or two

psychologists, several physicists and electronics engineers, and eventually some sociologists. His work will include a study of the way in which the brain deals with the information sent to it by the eyes and ears. Dr. Mackay hopes to discover whether the brain can translate a system of electronic sounds into words or letters of the alphabet. This might open the way to the development of a machine to enable blind people to "read" printed words "by ear". The Granada Chair is tenable in the first instance for seven years at a total cost of £45,000.

Westward TV Studios

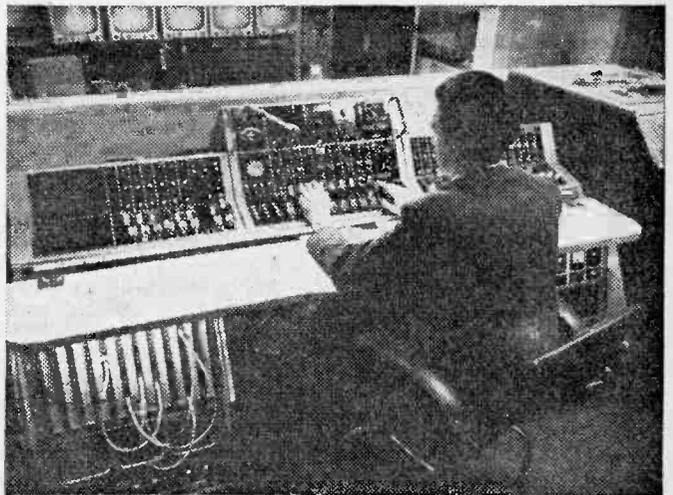WORK on the Plymouth site for Westward TV's studios was scheduled to begin on June 1st and completion is expected about



Nine television sound control desks of an entirely new design have been ordered from Marconi's by various programme contractors to the Independent Television Authority. The illustration above shows the "Major", one of the three versions of the control desk, in use at the Teddington studios of Iris Productions Ltd. (ABC Television Ltd.)

March 1961. Preliminary drawings have been prepared by the architects and in planning the lay-out, great care has been taken to preserve as many as possible of the existing trees on the site, which includes the present Crescent Gardens. A number of firms in Devon and Cornwall were interviewed before the contract was awarded to Garrett's of Plymouth, who built the North Hessay Tor Transmitting station for the BBC.

ITV in the Borders

THE application of a group formed under the Chairmanship of Mr. John L. Burgess, Managing Director of Cumberland Newspapers Ltd., to provide the programmes for transmission from the Authority's proposed two stations in the Border area has been accepted, subject to contract, by the ITA. The group, which will be known as Border Television, will have its headquarters and studios in Carlisle.

The Authority plans to build two transmitting stations in the Borders and to bring them both into operation next year. The first station to open will be at Caldbeck near Carlisle and it is hoped that this station will be on the air early in 1961. The other station will be near Selkirk, and it is hoped to open it around the end of 1961. The service areas of these two stations, taken together, will include over half a million people.

Australian TV Station

A NEW Australian television station was officially opened by the Australian Postmaster-General, Mr. C. W. Davidson, at Adelaide recently. Situated at Mount Lofty, at a height of 1,130ft above sea level, and about 13m east of Adelaide, the station was equipped by Marconi's of Chelmsford.

The order, placed by the Australian government with Amalgamated Wireless (Australia) Ltd., was part of a larger order for the supply and installation of transmitting stations and studio equipment worth approximately £400,000.


The equipment supplied for the national transmitting station at Adelaide included two 10kW television transmitters with associated 2kW FM sound transmitters, combining equipment and an eight-stack high gain aerial, a control desk, programme input equipment (vision and sound),

transmitter studio link and extensive monitoring facilities and spares.

TV for Wales

MR. HENRY BROOKE, Minister for Welsh Affairs, Mr. J. R. Bevins, Postmaster General and Lord Brecon, Minister of State for Welsh Affairs, had a discussion recently with members of the Continuation Committee of the National Conference on Television for Wales which met in Cardiff last autumn.

speaking viewers the opportunity to watch English-language programmes with a Welsh outlook. The various problems entailed in securing this were discussed, and the technical difficulties seen by the Post Office in the plans suggested in the Committee's memorandum were explained orally. The Committee said that they would like to examine these technical arguments further, and for this purpose the Ministers promised to furnish a technical memorandum which the

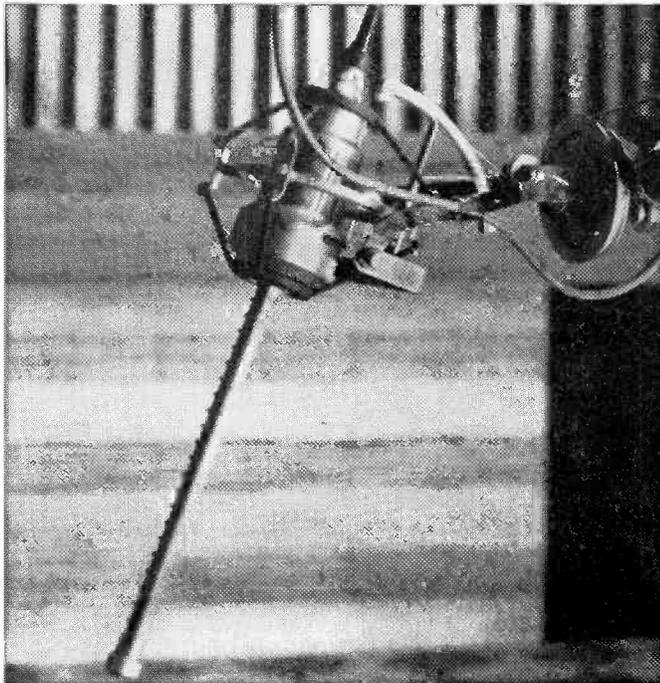

The Sound Section of Tyne Tees Television's Engineering Department has recently brought into service a new type of microphone (illustrated above) for use on sound booms. The microphone is manufactured by the Electrovoice Company of Michigan, U.S.A.

The Committee had sent to the Ministers a detailed memorandum on the practical possibilities of providing a television service, partly in Welsh and partly in English, designed particularly for Wales. The Ministers assured the Committee that they all fully appreciated the desire in Wales for a television service intended primarily for Welsh viewers. The committee indicated that its aspiration was to see television provided in the Welsh language for Welsh-speaking viewers at peak viewing hours, while ensuring for English-

speaking viewers the opportunity to watch English-language programmes with a Welsh outlook.

ITV in N.E. Scotland

THE Independent Television Authority early last month invited applications from new groups wishing to become the programme contractor for North East Scotland. This area will be served by two transmitting stations, one near Aberdeen and the other close to Inverness, and it is hoped that both stations will be opened around the end of next year. Over 850,000 people live within the two service areas.

Two-Band Pre-Amp

COMPLETING AND TESTING THE UNIT

(Continued from page 475 of the June issue)

By R. E. F. Street


THE article in the previous issue dealt with the design, layout and construction of this pre-amplifier. The importance of short wiring, particularly in the Band III circuitry was stressed, and it was mentioned that the leads wired to poles on S1B and S1C should consist of two wires in parallel in order to reduce the effective inductance. Those who have started the construction of this unit may have referred to valve manuals and found that the input triode of the PCC89 has two cathode leads. Although in the circuit diagram, pin 8 only was shown as being connected, pin 7 should be wired, at the holder, to pin 8. This reduces the effect of the inductance of the cathode lead of the input triode and results in improved performance. It should be noted that the triode connected to pins 9, 6, 8 and 7 should be used for the input and the one connected to pins 3, 2 and 1 for the output as the valve was designed for this arrangement.

Testing

When the pre-amplifier construction is finished, all wiring should be checked carefully; when using a few tags only on each wafer of the switch it is very easy to make errors. The unit may now be switched on and if possible the H.T. and L.T.

should be measured without the valve in position. If all is in order the unit should be switched off, the valve inserted and the unit switched on again. As a check, the H.T. and L.T. voltages may again be measured. Plug the downlead into the input socket and connect the output to the receiver aerial socket. Switch to the Band I position, as owing to the different propagation conditions on Band I and Band III, the Band I signal is usually the stronger of the two and it is easier to check that the pre-amp works satisfactorily by using the Band I signal first.

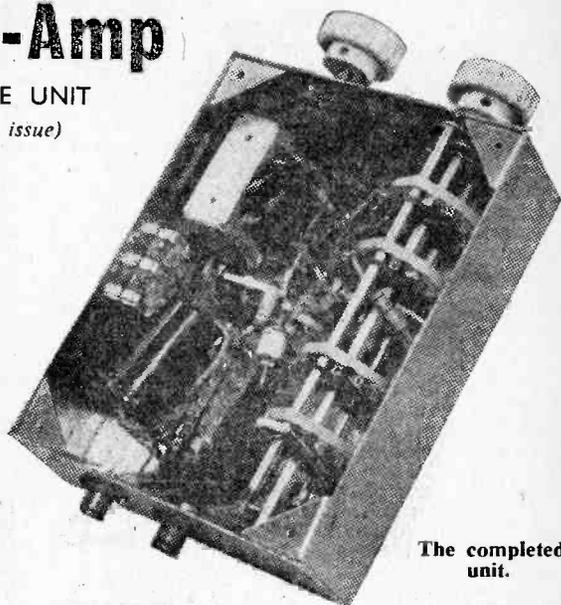The dust cores in L2 and L6 should be altered in position for best results and finally the positions of



The completed unit.

the two coupling coils L2 and L7; movement of these coils may necessitate altering the position of the slugs again. If the slugs are loose in the coil formers they should be removed and a piece of thin elastic inserted down the threads of the former and the slug screwed in again. When the best positions for the slugs and coupling coils have been found, the coupling coils may be lightly cemented in position. (A tool for adjusting the position of the cores can be made from a plastic knitting needle.)

Band III Alignment

The pre-amp may now be switched to Band III and the spacing of the turns on L3 and L8 adjusted with an insulated tool—the knitting needle will serve. If the Band III signal is very weak it may be found that the signal level from the pre-amp is less than the signal level direct from the aerial. Whilst this may be due to L3 and L8 resonating at the wrong frequency, it is more likely that the coupling between the aerial and L3 and the receiver and L8 is not optimum. Various alternative methods of coupling may be tried. Instead of using the coil L4, the wire from S1B can be tapped directly on to L3 and the optimum position be determined by trial. The effect of including a small capacitor—2-10pF—may also be tried. A coaxial line input may be used as indicated in Fig. 4, and the aerial input tapped down this line for best results. Naturally, as the signal level is stronger, matters are easier as far as L8 is concerned. The effect of omitting L9 and employing a small capacitor between the anode and the inner conductor of the output coaxial cable is certainly worth trying. The value of this capacitor may be, again 2-10pF. If good results are obtained with the initial arrangement the number of turns on L4 and L9 may be altered in an endeavour to secure better results.


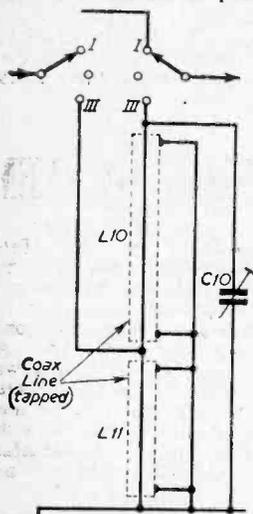


Fig. 4.—An alternative input circuit using coaxial lines with the input circuit tapped down this line for best results.

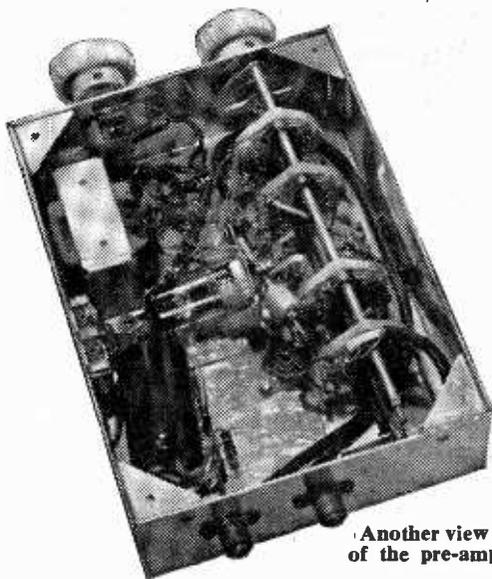

Another view
of the pre-amp.

The condenser C2 which is part of the neutralising network for V1 is best set for optimum results on the Band III channel and is simply adjusted until the best picture quality is obtained—for lowest noise. The turns of the inductance L5 may be opened out or closed up when switched to Band III. If it is desired to avoid the losses which may be associated with change of cable at the input socket this socket may be omitted and the aerial downlead wired directly to S1A.

Instability

Owing to the high gain of the pre-amplifier it is possible and, if construction is not particularly well

carried out, likely, that instability in the pre-amplifier will be experienced. This shows up when the screen of the cathode ray tube becomes extremely bright owing to the large signal developed in the oscillating stage. In curing this instability the positions of the output and input leads relative to each other are critical and arrangement will often effect a cure. The decoupling capacitors can likewise have a great effect upon the performance—particularly C6 and C7. In the event of instability, it is worth while to experiment with these condensers by putting others in parallel, perhaps connected to different earth points, until the instability is cured.

Housing

The finished unit may be housed in a wooden box which can be fitted or placed on top of the TV receiver where the knob for the band switching will be within reach and can be operated with the existing channel selector. The two relevant positions of the switch can be marked "BBC" and "ITV" for the non-technical members of the household. Although a great deal of heat is not generated in the unit, adequate ventilation should be assured to avoid frequency drift. During the testing, the unit can be operated direct from the mains supply but finally when it is fitted permanently to the receiver the mains supply should be taken direct from the set (after its mains switch) and then the pre-amplifier cannot be left switched on inadvertently.

Conclusion

It is worth while emphasising again that where signal strengths are low a pre-amplifier such as this must be "tailored" to suit the conditions of the location concerned. To obtain maximum transfer of energy from aerial to first grid and from second anode to receiver will necessitate, in most instances, some experiment, but it will then be certain that the best use is being made of the available signal.

THE HENRI DE FRANCE COLOUR TELEVISION SYSTEM

A UNIQUE demonstration was presented in April at The Institution of Electrical Engineers, when two French authors, MM. R. Chaste and P. Cassagne, described a new system of colour television transmission. Scenes originating in Paris were seen in full colour by a large audience in London, on screens which differed little, if at all, in their external appearance from those of ordinary "black and white" television receivers.

Moreover, the transmitted pictures were "compatible", that is to say, if fed into a colour receiver, they gave a coloured result; if fed into a normal television set, they gave a black and white picture. This "compatibility" is important, because it would provide a means of bridging the gap if a colour service were to be introduced, so that until a user bought a colour receiver his existing set would still give him a black and white result from the colour transmission.

Behind this feat lay a triumph of engineering co-operation. Experts in the French com-

panies responsible for the development of the system, the French Posts and Telegraphs, the Radio Television Française, the British Post Office and the BBC, together set up a complicated radio link comprising sections of the existing Eurovision network, with additional microwave links of the type used by the BBC. As an additional precaution, a video recording was made in London beforehand of the complicated colour signals transmitted from Paris, to be used in the event of there being any breakdown in the radio link between the two capitals. It is satisfactory to report that the recorded version was not in fact required.

PRACTICAL TELEVISION CIRCUITS

288 pages - - - 156 Illustrations

15/- net or 16/1 by post from

GEORGE NEWNES LTD.

Tower House, Southampton St., London, W.C.2

"Boosting" C.R. Tubes

MAKING SMALL TRANSFORMERS
TO IMPROVE EMISSION

By "Engineer"

THE price of picture tubes makes it necessary to retain these components just as long as possible. However, the emission of C.R. tubes gradually deteriorates and the picture brightness decreases. In many cases this state of affairs can be alleviated and the life of the picture tube prolonged by what is known as "rejuvenation"—treatment by means of which the cathode of the tube is persuaded to increase its emission. It will be clear that such treatment can do nothing to improve tubes which have gone soft, tubes in which the screen has deteriorated, or tubes in which defects such as enlarged gun apertures have arisen, but even so, cathode rejuvenation will give a very distinct improvement in the picture, and extend the life of a tube for a considerable time, in between 50 per cent and 85 per cent of old tubes so treated.

Rejuvenation is nothing new, for patents dealing with rejuvenation principles were being granted in 1926. Two basic methods are available, one a true rejuvenation process and the other a "brightening" process.

Construction

Cathodes are commonly formed of nickel alloy cylinders coated with an electron emitting chemical—barium and strontium oxide coatings are best. The coating is made in the form of barium carbonate or strontium carbonate, the carbonate coating then being activated by the process of heating the coating whilst the cathode has about 150V applied through a resistor. Under these conditions, the carbonates are thermally reduced to oxides and the oxide coating is bombarded by high energy ions. As a result the coating and cathode become highly emissive and normal operation can proceed at lower cathode temperatures. Different manufacturers' processes naturally contain various refinements and additions.

Throughout its life the cathode deteriorates. It may be over-worked or incorrectly energised (by too high or too low a heater voltage) or the oxide coating may be contaminated by occluded gases in the tube—under normal working conditions the outer oxide coating of the cathode evaporates and is replaced by oxide from deeper layers; contamination can occur when evaporation is more rapid than replacement. Electrons are then emitted less freely, the beam current falls and the picture on the face of the tube becomes progressively dimmer.

The Simplest Method

The simplest method of obtaining at least a further measure of life from the tube is to increase

the cathode temperature so that electrons can escape more readily; this is obviously achieved by supplying the tube heater with more than its rated voltage, an increase of 25 per cent or so being usual. It might seem that this would lead merely to rapid burning-out of the heater but in practice this rarely happens, heaters being conservatively rated since they are employed in the first instance to raise the cathode temperature for the original activation of the carbonate coating. Many "boosters" now sold consist of a small transformer supported in leads or in a plug-base. The connecting socket of the tube is removed from the base and the transformer assembly is plugged into this socket instead. A socket connected to the transformer assembly is slipped on to the tube pins, and in a surprising number of cases a dim, practically worthless tube is able to give months of extra service.

The advantage of any rejuvenation system is that whatever the result may be, nothing is lost (if the rejuvenator is built up from the spares box). If the tube responds to treatment it may give a further three, six or even nine months service—if it fails to respond or if the heater does burn out (very rarely) a new tube will be required in any case.

A booster may be either an auto-wound transformer, accepting heater power from the receiver from the original tube heater circuit and transforming this up to the higher voltage, or a two-winding transformer may be employed, the primary being fed from the mains and the secondary supplying the new heater voltage. In this case it is sometimes possible to overcome the effects of a cathode-heater insulation breakdown since the use of a two-winding transformer means that the heater and cathode can be strapped.

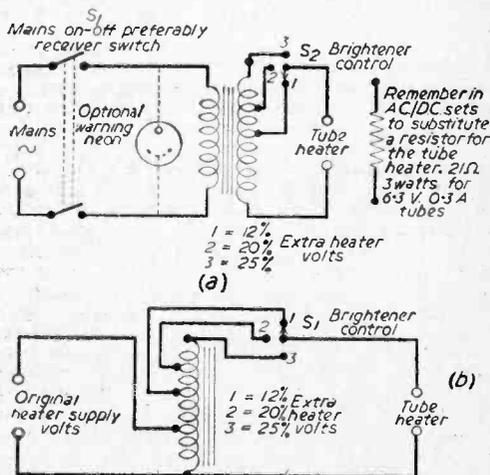


Fig. 1 (a).—A transformer tube booster and (b) an auto-transformer booster. (In A.C./D.C. sets, instead of substituting a resistor for the tube heater, as at (a), the voltage selector may be moved to the next highest position and the tube heater leads shorted together.)

One deciding factor on the system to be used is whether the receiver is an A.C. only or an A.C./D.C.

model—in the latter case an auto-transformer may not be used and a two-winding transformer can be employed only when the receiver is supplied from A.C. mains. If the set is fed with D.C. it is impracticable to build a brightener, and a rejuvenation process proper must be tried. When the picture tube forms part of the heater chain in an A.C./D.C. receiver an equivalent resistance must be wired in as a substitute for the tube heater, and some form of switching for two-winding transformers must be devised. In the majority of cases it will be possible to wire the transformer primary to the mains switch in the receiver.

Circuits

The circuit of a transformer booster is shown in Fig. 1, and it will be seen that in each case three heater taps are made available. This is in order that brightening may be progressive—when the tube first

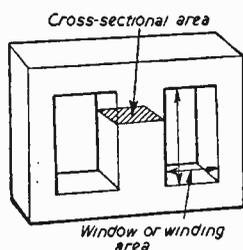


Fig. 2.—A typical transformer core, showing the cross-sectional and window areas.

loses brilliance to a marked degree the booster is put into circuit and the heater supplied from the first tap, which applies approximately 12 per cent extra voltage over the heater rating. The second tap can be used when the tube again dims, and applies 20 per cent approximately higher voltage. The third tap supplies the full 25 per cent extra voltage to the heater—still

higher percentages might be tried but by that time it is probable that the cathode would fail to respond to further brightening. Two-winding transformers may be constructed most easily and cheaply from the small-sized heater transformers at present in wide supply, rated to give an output of 6.3V at 1.5A. For the majority of tubes the basic heater rating is 6.3V at 0.3 or 0.6A, so that the existing secondary winding on a small heater transformer can be stripped off and a winding of thinner wire put on. (Choose for this purpose a heater transformer with the secondary winding on top of the primary, and ensure that there is perfect insulation between the windings when the secondary is remade.) Count the turns taken off the secondary and to find the number of turns per volt divide by 6.3 or, if this fails, to give a round number or at least a simple fraction, divide by 6.5. (The majority of small transformers have an extra turn or two to allow for a voltage drop on load.) If any doubt exists, a test winding can be put on, loaded by about 10Ω and the voltage across the winding measured by an A.C. voltmeter.

Using thinner wire than that removed, carefully wind on the new winding to give the three suggested heater voltages (basic rating plus 12 per cent., 20 per cent and 25 per cent.) For 6.3V tubes the final voltages should be 7.0, 7.5 and 8.0V. Suitable wire is chosen by reference to wire tables—for 0.3A tubes 24s.w.g. wire, and for 0.6A tubes 22s.w.g. wire will serve at current density ratings of 1,000A/sq. in. If the winding space appears too

small for these gauges it may be presumed that the transformer was designed to operate at current density ratings of 2,000A/sq. in. when gauges of 28s.w.g. and 24s.w.g. may be used for 0.3 and 0.6A heaters respectively.

Enamelled wire should be employed and tappings must be made with care. Good rubber-covered flex of thin diameter should be chosen for the tapping leads and the soldered joints where the taps contact the windings must be made neat and smooth, with no more enamel removed than is necessary. The joints must be perfectly insulated.

Winding Data

If it is desired to employ the auto-transformer type of brightener this may be wound up on any small core such as the stampings from an output transformer, since only between 2 and 5W approximately have to be handled. A former may be constructed from card or fibre, if one is not to hand with the transformer core, and the windings may be calculated from the simplified formula

$$N = \frac{5.6}{A}$$

where N is the number of turns per volt and A is the cross-section area of the centre leg of the transformer core (i.e. the leg round which the windings are to be placed). Thus if a core with a cross-sectional area of 1 sq. in. is used it will require 5.6 turns per volt (A is measured in square inches), and cores of lesser dimensions will require more turns per volt.

For 6.3V tubes the previously mentioned voltages of 7, 7.5 and 8V will be required, so that the whole winding will give 8V, the lower voltages being taken from taps. Remember that there must also be a 6.3V tap into which the original heater supply of the tube is fed.

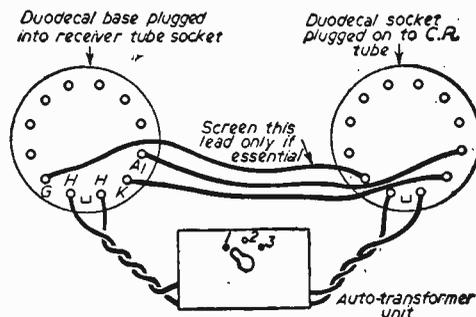


Fig. 3.—Typical arrangement of booster unit.

For the best possible efficiency and regulation the winding space of the transformer core should be full of wire—this will also mean that the thickest possible wire is used. The wire gauge should therefore be chosen from wire tables with reference to the size of the "window" (Fig. 2) and the number of turns of wire per sq. in. Allowance must be made for the dimensions of the former.

As mentioned the core of a miniature output transformer is suitable, and it may be of help to the constructor to run through the calculations which show how this might be used for an auto-

transformer for 6.3V tubes. The cross-sectional area of the core is

$$\frac{3}{8} \times \frac{7}{16} = \frac{42}{256} \text{ sq. in.}$$

Therefore the turns per volt may be taken as

$$N = \frac{5.6}{256} \times 42$$

which simplifies to

$$N = \frac{5.6 \times 256}{42} = 35 \text{ turns per volt.}$$

The area of the window is $\frac{3}{8} \times \frac{5}{8}$ sq. in., and

allowing for a thin-walled former this must be reduced to

$$\frac{5}{16} \times \frac{9}{16} = \frac{45}{256} \text{ sq. in.}$$

Thus the full winding, which is 35×8 turns, or 280 turns must be contained within this area and the wire chosen must be of a size such that in 1sq. in.

$$280 \times \frac{1}{256} \text{ turns are contained.}$$

This simplifies to

$$280 \times \frac{256}{45} \text{ turns per sq. in.} \\ = 1,593, \text{ say } 1,600 \text{ turns per sq. in.}$$

Reference to wire tables shows that 24s.w.g. enamelled wire can be wound with 1,794 turns per inch. This gives some small margin for bad winding, the affixing of tapping leads, etc. and with very careful winding this wire gauge could be employed—using 25 or 26s.w.g. enamelled wire would enable the 280 turns to be wound on with little difficulty. No allowance has been made for copper and iron losses, however, so that this transformer could handle only small currents—it should serve for an 0.3A tube. Larger cores would be preferable—with an increase in window space and a reduction in the number of turns per volt it would be possible to employ rubber-covered flex for the winding.

An ordinary output transformer has all the E and all the I laminations grouped together to give the effect of a gapped core. For use as an auto-transformer core the E's and I's should be interleaved, preferably one by one and at least in several groups.

Position

If a small auto-transformer is made it may be suspended in the wiring or assembled as a very small unit—two winding or other, larger transformers should be supported inside the receiver cabinet. It is important to keep the video signal lead as short as possible, and to achieve this it is worth while to unsolder the heater leads from the picture tube socket, leaving the rest of the leads untouched, should it not be possible to support the transformer in the leads. If a supported unit is employed it should be fitted and wired as shown in Fig. 3, using an old tube base as a plug which

fits into the present receiver tube socket. The socket fitted to the brightener unit then plugs on to the tube. As already explained, commence the brightening process by employing the lowest of the three input voltages.

When the picture tube is finally replaced remove the booster unit and store it until such time as it is again required. Do not touch the tube socket, base, or other circuits, until the receiver is switched off and the mains plug removed from the wall socket.

Rejuvenation

In rejuvenation proper, as distinct from brightening, the generally accepted method would appear to be the application of one and one-half times the normal heater voltage to the heater for one minute or so, with low voltages applied to the tube electrodes, the tube then being aged for two or three hours at normal heater voltage with no electrode voltages applied. Probably more satisfactory from the constructor's point of view is a method whereby the heater voltage is increased by 33 per cent and the tube "cooked" for a time with approximately 100V applied between the cathode and the control grid. The cathode temperature is thus raised both by the increased heater voltage and current and also by a relatively heavy current between it and the grid, the net result being the boiling off of the old oxide surface and the exposure of a new surface (or the bringing of fresh oxides up to the surface). Visual control by meter is obtained.

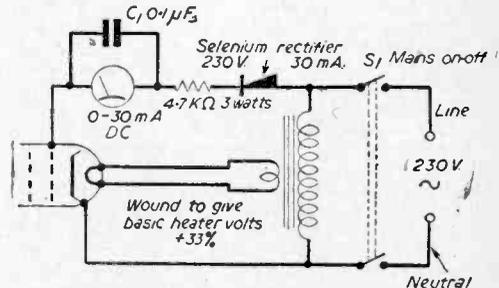



Fig. 4.—"Rejuvenator" for AC supplies.

The circuit for this type of rejuvenation is shown in Fig. 4, for A.C. supplies. In Fig. 4, a heater transformer is rewound to give 33 per cent extra heater voltage—in the case of 6.3 tubes the transformer must give 8.5 at 0.4 or 0.8A, for 0.3 and 0.6A heaters, respectively. The ordinary heater transformer already mentioned can easily be rewound for this purpose, a slightly thinner secondary wire being wound on so that the extra turns can be accommodated. Count the number of turns removed from the 6.3V secondary and multiply by 1.35 to obtain the number of turns required in the new winding.

Half-wave rectification direct from the mains side of the heater transformer is employed so that the circuit must be handled with care. It must not be directly earthed, or wired so that it can be touched accidentally. The use of a rectifier with no reservoir capacitor drops the D.C. output to

(Continued on page 516)

Servicing Television Receivers

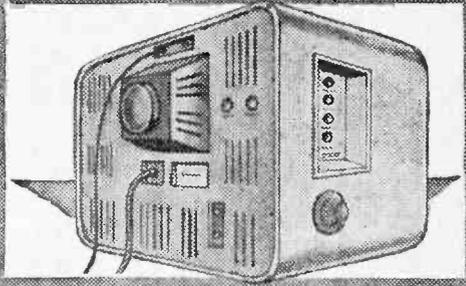

No. 57—THE H.M.V. 1824 SERIES

By L. Lawry-Johns

(Continued from page 459 of the June issue)

HAVING discussed, perhaps not in great detail, the tube circuit and timebase faults we should now turn to the vision signal circuits and from the diagram of the vision strip (Fig. 7) it will be seen that V5 is the video amplifier, this being an N153. R20, 4.7k is the anode load with a small metal rectifier as a cathode bias element. The grid leak is R19 which also functions as a load resistor for the crystal diode demodulator or detector.

Pale Picture

Although a weak picture is most often the sign of a failing tube, where it is necessary to advance the contrast and sensitivity fully, the video amplifier and detector stages should be checked. For example, the anode resistor R20 may have decreased in value thereby reducing the voltage drop and the level of the signal passed to the tube. In this case, the excessive signal passed on to the control grid by the advanced controls may overload the N153 and produce negative pictures similar to those produced when the tube is low. An ohmmeter check across R20 when the receiver is off or a voltage check when it is on will quickly reveal the presence of a faulty resistor. A voltage of about 150 should be recorded under no signal

conditions if the resistor is approximately correct but if it is low this reading will rise nearer to 200. Note however that the cathode voltage should not

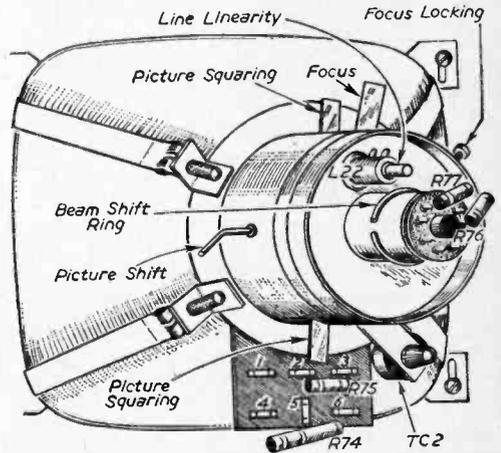


Fig. 5.—The tube unit (position of shift and L22 are different on some models).

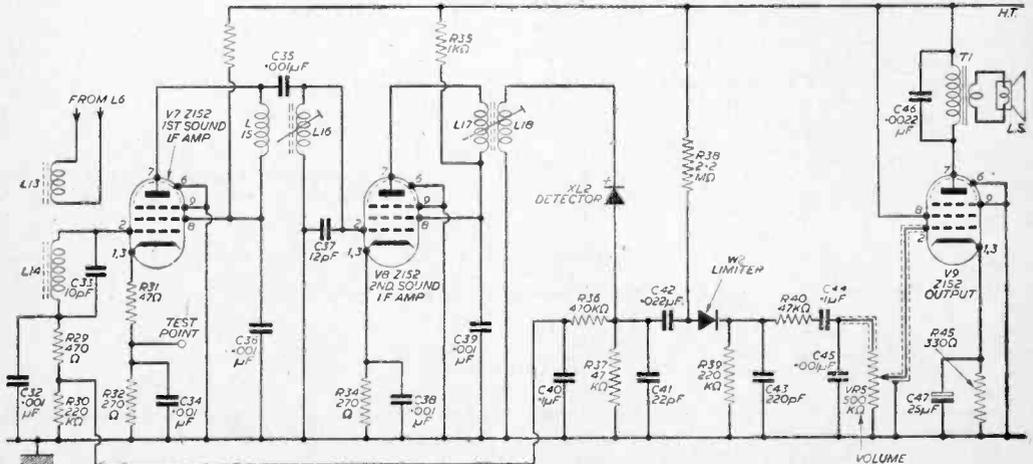


Fig. 6.—Circuit of the sound strip.

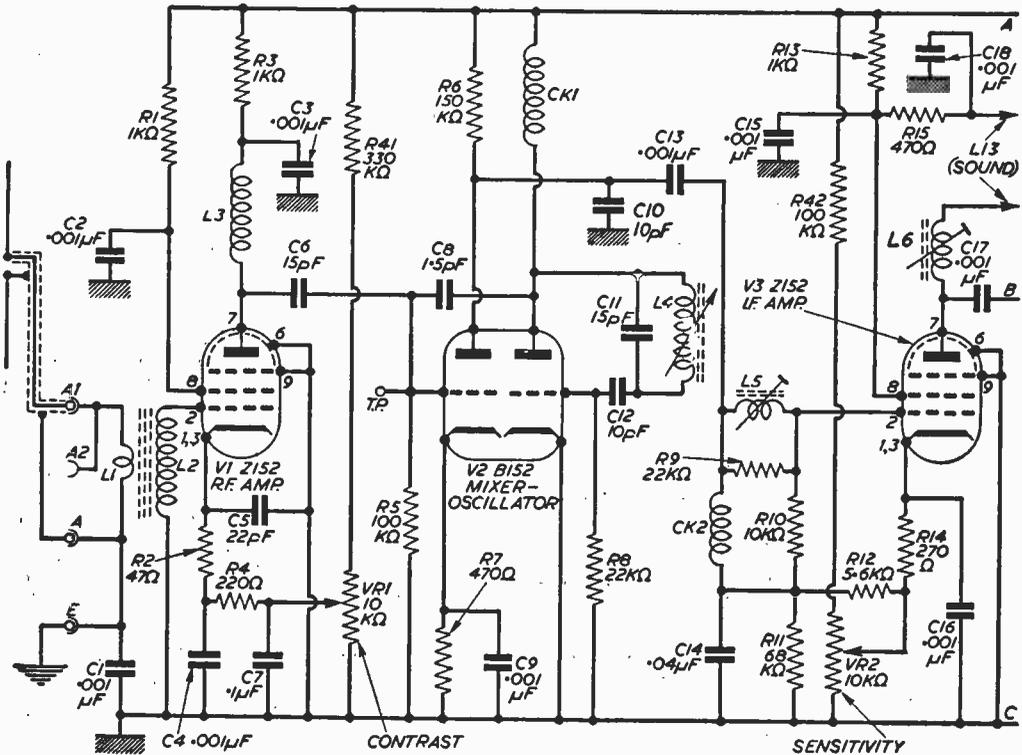


Fig. 7 (a) and, opposite, (b)—Circuit of the vision strip.

vary much from its correct value of 6. If it is much higher, the bias rectifier may have developed a high resistance causing the cathode voltage to rise, biasing back the valve resulting in reduced anode current which will again cause the anode reading to be nearer 200V. If, however, the 5V readings are reasonably correct, check the grid leak R19 as this could have fallen in value. Also check the crystal diode. Generally speaking, if the crystal diode is disconnected at one end, a resistance reading should show a high reading one way

(say over 100k) and a low reading the other i.e. when the test prods are reversed. If the same reading is obtained in either direction or even approximately the same, be this low or high, the crystal is at fault and should be replaced. The OA70 is a suitable replacement crystal (GD3, GEX35, CG12E etc.). If these stages are in order the operating conditions of V3 and V4 should be checked. It is somewhat surprising to find that a weak signal still manages to break through even when R13 or R18 have failed, although this results


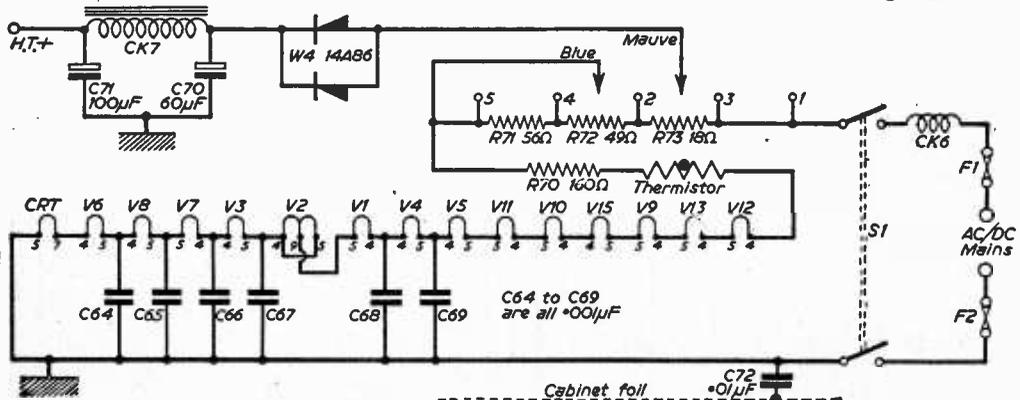


Fig. 8.—Power supply and heater chain.

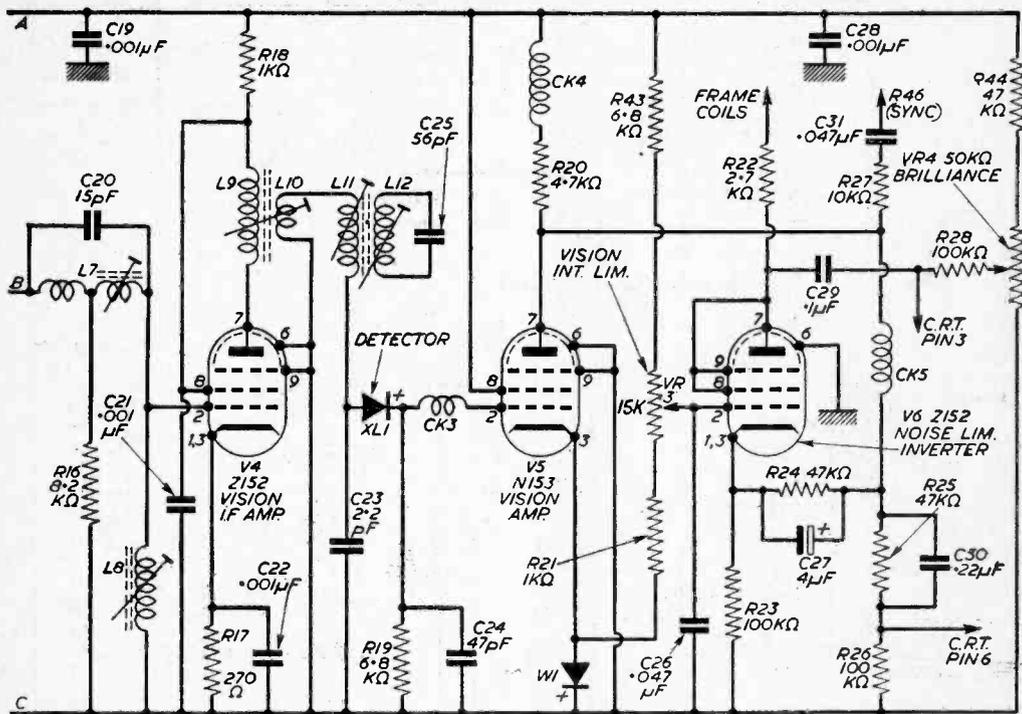

in a lack of voltage at the screen or anode and of course in the case of R13 the sound will also be almost entirely absent. These resistors often burn out as a result of a shorted 0.001 μ F decoupling capacitor or an internal short in a Z152 valve. Thus when a short is recorded at pin 8, before disconnecting the 0.001 μ F, always remove the Z152 to see if this is responsible after all.

Hum Bars

When the picture is heavily shaded so that the centre, top or bottom is lighter or darker than the rest, check V4 and V5 for heater to cathode leakage. When this accompanied by a hum on the sound, check V3, V2 and V1.

Oscillation

When the screen is brightly (but blankly) illuminated and V5 glows red hot inside, check the V4 stage 0.001 μ F (C21), which may well be open circuited. If the sound is also affected, being distorted or harsh, if present at all, check the V3 stage decouplers.

No Signals

If the raster is present but unmodulated and no sound signals are received, first see that the aerial plug is in and correctly wired. See that the tuner knob (clear plastic) has not been disturbed and then check V2 the B152 (12AT7—ECC81). If this does not produce any positive results, check V1 and V3 and the voltage supplies to all three stages.

Poor and Ragged Picture

Check as above and include C2 and the other decoupling capacitors.

Low and Distorted Sound (Fig. 6)

Check R38, the sound detector crystal diode and the limiter rectifier, then check C44 and C47, V7, V8 and V9.

Dual Band Versions

The 1824A and other models with the Suffix A have an incremental inductance tuner using a PCC84 and PCF80 to replace the V1 and V2 stages of the single band models.

After a period of use it may be found that the Band III signals deteriorate even though the tuner valves are up to standard. This can usually be overcome by careful tuning of the studs on the top of the tuner when switched to Band III.

No Signals

Check PCF80 and PCC84 making sure that these are replaced in their correct positions, and then check the resistors under the tuner unit as it is often the case that a shorted decoupling capacitor has burned out the feed resistor.

Conversion

When it is desired to fit a tuner unit to a single band model, several methods present themselves. The first and simplest method is to remove V1,

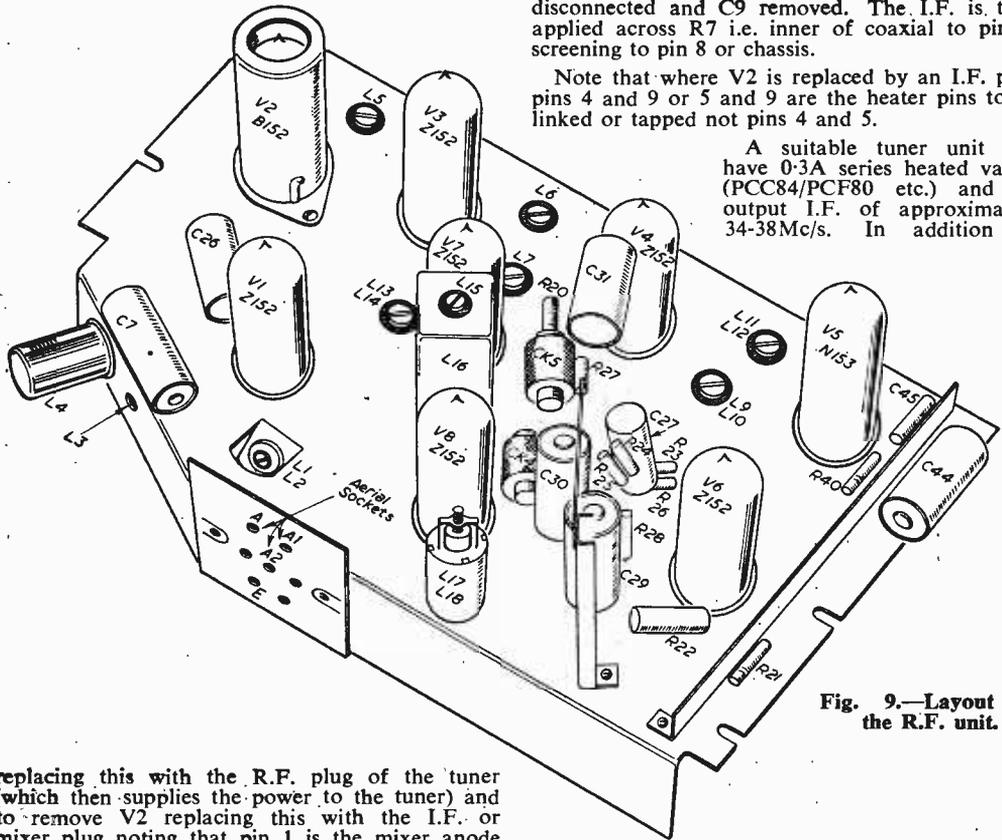


Fig. 9.—Layout of the R.F. unit.

replacing this with the R.F. plug of the tuner (which then supplies the power to the tuner) and to remove V2 replacing this with the I.F. or mixer plug noting that pin 1 is the mixer anode (not pin 6). This method is quite satisfactory in areas of reasonable signal strength but when extra gain is required, V2 can be left fitted, pins 6 and 7

disconnected and C9 removed. The I.F. is then applied across R7 i.e. inner of coaxial to pin 3, screening to pin 8 or chassis.

Note that where V2 is replaced by an I.F. plug pins 4 and 9 or 5 and 9 are the heater pins to be linked or tapped not pins 4 and 5.

A suitable tuner unit will have 0-3A series heated valves (PCC84/PCF80 etc.) and an output I.F. of approximately 34-38Mc/s. In addition to

the Cylton P38H and Brayhead 35s, several surplus tuners are suitable such as the G.E.C. BT204 and some of the Pye tuners.

BOOSTING CR TUBES

(Continued from page 512)

roughly half the A.C. input, and no elaborate smoothing is required. C1 is necessary to prevent meter flicker and the value of 0.5 μ F may need some variation with different meters—it will be sufficient with moving iron instruments which are quite satisfactory for this application, but it may have to be increased where moving-coil instruments are employed.

For greatest convenience the rejuvenator may have its output leads taken to a suitable picture tube socket so that tubes may be treated without being removed from the receiver cabinet. Switch off the receiver and remove the mains plug from the wall socket, then remove the wired socket from the base of the tube and plug in the rejuvenator socket instead. Connect the rejuvenator to the appropriate mains supply and switch on, watching the meter as the tube comes up to operating temperature. If the instrument pointer rises up the scale

to a fair reading—10mA or more—within a minute or so of switching on then the tube condition is one which rejuvenation cannot help—the screen has deteriorated, or the tube is, perhaps, gassy. If the meter reading is low, or if the pointer stays at zero, leave the rejuvenator switched on and keep a watch on the meter. A gradual rise in the current indicated shows that the cathode is responding to treatment, and rejuvenation should continue until the indicated current has risen to a final level and remained at that reading for a short time. With some tubes the treatment may be completed within minutes, with other tubes it may be worth while to continue the rejuvenation for an hour or so. The tube could then be run for an hour with normal heater voltage applied and with no voltage on the cathode, grid and anode; but usually the tube is put straight back into service. This type of rejuvenation is not always successful, or, if successful, the extra tube life gained may not be great before a further treatment is required, but every extra hour's run is worth having.

Instability

METHODS OF LOCATING AND REMOVING THIS FAULT

By K. Royal

THE term instability usually signifies that a stage in the receiver is either on the point of oscillation or that it is, in fact, vigorously oscillating. Generally, oscillation can only occur when there is some coupling between the output and input circuits of an amplifier, and when this coupling is such that the output signal fed back is in step, or almost in step, with the input signal.

In step, or in phase, feedback from output to input is known as positive feedback, and tends to increase the gain of the stage to a small degree before oscillation sets in. Oscillation will not occur if the phase of the signal fed back differs too much from the phase of the applied signal, and neither will it occur if the coupling is insufficient. When the feedback signal is exactly in phase with the applied signal, less coupling is required to promote oscillation, but progressively greater coupling is necessary as the feedback signal falls away from the phase of the input signal, until the phase difference is so great that even the tightest of coupling will not cause oscillation. The feedback signal then approaches the anti-phase condition: i.e., when the phase of the feedback signal is opposite to that of the input signal. This is known as negative feedback and results in degeneration of stage gain.

Frequency

The reference to input and output signals given above was primarily to illustrate phase- and signal-wise the conditions that must exist in order for feedback to occur. An amplifier will, in fact, oscillate without the presence of a signal given sufficient encouragement. This, of course, happens in all oscillators. The frequency of oscillation is governed by the tuned circuit elements, for it is at the tuned frequency that conditions for feedback usually occur, provided there is sufficient feedback coupling. With an oscillator, coupling is purposely introduced, but with an amplifier, positive feedback coupling is very much avoided, and various decoupling and screening artifices are adopted in order to preserve stability.

An I.F. amplifier in a TV receiver, for example, is suitably screened and decoupled so that it works only as an amplifier and not as an oscillator. However, in the event of a fault developing in one of the decoupling components or of a screen becoming disconnected from the chassis, sufficient coupling may then exist to cause oscillation, which, like a true oscillator, will generate a signal close to the tuned frequency of the I.F. transformers. If the coupling is not quite tight enough or if the phase is not quite right, the stage may only just approach the point of oscillation. In this case, oscillation may occur intermittently with applied signal or the signal may undergo distortion owing to its passage through a somewhat unstable stage.

Symptoms of Instability

There are various ways in which instability may reveal itself in a television receiver, and it may affect one or a number of stages, and not only those concerned with the signal proper. In the vision channel, instability to the extent of oscillation may result in the spurious oscillatory signal beating with the real signal, and as the two signals are not too far removed in frequency a beat frequency will be produced which gives rise to pattern interference on the picture. Since the spurious signal is somewhat unstable in frequency, the pattern effect usually drifts across the screen and alters considerably in formation (see Fig. 1). In the sound channel, the beat frequency often produces whistles on sound which alter in pitch in a random manner.

However, the spurious signal is usually of large amplitude, and in this case completely overrides the real signal. When this happens, the video detector produces a large D.C. voltage from the spurious signal which makes the control grid of the video amplifier valve positive. This causes abnormal conduction in the valve, which results in

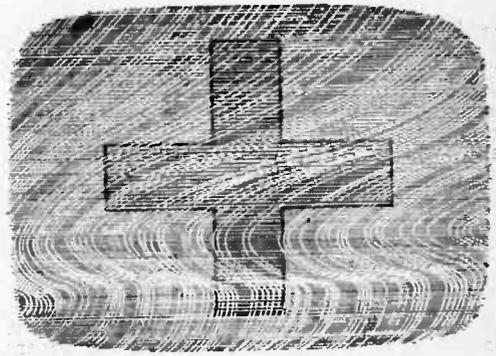


Fig. 1.—Moderate instability usually causes patterns to drift across the screen in a random manner, as shown.

a fall in potential at the anode, and since the anode is coupled to the picture tube cathode, a like reduction in potential also occurs here. This means that the tube grid is likely to be more positive than the cathode, and owing to this, a bright raster, which is often uncontrollable, appears on the tube screen. This symptom is invariably accompanied by overheating of the resistor in the anode circuit of the video amplifier valve as the result of the current rise. It should be pointed out that very

similar symptoms may be caused by a heater to cathode short in the tube itself, but instability can be proved as will be explained later.

Altered Bias Conditions

There are times, however, when the spurious signal produced by instability falls outside the passband of the tuned stages. A fault in an I.F. amplifier valve, for example, may cause a form of electron oscillation which is rectified by the vision detector, but owing to its difference in frequency from that of the real signal does not cause patterning. However, the D.C. voltage produced by the detector owing to the spurious signal could result in disturbance of the biasing of the video amplifier valve. When this happens, either an unmodulated raster may occur on the screen or, if a picture is present, this may appear somewhat weak and watery looking, and it may be difficult to hold it in lock.

Heavy oscillation in the vision channel could cause failure of the vision detector diode, especially if of the germanium type. Also, the D.C. applied to the video amplifier may overload this valve, and result in the screen grid becoming red hot.

In the sound channel, instability may cause a beat note, as mentioned earlier, but if the instability is heavy and the spurious signal much stronger than the real signal, the sound will not be heard, but the sound channel will seem extra lively and several valves may seem to have developed microphony, and give a ringing sound from the loudspeaker when they are tapped.

Instability in the Timebases

Instability sometimes occurs in the timebase circuits, but in this case it is usually a low-frequency oscillation that results. In the frame

picture may have the appearance of a sine wave or saw-tooth wave, depending on the kind of signal produced by the instability.

Checking for Instability

If a high resistance voltmeter is connected across the vision-detector load resistor with the aerial connected and the receiver working normally, a D.C. voltage will be recorded whose value alters with change in picture content. This is the normal action of the circuit. However, on removing the aerial from the set, the voltage should collapse to zero. A set which is unstable in the vision channel will give a constant voltage at this point (see Fig. 2) even with the aerial removed. If this voltage falls to zero when the control grid of the final vision I.F. amplifier valve is shorted to chassis, then one can be absolutely certain that instability is present. On sound, a similar test can be applied if it is not obvious that the sound channel is in a state of oscillation, as revealed from the symptoms given earlier.

If uncontrollable brightness leads one to suspect instability or a possible tube fault, the tube can be cleared from blame if the normal control of raster brightness is restored on shorting the control grid of the final vision I.F. amplifier valve, as before (see Fig. 2).

Cause and Remedy

In the majority of cases of sudden instability, open-circuit of one or more of the small decoupling capacitors associated with an I.F. amplifier valve is responsible, but it is often difficult to pinpoint the stage responsible since other stages may oscillate in sympathy, and the feedback loop may exist over two or more stages. One of the best ways of bringing the culprit to light is to shunt each decoupling capacitor in turn with a test component of a similar type while observing the instability symptom on the screen or on a meter (see Fig. 3).

The test component should have very short leads and can often be held in position without soldering by pressing the lead to chassis in good connection with a screwdriver and arranging for the other lead to make connection with the appropriate tag on valveholder or tag strip, etc. The actual component should not be touched when this test is made. If the instability is cleared on shunting a capacitor in this way, the original capacitor should be replaced, for it is almost certainly faulty. Alternatively, each capacitor can be replaced temporarily in turn until the faulty one is located.

Valves sometimes cause the trouble, and in some sets EF80's have been known to produce a spurious signal removed from the real signal's frequency.

(Continued on page 532)

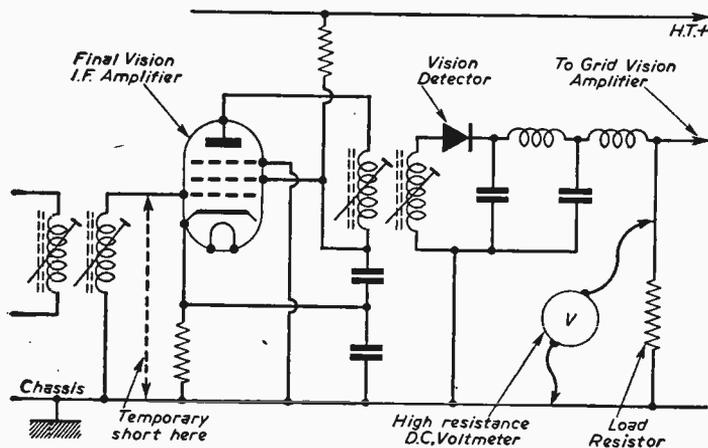


Fig. 2.—Instability may show as a constant voltage across the vision detector load resistor with the aerial disconnected from the set. This is proved by the voltage collapsing when a short is applied to the control grid of the final vision I.F. valve.

timebase, this could cause the picture to judder vertically either at a speed that is visible or so fast that the effect is essentially that of impaired interlace. In the line timebase, the vertical parts of a

TUBES

DIRECT FROM OUR FACTORY
New low prices. New top quality guns.
ALL GUARANTEED

Carrriage and Insurance 12/6

CRM92, MW2-7, MW22-14, MW22-14C, MW22-17, MW22-18, etc. £2

19KPA, 121K, C129, CRM121, CRM121A, CRM121B, CRM122, CRM123, MW31-14C, MW31-16, MW31-18, MW31/74, etc. £2-10

141K, 7201A, C14FM, CRM141, CRM142, CRM143, MW36-24, MW36-44, etc. £3-5

17ASP4, 171K, AW38/21, C17EM, CRM171, CRM172, MW43-84, MW43-89, 7401A, AW43-80, C14BM, C175M, CRM151, CRM152A, CRM152B, CRM153, CRM173, MW43-80, MW41-1, etc. £3-15

AW53-90, CRM21, MW53-20, MW53-80. £4-15

6 MONTHS REVAUCUMED £2

12 MONTHS REGUNNED £3-10

12 MONTHS NEW TYPES

MW31/74 £4-10

MW36/24 £7-15

MW43/84 £8-10

13 CHANNEL TV's

TABLE MODELS, FAMOUS MAKERS. Complete with all valves and tubes. These sets are unequalled in value due to huge purchase direct from source. They are untested and are not guaranteed to be in working order.

AMAZINGLY POPULAR-IDEAL SECOND SETS

12" - £3.19. (p. & p. 12/6)

14" - £6.19. (p. & p. 10/6)

17" - £9.19. (p. & p. 17/6)

12" 5 CHANNEL TV'S 45/- (p. & p. 12/6)

14" 5 CHANNEL TV'S 85/- (p. & p. 12/6)

SPECIAL OFFERS

ALL DRY PORTABLES
Stella Lightweight Shoulder-strap model. super finish, economy valves, listed at £13-2-6, medium and long waves, absolutely complete £7.19. in manufacturers sealed cartons.

4-SPEED RECORD PLAYERS
Latest B.S.R. TU9. Turntable together with lightweight Silar Galaxy dual sapphire crystal turnover pick-up head. £3.10. Carr. Truly amazing value at 3/-.

100 CONDENSERS 10/-
Assortment of miniature silver mica and ceramic condensers. 3-10,000 PF. List value over £5.

100 RESISTORS assortment 7/6
±2 watt.

PM SPEAKERS 3 ohms, top makes, performance guaranteed.
8in. 8/- 5in. 7X4 11/- 10in. 10Kx 13/- 6in. 7X4 11/- 10Kx 13/-

DIODES General purpose, famous make, 9d. 8/- doz. GEX44 type, 3/9.

CO-AX

standard and low loss, 25 yds. 12/6. 50 yds. 22/8. 100 yds. 42/8. Co-ax. Plugs 1/3. Wall outlet boxes, 3/6.

12in. TV's 5 channel table models including speaker, line trans. cabinet. Top makes requiring only valves and tube to complete, your choice if available (carr. 4/-). (Or £8 per dozen, carr. free.) 15/-

14in. TV's 5 channel as above 35/- (carr. 4/-).

CONNECTING WIRE
25 FT. P.V.C. Insul., excellent 1/- (5 coils, diff. colours, 4/6)

RECTIFIERS 12 volt 3 1/2 amps., 9/6. 250 v. 90 m.a., 5/-; R.M1, 6/6; R.M2, 8/-; R.M3, 9/-; R.M4, 15/6; R.M5, 21/-; 1A486, 17/-; 1A497, 23/-; 1A4100, 25/-; 19RCL1-1-1-1, 7/9; 18RA1-1-1-1, 7/9; 18RD2-2-2-2, 14/-; 14RA1-2-2-2, 17/-; 14RA1-2-2-3, 20/-

TURRET TUNERS
38 Mc. IF. Standard Famous Make with coils listed £7. Complete with PCF80 and PCF84 valves, boxed (carr. 3/-). 45/-
Ditto complete except for 1 oscillator coil, 29/-.
Ditto 16Mc. IF. complete all coils, 55/-.

EXTERNAL I.T.V. CONVERTERS WITH INTERNAL POWER PACK. Finished in hammered gold. Very compact. Trimming controls. Gain and Trimming controls listed at £7.7. Our Price, carr. 2/6. 59/-

SINGLE RECORD PLAYER (carr. 4/-)
COLLAIO 4-speed 4/36P ... £5 19 0
GARRARD 4-speed 4SP ... £7 7 0
GARRARD 4-speed TA MKII ... £8 19 0

10 RECORD AUTOCHANGERS (carr. 4/-)
B.S.R. Latest UA3 AUTO ... £7 19 0
H.S.R. (U8) AUTOCHANGERS ... £8 15 0
COLLAIO CONQUEST CHANGERS ... £9 0 0
GARRARD RC1201A MKII ... £8 7 6
GARRARD RC121/4 MKII ... £8 19 0

TAPE RECORDERS (Carr. Free)
LATEST ELPHO. Using the B.S.R. Monarchek 3 1/2 ips. takes 3 1/2. spools, and is absolutely complete in attractive carrying case. 26 sns. ALBA tape recorder. similar to above. 28 sns. FIDELITY Super tape recorder. 29 sns. B.S.R. MONARCHEK TAPE DECKS 29 10 0
GARRARD TRANSCRIPTION DECKS £13 15 0
SMASH HIT! Latest SAGATONE Recorder using Collaro Transcription 3-spd. Deck, Super-impose, 5 Valves, Ex-Replication, 2-Tone Case. Worth £45. Amazing Value. 29 Gns.

VALVES BY RETURN OF POST

10% DISCOUNT SPECIAL OFFER TO PURCHASERS of any SIX VALVES marked in black type (15% in dozen). Post: 1 valv, 6d., 2-11, 1/-.

NEW LOW PRICES GUARANTEED 3 MONTHS

FREE TRANSIT INSURANCE. All valves are new or of fully guaranteed ex-Government or ex-military origin. Satisfaction or Money Back Guarantee on goods if returned unused within 14 days.

02A	5/6 8AQ5	6/- 6KGT	7/9 6X50	5/6 12J5GT	3/6 43	7/8 DP33	9/9 EOC81	5/9 EL91	4/9 N103	18/- 8U2150A4	7/8 UCH81	8/6	
1ASGT	6/- 6AT6	7/- 6KGT	6/6 6X50GT	6/- 12K7GT	5/6 5905	9/8 DP91	4/- EOC82	8/6 EM34	8/6 N152	10/8 741	7/8 UCL81	11/3	
1A7GT	11/9 6AU6	7/9 6K7	5/9 7A7	10/6 12K9GT1	16/6 5L6GT	9/8 DP96	7/8 EOC83	7/8 EM80	9/3 PA1	4/6 TR30C	12/6 UCL83	12/6	
1C9GT	9/9 6B7	9/9 6K7G	5/9 7B5	12/8 12Q7GT	5/6 59K10	12/6 CB63	6/9 EOC84	8/6 EM81	9/3 PA1	9/3 PA1	8/- UP41	8/8	
1D5	9/9 6B9G	3/6 6K7GT	5/- 7B6	9/8 12M7	6/- 59K10	9/8 DP97	5/6 EOC85	8/6 EM84	9/9 PABCR90111	U18	8/6 UP42	6/9	
1D6	9/9 6B9G	3/6 6K7GT	5/- 7B6	7/3 12M7	5/6 61SPT	11/- DR77	7/8 EOC86	9/9 EM85	10/6 PCC84	7/8 ZT2	6/9 UP43	9/-	
1HGT	9/9 6B9G	6/- 6K8GT	10/- 705	7/6 12M7	5/6 75	8/- DK32	11/9 EOC87	9/9 EN81	16/- POC85	9/3 U34	15/- UP55	9/-	
1L4	3/6 6B9G	12/6 6K25	7/8 707	7/3 12N7GT	8/6 77	6/8 DK91	8/- ECH21	8/6 EY81	9/9 SMALL	8/9 POC86	13/9 U26	11/-	
1LD5	3/6 6B9G	6/- 6L1	12/6 708	9/8 12T7	9/8 78	7/8 DK92	8/6 ECH22	8/6 EY86	8/- POC87	7/8 U31	7/3 UP49	7/3	
1LN3	4/6 6B9G	6/- 6L5	9/9 7H7	7/8 1487	14/9 80	6/8 DK96	7/9 ECH23	8/6 EY86	8/- POC88	7/8 U31	11/- UP59	7/8	
1NGST	9/9 6B9G	9/3 6L6G	9/- 7K7	8/- 19A25	7/8 83	8/9 EDC13	8/9 ECH24	8/6 EY86	6/- POC89	7/8 U31	13/- UP64	12/6	
1R5	6/- 6B9G	7/8 6L7	9/- 7R7	10/6 19BGG015	90AV	4/8 EDC15	9/9 ECH25	8/6 EY86	6/- POC90	8/6 U35	8/9 UP46	9/8	
1S4	8/6 6B9G	6/6 6L7G	7/8 787	9/8 20D1	9/8 11727	10/8 EDC18	9/9 ECH26	10/- E241	7/8 PCL53	11/6 U37	26/8 UL84	7/6	
1S5	5/6 6B9G	6/6 6L18	9/- 7V7	7/9 20P2	9/8 135AT	16/- DL01	8/9 PCL33	14/8 E280	6/8 PCL4	9/9 U43	8/9 UM80	9/8	
1T4	4/- 6C4	3/6 6L19	12/6 7Y4	7/- 20L1	13/8 729A	28/- DL02	6/- E292	12/- E281	7/- PEN25	4/6 U60	6/- UM8	12/6	
2D21	4/6 6C5	5/6 6L13	8/6 7Z4	7/6 20P1	11/6 807A	5/- DL94	7/- E293	3/3 GT10	7/- PEN45	7/8 U25	5/- U77	9/8	
3A4	5/6 6C6	4/9 6L12	7/8 8D3	3/6 20P3	12/6 807B	3/9 DL96	7/8 E294	4/3 G232	8/9 PEN48	5/3 U78	5/8 U78	15/6	
3A5	9/6 6C9	9/6 6L20	8/6 10C1	11/- 20P4	17/- 808	15/- EA50	8d. FF40	13/8 G232	12/6 PL33	9/- U75	5/8 UY1N	11/6	
3Q4	7/3 6D0DG	18/6 8N7	6/8 10C2	13/6 30P5	18/- 955	3/9 EAC90	8/6 EF41	8/6 EF42	7/8 HADCS0	9/6 PL38	14/6 U281	9/8 UY21	11/6
3QG7	8/9 8C8	9/8 8P1	14/- 10C14	9/8 25AG	8/6 2050	3/6 EAF42	8/6 EFS0	8R-2	H1A1DD9	9/6 PL21	9/9 U282	15/- UY86	6/9
3S1	6/- 8D5	6/- 8P5	3/- 10P1	10/3 25LGT	8/- 5763	10/- EB34	1/6 EFS0	USA	7/8 PL92	7/8 U301	14/- UY80	5/8	
3V4	7/- 8D2	3/9 8P8	12/6 10P9	8/- 25Y6	9/- 9001	4/- EB41	7/-	2/- EK732	6/9 PL53	7/8 U302	12/6 UY81	11/6	
3E4G	9/6 8D3	12/6 8Q6GT	9/8 10L14	8/3 25Z40	7/3 9003	4/- EB42	3/9 EF54	3/9 EF54	6/9 PL53	11/- U329	12/6 UY81M	11/6	
3U4G	5/- 8D6	4/9 9Q7GT	9/8 10L13	8/3 25Z40	7/3 9003	4/- EB41	9/8 EF80	5/3 K738	9/- PM84	10/6 U339	11/- U76	6/8	
3V4G	9/6 8E1	5/9 8R7G	7/8 10L15	8/3 25Z58	9/- AZ31	9/- EBC33	5/- EF85	7/- K744	9/6 PZ25	16/- U403	9/6 U77	4/9	
3Y3G	6/- 8E6	6/3 8A7	5/9 10P13	9/8 27S10	16/- 836	3/8 EBC41	8/6 EF86	10/3 K745	8/6 PY31	8/3 U404	6/8 UY81	5/3	
3Z4G	8/6 8E12	3/8 8S17	4/8 10P18	8/- 30C1	7/8 885	4/9 EBC41	8/6 EF86	10/3 K745	8/6 PY31	8/3 U404	6/8 UY81	5/3	
3Z4GT	11/- 8F13	8/9 8A35	5/- 12A9	5/3 30P7	7/9 877	7/- CR131	21/- EBF90	8/6 EF91	9/- PY32	10/6 U481	19/- X61M	12/6	
3A7	10/- 8F14	8/8 8S17	5/3 12A9	9/9 30L1	7/9 8C133	13/- EBL21	14/- EBF95	9/9 K762	6/8 PY90	7/- UABCS0	8/9 X63	9/6	
3ASG	9/6 8F15	9/8 8S17GT	6/- 12A9H	7/9 30P4	12/6 8Y31	21/- EBL21	21/- EBF95	7/9 K762	6/8 PY90	7/- UABCS0	8/9 X63	9/6	
3ASGT	13/6 8F16	8/8 8S17GT	4/9 12A76	7/9 30P4	12/6 8Y31	21/- EBL21	21/- EBF95	7/9 K762	6/8 PY90	7/- UABCS0	8/9 X63	9/6	
3AB3	8/3 8F33	6/9 8S27	6/3 12A77	5/8 30P12	8/- 1943	1/8 ECE1	3/8 EL32	4/8 EL32	4/8 EL32	4/8 EL32	4/8 EL32	4/8 EL32	
3AC7	4/6 8G3	2/- 8S27	5/- 12A7	6/8 30P16	7/9 877	3/9 ECG0	3/8 EL33	9/- EY83	6/8 R15	12/6 UBF89	8/6 X79	10/6	
3AG5	4/3 8G5	4/3 8G5	4/3 8G5	7/- 30P14	10/6 8D152	6/8 ECG1	4/8 EL35	11/6 L83	2/9 R19	12/6 UBL21	14/6 Y68	8/8	
3AK5	8/6 8G5GT	3/9 6V8G	5/6 12B84	8/- 35LGT	9/- DA30	12/6 ECG11	9/8 EL37	11/6 LN152	7/8 SD6	9/- UOC84	8/4 Z83	6/8	
3AL5	4/9 8J6	4/- 8V8GT	8/8 12B7	10/6 35Z4GT	5/8 DA39	9/8 ECG33	4/9 EL41	8/6 MU14	8/- SP4	2/6 UCF90	16/- Z77	3/6	
3AM5	4/6 8J7	7/8 8Z8	8/8 12C8	8/8 35Z5GT	8/6 DA51	5/3 ECG4	9/- EL42	9/8 N7	11/- SP1	2/6 UCH21	4/6 Z152	5/3	
3AM6	3/6 8J7G	5/6 8X4	5/6 12E1	12/6 42	7/8 DA596	7/9 ECG35	6/9 EL41	7/- N78	15/- 8U25	15/- UCH42	7/8 Z152	5/3	

Post: 2 lbs. 1/6, 4 lbs. 2/-, 7 lbs. 2/9, 15 lbs. 3/6 etc. No C.O.D. ALL ITEMS LESS 5% & POST FREE IN DOZENS. (Callers always welcome). LIST OF 1000 SNIPS 6d. P.O. BOX 21 (W) 350-352 FRATTON ROAD, PORTSMOUTH.

TECHNICAL TRADING CO.

R.S.C. (BRADFORD, LEEDS) (Leeds) Ltd. and MANCHESTER

54-56 MORLEY ST. (Nr. Alhambra) BRADFORD. 5/7 COUNTY ARCADE, BRIGGATE, LEEDS, 1. 8/10 BROWN ST. (Market St.), MANCHESTER. Mail orders to Dept. N., 29-31 Moorfield Road, Leeds, 12.

ST. (Nr. Alhambra) BRADFORD. 5/7 COUNTY ARCADE, BRIGGATE, LEEDS, 1. 8/10 BROWN ST. (Market St.), MANCHESTER. Mail orders to Dept. N., 29-31 Moorfield Road, Leeds, 12.

Post Terms C.W.O. or C.O.D. No. C.O.D. under £1. Postage 1/9 extra under £2. 2/9 under £5. Open to callers 9 a.m. to 6 p.m. Wednesdays until 1 p.m. S.A.E. with inquiries, please. Trade supplied.

R.S.C. TRANSFORMERS

Fully Guaranteed
Interleaved and Impregnated
Primaries 200-230-250 v 50 c/s screened.
TOP SHROUDED DROP-THROUGH
280-0-280 v 70 ma, 6.3 v 2 a, 5 v 2 a .. 17/9
280-0-350 v 80 ma, 6.3 v 2 a, 5 v 2 a .. 18/9
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a .. 23/9
300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a .. 23/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a .. 23/9
350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a .. 29/9

FULLY SHROUDED UPRIGHT
280-0-280 v 60 ma, 6.3 v 2 a, 5 v 2 a
Midget type 21-3-3 in. .. 17/9
250-0-250 v 100 ma, 6.3 v 4 a, 5 v 3 a .. 25/9
300-0-300 v 100 ma, 6.3 v 4 a, 5 v 3 a .. 27/9
350-0-350 v 100 ma, 6.3 v 4 a, 5 v 3 a .. 27/9
350-0-350 v 150 ma, 6.3 v 4 a, 5 v 3 a .. 35/9
425-0-425 v 200 ma, 6.3 v 4 a, C.T. 6.3 v 4 a, C.T. 5 v 3 a .. 49/9

FILAMENT TRANSFORMERS
All with 200-250 v 50 c/s Primaries: 6.3 v 1.5 a, 5/9; 6.3 v 2 a, 7/6; 4.0-6.3 v 2 a, 7/9; 12 v 1 a, 7/11; 6.3 v 3 a, 8/11.

CHARGER TRANSFORMERS
200-250 v 0-9-15 v 11 a, 12/9; 0-9-15 v 3 a, 16/9; 0-9-15 v 5 a, 19/9; 0-9-15 v 6 a, 23/9.

OUTPUT TRANSFORMERS
Midget Battery Pentode 68.1 .. 3/9
Standard Pentode 5,000 to 3 ohms .. 5/9
Small Pentode 5,000 to 3 ohms .. 5/9
Standard Pentode, 7/8, 10 to 3 ohms .. 5/9
Push-Pull EL84 to 3 or 15 ohms .. 18/9
Push-Pull 10-12 watts 6V6 to 3 or 15 ohms .. 18/9
Push-Pull 10-12 watts 6V6 to 3, 5, 8 or 15 ohms .. 19/9

SMOOTHING CHOKES
100 ma 10 h 250 ohms .. 8/9
80 ma 10 h 350 ohms .. 5/6
60 ma 10 h 400 ohms .. 4/11

SELENIUM METAL RECTIFIERS

Special quotes for quantities of 50 to 5,000.
E.T. (H.V.)
250 v 50 ma .. 3/11
250 v 80 ma .. 5/11
250 v 100 ma .. 6/11
Contact Cooled .. 12/3
250 v 80 ma .. 6/11
250 v 75 ma .. 6/11
F.W. (Bridge) 8/11
6/12 v 1 a .. 3/11
6/12 v 2 a .. 6/11
6/12 v 3 a .. 9/9
6/12 v 4 a .. 12/3
6/12 v 5 a .. 14/6
6/12 v 6 a .. 15/6
6/12 v 10 a .. 25/9
6/12 v 15 a .. 27/9

CO-AXIAL CABLE in. 75 ohms 14/36 .. 8d. yd.

BATTERY SET CONVERTER KIT
All parts for converting any normal type of Battery Receiver to A.C. mains 200-250 v 50 c/s. Supplies 120 v, 90 v or 60 v at 40 ma, fully smoothed and fully smoothed L.T. of 2 v at 0.4 to 1 a. Price including circuit, 49/9. Or ready for use, 9/9 extra.

ALL DRY RECEIVER BATTERY ELIMINATOR KIT.—All parts for the construction of a unit (metal-case 5 1/4" x 2 1/2") to supply Battery Portable receivers requiring 90 v and 1.5 v. Fully smoothed. From 200-250 v 50 c/s mains. Price, inc. point-to-point wiring diagrams, 39/9. Or ready for use, 46/9.

D.C. SUPPLY KIT.—Suitable for Electric Trains. Consists of mains trans. 200-250 v 50 c.p.s. A.C. 12 v 1 a Selenium F.W. Bridge Rectifier, 2 Fuseholders, 2 Fuses, Change Direction Switch, Variable Speed Regulator. Partially drilled Steel Case, and Circuit. **33/9**

TELEVISION RECTIFIERS
250 v 200 ma. Size 3 x 1 1/2 in. Brand New. 6/9.

EX-GOVT. MAINS TRANSFORMERS

All 200-250 v 50 c/s input. Removed from New ex-Govt. units, **22/9**
270-0-275 v 100 ma, 6.3 v 7 a, 5 v 3 a
260-0-265 v 150 ma, 6.3 v 11 a, 5 v 3 a, 5 v 3 a .. 29/11
350-0-350 v 100 ma, 6.3 v 2 a, 5 v 2 a .. 18/9
0-10-25 v 24 a. .. 79/6. carr. 15/3

AUTO 0-110/120-220/240 v, 50 watts .. 8/11

EX-GOVT. SMOOTHING CHOKES—
60 ma 5-10 h 250 ohms .. 2/11
80 ma 10 h 150 ohms .. 6/9
100 ma 5 h 100 ohms Tropicalised .. 3/11
100 ma 8-10 h 100 ohms Parmeko .. 6/9
120 ma 12 h 100 ohms .. 8/9
150 ma 10 h 150 ohms .. 9/9
200 ma 3-5 h 100 ohms Parmeko .. 7/9

EX-GOVT. CASES. Well ventilated, black crackle finished, undrilled cover. Size 14 x 10 x 8 1/2 in. high. **IDEAL FOR BATTERY CHARGER OR INSTRUMENT CASE, OR COVER COULD BE USED FOR AMPLIFIER.** Only 9/9. plus 2/9 postage.

BATTERY CHARGERS
For 200/250 v 50 c/s A.C. mains. 12 months' guarantee. Attractive, well ventilated hammer finished cases, 8 v or 12 v, 4 amp. with meter and variable charge rate selector, as illustrated **69/9**
carr. 5/-
Or Deposit 13/3 and 5 monthly payments of 13/3. 6 v or 12 v 1 amp type. Also suitable for electric train power supply. Only 29/9 post 2/9.



NEW! DO-IT-YOURSELF TRAINING TECHNIQUE in RADIO & ELECTRONICS

You LEARN while you BUILD...

SIMPLE...PRACTICAL...FASCINATING...

ANNOUNCING—after years of successful operating in other countries—the latest system in home training in electronics introduced by a new British training organisation. **AT LAST**—a simple way of learning —by practical means—the 'how and why' of electronics with the minimum of theory and no mathematics! **YOU LEARN WHILST BUILDING** actual equipment with the components and parts which we send you —and you really have fun whilst learning! And afterwards—you have a first rate piece of home equipment plus the knowledge of how it works and how it can be serviced. **THIS NEW SYSTEM** brings an exciting new opportunity and is very moderate in cost. Post the coupon now without any obligation for full details.



LOTS OF INSTRUCTIVE EXPERIMENTS AT HOME!

No Mathematics!

FREE
POST TODAY

To: **RADIOSTRUCTOR** (Dept G29)
46 Market Place, Reading, Berks.
Please send brochure without obligation to:

Name

Address

(807) 7-60

RADIOSTRUCTOR
BRITAIN'S LEADING ELECTRONIC TRAINING ORGANISATION

TELEVISION TUBES REBUILT

- ★ A NEW GUN IN EVERY TUBE
 - ★ BUY DIRECT FROM THE FACTORY
 - ★ 12 MONTHS' GUARANTEE
- 12 inch £5.00**
14 inch £5.10.0
17 inch £6.10.0
- Immediate dispatch on receipt of Remittance*
- Carriage and insurance 12/6 extra
- £1 Refunded on receipt of your old Tube**
- SPECIAL TERMS TO THE TRADE**

MARSHALLS for TELEVISION LTD.
131 St. Ann's Road, Tottenham, London N15.
STAMFORD HILL 3267

Is There Enough Signal?

INVESTIGATING SIGNAL STRENGTH

By G. J. King

ONE of the major problems facing television experimenters and, indeed, service technicians lies in determining whether a poor picture is due to a set fault or weak aerial signal. After considerable experience of a particular type of set, using a specific make and type of aerial in an area of known signal conditions, the service technician is usually able to decide with reasonable accuracy whether it is the set or aerial at fault. Unfortunately, the original signal conditions are not always known. The area may be new to the technician or experimenter, or a poor picture after a Band III conversion may well pose the question—is there enough signal?

The strength of signal at the end of a downlead can be measured fairly easily in microvolts or millivolts on a signal strength or field strength meter, but as these are rather expensive instruments it is unlikely that the experimenter will have one at hand, and it may happen that the technician is similarly placed. There are several things that can be done to avoid making the answer to the question a total guess, but before considering these, let us examine the symptoms of insufficient signal.

Noise Effect

Noise on a television picture is the background grain and ragged vertical edges of a picture component when the contrast and gain controls are turned up in an endeavour to secure a desirable black/white ratio. In severe cases, the effect is much like random, closely-spaced, small white spots, giving the picture a grey, snow-storm appearance. This happens in many areas on ITA programmes owing to the Band III signals being weaker than the Band I signals, the latter giving a BBC picture mostly free from the noise effect.

Service Areas

It should be made clear that the signal strength on Band III is invariably below that on Band I due to the higher frequencies and other factors. This means that in the outer service area of co-sited BBC/ITA transmitters a change from BBC to ITA will result in a distinct increase in noise effect. This may be overcome to some extent by the use on Band III of an aerial which is of more elaborate design than that used on Band I, but the problem may not be fully resolved by this artifice.

The noise effect is caused by very small spurious signals being generated in the valves and

components of the early stages of the set. Random movement of electrons in resistors and the electron flow in valves contribute to the overall noise signal. In order to prevent the spurious noise signal from revealing itself in the form described earlier, the aerial signal must be far stronger so that the noise effect is masked by the required signal. The noise signal in a well designed set is often below 5 μ V. Virtually no noise is displayed when the aerial signal is some 100 times stronger than the noise signal, but when the signal noise ratio drops to about 10:1, slight picture noise is noticeable, and the noise effect progressively increases as the signal noise ratio decreases.

The noise signal not only modulates the picture tube in such a way as to cause spots on the picture but it also appears at the sync separator and thus enters the timebase circuits, resulting in irregular triggering of the timebases. This gives the ragged vertical edges to parts of the picture, and in severe cases causes vertical judder and intermittent rolling of the frame. On sound the effect is that a definite hiss forms a background accompaniment to the sound.

Increase in Receiver Noise Factor

It is now apparent that the ratio between the aerial signal and the noise signal generated by the set itself governs the extent of the noise effect on the picture. Unfortunately, there are various faults

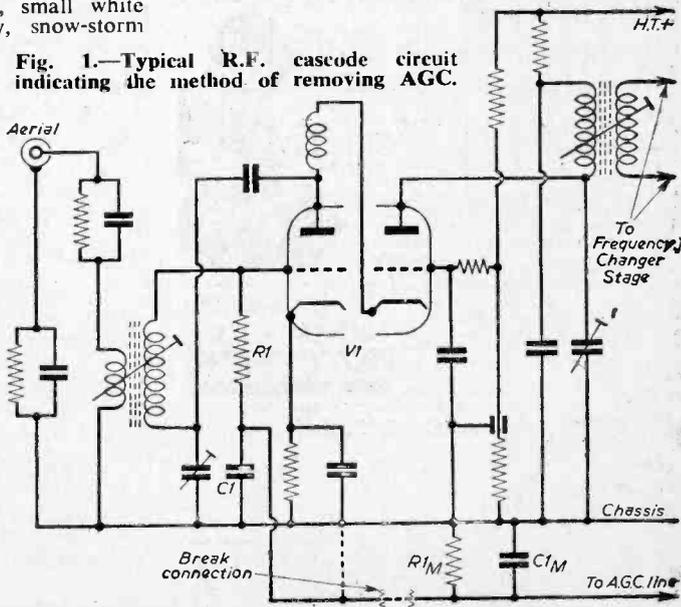


Fig. 1.—Typical R.F. cascode circuit indicating the method of removing AGC.

that can occur in the set to increase the generated noise signal. Thus, noise may show up on a picture even though the aerial signal remains unchanged. This is the reason why it is often difficult to decide without a signal strength test whether the set or aerial is at fault.

The receiver noise factor may increase due to a low emission R.F. or frequency changer valve, or as the result of an increase in value of a resistor, alteration in value of a capacitor or even misalignment. With sets using a multi-channel tuner a substantial increase in noise factor would be likely to be seen on both BBC and ITA pictures, though to a greater extent on ITA pictures for the reason given earlier. On the other hand, a small increase in noise factor may leave the BBC picture virtually unaffected and yet produce noise on the ITA picture. This is because the BBC signals are sufficiently strong to outweigh the increased noise factor, while the weaker ITA signals cannot do this.

Signal Strength Test

However, one cannot be certain that the increase in noise on ITA pictures is definitely caused by an increase in noise in the set, as the same symptom would result from a fault in the Band III aerial, downlead or both. A signal strength test would prove this without doubt, of course. Moreover, even if both pictures are suddenly affected by noise one still cannot be certain that the set is at fault, since if a diplexer is used to combine the two signals at the aerials, the downlead again may be defective, or a fault may have developed in the diplexer or aerial plug or socket at the set.

The query department of PRACTICAL TELEVISION is often asked to advise on how to eliminate noise on the ITA picture after a converter or tuner has been fitted, the BBC pictures being received without noise. It is almost impossible to answer this

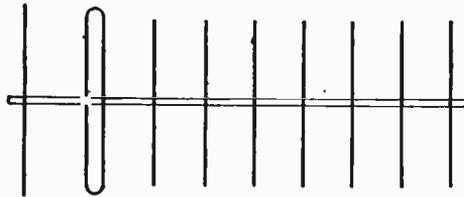


Fig. 2.— Typical multi-element aerial array. These arrays are often used indiscriminately in areas of poor signal strength; the most complicated array is not necessarily the optimum for a given location as much depends on the effects of reflections.

question as there is no relative signal factor which can be considered. This query usually comes from fringe areas where the Band I signal is only just about strong enough to mask noise while the Band III signal is nowhere near strong enough to outweigh the receiver noise, converter noise or both. The solution, in this case, lies in obtaining a stronger Band III signal by improving the aerial.

Combination

However, with simple add-on converters used with superhet receivers the overall noise factor is greater with the combination than when the set alone is used on Band I. This is because there are

two frequency changer stages, one in the converter and the other in the set. In addition, the front end noise factor of this type of converter is often less favourable than that of a multi-channel tuner used to replace the front end of the set. This means that even if a Band III aerial considerably more elaborate than the Band I aerial is connected to the converter, noise may be present on the ITA pictures. When the Band I aerial signal is just about strong enough to hold back the noise effect, a comparable picture can be obtained on Band III when the ITA signals are approximately twice as strong. This applies to a multi-channel set, but with a Band I-only set coupled to a Band III converter the ITA signals may have to be even stronger to secure a noise-free picture comparable with that of the BBC.

The best noise performance of an add-on converter can be obtained with the converter's gain control at maximum and the receiver's contrast control turned down to give the correct contrast ratio. If the converter's gain control is retarded to give the correct contrast ratio, then noise will appear on the ITA pictures.

Improving Noise Performance

In order to obtain the best noise performance in fringe areas the first R.F. stage to which the aerial signal is applied must be operating at maximum gain. When this condition exists, the following stage receives a strong enough signal to outweigh the noise that it is generating, and the noise of the first stage only need to be considered. Some sets feature a sensitivity control which adjusts the gain of the first stage. In fringe areas this should always be set at maximum. Other sets have AGC applied to the R.F. stage. Where the aerial signal is weak, this AGC can be removed with considerable advantage. Such AGC is often applied to multi-channel tuners—to the cascode R.F. stage, as shown in Fig. 1. Here the AGC is applied to the "bottom" of the grid resistor R1, decoupled by C1. AGC can be removed from the cascode stage V1 simply by shorting the "bottom" end of R1 to chassis. However, as this may upset the AGC applied to the I.F. valves, it is best to break the AGC line as shown in Fig. 1, short the bottom of R1 to chassis and then load the open-circuit AGC line with components R1M and C1M, the values of which should match R1 and C1.

It is surprising how this improves the noise performance, especially on Band III, in poor signal areas, since with the AGC line connected, a control voltage is usually present for even the smallest of signals. It should be noted, however, that on some sets a delay is given to the AGC applied to the cascode stage, in which case the alteration may not be so advantageous as on sets with the cascode coupled directly to the vision AGC line.

Diplexer Losses

The removal of a diplexer on Band III may also assist in obtaining an improved noise performance. Although the through loss of a diplexer is not usually excessive (one or two decibels), the extra signal thus obtained is well warranted in poor signal strength areas. This, of course, means changing over the aerial downleads when changing bands, unless a low-loss changeover switch is incorporated, which is a fairly easy matter.

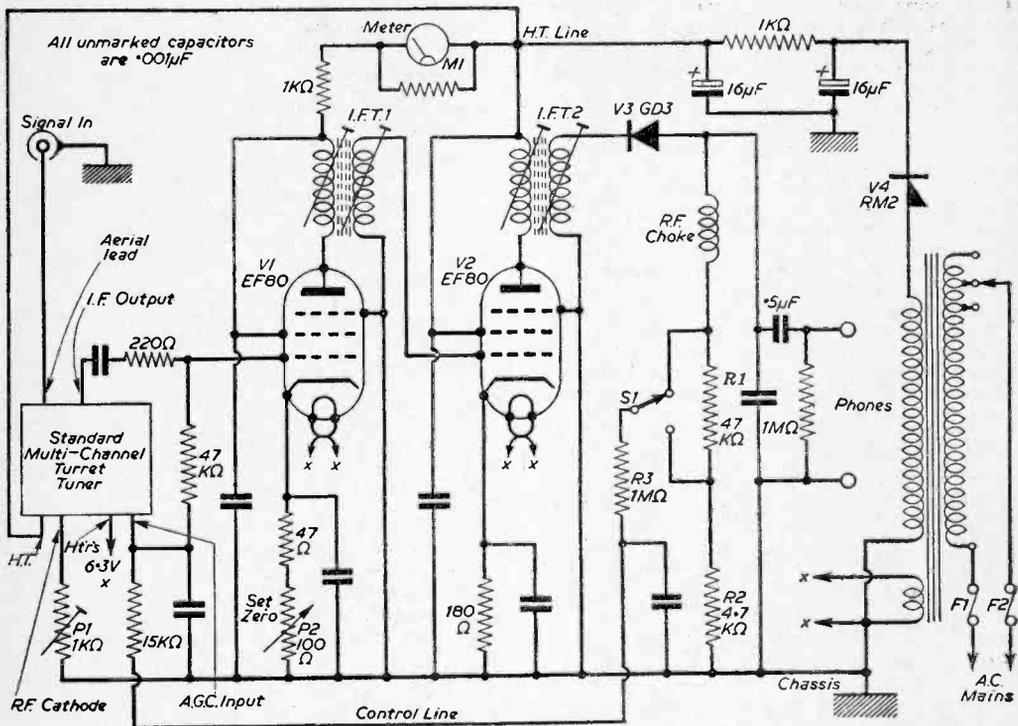


Fig. 3.—Circuit diagram of the signal strength meter for comparative tests.

Low-loss coaxial should always be used to connect the Band III aerial to the set when the signal is low. This pays dividends, as also does careful orientation of the aerial to get the best possible signal pickup. In very bad areas a reasonably noise-free picture can sometimes be obtained when the line tuning control on the turret is adjusted away from sound, thus resulting in an improved picture and very poor sound. The sound in this case can be restored by adjusting very carefully the sound I.F. transformers for maximum sound output after first setting the line tuner to the best position for picture. This should be done only as a last resort when it is absolutely impossible to improve the performance by other means.

Is there enough Signal?

We now get back to the original question. If in doubt about the signal conditions in the area, a relative idea can be gleaned by making inquiries of neighbours' reception. Most people are keen to talk about TV and the interference.

Arrays of complex aerials would indicate a weak signal area, and the use of a lesser aerial would be unlikely to give noise-free performance in such an area.

A sudden increase in noise on one channel only should lead to a check of the affected channel's aerial, while the same trouble on both channels should cast suspicion on the set. The downlead connections at the set and diplexer and the connections at the signal outlet socket. Check for a short

in the coaxial plugs, as a small, almost invisible, piece of braiding wire partially shorting between the inner and outer conductors can result in a loss of nearly all the aerial signal, leaving just enough to give a very noisy picture and sound.

In cases of doubt it often pays either to check the set on a friend's aerial or the suspect aerial on a friend's set. Alternatively, the local radio dealer may be prepared to measure the aerial signal for a small fee.

It is interesting to note that an increase in noise may be caused by a neighbour having his aerials co-sited on a shared chimney stack. The proximity of other aerials does not usually take the signal away from the affected aerial unless they are acting as some sort of screen, which is unlikely, but an impedance change occurs, and it is this which detracts from the signal transfer from the aerial to the set.

Design for Signal Strength Meter


In Fig. 3 is given a circuit diagram of a signal strength meter. The circuit consists of a standard multi-channel turret tuner feeding into two I.F. amplifiers. V1 and V2, the output of which is rectified by the germanium diode, V3. The resulting D.C. component of the I.F. signal is developed across R1 and R2 in series, and being negative in polarity with respect to chassis is fed as a control bias, via S1 and R3 to V1 and the turret R.F. stage.

(Continued on page 540)

Add-on Sound Unit

IMPROVE THE AUDIO SECTION OF YOUR TV RECEIVER
By "Electron"

IN the Editorial of the April issue it was mentioned that most of the modern developments in the design of TV receivers seem to be concentrated on improvements to the reproduced picture. The quality of the sound, far from being improved with the advent of new models, seems to be deteriorating. Many factors have given rise to this state of affairs, not the least of which is the increasing demand for so-called "slim" receivers where deflection angles of 110deg are used. Whilst it can be seen that the use of large diameter speakers should not be a deterrent to reduction of cabinet size, it seems absurd to obtain a small receiver with an excellent picture and very poor sound reproduction. Many older receivers, too, do not give the sound quality which can be obtained from the high fidelity TV sound signal which is transmitted. In many receivers the sound output stage is fed direct from the detector circuit and to secure an adequate volume of sound it is very often necessary to advance the volume control of the receiver to near the limit of its travel with the result that the signal-to-noise ratio is poor.

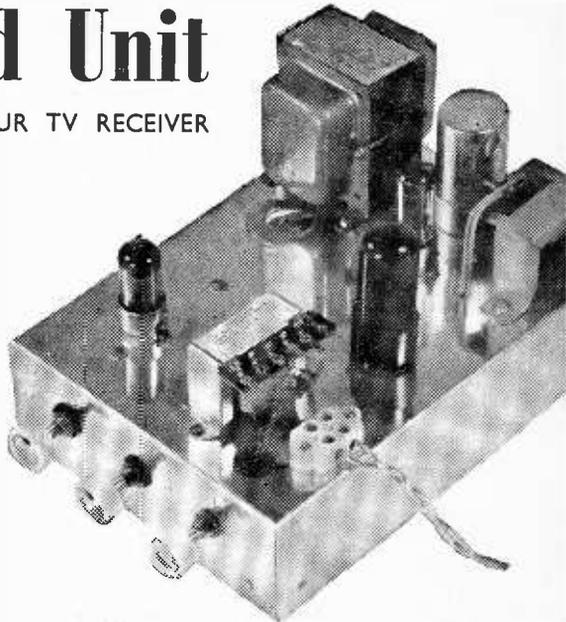

The completed amplifier.

Noise Levels

Two forms of hum are encountered in the sound circuit of TV receivers; one is caused by "vision

on sound" and takes the form of a 50c/s buzz which tends to be most wearing on the listener. Generally this is the result of misalignment in the R.F. circuits of the receiver or occasionally of


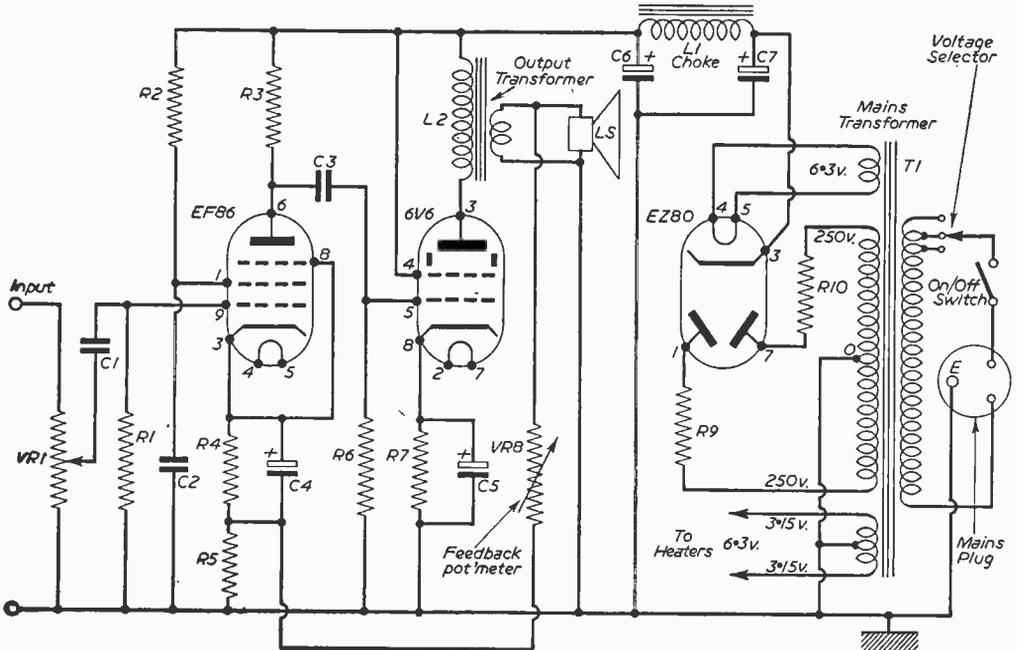


Fig. 1.—Circuit diagram (omitting tone controls).

standing waves on the aerial feeder which, in areas of high signal strength, may give rise to overloading of the vision circuits. The most common cause of hum in the sound output is poor smoothing in the H.T. circuits. Generally, smoothing is achieved by the use of high value electrolytic capacitors so that low resistance smoothing circuits may be employed. These electrolytic condensers may age and decrease in value and efficiency.

Fidelity

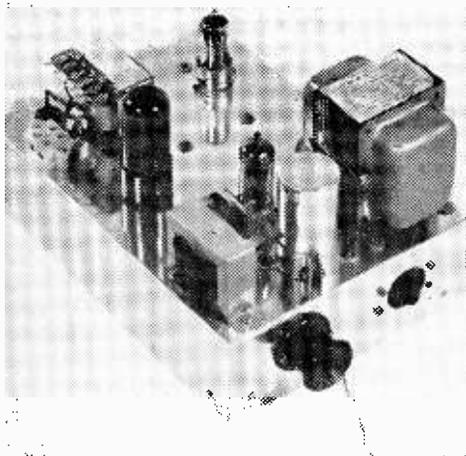Therefore, only rarely is the sound quality from TV receivers an approach to the fidelity of the signal transmitted. Apart from modifying the receiver itself—renewing components and employing new circuits—the only easy way of improving the sound reproduction is to employ a separate sound amplifier and such an amplifier is the subject of this article.



Another view of the amplifier.

Circuit Design

Many constructors advocate the use of a very high quality amplifying and loudspeaker system with television receivers. Some use amplifiers having rated outputs of 20W or more with comprehensive tone control circuits in the pre-amplifier including steep cut-off bass and treble filters. To my mind, it is unnecessary to go to great lengths in the design of a separate amplifier for TV sound. An output of say, 4W maximum should be more than adequate for most rooms especially when it is borne in mind that when watching television the attention of the viewer is concentrated for the most part on the picture and minor defects in sound quality will be evident only to the most critical constructor. The main requirement so far as I am concerned is that the level of mains hum and other noise in the output should be negligible and preferably inaudible. This requirement is not so difficult to meet as is so often suggested; careful circuit design and, more particularly, very careful thought in the layout of the amplifier can give eminently satisfactory results.

Operation

The circuit diagram of the amplifier is given in Fig. 1 and it will be seen to be quite straightforward. Three valves are employed; V1 is an EF86 in a voltage amplifying stage and V2 is a well known and well tried 6V6 in a conventional output circuit. The rectifier valve is a modern type; an EZ80, the smoothing circuit for which is normal except for the large values of electrolytic condenser employed. These condensers, C6 and C7, with the choke L1 ensure adequate smoothing and no hum is audible from the loudspeaker except by extremely careful listening near to it. No tone controls are shown in the circuit diagram but suitable circuits can be connected before the amplifier if required.

The signal input passes to VR1, a 500k pot, which functions as the volume control. The signal then passes via C1 to the grid of V1 where an amplified signal is developed across R3. This is then passed via C3 to the grid of V2 and the output from V2 is transferred via L2 to the loudspeaker.

COMPONENTS LIST

Resistors:

VR1—500k log pot with double pole switch.

R1—1M.

R2—1M.

R3—220k.

R4—1.5k.

R5—100Ω.

R6—270k.

R7—270Ω.

VR8—10k wire wound pre-set pot.

R9—150Ω.

R10—150Ω.

(All ½W types of 10 per cent tolerance).

Capacitors:

C1—0.1μF 150VW.

C2—0.1μF 350VW.

C3—0.25μF 350VW.

C4—25μF 12VW (electrolytic).

C5—50μF 25VW (electrolytic).

C6, C7—32+32μF 350VW (electrolytic).

Valves:

V1—EF86.

V2—6V6 (G or GT).

V3—EZ80.

Miscellaneous:

L1 choke 10H 50mA.

L2 multi-ratio output transformer to give 45:1.

(Wharfedale type P).

T1 mains transformer with tapped primary. 250V-0-250V 60mA, 6.3V-5V 2A, 6.3V 2A centre tapped.

(Ellison MT161).

Coaxial input socket; mains voltage selector panel; mains input socket; two B9A and one international octal valveholders; terminal block for output to speaker; eight way group board aluminium chassis approximately 10in. x 7in.; tag strips; nuts and bolts, etc.

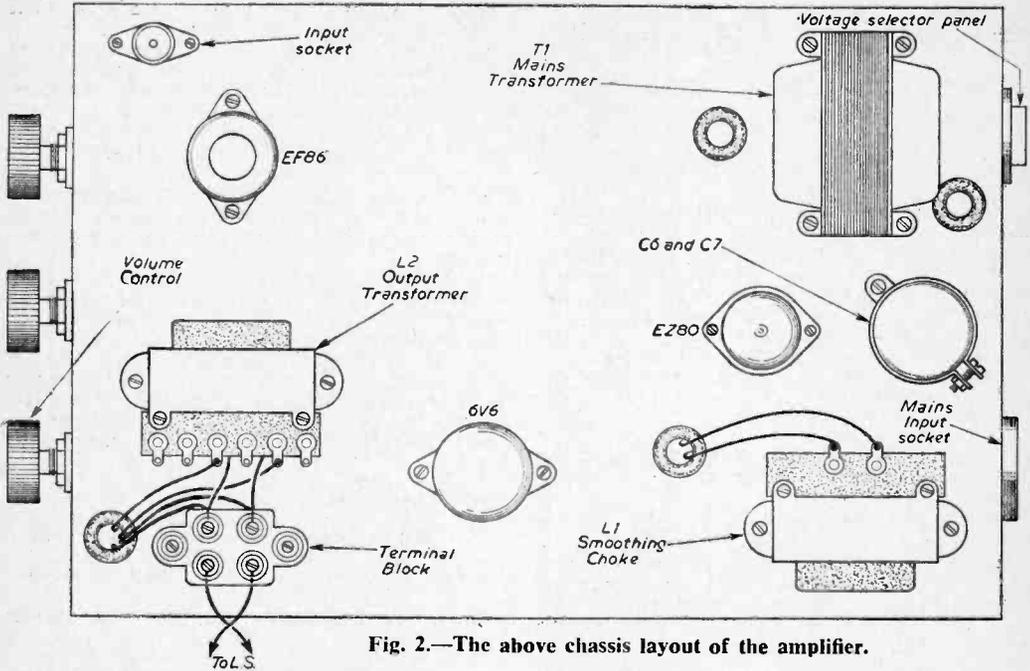


Fig. 2.—The above chassis layout of the amplifier.

It will be noted that the cathode circuit of V1 consists of two resistors in series R4 (1.5k) and R5 (100Ω). Only the resistance R4 is bypassed. This is achieved by C4. One side of the secondary of the loudspeaker transformer is earthed and the other side is connected via a 10k pot (VR8) to the junction of R4 and R5. Provided the correct side of the loudspeaker output is earthed, negative feedback occurs and the distortion introduced by V1 and V2 is reduced. If incorrect connections are made to the speaker output, then the amplifier will oscillate as feedback is positive. When the amplifier is constructed, it is a simple matter to make the necessary connections temporarily and when the correct phase has been determined the wiring may be made permanent.

Power Circuit

As previously stated, the power supply circuit is not unusual, but although the EZ80 rectifier valve can have its heater wired in parallel with those of the remaining valves, in this circuit it is operated from a separate winding. The H.T. secondary of the transformer gives 250V-0-250V and the centre tap is connected to the chassis. Resistors R9 and R10 are of low value (150Ω) and limit the peak currents which the rectifier must pass. The primary of the mains transformer is tapped so that the circuit can be used on varying mains voltages.

Construction

The layout of the principal components which are large in size is given in Fig. 2. It will be noted that three controls are shown; these are for volume, bass and treble although it is quite in order to omit the tone controls if required. Layout is straightforward but no detailed dimensions are given as much depends on the parts employed.

(To be continued)

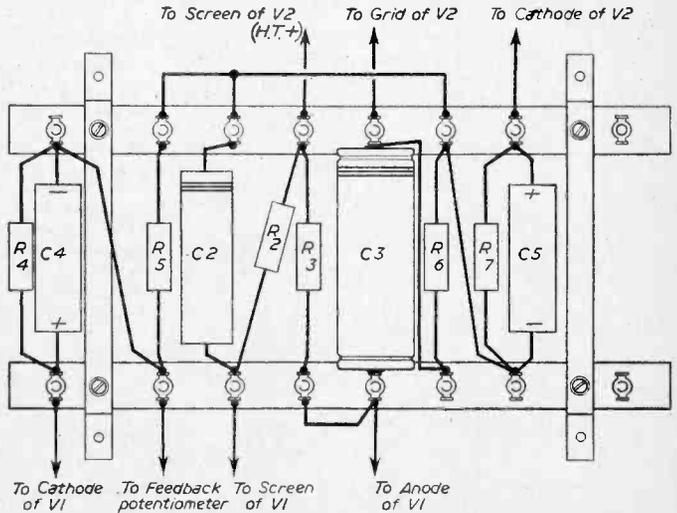


Fig. 3.— Wiring of the group board upon which the smaller parts are mounted.

Feeder Cables

TRANSMISSION LINE THEORY AS IT AFFECTS THE CONSTRUCTOR

By F. A. Palmer

AN expensive television receiver can have its performance ruined by incorrect choice and installation of the transmission line connecting the aerial to it; this part of the installation is too often taken for granted, yet the quality of the received picture is very dependent upon it and every constructor should make himself acquainted with its theoretical and practical characteristics.

Transmission lines used for television work fall into two categories:

- (a) Balanced twin cable.
- (b) Coaxial cable.

Whatever its type, the fundamental principles underlying its functions are the same.

Characteristic Resistance

It will be appreciated that every line has a certain amount of resistance; it also has a certain amount of "leakance" between the conductors. If we have a long line between two points "X" and "Y" (Fig. 1a), the total current at "Y" will be restricted by the series resistance of the line R1 and the leakance R2, and this can be represented in the equivalent circuit in Fig. 1b. (The series resistance is shown in one side of the line merely for convenience.)

Suppose we had a line which was similar in every respect but which was twice as long, then we could represent it as in Fig. 2a, because the series and shunt resistances are progressive along the line. A line three times as long could be represented as in Fig. 2b. Continuing this reasoning, a line extended to infinity could be represented as a number of series and shunt resistances R1R2—R3R4—R5R6—R7R8 . . . RnRn+1.

Coming back to Fig. 1b, let us assume that R1 is 10Ω and R2 is 100Ω. If a battery of 50V is applied to the line we shall have a certain amount of current flowing from the battery (Fig. 3). This current will be

$$I = \frac{E}{R} = \frac{50}{R_1 + R_2} = \frac{50}{110} = 454\text{mA}$$

and the overall resistance looking at it from "X" end (i.e., across TU) is 110Ω.

If the line is doubled in length then we shall have the condition shown in Fig. 4. To find the current flowing we must first find the effective

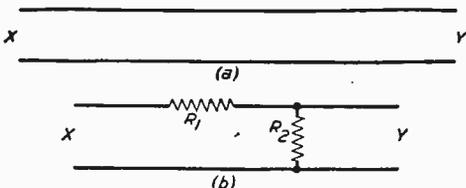


Fig. 1.—Diagram illustrating characteristic resistance of lines.

resistance across TU. An easy method of doing this is to take point PQ on the line. From this point looking towards "Y" we have a resistance of $R_3 + R_4 = 10 + 100 = 110\Omega$. This resistance is directly across R2 (i.e. across RS) therefore, across RS we shall have a resistance of

$$\frac{110 \times 100}{110 + 100} = \frac{11000}{210} = 52\Omega \text{ (approx.)}$$

The resistance across TU will therefore be $R_1 + 52 = 62\Omega$. (Note: we shall take all calculations to the nearest whole number for ease of illustration.)

Let us now take a line three times as long. This is shown in Fig. 5. By working out the resistances across XY, VW, PQ and back to TU we shall find that the effective resistance across TU is 48Ω.

A line four times as long will give us an effective resistance of 42Ω. Do you notice how the difference in values across TU is becoming less? The stages have been 110, 62, 48, 42, the jumps between successive calculations being continually reduced.

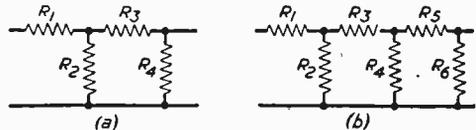


Fig. 2.—Rearrangement of line characteristic resistances.

Let us pursue this point a little further. Another section of line will give us an effective resistance of 38Ω, the next addition will give us 37.5Ω, and a further stage gives us 37Ω across TU. Adding yet another stage gives us 37Ω again.

At this point we could add on stages without making any difference to the resistance across TU. Furthermore we could short-circuit the "Y" end and still the resistance across TU would remain 37Ω. You can prove this yourself by continuing the calculations.

Characteristic Impedance

We have now arrived at a point where short-circuiting or disconnecting the far end of the very long line makes no difference to the effective resistance across TU or the input end. This resistance value we have obtained is termed the characteristic resistance of the line.

In the particular line which we have under discussion the characteristic resistance is 37Ω.

Now have a look at Fig. 6. Here we have disconnected the line at "XY", and inserted a load resistance of the same value as the characteristic resistance. Let us now calculate the value of the resistance which will appear across TU.

Across "VW" (ignoring the rest of the circuit back to the battery), we shall have a value of

$$\frac{R_4 \times 37}{R_4 + 37} = \frac{100 \times 37}{100 + 37} = 27\Omega.$$

Therefore, across PQ we have a resistance of


$$R_3 + 27 = 10 + 27 = 37\Omega.$$

Therefore, across RS we shall have a resistance of

$$\frac{R_2 \times 37}{R_2 + 37} = \frac{100 \times 37}{100 + 37} = 27\Omega.$$

Therefore, across TU we have a resistance of
 $R1 + 27 = 10 + 27 = 37\Omega$.

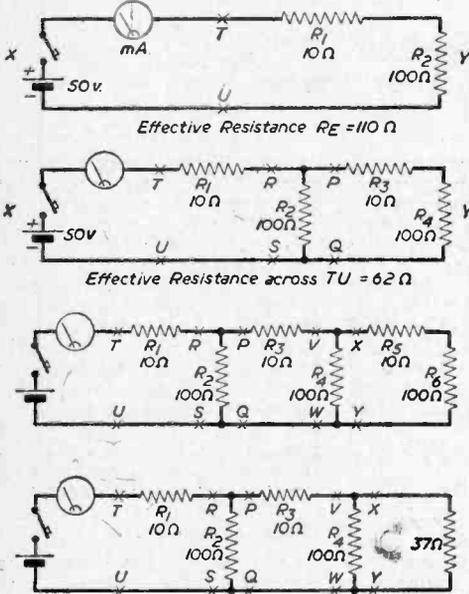This means that if we disconnect the line at any point and insert across it at that point its characteristic resistance, the characteristic resistance will appear at the input end.



Figs. 3, 4, 5 and 6.—Circuits showing the effect of various resistances, and the voltage and current distribution round the network.

Critical Length

It will be remembered that an infinitely long line will produce its characteristic resistance at the input terminals, and it does not matter if the far end of the line is short circuited or left open, the input resistance across the line remains unchanged. In other words if a line is extended towards infinity there will be a certain critical length beyond which no additional lengthening will alter the input resistance.

There is, therefore, a certain maximum amount of current which will flow in the line, and as power is the product of resistance times current squared ($W = R \times I^2$), there is a limit to the maximum amount of power which the line can handle.

Now maximum power is transferred from one circuit to another when the resistances of the two circuits are equal; for example, the maximum power is obtained from a battery when the load resistance is equal to the internal resistance of the battery. The same principle holds good for a D.C. generator.

If it is desired to transfer the maximum amount of power from a D.C. generator to a line, then the characteristic resistance of the line should equal the internal resistance of the generator. If the line is not infinitely long it should be made to appear so by making the load across the output terminals equal to the characteristic resistance of the line, and

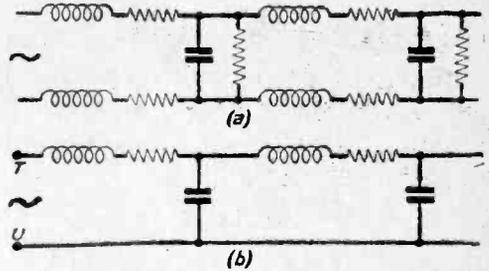


Fig. 7.—Circuits illustrating the characteristic impedance of lines.

this, as we have seen, makes the characteristic resistance appear across the input terminals of the line.

Characteristic Impedance

When dealing with A.C., several other factors have to be considered. The line contains series inductance and resistance, with parallel capacitance and leakage. Fig. 7a shows the effect.

In practice the leakage is so small that it can be neglected and to simplify the diagram the constants (inductance, series resistance and capacitance) are shown in one side of the line (Fig. 7b).

It will be observed that at the input end we have A.C. resistance (or impedance), instead of pure resistance. However, the same principles obtain in this case and a line extended to infinity will have a certain characteristic impedance.

It must be remembered that the constants which determine the characteristic impedance, are themselves determined by the physical make-up of the line.

A line which is not infinitely long can be made to simulate infinity conditions by terminating it with its characteristic impedance, as in the D.C. case.

Fig. 8 shows the scheme where we have an A.C. generator (A) with its internal impedance (Z_i), feeding into a line which is terminated with its characteristic impedance (Z_o). Under these conditions, maximum power will be transferred from the generator into the load.

If the load is any other value than Z_o maximum transference of power will not take place. Z_o can take any form such as a pure resistance, or lumped inductance and capacitance.


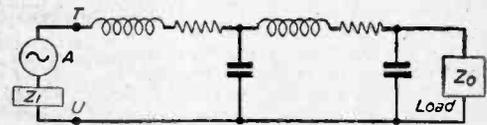


Fig. 8.—Diagram illustrating the effect of the impedance on the load.

Matched Line

In television we make use of a matched transmission line to obtain the transfer of the maximum amount of power from the aerial into the receiver. The aerial has A.C. induced into it by the incoming signal and can, therefore, be likened to a generator,

(To be continued)

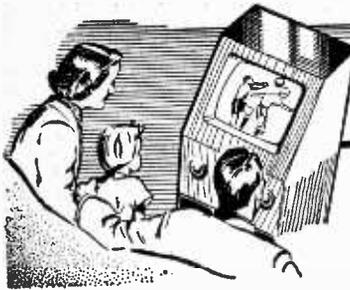

UNDERNEATH THE DIPOLE

A MONTHLY COMMENTARY

By Iconos

"TELEVISION is still in its infancy" is a remark I have heard so many times in the last few years that I have almost come to accept it as a fact. What nonsense! This assertion may have been true in 1936 and 1937, when the BBC were struggling to provide the first public television service in the world, but it is certainly not true now. Improvisation has long given way to careful planning; haywire pioneer experiments have been replaced by well-established production and engineering practices, and premises and equipment have acquired an appearance both functional and stylised. Cameras are no longer ugly square boxes and even the multitude of accessories have acquired a look which is as good as their performance. At British television transmitting stations and at the studios, the electronic equipment is mainly manufactured by E.M.I., Marconi, Pye or Rank-Cintel, and it is all of pleasing appearance, each make with its own characteristic styling.

Videotape and 16mm film

IN the wake of the main electronic equipment come the video tape machines of Ampex and R.C.A., each make well past its teething troubles and now with pleasing appearance as well as performance. Videotape has by no means reduced the amount of film used for outside events and even for telerecording, though the emphasis seems to be shifting from 35mm film to 16mm film. The latest 16mm film camera equipment to be unveiled is the new Debie "Mixte" combined picture and sound camera, in which a transistorised sound amplifier is an integral part of the camera itself. The cameraman can hear the sound off the recorded magnetic track as it goes through the

camera as an alternative to listening to the incoming sound. This well-designed instrument is another brain child of André Debie, the veteran French camera designer, who is also obviously an artist in the same sense as Bugatti, Telford, Stroudley, Rolls or Brunel—all of them artist-engineers who built bridges, cars or railways. A really good engineering work invariably carries with it the stamp of the originator—almost as much as the work of a great painter.


The Television Society

THE new Director General of the BBC referred at great length to the triumphs of the Corporation's Engineering Departments in a speech at the annual dinner of the Television Society, held on the evening of the Royal Wedding. His eulogies were well deserved, though his "commercial" far outran the

statutory natural-break time permitted to his competitors, the ITA programme contractors! As usual, Norman Collins, Deputy Chairman of ATV, outshone all the speakers (even Eamonn Andrews), with a highly topical summary of television people and places, given in the end-of-term manner of a headmaster. "Amongst other matters," he concluded with aplomb, "I have to report that Birkinshaw, D. C., and Bridgwater, T. H., show great promise"—which was his particular way of complimenting these two eminent BBC engineers.

Ulster's Success

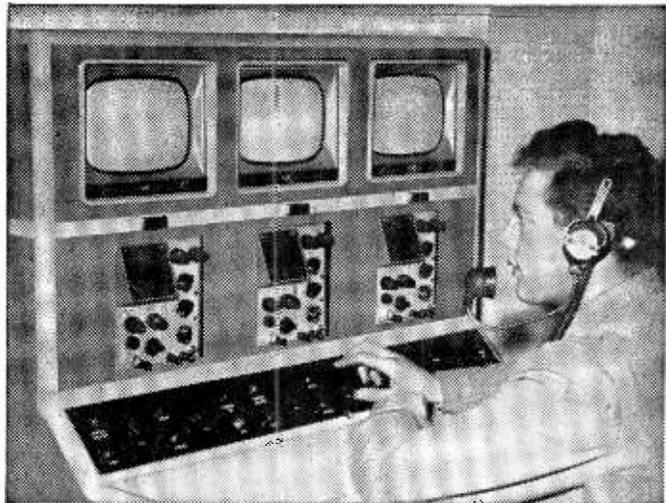ONE of the most pleasing success stories in television has been the rapid rise in popularity of Ulster Television, the ITA's smallest programme contractor. In the short space of six months, the set count for this station has increased



The Remote Control Console for Marconi Broadcast Vidicon cameras which is now installed in Havelock House, Belfast. It was designed and built by Ulster Television engineers.

from 97,000 to 143,000 not including a large number of viewers in Eire. During this time, the proportion of viewers able to receive both BBC and UTV transmissions has risen to 70 per cent in favour of UTV. The very name of the contractor, together with its lively local interview programmes, have contributed to this state of affairs. One regular early evening Ulster programme, "Roundabout", has achieved a rating of 50 per cent, which is considerably higher than similar types of programmes elsewhere. Another regional contractor with a large and loyal following is Tyne-Tees, which produces a relatively high proportion of local programmes, some of which are most ambitious. The BBC's regionals do excellent work, too, but their identity is not always obvious and their programmes are often erroneously presumed to originate in London, at Shepherd's Bush or Lime Grove.

SpooF

I STILL hear remarks about alleged "dishonesty" in the production and presentation of commercials on television. I suppose that such accusations are to some extent founded on fact—but there is just cause for the photographers to indulge in a little "pepping up" of the limited photographic tone range at their disposal, particularly as they do not have the advantage of colour. Even with the best of film or television cameras and systems, it is quite impossible to distinguish between the colours of milk and cream. Similarly the delicate distinction between dark greys and blacks is quite undetectable on home receivers. Therefore the television producers have to resort to a little mild deception to put over their stories. For years, the film people have made the froth on beer look fresher and brighter by adding a pinch of bicarbonate of soda; and cream has had to be darkened by adding a little yellow spice (turmeric). Meat is given a fresher look by painting the lean parts lightly with grape juice, and coffee has to be made very weakly indeed, otherwise it photographs as a black oily liquid. So much for making food look more appetising! For lengthy scenes in a television play, wooden or plaster imitations of foodstuffs are often required. The BBC prop depart-

ment excel in this mild deception! The white boiled shirts and ties of men's evening dress look far better if they are cream, or yellow coloured, or even pale blue. Sparkling jewellery has to be avoided wherever possible. Mashed potato makes a good substitute for ice cream, under the hot lights, and it is usually wiser for actors to drink glasses of weak tea rather than genuine whisky—especially if they have to take one-over-the-eight in front of the camera! Thick paper or parchment documents have to be damped, or otherwise they sound like dry potato crisps; which, incidentally, sound like a house on fire when crumbled near a microphone. I have lots of other disillusionments up my sleeve—but these examples surely indicate their professional necessity in the interests of both the dramatic and advertising arts.

Television Festivals

THE film industry is very prone to festivals. There are film festivals in Cannes, Venice and other glamorous places, at which new films from countries all over the world are shown and prizes are awarded. There are also film festivals much nearer home, mainly in the specialised and classic cinemas in London and the main provincial cities, at which old films of special merit are re-exhibited. Many of these films are grouped together into "festivals." Thus, several Marx Brothers films are shown in

rotation on different days of the week. Ealing comedies and Alec Guinness films have also been recognised in this manner as classics. The advent of videotape recording offers the television industry an opportunity of enabling viewers to see again their old favourites, not necessarily by retransmissions on BBC or ITV networks—but in other ways. If the BBC had a small "classic" theatre at Broadcasting House, at which certain especially popular or historic broadcasts could be seen again on closed-circuit, by paying patrons, I feel sure it would be successful. For instance, the wonderful videotape recording of Princess Margaret's Wedding would be sure to attract full audiences. Big sporting events, the Tony Hancock series and some of the top-line dramas would also arouse great interest. On the other hand, ITV programme companies could give their audiences in their "classic" preview theatre a chance of re-seeing some of the fine Armchair Theatres, Goon shows and outside broadcasts. Of course, such a service could be free to viewers who make written application for seats—or the closed-circuit performances might be tacked on to the end of existing audience participation shows, giving an extra half an hour or so's entertainment. It would be a fine public relations service—though I do not think anyone would object to paying for admission.

PRACTICAL WIRELESS

Chief Contents of July Issue

Now on Sale 1/6

- AN A.M. FEEDER UNIT
- USING MODERN TRANSISTORS
- TWO-VALVE CIRCUIT ANALYSER
- POCKET TRANSISTOR T.R.F.
- TRANSISTOR SUPERHET CIRCUITS
- A SIMPLE STEREPHONIC AMPLIFIER
- AUDIO TRANSFORMER DESIGN
- AN ELECTRONIC PHOTO-TIMER
- SHORT WAVE SECTION
- CONVERTING THE P104
- ETC., ETC., ETC.

Trade News

NEW PRODUCTS AND DEVELOPMENTS


Ultra "Bermuda" Range

TWELVE new television receivers to be known as the "Bermuda" range have recently been marketed by Ultra Radio and Television Ltd. The new 110 deg tube brings greater cabinet slimness and the use of tinted screens a picture with reduced glare and reflections. High gain valves give better reception, particularly with an indoor aerial and in weak signal areas. All the controls likely to be needed by the viewer are situated at the side on the table sets, and at the front on the luxury models. The luxury models in both 17in. and 21in. sizes have an "Auto-tuner" which automatically rotates at the press of a button to select the desired channel or VHF station. The cabinets are finished in edinam veneers with gold frames, in red fabric also with gold frames, and in blue fabric with white frames. (*Ultra Radio and Television Ltd., Stonefield Way, South Ruislip, Middlesex.*)

Capacitor Box

THE Heathkit Model DC-1 decade box is an instrument which offers convenience, accuracy and stability. The capacitors are silver mica types with a tolerance of ± 1 per cent. A special crystalline wax finish with an outer coating of wax ensures protection from moisture. Control of the capacitors is carried out by exposure to relative humidity

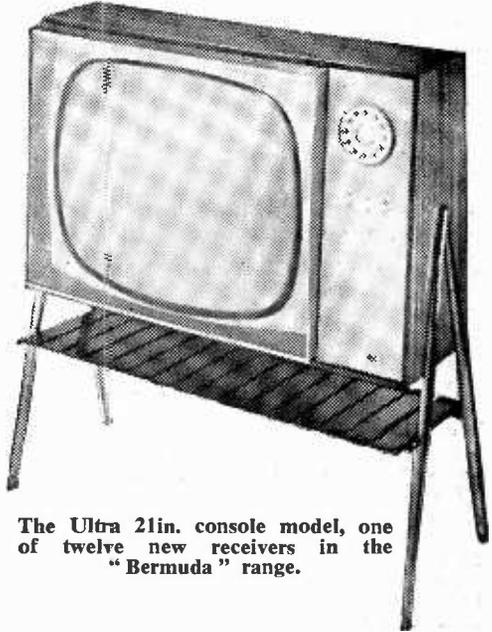above 95 per cent at a 24 hour cycling between 18 deg C and 35 deg C for a period of 7 days. The heavy duty switches are fitted with ceramic wafers and have a positive action. The Heathkit DC-1 is ideal for general experimental work and retails at £5 18s. 6d. It is manufactured by *Daystrom Ltd., Gloucester.*



The Ultra 21in. console model, one of twelve new receivers in the "Bermuda" range.

Aeraxial Trunk Cable

WITH the advance of national television relay Aerialite announce a development of interest to all relay companies concerned in the installation of television relay systems using coaxial cable distribution. They now offer a wide range of low radiation cables for trunk lines, with low attenuation in the frequency band used for direct signal television relay. These larger cables open up new possibilities, particularly in systems where extended cable runs are needed, as the number of repeaters can be significantly reduced. Full information may be obtained from *Aerialite Ltd., Cable Works, Stalybridge, Cheshire.*

Fansteel Capacitors

AS a result of an agreement concluded with the Fansteel Metallurgical Corporation of North Chicago, Illinois, the Plessey Company Ltd. now have exclusive selling rights in Great Britain of Fansteel tantalum capacitors. This range of capacitors extends from 325 μ F at 6V D.C. to 1.75 μ F at 125V D.C. both at 25 deg C. The range is-cased in three standard sizes, the smallest being 15/32 x 5/16in. diameter, and the largest 49/64 x .37/64in.




The Heathkit Model DC-1 decade capacitor box.

diameter. The three sizes are available in alternative tolerance grades, grade 1 from -15 to $+20$ per cent, and grade 2 from -15 to $+50$ per cent when referred to 120c/s at an ambient temperature of 25 deg C. At reduced working D.C. voltages these capacitors may be used in an ambient temperature up to 125 deg C. (*Plessey Chemical and Metallurgical Division, at Towcester, Northamptonshire.*)

Pam "Superslim"

THE new Pam "Superslim" 17in. television receiver, Model 804, is designed on console lines with a "streamlined" cabinet only 3in. in depth. From the normal viewing angle the body of the set is invisible. For servicing purposes the card back is removed and the chassis is laid open for inspection. The cabinet is finished in light natural walnut veneers which have the new polyester non-scratch finish. A polished brass trim surrounds the screen. The set retails at 64 guineas including tax and the fringe equivalent, Model 805F, retails at 71 guineas including tax. Details of this and other Pam receivers are available from Pam (Radio and Television) Ltd., 295 Regent Street, London W.1.

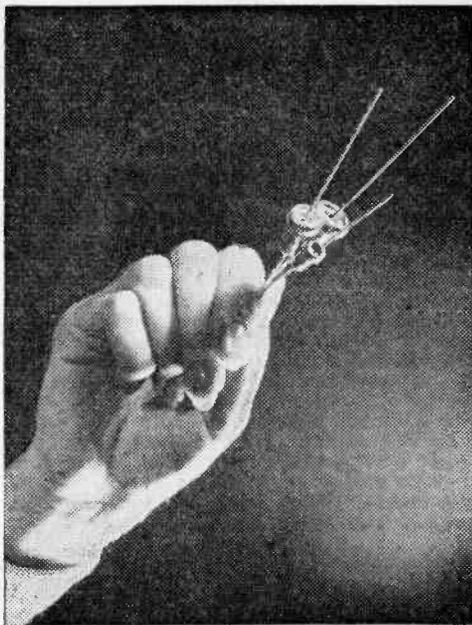The illustration on the right shows the three sizes available in the "Fansteel" range of capacitors.



INSTABILITY

(Continued from page 518).

This can be checked by replacing each valve in turn with one known to be in good order. Tapping the valves sharply with the handle of a screwdriver may reveal the trouble.

Sockets

Valveholders represent another potential cause of the trouble by developing poor R.F. connections between their sockets and the valve pins. Older sets which use EF50 valves are notorious in this respect. The trouble can often be remedied by

closing the contacts on the valve holder with a metal scriber or screwdriver blade. It also helps to clean the valve pins with fine emery cloth, taking care to remove all traces of emery powder after the operation. This trouble can usually be located very easily by gently rocking each valve in turn in its holder while observing the instability symptom.

Poorly soldered connections, especially those in R.F. or I.F. stages on the chassis proper or on an earth bus bar, should also be investigated in obstinate cases of the trouble. It is most important that all shields and coil screening cans are making perfect connection to chassis, and that the aerial downlead is connected adequately both at the aerial end and at the set. A mismatch in the aerial due to this or other causes often results in instability occurring when the contrast control is turned towards maximum. Attention should be directed along these lines if it is found that instability can be cured by moving the position of the feeder cable at the back of the set.

Poor Definition

When a set is unstable, but not quite to the point of oscillation, the overall response curve is somewhat modified, and in the vision channel this may well result in very much impaired definition accompanied by a "tadpole" interference effect on the picture with flaring or overshoot. In the sound channel, the sound will be distorted and tend to blur badly at high contrast or sensitivity control settings. Instability in the timebase circuits should first lead to a check of the valves followed by a check of the electrolytic decoupling and smoothing capacitors. In the line timebase, an increase in value of the resistors connected to the control grid of the line amplifier valve may give rise to a symptom that has some resemblance to instability, giving waviness to verticals.

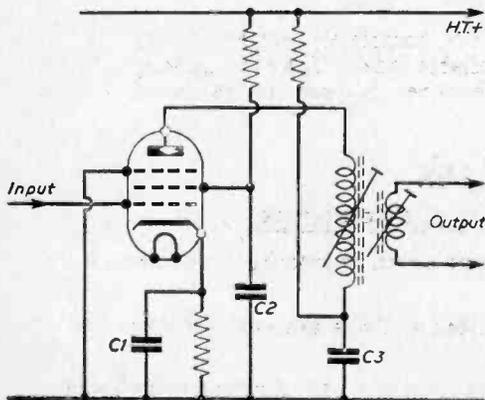


Fig. 3.—Decoupling capacitors, such as C1, C2 and C3, can be checked by shunting each in turn with a similar type of component while observing the instability symptom.

Just Right
for your pocket !

THE

MULTIMINOR

19 Ranges

D.C. Voltage: 0-1,000V in 7 ranges

A.C. Voltage: 0-1,000V in 5 ranges

D.C. Current: 0-1A in 5 ranges

Resistance: 0-20,000 Ω , 0-2M Ω .Pocket Size: $5\frac{1}{2} \times 3\frac{1}{2} \times 1\frac{1}{2}$ inches.

Weight: 1 lb. approx.

List Price **£9 : 10s.**

Complete with Test Leads and Clips.

Leather Case if required 39/-.

Sensitivity:

10,000 ohms per volt

on D.C. voltage ranges.

1,000 ohms per volt

on A.C. voltage ranges.

Accuracy:

On D.C. 3% of full scale value.

On A.C. 4% of full scale value.

To meet special requirements, instruments can be supplied to a higher degree of accuracy for a small additional charge.

Telephone: VICTORIA 3404 (12 lines)



This splendid AVO instrument has been developed to meet a definite demand for a sturdy pocket-size multi-range test meter at a modest price, suitable for use on modern electronic apparatus as well as for radio and television receivers, motor vehicles, and all kinds of domestic appliances and workshop equipment.

Readings are obtainable quickly and easily on a very open scale, and range selection is by means of a robust, clearly marked rotary switch of the characteristic AvoMeter type. Measurements of A.C. and D.C. Voltage D.C. Current and Resistance are made by means of only two connection sockets.

Designed and Manufactured by

AVO LTD AVOCET HOUSE • 92-96 VAUXHALL BRIDGE RD. • LONDON • S.W.1.

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES.

FROM YOUR POINT OF VIEW...

Midland "New Alumina" rebuilt C.R.T.'s, completely rescreened and aluminised offer you the finest value available today! The ever growing demand for these thoroughly reliable tubes is *your* assurance of satisfaction and service.

Now POPULAR TUBES
at POPULAR PRICES . . .

more Midland "rebuilt" — the tubes you can trust, at amazingly low cost

All types carry a 12-month guarantee and are available off the shelf NOW. Contact—

MIDLAND Tubes Ltd. 37, GEORGE STREET,
MANCHESTER, 1.


Telephone: CENTRAL 4568/9



RESTORE TV TUBE PICTURE QUALITY & BRIGHTNESS

PRICE **35/-**

plus 2/6 P. & P.

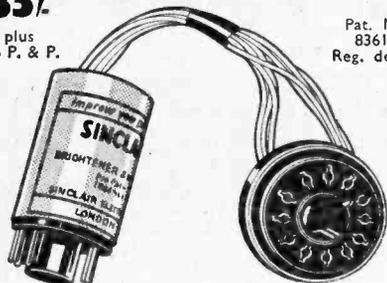

Pat. No. 836161
Reg. design.

JUST PLUG IN!
No technical knowledge required.

This Unit removes the cathode contamination, restores low emission on all sets operating off A.C. mains.
IMPORTANT. State make and model No. of set and tube in block capitals, please. If not satisfied money refunded if returned within 7 days.

REBUILT TUBES ALSO AVAILABLE
12 months guarantee

12" £5.0.0 14" £5.10.0 17" £7.0.0
carriage and insurance 7/6 extra.

SINCLAIR ELECTRONICS

33 BERWICK STREET, LONDON, W.1
Terms: C.W.O. C.O.D. Phone: REGENT 5520

Unrepeatable Offer

COSSOR 10" TUBE I08K — BRAND NEW

Twelve months guarantee

NOT A RE-GUN

—we have a few only

15/- each

10/- Packing, Postage and Insurance

HARVERSON SURPLUS LIMITED

83 High Street
MERTON, S.W.19

CHERRYWOOD 3985/6/7

VALVES SAME DAY SERVICE

NEW! TESTED! GUARANTEED!

SETS 1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, any 4 for 23/6
DAF96, DF96, DK96, DL96
6K7G, 6K8G, 6Q7G, 6V6G, 6X5G, or 5Y3G 4 for 30/-
.. .. . 5 for 27/-

1A7GT 12/-	6L18 12/3	25Z4G 8/-	EBF89 8/9	EZ41 7/8	R19 13/6
1D5 1 8/-	6LD20 10/-	25Z6GT 7/6	EBL21 20/6	EZ80 6/3	T41 15/6
1H5GT 10/-	8P25 9/-	30C1 9/3	EC92 11/-	EZ81 7/-	U25 13/-
1N5GT 10/-	6Q7G 6/9	30L1 7/9	ECC81 5/9	FW4/500 8/-	U28 11/6
1R5 8/9	6S17GT 9/8	35L6GT 10/-	ECC82 6/8	GZ32 9/-	U50 7/6
1S4 9/-	6S17GT 9/3	35Z4GT 6/8	ECC83 7/-	KT33C 7/-	U52 5/9
1S5 5/9	6S27GT 4/9	35Z5GT 8/6	ECC84 8/9	KT41 14/6	U78 6/-
1T4 4/9	6U4GT 11/-	50CD6G 26/9	ECC85 8/3	KT44 9/-	U78 6/-
1U5 6/6	6V6G 5/-	50L6GT 8/9	ECC86 10/-	KT61 10/-	UABC90 7/9
3A5 10/6	6V8GT 6/8	185BT 25/-	ECC87 10/-	KT63 6/8	UAF42 9/6
3C4 8/6	6X4 5/-	AZ31 9/6	ECH21 20/6	KT71 8/6	UBC41 7/9
3S4 8/9	6X5GT 5/6	B36 8/9	ECH35 6/9	MH4 6/-	UBF90 9/6
3V4 7/8	7B7 7/6	CL33 13/-	ECH42 8/9	MU14 7/6	UBF89 8/6
5U4G 5/3	7C5 7/6	DAC32 10/-	ECH41 8/6	MX40 12/6	UBL21 20/6
5V4G 9/6	7C8 7/6	DAF91 5/9	ECL80 8/-	N18 8/6	UCB24 12/9
5Y3GT 8/9	7W7 7/6	DAF96 7/9	ECL82 10/-	PCC84 7/9	UCC85 7/6
6Z4G 7/9	7S7 9/9	DCC90 10/6	EF39 4/6	PCC89 12/-	UCH90 14/-
6AL5 3/9	7Y4 7/-	DF33 10/-	EF41 8/9	PCF80 7/3	UCF81 20/6
6AM6 3/6	10C1 14/6	DF91 4/9	EF42 11/6	PCF82 9/3	UCH42 9/-
6AQ5 6/-	10C2 17/6	DF96 7/9	EF80 6/6	PCL32 8/-	UCH81 7/6
6AT8 7/6	10E1 15/6	DH78 6/6	EL38 6/9	PCL84 11/6	UCF82 10/9
6BA6 6/-	10P13 14/6	DH77 7/3	EP96 10/6	PCL84 8/-	UCL83 13/-
6BE6 6/-	12A18 10/6	DK32 12/-	EF89 8/3	PEN44 11/-	UF41 8/9
6BH6 5/9	12A17 5/9	DK91 6/9	EF91 3/6	PEN36C 8/6	UF42 7/6
6B36 5/9	12A17 6/8	DK92 8/6	EF92 4/6	PEN45 8/-	UF89 9/6
6BR7 10/-	12A17 7/-	DK96 7/9	EL33 10/-	PEN46 5/9	UL41 8/-
6BW8 8/6	12BA6 8/-	DL33 9/-	EL38 21/6	PL36 11/9	UL84 8/-
6BW7 6/8	12K7GT 5/6	DL35 10/6	EL41 9/-	PL38 14/6	UR1C 8/-
6CD6G 22/6	12K8GT 11/6	DL92 6/9	EL42 9/6	PL81 9/6	UY21 11/3
6E1 14/6	12Q7GT 5/6	DL84 7/6	EL84 9/6	PL82 7/6	UY41 6/6
6F6G 8/6	12Z3 7/6	DL96 7/9	EM34 8/6	PL83 8/-	UY85 6/9
6F13 12/6	14S7 16/9	EAB30 7/-	EM80 9/-	PY32 12/-	VP4B 9/6
6F14 17/6	19AQ5 7/-	EAF42 8/6	EM81 9/-	PY80 7/8	VP41 6/-
6K7G 3/9	20F2 17/6	EB91 3/9	EM84 10/-	Y81 6/9	W76 6/6
6K7GT 8/9	20L1 17/6	EB33 5/-	EY51 9/-	Y82 7/-	W77 4/6
6K9G 8/9	25A6G 8/-	EB41 8/6	EY85 8/3	Y83 7/9	X76M 11/6
6L1 15/-	25L6GT 9/-	EBF80 8/-	EZ40 6/9	PZ30 17/-	Z77 3/6

READERS RADIO

24 COLBERG PLACE, STAMFORD HILL
LONDON, N.16 STA. 4587

"AS-NU"

Regunned TV Tubes

Supplied from stock, and despatched by British Railways same day.

COMPLETE NEW GUNS

fitted in every tube and fully guaranteed for TWELVE MONTHS.

12 in. ...	Mullard	Mazda
14 in. ...	£4.10.0	£5.0.0
15 in. ...	£4.15.0	£5.10.0
16 in. ...	£6.10.0	£6.5.0
17 in. ...	£5.15.0	£6.0.0
21 in. ...	£8.10.0	£8.10.0

Pfus 10/- Carr. & Ins.

Other types available. Please contact:

J. P. WRIGHT

1c Shotton Street, Doncaster

Sole Distribution Agent

'Phone: DON 2636 or 66252

Post 6d. per valve extra.
Any Parcel Insured Against Damage In Transit 6d. extra.
Any C.O.D. Parcel 2/6 extra.

Letters to the Editor

The Editor does not necessarily agree with the opinions expressed by his correspondents.

SPECIAL NOTE: Will readers please note that we are unable to supply Service Sheets or Circuits of ex-Government apparatus, or of proprietary makes of commercial receivers. We regret that we are also unable to publish letters from readers seeking a source of supply of such apparatus.

SERVICING THE BUSH 24C

SIR.—In the May issue Mr. H. Partridge of Bradley, Staffordshire (Your Problems Solved) complained of lack of width on his set. I have serviced several of this type of set for the same fault and would suggest the following cure. If, after replacing the line oscillator, line output, boost diode and H.T. rectifier valves on the left side of the main deck, the fault is not corrected, the cure is replacement of the C22 80pF condenser which is on the right side of the panel containing the EY51. This condenser is a special Bush type and can be replaced with an 80pF 10kV ceramic disc type. If this condenser develops a leak, sometimes the 50k wire-wound control may burn out or give erratic operation. The cure is to replace both the condenser and the 50k pot.—S. WHITTON (Buckingham).

SAFE MODIFICATIONS

SIR.—With reference to Mr. Cobb's letter (May issue), an isolating transformer will not solve the problem because an inductive surge is generated in the secondary at the moment of break which could be lethal. As I see it, the only solution is a completely isolated chassis with a voltage controlled earth leakage circuit breaker between line and chassis (which should be at true earth potential). This breaker would be set to operate at any leakage above a normal 25V and should be subject to I.E.E. and B.S.I. approval. It should be incorporated in the mains switch on the set.—R. E. CLARK (Woolwich, S.E.16).

REMOTE CONTROLLER

SIR.—In view of the present campaign for safety in the home I feel bound to point out the dangers of the circuit published on page 420 of the May issue, in spite of your warning at the end of the article. There is so often the unexpected fault; I quote the instance of the reversible two pin plug which is fed from the solitary socket in the room and removed frequently to make way for other uses. Is it always replaced with the polarity correct? The person using this device may be extremely cautious and check for polarity whenever he employs it, but can he be certain that the neutral fuse will not blow, or the switch not develop a fault on the neutral side. If this should happen when somebody is using the earphones, as

suggested, this device can well become an "electric chair".—G. FELTON (Chelmsford).

[We think that the warnings given in our articles dealing with circuits using "live chassis" techniques are adequate and we shall continue to stress the dangers caused by careless wiring and handling.—Ed.]

SOUND REPRODUCTION

SIR.—May I pass to you an outline of my own experiments. Ignoring the 8in. speaker in console (and the amplifier) the extension is a 12in. enclosed in a bass reflex cabinet connected in parallel by jack-plug; also switch to cut out console speaker. The extension is several feet from the TV but ties easily with the picture even when console speaker is "cut". As there is a slightly better H.F. response from the console speaker, there is no necessity for any H.F. speaker (and crossover) to be added in the extension. Many sounds are greatly improved with the wider frequency response—examples: cymbals cease to sound like dust-bin lids, hoofbeats do not sound like knocking shells, etc.—W. CHESTER (Barnsley).

BARKHAUSEN EFFECT

SIR.—In reply to a reader's inquiry a few issues ago about lines running vertically down his screen, I would like to make one or two suggestions. Although it could be due to the effect mentioned as the heading to the correspondence, it might also be due to direct pick-up of interference from the timebases by the lead to the grid (or cathode) of the tube, in other words, the tube input. It could also be due to interaction between the timebases. I would offer the following suggestions for removing the lines. First, use the finest possible wire for the input lead—not thicker than 28s.w.g. Do not attempt to screen it. If the lines still persist, connect a 0.1 μ F condenser from input electrode (grid or cathode) to earth. If the lines vanish, then the interference comes from the input lead, or originates in some part of the circuit prior to that point. A clean raster should be left when the condenser is joined, but if the vertical lines still persist, the interference must come from interaction between the timebases, direct pick-up on the scanning coils or even the valves themselves.—H. REVLON (Penge).

SIR.—I was interested to read in your May issue about a reader who had "hum" bars on his screen. I, too, have experienced this fault on the vertical scan. I believe the effect is called the Barkhausen-Kurz effect, and is caused by parasitic oscillations (Barkhausen-Kurz oscillations), usually in the line output stage. In my case a cure was effected by changing the line output valve.—E. J. JONES (Monmouthshire).



Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDER-TAKE TO ANSWER QUERIES OVER THE TELEPHONE. The coupon from p. 540 must be attached to all Queries, and if a postal reply is required a stamped and addressed envelope must be enclosed.

PAM 982

I wish to alter this set to receive local ITV programmes. I do not have a circuit diagram.—W. Baxter (Motherwell).

To convert your receiver to ITA will involve fitting a turret tuner and the easiest one to fit is the Brayhead 35S in the 35BA7 adaptor. Full fitting details are provided with this unit which may be difficult to mount inside your cabinet and may need an external box.

MURPHY V310

I have moved my indoor aerial to several positions in the room but I still have very bad ghosting on this set. When I tried it in another room the result was double images. The outdoor aerial is just the same and this only happens on ITV.—W. Fry (South Hackney).

To remove ghosts satisfactorily will require something in the nature of a 7-element ITA aerial erected outside. Several positions may need to be tried before a solution is found and if no alternative chimney is available a cranked arm may be used from the present pole.

ALBA T321

The picture on this set is really good but is split in half. The vertical hold rotates the picture but will not hold on top (only in the centre). I have changed the valves, ECC83's, PL82's (interchanged) but with no result. I put in a new C63 condenser. The vertical form does not appear to have any effect on the picture in its present position. On the bottom half of the picture there are white lines and the flicker on the screen is pronounced.—J. Finch (Wigan).

The lack of sync may be attributed to a resistor or capacitor associated with the frame sync clipper ECC83. First check the 2.2M from H.T. to the junction of the 0.1 μ F and 470k/220k. Then check the 0.1 μ F and the 22pF—pin 6 to pin 1. Check 820k to hold control.

PETO SCOTT 1722,

The above set is second-hand and has developed the following faults: the vertical hold is critical, although its best position is still half way. The horizontal hold is the same—also at half way and although it can be held it takes an exceptionally long time to set it. When it is set, it intermittently pulls to the left and there is always a pull to the left about 1½ in. from the top. The valves have been checked and proved satisfactory. When I bought the set I found a grid short on the tube (MW43-69) but re-wired the base. When the set is laid on its side with the turret tuner uppermost there are three slider controls on the tag panels and the centre one was sparking slightly.—C. Ashall (Sheffield).

Switch the sync auto direct knob to direct. If both time bases are still "awkward" check rear left side PCF80 sync separator and the resistors associated with this valve base. These are 220k and 150k decoupled from the video amplifier by a 32 μ F which is also suspect.

PYE FV1

This set (12in.) has a thin white line across the screen. I have checked ECL80 which is in order and I now suspect the frame output transformer is open circuited. (Is it 10A or 11A?).—J. Hugh (Lanarkshire).

T10A is the oscillator transformer and T11A the output transformer. Of the two, T10A is the most likely failure. A check of its operation can be made by measuring the voltage at the ECL80 triode grid, which will be very negative if the transformer is oscillating.

MASTERADIO T917

After a few minutes viewing (ITV only) the frame starts to slip showing diagonal lines across the screen. Frame hold control is in midway position, movement either way makes frame slip upwards and downwards, locking now and again. Otherwise the picture is very good. As I am in a low-lying part of Bristol, would lack of signal strength be the trouble?—E. Caines (Bristol 5).

The use of a pre-amplifier would result in an increase of noise as well as signal and the net result would then be very little. It is the aerial which must receive attention; try to site it in a more receptive position. Also check the 10C2 sync separator and the resistors associated with this and the 20L1, coupling capacitors, etc.

DEFIANT T1410

The picture went very dim but focussed well. Suspecting a low emission tube, I bought a booster transformer marked 25 per cent, substituted a 450 3 W resistor in the heater chain and installed the booster, connecting one side of primary to fuse 2 and the other to chassis. This restored the picture brightness but it is unstable and the slightest change in aerial input causes the picture to vary in size and brightness and occasionally disappear. Altering the contrast will bring it back and the picture has several ghosts. I checked the voltage across the tube heater (15), across substituted resistor (15) and across some other valves and all seem to be about right. There is a steady raster

TELEVISION TUBES

REGUNNED 12 MONTHS' GUARANTEE

MW 31/74	£5.10.0
CRM 123	£5.10.0
CRM 141	£5.10.0
CRM 171	£6. 0.0
CRM 152B	£6. 0.0
MW 36/24	£5.10.0
MW 43/69	£6. 0.0

Carriage and Insurance 10/- extra.

ALLOWANCE ON OLD TUBE IF RETURNED

CO-AXIAL CABLE, semi-airspaced. 75 ohms. 6d. yard.

RECTIFIERS

RM1 5/3, RM2 6/9, RM3 7/6, RM4 13/6, RM5 19/6, 14A86 19/6, 14A97 19/6, 14A100 19/6, LW7 17/6, 18RA 1-16-1 8/-, FC31 (14RA 1-2-3-3) 22/6, FC101 (14RA 1-2-3-2) 16/6.

HEATER TRANSFORMERS

All 240 v. input. 4 v. 3 amp. 10", 6.3 v. 11 amp. 6/9, 6.3 v. 3 amp. 10", 12.6 v. 7 amp. 5/9, 5 v. 2 amp. 10", 2 v. 3 amp. 8/3.

PUBLICATIONS

Wireless World Valve Data Book, 5/-, post 4d. Data TV Fault Finding Book, 5/-, post 4d. Mullard Circuits for Audio Amplifiers, 8/6, post 6d. Short Wave Receivers for the Beginner, 6/-, post 5d.

ACOS MICROPHONE

Acos Mic 3911 Crystal Stick Microphone for use as hand, desk or floor stand units for high quality recording, broadcasting and public address work. List price £33.0. OUR PRICE 39/6. With table stand 47/6. With floor stand adaptor, 52/6. Postage 1/6.

ALPHA RADIO TERMS—Cash with order or C.O.D. Postage and Packing charges extra, as follows: Order value 10/- add 1/3; 20/- add 1/9; 40/- add 2/6; £5 add 3/6. Minimum C.O.D. Fee and Postage 3/-. For full terms of business see inside cover of our catalogue. Personal Shoppers 9 a.m. to 5 p.m. Monday to Friday, Saturday 10 a.m. to 1 p.m.

103 LEEDS TERRACE, WINTOUN STREET, LEEDS, 7.

ALPHA RADIO SUPPLY CO.

VALVES GUARANTEED ALL TESTED BEFORE DESPATCH

AZ1 10/-	CZ22 11/-	3S4 7/6
AZ31 10/-	CC84 19/-	3V4 7/6
DAF96 8/9	PCC85 9/6	5Y3G 8/-
DF96 8/9	PCF80 9/6	5Z4G 9/6
DK96 8/9	PCL82 12/-	6AL5 4/6
DL96 8/9	PCL83 14/6	6F1 14/-
EAP42 10/6	PL36 13/6	6FL5 14/-
EBC33 9/9	PL38 26/6	6J7G 6/6
EBC41 9/6	PL81 12/6	6K7G 3/6
ECC81 9/6	PL82 8/6	6K8G 6/6
ECC82 7/6	PL83 11/6	6K25 18/11
ECC83 9/-	PY32 17/6	6L6M 4/6
ECC84 10/-	PY31 8/6	6AM6 4/6
ECF80 12/-	PY82 7/-	6Q7G 7/6
ECF82 13/-	PZ30 19/11	6V6G 6/6
ECH42 9/6	TP25 10/-	6V6GT 7/9
ECH81 9/-	U5 15/-	6X5GT 7/-
ECL80 10/-	U26 10/6	7B6 10/6
EF39 5/9	U37 26/6	7H7 9/-
EF41 9/9	U21 19/11	7S7 9/6
EF80 7/6	U801 29/10	7Y4 8/-
EF86 13/-	UAF42 9/6	10F1 15/-
EL33 14/-	UB41 9/-	10P13 15/-
EL41 10/6	UCH42 10/6	12AT7 7/6
EL42 10/6	UF41 9/-	12AX7 8/-
EL84 9/-	UL41 10/-	12AU7 8/-
EM34 8/6	UY8 26/6	20F1 26/6
EM90 10/-	UYLN 12/6	2SA6G 10/6
EY51 10/-	UY41 7/6	2SZ4G 9/6
EY86 10/-	1R5 7/6	2T5U 19/11
ET240 7/6	1S5 6/6	35L6GT 10/-
EZ81 7/-	1T4 6/-	35Z4GT 8/-

WAVE CHANGE SWITCHES, etc.

3 pole 4 way 3/- ea.	2 pole 6 way 3/- ea.
4 pole 3 way 3/- ea.	3 pole 3 way 3/- ea.
1 pole 12 way 3/- ea.	4 pole 4 way 4/6 ea.
3 pole 3 way 3 bank	2/8 ea.

PRE-SET POTENTIOMETERS

1K, 2.5K, 10K, 11K, 50K, 100K, 1meg. 1meg. All 1/9 each.
TCC Visconal "Cathodray" condensers 0.001 mfd. 20 Kv. 10/-; 0.005 MFD. 20 Kv. 10/-

ELECTROLYTIC CONDENSERS

100 x 100 mfd., 275 v.	7/6
100 x 200 mfd., 275 v.	7/6
100 x 300 mfd., 275 v.	7/6

TANYA SOLDERING IRONS

220/240 volts, 40 watts, 16/9 each. Replacement elements and bits, always available.

CRT Boost and Isolation Transformers

Standard mains primary Input has one tape which increased the output by 25%. 3 types available to cover 2, 4, 6.3 v. tubes.

Universal Boost and Isolation Transformer

Input 200/220/240 volts. Output 2 v., 6.3 v., 13 v. and with 25% boost on all taps. PRICE 13/6. Post 1/-.

AUTOMATIC CHANGER UNITS

Monarch UA8 4-speed automatic record changer with Full-F) turnover crystal cartridge. £6.19.6. Carriage 3/6.

The new B.S.R. Model UA12 4-speed mixer

Automatic record changer, fitted with latest turnover cartridge. OUR PRICE £8.8.0. Carriage 3/6.

Collaro Conquest, 4-speed fully mixing

changer complete with Studio "O" Crystal cartridge, £7.19.6. Carriage 3/6.

Garrard, RC120D Mk. II, 4-speed unit

manual control to enable records to be played singly. £8.17.6. Carriage 3/6.

EMI Single Record Player, 4-speed, fitted

with stereo cartridge. £6.19.6. Postage and packing 3/6.

CATALOGUE

our 1960 catalogue is now available. Please send 1/- in stamps for your copy.

TV TUBES

WHY USE INFERIOR TUBES WHEN WE CAN SUPPLY ALL TYPES OF REGUNNED

REBUILT TUBES

FOR ONLY 75/-

12 months' Guarantee or

OUR FABULOUS NEW SILVER SCREEN TUBES AS USED BY LEADING TRADERS

Replacements for—

Mullard, Mazda, Cathodeon, G.E.C., English Electric, Emiscope, Emitron.

12", 14"—£6-15-0

15", 16", 17"—£7

21"—£8-10-0

24"—£10

Carriage and Insurance on all tubes, 10/- Trade Discount. 20 Weeks' Credit available

Please note our new address:

Express Electronics

40 LANDSDOWNE TERRACE
 KELVIN BRIDGE, GLASGOW, NW
 Phone: Wes 8436

VIDIO 'REBUILDS' COST LESS—BECAUSE THEY'RE BETTER!

TOP QUALITY

and NEW GUN UNITS

'NEW ALUMINIA'— a special service

Right up to Vidio-high standards, all types of re-screened and aluminised tubes are available now— immediate free delivery.

ALL TUBES GUARANTEED FOR ONE YEAR

Get full details NOW from

VIDIO

Replacements Ltd.
 HALES STREET
 DEPTFORD HIGH STREET
 LONDON, S.E.8
 Tel.: TID 4506



Let **I.C.S.** train YOU!



COURSES ON:—


- **RADIO and TELEVISION**
 - **SERVICING · ELECTRONICS**
- EXAMINATION COURSES FOR:—**

- **C. & G. Radio Servicing Certificate** (R.T.E.B.)
 - **C. & G. Radio Amateurs' Exam.** (Amateurs' Transmitting Licence)
 - **British Institution of Radio Engrs., etc.**
- Whether you plan to have your own business, to become an electronics engineer or to take up a career in industry, an I.C.S. Course will help you to succeed. You learn at home in your own time, under expert tuition. Moderate fees include all books.

LEARN - AS - YOU - BUILD

- **Practical Radio Course**
- A basic course in radio, electronic and electrical theory backed by thorough practical training. You build a 4-valve T.R.F. and a 5-valve superhet radio receiver, signal generator and multi-tester

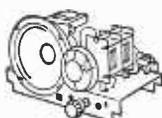
Other Learn-as-you-Build radio courses are available



5-VALVE SUPERHET RECEIVER



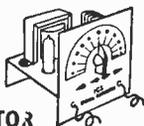MULTI-TESTER
(Sensitivity 1,000 ohms per volt)



RF/AF SIGNAL GENERATOR

Post this Coupon TODAY! for FREE book on careers in Radio, etc., and full details of I.C.S. Courses

International Correspondence Schools
(Dept. 164B), Intertext House, Parkgate Road, London, S.W.11.

Please send book on _____

Name _____ Age _____
(Block Letters please)


Address _____

Occupation _____ 7-60

INTERNATIONAL CORRESPONDENCE SCHOOLS

TV TUBES

Completely Remanufactured as new

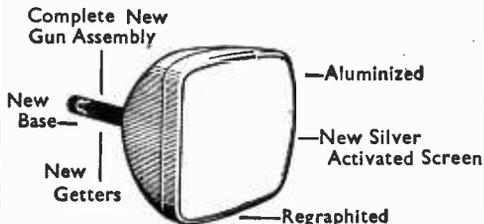

COMPLETELY NEW TUBES EXCEPT THE GLASS

ALL MAKES AND TYPES FROM STOCK

12"	£5 10 0
14"	£6 10 0
15"—17"	£6 19 0
21"	£8 15 0

12 months **NEW** tube guarantee.
C.W.O. or C.O.D. Carr. & Ins. 7/6 (passenger)
20/- refunded on your old tube if returned in our container.

The Finest Tubes. The Fastest Service

LAWSON TUBES

156 PICKERSLEIGH ROAD, MALVERN WORCS. MAL 3798

LINE OUTPUT TRANSFORMERS

Most types available. State Make and Model Number of Receiver when ordering.

S.A.E. please with all enquiries.

HOWORTH

51 POLLARD LANE, BRADFORD, 2, YORKS.
Tel. 37030

REBUILT TV TUBES

FULLY GUARANTEED 12 MONTHS
Complete New Gun fitted in every Tube

12in., 14in., ..	£5.0.0	17in.	£6.0.0
15in.	£5.10.0	21 in.	£8.0.0

Immediate Delivery
Carriage and Insurance 10/- extra

NU-GUN TELETUBES LTD.

3 The Mews, Duckett Rd., Harringay, London, N.4.
Telephone: MOUntview 2903

with no aerial but shadows seem to drift up and down.—G. Curnick (London S.E.13).

You should replace the U25 EHT rectifier wired on the right side line output transformer. The mains dropper is spring fitted and can be removed to enable the U25 to be reached a little easier.

BEETHOVEN 14in. CONSOLE

Is a Cyldon turret tuner E38H the correct one to use for the above set? I wish to take away the converter and replace with a turret tuner. This set is 5½ years old.—F. Morley (North Cray).

The Beethoven requires a P38H turret tuner for plug in conversion. The E38H could be used if separately supplied with a source of 6.3V for the parallel heaters. The reason being that the Beethoven has series heaters (0.3A) whilst the E38H has parallel heaters using ECC84 and ECF80 valves.

FRINGE RECEPTION

We are in a valley in a fringe area and television reception is difficult. I have two standard sets, an Ekco TC174 and a Ferguson 998T. The picture on the Ekco is quite reasonable but the sound on the Ferguson is faint, with a 4 element aerial at 30ft. There is no sound at all on the Ekco, I built an Argus pre-amp and a separate power unit H.T. 250V half-wave, L.T. 7.3V and completely screened the amplifier in a metal box, on the same chassis. I use a CV138 (6AM6) valve. I have checked and rechecked but can get nothing through it but very faint sound on the Ferguson. Both the TV chassis and pre-amp chassis were connected to the neutral side of the mains. The sound on the Ferguson is louder without the pre-amp. Is this type of pre-amp design suitable for very low signal areas? Would a cascode circuit be better. Should L1 and L2 be isolated from the chassis with 470pF capacitors?—J. Milton (Barnstaple).

Yours is a very difficult reception area in which, we understand, a "piped" TV service is being installed. A pre-amplifier cannot boost a signal which is not there, no matter how high the booster amplification. All that happens is an increase in background noise. In your case, however, it would seem that the pre-amplifier is failing to tune to the channel required. This may be caused by incorrect connection of the coils (or incorrect number of turns—try taking a turn off each coil), or incorrect alignment.

COLUMBIA C501N

I would like to add a turret tuner to this receiver and also modify the scanning to take a 17in. tube. Is this easily achieved or would it require considerable modifications.—T. Edwards (Chester).

In spite of the fact that a large number of Plessey Mk11 chassis were modified to take a 17in. CRT we do not consider this modification wholly satisfactory. You would need a new line output transformer, scanning coils, focus magnet and timebase valves and components to make a satisfactory job of it (such components are advertised together with the circuit) and of course a fair amount of experience to overcome the inevitable snags. However, the receiver is easily converted,

using a Cyldon E10L, a Brayhead 10P or a Teleng TT13P turret tuner. The I.F. is sound 10Mc/s, vision 13.5Mc/s.

ENGLISH ELECTRIC 16T110,

I suspect trouble in the line oscillation stage as I have touched a screwdriver on to the grid of this valve and voltage returned to normal for a couple of days. I have not been able to do this since. I have replaced rectifiers, (EHT) line output and efficiency diode.—J. Horner (Co. Durham).

Check the 4.7k resistor to pin 8 of the PL81, the 470k resistor to pin 7 of the EF80, the 47pF capacitor to pin 2 and the 0.1μF pin 7 to the control grid of the PL81. If the drive to the PL81 appears to be in order however, check the 0.001μF capacitors associated with the EY51 valves and the 470k resistors.

BANNER 124B

The above receiver has a Cyldon turret converter TV13K/P164. I am shortly moving to Andover and wish to take this set with me. What new coils do I require and the method of fixing these.—S. Whitewell (Wembley).

You will require coils for channels 3 (BBC) and 11 (ITV). This means you require two pairs of coil biscuits. These coils are 7/6d. per pair and when writing to the manufacturers you should state the type of tuner when ordering—Cyldon P16S (not P164).

REDIFFUSION R.T. 100/12

This is a 12in. set and in good working order but I would like to know if I could fit a larger tube. The existing tube is a Mazda 121A.—L. Massy (Southampton).

The use of a larger tube would necessitate replacement of the line output transformer, scanning coils, focus magnet etc., and a rebuilt line timebase. This is necessary to provide the extra scanning power and EHT required. Unless you have a good working knowledge of practical circuitry, we would advise you to adhere to the CRM121B (or CRM123) tube.

ARGOSY 14K41

About 15 to 20 minutes after switching the set on, and receiving good picture and sound, the picture starts to flicker or jump so that there are two pictures, vertically. If I switch off for a few minutes, then switch on again, I obtain a good picture for only 2 or 3 minutes. I have tried to adjust it by the frame hold, but to no avail.—D. Olley (Leicester).

There are two valves under the tube. That on the left centre is the PCL82 frame output-part oscillator, that on the right centre a PCF80 part-oscillator sync separator. Either could be at fault, probably the former (PCL82).

MARCONI VC59DA

This receiver has a 12in. tube (Emiscope) and I wish to fit a CRT isolation transformer to boost the tube, as the picture is very dull. Can you tell me the CRT heater voltage and current? — F. Smith (Watnell).

You should obtain a CRT isolation-boost transformer having a mains input primary and a

(13V + boost) secondary. Screw the transformer in a convenient position inside the cabinet, wire the primary tags, one to chassis, the other to terminal 1 on the mains selector panel. Remove the lead to 4 and place at 5 (or if now at 3, fit to 4). Remove the heater leads to the tube base pins 5 and 1 and connect these leads together. Connect the boost tags of the transformer to pins 5 and 7 in their place.

ULTRA WT917

For some time the picture has gradually been fading until it was impossible to see it. I fitted a new U25, U801, ZOP4 and 10P13. All the other valves have appeared reasonable when tested and all the valve heaters are in order. The raster is faint and has fold-over at the bottom. The sound is approximately half volume. There is no improvement on the raster when a 5k 10W resistor is placed between mains dropper yellow

lead and pin 12 of the CRT. The raster alters with adjustment of the controls—brightness, height. A good whistle is present which varies when controls are moved. I propose to fit a reconditioned CRT and would like advice on removing and fitting tube and also the reason for loss of volume. I have also fitted a new volume control (3M) because the on-off switch of the old one appeared to have burnt out. White lines at approximately 1in. intervals also appear across the raster. — W. Ramsden (Sheffield).

See that the ion trap magnet in the rear of the tube neck is correctly adjusted for maximum brilliance. Check parallel 8.2k anode resistors of V6—10F1 video amplifier and feed components to CRT cathode. CRT is removed with chassis and is secured to it by a front band and supports. Volume control is 0.5M. Check 20P3, alignment of sound I.F.'s and sound section electrolytic capacitors.

IS THERE ENOUGH SIGNAL?

(Continued from page 523)

The current in V1 is metered by M1, and in the no-signal condition the current through V1 is adjusted by P2 to give full-scale deflection of M1. When a signal is applied and tuned by the turret, the negative control bias which is then produced reduces the current of V1 and thus gives a deflection of M1 of magnitude depending on the applied signal. A very strong signal will make V1 tend towards anode current cut-off and give only a very small reading (large deflection for maximum current) of M1. This acts as an overload protection and prevents the meter movement from being damaged by a large signal.

Sensitivity

Switch S1 gives two positions of sensitivity. In the position shown, the full negative control bias (developed across R1 and R2 in series) is fed back to V1, and this is the most sensitive position. In the other position, the sensitivity is decreased by approximately ten times, since only the voltage across R2 is fed back to V1. In order to obtain a $\times 10$ reduction in sensitivity, R2 may have to be adjusted carefully in value by padding with either series of parallel resistors until the exact $\times 10$ decrease is secured. Exact calculation of this component is difficult owing to the curved characteristic of the controlled stage.

The video or audio of the rectified signal can be heard for signal identification by connecting a pair of headphones across the terminals indicated. The variable resistor, P1 should be adjusted to give the best accuracy over all the turret channels. The best position will normally be towards minimum resistance.

H.T. and L.T. Supply

The power pack is of very simple design, though adequate for this purpose. A simple mains transformer, with isolated primary, gives approximately 125V r.m.s. at 80mA maximum across its H.T. secondary, and 6.3V at 1.5A across the L.T. winding. The Brimar RM2 metal rectifier provides about 140V D.C., this being smoothed by two 16 μ F electrolytics and the filter resistor.

Meter M1 should have a full-scale deflection of 1mA or less, and a suitable shunt resistor can be connected across it to give full-scale deflection with the 'set zero' control at about the middle of its range.

The I.F. transformers should match the I.F. output of the tuner. These can be made in accordance with normal practice or can be purchased. Setting up involves connecting a signal to the input socket and adjusting the turret to the matching channel. A pair of headphones connected to the 'phones terminal assist in adjusting the I.F.'s to the vision signal with the fine tuner at midrange. The I.F.'s are simply peaked to the signal on the local channel. With other receivable channels, the oscillator cores in the corresponding coils are simply adjusted to give maximum vision signal with the fine tuner at midrange, it not being necessary to re-adjust the I.F.'s

The 'phones can then be disconnected and, with the signal removed, the 'set zero' control adjusted for full-scale deflection on the meter. When the signal is re-applied the meter deflection will decrease depending upon the strength of the signal. Calibration is best carried out by using a signal generator with a fairly accurate attenuator. If this is not available, most dealers catering for the experimenter would be prepared to calibrate the instrument for a small fee by plotting on a graph the meter deflection against signal voltage. Later, if required, the meter can be re-scaled in terms of microvolts (μ V) and millivolts (mV). The accuracy of the $\times 10$ attenuator and the calibration over all channels can also be checked at this time and suitable correction curves can be produced if necessary.

QUERIES COUPON

This coupon is available until JULY 22nd, 1960, and must accompany all Queries sent in accord with the notice on page 536.

PRACTICAL TELEVISION, JULY, 1960

TELEVISION SPARES

All Makes All Models By return of post

LINE OUTPUT TRANSFORMERS FRAME OUTPUT TRANSFORMERS
DEFLECTOR COILS

LINE AND FRAME BLOCKING OSCILLATOR TRANSFORMERS
ALL POTENTIOMETER AND SLIDER CONTROLS
MAINS DROPPERS METAL RECTIFIERS
GERMANIUM DIODES FOCUS MAGNETS
ION TRAPS E.H.T. CONDENSERS

Our Range of Spares is probably the most extensive in the country and includes all Spares for Tape Recorders, Radio and Record Player Units.

Technical Advice Free. Service Manuals supplied on loan.


Terms: C.W.O. or C.O.D. All Components are supplied at list prices, plus 2/6 p.p.

Please enclose S.A.E. with all enquiries.

NEWBURY RADIO

272, ROMFORD ROAD, FOREST GATE, LONDON, E.7.

MARyland 3100

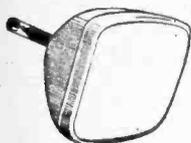

*** TOP QUALITY AT UNAPPROACHABLE PRICES**

With 12 Months Full Guarantee

NEW GUN TV TUBES

*This means Completely New Gun Assembly with New Button and Base. Rescreened and Realuminised. **VIRTUALLY A NEW TUBE.** All Mullard and Mazda and Hardglass Types.

12"-14"	-	-	£6.0.0
15"-17"	-	-	£6.10.0
21"	-	-	£9.0.0

Electrostatic Focus 10/- extra.
Trade enquiries welcomed.

All carriage and insurance now paid by us, to your address and on return of old tube all by passenger train, inclusive at £1 extra.

All C.W.O. Old tubes must be returned to us, or an extra charge of 10/- will be made on 12 to 17 in. tubes.

SABRINA C.R.T. COMPANY
"ELECTRON WORKS," NORTH BAR
BANBURY, Oxon. Phone 2390.

Still available - a practical comprehensive course in TV transmission and reception

A BEGINNER'S GUIDE TO TELEVISION

by F. J. Camm Covers:

Persistence of Vision and Scanning . Cathode-ray Tube . The Timebase . Receiving and Transmitting Systems . The Aerial . Tracing the signals through the Receiver . Video Section . The Television Camera . The tuning Signal, Test Card C, and tracing faults . Colour . The N.T.S.C. System—Tricolour Tubes explained . Telecine—Video Tape Recording . Stereoscopic Television . Technical Terms . Index.

With 61 illustrations



ONLY 7/6 FROM ALL BOOKSELLERS

... or in case of difficulty send 8s. 6d. to **GEORGE NEWNES LTD.,** Tower House, Southampton Street, London, W.C.2.

SETS & COMPONENTS

BRAYHEAD TURRET TUNERS for any area. Will convert over 600 models. Complete with fitting instructions. State set, model and two channels when ordering. 110m/c models 95/-. 16m/c and 35m/c 120/-. External cabinet (if required) 24/-. Carriage paid. CWO or C.O.D. **DURHAM SUPPLIES**, 175, Durham Road, Bradford 8, Yorkshire.

AERIALS AT TRADE PRICES

For Example **DOUBLE FIVE ARRAY COSTS ONLY 80/-**. Band III Self-contained Pre-Amplifiers. Only £3.15.0. Band III Converters, 100/- Turret Tuners, 94/- Complete Rebuilt TV Tubes from £5. Revacuumed ones. All Sizes, £2.10.0. All Tubes are Guaranteed. Super Low-loss Coaxial Cable, 1/1 yd. Standard, 6d. yd. Diplexers, 8/8 each. S.A.E. FOR FULL LISTS.

G. A. STRANGE, Broadfield, North Wraxall, Nr. Chippenham, Wilts. Tel.: Marshfield 236.

TV TUBES, factory rebuilt (re-gunned), fully guaranteed, 14in., £5, 17in., £6, p and p 10/-. 24, Bristol Road, Brighton.

BOURNEMOUTH

NATIONAL RADIO SUPPLIES

66 HOLDENHURST RD.

Tel.: 25232

Television Tubes. 12 month written guarantee. £6.19.6 and 10/- allowed on your old tubes. Carr. paid. 3 Element ITV and BBC dipole combined wall fixing, 34/6 and 4/6 carr. Complete range of capacitors, resistors, Hi-Fi radiogram chassis, amplifiers, motors and pick-ups, stereo and mono.

Bournemouth's Hi-Fi and constructors' centre.

NATIONAL RADIO SUPPLIES BOURNEMOUTH

TV TUBES. Factory rebuilt. Top quality with brand new gun assembly. 12 months' guarantee. All types. 12in., £5/10/6; 14 to 17in., £6. Carr. 12/6d. R. HAINSWORTH (Dept. C3), 31, Airedale College Mount, Undercliffe, Bradford 3, Yorks.

PENNINE I.T.V. converters 10 gns. type (used), 50/- p. paid. R. HAINSWORTH, 31 Airedale College Mount, Undercliffe, Bradford 3, Yorks.

T/V 100% SPARES

LARGE RANGE OF NEW AND USED SPARES

LINE OUTPUTS—ALL MAKES USED FROM £1. NEW FROM 45/-

Also breaking thousands of TVs for spares, i.e. Coils, Transformers, Chassis, Valves, etc. NO LISTS. Send S.A.E. and state requirements for immediate quote.

VALVES from 2/- each

Complete TV Valve Kit from 40/- Quote model number for exact price.

C.W.O. or C.O.D. ONLY.

S.O.S.

87 EVELINA ROAD, PECKHAM S.E.15

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Television," Tower House, Southampton St., London, W.C.2.

SETS & COMPONENTS (continued)

IS IT THE L.O.P.T.?

Be SURE with the SKANTEST. The most compact low-priced line output and time base component shorting turn tester. Will indicate even one shorting turn. £7.10.0. Carriage 5/-.



EAGLE MULTI-PURPOSE VALVE FILAMENT TESTER VT-41

Gives INSTANT check of:

- All radio and TV valves. • Fuses.
 - Pilot lamps. • Circuit continuity.
- Built-in 7 and 9 pin valve straighteners. Built-in battery tester. Aluminium front panel style printed in gold and black.

Complete with internal batteries, detailed instructions. ONLY 30/- (post 2/6)

NEW TUBES

	2 Years' Guarantee	1 Year Guarantee
12 in. MW 31-74	£5.5.0	£5.8.0
14 in. MW 36-24	£10.10.0	£8.0.0
17 in. MW 43-64/69	£12.0.0	£9.0.0
17 in. CRM	£13.10.0	£9.0.0

Carriage 7/6

LINE OUTPUT TRANSFORMERS

- Direct Replacements for 500 sets.
- Baird, T29, T163 ... 53/-
 - T164, T167, T172, 2014, 1712 ... 60/-
 - Bush, TV 11A, B; 12A, B; TVF 12A
 - TUG 12A, B; TRG 12A, B ... 45/-
 - TV12AM; TV22, 24; TRG24, TUG24 ... 60/-
 - Cosson, 830, 831, 833, 834, etc. ... 80/-
 - Ekco, TS46; TS113-114; T161, 164; T222, 231; TSC311, etc. ... 55/-
 - Ferguson, 841, 2, 3; 941 to 945 ... 55/-
 - 997-9987; 103-1457; 203-2467 ... 66/6
 - Ferranti, 1473, 17K3, 17T3 ... 45/-
 - 1472, T1205, T1215, T1225, T1325, T1405, T1415, T1425, T1505, T1825 ... 65/-
 - G.E.C. and H.M.V. mostly 55/- to 80/-
 - Invicta, T108 to T110 ... 52/-
 - T101-104; T114-126; T133-142 ... 60/-
 - Murphy, V114C, V116C, V118C ... 45/-
 - V120C, V180, V178, V200, V202C ... 57/6
 - Philips, 1114 UFUM, 1115 U, 1437 U, 1446 U, 1726 U, 1749 U, 1747 U ... 65/-
 - 383A, 483A, 563A, 663A ... 60/-
 - Pye, LV30, 16T, CS17, etc. ... 50/-
 - CTM4, V4, VT4; V7, VT7; VTI1 ... 80/-
- Add 2/6 post. S.A.E. with enquiries

WESTWAY RADIO

5 Westward Way, Harrow, Middlesex

RECLAIMED VALVES. All tested and perfect; modern and obsolete; huge stocks; all one price, 5/-, plus 6d. postage each, delivered by return. LEWIS, 46 Woodford Avenue, Ilford, Essex.

SETS & COMPONENTS (continued)

REBUILT TELEVISION TUBES—12in. £5; 14in. £5/10/-; 17in. £6/10/-. Twelve months guarantee. 10/- carr. **BRAYHEAD TURRET TUNERS**—£6/19/6. Carriage paid. State coils. All types BBC and ITA AERIALS. AIRSPAGED COAXIAL CABLE from 6d. per yard. **TELEVISION SPARES AND EXACT REPLACEMENTS**. The latest BSR, UA14 four-speed Changer £9/10/-. Carriage paid. All leading makes of TAPE RECORDERS, TAPES, AMPLIFIERS, TAPE DECKS, RECORD PLAYERS, TELEVISIONS and RADIOS. All new goods on Easy Hire Purchase Terms. **TRANSISTORS RED SPOT 5/6**. **TRANSISTORS WHITE SPOT 5/8** each. **GERMANIUM DIODES 1/-** each. Stamped addressed envelope please. For inquiries and callers are welcome.

DEVIZES TELEVISION SERVICE 29-30, The Nursery, Bath Road, Devizes, Wilts. Tel.: Devizes 1100.

TELEVISIONS.—Satisfaction guaranteed. 14in., 13 channel from £101 17in., 13 channel from £20. All in perfect working order. Sets for the engineer from £2 each, all complete. **RELYON RADIO** 439, Katherine Rd., Forest Gate, E.7.

"HEATHKITS" can now be seen in London and purchased on easy terms. Free brochure. **DIRECT TV REPLACEMENTS LTD.** 138, Lewisham Way, S.E.14. Tideway 6666.

AERIALS. Combined BBC dipole plus 3 element ITV with fittings 34/6 plus 4/6 post. TV Tubes 12 months' guarantee £6/19/6 post paid all sizes. Trade supplied. **NATIONAL RADIO**, 66, Holdenhurst Road, Bournemouth 25232.

NEW REBUILT TUBES, 12 months' guarantee. Free advice on fitting. Service Sheet Library. S.A.E. with enquiries... G. HURST, 3, Conlston Road, Sheffield 8.

TELEVISION TUBES

NEW TV TUBES. TWELVE Months' Guarantee

	Guarantee	£s.d.
12" MW 31-74	...	6. 0. 0
14" MW 36-24	...	7. 0. 0
17" MW 43-64	...	8. 0. 0
17" MW 43-69	...	8. 0. 0
Carriage	...	10/-

FULLY Rebuilt TV Tubes TWELVE Months' Guarantee

	Guarantee	£s.d.
12" MW 31-74 CRM 123	...	5. 0. 0
14" MW 36-24 CRM 141	...	5. 10. 0
14" AW 36-21 CRM 142	...	5. 10. 0
17" MW 43-46 CRM 171	...	6. 10. 0
17" MW 43-69 CRM 172	...	6. 15. 0
17" MW 43-80 CRM 173	...	6. 15. 0
21" MW 53-20 CRM 211	...	8. 15. 0
21" MW 53-80 CRM 212	...	8. 15. 0
15" CRM 152 CRM 153	...	6. 10. 0

Carriage paid

CATHODE RAY TUBE SERVICE

35 Broomwood Road, St. Paul's Cray Orpington 21285

SETS & COMPONENTS (continued)

C. EDWARDS

1070 HARROW ROAD
LONDON, N.W.10
LADBROKE 1734

Offers
S/H TV in
First-class
Condition.
12in. £5. 0/0
14in. £7.10.0
17in. £15. 0/0
(all 5 channel)
+15/- carriage.



Guaranteed VALVES
10F1, 10/-; 10C2, 7/6; 20D1, 6/-;
6Z1 5/-; 5P61, 7/-; 6K25, 8/-; 20P1, 10/-;
PZ30, 10/-; PL33, 7/-; ECL80, 8/-;
EB91, 6/- Plus 6d. post.
S/H. 12in. Tubes. 50/-, plus 7/6 post.

FERGUSON, EKCO

TV TUBES from stock. 17in. new gun £4/15/-, new gun and guaranteed. £5/15/-. 12 months' guarantee. TV ELECTRIC & CYCLE CO., 1 High Street, Chalvey, Slough, Bucks. Tel.: Slough 21860.

SALVAGED VALVES

2/6 each

Tested on Mullard High Speed Valve Tester

New and Boxed Valves all at 10/- each

S.A.E. FOR LIST

ARION TELEVISION, 4 Maxted Road, S.E.15 NEWX 7152

17 INCH tubes £5, new guns, all sizes available, guaranteed. STAR TUBES, Brief Street, Bolton.

THE TELEVISION TUBE SHOP

FOR FULLY REBUILT TELEVISION PICTURE TUBES
TWELVE MONTHS GUARANTEE

12in.	£4.10.0	allowance on
14in.	£4.10.0	old tube
14in. round	£5.5.0	10/-
15in. round	£5.15.0	10/-
17in.	£5.10.0	10/-
21in.	£8.0.0	20/-

Carriage 5/-

TAPE RECORDER

Build yourself a 57 guinea model 3-speed "STUDIO" deck fitted to motorboard with neon indicator and 7in. spool of tape ... **£15.15.0**
Ready built and tested 5 valve 5 watt amplifier. COMPLETE. No soldering required ... **£12.10.0**
Crystal Microphone and Plug ... **£2.10.0**
Cabinet to fit motorboard 7 deck also available.

48 Battersea Bridge Road, LONDON S.W.11. BATtersea 6859.

MULLARD TUBES, reclaimed, 6 months' guarantee. 9in., 30/-; 12-14in., 59/6; 17in., 79/6. All picture tested. FITTED FREE. Picture shown to callers. Other makes, types, cheap. Salvaged spares for modern and obsolete sets. Prices from: LOT 17/6, POT 7/6, Osc. Tr. 6/-, Mains Tr. 10/- Valves: 1,000 types in stock. EP91, EB91, 6/5; 2/6, EP80, 10P1, UP42, 3/6. Save money. Send a S.A.E. with enquiries or for free list. "ST. JOHN'S RADIO" 156, St. John's Hill, S.W.11. (BAT9838).

SETS & COMPONENTS (continued)

HAYNES O.P.T.'s. Line T33. Frame TK10/41. £1 each. 24 Doncaster Ave., Manchester 20.

**TV SPARES
LARGEST RANGE OF NEW
AND USED SPARES**

Line Outputs our Speciality. Used from £1. New from 45/-. Also breaking hundreds of TVs for Spares. All Coils, Transformers, Chassis, Valves, etc. No Lists. Send S.A.E. and State Requirements for Immediate Quote. **VALVE KITS**. A complete Kit for YOUR set (one of each type) from 50/-. Quote Model No. for exact price. **TV BARGAINS**. Reconditioned. All channel Models at New Low Prices. 14in. from 22 gns., 17in. from 29 gns. Fully guaranteed. Terms available.

T.C.S. LTD.

28 BROCKLEY CROSS, S.E.4.
112 CAMBERWELL ROAD, S.E.5.
Phone Tideway 5394.

TELEVISION TUBES! Rebuilt, new guns. 12 months' guarantee. 12/14in.. 70/-, 17in.. 79/6. Quantity discounts. 3, Pank Ave., New Barnet. BAR 3185.

**REBUILT
TV TUBES**

Fully Guaranteed

12 months

All makes—12" to 21"

**Blane & Martin
Electronics**

Sandown Lane, Liverpool

DETAILS ON REQUEST. Tel. SEF. 3428


HOLIDAY ACCOMMODATION

TORQUAY, "Springfield" Collaton Road. E. and B., 12/6. Parking.

MISCELLANEOUS

**"LITON" PHOTOELECTRIC
PARKING LIGHT SWITCH**

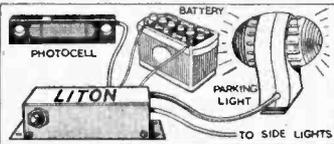Turns lights on and off, automatically as needed, while the driver is away.



Kit of parts: 52/6. Built: 57/6
Send 6d. stamp for Construction Manual
Photocells: 12/6 and 25/-. St. John's Radio
156 St. John's Hill, S.W.11. BAT 9838

FOR SALE

VALVE CARTONS at keen prices. Send 1/- for sample and list. J. & A. BOXMAKERS, 75a, Godwin Street, Bradford 1.

TELEVISIONS

All sizes including Projections. Require attention from £3. In working order—12in. BBC from £5. 12in. and 14in. BBC/ITA from £10. Re-gunned CRT £6 extra. 17in. from £25. Send for Lists. Carriage Paid.

CADMAN'S

SERVICE DEPARTMENT
BRYAN STREET, HANLEY
STOKE-ON-TRENT

100 BAYS of brand new adjustable steel shelving. 72in. High x 34in. wide x 12in. deep stove enamelled dark green, sent unassembled, six-shelf bay. £3/15/-. Sample delivered free, quantity discounts. N. C. BROWN LTD, Eagle Steelworks, Heywood, Lancs. Tel.: 69018.

SERVICE SHEETS! also Current and Obsolete Valves for sale. JOHN GILBERT RADIO, 20, Extension, Shepherds Bush Market, London W.12 (Phone: SHE 3052).

1,000 TELEVISIONS, all makes, from £3 working, 10/- not. Callers only 9 till 8, including Sats. 39, Whitehorse Lane, Stepley, London.

EXTENSION SPEAKER, 10/9. In attractive cabinet. Complete with 8in. P.M. Speaker, Flex and switch included. Standard matching to any receiver (2-5 ohms). Size 11 x 13 1/2 x 6 1/2 in. A nice present and a real bargain. P. & P. 3/6.

TELEPHONE SETS, 7/9. Ex. W.D. Wireless remote control unit E.Mk.II. New condition Morse tapper, switched, jack plugs, etc.; Less phone. Post 3/6.

P.P. COMPONENTS LTD.

219 Hiford Lane, Hford, Essex.
Mail Order only. Stamp for FREE catalogue.

WANTED

NEW VALVES WANTED. — EY51, ECL80, PCC84, PCF80, PCL83, PL81, PCL82, PY81, R19, U801, 30P4, etc. Best cash prices by return. DURHAM SUPPLIES, 175, Durham Road, Bradford 8, Yorkshire.

WANTED—VALVES. Modern TV and radio types. Large or small quantities. Box No. 22.

WANTED, Service Sheets. No quantity too large or too small; highest prices paid. SULTAN RADIO, 29, Church Road, Tunbridge Wells, Kent.

NEW TV VALVES WANTED. Send valves, cash by return to: P. J. F. Andrews, 81-63, Rosemary Road, London. SE.15.

A PROMPT CASH OFFER for your surplus Brand New Valves, Speakers, Components, Test Instruments, etc. R.H.S., 155, Swan Arcade, Bradford 1.

BEST PRICE paid by return for new Valves and equipment. STAN WILLETTS, 43, Spon Lane, West Bromwich, Staffs. Tel.: WES. 2392.

(continued overleaf)

EDUCATIONAL

"HOW AND WHY" of Radio and Electronics made easy by a new, non-maths, practical way. Postal instructions based on hosts of experiments and equipment building carried out at home. New Courses bring enjoyment as well as knowledge of this fascinating subject. Free brochure from Dept. 12, P.T. RADIO-STRUCTOR, 40, Russell St., Reading, Berks.

**★ LEARN
RADIO & TV
SERVICING
for your OWN
BUSINESS/HOBBY**

● by a new exciting non-maths system, using practical equipment, recently introduced to this country.

**FREE Brochure from:—
RADIOSTRUCTOR
DEPT. G78, 40 RUSSELL STREET
READING, BERKS. 7.60**

STUDY RADIO, TELEVISION AND ELECTRONICS with the world's largest home study organisation. Brit.I.R.E.; City and Guilds; R.T.E.B., etc. Also Practical Courses with equipment. No books to buy. Write for FREE Prospectus stating subject to I.C.S. Intertext House, Parkgate Road, (Dept. 516), London, S.W.11.

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text free. "The Practical Radio Engineer," journal, sample copy 2/., 6,000 Alignment Peaks for Superhets. 5/9. Membership and Entry Conditions booklet 1/., all post free from the SECRETARY, I.F.R.E., 20, Fairfield Road, London, N.8.

SERVICE SHEETS

SERVICE SHEETS. Largest stock Radio and TV Service Sheets North London. 4/., each with S.A.E. State make and model no. Circuit diagram only 2/6. Also Manuals for sale or hire. Radios over 20 years our speciality. All enquiries S.A.E. please. WYNDSOR TELEVISION, St. Albans Road, Barnet, Herts.

FAULTFINDER FILES (TV) showing common faults that each receiver is prone to and other useful servicing information 2/., each. List 9d. plus postage. S.P. DISTRIBUTORS, 11, Old Bond Street, London, W.1.

SERVICE SHEETS. Radio, T.V., 5,000 models. Lists 1/., S.A.E. enquiries. TELRAY, 11, Maudland Bk., Preston.

SERVICE SHEETS (continued)

SERVICE SHEETS.—Huge stock at 4/., ea. List 1/-. Immediate delivery. **GLOBE SUPPLIES**, 33, Fairfield Close, Sidcup, Kent.

SERVICE SHEETS for sale, all types from 1/- each, with free fault-finding guide. 125 Radio/TV Service Sheets, covering 370 popular models 20/-. S.A.E. lists/enquiries. **HAMILTON RADIO (T)**, 237, Sedlescombe Rd. N., Hastings.

SERVICE SHEETS.—We have the largest stock of Radio and TV Sheets in the country for sale at 4/., ea. 1960 Radio and Television Service Sheet List Now Ready. 1/-. Also Manuals for sale or hire. List 9d. S.A.E. please. Mail Order Only. S.P. DISTRIBUTORS, 11, Old Bond Street, London W.1.

SERVICE SHEETS. TV 4/- ea. Radio 3/- ea. List 1/-. All orders dispatched on day received. C.O.D. if required. Also manuals for sale and hire. **SULTAN RADIO**, 29 Church Road, Tunbridge Wells, Kent.

RES/CAP. BRIDGE 37/-
p. & p. 2/-
Checks all types of resistors, condensers
6 RANGES
Built in 1 hour. Direct reading
READY CALIBRATED
Stamp for details of this and other kits.
RADIO MAIL (Dept. AV)
Raleigh Mews, Raleigh Street, Nottingham

**A SUPER SPECIAL
TV TUBE OFFER**

Unused tubes made by world-famous manufacturers complete with 12 months makers guarantee. 17in. Tube to replace the MW43-64 43-69, 171K, 172K, 17 ASP4, 17 AXF4, C17-1, C17-A, CR17-22, C17-MW, MW 43-80, 68VW6 8/6, 6C4 3/3, 6C6 4/4, 6C9 9/3, 14-LP4, 141K, C98-24, or for AW 36-20, 36-21 12in. brand new 31 MW 31-74, all at 27 each. Also Cossor 65K 15in. 4 volt filament equivalent to TAI5 or 85K by fitting 6 volt filament transformer 10 gns. Cossor 108K 10in. equivalent to EMI 3/16 28.10.0. Ferranti 9in. T9/5 4 volt filament 50/- Post packing and insurance 10/- extra.

**NEW MAX
ELECTRONICS**

for London's Finest Bargains in electronic and radio equipment. Also Largest Selection of Tape Recorders in the U.K. Also in stock 500 shop soiled and H.P. reprocessed TV sets in all sizes. All Guaranteed.

220, Edgware Road, London, W.2.

Tel. PAD 5607

TRANSFORMERS

Suppliers to B.B.C.; I.T.A. and leading radio manufacturers, single or long runs, prompt delivery, home and export.

Rewinds to all makes.
H.W. FORREST (Transformers) Ltd.
Shirley, Solihull, Warwickshire
Tel.: SHIRLEY 2483

EDDY'S (Nottm.) LTD.

116-118 ALFRETON ROAD, NOTTINGHAM

**Build your own
CAR RADIO!**

★ 7 Transistors ● Long and Medium Waves ● Two Watts Output ● R.F. Stage and Automatic Gain Control



**10 1/2
Gns.**
P & P
5/- extra

6 or 12 volts (state which)
Supplied with full instructions
Size 7 1/2 x 7 1/2 x 2 1/2 in.
SPEAKER, extra 17/11

Surplus New and Guaranteed Valves

1A7GT 11/9	12K7G 5/3	ECH81 8/-
1D5 7/11	12K8GT 5/3	ECL80 7/6
1H5GT 9/6	11/3 1/3	ECL82 9/11
1L4 3/6	12SC7 7/11	EF36 3/-
1N5 9/6	12SH7 4/11	EF37 8/3
1R5 6/-	12S17 5/3	EF37A 7/11
1S5 5/11	12SQ7GT	EF39 4/-
1T4 3/11	5/11	EF40 13/3
3D6 4/11	12Q7G 5/3	EF41 8/3
3Q4 7/-	19AQ5 6/11	EF42 7/3
3Q5GT 8/6	25A6G 6/11	EF50 1/9
3S4 6/3	25L6GT 8/11	EF55 5/11
3V4 7/-	25Z4G 7/6	EF85 6/3
5U4G 5/-	25Z5G 7/11	EF86 10/-
5Y3GT 5/11	35A5 10/3	EF89 7/3
6AG5 4/-	35L6GT 8/11	EF91 3/6
6AL5 3/9	35W4 6/6	EF92 4/6
6AM6 3/6	35Z3 9/11	EF95 6/6
6AT6 6/11	35Z4G 5/3	EL41 8/3
688G 2/11	90AV 4/3	EL42 9/3
68A6 5/11	807B 3/3	EL84 6/6
68E6 5/11	954 1/6	EL85 10/3
68C6G 12/3	955 3/6	EL91 4/6
68J6 5/6	956 2/6	EY51 8/6
68VW6 8/6	9001 3/11	EY86 7/11
6C4 3/3	9004 3/11	EZ40 6/6
6C6 4/4	9006 3/11	EZ80 6/-
6C9 9/3	AZ1 12/6	EZ81 6/11
6CH6 9/9	CY31 9/6	GTIC 6/11
6D2 3/6	DAF96 7/9	KT33C 6/3
6F6G 6/-	DF96 7/9	OZ4 4/11
6H6 1/11	DH77 6/3	PCC84 7/3
6J5G 2/6	DK92 7/11	PCF80 7/3
6J5GT 3/6	DK96 7/9	PCL82 8/6
6I6 3/11	DL96 7/9	PCL83 11/3
6I7G 5/-	DM70 7/6	PL81 9/-
6K7G 1/11	EAB80	PL82 7/3
6K8G 5/6	6/11	PL83 7/3
6L6G 7/3	EAF42 8/3	PY32 10/11
6Q7G 6/-	EAL91 4/3	PY80 6/11
6Q7GT 9/-	EB34 1/3	PY81 6/-
6SK7GT 5/-	EB41 6/11	PY82 6/6
6SN7GT 4/3	EB91 3/6	UF42 8/11
6V6G 4/11	EB33 4/11	UB41 7/11
6V6GT 6/-	EB41 7/9	UB41 7/6
6X4 5/11	EBF89 6/3	UBF80 8/3
6X5G 4/11	ECC35 8/6	UCH42 7/6
7C5 7/6	ECC40 19/11	UCL82 11/3
7C6 7/6	ECC81 5/3	UF41 8/-
7H7 7/6	ECC83 6/11	UF42 7/3
7R7 10/3	ECC84 8/11	UF89 6/11
7S7 9/3	ECC85 7/11	UL41 7/3
7Y4 7/6	ECC91 5/3	UL84 7/3
12AH7GT	ECF80 9/6	UY41 6/3
6/6	ECF82 9/6	UY1N 10/11
12AH8 9/6	ECH42 8/3	VP41 5/11
12AT6 7/6		

Any parcel insured against damage in transit for only 6d. extra per order. All uninsured parcels at customers' risk. Postage and packing 6d. per valve extra. Over £3 Free C.O.D. or C.W.O. only. C.O.D. charge 3/- extra. Trade Supplied. S.A.E. with all enquiries.

BUY IT THE EASY WAY!

DUKE & CO. (London) LTD.
Dept. (E.7.)
621/3 Romford Rd., Manor Park, E.12. ILF 6001/3

NO DEPOSIT—INTEREST FREE—20 or 36 weeks to pay

STILL NO DEPOSIT ON OUR CREDIT SALES

SUMMER SALE! BARGAIN! 17" TV's COMPLETE 19 Gns.

Cash or terms over 20 weeks (NO interest charged). Initial payment £1.0.7 and 19 weekly payments of 19/11. Carr. and Ins. 30/- ITV/BBC. Beautifully styled polished cabinets. These are table models with the option of contemporary legs fitted (2 gns. extra). 17in. rectangular tube guaranteed for 12 months. Valves and chassis guaranteed for 3 months (chassis salvaged but reconditioned).


Where possible personal collection is advised.

Send for **FREE Catalogue**. Full details on goods and easy payments.


RECORD PLAYER CABINET R.P.2

59/6 CASH OR 4/1

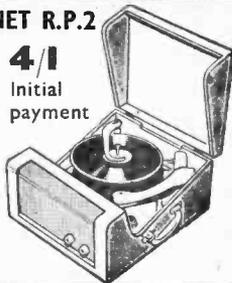Balance at 2/11 per week for 19 weeks. A beautifully styled cabinet. Made by a famous manufacturer. In polka dot cloth with clipped lid and carrying handle. Size 16 x 14½ x 8½ in. deep. Will take B.S.R. Monarch 4-speed Autochanger £6.19.6, and 7 x 4 in. Elliptical Speaker 19/6 and our Mk.D.2 Portable Amplifier 79/6. Carr. and Ins. 4/6.



Initial payment

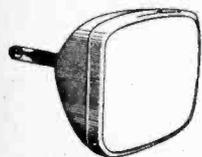

REPLACEMENT, REBUILT TV TUBES 12 MONTHS' GUARANTEE

21in. TUBE .. £8.10.0

17in. TUBE .. £7.10.0

12, 14, 15in. TUBES

TERMS AVAILABLE OVER 20 WEEKS £5.10.0

£2 allowed on old tube


£1 allowed on old tube

EXTENSION SPEAKERS 19/9

Polished oak cabinet fitted with 8in. P.M. speaker. Switch and flex included. Ideal kitchen, sheds, etc. Ins. & Carr. 3/9.

HOME RADIO 79/6 A.C. or Universal Mains

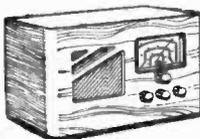5-valve octal superhet. 3 w/ band receiver. In attractive polished cabinet. Dimensions 9½ x 18½ x 11½ in. Ins. & Carriage 4/6. Terms available.



TV CHASSIS for SPARES

All this for only **9/6**

56 resistances including 7 variable controls. 54 condensers including electrolytics. Coils 7 i.F. and R.F. transformers. 13 valve holders (8-B8A, 2-B7G and 3 octal). 4 transformers: Mains, Output, Line, Frame. Chokes 250 mA. Metal Rectifiers: 300 volts at 250 mA. Fuse panel, scanning coils, focus magnets. Plugs, sockets, switch, chassis screws, tag strips, etc. 1.F strip can be separated. Power pack can be used without dismantling. These chassis have been used but were working when stored. 6 page circuit and instructions showing position of each component. Carriage 7/6.

REBUILT & REGUNNED C.R.T.s NEW ELECTRON GUNS FITTED

12 months' guarantee
Despatched Same Day

ALL types available:

Mullard, Mazda, G.E.C., Emiscope, Brimar, E.E., etc.

12"	£4. 5s. 0d.
14"	£4. 15s. 0d.
15"	£5. 5s. 0d.
17"	£5. 15s. 0d.
21"	£7. 0s. 0d.

Carriage and Insurance 7/6.

Cash with order to:

**REGAL ELECTRONICS
REGAL CHAMBERS
FERENSWAY, HULL**

For Safety's Sake use AVO Prodclips



Pat. No. 748811

...with Trigger-Action Spring-Loaded Clips

PRESS TRIGGER TO OPEN

RELEASE TO GRIP

Safety first every time with these patented spring-loaded AVO Prodclips.

Cleverly designed for use as insulated prods, they are invaluable for reaching and holding test points which are difficult of access.

Suitable for use with AvoMeter, Multiminor and Avo Electronic Test Meter Leads.

Post Free 15/- per pair.

AVO LTD • AVOCET HOUSE,
92-96 VAUXHALL BRIDGE ROAD, LONDON, S.W.1.
VICtoria 3404 (12 lines)

A MEMBER OF THE METAL INDUSTRIES GROUP OF COMPANIES

Go buy Suffolk Tubes . . . they're better!

EVERYTHING IN C.R.T.'s

REBUILT
RESCREENED
RE-ALUMINIZED



SUFFOLK TUBES LTD

SUFFOLK HALL 1-3 UPPER RICHMOND ROAD PUTNEY S.W.15

Tel. VANdyke 5267 and 4304

NEW VALVES!

Guaranteed Set Tested
24 HOUR SERVICE

1R5, 1S5, 1T4, 3S4, 3V4, DAF91, DF91, DK91, DK92, DL92, DL94, SET of 4, 21/6. DAF96, DF96, DK96, DL96, SET of 4, 27/6.

1D5	7/6	DL33	8/6	PCL82	7/6
1R5	6/3	DL35	10/6	PCL83	11/3
1S5	4/9	DL92	6/3	PEN44	11/-
1T4	4/-	DL94	7/3	PEN36C	8/-
3S4	6/3	DL96	6/11	PL38	11/6
3V4	7/3	EBC41	7/11	PL38	14/6
5U4G	5/3	EBF80	8/-	PL81	9/-
5Y3GT	6/-	ECC81	5/6	PL82	7/6
5Z4G	7/6	ECC82	8/-	PL83	7/6
6K7G	2/-	ECC83	6/6	PY32	11/-
6K8G	6/9	ECC84	8/3	PY80	7/-
6Q7G	6/3	ECC85	8/-	PY81	6/3
6SL7GT	6/-	ECC86	9/9	PY82	6/9
6SN7GT	4/9	ECH35	6/9	PY83	7/3
6V6G	5/-	ECH42	8/6	U25	13/-
6V6GT	6/3	ECL80	7/9	U26	11/-
6X5GT	5/-	EF41	8/6	U52	5/3
12K7GT	5/6	EF80	5/-	UA8C80	7/6
12K9GT	11/-	EF85	6/6	UF42	9/-
12Q7GT	5/6	EF88	10/3	UBC41	7/9
35Z4GT	9/-	EF89	7/6	UBF80	8/6
A231	8/9	EL84	6/9	UCC84	12/9
E36	8/8	EY51	6/6	UCC85	17/-
CL33	12/6	EY86	8/-	UCH42	7/9
DAC32	9/9	EZ40	6/9	UCH81	8/-
DAF91	4/9	EZ41	7/6	UCL82	10/-
DAF96	6/11	EZ80	6/3	UCL83	12/6
DF93	9/9	EZ81	7/-	UF41	5/3
DF91	4/-	GZ32	9/-	UF42	7/-
DF96	6/11	KT93	6/6	UF89	6/6
DH77	6/6	MU14	7/-	UL41	7/6
DK32	12/-	PC84	7/8	UL84	7/6
DK91	6/3	PC83	11/6	UY21	11/-
DK92	8/-	PCF80	7/-	UY85	6/9
DK96	6/11	PCF82	8/6	VP4B	9/6

Postage 6d. per valve extra. Any Parcel Insured Against Damage in Transit 6d. extra Any C.O.D. Parcel 2/6 extra. Office address, no callers.

GERALD BERNARD
90 CARR MANOR AVENUE
LEEDS 17

ALUMINIUM, LIGHT ALLOYS BRASS, COPPER, BRONZE

IN ROD, BAR, SHEET, TUBE, STRIP
WIRE, ANGLE, CHANNEL, TEE

3,000 STANDARD STOCK SIZES

H. ROLLET & CO. LTD.

6 CHESHAM PLACE, LONDON, S.W.1
BELgravia 4300

Works:
36 ROSEBERY AVE., LONDON, E.C.1

Branches at Liverpool, Manchester, Birmingham, Leeds.

"No Quantity too Small!"

B.B.C. - I.T.V. - F.M. AERIALS



B.B.C. (BAND 1). Tele-scopic loft, 19/6. External, S/D. 26/3.

I.T.V. (BAND 3). 3 Element loft array, 24/-, 5 Element, 32/6. Wall mounting, 3 Element, 33/9. 5 Element, 41/3.

COMBINED B.B.C. + I.T.V. Loft 1+3 Element, 41/3. 1+5 Element, 48/9. Wall mounting, 1+3 Element, 56/3. 1+5 Element 63/9. Chimney and mast mounting units also available.

F.M. (BAND 2). Loft "H", 28/-, 3 Element loft, 52/6. S/D loft, 12/6. External S/D. 26/3. State channel when ordering. C.W.O. or C.O.D. FP. 2/6. Coaxial cable, 8d. yd. Coaxial plugs, 1/3. Send 6d. stamps for illustrated lists.

K.V.A. ELECTRONICS (Dept.T.P.)
3B, Godstone Road, Kenley, Surrey

TELEVISION SERVICING PRACTICAL SERVICING AND FAULT-FINDING

More than 400 faults on a typical receiver have been considered, a large number of which have been placed on the receiver to obtain static and dynamic readings and oscillograph records.

By G. N. Patchett,

7/6. Vol. 4. Postage 6d.

THE RADIO AMATEUR'S HANDBOOK, by A.R.R.L. 1960 ed. 32/6. Postage 2/-.

A GUIDE TO AMATEUR RADIO an R.S.G.B. Pub. 3/6. Postage 6d.

TELEVISION SERVICING HANDBOOK by G. J. King. 30/- Postage 1/3.

PRACTICAL WIRELESS SERVICE MANUAL by F. J. Camm. 21/- Postage 1/-.

OSCILLOSCOPE TECHNIQUES by A. Haas 23/- Postage 1/-.

RADIO VALVE DATA 6th Ed. Compiled by "WW". Postage 9d.

1960 Catalogue 1/-.

THE MODERN BOOK CO.

BRITAIN'S LARGEST STOCKISTS of British and American Technical Books

19-23 PRAED STREET, LONDON, W.2

Phone : PADdington 4185.

Open 6 days 9-6 p.m.

FREE TO AMBITIOUS ENGINEERS

— THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

Have you sent for your copy?
ENGINEERING OPPORTUNITIES is a highly informative 156-page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses, administered by our Specialist Electronics Training Division—the **B.I.E.T. School of Electronics**, explains the benefits of our Employment Dept. and shows you how to qualify for five years promotion in one year.

We definitely Guarantee
“NO PASS—NO FEE”

Whatever your age or experience, you cannot afford to miss reading this famous book. If you are earning less than £20 a week, send for your copy of “ENGINEERING OPPORTUNITIES” today—FREE.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY (Incorporating E.M.I. Institutes)
 (Dept. SE/20), 29 Wright's Lane, London, W.8

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.,
 Electrical Eng.,
 Civil Engineering,
 Radio Engineering,
 Automobile Eng.,
 Aeronautical Eng.,
 Production Eng.,
 Building, Plastics,
 Draughtsmanship,
 Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

A.M.I. Mech. E.
 A.M.I.C.E.
 A.M.I. Prod. E.
 A.M.I.M.I.
 L.I.O.B.
 A.F.R. Ae. S.
 B.Sc.
 A.M. Brit. I.R.E.
 City & Guilds
 Gen. Cert. of Education
 Etc., etc.

PRACTICAL EQUIPMENT

Basic Practical and Theoretic Courses for beginners in Radio, T.V. Electronics, Etc., A.M. Brit. I.R.E. City & Guilds Radio Amateurs' Exam, R.T.E.B. Certificate P.M.G. Certificate Practical Radio Radio & Television Servicing Practical Electronics Electronics Engineering Automation

INCLUDING TOOLS!

The specialist Electronics Division of B.I.E.T. (Incorporating E.M.I. Institutes) NOW offers you a real laboratory training at home with practical equipment. Ask for details.

B.I.E.T. SCHOOL OF ELECTRONICS



POST COUPON NOW!

Please send me your FREE 156-page 'ENGINEERING OPPORTUNITIES' (Write if you prefer not to cut page)

NAME

ADDRESS

SUBJECT OR EXAM THAT INTERESTS ME (SE/20.)

GOVERNMENT SURPLUS & MANUFACTURERS CLEARANCE

TRANSISTORS

Red Spot (Seconds), 3/6 ea.
 OC71, 5/- ea. OC72, 7/6 ea.
 White Spot, 2.5 Mc/s, 6/6 ea.
 Yellow/Red Spot, 8 Mc/s, 12/- ea.
 Crystal Diodes, 1/- ea., 10/- doz.
 Specials, 2/- ea. Extra Sensitive, 3/- ea.

REBUILT TV TUBES

12in... .. £5.00
 14in... .. £5.10.0
 15in... .. £5.10.0
 17in... .. £6.0.0
 Mullard and Mazda types only.
 12 months' guarantee. Carriage and insurance 10/-.

VOLUME CONTROLS

Midget Long Spindle, 5 K ohms to 2 megohms. Less switch, 3/-. DP Switch, 4/6 Mixed Surplus Bargain Parcels. less switch, 15/- doz.

FERRITI POCKET MULTIMETERS

B.S.S. First grade Instrument. 500 ohms per volt. A.C., D.C., and ohms.
 UNUSED 70/- each

BATTERY CHARGER KITS

6 and 12 volt, 1 amp. .. 19/6 ea.
 6 and 12 volt, 2 amp. .. 29/6 ea.
 6 and 12 volt, 4 amp. ... 45/- ea.
 Ammeters for all types
 10/- extra.

I.F. TRANSFORMERS

465 kc/s Miniature 7/6 pair Combined
 465 kc/s and 10.7 Mc/s for P.M. 10/- pair.

ACOS CRYSTAL STICK MICROPHONES 39/6 ea.

PLASTIC RECORDING TAPE

5in. Standard, 600ft. 15/- ea.
 7in. .. 1200ft. 22/- ea.
 Long Play, 3in. 225ft. 7/- ea.
 .. 5in. 850ft. 21/- ea.
 .. 5 1/2in. 1200ft. 25/- ea.
 .. 7in. 1700ft. 32/6 ea.

EXTENSION SPEAKERS

5in. round, 3 ohm .. 16/6
 8in. round, 3 ohm .. 19/6
 12in. round, 3 ohm .. 29/6
 7 x 4in. elliptical, 3 ohm. 17/6
 8 x 5in. elliptical, 3 ohm. 21/6
 8in. round, in polished wooden cabinet, used .. 19/6

VALVES TESTED ON MULLARDS ELECTRONIC TESTER

1L4 5/-	6F1 7/6	8D2 4/6	EB41 7/6	P61 4/6
1T4 6/6	6F6 7/-	9D2 5/-	EB91 5/6	PEN45 7/6
1U1 6/-	6F13 7/6	10F1 7/6	ECH42 8/-	PEN48 7/-
3A4 6/-	6J5 6/-	12A6 7/6	ECL80 9/-	PL81 12/6
3Z4 9/-	6J6 6/-	12AH8 8/-	EF36 5/-	PL83 9/-
4D1 4/-	6J7 6/-	12AT7 6/-	EF37 9/-	SP41 4/-
6AG5 5/-	6K7 4/6	12AU7 7/-	EF39 5/6	SP61 4/-
6AL5 5/-	6L6 6/6	12AX7 7/-	EF50 3/6	VR15030
6AM5 5/-	6SA7 8/-	12BH7 10/-	EF50 5/6	
6AM6 6/-	6SC7 4/6	12SH7 5/-	EF80 8/-	UL84 9/-
6AQ5 6/-	6SJ7 5/-	12S17 6/6	EF91 8/-	VCR97
6AU6 7/-	6SK7 5/6	12SK7 6/-	EF92 7/-	
6BA6 8/-	6SL7 6/-	15D2 6/-	EL32 5/6	
6BE6 5/6	6SN7 7/-	50C5 10/-	EL91 5/6	15/-
6BH6 5/-	6T8 6/6	807 6/-	EF80 8/-	VCR138A
6BW6 6/6	6V6 6/6	EASO 1/6	EY51 5/-	25/-
6C4 5/-	6X4 7/-	EABCO80	EY51 8/-	VCR139A
6D2 6/-	6X5 7/-		EY86 9/6	25/-

SECONDHAND VALVES. YOUR CHOICE, £1.0.0 for EIGHT ECL80, 6C4, 6AM6, 6AG6, 6J6, EF50, 6BE6, 3A4, EF80, SP61, P61, 6J5, PY82, PY82, 7Z7, 6AL5, 6K7, 6SJ7, EL32, EF42, 6D2, 20P1, 6F13, SP41, EY51, EB91, EF91, EF93, PCL83, EF36, PEN45, PEN46.

ENQUIRIES—S.A.E. PLEASE

HUGGETT'S LIMITED
 2-4 PAWSONS ROAD WEST CROYDON

METERS. 500-0-500 Microamp, 3in. dia, 37/6 ea. Dual Range 0-5 v, 0-100 v. PSD 1 mA, 20/- ea.; 50-0-50 Microamp, 2 1/2in., 30/-
TV AERIALS. Combined BBC/ITV, 3 element, 32/6, 5 element, 37/6. ITV 3 element, 22/6, 5 element, 27/6.
CO-AX CABLE 6d. yd. AIR SPACED 1d. DIPLEXERS, 12/-
CONDENSERS. Twin Gang 0.0005 Standard, 5/6. Midget, 6/6.
VHF CHASSIS. contains over 50 components, 5/6 ea.
FERRITE ROD AERIALS. M. and L. wave, mfrs. surplus, 6/6 ea.
METAL BOXES. Well vent., ideal p. packs, etc. 11 x 11 x 7in. H. 8/6 ea.
SFL. RECS. 12 v, 1 amp., 5/-; 2 amp., 11/6. 4 amp., 15/- 500 v, 1 amp. containing 30/35 mm. discs., 10/- ea.
ELECTROLYTICS. Canned, 20±20 mid. 450 v., 2/6 ea., 25/- doz.
VAR. SLIDERS. 10 ohms 30 w. for chargers, trains, 3/- ea.
CONNECTING WIRE. P.V.C. 100ft., 2/6, various colours.
PICK-UP ARM with turn-over cartridge, 19/6.
SLEEVING 2, 3, 4, 5, M/m, 3d. yard, 2/6 dozen.
VENNER SILVER-ZINC ACCUMULATORS. H.105. New, 15/-
D.C. MOTORS. 3 x 1 1/2in. D.E. Spindle, very powerful, 12/6 ea.
SIEMENS HIGH SPEED RELAYS. 1000 plus 1000 ohms, 7/8 ea.
TANNOY RE-ENTRANT SPEAKERS. 7 ohms 8 w., 15/-, p. 3/6.
HEADPHONES. Moving Iron lightweight, low imp. 6/-; Bal. arm. 9/-. Moving Coil, 10/-.

REGUNNED TV TUBES

Supplied from stock and despatched by British Railways, same day. COMPLETE NEW MULLARD or SUPERIOR ELECTRON GUNS fitted in every tube, and fully guaranteed for 12 MONTHS FROM DATE OF INSTALLATION.

Mullard AW AND MW types available.

	Mullard	Mazda
12 in.	£5.0.0	£5.0.0
14 in.	£5.0.0	£5.0.0
15 in.	—	£6.0.0
17 in.	£6.0.0	£6.0.0
21 in.	£8.0.0	£8.0.0

Carriage & Insurance 10/- extra.

Other types available; Brimar, E.E., G.E.C. etc. C.W.O. to:—

CLARKSONS (Tube Distributors)

120 Commercial Road, LEEDS 5



RADIO-CONTROLLED MODELS by F. J. Camm . . . the book for the serious model maker.

12s. 6d. FROM ALL BOOKSELLERS

... or in case of difficulty 13s. 6d. by post from C. ARTHUR PEARSON LTD., Tower House, Southampton Street, London W.C.2.

SPECIAL VALVE OFFER

For Limited Period

EB91	4/-	UF42	8/6	6L1	8/-
ECL80	8/6	UL41	7/-	6L18	9/-
ECL82	9/-	UL44	7/6	6P25	9/6
EF80	5/-	UL46	7/6	6LD20	7/6
EF91	4/-	UBC41	7/6	6SN7GT	5/6
EL38	10/6	UCH42	7/6	7Q7	6/-
EY83	7/6	U35	8/6	10F1	6/-
GZ32	8/-	SP61	2/6	10P13	8/6
KT33C	6/6	3D6	2/6	10P14	8/6
KT36	8/6	6AT6	6/6	12AT7	6/-
PL33	8/-	6CH6	7/-	20D1	7/6
PL82	7/6	6BG6G	10/6	20P2	8/6
PL83	7/6	6F1	6/-	20L1	8/6
PY30	7/-	6F13	6/-	EC083	9/6
PY82	7/-	6F14	6/-	807	6/-
PZ20	11/-	6F15	6/-	PY31	7/6
UAF42	8/6	6JSQT	5/-	1625	6/-

Postage 4d. per Valve.

Coaxial Cable, 75 ohms. 6d. yd. Ion Traps, 5/-; Midget 2 Gangs, 6/6; 2Hn. Flush Meters, 0-100 mA and 0-500 mA. 15/-.

TV AERIALS: We carry large stocks, send S.A.E. with your requirements and we shall reply and send leaflets by return.

MAIL ORDER ONLY — NO CALLERS

Terms: C.W.O. or C.O.D., minimum C.O.D. 3/-; postage, packing, other than valves, under £2 1/6; under £5, 2/-; aerials 2/6.

ELECTRO SERVICES & CO.

221 BATTERSEA PARK RD., S.W.11

Mac. 6833/4

Factory Rebuilt . . . Super TELEVISION TUBES

All types fitted with New Gun Assembly. Fully guaranteed 12 months.

Mullard, Mazda, etc.:

12 inch	£5.0.0
14/15 inch	£5.10.0
17 inch	£6.0.0

Carriage and insurance 10/- C.W.O., C.O.D. or Credit terms available. S.A.E. for all enquiries.

Allowance on old tube.

K.V.A. ELECTRONICS (Dept. P/1)
3B Godstone Rd., Kenley, Surrey

A 3d. stamp will bring you a copy of our latest

RADIO & TELEVISION COMPONENT Catalogue
JAMES H. MARTIN & CO.
FINSTHWAITE, NEWBY BRIDGE
ULVERSTON, LANCs.

GUARANTEED VALVES

1L4	2/6	D77	3/6	PCF80	6/6
6F1	6/6	ECL80	7/6	PY30	6/6
6F15	7/6	EF80	5/-	PY32	6/6
10F1	6/6	EF91	3/-	SP61	6d.
20D1	6/6	EL32	3/-	UL46	7/6

All fully guaranteed for 3 months. Postage 6d. each. Send S.A.E. for list. SERVICE SHEETS, BOOKS COMPONENTS.

Send stamp for lists.
HAMILTON RADIO (T)
237 Sedlescombe Road North, Hastings, Sussex. (Mail orders only)

FIRST-CLASS TELEVISION and RADIO COURSES . .

GET A CERTIFICATE!

After brief, intensely interesting study — undertaken at home in your spare time—YOU can secure your professional qualification or learn Servicing and Theory. Let us show you how!

FREE GUIDE—

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success compelling qualifications as A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs' Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A. M. I. P. E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of SUCCESS OR NO FEE


Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSSES

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 462), 148, HOLBORN, LONDON, E.C.1.

S. Africa: P.O. Box 8417, Jo'burg.
Australia: P.O. Box 4570, Melbourne.

Build your own Aerials...

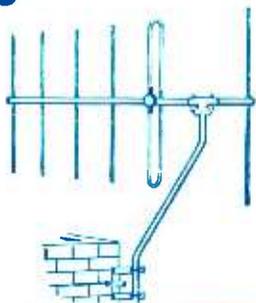

AT HOME

AERIAL FITTINGS FOR BAND III, BAND I & RADIO F/M. Useful formulae and hints for constructing your own aerial quickly and cheaply. Catalogue illustrating our increased range of Diecast Alloy Fittings, including Band III to Band I Mast Couplers, Reflector and Director Rod Holders, Insulators (both "Inline" and "H" types), Masthead Fittings, Masts and Elements, Chimney Brackets, etc. Send 1/- in stamps for the above, to:-

*Fringe*vision Ltd.

MARLBOROUGH, WILTS. Phone : 657/8

AS ADVERTISED ON TELEVISION

Save £££

12 Months' Guarantee

FACTORY REBUILT...

TELEVISION TUBES

ALL TYPES AND SIZES—Immediate Delivery

FITTED WITH COMPLETE NEW GUN

Price

12" £5.0.0 14" £5.0.0 15" £5.15.0 17" £6.0.0
21" £8.10.0

TERMS TO
THE TRADE

Plus 10/- carriage and insurance.
Cash with order or C.O.D.

RE-VIEW (LONDON) LTD.

10 High Street

Colliers Wood, S.W.19

Telephone: Liberty 3272

C.R.T. ISOLATION TRANSFORMERS
TYPE A. OPTIONAL 25% and 50% BOOST.
 2 V. OR 4 V. OR 6.3 V. OR 10.8 V. OR
 13.3 V. MAINS INPUT. 12/6
TYPE A2. HIGH QUALITY, LOW CAPACITANCE.
 10/15 p.p. OPTIONAL BOOST 25%. 50%.
 75%. MAINS INPUT. 16/6
TYPE B. MAINS INPUT. MULTI-OUTPUT 2, 4, 8.3, 7.3, 10 and 13 VOLTS. BOOST 25% AND 50%. LOW CAPACITY. 21/-

TRIMMERS, Ceramic. 30, 50 70 pF. 9d., 100 pF. 150 pF. 1/3. 250 pF. 1/6. 500 pF. 750 pF. 1/6.
RESISTORS. Preferred values. 10 ohms to 10 meg., 1 w., 4d.; 1 w., 4d.; 1 w., 6d.; 1 1/2 w., 8d.; 2 w., 1/-; 3 w., 1/1-; 4 w., 1/1-; 5 w., 1/1-; 10 w., 2/-; 20 w., 3/-; 50 w., 4/-; 100 ohm to 10 meg. 1/10, 5%, 100 to 5 meg. 1/9, 5 watt
WIRE-WOUND RESISTORS 1/3
 10 watt 25 ohms-10000 ohms 1/6
 15 watt 25 ohms-10000 ohms 2/-
 15,000 ohms-50,000 ohms, 5 w., 1/9; 10 w., 2/3.

PLASTIC RECORDING TAPE
 Long Play 7in. Plastic reel, 1700ft. 32/6
 Long Play 6 1/2in. Plastic reel, 1200ft. 22/6
 Long Play 5in. Plastic reel, 850ft. 19/6
 Long Play 3in. Plastic reel, 225ft. 7/6
 Standard 7in. Plastic reel, 1200ft. 21/-
 Standard 5in. Plastic reel, 800ft. 15/-
 "Initial" Bulk Tape Eraser and Head De-
 duxer, 200/250 v. A.C., 27/6. Leaflets, S.A.E.

O.P. TRANSFORMERS. Heavy Duty 50 A. 4/6.
 Multi-trap, push-pull, 7/6. Miniature, 384, etc. 4/6.
 Push-pull 10 w., 15/6. L.F. CHOKES 15 to 10 H. 60-65 mA, 5/-; 10 H. 85 mA, 10/6; 10 H., 150 mA, 14/-.

MAINS TRANSFORMERS 200/250 v. A.C. STANDARD. 250-0-250, 80 mA, 6.3 v. 3.5 a tapped 4 v. 4 a. Rectifier 3.5 v. 1 a. 5 v. 2 a. or 4 v. 2 a. ditto, 350-0-350 22/6
MINIATURE 200 v. 30 mA, 6.3 v. 2 a. 10/6
MIDGET, 220 v. 45 mA, 6.3 v. 2 a. 15/6
SMALL, 220-0-220, 50 mA, 6.3 v. 2 a. 17/6
STD., 250-0-250, 65 mA, 6.3 v. 3.5 a. 17/6
HEATER TRANS. 6.3 v. 1 1/2 amp. 7/6
 Ditto, tapped sec. 2, 4, 6.3 v. 1 1/2 amp. 8/6
 Ditto, sec. 6.3 v. 3 amp. 10/6

ALADDIN FORMERS and core. 1in., 8d.; 2in., 10d. 3in., FORMERS 5937/8 and Cans TV1 2. 4in. sq x 2in. and 4in. sq. x 1 1/2in. 2s. ea., with cores.
TYANA. Midget Solenoid Iron, 230 v. 25 w., 16/9.
REMPLOY Instrument Iron, 230 v. 25 w. 17/6.
MAINS DROPPERS. 3in. x 1 1/2in. Ad. Sliders, 0.3 amp., 1,000 ohms, 4/3, 0.2 amp., 1,000 ohms, 4/3.
LINE COIL. 0.3 amp., 60 ohms per ft., 0.2 amp., 100 ohms per ft., 2-way, 6d. per ft., 3-way, 7d. per ft.
LOUDSPEAKER P.M. 3 OHM. 5in. Kola, 17/6
 8in. Plessey, 19/6. 6in. x 4in. Kola, 18/-
 6in. Kola, 18/6. 10 x 6in., 27/6. 10in. Kola, 30/-
 4in. Hi-Fi Tweeter, 25/-, 12in. R.A., 30/-
 14 x 8in., 45/-, 12in. 15 ohm, 10 w. Plessey, 45/6
STENTORIAN HF 1012 10in. 3 to 15 ohm, 10 w., 95/-
 12in. Baker 15 watt 3 ohms, or 15 ohms, 105/-
CRYSTAL DIODE G.E.C. 2/-, GEX34, 4/-
HIGH RESISTANCE PHONES. 4,000 ohms, 16 6 pF
MIKE TRANS. 50 1/2, 3/3 ea., 100A, Potenti, 10/6
SWITCH CLEANER. Fluid squirt sprout, 4/3
TWIN GANG TUNING CONDENSERS. 365 pF miniature 1in. x 1 1/2in. x 1 1/2in., 0-9,000 Standard with trimmers, 9/-; less trimmers, 8/-; midget, 7/6
SINGLE. 50 pF, 25/-; 75 pF, 100 pF, 100 pF, 7/-; Solid dielectric 100, 300, 500 pF, 8/6.
SPEAKER FRET. GOLD CLOTH. 17in. x 2 1/2in., 5/-; 25in. x 3 1/2in., 10/-; Tyan 40in. 6in. wide, 10/-; 10in. 2ft. 3in. wide, 5/-; 10in. Samples S.A.E.

New and boxed VALVES 90-day Guarantee.

1R5	7/6	6BK84	7/6	6AR5	6/6	6HA80	12/6
1R5	7/6	6AL6	10/6	6EP1	6/6	6AR5	12/6
174	6/-	6NTM	6/6	6RC33	8/6	6HA2A	6/6
2X2	3/6	6Q7G	8/6	6EW11	8/6	6M14	9/-
3A4	7/6	68A7	6/6	6E1F6	10/-	6P1	3/6
3V4	7/6	68Y7	6/6	6E1C84	9/6	6E1C84	9/6
4C4	7/6	68S7	6/6	6E1F6	9/6	6E1F6	9/6
5Y3	7/6	6V90	6/6	6E1H42	10/6	6E1H42	11/6
5Z4	9/6	6HX4	7/6	6E1C82	10/6	6E1C82	6/6
6AM6	5/-	6X5	6/6	6E1F30	5/6	6E1F30	10/6
6BR	5/-	6Z47	8/6	6E1F41	6/6	6E1F41	7/6
6BE6	7/6	6E1F7	8/6	6E1F50	5/6	6E1F50	9/6
6RH6	9/6	6ZAX7	8/6	6E1F50	5/6	6E1F52	7/6
6BW6	9/6	62HE6	8/6	6E1F50	5/6	6E1F51	3/6
6D6	6/-	6C87	6/6	6E1F91	5/6	6E1C41	9/6
6E6G	7/6	6Q7	6/6	6E1F92	5/6	6E1H42	9/6
6T6	3/6	68S16	9/6	6E1F92	5/6	6E1P41	9/6
6T5	6/6	68Z74	7/6	6E1E84	8/6	6E1U41	9/6
6A7	6/6	68S0	9/6	6E1M1	9/6	6E1U41	9/6
6G6	6/6	68E07	8/6	6E1E84	7/6	6E1Y2	8/6
6K6GT	6/6	68Y54	1/6	6E1Z90	7/6	6E1R105	9/6
6K7G	5/6	6E1A60	1/6	6E1V118	1/6	6E1R105	9/6

TELEVISION REPLACEMENT LINE OUTPUT TRANSFORMERS

70/- ea. from stock.

For Makes and Models
Argosy: T2, CTV517. Decca: D17 & C. Defiant: TR1753. RGD: 6017T, 7017C, C54. Regentone: 17C, 17T, 17 Comb.

Argosy: T3. Decca: D14. Defiant: TR1453T. Regentone: 14T. RGD: 6014T.

Marconi: VT63DA. Baird: 2014, 2017, 2114, 2117.

Cossor: 930 & T, 931, 933-4-5, 937, 938 & A, & F. 939 & A & F, 943T, 946.

H.M.V. 1824 & A, 1825 & A, 1826 & A, 1827 & A, 1829 & A, 1865, 1869.

Marconi: VT68DA, VT69DA. Sobell: TS17, T.346.

Ferguson: 306T, 308T. Other makes available (7 days). S.A.E. with all enquiries.

LINE BLOCKING TRANSFORMERS, 10/- to 16/6.

FRAME BLOCKING TRANSFORMERS, 13/6 to 21/-
FRAME OUTPUT TRANSFORMERS, 27/6 to 39/-.
 Most makes available (7 days). S.A.E. with all enquiries.

TV and RADIO SERVICE SHEETS, 1,500 models. Send 2/6, your Model No. and S.A.E.

HIGH GAIN TV PRE-AMP KITS BAND I BBC
 Tunable channels 1 to 5. Gain 15dB ECUS valve. Kit price 29/6 or 49/6 with power pack. Details 6d. (PCUS valves if preferred)

BAND III ITA—Same prices. Tunable channels 8 to 13. Gain 17dB ECUS valve. (PCUS valves if preferred)

CRYSTAL MIKE INSERT by Avon, precision engineered. Size only 2 1/2in. x 3 1/2in. 6/6.

ALUMINIUM CHASSIS. 18 x 8 1/2 drilled. With 4 sides, riveted corners and lattice fixing holes, 2 1/2in. sides, 7 x 4 in., 4/6; 9 x 7 in., 5/9 1 1/2 in., 6/9; 13 x 9 in., 8/6; 14 x 1 1/2 in., 10/6 15 x 14 in., 12/6; 18 x 16 x 9 in., 16/6.

TELETRON "TRANSIDYNE" MIDGET SUPERHET PORTABLE 6 1/2 x 4 1/2 x 1 1/2 6 transistors, printed circuit, Ferrite aerial. All parts and cabinet, 9/6s.
 We include Ediswan Transistors for maximum performance. Details 9d.

BBC TRANSISTOR RADIO. Med. and Long Wave. Two transistors and diode. Complete kit, 32/6, phones 7/6 extra. Deaf Aid piece with Special Lead 15/-. Details 6d.

GARRARD RECORD PLAYERS

AUDIO PERFECTION

Designed to play 16, 33, 45, 78 r.p.m. Records 7in., 10in., 12in. Lightweight Xtal pick-up. G63 plug-in lead. Stereo Wired.
SINGLE PLAY TA MK II £8-8.
TRANSCRIPTION 4 HF £18.
AUTO CHANGER R.C. 121 £9-19-6.
 (Stereo heads 22 extra.) Leaflets, S.A.E.

Volume Controls 80 ohm CABLE COAX
 Long spindles. Guaranteed 1 year. Midget 5K ohms to 2 Meg. D.P.W. 3/-
 Linear or Log Tracks. Fringe Quality 1/- 7d.
 Post 1d. per yard extra. Semi-air spaced. 1in. dia. Losses cut 6d. yd.
 Fringe Quality 1/- 7d.
 Air Spaced 1/- 7d.

COAX PLUGS 2/- LEAD SOCKET 2/-
PANEL SOCKETS 1/- OUTLET BOXES 1/6
BALANCED TWIN FEEDER yd. 6d. 80 or 300 ohms
WITRO SCREENED per yd. 1/8. 80 ohms only
WIRE-WOUND POTS. WATT. Pre-set. Min. TV Type. All values 25 K to 25 K. 2/- ea. 30 K, 50 K, 4/-; (Carbon 30 K, to 2 meg. 3/-)
WIRE-WOUND 4 WATT. Pots Long Spindle Values, 100 ohms to 50 K, 6/6; 100 K, 7/6.
CONDENSERS. New Stock. 0.001 mfd. 7 kV. T. 5/6; 5/6; Ditto 20 kV., 9/6; 0.1 mfd., 7 kV. 9/6; Tubular 500 v. 0.001 to 0.05 mfd., 9d.; 0.1, 1/-; 0.25, 1/8; 0.5, 500 v. 1/8; 0.1, 350 v., 9d.; 0.01, 2,000 v., 0.1, 1/000 v. 1/8; 0.1 mfd., 2,000 volts, 8/6.
CERAMIC COMDS. 500 v., 0.3 pF to 0.1 mfd., 9d. **SILVER MICA CONDENSERS.** 10% 5 pF to 500 pF. 800 pF to 3,000 pF. 1/3. Close tolerance (±1 pF) 1.5 pF to 47 pF. 1/6. Ditto 1% 50 pF to 815 pF. 1/9; 1,000 pF to 5,000 pF, 2/-.

I.F. TRANSFORMERS 7/6 pair
 465 Kcs Slug Tuning. Miniature Cans. 3in. x 1in. x 1in. High Q and good bandwidth. By Eye Radio. Data sheet supplied.
WEARITE M800. Miniature, 12/6 pair. WEYMOUTH. Standard, 12/6 pair.

NEW ELECTROLYTICS. FAMOUS MAKES TUBULAR TUBULAR CAN TYPES

1.350v.	2/-	350/350v.	5/6	500v.	3/6
2.450v.	2/3	100/25v.	2/-	16,500v.	4/6
4.450v.	2	3.250/25v.	2/6	32.350v.	4/6
8.450v.	2	3.500/12v.	3/-	160/270.	5/6
8.500v.	2/8	1/8/450v.	4/6	2,500/30.	4/6
16.450v.	3/6	8/8/300v.	5/6	5,000/30.	4/6
16.500v.	4	8-16/450v.	5	32/350v.	4/6
32.450v.	5/6	8-16/500v.	5	32/32/350v.	7/6
35.250v.	1	9/16/16/500v.	5	5/50/50/300v.	7/6
50.250v.	2	16/16/2000v.	6/6	1/4/120/350v.	11/6
50.500v.	2	32/32/350v.	4/6	100/1/200/375v.	12/6

LATEST EMI. 4-SPEED SINGLE RECORD PLAYER. Avon 73 hi-fi stereo and normal crystal pick-up. Silent motor, heavy turntable. Special Offer, 22.18/6. Post 3/6

MAINS TYPE SELENIUM 300 v. 45 mA, 7/6.
CONTACT COOLED 250 v. 50 mA, 7/6; 60 mA, 8/6
 50 mA, 9/6; 200 mA, 12/-; 300 mA, 27/6
COILS. 100 pF, 100 pF, 200 pF, each. Reaction Midget 40/-; 400 pF, 1st core, 40/-; 400 pF, All ranges
TELETRON 1/2 & Med. T.R.F. with oscillator 3/6
FERRITE ROD AERIALS. M.W. 9/6 M. & L. 12/6
T.R.F. COILS 1/1H/7 pair. 11/6. H.F. CHOKES 2/6
FERRITE ROD. 7in. x 2in., dia., 2/6

JASON F.M. TUNER COIL SET. 26. H.F. coil, aerial coil. Oscillator coil, two I.F. traks. 10.7 Mcs. Ratio Detector and heater choke. Compact book using four G.M.C. 2/6.
COMPLETE JASON P.M. KIT. F.M.T. 5 kns. Set of valves, 20/-

FULL WAVE BRIDGE SELENIUM RECTIFIER: 250 v. 12 v. 1 1/2 amp. 9/6; 2 a., 11/3; 4 a., 17/6.
CHARGER TRANSFORMERS. Tapped output 200 v. for charging at 2, 3 or 12 v., 1 1/2 amps., 15/6. 2 amps., 17/6; 4 amps., 22/6. Circuit and led. VALVE and TV TUBE equivalent books, 5/-.
TOGGLE SWITCHES. S.P. 2/-; D.P. 3/6. D.P.D.T. 4/-
WAVELENGTH SWITCHES
 5 p. 4-way 2 water long spindle 0/0
 2 p. 2-way, or 3 p. 2-way short spindle 2/6
 2 p. 4-way, 4 p. 2-way, 4 p. 3-way long spindle 3/6
 3 p. 4-way, or 1 p. 12-way long spindle 3/6
VALVEHOLDERS. Pax Int. Oct., 4d. EF50, EA50 6d. 112A, CRT, 1/3. Eur. and Amer. 4, 5, 3 and 7 pins, 1/-
MOULDED MAZDA and Int. Oct. 6d. 87G, 85A, 86G, 19A, 9d. 87G with can., 1/8. 87A with can., 1/9. CERAMIC EF50, 67G, 87A. Int. Oct. 1/1. 50CAN 87G, 87A, 1/1-1/2

RADIO COMPONENT SPECIALISTS

Post and Packing 1/-, over £2 free. (Export post Extra.) C.O.D. 1/6. (Wed. 1 p.m.)

OUR ONLY ADDRESS
337 WHITEHORSE RD., WEST CROYDON
THO 1665. Buses 133 or 68