

TELEVISION


20p

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

DECEMBER
1973

VIDEO MIXER

FULL CONSTRUCTIONAL DETAILS

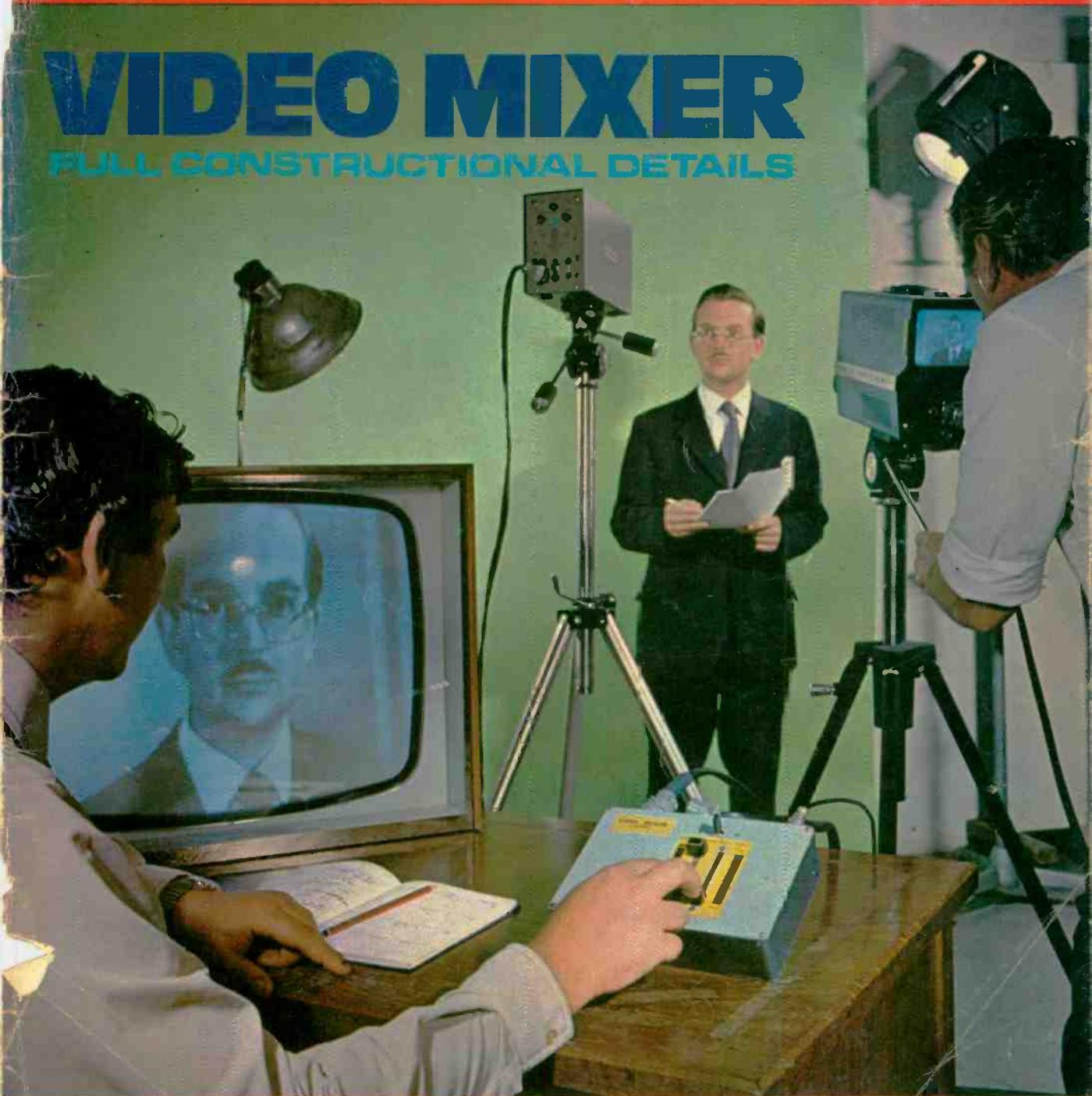

ALSO:-SERVICING THE GEC SERIES 1 CHASSIS-ADDITIONAL IF AMPLIFICATION

COLOUR, UHF AND TELEVISION SPARES

"TELEVISION" CONSTRUCTOR'S COLOUR SET. DEMONSTRATION MODEL. WORKING AND ON VIEW AT 172 WEST END LANE, N.W.6. ALREADY SEEN BY HUNDREDS OF CONSTRUCTORS. COMPLETE YOUR SET WITH MANOR SUPPLIES COMPONENTS. CALL. PHONE OR WRITE FOR UP-TO-DATE INFORMATION COLOUR LISTS.

MAINS TRANSFORMER 280W, for Colour Set. Guaranteed to give correct outputs under actual load conditions. Designed for original power board. No alterations. In successful use for ten months. £10.00 p.p. 70p.

SCAN PACK No. 21. Mullard or Plessey Scan Coils, Convergence Yoke, Blue Lateral, complete for £10.00 p.p. 45p.

PRINTED CIRCUIT BOARDS. Convergence 3 for £2.50 p.p. 30p. Decoder, I.F. amp. Time Base £1.25, Power £1.50 p.p. 25p. R.G.B. 70p p.p. 17p. Varicap, C.R.T. Base 66p p.p. 11p. Complete Set £8.25 p.p. 35p. Audio Panel & P.A. 263 £2.30 p.p. 15p.

PACKS (incl. p.p.). No. 2 £4.90, No. 5 £1.05, No. 9 45p, No. 12 31p, No. 13 35p, No. 14 £9.90, No. 15 £2.28, No. 16 £10.95, No. 17 £2.72, No. 19 £2.30, No. 21 £10.40, No. 22 £2.20, C.R.T. Base 30p, C.R.T. Shields £2.05 p.p. 55p, Varicap ELC1043 £4.50, TAA550 62p, AE Isolpanel 30p, Pack No. 23 £2.95, Pack No. 24 £1.25.

PACK 22. Manor supplies modification kit and circuit 30p.

CABLE 7 x 0.2 mm Screened 10 yds for 50p. Colours, 25p p.p. 10p. Line Osc. Coil 50p, 500 ohm Contrast 25p, 100 ohm W.W. 25p, 250 ohm 25W 30p, Slide Switches 15p, 14 MFD 1 KV 24p p.p. 10p.

SPECIAL OFFER I.F. Panel, leading British maker, similar design to "Television" panel. Now in use as alternative incl. circuit, and connection data £8.90, specially checked £13.80 p.p. 40p.

G.E.C. Colour decoder panels suitable for "Television" decoder parts incl. DL20, crystal, ident coil, etc., £3.50 p.p. 35p

CRT HEATER TRANSFORMERS 6-3V 1A £1.10 p.p. 25p.

PYE Line T.B. and power panels suitable for "Television" set parts £1.50 p.p. 35p.

MULLARD at 1023/05 convergence yoke. New £2.50 p.p. 25p.

PHILIPS G6 single standard convergence panel, incl. 16 controls, switches etc., and circuits £3.75 p.p. 30p, or incl. Yoke £5.00.

PHILIPS G8 decoder panel part complete incl. I/C £2.50, I.F. Panel part/compl. incl. modules £2.25 p.p. 30p.

BUSH CTV25 Mk. III Quadrupler Trays/E.H.T. £8.25 p.p. 25p.

KB CVCI convergence control panels. New, complete £3.75 p.p. 25p.

VARICAP/VARACTOR ELC 1043 UHF tuner (for "Television" colour receiver) £4.50. VHF Varicap tuners for band 1 & 3 £2.85. Varicap tuners salvaged, VHF or UHF £1.50 p.p. 25p.

UHF/625 Tuners, many different types in stock. Lists available. UHF tuners, transistd. £3.10, incl. s/m drive, indicator £3.85; 6 position or 4 position pushbutton £4.95. UHF/VHF transistd. tuner, latest type, incl. circuit £3.25. Cyldon valve type £1.50 p.p. 30p.

MURPHY 600/700 series UHF conversion kits in cabinet plinth assembly, can be used as separate UHF receiver £7.50 p.p. 50p.

SOBELL/GEC Dual 405/625 I.F. amp and o/p chassis incl. circuit £1.50 p.p. 30p. **PHILIPS 625 I.F. panel incl. cct** £1 p.p. 30p.

FIREBALL TUNERS Ferg. HMV, Marconi. New £1.90 p.p. 25p.

TURRET TUNERS. KB "Featherlight" VC11. Philips 170 series, GEC 2010 £2.50. AB Dual Stand, suitable Ferguson, Baird, KB, etc. 75p. Cyldon C 75p. Pye 110/510-Pam. Invicta. Miniature, increm. £1.95. Peto Scott 960, Decca 95/606 £1.50 p.p. 30p.

LINE OUTPUT TRANSFORMERS. Popular types available, brand new replacements, fully guar. A selection which can be supplied p.p. 30p. C.O.D. 28p.

MURPHY 849, 939, 153 24175 £4.90

PHILIPS 1768/2168, 1796/2196 £4.90

PHILIPS 17TG/100 Range

STELLA 1011/1029 £4.30

PHILIPS 19TG111/12 £4.40

PHILIPS 19TG121 to 156 £4.90

PHILIPS 19TG170, 210 series £4.90

BUSH TV92, 93, 105 to 186SS £4.90

ECKO 221/394 FERR 1001/1065 £4.30

ECKO, FERR. 418, 1093 etc. £4.30

DECCA DR95, 101/606, DRI,

2, 3, 121/123, 20/24, 2000 £4.70

FERR. 305 to 727, THORN 850 £4.70

FERR. HMV, MARCONI.

ULTRA, PHILCO 3600, 2600,

4600, 6600, 1100 series, Jell pot £4.70

KB VCI to VCI1 £4.40

GEC 302 to 456, 2000 series £4.90

P/SCOTT 960, COSSOR 1964 £4.70

PYE 17/21, 17/S, 110 to 510,

700, 830, 1, 2, 3, 11U to 64 £4.30

PYE 169, 569, 769 series £5.25

PAM, INVICTA equiv. LOPTS

to above PYE £4.30

SOBELL 195/282/1000 series £4.90

Transistorised I.F. panel (salvaged) £2.50 p.p. 25p

850 field output transformer £1.80 p.p. 20p

850 scan coils £4.40 p.p. 30p

THORN 850 Time Base Panel, Dual Standard £1 p.p. 30p.

THORN 850 Mains Droppers 30p p.p. 15p (state approx. values).

CALLERS WELCOME AT SHOP PREMISES

MANOR SUPPLIES


172 WEST END LANE, LONDON, N.W.6

(Near W. Hampstead tube stn; 28, 59, 159 Bus Routes) 01-794 8751

Mail Order: 64 GOLDERS MANOR DRIVE, LONDON, N.W.11

SOUTHEND ELECTRONICS

COLOUR 25 KV TRIPLERS

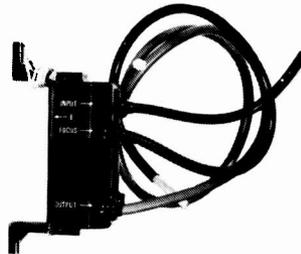

£1.70 + 17p V.A.T.

REPLACEMENT TRIPLERS

PYE C72 SERIES
GEC 2028 SERIES
PHILIPS G8 SERIES

£3.00 + 30p V.A.T.

E.H.T. RECTIFIER STICKS X80/150D

10p 1p V.A.T.

TRANSISTOR TUNER UNITS

VHF/UHF	£2.00	20p V.A.T.
6 Push Button VHF/UHF	£2.50	25p V.A.T.
6 Push Button UHF	£3.00	30p V.A.T.
UHF	£1.50	15p V.A.T.
300 Mixed Condenser	£1.00	10p V.A.T.
350 Mixed Resistor	£1.00	10p V.A.T.
100 w/w Resistor	£1.00	10p V.A.T.
40 Mixed Pots	£1.00	10p V.A.T.

PRINT PANELS WITH TRANSISTOR & RESISTOR & CONDENSER & RELAYS

£1.00 10p V.A.T.

Money returned if not completely satisfied

COLOUR PANELS
TRANSISTORS RESISTOR CONDENSER ETC.
£1.00 10p V.A.T.

I.F. PANELS, with Transistors & Resistor etc.,
10p 1p V.A.T.

SOUTHEND ELECTRONICS

240 RAYLEIGH Rd., EASTWOOD
LEIGH-ON-SEA, ESSEX

Telephone: Southend 521363

P.P. PAID UK ONLY

Reg: Office Only—No Personal Callers Please

TV LINE OUTPUT TRANSFORMERS

ALL MAKES SUPPLIED PROMPTLY by our
RETURN OF POST MAIL ORDER SERVICE

All Lopts at the one price

£4.40 TRADE £4.95 RETAIL (INCLUDING V.A.T.)

Except

BUSH MODELS TV53 to TV67, TV94 to TV101.
 EKCO MODELS TC208 to TC335, TV407 to TV417.
 FERGUSON MODELS 305 to 438, 506 to 546.
 FERRANTI MODELS 1084 to 1092.

Post and Packing 30p COD 33p
 HMV MODELS 1876 to 1878, 1890 to 1896, FR 20.
 MURPHY MODELS V280 to V330, V420, V440, 653X to 789 OIL-FILLED.
 REGENTONE MODELS 10-4 to 10-21, 1718, R2, R3, 191, 192.
 RGD 519-621, 710, 711.

ALL AT £2.75 + 30p P&P

EHT TRAYS SUPPLIED—MONO & COL.

All Lopts NEW and GUARANTEED for SIX MONTHS

E. J. PAPWORTH AND SON Ltd.,
 80 MERTON HIGH ST., LONDON, S.W.19

01-540 3955
 01-540 3513

PADGETTS RADIO STORE

OLD TOWN HALL, LIVERSEDEGE,
 YORKS. WF15 6PQ.

TEL: HECKMONDWIKE 405285

The T.V. Graveyard of the North, as seen on T.V. Close to the Motorway. Plenty of Free Parking Space. Est. 1935.
 FAMOUS R & A SPEAKERS. 30HM. 50p P & P. 12p.
 NEW TOP QUALITY MAINS TRANSFORMERS. 250v-250v at 80ma. 6-3v at 4 Amp. Not to be missed at £1.80. Post paid. Weight 10 lbs.
 COMPLETE UNTESTED T.V. SETS. With back and all valves. BBC1 & ITV. 17" 90° Tube £1. 17" 110° Tube £2.20. 19" £3.30. Carr. and Ins. on any set £1.65.
 50 UNTESTED T.V. VALVES 50p. Post PAID.
 1/2 CWT. OF EX GOVERNMENT ELECTRONIC SCRAP. Resistors, Panels, Gears, etc. 30p. Carr. 80p
 19" UNTESTED BBC2 SETS. When available £6. Carriage and Ins. £1.65.
 SPEAKERS. Removed from T.V. sets. all 3 ohm. 7 x 4", 8 x 2 1/2", 6 x 4" 27p. post 11p.
 TOP QUALITY TAPE. Reel to reel. 5" ST. 44p. 5" LP. 55p. 3 1/2" LP. 60p. 7" ST. 66p. 7" LP. 80p. Post on any Tape 11p. Tapes Cassette Type. C60 35p. C90 45p. C120 55p.
 JAP EARPIECE. 8 ohm Magnetic 2-5 12p. 3-5 12p.
 EX EQUIPMENT VALVES. All tested on our Mullard Valve Tester before despatch. 3 months guarantee on all Valves. Single Valves Post: 3p. Over post paid.

ARPI2	6p	PCF80	6p	PY82	10p
EB91	5p	PCC84	6p	PY33	20p
EF80	10p	PCL82	14p	U191	20p
EBF89	15p	PCL83	15p	6BW7	12p
ECC81	12p	PCL84	15p	6U4	12p
ECC82	12p	PL82	10p	6F23	20p
EF91	5p	PL83	10p	20P1	15p
EY86	22p	PL36	17p	20P3	12p
EF183	20p	PY81	10p	30F5	12p
EF184	20p	PY801	17p	30FL1	20p
		PY800	17p		

LAWSON TELEVISION TUBES



NEW TUBE SPECIFICATION

THE LAWSON RANGE OF NEW TUBES ARE DESIGNED TO GIVE THE ULTIMATE IN PERFORMANCE AND LIFE. MANUFACTURED BY BRITAIN'S LARGEST CRT PRODUCER. THEY ARE EXACT REPLACEMENTS AND INCORPORATE THE VERY LATEST DESIGN IMPROVEMENTS.

REBUILT TUBES

LAWSON
 "RED LABEL"
 CRTs ARE REBUILT
 FROM SELECTED
 GLASS AND ARE
 DIRECT
 REPLACEMENTS
 FOR ALL TYPES

	New Tubes £	Red Label £	Colour Tubes old glass not required
14"	3.85	—	
17"	6.87	5.47	19" £43.45
19"	7.97	5.77	
21"	9.35	7.65	22" £47.85
23"	10.70	7.97	
19" twin panel	11.28	9.07	25" £52.25
23" twin panel	17.05	10.72	
16" panorama	9.35	—	26" £54.45
19" panorama	10.32	7.65	
20" panorama	11.55	—	Carr. £1.65
23" panorama	13.15	9.63	

LAWSON TUBES

18 Churchdown Rd.

MALVERN
 WORCS.

Malvern 2100

2 year guarantee
 PRICES INCLUDE VAT

Carr./ins.
 14"-19" 68p
 20"-23" 82p





BENTLEY ACOUSTIC CORPORATION LTD.

7a GLOUCESTER ROAD, LITTLEHAMPTON, SUSSEX
All prices inclusive of V.A.T. Telephone: 6743

EA2	0-33	6A25	0-35	6F23	0-85	7B7	0-50	20D1	0-55	50B5	0-35	CV1C	0-55	EBL21	1-50	EP184	0-30	HVR2	0-53	PCL83	0-54	RY00	0-31	UY41	0-38
OB2	0-33	6A3	0-55	6F24	0-85	7D7	1-00	20D4	0-50	50C5	0-32	CV31	0-55	EC54	0-20	EP85	0-28	HVR2A	0-53	PCL84	0-54	RY81	0-31	UY85	0-23
OZ4	0-44	6A6	1-00	6F25	0-51	7H7	0-55	20P2	0-87	50CD662-17	1-7	D63	0-20	EC86	0-59	EP80	0-27	W37	0-37	PCL85	0-54	PZ30	0-48	U10	0-45
1A3	0-49	6A7	0-30	6F28	0-80	7R7	1-50	20L1	0-80	50EH5	0-55	DAC32	0-55	EC88	0-59	EP80	0-27	W37	0-37	PCL85	0-54	QV03/10	0-37	U16	0-74
1A5GT	0-49	6A8	0-28	6F32	0-30	7V7	1-00	20P1	0-55	50L6GT	0-85	DAF91	0-20	EC92	0-34	EP80	0-27	W37	0-37	PCL85	0-54	Q875/20	0-83	U17	0-35
1A7GT	0-33	6A9	0-33	6GH8A	0-75	7Y4	0-85	20P3	0-75	72	0-33	DAF96	0-36	EC93	1-50	EP80	0-27	W37	0-37	PCL85	0-54	Q895/10	0-49	U18/20	0-75
1B3GT	0-49	6AW8A	0-65	6GK5	0-65	7Z4	0-80	20P4	0-80	85A2	0-48	DC90	0-60	EC93	1-50	EP80	0-27	W37	0-37	PCL85	0-54	Q8150/15	0-63	U19	1-73
1D5	0-55	6AX4	0-55	6GU7	0-75	9B6	0-65	20P6	0-95	85A3	0-40	DD4	1-00	EC95	0-95	EP80	0-27	W37	0-37	PCL85	0-54	U22	0-39	U25	0-85
1D6	0-75	6BBG	0-55	6H6GT	0-18	9C2	0-40	25AG	0-35	90AG	3-38	DF93	0-60	EC98	0-75	EP80	0-27	W37	0-37	PCL85	0-54	U26	0-60	U31	0-83
1G8	0-75	6BA6	0-23	6J3GT	0-29	10C2	0-85	25L6G	0-20	90AV	3-38	DF91	0-20	EC98	0-75	EP80	0-27	W37	0-37	PCL85	0-54	U32	0-30	U34	0-30
1H3GT	0-55	6BC8	0-60	6J6	0-20	10DE7	0-55	25V5	0-38	90CG	1-70	DF96	0-36	EC98	0-25	EP80	0-27	W37	0-37	PCL85	0-54	U35	0-30	U36	0-30
1L4	0-14	6BE6	0-23	6J7G	0-24	10F1	0-50	25Y0	0-70	90CV	1-68	DF63	0-50	EC98	0-25	EP80	0-27	W37	0-37	PCL85	0-54	U37	0-30	U38	0-30
1LD5	0-66	6BG6G	1-05	6J7(M)	0-38	10F9	0-65	25Z4G	0-33	90C1	0-59	DF76	0-45	EC98	0-30	EP80	0-27	W37	0-37	PCL85	0-54	U39	0-30	U40	0-30
1LN5	0-66	6BH6	0-70	6J8A	0-75	10F18	0-55	25Z5	0-60	150B2	0-60	DF77	0-30	EC98	0-34	EP80	0-27	W37	0-37	PCL85	0-54	U41	0-30	U42	0-30
1NSGT	0-60	6BJ6	0-44	6K7G	0-19	10LD11	-70	25Z6GT	-70	301	1-00	DF81	0-75	EC98	0-85	EP80	0-27	W37	0-37	PCL85	0-54	U43	0-30	U44	0-30
1R5	0-55	6BK7A	0-60	6K8G	0-33	10P13	0-54	3012	0-70	302	0-63	DK32	0-33	EC98	0-44	EP80	0-27	W37	0-37	PCL85	0-54	U45	0-30	U46	0-30
1S4	0-33	6BQ5	0-23	6L1	2-00	10P14	2-00	30A5	0-85	303	0-75	DK40	0-20	EC98	0-59	EP80	0-27	W37	0-37	PCL85	0-54	U47	0-30	U48	0-30
1S5	0-22	6BQ7A	0-50	6L6GT	0-55	12A6	1-00	30C1	0-28	305	0-83	DK91	0-28	EC98	0-55	EP80	0-27	W37	0-37	PCL85	0-54	U49	0-30	U50	0-30
1U4	0-44	6BR7	0-90	6L7	0-50	12AC9	0-55	30C5	0-58	306	0-65	DK92	0-50	EC98	0-75	EP80	0-27	W37	0-37	PCL85	0-54	U51	0-30	U52	0-30
1U5	0-80	6RR8	0-75	6L12	0-34	12AD6	0-50	30C7	0-78	807	0-59	DK96	0-45	EC98	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U53	0-30	U54	0-30
2D21	0-44	6BS7	1-40	6L18	0-49	12AE6	0-60	30C18	0-70	1821	0-53	DL33	0-55	EC98	0-34	EP80	0-27	W37	0-37	PCL85	0-54	U55	0-30	U56	0-30
2GK5	0-55	6BW6	0-72	6L19	2-00	12AT6	0-28	30F5	0-61	4033X	1-25	DL92	0-28	EC98	0-84	EP80	0-27	W37	0-37	PCL85	0-54	U57	0-30	U58	0-30
3A4	1-00	6BW7	0-50	6LD12	0-30	12AT7	0-20	30FL1	0-75	5702	0-80	DL96	0-38	EC98	0-42	EP80	0-27	W37	0-37	PCL85	0-54	U59	0-30	U60	0-30
3B7	1-00	6BZ6	0-49	6L20	0-55	12AU6	0-38	30FL2	0-75	6060	0-30	DM70	0-20	EC98	1-50	EP80	0-27	W37	0-37	PCL85	0-54	U61	0-30	U62	0-30
3D6	0-19	6C4	0-28	6N7GT	0-60	12AU7	0-25	30FL12	0-89	7193	0-53	DM71	0-50	EC98	0-50	EP80	0-27	W37	0-37	PCL85	0-54	U63	0-30	U64	0-30
3Q4	0-49	6C6	0-22	6P15	0-23	12AV6	0-28	30FL13	0-50	7475	0-70	DW4/600-38	0-38	EC98	0-50	EP80	0-27	W37	0-37	PCL85	0-54	U65	0-30	U66	0-30
3Q5GT	0-55	6C9	1-00	6P28	0-70	12AX7	0-23	30FL14	0-68	1834	1-00	DY87/60-30	0-30	EC98	0-28	EP80	0-27	W37	0-37	PCL85	0-54	U67	0-30	U68	0-30
3S4	0-26	6C12	0-28	6Q7G	0-50	12BA6	0-30	30L1	0-29	A2134	0-98	DY802	0-30	EC98	0-44	EP80	0-27	W37	0-37	PCL85	0-54	U69	0-30	U70	0-30
4CB8	0-55	6C17	1-00	6Q7(M)	0-55	12BE6	0-30	30L15	0-55	A3042	0-75	E80CC	1-65	EC98	0-44	EP80	0-27	W37	0-37	PCL85	0-54	U71	0-30	U72	0-30
5CG9	0-55	6CB8A	0-40	6Q7GT	0-50	12BH7	0-27	30L17	0-65	AC2/PEN	0-98	E80F	1-20	EC98	0-40	EP80	0-27	W37	0-37	PCL85	0-54	U73	0-30	U74	0-30
5R4G	0-70	6CD8G	0-80	6R7	0-75	12JGT	0-30	30P4MR	0-98	E83F	0-98	E83F	1-20	EC98	0-28	EP80	0-27	W37	0-37	PCL85	0-54	U75	0-30	U76	0-30
5T4	0-30	6CG8A	0-75	6R7G	0-60	12J7GT	0-55	30P12	0-89	AC6/PEN	0-38	E88CC	0-40	EC98	0-52	EP80	0-27	W37	0-37	PCL85	0-54	U77	0-30	U78	0-30
5U4G	0-30	6CH6	0-55	6SA7	0-44	12K5	0-53	30P16	0-31	AC2/PEN	0-98	E92CC	0-40	EC98	0-54	EP80	0-27	W37	0-37	PCL85	0-54	U79	0-30	U80	0-30
5V4G	0-30	6CL6	0-55	6SC7GT	0-33	12K7GT	0-38	30P19	0-98	DD	0-98	E180F	0-90	EC98	0-54	EP80	0-27	W37	0-37	PCL85	0-54	U81	0-30	U82	0-30
5Y3GT	0-30	6CL8A	0-80	6S07	0-44	12Q7GT	0-45	30P4	0-75	AC/PEN(7)	0-98	E182CC	1-00	EC98	0-33	EP80	0-27	W37	0-37	PCL85	0-54	U83	0-30	U84	0-30
5Z3	0-53	6CM7	0-75	6S17	0-44	12S7GT	0-55	30P11	0-57	E1148	0-53	E80	0-53	EP80	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U85	0-30	U86	0-30
5Z4G	0-54	6CU5	0-75	6S17	0-35	12S7	0-50	30P12	0-32	FA50	0-27	EP80	0-27	EP80	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U87	0-30	U88	0-30
5Z4GT	0-38	6CW4	0-70	6SK7GT	0-44	12S0G	0-38	30P113	0-75	AC/TP	0-98	EA76	0-88	EP80	0-49	EP80	0-27	W37	0-37	PCL85	0-54	U89	0-30	U90	0-30
630L2	0-85	6D3	0-60	6S07GT	0-38	12SH7	0-35	30P14	0-75	AL60	0-75	EABC80	0-30	EP80	0-41	EP80	0-27	W37	0-37	PCL85	0-54	U91	0-30	U92	0-30
6A8G	0-48	6DE7	0-75	6U4GT	0-70	12S7	0-44	30P115	0-87	ARP3	0-35	EAC91	0-38	EP80	0-42	EP80	0-27	W37	0-37	PCL85	0-54	U93	0-30	U94	0-30
6AC7	0-15	6DT6A	0-75	6U7G	0-75	12S7	0-55	35/51	0-63	ATP4	0-40	EAF42	0-48	EP80	0-75	EP80	0-27	W37	0-37	PCL85	0-54	U95	0-30	U96	0-30
6A05	0-27	6E2W6	0-75	6V6G	0-17	12S7	0-60	35A3	0-48	AZ1	0-40	EAF801	0-50	EP80	0-23	EP80	0-27	W37	0-37	PCL85	0-54	U97	0-30	U98	0-30
6A16	0-50	6E5	0-75	6VGT	0-27	12S7GT	0-55	35A5	0-75	AZ1	0-48	EP80	0-27	EP80	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U99	0-30	U100	0-30
6A35	0-75	6F1	0-70	6X4	0-30	14H7	0-55	35D5	0-70	AZ1	0-53	EP80	0-27	EP80	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U101	0-30	U102	0-30
6AK5	0-27	6F6G	0-50	6X5GT	0-28	1487	0-75	35L6GT	0-55	B38	0-80	EP80	0-27	EP80	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U103	0-30	U104	0-30
6AK6	0-80	6F13	0-45	6Y6G	0-85	19A05	0-42	35W4	0-30	B319	0-20	EP80	0-27	EP80	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U105	0-30	U106	0-30
6AM6	0-17	6F14	0-40	6Y7G	1-00	19BGG	0-80	35Z2	0-50	CI33	0-20	EP80	0-27	EP80	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U107	0-30	U108	0-30
6AM8A	0-55	6F15	0-65	7A7	0-29	19G6	1-40	35Z4GT	0-42	CV6	0-53	EP80	0-27	EP80	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U109	0-30	U110	0-30
6AN8	0-49	6F18	0-55	7B8	0-75	19H1	2-00	35Z5GT	1-00	CV63	0-53	EP80	0-27	EP80	0-27	EP80	0-27	W37	0-37	PCL85	0-54	U111	0-30	U112	0-30

All goods are unused, boxed, and subject to the standard 90-day guarantee. Cash or cheque with order. Despatch charges—Orders below £5, add 10p per order up to three items, then each additional item 3p extra. Orders between £5 and £10 add 25p total. Orders over £10 post free. Same day despatch. Any parcel insured against damage in transit for only 3p extra per order. Terms of business free on request. Business hours Mon.-Fri. 9-5.30 p.m. Closed 1-2 p.m. We do not handle seconds nor rejects, which are often described as "New and Tested" but have a limited and unreliable life. No enquiries answered unless S.A.E. is enclosed for a reply. No overseas orders.

COLOUR TV

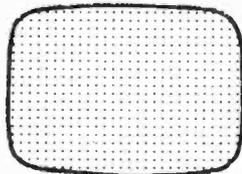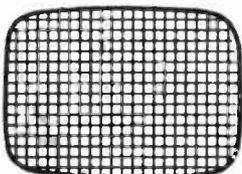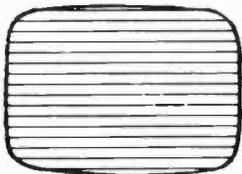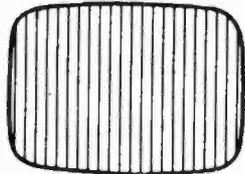

CROSS HATCH GENERATOR

Complete kit for Cross Hatch Generator as described in "TELEVISION"

September 1972 issue

The only way to obtain 100% convergence of colour guns in any colour TV

£3.85

A. MARSHALL & SON (LONDON) LTD.,

SEMICONDUCTOR SPECIALISTS

42 CRICKLEWOOD BROADWAY, LONDON, N.W.2
Telephone: 01-452 0161/2 Telex: 21492 Cable: Coninst London
NEW LOW PRICES LARGEST RANGE BRAND NEW
FULLY GUARANTEED

★

COLOUR TELEVISION

- Television Kit No. 1 **£8.42**
PAL Decoder
- Television Kit No. 4 **£8.26**
I.F. Strip
- Television Kit No. 8 **£6.66**
R.G.B Board
- Television Kit No. 10 **£7.50**
Time-Base

For Colour Television Project
featured in this Magazine

SPECIAL OFFER

Recording Tapes Standard Play
10½" 2,400ft. £1.25 to clear
Package & Posting 20p

100-watt Guitar Amplifier—complete
kit with case and all components **£23.50**

"SCORPIO"

Capacitor discharge ignition system (as described in
Practical Electronics, Nov. 1971).


COMPLETE KIT **£10.00** P. & P. 50p.

We Stock Full Range of:
Motorola consumer I.C.s
RCA Cos-Mos
Signetics popular I.C.s

★

**ALL PRICES EXCLUSIVE
OF V.A.T.**

look!

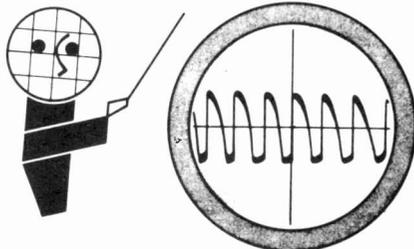

electronics really mastered

...practical ...visual ...exciting!


no previous knowledge no unnecessary theory no "maths"

BUILD, SEE AND LEARN


step by step, we take you through all the fundamentals of electronics and show how easily the subject can be mastered. Write for the free brochure now which explains our system.

1/ BUILD AN OSCILLOSCOPE

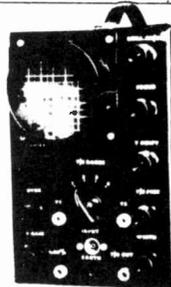You learn how to build an oscilloscope which remains your property. With it, you will become familiar with all the components used in electronics.



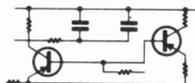2/ READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS



as used currently in the various fields of electronics.

3/ CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS & SEE HOW THEY WORK, including :

valve experiments, transistor experiments
amplifiers, oscillators, signal tracer, pho-
to electric circuit, computer circuit, basic
radio receiver, electronic switch, simple
transmitter, a.c. experiments, d.c. experi-
ments, simple counter, time delay circuit,
servicing procedures

This new style course will enable anyone to
easily understand electronics by a modern,
practical and visual method—no maths, and
a minimum of theory—no previous knowledge
required. It will also enable anyone to under-
stand how to test, service and maintain all
types of electronic equipment, radio and TV
receivers, etc.

FREE POST NOW
for
BROCHURE

or write if you prefer not to cut page

BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL P.O. BOX 156, JERSEY
CHANNEL ISLANDS we do not employ representatives

Please send your free brochure, without obligation, to:

NAME _____ BLOCK CAPS
ADDRESS _____ PLEASE TL123

**special free gift
also to all our students**

**Still waiting for spares Tom?
You should have phoned**



WHEREVER YOU ARE FOR BY
RETURN DESPATCH. WILLOW
VALE IS AS NEAR AS YOUR
PHONE.....

WILLOW VALE

The Wholesaler who knows what SERVICE is really about!



BY RETURN DESPATCH:- HOT LINES: 01-567 5400/2971

L.O.P.T's, TRANSISTORS, RECTIFIER TRAYS, COMPONENTS
MONOCHROME and COLOUR C.R.T's, new and re-built.
HUGE RANGE OF VALVES up to 46% DISCOUNT



A FULL RANGE OF TEST - METERS, SERVICE AIDS, TOOLS, ELECTROLUBE
and Servisol products. Multicore solders, plugs and sockets, capacitors, bias and
smoothing electrolytics, volume controls, pre-sets, $\frac{1}{2}$, 1 and 2 watt carbon film res.



We SPECIALISE in supplying the Service Engineer

Test equipment by : Labgear, Philips,
Meteronic etc. Colour bar & Pattern
generators, oscilloscopes & meters



**68 PAGE CATALOGUE
FREE ON REQUEST**

**Hot line
orders:- willow vale**

The Service Department Wholesalers

LONDON: 4/5 The Broadway · Hanwell · London W7 · 01-567 5400

GLASGOW: 74 Maxwellton Road · Paisley · 041-887 4949

SOMERSET: 42 West End · Street · Somerset · 045-84 2597



I would like a free copy of your catalogue:

Name _____

Address _____

STRICTLY WHOLESALE ONLY NO RETAIL ENQUIRIES PLEASE.

TELEVISION

SERVICING · CONSTRUCTION · COLOUR · DEVELOPMENTS

VOL 24 No 2
ISSUE 278

DECEMBER 1973

DEVIOUS ROUTE

Have you purchased any good semiconductors lately? For those who may think this a music-hall joke line, it is not intended that way. The fact is we often don't know by what method or route semiconductors come into our hands. We pay our money and receive the goods. How many really care beyond checking that a "fair" market price has been paid? In all innocence, however, you may not be buying what you think you are, and this is increasingly the case in all parts of the world.

In America cases have been reported of employees of large manufacturers setting up "black market" operations for private gain through what is called "back door selling". This is particularly so where there is a shortage of popular components. Unfortunately "industrial diseases" like this tend to spread, and the UK which is dependent to some extent on imported devices has become infected.

Another trouble arises when devices classified as "sub-standard" leave the factory back door as scrap but get recycled or remarked with specified type numbers and turn up classified as "good". Worse still, such devices can get mixed up with genuine standard stock. How such operations work is not too clear but such stocks can find their way into almost any outlet, be it a large equipment manufacturer or a small high street shop. The ethics of this kind of operation are very clear; the victims, however, are usually completely oblivious unless full acceptance testing is carried out.

Discrete transistors are nominally classified within wide gain spreads which can conceal such subtle features as noisy operation or relatively high leakage currents. We have even heard of cases where a device is electrically satisfactory but two of the lead-out connections are transposed, contrary to the published data sheets.

Integrated circuits have been known to have open-circuit terminals or intermittent internal connections.

It is unfortunately almost impossible to locate or prove dubious operations. The best advice to all purchasers is: buy through reliable organisations with well established reputations; know where your components come from; make sure you have proper protection options in Law in the event of faulty goods; know whether you are buying from a recognised franchised distributor (such as a member of AFDEC), a retailer or direct from the manufacturers; above all test transistors and i.c.s *before* fitting them into your equipment.

M. A. COLWELL—*Editor*

THIS MONTH

Teletopics	54
Adding IF Amplification <i>by Keith Cummins</i>	56
Renovating the Rentals—Part 18—Philips G6 Colour Chassis, Decoder—1 <i>by Caleb Bradley, B.Sc.</i>	59
Video Mixer <i>by M. J. Hughes, M.A.</i>	64
Colour Brightness Control—Part 1 <i>by S. George</i>	68
Servicing Television Receivers—GEC Series One Chassis <i>by L. Lawry-Johns</i>	71
Receiver System for Long-Distance Reception <i>by Roger Bunney</i>	74
Letters	77
The TELEVISION Colour Receiver Forum	78
Service Notebook <i>by G. R. Wilding</i>	84
Long-Distance Television <i>by Roger Bunney</i>	86
Your Problems Solved	89
Test Case 132	91

THE NEXT ISSUE DATED JANUARY
WILL BE PUBLISHED DECEMBER 17

Corrections: Our apologies for the omission of (f) in the caption to Fig. 3, page 21, last month. The waveforms shown in (f) are the burst output at pin 7 of the TBA560 (top) and the burst input at pin 5 of the TBA540 (bottom).

Alan C. Ainslie's name was accidentally omitted from the heading to his article on page 12 last month.

There were some signal path indication errors (i.e. arrowheads wrong or missing) in the block diagram included with our *Basic Colour Faults Guide* in the October issue. An *output* goes from the reference oscillator to the phase discriminator; the chroma amplifier output goes to the chroma delay line and to the add and subtract summing networks.

TELETOPICS



MINIATURE SOLID-STATE TV CAMERAS

It looks as if the time when miniature all solid-state TV cameras will be readily available for a wide variety of applications including home use is fast approaching. A couple of months ago we mentioned Fairchild's introduction of a 500-element solid-state charge-coupled device (c.c.d.) for image sensing. Fairchild have now announced the development of a low-resolution TV camera using a 10,000-element c.c.d. array to convert the scene into a corresponding video signal. The camera, Model MV100, is the size of a cigarette pack and weighs only six ounces. It is said to be the forerunner of a new range of colour and monochrome cameras using c.c.d. arrays to be announced "over the next few years". The camera can operate under lighting conditions ranging from bright sunlight to subdued room lighting. TV receivers require slight modification for use with it though no alteration is required to a videotape recorder. Suggested applications include security surveillance, instruction and industrial process control.

The potential market for such cameras is obviously very considerable and a number of firms are at work developing solid-state sensing arrays and complete cameras. Announcements about successful development work in this field have come recently from Bell, RCA and GE of Australia. Whoever comes up first with a reliable high-resolution camera will be on to a good thing indeed.

The latest news from RCA is of their development of a 120,000-element c.c.d. image sensor, the largest announced to date and claimed by RCA as "a key milestone in the creation of a new generation of tubeless TV cameras for government, commercial and consumer use". A demonstration of this device was given at the recent Electro-Optical Systems Design conference in New York. RCA are aiming to demonstrate shortly the feasibility of manufacturing a c.c.d. image sensor with a performance substantially equivalent to that of a two-thirds inch silicon vidicon tube. Half the elements in RCA's c.c.d. sensor form the imaging array, transforming the picture into individual charge packets which are then rapidly read out by charge transfer technique using the other half of the elements.

WHICH? ON COLOUR RECEIVERS

The Consumers' Association has reported again in their magazine *Which?* on colour receivers. Last time they did so they suggested that on balance provided a reasonable discount was given it was better to buy

than to rent a colour set. This time they report that the introduction of VAT has moved the advantage further in favour of purchase. *Which?* comments that now production has risen to meet demand customers should be more choosy about the set they obtain and the discount offered. Proper setting up and installation are emphasised, with the recommendation that final adjustments to a set should be made on a transmitted test card at the purchaser's home. Of the 16 sets tested the best buy given was the Philips Model 523 at about £200. This is fitted with the well known Philips G8 chassis.

Which? complains that the BS safety requirements are still not adequate. Half the sets tested were rejected because they were fitted with plastic rear covers which when set on fire burned fiercely, pieces of flaming plastic dropping on the floor. Another safety feature commented upon is the fact that it is too easy in spite of BS recommendations being followed to come into accidental contact with the chassis: narrow necklaces can for example pass through the ventilation holes in many colour set rear covers. The answer to this type of problem seems to be to cover the slots on the inside with nylon mesh.

It says something for the reliability of modern, single-standard colour chassis that outright purchase should be recommended and our only comment is that we are not so sure that the supply situation is as rosy as *Which?* suggests.

VIDEO RECORDING

A magnetic disc video record/playback system that operates using a conventional turntable is under development by Bogen (Berlin). Approximately half the disc consists of a spiral groove which guides an arm/stylus arrangement to which a magnetic head with an $0.01\mu\text{m}$ gap is linked. This head scans the other, magnetic half of the disc which is treated with chromium dioxide. So far a playing time of five minutes and a bandwidth of 2.5MHz have been achieved with this magnetic videodisc system, operating at 156 r.p.m. The present aim is to extend the playing time to twelve minutes and the bandwidth to 3MHz, with a speed of 78 r.p.m.

The TED videodisc playback system is now understood to be in production in W. Germany and is expected to be on the German market in January. Prices quoted are roughly equivalent to £165 for the player and £1.50-£4 each for the videodiscs. Plans are said to be under way to supply Scandinavian countries soon afterwards.

Philips hopes to have sold some 8,000 of their videocassette machines in the UK this year, out of a total expected European sales figure of some 75,000,

and anticipates a doubling of these figures the following year. Hitachi have now joined the already extensive list of companies who have entered into agreements with Philips to produce machines to their standard. Hitachi have previously concentrated on EVR players. Siemens are to join the ranks of those offering Philips type VCR machines in the UK.

Bell and Howell are introducing on the European market, including the UK, two videocassette machines designed and built by the Victor Company of Japan. They are the CP5000E cassette player and CR6000E recorder/player. Both machines are for colour and monochrome operation and use the self-contained U-type cassette containing $\frac{3}{4}$ in. tape developed jointly by JVC with Sony and National. The record/player machine will record off-air or from a camera. There are two sound channels.

STATION OPENINGS

Two new high-power u.h.f. transmitters have been brought into service by the IBA. **Llanddona** (Anglesey) transmits HTV Wales programmes on channel 60 (receiving aerial group C). **Rosemarkie** (N.E. Scotland) transmits Grampian programmes on channel 49 (receiving aerial group B). The transmissions from both stations are horizontally polarised. The following relay stations have been brought into operation.

Abergavenny (Monmouthshire) channel 49 carrying HTV Wales programmes (receiving aerial group B).

Bethesda (Caernarvonshire) channel 60 carrying HTV Wales programmes (receiving aerial group C).

Congleton (Cheshire) BBC-1 channel 51, BBC-2 channel 44 (receiving aerial group B).

Ebbw Vale (Monmouthshire) BBC-Wales channel 55, HTV Wales channel 59, BBC-2 channel 62 (receiving aerial group C).

Marlborough BBC-1 channel 22, BBC-2 channel 28 (receiving aerial group A).

Mynydd Bach (Monthmouthshire) channel 61 carrying HTV Wales programmes (receiving aerial group C).

Weymouth (Dorset) channel 43 carrying Westward programmes (receiving aerial group B).

All these relay transmissions are vertically polarised.



The JVC CR6000E videocassette recorder/player.

NEWS FROM THE TRADE

An 18in. colour receiver, Model 7018, has been added to the **Invicta** range. This is fitted with the Pye group's 713 chassis and a varicap tuner. The suggested price of £205.24 includes a £7 service allowance to the dealer. UK produced colour sets are to be sold under the new brand name **Concorde**. There will be 20, 22 and 26in. models fitted with a modular chassis and varicap tuners.

Bush have added a 12in. mains/battery portable, Model TV350, to their range. The suggested price is £62.95. RRI are to concentrate UK production of monochrome receivers at a new factory at Stoke, near Plymouth. Production of the Murphy Traveller 12in. mains/battery portable is due to start there shortly. Production at the new plant is expected to build up to 4,000 a month of which 2,500 will be portables. Thorn estimate that their production of TV sets this year will reach 745,000 colour and 620,000 monochrome receivers.

A new range of colour sets has been introduced by **Telefunken** who have just opened a new UK headquarters at Bath Road, Slough. Several of the models in this range are fitted with an audi-visual control for operation in conjunction with a videotape recorder. Top of the range Model 773 at £455 also features cordless supersonic remote control. A West German firm, Ebdö Elektronik Baulemente of Dortmund, is to set up a colour set production plant at Newcastle West near Limerick in the Republic of Ireland. The aim is to overcome the effect of currency fluctuations on their operations in the UK market.

ITT have announced that production of colour TV tubes at their Esslingen W. German plant is to be doubled and that within two years they expect to be producing the latest type with in-line guns and integral neckware (see TELEVISION, June 1973). The Central Applications Laboratory at Esslingen is developing circuits for use with the new tubes. It is understood that some sixteen of Europe's largest TV setmakers are at present producing sets to designs developed at Esslingen. Present tube output consists mainly of thick-neck 110° types, with smaller numbers of 90° and thin-neck 110° tubes also in production. Amongst the work in progress at the Central Applications Laboratory is the development of m.o.s. shift registers for use in TV sets, presumably to replace the ultrasonic glass delay lines at present used in colour receivers.

Sharp have introduced an 18in. colour set, Model C18-31H, at £259.95. This is said to include a new system giving improved colour definition but we have no details so far. A 12in. mains/battery portable, Model 3410UK, has been added to the JVC range. The new **Hitachi** 9in. portable Model 190 can be operated from the mains, a car battery or twelve rechargeable batteries which cost £8 extra. Japanese setmakers have announced that they are prepared to limit TV set exports to the UK during 1973/74 to 275,000 colour and 220,000 monochrome receivers but the UK industry is pressing for lower figures. It is estimated that Japanese colour set exports to the UK during 1972/73 reached 300,000.

RCA have announced that they have received a substantial order for the export of US produced colour sets to Taiwan. Could this be the turn of the tide in Western/Far Eastern electronic trading?

ADDITIONAL AMPLIFICATION

KEITH CUMMINS

A young colleague recently acquired an "old banger" 405-line TV set. The tuner was almost a total wreck and the overall performance was poor. In order to assist with this problem I suggested that we should carry out a tuner "transplant" from another receiver: we discovered a suitable set with a defective tube and substituted the tuner. The receiver then operated rather better: the tuner was at least reliable and selected channels correctly. The overall gain and sensitivity were still low however. Here came the crunch—the only obvious way to improve matters could involve multiple valve replacements and the whole business would then become totally uneconomic.

At this point I suggested that an additional i.f. amplifier stage would be helpful. Long faces were pulled at the prospect of mounting a valve on a bracket, winding i.f. coils etc. and an alternative approach was sought. When one considers the problem, it is helpful to realise that the i.f. connection between the tuner unit and the i.f. stages is made by coaxial cable at low impedance: if a current amplifying device with low-impedance input and output is connected between the tuner and i.f. strip additional gain will result.

A valve i.f. stage is unattractive from this point of view but the use of a transistor seemed very promising. Both the input and output impedances are low. They may not match the rest of the circuit exactly, but they are near enough to enable the transistor to be interposed between tuner and i.f. strip. While tuned circuits could be employed to improve the matching and gain, if simplicity is to remain the keynote the circuit should be reduced to the minimum number of components possible.

The circuit devised is shown in Fig. 1. It consists of one transistor, two resistors and two capacitors—a circuit "cut to the bone" so to speak. By feeding the collector of Tr1 from the h.t. line via a high-value resistor (R1, 100k Ω) the need for a separate power supply is eliminated. Forward base bias is provided from the collector via R2 and the transistor thus protected against h.t. The i.f. signal from the tuner is fed via C1 to Tr1 base and is taken to the i.f. strip from its collector via C2.

This simple circuit was found to provide a gain of around 12dB (assessed by calibrated attenuation at the aerial input). The overall performance was thus vastly improved and the "old banger" came very much to life, much to our amusement and delight. A few vertical bars were in evidence on the screen however. This proved to be line timebase ripple on the h.t. line reaching Tr1. A decoupling network connected between the h.t. rail and the transistor

cleared up the trouble—values of 10k Ω and 0.1 μ F are adequate.

The circuit was built up on a piece of tagstrip as shown in Fig. 2 and attached to the inside of the cabinet.

Many people bring TV receivers into this country from abroad unaware of the incompatibility between the standards used by the differing TV systems and on numerous occasions I have been asked to modify a 625-line v.h.f. only receiver (with 5.5MHz inter-carrier sound) to UK standards. In such cases it is first necessary to replace the v.h.f. tuner with a u.h.f. one: if the gain of the u.h.f. tuner is lower than that of the v.h.f. one removed it is essential to provide additional i.f. gain.

Sometimes a u.h.f. tuner of Japanese origin with a diode mixer is encountered. By replacing the diode by a transistor and arranging for this mixer to be the lower half of a cascode i.f. amplifier improved mixing and higher i.f. gain are achieved simultaneously.

A suitable circuit is shown in Fig. 3. The pickup loop in the tuner is the original one used to feed the diode mixer. A coaxial lead is used to connect Tr1 collector to the emitter of Tr2 which operates as the grounded-base half of the cascode pair.

A tuned circuit is used in this case, to enable maximum energy transfer to take place from Tr2 collector to the main i.f. strip. A certain amount of experimenting is necessary with L1 and L2. Too loose a coupling will result in instability, while too tight coupling results in loss of gain. L1 usually works out at about 15 turns wound on a $\frac{1}{4}$ in. former fitted with a dust-iron core. L2 is three turns wound on the earthy end of L1.

Since this article deals with i.f. amplification I will not pursue other details concerning TV conversions at this stage: these will form the basis of an article to follow later. ■

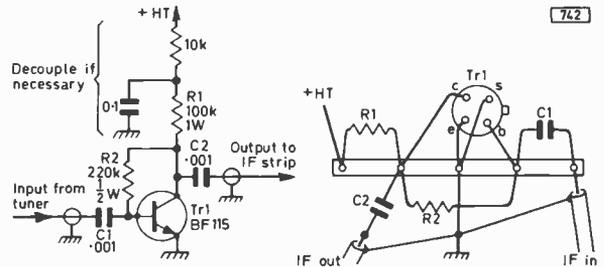


Fig. 1 (left): Simple untuned transistor i.f. stage.

Fig. 2 (right): Layout on a five-way tagstrip.

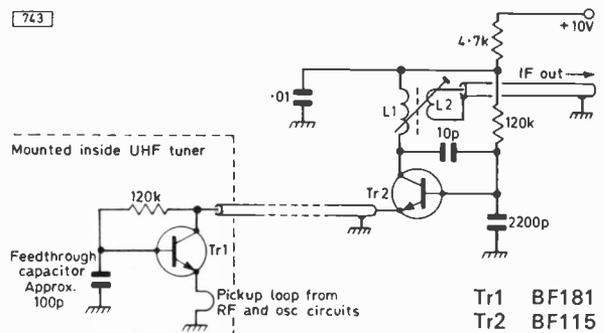


Fig. 3: Cascode mixer-amplifier circuit.



LEARN about MODERN TV Design by building this Heathkit 12" B/W Portable

The new Heathkit GR-9900 portable 12" UHF Monochrome Television kit. A unique chance to double the pleasure available from any other television set — because you build this yourself.

We've used the latest modular construction and advanced design concepts to produce an outstandingly high performance TV worthy of the Heathkit name. All the main electronics are mounted on two easy-to-assemble printed circuit boards—this plus the use of no less than four integrated circuits perform the complex function of IF, video, sound, line frame and scan. Factory pre-aligned coils make alignment very easy and there are four presettable pushbutton controls for channel tuning—a luxury found in very few other models. The quality and fidelity is therefore excellent, and of a far higher standard than most ready-built televisions in the shops.

The GR-9900 is portable too—equally at home on

the mains or off your 12 volt battery for car, boat or caravan use. Add to this Heath's world renowned experience in the design of equipment for first-time kit builders, and you will be impressed on all counts of engineering, styling, and performance.

The instruction manual is surprisingly simple with big, clear illustrations to map out your way. Would-be TV engineer? Here's your chance to learn—by actually building a television yourself. The manual not only shows you how to get 100% personalised quality control on your own; in the event of anything going wrong, a Trouble-Shooting section enables you to find the fault—and, in most cases, to put it right unaided.

The GR-9900 is a kit you'll be proud to build and own. You have a choice of fully finished cabinets in teak or modern white and the kit price, £62.70 (carriage extra), includes a FREE high performance indoor aerial.

FREE Heathkit Catalogue

Contains something for everyone: Hi-Fi Stereo, Testers & Instruments, SWL, Metal Detectors... even a Battery charger Kit. Mail the coupon... Today! Heath (Gloucester) Limited, Gloucester GL2 6EE.

LONDON showroom
233 Tottenham Court Road
Tel 636 7349



Choose cash or Heath Monthly Budget Plan

(Mail order prices and specifications subject to change without notice)

Please send me a FREE Heathkit catalogue

Name _____

Address _____

HEATH

Schlumberger

Heath (Gloucester) Limited, Dept T.12.73
Gloucester GL2 6EE. Telephone 0452 29451

COLOUR TUBES STANDARD TUBES

METAL BAND TUBES

TWIN PANEL TUBES

Rebuilt with new Electron
Guns to British Standard
415/1/1967.

SUFFOLK TUBES LIMITED

261 CHURCH ROAD
MITCHAM, SURREY GR4 3BH
01-640 3133/4/5

Britain's Largest Independent
TV Tube Rebuilder

REBUILT COLOUR TUBES

19"	£22.50	22"	£25.00
25"	£27.00	26"	£28.00

Exchange prices: Tubes
supplied without exchange
glass at extra cost, subject
to availability.

Colour Tubes demonstrated
to callers.

Carriage extra
all types.

Full range of rebuilt mono
tubes available, Standard,
Rimband and Twin Panel

- ★ Complete new gun fitted to every tube.
- ★ 2 years' guarantee mono-chrome, 1 year colour.
- ★ 16 years' experience in tube rebuilding.
- ★ Trade enquiries welcomed.

N.G.T. ELECTRONICS LTD.
(Nu Gun Teletubes)

22-24, Anerley Station Road,
London S.E.20.

Telephone: 01-778 9178.

TELEVISION TUBE SHOP

BRAND NEW TUBES AT
REDUCED PRICES

A31-18W	£12.50
A47-11W	£9.95
A47-13W	£12.50
A47-14W	£8.25
A47-26W	£10.75
A50-120WR	£12.50
A59-11W	£12.95
A-59-13W	£13.50*
A59-15W	£9.95
A59-23W	£14.75
A61-120WR	£16.50
AW43-80	£6.95
AW43-88, 43-89	£6.75
AW47-90, 47-91	£7.50
AW53-80	£7.50*
AW53-88, 53-89	£8.25
AW59-90, 59-91	£9.00
CME1201	£12.50
CME1601	£10.50
CME1602	£12.00
CME1705	£7.75
CME1713/A44-120	£14.50
CME1901, 1903	£7.50
CME1906	£12.50
CME1908	£7.75
CME2013	£12.50
CME2101, 2104	£8.25
CME2301, 2302, 2303	£9.00
CME2305	£14.75
CME2306	£13.50*
CME2308	£9.95
CME2413R	£16.50
MW43-80	£6.75
MW53-20, 53-80	£7.50
TSD217, TSD282	£14.00†
13BP4 (Crystal 13)	£14.00†
190AB4	£9.25
230DB4	£11.25

* These types are fully rebuilt.

† Rebuilt tubes also, at £7.00 plus
carriage and old bulb.

COLOUR TUBES NEW R/B

	£	£
19" Unprotected	25	-
A49-120X	45	-
A56-120X	72	48
A61-15X	78	52
A63-11X	-	52
A66-120X	82	55
A67-120X	85	-

SHOP-SOILED COLOUR TUBES

19", 22" & 26" NOW AVAILABLE
Brand new, with slight scratches.
Prices from £20. Callers only.
Add Carriage and Insurance: Mono-
chrome 75p, Colour £1.50.

ALL PRICES SUBJECT TO V.A.T.

TELEVISION TUBE SHOP

48 BATTERSEA BRIDGE ROAD,
LONDON, S.W.11. BAT 6859
WE GIVE GREEN SHIELD STAMPS

color TV

NEW TRADE & RETAIL
WAREHOUSE NOW OPEN IN
BIRMINGHAM, easy access, callers
welcome

Bush CTV25 — CTV167, PYE CT70,
THORN 2000, DECCA CTV19—25,
PHILIPS G6 etc. etc. as available.
Some non-working sets from £25 as available.
ALL with repolished cabinets.

MONO
BBC 2 TV's WORKING — £10
BBC 2 Non-working — £8
VHF Working — £3
Carr. £2.50 per set. Add VAT to total price.

G.E.C. COLOR DECODER PANELS
NEW appearance, 11" x 5 1/2" approx. Grade
B Complete untested. £4.50+25p p & p.
Grade C. Some physical damage but com-
plete with DL 20 £3.00 + 25p p & p (2 for
£6 post paid)

XTALS — 4.43MHz 40p carr. paid
DL20 COLOR-DELAY LINE
£2.50 carr. paid (both ex-equip.)

UHF TRANSISTOR Tuners
New, untested £5 + 25p carr.

TV STANDS £3.25
Specially made to your order.
(Regret we can no longer arrange delivery
—callers only.)

SUMIKS

Please note our new address:
1532 Pershore Road,
Stirchley, BIRMINGHAM, 30
(Main A441 from city centre,
Look for the 'COLORCARE' sign)

DISCOUNT COLOUR!

Perfect working order. Repolished
cabinets. 30 DAY GUARANTEE!

19" DECCA £77
19" GEC £88
22" PHILIPS/DECCA £132
26" DECCA/BUSH/GEC
BRC 2000/PYE £110

CASH and COLLECT PRICES,
VAT included.

3 or over less 10% discount.

Brand New 26" Colour TV Cabinets
Slight seconds without backs. All with
doors in Dark Teak. Delivered for £10 cwo

Mono UHF TV's
Sold complete but unserviced with
tube tested. Good cabinets, Valve tuner
type inc.:-

BUSH 128, SOBELL 1000, GEC 2000,
THORN 900. Singles £5 each (add £2
delivery. 6 for £25). Delivery extra.

Transistorised tuner type makes inc.:-
THORN 950, BUSH 141, GEC 2010 to
2038. Philips style 70. Singles £10
each (add £2 delivery. 6 for £50).
Delivery extra.

UHF Tuners ex. T.V. tested
Pye 11U type. Sobell 1000
Thorn 850/900. Adaptable to most makes
Send £2.50 cwo.

Send SAE for list of UHF tuners, valves,
tubes, washing machines etc.
Open 6 days every week.

TRADE DISPOSALS
1043 Leeds Road, Bradford 3.
Tel Bradford (0274) 668670
and

Peacock Cross Industrial Estate,
Burnbank Road, Hamilton,
Tel Hamilton (04882) 29811

RENOVATING the RENTALS

18 PHILIPS G6 CHASSIS

CALEB BRADLEY B Sc

DECODER—1

THE PAL decoder used in the Philips G6 chassis is almost entirely valved and is one of the most elaborate decoders ever mass-produced. In spite of this it is fairly reliable, although some very peculiar faults are possible.

The circuit of the decoder is shown in Fig. 9: it bristles with unusual features. Chroma from the i.f. panel is initially amplified by V7001, a familiar gain-controlled vari- μ valve (EF183). The first unusual feature is the chroma noise clipper circuit connected across this valve's anode load L7506. The v.d.r. R7145 provides a stabilised 5V across C7022/3; if a noise pulse exceeds this amplitude X7315 conducts and the excess voltage is shunted to chassis by C7021. Chroma noise clippers are not usually found in solid-state designs where the lower h.t. supply automatically limits the signal swing.

Amplified chroma is coupled by C7026 to the second chroma amplifier V7002, and via L7508/9 to the gated burst amplifier. V7002 is a straight EF184 pentode. The reference burst is removed from the chroma (to prevent a vertical strip of colour on the screen) by a line pulse which causes X7318 to conduct and shunt the tuned anode load L7517/C7516. Chroma is coupled by L7518 to the usual one-line (64 μ sec) delay line/matrix circuit where direct and delayed chroma signals are summed to feed the B-Y preamplifier T7011 and differenced to feed the R-Y preamplifier T7012 via the PAL switch which in this chassis works on the R-Y chroma instead of the reference signal feed to the R-Y demodulator. The 4.43MHz tuned circuit L7513/C7514 can be detuned slightly to modify the delay; it should be adjusted together with R7159 (matrix balance) to eliminate Hanover blinds on a colour-bar pattern.

The B-Y and R-Y preamplifiers are similar except that the R-Y one has high-pass input filtering (L7524) to remove any half line frequency content introduced by the PAL switch, and a gain control R7173. The two preamplified chroma signals are then fed into a dual demodulator assembly in one can. Here the reference signal (4.43MHz) is received on pin 1 from the crystal oscillator. At this point the reference signal has the same phase as the B-Y chroma signal component. A 90° phase shift is introduced by L7559/60/C7534 so that correctly phased 4.43MHz reference signal is applied to X7570/1 to demodulate R-Y. A further 90° shift is provided by L7562/3/C7535 so that the 4.43MHz reference signal once again on the B-Y axis is applied to X7568/9 to demodulate B-Y.

The Burst Channel

The reference burst signal needed for phase control of the reference oscillator is extracted from the

chroma signal at L7508 by means of a gate pulse fed through L7509 to V7008. The burst gate pulse is derived from a 160V line pulse as follows. On the main positive part of the pulse X7316 blocks but on the negative backswing it conducts and tuned circuit L7574/C7043 is excited. The tuned circuit rings to provide a positive-going pulse which passes via C7045, R7189, L7509 and R7255 to turn on V7008 simultaneously with the burst. The gate pulse is clamped at approximately 0V by X7317 to avoid overdriving V7008. The viewer colour saturation control varies the d.c. conditions of the burst amplifier V7008 and hence its gain: since the automatic chrominance control (a.c.c.) potential is derived from the amplified burst this indirectly controls the chroma gain.

Passing over the a.c.c. arrangements for the moment, the amplified burst is coupled by tuned transformer L7624-6 to the usual burst demodulator (phase discriminator) where the output of the crystal reference oscillator (V7009), shifted to the R-Y axis by L7627/C7608, is compared with the burst phase. The error voltage appearing at R7618 slider is smoothed by C7101/2 and used to control the oscillator via the reactance triode V7009a. The oscillator circuit uses a PCF802 valve, better known for its use in timebase oscillators, oscillation being sustained by feedback between the control and screen grids of the pentode section at the crystal frequency. Capacitive anode-grid feedback via C7103 around the triode section makes it appear as a reactance loading one end of the crystal; its reactance is varied by the phase error voltage applied to its grid.


PAL Switch

The ident amplifier and PAL bistable circuits at least hold few surprises. The half line frequency (7.8kHz) component (burst ripple) of the unsmoothed phase error voltage, caused by the $\pm 45^\circ$ alternations of successive bursts about the R-Y axis, is extracted by C7092, amplified by the tuned stage T7015 and applied by C7095 to the PAL bistable to phase correct it if necessary. The bistable is reversed ("toggled") by line pulses coupled to the bases of T7013-4. The opposite-polarity squarewaves at T7013-4 collectors alternately switch on X7320 and X7321 thereby operating the R-Y signal reversing switch. Extensive choke and capacitive smoothing is used to prevent switching transients entering the R-Y signal.

Automatic Chrominance Control

Since the chroma amplitude can vary greatly with such things as channel changing, tuning drift or aircraft flutter some form of chroma a.g.c. (i.e. a.c.c.)

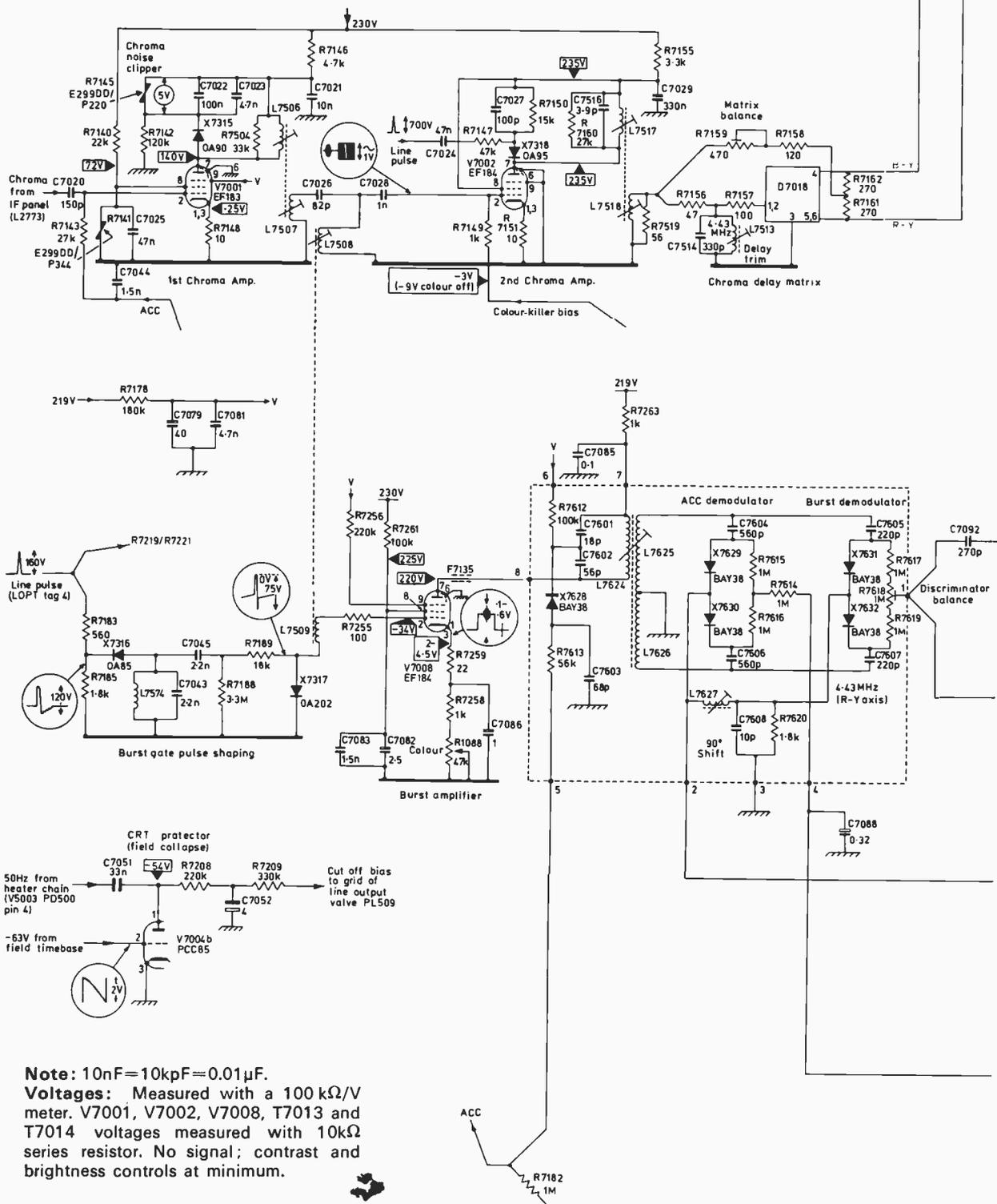Modifications: V7004 removed, an OA91 diode being fitted in place with its anode to the junction R7196/R7199 and cathode to chassis. The secondary side of the reference oscillator output circuit was rearranged, also the h.t. switch connections may differ. With a later delay line the component values in the matrix circuit differ.



Note: 10nF=10k μ F=0.01 μ F.
Voltages: Measured with a 100 k Ω /V meter. V7001, V7002, V7008, T7013 and T7014 voltages measured with 10k Ω series resistor. No signal; contrast and brightness controls at minimum.

Fig. 9: Circuit of the decoder used in the Philips

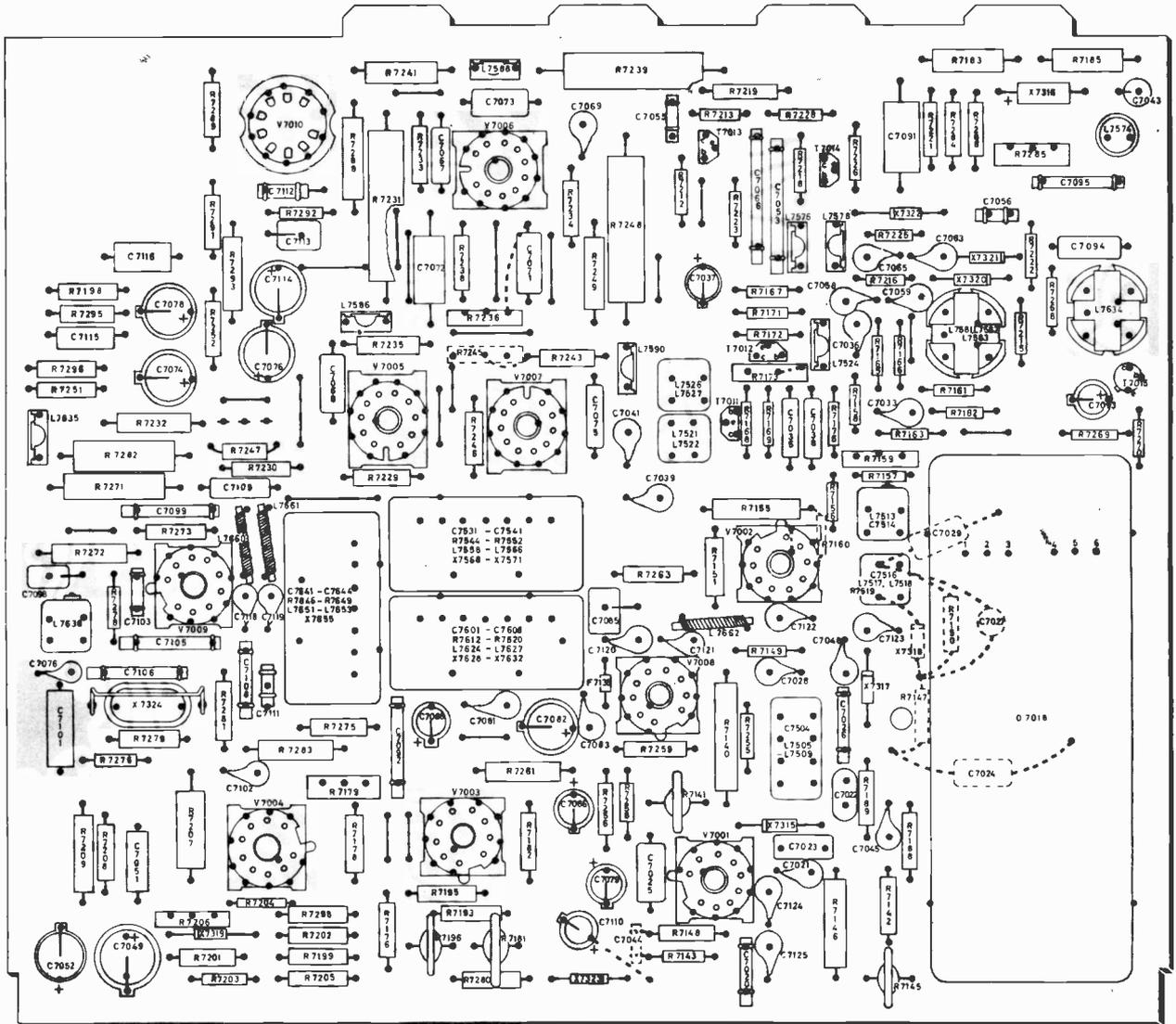


Fig. 10: Layout of the decoder panel. The author advises cutting out R7209 (if present) at lower left. On some panels the sound output transformer is mounted above left. Corrections: C7504 should read R7504 and L7505, L7506 (can with L7509); C7076 should read C7096 (left-hand side beneath L7638).


should be provided to keep the colour saturation constant. The usual method of obtaining a control voltage proportional to the chroma signal strength is by simple envelope detection of the burst and this is done by X7628 which rectifies part of the amplified burst tapped off C7601/2. The smoothed negative-going voltage across C7603 is fed back via R7613 and R7143 to control the gain of the first chroma amplifier V7001. This is only part of the a.c.c. arrangement however; there is also a special synchronous a.c.c. demodulator which gives more accurate control.

This is similar to the burst demodulator except that the diode junction (X7629/30) is supplied with reference oscillations on the B-Y axis. Provided the oscillator is locked to the burst this will result in the same amplitude output on each burst, proportional to the burst (chroma) amplitude. These positive pulses are smoothed to a d.c. level by C7088

and tend to turn on the a.c.c. amplifier V7003a. The anode voltage is shifted negatively about 45V by the v.d.r. R7181 to provide a second negative-going chroma a.c.c. supply which is fed by R7182 and R7143 to V7001. The interesting feature of this dual a.c.c. arrangement is that when a colour transmission is first tuned in and the oscillator is not yet locked the phase-dependent a.c.c. demodulator does not produce an output and the resulting high gain of V7001 helps to establish reference oscillator a.p.c. loop lock. Once the oscillator is in lock the chroma gain depends so closely on the burst amplitude from V7008 that R1088 provides effective saturation control.

Colour Killer

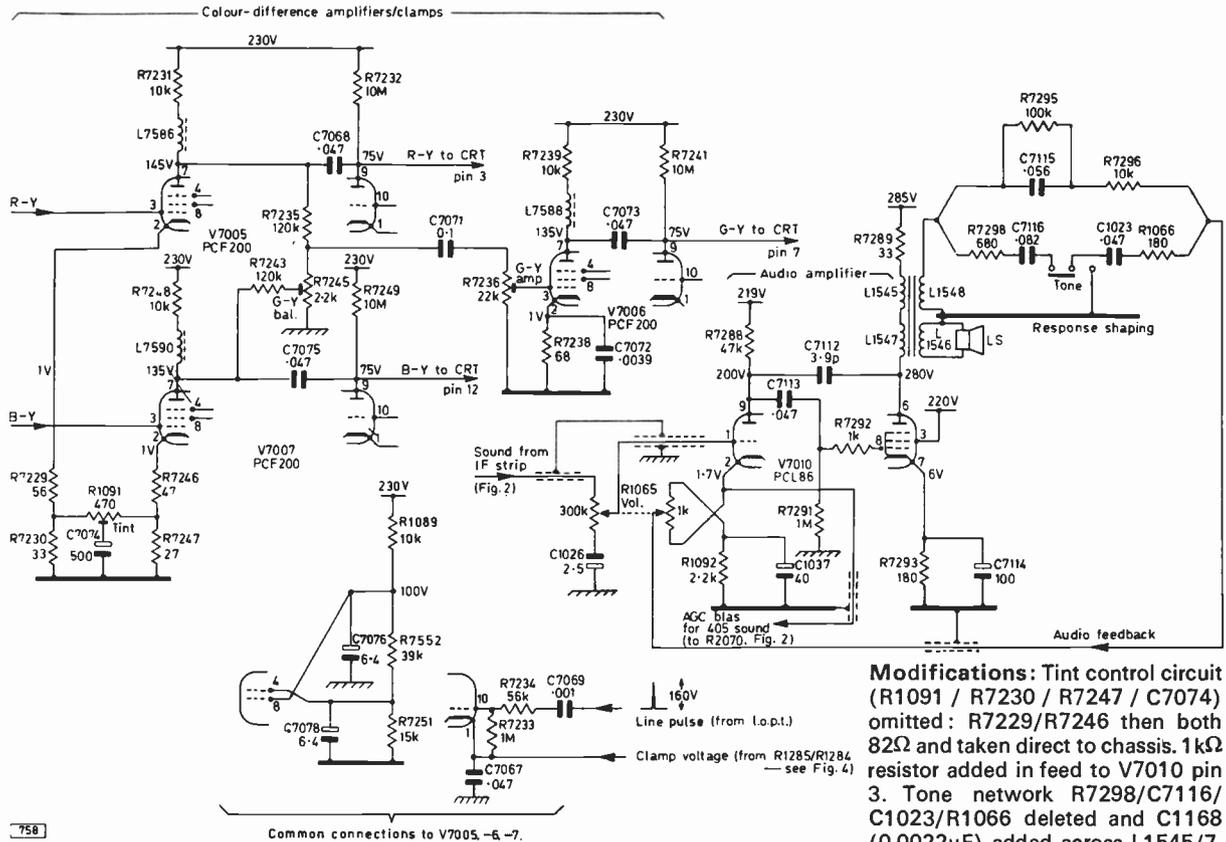This stage (V7003b) is similar to the a.c.c. amplifier but acts as a switch. If chroma is present the few



Modifications: Tint control circuit (R1091 / R7230 / R7247 / C7074) omitted: R7229/R7246 then both 82Ω and taken direct to chassis. 1kΩ resistor added in feed to V7010 pin 3. Tone network R7298/C7116/C1023/R1066 deleted and C1168 (0.0022μF) added across L1545/7.

Fig. 11: The colour-difference amplifiers and the audio channel.

volts negative at V7003b grid hold it cut off and approximately 0V "colour killer bias" is fed to the second chroma amplifier V7002 allowing it to function. If chroma is absent however so that V7003b conducts, or if the colour on-off button is depressed, about -12V bias is fed to V7002 cutting it off. Although the colour killer merely switches the colour killer bias, the bias line is also used for gain control of V7002 during colour reception by means of X7319 which provides tracking between the contrast control and colour saturation, i.e. saturation is automatically reduced as contrast is reduced, the amount of interdependence being set by R7206. If R7206 has no effect X7319 is probably open-circuit.

The colour/monochrome relay fitted in early sets has been described; it is energised by V7004a being biased on during colour reception.

Colour-Difference Amplifiers

The colour-difference amplifiers and clamps shown in Fig. 11 are conventional although it is unusual for the G-Y matrix network (which derives this signal by summing weighted amounts of the demodulated R-Y and B-Y signals) to be adjustable. R7245 and R7236 can be easily set up viewing a colour-bar pattern.

Audio Circuit

The audio amplifier has its own sophistication: a "loudness" control instead of a simple volume control. This is intended to give increased bass content as

the volume setting is reduced, to give a more "natural" effect. The frequency response modification is performed by the 1kΩ potentiometer which is ganged to the main 300kΩ volume control: it injects a negative feedback signal from the response shaping network into the cathode of the triode stage. At minimum volume setting the 1kΩ potentiometer slider is at the cathode end of the track for maximum tone correction. There is a push-button manual tone control also, in the feedback circuit.

For 405 sound (a.m.) only, the d.c. component from the detector is passed through the triode stage which acts as a cathode-follower to this signal and is returned to the first sound i.f. transistor to provide a.g.c.

CRT Protection

The c.r.t. protector stage (V7004b) is normally held cut off by a negative potential generated in the field timebase and in these conditions has no function. The idea is that if the field timebase should fail V7004b will conduct and rectify the a.c. at its anode to produce on C7052 a very strong negative voltage which will disable the line output stage and hence the e.h.t. supply to prevent a horizontal line being burnt into the tube face. This stage has little use however and can be misleading to the uninitiated. It is quite in order therefore to disable it permanently by cutting out R7209.

NEXT MONTH: FAULTS AND SETTING UP

VIDEO MIXER

M J HUGHES MA



THIS unit is designed for use with any standard video system in which the cameras are synchronised and there is a composite video signal available from at least one camera. The mixer provides fades, dissolves, switch cuts and superimposition and has the possibility of adding an effects unit to permit electronic wipes and split-screen operation.

No dramatic claims are made for the bandwidth of the unit but the insertion loss is negligible compared with the bandwidth limitations of most medium priced video recorders. The circuit has been designed for simplicity of construction and uses no inductors. High-frequency response is maintained by operating throughout at low impedances—a glance at the circuit (Fig. 1) reveals the extensive use of emitter-follower stages. The layout is not critical and although a d.c. oscilloscope is very useful for the initial setting of the preset controls these can be adjusted quite successfully by viewing the final picture on the normal monitor.

The prototype was used in conjunction with a Crofton Educational Camera, an Ikegami VF302 viewfinder camera and a Shibaden SV610 videotape recorder. As standard 1V composite video signals from a 75Ω source are required there is no reason why other camera/VTR configurations should not

be used. Also, although it has been used in only a two-camera system to date there is no reason why it should not be extended to three or more cameras—this point is referred to in the description that follows.

Inputs


The video inputs enter the unit via multipin camera connectors which also carry mains and synchronisation lines. There was no need for provision to monitor the individual camera outputs before mixing in the prototype set-up but monitor points could be provided by looping into the input signal points—R8 and R15 ought then to be switched out and the monitors terminated in 75Ω. A single mixed output is available capable of driving a chain of monitors—again the last in the chain being terminated at 75Ω—or a VTR which would probably have its own monitor output.

Video Stripper

One camera signal *must* be composite, i.e. video plus sync pulses. This input is designated "1" in the circuit diagram. Tr1 and Tr2 act as a "video stripper"—effectively removing all video signals but leaving the sync pulses. Tr1 is biased *just* into conduction: thus positive-going video will not appear at its collector although the negative-going sync pulses will appear as quite a high-level inverted signal which is reinverted and its rise time sharpened by the direct-coupled grounded-emitter stage Tr2. In the absence of D2 and D3 the sync pulses would comprise a 12V negative-going signal at Tr2 collector: they are clipped however by the diodes, giving clean sync pulses with a black level of +1.2V—the amplitude being between +1.2V and ground.

Sync Strippers

Input "1" is also applied to the "sync stripper" circuit comprising Tr3 and Tr4. This circuit effectively removes the negative-going sync pulses but leaves the video signal untouched. Tr3 is an emitter-follower with its base biased at 0.6V: thus all the positive-going video appears across its emitter load VR1. The latter acts as the level control for that channel. The output of channel "1" can be blanked by SW1 which simply grounds the video signal at

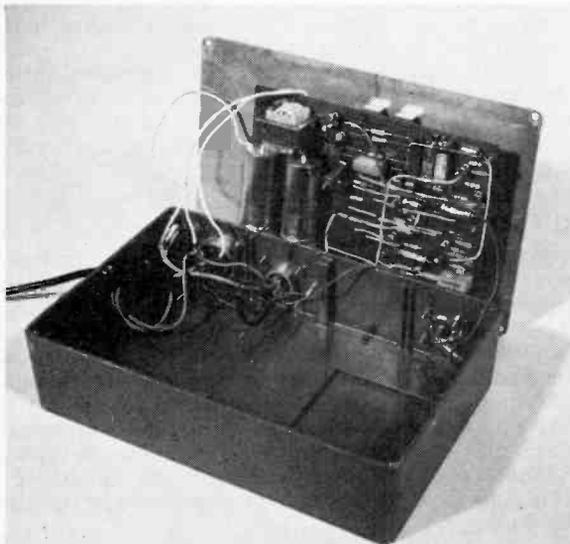

View of the mixer with the top cover removed.

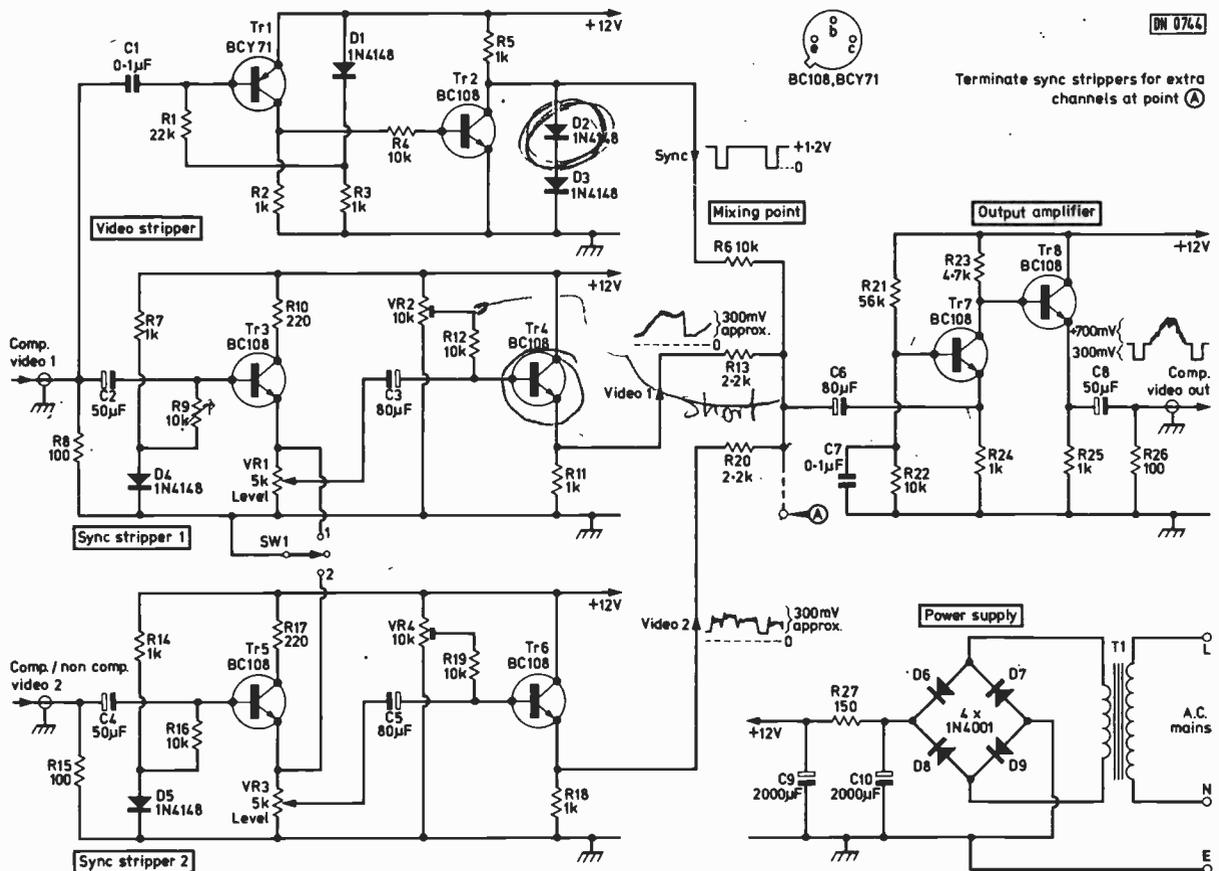


Fig. 1: Circuit diagram of the video mixer—two-channel version.

that point (R10 is included to limit the transistor's collector current).

Tr3 emitter could be coupled through suitable diode gating to an effects monostable operating from a negative rail and triggered by the sync pulses: this would permit alternate switching between channels in order to give wipes and split-screen operation (this has not yet been done with the prototype but is mentioned as a useful idea for those wishing to take the circuit a stage further).

The required video level—set by VR1—is a.c. coupled to emitter-follower Tr4 whose output is biased by VR2 (preset) to +1.2V. Any positive-going video is thus placed on a 1.2V pedestal.

Tr5 and Tr6 form an identical sync stripper for the second channel, the input of which can be either of composite or non-composite form.

Mixing

The outputs of the two sync strippers (the video signals in their desired proportions) and the sync pulses from the video stripper are combined at the mixing point A through resistive arms and then pass to a grounded-base amplifier (Tr7). There is a certain amount of level loss due to the signal processing and the amplifier is designed to compensate for this. The sync needs attenuation by a factor of about two while in the prototype it was found that a gain of two was required for the two video signals. The values of R6, R13 and R20 are selected to give

the correct gain and mixing in the correct proportions. The level of each signal can be increased by reducing the value of its respective mixing resistor and vice versa. No problems should be expected in this respect: it is suggested that the values shown are used and altered only if problems arise.

The grounded-base stage Tr7 is terminated into

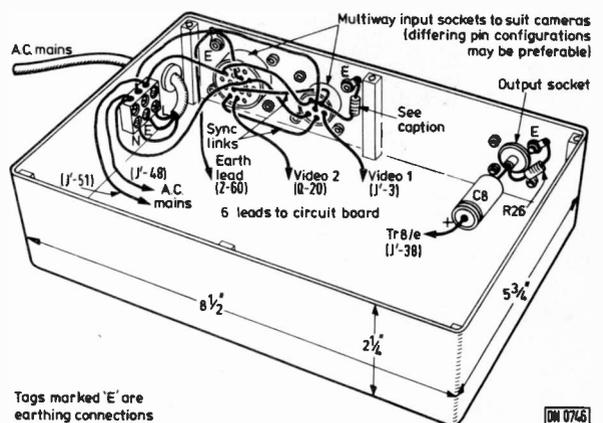


Fig. 2: Wiring to the case. The board and the controls are mounted on the lid of the diecast box. The resistor (say 100Ω) shown terminating the sync link at the camera 1 socket may be necessary to match sync lines.

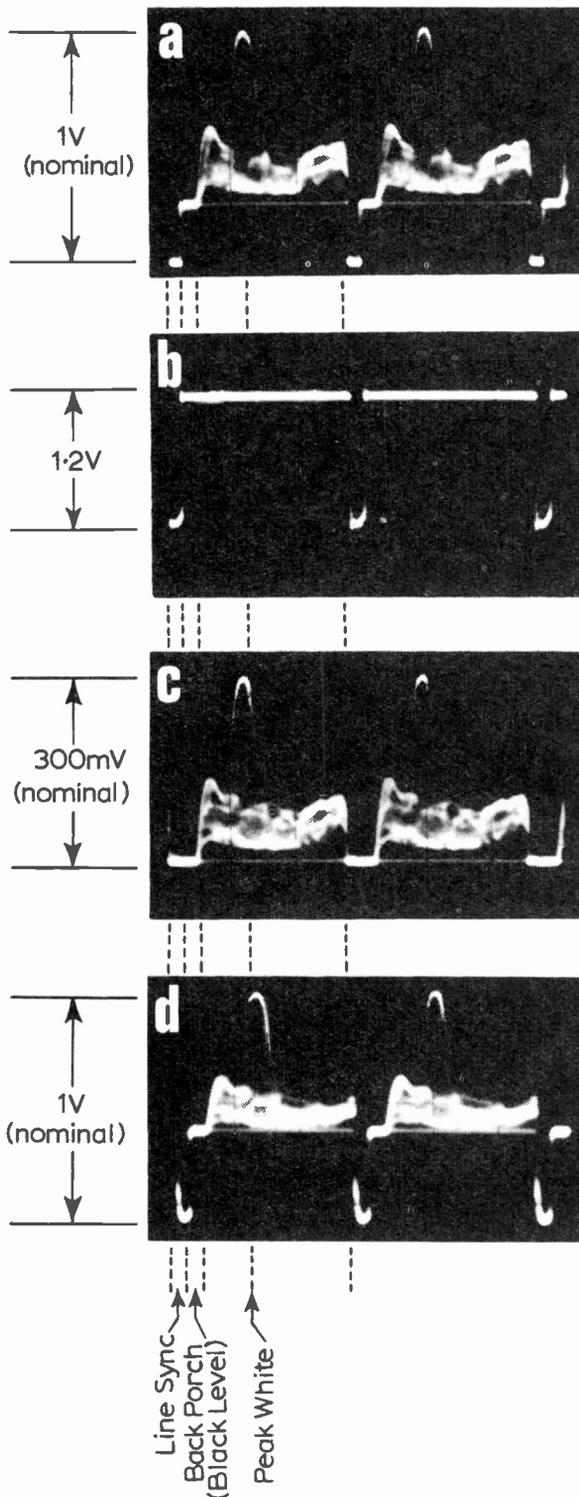


Fig. 3 (left): Waveforms. (a) Input from camera (250mV/cm vertical deflection). (b) Sync pulses at Tr2 collector, extracted from the composite input signal (500mV/cm vertical deflection). (c) Video signal at Tr4 emitter, with sync pulses removed (500mV/cm vertical deflection). (d) Mixed and processed video signal recombined at the mixer output (junction C8/R26) with the sync pulses (250mV/cm vertical deflection). The video and sync ratios are controlled by the values of R6, R12 and R20.

from a simple unstabilised supply—it is only necessary to ensure that all ripple is removed with adequate smoothing.

Operation

Switch cuts can be effected quite simply by means of SW1 (toggle, rotary or pushbutton types will suffice). The advantage of this circuit is that normal break-before-make switches can be used without causing momentary screen blanking. During the switch over both video signals appear on the screen for a fraction of a second.

For switched cuts set both faders at high and move the switch quickly from one camera position to the other. For cross fades or dissolves set the

★ components list

Resistors:

R1	22k Ω	R15	100 Ω
R2	1k Ω	R16	10k Ω
R3	1k Ω	R17	220 Ω
R4	10k Ω	R18	1k Ω
R5	1k Ω	R19	10k Ω
R6	10k Ω *	R20	2.2k Ω *
R7	1k Ω	R21	56k Ω
R8	100 Ω	R22	10k Ω
R9	10k Ω	R23	4.7k Ω
R10	220 Ω	R24	1k Ω
R11	1k Ω	R25	1k Ω
R12	10k Ω	R26	100 Ω
R13	2.2k Ω *	R27	150 Ω 1W
R14	1k Ω		* See text

All $\frac{1}{4}$ W 10% unless otherwise indicated.

VR1, VR3, 5k Ω lin. (slider or rotary)

VR2, VR4 10k Ω rectilinear presets (normal rotary presets will do with appropriate layout change).

Capacitors:

C1	0.1 μ F	C7	0.1 μ F
C2	50 μ F 12V	C8	50 μ F 12V
C3	80 μ F 12V	C9	2,000 μ F 20V
C4	50 μ F 12V	C10	2,000 μ F 20V
C5	80 μ F 12V	C1, C7	polyester
C6	80 μ F 12V		

Semiconductors

Tr1	BCY71	D1-5	1N4148
Tr2-8	BC108	D6-9	1N4001*

* or encapsulated bridge, 20V 500mA minimum rating

Miscellaneous

SW1 Single-pole; 3-way. Preferably toggle with centre neutral or three-section push-button bank.

T1 240V primary, 12V r.m.s. 100mA secondary.

Multitway sockets to suit equipment interfaces.

an emitter-follower (Tr8) to provide a low output impedance for the mixed composite signal.

It should be possible to add extra sync strippers to the circuit, coupling them into point A through suitable mixing resistors, if mixing between more than two channels is required.

There should be no problems in powering the unit

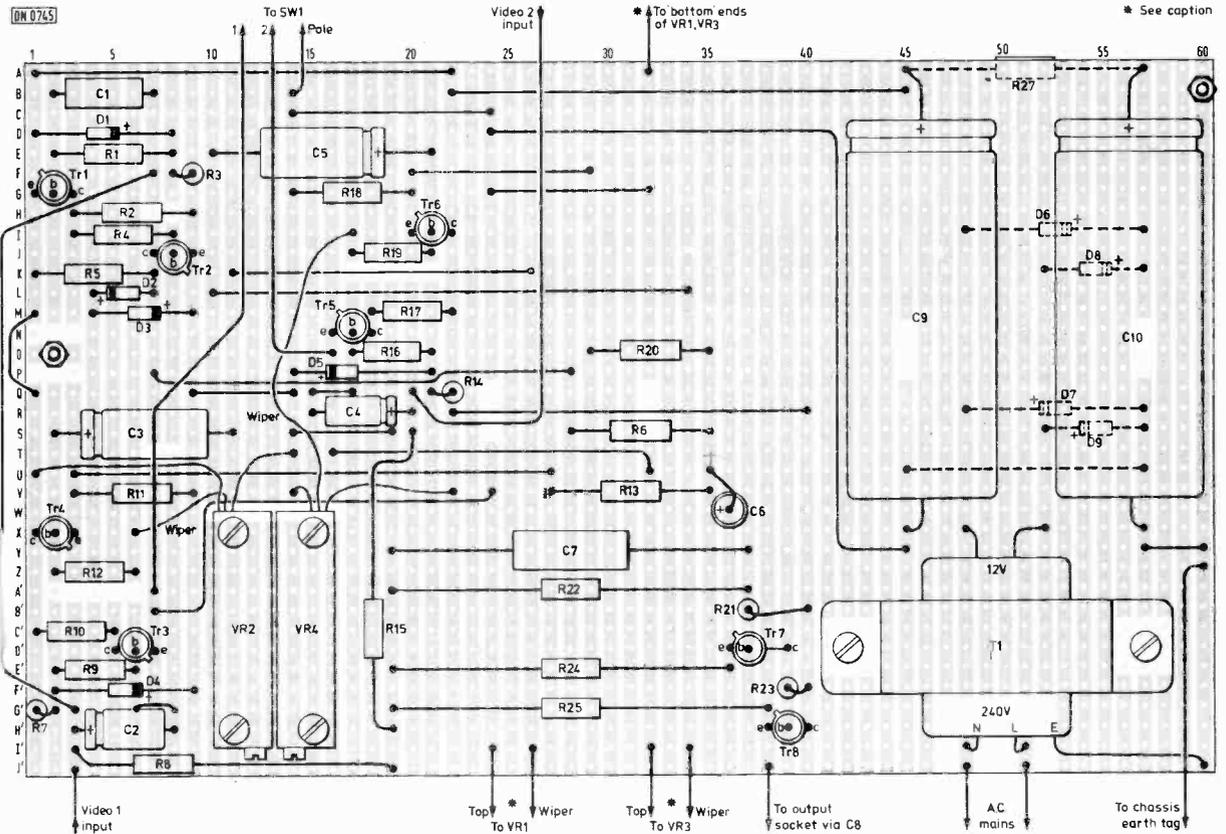


Fig. 4: Veroboard layout, viewed from the component side (0.1 in. Veroboard used). R27 and D6-9 are mounted on the copper side. Connections to VR1 and VR3 can be made via flying leads or if sliding potentiometers are used (as in the prototype) these can be soldered directly to the copper side. Ensure that the mains connections are well insulated from the rest of the circuit board.

switch in the centre position and use the faders as necessary. For fade outs leave the switch towards the camera concerned and use the appropriate fader.


Setting Up

To set up the unit it is necessary to adjust the presets VR2 and VR4 which determine the black level of the video signal. Ideally this should be at +1.2V relative to ground at the emitters of Tr4 and Tr6 respectively. The best way of carrying out this adjustment is to make sure that both sliders are at

the earthy end of the tracks. Set VR1 to maximum level and have camera 1 viewing a test card. VR2 should then be adjusted until a satisfactory picture is produced (peak video will be seen to "lift" out of the black level as adjustment is made). Adjustment should be carried out slowly due to the time-constant of C3 with R12, and the picture allowed to stabilise after each adjustment. The setting is correct when a complete grey scale can be resolved on the monitor. Channel 2 should be adjusted in like manner. Once set there should be no need for any readjustment. ■

NEW ANTIFERRENCE AERIALS

A new range of two extra-gain aerials designed to give improved fringe area reception has been introduced by Antiferrence. The dipole and director assemblies each consist of four half-wave in-phase elements in a shallow X formation. A large six-element full-wave reflector assembly is used with these. The XG8 has eight director assemblies while the XG14, intended for use in outer fringe areas, features 14 director assemblies. Accurate matching to the full-wave dipole is achieved by means of an integral balun plus resonator. Full details are available from Antiferrence Ltd., Aylesbury, Bucks.

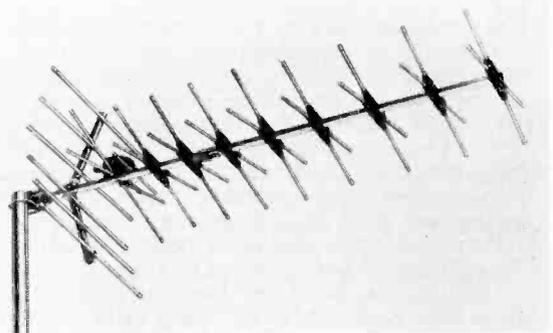

The new Antiferrence aerial type XG8.

PART 1



S. GEORGE

COLOUR BRIGHTNESS CONTROL

BRILLIANCE control in a monochrome receiver is a simple matter of directly varying the c.r.t. grid-cathode potential, complicated only by switch-off spot elimination arrangements. The c.r.t. cathode potential may be kept at a constant bias level and the grid voltage varied by means of the brilliance control or vice versa. With a colour set however there are three c.r.t. beams to be considered and the three beam currents must be balanced throughout their operational range to prevent picture tinting at different brightness levels. For this reason the brightness control must be placed farther back in the receiver circuitry. The brilliance control system adopted depends on whether colour-difference or RGB tube drive is employed. In the present article we will look at brightness control with colour-difference c.r.t. drive; a second instalment will deal with the techniques used with RGB tube drive.

Fig. 1 shows the luminance output stage used in the Pye 691 single-standard chassis, including the brilliance control and beam limiter circuitry. The techniques used in this chassis were very widely employed in colour sets with colour-difference c.r.t. drive.

As there is always more than one stage in the luminance channel it is common practice to use RC coupling at some point. It is then necessary to re-establish the d.c. level of the signal, either by means of a d.c. restorer diode or a clamp circuit, in order to ensure that the luminance signal is based on a constant potential. In the Pye 691 chassis a d.c. restorer diode (D39) is used for this purpose.

D.C. restorer diodes used in monochrome receivers (e.g. in the Philips 210 chassis) are usually simply shunted across the video output pentode grid circuit with the anode to chassis. In a colour receiver however this is a convenient point at which to introduce the brilliance control action. As can be seen in Fig. 1 the anode of the d.c. restorer diode D39 is returned via a 22k Ω resistor (R201A) to the slider of the brilliance control. The track of the brilliance potentiometer is connected between negative and positive rails via limiting resistors. The tapped off potential does not go positive however, the arrangement simply allowing the beam limiting transistor (VT35) to operate. The net result is that the voltage tapped from the brilliance control forms a d.c. base on which the d.c. restored luminance signal is superimposed. This signal is applied to the luminance output pentode (V6) grid via R351: thus altering the brilliance control setting varies the valve's operating point. As the anode of the luminance output pentode is directly linked to the three cathodes of the shadowmask tube variations in the mean anode voltage of V6 due to changes in its negative grid

bias are transmitted to the c.r.t., varying the brightness of the display.

Following usual practice the luminance output is applied at full amplitude to the c.r.t. red gun cathode but via preset drive potentiometers to the green and blue gun cathodes. To ensure that adjustments made to these controls do not materially affect the working d.c. potential of the tube they are connected between the luminance output feed and the junction of the two resistors R356 and R358 which are connected between the h.t. line and chassis. The voltage at the junction of these two resistors is 220V, the same as that at the anode of V6 during the blanking intervals on full drive. There is zero voltage therefore across the blue and green drive potentiometers during these intervals and adjusting them will not affect the d.c. conditions significantly.

As on the other hand the live end of the drive potentiometers is connected to V6 anode while the earthy end is connected to chassis via the 8 μ F electrolytic C354 they are right across the luminance output from the signal point of view and can provide luminance outputs from zero to maximum to the blue and green guns. The 25pF capacitors C501 and C502 which shunt the drive potentiometers maintain full luminance drive at h.f. regardless of the setting of the potentiometers.

Beam Limiter

The beam limiter transistor VT35 controls the voltage applied to the top end of the brightness control and is driven from the cathode of the line output pentode. Under normal conditions, i.e. when the contrast and/or brilliance control settings do not result in excessive c.r.t. beam currents, VT35 is reverse biased by the voltage applied to its emitter from the potential divider R214/RV16. If the e.h.t. demand is excessive however the line output pentode conducts more heavily than normal and the voltage developed across its 10 Ω cathode resistor R226 is sufficient to bias VT35 on—provided the beam limiter preset RV16 is correctly set. VT35 then passes collector current, and the increased current drain through R213 reduces the voltage at the junction of R213/R212 and thus the potential tapped from the slider of the brilliance control. This of course biases V6 back, reducing the drive to the c.r.t.

Flyback Blanking

Line and field flyback blanking are effected by using transistor VT28 to cut off V6 during these periods. V6 cathode is returned to chassis via R359

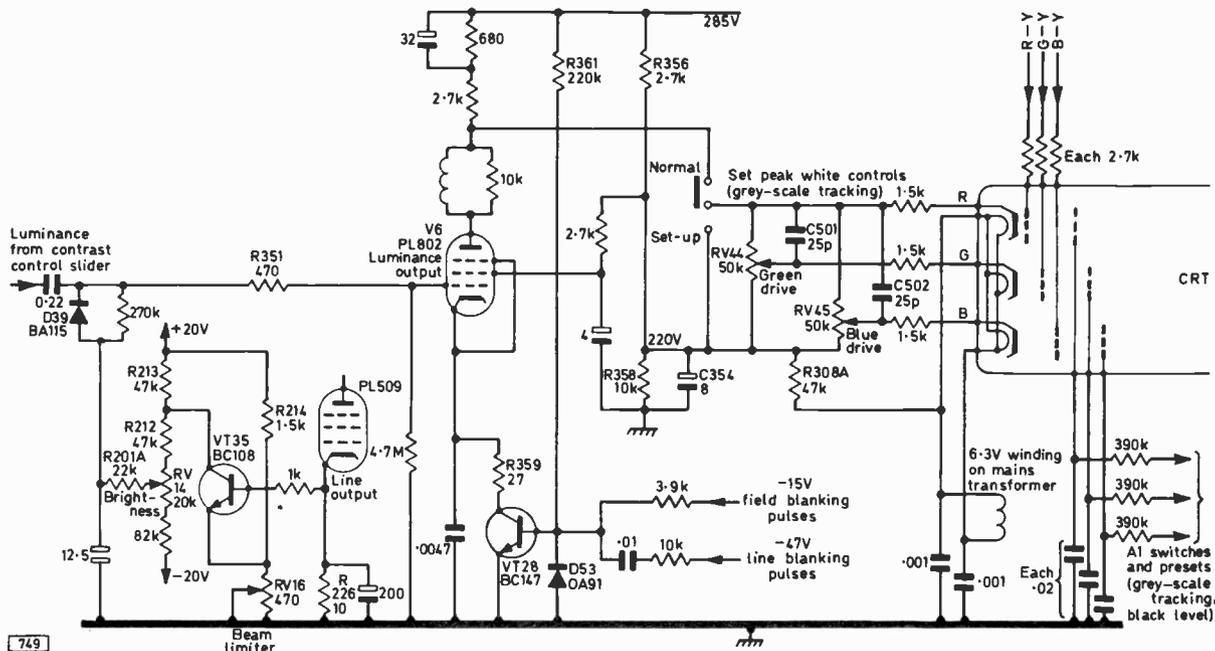


Fig. 1: The luminance output circuit used in the Pye 691 chassis, showing the brightness control, flyback blanking and beam limiting arrangements.

and VT28 which is normally held conducting by the bias applied to its base via R361 from the h.t. line. Negative-going line and field flyback pulses are applied to VT28 base so that during these periods it cuts off: since V6 cathode is then virtually open-circuit its anode voltage rises to the full h.t. line potential and the c.r.t. is cut off, blanking out the flyback. D53 protects VT28 base-emitter junction by clipping the blanking pulses.

Note incidentally that c.r.t. heater-cathode strain in this chassis is minimised by connecting one side of the heaters via R308A to the junction of R356 and R358.

Driven Clamp

Very similar brightness control and flyback blanking arrangements are used in the GEC group chassis, the Decca CTV25 and the Bush/Murphy CTV25/CV2510 series. In the latter however a driven double-diode clamp is used in place of a simple d.c. restorer. A d.c. restorer diode conducts when the negative-going line sync pulse arrives, the coupling capacitor then charging to the potential tapped from the brightness control. The driven clamp (Fig. 2) used in the Bush/Murphy dual-standard chassis is driven into conduction once each line by positive- and negative-going drive pulses from the line output stage. The action of a driven clamp is faster and more accurate than that of a simple d.c. restorer.

Alternative Techniques

With colour-difference c.r.t. drive then it is the usual practice to incorporate the brightness control in the luminance channel d.c. restorer/clamp circuit. Two exceptions are the various versions of the Philips G6 chassis, in which the brightness control varies the luminance output pentode screen grid

voltage, and those Korting chassis in which the brightness control acts in conjunction with driven clamps in the colour-difference output stages. This latter arrangement is necessitated by the fact that in these chassis the luminance channel is d.c. coupled throughout: an example was described and illustrated in the July 1973 issue (page 393).

Fault Conditions

Finally let us consider the types of fault that can develop with the circuitry shown in Fig. 1. Inability to obtain an untinted raster throughout the range of the brilliance control is almost always due simply to incorrect setting of the grey-scale tracking adjustments. Inability to obtain normal peak brightness is commonly caused by an incorrectly set beam limiter but can also of course be due to a low-

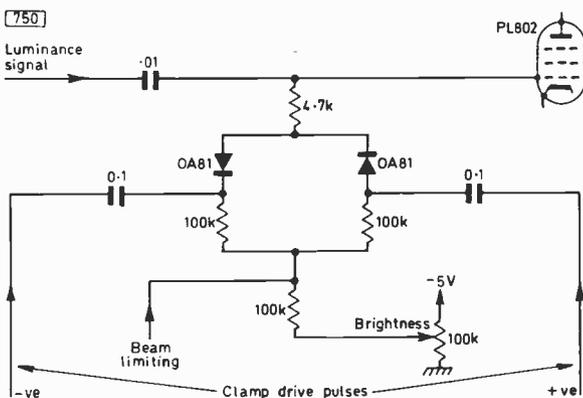


Fig. 2: Double-diode driven clamp used in the RBM dual-standard colour chassis.

72

Fig. 1: Circuit of the GEC Group Series One chassis. Tuner and i.f. shaping filter circuits will be shown next month. Several different intercarrier sound i.c.s. have been used: their external circuits differ.

side than replacing the line output transformer which will be the casualty if the control is left flat out. The value of the control is not too critical—from 500kΩ up.

More often however the control is not at fault: We have not yet had a case in these receivers of the boost line capacitor (C230) shorting. It should be remembered however that this component is not returned to the h.t. line as is the usual practice but to chassis via the line scan coils and the output transformer. Thus if C230 shorts the PY88 will get rather hot under the collar and won't survive very long unless something farther up the line goes first—this won't always be the fuse as R303 doesn't need much of an excuse to pop off.

CONTINUED NEXT MONTH

73


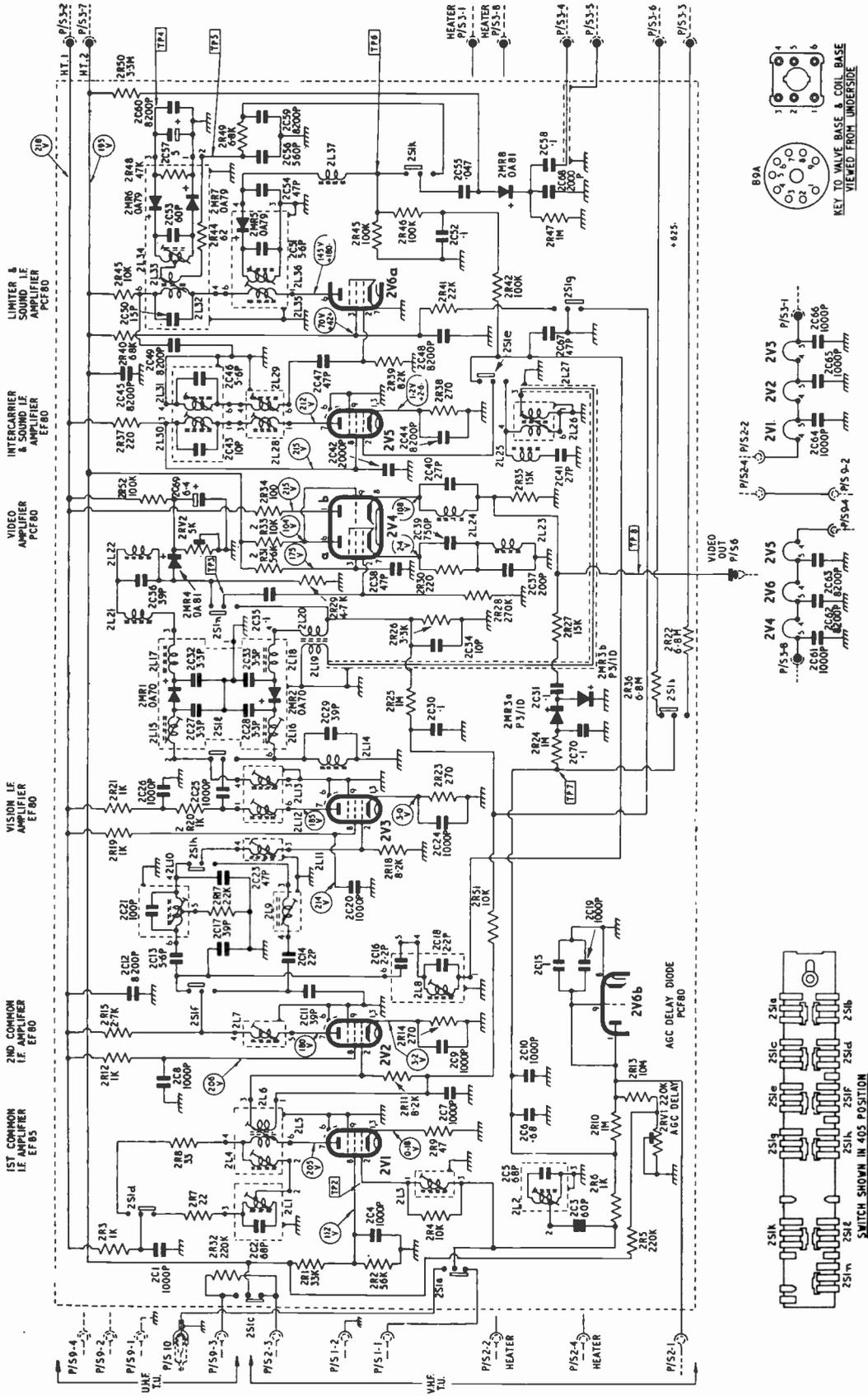
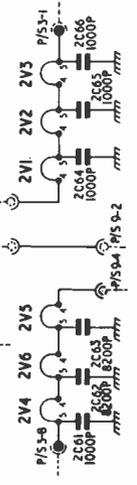


Fig. 1: Circuit of the receiver unit (type A348) used in the Bush/Murphy TV125/V849 series of dual-standard models.

405/625 System switch (Receiver unit A348)

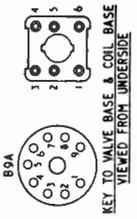

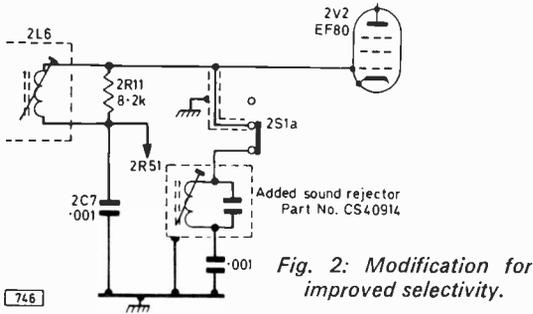


Fig. 2: Modification for improved selectivity.

second vision i.f. stage. This (see Fig. 2) is switched into circuit on 405 only by using the otherwise redundant 2S1a—the rejector can be mounted adjacent to the switch by means of a solder tag.

While tuning across strong signals it was noticed that the a.g.c. line response lagged unduly. To overcome this the a.g.c. line smoothing capacitor 2C6 was reduced in value from $0.68\mu\text{F}$ to $0.1\mu\text{F}$.

IF Bandwidth

The next thing to consider is the question of the i.f. bandwidth. With the detector switching made independent of the other i.f. switching we can use the negative output detector with the narrow bandwidth (405) as well as the wide bandwidth (625). Many of the signals encountered are of marginal strength and a better image (i.e. less noisy) will be seen when narrow bandwidth i.f. strip operation is used. For this reason it is the general practice in DX-TV operation to use narrow i.f. bandwidths with weak signals and to switch to a wider bandwidth only on very strong signals. I have found that during Tropospheric openings signals that have been virtually lost in noise on the wide bandwidth (5.5MHz/625) have been noted by using the narrow bandwidth (3MHz/405). It is necessary to adjust the tuner slightly because of the different i.f.s required with the different i.f. bandwidths. Over many years of DX operation however I have always used receivers with narrow i.f. bandwidths. One very important advantage is the inherent selectivity, which is invaluable when signals are present on adjacent channels. For example in the case of channel E2 vision (48.25 MHz) and channel R1 vision (49.75MHz) a narrow bandwidth receiver will enable each channel to be tuned in whereas operating with wide bandwidth results in the two channels tending to float over each other.

To maintain selectivity at a high level for both positive and negative vision modulation it is necessary to modify the components associated with the vision detector input switching. The i.f. coil 2L13

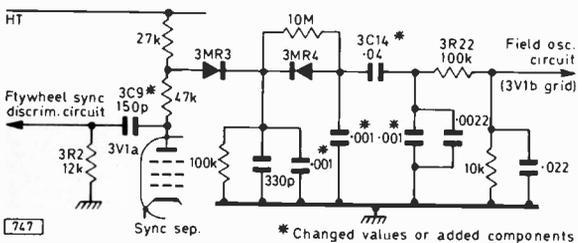


Fig. 3: Sync circuit modifications.

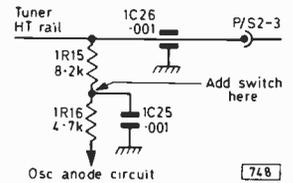


Fig. 4: A switch was fitted between 1R15 and 1R16 in the v.h.f. tuner to switch the oscillator in and out of circuit.

originally connected to the upper contact of 2S11 is connected to the centre contact instead so that it is in circuit for both vision modulation senses while 2L14 and 2C29 are removed. The i.f. coil 2L16 (top core in the large i.f. can) is then reaped for maximum gain with the i.f. strip itself switched to the 405-line (narrow bandwidth) position.

Switch section 2S1g requires separate operation from the main i.f. strip switching unfortunately. This switch performs the following functions: with negative-going vision (625) it brings into circuit the so-called "anti-lockout" a.g.c. supplementary voltage and brings 2R41 into circuit to alter the screen grid voltage of 2V6a so that it acts as a limiter for the f.m. sound signal; with positive-going vision (405) it earths the "anti-lockout" line. I found it convenient to use instead a small slide-action single-pole changeover type switch. It can be soldered to the bracket which protrudes from the i.f. chassis, carrying the various tuner unit power sockets. This means an extra operation when changing from positive to negative vision modulation: possibly some mechanically-inclined reader can suggest some form of linkage to operate it from the detector switching strip?

Timebase Modifications

Little modification seemed necessary to the timebase sections of the receiver. The existing sync circuit produced good locking. Slight improvement was obtained however by making the following modifications: 3C9 which couples the line sync pulses to the flywheel sync discriminator circuit was increased in value from 82pF to 150pF; the field sync pulse coupling capacitor 3C14 was increased in value from 4,700pF to $0.04\mu\text{F}$; additional filtering was introduced by including 1,000pF capacitors from the following points to chassis, junctions 3MR3/4, 3MR4/3C14, 3C14/3R22 (see Fig. 3).

Since for DX reception the receiver usually operates on 625 lines on either vision bandwidth the mechanical timebase switching arrangement was disconnected at the 405/625-line push-buttons so that this control when operated gives either wide or narrow bandwidth i.f. operation. The freed timebase switching cable was wired to one of the vertical upright chassis members where in the event of 405-line timebase operation being required it can be adjusted accordingly.

Front-end Modifications

The final receiver modification was to alter the front-end to operate in conjunction with the varicap tuning unit. In order to achieve high gain the v.h.f. tuner is used as an i.f. preamplifier, both stages being employed for this purpose. A single-pole changeover switch was fitted on the upper side of the tuner adjacent to the PCC89 valve base. Two wires were taken from this to 1R15 ($8.2k\Omega$) and 1R16 ($4.7k\Omega$),

the junction of these resistors being separated inside the tuner. Thus with the switch in one position h.t. is removed from the triode section of the PCF86 mixer valve so that it then acts as a straight pentode amplifier while when the switch is closed the h.t. to the triode section is restored and normal v.h.f. tuner operation commences. For use with the varicap tuner unit the h.t. to the triode section of the PCF86 is isolated by means of this switch and the pentode section gives i.f. amplification.

To tune down to i.f. mechanically it is necessary to study the pushbutton mechanism carefully. It will be seen that as a pushbutton is tuned by being turned a nylon collar moves down a long thread and is eventually stopped by a washer and circlip on the end of the threaded section. Removing the circlip allows tuning below channel B1 and observing the screen shows a definite peak in vision noise. The position then reached is the optimum gain position for operation as an i.f. amplifier (with the changeover switch open of course so that the h.t. supply to the triode section of the PCF86 is removed).

Operation

This completes modification and the i.f. output from the varicap tuning unit can be fed straight into the v.h.f. aerial socket. The gain is of a high order.

With the v.h.f. tuner acting as an i.f. preamplifier and no input signal fed in the noise on the screen is very low—light drizzle is a good description. When the output from the varicap tuning unit is fed in the drizzle changes to a blizzard.

I found in practice that with the aerial preamplifiers I use ahead of the varicap tuning units the varicap tuner gain control is best set halfway for Band I and at maximum for Band III. On u.h.f. the varicap tuning unit gain control is best set to maximum except when working on channels adjacent to the local ones. The varicap tuning unit gain control will obviously require different settings depending on the amount of aerial preamplification used.

The main receiver contrast control is usually advanced only one third from minimum with the a.g.c. delay control on the main i.f. strip set half way. This avoids overloading while retaining the lowest noise figure.

Line Sync Adjustment

As a final adjustment when all modifications have been made check the line synchronisation by rapidly reducing the tuner gain and then advancing it to simulate a weak, fluctuating signal. It should be possible to synchronise to a signal as soon as it appears. If problems are experienced with line synchronisation adjust the flywheel line sync discriminator phase control 3RV1 as follows.

Switch to 405 and adjust the line hold control 3RV5 to mid-travel. Remove the sync pulse input to the discriminator circuit by connecting a shorting link across 3R2. Set 3RV1 to mid-travel and then adjust 3TC1 in the line oscillator circuit to give a stationary display. Switch to 625 and adjust the 625-line preset hold control 3RV3 for a stationary display. Then remove the shorting link across 3R2. Finally check the pull-in range of the line hold control 3RV5.

If the pull-in range limits are displaced clockwise readjust the phase control 3RV1 slightly clockwise and vice versa. Short 3R2 and set the line hold control to mid-travel. Adjust 3TC1 for a stationary display. Repeat this procedure until the pull-in range is placed correctly either side of the line hold control setting.

Conclusion

Carrying out all these modifications should result in a versatile high-gain receiver capable of working with marginal-level vision signals which would be virtually unseen on a conventional receiver.

Finally my thanks to Hugh Cocks for his assistance in obtaining a quantity of these Bush/Murphy receivers. ■

LETTERS

I would like to add to John Law's comments in the August issue on faults in the line timebase used in the Pye 11U series. In my experience—and I have renovated a very large number of these chassis—one of the most frequent causes of line timebase malfunction is R119 (270k Ω , $\frac{1}{2}$ W). This resistor is connected via a 12pF 5kV capacitor (C94) to tag 8 on the line output transformer and small in value though C94 is quite high pulse voltages occur across R119. On most of the sets passing through my hands R119 has been found to be discoloured, and resistance checks often reveal that it has gone high-resistance. The symptoms produced by its failure vary from weak and drifting line hold to a complete refusal of the timebase to oscillate at all. In some cases the timebase oscillates but at a drastically reduced frequency, in others there is a buzzing sound as if something is arcing over, while in yet others all appears well except that the timebase takes an inordinately long time to start oscillating.

I recommend replacing R119 with a 1W type, or

alternatively with a 120k Ω plus 150k Ω pair of $\frac{1}{4}$ W resistors. In both cases increased spacing between C94 and V14B pin 1 should help deter high voltages from sparking over. Care should be taken to ensure that neither C94 nor the replacement R119 touches the line output transformer cover.—P. Lane (Llanerchymedd, Anglesey).

TCE 8000 CHASSIS

As a bench engineer employed by a company within the Thorn group I would like to provide a practical appraisal of the 22kV e.h.t. and line output transformer used in the 8000 chassis (see comments on this subject earlier this year). We have a large number of 8000 series receivers operating in customers' homes within our service area and to date have had no serious problem with line output transformer failures—indeed we have had to replace only two. This compares very favourably with the 3000/3500 chassis with its tripler and lower-voltage overwinding.—P. C. Allen (Stirling).

(See letter on page 367, June issue, and IBC-72 review in the March issue.)

THE 'TELEVISION' COLOUR RECEIVER

FORUM

THE purpose of this feature, started last month, is to co-ordinate hints and tips from readers who have successfully completed the TELEVISION Colour Receiver and to pass them on for the benefit of others. We have already been in touch with a number of successful constructors as a result of which it has been possible to present readers with a considerable amount of useful material. We invite others to contribute notes on their findings, comments or suggestions that may be useful to others. Clear sketches and monochrome photographs of sets or parts of sets are welcome. All contributions pub-

lished in this feature will be paid for at our normal rates. Contributors' addresses will not be published.

Please do not send in parts of receivers unless requested to do so. We regret that it is not possible to answer telephone enquiries regarding this feature or the set itself.

The Fault Finding Advisory Service (form in the August, September and October issues) will be continued until further notice.

Two constructors outline below their own power supply circuits: both seem to be very satisfactory and have their own obvious advantages.

Dear Sir,

POWER SUPPLIES

In order to get the set working without further loss of time I decided to forgo the advantages of using a mains isolating transformer and having the chassis earthed, taking the chassis to the neutral side of the mains supply instead. This is safe so long as you ensure that (1) all exposed metalwork goes to mains earth, i.e. disconnect the braiding connections to the front panel, and (2) the c.r.t. protection band is connected to chassis via an RC leakage path, not directly (use a $3.3M\Omega$ 1W resistor and $0.0018\mu F$ 4kV tubular ceramic capacitor in parallel). The circuit I used is shown in Fig. 1. The resistor connected from one side of the c.r.t. heaters to the red gun cathode is to ensure that the safe c.r.t. heater-cathode voltage is not exceeded; it also removes hum injection. The slightly increased complexity of the 20V supply is well worthwhile. Note that the audio board supply (6L) will rise above 30V if the 20V load is reduced, so 6L should be connected last—if you are a purist! Incidentally I feel that the line output valve screen feed resistor would be better rated at 10W: this is not essential but is advisable in the interests of reliability and stability.

WIRING

(1) I recommend that the signal connections to the RGB board, from 2E to 3C, 1E to 3E and 1F to 3D, be made with v.h.f. coaxial cable. This avoids loss of h.f. signal components and spurious pick-up. Earthing at both ends has not caused any hum loops. If any setting up is done without the decoder fitted, i.e. with 3D and 3E disconnected, these two points should be taken to earth via $10\mu F$ electrolytics.

(2) On the decoder board I have found that to prevent subcarrier pickup it is best to use v.h.f. coaxial

cable for the link designated V, from D16 cathode to C43: earth the ends at the earthy end of R63 and to L6 can earth respectively.

Coaxial cable earthed at both ends should also be used for the $-80V$ pulse feed to 1D on the decoder from tag 9 on the line output transformer. Otherwise unstable sync can result due to radiation.

BEAM LIMITING

I found that the beam limiting circuit tends to spoil the effectiveness of the black-level clamping system by endeavouring to maintain a constant average beam current. Accordingly I have modified the circuit as shown in Fig. 2 (left-hand side). Tr702 is now normally off. When excessive beam current flows the voltage at 4H/9Q rises until 0.6V is developed at Tr702 base. It then turns on, holding the c.r.t. grids at 23V or so thus limiting the beam current to a safe value.

FLYBACK BLANKING

The arrangement I used for field flyback blanking is shown on the right-hand side of Fig. 2. The flyback pulse appearing at D305 cathode is inverted by the BC107 and used to cut off the c.r.t. grids. I also found that improved line flyback blanking was obtained using the circuitry shown.

DECODER

The reference oscillator refused to lock with L2/C13 in circuit. No trouble was experienced after removing them. I found that the preceding d.c. amplifier Tr3 likes to oscillate as well: a $470pF$ capacitor from collector to chassis stops this.

Low ident output was cured by changing L4 core, adding an $0.068\mu F$ capacitor across the coil and changing Tr6 to a high-gain BC149 transistor.

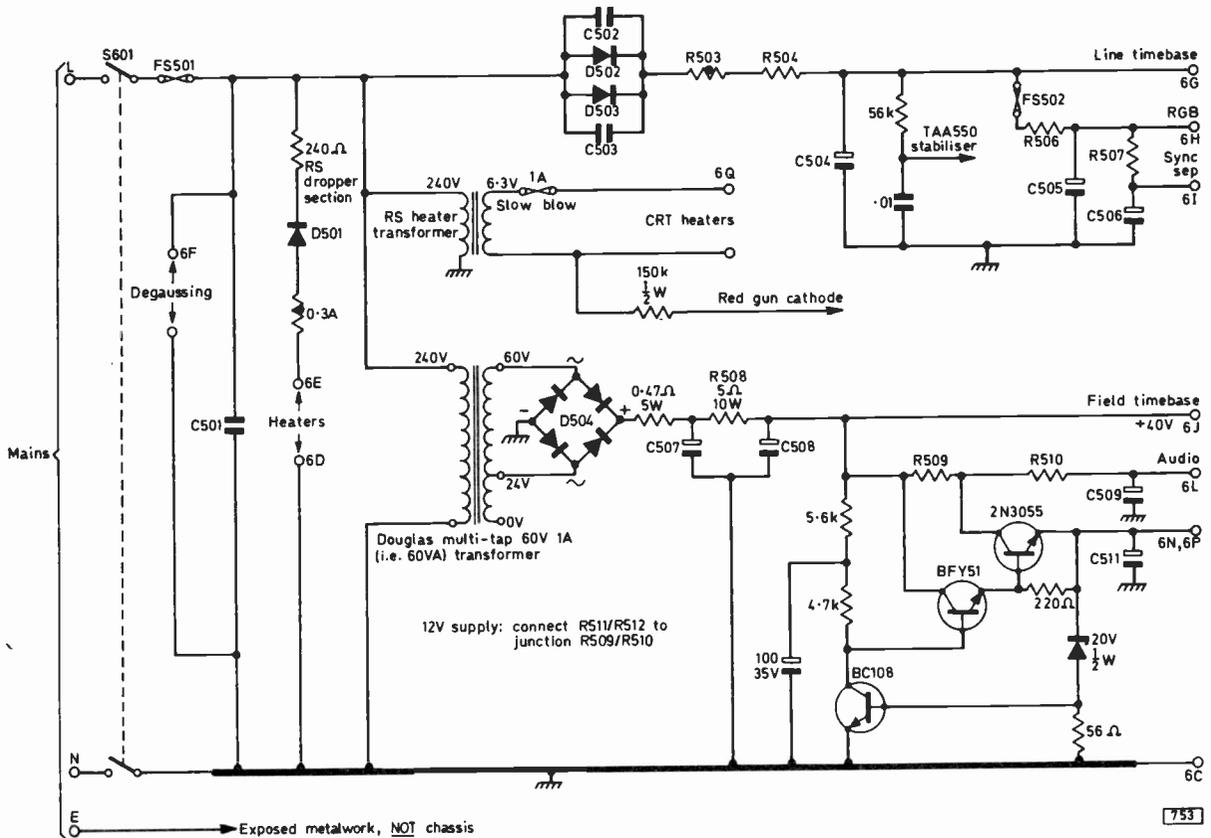


Fig. 1: Power supply circuit used by L. Cook, with stabilised 20V line. 36V a.c. is obtained across the 24V and 60V taps on the secondary winding of the Douglas multi-tap transformer.

Difficulty in getting the bistable to trigger reliably was cured by changing C40 to 0.0068 μ F and R53 to 82 Ω ; also an extra 0.0068 μ F capacitor may be needed across C39. It is possible however that L5 may be faulty, so these last amendments are only tentatively suggested though I have found them to work.

L. Cook

Editorial comment: We have heard from other readers of trouble with the network L2/C13 but do

not recommend its removal. The trouble appears to be due to spreads in the value of the coil. Likewise the bistable triggering difficulty seems to be due to spreads in the value, which is quite critical, of L5.

Dear Sir,

BOARD LAYOUT

As mentioned last month improved performance can be obtained by mounting the three signal boards side-by-side on a sheet of hardboard (make cut-outs for access to the printed side of the boards) at the left-hand side of the cabinet. The arrangement is shown in Fig. 3. Fig. 5 shows the small board on which the RGB drive controls are mounted (so that the signals, with the RGB board mounted towards the centre of the chassis to the left of the c.r.t., can be fed via short connections to the c.r.t. base panel).

In connection with the modified blanking circuit described last month it should perhaps be made clear that the line flyback blanking pulses are taken, as in Fig. 4 on page 403 of the July issue, from 9N via C704 and R709 to the junction R712/R708.

ADJUSTMENT IMPROVEMENTS

I have found that horizontal centring can be achieved much more satisfactorily if a centre-tapped potentiometer is used for R354. Connect the centre tap to PL301: the flying lead to SKT301/2 is then

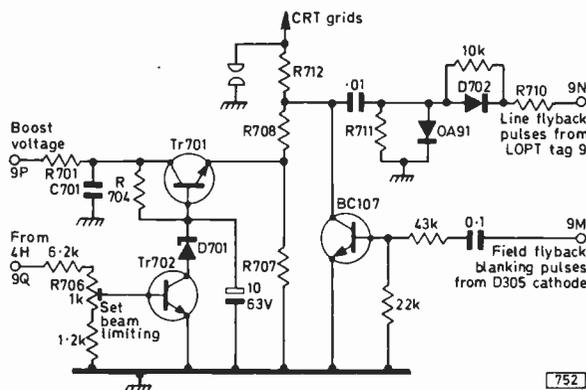


Fig. 2: Beam limiting and flyback blanking circuit used by L. Cook.

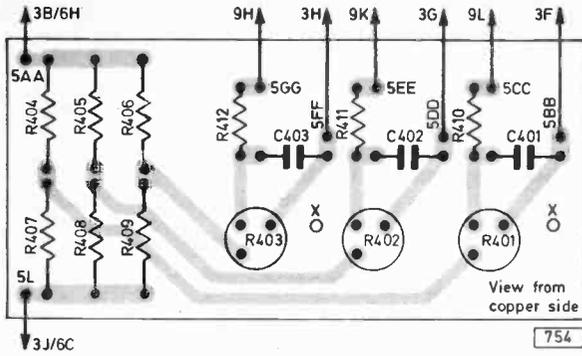


Fig. 5: The small board used by E. Erven to mount the RGB drive controls: drill $\frac{1}{8}$ in. holes in the positions marked X to secure the board to two of the RGB output transistor heatsinks—ensure that the board is insulated from the heatsinks. Shown half scale (viewed from the copper strip side).

carry out: the potentiometers are simply adjusted to give the stated outputs.

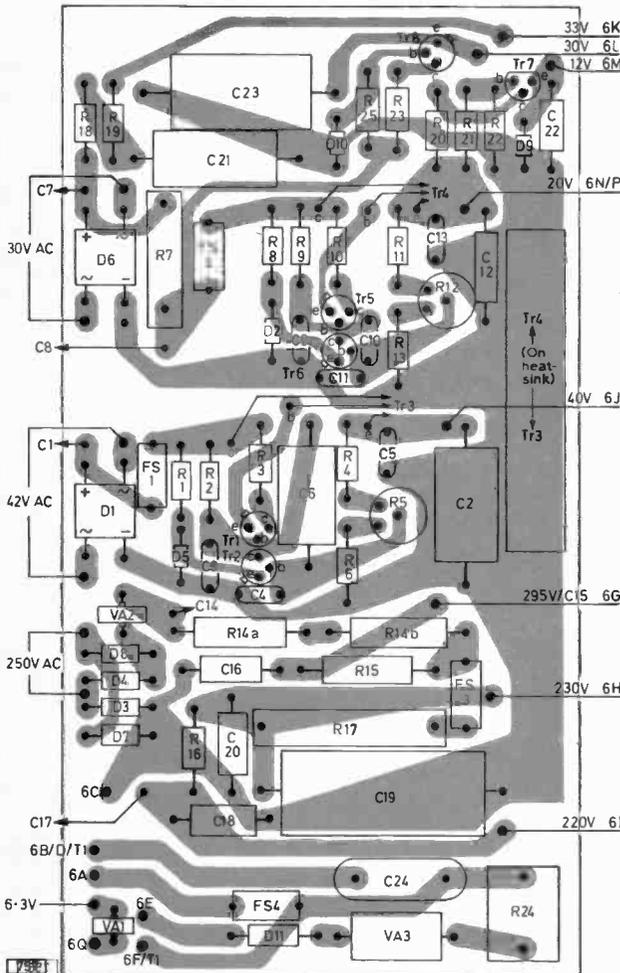


Fig. 6 (left): Layout of E. Erven's power supply, viewed from the component side. C1, C7/8, C14 and C15 are mounted off the board.

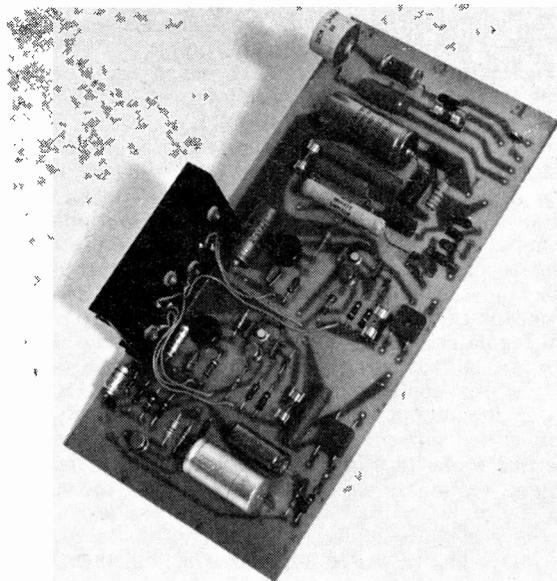


Fig. 7 (right): Printed panel pattern (copper side), shown half scale.

The stabiliser circuits have been devised so that if the outputs are inadvertently short-circuited the fuses will blow without the transistors going.

The ratings of the various mains transformer secondary windings are as follows: 0–250V 1A, 0–42V 1A, 0–30V 500mA, 6.3V 1A.

Measurements on the circuit give the following performance figures. The output from the 40V regulator is 40V with no load falling to 39.9V at an output of 1A into a resistive load. 2.5V p-p ripple at the input is reduced to 50mV p-p at the output. The regulator draws 12mA, the short-circuit current is 5.6A and the output can be adjusted from 36–44V by means of R5. With no load the output from the 20V regulator is 20V, falling to approximately 19.9V with an output of 500mA into a resistive load. 400mV p-p ripple at the input is reduced to 10mV p-p at the output. The regulator draws 12mA, the short-circuit current is 2.2A and the output can be adjusted from 18.5–22V by means of R12. The h.t. supplies remain stable to within $\pm 10\%$ of the specified figures at normal average brightness levels: at excessive brightness levels the voltage falls to -10% or worse. The regulated supplies will hold their out-



E. Erven's power supply unit. Four large can electrolytics are separately mounted using suitable clips.

puts within 0.5% for a variation of the nominal mains voltage of $\pm 15\%$.

E. Erven

Editorial comment: The power supply circuit devised by E. Erven is illustrated in the accompanying photograph. We have found it to provide wholly satisfactory results. We understand that the components required can be obtained from Forgestone Components.

CROSSHATCH GENERATOR

It was originally intended to publish details of a crosshatch generator devised specifically for the colour receiver. After costing this out however we have found that the advantage lies with using the design by C. R. Bradley B.Sc. published in the September 1972 issue (during the series on the colour receiver). This has been tried out with the colour receiver and operates perfectly satisfactorily. Line pulses can be picked up by wrapping the generator's insulated input lead around C327 (timebase board); feed the video output signal from the generator to the base of Tr109 on the i.f. panel. Note the crosshatch generator modification given in the January 1973 issue (page 129)—adding a 200pF capacitor from Tr1 base to chassis.

The generator (assuming purchase of a Bi-Pre-

components list (Fig. 4)

Resistors

R1 6.8k Ω	R7 10 Ω 10W	R14 47 Ω * 15W	R21 6.8k Ω
R2 8.2k Ω	R8 5.6k Ω	R15 50 Ω 10W	R22 12k Ω
R3 200 Ω 2W	R9 12k Ω	R16 3.3k Ω 1W	R23 10 Ω
R4 27k Ω	R10 470 Ω	R17 1.8k Ω 15W	R24 220 Ω 0.3A
R5 2.2k Ω $\frac{1}{4}$ W pot	R11 8.2k Ω	R18 1.5k Ω	R25 560 Ω
R6 8.2k Ω	R12 2.2k Ω $\frac{1}{4}$ W pot	R19 470 Ω	
	R13 10k Ω	R20 1k Ω	

All $\frac{1}{2}$ W unless otherwise indicated.

*See Fig. 4 caption.

Capacitors

C1 3300 μ F 63V	C7 1650 μ F } 63V	C13 0.1 μ F 50V	C19 50 μ F 350V
C2 250 μ F 50V	C8 1650 μ F }	C14 400 μ F 350V	C20 0.1 μ F 400V
C3 0.01 μ F 50V	C9 0.01 μ F 50V	C15 400 μ F 350V	C21 100 μ F 35V
C4 0.01 μ F 50V	C10 0.01 μ F 50V	C16 0.1 μ F 400V	C22 100 μ F 15V
C5 0.1 μ F 50V	C11 0.01 μ F 50V	C17 100 μ F 275V	C23 2200 μ F 35V
C6 1 μ F 50V	C12 10 μ F 25V	C18 0.1 μ F 400V	C24 0.1 μ F 900V

Semiconductors

D1 2A bridge	D9 12V 1W zener (1N3022)	Tr6 BC107
D2 10V 1W zener (1N3020)	D10 30V 1W zener (1N3031)	Tr7 BC183LA
D3 BY133/1N4007	D11 BY127	Tr8 2N3053
D4 BY133/1N4007	Tr1 2N3053	VA1 VA1033
D5 10V 1W zener (1N3020)	Tr2 BC107	VA2 VA1104
D6 1A bridge	Tr3 2N3055	VA3 VA1026
D7 BY133/1N4007	Tr4 2N3055	
D8 BY133/1N4007	Tr5 2N3053	

D3, D4, D7 and D8 must be the same type.

Miscellaneous

FS1 1A
 FS2 500mA
 FS3 100 mA
 FS4 3A
 All anti-surge.

T1 Mains transformer (see text)
 Heatsink assembly type
 A1057D/T03; transistor mounting
 kits; printed board; capacitor
 mounting clips.

Pack kit) can be mounted in the receiver as follows. Discard the original box. Mount the rotary switch in the normal position but for the slide switch break off the mounting side plates and bend back the three contacts opposite the slide switch lever itself. Mount these three contacts through the holes in the board closest to the edge and wire up the other three contacts with connecting wire. Discard the original VR2/S3 and use instead an RS 4.7k Ω 16mm potentiometer with s.p.s.t. switch. Glue this on the corner of the board where the original component was to be mounted, using Araldite: the switch contacts should hang over the edge of the board. Wire the potentiometer and switch contacts to the printed circuit tracks with connecting wire. Mount all the other components in the usual way. The generator can then be positioned in the convergence drawer behind board three. We expect to be able to provide details of the convergence drawer top panel shortly.

DEGAUSSING

C.R.T. demagnetising was not mentioned in the setting-up instructions. Several constructors with whom we have talked have reported that they found it unnecessary. It is possible however that some c.r.t.s may have become excessively magnetised before use, making purity difficult to obtain. Details for the construction of a suitable degaussing/demagnetising coil were given in the June 1972 issue, during the series on the colour receiver, on pages 368/9, together with instructions on its use.

SETTING-UP PROCEDURE

First a correction: the instruction to restore the power supply connection to 5P should have been given under the heading "Timebase Checks" along with the instruction to restore the connection to 4B, not just prior to making the picture geometry adjustments.

Secondly mention of the coil (L501) on the tuner/i.f. preamplifier board was omitted. The tuning is not very critical: adjust for maximum output, after tuning in the varactor control panel on one push-button. This is done during the "initial stages".

We shall be publishing next month a detailed procedure for aligning the decoder using just a multi-meter and a simple diode probe.

MODULE INTERCONNECTIONS

The fact that there are two earth pads marked 8D on the tuner board was overlooked in the module interconnection list given in the July issue. As mentioned in the alignment instructions (May) the i.f. preamplifier output (8K) should be connected to the input point (2B) on the i.f. board via coaxial cable (no longer than 10in.) with the cable screen earthed at both ends, i.e. at 8D adjacent to 8K at one end and 2J adjacent to 2B at the other. This is important. Connect the other 8D pad to the main 2J to 6C point on the i.f. board (not direct to 6C).

BOARD POSITIONS

A number of readers have pointed out that the line output transformer and e.h.t. tripler cannot be mounted between the boards on the right-hand side of the cabinet as suggested in the June issue: they should be mounted behind the RGB board.

TIMEBASE FUSE

Note that the 500mA fuse FS301 on the timebase board must be an anti-surge type (otherwise you may get repeated fuse blowing).

CRT FIRST ANODE SWITCHES

Several readers have complained about a crack from these switches when they are operated. One of the modifications given in E. Erven's letter last month, decoupling the c.r.t. first anodes with 0.01 μ F capacitors, has been found to overcome this.

POWER SUPPLY

In the event of it being necessary to replace the zener diodes D506, D507 or D508 following the power supply modification suggestions made last month we recommend the use of 7 or 10W types.

Partial loading of the low-voltage d.c. outputs is not recommended otherwise these will rise excessively giving false operating conditions.

MISCELLANEOUS

The component reference number R605 was unfortunately used twice in the project. There should be no confusion however since one "R605" is the 470 Ω 1W carbon resistor connected in series with the black lead from the e.h.t. multiplier unit while the other one is the VA8650 positive temperature coefficient thermistor in the degaussing circuit.


A number of readers have asked why a ferrite loudspeaker was specified. The author states that this type of loudspeaker has a low radial field compared to its fairly large axial field: the low radial field minimises its effect on the picture purity/convergence.

It is possible however that some slight picture discoloration may still be experienced if the loudspeaker is close enough to the tube: its siting is an important factor therefore.

NEW FROM MULLARD

An improved version of the Mullard luminance and chrominance signal processing i.c. is being introduced: the new version is designated TBA560C. It offers the following advantages over the earlier version: full short-circuit protection; increased automatic chrominance control (a.c.c.) range; reduced crosstalk between the chrominance and luminance channels; improved black level stability with variations in picture content and contrast control setting. When a C version is used to replace the original TBA560 certain minor component changes in the peripheral circuitry are necessary.

For applications—including line timebase circuitry—where a fast diode "snap off" characteristic can introduce unwanted interference Mullard have introduced four new "soft recovery" diodes, types BY206, BY207, BY210-400 and BY210-600. The soft recovery characteristic is obtained by using a p diffusion into an n substrate. This results in a more gradual reduction of the stored charge when the device cuts off. The BY206 is a direct and improved replacement for the BA145 and BA148 which are found quite widely in line timebase circuits and are now being phased out by Mullard.

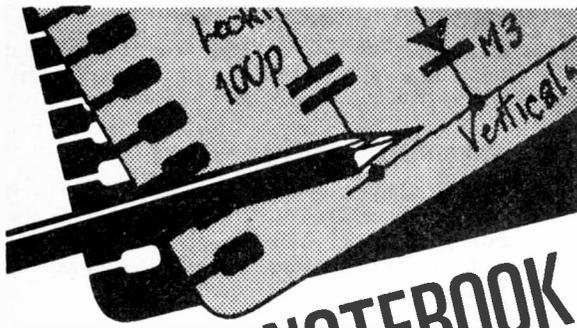

SERVICE NOTEBOOK

G. R. WILDING

Erratic Width

The problem with a Philips colour set fitted with the G6 single-standard chassis was occasional erratic changes in picture width. The impression was of a dry-joint in the timebase circuit rather than impending transformer breakdown. The line stabilisation control R5040 (Fig. 1) operated smoothly, with no suggestion of a bad spot on the track, and the two series-connected $3.3\text{M}\Omega$ resistors connected from a tapping on the line output transformer primary to the width stabilising v.d.r. were replaced without any improvement (such high-value resistors are found in the width circuits of all modern receivers and frequently go high-resistance to cause reduced width, but the possibility of a poor connection between one of the lead-out wires and the composition body must always be considered). Slight voltage variations at the line output valve control grid indicated that the fault was in this part of the circuit, the possibilities being the v.d.r. itself, the $1.8\text{M}\Omega$ grid resistor, the coupling capacitor from the line oscillator stage and the 150pF pulse feedback capacitor C5017 across the two $3.3\text{M}\Omega$ resistors. As this latter component is subject to

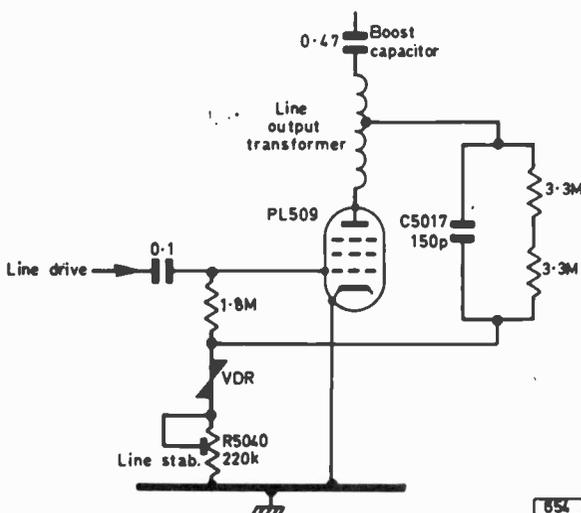


Fig. 1: Line output valve grid circuit of the Philips G6 chassis (single-standard version). The complaint was occasional erratic width reduction.

high-voltage pulses it seemed the most likely suspect and although its insulation seemed to be in order when tested with a Megger replacing it completely cured the trouble. Once again the only sure capacitor test, especially when the fault is intermittent, is replacement.

Dark Band Across Screen

The complaint with a 19in. Defiant model (Plessey chassis) was the appearance of a dark band across the screen. The owner mentioned that sparks and flashes could be seen through the back of the set following the development of the trouble. These models have two large printed panels, one carrying the i.f./video and the other the timebase circuitry. We found that a section of the former panel near the PCL84 video pentode had darkened considerably, current tracking across intermittently in two places. This was probably due to the effect of prolonged heat from adjacent high-wattage resistors. The main leakage was between the printed wiring to heater pin 5 on the PCL84 valveholder and the valve's control and screen grids.

Tapping the discoloured panel areas with a sharp-bladed screwdriver resulted in the defective paxolin flaking off without weakening the valveholder mounting. The strips of printed wiring originally crossing these areas, plus those crossing even slightly discoloured sections, were completely peeled off therefore and replaced by jumper leads. The PCL84 appeared to be in order but was replaced since this type of valve frequently develops internal shorts after some years in service, and this one had certainly been subject to ill treatment. On retesting perfect results were obtained with no suggestion of the original screen hum bar.

If tracking or arcing across insulating panels of any type is caught in time and the defective areas chipped out the repair is usually a complete success.

No Field Lock; also Contrast Fault

THE COMPLAINT with a set fitted with the BRC 1400 chassis was that the picture could not be locked. On inspection it was found that although line lock could be obtained after careful adjustment it was impossible to obtain vertical lock, while the picture shape suggested that there was more at fault than the field timebase running too fast. On removing the back the cause of the trouble was obvious—all valves were glowing far too brightly as a result of the heater rectifier being short-circuit. This particular rectifier (a BY130) is mounted at the top of the swing-out chassis, near the left-hand side of the multiple dropper, and is so small (about the size of a vision detector diode) that it is easily overlooked. When it goes short-circuit a.c. appears on the heater line and as on this chassis the bias for the pentode section of the field timebase valve (PCL85) is taken from a point along the heater chain the result is constant field tripping and a distorted raster—this safety feature prevents the set being used until the fault has been cleared. On replacing the rectifier a normal picture was obtained but the contrast on both standards was found to be well below standard.

The rear-mounted 405/625 contrast controls had only slight effect. As is usual in valved dual-standard

LONG-DISTANCE TELEVISION

ROGER BUNNEY

SEPTEMBER has displayed a slackening in the field of long-distance television reception, at least compared with recent months. This is to be expected of course at this time of the year. Fortunately the log has been enlivened by improved tropospheric reception while at times Sporadic E propagation has shown itself, with reception of several distant countries. I took the opportunity of visiting Ian Beckett at Buckingham towards the end of the month—more about that later.

My own log is as follows; the period 16th-22nd inclusive is the log from Garry Smith (Derby) who held the fort during this time whilst I was away.

- 1/9/73 SR (Sweden) ch. E2—SpE (Sporadic E).
- 2/9/73 NOS (Holland) E4; BRT (Belgium) E8, 10—all trop.
- 3/9/73 DFF (East Germany-GDR) E4; DR (Denmark) E4—both MS (Meteor Shower); TVE (Spain) E2—SpE; NOS E4—trops. The tropospheric conditions showed a lift on this day into Central France—particularly at u.h.f. (new ORTF station logged, Amiens E47).
- 4/9/73 CST (Czechoslovakia) R1; DFF E4—both MS; R1 unidentified SpE signal.
- 5/9/73 CST R1; RAI (Italy) IB—both MS; NOS E4—trops.
- 6/9/73 DFF E4—MS; TSS (USSR) R1, 3; CST R1; TVP (Poland) R2, 3; NRK (Norway) E2—all SpE; also unidentified signals; NOS E4—trops. u.h.f. trop into ORTF (France).
- 7/9/73 DFF E4—MS.
- 8/9/73 WG (West Germany) u.h.f. trop opening in Band III through u.h.f. Two new u.h.f. stations logged, both WDR—3.
- 9/9/73 DFF E4—MS; NOS E4; several WG u.h.f.—all trop.
- 10/9/73 DFF E4; DR E4—both MS.
- 11/9/73 DFF E4—MS; NOS E4; E21 u.h.f. WG—just out of the noise—all trop.
- 12/9/73 CST R1; RUV (Iceland) E4—both MS; NOS E4—trops.
- 13/9/73 CST R1; WG E2; ORF (Austria) E2a—all MS.
- 14/9/73 DFF E3, 4; CST R1—both MS; SR E2—SpE; NOS E4—trops.
- 15/9/73 CST R1—MS; unusual trop opening to the NE, NOS only at u.h.f., particularly Wieringermeer E39 with a good signal; also DR E6, 7 (three new stations this day). At 1526 whilst sitting on Lille-2 E21 the Fubk card was noted to be alternating with the ORTF station—this can only be CLT Luxembourg!

Now to Garry Smith's log:


- 16/9/73 TVE E2; CST R1—both MS.
 - 17/9/73 CST R1; TVP R1; ORF E2a—all MS.
 - 18/9/73 CST R1 twice; TVP R1; RTE (Eire) B7—latter trop, others MS.
 - 19/9/73 TSS R1; CST R1; MT (Hungary) R1; WG E2, 3; SR E3; NRK E3—all MS.
 - 20/9/73 CST R1; TVP R1—both MS.
 - 21/9/73 CST R1; ORF E2a—both MS.
 - 22/9/73 TSS R1—SpE.
- Back to my log:
- 23/9/73 DFF E4; CST R1—both MS.
 - 24/9/73 DFF E4—MS.
 - 25/9/73 TSS R1; DFF E4—both MS.
 - 26/9/73 CST R1—MS; NOS E4—trops.

It is interesting to note that the majority of my loggings are in the early mornings whereas Garry's are between 1215-1330.

From the results over the past month I have been able to evaluate the new aerial system thoroughly. In Band I NOS ch. E4 is received much more regularly, to the extent that I propose to discontinue logging it if the reception frequency remains as at present. Band III has been more difficult to evaluate though the BRT/RTB E8/10 transmitters in Belgium are received much more easily. With the dish paraboloid now at 51½ft. (centre), u.h.f. has shown a remarkable improvement, so much so that Paris ch. E22 is received daily (although well into the noise—previously it was 'in' only during openings). The ch. E25/28 Wavre transmitters are also received daily (of sorts) whereas previously they were just not visible.

Aerials

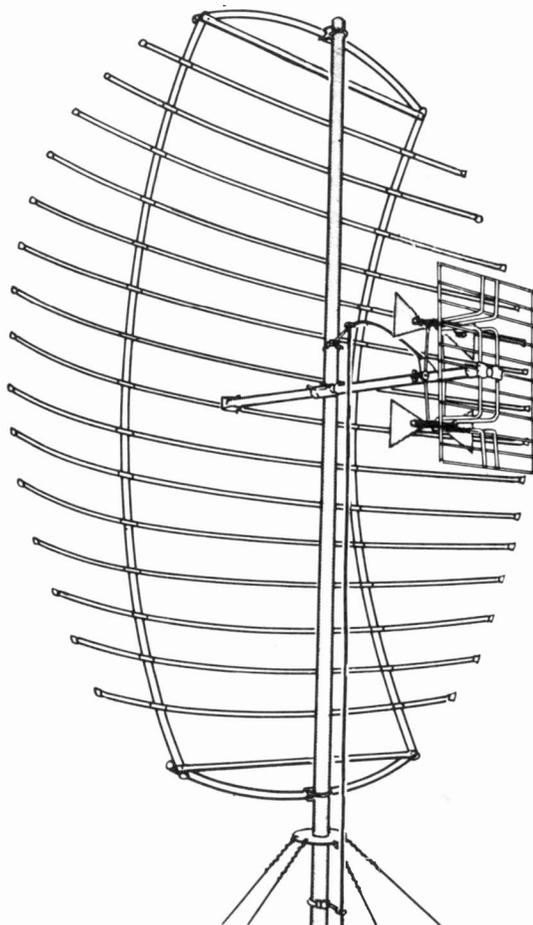Elsewhere in this column are illustrations showing the mast and a detailed sketch of the dish. This latter array is some 7ft. high and 5ft. wide, having at the paraboloid



Drawing of the Channel Master paraboloid "Super Panascope" u.h.f. aerial.

focal point a twin stacked bowtie arrangement. The element rods comprising the reflector dish are $\frac{1}{4}$ in. diameter alloy. The quoted gain is 18dB at 450MHz rising to just under 24dB at 900MHz. The array is of USA origin and imported into the UK by CATV Services Ltd., 2 Leeson Park, Dublin 6, Eire. (This firm is also known as Phoenix Relays Ltd.) They tell us that a professional u.h.f. dish is also available from stock: this has a gain of 30dB, is constructed of aluminium with a weldwire surface and is priced at £1,000 or alternatively in a kit form. This must be the ultimate for DX-TV work!

Whilst on the aerial theme, during my visit to Ian Beckett I took the opportunity of visiting the Antiference factory at Aylesbury. By coincidence our visit came at a time when a new u.h.f. array was being launched and we were able to study the whole process of aerial manufacture from development through to the packing of the finished product. The new array certainly looked impressive on paper. Known as the "extra gain", it resembles the Fuba type multiple director array although with a large reflector assembly. The quoted gain figures for the two models are type XG8 15.5-17.5dB, type XG14 17-19dB, with front-to-back ratios averaging 30dB (the poorest figure quoted is 27dB).

Round Up


During a recent tropospheric opening Hugh Cocks (Mayfield) noted the WDR ch. E32 transmitter radiating the EBU bar carrying an identification "Zentrale Kontrollstelle Frankfurt/Main". Hugh also noted BRT carrying a Eurovision transmission of a cycle race from TVE (2nd September)—the point worth noting is that this race was in colour. I feel that TVE will be carrying increased programming in colour over the next year with the possibility of appropriate test patterns. Whilst in the PM5544 region (!), both the BBC and IBA will be making increased use of this card. It has been noticed already in Ulster. The reason is to enable the GPO lines to be used for other purposes.

Peter Vaarkamp comments that WDR-1 uses the SWF/Fubk pattern now with "WDR-1" as identification. WDR-3 is similar but varies at times to an alternative "WDR-Z" when the pattern comes from the transmission centre. Peter also mentions that a list of both West German and East German (GDR) transmitters can be obtained from Fernmeldetechnisches Zentralamt Deutsche Bundespost, 61 Darmstadt, Postfach 800, West Germany at five German marks.

I was very pleased to meet Dieter Scheiba of Brussels, Belgium recently here at Romsey. Amongst the things we discussed were the BRT/RTB test transmissions—there has always seemed to be some variation with the timings of these. The position is as follows. Both v.h.f. and u.h.f. test transmissions vary daily depending on the transmitter. Antwerp may transmit both early and late. Other transmitters can remain on test card for considerable periods after programmes finish at night. Generally, programmes commence at approximately 1800-2300 during the week. On Saturdays the situation varies according to the sports activities, at times opening during the afternoon but otherwise at 1800. On Sundays the hours are generally 1000-1200, 1400-1700, 1800-2300.

The reasons for the ORTF-1 625-line tests were also discussed. It seems that there was a plan to change the 819-line service to 625 lines to coincide with the start of ORTF-3. Due to the numbers of 819-line receivers in use as the time approached however the plan was dropped, but 625-line tests continue on Tuesday mornings at 1000-1200.

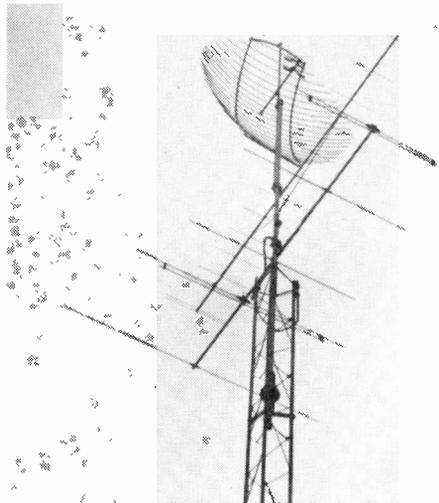The WTFDA (USA DX TV club) bulletin recently came to hand and of particular interest is the description of the Mexican TV network. Two WTFDA members spent some time travelling in Mexico and found an unusual transmitter at Monterrey. This transmitter—XET-6—always seemed to provide an excellent signal at great distances. It is sited atop the high Cerro de la



The top section of Roger's present aerial structure, with the u.h.f. paraboloid atop.

Silla mountain. The inaccessible site is floodlit at night and is visible from afar. The crew ascend for shift duty for one or two week spells, the final part of the journey being on muleback!


ORTF now have regional programming on all three networks between 1820-1840 GMT. For example the Paris region has "Ile de France" whereas the Lille area carries the "Nord Picardie" programme, Reims the "Champagne" programme and so on. This is a very convenient way of identifying transmitting stations.

News Items

China: We understand that the Peking Broadcasting Administration has purchased colour TV equipment from a UK manufacturer for the forthcoming introduction of colour to their TV network. Of the 29 provinces in China 25 have monochrome TV coverage. We understand that the PAL system is to be used. There are apparently 30,000 colour receivers in China.


West Germany: The American Forces Radio and TV Service is to increase its TV coverage in West Germany and to this end a list of new transmitters throughout West Germany has been made available. The transmitters will have powers up to 8kW maximum—several are located at principal transmitting sites.

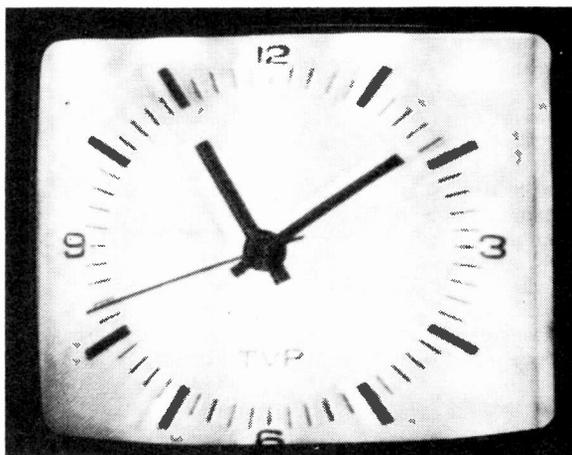West German engineers predict that by 1980 an



TVP (Poland) 1st chain clock.

Courtesy C. Athowe.

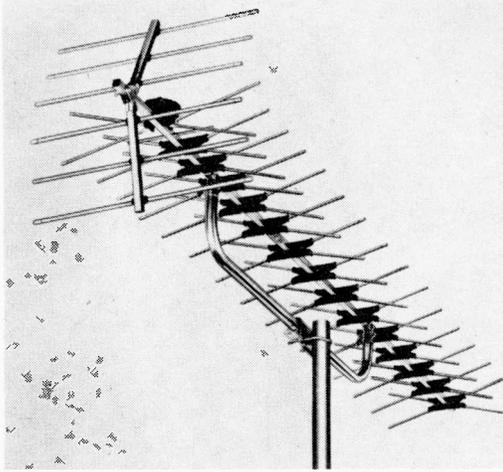

The new Antiference "Extragain" Model XG14.

operational satellite TV system providing up to five channels and operating at 12GHz could be in being, giving coverage to West Germany and other parts of Europe. Will we have to look to the skies for our TV-DX in future?

Canary Islands: The Europese Testbeeldjagers advise that transmission times are as follows—weekdays 1315-1615 and 1745-2400; Saturdays 1515-2400; Sundays 1045-2400. All times GMT. The test card is similar to the TVE mainland type. Apart from the time difference (1 hour) the other way of identifying the ch. E3 Izana transmitter is the caption "TeleCanarias" which follows the end of the satellite-linked "Telediario" programme.

Spain: The Europese Testbeeldjagers also tells us that Santiago TVE-2 is to go u.h.f. within two years, with some joint working for a few months between the present ch. E2 outlet and the new u.h.f. outlet. The only regional programme transmission in Spain originates from the Barcelona area and is known as "Programa Catalán". It is radiated on the last Tuesday of each

New US Forces TV Transmitters in West Germany

Powers range up to 8kW (e.r.p.). 525 lines, 60 fields, 4.5MHz sound-vision spacing, f.m. sound.

Butzbach	E21	Wildflecken	E48
Crailsheim	E21	Stuttgart	E48
Schwabisch Hall	E21	Hanau	E48
Ansbach	E22	Hahn	E50
Bindlach	E27	Heilbronn 1	E51
Erlangen 1	E27	Schwabach 2	E51
Munster	E27	Katterbach	E51
Herzogenrauch	E28	Zirndorf	E52
Gieben	E30	Bad Hersfeld	E53
Furth 1	E30	Illesheim	E53
Erlangen 2	E31	Furth 2	E53
Wertheim	E31	Kirch-Gons	E53
Babenhausen	E32	Kitzingen 2	E54
Friedberg	E32	Heilbronn 2	E55
Neckarsulm	E32	Hohenfels	E56
Bamberg	E39	Budingen	E57
Bad Nauheim	E41	Bitburg	E57
Grafenwohr	E41	Bad Kissingen	E57
Schwabach 1	E42	Nurnburg 2	E57
Kitzingen 1	E44	Fulda	E58
Nurnburg 1	E44	Schweinfurt	E59
Vilseck	E45	Wurzburg 1	E59
Gelnhausen	E46	Wurzburg 2	E60
Amberg	E48		

month from 1700, preceded by the normal test card. Captions to look out for on ch. E4 are "Teatro Catalan" or "Mare Nostrum". Programme language is Catalan.

It is still possible to sight the old TVE test card. Apparently the Madrid TV centre produces a special Spanish programme for Spanish workers in West Germany and Holland. This card precedes the programme and is radiated by a number of West German and Dutch transmitters.

Eire: RTE have plans for a second service, RTE-2. This will be all colour with selections of BBC/IBA programmes and approximately eight hours of locally produced material. Transmitters will be at v.h.f. and u.h.f.

Finland: Seppo J. Pirhonen tells us that the following u.h.f. transmitters are to go into operation: Lapua E24 1000kW, Kuopio E36 600kW, Joutseno E32 600kW, Mikkeli E38 600kW. The latter will be early 1974, the others late 1973. All transmissions will be horizontally polarised.

Wideband Band I Aerials

Following recent articles on wideband Band I arrays we understand that several aerial manufacturers have been approached regarding the supply of the arrays shown. We must stress that these are not available from any UK aerial manufacturer at the moment, there being relatively little demand for such arrays. We are however looking into the possibility of locating a source to supply a complete kit of parts for a wideband 1-3 element array covering 47-66MHz. As soon as there is more definite news we will report further.

From Our Correspondents . . .

It has been what can only be described as a chaotic month for letters. Since taking over this column some 2½ years ago a record monthly number has come in! All have been replied to with the least delay and several interesting items have come to light.

Lothar Scholt (Ziegelroda, GDR) wrote enclosing two photographs. These were ch. E3 test card signals (RETMA with a checkered border). The odd thing is that the signals were 525 lines, 60 fields. They can originate only from station HZ22, Dhahran ch. A2, Saudi Arabia. The signal was noted at 0715 GMT on June 29th and was quite clean. A caption, "Afris", followed at 0720.


Clive Athowe (Norwich) has written about the excellent tropospheric signals in the East Anglian area over the past few weeks. The most spectacular reception was an RTB ch. E45 transmission from the new 500W relay at Brussels!

Tropospherics also feature in a letter from Cliff Dykes (Sutton). Cliff lives in a flat and can use only loft aerials. Despite this he has with a fixed Band I dipole and a log-periodic u.h.f. array received a number of excellent signals including the ch. E33 Ostfriesland transmitter.

John White (Scunthorpe) has also been using the u.h.f. bands—with his Fuba XC391d array—and has received excellent u.h.f. signals from Sweden. He intends to instal a v.h.f. to u.h.f. upconverter shortly to give coverage of Bands I and III.

James Burton-Stewart from Stowe School, Buckingham has triumphed early in his TV-DX career with reception of CLT Luxembourg ch. E21 on EBU bar pattern. A very long log has been sent in by James and by all accounts his aerial system is working well.

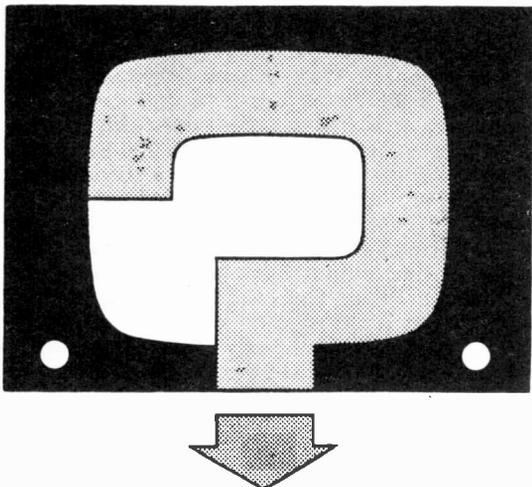Finally Garry Smith comments on an unusual programme seen over TSS. Garry noted on July 14th a programme preceded by a "star" caption. A large picture was then noted of the 0249 card, with a man pointing at the identification area. In his hand was a globe which also had the identification written on it. Does anyone recall seeing this?



YOUR PROBLEMS SOLVED

ULTRA 6632

When the brightness control is turned up the picture balloons and disappears. The line output and boost valves have been replaced, also the e.h.t. tray. This later resulted in much more e.h.t. but the picture is now about two inches in at the sides of the screen all round. The set is fitted with the BRC 950 chassis—T. Singer (Harrow).

There are both three- and five-stick e.h.t. trays for these BRC sets: using the wrong type can cause all kinds of symptoms. Assuming that the type you are using is identical to that originally fitted however the next check should be on the value of the 330k Ω resistor in series with the width control. Also check the line output valve screen grid circuit components—R128 feed resistor (2.2k Ω) and C103 decoupling electrolytic (1 μ F). Further checks if necessary should be the value of the 2.2M Ω resistor (R130) and 1.8M Ω resistor (R131) in the line output valve grid circuit and the 1 μ F electrolytic (C100) which decouples the boost line to the h.t. rail.

EKCO T418

A short occurred in the heater line, blowing the c.r.t. heater. Before this happened the set was operating normally. On replacing the c.r.t. a full raster was obtained but there is no vision signal. The sound is OK. Both vision i.f. valves have been replaced.—K. Jowett (London SE9).

The PCL84 video amplifier valve is inclined to suffer from internal shorts and we suspect that this valve is the cause of your loss of vision. It may be necessary to check the resistors in this stage, also the vision detector diode V7 (CG64H). (Pye 11U series.)

GEC 2018

When the camera traverses a scene on u.h.f. there are two sets of line tearing across the screen. The picture is then perfect and steady until the camera swings again.—G. Younger (Felstead).

There are two extra capacitors in the coupling from the video amplifier to the sync separator on 625 lines, C97 (0.047 μ F) and C98 (0.002 μ F). These could be faulty and should be replaced.

★ Requests for advice in dealing with servicing problems must be accompanied by an 11p postal order (made out to IPC Magazines Ltd.), the query coupon from page 91 and a stamped, addressed envelope. We can deal with only one query at a time. We regret that we cannot supply service sheets or answer queries over the telephone. We cannot provide modifications to circuits published nor comment on alternative ways of using them.

PYE 48

The overall field linearity control is at one end of its travel and it is impossible to fill the screen without excessive adjustment of the top linearity or height control. The picture is then expanded at the top and bottom. If the overall linearity control is set to mid-travel the picture is excessively cramped at the bottom. The PCL85 and ECC82 field timebase valves, the capacitors in the oscillator, linearity and output circuits and most of the resistors in these circuits have been checked or changed.—T. Grower (Norwich).

The field output transformer could be the cause of the trouble, as could the field deflection coils. Embedded in the latter is a thermistor which can give trouble: it can be shorted out as a quick check. (Pye group 67 chassis.)

HMV 2629

The troubles with this set are lack of brightness, test card dicing cramped at the top and on switching off the picture disappears as a small rectangle instead of a dot. The video amplifier and line timebase valves have been replaced. The voltage on the c.r.t. first anode (pin 3) is only 120V which seems to be low.—R. Clarkson (Potters Bar).

The c.r.t. first anode voltage is certainly low. As a quick check remove the existing lead to pin 3 and link pins 3 and 4 (focus). This latter pin usually stands at 400V and this action should restore normal brightness. If it does the cause of the trouble is that the 0.1 μ F capacitor C93 which decouples the first anode feed to the h.t. line via a 2.2k Ω resistor is short-circuit. C93 also affects the spot decay, so replacing it should remove this trouble as well. For the top cramping first adjust the top linearity preset on the extreme left side of the chassis then if necessary check the linearity feedback capacitor C90 which is connected to the anode of the field output pentode. (BRC 950 chassis).

BUSH TV181S

The picture is perfect except for the top two inches or so where vertical lines on the picture pull towards the left and waver a bit. Often a good tap on the cabinet top produces a very brief small picture after which the fault clears, only to return again however. The aerial is in order and there are no signs of ghosting.—R. Evans (Southampton).

Check carefully the soldering of the vertical metal strip to the panel in the vicinity of the EF184 line oscillator valve—poor soldering causes a lot of troubles on this chassis. If all is OK here check the 10 μ F electrolytic 3C31 which smooths the supply to the line oscillator valve.

GEC 2035

We are having difficulty with the channel selector switch. This was removed for cleaning but after re-fitting it only BBC-1 and ITV can be obtained—BBC-2 is absent.—F. Blaise (Birmingham).

The system switch linkage is operated by a large plastic cam at the rear of the v.h.f. tuner. At the tuner end the coupling rod is held in the correct position by means of a pivot and screw which is set so that the system switch changes over to 625 lines when the v.h.f. tuner is in the u.h.f. position.

PYE 11U

The sound is OK but the screen blank. A high-pitched note is present in the background however. All valves in the line output stage have been changed.—G. James (Consett).

We assume that the high-pitched note is line whistle, so there seems to be some sort of line timebase operation. The 0.01 μ F coupling capacitor C87 to the line output valve is inclined to give trouble in this chassis so the first move should be to replace it. If this does not restore results the line output transformer could well be faulty.

MARCONIPHONE 4614

This set works perfectly on v.h.f. but when operating on u.h.f. there is occasionally a broad grey line which rolls from the bottom to the top of the screen, causing distortion of the picture.—R. Smales (Keighley).

The cause of the fault is impaired smoothing. It is evident on 625 lines only since on this system the field frequency is not locked to the mains frequency. Any discrepancy in frequency produces a mild hum bar which on 405 lines is blanked out during the fly-back. Stab a high-voltage electrolytic of about 50 μ F or thereabouts across each of the main electrolytic decouplers—C112, C113, C91 and C41—in turn. If you find that the effect is removed when one of these is bridged you know that the original needs replacement. It is also possible for the effect to be caused by slight heater-cathode leakage in one of the valves, even the PCF805 in the v.h.f. tuner (it acts as an additional i.f. stage on 625). Before going to the expense and trouble of trying out new valves however check the smoothing capacitors. When the fault is not apparent this doesn't mean that the smoothing is adequate, merely that the mains frequency is spot on at 50Hz. (BRC 950 chassis.)

KB WV90

There are two problems. First the picture takes some time to appear. When it does it increases from nothing until it fills the screen. It is dull during this time and when it is full size the screen briefly goes blank before the picture appears normally. Secondly, on switching off the picture reduces to a single bright spot instead of diminishing to nothing.—J. Slater (Barnsley).

The late arrival of the picture is due to a lazy valve in the line output compartment. Check the PY801 and the PL36. The residual spot should not appear if the set is switched off using its own on-off switch (not the wall switch) provided the brightness control is wired correctly. On the chassis as produced the earthy end of the brightness control is returned via a 47k Ω resistor to the neutral side of the on/off switch (not to chassis). Consequently on switching the set off with its own on/off switch the c.r.t. grid is briefly at h.t. potential and the e.h.t. rapidly discharges to prevent spot formation.

MURPHY V310

Could you advise on boosting the c.r.t. (CRM 172) in this receiver which I intend to use as a second set. The raster can be seen only when the brilliance control is turned up two thirds of the way. If it is turned right up the picture disappears. I would also like to replace the LW7 h.t. metal rectifier with a silicon type.—J. Hennesy (Ayr).

Use a 13V booster transformer to boost your c.r.t. heater. Connect the mains side to the on/off switch and the boost side to the c.r.t. heater—having previously disconnected the existing heater leads and taped them together to complete the heater chain. A BY127 silicon rectifier with a 10 or 15 ohm (10W) surge limiter resistor in series can be used to replace the LW7. A new U26 is probably required.

PYE 60

The problem with this set is no line output—with absence of line whistle. All valves in the line output stage have been replaced. A slight crackle is obtained by touching the PY800 top cap but that is all. Removing the PY800 top cap does not produce any results.—B. Harris (Dunstable).

Since you do not mention overheating, the line oscillator seems to be operating. Your other tests indicate that the output stage valves are passing current and that the boost reservoir capacitor is in order. It seems likely therefore that the line output transformer is the cause of the trouble. First however make sure that the scan coils are OK by disconnecting them. If they are faulty the e.h.t. will then return. (Pye group 368 chassis.)

MURPHY V410

Sound is OK and the e.h.t. present but there is no picture or raster. On checking the c.r.t. base voltages I found that a picture appeared when the meter was applied to the cathode (pin 11) but it soon went negative. I checked the components in the cathode circuit but all appear to be in order.—T. Smith (Welwyn Garden City).

Either the c.r.t., the 30FL1 video amplifier valve (V6) or its 10k Ω anode load resistor R37 is faulty.

WEAK CRT

In a recent issue it was stated that to check the condition of the c.r.t. in an old set the brilliance control should be turned up. If the picture then takes on a silvery appearance and details in the white areas of the picture start to disappear the c.r.t. is probably starting to fail. This is the condition I have encountered and I am wondering whether a session with one of the c.r.t. rejuvenators for which you have published details would be worth while.—V. Bartlett (Chelmsford).

We have no doubt that the use of a c.r.t. rejuvenator would improve the results obtained from the c.r.t. in this set. As a quick way of improving picture sparkle however you could do what many service engineers do when they want to revive a weak tube and the condition of the set does not justify fitting a new one. That is to connect a high-wattage resistor of 5 to 10k Ω from the fuse side of the live mains input—say a point on the mains dropper—to the unearthed c.r.t. heater pin. Leave the other pin connected to chassis of course. The extra current supply will boost the tube and extend its life for a while longer without over-running the valves.

McMICHAEL 3011

The trouble with this set is that the top of the picture curves over to the left from time to time with intermittent loss of line hold. By reducing the setting of the contrast control some improvement is obtained.—E. Smith (Poole).

The fault could well be in the aerial, download or plug so these should be checked. If necessary then turn attention to the flywheel line sync circuit, checking the flywheel sync discriminator diodes (MR1/2), their load resistors (R113 and R115, both 330k Ω) and input coupling capacitors (C160 and C162, both 470pF). (GEC 2012 series.)

QUERIES COUPON

This coupon is available until December 17 1973 and must accompany all Queries sent in accordance with the notice on page 89. Don't forget the 11p (inc. VAT) postal order!

TELEVISION DECEMBER 1973

TEST CASE

132

Each month we provide an interesting case of television servicing to exercise your ingenuity. These are not trick questions but are based on actual practical faults.

Q Lack of colour was the symptom on a Ferguson model fitted with the 2000 series dual-standard chassis. Sound was unaffected and the display on monochrome was fully defined.

The receiver was brought into the workshop for detailed tests and much to the amazement of the field technician a picture in perfect colour appeared immediately upon switching on. The receiver was left running for the whole morning and was then switched off for lunch. Switching on again afterwards produced a perfect picture in monochrome—but no colour!

With the circuits active, tests with a multimeter and scope were commenced in the decoder section and after one or two measurements the colour suddenly appeared. It was soon discovered that by applying a meter probe to certain parts of the decoder circuit the colour could be restored. There were also times when the colour would appear straight away on switching on, as during the first test. The intermittency was such that the colour

could sometimes be triggered on by channel changing, by switching the receiver off then on again and by bursts of electrical interference.

Where in the decoder circuit would a fault producing this kind of symptom most likely be, and why was the colour triggered on by electrical disturbances?

See next month's TELEVISION for the solution and for a further item in the Test Case series.

SOLUTION TO TEST CASE 131

Page 43 (last month)

The three tests made by the technician to determine the cause of the intermittent flashes were all associated with the first anode feed to the picture tube. The first test made at this electrode, of voltage, showed that this varied significantly while the flashes were occurring.

Next the first anode decoupling capacitor was disconnected at one side and the varying voltage continued. The third test was of the voltage at the input to the first anode feed resistor (1.2M Ω). This remained constant in spite of the fluctuations at the other side. The 1.2M Ω feed resistor was then replaced and the fault was cleared.

The usual trouble in this area is a shorting decoupling capacitor, but this commonly removes the first anode potential completely. The feed resistor rarely goes open-circuit, though any high-value resistor in a high-voltage circuit is always suspect.

Similar symptoms would have been produced by first anode leakage in the picture tube, but it is generally easier to clear the feed circuits before checking the tube by substitution!

TELEVISION CLASSIFIED ADVERTISEMENTS

Classified advertisements 6p. per word (minimum 12 words). Box No. 20p. Semi-display setting £3.50 per single column inch. Advertisements must be pre-paid and addressed to Classified Advertisement Manager, TELEVISION, IPC Magazines Ltd., Fleetway House, Farringdon Street, London EC4A 4AD. All cheques, postal orders, etc., to be made payable to TELEVISION and crossed "Lloyds Bank Ltd."

AERIALS

GENUINE FULL SIZE
18 element TV aerial
as used by leading
TV companies

FOR ONLY
£2.20
incl. V.A.
+ 35p car



ITV, BBC1 & 2B/W & Colour Guaranteed Perfect Pictures Save £1s. We supply this genuine U.H.F. aerial for only £2.20. can be fitted outside or inside Quality made technically advanced design Precision grid/reflector eliminates ghosting Complete with clamp instructions advice Money Back Refund Wall Caravan Bracket 25p. Low Loss Cable 10p per yard Plug 8p & FREE with order maps & channel reference of all Radio & TV Transmitters. SEND DIRECT TO DEPT. P.T.10 218 Mansfield Rd. Nottingham.

IMPERIAL TRADING (AERIALS) LTD.
the quality Aerial Specialists

SAVE ON COLOUR

Just change your set top or indoor aerial for the Panorama MCA11 and save over £5 of aerial installation cost.

- Aerial cost refund if returned in 7 days.
- Covers all bands present and future.
- TV top, shelf or wall mounting.
- High gain directional design for minimum 'ghosting'.
- ONLY £2.92+25p p & p or send S.A.E. for leaflet.

ELECTRONIC INNOVATIONS,
6 Serpentine Road, Sevenoaks TN13 3XP.

BAINES for High Frequency Aerials

Full range of J Beam Aerials

Parabeam UHF PBM 12 £3.35, PBM 18 £4.30
Multibeams UHF MBM 30 £4.40, MBM 46 £6.90, MBM 70 £12.10, 2MBM 70 £28.40
Stereobeams VHF/FM SBM 1 £2.20, SBM 2 £2.95, SBM 3 £4.40, SBM 4 £4.80, SBM 6 £7.25, PM 3 £2.20. Rotators £23.20 & £29.00, JB 75/300 £1.60
Accessories: SAE please. Co-Ax 4p and 8p
11 Dale Cres, Tupton, Chesterfield S42 6DR
863755

EDUCATIONAL

COLOUR T.V. SERVICING

Be ready for the coming Colour TV boom. Learn the techniques of servicing colour TV sets through new home-study courses specially prepared for the practical TV technician, and approved by leading manufacturer.

Full details from ICS, (D.750A)
Intertext House, London SW8.

COLOUR TELEVISION TRAINING



11 WEEKS' practical and theoretical Colour training course commences Jan. 14th for men with Mono experience. Hours 2 to 5 p.m. Mon. to Friday.

13 WEEKS' (full-time) combined Mono and Colour training course commences Jan. 2nd for men with a good electronics background.

(The above courses are supplementary to the 16 months' full-time course for beginners.)

Prospectus from: London Electronics College, Dept. T.12, 20 Penywern Road, London SW5 9SU. Tel. 01-373 8721.

T.V. Studio Engineer

The Road Transport Industry Training Board has in operation at its Wembley Headquarters, a 3 camera broadcast-quality colour television studio with full telecine and video recording facilities which includes R.C.A. TR 50 and 1" Helical Scan systems. We now wish to appoint an experienced studio engineer to join a small team working on the production of training and educational television programmes.

The applicant should not be less than 24 years of age and have a good working knowledge of the above equipment. Salary will be negotiable depending on qualifications and experience. Three weeks holiday, contributory pension and life assurance scheme.

Please send all relevant personal history stating how the above requirements are met, and quoting reference .335, to:

**Mrs. H. M. Brown, Personnel Manager,
Road Transport Industry Training Board,
Capitol House, Empire Way,
Wembley, Middlesex HA9 0NG.**

FOR SALE

"TELEVISION" COLOUR I.F. Strip. Professionally built, but not aligned. £8.98 Green Hill, High Wycombe, Bucks.

WANTED

NEW BVA valves of popular types, PCL805, PY800/1, PL504, etc. Cash waiting. Bearman, 6 Potters Road, New Barnet. 449/1934-5.

SERVICE SHEETS purchased. HAMILTON RADIO, 47 Bohemia Road, St. Leonards, Sussex.

TOP PRICES PAID for NEW VALVES and TRANSISTORS popular T.V. and Radio types
KENSINGTON SUPPLIES (A)
367 Kensington Street, Bradford 8, Yorkshire.

NEWNES RADIO and TV Servicing books wanted. From 1960-1966, £2.00 paid per copy by return post. Any quantity bought. Bell's Television Services, Albert Place, Harrogate, Yorks. Telephone: 0423 86844.

TELEVISION issues April, May and June 1972. Pay £3 and postage. R. McCoy, 34 Karana Avenue, Grovedale, Victoria, Australia 3221.

SERVICE SHEETS

SERVICE SHEETS

(1925-1973) for Radios, Televisions, Transistors, Radiograms, Car Radios, Tape Recorders, Record Players, etc. with

FREE FAULT FINDING GUIDE

PRICES FROM 5p

Over 10,000 models available.
Catalogue 15p + SAE

Please send stamped addressed envelope with all orders and enquiries.

Hamilton Radio

47 Bohemia Road, St. Leonards,
Sussex. Telephone Hastings 29066.

SERVICE SHEETS, Radio, TV etc. 8,000 models. Catalogue 15p. S.A.E. enquiries. Telray, 11 Maudland Bank, Preston.

A.L.S Service Sheet Service

10 Dryden Chambers, 119 Oxford Street
LONDON W1R 1PA

Please always state
Make & Model Number, and whether TV, AMP, RADIO, TAPE, etc;

SERVICE SHEET SERVICE ONLY 30p Plus large s.a.e.

Lists covering Mono & Colour TVs, Radio, Tape, Record Players, Books, Manuals, Newsletter, etc Only 5p Plus s.a.e.

COMPREHENSIVE COLOUR TELEVISION MANUAL. BY McCOURT Contains Faults & Causes on most British sets. NOW ONLY £2 post paid

"A GUIDE TO TELEVISION ALIGNMENT USING ONLY TRANSMITTED TEST SIGNALS" By B.R.Epton. price 30p plus S.A.E.

We can supply Manuals for most makes of TV both Mono and Colour including Bush, Murphy, B.R.C., Ferguson, H.M.V., Decca, Sony, Sanyo, Hitachi, etc; Most Colour TV require a Manual to cover the large amount of information that is necessary. S.A.E. for quote price and delivery

Please Note
Mail
Order
Only
return service

One title recommended from our now extensive book list.
"SERVICING WITH THE OSCILLOSCOPE" (KING) (1969) 176 pages illustrated PRICE£2 POST PAID
A S.A.E. FOR FULL LIST

OUR STOCKS NOW EXCEED 20000 ITEMS covering 1000s of makes and models of TV, Radio, Amps, Recorders, etc;

SERVICE SHEETS • MANUALS • BOOKS

SERVICE SHEETS 40p plus S.A.E. * SERVICE SHEET CATALOGUE 25p
OVER 12,000 SERVICE SHEETS & MANUALS IN STOCK ON COLOUR/MONO TELEVISIONS
RADIOS, RADIOGRAMS, T/RECORDERS, R/PLAYERS, ETC. S.A.E. WITH ENQUIRIES

* COLOUR TELEVISION SERVICING MANUALS. Prices include postage. *

ALBA TC1525 TC1626 £1.60, TC1717 TC2222 £2.10, TC2022 £2.60, TC2122 TC2126 £4.00...
BRC 2000 £3.75, 3000 3500 8000 8500 £2.10, BUSH CTV174D CTV182S CTV184S CT187CS C
TV192 CTV194 CTV196 CT197C CTV199 CTV1026 CTV1120 CTV1122 CTV1126 CT1226C £3.25...
DECCA CTV19 CTV19G CTV22C CTV22G CTV25 CTV25C CTV2200 CTV2203 CTV2207 CTV2225
CTV2500 CTV2503 CTV2505 CTV2506 CTV2509 CTV2520 £3.75, CS1730 CS1733 CS1910 CS20
30 CS2213 CS2230 CS2520 CS2611 CS2630 30-Series CS2631 £2.60, DER 5705 5706 5707 574
2 £2.10, EKCO All Models £4.50, FERGUSON 3700 3701 3702 £3.75, Colour-Star 3703 3704
3705 3706 3707 3710 3711 3712 3713 3714 £2.10, FERRANTI CT1166 CT1167 £4.50, GEC 2028
2028A 2028B 2029 2029A 2029B 2030 2030A C2040 C2040B C2041 C2041B C2073B C2100 C210
3 C2107 C2110 C2115 £2.10, HMV 2700 2701 2702 £3.75, 2703 2704 2705 2711 £2.10, ITT/KB
CVCS CK500 CK550 CK600 CK701 CK750 Studio-100 £2.60, INVICTA All Models £4.50 each
MARCONIPHONE 4700 4701 4702 £3.75, 4703 4704 4705 4711 4714 £2.10, MURPHY CV1916S
CV1917 CV2011 CV2210D CV2211 CV2212 CV2213 CV2214 CV2215 CV2516C CV2610C CV2611
CV2614 £3.25, PHILIPS G6-0/Std G25K500 G25K501 G25K502 £1.60, G6-S/Std G22K511...
G25K512 £2.60, G26K521 G26K522 G22K523 G22K524 G26K525 G22K532 G22K533/534 £4.00,
PYE All Models £4.50 each, SOBELL 1028 1029 1040 1060 C1100 £2.10, 1028A 1028B 1029A
1029B C1040 C1040B C1060B £2.10, ULTRA 6700 6701 6702 £3.75, 6703 6706 6713/14 £2.10.
Special Offer. 1972 Edition of WORLD RADIO-TV HANDBOOK £1.50 post free, usually £2.80.
NEWNES RADIO & TELEVISION SERVICING books bought & sold (all years) Good price paid.
Send large S.A.E. for FREE booklists and book pamphlets on Radio, Television & Electronics

BELL'S TELEVISION SERVICES

ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844

BOOKS AND PUBLICATIONS

WORLD RADIO TV HANDBOOK 1974, details of virtually all stations (published December), £3.15 inclusive. David McGarva, PO Box 114, Edinburgh EH1 1HP

LADDERS. 'Special offer' 9' 7" closed—24' 7" extended. Unvarnished Timber. £13.20 delivered. Home Sales Ladder Centre (PTT2), Haldane (North) Halesfield (1), Telford, Shropshire. Tel: 0952 586644.

SETS & COMPONENTS

Components Galore. Pack of 500 mixed components, manufacturers' surplus plus one used. Pack includes resistors, carbon and W.W., capacitors various, transistors, diodes, trimmers, potentiometers etc. Send £1 + 10p P. & P. C.W.O. To: Caledonian Components, Strathore Road, Thornton, Fife.

250—New Resistors well assorted ½—2 watts. Carbon—Hi-Stab Oxide etc. £1.00 Post Free. Whitsam Electrical, 33 Drayton Green Road, London W.13.

LARGE SUPPLIER OF SERVICE SHEETS

All at 40p each

(T.V., RADIO, TAPE RECORDERS, RECORD PLAYERS, TRANSISTORS, STEREOGRAMS, RADIOGRAMS, CAR RADIOS)

"PLEASE ENCLOSE LARGE S.A.E. WITH ALL ENQUIRIES & ORDERS"

Otherwise cannot be attended to

(Uncrossed P.O.'s please, original returned if service sheets not available.)

PLEASE NOTE

We operate a "by return of post" service. Any claims for non-delivery should be made within 7-days of posting your order.

C. CARANNA
71 BEAUFORT PARK
LONDON, N.W.11

We have the largest supplies of Service Sheets (strictly by return of post). Please state make and model number alternative.

Free T.V. fault tracing chart or T.V. list on request with order.

Mail order or phone 01-458 4882

EX RENTAL TV's BARGAIN

23" & 19" 3 Channel with U.H.F. Tuner £3.50
19" & 25" Colour from £50.00
19" & 23" tubes guaranteed from £2

All sets complete.

EDWARDS & SONS
103 Goldhawk Road, London W.12
Telephone 743-6996

COLOUR TV's

19" Decca £133
25" Decca £115
25" RBM/Phillips £120
25" Thorn £125

Fully Serviced, one months' guarantee. Delivery & Terms can be arranged. Non-Workers available.

S.A.E. details please.

T.E.S.T. P.O. Box 1,
Kirkham, Preston PR4 2RS.
Telephone 077-48 2796.

For quality Hi-Fi Equipment, records and Colour Television, Visit

HANSPAL'S AUDIONICS

488 Lady Margaret, Southall, 01-578 2258;
54 St. Anns Road, Harrow, 01-863 3400.
24 hours Autophone Service. Marantz, Pioneer, Sansui, Akai, Rotel, Nikko, Lux, Telefunken, Sony, Sanyo, Tandberg, Hitachi, Grundig, Scan-Dyna, KEF, TEAC, National, Quad, Telefunken, Hitachi, Sony and Grundig Colour T.V. Always in stock.

Up to 5 years Colour Tube guaranteed and 1 year Free Servicing and Labour. Late evening: Friday until 7.00 p.m.

EXCELLENT CREDIT FACILITIES

MAINS DROPPERS.

37-31-97-26-168 Ω 50p.
25-35-97-59-30 Ω 50p.
14-26-97-160 Ω 50p.
14-26-97-173 Ω 50p.
15-19-20-70-63-28-63 Ω 50p.
Post free. C.W.O.

Durham Supplies, 367 Kensington Street, Bradford, 8, Yorkshire.

Top 20 Plus Tested TV Valves

PL504	18p	PCL84	10p
PCF801	15p	PCL82	10p
30L15	15p	PFL200	10p
PL36	15p	ECC82	10p
PCL805/85	15p	EH90	10p
30FL1/2	15p	30PL13	15p

Colour Valves Fully Tested

PL509	30p	PY500/A	30p
PL508	30p		

Many others available including Mazda Types.

P. & P. 4p per valve, over 12 23p per valve, orders over £4 post free.

Prompt service.
S.A.E. for free list
Mail order only.

L. & D. COMPONENTS LTD.,
71 Westbury Ave., London N22 6SA.
Tel. 01-888 2701.

CHEAPER TV SETS

405 from 50p. D/S 625 from £2.50.

Colour also available.

Mon./Sat.—9.00 a.m. to 5.30 p.m.

PREMIER TV WAREHOUSE,
Bridge Works, East Farleigh,
Maidstone.

Tel: Maidstone 26007

B.B.C. 2 19" £10.00

3 channel working

S.A.E. brings List of Radio TV components including L.O.P.T.'s transformers, valves, transistors, tubes, capacitors, resistors, tuners etc.

A.J.M. ELECTRONICS

1 Kings Road, East Sheen, S.W.14.
Phone: 876 5033.

MISCELLANEOUS

25" COLOUR TVs

£120 + VAT

Serviced in our workshops
CWO, SORRY, NO CHEQUES

Also 25" wired Colour TVs

£35 + VAT

Most Bush CTV25 and Baird 700 spares

25" colour tubes £20

SECONDHAND COLOUR

Towerton Works, Oxford Road
Stokenchurch, Nr. High Wycombe
Bucks (End of M40)

Telephone 024 026 (Radnage) 3321

QUANTITY TRADE ENQUIRIES
WELCOMED

BRAND NEW 22" and 26" COLOUR TV CABINETS. Slight seconds without backs, all with doors in Dark and Light Teak. Delivered for £7.50. Backs at extra cost, 19" and 25", rebuilt colour tubes £20 & £25 respectively. Demistic Electronics, 44 Bradley Street, Town Centre, Huddersfield, Yorks. HD1 2RF.

UHF TV's. Working. 23" £9 each. Others available. Tel: Hitchin (0462) 54727 Day, Stevenage (0438) 55808 Eves, mentioning Television Magazine.

CABINETS for Television colour receivers Having any difficulty finding a decent cabinet or front control panel contact K. Herr, 36 Hibernia Road, Hounslow, Middx.

ALUMINIUM SHEET to individual sizes or in standard packs, 3p stamp for details. Ramar Constructor Services, 29 Shelbourne Road, Stratford-on-Avon, Warks.

Build the Mullard C.C.T.V. Camera

Kits are now available with comprehensive construction manual

(also available separately at 761p)

Send 5" x 7" S.A.E. for details to

CROFTON ELECTRONICS

15/17 Cambridge Road, Kingston-on-Thames, Surrey KT1 3NG

SCRATCHED FACE!

Expert service for removing and repolishing your scratched tubes, colour and mono chrome. Standard charge £3.85 carriage paid. Cash with order, satisfaction guaranteed. Completed in one week and returned B.R.S.

RETUBE LTD.
North Somercotes, Louth, Lincs.
North Somercotes 300

COLOUR TELEVISION SERVICE MANUALS

(PRICES INCLUDE POST & PACKING)

ALBA		CS2211	£2.60	CT1167	£2.60	CK750	£2.60	G26K526	£4.00
TC1525	£1.60	CS2213	£2.60			CK822	£2.60	G26K527	£4.00
TC1626	£1.60	CS2220	£3.75	FERGUSON		Studio 100	£2.60	G22K532	£4.00
TC1717	£2.10	CS2225	£3.75	3700	£3.75	Colourscene 2.60		G22K533	£4.00
CS1919	£3.25	CS2227	£3.75	3701	£3.75			G22K534	£4.00
TCS2022	£2.60	CS2230	£2.60	Colour-star	£1.60	INVICTA		G22K536	£4.00
TC2122	£4.00	CS2500	£3.75	3703	£1.60	CT7050	£2.60	G22K537	£4.00
TC2126	£4.00	CS2520	£3.75	3704	£1.60	CT7051	£2.60		
TC2222	£2.10	CS2611	£2.60	3705	£1.60	CT7051/G	£2.60	PYE	
8000 series	£2.10	CS2612	£2.60	3706	£1.60	CT7051/L	£2.60	691 series	£2.60
		CS2630	£2.60	3707	£1.60	CT7051/T	£2.60	693 series	£2.60
BRC/TCE		30 series	£2.60	3710	£2.10	CT7052	£2.60	697 series	£2.60
2000 series	£3.75	CS2631	£2.60	3711	£2.10	CT7053	£2.60	CT70	£2.60
3000 "	£1.60	DEFIANT		3712	£2.10	CT7056	£2.60	CT71	£2.60
3500 "	£2.10	2001	£3.25	3713	£2.10	CT7056/1	£2.60	CT72	£2.60
8000 "	£2.10	2201	£3.25	3714	£2.10	CT7056/2	£2.60	CT73	£2.60
8500 "	£2.10	2202	£3.25	3717	£2.10			CT78	£2.60
BAIRD		DE R		GRANADA		MARCONI		CT79	£2.60
8741	£1.60	5705	£1.60	GC25-IT2	£1.60	4701	£3.75	CT152	£2.60
		5706	£1.60	GEC		4702	£3.75	CT153	£2.60
BUSH		5707	£1.60	2028	£2.10	4703	£1.60	CT154/W	£2.60
CTV182S	£3.25	5742	£2.10	2028A	£2.10	4704	£1.60	CT154/T	£2.60
CTV184S	£3.25	DYNATRON		2028B	£2.10	4705	£1.60	CT201	£2.60
CT187CS	£3.25	CTV1	£2.60	2029	£2.10	4711	£2.10	CT202	£2.60
CTV192	£3.25	CTV1CH	£2.60	2029A	£2.10	4714	£2.10	CT203	£2.60
CTV194	£3.25	CTV2	£2.60	2029B	£2.10	MASTERADIO		CT203/1	£2.60
CTV196	£3.25	CTV3	£2.60	2029B	£2.10	4030A	£2.10	CT204	£2.60
CT197C	£3.25	CTV4	£2.60	2030	£2.10	MURPHY		CT205	£2.60
CTV199	£3.25	CTV5	£2.60	2030A	£2.10	CV1916S	£3.25	CT4212/H	£2.60
CTV1026	£3.25	CTV6	£2.60	C2040	£2.10	CV1917	£3.25	RGD	
CTV1120	£3.25	CTV7	£2.60	C2040B	£2.10	CV2011	£3.25	CR20	£2.60
CTV1122	£3.25	CTV8	£2.60	C2041	£2.10	CV2211S	£3.25	CR22	£2.60
CTV1126	£3.25	EKCO		C2041B	£2.10	CV2212	£3.25	CR26	£2.60
CT1226C	£3.25	CT102	£2.60	C2073B	£2.10	CV2213	£3.25	SOBELL	
A823A	£3.25	CT103	£2.60	C2100	£2.10	CV2214	£3.25	1028	£2.10
A823AV	£3.25	CT104	£2.60	C2103	£2.10	CV2215	£3.25	1028A	£2.10
DECCA		CT105	£2.60	C2107	£2.10	CV2516CS	£3.25	1029	£2.10
CTV19	£3.75	CT106	£2.60	C2110	£2.10	CV2610C	£3.25	1029A	£2.10
CTV19G	£3.75	CT107	£2.60	C2115	£2.10	CV2611C	£3.25	C1040	£2.10
CTV22C	£3.75	CT108	£2.60	HMV		CV2612C	£3.25	C1040B	£2.10
CTV22G	£3.75	CT109	£2.60	2700	£3.75	CV2614	£3.25	C1060	£2.10
CTV25	£3.75	CT110	£2.60	2701	£3.75	PHILIPS		C1060B	£2.10
CTV25C	£3.75	CT111	£2.60	2703	£1.60	G6 D/Std	£1.60	C1100	£2.10
CTV2200	£3.75	CT112	£2.60	2704	£1.60	G6 S/Std	£2.60	STELLA	
CTV22C3	£3.75	CT121/W	£2.60	2705	£1.60	G8 series	£4.00	ST2211	£1.60
CTV2207	£3.75	CT121/T	£2.60	2711	£2.10	G25K500	£1.60	ST2500	£1.60
CTV2225	£3.75	CT122	£2.60	2714	£2.10	G25K501	£1.60		
CTV2500	£3.75	CT122/T	£2.60	2717	£2.10	G25K502	£1.60	ULTRA	
CTV2503	£3.75	CT252	£2.60	ITT/KB		G22K503	£1.60	6700	£3.75
CTV2505	£3.75	CT252/1	£2.60	CVC1	£2.60	G22K511	£2.60	6701	£3.75
CTV2506	£3.75	CT253	£2.60	CVC2	£2.60	G25K512	£2.60	6702	£3.75
CTV2509	£3.75	CT253/1	£2.60	CVC5	£2.60	G26K513	£2.60	6703	£1.60
CTV2520	£3.75	CT254	£2.60	CK403	£2.60	G22K520	£4.00	6704	£1.60
Bradford	£2.60	CT255	£2.60	CK405	£2.60	G26K521	£4.00	6705	£1.60
CS1730	£2.60	CT255/1	£2.60	CK500	£2.60	G26K522	£4.00	6706	£1.60
CS1733	£2.60	CT255/2	£2.60	CK550	£2.60	G22K523	£4.00	6710	£2.10
CS1830	£2.60	FERRANTI		CK600	£2.60	G22K524	£4.00	6713	£2.10
CS1910	£2.60	CT1166	£2.60	CK701	£2.60	G26K525	£4.00	6714	£2.10
CS2030	£2.60								

BELL'S TELEVISION SERVICES

ALBERT PLACE, HARROGATE, YORKSHIRE. Telephone 0423-86844

COVENTRY COLOUR
25" COLOUR TVs
 Complete with matching teak stand
£120 + VAT
 Fully reconditioned
 Cabinets refinished
 Also non-workers at
 various prices

COLOURCARE
 67 Earlsdon Avenue South
 COVENTRY (0203) 79400

QUANTITY TRADE ENQUIRIES
 WELCOMED

AERIAL BOOSTERS—£3.25
 We make three types of Aerial Boosters:
**B45—UHF 625, B12—VHF 405, B11—VHF
 RADIO**

VALVE BARGAINS
 Any 5—50p, 10—75p, 50—£3.30:—
 ECC82, ECL80, EB9, EBF8, EF80,
 EF85, EF183, EF184, EY80, PCC84,
 PCC89, PCC189, PC97, PCF80, PCF86,
 PCF805, PCF808, PCL82, PCL83, PCL84,
 PCF85, PFL200, PL36, PL81, PL504,
 PY33, PY82, PY800, PY801, 30L15,
 1E990

19" UHF/VHF (BBC2)—£6.00
 Thorn-850 or Pye, with set of spare
 valves. Carriage £2.00 (Untested).

100 MIXED RESISTORS—65p
 1 to 2 watt—10 ohms to above 1m-ohms
 (our choice) 100 mixed Capacitors up
 to 500MFD—£1.10 (our choice).

BARGAIN PARTS
 Transistor UHF Tuners—£2.00, 500K-
 ohms V/C with Switch—20p, 50 mixed
 Tuner Valves—£2.25, Brand New Trans-
 istors: BF115, BF173, BC171, BC153,
 BC133, BC113, BC117, BC115, BA102,
 BA129. All 10p each
 All prices include V.A.T. p. & p. 10p
 per order. Money back refund. S.A.E.
 for leaflets.

**ELECTRONIC MAILORDER
 (BURY) LTD.**
 62 Bridge St., Ramsbottom, Bury,
 Lancs. Tel. Rams 3036

**REBUILT T.V. TUBES
 FOR MEN OF VISION**

Current types			
17"	£4.00	21"	£5.00
19"	£4.00	23"	£5.00
Panorama & Ringuard types			
19"	£6.00	23"	£8.00
Twin panel			
19"	£7.50		

Cash or P.O. with order, no C.O.D.
 Carriage 75p in England, Scotland, Wales.
 Add £1.25 for carriage Northern Ireland.
 For all enquiries please send S.A.E.
 Each tube fitted with new electron gun
 assembly. Fully guaranteed for two years
 against any fault except breakage.

k.s.t. Ltd.
 Providence Mills, Viaduct St., Stanningly,
 Nr. Leeds, Yorks. Tel. Pudsey 78177

SOUTHERN VALVE CO. P.O. Box 144
 BARNET, HERTS.

All new and boxed, Mazda & Mullard wherever possible. Lists sae. Mail order only

AZ31 62p	EZ40/1 40p	PL81A 48p	U801 90p	30PL13 75p
DY86/7 34p	EZ80 35p	PL82 37p	5Y3 35p	30PL14 80p
DY802 40p	EZ81 25p	PL83 45p	5Z4 35p	30PL15 80p
EB91 15p	GY501 75p	PL84 45p	6J30L2 60p	30P4MR 88p
ECC81 34p	GZ30 40p	PL500 58p	6AT6 30p	35W4 35p
ECC82 25p	PC86 46p	PL504 70p	6BW7 60p	50CD6G £1.25
ECC83 25p	PC88 46p	PL508 70p	6CD6G 80p	ETC., ETC.
ECC85 36p	PC97 38p	PL509 £1.40	6F24/5 60p	
ECC88 45p	PC900 45p	PL802 85p	6F28 60p	
ECH42 70p	PCC84 33p	PL805 78p	6K7.8 35p	Service & Civility.
ECH81 34p	PCC85 35p	PY32/3 47p	6V6 35p	The above types,
ECH84 50p	PCC88 60p	PY81 31p	6X4 30p	and many others,
ECL80 40p	PCC89 45p	PY88 33p	6X5 35p	are in stock at
ECL82 45p	PCC189 48p	PY800 31p	9D7 40p	time of going to
ECL83 40p	PCF80(L) 28p	PY801 31p	10C2 75p	press.
ECL86 40p	PCF80(Br) 38p	PY500 80p	10F1 45p	These are new
EF80 24p	PCF82 50p	UBF89 35p	10P13 70p	lower prices,
EF85 36p	PCF86 48p	UCC85 40p	12BA6 40p	including V.A.T.
EF86 50p	PCF200 45p	UCH42 50p	20L1 80p	at 10%.
EF89 30p	PCF801 48p	UCH81 40p	20P3 80p	Transistor lists
EF183 32p	PCF802 45p	UCL82 40p	20P4 80p	s.a.e.
EF184 32p	PCF805 55p	UCL83 50p	20P5 20p	All valves new
EH90 45p	PCF806 55p	UF41 50p	30C1 38p	and boxed but
EL34 54p	PCF808 50p	UF85 35p	30C15 70p	we cannot always
EL41 50p	PCH200 55p	UF89 35p	30C18 55p	guarantee any
EL42 47p	PCL82 32p	UL41 55p	30F5 75p	specific make.
EL84 30p	PCL83 45p	UL84 42p	30FL1 50p	Postage: 3p per
EL86 38p	PCL84 32p	UY41 35p	30FL2 50p	valve / post free
EL90/1 40p	PCL85 40p	UY85 30p	30L1 33p	over £2.00.
EL95 40p	PCL805 40p	U25 62p	30L15 75p	Tel. (Office):
EM80/1 40p	PCL86 32p	U26 60p	30L17 70p	440 8641
EM84 40p	PFL200 55p	U191 60p	30P12 70p	Closed Thursday
EY51 45p	PL36 52p	U193 31p	30P19 70p	& Saturday
EY86/7 35p	PL81 45p	U404 40p	30PL1 60p	afternoons.

If you have difficulty in obtaining
TELEVISION

Please place a regular order with
 your newsagent or send 1 year's
 subscription (£2.65) to:
**Subscription Department, Television, Tower
 House, Southampton St., London, WC2E 9QX**

Registration London 53626

PHILIP H. BEARMAN
 (VALVE SPECIALISTS) SUPPLIERS TO
 H.M. GOVT. Etc.

NEW valves by Mullard, Mazda, Telefunken etc.,
 IMMEDIATE POSTAL DESPATCH, LISTS S.A.E., DISCOUNT PRICE

PRICES FROM 1.4.1973 (INCL. V.A.T.)

DY86/7 33p	PC88 61p	PCL86 53p	6/30L2 80p	30PL 13/4 95p
DY802 37p	PCF80 43p	PL36 70p	6BW7 66p	30PL 15 95p
ECC81 40p	PCF801 53p	PL84 53p	6F23 85p	NOTE:
ECC82 37p	PCF802 55p	PL500/4 70p	6F28 60p	PRICES ARE
ECL80 43p	PCF805 73p	PY81 40p	20L1 88p	TO NEAREST
EF80 37p	PCF808 70p	PY800 40p	20P4 88p	NEW PENNY
EF183 49p	PCL82 41p	PY801 40p	30C15 84p	QUANTITY
EF184 49p	PCL83 53p	U25 80p	30FL1/2 60p	PRICES ARE
EH90 46p	PCL84 49p	U26 80p	30L15 84p	LOWER.
EY51 60p	PCL85 53p	U191 80p	30L17 84p	Enquiries welcomed
EY86/7 33p	PCL805 40p	U193 40p	30P12 84p	BF100-127 with
GZ34 63p	PCL805 (non BVA) 48p	U251 83p	30PL1 66p	10W res. 16p

**POST FREE OVER £3, BELOW THIS add 4p per valve +
 PLENTY OF OTHER TYPES AVAILABLE. 3p for subsequent ones**

Large PCF80 30p. Sorry, no X78, X79 but EQUIVS, 12A48 & 10C1
 See separate Component, CRT and Transistor Lists. Many obsolete types available

(Adjacent to Post Office) **6 POTTERS RD., NEW BARNET
 HERTS. Tel: 449/1934-5 any time.**

Local Agents: MANOR SUPPLIES, 172 WEST END LANE, LONDON NW6
 Tel: 794/8751. (Near West Hampstead Tube Station)

PHILIP H. BEARMAN, 6 POTTERS RD., NEW BARNET, HERTS.

One of the finest range of new and makers rebuilt tubes in the country; every tube is tested before it leaves the premises. Delivery usually ex stock and sent securely packed daily. Commonwealth deliveries arranged.

FOR EXAMPLE: NEW TUBES TWO-YEAR GUARANTEE

			Carriage
CME1702, AW43-80, CRM173, MW43-80, MW43-69, CRM172, AW43-88, AW43-89, CME1705, CME1703, C17AF	17"	£6.46	+ 60p
CME1903, CME1902, CME1901, AW47-90, AW47-91, A47-14W, C19AH	19"	£7.56	+ 66p
CME2101, AW53-88, AW53-89, CRM211, CRM212, MW53-20, MW53-80, CME2104	21"	£8.66	+ 71p
CME2303, CME2301, AW59-90, AW59-91, A59-15W, CME2308	23"	£10.45	+ 71p

Rebuilt Tubes:

CME 1908 } £6.05	CME2308 } £8.25
" 1903 } £6.05	" 2303 } £8.25
AW47-91 } £6.05	AW59/91 } £8.25
A47-14W } £6.05	A59/15W } £8.25

NEW MULLARD A56/120X £49.50
A66/120X £57.20
" " One Year Guarantee
" " Four Year Guarantee
EXTENSION £7.70 extra
Incl. V.A.T. Cge / Ins £1.65

MAKERS COLOUR TUBES

A49/191X (A4911 & A49 120X)	£53.90 + £1.65 cge/ins.
A55/14X & A56/120X	£58.30 + " "
A63/200X (A63.11X & 120X)	£62.70 + " "
A67/120X	£64.90 + " "

NOTE: Above prices from 1st April 1973 include 10% V.A.T.

TELEPHONE: 01-449 1934/5. ALL ENQUIRIES SAE PLEASE

ADD 50p FOR SHORT SEA JOURNEYS

NEW TUBES

*TSD282 (TSD217)	£13.75
MW31-74	£3.30
TSD290/CME1201	£10.78
A31/120W-CME1220	£10.78
*13BP4	£15.40
MW36/24 & 44	£5.23
CME1601	£10.40
CME1602	£11.00
CME1713	£13.20
CME1906	£12.10
A47-13W }	
A47-11W & 26W	£9.35
A50-120W/CME2013	£11.55
†CME2306 }	£14.85
A59-13W }	
A59-11W & 25 or 23W	£12.65
CME2413/A61, 120W	£14.30

Two year Guarantee except TSD282 and 13BP4 1 year.


Please enquire regarding availability of rebuilds. Also seconds in colour tubes. Telephone enquiries welcomed.

MONO QUANTITY DISCOUNTS IN CERTAIN CASES

OPEN SATURDAY MORNINGS

CLOSED THURSDAY AFTERNOONS

REBUILT TUBES!

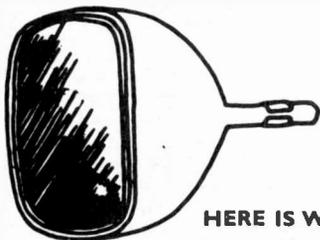

YOU'RE
SAFE
WHEN YOU
BUY FROM
RE-VIEW!

HERE IS WHAT YOU PAY:

	Mono	Rimband & Twin Panel	Colour
15-17"	£5.00	19" £7.00	19" £25.00
19"	£5.50	23" £9.00	22" £27.50
21"	£6.50	24" £10.00	25" £30.00
23"	£7.50		26" £32.50

Carriage 75p

Exchange Basis
(carriage-ins. £1.50)

INC. VAT


Cash or cheque with order, or cash on delivery

- ★ Each tube is rebuilt with a completely new gun assembly and the correct voltage heater.
- ★ Each tube comes to you with a guarantee card covering it for Mono Tubes 2 years, Colour Tubes 1 year, against all but breakage.
- ★ Each tube is insured on the journey.
- ★ Each tube is rebuilt with experience and know-how. We were amongst the very first to pioneer the technique of rebuilding television tubes.

RE-VIEW ELECTRONIC TUBES

237 London Road, West Croydon, Surrey
Tel. 01-689 7735

THE UM4 "COLOURBOOSTER" UHF/625 LINE

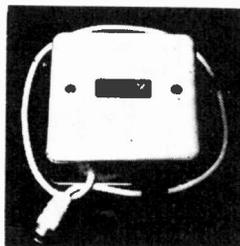

CAN PRODUCE
REMARKABLE
IMPROVEMENTS IN
COLOUR AND
PICTURE QUALITY
IN FRINGE OR
DIFFICULT AREAS
WITH SIGNIFICANT
REDUCTION IN
NOISE (SNOW).

HIGH GAIN—VERY LOW NOISE
FITTED FLY LEAD—INSTALLED IN SECONDS
HIGHEST QUALITY COMPONENTS
IVORY PLASTIC CASE 3½ x 3½ x 1½ CORK BASE
CHANNELS: Group A, Red code 21-33
Group B, Yellow code 39-51
Group C-D, Green code 52-68

EQUALLY SUITABLE FOR BLACK AND WHITE

Also the M4 DUAL BAND VHF UNIT

BOOSTS ALL BAND III and ANY SPECIFIED
BAND I CHANNEL SIMULTANEOUSLY
NOMINAL GAIN 16-18 DB BOTH BANDS

PRICES BOTH TYPES:

Battery model £4.17 Mains version £6.50
Including VAT postage 13p

TRANSISTOR DEVICES LIMITED
6 ORCHARD GDNS., TEIGNMOUTH, DEVON

Telephone: Teignmouth 4757

WITWORTH TRANSFORMERS

MONOCHROME TV Line out-put transformers (Discounts to Trade)

ALL ONE PRICE £5.17 EACH V.A.T. & CARRIAGE PAID

BUSH

TUG versions	TV125
TV75 or C	TV125U
TV76 or C	TV128
TV77	TV134
TV78	TV135
TV79	TV135R
TV83	TV138
TV84	TV138R
TV85	TV139
TV86	TV141
	TV145
	TV148
TV91	TV151
TV92	TV165
TV93	TV166
TV94	TV171
TV95 or C	TV175
TV96 or C	TV176
TV97	TV178
TV98C	TV1815
TV99 or C	183
TV100C	183D
TV101C	183S
TV102C	183S
TV103 or D	183SS
TV105 or D or R	185S
TV106	186
TV107	186D
TV108	186S
TV109	186SS
TV112C	191S
TV113	191D
TV115 or C or R	193S
TV118	193D
TV123	
TV124	

From model TV123 to TV139 there have been two types of transformer fitted. One has pitch overwind, the other has plastic moulded overwind.

BAIRD

600	628	662	674
602	630	663	675
604	632	664	676
606	640	665	677
608	642	666	681
610	644	667	682
612	646	668	683
622	648	669	685
624	652	671	687
625	653	672	688
626	661	673	

Please quote part No. normally found on tx. base plate; 4121, 4123, 4140 or 4142.

DECCA

DR20	DR34	DR71	DR505
DR21	DM35	DR95	DR606
DR23	DM36	DR100	666TV-SRG
DR24	DM39C	DR101	777TV-SRG
DR29	DR41	DR121	
DR30	DM45	DR122	MS1700
DM30	DR49C	DR123	MS2000
DR31	DM55	DR202	MS2001
DR32	DM56	DR303	MS2400
DR33	DR61	DR404	MS2401

SOBELL

T24	ST284 or ds	1010dst	1033
SC24	ST285 or ds	1012	1038
TPS173	ST286 or ds	1013	1039
TPS180	ST287 or ds	1014	1047
ST195 or ds	ST288 ds	1018	1048
ST196 or ds	ST290ds	1019	1057
ST197ds	ST291ds	1020	1058
SC270	ST297ds	1021	1063
T278	1000ds	1022	1064
ST282	1002ds	1023	1065
ST283	1005ds	1032	1066

MURPHY

V430	V520
V310A	V430C
V310AD	V430D
V310AL	V430K
V310CA	V440
V320	V440D
V330 or D	V440K
V330F or L	V470
V410	V480
V410C	V490
V410K	V500
V420	V510
V420K	V519

*Two types fitted. One has pitch overwind, the other has plastic moulded overwind. Please state which type required as they are not interchangeable.

PHILIPS

23TG111a	G19T210	G23T210
23TG113a	G19T211	G23T211
23TG121a	G19T212	G23T212
23TG122a	G19T213	G24T230
23TG131a	G19T214	G24T232
23TG142a	G19T215	G24T236
23TG152a	G20T230	G24T238
23TG153a	G20T232	G24T300
23TG156a	G20T236	G24T301
23TG164a	G20T238	G24T302
23TG170a	G20T300	G24T306
23TG171a	G20T301	G24T307
23TG173a	G20T302	G24T308
23TG175a	G20T306	
23TG176a	G20T307	
23FG632	G20T308	

GEC

2000	2015	2022	2043	2064
2001	2017	2023	2044	2065
2010	2018	2032	2047	2066
2012	2019	2033	2048	2082
2013	2020	2038	2063	2083
2014	2021	2039		

PYE

11u Series	
12u	
13u	State Pt. No.
14u	required
15u	AL21003 or
20u	772494

V700 or A or D	
V710 or A or D	State Pt. No.
V720	required—
V830A or D or	772444 or
LBA	771935

FERGUSON, ULTRA, MARCONI, H.M.V. ALL MODELS IN STOCK.

(BRC, Jellypots).

ALBA, COSSOR, EKCO, FERRANTI, K.B., PYE. ALL MODELS IN STOCK.

E.H.T. RECTIFIER TRAYS

THORN B.R.C. MONOCHROME	ORDER Ref.	
980, 981, 982	RT1	£3.30
911, 950/1, 960	RT2	£3.60
950/2, 1400-5 stick	RT3	£3.90
1400 Portable-3 stick	RT3A	£3.60
1500 20" 3 stick	RT4	£3.60
1500 24" 5 stick	RT5	£3.90
1580 Portable-2 stick	RT16	£3.50
1590, 1591	RT17	£1.30

MAKE	CHASSIS COLOUR	
DECCA	CTV19, CTV25	£6.30
DECCA	CS1910, CS2213	£6.30
DECCA	CS1730	£5.80
GEC	Dual & Single std.	£6.10
ITT-KB	CVC-1, 2, 3	£6.30
PHILIPS	G8	£6.30
PYE	691, 692, 693, 697	£6.10
PYE	713	£6.40
BUSH MURPHY	Single std plug-in	£6.30
BUSH MURPHY	Dual standard	£8.40
THORN BRC	2000	£7.30
THORN BRC	3000	£6.60
THORN BRC	8000	£4.10
THORN BRC	8500	£4.20

COLOUR TV Line out-put transformers

THORN (BRC) 2000 Chassis Scan O/P Tx. EHT O/P Tx. 3000 Chassis Scan O/P Tx. EHT O/P Tx. 8000 Chassis 8500 Chassis All £6.80 ea.	BUSH CTV25 Mk. 1 & 2 £10.10 ea. CTV25 Mk.3 CTV162 £7.90 ea. CTV167 Mk. 1 & 2 £10.10 ea. 8000 Chassis CTV167 Mk.3 CTV174D CTV182S CTV184S CTV187CS CTV194S CTV197C CTV199S £7.10 ea.	EKCO CT102 CT104 £11.70 ea. CT103 CT105 CT106 CT107 CT108 CT109 CT111 CT110 CT121 & T CT122 £8.90 ea.	PYE CT70 CT71 £11.70 ea. CT72 CT73 CT78 CT79 CT152 CT153 CT154 £8.90 ea.	DECCA CTV19 Valve Rec. CTV25 Overwind 'Coil' £5.10 ea. Primary Coil £3.70 ea. CTV19 D/S Tripler CTV25 CTV25 S/S Tripler CS1730 £7.80 ea. CS1910 CS2213 £7.10 ea.	PHILIPS G6 Chassis D/S G6 S/S £8.70 ea. G8 Chassis £7.90 ea.	MURPHY CV1912 CV2510 Mk.3 CV1916S CV2511 Mk.3 CV2210 CV2516S CV2212 CV2610 CV2213 CV2611 CV2214 CV2614 CV2510 Mk. 1 & 2 CV2511 Mk. 1 & 2 £10.10 ea.
---	---	--	--	---	--	---

Every item listed stocked. Most newer and older models in stock. S.A.E. for quotation For by-return service contact your nearest depot. Callers welcome.

Tidman Mail Order Ltd., Dept. NA.
236 Sandycombe Road,
Richmond, Surrey.
London: 01-948 3702

Hamond Components (Midland) Ltd., Dept. NA.
89 Meriden Street,
Birmingham 5.
Birmingham: 021-643 2148

NO HIDDEN EXTRAS - PRICES INCLUDE V.A.T. and CARRIAGE

130 LOVEFACE

Which of these 165 career opportunities could earn you £10... £15...even £30 extra a week?

In a job you really enjoy

How to qualify in your spare time for a better job

Make yourself *worth* more and you'll earn more. It's as simple as that. There are always plenty of people to do the routine work - but, right now, key jobs are going begging for lack of suitably qualified men to fill them. *The basic qualification is technical know-how.* When you've got that, you're in demand - out in front.

Are you ambitious - willing to set aside about 60 minutes a day for home study? If you are, B.I.E.T. can give you the technical knowledge you need - change your entire future prospects.

It's easier than you think...

Make no mistake about it - you *could* do it. Most people have unused ability. A low-cost B.I.E.T. course helps you discover this hidden ability - makes learning enjoyable and so much easier than it used to be. The B.I.E.T. simplified study system gets results fast.

We've successfully trained thousands of men at home - equipped them for higher pay and better, more satisfying jobs, steered them safely through City and Guilds examinations - enabled many of them to put letters after their name.

With the help of B.I.E.T., you too could soon be on your way to better things.

OTHERS HAVE DONE IT - SO CAN YOU

Many of the successful B.I.E.T. students who get a recognised qualification never thought they had the brains to do it. But you don't need outstanding brain-power or talent - not even any special education. With enthusiasm, a little determination and a B.I.E.T. home training, ordinary, average ability will see you through. We've proved it over and over - *thousands* of times, in fact!

BEST VALUE FOR MONEY HE EVER OBTAINED.

"Yesterday I received a letter from the Institution informing that my application for Associate Membership had been approved. I can honestly say that this has been the best value for money I have ever obtained - a view echoed by two colleagues who recently commenced the course" - *Student D.I.B., Yorks.*

HE GOT OUT OF A BAD JOB INTO ONE HE LOVED.

"Completing your course, meant going from a job I detested to a job that I love, with unlimited prospects" - *Student J.A.O., Dublin.*

HE MADE FOUR TIMES AS MUCH MONEY.

"My training with B.I.E.T. quickly changed my earning capacity and in the next few years, my earnings increased fourfold" - *Student C.C.P., Bucks.*

FREE 76-PAGE BOOK

can put you on the road to success through a B.I.E.T. Home Study Course. It's yours for the asking, without obligation. Post coupon for your FREE COPY TODAY!



ACT NOW - DISCOVER FOR YOURSELF

It costs no more than a stamp to find out how we can help you. Tick the subject that interests you. Then post the coupon (or write). We'll send you an interesting 76-page book that will open up for you a whole new world of opportunity - and it's FREE.

B.I.E.T., Aldermaston Court, Reading RG7 4PF.

Tick or state subject of interest. Post to address below.

- | | | |
|---|---|--|
| <p>MECHANICAL
Society of Engineers—
A.M.S.E. (Mech.) <input type="checkbox"/>
Institute of Engineers & Technicians (A.M.I.E.) <input type="checkbox"/>
CITY & GUILDS Gen. Mech. Eng. Maintenance Eng. Welding Gen. Diesel Eng. Sheet Metal Work <input type="checkbox"/>
Eng. Inspection Eng. Metallurgy <input type="checkbox"/></p> <p>ELECTRICAL & ELECTRONIC
Society of Engineers—
A.M.S.E. (Elec.) <input type="checkbox"/>
CITY & GUILDS Gen. Electrical Engineering <input type="checkbox"/>
Electrical Installations <input type="checkbox"/>
Electrical Maths <input type="checkbox"/>
Computer Electronics <input type="checkbox"/>
Electronic Eng. Practical Radio & Electronics (with kit) <input type="checkbox"/></p> <p>MANAGEMENT & PRODUCTION
Institute of Cost & Management <input type="checkbox"/>
Accountants <input type="checkbox"/>
Computer Programming <input type="checkbox"/>
Works M'ment. <input type="checkbox"/>
Work Study <input type="checkbox"/>
Gen. Production Eng. <input type="checkbox"/>
Estimating & Planning <input type="checkbox"/>
Storekeeping <input type="checkbox"/>
Management <input type="checkbox"/>
Skills <input type="checkbox"/>
Quality Control <input type="checkbox"/></p> | <p>DRAUGHTSMANSHIP
Institute of Engineering Designers (A.M.I.E.D.) <input type="checkbox"/>
General Draughtsmanship <input type="checkbox"/>
Elec. Draughtsmanship <input type="checkbox"/>
Architectural Draughtsmanship <input type="checkbox"/>
Technical Drawing <input type="checkbox"/></p> <p>RADIO & TELECOMMUNICATIONS
CITY & GUILDS, Radio, TV/ Electronics <input type="checkbox"/>
CITY & GUILDS Telecoms. <input type="checkbox"/>
Gen. Radio & TV Eng. <input type="checkbox"/>
Radio Amateurs Exam <input type="checkbox"/>
Radio Servicing <input type="checkbox"/>
TV Servicing <input type="checkbox"/>
Colour TV <input type="checkbox"/></p> <p>AUTOMOBILE & AERONAUTICAL
Institute of the Motor Industry <input type="checkbox"/>
A.M.I. <input type="checkbox"/>
M.A.A./I.M.I. <input type="checkbox"/>
CITY & GUILDS Auto Eng. <input type="checkbox"/>
Gen. Auto Eng. <input type="checkbox"/>
Motor Mechanics <input type="checkbox"/>
Auto Diesel Eng. <input type="checkbox"/>
Garage M'ment. <input type="checkbox"/>
ARB Aero Engineering Certs. <input type="checkbox"/>
Gen. Aero Eng. <input type="checkbox"/></p> <p>CONSTRUCTIONAL
Society of Engineers—
A.M.S.E. (Civ.) <input type="checkbox"/>
Institute of Building—L.I.O.B. <input type="checkbox"/></p> | <p>A.B.T. Clerk of Works <input type="checkbox"/>
Construction Surveyors Institute—L.C.S.I. <input type="checkbox"/>
CITY & GUILDS General Building (all branches) <input type="checkbox"/>
Heating & Vent. Inst. Clerk of Works <input type="checkbox"/>
Site Surveying <input type="checkbox"/>
Health Engineering <input type="checkbox"/>
Road Construction <input type="checkbox"/>
Quantities, Estimates <input type="checkbox"/>
Hydraulics <input type="checkbox"/>
Structural Eng. <input type="checkbox"/></p> <p>GENERAL
Agricultural Eng. <input type="checkbox"/>
Council of Eng. Institutions <input type="checkbox"/>
Farm Science <input type="checkbox"/>
Plastics <input type="checkbox"/></p> <p><i>Supplementary courses for Nat. Certificates.</i></p> |
|---|---|--|

G.C.E.
- choose from 58 'O' & 'A' level subjects.

Coaching for many exams, including C & G and assistance in ONC/HNC.

IT PAYS TO BE QUALIFIED! POST TODAY FOR A BETTER TOMORROW

To B.I.E.T., Dept BTVII
Aldermaston Court, Reading RG7 4PF BTVII

NAME _____
Block Capitals Please
ADDRESS _____

OTHER SUBJECTS _____ AGE _____
Accredited by C.A.C.C.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY