


Jeff

1/-

Vol. 27 No. 535
MAY, 1955

EDITOR:
F.J. CAMM

PRACTICAL WIRELESS

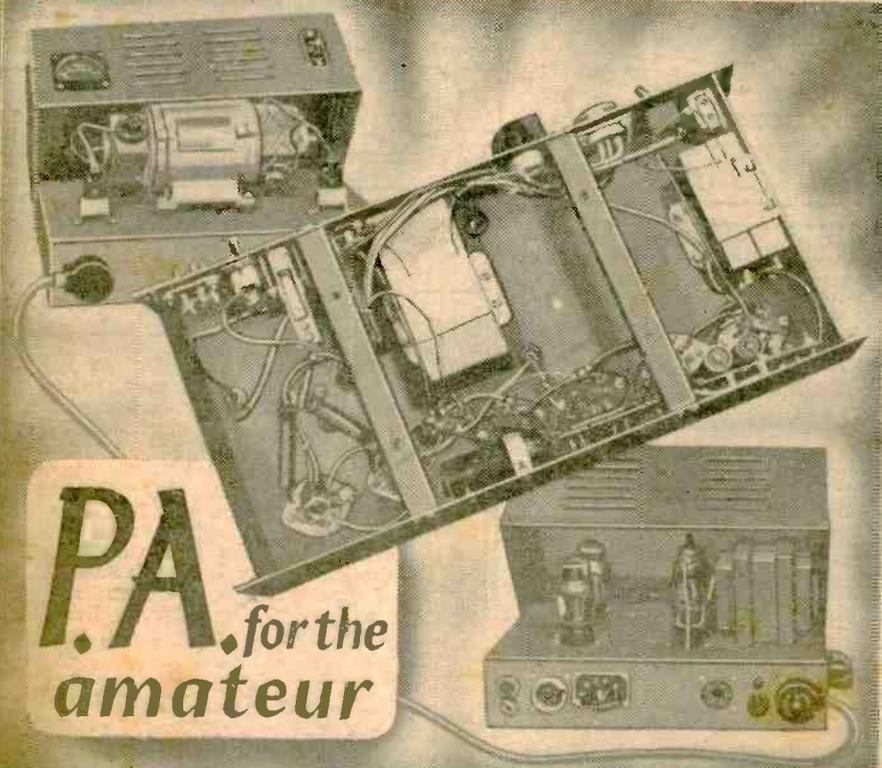


P.A. for the
amateur

IN THIS ISSUE

Converting R25 to Superhet
Efficiency in 2-metre P.A.
Superhet Tuning Unit



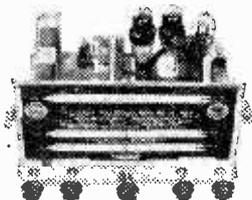Improved Crystal Receivers
R.E.C.M.F. Exhibition
Three-band Superhet



Figures Talk!

| | |
|---------------------------------------|----------------|
| Model | 103 |
| Stages of I.F. | 2 |
| Selectivity better than (kc/s) | 7 |
| Stages of A.V.C. | 3 |
| No. of Valves | 10 |
| No. of Wave Bands | 3 |
| ADDING UP TO ONLY | 19 Gns. |

No other radio chassis offers all that the Armstrong RF. 103 so efficiently provides at such a low cost.

OTHER ARMSTRONG CHASSIS

Model EXP. 833. An eight-stage all-wave radiogram chassis is designed to provide quality radio and record reproduction for the "not-so-rich" £15.8.8. Plus P. Tax.
 Model 125/2. The "Armstrong" triumph—a 14-valve all-wave radiogram chassis with short wave bands down to 10.9 metres. The chassis for the man who wants the best. £33.12.0. Plus P. Tax.
 ARMSTRONG TELEVISION—MODEL TV.20. A wide-range 21-valve instrument incorporating a 12in. C.R. Tube. £52.10.0. Plus P. Tax.

Write now for full information.

Armstrong

THE CHASSIS PEOPLE


Armstrong Wireless & Television Co., Ltd., Warlters Road, Holloway, London, N.7. Tel: NORTH 3213.
 Sole Birmingham Agent: Hayes Company, 1, Alcester Road, Birmingham, 13.

SOUTHERN RADIO'S WIRELESS BARGAINS

- R.3515 TELEVISION UNITS.** 21 valves with 6-stage 14 m.c. I.F. strip, recommended for ideal T.V. conversion by all experts. Brand new in original wooden cases. £31/0/-.
- R.1355 RECEIVERS.** Brand new and unused, as specified for Inexpensive Television. £31/5/-.
- T.R.1196 6-Valve superhet receivers.** Perfect and guaranteed. 22/6, plus 1/4.
- THROAT MICROPHONES.** With Lead and Plug—Magnetic 4/6.
- CONTROL CABLES,** 14ft. with adaptors or B.C.453/4/5. 9/6 each.
- R.A.F. BOMBSIGHT COMPUTERS.** Complete, brand new, with motors, gyro gears, blowers, etc., etc. Ideal for model makers, etc. The best component value ever offered. 55/- each, plus 5/-.
- LUFBRA HOLE CUTTERS.** Adjustable from 1" to 3 1/2" for use on wood, metal, plastics, etc. 5/6.
- CONTACTOR TIME SWITCHES.** By Smith or Venner. 10-hour movement with thermostatic control. 2 impulses per second. Complete in sound-proof case. 10/-, plus 1/4.
- HAND GENERATORS.** 6 volts at 5 amps. Complete with crank. 21/-.
- RECEIVERS TYPE CCT-46104.** Frequency 1.5 mcs to 3 mcs for 28 volts. Complete with 28 volt Dynamotor, 6 valves. Brand New. Black Crackle Finish. 90/-.
- SPEAKERS.** Celestion 2 1/2 in. P.M. 3 to 5 ohms. Moving Coil, 17/6.
- PLASTIC TRANSPARENT MAP CASES.** 14 inches by 10 1/2 inches. Ideal for Maps, Charts, Photographs, etc. 5/6.
- CONDENSERS.** 100 Assorted Mica and Tubular up to 2 Mf, all useful sizes. 15/-.
- RESISTANCES.** 100 Assorted all useful sizes up to 3 watts, 12/6.
- RADIO COMPASS INDICATORS,** with internal Selsyn motor. 3" dial, 13/6; 5" dial, 15/6.
- WALKIE-TALKIE (TRANS RECEIVER) Type 38, Mark II.** Complete with 5 valves; Throat Microphones; Headphones and Aerial. Guaranteed working. £31/0/-, carriage paid.

Radio Publication List 2 1/2.

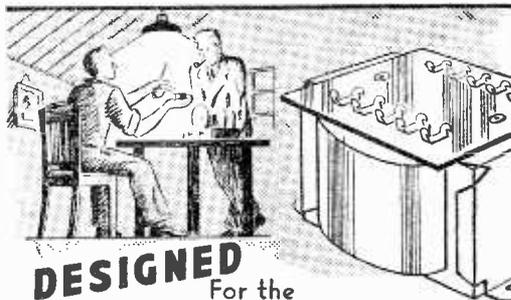SOUTHERN RADIO SUPPLY LIMITED
 11, Little Newport Street, London, W.C.2 Gerrard 6653



DESIGNED For the CONSTRUCTOR

UNIVERSAL 8 WATT OUTPUT TRANSFORMERS—T98—T99

No constructors' work bench is complete without one of these truly amazing output Transformers. Their Universal characteristics enable them to be used in a wide range of circuits. Covers any ratio from 11 : 1 to 105 : 1—the ideal component for all experimental work. TYPE T98 for single ended valves, TYPE T99 for push-pull. The superior design and high quality of Gardners Transformers ensure better home construction.

Fully descriptive literature on Somerford and Miniford Components will be sent upon request.

RETAIL PRICE
21/-
 CARRIAGE PAID

GARDNERS RADIO Ltd

SOMERFORD, CHRISTCHURCH, HANTS
 Phone: CHRISTCHURCH 1025



HOME STUDY backs radio experience with sound technical knowledge

MANY men who wished to link their radio experience with a sound technological background have received successful instruction by means of an I.C.S. Course. Its value has been proved not only to amateurs but to men who already have a professional interest in radio and television engineering, including those taking qualifying examinations. It is invaluable, also, to students who wish to prepare themselves for a job in this field. Courses of Instruction covering radio and, if necessary, television including the following:

- Complete Radio Engineering. Radio Service Engineers Radio Service and Sales. Advanced Short-Wave Radio Elementary Electronics, Radar, Radio, and Television Technology.
- And the following Radio Examinations:
 - British Institution of Radio Engineers
 - P.M.G. Certificates for Wireless Operators
 - City and Guilds Telecommunications

Write today for our FREE "Radio" booklet, which fully describes the above ICS Courses.

International
CORRESPONDENCE SCHOOLS

Dept. PW16, International Bldgs., Kingsway, London, W.C.2


Build a professional-looking Radio at less than half today's price

The Kits are housed in attractive Bakelite Cases, size 12in. x 5in. x 6in. Each Kit is complete in every detail, nothing has to be made or improvised. Easy to follow, point-to-point diagrams are supplied, making construction very simple. They are for use on 200-250 volt mains, and both A.C. and Universal Models can be supplied. The Dials are illuminated, and the receivers present an attractive appearance. We regret the necessity for the increase of prices due to continually rising costs.

PREMIER RADIO CO

MORRIS & CO. (RADIO) LTD.

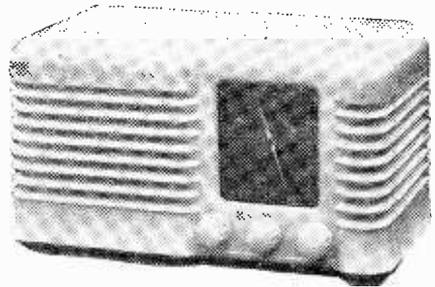ALL POST ORDERS TO OUR NEW FACTORY AT—
740, HIGH ROAD, TOTTENHAM, N.17. Tottenham 5371-2-3.
CALLERS TO: 152/3, Fleet Street, E.C.4. Central 2833.
207, Edgware Road, W.2. Ambassador 4033. This branch is open until 6 p.m. on Saturdays.



TRF

Valve line up: EF22 H.F. Pentode; VR116 Detector; CV1510 Beam Power Output in the A.C. Model. The A.C./D.C. Output Valve is 12A6. Both use Metal Rectifiers. Waveband coverage is for the Medium and Long bands. Price £5/19/6 (carriage and packing 2/6). With Walnut or Ivory Cabinet.


SUPERHET

Valve line up: 6K8, 6K7, 6Q7, and CV1510 Beam Power Output in the A.C. Model. The A.C./D.C. Output Valve is 12A6. Both use Metal Rectifiers. Waveband coverage is 16-50, 190-540 and 1,000-2,000 m. Price £7/19/5 (carriage and packing 2/6). With Walnut or Ivory Cabinet.

Circuit diagrams only can be supplied at 1/6 each. Cabinets only available at 17/6.

RADIO'S "PUZZLE CORNER"

cleared up with an

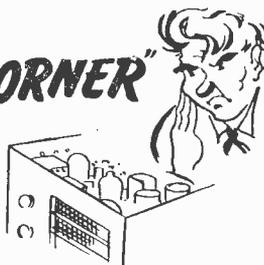

OSMOR "Q" COILPACK

Your coil and switching problems are solved in a matter of minutes with the pre-aligned OSMOR "Q" Coilpack. No complicated wiring circuits—just five simple connections and you're all set for better "whistle-free" listening. All types available for mains and battery sets, complete with full instructions and circuit diagrams.

Send 5d. (stamps) for complete receiver circuit, also lists of Coils, Coilpacks and all Radio Components.




As specified for conversion of the Type 25 unit of the TR.1196 also Type 18 and wartime utility receivers etc.

OSMOR RADIO PRODUCTS LTD.

(Dept. P.12), BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY.

Telephone: Croydon 1220

Three heads are better than one!

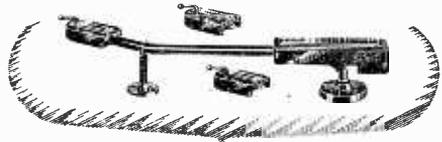

For Standard and Microgroove recordings

Microgroove recordings Green Spot.
Modern standard recordings Red Spot.
Older standard recordings Yellow Spot.

These pickup heads are fitted with an easily replaceable armature system complete with a semi-permanent sapphire. Downward pressure 10-12 grams for standard recordings, and 5-7 grams for microgroove recordings.

Prices: With one Head £4.0.0, plus £1.14.8 Purchase Tax. Extra Heads each £2.10.0, plus £1.1.8 Purchase Tax. Spare Armature System with sapphire 14s. 8d. including Tax.

a Connoisseur product

Telephone: HALIFAX 69169

A. R. SUGDEN & CO. (ENGINEERS) LTD.
Well Green Lane, Brighouse, Yorkshire.


W B THERE IS A
Stentorian
 LOUDSPEAKER
For every need

The W.B. range includes speakers from 2½" to 18", among them the famous Concentric Duplex 10" and 12" models.

Illustrated here is the Concentric Duplex Twin Corner Reflex Console with 10" Speaker.

★ Details on request

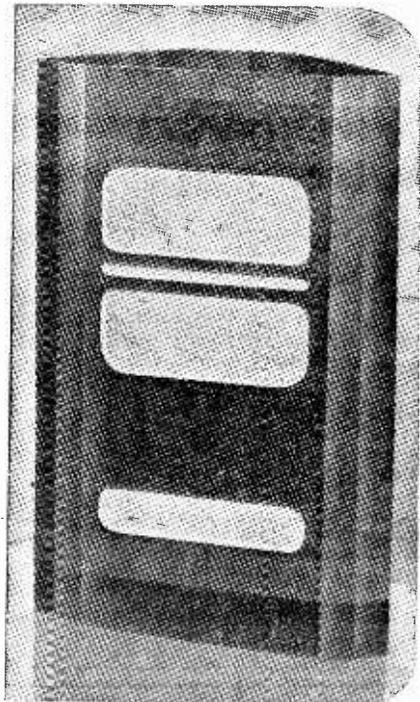WHITELEY ELECTRICAL RADIO CO. LTD.
 MANSFIELD NOTTS.




**LASKY'S
 RADIO**

**TELEVISION SOUND AND VISION
 ON ONE CHASSIS** Size 10in. x 4½in. x 1in.

Made possible by the use of miniature valves

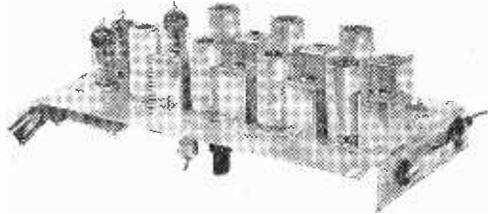Please state London or Birmingham frequency. (London model can be converted to Home Mass frequency.)



These units are not ex-Government, but are brand new manufacturer's surplus. They may be used with any type time base and c.r. tube, are fully assembled and wired, supplied with all valves. Voltages required:—L.T. 6.3 volts 3 amps., H.T. 270 volts 80 m.a.

Valve line-up:—5 6AM6's R.F. amplifiers sound and vision, one common to both. 2 6AL5's sound and vision detectors. 6AM6 video amplifier, 6AM6 sync. sep., 6AM6 sound output. Send 6d. for a copy of the full data, circuits and photographs dealing with this unit.

Price complete as illustrated - £6.19.6
 Carriage and packing 3/6 extra.

SAFETY FIRST. Fused test prods. Fully insulated pencil type with retractable point. Contact is only made when desired by pressing top. Each prod. contains a cartridge type fuse and spring.

LASKY'S PRICE 4.11 PER PAIR. (One red, one bla k.) Post 6d. extra.

VIBRATOR PACKS. Brand new, in original cartons. Manufactured in U.S.A. For 6 or 12 volt input. Output 300 volt., 60-80 m.a. Supplied complete with 4-pin non-synchronous vibrator and either OZ1 or 6X5 rectifier.

Size of unit:—7in. x 5in. x 3½in.
 LASKY'S PRICE, 27.6. Postage and packing, 2/6 extra.

ANTENNA RELAY UNITS TYPE GBY 29125. AMERICAN AIR CORPS. Contains 0.5 m.a. Western moving coil meter. Also relay, insulators, 0.75 amp. heating element with switch. A 50p.f. vacuum condenser, 5 kv. working. In black crackle metal case, size:—4½in. x 5in. x 3½in.

LASKY'S PRICE, NEW BOXED, 12 6.
 Postage 1/6 extra.
 SOILED, 7.6. Postage 1/6 extra.

LASKY'S RADIO,

370, HARROW ROAD, PADDINGTON,
 LONDON, W.9. (Opposite Paddington Hospital.)

Hours: Mon. to Sat. 9.30 a.m. to 6 p.m. Thurs. half-day.

Phone: Cunningham 1979 and 7214.

Send a 2d. stamp with your name and address for a copy of our current Bulletin. We have large stocks of new surplus radio components, valves, transformers, etc., details of which are given in our Bulletin.

Practical Wireless

19th YEAR
OF ISSUE

EVERY MONTH.
VOL. XXVII. No. 535. MAY, 1951

Editor F. J. CAMM

COMMENTS OF THE MONTH

BY THE EDITOR

18th National Radio Show

THE 18th National Radio and Television Exhibition will be held this year at Earls Court from August 29th to September 8th. Thus is broken the long association which tied the name of the Radio Show with Olympia. In future we shall refer to this high spot of the Radio and Television Year as the National Radio Show. In many respects Olympia had proved itself to be unequal to the expanding demand of our twin industries. The last Exhibition to be held there was cramped; a much larger number of firms had to be accommodated, with the foreseen result that the gangways were reduced and on the busy days, notably early closing days and Saturdays, it was impossible for visitors to examine the exhibits in comfort.

The more spacious floor space at Earls Court will eliminate this main difficulty, and now that television is developing rapidly a fair proportion of this space will be devoted to special television booths, so that the public can see television programmes on the receivers exhibited.

The first day of the show, namely, August 28th, is to be "Invitation Day" for overseas and other special visitors, and it is expected that Earl Mountbatten will open the Exhibition to the public on August 29th.

The scope of this year's exhibition has been considerably broadened, for every branch of the radio and electronic industry will be represented, and in addition there will be exhibits of gramophones, records and accessories, electro-medical equipment, electronic scientific instruments and test gear, including related products and services, trade exhibits and dealer aids.

Services and Government Departments will be represented by exhibits from the Army, the Royal Air Force, the Board of Trade, the Ministry of Civil Aviation, the Department of Scientific and Industrial Research, and British Railways.

The B.B.C. has promised full co-operation, and visitors will have a much better view this year of the television studio and of the artistes and technical personnel in action.

There will be improved facilities for comparing the various television receivers on exhibits in a 250ft.-long gallery. The control of the distribution of sound and vision will form an exhibit which will be of interest to every technician. There will be glass-walled continuity suites for both radio and television, with the announcers in public view.

We learn that the emphasis in the exhibition will be on export, because invitations to the show have already been distributed widely overseas, and a 28-page booklet entitled "British Radio for the World" has been prepared for overseas circulation only.

The exhibition comes within the Festival of Britain period and visitors who come to Britain in the late summer will also be able to visit the Marine and Engineering Exhibition, and the Flying Display and Exhibition of the Society of British Aircraft Constructors as well as the Motor Show.

The British Institution of Radio Engineers is holding one of the sessions of its 1951 Convention at the National Radio Show.

For the demonstration of radio receivers soundproof enclosures will be provided, a special radio signal being piped to exhibitors requiring it. It will be generated in the control room and will be within the medium-wave coverage of normal broadcast receivers. Only one signal will be transmitted over this network and it will be modulated with good quality speech and music obtained from recordings on magnetic tape, and it will simulate as nearly as possible a typical medium-wave broadcasting station for the demonstration of complete radio receivers.

The technical committee are hoping to provide for the benefit of exhibitors of high-grade low-frequency apparatus, a high-quality audio-signal superimposed on the cable of network carrying the radio programme referred to above. A simple filter will be installed in each demonstration room using the service so that either or both signals can be provided using the same cable run. It is proposed to send out a standard B.B.C. programme taken direct from the B.B.C. over the music lines which will be available in the control room.—F. J. C.

ROUND the WORLD of WIRELESS

Broadcast Receiving Licences

THE following statement shows the approximate number of licences issued during the year ended 31st January, 1951.

| Region | Number |
|--|-------------------|
| London Postal | 2,331,000 |
| Home Counties | 1,641,000 |
| Midland | 1,736,000 |
| North Eastern | 1,896,000 |
| North Western | 1,604,000 |
| South Western | 1,060,000 |
| Welsh and Border Counties | 728,000 |
| Total England and Wales | 10,996,000 |
| Scotland | 1,118,000 |
| Northern Ireland | 208,000 |
| Grand Total | 12,322,000 |

The above total includes 657,950 licences for television.

New Transmitter for Third Programme

A NEW high-power transmitter and mast radiator are shortly to be put into service at Daventry for the Third Programme. The installation has two of the latest Marconi 100 kW. air-cooled transmitters, with paralleling equipment, to give an output of 200 kW. but, to conform with the Copenhagen Plan, the actual power used will be limited to 150 kW.

This newest design of broadcasting equipment is housed in the oldest surviving B.B.C. transmitting station and now occupies the space where, 25 years ago, the B.B.C. installed their first high-power transmitter for long-wave broadcasting — the famous "old gentleman" of radio, 5XX. This venerable transmitter, which was in service until 1948, was also Marconi engineered, and replaced the historic 5XX which had been used for experimental broadcasting by the Marconi Company from their own works at Chelmsford.

The new installation consists of two complete transmitters of 100 kW. output. They are arranged in line with a special paralleling unit between them, in which the outputs are combined.

Death of Mr. P. C. Bullock

THE B.B.C. announces with regret the death of Mr. P. C. Bullock, A.M.I.Mech.E., A.M.I.E.E. Mr. Bullock joined the Station Design and Installa-

tion Department (now Planning and Installation Department) of the B.B.C. in 1931, having previously been with the English Electric Company, and shortly afterwards became head of the power section of this department. In 1944 ill health compelled him to resign this post, but he has since been responsible for the technical negotiation of all agreements for electricity supply for the B.B.C.'s stations.

E.M.I. and the Festival of Britain

THE Land Travel Exhibition, which forms part of the Festival activities, will feature a display of Amateur Radio Equipment.


An E.M.I. Absorption Wavemeter has been selected for exhibition in the Amateur Radio Section. This wavemeter employs a germanium crystal rectifier. It operates over the range of 1.6 to 30.0 Mc/s.

Special Magnetic Recorder

A SPECIAL E.M.I. portable magnetic tape recorder is being supplied to the Festival authorities for use in the Dome of Discovery.

The number of enquiries, in many languages, that are expected will necessitate the services of expert translators and technicians.

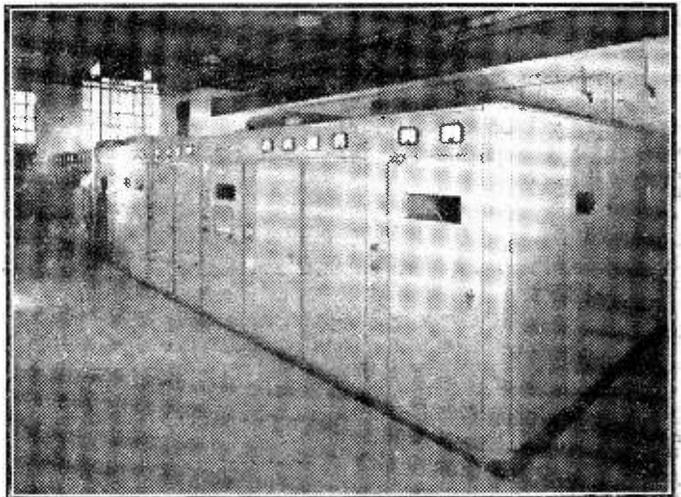To enable a query to be "stored" when it is impracticable to give an "on-the-spot" answer, this latest type of professional magnetic-recording apparatus is being used. The enquirer will deliver his questions into the microphone and the recording can then be played back at a suitable time and an answer given.



The two 100 kW. Marconi transmitters at Daventry. The transmitters are worked in parallel to give 200 kW.

The machine will record up to 60 minutes on each 1,200 ft. reel of recording tape and once the queries have been dealt with the recordings can be erased and the tape used again and again.


The machine and the Emitape recording medium is being provided by E.M.I. Factories, Ltd., Hayes, Middlesex, England.

Ultrasonics

UNDERWATER sound can be picked up by an entirely new method recently reported to the Acoustical Society of America. When ultrasonic waves strike a wire covered with a porous coating and immersed in water, an alternating potential of the same frequency as the waves is set up within the wire. The kind of metal used in the wire makes no difference, but the effect seems to depend on the kind of porous coating and on the solution with which the wire is covered. The voltage produced is very small, but it can be amplified to useful magnitudes. This discovery, says *Radio Electronics*, may be useful for submarine detection and it will be used for laboratory study of various kinds of underwater effects.

Brain Diagnosis

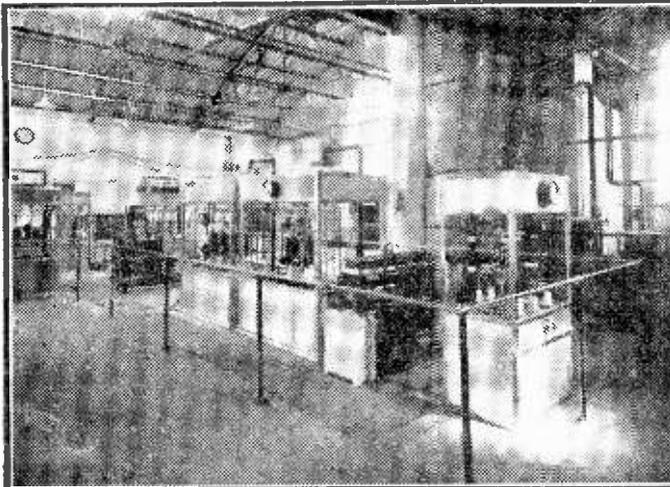
ULTRASONICS are also being used in research into brain disorders. Radiations are passed through the brain and are attenuated through tissues, etc., but remain undisturbed when passed through fluids. As a result a "map" of the brain may be "drawn" to show the presence of fluids, and it is claimed that this is superior to X-ray examinations.



Compare this view of the original 5XX transmitter at Daventry.

The Ham Spirit

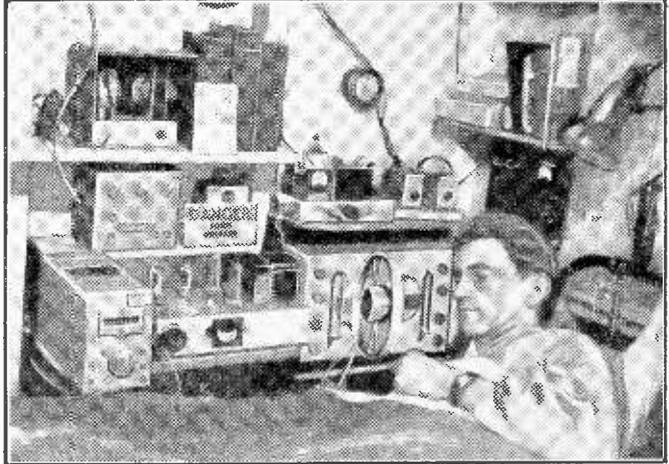FOR five years 24-year-old Len Chastey, of Bridestowe, nr. Okehampton, has lain in his hut at the Cornish Riviera Sanatorium, Roschill, Penzance. As a result of the efforts of the Cornwall Amateur Radio Club he has now obtained a trans-



Len Chastey with his finely equipped "shack." See story above.

mitting licence and his "hut" has been well equipped. Now, instead of being cut off from the rest of the world, he is in constant touch with amateurs in all parts. His call is G3GZK and his equipment is rated at 25 watts.

Oliver Heaviside

IN a lecture recently to the Junior Section of the Cambridge branch of the Institution of Post Office Engineers, Dr. G. F. C. Searle, F.R.S., described "the man as he was." Dr. Searle is probably now the only surviving scientific man who met Heaviside during his work.

Town Relays

STOKE-ON-TRENT Corporation recently considered the question of town relays of radio and television and it was recommended that offers made by two companies be examined in further detail, and that systems already in operation in two other districts be inspected.

At Dover, the Town Council decided to postpone for a month a proposal to enter into an agreement. In the meantime local traders will have an opportunity of putting forward alternative systems. A similar scheme proposed by traders had been turned down some time ago.

Three Waveband Superhet for the Beginner

A Simple, Inexpensive Superhet Especially Suitable for the Newcomer

By "ELECTRON"

THERE has apparently grown a legend that to build a superhet one must have a wide experience in receiver construction, and in any case, superhet teething troubles are no task for the beginner to tackle. Whilst a superhet is admittedly a more complex unit than a straight of the 0-v-2 variety, and there may occur more involved faults and difficulties, the constructional snags are, in the main, greatly exaggerated. True, the theory of the superhet is more involved (and one is advised to glean at least a working knowledge of this before such a receiver is built), and the initial adjustments more complicated than with a straight receiver; but the problems facing the prospective builder of a superhet are no more than the average constructor can deal with.

All thoughts of point-to-point wiring diagrams must be instantly dismissed. The theoretical circuit diagram and a rough idea of the main component dispositions are all that is necessary, plus common sense and thoughtfulness in the constructional work.

Thus a superhet, even of the simplest type, although not for the real beginner, is well within the capabilities of constructors who have had a priming in various T.R.F. receivers. The receiver about to be described is ideal for enthusiasts who feel they want to progress from the T.R.F. receivers which have been their outlet for constructional work in the past.

The receiver has nothing formidable in its design

or construction and can be built very quickly and cheaply. Moreover, it is surprisingly efficient for its size, and will illustrate to hitherto anti-superhet readers that the difficulties often associated with such receivers are largely mythical.

Requirements

When the receiver was designed, the essentials required were that it should be simple, easy to construct, and of reasonably good quality in reproduction. Additionally, coverage on medium and short wavebands was envisaged, and operation on a short indoor aerial was required.

The theoretical circuit will show that medium and short wavebands are included, but many readers, especially those living in the Midlands area, would, no doubt, desire the inclusion of a long waveband for reception of the Droitwich station. This is a simple enough matter, and it only requires the addition of a further set of coils; the wave-change switch mentioned will accommodate the extra ones. For details, see coil data table. Again, if only medium-wave coverage is required, the short-wave range can be completely ignored.

The Circuit

As will be seen from the diagram, five valves are used in the receiver. The first valve operates as frequency changer and local oscillator—it is a 6K8, a triode hexode. Incoming signals (as applied to the hexode grid and selected by the tuning circuit

LIST OF COMPONENTS

Resistors

R1 47,000 Ω
R2 47 Ω
R3 47,000 Ω
R4 47,000 Ω
R5 47,000 Ω
R6 10,000 Ω
R7 350 Ω
R8 470,000 Ω
R9 47,000 Ω
R10 470,000 Ω
R11 1 M Ω
R12 47,000 Ω
R13 240,000 Ω
R14 2,000 Ω
R15 1 M Ω
R16 500,000 Ω potentiometer
R17 47,000 Ω
R18 240 Ω
R19 4,700 Ω
R20 22,000 Ω
R21 47,000 Ω

Capacitors

C1/C2
C3 0.1 μ F
C4 100 pF silver mica
C5 0.1 μ F
C6 0.1 μ F
C7 0.1 μ F
C8 100 pF silver mica
C9 0.1 μ F
C10 0.05 μ F
C11 150 μ F silver mica
C12 0.1 μ F
C13 50 pF silver mica
C14 4.0 μ F
C15 100 μ F
C16 0.05 μ F
C17 25 μ F 25v. wkg.
C18 0.005 μ F
C19 25 μ F, 25v. wkg.
C20 16 μ F
C21 16 μ F
C22 0.05 μ F
C23 0.01 μ F, 750v. wkg.

Inductors

L1-3 Aerial coils (see table).
L4-6 Oscillator coils (see table).
L7 Smoothing choke, 60 mA. 10 Henries. (Or field coil of loudspeaker if mains energised type is used.)

Switches

S1, 2, 3, 4, Wavechange switch. 4-pole, 3-way.
S5 Pickup-radio switch. Single pole 2-way.
S6 Tone control selector. Single pole 4-way.
S7 On-off switch, incorporated with R16.

Valves

V1 Frequency changer, 6K8 (or X65, ECH35, etc.).
V2 I.F. Amplifier, 6K7 (or KTW63, EF39, etc.).
V3 Second Detector, 6Q7 (or DH63, EBC33, etc.).
V4 Output, 6V6 (or KT63, EL32, etc.).
V5 Full-wave rectifier, 5Y3 (or U50, etc.).

Transformers

T1 Loudspeaker transformer.
T2 Primary to suit mains. Secondaries: 300-0-300v. at 100 mA, 5v. at 3a. and 6.3v. at 2a.
I.F.T.1, I.F.T.2: I.F. Transformers for 465 kc/s.

L1/C1) are mixed with oscillations created in the triode circuit of the 6K8. These two carriers (the signal received and the local oscillations) will produce a beat note, the frequency of which will be out of the audible range, i.e., supersonic, hence the name of the circuit as supersonic-heterodyne, to give it the full name. It will be seen therefore that, since the I.F. transformers must tune to this beat frequency (or intermediate frequency as it is called) in order to provide sufficient amplification, it is essential that the oscillator coils used must be those designed for the intermediate frequency transformers used. Since the receiver being described uses I.F. transformers of 465 kc/s, then oscillator coils for a 465 kc/s I.F. must be used. Also of some importance is the matter of the oscillator padders: details of these and of oscillator and aerial coil trimmers are given in the coil data tables.

The frequency changer is coupled to the I.F. amplifier, a 6K7, in the orthodox manner, with the earthy end of the I.F. transformer secondary taken to the A.V.C. line. Full A.V.C. is applied to the signal grid and the actual A.V.C. components are of such a value as to be very suitable for the type of fading normally met with in medium-wave reception. Should the receiver be built with the object of using it mainly on the short waveband, then the values of R11 and C9 could be reduced in order to counteract the more rapid fading typical of short-wave reception.

Many of the troubles encountered in superhets are due to badly designed or constructed oscillator stages. In the receiver described, parallel-feed is used, and it is important to install the coils in the correct phase. If the secondary winding is the wrong way round, as likely as not no signals will be received. So, if you cannot get the correct connections for the coils you use, be prepared to change over the secondaries if the necessity arises!

The I.F. amplifier (or first detector as it is sometimes called) is a perfectly straightforward circuit, following normal pattern. The following valve, a 6Q7 double-diode-triode, conforms to standard

practice and acts as second detector/A.V.C./1st audio amplifier. The audio side of the 6Q7, i.e., the triode section, is generously decoupled in the anode circuit.

Provision for a pick-up is made, and the switch S5 feeds either the pick-up or the IF output to the grid of the 6Q7. On pick-up position the coupling capacitor C10 is cut out and automatically mutes the radio side.

The output of V3 is coupled to the output valve, a 6V6, through a 0.05 μ F capacitor, and the grid leak of that stage acts as the volume control (R16). A 47,000-ohm resistor is included as a grid stopper.

In place of the more usual fixed-capacitor/variable-resistor, tone-control arrangement, a simple switched circuit is included. This uses the normal fixed capacitor, but the switch (S6) selects various fixed resistors to give three pre-arranged tonal values. Individual constructors may wish to experiment to find values to suit their personal tastes, but the three values given here will cater for most likes. The fourth position, with no resistor in circuit, is specially useful when a lot of bass is required.

Nothing much need be said about the power supply, since this follows normal practice, consisting simply of a 5Y3 full-wave rectifier with standard capacitor-input filter circuit.

Construction

The accompanying layout sketches show the disposition of major components. There is nothing fanciful about the construction, but an attempt was made to place the above chassis components in some semblance of balance. Neatness, providing electrical efficiency is not impaired, always adds to the final pleasure of building radio gear.

Starting from the right-hand bottom corner (front) is the 6K8, followed by the first I.F. transformer and the 6K7. Next to this, along the back, is the second I.F.T., the 6Q7 and the output 6V6. The power supply components have been mounted as far away from the receiver section as

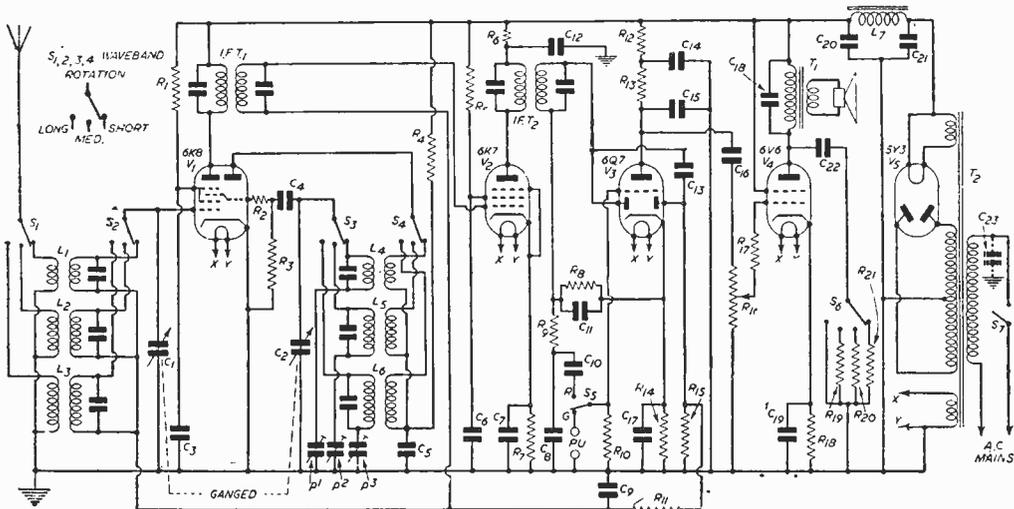


Fig. 1.—Theoretical circuit of the receiver.

practical. No screening was found to be necessary since, with the gain turned fully on, there is no more than the usual very faint hum—hardly audible.

So much for above chassis layout. The below-chassis wiring contains no real snags, and Fig. 3 will show all that one needs to know of the positioning of components. Those not marked should be taken to the nearest appropriate terminal and, in the case of earth return, leads to the nearest position on the earth bus-bars. As far as possible make all earth returns from each stage to a common point. Thus, in the V2 stage, C6, C7, R7 and C12 are all taken to the same point. These common return points are then interconnected by the bus-bars. This procedure is well worth while in the interests of stability, and it prevents receiver earth points being at different potentials throughout the stages.

One hears much about needing an abundance of screened leads in superhet receivers but this is not always strictly necessary. In fact, screening can be overdone because the more screening there is the greater will be the by-pass to earth. Hence the ideal set has just the minimum of screening—and no more. In practice, a certain amount of trial and error is suggested; starting off with only the very obvious leads screened, others being screened if any form of instability or other symptoms appear which suggests insufficient isolation.

Four leads only have been made with screened wire in the original model. They are: (1) From the aerial terminal to the wiper of S1; (2) From the top cap (grid of hexode) of V1 through the chassis; (3) From the rotor of C2 through the chassis to S3; and (4) From the top cap of V3 (grid) through chassis to S5.

No other leads have been screened, since there is no trace of instability, or other annoying symptoms. The valves can be fitted with valve cans (that is, V1, V2 and V3) in order to shield them; in actual fact this was done on the original receiver but they were later removed as an experiment, and since no signs of misbehaviour occurred they were left off.

No leads, apart from the four already mentioned, have been screened, and providing that short and direct wiring is made, that the soldered joints are sound, and that the earth returns are made as previously suggested, there should be no difficulties in getting good initial results from the receiver.

Rigidity is another important point. Com-

ponents such as resistors, capacitors and so forth, should be taken to "natural" anchor points wherever possible, as in the case of valve-holder tags, I.F.T. terminals and switch connections. Where necessary, insulated anchor tag strips (those with one earthed and two insulated tags are very convenient) should be fitted to provide additional securing points. Only three were found to be necessary and these are shown in their approximate positions in the under-chassis sketch. Even the rawest beginner should have little trouble in wiring-up this receiver, and components will be found to "fall into position" quite easily.

A word on the coils used. These are Wearite "P" type coils as they fitted into the scheme of things quite nicely. Other similar coils could, of course, be used where desired. The R.F. coils are banked horizontally along the rear of the chassis, next to the wave-change switch; the oscillator coils are banked vertically. It was found quite unnecessary to use coil shields since in the arrangement used the two coils in use for any one given position are far

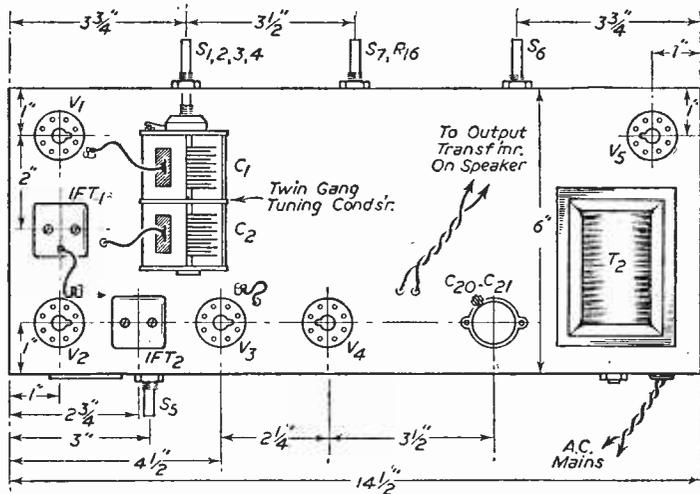


Fig. 2.—Above-chassis marking out and wiring details.

enough apart to prevent any troubles arising. For instance, when on short waves, the two coils in circuit (L1 and L4) are well spaced and are, additionally, in different planes. Similarly, of course, with the other ranges.

Wiring

The procedure for wiring is largely one of common sense. The layout diagram and the theoretical circuit should be studied closely and the various wiring sequences worked out mentally, with any snags ironed out, before any practical work begins.

| | AERIAL COILS | | | COIL TABLES | | | OSCILLATOR COILS | | |
|----------------|--------------|----------|---------|-------------|----------|---------|------------------|--|--|
| | Ref. No. | Type No. | Trimmer | Ref. No. | Type No. | Trimmer | Padder | | |
| Short Wave .. | .. L1 | PA3 | 60 pF | L4 | PO3 | 60 pF | 5,000 pF (P1) | | |
| Medium Wave .. | .. L2 | PA2 | 60 pF | L5 | PO2 | 75 pF | 450 pF (P2) | | |
| Long Wave .. | .. L3 | PA1 | 70 pF | L6 | PO1 | 100 pF | 150 pF (P3) | | |

Time spent in working out these details will be well worth while—in fact it is more or less vital. There is, however, one point:—The wiring around the V1 valve-holder should be completed as far as possible before the coils L1, L2 and L3 are fitted into position, otherwise it may be difficult to insert the soldering iron without damaging the coils.

There is nothing outside of normal constructional practice involved, but there are a few points which should be mentioned. In the first place, C23, shown in the under-chassis sketch, was fitted in order to cure some modulation hum which appeared—i.e., a hum which appears only when stations are tuned in—the louder the signal, the greater the hum. Modulation hum is very unpredictable as it usually vanishes when the receiver is plugged into the mains of another house. It can be due to various reasons and likewise there are various cures for the trouble. However, the simplest, and usually most effective, is by the insertion of a capacitor in the position shown. If such a capacitor is installed, the working voltage must be at least 750.

Secondly, the component marked C20/C21. This contains two 16 μ F sections—the casing being the negative common. An economy can be effected by using one of the 16 + 16 + 25 μ F combined capacitors,

The newcomer to superhets will be pleasantly surprised at the "punch" on the short wavebands. The background level is very low—mainly hum for all practical purposes being non-existent and superhet "hiss" being similarly inconspicuous.

In lining up the completed receiver it is, of course, ideal to use a signal generator. However many constructors, especially newcomers, will not have this facility and so a more crude method must be used. It must be remembered that a completed superhet may after the initial switch-on appear to be completely "dead." This is because the trimmers and padders and the I.F.T.s are so far out of alignment. The medium waveband should be tackled first, and the twin gang rotated slowly for any signs of a station. When one has been located it is more than likely very faint, but adjustment of the I.F.T. trimmers will bring the transformers into tune and the station will peak up. Always start at the V3 end and work backwards to the V1 anode winding. When the I.F.T.s have been roughly aligned, the trimmers and padder remain to be dealt with: if a tuning dial is used, the padder (in this case P2) is adjusted until the station received corresponds to its marked position on the dial. Mutual adjustment of trimmers and padder will be necessary for correct "tracking."

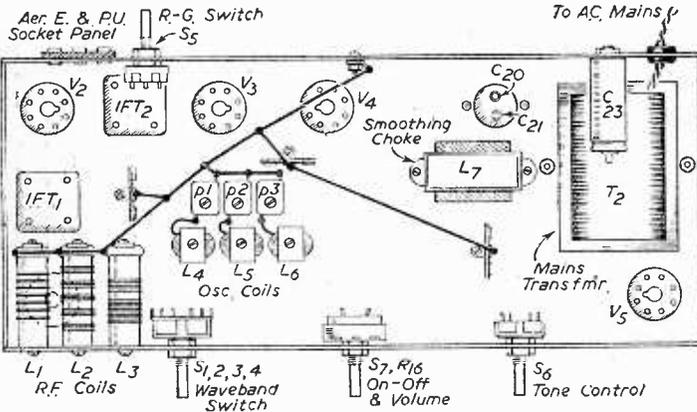


Fig. 3.—Under-chassis layout and wiring details.

with the latter section being used for the output bias smoothing (C19).

In the matter of the twin-tuning gang, the one on hand when the receiver was built had only a single-speed spindle, so a small epicyclic drive was attached to give slow-motion control—so essential if any measure of success is to be attained on the short waveband.

Results

As to results, these have been entirely satisfactory. On medium waves the various European stations provide good, strong signals, and the sensitivity as a whole is good. Quality is also up to standard and will satisfy even the fastidious. The short waveband is well worth while and brings in scores of stations at good, strong entertainment strength, and considering that only a short throw-out aerial of about 4ft. of wire has been used the results are extremely good.

The trimmer on the aerial coil (L2) is the final adjustment required.

The above is a necessarily brief idea of how to bring the circuits into alignment. If the constructor requires to be specially exact then reference to available textbooks is suggested. Incidentally, one way of getting the receiver roughly in tune is that used by the writer.

Anxious to check the performance in the absence of a test oscillator—for no signals of any description could be heard—the domestic vacuum cleaner was switched on! The I.F.T.s were then trimmed until the noise in the speaker became at its loudest, and a flip of the twin-gang soon produced stations. Often similar interference

noises are already laid on, but they can be self produced with any appropriate apparatus—vacuum cleaner, electric razor and so on. In an emergency this is quite a useful dodge!

Before attempting to align the receiver, the normal tests should be made to ensure that no dead shorts are present and that the correct voltages are applied to the various valves.

The short-wave fan could fit band-spreading, and this, in conjunction with a good outdoor aerial, will result in a splendid short-wave performance.

Practical Television

Edited by F. J. Camm

No. 11. Now on Sale Price 1/-

Get Your Copy Now!

Short-wave Topics

Interesting Information for the Expert and the Beginner

By A. W. MANN

Moving-coil Headphones

MOVING-COIL headphones are very popular nowadays, due in part to the low price of ex-Service types.

Those used until recently by the writer are of the ex-R.A.F., large earpiece type. During the past week, however, I have been testing a pair which are of American manufacture.

At the time of writing there is available in the surplus market a headset adaptor known as type MC385C, high-to-low impedance. This, however, does not accurately match the R.A.F. type headphones to my receiver outputs.

It is designed for use with the American type HS33 and HS38 moving-coil headset.

A pair of HS33 type were purchased at a very reasonable figure from a well-known Liverpool firm, new and unused, the workmanship being of a very high order. Using the 385C matching transformer unit with the R1116A and an unmodified R1155A receiver, the response is exceptionally good. From comments heard on the amateur bands, a well-known G station operator uses the same type headset in conjunction with National H.R.O. The high sensitivity of these 'phones makes them most suitable for DX reception.

QRP Activity

Amateur radio in this country is represented to a considerable extent by comparatively high-power stations on most bands. This rather reduces the chances of QRP transmissions being heard. There are, however, periods of low activity, when the low-power stations can be heard. Under the circumstances QRP operators who fail to raise the station called, or find their repeated CQ calls remain unanswered, would be well advised to put out a general call to short-wave listeners, together with QTH. The results would provide much useful data as to coverage, together with some surprises.

They might be surprised to know just how far away their signals have been heard. The writer would like to compile a comprehensive list of G QRP 'phone stations and full details will be appreciated from those who care to let me have them.

Transmitter Receivers

This brings to mind the fact that there must be a considerable number of battery type ex-Service transmitter-receivers in the hands of experimenters. Some have been purchased with the object of modifying or adapting the receiver section, the transmitter being dismantled for spare parts.

On the other hand, the complete outfit may be stored away until such times as the owner is qualified to obtain an amateur licence. Amongst such apparatus there are, no doubt, quite a number of the ex-R.A.F. TR9 type.

I cannot, however, call to mind hearing any QRP 'phone stations which during a contact men-

tioned that one of these transmitter-receivers was in use.

There are various models of this transmitter-receiver including the TR9F. This consists of a T1138 transmitter, and a R1139 receiver. The frequency range being 6.6 Mc/s to 4.3 Mc/s. This transmitter was designed for use with the well-known inter-comm. amplifier A1134.

The TR9D included a T1119 transmitter unit and a R1120 receiver. While electromagnetic microphones were used with TR9F and TR9D there were certain modifications in the latter instance, and a A1134 was not used. One form of TR9F, however, was designed for use with carbon granular microphone.

At present the models available are of the TR9H type. The units being a T1396 transmitter and a R1139 receiver. The receiver is a six-valve TRF and incorporates H.F. regeneration. I will further discuss this receiver in the future.

The Amateur Bands

Pirates are to be heard on various bands. It would appear that the abolition of the artificial aerial licence was a retrograde step. In addition to its many other advantages its reintroduction might assist in curbing such misdirected enthusiasm.

Some may disagree with the personal opinion expressed, and in any case consider that the scope for experimental work which this form of licence allowed no longer exists. The increasing interest which is being shown in QRP transmitters is at least sufficient proof.

Simple Receivers

Much can be accomplished with simple receivers. Chassis constructional methods are an assurance to some extent against instability. Constructors, however, who have reverted from plywood to metal panels, should not overlook the fact that the L.T. on-off switch should be insulated from the panel or chassis according to where it is mounted.

Surplus Radio Apparatus

One sometimes sees for sale receivers which have suffered from attempts at modification by those lacking sufficient experience to carry out the work. Such receivers usually find their way into the junk shop.

Before attempting conversions and modifications, it is policy to obtain as much official data, together with theoretical diagrams, etc., as possible.

If possible get the receiver working in its original form. Meanwhile, study the necessary modification data, or work out your own, so that you not only have a clear understanding as to what you are going to do but, in addition, how to do it.

It is a sound idea to redraw the basic circuit, and include the modifications. This takes time, but often saves hours of wasted effort.

Modern Superhet Tuning Unit-2

A Receiver Unit for Use with the Amplifier Described in our July, 1949, Issue
By R. HINDLE

THE connections to the ganged condenser are so made intentionally because it fits in better with the construction, and it is quite harmless so long as the leads are screened (as they would be in any case). Short pieces of coaxial cable are used, earthed by screws fitted in the condenser main frame, taking care not to distort the plates of the component. Note that the I.F. transformer between the frequency changer and the I.F. amplifier is the one with the pigtail, which lead should be cut as short as possible, allowing for connection to the grid cap.

Screened leads (again, coaxial cable) are used for leads carrying the audio signal between panels to avoid hum pick-up. This part of the circuit is vulnerable, and even a short, unscreened lead may introduce hum. Coupling condensers on the chassis, C36 and C37, are metal-cased, with the casing earthed, and open leads are limited to a fraction of an inch.

A thin, twin plastic flex is run from the heater pins of V5 to the two dial lampholders provided, and a five-core cable through the larger hole in the back of the chassis brings in the heater and H.T. voltages and mains control leads. A coaxial socket is provided for the pick-up connection, and another provides the aerial and earth connection. Coaxial cable is quite suitable for the latter purpose and is much neater than separate cables.

Two drive cords, fitted in the conventional manner, are used for the Osmer dial. One drives the condenser from the tuning spindle and provides the reduction ratio of the drive. The other drives the dial from the condenser spindle, using the two drums of equal size provided by the makers of the dial.

Alignment

In view of the recent shifting downwards of the B.B.C. wavelengths, it is important to keep all stray capacities low whilst wiring so that the necessary sweep is obtained. There is no difficulty in ensuring this with the layout given. A glass dial marked with the revised station positions is available and is now supplied with the assembly.

After carefully checking the constructional work, connect the chassis to the amplifier chassis by means of the five-core cable and the coaxial cable, and switch on. It is necessary, for best results, to ensure first that the I.F. circuits are correctly tuned to 465 kc/s, and if at all possible this should be done with a signal generator. If this cannot be done, however, these circuits should be left until later.

Check that the dial pointer sweeps exactly over the 180 degrees of the dial and short out the A.V.C. condenser until the aligning is completed (C44). Switch to medium waves and, with the aerial connected, it should be possible to tune-in a signal

without any adjustment of the trimmers. If nothing can be tuned-in, and no faults can be found, it may be that the I.F. circuits are too far out of tune (if a signal generator has not been used), and these should be given a preliminary adjustment, listening for the rustling noise that indicates approach to tune.

When signals have been received, proceed as follows. Screw all trimmers (*not* coil cores) full in, and then slacken half a turn. Remove the top cap connections normally on V1 and V2, and connect the lead normally on V1 and V2 instead: the other is left disconnected. This eliminates the R.F. stage, and only the pack underneath the chassis will need adjusting. Set the dial to a station in the middle of the range that is normally well received and identifiable with certainty, and tune it in with the medium-wave oscillator coil core to maximum. This coil is the one between the trimmer banks. Now finally trim the I.F. transformers if these have not

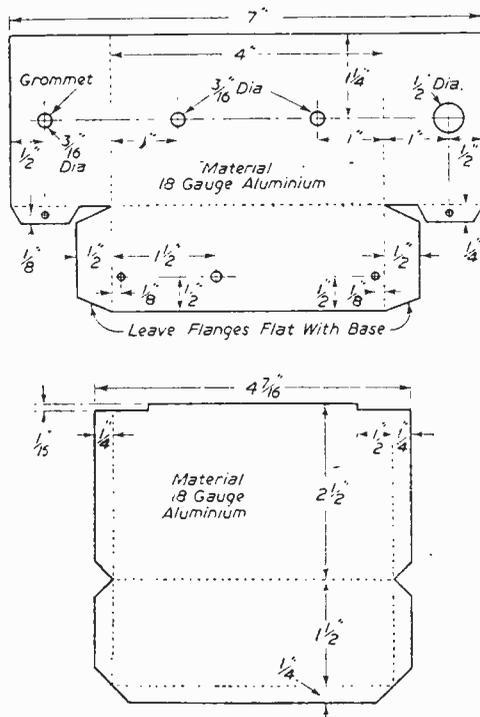


Fig. 5.—At the top (a) is the chassis layout and cutting plan, and at the bottom (b) the remainder of the box.

previously been set up with a signal generator; if they have, let well alone! Then set the dial to the position of the medium-wave Light programme as marked on the dial, and tune the signal to maximum with the oscillator trimmer, leaving the core alone. The third step is to set the dial to the North Regional position and then to adjust the oscillator core for maximum for this station. Now alternate on Light and North Regional transmissions, adjusting only the trimmer on the former and only the core on the latter, until satisfied that no further adjustment is required on either. Then, on the same two tuning points, using the same method with the aerial core and trimmer, bring this circuit into line. Finally, check the adjustments, using weak transmissions near to the two previously used.

Where the location of the constructor provides a very strong signal from any of the transmissions required for the adjustments they should be reduced in strength by working only with a short aerial. Later, when the main aerial is connected, the aerial circuit can be finally adjusted on weak transmissions at about the same frequency.

On long waves set the dial at 1,500 metres and tune in the Light programme on the oscillator core. Then, using any signals at the upper and lower part of the range whose frequency can be recognised, adjust the core and trimmer alternately, as before.

It is not so easy to find identifiable signals on the short waves and it will be better not to adjust the cores at all unless quite certain what is required. They will not be very far out and the aerial trimmer can be adjusted to resonance at the lower end of the range. If, however, a signal generator is available, a procedure similar to that described for medium waves will ensure best results.

The various trimmers and coils can be identified from the literature supplied with the coil units. If a calibrated signal generator is used for the adjustments the procedure is as described above, except that the following frequencies are substituted for the stations previously specified:

| | | |
|--------------|--------------|--------------------|
| Long Waves | 1,800 metres | 166.7 kc/s Core |
| do. | 1,000 do. | 300 kc/s Trimmer |
| Medium Waves | 450 do. | 666.7 kc/s Core |
| do. | 250 do. | 1,200 kc/s Trimmer |
| Short Waves | 45 do. | 6.67 Mc/s Core |
| do. | 20 do. | 15 Mc/s Trimmer |

When the above adjustments are completed restore the grid top caps to their normal positions and, on the same transmissions or generator signals as before, adjust cores and trimmers respectively of aerial and R.F. stages, but leaving the oscillator section alone. Finally, check these two stages on weak signals at about the same position on the dial, or, with signal generator, by reducing the signal to the minimum readable intensity.

Tone Control Unit

The separate tone control unit is built up on an aluminium chassis cut and drilled as in Fig. 5a and bent (markings inwards) to form four sides of a box. The two narrow flanges are bent up first. These are bolted to the base with countersunk bolts. The $\frac{3}{4}$ in. flanges are not bent; they are intended for screwing the chassis to the cabinet.

The other piece of aluminium Fig. 5b is bent to form the other two sides of the box with all the flanges bent at right-angles with the markings

inwards. This should then fit snugly to the first part with the flanges inside the chassis walls. It will be necessary to round off corners with a file to ensure a good fit. Eventually, when wiring and testing is complete, the two parts should be screwed together with small, self-threading screws.

Looking into the chassis part as it stands on the bench, the hole on the left side wall is fitted with a grommet to take a piece of coaxial snugly. The 1 megohm potentiometer R28 is mounted in the adjacent hole in the front; the 100 K. potentiometer R26 goes to the right. A coaxial socket for the input is fitted in the right-hand side wall. A two-way fixing tag is screwed to the hole in the base at $1\frac{1}{2}$ in. from the left-hand side, the screw being countersunk.

Fix C40, R29 from the earthy ends of the controls to the earth tag. Join the two potentiometer moving arms together and to the unearthed soldering tag and then wire in rigidly C41 and C42. From the input coaxial socket wire C39, R27 to the upper ends of their respective controls. Finally, feed a length of coaxial cable through the hole and solder to the two tags of the tag board.

New Valve Voltmeter

A NEW valve voltmeter for use on D.C. and on A.C. over a frequency range of 50 c/s. to 150 Mc/s. is announced by the General Electric Co., Ltd. The instrument is mains operated (230 or 115 volts, 50 c/s.); has ranges of 1.5, 5, 15, 50 and 150 volts R.M.S. and D.C.; and costs £61 12s. 0d.

Principle of Operation

In the case of A.C. measurements, the voltage to be measured is applied to a diode valve rectifier which has a high load resistance so that the input capacitor is charged to a negative voltage almost equal to the peak of the applied voltage. This voltage is passed through a D.C. amplifier which has a degenerative action, and so eliminates errors due to changes in valve characteristics. The amplifier is connected in a bridge circuit and the out-of-balance current indicates the voltage under test.

The detecting diode valve is contained in the portable probe and is connected to the set by a flexible cable. This enables the diode valve to be taken direct to the point at which the voltage is to be measured, which reduces errors normally caused by long leads. Special arrangements are taken to maintain input impedance as high as possible at high frequencies.

For D.C. measurements the unknown voltage is connected directly to the D.C. amplifier and, as the bridge circuit is highly degenerative, a very high input resistance is obtained when making these measurements.

A particularly interesting feature of the circuit of the instrument is that when the zero is set on the lowest range it will hold good for all the other ranges.

REFRESHER COURSE IN MATHEMATICS

8/6, by post 9/- 4th Edition By F. J. CAMM

From: GEORGE NEWNES LTD.

Tower House, Southampton Street, Strand, W.C.2

On your Wavelength

By THERMION

Isle of Wight and Television

THE inclusion of the Isle of Wight in the map issued in connection with the Beveridge Report, showing the locations of present and proposed television stations, has brought me a number of letters asking whether this presages the erection of a transmitting station on that delectable spot.

One newspaper, more noted for its sensational style than for its accuracy, boldly asserted a week or two ago that this was to be the case. I have the highest authority for stating that an I.W. television station is not contemplated at the present time. It is possible that the island will be served by one of the stations on the mainland.

Discless Gramophones

I WROTE in last month's issue a note concerning the discless gramophone marketed some years ago, but which enjoyed a very short commercial life, and made use of a photo-electric cell and a celluloid sound track, by means of which one could have a record which played continuously, the duration of play being limited only by the length of the celluloid strip which somewhat resembled the sound track of a talking film.

Mr. P. W. Feesey, of Raynes Park, writes to say that the company which marketed it was the British Ozaphane Co., which had the enterprise to market a domestic instrument in this country. It was housed in a conventional radiogram cabinet round about the year 1936, and they had as their slogan "Music on a beam of light," and Sir Malcolm Sargent recorded several orchestral works on films for them, and half-hour reels of dance music were also produced.

Such a development is inevitable, but I think it will be many years before the standard system changes.

L.P.R.

THIS reader tells me that after brief experience in long-playing records he finds them remarkably satisfactory; although there are some reasons, he says, for criticism of it, there are many others to justify, as I have already pointed out, the continued use of the present standard 78 r.p.m. records. He considers the introduction of a third speed such as 45 r.p.m. would be a folly; 33½ (why not an integral number?) and 78 records between them cater adequately for all disc recording.

He comments that we do not, in our feature entitled "Impressions on the Wax," review Decca records. The answer is a simple one; they do not send them in!

Of course, the question of gramophone needle and record wear depends very much upon the user and the type of pick-up, as well as the quality of the needle. I have some records at home which are over thirty years old and do not exhibit very many signs of wear or deterioration of musical quality after all those years of fairly frequent playing. I agree with my correspondent when he says that

the two most important features in avoiding record wear are lateral freedom of movement of the stylus and lightness of the pick-up head. One such head is the Aco's G.P. 20. A sapphire stylus operates satisfactorily with this pick-up.

Summing up the argument, therefore, we are all agreed that a device requiring no needle would be ideal, that sound-on-film fidelity is not equal to present-day disc recording, and that we shall have to be satisfied with present discs for many years to come, not because of technical difficulties, but purely because of economic conditions.

Growth of Clubs

IN the early 'twenties wireless clubs sprang up in almost every street, and they performed a very useful function in mutual aid when technical difficulties arose, as they often did. They began to fade away in the middle 'thirties until in 1939 there were only a couple of dozen spread throughout the country. The advent of television has given a fresh impetus to the club movement, for not only are television clubs being formed, but also combined radio and television clubs.

This journal and its companion journal *Practical Television* have already appealed to the B.B.C. to issue special experimental programmes for television experimenters. They did this many years ago in connection with radio, and I see no reason why it should not be done with the new science. In fact, there are even more reasons why it should be done.

There are many uncharted problems in connection with TV which cannot be solved by the engineers of Alexandra Palace alone, not because they lack the necessary technical skill, but because they cannot be all over the country at the same time.

Such an experimental programme would mean that every time it was radiated some of the best brains in the country would be checking up and reporting to the B.B.C.

I have no doubt that the R.S.G.B., and some of the more important of the television clubs will support this plea.

Club Lectures

I OFTEN receive requests to lecture to clubs. Too often I am compelled to decline the invitation because insufficient time is given to me. I am always delighted to give a lecture, but in view of my other commitments I must have at least three months' notice. As the lecture season has now practically ended and will not commence until October, I suggest that club secretaries plan their next season's programme now and make arrangements for speakers accordingly.

Although I was unable to be present in person at one club meeting, I was able to record a lecture on wire so that the members could hear my voice. The recorder I am operating at present is the Wirek, made by Boosey and Hawkes. The spools contain enough wire for over one hour's recording.

Type R25 Conversion

How to Convert this ex-Service Unit into an Efficient Communications Receiver

By T. S. WHITE

THE Receiver Type 25, part of the ex-R.A.F. Transmitter-Receiver TR1196 is still readily available on the surplus market at an exceptionally modest price. Details of its conversion to a broadcast receiver have already appeared in these pages. The R25 unit however, contains much of the circuitry of a very efficient receiver of the Communications type, and this article describes a method of conversion with a minimum amount of alteration to the existing wiring, and utilising as many of the existing components as possible. The additional components required are the ganged tuning condenser, coils, one I.F. transformer and a few smaller items usually found in the experimenter's "spares box." One valve only (an output pentode) is required in addition to the six valves contained in the receiver unit.

Circuit Description

One of the EF36 (VR56) valves is utilised in the

R.F. stage. No A.V.C. is applied, but the gain is controlled by a variable resistance in the cathode circuit. The existing EK32 (VR57) valve is retained in the mixer stage, followed by two stages of J.F. amplification, both using EF 39 (VR53) valves. A double diode-triode EBC33 (VR55) is used as detector and first audio valve and also provides AVC which is applied to the two I.F. amplifiers. Any small pentode such as the 6V6 or EL32 may be used in the output stage. The Beat frequency oscillator uses the remaining EF36 (VR56). The complete circuit is shown in Fig. 1.

Chassis Layout

After removing the existing tuned circuits from the chassis, it will be seen that there is very little space in which to place the necessary ganged tuning condenser, coils and wavechange switch. The top cover to the unit is therefore pressed into service and is bolted to the chassis as shown in Fig. 2. The

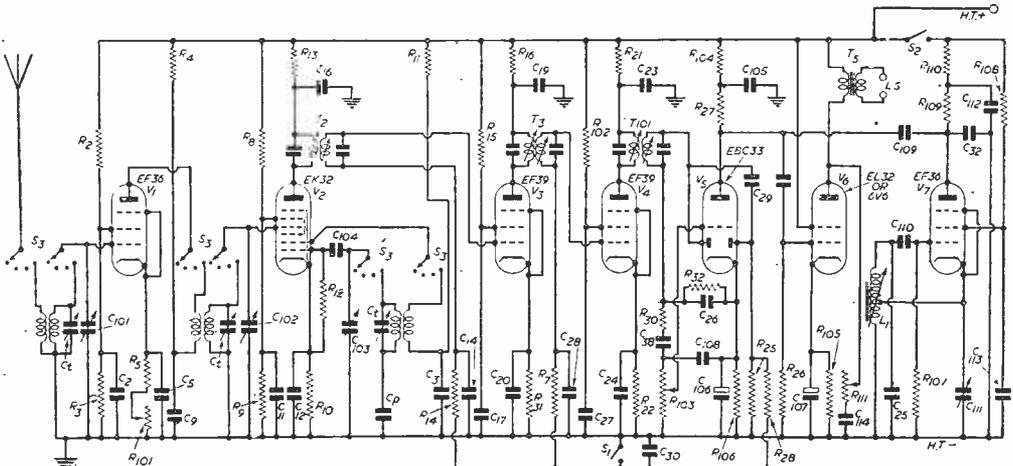


Fig. 1.—Theoretical circuit. Coil connections for Band 4 only shown. Resistors R2-R32, Condensers C2-C33 I.F. transformers T2 and T3, and coil L1 are as used in R25 unit.

ADDITIONAL PARTS REQUIRED

I.F. transformer T101—460 kc s.
Aerial, H.F. and oscillator coils.

12 50pF pre-set condensers. W/C switch (S3)
2 S.P.S.T. toggle switches.

CONDENSERS

C101, 102, 103—300-350pF. (ganged)
variable.
C104, C110 —100 pF.
C105 —8 μ F.
C106, C107 —25 μ F. 25 v.
C108 —200 pF.
C109 —2 pF.
C111 —25 pF. variable.
C112 —.001 μ F.
C113, C114 —.05 μ F.

RESISTORS

R101 —5,000 Ω Pot.
R102, R107, R108—50,000 Ω $\frac{1}{2}$ watt.
R103 —.5 M Ω Pot.
R104 —40,000 Ω 1 watt.
R105 —470 Ω 1 watt.
R106 —2,500 Ω 1 watt.
R109 —1,000 Ω .
R110 —10,000 Ω .
R111 —10,000 Ω Pot.

hinged lid on the chassis cover is removed and a piece of mica substituted to hold the oscillator paddler condensers.

On the receiver unit chassis the Jones type plug is removed, L.T.+ and H.T.+ from the I.F. section being transferred to pin 7 of V1, and the H.T.+ side of R2 (100,000 Ω) respectively. A diagram showing the position of these components will be found pasted to the bottom plate of the unit. Condensers C35, C36 and C37, transformers T4 and T5, potentiometers R18 and R23 and coil L1 are also removed.

Transformer T5 may be used as the output transformer if headphone reception only is required. The additional I.F. transformer is mounted as shown in Fig. 2. The lead from the first I.F. transformer to the top grid-cap of V4 should be removed and the second I.F. transformer modified by removing the yellow lead from pin 5 of the EBC33 valveholder and taking this lead to the top grid-cap of V4. The additional wiring required to conform with the circuit diagram Fig. 1 can now be carried out.

The Tuned Circuits

The author wound coils on 1in. paxolin formers to cover the frequency range of 30 Mc/s to 600 Kc/s (10-500 metres). Several manufacturers are able to supply coils to cover this frequency range with a ganged .0003 or .00035 μ F. condenser at reasonable prices, and therefore no details of the coils are given. Winding all the necessary coils is a long and tedious task and is not to be recommended. The values of the oscillation paddler condensers have not been given as coil manufacturers will specify optimum values. The wave-change switch is a four-position Yaxley type consisting of three two-pole wafers mounted inside the chassis cover as shown in Fig. 2. Complete screening of the coils is unnecessary if the layout shown is adopted.

The Beat Frequency Oscillator

The coil L1 taken from the receiver unit is utilised in this circuit and the cathode tap is obtained by unwinding approximately one-third of the coil, fixing the tap, and rewinding. Note that the tapping point is nearest the earthy end of the coil. The

leads to the top grid-cap of the valve, to the diode signal anode and to the B.F.O. pitch control should be screened, and a screen placed round all the B.F.O. components to prevent injection of beat frequency voltage into the early stages of the I.F. amplifier.

Power Supply

The requirements of the power supply are 200-250 volts at 70-80 mA for H.T. and 6.3 volts at 1.5 A. for L.T. An octal valveholder on the rear of the chassis cover is used to connect the supply to the receiver.

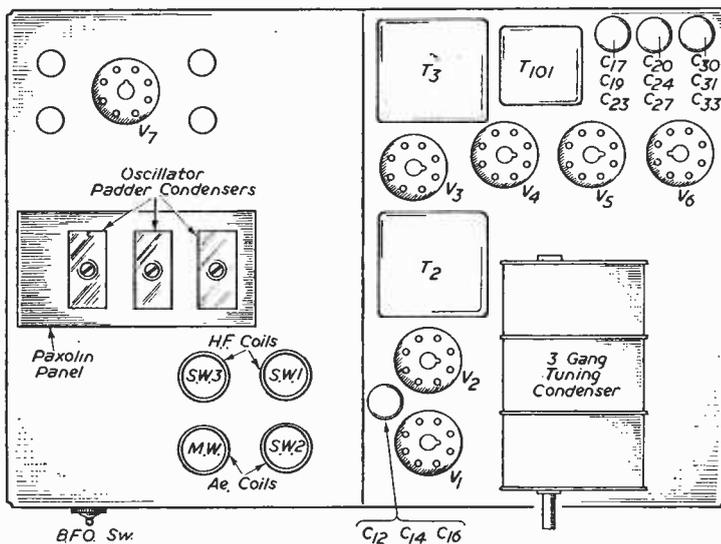


Fig. 2 (a).—Top of chassis layout.

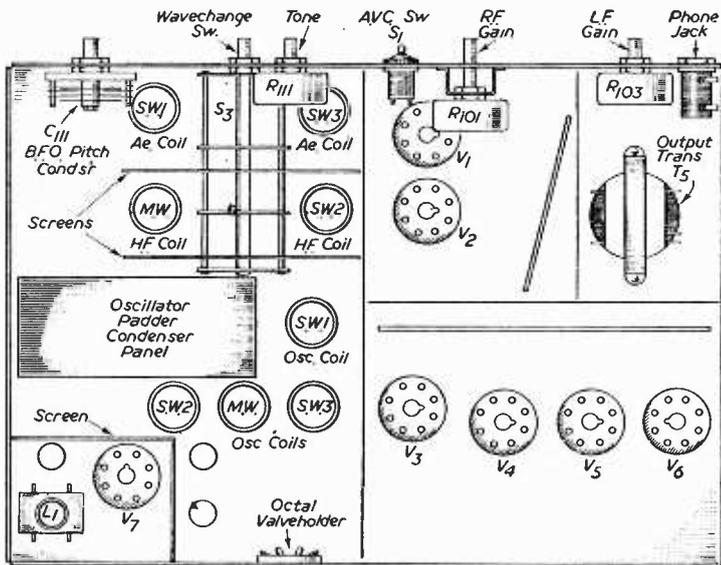


Fig. 2 (b).—Under chassis layout.

General

A slow-motion drive giving a reduction of at least 50-1 is recommended for use as the main tuning control. Fig. 3 gives the position of the controls. It will be seen that the space left by the removal of the Jones type plug must be covered to enable the R.F. gain control to be fitted. We must point out that we are unable to answer queries or give instructions for using alternative models of the R.25 or for making other modifications. We are, of course, always pleased to deal with problems arising directly from the details given, in constructional articles such as this, but must remind readers that a stamped-

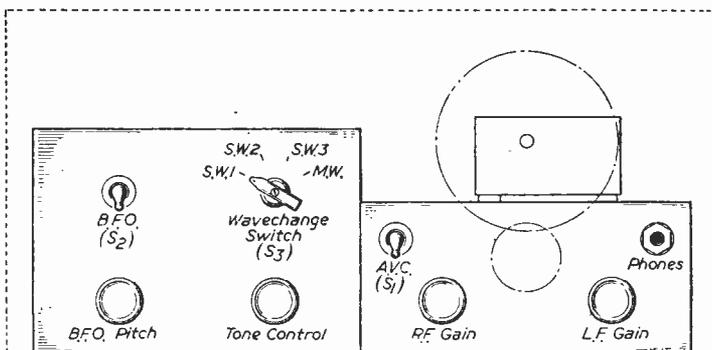


Fig. 3.—Panel layout.

addressed envelope must be enclosed if a postal reply is required.

Improved Crystal Receivers

Using the Germanium Crystals, and an Interesting Experimental Push-pull Circuit

By W. J. DELANEY (G2FMY)

ON several occasions recently young readers have asked whether it is possible to obtain improved signals in a crystal receiver by connecting two crystals in parallel. It is quite understandable that a beginner should reason that an increased output should be obtained if each detector gives a certain signal and these are combined before passing to the headphones, but unfortunately all that does happen is that the incoming signal is split between the two crystals, and thus each only handles half of the signal so that the combination, after detection, is only approximately the same as that given by one. There is quite a lot in this problem, however, and it will be shown later in this article that two crystals can be used to give an increased signal, and, in fact, a small crystal set can be built to operate a small loudspeaker provided that you are near enough to a powerful station. Before dealing with this, however, it should be pointed out that the crystal set should not be despised. Apart from the fact that the young newcomer to radio should start off on a crystal set in order better to understand some of the principles involved, there is a real field for this type of receiver: For bedside listening for the younger generation, at school, camp or other places where a battery or mains receiver would be inconvenient, and even for the old folk who want a little private listening to avoid interference with others.

Germanium Rectifier

The days of the catswhisker are, of course, over. There is no need to fiddle with delicate adjustments which are upset by the slightest vibration. Even the so-called pre-set detector is now superseded by the germanium type of permanent detector perfected during the war and now available in various types as a war-surplus item. Naturally new types

are of improved design and may be preferred by those who can afford them. For experimental use, however, the surplus items will be found very useful and in most cases give a much better signal than the ordinary crystal detector. The signal is, of course, very weak with the simple crystal receiver, owing to the fact that there is no amplification, and therefore every care must be taken to avoid losses and to develop the maximum signal voltage across the tuning circuit. Fig. 1 shows the basic crystal receiver the coil being tuned by a standard variable condenser of .0003 or .0005 μ F and the small condenser across the phones being of .001 μ F. It will be noted that the aerial is coupled to the main coil through a smaller coil, and it is here that considerable time may be spent in experiment. The main coil is "damped" by the load of the crystal and here also improvements may be carried out by reducing the damping effect. Fig. 2 shows how this may be carried out by tapping the crystal down the coil. The young experimenter has, therefore, two interesting fields for work, and the following are some suggestions of the lines

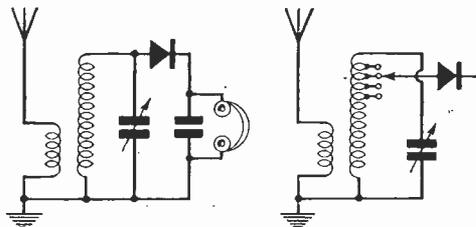


Fig. 1 (left).—A simple receiver circuit, and Fig. 2 (right).—An improved tuning coil.

upon which he may work. Firstly a single coil may be wound and arrangements made for connecting the acria and the crystal to various points.

Coil Design

The simplest way of doing this is to use ordinary enamel-covered wire for the coil and to support the coil firmly so that a strip of brass may be fixed to the same board in such a manner that it can pivot on one end and the other end run across the coil.

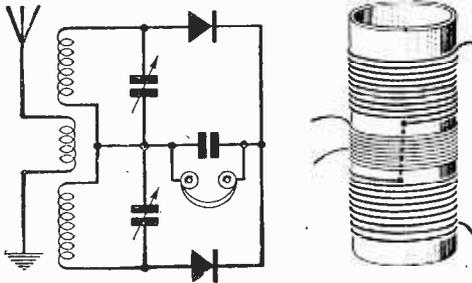



Fig. 5 (left).—A push-pull crystal circuit, and Fig. 6 (right)—Coil-winding details.

A punch mark in the brass where it touches the turns of wire, if run backwards and forwards several times over the coil, will scrape off the insulation and make contact with the bare wire. One such strip may be used for the crystal connection, and another for the aerial, and these may then be adjusted over very wide limits. Alternatively, loops may be made in the wire when it is wound on, and these may be used as connecting points, or they may be connected to multi-point selector switches. It will be found that the crystal connection will show a definite improvement at a certain position, any movement above or below that position reducing the signal strength. On the aerial side it is usually a matter of compromising between the loudest signal and the most selective point. If there is only one powerful station near you, then you can probably connect the aerial direct to the "top" of the coil. In London, however, where the Light and Home are both received very loudly, such a connection would result in both stations being heard together and therefore the aerial tapping point will have to be down near the earth end, thereby obtaining selectivity, but at the expense of signal strength or sensitivity. The tightness of the aerial coupling will also affect the selectivity and experiments may be made by interwinding a thin wire in between the lower turns of the other coil, or by winding the aerial coupling coil over thin strips of wood or other insulators stuck across the bottom end of the main coil. The size of the former on which the coil is wound will also affect results and also the number of turns of wire which are needed. The best idea is to try out various coil formers from, say, 1in. up to 3in. in diameter, and if you cut off about 40ft. of wire—about 24 gauge is most suitable—you can wind all of this on any size of former and it will cover roughly the Medium waveband. If you find in your particular locality that your station is received too near the ends of the tuning adjustment, take off or put on turns to suit. If the condenser is nearly wide open, then

you need to take off some turns, whereas if it is practically closed, then you need more wire on.

Push-pull Circuit

Those readers who understand the A.C. type of receiver will know that the mains transformer secondary is wound to give double the required voltage, and each end of the winding is taken to one side of a half-wave rectifier. In this way, as the A.C. voltage changes its direction each half cycle there is always a rectifier waiting for it, and each half therefore works in turn. The same idea is seen in the ordinary push-pull output stage found in high-power amplifiers, and it may be applied to the crystal receiver as shown in Fig. 5. It will be seen here that there are two circuits each feeding a rectifier and the centre point is neutral. Two separate tuning condensers will have to be used, or a two-gang condenser may be employed if the trimmers are working satisfactorily. The coil is made up as shown in Fig. 6, the centre of the main coil being opened to allow the aerial or primary coil to be wound in between the two halves. Only about $\frac{1}{4}$ in. to $\frac{1}{2}$ in. need be allowed, and again the number of turns for the aerial coil will have to be found by experiment to suit the particular locality. This is a very interesting circuit and will be found very good for giving improved signal strength at places where only a weak signal is

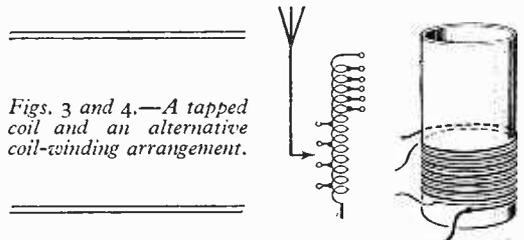

Figs. 3 and 4.—A tapped coil and an alternative coil-winding arrangement.

normally received. A good aerial is needed, as it does not seem to react very favourably with very weak signals. In the London area, however, both the Light and Home programmes may be heard on a 2in. P.M. loudspeaker with an outdoor aerial, and it will be found a very interesting circuit for the experimenter.

V.H.F. at the Festival

THE lighthouse on the Shot Tower at the Festival will be switched on and off by V.H.F. Radio over a distance of approximately 3 miles.

The transmitter will be installed at Chance Brothers' London office with a four element Yagi directional aerial providing a horizontal polarization, mounted on the roof of the building. The transmitter will be operated from the A.C. mains supply requiring 100 watts for operation when transmitting with a power output of 5 watts.

A total of six valves are employed in the transmitter which comprises a crystal-controlled oscillator followed by three multiplication stages, power amplifier and modulator stages.

The receiver is mounted in the lighthouse lantern with a four element Yagi aerial mounted on the outside balcony of the Shot Tower. The receiver is operated from the A.C. mains supply requiring 120 watts for operation and with crystal controlled frequency.

Simple Extension Speaker and Inter-communication System

A Domestic Aid and Experimental Set-up

By R. V. HARDY

THE usefulness of the extension loudspeaker is now generally recognised, and in many homes an additional speaker is installed in the "other room." However, comparatively few people appear to take advantage of the excellent microphone characteristics of the moving-coil extension speaker, by arranging inter-communication between the various rooms in the house. Perhaps this is partly due to the somewhat complicated designs which are sometimes published, and the mistaken idea that the system will be difficult to install.

The circuit shown on the right is extremely simple, very efficient and requires few components, while the advantages it affords are numerous. Normally, the speakers relay the radio programmes in the usual manner, but by turning a switch the extension speaker becomes a microphone and the user is able to carry on a conversation with the occupants of other rooms. This is useful for talking between the dining-room and kitchen, or the workshop and house. The system is also extremely effective for relaying amateur concerts and plays to other rooms in the same way that radio plays are produced, and has the great advantage that the actors can read their parts direct from a script. This facility is much appreciated by the younger members of the family.

If desired, the extension speaker may be placed near baby's cot, and will give audible warning should the youngster wake and commence crying. Mother can then switch over her speaker and say a few comforting words, which will often save a tiresome journey upstairs. When this service is required, a slight alteration in the positioning of the controlling switch is indicated, and will be dealt with later.

Circuit

The diagram shows the connections necessary for two-way communication between the radio set and one extension speaker. Any number of additional speakers may be connected in parallel, provided due regard is paid to matching them to the set. Normally, one or two extensions will not materially affect results.

The output transformer is that which is incorporated in the radio set. Disconnect the secondary from the speaker speech coil, earth one side and connect the other side to contacts A on switches SW.1 and SW.2. Switch SW.1 is mounted on or near the radio set, while SW.2 controls the extension loudspeaker. One side of the speech coil of the internal speaker is earthed and the other side taken to the centre, or moving contacts, of switch SW.1. Earth one side of the speech coil of the extension speaker and take the other side to the centre contacts of switch SW.2.


Mic.-trans. is an ordinary output transformer with the high-impedance primary connected to the pick-up terminals of the radio set, and one side of the low-

impedance secondary earthed, the other side being connected to the contacts B of the single-pole double-throw switches SW.1 and SW.2.

It will be observed that, apart from the earth connections, only two leads connect the loudspeakers; these may consist of twin bell wire. If a convenient earth is not available, a third wire will have to be used and the earth connections taken to this.

In many radio sets the pick-up terminals are permanently in circuit, but where this is not the case, the radio-gram. switch will have to be shorted out, when speech will be heard through the radio programmes. When conversations are required the set should be detuned, or the aerial unplugged.

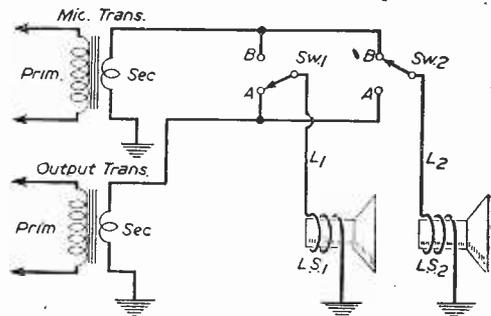Operation is simple. With both switches in the A position, normal radio is heard in both speakers. By turning either switch to the B position, the



Circuit of the arrangement suggested by Mr. Hardy.

associated speaker can be used as a microphone, the switch being returned to position A when an answer is required.

When the extension speaker is installed near a child's cot, it is better to have the controlling switch placed by the side of the internal speaker switch and the lead L2 run to the speaker. The mother will then be able to switch the speaker over at the radio set.

BUILDING THE "PRACTICAL WIRELESS" TELEVISION RECEIVER

A large number of readers unable to obtain back numbers of the issues containing the series of articles on the construction of the "Practical Wireless" television receiver, have asked us to reprint these articles in book form. This has now been done, and copies may be obtained from or through any newsagent, or for 3s. 9d. by post from us.

Orders should be addressed to The Publisher, Book Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Printed on good quality paper, this 32-page book gives complete stage-by-stage instructions for the construction of this highly efficient 18-valve television receiver, which received so many favourable comments when it was exhibited on our stand at the recent Radio Show at Birmingham.

In order to secure a copy of this limited edition readers should place their orders without delay.

NOVELTY MAINS BATTERY RADIO


Novelty radio in coloured plastic cabinet, only 6ins. high, ideal for a Nursery or a Bedroom, complete with built-in moving-coil speaker, 2-gang tuning condenser, volume control and ON/OFF switch, all wired up ready to operate as soon as valves are fitted. Works off dry batteries or through our 19/6 power units. Valves required are three of type 1T4 and one of 3V4 or 3S4. Because of a frustrated export order, we are able to offer these sets brand new and perfect, complete except for valves, at the remarkable price of 49/6 each, postage and insurance 2/6 extra. Don't delay—send your order to-day.



POWER PACK to work the above from A.C. or D.C. Mains, 19/6.

4-VALVE MAINS RADIO

All wired up ready to work, not a kit, A.C. or D.C. all mains. Four modern valves, gang tuning—high precision dust cored coils, first grade condensers, resistors and other parts. Metal chassis. Tunes Long and Medium wave bands—large, clear dial with station names—gets Home and Light, Luxembourg, etc. Ample volume, only short indoor aerial required. Chassis size approx. 9in. x 4in. x 5in. Complete with valves but less speaker, 57/6. Suitable speaker with matching transformer, 15/6. Nothing else needed.

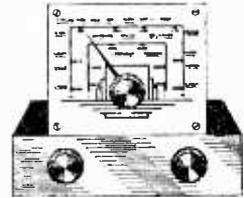

ELECTRONIC PRECISION EQUIPMENT

7, ELECTRON HOUSE
RUISLIP MANOR, MIDDX

SENSATIONAL DEVELOPMENT of The New 1355 Conversion



SOUND, VISION, TIME-BASES, POWER PACK and SPEAKER on One 1355 Chassis.

Data for ALL FIVE TV CHANNELS, 3/- ACCUMULATORS.—Brand New, Multi-plate, in unspillable

celluloid cases (3 1/4 in. x 1 1/4 in. x 4 in.), 7 A.H., 2v., 5/11.
RECEIVER & VIBRATOR PACK 21.—Complete with 9 valves, BFO, crash limiter and circuit, these cover 4.2-7.5 and 18-31 mc/s. but may have slightly damaged switch spindles (wafers intact); pack delivers approx. 140v. at 40 mA. from 6v. input. 37/6 complete.

VIBRATOR PACK 21.—Soiled, for stripping, 9/- P.F.
TRANSMITTER 21.—Complete with panel, control box, key, valves, circuit, etc., the above two units may be remounted behind the panel to form a complete station. For CW, MCW or speech transmission, these also cover 4.2-7.5 and 18-31 mc/s. PA coils (but NOT formers) and relays have been removed by Ministry of Supply, but may easily be replaced. In first-class condition. 25/-.

AMPLIFIER 1135A.—With EF39, EK32, EL32, Twin inputs, output transformer, and suitable for modification into a really fine small PA amplifier. Complete with circuit and our "10 min. Conversion data." 16/6.

POWER PACK KIT.—Suitable for above, with our "revised data"—19/6.

RADIO EXCHANGE CO.

9, CAULDWELL STREET, BEDFORD. Phone 5568

The solder for all HOME TELEVISION CONSTRUCTOR SETS

Designers of television constructor sets know that the efficiency of their equipment depends on the solder used by the constructor—that's why they recommend Ersin Multicore for trouble-free, waste-free soldering. Ersin Multicore, the only solder containing three cores of extra-active, non-corrosive Ersin Flux, is obtainable from all leading radio shops. Ask for Cat. Ref. C.16018, 18 S.W.G. 60/40 High Tin Television and Radio Alloy. The size 1 Carton contains 41 feet of solder, costs 5/-.




Ersin Multicore Solder

In case of difficulty in obtaining supplies, please write to:
MULTICORE SOLDERS LTD.,

MELLIER HOUSE, ALBEMARLE STREET, LONDON. W.1 • R2Gent 1411

THE *New* WINDSOR Television WOBBULATOR

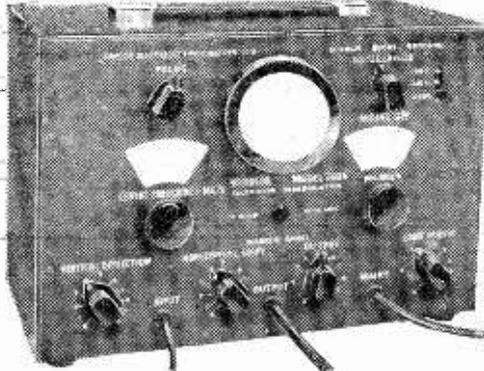

EARLY DELIVERY
Please write for further details and information on other WINDSOR and TAYLOR products.

TAYLOR ELECTRICAL INSTRUMENTS LTD.
419/424 MONTROSE AVENUE, SLOUGH, BUCKS
Telephone : SLOUGH 21381 (4 lines). Grams & Cables : Taylins, Slough

MODEL 260A

The first self-contained electronic instrument providing visual alignment facilities for television receivers. Simple, compact and efficient—its use will save many hours of valuable time in the service department.

FEATURES

- **CARRIER FREQUENCY.** 5-70 Mc/s. 10-140 Mc/s (on 2nd harmonic).
- **BANDWIDTH.** 0-5 Mc/s total. 0-10 Mc/s (on 2nd harmonic).
- **SWEEP FREQUENCY.** 50 c.p.s. sinusoidal, return trace blacked out automatically.
- **OUTPUT.** Adjustable from 0-10 mV. approx. Fixed and variable attenuators are fitted. Output impedance 75 ohms.



CLYDESDALE

Bargains in Ex-Services Electronic Equipment

R.1155 (lower) COMMUNICATIONS RECEIVER features a 7-valve superhet with 1 R.F. stage and 2 I.F. stages (465 K.c.s.), B.F.O., AVC/MVC, C.W. Filter, Cathode Tuning Indicator. An ultra-slow motion drive provides back lash free tuning, the dial scale being graduated in megacycles and kilocycles. Five wavebands cover 18 to 7.5 Mc/s. (20 metre band), 7.5 to 3 Mc/s. (40 and 80 metre bands), 1.590 to 800 K.c.s. (Broadcast band), 500 to 75 K.c.s. (2 L.W. bands).

The present output is taken from a Double Diode Triode (MHLD6) and provides a high impedance output via a 1:1 transformer for use with phones, an end-stage can be added on with great ease to provide L.S. operation.

Complete in a metal case finished in black. Dim. : 16 1/2 x 9 x 9 ins.

CLYDESDALE'S PRICE ONLY £12-12-0

This receiver can be supplied together with an A.C. mains power pack, with integral amplifier—end stage and 8in. speaker. Complete and in a metal cabinet finished in grey, with linking cables, plugs and circuits. Dim. : 14 x 14 x 7 ins.

CLYDESDALE'S PRICE ONLY £18-10-0

2 METRE EQUIPMENT.—This is the R28/ARC5 10 valves VHF Receiver in the same class as the Command Receivers. Frequency coverage, 100 to 150 mc/s. 4 Spot channels are crystal locked and selected by motor tuning.

Valves include : 4717A's (mushroom). These valves have a very favourable signal noise ratio, with high gain. Power requirements 220 v. D.C. 70 ma. H.T. and 28 v. L.T. An excellent basis for a mobile unit.

CLYDESDALE'S PRICE ONLY 37/6

RECEIVER TYPE 6A.—This is a channel checking receiver working on 49/100 metres which includes 5VR91 (EF50), 1.6KB, 1VR55 (EF39) and 1VR53 valves. Included in the circuit is a terminal switch breaking at 88 Degrees F. Enclosed in a metal case.

CLYDESDALE'S PRICE ONLY 45/-

SINGLE ENDED MODULATOR.—The BC-456 is a speech modulator which can be modified for use from A.C. Mains supply, ample room being available on the chassis for the installation of the power pack. Sufficient modulation to swing a 35-watt carrier is available, just right for that single-ended 807 rig. The unit employs a 1.625 directly-driven, A 12J5 side-tone monitor, a VR150/30. Components include : transformers, chokes and relays. Chassis dimensions : 10 1/2 x 7 1/2 x 4 1/2 ins.

CLYDESDALE'S PRICE ONLY 19/6 (less dynamotor)

INFRA-RED IMAGE CONVERTER CELL.—Sniper-scope, Snooper-scope. This cell converts images bathed in infra-red light into normal visible objects.

CLYDESDALE'S PRICE ONLY 12/6 each **POST PAID TELEVISION**

VIEWING UNIT.—Indicator 6 Series. These units are brand new in excellent condition and are fitted with a VCR97 Cathode ray tube which is ideal for "INEXPENSIVE TELEVISION" circuits. Valves include : 4BF50, 3EB34, plus a host of T.V. components including EHT condensers and potentiometers. Enclosed in a metal box 18 x 8 1/2 x 7 1/2 ins.

CLYDESDALE'S PRICE ONLY £3-19-6 **CARRIAGE PAID**

Please include 10/- for transit case to ensure safe transit of unit. Refund of 10/- on return of case.

FOR VIEWING.—Indicator Unit Type 62 contains a VCR97 Cathode Ray Tube with a mu-metal shield plus a host of other components suitable for the TV constructor and the following valves make suitable spares for the R1355 : 18/SP61's, 2/EB34's, and 2/EA50's.

The complete unit is housed in a metal retainer 18 x 8 1/2 x 11 1/2 ins.

CLYDESDALE'S PRICE ONLY 67/6 each **POST PAID**

I.F. VIDEO RECEIVER. The Ex-R.A.F. R1355 provides an excellent I.F. strip for both vision and audio reception and is fitted with a recess into which the R.F. Unit fits. An integral 250 A.C. Mains power pack can be fitted into the position on the chassis previously occupied by the high freq. power unit located at rear of receiver.

The R1355 is complete with valves—5 stages of I.F. at 7.5 Mc/s. (SP61's), Detector (EA50), Video Amplifier (SP61) and Cathode Follower (SP61)—EHT rectifier (SU2150) and H.T. rectifier (3U4G). Complete in metal case 18 x 8 1/2 x 7 1/2 ins.

CLYDESDALE'S PRICE ONLY 67/6 **CARRIAGE PAID**

RADAR REPEATER AMPLIFIER.—The AN/APA-1 Repeater Amplifier constitutes a self-contained unit housed within a black crackle finished cabinet and comprises an 11-valve line-up—7.6SN7GT, 616, 6G5, 2X207B, and a 6X5. The integral power pack is suitable only for 110/120 v. 50/2,000 Cy.

A separate assembly houses the 3BP1 cathode ray tube. **CLYDESDALE'S PRICE ONLY £4-19-6** each **CARRIAGE PAID**

Order direct from :

CLYDESDALE SUPPLY CO. LTD.

2, Bridge St., Glasgow, C.5. Phone : SOUTH 2706/96
Visit our Branches in Scotland, England and N. Ireland.

British Radio Components Show

Preliminary Details of This Year's Exhibition of Spare Parts

THE eighth annual private exhibition of British radio and electronic components, to be held by the Radio and Electronic Component Manufacturers' Federation at Grosvenor House, London, from April 10th to 12th, gives every sign of being as successful as the 1950 exhibition, which was attended by over 20,000 visitors from 21 countries.

Over 100 firms have arranged to take part in the exhibition, which has been carefully arranged to give an improved layout of the stands and better provision for the comfort of visitors.

The important contribution made by the industry to Britain's defence programme is borne out by the display of special components and apparatus made to conform to Service requirements. Valves are again included in the exhibition.

The following components and apparatus are being shown for the first time.

Capacitors

New moulded casings, giving complete protection against moisture, have been developed by A. H. Hunt Ltd. (Stand 20), and by the Telegraph Condenser Co. (Stand 44). These new types of sealing have been applied to ceramic, tubular foil, and silvered mica capacitors, and a complete range is available.

The Telegraph Condenser Co. have also improved their "Plastapack" plastic film capacitors, which are particularly suitable for use in electronic counting circuits and computers.

Notable this year is an entirely new and completely satisfactory method of sealing ceramic, stacked foil, and silvered mica condensers. Each condenser is mounted in a moulded casing which is then filled with a specially developed plastic-immersion sealing ("Plimoseal"). This method enables the 100 per cent. humidity, 100 deg. C. requirements of "Category A" Ministry specifications to be met.

Electrolytic Condensers

The comprehensive range of wet and dry electrolytics of all-aluminium construction will be on view and is sure to be of interest to manufacturers, engineers and traders alike. Also distinctive types of single, dual, and triple section "Lectropacks" in standard or twist prong mounting, together with Micropacks and the miniature Picopacks, all with the guarantee associated with T.C.C. standards of quality ensuring a long and trouble-free life.

Resistors

The high-stability carbon resistors introduced last year by Painton & Co. (Stand 62) have been improved in the higher ohmic values to give greater stability, and are now available up to 1.0 megohms in half-watt rating. A new type of

compact audio-frequency fader resistor is now being made.

An outstanding new development of the British Electrical Resistance Co. (Stand 59) is a hermetically-sealed potentiometer particularly intended for use in severe atmospheric conditions and in corrosive atmospheres. This is rated at 5 watts with resistances up to 50,000 ohms, and conforms to Service standards.

A scaled potentiometer of the midget type (Code GS) has also been developed by the Morganite Resistor Co. (Stand 54), who are noted for their range of very small diameter variable resistors.

Eric Resistor Ltd. (Stand 24) have produced the first fully-insulated grade I resistor of high-stability cracked carbon, suitable for operation under tropical or other severe conditions. It is made in three ratings: $\frac{1}{2}$, $\frac{1}{4}$ and $\frac{1}{8}$ watt, and in the usual range of values from 10 ohms to 3 megohms.

Other Components


A. F. Bulgin (Stand 21) are introducing a new range of control knobs suitable for high-quality radio cabinets, together with small lever and dial knobs for

special apparatus.

A new mains voltage signal lamp for panel fitting uses a standard 15-watt sign lamp in an all-insulated holder behind a moulded glass lens.

A new vibration-proof combined screw and lock-washer is marketed by Guest, Keen and Nettlefold (Stand 106), in which the washer cannot become detached from the screw, but is nevertheless free to operate effectively.

(Continued on page 215)

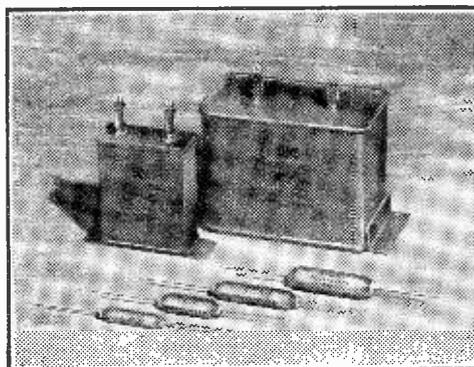

The new T.C.C. components which are being shown for the first time. The large items are the new Plastapack condensers in high values, whilst the small items are low values in the same form.

LIST OF EXHIBITORS AND STAND NUMBERS

| <i>Exhibitor</i> | <i>Stand No.</i> | <i>Exhibitor</i> | <i>Stand No.</i> |
|---|------------------|--|------------------|
| A.B. Metal Products, Limited..... | 36 | Long and Hambly, Limited..... | 16 |
| Acoustic Products, Limited..... | 56 | Magnetic and Electrical Alloys, Limited..... | 33 |
| Advance Components, Limited..... | 73 | Marconi Instruments, Limited..... | 97 |
| Antiference, Limited..... | 68 | McMurdo Instrument Co., Limited..... | 70 |
| Associated Iliffe Press, Limited..... | 112 | Measuring Instruments, Limited..... | 109 |
| Associated Technical Manufacturers, Limited.... | 74 | Micanite and Insulators, Limited..... | 41 |
| Automatic Coil Winder and Electrical Equipment Co., Ltd. | 86 | Morgan Bros. (Publishers), Limited..... | 85 |
| Belling and Lee, Limited..... | 12 | Morganite Resistors, Limited..... | 54 |
| Bird, Sydney S., and Sons, Limited..... | 8 | Mullard Electronic Products, Limited (Components) | 31 |
| Birmingham Sound Reproducers, Limited..... | 66 | Mullard Electronic Products, Limited (Valves).... | 101 |
| Bray, Geo., and Co., Limited..... | 111 | Multicore Solders, Limited..... | 17 |
| British Electric Resistance Co., Limited..... | 59 | Murex, Limited..... | 100 |
| British Insulated Callenders Cables, Limited..... | 57 | Mycalex Co., Limited..... | 83 |
| British Mechanical Productions, Limited..... | 27 | Oliver Pell Control, Limited..... | 25 |
| British Moulded Plastics, Limited..... | 88 | Painton and Co., Limited..... | 62 |
| British N.S.F. Co., Limited..... | 61 | Parmeko, Limited..... | 32 |
| British Rola, Limited..... | 48 | Partridge Transformers, Limited..... | 55 |
| Bulgin, A. F., and Co., Limited..... | 21 | Permanent Magnet Association..... | 84 |
| Bullers, Limited..... | 75 | Plessey Co., Limited..... | 64 |
| Carr Fastener Co., Limited..... | 60 | Plessey International, Limited..... | 65 |
| Clarke, H., and Co. (Manchester), Limited..... | 105 | Pye, Limited..... | 107 |
| Colvern, Limited..... | 51 | Reliance Electrical Wire Co., Limited..... | 22 |
| Cosmocord, Limited..... | 71 | Reslosound, Limited..... | 23 |
| Daly (Condensers), Limited..... | 81 | Salford Electrical Instruments, Limited..... | 35 |
| Dawe Instruments, Limited..... | 49 | Sangamo Weston, Limited..... | 87 |
| Decca Record Co., Limited..... | 94 | Scharf, Erwin, Limited..... | 52 |
| De La Rue, Thomas, and Co., Limited (Plastics Div.) | 96 | Scott, Geo. L., and Co., Limited..... | 103 |
| Diamond 'H' Switches, Limited..... | 3 | Simmonds Accessories, Limited..... | 30 |
| Dubilier Condenser Co. (1925), Limited..... | 29 | Stability Radio Components, Limited..... | 78 |
| Du Bois Co., Limited..... | 2 | Standard Telephones and Cables, Limited (Components) | 10 |
| Duratube and Wire, Limited..... | 40 | Standard Telephones and Cables, Limited (Valves) | 7 |
| Edison Swan Electric Co., Limited..... | 38 | Static Condenser Co., Limited..... | 77 |
| Egen Electric, Limited..... | 26 | Steatite and Porcelain Products, Limited..... | 28 |
| Electro Acoustic Industries, Limited..... | 58 | Suflex, Limited..... | 6 |
| Electrothermal Engineering Co., Limited..... | 102 | Supply, Ministry of..... | 92 |
| English Electric Co., Limited..... | 95 | Symons, H. D., and Co., Limited..... | 110 |
| Enthoven, H. J., and Sons, Limited..... | 47 | Taylor Electrical Instruments, Limited..... | 1 |
| Erie Resistor, Limited..... | 24 | Taylor Tunnicliffe (Refractories), Limited..... | 5 |
| Ever Ready Co. (Great Britain), Limited..... | 82 | Telegraph Condenser Co., Limited..... | 44 |
| Ferranti, Limited..... | 9 | Telegraph Construction and Maintenance Co., Limited | 50 |
| Fine Wires, Limited..... | 108 | Telephone Manufacturing Co., Limited..... | 45 |
| Garrard Engineering and Manufacturing Co., Limited | 69 | Thermo Plastics, Limited..... | 14 |
| General Electric Co., Limited..... | 93 | Truvox Engineering Co., Limited..... | 19 |
| Goodmans Industries, Limited..... | 18 | Tucker, Geo., Eyelet, Limited..... | 4 |
| Guest, Keen and Nettlefold (Midlands), Limited.. | 106 | Vitavax, Limited..... | 43 |
| Hallam, Sleigh and Cheston, Limited..... | 104 | Walter Instruments, Limited..... | 80 |
| Hellermann Electric, Limited..... | 42 | Walter, J. and H., Limited..... | 79 |
| Hunt, A. H., Limited..... | 20 | Wego Condenser Co., Limited..... | 34 |
| Igranic Electric Co., Limited..... | 72 | Welwyn Electrical Laboratories, Limited..... | 11 |
| Imhof, Alfred, Limited..... | 89 | Westinghouse Brake and Signal Co., Limited..... | 13 |
| Jackson Bros. (London), Limited..... | 37 | Weymouth Radio Manufacturing Co., Limited.... | 46 |
| London Electric Wire Co. and Smiths, Limited.... | 76 | Wingrove and Rogers, Limited..... | 53 |
| London Electrical Manufacturing Co., Limited.... | 39 | Wireless Telephone Co., Limited..... | 63 |
| | | Woden Transformers, Limited..... | 67 |
| | | Wright and Weaire, Limited..... | 15 |

(Continued from page 213)

Test Instruments

Taylor Electrical Instruments Ltd. (Stand 1) are exhibiting three new models in their range of test instruments. Types 72A and 77A are universal test meters in the moulded cases with overload protection. The design of the meters was undertaken by a firm of industrial designers, and the result is a pleasing and efficient appearance. Type 88A is a larger type of test meter in a wooden case with a single linear scale for all ranges.

An interesting exhibit is the quartz crystal activity test set manufactured by Salford Electrical Instruments Ltd. (Stand 35), which in addition to measuring the activity of crystals can also measure the dynamic resistance of parallel-tuned circuits, giving a direct indication.

Dawe Instruments Ltd. (Stand 49), whose range of test equipment is well known, are showing a new high-speed level recorder (Type 1406), which provides a means of rapidly recording response characteristics with an accurate logarithmic scale. This is particularly suitable for amplifier testing. Another new instrument is the peak strain gauge for determining the maximum strain imposed on mechanical structures.

Other Items of Interest

A new type of magnetic high-fidelity pick-up—the "Minuette"—is shown for the first time by the Edison Swan Electric Co. (Stand 38).

The Telegraph Construction & Maintenance Co.

(Stand 50) manufacture a new type of air-spaced coaxial cable, having a helical membrane applied edge-on to the conductor. This construction is robust and results in an effective dielectric constant of 1.08. The cable is particularly suitable for wide-band transmission. Other new developments include "Permendur"—a special alloy with the highest known magnetic induction (24,000 lines), and a nickel-copper alloy substitute LM.326.

The production of zirconium on a commercial scale has recently been attained by Murex Ltd. (Stand 100), and it is now available in rod, sheet or wire form. It has a high melting point and excellent corrosion resistance, and is particularly suitable as an alternative for tantalum or molybdenum in certain applications.

The main features of the G.E.C. exhibit will be Osram valves and other electronic devices. In the valve field will be a complete range of miniature valves for battery-operated A.C. and D.C./A.C. receivers. Outstanding in this group of valves is the X79 triode-hexode frequency changer for A.C. use; the X17 heptode frequency changer, which gives excellent short-wave performance with a wide range of battery voltages. For D.C./A.C. uses the X109 triode hexode is also very good on the short wavelengths.

High-slope output pentodes are represented by the N78 (for A.C.) and the N108 (for D.C./A.C.), both with a conductance of 10 mA/v.

A number of special types of valves will be shown and there will be a particularly strong exhibit of voltage and current stabilizers, including some of the "Stabilivolt" type.

CANBERRA—ATLANTIC CROSSING

THE English Electric Canberra which set up the fastest time for a transatlantic crossing, on February 21st, 1951, was fitted with a radio installation designed to meet the very special requirements of this unique aircraft.

To ensure that the Canberra's fighter-like performance and manoeuvrability are not impaired by the usual protruberances associated with aircraft wireless aerials, the suppressed direction-finding loop recently designed by Marconi engineers was employed, and the radiator for the high-power communications transmitter was a special type of buried antennae, designed by the Royal Aircraft Establishment in conjunction with the Marconi Company.

A.D. 106/108

The radio equipment carried by the Canberra on this flight consisted of the A.D.107 high-power transmitter, the A.D.108 receiver and the A.D.7092A automatic radio compass. All this equipment, which was originally designed for the aircraft of the British Air Lines Corporations using normal types of aerials, gave a performance under the exacting conditions of high altitude, high-speed flight, which enabled the aircraft to remain in perfect communication when 1,500 miles out over the Atlantic. The use of the suppressed D.F. loop in no way reduces the ranges at which good bearings can be taken, and on this flight the navigator of the Canberra was obtaining navigational aid from the radio compass

when the aircraft was 500 miles from the Newfoundland coast.

T1154 and R1155

The Marconi Company is proud of its association with this great flight and especially as this is the first occasion on which the Royal Air Force have used the successors of the famous T1154/R1155 equipment which, introduced by Marconi's in 1939, became standard equipment for every type of British bomber and flying boat used during the War. The T1154/R1155 is still the standard equipment for the British heavy aircraft used by the R.A.F., and it is gratifying that the performance of the new equipment installed in the Canberra should have followed in the great tradition.

Books Received

RADIO LABORATORY HANDBOOK.

By M. G. Scroggie, B.Sc. M.I.E.E. 430 pp., 216 illustrations. Published by Hiffe & Sons, Ltd., Dorset House, Stamford Street, S.E.1. Price 15s.

THE RADIO LISTENERS' WEEK-END BOOK.

By John Pringle. 288 pp., illustrated. Published by Odhams Press Ltd., Long Acre, London, W.C.2. Price 6s. 6d.

TELEVISION RECEIVING EQUIPMENT.

Third Edition. By W. T. Cocking, M.I.E.E. 374 pp., illustrated. Published by Hiffe & Sons, Ltd., Dorset House, Stamford Street, S.E.1. Price 18s.

OXFORD JUNIOR ENCYCLOPEDIA.

(Vol. IV—Communications.) 495 pp. Published by Oxford University Press. Price 30s.

THE object of this article is to provide the constructor with some practical ideas on the subject of Public Address, and it is therefore proposed to discuss points which arose from the construction of apparatus now in regular use by the author.

Cost has been kept to a minimum consistent with reliability, and advantage has been taken, where possible, of the ex-W.D. surplus readily available.

In view of the fact that the outfit was liable to transportation to various halls in the district, the probability of encountering either A.C. or D.C. mains supply was real. Therefore it was obvious that the amplifier must be designed on "universal" principles if it was to be suitable.

Probably the main disadvantage is that in common with most universal designs, under certain supply conditions the chassis may be "live." Reasonable care on the part of the operator must therefore be taken to ensure correct polarity of the mains plug when on A.C. If D.C. supply is used, the amplifier will not function unless polarity is correct, automatically rendering chassis safe.

Design

With the universal arrangement, the A.C. mains transformer is eliminated thus considerably reducing expenditure. This in turn means that the H.T. is limited by the value of the mains supply voltage, which if designing a high-power outfit would be a considerable disadvantage. However, 10 or 15 watts of audio is readily available with a

P.A. for the

Description of a Complete Universal Unit for

By S. A. DE

230 volt supply and this is more than sufficient for use in the average hall likely to be encountered. Also, the cost of a loudspeaker large enough to handle powers in excess of this figure would mean an expenditure not proportional to the results obtained.

It was considered an advantage to construct a pre-amplifier as a separate unit for two reasons. One, because it is only required when a microphone in addition to record reproduction is wanted. Two, in the interests of efficiency it is wise to keep this high-gain sensitive unit quite separate from the main amplifier, and thorough screening is also highly desirable.

The circuits are quite straightforward and no originality is claimed, except perhaps in their application, and through the article emphasis is on the practical rather than theoretical.

The Main Amplifier

The function of VC1 in Fig. 1 is to provide a control for setting the level at which it is desired to operate the amplifier. Individual

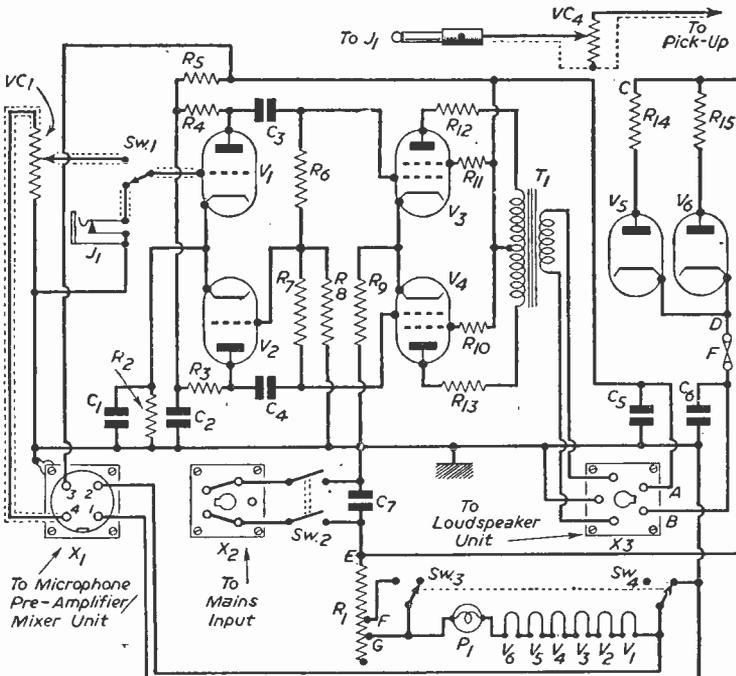


Fig. 1.—Circuit of the main amplifier section.

**LIST OF COMPONENTS
A.C./D.C. AMPLIFIER.**

- Resistances. All $\frac{1}{2}$ watt rating unless otherwise stated.
- R1—3A. mains-dropper with fixing feet and variable tap.
- R2—1.5 k Ω .
- R3, R4—100 k Ω .
- R5—10 k Ω .
- R6, R7, R8—250 k Ω .
- R9—125 Ω 5 watt.
- R10, R11—100 Ω .
- R12, R13—100 Ω 1 watt.
- R14, R15—100 Ω 3 watt.

- Capacitors.
- C1—25 μ F. 25 v.w. Elec.
- C2—8 μ F. 350 v.w. Elec.
- C3, C4—1 μ F. 350 v.w. Tub.
- C5, C6—16-16 μ F. 500 v.w. Elec.
- C7—1 μ F. 500 v.w. Mica.

- Valves.
- V1, V2—6J5/GT.
- V3, V4—KT33C.
- V5, V6—6V6.
- VC1—5M Ω potentiometer.
- VC4—5M Ω potentiometer (on turntable unit).
- F—250 mA. fuse and holder.
- J1—Closed circuit jack (and two plugs).
- P1—6v. 3A. pilot lamp and holder.
- 6 International octal valve holders.
- T1—Output transformer 40 : 1 (Premier "Match-maker," MO.15).
- SW1—S.P.D.T. toggle.
- SW2—D.P.S.T. toggle.
- SW3/SW4—D.P.D.T. toggle.
- X1, X2, X3—Connectors (see text).
- Sheet metal for chassis (20 s.w.g. Alclad or similar.)
- Paxolin and solder tags for component board.
- Sleeving, connecting wire, screws, nuts, grommets, knob, scale, screened wire, etc.

Amateur

all Public Address Requirements

VEY

microphone and gramophone gain controls are incorporated in the pre-amplifier unit.

It will be observed that when SW1 is down, i.e. grid drive being supplied via J1 from a gramophone pick-up source, there appears to be no method of volume control, and likewise no grid leak for V1. The reason for this is that control of audio level is desirable from the point where the operator's attention is most required—at the gramophone turntable. This method of control is shown at the bottom of Fig. 1 and VC4 is mounted in the turntable case.

Two U31's are used in parallel for V5 and V6 for the reason that current consumption of the amplifier exceeds the rating of one valve. It is wise to include the surge limiting resistors R14 and R15 to safeguard these valves in the event of a fault developing.

If it is intended that the amplifier is to be used solely on D.C. mains, then V5 and V6 need not be incorporated, the point marked C on Fig. 1 being connected directly

to D. It is important, however, that in the event of this being done, the dropping resistor R1 be adjusted to compensate for the exclusion of the two 26-volt filaments.

To calculate value of R1, assume SW3/SW4 in position shown (i.e., filaments of pre-amplifier not in circuit). The value of EG in ohms will be that which will drop the mains voltage to a value equal to the sum total of the filament voltages of V1, V2, V3, V4, V5, V6 and P1.

| | | |
|---------------|-----------------|-----------|
| V1, V2 and P1 | are 6.3 v. each | = 18.9 v. |
| V3 V4 | are 25.0 v. ,, | = 50.0 v. |
| V5 V6 | are 26.0 v. ,, | = 52.0 v. |

Total = 120.9 v. say 121 v.
Therefore, the required voltage drop across EG

LIST OF COMPONENTS PRE-AMPLIFIER/MIXER

Resistances. All $\frac{1}{2}$ watt rating unless otherwise stated.

- R16—250K Ω .
- R17, R20—50 K Ω .
- R18, R21, R22—100 K Ω .
- R19—2.5 K Ω .
- R23—1.5 K Ω .
- R24, R25—.5 M Ω .

Capacitors.

- C8, C9—.5 μ F. 350 v.w. Tub.
- C10, C13—25 μ F. 25 v.w. Elec.
- C11—.01 μ F. 350 v.w. Tub.
- C12—8 μ F. 350 v.w. Elec.
- C14—.05 μ F. 350 v.w. Tub.

Valves.

- V7—6J7/GT.
- V8—6SL7 (see text).
- VC2—.5 M Ω potentiometer (small).
- VC3—.5 M Ω potentiometer (small).
- J2, J3—Closed circuit jacks.
- P2—6.3 v. .3A. pilot lamp and holder.
- T2—Microphone input matching transformer.
- 2 International octal valve holders.
- 1 valve cap.
- SW5—D.P.S.T. toggle.
- X4—Connector (see text).

Sheet metal for box (20 s.w.g. Alclad or similar).

Paxolin and solder tags for component board.

Sleeving, connecting wire, screws, nuts, grommets, 2 scales, 2 knobs, screened wire, etc.

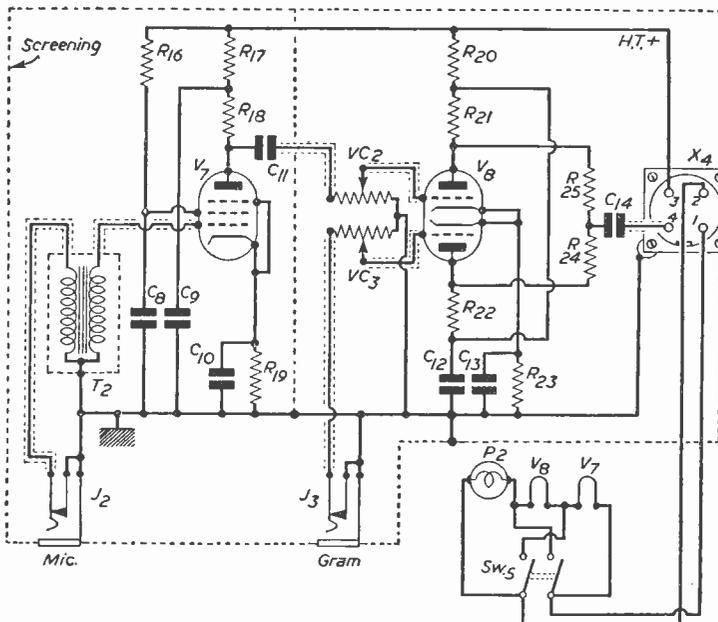
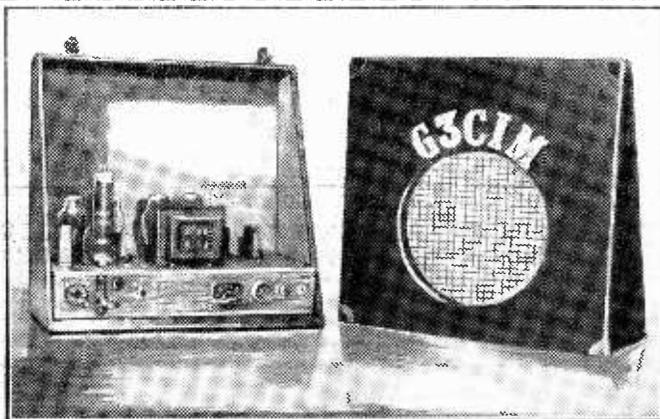


Fig. 2.—Circuit of the pre-amplifier/mixer unit.

will be the mains supply voltage minus 121 v. Assuming the former to be 230 v., this will be 230-121=109 v. The value of EG in ohms will be $R = \frac{E}{I}$ where I is filament current, i.e., .3 A.

Therefore, $R = \frac{109}{.3}$ ohms = 363.3Ω. Now if the pre-amplifier is put into circuit, SW3/SW4 is

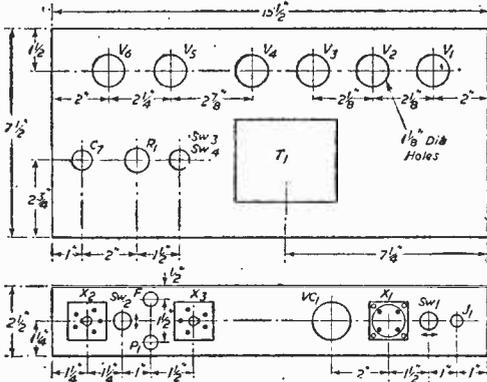


Fig. 4.—Cutting and drilling details of the chassis.

thrown. SW4 opening up the heater line and SW3 short-circuiting part of R1 to allow more voltage to be available. The value of FG in ohms being calculated as follows: Additional voltage required = V7, V8 and P2=6.3 v. each=18.9 v. total.

$$FG = R = \frac{18.9}{.3} = 63\Omega.$$

It is necessary that some method be used to link up the various units of the outfit, and probably the constructor has ideas of his own on this subject. On reference to Fig. 1, three connectors are shown marked X1, X2, X3. Their function is as follows.

X1 serves to make the necessary connection between the pre-amplifier and the main amplifier. Pins 1 and 2 are filament supply, Pin 3 H.T., Pin 4 grid input (use screened lead) and the chassis line is via the metal screw connector and "breeze" connecting cable. X2 connects amplifier to mains supply.

X3 connects audio output to loudspeaker; also H.T. to loudspeaker energising.

These connectors are clearly shown in the

photographs and were obtained from radio surplus shops. X1 is a "breeze" connector. X2 and X3 were taken from a stripped ex A.M. I.F.F. unit.

It is, of course, not necessary that the constructor should use exactly the same method as that described, and provided the method used has the same function, all will be well. The main point to remember is that the grid lead between Pin 4 and the pre-amplifier must be screened, and the screening connected to chassis at each end.

One disadvantage of the mains-energised loud-speaker is that a fair quantity of multicore cable is needed, so if the constructor wishes to utilise a P.M. type, it will be necessary to connect an L.F. smoothing choke between points A and B in Fig. 1, to replace the energising coil on the speaker. This should be in the region of 15 Henrys with as low a resistance as possible, and in any case not more than 500Ω.

The author used an R.G.D. 10in. energised type, mainly because a quantity of suitable cable was available. Any good quality P.M. 10in. will be suitable.


For the sake of neatness the constructor is strongly advised to make up a component board as shown in Fig. 3(b). First obtain a strip of paxolin 5 1/2 in. x 2 in. and lay the components on the board, then with a pencil mark the position where solder tags are required. It is simplicity itself to drill the 4BA clearance size holes, insert the tags and punch over. The board can then be wired up on the bench with comfort, and fitted in the chassis with ease.

Chassis

Little need be said on the metal work. The author made up the chassis with the aid of a bench vice, mallet, length of angle iron, block of wood and a small square. Figs. 4 and 5 provide all the necessary data for the construction of a chassis similar to the author's. Aluminium was not used because in the view of the author it is difficult to work with. Its inherent softness causes it to "tear" when using cutting tools.

Pre-amplifier/Mixer Unit

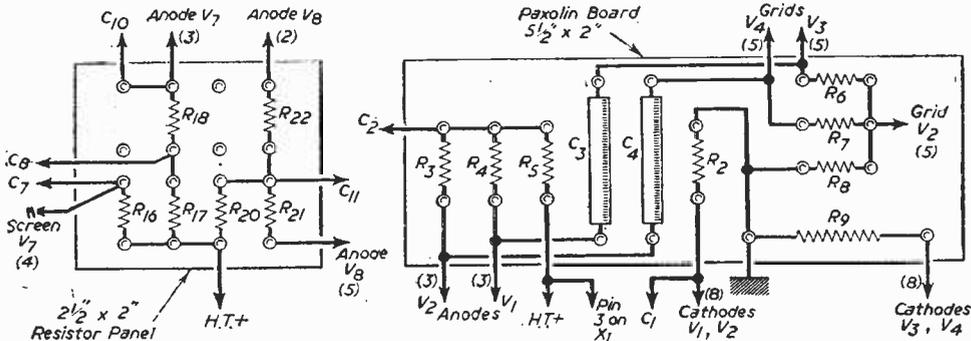The intention when building this compact little unit, was to be able to use it in conjunction with an amplifier having a 6 volt filament supply, and the universal amplifier just described. Some means was therefore needed whereby the valve filaments could be quickly connected in series or parallel.



Figs. 3 (a) and (b).—Details of the component mounting boards.

S.W.5 in Fig. 2 carried out this operation simply and efficiently. It consists of a small bakelite toggle switch purchased together with all the other switches, from the radio surplus dealer.

With the switch open as shown, the filaments are connected in series for use with the universal amplifier.

With it closed, the filaments are connected in parallel for use with a 6 volt supply.

Possibly, a 6SN7 would be an ideal valve for VS from the point of view of characteristics, particularly when used with a 6 volt filament supply. Unfortunately, however, it is unsuitable for series connection, due to its high heater current (.6 A) and therefore a compromise has to be made if it is desired to utilise the pre-amplifier with the two kinds of filament supply.

The 6SL7 has a .3 A filament and the base connections are the same as for the 6SN7 and can be substituted without complication.

It should be noted that the 6SL7 is a high μ valve, and the stage gain is slightly more than is necessary, but its performance proved quite satisfactory and it was therefore permanently substituted.

It will be observed that X4 is a "breeze" connector and is identical to X1 used on the main amplifier, shown in Fig. 1 and described in the text earlier.

As with the main amplifier, it is desirable to make up a component tag board before assembly, as in this instance particularly there is not a great deal of space available for welding a soldering iron inside the box. Reference to Fig. 3 (a) will show the component layout.

Further reference to Fig. 2 shows the microphone transformer T2. This should be small physically and preferably have a mu-metal cast case. It is usual for the microphone manufacturer to supply a correct matching transformer for use with his product, and it is wise to inquire about this when making the purchase.

Mixing control is provided by VC2 and VC3, and the combined signal passed via C.14 to the main amplifier for further amplification.

Figs. 5 and 6 provide all the necessary information on the metal work, and the photograph gives a general view of the complete unit.

The Carrying Case

As can be observed from the photograph on page 217, the carrying case is built in two halves, these are connected together by the hinges, and two case catches. The hinges are the type which allow the two halves of the case to separate.

It is not proposed to describe the carpentry. The author, recognising his limitations in this direction, enlisted the help of a cabinet-maker friend, and satisfied himself with the covering operation and generally finishing off.

In view of the fact that there is a considerable

area to cover, it is advisable to use carpenter's glue, as this is economical and more convenient to use.

The method of covering depends to a great extent upon the amount, and shape of the artificial leather cloth available, but a good plan is to cut two big squares first, and cover the front and back, gluing over the edges about an inch flange all round. Next cover the ends with pieces cut to the correct size.

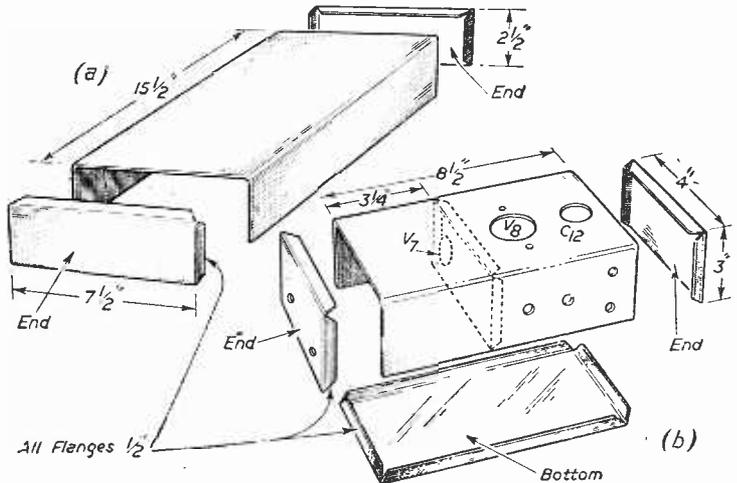


Fig. 5.—Chassis construction details.

The loudspeaker hole should then be cut out, leaving sufficient at the edge to cut star fashion and glue inside the rim. A strip of roxine 1/4 in. wide should then be glued right round the inside of the rim.

Purchase, and fit, the corner protectors and the rubber feet.

(To be continued.)

NOW READY!

The Entirely New 12th Edition of The Famous Standard Work

THE PRACTICAL WIRELESS ENCYCLOPÆDIA

By F. J. CAMM

Considerably enlarged, amplified and entirely re-written and re-illustrated. Complete Television Section, with theoretical and constructional data.

All the facts, figures, and constructional data of Radio and Television—Definitions, Terms, Units—Principles, Circuits, etc.

Over 300,000 copies sold!

Price 21/- or 21 10 by post from:

GEORGE NEWNES LTD., Tower House, Southampton Street, Strand, W.C.2.

For the Transmitter

2-metre P.A. Efficiency

How to Obtain More Efficiency in your Transmitter at V.H.F.

By C. ELLIOTT

MANY amateurs are using the 832 or 832A twin tetrode power amplifier tube for the P.A. stage in their transmitters on 2 metres. The 832 is specially designed for V.H.F. work up to 250 Mc/s, and is readily obtained from government surplus sources at a reasonable price, so is consequently very popular. The power input generally has to be limited to about 36 watts and the corresponding R.F. output is given by the manufacturers as 26 watts, under the correct operating conditions. The actual power supplied to the aerial system, however, will depend on the efficiency of the P.A. tank circuit and of the method of coupling to the aerial, and, consequently, in many cases nothing like the 26 watts finds its way into the aerial system.

Another source of inefficiency frequently lies in the system of modulation. Many experimenters have found that the 832 is a difficult valve to modulate by the usual plate-and-screen system. Whether this is due to difficulties of matching the valve to the modulator load or lack of driving power to the P.A. or other causes is not clear. A carrier with a low percentage of modulation is of little use on 2 metres for long distance communication, where the average signal strength at the receiving end is very low. One hundred per cent. modulation with plenty of sideband power is required under these conditions to give a solid reasonable signal. Many carriers have been received from time to time at S4 to 5, but have been unreadable on 'phone, due to being only about 70 per cent.

modulated. It is the object of this article to show how one can obtain the maximum R.F. output from the P.A. stage and how the stage can be fully modulated without the use of the expensive plate-and-screen system.

The P.A. Tank Circuit

Of the possible types of circuit which can be used, the type frequently employed, consisting of the well-known centre-tapped coil and condenser combination, is the least efficient. See Fig. 1. The tank coil of, say, 2 turns of 12 s.w.g. wire is about 1½ in. diameter and 1½ in. long, split in the centre to accommodate the aerial coupling coil. When the tuning condenser is adjusted to resonance, the capacity employed is about 4pF for each section. The plate-to-cathode capacity for each section of the 832 is 3.8pF, increasing the total capacity to 7.8pF, and if we include stray capacities in the circuit the total is probably about 10pF on each section of the tuned circuit. Now, the tuned circuit has its own losses, and the power dissipated in this way is subtracted from the total available R.F. power, so that the highest output efficiency can only be obtained by making these losses negligible. It can be shown that greater efficiency can be obtained by making the ratio L/C high, up to a certain value. This limiting value is set by various requirements, such as the need for a "flywheel" effect in the tuned circuit, the minimisation of harmonics, and the prevention of distortion during 'phone operation. In the case of an 832 working

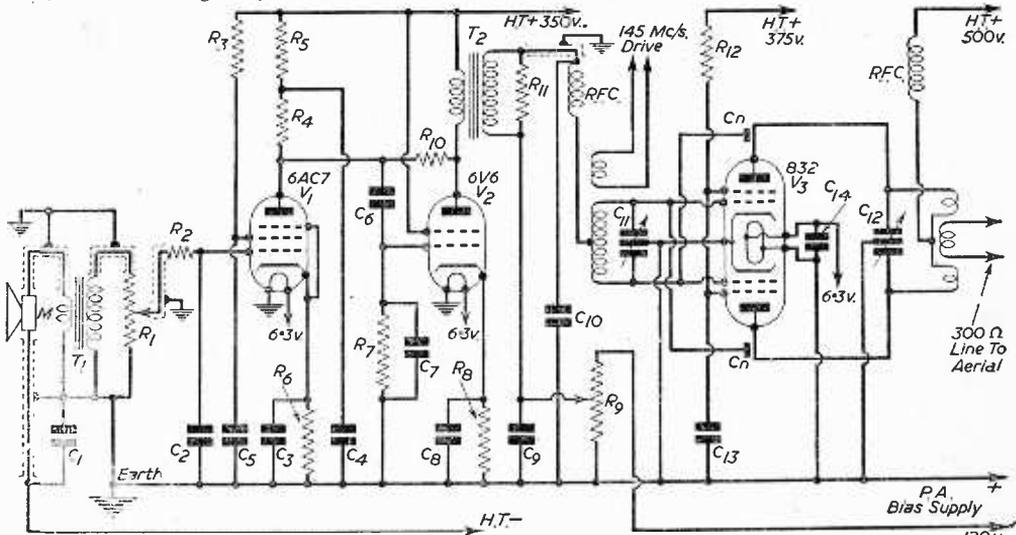


Fig. 3.—Modulator and P.A. stage of grid-and-screen modulated transmitter. Although shown theoretically as coils, the coiled lines feed is actually 'linear.'

at 500 volts on the anodes and passing 70 mA the optimum capacity for each side of the split stator condenser works out at about 3.5pF for 2-metre operation. This figure will be the total capacity required, including anode-to-cathode capacity and stray capacities, but, as we have already noted, the anode-to-cathode capacity itself is 3.8pF, which together with strays probably gives a total of 6pF.

Thus, on 2 metres it is not possible to attain the best L/C ratio, but by practically eliminating a tuning capacity in the tank circuit it is possible to attain a much higher value than that given by a normal tuned circuit. The obvious solution is to use $\frac{1}{2}$ -wave lines for the tank circuit, which are tuned either by a shorting bar and resonate with the anode-cathode capacity exact or by a very small condenser with a swing of 1 or 2pF. Tuning for resonance is rather difficult with a shorting bar, so it was decided to tune by means of a small 4 x 4pF split stator condenser, the capacity in use at the resonance point being only about 0.5pF per section. In linear tank circuits the coupling to the aerial is liable to be less efficient and there may be some loss of R.F. by direct radiation from the lines. It was decided to make use of a circuit which combines the advantages of the tuned coil and linear tank circuit, namely, coiled lines. Coiled lines take up no more space than a conventional coil, while the normal lines take up rather

Construction

The actual construction of the lines is shown in Fig. 2. 14in. of 12 s.w.g. wire are taken for their construction and the exact centre of the length is found. The wire is then folded into a hairpin shape, with a straight section in the centre about 0.6in. long. The two ends are then wound around a

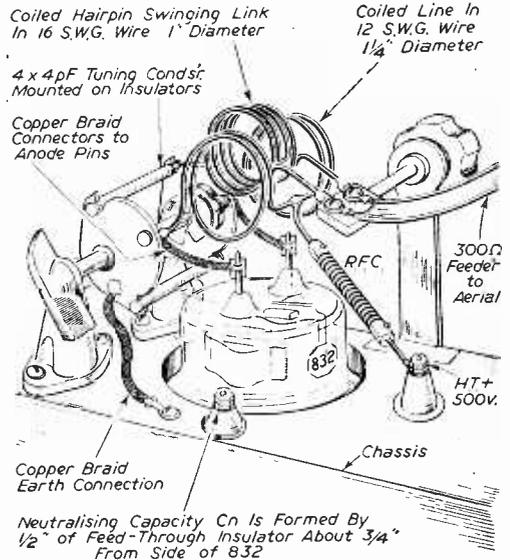


Fig. 2.—Coiled-lines tank circuit.

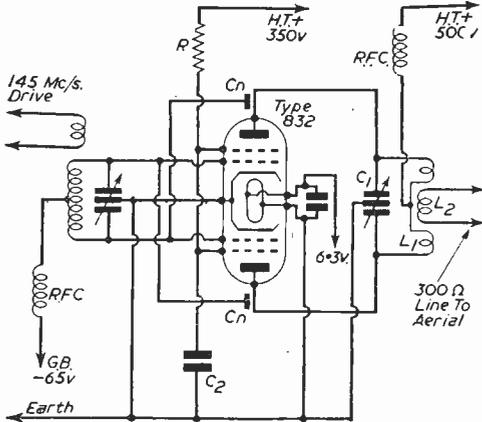


Fig. 1.—An 832 P.A. stage with normal tank circuit.

a lot of room on the chassis (they are generally about 14in. long on 2 metres), and, furthermore, there is less direct radiation from the coiled lines, due to their compact construction, and they should give more R.F. to the aerial circuit.

LIST OF COMPONENTS FOR FIG. 1.

- C1—15 x 15 pF. split stator.
- C2—500 pF. mica (R.F. bypass).
- Cn—Very small neutralising capacity (see Fig. 2).
- R—20,000 ohms.
- L1—2 turns 1 1/2 in. diam., 1 1/2 in. long, 12 S.W.G.
- L2—2 turns 1 in. diam., 1/2 in. long, 14 S.W.G.

suitable former to give a coil about 1 1/2 in. in diameter, winding away from the centre. It can be seen that each half of the winding is in the opposite sense to the other, so that the whole does not form a single inductance, but behaves simply as a normal $\frac{1}{2}$ -wave line. In order to couple the tank circuit to the aerial it is not possible to use a coupling coil of one or two turns, as each half of the tank circuit will induce opposite voltages in the coil and no transference of energy will occur. In the only example of the coiled line which the author has seen the aerial was directly tapped on to the lines via blocking condensers, but this method is not so suitable for making the fine adjustments necessary for optimum coupling and also is not regarded with favour by the Post Office! The best coupling system, as shown in Fig. 3, consists of another coiled line, wound in the same manner as the tank coil and mounted as a swinging link. It is formed with 16 s.w.g. wire by winding on a suitable former to give a coil diameter of about 1in., and each half of the winding contains two turns.

In operation the tank circuit is tuned to resonance by the condenser in the usual manner, and the increased efficiency is immediately apparent, for in the unloaded condition the anode current at resonance will dip to about 25 mA. With the normal tuned circuit of Fig. 1, the resonance dip is about 35-40 mA. The link can then be swung in to give optimum coupling by watching for maximum feeder current or maximum reading on a remote field-strength meter. The loading at 500 v. can

be 70 mA., if one wishes to keep within the manufacturers' specifications, but there is no reason why the input should not be increased to 40 watts (80 mA.), as with the high efficiency of the tank circuit and coupling arrangements this input should be well within the anode dissipation of the 832. Even 50 watts input is just within the capabilities of the tube, the R.F. output then being 36 watts, giving 14 watts to be dissipated at the anodes (rated at 15 watts). This is for C.W. operation, of course. When swinging in the coupling link practically no retuning of the tank circuit should be required if there are no standing waves on the feeders. There is a perceptible resonance dip even when the P.A. is correctly loaded when using coiled lines, but no such dip is noticeable in a normal tank circuit on 145 Mc/s.

The Modulation System

It must be admitted that this modulation system, to be described, was tried out in the first place as a rapid method of getting going on 'phone without the time and expense required for providing a high-level modulator with an output of 20-30 watts, as needed for plate-and-screen modulation. Evidence from other amateurs has shown, however, that the application of 20-30 watts of audio to a 40-watt carrier does not necessarily give 100 per cent. modulation with an 832, but with this particular modified grid-modulation system, 100 per cent. modulation with good communication quality can easily be obtained. The principles of grid modulation have been adhered to on the whole, but the difference lies in the screen circuit of the 832, where the dropping resistor has not been by-passed for audio-frequency, thus enabling the screen voltage to swing up and down as modulation is applied to the grid. (Refer to Fig. 3.) The system is therefore grid-and-screen modulation.

To commence at the modulator end of the circuit, a carbon microphone is used with a 1:50 ratio transformer to feed a 6AC7 in a high-amplification circuit. The whole of the modulator current is taken through the carbon microphone in order to energise it without the use of a battery. As the modulator works Class A, there are no current fluctuations and so no undesirable effects. Stability is ensured by means of the high-capacity by-pass condenser C1. R2 is a stopper resistor and C2 and C7 are R.F. by-pass condensers, all to ensure that no R.F. enters the modulator circuit. Screened wiring is indicated in Fig. 3 at points where it is important that no R.F. currents should be picked up. The 6V6 output valve works at a fairly high bias, produced by a 1,000-ohm cathode resistor, and this is mainly to reduce the anode current, as the full output is not required. It is also important not to saturate the core of the modulation transformer T2 by excessive current. The transformer used by the author was a small 1:3 type, originally designed for directly-fed amplifier stages in receivers, and it handles 25 mA on the primary quite easily.

As for normal grid modulation, it is desirable to use a very low-impedance valve for the modulator (e.g., a triode), for the load on the modulator varies over the A.F. cycle as the rectified grid current of the modulated amplifier changes. However, perfectly satisfactory results are obtained with a 6V6, by using negative feed-back via R10 to reduce the anode impedance and swamping the trans-

former secondary by a load resistor R11. The grid-bias supply should have a very low resistance, to prevent variations in the grid current from opposing the modulation voltages. The potentiometer R9 only offers about 3,000 ohms resistance when correctly set, and this seems to cause no difficulty. The load on the driving stage varies with modulation and a linear modulation characteristic may not be obtained if the R.F. voltage from the driver varies with load. It is sometimes recommended that the driver should supply several times the required driving power, the excess being dissipated by a load resistor across the circuit, the load variations thus being reduced in proportion to the total load. However, on 145 Mc/s the dynamic impedance of circuits is very low and they are, in effect, already loaded, and it was found that no trouble was experienced. Note that C13, in the screen circuit of the

LIST OF COMPONENTS FOR FIG. 3

| | |
|---|-----------------------------------|
| C1—50 μ F, 12v. | R1—500 k Ω pot. |
| C2—100 pF, mica. | R2—10 k Ω . |
| C3—25 μ F, 12v. | R3—500 k Ω |
| C4—8 μ F, 350v. | R4—50 k Ω . |
| C5—0.5 μ F. | R5—10 k Ω . |
| C6—0.05 μ F. | R6—250 Ω . |
| C7—100 pF, mica. | R7—250 k Ω . |
| C8—50 μ F, 50v. | R8—1,000 Ω , 1 watt. |
| C9—2 μ F, 200v. | R9—5,000 Ω , 5 watt. |
| C10—500 pF, mica. | R10—50 k Ω . |
| C11—15 x 15 pF, split stator. | R11—25 k Ω , 1 watt. |
| C12—4 x 4 pF, split stator. | R12—15 to 20 k Ω , 3 watt. |
| C13—500 pF, mica. | |
| Cn—See Fig. 2. | |
| C14—500 pF, mica. | |
| All resistances $\frac{1}{2}$ watt unless otherwise stated. | |
| M—Carbon microphone. | |
| T1—1:50 microphone transformer. | |
| T2—1:3 modulation transformer. | |
| V1—6AC7, V2—6V6, V3—832. | |

832, has a capacity of only 500 pF and is a by-pass for R.F. currents only. The supply voltage to the screen was chosen to give roughly the correct audio load of 15,000-20,000 ohms without exceeding the working voltage of 250 volts.

Setting Up the Circuit for Operation

Adjust the potentiometer R9 to give about 90 volts bias on the 832 and apply drive to the grid circuit so as to give about 80 mA when the P.A. is fully loaded. Swing the link in to give optimum loading, as indicated by feeder current or a remote signal strength meter, and make a final adjustment to the tuning of the tank circuit for maximum output. Now increase the coupling a little so that the observed R.F. output drops, and apply modulation, using R1 as a volume-control. There should be about a 10 per cent. increase in the reading of the feeder current or signal strength meter, and the P.A. anode current should krek upwards to 95 to 100 mA on modulation peaks. If downward modulation is encountered, then coupling to the antenna should be increased. It is possible to modulate successfully at lower values of grid-bias by suitably adjusting the drive, but 90 volts is about the best figure, and very low bias with low drive will again result in downward modulation. The most important adjustment

(Continued at foot of page 224.)


PRATTS RADIO

1070 Harrow Road, London, N.W.10

Tel.: LADbroke 1734.

(Nr. Scrubbs Lane)

AMPLIFIERS READY TO USE.

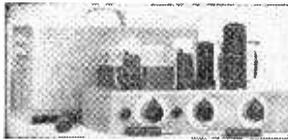

MODEL AC10E (as illustrated). 10 watt, 4 valve unit, neg. feedback, separate mike stage and separate mike and gram inputs, 2 faders and tone control. Input volts, mike .002, gram .21 v., £9-9-0.

MODEL AC18E, 6 valve unit with p/pull output of 191 watts, separate mike stage and separate mike and gram inputs, 2 faders and tone control, feedback over 3 stages, input volts, mike .003, gram .3 v., £13-19-6. **MODEL AC32E**, 6 valve unit with p/p output of 32 watts. Spec. as AC18E, £17-17-0. **MODEL U.10E**, D.C./A.C. mains, P/p output of 10 watts. Spec. as AC18E, £11-15-0. All above are COMPLETE WITH CASES and chrome handles. Outputs match 3, 9 or 15 ohm speakers. **MODEL AC4C**, A.C. or D.C./D.C./A.C., 3 valve, 4 watt amplifier chassis, output to 3 ohms, £5-5-0. All above carriage paid. As supplied to domestic and industrial users since 1945.

SPEAKERS, Plessey, 5in., 12.6. W.B., 2 1/2in., 17.6. 5in., 19-. Goodmans, 12in., 130-. Rola, 8in., 30-. 10in., 35-. 3in., 21-. **RECORD PLAYERS**, Collaro, A.C. only. Rim drive, complete with pick-up, auto-stop. Magnetic £6-9-0. Crystal £6-15-6. **VALVES**, 184, 1T4, 1R5, 1S5, all at 7.3. 25A6, 6V6, 6Z4, 6S6, 6X5, all 8/-, 6J7, 6U5, 6K7, all 5/9. Brand new.


COILS, ETC. Wearite "P" coils, all types, 3/- ea. Weymouth "H" coils, 3/3. Osmer "Q" coil packs, 4/4. Tax paid. Wearite M400 L.F.'s, 10 6 ea. Weymouth P4's, 15/- pair. Denco T.R.F. with reaction L. & M.W., 6/6 pair. Dual range coil with reaction, 4/6. **TRANSFORMERS**, CHOKES, ETC. Mains, 2 x 350 v., 80 m.a., 0-4-5 v., 2 a.; 0-4-6.3 v., 4 amp., 18 6. Dittc, 2 x 250 v., 16 6. **Speaker Transformers**, 6V6 P/P to 3, 8, 15 ohms, 18/-; miniature 184, 354 O/Transfs., 4, 2. **Chokes**, 60 m.a., 20 hy., 380 ohms, 6/9; 20 hy., 100 m.a., 400 ohms, 14/6; 10 hy., 150 m.a., 200 ohms, 14/6; 90 m.a., 10 hy., 180 ohms, 11/6; 40 hy., 20 m.a., 1250 ohms, 5/9.

CONDENSERS (only 1951 stock offered). .001, 2/3.5, all 7d. ea. .01, .05, .001, all 9d. .05, 1 x 500 v., 10/4. B.I. (all 500, 550 v.) .04 mid., 2/9; .8 mid., 3/3; 8+3, 4/9; 16 mid., 4/-; 8+16, 6/-. **MISCELLANEOUS**, Octal bases, Pax., 4d. Amphenol, 6d. Voltage droppers with feet and two sliders, .2 a. 920 ohms or .3 a. 750 ohms, 5/- ea. Linecord (thick good quality type), .3 amp, 3 way, 60 ohms ft., 7d. ft. Presets, 50 pf., 4d.; 100 pf., 1/11; 250 pf., 1/9; 500 pf., 2/-, ETG valve bases, Pax., 9d.

All goods new and unused. No W.D. or manufacturers' surplus components offered. Post paid over 10/-, C.W.O. or C.O.D.

Reception for the connoisseur

THE RC TUNING UNIT

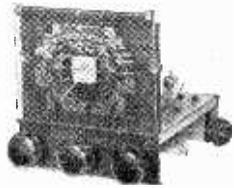

The RC Tuning Unit is a highly sensitive, attractive-looking, 3-waveband, 4-valve unit employing an RF Stage on all bands. It brings in Continental stations, short-wave signals and the BBC Third Programme with remarkable fidelity, even in difficult areas. A switch permits superhet or high quality TRF performance from local stations. Price £14.18.6 (Inc. P.T.). Guaranteed 2 Years.

30-PAGE ILLUSTRATED CATALOGUE of Amplifiers, Tuning Units, Speaker Chambers, etc.

★ Write for YOUR copy TODAY!

PHONE WEstern 3350

Charles
AMPLIFIERS
(SALES) LTD

181, KENSINGTON HIGH ST., LONDON, W.8



FOR PUBLIC ADDRESS, RECORDINGS, AMATEUR RADIO TRANSMITTERS

TYPE MIC 22



Incorporates the Acos "Filtercel" insert giving extreme sensitivity and high fidelity. Response substantially flat from 40-6,000 cps. Vibration and shock-proof. Not affected by low-frequency wind noises. Two alternative mountings available as illustrated (MIC 22-2 and MIC 22-1).

Price £6 6s. 0d. (either model).

TYPE MIC 16



Incorporates the Acos Floating Crystal Sound Cell giving a response substantially flat from 30-10,000 cps. Unaffected by vibration, shock and low-frequency wind noise. Alternative mountings as shown (MIC 16-2 and MIC 16-1).

Price £12 12s. 0d. (either model).

COSMOCORD LTD., ENFIELD, MIDDLESEX.

SUCCESS?

Never before has such a vast field of opportunity been open to the technically minded. Because we can call on the unique experience of the great E.M.I. Group ("H.M.V.", Marconiphone, etc.), our courses are based on the needs of modern industry. Let us help you to take advantage of the great demand for technicians in Radio, Television and all branches of Engineering. Take the first step NOW!

FILL IN FOR FREE BROCHURE

Mark the subject(s) which interest you, and post (without obligation) :-

E.M.I. INSTITUTES, Dept. 155, 10, Pembroke Sq., London, W.2

- Radio
- Aeronautical Eng.
- Production Eng.
- Television
- Draughtsmanship
- Matric
- Electrical Eng.
- Mechanical Eng.
- Civil Service
- Other Subjects.....

NAME

ADDRESS.....

.....

..... (BLOCK CAPITALS)

E.M.I. INSTITUTES—The only Postal College which is part of a great Industry.

Simple Resistance Meter

A New Idea for the Experimenter

By J. S. KENDALL

THIS unit, which is the very essence of simplicity and can be made for a matter of coppers, presents a means of measuring resistance which is very efficient for a range of a few hundred ohms down to about 1/10. The parts in the main can be found in the junk box.

The parts required are:

- One rotary switch with up to five positions.
- One double-pole double-throw toggle switch.
- A selection of close tolerance resistors of suitable rating.
- One suitable dry battery (a three-cell torch battery is quite good).

The principle of the instrument is that with a constant current the voltage drop along a resistor is directly proportional to the value of the resistor.

The circuit is shown on the right. The object of the 5-ohm resistor is to limit the current flow to a safe value when checking very low resistances. The meter used with the unit can be almost any radio meter that has a resistance of at least ten times the value of the standard or the resistance being measured whichever is the greater. If the meter resistance is too low the current drain gives inaccurate measurement. Suitable values for the resistances are 1 ohm, 3 ohms, 10 ohms, 30 ohms and 100 ohms. Quite a number of ex-W.D. units have 10-ohm resistors in the form of anode stoppers. If possible gold-tipped resistors should be used.

The 1- and 3-ohm resistors are not readily obtainable but can be made to a fair degree of accuracy by comparing with the 10-ohm standard.

Using the Meter

The method of use is simple. First switch the voltmeter across the unknown resistor and adjust the range switch so that the voltage reading is as near as possible to half the battery voltage, then throw the toggle switch so that the voltmeter is across the standard resistance. The actual resistance of the unknown is expressed in the formula $R? = \frac{Rs (V1)}{V2}$ where $R?$ is the unknown, $V1$ the voltage across the unknown, $V2$ the voltage across the standard resistance and Rs the standard resistance. It will be seen that as long as the meter scale is linear the actual voltage need not be expressed as such and can be expressed in "degrees." This allows the use of a cheap moving-coil meter of low current drain if the user prefers a built-in meter.

An example of the calculation with the unit would then be:

$V1$ equals 4.72.
 $V2$ " 2.82.
 Rs " 32.


Then applying the formula $R? = \frac{Rs (V1)}{V2}$

$R? = \frac{3 \times 4.7}{2.8} = 5$. Remember it is not possible to

make measurements to a greater accuracy than the standards being used. If, then, ordinary untipped resistors are used the accuracy cannot be better than one part in five, but if gold-tipped resistors are used the accuracy will be about one part in twenty. The inaccuracies also grow as the readings increase in difference, i.e., at the top and bottom of the range.

A few of the uses of the instrument are:

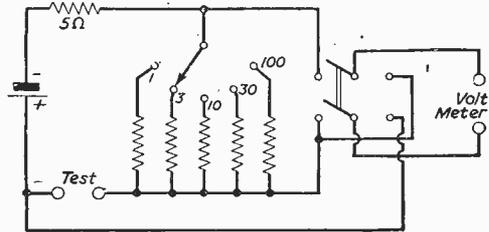To measure contact resistance of a wave-change switch. For this measurement the battery voltage should not be more than 1.5 or the voltage will overcome the barrier layer effect of the dirt and oxide on the switch. Shunt resistors for meters can



Circuit of the arrangement described here.

be measured with it and the resistance of earth connections on chassis. The latter gives some surprising readings and as high-resistance earths are one of the greatest causes of instability it is worth the trouble in making the meter if only to check these.

2-metre P.A. Efficiency

(Continued from page 222.)

is that of the aerial coupling, which is why a swinging link coil is specified. The coupling should not be increased any more than that required for good upward modulation, as this will result in lower R.F. output and increased anode dissipation.

It can be seen that, using the circuits described, the 832 will work at 40 watts input, 100 per cent. modulated. No overheating has been observed and the circuit has been successfully in use for some time. Reports show that the upward surge of the P.A. current and R.F. currents do not indicate over-modulation with this circuit. The carrier does not become broken, but the signal appears to have increased punch and penetration over a plate-modulated transmitter. It is not certain exactly how the circuit works, but the effects described could be explained by an increase in average carrier level during modulation, with an accompanying increase in power radiated in the sidebands. The results would thus have some resemblance to those produced by the "super-modulation" systems recently described. These systems also make use of grid modulation, but employ a separate valve to generate the increased carrier level on modulation.

Designing Your Own Receiver—7

Advice and Guidance for the Beginner

By STANLEY BRASIER

Ohm-meter

THE remaining essential instrument which the amateur should possess is the ohm-meter, and here again our old friend the 0-1 milliammeter forms the basis of the instrument.

The principle on which the ohm-meter functions was shown in Fig. 8. The values of voltage and resistance are arranged so that when the X terminals are short-circuited, the variable resistor can be adjusted so that the full scale current of 1 mA is registered. Thereafter, if the short-circuit is removed and replaced by a resistor having a value between certain limits, a current dependent upon this value will be registered. From Ohm's Law it is then possible to calculate the value of the resistor. In general, the range of values which can be determined is dependent upon the basic current range of the meter, but for general work the 0-1 mA type enables resistors from approximately 200 to 200,000Ω to be measured, especially if a long scale is available. In order to obviate the necessity of calculation every time an unknown resistor is measured it is usual to calibrate the scale, and perhaps the easiest and less tedious of all methods is by the application of known values. For this type of ohm-meter is not usually so accurate that it can discriminate between percentage tolerances of resistors normally used in receiver work, and since these are the type of resistors checked, there is no point in aiming at an accuracy which is any higher. But here again, if another ohm-meter can be borrowed for checking purposes, so much the better, and it is only necessary to connect in turn as many different values as are required to the X terminals and mark the points on the scale. This subject, however, will also be dealt with later.

Other Instruments

During all our checks on receiver performance we relied on the fluctuating programme signal for the input, and upon our aural interpretation of the output from the loudspeaker. Although, as we have seen, this system is fairly satisfactory it is usual to use instruments which will give an indication of improvement, or otherwise, to a finer degree. These consist of what is known as an oscillator, to feed a signal into the receiver, and an output meter, which gives visual indication of the final results obtained.

The Oscillator

A test oscillator may consist of an extremely complicated piece of apparatus where specific H.F. measurements are required, but in the case of the amateur—and especially the beginner—all that is needed is a small signal of constant intensity which can be fed into a receiver under test. This may consist of a simple single valve circuit which is so adjusted that the valve is in a state of continuous oscillation (similar to an oscillating one-valve receiver) and this signal, which will be at high frequency, is applied to the receiver. Even this, however, will not be strictly audible at the output of the receiver, but the sound will be similar to that which is heard when a local station is radiating without a programme. The "programme" in the oscillator consists of a signal from another valve which, oscillating at low frequency, is superimposed on the H.F. signal, and produces an audible note which is heard in the loudspeaker of the receiver. The wavelength of the oscillator signal must, of course, be identical with that of the receiver and under these conditions will provide a steady unfluctuating signal, the advantage of which will be appreciated when testing.

As a guide towards the construction of a simple oscillator for testing and trimming purposes, Fig. 9 shows a suggested circuit. It should be made up in a metal box and if miniature low-consumption triodes are used the whole instrument could be very compact. If only the medium and long waveband

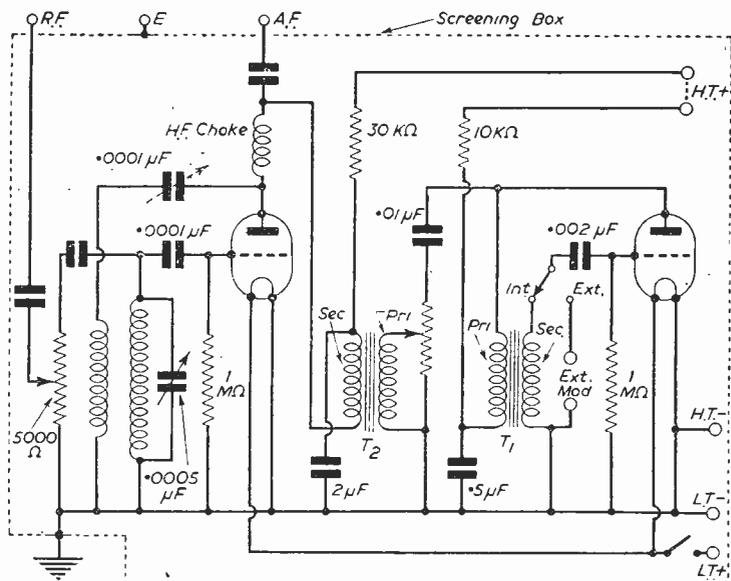


Fig. 9.—Suggested circuit for a modulated oscillator. T₁ and T₂ are midget L.F. transformers. H.T. may consist of a few grid-bias batteries.

are required the coil may consist of any good quality dual-range type. The tuning condenser should have a value of $.0005 \mu\text{F}$ approximately and the "reaction" condenser should be of a value that just permits of continuous oscillation. The pitch of the modulation note will be dependent upon the type of transformers used but may, to some extent, be varied by a small condenser connected across T1. Output is controlled by the potentiometer and should feed into a screened lead via an artificial aerial. This can conveniently be made up in a small tin box.

Output Meter

Coming now to the output end of the receiver it is usual to record the amplified signal from the oscillator by means of an output meter. Such an instrument gives visual indication and is connected in place of the loudspeaker. The eye is more sensitive to perception of movement than is the ear to differences of sound and thus finer adjustments to the receiver are usually made possible.

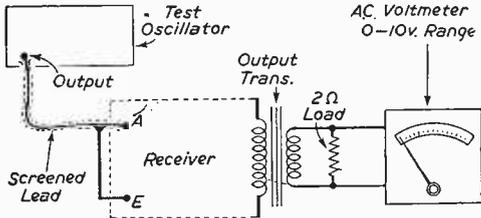


Fig. 10.—Showing how the A.C. voltmeter may be connected for use as an output meter.

To record the output signals from a receiver it is necessary to use an instrument that will respond to an alternating current, therefore the A.C. voltmeter previously referred to will be entirely suited to the purpose. The meter is connected to the secondary of the output transformer but the resistance (or rather, impedance) of the loudspeaker must be represented by an artificial load in the form of a resistor, which is also connected across the output meter. The lowest range of the meter is used and it should be noted that the instrument in no way gives any specific quantitative indication—it merely records differences in output—and for this purpose it is most convenient. For connection see Fig. 10.

Thermo-ammeter

Another instrument which is available at low cost in the form of Government surplus is the thermo-ammeter, and because it is responsive to alternating current, such meters are extremely useful. The type reading 0-350 milliamps is applicable to checking the current of 0.2 Amps. and 0.3 A.C./D.C. valve heaters and many other A.C. measurements. It can also be used in place of the A.C. voltmeter as an output meter. In this case the resistor should be joined in series with the thermo-ammeter. It is necessary to warn the amateur that this type of instrument is very susceptible to breakdown if the full-scale current is exceeded or if there is an initial "surge" at the moment of switching on. For this reason it is sound practice to fit the meter with a shorting switch which may

be "opened" when circuit conditions have assumed normal proportions.

There are many more instruments useful to experimenters such as the valve voltmeter, beat-frequency oscillator, oscilloscope, etc., but these may be acquired if, or when, such interests develop. The instruments described, however, if used intelligently, will provide the amateur with much knowledge with regard to the development and testing of receivers.

The Final Effect

Although the appearance of a completed receiver or test instrument makes not the slightest difference to the performance it is well to cultivate an artistic sense towards construction. For surely it is better to have apparatus that looks well in addition to working efficiently. This attitude also reflects to the unseen parts of the chassis work, as it should, and one soon finds that attention is paid to every single detail in connections, wiring, etc., and altogether a great pride can be taken in one's mechanical work.

The object of this last section in the series is to show how the appearance of instruments made at home can be constructed to almost professional standards, by the use of certain materials and methods.

These are mostly concerned with the panel arrangements but, first let us consider for a moment the question of suitable cases to house the instruments. The easiest way, of course, is to use an ex-Government case if such is available in convenient size. Very often only a "finish" is required to make them look like new. For home construction 16 gauge aluminium is very suitable and the main body of the case may be made up by bending to size. But a better method, and one which enables nice sharp corners to be obtained, is to use L-section angle strip, also of aluminium. This is available from advertisers and may be cut to form the foundation supports. For, in addition to providing the case with much greater strength, the method obviates the necessity of making short angle bends along a length of metal—a procedure which is not easy, without special presses, if a good symmetrical appearance is to be presented.

Finishing

For finishing there are now quite a variety of brushing cellulose materials on the market which, when applied, are indistinguishable from the sprayed method and have sufficient "body" for one coat to suffice. This type of cellulose is likely to "run," however, and for this reason it is advisable to work on one horizontal surface at a time. If the case is made up in sections as above, it may easily be dissembled for finishing.

(To be continued)

NEWNES' RADIO ENGINEER'S POCKET BOOK

By F. J. CAMM

5/-, or by post 5/6

Obtainable from booksellers, or by post from
George Newnes, Ltd. (Book Dept.), Tower House,
Southampton Street, Strand, W.C.2.



MAINS TRANSFORMERS & CHOKES



All "Varley" products are manufactured from the highest quality materials.

Transformers, etc., are individually wound and have interleaved windings with ample insulation, ensuring freedom from breakdown.

The comprehensive range of Shielded and Open Type Transformers available meets the requirements of every circuit.

Write for list, etc.

Made by

OLIVER PELL CONTROL LTD
CAMBRIDGE ROW · WOOLWICH · S.E.18
Telephone: WOOLWICH 1422

G2AK This Month's Bargains G2AK

RECEIVERS TYPE 18.—Cover 6-9mc/s and are for battery operation. Good condition, 17/6. Packing and postage 1/-.

OSMOR Coil Packs for conversion of above complete with frame aerial, 45/10. All types of OSMOR packs available Ex stock.

MIDGET SPEAKERS.—Philips 2½ in., 12/11. Goodman and W.B. 2½ in., 16/6. J. and P. 3½ in., 13/11. Elac 6 in., 17/6.

WEYMOUTH MIDGET I.F.'s 465 kc/s. Type P4J and P4K, 15/- pair. Kit of 4 Midget 1.4 v. valves 1R5, 1T4, 1S5 and 1S4, 25/-.. New and Boxed.

MIDGET OUTPUT TRANS. for Personal Portables, 5/3 each. Balanced armature L.R., 'Phones, 6/6 pair.

XTAL DIODES, 3/9 each, or 4 for 14/-. Germanium diodes, 5/6 each.

AEROVOX 2 mfd., 1,000 v. oil filled Conds., 2/6 each, or 10 for £1.

POTENTIOMETERS.—5 watt wire-wound .20 k., 25 k., 2l-. 500 ohm and 2,000 ohm 50 watt wire-wound, 3/6 each. Carbon Type Potentiometers, .50 k., 100 k., 1 meg., 2 meg., 1/6.

TEST METER.—7 ranges as follows: 1.5 v., 3 v., 150 v., 6 mA., 60 mA., 5,000 ohms, 25,000 ohms, 2½ in. dia. scale M.C. meter. Rotary selector switch. Black bakelite case, 6 in. x 4½ in. x 4½ in., fitted with removable lid, also provision for internal batteries. Ranges can be extended very easily. Bargain price, 25/-, plus 1/6 post.

Please print your name and address.

CHAS. H. YOUNG, G2AK

All Callers to 110 Dale End, Birmingham
CENTRAL 1635

Mail Orders to 102 Holloway Head, Birmingham
MIDLAND 3254

HR TELEVISION

TELEVISION RECEIVERS
SCANNING AND FOCUS COILS
P.M. FOCUS UNITS
5/10 kv. R.F., E.H.T. UNITS
E.H.T. and OUTPUT TRANSFORMERS

Technical Publications post free.

"TELEVISION CIRCUITS"
Second Edition, post free 1/6

HAYNES RADIO Ltd., Queensway, Enfield, Middlesex.

Hitch your AERIAL to a STAR.

Skyway "Seven" RADIOGRAM CHASSIS

3-wave S'het 16-2000m. Push-pull 6V6s. Separate POWER PACK for easy fitting.

Basic Parts cost less than (including valves) **£5**

Full home constructor design in **FOUR EASY STAGES** 1/- post free

3rd RADIOCRAFT Ltd. PHONE 58927
60-71 CHURCH GATE-LEICESTER

FREE TO AMBITIOUS ENGINEERS!

This 176-page Book

Have you sent for your copy ?



'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £12 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

*** FREE COUPON ***
Please send me your FREE 176-page "ENGINEERING OPPORTUNITIES"

WHICH IS YOUR PET SUBJECT?

Mechanical Eng.
Electrical Eng.
Civil Engineering
Radio Engineering
Automobile Eng.
Aeronautical Eng.
Production Eng.
Building, Plastics,
Draughtsmanship
Television, etc.

GET SOME LETTERS AFTER YOUR

NAME!
A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.P.E.
A.M.I.M.I.
L.I.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
CITY & GUILDS
MATRICULATION, etc.

NAME

ADDRESS

Subject or Exam.

What interests me

British Institute of Engineering Technology
409B, Shakespeare House,
17/19, Stratford Place, London, W.1

BIET

THE NEW BRADMASTER MODEL 5 TAPE DESK for 1951

- Built to professional standards ● Two speeds—3½ and 7½ inches per second ● Fast wind and rewind—full reel rewound in 1½ minutes ● Heavy alloy flywheel. Freedom from "wow" and "flutter" ● Double servo brakes on each hub ● Push Button control ● Three heavy duty motors ● Three shielded Bradmatic heads
- Size: 13½ in. x 15½ in. x 6½ in. deep.

PRICE: £37.10.0

A **PLUG BOX** can also be fitted to the above equipment containing three compartments which provide shielding for the head leads and eliminating hum and cross talk. Also fitted with three coaxial plugs and sockets, facilitating connection of the desk to amplifiers, etc. **PRICE** (fitted underneath desk) £1.5.0

| | | | |
|---|---------|------|--|
| Hi-fidelity magnetic sound heads: | | | |
| Type 5 R.P. (record/play head) | £3. 5.0 | each | |
| Type 5 E (erase head) | £3. 5.0 | " | |
| Super fidelity magnetic sound head, type 6 R.P. (record/play head) | £3.15.0 | " | |
| Screening Cans, best quality (all mumetal) composite | 8.0 | " | |
| (constructed of steel and mumetal) | 4.6 | " | |
| Oscillator coils | 8.0 | " | |
| Tape on 7 in. reels, 1,200 ft. | | | |
| Emitate, type 65 | £1. 5.0 | | |
| G.E.C. Grade "A" | £1.10.0 | | |
| Durex type, MC I—III | £1.15.0 | | |

Trade supplied. Send for lists to Sole Manufacturers —

BRADMATIC LIMITED

STATION ROAD, ASTON, BIRMINGHAM, 6

Telephone: East 0574 Telegrams: Bradmatic, Birmingham

HENRY'S

3547 RECEIVERS. Absolutely brand new, in sealed manufacturers' packing cases. Incorporating 15 valves type EF50, 2 of SP61, EF36, EBC33, 3 of EB34. Complete 45 Mcls. I.F. Strip, motor dial and drive, pots, etc. £6 only, plus 10/- packing and carriage. Whilst they last!

EX-R.A.F. INDICATOR UNIT TYPE 62. Containing VCR97 CRT with mu-metal screen; Crystal Unit and valves 16VR65 (SP61), 2IVR54 (EB34), 2IVR92 (EA50), etc., etc., two deck chassis in metal case, 18 x 18½ x 11½ in. New condition. 67/6 each. Plus 7/6 packing and carriage.

No. 39 "WALKIE TALKIE" TRANS-RECEIVERS. Complete with Throat Mike, Phones, Aerial Rods and Junc. Box. Freq. Range: 7.4 to 9 Mcls. Brand new and guaranteed, £4/19/6. Carr. 2/6.

RECEIVER TYPE 21. The receiver portion of the WIS 21 operating from 4.2-7.5 Mcls. Double superhet from 18-30 Mcls. Incorporating B.F.O. and crash limiter. Valve line-up 7-AR12 (VP23) and 2-AR8 (HL23DD). Absolutely brand new, complete with circuit. Only 45/- complete. Vibrator power unit for above, brand new, 17/6 only.

R.3084 RECEIVER. Incorporating 7 EF50, 2 EF54, 1 EC52, 1 VU39A, 1 HVR2, 1 EA50, plus 30 Mcls. I.F. Strip. Guaranteed absolutely brand new in maker's original packing case. 75/-. (Plus 10/- carriage and packing.) This receiver is ideal for conversion to vision receiver.

METAL RECTIFIERS. S.T.C., 300 volts 75 ma., 5/-; S.T.C., 24 volts 2½ amps., 17/6. G.E.C., 6 volts 1 amp., 4/-. Westinghouse, 12 volts 2 amp., 12/6. Pencil Type E.H.T., 600v. 1 ma., 4/7; 1,000v. 1 ma., 6/-; 2,400v. 3 ma., 15/-; 150, 500v. 2 ma., 7/6.


5MIA METER RECT. 5/-; W.6 and WX6, 11/6.

FILAMENT TRANSFORMERS. All Inputs 200/50 A.C. 6.3v. 1.5 amp., 7/6; Igranic, 6.3v. 2½ amp., 10/-; 6v. or 12v. 3 amp., 15/-; 6.3v. 12 amp., 37/6.

MAINS TRANS. (PARMEKO). 250-0-250, 90 ma. 6.3v. 3 amp., 5v. 2 amp. Input, 110/250, 15/-. Min. Mains Trans., 3½ high by 3 x 2½, fully shrouded, 250-0-250, 60 ma., 6.3v. 3 amp., 5v. 2 amp., 21/-.
Send stamp for current Component List—Probably the most Comprehensive in the trade.

5, HARROW ROAD, LONDON, W.2
PADDington 1008/9 and 0401.

4 VALVE MAINS RADIO

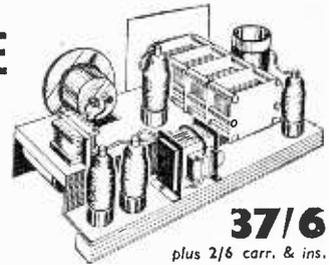

with

Miniature Loudspeaker

200-250 volt A.C.—D.C. mains. Size approximately 10½ in. x 7 in. x 6 in. Low running costs, completely self contained. Receives medium waves, Home and Light, etc. Moving coil 1½ in. speaker. **ALL COMPONENTS, INCLUDING VALVES, CHASSIS, etc., INCLUDED.** Build this fine set yourself—*from easy Plans!*

37/6

plus 2/6 carr. & ins.

ELECTRICAL SETS

The Electrical Experimenters' Kit! **19/6**
Stout compartment box contains 84 parts. This kit contains Coils, Magnets, terminals, wire, etc., and completely comprehensive Instruction Book, with instructions for making Voltmeters, Ammeters, Electric Motors, Bells, Dynamos, Buzzers, Telephones, etc.

INSTRUMENT CO. (Dept. P.W.), 6, HIGH STREET, THAME, OXON

C. & W. ELECTRONICS TEST INSTRUMENTS

18 Range Multimeter M.M.2.
A C.D.C. Volts from .25v. to 2,500v. at 4,500Ω r.
Basic Movement 200 μA.
Scale Length, 3½ in.
D.C. current from 10 μA. to 1 amp.
Resistance from 1 ohm to 5 megohms.
Power and D.B.s.
1st Grade Accuracy on all ranges.
Complete with Test-prods and instructions. £7.2.6.

Signal Generator S.2.
Range 109 kc/s. to 70 mc/s.
400 c.p.s. Audio. Int. & Ext. Mod.
Ladder and fine Attenuator.
Direct Reading Frequency Dial.
Grey Crackle finish.
Complete with R.F. & A.F. leads. £7.10.0.

12 months' guarantee on all instruments.
Send S.A.B. for leaflets.

C. & W. ELECTRONICS, 17 CROSS STREET, OSWESTRY, SALOP

"ADCOLA" SOLDERING INSTRUMENTS

Reg. Trade Mark



Read Design No. 800302
(British, U.S. and Foreign Patents.)

For Wireless and Television Assembly
The advanced design of the Adcola Instruments meets the modern requirements of Television, Telecommunication and Radar Engineers.

SUPPLIED FOR ALL VOLT RANGES FROM 617v. to 230/250v.
3/16 in. dia. Bit. Standard Model 22/6.
3/16 in. dia. Bit. Standard Model 25/-
3/16 in. dia. Detachable Bit. Model 30/-

Sole Manufacturers:

ADCOLA PRODUCTS LIMITED

SALES & SERVICE: 50, CLAPHAM HIGH STREET, S.W.4.
Telephone: MACaulay 4272

Programme Pointers

This Month MAURICE REEVE Deals with Some More Recent Programmes

THE relief and thankfulness with which I learned that "Music Hall" and "Variety Handbox" were no longer going to inflict upon us their witless wit and their horrible noises alias music, were slightly tempered by the subsequent news that the former programme's title was going to be bequeathed to an "entirely new type of show," whilst the latter, title, show and all, was to be restored in the summer.

When we see "Music Hall" in our future programmes it will be difficult to remember—at first, at any rate—that it is not the same collection of nitwitty, half-baked oafery and cacophonous jargonry which has inflicted itself upon us for countless Saturday evenings in the past. I cannot think why the whole works, title and all, are not cast as far away as it is possible to cast anything. For years now the radio critics, almost with one voice, have written of B.B.C. variety, including some of the regular weekly shows of the "Keep Smiling" type, in such terms of sweeping condemnation that something ought to have been done about it a very long time ago. There simply are not enough Music Hall variety turns of sufficiently high quality to fill a quarter of the many hours which are allotted to variety on the air. Further, there is no liaison between programmes to avoid the sickening repetition of topical jokes such as we had about groundnuts and Sir Stafford Cripps, and as we are now getting about the coal shortage. The best of them are not frightfully funny, but their plugging is inexcusable. And last, but by no means least, is the "dead head" studio audience, for which no defence can be found in any quarter.

No : critics must just keep pegging away at these points, knowing they are right and hoping that some day something will be done about them.

Saturday Night Theatre

"Dear Octopus," Dodie Smith's colourful comedy of family life, was notable for being "Saturday Night Theatre's" four hundredth production. Although this large total includes some repetitions, it is a fine achievement by all concerned. We should all be grateful. Gladys Young's appearance in the New Year's Honours was not only thoroughly merited but was, I presume, proof that we do all appreciate hers and the others efforts.

"Travellers' Joy," that enormously successful skit on the topical problem of our currency troubles when travelling abroad—considerably eased since the play was written—came over well, with the ever charming Yvonne Arnaud in her most attractively loquacious mood. The other characters, and

the play generally, lost a little of the sparkle and gaiety it had at the Criterion through not being visual.


The two plays I liked most during the past few weeks were "Monsieur Lamberthier," by Louis Verneuil, with Marius Goring, Lucie Mannheim and John Buchelle; and "Such Men Are Dangerous," adapted by Ashley Dukes from "The Patriot" of Alfred Neumann, with, amongst others, Henry Oscar, Phyllis Neilson-Terry, Brian Powley, Kenneth Kent and Lewis Stringer.

"Monsieur Lamberthier" is a typical French plot of love, jealousy and intrigue, such as only our Gallic friends seem able to convincingly contrive. Miss Mannheim seemed quite terrific as the wife with a secret, and her succession of cajoleries and swindles of her poor wretched husband left us almost as bewildered and exhausted as the poor man himself.

"Such Men Are Dangerous" is a powerful presentation of the plot of the Chancellor and others to murder the infamous and lunatic Czar Paul of Russia, and to place his son Alexander—the Alexander of Tilsit fame and to whom Napoleon showed his heels when retreating from Moscow—on the throne in his stead. I well remember the magnificent silent film, "The Patriot," with the late Emil Jannings, Adolphe Menjou and Pola Negri.

Ibsen's masterpiece, "The Doll's House," came to us on the "Third." I only have room to say that Marjorie Westbury was very effective as Nora Helmer, the "little song-bird" of Torvald Helmer, who, after enduring a particularly cruel piece of tyranny, not only leaves her gilded cage—her "doll's house"—to fight her own way in the world, but who thereby set the whole feminine

PROFESSOR BOFFIN

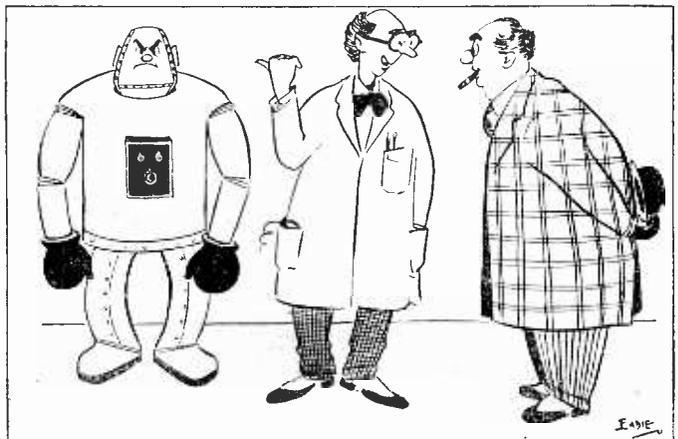

"And here, Mr. Solomons, is the answer to the American heavy-weight problem."

world afire to do the same. One of the great women's dramatic rôles.

Verdi

The Verdi half-centenary celebrations received due recognition, and, for the most part, there were good performances. Verdi was one of the great masters of music, and in the course of his artistic development, covering an exceptionally long life, he must have passed through more phases than even Wagner. "Falstaff" differs from "Traviata" even more than "Parsifal" does from "Rienzi."

"Afghan Adventure," the record of a year spent at the British Legation in Kabul, in 1924, by Muriel Miller, wife of a member of the Legation staff of that time, was a pleasant enough narrative, but far too long. There was neither material nor excitement sufficient to occupy a whole hour on a Sunday evening.

Quiz

Quiz programmes continue to hold their popularity, though some of the more juvenile ones seem

a little redundant outside of Children's Hour. It is fascinating to follow the adult mind searching for a piece of information by often devious and tortuous ways, more especially when the listener thinks he has come across it down a more direct path.

"The Wonderful Year" sickened me. Is it remotely possible that 2051 will be describing 1951 in similar terms? I doubt very much whether there was anything at all special about 1851 other than the exhibition. And does an exhibition, by and of itself, make a year "wonderful"? I'm afraid the opening sentences about the blue sky, the sunshine and—above all—God's blessing, rather prejudiced me against the whole thing. Is God blessing our present efforts at assembling specimens of our genius and handiwork on the south bank? Perhaps it is a little too early to tell; perhaps we shan't know till 2051.

The current Sunday evening serial, "The Mayor of Casterbridge," seems as good as any that have gone before. A great story is doubtless the chief contributory factor.

News from the Clubs

THE GRAFTON RADIO SOCIETY (G3AFT)

Hon. Sec.: W. H. C. Jennings (G2AIB), Grafton School, Eburne Road, Holloway, London, N.7 (one minute from the Nag's Head).

MEETINGS continue every Monday, Wednesday and Friday at 8 p.m., and the Morse classes (beginners to advanced) continue to progress excellently. A. Appleby and F. L. Rogers both successfully passed the G.P.E. examination and are now G3HMS and G3HGX respectively. A lecture and demonstration entitled "Radio Control of Model Aircraft," by courtesy of Messrs. Iford Electrical Company, will be held on Friday, April 13th, at 8 p.m., by F. C. Judd, Esq. (G2BCX), and W. Taylor, Esq. Refreshments will be provided free of charge and visitors are cordially invited to this special show. In order to facilitate entering arrangements, visitors are requested to send the hon. secretary a postcard advising their attendance.

CRAV VALLEY RADIO TRANSMITTING CLUB

General Secretary: A. Swindon (G3ANK), 135, Station Road, Sidecup, Kent.

MEETINGS of the C.V.R.T.C. are held on the fourth Tuesday of each month at the Station Hotel, Sidecup, at 7.30 p.m.

CLIFTON AMATEUR RADIO SOCIETY (G3GHN)

Hon. Sec.: W. A. Martin (G3FVG), 21, Brixton Hill, Brixton, S.W.2.

THIS society meets every Friday evening at 8 at 225, New Cross Road, New Cross.

The club station is now licensed for 'phone and is active on 50 and 160 metres.

Club membership stands at 50, with 19 licences.

TORBAY AMATEUR RADIO SOCIETY

Hon. Sec.: K. J. Grimes (G3AVF), 3, Clarendon Park, Tor Vale, Torquay.

THE Field Day Rules and other F.D. matters were discussed at the February meeting.

At the March meeting (the 17th) judging took place of the entries for the club's contests. Trophies will be awarded at the A.G.M. in April.

Technical films and demonstrations are on the programme of future events.

Visitors to Torquay interested in radio are invited to attend. The meetings of the society are held on the third Saturday of each month at the Y.M.C.A., Castle Road, commencing at 7.30 p.m.

NEWARK AND DISTRICT AMATEUR RADIO SOCIETY

Secretary: John R. Clayton, 160, Wolset Road, Newark, Notts. **T**HIS club has been invited to take part in the Newark "Festival of Britain Exhibition" to be held for one week during July next.

GILLINGHAM TELECOMMUNICATIONS SOCIETY

Secretary: C. E. Pellatt (G2FAQ), 101, Boundary Road, Clatham, Kent.

AT the society's second A.G.M. on March 6th, the following officers were elected: Chairman, Mr. A. Walker; Treasurer, Mr. C. W. Booth, M.B.E. (G3GSP); Secretary, Mr. C. E. Pellatt (G2FAQ). Meetings are held at the Medway Technical College, Gardner Street, Gillingham, on alternate Tuesdays at 7.30 p.m. Newcomers will be very welcome. The society's transmitter, G3RTE, is licensed for 'phone and the full 150 watts. Members will be operating the Medway Area "A" station during N.F.D. on June 2-3. All R3GB members will be welcome at the site. The call sign will be G2CMF.

BRIGHTON AND DISTRICT RADIO CLUB

Hon. Sec.: R. T. Parsons, 14, Carlyle Avenue, Brighton, 7.

AVERY full programme of instructive lectures and demonstrations has been arranged; in fact, time for informal "ratchew" evenings seems very limited at present!

Several new members have come along, and those intending are asked to contact the Hon. Sec. Meetings are held every Tuesday evening at the "Eagle Inn," Gloucester Road, Brighton. Programme includes further Mullard film strip lectures and a promise of a repeat and more advanced demonstration on tape recording by G5ZQ.

COVENTRY AMATEUR RADIO SOCIETY

ON February 12th a colour and sound film show upon plastics was put on by G2BET and proved an absorbing subject. The manufacture of laminated plastics for radio and electrical use was covered, and G2BET answered his many questioners with the authority his many years in the industry have given him.

A most interesting event took place on February 26th, when the lecture on super modulation by G3RF took the form of a two-way contact between G3RF using his super-mod. rig at home and the society members with the club transmitter G2ANF. The conclusions reached by G3RF as the result of many weeks' experimenting provided members with a clear exposition of this much-argued system of modulation.

Members of other local clubs joined a large gathering on March 12th to see a demonstration of radio-controlled models given by members of the International Amateur Model Constructors Society. The ingenuity shown in the adaptation of single-tube QRP transmitters and receivers and the degree of control obtained over the moving models impressed the audience greatly.

NEW CLUB FOR MANCHESTER

IT has been decided to form a radio club in the Cheetham Hill district of Manchester, and any reader interested in becoming a member should write as soon as possible to either Mr. H. B. Knowles, 36, Oak Road, Crumpsall, Manchester, 8, or J. C. Henderson, 47, Maple Street, Cheetham, Manchester, 8.

"MUST HAVE" BARGAINS

COMMUNICATIONS RECEIVER

R.1155. Another purchase from the Ministry of Supply enables us to once again offer this superlative communications receiver at "give away" prices. A World Station Getter, this 10-valve set covers 5 wave ranges; 18.5-7.5 mcs., 7.5-3.0 mcs., 1,500-600 kcs., 500-200 kcs., 200-75 kcs., and is easily adapted for normal mains use. Full details being supplied. Prices to suit every pocket, as follows:

- Used, good condition, and aerial tested ... £7-19-6
- Used, good condition, untested ... £6-19-6
- New in Makers' Cases and aerial tested ... £9-15-0
- Carriage in all cases 10/- extra.

MAKING AN OSCILLOSCOPE ?

Then you want the INDICATOR UNIT TY1E 6. As recommended for the "Wireless World General Purpose Oscilloscope" Fitted with 6in. C.R. Tube type VCR 97, 4 valves, EF 50 and 3 of EB 34. Another purchase from the Ministry of Supply enables us to offer these units which are BRAND NEW IN MAKERS' CRATES at ONLY 79 6 (carriage 7/6). Constitutional data as above supplied free with each unit or available 9d.

The following component parts are in stock: EHT Transformer for VCR 97 tube, ONLY 30/- (Postage 1/6). 4v. EHT Rectifier with ceramic base, ONLY 8 6 (Post 9d.). CHOKES, 20h. 30 ma. ONLY 6 6 (Post 9d.).

INDICATOR UNIT TYPE 62. Contains VCR 97 Tube, 16 valves VR 55, 2 VR 54, 2 VR 92, and shoals of condensers, resistors, potentiometers, etc., etc. The last few to clear at ONLY 59/6 (Carriage, etc., 12/6).

AMERICAN COMMAND SET BC454. Contains 6 valves: 3 of 12SK7 and 1 each 12K6, 12A6, 12SR7. Covers Travler Band 100-300 metres, 59/6.

BATTERY SUPERSOLDER. With restrictions on the use of zinc those H.T. Batteries are likely to be scarcer. Fit a supersolder and forget. Operates on a 2v. accumulator and delivers 67 volts at 4.7 ma., 120 volts at 12-25 ma., also 14v. L.T. Originally designed for use with Canadian Walkie Talkie equipment, this American made unit can be easily adapted for use on any set, and full illustrated details are supplied, ONLY 60/- (Postage 1/6), or with Two 2 volt accumulators in metal case 90/- (Carriage, etc., 5/-).

TELESCOPIC AERIALS extending from 15in. to 102in. Just pulls out of steel tube. Very strong, BRAND NEW, ONLY 12/6 (Postage 10/-).

HEADPHONE & MICROPHONE SET. A pair of 4,000 ohms phones fitted with rubber noise excluders, and a high grade carbon microphone. BRAND NEW, ONLY 12/6 (Postage 10d.).

AMERICAN LORAN RECEIVER APN4. Contains 16 valves: 3 6B1, 2 2X2, 4 6SK7 and 1 each 5U4G, 6H6, 6SU7, 6SL7, 6SN7, VR. 135. Covers approx. 550-650 metres in 4 switched bands. ONLY 69/6 (Carriage, etc., 5/-).

RECEIVER 3547. Contains the "Pye" 45 mcs. I.F. Strip, which is easily removable, and 15 valves EF50, 3 FB34, 2 SP61 and 1 each EA50, EBC33, EF30. BRAND NEW IN MAKERS' CASES, ONLY 120/-.

MINIATURE DYNAMOTOR UNIT, D.C. Input 23 volts at 1.1 amps. D.C. Output 50 volts at .06 amps. BRAND NEW, ONLY 12/6 (Postage 1/-).

MODULATOR & MIXER, W6391.

A very fine ex-Admiralty unit containing 8 valves: 1 each 5U4G, SP61, EB34, 2 of 6J5G and 3 of 1P61. ONLY 22 6 (Carriage, etc., 7/6).

Cash with order please, and print name and address clearly.


U.E.I. CORPORATION

The Radio Corner

138 Grays Inn Rd., LONDON, W.C.1 (Phone: TERMINUS 7537.)

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Stn.) and 3 mins. by bus from Kings Cross.)

CHASSIS

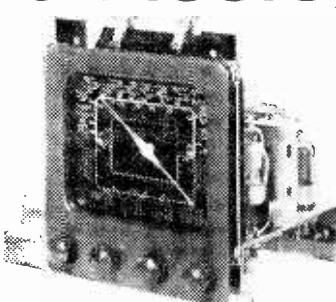

HAYES RG/120 RADIOGRAM CHASSIS. The demand for this attractive and popular chassis increases month by month. The total price of £1317/6 includes an 8in. loudspeaker, and all packing and carriage charges, representing real value-for-money in these days of rising prices. A 10in. L.S. can be supplied at a slight extra cost. Fully guaranteed for one year. Full details will gladly be sent you by return of post.

ARMSTRONG CHASSIS. We hold the largest stocks of Armstrong chassis in the Midlands, and are the sole Birmingham agents. The full range can be seen and heard in our showroom. Open all day Saturdays.

THE HAYES COMPANY

1 ALCESTER RD., MOSELEY, BIRMINGHAM, 13.

'Phone: SOUTH 0202.

If you care to call at

MODERN ELECTRICS LTD.

164, Charing Cross Rd., W.C.2
TEMple Bar 7587

we should

be pleased to demonstrate and give immediate delivery of the

"SOUND MIRROR"

Tape Recorder

"NOT the cheapest but certainly the best."

S.A.E., please, for catalogue.

Export enquiries welcomed.

"DEMOBBED VALVES" MANUAL



giving details of Service valves and their commercial equivalents—2/9, post free. Manual giving also British, American and Continental types. If yours is a valve problem—Bulls are the people to solve it. Send stamp for FREE comprehensive Valve

Lists. Please enquire for any new or obsolete types. Order C.O.D. ARP3 Special-purpose Tube, post free, 5/-.

TELEVISION Receiver Construction, a Wireless World Reprint. Post free, 2/9.

THE "Q-MAX" CHASSIS PUNCH—58in., 1in., 9/6 ea., 1in., 10/6; Key 9d.; 1in., 1in., 1in., 1in., 12/6 ea., 1in., 15/-; Key 1/-; 2-3/2 1in., 25/-; Key 1/-; 1in. sq., 19 6, Key 1/-.

TAYLOR ON EASY TERMS.—EASY TERMS up to 10 months—and very near Cash Price on all TAYLOR meters. Catalogue FREE. Taylor 240A Pattern Gen.; 30A, Oscilloscope; 47AS, Valve Tester; 55A, Wobbulator; 65C, W.R. Sig. Gen.; 70A, Multi-range Meter; 70B, Multi-range Meter; 75A, Multi-range Meter; 85AP, Multi-range Meter; 110B, Bridge; 170A, Electronic Test Meter, and the complete range.

AMPLION TEST METER.—1,800 ohm per volt on all D.C. and A.C. ranges; 10v., 100v. and 500v. D.C. and A.C.; 50 mA. and 500 mA. D.C. Resistance up to 200,000 ohm (3,000 ohm centre scale) with self-contained battery; 5,000 volt range with a separate H.T. test prod (8/6 extra). Supplied with test prods. Multi-colour scale easily readable, £4/7 6.

SPEAKER MATCHING TRANSFORMERS.—Ex-Govt. Surplus, only 1 9 ea.

TRIMMER TOOL SET. THE TRIMMER KIT which no Amateur or Professional Radio or Television Engineer, or serviceman, can afford to be without. Contains 1 End Trimmer, 1 Side Trimmer, 1 Yaxley Switch contact adjuster, 1 Low Capacity Trimmer, 1 screwdriver, 1 set of Feeler Gauges, 1 set of 6 Box Spanners from 1 to 8 B.A., 1 Set of 4 Spanners from 0 to 8 B.A., Endurable black crackle finish metal case. 25 6.

TALK on your Own Radio SING
RADIOMICROPHONE
HOME BROADCASTER

Connects to your radio pick-up or gram sockets. Talk or sing over your own radio from room to room! Easy to fix. With 2 microphones you can fix two-station house-phones in your own home! Order to-day!

Kindly mark envelope P.W.5. **12/6** Post 1/6

RADIO BULLS VALVES
246 HIGH ST., HARLESDEN NW11

DUKE & CO. SPACE URGENTLY REQUIRED, MUST BE SOLD.

TYPE 22/49 TRANSMITTER. 2.8 each, mostly brand new. Relays, crystal and coil wire removed (not the formers). Otherwise perfect as far as we can see. Transmitter includes: 11 resistors, 11 fixed condensers, 6-way Jones socket, 3 International V-holders, 2 tag panels, press-button switch, panel of sockets for crystals, 5-way choke, 3 bank Yaxley switch, aerial panel, intervalve trans., locking clamps, lamp-holder, 4 slow motion drives, valve caps, metal chassis and cover. No valves. Ideal for amplifier. Approx. contents not guaranteed. Post 1/6.

TYPE 25/1198 SUPERHET RECEIVER. 9/8. For short-wave reception. These convert easily to A.C. Universal or Battery All-wave receivers, 465, I.F.s, 4 tuning cond.; 28 fixed cond.; 32 resist.; trans.; switches, Vcontrols. Vholders, and all usual parts, less valves. NOTE. We supply FREE mains drawings. Post 1/6.

TYPE 53 TRANSMITTER. 3/6. 2.4 to 6.5; 4.8 to 13 mc's.; some cases and knobs are damaged and a little dirty, owing to bad storage. Contains: 44 cond. (incl. 5 tuning); 17 resist.; midket Vcontrol for speaker, 3 Vholders (less valves); choke; dial working on continuous scroll (slow motion); lamp-holder; toggle type switch; 2 coaxial sockets; Wchange switch; 3 P.B. worm drives; 2 chassis sockets (folding handle); 12-way Jones socket; springs; 5-coil formers; metal chassis in aluminium case, 9 1/2 in. x 8 1/2 in. x 6 1/2 in. All sets appear to contain all this, but not guaranteed either repairable or serviceable. Post 1/6.

T.V. PRE-AMPLIFIER. 7/6 POST FREE. Requires 1 valve EF54.

ELECTRIC MOTOR BLOWERS. 50/-, 13/6d h.p. S/phase A.C. 110 volt. Can be converted to 230 volt complete with forge type blower, 3 1/2 in. dia. outlet. Motor is 2,850-3,450 r.p.m., 1/2 in. spindle. Carr. each. **NOTE.** Ex-L.P.T.B. seat covers, 4/6 each. (Post 1/6 half doz.) Money Back guarantee if not satisfied. Cash with order please. Stamps ONLY. For lists.

218, ILFORD LANE, ILFORD, ESSEX.

LONDON CENTRAL RADIO STORES

PHILCO 5-VALVE RECEIVER. Superhet, long and medium wavebands. A.C. or A.C./D.C. 200-250 volt mains energised Speaker in Walnut cabinet slightly soiled. 90/- plus 7/6 carriage and packing.

3 WAVEBAND PHILCO. Long, medium or short. A.C. or A.C./D.C. £6.10.0 plus 7/6 carriage and packing.

THE FAMOUS R1155 10-VALVE COMMUNICATION RECEIVER. Equal to new. Frequency range 7.5 mc/s. 75 kc/s.; Five waveband. Complete 10 valves, including Magic Eye. Enclosed in metal case. Every Receiver aerial-tested. Complete with power pack and speaker for A.C. mains. 220-250v. £15, carriage and packing. 10/5. Circuit booklet with every set.

2-VOLT VIBRATORS. Type R76C. 7-Pin Self-Rectifying, 200 volt at 60 mA., made by Electronic Laboratories Inc., 7/6.

6-VOLT VIBRATORS. Type 560. Mallory 6-pin self-rectifying, 7/6. Type 550. 6-volt 4-pin, American base, 7/6.

12-VOLT VIBRATOR. Mallory, Type G629C. American base, 7/6.

ASTRA COMPASSES. Complete in transit box; useful for surveying, 15/6.

NEW NIFE ACCUMULATORS. 2.5v. 21 amp., for 8 hours. Size 3 1/2 in. x 4 1/2 in. x 1 1/2 in. Flat, 6/8.

VOLT METERS. Centre zero, 0.3 and 0.30 D.C., 17/6.

MAP READING TORCH. Magnifying lens, 3 1/2 in. diameter, in bakelite case, with dimmer switch. Takes two U.2. batteries, 22/6, less batteries.

UNISELECTOR SWITCHES. 4 bank, full wipe, 37/6; 6 bank, 1 wipe, 37/6; 3 bank, full wipe. Have various applications. Operates 25-50 volts.

10,000 OHM WIRE WOUND POTENTIOMETERS. 2/6.

EVERLASTING NEW INERT CELL ACCUMULATORS. No acid or charging required; great many uses for them. 1.5 volts. Size 2 1/2 in. x 2 1/2 in. x 5 1/2 in., 2/9 each; 3 for 7/6.

BRAND NEW MAINS TRANSFORMERS. 200-250 volts, 350-350. 6.3, tapped 4 volts 4 amp.; 5 volts tapped 4 volts 2 amps., 17/6; carriage and packing 1/6.

EX - ADMIRALTY PHOSPHOR BRONZE AERIAL WIRE. 100ft. on drums, 5/6.

NEW 130 H.P. A.C./D.C. DOUBLE-ENDED SPINDLE MOTORS. Size 5 1/2 in. x 3 1/2 in., 200-230 volts, 37/6; packing and carriage 2/6.

5-WAY V.L.R. FLEX CABLE. 6/6 12 yds.

5-WAY WORKSHOP CABLE (canvas covered), 5/6 12 yds.

WE DO NOT ISSUE LISTS.

Carriage charges relate to British Isles only.

23, LISLE STREET, W.C.2.

Telephone: GERrard 2969.

2 VOLT BATTERY SUPER-HET. 6-9 mcs. Chassis taken from the No. 18 Tx/Rx. Tested ready for use. 25/-.

New IN34 CRYSTAL DIODES. 5/6.

METERS. M/c 0-300v. 2in., 10/-; 0-40v. 7/6.

MULTIMETERS. 2 1/2 in. Supplied as kit with black bakelite cases, 6 x 4 1/2 x 1 1/2 in. and resistors for D.C. ranges 0-3, 0-30, 0-150, 0-300, 0-600v. and 60mA. Scale also reads OHMS 0-5,000 with 1 1/2 v. battery. 17/6.

MOVING COIL MICROPHONES with switch, 6/6. Trans to match, 5/-.

American MINIATURE LIGHTWEIGHT HEADPHONES. 8/6.

New 12in. ULTRA ELLIPTICAL ENERGISED SPEAKER with transformer. 400 ohm field. Magnificent tone. 21/6.

24v. AC/DC MOTORS 5 x 3in. fitted with powerful blower fan. 14/-.

R.C.A. 100 kc CRYSTALS. First Grade, 25/6.

TRANSFORMERS 230, 24v. 1A., 13/6.

SIGNAL GENERATOR, 200 mcs., easily converted to 144 mcs or TV bands. Complete with 6v. vibrator pack, in black metal case, 32/-, SIG. GEN. only, 11/6.

ARMY CARBON MICROPHONE with switch, 4/6. Trans to match, 3/6.

ADMIRALTY SLOW-MOTION DIALS. 100-1 with vernier. White ivory dial, 0-100. Worm driven. Beautifully made, new and boxed, 8/6.

All Carriage Paid. Money back Guarantee from—

THE RADIO & ELECTRICAL MART

253b, Portobello Road, London, W.11.
Phone: Park 6026.

HIGHSTONE UTILITIES

Crystal Sets, which are fitted with a permanent crystal detector. Why not have a set in your own room—10/6, post 6d. De Luxe set in polished oak cabinet, 18/6, post 1/-, Spare Permanent Detectors, 2/- each. When ordered separately, 2/6. With clips and screws, 2/10, post 3d.

Headphones, in good order, 4/6 and 5/6, post 6d. (Better quality) 7/6. **New Headphones,** 10/- a pair. Balanced armature type (very sensitive), 12/6 a pair, all post 6d. **New Single Earpieces,** 3/6. Bal. armature type, 4/6; ex-R.A.F. earpieces, 2/-, post 4d. All headphones listed are suitable for use with our crystal sets.

Hand Microphones, with switch in handle, and lead, 4/-. Similar instrument moving coil, 7/6, post 6d. **Sparkling Plug Neon Testers,** with test pocket clip, 3/6, and with gauge, 3/6, post 3d. **Soldering Irons.** Streamlined iron, with two interchangeable bits, one each straight and curved; 200/250 50 w., 10/-. **Standard Iron** with adjustable bit, 200/250v., 60 w., 12/-. **Heavy Duty Iron,** 150 w., 14/6, all post 6d. **Magnets,** Small ex. 2in. meters, 1/- each, post 3d. **Telephone Hand Generator** with handle, 7/6, post 1/6. **Rel. 3/6, post 6d.**

EX-R.A.F. 2-Valve (2-volt) Amplifiers, can be used to make up a deaf aid outfit, intercommunication system, or with crystal set, complete with valves, 20/-, post 1/6. Ditto, less valves, 10/-. **Wooden box to hold amplifier** 2/- extra. **3 Meters,** 10v., 2 1/2in. Rectifier (a.c.), in wooden carrying case, 14/6; 15 v., 2 1/2in., m.c., 9/6; 150v., 2in., m.c., 10/-; 3,500v., 3 1/2in., m.c., 20/-; 6,000v., 3 1/2in., m.c., 47/6; 15,600v., 2in., m.c. double reading, 8/-; 100 m.a., 2in., m.c., 7/6; 3.5 amp. 2in., T.C. 5/-; 4 amp., 2 1/2in., T.C. in case with switch, 7/6; **Meter Movements,** 2in. size with magnet and case (500 microamp), 2/6. **Units containing two movements** 5/-. All meters post extra. Money refunded if not completely satisfied.

HIGHSTONE UTILITIES. 58, New Wanstead, London, E.11. Letters only. New Illustrated List sent on request with 1d. stamp and s.a.c.

Cabinets of Distinction . . .

RADIOGRAM CABINETS
RECEIVER CABINETS
RECORD CABINETS
DRAWER UNITS

Catalogue available on request.

Chassis

A.C., 5-valve 3 w/b Superhet Radiogram chassis. Absolutely complete kit of parts, including wiring diagram £10.10.0
Or fully wired and tested £12.5.0

Amplifiers

Four to fifteen watts output. Wired, or in kit form, from £3.19.6

Full details of above available on request.

LEWIS RADIO CO.

(Dept. K9), 322, HIGH ROAD,
WOOD GREEN, LONDON,
N.22.

Telephone - - BOWes Park 5997



The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

Training Service Engineers

SIR,—Referring to D. F. C. Smyth's letter in the January issue of PRACTICAL WIRELESS. I was very surprised by the writer's statements regarding service engineers' wages, although he claims to have been associated with the radio industry since 1932. I should like to point out to Mr. Smyth that there are qualified bodies to represent the radio and television service engineer. During December, 1949, an agreement was arranged indicating amongst other things the *minimum* wages for a "qualified radio and television engineer." It should, therefore, interest your writer to know that the *minimum* rate for a fully-qualified radio service engineer is £6 12s. 6d., and for a television engineer of the same standing, £6 17s. 6d. per week. It should be noted that these rates are "rock bottom," and in practice enlarged upon. It also appears as though your writer is rather hazy about the term he uses, "competent radio engineer." The term *fully qualified* in reference to the above agreement indicates that the engineer holds the "A" certificate of the "Radio Service Trade Register." Before this certificate is issued the engineer must have passed the "R.T.E.B." radio examination or equivalent, which in itself is very comprehensive, and, further, before he is able to sit for the examination he must be able to satisfy the examination board that he has been gainfully employed in the industry for at least five years. In order to qualify for the television certificate the engineer must pass either the R.T.E.B. television examination or a manufacturer's course. I can guarantee that Mr. Smyth will be able to ask for much more than £5 10s. when he can satisfy the above conditions. I should like to add that it is the aim of the G.R.S.E. to "stamp out" for ever these self-named "radio engineers"—these in the trade are known as "quacks" and are they who have given the trade such a bad name in the past.—GORDON J. KING (Oxford).

[This correspondent has missed the whole point. Not all employers recognise minimum rates, nor do they belong to Federations signatory to the agreement and are not therefore tied by it. Even service engineers sometimes work under rate!—E.D.]

SIR,—From the point of view of an enthusiast from the earliest days of wireless, when you had to understand Morse to enjoy the hobby, and when the V24 was the valve of the day for H.F. work, I found this correspondence very interesting.

When the hobby palled and I sold my equipment

(I bitterly regret this sale, and will tell you why), I acquired a radiogram by a world-famous maker which gave excellent service for a long time, but when trouble eventuated I called in the firm of local experts, complete with letters after their names, etc., and when these "qualified servicemen" had returned the set with a bill for 35s. and a new on/off switch wired in parallel with the original, I found the condition of the set absolutely unaltered, and sent it back again. With its return once more and another bill for 10s. the set was still quite useless, but as I was due to move to another town I could not do much about it. In Hove the qualified dealer charged me for a new frequency changer and a few other items, which added up to two bills totalling £3 10s. 0d.

I moved to my present address, although in the meantime I had laid the set up pending finding someone who really was a good serviceman, and for nearly twelve months was without it.

Then the largest firm of electrical and radio dealers, and, incidentally, the agents for the makers of my set were called in, and they were reluctant even to look at anything which was more than three years old. I eventually got them to have the set in for inspection and they said it was not too bad, and after five deliveries to me and return to the "shop" they said that the set was now as good as it would ever be. The distortion was terrible, the H.F. side grossly mis-aligned, and the needlecup had been brutally dug out of the polished wood panel with a screwdriver, and was ringed with marks radiating in all directions. I called in the chief of the service department to inspect this damage and to hear the set and comment on its poor performance; he said he would make inquiries, but I have heard nothing further, although I have received a bill for £4 10s. 0d.

For Mr. Harrison's benefit I would say that this set has never been handled by a dabbler, never by anyone but the three "experts" in three separate towns. An amateur would not have done worse; he would very likely have done a much better job and charged me less. The set concerned is straightforward and no super-compact article.

The trouble with this set was that it needed the dust blown out, a new volume control, and *nothing else*, and I have had to pay £10 to the "experts." The radio service business is a racket. Charges of 30s. for unsoldered connections, or the replacement of 6d. components are commonplace. The string of letters after the "service engineer's" name is a mumbo jumbo which involves a cloak

for inefficiency, and a desire for a closed shop in radio.

The device described by Mr. Harrison, where invoices are endorsed: "Cost increased due to inexpert attention" is presumably designed to discourage the employment of free-lance servicemen by set owners. If the radio trade itself were not full to overflowing with people with little or no radio knowledge, although possibly with a sufficiency of capital to run a shop, there might be an excuse for the sneers at the "dabbler." My experiences tell me that there is probably a large slice of truth in the contentions of Bernard F. Appleton and others.—G. H. GUNTER (Eastbourne).

Resistance and Ohms Law

SIR,—With reference to my letter on page 138 in the March issue, I should like to point out that the printers have mistaken the symbol ρ (rho). As printed it does not make sense. The eleventh line from the bottom of the first column should, therefore, read: "Even if we calculate the value of R, we still have to use ρ , the value of which. . . ."—SIMPLETON (S.W.1).

A Small Oscilloscope

SIR,—I have constructed the small oscilloscope recently described in your magazine.

The result was most satisfactory and, except for one or two small details, the construction was comparatively easy.

One of the biggest snags was interference by the magnetic field of the mains traus.

This field affected the spot when at rest, and to effect a remedy I had to move the tube forward about 2 to 3in.

To support the tube I had to fit an extension tube; this, however, does not affect the appearance of the set.

The wiring is formed and laced and the grid leads are screened and earthed.—ALAN CRONIN (Belvedere).

Programme Pointers, etc.

SIR,—I have just been reading Mr. Maurice Reeve's attack on "The Life of Leslie Stuart," a programme that I enjoyed very much. This is his second attack on the pre-First World War composers. (The first occurred some months ago.) This time Lionel Monckton, Leslie Stuart, etc., are the victims; who knows, Sir Arthur Sullivan may be next! The music alone of the "Arcadians" makes it an evergreen.

The music by English composers of the period 1870-1914 is far away ahead of the music of the past 35 years. I am referring, of course, to musical comedy and light opera.

Although not a B.B.C. subscriber, I would love to hear a series of programmes of the works of Sir Arthur Sullivan.—G. BYRNE (Eire).

Heater Supplies

SIR,—I think, perhaps, that a word of warning should be added to "Electron's" article in the March issue concerning heater supplies. It is

an attractive proposition to use the odd tappings when an appropriate secondary winding is not available, but the matter is fraught with pitfalls for the inexperienced.

For instance, when using the circuit shown in Fig. 1 of the article for a rectifier and the live mains lead is connected to the 220v. tapping, the full mains voltage, very nearly, appears across the heater/cathode insulation with the usual form of circuit because the reservoir condenser between cathode and earth has negligible impedance to mains frequency. This is not quite what the valve makers recommend for most of their valves. Another point to note is that the rectifier heater cannot be tied to the rectifier cathode, as is common practice in A.C. sets or the H.T. line will be connected direct to the mains, nor can it be tied to earth because, if the live mains lead should then be connected to the 220v. tapping, there would be an almost dead short across the mains. The heater would necessarily, therefore, be left floating, as shown in Fig. 1.

The method of splitting the 200v. tapping loop, as shown in Fig. 2, is not without danger either. These wires are generally enamelled and lie in contact with each other for some inches. Now if the mains live lead is connected to the 200v. tap, i.e., to one end made by breaking the loop, the mains voltage will appear across the two adjacent wires insulated only by the enamel.

Due regard to these points should be paid if these circuits are used, and the circuit decided upon should be carefully checked to ensure that the D.C. voltage between heater and cathode is not higher than that quoted as maximum by the makers. For instance, if the circuit of Fig. 2 is used for a rectifier and the heater is earthed as shown, the full H.T. appears across the heater/cathode insulation; if, to avoid this, the heater is tied to cathode the H.T. voltage appears across the two severed ends of the 200v. tapping loop, plus the peak mains voltage on one half cycle if the live lead of the mains is connected to the other wire of the loop.

A point arises in connection with Fig. 3. It will probably be desirable to connect the earth direct to the most vulnerable valve heater, i.e., the detector of a receiver or the first valve of an amplifier if such is fed from the arrangement.

I would suggest that the auto-transformer arrangement shown in Fig. 4 would be far better in all cases, and it would not be difficult to extend its construction to permit the operation of valves of any standard heater arrangement from the 4v. or 6.3v. winding usually available.—R. HINDLE (Wallasey).

Two-band Aerial

SIR,—In the April issue your correspondent, Mr. O. J. Russell, credits WØWO with the development of this off-centre fed antenna using a 300 ohm line.

I have been using it with success since I read a reference to the system in QST shortly after the bands were reopened.

Therein G8IG was mentioned, although no claim for originality was made for his use of the idea. However, he does considerably pre-date WØWO.—CHAS. MCCARTHY (E16G) (Cork).


FAME!

Our famous "HOME CONSTRUCTOR'S HANDBOOK" has been acclaimed the world over, and from the vast quantities sold, also from letters in our files, there is no doubt this book satisfies ALL interested in radio. If, by chance, you haven't had a copy you really are missing out on the best value! Send to us NOW for the latest issue price 2/- (Worth very many times this purely introductory price.)

- **30 TUNING UNIT.** 3-wave (iron-cored coils), sheet coil pack, iron-cored I.F.T.'s, J.B. 2-gang, and latest 3-colour 8 x 6 dial. **ALIGNED AND SEALED IN OUR STANDARD 5-VALVE RECEIVER.** No further adjustments necessary! 69 9 inc.
- **40 TUNING UNIT.** Similar to above BUT WITH R.F. STAGE! 99 6 inc.
- **NEW AND IMPROVED 40N-STRUCTION SHEETS!** These famous sheets have been improved and are now the last word in simplicity. You need no radio knowledge to build our elegant sheetsets! No test equipment required whatsoever.
- Our standard range of highest quality coil packs, chassis, components, etc., always available.
- Complete J.B. dial units to match our coil packs, including S.L.8 spin-wheel tuner, 25/- for 20 9, with either Tuning Unit.

Remember—SERVICE TO OUR CUSTOMERS ABOVE ALL! is a maxim we constantly bear in mind, and our large Mail Order Service, in our excellent packing department, ensures that all goods quickly reach your door in A1 condition.

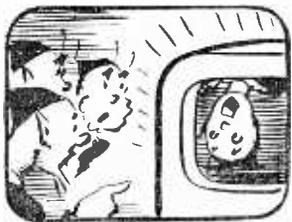MAIL ORDER ONLY.
RODING LABORATORIES
 (MAIL ORDER DEPT. W.M.)
70, LORD AVENUE, ILFORD.



The "Fluxite Quins" at Work
 "Now stop all this acting the fool
 You all know the one golden rule.
 If you'll get some FLUXITE
 And put this set right
 We'll continue with Muffin the Mule."

See that **FLUXITE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in this, from 1/- upwards.
The FLUXITE GUN puts **FLUXITE** where you want it by a simple pressure. Price 2/6, or filled 3/6.

FLUXITE

SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT" Soldering and for Leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with **FLUXITE**. Price 14, each.
FLUXITE Ltd., Dept. W.P.
 Bermondsey Street, London, S.E.1.

VALVES

ABSOLUTELY BRAND NEW— ORIGINAL CARTONS

6V6GT, 5Z4M, 5U4G, 6E6, 1S4, 1S5, 1R5, 3S4, 1T4, 41, 78, 6C6, 6D6, U18, EF8, 5Y4, FW4/500.

ALL AT 7/6 EACH.

6K7G, EBC33, 6K7GT, VR137, EF36, EK32, 6N7, 6C5, 6SK7, 6B8, 12A6, 7Q7.
 ALL AT 6/- EACH.

| | | | |
|-------------|-----|----------|------|
| VR150/30 .. | 7 9 | 6H6 .. | 4/6 |
| 12K8 .. | 6 9 | 6J5 .. | 4/6 |
| 6X5 .. | 7/- | VU111 .. | 4/6 |
| EF39 .. | 6/6 | DDL4 .. | 4/6 |
| EL32 .. | 7/- | 955 .. | 3/- |
| 807 .. | 7/- | EA50 .. | 2/9 |
| 1C5 .. | 7/- | SP61 .. | 3/6 |
| 6L6 .. | 9/6 | SP41 .. | 3/- |
| 954 .. | 3/0 | EF8 .. | 7/6 |
| EF50 .. | 7/- | 6SH7 .. | 4/6 |
| 6J7 .. | 6/9 | 37 .. | 4/6 |
| MS/PEN .. | 8/- | VR54 .. | 4/6 |
| 9D2 .. | 5/- | CV6 .. | 1/9 |
| 956 .. | 3/- | KT66 .. | 10/6 |

SEND FOR COMPONENT LIST.
 CARRIAGE PAID OVER £1. C.O.D. or C.W.O. POST ORDERS ONLY.

ALPHA RADIO SUPPLY CO.
 5/6, Vince's Chambers,
 Victoria Square, LEEDS 1

MIDLAND INSTRUMENT CO.

For Govt. Surplus Stock, Etc.

MODULATOR UNITS Type 169, contains CV-87 Klystron valve, 5U4C, EF50, also B401 spark valve, 3 neon stabilizers complete with batten type holders, small motor fitted reduction gearing, various oil-filled and other condensers, transformers, pots and many other incidentals in metal cases size 18in. x 8 1/2in. x 7 1/2in., new in wood cases, bargain offer 37 6, carriage 7 6. **MAINS TRANSFORMERS**, 200-220-240v., 50 cycles, 1 phase, tapped output giving 3-4-5-6-9-10-12-15-18-20-24-30v., at 2 amps., new boxed with all termination data, 20/-, post 1 3. **VOLTMETERS**, 0-100 v. A.C., fitted internal instrument rectifier, basic movement 1 m.A., 2 1/2in. scale, flush panel mounting, new boxed 20/-, post 6d. **FEEDER COUNTERS**, 0-9999, enclosed in plated cases, 5/-, post 3d. **CRYSTAL RECTIFIERS** CV-102, new in lead capsules 3 6, post 3d. **MOVING COIL HEADPHONE**, with attached 16 moving coil microphone, hand type fitted switch, 6/1 set, post 10d. **FUSEHOLDERS**, bakelite, single hole panel mounting, containing a 3 or 10 amp. fuse, 1/-, post 3d.; 10/- doz., post 7d. **PANEL RADIO TRANSFORMERS**, iron through shrouded type with long leads, primary 110-225-245v., secondaries 250-0-250v. at 90 m.A., 5v., 2 amp., 0.3v., 3 amp., screen, a high grade transformer, new boxed 17 6, post 1 3. **VALVE HOLDERS** for 6B6 range, bakelite 8-pin metal shroud with spring lock, new stock, 1/-, post 3d.; 10/- doz., post 6d. **TOGGLE SWITCHES** 5D 531, single hole panel mounting, 250v., 2 amp., s.p.c.o. or on/off, new boxed 6d., post 3d.; 7 6 doz., post 6d.; 72/- gross, post 1 6. **MOTOR BLOWERS**, 24v. A.C.D.C., new unused 7 6, post 1 1. **ROMEX VACUUM PUMPS**, new unused 12 6, post 1 4. **MOTOR GENERATORS** TYPE 34, input 24v., output 200 v., 30 m.A., and 6.3v. at 2 amp., unused 5/-, post 1 8. **SLYDLOK 30 amp. FUSES**, new unused 2 6, post 4d.; 24/- doz., post 1 3. **R.F. METERS**, 350 m.A., new boxed 3 6, post 6d. Send s.a.e. for current lists with supplement.
MOORPOOL CIRCLE, BIRMINGHAM, 17
 HARborne 1308 or 2624.

MORSE CODE Training



COURSES for **BEGINNERS** and also **OPERATORS**, also a **SPECIAL COURSE** for passing the **G.P.O. Morse Test** for securing an **AMATEUR'S TRANSMITTING LICENCE**.
 Send for the **Candler BOOK OF FACTS** It gives details of all Courses.

THE CANDLER SYSTEM CO.
 (Dept. 5L0), 121 Kingsway, London, W.C.2.
 Candler System Co., Denver, Colorado, U.S.A.

NEW BOXED VALVES—6K8M, ECH35, N66, 6V6, 6L6, KT66, KT33C, 10-; 1R5, 1T4, 1S5, 3S4, 6SA7, 6C6, 6D6, 20VP2T, Z21, VP2B, TD2A, PEN220A, KT61, KT63, EF39, EBC33, VP4, MS PEN, SP4B, VP13, HL13DD, 8 6; 1L4, 1S4, 3A4, 3Q4, 6K7M, 6X5GT, 5U4G, 6C4, 6SJTGT, 6V6, ATP4, 7 6; EF36, EL32, 6ACTM, 6K7G, 9002, 8 6; 6C6GT, 6D2, 5-; 6J5GT, 954, 955, 3 6. Many other types of valves available at Bargain Prices. Send S.A.E. for full list.
2-BANK 11-WAY YANLEY SWITCHES, 1 6 each.
250 VOLT 80 M.A. SELENIUM RECTIFIERS, 5 6 each.
ALADDIN COIL-FORMERS, 24, each.
TABLE MIKES (BAL. ARM.) with switch in Base, 3 6.
 Large selection of Tag Strips, Socket Strips, Plugs and Sockets, and other Sundries. Please add postage on Orders under £1.
ELECTRAD RADIO
 64, Gt. Victoria Street,
 BELFAST, NORTHERN IRELAND.

OUTSTANDING OFFERS

1155 Receivers. Complete with Valves. Brand new in transit cases, 10 gns., carr. 7 6.
EX ARMY R107 Famous Communications Receiver. 9 valves, 17.5 to 1.2 mcs. Brand New and unused. Complete with Manual 16 gns. Carr. Paid.
Collaro Gram Units AC504. Brand New. Latest rim drive. Complete with pick-up (not auto-change), £6 11s., carr. 1/6.
Viewmaster Parts. A quantity to be cleared at greatly reduced prices. State wants.
Ex R.A.F. 4v. Battery Receivers. Wooden Cabinet. 18in. x 18in. x 8in. medium wave. Complete with valves, 59 6, carriage paid.
87 Rotary Power Units. Brand New. Input 24 volts. Output 250 v. 65 ma., 614 v. 2.5 a. Length 8 1/2in., depth 7in., width 4 1/2in. Weight 11 lbs. Neat black case with detachable top. Base incorporates elaborate smoothing circuit, 10/-. Postage 1/6.
Heavy Duty Smoothing Chokes. About 300 ma., 10/-, plus 2/6 carriage. Weight 19 lbs.
 LIST FREE.
 Prompt delivery and satisfaction Guaranteed.
H.P. RADIO SERVICES LTD.
 Britain's Leading Radio Mail Order House.
55, COUNTY ROAD, WALTON, LIVERPOOL, 4. Tel.: Aintree 1445.

Impressions on the Wax

Review of the Latest Gramophone Records

THE recording of "Giselle" by the Royal Opera House Orchestra, Covent Garden, conducted by Robert Irving, who shared in the Sadler's Wells Company's phenomenal American success, will give immense pleasure to the large audience of ballet-goers who follow the company. The music is played here as for the Sadler's Wells' staging of "Giselle," and comprises scenes from Act I. Its composer, Adolphe Adam, was considered a leading figure in the spheres of ballet and "opéra-comique" during his mid-nineteenth-century reign of popularity. Now his work survives only in the one ballet, "Giselle." Automatic couplings only are supplied on *H.M.V. C7834-5*.

Of the many waltzes that Josef Strauss gave to the world, undoubtedly the "Music of the Spheres" is one of his masterpieces. This recording of it by the Vienna Philharmonic Orchestra, conducted by Karl Böhm, on *H.M.V. C4070*, comes from the city that gave the waltz its greatest impetus.

The overture to Nicolai's opera, "The Merry Wives of Windsor," has been heard many times, but the recording by the London Philharmonic Orchestra, conducted by Sir Adrian Boult, on *H.M.V. DB21223*, seems to gain for it additional attractions.

Dvorak's "Symphony No. 4 in G," sometimes known as the "English Symphony" for the slim reason that it was published in this country, has been admirably recorded by Bruno Walter conducting the Philharmonic Symphony Orchestra of New York on *Columbia LX1365-8*. In the fourth symphony Dvorak wrote music of a more arresting colour and effect than the majority of orchestral composers.

Columbia LX1360 presents a splendid version of the wedding celebrations, included in the introduction to Act III of Wagner's "Lohengrin." It has been recorded by the Vienna Philharmonic Orchestra conducted by Herbert von Karajan, and the Vienna State Opera Chorus. The "Bridal Chorus" never fails to impress one as an outstanding example of the composer's skill.

Vocal

It seems particularly fitting that Gigli should provide us with a version of Cottrau's famous "Santa Lucia" with all the advantage of modern recording. He sings it in Neapolitan on *H.M.V. DA1963*. On the reverse is a song in Italian, worthy companion to its more familiar neighbour, and ample material for Gigli's voice.

Another Italian tenor is introduced on *Columbia LX1364*. The excerpt he sings from Donizetti's opera, "La Favorita," is the aria, "Spirto Gentil," (Spirit so Fair) from Act IV. It is regarded as a test

of a tenor's skill, and Poggi's interpretation does him great credit. On the reverse is the aria, "M'appari tutt' amor," which is one of the gems of Flotow's "Marta."

The two songs chosen by Webster Booth for his latest recording come into the category of ballads. "May the Good Lord" is the signing-off song of one of America's biggest weekly radio programmes, "The Big Show." The coupling, "No More," is Jack Popplewell's adaptation of Sebastian Yradier's "La Paloma." The number of the record is *H.M.V. B10035*. The accompaniment is by Sidney Torch and his Orchestra.

The *H.M.V.* series of recordings from the Glyndebourne production of Mozart's delightful ensemble opera, "Cosi fan Tutte." On one side is a trio and on the other a soprano solo from Act I. *H.M.V. DB21118* is the third in the series by the Glyndebourne Opera Company.

Variety

Many listeners no doubt heard the French singer, Line Renaud, when she appeared in Henry Hall's Guest Night, and she now makes her debut on *Columbia DB2830*, singing "Cabin in Canada" and "Au Revoir Again," accompanied by Philip Green and his Orchestra.

Two of the songs from the musical, "Kiss Me Kate," which recently had its opening night in London, have been chosen by Dinah Shore for her recording on *Columbia DB2820*. They are "Always True to You in my Fashion" and "So in Love." This popular singer was recently voted America's favourite woman vocalist in a nationwide survey carried out by the A.I.P.O.

Recently, Donald Peers recorded for the first time with The Merry Maes, the celebrated American vocal team. In his latest recording on *H.M.V. B10039* he is again joined by them for unusual renderings of the "Tennessee Waltz" and "My Heart Cries for You."

Dance Music

Geraldo's new titles couple a waltz revival, "If," with Eve Boswell singing the refrain, and a one-step, "Ferryboat Inn," in which the Geraldtones group is heard. This is on *Parlophone F2453*. Other popular recordings by dance-bands include "The Roving Kind" and "I do, do, do Like You," by Sid Phillips and his Band, on *H.M.V. BD1269*; "My Heart Cries for You" and "Tennessee Waltz," by Joe Loss and his Orchestra, on *H.M.V. BD6687*; and "So in Love" and "Can't Seem to Laugh Any More," by Victor Silvester and his Ballroom Orchestra, on *Columbia FB3598*.

Editorial and Advertisement Offices :
 "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone : Temple Bar 4363.
 Telexgrams : Newnes, Rand, London.
 Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed to The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

BOOKS

TWO BOOKS, which are still the first of their kind to be published, are still the best value you can get—at least, so our readers say time after time. They are "Personal Portables," at 2/8 post paid, and "A Portable Television," at 3/2 post paid. Both by E. N. Bradley; both from BRADBROOKS, Sennen, Penzance, Cornwall.

R.S.G.B. "Amateur Radio" publications: Transmitting Licence, 32pp., 1/-; Service Valve Equivalents, 32pp., 1/3; Transmitter Interference, 32pp., 1/6; Simple Transmitting Equipment, 52pp., 2/3; Microwave Technique, 68 pp., 2/3; Receivers, 96pp., 3/9; Valve Technique, 104pp., 3/9; V.H.F. Technique, 96pp., 3/9; R.S.G.B. Bulletin, current issue, 1/6. Five recent issues, 2/6. Prices include postage. **RADIO SOCIETY OF GREAT BRITAIN**, 28, Little Russell St., London, W.C.1.

RECEIVERS & COMPONENTS

R3132 U.H.F. RECEIVERS, 7 EF50, 2 EF52, 1 VR137, 1 5Z4, consists of a two-stage RF amplifier, mixer and oscillator, a three-stage IF amplifier and AF amplifier, suitable for modification to television. £3/15/- each 10/- post. Slow motion drives, 6in. dia. scale, brand new, surplus, 8/6 each, inc. postage. Bakelite cabinets, 9in. long, 5in. wide, 7in. tall, with drilled chassis, back cover, and dial, 22/6. 3in. Speaker, 22/6 extra; carriage 5/- **ARTHUR THOMAS & CO.**, 532, Garratt Lane, London, S.W.17.

PHOTO-ELECTRIC METER COMPONENTS. Selenium Light Cell, 6/6. Micro-amp. Meter Movement, 16/6. Perspex Case, 10/6. Assembly instructions, 2/6. **G.R. PRODUCTS**, 22, Runnymede Ave., Bristol, 4.

MIDDLESBROUGH . . . phone 3096 or call PALMERS, 114, Waterloo Road. Large stocks Radio and TV components.

BUILD with our concise instructions: AC/DC complete in cabinet, T.R.F., £5/10/-; M.S.S. Superhet, £6; L.M.S. Superhet, £6/5/-; Amplifier, suitable for gram or mike, £4/10/-. We still publish the "Cheapest List in England." **SUSSEX ELECTRONICS, LTD.** (W), Princess St., Brighton.

SPK. TRANS. 1/-, M/R 2/6, 200/250v Mains Sec. 4v and 8v, 2/6. Small Choke, 300 ohms, 50ma, 1/6. Resistors, 25 ass. 2/6. Midget Components. List 21d. **CARTER'S**, 67, Bell Lane, Marston Green, B'ham.

AUDIO OSCILLATOR. Rotary Converter. Test Equipment. Components for sale. Amateur giving comp. List available. **TOVEY**, 63, Hythe Rd., Swindon.

ALIGNMENT PEAKS. Second edition. 5,000 superheterodyne alignment peaking frequencies, 4/9 post free. The Practical Radio Engineer, quarterly publication of the Institute, sample copy 2/- post free. Membership and examination data 1/- post free. Secretary, I.P.R.E., 20, Fairfield Road, London, N.8.

AMATEURS, Dealers, Servicemen.—Why pay fancy prices? "Be in the know." Send S.A.E. to-day for list that will save you pounds. Goods C.W.O. No "C.O.D." Money back guarantee. **ANNKIN**, 25, Ashfield Place, Otley, Yorks.

RATES: 4/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 6d. extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

.01 1,000v., 2/6 doz., .1, 350v, 2/6 doz., .0001, mica, 2/- doz., etc. List from T. G. HOWELL & CO., 29, McWilliam Rd., Brighton, 7.

VALVES—New, boxed: 954 at 2/6; VU120A at 4/6; 6D6, 6K7G, 6SG7, CV321 (KT66), at 6/6; 1S4, 807 at 7/6; (RT/5CP1 at 22/6. Mazak Sockets for SCR.522-10H/402-404-419 at 1/6; 10H/414 (6 way), 10H/416 (12 way) at 2/-; 10H/417 and 418 (18 way) at 2/6. New, boxed. Power Units for W/S/19 Mk.II, new condition, 27/6 each. SCR522, must sought after V.H.F. set good condition, 7/6 with valves in case, nothing missing, £12 each; only few left. Postage 6d. under 15/-. **GILFILLAN & CO.**, 52, South St., Worthing, Sussex. (Tel.: Worthing 3127.)

ELECTROSTATIC VOLTMETERS, 0.3-500, plug-in, 2 1/2in., 25/-; Meters, 2 1/2in., flush mounting, F.S.D. 250 microamps, shunted and scaled, 0-1ma, 10/-; Voltmeters, double reading, M/C, 0-15/250, with spike and test prod., 12/6; Twin I.F. Filter Units 465 Kc/s., 10/-; I.F. 1/5 20 meg. c/s. cond. T. 5/-, 465 c/s. slug. T. 6/-; H.D. F.I.s, input 200-230v 50 c/s. output 2-0-2v, 7a, 6-0-6v 8a, and 5v, 35/-; Tubular W.W. Resistances, 4.8w 1/-, 10w 1/3, 20w 1/6, 60w 2/-; Condensers, Tubular, 30,000v .01 mfd 15/-, 600v .01 mfd Sprague 6d., Electrolytics, 12v 50 mfd 6d., 12v 4 mfd 4d., oilfilled 8 mfd 600v 7/6, 5 mfd 1,000v 8/-, 4 mfd 600v 5/-; Orders over £2 post free. **F. R. BARRETT**, 7, Upper Kent St., Leicester.

BRAND NEW Guaranteed Goods—Mains Transformers, fully interleaved and impregnated, primaries 200-230-250v screened. Drop through types, with Top Shroud: 260-0-260v 70ma, 6.3v 3a, 5v 2a, 13/3; 250-0-250v 70ma, 6.3v 2a, 5v 2a Midget, 24-3-2 1/2in., 14/11; 350-0-350v 70ma, 6.3v 3a, 5v 2a, 16/9; 350-0-350v 80ma, 6.3v 4v 5v, 17/9; 350-0-350v 90ma, 6.3v 3a, 5v 2a, 19/9; 350-0-350v 100ma, 6.3v 3a, 5v 3a, 21/6; 350-0-350v 120ma, 6.3v 4a, 5v 3a, 26/9; 350-0-350v 150ma, 6.3v 4a, 5v 3a, 28/9. Fully Shrouded Upright Mounting Types: 250-0-250v 60ma, 6.3v 3a 5v 2a Midget, 24-3-3in., 16/9; 250-0-250v 100ma, 6.3v 6a, 5v 3a, 26/9; 350-0-350v 70ma, 6.3v 2a, 5v 2a, 18/6; 350-0-350v 100ma, 6.3v 4v 4ma C.T., 0-4-5v 3a, 23/11; 350-0-350v 120ma, 6.3v 2a, 6.3v 2a, 5v 3a, 31/9; 425-0-425v 200ma, 6.3v 4v 4a C.T., 6.3v 4v 4a C.T., 0-4-5v 3a, 47/9. Smoothing Chokes: 40ma 10h. 360 ohms, 3/3; 80ma 12h. 350 ohms, 5/3 ea.; 100ma 10h. 100 ohms, 200ma 5h. 100 ohms, 7/6 ea. Output Trans.: push-pull 10 w. 6V6, PX4, 6L6 to 3-5-8-15 ohms, 15/9; Williamson type, exact to author's spec., 12/-; Misc. Items: Ex-Gov. Smoothing Chokes, Trop., 100ma 10h. 100 ohms, 4/3 ea. T.V. Masks, 12in., cream, 12/9. New boxed Ex-Gov. Smoothing Chokes, Trop., 956, 2/9; 6J5GT 3/9; 6K7GT, 5/3; 1S4, 6D6, 6C6, EF50, 6C5GT, 6J7 Met., 1L4A, 6B8 Met., 6AC7, VR150, 6/6; KT66, 7/11; KT2, VU171, 4/3. Following Ex-Gov. New Equipment: HL210 2/3; SG215, SP1, 3/9; EP33, EP39, 2/6; 12SK, 12SV7, 5/9; 6CA, EF36, EF50, 4/9; EL32, 6/11; 1D, 11d. C.W.O. or C.O.D. over £1. P. and P. 1/2 all orders under £3. Full list 3d. Special list for trade 3d. **RADIO SUPPLY CO.**, 34, Hanover St., Park Lane, Leeds.

VALVES

NEW BOXED VALVES—6K7G 4/9, 8D2 3/9, 6P6G 7/6, ECH35 9/6, 6V6 7/6, 5Z4 6/6. Thytron CV-1798, 7/6. SP41 4/6. SP61 4/6. 25Z6 10/-. Large range other surplus types in stock. With B.V.A. stock we suggest you order C.O.D. New Speakers: 3in. 10/6, 5in. 12/6, 6in. 13/6, 8in. 15/6, 10in. 18/6, 12in. 45/-. Coax Cable, 80 ohms, 10/- doz. yds. Valve Hldrs. Int/oct (Amph), 7/- doz. EF50, 5/- doz. Pre-amp Chassis with v/hldrs., resistors, condensers, etc. brand new, condn., 4/6. Micamold, 1350v, Conds., 7/- doz., 8mf 45v, 2/9. Resistors, 1 watt, 4d., 1 watt, 7d. New lists available. Id stamp, "RAEMOS," 52, Pendlestone Rd., Walthamstow, London, E.17.

VALVES (new bxd.)—6AC7, 6C5, 6Z7, 6K6, 6K7, 6N7, 6X5, KTW61, 54M, 6J5, 12A6, EF36/VR56, 9003, 4D1, SP61, SP41, VU11, 6B8, all at 6/6 each. 1R5, 1S4, 1S5, 1T4, 3S4, EK32, 6V6, EF39/VR53, all at 7/9 each. "Universal" Mntg. Mains Transformer, 350/0/350 80ma, 6v 5v, both tapped at 4v impt. 200/240, 16/6 post pd. Still Going Strong * * * Room to Room Telephone (see March "P.W."), 5/11. Thousands of lines stocked, suitable enquiry to **LORNE RADIO SUPPLIES**, Mail Order, 7, Lorne Rd., Walthamstow, London, E.17. Your best supplier.

VALVES—EL50, 6F6G, 6K7G, 6N7GT, 6AC7, 6SG7, 7Q, 7V7, EF54, 12A6, EL16, EF36, EF39, S19, RK34, EBC33, 6C6, 6D6, 42, 6SK, 1IN5GT, VU120A, KTZ63 (6J7G), MS/PEN, MS/Pen/B, at 6/6; 1T4, 1S5, 1R5, 3A4, 6K6GT, 6SA7, 5Z4, 5U4G, U14, VR150/30, EP91, at 7/6; 6L6G, KT66 (CV321), Pen46 at 10/-; EF50, 9003, 6AC7, 2X2, at 5/6; ML4, 6J5GT, at 4/6; 954, 955, 956, at 4/-. Post 6d. under 20/-. **R. T. & I. SERVICE**, 254, Grove Green Rd., London, E.11.

GUARANTEED Boxed Valves—1R5, 7/6; 1S5, 7/6; 1T4, 7/6; 1S4, 7/6; 3S4, 9/-; 2X2, 7/6; 4D1, 7/6; 5U4, 8/6; 5Z4, 7/6; 6AC7, 7/6; 6AM6, 10/6; 6B8, 6/6; 6E6, 3/6; 6J5, 6/6; 6K6, 7/6; 6K7, 7/6; 6K8, 10/6; 6J7, 7/6; 6V6, 7/6; 6X5, 7/6; 8D2, 7/6; 9D2, 7/6; 12K8, 8/6; 25A6, 8/6; 25L6, 8/6; 50L6, 8/6; 8/6; 807, 8/6; ECC91, 10/6; EP91, 10/6; HVR24, 7/6; KT66, 10/6; MS/PEN, 7/6; VR53, 7/6; VR54, 3/-; VR55, 7/6; VR57, 7/6; VR65, 5/6; VR65a, 5/6; VR66, 5/6; VR78, 2/-; VR91, 6/-; VR92, 2/6; VR16, 5/6; VR136, 6/-; 100 K.C. Xtal R.C.A., 10/6. TRS, 71, Headvale Rd., E. Croydon. Callers: 2 Pawsons Rd., W. Croydon. (Tel. 1665.)

RF UNITS TYPE 24, and 24 mod. 27 at 42/6 ea., plus 1/3 car. £1124, with 6 universal valves. OK for TV sound, 21/- ea. We have large stocks of ex Gov. Radio, Electrical and Optical goods. S.A.E. will bring you complete lists. **H. ENGLISH**, Rayleigh Rd., Hutton, Brentwood, Essex.

REPAIRS AND REWINDS

LOUDSPEAKERS repaired promptly. **MODEL LOUDSPEAKER SERVICE**, 34a, Billington Road, Oxford.

VACUUM CLEANERS and Gram. Motors, repairs our speciality. Armature rewinds, new bearings and commutators fitted, also transformers removed, speakers repaired. Competitive prices. Trade enquiries invited, 2 to 5 days c.o.d. service. Send s.a.e. for price lists to: **A.D.S. CO.** (V.E.M. Dept.), 261-3, Lichfield Rd., Aston, Birmingham, 6. Est. 1935.

HI-FI



AMPLIFIER A1

For use on A.C. 200-250v. only. Complete kit incl. valves for a first-class gramophone amplifier giving high quality reproduction. Simple instructions coupled with many illustrations enable even those without previous experience to construct this amplifier. Kit complete in every detail down to solder tags and solder. Pre-drilled chassis. Group board containing all resistors and condensers, etc.

| | | |
|--------------------------------------|--------|----------|
| Complete kit with instruction manual | | £4 2. 6. |
| Instruction manual only | | 3. 0. |
| Tone control kit | | 5. 0. |


AMPLIFIER TYPE A2 for use on AC/DC 200-250v.

This amplifier employs the same fundamental circuit as the A1. It also gives first-class reproduction, and the kit itself is absolutely complete in every detail.

| | | |
|--------------------------------|--------|------------|
| Complete kit with instructions | | £2. 19. 6. |
| Instruction manual only | | 3. 0. |
| Tone control kit | | 5. 0. |

RADIO TUNING UNIT TYPE RF1.

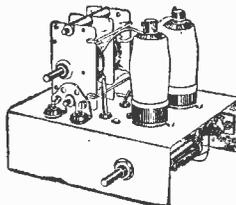A complete Medium Wave Radio Tuning unit for use with the A1, or any other A.C. only amplifier. A "straight" T.R.F. circuit is employed using two high-gain pentodes, and the reproduction is excellent. The high sensitivity means it may be used in areas of moderate signal strength from the transmitter to the receiver. Kit absolutely complete.



| | | |
|--------------------------------|--------|---------|
| Complete kit with instructions | | £2 5. 0 |
| Instruction manual only | | 2. 0. |

The BURGROYNE SOLDER GUN

SAVE TIME ON SOLDERING!

Just press the button, count seven, and solder and the bit will remain at soldering heat until you release the pressure, when it cools off instantly. No waiting to warm up or cool down—No element to burn out—No mica to crack or splinter—No risk of shock. £10,000 was spent on the design of this famous tool originally!

Few tools possess so many advantages as the "Seven-Second" Solder Gun; and certainly no engineer can consider himself up to date without one. For A.C. mains, 200-250v.

79/6

Post Free

Two Years Guarantee

"IVALEK" CRYSTAL SET

A radio set in the palm of your hand! A beautifully made receiver, that looks good and IS GOOD. The receiver is constructed on an aluminium chassis and the circuit used, although simple, is highly efficient. All that is required is an aerial and earth, and a pair of high-resistance headphones for good trouble-free reception. 17/6

Post and packing 9d. Standard Model, without tuning dial 12/6, postage and packing 9d.

SEND for DETAILS of our HIRE-PURCHASE plan for

"VIEWMASTER" COMPONENTS

Start Building this magnificent Receiver for **£5 DOWN**

M-O-S MAIL ORDER SUPPLY CO., THE RADIO CENTRE
33 Tottenham Court Road, London, W.1. Museum G667

E.M.I.

SPOT FREQUENCY MARKER

*The most accurate
Frequency Checking Equipment
yet designed*

- Extended range from 1 M/c's to 200 M/c's.
- Ex-Works, the accuracy is within .01%, but provision is made for setting the crystal against a suitable frequency standard permitting accuracy to be permanently maintained within a few cycles.
- Variations in H.T. supply between 150/250 volts will not affect the output frequency.
- The crystal harmonics on 144-146 M/c Band is sufficiently powerful to facilitate receiver alignment.
- Enables accurate calibration of Signal Generators, V.F.O.'s and S.W. receivers.
- Price **£7.15.0** Nett.

Write for full details of this and the complete range of special E.M.I. equipment for the Amateur.

E.M.I. SALES & SERVICE LTD.

AMATEUR DIVISION,
HEAD OFFICE: HAYES, MIDDLESEX,
ENGLAND.

E.211

STUDY AT HOME

IN YOUR SPARE TIME

THE BENNETT COLLEGE

will set you on the right course for success

You make sure of planned progress in the career of your choice when you let the most progressive, most successful Correspondence College in the world coach you through the post. By friendly, individual training we equip you with the specialised knowledge you must have for a well-paid key position. Make the first move TO-DAY—post the coupon below.

ALL TEXT BOOKS ARE FREE!

to students of The Bennett College. We send as many volumes as the subject demands, and they become your personal property.



IS YOUR CAREER HERE?
IF NOT, WRITE FOR FREE ADVICE

- | | |
|-----------------|--------------------|
| Accountancy | Engineering |
| Blue Prints | Languages |
| Book-keeping | Mining |
| Chemistry | Secretaryship |
| Civil Service | Shorthand (Pitman) |
| Commercial Art | Wireless |
| Draughtsmanship | Works Managers |

To Dept. 104, THE BENNETT COLLEGE LTD., SHEFFIELD.

Please send me (free of charge)

Particulars of } Cross out line which does not apply

Your private advice about }
PLEASE WRITE IN BLOCK LETTERS

Name

Address

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

CRYSTAL SETS

- Blueprints, 1s. each.
1937 Crystal Receiver .. PW71*
The "Junior" Crystal
Set PW94*

STRAIGHT SETS

Battery Operated

- One-Valve : Blueprints, 2s. each.
The "Pyramid" One-
valver (HF Pen) .. PW93*
Two-valve : Blueprints, 2s.
The Signet Two (D &
L F) PW76*

- Three-valve : Blueprints, 2s. each.
Summit Three (HF Pen,
D, Pen) PW37*

- The "Rapide" Straight
3 (D, 2 LF (RC &
Trans)) PW82*

- F. J. Camm's "Sprite"
Three (HF, Pen, D,
Tet) PW87*

- Four-valve : Blueprints, 2s. each.
Fury Four Super (SG,
SG, D, Pen) PW34C*

Mains Operated

- Two-valve : Blueprints, 2s. each.
Selectone A.C. Radio-
gram Two (D, Pow) PW19*

- Three-valve : Blueprints, 2s. each.
Double - Diode - Triode
Three (HF Pen, DDT,
Pen) PW23*

- Four-valve : Blueprints, 2s. each.
A.C. Fury Four (SG, SG,
D, Pen) PW20*
A.C. Hall-Mark (HF
Pen, D, Push-Pull) .. PW45*

SUPERHETS

- Battery Sets : Blueprints, 2s. each.
F. J. Camm's 2-valve
Superhet PW52*

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprint, 2s.
Simple S.W. One-valver PW88*

- Two-valve : Blueprints, 2s. each.
Midget Short-wave Two
(D, Pen) PW38A*

- Three-valve : Blueprints, 2s. each.
Experimenter's Short-
wave Three (SG, D,
Pow) PW30A*

- The Prefect 3 (D, 2 LF
(RC and Trans)) .. PW63*

- The Band-spread S.W.
Three (HF Pen, D
(Pen), Pen) PW68*

PORTABLES

- Four-valve : Blueprint, 2s.
"Imp" Portable 4 (D,
LF, LF, Pen) PW86*

MISCELLANEOUS

- Blueprint, 2s.
S.W. Converter-Adapter
(1 valve) PW48A*

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

- One-valve : Blueprint, 2s.
B.B.C. Special One-
valver AW387*

- Two-valve : Blueprints, 2s. each.
A modern Two-valver .. WM409*

Mains Operated

- Two-valve : Blueprints, 2s. each.
Consoelectric Two (D,
Pen), A.C. AW403

SPECIAL NOTICE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.
The index letters which precede the Blueprint Number indicate the periodical in which the description appears: Thus P.W. refers to PRACTICAL WIRELESS, A.W. to *Aerial Wireless*, W.M. to *Wireless Magazine*.
Send (preferably) a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

- One-valve : Blueprints, 2s. each.
S.W. One-valver for
America AW429*

- Two-valve : Blueprints, 2s. each.
Ultra-short Battery Two
(SG, det Pen) WM402*

- Four-valve : Blueprints, 3s. each.
A.W. Short-Wave World-
beater (HF Pen, D, RC,
Trans) AW436*

- Standard Four-valver
Short-waver (SG, D,
LF, P) WM383*

Mains Operated

- Four-valve : Blueprints, 3s.
Standard Four-valve A.C.
Short-waver (SG, D,
RC, Trans) WM391*

MISCELLANEOUS

- Enthusiast's Power Am-
plifier (10 Watts) (3/-) WM387*
Listener's 5-watt A.C.
Amplifier (3/-) .. WM392*
Harris Electrogram
battery amplifier (2/-) WM399*
De Luxe Concert A.C.
Electrogram (2/-) .. WM403*

HINTS COUPON

This coupon is available until May 7th, 1951, and must accompany all Practical Hints PRACTICAL WIRELESS, MAY 1951.

TRANSFORMERS (All tested 2,000 volts to earth and between windings.)
 RE1/80, 80 mA (chassis drop through), 210/230/250 input. 250-0-250.
 4 volts at 4 amps, 5 volts at 2 amps, 6.5 volts at 4 amps. Screened Primary.
 RE2/80, 80 mA. (Shrouded drop through) 210/230/250 input. 350-0-350. 6.3
 volts at 5 amps, 6 volts at 2 amps.
 RE1/120, 120 mA. (Fully shrouded), 200/230/250 volts input. 250-0-250.
 6.3 volts at 7 amps, 5 volts at 3 amps.
 RE2/120, 120 mA. (Fully shrouded), 200/230/250 volts input. 350-0-350.
 6.3 volts at 5 amps, C.T., 5 volts at 5 amps.
 RE1/EHT. Primary 200/210/220/230/240/250 volts. 2.5 kV. at 4 mA. 4 volts
 at 1.5 amps, 4 volts at 2 amps. C.T. (Tested fit 10,000 volts to earth and
 between windings.)
 RE1/80, 21.9; RE2/80, 22.6; RE1/120, 29.6; RE2/120, 33.6; RE/EHT 37.6

| NEW VALVES BOXED | | ELECTROLYTIC CONDENSERS | |
|------------------|-----------------|-------------------------|------------------|
| part no. | valve | mfid. volt. each | mfid. volt. each |
| REN 46 | 8/4 6LGT | 8 - 500 | 2.0 25 - 50 |
| 6K70T/O | 7/8 6F50 nboxed | 8 - 450 | 2/6 8/16 - 450 |
| 6K70 | 6/8 6S67GT | 16 - 500 | 3/8 8/8 - 450 |
| 6V60T/O | 8/8 YU111G | 16 - 350 | 2/8 16/16 - 350 |
| 6Z6GT | 7/6 12A6GT | 32 - 500 | 6/0 16/16 - 450 |
| 6P50 | 7/8 6A5 (6AK5) | | |

Valves, Coils, Condensers, Speakers, Transformers, Meters, Batteries, Chokes, Wavechanging Switches, etc., etc. "Cheapest in London." Prompt and Personal Service. Write, Call or "Phone. Please send S.A.E. for lists.

"R.E.Co.," TELE-RADIO HOUSE,
 42, GODGE STREET, LONDON, W.1. LAN 2335

RADIO UNLIMITED, ELM ROAD, LONDON, E.17

| | | | |
|-------|-----------|----------|-----|
| 6V6 | 7/6 524 | 6/6 174 | 7/6 |
| 6F6 | 7/6 5U4 | 9/0 154 | 7/6 |
| 6N7 | 6/6 6E6 | 5/6 185 | 7/6 |
| 6V7 | 6/6 6E6C3 | 7/6 105 | 7/6 |
| 6B8 | 6/6 6K32 | 6/6 617 | 7/6 |
| 6SG7 | 6/6 6R8 | 9/0 9P21 | 6/6 |
| ECH35 | 9/0 6K8 | 9/0 6S17 | 9/0 |
| 2526 | 10 - 6SN7 | 7/6 9D2 | 3/8 |
| 6J5 | 4/3 6K5 | | |

SPECIAL THIS MONTH, 6L57G, 3 for 13/6.
 In addition to the Surplus types listed we have large range of B.T.A. types in stock. Quotation by return, or order by C.O.D.
ALUMINIUM CHASSIS (screened).—Ideal for pre-amp. Complete with two i.n.c. holders, 8 resistors, and condensers. Brand new condition. 4/8. post free.

YOUR GREAT CHANCE!

New, boxed components by leading manufacturer.
3-WAVEBAND SUPERHET COILS (AE and OSC). 8/6 pair
MIDGET 465 Kcs I.F. TRANS. (1in. x 2 1/2in.). 9/9 pair.

Experimenters! Build the MATCHBOX RADIO SET
 With the aid of our full instructions you can build a complete radio set in a matchbox, using parts purchased from your radio dealer.
 Tuning arrangements include a medium-wave inductor with station selector switch, and a long-wave coil for the B.B.C. Light Programme on 1,500 metres.
 Demodulation is achieved by the use of a non-linear impedance unit of a new type, giving loud, clear reception.
 This receiver works off a short indoor aerial in many districts, and being powered entirely by the incoming signal requires no batteries.
 Full step-by-step instructions, working drawings, and theoretical wiring diagram.
 PRICE 3/-. POST FREE.
JOHN O'BRIEN (W),
 137, COTHAM BROW, BRISTOL, 6.
 MAIL ORDER ONLY.

The Electronic Musical Instrument Manual
 By Alan Douglas
 A useful guide to the theory and design of these instruments. With its numerous circuit diagrams and other illustrations it will greatly assist all concerned with this branch of electronics. 106 illustrations, 18/- net.
PETMAN, Parker Street, Kingsway, London, W.C.2.

You're SURE to get it at STERN'S ESTABLISHED 25 YEARS

A 4 Station A.C. Mains "Pre-Set" Receiver. We now have available complete Assembly Instructions for the construction of a midget "Pre-Set" Superhet Receiver, showing also Wiring Diagram, Component Layout, and point-to-point connections. This Set will select 4 Stations, 3 on Medium Waveband and 1 on Long Wave by the turn of a Rotary Switch, no tuning being necessary. It is of midget size, and is simple to assemble, the completed chassis being 8 1/2 in. x 4 1/2 in. x 7 in. high, and can be completely built, including Valves and Moving Coil Speaker for £5/19/6. Price of Circuit and instructions, 1/6 (plus 3d. post).

A Midget T.R.F. Battery Portable "Personal" Kit. A complete Kit of Parts to build a midget 4-valve All-dry Battery Personal Set. Consists of Regenerative T.R.F. Circuit employing Flat Tuned Frame Aerial, with Denco Iron Dust Cored Coil, thereby ensuring maximum gain for Single Tuned Stage covering Medium Waveband and Valve Line-up: IT4 (R.F. Ampl.), IT4 (Detector), 1S5 (1st A.F.), and 3S1 (output). Includes latest Rola 3in. Moving Coil Speaker, and a Chassis already drilled and shaped. A Kit is designed for only 7 mA ensures long battery life. The Kit is designed for a cabinet, minimum size 6 1/2 in. x 4 1/2 in. x 3 in. Detailed Building Instructions, with Practical Layout and Circuit included with Kit make assembly easy. Price for Complete Kit, £3/18/9 (plus 18/7 P.T.). Suitable unpainted Cabinet, 6 1/2 in. x 4 1/2 in. x 3 in., 12/9. Ever Ready B14 Battery, 10.8. Building Instructions, Circuit, etc., supplied separately, 1/-.

For Under £6! A Complete Kit of Parts, including drilled chassis and valves to build a 6-8 watt P-Pull amplifier for A.C. Mains. Is suitable for use with magnetic, crystal or lightweight pick-up and incorporates Tone controls. Theoretical and practical diagrams supplied. Price of complete kit, £5/18/9, or completely assembled, ready for use, £7/10/0. Circuit and component lists, 9d.

Mains or Battery Personal Kit. A Kit of parts to build our new Midget 4-Valve Superhet "Personal" Set, covering Medium and Long Wave-bands and designed for Mains or

Battery operation is now available. This 2-waveband superhet receiver is designed to operate on A.C. mains 200-240 v. or by an "All-Dry" battery, either means being selected by the turn of a rotary switch. It is so designed that the mains section, size 4 1/2 in. x 3 1/2 in. x 1 1/2 in. is supplied as a separate kit (which may be added at any time). The kit can therefore be supplied either as an "All-Dry" Battery Personal Set, or by incorporating the mains section as a Midget receiver for combined Battery, Mains operation. The circuit incorporates delayed A.V.C. and pre-selective audio feedback. A Rola 4in. P.M. Speaker with a generous sized output transformer ensures excellent quality reproduction. Two ready wound frame-aerials and a drilled midget chassis are included. The overall size of chassis when completely wired is 8 1/2 in. x 4 1/2 in. x 2 1/2 in. (valve line-up IR5 (freq. ch.), IT4 (R.F. amp.), 1S5 (diode det. and audio amp.), and 3S1 (output tet.). The set is easily built from the very detailed building instructions supplied, which includes a practical Component Layout, with point-to-point wiring diagram, and a circuit diagram. Price of Complete Kit (less Mains Unit), including P.T., £6/18/9. Price of Mains Unit Kit, £11/7/6. A Walnut-finished Portable Cabinet to house this receiver is also available, Price 19/9. The complete assembly instructions above can also be supplied separately for 1/9.

A complete Kit of Parts to build a Miniature "All-Dry" Battery Eliminator, giving 69 volts H.T. (approx.) and 1.4 volts L.T. This Eliminator is suitable for use with any Superhet Personal battery set requiring H.T. and L.T. as above. It is housed in a light aluminium case, size 4 1/2 in. x 3 1/2 in. x 1 1/2 in., and can therefore be accommodated in most makes of personal receivers. Price of Complete Kit, including detailed assembly instructions and layout, £11/7/6.

The Midget A.C. Mains 3-Valve Receiver circuit, as published in the "Wireless World." We can supply all the components to build this set, which covers Medium and Long Waves, for £4/10/0 (including complete assembly instructions). A reprint of complete assembly instructions can be supplied separately for 9d. (including postage).

* Send 6d. P.O. for our NEW STOCK LIST, showing many KITS OF PARTS for Sets and Battery Chargers and "hundreds" of Wireless Components. When ordering please cover postage and packing.

STERN RADIO LTD., 109 & 115, FLEET STREET, E.C.4. Telephone: CENTRAL 5814 & 2380