

MIDGET 12-WATT STATION

1/-


Vol. 29. No. 557
MARCH, 1953

EDITOR:
F.J. CAMM

PRACTICAL WIRELESS

AN H.F. STAGE

FOR THE

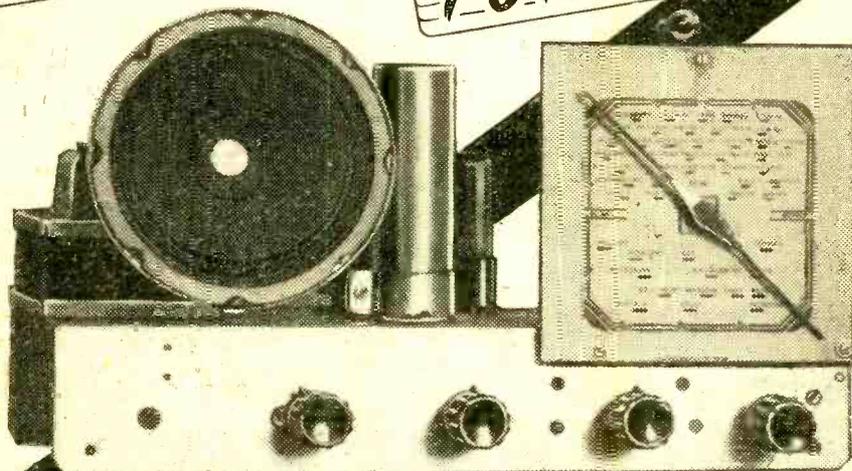

A.C. BAND-PASS 3

IN THIS ISSUE :

THE "MODERN" QUALITY
AMPLIFIER
ELECTRONIC V.T.V. METER
INCREASING THE OUTPUT


END-FED AERIALS
OUTDOOR RADIO
AUTO POLARITY INDICATOR
LONG-PLAYING RECORDS

Examples from the new range of TAYLOR INSTRUMENTS

Model 77A Multirange Universal Meter

20,000 o.p.v. D.C., 5,000 o.p.v. A.C. Five inch, easy-to-read scale with knife edge pointer. Instantaneous overload protection. Buzzer for continuity testing. Rugged black moulded case with carrying handle.

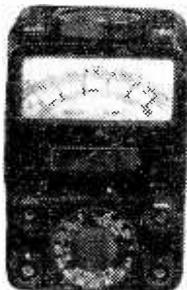Ranges: Volts D.C. 0-7.5-30-75-300-750-3,000. Volts A.C. 0-7.5-30-75-300-750. Milliamps. D.C. 0-15-1.5-15-150-1,500. Amperes. D.C. 0-15. Resistance 10 ohms-5 megohms in two ranges with self-contained battery.



Price **£15.0.0** Immediate delivery



Model 120A Taylor Junior

Multirange Universal Meter

1,900 ohms per volt A.C. and D.C. 2½ in. scale with knife-edge pointer, instantaneous overload protection. Rugged black moulded case with separate battery compartment. 19 ranges:

Volts. A.C. and D.C., 0-2,500.

Milliamps. D.C. and A.C., 0 to 500.

Resistance. 0-200,000 ohms in two Ranges. Complete with leads, prod., etc.

List Price **£9** Immediate delivery

★ Illustrated instruments are available on Hire Purchase

These instruments are available through your usual supplier. For full details of the complete range of Taylor instruments please write for our new 16-page catalogue.


TAYLOR ELECTRICAL INSTRUMENTS LIMITED

MONTROSE AVENUE, SLOUGH, BUCKS.

Telephone: SLOUGH 21381

Armstrong

THE Chassis People

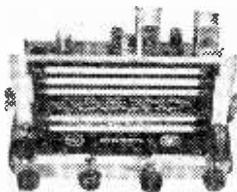

The prestige of Armstrong chassis is firmly based upon many years of constant endeavour to produce reliable and efficient receivers at an economical price. Our present range of chassis will even further advance the already high reputation enjoyed by our receivers.

We are delighted to give demonstrations in our showroom and our illustrated catalogue will be gladly sent on request.

MODEL EXP 125/3. 14-VALVE ALL-WAVE RADIOGRAM CHASSIS. 5 wave bands covering from 10.9 to 550 m. and 800 to 2,000 m. R.F. pre-amplifier. Two I.F. stages with variable selectivity. Bass and treble controls. 15-watt push-pull output. For A.C. mains. **£36.15.0**, plus P.T.

MODEL RF 104. 10-VALVE ALL-WAVE RADIO CHASSIS. 4 wave bands. R.F. pre-amplifier. Two I.F. stages with variable selectivity. 10-watt push-pull output. For A.C. mains. **£24**, plus P.T.

MODEL EXP 73. 8-STAGE ALL-WAVE RADIO CHASSIS. 3 wave bands. Variable selectivity. Fly-wheel tuning. 8-watt push-pull output with negative feedback. For A.C. mains. **£17.15.0**, plus P.T.

ARMSTRONG WIRELESS & TELEVISION CO., LTD.
Warlters Road, Holloway, London, N.7. Tel.: NORth 3213

Seventh Edition

Radio Upkeep and Repairs

By Alfred T. Witts, A.M.I.E.E. This well-known handbook gives detailed information on the location and correction of faults in the radio receiver. Originally written to help the ordinary owner, it has become more and more the stand-by of the budding service engineer and all who are professionally or otherwise concerned with this type of work. 12/6 net.

"This book is commended. The methods advocated require a minimum of equipment."

—ELECTRICAL TIMES.

"Full of useful suggestions which will be appreciated

by the service engineer in addition to the amateur."

—ELECTRONIC ENGINEERING

"A helpful introduction to practical radio servicing"

—PRACTICAL WIRELESS.

From all booksellers. Published by


PITMAN, Parker St., Kingsway, London, W.C.2

First Class



FULLY REDESIGNED COIL TURRETS

Steel Frame — Rotary Turret
 — Silver Plated Contacts —
 Polystyrene Insulation — Six
 Colour Dial — Flywheel and
 Cord Drive — Fully Assembled
 and Factory Aligned —
 150 Kc/s. to 30 Mc/s. in Five ranges.

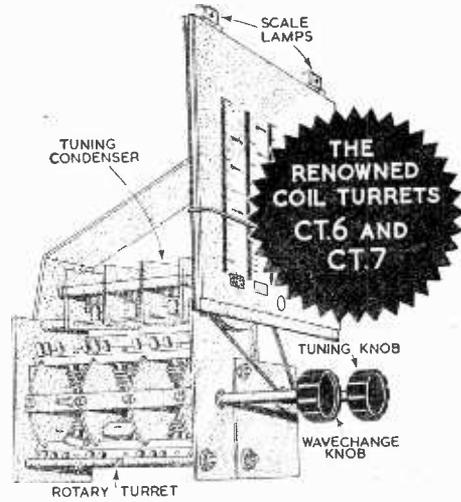

CT.6 — Mixer and Oscillator — £7- 4-4 inc. P. T.
 CT.7 — R.F., Mixer and Osc. — £9-15-0 inc. P. T.



Full application data and technical information appears in
 TECHNICAL BULLETIN DTB.2 price 1/6d.

DENCO (CLACTON) LIMITED, 357/9 Old Road, Clacton-on-Sea, Essex.

faithful reproduction

from 50 c/s to 10 Kc/s at 7½ in/sec using



High-quality recorder reproducers demand high-quality tape to produce results that will satisfy the discriminating listener.

"SCOTCH BOY" MAGNETIC TAPE HAS:

- High, uniform sensitivity
- High fidelity at low speeds
- High signal/noise ratio
- Medium coercivity, easy erasure
- Low distortion and transfer
- Special cellulose acetate base giving strength and durability.

in 1200', 600', 300' reels and other sizes.

Further information obtainable on request.

MINNESOTA MINING & MANUFACTURING Co: Ltd
 167 Strand, London, W.C.2. Telephone: TEMple Bar 6363

The solder for all
**HOME TELEVISION
 CONSTRUCTOR SETS**

Designers of television constructor sets know that the efficiency of their equipment depends on the solder used by the constructor—that's why they recommend Ersin Multicore for trouble-free, waste-free soldering. Ersin Multicore, the only solder containing three cores of extra-active, non-corrosive Ersin Flux, is obtainable from all leading radio shops. Ask for Cat Ref. C.16018, 18 S.W.G. 60 40 High Tin Television and Radio Alloy. The size 1 Carton contains 47 feet of solder, costs 5/-.



Ersin Multicore Solder

In case of difficulty in obtaining supplies, please write to :

MULTICORE SOLDERS LTD. MULTICORE WORKS, MAYLANDS AVENUE, HEMEL HEMPSTEAD, HERTS. • Boxmoor 3636

For the discriminating listener—

The **BURGOYNE** 3 SPEED RECORD PLAYER



Outstanding in appearance, this high fidelity unit incorporates the famous BSR type GU4 gramophone unit with lightweight crystal head. Special features of this unit are the automatic stop operating on all types of records, 33 $\frac{1}{3}$ -45-78 r.p.m., speeds by switching and the high fidelity pick-up. The cabinet is of a beautifully polished walnut streamlined design.

LIST PRICE*
13 gns.

or H.P. Terms 91/- deposit
and 12 monthly payments
of 18/6. For use on all

voltages 100-250v. A.C. 50/60 c/s. FULLY GUARANTEED. Also available without cabinet as the GU4/TOH motor unit complete with pick-up, £9.19.11. H.P. terms 66/11 deposit and 12 monthly payments of 14/5.



MAIL ORDER SUPPLY CO.

33, Tottenham Court Road, W.1.

The Radio Centre

MUSEum 6667

STILL GOING STRONG The **BURGOYNE** TAPE RECORDER

● Delivers in rotation due to the huge demand! ● Complete ready to use in handsome walnut table cabinet. ● 64 minutes playing time from 7in. reel. ● Fast forward and rewind. ● Instantaneous braking. ● Frequency response 30-9,000 c/s, at 7 $\frac{1}{2}$ in. per second. ● Three heavy duty motors. ● Output 4 watts. ● Dimensions 21in. x 13in. x 13in.

32 gns.

complete with Ronette Xtal Microphone.

Carriage and packing 21/-.
H.P. Terms £11.4.0 deposit and 12
monthly payments of 42/9.

**SHORTAGE OF
RADIO & T/V
ENGINEERS**

The demand of Industry for our trained students is still greater than we can supply—and is likely to remain so for many years.

We offer

FULL TIME DAY COURSE

1 year course in Principles and Practice of Radio and Television.

Next course commences 14th April, 1953.

Write for FREE BROCHURES giving details of the above, of our 3-year course, and of others.

E.M.I. INSTITUTES—the only college which is part of a great industry.

E.M.I. INSTITUTES (Dept. 32A)

10, PEMBRIDGE SQUARE,
LONDON, W.2.
Tel: BAYwater 5131/2.

Associated with
"H.M.V."
**MARCONIPHONE
COLUMBIA
ETC.**

1A.1b

ARMY CARBON MICROPHONES complete with switch, 5/9. Matched transformer, 4/6.

A.C./D.C. T.R.F. kit L. and M. band, complete with beautiful polished wood cabinet and 5in. speaker, £6/15/-.

TR1196 CIRCUIT AND CONVERSION DATA, 1/3. 1147A or B, 1/6. Any CRT Unit to Oscilloscope 2/9.

GERMANIUM DIODES, 3/9.

P.M. SPEAKERS, Goodmans 8in., 20/- 10in., 32/6. 5in. 14/6. 6in. 16/6. 10in. Plessey, 29/6.

SELENIUM RECTIFIERS. F.W. 6 or 12v. 4 A., 26/-; 6 A., 30/-; 3 A., 14/6; 1 A., 10/6; 250v. 100 mA. H. W., 9/-; 24v. 2A., 30/-.

TRANSFORMERS, 200-240 volts, tapped 3-4-5-6-8-9-10-12-15-18-20-24 and 30 volts at 2 A., 21/6. One year guarantee.

TYPE 18 TRANS. CHASSIS, clean condition, partly stripped, 8/6 to clear.

TRANSFORMER, SHROUDED. Input 250/230, Output 50-25v., 2 A., 16/6.

PRACTICE MORSE KEY AND BUZZER SETS, 7/6.

VCR97 C.R. TUBES, picture tested, new and crated. 45/-; base, 3/6.

EX W.D. PHONES, Low Resistance, 8/6.

TYPE IN34 GERMANIUM CRYSTAL DIODES, 5/6.

MINIATURE VALVES. New. CK512AX, 9/-; 9001, 9002, 9003, 7/6; 6AG5, 10/6; 1S4, 1S5, 1T4, 1R5, 10/6; 6AL5, 8/6; 12AT7, 6AM6, 6AQ5, 6BR7, DH77, 6AT6, EY51, 12/6.

NEW VALVES. 35Z4, 35L6, 25Z4, 25L6, U281, VP48, U50, 5Y3GT, 6K7GT, 6V6GT, 11/6; 6K8GT, 11Z26, 80, 40, 12/6.

NEW 2 VOLT II A.H. EXIDE ACCUMULATORS, 7/-.

R.1224 BATTERY SUPERHET RECEIVER, 1-9 Mc/s, £6/10/-.

One of the best sets used by the R.A.F.

MULTIMETER KIT, 2 $\frac{1}{2}$ " M/c calibrated meter. D.C. Volts 0-3-30-150-300 and 600, mA. 0-6-60. Black ebonite case. Also reads 0-5,000 ohms with 1 $\frac{1}{2}$ v. battery, 24/6.

W.D. TRANSFORMERS. Input 200/250 v., Output 0-460 v. 200 mA. 6.3 v. 5 a., 22/6.

ALL POST PAID

THE RADIO & ELECTRICAL MART

253b, Portobello Road, London W.11 'Phone: Park 6023

HENRY'S

INDICATOR UNIT TYPE 192A. This unit contains VCR517 Cathode Ray 6in. Tube, complete with Mu-metal screen, 3 EF50 4 S1P61 and 1 5U4G valves, 3 wire-wound volume controls and quantity of Resistors and Condensers. Suitable either for basis of Television (full picture guaranteed) or Oscilloscope. Offered BRAND NEW (less relay) in original packing case at 79/6d. Plus 7/6 carr. "W.W." Circuit supplied Free.

2 Gang .0005 Condensers Midget. 5/-	
2 " .0005 " " with Trimmers. 6/6.	
2 " .0005 " " with 4-way Push-Button. 8/6.	

WEARITE MAINS TRANS. Input 110 250v. output. 325-0-325. 80 m.a. 6 v. 2.5 amp., 5 v. 2 amp. £1 1/-.

PLESSEY MIDGET TYPE. 200 250 output. 230-0-230 50 m.a. 6 v. 2.6 amp. 12/6. P.P. 1/-.

I.F.T.'S. Wearite 501 and 502, 465 kc's. 10 - pair, P.P. 1/-.
.. Plessey 465 kc's Permeability. 8/6 pair, P.P. 1/-.

EXCEPTIONAL VALVE OFFER

Ten EF50 Brand New (Ex-Units)...	55/-	Set
6K8G, 6K7G, 6Q7G, 5Z4G, 6V6G (or KT61)	42/6	..
1H5, 1S5, 1T4, 1S4 or (3S1 or 3V4)	32/6	..
TP25, HL23 DD, VP21, PEN25 (or QP25)	27/6	..
6K8G, 6K7G, 6Q7G, 25A6G, 25Z5 or 25Z6G	42/6	..
12K6GT, 12K7GT, 12S9GT, 3Z4GT, 35L6GT or 50L6GT	42/6	..
12S4GT, 12SK7GT, 12S9GT, 35Z4GT, 35L6GT or 50L6GT	42/6	..

Complete set of specified valves for "P.W." Personal Rec. 5A6AM, 2-6AK5, 1 6J6, 1 6J4, 1 EA50, and 3BP1 C.R. Tube with base. £5 12/6.

PYE 45 Mc'S STRIP. Size 15in. x 8in. x 2in. Complete with 45 mc's Pye Strip, 2 valves, 10 EF50, EB34 and EA50, volume controls and hosts of Resistors and Condenser. Sound and vision can be incorporated on this chassis with minimum space. New construction. Modification data supplied. Price £5, carriage paid.

ELECTROLYTIC CONDENSERS

Midget Type metal tubular wire ends with sleeves.		Small standard metal case.
8 mfd. 450v. wkg. ...	2/6	32 x 32 mfd. 275v. wkg. ... 5/-
18 mfd. 450v. wkg. ...	3/6	32 x 32 mfd. 450v. wkg. ... 7/-
8 x 8 mfd. 450v. wkg. ...	4/-	16 x 8 mfd. 350v. wkg. ... 3/6
16 x 8 mfd. 450v. wkg. ...	5/-	60 x 40 mfd. 350v. wkg. ... 5/-
16 x 16 mfd. 450v. wkg. ...	5/-	B.I. 8 mfd. 500v. Block 2/-
25 mfd. x 25v. wkg., 50 mfd. x 12v., 12 mfd. 50v. wkg. ...	1/6	50 mfd. 50v. wkg. 2/-

CATHODE RAY TUBES :

VCR97. Guaranteed full picture, 40"- carr. 5/-.
VCR517. Guaranteed full picture, 40"- carr. 5/-.
3BP1. Suitable for scopes and Tel. 25"- carr. 3/-.
MU-METAL SCREEN for VCR97 or 517. 12/6d.

P.M. SPEAKERS (Inc. Tax)

Plessey 2 1/2in. with Trans. 15/-	Rola 10in. with Trans. 30/-
Celestian 5in. with Trans. 16/-	Goodman's 10in. with Trans. 30/-
Rola 5in. less Trans. ... 12/6	
Plessey 5in. less Trans. ... 12/6	Electrona 10in. with Trans. 25/-
Plessey 6 1/2" L/T ... 15/-	

Postage and packing 1/- extra.

SEND POSTAGE FOR NEW 1953 COMPREHENSIVE 28 PAGE CATALOGUE:

Open Mon.-Fri., 9-5.30. Sat. 6 p.m. Thurs. 1 p.m.

5, HARROW ROAD, PADDINGTON, LONDON, W.2. TEL. : PADDINGTON 1008/9, 0401.

HANNEY of BATH offers :

LANE Mark 3 Tape Decks, with 3 Collaro motors. £16 10/- plus 10/- carriage and packing. Constructors' envelope for the Lane Record-Playback Amplifier. 5/-.

EDDYSTONE 740 Receivers. Two only left at the old price of £38 15/-.

GRAM-MOTORS. B.S.R. single-speed MU15. 60/-; MU10. 2-speed. 78/7; GU4. 3-speed with Hi-Fi turnover crystal head. £10; Monarch 3-speed autochanger, with turnover crystal head £17/17/-; COLLARO 3RC/321 3-speed autochanger with 2 GP27 plug-in crystal heads. £17/18/5; Type 3RC/522, as 521 but plays 10in. and 12in. records intermixed. £20 8/4.

PICK-UPS. New ACOS GP30. 7/15; Acos GP20. 7/15 (std. or L.P. head), spare heads, 43/3; Collaro magnetic (std.), £2; Collaro GP29, turnover crystal. 80/8; Collaro orthodynamic with trans. 67/8; Goldring 1055, turnover magnetic for all speeds, all records. 7/15; Goldring Bantam (std.). 35/10; Rothermell U38 crystal (std.). 28/2.

DIALS. J.B. SL8. 27/6; J.B. SL5RV. 28/6; Osmor Type A. 24/6; Osmor cream escutcheon. 4/-.

THE MAGNAVIEW. LARGE SCREEN TV for the HOME CONSTRUCTOR, as described in the book issued by BRIMAR valves. Price list available from us, giving details of all components.

TELEKING Constructors' envelope. 6/-; Chassis kit. 70/-; Coil Kit. 54/3; TCC kit. £7/4/3; Allen Sc.312. 22/6; AT310. 30/-; OP117. 9/-; BT314. 15/-; Wide angle components below.

WIDE ANGLE VIEWMASTER. All the special TCC condensers in stock.

ALLEN wide angle components, LO308. 50/-; FO205. 21/-; DC300. 42/-; FC302. 35/-; GL16 and GL18. 10/- each.

STANDARD VIEWMASTER. We supply GENUINE parts only. Complete kit less valves and tube. £31. or in 7 easy stages, prices as per our list. Send 62/3 for Stage 1 now.

SUNDRIES. Osmor Q coilpacks, HO. 52/-; LM. 43/4; TRF. 43/4; Osmor Q coils. 4/- each; QCI chokes. 4/-; Weymouth H coils. 3/9; Wearite P coils. 3/-; Denco Maxi-Q coils. 3/11; Denco type C TRF coils. 8/- pr.; Astral TRF coils. 4/3 each; Polystyrene Varnish, genuine Distrene. 1/10 tube; 50 watt potted output trans. for 6L6, KT66, 6V6 or PX4 in P.P. 47/3; Taylor Montrose meters. 50/-; Valve Manuals, by Brimar, Osmor, and Mullard. 6d. stamp for our list covering Teleking, Viewmaster, Magnaview, Williamson Amplifier, P.W. 3-speed Autogram, Tape-Deck Amplifier Modern 1 and 2 Valver, Highspeed Fault Finder, Battery-Mains Attaché Case Portable, also General Components, chassis, etc.

L. F. HANNEY,

77, LOWER BRISTOL ROAD, BATH. Tel. 3811


DIRECT FROM THE MANUFACTURER

DULCI RADIO/RADIOGRAM CHASSIS

A/C 100-120 & 200-250 VOLTS

OUTSTANDING VALUE OF NEW PRODUCTION!

Fully Guaranteed

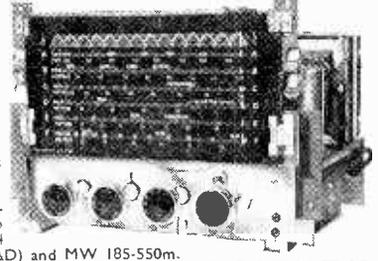

Model B. Six Wavebands. 11-115

metres continuous in 5 ranges (4 BANDSPREAD) and MW 185-550m. Six position Tone Switch (3 radio-3 Gram.). Price ... Tax Paid **£15/15/0**

Model B3. Three Wavebands. Long. Medium. Short. Gram. switching on W/Change switch. 3 position Tone. Price ... Tax Paid **£12/12/0**

Both chassis 11 1/2in. x 7in. x 8 1/2in. high. Latest type valves: 6BE6, 6BA6, 6AT5, 6BW6, 6X4. Flywheel tuning Negative Feedback over entire audio section. Engraved knobs.


BUILT TO HIGHEST PERFORMANCE STANDARD & SPECIFICATION

Cabinet Escutcheon for 9in. x 5in. dial for 4/9 extra. Chassis despatched under Money-Back Guarantee conditions on receipt of remittance. Further particulars from:


THE DULCI CO. LTD.,

99 VILLIERS ROAD, LONDON N.W.2
Tel. : Willeiden 7778

RADIO-GRAM CHASSIS

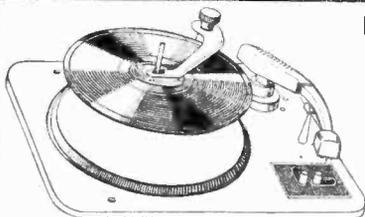

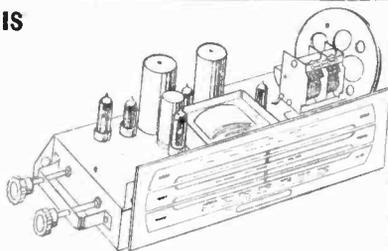
End Drive. Slightly coiled, but re-sprayed. 5 valve. superhet, latest pin type valves. Ext. speaker and gram. pick-up sockets. 4 watts A.F. output. Drive any low imp. P.M. speaker. Price £7-17-6. Carr. 4/6. Also brand new Front Drive models. 1953. Six wave-band £15-15-0. Three wave. £10-17-6.



RECORD-CHANGERS Brand new, but superficial foam damage. Completely overhauled and tested. Collaro. Takes eight 10in. or 12in. records. Single speed. Approximately half list price. Either crystal or magnetic heads can be supplied on request. £5-19-6. Carr. 4/8.

TRF KIT Ideal bedroom set. Complete wiring details and assembly instructions. 4 valve, all mains. Perfect reception on Long and Medium bands. Cabinet of plastic (brown or white) or wood (polished walnut). Lowest priced TRF available to-day. Complete kit £5-19-6. Can be supplied assembled ready for use. 20/- extra. Carr. 3/6.

SPEAKERS Brand new extension speakers. 5in. P.M. mounted on latest type baffle stand. polished, gold sprayed metal fret, 5 feet lead connected. 19/9. Or in totally enclosed cabinet type stand. 25/9. Post 1/9. Brand new 6in. P.M. speakers at 22/6, and 10in. at 27/6. Twin tone (bass and treble) reconditioned 6in. P.M. speakers, matched and mounted on a baffle board, 24/6 complete. Post 1/9. Miniature moving coil 'phone speakers, ideal personal extension speakers, or quality microphones. 2/9. Post 6d.

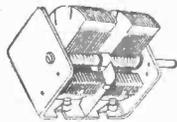


CONDENSERS Bargain offer of 0.005 mfd. two gang tuning condensers. Standard size (store soiled) and half size (brand new. Plessey). All at 2/9. Post 6d. Special offer of three for 7/-.

ELECTROLYTICS.—Daly, unused. 30-30 mfd., 450 vdc. 3/9; 32 mfd., 276 vdc. single tag. 2/9. 8 mfd., 350 vdc. bolt fixing. 1/6. Solar bias condensers. 50 mfd., 12 vdc. 3/4, each, or 2/9 a dozen.

VALVE CLEARANCE. SURPLUS STOCKS

11/9	10/9	8/9	6/9	5/9	3/9
PL81	5U4	1S4	PP225	1A5	4D1
PL82	5Z4	1S5	77	9D2	AR6
PL83	6V6	1R5	EB91	15D2	VP133
PY80	EF80	1T4	ARF13	SP2	CV6
PY82	20D1	EF91	EF92	UY11	955
ECL80	35Z4	10F1	RKR72	UP41	8001
GT1C	10P13	6F15	KTW61	OZ4A	1233A
20F2	X65	EL91	7B6	1T11	LP2

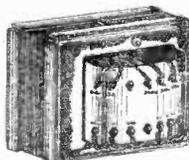TRANSFORMERS Mains (salvage) transformers, 260-0-260, 6.3 v, 3 A, 6.3 v, 1.5 A. Tapped 250, 210, 110 v. All tested and guaranteed for three months. Price reduced to 9/9. Post 2/-.



Also O.P. transformers, matching all normal O.P. valves to 2-5 ohm speech coil. Clearance at 2/9. Post 9d.

C.W.O.
OR
C.O.D.

DUKE & CO., 621, ROMFORD ROAD, LONDON, E.12. GRA. 6677

STAMP FOR CATALOGUE.
MONEY BACK GUARANTEE.

Have You Seen the
CONSTRUCTORS ENVELOPE
Containing Comprehensive Instructions
For Building the
**LANE RECORD-PLAYBACK
AMPLIFIER** (5/-)

THE
LANE
RECORD/
PLAYBACK
AMPLIFIER KIT


This high-grade kit incorporating modern miniature valves, punched and drilled chassis, ready assembled and screened switch and detailed theoretical and practical blueprints is supplied complete in every detail. No surplus items included. All components are of well-known makes and fully guaranteed.

Price £13.00.

Amplifier ready built and tested, £15.10.0.

**THE LANE
TAPE TABLE**

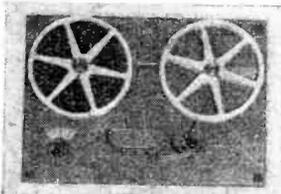Three motors. Fast forward and reverse rewind. High fidelity twin track heads. Positive braking. £16.10.0. A combination of these two items provides tape recording in its most perfect form.



From your local dealer—in case of difficulty write to:

VERDIK SALES LTD
17 SHAFTESBURY AVENUE, LONDON, W.1

Phone: Gerrard 8266

THE FAMOUS BENNETT COLLEGE

can help your career through personal postal tuition

in any of these subjects:

- Accountancy Exams. ★ Aircraft Eng. & Radio ★ Architecture ★ Auditing ★ Book-keeping ★ Building ★ Carpentry ★ Chemistry ★ Civil Service ★ Commercial Art ★ Commercial Arithmetic ★ Company Law ★ Costing ★ Diesel Engines ★ Draughtsmanship ★ Electric Wiring ★ Engineering (Civil; Electrical; Mechanical; Motor; Steam; Structural) ★ Jigs, Tools & Fixtures ★ Journalism ★ Languages ★ Mathematics ★ Mining ★ Modern Business Methods ★ Plumbing ★ Police ★ Press Tool Work ★ Quantity Surveying ★ Radio ★ Salesmanship ★ Secretarial Exams. ★ Shorthand ★ Surveying ★ Telecommunications ★ Television ★ Textiles ★ Works Management ★ Workshop Practice

and GENERAL CERTIFICATE OF EDUCATION

SUCCESS WILL BE YOURS

As a Bennett College Student your own Personal Tutor will coach you until you qualify, at your pace, with no time wasted. You will learn quickly, easily.

SEND TODAY FOR A FREE PROSPECTUS

TO THE BENNETT COLLEGE, DEPT. C. 104, SHEFFIELD.

Please send me your prospectus on..... (Subject).....

NAME

ADDRESS

..... AGE (IF UNDER 21).....

PLEASE WRITE IN BLOCK LETTERS.

CLYDESDALE

Bargains in Ex-Service Radio and Electronic Equipment

THE R1155 AS A COMMUNICATIONS RECEIVER

with 9 valves for 200-250 V. A.C. Mains. Comprises RECEIVER UNIT R1155 with: 5 switched bands 18-7.5 Mc s-17.43 metres, 7.5-3 Mc s-10-100 metres, 1.570-3.0 kc s-200-360 metres, 500-200 kc s-500-1,500 metres, 230-75 kc s-1,500-3,000 metres, 7 valves - VR9 (X55), 2 VR100 (KTWid), 2 V1101 (H53), V1103 (V53) ME, D.F. valves left out. Simple controls. Slow-motion 2-speed tuning, manual volume control. Wave-change switch. Also optional B.P.O., A.V.C., Magic Eye tuning indicator. In black metal case 16 1/2 x 9 x 2 1/2. Plus

COMBINED OUTPUT/POWER PACK
With 2 valves, pentode output and rectifier, 8-in. speaker, mains and output transformers, tone control, on/off switch. In black crackle metal case, 15 1/2 x 9 x 9 1/2

Ask for No. P.F.9A. **£18/10/0** Carriage Paid

A few only: R1155-N Model. Range: 18-1.5 mc s., 1500-600 500-230 kc s.

Ask for No. P.H.181 **£18/18/0** Carriage Paid
Or with combined Output/Power Pack at £22.19.6.

SPECIAL OFFER

R1155, R1155A RECEIVER UNITS

Used, fully reconditioned and tested (complete, less power pack), limited quantity only.

Ask for No. P.H.833 **£7.19.6** Each Carriage Paid

SPECIAL OFFERS

VALVE HOLDERS, TOP GRADE

E67 International Octal. Ceramic 1/- each. post 1/4.
H329 International Octal Moulded 9d. each, post 1/4.
E63 B4C (EF50) Loctal. Ceramic 1/- each. post 1/4.
H290 BTG (GAMS) Noval. Moulded 9d. each. post 1/4.
H37 B9A (12AU7) Noval. Moulded 9d. each. post 1/4.
Dozen lots, Ceramic 10 6 doz. Moulded 7 6 doz.

192 page CATALOGUE, NEW LIST No. 817 now in the press. Available when ready, price 1 6. Price credited on first purchase of 10/- or over.

ELECTROLYTIC CONDENSER

32µF capacity 450 V.D.C. wkg. Aluminium cased, tubular with waxed cardboard insulating cover. Dim.: 4 1/2 in. long, 2 in. dia.
Ask for No. P.H.452 **3/-** Each Post 6d.

SPECIAL CONDENSER OFFER

Comprising 3 (H352), 32µF EI. Condensers with mounting plates in original carton.
Ask for No. P.H.352 **7/6** Each Post 6d.

FOR INEXPENSIVE TELEVISION

IF/AF AMPLIFIER UNIT R.1355

The popular TV Sound and or Vision Unit, 5 i.f. stages, 19 valves 8 VR65s (SP61), 5U4G, YU120A, etc., etc. In metal case 16 x 8 1/2 x 7 1/2 in. Used, good condition. In Original Case **47/6** Carriage Paid
Ask for No. P.E.770
2nd Grade in Transit Case **42/6** Carriage Paid
3rd Grade, loose stored **35/-** Carriage Paid
Circuit of R1355 available at 1/3.

5 CUP CATHODE RAY TUBE

Ask for No. P.H.529 **35/-** Post Paid

INDICATOR UNIT TYPE 62 in Maker's original case

Ask for No. P.H.526 **£5/9/6** Carriage Paid

Also available, used, good condition.

Ask for No. P.E.774 **79/6** Carriage Paid

INDICATOR UNIT TYPE 62A Used, good condition.

Ask for No. P.H.933 **£7/19/6** Carriage Paid

INDICATOR UNIT TYPE 61I Used, good condition.

Ask for No. P.E.777 **£4/9/6** Carriage Paid

TRANSFORMERS

E.H.T. 55/-, 57/6, 59 6 or 65/- each. Mains (Morley), 55 -, (Argus), 69.6 each.

Order direct from:

CLYDESDALE SUPPLY CO., LTD.

2 Bridge Street, Glasgow, C.5.

Visit our Branches in Scotland, England and N. Ireland

Phone: SOUTH 2706/9

R O M

RIGHT FIRST TIME!

Trial and error is a costly and often disappointing business. For too long the radio amateur has had such methods forced upon him by the high cost of test instruments. The RADIO MAIL RES/CAP. BRIDGE has changed all that. For 31/6 he now has at his command an instrument to check each component before use, and ensure 100% results.

THE PRICE OF 31/6 COVERS THE COMPLETE KIT FOR THIS SELF-CONTAINED INSTRUMENT

5 Megohms—50,000 ohms 50 mfd.—.2 mfd.
100,000 ohms—1,000 ohms 1 mfd.—.01 mfd.
1,000 ohms—10 ohms .01 mfd.—.0005 mfd.

NO CALIBRATING

The panel bears six separate scales, one for each range, ready calibrated in ohms and mfd's, for direct reading. Each range is fully variable, covering all intermediate values.


New components, specially selected for accuracy. Instructions and diagrams for easy assembly. Prompt delivery. Cash with order or C.O.D.

RADIO MAIL, 4, RALEIGH STREET, NOTTINGHAM

Stamp with all enquiries, please.

BUILD THIS AMAZING RADIO POWERFUL! PERSONAL! PORTABLE!

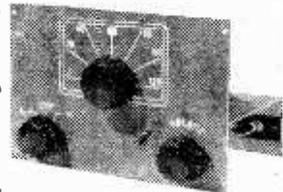- Long and Medium Waves.
- Selective Tuning.
- Acorn Low Drain Valve.
- Loud Clear Tone.
- Long Range.
- Only short Aerial Needed.
- No Earth Necessary.
- Easy to Assemble.



FOR **25/-** Post Free

This neatly engineered little set was designed to give you a real personal, portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office or just anywhere. This is not a weak crystal set, but a powerful valve set that will give good local and long-distance reception.

Send 2/- for Layout, Wiring Diagram and Component Price List. This will be refunded on Orders over £1. Mail Order only.

R.C.S. PRODUCTS

DEPT. A. 11, OLIVER ROAD, LONDON, E.17.

miniature in size... mighty in performance



Little wonder that OSMOR "Q" RANGE COILS are the "big noise." No imitations regardless of price, can compare with them for super selectivity and sensitivity. And you don't just have to take our word for it—the watertight guarantee makes your satisfaction certain! Consider these points of superiority:—

- ★ Only 1in. high.
 - ★ Variable iron dust cores.
 - ★ Low loss Polystyrene formers.
 - ★ Packed in damp-proof containers.
 - ★ Fitted tags for easy connection.
- 4/-**
each

COILPACKS.—A full range is available for Superhet and T.R.F. Mains or Battery. Size only 1½in. high x 3½in. wide x 2½in. Ideal for the reliable construction of new sets, also for conversion of the 21 RECEIVER, TRI196, TYPE 18, WARTIME UTILITY and others Aligned and tested, with full circuits, etc. Fully descriptive leaflets available.



Outstanding

OSMOR

Quality Lines of Interest

A spotlight on just one of the range of Osmor "Q" coils.

H.F. CHOKE Type Q.C.1.

Frequency coverage 150 kc/s to 20 m/c. Iron-dust core and single-screw fixing. Prototype tested and approved by M. G. Scroggie, B.Sc., M.I.E.E. Ideal as anode load in T.R.F. receivers, for decoupling and general purposes. Price 4/-.



FOUR for the Price of TWO!
THE NEW "FOUR-TWO" CHASSIS CUTTER
of entirely new design. Cuts two sizes of holes with any one reversible punch and die; and can be operated with a spanner or tommy-bar. Blanks easily removed.



PUNCH and DIE SIZES:
No. 2 1/8 x 1/16 in.
No. 3 1/8 x 1/16 in.
Supplied complete with both No. 2 and No. 3 punches and dies for 30/- (postage and packing 1/3), or 16/- one punch and die only. (Please state which.)
Tommy Bars 1/3 each.
The OSMOR "JIFFY PUNCH" cuts a 3/16 in. hole with one blow of a light hammer.



Complete with Punch and Die, 5/9 post free.

Dear Reader,
We can't mention all our products here, but shall be glad to receive your enquiries. If it's top-quality components and a speedy, courteous service you are looking for—try Osmor. We really shall do our best for you.



You won't believe it—

the first time you hear your own voice! Have fun and find endless pleasure in using an **INEXPENSIVE TAPE RECORDER**—you can build yourself. We can supply all the parts to make a really efficient unit, utilising your gramophone turntable (which can still be used for its normal purpose). Send 2/6 for easy-to-follow blue-prints and instructions, or ask for details.

- CRYSTAL MICROPHONES**
As used in the Tape Recorder mentioned above and for almost any equipment where quality at a low price is desired.
- ACOS 22-2.** Table or hand model, as illustrated, including removable base. Uniform response. 40-6,000 c/s. £6/6/-.
- ROTHERMEL 2AD56.** Black anodised finish, as illustrated, for hand or table use. Tapped to fit any standard base. (Table-bases available shortly at approximately 10/- each.) Uniform response. 30-10,000 c/s. With cable, £3/3/-.



We keep stocks of many radio components for use in published circuits, including the following:

- "PRACTICAL WIRELESS"
3-Speed Autogram; Modern I-Valver; A.C. Band-pass 3; RI155 Converter.
- "WIRELESS WORLD"
No Compromise T.R.F. Tuner (Osmor coils QA11 and QHF11 for M.W. and QA12 and QHF12 for L.W. are suitable, price 4/- each.)
- Midget Mains Receiver (Osmor coils QA11 for M.W. and OA12 for L.W. are suitable. Price 4/- each.)

FREE! Send 5d. (stamps) for FREE CIRCUITS and full lists of coils, coil-packs and radio components.



Keep those small components—resistors, condensers, etc., neatly stored yet visible, by using an OSMOR "JAR-RACK"

(If you're a generous husband you'll buy one or two for your wife's larder, too.) Holds any 1-lb. jam jars which are easily removed but cannot fall out. Just the thing for the tidy "HAM" or Radio Dealer.
Type 1 for wall-fixing, as illustrated, 6/9 each, holds 8 jars. (Jars not supplied but easily obtained.) Length 24in., enamelled olive green.
Type 2 for screwing under a shelf, 5/9 each, holds 6 jars. Length 18in., enamelled green. Post and packing 1/- (either type). (Trade discount allowed to Dealers.)

I.F.s. 465 k/c. Permeability-tuned, with flying leads. Standard size 1½in. x 1½in. x 3½in. For use with OSMOR coil-packs and others, 14/6 pair. PREALIGNED, 1/6 extra.

DIALS

Metal dials, overall size 5½in. square, as illustrated. Cream background, 3-colour. Type M1, L.M.S. waves. M2, L. & M. waves. M3, M. & 2/S. waves 3/6. Pointer, 1/6; Drum, Drive, Spring and Cord, 3/2. Type A glass dial assembly, measuring 7in. x 7in. (9½in. x 9½in. overall). Mounts in any position. Choice of two 3-colour scales, 24/6. P. & P. 1/6.



Osmor Radio Products Ltd.

(Dept. P33) BRIDGE VIEW WORKS, BOROUGH HILL, CROYDON, SURREY. Tel.: Croydon 5148/9

Practical Wireless

EVERY MONTH
VOL. XXIX, No. 557 MARCH, 1953
COMMENTS OF THE MONTH

Editor F. J. CAMM

21st YEAR
OF ISSUE

By THE EDITOR

V.H.F.

HAS the BBC come to the conclusion that V.H.F. does not warrant further expenditure or development? We ask this question because it received high recommendation in the Beveridge Report, and suggested that the BBC should develop this system of broadcasting which, it is claimed, provides reception practically free from interference.

Transmissions on frequency-modulated V.H.F. are regularly radiated from Wrotham and we wonder why the BBC has not invited the vast army of radio experimenters in this country to co-operate with them by sending in reports on those transmissions. There are radio amateurs in every part of the British Isles, even in the remotest villages and hamlets. These are the knowledgeable listeners, able to send intelligent reports and draw proper conclusions from the transmissions. The BBC has on tap the unpaid and enthusiastic services of these keen experimenters, whose experience goes back in a high percentage of cases to the earliest days of radio.

The paucity of information on the subject and the comparative silence of the BBC implies that the results of experiments have been disappointing. It will be remembered that America became almost wildly enthusiastic about V.H.F., but after an experimental period they changed their views. It is true that they are still using frequency-modulated V.H.F.

21 THIS YEAR!

THIS journal celebrates its coming of age in September this year. The first issue of this journal was published on September 24th, 1932. From 1932 until 1940 it appeared as a weekly publication. In its early years it had eleven weekly competitors. To-day ten of those do not exist. We naturally expected fierce competition in our early years and we certainly had it! But one by one these journals died, unable to meet the competition which we put up in return. Those were the days when a new receiver was described practically every week—in every journal except P.W. The specifications for those receivers were more like a wholesaler's catalogue than a straightforward specification for a receiver. Practically every

supplier of each individual component was listed and the amateur was left to take his choice. It is not surprising that he struck difficulties as a result of this. In some cases the components could not be accommodated on the base-board. In others the characteristics were so widely different from those required by the circuit that the set was unstable.

The basis of our editorial policy, from which we have not departed, is that only the parts used in the prototype receiver were specified. We did not give alternatives and as a result readers were able to achieve the same results as we did. If they struck snags we were easily able to discern the cause of the trouble.

The second part of our policy was that we answered readers' questions free of charge. Most other journals charged a fee, anything from 2s. up to 5s. per query. Needless to say, the trade welcomed our policy and they rallied round our banner. To us the reader comes first, and this is in the best interests of the trade. We exercise the greatest care in our selection of advertisers and, if an advertisement appears in these pages readers may rest assured that we have investigated the bona fides of the proprietors. Wherever a reader fails to obtain satisfaction we stand behind him. It is a pleasure to us to note that many of our advertisers have regularly supported this journal from its commencement. It is also with justifiable pride that we can say that P.W. has a larger circulation to-day than ever and it is an ever-growing circulation.

Our September issue will be a special number, a souvenir issue with more pages and many special features. We shall have more to say about this as the time approaches.

PREMIUMS FOR TECHNICAL WRITERS

THE panel of judges appointed by the Radio Industry Council to award premiums for technical writing will soon be considering what articles qualify for the awards this year. They are made to non-professional contributors of technical articles on radio, published during 1952 in any journal on sale to the public.

The awards are of twenty-five guineas each and up to six are awarded each year. F.J.C.

ROUND the WORLD of WIRELESS

Broadcasting Receiving Licences

THE following statement shows the approximate number of sound licences issued during the year ended November, 1952. The grand total of sound and television licences was 12,844,740.

Region	Number
London Postal ...	1,792,499
Home Counties ...	1,501,761
Midland ...	1,375,000
North Eastern... ..	1,804,256
North Western ...	1,445,881
South Western ...	1,051,966
Welsh and Border ...	703,579
Total England and	
Wales	9,674,942
Scotland	1,142,779
Northern Ireland ...	213,229
Grand Total	11,030,950

These figures include licences issued to blind people without payment.

Capt. R. T. Paul

CAPT. R. T. PAUL, C.B.E., R.N.(retd.), A.M.I.E.E., has joined the Equipment Division of Mullard, Ltd., as commercial manager, co-ordinating the activities of the three product groups—radio, telephone and electronic equipment.

Capt. Paul's distinguished career in the Navy included acting as Chief Signal and Radio Officer to the Allied Naval C.-in-C., Expeditionary Force, and he was responsible for the naval signal, radio and radar organisation for the Normandy invasion. Later he was in charge of the naval wireless network and was the first chairman of the Western Union Communications Committee (Naval).

Sir Harold West

SIR HAROLD WEST, Sheffield's Master Cutler, has been elected chairman of the reception committee for the annual summer meeting of the Institution of Mechanical Engineers to be held in the City next July. Between 600 and 700 members of the Institution are expected to attend. Dr. J. M. Whittaker, Vice-Chancellor of Sheffield University, has been elected

vice-chairman of the reception committee.

Elections for members of the executive and reception committees to arrange the three-day visit of delegates have been made from the Yorkshire branch of the Institution.

Germany Honours British Radio Amateur

THE German Amateur Radio Society has elected Major Rowland Shears, a Senior Development engineer at the Electronics Laboratory of Burndep, Ltd., Erith, their Honorary Member Number One.

This is in recognition of the services he rendered German amateur radio, first in forming a club and later obtaining transmitting licences from the German Post Office.

Major Shears became a licence holder at 16, and now operates a transmitter which he describes as "the most powerful permitted by the licence." Under the call-sign of G8KW he has contacts in all parts of the world. At the end of the war he was responsible for the rebuilding of the German Broad-

casting Station at Langenberg, and later the organisation of the police radio communications throughout the British Zone.

Realism in Sound Broadcasting

IN a lecture on "Sound Broadcasting" for children at the Institute of Electrical Engineers in London, Dr. K. Sturley, head of the engineering training department of the BBC, explained some of the difficulties that sound presented to the technicians.

He allowed children to see their own voice vibrations on a cathode ray tube.

Equipment in R.A.F. Austers

IN order to standardise the V.H.F. equipment in Austers engaged in artillery co-operation, the R.A.F. is to install in all these machines the Plessey transmitter-receiver type P.T.R.61. This makes communications available on six channels within the band 116-132 Mc/s., the crystals controlling which may be changed in flight.

Specifically designed for light and medium aircraft, the transmitter receiver, which is particu-



Clive Simpson, of Laleham, Middlesex, talks into the microphone held by Dr. K. Sturley, of the BBC, during his lecture on sound at the Institute of Electrical Engineers, London.

larly simple to operate by virtue of single knob tuning on both sections, has already been adopted by the Belgian and Netherlands Air Forces, and by civil airlines in many parts of the world.

Honour for Vidor Executive

MR. WILLIAM R. T. MILNE, Personnel Officer for the Vidor-Burndept Group, appeared in the Colonial Office list of the New Year's Honours with the Order of the British Empire.

Mr. Milne served from 1930 to 1952 in Nigeria and was lately Civil Service Commissioner there.

Obituary

WE regret to announce the death in Bridgewater Hospital on December 27th of William Thomas Gibson, O.B.E., M.A., B.Sc., M.I.E.E., of Ivy House, Chard, Chief Valve Engineer of Standard Telephones and Cables Limited and Manager of their Ilminster laboratories and factory. Born in 1899 at Northampton, he set up the valve laboratory of Le Matériel Téléphonique in Paris in 1928, and the Newark, New Jersey, valve laboratory of Federal Telephone Laboratories in 1932.

W. T. Gibson was a member of the Institution of Electrical Engineers and served on the committee of its South Western Sub-Centre. He was a member of Chard Rotary Club and of Chard Musical Society. His hobbies were music and photography.

Delivering the "Goods."

IN Manchester recently, Mr. J. Allanson, a Vidor representative, emerged from a shop and noticed that his van had been opened at the rear. Although it was dark, he could see the form of a man inside, so he slammed down the shutter, locked it and drove his uninvited passenger to the nearest police station.

The police extracted the "goods" from the van and the short ride cost him no less than five pounds. Mr. Allanson received high praise from the police for the presence of mind he had shown.

New Instalment Scheme

EKCO dealers are being invited to participate in a scheme which will draw in the large number of would-be purchasers of radio and TV who have difficulty in finding the 33 1/3 per cent. of total price with which to include a H.P. agreement.

The dealer's first step is to conclude an Agreement with Bowmakers who handle Ekco H.P. The potential customer then pays in through regular Bowmaker channels weekly, monthly, or even irregular, payments of as much as he can afford. When these payments total 33 1/3 per cent. of the total price of the set he has chosen, a normal H.P. agreement is signed and the set is delivered.

Remainder of payments are made in the normal way.

"Welcome to Britain"

FOLLOWING the "Welcome Stranger" programmes broadcast during Festival Year and 1952 with Eamonn Andrews as host to visitors to London, another series of "Welcome" programmes, this time "Welcome to Britain," starts on February 15th in the Light Programme. Although listeners will again be meeting visitors from Home and Overseas, the series will be presented in a different form, and each programme will last for an hour.

European Songs

IN the various European broadcasting sections of the BBC in Bush House are many foreign recordings not often heard in the domestic services.

Light Programme announcer Roy Williams has drawn on these for a new nine-weekly series which he begins on February 7th under the title "Songs of the Traveller."

End Licence Demand

THE Liberal Party Council of Canada, in session at Ottawa recently, decided to demand the ending of radio licence fees and to ask for permission for private broadcasters to transmit their own television programmes.

Revenue Minister, Mr. McCann, however, stood by the Government's policy of holding its own rights in the Canadian Broadcasting Company.

Private Call Service

THE personal radio-message service already in operation in New York and

Cincinnati has been inaugurated in Cleveland, Ohio, U.S.A.

The subscriber wears a vest-pocket size receiver pre-tuned to 43.58 Mc/s on which he hears his own personal call sign, the signal for him to contact the service office for the message.

Aberdeen Coronation Award

TO mark the coronation of Her Majesty Queen Elizabeth, the Aberdeen Amateur Radio Society is to issue a certificate to any amateur who contacts four member stations of the society between January 1st, 1953 and December 31st, 1953.


In addition, stations located in any other "Aberdeen" in the world will automatically be elected to honorary membership of the society. To claim the certificate, only the call signs of the stations contacted, date and time of QSO's need be submitted.

Claims should be sent, together with 2s. 6d. (50 cents Canada U.S.A. and Possessions), to Aberdeen Amateur Radio Society, 1-6, Blenheim Lane, Aberdeen.

No Effects from Fire

THE recent fire which broke out at the Hirwaun, Glamorgan, factory of Thorn Electrical Industries Ltd. has not interrupted the production of Ferguson radio and television receivers.

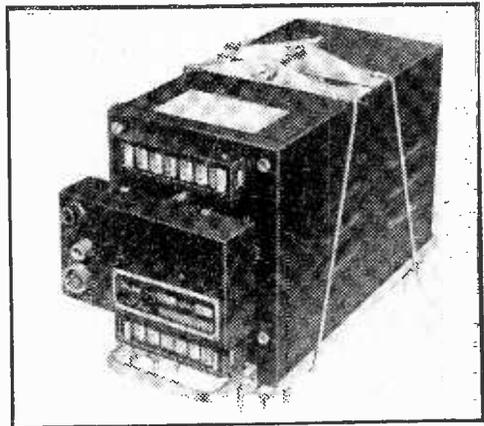In spite of damage to machinery and property, no noticeable effect is expected, as much production work will be transferred to other Thorn factories.



The Plessey transmitter/receiver, type P.T.R.61, fitted with standard remote-control adaptor, which is being installed in R.A.F. Austers.

out of phase with that caused by the first half so that, in effect, only the difference between the two signals is passed to the second half and the two halves settle slightly out of balance such that the signal from the first half is slightly greater than that from the second half. This out-of-balance ratio is not serious in practice and the automatic operation completely outweighs the disadvantage of the slight unbalance.

Equalising Circuit

For the purist, however, there is a way to bring the circuits into even closer balance, and here is the first deviation from the original design. The theory of automatic balancing deals with anode currents and not anode voltages; by using different values for the two anode loads, R9, R11, the voltage outputs can be equalised, and it is the voltage output signal that is required to drive the output valves. The actual sizes required for this purpose can be calculated, assuming valve characteristics and resistance values to be accurately as specified, but in fact both valves and resistors vary from specification. One theoretically correct combination is 52K Ω for R11 and 45K Ω for R9. To adjust for variations in components used, however, a potentiometer VR1 is introduced. With the slider C at the A end of the element the whole of VR1 is added to R11 in the circuit of the second half of the valve; at the other extreme, the slider at B, VR1 is added to R9, and the second half is left with only R11. Between these extremes any intermediate state of balance can be set up. R9 is made 39K Ω and R11 is 47K Ω . These are standard values in the 10 per cent. tolerance range, which should be used in these positions. Now, if a 10K Ω potentiometer is used (wirewound) and the resistance between A and C is made 6K Ω the load on the first half will be 39K Ω plus 6K Ω , i.e. 45K Ω as specified above, whilst the load to the second half will be 47K Ω plus 4K Ω making 51K Ω also as specified previously, but moving the slider from this position one way or another will serve to balance for any imperfections in components.

In the H.T. lead to the output transformer is inserted a resistance, R21, to be used in balancing, VR1 being adjusted for minimum signal across this resistance. As an indicator, an output meter is preferable, but a pair of ear-phones will serve quite well. These should be of high resistance (or, if they are low resistance they should be coupled through a transformer across R21) and condensers of, say .01 μ F should be interposed between each end of the resistor and the phones (or transformer) to keep out D.C. When the balancing is complete R21 can be removed from the circuit, or shorted out. By taking the indication of balance in the output circuit the balance adjustment will take into account also differences in the output circuit, including output valve differ-

ences, and the setting will not hold if these valves are changed or reversed. It is wise to mark which valve is to be used in which socket when the balancing is completed.

It will be necessary to mute the loudspeaker whilst balancing with earphones or otherwise it will be impossible to hear when the position of minimum signal is reached. This is best done by disconnecting the loudspeaker from the secondary of the output transformer and in its place a resistor about equal to the speech coil impedance (i.e., 3 ohms or 15 ohms as the case may be), should be connected. Remember the power that might be dissipated across this resistor; if the amplifier is fully loaded during balancing operations, the full audio output rating of the amplifier will be dissipated and a resistance of suitable wattage will be needed. A "humdinger" resistor will be quite suitable and it is not necessary to go to any trouble to see that its resistance is exactly the same as the speech coil impedance.

The output KT66's are fed one from each half of V2, R16 and R18 being grid stoppers. A common cathode biasing resistor, R17 is used. As the output signals have been balanced the signal currents through this resistor from each output valve will cancel and no useful purpose would be served by including a bypass condenser. It is, of course, common to omit such a condenser in push-pull output circuits because, should the valves be unbalanced, feedback in this resistor will tend to reduce the degree of unbalance, but in the present case balancing has been carried out and the bias resistor is not relied upon for the purpose.

Feedback Circuit

A variable resistor, VR2, has been introduced in the present case in place of the fixed resistor specified in the earlier version. It is interesting to see the effect of varying the feedback ratio and, when no elaborate test equipment is available to trace distortion and instability, it is possible to ensure that there is a

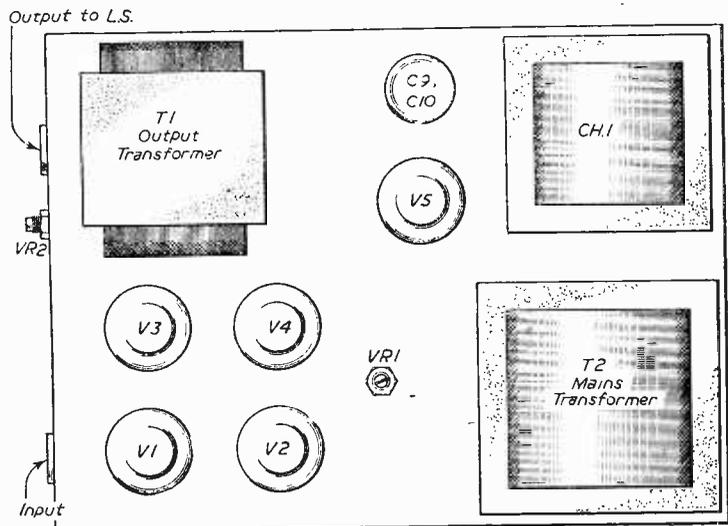


Fig. 2.—Suggested layout of the main components.

sufficiently wide margin of stability by reducing the resistor below the operating point temporarily. It should be possible to reduce the resistor quite appreciably before instability sets in or the operating setting decided upon is too low. At the other end of the feedback loop, it is possible to effect an economy by using the cathode bias resistor of V1 as the feedback resistor, thus eliminating the condenser and resistor previously used.

The weak link in the chain of an amplifier with feedback is generally the output transformer, and the symptoms produced arise from the undesired phase-shifting of the higher frequencies, generally above the audio range, making the feedback positive instead of negative at those frequencies and so setting up oscillations that undo all that has been done in an attempt to improve quality. Quite expensive transformers have been produced for incorporation in feedback amplifiers and this is the only theoretically perfect solution to the problem. Unfortunately, few of us can afford the price of such a component and the earlier amplifier was designed specifically to see what kind of results could be obtained using a cheaper component. The network R1, C2 was introduced to help in this connection and the action is to reduce the gain at the frequencies likely to be sufficiently phase-shifted to give trouble so that they would be of insufficient amplitude to cause trouble. This filter is retained and an additional precaution is taken. C8 is introduced across VR2. This increases the degree of feedback to those higher frequencies and corrects the undesired phase-shifts that have taken place. A still further step is taken by using a triode in V1 position in place of the pentode previously used, thus reducing the forward loop gain somewhat, though it is still found quite adequate for the purpose. The result is an all-triode arrangement, such as has always been considered the ultimate for best quality.

Earth Returns

A final modification incorporated in this design is the apparently complicated method of arranging earth returns. When designing amplifiers to give high gain for small signals it is necessary to take careful precautions with earth return wiring so that no part of the return path is via the chassis. The method is similar to that used in short-wave equipment of returning all points in one circuit to the same earth point. The present is not a case requiring high gain for small signals and generally such precautions are

not taken. At the same time, this amplifier is inherently hum-free and has a remarkably quiet background, so that it is worth while taking extra precautions to keep hum out of the input circuit where feedback cannot help in suppressing, particularly as the speaker wiring is actually in the input circuit and, of course, may wander about the house.

It will be seen that a screened two-core cable is used for the input. Actually a twin-core TV coaxial cable was used for this purpose, being neat and very effective. The actual connector used is a miniature, four-pin plug and socket with metal skirt, such as is easily obtainable. The cable braid is connected to two pins and the equivalent sockets are connected to the amplifier chassis. The remaining two pins go to the cable inners for the input signal and the earth return.

As before, power is fed via a five-pin connector to the associated feeder and the mains switching is also operated from the feeder via two cores of the five-core connecting cable. Thus, any of the "Modern" series of feeders will be suitable with appropriate modifications to the output circuit to allow for the return earth feature.

Construction

The layout used in the prototype is similar to that used for the earlier model and is given in Fig. 2. The position of the preset variable resistors is indicated. These will not require adjustment after the preliminary setting-up process unless valves are changed or unless, in the course of time, balance is lost to some degree due to uneven ageing of the valves. Screwdriver adjustment is all that is required, therefore, and these need not be accessible when the equipment is built into its cabinet.

The need for introducing the compensating resistor in the internal/external speaker switching, given in the previous article in the July, 1950, issue, has been queried. In actual fact, the addition of extra speakers in parallel in the output of the feedback amplifier makes no noticeable change to the volume of sound from the original speaker. This is because the feedback is thereby reduced and consequently compensates for the changed load conditions. At the same time, if the degree of feedback is to change to allow for the additional speakers it can no longer be of the optimum degree decided upon from a quality point of view and the suggested circuit does allow for constant

(Continued on page 130)

COMPONENT LIST FOR FIG. 1. THE AMPLIFIER

R1—47 K Ω	R18—4.7 K Ω	C8— (.001 μ F 350 V for 3 ohm speaker 500 pF 350 V for 15 ohm speaker)
R2—33 K Ω 1 watt	R19—100 Ω	C9—16 μ F 450 V elec.
R3—47 K Ω 1 watt	R20—100 Ω	C10—8 μ F 450 V elec.
R4—680 Ω	R21—100 Ω	C11—32 μ F 450 V elec.
R5—1M Ω	R22—(if required) 1M Ω	V1—Brimar 6J5 (or 6J7 strapped as triode)
R6—15 K Ω	VR1—10K Ω wirewound	V2—Brimar 6SN7 5 Volts 3 Amps
R7—4.7 K Ω	VR2—10K Ω wirewound	V3—Osram KT66 6 Volts 5/6 Amps
R8—470 Ω	C1—8 μ F 450 V elec.	V4—Osram KT66 CH1 20 H. 150/200 mA
R9—39 K Ω 1 watt	C2—200 pF 350 V	V5—Brimar 5U4 CH2 20 H. 50 mA
R10—22 K Ω 1 watt	C3—.1 μ F 450 V	T1—To match speaker to 4,000 ohms (i.e., 16 : 1 for 15 ohm speaker or 36 : 1 for 3 ohm speaker)
R11—37 K Ω 1 watt	C4—8 μ F 450 V elec.	T2—Mains transformer 450 0 450 Volts 150/200 mA (depends on needs of feeder used)
R12—4.7 K Ω	C5—.25 μ F 450 V	
R13—1M Ω	C6—.25 μ F 450 V	
R14—100 K Ω	C7—.25 μ F 450 V	
R15—100 K Ω		
R16—4.7 K Ω		
R17—220 Ω 4 watt		

Increasing the Output

A SMALL AUDIO AMPLIFIER WHICH CAN BE USED WITH MOST TYPES OF OLD SET

By K. C. Ireland, A.R.I.C.S.

THIS little amplifier was especially built to be used with a 12-year-old set. The requirements were:

- High-quality output.
- Low cost.

Must be easily connected to existing set without extensive alterations.

Of small dimensions to enable the complete amplifier to be installed inside the existing cabinet.

To reduce the cost it was decided to use the existing power supply for the H.T. current.

The amplifier was to be used in conjunction with a 1937 five-valve superhet, using 4-volt valves. This set was satisfactory in all respects save that it lacked the crisp high-quality output expected to-day. As the audio section consisted of a single pentode fed directly from the signal diode of the previous valve, a 2D4A, there was insufficient amplification available to introduce a negative feedback system. It was, therefore, decided to build a two-stage amplifier and connect this into the circuit and dispense with the existing output valve but retain the coupling system which included the volume control.

The cabinet was of large dimensions, being 18in. high by 15in. wide by 10in. deep, and of substantial construction. In addition to the chassis the cabinet contained an 8in. P.M. speaker, and it was found that by using a little care and all available space to employ a 10in. speaker in its place and still leave room for a small amplifier.

The alternative to a new amplifier was to incorporate a further audio stage prior to the pentode output, but this would have entailed much rebuilding, further complicated by finding room on the chassis for the additional valve and components. There would have been also the risk of over-running the mains transformer if a further 1 amp were taken from it to provide heater current for the new stage. It was felt that an amplifier using modern 6-volt valves would be a better proposition. The amplifier valves were supplied with heater current by means of a small filament transformer obtained from an

advertiser in the pages of this journal. The total heater consumption is only .75 amps. The H.T. current required is in the region of 50 milliamps, and only a few more than that consumed by the single pentode of the set. It was felt that the small additional current could safely be provided from the present rectifier.

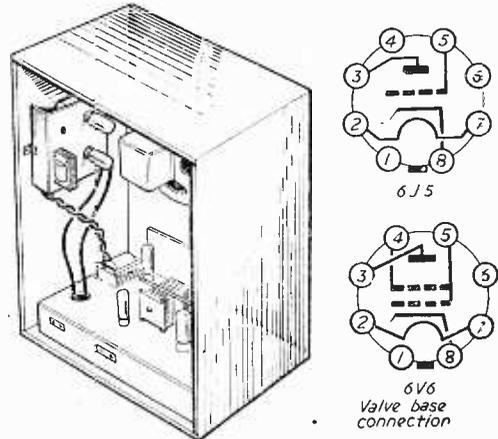


Fig. 2.—Position of amplifier in existing cabinet and valve base data.

The Circuit

The circuit chosen was quite conventional in design (Fig. 1), and utilises a 6J5 as a first-stage amplifier and a 6V6 as output. Both valves are easily obtained on the surplus market, and were chosen for this reason. The first acts as a voltage amplifier and is resistance coupled to the 6V6. Anode decoupling is used between stages consisting of a 5,000 Ω resistance and 8 μ F condenser. No bias condenser was found necessary in the cathode circuit of the 6J5.

Negative feedback is provided over the whole amplifier by feeding back a portion of the signal from the L.S. speech coil to the cathode grid system of V1.

Construction is simple, and the whole amplifier was built on a metal chassis 6in. by 6in. by 1½in. deep. All components must be of small size, but nothing special is

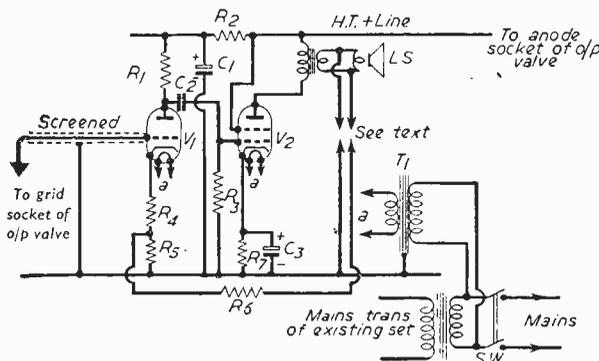


Fig. 1.—Theoretical circuit of the amplifier.

LIST OF COMPONENTS

- | | |
|-----------------------|-----------------------------|
| R1—25,000 Ω . | Two Octal valveholders. |
| R2—5,000 Ω . | C1—8 μ F Elec. 350 v.w. |
| R3—100,000 Ω . | C2—.1 μ F Mica. |
| R4—1,000 Ω . | C3—50 μ F 25 v.w. |
| R5—100 Ω . | T1 { Heater transformer. |
| R6—500 Ω . | { 6.3 v. 1.5 amp. |
| R7—240 Ω | V1—6J5. |
| (2 watt). | V2—6V6. |

required. All resistances can be of the $\frac{1}{2}$ -watt type with the exception of the cathode bias resistor for the 6V6 (V2) which should be of 2-watt rating.

It was not found necessary to screen any lead except that to the grid of V1.

The underside of the chassis is shown in Fig. 3, which also shows the wiring and connections to existing receiver.

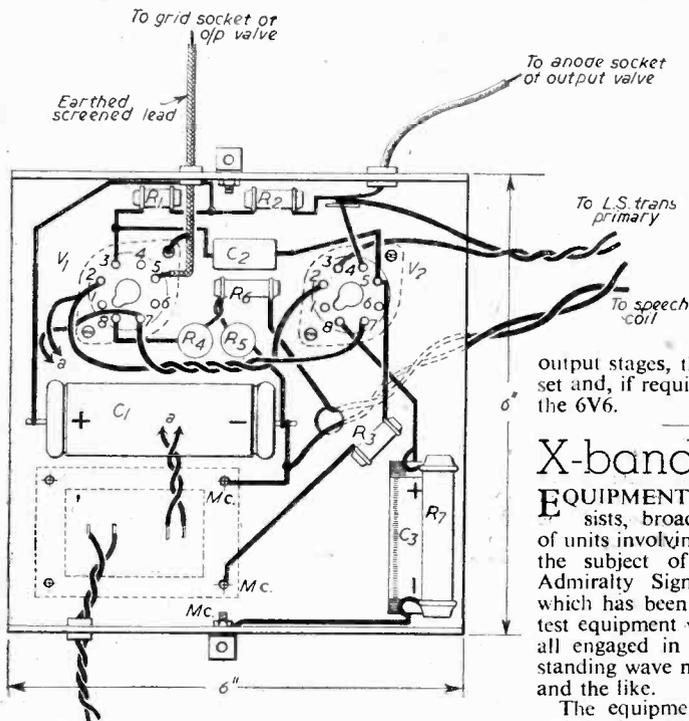


Fig. 3.—Practical wiring diagram.

Modifications

No under-chassis alterations are necessary to the existing set. The following external modifications and connections are required:

Remove the output valve.

Connect H.T. line of amplifier to anode socket of output valveholder in set.

Connect inner wire of screened lead from amplifier to grid socket of output valveholder in set.

Connect amplifier chassis to set chassis as negative line.

Wire heater transformer primary of amplifier across primary of set transformer.

Disconnect leads from set to loudspeaker transformer primary and reconnect primary to speaker leads coming from amplifier. Join together the free ends leading back to chassis. This is necessary to provide a source of H.T. at the anode socket.

Connect the appropriate leads from amplifier to speech coil of L.S. If, on testing, there is severe distortion this indicates a positive feedback and not negative. Reversal of these leads should cure this trouble.

The set volume control will still be operative, and

the on-off switch will operate both set and amplifier.

If, after test, all appears satisfactory, screw the amplifier to the inside of the cabinet. Fig. 3 shows the method adopted in the original model.

To assist ventilation and dissipation of heat a small metal shield was provided to the underside of the top of the cabinet and a slot cut in the top edge of the cabinet back.

The amplifier will provide sufficient output to adequately load a 10in. speaker.

If the existing speaker is mains energised, the energising coil can remain as the smoothing choke and only the connections to the transformer primary need be disconnected and reconnected to the amplifier.

No tone-control system was provided for as it was felt that the negative feedback system should improve the frequency response to an extent as to make this unnecessary.

If the existing set does contain the usual top cut tone control normally provided with pentode output stages, this should be disconnected from the set and, if required, wired across anode and earth of the 6V6.

X-band Test Equipment

EQUIPMENT for a microwave test bench consists, broadly, of mechanical components and of units involving circuitry. This latter group formed the subject of a development contract for the Admiralty Signals Research Establishment, from which has been evolved a tailored range of X-band test equipment which should fill a long felt want for all engaged in microwave measurements involving standing wave measurements, frequency calibrations, and the like.

The equipment comprises high and low voltage stabilised power supplies, a modulator and a selective amplifier.

Selective Amplifier

This instrument may be used as a selective or broad band amplifier over the frequency range 300-6,000 c.p.s.

As a selective amplifier the maximum sensitivity of the unit is such that an input signal of 1.6 microvolts produces full scale deflection on the output meter with a signal-to-noise ratio of not less than 26db.

The selectivity of the amplifier in the selective condition is such that if the input signal frequency is detuned by 10 per cent. the reading on the output meter is halved.

There are two independent input sockets, each of which is provided with a gain control. The amplifier also has a calibrated attenuator, a fine gain control and two output sockets. One of these latter is for a cathode-ray oscilloscope and the other for an external output meter.

The input impedance of the instrument is 5,000 ohms.

Initial development of this equipment, which is still in limited production, was carried out by The Plessey Company Limited, Ilford, Essex.

Wiring

After mounting the parts wiring can be commenced. This process is quite simple but it is advisable to use only soldered joints and wire short and direct.

Components

All fixed resistors are $\pm 2\%$ of value stated. Suitable combinations of resistors may be connected in series or parallel to produce the required total, but where this is done, both or all the resistors must be of the same tolerance value. If some old parts are already to hand, i.e., switches, resistors, etc., these may be used, but be sure that the values are correct, and in the case of resistors check their value with a

volt. When 1 volt is accurately obtained remove the meter and connect the V.T.V.M. and observe reading. Adjust calibration control to make meter read 1 volt.


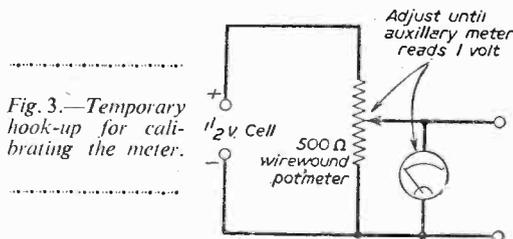



Fig. 3.—Temporary hook-up for calibrating the meter.

Reverse test leads and note reading on opposite side. If reading there is not 1 volt as it should be, remove test leads from the input jacks of V.T.V.M. and recheck zero. Repeat performance as before and adjust R3 until accurate 1 volt readings are obtained either side of zero. It may be necessary to try a few resistors in the R4 position to establish the zero—1 volt either side. When completed seal R3 with a drop of nail varnish, and care should be taken not to disturb it once set. Check the 25 volt range with a battery of, say, 12 volts and the 250 volts with a source of approximately 200 volts. All readings should be compared with a good low resistance meter of 1 K Ω per volt or more, to ensure accuracy of V.T.V.M. due to possible error in value of some of the resistors used.


When completed the original model was found extremely useful in measuring all D.C. voltages with great accuracy from .1 of a volt through to 250 volts D.C. It was capable of measuring minute voltages in circuits which called for a meter having an extremely high input resistance, and everything considered it was found to be a valuable accessory in the workshop, and well worth the time and money spent in building and calibrating it.

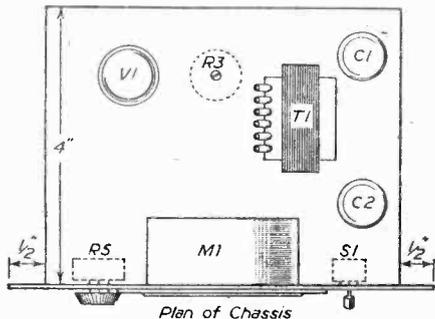

Plan of Chassis

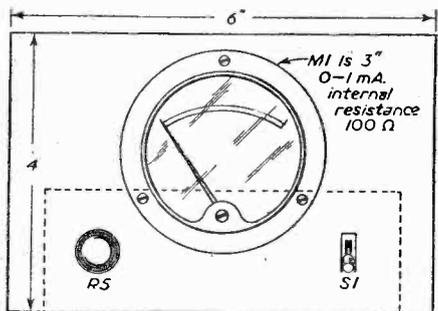

Front of Panel

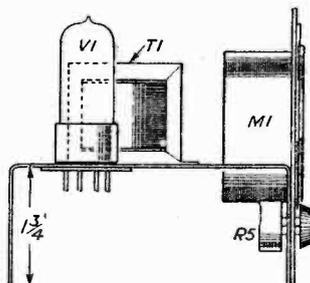

End view of Chassis

Fig. 2.—Details of the chassis and assembly.

good ohmmeter before installing. The switch must make good contact otherwise operation and observations will be erratic.

Calibration

The scale of the meter is removed and a duplicate copy of the arc is made on thin white card, marking the exact centre of the scale. Each side of the centre point is divided into five equal divisions, and these are marked for 0-2.5, 0-25 and 0-250 volts either side of centre scale. If this operation is done with a good compass, a fine pen point and drawing ink, no trouble will be experienced. With all wiring done and rechecked, switch on and allow two minutes for valve to heat. The needle will climb toward or past centre scale. Rotate zero control (R5) to bring needle to exact centre zero. Hook up temporary calibration circuit as shown in Fig. 3. With a good quality meter adjust the wire-wound potentiometer (Fig. 3), to give an output of 1 volt. (The better the meter used for this operation the better will be the calibration.) Do not use a meter less than 1 K Ω per

PARTS LIST

- All resistors 1 watt $\pm 2\%$.
- R1—10M Ω .
- R2—820,000 Ω .
- R3—250,000 Ω (pot).
- R4—2,700 Ω .
- R5—25,000 Ω (pot)
- R6—68,000 Ω .
- R7—1,000 Ω .
- R8—2,200 Ω .

Note :—R3—Semi-variable type potentiometer.

- C1, C2, 8 x 8 μ F Electrolytic.
- S1, S.P.S.T. toggle.
- S2, S.P. 3-way wafer.
- J1 } Insulated input jacks.
- J2 }
- M1—0-1 milliammeter (int. res. 100 Ω).
- FI—500 mA. fuse.
- TI—Mains transformer.
 - PR1, 220/230 volts
 - Sec. 1, 250 volts 20mA.
 - Sec. 2, 6 volts 3a. (see text).

SUPER-REGENERATION

A FIELD FOR THE SERIOUS-MINDED RADIO EXPERIMENTER

By E. G. Bulley

THE super-regenerative circuit is credited to E. H. Armstrong, who developed this type of circuit as far back as 1922. Since its origination, however, many variations have appeared, and various applications found. Nevertheless, this type of circuit lost favour in professional circles, but was always popular prior to the war with the radio amateur. This, perhaps, can be attributed to the fact that such circuits are fairly cheap to construct.

With the outbreak of war, the super-regenerative circuits, along with others, were once again investigated by various research engineers and applications found in radar, telemetering and remote control circuits.

Because of the uses found in wartime equipments, it is the writer's opinion that much more work will be carried out in this field. However, the reader whose hobby is that of experimenting with circuitry will find this field most interesting and not costly, and above all ideal for exploring the V.H.F. bands.

This article is written to assist such experimenters, and before proceeding therefore, it is necessary to appreciate what is meant by the term regeneration.

It can best be defined as the production of an oscillatory condition, which at the same time is prevented from becoming a sustained one by means of a quenching action.

Super-regenerative receivers are most successful at V.H.F., and with valves such as the 6F12 and 6L18 that are today available, little difficulty will be encountered on this score.

The regenerative receiver utilises a detector valve with reaction, and thereby, when the reaction is increased above a certain limit (dependent upon circuit conditions), oscillatory phenomena is created. This oscillatory condition must not be maintained, so to overcome this, another voltage is introduced into the detector. The frequency of such a voltage must be above audibility, and must be introduced in such a way as to cause the oscillatory condition to cease every half cycle of frequency. This frequency is commonly known as the "quench," and can be introduced into the grid or the anode of the detector valve. Nevertheless, it is as well to mention, how-

ever, that this quench frequency can be created by a separate oscillatory valve or by using the detector valve itself.

An important point one must bear in mind, is that the frequency of the quenching voltage is such as to avoid the possibility of a sustained oscillatory condition. Such a condition can result from the quench voltage frequency being too high. On the other hand, a quench voltage whose frequency is too low will undoubtedly create a high pitched signal note which will be audible. It is, therefore, essential that great care be taken in this matter, so that the created oscillatory condition can be stopped at every negative half cycle.

Basic Circuit

A basic super-regenerative detector which is self-quenched is shown in Fig. 1. This circuit is of the inductive type and trimmed by a suitable condenser C1. A similar circuit to that of Fig. 1 is that of a capacitive tuned arrangement shown in Fig. 2. This circuit is also self-quenched. Both these circuits, however, depend upon the relationship between C3 and R1 for the periodic blocking of the oscillatory condition.

Fig. 3 is a typical super-regenerative circuit, wherein a separate quench circuit is utilised. This circuit, although having a separate valve for quenching purposes, is capacitive tuned.

Advantages and Disadvantages

There are many advantages as well as disadvantages with this type of circuit, however, and for the convenience of this article both will be discussed so as to enable the reader to appreciate them. The main feature of the super-regenerative receiver is its very high sensitivity, especially at very high frequencies. The higher the frequency, the higher the sensitivity. It can therefore be appreciated why this type of receiver is successful at V.H.F. Nevertheless, a disadvantage which cannot be overlooked is that of the noise factor. One will notice that as the sensitivity is increased so is the inherent noise, in the

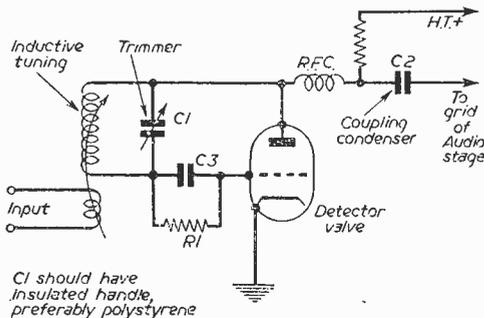


Fig. 1.—Basic self-quenched inductive circuit.

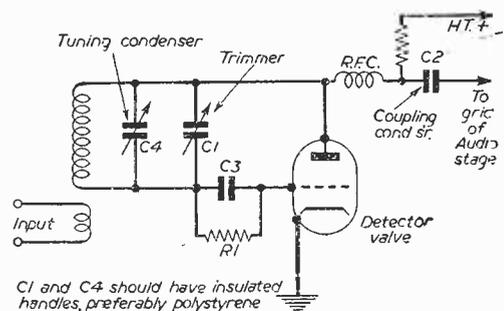


Fig. 2.—Basic self-quenched capacitive circuit

form of a continuous hissing sound. This noise can be reduced, however, by sacrificing some of the sensitivity of the receiver.

Receivers of this type suffer from what may be termed "Body capacity" effects. It is, therefore, essential to include suitable R.F. filters in the feeds, as well as foolproof screening. It may be as well to mention, however, that this capacitive effect can be the result of the coupling of the aerial to the detector being too tight. Furthermore, the matching of the aerial is important, because dead spots in the tuning will occur if the tuning is again too tight. Nevertheless, the loosening of the coupling usually overcomes this fault.

In the case of the self-quenching circuit, smooth operation can be had if one pays special attention to the grid condenser and resistor, namely C3 and R1 in Fig. 1. The reason for this is that these components determine the frequency and amplitude of the quenching

voltage. A characteristic of the super-regenerative circuit is the continual hissing when one is tuning to a specific signal. This does, however, disappear as soon as the signal is tuned in. The absence of this

hissing phenomena usually indicates that the quenching voltage is insufficient.

Warning

In conclusion, it is felt that it is necessary to mention that all super-regenerative receivers radiate

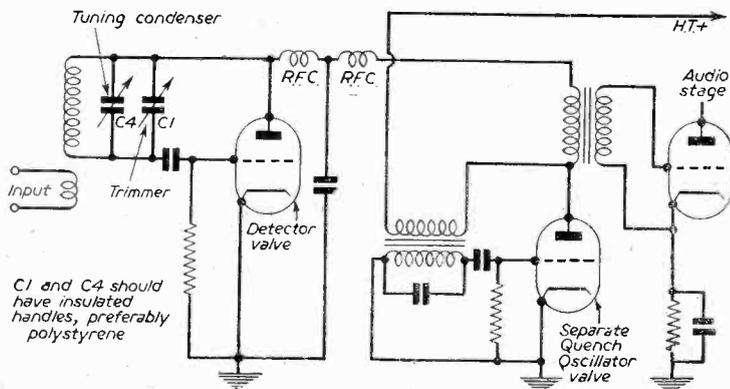


Fig. 3.—Basic externally quenched (capacitive) circuit.

R.F. energy which causes unwanted interference. Care must, therefore, be taken to prevent this happening. This can be done most satisfactorily by preceding the detector stage with a suitably designed R.F. stage, not forgetting, of course, to screen the receiver as previously mentioned.

The "Modern" High-power Quality Amplifier—1

(Continued from page 124.)

feedback conditions. It is up to the constructor to decide. If it is desired to get the last ounce of power available from the amplifier to the speaker he will avoid the use of such a compensating resistor so long as he will accept changing feedback degree. On the other hand, if he wishes to have optimum feedback under all circumstances he will include the resistor and sacrifice part of the amplifier power when working on the internal speaker alone.

Setting Up

When the amplifier is completed and the wiring checked it can be connected to the mains for D.C. tests, but little can be done until the feeder is available, unless an audio generator is available. To operate the amplifier alone, of course, it will be necessary to short-circuit the mains switching points of the output power socket and to tie the input and earth return sockets of the input plug to earth. If the amplifier is to be used with a feeder not providing a D.C. path across its output, or if the amplifier is likely to be switched on without a feeder, R22 should be included across the input of the amplifier.

Let it be assumed, however, that a suitable feeder has been completed and the two units have been plugged together. It will be noted that there is no input condenser in the amplifier. This must be included in the feeder, but it is usual to do so anyway and a condenser in the main amplifier merely reduces

the effective coupling capacitance. It is as well to disconnect the feedback circuit at first. Quite reasonable quality should be available without feedback, though there will probably be some hum. It is bad practice to use feedback on an inherently bad amplifier, and if results without feedback are not what they should be the faults must be found first and corrected. Be careful, however, not to overload the amplifier without feedback. Only a very small input signal will be needed, so start with the feeder volume control right off and then advance just far enough to give a comfortably loud signal.

Balancing can be done with or without feedback being applied. First set the moving arm of VR1 to the relative resistance positions indicated earlier. These need not be measured with exactitude. A rough estimate of the position that will put just over half of the resistance between A and C will do. Now connect the indicator, be it output meter or 'phones, across R2, using isolating condensers of say .01 to .1 μ F. to keep the H.T. out of the indicator. A steady signal is preferred for balancing, such as the note of a signal generator or maybe the tuning note transmitted before programmes start.

The operation of balancing is simply to rotate VR1 to the position of minimum signal in the indicator. It is unlikely that such perfection as an absolute null on an indicator so sensitive as a pair of 'phones will be obtained, nor is it necessary but with a fully loaded amplifier the signal in the prototype was reduced to negligible proportions. The minimum point should not run off the control unless, of course, there is a serious mismatch of resistors or valves.

(To be continued.)

Here it is...



STANDARD-LONG PLAYING


The G.P.30 crystal turnover pick-up is intended to provide the largest number of record enthusiasts with the best possible reproduction of standard and microgroove records.

So this pick-up satisfies four all-important requirements :

- ★It will reproduce both standard and microgroove records. ★It is simple to operate ; a turn of the front knob brings either stylus into use. ★The output characteristics give balanced, distortion-free reproduction with minimum surface noise when used in conjunction with commercial equipment such as the normal radio set. ★It is extremely kind to the record—giving long record life. The careful design gives exceptional tracking capabilities at the low stylus pressure of ten grammes.

Price in Great Britain **£2.10.0** plus P.T. 21/5d.

always well ahead

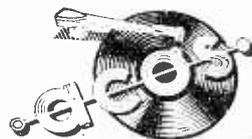

COSMOCORD LIMITED • ENFIELD • MIDDLESEX

80 ohm CABLE COAX STANDARD 1/4 diam.

Polythene insulated. NOT EX. GOV. 10d. per yd.

COAX PLUGS, 1/2 each. SOCKETS, 1/2 each. LINE CONNECTOR, 1/2

BALANCED TWIN FEEDER, per yd. 6d. TWIN SCREENED FEEDER, per yd. 1/-.

CONSTRUCTORS' HIGH QUALITY CHASSIS.—5 v. Sheet, cast-iron plated fitted Octal valveholders, tapping panel, cut out for transformer, and I.F.s., drilled for twin gang and controls. Ea. 14/-. DIAL ASSEMBLY to suit above, J.H. SL/8 glass L. M. S. dial. Flywheel tuning escutcheon, 9in. x 4 1/2in. Ea. £17/6.

Type "Full Vision" L. M. S. with escutcheon, 7 1/2in. x 3 1/2in. Ea. 13/-. MIDGET T.R.F. or S.H.E.T. WALNUT CABINET AND CHASSIS. Complete Dial, Drum, Drive, etc., 29/6.

WAVELENGTH SWITCHES 2-pole 2-way, 3/6 4-pole 3-way, 3/9. 2-pole 5-way, 3/9, etc. Slow motion drives, 3/9. Spindle drives, 2/- 2 1/2in. drum, 1/6.

I.F. TRANSFORMERS. 465 kc/s. Wearite Midget, 15/6; Wearite Standard, 12/6 pr; Plessey Type Semi-induct, 12/6 pr.; ditto, cast solder, 2/6 pr.; Twin Gang .0005 mfd., 8/6, ditto. Slightly gilded, 5/2c. 0005 Midget Twin Gang, 10/6; ditto, 37/6; 7/6, with dust cover and trimmers, 10/3.

COIL PACKS.—Osamor L. M. S., 52/-; Wearite, L. M. S. and Gram. 53/-. SENTERCEL MIDGET H.T. RECTIFIERS RM1, 125 v. 60 ma., 5/3; RM2, 125v. 100 ma., 5/8; RM3, 150 v. 120 ma., 7/-.

Two required for 250 v. etc. RM4, T.V., H.T. 230 v. 270 ma., 21/-. SENTERCEL E.H.T. RECTIFIERS K3/100, 8 kV, 1 ma., 14/8; K3/50, 1 kV, 1 ma., 8/8; K3/45, 3/6 kV, 1 ma., 8/2; K3/40 3.2 kV, 1 ma., 7/6; K3/25, 650 v., 1 ma., 5/6.

MANUFACTURERS' SURPLUS E.H.T. Transf. 4 kV, with Rect. U22 mounted on panel, complete unit, 39/6.

TRANSFORMER FOR OSCILLOSCOPE.—800 v. 150 ma., 5 v. 2 a., 5 v. 2 a., 4 v. 1 a. Primary 230 v. 50 cps.

RADIO TRANSFORMERS.—Tapped, primaries, 275-0-275 6 v. 3 a., 6 v. 1 a., 60 ma., 10/6; ditto, 250-0-250 6 v. 3 a., 4 v. 1 a., 80 ma., 12/6; ditto, 250-0-250 v. 63 ma. 6 v. 3 a., 4 v. 2a., complete with MU14 Rect. on panel, 27/6.

KNOB'S, GOLD ENGRAVED.—Walnut, or Ivory 1 1/2in. diam., 1/6 each. "Focus," "Contrast," "Brilliance," "Brilliance—On-Off," "On-Off," "Volume," "Vol.—On-Off," "Tone," "Tuning," "Trebble," "Bass," "Wavechange," "Radio-Gram," "S. M. L. Gram," "Record-Play," "Brightness," ditto. "Plain," 1/- each.

ALL-DRY BATTERY PLUGS or sockets. 2, 3 or 4 pin, 5d. ea. Wander plugs, 3d. ea.

TAG STRIPS.—1 and 2 tags. 3d., 3 or 4, 4d.; 5 or 7, 6d., etc. 28 way, 1/3.

SLEEPING.—Various colours. 1, 2, 3 mm. 4d. yd.; 5 and 6 mm. 6d. yd.

RESISTORS.—All values. 4 w., 4d.; 1 w., 6d.; 1/2 w., 8d.; 2 w., 1/-.

NEW BOXED SURPLUS VALVES ALL GUARANTEED SPECIAL SALE PRICES

Table listing various vacuum tube valves with their specifications and prices. Columns include valve type (e.g., 1A5, 1R5, 1S5), price, and other details.

SPECIAL PRICE PER SET: 1R5, 1T4, 1S5 and 381 ... 32/6. 1K5, 6K7, 6U7, 6X8, 3Z4 ... 40/-. 10EP91 Unit. Television A.C. D.C. TV. ... 85/-.

VIEWMASTER.—Set 12 valves, £8 10/0, with EY01, 47. TELEKING.—Set 17 Valves £9 10/-.

BRAND NEW RADIOGRAM CHASSIS.—5 v. Superhot, L. M. & S.W. 8 gram. piston. All Mains, 200-250 v. 12 I sockets. Large, easy viewing dial, 4 1/2in. x 4 1/2in. Latest Mullard valves. Chassis size, 13 1/2in. x 5 1/2in. x 2in. 4 front controls and knobs. Requires only P.M. Speaker. Fully guaranteed. Special offer, £9/5/0, carr. and packing, 3/6.

ALL VIEWMASTER and TELEKING Components in stock

Table listing components for Viewmaster and Teleking sets, including Allen Angle Components, Chassis, Coils, and various electronic parts with their retail prices.

Table listing ION ANGLE P.M. FOCUS RINGS for use with 14in. to 17in. Ion Traps, including W.22, W.20, W.25, and Bernard's Teleking envelope.

MISCELLANEOUS HARDWARE Pilot lampholders, clip on, 8d. ea. Dial bulbs, 6.3 v. 3 a., round 9d. (tubular 1/-, 12 v. 2 a., 1/- ea. Crocodile clips, 4d. ea. Bolin Panel Indicator Lamps, Red, 2/6. P.V.C. twin mains flex, 5d. yd. 2 Pin 5 amp. plug tops. 8d. Nuts or Bolts, 2, 4, 6, 8d. Joz. Brass Spindle Couplings, 8d.; extenders, 2in., 9d. M'cure Solder 16g 60/40, 4d. yd., 10/6 lb. Tinned Copper Wire, 18g-22g, 2d. yd. P.V.C. Connecting Wire, all colours, stranded or single, 2d. yd. Met. Rect., 280 v., 90 ma., 9/- 2 v. Exide Acc. 10 AH, 4/9. Aladdin lamps, and cores, 1 1/2in. diam., 8d., 1 1/2in. diam., 10d. Mains Drimmers, adjustable sliders, 3 amp. 300 ohms, 5/-; 2 amp. 1,000 ohms, 5/-. Toggle Switches, "On-Off" 2/6, ditto ex. Gov. "On-Off", D.P., 9d. Fuse, all values, 60ms. to 15 a., 1/6. .0005 and .0003 mfd. Reaction Condensers, 3/6. Midget H.F. chokes, dust cored, 14 M.H., 2/6. Tele Tube Masks, 9in., cream finish, 11/-; 12in., 19/6. R.F. E.H.T. Units 5 to 7 kV, £5 19 6; 7 to 12 kV, £9 9 6. Brinistors, C/21 for 3 amp. heater chains, 3/6; C/22 for .15 amp. or 2 amp., 2/6.

COPPER ENAMEL WIRE 1 lb. REELS 14 to 20 s.w.g., 2/9; 22 to 25 s.w.g., 3/-; 30 to 40 s.w.g., 3/9.

VOLUME CONTROLS Midget Ediswan type. Long spindles. Guaranteed 1 year. LESS Sw. S.P. Sw. D.P.Sw. 3/- 4/- 4/9 ALL VALUES.—10K. to 2 MEG.

TRANSFORMERS Made in our own Workshops to Top Grade specification. Interleaved and impregnated. P.P. O/P Trans. to spec. from 15/6. Quality ditto, Stalloy Lamin. and low leakage windings from 35/-, Williamson Mains Transformer, 57/6. Heater Transformer prin., 6.3 v. 14 amp., 7/6. 350-0-350, 80 ma., 6.3 v. 4 a., 5 v. 2 a., ditto 300-0-300 ditto 250-0-250, 21/-, Viewmaster Mains Transformer, latest type, 35/-.

P. & P. 1/- extra on Transformers. Quotations for specials and rewinds per return.

O/P TRANS.—Small tapped Pentode 3.9. Heavy Duty, 70 ma., 4.6; Dito tapped, 4/9. L.F. Chokes 10 H., 65 ma., 4/6; 20 H. 150 ma., 12/6; 5 H., 250 ma., 15/-.

VALVEHOLDERS Int. Oct. moulded, 6d.; Paxolin, 4d.; Mazda Oct. moulded, 6d.; EP50, BTG, 9d.; B8A, B9A, etc., 1/-; UX types, 9d. Tube Holders, Duotek B12A, 1/3. Valve plugs, Int. Octal, Mazda Oct. UX 1, 2/- ea.; BTG Holders and Screening Caps, 1/6. Screened Valve top cap Octal or Eng., 8d.

WIRE-WOUND RESISTORS.—Best makes Miniature Ceramic Type.—5 w., 12 ohm to 4 K., 1/9; 10 w., 20 ohm to 6 K., 2/3; 15 w., 30 ohm to 10 K., 2/9; 5 w. Vitreous, 12 K. to 25 K., 3/-.

W/W POTS.—T/V Type Pre-Set. Miniature. Fitted knob is knurled and slotted. 25, 50, 100, 200, 500 ohm, 1 K., 2 K., 2.5 K., 3 K., 10 K., 15 K., 20 K., 30 K., each 3/6. 10 K. Colvern, lin. spindle, 2/6. 2 K. Heavy Duty, 3 watt, lin. spindle, 4/6.

COILS.—All ranges Wearite "P" 3/-, Osamor Midget "Q", 4/- each.

ELECTROLYTICS.—New stock. 8/450 v. B.E.C. Midget Tub. 2/6. 8/500 v. Dubilier Drilite Tub, 3/-. 16/450 v. B.E.C. Med. Can. 3/-. 16/450 v. T.C.C. Small Can, 3/6. 16/500 v. Dubilier Tub, 3/-. 16/500 v. B.E.C. Drilite Tub, 4/-. 8/- 8/450 v. B.E.C. Small Tub, 4/-. 8/- 8/500 v. Dubilier Small Can, 4/6. 8/- 16/450 v. B.E.C. Midget Tub, 5/-. 8/- 16/500 v. Dubilier Small Can, 5/6. 16/- 16/450 v. B.E.C. Med. Can, 4/-. 32/500 v. Dubilier Drilite Tub, 5/-. 25/25 v. B.E.C. Tub, 1/9. Dito 50/50 v. 2/-; 60 mfd. 350 v. T.C.C., 6/6; 250 mfd. 350 v. B.E.C., 8/6.

CONDENSERS.—New stock, best makes. .01 mfd. 6 K., TCC, 5/6; ditto, 12 K., 9/8; 15 K., 10/-; .002 mfd., 8 K., Muirhead, 2/6; all values 2pf. to 500pf., 6d. .001 mfd., 6d.; .001, .002, .005, .01, .02 450 v. tub. and 1 mfd., 350 v., 8d.; .05, 1, 450 v., 1/-; .25, .5, 450 v., 1/9; .01 Sprague 1,000 v. short ends, 5d.

TRIMMERS. Ceramic. 35, 50, 70, pf., 9d., 100pf., 1/3. 250 pf., 1/6. 600pf., 1/8.

LOUDSPEAKERS P.M., 3 OHM. 9in. Lectra, 13/6. 6in. Plessey, 14/6. 9in. Plessey, 15/6. 10in. Plessey, 25/-.

T.R.S. Bargain Lists, 3d.

307, WHITEHORSE ROAD, WEST CROYDON. Telephone: THORnton Heath 1665. Mail Order: 71, Meadvale Road, East Croydon. Terms C.W.O. or C.O.D. Over £1 post free. P. & P. 6d. extra.

On your Wavelength

By THERMION

The W.F.S.R.A. Again

In the February issue I dealt with the aims and objects of the World Friendly Society of Radio Amateurs. I did so at the express invitation of readers who wished to know more about it as a result of the publication in this journal of a notice concerning the "Bedfast" section of this society. I fairly summarised all of the information I have been able to obtain. Re-reading the article I do not think any reasonable person could take exception to what I had to say. Mr. F. Allan Herridge, however, the S.E. Regional representative, has sent me a letter of protest at the tone of my comment. He says that he has been a member for two and a half years and can, therefore, speak from personal experience entitling him to answer some of my comments. He says that my "biggest *faux pas* is the contention that the society can do nothing to further the objects of world friendship. I would stoutly maintain that each and everyone of us as individuals can do much towards this end. It should be obvious that world wars are caused mainly through ignorance of the other fellow and his way of life. Through our correspondence, our contacts over the air, and through personal contact, we can learn of our fellow amateurs overseas and they become friends to us. To my knowledge we have members in 18 countries."

According to the secretary the membership to date, after 17 years, is 142—not a very large band of Gallahads to crusade throughout the world, to promote world friendship. However laudable that object may be, it certainly did not prevent the last war and as far as I have been able to trace it has made no impact at all on the one country which is disturbing world peace, namely Russia. How many members has the W.F.S.R.A. in Russia? Am I not right in saying that no one in Russia to-day would be permitted to own an amateur radio station except as a member of the Ogpu?

I said last month that the promotion of world friendship is a political issue best left in the hands of politicians. Their efforts towards world friendship through UNO and NATO are well known. They could be seriously hampered in their efforts, which are backed by their respective governments, by any society which is not nationally recognised.

Regarding the society service scheme, the reader informs me that this is a newly formed section, hence its limited coverage. It is composed, says he, of members who give their services voluntarily, which, he thinks, is a rare phenomenon nowadays. It is not rare. There are literally thousands of societies in this country, working for the good of others in one way or another, whose services are voluntary. My critic seems hurt because I dismiss their Bedfast Club in one short sentence. He tells me that "this is one of the most valuable and appreciated of the society's services. Any amateur bed-ridden, disabled, or otherwise unable to follow his hobby is made a member free and can receive letters through the Pen-Pal section, books and magazines." It will be interest-

ing, therefore, to know how many honorary members have been created under this scheme. Out of a total membership of 142 would I be incorrect in saying that it is about a dozen?

The unsettled state of the world is not likely to be rectified in this way, especially as the dissident nations are ruled by dictators where democratic government, likely to be affected by public opinion, is unknown.

I was taken to task for referring to the society as a club. It is a distinction without a difference, for the terms are synonymous. My critic tells me that notices of the society have been published in a contemporary and one notice has appeared in the official journal of the R.S.G.B.

Newcomer in the Record Field

I AM very interested to note that the famous firm of Philips has now entered the gramophone record field and records bearing their famous name are now on sale. Well-known artistes are making recordings for them. The company will have under exclusive recording contracts such famous British artistes as Gracie Fields, Flanagan and Allen, David Hughes, Gary Miller, Jean Carson and Johnny Brandon. Various musical directors will be used and the first issue contains the names, Norman Warren, Geoff Love, Bruce Campbell, Geraldo and Peter Yorke. They are not exclusively employing any musical directors as the company intends to promote a policy of experimenting in the arranging field and building up names to world prominence. The gramophone recording field has been a closed corporation for many years, especially to those with musical qualifications every bit as good as those who are recorded, but who cannot even get an audition. If a gramophone war is to start it can only be to the benefit of the purchaser. The Philips policy will enable unknown people to achieve fame. They intend to build up British personalities for world exploitation. Recording is to be undertaken for the time being by Universal Programmes Corporation, of Portland Place, and recording will be at Portland Place and Conway Hall.

Education for Technicians

I CONGRATULATE E.M.I. Engineering Development, Ltd., who, at their factory in Wells, Somerset, in co-operation with E.M.I. Institutes, have inaugurated a new approach to the further education of industrial technicians and junior technologists. All employees over the age of entry to the normal apprenticeship and part-time day release scheme have been given the opportunity to further their technical knowledge and obtain professional qualifications. The employees enter for a special, self-educational home study course of training under the supervision of a tutor who makes regular weekly visits to give individual and class tuition during working hours. Periodic tests are given as in a school or college and progress reports are made out for each student. The courses are run over the usual academic session from September to June.

A Midget 12-watt Amateur Station

A COMPACT, COMPLETE TRANSMITTER AND RECEIVER

By T. W. Dresser

RADIO, in any of its varied forms, still remains probably one of the most interesting and one of the least costly of hobbies even today, and it is a pity that many enthusiasts are prevented, either by the present-day cost of transmitting gear or lack of accommodation to install the equipment, from following their pastime in their leisure hours as they would like to do. And certainly rack-built transmitters, commercial communication receivers and the equally important keying desk call for a good deal of space in themselves without considering the extras.

I enlisted the aid of a friend, and working in his shack evolved a complete twelve-watt station which even the family could not object to on the score of size and which adequately fulfilled my desire to get on the air again. Fig. 1 shows the diagram of the station.

It will be obvious from a glance at the schematics that the "rig" devised, which consists of a 12-watt transmitter and a miniature superhet receiver, cannot possibly be the ultimate of its type, but it is efficient, extremely easy to construct—it can be finished in an evening with the aid of a few simple

tools—it is ideal for the beginner and it also fulfils the purpose of the fellow who needs a stand-by rig. Its very compactness has a considerable measure of attractiveness after working large, rack-built transmitters, and, as any amateur will agree, plenty of DX work can be got with 12 watts C.W. In addition it has the advantage that it does not require elaborate apparatus with which to tune it before putting it on the air—a loop of wire and a flashlamp bulb are all that are necessary—nor does it require anything special in aerials. Any old length of wire at any height will serve the purpose although, of course, the higher the better.

Circuit

The transmitter consists of a crystal-controlled 6V6 pentode oscillator working directly into the aerial, while the receiver is a two-valve superhet using a 6K8 as mixer-oscillator and a 6SN7 functioning as second detector and output stage. That half of the 6SN7 which operates as the output stage is arranged to feed either a 2½ in. speaker, permanent-magnet type, or a pair of headphones as desired, by means of a phone jack in the anode circuit of the valve and the complete station—xmitr and receiver—is built on an aluminium chassis 8 in. × 5 in. × 2½ in. deep with a front panel 8 in. × 7 in. high of 16 s.w.g. sheet aluminium. Mounted on the chassis are the mains transformer, metal rectifier, electrolytic condensers, all valves, transmitter tank coil, crystal holder and receiver coils and tuning condenser. Below the chassis are mounted all other components, including the smoothing choke which should be of the

smallest possible physical dimensions consistent with good performance. A similar requirement also applies to the mains transformers; that used by the writer measures 3 in. × 3 in. × 2 in. and was purchased from Davis & Vallance, of Leeds, two or three years ago, although there should be no difficulty in getting similar transformers, or smaller ones, from a number of sources today. The primary winding should be the usual tapped 200-250-volt winding and two secondary windings are needed; one for 6.3 volts at 1.25 amps, and the other a half-wave winding to give 250 volts at 70 mA, for H.T. Naturally this will not be centre tapped.

Aerial

In the anode circuit of the transmitting valve a "pi" network is used to make it possible to load almost any aerial, and eliminating the need to cut wires to specific lengths. Thus, providing it is not grounded or presents a danger to human life, any length of wire slung up roughly will enable you to radiate a respectable signal. This, incidentally, makes the gear very useful for "field

day" operations, provided a little "wangling" is done with the power supplies.

The transmitter is intended only for use on 40 and 80 metres and coil data for both transmitter and receiver is given only for these bands on page 137 but it should be a simple matter to compute coils for the 20-metre band if they are required. Bandchanging, of course, is a simple matter merely involving changing the transmitting coil and crystal, and can be accomplished in a few seconds.

Receiver

While the receiver is a straightforward superhet, more or less reduced to essentials, it gives a surprisingly good performance even in conditions of bad QRM. The standard mixer-oscillator stage feeds into the second detector, one half of a 6SN7, which is fixed-tuned to an approximate frequency of 1,600 kc/s. Reaction is applied to the second detector to increase sensitivity, and this stage is then transformer coupled to the output stage, the other half of the 6SN7, and thence to the speaker or phones. Bandsread tuning on the oscillator is obtained by means of a small trimmer condenser paralleled across the main oscillator tuning condenser, and once the mixer grid tuning condenser has been adjusted to peak signal on the band it can be forgotten and any further adjustments made with the bandsread trimmer. To all intents and purposes this makes the receiver a one-knob affair.

All coils are home made, but a commercial 1,600 kc/s I.F. transformer can be bought and the secondary

Readers are reminded that it is illegal to install or operate wireless telegraphy equipment, except under the conditions of the licence issued for that purpose by the P.M.G. Full details of this may be obtained from The Engineer-in-Chief, Radio Section, G.P.O., London, E.C.4.

adjusted for use as the regeneration coil if the constructor wishes.

The chassis is wired up just like any other radio job, carefully, with short and direct connections and good, sound-soldered joints. There are no peculiarities or snags to anticipate, but the R.F. chokes in the trans-

lator tuning and handsread condensers. When a signal has been found it should be brought up to its peak by means of the grid tuning condenser. That and the main oscillator tuning condenser can then be ignored and only the handsread condenser used while you remain on that band.

Tuning the transmitter is even simpler, if that is possible. With the aerial connected and the send-receive switch in the send position, turn the condenser C8 to maximum and then rotate the tank tuning condenser C7 until oscillation occurs. A flashlamp wired into a single wire loop, as in Fig. 2, and held fairly close to the 6V6 will light up when the transmitter is oscillating. The next step is to ensure the maximum transfer of energy from the tank circuit into the aerial. This is done by reducing C8 in small steps, re-tuning C7 each time to retain resonance, and continuing the process until the lamp is at its dimmest. The assistance of another amateur in the district reporting as you go along would help considerably here, or listening on a spare receiver to a harmonic while the transmitter is being keyed would give a good idea of the strength of the radiated signal.

As much depends upon the coupling it is advisable to take some care with this proceeding. If the coupling is too tight the oscillator may behave

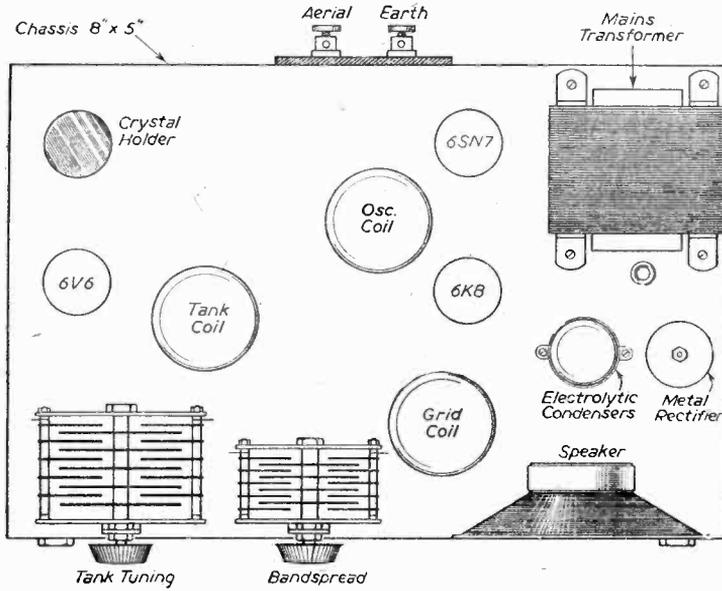


Fig. 3.—Above chassis layout.

mitter grid and anode circuits should not be identical in order that parasites of the T.P.T.G. type should not be set up. Different makes will suffice to clear this possibility.

Testing

Once the receiver and transmitter have been assembled and wired in accordance with the diagrams they should be checked over to ensure that the wiring is correct and all joints are electrically sound, and then the set can be put through its tests.

The procedure is quite simple. Starting with the receiver, attach an aerial, switch the send-receive switch to receive, and advance the reaction control until a slight plop is heard in the speaker or 'phones, just as you would do with a T.R.F. receiver. If no plop is heard, re-check the wiring, and if it is in order add a few turns to the reaction winding. Before doing so, however, try reversing the connections to the reaction coil.

When this stage is operating correctly the mixer stage can be tuned. It should be an easy matter to locate a signal in the band by adjustment of the oscil-

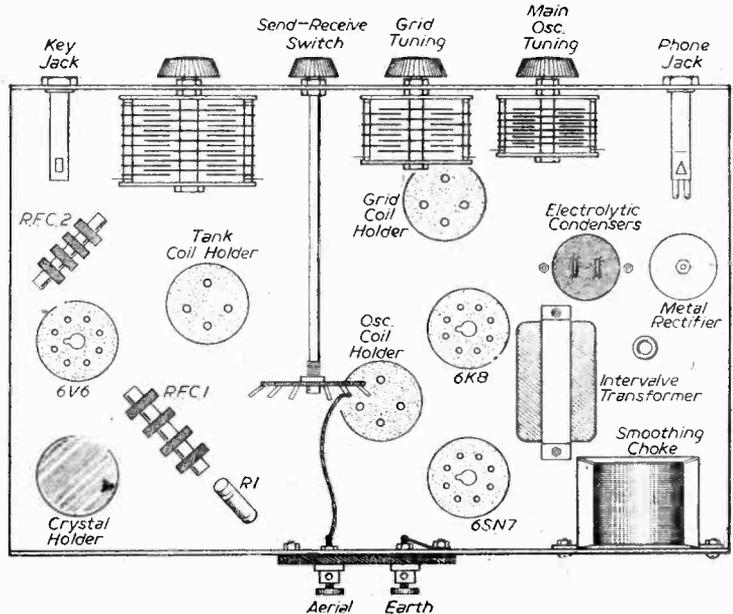


Fig. 4.—Below chassis layout.

erratically or even refuse to oscillate at all due to heavy damping; and, on the other hand, if the coupling is too loose there will be an inadequate transfer of energy from the tank coil into the aerial and consequently a weak signal radiated.

An alternative method of checking oscillation is to wire a 100 mA. meter to the key plug and insert it into the key jack. When the 6V6 has warmed up, with C8 at maximum as before, rotate C7 until the meter reading commences to drop. The point

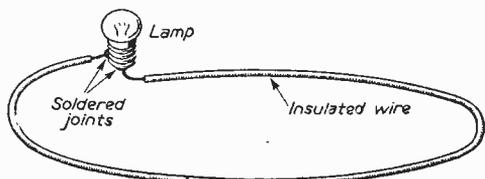


Fig. 2.—Simple oscillation tester.

of minimum current, or dip point is, of course, also the tune point, and should occur between 40 and 50 mA. with the 6V6.

In Figs. 3 and 4 are shown the top layout of the set and the below chassis layout respectively, and as many of the components, such as tuning condensers, ceramic switch, valveholders and metal rectifier are still obtainable at surplus dealers, and the coils are home-wound, the cost of building the station can be

very cheap, in proportion to the pleasure that will be secured from it.

In conclusion, while this little outfit cannot be expected to compete with the 100-watters and the American kilowatters, it will certainly provide many

TRANSMITTER COILS (L1)					
Band	Turns	Wire	Wound single layer on 1 1/4 in. ribbed former (4-pin base)		
80metres	35	22 DCC			
40metres	17	22 DCC	Wound single layer on 1 1/4 in. ribbed former (4-pin base)		
Receiver I.F. coil.		32 s.w.g. enamel wire, close wound on 1/2 in. former			
L6 48 turns, L7 21 turns.					
Receiver coils.	Grid		Oscillator		
80-metre band	L2 10 turns	L3 36T	L4 19 turns	L5 9 turns	
40-metre band	L2 8 turns	L3 18T	L4 15 turns	L5 7 turns	
All coil formers, except I.F., 4-pin plug-in type.					

pleasant DX contacts and many hours of fun. Moreover, it is small enough to put by the bedside for that last QSO before you fall asleep, if you wish, without calling down upon your head rude remarks about messing up the room.

Radio Road Patrols

THE Automobile Association recently announced the introduction in the London area of the first stage of a national radio network designed to provide continuous two-way verbal communication between A.A. Patrols and their local headquarters throughout the country. The object is to ensure prompt help for motorists and motor-cyclists whenever a breakdown occurs on the road. All they will then need to do is to telephone the nearest A.A. office, who will at once direct a patrol to their assistance.

The Radio Patrols are a logical extension of the Association's radio-controlled Night Breakdown Services which have been operating in London, Birmingham and Leeds for some time and which now assist over 20,000 motorists in a year. The advantages of radio control will now be available to motorists in the London area throughout the 24 hours.

Initially the new service will cover a radius of approximately 20 miles from Fanum House, the the Association's London headquarters. This area has been divided into six zones, in each of which patrols with equipment for carrying out roadside emergency repairs will operate daily from 9 a.m. until 6 p.m.

Garage Links

The intention is to concentrate on the main London approaches and exits, although the flexibility offered by radio control will enable the patrols to be directed from point to point as need be. In this way they will supplement the existing A.A. Free Breakdown Service operated through garages. Some

London garages which take part in the Breakdown Service already have their vehicles linked with the A.A. radio network.

The first explorations into the use of radio for the control of A.A. Road Service were made before the war, but recent technical developments in this field have given an impetus to the experiments, and it has now been possible to evolve a sufficiently light and compact very high-frequency installation to be carried in the side-car boxes of the A.A. motor-cycle Road Service Outfits and to obtain efficient reception over a considerable range. The scheme now launched in London is regarded as the first full-scale operational experiment, and plans have already been made for extending the service, stage by stage, so that it will eventually cover all parts of the country where the demand is sufficient to justify it.

Further Transmitters

Sites have been surveyed for further transmitting stations to give local A.A. offices radio control over the men in the surrounding areas. It is hoped to establish the first of these in the vicinity of Guildford. Tests have shown that the range obtainable will probably be sufficient to operate the scheme throughout Surrey, in Sussex and Hampshire as far as the coast, and also north-westwards into parts of Buckinghamshire and Berkshire.

In addition to providing assured help for motorists in cases of mechanical and other troubles, the Radio Patrols will greatly increase the Association's ability to give road service in various ways; for example, in dealing with traffic congestion, providing help in accidents and other emergencies, and particularly in obtaining rapid reports of changing conditions when roads are affected by fog, snow, ice or floods.

Contact Operation and Maintenance

THE PROTECTION OF CONTACTS AGAINST ARCING AND INTERFERENCE GENERATION

By D. E. S. Isle

THE majority of radio and television interference may be traced to the operation of current-carrying contacts. If a little attention be paid to every contact in a system during maintenance schedules, then a major source of trouble will be eliminated.

In all fields of electrical and electronic engineering, contacts are called upon to perform their duties repeatedly, open to the atmosphere or to the gaseous products of processing plant.

In considering the circuit conditions which pertain to a reasonable length of life for such contacts, whether or not the current carried be high, we must not assume that any contact material is perfect, for indeed it is not, and it is only by careful maintenance and attention to circuit design that the worst conditions do not prevail.

When a circuit is broken by means of a pair of contacts, several separate conditions make themselves shown.

First, many circuits tend to exhibit a property analogous to inertia, the immediate result of this being a spark of continuous arc between the contacts, until the contact points or faces are too far apart for the ionisation of the air gaps to support the continuance of a current flow. Two different characteristics are shown by the use of contacts in A.C. and in D.C. circuits. The A.C. circuit is easier in some respects to control, in view of the fact that the voltage (for a 50-cycle supply) falls to zero every half-cycle, i.e., 10 milli-seconds. The D.C. circuit, of course, does not exhibit this feature, and thus it is with D.C. supplies and their control that we are mainly concerned.

Secondly, as a direct result of the above spark or arcing, a small quantity of the gas ozone is liberated between the contacts. Ozone is one of the most powerful oxidising agents known, as immediately on formation it breaks up into oxygen and nascent oxygen as follows:



It is the nascent monatomic oxygen which causes the main contact deterioration, uniting as it does with the nearest available material which can be oxidised. Most metallic oxides are non-conductors, or semi-conductors, and it is the deposit of these materials which causes the majority of contact failures.

Thirdly, as a result of the heat generated by the arc taking place, there may be actual physical disintegration of the contact material, both at the surface and at the joint between the contact material and base material. This results in a contact face which is pitted and cratered, so that when the contacts remake the current rating per unit area is raised by a large factor, producing undesirable resistance and therefore reheating of the contacts. The current rating should not be higher than 100 amperes per sq. in. of contact area.

It may be seen from the above that, provided one uses conventional and well-chosen contact materials, the source of the trouble lies in the circuitry and the

surges which appear across the contacts. Where the current is of a very low order, the above arc characteristics do not take place unless the circuit is highly inductive, but normal oxidation does. This is overcome usually by arranging the contacts to "wipe" on making and breaking, thus giving a small measure of self-cleaning action.

The main source of trouble is therefore met in contacts carrying an appreciable current. These may be sub-divided into two classes, viz., power contactors and control relays.

Power Contactors

The problem here, especially with direct current, is to extinguish the arc at the contacts as soon as possible after its formation. The contacts usually are built up from copper laminations which make on to a plain copper block. Three methods are used, in conjunction, only when the current loading is very heavy.

(a) Magnetic Blow-out:

This consists of using the field of a permanent or electro-magnet to extinguish the arc by the mutual repulsion of the field of the magnet and of the arc itself.

(b) Mechanically-assisted Release:

There are many types of assisted release of the contactor armature, a common form being a manually-set triggering device which releases the armature under the action of a heavy spring.

(c) Immersion of the Contacts:

In order to improve the immediate insulation value of the gap between the contacts on releasing, the whole of the contact assembly may be immersed in insulating oil or in a similar liquid which has been manufactured specially for its insulating properties.

When all the above methods are applied it may be safely stated that no undue deterioration of the contacts will occur.

Control Relays

Different methods must be used for the protection of contacts in control relay work. These methods differ with the size of the relay in question and, indeed, where the size of the relay is large it is often wise to try and incorporate one or other of the methods employed for power contactors.

The spark at the contacts of a relay varies in intensity with the variables of the circuit in which the said contacts are used. Where the load to be switched is mainly inductive, there is far more necessity for the insertion of a spark-quenching device. Where the load is mainly resistive, the spark will be of lesser intensity. A mainly capacitive load is not often encountered, but where this is so, the circuit should be treated as for inductive loads.

The method is to absorb, as far as is possible, the oscillatory potential across the contact points. This is best accomplished by means of a capacitor

(Concluded on page 173)

Great Britain's Valve Mail-Order House

RADIO BULLS VALVES
246, HIGH ST., HARLESDEAN NW11



CONDENSER TESTERS & RECTIFIER UNITS

Plugs straight into A.C. mains. 200-240 v., and is indispensable for examination of condensers. Very slight and intermittent leakages which cannot be discovered by conventional instruments can be traced by this unit. Complete. Supplies are becoming limited.
Post 1/6 **39/6**

SOME OF OUR VALVE BARGAINS

- IC6 3/-
 - KT241 4/-
 - 6AB7 5/-
 - 215SG 6/-
 - Pm22c 7/-
 - Px25 15/-
- Post 6d.

A.C. D.C. NEON TESTER TYPE 400

This new model is specially designed for one-pole tests on mains, incorporating a highly sensitive neon tube—striking voltage 100 500 v. A.C./D.C. Also suitable for indicating polarity on D.C. current, when the glow of the lower electrode will indicate the negative pole.
Post 9d. **11/3**

AMERICAN Electric British made A.C. PAINT STRIPPER

Just plug in and spray. Easier than a brush and twice as fast.
Tax free **75/-**
Post 2-

JEWEL (SAPPHIRE mounted). Suits any type of Pick-up or Record. Improves quality, eliminates record wear. 3 Types: Loud, Soft and Trailer.
3 for 10/- or **3/6** each



"WONDER" HAND TOOL 6 TOOLS IN ONE

Plus 1/6 post and pkg. (reduced from 20/-). Punches, Bends and Shears Metal Strip, Rod and Angle. Very Handyman, Mechanic and Service Engineer needs one!
Thousands used! Unique! Order TO-DAY



ELECTRIC ENGRAVER

For all metals, plastics, etc. Plugs into A.C. light socket. Powerful.
Post 1/- **15/-**



HOME BROADCASTER

Connects to radio or gram. Talk over your own radio, room to room. Easy to fix. Two makes make 2 station house phone in your own home. Order to-day.
Post 16. **12/6**



High-power super-heat flame PERFECT for Light Brazing

Tempering, Hard Soldering, Silver Solder, Tinning, Sweating, etc. Fits into ordinary Gas Tubing. No extra air pressure. Full instructions. **2/6** 6d.



CONDENSERS Wire Ends

2 m/d 450 v.	2-	BRAND	8 8 m/d 500 v.	2 6
4 .. 450 v.	2 6	NEW	8 16 .. 500 v.	4 9
8 .. 500 v.	2 6		16 16 .. 500 v.	5 9
16 .. 500 v.	2 9	GUARD.	16 21 .. 350 v.	5 9
25 .. 25 v.	1 3		16 32 .. 275 v.	6 6
50 .. 50 v.	2-		16 m/d. Govt. Surplus 175 v. each 1/-	


Post 6d.

CANS

CV 21	CV 511	CV 55A	CV 608	CV 659	CV 758
.. 26	.. 522	.. 591	.. 609	.. 665	.. 773
.. 32	.. 523	.. 571	.. 613	.. 692	.. 781
.. 65	.. 525	.. 573	.. 614	.. 694	.. 782
.. 74	.. 529	.. 575	.. 615	.. 697	.. 783
.. 118	.. 531	.. 563	.. 616	.. 700	.. 781
.. 124	.. 534	.. 585	.. 619	.. 703	.. 785
.. 133	.. 538	.. 588	.. 621	.. 706	.. 788
.. 138	.. 543	.. 591	.. 625	.. 711	.. 815
.. 141	.. 545	.. 596	.. 640	.. 728	.. 822
.. 216	.. 549	.. 605	.. 619	.. 730	.. 845
.. 390	.. 552			.. 731	.. 818
.. 500	.. 554			.. 747	.. 851
.. 504	.. 555			.. 759	

CV 856	CV 938	CV 1057	CV 1137
.. 858	.. 945	.. 1059	.. 1108
.. 862	.. 947	.. 1060	.. 1109
.. 873	.. 949	.. 1064	.. 1110
.. 877	.. 1023	.. 1069	.. 1113
.. 885	.. 1027	.. 1073	.. 1118
.. 887	.. 1035	.. 1075	.. 1123
.. 895	.. 1037	.. 1078	.. 1127
.. 901	.. 1052	.. 1091	.. 1129
.. 916	.. 1053	.. 1092	.. 1130
.. 922	.. 1054	.. 1095	.. 1169
.. 924	.. 1055	.. 1190	.. 1189
.. 931	.. 1056	.. 1106	.. 1189

CV 1189	CV 1336	CV 1819	CV 1934
.. 1191	.. 1341	.. 1851	.. 1937
.. 1195	.. 1350	.. 1851	.. 1939
.. 1281	.. 1401	.. 1861	.. 1912
.. 1287	.. 1419	.. 1861	.. 1912
.. 1296	.. 1432	.. 1861	.. 1943
.. 1300	.. 1433	.. 1861	.. 1945
.. 1306	.. 1456	.. 1861	.. 1949
.. 1308	.. 1457	.. 1861	.. 2511
.. 1320	.. 1463	.. 1861	.. 2511
.. 1323	.. 1752	.. 1866	.. 2511
.. 1327	.. 1755	.. 1890	.. 2543
.. 1331	.. 1769	.. 1925	.. 2556
.. 1335	.. 1817	.. 1921	.. 2557

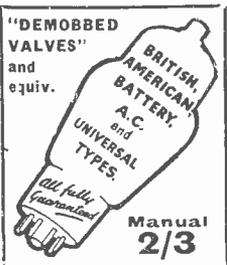

Radio valve application Manual	5/-	B	Radio Data Charts	7/6
Constructors Manual	5/-	O	T.V. Servicing	4/6
Designs Manual	2 6	O	Radio and T.V. Laboratory	3/6
Midget Construction	3 6	O	T.V. Interference	2/-
Practical Beginner	3 -	K	T.V. Fault Finding	5/-
40 Germanium Diode Circuits	3/-	S		

Radio valve application Manual

Radio Data Charts

SOLDERING IRON
● The Perfect Small Soldering Iron.
● Adjustable Bit. ● Easy to Handle.
● Weight approx. 4oz. ● Heating Time 3 min. ● 40 watt Economy Consumption.
● Voltage Ranges 100 110 v., 200 220 v., 230 250 v., other ratings available on request. ● Long life and Efficiency. ● Replacement Elements and Bits always available. Just the convenient Iron required for intricate and fine soldering.
16/9

SERVICE SHEETS
The one you require enclosed if available in a dozen assorted of our best choice.
10/6

Electric PAINT STRIPPER

A.C. and D.C. SAFE... puts the heat just where it's wanted—no where else. **CLEAN** no fumes—no messy films up. **EASY**... a little practice and you're expert. **ECONOMICAL**... runs for 8 hours for 3d. List 47 6. Q.T.R. Post 1 3. PRICE **37/6**

PAINT SPRAYER

foreasyspraying any liquid or paint. Gives fine finish to your car, bike, furniture, etc. Makes every man a Handyman.
Post 9d. **15/6**

PIFCO

All-in-one Radiometer A.C. D.C. Tests everything in Radio. Complete with Test prods.
Post 1 6. **29/6**

TAYLOR Montrose 7-range Multi-meters, A.C. D.C.

3 amp precision M.M. movement. 0-6-30-150-300 volt. 0-30 mA.—300 mA. **50/-** Post free



Universal Minor £10. Model 7 and 40 Avometers, £19. Electronic Testmeter, £40. AVO model 8 in stock, £23.

RADIO BULLS VALVES
246, HIGH ST., HARLESDEAN NW11

(Kindly mark envelope PW3).

COPPER INSTRUMENT WIRE (ex-stock)

	ENAMELLED		TINNED		COTTON COVERED		SILK COVERED	
	2 ozs.	4 ozs.	2 ozs.	4 ozs.	2 ozs.	4 ozs.	2 ozs.	4 ozs.
SWG Inch								
16 .064	1/4	2/-	1/4	2/-	1/4	2/-	1/4	2/-
17 .056	1/4	2/1	1/4	2/1	1/4	2/1	1/4	2/1
18 .048	1/4	2/2	1/4	2/2	1/4	2/2	1/4	2/2
19 .040	1/4	2/3	—	—	1/5	2/3	1/6	2/5
20 .036	1/5	2/4	—	—	1/5	2/4	1/7	2/8
21 .032	1/5	2/5	1/6	2/5	1/5	2/5	1/8	2/10
22 .028	1/6	2/6	1/6	2/6	1/6	2/6	1/9	3/-
23 .024	1/7	2/7	1/7	2/7	1/7	2/7	1/10	3/2
24 .022	1/7	2/8	1/7	2/8	1/7	2/8	1/10	3/2
25 .020	1/8	2/9	1/8	2/9	1/8	2/9	1/11	3/4
26 .018	1/8	2/10	1/8	2/10	1/9	2/11	2/-	3/6
27 .0164	1/9	2/11	1/9	2/11	1/10	3/1	2/1	3/8
28 .0148	1/9	3/-	1/9	3/-	1/10	3/2	2/2	3/10
29 .0136	1/10	3/1	1/10	3/1	1/11	3/4	2/3	4/-
30 .0124	1/10	3/2	1/11	3/5	2/-	3/6	2/4	4/2
31 .0116	1/11	3/3	2/-	3/6	2/1	3/7	2/5	4/4
32 .0108	1/11	3/4	2/1	3/8	2/1	3/8	2/7	4/8
33 .010	2/-	3/5	2/2	3/10	2/3	3/11	2/10	5/2
34 .0092	2/-	3/6	2/3	4/-	2/4	4/2	2/11	5/4
35 .0084	2/1	3/7	2/4	4/2	2/6	4/5	3/1	5/8
36 .0076	2/1	3/8	2/6	4/5	2/7	4/8	3/3	6/0
37 .0063	2/2	3/10	2/7	4/8	3/-	5/6	3/5	6/4
38 .006	2/3	4/-	2/9	4/11	3/4	6/2	3/7	6/8
39 .0052	2/4	4/2	2/10	5/2	—	—	3/10	7/2
40 .0043	2/5	4/4	3/-	5/6	4/7	8/2	4/1	7/8
41 .0044	1/6 per oz.		1/9 per oz.				2/3 per oz.	
42 .004	1/9 " "		2/- " "				2/6 " "	
43 .0036	2/3 " "		2/6 " "				3/- " "	
44 .0032	3/- " "		— " "				4/- " "	
45 .0028	4/- " "		— " "				5/6 " "	
46 .0024	5/- " "		5/- " "				7/6 " "	

47 and 48 swg Enam. and 47 swg E.S.S.C. wires in stock. State needs. All above postage extra. **POST ORDERS ONLY PLEASE.** Send stamp for comprehensive lists.

POST RADIO SUPPLIES

33 BOURNE GARDENS, LONDON, E.4 TEL: CLISSOLD 4688 & 2021

EUREKA & CONSTANTAN RESISTANCE WIRES
"ALL GAUGES STOCKED"

G.E.C. & B.T.H. GERMANIUM CRYSTAL DIODES

G.E.C. GLASS TYPE 5/16in. x 3/16in. B.T.H. LATEST TYPE MOULDED IN THERMO-SETTING PLASTIC

Both Wire Ends for Easy Fixing. 4/6 each, postage 2d.

B.T.H. SILICON CRYSTAL VALVE
3/6 each, postage 2d. Fixing Brackets 3d. Extra.

Wiring instructions for a cheap, simple but high quality Crystal Set included with each Diode and Crystal Valve.

CRYSTAL SET

INCORPORATING THE SILICON

CRYSTAL VALVE

Adjustable Iron Cored Coil.

RECEPTION GUARANTEED


Polished wood cabinet, 15/-, post 11d. A REAL CRYSTAL SET, NOT A TOY

CRYSTAL SET

As above, but with Germanium Crystal Diode, 16/-. Postage 11d.

B.A. SCREWS, NUTS, WASHERS soldering tags, eyelets and rivets. **EBONITE AND BAKELITE PANELS,** TUFNOL ROD, PAXOLIN TYPE COIL FORMERS AND TUBES, ALL DIAMETERS.

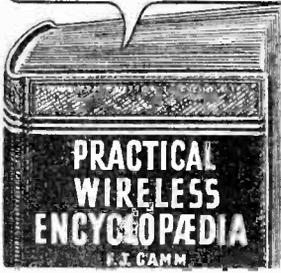How much do you know about **RADIO** and **TELEVISION?**



This world-famous book contains all latest radio and television developments. Earlier copies sold 300,000; this entirely new volume has 400 pages, 1,440 entries, hundreds of illustrations, covers every aspect of radio; new sections include radar, television, remote control, oscillators, Kirchoff's laws, photo-electric cells, new series of modern circuits for receivers and amplifiers; automatic station sel., car radio, electron multipliers, fault finding, building television receiver, new colour codes, etc.—contains all the accumulated knowledge of radio science! Examine this grand book on our 5 days' approval terms—if you do not wish to retain it, return and your purchase money is refunded in full.

MAKE SURE OF YOUR COPY—POST COUPON NOW

To: **A. THOMAS & Co. (PW2), 111 Buchanan St. BLACKPOOL**
I enclose 22/- for one copy of above **OR** Please send C.O.D.
If I return book in 5 days you refund in full.

Name _____
Address _____



Let **ICS** perfect YOUR knowledge of radio and TV

THOSE who wish to supplement their existing knowledge with a sound technological background and, if necessary, pass qualifying examinations, can do so by means of I.C.S. Home Study Courses. These include **RADIO SERVICE ENGINEERING · RADIO ENGINEERING · T/V TECHNOLOGY · ELEMENTARY ELECTRONICS · RADAR · ADVANCED SHORT WAVE RADIO · RADIO and training for the following examinations—B.I.R.E. · P.M.G. CERTIFICATES FOR WIRELESS OPERATORS · C. & G. TELECOMMUNICATIONS · C. & G. RADIO SERVICING CERT. (R.T.E.B.) · C. & G. RADIO AMATEURS · etc. etc.**


Students are coached until successful. Fees are moderate and include all books required.

GENEROUS DISCOUNT TO H.M. FORCES
WRITE TODAY for FREE BOOKLET describing complete facilities for the successful study of Radio and TV technology.

INTERNATIONAL CORRESPONDENCE SCHOOLS
Dept. 170B, International Bldgs., Kingsway, London, W.C.2

Please send booklet on subject _____
Name _____ Age _____
(BLOCK LETTERS PLEASE)
Address _____

TRANSMITTING TOPICS

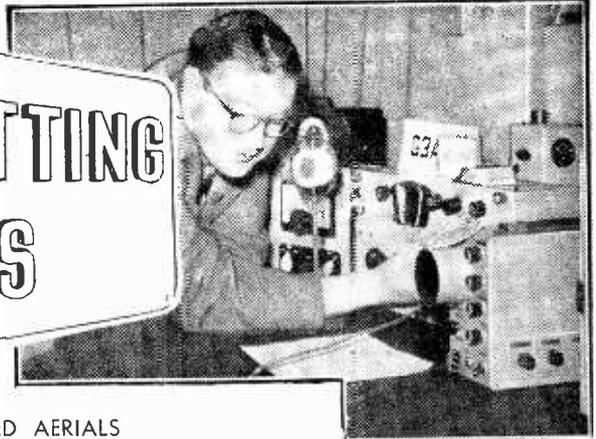

END-LOADED AERIALS

By O. J. Russell, B.Sc. (G3BHJ)

FOLLOWING upon the centre-loading of aerial elements to make better use of short aerials, the use of "end" loading may now be considered. In view of the action of the centre-loading coil in displacing the high current portion of the aerial tuning system, so that the aerial carries a higher current, and consequently is a more effective radiator, it might be assumed that the "best" place for the loading coil is at the extreme end of the aerial (Fig. 1).

In practice, however, this is *not* satisfactory, and due to various considerations the extreme end of the aerial is not recommended as the "best" place for the loading coil. There are a number of conflicting factors, and it turns out that the most useful place for the auxiliary loading coil is at a position of approximately one twentieth of a wavelength from the free end. This immediately indicates that "end" loading is of value when the length of the radiating portion is one tenth of a wavelength or more. In the case of very short aerials, particularly for short, vertical rod aerials, the auxiliary loading coil is best placed in the centre of the element. It is only when the aerial is of sufficient length to give an appreciable amount of wire between the auxiliary loading coil and the base loading coil that the question arises. Hence end-loading (Fig. 2) is best employed for aerials that are at least one tenth of a wavelength long, and in this case the coil is still at the centre of the radiating element. However, as the radiator length increases above one tenth of a wavelength, the loading coil is retained at the position of one twentieth of a wavelength from the free end.

In the case of the top-band, when a "nominal" half-wave may be taken as 270 feet, the change over from "centre" loading to "end" loading thus occurs with aerials of 54ft., and longer wires are

to be "end" loaded. The centre-loaded aerials that are shorter than 54ft. will, of course, still radiate much more effectively than an unloaded plain wire. However, the improvement in slightly longer wires that are "end" loaded is very appreciable.

Quoted figures for an "end" loaded wire one eighth wavelength long show how effective. "end" loading can be. It will be noted that on the top-band one eighth wavelength is a nominal 61ft., which is only some 7ft. longer than the one tenth wavelength case at which

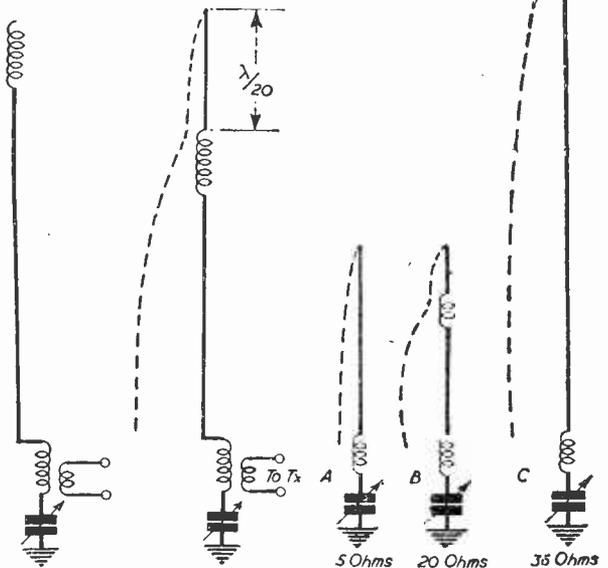


Fig. 1.—An extreme case of end-loading. Not recommended.

Fig. 2.—Correct position for an end-loading coil. Current distribution shown dotted.

Fig. 3.—The 1/8th wavelength Marconi (A) if end-loaded, (B) becomes comparable to a full 1/4-wave Marconi, (C) as its radiation resistance is greatly increased.

"end" and "centre" loading become the same. However, the figures for radiation resistance of an unloaded one eighth wave Marconi of the familiar series-tuned type is only some five ohms; this figure is increased to some 20 ohms by end-loading. This compares very well with the 36 ohms radiation resistance of a full quarter-wave Marconi, which for top band requires 132ft. of wire. In effect the 6ft. of wire is nearly as effective a radiator as the full quarter-wave of 132ft. length (Fig. 3). Clearly this is of very practical interest to the top-band enthusiast with limited garden space! It is also valuable as an expedient for efficient 80-metre operation in very confined quarters. However, despite the emphasis on the value of auxiliary loading coils upon the L.F. bands, where space considerations virtually dictate the use of "short" aerials, it is not generally realised that such end-loaded systems are perfectly practicable upon the higher frequency bands. In fact, for pack sets operating on 50 Mc/s., loading coils of this type enable a very short rod aerial to be used with high radiating efficiency.

Possibilities

The fact that a reasonable radiation efficiency can be obtained with shortened aerials offers some remarkable possibilities, as a 16ft. radiator operated as a Marconi will be highly effective upon 40 metres,

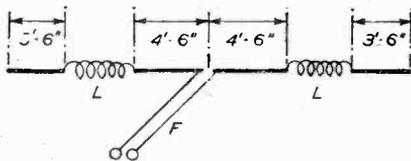


Fig. 4.—End-loading enables an efficient radiating system to be accommodated in a small space. The above aerial is some 16ft. in length, yet radiates effectively on 14 Mc/s.

being, in fact, one eighth of a wavelength long. This becomes more surprising still, in terms of 20 metres, as an end-loaded Marconi will be quite efficient on 14 Mc/s. when it is only 8ft. in length! These lengths, in fact, are only the case of the top-band end-loaded aerial scaled down for the frequency bands in question. However, as an end-loaded 4ft. aerial is the size for 10 metres (21 Mc/s. requires 6ft.), these possibilities open up new avenues for the flat dwelling amateur, as an efficient radiator for the DX bands can be accommodated in very small space. Indoor aerials of efficient performance thus come within the realms of practicability.

It should be remarked that the difficulty with indoor aerials is the problem of getting an adequate length of radiator. In a normal brick and mortar house the mere fact of being indoors does not cause any appreciable loss, and an efficient aerial works almost as well as if outdoors. In fact an indoor aerial does have the advantage that adjustments can be made without having to go outdoors! The writer's experience with indoor radiators has shown that there is no great difficulty about DX contacts—provided an efficient type of radiator is used. For obvious reasons the type of most suitable radiator for indoor use is not necessarily that for normal outdoor use. End-loaded aerials offer very great

advantages in this respect, as the loading coil provides a more advantageous use of a limited length of radiator.

Previously, a "compressed" version of a dipole with centre-loading coils in each side was shown. To illustrate the fact that a compact loaded radiator for the H.F. bands can be constructed, Fig. 4 gives the dimensions of a centre-fed end-loaded "compressed dipole" for twenty metres that can be accommodated indoors in a modest sized room, as it requires 16ft. of clear span. Indeed, as previously intimated in earlier articles, if this clear span is not available, the extreme ends of the aerial may be allowed to hang down. One or two points to notice must be mentioned. It should be clear that these compressed aerials are derived basically from the quarter-wave Marconi, so that in "compressing" a half-wave dipole, each of the quarter-wave halves is end-loaded. In a similar way other aerial systems can be "compressed." However, in the case of parasitic beam arrays, one can *not* scale down the element spacings, although the elements can be compressed in length. However, as a close-spaced beam may have elements spaced by only one tenth of a wavelength, an indoor rotary for twenty metres can be built occupying a space of some sixteen feet by sixteen feet, by using a compressed director, a compressed radiator and a compressed reflector. Each element would preferably have two loading coils,

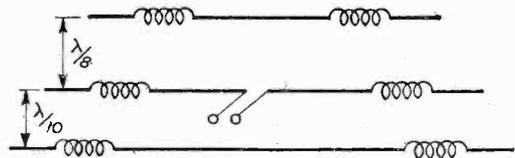



Fig. 5.—A compact close-spaced beam offers scope for experiment.

each one twentieth of a wavelength distant from the tips of the element. However, a considerable amount of juggling with element lengths for correct operation would be necessary, as such a close-spaced beam with "compressed" elements would tend to be very sharply tuned. Nevertheless, it must be noted that compressed element television aerials and a compressed element beam for 5-metre use have been recorded. Fig. 5 shows such a beam diagrammatically.

The Loading Coil

Finally, a word on the loading coil. As previously stated, low-loss construction with thick wire is desirable to avoid excessive losses in the coil. For end-loading as described, the coil should be wound with approximately the length of wire by which the element is short of the quarter-wavelength. Thus on top-band, assuming that a quarter-wave is 132 ft., a 62ft. length of wire would be end-loaded by a coil wound with 60ft. of wire. This would be inserted at a distance of 26½ft. from the free end, which is the one twentieth wavelength distance. Dimensions of aerials for various bands can be scaled down from the top-band dimensions. It should be noted that wires longer than 62ft. can, of course, be end-loaded up on top-band, thus 100ft. of wire requires a coil wound with 32ft. of wire to load it, the coil being placed again at 26½ft. from the free end. The coils are often made somewhat larger than specified here, and are not critical.

*An H.F. Stage
for the*

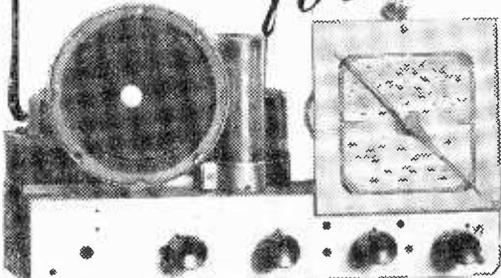

A.C. BAND-PASS 3

INCREASING THE RANGE OF THE
RECEIVER DESCRIBED IN THE
DECEMBER, 1952, ISSUE

THIS receiver, in its original form, lends itself very well to the addition of an R.F. stage. Two tuned circuits, with top-capacity coupling, are already present, and the R.F. valve may be added between these circuits, employing the coils already fitted. The addition of such a stage brings about a considerable increase in sensitivity, so that those stations already received will be heard at greater volume, and other, more distant, transmitters will also be received. Accordingly, it is felt that after the constructor has employed the receiver in its original form for a time it may be desired, in some cases, to add this extra stage. The necessary modifications can be made quite easily, and the circuit will then be one employing three pentodes (plus rectifier) and having a good degree of sensitivity. This should be particularly useful where reception conditions are poor or where only a small and comparatively inefficient aerial is possible.

From consideration of the circuit it will be seen that H.F. transformer coupling is used between the valves; this is a selective and stable form of coupling. Reaction is now not used, but the H.F. volume control is so arranged that the receiver is upon the point of oscillation when this control is at maximum, thus enabling the maximum degree of sensitivity to be achieved.

The same wavechange switch, gang condenser and coils are used. A few extra resistors and condensers are necessary, in addition to the 6K7 valve, and these are listed elsewhere. As a low-frequency form of volume control is now unnecessary, a .25 megohm fixed resistor replaces this. It is possible, of course, to leave the L.F. control in position—it would be useful, for example, if records are played with a pick-up. All the other sections of the original receiver remain unchanged.


Positioning of Coils

The aerial coils are mounted above the chassis, as depicted, with the H.F. coils below. This avoids

coupling between aerial and H.F. coils, which could cause uncontrollable oscillation. Valves differ quite considerably in efficiency, and it should be noted that the receiver may go into oscillation when the H.F. control is at maximum sensitivity, with some valves. This is no particular disadvantage. At the same time, wiring to the wavechange switch should be as short and direct as possible to avoid unnecessary instability. The leads to the aerial coils should also be kept away from those to the H.F. coils.

The coils are mounted by flat spring clips (these are provided), and the notch in each coil is positioned as shown in order that connections to the tags will be correct. As before, the coils are quite separate, and the receiver can be tried upon the M.W. band, for example, before the L.W. coils are added.

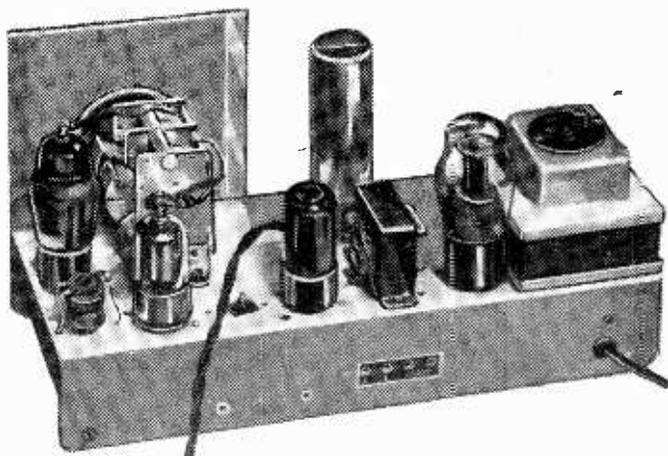Wiring is straightforward and all leads are shown. Two leads pass up through the chassis to the gang condenser, being taken to the tags of the front and rear fixed-plate sections. On top, two further leads go from these sections, as shown (one to the 6K7 valve grid, and the second to the 2.2 megohm resistor



Rear view of the modified receiver.


and .0001 μ F condenser). The grid lead of the 6J7 should be as short as possible.

The 6K7 and 6J7 valve heaters are wired in parallel with the 6V6 heater, and operated from the 6.3 volt winding of the mains transformer. The latter, if of

left between valveholder or switch contacts or elsewhere.

Alignment Instructions

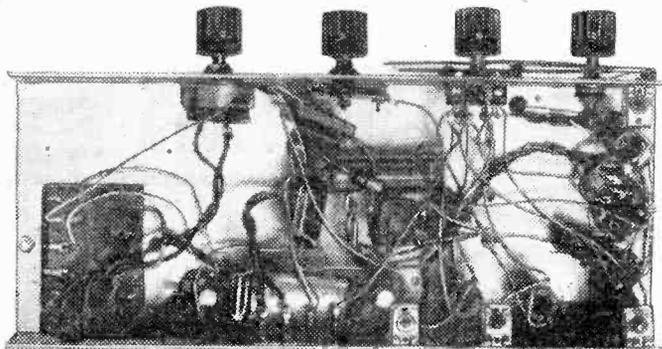Maximum results will only be obtained when the tuned circuits gang accurately together, but adjustments are very simple in a receiver of this type. The coil cores should be set so that six or eight threads of the core-adjusting screws project, and the 50 μ F




Underside view of the receiver.

the type originally specified, can easily supply current for a 6.3 volt .3 amp. dial-light, which is wired in parallel with the heaters if required.

Some of the leads from the wavechange switch are numbered for identification. These are taken to the tags of the coils marked with the same numbers. All wiring should be checked carefully before trying the receiver, which should then work immediately it has warmed up. In particular, wrong wiring or short-circuits which may cause a shorted H.T. or heater supply should be looked for, since if the receiver is left switched on with such a fault, rectifier, smoothing choke or mains transformer may be damaged. No loose pieces of solder or fragments of wire should be

condensers are set about half open. The local stations will then be heard if an average aerial is connected.

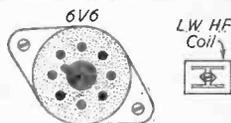
A station high in the M.W. band should now be tuned in. (The higher wavelength third programme transmitter is suggested.) The M.W. coil cores



Note: Points marked MC, are connections to chassis

Twin gang tuning condenser
.0005 μ F each section

Top of chassis

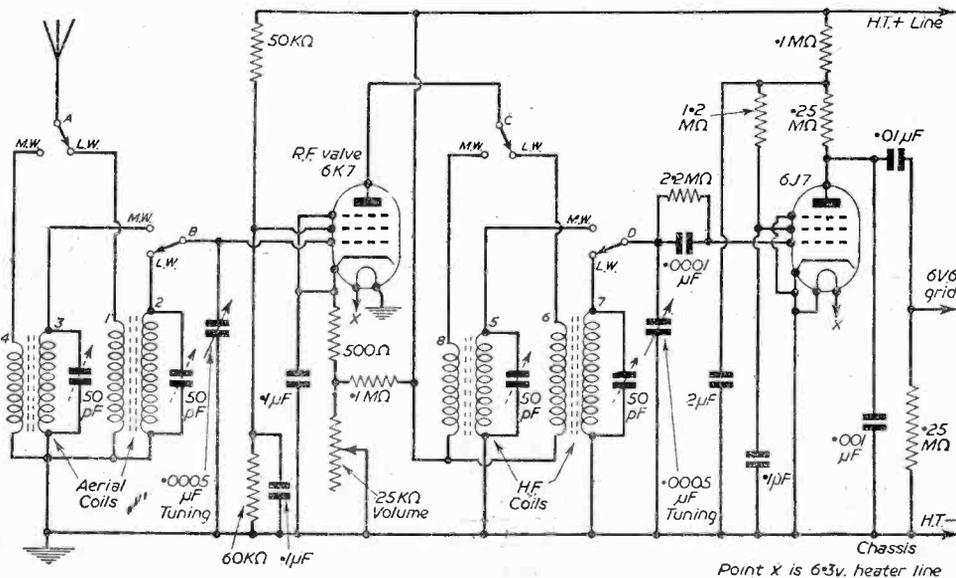


Theoretical circuit of the H.F. and Detector stages. Point x is 6.3v. heater line

25,000
60,000
mega
50,000 oh
Two .1 μ F
6K7 valve


are now adjusted for maximum volume, and should peak quite sharply. If the dial pointer does not give an accurate indication this can be adjusted by operating the tuning control slightly and readjusting the cores. As the tuning condenser is closed, the cores require to be unscrewed to keep the station in tune, and vice versa. A correct dial indication can therefore be obtained, and both cores adjusted for maximum sensitivity.

The receiver is then tuned to a

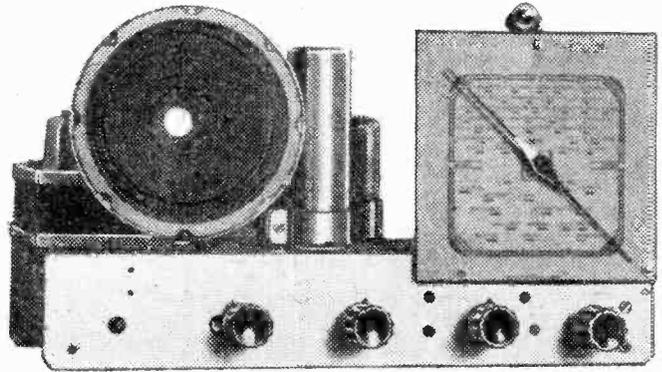method is used, the operation must commence at the low wavelength end of the band, proceeding step by step to the high wavelength end. If the reverse is attempted, subsequent bending of those sections of the plates which appear as the gang



The complete receiver.

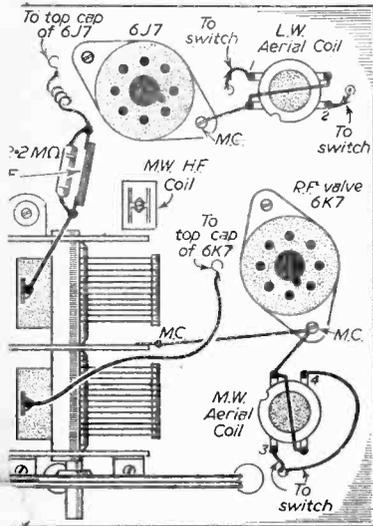

ew of H.F. section.

station of low wavelength, and the M.W. trimmers adjusted in the same way. This may make necessary some very slight readjustment of the cores, at a high wavelength. After-


condenser is opened will upset the first adjustments made with the condenser closed.

Test voltages, using a 10,000 ohm per volt meter, were as follows, and may be used to check operation.

H.T. supply line—250 v. Positive tag of 2- μ F condenser—200 v. 6J7 anode—50 v. 6J7 screen—30 v. 6K7 anode—250 v. 6K7 cathode, up to 60 v., according to setting of V.M. volume control. 6K7 screen—150 v. approx.

wards, the wave-change switch is tuned to the L.W. position, and the procedure repeated with the L.W. coils.

For maximum sensitivity it is only necessary to remember that the cores are adjusted at a high wavelength setting and the trimmers at a low wavelength, in each waveband. The gang condenser has split end vanes, and it is possible to bend these slightly to obtain perfect alignment throughout the M.W. band. However, this is scarcely necessary unless the absolute maximum degree of sensitivity is required. It should be undertaken carefully, otherwise it is preferable to leave the condensers untouched. If this

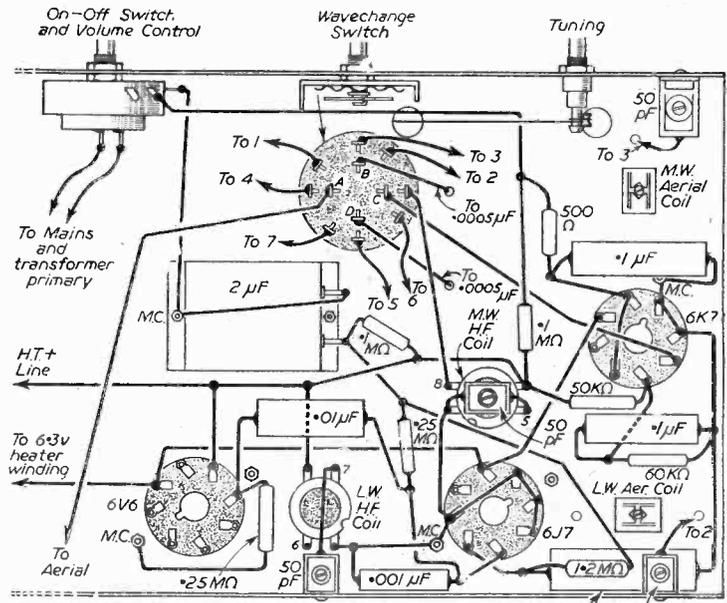

Note: Points marked MC, are connections to chassis

Wiring diagram below chassis of the H.F. end of the receiver.

- LIST OF COMPONENTS**
 potentiometer with switch.
 ; 500 ohm ; 1 megohm ; and .25
 fm $\frac{1}{2}$ -watt resistors.
 m 1-watt resistor.
 condensers.
 : McMurdo octal valvholder.

Programme Pointers

By MAURICE REEVE



Mr. Pickwick

IT is only 130 years or so since Mr. Pickwick and his friends spent the most famous of all Christmases, that at Dingley Dell. And the conditions prevailing in that ever-to-be-lamented oasis from the past—wherein no one had any entertainment or food other than what he himself prepared plus nature's contribution of copious quantities of ice, frost and snow—pertained for many subsequent seasons. How things have changed! How the wheel has come round full circle! Now that we employ others to entertain us at miles and miles distance by turning on "that knob," we are even saved the necessity of having to cease our play in order to join the festive board. If ever two jobs were able to be done at one and the same time it is surely at the modern Yuletide. From morn till night we are, by turns, amused, soothed, enraptured, lulled, enraged, enthused, enlightened, exalted, exasperated and, finally, sated, without having to pause a second or raise an eyebrow other than to "turn that knob"! Go and give those carols a shilling, no, they are in "the box." Three cheers, Chelsea have scored—"in the box." Vic Oliver's funnier than ever—"in the box." The ravishing strains of "Enigma" are there, too—"in the box." What would Messrs. Snodgrass, Tupman and Winkle, the two Samuels themselves, Mrs. Bardell and all the illustrious company, think of our modern Christmas? Alas, we shall never know. But perhaps it is as well.

Varied Fare

Once again we were treated to as broad-minded and as generously varied a bill of fare as could reasonably be looked for. Something for most of us and a few things for all. As usual, the most eagerly-looked-for item was the tour round that considerable portion of the earth's solid and liquid surface styled the Commonwealth and Empire, culminating in the Sovereign's address. The latter was listened to with an especial eagerness as it was the first ever to pass the lips of a Queen. It was in every way a success: the context was of high purpose and firm determination whilst the delivery was a most felicitous combination of charming and youthful femininity and regal dignity.

The tour, too, was good, if not quite so colourful as in some past seasons. The contacts with Wynford Vaughan Thomas in a jet plane was a happy thought, but the failure to pop in and pay Kenya a visit was conspicuous. The Commonwealth didn't seem nearly so much of an entity as in seasons prior to the war. But then it isn't. Robert Donat's commentary provided just the right touch of beautifully modulated sincerity and enthusiasm.

Piano Recital

To follow this up with a very highbrow piano recital by one of our least exciting pianists seems a great mistake for all concerned. Surely it can only

get a small and not very attentive audience, who must all be giving vent to their feelings and expressing their opinions on the Queen's speech following their enforced attention to it and to the tour immediately preceding.

Itma

Dear old Itma! What we have had to do without since Tommy Handley's lamented death is only realised when his programmes are resurrected. A very good one was put on—they were all, of course, very good—but the best can only be those with Col. Chinstrap in them. Both for high speed and faultless delivery as well as a script almost continuously sustained at the highest level of wit, originality and topicality, the Itma programmes have never had an equal. Although the war must have acted as a great stimulus, that same level was uniformly maintained right on afterwards and to the end. It does seem strange that nothing comparable has since been found, for I cannot admit that "Take It From Here," good as it is in odd moments, is comparable in all round, week in and week out excellence.

Out of Place

There were many excellent musical programmes which, in maintaining the Christmas spirit, never let down the catholicity of the art. But, here again, I thought the fifth symphony out of place and unlikely to attract any large number of auditors.

Willfred Pickles' Christmas Party, which, incidentally, followed hard on the Queen's speech on the Light, was in his most intimate and appealing manner. I would award a special "oscar" to Gilbert Harding's programme "But Once a Year," a charming miscellany of thoughts on Carols, Christmas Cards, the real origin of Christmas, etc. It was the first time I had heard Mr. Harding away from one of his many team shows.

Die Fledermaus

The relay, from Sadler's Wells, of an act from Strauss's masterpiece, "Die Fledermaus," would have helped remind Mr. Pickwick that he did not own the earth when he was on it.

Any Questions, Life with the Lyons, Bedtime with Braden, Ray's a Laugh, Variety Fanfare, Welsh Rarebit, Family Favourites, These you have Loved and many other established favourites, not forgetting the BBC Symphony Orchestra, went into the enormous bran tub, or on to the Christmas tree—whichever simile you prefer—forming the season's programmes. Space precludes my dealing in detail with the many items I listened to. But I must not forget the interesting narrative of the famous Baccarat Scandal which, whilst incomplete in some important details, made an exciting item.



OPEN TILL 6 P.M. SATURDAYS

TELEPHONS: AMBASSADOR 4033 & PADDINGTON 3271/2

PREMIER RADIO Company


(REGD.) B. H. MORRIS & CO (RADIO) LTD. EST. 40 YRS.

THIS IS OUR ONLY ADDRESS (Dept. P.W.) 207 · EDGWARE ROAD · LONDON · W2 (THIS IS OUR ONLY ADDRESS)

BUILD A PROFESSIONAL LOOKING RADIO SET AT LESS THAN HALF TO-DAY'S PRICE

We can supply all the parts to help you.

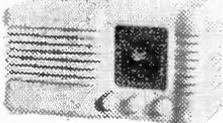- Drum (2 1/2 in. diam.) 1/6
- Driving head 1/6
- Double pointer 4d.
- Spring 3d.
- Nylon Cord (yard) 6d.



Dial Front Plate 2/6

Engraved Glass Dial, 180-550 and 800-2,200m. 1/6

With station names, new wavebands 6/6

T.R.F. Coils, 180-550, 800-2,200 metres, pair 3/9

Punched chassis, 3-valve plus rectifier T.R.F. 3/9

Cabinet, Bakelite, in Walnut or Ivory or W.wooden in Walnut finish 17/6

Packing and insurance 2/6

SEND 1/6 FOR EASY TO FOLLOW POINT-TO-POINT DIAGRAMS AND CIRCUIT DIAGRAM, which shows how YOU can build the Receiver illustrated above.

THE COMPLETE KIT

to construct a 3-valve plus rectifier T.R.F. Receiver for use on 200-250 v. A.C. mains can be supplied at £9 9/6, plus 2/6 packing and carriage. Each Kit is complete in every detail, nothing has to be made or improvised. Easy to follow, point-to-point diagrams are supplied, making construction very simple. The Dial is illuminated, and the Receiver housed in its Cabinet size 12in. x 6in. x 6in. presents an attractive appearance. The valve line-up is: 117A - I.F. Pentode, YR116 - Detector, APT4 - Output, and Metal Rectifier.

A wave band coverage is for the medium and long bands. Choice of 3 Cabinets: Bakelite in Walnut or Ivory, or W.wooden (Walnut finish).



WILLIAMSON AMPLIFIER KIT

A complete kit of parts for the construction of the latest version of this famous amplifier, complete with valves, output and mains transformers.

15 Gns.

Plus 7/6 pkg., carr. and ins.

WILLIAMSON AMPLIFIER TRANSFORMERS (To specification)

The Output Transformer 3.6 ohms sec., £4 7/6. The Mains Transformer PREMIER SP425A, £3/7/6

MOVING COIL MICROPHONE

Low impedance. Incorporates press-to-talk switch. Housed in strong black bakelite case. Dimensions: 2in. wide, 2 1/2 in. high, 1 1/2 in. deep.

Plus 1/6 post and packing. A matching transformer for high impedance can be supplied at 3/6 extra.



H.T. ELIMINATOR AND TRICKLE CHARGER KIT

All parts to construct an eliminator to give an output of 120 volts at 20 mA, and 2 volts to charge an accumulator. Uses metal rectifier, £2.

FOR 'HI-FI' ENTHUSIASTS

QUALITY LOUDSPEAKERS

We have a small quantity available at pre-purchase Tax price.

GOODMANS 12in. 15 ohms top ... £9. 9. 0

VITAVOX K12-20, 15 ohms imp ... £11. 11. 0

Packing and carriage on each of the above 5/-. These are all BRAND NEW and in manufacturers' original cartons.

Famous Set Manufacturer's surplus of - ELECTRIC 'GRAM UNITS

Two-speed, 33 1/3 and 78 r.p.m. For playing Standard and L.P. recordings. Complete with Turntable. For use on 200-250 v. A.C. mains. Each unit is in its original manufacturer's carton and is fully guaranteed. Limited quantity only available at approx. half list price.



£3. 19. 6

Plus 2/6 pkg., carr. ins.

SPECIAL OFFER THE FAMOUS "CHANCERY" HIGH FIDELITY MICROCELL PICK-UP TYPE GPX for Standard and Long Playing



The Chancery Light Weight GPX Pick-up embodies certain unique features achieving a standard of performance not possible with normal magnetic or crystal pick-ups. The secret of the high standard of performance is in the use of the special microcell crystal cartridge assembly which has an unusually wide frequency response. The sapphire stylus is precision ground and semi-permanent. With two cartridges either L.P. or Standard. Price £2/6. Additional L.P. or Standard Cartridges can be supplied from stock at £1 1/6 each.

PORTABLE GRAMOPHONE CABINETS

A fortunate purchase of a manufacturer's surplus stock enables us to offer this first grade Portable Cabinet made by a famous manufacturer at the ridiculously low price of 39/6

Plus 2/6 P. & P. Specification: Substantial Wooden Case. Resine covered, including w.wooden motor board, already cut to take a Gramophone unit. Almost any make of Rim Drive Unit can be accommodated with ease. Outside dimensions: Height (when closed) 14in. Length 14 1/2 in. Depth 13in. Inside dimensions: Length 14 1/2 in. Depth 12in. Clearance space under motor board: 2 1/2 in. Clearance space from motor board to inside lid when closed, 2 1/2 in. These Cabinets are slightly varnished solid, i.e. the nickel plated fittings being a little rusted and the resin requires polishing.



As a special offer for a limited period only the above Gramophone Unit, Pick-up and Cabinet, which will assemble into a complete Portable Electric Gramophone ready to plug-in to your Radio or Amplifier, £8. 5. 0

Plus 5/- Pkg., Carr. & Ins.

GRAMOPHONE UNITS

GARRARD TYPE 70B. Autochange unit complete with Garrard magnetic pick-up head 78 r.p.m. ... £8.8.0

GARRARD Rim Drive 78 r.p.m., complete with magnetic pick-up and turntable ... £5.19.6

COLLARO 3-speed single gram. unit, complete with head for L.P. and Standard recordings ... £3.9.0

COLLARO RC500 Autochange unit, 78 r.p.m. ... £8.8.9

All the above are for use on 200-250 v. A.C. mains. Packing and carriage on each of the above units 5/-.

PREMIER MAINS TRANSFORMERS

All primaries are tapped for 200-230-250 v. mains 40-100 cycles. All primaries are screened. All LTs are centre tapped.

SP175B, 175-0-175, 50 mA., 4 v. @ 1-2 a. 4 v. @ 2-3 a. ...	25/-
SP250B, 250-0-250, 60 mA., 4 v. @ 1-2 a. 4 v. @ 3-5 a. ...	25/-
SP300A, 300-0-300, 60 mA., 6.3 v. @ 2-3 a., 5 v. @ 2 a. ...	25/-
SP300B, 300-0-300, 60 mA., 4 v. @ 2-3 a. 4 v. @ 3-5 a. 4 v. @ 1-2 a. ...	25/-
SP301A, 300-0-300, 120 mA., 5 v. @ 2-3 a. 6.3 v. @ 3-4 a. ...	28/-
SP301B, 300-0-300, 120 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-5 a. ...	28/-
SP350A, 250-0-350, 100 mA., 5 v. @ 2-3 a. 6.3 v. @ 2-3 a. ...	29/-
SP350B, 350-0-350, 100 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-5 a. ...	29/-
SP351, 350-0-350, 150 mA., 4 v. @ 1-2 a. 4 v. @ 2-3 a. 4 v. @ 3-4 a. ...	36/-
SP375A, 375-0-375, 250 mA., 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 5 v. @ 2-3 a. ...	39/6
SP375B, 375-0-375, 250 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-6 a. ...	39/6
SP501, 500-0-500, 150 mA., 4 v. @ 2-3 a. 4 v. @ 2-3 a. 4 v. @ 3-5 a. ...	47/-
SP501A, 500-0-500, 150 mA., 5 v. @ 2-3 a. 6.3 v. @ 2-3 a. 6.3 v. @ 2-3 a. ...	50/-
SP425A, 425-0-425, 200 mA., 6.3 v. @ 2-3 a. 6.3 v. @ 3-5 a. 5 v. @ 2-5 a. ...	67/6

WEYMOUTH MINIATURE I.F. TRANSFORMERS

465 K/C's iron core, permeability tuned—10-8 pair

METERS

Large stocks available, a few of which are enumerated below —

Full Scale Deflection	Scale	External Length	Dimensions in. in.	Movement	
5 A	1 1/2	2 1/2	2 1/2	R.F. Thermo	7/6
2 A	1 1/2	2 1/2	2 1/2	M/C	8/6
25 A	1 1/2	2 1/2	round	R.F. Thermo	7/6
3 A	1 1/2	2 1/2	round	R.F. Thermo	7/6
3.5 A	1 1/2	2 1/2	2 1/2	R.F. Thermo	7/6
4 A	1 1/2	2 1/2	2 1/2	R.F. Thermo	7/6
8 A	1 1/2	2 1/2	2 1/2	M/C	12/6
20 A	1 1/2	2 1/2	round	M/C	8/6
50 A	1 1/2	2 1/2	2 1/2	M/C	8/6
40 A	1 1/2	2 1/2	round	M/C	8/6
1.5 mA.	1 1/2	2 1/2	round		12/6
5 mA.	1 1/2	2 1/2	2 1/2	M/C	8/6
6 mA.	2	3 1/2	round		16/9
50 mA.	1 1/2	2 1/2	2 1/2	M/C	8/6
100 mA.	1 1/2	2 1/2	2 1/2	M/C	8/6
5 A	1 1/2	2 1/2	2 1/2	M/C	10/6
500 Microamp.	1 1/2	2 1/2	round	M/C	15/-
20 V	2	3 1/2	round	M/C	8/6
40 V	1 1/2	2 1/2	2 1/2	M/C	8/6
6.3 V	2	3 1/2	round	M/C	25/-

1 mA METER IN PLASTIC CASE

The movement is 1 mA mounted in a case 3 1/2 in. square and 3 1/2 in. high. The scale is 2 1/2 in. long and the dial is 2 1/2 in. diameter. There is ample room in the case for a switch and multipliers. Internal Resistances 100 ohms. Price 27/6



MOVING COIL METER

A super quality Moving Coil Meter basic movement 2 mA. Scale dimension, 2 1/2 in. Overall dimensions, 2 1/2 in. diam., 1 1/2 in. deep. Bakelite Case projecting type. At present scaled 1 amp. R.F. By removing thermo couple, reversing scale and recalibrating the meter, a high grade test instrument with any range above the basic F.S.D. may be built up. Price 4/9.


TERMS OF BUSINESS:—CASH WITH ORDER OR C.O.D. OVER £1. Please add 1/- for Post Orders under 10/-, 1/6 under 40/-, unless otherwise stated.

PRATTS RADIO

1070 Harrow Road, London, N.W.10

Tel.: LADBroke 1731.

(Nr. Scrubs Lane)

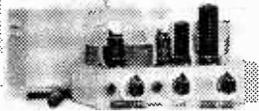

AMPLIFIERS ready to use. Model AC10E (as illustrated) 10-watt, 4-valve unit, neg. feed-back, separate mike stage and separate mike and gram inputs. 2 faders and tone control. Input volts mike .002, gram. .2lv. £10.7.6.

MODEL AC18E. 6-valve unit with p/pull output of 181 watts. Separate mike stage and separate mike and gram inputs. 2 faders

and tone control. Feedback over 3 stages. Input volts: mike .003, gram .3v. £15.5.0.

MODEL AC32E. Spec. as AC18E but with larger output stage of 32 watts. £18.18.0. **MODEL U10E.** D.C. A.C. mains, p/pull output of 10 watts. Spec. as AC18E. £12.19.6. All the above amplifiers are complete with metal case, chrome handles and outputs to match 3, 8 or 15 ohm speakers. All A.C. models have H.T. and L.T. output sockets for tuning units.

SMALL RECORD AMPLIFIER CHASSIS. MODEL AC4C. A.C. or MODEL U4C D.C. A.C. 3-valve units for radio records. Output to 3 ohms. £5.15.0.

QUALITY AMPLIFIER CHASSIS FOR RECORDS, ETC.. MODEL Q4C. 4-valve chassis with bass and treble controls. Inputs for radio/stand'd L.P. records. Sectionalised output transformer with adjustable negative feed-back. £9.15.0.

MODEL Q9C 6-valve version of Q4C. Details as Q4C. Output of 9 watts. Output impedance to choice of customer. This amplifier uses a Williamson 18 section output transformer £13.19.6.

TUNING UNITS Collette TU2 M.W. superhet circuit. £4.19.6. TU1 3-waveband superhet unit £10.9.5. Both plug straight into all our A.C. amplifiers.

MICROPHONES. Moving coil w/trans'r. £5.12.6. Acos. 22-1 or 22-2. £6.6.0. Rothermel, D.104, 105 - 2, 2D56 59 6.

PICK-UPS. Acos GP20 with standard head. £3.11.5.

GRAMOPHONE UNITS. Send for list. All types available, with or without pick-ups.

SPEAKERS. A very good general-purpose unit is the W.B. 10tn. with a 12,000 line magnet. Ex stock, 74 9.


All good are brand new, no surplus components used. Our AC10E, etc., have been advertised since 1946 and are in daily use throughout the world. Stamp for list, state interest P.A. or records.

PREPARE NOW

FOR WINTER TV

The NEW 1355 Conversion data for all five Channels. Sound, Vision, T.B.'s, Power, on one 1355 Chassis.

NEW EDITION, 3/- per copy.

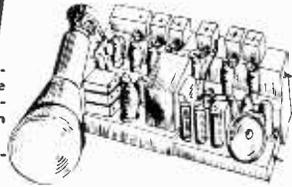

NEW 1355's in original cases, 45/-.

CARBON MIKES	TRANSMITTER 21	RECEIVERS
BRAND NEW 5/5	for speech, MCW or CW on 4.2-7.5 or 18-31 mc/s: PA coils and relays, stripped by Ministry, may be replaced with our data. With circuit, control box and key. First-class condition (less valves) 12/6	S450. 4 EFS4's (RF, mixer, LO multipliers), 2 EF39's (2.9 mc/s IF's), EB34 (det) 6J5 and 6V6 (audio). 65/85 mc/s. Measuring 12 x 5 x 6, with circuit. (Post 2/-) 49/6

CHASSIS	INDICATOR 182A	NEW 1155's
with 5Z4, VU120 (E.H.T. rect.). Transformer, choke, relay, etc., 12/6	with 6in. C.R.T., 3 EF50's, 4 SP61's. 5U4, dozens of resistors and condensers, 9 W/W pots, these are suitable for conversion to 'scope or TV. BRAND NEW (less relay) in original cases Only 79/6 Less EF50's and 5U4G. 50/-.	Most famous ex-R.A.F. communications Receiver—AIR TESTED, BRAND NEW in original cases. Only £10 15s.

RADIO EXCHANGE CO.
9 CAULDWELL STREET, BEDFORD
Phone 5568

FREE

A VALUABLE BOOK

which details the wide range of Engineering and Commercial courses of modern training offered by E.M.I. Institutes—the only Postal College which is part of a world-wide Industrial Organisation.

Courses include training for:

- City and Guilds Grouped Certificates in Telecommunications;
- A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio & Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering.

NEW!

HOME EXPERIMENTAL KITS NOW AVAILABLE

EMI Institutes associated with MARCONI PHONE COLUMBIA H.M.V. ETC. COURSES FROM £1 PER MONTH

POST NOW

Please send, without obligation, the FREE book. E.M.I. INSTITUTES, Dept. 32K 43 Grove Park Road, London, W.4

Name _____

Address _____

IC 10BK

Classic Electrical for

ALL TAPE RECORDING REQUIREMENTS

TAPE DECKS, TAPE EQUIPMENT, COMPONENTS, AND COMPLETE TAPE RECORDERS, AVAILABLE FROM STOCK.

AGENTS FOR:

Wearite Tape Deck	£35.0.0
Bradmatic Tape Desk	£42.0.0
Truvox Tape Desk	£23.2.0
Lane Tape Desk	£16.16.0
Simon 2B	£60.0.0
Scophony	£65.0.0
Ferrogaph	£79.10.0
C.J.R. Portable	£119.10.0
Quad Tape R.	£16.16.0
Bradmatic Circuits	5.0
Bradmatic Oscillator Coil	9.0
Bradmatic Plate Coil	9.0
Bradmatic Mumetal Screens	4.0
Bradmatic Guide Pillars	5.0
Bradmatic 6 RP Heads	£3.15.0
Bradmatic 5 RP Heads	£3.5.0
Bradmatic SE Erase Head	£3.5.0
Spare Spools 600 ft.	4.6
Spare Spools, 1,200 ft.	6.6
Tapes G.E.C.	£1.15.0
Tapes, Scotch Boy	£1.15.0
Tapes, E.M.I.	£1.15.0

Tape Recording Specialists. Demonstrations Daily. Credit sale and hire purchase facilities available.

Additional new Showrooms opening shortly.

THE CLASSIC ELECTRICAL CO. LTD.

"The Hi-Fi Television Specialists"

364, Lower Addiscombe Road, Croydon, Surrey. Tel.: ADDIScombe 6061/6062.

OUTDOOR LISTENING

HINTS ON THE CHOICE OF RECEIVER FOR HIKERS, CYCLISTS, AND MOTORISTS

By W. J. Delaney (G2FMY)

ABOUT this time of the year the listener begins to look forward to outdoor activities and quite naturally the problem of outdoor radio crops up. There are, unfortunately, a number of problems which arise in connection with outdoor radio, and an attempt will be made to deal with them. Outdoor listeners fall roughly into three groups—hikers or walkers, cyclists and motorists. Each will find particular problems arising either from the question of portability or actual use.

Hikers

The hiker or walker will require a receiver which is of minimum size and weight, and in most cases his journeys will not take him far from his home, or at least his movements will be in a more or less restricted area. He can therefore decide upon a circuit which will give him the necessary choice of stations in that area, and will obviously be forced to adopt a receiver in which the all-dry type of valve is employed. This will remove the difficulty of accumulator supplies, and a simple battery of the combined type will provide the necessary voltages in a very compact form. It must be remembered, however, that these compact batteries are not intended for long periods of use, and as a general rule they should not normally be left running longer than a quarter of an hour. A period of rest will give the batteries a chance to recover and a longer general period of life will result. If it is particularly required to hear a programme of half an hour or longer, the overall life of the battery will be correspondingly shortened. The choice of the circuit, as already mentioned, will depend upon the locality and it is not possible to generalise. In one area it may be found that a three-valve straight circuit will give adequate performance, whilst if the set is taken into a neighbouring county it may be found that nothing at all can be received. A four-valve superhet, however, can generally be relied upon to provide some signal, although it cannot be said that it will definitely provide a choice of signals in all parts of the country. The Mini-Four is a good example of a receiver which answers all the above requirements. Such a receiver, however, with pre-set tuning, should not be taken far afield, as the same set of stations may not be so well received in the new area and variable tuning is therefore desirable for a set which is to be taken long distances.

Aerials

The question of the aerial is quite important, and many constructors prefer the throw-out type. Frame aerials would round a case, or on a former fitted into the case, are directional and the set must therefore be turned about until maximum performance is obtained. The best position may not be convenient for some reason, and therefore a wire thrown over a tree branch may be more suitable. Such an aerial is not directional in such a marked degree, although it will generally be found that strongest signals are received in the direction of the free end of the wire. A further advantage is that height may be gained

and will provide a stronger signal than a frame aerial at ground level. It will therefore be found that in general a less powerful type of circuit may be used with a throw-out aerial than a frame-aerial design. The advantages of the throw-out aerial may be obtained, with a set which has a built-in frame, by winding two or three turns round the case, if possible over the actual frame winding, and connecting a throw-out wire to one end of this additional winding and connecting the other end to earth. This will destroy the directional properties of the frame, and the exact number of turns of wire round the case should be found by experiment. Similarly, it may be found worth while to experiment with the aera and earth connections, as the ends to which they are respectively joined will affect the strength of the signals.

With most portables it will generally be found worth while to obtain an ordinary straight metal meat skewer and solder about four or five feet of wire to it. The wire should be attached to the H.T.—terminal of the battery (or an earth terminal if one is fitted to the set) and the skewer pushed into the ground. In many cases it may be found that this alone will give adequate signals without the use of an aerial.

Cyclists

The cyclist is in a slightly more favoured position than the hiker—he does not have to be so particular concerning weight or portability, and he can travel further afield. Therefore he can make use of a larger type of receiver and, in fact, would need a more powerful type to cover all his possible travels. Undoubtedly a superhet is called for, and this may be in the form of an attache case or specially built to be accommodated in a saddle or pannier bag. Batteries may be larger, and a separate L.T. battery or small accumulator may be used to avoid short-period listening. As correspondence has shown, the apparatus may even be built to the cycle so that it may be used whilst riding. A small speaker clipped to the handle-bars, the cycle frame used as an aerial or a small whip-type aerial clipped to the front or rear forks, have been used very successfully, but a single headphone should not be worn in the interests of safety. When stationary, picnicking, etc., the conditions are parallel with those of the hiker and the previous remarks concerning aerials, etc., apply.

Motorists

Motorists are in a much better position, as weight and portability do not have to be considered. A further advantage is that they have unlimited power available, either in the form of L.T. (from the car battery) or in H.T. through the medium of a vibrator power pack operated from the battery. Thus a mains-type of receiver may be used if a car-radio is not fitted. A portable is useful for listening when halted, but usually is unsatisfactory for use inside the car whilst travelling, as the metal body acts as a most satisfactory screen and the self-contained aerial will pick up considerable interference. It is hardly

worth the trouble of fitting plug suppressors, etc., for a portable. In all other respects all the previous remarks apply, with the added point that the car body may be used as a most satisfactory aerial when halted.

Finally, a word of advice to all who use the radio in the open air. If at a picnic site or place where there are other visitors, please keep down the volume

so that it does not annoy others. Nothing is worse than to travel to some picturesque spot, to be quite away from the toil and broil of a city, than to have someone come along and park themselves some distance from you and turn on a blaring radio. A little consideration for others is most important to all users of outdoor radio.

Calling a Taxi-cab by V.H.F. Radio

ANYONE in the London area wanting a taxi-cab has only to dial Waterloo 7722 and almost invariably within a matter of minutes one will be waiting at the door. Waterloo 7722 is the control room of Metropolitan Radio Taxis Ltd., from where contact is maintained with a fleet of radio-equipped cabs wherever they are cruising or waiting. By 'phone and V.H.F. radio a "dispatcher" in the control room acts as a direct link between the prospective hirer and the taxi-driver.

On a call being received a time-stamped instruction slip is immediately handed to the dispatcher who sends out a call for taxis in the area of the pick-up point. Radio-cab drivers in that area reply and give their exact position and identification number. In the interests of speed and economy the cab nearest the pick-up point is selected for the job by the dispatcher who knows London so well that he is able to give precise instructions to the driver. In every case these instructions are confirmed by the driver and, if requested, the hirer is informed by telephone when his taxi is on its way.

A cab may be only a few yards from the pick-up point so that before the fare has had time to put on his overcoat the driver is ringing the door bell!

The several hundred radio-taxis now operating in London provide a unique public service, day and night, all the year round. The dispatcher can route radio-cabs from place to place, or can be called up by a driver who has taken a fare from Central London to the suburbs and does not want to return empty. Drivers have assisted the police by sending back urgent messages to the control room to be passed on to Scotland Yard.

In addition, a taxicab can be pre-booked at no extra charge—a method of hiring that has been found extremely useful to people catching early morning trains or planes. For the business house a monthly credit account system has been found very convenient, particularly when several members of the staff require transport at the same time.

The Service

Metropolitan Radio-Taxis Ltd. is owned jointly by several of the largest London taxi operators. There is a Marconi V.H.F. transmitter of 20 watts located in the control station in London Road, just off the famous Elephant and Castle. This transmitter is paralleled by means of a land-line with an 8-watt transmitter located in a garage, opposite the old Crystal Palace site, on top of a hill in Sydenham, London, S.E.19. A typical taxi radio set is the Marconi type H.67 V.H.F. equipment used in the London General Cab Company's fleet, which is the largest in Great Britain. This fleet operates from the well-known Brixton Garage at Kennington, S.W.9, built in 1907 to accommodate taxis brought over from Paris—the first to run in London.

A quarter-wave long, whip-type aerial, fixed to the roof of the cab, is connected by a coaxial cable to the transmitter-receiver assembly. This is a two-way radio-telephone set developed for Marconi's Wireless Telegraph Co. Ltd., by British Communications Corporation Ltd., for a frequency range of 156-184 Mc/s. It is supplied from a power pack, giving an output of 112 milliamps at 300 v. for the transmitter or 50 milliamps at 250 v. for the receiver; together with a low voltage supply for the valve filaments.

To avoid the use of additional batteries, difficult to accommodate on a taxi, the London General Cab Company's radio equipment is operated from a power pack energised from the "Young" battery that is fitted as standard to all their cabs. The same 12-volt battery system is used for starting and lighting but despite the extra power demand from the battery, arising from the radio being in constant service, there is no appreciable effect on its life. This is partly due to the fact that careful attention is given to maintenance; the battery being regularly serviced by Brixton Garages.

H.M.V. New Auto Player

LAATEST addition to the "His Master's Voice" range of record playing equipment is Model 2127, a high grade 3-speed automatic record player housed in a distinctive walnut finish cabinet. It is suitable for use with most radio receivers and radio-gramophones.

The record changing mechanism is an extremely versatile unit capable of playing up to eight 78 r.p.m. records, 10in., 12in. or mixed; ten 33½ r.p.m. Long Play records 10in., 12in. or mixed; or, by means of a button adaptor, single 7in. 45 r.p.m. records.

A special slip-on centre post, shortly to be available as an optional extra, provides for the automatic playing of up to eight 7in. 45 r.p.m. records.

The pick-up is a special featherweight type with an output sufficient to give ample volume from most instruments. Separate plug-in heads for 78 and 33½/45 r.p.m. records are provided.

Loading of records is made particularly easy by the novel design of the cabinet. Opening the door slides the turntable forward and raises the lid automatically to allow easy access to the mechanism.


Model 2127 is now available from "His Master's Voice" dealers, price 29 guineas, tax paid. The price of the 45 r.p.m. centre post is 17/6, tax paid.

Build the 'P.W.' ELECTRONIC ORGAN

Full-size Blueprints now available, Price 7/6 (Two Sheets.)

From the Publishers, GEO. NEWNES, LTD.,
Tower House, Southampton Street, Strand, W.C.2.

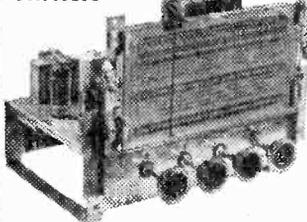A COMPLETELY ASSEMBLED "ALL-WAVE" SUPERHET CHASSIS



MODEL B.3.—A 5-valve 3-waveband Superhet Receiver, for operation on A.C. mains 100-120 volts and 200-250 volts, employing the very latest miniature valves. It is designed to the most modern specification, great attention having been given to the quality of reproduction which gives excellent clarity of speech and music on both Gram and Radio, making it the ideal replacement Chassis for that "old Radiogram," etc.


Brief specifications:—Model B.3.—Valve line up, 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Waveband coverage, Short 16-50, Medium 187-550, Long 900-2,000 metres. Controls (1) Volume with on/off; (2) Tuning (fly-wheel type); (3) Wave change and Gram; (4) Tone (3 position switch operative on Gram and Radio).

Negative Feedback is employed over the entire audio stages. Chassis size, 1 1/2 in. x 7 1/2 in. x 8 1/2 in. high. Dial size, 9 1/2 in. x 4 1/2 in. Price, complete and READY FOR USE, excluding speaker, £12/12/- (Carr. and Pkg. 7/6 extra.)

A QUALITY "PUSH-PULL" AMPLIFIER

A Kit of Parts to build a 6-8 watt Push-Pull Amplifier for operation on A.C. mains 200-250 volts. Incorporates a simple arrangement to enable either a magnetic, crystal or lightweight pick-up to be used. A 10-watt Output Transformer is designed to match from 2 to 15 ohm speakers. Tone control is incorporated. The overall size of the assembled chassis is 10 in. x 8 in. x 7 1/2 in. high. Price of kit complete in every detail, including drilled chassis and valves, £6/17/6. Component layout is supplied.

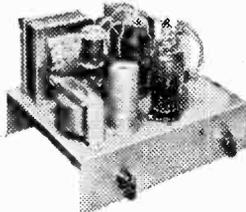Price of assembled chassis, supplied ready for use, £8, 2/6. Instructions, layouts and price list 1/-.



A DUAL CHANNEL PRE-AMPLIFIER and TONE CONTROL UNIT

This comprehensive PRE-AMPLIFIER and TONE CONTROL UNIT provides full control of Bass and Treble in conjunction with a main Volume/Mixer Control. It can be used with any Amplifier and any Pick-up, the range of frequency control provided by the unit affording ample compensation for all types of Pick-up and all natures of recordings, i.e., English, American and Long Playing, without recourse to Pick-up correction. The extreme flexibility of the Bass and Treble Controls is such that the level of Bass and Treble can be set to suit any conditions irrespective of the volume output of the amplifier.

Response characteristics are given in 12-watt Amplifier advt. The Unit measures only 7 in. x 4 in. x 2 in., including self-contained Power Supply, and can be accommodated either on or away from the main Amplifier, i.e., in the front panel of a Cabinet or any other position. Price including drilled chassis, valves (6SN7 and 6J5), £3/16/9. Complete assembly data is available separately for 1/-, Completely assembled and ready for use, £5/5/-.

"PERSONAL SET" BATTERY ELIMINATOR

A complete kit of parts to build a Midget "All-dry" Battery Eliminator, giving approx. 69 volts and 1.4 volts. This Eliminator is for use on A.C. mains and is suitable for any 4-valve Superhet Receiver requiring H.T. and L.T. voltage as above or approx. to 69 volts. The kit is quite easily and quickly assembled and is housed in a light aluminium case, size 4 1/2 in. x 1 1/2 in. x 3 1/2 in. Price of complete kit with easy-to-follow assembly instructions, 42/6. In addition we can offer a similar COMPLETE KIT to provide approx. 90 volts and 1.4 volts. Size of assembled Unit 7 in. x 2 1/2 in. x 1 1/2 in. Price 47/6.

A Genuine

SPECIAL OFFER! PLESSEY 3-SPEED AUTO CHANGE UNITS

Brand New in maker's cartons, complete with mounting instructions.

£11. 19. 6

(Normal price is £23/10/-)

- ★ These units will auto change on all three speeds, 7 in., 10 in. and 12 in.
- ★ They play MIXED 10 in. and 12 in. records.
- ★ They have separate sapphires for L.P. and 78 r.p.m., which are moved into position by a simple switch.
- ★ The size of the unit deck is 14 in. x 10 in., with 6 in. above deck and 2 1/2 in. below.

A bulk purchase enables us to offer these BRAND NEW UNITS at this exceptional price.

Please include 7/6 packing, carriage and insurance.

A MAINS OR BATTERY PORTABLE KIT

A midget 4-valve Superhet Portable Set covering medium and long wavebands.

Designed to operate on A.C. mains 200-240 volts or by an "Alldry" battery. The set is so designed that the mains section is supplied as a separate unit which may be added at any time. The Kit therefore can be supplied (a) as an "Alldry" Battery Superhet Personal Set which can be accommodated in the Attache Case as illustrated (size 9 1/2 in. x 4 1/2 in. x 7 1/2 in.). This is attractively finished in lizard, maroon, dark green, or blue rexine, (b) or as a Combined Mains/Battery Superhet Portable Receiver, for which a polished Wood Cabinet is available to accommodate both Mains Unit and Batteries together.

Circuit incorporates delayed A.V.C. and Pre-selective Audio Feedback. Kit is complete in every detail and includes ready-

wound Frame Aerials, fully aligned I.F. Transf. and drilled chassis, etc. Overall size of assembled chassis 8 in. x 4 in. x 2 1/2 in. This receiver as illustrated can be completely built for approx. £10 (plus Mains Unit if required). Send 1/9 for the fully descriptive Assembly Book which includes Practical Layouts and complete price list of Components.



Can be built for 37/6, plus 9/6 for attractive Plastic Case and 14/9 for suitable headphones. Complete instructions, layouts and price list 1/3.

THE "MINI FOUR."—A 4-valve Battery Superhet Receiver, designed by "Practical Wireless" to receive 4 Pre-set Stations, no tuning being necessary. The complete Receiver can be built for £9/10/0 (plus case, 15/6). Send 1/6 for Assembly Instructions, Layouts and Component Price List.


THE "MINI TWO-THREE."—Complete diagrams and layouts from which either a T.R.F. 3-valve set or a 2-valve set (afterwards easily converted to the 3-valve) can be made for £5/3/- or £4/3/6 respectively (plus case, 15/6). Full Instructions, Layouts and Component Price List, 2/6.

THE "MINI TWIN."—The ideal set for the beginner! A simple 1-valve 2-stage Battery Set covering Long and Medium Wavebands.

THE "WIRELESS WORLD" 3-VALVE SET

A Midget 3-valve T.R.F. Receiver for operation on A.C. mains, covering long and medium wavebands. We are able to supply all of the components to build this set, as designed, and specified in the Feb. 1950 issue, including the drilled chassis, valves and moving coil speaker, etc., at the following prices:—

To construct complete chassis, less dial and drive assembly, £5/5/-. Ditto, including dial and drive assembly, £6. To construct the complete Set, including dial and drive assembly and cabinet, £7/3/6. Overall size of cabinet is 7 1/2 in. x 5 1/2 in. x 1 1/2 in. A reprint of the designer's article, giving Circuit and Assembly Instructions (this is available separately for 9d.), together with a Practical Component Layout is included with each of above assemblies.

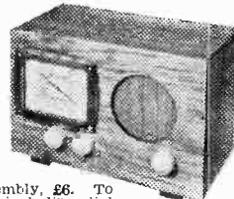

★ Send 9d. P.O. for our STOCK LIST, showing many KITS OF PARTS for Sets and Battery Chargers and "hundreds" of Radio Components. When ordering please include 1/6 to cover cost of postage and packing.

STERN RADIO LTD.
109 & 115, FLEET STREET, E.C.4
TELEPHONE: CENTRAL 5812/3/4.

★ **NOW READY**

The **Skyway**
TAPE RECORDING MANUAL

Complete Building INSTRUCTIONS
for making a
DE LUXE TAPE RECORDER

36 pages packed with information, drawings, plans and amplifier wiring diagrams
PRINTED ON HIGH QUALITY ART PAPER

Direct from:
FRITH RADIOCRAFT LIMITED,
LEICESTER

3/6 PLUS 3d.
POST

OR THROUGH ANY OF
W. H. SMITH & SON'S
BOOKSTALLS

REDUCED PRICES for SKYWAY RECORDING UNITS

Increased manufacturing facilities have made possible substantial price reductions on the RECORDING UNIT in either kit or complete form. We are now also able to offer kit parts separately or in sections, to meet the needs of those who already have motors and recording heads on hand. Easy payments are also available.

RECORDING UNIT	Cash Price	Deposit	Monthly pmts.
Recording unit kit, all parts except motors and heads	£5.15.0	£2. 0.0	4½ at £1.0.0
Recording unit kit, including motors but less heads	£9. 5.0	£3. 5.0	7 at £1.0.0
Recording unit kit, including motors and heads	£15.15.0	£5. 5.0	12 at £1.0.0
Recording unit complete, wired and tested but less tape and reels ...	£18. 0.0	£6. 0.0	12 at £1.3.0
Recording unit with tape and reels ...	£19.19.0	£6.18.0	12 at £1.5.0

RECORDING AMPLIFIER	Cash Price	Deposit	Monthly pmts.
Complete amplifier kit, less valves ...	£12. 3.9	£4. 7.9	9 at £1.0.0
Complete amplifier kit, with "surplus" valves	£14.14.0	£5. 0.0	11 at £1.0.0
Complete amplifier kit, with B.V.A. valves	£16.16.0	£5.12.0	12 at £1.1.8
Complete amplifier, wired and tested with B.V.A. valves	£19.19.0	£6.18.0	12 at £1.5.0

Parts Price List and Descriptive Leaflet on request.
EXPORT AND TRADE ENQUIRIES FOR KITS, COMPLETE UNITS AND MANUALS ARE WELCOMED

FRITH RADIOCRAFT LTD.

69-71, CHURCH GATE, LEICESTER

PHONE 58927

FREE TO AMBITIOUS ENGINEERS!

This 144-page Book



Have you sent for your copy?

'ENGINEERING OPPORTUNITIES' is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £15 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

--- FREE COUPON ---
Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

WHICH IS YOUR PET SUBJECT?

- Mechanical Eng.
- Electrical Eng.
- Civil Engineering
- Radio Engineering
- Automobile Eng.
- Aeronautical Eng.
- Production Eng.
- Building, Plastics, Draughtsmanship
- Television, etc.

GET SOME LETTERS AFTER YOUR NAME!

- A.M.I.Mech.E.
- A.M.I.C.E.
- A.M.I.P.E.
- A.M.I.M.I.
- L.I.O.B.
- A.F.R.Ae.S.
- B.Sc.
- A.M.Brit.I.R.E.
- CITY & GUILDS
- GEN. CERT. OF EDUCATION
- etc., etc.

SOUTHERN RADIO'S WIRELESS BARGAINS

- TRANSMITTER-RECEIVERS**, No. 18, Mark III. Brand new, complete in original packing cases. Complete with all attachments. Headphones, aeriels, microphones, tappers, etc., and complete set of spares, including duplicate set of valves, £18.
- RECEIVER** No. 18, Mark III. As above less attachments. Complete with valves. Guaranteed perfect, £7 13/-, plus 7/6 carriage.
- TRANSMITTER-RECEIVERS** (Walkie-Talkie). Type 38 Mark II. With 5 valves, microphone, headphones, aerial. Less batteries. Fully guaranteed, £4/15/-, post paid.
- RECEIVERS**, Teleonic 4-valve battery portable. Complete with 4 Hvac valves. Contained in metal carrying case. Easily convertible to personal portable. Brand new, £2, including conversion sheet.
- RECEIVERS** R109. Complete with 8 valves. Vibrator pack for 6 volts. Contained in metal case with built-in speaker, 1.3 to 8.5 mcs. Guaranteed, £7 15/-, plus 7/6.
- AERIAL COUPLING UNITS "TYPE C"** with Meter in Metal Case, 10/-.
- INDUCTION MOTORS**, shaded pole A.C. 120/240 volts, 2,800 r.p.m. Ideal for recorders, models, etc., 23/-.
- GRAMOPHONE MOTORS**, Garrard induction 100/250 volts A.C., 78 r.p.m. Brand new with turntable, £4/17/6.
- AUTO-TRANSFORMERS**, 110/250 volts, 500 watts—Metro-Vickers. Brand new, £3 15/-.
- LUBRA HOLE CUTTERS**, Adjustable 1 to 3 1/4 in. ... 5/9
- THROAT MICROPHONES**, with lead and plug ... 4/6
- PLASTIC MAP CASES**, 14 by 10 in. ... 5/6
- STAR IDENTIFIERS**, A-N type, in case ... 5/6
- WESTECTORS** W x 6, W12 ... 1/-
- MARCONI** aerial filter units ... 4/6
- CONTACTOR** Time Switches in case ... 11/6
- REMOTE CONTACTORS** for use with above ... 7/6
- MARCONI AERIAL FILTER UNITS**, Type "916" ... 4/6
- P.O. Specifications. Full Fixing Instructions ... 4/6
- RESISTANCES**, 100 assorted values, wire ended ... 12/6
- CONDENSERS**, 100 assorted tubular and mica ... 15/-

HUNDREDS OF FURTHER LINES FOR CALLERS

SOUTHERN RADIO SUPPLY LTD.

11, LITTLE NEWPORT ST., LONDON, W.C.2

GLRrad 6653

BIET

An Automatic Polarity Corrector

A RELAY-OPERATED AID FOR MAINS EQUIPMENT

By M. C. Paul

THE hazards associated with the handling of A.C./D.C. type equipment are too well known to require comment here. High component prices do, however, necessitate the frequent construction and use of gear of this type where expensive components are few and design simple. In utilising such equipment in the home or workshop, it is wise to employ some means of checking mains polarity, and in this respect some form of

across it from phase to earth, and will reset its switches from their former setting. The resulting current paths can be studied in Fig. 1, and the fact that the output terminals P and N retain their individual polarities irrespective of A and B polarities, will be apparent.

The Relays

In Fig. 1, A.C. type relays are shown, the windings of which must be rated at 230-240 volts. This is an undesirable limiting factor and may be overcome by utilising D.C. relays and rectifiers such as abound in Government surplus equipment and are thus inexpensive. If a "series" resistance be placed in the common earth lead, a wide range of voltage ratings is possible, bearing in mind that both relays chosen should be, at least, similar as to resistance and working voltage of the windings. The associated switching should be similar to that of Fig. 1, but any form of single-pole, two-way action will do, a good positive action being preferred. Relays rated lower than 100 volt working should not be considered unless of extremely low current rating, as the series resistances' "wattage" would become prohibitive. Even if such a resistance was available, its size would be rather too large for any compact unit to be considered. Many obtainable types of relays are provided with their own small rectifiers; where none such are obtainable, any small half-wave 240-volt type will be found adequate, though perhaps a little larger. Some surplus vibrator units provide up to four such rectifiers in a bridge assembly.

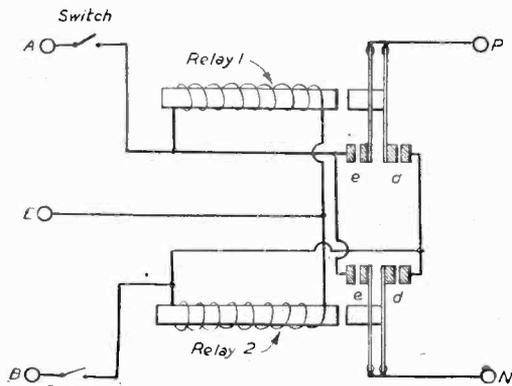


Fig. 1.—Standard circuit recommended by the author—e and d depict energised and de-energised positions respectively.

"fountain pen" type tester is the most useful, although several easy check methods suggest themselves. Such necessary and irksome testing is all too frequently neglected or forgotten, and the cost of a commercial "test-scope" high when its fragility is considered. In any permanent workroom much may be done to ensure correct polarity of supply points and wiring. The kitchen table enthusiast will not usually be so fortunate, and in many cases will have only a lighting pendant as a power source. Fig. 1 outlines the author's answer to these difficulties. It will be seen that an earth connection is essential to the device, and practically any form of earth will do, as only the shunting current of one relay (a matter of milliamperes) must be dissipated, and a regulation "dead-earth" characteristic is therefore unnecessary. An earth rod or plate buried outside a convenient window or a twisted wire connection to a convenient waterpipe will suffice.

The Operating Principle

Since the neutral line of the orthodox 230/240 volt supply is earthed at its sub-station transformer, it is at earth potential. If, as indicated in Fig. 1, two similar relays are connected in series across a 230/240 volt A.C. supply A and B, and their common connection earthed, no potential can develop across that relay wired between neutral and earth. This relay will thus retain its former setting. The second relay will, however, be fully energised by the A.C. mains voltage

Further Improvements

Should low-current consumption relays be utilised, as in the author's model, a low-wattage lamp can replace the series resistance (Fig. 2). Such a lamp should be chosen carefully, so that it will at least glow under operating conditions, thus acting as a visual indicator that there is current in the earth line and that the device is functioning. It is obvious that should the earth connection fail, that apparatus being fed through the device will become "alive" at chassis. The lamp can, of course, do nothing to prevent this

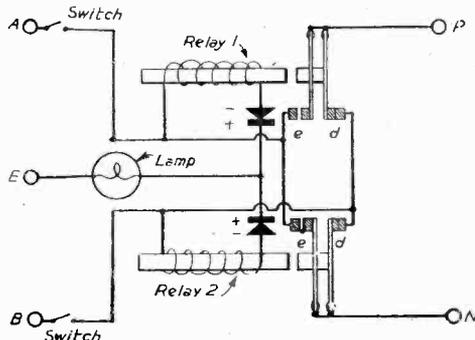


Fig. 2.—Modification for use with low-current relays.

condition, which might in certain circumstances be dangerous.

The Third Relay

The answer to the above problem was the inclusion in the earth line of a third relay, which would be energised under operating conditions by the D.C.

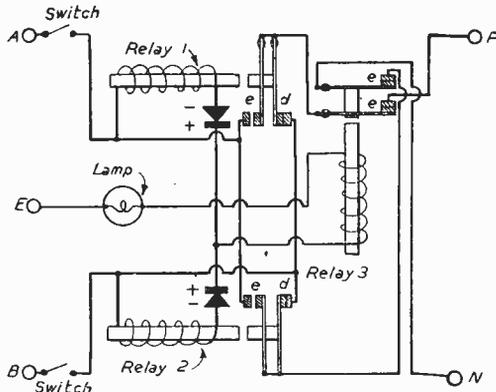


Fig. 3.—Inclusion of a third relay.

pulses in the earth line, and would thus require no extra rectifier. This relay would hold its switches closed when energised and isolate the terminals P

and N from the device, in the event of an earth line rupture or relay failure, etc. The wiring for the corrector utilising a third relay is shown in Fig. 3. If required, a small flashlamp bulb or low-wattage lamp may also be included as shown, serving the dual function of indicator and fuse. If the latter function is required of the lamp, a good "dead-earth" is essential. Since practically all relays possess more than one switch action, it is obvious that the single make-break action of the third relay would at least be duplicated on such types as those previously utilised. In fact, by far the easiest way in choosing a set of three relays is, if possible, to obtain three electrically similar in the 100-240 volt range, and choosing a suitable wattage lamp to drop the remaining voltage; if any, its filament resistance being the appropriate fraction of one relay coil resistance. Since the rectifiers are opposed, i.e., positive to positive, no appreciable current will flow directly between A and B should an earth rupture occur. A two-pole on/off switch should be incorporated as shown in Fig. 3, also fuses, if the supply is not fused at the supply point in the workshop. It must be observed that whilst an earth line fusc will clear a short to earth of the mains phase line, due to a possible relay failure, it will not fuse the supply circuits themselves.

The completed unit as shown in Fig. 3 will be found extremely useful, and the author suggests that as a compact bench unit its use will prevent many nasty experiences to the maker and user of A.C./D.C. type equipment.

News from the Clubs

IXWORTH RADIO CLUB

Hon. Sec.: P. G. Wright, Thurston Road, Gt. Barton, Bury St. Edmunds.

THE recent working station, G3CZY/A, at the Bury St. Edmunds Handicrafts Exhibition, proved a great attraction to visitors. In January began an intensive series of Technical and Morse classes. Local P.W. readers will be welcomed, should they wish to attend.

EDINBURGH AMATEUR RADIO CLUB

Hon. Sec.: D. B. R. Black, 16, Edina Place, Edinburgh.

THE club meets every Wednesday evening at 7.30 p.m. in Unity House, Hillside Crescent. December's programme included: Dec. 3rd.: Talk on Aerials. Dec. 10th.: Club T.X. Dec. 17th.: Amplifiers Lecture. Dec. 24th.: Club T.X.

New members will be welcomed. Particulars obtainable from Secretary.

HASTINGS AND DISTRICT AMATEUR RADIO CLUB

Hon. Sec.: W. E. Thompson, 8, Coventry Road, St. Leonards-on-Sea.

THE Club Annual Dinner was held on December 2nd at the Regent Hotel. Most members attended and we were pleased to entertain ladies and friends. Everyone expressed complete satisfaction with the excellent repast, and the evening went all too rapidly. We were surprised to find out how much the XYL's knew about radio in their answers to the "20 Questions" quiz!

At the general meeting held on November 18th two lectures were given, one on the principles and circuitry of radar, by J. D. Heys (G3BDQ) and the other on mechanical and electrical design features of 3,000-type relays by W. E. Thompson.

The committee has drawn up a tentative programme for the early 1953 meetings, so for the next three months at least members can look forward to several interesting sessions. Meetings will be held on January 13th and 27th at the Saxon Cafe; VHF aerials is the subject for the first meeting, and Tape Recorders for the second.

BRIGHTON AND DISTRICT RADIO CLUB

Hon. Sec.: R. T. Parsons, 14, Carlyle Avenue, Brighton, 7.

THE A.G.M. was held on January 6th. Officers for 1953. Chairman, Mr. C. T. Fairchild. Vice-Chairman, Mr. R. T. Henley. Hon. Sec., Mr. R. T. Parsons (re-elected for third

year). Hon. Treasurer, Mr. W. G. Pitfield (re-elected). Mr. F. R. Jupp was elected to serve on the committee. The past year's activities were reviewed and the future discussed. It is hoped to continue the interesting programme of lectures and talks with more emphasis on elementary subjects in order to aid younger members.

Forthcoming events include:

Feb. 17th: Tape and Disc Recording, by Mr. G. Austin.

Mar. 3rd: Radio Autobiography, by Mr. R. T. Parsons.

This last programme follows upon the suggestion of a member and if successful it is hoped to invite other members to perform at later dates.

COVENTRY AMATEUR RADIO SOCIETY

Hon. Sec.: K. Lines, 142, Shorncliffe Road, Coventry.

WITH a varied programme recently, including a Sausage and Mash Supper, Junk Sale, M.C.C. Contest, lecture on "Workshop Practice," by "Monty," and the regular monthly Night-on-the-Air, the Society has had a successful month. New members are needed and will be welcomed at any of the regular fortnightly meetings held at the Y.W.C.A., Queen's Road, at 7.30 p.m.

STOKE-ON-TRENT AMATEUR RADIO SOCIETY QHT.

Rear of Cottage Inn, Oakhill, Stoke-on-Trent.

REGULAR weekly meetings have been held every Thursday at 7.30 p.m. and during the last few weeks much equipment has been completed, including several T.V. sets, hot supers, etc.

The routine of minutes, lectures, morse training, practical work and rag chew has once again been instituted, as although previous meetings excluding lectures for some time have been popular, the members thought that they were missing a definite advantage.

The club TXG3GBU is hors de combat awaiting the rebuild of a Marconi TX salvaged from beneath three tons of scrap for £3.0.0.

Any person wishing to join the Society should write in the first instance to the club Hon. Secretary.

RADIO SUPPLY CO.

(LEEDS) LTD.

15 Wellington Street, Leeds, I.

Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/- extra under £1, 1/6 extra under £3.

Open to callers 9 a.m. to 5.30 p.m. Sats. until 1 p.m. FULL PRICE LIST, 5/- TRADE LIST, 5/- Please enclose S.A.E. with all enquiries.

SPECIAL OFFERS. Midset Mains Transformers (size approx. 2 1/2 x 3 x 2 1/2 in.) Drop-through chassis type. Screened Primary 220 240 v 50 c/s. Output 250-0-250 v 60 mA. 6.3 v 2.5 a. Only 10/9. Small Filament Transformers, 220 240 v input. 6.3 v 1.5 a output, 5/9. Auto Transformers (with separate l.t. 6.3 v 1.5 a), 0-110-200-210, 230-250 v 50 watts, 4/9 each. New Boxed Ex-Govt. Valves, VR12S (4 v 7-pin H.F. Pentode), 1/9 each.

BATTERY SET CONVERTER KIT. All parts for converting any type of Battery receiver to All Mains. A.C. 200-250 v 50 c/s. Kit will supply fully smoothed h.t. of 120 v 90 v or 60 v at up to 40 mA, and fully smoothed l.t. of 2 v at up to 1 a. Price complete with circuit, only 4/9.

PERSONAL SET BATTERY SUPERSEDER KIT. A complete set of parts for construction of a Unit (housed in Metal Case) to replace Batteries where A.C. Mains supply is available. Input 200-250 v 50 c/s. Outputs 90 v 10 ma and 1.4 v 250 ma fully smoothed. Price complete with circuit. Only 29/6.

H.T. ELIMINATOR AND TRICKLE CHARGER KIT. Consists of h.t. and l.t. transformer, h.t. and l.t. rectifiers, smoothing electrolytic, and choke, adjustable charge resistor. For Mains input of 200-250 v. Output 120 v, 40 mA and 2 v 1 a. Price, with circuit, 29/6.

BATTERY CHARGER KITS
To charge 6 or 12 v acc. at 2 A, 29/6.
To charge 6 or 12 v acc. at 1 1/2 A, 45/-.
Above consist of transformer, bridge rectifier, fuse, fuseholder and case.

EX-GOVT. VALVES (NEW)

Each	Each	Each	Each
IT4	8/11	6SL7GT 11/9	12SR7 7/9
IS5	9/6	6SN7GT 12/9	15D2 5/8
IR5	9/6	6SG7 6/9	10Z5 5/8
3S4	9/6	6V6G 8/11	35Z4GT 10/6
5Y3C	9/6	6V6GT 10/6	1L 1/3
5U4G	10/6	6X3GT 8/9	EP35 6/11
5Z4G	9/6	7V7 6/9	EF39 7/6
6AL5	9/6	7D8 6/9	EL33 10/6
6FG6	9/6	8D2 2/11	EF91 11/9
6AM6	11/9	9D2 2/11	EB91 9/9
6BE6T	9/9	954 1/11	KT61 10/6
6J3G	9/9	12H6 2/3	KT86 11/6
6J7G	7/6	12K7CT 10/6	MU14 9/6
6K7G	6/11	12K8CT 10/6	MS Pen 5/9
6K8G	12/9	12Q7GT 10/6	SP1 5/9
6Q7G	8/11	12SK7 6/11	U50 9/6
			UV120 2/11

EX-GOVT. ITEMS. Pvc coaxial plugs and sockets, 7/6 doz. pyre. Bealings Lee moulded type 5-pin plugs and sockets, 1/11 pr. Int. Octal Valve Screening Cans, 3 piece, 1/3 each, 11/9 doz. .02 mid 5,000 v Tubulars, 1/9. .05 mid 3,500 v Tubulars, 2/11.

ELECTROLYTICS (Current production. Not ex-Govt.)

Tubular Types	Can Types
8uF 350 v	1/9
8uF 450 v	1/11
8uF 500 v	2/9
16uF 350 v	2/3
16uF 450 v	2/9
16uF 500 v	3/11
32uF 350 v	3/3
32uF 450 v	3/3
8-16 uF 500 v	4/11
25uF 25 v	1/3
25-25 uF 50 v	1/3
50uF 12 v	1/3
25uF 50 v	1/9
50uF 25 v	1/9
50uF 50 v	2/3

Can Types	Price
32-32uF 350 v (small)	5/11
15-16uF 450 v plus 20uF 25 v	5/3
32-32uF 350 v plus 25uF 25 v	5/11
50uF 350 v plus 250uF 12 v	4/11

EX-GOVT. SMOOTHING CHOKES (POTTED)
300 mA 5 H 50 ohms ... 12/9
220 mA 5 H 50 ohms ... 10/9
150 mA 10 H 200 ohms ... 10/9
50 mA 50 H 1,250 ohms ... 8/11

EX-GOVT. BLACK PAPER MANS-BRIDGE TYPE CONDENSERS
4uF 500 v T.C.C. ... 2/9
4 1/2 uF 1,000 v T.C.C. ... 3/3
8 1/2 uF 500 v T.C.C. ... 4/9

COAXIAL CABLE, 75 ohms. 1in. 100 yard.

DIAL BULBS, M.E.S., 6.5 v 0.15 a, 8 v 0.15 a, 6/9 dozen.

SELENIUM RECTIFIERS, 230 v 50 mA, H.W. (small), 6/9. 120 v 40 mA, H.W. (small), 4/6. 12-15 v 2 a F.W. Bridge, 10/9. 12-15 v 4 a F.W. Bridge, 18/9.

CHASSIS, 16 s.w.g. Undrilled Aluminium. Receiver Type 10 x 5 1/2 x 2 1/2 in.; 3/9; 11 x 6 x 2 1/2 in.; 4/3; 12 x 8 x 2 1/2 in.; 5/3; 16 x 8 x 2 1/2 in.; 7/6; 20 x 8 x 2 1/2 in.; 8/11. Amplifier Type, 12 x 8 x 2 1/2 in.; 7/11; 16 x 8 x 2 1/2 in.; 10/11; 14 x 10 x 5 in.; 12/6; 20 x 8 x 2 1/2 in.; 13/6.

SILVER MICA CONDENSERS, 5uF, 10uF, 15uF, 20uF, 25uF, 30uF, 35uF, 50uF, 120uF, 150uF, 180uF, 200uF, 230uF, 300uF, 330uF, 400uF, 470uF, 500uF, 1,000uF, (0.01uF), 2,200uF, (0.002uF). All at 5d. each, 3/9 dozen, one type.

TUBULAR WIRE-ENDED CAPACITORS (New Stock). 0.01uF 750 v, 0.01uF 750 v, 0.02uF 1,500 v (large), 0.05uF 350 v, 1uF 350 v, 25uF 350 v, 5uF 400 v. All at 4d. each, 3/3 dozen, one type, 27/6 gross.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and Impregnated. Primaries 200-230-250 v 50 c/s Screened. **TOP SHROUDED, DROP THROUGH**
260-0-260 v 70 mA, 6.3 v 3 a, 5 v 2 a ... 14/11
260-0-260 v 80 mA, 6.3 v 2 a, 5 v 2 a ... 14/11
350-0-350 v 80 mA, 6.3 v 2 a, 5 v 2 a ... 17/9
350-0-350 v 90 mA, 6.3 v 3 a, 5 v 2 a ... 21/9
250-0-250 v 100 mA, 6.3 v 4 a, 5 v 3 a ... 23/9
300-0-300 v 100 mA, 6.3 v 4 v 4 a, c.t. ... 23/9
0-4-5 v 3 a ... 23/9
350-0-350 v 100 mA, 6.3 v 4 v 4 a, c.t. ... 23/9
0-4-5 v 3 a ... 23/9
350-0-350 v 120 mA, 6.3 v 4 a, 5 v 3 a ... 28/9
350-0-350 v 150 mA, 6.3 v 4 a, 5 v 3 a ... 29/11
350-0-350 v 150 mA, 6.3 v 2 a, 6.3 v 2 a ... 29/11
5 v 3 a ... 29/11

FULLY SHROUDED UPRIGHT
250-0-250 v 60 mA, 6.3 v 2 a, 5 v 2 a ... 17/6
Midset type 21-3-3in. ... 17/6
300-0-350 v 70 mA, 6.3 v 2 a, 5 v 2 a ... 18/9
250-0-250 v 100 mA, 0-4-6.3 v 4 a, 0-4-5 v 3 a ... 25/9
250-0-250 v 100 mA, 6.3 v 6 a, 5 v 3 a ... 29/9
300-0-300 v 100 mA, 0-4-6.3 v 4 a, 0-4-5 v 3 a ... 25/9
350-0-350 v 100 mA, 0-4-6.3 v 4 a, 0-4-5 v 3 a ... 25/9
350-0-350 v 150 mA, 6.3 v 4 a, 5 v 3 a ... 33/9
350-0-350 v 150 mA, 6.3 v 2 a, 6.3 v 2 a, 5 v 3 a ... 33/9
350-0-350 v 160 mA, 6.3 v 6 a, 6.3 v 3 a, 5 v 3 a ... 45/9
350-0-350 v 250 mA, 6.3 v 6 a, 4 v 3 a, 0-2-6 v 2 a, 4 v 3 a for Electronic ... 67/6
ENK. Television ... 67/6
425-0-425 v 200 mA, 6.3 v 4 v 4 a c.t., 6.3 v 4 a, c.t., 0-4-5 v 3 a, suitable Williamson Amplifier ... 51/-
425-0-425 v 250 mA, 6.3 v 6 a, 6.3 v 3 a, 5 v 3 a ... 65/6
325-0-325 v 20 mA, 6.3 v 0.5 a, 6.3 1.5 a, for Williamson Pre-amplifier ... 17/6

FILAMENT TRANSFORMERS
All with 200-250 v 50 c/s primaries
2 a, 7.6 v, 0-4-6.3 v 2 a, 7.9 v, 12 v 1 a, 7/11
6.3 v 3 a, 10/11; 6.3 v 6 a, 17/6; 0-2-4-5-6.3 v 3 a, 16/9; 12 v 3 a or 24 v 1.5 a, 17/6;
0-5-6.3 v 5 a, four times, giving up to 24 v 5 a up to 12.6 v 10 a, up to 6.3 v 20 a by series or parallel connections, 55/-

BAKELITE (Brown or White) and WOOD (Walnut veneered) CABINETS. Size approx. 12 x 6 1/2 x 3 in. Very attractive appearance. For illustration see our list. Supplied complete with fully punched T.R.F. 3-valve Chassis, back, 2 or 3 wave. Glass scale with coloured station names, Dial Backplate, 25/-, plus Carr. 2/6. All parts available for construction of T.R.F. or Superhet Receiver in above cabinets.

CLEARANCE LINES. .0005uF 2-gangs with short spindle, 4/6. Vol. Controls, 1 Meg with S.P. switch and long spindle, 2/9. 25K with D.P. switch and lin. spindle, 2/9.

VOLUME CONTROLS with long spindles, all values less switch, 2/9, with S.P. switch, 3/11.

WIRE WOUND POTS: 20 ohms, 5K, 20K, 25K, 50K (medium length spindles) 2/9.

FOR CALLERS ONLY. Mains Trans. drop-through type with top shroud. Primary 230-250 v. Secs. 425-0-425 v, 200 mA, 300-0-300 v 100 mA, 6.3 v 2 a, 6.3 v 2 a, 5 v 3 a, 29/9.

P.A. SPEAKERS. All 2-3 ohms. 5in. Plessey 13/9, 5in. Goodmans 14/9, 6in. Elac 14/11, 6in. Goodmans 15/9, 6in. Plessey 15/9, 10in. Goodmans 31/-, 10in. Plessey 15/6.

M.E. SPEAKERS. All 2-3 ohms, 4in. E.M.I. with trans. Field 700 ohms 14/9, 6in. Rola field 700 ohms 11/9, 8in. R.A. field 600 ohms, 12/9. 10in. R.A. field 600 ohms, 23/9.

CLAMPED UPRIGHT MOUNTING.
300-0-300 v 100 mA, 6.3 v 3 a, 5 v 3 a ... 21/9
350-0-350 v 100 mA, 6.3 v 3 a, 5 v 2 a ... 21/6

CHARGER TRANSFORMERS
All with 200-230-250 v 50 c/s Primaries
0-9-15 v 1.5 a, 14/9; 0-9-15 v 3 a, 16/9
0-9-15 v 6 a, 22/9; 0-4-9-15-21 v 3 a, 22/9
0-9-15-30 v 3 a, 23/9.


SMOOTHING CHOKES
250 mA, 8-10 H, weight 12 lb ... 16/9
100 mA, 10 H 200 ohms ... 7/6
80 mA, 10 H 350 ohms ... 5/6
60 mA, 10 H, 400 ohms ... 4/11
50 mA, 50 H, 1,000 ohms ... 8/11

ELIMINATOR TRANSFORMERS
Primaries 200-250 v 50 c/s
120 v 40 mA ... 7/11
120 v 40 mA, 6 v 1.5 a ... 14/9
120 v 40 mA, 6-0-6 v 1.5 a ... 16/9

E.I.T. TRANSFORMERS
5,000 v 5 mA, 2 v 2 a ... 39/6
2,500 v 5 mA, 2-0-2 v 1.1 a, 2-0-2 v 1.1 a, for VCR97, etc. ... 37/6

OUTPUT TRANSFORMERS
Midset Battery Pentode 66:1 for 354, etc. ... 3/6
Small Pentode, 5,000 Ohm to 30 Ohm ... 3/9
Small Pentode, 8,000 Ohm to 30 Ohm ... 3/9
Standard Pentode, 5,000 Ohm to 30 Ohm ... 4/9
Standard Pentode, 8,000 Ohm to 30 Ohm ... 4/9
Multi-ratio 40 mA, 30:1, 45:1, 60:1, 90:1, 1 Class B Push-Pull ... 5/6
Push-Pull 10-12 Watts 6V6 to 3Z2 or 15Z2 ... 16/9
Push-Pull 10-12 Watts to match 6V6 to 3-5-9 or 15Z2 ... 16/9
Push-Pull 15-18 Watts to match 6L8, etc., to 3Z2 or 15Z2 Speaker ... 22/9
Push-Pull 20 Watts, high-quality, sectionally wound, 6L6, KT86, etc., to 3, 7.5 or 15 Ohm (including in 4 sections of 3.75 Ohm each) ... 51/9
Williamson Type, exact to author's specification ... 85/-

"TYANA"
SOLDERING IRON 16/9

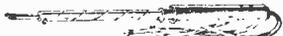

The Perfect Small Soldering Instrument

- Adjustable Bit. ● Easy to handle. ● Weight approx. 4 ozs. Overall Length 4 1/2 in. and the Diameter of the Bit is 3/16 in.
 - Heating Time 3 min. ● 40 Watt economy Consumption. ● Standard Voltage Ranges (other Ratings Available on Request). ● Long Life and Efficiency.
 - Replacement Elements and Bits always available.
- Just the Convenient Iron Required for Intricate and Fine Soldering.

Maintenance Service for Industrial users.
British made by:—

KENROY LIMITED
152/297, Upper Street, Islington, London, N.1.
Telephone: Canonbury 4905-4663

**TECHNICAL
BOOK SERVICE**



for the
Radio Industry


For all your technical books and periodicals you need go no further than the nearest shop or bookstall of W.H.S. Whilst it is not practicable to maintain a big stock of such books at every branch—the Daily Supply Service from Head Office will quickly deliver the books you want to your local branch. We will gladly supply lists of the standard works on any subject and welcome inquiries from students and librarians.

★ Our Postal Service can send technical books and periodicals to any address at Home or Overseas.

W. H. Smith & Son

TECHNICAL BOOK SERVICE

HEAD OFFICE: STRAND HOUSE, LONDON, W.C.2

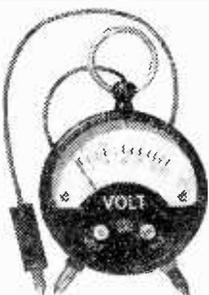

**DUAL RANGE POCKET
—VOLTMETER—**

0-12 v., 0-250 v. A.C./D.C.
Robustly constructed in Black Lacquered Brass Case, this accurate and well-finished instrument has many uses in the workshop and the home. The Dual Range makes possible the accurate testing of Car, and all L.T. and H.T. Batteries, and house and workshop wiring. The moving Iron System permits considerable overload without damage to the instrument. Particular attention has been paid to Scale Clarity.

DIAMETER 2ins. DEPTH 1in.
**THE TECHNICAL SERVICES
CO.**
Shrubland Works, Banstead, Surrey.

Price 19/- each.
Plus postage and packing 1/-.

COVENTRY RADIO

COMPONENT SPECIALISTS SINCE 1925

189, DUNSTABLE ROAD, LUTON

Phone: LUTON 2677

WE SEND COMPONENTS ALL OVER THE WORLD. LET US KNOW YOUR REQUIREMENTS. NO ORDER TOO SMALL. QUOTATIONS GIVEN.

CLEARANCE OFFER!!

Of special interest to Experimenters, Service Engineers, Dealers, and all Radio Constructors.

100 RADIO CONDENSERS, all brand new Ex-Govt. Stock and comprising Electrolytic, Paper, Mica, and Ceramic types.

Capacities 2 P.F. to 8 mfd. (at least one 8+8+8 mfd. at 500 v. working included in each selection).

NOTE.—We cannot guarantee any one particular type of condenser to be included, but we do guarantee that the normal retail price for the parcel to be not less than £3.10.0d.

Our Special price for the 100 Condensers

15/- (Post & Packing 1/6d.)

WALTON'S WIRELESS STORES

48, STAFFORD STREET, - WOLVERHAMPTON

Send S.A.E. and 3d. in stamps for our latest list.

Amplifier Chassis Type 1135, containing three valveholders, 3 transformers, 100K potentiometer, 10-way Jones socket, 10 condensers, 17 resistors mounted on small chassis with hinged sides, 9in. x 2 1/2in. x 3in. Store soiled, special price to clear our warehouse, 4 for 10/-, post 2/-.

VCR97 Tubes, Special offer. Brand new in makers' cartons, price 25/-. Postage 2/6. We cannot repeat at this price when our present stocks are cleared.

Direction Finding Frame Aerials. Collapsible. Contained in green canvas bag, 4ft. x 6in. long. A real Bargain. Price 6/6. Post 6/-.

Receivers Type 3039A. Containing 8 EF50 valves, 1 VU120, 2iv. motor, switch unit, IP strip, resistances, condensers, etc. Price 40/- Carriage 7/6. Used condition.

Our New list, No. 9, containing over 400 ex-Government items, is now available, price 6d. inland, 1/6 overseas Air Mail.

A. T. SALLIS

83, North Road, Brighton, Sussex.
Phone: Brighton 28006.

**ELECTRAD
RADIO**

GUARANTEED VALVE BARGAINS
6AK5, 9/6 each. 6F33, 10/6; 6K8, 9/6 each. 3 for 28/-; 6AC5, 6/6 each. 3 for 16/6; 807, 8/6 each. 3 for 24/6; 6L7M, 6/6 each. 3 for 16/6; 6N7M, 6/6 each. 3 for 16/6; 6SF5, 7/6 each. 3 for 21/-; EA50, 2/- each. 3 for 5/-; 3A1, 4/-; 185BT, 12/6; CV286, CV287, (B7C Stabilisers), 12/6; GS16, GS46 (P.E. Cells), 22/6; IT4, 7/6; 3Q4, 8/6; GSA7, 8/6; 12SG7, 4/-; 6J6, 12A17, 10/6. Postage 9d. on orders under £2. Send for full valve list.

TELEVISION COMPONENTS. Full range of components and valves stocked for the TELE-KING, VIEWMASTER, "ARGUS," etc.

69, HIGH STREET,

BELFAST

**TWIN TRACK TAPE
RECORDING**

Complete Kit, £24.10.0 (Carr. Paid)

LANE MK II. TAPE TABLE
Only, £16.10.0 (Carr. 10/- extra)

Detailed Plans & Instructions, 2/6.

Demonstrations daily at our Shop. Open 8.30 a.m.-6 p.m., including Sats. Send 6d. for our new 24-page Catalogue of Radio and Engineering Supplies.

Tel.: St. Albans 5951.

BOLD & BURROWS,
12/18 VERULAM ROAD (A5),
ST. ALBANS, HERTS.

LONG-PLAYING RECORDS

PRINCIPLES OF THE L.P. AND CIRCUIT REQUIREMENTS

By Gordon J. King

NOW that at least another four record manufacturers are producing long-playing records, enabling most musical tastes to be satisfied, many more constructors will, no doubt, start surveying the problem of converting their existing 78 r.p.m. record reproducing equipment to cater also for this current style of record reproduction. In the first place, therefore, let us get a brief glimpse of what the long-playing record has to offer over its older-style counterpart.

The degree of satisfaction derived from any recorded music is limited in part on the quality of reproduction, that is, the closeness of approach between the original and the reproduced, considering, of course, the disconcerting accompaniment of surface noise—or record hiss; and perhaps to a greater extent on the arbitrary intervals between a series of records which may comprise a complete concert performance. In these respects, at least, the long-playing record yields a great increase in musical satisfaction, particularly to those interested in the longer works, for apart from the much extended playing time per disc, the quality of reproduction, including the minimisation of record hiss, is much enhanced.

It is necessary, however, in order to gain the full advantages afforded by these new records, to know something about how they differ from ordinary 78 r.p.m. recordings, and how the amplifier circuits must be altered to cater for their modified frequency response.

General Characteristics

One of the salient features of these new recordings is, of course, the much extended playing time, brought about by a 2.35:1 reduction in turntable speed, coupled with an increase in record groove pitch. In this respect long-playing records have approximately 300 grooves to the inch, as compared with something less than 100 on 78 r.p.m. records. These two factors combined create an increase in

duration of playing time of almost six times longer than that available from 78 r.p.m. records.

Because of the increase in record groove pitch it obviously follows that the actual groove width is reduced; which means that a considerably lower recording level is demanded to prevent the risk of breaking down the groove walls on heavy modulation peaks. This represents one of the reasons why the new records are quite unsuitable for use with the acoustic gramophone—although, needless to say, the recording engineer is at last able to concentrate solely on the quality aspect, instead of, as hitherto, having to compromise between quality and record magnitude. As opposed to a groove width of 0.007in. and a groove depth of 0.0029in. employed on 78 r.p.m. discs, the corresponding figures for a long-playing record are 0.003in. and 0.002in. respectively—and for this reason the new discs are frequently called *microgroove* long-playing records.

To combat the resulting increase in record hiss, due to the reduction in modulation amplitude, a new record material is adopted, entirely different from shellac used for 78 r.p.m. discs. This new material comprises a Vinyl compound, and though “unbreakable” is softer than shellac and consequently much more easily scratched. Great care is, therefore, necessary in handling the records, and in particular they should be at all times protected from contact with substances that may scratch or abrade their surface. Furthermore, they readily acquire a static charge and so are more difficult to keep free from dust and foreign particles. The most impressive feature of the material, however, is that it gives a very much lower surface noise than shellac base discs—an advantage which means a great deal to the high-fidelity enthusiast.

Stylus Pressure and Dimension

The new groove dimensions demand a reproducing needle having a tip radius of 0.001in., as opposed to

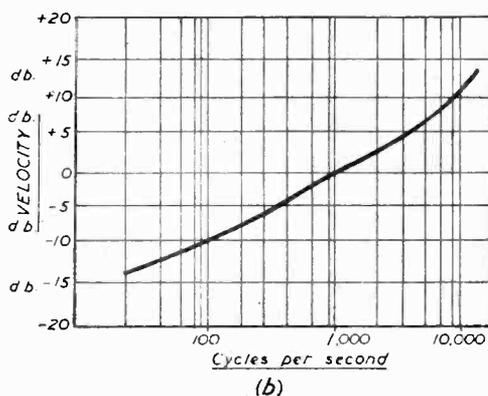
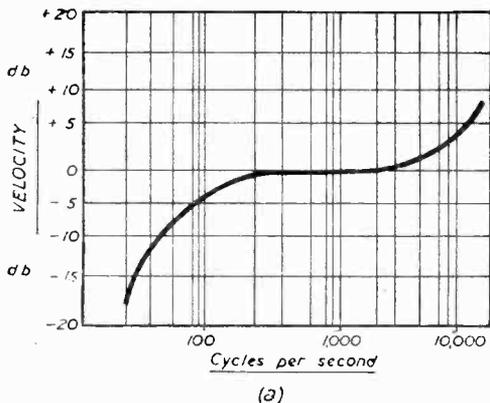


Fig. 1(a).—78 R.P.M. recording characteristic and (b).—Microgroove recording characteristic.

the 0.0025in. tip radius needed for 78 r.p.m. records. It should be emphasised here that to use a standard needle on microgroove recordings will, even on a single playing, ruin the record.

In addition to this, the needle pressure must be considerably less than that used on standard records, for excessive pressure will tend to damage the delicate walls of the groove. With this in mind, manufacturers have developed special light-weight pick-ups employing a stylus of "permanent" material, such as sapphire, and having a greatly reduced needle pressure. As it is virtually impossible to change this type of stylus without upsetting the tracking, and promoting consequent damage to the record, it is

records, the groove walls would break down on peak modulation. Nevertheless, the constant rise curve of Fig. 1b greatly improves the ratio of the high-frequency recorded amplitude to the surface noise; although, on the other hand, it does give rise to an extra large degree of tracking distortion. But owing to the fact that microgroove records are not modulated so near the centre of the disc as is usual with standard records, coupled with the reduction in the size of the stylus point, little difference in this respect is discerned between the two kinds of records.

Both crystal and magnetic types of pick-ups are employed for playing microgroove records. They differ in function in as much as the voltage generated

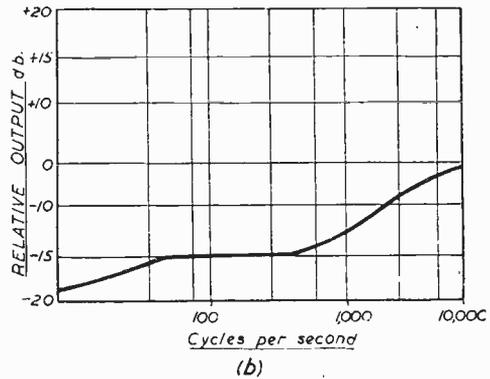
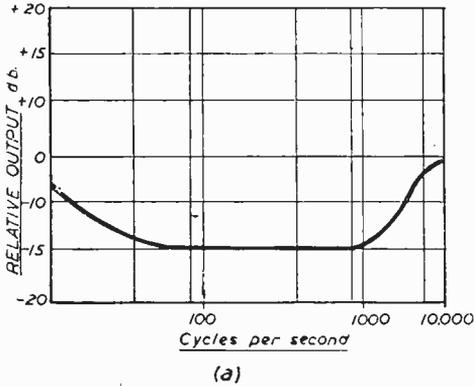


Fig. 2(a).—Approximate crystal pick-up response and (b).—Approximate magnetic pick-up response.

necessary to have two interchangeable pick-up heads, one for standard and the other for microgroove recordings. These, if necessary, should be counter-balanced so that the needle pressure on the microgroove record does not exceed 10 grams, which is the maximum approved weight.

Pick-up Design

Pick-ups have been designed fitted with a stylus of each type, and so arranged that it is possible by turning the head over to bring the appropriate one into use. This arrangement, of course, has a distinct advantage from the user's point of view, but unless facilities which provide a change of tone-arm balance are also incorporated, the long-playing record may suffer undue wear, for it must be borne in mind that the weight requirements differ between the two types of records. An "all-purpose" stylus in a head of compromise design is sometimes used to reproduce alike standard and long-playing records. This method, however, is not considered the best practice, for both record and stylus wear are accelerated after the first few playings.

The curves of Fig. 1 illustrate the difference between standard and microgroove recording characteristics, and, as will be observed, the most striking difference is the reduced bass response of the long-playing records, for it shows an almost constant rise from the low to the high frequencies, as compared with the much more linear response of standard records.

This is made necessary by recording amplitude limitations governed by the spacing between the grooves, for it follows that if the recording amplitude were to take the more linear form adopted on standard

by the crystal bears a relationship proportional to the amplitude of needle movement, whereas with the magnetic type it is the velocity of the needle movement that determines the generated output. In any case, the output from both types will, of course, be less with microgroove than with 78 r.p.m. recordings, owing to the enforced reduction in general recording level of the former, which amounts to about minus 8 db. at 1,000 c.p.s. On the other hand, however, a reduction in velocity of movement affects the magnetic pick-up to a greater extent than the reduction in

(Continued on page 161)

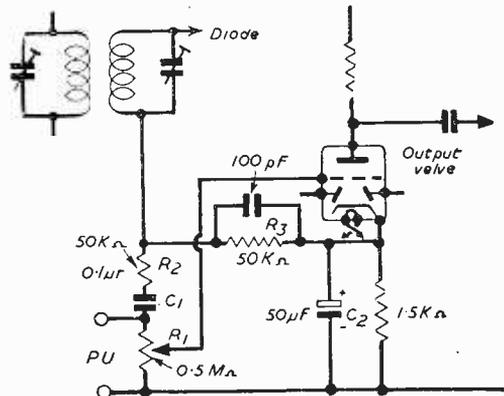


Fig. 3.—A typical pick-up input circuit of an average receiver.



22/6 FLUORESCENT LIGHTING
40 WATT

Complete kit comprises Hi-craft 40 watt control unit, starter lamp, lamp holders, clips, and wiring diagram. Price 22/6 plus 1/6, or for callers only, complete with 40 watt daylight tube, 32/6.

FLUORESCENT LIGHTING BALLAST UNITS

40-Watt Type. This is a combination condenser and choke unit for controlling fluorescent tubes. The only other item needed is a starter switch which can be an automatic type or an ordinary on/off manually operated type. We offer these well priced units at less than half price, namely 16/6 each.

STARTER LAMP

For fluorescent lighting 2-pin SBC, suits all types of tubes. 3/6 each. Lamp holder 2-pin SBC, 1/9.

OUTSTANDING VALUE OF NEW PRODUCTION

MODEL B. Six Wavebands, 11-15 metres continuous in 5 ranges (4 Bands spread) and M.W. 185-550 metres. Six position Tone Switch (3 Radio-3 Gram). Price £15/15/- plus 7/6 carr. and insurance, or H.P. Terms £5/9/- deposit.

MODEL B3. Three Waveband. Long, Medium, Short Gram. switching on wave change switch, 3 position Tone. Price £12/12/- plus 7/6 carr. and insurance, or H.P. Terms £4/6/- deposit. Both chassis 1 1/2 in. x 7 in. x 8 in. high. Latest type valves: 6BQ6, 6BA6, 6AT6, 6BW6, 6X4. A.C. mains operated, flywheel tuning, negative feedback over knobs, fully guaranteed.

BUILT TO HIGHEST PERFORMANCE STANDARD AND SPECIFICATION

MAGNETIC TAPE RECORDER KIT—YOURS FOR £11/14/6



Total cost, £35.
Cabinet only, £4/17/6.
Tape Deck only, £16/10/-.

Tape Deck. Fitted with 3 motors giving fast rewind/forward run and no friction. High fidelity record playback giving approximately 1 hour playing from standard 1,200ft. tape. Tape, 35/- per reel.

Amplifier. High gain enables recording to be made from microphone, pick-up, or loudspeaker. Separate bass and treble lift controls.

Cabinet. Portable. is rexine covered, table model is polished walnut.


Instruction Booklet. Shows in close detail exactly how to assemble and operate the recorder. is free with kit or available separately at 5/- (credited if you buy kit or complete recorder). Complete kit of parts, including 6 B.V.A. valves, loudspeaker and cabinet (state whether portable or table model required). Price £35, or £11/14/6 deposit and 12 monthly payments of £2/6/3. Carriage/ins. 10/- extra.

RADIO STETHOSCOPE

A novel device aptly called a Radio Stethoscope is described in a recent edition of the "Radio Constructor," this is compact and can be slipped into the pocket rather like a fountain pen. With it in most districts a receiver can be checked from the grid of the first valve right through to the output without a signal generator, the stethoscope will operate in both L.F. and R.F. circuits without alteration. It is a complete fault finder.

The only parts needed to make the simple circuit tracer are a pair of crocodile clips, a germanium crystal, and a paper tubular condenser and we will supply whole outfit for 6/6, post free, and with each outfit we will give re-print of the article as it appeared in the "Radio Constructor."

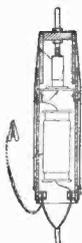
NOTE.—If you wish to make it up as a pocket unit then you will need a few other odds and ends, solder tags, etc., from your spares box.



T.V. SERVICING AID

Will enable service engineers to check video response, stage gain, etc., without removing the chassis from the cabinet.

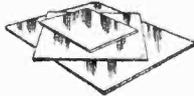
Kit comprises BTG Plug, germanium crystal and indicator lamp together with making and operating instructions. Price only 6/6. Ditto, available for B9A, also 6/6.



SHEET PAXOLIN

Invaluable for when you are experimenting. Size 12in. x 8in. 2/- Size 12in. x 12in. 3/6. Size 24in. x 12in. 6/-

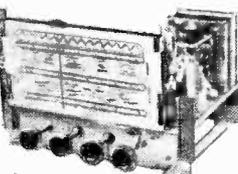Special offer this month—12 pieces, each 8in. x 5in. medium thickness for 6/-.



29 GNS. AUTO RADIO GRAM 29 GNS.

Console type Cabinet. With full grained walnut finish, will take standard type auto change gram. unit. Price £11/10/-, H.P. Terms, £3/17/- deposit and 12 monthly payments of 16/9, plus 15/- carriage. **Radio Chassis to suit, £8/19/6.** H.P. Terms, £3 deposit and 10 monthly payments of 13/-, plus 7/6 carriage.

Auto Change Units. For long playing and standard records with suitable pick-up head. £11/11/-, 5 years of service. Slightly **SPECIAL OFFER.**—Cabinet, Radio chassis and Auto Changer, 29 Gns. H.P. Terms, £10/14/- deposit and 12 monthly payments of £2/3/-. Non-callers add £1 carr. and ins.



R.1155 FOR £2/14/-




This set, as most will know, is considered to be one of the finest communications receivers available today. The frequency range is 70 kc/s to 18 Mc/s. It is complete with 10 valves and is fitted in a black metal case. Made for the R.A.F., so obviously a robust receiver which will give years of service. Slightly used but completely overhauled and guaranteed in perfect working order. Price £7/19/6, or will be sent against a deposit of £2/14/-, balance 12 monthly payments of 11/6. If you cannot call to collect please include an additional 10/- to cover cost of transit and carriage. This partly returnable to you if and when you return the transit case.

MAINS POWER PACK FOR R.1155
With pentode output stage. Plugs into socket on receiver so no internal modifications are required. Price £5/10/- complete with 5in. speaker ready to work, carriage 3/6.

PROFESSIONAL RADIOS YOU CAN MAKE


You will find that the building of our all-mains radio receivers is simplicity itself, and the more you make the less time each takes; everything down to the last nut and bolt is supplied and everything fits together in a professional manner. When finished the receiver looks and plays as well as those being offered in radio shops at anything between £10 and £14. The one illustrated above we call the "Occasional," in a choice of colours, Ivory or Walnut and the T.R.F. costs £6/1/6 plus 2/6 post and insurance (H.P. terms being £2/1/6 deposit and 10 monthly payments of 10/6), while the superhet costs approximately £9 (H.P. terms £3/2/- deposit and 12 monthly payments of 13/6).

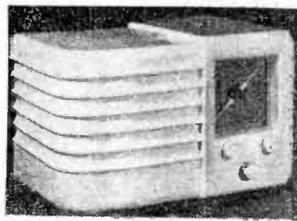

The other radio illustrated we call the "White Lady." This is an extra fine cabinet, pure white. The complete T.R.F. receiver costs £6/5/-, H.P. terms being £2/3/- deposit and 10 monthly payments of 10/9. Constructional data for either set is available at 1/6, post free.

ADJUSTABLE THERMOSTATS

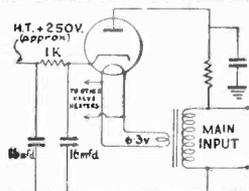250 v. heavy silver contacts can be adjusted to operate between 70-300 deg. F. These are suitable for aquarium heaters, electric blankets, etc. 1 Amp. Model 3/6. 2 Amp. Model 5/6. 5 Amp. Model 14/6. Post, etc., 6d. extra. Don't be cold this winter, make an Electric Blanket, blueprint 1/6, post free.



A POWER PACK FOR 15-

Efficient power supply, O.K. for operating a receiver, amplifier, instrument or other device requiring up to 60 mA. at approx. 250v. Parcel consists of filament transformer, rectifying valve, smoothing resistor and 16 x 16 md. 350v. electrolytic condenser. Note the filament transformer will supply enough current to operate 3 or 4 other valves.

SMALL CONDENSERS

Moulded mica, silver mica, ceramic, paper tubular, all values up to .01 mfd. normal 350v. working, 6d. each, 1 mfd. 9d. each, .5 mfd. 7d. each, 1 mfd. 1/3 each.

ELECTRONIC PRECISION EQUIPMENT DEPT. 7
42-46 WINDMILL HILL RUISLIP MIDDLESEX
152-3 FLEET ST. LONDON E.C.4.

MINIATURE SWITCHES

for
constructors
and
engineers



by

ARROW

ARROW offer you a special range of miniature switches at competitive prices. Look in your local dealer's window for the Arrow Display Box showing 10 different types or ask him to get you full particulars of the switch you want. Insist on ARROW switches and get the best results.

ARROW ELECTRIC SWITCHES LTD.
HANGER LANE · EALING · W.5

Best Buy at Britain's

U.F.E. Receiver R1132A covers 100-124 Mc/s with variable slow-motion tuning. A complete receiver with all normal controls. 11 valves, tuning meter, etc. Brand new in case with circuit. **ONLY £4/10/-** Jones' plus supplied free. Carriage 10/6 extra. Coils easily converted for Wrotham or 144 Mc/s.

Communication Receiver R1155—Brand new with 10 valves. £11/19/6. Soiled for £7/19/6. Carriage 10/6 extra. Send 1/3 for full details and circuit.

Power Pack/Output Stage enables R1155 to be operated from A.C. mains. Complete with valves, plugs, etc., and 6 months' guarantee. Price £4/10/- plus 3/6 carriage. **Save Money**—A brand new R1155 with power pack/output stage, only £15/19/6, plus 12/6 carriage.

R.F. Units—Type 26 and 27—Type 26 covers 50-65 Mc/s and type 27 covers 65-85 Mc/s. These are converter units for the R1355, but can be used with any receiver tuning to 7.5 Mc/s. Brand new and boxed, either type 55/6 post paid.

Miniature Transformer—Primary 230 volts 50 cycle. Sec. 230-0-230 volts 50 mA., 6.3 volts 2.5 amps. Brand new and boxed, 10/- plus 1/- post.

Standard Transformer—200 230 250 volts 50 cycles. Sec. 325-0-325 volts 72 mA., 6.3 volts 2.5 amps., 5 volts 2 amps. Half-shrouded, drop-through. Brand new at 12/6, plus 1/6 post.

EF50 Red Sylvania Valves at 8/6 each. British types at 5/- each, postage 6d. Many other valves in stock.

Time Switches, 230 volts 50 cycles. Makes or breaks a circuit. Two types—0-15 or 0-30 minutes. Either type, 17/6, plus 2/6 post-packing.



CHARLES BRITAIN (RADIO) LTD.

11, Upper Saint Martin's Lane, London, W.C.2. **TEAM 0545**

Shop hours, 9-6 p.m. (9-1 p.m. Thursday)

—OPEN ALL DAY SATURDAY—

CHOOSE YOUR FREE GIFT!

FULL DETAILS FOR CONSTRUCTING EITHER A **CAR RADIO**

OR **ECONOMY SUPERHET**

GIVEN

FREE

with every copy of our

HOME CONSTRUCTORS HANDBOOK

Price 2/6 Post Free.

With 15 tried and tested circuits, constructional notes, hints, data, and full details on how to build a Superhet Coil Pack

This is

1953's BEST BARGAIN

SEND FOR YOUR COPY TO-DAY Full Illustrated Catalogue included.

NEW COMPONENT BARGAINS!

- Resistors, 25 standard values (mixed) ... 7/6
- Condensers, 25 standard values (mixed) ... 12/-
- I.F. Trans., *aligned 465 Kc/s (pair) ... 12/5
- T.R.F. Coils. Dual range (pair) 8/-
- Dials, Gangs, Transformers, Chassis, Valves, Holders, Switches and all Components in stock.

Stamp for Catalogue.

SUPACOILS MAIL ORDER OFFICE
98, GREENWAY AVENUE, LONDON, E.17.

LONDON CENTRAL RADIO STORES

Philco. Reconditioned. 5 Valve. 2 Waveband. A.C. or A.C./D.C. Size 18 1/2 in. x 14 1/2 in. x 9 1/2 in. Equal to New. £7-10-0. P.P. 10/6.

Cossor Double Beam Oscilloscope, 3339A, £37-10-0.

Ex-R.A.F. Aerial Coupling Unit. Fitted with Ammeter 0-30 in Metal Case. Size: 6 in. x 5 in. x 5 in., 9/6.

New Browns Single Adjustable Phones, 60 ohms. 5/6 each.

P.A. Loudspeakers, with Metal Frame about 4 1/2 long. £5-10-0.

New Instrument Metal Rectifiers, 24-volt 80 mA., 2/3.

New P.O. Plugs and Jacks, 2/6.

New P.O. Carbon Mike Inserts, 2/6.

Cosalt Cable for Television, 70 ohms. 15-12 yds.

P.O. Electro Magnetic Counters, 15-, 9d. P. & P.

P.M. Loudspeakers, 9-, 1/6 P. & P.

Glass Cell Accumulators, 12 in Crate, 24 volt, 3 amp, 17/6.

Can still supply Reconditioned Philco Sets, 220-230 v. All Guaranteed. A.C. or A.C./D.C. £4-0-0, 10/6 Carr. and Packing.

A.C./D.C. Geared Laminated Motors, 24 v. unshrouded. Size: 5 in. x 3 1/2 in. x 2 1/2 in., 22/6.

Infra-Red Photo Electric Cells, Type CV143. Image Converter Tube, 14/6.

For Walkie-Talkies, Uniselectar Switches, Vibrators, etc., etc., see previous issue.

WE WANT TO BUY RADIO EQUIPMENT — AMPLIFIERS — TAPE RECORDERS — TELEVISION TEST EQUIPMENT — COMPONENTS

London Central Radio Stores

23, LISLE STREET, W.C.2

Phone Grams: GERrard 2969

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH

CALL OR SEND DRAWINGS FOR QUOTATION

B. KOSKIE

(DEPT. C.)

72-76 Leather Lane,

Holborn, E.C.1

Phone: HOLborn 4777

NEW GOODS ONLY

CONDENSERS—50 v. wkg. 1 mfd. 2/9; 1.32; 8; 3-; 16.46; 32.510; 8-4.48; 8-16.5/8; 16-16.6/9; 500 v. wkg. 1 mfd. 3-; 2.3/-; 4.33; 8.3/6; 16.6/-; 32.8/-; 38.7-; 8-16.8/3; 16-16.9/6; 25 x 25 v. 50 x 50 v., 50 x 12 v., 2.3; 50 x 50 v., 2/6.

Tubulars, 500 v. wkg. up to 0.005. 8d.; 1c 006. 9d.; to .01. 11d.; to .1. 1/2; .2. 25. 1/6; .5. 2/3; Moulded Mica. up to .002 1/-; to .01. 1/6; Sil. Mica. 500 v. wkg. up to 100 pf. 9d.; to 500 pf. 1/-; to 1,000 pf. 1/2. 2.000, 3.000 pf. 1/3.

SMOK & BEMCO PARTS at list prices **VOLUME CONTROLS**—Lg. Spdls., all Values, 3/-; with Sw. 5/-; with D.P. sw. 5/9; Semi Midg. type, 1. 1. 1. 2 meg., 4/-; with sw., 5/9; D.P. sw., 6/6; Wire Wound less sw., 1 k. to 80 k., 6/6; 100 k., 7/9.

RESISTORS—All Std. values, 20% Tol 4 w. 5d.; 4 w. 6d.; 1 w. 8d.; 2 w., 1/-; Wire Wound, 3 w. to 5 k., 1/9; 5 w. to 5 k., 2/-; 10 w. to 10 k., 2/9. Terms: Orders up to 10/-, post 6d.; up to £1. 9d.; over, post free. Cash with order, no C.O.D.; lists 3d.

RADIO ELECTRON
22, FRANCES STREET, SCUNTHORPE, LINCOLNSHIRE.

VALVES—6J6, 6SN7GT, 6BW6, 6BE6, 6BA6, 6A6, 6L6, 12BE6, 12BA6, 807, 9/6, EF92 (W77, 9D6), 5Y3GT, 717A, VS70, V508, CV57, 6U5G (Magic Eye), 6K7MET, 6AT6 (0.1H7), 80L2, 6AM6 (RD3, EF91, Z77, 6F12), 8-174, 185, 3V4, 3A4, 1U5, 6N7GT, VS110A, 7/6, EL32, 7-; PEN46, 6K7G, 6K7GT, 12SL7GT, 12U5GT, 12SH7, 6B8, 6/6, 6AL5 (EB91, D77, 6D2, DD6), 6/-; VG12B8, 12B9A, VT101, VR137, 5/6, 1625, 5/-; VT20A, VR85, 7/9; 3/6, VR3, 3/-; VR92, 2/6, OC3-VR105, 9/6, 6SL7GT, 10/6, 80, 11/-; EF39, 11/6, 6K8G, 8K8GT, 8/6, 6V6G, 6V6GT, 7/6, 1A5GT, 5/-.

All Valves despatched by Return of Post. **VALVEHOUSERS**—EF50 Ceramic, 2/6 for 6. Mazda Catal. 2/6 for 6. B7C Amphenol, 5/- for 6. B8A Amphenol, 5/- for 6. British 4-pin Ceramic, 1/- for 2. UX 7-pin Ceramic, 2/6 for 2. UX 5-pin, 1/3 for 2. VCR97 Base, 2/6 each.

HEADPHONES (U.S.A. Manufacture)—75 ohms, 6/- pair. Single Earphone (U.S.A. Manufacture), 150 ohms, 2/6 each. Headphones, M/c. 40 ohms, very sensitive, 7/6 pair.

HEADSET ADAPTORS—High to low impedance, 2/6.

HAND MIKES—M/c. with Switch, 7/6. Transformer to match, 3/6.

HAND MIKES—Carbon with Switch (Shure Manufacture), 9/6.

HAND MIKES—Moving Iron with Switch, 4/6. Transformer to match, 3/6.

TROUPE MIKES—Moving Iron, 2/6.

VOLUME CONTROLS—Short Spindle, 2K, 3K, 5K, 20K, 50K, 100K, 7/6. For 6 assorted or one type only. Twin Gang, 1 meg., 2/6 each.

CONDENSERS—Block Type, approx. 2 x 1 x 3 in., 1 mfd., 5 mfd., 1 mfd., 2 mfd., 400 v. working, .25 mfd., 1,500 v. working 4/6 for 4 or 11/6 for 12. Multiblock Type, approx. 2 x 2 1/2 x 2 1/2 in., 2 mfd., .25 mfd., 2 mfd. twice, 3 mfd., 350 v. working, 2/9 each.

CONDENSERS—Tubular, .25 mfd., 800 v. working, 2/- for 2.

CONDENSERS—Sprague Tubular, .25 mfd., 500 v., 2/- for 3. Special Offer Sprague .05 mfd., 160 v., 5/- each.

J. B. SERVICE

(BEXLEYHEATH), LTD.

5, MAYPLACE ROAD WEST, BEXLEYHEATH, KENT.

(Continued from page 158)

amplitude affects the crystal. Furthermore, the properties of the crystal provides an increase in output voltage at the lower frequencies (see Fig. 2a), but, although this does not wholly counteract the deficiency of bass in the recording, it does enable the crystal pick-up to be used, to a degree of satisfaction, on standard amplifiers and radios without extensive bass correction measures being necessary.

Owing to the reduction in needle velocity, coupled with the reduced response of long-playing records at the lower frequencies, it is easily realised that if we reproduce them via the medium of a magnetic head, the loss of bass will be more apparent than ever (see Fig. 2b), and will result in thin and reedy reproduction. Extensive measures are, therefore, necessary to give the desired bass-boost to an amplifier used in conjunction with a magnetic head to reproduce long-playing records—for usually the degree of compensation afforded by standard equipment is sufficient only to give the correct bass-boost to 78 r.p.m. records.

Another added advantage in favour of the crystal pick-up for general use is that it generates nearly three times as much voltage as the magnetic type

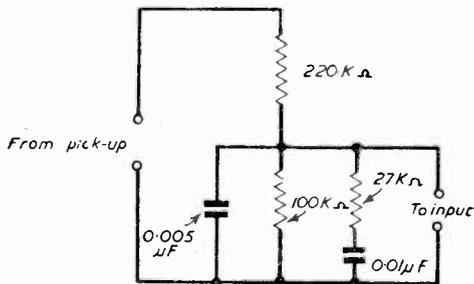


Fig. 4.—A bass-boost circuit for a magnetic long-playing pick-up.

operating under the same conditions. Therefore, apart from requiring extensive bass-boost, magnetic heads invariably require a pre-amplifier stage before they can be used successfully to drive a standard radio or amplifier.

The Motor

It is of paramount importance to the good reproduction of microgroove records that the motor speed be constant. With induction type motors, power-cuts obviously have some effect on their speed, but in this connection little can be done by the constructor. He should, however, ensure that the motor is free from drag, and that the moving parts are free-running and as near to being frictionless as mechanical ability will allow.

A motor which is running constantly a revolution or so fast or slow, will have little effect on performance; the trouble starts when the motor speed changes during an actual playing, for the effect is much more discernible on microgroove than on 78 r.p.m. discs.

The rim-drive motor is commonly employed nowadays, and is easily arranged to cater for the three speeds demanded of present-day records. These are much less expensive than their governor type counterparts, and are adequately suited for the needs of the home constructor. They should, of course, be well

maintained; should a rumble or uneven motion suddenly develop, however, the rubber drive pulley will often be found to be worn, not perfectly even and smooth, but with a slight flat, which necessitates only the replacement of the worn pulley to bring the motor back to its normal smooth running condition.

Three-speed automatic record-changers have been developed using the rim-drive method, and follow closely the standard style of machine apart from, perhaps, the auto-trip mechanism. The old style of rotating striker would, of course, tend to jar the needle out of the groove each time it came into operation, so now a very light ratchet arrangement is employed which functions on the outward swing of the tone-arm from the centre of the eccentric play-out groove.

Pick-up Matching

In the main, the problems associated with changing over from 78 r.p.m. to long-playing records boil down to a poor bass response, coupled with inadequate volume. It matters not whether one is using an ordinary radio receiver or high-fidelity amplifier, the problems are there just the same, although, in certain cases, they may be more pronounced than in others.

Let us suppose, for instance, that we have a standard

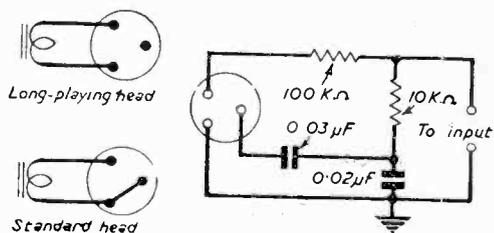


Fig. 5.—Automatic compensation system used in conjunction with Decca pick-ups.

radio receiver installed with pick-up terminals; and in conjunction with this we wish to use an add-on long-playing record unit which incorporates a crystal pick-up. As previously intimated, sufficient voltage is usually provided by this style of pick-up to feed straight into the pick-up terminals of an average receiver, therefore in this respect, at least, little trouble should be experienced. But from the quality point of view, the story might well be a little different.

It is most important to remember that when using a crystal pick-up its frequency response is critically dependent on the value of load impedance it works into. The correct figure is always given by the manufacturers, and should be strictly adhered to by the constructor. Too low a value has the effect of severely limiting the bass response of the pick-up, just the opposite to what we want for good reproduction.

Now to get back to our receiver. If we examine the input section we shall find quite probably that it closely follows the circuit of Fig. 3. Here R1 constitutes the volume-control, across which the pick-up terminals are connected. This style of receiver rarely employs a "gram/radio" change-over switch, for it is left to the operator either to de-tune the receiver or take out the aerial to prevent radio break-through whilst using a record-player. This means, then, that the pick-up is shunted not only with the ½ megohm volume-control, but also with the additional im-

pedance offered by the elements comprising C1, R2, R3 and C2. These, as will be seen, are fairly low in value, and result in an overall pick-up load impedance far too small for a desirable bass response.

The situation in this case may be eased by providing a "gram/radio" switch to disconnect C1 from the top end of R1 and the pick-up terminal. The total pick-up load impedance will then be governed solely by the value of the volume-control.

In older receivers a capacitor resistor combination was often employed across the pick-up terminals to damp the high resonant frequencies, which characterised the vintage type magnetic pick-ups. It follows, of course, that components of this nature must be removed from the circuit before satisfactory long-playing record reproduction can be attained.

If the inherent receiver design does not allow the necessary high value pick-up load impedance to be acquired, an additional resistor, to make up the stipulated value, should be included in series with the pick-up and the pick-up sockets. This arrangement not only facilitates the matching, but as it functions as a form of potential divider, it attenuates the voltage from the pick-up as fed to the grid of the valve by a ratio dependent on the value of the series resistance, and the impedance as measured at the pick-up sockets of the receiver.

If the constructor desires to play both kinds of records on an existing amplifier or receiver, it will be as well to fit a two-way switch arranged so that the long-playing position cuts out the existing compensation, and brings in the necessary matching components. In fact, some long-playing record units can be obtained already fitted with this kind of change-over switch.

Maintaining the bass response from a receiver used in conjunction with a magnetic pick-up demands different tactics. In this case it is usually found necessary to employ a tone-compensating network in series with the pick-up and input terminals. The component values used in the network will depend to a large extent on the design of the pick-up, and in this respect it is always advisable to seek assistance from the appropriate manufacturer.

For experimental purposes the simple circuit of Fig. 4 can be used, and if the indicated component values are employed the circuit will give a response very nearly equal to the reciprocal of the microgroove recording characteristic curve of Fig. 1b.

The Decca magnetic interchangeable head pick-up uses a similar circuit, which is automatically brought into operation by plugging in the long-playing head. This is facilitated by means of a three-pin plug on the head and a three-pin socket on the tone-arm. Fig. 5 illustrates this point, and it is clearly seen how the appropriate compensation is achieved. Furthermore, as the heads are of different weights, the problem of needle-pressure compensation is also solved.

No matter what method is adopted to provide bass-boost, however, the effective pick-up output voltage is bound to be attenuated, and very little is left to feed the receiver or amplifier—often little more than 20 milli-volts! When it is realised that a normal receiver needs at least a quarter of a volt to give satisfactory volume, it becomes obvious that additional features are demanded for the reproduction of long-playing records when using a magnetic pick-up. In certain receivers it will probably be necessary to add an extra valve, though it is sometimes possible to

change one of the audio valves to a type giving a higher gain.

Hum troubles are likely to develop in the course of these modifications, and this point should be carefully considered, for the brilliant quality which long-playing records are capable of giving can be easily spoilt by a background of hum.

PHILIPS' ARTISTES DEPARTMENT

PHILIPS announce the acquisition of the Columbia American label, which means that they will periodically be issuing records of such famous celebrities as Frankie Laine, Jo Stafford, Guy Mitchell, Johnnie Ray, Doris Day, Rosemary Clooney, Mitch Miller, Paul Weston, Toni Arden, Frank Sinatra, etc.—names already established throughout Great Britain.

They also have under exclusive recording contracts the following British artistes, Gracie Fields, Flanagan and Allen, David Hughes (now starring in the London show, "Paris to Piccadilly"), Gary Miller, Jean Carson and Johnny Brandon (two latter names currently appearing in Emile Littler's "Love From Judy"), Hermione Gingold, Gilbert Harding and Geraldo.

They will be utilising various musical directors and arrangers and the first record issues contain the names Norman Warren, Geoff Love, Bruce Campbell, Geraldo and Peter Yorke. They are not exclusively employing any musical directors on Philips records as they intend to promote a policy of experimenting in the arranging field and building up names to world prominence.

It is also intended to build up as many new British personalities as possible for world exploitation by the Philips organisation, following the practice previously adopted by Leonard Smith and Norman Newell, late of Columbia records, and now responsible for the artistes side of the Philips organisation. Rita Williams will be responsible for vocal group commissions on Philips records.

As a temporary measure recording will be undertaken by Universal Programmes Corporation, 35, Portland Place, W.1, and until the acquisition of their own studios they are recording at Portland Place and Conway Hall.

JOIN THE PRACTICAL GROUP

Edited by F. J. CAMM

PRACTICAL WIRELESS, 1/-
Every Month.

PRACTICAL MECHANICS, 1/-
Every Month.
Devoted to Mechanics, Science and Invention.

PRACTICAL ENGINEERING, 6d.
Every Friday.
For Engineers, Mechanics, Designers and Works Managers.




A PORTABLE TAPE RECORDER

NOT A KIT BUT A FACTORY BUILT JOB. By a well-known manufacturer. Simple to operate. Finest quality components throughout.

BRAND NEW—UNUSED—COMPLETE

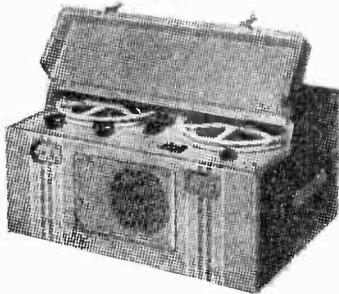- ★ Attractive carrying case.
- ★ Twin track recording.
- ★ Instant playback.
- ★ Size of case : 17 x 12 x 7in.
- ★ Total playing time of 66 mins.
- ★ 6 Valves.
- ★ Weight 31 lbs.
- ★ A.C. mains 200-250 v.
- ★ Fast rewind.
- ★ Record level indicator.
- ★ Complete. Ready to switch on.



Supplied fully assembled and wired, with all valves, 1,200ft. spool of tape, take-up spool, crystal hand microphone, instruction book, and circuit diagram.

MAKE NO MISTAKE—YOU MUST SEE AND HEAR THIS

LASKY'S PRICE
£34 - 19 - 6


Carriage and insurance 15/-

THE RECORDING AMPLIFIER

As used in the recorder above. 6 valves, 2 6V6 ; 2 6J7 ; 1 6J5 ; 1 5Z4. Supplied fully assembled and wired, with all valves and 5in. speaker. Ready for use, 200-250 volt A.C. mains. Size —15in. wide, 8in. deep, 6in. high. Circuit available.

LASKY'S PRICE
£8 - 19 - 6

Carriage and insurance 10/- extra.

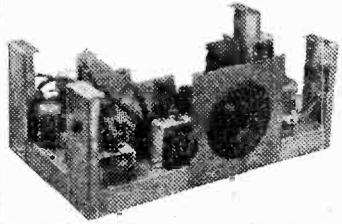

PORTABLE CABINETS
As illustrated. Can be supplied separately.
LASKY'S PRICE £3.15.0 Carriage 10/- extra

1S4	9/-	1A5	9/-
3S4	9/-	XSG	5/-
1T4	9/-	XP	5/-
1R5	9/-	XH	3/6
1S5	9/-	3Q5	9/-
1C5	9/-	6K7	6/6
VU111	3/6	VU120	2/6

6J7	6/6	EF39	7/6
HL2	3/6	12K7	10/6
KT2	3/6	6L5	10/6
6K3	13/6	EASO	2/6
U50	9/-	EBC33	7/6
ECH35	13/6	35L6	10/-
RK74	2/-	FX25	10/-

50L6	10/-	35Z4	9/-
6AM6	10/6	6H6	2/6
EF50, Red	10/-	ECH35	13/6
New Sylvania	12/6		

VALVES. 10,000 IN STOCK. AT THE LOWEST POSSIBLE PRICES.

Write for complete list.

12 Valves for the Viewmaster. All as specified £8/10/0.

17 Valves for the Tele King. All as specified. £12 4/10.

OUTPUT TRANSFORMERS

40 mA Multi ratio	6/11
80 mA Multi ratio	14/11
80 mA Pentode	12/6
60 mA Plessey, 6,000 ohms	5/11
Standard pentode	4/11
Pentode	3/6
Midret. Pentode	4/3
Miniature pentode, 3S4, JS4	4/6
PX4 Intervalve	8/6
5:1 Intervalve	5/11

P.M. LOUDSPEAKERS

All less o'trans. new and unused. First quality.

3in. Elac	12/11
5in. Plessey	12/6
6in. Goodmans	13/6
8in. Rola	15/-
10in. Plessey	25/-

EX-A.M. RECEIVER TYPE R1155

Brand new and unused. Aerial tested before despatch. Supplied complete with 10 valves. Circuit : B.P.O. A.V.C. R.F. Amp., two I.F. Stages, Magic Eye, etc. etc.

5 Frequency ranges : 18.5-7.5 Mc/s ; 7.5-3.0 Mc/s ; 1,500-600 Kc/s ; 500-200 Kc/s ; 200-75 Kc/s.

Supplied in maker's original wood transit case. LASKY'S PRICE. £11 19/6. Complete. Carriage 12/6 extra.

USED MODEL R1155 RECEIVERS.

Aerial tested before despatch. Complete with 10 valves.
LASKY'S PRICE £7/19/6. Carriage 12/6 extra.

FULLY ASSEMBLED POWER PACK AND OUTPUT STAGE FOR R1155 RECEIVERS. For use on 200-250 volt A.C. mains. Wired and complete with valves.
LASKY'S PRICE 79/6 Carriage 5/- extra.

ROTHERMEL (DEAF AID) CRYSTAL MICROPHONES. Diaphragm driven. Extremely sensitive, can be used for tape recording, etc. Miniature 1 1/2in. diam., 1/2in. thick. 7/6 POST FREE.

SUPERHET COILS

Aerial and oscillator. For 465 Kc/s I.F. Supplied with circuit. Size, each coil : 1 1/2in. high, 1 1/2in. diam. No. 1. Long and medium wave. 2/11 per pair. No. 2. 10-30 Metres. 1/11 per pair. Postage 9d. per pair extra.

SUPERHET COIL PACKS

3 Wavebands : 12-35 metres ; 35-100 metres ; 200-550 metres. Size : 4 x 4 x 3in. Price 16/-.


I.F. TRANSFORMERS

465 Kc/s Iron dust cores, in cans, midret. type. Size : 1in. x 1in. x 2in. Price, 12/6 per pair.

Wearite Type 550. Permeability tuned, 445-520 Kc/s. In cans, size : 3in. high, 1 1/2in. square. Price 12/6 per pair.

Wearite Type 500. Range 450-470 Kc/s, air cored, compression trimmer tuncd. In cans, size —3 1/2in. high 1 1/2in. square. 12/6 per pair.

INTER-COM. SETS

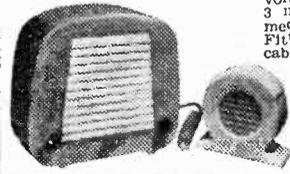

4-station operation. For use on A.C./D.C. mains 200-250 volts. Supplied complete, with 3 new valves, ready for immediate installation. Fitted in attractive plastic cabinet.

Can be used as baby alarm **MASTER UNIT, £7/15/0.** Carr. 5/- extra.

Extension Units. As illustrated, £11/1/-, Carriage 2/- each extra.

TWO-GANG TUNING CONDENSERS .0005MFD.

No. 1. Miniature. With Perspex dust cover and trimmers. Size : 1 1/2in. x 2in. x 1 1/2in. spindle. LASKY'S PRICE, 8/6.

No. 2. Midret. With trimmers. Size : 2in. x 1 1/2in. x 1 1/2in. spindle. LASKY'S PRICE, 8/6.

No. 3. Midret. Less trimmers. Size : 2in. x 1 1/2in. x 1 1/2in. spindle. LASKY'S PRICE, 6/6.

No. 4. Standard type. Size : 2 1/2in. x 2 1/2in. x 1 1/2in. spindle. LASKY'S PRICE, 6/6.

SPECIAL PARCEL OF MAINS DROPPING RESISTANCES.

Wire wound, 1, 2, 3 amp. 12 Assorted. 15/- POST FREE.

MAINS TRANSFORMERS

All 200-250 volts c.p.s. primary. Finest quality, fully guaranteed.

MBA 3. 350-0-350 v. 30 mA. 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. An ideal replacement trans. Price, 18/-.

MBA 5. 350-0-350 v. 125 mA. 6.3 v. 4 a., 5 v. 3 a. With mains tapping board. Price, 27/6.

MBA 6. 350-0-350 v. 100 mA. 6.3 v. 3 a., 5 v. 2 a. With mains tapping board. Price, 22/6.

MBA 7. 250-0-250 v. 60 mA. 6.3 v. 3 a., 5 v. 2 a. Both filaments tapped at 4 volts. Price, 18/-.

AT 3. Auto transformer. 0-10-120. 200-230-240 volts, 100 watt. Price, 17/6.

FILAMENT TRANSFORMERS

6.3 v. 1.5 a., 7/11
6.3 v. 4 a., 12/6
Special transformers. 2 amps, with the following tappings : 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volts. PRICE, 17/6.

LASKY'S RADIO

Lasky's (Harrow Road), Ltd.,
370, Harrow Road, Paddington, London, W.9

Telephone : CUNningham 1979-7214.

MAIL ORDER AND DESPATCH DEPARTMENTS : 485-487, HARROW ROAD, PADDINGTON, LONDON, W.10. Telephone : ADBrook 4075.

Hours : Mon. to Sat. 9.30 a.m. to 6 p.m. ; Thurs., half day, 1 p.m. Postage and packing charges (unless otherwise stated) : on orders value £11.5d. extra ; £5-25.0d. extra ; £10-35.6d. extra ; over £10 carriage free unless specifically stated otherwise. All goods fully insured in transit.

CONSTRUCTOR'S POLISHED CABINET. Size 10 x 6 1/2 x 5 1/2. approx., supplied in flatted form, grooved and ready to glue together. Complete with plastic front, 5 valve chassis, cadmium plated, size 8 1/2 x 4 x 1 1/2 in., tuning scale, knob and back. 10/- post and packing. 1/6.

Twin-gang and Pair of L. and M. T.R.F. Coils with circuit to suit above. 8/6.

Standard Wave-change Switches, 6-pole 3-way, 2/-; 4-pole 3-way 1/9; 5-pole 3-way, 1/9. Miniature 3-pole 4-way, 2-pole 5-way, 4-pole 3-way, 2/6.

Valveholders, Faxolin octal, 4d. Moulded octal, 7d. EF50 ceramic, 7d. Moulded BTG slightly soiled, 6d. Octal amphenol, 7d. Octal pax., 4d. Mazda Amph. 7d. Mazda pax., 4d. B3A, B3A amphenol, 7d. BTG with screening can, 1/6.

Trimmers, 5-40 pf., 5d.; 10-110, 10-250, 10-450 pf., 10d.

Twin-gang .0005 Tuning Condensers, 5- . With trimmers, 7/6.

Midget .00037 dust cover and trimmers, 8/6.

P.M. SPEAKERS

	with trans.	less trans.
2 1/2 in.	15/6
3 in.	13/6
3 1/2 in.	16/6
4 in.	12/6
4 1/2 in.	18/6
5 in.	15/-
10 in.	25/-

Post and packing on each of the above, 1/- extra.

Crystal pick-up with Sapphire Trailer Needle, 2/- each; with volume control, 23/-; post and packing on each, 1/-.

Constructor's Parcel, comprising chassis 8 in. x 4 in. x 1 1/2 in., with speaker and valveholder cut-outs, 5 in. P.M. speaker with transformer, twin gang with trimmers, pair T.R.F. coils long and medium, iron cored, four valveholders, 20 K. volume control and wave-change switch, 23/-, post and packing, 1/6.

Output Transformers, Standard type 5,000-ohms imp., 2-ohms speech coil, 4/9; Miniature type 42-1, 3/3. Multiratio 3,500, 7,000 and 14,000 2 ohms speech coil, price 5/6. 10-watt push-pull 6V6 matching 2 ohms speech coil, 7/-.

Mains transformers, primary 200-250 v. 280-0-280, 250 mA., 6 v. 6 amp., 5 v. 3 amp., drop-through, 29/6. P. & P., 3/-.

Mains Trans. Pri., 200-250 v. Sec., 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volt at 2 amps., 13/-; P. & P., 1/6. 300-0-300 100 mA., 6 v. 3 amp., 5 v. 2 amp., 25/-.

Terms of business:—Cash with order. Dispatch of goods within three days from receipt of order. Where post and packing charge is not stated, please add 1/- up to 10/-, 1/6 up to 21, and 2/- up to £2. All enquiries and Lists, stamped, addressed envelope.

D. COHEN RADIO AND TELEVISION COMPONENTS **23, HIGH STREET, ACTON, W.3.** (Opposite Granada Cinema)
Hours of Business: Saturdays 9-6 p.m. Wednesdays 9-1 p.m. Other days 9-4.30 p.m.

Drop-thro', 350-0-350 v. 70 mA., 6 v. 2.5 amp., 5 v. 2 amp., 14/6. 280-0-280, semi-shrouded drop-through, 80 mA., 6 v. 3 amp., 5 v. 2 amp., 16/6.

Semi-shrouded, drop-through, 280-0-280, 80 mA., 4 v. 6 amp., 4 v. 2 amp., 12/6.

Auto-wound, H.T. 280 v. at 360 mA., 4 v. 3 amp., 2 v. 3 amp. or 6 v. 3 amp. Separate 4 v. 3 amp. rectifier winding (upright or drop-through), 10/6.

350-0-350, 120 mA., 4 v. 4 amp., 4 v. 3 amp., drop-through, 21/-.

Auto-transformer, various combinations of voltages including 110 v. 70 watts, and 34 v. windings at 1 amp., 2 v. 1 amp., drop-through or upright mounting, 10/6.

250-0-250, 80 mA., 6 v. 3 amp., 12/6.

250-0-250, 80 mA., 6 v. 4 amp., 14/-.

Pri. 230 v. Sec. 200-0-200 35 mA., 6 v. 1 amp., 1 amp., 8/6.

Heater Transformer, Pri. 230-250 v. 6 v. 11 amp., 6/-; 2 v. 21 amp., 5/-; P. & P. each 1/-, 2, 4, or 6 volt 2 amp., 7/6.

Primary, 200-250 v. P. & P. on each, 1/6 extra.

Kit of parts for Signal generator. Coverage

110 Kcs.-320 Kcs., 320

Kcs.-900 Kcs., 900 Kcs.

2.7 Mcs., 2.75 Mcs.-8.5

Mcs., 8.5 Mcs.-20 Mcs.

Metal case 10 in. x 6 in.

x 4 in., size of scale

6 1/2 x 3 1/2, 2 valves

and 1 rectifier valve

A.C. mains 230/250.

Internal modulation 400

cps. to a depth of 30 per

cent. Frequency calibration

accuracy plus or minus

1 per cent. Modulated

or unmodulated

R.F. output continuously

variable 100 millivolts.

£3 10/- P. & P. 4/-


Circuit diagram and

point-to-point, 3/6. This


includes the return to us

for checking and calibration.

We will build for 15/- extra.

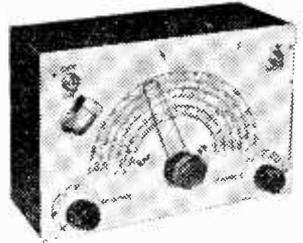

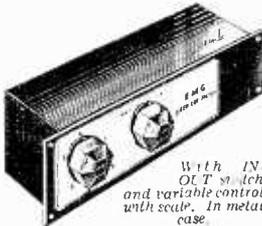A REMARKABLE ACHIEVEMENT IN FILTER DESIGN



With IN OUT switch and variable control with scale. In metal case.

THE E.M.G. STEEP CUTTING FILTER is infinitely variable, cutting at any desired frequency between 4,000 and 8,000 c.p.s. Connects between output transformer and 15 ohm speaker. Ideal for long playing and ordinary records, and heterodyne whistles on radio. No distortion, hum or appreciable loss of volume. Cuts at an average steepness of 30 db. per octave.

£4-10-0

Leaflet from the makers.

E.M.G. LTD. 6, NEWMAN ST., LONDON, W.1.

THE POCKET LOUDSPEAKER SET

Using our clear drawings and instructions you can build a midget loudspeaker receiver small enough to fit in the jacket pocket. This receiver is fully self-contained—no aerial, earth, or external power supply being required. The midget batteries used are of the new layer type specially produced by a famous British maker for this class of receiver. Only one single-gang midget variable condenser is used for tuning, and the receiver requires no alignment. The midget components chosen are current British production, not surplus or foreign.

Instructions and Drawings, including Theoretical Circuit and Point-to-Point Wiring Diagram.

PRICE 3/6 POST FREE.

SWIFT RADIO (W), 137 COTHAM BROW, BRISTOL, 6

Orders by Post Only.

"ADCOLA" SOLDERING INSTRUMENTS

Read Trade Mark



Regd. Design No. 800362 (British, U.S. and Foreign Patents)

For Wireless and Television Assembly

The advanced design of the Adcola Instruments meets the modern requirements of Television, Telecommunication and Radar Engineers

SUPPLIED FOR ALL VOLT RANGES FROM 6/7v. to 230/250v

3/16 in. dia. Bit. Standard Model ... 25/6

1/4 in. dia. Bit. Standard Model ... 28/-

3/16 in. dia. Detachable Bit. Model ... 33/6

Sole Manufacturers:

ADCOLA PRODUCTS LIMITED

GENERAL OFFICES & WORKS: CRANMER COURT, CLAPHAM HIGH STREET, LONDON, S.W.4. (MACaulay 4272)

SPARKS' DATA SHEETS

are the Safest and Finest Constructional Sheets of Guaranteed and Tested Radio Designs.

THE "MIDDY"

The finest Two-Valve All-dry battery design obtainable. Most popular and always praised. Med. and Long-waves plus "Ship-to-Shore" transmissions. Full-size Data Sheet, 3/21 Post Paid.

THE "BOSUN"


A Three-valve version of the above giving greater Range and Power. Full-size Data Sheet, 3/21 Post Paid.

NOW MEET THE "SKIPPER"

This is my Latest design. It is an exceptionally fine T.R.F. 4-valver having the same waveband coverage as those above. Safe and Efficient in any area. Good Selectivity, Range and Power. A fine Set for the Home. Data Sheet, etc., 3/21 Post Paid. SPARKS' DATA SHEETS COVER DESIGNS FROM A CRYSTAL SET TO A 9-VALVE QUALITY RADIOGRAM. SEND STAMP FOR LIST.

You can progress from "Middy" to "Bosun" to "Skipper" without wasting one Component.

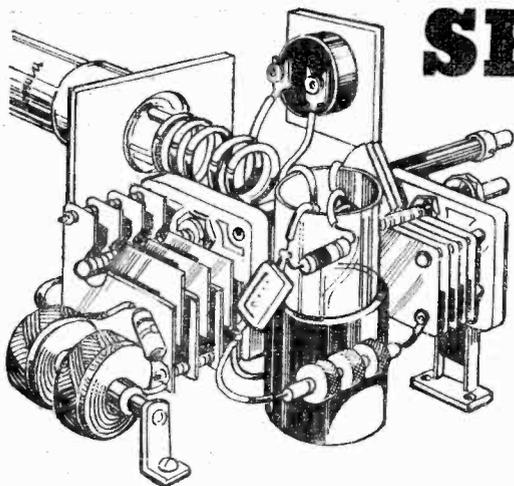L. ORMOND SPARKS (P), 48A, HIGH STREET, SWANAGE, DORSET.



SHORT-WAVE SECTION

Modern American Amateur Communication Receivers

2.—THE NATIONAL H.R.O. "SIXTY"

By A. W. Mann

The latest models designed and produced by the company are the H.R.O. "Sixty" and the N.C. 183D. In this article we are concerned with the former.

The H.R.O. "Sixty"

This design retains the well-known drawer type plug-in coil units, together with the National precision type tuning dial, but, in addition, an edge lighting, direct reading frequency scale is included. The range in use only being shown at one time.

THE senior model National H.R.O. amateur communications type receiver as available in this country previous to the war, was listed at £49 15s. complete with four plug-in coil units. The power pack and matched loudspeaker being available as separate items.

So far as the average amateur station receiving equipment was concerned, an H.R.O. senior model was the exception rather than the rule. Due to government disposal of surplus radio equipment, however, a considerable number of British amateur transmitting stations now include a senior H.R.O. among their receiving equipment.

Data

The valve line-up of this pre-war model was as follows: 1st R.F., 2nd R.F. and two I.F. valves were type 58. Mixer, 57. Second Det. 2B7, R.F. oscillator and B.F.O. respectively were type 57. Output valve, 2A5. The I.F. transformers being tuned to 456 kc/s.

The outstanding features of this model were the precision tuning dial, very efficient drawer type plug-in coil units, and band-spread facilities. The ranges covered being 1.7 to 4 Mc/s, 3.5 to 7.3 Mc/s, 7.0 to 14.4 Mc/s and 14.0 to 30 Mc/s. Additional coils were available if required.

The Senior H.R.O. is undoubtedly a very good receiver and still meets the requirements of many amateurs. So far as the 100 per cent. DX amateur is concerned, however, the rapidly increasing congestion on the amateur bands clearly demonstrates that even better amateur communications receivers will be required in order to guarantee a reasonable measure of consistent QSOs.

Post-war Models

The National Company, being fully aware of the situation, planned accordingly and produced the H.R.O. 50, followed by the H.R.O. 51, as well as other models.

Dual Conversion


In keeping with modern practice, dual conversion is used, the H.R.O. "Sixty" being what we term here a double superheterodyne.

There are three 456 kc/s I.F. stages employing 12 permeability tuned circuits on all bands and in addition one 2,010 kc/s I.F. stage on all frequencies above 7 Mc/s.

National Company practice in the past has been to build the heavy-duty power supply as a separate unit. In the present instance the power supply is built in, but very effectively isolated from the receiver section.

H.R.O. "Sixty" Coverage

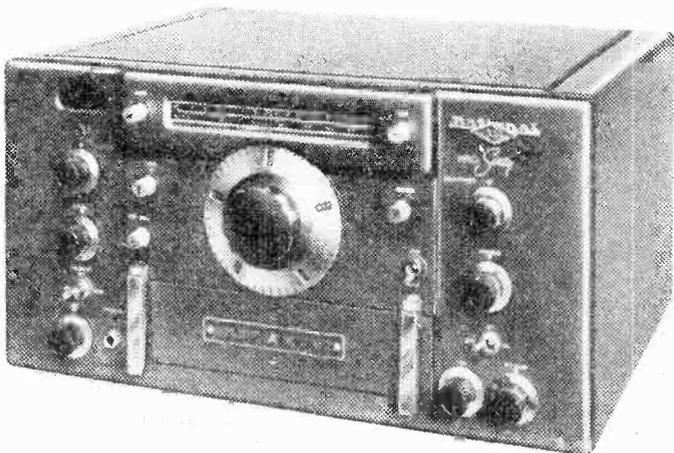The coverage of this receiver as supplied is as follows: 50 to 430 kc/s, 480 to 35 Mc/s, 50 to 54



The H.R.O. "Sixty." Photo by courtesy of the National Co., Inc.

Mc/s. "Phone, C.W. and N.F.M. being available with an adaptor.

Valve Complement

6BA6, 1st R.F.; same for 2nd R.F.; 6BE6, mixer; 6C4, H.F. osc.; 6BE6, 2nd H.F. converter; 6SG7, 1st I.F.; same for 2nd and 3rd I.F.s., 6H6, det. and A.V.C.; 6H6 auto noise limiter; 6SJ7, 1st audio; 6SN7 phase splitter and S meter amplifier; 6V6GT (two) PP audio; 5V4G, rectifier, 6SJ7, B.F.O.; OB2, voltage regulator; 4H4, osc. filament current regulator.

Sensitivity, 1Mv or better at 6 db signal-to-noise; selectivity being variable from 8 kc/s overall to approximately 1,200 cps at 40 db.

Power output 8 watts undistorted push-pull audio amplifier; fidelity plus or minus 2 db, 50-15,000 cycles at gramo input.

Image ratio: better than 65 db at any frequency up to 35 Mc/s. The makers claim that after warming up receiver frequency drift is negligible.

Other New Features

It is worthy of note that in the H.R.O. "Sixty," the H.F. oscillator and 6BE6 mixer heaters are current-regulated, and the H.F. oscillator and S meter amplifier are voltage-regulated.

Readers who were interested in the Select-0-Ject as described in Q.S.T., November, 1949, issue, will remember that this device will reject an unwanted signal, or on the other hand, boost a wanted signal above interference and background noise. A special accessory socket is fitted for the use of this unit, of which the National Company produce a commercial version.

Panel Controls

If readers will refer to the illustration accompanying this article they will gain a good idea as to the panel control layout. Top, centre: edge-lighted frequency scale; in centre, increasing the total power for logging.

Bottom, centre: plug in coil unit A shown in place. At extreme left, top limiter control. Centre A.F. gain; next, calibration switch, bottom C.W.O., and 'phone jack. Centre panel, smaller control knobs are, top left, band switch, centre tone, and antenna trimmer respectively. Right of centre panel: top oscillator, dimmer, A.V.C. switch.

Extreme right: top selectivity, centre phasing, H.T. switch; bottom right: R.F. gain; left: combined Am-NFM-Phono switch.

The dimensions of the table model are 19½ in. × 10½ in. × 16½ in. The shipping weight, complete with speaker and four coils, is 100 lb. Rack models are also available.

Precision Engineering

The H.R.O. "Sixty" specification and high-class workmanship, places it in the precision radio instrument class. Like its predecessors, it is somewhat higher-priced than the types which fall within the province of the average transmitting amateur and short-wave listener. There are several outstanding short-wave receivers in the lower-priced classes, it is admitted, but those who can afford the necessary outlay will enjoy short-wave amateur band listening at its best.

Extra Coil Units

Additional coil units are available should they be required. These are listed as: H.R.O. 60AA, 27-30 Mc/s; 60AB, 25-35 Mc/s; 60AC, 21-21.5 Mc/s; 60AD, 50-54 Mc/s; 60A, 14-30 Mc/s, bandspread, 27-30 Mc/s; H.R.O. 60B, 7-14.4 Mc/s, bandspread, 14.0-14.4 Mc/s; 60C, 3.5-7.3 Mc/s, bandspread, 7.0-7.3 Mc/s; 60D, 1.7-4.0 Mc/s, bandspread, 3.5-4.0 Mc/s. The A, B, C, D being supplied with the receiver as standard equipment.

For the lower frequency bands, the following are available: H.R.O. 60E, 900-2,050 kc/s; 60F, 480-960 kc/s; 60G, 180-430 kc/s; 60H, 100-200 kc/s; 60J, 50-100 kc/s.

Barnstaple Transmitting Station

ON December 11, 1952, the new permanent transmitting station, at Frenington, between Barnstaple and Bideford, took over the West of England Home Service on 285 metres (1,052 kc/s) from the temporary transmitter which has been operating from a caravan on the site. This is one of a number of low-power stations being built by the BBC to improve reception of the Home Service in certain areas.

The new transmitter, which is of higher power than the caravan transmitter, will extend the area of improved reception beyond the immediate surroundings of Barnstaple and Bideford to include outlying districts such as Northam, Great Torrington, and South Molton.

The equipment, housed in a building some 14ft. square, is designed for completely automatic operation without the attendance of staff. It comprises two Marconi transmitter units working in parallel to give an output of 1½ kW. Later a third transmitter unit will be added, increasing the total power to 2 kW.

Main and reserve crystal controlled drives are provided, and automatic frequency control equipment will shortly be installed which, using the Droitwich 200 kc/s carrier as a reference, will maintain the

transmitter drive frequency within very close limits of accuracy.

Automatic monitoring equipment supervises the performance of the transmitting equipment itself by comparing the programme fed to the transmitter with that being radiated. Each transmitter unit is fitted with a monitor which checks the input against the output before the latter reaches the combining circuit, and in the event of a fault in one of the transmitter units it would be automatically disconnected, leaving the station running on reduced power. Should further faults occur, the affected transmitter units would be closed down by their respective monitors.

In order that the engineering staff at the parent centre at Bristol may obtain information regarding the condition of the equipment at Barnstaple a telephone indicator device has been installed. A telephone call to the station will cause this equipment to send to line a series of coded tone-pulses—similar to those used on an automatic telephone system for indicating "dialling," "ringing" or "number engaged." From the particular tone code heard the engineers can determine the state of the various items of equipment at the station. Such calls are made as a matter of routine during programme hours so that, if necessary, an engineer can be sent out.

ALPHA RADIO SUPPLY CO.

INDICATOR UNIT

Type 239. Complete with 10 valves, VCR97 Tube, Volume Controls, Resistors, Condensers, etc., etc. 70/- each, carriage 7/6 each.

11 METRE SUPERHET

10 Valves. Ideal for conversion into TV. Receivers. I.F. 12 megs. Band width 4 megs., co-axial input and output, 65/- ea., carriage 7/6 ea.

INDICATOR UNIT

Type 6. In good condition, with EF50 Valves, etc., wire wound Volume Controls, VCR97 Tube. Complete in case 79/6 ea., carriage 7/6 ea.

COLLARO AC37

4-Pole shaded pole. Variable speed 0-100 r.p.m., fin. spindle, 110/130 v., 200/250 v. 32/6 ea., post 1/6.

COLLARO MOTOR AND TURNTABLE

AC37. Specification as above, with turned spindle and fitted with 10in. E.M.I. type turntable, 46/- ea., post 2/-.

SPARES CHASSIS

Contains 12 Valves, VCR138 Tube. Complete with base and a host of Condensers and Resistors. A real bargain! 40/- ea., carriage 5/6 ea.

METAL RECTIFIERS

12 v. 1 amp., 1/6 ea.; 12 v. 1 amp., 4/6 ea.; 12 v. 3 amp., 18/6 ea.; 12 v. 5 amp., 18/6 ea.; 250 v. 45 m.a., 6/9 ea.; 250 v. 75 m.a., 7/6 ea.; S.T.C., R.M.L., 4/- ea.; R.M.2., 4/6 ea.; R.M.4., 16/6 ea.; 2 to 6 v. 1 amp., 3/- ea.

MOULDED MICA CONDENSERS

.0001, .0002, .00027, .0003, .0004, .0005, .0006, .01, .001, .002, .003, .005, etc. All 4 1/2 ea.

AERIAL RODS

Copper plated tubular rods, 12in. long. Will plug into one another to make a rod aerial, 3d. ea.

BUZZERS

Electric buzzer. Loud tone, bakelite case, 1/6 ea.

BALL DRIVES

Epicyclical friction drive, ratio 8-1, 1/6 ea.

CLIPS

Crocodile clips, very strong, 2d. ea. Bulldog clips, 3in. long, suitable for battery chargers, etc., 6d. ea.

CHASSIS

Aluminium undrilled with reinforced corners. 6in. x 4in. x 2 1/2in., 4/6 ea.; 8in. x 6in. x 2 1/2in., 6/9 ea.; 10in. x 7in. x 2 1/2in., 7/9 ea.; 12in. x 8in. x 2 1/2in., 8/6 ea.

GROMMETS

Rubber Grommets, mixed sizes, 6d. doz.

GRID CAPS

Octal size push-on type, 6d. doz. British type, screened, 3d. ea.

HEADPHONES

High resistance headphones, 10/6 pair; low resistance headphones, 7/6 pair.

YAXLEY SWITCHES

2-Pole change-over switch, 1/- ea.
1 Pole 3 Bank 6 way.
1 " 2 " 6 " "
2 " 1 " 3 " "
3 " 1 " 3 " "
4 " 1 " 3 " "
2 " 1 " 6 " "
4 " 3 Way 2/6 ea. All 1/6 ea.

JACK SOCKETS

Panel mounting type, 2-hole fixing, 6d. ea.; Pilot's quick-release socket, suitable for mic. and tele. plugs, 2d. ea.

SCREWS

P.K. self-tapping screws, 1in., 3 1/2d. doz.

WIRE WOUND VOLUME CONTROLS

5Ω, 200Ω, 1 KΩ, 2 KΩ, 5 KΩ, 10 KΩ, 15 KΩ, 20 KΩ, 30 KΩ, 50 KΩ. All 2/- ea.

ENAMELLED COPPER WIRE

1 lb. reels 14 S.W.G., 1/9 ea.; 1 lb. reels 16 S.W.G., 1/9 ea.

EN. GOVERNMENT V.C. CARBON TYPE

5 KΩ, 50 KΩ, 200 KΩ, 10 KΩ, 20 KΩ, 25 KΩ. All at 1/- ea.

NO GLARE TV. FILTER

Convert your set into a Dark Screen Model. Fits any size up to 12in., 9/6 ea.

INSULATED SLEEVING

1 mm., 1/- dz. yds.; 2 mm., 1/6 dz. yds.

MAINS DROPPING RESISTORS

3 amp. 71Ω Vitreous Type, tap at 60Ω, 1.3 ea.; 3 Zenith 450Ω Vitreous Type, 5 taps, 2/3 ea.

LINE CORD

3 amp. 3 Core 60Ω per foot, 1/6 yd.

R.I. CONDENSERS

Waxed carton types with flying leads. 4fd. 500 v. 1/8 ea.; 4-4 mfd. 530 v., 3/4 ea.

VALVE RETAINERS

Screw Type 2 Hole Fixing EF50 Type, 7/- dz.

MAINS TRANSFORMERS

2 1/2" Mounting Type. Primary 200-220-230 v. Secondaries 350-0-350 v., 83 m.a., 0-4 v., 5 amp.; 0-6.3 v., 4 amp.; 0-4-9 v., 2 amp., 17/6 ea.; as above with sec. 250-0-250, 17/6 ea.; ex Gov. Equip. 350-0-350 v., 80 m.a., 2-6.3 v. Windings and 5 v. tapped primary Surface Mounting. Wax Dipped, 19/6 ea., post 1/6.

DIAL BULBS

6.3 v., 15 a., 15 mm., Ball Type, M.E.S., 6/6 dz.; 6.3 v., 3 a., 10 mm., Tubular Type M.E.S., 8/6 dz.

ENGRAVED KNOBS

1 1/2in. dia. for 4in. spindles, available Cream or Brown, as follows: "Focus," "Contrast," "Brilliance," "Brightness," "Brilliance On/Off," "Wave-change," "On / Off," "Tuning," "Volume," "S.M.L. Gram," "Tone," "Vol. On/Off," "Radio-Gram," "Bass," "Trebble," "Record-Play," also Plain Knobs to match, 1/6 ea.

MIDGET CHASSIS. Holes cut ready for Valve holders, Speaker and Controls. Cad'm plated, 1/- each. Post 1/-.

THREAT MICROPHONES.

2 units 2/- per box.

MORGANITE VOLUME CONTROLS: 1 Meg., 2Ω, 1 Meg., 1 Meg., 3Ω. All with single pole switch.

VALVES

Guaranteed new and boxed. Majority in maker's cartons

OZ4	7/-	6C8	7/6	12K7	9/6
1A6GT	8/-	6D3	7/6	12K3	9/6
1C5GT	8/6	6F6G	8/-	25A6G	9/6
1L4	8/-	6H9	4/6	25L6G	9/6
1LA4	4/6	6J5GT	5/6	35L6GT	10/-
1LD5	6/9	6J7G	8/6	35Z4GT	9/6
1LN5	4/6	6K7G	6/6	30L5GT	9/-
1R5	8/6	6K8G	10/6	AZ31	10/-
1S4	8/6	6L6M	10/6	CV71	1/-
1S5	8/6	6N7	7/9	DDL4	5/-
1T4	8/6	6Q7	10/-	ECH21	11/-
1U5	10/6	6SA7GT	9/-	ECH42	10/6
2A3	7/9	6SF7	7/6	E1143	2/-
2I55G	4/-	6SG7	9/-	HL23DD	8/6
2X2	5/6	6SH7	6/-	KT39C	11/6
3A4	9/-	U4G	8/6	KT61	10/6
3D6	8/6	6SK7	7/-	MH4	7/-
FC13	9/-	6SL7	9/-	MSPen	5/-
3Q5GT	10/-	6SN7	10/6	PEN25	8/6
3S4	10/-	6SQ7	9/6	PEN230A	4/9
3V1	9/-	6V6G	8/6	PM2A	4/9
4D1	4/-	6X5GT	7/9	UCH42	11/6
5R4	9/-	6Z4	3/6	UY41	10/-
5T4	8/-	7B7	7/6	EF39	7/6
5V4G	9/-	7C5	7/6	EBC33	8/-
5V4G	9/-	7C5	7/6	EF36	7/6
5Y3G	8/6	7C7	7/6	EK32	8/-
5Y3GT	8/6	7H7	7/6	SP61	4/-
5Z4G	8/6	7Y4	7/6	SP41	3/6
6A3	9/-	80	9/-	P61	3/9
6A8	11/-	807	10/-	EF50	6/-
6AC7	6/6	8D2	3/-	EA50	2/6
6AG5	8/6	954	2/-	EF8	8/6
6AL5	8/6	955	5/-	VR136	7/-
5AM6	9/6	956	3/6	VR137	5/-
6AT6	10/-	9D2	3/-	EL32	8/-
6B1	8/-	9001	6/6	VP23	8/-
6B7	8/-	9002	6/6	VU39	9/-
6B3	7/-	9003	6/6	VU111	3/6
6C4	8/6	12A6	5/9	VU120A	3/6
6C5	7/9	12C8	9/6	Y63	9/-

SPEAKERS

Plessey round type for personnel portables, 3in. diam., 3Ω speech coil, 12/9 ea.; Elac., 3 1/2in. square, type 3/09, 3/2, 13/6 ea.; Goodmans, 5in. lightweight, 13/9 ea.; Plessey, 5in. lightweight, 13/9 ea.; Elac., 6in. Type 6/19, 14/9 ea.; Truvox, 6in., complete with output transformer, 16/6 ea.; Elac., 8in., type 8/7, 17/6 ea.; Plessey, 10in., lightweight, 10/6 ea.; Truvox, 12in., BX11, lightweight, 57/6 ea.; Truvox, 12in., heavy duty model, 10 watts, 26/6 0 ea.; Rola, 10 in. F.M. 30/- ea.

TERMS: Cash with order or C.O.D. MAIL ORDER ONLY. Full illustrated List available; send 6d. in stamps. Postage, 6d. to 10/-; 1/- to 20/-; 1/6 to 42; 2/- to 55. Minimum C.O.D. and postage charge 2/3.

5/6 VINGES CHAMBERS, VICTORIA SQUARE, LEEDS, 1

VALVES BY RETURN

1G6	4/6	6L6G	12/6	EL91	10/6
1G8CT	5/-	6N7	8/-	KT81	10/-
1LD5	6/6	6SG7	8/-	KT83	7/6
1LN5	6/6	6SH7	5/6	KTW63	7/6
1R5	9/-	6SN7	9/6	OZ1	7/6
1S4	9/-	6SN7	10/6	PEN16	7/6
1S5	9/-	6SS7	7/6	QP25	7/6
1T4	9/-	6L7	6/6	RK31	3/-
1E25	5/-	6V6G	9/-	RL37	3/-
25A6	9/-	6X5GT	7/6	RR72	2/6
2C34	3/-	7192	3/6	SP41	3/-
35L6	11/6	77	7/6	SP81	3/6
3D6	5/-	7B6	6/6	TP25	2/6
3S4	10/-	954	2/6	U21	10/6
50Y6GT	7/6	9D2	3/6	U404	9/-
5U4G	9/-	12A6	7/-	VR21	3/6
6Y3BZ4	9/6	12J3	5/6	VR53	6/6
6AC7	7/6	12SG7	5/-	VR51	2/8
6BR	7/-	12SH7	5/6	VR65	3/6
6F6	8/6	12SL7	7/6	VR65A	3/-
6F8	5/-	A915	5/6	VR69	3/-
6CGGT	9/-	CV6	2/6	VR78	2/6
6H6	5/-	D1	2/6	VR150	10/6
6J5GT	5/6	E1148	2/6	VU110	7/6
6J6	10/-	EA50	2/6	VU39	10/6
6J7G	7/6	EP39	6/-	VU111	3/6
6K6	8/6	EP39	6/6	VU102A	3/6
6KTG	6/6	EP34	4/6	VU133	3/6
6K9G	11/-	EF91	10/-		

All the above are boxed and tested and carry my guarantee.

AMPLIFY YOUR GRAMOPHONE
A1219. Battery Amplifier. Complete with VR35 and VR21 valves for use as intercom or with slight alteration as Gram. Amplifier... in metal case 7in. x 4 1/2in. x 4 1/2in. Complete with instructions for modification. **15 - POST FREE.**

MAIL ORDER ONLY
E. MINETT (P.W.)
54, RETREAT STREET,
WOLVERHAMPTON.

Amateur Radio Enthusiasts
THE INCOMPARABLE
GLOBE-KING
SINGLE VALVE S.T. RECEIVER
• WORLD-WIDE RANGE 11-100 METRES • CRYSTAL-CLEAR NOISE-FREE RECEPTION • ELECTRICAL BAND-SPREAD TUNING • EXTREMELY LOW RUNNING COSTS
Catalogue Free. Stamp for postage.
JOHNSONS (RADIO)
46, FRIAR STREET, WORCESTER




"AUTOMAT" CHARGER KIPS
This shows the No. 1 kit assembled into its case. Built in one hour, it is simple, foolproof and troublefree. All new material with full guarantee. Generous size components. No. 1 kit 8/12/-, 2 amp. Filtrator Kit, trans, 135v. 30 ma. h.t. rect., 2v. 1a. trickle rect., 2 x 10 mfd. condensers, case, screws, grommets for 120v. 20/30 ma. eliminator with trickle charge, 42/-, postage 1/4d., or less case. 35/-, postage 1/4d.
CHAMPION PRODUCTS,
43, Uplands Way, London, N.21.
Phone: LAB 4457.

MORSE CODE Training
Send for the Candler
BOOK OF FACTS
It gives details of all Courses which include a Special one for securing Amateur Licence.
CANDLER SYSTEM CO. Dept. 510
52b, Abingdon Road, London, W.8.
Candler System Co., Denver, Colorado, U.S.A.

CABINETS

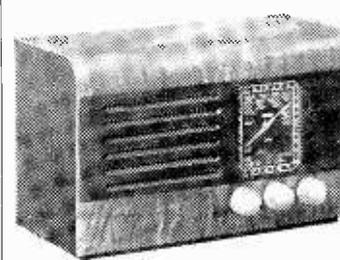Our latest illustrated catalogue of all types of Cabinets now available.



A SPECIAL OFFER
Walnut Cabinet, complete with punched chassis, dial, backplate, drum, drive, spring, pointer and cord. **28/6 plus 2/6 p. and p.**

CHASSIS
A.C., 5-valve 3 w/b Superhet Radiogram Chassis. Absolutely complete kit of parts including wiring diagram, **£10/10/0**. Or fully wired and tested, **£12/10/0**.

LEWIS RADIO CO.
(Dept. K.19),
120, Green Lanes, Palmers Green,
London, N.13. **BO Wes Park 6064**

YOU can become a well-paid RADIO ENGINEER
Our Home-Study Courses in Radio, Television and Mathematics are a proved success. We train men to earn good money in their spare time, start businesses of their own, or get bigger salaries. Post coupon for free details.

T. & C. RADIO COLLEGE
Post in unsealed envelope, 1 1/2d. postage
To: **T. & C. RADIO COLLEGE,**
36, Northfield Road,
Ringwood, Hants.

NAME

ADDRESS

P3/53

THE MODERN BOOK CO.

- Principles of Radar, by M. I. T. 55s. 6d., postage 1s. 0d.
 - Radio Engineer's Servicing Manual, by Molloy (ed.) 42s. 0d., postage 1s. 0d.
 - Amplifiers, by G. A. Briggs and H. H. Garner. 15s. 6d., postage 9d.
 - Mathematics for Telecommunications, by D. P. Spooner and W. H. Crinsted. 10s. 6d., postage 9d.
 - Wireless Servicing Manual, by W. T. Cockin. 12s. 6d., postage 6d.
 - Foundations of Wireless, by M. G. Scroggie. 12s. 6d., postage 9d.
 - Thermionic Valve Circuits, by E. Williams. 21s. 0d., postage 9d.
 - TV. Fault Finding, Compiled by Radio Constructor. 5s. 0d., postage 3d.
 - Practical Wireless Encyclopaedia, by F. J. Camm. 21s. 0d., postage 9d.
 - The Amateur's Guide to Valve Selection, by Mullard. 1s. 6d., postage 3d.
 - Personal Receivers, by E. N. Bradley 3s. 6d., postage 3d.
 - Radio Valve Data, compiled by "Wireless World". 2s. 6d., postage 3d.
 - Magnetic Recording, by S. J. Degun. 25s. 0d., postage 9d.
 - The Use of Radar at Sea. 30s. 0d., postage 1s. 0d.
- We have the finest selection of British and American radio books in the Country. Complete list on application.
19-23, PRAED STREET,
(Dept. P.3) **LONDON, W.2**
PADdington 4185.

BENTLEY ACOUSTICS LTD.
38, Chalcot Road, N.W.1. *PRImrose 9090.*

12J5	4/9	7C8	7/6	6X5	7/-
6SK7	6/6	7S7	7/6	6SL7	8/-
129CT	6/6	7Y4	7/6	6N7	6/6
7C3	7/6	6SS7	5/-	6AC7	5/-
9B3	5/6	6SN7	8/6	6J5	4/6
6K1	7/6	807	9/6	6K7	4/6
77	6/6	6IP	9/6	12SE7	4/6

All Guaranteed Post 6d

LAWRENCE IS STILL GOING STRONG

TESTED Secondhand and New VALVES from 5-
1151 Transmitter. **£8.0.0.** post paid.
1155 Receiver with Power Unit and 10in L.S. **£19.0.0.** post paid.
Wavemeter W 117. 125 KC to 20 MC. **£7.7.6.** post paid.
Wavemeter W 123. 231 MC to 100 MC. **£4.7.6.** post paid.
Wavemeter W 1081. 135 KC to 15 MC. **£3.7.6.** post paid.
Also Quick Repair Service.
S.A.E. for complete list, including Model Railways, Technical Books.

LAWRENCE FRANKEL
MAIL ORDER,
134, Cranley Gardens, London, N.13
TUDor 1404.



TESTOSCOPE Mains Tester
For high and low voltage testing — 1-30 and 100-850 volts A.C. or D.C.
Write for interesting leaflet 29F.
RUNBAKEN - MANCHESTER

News from the Trade

New EKCO Export Table Autoradiogram

ANNOUNCED a short time ago by E. K. Cole, Ltd., and now in full production, is a new export three-speed table autoradiogram, the TRG189, which possesses several outstanding features.

Playing automatically all sizes of standard and long-playing records, the TRG189 covers medium and short waves in three ranges and is fed from A.C. mains of 100/150 volts or 200/250 volts, 50 or 60 cycles. These features make it particularly suitable for overseas purchasers, including visiting forces, who wish to use the set in this country and later take it overseas.

The radio unit incorporates a two-speed tuning control and the 5-valve circuit gives excellent reception on short-waves, including the 11-metre band. The set is fully tropicalised.

E. K. Cole, Ltd., Southend-on-Sea, Essex.

Windsor Capacity and Resistance Bridge (Model 110c)

THIS new bridge from Taylor Electrical Instruments, Ltd., operates from A.C. mains and is designed to give accurate measurements of capacity and resistance at 50 cycles.


Eight capacity ranges enable measurement to be made from 5 pF to 1,200 μ F, and eight resistance ranges are available covering from 0.1 ohm to 120 megohms.

Special comparator scale marked in percentage is incorporated for checking components against external standard.

Power factor measurements up to 50 per cent. are available on all capacity ranges.

A conventional bridge circuit is used and when measuring capacity an internal standard capacity with a variable series resistance constitutes one arm of the bridge. The other arms comprise a vari-

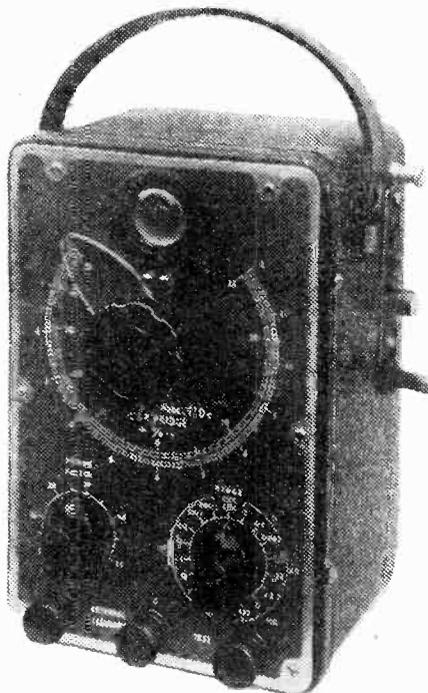able resistance calibrated 0—12 and a fixed resistor. The condenser under test makes the fourth arm of the bridge. A.C. volts from a low-voltage screened secondary winding of the mains transformer are applied to the bridge and the out-of-balance voltage is amplified by a 6J5 valve which is resistance coupled



The new Model 110c Windsor Bridge.



The Ekco Model TRG189.

able resistance calibrated 0—12 and a fixed resistor. The condenser under test makes the fourth arm of the bridge. A.C. volts from a low-voltage screened secondary winding of the mains transformer are applied to the bridge and the out-of-balance voltage is amplified by a 6J5 valve which is resistance coupled to a "Magic-eye" valve. This combination is very sensitive and small out-of-balance voltages are indicated by a blurring of the "X" shaped shadow of the "Magic-eye" valve. The variable resistance in series with the condenser is calibrated 0—50 and measures the power factor. On resistance ranges the internal resistance standard is switched into the bridge in place of the condenser and the power factor control.

The outer scale marked 0—12 is used on all capacity and resistance ranges and has a length of 9in., giving a total scale length of 72in. on both capacity and resistance measurements.

The inner scale is marked in percentage giving plus 50 per cent. and minus 25 per cent. for comparison purposes when components are checked against external standard.

The complete instrument is 8in. x 5½in. x 5in. deep and weighs 6 lbs. Mains consumption is 15 watts, and the price £14 10s.

Taylor Electrical Instruments, Ltd., 419/424, Montrose Avenue, Slough, Bucks.

OPEN TO DISCUSSION

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

"Safe" Universal Circuits

SIR,—With reference to the article in the October issue on this subject, I would like to point out a consideration when using an A.C./D.C. circuit off a D.C. supply.

Correct polarity is necessary, of course, before the circuit will operate, the chassis usually being negative. On examining a D.C. supply it may be found that the positive line is approximately at earth potential, i.e., the positive line is the neutral. It would obviously be useless to connect the neutral to the chassis in this instance, and there is no simple alternative but to operate the circuit with the chassis "line" to earth.

The reason for this somewhat peculiar state of affairs is the "three-wire" system of distribution often used in the case of D.C. supplies. The voltage originates at twice the value at which it is used by a normal domestic consumer and the centre point is earthed. The result is that one line is at, say, 240 volts above earth potential and the other at 240 volts below earth potential.

Briefly, it must not be assumed that the negative line is at approximately earth potential.—E. C. COX (Chesterfield).

High Fidelity Record Reproduction

SIR,—In the search for better listening, I have worked through the usual apprenticeship—building quality amplifier, good speaker in bass reflex cabinet, etc.—studying, reading and researching at each step, and I now find myself back at the beginning of things, the place where the noise comes from—the point of contact between stylus and record. I am driven to conclude that the greatest obstacle today to good listening is surface hiss. The more one strives after distortionless output and extended frequency range, the more obtrusive becomes that hiss and the more pressing the question of what can be done about it.

Assuming that the practice has ceased of incorporating abrasives with the material from which the record is pressed in order to grind the needle quickly to the shape of the groove, and that a modern resonance-free pickup has made scratch-filter circuits superfluous, the answer seems to be nothing but top cut. The latest oscillograph investigations show the hiss evenly distributed over the whole of the range of audibility. Having striven for extended frequency response, to cut that top is not encouraging.

It has occurred to me that perhaps a lubrication of the stylus point might help. I have been trying the old idea of using a record polish, a mixture of one third linseed oil and two thirds white spirit (turps substitute). The record is first cleaned with a velvet pad, oiled as sparingly as possible, polished with a soft cloth and played through with a sapphire needle. It is then polished again and set aside to dry. Judging by ear alone, I fancy the results are encouraging.

Could any fellow sufferer suggest another mixture that I could try on my worn shellac discs? Being only an impecunious schoolmaster, I can't afford to throw them all away because I see no hope of ever replacing them, on my salary.

Finally, how much extra would it actually cost the customer to buy 78 r.p.m. records pressed in noise-free plastic instead of slate-filled shellac?—R. E. THOMAS (Totworth).

Battery-Mains Portable

SIR,—I have just successfully completed the Battery-Mains Attaché Case Portable, described in the January, 1953, publication of PRACTICAL WIRELESS, and there are one or two points which I feel may be of interest to future constructors.

The only "snag" I met with was acute distortion on maximum volume, and I found this to be due to bias trouble in the second detector and output stage.

The reproduction was 100 per cent. improved by replacing R4 (10 M Ω) with a 470 K Ω , similarly one 470 K Ω replacing R7 (2.2 M Ω) and R8 (680 M Ω), entirely eliminated the distortion with a very slight drop in volume.

The second point which may be of interest is that a slightly larger frame aerial did improve sensitivity quite appreciably. This was wound with 12 turns of 30 s.w.g. enamelled wire on a former having dimensions of 10½ in. \times 9½ in. I also found that this increase in size also affected the overall gain of the set, thereby increasing the number of foreign stations received at a comfortable "listening" volume.—I. S. R. HAYNES (Croydon).

Accurate Diagnosis

SIR,—My belated thanks for your assistance in solving my valve-voltmeter problem.

By pin-pointing the possibility of the trouble being in the earth leads I was led directly to the fault. I had too readily assumed the trouble in the home-

(Continued on page 173)

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for constructional articles which appear in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.



DEPT. P.W.
18 TOTTENHAM CT. RD
LONDON, W.I.
MUSeum 4539/2453

Ronette Microphone. The latest Ronette XTAL take B110 Freq. 40-7,500 cps. Only 52".
A.D.S. III. FIDELITY AMPLIFIER. This is our latest gramophone amplifier which you MUST hear. P.P. 6V6 output. Freq. 25-18,000 cps. + 1db Hum—60db at 64 watts. Treble boost and cut—Bass boost—1.5 db. correction. Provision for Feeder Unit. Max. UNDISTORTED OUTPUT 31 watts. Price 16 gns. plus 7/6.

NOW AVAILABLE. Kit of Parts, complete with fully illustrated instructions, 12 gns. plus 5/- carriage.

3 W/Band Feeder Unit, ready to plug into this amplifier, 10 gns., plus 5/-
SPECIAL—HIGH QUALITY 41-watt AMPLIFIERS. Separate treble and bass filter. In black crackled case, £9/17/6, plus 5/-
GRAMOPHONE EQUIPMENT. B.S.R., 311-78 R.P.M. Motor Unit, 78/7, plus 1/6. B.S.R., 3-speed Motor unit, £8/8/6, plus 1/6. DECCA XMS P.U.P., £7, plus 1/-. Connoisseur STD P.U.P., £4/11/8, plus 1/-. 8-light weight, one head, £8-9-. L.P. Head, 7/1.8. Trans., 15/-. Fibre P.U.P., £4/3/2. Trans., 25/-

SPECIAL OFFER—CHANCERY XTL P.U.P. complete with L.P. and 78 inserts, 59/8, plus 2/- postage.

GARRARD HEADS.—HFI, 59/11. Miniature, 54/4. Standard 26/6, plus 1/- post. Adaptors Type A, 9/3. H, 6/7. C, 4/8, plus 1/- post.

NEW! ACCOS GP39 Turnover Crystal. £3/11/5, plus 2/-. Garrard AC8 Speed Controlled 78 R.P.M. 12in. Table, £4/12/6, plus 2/6.

NEW GARRARD 3-SPEED AUTO RC75A Turnover Head. Crystal or magnetic. £18/14/0, plus 5/- post.

NEW RELEASE Garrard RC75A A.C./D.C. 3-speed auto units £27/3/8, plus 5/-
METAL RECTIFIERS, R.M.2 £25 v. 110 mA., 5/9. R.M.L. £25 v. 60 mA., 5/5, plus 1/-. Type 280 V.T.C. 280 v. 80 mA., 10/-

DEMCO "C" T.R.F. COILS. Medium and Long wave, 9/- plus 1/6 post.

BRANDENBURG E.H.T. UNIT.—6.9 kv., 6 gns. Coil only 39/-. Coil with U22 rectifier 69/6.

1915 K.V. COILS, 55/-
QUALITAPE NEW PRINCIPLE 2-SPEED RECORDER now available, 16 gns., plus 3/6.

MOTEK 8 MOTOR TAPE DESK. High impedance heads. A first-grade instrument, 15 gns., plus 3/6.

MOTEK RECORD AND ERASE HEADS, 39/8 each, plus 1/6.

MOTEK OSC. COILS, 8/6.
COLLARO TAPE DESK MOTORS. Left and right-hand drive, 38/8 each, plus 1/6.

SCOTCH BOY. EM1 Tape, 35/-, plus 6d. GEC, 30/-

REXINE PLAYER DESK, with lid. Cut for BSR Motor, 24/6, plus 3/- postage.

TRANSFORMERS. 6.3 v. 1.5 a., 7/6, plus 9d. 4 v. 2 a., 7/6, plus 9d. 12 v. 1 a., 8/6, plus 9d. 6.3 v. 6 a., 19/6, plus 1/6. Williamson Output, 78/9. Choke, 27/9, plus 1/6.

CHOKES. 10 h. 150 mA., 16/3, plus 1/3. CH5, 10 h. 60 mA., 30/0, 5/8, plus 1/6. CH4, 10 h. 75 mA., 15/0, 5/8, plus 1/6. 50 h. 30 mA., 1,500/2, 6/8, plus 1/6. 50 h. 20 mA., 1,100/2, 6/11, plus 1/6. 30 h. 20 mA., 6/11, plus 1/6. 20 h. 10 mA., 5/9, plus 1/6.

EARPHONES! By Brown 4000/2. Brand New, boxed, 18/8 pair, plus 1/6.

WEARITE TAPE DECKS.—Delivery from stock, £35, plus 7/6.

Cheapest A.L.I. chassis in London 6 x 4, 3/9. 8 x 6, 4/3. 10 x 7, 5/6. 12 x 8, 6/9. All by 2 1/2 in. Postage 1/3 on each.

FULL MAIL ORDER FACILITIES

(Please add postage)

Shop Hours, Monday to Friday,
9—5.30 p.m., Saturday, 1 p.m.



FOR UNRIVALLED
VARIETY OF STOCK



COMMUNICATIONS RECEIVERS

used by all discerning short-wave listeners:—

MODEL "740", eight valves in high-performance circuitry. £42 15s. 0d.

MODEL "750", eleven valves, double superheterodyne with variable selectivity and comprehensive communications specification. £68 0s. 0d.

LOW IN PRICE!

HIGH IN PERFORMANCE!

TWO AMPLIFIERS GIVING A NEW CONCEPT OF HIGH FIDELITY:—
SOUND SALES "MINIATURE A-Z"—
AMPLIFIER follows the same high performance and workmanship as its famous larger companion the "A-Z" amplifier. Gives 3.2 watts, with full compensating circuits for all types of records. Uses the best components and a clever compact design, size 10 1/2 in. by 7 1/2 in. For panel mounting a cut-out of 7 in. by 2 1/2 in. is required. £10 15s. 0d.

ROGERS "R.D. MINOR" AMPLIFIER has a frequency response flat within 1 dB from 40-15,000 cycles. Compensated for 78 and L.P. records, working direct from modern pick-ups. 3.2 watts output with less than 0.5% distortion. Size 9 1/2 in. by 7 in. £11 10s. 0d.

(A veneered cabinet is available price £1 19s. 6d.)

INCREASE THE REALISM
of your reproduction by using a
WEBB'S "CROSS-OVER UNIT"

to feed separate bass and treble loudspeakers:—

TYPE "A" Cross-over 2,000 cycles, £2 2s. 0d.

TYPE "B" Cross-over 1,000 cycles, £2 12s. 6d.

TYPE "C" Cross-over 1,500 cycles, £3 13s. 6d.

(If you prefer to build your own units, ask Webb's for circuit details, available free on request.)

All Post Enquiries and Orders receive our "Same Day" service.



14, SOHO ST., OXFORD ST., LONDON, W.I.

Telephone: GERrard 2089

Hours: 9—5.30, Sats. 9—1.

£7-19-6

for a first-class COMMUNICATIONS RECEIVER. This is the famous ex-R.A.F. type R.1155, which is justly known as being a really tip-top set. Covers 5 wave ranges, 18.5-7.5 mcs, 7.5-3.0 mcs, 1,500-600 kc/s, 500-200 kc/s, 200-75 kc/s, and is easily and simply adapted for normal mains use, full details being supplied. These receivers have had some use, but are in very good condition, and are all aerial tested and guaranteed in working order before despatch. Also available:

BRAND NEW IN MAKERS' CASES & AERIAL TESTED £11-19-3
USED, GOOD CONDITION, UNTESTED £6-19-6

FACTORY MADE POWER PACK OUTPUT STAGE & SPEAKER, which operates the receiver immediately. £5-10-0

Carriage costs of 10s for Receivers, 5/- for Power Pack, extra please.
SPECIAL REDUCTION OF 10% IF POWER PACK & RECEIVER ARE PURCHASED. Where used receivers are purchased, they may be exchanged for new ones within 14 days: you only pay the extra and carriage.

CLASS D WAVEMETER.—A further supply of these superb instruments which conform to G.P.O. requirements. Covers 1.9-8.0 mcs (direct reading without charts), and are supplied with 100/1,000 kc/s dual crystal, 1 valve ECH35, and 1 6v. vibrator. Designed for use on 6v. D.C. but is easily modified for A.C. operation, full details being supplied. A suitable transformer is available for only 7/6 extra. BRAND NEW IN MAKERS' TRANSIT CASES, ONLY £5-19-6 (carriage, etc., 5/6).

6-VOLT VIBRATOR UNIT.—Made by the National Co. of America for their HRO Communications Receivers, supplying 185 volts at 85 mills fully smoothed D.C. Complete with vibrator and 6X5 rectifier in black crackle cabinet, size 7 1/2 in. x 6 in. BRAND NEW IN MAKERS' CARTONS with full operating instructions, ONLY 52/6.

P.M. SPEAKERS (With Transformer).—6in. Goodmans, 15/-.

P.M. SPEAKERS (Less Transformer).—5in. Rola, 18/6. 8in. Plessey, 14/6. 10in. Rola, 27/6. (Postage 1/6 per speaker).

VENODE OUTPUT TRANSFORMER.—Goodmans, 5/-.

CHOKES.—10H, 60 ma., 3/9. 30H, 100 ma., 12/8. 5H, 200ma., 6/- (Postage 1/- per choke.)
TRANSFORMERS.—Manufactured to our specification, and fully guaranteed. Normal Primaries. 425v.-0-425v. 200ma., 6.3v. 6A. 6.3v. 6 a., 5v. 3a., 0-2-4.5v. 3a. ONLY 72/6. 425v.-0-425v. 200ma., 6.3v. 4a. 6.3v. 4a., 5v. 3a. ONLY 50/-. 350v.-0-350v. 160ma., 6.3v. 6a., 6.3v. 3a., 5v. 3a. ONLY 42/6. 250v.-0-250v. 100ma., 6.3v. 6a., 5v. 3a. ONLY 32/6. The above are fully shrouded, upright mounting. The following are upright mounting, EHT for VCR97 Tube, 2,500v. 5ma. 2v.-0-2v. 1.1a., 2v.-0-2v. 2a. ONLY 37/6. EHT 5,500v. 5ma., 2v. 1a., 2v. 1a. ONLY 72/6. EHT 7,000v. 5ma., 4v. 1a. ONLY 82/6.

PLEASE ADD 10 PER TRANSFORMER POSTAGE.

TRANSFORMERS.—Ex W.D. and Admiralty built to more than 50% safety factor, with normal A.C. Mains Primaries. All Brand New and Unused. 300v.-0-300v. 200ma., 5v. 3a., 6.3v. 5a. C.T., 20v. 750ma., 70v. 100ma., Weight 12 lb. ONLY 42/6 (postage, etc., 3/6). 300v.-0-300v. 200ma., 4v. 3a. Weight 7 lb. ONLY 22/6 (postage, 1/6). I.T. 5v.-0-5v. 5a., 5v.-0-5v. 5a. By using combination of windings will give various voltages at high current. Weight 11 lb. ONLY 35/- (postage, etc., 2/6). L.T. 6.3v. 7.7a., 4v. 2.5a., 4v. 1a. ONLY 19/6 (postage, 1/6). EHT 1,400v. 2ma., 5.2v. 10ma., 300v. 10ma., 2v. 1.5a. ONLY 21/- (postage, 1/6).

U.E.I. CORPORATION

THE RADIO CORNER
138 Gray's Inn Road, London, W.C.1
(Phone TELminus 7937)

Cash with order, please, and print name and address clearly.

Open until 1 p.m. Saturdays, we are 2 mins. from High Holborn Chancery Lane Station, 5 mins. by bus from King's Cross.

CITY & RURAL

Immediate delivery from stock.

"VIEWMASTER"

SPECIFIED COMPONENTS
SEND FOR STAGE 1 NOW—
price £3.2.3 post free.

Complete Kits. Stage-by-Stage and Single Components Supplied. "VIEWMASTER" ENVELOPES, 7/6.

COMPLETE SET OF GUARANTEED VALVES FOR "VIEWMASTER" £8-15-0

Television Explained, by W. E. Miller, 5s. 6in. CRT Magnifier Lens, 22/6. Belling 72-ohm Twin Feeder, 7/4. yard. Electrolytics, Tubular, 8 mid. 450v. 2/3; 32-32 mid. 275v., 3/6. Multi-Ratio O/P Transformers, 5/11. Speakers P.M., 3in., 13/6; 5in., 14/8; 6in., 16/6; 8in., 19/6. 6V6GT, 10/6, VR91, 8/6. 5Z4G, 10/6. Heater Transformers, 6.3v. 1.5A., 7/6. 2.5 Kv. Transformer, 45-. Smoothing Chokes, 10H 100 mA., 8/3; 15H 60 mA., 5/11.

Extensive Stocks New & Surplus Components & Valves

For Attention—Advice—Service write

CITY & RURAL RADIO
101, HIGH STREET,
SWANSEA, GLAM.

Telephone: Swansea 4377

DUAL-WAVE COIL

for MODERN ONE- AND TWO-VALVER SUMMER ALL-DRY PORTABLE, ETC. 4/3. Post and packing, 3d., Circuits, 3d. K TYPE COILS FOR A.C. BAND PASS 3, 3/3d. each.

T. G. HOWELL,
29, McWilliam Road, Brighton, 7

CRYSTAL MICROPHONES

for tape decks, transmitters, P.A., etc. ACOS desk-stand (illustrated)... £6-6-0 ACOS hand-stand model ... £4-4-0 ROTHERMEL hand mic. with lead ... £2-19-6 SIMPHONIC hand mic. with lead ... £2-10-0 Send s.a.e. for full details of these microphones.

HOME RADIO
187, London Road,
Mitcham, Surrey.

"The quality radio component specialists"


S.E. LONDON CONSTRUCTORS

We hold good stocks of new and guaranteed

COMPONENTS AND VALVES

Rewinds, loudspeaker repairs, communication and TV receiver alignment, etc.

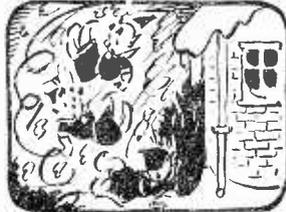GLYNDON RADIO SERVICE
68, Wellington St., Woolwich.
W00 2749.



The "Fluxite Quins" at Work

"Fixing an aerial's all right,
And making it sound with FLUXITE,
But working in snow
Is snow joke," bawled OH.
"It's the third time we've skidded tonight!"

See that **FLUXITE SOLDERING PASTE** is always by you—in the house—garage—workshop—wherever speedy soldering is needed. Used for over 40 years in Government works and by leading engineers and manufacturers. Of all ironmongers—in tins, from 1/- upwards.

FLUXITE

SOLDERING PASTE

A Staunch Companion to Fairlie Soldering Fluid.

SIMPLIFIES ALL SOLDERING

Write for Book on the Art of "SOFT" Soldering and for leaflets on CASE-HARDENING STEEL and TEMPERING TOOLS with FLUXITE. Price 1/4. each.

FLUXITE Ltd.,
Bernoldsey Street, London, S.E.1.

RUNLIMITED

Unrepeatable Unstable, Unbelievable MAINS TRANSFORMERS, by leading manufacturer. 325-0-325. 6 v.-2.5 A., 5 v.-2 A., 80 MA., 19/6.

1953 Model RADIOGRAM CHASSIS, 3-waveband, 5-valve superhet, complete with 10in. P.M. speaker, 12 gns.

STOCKTAKING VALVE SALE.—Full detailed list of types sent you by return of post. Limited supplies of each type available. Write or phone to-day.

LOUDSPEAKERS

3in., 5 ohm., L/tr ... 10/6
3 1/2in., 2/3 ohm., L/tr ... 14-8
5in., 2/3 ohm., L/tr ... 15-8
6in., 2/3 ohm., L/tr ... 16-16
8in., 2/3 ohm., L/tr ... 17-32
10in., 2/3 ohm., L/tr ... 21-32
10in., 2/3 ohm., W. tr ... 30-16

ELECTROLYTICS

450 v.w. 2-8 mt. ... 2-8
8 x 8 ... 3-8
16-16 mt. ... 3-8
32 mf. ... 3/9
32 x 32 ... 5/8
16 x 16 ... 4-8



All models have variable selectivity, high quality detector, triode output stages, 7 valve model illustrated £21-15-0. De-luxe 9-valve, £25-5-0. Major 10-valve, £32-15-0. Minor 6-valve, £17-10-0. Data sheets on request.

Fidelia Equipment
2 Amhurst Road, Teiscombe Cliffs, Sussex

Electronic Music

Throw away your violin or flute and start building your new 3-octave electronic keyboard. Free leaflet available. Imitates most orchestral instruments—has range of 5 octaves. With its variable attack you can put in the "plonk" of a plucked string. Parts are easily obtainable—uses 8 octal valves. Write NOW for free leaflet.

This instrument is not that described in P.W. Special "less 25%" offer for this month only. Write now for your free descriptive leaflet.

CIRCUITS AND SUPPLIES,
10, Duke Street,
Darlington, Co. Durham

REP

HIGH GAIN DUAL RANGE COIL WITH REACTION.

Complete with 2 Battery and 2 Mains Circuits. PRICE 4/- Post 3d. (Trade Supplied.)

RADIO EXPERIMENTAL PRODUCTS LTD.

33, Much Park Street, Coventry.



H.A.C. SHORT WAVE EQUIPMENT

Noted for over 18 years for S.W. Receivers and Kits of Quality.

Improved designs with Denco coils: One-Valve Kit, Model "C" Price, 25/- Two " " " " " " " " 50/-

All kits complete with all components, accessories, and full instructions. Before ordering call and inspect a demonstration receiver, or send stamped, addressed envelope for descriptive catalogue.

"H.A.C." SHORT-WAVE PRODUCTS (Dept. TH), 11, Old Bond Street, London, W.1.

Quixo RADIO Cell Tester

Accurately tests High, Low and Grid Bias Batteries. Write for leaflet 29 M.



RUNBAKEN MANCHESTER

(Continued from page 170)

built unit—in fact, the earth lead of the Avo oscillator was sheared clean through inside the insulation.

You feel silly when one like that beats you.
—P. BURGESS (Paisley).

TV Harmonic

SIR,—I noted with interest the letter by Mr. J. Law, under the heading "TV Harmonic," as some time ago I experienced a similar instance.


I was servicing a Cossor 916 TV receiver and after completing the repair work I left it, still out of its cabinet, on soak test. At a distance of about 3 yards away, on another bench, I was checking a four-valve battery superhet for S.W. performance when I came across the TV sound transmission on approximately 30 metres. Upon switching the TV on and off the transmission on the radio went on and off in sympathy.

As the frequency of the sound I.F. of the TV is 9.5 Mc/s, it would appear that some form of I.F. radiation (complete with modulation) was taking place.

If Mr. Law has a TV set himself (or his immediate neighbours), it would account for his experience.
—W. J. BLANCHARD (Ulceby, Lincs).

Quick Capacitor Tester

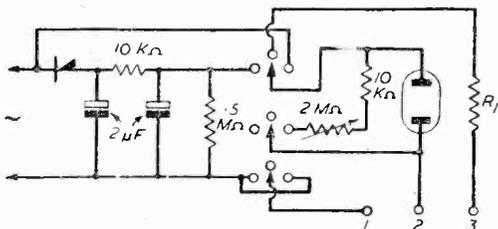SIR,—I would like to suggest that the "Quick Capacitor Tester," as described in the January, 1953, issue, could be made more useful if a third terminal was added, and connected via a resistor R₁ to the centre ("off") contact of the upper switch wafer. Then the neon tube could be used as a voltmeter, using the right-hand test terminal and the extra terminal (2 and 3 in the diagram). Also, by



Circuit referred to by Mr. Reakes.

connecting a resistor between terminals 1 and 2 (marked "Test" in the original article) and a capacitor between 2 and HT+, and setting the switch to the D.C. position, the circuit would become an oscillator whose frequency is given by the formula

$$f = \frac{1}{CR \log e \frac{V_3 - V_1}{V_3 - V_2}} \dots \dots \dots (1)$$

where f = frequency c/s

C = Capacity across 2 and HT+ μF

- R = Resistance across 1 and 2 M Ω
- V₁ = Extinction voltage of neon tube
- V₂ = Striking voltage of neon tube
- V₃ = H.T. voltage

and for a given neon tube and H.T. voltage is

$$f = \frac{K}{CR} \text{ where } K \text{ is a constant whose value depends on } V_1, V_2 \text{ and } V_3 \text{ as in equation (1).}$$

Most small neon tubes will oscillate from very low frequencies up to low radio frequencies.

The amplitude of the oscillation is approximately V₂ - V₁ volts peak-to-peak.

The output is taken from across terminals 1 and 2, via a capacitor to block the D.C. component.

In the diagram the circuit component values are as given in the article referred to. The series resistor R₁ is merely to limit the current through the neon tube and a value of 10-100 K Ω should prove satisfactory. A little experiment will soon satisfy this point.

The use of such a voltmeter for checking which side of the mains the chassis of an A.C./D.C. set is connected, if switches are connected in the "live" leads or not, the presence (or absence) of screen and anode voltages of valves are a few of the more obvious uses of this device.

Because the waveform of the oscillator contains a large number of harmonics, it can be used to calibrate other oscillators if the fundamental frequency (f in equation (1)) can be set accurately—say, by beating with the 50 c/s mains.—E. R. REAKES (Worthing).

Contact Operation and Maintenance

(Concluded from page 138)

across the contacts. This capacitor should be of mica construction and 1 μF to 4 μF in value. In order that the capacitor should not immediately discharge across the contacts during the opening time, a resistor of value 25 Ω to 100 Ω should be inserted in series with the capacitor. Higher values of resistor should not be used, as this will reduce the effectiveness of the capacitor during its primary charging cycle.

Summarising, the following points should therefore be noted for the operation of contacts in electrical equipment :

The contacts should be aligned so that the maximum surface area is used.

Where possible a dust-cover and flame barriers should be used.

Contacts carrying high values of current should be oil-immersed, have a fast release movement and, if possible, be assisted by a magnetic blow-out.

Contacts carrying low values of current should have a degree of self-cleaning action, and in all cases a dust-cover should be fitted.

Maintenance tools should be capable of adjusting operating travel, tension and rest position. Carbon tetrachloride should be used in conjunction with a dead-smooth contact file to ensure cleanliness of contacts.

Editorial and Advertisement Offices :
"Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone : Temple Bar 4363.
Telegrams : Newnes, Rand, London.
Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed : The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporates "Amateur Wireless."

BOOKS

LATEST AMERICAN RADIOS.—New and novel miniature receivers, portables, all-wave receivers, 1 to 6 tube. Electronic equipment, etc. Build your own from available parts. Complete list of blue-prints and parts lists available with full details. 3d. **AMERICAN PUBLISHERS**, Sedgford, Norfolk.

AMERICAN MAGAZINES, 1 year incl. "Audio Engineering," 28/6; "High Fidelity," 43/-; "Radio Electronics," 32/3, etc. Send for free booklet. **WILLEN LTD.** (Dept. 40), 101, Fleet St., London, E.C.4.

I.P.R.E. TECHNICAL PUBLICATIONS: 5,500 Alignment Peaks for Superheterodynes, 5/9, post free. Data for constructing TV Aerial Strength Meter, 7/6. Sample copy: The Practical Radio Engineer, quarterly publication of the Institute, 2/-; membership and examination data 1/-; Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8.

BRITISH SHORT WAVE LEAGUE is devoted to the interests of amateur radio enthusiasts. Publishes 12-page "BSWL Review," monthly (members only). Offers many services and activity departments. World wide membership. Founded 1935. Apply for details to: **BRITISH SHORT WAVE LEAGUE**, 55, Victoria St., London, S.W.1. (Abbey 5341.)

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-64, inclusive, or a woman aged 18-59, inclusive, unless he or she, or the employment, is exempted from the provisions of the Notification of Vacancies Order, 1952.

T.V., RADIO components shop in B'ham requires Technical Salesman, with good appearance and pleasant personality; able to give advice gained from personal experience. Please state age, wages and experience in confidence; all replies answered. Box No. 228, c/o PRACTICAL WIRELESS.

TAPE RECORDINGS, ETC.

THE NEW LINE-A-TONE Tape Recording Panel, no threading of tape, fast forward and rewind, 3 speeds, complete freedom from wow or flutter; in fact this panel embodies all the requirements of the professional recordist. The price still remains at £20. Place your order early. **MORECAMBE SOUND SERVICE**, "Sealand Works," Cross Cop, Morecambe.

RECORD-PLAYBACK Amplifier Kit complete, high impedance, 4 watts output, 4 BVA valves and speaker. £5/15/-; Power Pack, £2/17/6; both wired and tested. £10; post and packing. 5/- c.w.o. **SOUTHERN RADIO**, Dominion Rd., Worthing.

RADIO, Television, Electrical and Recording Components and Equipment. Send stamp for lists and compare our prices. **R.K. SUPPLIES LTD.**, 58, Athlone Road, Tulse Hill, London, S.W.2.

RECEIVERS & COMPONENTS

BARGAIN LIST of Television and Radio Spares. S.A.E. to **SWIFT RADIO**, Mail Order Department, 21, Hibbert Road, Harrow Weald, Middx.

M & L CRYSTAL COIL, 2/6; M & L w/raction and circuits, 3/6; Nuts & Bolts, etc., ass., 2/6 lb. List 4d. **CARTER'S**, 578, Washwood Heath Road, B'ham, 8.

RATES: 5/- per line or part thereof, average five words to line, minimum 2 lines, Box No. 1/- extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

RECEIVERS & COMPONENTS

RADIO SUPPLY CO. (LEDS), LTD., 32, The Calls, Leeds, 2.—Ex. Gov. Smoothing Chokes, 90 ma. 3h, 100 ohms. 3/11; 50 ma. 50h, 1,000 ohms. Tropicalised, 4/9; Standard Pentode Output Transformers, 2/11; Push-pull, 6-8 watts. 5V6s to 3 ohms, 7/9; Vol. Controls, long spindle, less switch, 25K, 50K, 100K, 500K, 1/9; with switch, 25K, 100K, 500K, 1 meg., 2 meg., 2/11; Standard I.F. Trans., 465 kcs., 8/9 pr.; L. and M. T.R.F. Coils (high gain), 6/6 pr.; c.w.o. or c.o.d. under £1; post 1/- under £1; 1/6 under £3.

OSMOR for really efficient coils, coils-packs and all radio components, as specified for many "Practical Wireless" circuits. See our advert. on page 118 of this issue for free circuit offer, or send 5d. stamp to address below. **OSMOR RADIO PRODUCTS LTD.** (Dept. PC1), Borough Hill, Croydon, Surrey. (Tel.: Croydon 5148/9.)

6 VALVE Short Wave Battery Receivers: Rx. section of TR9D, 2RF stages, det., 2LF stages and KT2 O.P. stage; ready to operate on 3-6 mcs (wave band easily extended), (see "P.W." April, 1951), complete with all valves, a snip at 19/6 (post and pkg., 1/6). Smoothing Chokes. Adm. Rating, 6h at 70 ma, actual rating 10h at 100 ma. 140 ohms, size 3in. x 2in. x 2 1/2in. ideal choke for all normal smoothing; 4/6; new, in original packing, 4/6; 3-speed Gram. Motors (BSR), 78 r.p.m. and 33 r.p.m. for 200/250 A.C. volts, or 100/125 A.C. volts, complete with turntable and rubber mat. Full instructions enclosed, £3/18/7, inc. P.T.; Silver EF50s, ex brand new equipment, spotless condition, 7/6 each; 6v, 4-pin Oak Vibrators, 9/- each. We are still offering Free Gifts on our free catalogue, write for one to-day. **SERVIO RADIO**, 156-3, Merton Rd., Wimbledon, S.W.19. (Phone: LIB. 6525.)

TV WITHOUT MAINS.—Picture equal to mains supply, special Chorehorse AC/DC petrol electric generators, self-starting, self-contained, compact, AC voltage 220/250, 50/60 cycles, 250/350 watts; will also run radios, vacuum cleaners, small tools, etc.; DC output will charge batteries for permanent lighting; price £47/10/-, plus 10/- delivery. Below.

STORAGE BATTERIES, finest possible specification, dry, uncharged, 12v, 75 AH heavy duty, 29 plates, separate cells, in hardwood cases; price £7/17/6, delivery 9/6; 6v 90 AH, 15 plates, hard rubber cells, also suitable for cars, tractors, lorries; price £3/7/6, delivery 7/6. **TEDDINGTON ENGINEERING CO. LTD.**, Dept. "C," High Street, Teddington, Middx.

COMPONENTS. Our 1953 Catalogue is now available giving full details of our comprehensive range of components. **WATTS RADIO**, 8, Baker Street, Weybridge, Surrey.

RADIO AND T.V. Components. B.V.A. Valves, Chassis, Instrument Cases, Laboratory Equipment. Quick postal service. **KENDALL AND MOUSLEY**, 99, Dudley Port, Tipton, Staffs.

RECEIVERS & COMPONENTS

EDE'S STUDIOS offers some real bargains in new components this month. Electrolytic Condensers, TCC, 16 mfd, 350v can with tags, 2/- ea.; TCC, 32-16 mfd, 275v wkg. can, 3/6 ea.; BEC, 64 mfd, 450v. wkg, 525v surge, 4/6 ea.; BEC 32-32, 275v, also in same can, 50 mfd, 25v, small can, 4/6 ea.; Micamold, 1 mfd, 350v, metal cased wire-ended tubular, 8/6 doz. Micamold small, 0.1 mfd, 600v, 4/- doz. ELAC heater Transformers, prim 230v, sec 6.3v 1.5 amp, 7/6 ea., or large type 3 amp, 12/- ea. Wearite I.F. Trans., 465 K/cs. can, no. 501a and 502, 12/6 pr. Send cash with order or c.o.d. over £5 and add a little for postage, please to **EDE'S STUDIOS**, 274, Haydons Rd., Wembleton, London, S.W.19. (Phone: LIBerty 5327.)

BARGAIN PARCELS (advert. last month) still available. "A" 10 all. can Electrolytics (inc. 2 8x5000, 5/-; "B" Valveholders, tub. mica. etc., 5/- each, plus 1/- post; Coils, TRF, 5/- pr.; "P" 2/3, "Q" 2/9; brand new int. oct. V/holders, 4d. ea., 3/- dz.; Sleeving, 1/- dz. yds.; Multicore Solder, 2/6 dz. yds.; PK self-tap Screws, asst. gr., 3/-; BA Screw and Nuts, brand new, 2 gr. asst., 5/-, ex equip. lb. (approx. 500 pcs.), 5/-, Min. D. & P. 1/- List 3d. Instruction book for £6 S/het and £5/5- TRF, 1/6. **SUSSEX ELECTRONICS LTD.**, Princes Street, Brighton.

AMATEUR has quantity of Valves, Components, Loudspeakers, Pickups, Gramophone Records, etc., for disposal; no callers. Apply **PEPPER**, Bibury Road, Birmingham, 28.

SURPLUS 465KCs iron dust cored aligned and spaced IFTs (marked red, green, yellow, black), perfect + twin 500 per gang Condenser, 6/-, post 1/- American and British resistance Boards, 2lb. parcel 2/6, post 1/-. New list of Radio Bargains (inc. valves available. S.A.E. **THE RADIO SERVICES**, Lr. Bullingham, Hereford.

WALNUT Radiogram Cabinets, Stamp details. **E WISKER**, 501, Hale End Road, Highams Park, E.4.

WALNUT Radiogram Cabinets of distinction, stamp details. **R. SHAW**, 69, Fairlop Rd., E.11.

VALVES

"VIEWMASTER" Valves, exact to specification, guaranteed new and boxed, comprising 5 EF50, 1 6P25, 1 KT61, 1 EB91, 1 EB91, 2 6K25, 1 6P28, set of 12, £62/6 (post and insurance, 2/-); 6AM6, EF91, 6F12, Z77, 8D3, W77, EF92, 7/9; EB91, 6A15 6/9; 6V6G, 5Z4G, EPC33, MU14, U22, DH77, 6AT6, Pen46, L63, 6J5G, 1S5, 1R5, 1T4, 3V4, 354, 1S4, 8/6; P230, EL38, 17/6; EY51, ECC91, EF42, DK32, 1A7G, UBF80, PL81, PL83, U37, R16, CCH35, 10F1, 20L1, 6P15, 6C9, 12/-; UAF42, 6K8GT, CL33, PL33, PL82, 10F9, 10P13, 11/-; UL41, EL41, KT61, UDC41, EF41, UCH42, E240, PY30, 12A77, 10/6; 6J6, UY41, UF41, U404, ECH42, DL35, 1CSG, 10/-; ECL80, EF80, KTW61, 6SN7GT, 6SL7GT, 6Q7GT, 12Q7GT, 12K7GT, 12K8GT, 9/6; U50, 5Y3G, U78, 80, 25L6GT, 35L6GT, 50L6GT, 35Z4GT, 6V6GT, 9/-; EF39, EF8, EF50, 7C5, 7B7, 7HT, 7ST, 7/6; HVR2A, 6K7G, 6/3. All new and boxed; postage 4d. per valve extra. **READERS RADIO**, 24, Colberg Place, Stamford Hill, London, N.16.

PORTABLE MASTS. complete assemblies, including guys, bases and pickets; all rustproofed; 5ft. sections; stable in highest winds; 25ft. set 60/-, 30ft. 67/6, 35ft. 75/-; carriage paid; from **POST-MARINE**, The Willows, Windsor.

VALVES

WINWOOD FOR VALUE.—New boxed Valves. 6V6, 6F6, 6K6, 6Q7, 1C5, 1T4, 6B8, 6D6, 6K5, EL32, EF39, EF80, EF50, SP61, 5Y3, U50, 4 of any type or mixed 30/-; 6K7, 6J5, 757, 6SK7, 6N7, 6SS7, EB91, EF36, 12J5, 6C5, D63, 9D2, 4 any type 24/-; 6U7, soiled, tested, 4 for 16/-; 6K7, 6K8, 6Q7, 6V6, 5Z4, 37/6 set; 1T4, 1S5, 1R5, 3S4, 2S/- set; hundreds other types, stamp list. W and W Mains Trans. 325-0-325. 6v, 5v, 80ma. 19/6, post 1/-. New Mic. Trans. 3/6; P/pull O/rns., 10,000, 5 ohm. 5/6. Miniature 3-wave Coilpacks with circ., 32/6. **WINWOOD**, 12, Carnarvon Road, Leyton, E.10. (Mail only)

VALVES. types 6K7, 6K8, 6Q7, 5Z4, 5U4G, 1R5, 1S5, 1T4, 3S4, 807, 813, 829, 832, 723, A/B, etc., wanted urgently. Immediate collection. Write or phone: **PEPE HAYES RADIO**, 606, Kingsbury Rd., B'ham, 24. (ERD. 4942.)

RADIO and T/V Valves, new and boxed. EB91, EF92, EF80, EB91, 20D1, 6V6, 6F6, 6K6, EL32, 8/9 each; ECH35, EL38, 6K8, EL33, 11/- each; SP61, 6J5, 6C5, 6K7, 6J7, 6N7, 6Q7, 6/- each. **RADIO UNLIMITED**, Elm Road, London, E.17. (KEY. 4813.)

NEW VALVES WANTED, small or large quantities, all Television Valves and ECL80, EF80, EBC33, FN4/500, VU39, 6SJ7, 6V6, 6K8, 5Z4, etc., etc. Prompt cash. **W.M. CARVIS**, 103, North Street, Leeds, 7.

VALVES YOU CAN TRUST!

A—Maker's cartons.		B—Plain or Service cartons.	
Type	A/B	Type	A/B
6C20	4/0	6K34	— 2/6
6F60	9/6	6R8GT	12/6
6I16	5/-	6Q7G	10/9
6J56T5/9	—	6Q7G12/610/9	—
6J9	11/8	6R7	9/8
6K73	— 6/6	6R7W	— 8/6
6K87	7/6	6V6G11/7/3	— 8/6
6K7	7/0	6V6G	— 8/6
6K7G	8/6	— 12H6	— 2/9
6K71/6	5/9	954	2/6
7193	3/6	EA50	— 3/-

3d. stamp brings list of 250 other types available at surplus prices, details of Chassis Cutter Hire Service, etc., etc.

VC97: Full picture, 37/6 (carriage 3/-).
VALVEHOLDERS—1.0., BTG, amphenol, 9d.; 8/- doz.; BSA, BBR, B9A, 1/1; M.O. (pax), 5d.
CO-AX—Standard 30 ohms, 10d. yd.
RESISTORS—All valves, & w. loading, 8d.; 1 w., load, 9d.

2,000 MFD.—15 v. Mallory, metal can, 8/6. Post extra on orders under £1.

REED & FORD, 2A. BURNLEY ROAD, AINSDALE, SOUTHPORT.

WILCO ELECTRONICS

SEND FOR OUR NEW COMPREHENSIVE 38-PAGE LIST IN STAMPS

VALVES—Guaranteed Govt. surplus.

155	8/-	6SH7	5/6	EF36	7/6
174	8/-	6SL7GT	9/6	EF50	7/6
2X2	6/6	6SN7GT	10/6	EF54	6/6
5U4G	8/6	6SU7	10/6	EL35	11/6
5Z4G	8/6	6SVGT/G	8/6	EZ40	10/6
6AC7	5/6	6X5GT	9/6	H63	6/6
6B8G	12/6	12K8GT	12/6	KT61	10/6
6CD6	12/6	12SH7	5/6	KT66	11/6
6C9G	7/6	25L8GT	10/6	KTW63	8/6
6E6	4/-	35L6GT	19/-	L63	9/6
6J5G	6/6	50L6GT	10/-	M14	6/6
6J6	12/6	807	10/6	SP61	5/6
6J7GT	9/6	B36	10/6	11W/20	9/6
6K7G	8/6	DH77	10/-	V872	6/-
6K8GT	12/6	EC52	8/6	V870	10/6
6L8GT	11/6	EC54	6/6	W77	10/6
6N7GT	10/6	ECL80	12/6	Z77	11/6

POWER PACK—Input 230v., output 350-0-350v., 80 mA., with 5Z4 valve, 2-6.3v. windings, 40/-. Carriage 2/6.

LOW COST ADDRESSABLE ROAD, 204, CROYDON, TEL. AD 2027

FLUORESCENTS—Kits from 30/- "DYNALITE," 38, Stevedale Rd., Welting, Kent.

EDUCATIONAL

MERCHANT NAVY and Air Radio—Here is an opportunity to train as Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate. Day, Evening and "Radiocerts" postal courses. Estd. 30 years; s.a.c. for prospectus from Director. **THE WIRELESS SCHOOL**, 21, Manor Gardens, London, N.7. (Tel.: ARC 3694.)

BRITAIN'S Leading Radio College has vacancies for admission in April next; boarders accepted; scholarships available; training fees can be paid after appointment. Send stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

RADIO AND ELECTRONICS Correspondence School. Easy postal courses in radio and electronics; our courses are specially prepared for the amateur and beginner; moderate fees. Syllabus free. Write **THE SECRETARY**, Radio and Electronics Correspondence School, 27, Belmont Road, Wallington, Surrey.

WORLD TRAVEL and Adventure in the Merchant Navy. Young men, 15 years upwards, required for training in Marine Wireless and Direction finding at Sea. (Trainees in forthcoming Registration Groups are eligible for deferment of Military call-up.) Immediate sea-going positions on completion of training. Suitable candidates will be entered as officers and must be prepared to sail to all parts of the world. Low training fees. Send 1/- P.O. for Prospectus to **OVERSEAS HOUSE** (Dept. P.W.), Brooks' Bar, Manchester, 16. (Tel.: MOSS-side 2047.)

NEW YEAR BARGAINS!

RECORD-PLAYER CABINETS, ex-manufacture motorboard 14in. x 12in., internal height 5in., dark brown veneer, carried, carrying-handle and two basses, new cleaning up. Price 39/6, plus post and packing 2/6. **OUR OWN MAKE** ditto, brand new, uncut motorboard 15in. x 12in., internal height 6in., ideal for G4A, Collaro and Garrard Gram Units. Price 57/6, plus post and packing 2/6.

MICROGRAM CABINETS, ex-manufacturer. Overall dimensions: 18in. back to front x 8 1/2in. wide x 8 1/2in. high. takes any modern Gram Unit (not auto.). 2-3 watt amplifier and 6in. speaker. Store-soiled 35/-, carriage 3/6. Ditto cleaned up and fitted with 4in. uncut motorboard and cream experiment speaker grille and surround, 59/6, carriage 3/6.

DE-LUXE CONSOLE RADIOGRAM CABINETS in figured medium walnut, uncut motorboard, will take any modern Gram Unit or Autochanger etc. with R/G Chassis. Overall dimensions: 33in. high by 36in. wide x 15in. deep, large horizontal speaker grille. Callers only, £11.19.6.

GRAMERCY SUPER LIGHTWEIGHT CABINETS fitted Acos crystal insert for 78 or L.P. Bargain price, 50/-. Or with two interchangeable inserts for 78 and L.P. 80/-. Post 1/6.

TABLE-MODEL RADIOGRAM CABINETS, take Gram Unit, small receiver and speaker, beautifully made in figured medium walnut with angled, felt-lined lid. Only 65/-, carriage 2/6.

VALVES, unused, guaranteed: 6K7, 6Q7, VR56-EF36, EL32, 7/6 each. 3 for 21/-. Post 9d.

FULL CATALOGUE giving details of our famous "SYMPHONY" AMPLIFIERS, 3-speed Gram Units and Autochangers, and Complete Record-Players, Bass Reflex Cabinets (from 85/-), etc., etc. Two 21d. stamps.

NORTHERN RADIO SERVICES

16, Kings College Road, Swiss Cottage, London, N.W.3. Tel.: Primrose 8314

EVERYTHING for radio constructors, Condensers, Coils, Valves, Resistors, etc. Send stamp for list. **SMITH**, 98, West End Road, Morecambe. Quick service.

EDUCATIONAL

A.M.I.MECH.E., A.M.Brit.I.R.E. City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams. and courses in all branches of engineering, building, etc., write for 144-page handbook—free. **B.I.E.T.** (Dept. 242B), 17, Stratford Place, London, W.1.

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the College operated by Britain's largest electronic organisation. Moderate fees. Write to **E.M.I. INSTITUTES**, postal Division, Dept. PW28, 43, Grove Park Road, London, W.4. (Associated with H.M.V.)

THE INSTITUTE of Practical Radio Engineers Home Study Courses are suitable coaching text for I.P.R.E. and other qualifying examinations. Fees are moderate. Syllabus of seven modern courses post free from **SECRETARY**, I.P.R.E., 20, Fairfield Rd., London, N.8.

WIRELESS—Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only, if required, also postal courses. Apply **B.S.T. LTD.**, 179, Clapham Rd., London, S.W.9.

RADIO G200 ANNOUNCES!

VALVES at 2/9: RK34/2C34, D1, EA50, 7193, 954, 2x2/879; at 4/6: 4D1, 6H6, 12H6; at 5/6: 12H7, 4D1, 6S57; at 6/9: 9006 SC11, 6T5G, 6S67, 6SK7G, 6U5G, 12SC7, EC52, EF5G, EF54, U74, 12S17; at 7/9: 15C, 7C5, 7R7, 757, 7Y4, 1619; at 8/6: 1S4, 1R5, 1T4, N18, DH77, W77, 6AC7, KT44, 6K7Gs, 25L6Gt, 35L6Gt, 50L6Gt, D77, 6V6Gt, 6K6Gt, KL35, 6C6, 6D6; at 9/6: 6B6G, 6CH6, X78, 6N7Gt, 6B8Gm, 12AX7, 12AU7, 12AT7, K781, 2A3, 6B4; at 10/6: 6K8Gt, 6K8G, 12K8Gt, 5U4g, 5Z4g; at 12/6: CV2, 8012, 801, 5Z3; at 3/6: NGT1.

ARTHUR HOILE,
55, UNION STREET,
MAIDSTONE, KENT.

'Phone: 2812

STAN WILLETTS

111, High St., Blackheath, Birmingham.
SPECIAL OFFER—1T4, 1S5, 1R5, 3S4, brand new, 29/6 set or 7/9 each, post 6d.
VALVES, all brand new—RK34, 2C34, 1C6, EA50, 1R, VU111, 2/-, ATTA 3/6, KT241, 4/6, 11D5, 4/6, 3D5 3/6, 6J6, 10/6, EL91, 9/6, 6K7, 5/6, 6SN7, 8/11, 6V6, 8/9, 8D2, 1/9, 35L6, 8/6, EC52, 4/9, MU14, 8/11, 954, 1/6, 6F6, 8/9, 6K5, 11/6, 6J7, 5/9, 12A17, 9/6, 12U5, 4/-, 5Z4M, 8/6, VR135, 12A7, 5/9. Post extra.
IMA METER RECTIFIERS, new, 5/8.
GERMANIUM CRYSTAL, new, 3/6.
50 PFD. AIR-SPACED TRIMMERS, ceramic based, silver plated, new, 5/6 doz., post 6d.
OUTPUT TRANSFORMERS, 32-1, 55-1, 80-1, 80 mA., brand new, 3/11, post 6d.
32 PFD. CONDENSERS, 450v., guaranteed brand new, 6 for 8/9.
R155 complete with valve tester, guaranteed, £7-19-6.
WANTED—AR88, BC221, Eddystone 640, etc. Taylor, AVO, Meters, Valves, C.R.T. Tubes.

IS THIS YOU?



STOP before you build that superhet! Why burden yourself with complicated test gear, padding and trimming, etc., when you can so simply get our new and improved

3 waveband PRE-ALIGNED AND SEALED R.L.30 TUNING UNIT

If you can solder you can build our famous superhets, and literally have the World at your finger-tips! To make quite sure you cannot possibly fail, we are giving away, **ABSOLUTELY FREE** with each unit a 3/6d. set of *unique* Construction Sheets, containing our easy-as-A.B.C. diagrams and instructions to build the world-renowned **RODING 5-VALVE SUPERHET**. Send 2/6d. NOW for our new 1953 "HOME CONSTRUCTOR'S HANDBOOK," the radio book for the go-ahead man! This 46-page book contains all of our famous circuits and comes complete with current Catalogue.

RODING LABORATORIES (P3)
301 Hurn Airport, Christchurch, Hants.

HIGHSTONE UTILITIES

Soldering Irons, streamlined iron, with curved Pencil Bit, 200/250 v. 50 w., 11/6. Standard Iron, with adjustable bit 200/250 v. 60 w., 13/6. Heavy Duty Iron, 150 w., 16/6, all post 6d. Magnets, small ex 2in. meters, 1/- each, post 3d. Telephone Hand Generator, with handle, 9/6, post 1/6. Bell Transformers, for use on 200/250 v. A.C. Mains. Output 3, 5 or 8 volts at 1 amp. 9/- post 3d. Crystal Sets, which are fitted with a permanent crystal detector. Why not have a set in your own room—12/6, post 8d. De Luxe receiver in polished oak cabinet, 18/6, post 1/- Spare Permanent Detector, 2/- each. When ordered separately, 2/6. With clips and screws 2/10, post 3d. Headphones, in good order, 6/-; better quality, 7/6. New Headphones, 10/- a pair. Balanced armature type (very sensitive), 12/6 a pair, all post 8d. New Single Carcipes, 3/6. Bal. armature type, 4/6; ex-R.A.F. carcipes, 2/6, post 4d. All headphones listed are suitable for use with our crystal sets. Hand Microphones, with switch in handle and lead, 4/6. Similar instrument, moving coil, 7/8, post 9d. Sparking Plug Neon Testers, with vest pocket clip, 3/3, and with gauge, 3/6, post 3d. Ex-R.A.F. 2-valve (2-volt) Amplifiers, can be used to make up a deal and outfit, intercommunication system, or with crystal set, complete with valves and fitting instructions, 20/-, post 2/-. Ditto, less valves, 10/-. Wooden box to hold amplifier, 2/- extra. One valve amplifier, complete with valve, 10/6, post 1/8. Meters, 10 v., 2in. Rectifier (a.c.) in wooden carrying case, 14/6; 15 v. (a.c.) m.c., 9/6; 150 v., 2in. m.c., 10/-; 3.5 amp. 2in. T.C., 6/-; 4 amp., 2in. T.C. in case with switch, 7/6; 100 m.A. 2in. m.c., 7/8. All meters post extra. Meter units containing 2-500 microamps movements, 7/-, post 1/-. Money refunded if not completely satisfied.

HIGHSTONE UTILITIES,
58, New Winstead, London, E.11.
Letters only. New illustrated list sent on request with l.i.d. stamp and s.a.e.

FIRST-CLASS RADIO COURSES . . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—**YOU** can secure your professional qualification. Prepare for **YOUR** share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such success-compelling qualifications as **A.M.Brit.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London, B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches),** etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER 150,000 SUCCESSES

NATIONAL INSTITUTE OF ENGINEERING
(Dept. 461), 143, HOLBORN, LONDON, E.C.1

VALVES

All Guaranteed—24 hours service

41MP	5/-	EF80	10/6	6Q7	10/-
41MPT	5/-	ECL80	11/6	6K7	6/6
DDL4	4/6	EF91	10/6	6V6	9/6
MH1	4/6	6J7	9/6	5Z4	9/6
48SP1	5/-	6J7 (Z62)	4/6	FW4 500	9/6
CV86	5/-	6J5	5/6	EA50	2/6
CV9	4/6	6SN7	10/6	951	2/6
8D2	4/6	VR65	4/6	185	9/-
9D2	4/6	VR66	1/6	1R5	9/-
15D2	5/-	SP4	2/6	1R5	9/-
KT4	5/-	VR54	4/-	1T4	9/-
AR3	5/-	MSPEN		12K8	9/6
4V-triode	4/9	(7-pin)	4/6	ECH35	12/6
KT24-2v.		EF50	5/6	5U4G	9/-
Pen.	4/9	EF50		KT241	4/6
	9/-			(SYL)	8/6

SPECIAL CLEARANCE OFFERS

50yds. Adhesive Tape, 1.3. 6 Position Push-Pull Unit, 1.6. Voltage Regulator Panel, 3/- doz. Epicycle Drives, 1.6.

CONDENSERS.—B1, 4 mid., 500 v.w.v. 1.6. 8mtd. 2 mid., 500 v.w.v. 1.3. R.E.C. Midget Hunt, J50 v.w. 2.3. B.E.C. 8-16-450 v.w. 3/9. Mica Cond., .01, .001, 4/6 dz. Sprague, .001, 1/90 v.w. 5 - dz. Bulgin Red Lampholders, 1.6. Morse Code Tapper, wood base with buzzer, 5/6. Cond. Paper, 22-1 watt Resistors, 3 Westectors, 4/9.

SPEAKERS.—8in. M.E. 600 field resistance, 12/6. Celestion, 10in. P.M., 29/6.

Cp-Axial Cable—30 ohms per ft., 10d. yd. Control Unit, 1 Hoover Switch, 1 Yaxley switch, 1 Black Knob, 1.5 pin Plug and Socket, 1 7-pin Plug and Socket, 4/6.

Irganic Jack Socket, 1.6. Sleeving, 2 mm., 12 yds. for 2/9.

For these bargains write to :

REX RADIO

37, LOUIS ST., LEEDS, 7

New list ready. Mail order only.

PERISCOPES



Crowds can never stop you getting a good view at Football Matches, Sports Meetings, Parades and the Coronation, etc., if you have one of these periscopes. Beautifully made precision instruments, ex-W.D. Model in aluminium case, 3 1/2" x 4 1/2" x 1 1/2" each, fitted two angle prisms. Can easily be extended by metal or wood strips to the height required. (See sketch)

6/3 Per Pair
Plus 1/3 Post.

DYNAMO BARGAINS. H 39 volt, 9 amps., ball bearings, shunt wound, 2,500 r.p.m., by leading British Makers. **70/-** carr. 7/6.

CRYSTAL SETS, MORSE KEYS, MICROPHONES, TRANSFORMERS, BATTERY CHARGERS, ETC. Send us your enquiries.

ELECTRADIX RADIOS

Dept. G.214, Queenstown Road, Battersea, London, S.W.8.

Telephone : MACaulay 2159

LYONS RADIO

LTD.

3 GOLDHAWK ROAD Dept. M.P., SHEPHERDS BUSH, LONDON, W.12

Telephone : SHEPherds Bush 1720

VAC DIODES.—For the experimenter, 2 types of xtal diodes and constructors handbook for making 24 different devices such as electronic door lock, dry battery charger, radio control for models, etc. **PRICE 7/-.**

SCREENED CABLE.—Outside dia. 3/16in. copper conductor, screened and with outer insulating cover which gives it the appearance of coax. cable. Good for mike lead, etc. 12 yards, 9/6; over 12 yds. at 7/1d. per yd., 100 yd. coil, 50/-. Similar to above but less outer insulation, 6/9 for 12 yds.; 6/1 yd. over 12 yds., 100 yd. coil, 37/6.

CERAMIC ROTARY SWITCHES.—3 water, each water single pole 5 way, single hole fixing. **PRICE 4/3** each or 3 for 11/9 post free.

VALVES FOR R.1155.—New and tested, Type VR99 and VR102 at 7/6 each; VR100 and VR101 at 9/6 each; VR103 at 10/6 each. Postage any quantity, 1/-. Complete set of 7 for the receiver, i.e. (3) VR100, 2 VR101, and 1 each VR102 and VR99, at 52/6 post free.

INDICATOR UNITS TYPE 132.—Fitted with C.R. Tube type VCR517 suitable for scope or TV, 3 VR91's, 4 VR65's, 1-5U4, 9 wire-wound pots, mu-metal screen and a wealth of other useful components, in good condition and C.R.T. tested to ensure freedom from cut-off. At the special bargain price of 65/-. carriage 6/6.

ROTARY CONVERTER TYPE 3.—Air Min. ref. 5U2400. Input 24 v. D.C., 40 A. Output 115 v. A.C. single phase, 1,200 cycles at 4.35 A. Output power at unity p.f. 0.5kVA. **PRICE £3.10.**, carriage 6/6.

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

*No. of
Blueprint*

CRYSTAL SETS

- 1s. each.
1937 Crystal Receiver... PW71*
The "Junior" Crystal
Set PW94*

STRAIGHT SETS

Battery Operated

- One-valve : 2s. each.
The "Pyramid" One-
valver (HF Pen) ... FW93*

- Two-valve : 2s. each.
The Signet Two (D &
LF) FW76*

- Three-valve : 2s. each.
Summit Three (HF Pen,
D, Pen) PW37*

- The "Rapide" Straight
3 (D, 2 LF (RC &
Trans)) FW82*

- F. J. Camm's "Sprite"
Three (HF, Pen, D,
Tct) PW87*

- Four-valve : 2s. each.
Fury Four Super (SG,
SG, D, Pen) PW34C*

Mains Operated

- Two-valve : 2s. each.
Selectone A.C. Radio-
gram Two (D, Pow)... PW19*

- Three-valve : 2s. each.
Double - Diode - Triode
Three (HF Pen, DDT,
Pen) PW23*

- Four-valve : 2s. each.
A.C. Fury Four (SG, SG,
D, Pen) PW20*

- A.C. Hall-Mark (HF
Pen, D, Push-Pull) ... FW45*

SUPERHETS

- Battery Sets : 2s. each.
F. J. Camm's 2-valve
Superhet PW52*

*No. of
Blueprint*

SHORT-WAVE SETS

Battery Operated

- One-valve 2s. each.
Simple S.W. One-valver PW88*

- Two-valve : 2s. each.
Midget Short-wave Two
(D, Pen) PW38A*

- Three-valve : 2s. each.
Experimenter's Short-
wave Three (SG, D,
Pow) PW30A*

- The Perfect 3 (D, 2 LF
(RC and Trans)) ... PW63*

- The Band-spread S.W.
Three (HF Pen, D
(Pen), Pen) FW55*

PORTABLES

- Four-valve : 2s.
"Imp" Portable 4 (D,
LF, LF, Pen) FW86*

- 1s.
The "Mini-Four" All-
dry (4 valve superhet) PW

MISCELLANEOUS

- 2s. each.
S.W. Converter-Adapter
(1 valve) PW48A*
(2 sheets), 7s. 6d.

- The P.W. 3-speed Auto-
gram.

- The P.W. Electronic Organ
(2 sheets), 7s. 6c.

TELEVISION

- The Practical Television Receiver,
(3 sheets) 10/6

- The "Argus" (6in. C.R. Tube) 2/6

AMATEUR WIRELESS AND WIRELESS MAGAZINE STRAIGHT SETS

Battery Operated

- One-valve : 2s.
B.B.C. Special One-
valver AW387*

- Two-valve : 2s. each.
A modern Two-valver ... WM409*

Mains Operated

- Two-valve : 2s. each.
Consoelectric Two (D,
Pen), A.C. AW403

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk beside the blueprint number denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to Amateur Wireless, W.M. to Wireless Magazine.

Send (preferably) a postal order to cover the cost of the Blueprint (stamps over id. unacceptable) to PRACTICAL WIRELESS Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

*No. of
Blueprint*

SHORT-WAVE SETS

Battery Operated

- One-valve : 2s. each.
S.W. One-valver for
America AW429*

- Two-valve : 2s. each.
Ultra-short Battery Two
(SG, det Pen) ... WM402*

- Four-valve : 3s. each.
A.W. Short Wave World-
beater (HF Pen, D, RC,
Trans) AW436*

- Standard Four - valver
Short-waver (SG, D,
LF, P)... .. WM383*

Mains Operated

- Four-valve : 3s.
Standard Four-valve A.C.
Short-waver (SG, D,
RC, Trans) WM391*

MISCELLANEOUS

- Enthusiast's Power Am-
plifier (10 Watts) (3/-) WM387*

- Listener's 5-watt A.C.
Amplifier (3/-) ... W.M.392*

- De Luxe Concert A.C.
Electrogram (2/-) ... WM403*

QUERY COUPON

This coupon is available until March 2nd, 1953, and must accompany all Queries, sent in accord with the notice on page 170
PRACTICAL WIRELESS, Mar., 1953.

HAVEN'T YOU OBTAINED YOUR "MAXIMITE" plans?

A modern Super-Midget Superhet. only 6in. x 3 1/2in. x 2 1/2in. Latest modern miniature components used. to ensure maximum *Gain *Sensitivity *Troublefree working. No surplus parts specified; therefore avoiding possibility of leaky condensers and inability to supply exact specified components over a lengthy period. The receiver operates on A.C./D.C. and large mainsdroppers. Linecord etc., have been avoided. **FULL PLANS**, including point-to-point wiring, 1/5, post free.

METAL RECTIFIERS.—Westinghouse 14A95, 20/-; 1D36, 11/-; WX3, WX6, 3/9; 36EHT100, 29/4; LT52 (12v. 11a.), 19/6; 1 m.a. Meter, 12/6; 36EHT40, 21/6; 36EHT45, 23/8; 36EHT50, 26/-; S.T.C. Type K9/100, 14/8; K3/45, 9/-; RM1, 4/6; RM2, 5/-; RM3, 6/-.

***Q-MAX CUTTERS.**—Chassis Punch complete with Key: 4in., 4in., 12/4; 4in., 13/4; 4in., 14in., 14in., 16/-; 4in., 11in., 17/9; 4in., 19/9; 2/3-3 1/2in., 31/9; 4in. Square, 24/3.

HUNTS' MIDGET MOLD-SEAL CONDS.—1 mfd. 150v., 1/6; .02 mfd. 150v., 1/6; .005 mfd. 350v., .01 mfd. 350v., 1/6; .02 mfd. 800v., 1/2; .001 mfd. 350v., 1/3; .002 mfd. 350v., 1/3; Midget Electrolytics, 32-32 mfd. 250v., 2in. x 1in., 9/-; 16 mfd. 350v., 4/-.

VALVE HOLDERS.—10. Mazda 4-pin, 5-pin, 7-pin, 6d.; UX4, 5, 6, 7-pin, 6d.; BA, B8C, 1/3; B9A, 1/-; Ceramic, 1/8; B9G, 1/-; BTG, 1/- with Can., 2/6; Valve Cans (3-piece Octal), 1/6; B12A (Duo-decal), 2/6.

MAINS DROPPERS (New).—2a. 250 Ohms, .3a. 900 ohms, 5/-; Midget, 6/3; Linecord 2a. 100 ohms ft., .3a. 60 ohms ft., 8d. per ft. ADCOLA Pencil Bit Irons, 200-220v., 230-250v., 25/6.

I.F. TRANSFORMERS.—RSGB, 12/6; Wearite M600, 21/-; Super Midget RSRS, 21/-; All for 465 Kc/s. incl. Weymouth P4 type, 15/- per pair.

JACKSON.—Midget Perspex enclosed Twin Gang with Trimmers, 11/-; SLS Scale Drive Assembly, 27/6; SLS, 27/6; Full Vision, 13/9; Square-plane, 13/-.

COLVERN PRESET WIRE-WOUND POTS.—100, 250, 500, 1 K., 2 K., 2.5 K., 5 K., 10 K., 20 K., 25 K., 30 K., 3/3 each.

FILAMENT TRANSFORMERS.—200/240v. to 6.3v. 3a., 12/6; 200/240 v. 6.3v. 11a., 8/6; 200/240v. to 3-30v. 2a., 24/-.

CHASSIS.—Four sides folded with Angle Brackets (aluminium). 6in. x 4in., 5/9; 8in. x 6in., 7/3; 10in. x 7in., 8/3; 12in. x 8in., 9/3. All 24in. deep. All prices include postage on chassis.

COILS.—All Wearite "P" type, 3/- each; Weymouth "H" type, 3/9 each; "K" type, 5/-; CT2W2, 10/6 a pair; CS3W3, 12/6 a pair; T.R.F. Coils, M.W.L.W. with reaction, 7/6 a pair; "Viewmaster" Coils, London, 2/-; Birmingham, Holme Moss, Kirk o' Shotts, Wenvoe, 23/6 per set.

MIDGET ROTARY SWITCHES.—2p. 6v., 3p. 4v., 4p. 3v., 1p. 12v. (New), 4/-; Surplus, 8p., 4w. (4 Bank), 4/6; 6p. 3w., 3/6; 1p. 2w., 2/-; 1p. 3w., 1/3; 2p. 2w., 2/-.

T.C.C.—Picopack, 1 mfd. 350v., 2 mfd. 150v., 10 mfd. 25v., 20 mfd. 12v., 2/6; 100 mfd. 350v., 13/6; 250 mfd. 60v., 10/-; 2,500 mfd. 3v., 6/9; .001 mfd. 6 kV., 6/-; 12 kV., 10/-; 15 kV., 10/-; .01 mfd. 6 kV., 10/-; 1 mfd. 7 kV. (Dubilier), 20/-.

CHOKES.—40 m.a. Midget 5/6; 50 m.a., 15H, 6/6; 90 m.a., 10H, 14/-; 70 m.a., 1,200 ohms 40H, 17/6; 250 m.a. 5Hv., 19/6; Surplus, 150 m.a. 5H, 7/6; R.F. Chokes, TV diode, L9, 2/-; M.W.L.W., 2/6; Audio 3,000 ohms, 10/-.

SCOTCH BOY TAPE.—1,200ft., 35/-; Spare reels, 4/6.

VIEWMASTER VIB PARTS.—Width Control 10/-; Boost Choke, 5/9; Frame Trans., 25/6; Line Transformer, 32/6; Focus Magnets, 22/6; Vision Chassis, 18/6; Sound and T.V., 18/6; Bracket 6/-; Scanning Coils, 33/3.

RESISTORS.—Surplus 1 and 4 watt, 4d.; 1 watt, 6d.; Midget TV Type (New), 4 watt, 6d.; 1 watt, 8d. All standard 72 sizes stocked.

VIEWMASTER ENVELOPES 7/9 post free.

VALVES.—New Silver VR91 (EF50), 7/6; 12AX7, 6/-; 12AT7, 9/6; 6X6G5, 10/6; 5Z4G, 9/6; EZ40, 10/-; EF41, 10/-; EB91, 7/6; 6F14, 10/6; EB41, 10/-; 6N7, 8/-; EF36, 6/6; 6AG5, 8/6; 12K82, 9/-; 12AH7, 7/-; KT211, 7/6; 6H6A, 4/6; VU120a, 7/6; 6U5 (magic eye), 3/6; 6CD6G, 10/6; MS.PFN, 7/6; 12SC7 6/6.

"YOU CAN RELY ON US"

RADIO SERVICING CO.

444, WANDSWORTH ROAD, CLAPHAM LONDON, S.W.8.

Our No. 11 Catalogue, price 6d., Post Free. Postage: Over £2 free, below 10/-, 6d.; £1.9d., £2.1/-.

Telephone: MACaulay 4155. S.R. Station: Wandsworth Road. Open till 6.30 p.m. 1 o'clock Wednesday.

GARLAND BROS. LTD.

CHESHAM HOUSE, DEPTFORD BROADWAY, S.E.8. 5 OBELISK PARADE, LEWISHAM, S.E.13.

TEL: TIDEWAY 4412/3 TEL: LEE GREEN 4038

TRUVOX TAPE DESK.—Two-speed, pushbutton, high-impedance heads, £23.2.6, plus 15/- carriage, etc.

GARLAND RP.8.—6-watt, push-pull record-playback gramophone amplifier for use with Truvox Tape Desk, £19.10.0, plus 15/- carriage, etc. Send 2d. stamp for details of Desk and Amplifier.

THE NEW GARLAND LUB7 PORTABLE TAPE RECORDER.—Incorporating the Lane Tape Table, the New Garland UE7B Amplifier, high-fidelity cell microphone and 8in. loudspeaker, housed in a portable cabinet covered in attractive vinyl plastic. Price 41 guineas, plus 10/- carriage and packing. Trade supplied.

LANE TAPE TABLE.—3-motors, auto-brake, high-impedance heads, £16.10.0, plus 10/- carriage, etc. Trade supplied.

GARLAND UE7B RECORD PLAYBACK AMPLIFIER.—A revised version of our popular amplifier, designed to suit Truvox Tape Desk or Lane Tape Table. New features include higher gain, magic eye record-level indication, and smaller size for incorporation in portables. Oscillator and power supplies included. Standard valves throughout. Supplied complete with 8in. high-flux P.M. speaker. Price £13.2.6, plus 7/6 carriage, etc. Trade supplied.

GARLAND AMPLIFIER AC.11.—Quality amplifier giving 4 watts output. Transformer power supplies and isolated chassis. Price £6.2.6, plus 5/-, carriage, etc.

GARLAND KIT FOR AC.11.—£5.2.6, plus 5/- carriage, etc.

TAPE MASTER RECORDING HEADS.—Senior R/P Head, 5,000 ohms, 45/-; Junior R/P, 3,000 ohms, 39/6; Senior Erase, 45/-; Junior Erase, 39/6. Erase are low impedance. Tape Master Oscillator Unit, 45/-; Tape Master Oscillator Coil, 10/6.

ELECTROLYTIC CONDENSER OFFER.—8 mfd. 450v., 1/9 each; 8-32 mfd. 475v., 5/- each; 32-32 mfd. 350v., 4/9 each; 500 mfd. 15v., 2/9 each; 1,500 mfd. 6v., 2/- each.

METAL-CASED TUBULAR CONDENSERS.—.01 mfd. 1 kV., 1/- each; .02 mfd. 750v., 9d. each; .1 mfd. 350v., 9d. each; .25 mfd. 500v., 1/- each.

TWO-GANG CONDENSERS.—.00035 mfd., with fixing feet, 8/6 each.

I.F. TRANSFORMERS.—465 Kc/s, standard fixing, 13/6 per pair.

T.R.F. COILS.—Medium and long wave, aerial and H.F., 6/- per pair; with reaction windings, 6/9 per pair.

L.F. CHOKES.—10H 70 ma., 5/6 each.

PUSH-PULL OUTPUT TRANSFORMERS.—45/1 to match 6V6; etc. 4/6 each.

RESISTORS.—Up to 1 watt, 4d. each; 1 watt, 6d. each. Nearest value supplied unless otherwise specified.

DECALS.—Book of 500, white tin transfers for marking electronic and radio equipment: 4/9 per book.

GARLAND BROS.—Please send Post Orders to Deptford Branch

B.S.R. GRAMOPHONE UNITS.—3-speed motor with pick-up mounted on plastic playing table. Price £9.19.11, including purchase tax.

B.S.R. SINGLE SPEED PLAYER.—78 r.p.m. in portable plastic case. Provision for mounting pick-up. Price, £4/10/- and 5/- carriage.

MULTI-PURPOSE TOOL.—Bends, shears, punches and threads sheet-strip and rod. For all the little construction jobs that waste your time! With jig, gauge and protractor for accurate repetition work. Price 17/6.

H.R. HEADPHONES.—4,000 ohms, 15/- per pair.

ENGRAVING TOOL.—Operates direct from 200-240 volt A.C. mains for engraving on metal and plastic. Price 12/6.

TYANA SOLDERING IRONS.—Light-weight, 40 watt irons with easily replaceable elements and bits. Voltage ranges, 100/110v., 200/220v., 230/250v. Price 16/9.

"The iron that makes soldering a pleasure."

GARLAND OSCILLATOR UNIT.—For magnetic recording. Incorporating 6V6G Oscillator Coil, and supplying H.F. bias and erase for high impedance heads. Price £2.2.0, plus 2/6 post. Oscillator coil only, to resonate at 45 kc/s with 0.002 uF condenser, 6/9 each. Trade supplied.

WIREWOUND RESISTORS.—Open, cement-coated or vitreous enamelled. 4-watt, 21, 50, 90, 100, 200, 1k, price 1/- each; 6-watt, 30, 145, 250, 270, 10k, 15k, price 1/6 each; 10-15 watt, 5, 90, 100, 120, 170, 175, 200, 250; 400, 500, 600, 700, 750, 950, 1k, 1690, 3.5k, 3.6k, 4.5k, 4.7k, 11k, 15k, 20k, 25k, 47k, 50k, price 1/9 each; 15 watt, 650 ohm, price 2/- each.