

BEGINNER'S GUIDE TO RADIO



Vol. 30 No. 574

AUGUST 1954


EDITOR:
F.J. CAMM

PRACTICAL WIRELESS

A
UNIVERSAL

PUSH-BUTTON

4

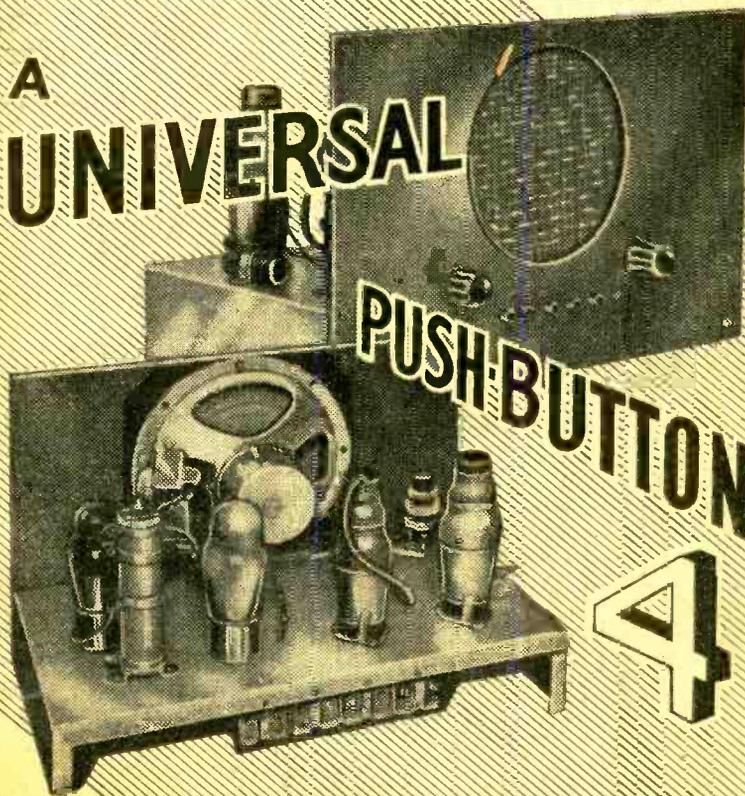

IN THIS ISSUE :


AMPLIFIER DESIGN
IMPROVING THE TAPE DECK
AMPLIFIER
SURPLUS R.F. PENTODES

WIDE-BAND COUPLERS
MAINS SUPPLIES FOR BATTERY VALVES
NOISY RECEPTION
STABILISED POWER SUPPLIES

R.S.C. 25 WATT QUALITY AMPLIFIER 9 Gns.

We firmly believe our All "Push-Pull" Quality Amplifier to be by far the best value in amplifiers offered to-day. The volume of its high fidelity reproduction is completely controllable, from the sound of a quiet intimate conversation to the full, glorious volume of a grand orchestra. Its sensitivity is so high that in areas of fair signal strength it can be operated straight from a crystal receiver. Entirely suitable for standard or long playing records in small homes or in large auditoriums. For electronic organ or guitar or for garden parties or dance bands. The kit is complete to the last detail, and includes easy to follow point-to-point wiring diagrams.

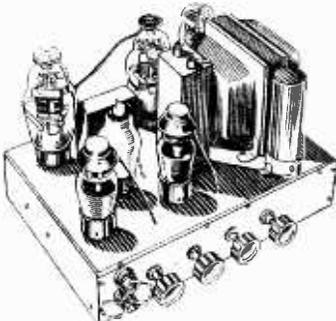Outputs for 3 or 15 ohm speakers. Twin volume controls with twin input sockets allow SIMULTANEOUS INPUTS for BOTH MICROPHONE and GRAM, or TAFE and RADIO. SEPARATE BASS and TREBLE CONTROLS, giving both LEFT and CUT. FOUR NEGATIVE FEEDBACK



1,000PS with 15 db in the main loop from output transformer to voltage amplifier. Frequency response 3 db. 50-20,000 c.p.s. HUM and DISTORTION LESS THAN 0.5

percent, measured at 10 watts, comparing favourably with most highest priced amplifiers. Six B.V.A. valves, Marconi Osram KT series output valves. A.C. only. 200-230-250 v. 50 c.s. input. A.C. only. H.F. LINE. Paper reservoir condenser. Complete on basis. Matched components. Size 14-10-9in. Available in kit form at the amazingly low price of 9 gns. Plus carriage 3s. Or ready to use 50/- extra.

R.S.C. 8-10 WATT "PUSH-PULL" HIGH-FIDELITY AMPLIFIER A3

Complete with integral Pre-amp. Tone control stage (as All amplifier), using negative feedback, giving humproof individual bass and treble lift and cut tone control. SIX Negative Feedback Loops. Completely negligible hum and distortion. Frequency response 3 db. 30-20,000 c.p.s. Two independently controlled inputs. Six B.V.A. valves. A.C. mains 200-230-250 v. input only. Outputs for 3 or 15 ohm speakers. Kit of parts complete in every detail. £7.10.6. plus carriage, for ready to use. 45/- extra.

H.V.A. LONG PLAYING RECORD UNSTABLE WITH CRYSTAL PICK-UP (Sapphire Stylus). Speed 33 1/3 r.p.m. For A.C. mains 200-250 v. Limited supply. Brand New Cartoned. Perfect. Only £3-19.6. Plus carr. 7s. (Normal price £8 approx.)

BATTERY SET CONVERTER KIT. All parts for converting any type of Battery receiver to a Full Mains A.C. 200-250 v. 50 c.s. Kit will supply fully smoothed H.T. of 120 v., 90 v. or 60 v. at up to 40 mA. and fully smoothed L.T. of 2v. at 0.4 to 1 a. Price, complete with circuit, wiring diagrams and instructions, only 48/6. Or ready to use. 8/9 extra.

PERSONAL SET BATTERY SUPERSEDER KIT. A complete set of parts for construction of a Full Mains (or metal case) to replace Batteries where A.C. Mains supply is available. Input 200-250 v. 50 c.s. Outputs 90 v. 10 mA and 1.4 v. 250 mA. fully smoothed. For 4-valve receivers. Price complete with circuit. Only 35/9. Or ready for use. 42/6. Size of unit. 9 1/4 x 4 1/2 in.

BATTERY CHARGER KITS For mains 200-250 v. 50 c.s. To charge 6 v. acc. at 2 a. 25/6. To charge 6 or 12 v. acc. at 2 a. 31/6. To charge 6 or 12 v. acc. at 4 a. 49/6. Above circuit of transformer, full wave rectifier, fuse, resistors and steel case. Any type assembled and tested. 6/9 extra.

THE SKY CHIEF T.R.F. RECEIVER A design of a 1-stage, 3-valve 200-250 v. A.C. Mains receiver with selenium rectifier. It consists of a variable Mu high gain H.F. stage followed by a low distortion grid detector triode. The next stage is a further triode amplifier with tone control by negative feedback. Finally comes the output stage consisting of a parallel connected double triode giving ample output at an extraordinary low level of distortion. Point to point wiring diagrams, instructions and parts list 2/6. This receiver can be built for a maximum of £4 16/- including attractive Brown or Cream Bakelite or Walnut veneered wood cabinet 12 x 6 1/2 x 5 1/2 in.

ELECTROLYTICS - Current production. Not ex-Govt.

Tabular Types	8µF 500 v.	2 1/1
8µF 350 v.	16µF 450 v.	2 1/2
8µF 450 v.	24µF 350 v.	2 1/1
8µF 500 v.	32µF 350 v.	2 1/1
16µF 350 v.	32µF 150 v.	4 1/9
16µF 450 v.	40µF 450 v.	4 1/11
16µF 500 v.	64µF 450 v.	4 1/9
24µF 350 v.	8-8µF 450 v.	3 1/9
32µF 350 v.	8-8µF 450 v.	3 1/9
25µF 25 v.	8-16µF 450 v.	2 1/11
50µF 12 v.	8-16µF 450 v.	3 1/11
50µF 25 v.	16-16µF 450 v.	4 1/11
	16-32µF 350 v.	5 1/3
	32-32µF 150 v.	5 1/11

Cap Types

8µF 450 v.	2/3
------------	-----

RECORDING TAPE. Best Quality. Plastic. 1,200 ft. Reels only 18/9.

Terms C.A.O. or C.O.D. NO C.O.D. under £1. Post 1/- extra under 10/-, 1/6 extra under £1 : 2/- extra under £2 : 2/6 extra under £3. Open 9 to 5.30 : Sat. 10 till 1 pm. List 6d. Trade list 5d. S.A.E. please with all enquiries.

A PUSH-PULL 3-4 watt HIGH-GAIN AMPLIFIER FOR £3 12/6. For mains input 200-250 v. 50 c.s. Complete kit of parts including fruit, point to point wiring diagram, and instructions. Amplifier can be used with any type of Feeder Unit or Pick-up. This is not A.C. D.C. with "live" chassis, but A.C. only with 300-0-300 v. trans. Output is for 2-3 ohm speaker. (We can supply a suitable 10in. unit by Rola at 27/9.) The amplifier can be supplied ready for use for 25/- extra. Carr 2/6. Full descriptive leaflet, 7d.

BRAND NEW COLLARO 3 SPEED AUTOMATIC RECORD CHANGERS. Type RC3 521, with Orthodynamic Magnetic Pick-up and matching trans. Separate (switched) Alloy Styl for standard or long playing records. Mains input 200-250 v., £9 19/6. Plus Carr. 5/-.

COLLARO 3-SPEED MIXER AUTO-CHANGERS. RC3 522 with "Plus-in-1" Crystal Heads for Mains 200-250 v. 50 c.s. Brand New cartoned. £10 10/-, Carr. 9/-.

MICROPHONES. Crystal type, good quality. Recommended for use with our amplifiers. Hand type. 59/6; Stand type. £6 19/6.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and impregnated. Primaries 200-230-250 v. 50 c/s Screened

TOP SHROUDED DROP THROUGH

250-0-250 v. 70 mA. 6.3 v. 2.5 a	12 1/11
260-0-260 v. 70 mA. 6.3 v. 2.5 a	14 1/11
350-0-350 v. 80 mA. 6.3 v. 2.5 a	17 1/9
275-0-275 v. 80 mA. 6.3 v. 2.5 a	14 1/11
250-0-250 v. 100 mA. 6.3 v. 4 a	21 1/11
300-0-300 v. 100 mA. 6.3 v. 4 a	21 1/11
0-1.5 v. 3 a	21/-
350-0-350 v. 100 mA. 6.3 v. 4 a	21 1/6
350-0-350 v. 150 mA. 6.3 v. 4 a	27 1/9
350-0-350 v. 150 mA. 6.3 v. 2 a	29 1/11
5 v. 3 a	29 1/11

FULLY SHROUDED UPRIGHT

250-0-250 v. 60 mA. 6.3 v. 2 a	5 v. 2 a	16 1/8
350-0-350 v. 70 mA. 6.3 v. 2 a	5 v. 2 a	18 1/9
250-0-250 v. 100 mA. 6.3 v. 4 a	5 v. 3 a	22 1/9
250-0-250 v. 100 mA. 6.3 v. 6 a	5 v. 3 a	22 1/9
for RI-355 conversion	...	29 1/9
300-0-300 v. 100 mA. 0-4-6.3 v. 4 a	0-4.5 v. 3 a	22 1/9
250-0-250 v. 100 mA. 0-4-6.3 v. 4 a	0-4.5 v. 3 a	22 1/9
350-0-350 v. 150 mA. 6.3 v. 4 a	4 v. 3 a	31 1/6
350-0-350 v. 250 mA. 6.3 v. 6 a	4 v. 8 a	31 1/6
0-2-6 v. 2 a. 1 v. 3 a. for Electronic Eng. Amplifier	...	69 1/6
425-0-425 v. 200 mA. 6.3 v. 4 a. C.T.	...	69 1/6
6.3 v. 4 a. C.T. 5 v. 3 a. Suitable Williamson Amplifier, etc.	...	47 1/6
Economy Quality Amplifier type	...	52 1/6
450-0-450 v. 250 mA. 6.3 v. 6 a	6.3 v. 6 a	69 1/6
5 v. 3 a	...	69 1/6

ELIMINATOR TRANSFORMERS Primaries 200-250 v. 50 c/s. 120 v. 40 mA 7/9 90 v. 10 mA. 7-0 v. 250 mA. ... 8 1/11

CONNOISSEUR HIGH FIDELITY LIGHTWEIGHT MAGNETIC PICK-UP COMPLETE WITH MATCHING TRANSFORMER. A fortunate purchase enables us to offer limited supplies. Brand New and Perfect at a fraction of normal price. Only 26/6.

FOUR STAGE FEEDER UNIT. Design of a High Fidelity Tuner Unit. L. & M. Wave. Full de-coupling. Self contained heater supply. Detailed wiring diagrams parts list and illustration. 2/6. Total building cost. £3 15/-.

COAXIAL CABLE. 75 ohms. 1 in., 70 yard. Twin Screened Feeder. 9d. yard.

P.M. SPEAKERS. All 2-3 ohms. 6 in. Goodmans. 16 9. 8 in. Plessey. 15 9. 10 in. Plessey. 18 6. 10 in. R.A. 29 6. 10 in. Rola with trans. 29 6. 12 in. Truvox. 49 9. 10 in. W.B. "Stentorian" 3 or 15 ohm type HF1012 10 watts. Highly recommended for use with any of our amplifiers. £3 13 1/6.

M.E. SPEAKERS. All 2-3 ohms. 6 in. Rola. Field 600 ohms. 11 9. 10 in. R.A. Field 800. 1,000 or 1,500 ohms. 23 9.

VOLUME CONTROLS with long (2 in.) spindles, all values, less switch 1/9. with S.P. switch 3/9. D.P. sw. 4/9.

R.S.C. MAINS TRANSFORMERS (FULLY GUARANTEED)

Interleaved and impregnated. Primaries 200-230-250 v. 50 c/s Screened

FILEMATE TRANSFORMERS

All with 200-250 v. 50 c/s primaries	6.3 v.	1.5 a	5 9	
	6.3 v. 2 a	7 6	0-4-6.3 v. 2 a	7 9
	12 v. 1 a	7 11	6.3 v. 3 a	8 11
	6.3 v. 6 a	17 6	12 v. 3 a or 2.4 v. 1.5 a	17 6

CHARGER TRANSFORMERS All with 200-230-250 v. 50 c/s Primaries : 0-9-15 v. 1.5 a. 14 9 : 0-9-15 v. 3 a. 16 9 : 0-9-15 v. 6 a. 22 9 : 0-14-15-24 v. 2 a. 22 9.

SMOOTHING CHOKES

270 mA 4.5 H 50 ohms	11 9
100 mA 10 H 175 ohms Potted	8 9
80 mA 10 H 350 ohms	5 6
80 mA 10 H 400 ohms	4 11
20 mA 30 H 1,000 ohms	4 9

E.H.T. TRANSFORMERS 2,500 v. 5 mA. 2-0-2 v. 1.1 a. 2-0-2 v. 1.1 a. for V.C.T. RC3517, etc. ... 36 6 5,000 v. 10 mA 2 v. 2 a. ... 39 6

OUTPUT TRANSFORMERS

Midget Battery Portode 68:1 for 354 etc. ... 3 9

Small Pentode 5,000Ω to 3Ω ... 3 9

Standard Pentode. 5,000Ω to 3Ω ... 4 9

Standard Pentode. 7,000Ω to 3Ω ... 4 9

Multi-ratio 40 mA. 20:1. 45:1. 80:1. 90:1 Class B Push-Pull ... 5 6

Push-Pull 10-12 watts 6V6 to 3Ω or 15Ω ... 15 9


Push-Pull 10-12 watts to match 6V6 to 3-5-8 or 15Ω ... 16 9

Push-Pull 20 watts. sectionally wound. 8L6, KT66, etc. to 3 or 15Ω ... 47 9

Economy Quality Amplifier type ... 47 9

(LEEDS) LTD.

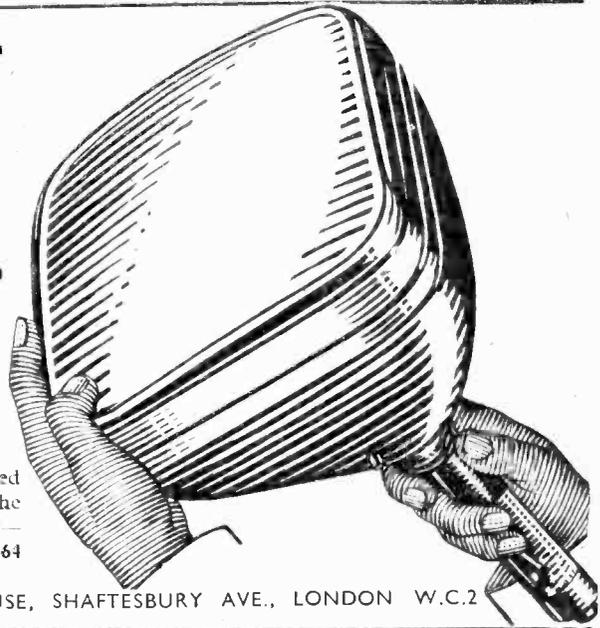A GOOD SET deserves a **Mullard** long life picture tube



Technical Service Department will be pleased to send you Data Sheets describing any of the following Mullard Long Life Picture Tubes:—
12" MW31-74 14" MW36-24 17" MW43-64




MULLARD LTD., CENTURY HOUSE, SHAFTESBURY AVE., LONDON W.C.2

MVM 262

Masterpieces in miniature 'METALMITE' CONDENSERS

This T.C.C. "Metalmite" range of condensers sets a new standard both for compactness and ability to withstand extreme tropical conditions: satisfactory insulation resistance is maintained after extensive tests at 100°C. and 100% humidity. "Metalmites" are suitable for use in miniature receivers and transmitters, hearing aids, and in the most compressed types of portable equipment.

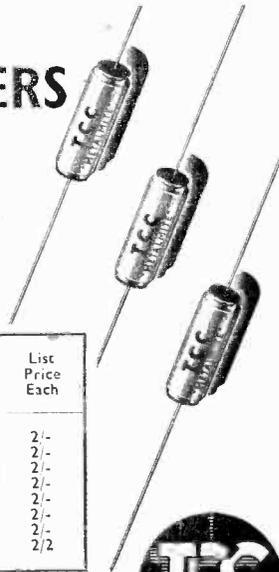Capacity tolerance - ± 25%
Temperature range - 40°C. to + 100°C



SUPER TROPICAL MINIATURE "METALMITES"

Capacity μ.F.	Working Volts D.C.		Dimensions in inches		Type No.	List Price Each
	At 70°C.	At 100°C.	L.	D.		
.0002	500	350	1 1/4	.2	CPI10S	2/-
.0003	500	350	1 1/4	.2	CPI10S	2/-
.0005	500	350	1 1/4	.2	CPI10S	2/-
.001	350	200	1 1/4	.2	CPI10N	2/-
.002	350	200	1 1/4	.22	CPI11N	2/-
.005	200	120	1 1/4	.22	CPI11H	2/-
.01	200	120	1 1/4	.25	CPI12H	2/-
.01	350	200	1 1/4	.34	CPI13N	2/2

DETAILS OF COMPLETE RANGES AVAILABLE ON REQUEST



THE TELEGRAPH CONDENSER CO. LTD

RADIO DIVISION · NORTH ACTON · LONDON · W3 · TELEPHONE: ACORN 0061



Never before

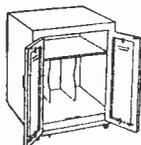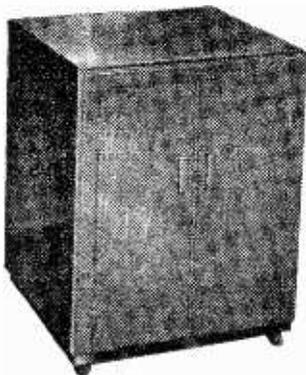SUCH VALUE, EYE-APPEAL AND WORKMANSHIP...



These two Cabinets set a new standard in value and workmanship. The traditional excellence so long associated with W B is evidenced in pleasing design, finest materials and superb finish; here are cabinets that will enhance any room, provide ample storage space in compact form.



'MELODY' TV and RECORD CABINET

(As illustrated)

Accommodates TV or radio receiver on top; room inside for 150 10" or 12" records. Highly polished French walnut veneer finish, interior in lacquered birch. Fitted with easy-running castors and has removable record index cards clipped inside doors. Rubber buffers at back of cabinet. No Purchase Tax.

Size: 26" x 20" x 18½". Price **£9.17.6**

WHITELEY ELECTRICAL RADIO CO. LTD.

MANSFIELD · NOTTS

'SYMPHONY' RECORD CABINET

Capacity: 250 300 10" records. Top is large enough to take record player or medium-size TV or radio set. Highly polished French walnut veneer finish, interior in lacquered birch. Easy-running castors, removable record index cards in doors, rubber buffers at back of cabinet. No Purchase Tax. Size: 29½" x 20" x 14½". Price **£9.7.6**

MAKERS OF THE FAMOUS RANGE OF STENTORIAN SPEAKERS

MAXI-Q
REGD.

STOP PRESS! WE PROUDLY PRESENT OUR LATEST HIGH STANDARD LOW PRICED INSTRUMENT WHICH WE KNOW WILL BECOME A PRIZED AND INDISPENSABLE POSSESSION IN EVERY CONSTRUCTOR'S SHACK



MODULATED TEST OSCILLATOR MTO.1

- ★ Provides a modulated signal suitable for I.F. alignment also trimming and tracking R.F. circuits.
- ★ Frequency is continuously variable from 170-475 Kc/s and 550-1600 Kc/s.
- ★ Operates from a single 9 volt grid bias battery which is housed within the unit.

Price **£3.15.0** obtainable from all reputable stockists or in case of difficulty direct from works. Send for our General Catalogue (9d. post free).

DENCO (CLACTON) LTD. 357/9 Old Road, Clacton-on-Sea, ESSEX



radio products ltd. (Dept. P50)
 418, BRIGHTON ROAD, SOUTH CROYDON, SURREY. 'phone CRO 5148

OSMOR COILPACKS give quality and performance right out of proportion to their midget size and modest cost. They have everything that only the highest degree of technical skill can ensure—extra selectivity, super sensitivity, adaptability. Size only 1 1/2 in. x 3 in. x 2 1/2 in. with variable iron-dust cores and polystyrene formers. Built-in trimmers. Tropicalised. Prealigned, receiver-tested and guaranteed. Only 5 connections to make. All types for Mains and Battery superhets, and T.R.F. receivers. Ideal for the reliable construction of new sets, also for conversion of the 2I Receiver, TR1196, Type 18. War-time Utility and others. Send to-day for particulars!




CHASSIS CUTTER

Type	Hole Sizes
1	1 in. x 1 1/2 in.
2	3/4 in. x 1 1/2 in.
3	3/8 in. x 1 1/2 in.
4	1 1/2 in. x 2 in.

Illustr. price list on request.

I.F.s. 465 k/c. Permeability-tuned with flying leads. Standard size 1 1/2 in. x 1 1/2 in. x 3 in. For use with OSMOR coilpacks and others, 14/6 pair. MIDGET I.F.s. 465 k/c. 3/4 in. x 3/4 in. x 2 1/2 in. 21/- pair. PREALIGNED 1/6 extra. Both types.

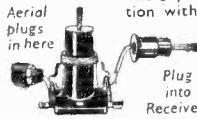- TYPE METRES
 1—141-250
 2—218-283
 3—267-341
 4—319-405
 5—395-492
 6—455-567
 7—1450-1550
 8—410-550 k/c



OSMOR STATION SEPARATOR

The Separator may easily be tuned to eliminate any one Station within the ranges stated and fitting takes only a few seconds. Sharp tuning is effected by adjusting the brass screw provided. Complete with plug, socket and full instructions—nothing to add.

7/6 POST FREE Satisfaction guaranteed.

SEPARATE COILS
 4/- EACH



A full range is available for all popular wavebands and purposes. Fully descriptive leaflet and connection data available. List note these 5 star features:—
 ★ Only 1 in. high. ★ Packed in damp-proof containers. ★ Variable iron-dust cores. ★ Fitted tags for easy connection. ★ Low loss Polystyrene formers.

We keep stocks of many radio components for use in published circuits, including:

"WIRELESS WORLD"

No Compromise T.R.F. Tuner. Midget Mains Receiver. Sensitive 2-Valve Receiver. Television Converter, etc. Midget Sensitive T.R.F. and Many Others.

"PRACTICAL WIRELESS"

Coronet "FOUR," Beginners' Superhet. Modern High Power Amplifier 2. Attache Case Portable; R1155 Converter; A.C. Band-pass 3; Modern 1-Valver; 3-Speed Autogram, etc., etc.

FREE!

Send 5d. (stamps) for literature including The really efficient 5 valve Superhet Circuit, 6-valve ditto, 3-valve (plus rectifier) T.R.F. circuit. Battery portable superhet circuit. Coil and Coilpack leaflets, radio and component lists, and interesting miniature circuits, etc.

OUR TECHNICAL DEPT. WILL BE PLEASED TO ANSWER (BY LETTER ONLY) ANY ENQUIRY RELATING TO CIRCUITS IN WHICH OSMOR COILS OR COIL PACKS ARE USED OR ARE INTENDED TO BE USED.

BRIMAR VALVES

More Reliable than EVER!



Brimar's long experience in the manufacture of special quality TRUSTWORTHY valves is now being reflected throughout the entire Brimar range. Improved production methods, new and better assembly jigs, tighter control on the composition of materials, and the closer supervision of vital processes have resulted in valves with more uniform characteristics, greater mechanical strength and a higher standard of reliability as shown in the 12AT7.

The 12AT7 is a very reliable frequency changer and is widely used in modern TV receivers, VHF and UHF communications equipment. It is also frequently employed in industrial equipment, computers, navigational aids and test equipment.

Use the BRIMAR 12AT7—with improved performance —at NO EXTRA COST now is the time to



BRIMARIZE!

BRIMAR	MULLARD	MARCONI OSRAM	COSSOR EMITRON
12AT7	ECC81	B152 & B307	12AT7

Standard Telephones and Cables Limited FOOTSCRAY, KENT. FOOTSCRAY 3333

Great Britain's Valve Mail-Order House



SALE (2,000 101 TYPES) VALVES FROM 2/- (post. 9d.)

Types and Prices subject to stock. We may send equivalents. When ordering cross (blank) postal order.

RADIO BULLS VALVES 246, HIGH ST. HARLESDEN NW11



SERVICE SHEETS The one you require enclosed if available in a dozen assorted of our best choice.

TAYLOR METERS ON EASY TERMS Table with columns for Total Cash Price, Deposit, 10 Monthly Payments of, and Total H.V. Price.

Valve list table with columns for valve type (e.g., 1B5, 1B6, 1B7) and price.

Valve list table with columns for valve type (e.g., 61A, 61B, 61C) and price.

2/3 MEMORABLE VALVES MANUAL 2/3 Giving equivalents of British and American Service and Cross Reference of Commercial Types with an Appendix of B.V.A. Equivalents and Comprehensive Price List. We have still some Valves left of rare old British Range (33/2).

ROD ANTENNAS, 10" sections interlocking and extending copper plated steel. BARGAIN. 2/6

TYANA TRIPLE THREE Small folding iron. Latest development. Complete with detachable brush and Post 1/-

B.T.H. GERMANIUM CRYSTAL DIODE Complete with Blueprint and operating instructions. 3/-

HEADPHONES

Ex-Govt. BARGAIN



TUBES

TYPE 511, 12". Electrostatic (same base as VCR97). £4-10-0

VCR97 20/-

EMISCOPE TYPE 4, 1 3". Electrostatic in Sealed Box. 20/-



2000" AUTOMATIC BLOWLAMP Burns naphthalene spirit. Completely Automatic. Absolutely safe. Suitable for all kinds of nuts and silver soldering, glass bending, etc. 2,600 deg. Fahrenheit flame. Post 9d.


Deposit and Monthly 10 AC ELECTRIC PAINT SPRAYER



NEW! RADIO & T.V. OUTFITS

LEARN THE PRACTICAL WAY

Specially prepared sets of radio parts (which you receive upon enrolment) with which we teach you, in your own home, the working of fundamental electronic circuits and bring you easily to the point when you can construct and service radio sets. Whether you are a student for an examination; starting a new hobby; intent upon a career in industry; or running your own business — these Practical Courses are intended for YOU — and may be yours at very moderate cost.

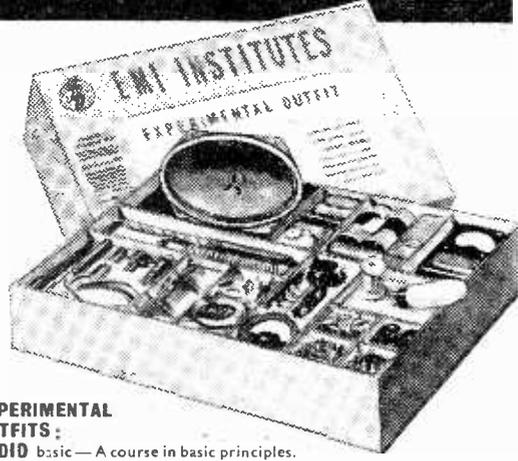

EASY TERMS FROM £1 A MONTH

All lessons and equipment supplied immediately and becomes your own property.

POST THIS COUPON TODAY Please send me your FREE book on Practical Courses: I am interested in..... To: E.M.I. INSTITUTES, Dept. 32X, 43 Grove Park Road, Chiswick, London, W.4. NAME..... ADDRESS..... POST.....

EXPERIMENTAL OUTFITS: RADIO basic — A course in basic principles. RADIO — Instruction and equipment from which you build a Radio Receiver. TELEVISION — Instruction and equipment for building a Television Receiver. Also for Mechanics Electricity, Chemistry, Photography, Carpentry, Draughtsmanship, Commercial Art, Amateur S.W. Radio, Languages.


E.M.I. INSTITUTES The only Postal College which is part of a world-wide Industrial Organisation

**Positively the 2 BEST T/Vs yet built
for the Home Constructor!**

The STERN'S "TELE-VIEWERS"

5 CHANNEL SUPERHET RECEIVERS

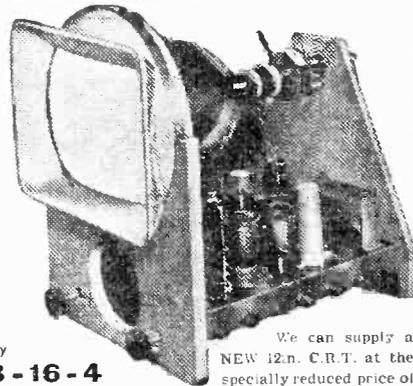Suitable for any transmitting channel and for which commercial adaptors will be available.



We can supply a NEW 12in. C.R.T. at the specially reduced price of £12.19.5. (Carr. & Ins. 15/- extra.)



PERFECT PICTURE QUALITY
SIMPLE DIAGRAMS MAKE CONSTRUCTION EASY



BETTER FRINGE AREA RECEPTION
BETTER RECEPTION AT HALF COMMERCIAL COST


The "WIDE-ANGLE" TELE-VIEWER

- * This is the most efficient large screen TV set offered to constructors.
- * Excellent Time Base efficiency producing 15 to 16 Kv with ample scanning power for C.R.T.'s up to 17 inch.

CAN BE COMPLETELY BUILT FOR

£33 - 0 - 0

(Plus cost of C.R.T.)

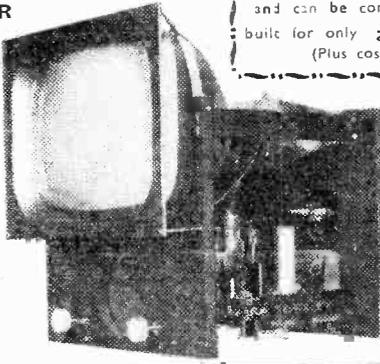

This is the 12" TELE-VIEWER and can be completely built for only **£28 - 16 - 4** (Plus cost of C.R.T.)

The complete set of ASSEMBLY INSTRUCTIONS for these T/Vs are available for 5/- each. They include really detailed PRACTICAL LAYOUTS, WIRING DATA AND COMPONENT PRICE LIST. ALL COMPONENTS ARE AVAILABLE FOR INDIVIDUAL PURCHASE. AN ATTRACTIVE TABLE MODEL CABINET FOR THE 12in. Model IS AVAILABLE FOR £6.19.6.

STERN RADIO LTD.

109 & 115, FLEET STREET, E.C.4.

TEL.: CENTRAL 5812-3-4.



ALPHA . . . an exclusive offer

PORTABLE RADIO ATTACHE CASE

SIZE : 11in. x 9in. x 3 1/2in.

available in the following colours :

- LIZARD GREY ● MAROON
- BLUE ● BROWN

COMPLETE WITH FACIA BOARD AND REMOVABLE INSERT IN LID FOR FRAME AERIAL.

PRICE **36/6** ONLY

We can supply components for making 4-valve Superhet to fit the above case and a circuit diagram and full instructions available at 2/- each.

PRICE OF COMPLETE KIT

6 1/2 GNS.

All components can be purchased separately.



ENGRAVED KNOBS

1 1/2in. diameter for 4in. spindles, available Cream or Brown as follows: "Focus," "Contrast," "Brilliance," "Brightness," "Brilliance On/Off," "Wavechange," "On/Off," "Tuning," "Volume," "S.M.L. Gram," "Tone," "Vol. On/Off," "Radio-Grain," "Bass," "Treble," "Record-Play." Also Plain Knobs to match. 1/6 each.

LOUDSPEAKER UNITS


Plessey 6in. Round type for personal portables, 2 to 3 ohms	13/9
Elac 5 1/2in. Square type 2009, 2 to 3 ohms	13/6
Elac 4in. Square type 4/62, 2 to 3 ohms	13/9
Elac 5in. Round type 5/61, 2 to 3 ohms	13/6
Goodmans 5in. Round type	14/9
Plessey 6in. Latest type	13/6
Goodmans 6in. Round type	15/11
Leetrona 6 1/2in. With transformer	18/-
Plessey 6 1/2in. Round type, 2 to 3 ohms	14/11
Elac 6 1/2in. Type 6/19, 2 to 3 ohms	15/6
Truvox 6 1/2in. Wafer, only 1 1/2in. deep, 2 to 3 ohms R. & A. 8in. Lightweight, 2 to 3 ohms	20/-
Plessey 6 1/2in. Mains energized	18/11
Plessey 8in. Mains energized	17/6
Plessey 8in. Mains energized	21/-
Leetrona 8in. PM 2 to 3 ohms	16/6
Elac 8in. PM 2 to 3 ohms	17/6
Elac 10in. 1 1/2in. 2 to 3 ohms	22/6
Plessey 10in. Lightweight	19/6
Truvox BC11 12in. Lightweight	49/6

CABLES, WIRE, Etc., Etc.

Push Back Wire 7/0076 size. Colours available: Blue, Yellow, White, Blue, Green . . . all 2d. per yd.
Twin Ribbon Feeder 2002 . . . 8d. per yd.
Screened Microphone Cable with outer cover of P.V.C. 7/0076 . . . 1/- per yd.
Flex Mains Type: Twin 14/0076, P.V.C. covered 3d. per yd.
Screened Cables:
Single Type . . . 6d. per yd.
Twin Core . . . 7d. per yd.
Three Core . . . 9d. per yd.

FOR TERMS SEE OUR FULL PAGE ADVERT ON PAGE 487

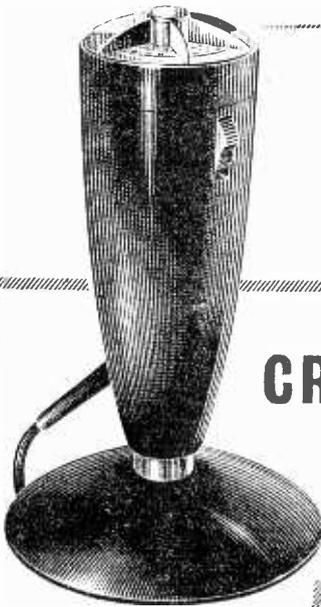ALPHA RADIO SUPPLY CO.
5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.



Another Fine

ACOS

CRYSTAL MICROPHONE...



**Desk
Stand
or Hand**

**MIC 36
SERIES**

MODEL Nos.

Microphone without switch and with table stand - - - **MIC 36 3**
 Microphone with switch and table stand - - - **MIC 36 4**
 Microphone without switch and with floor stand adaptor - - **MIC 36 5**
 Microphone with switch and floor stand adaptor - - **MIC 36 6**

All models are suitable for hand use.

SPECIFICATION

always well ahead

This new ACOS microphone has all the signs of being a "winner". It is a very handsome instrument — and its performance matches its looks. The die-cast microphone insert has a high sensitivity with a pick-up field that may be considered as omni-directional. Alternative models, with or without switch are available with suitable adaptors for floor or table stands.

Output level: - 55 db. ref. 1 volt dyn/cm².

Nominal capacity: 10-20mf.

Omni-directional frequency response: Substantially flat from 30-7,000 c/s.

Recommended load resistance: Not less than 1 megohm dependent on the low frequency response required.

Retail Price in Gt. Britain

Models without switch	-	-	-	£3-3
Models with switch	-	-	-	£3-8

Acos crystal devices are protected by patents, patent applications and registered designs in Gt. Britain and abroad.

COSMOCORD LIMITED • ENFIELD • MIDDLESEX

Practical Wireless

EVERY MONTH
VOL. XXX, No. 574, AUGUST, 1951

Editor: F. J. CANN

22nd YEAR
OF ISSUE

COMMENTS OF THE MONTH

By THE EDITOR

The Interference Problem

IN the early days of radio there were many complaints of interference caused by re-radiation from receiving aerials. In those days when it was necessary to turn the reaction knob to its fullest extent in order to build up signals radiated from low-power transmitters, because of the comparative inefficiency of valves and deficiency in design, the BBC frequently broadcast advice on how to avoid it. Complaints were very general. To-day, the trouble is all but vanished so far as radio sets are concerned.

Now owners of TV sets complain of interference from electrical apparatus, including radio sets, forgetful of the fact that TV can and does undoubtedly cause interference with radio reception. The complaints are widespread and TV owners are pressing for the compulsory suppression of all electrical apparatus likely to cause interference. Suppressors cost a comparatively small sum. Soon there will be an outcry on the part of owners of radio receivers pressing owners of TV sets also to fit suppressors. It is a point when they voice their own grievances in this respect that they often overlook.

RADIO SHOW ARRANGEMENTS

SIR MILES THOMAS will open the National Radio Show, at Earls Court, on August 25th. It will remain open until September 4th. For the first time it will include a demonstration by the BBC of outside TV broadcasts as well as studio broadcasts on sound and TV. This year the Royal Navy rejoins the Army and the Royal Air Force in the Services Section and radio controlled models will be among the electronic sideshows.

TV programmes from seven different sources—six of them within the exhibition—will be seen continuously on the screens of several hundred domestic receivers, and cameras used will include the small industrial types and the "roving eye," which is a self-contained camera and transmitting unit, making it free of cable connections.

BBC STATISTICS

EVEN statistics can be interesting, as Doctor Kinsey has proved! Figures recently issued by the BBC are certainly so, but it would be wrong to draw false conclusions from them. Statistics may indicate a trend, but not an irrevocable trend. Sign posts, it was once said, often

point both ways. We are referring to the drop in listening reported by the BBC, who draw the conclusion that it is due to the competition of television. Not entirely so, in our view. It would appear that those on the sound side of radio have given up what they consider to be an unequal struggle with the new medium and the sound programmes suffer in quality as a result. To-day, indeed, some of the main programmes merely consist of a series of silly, childish party games, such as "Twenty Questions," "Round Britain Quiz" and "What's It All About." There are far too many programmes of this sort, which do not require a great deal of effort or brains in their creation and production. Sound programmes have definitely deteriorated. The BBC should remember that it still draws most of its revenue from the largest percentage of its customers—the listeners. It would appear to us that some fresh blood is required in the BBC on the production and programme planning side.

It is unfortunate perhaps for viewers that many of the TV programmes are based on the same old sound radio formula. "Down You Go," for example, underestimates the intelligence of viewers. The viewing public has not yet grown critical and is hypnotised by the marvels of the new entertainment medium, as in sound broadcasting; listeners were blinded by the scientific miracle of radio and would listen to any set which could squawk even though the sounds were unintelligible. Our programmes in toto are not bad but they are in need of great improvement. If it were not so the question of alternative commercial programmes would not arise.

"THE PRACTICAL MOTORIST AND MOTOR CYCLIST"

WE are pleased to be able to announce that we have overcome some of our production difficulties which prevented us from meeting the almost unprecedented demand for our new companion journal, *The Practical Motorist and Motor Cyclist*. Number three is now on sale, and greatly increased supplies are available. Many readers of this journal also read our companion journals and they will welcome this news. Even so, to avoid disappointment we do urge all readers to place a regular order with their news-agent to ensure delivery of future issues.—F.J.C.

ROUND the WORLD of WIRELESS

Radio for Police Squads

IT is reported that Birmingham police are to fit radio communication equipment to the machines of their motor-cycle squads.

New Ediswan Representative

MR. J. O. WILSON has joined the Edison Swan Electric Co. Ltd. as representative to Southampton district office.

Mr. Wilson was formerly representative attached to the Domestic Appliance Division of the English Electric Co. Ltd. He also spent fourteen years with Kennedys, (Bournemouth) Ltd., electrical wholesalers, attaining the position of assistant manager, Southampton branch.

During the war Mr. Wilson served for seven years in the Royal Artillery and reached the rank of staff captain.

"Clearadio"

ONE of the features of this year's National Radio show will be a demonstration of "Clearadio," the BBC's V.H.F. system designed

to provide interference-free reception.

Visitors to the show will be invited to listen to programmes broadcast over the present medium wave and then by the very high frequencies and judge for themselves the difference in sound.

Broadcast Receiving Licences

THE following statement shows the approximate number of licences issued during the year ended April, 1954. The grand total of sound and television licences was 13,455,061.

Region	Number
London Postal	1,628,177
Home Counties	1,442,147
Midland	1,243,694
North Eastern	1,621,831
North Western	1,261,933
South Western	1,010,350
Wales and Border Counties	628,921
Total England and Wales	8,837,053
Scotland	1,093,561
Northern Ireland	223,609
Grand Total	10,154,223

New Research Building

MR. R. L. SMITH-ROSE, C.B.E., director of the Radio Research Station at Ditton Park, Langley, Bucks, recently turned over the first spadeful of soil on the site for a new building which will take an estimated £250,000 to £300,000 to build.

It has been designed by Mr. H. A. Snow, senior architect at the Ministry of Works, and will replace the wooden huts that have so far housed the equipment used by the research workers. When the building is completed in about two years, time the staff of 100 will be increased to 300 and the work of the station expanded a great deal.

East African Link

AT an overall cost of approximately £100,000 or so, an important addition to the communications system of East Africa was recently made with the completion of a V.H.F. multi-channel radio link between Nakuru in Kenya and Jinja in Uganda, affording an immediate increase of 12 channels to the four already available between Nairobi and Kampala, with provision for 12 more in 1955 and another 12—36 in all—when traffic demands justify their introduction. Stand-by equipment allows for 36 alternative speech circuits to be automatically available in the event of breakdown or deterioration of those in use.

Pleasure Cruise for Dealers

A PARTY of 127 people sailed from Tilbury on Saturday, May 22, in the liner *Arcadia* on the start of the Philips Mediterranean cruise. A number of dealers decided to pay for a passage for their wives so that they could accompany the party, the dealers invited being those who had made the most outstanding contribution to the Philips crusade to put radio sets and record-playing equipment "back on the map." First port of call was Ceuta in Spanish Morocco, then Naples and finally Barcelona on May 30. A farewell party was held towards the close of the return journey.



Hattie Jacques, Max Bygraves, Adele Dixon and Spike Milligan are seen recording another edition of "Paradise Street," a weekly comedy series broadcast in the Light Programme.

I.P.R.E. Yorkshire Section

A YORKSHIRE Section of Incorporated Practical Radio Engineers was inaugurated at the Midland Hotel, Bradford, on June 9.

S. Gordon Bromby was elected chairman, with a supporting committee consisting of Messrs. R. N. Balmforth, A. Booth, A. R. D. Hall, F. Wade and R. P. B. Williams. The address of the local secretary, P. A. Senior, is 5, Calverley Moor Avenue, Thornbury, Bradford 3. Including members, 159 engineers and traders were present at the film lecture given for Mullard Ltd. by C. H. Gardner, who is a vice-president of the I.P.R.E. This followed the business of the meeting.

Direction-finding Equipment

THE equipment division of Mullard Ltd. recently installed a Mullard "Discovery" direction-finding set on the world's largest cable ship, H.M.T.S. *Monarch*. The *Monarch*, one of four cable ships for which Mullard have contracts to supply direction-finders, operates in any part of the world.

She will soon be employed on the arduous task of laying part of the transatlantic repeater telephone cable.

Anniversary of Pioneer

JUNE 18, 1954, marked the sixtieth birthday of a famous personality of the Danish Press — Mr. George W. Olesen, editor-in-chief and publisher of the monthly magazine *Radio Ekko*. He has been an amateur radio operator since 1914 and served as a ship's wireless operator in his younger days.

Mr. Olesen founded the *Radio Ekko* seventeen years ago and under his editorial guidance the paper still remains the only Scandinavian radio magazine known and read in all continents of the world. His sixtieth birthday coincides with his thirtieth anniversary as an editor-in-chief, for he headed the weekly journal *Radio-Uge-Revue* in 1924, when his wireless articles soon began to gain popularity.

Syrian Contract

MARCONI'S Wireless Telegraph Co. Ltd., and International Aeradio Ltd. have together secured a substantial contract for radio communication and direction-finding equipment from the Ministry of Defence of the Republic of Syria.

This contract entails the planning and engineering of a complete radio communications network, which is to include automatic and manual

V.H.F. direction-finding stations (both mobile and static), with associated V.H.F. ground and air communications facilities. A training school for personnel of the Syrian Air Force is also to be provided.

Radio Show

THE National Radio Show will be opened at Earls Court, London, on August 25 by Sir Miles Thomas, chairman of the British Overseas Airways Corporation, and will remain open to the public until September 4.

Hotel Wireless Licences

UNDER the Wireless Telegraphy Act, 1949, of which Section One came into force on June 1, it is still necessary for hotels and boarding-houses to have broadcast receiving licences.


A normal licence covers the use of a set in the public rooms of the hotel and private rooms of the proprietor, but each permanent guest or boarder with his own private receiver must take out his own licence. There is also a new comprehensive type of licence which is taken out by the proprietor to cover his own sets and all private sets owned by his guests or boarders.

R.S.G.B. Exhibition

THE Council of the Radio Society of Great Britain have approved the plans for the eighth R.S.G.B. Amateur Radio Exhibition to be held on November 24th to 27th at the Royal Hotel, Woburn Place, London.

P. A. Thorogood, M.A.S.E.E., G4KD, general manager of the Electrical Engineers' Exhibition, has agreed to be exhibition manager

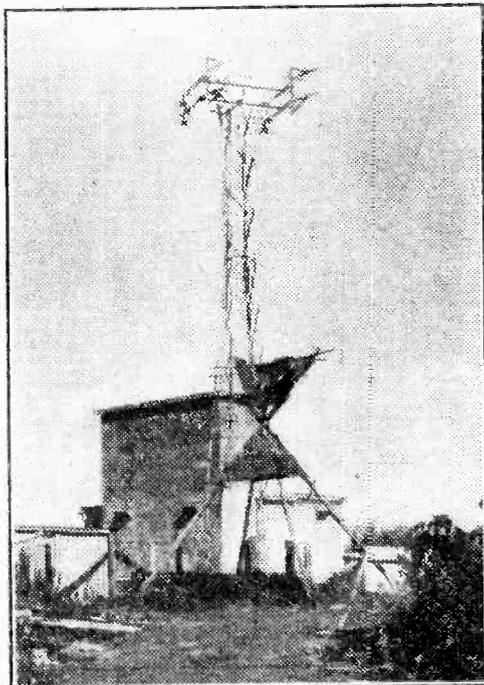for the eighth exhibition. Mr. Thorogood is a past member of R.S.G.B. Council and is an active amateur on 145 Mcs. and 70 cms.



Repeater station and yagi aerials on Loldiani Mountain, 10,000ft. above sea level. Duplicate 36-channel V.H.F. multi-channel radio-telephone link was recently completed. (See paragraph opposite.)

Obituary


WE regret to record the death on Monday, April 26, of Mr. P. Moseley, managing director of Osmor Radio Products, Ltd., South Croydon, Surrey, at the age of 32.

He was a keen radio enthusiast and controlled his business of the manufacture of coils, coil assemblies and radio components since 1947.

"Blackpool Night"

FOR consecutive Wednesday evenings during the summer months Light Programme listeners will again hear "Blackpool Night."

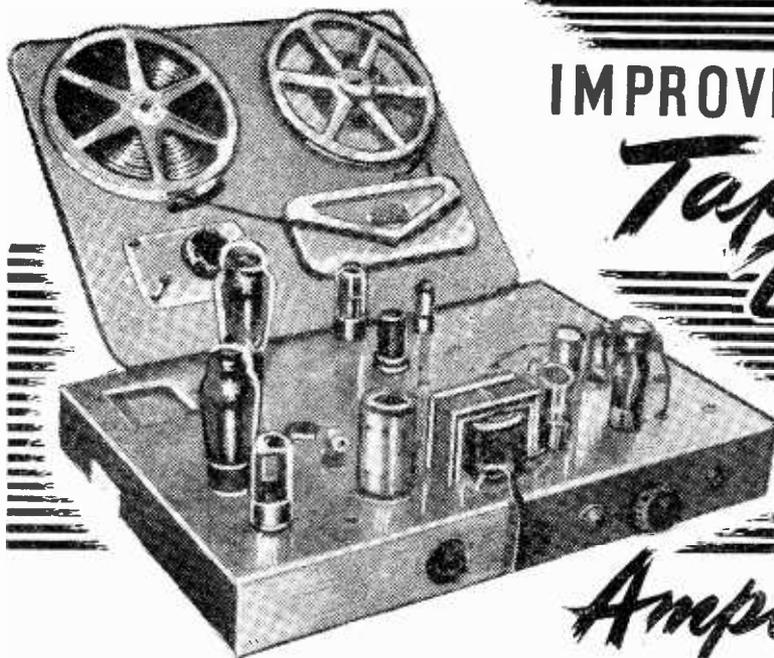The cream of the country's variety talent is attracted to the theatres of Blackpool to entertain the thousands of holidaymakers that flock there each week. Many of these top artistes will be heard in the series.



IMPROVING THE *Tape Deck* *Amplifier*

COMPARED with the original Wright and Weaire tape deck around which the associated electronic equipment was designed, the new tape deck is such that it is worth while to see what can be done to improve the original amplifier performance. Not only has the deck been improved, but since 1952 much experience has been gained in the manufacture of magnetic tape which, among other things, has resulted in a higher signal-to-noise ratio: combining the two enables the writer to put forward an improved specification.

The new record/playback and erase heads were investigated and it was found that for the same minimum distortion level the bias volts across the recording head could be reduced. Referring to page 460, this means that R53 should now be increased to 300 ohms. Many queries have been received on how to measure the bias and erase volts, so that it will be a good thing to say here that with the equipment to be found in the average constructor's workshop it will not be possible to get an accurate measurement; what is possible, provided that the meter used has a sufficiently high impedance, is a comparative reading. As a guide—and it must be reiterated that it is a guide only—the reading given on a Pullin 10,000 ohms per volt meter was 20 volts measured from R53 to chassis. Since the original specification was published, two of the components used in the bias and erase oscillator are no longer on the market, and the opportunity is taken to replace these with components that are freely available. No change in the general design was found necessary, the require-

ments of good waveform, stability and ample output for erase being already there, so that the only changes required are the replacement of the original centre-tapped oscillator coil by the Osmor type QT8, and the replacement of the original H.F. choke by either the

Wright and Weaire type 666, or two Osmor type QC1 connected in series. As shown in the drawing, if using the Wright and Weaire type 666 a 500 pF condenser should be connected in parallel. On technical grounds the W. & W. coil is to be preferred as it can be tuned to give rejection of the oscillator volts on the H.T. line, but where no test equipment exists it is better to use the two Osmor type QC1.

Frequency Response

A consideration of the first frequency response characteristic suggests that not only should the higher frequencies be extended and maintained, but that to keep a proper balance the bass response should be extended and maintained too, so that the new specification now runs $\pm 3/\text{DB}30\text{-}9,000$ cycles/sec., with

MODIFICATIONS AND AN ALTERNATIVE BIAS AND ERASE OSCILLATOR ARRANGEMENT

By C. L. White, Assoc. Brit. I.R.E.

RECORDING AMPLIFIER

Layout identical with original.

Parts List Changes :

C4 = 0.05 μF .

C7 = 0.05 μF .

R8 = 2.2 K Ω .

VC1 = 100 K Ω .

C41 = 50 μF 12-volt wkg. } optional (see text).

R29 = 100K.

a drop of not less than 12DB at 12 kc/s. Two further modifications were included, in that it was found that there was a 4db loss at 9 kc/s at the output terminal marked "Output to quality amplifier" when used with approximately 5ft. of coaxial, and there was a variation of frequency response of H.F. during recording depending on the position of VC1 amounting to ± 3 db. Checking on the recording amplifier it will be seen that VC1 is a 500,000-ohm potentiometer. Using so high a resistance as this will keep the gain of the stage at maximum, but will result in a loss at high frequencies when the arm is otherwise than at maximum. The simplest way out of the difficulty is to allow for the slightly reduced gain and use a potentiometer of approximately one-fifth the original value, making it 100,000 ohms. Now that the top response is to be extended, the small changes in the equalisation that are needed can be incorporated in such a way that the small loss of gain occasioned by the use of a 100 K potentiometer for VC1 can be made up. These changes are tabulated on page 458.


Modifications

Coming now to the playback amplifier, the first modification is the correction of the fixed potentiometer "Output to quality amplifier." The correction consists of "bridging" the feed resistance R38 by a

condenser C39, and a series resistance R54 whose values are 30 pF and 660 K. This will compensate for up to 8ft. of coaxial cable. This, of course, does not correct for changes caused by the variation of VC2 when using the integral amplifier, but generally these can be neglected. C22 and C26 are now disconnected and removed, and altering the value of R28 to 500 ohms completes the changes as far as the H.F. response is concerned, excepting that the feedback is also to be increased which will make the changes more effective. In order to maintain the bass response and extend it to 30 cycles per second, it will be necessary to increase the gain of the playback amplifier V5 and V6. This is done by changing R35 to 220 K Ω , R36 to 1.2 M Ω , fitting a decoupling condenser C37 0.25 μ F and decoupling condenser C38 50 μ F and increasing the H.T. line volts to 300.

Though some critics will doubt whether the cost of increasing the bandwidth of a reproducing system from the 60-8 kc/s to the new one of 30 cps-12 kc/s is worth while, to those who have heard the modified amplifiers there is no possible doubt. As some indication of the subjective tests that the new equipment has come through with 100 per cent. marks is that of re-recording the special Audiophile records which on playback are indistinguishable from the original.

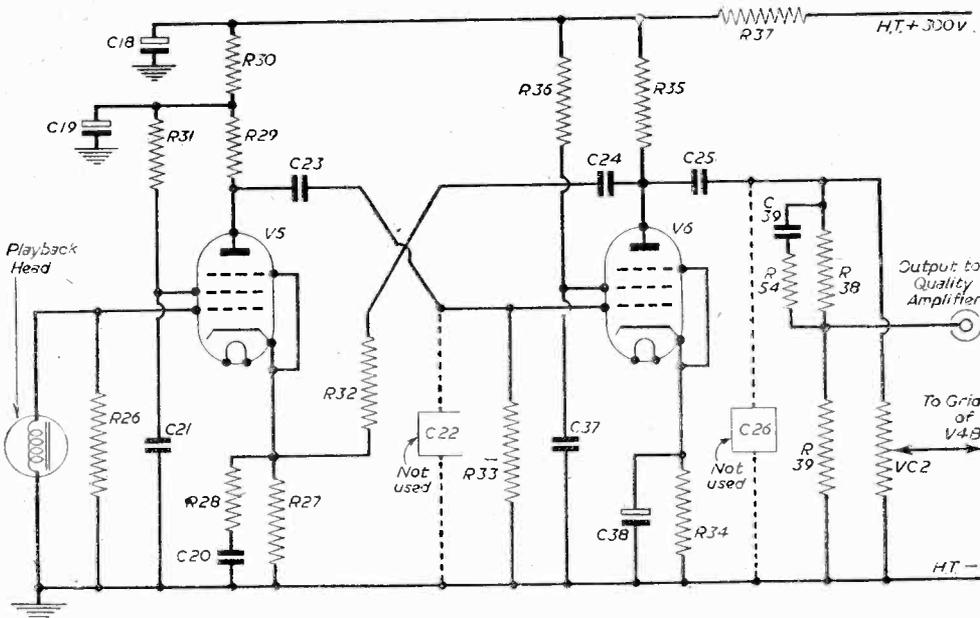The final frequency response characteristic is




PLAYBACK AMPLIFIER

R26 = 1.5M Ω .	R34 = 1.5 K Ω .	VC2 = 500 K Ω .	C24 = 0.001 μ F.
R27 = 2.2 K Ω .	*R35 = 220 K Ω .	V5 = EF40.	C25 = 0.25 μ F.
*R28 = 500 Ω .	*R36 = 1.2 M Ω .	C18 = 16 μ F elect.	*C26 = Not Used.
R29 = 220 K Ω .	R37 = 50 K Ω .	C19 = 16 μ F "	V6 = EF40 or EF37.
R30 = 27 K Ω .	R38 = 470 K Ω .	C20 = 0.01 μ F.	*C37 = 0.25 μ F.
R31 = 1.2 M Ω .	R39 = 47 K Ω .	C21 = 0.25 μ F.	*C38 = 50 μ F elect (6v.) wkg.
R32 = 120 K Ω .	*R54 = 660 K Ω .	*C22 = Not Used.	*C39 = 30 pF.
R33 = 1 M Ω .		C23 = 0.25 μ F.	

* Indicates components where a change has taken place.

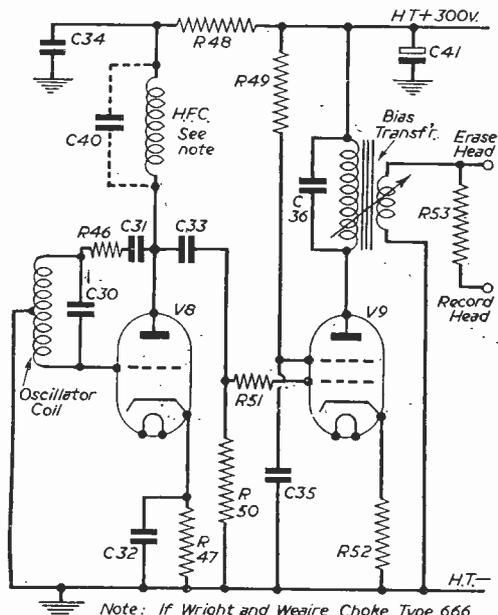tabulated below. It will be found a very close fit to the specification.



Note: If Wright and Weaire Choke Type 666 is used C40 must be connected as shown

SUPERSONIC BIAS SUPPLY

- | | |
|---|------------------------|
| *Oscillator Coil, Osmor Type Q18. | R46 = 1.0 K Ω . |
| *H.F. Choke, either 2 Osmor type QCl or | R47 = 4.7 K Ω . |
| *1 Wright and Weaire type 666. | R48 = 25 K Ω . |
| C30 = 0.005 μ F. | R49 = 4.7 K Ω . |
| C31 = 0.001 μ F. | R50 = 250 K Ω . |
| C32 = 0.1 μ F. | R51 = 1.0 K Ω . |
| C33 = 0.001 μ F. | R52 = 270 Ω . |
| C34 = 0.1 μ F. | *R53 = 300 Ω . |
| C35 = 0.1 μ F. | |
| C36 = 0.005 μ F. | |
| *C40 = 0.0005 μ F. | |
- I Wright and Weaire Bias Transformer type 579.
- * Indicates components where a change has taken place.

30 cps	= 17.0 db.
40 cps	= 18.0 db.
60 cps	= 19.0 db.
100 cps	= 19.0 db.
250 cps	= 19.0 db.
1,000 cps	= 19.0 db.
4,500 cps	= 21.0 db.
7,000 cps	= 20.0 db.
8,000 cps	= 18.0 db.
9,000 cps	= 15.0 db.
10,000 cps	= 11.0 db.
11,500 cps	= 8.0 db.

There is one further modification, which can be considered as optional, in that it is only required when insensitive microphones are used. It is that the gain of the recording amplifier may be increased by changing the value of R2 to 100 K Ω and connecting a decoupling condenser C41 (50 μ F) from the cathode of V1 to earth.

International Sound Recording Congress

THE Société des Radioélectriciens, in conjunction with important French broadcasting, cinema, acoustical and television groups, recently organised a conference at which all sound recording processes could be discussed, as well as the use of these same techniques for the recording and storage of "information" in comparatively new fields, such as magnetic recording of images, memory devices, electronic calculators, computing and statistical machines, automatic telephony devices, and so on.

The Congress, which lasted a week, was held at the Maison de la Chimie, in the rue Saint-Dominique, Paris, and over 600 delegates from 22 countries, including the U.S.S.R. and Czechoslovakia, attended, with, of course, the largest contingent from France herself. The British delegates included Dr. O. K. Kolb (British Acoustic Films), A. J. Forty (British Post Office), M. M. Freeland (Radio Malaya, Singapore), C. M. Phillips and J. A. Clark, of S.R.D.E. and the Acoustics Group, Hants, D. W. Aldous (British Sound Recording Association), Dr P. E. Axon and H. J. Houlgate (BBC), A. Tutchings, R.R.E., Malvern, D. G. Jaquess (Decca), H. A. Thomson (Kelvin & Hughes, Glasgow), and Prof. D. Gabor (Imperial College of Science).

An exhibition of the latest sound recording and reproducing equipment was a popular feature of the proceedings, to which the public were admitted for 150 francs (about 3s.) and given the opportunity of making personal voice recordings and hearing the playback.

About 50 exhibitors and distributors took space, but only two British firms were represented—Gramphon Reproducers, Ltd., Feltham, Middlesex, and Truvox, Ltd., of Harrow, Middlesex, with Mr. Robert Bradford, of the former company, in attendance. The display on his stand of the modified BBC pattern negative feedback disc cutter-head, developed with the Reeves Equipment Corporation of New York, and the associated 40VA and 60VA output feedback amplifiers, attracted much interest, as did the Truvox Mark III Tape Deck.

Five Sections

The Conference proper was divided into five sections: (a) history, communication and methods of measurement; (b) magnetic recording; (c) photographic recording; (d) mechanical recording; and (e) applications and their extension into the realm of information storage.

As over 60 papers were given in four days, meetings were running simultaneously and the British visitors split up to cover these diverse sessions and subjects, ranging from studies of "wow" and flutter to an artificial variable delay line using magnetic tape designed as an analogue correlator to a survey of the fascinating *musique concrete*, in which an analysis of the form of music and the examination of its transient and spectral constitution leading to its application in objective music was discussed.

In the exhibition all forms of magnetic tape and wire recorders were displayed and demonstrated, with some good examples of American design (notably the Ampex models).


D. W. ALDCUS.

Stabilised Power Supplies

SOME THEORETICAL NOTES
AND CONSTRUCTIONAL
DETAILS

By E. N. J. Marguerit

THERE is always a controversy in the amateur world as to whether one should have a stabilised power unit in the "den" or have each piece of equipment fitted with its own power supply. The answer seems to be that a highly stable and ripple-free source of power is desirable, as it enables one to use it for supplying the necessary power to a new piece of circuitry while it is being tried and experimented upon. When the design, possibly suitably modified, has been found satisfactory, it can be fitted into the equipment it was designed for and its own unstabilised supply built for it. It does,

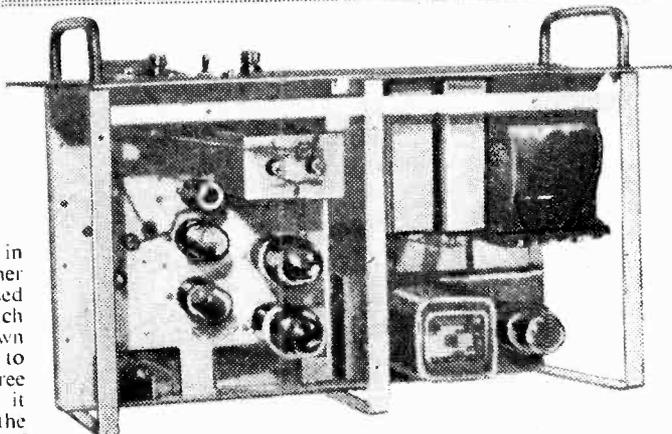

Whichever system is used in a simple power unit there is an inherent disadvantage in both, that they have poor regulation. That means that the output current is a function of the output voltage. If we plot output current against output voltage we obtain a curve as shown in Fig. 1.

As the current taken from the power supply increases its voltage drops. Another consideration, of course, is that if the mains voltage feeding the system fluctuates, the output follows these fluctuations fairly faithfully.

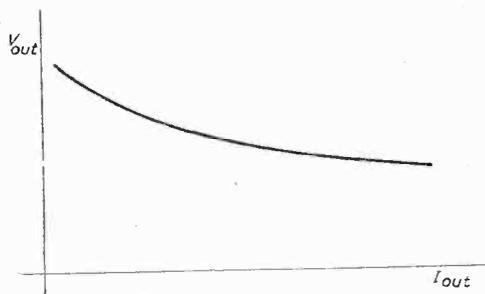


Fig. 1.—Plotting current against voltage.

therefore, seem that a stabilised power supply is a necessity for any serious experiments in the field of electronics.

Power Supplies

In this article this heading embraces any device that will convert an alternating potential into a direct potential. The main component for this purpose is the rectifier. Rectifiers can take the following forms:

1. Metal rectifiers.
2. Cold cathode rectifiers.
3. Thermionic rectifiers:
 - (a) Hard vacuum;
 - (b) Gas filled.

All these can be used in half-wave or full-wave circuits. Half-wave rectifier circuits are perhaps cheaper to build, but have the disadvantage of requiring large values of smoothing capacitors.

Methods of Improving the Regulation

1. A choke-input filter can be used after the rectifier to obtain a better regulation. However, the output voltage in this case will not be as high as with a capacitor input filter. This means that if a high output voltage is required, using a choke-input filter circuit, a fairly large mains transformer will be needed. Fig. 2 shows the two types of circuit with some typical figures to illustrate the above.

2. Another method of improving the regulation is to use a voltage regulator tube across the smoothed output of the rectifier.

Those gas-filled tubes such as the VR75, VR105, VR150, 90C1, 85A2 and many others have the

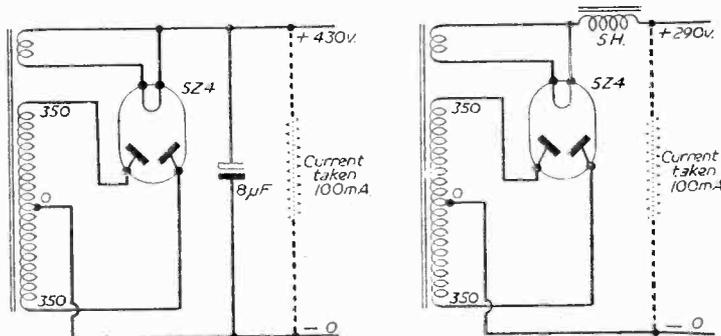


Fig. 2.—Capacitor and choke-filter circuits.

property of maintaining, within limits, a constant voltage across them.

In Fig. 3 a potential E_1 is connected in series with R_1 and the regulator tube. The potential E_2 , which is the burning voltage of the tube, is also the output of the system. E_1 must be large compared to E_2 for good regulation.

To calculate the value of R_1 in Fig. 3 one must remember that two currents flow through it: one is the current through the tube needed in order to maintain the ionisation of the gas, the other is the current taken by the outside source fed by the neon.

Let I_1 be the current required to maintain ionisation. This current varies from 1 to 5 milliamperes according to types, and let I_2 be the current required by the outside load, then if E_1 and E_2 have the meaning of Fig. 3,

$$R_1 = \frac{E_1 - E_2}{I_1 + I_2}$$

The output current obtainable from these tubes is in the region of 10 to 40 milliamperes.

If we plot the burning potential (E_2) against output current we get a graph as shown in Fig. 4.

For example, the regulation of a VR150 from minimum to maximum current is 5.5 volts.

3. The third method is to use an electronic circuit to compensate for variations in the output due either to fluctuations in the mains supply or to varying loads.

Electronically Stabilised Power Supplies

Theoretical Considerations

If the output voltage is to vary, due to the causes mentioned earlier, use is made of the control characteristic of a triode to compensate for that variation.

Consider the circuit of Fig. 5 where the tube T_1 is connected in series with a potential E_{in} , obtained from a suitable rectifier-smoothing arrangement. The output voltage appears between the cathode of T_1 and the negative line. The grid of this tube, known as the series valve, is connected via R to a source of negative voltage with respect to the cathode. Consider also a load resistor R_L connected across the output. Now, if the grid of T_1 is very negative with

respect to the cathode, so much so that T_1 is cut off and, therefore, passes no current, no current will flow through R_L . But as the bias is gradually

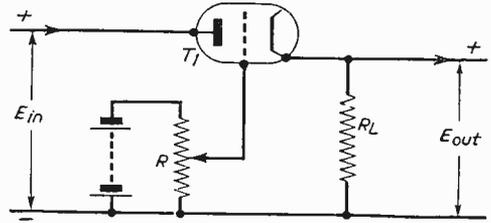


Fig. 5.—Using a triode to control output.

decreased (i.e., the grid becoming more positive with respect to the cathode) the valve will pass more and more current and this current must flow through R_L . In other words T_1 is used as an electronic resistance.

Consider now Fig. 6, similar to Fig. 5, but R_L is now variable. Suppose that R is at some position which determines a certain value of bias for T_1 . We have seen above that this value of bias will allow a certain current to flow through T_1 and R_L . Keeping R fixed, we now vary the value of R_L . Let us decrease R_L in an effort to increase the current through it, but as T_1 has a fixed bias it cannot pass that higher current, hence to obey Ohm's Law E_2 must necessarily fall. Therefore, if we wish to pass the higher current through R_L we must decrease the bias on T_1 by altering the setting of R . It now seems obvious that if we had an electronic means of altering the bias on T_1 for varying load currents we would have solved our problem.

This is conveniently achieved by using a D.C. amplifier. The type of D.C. amplifier used for this purpose is known as a difference amplifier.

In the above discussion we have assumed that E_1 is always constant, but we know that in practice this is not so as it depends primarily on the mains voltage. It is proposed now to consider the action of the regulator as E_1 varies.

Referring to Fig. 6, suppose that a fixed potential E_2 is required, and that a current $\frac{E_2}{R_L}$ should flow

through R_L . To do this R must be adjusted so that T_1 has the required bias to pass that current. Imagine now that E_1 increases due to an increase in the mains voltage; E_2 will also rise, but as E_2 increases the bias on T_1 will also increase, therefore allowing T_1 to pass less current, but R_L is fixed, therefore the increased potential E_1 will bring E_2 down to almost its original value. Hence the regulator will automatically compensate for mains voltage fluctuations.

Difference Amplifiers

By definition a difference amplifier is a two input device which will amplify the voltage difference existing across its inputs.

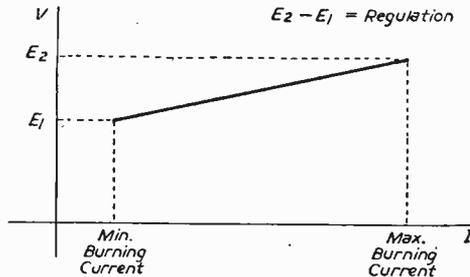


Fig. 4.—Plotting burning potential against output current.

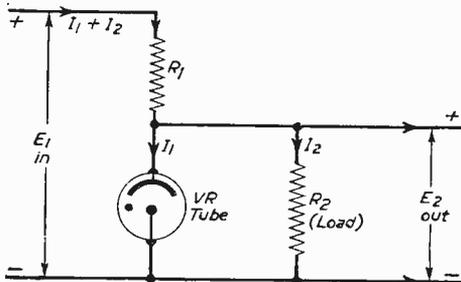


Fig. 3.—A voltage regulator tube and associated circuit.

Consider the circuit of Fig. 7 where T is a triode having an anode load R_L . If the cathode is held at a steady potential E_2 , from a low-impedance source, and the grid connected to a potential E_1 varying within small limits, then the circuit will amplify the difference of voltage ($E_2 - E_1$). This output will be developed across R_L .

Another form of D.C. amplifier is shown in Fig. 8. Here two triodes or a double triode are used with their two cathodes connected to a common resistor

The anode of T2 is fed from E out via a resistor R_L across which is developed the bias for T1. The grid of T1 is returned to the anode of T2.

It is clear from this diagram that T2 is connected as a difference amplifier, its inputs being E_1 , which is fixed and known as the reference voltage, and E_2 .

To explain the behaviour of the circuit let us assume that E out rises. This increase in output voltage will increase E_2 , thereby decreasing the bias of T2, because the value of E_2 approaches that of E_1 . This will make T2 more conductive and the anode voltage will fall. Consequently the voltage across R_L increases. But this voltage is the bias of T1, and if its bias increases so does its resistance. This fall compensates for the tendency of E out to rise.

Mathematical analysis of this type of circuit shows that to obtain satisfactory results it is essential that T1 has a high amplification factor and T2 a high value of mutual conductance.

Practical application of this circuit would make use of a beam tetrode for T1 such as a 6V6, 6L6, 6Y6, 12E1, etc., and a high gm pentode for T2 such as a 6SJ7, 6SH7, etc.

A circuit utilising the second type of D.C. amplifier is shown in Fig. 10. The behaviour is the same as that explained for the circuit of Fig. 9.

The type of double triodes normally used with this circuit are 6SL7 and 12AX7.

(To be continued.)

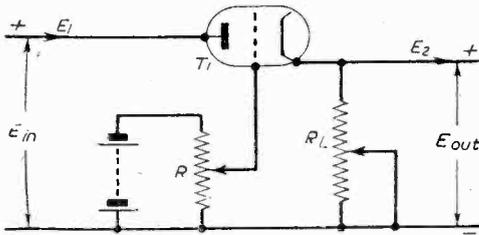


Fig. 6.—In this modification of Fig. 5, R_L is made variable.

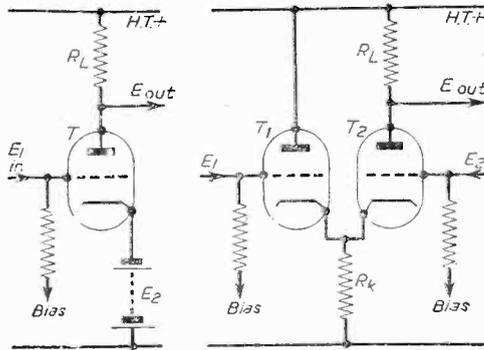


Fig. 7.—A simple triode circuit.

Fig. 8.—An alternative triode circuit using a double triode.

R_k . The inputs E_1 and E_2 are applied to the grids. Suppose that E_2 is fixed and E_1 varies, then the amplified difference will appear across R_L of T2. It is essential that the D.C. amplifier used to regulate a power supply has a high gain, and as the gain of a triode amplifying stage depends on the amplification factor of the triode and on the value of the anode load, it is necessary that a high μ triode be used and that R_L be large.

We shall now see how a D.C. amplifier can be used to regulate or stabilise a power supply.

Consider the circuit of Fig. 9 where T1 is the series valve and T2 the simple form of difference amplifier shown in Fig. 7. T3 is a voltage regulator, i.e., a low-impedance source, fed from the H.T. line through R_3 . This maintains the cathode of T2 at a steady potential E_1 . R_1 and R_2 are connected in series across the output in such a way that the potential at the junction of the two resistors with respect to the negative line is smaller than E_1 by an amount which determines the bias of T2. Let this potential be E_2 .

The expression for E_2 is

$$E_2 = E_{out} \times \frac{R_2}{R_1 + R_2}$$

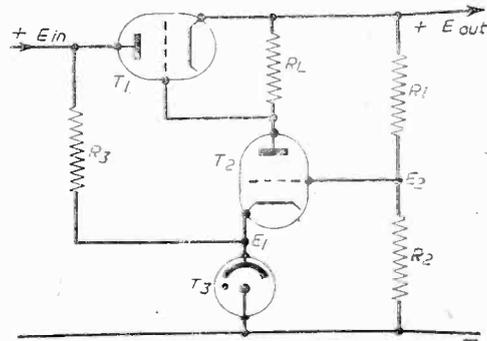


Fig. 9.—Simple difference amplifier.

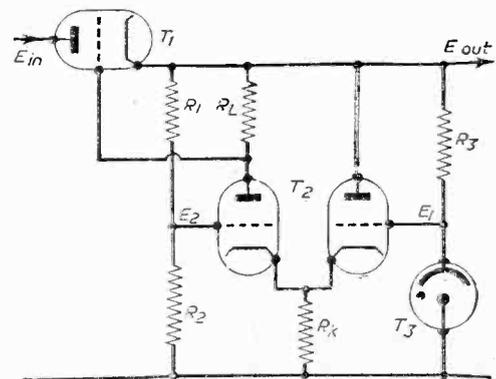


Fig. 10.—A D.C. amplifier circuit.

the curves of (a) the unit's output voltage against current, and (b) the variation of valve filament current with applied voltage. Where these graphs intersect, will give the operating condition for any selected number of valves. The form in which they appear is shown in Fig. 3.

The following figures were not taken from any particular unit. They represent an average case, but it should be stated that in many miniature battery-eliminators where the transformer core is small and therefore nearer saturation, conditions may be even worse. Let the five valve filaments be operating at, say, 1.25 volts and drawing .23 amps. from the power supply. When one fails, the current drain falls to .21 amps; there will be a decreased voltage drop across the smoothing choke and a rise in output volts due to transformer regulation. In fact, the filaments have now to run with an L.T. potential of 1.7 volts. This is dangerously high. With the 20 ohm choke, matters are worse, the voltage rising from 1.25 to 1.8 volts in similar circumstances. If the set is not switched off immediately, such an increase may cause the next weakest filament to go and the remaining valves are receiving over two volts. It has been known for an unattended parallel fed receiver, operating from a standard commercial mains unit, to burn out all four valves in ten minutes of silent destruction.

In a pure series arrangement, if one filament fails, the rest are open circuited and immune from damage. A more usual practice is to shunt some, or all of them, with resistors, so that filaments low in the chain shall not have to carry the anode and screen currents of those higher up. In such cases the effect of a burn-out will depend on the position of the valve and the values of the associated shunts. As it is readily possible, using the series circuit, to give adequate protection to the remaining valves after a filament failure, this method is preferable.

H.T. Supplies

Another hazard which these valves are expected to endure is that of having heater and anode voltages

applied simultaneously. It is assumed that the fine, directly-heated element will warm up and be

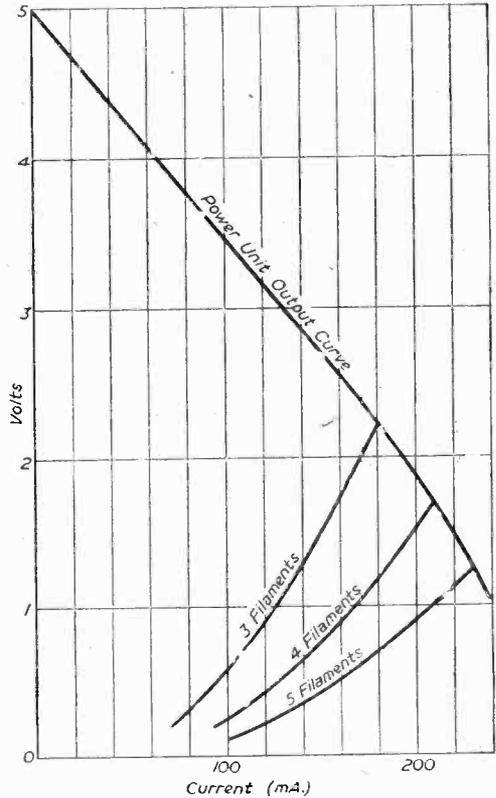


Fig. 3.—Setting out a graph plotting volts and current for various valve combinations.

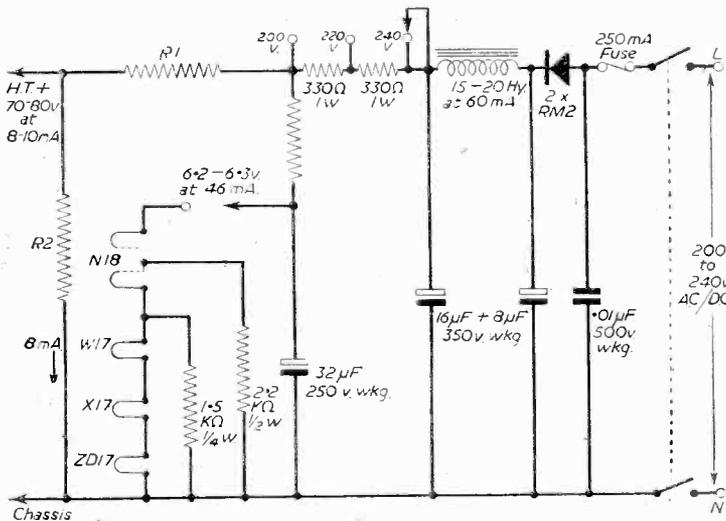


Fig. 2.—The series-fed filament arrangement.

ready to emit instantaneously, but this, of course, is not the case. A time interval of between one-fifth and one-third of a second may be involved.

When batteries are used, due to their relatively good regulation, no serious harm is done, but with a mains unit incorporating metal rectifiers, the valves may have to warm up in the presence of an H.T. voltage greatly in excess of their rated maximum (90 volts). This is particularly true of the series-fed arrangement in Fig. 2. Unless the divider network (R1 and R2) allows a drain at least as great as the total valve H.T. current, then a voltage of 150 volts or more will appear when switching on, or after a filament casualty.

It is emphasised that the

variations in H.T. voltage which occur under the conditions mentioned are unlikely in themselves to cause immediate failure. They are merely recurring instances of misuse and their elimination can add materially to the emissive life of the valves.

Surges

Heater current surges are common in receivers with series arrangements, and these are due entirely to the resistance/temperature characteristic of the wire elements. In the case of tungsten, the ratio of resistance hot to resistance cold is of the order five to one. This represents a serious problem where the greater part of the chain consists of valve heaters as opposed to voltage dropping resistors. The nickel-aluminium alloy used in these particular battery valves has a ratio of about four to one. This is still in itself sufficient to invite a substantial surge, though the valve heaters normally represent only a small fraction of the chain.

A convenient method of overcoming the problem is to insert a surge limiter, known commercially as a Brimistor or Thermistor, in series with the heaters. These devices have an inverse resistance/temperature characteristic and are quite suitable where the H.T. rectifier is a valve and forms part of the chain. To use this type of rectifier in a small, portable receiver, would inevitably add to the heat and size problems; for this reason the metal rectifier is preferred, and surge limiters are omitted.

Also, when switching on series heater chains in A.C./D.C. mains sets, it is often noticeable that one of the valves invariably warms up first. Its filament may glow very brightly in one spot for a brief period before the chain settles down, though normally its robust nature makes it capable of standing the strain. Such a phenomenon can be caused by close coiling in a spirally-wound heater, or by local thinning of material where the wire is welded to its connecting strip inside the valve. This may also occur in battery valves, but will not be readily visible and, in view of the relatively delicate nature of the heater strip, prevention is a wise move.

The battery/mains set designer is thus presented with a difficult situation. A "Brimistor" may protect the heaters from sudden mechanical expansion due to the heating effect of current surges, but it will also prolong the period during which the barium oxide coating may be forced to emit before it is up to an even temperature. In addition, the H.T. voltage may temporarily reach a very high level.

Undoubtedly, the ideal solution is to hold off the H.T. supply while the heaters warm up slowly, but to do this involves extra expense which often cannot be tolerated.

Other switching surges involving the charging and discharging of condensers are more likely to damage the rectifiers and condensers themselves than harm the valves.

(To be continued.)

New Wireless Transmitting Licence Regulations

THE Wireless Telegraph (General Licence charges) Regulations 1954—Statutory Instrument 1954 No. 439, published by the Stationery Office, price 6d.—have now been laid before Parliament and give the charges for the main licences other than those for broadcast sound and television receivers.

These regulations, which came into operation on the 1st June, 1954, describe the fees and the scope of all the major licences. The fees of these licences have now been assessed so that the revenue obtained from each type of licence will cover the costs incurred in connection with that licence.

The following are the most important changes involved:

(a) The Amateur (Sound) Licence allows amateurs to work their stations anywhere in the United Kingdom. Originally they required special Alternative Address or Portable Licences for this purpose. Hitherto the power at which newly licensed amateurs could operate was lower than that allowed to established amateurs; this distinction has now been abolished, as has the different charges varying with the power used. An Amateur (Sound) Licence will cost £2 a year.

(b) A new licence, the Amateur (Sound Mobile) Licence, has been introduced which, for the first time, allows amateurs to operate from a moving vehicle. This licence will be available only to holders of an Amateur (Sound) Licence and will cost £1 a year.

(c) The annual royalty of the Amateur (Television) Licence has been reduced from £3 to £2.

(d) Radio controlled models become subject to

licensing for the first time. The licence fee of £1 will cover a period of 5 years.

(e) The annual royalty for the Business Radio Licence, originally £5 per licence plus £5 for each station covered by the licence, is now reduced to £3 for each station. The name of the licence is changed to the Private Mobile Radio Licence.


(f) All Radio Beacon Licences now cost £1 for five years. This is a reduction for Aeronautical Beacon Licences which at present cost £1 a year.

(g) Firms who require licences for testing and developing radio equipment will no longer be issued with Experimental Licences but will be given a Testing and Development Licence. If their tests are conducted exclusively under suppressed radiation conditions they will be given a licence costing £1 for five years; if it is necessary for them to radiate, the licence fee will be £2 a year.

(h) Wireless schools and technical institutes paid 10s. a year for their licences and an additional 10s. a year if they used radar. Under the new Training Establishment Licence they will pay £2 for five years; this licence will include the use of radar for training purposes.

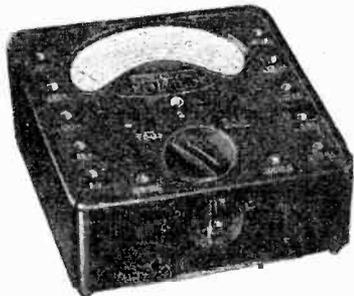(i) The annual fee for ship licences is now £2 whether the ship is compulsorily fitted with radio or voluntarily fitted. This fee includes a charge for receiving broadcast (but not television) programmes, but does not include the cost of inspecting the equipment. The inspection charge, hitherto included in the licence fee for a ship voluntarily fitted with wireless, will be separately chargeable.

(j) The fee for aircraft licences is increased from 5s. to £1 a year. The new licence covers the reception of broadcast programmes.



'AVO' Precision ELECTRICAL TESTING INSTRUMENTS

Registered Trade Mark

A dependably accurate instrument for testing and fault location is indispensable to the amateur who builds or services his own set.

The UNIVERSAL AVOMINOR

(as illustrated) is a highly accurate moving-coil instrument, conveniently compact, for measuring A.C. and D.C. voltage, D.C. current, and also resistance: 22 ranges of readings on a 3-inch scale. Total resistance 200,000 ohms.

Size: 4 1/2 ins. x 3 1/2 ins. x 1 1/2 ins.
Net weight: 18 ozs.

Complete with leads, interchangeable prods and crocodile clips, and instruction book.

Price: £10 : 10 : 0

The D.C. AVOMINOR

is a 2 1/2-inch moving coil meter providing 14 ranges of readings of D.C. voltage, current and resistance up to 600 volts, 120 milliamps, and 3 megohms respectively. Total resistance 100,000 ohms.

Size: 4 1/2 ins. x 3 1/2 ins. x 1 1/2 ins.
Net weight: 12 ozs.

Complete as above
Price: £5 : 5 : 0

D.C. Voltage
0-75 millivolts
0-5 volts
0-25 "
0-100 "
0-250 "
0-500 "

A.C. Voltage
0-25 volts
0-100 "
0-250 "
0-500 "

D.C. Current
0-2.5 milliamps
0-5 "
0-25 "
0-100 "
0-500 "

Resistance
0-20,000 ohms
0-100,000 "
0-500,000 "
0-2 megohms
0-5 "
0-10 "

GUARANTEE: The registered Trade Mark "Avo" is in itself a guarantee of high accuracy and superiority of design and craftsmanship. Every new AvoMinor is guaranteed by the Manufacturers against the remote possibility of defective materials or workmanship.

Sole Proprietors and Manufacturers —

AUTOMATIC COIL WINDER & ELECTRICAL EQUIPMENT CO., LTD.
Winder House, Douglas Street, London, S.W.1.

Phone: VICTORIA 3404-9




Pointers for Designers

AND CONSTRUCTORS NUMBER ELEVEN

VALVES FOR TAPE RECORDERS

INPUT STAGE Z729


(low noise pentode)

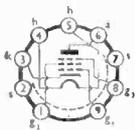

V_h 6.3V
 I_h 0.2A
 V_a 250V
 V_{g2} 140V
 g_m 1.85m/AV
 V_{hum} 1.5V
 $R_{g1-k} = 470\Omega$
Base B9A


Tone correction and intermediate stages B309

(double triode)

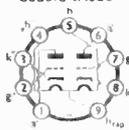


V_h 6.3V
 I_h 0.6A
 V_a 250V
 g_m 5.5 mA/V
 r_a 10 kΩ
Base B9A

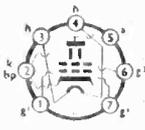Output and bias oscillator N727/6AQ5 or N78



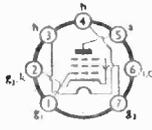
V_h 6.3V
 I_h 0.45A
 V_a 250V
 V_{g2} 250V
 I_k 50 mA
 V_{g1} -12.5V
 P_{out} 4.5W
Base B7G



V_h 6.3V
 I_h 0.64A
 V_a 250V
 V_{g2} 250V
 I_k 40 mA
 V_{g1} -5V
 P_{out} 4W
Base B7G

Rectifier U709

(full-wave rectifier)

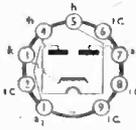

V_h 6.3V
 I_h 0.95A
 V_{h-k} 450V (max.)
 V_{in} 350 rms (max.)
 I_{out} 150 mA
Base B9A
The heater-cathode rating of the U709 permits operation from a common 6.3V heater winding

For further information and full technical data write to: The Osram Valve and Electronics Dept.
THE GENERAL ELECTRIC CO. LTD., MAGNET HOUSE, KINGSWAY, LONDON, W.C.2

S.R.S.



**THE "SUPEREX"
BATTERY PORTABLE
4 VALVE SUPERHET
L-M WAVE**

A really magnificent portable receiver which you can easily build in time for your holiday or week-end runs in the country. Very handsome design and soundly constructed in every respect. Covered in two contrasting colours of the latest high quality I.C.I. Plastic Skin, which is very hard wearing and damp resisting. The receiver is a 4 Valve Superhet, which ensures the best performance. No trouble has been spared to ensure that this receiver will be equal to any of the ready-made models selling at around £20.

All brand new components. Valves, Chassis, Resistors, Condensers, etc., etc. Cabinet size 10 1/2 in. long by 8 1/2 in. high by 5 in. deep, available in various colours.

Complete Building Cost Approx. £7.15.0

Send for "Superex Construction Booklet," which gives complete assembly instructions with theoretical and practical diagrams, Price 1/6. This is credited, if components are purchased later.

TERMS.—Cash with order or C.O.D. Extra charge for C.O.D. Please add postage.

OPEN.—9 a.m. to 6 p.m. Monday to Saturday; 1 p.m. Thursday.

SUPERIOR RADIO SUPPLIES
37, HILLSIDE, STONEBRIDGE, N.W.10.
Phone: ELGAR 3644

- T/V TECHNOLOGY
- RADIO ENGINEERING
- ELECTRONICS
- RADIO SERVICING



There's a big future in T/V and Radio. Act now! Increase your knowledge. Back up experience with a sound theoretical background. I.C.S. offer courses of instruction in—

**T/V TECHNOLOGY
ADVANCED SHORT-WAVE RADIO
RADIO ENGINEERING
RADIO SERVICE ENGINEERING
RADAR**

ELEMENTARY ELECTRONICS
I.C.S. will also coach you for the following examinations:—

B.I.R.E.; P.M.G. Certificate for Wireless Operators; Radio Servicing Certificate (R.T.E.B.); C. & G. Telecommunications, etc., etc.

DON'T DELAY—WRITE TO-DAY for free descriptive booklet, stating which subject or examination interests you. Fees include all books needed. Examination students coached until successful.

Dept. 170E, I.C.S., 71, Kingsway, W.C.2.

INTERNATIONAL CORRESPONDENCE SCHOOLS,
(Dept. 170E), International Buildings, Kingsway,
London, W.C.2.

I am interested in your special Summer Term Offer.

Subject

Name..... Age.....

(Block letters, please)

Address



The Complete Home Entertainer

THE 'Editor'



SUITCASE TAPE RECORDER
Easy to carry—easy to look at. Operating height only just over 5 inches. The "EDITOR" is the smallest, mains-operated fully automatic portable tape recorder with 7 in. spools on the market. Finest value and quality at only

45 GNS COMPLETE WITH MICROPHONE & 1200' TAPE

SPECIFICATION

* Mullard miniature valves * Twin track heads * Three high-grade specially designed motors * Independent Bass and Treble Controls for recording and playback * Overall negative feedback * Amplifier may be used independently for very high quality record reproduction and public address * High fidelity Record head * Provision for external speaker * Speaker muting switch * 4 watts output—brilliant reproduction * Positive servo braking on all functions * Size only 16 1/2 in. x 12 in. x 5 in. (without li.) * Radiogram and microphone inputs * For 200-250 v. A.C. mains * Automatic Erasure.

TWO SPEEDS 7 1/2 IPS & 3 1/2 IPS 2 Hours Recording.

HIRE PURCHASE & CREDIT SALE TERMS

H.P. TERMS: £15/15/- Deposit, 12 monthly instalments of 60/- or 18 instalments of 42/-.

CREDIT SALE TERMS
Send only £6 to secure with 8 further monthly payments of £6.

E & G MAIL ORDER SUPPLY The Radio Centre
33 Tottenham Court Road, London, W.1. Tel. MUS 6667

SOUTHERN RADIO'S WIRELESS BARGAINS

TELESONIC 4-Valve Battery Portable. Complete with Hivac Valves. In Metal Carrying Case. Simply converted to Personal Portable. £2 including Conversion Sheet.
TRANSMITTER-RECEIVERS. Type "18" Mark III. COMPRISING SUPERHET RECEIVER and TRANSMITTER. TWO UNITS CONTAINED IN METAL CARRYING CASE. Complete. 8-Valves. BARGAIN CLEARANCE OF REMAINING STOCK, £4/10/0.

RECEIVERS TYPE "109." 8-VALVES WITH VIBRATOR PACK FOR 6-volts BUILT-IN SPEAKER. 1.8 to 8.5m/cs. Contained in Metal Case. Perfect. 100 ONLY, £5. Bargain Clearance of Remaining Stock.

BOMBSIGHT COMPUTERS. Ex-R.A.F. New. Contains Gyro Motors. Rev. Counters, Gear Wheels, etc., etc. Ideal for Model Makers, etc., £3/5/0, plus 10/- carriage.

CRYSTAL MONITORS. Type 2. New in Transit Case. Less Crystals, 8/- each.

LUFBRA HOLE CUTTERS. ADJUSTABLE 1/2 in. to 3 1/2 in. For Metal, Wood, Plastic, etc., 6/6.

RESISTANCES. 100 Assorted. Useful Values, Wire end, 12/6 per 100.

CONDENSERS. 100 Assorted. Mica, Metal Tub, etc., 15/- 100.

PLASTIC CASES. 14 in. by 10 1/2 in. Transparent, Ideal for Maps, Photos, Display, etc., 5/6.

STAR IDENTIFIERS. Type 1 A-N. Covers both Hemispheres. In Case, 5/6.

CONTACTOR TIME SWITCHES. Complete in Sound Proof Case. 2 Impulses per sec. Thermostatic Control, 11/6.

REMOTE CONTACTORS for use with above, 7/6.

MORSE TAPPERS. Standard Type ex-Govt., 3/6. Heavy Duty Type "D", 8/6. COMPLETE MORSE PRACTICE SET with BUZZER, 6/6.

DIMMER CONTROLS. Bakelite. Wire Wound. New, 1/3 each.

MAGNETIC RELAYS SWITCH. Bakelite. 5 c/723. 2/6 each.

METERS AND AIRCRAFT INSTRUMENTS. Only need adjustment or with broken cases. TWELVE INSTRUMENTS (including 3 brand New Aircraft Instruments), 35/- for TWELVE ITEMS.

Full List of RADIO BOOKS, 2/6.

SOUTHERN RADIO SUPPLY LTD.,
11, LITTLE NEWPORT STREET, LONDON, W.C.2
GERrard 6653.

The Beginner's Guide to RADIO



The Sixteenth Article of a Series Explaining the Fundamentals of Radio Transmission and Reception. This Month the Transformer, the Output Valve, and Speaker are Dealt With, With Notes on How to Read a Circuit Diagram

By F. J. CANN

I HAVE already dealt briefly in earlier articles with the transformer explaining why it is used and what is meant by transformation ratio. An explanation of how it is made will help the reader to understand its function. The action of a transformer differs from that of a resistance. The simplest transformer consists of two coils of insulated wire wound round an iron rod and the coils may be wound either side by side or one over the other. When a fluctuating current is passed through one of the coils (the primary) a difference of pressure (voltage or potential) arises between one and the other. Also, the current passing through one coil induces a current in the other coil.

Now, if each coil has the same number of turns, then the difference in voltage between the ends of the second coil will be the same as that between the ends of the first. Similarly, if the second coil has more turns than the first, then the voltage produced will be greater than that across the first coil.

This is where the usefulness of a transformer becomes apparent. It enables the voltage to be stepped up any desired amount (1 am, of course, referring to alternating current; it is impossible to step up direct current). Thus, if the second coil has twice the number of turns as the first, then the voltage across the second will be twice as much as the first, and if the second coil has three times as many turns the voltage will be three times as great as the first. A transformer can be wound to give any desired transformation ratio. This ratio is selected according to the characteristics of the valve it is to "feed." If the transformation ratio is too high, distortion will occur. Generally, a low-frequency transformer coupled to the output valve has a ratio varying between $3\frac{1}{2}$ to 1 and 6 to 1. The output valve selected must, of course, be "matched" to the loudspeaker. It would, for example, be wrong to use a transformer and output valve giving an output of, say, 3 watts undistorted, in connection with a loudspeaker which would overload at less than this.

Transformers used in wireless sets are not made on the simple lines just described for purposes of illustration. It would indeed be very inefficient. Wireless transformers have soft iron cores, not in the form of a rod, but in the form of thin plates. These plates interleave as will be seen in Fig. 71 so that they provide a rectangle with a bar connecting two of the sides. A well-known material for these cores is Stalloy, and it is available already stamped in various sizes. It will be seen that this extends right round the outside of the coils as well as passing

through the middle of them. The coils are, of course, very carefully insulated from one another, and are nearly always wound on the same bobbin. First, the primary winding is wound on then a layer of wax paper or insulating material such as Empire tape and, finally, the secondary winding is put on.

The power valve acts in exactly the same way as the previous valve, small variations of current at the grid giving large variations in the plate current.

The amplifying property of the valve itself added to the step-up effect of the transformer causes the total amplification to be considerable.

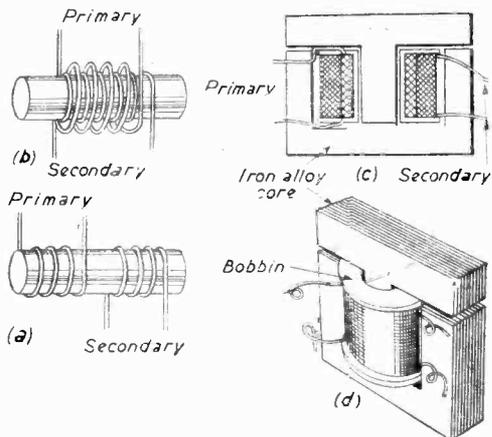


Fig. 71.—The essential parts of a simple transformer are shown at a and b; c and d illustrate the actual form of a transformer used in a wireless set.

At this stage we may connect up the loudspeaker. It is connected in the plate circuit of the output or power valve. That is to say, between the plate and the positive end of the high-tension supply.

In order to understand the working of the loudspeaker I will deal with the very simplest type, one consisting of a vibrating reed, not used nowadays. It consists of a permanent magnet, a strip of flexible iron known as the reed, a coil of fine insulated wire and a cone attached to the reed by a small metal rod. The coil is wound on a small bobbin which fits over one end of the magnet, while the reed, which is of a springy nature, is screwed to the other end of the

magnet. Its action is as follows : the current from the plate of the power valve passes through the coil ; this tends to increase the power of the magnet, for it is a well-known fact that if an electric current is passed through a coil of wire wound round a piece of iron the iron will become magnetised—in other words an electro-magnet or solenoid. In the case of the speaker, however, the iron is already magnetised. In other words, it is a permanent magnet. The current passing through the coil, therefore, increases the magnetism. We have already seen that when music or speech or any other sound is being received this current fluctuates in harmony or *syntony* with the sound vibrations of the instruments being played and this means that the magnetism produced by the current will also fluctuate, thus causing the reed to vibrate and communicate the sounds to the cone.


Whatever type of speaker is used (and there are several types) this principle applies.

Reading a Circuit

In the early part of this series, I illustrated a very simple circuit with diagrams showing the theoretical circuit and the wiring diagram, numbering the parts to correspond. As the circuit made use of very simple components, such as a home-made coil and a triode detector valve, which is scarcely ever used to-day, I think it advisable, now that the reader has become accustomed to more modern components, to illustrate a modern three-valve circuit in theoretical and practical form, with each component numbered to correspond. This circuit does not make use of triodes but employs two pentodes and a tetrode valve. The pentode valve, of course, gives much greater amplification.

(To be continued)

Fig. 72.—(Bottom right) Theoretical circuit of a modern three-valve receiver. (Above) Top and underneath views of a receiver built to the circuit showing position of wires. The numbers on the circuit correspond to the numbers on the wiring diagrams.

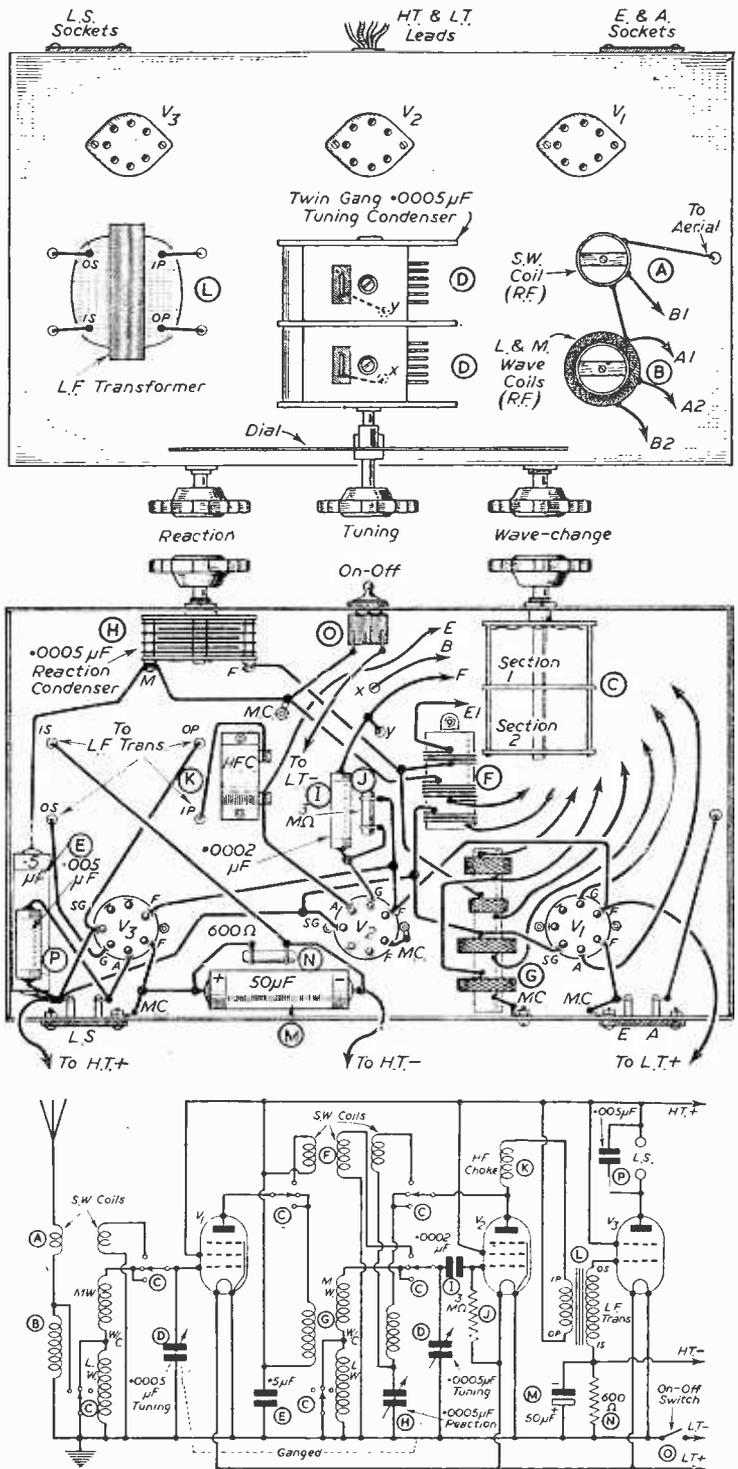

On Your Wavelength

BY THERMION

Ionospheric Conditions

ONE of the major studies at the Radio Research Station, Slough, continues to be into ionospheric "weather" and its effect on long-distance radio communication. Data on local ionospheric conditions are supplied to the station from its own observatories in various parts of the world and from those maintained by other countries. This information is used in the preparation of forecasts six months ahead of transmission conditions for the users of high-frequency radio communications.

A recent development has been the construction of special "British Zone" charts which forecast conditions for circuits terminating in the British Isles. It is hoped that these local charts will give more accurate forecasts than the general charts previously used.

The station is also using a method of investigating ionospheric conditions by studying long-distance back-scatter (that is, "echoes") from the earth's surface of high power pulses transmitted from the observation point. Sharply beamed aerial systems directed along fixed azimuths and capable of operating over a wide frequency band are used for this purpose. A rotating beamed aerial system of restricted frequency coverage has also been developed for use with a Plan Position Indicator display. Propagation conditions within a circular area of 5,000 km. radius from the observation point are shown on the P.P.I. as the aerial rotates. In addition a camera is arranged to take one photograph at each revolution of the aerial. By projecting the developed film at a greatly increased speed a vivid picture is obtained of ionospheric changes within 5,000 km. of Slough.

Radio Navigational Aids

THE study of phase changes in low-frequency ground waves, as they pass over geological boundaries or from a path over land to a path over water, is important for those types of radio aids for marine and air navigation which are based on the reception of low-frequency signals from fixed transmitters. The new system of phase measurements which employs an ultra-high frequency radio link to convey a phase-reference signal has been completed and proved satisfactory in use.

Germanium Diodes

THE work of the station on germanium diodes includes the examination of the current voltage temperature characteristics and noise spectra of point-contact and junction diodes together with related theoretical studies.

The Guitar Again

I HAVE received a number of letters concerning my paragraph on the guitar, in answer to a comment in an obscure little pamphlet which masquerades as an official journal. I was invited to comment by the editor of this precious publication, but he does not like my comments. He labelled all electrified instruments as tin pan alley trash. Sorry I cannot accept him as an authority on music. Having studied my Groves, I have a better understanding of what comprises a musical instrument than he does. I have no doubt that members of the Classic Guitar Association are a little peeved at the competition from these modern instruments, not having yet realised the revolution in public taste especially in music and musical instruments which has taken place in the past 30 years.

Another letter on the topic comes from the editor of *B.M.G.*, the oldest established journal dealing with fretted instruments. He is in full agreement with my comments. He points out that there are three kinds of guitars—spanish guitar (strung with gut or nylon and played with the fingers); plectrum guitar (strung with wire and played with a plectrum) and Hawaiian guitar (strung with wire and played with finger picks). He comments: "The Editor of the journal you have mentioned considers neither of the latter should be called a 'guitar.' If his instrument were the violin, I suppose the hill-billy player of this instrument would be told to find another name for the stringed instrument he 'debases.'"

Another correspondent, R. L. Williams, of Craven Arms, Salop, congratulates me on the "obscure paragraph" I wrote on the subject, and having so labelled it by the rest of his letter shows that he completely understood it. He acknowledges the "far-reaching influence" of my page, not a bad admission from one who admits that he cannot understand what I write. However, I am sorry to have caused this rift in the guitar.

Important Work of the Clubs

THERE are some radio clubs with very full memberships which operate as little friendly gatherings of keen amateurs, meeting once a week in a private room at the local or in a school room loaned by a friendly schoolmaster. Some of the latter encourage their scholars to join, and in such cases the handicraft room and its equipment are placed at the disposal of members. There are much larger clubs run on advanced lines which perform valuable experimental work, and one of these is the Leicester Radio Society, which between the night of the 4th of May and the morning of the 5th assisted G3CCA to make the first all-transistor contact without the aid of any thermionic valves whatsoever. That station made contact with G6PO in Buckingham, a distance of 45 miles.

Noisy Reception

DETAILS OF THE VARIOUS CAUSES OF NOISE AND HOW TO MEASURE SIGNAL/NOISE RATIO

By F. E. Apps

IN this article I am dealing with the noise actually created in the receiver and not with noise received by it. All radio receivers generate a certain amount of noise and this noise will increase as the amplification of the receiver is increased. Now as weak signals require high amplification, it necessarily follows that reduction of this noise becomes more difficult as the sensitivity of the receiver is increased.

All of the probable causes of noise in a radio receiver can be minimised if not entirely eliminated. The types of noise can be stated to be as follows :

- (i) Shot effect.
- (ii) Thermal agitation.
- (iii) Microphonics.
- (iv) Hum.
- (v) Imperfect contacts, dry joints, etc.

Shot Effect

This noise is generated entirely by the valves in a receiver. It is due to the fact that the stream of electrons from cathode to anode is not absolutely steady (ignoring, of course, the effect of the other electrodes). The electrons do not leave the cathode at the same velocity and consequently the electron current is spasmodic. This causes a minute current of irregular value to be superimposed on the main anode current of the valve, thus setting up in the anode circuit a superimposed minute voltage. This is then amplified throughout the receiver to the output stage. This noise from shot effect will appear on the whole of the frequency bands of the receiver.

It will be found that in a valve that has very little space charge the shot effect is very pronounced, so that to keep this effect as low as possible various valves should be tried. If not successful in reducing it this way reduction of the voltages on the electrodes and the reduction of cathode temperature will often effect it. The reduction of cathode temperature can, of course, be effected by reducing the heater voltage slightly.

Thermal Agitation

As can be seen by its title, this noise is caused mainly by temperature changes. The reason for this is as follows : when a current flows through a conductor it consists of a flow of free electrons. Now these free electrons are in random motion with velocities that depend upon the temperature of the conductor. These random motions of the free electrons cause minute variations of current that produce a fluctuating voltage between the ends of the conductor. If this noise is developed across a resistor in the input stage of the receiver it will, of course, be amplified with the signal and passed with it to the output stage. It will be seen, therefore, that to keep this noise within limits, and keep a reasonable signal/noise ratio, it is necessary to see that resistors are of good make and of correct wattage and to see that good joints are made at soldered points. Components should also be as far apart as space will allow so as to keep

temperature down. The effect upon thermal noise will be seen in the formula

$$E = \sqrt{4KTR\Delta f}$$

where E=RMS noise voltage.

K=Boltzmann's constant.

T=Absolute temperature.

R=Resistance in ohms.

f=Frequency.

$K=1.37 \times 10^{-28}$ joules per degree absolute T in degrees Kelvin.

Microphonics

This type of noise is caused by the mechanical vibration of the elements in the valve or valves. It may be due to vibration of the chassis, the valve-holder or the valve itself, and is caused by sound waves from the speaker. It can also be caused by long leads (especially in the oscillator circuit) vibrating. Some types of valve are more subject to this fault than others, those most liable being the second detector, usually a double diode triode, and the frequency changer. Apart from using other valves, precautions should be taken either to mount the chassis, or gang, or valve holders on rubber. Long leads in frequency changer circuits should be avoided, and care taken to ensure valves are protected from acoustical vibrations from the speaker by enclosing them in cans.

Bad Contacts, Dry Joints, etc.

The noise that these faults can produce is obvious. Amongst bad contacts the following are very necessary to check. Bad contact in valve sockets ; bad welding inside valves ; bad tracks or poor contact in gain controls ; loose laminations of mains transformer or chokes ; loose filaments in dial lamps ; weak springs in mains switch causing intermittent contact ; poor aerial and earth contacts ; dirt in vanes of gang condenser.

Signal/Noise Ratio

Reference has been made in this article to signal/noise ratio. A brief description of how this is taken follows.

The receiver to be checked should be in a place where little outside electrical interference is likely to affect it. A screened box in which the receiver could be placed would be ideal. The receiver should be tuned to the highest frequency on the scale (i.e., minimum gang) and all controls at maximum. Using a reliable signal generator which will give a modulated and an unmodulated signal, tune to the frequency of the receiver. Now reduce the output of generator until the output from the receiver shows 1 milliwatt on output meter. Now replace milliwatt output meter with a microwatt output meter and switch off modulation from generator. The reading on the microwatt meter will now show residual noise. From this reading the noise level in db can be calculated.



TRANSMITTING TOPICS

WIDE-BAND COUPLERS IN THEORY AND PRACTICE

By Wm. A. Hope

THE modern trend in transmitter design is to eliminate the use of unwieldy components, especially in the intermediate stages, by using W.B.C. techniques. The purpose of this article is to explain, basically, the theory and practice of W.B.C. circuitry based on the author's experiments. For those of us who are mathematically minded, the derivation of certain formulæ will be given in the Appendices.

Basic Theory

Two circuits are said to be inductively coupled when mutual inductance exists between them. This, in turn, enables energy to be transferred from one circuit to the other by transformer action. Although the overall behaviour of coupled circuits is rather complex, we can enunciate certain conditions which will satisfy our needs, no matter what type of coupling is used.

Law A.—The effect of the secondary circuit is equivalent to an impedance of $\frac{(\omega M)^2}{Z_s}$ ohms, added in series with the primary. Z_s being the vector value of the series secondary impedance alone, M is the mutual inductance between the coils L_p and L_s and ω is the angular velocity in radians/sec. Reference should be made to Appendix A.

Law B.—The induced secondary voltage, produced by a primary current of I_p , is equal to $\omega \cdot M \cdot I_p$ volts, and is 90 deg. out of phase with I_p .

Law C.—One question which has previously cropped up in the discussion of W.B.C. principles is: "If the secondary is considered as reflecting an impedance into the primary circuit, why cannot we consider the primary as reflecting an impedance into the secondary?" The reason for this is that the impedance reflected into the primary circuit takes into account the back E.M.F. induced in the primary by the secondary current I_s . Reference to Appendix A will clarify this. We can now enunciate Law C:

The secondary current, I_s , can be considered equal to a current that would flow if the induced voltage was applied directly in series with the secondary and the primary circuit eliminated. These three simple laws will hold good for all types of coupled circuits connected with the design of the couplers, and are essential in determining the circuit conditions, as detailed later.

Circuit Calculations

A. Determine the primary current, I_p , by means of Law A.

B. Knowing I_p , calculate the induced secondary voltage by means of Law B.

C. Once the induced secondary voltage has been found, calculate the secondary current, I_s , using Law C. The formulæ given below are used in direct calculation of the circuit constants and are valuable in assessing the limits of the W.B.C.

$$\frac{\text{Reflected secondary impedance to primary circuit } (\omega M)^2}{Z_s} \dots \dots \dots \text{Eqn. 1}$$

$$\text{Equivalent primary impedance} = Z_p + \frac{(\omega M)^2}{Z_s} \text{ Eqn. 2}$$

$$\text{Primary current, } I_p = \frac{E}{Z_p + \frac{(\omega M)^2}{Z_s}} \dots \dots \dots \text{Eqn. 3}$$

$$\text{Secondary current, } I_s = \frac{\omega M I_p}{Z_s} = \frac{\omega M E}{Z_p Z_s + (\omega M)^2} \text{ Eqn. 4}$$

In connection with Eqn. 3, it must be remembered that there will be either a lead or lag of 90 deg., dependent on the effect of M . Z_p and Z_s are the respective vectorial values of the primary and secondary impedances. The reflected impedance

to the primary circuit, $\frac{(\omega M)^2}{Z_s}$, is a vector quantity having both resistive and reactive components, as given in Eqns. 5 and 6.

$$\text{Resistive component of reflected impedance} = \frac{R_s^2 + X_s^2}{Z_s^2} \dots \dots \dots \text{Eqn. 5}$$

$$\text{Reactive component of reflected impedance} = \frac{-X_s (\omega M)^2}{Z_s^2 + X_s^2} \dots \dots \dots \text{Eqn. 6}$$

R_s and X_s being the two components of the secondary impedance, a positive reactance being inductive. If the value of M is small, or the value of Z_s large, the reflected impedance to the primary is small. Thus the primary circuitry is only slightly influenced by the presence of the coupled secondary circuitry. Conversely, if M is large and Z_s small, the reflected impedance to the primary circuit will be great, thus determining the behaviour of the primary to a very great extent.

Coefficient of Coupling (k) Factor

It is not intended to review the various types of

coupled circuits here, as the author considers that these are already well known, and to go into their respective merits would be futile. We will now proceed to examine the effect of the *k* factor between two coupled circuits. If the coefficient of coupling, *k*, between two coupled circuits is low then it follows that the secondary current, *I_s*, is small and the resultant response curve is peaked. As *k* is increased, the magnitude of *I_s* increases and the response curve begins to "flatten out." This will continue until the reflected resistance from secondary to primary, at resonance, is equal to that of the primary. At this stage the value of *k* to produce this result is critical and is termed the "critical coupling"—an important factor in W.B.C. design—and determines the maximum possible secondary current that is obtainable. If we increase the *k* factor beyond this value the current, at resonance, will become less than that at the critical coupling value, while new peaks of secondary current will appear equidistant from the point of symmetry, i.e., the resonant frequency point—the spacing between the peaks varying directly as *k*. Fig. 1 shows this phenomenon which results from the nature of the reflected impedance, produced by the resonant secondary circuit. When *k* is small, it follows that the secondary voltage and current will also be small, bearing in mind that the shape of the secondary current curve will be much sharper than the resonant response of the secondary circuit since the induced voltage is directly proportional to primary current and must, therefore, be greater in the resonant condition. If, on the other hand, *k* is large, the reflected impedance, at resonance, will be large also, thus causing a reduction in primary current, ultimately resulting in a low induced voltage, as well as secondary current. The double humps are due to the fact that, with a tuned secondary circuit, the reflected reactance into the primary circuit is inductive at frequencies less than that of resonance, while it is capacitive at frequencies above resonance.

Since the algebraic sum of the reflected reactance and the primary reactance must always be zero at any one given frequency, the effect of the secondary circuit will reduce the impedance that the primary offers to the applied voltage from the generator. This results in an

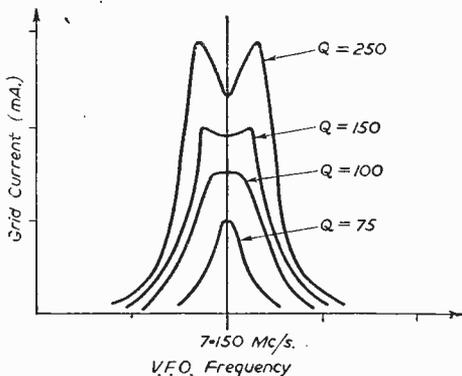
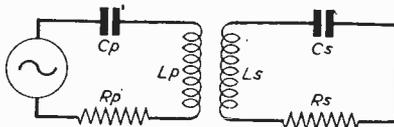


Fig. 1.—Effect of varying *Q*.

increase in *I_p* and thus will increase the induced voltage at points just off the point of resonance. It will therefore be apparent that two new resonant frequencies are introduced at such values of *k*. Thus the critical coefficient of coupling is reached when the reflected reactance, at resonance, is equal to the resistance of the primary circuit, i.e.,

$$\frac{(\omega M)^2}{R_s} = R_p$$

Therefore : $(\omega M)^2 = R_p R_s$

and, for critical coupling, $\omega M = \sqrt{R_p R_s}$Eqn. 7

Since the "Q" factor of the circuit is numerically equal to the ratio of reactance to resistance, we get :

$Q_p = \frac{\omega L_p}{R_p}$ and $Q_s = \frac{\omega L_s}{R_s}$, where *R_p* and *R_s* are the respective resistances of the primary and secondary ; and *L_p* and *L_s* are the respective primary and secondary inductances.

$$\text{Hence : } \omega M = \sqrt{\frac{\omega L_p}{Q_p} \times \frac{\omega L_s}{Q_s}}$$

Substituting $k = \frac{M}{\sqrt{L_p L_s}}$, see Appendix B.

$$\text{Critical coupling factor, } k_c = \frac{1}{\sqrt{Q_p Q_s}} \text{Eqn. 8}$$

Since the critical coupling factor is usually small, a typical value of 0.01 will result if the *Q*'s are each equal to 100.

Estimation of W.B.C. Bandwidth

We have seen from Fig. 1 that the response is virtually flat over a certain range of frequency, near that of resonance, while the response becomes steep at frequencies farther from the resonance point. This is the correct relative response for any band-pass filter ; and will, we hope, be the ultimate aim of our W.B.C. responses, when the unit is finally complete ; since uniformity, over certain frequency limits, is our theoretical aim. The bandwidth is given by the approx. value of Eqn. 9.

$$\text{Bandwidth} = k \text{ (resonant frequency of tuned circuits) Eqn. 9}$$

The author would like to indicate, at this point, that, for uniform transmission within the limits of the W.B.C., it is advisable to raise the *Q* factor of the circuits at the critical coupling point by 1.5.

(Continued on page 477.)


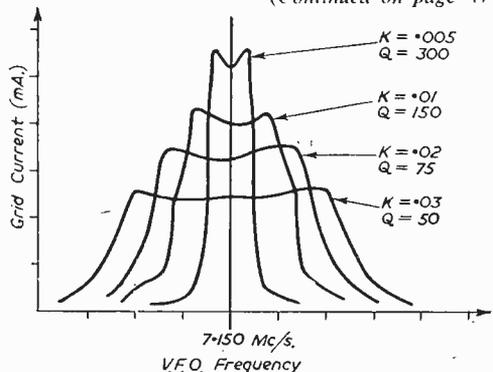


Fig. 2.—Effect of varying *K*.

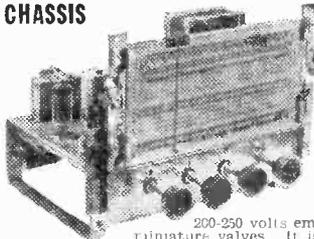A COMPLETELY ASSEMBLED "ALL-WAVE" SUPERHET CHASSIS




200-250 volts employing the very latest miniature valves. It is designed to the modern specification, great attention having been given to the quality of reproduction which gives excellent clarity of speech and music on both Gram and Radio, making it the ideal replacement Chassis for that "Old Radiogram," etc. Brief specifications—Model B3—Valve line up, 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Waveband Coverage: Short 16-56; Medium 187-556; Long 900-2,000 metres. Controls (1) Volume with on/off; (2) Tuning (flywheel type); (3) Wave change and Gram; (4) Tone (3 position switch operative on Gram and Radio). Negative Feedback is employed over the entire audio stages. Chassis size, 11in. x 7 1/2in. x 8 1/2in. high. Dial size 9 1/2in. x 4 1/2in. Price, complete and READY FOR USE excluding speaker, £12 12/- (Carr. and Pkg. 7/6 extra.) Or H.P. Terms £14 4/- Dep. 12 Months at 15%.

MODEL B3 P.P.—This model is the B3 Receiver but incorporates two 6BW6 VALVES in PUSH-PULL, resulting in really excellent quality reproduction up to approximately 6 watts. Price £15 15/- (Plus 7/6 carr. and ins.) or H.P. Terms £5 5/- Dep. 12 months at 15%.

A REPLACEMENT RADIO-RADIOGRAM CHASSIS

MODEL AW3-5. A 5-Valve Superhet Receiver covering the standard 3 wavebands, 16-50, 190-550, 900-2,000 metres. PRICE COMPLETELY ASSEMBLED AND READY FOR USE £10 10/- (Plus 7/6 carr. and ins.) H.P. Terms £3 10/- Dep. and 10 Months at 15%. This receiver is for operation on A.C. Mains 200-250 volts. It contains the latest MULLARD VALVE LINE UP, being ECH42 (Freq. Ch.), EF11 (I.F.), EBCH (Det. 1st Audio), EL11 (Output) and EZ11 (Rect.). It incorporates Negative Feedback and delayed A.V.C., the four controls being: (1) Tuning, (2) Wavechange and Gram Switch, (3) TONE, (4) VOLUME-OFF. It provides really good reproduction on both Gram and Radio and gives an exceptionally good range of station selection. Overall size 13 1/2in. x 7in. high x 6in. deep. Dial aperture 13in. x 4 1/2in.

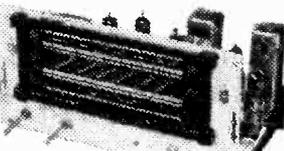

COMPLETE KIT for 12 WATT HIGH FIDELITY "Push-Pull" AMPLIFIER

Designed for A.C. mains 200 to 250 volts, employs 6 valves plus rectifier, with negative feedback, and comprises a main amplifier chassis and a remote controlled Pre-amplifier and Tone Control Unit, incorporating four controls—bass, treble, main volume or mixing control, and a radio, gram, microphone selector switch. This control unit measures only 7 x 4 x 2in. The measured frequency range of the amplifier with this unit shows an excellent response: from 14,000 cycles down to 20 cycles, the bass and treble controls allowing independent control of gain at both ends of the frequency range from zero to a gain of 50. It can be seen, therefore, that ample correction is provided for any type of pick-up with any type of recording. Input voltage for maximum output is 70 mV, 6.3 volts at 2 amps, and 20 mA. H.P. is provided for tuning unit, etc. Price of complete kit, Amplifier and Control Unit, including drilled chassis and valves, £14. Complete specification and layout 2/-. We can also supply completely assembled and ready for use at £17. Hire Purchase Terms (Assembled Chassis Only) £5 13/3. Deposit and 12 months of £1 1/4. Please add 7/6 carr. and insurance. THIS AMPLIFIER COMPARES WELL WITH THE WILLIAMSON AND SIMILAR DESIGNS AT A FRACTION OF THE COST.

microphone selector switch. This control unit measures only 7 x 4 x 2in. The measured frequency range of the amplifier with this unit shows an excellent response: from 14,000 cycles down to 20 cycles, the bass and treble controls allowing independent control of gain at both ends of the frequency range from zero to a gain of 50. It can be seen, therefore, that ample correction is provided for any type of pick-up with any type of recording. Input voltage for maximum output is 70 mV, 6.3 volts at 2 amps, and 20 mA. H.P. is provided for tuning unit, etc. Price of complete kit, Amplifier and Control Unit, including drilled chassis and valves, £14. Complete specification and layout 2/-. We can also supply completely assembled and ready for use at £17. Hire Purchase Terms (Assembled Chassis Only) £5 13/3. Deposit and 12 months of £1 1/4. Please add 7/6 carr. and insurance. THIS AMPLIFIER COMPARES WELL WITH THE WILLIAMSON AND SIMILAR DESIGNS AT A FRACTION OF THE COST.

"PERSONAL SET" BATTERY ELIMINATOR

A complete kit of parts to build a Midget "All-dry" Battery Eliminator, giving approx. 69 volts and 1.4 volts. This Eliminator is for use on A.C. mains and is suitable for any 4 valve Superhet receiver requiring H.T. and L.T. voltage as above or approx. to 69 volts. The kit is quite easily and quickly assembled and is housed in a light aluminium case, size 4 1/2in. x 1 1/2in. x 3 1/2in. Price of complete kit with easy-to-follow assembly instructions, 4/6. In addition we can offer a similar COMPLETE KIT to provide approx. 90 volts and 1.4 volts. Size of assembled Unit 7in. x 2 1/2in. x 1 1/2in. Price 4/6 (Plus 1/- carr. and ins.).

MODERNISE YOUR OLD RADIOGRAM FOR



We offer this Auto-changer complete with Model B3 3-waveband as advertised together with 10in. p.m. Speaker for £23 plus 10/- carr. and ins. or H.P. Terms £7 15/6 Dep. and 12 months of £1 9/2. or with B3PP Model for £26, plus 10/- carr. and ins. or H.P. Terms £9 16/6 Dep. and 12 months of £1 13/1.

MODEL B3-A 5-Valve 3 waveband Superhet Receiver for operation on A.C. mains 190-250 volts and 200-250 volts employing the very latest miniature valves. It is designed to the modern specification, great attention having been given to the quality of reproduction which gives excellent clarity of speech and music on both Gram and Radio, making it the ideal replacement Chassis for that "Old Radiogram," etc. Brief specifications—Model B3—Valve line up, 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Waveband Coverage: Short 16-56; Medium 187-556; Long 900-2,000 metres. Controls (1) Volume with on/off; (2) Tuning (flywheel type); (3) Wave change and Gram; (4) Tone (3 position switch operative on Gram and Radio). Negative Feedback is employed over the entire audio stages. Chassis size, 11in. x 7 1/2in. x 8 1/2in. high. Dial size 9 1/2in. x 4 1/2in. Price, complete and READY FOR USE excluding speaker, £12 12/- (Carr. and Pkg. 7/6 extra.) Or H.P. Terms £14 4/- Dep. 12 Months at 15%.

- auto-change on all three speeds, 7in. 10in. and 12in.
- Incorporating 11-in. Crystal "Turnover" Head.
- They have separate sap-phires for L.P. and 78 r.p.m. which are moved into position by a simple switch.
- Minimum base-board size required 13 1/2in. x 12 1/2in. with height above 5 1/2in. and height below base-board 2 1/2in. A bulk purchase enables us to offer these BRAND NEW UNITS, including mounting instructions, at this exceptional price.

A GENUINE SPECIAL OFFER!

The COLLAR 3RC 521 3-SPEED AUTO-CHANGE UNIT £9/19/6. H.P. Terms £3 6/- Dep. and 10 months at 15% (plus 7/6 carr. and ins.) Normal price £18 10/-.




A NEW DESIGN FOR HOME CONSTRUCTORS

The STERNS "SUPER SIX"

A compact and highly efficient Superhet Radio-Radiogram Chassis of outstanding quality, far above any other design yet offered to the HOME CONSTRUCTOR. YOU can build it for

£10/7/6

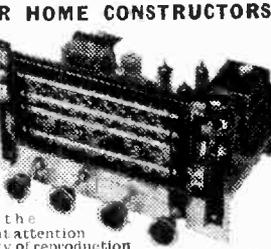
- Covers 3 Wavebands 18-50 metres, 190-550, 800-2,000 metres.
- Employs 6 Valves having PUSH-PULL for 5-6 watts OUTPUT
- DELAYED A.V.C. on all WAVEBANDS.
- PRE-SELECTIVE FEEDBACK.
- 4 POSITION TONE CONTROL.



- REAL QUALITY ON BOTH RADIO AND GRAM.
- PROVIDES INDEPENDENT MAINS SUPPLY FOR RECORD PLAYER (if required).
- FOR A.C. MAINS SUPPLY 200-250 Volts, 50 Cycles.
- Size of assembled CHASSIS 12in. long x 8in. x 8in. Dial Aperture 8 1/2in. x 4 1/2in.

DESIGNED TO THE VERY LATEST SPECIFICATION, GREAT ATTENTION HAVING BEEN PAID TO THE QUALITY OF REPRODUCTION WHICH GIVES EXCELLENT CLARITY OF SPEECH AND MUSIC ON BOTH RADIO RECEPTION AND RECORD PLAYING. A few brief details:

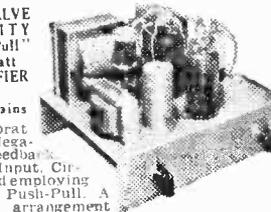THE COMPLETE RECIPIER CAN BE BUILT FOR £10 7/6 WITH THE OCTAL VALVE LINE UP or for £12 7/6 with Miniature Valves.



- A 4-VALVE QUALITY "Push-Pull" 6-8 watt AMPLIFIER for A.C. mains
- Incorporating Negative Feedback
- Filter Input Circuit and employing 6V6s in Push-Pull. A simple arrangement is provided to enable either a magnetic crystal or light-weight pick-up to be used, and is suitable for use with Standard or Long-playing records. A tone control is incorporated, and the 10-watt output transformer is designed to match 2 to 15 ohm speakers.
- The overall size of the assembled chassis is 10in. x 8in. x 7in. high and full practical diagrams are supplied. Price, including drilled chassis and valves, of complete kit, £6 17/3. Price of assembled chassis, supplied ready for use, £8 12/6. Full descriptive leaflets are available separately for 1/-

STERN RADIO Ltd. 109 & 115, FLEET STREET, E.C.4. TELEPHONE: CENTRAL 5812/3/4

"High Fidelity at moderate cost"...

Introducing the

"RD MINOR" MK. II

*A compact high-performance
gramophone amplifier*

MAIN FEATURES:—

★ 4.5 watts Output ★ Distortion at 3.5 watts less than .25% ★ Frequency response +.5DB 30-15,000 cps. ★ Hum -80DB below 3.5 watts ★ NFB 16DB ★ Matching for 3 and 15 ohm speakers ★ Operation from the majority of modern lightweight pick-ups ★ Treble cut control ★ Compensation for STD and LP records ★ Miniature valves throughout.

PRICE: **£12.17.6**

Illustrated leaflets describing the MINOR II and our other current high fidelity products available post free on request.

ROGERS DEVELOPMENTS Co.

Manufacturers of Precision Built Sound Equipment

"RODEVCO HOUSE,"

116, BLACKHEATH ROAD, GREENWICH, S.E.10

Telephone: TIDeway 1723.

Demonstration Times: Mon.-Fri. 9.30 - 5.30
Sat. - - 9.30-12.30

BUILD THIS AMAZING RADIO FOR YOUR HOLIDAY

FOR **30/-**

POST FREE

- Selective tuning.
- Acorn low drain valve.
- Loud clear tone.
- Long range.
- No earth.
- Short aerial, 2ft.
- Welded steel case.
- Easy to assemble.
- All parts for this set are sold separately.

Ideal for:


- Fishing, Camping
- Cycling, Touring
- On the beach, etc.

MAIL ORDER ONLY

This little set was designed to give you a real personal portable radio that you can enjoy anywhere without disturbing others. Use it on camping trips, in bed, in your office, or just anywhere. Send 2/- for layout, Wiring diagram and Component Price List.

Details of our 30/- Short Wave Receiver are now ready. Send 2/- for Layout, Circuits and Component Price List.

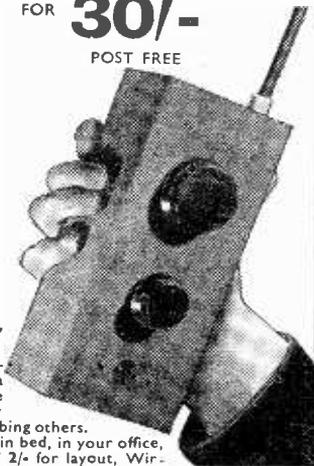R. C. S. PRODUCTS (RADIO) LTD.,
11, OLIVER ROAD, LONDON, E.17



SHORTAGE OF RADIO & T/V ENGINEERS

The demand of Industry for our trained students is still greater than we can supply—and is likely to remain so for many years.

We offer

FULL TIME DAY COURSE

1-year course in Principles and Practice of Radio and Television.

Next course commences 30th August, 1954.

Write for FREE BROCHURES giving details of the above, of our 3-year course (commencing 30th August) and of others.

E.M.I. INSTITUTES—the only college which is part of a great industry.

E.M.I. INSTITUTES (Dept. 32K)

10, PEMBROKE SQUARE,
LONDON, W.2.

Tel.: BAYswater 5131/2.

Associated with
"H.M.V."
MARCONIPHONE
COLUMBIA
ETC.

1A 18

HANNEY OF BATH offers:—

P.W. SIX-VALVE A.C. SUPERHET. Osmor 3-Band R.F. coilpack, 69/-; Osmor pre-aligned I.P.F.s, 16/- pr.; Elstone mains trans. to specification, 32/-; Denco 16 x 8 x 2 1/2 in. chassis, 11/-, etc., etc. Priced parts list available on application.

FREQUENCY MODULATION. For Wrotham high fidelity Transmissions. Denco technical bulletin giving circuit and point to point wiring diagram for building an F.M. Feeder unit, 1/8. We have all components available. Priced parts list on application.

W.B. STENTORIAN High Fidelity Speakers, HF610, 50/6; HF610 60/6; HF912 67/-; HF1012 (3 or 15 L.), 73/6.

ACOS Hi-g Pick-ups. HGP 29-1 std. or LP 68/8. Heads only std. or LP 42/3.

COILPACKS. Denco, CP 4-L and CP 4/M, 33/4; CP 3/70 pf. and CP 3/500 pf., 42/8. OSMOR "Q" HO 48/-; LM, 40/-; Batt., 50/-; TRF, 40/-; HF stage for HO pack, 20/-; ETA 4-Station pack, 43/8. We stock COILS by Weymouth, Osmor, Wearite, Denco, Teletron and R.E.P.

ELSTONE Mains Trans. for the SIMPLEX TV, 48/-.

VIEWMASTER. WIDE ANGLE VIEWMASTER CONVERSION. Complete set of parts for converting existing Viewmaster to W.A. less valves, tube and mask £14/13/6. W.A. Conversion instructions, 3/6; WB.113, 48/6; WB114, 23/6; WB115, 42/-; WB116 and WB117, 7/8 each; WB118, 22/6; WB119, 26/9; WB121, 3/6; WB124, 10/6; Westinghouse 36/EHT/30, 17/-; Plus condensers and resistors as per our general list.

MULLARD "UNIVERSAL." LARGE SCREEN A.C./D.C. TELEVISOR. Denco drilled chassis with all mechanical parts, 53/6; FD124 duomag focaliser, 37/6; 14A/342 rectifiers, 37/2; Goldsman droppers DK37/6, 8/9; DK35/6, 7/6. VA1008 varite res., 4/6. Other Denco parts, please see below.

WIDE ANGLE COMPONENTS. ALLEN. Teleking Chassis, 50/-; Coils (TK & Super-Visor), 44/6; LO.308, 40/-; FO.305, 21/-; DC.303, 39/6; FC.302, 31/-; GL.16 & 18, 7/6 each; SC.312, 21/-; AT.310, 30/-; OP.117, 9/-; BT.314, 15/-; Denco Chassis Magnaview, 37/6; Chassis, Super-Visor, 51/6; Coils, Magnaview, 41/2; WA/DCAL, 43/-; WA/FCAI, 31/-; WA/LCI and WCI, 7/6 each; WA/FMAL, 21/-; WA/LOTI, 42/-; WA/FBTI, 16/-; Send 6d. stamps for our General List of components for Viewmaster, Soundmaster, Williamson Amplifier, Teleking, Magnaview (Brimar & English Electric large screen TV), Super-visor, Mullard Universal, Close tolerance Silver Micacs, etc., etc. Please add 1/- postage to orders under £1.

L. F. HANNEY

77, LOWER BRISTOL ROAD, BATH

Tel.: 3811

Hence, $k = \frac{3}{2\sqrt{Q_p Q_s}}$ Eqn. 8A

In designing the W.B.C. it is advisable to proceed as follows :

- (1) Use Eqn. 9 to find a suitable value of k, to give the required bandwidth.
- (2) Use Eqn. 8A to determine the best Q values for uniform transmission response, within the frequency limits. From Eqns. 8 and 9, we see that if the bandwidth is large, the value of k must be large and the relative circuit Q values will be low. This results in the secondary voltage and current values being small; thus the smaller the bandwidth, the greater will be the output, for a fixed R.M.S. generator voltage input to the primary circuit. Fig. 2 shows the relationship between k, Q and bandwidth, utilising the equations above. Having decided upon our circuit constants, it is simply a question of constructing our W.B.C.s separately, after having determined the values of L and C, to resonate in the centre of the pass-band of the amateur band under question; i.e., resonating on 7.150 Mc/s for the 40-metre band. These values can be readily determined using the various formulae given in Appendix C.

Fig. 3 — Pulse width and harmonic relationships.

Harmonic of Fundamental Frequency (f)	Optimum Ia pulse length, at f c/s, expressed in electrical degrees (values are approximate)	Approx. Percentage Output comparable with Class C Amplifier (Class C taken as 100%)
2	80°-120	65
3	70°-110°	45
4	60°-85°	30
5	50°-70°	25
6	40°-50°	21

Frequency Multipliers

It is common practice to construct the V.F.O. for the lowest frequency band to be covered and multiply up to each separate band, using the W.B.C. stages. It is a well-known fact that, since the pulses of anode current of a Class C amplifier have a high harmonic content, it follows that this type of amplifier is ideal for W.B.C. operation; since it is only necessary to adjust the anode current pulse width for favourable harmonic generation, provided that the bias is increased as the output harmonic is increased. ("Principles of Frequency Multiplication," PRACTICAL WIRELESS, December, 1952.) The shorter the length of the Ia pulse, the higher is the plate efficiency, but more bias and exciting voltage are needed to produce any given harmonic. The plate efficiencies given in Fig. 3 are less than those normally associated with Class C operation standards; but since the output is normally less than Class C, the anode dissipation will, therefore, not be exceeded. Fig. 4 shows the various voltage waveforms to be expected with the average frequency multiplier valve and, although not to scale, suffices to illustrate the point in hand.

Experimental Circuitry

The circuit shown in Fig. 5 was the basis of the experiments conducted on W.B.C. techniques. It

is seen that mutual inductance coupling is used to couple the two windings and relevant coil winding data are given in Fig. 6. Details of coil spacing are not given, since the relative positions must, usually, be determined by experiment.

The former used was the Aladdin Type 5937/6, which has an overall diam. of $\frac{1}{8}$ in. and has a winding capacity of 1 $\frac{1}{8}$ in. Incidentally, the complete coupler can be constructed from Aladdin accessories and is comparable with the dimensions of a midget I.F. transformer. A 6SN7 double-triode was used for all experiments and the response curve, in each case, was drawn by plotting frequency against grid current. The V.F.O. should be set to the H.F. end of the band in question and the primary trimmer of the coupler adjusted for maximum drive; then set the V.F.O. to the L.F. end and adjust the secondary trimmer for maximum grid drive. It may be necessary to move the relative positions of L1 and L2, but the author did not find this necessary in his case. Now swing the V.F.O. over the entire range and note the grid current. If it is not fairly steady, reduce the capacity of the 30 pF trimmer and repeat the process until flat grid drive is obtained. The grid current should drop abruptly just outside the band

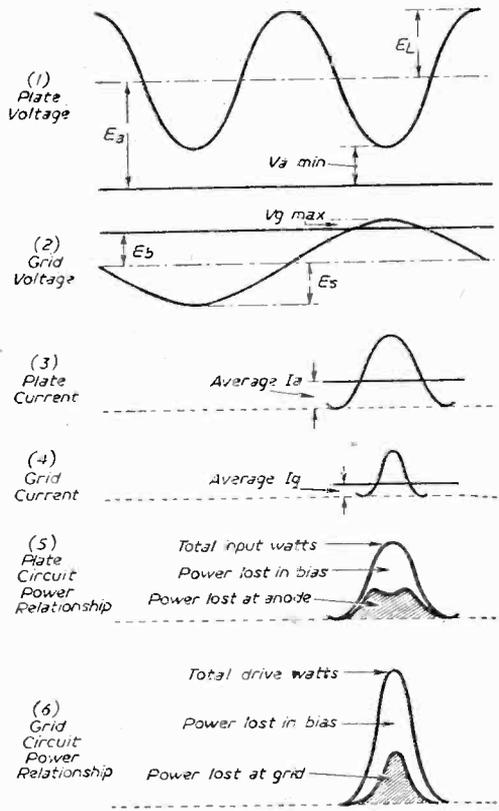


Fig. 4. — Typical Class C harmonic generator waveforms.

Ea = H.T. volts. Eb = Bias volts. Va min. = Minimum anode volts. EL = Volts across anode load. ES = Input drive voltage. Vg max. = Maximum control-grid volts.

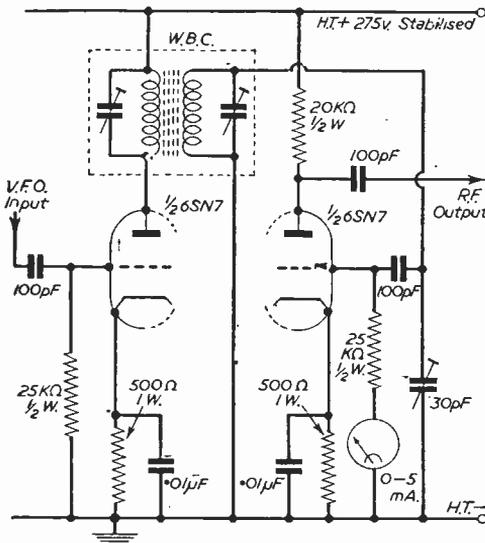


Fig. 5.—An experimental circuit.

COMPONENT LIST

- Two 25,000 ohm ½ W. Resistors
- Two 500 ohm 1 W. Resistors
- One 20,000 ohm ½ W. Resistor
- Three 100 pF Mica Capacitors
- Two 0.01 μF Capacitors
- One 30 pF Trimmer
- One F5937/6 Aladdin Former
- One PP5939 Aladdin Core
- One Top Plate to fit F5937/6
- One Solder Tag Ring for F5937/6
- One Aluminium Screening Can 2 3/4 in. x 1 3/16 in. square.

limits; if this is not the case, the coupler is incorrectly adjusted. The response curves obtained, using these couplers, are reproduced in Fig. 7. The output of the V.F.O. on the 160 metre band was in the region of 10 volts R.M.S., while the H.T. voltage was 275. Great care should be exercised in the coupler construction, since it will give endless pleasure and ease of transmitter operation.

APPENDICES :

Appendix A. The secondary voltage is produced by I_p , the primary current. The voltage induced in the secondary is $\omega M I_p$ and is 90 deg. out of phase with I_p .

Hence, the secondary current is $\frac{\omega M I_p}{Z_s}$, Z_s being the secondary impedance. This current produces a back E.M.F. of $\frac{\omega M(\omega M I_p)}{Z_s}$ or $\frac{I_p(\omega M)^2}{Z_s}$

Band	Prim. Turns	Sec. Turns	Wire Gauge	Approx. Parallel Capacity
1.7 Mc/s	70	70	40g. Enam.	20pF.
3.5 Mc/s	35	35	32g. Enam.	9pF.
7.0 Mc/s	28	28	32g. Enam.	5pF.
14.0 Mc/s	22	22	32g. Enam.	2-5pF.
21.0 Mc/s	17	17	32g. Enam.	2-5pF.
28 Mc/s	12	12	32g. Enam.	2-5pF.

Fig. 6.—W.B.C. coil winding data.

volts in the primary circuit. Since this voltage is 90+90 deg., i.e., 180 deg., out of phase with I_p , it is a back E.M.F. The reduction in voltage, due to this back E.M.F., is $\frac{(\omega M)^2}{Z_s}$ times the primary current; so that the effect of the secondary circuit, upon the primary circuit, is the same as adding an impedance of $\frac{\omega M^2}{Z_s}$ to the primary circuit.

Appendix B. The coefficient of coupling, k , is defined as: "The ratio of mutual impedance component of the two circuits to the square root of the product of the separate primary and secondary impedance components, of the same kind."

- Mutual impedance component = ωM .
- Primary impedance component = ωL_p .
- Secondary impedance component = ωL_s .

$$\text{Therefore } k = \frac{\omega M}{\sqrt{\omega L_p \cdot \omega L_s}} = \frac{\omega M}{\sqrt{\omega^2 \cdot L_p \cdot L_s}} = \frac{\omega M}{\omega \sqrt{L_p \cdot L_s}} \quad \text{Thus } k = \frac{M}{\sqrt{L_p \cdot L_s}}$$

(Concluded on page 506)


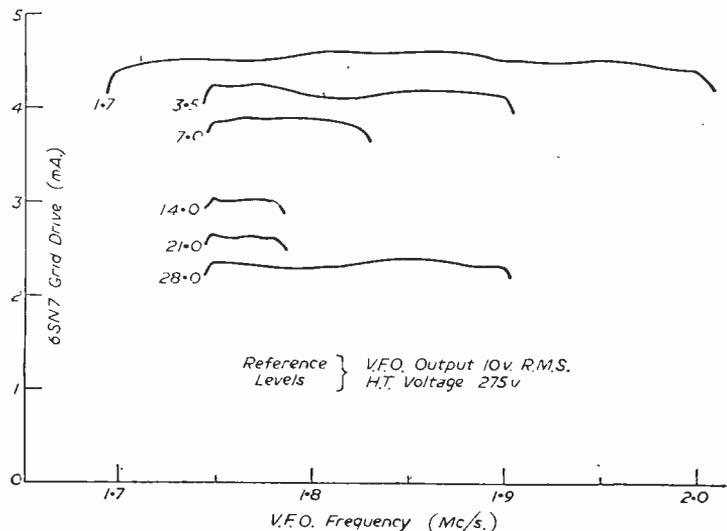


Fig. 7.—W.B.C. frequency response curves.

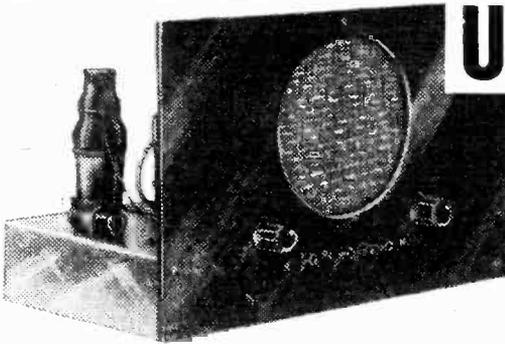

UNIVERSAL PUSH-BUTTON



AN A.C./D.C. RECEIVER WITHOUT MANUAL TUNING. PRE-SELECTED STATIONS ARE CHOSEN BY A PUSH-BUTTON UNIT

THIS circuit was designed with several requirements in view, and it ably fulfils them. A good degree of selectivity and sensitivity was desired, without the complication of a superhet circuit, and this was achieved by using two tuned circuits with loosely-coupled primaries, in conjunction with an anode bend detector, which is comparatively insensitive to weak signals. As a result, the four desired stations were received quite free of interference, with a very short indoor aerial.

Particular attention was given, in the layout and circuit, to avoid hum, which so readily arises in A.C./D.C. receivers. The anode bend detector cannot operate at hum frequencies, since the tuning coil is then of negligible impedance, so no hum is

passed on to be amplified by the output stage. (Changing the detector to one of the more usual type, with grid condenser and leak, resulted in a noticeable increase in hum.) The hum level is so low that it is difficult to hear any hum at all, unless the ear is placed near the loudspeaker when no signal is being reproduced.

Further to simplify operation, the on/off switch is separate from the volume control, so that the latter can be left at any previously obtained setting—a small point which is found well worth while in a receiver of this type. A double-pole rotary mains switch is used, so that the set is effectively disconnected from the mains when switched off.

The push-button unit is wired to provide one


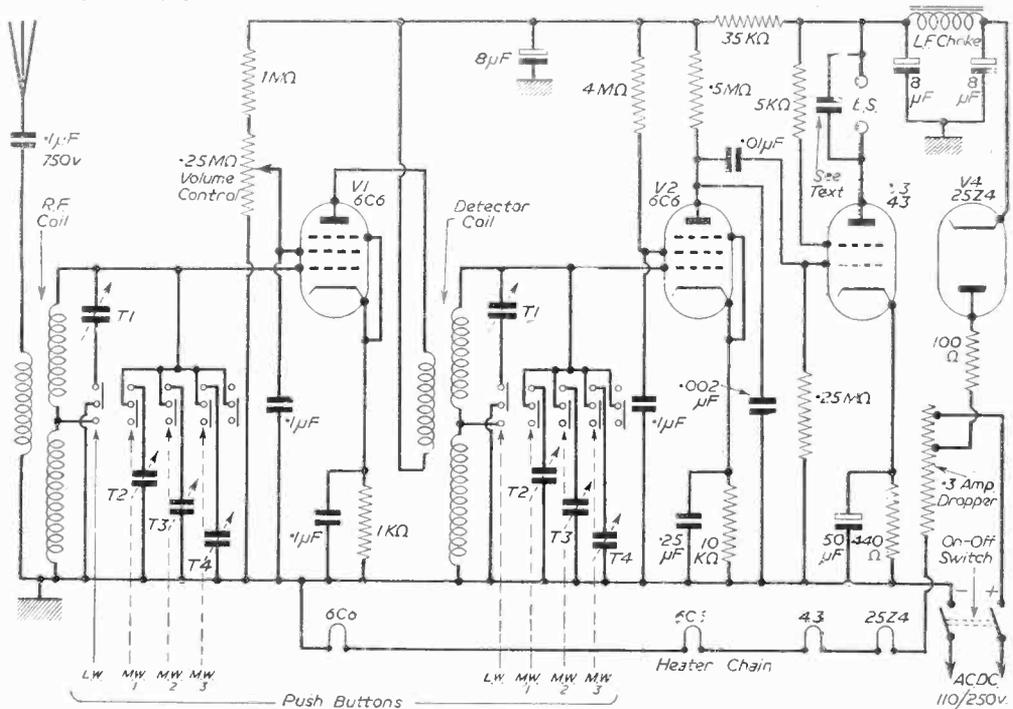


Fig. 1.—Circuit diagram.

long-wave and three medium-wave stations, as shown in Fig. 1. Each button operates a double-pole, double-throw switch combination. When the long-wave button is depressed, both trimmers T1 are brought into circuit. When any of the other buttons are operated, the pairs of trimmers T2, T3 and T4 are switched in, and the coils are switched to medium-waves as the first button springs out. If no long-wave station is required, four or five medium-wave

As there is only one stage of L.F. amplification, very little distortion is introduced and quality of reproduction was surprisingly good. If desired, a measure of negative feedback could be introduced over the output stage, by wiring a .25 megohm resistor, with .5 μ F condenser in series, from 43 anode to 6C6 anode.

In the event of manual tuning being required, the unused switch contacts should be used to bring into circuit a 2-gang .0005 μ F tuning condenser, and the layout should be suitably modified to accommodate this component. If a pilot-lamp is wanted, a .3 amp. 6.3 volt type, shunted by a 40 ohm 1 watt resistor, should be wired between rectifier heater and mains dropper. If these changes are made, care should be exercised to assure that hum is not caused. Twin flex should be used for the pilot bulb connections, and should be well away from grid and anode wiring.

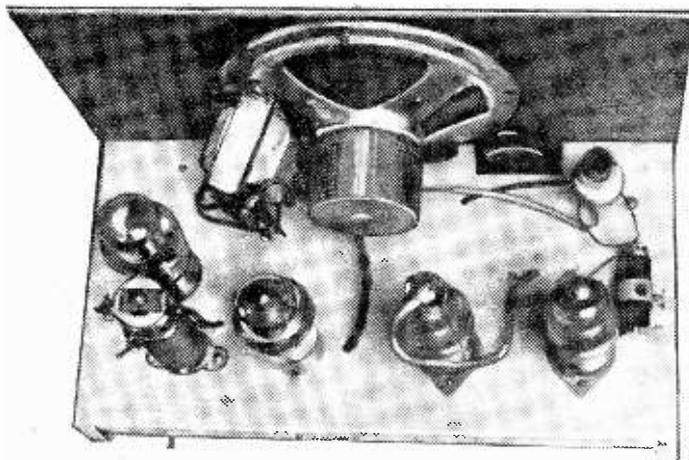

Top of chassis view.

stations could be provided for, and the spare button can, of course, be used for an additional station, or for "gram" reproduction. Tuning is accurately maintained, even with changes in the aerial, because of the loosely-coupled primary winding, and it was for this reason that this type of coil was selected here.

COMPONENT LIST

Resistors :

100 ohm, 440 ohm, and 5,000 ohm (1-watt).
1,000, 10,000, and 35,000 ohm ($\frac{1}{2}$ -watt).
.25 megohm, .5 megohm, 1 megohm, and 4 megohm ($\frac{1}{2}$ -watt).

Condensers :

Three .1 μ F (350v. w.).
.1 μ F (750 v. w.).
.002 μ F and .005 μ F (350 v. w.).
.01 μ F mica.
.25 μ F.

50 μ F (25-50 v. w.).

Three 8 μ F (350 v. w.).

Four twin pre-set condensers.

Pair "Astral" Dual-Range coils.

.3 amp 800 ohm mains dropper with two adjustable clips.

6C6, 6C6, 43, and 25Z4 valves, or equivalents.

Holders for same.

Double-pole 5-button push-button unit with knobs.

Double-pole mains rotary on/off switch (Bulgin).

60mA smoothing choke.

Chassis, P.M. speaker with transformer, control knobs, 3-ply for panel, screened brading, etc.


a result, there are no live bolt heads or similar exposed metal parts, and the receiver is safe.

The aerial condenser is to keep mains voltages out of the aerial, and should be of good quality. If the aerial is long, a small condenser may be introduced in series with it, to sharpen aerial tuning. A 50 pF pre-set condenser is admirable for this position. The aerial coil and associated wiring is above the chassis, and not screened.

Tag A on the mains dropper is the bottom fixed clip, and goes to the switch. Tag B is the central adjustable clip, and goes to the 100 ohm resistor. Tag C is the upper adjustable clip, and goes to the rectifier heater.

The condenser wired in parallel with the speaker transformer is connected directly to the transformer tags, and a capacity of .005 μ F is suggested. A larger capacity will result in a more "mellow" tone.

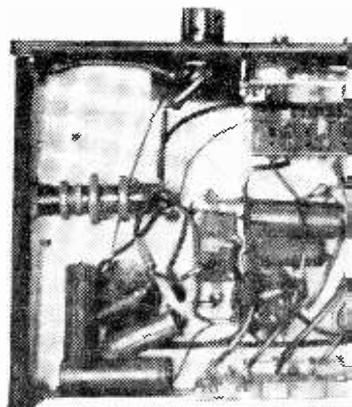The front of the chassis is cut to accommodate the on/off switch and



Below chassis.

volume control. These are secured to the plywood panel, and are not in contact with the chassis. As a result, fixing bushes and spindles are "dead" as regards possible mains voltages.

Sub-chassis Wiring

Wiring below the chassis will become clear from the illustration at the foot of this page, but a few points require special note. The heater wiring should be put on first, and should be right against the chassis. Other wiring is kept clear of these leads. The two leads to the on/off switch pass directly through the side runner, between choke and panel, and these are kept away from the aerial, externally, to avoid possible modulation hum.

The 43 valve grid lead is screened, as is the lead from the detector grid cap, to avoid hum and instability. The side of the switch near the chassis is used for R.F. stage switching, and the leads from the tags on this, to the pre-sets, are screened. All the screening braiding should be bonded to the chassis. This can be done by forming loops of connecting wire round the screened leads, and soldering.


The other side of the push-button switch deals with the detector circuit. Only the leads to the long-wave pre-set need be screened here. Wiring for the other side of the switch is exactly the same, the leads being added before the switch is secured in place.

Best alignment between push-buttons and panel holes was obtained when the switch was securely bolted to the panel. The frame of the switch should be connected to chassis, to preserve stability, so the 6 B.A. bolts used were insulated from the switch by means of ebonite bushes. This is desirable since the heads are flush with the panel.

Each of the trimmers T1 to T4 is a double trimmer, one section tuning the R.F. stage, and one the detector stage. The various leads should go directly to the tags, or stray coupling may result in instability if the volume control is turned to maximum. It is also desirable that all other connections be short. Leads from the aerial coil pass down through the chassis to the switch.

The trimmers are bolted along the rear runner of the chassis, this position being chosen so that easy adjustment is possible when receiver is in its cabinet.

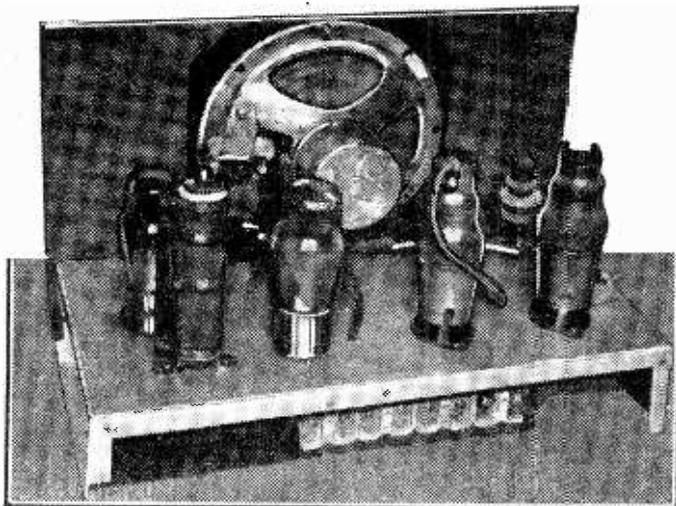Connections for the detector coil are shown on the right. This coil is mounted by its earthing tag, as is the aerial coil. No reaction is used, but a coil with reaction winding can be utilised by leaving the reaction winding disconnected.




Rear view showing pre-sets

Full details of the chassis and wiring diagrams will be given next month, along with further details of the actual construction. In the meantime, for those who are able to build from a theoretical circuit some notes may be appropriate concerning the setting up of the receiver. It should be emphasised, however, that as with all A.C./D.C. types of equipment the utmost care is necessary to ensure that there is no possibility of the user making contact with the mains. One side of the mains supply, being connected to the chassis, renders this "live" unless it is, as already stated, placed in the cabinet, and therefore all bench tests or other experiments, carried out with the set out of its cabinet, must be carried out with the greatest care.


Setting-Up.

The upper clip of the mains dropper should be adjusted until the heater voltage, as measured across rectifier or output valve, is 25.

(To be continued)

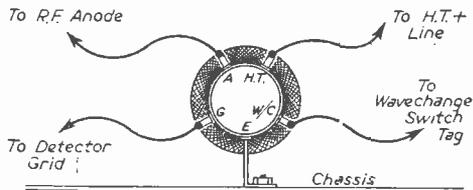

Coil data.

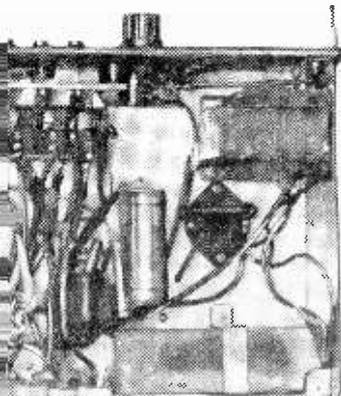


wiring view

A Modern Reflex Receiver

A NUMBER of queries have been raised concerning the circuit published under this title in last month's issue. First, no practical layout diagram is available, and the only information we can supply is that in the issue in question. Secondly, there is no battery version of this particular type of valve and, therefore, it is not possible to make a battery version of this circuit. Thirdly, the coils may be any standard screened or unshielded modern types, although if unshielded it is preferable to mount them one above and the other below the chassis or otherwise screen them from one another.

The circuit showed the mains input connected both to earth and aerial, and it should be stated that this can be dangerous. The coil on the right, therefore, should be the secondary of a mains transformer in order to isolate the receiver from the mains, or, if expense is to be saved by using only a heater transformer, then the aerial and earth leads should be isolated by means of fixed condensers rated for at least 600 volts working. That on the earth side should be $.1 \mu\text{F}$ and that in the aerial lead some value between $.0001$ and $.0005 \mu\text{F}$. A revised diagram is given below.

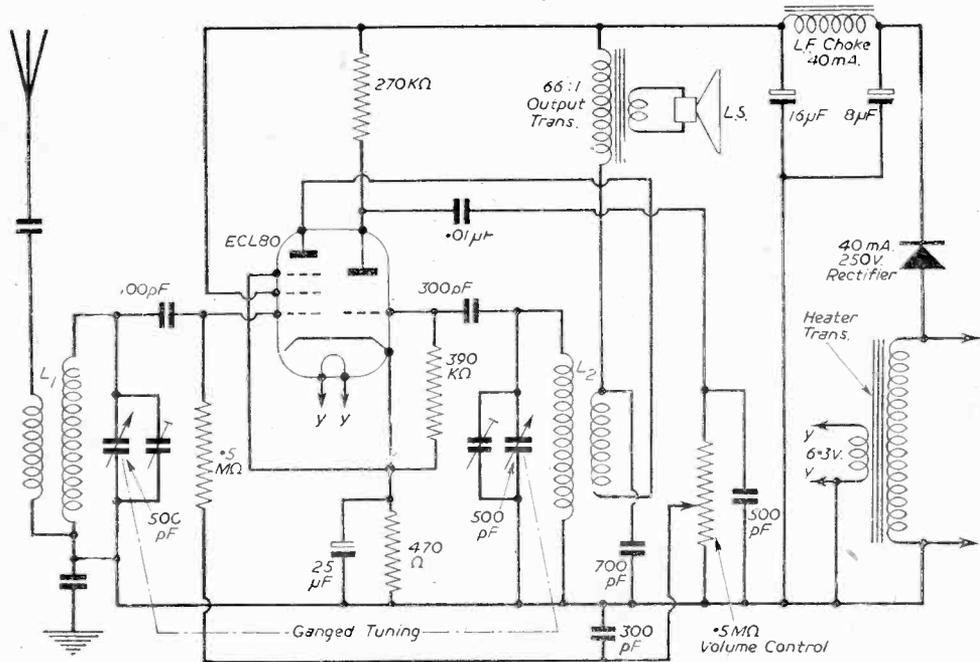

The modern reflex receiver.

News from the Clubs

CLIFTON AMATEUR RADIO SOCIETY

Hon. Sec.: C. H. Bullivant, G3DIC, 25, St. Fillans Road, London, S.E.6.

THE membership of this society is continually on the increase and each week sees one or two new members. The Clifton caters for all aspects of amateur radio from the constructor to the short-wave listener and licensed operator. Programmes are arranged to suit all tastes. For instance, on May 7th club member D. Vasey gave a talk on "Hi-Fi" and demonstrated his home-built amplifier with standard and L.P. recordings, whilst on May 21st another popular Junk Sale was held. On this occasion there was a record attendance of 48 and many pieces of equipment changed hands, including, for the first time, a complete television set.

Constructional evenings were held on May 14th and 28th, when members busily engaged themselves on building up new equipment or repairing faulty equipment.

During July it is proposed that the following meetings and events take place:


July 9th, Constructional evening: July 16th, Any Questions?; July 18th, Second D.F. contest: July 23rd, Constructional

evening: July 24th/25th, Transmitting and receiving contest. Meetings are held every Friday at 7.30 p.m. at the club-rooms, 225, New Cross Road, London, S.E.14. A warm and cordial welcome awaits visitors and new members.

SOUTHEND AND DISTRICT RADIO SOCIETY

Hon. Sec.: J. H. Barrance, M.B.E., 49, Swanage Road, Southend-on-Sea, Essex.

THE Southend group of radio amateurs took part in the National Field Day organised by the Radio Society of Great Britain recently in a 24-hour continuous watch. Two portable stations were manned: one at Thundersley Glen, working on 80 and 160 metres, and one at Pulpitts Hockley, working on 20 and 40 metres. Contacts were made with some 200 similar portable stations in the British Isles and about a dozen foreign countries, in spite of the rain, thunder and lightning. At one period during the night, the rain was electrostatically charged, as was also the tent and the whole area. The conditions were the worst ever experienced at this annual event; proving that in an emergency communications could be maintained without mains or wire in extremely adverse circumstances.

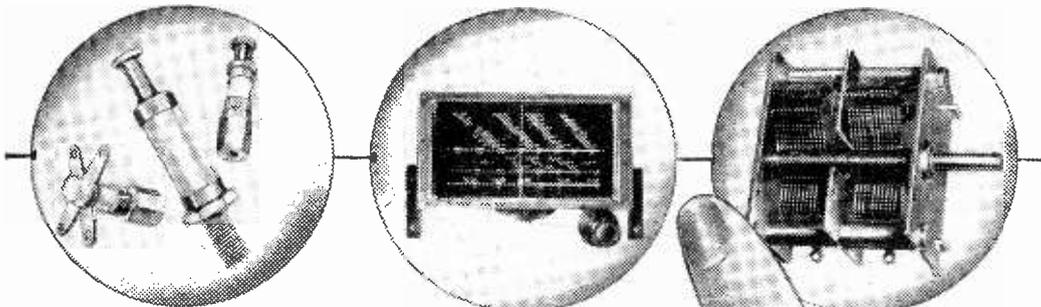


**You can count on these
 . . . for a reliable performance**

STAND-OFF INSULATORS. Working voltage 1,500/5,000. Very high insulating resistance. Ceramic non-tracking. Silicone treated to repel moisture (ideal for tropics). Tag or spill end. We have a full range to cover most needs.

S.L. 8 SPIN WHEEL DRIVE. A precision slide rule drive complete with 3 band glass scale. The spin wheel drive gives perfect control through ratio 24 : 1. Fitted with constant velocity coupling, eliminating strain on condenser and providing mechanical and electrical isolation from vibration and noise. Price 27/6.

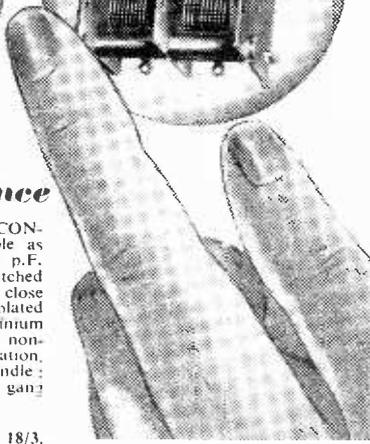M.G. GANG CONDENSER. Available as 1, 2 or 3 gang, 490 p.F. nominal capacity, matched and standardised to close limits. Cadmium plated steel frame. Aluminium Vanes. Low loss non-hygroscopic insulation. Length excluding spindle: 1 gang—1 7/8 in. to 3 gang—3 5/8 in. Price 1 gang, 9/3. 2 gang, 14/-, 3 gang, 18/3.



JACKSON BROTHERS (London) LTD., KINGSWAY · WADDON · SURREY
 Telephone : CROydon 2754-5. Telegrams : WALFILCO, SOUPHONE, LONDON.


20 to 200~ 200~ to 2kc/s 2 to 20kc/s 20 to 200kc/s

WHEN YOU CONSIDER the enormous frequency range of this instrument (10,000-1) we feel you must agree that it represents quite outstanding value at its very modest price. "Providing," you will say, "it is all you claim it to be."

OF COURSE. We say that this instrument is good, but let the specification speak; hyperbole cannot enhance facts. The workmanship is sound and, where necessary, robust—we have a hard experience of sending many thousands of our instruments on long postal journeys. The mechanical design and layout are, we think, eminently practical—knobs where you want them and a desk type cabinet which removes the backache from scale reading.

We make no claims for our instruments which are not true, and if you wonder why the price is so low we can give the reason. We make instruments and sell them direct to the user—it is as simple as that!

LOW FREQUENCY SIGNAL GENERATOR

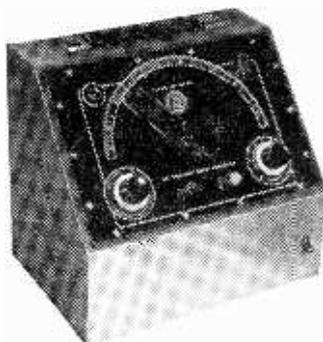

PRICE : £15-15-0
 or £5-5-0 Deposit and 6 Monthly Payments of £2-2-0
 (Post and Packing 5/- Extra)

- R-C Wien Bridge oscillator circuit with automatic amplitude stabilisation.
- Buffer amplifier protects oscillator from effects of varying external loads.
- Cathode-follower output stage.
- Frequency coverage 20~ to 200 Kc/s, in four decade ranges.
- Sine wave output with less than 1% distortion.
- Output power and voltage : 0.1 watt into 600 ohms or 10 volts across 5,000 ohms.
- A.C. mains operation—110 and 200-250 volts 50-100~.

Call and inspect this instrument (we are open until 12.30 p.m., on Saturdays) or send for full technical details. Our range includes **SIGNAL GENERATORS ● PATTERN GENERATORS ● CALIBRATED VARIABLE CONDENSERS ● SUBSTITUTION BOXES.**

EXPORT ENQUIRIES WELCOMED

HOMELAB INSTRUMENTS LTD., 615-617 High Road, London, E.10
 Phone : LEY 5651 Telegrams : HOMELAB, LEYSTONE, LONDON Cables : HOMELAB, LONDON

IMPORTANT NEW BOOKS

Crystal Rectifiers and Transistors, edited by M. G. Say. 21s. 0d. Postage 6d.

Practical Television Circuits, by F. J. Camm. 15s. 0d. Postage 6d.

Practical Wireless Circuits, by F. J. Camm. 10s. 6d. Postage 4d.

Television Circuit Refinements, by C. H. Banthorpe. 5s. 0d. Postage 3d.

The Oscilloscope at Work, by A. Haas and R. W. Hallows. 15s. 0d. Postage 6d.

Please write or call for our catalogue.

THE MODERN BOOK COMPANY

Britain's Largest Stockists of Technical Books

19-23 PRAED STREET
(Dept. P.7.)
LONDON, W.2

Phone: PADdington 4185.
Open all day Saturday.

COMMUNICATIONS RECEIVER R.1155. The famous ex-Bomber Command Receiver known the world over to be supreme in its class. Covers 5-8 wave ranges 13.5-7.5 mc's. 7.5-10 mc's. 1,500-500 kc's. 500-200 kc's. 200-75 kc's. and is easily and simply adapted for normal mains use. Full details being supplied. Aerial tested before despatch these are IN EXCELLENT CONDITION. IN MAKERS' ORIGINAL TRANSIT CASES. ONLY £9 19 6.

A few partly dismantled receivers are available FOR CALLERS ONLY. Ideal as a source of spare parts. ONLY 30/- each. A factory made Power Pack, Output Stage and Speaker, contained in a black cracked cabinet to match the receiver, can be supplied at ONLY £5 10/0. Operates receiver immediately.

DEDUCT 10/- IF PURCHASING RECEIVER & POWER PACK TOGETHER. Please add carriage cost of 10/6 for Receiver, and 5/- for Power Pack.

100 MICROAMPS METERS. 2 1/2 in. Circular Flush Mounting. Widely calibrated scale of 15 divisions marked "Yards," which can be re-written to suit requirements. These movements are almost unobtainable to-day and being BRAND NEW. MAKERS CARTONS are a snip. ONLY 42 6.

TRANSFORMERS.—Manufactured to our specifications and fully guaranteed Normal Primaries. 425-0-425 v. 250 m.a., 4.2 v. 4 a., 6.3 v. 4 a., 5 v. 3 a. ONLY 50/-; 350 v. 0-350 v. 150 m.a., 6.3 v. 6 a., 6.3 v. 3 a., 5 v. 3 a. ONLY 42 6.; 250 v. 0-250 v. 120 m.a., 6.3 v. 6 a., 5 v. 3 a. ONLY 32 6.; 350 v. 0-350 v. 150 m.a., 6.3 v. 5 a., 0-1.5 v. 3 a. ONLY 32 6. The above are fully shrouded upright mounting, 5.5 kV. E.H.T. with 2 windings of 2 v. 1 a., ONLY 72 6.; 7 kV E.H.T. with 4 v. 1 a. ONLY 82 6. PLEASE ADD POSTAGE FOR EACH TRANSFORMER.

500 KC. CRYSTALS.—Standard 2 pin mounting. Ex-new equipment and perfect. ONLY 15/- (postage etc. 1/-)

8 VOLT VIBRATOR PACKS.—Made by H.R.O. of America. Output 165 v. 30 ma., 6.3 v. 3 a. Contains 6X5 rectifier, and full smoothing. Self contained in black cracked cabinet size 7 in. x 7 1/2 in. x 6 in. ONLY 29 6. (postage etc. 2/-).

AMERICAN ROTARY TRANSFORMERS.—12 v. D.C. input, output 250 v. 65 ma. Useful for car radio, or running electric shaver from car battery, etc. ONLY 22 6.

VACUUM PUMPS.—These are ex-R.A.F. rotary vane type, and are ideal for handymen and model makers, etc. New and Unused. ONLY 22 6. (postage etc. 2/-).

INDICATOR UNITS, TYPE 6.—Contain VC897 Tube with mu-metal screen. 4 valves: EF50 and 2 of EB31. NEW CONDITION. ONLY 59 6. (carriage, etc. 7 6).

METERS		
F.S.D. SIZE AND TYPE		PRICE
1 m.a. D.C. 2 1/2 in. Flush square	15 6
1 " D.C. 2 1/2 in. Flush circular	22 6
1 " D.C. 2 1/2 in. Desk type	25 6
5 " D.C. 2 1/2 in. Flush square	7 6
10 " D.C. 2 1/2 in. Flush circular	12 6
150 " D.C. 2 in. Flush square	7 6
300 " D.C. 2 in. Flush circular	12 6
500 " thermo 2 in. Flush square	5 6
500 " thermo 2 in. Proj. circular	5 6
20 amps D.C. 2 in. Proj. circular	7 6
40 amps D.C. 2 in. Proj. circular	7 6
30-0-30 amp D.C. Car Type moving iron	5 6
15 volts A.C. 2 1/2 in. Flush, etc., mov. iron	8 6

All meters Brand New in Maker's Cartons

Amounts given for carriage refer to inland only.

U.E.I. CORPORATION,
133, Gray's Inn Road, London, W.C.1
(Phone: TERMINUS 7937)

(Open until 1 p.m. Saturdays. We are 2 mins. from High Holborn (Chancery Lane Station) and 5 mins. by bus from King's Cross.)

FIRST-CLASS RADIO COURSES . .

GET A CERTIFICATE!

QUALIFY AT HOME—IN SPARE TIME

After brief, intensely interesting study—undertaken at home in your spare time—YOU can secure your professional qualification. Prepare for YOUR share in the post-war boom in Radio. Let us show you how!

FREE GUIDE

The New Free Guide contains 132 pages of information of the greatest importance to those seeking such successful-earning qualifications as A.M.Bric.I.R.E., City and Guilds Final Radio, P.M.G. Radio Amateurs, Exams., Gen. Cert. of Educ., London B.Sc. (Eng.), A.M.I.P.E., A.M.I.Mech.E., Draughtsmanship (all branches), etc., together with particulars of our remarkable Guarantee of

SUCCESS OR NO FEE

Write now for your copy of this invaluable publication. It may well prove to be the turning point in your career.

FOUNDED 1885—OVER
150,000 SUCCESSSES

NATIONAL INSTITUTE OF
ENGINEERING

(Dept. 461), 148, HOLBORN,
LONDON, E.C.1



Don't scrap that failing car battery or radio cell. Try RENEWBAT conditioner. Works like a charm. Simple and safe to use. Full instructions. Car size 3/-, p.p. 6d.; Radio size, 1/9.

CHAMPION PRODUCTS,
43, Uplands Way, London, N.21.
Phone: LAB 4457

Introducing the:—



**TYANA TRIPLE
THREE**
MAKE SOLDERING
A PLEASURE
SMALL


SOLDERING IRON
Complete with detachable BENCH STAND 19/6
The smallest high-power soldering iron. Length only 8 1/2"; adjustable long bit dia. 3/16"; mains voltages 100/110, 200/220, 230/250.
The "STANDARD" Popular Soldering Iron now reduced to 14/11.
Replacement Elements and Bits for both types always available.

KENROY LIMITED,
152/297 UPPER ST.,
ISLINGTON, LONDON,
N.1.
Telephone: Canonbury 4905-4663

Reg. Design No. 867801

TELETRON SUPER INDUCTOR COILS WITH MINIATURE DUST CORES

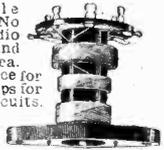TYPE HAN.—Triple wound for Xtal diodes. No over lap. Ideal Radio "Head" for Recording and Quality Amplifiers. 3/- ea. Coils of guaranteed performance for every purpose. 3d. stamps for full range, data and circuits.



THE TELETRON CO.,
266, Nightingale Rd., London, N.9.

SPARKS' DATA SHEETS

Constructional Sheets of Guaranteed and Tested Radio Designs
LO 31. 2-Valve Portable M.L. waves.
LO 15. 2-Valve All-dry 13-2,000 mc. Receiver.
LO 21. 3-Valve All-dry T.R.F. M.L. waves.
LO 27. 4-Valve All-dry All-wave Superhet.
LO 30. 2-Valve All-dry M.L. wave Superhet.
LO 31. 3-Valve version of above.
LO 31. 4-Valve T.R.F. version of 30 and 31.
LO 33. 4-Valve Superhet M.L. Portable.
LO 18. 2-Valve Plus Rect. A.C. D.C. M.L.
LO 33. An A.C. only version of the above.
LO 14. 3-V Plus Rect. T.R.F. A.C. D.C. M.L.
LO 32. An A.C. only version of the 14.
LO 17. A.C. D.C. 3-V Plus Rect. Portable. M.L. waves self-contained aerial.
LO 22. 4-Valve Plus Rect. A.C. D.C. All-wave Superhet.

AMPLIFIERS

Wide range of Designs available.
FULL-SIZE DATA SHEETS FOR ABOVE WITH DETAILED DESCRIPTIVE INSTRUCTIONS, ETC.
ATL 2/8, excepting LO 17 and 22, which are 3/-; and LO 11, 3 3. All Plus 2/d. stamp.
For My Latest List giving full details of above and other designs send 2/d. stamp.

COMPONENTS AND DRILLED CHASSIS SUPPLIED

L. ORMOND SPARKS (P.)
8, COURT ROAD, SWANAGE, DORSET.
(Note New Address)

AMPLIFIER DESIGN

5.—UNTUNED AMPLIFIERS—CONTINUED

By R. Hindle

(Continued from page 396 July issue)

AS a matter of fact, a number of such curves are given on the same graph; each curve is for a different grid voltage, but along any particular curve the grid voltage is constant. If the valves were perfect

these lines would be perfectly straight and the "curves" for different grid voltages in equal steps (say each curve is for a grid voltage of 1 volt different from its neighbour) would be parallel and equally spaced. Such idealised curves for a fictitious perfect valve are shown in Fig. 20, for $E_g=0$ volts to $E_g=-9$ volts in steps of one volt. Supposing the anode load is $50\text{ K}\Omega$ and the H.T. applied is 250 volts. Now if 250 volts appeared actually at the anode of the valve (Fig. 20b) there must be no current flowing because there is no voltage drop in the anode load, so the first point of the resistance graph, which is being superimposed on the anode volts/anode current graph, is for $E_a=250$ volts and $I_a=0$ mA. At the other extreme, if the whole 250 volts appeared across the load, so that, in effect, the valve was a short circuit, there would be 0 volts at the anode and the current flowing would be, by Ohm's Law, $\frac{E}{R}=5$ mA. The second point to plot on the

graph is, therefore, for $E_a=0$ and $I_a=5$ mA. These two points are A and B respectively on Fig. 20a, and the line joining them is called the load line for $50\text{ K}\Omega$. The valve, working with such a load, must always operate according to a point resting along this line. When a signal is applied to the grid the operation of the valve will carry it along the load line between the extremes represented by the voltage of the signal. The requirement for distortionless amplification is that for a certain slight change in grid voltage there must always be the same change in anode current, and this is clearly the case with this imaginary valve because the various curves are parallel and at equal distances and anywhere along the load line the distance between two adjacent "curves" along the load line extends over an equal part of the E_a volts scale. Load lines for different anode loads will all start from the same point on the baseline (assuming that the H.T. voltage remains constant), i.e., at the point representing the H.T. supply, 250 volts in our example, but they will run to different points on the I_a scale because the maximum current for the condition of zero volts at the valve anode will vary. For instance, a load of $25\text{ K}\Omega$ permits a maximum current of 10 mA and so the load line is AC; for $100\text{ K}\Omega$ the maximum current is 2½ mA and the load line is AD. The greater the load the less steep the load line. On all these lines distortionless amplification is possible and so the obvious inference is to use the bigger load if the maximum amplification is required.

But, to leave the world of imagination and to get down to the practical facts, the real valve curves are not at all like Fig. 20; they are curved and they are

A Series of Articles Dealing with the Theoretical Considerations of Amplifier Design, and Containing at a Later Stage Constructional Details of Various Types of Amplifier.

somewhat irregularly spaced and hence the distortion to which valves are prone. Fig. 21 gives the actual curves of a triode. They would be curved over also at the upper end if they were extended so far, but the

makers set a limit to the amount of power that may be dissipated at the anode. In this case it is 1.5 watts, which means that the H.T. power (volts multiplied by mA) consumed must not be more than this figure. The dotted curve on the characteristic curves indicates this maximum and there is little point in drawing the curve farther into the realms that may not be used. On this set of curves is superimposed the load lines for the three load resistance values considered for the idealised valve, i.e., $25\text{ K}\Omega$, $50\text{ K}\Omega$ and $100\text{ K}\Omega$. Now the load lines do not cross the curves at exactly regular intervals. The $25\text{ K}\Omega$ load is not too bad, however, over part of its length, though at its extremes the spacing becomes erratic. The region between -2 volts and -6 volts gives reasonably constant spacing between the curves and the 4 volts grid swing gives an anode voltage swing of from about 135 volts to 205 volts (read from the base scale corresponding with the two extreme points along the load line over which the valve is worked).

Input 4 volts, output 70 volts, amplification $\frac{70}{4}=17\frac{1}{2}$ times. That is easy!

The $50\text{ K}\Omega$ load line will allow an equal input signal, but the anode now swings from 110 volts to 190 volts; now input 4 volts, output 80 volts amplification 20 times—better than the smaller load. How about a larger load still, then? According to the $100\text{ K}\Omega$ load line the same input swing takes the

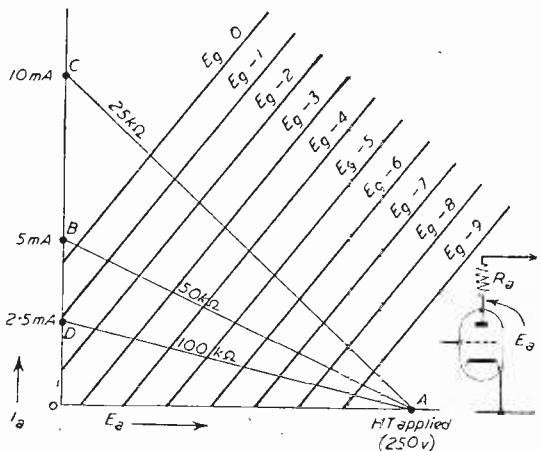


Fig. 20.—Load lines of an imaginary perfect triode.

anode volts over the range 85 volts to 180 volts, a signal peak-to-peak of 95 volts, making the gain $\mu =$ nearly 24 times. This is better still, but notice that the load line is getting near to the curved ends of the characteristic, where the spacing is less regular, indicating that the proportion of distortion is on the increase, and the load line for 250 K Ω also shown is even worse so far as distortion is concerned. If, however, the input signal is less than that already considered the distortion caused by the curvature

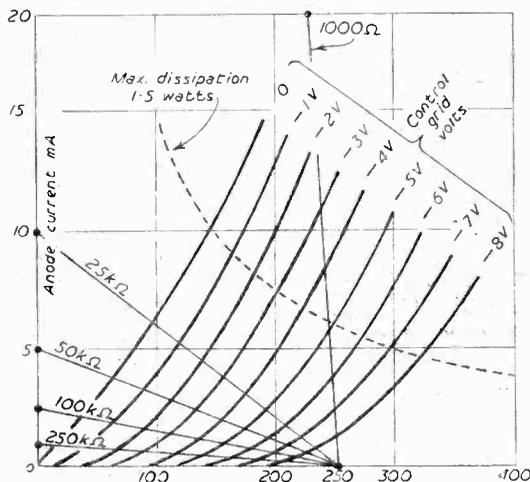


Fig. 21.—Load lines of a triode.

will be proportionally less. The rule is, then, that the load can be made larger, and consequently a greater amplification obtained, for a given degree of distortion for a smaller input signal.

Grid Current

In considering the permissible grid voltage swing the risk of grid current has to be borne in mind. Electrons that are attracted to the grid of the valve have to pass through the grid resistor, in which process they will produce a voltage that will upset the working point of the valve and so cause distortion. That is quite generally known, but what is not always realised is that grid current can flow before the grid goes positive. For instance, in the case of an ordinary triode such as is now being considered grid current begins to flow when the grid is -1 volt, and consequently the input signal must not be allowed to drive the grid more positive than this point.

Small Load

Now consider the other extreme—the reduction of the load to a smaller value. It will be seen that as the load is decreased the load line takes on a steeper and steeper angle, cutting the grid volt curves more and more obliquely. Now if the spacing of the curves is varying, and we know that such is the case, by cutting the curves more obliquely the variation in spacing is more and more accentuated and so distortion becomes worse and worse. Another effect is that, to keep below the maximum permitted dissipation line the range of grid voltage permissible becomes more restricted for the H.T. voltage assumed. For a load

of 1,000 ohms, as will be seen from Fig. 21, the grid voltage has to be kept more negative than -5 volts with 250 volts H.T. to avoid the maximum dissipation line and the erratic spacing of intersections with the grid voltage curves indicates a high degree of distortion.

To sum up the triode case, therefore, the optimum load is the load represented by a load line drawn from the applied H.T. voltage and at an incline such as to cut the curves as near as possible at right angles. The value of the load is calculated by observing the current indicated on the Ia axis where the load line cuts the Ia axis. Then by Ohm's Law $R = E.I.$, i.e., H.T. voltage multiplied by Ia (multiplied by 1,000 because Ia is measured in mA). The load can be made somewhat larger than this optimum with an increase in gain, but if made much larger the input signal must be kept small or else the H.T. supply must be increased to avoid undue distortion. On the other hand, if the load is made less than optimum the gain will be reduced and if much smaller the degree of distortion will be seriously increased. Generally, the anode load of a triode should not be less than three times r_a as specified by the valve makers.

Pentode

Now consider similarly a pentode, for which the equivalent curves are given in Fig. 22. The same considerations apply, i.e., to avoid distortion the load line must cut the curves for the range over which the grid is to swing so that they are as near as possible equidistant. We already know that the pentode will not accept so great a grid signal as the triode without serious distortion, and these curves bear out this fact. The optimum load will be represented by the lowest grid voltage reached by the signal input just above the curved foot. For instance, an anode load of 100 K Ω will allow the grid to swing to about -2.5 volts without a great deal of distortion. Increasing the load increases the distortion and requires a reduction in input signal for equally tolerable results: on the other hand, decreasing the load actually decreases the distortion at the expense of gain. In fact, because the curves are nearly horizontal the load line has to be practically vertical, indicating a zero load, to cut the curves at right angles and so to give the minimum distortion. At best, however, a pentode can accept only a small input unless considerable distortion can be tolerated.

Practical Design Considerations

It will be remembered from the earlier discussion that the shunt capacitance across the load resistance is the stray capacitance from anode to cathode (C_{ak}) of the amplifying valve plus the input capacitance of the following valve (C_{gk} : this is the "cold" input capacitance, i.e., that before power is supplied to the valve) plus the capacitance fed back from anode to grid of the following valve by virtue of the Miller Effect, and this fed back component amounts to $(\mu - 1) C_{ag}$: these are the inter-electrode capacitances, the electrodes involved being indicated by the little letters, g being grid, a being anode and k being cathode.

In Table I are given the values of inter-electrode capacitances of some valves likely to be used for resistance coupled amplification. The total shunt capacitances are given also, assuming a gain of 12

(Continued on page 489.)

ALPHA FOR SETS OF VALVES

10 EF50 Valves (Ex New Units), 45/- per set.
 6K93, 6E73, 6V75, 6V83, 6Z45 8/- per set.
 1R5, 1S5, 1T4, 1S4 or (3S4 or 3V4), 30/- per set.
 757, 787, 7C6, 7C5, 7Y4, 42/- per set.
 ECH42, EF41, EBC41, EL41, EZ40, 50/- per set.
 UCH42, UF41, UB041, UL41, UY41, 50/- per set.
 12K8, 12K7, 12Q7, 35Z4, 35L6 or 50L6, 37/6 per set.

CHASSIS

Aluminium, un drilled, reinforced corners, available in following sizes: 6in. x 1in. x 2 1/2in., 4/6 ea. 8in. x 6in. x 2 1/2in., 6/3 ea. 10 in. x 7 1/2in. x 2 1/2in., 7/3 ea. 12in. x 8in. x 2 1/2in., 8/6 ea. 14in. x 8in. x 2 1/2in., 9/6 ea. 16in. x 9in. x 2 1/2in., 12/- ea. All air four sided type suitable for amplifiers, radio receivers, etc., etc.

LINE CORD

2 amp. 3 core ... 1 1/4 d.
 3 amp. 4 core ... 1 6/8 d.

ELAC 4in. x 7in. ELLIPTICAL TYPE SPEAKER COMPLETE WITH OUTPUT TRANSFORMER, 19/6 ea.

HAND MICROPHONE BY "REGENT"

complete with screened lead and plus Crystal insert, nickel chrome plated head, listed at 2 kns. Our price, 21/- each.

HEATER TRANSFORMERS

230 v. Input 2 volt. 5 amp. ... 4/6
 230 v. Input 2 volt. 3.0 amp. ... 7/9
 230 v. Input 4 volt. 1.5 amp. ... 5/-
 230 v. Input 4 volt. 3.0 amp. ... 10/-
 230 v. Input 5 volt. 2.0 amp. ... 10/-
 230 v. Input 6.3 volt. 2.0 amp. ... 5/-
 230 v. Input 6.3 volt. 1.5 amp. ... 6/-
 230 v. Input 6.3 volt. 3.0 amp. ... 9/-
 230 v. Input 12 volt. 7.5 amp. ... 5/-
 230 v. Input 6.3 volt. 1.5 amp. and 6 volt. 2 amp. ... 14/3

HEADPHONES

C.L.R. Low resistance, 120Ω 7/6 pr.
 C.H.R. High resistance ... 11/- 1/4.
 American lightweight 'phones, 1,200Ω each earpiece ... 13/6 pr.
 Headband, wide type ... 1/9 ea.
CRYSTAL DIODES, 2 for 2/-.

SUMMER VALVE OFFER
 EFG, 8/- EL2, 6/- S130, 5/-
 220 IPT, 6/- ML13C, 2/6
 MHL4, 5/- GA6, 3/9 7D8, 6/9.

VALVES GUARANTEED NEW AND BOXED

0Z4	6/-	6H6G	6/8	8/6	6H7M	9/-	PY2	11/6	
1A3GT	6/6	6H6	4/6	807	8/3	P1148	2/-	PY80	11/6
1C5V4	8/-	6H7A	5/-	8132	2/9	RB44	11/-	PY81	11/6
1L4	7/6	6J5GT	5/6	954	2/6	EK42	11/6	QPT2B	7/6
1K5	7/6	6J5M	6/6	955	4/0	EK41	14/6	QPT21	7/6
1R4	7/6	6J7A	6/6	956	3/6	ECH12	10/6	TP22	9/-
1R5	7/6	6K7A	5/6	9001	6/-	EK135	13/-	Y22	8/-
1T4	7/6	6K7M	6/6	9002	6/-	EB180	11/6	Y81	10/-
1U5	10/-	6K7GT	6/6	9004	6/-	EB41	11/-	Y84	9/6
220VSG	6/6	6K80	8/6	9006	6/-	EK180	11/6	Y84	11/6
2X2	5/-	6K9GT	6/6	1001	11/-	EB26	6/6	YH42	12/6
3A4	6/-	6K9GT	9/-	1002	6/-	EK135	13/-	Y84	12/-
304 (N18)	8/6	6G6	8/6	1009	11/-	EB50	11/6	YV41	10/-
306	5/-	6L6G	9/6	10D11	11/-	EZ40	12/-	YF30	6/6
384	8/6	6L7A	7/6	10P14	11/-	EM31	9/-	EB34	2/6
3V4	8/-	6N7	7/6	12A6	6/6	EY91	9/-	EB67B	7/6
401	6/-	6R7A	9/-	12A07	9/-	EY31	13/6	EP41	3/6
42	8/-	6R7GT	9/-	12A77	9/6	EZ41	11/-	EK32	8/6
504G (N18)	8/6	6A7GT	8/6	12A8	8/-	EY13	9/-	EP41	3/6
5V3GT	8/-	6B07	7/6	12H6	5/-	FWH, 500	10/6	EP50	6/-
5Z3	6/6	6B17	6/-	12L5	6/-	HD14	10/-	EP50	8/6
5Z4G	6/6	6B37A	8/6	12K7	9/-	H63	7/6	EA50	2/-
6A7	9/6	6B67	8/6	12K8GT	9/-	HD18	8/-	YR16	4/-
6A84	9/6	6B87	8/6	12K8G7	9/6	EZ41	11/-	EK32	8/6
6A84GT	10/6	6B87GT	9/-	12K87	5/6	HE11D	8/-	EP8	6/6
6A07	6/6	6B97	9/-	12S17	7/6	KT2	5/-	EP54	7/-
6A45	7/6	6B97	8/-	12K87	7/6	KT61	10/6	EP52	5/9
6A45 7	8/6	6V6G	7/6	12R87	7/6	KT74	8/-	YR16	3/9
6A45 7	8/6	6V6GT	7/6	12K97	7/6	KT78	10/-	YR150	3/9
6A76	9/-	6X4	8/-	12Q7	8/6	KT561	7/6	EL32	8/-
6A45 9	8/6	6X3G	7/6	20D1	10/6	KT263	6/6	VP23	8/-
6B8G	9/-	7B7	8/6	25A6G	9/-	MH4	5/6	YU39	8/6
6B8G	9/-	7C3	8/6	25L6GT	8/6	MT8	5/6	YU11	3/6
6B8G 6	9/-	7C6	8/6	25Z4G	9/-	OM9	9/-	YU120A	3/6
6C4	8/-	7B7	8/6	25Z6GT	8/6	PE25	8/-	YU133	3/6
6C5GT	7/6	7B7	8/6	35Z4GT	8/6	PE26	8/6	YU77	8/6
6C6	6/6	77	8/-	35L6GT	8/6	PE220A	4/9	W81	10/-
6C3	5/-	787	8/6	ATP4	6/6	PL33	9/6	X65	10/-
6C3	5/-	787	8/6	AC6PEN	5/6	PL83	13/-	X66	11/6
6B6G	7/6	7Y4	8/6	CV96	6/-	PL82	11/6	Y63	9/-
6F8G	7/-	75	10/-	CV71	11/-	PL81	13/6	Y61	9/-

A SPECIAL PURCHASE OF TUNGSRAM VALVES ENABLES US TO OFFER THE FOLLOWING:

25Z5	8/-	6V6G	9/-	AS4125	11/6	25Y5	9/-	L4210	6/-
HP401	11/6	6V6GT	9/-	EPF11	6/3	6174	8/6	8120	5/9
6J7G	8/6	80	9/-	PV30	9/-	LP220	9/-	HR210	5/9

WHEN ORDERING PLEASE QUOTE "DEPT. P.W."

CONDENSERS

The following is a selection from our stocks of manufacturers' surplus condensers, all by well-known makers.

Aluminium Can types, Clip fixing									
4-8 mfd. 450 v. ...	4/-								
8-16 mfd. 450 v. ...	4/-								
8-24 mfd. 450 v. ...	3/-								
8-32 mfd. 475 v. ...	3/9								
12-4 mfd. 450 v. ...	2/-								
16 mfd. 450 v. ...	3/-								
16-8 mfd. 350 v. ...	4/-								
16-16 mfd. 350 v. ...	3/3								
20-20 mfd. 500 v. ...	4/9								
24 mfd. 450 v. ...	2/9								
25-16 mfd. 350 v. ...	3/6								
25-8 mfd. 350 v. ...	3/6								
32-16 mfd. 350 v. ...	4/6								
32-32 mfd. 450 v. ...	6/11								
32-32 8 mfd. 350 v. ...	5/6								
32-32 mfd. 350 v. 25 mA.									
25 v. ...	5/9								
16 mfd. 350 v. ...	2/-								

(B.R. Range)

BR.530 16 mfd. 500 v. ...	ea. 7/9
BR.1650 16 mfd. ...	ea. 3/3
BR.2050 20 mfd. 500 v. ...	ea. 3/6
8-8 mfd. 500 v. ...	ea. 4/-
BR.501 50 mfd. 12 v. ...	ea. 1/9

Midget Metal Types

2 mfd. 350 v. ...	1/9
8 mfd. 350 v. ...	1/1
8-8 mfd. 350 v. ...	3/-
8-8 mfd. 450 v. ...	4/-
16 mfd. 350 v. ...	2/9
16-8 mfd. 450 v. ...	4/-
16-16 mfd. 450 v. ...	4/6
16-24 mfd. 350 v. ...	4/9
24 mfd. 350 v. ...	2/9
32 mfd. 350 v. ...	1/9
32-32 mfd. 350 v. ...	4/9
50 mfd. 12 v. ...	1/9

Wire ended Types

5 mfd. 450 v. Cardboard	1/11
30 mfd. 450 v. ...	3/9

Bias Condensers

Tuf ended metal types									
12 mfd. 50 v. ...	1/-								
25 mfd. 25 v. ...	1/3								
50 mfd. 12 v. ...	1/-								
50 mfd. 50 v. ...	2/6								
100 mfd. 12 v. ...	1/9								
100 mfd. 25 v. ...	1/9								

Wire ended Types, Cardboard covered

25 mfd. 25 v. ...	1/9
50 mfd. 12 v. ...	1/9
50 mfd. 50 v. ...	2/3

CHARGER TRANSFORMER, High Grade Wax Dipped 220/240 v. input, 6 and 12 v. 2 amp. output, 10/6 each.

FLEX CONNECTORS, 5 amp. size, 2 pin, 1/- ea.

NYLON DRIVE CORD, 25 yds. on Wooden Reel, Best quality, special price, 2/8 reel.

RADIO CRYSTALS, 1/6 doz.

ELECTRIC LIGHT CHECK METERS, 200-250 v. A.C. at 10 amps. Bakelite case, in very good condition, 15/-, D.P. 2/6.

PRE AMPLIFIER

Complete in every detail, co-axial plugs and supply leads. EF42 valve supplied. A modern unit by well-known maker—not ex-Government. Price 21/- ea.

GOLLARO AC37 GRAMOPHONE MOTORS

Special purchase once again enables us to offer this splendid unit, order yours now and make sure while stocks last. Gollaro AC37 Gram motor, complete with 10in. turntable, governor controlled to run at 78 r.p.m. Suitable for 100/125 v., 2SD/252 v.

46/- each.

plus 2/6 packing and post.

42in. EXPONENTIAL HORNS, 1 1/2in. fitting. These horns have a 28in. square flare, weigh approx. 25 lbs., and measure 44in. from top to bottom. 22/10 6, carriage 7/6.

VITAVO PRESSURE UNITS, Heavy Duty P.M. 20 watts. To fit the above horns. Brand new. £4/9/6, carriage 6/-.

ION TRAPS, Type 1D6, 2/6 ea. OUTPUT TRANSFORMER, Standard Pentode, 2/9 ea.

I.F. TRANSFORMERS, 465 kc/s, 6/3 each.

MAINS TRANSFORMERS 3-way mounting type

MT1—Primary 0-210-230-250 v. Secondary 250-0-250 v. 80 mA 4 taps, 4 v., 2 amps with taps at 4 v. on filament winding. Price, 17/6 each.

MT2—Primary 0-210-230-250. Secondary 250-0-250 v. 80 mA 4.3 v., 4 amps, 5 v., 2 amps. Both filament windings tapped 4 v. Price 17/6 each.

METAL RECTIFIERS

12 volt 1 amp. ...	1/6 ea.
2 volt 1 amp. ...	3/6 ea.
250 volt 45 mA. ...	6/9 ea.
250 volt 75 mA. ...	7/6 ea.
300 volt 60 mA. ...	7/6 ea.
Full Wave 12 volt 1 amp. ...	4/9 ea.
12 volt 2 amp. ...	8/6 ea.
12 volt 3 amp. ...	13/6 ea.

HALF WAVE 1/2 A PENCIL RECTIFIERS

K325 665 v. ...	4/6
K340 1 kV. ...	6/-
K345 1 140 kV. ...	7/9
K350 1 260 kV. ...	8/3
K360 1 5 kV. ...	9/6
K3, B90 2 550 kV. ...	14/-

STANDARD S.T.C. RECTIFIERS

RM1 125 v. 60 mA. ...	3/6 ea.
RM2 125 v. 80 mA. ...	4/3 ea.
RM3 125 v. 100 mA. ...	5/- ea.
RM5 250 v. 250 mA. ...	18/- ea.

THE "COMPACT" TELEVISION AERIAL

By Antiferreus, Ltd., type CD4, listed at 50/-, our price 18/6.

★ SEND FOR OUR CATALOGUE


(6d. in stamps.)

All components for "Modern Reflex Receiver" July issue listed.

TERMS: Cash with order or C.O.D. Postage and Packing charges extra as follows: Orders value 10/- add 5/-; 20/- add 1/-; 40/- add 1/6; 60/- add 2/- unless otherwise stated. Minimum C.O.D. fee and postage, 2/3. MAIL ORDER ONLY.

ALPHA RADIO SUPPLY CO.

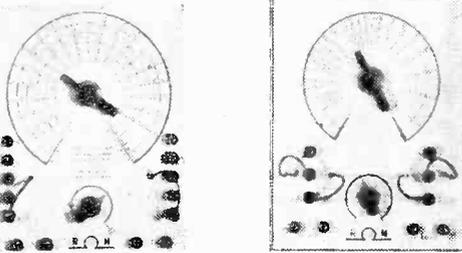5/6 VINCES CHAMBERS, VICTORIA SQUARE, LEEDS 1.



DESIGNED FOR YOU!

NO additional

- power supply
 - energising
 - tone source
 - calibrating
- or
● metal work
- are required with any of these Kits

EACH KIT IS A COMPLETE WORKING INSTRUMENT ON ASSEMBLY

Only the simplest of tools are required for assembling and ample diagrams with step by step instructions are supplied in each case.

All Kits operate from a standard 1½ volt torch cell.

SPOT FREQUENCY SIGNAL GENERATOR

Fully screened in steel case 4in. x 4in. x 3in. Provides modulated signal on six switched spot frequencies, three on long waves and three on medium.

35/- P. & P. 1/6

465 Kc/s I.F. ALIGNER

Fully variable tuning from 445 to 485 Kc/s. All other details as in Sig. Gen. above.

17/6 P. & P. 1/6

R. M. TWIN MULTI-OHMER

Resistance substitution set with both fixed and variable outlets, covering all useful values up to 7 megohms.

25/- P. & P. 1/6

RES/CAP. BRIDGE

Six ranges. 500 pF to 50 mfd. 10 ohms to 5 megohms. For use with any type 'phones.

31/6 P. & P. 1/6

INDUCTANCE BRIDGE

Five ranges. 50 micro/Hy. to 100 Hy. For use with any type 'phones. As illustrated above.

42/6 P. & P. 1/6

AUDIO BRIDGE

Three ranges. 40 to 16,000 cycles. As illustrated above.

38/6 P. & P. 1/6

Stamp for illustrated leaflets. Cash with order or C.O.D. Overseas 3/6 extra.

Our research department has the following for disposal: Crystal controlled Sig. Gen., with Crystal Oven, all complete. Portable sub-standard meters. Details on request.

RADIO MAIL

DEPT. F.
4-6, RALEIGH STREET,
NOTTINGHAM.

5000

25 PF AIR SPACED CERAMIC TRIMMERS IN ORIGINAL BOXES. LARGE OR SMALL

QUANTITIES SUPPLIED AT CLEARANCE PRICES.

P. K. Utilities

RALEIGH STREET
NOTTINGHAM

MONEY BACK GUARANTEE **DUKE & Co** Tele: GRA 6677 CWO COD
621 ROMFORD RD. LONDON. E.12.

T.V. TUBES. GUARANTEED 3 MONTHS.

£5 12in. £3 9in. Most makes, no E.M.I. Picture shown to callers. Not Ex-W.D. Carriage and insurance 15/6 extra.

AMPLIFIERS

57 6. A.C. or A.C./D.C. 3 valve, ideal for pick-ups or microphone. watts output. Chassis 6in. x 4in. Post 2/6.

77 6. 4 valves and rec. push-pull type. Approx 7 watts output. A.C. or A.C./D.C. Chassis 9in. x 4in. Post 2/6. Both these amplifiers are ready for use with the addition of a speaker.

SPOTLIGHTS.—8/9. Butlers, new but ex-W.D. 7in. dia. 6in. deep. These lights are similar to those sold for £3-£5. but finished Black. The lamp fitting is of the pre-focus type. This can be easily changed by fitting a holder from side light (1/9). Also a chrome screw is required to cover hole in centre of glass. Post 1/3.

BULBS for above. 6 volt 36 watt. 12 volt 48 watt. 4/6 each. SIDE LIGHTS.—1/9. Fitted with infra-red glass, but easily changed for clear or red. Post 9d.

CRYSTALS GERMANIUM.—1/9. With 3 FREE circuits. Brand new by B.T.H. Long wire ends. Post 6d.

TRANSFORMERS.—Microphone trans. 2/9. Ex-W.D., new condition in fully shielded case. Post 9d. Pick-up trans. 2/9. new ex-W.D. unused. E.M.I. type. Fully shielded. Post 1/-.

ROTARY CONVERTER.—12 6. Power unit type. 523. In 2iv. out 220v. at 50 m/A. Carriage 2 6.

DUNLOPILLO ex-coach seats. 37/6. 34in. x 16in. x 4in. thick. complete with back. Moquette or hide covered. Carriage 4 6.

DUNLOPILLO Luxury type complete seat. 37/6. 34in. x 16in. back 28in. high. Carriage 1 6.

RECTIFIERS

3 9. Brand new selenium. Approx. rating 180v., 40 m/A. Post 6d. 8 9 T.V. type. 300v. 25j m/A. Salvage, guaranteed. Post 1 3. 12 9. New T.V. type. 300v. 250 m/A. Post 1 3.

H.T. BATTERIES. 3 9. 60v. 90v. portable. 7/9. 90v. x 1 1/2 9. Post 1 9 each. L.T. 4 1/2. 1 8. Post 6d.

ACCUMULATORS. 2v. 45 ampere 7 3. Post 2 3. *Send Stamp for 1954 Catalogue.*

SOUND MASTER SERVICE

The Sound Master is an entirely new Portable Tape Recorder which has been produced especially for the Home Constructor by the designer of the famous View Master Telescope.

Full constructional details are now available.

INSTRUCTION ENVELOPE, 6 3d. post free.

WRITE NOW for our fully detailed price list. We carry full stocks of all items needed for the Sound Master and can offer a

RETURN OF POST SERVICE. FULL HIRE PURCHASE FACILITIES AVAILABLE on complete or part kits.

WATTS RADIO

(Weybridge), LTD.

8, BAKER STREET, WEYBRIDGE, SURREY

A REALLY SMALL RADIO RECEIVER

This radio receiver, although as small in size as a matchbox, gives loud, clear reception of the BBC Home, Light and Third Programmes on the medium waveband, about 180-550 metres. The set also tunes the Light Programme on the long waves, 1500 metres. No catwhiskers, valves or batteries are required, and the receiver works off a short indoor aerial in many districts.

PRICE **9/-** POSTAGE **3d.** EXTRA

This offer applies only to Gt. Britain and Northern Ireland.

SWIFT RADIO

-102, BATH RD., WILLSBRIDGE, Nr. BRISTOL

times in the case of a triode and 80 times in the case of a pentode, the following valve in each case being assumed to be a similar valve (or in the case of the 12AU7 the second half of the same valve; the two figures given for Cak for this valve are for the two halves of one valve. In all other respects the two halves are identical).

Wiring and component strays, apart from the valve itself, of 15 pF, a likely figure, are taken in assessing the total shunt capacitance. The superiority of the pentode over the triode in this respect is clearly indicated, and also the improvement made in new

upon previously from the point of view of load lines and so in practical design the value indicated by the load lines would be accepted, knowing that the frequency characteristic will actually be better than that stipulated.

It is not always desirable, of course, to extend the frequency characteristic beyond that which can be usefully employed. A case in point is the design of a feedback amplifier such as will be coming up for consideration later. Often such an amplifier can be unstable at a frequency above audibility and this can cause havoc with the fidelity of the amplifier. The

cure is to reduce the gain at those high and unwanted frequencies. If the stray capacitances are found to be too small to give the necessary restriction in range with the chosen size of load extra capacitance can be added across the load to give the required compensation.

Let there be given, however, one further reminder that Req, as determined above, is not only the anode load resistor, but that resistor in parallel with the grid resistor of the following valve. The grid resistor will very likely be about 1 MΩ if the following valve is an amplifier and not a power valve. So, having decided from a load line analysis what size of load the valve would prefer and having checked from a consideration

of strays, in relation to the maximum frequency required, the highest value of resistive load permissible, the choice will be for the smaller of the values indicated by these two methods. For instance, an effective load of 100 KΩ was found practicable for the triode, but any increase was seen from the load line to introduce distortion. Now it is found that an anode load up to 230 KΩ is permissible from the stray capacitance point of view, but the smaller figure 100 KΩ is chosen. The 1 MΩ

TABLE 1
Table showing magnitude of stray capacitances in a R.C. amplifier.

	6J5	12AU7	6BR7		6SJ7
	Octal Triode	B9A Double Triode	B9A Triode Connected Pentode Connected		Octal Pentode
Cgk	3.4 pF	1.6 pF	3.2 pF		6 pF
Cak	3.6	.5 .35	6.7		4
Cga	3.4	1.5	1.1		.005
Cga x valve gain	40.8	18	13.2		.8
Total Valve Shunt C (Cgk Cak Miller Effect)	47.8	20.1	23.1		9.05
Add strays external to valve, say, about	15 pF.				
Total shunt C	63 pF	35 pF	38 pF		24 pF
Reactance of Strays at 20 Kc/s	120 KΩ	230 KΩ	200 KΩ		330 KΩ
					270 KΩ

Miller fed back capacitance assumes gain for triodes to be 12 and for pentodes to be 80.

miniature valves compared with the octal variety; obviously, the small modern valve is preferable and should be used wherever possible. Using the figures in this table, the maximum permissible resistive load for a given upper frequency range can be worked out.

Consider now the design of an audio amplifier of which, let it be assumed, the load may be allowed to drop to .9 of the mid-frequency value at 10 Kc/s. As shown previously the load drops to .7 of maximum at the frequency at which the reactance of the total stray capacitances equals the resistance of the load Req (the anode load resistance RL in parallel with the grid resistance in the circuit of the following valve Rg) and it drops to .9 of maximum at half the frequency of equality. In the present case, therefore, the maximum resistance for Req is equal to the reactance of the strays at twice the stipulated upper frequency limit, i.e., 20 Kc/s. The reactance of the capacitance can be calculated by the standard formula

$$X_c = \frac{1}{2\pi fC}$$

but to ease matters, because it is one thing to know how to work out these things, but quite a different matter to make the calculations frequently, Table 2 has been prepared and the values required for the case now being considered are also presented in Table 1. The maximum permissible load Req for the stipulated frequency response is, then, a half of the reactance figure given in Table 1. These indicate permissible load resistors higher than those decided

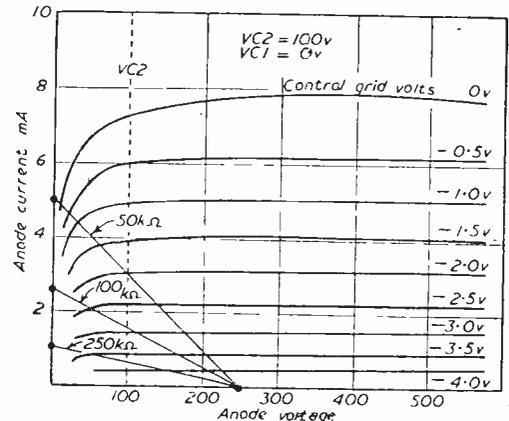


Fig. 22.—Load lines of a pentode.

grid resistor will have comparatively little effect in this case, and a 100 KΩ resistor will be used as anode load. This, in parallel with the 1 MΩ grid resistor, will give an actual load Req of 91 KΩ. In view of the normal tolerance in components of 20 per cent., we are not likely to lose any sleep over the difference between a load of 100 KΩ and 91 KΩ.

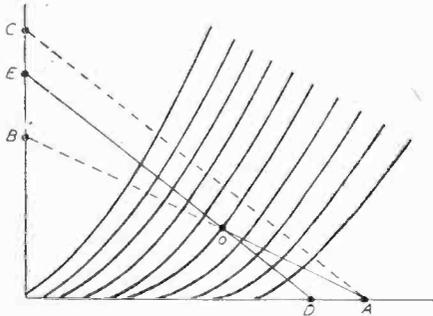


Fig. 23.—Triode load line allowing for differing D.C. and A.C. load.

There is a complication in the drawing of a load line that should, perhaps, be mentioned due to the fact that the coupling capacitance C_c , which has been conveniently forgotten at middle and upper frequencies so that R_{eq} has become R_L and R_g in parallel, does, in fact, isolate R_g from the H.T. supply point of view. This means that R_L alone must be considered when determining the initial working point of the valve before signal is applied. The correct procedure is first to draw the load line for the actual anode load resistor alone. The working point will be along this line. Fig. 23 shows this for the triode case and Fig. 24 for the pentode case, the load line being AB. Now the working point is so chosen that the grid can swing in each direction to follow the amplitude of signal fed to the valve, seeing that the requirements of linear amplification, i.e., that the load cuts the curves with reasonably equal spacing, are met. This working point is O. Now the load line for R_{eq} (R_L in parallel with R_g) is drawn, AC in the illustrations. Now through O is drawn a line parallel to AC, shown as DE, and this is the true working load line when the signal is applied. In actual fact, where R_g is large compared with R_L , this is not likely to be much different to the simpler method in result.

Practical Application of Valve Data

The reader may well be thinking how he can possibly work through this maze of design work when he wishes to build an amplifier. The truth of the matter is that in most cases he will not have to. Most amplifier requirements are more or less stereotyped, and standard design data can be used to provide short cuts. It is necessary, of course, to understand the foregoing theory so that the standard data can be

correctly used in appropriate cases and so that, in the cases where a divergence from standard is necessary, the correct steps to allow for the exceptional circumstances will be known.

Dynamic Curves

The method adopted by the valve makers is to determine the most suitable load resistances in normal circumstances and to redraw the curves allowing for these load resistors. The effect is, of course, to reduce the steepness of the Ia/Eg curve. These are known as the dynamic curves. In addition to the Ia/Eg curve the values of r_a , μ and g_m are plotted on these diagrams. There is nothing very magical about these curves, and the foregoing discussion will have made clear to the reader what problems have been faced in preparing them. In fact, the main curve is merely the plotting of the points of interception of the load line on the static curves with the curves for the various grid voltages.

Suitable Design

Perhaps the best way to bring out some further theoretical and practical points concerning resistance coupled amplifiers is to tackle the actual design and construction of an amplifier, starting with none too rigid a specification, but rather aiming at a unit of utility and versatility such as one would like to have about in the workshop to press into use whenever occasion arises and which might well form part of a more specialised piece of equipment, even a

TABLE 2
Table giving reactance of capacitances at higher frequency limit.

	3 Mc/s	2 Mc/s	1 Mc/s	40 Kc/s	20 Kc/s	10 Kc/s	5 Kc/s
1 pF	53 KΩ	80 KΩ	160 KΩ	4 MΩ	8 MΩ	16 MΩ	32 MΩ
5	10.6 KΩ	16 KΩ	32 KΩ	800 KΩ	1.6 MΩ	3.2 MΩ	6.4 MΩ
10	5.3 KΩ	8 KΩ	16 KΩ	400 KΩ	800 KΩ	1.6 MΩ	3.2 MΩ
20	2.7 KΩ	4 KΩ	8 KΩ	200 KΩ	400 KΩ	800 KΩ	1.6 MΩ
30	1.8 KΩ	2.7 KΩ	5.3 KΩ	135 KΩ	270 KΩ	530 KΩ	1.1 MΩ
40	1.3 KΩ	2 KΩ	4 KΩ	100 KΩ	200 KΩ	400 KΩ	800 KΩ
50	1,060 Ω	1.6 KΩ	3.2 KΩ	80 KΩ	160 KΩ	320 KΩ	640 KΩ
60	880 Ω	1,350 Ω	2,650 Ω	67 KΩ	135 KΩ	265 KΩ	533 KΩ
70	750 Ω	1,150 Ω	2,300 Ω	57 KΩ	115 KΩ	230 KΩ	460 KΩ
100	530 Ω	800 Ω	1,600 Ω	40 KΩ	80 KΩ	160 KΩ	320 KΩ

complete receiver, at a later date.

Supposing that a gain of about 150 times is aimed at. This is rather more than is likely to be obtained from a single pentode in a reasonably stable wideband audio circuit and, in any case, it sets a nice problem in design for triode working.

(To be continued)


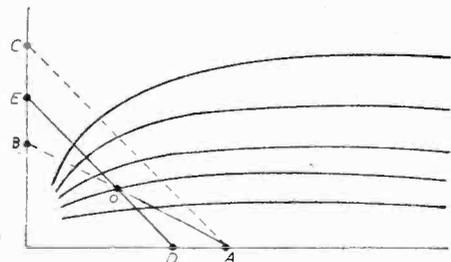


Fig. 24.—Pentode load line allowing for differing D.C. and A.C. load.

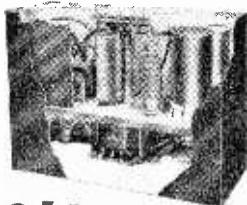

9/6 Post 2/-

VIBRATOR UNIT Complete in case—six-volt operation.

1/- Post 1/- for 5.

UNBREAKABLE GLASS PANELS

Size 10 1/2 x 9 1/2 in.—parcel of five panels 5/-

12/6

Post 1/-

CONSTRUCTORS PARCEL

Five valve superhet chassis—size 15 x 5 x 2 1/2 in. with three-waveband glass scale, pulley, driving head, etc.

Also **TABLE CABINET** Veneered and polished—takes the above chassis. 32/6. Post 2/6.

£9.10.0
Carr. 15/-

CONSOLE CABINET

Walnut veneered and polished with record space and uncut motor-board.

39/6

Post 3/6.

THREE-SPEED GRAM MOTOR


200-240 A.C. mains-operated, complete with turntable—plays 33, 45 and 78 r.p.m. records.

3/6

Post 1/-

CLOCK CASE

Veneered and polished—undrilled.

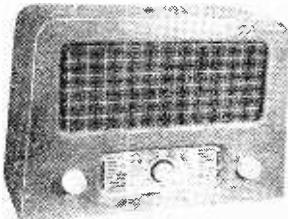

17/6

Post 2/6.

Excellent resin-covered cabinet—over-production by one of our very famous makers. Complete with three-colour scale and metal chassis. Suitable for battery or mains receiver. Size approx. 13 x 9 1/2 x 6 1/2 in. Limited quantity.

Mains Chassis—new working L. and M. mains superhet radio to fit this cabinet is available. Price £7 10/-. (Limited quantity only.)

— FREE THIS MONTH —

Customers spending one pound or more this month will receive a free copy of our constructional booklet, "The Stroller" (see last month for full details of this fine receiver). Booklet available separately price 2/6, refunded when parts purchased.

Elopec

STROLLER

PORTABLE BATTERY RADIO

ALSO CONTAINING DATA FOR CONVERSION TO THE PICNIC PLAYER

2/6

100 ft. Post free.

CONNECTING WIRE

P.V.C. covered in 100 ft. coils—most colours—four coils—different colours. 9/-



39/6


Carr. 3/6.
12" TELE-CABINET



Veneered and polished—with glass or perspex front.

9/6

Post 1/6.

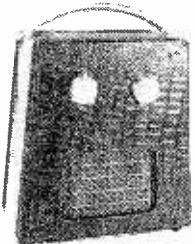

PORTABLE RADIO CABINET

With special crackle finish—with handle and back.

10/-

Carr. 3/6.



BAKELITE CABINET

Two tone with built-in handle. Note.—All have slight imperfections but these are hardly noticeable and will not affect the soundness of the set.

4/6

Post 1/-



ALTIMETER

(Imperfect). These contain aneroid barometer movement.

12/6

Post 2/6



CONSTRUCTORS PARCEL

Bakelite cabinet, complete with dial pointer, metal chassis and bak. Or with all the parts to make excellent T.R.F. Radio £3 10/-.

ELECTRONIC PRECISION EQUIPMENT, LTD.

Post orders should be addressed to Dept. 7, RUISLIP

Personal shoppers, however, should call at:

42-46, Windmill Hill,
Finsbury, Middx.
Phone: RUISLIP 5780
Half day, Wednesday.


152-3, Fleet Street, E.C.4,
Phone: CENTRAL 2833
Half day, Saturday.

29 Strand Green Road,
Finsbury Park, N.4.
Phone: ARCHWAY 1049
Half day, Thursday.

THE HAM'S SHOP Definitely the Cheapest Radio, Television and Electrical Shop in Great Britain.

70, KING STREET, BELFAST, NORTHERN IRELAND.
WALKIE TALKIES.—Type 18 as new. £6-10-0.
INDICATOR UNITS.—Type 62. £3-5-0, complete with Valves and Tube. Type 6A. £3-5-0.
TANNOY AMPLIFIERS.—60 watt. £5-10-0, less Valves. (Only a few left.)
CRYSTAL MONITORS. 6.6 each.
TUNING UNITS.—T.U.8 and 9. 12.6 each.
CONTROL UNITS.—On Chassis 6in. x 5in. x 1 1/2in. 2 pots. switches. knobs. etc. 2.6.
MAINS TRANSFORMERS.—350-0-350. 80 m.amp. 4v. 4 amp. 1v. 4 amp. 15/- each. (These are new and boxed and cannot be repeated.) 350-0-350. 6.3v. 4 amp. 5v. 3 amp. £1.
HOOK UPS.—300 m.amp. 3.8 each.
MIDGET OUTPUT TRANSFORMERS.—3.6 each. **MIKE TRANSFORMERS.** 2.8 each.
RESISTORS. with slider adjustment. 500 ohms. 50 watt. 1.3 each
MICROPHONE AND HEADPHONE SEES.—Breast. 10.6.
THROAT MIKES.—3.6 each. **CARBON MIKES.** 1.8 with Transformer. 4.6.
MOUSE KEY AND BUZZER SEES. 5-.
RELAYS.—625 ohms. 2.6.
NEON LAMPS.—1.6.
CUT-OUTS.—12 and 24v. 60 amp. 8.6.
ALUMINIUM RIVETS.—2.6 per lb. box.
SLOW MOTION TUNING DIALS.—With glass and metal frame. 5/- each.
SIGNAL LAMPS.—4 1/2in. plated reflector. 6ft. rubber covered lead. in wooden box with handle. 7.6.
WIRE STRIPPERS.—5-
REV. COIL SETS.—1.8 each only a few left.
BULGIN TEST PRODS.—4.6 per pair.
COILS.—32 gauge enamelled wire. 1.3 each.
COIL FORMERS.—6 x 1 1/2 and 6 x 1. 6d. each.
SOLDERING IRONS.—110 volt. 7.6 each.
METERS.—2.6 kv. 35/- ea. (Seasonal Offer.)
CHASSIS.—All types. Chassis for Simplex TV in heavy gauge aluminium. drilled. £1-2-6.
C.R. TUBES.—5CP1. £1 : VCR97. 35/- : 3BP1. 25/- . (Prices of other tubes on application.)
 (Look out for our 24in. Tube advert. in the near future.)
POLISHED BOSTON RODS.—9d. each.
A.C. MOTORS.—220v. suitable for Tape Recording. 15/- each.
SPEAKERS.—5in. 6in. and 8in. from 12/6 each.
THOUSANDS OF VALVES in Stock.—Price on application.
I.F. TRANSFORMERS.—45 K.C. 7/6 pair.
CHASSIS WITH COMPONENTS.—5/- each. (2/- carriage.)
THOUSANDS OF OTHER BARGAINS
PACKING AND CARRIAGE EXTRA. Please enclose S.A.E. with enquiries. DELIVERIES WITHIN 14 days.
ALWAYS AT YOUR SERVICE.

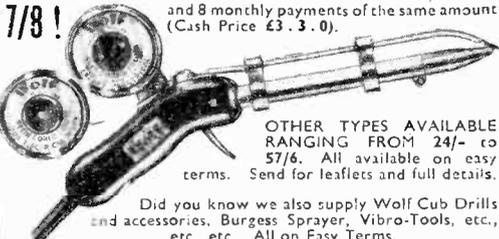THIS CAN BE YOURS FOR 7/8! and 8 monthly payments of the same amount (Cash Price £3.3.0).



OTHER TYPES AVAILABLE RANGING FROM 24/- to 57/6. All available on easy terms. Send for leaflets and full details.

Did you know we also supply Wolf Cub Drills and accessories. Burgess Sprayer, Vibro-Tools, etc., etc., etc. All on Easy Terms.

Let us have your enquiries. No Order too Small.

LAFCO COMPOUNDS, LTD. (Desk 49)
 3, Corbetts Passage, Rotherhithe New Road, London, S.E.16.
 Telephone: BERmondsey 4343.

REP HIGH GAIN COILS



Dual Range Miniature Crystal Set Coil 2/6 with Circuit

Dual Range Coil 4/- with 2 Mains and with Reaction 2 Battery Circuits

Matched Pair Dual Range T.R.F. Coils with Reaction 8/- pair With Battery and Mains Circuits

- All coils wound on low loss formers.
- Individually tested and guaranteed.
- Post 3d. on all orders.
- Trade supplied.

RADIO EXPERIMENTAL PRODUCTS, LTD.
 33, MUCH PARK ST., COVENTRY

COVENTRY TECHNICAL COLLEGE
 Session 1954-55
ELECTRONIC ENGINEERING

Applications invited for entry to 3 year full-time course commencing September, 1954, from those requiring comprehensive training to advanced level in **ELECTRONIC ENGINEERING**, qualifying for technical posts in radio, telecommunications, television and industrial electronics. Syllabus will cover requirements of C. & G., Brit.I.R.E., and I.E.E. examinations. Entry age 16 or over. Application forms and further information from **Principal, Technical College, The Butts, Coventry.**

THE POCKET LOUDSPEAKER SET

Using our clear drawings and instructions you can build a midjet loudspeaker receiver small enough to fit in the jacket pocket. This receiver is fully self-contained—no aerial, earth or external power supply being required. The midjet batteries used are of the new layer type specially produced by a famous British maker for this class of receiver. Only one single-gang midjet variable condenser is used for tuning, and the receiver requires no alignment. The midjet components chosen are current British production, not surplus or foreign. Instructions and Drawings, including Theoretical Circuit and Point-to-Point Wiring Diagram.

PRICE 3/6 POST FREE

This offer applies only to Gt. Britain, Irish Republic and Northern Ireland.

SWIFT RADIO
 102, BATH RD., WILLSBRIDGE, Nr. BRISTOL
 Orders by post only.

Build a really portable Tape Recorder with the New

"CHALLENGER"

Three Speed High Fidelity Tape Deck.

A first-class precision built deck. Beautifully finished in Old Gold stove enamel. Size only 11in. x 7 1/2in. Weight 6 lbs.


Britain's lowest priced Tape Deck.

Price £10.10.0.

Ask your dealer or send stamp for details to:—

E.W.A.,
 266, Warbreck Drive, Blackpool.

Fidelia

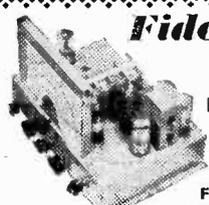

HAND BUILT RADIO UNITS

THE FIDELIA MAJOR 10

Hand built high quality radiogram chassis at economic price. 10 valve, model illustrated. £32-8-4, De-luxe 9 valve model £24-6-6, 7 valve £21-12-0, 6 valve £23-18-4

Technical data sheets free. Electro Acoustic Developments, 2, Amhurst Road, Teiscombe Cliffs, Sussex.

H.A.C. SHORT WAVE EQUIPMENT

Noted for over 18 years for . . . S.W. Receivers and Kits of Quality.

Improved designs with Denco coils :
 One-Valve Kit, Model "C" Price, 25/-
 Two " " " " " " " " 50/-

All kits complete with all components, accessories, and full instructions. Before ordering call and inspect a demonstration receiver, or send stamped, addressed envelope for descriptive catalogue.

"H.A.C." SHORT-WAVE PRODUCTS
 (Dept. TH), 11, Old Bond Street, London, W.1.

DESIGNING Oscilloscopes

A SHORT SERIES FOR THE
SERVICEMAN AND EXPERIMENTER—
PART 2 DEALS WITH "X" AND "Y" AMPLIFIERS

(Continued from page 398, July issue.)

As it is very rare that the signal to be examined is of sufficient amplitude to deflect the spot across the screen an amplifier has to be used. The gain of the amplifier will vary, depending on the amplitude of the signal to be examined. For example, a C.R.T. requiring a peak-to-peak voltage of 140, i.e., an R.M.S. of 50 volts, will, with an input of one volt, require an amplifier that will give a gain of fifty. If, however, the output from the amplifier is push-pull, then only 25 volts will have to be supplied by each output. Again, if the amplifier is made of high gain, a suitable attenuator can be incorporated to reduce the gain, so that in the example given above with a gain of 500 it would be possible to scan the screen with an input of only 0.1 volts, and with the use of the attenuator the gain may be controlled at high inputs.

Matters, however, are not as simple as this, as it is not possible to get the amplification and the bandwidth. Again, the amplification of low frequencies can be a problem; special amplifier circuits have been designed, and will be described later in this series.

The normal amplifier circuit differs from the normal audio amplifier circuit in that it must be capable of a high output at very low distortion, and also phase shift must be kept at a minimum. The high frequencies must also be reproduced in full, and this is not always possible. It has been stated by one authority (Dr. F. E. Terman) that for a saw-tooth or square-wave to be reproduced correctly all frequencies from the fundamental to the 27th harmonic must be produced in correct phase and amplitude. However, the writer has found that quite good results can be obtained with circuits that do not reproduce more than the first six or eight har-

monics. It is interesting to see just how a wave becomes if all above the fifth harmonics are removed.

An Example

The operating condition of a triode for the minimum distortion is the same as for the maximum output in the case where it is terminated with a resistance equal to its impedance. The gain of the stage under these conditions is equal to a half of the amplification factor. For example, a 6C5G will, with a 7 K Ω anode load and a supply voltage of 300, give a gain of 10, and an output swing of about 200 peak-to-peak at very low distortion. Increasing the H.T. will give a greater output for the same amount of distortion. The bandwidth that can be obtained from such a simple circuit runs up in the megacycle range, but will depend on the stray capacity of the circuits. If, however, it is desired that a greater gain, say, 100, is required, the two sections of a 6SN7 can be used, one feeding the other. Decoupling will have to be used, and the circuit of Fig. 5 is quite useful.

Phase Shift

Single-ended output amplifiers allow the shift voltage to be fed to one plate, but there are circuits where the output can be fed direct from the plates of the amplifiers in such a manner that electronic shift can be used. These circuits have several advantages—they reduce the output capacity of the circuit, reduce the number of the components, and also operate in such a manner that the centre of the screen is at all times the point of no distortion. That is, the shift can be applied to a wave in such a manner that the amplifier can be heavily overloaded, and yet the portion of the wave at the centre of the screen is being amplified in a distortionless manner. The

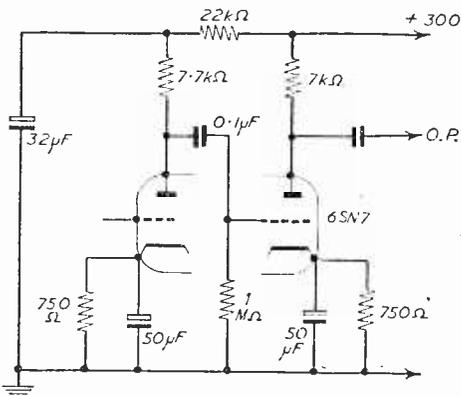


Fig. 5.—Using a 6SN7 with the two sections in cascade.

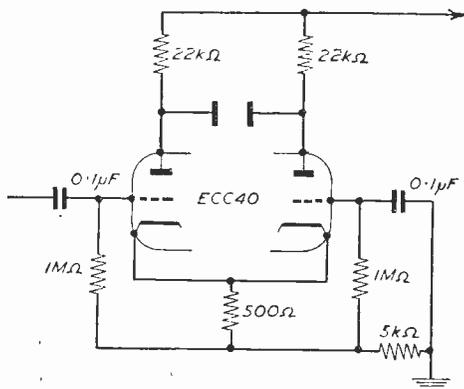


Fig. 6.—This circuit is known as the Schmitt.

circuit is the Schmidt, and it consists of two valves with the cathodes joined and operating with a common cathode resistance. The basic circuit is shown in Fig. 6. The circuit values in this circuit are "calculated," but in practice, of course, the 500Ω could be 470Ω or 510Ω and the $5,000\Omega$ either $4,700\Omega$ or $5,100\Omega$. If the reader studies the valve data for the Mullard ECC40 he will see that

and the cathode coupling resistor is made ten times this value. A coupling resistor of lower value can be used, but the balance will not be as good. An increase in resistance over ten times will only decrease the output for a given distortion.

If, with this circuit, the grid of the second half is fed with a D.C. potential, and not earthed via a condenser, it is possible to vary the bias on one half of the valve. This will upset the ratios of the anode currents in the two valves, so that the voltages developed in the two anode load resistors will be quite different. With the anodes of the valves coupled direct to the deflector plates this can be used as shift control. The values of the resistors in series with the potentiometer will have to be calculated, as if the control were placed between H.T. line and chassis only a portion of the track would be used. The change of only a few volts is usually quite sufficient.

Practical Circuit

An amplifier circuit described several years ago by the writer gave a gain of some 3,000 with a zero phase shift down to zero frequency. The circuit (Fig. 7) is quite simple, but a little unusual. The first valve is a conventional 6SL7 used with one section as an anode load for the other. This is not new, but it reduces the distortion to the lowest possible value, and was first used in the 1920s. The bias of both sections is obtained with the aid of the normal cathode bias resistor—in this case $4.7\text{ K}\Omega$. The H.T. supply to this valve is stabilised by the use of a voltage halving circuit. Here an EF50 was used in the original circuit, but later experience has shown that the EL84 is far more efficient, as it has a larger slope and higher current-carrying capacity. The second 6SL7 is in a conventional Schmidt circuit. The value of the cathode coupling resistor of the second valve will have to be found by trial and error. The top frequency that one can expect to reproduce with this type of circuit is in the region of 20 Kc/s. but there is no zero. If, however, it is required to use the circuit for frequencies below 1 c/s, then the H.T. supply must be stabilised. The output voltage for sweep purposes is about 150 volts.

(To be continued)

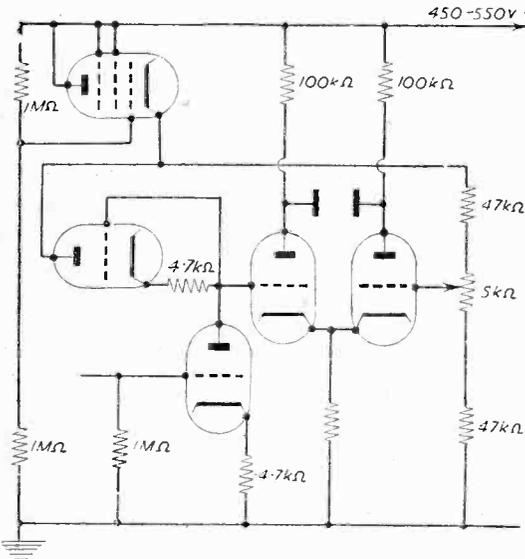


Fig. 7.—An elaborate circuit which has very high gain and minimum phase shift.

in the data the impedance of the valve is given as $11\text{ K}\Omega$ whereas in the circuit the values of the load resistors are $22\text{ K}\Omega$. The reason for this is that the feedback in the cathode coupling circuit has the effect of doubling the impedance of the valve. The calculations for the circuit are quite simple. The cathode resistor is calculated in the normal manner by dividing the bias voltage by the anode current,

Complete Installation for Small Craft

A NEW complete three-in-one radio installation, designed with a particular view to meeting the requirements of near- and middle-water fishing vessels, is now in production by the Marconi International Marine Communication Co., Ltd. Known as the "Guillemot/Renown/Seapilot" installation, it provides full facilities for radio-telephony transmission and reception as well as for direction-finding.

The transmitter, designed only for radio-telephony working, is crystal-controlled and operates in the frequency band of 1.6 to 2.85 Mc/s. This coverage is subdivided into six sections selected by a switch and six preselected spot frequencies can be provided for. Power is obtained from 24-volt accumulators, and the power output to the aerial, unmodulated, is 14 watts.

Operational controls have been kept to a minimum and apart from the "On/Off" switch, consist only of the aerial tuning circuit control and the frequency selector switch. Both the frequency controls are

fitted with dials large enough to be operated while wearing gloves.


The "Renown" section of the installation is a seven-valve superheterodyne receiver specially designed for use with a rotating loop aerial to provide both reception and direction-finding facilities. It is fitted with a built-in loudspeaker and covers three frequency ranges of 131 to 45 kc/s, 375 to 1,250 kc/s and 1,154 to 3,400 kc/s, thus giving full coverage of all the necessary marine frequencies, including those used for the transmissions of the "Consol" position-fixing system and the BBC weather reports, forecasts and warnings, as well as those on which the coastal radio-beacon stations transmit.

As in the case of the "Guillemot," controls have been kept to a minimum and made as simple to operate as possible. The frequency band selection switch, tuning and volume controls have all been provided with easily-handled knobs, and the "Renown" and "Guillemot" being of approximately the same dimensions may be fitted one above the other to make a neat and compact installation ideal for the small wheelhouse.

Volume Controls

Midget Edison type. Long Leads. Guaranteed 1 year. S.P. Sw. 2/-. D.P. Sw. 4/-. ALL VALUES. 10-100 ohms to 10 Megohms.

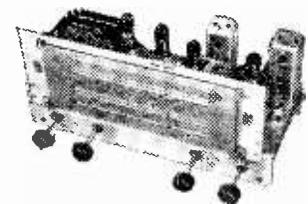80 ohm COAX CABLE STANDARD fin. diam. Polythene insulated. GRABBER ONLY Not Ex-Govt. 8d. yd. COAX PLUGS, 1/- each. COCKS, 1/- each. LINE CONNECTOR, 1/2. OUTLET BOXES, 4/6.



ALL WAVE RADIOGRAM CHASSIS THREE WAVES/IDS FIVE VALVES S.W. 18 m. - 50 m. LATEST MULLARD M.W. 200 m. - 500 m. ECH42, EP41. L.W. 500 m. - 2,000 m. EBC41, EL41, EZ40.

BALANCED TWIN FEEDER per yd. 6d. 80 TWIN SCREENED FEEDER per yd. 1/- 10 ohms 50 OHM COAX CABLES, 8d. per yd. fin. dia. TRIMMERS, Ceramic, 30, 70 pf. 8d. 100 pf. 15d. 150 pf. 1/3. 200 pf. 1/6.

RESISTORS.—All values, 10 ohms to 10 meg., 1/4 w. 4d.; 1 w. 1/4. 1/2 w. 8d.; 3/4 w. 1/3; High Stability, 1 w. 1/2, 2/-.

WIRE-WOUND RESISTORS.—Best Make Miniature Ceramic Type. 5 w., 15 ohm to 4 K., 1/9; 10 w., 20 ohm to 6 K., 2/3; 15 w., 30 ohm to 10 K., 2/9; 5 w. Vitros, 12 K. to 25 K., 3/-.

WIRE-WOUND POTS. 3 WATT, FAMOUS MAKE Pre-Set Min. TV. Type. Knurled Slotted Knob. All Values, 50 ohms to 50 K., 3/- each. 50 ohms, 4/-. Ditto Carbon Track 50K to 2 Meg., 3/-.

O/T TRANSFORMERS. Small Tapped pentode, 3/9. Heavy duty 70 ma., 4/6. Ditto, tapped, 4/9.

L.F. CHOKES 10 h. 65 ma., 5/-; 20 25 h. 100 150 ma. 12/6; 5 h. 250 ma. 15/-; 1 1/2 h. 100 ma. 10/6. L.Y.N.X. 3b. 250 ma. 6/6. SIMPLEX, 10h. 150 ma. 10/6. 10.6. MAINS TRANS. Made in our own workshops to high grade specification. Fully inter-leaved and impregnated. Tapped 100 v. 250 v. 500 v. 6.3 v. 11 amp. 7/6; ditto 6.3 v. 3 amp. 10/6; ditto, 12 v. 5 amp. 7/6; 250-0-250 80 ma., 6.3 v. 4 a., 5 v. 2 a., ditto 200-0-200, ditto 250-0-250, 21/-.

AMPLIFIER TRANS. 250 v. 50 ma. 1/2 wave, 6.3 v. 2 a. Fully shrouded, 17/6. Viewmaster, Auto Type, 35/-. Tricking, 30/-.

CONVERTERS, Simplex, 35/-. Rewinds and Specials to requirements.

SOUNDMASTER SPECIALS.—Mains Trans. 35/-.

L.F. Choke, 10 h. O.P. Trans., 5/6. Envelope, 6/6. Specified Water Switches, 22/6 per set of 3.

GOODMANS. Latent Wave Angle Damping Type, Focus Unit, Variable Focus and adjustable Reticle Shift, 35/-.

E.L.A.C. C.R.T. Ion Traps, 2/6.

TAPE RECORDING BARGAINS LIGHTWEIGHT XTAL HAND MIKES. Chrome Mesh—Quality and sensitivity for only 25/-.

ELECTRODYNAMIC MIKE INSERT.—U.S.A. make, precision engineered. Size only fin. diam. by fin. Bargain Price, 3/9. Matching Trans. 3/9.

WOODEN WALNUT CABINET.—12in. x 7in. x 5in. TRF or superhet, comp. pitched chassis, dial, back-plate drive, pointer, etc., 26. plus post 2/-.

TYANA.—Midget Soldering Iron. 200/220 v. or 220/220 v., 14/11. TYANA TRIPLE THREE.—Complete with cabinet and stand, 19/6.

NEW SOLON MIDGET IRON.—35 w., 18.6. 10KAL FOR RADIO CONSTRUCTORS.

C.R.T. HEATER ISOLATION TRANSFORMER.—Low leakage winding with 25% spec. boost. Ratio 1:1.25, 2 v., 10/6; 4 v., 10/6; 6.3 v., 10/6; 12 v., 10/6.

MAINS PRIMARIES and Specials to Order. MIKE TRANS. Excellent. Ratio 50:1, 1/3 9/6 each.

V.HOLDERS.—Pat. Int. Oct. 4d. EP50. EA50. 6d. 1/2A.C.T. 13. Moulded: Int. Oct. 6d., 8/6; 9d., with screening can, 1/6; 18A, 8/6d.; B7C, 9d.; VYR87, 2/6. Ceramic: EP20, 8/6; 12. EMO. G.LAMER, 7/6 and 9/6, etc. 1/-.

GAY STRIPS.—2 or 3-way, 2d.; 4 or 3-way, 3d.; 6-way, 4d.; 9 or 1-way, 6d., etc.

T.V. PRE-AMP.—4 channel 1. Easily modified for other Channels or Converter use. Midget Chassis, 4/- 2/- 1/4. Coupler with P.F. valve, coils, lead and plug. Ready for use. Brand New Mrs. Surplus. Listed £3 15s. Special Clearance Price, 27/6; p. & p., 1/6.

TOGGLE SWITCHES EX-GOV'T.—"On-Off" 9d. Esin 3/100s solder 60/40. 16 g. or 18-22, 5/6 1/2 lb.; 1/4 C. wire, 18 g. 1/2 lb.; 20 g. 1/2 lb.; 24 g. 1/2 lb. connecting wire, 10 colours. Single or Stranded, 2d. yd. 2 K. 5 w. H.D. w. Pots, 4/6. 10 K., 25 K. Govern w. Pot, fin. spindle, 3/6. SCREENED GRID CAPS, 1/6ct., or Mazda, 6d. ea. BULGIN HIGH VOLTAGE VAVE CAPS, 1/6ct., 1/-.

FUSES.—1 1/2 in. all values 60 ma. to 10 a. 6d. ALADDIN FORMERS and cores, fin., 6d.; 2in., 10d. SLOW MOTION DRIVES.—Epicyclic ratio 4:1, 1.2.3. INT. OCTAL CABLE PLUG (8-pin), with cover, 1/3. 200-250 Volt SELECTOR SOCKET (2in. x 1in.) with Plug 1/2. PILOT LAMPS.—6.3 v. 300 mA. 8d. SPEAKER FRET.—Expanded anodized metal, 14in. by 9in., 3/-. EXT.L.S.—Switched socket, on-off and parallel switching, complete with plug, 2/-. COPPER PLATED AERIAL RODS. 3in. x 12in. mesh fitting, 2/6 doz., P. & P. 9d.

MAINS LEAD.—3 Yds. Twin Twisted Matcon Flex. Top Quality 25/0076 Core, 1/2.

Brand New and Guaranteed, with 10in. P.M. Speaker, A.C. 200/250 v. Four position Wave-change Switch. Short-Medium-Long-Extra. Slow Motion Tuning. Speaker and Pickup connections. High Q dust-proof coils, 465 kc/s f.e.f. Latest circuit technique delayed. A.V.C. and Negative feedback. Output 4.2 watts. 3 ohms output transformer on chassis. Chassis size 1 1/2 x 5 1/2 x 4 1/2 in. Glass dial, 10in. x 4 1/2 in. horizontal or vertical type available, fit by 2 Pilot Lamps. Colour Brand Station names, L.W. Green, M.W. Red, S.W. White. Four knobs supplied. Walnut or Ivory to choice, aligned and calibrated. Chassis isolated from mains. PRICE, £10 15/0. Carriage and Insurance, 4/6. (Without 10in. Speaker, £9 15/0. Carr. & Ins., 4/6.)

BARGAIN OFFERS RECOMMENDED FOR ABOVE CHASSIS GREAT REDUCTIONS Brand new Plessey 3-speed Antochanger Mixer Unit for 7, 10 and 12in. Records. Twin Rizer Xtal Head with Duopoint sapphire styms. Plays 4,000 records. Spring mounting. Superb Quality. Bargain Price, 91 gns. post free. Radio-gram Cabinets, superb Walnut finish. Size 30in. x 29in. x 15in. Lift-up lid. Int. Record Storage space. Facing cut out for above Radio Chassis. Soundly constructed. Complete with Back, Speaker Baffle and Fret. Bargain 29 19s. 6d. Callers only please.

Table with columns: NEW BOXED, VALVES, ALL GUARANTEED. Lists various valve types and prices.

SUB MINIATURE VALVES WIRE ENDS R.F. Pent. 125 v. Fil. L.F. Pent. 125 v. Fil. Brand new Ex-Dept. Aid Apparatus, by Mullard and Hivac. Types: 1/6 DPF6, 1/6 XFW10, 1/6 DPT0, 1/6 XFW20, 1/6 D156, 1/6 XFY11, 1/6 D172. 7/6 each post free.

CRYSTAL DIODE.—Very sensitive. G.E.C. 3 S. H.E. PHONES.—(Hi-grade Amer.), 15/6 pr. S. G. BROWN'S, 4,000 ohms, 15/6 pr.

T.R.S. SPECIALISTS THO 1665. Buses 133 or 68 pass door. 307, WHITEHORSE ROAD, WEST CROYDON P. and P., 6d. £1 orders post free. Lists 5d. A.L. MAINS TRANS.—1/- extra.

CONDENSERS. New Stock 601 mfd. 6 kV. T.C.C. 5/6. Ditto, 12.5 kV., 9/6; 2 pf. to 200 pf. Mica, 6d.; 201. Mica or Tub. T.C.C. 500 v., 101 Sprague 500 v., 102 S.P.F. 500 v. 1 pf. mfd. 250 v. Micanoid Tub., 9d.; 100. Hants. Mica-lead 500 v., 0.005, 301 mfd., 9d.; 0.05 mfd., 5/6; 1/2; 25 mfd., 1/6; Tubular 5 mfd., 350 v., 1/9. SILVER MICA CONDENSERS.—10%. 5 pf. to 500 pf., 1/-; 500 pf. to 3,000 pf., 1/3. DITTO 1% (ex stock) 1.5 pf. to 500 pf., 1/9; 515 pf. to 1,000 pf., 2/-.

Table with columns: ELECTROLYTICS ALL TYPES NEW STOCK. Lists electrolytic capacitor values and prices.

SPECIALS.—Can Types. 500 mfd. 12 v., 3/-; 1,000 mfd. 12 v., 5/-; 1,000 v. mfd. 6 v., 4/6; 16 mfd. 70 v. Hants, 6/6; 1 mfd. 2 kV., 4/6; 3 mfd. 10 v., 5/6.

SEMI-CONDUCTORS. E.H.T. type FLY-BACK VOLTS.—K325 2 kV., 4/3; K340 3.2 kV., 6/4; K3 45, 3.6 kV., 6/6; K3 50 4 kV., 7/3; K3 100 8 kV., 12/6; K3 160 14 kV., 18/-.

MAINS TYPE.—RM1, 125 v., 60 ma., 4/-; RM2, 100 ma., 4/-; RM3, 120 ma., 5/9; RM4 250 v., 275 ma. 10v., 4/6.

KNOB, GLOSS ENGRAVED.—Walnut or Ivory, 1 1/2 in. dia., 1/6 each. "Contract", "Brilliant", "Brilliance On-Off", "On-Off", "Volume", "Vol., On-Off", "Tone", "Tuning", "Trebble", "Bass", "Wavechange", "Radio-gram", "S.M. L. Gram.", "Record-Play", "Brightness." Ditto not engraved, 1/- each.

POINTER KNOBS.—Brown with white marking line, small, 9d., large, 1/4.

COILS.—Wearless "P" type, 2/8 each. Outer "Q" Type, add. dist. core, 3/6 each. All ranges.

REACTION COND.—0001, 0003, 0005 mfd., 3/6 ea. E.H.T. TRANS.—4 kV. A.C. 2 v., 2 a., 45/-.

VIBRATOR TRANS.—6 v. input, 250 v. 50 ma. output, 9/6. P. & P. 1/3.

VIBRATORS.—4-pin 12 v. Mallory, etc., 7/6.

VCR97 £2 TESTED FULL PICTURE P. & P. 2/-

CHARGER TRANS. PRIM.—0-200/250 v., Sec. 0 v.-15 v. 1a., 13/6; 2 a., 16/-; 3 a., 18/6 4 a., 21/-; 6 a., 26/-.

FULL WAVE BRIDGE SELENIUM RECTIFIERS.—6 or 12 v. 11 amp. 8/9; 3 a., 12/6; 4 a., 15/-; 6 a., 23/6. Ditto P.W. only 9 v. 1 a. 9/-; 6 v. A.C. 5/6.

ACID HYDROMETER.—New octagon. Unbreakable. Packed in metal case, 7in. x 1 1/2 in. dia., 4/6.

H.F. MIDGET CHOKES.—14 A.H.F., 2/6 each. BRIMISTORS.—421 for 3 a. heater chokes, 3/6 (722 for 15 a., or 2 a., 2/6. (723 Pilot Lamp, 1/6).

COPPER ENAMEL WIRE.—1 lb. 14 to 20 s.w.g., 2/-; 22 to 28 s.w.g., 2/6; 30 to 40 s.w.g., 3/6.

SWITCH CLEANER FLOID, spirit, squirt, 3/9 1in. dia. RADIO SCREWDRIVERS.—shell-rod made blade, 2 1/2 in. x 1in. Ins. handle, 5,000 v., 4 1/2. each.

TWIN GANG TUNING CONDENSERS. 0.005 mfd. midget with trimmers, 3/6; 355 pf. midget, less trimmers, 6/6; 500 Standard size with trimmers and feet, 9/6; less trimmers, 8/6; ditto, solid, 2/6.

VIBRATOR POWER PACK (J-6)-Tr. U.S.A.—Copper-steel Case 7in. x 6in. x 5in., 12 v. Input, Output, 90 v. H.T., 6 v. and 1.5 v. L.T. Complete, 25/-; p. & p., 2/6. Suitable Factory Portable Sets.

LOUDSPEAKERS P.M. 3 OHM. 3in. Plessey, 12/6. 5in. Goodmans, 13/6. 6in. Elec. 14/8. 8in. R. & A., 17/6. 10in. Plessey, 25/- 12in. Trivox, 55/-.

I.F. TRANSFORMERS

465 Kc/s Six tuning Minuteman Circular Can, 2 1/2 in. by 1 1/2 in. diam. Fits octal V-holder cut out. High Q add good bandwidth. By Pye Radio. Two mounting feet.

BRAND NEW, 6/9 PAIR

BENTLEY ACOUSTIC Corp., Ltd.

38, Chalcot Road, N.W.1. P/rimrose 9090

0Z1	5/6	7Y1	8/6	ECC81	8/6
1D5	8/6	8D2	2/6	EC130	10/6
106	8/6	9D2	3/6	EF37	10/6
1L4	6/6	10F1	10/6	EF39	10/6
1LD5	4/6	10P3	10/6	EF91	7/6
1LN3	4/6	11D3	6/-	EL38	20/-
1R5	7/-	12A6	0/6	EL91	7/6
1T4	6/6	12A8	15/-	FM34	12/-
2D21	8/6	12AT7	7/-	FY61	11/6
3D6	9/-	12AU7	10/-	GY41	9/-
3Q6	12/-	12AX7	7/-	H30	7/6
5U4G	8/-	12BE6	7/6	HL2	2/-
5Y3C	7/6	12H6	3/-	HL320	6/-
6Z4C	8/6	12K8	8/6	KT2	8/6
6AK5	7/6	12SH7	5/6	KT3C	10/6
6AK6	8/6	12SJ7	6/6	KT36	17/6
6AM6	8/6	12SK7	6/6	KT6W2	5/-
6A3	8/-	12SG7	8/6	MH4	5/6
6B8	4/-	12SR7	7/6	MHD4	10/6
6BA6	7/-	13D3	9/-	M5 Pen	5/-
6BE6	7/-	18D2	4/-	MVS Pen	7/6
6B18	7/6	19AQ3	12/6	PL38	20/-
6BW6	7/6	20F2	8/6	PM24M	12/6
6CH6	6/6	20L1	12/6	PR2	8/6
6F7	6/-	25L6	8/6	PZ30	16/6
6F12	7/6	25Y5	8/6	QF230	8/6
6F33	9/6	35L6	8/-	SP61	2/6
6H6	2/6	35Z4	8/6	TP22	10/6
6J5	5/-	42MPT	12/6	TF230	10/6
6J6	7/-	43	8/6	UF42	13/6
6J7	5/-	50L6	8/-	UBL21	12/6
6K6	6/6	77	8/6	UCR21	13/6
6K7	6/6	78	8/6	UL41	9/-
6K8	8/-	80	8/6	UR3C	10/6
6L7	7/6	85A2	10/6	UU6	10/6
6L18	9/6	210LF	2/-	UUR	16/6
6N7	3/6	215SG	7/6	UY41	9/-
6O7	8/6	255SG	7/6	U12	8/6
6R7	8/6	5763	9/-	U403	10/6
6SA7	7/6	9002	6/-	V5A92	8/6
6SC7	7/6	9003	6/6	VP2	8/6
6SJ7	7/6	AC PEN 10	10/6	VP23	6/6
6SK7	6/6	CB131	17/6	VR53	5/-
6SL7	8/6	DH30	15/6	VR55	7/6
6SN7	8/6	EB91	6/-	VR57	8/-
6V6	7/-	EB131	17/6	VR91	5/-
6X5	7/-	EC91	7/6	VR136	6/6
6Y6	3/-	EC53	7/6	VR105	9/-
7C5	7/6	ECC33	10/-	X21	10/6
7C6	7/6	ECC34	10/-	X65	7/6
7C7	8/6	ECC35	10/-	X63	7/6
7S7	7/6	ECC35	10/-	X63	7/6

Post paid. 24 hour C.O.D. service. All guaranteed. Many others. S.A.E. free list.

VALVES Ex-Govt. Boxed and Guaranteed.

1R5	8/-	6SN7GT	11/-	EF38	7/6
1S8	8/-	6V6GT G	9/-	EF39	9/6
1T4	8/-	6X5GT	9/-	EF59	7/6
3V4	8/-	12A6	8/-	EF54	6/6
5U4G	8/6	12SH7	5/6	FK32	9/6
5Z4C	9/6	25L6GT	10/-	EL35	11/6
6A4G	7/6	35L6GT	10/-	KT33C	10/-
6AL5	7/6	50L8GT	10/-	L63	6/6
6AM6	11/6	807	10/6	PEN16	10/6
6B6G	7/6	931A	9/6	S130	7/-
6H6 & GT	4/-	ACV14	4/6	SP41	3/6
6J5G & GT C	6/6	CV67	25/-	SP61	5/-
	6/6	CV174	25/-	V872	6/-
6J6	11/6	DA11	20/-	V1120B	8/6
6K7M	8/6	E1192	7/6	VR105/30	11/-
6K7GT	8/-	E1230	10/6	VR150	30/10
6L6G	11/6	E1436	10/6	V870	10/6
6N7C	10/6	EB34	3/6	VS110A	7/-
6SL7GT	9/6	EC52	6/6	VU111	4/-
		EC54	8/6	VU120A	4/6

WILCO ELECTRONICS Dept. P.W.

204, Lower Addiscombe Rd., Croydon

STAN WILLETTS

43, SPON LANE, WEST BROMWICH STAFFS. TEL: WES 2392.

VALVES. — Brand New, every one guaranteed. D77, Z77, 6AM6, 8D3, CV138, CV640, CV136, CV131, W77, N77, EL91, OK7C, VT82 (EL32), R17, 5/- each, 54/- doz. 6V6GT, 6K5GT, 6A4G, DH77, 6A7B, 6/9 each, 6K7 (metal), 5/-, 6P6, 5/-, SP61 or 41, 2/6, RK34 (2C34), 1/9, ATP4, 2/6, 24/- doz. EA50, 1/9, MU14, 8/6, 5Y3CT, 7/9, KT4, 5/9, 8A4, 1/6, EC52, 4/9, EF50, VR91, 4/6, R10, 5/6, KT41, 3/-, post 6d.

SET OF 4 BATTERY VALVES.—1R5, 1S5, 1T4, 3S4, 27/- set or 7/- each, post 6d. **RESISTORS.**—12 1 watt assorted. Brand New, 1/8 box of 12, post 4d. 32 mfd. 450 v. (U.S.A.) brand new, 1/8 each, 6 for 7/9, post 10d.

WANTED

VALVES, C.R.T., TEST EQUIPMENT




This small sum will bring you fifteen blueprint circuits, parts lists and technical descriptions* enabling YOU to build all of the following high-class equipment:—

- ***3-VALVE 3-BAND SUPERHET. FEEDER UNIT.
- ***4-VALVE 3-BAND SUPERHET. "NORM. / HI-FI / GRAM." FEEDER UNIT.
- ***4-VALVE 3-BAND A.C. SUPERHET. ("CORONET.")
- ***5-VALVE 3-BAND A.C. SUPERHET. RECEIVER.
- ***5-VALVE 3-BAND A.C./D.C. SUPERHET. RECEIVER.
- ***6-VALVE 3-BAND A.C. SUPERHET. RECEIVER.
- ***6-VALVE 3-BAND A.C./D.C. SUPERHET. RECEIVER.
- ***3-VALVE 2-BAND T.R.F. SUPER QUALITY FEEDER UNIT, ETC.
- ***FEEDER AMPLIFIER AND POWER PACK.
- ***MAGIC EYE TUNING INDICATOR UNIT.
- ***SIGNAL TRACER A.C.
- ***5-WATT QUALITY AMPLIFIER A.C. WITH NFB.
- ***10 - WATT PUSH - PULL QUALITY AMP., A.C. WITH NFB.
- ***SIGNAL GENERATOR, A.C. ETC., ETC.

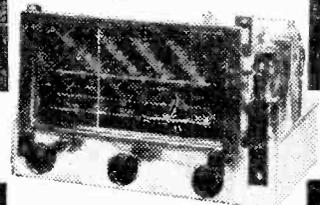*** RODING'S "HOME CONSTRUCTOR'S HANDBOOK"**

is printed on the best glossy art paper and also contains

Set Building Hints, Servicing Hints, Facts and Formulae, Resistance Colour Code, Symbols, etc., etc. AND our current Catalogue, **WHAT MORE COULD YOU WANT FOR ONLY HALF-A-CROWN! SO DON'T DELAY SEND FOR YOUR COPY TO-DAY!!**



This is one of the sets you can build using our *pre-designed units!* (AS USED BY MR. F. J. CAMM IN HIS FAMOUS "CORONETS.")

Send stamp for priced parts lists of "P.W." A.C., A.C./D.C. or Battery "Coronets." All parts in stock.

RODING LABORATORIES (DEPT. P8), BOURNEMOUTH AIRPORT, CHRISTCHURCH, HANTS.

VALVES

All Valves Guaranteed. 24 Hours Service

PY82	9/6	Y63	8/6	6SN7	9/6
6X5	7/6	42SPT	6/-	6L6	10/6
954	2/-	35Z4	9/6	787	9/6
EA50	2/-	35L6	9/6	7B7	9/6
SP11	3/6	2X3	4/6	707	9/6
SP61	3/6	42SPT	6/6	50L6	8/6
MSPEN	5/-	1P2	4/6	5U4G	8/6
VR137	4/-	KT24	4/6	807	8/6
80	9/6	HP4101	5/6	ECL90	11/6
6C5	8/6	DDL4	5/6	EP90	11/6
7C6	9/6	6U5	8/6	12B3	9/6
6K7	5/6	IT4	8/-	12K7	9/6
EF50 (Syl.)	1R5	8/-	KT33C	10/6	
	7/-	3S4	8/-	EB91	7/6
VR116	4/6	IS5	8/-	EF91	9/-
5Z4	8/6	6V6	8/-	41MTL	6/-
7Y4	8/6	6K8	9/6	ARF12	9/-
6Q7	9/-	EF39	8/6	12Q7	9/6
787	8/6	774	8/6	7C6	8/6

- * G.F.C. crystal diodes, 2/-.
- * Pvc plug and sockets, 6d. pair.
- * B.L. Cond., 4 mfd. 500, 1/8.
- * Conn. Panel, 3 Westectors, 22 1-watt Resistors, Condensers, 3/-.
- * 6 Position Push-pull Unit, 1/9. Post 4d.
- * Special Valve Offer. IT4, IR5, 3S4, 3V4, or IS5, 29/6 the Set.
- * 6K8, 6K7, 6Z7, 5Z4, 6V6, 37/- the Set.
- * 6AM6, 6 for 42/-.
- * Coil Packs, L. M. S. 25/-, with circuit.
- * Block Cond., 4 mfd. 500 v.w., 2/9.
- * Rev. Counters, Total count .999. Uses Flash-lamp battery 5/6.
- * Co-Axial Cable, 80n per ft. 8d. yard. Post 1/- per 12 yards.
- * W.W. Pots, Midget 10g. 2/9.
- * Fuses, 11in. 1 a., 1.5 a., 2 a., 3 a., 5 a. 3/6 doz.
- * Jack Sockets, 2 hole fixing, 6d.

Mail Order only. Catalogue 6d.

REX RADIO, 27, Louis Street, Leeds, 7.

Terms: Post, 9d. up to 10/-, 1/- up to 20/-, 1/6 up to 40/-.

ASTRAL RADIO PRODUCTS (T. G. Howell)

SPECIAL OFFER, still available Midget C.P.T.s. 455 Kcs. 13 1/2in. square x 1 1/2in. high. BRAND NEW, 6/- pair, high "Q" postage 6d.

T.R.F. COILS as used in the original model 3 Band, all dry 3 (April '53 P.W.). 6/6 pair, postage 6d.

DI. AL. WAVE. H.F. Coil as used in original models Summer All Dry Portable, Modern 1 & 2 Valve, etc. 4/3 each, postage 3d.

"K" TYPE COILS as used in the original model A. C. Bandpass 3, 33 per coil, Osc. & S.W. Band also available. Postage 6d.

NOW READY our new booklet "HOME RADIO" containing full details for constructing from a crystal set to 3-valver, fully illustrated with list of component suppliers, etc. 32 pages, beautifully printed and in simple language, price 2/- per copy, plus 2d. postage. Send for your copy now. Frame, Aerials, chokes, etc., etc. List 1/6, stamp.

158, THE RIDGWAY, WOODINGDEAN, BRIGHTON, 7.

TELEKIT SUPPLY

MAIL ORDER DEPT.

Chantry Lane Works, Chantry Lane, Bromley, Kent. Phone: Rav. 9845.

VALVES, NEW & SURPLUS, GUARANTEED.

OZ4	4/6	6BA6	7/-	9D2	6/-
1T4	5/6	6BE6	7/-	11D3	6/-
1LN5 (soiled)	8/6	6B7	8/6	12AT7	7/-
1S5	5/6	6BW6	7/-	12A6	12/9
1U5	6/6	6CH6	8/6	(soiled) 5/-	
1T5	6/6	6J5	5/-	6SH7 (soiled)	
104	6/6	6K7	4/6	15D2	2/-
3V4	6/6	6V6	6/6	AL60	4/6
6A8	8/-	6X5	7/6	CV181	8/-
6AL5	7/6	7D5	6/-	EP50	5/-
6AM6	6/6	7D8	6/-	VR21	3/-
6AT6	7/6	7B7	6/-	W77	7/3
6B8	6/-	787	6/-		

BECKENHAM, KENT

THE SHOP FOR THE CONSTRUCTOR NOW OPEN AT 104, HIGH STREET.

Surplus R.F. Pentodes

DETAILS OF EX-SERVICE VALVES, WITH BASE CONNECTIONS

By E. G. Bulley

THE valves that are today available upon the surplus market are shown in table 1, and comprise two specific types, namely one that is termed the "variable mu," and the other having a sharp cut-off characteristic. The former derives its name from the fact that the pitch of the grid helix is varied along its active length, resulting in the mu of the valve being varied as and when the bias voltage is altered. That is to say, as the bias voltage is taken more negative so the mu of the valve will decrease. This characteristic, therefore, allows the valve to handle much larger signal inputs without distortion in the circuit in which it is being used.

In the case of the sharp cut-off type, the grid pitch is uniform along its entire length and therefore one can say that the mu characteristic is more or less constant, and is not therefore affected by the bias on the valve.

The amount of amplification effected by the valve in question can therefore be controlled by the variation of the signal input to the grid, or in some cases by variation of the screen voltage. The latter affects the slope of the valve. By varying the slope characteristic, it in turn affects the amplification factor.

TABLE 1—SURPLUS VALVE TYPES

	E.F.	I.F.	Max. E.A. Voltage	Max. Screen Voltage	Max. Wa	Max. Screen Dis.	Slope Ma/V	Max. Op. Freq. (Mc/s)
VR65	6.3	.63	250	250	4.5	1.25	8.5	100
CV136	6.3	.2	300	275	4.75	0.8	2.6	100
CV138	6.3	.3	300	300	3.0	0.9	7.5	—
6C6	6.3	.3	250	100	—	—	1.25	—
VT193	6.3	.3	250	100	2.0	—	2.85	—
NR64	6.3	.3	250	100	2.0	—	2.85	—
VR106	13.0	.2	250	125	—	—	1.65	—
VR108	13.0	.2	250	125	—	—	1.25	—
NR79	6.3	.45	300	150	3.0	0.5	7.5	—
ARP21	6.3	.45	300	150	3.0	0.5	7.5	—
ARP24	2.0	.21	150	60	—	—	1.0	—
ARP20	4.0	.95	200	200	4.0	—	8.5	—
ARP38	4.0	.25	250	100	1.25	—	2.2	—
VT149	4.0	.25	250	100	1.25	—	2.2	—
VR91A	6.3	.3	300	300	3.0	1.7	6.5	125
VR100	6.3	.3	250	100	2.0	—	2.85	—

Cross-modulation

The adoption of the variable-mu valve does prevent what is known as cross-modulation, that is to say,

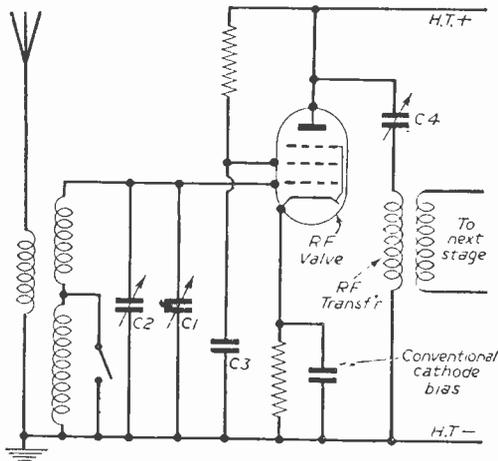


Fig. 1.—A conventional H.F. stage in a modern receiver.

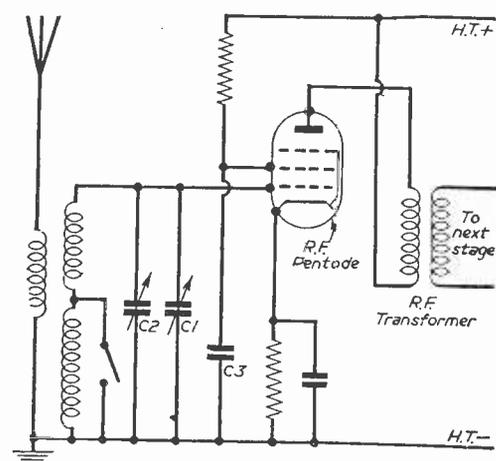


Fig. 2.—An alternative to the circuit shown in Fig. 1. Here the R.F. transformer primary carries the anode current of the valve.

the use of such a valve prevents the interference which can be set up by the modulation of two or more signals.

A typical R.F. stage is shown in Fig. 1, and in such a circuit, screening is an essential requirement. This can be appreciated when one realises that any stray reaction effects will create instability. However, upon examination of the circuit, it will be seen that

frequency changers so long as there is a separate oscillator valve. This practice, however, is not recommended for U.H.F. work, the reason being that there is always the possibility of interference from the output of the local oscillator. A typical circuit in which the valve is used as a frequency changer is shown in Fig. 3, and is included so that the reader will appreciate the application of such valves. Fig. 3 shows the method by which the output from the local oscillator is injected into the grid of the R.F. valve which is being used as a frequency changer.

An advantage of an R.F. stage, however, is that it provides greater gain with improved signal/noise ratio.

A.V.C.

A further advantage of the

variable-mu type of R.F. pentode is, of course, the ability to use the variation in gain afforded by the variable-mu characteristic in an attempt to overcome the drawbacks of fading when receiving long-distance signals. Variation in the bias voltage over quite a wide range varies the gain of the valve, and therefore it is usual in the superhet type of receiver to use this type of valve in both the R.F. and I.F. stages. After the I.F. stages the signal is rectified and applied not only to the A.F. amplifiers, but also back to the R.F. and I.F. stages. The voltage produced by the rectified signal is used for the bias of the controlled stages

(through suitable filters to avoid instability) and thus as the signal becomes stronger more bias is applied to the valves and the gain thus reduced. This type of valve is available in both "short grid base" and "long grid base" and therefore alternative types may be used according to the degree of control desired.

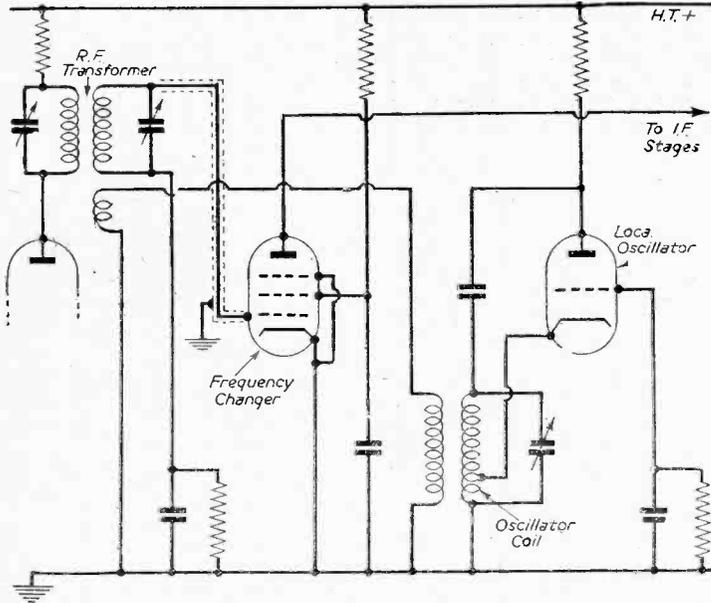


Fig. 3.—Circuit of a superhet frequency changer stage in which an R.F. pentode acts as frequency changer.

the aerial is inductively coupled to the grid coil, the latter being tuned by a suitable condenser C1 to the frequency required; C2 is the trimming condenser. The screen grid is suitably by-passed by a condenser C3, and the output from the R.F. pentode appears across the primary of the R.F. transformer. This, in turn, is transferred to the secondary of the transformer and hence passed on to the next stage. In this arrangement, condenser C4 is used to adjust the coupling between the valve and the R.F. transformer primary.

An Alternative

However, an alternative arrangement which is more commonly used is shown in Fig. 2.

Furthermore, such valves can also be used as

TABLE 2—PIN CONNECTIONS

1	2	3	4	5	6	7	8	T.C.	Base
H	K	A	G2	G3	M	—	H	G1	M.O.
G1	K & G3	H	H	A	—	G2	—	—	B7G
G1	K	H	H	A	G3 & I.S.	G2	—	—	B7G
H	A	G2	G3	K	H	—	—	G1	USS6
—	H	A	G2	I.S.	—	H	K	G1	I.O.
—	H	A	G2	I.S.	—	H	K	G1	I.O.
—	A	G3	H	H	K	G2	—	G1	B7
—	A	G3	H	H	K	G2	—	G1	B7
—	H	A	G2	G3	—	H	K	G1	I.O.
—	H	A	G2	G3	—	H	K	G1	I.O.
M	A	G3	H	H	K	G2	—	G1	B7
H	K	A	G2	G3	M	—	H	G1	M.O.
M	H	A	G2	G3	—	H	K	G1	I.O.
M	H	A	G2	G3	—	H	K	G1	I.O.
H	G2	A	G3	I.S.	K	G1	I.S.	(Pin G-H)	B9G
—	H	A	G2	I.S.	—	H	K	G1	I.O.

(I.S. = Internal shield or screen.)

BARTON'S (Radio) LIMITED


(Dept. PW) 42 TOTTENHAM CT. RD., LONDON, W.1. Telephones: LANGHAM 1151/2

Money Back Guarantee on All Goods

BUILD YOUR OWN RADIO!



We can supply all the parts (including valves, 5in. moving coil speaker, cabinet, chassis, and everything down to the last nut and bolt) to enable YOU to build a professional-looking radio. The chassis is punched and drilled ready to mount the components. There is a choice of any of three attractive cabinets of 12in. long, 5in. wide by 6in. high, as follows: either ivory or brown bakelite, or wooden, finished in walnut. Complete and easy-to-follow point-to-point and circuit wiring diagrams supplied.

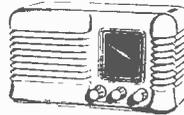

Model 1. T.R.F. RECEIVER This is a 3 valve plus metal rectifier TRF receiver with a valve line-up as follows: 6K7 (HF), 6J7 (Det) and 6V6 (Output). The dial is illuminated and when assembled the receiver presents a very attractive appearance. Coverage is for the Medium and Long Wave bands. Operates on 200/250 volts A.C. Mains.


Plus 2/6 Packing, Carriage, Insur. **£5.10.0**

Model 2. SUPERHET RECEIVER This is a powerful midget 4 valve plus metal rectifier Superhet Receiver with a valve line-up as follows: 6K8, 6K7, 6U7, 6V6. The dial is illuminated and coverage is for the Short Wave bands between 16.50 metres. The Medium Wave bands between 180-550 metres, and the Long Wave bands between 800-2,000 metres. Operates on 200 250 volts A.C. mains. Plus 2/6 Packing, Carriage, Insur. **£7.19.6**

T.R.F. RECEIVER We can supply this Receiver ready built at **£6 15s. 6d.** plus 3/6 p.c.

ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR
NOTE: We would respectfully suggest to those interested in building this receiver that they send for OUR instruction Booklet. Intending constructors can then judge for THEMSELVES how comprehensive this Booklet is.
Instruction Eooklet and Priced Parts List for either of the above available separately at 1/-. This money will be refunded if circuit diagram is returned as NEW within 7 days. When ordering please state Model No.

HIGH QUALITY A.C./D.C. AMPLIFIERS—NEW For 200-250 A.C./D.C. Push-pull output (approx. 3 w.). Valve line-up: 4 latest type miniature Mullard valves — 1 UCH42, 1 UAF41, 2 UL41 in push-pull. Special feature — separate smoothed H.T. supply is incorporated to enable an R.F. tuner unit to be powered by the amplifier. Dimensions, 9in. x 4in. x 4in. Supplied complete with circuit diagram. **69/6** Packing, carriage, insurance on each model, 3/6.

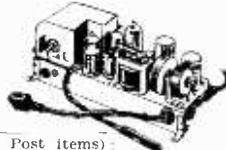

TERMS OF BUSINESS: Cash with order (or C.O.D. Post items) all orders for small items totalling over £2 post free unless otherwise stated.

NOW OPEN ALL DAY SATURDAYS 9-6 p.m. ● PERSONAL SHOPPERS ALWAYS WELCOMED.

4 watt AMPLIFIER KIT


This is a 3 valve 3 stage Amplifier for use with Gramophone, Microphone or Radio. Valve line-up is as follows: 6N17: 6V6: 5Z4. Negative feed-back. Tone control. Voltage adjustment panel incorporated. 4 watts output. For operation on A.C. Mains 200 250 volts.

The Complete Kit includes every item down to the last nut and bolt, drilled and punched chassis and comprehensive point-to-point wiring circuit diagram. Chassis dimensions: 8in. x 6in. x 2 1/2in.

ALL COMPONENTS SUPPLIED ARE GUARANTEED FOR ONE YEAR

PRICE **£4.5.0**

Plus 2/6 Pkg.Carr. & Ins.

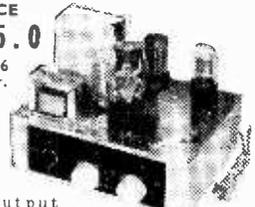

The Output Transformer supplied is for use with a loudspeaker of 3 ohms impedance and we would suggest that the output of the completed amplifier justifies the use of one of the latest W.B. H.F. Speakers which can be supplied as follows: 8in., 60¢; 9in., 67¢; 10in., 73¢. All plus 2/6 pkg., carr. ins.

Circuit Diagram only, available separately at 1/-. To those who require this Amplifier ready-built we can supply it at £5.1.0. plus 3/6 pkg., carr., ins.

HENRY'S (RADIO LTD.)

We have over 20,000 American and B.V.A. valves in stock.

ALL VALVES NEW AND GUARANTEED.			
0Z4A	7/- 6K8G	9/- 12SG7	7/6 EY51
1F6	6/6 6K8GT	9/- 12SH7	7/6 EK32
1R5	6/6 6U5	10/- 12SJ7	8/6 EF91
1S4	7/6 6U5	7/6 12SR7	10/- CV68
1S5	7/6 6U5G	7/6 12SR7	7/6 EL32
1T4	7/6 6L7	7/6 14A7	8/6 EF50 (Regd. CK510AX 5/6 Sv1.)
1C5	8/- 6N7GT	7/6 25Z6GT	8/6 EF50
1LN7	8/- 6Q7GT	8/6 25Z5	5/- AC8P8
2X2	5/- 6SA7GT	8/6 35Z4GT	8/6 AC5 PENDING
3A4	9/- 6R7	8/6 25A6	8/6 VP2
3V4	7/6 6X5G	8/6 35L6	8/6 TDD2A
354	7/6 6SA7GT	8/6 50L6GT	8/6 DK40
5Z4G	8/6 6S07GT	8/6 42	9/- QP25
5U4G	8/6 6S7	7/6 43	8/6 UY31
5Z4G	8/6 6SH7M	7/6 75	9/- SP61
6A7G	8/6 6SK7GT	7/6 78	8/6 D1
6AC7	6/6 6SL7GT	9/- 80	8/6 8D2
6AG5	7/6 6SN7GT	9/- 866A	8/6 9D2
6AB6	6/6 6SCT	10/- 9001	8/6 R3
6AM6	9/- 6S87	7/6 9002	6/- D41
6B8	7/6 6V6GT	7/6 9003	5/- D42
6C4	5/- 7C5	8/6 9004	6/- D63
6CSGT	5/- 7A7	8/6 9003	6/- KT2
6C6	6/6 7C7	8/6 954	6/- U52
6D6	6/6 7H7	8/6 955	6/- U9
6P6G	6/6 7B7	8/6 956	8/6 Y93
6G6G	6/6 7S7	10/- 1299A	6/- P2
6H6G1	5/- 12A6	7/6 TZ40	7/6 MU11
6H6M	8/6 12C3	7/6 931A	37/6 PX25
6J5GT	5/- 12H6	8/6 EA59	50/- KT33C
6J6	9/- 12K7GT	8/6 EF51	10/- VT501
6AK5	9/- 12K8GT	8/6 EB34	12/- AC'PEN (7)
6J7M	8/6 12L7GT	8/6 EBC33	12/- GUSO
6K6	9/- 12SA7GT	8/6 EP36	12/- MS'PEN
6K7G	6/6 12SQ7GT	8/6 EF39	6/- XP25
			3/6 NH (15)
			8/6 VU111
			4/- FC13
			4/- VP47
			4/- ID5

SETS OF VALVES
Ten EF50 (Ex-Brand New Units), 5 - each **45/-** Set
6K8G, 6K7C, 6Q7G, 5Z4G, 6V6G (or K761) ... **37 6 ..**
1R5, 1S5, 1T4, 1S4 (or 3S1 or 3V4), 2T3 ...
TP25, HL23 (D.D. VP23, PEN23 (or QP23) ... **25/-** ..
6K8G, 6K7C, 6Q7G, 25A6G, 35Z5 (or 25Z6G) ... **37 6 ..**
12K8GT, 12K7GT, 12L7GT, 35Z4GT, 35L6GT or 50L6GT 137 6 ..
12SA7GT, 12SK7GT, 12SQ7GT, 35Z4GT, 35S6LGT or 50L6GT **37 6 ..**

CRYSTAL MICROPHONE INSERTS
8/6 **8/6**
POST POST
FREE FREE
Ideal for tape recording and amplifiers. No matching transformer required.

RECORDING TAPE G.E.C.
600 feet Reels **10/-**
1,200 feet Reels **17/6**

Brand New R.F. UNITS
RF24 20-30 mc s **15/-** post free
RF25 40-50 mc s **15/-** post free
RF26 50-65 mc s **19/6** post free
T.C.C. 1.5, 7000 v. wkr. Type CP53Q0, Bakelite Case, 7/6 each.

62A INDICATOR UNIT
Complete with 12-EP50, 4-SP61, 3-EA50, 2-EBM on Double-deck Chassis, V control, Resistors, etc. In absolute New Condition. **69/6**, Carr. 7/6.

VCR57C Blue and White
6in. Tube. This Tube replaces the VCR97 and VCR51 without alteration and gives a full Blue and White picture. Brand new in original cartons. **35/-**, carr. free.

"428" CONTROL UNIT
Containing 4-REDF50, 2-SP61, 2-EA50, 1-EB34, 2-Single-gang .0005 Condensers, W.W. Vol. controls and Switches, etc. Size: 12in. x 9in. x 5in., **35/-**, Carr. 3/6.

"182A" INDICATOR UNIT
Complete with VCR517 and Screen 3-EP50, 4-SP61 and 1-5U4G W.W. V controls. Ideal for TV or Scope. Brand New (less relay) In original cases, **67/6** plus 7/6 carr.

MORSE PRACTICE BUZZERS
Morse tapper and 4 volt buzzer complete on baseboard, with battery and headphones. Brand New complete 15/- p.p., or less Headphones and Batteries. **6/-** post paid.

28-page Catalogue, 3d. Open Mon.-Sat. 9-6. Thurs. 1 p.m.
5, HARROW ROAD, PADDINGTON, LONDON, W.2

TEL: PADDINGTON 1008/9, 0401.

Wireless Supplies Unlimited

(founded 1925, originally Stratford, E.15.)

Still on the go, and STILL carrying the MOST COMPREHENSIVE STOCKS of Component Parts in the Industry!

Get all your requirements from one source, and experience SAME-DAY SERVICE!

POLAR Tuning Condensers, brand new, not salvage. Ceramic insulation. 470 pF, swing (Nominal .0005 μ F.) Full length spindle. Eyebolts supplied for mounting on any plane.
2-gang, 8/6d. post paid.
3-gang, 9/6d. " "
Also 2-gang 300 pF. for Denco Coils, 7/9d.

WIRELESS SUPPLIES UNLIMITED

(Proprs. Unlimitex Radio Ltd.)

264-266, OLD CHRISTCHURCH RD., BOURNEMOUTH, HANTS.

Bournemouth 4567.

*Grams: Linnitrad, Bournemouth.

ANNOUNCEMENT DENCO (CLACTON) LTD.

In order to avoid confusion between the well-known trademark "DELCO" and our own trademark "DENCO" and as "DELCO" was registered as a trademark before "DENCO," we have agreed to withdraw our "DENCO" trademarks from the Register and revert to our former trademark "MAXI Q." In future all of our products will be manufactured, advertised and sold under the registered trademark "MAXI Q."

DENCO (Clacton) Limited,
357/358 Old Road,
Clacton-on-Sea, Essex.

MULTIMETER KIT, WITH FREE OFFER

See June issue for details. Price 23/6.

UNIVERSAL SHUNTS.—High accuracy, for any 1 mA. or 500 μ A meter. Only one simple adjustment to make, no calibrating meter being required. Boxed, with instructions and one year's guarantee for 1 mA., covers 1, 5, 25, 100 and 500 mA. 501 (1 mA.), covers 2, 10, 50, 200 mA. and 1 Amp. Price 11/9.

FIXED UNIVERSAL SHUNTS.—Specially designed for 100 ohm 1 mA. meters and 500 ohm 500 μ A meters. No calibrating or adjustment necessary. Just wire up and use. Ranges as 501 and 500; order S21A for 1 mA., and S206A for 500 μ A meters. One year's guarantee. Price 11/0.

UNIVERSAL SHUNTS for any meter in the range 50 μ A to 5 mA. Details on request.

MASSEY

58, WAKEFIELD AVENUE, HULL

58

Pages

16

Circuits

2/6

only

Enlarged again!

Our Handbook, "The Home Constructor," with its supplements, now incorporates all the above PLUS supra-simplified layout and point-to-point wiring diagrams and FULL constructional details for building a variety of superhets PLUS full constructional details for building a superhet coil Pack PLUS pages of Radio Information, Resistance Colour Code, Formulae, etc. PLUS priced parts lists for structural details for building a superhet Car Radio PLUS profusely illustrated catalogue.

YOU CAN'T GET BETTER VALUE!

IT'S TOPS!

SEND FOR A COPY TODAY

SUPACOILS (Dept. P.8)

21, Markhouse Road, London, E.17

A RADIOGRAM FOR 6 GNS.?



DECCA RECORD PLAYERS

Standard or L.P.
List Price £12/1/6

OUR PRICE 6 GNS.

Well, hardly! But you can convert your own radio by plugging in one of our Record Players. Many surplus models to be cleared at half price.

COLLARO 3-speed Gram Motor Units with turn-over pick-up.
List Price 10 gns.
OUR PRICE £5/19/6



Send stamp for Lists of other Record Players.

RONALD WILSON & CO.
12, BRIDGE STREET, WORCESTER

5 in 3

Free leaflet tells how range extender gives 5 octaves from 3 octave electronic keyboard. Imitates whole orchestra. Is simply built from simple instructions. Get your free copy now.

C & S, 10 Duke St., Darlington, Co. Durham

ALFRED PADGETT

40 MEADOW LANE, LEEDS, 11

(Established 20 years)

All Goods fully guaranteed. Cash refunded if not 100% satisfied with your purchase.

Mail Order Address:

GLOBE WAREHOUSE

Globe Court Liversedge Yorks

300 ONLY. TYPE 17 SETS, less valves. Many useful spares, store soiled. 3/6 each. Post 2/4. Circuit and Full Working Instructions for these sets. 1/- post free.

2,000 SELENIUM METAL RECTIFIERS, 250 volts at 100 mA. Brand new. 6/5 each, post free; 50/- per doz.

1,000 1124 SETS, less valves, but otherwise complete. 6/6 each, Post 2/4.

UNLIMITED QUANTITY of New Coaxial Cable. 1/2 in. 80 ohm, 6d. yd; 20 yds., 8/6, post free.

LARGE STOCKS OF THE FOLLOWING: 100 K. pots., less switch, 1/4 each; 6.2 volt 3 amp. M.E.S. Lamps, 5/- doz.; Crystal Diodes, 2 for 2/2, 12/- doz.; 6V6 G.T., 6/6 each; 6K7 G. 4/- each; M.S. Pen., 7-pin, 2/6 each. All post free.

MIXED RADIO PANELS, full of resistors and condensers. 12 panels, 4/6, post free. 30/- of value. Not to be missed.

SOME OF GOODS PREVIOUSLY ADVERTISED STILL AVAILABLE.

Television, Radio, Record CABINETS MADE TO ORDER

ANY SIZE OR FINISH

CALL OR SEND DRAWINGS FOR QUOTATION

B. KOSKIE

(DEPT. C.)

72-76 Leather Lane, Holborn, E.C.1

Phone: CHAncery 6791/2

J. B. SERVICE (BEXLEYHEATH) LTD.

RADIO COMPONENT SPECIALISTS

5, MAYPLACE ROAD WEST, BEXLEYHEATH, KENT.

Phone: BEXLEYHEATH 1000
Wednesday Half Day

44, CHURCH ROAD, UPPER NORWOOD, S.E.19

Phone: LIVINGSTONE 6222
Wednesday Half Day

104, BROCKLEY RISE, HONOR OAK PARK, S.E.23

(10 yards "Chandos" Bus Terminus)
Phone: FOREST HILL 3428

Thursday Half Day

All Mail Orders to Bexleyheath

Programme Pointers



Repeated Description

I HAVE often complained of the BBC's insensitivity to repetition in many of its programmes, most notably the weather forecasts, news bulletins and other items of topical interest. Also, to me, the needless reading out of casts and other detail after some of the shortest items and, not infrequently, before as well, when all of it is at our elbow in the *Radio Times*.

A notable instance of this occurred during the past month on the occasion of Her Majesty's visit to the City to take luncheon with the Lord Mayor. Three commentators were posted along the route: Max Robertson at Temple Bar describing the "Ceremony of the Sword," Wynford Vaughan-Thomas outside the Mansion House to tell of the arrival there, and Godfrey Talbot inside to whet our appetites and thirsts for the lunch itself. All three told us that (a) the Queen was wearing a green hat and a fur cape, (b) the Duke of Edinburgh was in the uniform of an Admiral of the Fleet, (c) the sky was of Mediterranean blue and the sun was shining down, (d) it was a great historic occasion and the pageant of our glorious history was rolled out before us in the various rites, etc., that were performed, and so on and so on. As the whole broadcast took less than 30 minutes the total effect was one of boredom and annoyance such as we feel on hearing three consecutive news bulletins with scarcely a word changed in each.

A liaison between commentators should not only be the simplest matter possible, but should be obligatory and part of the routine on such occasions. One commentator only should describe the dresses and uniforms (unless, as with a famous pianist, they are changed between courses, etc.). Another should be deputed to "do" the weather, crowds and related events, whilst the third should explain the historical origins and significance of the ceremonies enacted. We should then have a continuous picture of what is taking place unfolded for us instead of, as it were, constant references back to what has already gone by and dips into an index to see what is coming. So simple yet so rarely met with.

"Between the Wars"

Mr. Wickham Steed, late editor of *The Times* gave a talk on the origins of the *Entente Cordiale* and is at present engaged in a series of six programmes of reminiscences styled "Between the Wars." They are very interesting and a forceful radio personality, akin to Bertrand Russell's, is behind them. The talk on the *Entente* might well have had the sub-title "... or how the 1914-18 war came about."

Cobbett's "Rural Rides" is one of the great books on England and those who finish it are well rewarded. Stimulating, racy, forthright, if not always quite accurate, it makes us smell the new mown hay and the freshly turned soil. This is exactly what Ralph Wightman is and did, though I am sure he is more

By MAURICE REEVE

accurate than Cobbett was said to have been. So the three trips that Mr. Wightman took over some of Cobbett's own route were thoroughly enjoyable. I thought the editing and production most agreeable and apposite, and appreciated the reading of passages from Cobbett by John Sharp.

BBC Dictatorship

The new radio play "Defeat," by Graham Sutton, was another disquisition on dictatorship which the BBC seems to be fathering, or mothering, just now. I liked it very much. Dealing with the Athenian expedition to Sicily in 415 B.C. and its utter rout, it has, as all the plays in this recent bunch have had, its pointer to topical events. I was rather tickled at the request of one of the characters to another to "shut the window." I didn't know there were any so long ago.

Dame Myra Hess

Dame Myra Hess played Beethoven's greatest sonata, Op. 111, most beautifully, with all the love and affection of years of association with it and other Beethoven masterpieces, and with sufficient technical mastery to do full justice to the incomparable variation writing, trills, etc.

Mr. Ernest Newman gave an appreciative and interesting talk on Elgar on the occasion of the centenary of the master's birth.

The BBC's "originality" staff worked at full pressure for the 90-minute variety bill which formed part of the programmes celebrating the Queen's return. Items I recognised of truly staggering novelty were some bagpipes, "All Through the Night" and "Home Sweet Home."

Plays

"Odd Boy Out," a school story, savoured up to a point of "The Winslow Boy," inasmuch as one of the boys at a preparatory school was wrongfully accused. But it differed greatly when the headmaster was shown up as a nefarious scoundrel. A good story well acted.

So was "The Little Foxes," Lillian Hellman's story of the aftermath of the American Civil War. But some of the Southern accents were dubious to the point of being untruthful.

"Stop Press Murder" was the usual mixture which cast suspicion on every innocent person without showing up the real culprit too vividly. It had some merits. It was adapted by Rex Rienits from the novel of Guy Ramsey.

News from the Trade

New Mullard Multi-purpose Beam Tetrode

A NEW beam tetrode valve likely to be of great value to designers of compact audio, video or radio frequency equipment has recently been made available by the Communications and Industrial Valve Department of Mullard, Ltd. This is the QVO6-20, which has an anode dissipation of 20 watts. The new valve is intended for operation at full ratings as a power valve at any frequency up to 60 Mc/s, and at reduced ratings to 175 Mc/s. It has been designed to meet the requirements of a very wide variety of applications, from servo amplifiers to video modulators, and it will function equally well in radio transmitters as driver, frequency multiplier, power oscillator, or output valve.

A single QVO6-20 in Class "C" will deliver 69 watts at 60 Mc/s, while at audio frequencies a pair in push-pull, Class AB1 will provide 120 watts output. The mutual conductance of 7mA/V ensures high power sensitivity even at low anode voltages.

As a precaution against internal feedback, the anode is brought out to a top cap and the lower part of the valve is provided with a short metal screen connected to one of the pins. The heater voltage is 6.3 volts and the base is International octal. The QVO6-20 is a direct replacement for the American 6146.—Mullard Ltd., Century House, Shaftesbury Avenue, W.C.2.

The "New Radiotime"

VERSATILITY and ease of operation are the keynotes of the Ekco "New Radiotime" (Model A222), for it combines a switch-tuned radio with a Smith's self-starting, mains-operated clock, complete with automatic time-switching and alarm facilities.

For operation on 200-250 volts, 50 cycles, A.C. mains, the "New Radiotime" is a transportable, four-valve receiver incorporating pre-selected tuning of three medium and one long-wave stations by rotary switch.

Housed in a brown and cream plastic cabinet of compact dimensions (9½ in. high, 13 in. wide, 6½ in. deep), Model A222 has a 6 in. speaker which handles a 2½-watt output with good quality reproduction, the in-built, twin-frame aerial system giving excellent signal pick-up. Extension speaker sockets allow either entertainment or radio alarm in more than one room.

A unique feature of the receiver is that it can be set to switch "on" to a pre-selected radio programme and then, after a short interval, sound a buzzer alarm to wake the extra-heavy sleeper. It can also be set to switch "on" automatically at any time of the day without sounding the alarm buzzer.

A further outstanding feature of Model A222 is that it can be used when retiring to bed in the knowledge that it will switch itself off after a pre-determined period. List price £15 17s., purchase tax £5 3s., total price 20 guineas.—E. K. Cole, Ltd., Southend-on-Sea, Essex.

Six-second Soldering Iron


A NOVEL soldering iron of Australian design is being marketed in this country by the well-known traders Arthur's, of Charing Cross Road. This iron, known as the "Scope," is intended for operation from either A.C. or D.C. from 2.5 to 6 volts, and is

primarily recommended for use with a 4-volt transformer from A.C. mains. The heating time is then six seconds, and the current drain approximately 30 amps. A switch ring is fitted round the handle which is slid forward to bring the element into circuit. As soon as the required heat is obtained the switch is drawn back and thus the load is applied intermittently. It must not be left switched on for too long a period or the bit will be burnt. In such a case the tip will have to be cleaned up. Each iron is guaranteed for three months, and the price is £1 19s., and the transformer, if required, costs £1 17s. 6d.—Arthur's, 150-152, Charing Cross Road, W.C.2.

Whiteley Electrical Record Cabinets

TWO new storage cabinets are announced by the makers of the well-known W/B speakers. Known as the "Melody" and "Symphony" these cost £9 17s. 6d., and the following are general descriptions. The "Melody" accommodates TV or radio receiver on top; room inside for 150 10in. or 12in. records. Highly polished French walnut veneer finish, interior in lacquered birch. Fitted with easy-running castors and has removable record index cards clipped inside doors. Rubber buffers at back of cabinet.

The "Symphony" has a capacity of 250/300 10in. and 12in. records. Top is large enough to take record player or medium-size TV or radio set. Highly polished French walnut veneer finish, interior in lacquered birch. Easy-running castors, removable record index cards inside doors, rubber buffers at back of cabinet.—Whiteley Electrical Radio Co., Ltd., Mansfield Works, Victoria Street, Mansfield, Notts.

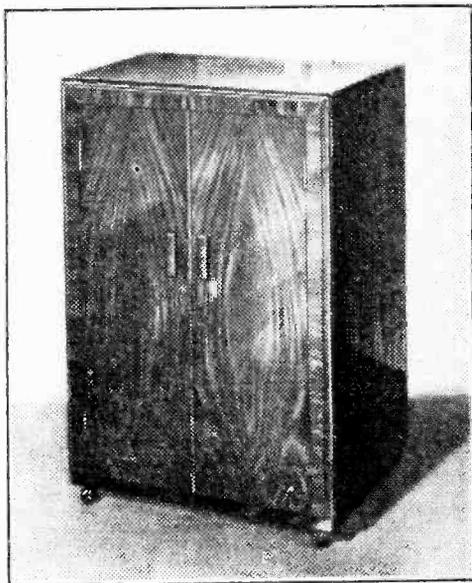

Record storage cabinet by Whiteley Electrical.

Prices slashed at Clydesdale

PLEASE NOTE.—Carriage and Postal charges refer to the U.K. only. Overseas freight, etc., extra.

SUPPLY UNIT RECTIFIER for No. 43 Transmitter.

Ex-Canadian Army, in original wood case. Input 110 volts A.C. 50/60 c/s. 17 kVA. Output (HT1). 2,100 v. 375 mA.; (HT2). 500 v. 400 mA. plus H.T. lines 450 v., 265 v., also 383 v., regulated and neg. bias 250 v., 150 v., 80 v. Making three complete power supplies to all, led via double choke condenser. Input circuits. Valves are 4 866A, 866, 5Z3, 6SJ7, 2/6A3, VR150/30 (Stab.) and 1V (Time delay). The complete unit mounted in metal case with lid shock mounted. Dim.: 2 1/2 in. x 1 1/2 in. x 1 1/2 in. Finish: Olive Drab. Weight: 42 lb. Ask for P/H326

£25.00 Each Carriage Paid

RECEIVER 6A

Channel checking unit working on 49-100 metres, contains 5 VR91 (EF50), 1/6K9, 1/VR35 (EBC33), 1 VR33 (PF36) valves. Thermal switch breaking at 85 degrees F., etc., in metal case 9 1/2 in. x 7 in. x 10 in. Carriage Paid

29/6 Each Carriage Paid

POWER UNIT TYPE 263

In Transit case. Input 80 v. 1.5 K cps. A.C. Output H.T. 120 v. D.C. bias 3 and 9 v. I.C.T. 2 v. Smoothed and stabilised. Complete with 5U4G valve, VS110 stabiliser, 12 v. 1 A. Metal Rectifier, etc., etc., in attractive metal case with handles. Dim.: 1 1/2 in. x 9 1/2 in. x 7 1/2 in. Ask for P/H370

22/6 Each Carriage Paid

5-WAY GROUPBOARD

Paxolin panel 2 1/2 in. x 2 1/2 in., with tags for mounting 5 condensers or resistors; two-hole fixing. Ask for P/H981

6d Each Post 3d.
Or 3 for 1/6. post paid

SUPPRESSOR UNIT 5C/870

Contains 4 H.F. Chokes and 4 Tubular Condensers 0.1 mfd., 250 v. D.C. carrying 5 amps. (2 sets on each lead), each choke and condenser separately screened in compartments of aluminium alloy. Box: 4 1/2 in. x 4 in. x 2 in. (4-hole fixing). Ask for P/H907

2/6 Each 1/- extra

ELECTROLYTIC CONDENSERS

Metal Can. Clip Mtg. Types

Cap. 24-24 mfd., 450 v. D.C. wkg. Dia. 1 1/2 in. x 2 in. Ask for P/H971

3/- Each Post 3d.
Or 3 for 7/6. post paid

Cap. 16-24 mfd., 450 v. D.C. wkg. Dia. 1 1/2 in. x 2 1/2 in. Ask for P/H972

3/- Each Post 3d.
Or 3 for 7/6. post paid

Cap. F-16 mfd., 450 v. D.C. wkg. Dia. 1 1/2 in. x 2 1/2 in. Ask for P/H918

3/- Each Post 3d.
Or 3 for 7/6. post paid

Cap. 32 mfd., 450 v. D.C. wkg. Dia. 2 in. x 2 in. plate. U.S.A. made. Ask for P/H852

1/9 Each Post 6d.
Or 3 for 5/-. post paid

Cap. 3 mfd., 450 v. D.C. wkg. Dia. 1 in. x 2 in. Ask for P/H973

1/9 Each Post 3d.
Or 3 for 5/9. post paid

Cap. 8 mfd., 450 v. D.C. wkg. Dia. 1 in. x 2 1/2 in. Tubular card covered wire ends. Ask for P/H980

1/6 Each Post 3d.
Or 3 for 4/-. post paid

Cap. 50 mfd., 12v. D.C. wkg. Dia. 1 in. x 1 1/2 in. Clip mtg not necessarily. Ask for P/H974

1/- Each Post 3d.
Or 3 for 3/-. post paid

24-WAY GROUPBOARD

Paxolin panel 12 1/2 in. x 2 1/2 in. wide, with holes to carry 24 condensers or resistors. Ask for P/H982

6d Each Post 3d.
Or 3 for 1/6. post paid

PAXOLIN WAFER ROTARY WAVE-CHANGE SWITCH

3 wafers, each 3-pole 5-way. Dim.: 3 1/2 in. x 2 1/2 in. x 2 in. Spindle projects 1 in.; single hole mounting. Ask for P/H975

2/6 Each Post 6d.
Or 3 for 7/6. post paid

CORD DRIVE SPINDLE (Ratio 6:1)

Reverse vernier drive, i.e., cord runs outside chassis. Ask for P/H976

1/- Each Post 3d.
Or 3 for 3/-. post paid

I.F. TRANSFORMER

465 kc/s. Stairard type. Dim.: 3 1/2 in. x 1 1/2 in. x 1 in. Partial and plain. A.D.T. Ask for P/H977

10/6 Per Pair Post 1/-
Or 3 pairs for 27/6. post paid

I.F. TRANSFORMER

465 kc/s. Miniature type. Dim.: 2 1/2 in. x 1 1/2 in. x 1 in. Plain, permeability tuned. Ask for P/H978

10/6 Per Pair Post 1/-
Or 3 pairs for 27/6. post paid

Order direct from:—

CLYDESDALE SUPPLY CO. LTD.

2, BRIDGE STREET GLASGOW CS.

Phone: South 2706/9

FREE TO AMBITIOUS ENGINEERS!

This 144-page Book

Have you sent for your copy?

'ENGINEERING OPPORTUNITIES'

is a highly informative guide to the best-paid Engineering posts. It tells you how you can quickly prepare at home on "NO PASS—NO FEE" terms for a recognised engineering qualification, outlines the widest range of modern Home-Study Courses in all branches of Engineering and explains the benefits of our Employment Dept. If you're earning less than £15 a week you cannot afford to miss reading this unique book. Send for your copy to-day—FREE.

--- FREE COUPON ---

Please send me your FREE 144-page "ENGINEERING OPPORTUNITIES"

NAME
ADDRESS

Subject or Exam. that interests me
British Institute of Engineering Technology
409B, College House, 29-31, Wright's Lane,
Kensington, W.8.

WHICH IS YOUR PET SUBJECT?


- Mechanical Eng.
- Electrical Eng.
- Civil Engineering
- Radio Engineering
- Automobile Eng.
- Aeronautical Eng.
- Production Eng.
- Building, Plastics, Draughtsmanship
- Television, etc.

GET SOME LETTERS AFTER YOUR AFTER YOUR

- NAME !
A.M.I.Mech.E.
A.M.I.C.E.
A.M.I.P.E.
A.M.I.M.I.
L.I.O.B.
A.F.R.Ae.S.
B.Sc.
A.M.Brit.I.R.E.
CITY & GUILDS
GEN. CERL.
OF EDUCATION
etc., etc.

WEYRAD

IRON-CORED COILS

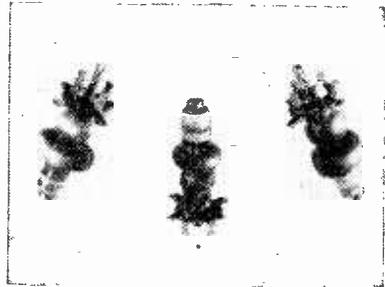

TYPE "H"

Individual Aerial, H.F. Transformer and Oscillator Coils for each band provide continuous coverage from 12 to 2,000 metres, as below:—

- | | | |
|---------|-------------------|-------------------|
| BAND 1. | 800-2,000 metres. | HA1, HH1 and HO1. |
| " 2. | 250-800 | HA2, HH2 and HO2. |
| " 3. | 190-550 | HA3, HH3 and HO3. |
| " 4. | 90-250 | HA4, HH4 and HO4. |
| " 5. | 33-100 | HA5, HH5 and HO5. |
| " 6. | 16-50 | HA6, HH6 and HO6. |
| " 7. | 12-35 | HA7, HH7 and HO7. |

Single Point Fixing. Connections to Four Coded Tags.

RETAIL PRICE.....3/9d. each.

BIET

WEYMOUTH RADIO MFG. CO. LTD.
CRESCENT ST., WEYMOUTH DORSET.

COPPER WIRE

Table with columns: ENAMELLED, TINNED, and rows of wire specifications (e.g., 16 W.G. 2 ozs., 1/4 2/-, 1/4 2/-).

POSTAGE EXTRA.

POST ORDERS ONLY PLEASE.

Send stamp for comprehensive lists.

CRYSTAL SET

INCORPORATING THE SILICON

CRYSTAL VALVE

Adjustable Iron Cored Coil.

RECEPTION GUARANTEED

Polished wood cabinet, 15/-, post 1/-

A REAL CRYSTAL SET, NOT A TOY

POST RADIO SUPPLIES

33 Bourne Gardens, London, E.4

LYONS RADIO LTD.

3, GOLDHAWK ROAD, Dept. W.P., SHEPHERDS BUSH, LONDON, W.12.

Telephone: SHEpherds Bush 1729

RECEIVERS TYPE R.1155. One of the best known and most popular of ex-Government communications receivers.

R.1155 POWER PACK OUTPUT-STAGE UNITS. Designed to operate the R.1155 direct from A.C. mains 230/250v.

L.F.E. UNITS. Less valves and relays fitted with mica tubular, metal cased and variable condensers, resistors, valveholders.

VALVE SPECIAL. VR65A (SP61 4v. htr.) 2/6 each, post 6d., or 3 for 6/- or 6 for 10/-.

BENSON'S BETTER ARGAINS

METERS. New boxed. M.C. 2 1/2 in. P.I. rd., 150 v. (1 m.a. P.S. 14). Recs. 15/8. 1 1/2 in. 30 m.a. 100 m.a., 200 m.a., 300 m.a., M.I. 1 1/2 v. 20 v. Proj. T.C. 1 in. M.C. 30 v. All at 7/- each.

List and enquiries, S.A.E. please! Terms: Cash with order. Postage extra. Immediate despatch.

Callers and Post Callers only W. A. BENSON (PW), SUPERADIO (W chapel) 303 Rathbone Rd., LTD., 118 Whitechapel, Liverpool 13, STD 1604 Liverpool, 1 ROY 1130

BARGAINS IN UNUSED EX-GOV'T. COMPONENTS POTENTIOMETERS. All suitable for knob (not pre-set) (33/1). discount on doz or more, send if you wish! Carbon 2 M. 1/6; 1 M. 1/4; dia. 100 K. 1/6; boxed, 1/9. 1 1/2 in. dia. boxcd. 1/8.

REED & FORD, 2A, BURNLEY ROAD, AINSDALE, SOUTHPORT.

WATERLOO RADIO

VALVES at 2/6 ea., 10 for £1. 2C34 RK34, VR78, D1, VR54 EB34. 6 for 30/- value selection. 174, 374, GB3, 6K7C, 6X4, 6AM6, 6A1, 6W6, 6CH8, 6AT8, 6AU6, 12BB6, 6B2A, 6B16, 6B2, 27T, 1U5, 50C5, 12A6, 6V6G, 35W4, 6C6, 8D3, 6A7, 6F50 VR91, 50L6, 2L6, 7H7, 12SL7, 6AC7, 6L7, 6N7, NR73, ECC31, 6S67, 6SK7, 6S87, 6U6G, Germanium diode 2/- each.

Best Buy at Britain's

SUPER SPECIAL OFFER.—E. M. I. Desk type output meter. Consists of a 2 1/2 in. 1 m.a. meter with full-wave bridge rectifier.

AVO UNIVERSAL METER MODEL 40.—Only slightly used, all tested. A few of those again available at £9.19.6.

BRAND NEW METERS.—2 1/2 in. barrel circuit board panel type. Moving coil 1 m.a. at 22 1/2, 100 micro-amp at 42 1/2, 200 m.a. at 10 1/2.

R.1155 RECEIVERS.—Brand new £11.19.6. Solder £7.19.6. carr. 10/6 extra.

VALVE SPECIAL.—S.T.C. full-wave bridge rectifier. Brand new. Snp. 5/6 each.

VALVE BARGAINS.—Brand New boxed E150 heavy duty output pentode. 6.3 v. 8.8 watts at 7 1/2, 7193 same as 6J5 but with top grid and anode at 6 for 10/6, post paid.

ROTARY TRANSFORMERS.—Ex power unit type 10s input 12 volts. Output 290 volts 95 m.a. and 6.3 v. 2.5 amps.

CHARLES BRITAIN (RADIO) LTD.

11, Upper Saint Martin's Lane, London, W.C.2.

Shop hours, 9-5 p.m. (9-1 p.m. Thursday)

—OPEN ALL DAY SATURDAY—

11-MIDGET COIL PACK KIT 11-

Comprising chassis 3 1/2 x 2 1/2 x 1 1/2. LMS iron cored coils, padders, trimmers, nuts and bolts, wire, sleeving, circuit diagram, 456 Kc. Brand new set. Oct. Valveholders, 2 1/4 in. doz., A.H. Can. Electrolytic, 8 x 500 1/2, 12/- doz., 100 x 80, 6/- doz.; 200 x 12 1/2, 4/6 doz.; 100 x 6 3/4, 2/- doz.; Coils, Coils, P.P. Type 2-1, Q Type 2/3, TRF 4/- pr.; MSS Superhet 6 coils with circuit, 4/- set; HF Dual-wave 290, Oct. Valveholders, 2 1/4 in. Tub Cond. 1 x 500 3/- doz., 1 x 500 2/9 doz.; Asst. Grommets 6d. doz.; 2, 4, & 6 BA Nuts 2/- gr.; Brand new BA Nuts & bolts asst. 2 gr. 5/-; Ex-equip. BA nuts, bolts, washers 2/6 lb.; approx. 500 pieces; PK set of 10 screws 2/6 ea.; 18 SWG Multicoils, 2/6 doz. yds.; 1 mm sleeving 1/- doz. yds.; meg. vol. con. with DP sw. 3/-.

2 WAVE SUPERHET & TRF RECEIVERS Superhet £6 10/-, TRF 5/5/- including all components, valves, cabinet, set. Book of instructions 1/6 post free.

Latest list 3d. Min. P. & P. 1/-.

SUSSEX ELECTRONICS 5, WHITE LODGE CRESCENT, THORPE-LE-SOKEN, ESSEX.

RADIO KIT 19/6

Build this high-quality portable radio for under 45/-! Exceptionally sensitive for twin-triode circuit, using unique assembly system. Can be built by anyone in 45 mins. Size only 6 1/2 in. x 5 1/2 in. x 3 1/2 in. in handsome black-cradle steel case with beautiful black and gold slide stations printed 1/1. See back and gold slide stations printed 1/1. See back and gold slide stations printed 1/1. See back and gold slide stations printed 1/1.

HASTINGS RADIO CO.

18, NORMAN ROAD, ST. LEONARDS, SUSSEX.

OPEN TO DISCUSSION

The Editor does not necessarily agree with the opinions expressed by his correspondents. All letters must be accompanied by the name and address of the sender (not necessarily for publication).

Interference Suppression

SIR,—I have read A. E. Lofting's article on "Radio Interference Suppression" (May issue, and also the petty comments on it by A. Hale, June issue). May I now add my comments to Mr. Lofting's well-written article, trusting they will be accepted as constructive, not destructive.

Dealing with the question of C.T. to earth capacitor arrangements, providing a source of danger, a low rating fuse in all short connected arms affords excellent protection. Some really good units are available on the market, these incorporate cartridge type fuses from 60 mA. upwards.

The question arises of certain motors requiring inductors in the filter units. Before going to the trouble of winding these it would be well worth while investigating the field arrangements of such machines. In many cases the field coils of a two-pole universal series motor are not arranged symmetrically about the armature, but to one side. This results in virtually no inductance in the line which is connected directly to the commutator. If no external inductors are used with this arrangement some of the H.F. interference voltage escapes the reactance path of the capacitor and travels along the conductor to be radiated. In some cases this can be overcome by arranging the two field coils symmetrically about the armature. The result would be an arrangement like Fig. 1 of Mr. Lofting's article, where L1 and L1 would be the series field and where the motor would be the armature. It can be readily seen that by this arrangement the fields tend to act as inductors in a low-pass filter unit. The method is by no means foolproof; self-capacitance of the field coils, together with inductive effects from the H.F. voltage in the armature, all take their toll of its efficiency. However, it is worth a trial. A third capacitor connected directly across the commutator is often desirable to provide a path for the symmetrical H.F. component.

As the oscillatory nature of the brush spark is the main source of interference in this type of motor, attention should always be paid to the brush gear. The spring tension of the bushes should be about 2 lb. per sq. in., and the brush should always be perfectly free in its holder.

Mica should be undercut unless a class "C" brush or its equivalent is used.

Finally, for Mr. Hale's information the majority of washing machines are for use on A.C. mains and have induction motors that require no suppression. —K. R. WALPOLE (Electrical Engineering Instructor) (Exeter).

Amateur Transmitting

SIR,—Can anyone wonder why there is so much red tape attached to radio transmitting when we get this reaction as exemplified by the correspondent in the July issue.

All because Mr. Bradley wanted to work a walkie-talkie without having to have the same qualifications and conditions of a chap on 100 watts. (Would one have to have a master mariner's certificate to set sail in a 12-footer?) Incidentally, we all know that when the war was on all sorts of chaps—Home Guard and the rest—were playing about with walkie-talkies. How many of them had heard of the morse code? How many could read a circuit? But, of course, there are no essential stations during war time!

Ham radio, over the years, has built up a tradition to which its adherents are fanatical. By their standards it is a crime that there should be an easy way to transmitting. There must, it seems, be some test, some ordeal, by which only the brave and the strong

shall survive. Thus, this mutual admiration society can, by licking the hand of authority, perpetrate its philosophy over all.

Can they get away with it for ever?

The influence of change in other countries might open things out. Or we might get a modern William Wilberforce (if only some V.I.P. could be interested). By the way—how many saw the TV film, "Back of Beyond"? The farmer's wife calling her neighbour on the trans-receiver—the chap with the portable relaying the message for a doctor. Wonder if they would be interested in Atlantic conventions or compulsory morse tests?

Finally, I'd like to point out that if a novice band were created it must be isolated from "Ham" radio—a thing apart. It must have its own code and frequency and not be just an unwanted appendix. —HECTOR COLE (Workington).

Mathematics and the Service Engineer

SIR,—Mr. Apps, in his brief reply to the comments of Mr. W. F. Ritchie, jumps with surprising verbal agility from the mathematical frying-pan to its associated fire.

Such sweeping statements which imply that the mathematical ability of a successful candidate in the General Certificate of Education does not go beyond simple arithmetic cannot be left unchallenged. It is extremely questionable whether a candidate at "O" level would succeed on arithmetical ability alone; I am sure the examiners never intended this. If

Whilst we are always pleased to assist readers with their technical difficulties, we regret that we are unable to supply diagrams or provide instructions for modifying surplus equipment. We cannot supply alternative details for receivers described in these pages. WE CANNOT UNDERTAKE TO ANSWER QUERIES OVER THE TELEPHONE. If a postal reply is required a stamped and addressed envelope must be enclosed with the coupon from page iii of cover.

Mr. Apps' remarks are applied to the papers at Advanced and Scholarship levels, then his comments are patently false. Please, Mr. Apps, be more specific and less misleading.—G. W. F. ASHFORD (King's Lynn).

SIR,—Your contributor, Mr. Apps, in his reply to the letter of Mr. W. F. Ritchie, does not save himself by the assertion that people who have attained the level (he does not say which level) of the General Certificate of Education can tackle only simple arithmetical problems.

A glance at the syllabuses of the Northern Universities Joint Matriculation Board reveals that, for the "Ordinary" level, there are three papers of two, two, and two and a half hours each, dealing with Arithmetic and Trigonometry, Algebra and Geometry respectively.

The syllabuses for the "Advanced" and "Scholarship" levels of the G.C.E. in "Mathematics" and in "Mathematics and Theoretical Mechanics" make it clear that these levels are well beyond the standard required for the Ordinary National Certificate.

Whichever level Mr. Apps was referring to, it is quite clear that he is wrong, and I would suggest that he makes sure of his facts before galloping into print in future.—J. W. WHITEHEAD (Headmaster, Central High School, Leeds).

Dabbler

SIR,—In your June issue of PRACTICAL WIRELESS— which, by the way, I have had from the first number, and *Amateur Wireless* before that—Thermion asks: what is a dabbler? He goes on to expose some of the so-called radio engineers and good luck to him.

I suppose I would now qualify as a "dabbler" but for many years past I was a professional radio engineer and I can vouch for Thermion's statement as to sharp practitioners—I worked for some. But only this week an old customer of mine phoned to ask if I would repair his set (I have many of these). The set was one I built 12½ years ago and this was the first time it had gone wrong—worn out switch contacts.

I put in a new switch and my friend has asked me to build him a "gram." He has no faith in shop-made stuff, he says.

So thank you, Thermion, for your straight-from-the-shoulder speech on our behalf. I shall keep on "dabbling" which helps me and helps the people who like a square deal at a right price.

The gentleman I made the set for is only one of many, I am proud to say, who will not allow anyone else to touch their sets.—PERCY IMHOF (Walthamstow).

Battery Sets

SIR,—I was very interested in H. Whetter's letter, in May issue, on "Battery Receivers." I do certainly agree that a set that is badly needed is the

one for the over 60s (mains and battery) as stated (also at the right price). I do not, however, agree altogether with regard to the reason many people prefer a battery set to a mains set (because it is much quieter in operation), but go for a mains set because the majority of battery sets give such poor reproduction. It is, however, true to say that battery sets generally do not render such a good performance as they are so much more sensitive than a mains set, in that they are more easily rendered inefficient in their operation by high resistance connections to their operating supplies, and also corrosion set up by fumes, etc., from accumulators and spent batteries within the set itself. I would like also to say that many people are not able to use a mains set for lack of mains supply. I do, however, think that most people prefer a "mains set" because of the following reasons:

1. Cheaper by far to operate.
2. No worry with the changing of accumulators, etc.
3. No 13s. 9d. or so for H.T. batteries every three or four months.
4. More efficient in operation.—J. H. ROBINSON (Fife).

TRANSMITTING TOPICS

(Continued from page 478)

Appendix C. Additional calculation formulae:

$$\text{Resonant Frequency: } f = \frac{10^6}{2\pi\sqrt{LC}} \text{ Kc/s.}$$

L is in micro-henrys; C is in pico-farads and π is 3.142.

$$\text{"Q" Factor of Circuit: } Q = \frac{2\pi fL}{R} = \frac{\omega L}{R}$$

f is in cycles/sec., L is in Henrys and R is in ohms.

COIL INDUCTANCE:

1st Adaptation of Wheeler's Formula:

$$L = \frac{N^2 \cdot r^2}{10l + 9r}$$

L is in micro-henrys, r is outside radius of the coil in inches, l is the winding length in inches and N is the number of coil turns.

2nd Adaptation of Wheeler's Formula:

$$N = LX \left(1 + \sqrt{1 + \frac{9}{aLX^2}} \right)$$

N is the number of turns, L is the inductance in micro-henrys, a is the outside radius of the coil in

inches, X equals $\frac{20}{nd^2}$ where n is the number of turns

per inch and d is the coil diameter in inches.

40 gauge enamelled wire has 188.7 t.p.i.

32 gauge enamelled wire has 85.47 t.p.i.

Editorial and Advertisement Offices:

"Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Phone: Temple Bar 4368.

Telegrams: Newnes, Rand, London.

Registered at the G.P.O. for transmission by Canadian Magazine Post.

The Editor will be pleased to consider articles of a practical nature suitable for publication in "Practical Wireless." Such articles should be written on one side of the paper only, and should contain the name and address of the sender. Whilst the Editor does not hold himself responsible for manuscripts, every effort will be made to return them if a stamped and addressed envelope is enclosed. All correspondence intended for the Editor should be addressed: The Editor, "Practical Wireless," George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2. Owing to the rapid progress in the design of wireless apparatus and to our efforts to keep our readers in touch with the latest developments, we give no warranty that apparatus described in our columns is not the subject of letters patent. Copyright in all drawings, photographs and articles published in "Practical Wireless" is specifically reserved throughout the countries signatory to the Berne Convention and the U.S.A. Reproductions or imitations of any of these are therefore expressly forbidden. "Practical Wireless" incorporated "Amateur Wireless."

EX-A.M. RECEIVER TYPE R1155



Brand new and unused
5 Frequency ranges: 18.5-7.5 Mc's; 7.5-3.0 Mc's; 1,500-600 Kc's; 500-200 Kc's; 200-75 Kc's
Supplied in maker's original wood transit case. LASKY'S PRICE, £11 19 6. Complete. R.1155 Receivers. Secondhand aerial tested, £7 19 6.
Carriage and packing: 12/6 per unit extra, including 1/-, which will be refunded on return of packing case.

ASSEMBLED POWER PACK OUTPUT STAGE FOR R1155 RECEIVER

For use on 200-250 v. A.C. mains. Complete with 2 valves. In metal case size: 12 x 7 x 5 1/2 ins. LASKY'S PRICE, 79.6. Carr. 5/- extra.
Power Pack as above. Fitted with 6in. d.m. speaker. LASKY'S PRICE, £55/- Carriage 5/- extra.

PLASTIC ESCUTCHEON MASKS

With dark screen filter.
12in. 12/6
16in. 25/-

MAGNETIC RECORDING TAPE By Famous Manufacturer.

Elastic, on Cyloid metal spools.
630ft. 6/11. Postage 1/6 ex.
1,200ft. 14/11. Postage 1/6 ex.

CRYSTAL DIODES

Glass type. Wire ends, 1 1/8 each.

LINE FLYBACK E.H.T. TRANSFORMER

Output 7.9 kv. E.H.T. with heater winding for EY51. 19.6.

6V6	7/6
3Z5A	9/-
6AM6	7/6
6H6	2/6
EF50, Red	
New Sylvania	10/-

1S1	7/6	1A5	9/-
3S4	9/-	12K3	8/6
1T4	7/6	12Q7	8/6
1R5	7/6	CAL5	3/-
1S7	7/6	6K7	4/6
1C5	7/6	1D5	8/6

VALVES, 10,000 IN STOCK AT THE LOWEST POSSIBLE PRICES. SOME EXAMPLES

SPECIAL OFFER, 4 Valves: 1 each
1R5, 1T4, 1S5 and 3S4.

LASKY'S PRICE 30/- POST FREE

6J7	6/6	EF39	7/6
6Z4	3/6	12K7	10/6
6E2	3/6	6L5	10/6
6K8	8/-	EA5	2/6
U50	7/6	EBC43	7/6
ECH35	13/6	35L5	10/-

CAR RADIO SPECIAL—PARTLY ASSEMBLED CAR RADIOS


Small size case, 12 x 4 x 6 in. Will fit most cars. For either 6 or 12 volts depending on vibrator. Chassis supplied with 5 octal valve holders, medium wave aerial and oscillator coils, output transformer, volume control, sundry resistances and condensers. Case finished in brown crackle. Dial calibrated 150-550 metres. 5 valves to suit. One each, either GT or metal: LASKY'S PRICE £25.5. Carriage 5/- extra. Or less valves, 69.6. Carriage 5/- extra. Other chassis in various conditions of completion are available for personal callers only. CIRCUIT for 5 valve car radio, using above chassis. PRICE 1.6.

COLLAPO 3-SPEED CHANGERS
Studio xtal. turnover p.u. £9/19/6.

LASKY'S RADIO, 370, HARROW ROAD, PADDINGTON, LONDON, W.9.

Telephone: CUNningham 1979-7214.
Hours: Mon. to Sat. 9.30 a.m. to 6 p.m.; Thurs. half day 1 p.m. Postage and packing charges (unless otherwise stated): on orders value £1.-1s. 0d. extra; £5.-2s. 0d. extra; £10.-3s. 6d. extra; over £10 carriage free. All goods fully insured in transit.

CYLDON 5-CHANNEL SWITCHED TELETUNERS

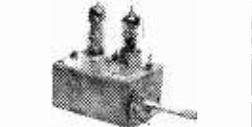

Instant and positive selection of any one of the 5 R.B.C. telev-slot channels, by a single control knob. Uses EF-80 R.F. pentode and ECC81 or 12AT7 Double Diode Triode as frequency changer. Tuning is obtained by switching incremental inductances. Size: 4 1/2 x 2 1/2 ins. Spindle 2 1/2 in. long. 1 in. diameter I.F. Output 9.5-14 Mc's, noise figure on all channels better than 10.5dB. I.F. rejection better than 45dB on all channels. Power gain 24dB. LASKY'S PRICE.....12/6 Postage 2/6 extra. Valves for tuner available, at 12/6 each.

I.E. TRANSFORMERS
MINIATURE TYPE 465 Kc/s. 4 x 1 x 2 1/2 ins. PRICE, 9/6 pair.
MIDGET TYPE 465 Kc/s. 1 x 1 1/2 x 2 1/2 ins. PRICE, 8/6 pair.
WEARITE TYPE 550. 445-520 Kc/s. 8/6 per pair.
WEARITE TYPE 500. 450-470 Kc/s. 8/6 per pair.

LOUDSPEAKERS
First Quality. All 3 ohms speech coil. Less output trans.
3in.....14/6 6in.....15/-
4in.....12/6 8in.....19/11
5in.....14/6 10in.....19/6
Now available. 12in. Goodmans heavy duty. 15 watts, 15 ohms.
LASKY'S PRICE, £5/10/3. Carriage 3/6 extra.

RADIO SUPPLY CO. (LEEDS) LTD. 32, THE CALLS, LEEDS, 2

Terms C.W.O. or C.O.D. No C.O.D. under £1. Postage 1/- extra under 10/-, 1/6 extra under £1. 2/- extra under £2, 2/6 extra under £3. Open 9 to 5.30. Sats. until 1 p.m. Catalogue 6d. Trade List 5d. S.A.P. please with enquiries.

SELENIUM RECTIFIERS

L.T. Types		H.T. Types H.W.	
2/6 v. 1 a. H.W. 1/9		70 v. 20 mA. 2/11	
6/12 v. 1 a. H.W. 2/9		50 v. 30 mA. 3/6	
		120 v. 40 mA. 3/9	
		RM2 125 v. 100 mA. 3/11	
		RM3 125 v. 124 mA. 2/9	
		6/12 v. 1 a. 4/9	
		6/12 v. 2 a. 8/9	
		250 v. 50 mA. 4/11	
		250 v. 60 mA. 6/11	
		RM4 250 v. 250 mA. 10/11	
		6/12 v. 9 a. 19/9	
		6/12 v. 10 a. 29/9	
		300 v. 275 mA. 12/9	

Following suitable for chargers, etc.
8.8 v. 4 a. 9/9; 0-11-22 v. 30 a. 72/6;
0-11-22 v. 15 a. 35/9; 0-16-18-20 v. 35 a.
79/6; 7.7 v. 7 a. C.T. 4 times, 25/9.

Misc. Types
250-0-250 v. 40 mA. 6.3 v. 2 a. 5 v. 2 a. 9/11;
48 v. 1 a. 9/9; 175 v. 100 mA. 9/9; 300 v.
200 mA. 9/11; 450 v. 200 mA. 6.3 v. 5 a. 27/9;
2,800 v. 30 mA. 22/9; 400 v. C.T. 150 mA.
4 v. 6 a. 6.3 v. 6 a. 6.3 v. 0.6 a. 4 v. 6 a. 1 v. 3 a.
4 v. 3 a. 5 v. 2 a. 22/9; 1,220 v. 350 mA. 610-0-610 v. 150 mA.
400-0-400 v. 150 mA. 29/9; 895-775-0-895-775-865 v. 500 mA. 29/6;
4 v. 2.5 a. 4.9; 4 v. 6 a. High Ins., 7/9. All 50 c.c.

EX GOVT. AUTO TRANSFORMERS

Double Wind. 50 c.c.s.
10-0-20-220-240 v. to 10-0-270-200-310 v. 200 watts, 25/9;
0-230 v. to 15-10-0-5-195-215-235 v. 200 watts, 26/9;
10-0-200-220-240 v. to 10-0-275-295-315 v. 500 watts, 69/6;
0-230 v. to 0-230 v. (tapped every 11 volts); from 57.5 v. 5,000 watts (21 amps), 26/15-sz. winding 0-110-190-230 v. 400 watts, 49/6.

RHOSTATS (Variable Resistors)

Suitable chargers, speed control, etc. 2 ohm, 5 a. 7/9; 7.5 ohm, 5 a. 7/9; 0.4 ohm, 25 a. 8/9; 150 ohm, 1.5 a. 11/9. All complete with Control Knob.

AMPLIFIER OR CHARGER CASES
Size approx. 15 x 5 1/2 x 7 in. high. Strongly made in perforated steel. Finished in grey enamel. 9/6.

AMMETERS
Moving coil, G.E.C. 0-5 amps, 2in. scale, 11/9.

EX-GOVT. SMOOTHING CHOKES	
250 mA. 10 H 50 ohms	14/9
250 mA. 10 H 100 ohms	14/9
150 mA. 10 H 100 ohms	11/9
100 mA. 10 H 150 ohms Trop.	8/9
50 mA. 5-10 H 200 ohms	2/9
L.T. type 1 amp.	2/9

EX-GOVT. METAL BLOCK (PAPER) CONDENSERS
4 mfd. 500 v., 2/9; 4 mfd. 750 v., 3/9; 4 mfd. 1,500 v., 4/9; 4 mfd. 2,000 v., 7/9; 6-4 mfd. 400 v., 5/11; 11 1/2 mfd. 500 v., 7/9; 4 mfd. 400 v. plus 2 mfd. 250 v., 1/11; 8 mfd. 300 v., 4/9; 15 mfd. 500 v., 5/9.

EX-GOVT. E.H.T. SMOOTHERS
0.02 mfd. 8,000 v. cans. 111; 25 mfd. 4,000 v. Blocks, 4/9; 5 mfd. 2,500 v. Blocks, 3/9; 5 mfd. 3,500 v. cans. 3/3; 1.5 mfd. 4,000 v. Blocks, 5/9; 1 mfd. plus 1 mfd. large Blocks 8,000 v., 9/6.

LONDEX RELAYS
For 230 v. 50 c.c.s. mains, 4/9.

TV. PREAMPLIFIER (Plessey).
For Fringe Areas. Brand New. Complete with 6F7 valve. Under 22/6.

EX-GOVT. ACCUMULATORS
With Non-Spill Vents. Unused and guaranteed 2 v. 16 A.H.; 5/9 each or 3 in wood carrying case 9 7/8 ins., 14/9, plus 5/- carr.

MIDGET MAINS TRANSFORMER.
Manufacturers Surplus. Primary 220, 240 v. Secs. 250-0-250 v. 50 mA, 6.3 v. 2 a. 10 v. 8/9.


R.S.C. MASTER INTERCOM. UNIT
with provision for up to 4 "Listen-Talk Back Units" individually switched. A high gain amplifier enables speech and other sounds emanating from the rooms containing remote control units to be heard at the master control. The unit is in kit form and point-to-point wiring diagrams are supplied. A walnut veneered wood or Brown Bakelite cabinet is included. Mains input is 200-250 v. 50 c/s. H.T. line 300 v. CHASSIS IS NOT "ALIVE". Ideal also for use as "Baby Alarm". Sound amplification 4 watts. Price only 25/-9.6. "Listen-Talk Back Unit" can be supplied at 30/- each. Full descriptive leaflet 10d. The Master Unit can be supplied assembled and tested for 30/- extra.

EX-GOVT. VALVES (NEW)			
Each	Each	Each	Each
1T4	7/11	6SK7Met 7/9	25Z4G 9/6
1R5	7/9	6S7Met 7/9	35Z4GT 10/6
1S5	7/9	6SN7GT 1/9	35Z4GT 9/11
3V4	7/11	6SN7GT 1/9	ASpent 10/9
5Y3G	8/9	6V6G 8/9	UL41 10/9
5U4G	10/6	6V6GT 7/9	EF36 5/9
5Z4G	9/6	6X5GT 8/9	EB71 8/9
6AL5	8/9	6D2 2/11	EF91 6/9
6F6G	7/11	6E7 1/11	MU4 9/6
6AM6	6/9	9D2 2/11	MS/Ten 5/9
6J5G	5/9	12A6 7/9	SP4 5/9
6J7G	6/6	12K7CT 10/6	SP11 1/11
6K7G	5/11	12Q7CT 10/6	SP61 2/9
6X8G	8/9	15Z2 4/9	VO120 2/11

H.T. ELIMINATOR AND TRICKLE CHARGER KIT. Input 200-250 v. A.C. Output 120 v. 40 mA. fully smoothed, and rectified supply to charge 2 v. acc. Price with steel case and circuit, 29/6. Or ready for use, 8/9 extra.

SILVER MICA CONDENSERS. 5, 10, 15, 20, 25, 30, 35, 40, 50, 100, 120, 150, 200, 230, 400, 500, 1,000 (0.01mfd.), 2,000 pfd. (0.02 mfd.), 50, each; 3/9 doz. One type.

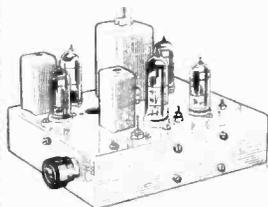DO YOU LIVE IN LONDON, S.E. ENGLAND, OR THE HOME COUNTIES?




If so you can receive the 90 mes VHF super quality transmissions and enjoy a new radio thrill! The superb quality has to be heard to be believed. No static, mush, or interfering stations. This is the NEW THING in radio. This Maxi-Q tuner can be built for about £8 complete. Send for full instructions, drawings, circuit, and parts list, price 1/6. TO-DAY.

Another HOME RADIO winner!

The "HOLIDAY FOUR"

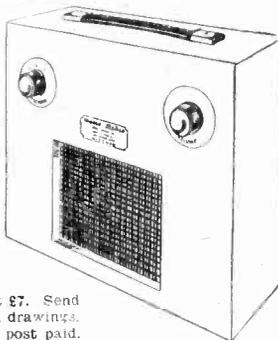A four valve superhet all-dry portable with amazing quality and volume. Ideal for camping, boating, touring, holidays, etc. Frame Aerial and pre-set stations. Can be assembled in a couple of hours at a cost of about £7. Send today for full instructions, drawings, circuit, and price list, 1/- post paid.



HOME RADIO OF MITCHAM

187, LONDON ROAD, MITCHAM, SURREY. MIT 3282.

Open every day including Saturdays until 6.30 (Wednesdays 1.0)

VALVE VOLTMETER VV50

measures 0-2.5, 5, 25, 50 and 250 volts D.C (5 ranges) with input impedance of 11 megohms, that is, over 4.4 megohms per volt on lowest range. Direct readings are given on standard 2 1/2 in. meter having 100 micro-amp movement. A special three way probe unit which is supplied enables AF and RF voltages to be measured with same ranges as for D.C. The rms value is indicated. Polarity reversing switch enables positive or negative readings with respect to earth to be taken. Specially designed for bench use with case and panel of 18 gauge steel finished black crackle. Complete with valves and instructions for 200/250 volts A.C. Price £7.19.6, plus 4/6 carr. SPECIAL OFFER of 10/- discount for one month ONLY.

CAPACITY RESISTANCE BRIDGE CR50

measures 10pFd to 100mFd and 1 ohm to 10 megohms in fourteen ranges with leakage test for condensers. Balance indication given by magic eye fed from high gain pentode. Housed in similar matching case to VV50 meter. Entirely complete with valves and instructions, only £6.19.6, plus 4/6 carr.

SIGNAL GENERATOR SG50

covers 100kc/s to 80 Mc/s on fundamentals (not harmonics) either unmodulated or internally modulated with 400 cycles. Uses EF91s and SenTerCel rectifier. Price £7.19.6, plus 6/- carr.

NOTE that all the above are current manufacture (not surplus) and are supplied with the guarantee that if not satisfied you may return within three days and money refunded IN FULL. Obtainable from Charles Britain (Radio) Ltd., 11 Upper Saint Martin's Lane, London, W.C.2, or direct from the manufacturers. Please send stamped addressed envelope for further particulars. H.P. terms available.

GRAYSHAW INSTRUMENTS,

54, Overstone Road, Harpenden, Herts.

FREE

POST THE COUPON TODAY FOR OUR BROCHURE ON THE LATEST METHODS OF HOME TRAINING FOR OVER 150 CAREERS & HOBBIES

NEW!

EXPERIMENTAL OUTFITS INCLUDE: Radio, Television, Mechanics, Electricity, etc.

P.M.G. Certificates, City and Guilds Grouped Certificates in Telecommunications; A.M. Brit. I.R.E. Examination, Radio Amateur's Licence, Radio and Television Servicing Certificates, General Radio and Television Courses, Radar, Sound Recording, etc. Also Courses in all other branches of Engineering.

COURSES FROM £1 PER MONTH

POST THIS COUPON TODAY

Send without obligation your FREE book E.M.I. INSTITUTES. Dept. 32k, 431 Grove Park Road, London, W.4.

E.M.I. INSTITUTES

NAME _____

ADDRESS _____

The only Postal College which is part of a world-wide Industrial Organisation.

Subject(s) of interest _____
A.T.G. IC18

G2AK This Month's Bargains G2AK

FISK SOLARISCOPIES.—Complete with charts. Give World time, light and darkness paths. Invaluable to the DX man. List, 2/1/-, our price 7/6, post free.

PANL Home Crackle. Black, Brown or Green, 3/6 bottle. P. & P., 1/-.

TEST METER. 7 ranges as follows: 1.5 v. 3 v. 150 v. 6 ma., 60 ma., 5,000 ohms, 25,000 ohms, 2 1/2 in. Dia. scale M.C. meter. Rotary selector switch, Black bakelite case, 6 x 4 1/2 x 4 1/2; fitted with removable lid, also provision for internal batts; ranges can be easily extended. Bargain Price, 30/-, plus 1/6 post.

MULTI-METER BASIC UNIT.—400 Microamp. F.S.D., scaled 8 ranges A.C./D.C. volts, HI and LO ohms, complete with rectifier made by Triplett, U.S.A. Only 32/6 post free.

VIBRATOR UNITS. 6 v. in., 230 v. ma. out., 30/-; 12 v. in., 300 v. 100 ma. out., 39/6. Few only.

CRYSTAL HAND MICROPHONES. High quality, very sensitive. Chrome finish, complete with screened lead and standard jack plug. Our price only 25/- ea. Few only.

VALVES. B7G base, 1T4, 1S5, 1R5, 1S4, 354, 3V4, 7/6 ea., or 4 for 27/6. 807's, 10/- ea. or 2 for 17/6. Most of the 1.4 v. B7G range available at 8/6 ea.

HEADPHONES. Low resistance type CLR No. 3, 9/6, DLR No. 2, 13/6. High resistance CHR Mark 2, 17/6, and the most sensitive of all DHR. No. 5B, 18/6 per pair. P. & P. 1/- pair.

METERS. 0-5 ma. 2 in. square, 10/-; 0-50 ma., 7/6; 0-10 A. D.C., 7/6; 0-1 ma. 20/-; 0-350 ma. thermo, 7/6; 0-4 A. 5/-; 2 1/2 in. flush 0-100 mA, 0-10 mA, 12/6 ea. Germanium Diodes, 2/- ea., or 6 for 9/-.

Deaf-Aid Crystal mike units, 12/6 ea. **V.H.F. FANS.** Air space Co-axial Cable, 150 ohm, good to 600 Mc/s; normal price, 3/11 per foot. Our Price, 20 yard coil, £1. Very limited quantity available.

Postage free on all orders over £1 except where specifically stated. **PLEASE PRINT YOUR NAME AND ADDRESS.**

G. H. YOUNG, G2AK

All callers: 110, Dale End, Birmingham 4 (CEN 1635) Mail Orders: 102, Holloway Head, Birmingham 1 (MID 3254)

RADIO BARGAINS— NEW, SURPLUS, CLEAN COMPONENTS

SPEAKERS.—5 in. P.M. Boxed, 15 6. 5in. M.E. 1.000 ohm field with Pen. tra. s. 15-. 6in. P.M. 15 6. All above 2-3 ohm.

RADIO COILS.—Crystal Set Coil, 2/6. H.F. Coil, 4/-. T.R.F. Pair, 8/-. These are all midget Polystyrene type and are supplied boxed with suggested circuits enclosed. We stock also: Denco, Csmor, Weymouth, Wearite.

SPEAKER TRANSFORMERS.—New Goodman's Standard Pentode type, 4 6 Triode type, 30 : 1, 3/6 Midget Mains Pentode, 4/9. Super Midget Battery 184, 8/4. DL92, etc., 5/-. 6V P/pull Filstone MR7, 18/9.

MISCELLANEOUS.—Pair of test Prods, 1/9. 2 gang .0005 mfd., 6/-. Crystal Diodes, 1/6. Tyana Soldering Iron, 14 11. Adcola Pen-ll Bit Iron, 25/6. Henley Instrument Iron, 18 9.

BOOKS.—Radio Servicing Instruments, 4 6. How To Make Electronic Gadgets, 3/6. T.V. Fault Finding, 5/-. Personal Receivers and Power Packs, 5/-. The Oscilloscope Book, 5/-. Book of Valve End Tube Equivalents, 2/-. Valve Data Book No. 1, 5/-. No. 2, 5/-. HIGH STABILITY PRECISION RESISTORS, 1 w. 2%, 100 ohms to 2 mg. (preferred values), 1 6 each. 1 w. and 1 w. Standard Resistors, 4d. each. Midget, 6d. 1 w. 6d. Wirewound 7 watt max., 2/3. 10 w. max. 2/9. (Up to 10K only.)

DENCO COILPACKS.—CP1L, 33 4 : CP4M, 33 4 : CP3 500, 42/8. Boxed with Circuit.

VOLUME CONTROLS.—Long Spindles, less switch, 2 6. With S.P. switch, 4/-. D.F. switch, 5/9. (Any standard value.) Wirewound Colvern Pre-set type CLR901, 250 ohms to 20K, 3/2 each. Midget Wirewound for L/speaker controls, .25 ohm, 100-ohm, 50 ohm, 5/6 each.

ELECTROLYTICS.—New. Wire-end, 8 mfd, 450 v., 2/6. 16 mfd, 450 v., 3/6. 32 mfd, 500 v., 6 6. Special Offer of French 8 mfd, 500 v. 1/6 each, four for 5/-. 100 mfd, 25 v., 4 -. 25 mfd, 25 v., 1 6. 25 mfd, 50 v., 1 6. 50 mfd, 50 v., 50 mfd, 50 v., 52 -. 9 16 mfd, 50 v., 5/-. 8-8 mfd, 500 v. (chassis type), 4 8. 16-24 mfd, 350 v. 5/6. 2 mfd, 350 v., 1/3. Special Offer : Italian 8 mfd, 500 v. Card Tubular 1 10 : Box of 10 17 6.

VALVES.—6X5GT 7/6. 6V6G, 7/6. 6U5 7/-. 6BW6, 8/-. MS PEN, 6/6. KTZ41, 5/-. 6KT7, 7/6. 6KTG, 7/6. VU39A, 8/-. 6AM6, 7/-. **CONDENSERS.**—0031, .0022, .0033, .001, .005, .01, .02, .05, .1 mfd., 6d. each. .5 mfd., 1/-. 1/-. each. .5 mfd, 400 v. (large type), 8d. each. 5/- per doz.

Price Booklet of Bargain Components 6d.
Valve List or Quotation S.A.E.

Post 6d. up to 5/-. 1/- up to £1. 1 6 to £2, C.O.D. (over £1).

RADIO SERVICING CO. 82, SOUTH EALING ROAD
LONDON, W.5.


EALING: 5737. Next to South Ealing Tube Station.

DIRECT FROM THE MANUFACTURER

DULCI RADIO/RADIOGRAM CHASSIS
Built to Highest Technical Standards

FULLY
GUARANTEED

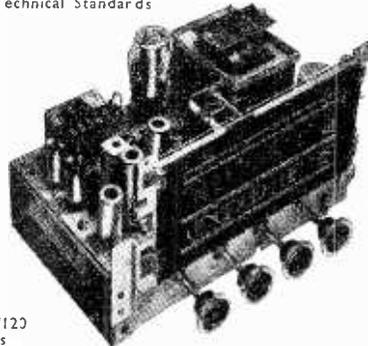All chassis 11in. x 7in. x 8in. high. Latest type valves 6BE6, 6BA6, 6AT6, 6BW6, 6X4. Flywheel tuning. Negative feedback over entire audio section. Engraved knobs. 3 tone positions for radio and gram.



For A.C. Mains 100/120 and 200/250 volts

- Model B2.—Long, Medium, Short 5 Valves, Output 31 watt **£12/12/0**
- Model B2.—Plus Push Pull Stage 6 Valves, Output 6 watt **£15/15/0**
- Model B3.—Double Feature with P/Pull C. R.F. Stage, 7 Valves, Output 6 watt **£18/18/0**
- Model B6.—8W Wavebands, Med., Long, 4 Short, 3 Bands per stage, 5 valves, Output 32 w. **£15/15/0**
- Model B6.—Plus Push Pull Stage 6 Valves, Output 6 watt **£18/18/0**
- Model B6.—Double Feature with P Pull & R.F. Stage, 7 Valves, Output 6 watt **£23/2/0**

ALL PRICES TAX PAID

Escutcheon for 9in. x 5in. dial, 4/9 extra. Matching speakers P.M. type 3 ohms, 6in. or 10in. available. Chassis sent under money back guarantee conditions against remittance. Free particulars from the manufacturers.

THE DULCI CO. LTD.,

99 VILLIERS RD., LONDON, N.W.2. Telephone: Willesden 7778

WE PAY TOP PRICES

FOR
AMERICAN SURPLUS ELECTRONIC EQUIPMENT
LOOK AT THESE EXAMPLES

For equipment in good condition

Receiver, R54/APR4 complete	£200
Transmitter, ET436	£110
Searcher, RC4	£100
Test Set, TS13	£100
Frequency Meter, TS175/U	£80
Frequency Meter, BC221	£26
Receiver, BC348R	£25
Receiver, R89 ARN5	£25
Control Box, 22270	£5

We pay similar remarkable prices for:

- RECEIVERS, R111 APR5, R5/ARN7, AR38D, BC1033, BC348.
- TRANSCIVERS, ARC1, ARC3, TCS, BC900, RT1 APN2.
- TRANSMITTERS, T11 APN3, ART13.
- INDICATORS, ID17 APN3, BC1151, I-81A.
- TEST SETS, Any unit with prefix "TS" and IE19, I-208, I-100.
- MODULATORS, BC1091, BC1142.
- SYNCHRONISER, BC1148.
- POWER UNITS, RA34, RA42, RA52, RA88, RA99, MG149, PE99, PE158, DM28, PUL6.
- TUNING UNITS, TN17, TN19, TN19, TN54, TU57, TU59, TU59.
- CONTROL GEAR, BC1150, BC1145, JB91, JB95, JB99, JB102, C45-ARC1.

And almost every American made unit even if not mentioned above. Phone us immediately, transfer charge.

TO OVERSEAS BUYERS

We have the largest stock in Europe of American Government surplus electronic equipment and we would be pleased to quote by return of post against your enquiries. The following are a few examples only of the equipment which we can supply from stock.

- ET436 Transmitter.
- SCR20C Search Radar, complete.
- BC349 Receiver.
- ART13 Transmitter.

Deal with the firm that has been established for twenty-five years.

ALTHAM RADIO COMPANY
JERSEY HOUSE, JERSEY STREET, MANCHESTER 4.
Telephone: Central 7834/5/6.

SAFEGUARD YOUR SET ECONOMICALLY

55' FOR 5/-

AND NOT AN INCH WASTED

ERSIN
Multicore
SOLDER



ERSIN MULTICORE SOLDER makes every electrical connection in your equipment a sound, permanent joint. Countless jobs—construction, repair—can be done with one 5/- carton. And because ERSIN MULTICORE contains 3 cores of extra-active, non-corrosive Ersin Flux to prevent oxidation, 'dry' and H.R. joints, it solders instantly, without trouble, waste or extra flux. Get a carton today.

MULTICORE SOLDERS LTD.
MULTICORE WORKS, HEMEL HEMPSTEAD, HERTS • BOXMOOR 3636.

RECEIVERS & COMPONENTS

R.F. UNITS. Types 26 at 37/6, 25 at 17/6, 24 at 12/6; brand new in original cartons. E.W.S. CO., 69, Church Rd., Moseley, Birmingham.

WINWOOD FOR VALUE. One-valve Receiver kit, incl. valves and battery. 23/6. Push-pull Amplifier kit, incl. 5 valves. 27/19/6. Inter-cont. Master Unit, ready for use. 25/19/6. Cabinet kit, comprising cabinet, chassis, dial, drum, drive, pointer, knobs, etc.. 23/6, post 1/4. Tuning Conds., Std. 0005 5/6, 465Kcs I.F.s 8/6 pair. 1/2 doz TRF Coils, 6/- pr. Resistors, 3/- doz. Small waxed Conds., .01, .04, .001, .002, .005, 1/6 doz. 32 x 32mf, 350v Can. 3/6. List available. WINWOOD, 12, Carnarvon Road, Leyton, E.10. Mail only

OSMOR for really efficient Coils, Coilpacks, and all Radio Components as specified for many "Practical Wireless" circuits. See advert. on page 451 for free circuits offer, or send 5d. (stamps) to OSMOR RADIO PRODUCTS LTD. (Dept. PCB), 418, Brighton Road, South Croydon. (Tel.: Croydon 5148/9.)

SALE, bargain, Battery sw. Rk. 3 valves, excellent DX. 190-8M. set and spread; very portable; ideal outdoor use; with phones; perfect; o/s? S.A.E. for details. Box No. 248, c/o PRACTICAL WIRELESS.

ELECTROLYTICS, capacity, voltage, size, type, of mounting, price post paid; 8. 450v, 1 x 2, clip. 2/-; 50, 12v, 3 x 1 1/2, tag. 1/6; 150, 25v, 4 x 1 1/2, clip. 2/-; 250, 12v, 3 x 1 1/2, wire. 2/3; 16 + 16, 450v, 1 1/2 x 2, clip. 4/-; 40 + 40, 275v, 1 1/2 x 2, clip. 3/3; 24 + 24 + 16, 350 425v, 1 1/2 x 2, clip. 4/9; 60 + 200, 275 350v, 1 1/2 x 1 1/2; 500 6/6; 4, 150v, 1 x 1 1/2, clip. 1/1; 500 12v, 3 x 1 1/2, tag. 1/6; 150, 25v, 4 x 2, clip. 1/9; 32 + 32, 350 425v, 1 1/2 x 2, clip. 5/-; 8 + 16, 450 525v, 1 x 2, clip. 4/-; 2, 450 525v, 4 x 1 1/2, tag. 1/6; 2, 350v, 4 x 1 1/2, tag. 1/3; 8, 450v, 4 x 2, clip. 1/9; 32 + 32, 450 525v, 1 1/2 x 3, W/E 5/6; 16 + 16, 450 525v, 1 1/2 x 2, W/E 4/6; all alicians. Some with sleeves, all voltages w/g. surge where marked, new stock, guaranteed. Set of 3 Components comprising line output trans. with E.H.T. winding to give 7K5, using EY51; heater winding for EY51 also included, and fitted with width control. Scanning coils low impedance line and frame, focus coil optional high (10 000 ohms) or low (200 ohms). Set of 3, 12/-, plus 2/- postage. Diagram of line trans. supplied. Mains Trans. P.R.I. 0-210-240, SEC. 250-0-250v, 80ma; 6.3v, 2.5a; 6.3v, 0.6a, 12/-; Mains Trans. P.R.I. 200-250v, SEC. 305-0-305v, 80ma, 800v, 5ma, 6.3v, 4.2a, 6.3v, 0.7a, 2v, 24, 4v, 1.14, 5v, 2.3a. These mains have been taken from ex-Govt. equipment, some may have tag panels broken but guaranteed O.K., 12/6 post paid and ideal for 'scopes. RADIO CLEARANCE LIMITED, 27, Tottenham Court Road, London, W.1. (Telephone: Museum 9188.)

A NEW ECONOMY Mains Transformer. Made to our own specification by a leading manufacturer. Size 2 1/2in. x 2 1/2in. x 3 1/2in. Prin. 0-230v. A.C. (0.k. for all mains. 200-250 v. A.C.; Sec. 220-0-220v at 50 ma (gives 250v H.T.) and 6.3v at 1.5A. The ideal transformer for that small radio, amplifier, or small piece of test equipment. Price, 15/6, p.p. 1/6. Many other bargains available. Stamp for free list. SERVO RADIO, 158/9, Merton Rd., Wimbledon, S.W.19. (Liberts 6525.)

EVERYTHING for radio constructors. Condensers, Coils, Valves, Resistors, etc. Send stamp for list. SMITH, 98, West End Road, Morecambe. Quick service.

RATES: 5/- per line or part thereof, average five words to line, minimum 2 lines. Box No. 1 extra. Advertisements must be prepaid and addressed to Advertisement Manager, "Practical Wireless," Tower House, Southampton St., Strand, London, W.C.2.

MICROGRAM AMPLIFIERS, 23/19/6, p. and p. 2, fits inside your record player, leaving room for speaker, dimensions 10in. x 3 1/2in. x 2 1/2in., suitable all speakers and with standard or L.P. pickups; valves 6K7 and 6V6. 20/- per pair extra if required; chassis finished in black and brown crackle, other models from 24/12/6, also cabinets in wood and steel. Send 6d. for 8-page illustrated catalogue. ELECTRO-ACOUSTIC LABORATORIES, Tain, Ross-shire, Scotland.

B.S.R. MONARCH 3-speed Mixer, Autochanger, brown. 29/10/- (15/- carriage) or cream. 210/5/- (15/- carriage). Rectifiers, WX6, at 1/6, and 230v, 40ma, selenium. 5/-; bargain 20/- parcel, 30 new components—resistors, condensers, switches, etc. retail price 24/- over. 24, mica Condensers, moulded case, 1mf, 1,500v, D.C. W. 4/-; 50 different Condensers and Resistors. 10/-; Potentiometers, 8 different, 100 ohm to 2M, for 12/-; selection. 25yds. insulating sleeving, 1mm to 8mm, in 4 sizes, 4/-; Allen mains Transformer, std. input, 250-0-250v at 80ma, 6.3v 3a, and 6.3v 6a, 25/-; high gain 4w. 200-250v, A.C. Audio Amplifier for mike and gram, with tone control and suitable speaker, chassis 8in. x 6in., price 25/-, complete with valves and workings, oak 5-position tone control switch, with s.p. on-off (2in. spindle), 2/6; B.T.H. diode CG5M, 2/- (18/- doz.); dial and pointer 2/- (62in. x 2 1/2in.). 19, 25, 31 MSW and MW; plastic dial with pointer (5in. x 1 1/2in.). MW and LW, 1/6; unused TCC 1mf 5KV type 191 Condenser, 10/-; unused TCC 5mf 6 KV dc.w., 20/- All new goods, except rectifiers and last two items, all goods guaranteed. GLADSTONE RADIO, Gladstone Place, Newton Abbot, Devon.

RADIO UNLIMITED for guaranteed Components. Boxed Valves, 6K7, 1T4, 1L4, 3A4, 6J5, 6SK7, 12J5, D63, EF36, LL4, LP2, LP220, LD210, ARP12, AR8, VR101, 6B8, 5/6 each, 6AM6, 6AL5, 6AK5, 6V6, 6F6, 6X5, 6J7, 6BE6, 6BA6, 6BW6, EF39, EF50, EL32 at 8/6 each, 6K8, 6Q7, 5Z4, U14, 6L6C, 8/6 each, EC180, EF80, PY82, PY80, UY41, UL42, 9/- each, 13,000 in stock. Stamp list. Coilpacks, miniature 3-wave with circ., 24/6. TRE, Coils M & L, 8/6 pair. Weyrad, 465Kcs, I.F.s 8/6 pair. Amplifier kit, A.C. or Uni. mains, complete with valves, 59/6. Dubilier, 8 x 8-500v Card/tub., 3/6, 16 x 10mf, 4/6, 1954 stock, 32 x 32-350v, Can. 3/6. Good mains 4in. P.M., 14/6; 7in. x 4in. Slip/P.M., 14/6. Full list available. RADIO UNLIMITED, Elm Road, London, E.17. (KEY 4813.)

MAGIC EYE TUNER. Add this very useful device to your present receiver, as described in March issue of P.W. Complete kit, including valve, 15/-; p.p. 9d. KEITH PRETTY, 17, Ashmead Road, London, S.E.8.

GERMANIUM DIODES, 1/- each; large quantities cheaper. BDC, 591, Green Lanes, London, N.8.

WALNUT Radiogram Cabinets of distinction; stamp details. R. SHAW, 69, Fairlop Rd., E.11.

LOUDSPEAKERS repaired promptly. MODEL LOUDSPEAKER SERVICE, Bullington Rd., Oxford.

FOR SALE, Eddystone 504, 580 kes/30.5 mes, continuous cover, complete with 12in. speaker, excellent working order. Offer nearest £30. Manchester, Galley 321, Ext. 108.

SERVICE SHEETS for Radio and Television, over 2,000 models. S.A.E. enquiries. W. GILBERT, 24, Frithville Gardens, London, W.12.

OUR NEW 76-page Illustrated Catalogue of Government Surplus Equipment, 1/-, post free. A. T. SALLIS, 93, North Road, Brighton, Sussex.

SITUATIONS VACANT

The engagement of persons answering these advertisements must be made through a Local Office of the Ministry of Labour or a Scheduled Employment Agency if the applicant is a man aged 18-34, inclusive, or a woman aged 18-34, inclusive, unless he or she, or the employment, is exempted from the provisions of the Notification of Vacancies Order, 1952.

T.V. AND RADIO—A.M. Brit. I.R.E., City and Guilds, R.T.E.B. Cert., etc., on "no pass—no fee" terms. Over 95% successes. Details of exams and home training courses in all branches of radio and T.V.; write for 144-page handbook—free. B.I.E.T., Dept. 242C1, 29, Wright's Lane, London, W.8.

WIRELESS STATION SUPERINTENDENT required by the Nigeria Government Posts and Telegraphs Department for one tour of 18 to 24 months in the first instance. Option of appointment (a) temporary terms with salary, etc., in scale £364 rising to £1392 a year and gratuity of up to £150 a year, or (b) with prospect of pensionable employment with salary, etc., in scale £750 rising to £1,715 a year. Outfit allowance £60. Free passages to and from Officer and wife. Assistance towards cost of children's passages or grant of up to £150 annually for their maintenance in U.K. Liberal leave on full salary. Candidates must have had wide practical experience of modern radio techniques and equipment, in particular V.H.F. equipment, and preferably also V.H.F. multi-channel equipment. Write to the Crown Agents, 4, Millbank, London, S.W.1. State age, name in block letters, full qualifications and experience and quote M/C 30086 PU.

CITY AND GUILDS (Electrical, etc.) on "no pass—no fee" terms. Over 95% successes. For full details of modern courses and all branches of Electrical Technology send for free 144-page handbook—free and post free. B.I.E.T. (Dept. 242A), 29, Wright's Lane, London, W.8.

AIRCRAFT Radio Mechanics skilled in workshop practice or aircraft installations to work at Stansted Airport, Essex; hostel accommodation available; minimum hourly rates 3/9. Write to the PERSONNEL MANAGER, 1, Berkeley St., W.1.

BRITISH EUROPEAN AIRWAYS have vacancies at London Airport for fully-skilled Radio Mechanics. Basic rate of pay 3 8d. per hour, plus bonus; up to 3d. per hour proficiency pay can be earned; shift premium pay where appropriate; 44-hour week. After qualifying period, pension, insurance and sick pay schemes, air travel concessions, 2 weeks annual holiday. Written applications, giving full particulars, to PERSONNEL OFFICER, Engineering Base, B.E.A., London Airport, Hounslow, Middx.

A.M.I.MECH.E., A.M. Brit. I.R.E., City and Guilds, etc., on "no pass—no fee" terms; over 95% successes. For details of exams, and courses in all branches of engineering, building, etc., write for 144-page handbook, free. B.I.E.T. (Dept. 242B), 29, Wright's Lane, London, W.8.

ALUM CHASSIS, 4-sided, 18 s.w.g., 13in. x 9in. x 2in., 5/9, plus 9d. postage; special sizes, prices in proportion; Riveted Corners, 1/- extra; Holes, 2d. each (send sketch). **WOOD & TOY**, 51, Whitfield Road, Worcester.

BOOKS

I.P.R.E. TECHNICAL PUBLICATIONS, 6,500 Alignment Peaks for Super-heterodynes, 5/9, post free. Data for constructing TV Aerial Strength Meter, 7/6. Sample copy The Practical Radio Engineer, quarterly publication of the Institute, 2/-; membership and examination data, 1/-; Secretary, I.P.R.E., 20, Fairfield Rd., London, N.8.

NEW and Used Correspondence Courses, Educational Books, bought, sold. Catalogue, **COURSES**, 28, Dean Road, London, N.W.2

BOOKLETS How to Use Ex-Gov. Lenses and Prisms, Nos. 1 and 2, price 2 6 ea. Ex-Gov. Optical lists free for s.a.e. **H. ENGLISH**, Rayleigh Rd., Hutton, Brentwood, Essex.

AMERICAN MAGAZINES.—One year "Audio Engineering," 28/6, specimen copy, 3/-; "Popular Science," 28/6; "High Fidelity," 50/-, specimen copy, 4/6. Free booklet quoting others. **WILLEN LTD.**, Dept. 40, 101, Fleet Street, London, E.C.4.

VALVES

45/- OFFERED for 813 Type Valves: any quantity purchased. Write: **PYPE-HAYES RADIO**, 606, Kingsbury Road, Birmingham, 24.

PROMPT CASH PAID for any quantities of VRT5A's, ARP26's or equivalent. **RADIO SUPPLY CO. (LEEDS)**, LTD., 32, The Calls, Leeds, 2.

6V6G AND GT, matched in pairs, new, boxed, 17/- per pair; p. and p. 1/- **R. J. COOPER**, 32, South End, Croydon, Surrey.

VALVES. Same day service. All guaranteed new and boxed: 1.4v. miniatures: 1S5, 1R5, 1T4, 3V4, 3S4, 1S4, DK92, DK91, DF91, DL91, DAF91, DL92, DL94, 7/6, any 4 for 27.6; 6AMS, EF91, 6P12, Z77, 8D3, 6AL5; EB91, 6X5GT, EF39, HVR2A, 6/9, any 8 for 50/-; 6K7G, 6K7GT, 6/4; EF92, W75, 5/6; 1C5GT, DL35, 6/4; 6AM5, EL91, 7/9; 6V6G, 6V6GT, 6J7G, 6F6G, KT63, EBC33, U22, EF50, 6BA6, 6BE6, 6BH6, 6BJ6, 7B7, 7/6; 7C6, 7H7, 7S7, 7/6; 5Z4G, 5Y3GT, U50, MU14, 7X4, U78, 6X4, DH77, 6A76, 6J6, 25Z5, 35Z6GT, 35L6GT, 50L6GT, 25L6GT, 35Z4GT, 35Z5GT, 80, EC91, PY82, 6BW6, 6LD26, 8/6; FL38, EL38, 22/6; P230, 6U4GT, U98, 275U, 17/-; G232, DK32, 1A7GT, 6P25, N76, 15/-; U25, UF42, KBF80, UBF80, R19, 13/6; EY31, KT33C, 10G1, 10G2, EM34, 1HG5T, DAC32, 1NSGT, DF33, 3Q5GT, DL33, CY31, AZ31, ECC91, 12/-; PL81, PL82, PY81, 11/-; ECL80, EF80, 12K8GT, 6A7, UCH42, EAF42, R10, 6F1, 6P15, 12AU7, 10P1, 10P13, 10/6; PY80, EL41, ECH42, EBC41, UBC41, UF41, 10LD11, 10F9, 10/6; 25Z4G, 6A8G, 6K8C, 6K8GT, 6Q7GT, 12AT7, 12AX7, 6W7, 12K7GT, 12Q7GT, 6SN7GT, UY41, UL41, 4F41, EZ40, EZ41, EAC91, ECC81, UO9, U404, 9/-; postage 4d. per valve extra. **READERS RADIO**, 24, Colberg Place, Stamford Hill, London, N.16

MORSE CODE Training

Send for the Candler

BOOK OF FACTS

It gives details of all Courses which include a Special one for securing amateur licence.

CANDLER SYSTEM CO. Dept. 5, 5/0 52b, Abingdon Road, London, W.8. Candler System Co., Denver, Colorado, U.S.A.

ELECTRONIC COMPONENTS. Send stamp for interesting comprehensive bargain list. **A. J. McMILLAN**, 5, Oakfield Road, Bristol, 8.

NEW VALVES WANTED, small or large quantities: PL81, EY51, KT61, 5Z4G, 5R4, 5U4, 3Q5, all television; prompt cash. **WM. CARVIS LTD.**, 103, North St., Leeds, 7.

1954-5

CATALOGUE

JUST RELEASED

- ★ 60 PAGES
 - ★ 2000 COMPONENT TYPES
 - ★ 500 ILLUSTRATIONS
- PRICE 1/-

COVENTRY RADIO

189, DUNSTABLE ROAD, LUTON

Tel: Luton 2577

COMPONENT SPECIALISTS SINCE 1925

CYLDON 5-CHANNEL TV. PRE-TUNER VALVES, 6BW7 and 12AT7. Fit one of these to your set for better pictures, 52/6. Less valves, 15/-.

SPECIAL OFFER. New and boxed ARP12 VP23 valves, 5/6 each, 4 for £1.

TYPE 6c "SCOPE" UNIT with VCR 138 34in. C.R. Tube, etc., and Conversion Circuit, 58/6.

FISHING ROD AERIALS, 12ft., Set 3, 7/6. Mounting Base, 3/6.

0.5 AMPMETERS, 2 1/2in. square M.C., 11 GERMANIUM DIODES, 3/6.

P.M. SPEAKERS, 8in., 20 - 5in., 14 6; 6in., 16 6; 10in., 27 6. Leading makes, **SELENIUM RECTIFIERS**, F.W. 6 or 12v. 4A., 22 6; 6A., 30 -; 3A., 14 6; 100 mA., 3/6; 1A., 8/6; 24v. 2A., 30 -; 250v. 100 mA., H.W., 9/-; 250v. 275 mA., 17/6. 250v. 60mA 8 6.

TRANSFORMERS, 200-240 volts, tapped 3-4-5-6-8-9-10-12-15-18-20-24 and 30 volts at 2A., 21 6. Tapped 17-11-5 volt 11 A., 22 6; Tapped 17-11-5 volt 11 A., 16 6; 6.3v., 21 A., 8/6. One year guarantee.

M/C MICROPHONES AND TRANSFORMERS, 15/6.

EX-W.D. PHONES, Low Resistance, 9/6.

MINIATURE VALVES, New 9001, 9002, 9003, 7 8; 6AG5, 1S4, 1S5, 1T4, 1R5, 10 6; 6AL5, 8/6; 12AT7, 6AM6, DH77, 6A76, EF91, EF92, EY51, 6BE6, 11/6.

NEW VALVES, 35Z4, 35L6, 25Z4, 25L6, U281, U50, 5Y3GT, 6K7GT, 6V6GT, 50L6, 42, 80, 11/-; 6K8GT, 11/26, 12 6.

NEW 0-100 MICRO-AMP. METERS, 4 1/2in. Flush Mounting. Made by Ernest Turner, 23/12 6.

TR.1198, Transmitter Section. New and complete, 4.6/6.8 Mc's. Easily converted. Less valves, 15/-; with valves, £2.

Throat Microphones with cord, 4/-

ALL POST PAID IN U.K.

THE RADIO & ELECTRICAL MART

253b, Portobello Road, London, W.11. Phone: Park 6028.

EDUCATIONAL

MERCHANT NAVY and Air Radio.—Here is an opportunity to train as Radio Officer. The big liners are open to you, but you must qualify for the P.M.G. Certificate. Day, Evening and "Radiocerts" postal courses, 1st. 30 years; s.a.e. for prospectus from Director. **THE WIRELESS SCHOOL**, 21, Manor Gardens, London, N.7. (Tel.: ARC. 3694.)

WIRELESS.—Day and Evening Class instruction for P.M.G. Certificate of Proficiency and Amateur Wireless Licence. Morse instruction only if required, also postal courses. Apply **B.S.T. LTD.**, 179, Clapham Rd., London, S.W.9.

THE INSTITUTE of Practical Radio Engineers Home Study Courses are suitable coaching text for I.P.R.E. and other qualifying examinations. Fees are moderate. Syllabus of seven modern courses post free from **SECRETARY, I.P.R.E.**, 20, Fairfield Road, London, N.8.

WORLD TRAVEL and adventure in the Merchant Navy. Young Men, 15 years upwards, required for training in Marine Wireless and Direction-finding at sea. (Trainees in forthcoming Registration Groups are eligible for Deferment of Military call-up.) Immediate sea-going positions on completion of training. Suitable candidates will be entered as Officers and must be prepared to sail to all parts of the world. Courses: Full or Part-time, also by Correspondence. Recognised by Ministry of Education. Scholarships available. Boarding and modern canteen facilities; low training fees. Send 1/- P.O. (stating age and height, etc.) for complete prospectus to: **OVERSEAS HOUSE** (Dept. 14), Brooks' Bar, Manchester, 16. (Tel.: MOSS-side 2047.)

FREE! Brochure giving details of Home Study Training in Radio, Television, and all branches of Electronics! Courses for the hobby enthusiast or for those aiming at the A.M.Brill.I.R.E., City and Guilds Telecommunications, R.T.E.B., and other professional examinations. Train with the College operated by Britain's largest electronic organisation; moderate fees. Write to **E.M.I. INSTITUTES**, Postal Division, Dept. PW28, 43, Grove Park Road, London, W.4.

SEE THE WORLD as a Radio Officer. Short training, low fees; scholarships; boarding/day students. Stamp for prospectus. **WIRELESS COLLEGE**, Colwyn Bay.

Amateur Radio Enthusiasts

THE INCOMPARABLE

GLOBE-KING

SINGLE VALVE S.W. RECEIVER • WORLD-WIDE RANGE 11-100 METRES • CRYSTAL-CLEAR NOISE-FREE RECEPTION • ELECTRICAL BAND-SPREAD TUNING • X-TREMELY LOW RUNNING COSTS Catalogue Free. Stamp for postage.

JOHNSONS (RADIO)

46, FRIAR STREET, WORCESTER

ANNAKINS SUPER BARGAINS


Condensers. American Blocks, .05 + .05 + .05 mfd., 300 v., 34. .05 mfd., 800 v., .05 + .5 mfd., 300 v., 6d. Electrolytic 5 + 20 mfd., 35 v., 9d. Resistors. American ceramic, 42 ohm 7 w., 6d.; 10 k., 7 w., 6d.; 15 k., 15 w., 9d.; 20 k., 15 w., 9d. Transformers. American metal cased, Mike 10-1, 1/-. Blocking Oscillator, 1/-, British Blocking Oscillator, 2/-. AF 6 k. to 40 ohms, 9d.

Money back guarantee. C.W.O. only. All above postage extra. Free lists. 25, ASHFIELD PLACE, OTLEY YORKS

PRATTS RADIO

1070 Harrow Road, London, N.W.10.

Tel. LADbroke 1734.

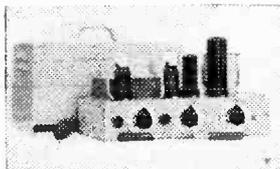

(Nr Scrubbs Lane)

AMPLIFIERS College General Purpose, ready to use, units. **Model AC10E** (as illustrated). 10 watt, 4 valve unit. Neg. Feedback. **Separate Pentode** Mike Stage and Gram Inputs. 2 Faders and Tone Control. £10.7.6. **Model AC15E** 6 Valve Unit with P Pull Output of 14-15 watts. **Separate Pentode** Mike Stage and **Separate**

Mike and Gram Inputs. 2 Faders and Tone Control. Feedback over 3 Stages £14.14.0. **Model AC32E** larger version of AC15E with output of 32 watts £19.15.0. **Model U10E** for D.C. A.C. Mains. SPEC. as AC15E output 9-10 watts, 6 valves. £12.19.3. All the above amplifiers are complete with cases and chrome handles. Outputs match 3, 8 or 16 ohm speaker. All A.C. models (inc. Q9C) have E.T., L.T. outlet for tuning unit, etc. All amplifiers are enclosed and have sectionalised output transformers with Super Silcor Laminations.

QUALITY AMPLIFIER CHASSIS for Records Radio and Crystal Pick-up. **Model Q9C** 6 Valve Unit with Bass and Treble Controls. Williamson 18 Section Output Transformer. Output 9 watts push-pull. Input switching for L.P. Standard Radio. Adjustable Neg. Feedback. £14.14.0. Stamp for fuller details of above Amplifiers.

MICROPHONES AND PLAYERS. Full range for use with our Amplifiers. Latest ACOS. Collard, B.S.R. and Garrard types available. B.S.R. 3-speed Single Player in Rexine Case. £9.9.0 Three-Speed Auto-Changer (mixed) version. Monarch Changer £16.16.0.


SPEAKERS QUALITY TYPES. W.B. H.F. 8in. 60/8; 9in. 67/-; 10in. 73/6. Goodmans Axiom 150 £10.7.8. Audion 60 £3.12.6.

TAPE RECORDING. Complete Recorders from £44.13.0. Tape Amplifiers £15. Truvox Tape Deck £23.2.0. Wearite £35. OSC. Units, etc., available. Send for List "TR".

ALL GOODS AVAILABLE ON ONE-THIRD DEPOSIT. BALANCE OVER 12 MONTHS. ALL GOODS ARE BRAND NEW AND CARRIAGE FREE. DEMONSTRATIONS DAILY NEAREST STATION KENSAL GREEN.

YOU CAN EASILY MAKE... the "ATOMIC"

A.C. SET FOR 90/-

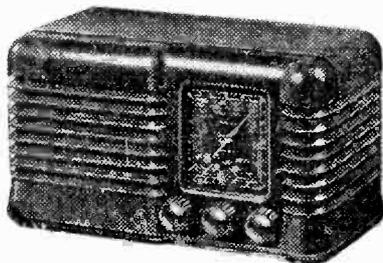

- Screwdriver, Pliers, and Soldering Iron, only tools required.
- All Parts sold separately.
- Money Back Guarantee.
- No Radio knowledge required.

SEND FOR POINT-TO-POINT WIRING DIAGRAM AND LIST OF PARTS, 1/- POST FREE.

Attractive C-valve A.C. Mains Set (2 Wavebands). Send only 90/- plus 3/- Carr. & Ins., and complete parts, including Valves. Ready-to-Use Chassis, Moulded Cabinet in Ivory or Walnut and full illustrated instructions will be sent by return. YOU CAN MAKE MONEY MAKING THESE SETS FOR FRIENDS—they're simple to construct and amazing value. Many already in use.

Call and hear this quality Receiver working at Birmingham's largest Radio Home Constructors' Shop (opposite the Hippodrome).

Every courtesy will be extended to you.

Norman H. Field Tel. MIDLAND 3619
68 HURST STREET, BIRMINGHAM 5

THE FAMOUS BENNETT COLLEGE

can help your career through personal postal tuition

in any of these subjects:

- Accountancy Exams. ★ Aircraft Eng. & Radio ★ Architecture ★ Auditing ★ Book-keeping ★ Building ★ Carpentry ★ Chemistry ★ Civil Service ★ Commercial Art ★ Commercial Arithmetic ★ Company Law ★ Costing ★ Diesel Engines ★ Draughtsmanship ★ Electric Wiring ★ Engineering (Civil); Electrical; Mechanical; Motor; Steam; Structural ★ Jigs, Tools & Fixtures ★ Journalism ★ Locomotive Engineering ★ Languages ★ Mathematics ★ Modern Business Methods ★ Plumbing ★ Police ★ Press Tool Work ★ Quantity Surveying ★ Radio ★ Salesmanship ★ Secretarial Exams. ★ Shorthand ★ Surveying ★ Telecommunications ★ Textiles ★ Wireless Telegraphy ★ Workshop Practice

and GENERAL CERTIFICATE OF EDUCATION SUCCESS WILL BE YOURS

As a Bennett College Student your own Personal Tutor will coach you until you qualify, at your pace with no time wasted. You will learn quickly, easily.

SEND TODAY FOR A FREE PROSPECTUS

TO THE BENNETT COLLEGE (DEPT. H.104), SHEFFIELD

Please send me your prospectus on..... (Subject)

NAME.....

ADDRESS.....

..... AGE (IF UNDER 21).....

PLEASE WRITE IN BLOCK LETTERS

VALVES

EX GOVT. SURPLUS GUARANTEED

4/- EF50 SP61 2/6

SP41	2/6	GAM6	7/6	D1	2/-	EB34	2/-
RK34	2/6	EA50	2/-	CV188	5/-	VR135	2/6
Pen22)	3/-	CV63	5/-	VR18	3/6	KT2	6/-
6AL5	7/8	VR21	2/6	VR116	4/-	HL2	2/6
EF8	8/-	CV73	4/-	EP39	7/-	EF54	5/-
EP55		EF36	4/8	EC54	4/8	EBC33	7/6
(CV173)	9/-	EC52	5/-	6K7	6/-	6K8	11/-
6J5	5/-	GJ5M	6/-	6V6	8/6	6SH7(M)	6/-
6SN7	10/-	6N7	8/-	12A6	6/-	6SK7(M)	6/-
12H6	5/8	6H6	4/8	VS71	5/-	S130	6/-
H39	7/8	PX25	10/6	5Z4M	9/-	5U4G	9/-
5Z3	8/8	5Z4	8/6	VU39	8/6	2X2	7/-
6X5	7/6	1W4	5/0	VU29	13/6	VT62	9/-
U22	7/-	MU2	6/-	1T4	7/-	154	7/6
EL32	7/-	EK32	7/6	354	7/6	3V4	8/6
1R5	7/-	1S5	7/6	9BW3	9/-	R19	13/-
6BW6	8/8	6BW7	8/8	3A1	8/-	6AT6	8/6

CONDENSERS.—W.E. 450 v. wkg. 8 mfd., 2/-; 8-8 mfd., 3/3. 16-16 mfd., 4/6; 32-32 mfd., 6/-; Dubilier 500 v. wkg. 20 mfd., 3/-; 32 mfd., 5/-; 25 or 50 mfd., 25 v., 2/-.

POTENTIOMETERS.—All Values L/S.W. to 2 megs. 2/6 each. With I.S.W. 100 K. 1, 1.1, 2 meg., 3/9 each.

RESISTORS.—1, 1.1, 2 megs. Our Selection, 12/6 per 100.

VINER'S (Middlesbrough)

Radio Electrical

26, EAST STREET MIDDLESBROUGH

Telephone: MID 3418

Practical Wireless BLUEPRINT SERVICE

PRACTICAL WIRELESS

No. of
Blueprint

CRYSTAL SETS

1/6d. each	
1937 Crystal Receiver ...	PW71*
The "Junior" Crystal Set ...	PW94*
2s. each	
Dual - Wave "Crystal Diode" ...	PW95*

STRAIGHT SETS

Battery Operated

One - valve : 2s. each	
The "Pyramid" One-valver (HF Pen) ...	PW93*
The Modern One-valver ...	PW96*
Two-valve : 2s. each.	
The Signet Two (D & LF) ...	PW76*
3s. each.	
Modern Two-valver (two band receiver) ...	PW98*
Three-valve : 2s. each.	
Summit Three (HF Pen, D, Pen) ...	PW37*
The "Rapide" Straight 3 (D, 2 LF (RC & Trans)) ...	PW82*
F. J. Camm's "Sprite" Three (HF, Pen, D, Tet) ...	PW87*
3s. each.	
The All-dry Three ...	PW97*
Four-valve : 2s. each.	
Fury Four Super (SG, SG, D, Pen) ...	PW34C*

Mains Operated

Two-valve : 2s. each.	
Selectone A.C. Radiogram Two (D, Pow) ...	PW19*
Three-valve : 3s. 6d. each.	
A.C. Band-Pass 3 ...	PW99*
Four-valve : 2s. each.	
A.C. Fury Four (SG, SG, D, Pen) ...	PW20*
A.C. Hall-Mark (HF Pen, D, Push Pull) ...	PW45*

SUPERHETS

Battery Sets : 2s. each.	
F. J. Camm's 2-valve Superhet ...	PW52*
Mains Operated : 3s. 6d. each.	
"Coronet" A.C.4 ...	PW100*
AC/DC "Coronet" Four ...	PW101*

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

One-valve : 2s. each.	
Simple S.W. One-valver ...	PW38*
Two-valve : 2s. each.	
Midget Short-wave Two (D, Pen) ...	PW38A*
Three-valve : 2s. each.	
Experimenter's Short-wave Three (SG, D, Pow) ...	PW30A*
The Perfect 3 (D, 2 LF (RC and Trans)) ...	PW63*
The Band-spread S.W. Three (HF, Pen, D, (Pen), Pen) ...	PW68*

PORTABLES

1s. 6d.	
The "Mini-Four" All-dry (4-valve superhet) ...	*

MISCELLANEOUS

2s. each.	
S.W. Converter-Adapter (1 valve) ...	PW48A*
(2 sheets), 7s. 6d.	
The P.W. 3-speed Autogram ...	*
The P.W. Electronic Organ (2 sheets), 7s. 6d.	*

TELEVISION

The Practical Television Receiver. (3 sheets), 10/6	
The "Argus" (6in. C.R. Tube), 2/6*	
The "Super-Visor" (3 Sheets) 7/6*	
The "Simplex" 3/6*	

All the following blueprints, as well as the PRACTICAL WIRELESS numbers below are pre-war designs, kept in circulation for those amateurs who wish to utilise old components which they may have in their spares box. The majority of the components for these receivers are no longer stocked by retailers.

AMATEUR WIRELESS AND WIRELESS MAGAZINE

STRAIGHT SETS

Battery Operated

One-valve : 2s.	
B.B.C. Special One-valver ...	AW387*

Mains Operated

Two-valve : 2s. each.	
Consolelectric Two (D, Pen), A.C. ...	AW403

SPECIAL NOTE

THESE blueprints are drawn full size. The issues containing descriptions of these sets are now out of print, but an asterisk denotes that constructional details are available, free with the blueprint.

The index letters which precede the Blueprint Number indicate the periodical in which the description appears. Thus P.W. refers to PRACTICAL WIRELESS, A.W. to *Amdleur Wireless*, W.M. to *Wireless Magazine*.

Send preferably, a postal order to cover the cost of the Blueprint (stamps over 6d. unacceptable) to PRACTICAL WIRELESS, Blueprint Dept., George Newnes, Ltd., Tower House, Southampton Street, Strand, W.C.2.

No. of
Blueprint

SHORT-WAVE SETS

Battery Operated

One-valve : 2s. each.	
S.W. One-valver for American ...	AW429*
Two-valve : 2s. each.	
Ultra-short Battery Two (SG, det Pen) ...	WM402*
Four-valve : 3s. each.	
A.W. Short Wave World-beater (HF Pen, D, RC Trans) ...	AW436*
Standard Four-valver Short-waver (SG, D, LF, P) ...	WM383*

Mains Operated

Four-valve : 3s.	
Standard Four-valve A.C. Short-waver (SG, D, RC, Trans) ...	WM391*

MISCELLANEOUS

Enthusiast's Power Amplifier (10 Watts) (3/-)	WM387*
Listener's 5-watt A.C. Amplifier (3/-)	WM392*
De Luxe Concert A.C. Electrogram (2/-)	WM403*


QUERY COUPON

This coupon is available until Aug. 5th, 1954, and must accompany all Queries, sent in accord with the notice on page 505.
PRACTICAL WIRELESS, Aug., 1954.

PLASTIC CABINET as illustrated, 11½ x 6½ x 5½ in. in walnut cream, or green. ALSO in **POLISHED WALNUT**, complete with T.R.F. chassis, 2 waveband scale, station names, new waveband, backplate, drum, pointer, spring, drive spindle, 3 knobs and back, 22/6. P. & P., 3/6.

As above with Superhet Chassis, 23/6. P. & P., 3/6.

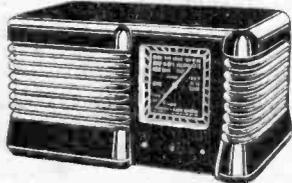As above complete with new 5in. speaker to fit and O.P. trans. 35/- P. & P. 3/6 with Superhet Chassis. 36/- P. & P. 3/6.




1 set metal rectifier, 230 v. 50mA., 3/6. gang with trimmers. 6/6. M. & L. T.R.F. coils. 5/- 3 Govt. valves, 3v h and circuit. 4/6. heater trans. 6/- volume control with switch. 3/6. wave-changed switch. 2/- 32 x 32 mfd., 4/- bias condenser. 1/- resistor kit. 2/- condenser kit. 4/-

M. & L. Superhet Coils with circuit. 6/6. Iron core 465 Hz. 7/6. min. gang. 5/6. volume control with switch. 4/- wave change switch. 2/6. heater trans. 7/6. 4 v.h. 1/6. 4 Ex. Govt. valves, metal rectifier and Met. diode with circuit. 14/6. 25 x 25 mfd., 1/- 16 x 15 mfd., 3/3. condenser kit (17). 7/6. resistor kit (14). 3/6.

All dry A.C. mains battery unit, 200/250 v. Metal case size 8 x 5 x 3in. by famous manufacturer incorporating Westinghouse metal rectifiers, 3 500 mfd., 16-24 mfd. mains trans., 3 smoothing chokes, output 90 v. 10 mA. 1.4 v., .35 amp. P. & P. 23/6. 39/6.

COMPLETELY BUILT SIGNAL GENERATOR

Coverage 100 Kcs-320 Kcs., 200 Kcs-900 Kcs., 900 Kcs-2.75 Mcs., 2.75 Mcs-3.5 Mcs., 3.5 Mc-26 Mcs., 27 Mcs-50 Mcs., 25.5 Mc-75 Mcs. Metal case 10 x 6½ x 4½ in. Size of scale 6½ x 3½ in. 2 valves and rectifier, A.C. mains 230 250 v. Internal modulation 400 c.p.s. to a depth of 30%. Modulated or unmodulated R.F. output continuously variable 100 millivolts. C.W. and mod. switch, variable A.F. output and moving coil output meter. Black crackle finished case and white panel, 24 19/6. or 34/- deposit and 3 monthly payments of 25/-. Post and Packing 4/- extra.

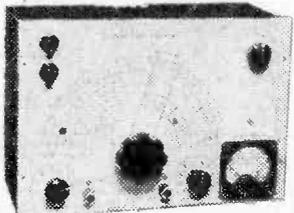

High impedance plastic recording tape by famous manufacturer. 1.20 feet complete on spool. 17/5. P. & P. 1/6. 600 feet 8/-, P. & P. 1/-.

Terms of business: Cash with order. Dispatch of goods within three days from receipt of order. Where post and packing charge is not stated, please add 1/6 up to 10/-, 2/- up to £1. and 2/6 up to £2. All enquiries S.A.E. Lists 5d. each.

D. COHEN, 23, HIGH STREET, ACTON, W.3.

Hours of Business: Saturdays 9-5 p.m. Wednesdays 9-1 p.m. Other days 9-4.30 p.m.

Opposite Granada Cinema

Pr. 200/250 v., secondary 3, 4, 5, 6, 8, 9, 10, 12, 15, 18, 20, 24 and 30 volt at 2 amps. 13/-

Drop thro' 240-0-240, 200 mA., 6 v. 5 amps., 5 v. 3 amps. 27/6

Heater Transformer, Pri. 230-250 v. 6 v. 1 amp. 6/- 2 v. 2½ amp. 5/-

R.L. MAINS TRANSFORMERS, chassis mounting, feet and voltage panel. Primaries 200 250.

350-0-350 75 mA. 6.3 v. 8 a. tap 4 v. 6.3 v. 1 a. 13/6.

350-0-350 70 mA. 4 v. 5 a. 4 v. 2.5 a. C.T. 13/6. P. & P. on above transformers 2/-

500-0-500 120 mA. 4 v. C.T. 4 a. 2 v. C.T. 4 a. 4 v. C.T. 2.5 a. 27/6.

500-0-500 250 mA. 4 v. C.T. 5 a. 1 v. C.T. 5 a. 4 v. C.T. 4 a. 39/3.

P. & P. on the above transformers 3/-

32 mfd., 350 wkg. 2/-

16 x 21 350 wkg. 4/-

4 mfd. 200 wkg. 1/3

40 mfd., 450 wkg. 3/6

15 x 8 mfd., 500 wkg. 4/6

16 x 16 mfd., 500 wkg. 5/9

8 x 16 mfd., 450 wkg. 3/9

32 x 23 mfd., 350 wkg. 4/-

32 x 32 mfd., 350 wkg. and 25 mfd., 25 wkg. 6/6

25 mfd., 25 wkg. 11/4.

250 mfd., 12 v. wkg. 3/3

16 mfd., 500 wkg. wire ends 2/6

8 mfd., 500 v. wkg., wire ends 2/6

8 mfd., 350 v. wkg., tag ends 1/6

8 mfd., 25 v. wkg., wire ends 1/9

100 mfd., 350 wkg. 9/6

100 1200 mfd., 350 wkg. 9/6

16 x 16 mfd., 350 wkg. 3/3

Ex. Govt. 8 mfd. 500 v. wkg., size 31 x 11, 2 for 2/6

60 x 100 mfd., 280 v. wkg. 6/7

16 x 32 mfd., 350 wkg. 6/6

50 mfd., 180 wkg. 1/9

65 mfd., 220 wkg. 1/6

8 mfd., 150 wkg. 1/6

60 x 100 mfd., 280 wkg. 8/6

30 mfd., 15 wkg. 11/4.

32 x 32 mfd., min. 275 wkg. 4/-

50 mfd., 50 wkg. 8 mfd., wkg. wire ends 1/9

Miniature wire ends moulded 100 pt., 500 pt. and .001 ea. 7/4.

CONSTRUCTOR'S PARCEL, comprising chassis 12½ x 8 x 2in., cad. plated 18 gauge, v.h., 1P and trans. cut-outs, backplate, 2 supporting brackets, 3 waveband scale, new wavelength station names. Size of scale 11 x 4½ in., drive spindle, drum, 2 pulleys, pointer, 2 bulb holders, 5 paxolin international octal valve holders, 19.

AS ABOVE, but complete with 16+16 mfd. 350 wkg. and semi-shrouded drop thro' 250-0-250 60 mA., 6 v. 3 amp. Pri. 200-250, and twin-gang, 31/6. P. & P. 3/-


Trimmers, 5-40 pt., 5d.; 10-100, 10-250, 10-1000 pt., 10d.

Germanium crystal diode, 1/6, post paid.

PATTERN GENERATOR 40-70 Mc's direct calibration, checks frame and line time base, frequency and linearity, vision channel alignment, sound channel and sound selection circuits, and vision channel band width. Silver plated coils, black crackle finished case, 10 x 6½ x 4 in. and white front panel. A.C. mains 200 250 volts. This instrument will align any TV receiver. Cash price, £3.19.6 or £19.0 deposit and 3 monthly payments of £1. Post and packing 4/- extra.

TV. CONVERTER for the new commercial stations, complete with 2 valves. Frequency can be set to any channel within the 199-196 Mc's band. I.F. will work into any existing TV. receiver, designed to work between 49-68 Mc's. Sensitivity 10 Mu v. with any normal TV. set. Input is arranged for 300 ohm feeder. 30 ohm feeder can be used with slight reduction in R.F. gain. Circuit EF50 as local oscillator. ECC81 as R.F. amplifier and mixer. The gain of the first stage, grounded grid R.F. amplifier, 10db.

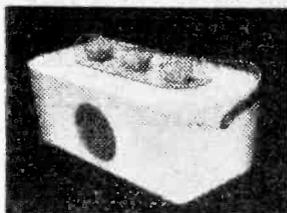Requires power supply of 200 v. D.C. at 25 mA. 6.3 v. A.C. at 0.8 amp. Input filter ensuring complete freedom from unwanted signals. 2 simple adjustments only. £2.10.0 Post and packing 2/6.



PERSONAL PORTABLE CABINET in cream-coloured plastic, size 7 x 4½ x 3in. Complete 4-valve chassis. Scale and 0-1 pole 4-way used as Volume and 0-1 2/- 4 BTG valveholders, 2/4. Midget twin gang tin. dia., 1in. long and pair medium and long-wave T.R.F. coils 3in. long x 1in. wide; complete with 4-valve all-dry mains and battery circuit. 9/6. Condenser kit, comprising 11 miniature condensers, 3/6. Resistor kit, comprising 15 miniature resistors, 4/6. 25 x 25 mfd., 1.6 P. & P. 2/6. Valves to suit above 10/- extra. Point to Point Wiring Diagram 1/-

3in. P.M. SPEAKER to fit above. 10/- Miniature output transformer, 5/- Miniature wave-change switch, 2/- Miniature 1-pole 4-way used as Volume and 0-1 2/- 4 BTG valveholders, 2/4. Midget twin gang tin. dia., 1in. long and pair medium and long-wave T.R.F. coils 3in. long x 1in. wide; complete with 4-valve all-dry mains and battery circuit. 9/6. Condenser kit, comprising 11 miniature condensers, 3/6. Resistor kit, comprising 15 miniature resistors, 4/6. 25 x 25 mfd., 1.6 P. & P. 2/6. Valves to suit above 10/- extra. Point to Point Wiring Diagram 1/-



View of chassis as it would look when assembled with valves inserted.

Extension speaker cabinet, in contrasting walnut veneers, size 15 x 10½ in. Will take 6in or 8in. speaker. 17/6. P. & P. 2/-

Volume Controls, Long spindle less switch, 50 K., 500 K., 1 meg. 2/6 each. P. & P. 1d. each.

Volume Controls, Long spindle and switch, 1, 2, 1 and 2-meg. 4/- each; 10 K. and 50 K., 3/6 each. 1 and 1 meg. long spindle, double pole switch, miniature, 5/-

Standard Wave-change Switches, 4-pole 1-wav. 1/9; 6-pole 3-way, 1/9. Miniature 3-pole 4-way 6-pole 3-way, 2/6.

Valveholders, Paxolin octal, 4d. Moulded octal, 7d. EF50, 7d. Moulded BTG, 7d. Loctal amphenol, 7d. Loctal pax., 4d. Mazda Amph., 7d. Mazda pax., 4d. B8A, B9A amphenol, 7d. BTG with screening can, 1s. Duodecal paxolin, 9d.

Twin-range .0005 Farad Condensers, 5/- With trimmers, 8/6.

Midget .00037 dust cover and trimmers, 8/6.

P.M. SPEAKERS

	with trans.	less trans.
3½ in.	18/6	13/6
5 in.	18/6	13/6
6½ in.	18/6	13/6
8 in.	18/6	15/-
10 in.	18/6	19/6

Post and packing on each of the above 1/6 extra.

RADIOGRAM CHASSIS—5 valve A.C. D.C. 2-way band superhet. 195/255 volts. 19-49, 200 550 and 1,000-2,000 metres, fly-wheel tuning frequency, 470 Kcs iron-cored coils and I.F.s. Size of chassis, 13 x 6½ x 2½. Complete with valves and 6in P.W. speaker, p. & p. 5/- £3 17/6.