

*The*  
**RADIO  
Constructor**



*RADIO · TELEVISION · AUDIO · ELECTRONICS*

*The Teletron* “**TRANSIDYNE**”



**6-TRANSISTOR  
POCKET PORTABLE  
SUPERHET RECEIVER**

*described by*  
**EDWIN MARSHALL**

*Included in this issue*  
CORNER REFLECTOR BAND 3 AERIAL  
PRE-TUNED SUPERHET RECEIVER  
STABILISED AUDIO OSCILLATOR  
MULTI-RANGE ELECTROSTATIC VOLTMETER  
WAVEMASTER RADIO CONTROL CABIN CRUISER  
MULTI-PURPOSE NEON TESTER

**DATA  
Publications 19**

# THE MODERN BOOK CO

**A Beginner's Guide to Television.**  
By F. J. Camm. 7s. 6d. Postage 6d.

**TV Fault Finding.** A Data Publication.  
5s. Postage 6d.

**Oscilloscope Equipment.** By D. W. Easterling. 5s. Postage 4d.

**Elements of Tape Recorder Circuits.**  
By H. Burstein and H. C. Pollak. 23s.  
Postage 9d.

**The Radio Amateur's Handbook.**  
By A.R.R.L. 32s. 6d. Postage 1s. 9d.

**World Radio Handbook for Listeners.** 1958 ed. 13s. 6d. Postage 1s.

**Radio Valve Data.** 6th Ed. Compiled by "WV". 5s. Postage 9d.

**Quality Amplifiers for A.C. Mains.**  
Data Publications. 4s. 6d. Postage 4d.

**Electronic Puzzles and Games.** By M. Mandl. 15s. Postage 8d.

**An Electronic Organ for the Home Constructor.** By A. Douglas. 15s.  
Postage 9d.

**Electronic Hobbyists' Handbook.**  
By R. P. Turner. 20s. Postage 9d.

**High Fidelity Sound Reproduction.**  
By E. Molloy. 20s. Postage 1s.

**Basic Mathematics for Radio and Electronics.** By F. M. Colebrook and J. W. Head. 17s. 6d. Postage 1s.

**Transistor Circuits.** By R. P. Turner. 22s. Postage 9d.

We have the Finest Selection of British and American Radio Books in the Country

Complete catalogue 6d.

19-23 PRAED STREET (Dept RC) LONDON W2

Telephone PADdington 4185

## CONSTRUCTORS CORNER

### PERSONAL PORTABLE RADIO

Ideal for the holiday, hiking, fishing, camping, cycling, etc. Use it at home, at the office, in bed, or just anywhere.



35/-

### TRANSISTOR COMPONENTS

**Miniature A.F. Transformers,** specially designed for coupling transistor output stages, fully coded, 7/6 each

**Transistors,** Red spot, 100% tested, 10/- each

**Crystal Diodes,** 100% tested, 2/6 each

**Miniature Condenser,** variable, single-hole fixing, 0.0004µF, 4/- each

### ALL-WAVE RADIO



35/-

This 1 valve S.W. receiver can be built for 35/- from our list of components, which can be purchased separately. It includes valve and 1 coil covering 24-40 metres. Provision is made to increase to 2 or 3 valves if required, and all components are colour-coded so that the beginner can build this set quite easily.

**Headphones,** 1,000 ohms impedance, specially designed for above receivers, 14/- per pair

**Power Unit type PU1.** Input 250V a.c.; output 120V at 20mA, 6.3V at 1.5A. Ideal for small receivers, test equipment, etc. Kit of Parts 32/6  
Built and tested £2 each

All components for the receivers advertised are sold separately. Full construction data, point-to-point wiring diagram, parts lists, etc., are available at 2/- for each receiver.


Postage: Under 10/-, 9d. Under 40/-, 1/6. Over 40/-, post free

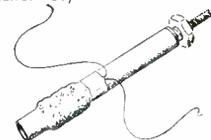**R.C.S. PRODUCTS (RADIO) LTD**


11 OLIVER ROAD (Mail order only) LONDON E17



**Transistor Pocket Radio,** low cost and ideal for the beginner. Using the Variloopstick aerial (see below) and miniature condenser, the whole Medium Wave is covered. Fits the palm of the hand. 30/-



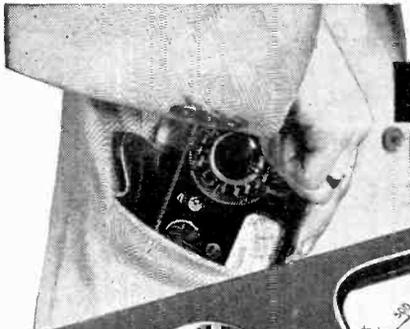**Variloopstick,** specially designed for maximum transistor receiver performance, high 'Q' 4/6



**TO FIT THE POCKET**



**TO FILL THE BILL**

**19 Ranges**

- |                     |                     |
|---------------------|---------------------|
| <b>D.C. Voltage</b> | <b>A.C. Voltage</b> |
| 0—100mV             | 0— 10V              |
| 0— 2.5V             | 0— 25V              |
| 0— 10V              | 0— 100V             |
| 0— 25V              | 0— 250V             |
| 0— 100V             | 0—1000V             |
| 0— 250V             |                     |
| 0—1000V             | <b>D.C. Current</b> |
|                     | 0— 100μA            |
|                     | 0— 1mA              |
|                     | 0— 10mA             |
|                     | 0— 100mA            |
|                     | 0— 1A               |

**Sensitivity**  
 10,000 Ω/V on D.C. voltage ranges  
 1,000 Ω/V on A.C. voltage ranges

**Accuracy**  
 3% of full scale value on D.C.  
 4% of full scale value on A.C.

To meet special requirements, instruments can be supplied to a higher degree of accuracy for a small additional charge.

This splendid new AVO Instrument has been developed to meet a definite demand for a sturdy pocket-size multi-range test meter at a modest price, suitable for use on modern electronic apparatus as well as for radio and television receivers, motor vehicles, and all kinds of domestic appliances and workshop equipment.

Readings are obtainable quickly and easily on a very open scale, and range selection is by means of a robust clearly marked rotary switch of the characteristic AvoMeter type. Measurements of A.C. and D.C. Voltage, D.C. Current and Resistance are made by means of only two connection sockets.


**THE MULTIMINOR**

List Price: **£9 : 10s.**  
 complete with Test Leads and clips      Size: 5½ × 3½ × 1½ inches  
 Leather Case if required **32/6**      Weight: 1lb approx.  
**Write for fully illustrated pamphlet**



**AVO Ltd. AVOCET HOUSE • 92-96 VAUXHALL BRIDGE ROAD • LONDON • SW1**

Telephone: VIctoria 3404 (9 lines)

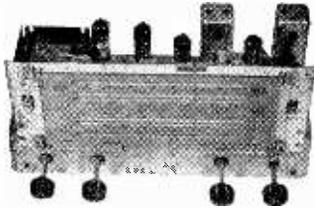

### 1958 RADIOGRAM CHASSIS

THREE WAVEBANDS FIVE VALVES  
S.W. 16 m.-50 m. LATEST MULLARD  
M.V. 200 m.-550 m. ECH42, EF41, EBC41,  
L.W. 800 m.-2,000 m. EL41, EZ40  
12 month Guarantee. A.C. 200/250V, 4-way switch.  
Short-Medium-Long-Gram. A.V.C. and negative feed-  
back. 4.2 watts. Chassis 13 1/2" x 5 1/2" x 2 1/2". Glass dial  
10" x 4 1/2" horizontal or vertical available. 2 pilot lamps.  
Four knobs, walnut or ivory, aligned and calibrated.  
Chassis isolated from mains. Immediate delivery.

**BRAND NEW £9.10.0 Carr. 4/6**

TERMS: Deposit £5.5.0 and 5 monthly payments of £1  
MATCHED SPEAKERS: 8" 17/6, 10" 25/-, 12" 30/-

### ★ GARRARD 4-SPEED SINGLE RECORD PLAYER 4SP ★

**£8 AUDIO PERFECTION POST FREE**

Designed to play 16, 33, 45, 78 r.p.m. Records, 7", 10", 12". Lightweight Xtal pick-up, GC2 turnover head, two separate sapphire styli. Standard and L.P.

### BUILD THIS REPRODUCER BARGAIN

#### SPECIAL SINGLE PLAYER KIT

COLLARO 4-speed Gram-Pick-up Unit £4.12.6  
Handsome portable case 17 1/2" x 13 1/2" x 7" £2. 5.0  
Ready-built 3 watt amplifier with two valves and 7" elip. speaker, printed circuit £3.12.6

All available separately

**£9.15.0 complete kit post free**

#### I.F. TRANSFORMERS 7/6 pair

465 kc/s slug tuning miniature can 2 1/2" x 1" x 1". High Q and good band width. By Pye Radio. Data sheet supplied.

Wearite M800 Midget I.F.S. 465 kc/s 12/6 pair  
Wearite 550 Standard I.F.S. 465 kc/s 12/6 pair

#### New boxed VALVES 90-day Guarantee

1R5	8/6	6K8	8/6	EAS5	1/6	EZ81	11/6
1S5	8/6	6L6	10/6	EABC80	10/6	E1148	1/6
1T4	8/6	6Q7	10/6	EB91	6/6	HABC80	12/6
2X2	2/6	6SA7	10/6	EBC33	8/6	HVR2A	7/6
354	8/6	6SJ7M	10/6	EBC41	10/6	MU14	10/6
3V4	8/6	6SN7	8/6	EBF80	10/6	P61	6/6
5U4	8/6	6V6G	7/6	ECC84	12/6	PCC84	12/6
5Y3	8/6	6V6GT	8/6	EFC80	11/6	PCF80	11/6
5Z4	10/6	6X4	7/6	ECF82	11/6	PCF82	11/6
6AM6	8/6	6X5	7/6	ECH42	10/6	PCL82	11/6
6B88	5/6	6T7	10/6	ECL82	12/6	PEN25	6/6
6BE6	7/6	12A8H	10/6	EF39	7/9	PL82	10/6
6BH6	10/6	12AT7	10/6	EF41	10/6	PY80	10/6
6BV6	10/6	12AU7	9/6	EF50	5/6	PY81	10/6
6CH6	10/6	12AX7	9/6	Equip.		PY82	10/6
6D6	7/6	12BE6	6/6	EF50	8/6	SP61	5/6
6F6	7/6	12K7	8/6	Sylv.		UBC41	10/6
6H6	3/6	12Q7	8/6	EF80	10/6	UCH42	10/6
6J5	6/6	35L6	9/6	EF92	5/6	UF41	10/6
6J6	7/6	35Z4	9/6	EL32	5/6	UL41	10/6
6J7	8/6	80	10/6	EL84	10/6	UY41	10/6
6K6	6/6	807	6/6	EY51	12/6	U22	10/6
6K7	5/6	954	1/6	EZ40	10/6	X79	10/6

### C.R.T. ISOLATION TRANSFORMERS

For Cathode Ray Tubes having heater-cathode short circuit and for C.R. Tubes with falling emission.  
**Type A.** Low leakage windings. **Optional 25% and 50% boost on secondary:** 2V, or 4V, or 6.3V, or 10.3V, or 13.3V, with mains primaries, 12/6  
**Type B.** Mains input. Low capacity. Multi-output 2, 4, 6.3, 7.3, 10 and 13V. Boost 25% and 50%. This transformer is suitable for all TV tubes. 21/- each  
**Type C.** Low capacity transformer for 2V tubes with falling emission. Mains input. Output 2, 2 1/2, 2 1/2, 3V at 2A, 17/6 each

**RESISTORS.** Preferred values. 20% 10 ohms to 10 meg. 1/2W 4d., 1/2W 4d., 1W 6d., 1 1/2W 8d.

**HIGH STABILITY.** 1/2W 19s., 2/- All preferred values 100Ω-10MΩ. Ditto 5% 100Ω-5MΩ 9d. each

5 watt } **WIRE-WOUND RESISTORS** 1/3  
10 watt } 25 ohms-10,000 ohms 1/6  
15 watt } 2/-

15,000 ohms-50,000 ohms, 5W, 1/9; 10W, 2/3

**WIRE-WOUND POTS** 3W Lab. Colvern, etc. Pre-set min. TV type. Standard size Pots, 2 1/2" Knurled slotted knob. Spindle, high grade. All values, 100 ohms to 50k, 3/- each. 50k, 4/- 5/6; 100k, 6/6  
Ditto Carbon Track 50k W/W EXT. SPEAKER to 2 Meg, 3/- CONTROL 10Ω, 3/-

### MAINS TRANSFORMERS

**STANDARD.** 250-0-250, 80mA, 6.3V tapped 4V 4A. Rectifier 6.3V 1A tapped 5V 2A and 4V 2A 22/6  
Ditto 350-0-350 22/6

**MINIATURE.** 200V 20mA, 6.3V 1A 10/6

**MIDGET.** 220V 45mA, 6.3V 2A 15/6

**SMALL.** 220-0-220, 50mA, 6.3V 3A 17/6

**STANDARD.** 250-0-250, 65mA, 6.3V 3.5A 17/6

**HEATER TRANS.** 200/250V, 6.3V 1 1/2A 7/6

Ditto, tapped sec. 2, 4, 6.3V 1 1/2A 8/6

Ditto, sec. 6.3V 3A 10/6

Mullard "510" Mains Transformers 38/6

**O/P TRANSFORMERS.** Heavy duty 50mA, 4/6. Multi-ratio push-pull, 7/6. Miniature 3V4, etc., 4/6. Small pentode, 4/6. Hygrade push-pull 7 watts, 15/6. Mullard "510" 6k or 8kΩ, 30/-

**L.F. CHOKES** 15/10H 60/65mA, 5/-; 10H, 85mA, 10/6; 20/15H, 120/150mA, 12/6; 5H, 250mA, 15/-

### CRYSTAL MIKE INSERT by Acos, 6/6

Precision engineered. Size only 7/8" x 1 1/8"  
**ACOS CRYSTAL HAND MIKE**, complete, 25/-

**ALADDIN FORMERS** and cores. 1 1/2" 8d., 3/4" 10d., 0.3" FORMERS 5937/8 and cans TV1/2. 2 1/2" sq. x 2 1/2" and 3 1/2" sq. x 1 1/2", 2/- complete with cores

**LOW MOTION DRIVES.** Epicyclic ratio 6-1, 2/3 TYANA. Midget Soldering Iron. 200/250V or 230/250V, 16/9. **SOLO MIDGET IRON**, 25W, 24/-

**MAINS DROPPERS.** 3" x 1 1/2". Three adj. sliders, 0.3A 750 ohms, 4/3; 0.2A 1,000 ohms, 4/3

**LINE CORD.** 0.3A 60 ohms per foot, 0.2A 100 ohms per foot, 2-way, 6d. per foot; 3-way, 7d. per foot

**MIKE TRANSF.** 50:1, 3/9; 100:1, potted, 10/6

**LOUDSPEAKERS.** P.M. 3 ohm. 2 1/2" and 5", 17/6; 7" x 4" Goodmans, 21/-; 4" Hi-Fi Tweeter, 25/-;

8" Plessey, 19/6; 6 1/2" Goodmans, 18/6; 10" R.A., 30/-;

12" Plessey, 30/-; 8" 2.5k field tapped, o.p. trans., 24/6;

15 ohm Plessey 10W 12", with tweeter, 97/6;

Stentorian HF1012 10" 3 to 15 ohms 10W, 99/6

**CRYSTAL DIODES.** G.E.C., 2/-; GEX34, 4/-

**40 CIRCUITS FOR GERMANIUM DIODES, 3/-**

**TUNING AND REACTION CONDENSERS** 100pF, 300pF, 500pF, 3/6 each, solid dielectric

**H.R. HEADPHONES** 4,000 ohms, brand new, 16/6 pr.

**SWITCH CLEANER FLUID**, squirt spout, 4/3 tin

**TWIN GANG CONDENSERS.** 365pF, miniature, 1 1/2" x 1 1/2" x 1 1/2", 10/-; 0.0005 standard with trimmers, 9/-; less trimmers, 8/-; Midget 7/6; 50pF single, 2/6

## 48-HOUR POSTAL SERVICE

Our written guarantee with every purchase

# RADIO COMPONE

Buses 133 or 68 pass door S.R. Scn. Selhurst

**Aluminium Chassis.** 18 s.w.g. Plain, undrilled, with 4 sides, riveted corners and lattice fixing holes, with 2 1/2" sides. 7" x 4", 4/6"; 9" x 7", 5/9"; 11" x 7", 6/9"; 13" x 9", 8/6"; 14" x 11", 10/6"; 15" x 14", 12/6"; 18" x 16" x 3", 16/6

**Volume Controls**

Midget size  
Long spindles. Guaranteed 1 year. All values 5,000 ohms to 2 Meg.  
No Switch D.P. Switch  
3/- 4/9  
Linear or Log Tracks

**80Ω Coaxial Cable**

Semi-air spaced Polythene insulated 1/4" dia. stranded core. Ideal Band III 9d. yd  
Losses cut 50%

**FRINGE QUALITY**

Air-spaced Coaxial 1/6 yd

**Coaxial Plugs** 1/- **Double Socket** 1/3  
**Sockets** 1/- **Outlet Boxes** 4/6  
**Balanced Twin Feeder**, per yd 6d., 80Ω or 300Ω  
**Twin Screened Balanced Feeder**, 1/6 yd, 80 ohms  
**Trimmers**, Ceramic 30, 50, 70pF, 9d.; 100pF, 150pF, 1/3; 250pF, 1/6; 600pF, 750pF, 1/9. Phillips, 1/- each  
**BLACK CRACKLE PAINT**, Air drying, 3/- tin  
**P.V.C. CONN. WIRE**, 8 colours, single or stranded, 2d. yd. Slewing 1, 2mm, 2d., 2, 3mm, 3d., 6mm, 5d. yd  
**5" RADIO SCREWDRIVERS**, 6d. each  
**NEON MAINS TESTER SCREWDRIVERS**, 5/3  
**SOLDER RADIOGRADE**, 3 yds 9d., 1lb 2/6  
**Sentercel Rectifiers**, E.H.T. Type, Flyback. Voltages: K3/25 2kV, 5/-; K3/40 3.2kV, 7/-; K3/45 3.6kV, 7/6; K3/50 4kV, 8/-; K3/100 8kV, 14/6

50 cps voltage 30% of above ratings  
**Mains Type RM1**, 125V 60mA, 5/-; **RM2** 100mA, 6/-; **RM3** 120mA, 8/-; **RM4** 250V 275mA, 16/-; **RM5**, 20/-  
**Miniature Contact Cooled Rectifiers**, 250V 50mA, 8/6; 250V 85mA, 9/6. Selenium Rect. 300V 85mA, 7/6  
**Coils**. Wearite "P" type, 3/- each. Osmor Midget "Q" type, adj. dust core, from 4/- each. All ranges  
**Teletron**. L. & Med. T.F.R. with reaction, 3/6  
**Ferrite Rod Aerials**, M.W., 8/9; M. & L., 12/6  
**T.R.F. Coils** A/H.F. 7/- pair, H.F. Chokes, 2/6  
**Speaker Fret**, Gold cloth, 17" x 25", 5/-; 25" x 35" 10/-  
**Expanded metal**, silver, 15 1/2" x 9 1/2", 2/- each; **Tygan**, 4" 6" wide, 10/-; 2" 3" wide, 5/- ft. Samples

**SUPERHET COIL PACK 27/6**

Miniature size high Q coils. Short, Med., Long. Gram. switching, with connection diagram. 465 kc/s i.f.

**Condensers**. New stock, 0.001μF 7kV T.C.C., 5/6 ditto 20kV, 9/6; 100pF to 500pF Micas, 6d.; Tubular 500V 0.001 to 0.01μF, 9d.; 0.05, 0.1, 1/-; 0.25, 1/6; 0.5, 1/9; 0.1/350V, 9d.; 0.01/2,000V, 1/9; 0.1/2,000V, 3/6  
**Ceramic Condensers**, 500V 0.3pF to 0.01μF, 10d.  
**Silver Mica**, 10% 5pF to 500pF, 1/-; 600pF to 3,000pF, 1/3; close tolerance (plus or minus 1pF), 1.5pF to 47pF, 1/6; ditto 1/5, 50pF to 815pF, 1/9; 1,000pF to 5,000pF, 2/-

**NEW ELECTROLYTICS FAMOUS MAKES**

TUBULAR		TUBULAR		CAN TYPES	
1/350V	2/-	100/25V	2/-	8-16/450V	5/-
2/450V	2/3	8+8/500V	6/-	16+16/450V	5/6
4/450V	2/3	16+16/500V	6/-	6,000μF 6V	6/6
8/450V	2/3	<b>CAN TYPES</b>		32+32/350V	4/6
8/500V	2/9	<b>Clips</b>		32+32/450V	6/6
16/450V	3/6	16/500V	4/-	64+120/275V	7/6
16/500V	4/-	32/350V	4/-	60+100/350V	11/6
32/450V	5/6	100/275V	5/6	100+200/275V	5/6
25/25V	1/9	50+50/350V	7/-		10/6
50/25V	2/-	500/12V	3/-		1,000+1,000/6V
50/50V	2/-	2,500/3V	4/-		6/6

**Full Wave Bridge Selenium Rectifiers**, 2, 6 or 12V 1 1/2A, 8/9; 2A, 11/3; 4A, 17/6. Free charger circuit  
**Charger Transformers**, Tapped input 200/250V for charging at 2, 6 or 12V 1 1/2A, 15/6; 2A, 17/6; 4A, 22/6

**12/6 PURETONE RECORDING TAPE**

1,200ft on standard fitting, 7" metal reels. Spare reels 7" metal, 2/3; 5 1/2" plastic, 3/-; 7" plastic, 4/-

**SUPERIOR** 1,200ft plastic tape, 21/-, 7" plastic reel  
**EMITRAC** 7" Long Play 1,800 ft. 45/-

**TELETRON MINIATURE**

**"TRANSIDYNE" Superhet Portable**

6 Transistors, T.C.C. Printed Circuit

Ferrite aerial, cabinet and all parts. For medium and long wave reception

Our price

**£12.19.6**

post free



Size 6" x 4" x 1 1/2"

Plans and parts list

9d.

**6 GENUINE PYE GOLTOP TRANSISTORS ARE INCLUDED WITH THIS KIT, FOR MAXIMUM RESULTS**

**TRANSISTORS**. Pye Goltop Audio V10/15A, 15/-; R.F. 3 Mc/s, V6/R2, 24/-; Sub-miniature Electrolytics 5μF 12V, 8μF 6V, 16μF 12V, 25μF 6V, 3/- each

**THE HIGH GAIN BAND III TV PRE-AMP**

**Tunable Channels 8, 9 and 10, Gain 17dB, Cascode Circuit**. Complete kit with ECC84 valve, plans and instructions, 29/6 less power, or 49/6 with power pack. Plans only, 6d. Band I version available for channels 1 to 5, same prices

**Wavechange Switches**, 2 p 2-way, 3 p 2-way, short spindle, 2/6; 5 p 4-way 2 wafer, long spindle, 6/6; 2 p 4-way, 4 p 2-way, 4 p 3-way, long spindle, 3/6; 3 p 4-way, 1 p 12-way, long spindle, 3/6; wave change "MAKITS", 1 wafer, 8/6; 2 wafer, 12/6; 3 wafer, 16/-; 4 wafer, 19/6; 5 wafer, 23/6; 6 wafer, 26/6  
**Toggle Switches**, s.p. 2/-, d.p. 3/6, d.p.d.t. 4/-

**JASON FM TUNER COIL SET, 26/-**. H.F. coil, aerial coil, oscillator coil, two i.f. transformers 10.7 Mc/s, detector transformer and heater choke. Circuit and component book using four 6AM6, 2/-  
**Complete Jason FM Kit**, with valves and Jason superior calibrated dial, £6.15.0, post free  
**Mullard 3-3**. Amplifier ready built, with power socket for tuner, £7.17.6

**Valveholders**, Eng. int. oct., 4d. EF50, EA50, 6d. B12A, CRT, 1/3. Ex. and Amer. 4, 5, 6, 7 and 9 pin, 1/-  
**MOULDED** Mazda and int. oct., 6d.; B7C, B8A, B8G, B9A, 9d. B7G with can, 1/6; VCR97 2/6. B9A with can, 2/6. Ceramic, EF50, B7C, B9A int. oct., 1/-; B7G with can, 1/9; B9A with can, 2/9

**HANDY VOLTMETERS**, 2" Twin Range 0-25V, 0-250V d.c. with leads and leather case, 9/6 each

**TV Fault Finding**, Data Publications 5/- each  
**Radio Valve Guide**, Books 1, 2 or 3 5/- each

**TELETRON 'COMPANION' PRINTED CIRCUIT TRANSISTOR THREE**

**£5.15.0**

WITH 3 PYE GOLTOP TRANSISTORS



Pocket receiver kit, 4 1/2" x 3" x 1 1/2" with plans, cabinet, all parts and batteries. Fitted speaker reproduces strong local stations on Ferrite Aerial. Distant reception with simple aerial or earth

**NT SPECIALISTS**

**337 WHITEHORSE ROAD WEST CROYDON**

Catalogue 6d.

Telephone THO 1665

P. & P. 1/-, over £2 post free. C.O.D. 1/6 (Export C.W.O. post extra, no H.P.)

OPEN ALL DAY (Wed. 1 p.m.)

# CLYNE RADIO LTD.



**"The Component Specialists"**

ALL POST ORDERS AND CORRESPONDENCE TO  
162 HOLLOWAY ROAD · LONDON N7  
NOR 6295/6/7

18 TOTTENHAM COURT RD. LONDON W1  
MUS 5929/0095

Callers welcome at both branches

PRINTED CIRCUIT

## THE "TRANSIDYNE"

TRANSISTOR POCKET SUPERHET

A printed circuit pocket size Transistor Receiver, professional in appearance and of outstanding performance. Incorporates T.C.C. printed circuit, six transistors (push-pull) to cover medium and long waves, utilises 2 Ever-Ready, or equivalent, No. 8 batteries. Attractive cream and red plastic cabinet with engraved dial. Overall dimensions  $7\frac{1}{2}'' \times 3\frac{1}{2}'' \times 1\frac{1}{2}''$ . Total weight when assembled, including batteries, only 20 oz. Our price for all required components, including batteries,

**£11.19.6** plus 2/6 p.p.



### A NEW TELETRON PRODUCT

(as described in this issue)

A receiver can be seen and heard working at both our branches, and is of outstanding value at the price

All resistors and condensers are identifiable and individually mounted on cards. Full instructions and individual priced parts list 1/- post free. All components can be supplied separately, for example: Complete cabinet and dial assembly, printed circuit, battery holder, nuts and bolts and full assembly instructions. 25/- plus 1/6 p.p.

3 required Audio Transistors—22/6 per set

3 required R.F. Transistors—45/- per set

### "R.E.P. MINI-7"

POCKET TRANSISTOR PORTABLE

STAR FEATURES

- ★ Utilises 7 specially selected transistors
- ★ Push-pull output
- ★ Hi-Grade  $2\frac{1}{2}''$  p.m. loudspeaker
- ★ Ferrite slab aerial
- ★ Most attractive appearance
- ★ Exceptionally good quality output
- ★ Unequaled performance

Overall dimensions only  $5\frac{1}{2}'' \times 3\frac{3}{8}'' \times 1\frac{11}{16}''$ . Powered by two miniature 3V transistor batteries. Plastic case finished in dove grey with scarlet knobs.

ALL NECESSARY COMPONENTS AT SPECIAL INCLUSIVE PRICE OF

**£9. 19. 6**

P. and P. 2/6

PRINTED CIRCUIT

TELETRON

### COMPANION

(As described in July issue.) All required components available at special **INCLUSIVE** price of 99/6 plus 1/6 p. and p.

Constructional details and itemised price list 6d. post free

### CONSTRUCTORS BARGAINS!

**Mains Transformer (Special).** Superior quality drop through type, half shrouded. Primary 200/250V. Secondary 350-0-350V at 80mA. 6.3V 3A, 5V 2A. Ex-equipment, but guaranteed O.K. Only 9/6 plus 1/- p. & p. **6V Vibrator Pack.** Ex-W.D. Output 140V 30mA. Fully smoothed. Size only  $6\frac{1}{2}'' \times 5'' \times 2\frac{1}{2}''$ . New condition. 12/6 plus 1/6 p. and p. **12V Vibrator Pack.** Mallory, brand new. Output 150V 40mA. Complete with synchronous vibrator. 12/6 plus 1/6 p. and p. **12" Bakers Selhurst Loudspeakers.** 15 ohm, 15 watt, 30/14,000 c/s. Few only. Brand new. £4-10s. plus 3/6 p. and p. **Wiring Wire.** 5 coils 10yd. each coil, in different colours, contained in cellophane bag. 5/- plus 9d. p. and p. **3-Section Whip Aerials.** Ideal for fishing rods, etc. Each section 4ft. Only 7/6 set, plus 2/6 p. and p.

**12" Plessey P.M. Loudspeaker.** 3 ohm speech coil. Brand new. Only 32/6 plus 2/6 p. and p.

**H.G.P.59 Crystal Insert.** Complete with i.p. and std. sapphire styli. Brand new, 18/- plus 9d. p. and p. Suitable for B.S.R., Monarch, etc.

**H.3 AM/FM Chassis.** (By well-known manufacturer.) Covering medium, Long and f.m. bands. Brand new and fully guaranteed. Whilst stocks last £17.19.6 plus 5/- p. and p. Leaflet on request.

**Manufacturers' Surplus Component Strips.** Comprising approx. 12 capacitors from 0.25µF to 100pF and approx. 12 resistors. All useful values. Mounted on sturdy tag board. **4 Strips** (approx. 100 components) for 5/- plus 1/- p. and p.

**Nylon Drive Cord.** 12yd. reels. Best quality 3/6 plus 6d. p. and p.

**CLR Low Impedance Headphones** 7/6 pair plus 1/- p. and p.

**Brand new imported High Impedance Lightweight Headphones.** Finished in cream. 15/- pr. plus 1/- p. and p.

**Carbon Hand Microphones** complete with press to talk switch. Lead and jack plug. 5/- each, plus 1/- p. and p.

**Morse Keys. Superior Quality.** Brand new 2/6 plus 1/- p. and p.

**Octal Plugs.** Ex-equip. 9d. each, plus p. and p. 6d.

**Packard Bell Pre-Amplifier. Snip!** With 6SL7GT, 28D7GT, plugs, hand switch, many components contained in useful metal case. Brand new, boxed complete with circuit diagram and instruction book. Only 12/6 plus 1/6 p. and p.

**Polystyrene Coil Cement.** 1/10 per bottle plus 6d. p. and p.

**We Specialise in VALVES · COMPONENTS · AM & FM CHASSIS TUNERS · AMPLIFIERS · LOUDSPEAKERS · CABINETS · RECORD PLAYERS · TAPE RECORDERS and all HI-FI EQUIPMENT Enquiries invited**

# PREMIER RADIO COMPANY

B. H. MORRIS & CO (RADIO) LTD

(Dept. R.C.7) 207 EDGWARE ROAD LONDON W2

Also 23 Tottenham Court Road London W1

Telephone  
AMB 4033  
PAD 3271

Open till  
6 p.m. Saturday



## THE "PETITE" PORTABLE

MAY BE  
BUILT FOR **7 GNS.**

plus 3/- post. & pkg.

Batteries extra

H.T. 10/- (Type B126) or  
equivalent.

L.T. 1/6 (Type AD 35) or  
equivalent.

- ★ Size only 8" x 8" x 4½"
- ★ Weight including batteries 5½lb
- ★ 4 valves of the economy type
- ★ Medium and long wave superhet circuit
- ★ High Q frame aerial
- ★ High sensitivity on both wavebands
- ★ Pre-aligned i.f. transformers
- ★ 5" speaker of the latest type
- ★ Automatic on/off switch operated by lid
- ★ Designed in our own laboratory
- ★ Backed by an up-to-date Technical Information Dept.
- ★ Components available separately if desired
- ★ Simple to construct, using normal soldering methods
- ★ Instruction book 1/6

## THE "PETITE" PORTABLE & REPRODUCER

MAY BE  
BUILT FOR **13 GNS.**

plus 5/- post. & pkg.

Batteries extra: H.T. 10/-  
(Type B126 or equiv.) L.T.  
996, 3/6



45 r.p.m. Single Record Player  
£5.5.0 including P.T.

"Petite" Components  
£5.13.0

Portable Case £2.10.0

- ★ Size 10¼" x 9¾" x 6"
- ★ Weight including batteries 7lb
- ★ 45 r.p.m. single record player complete with pick-up
- ★ 6V battery operated
- ★ Incorporates pick-up head protection dome and automatic stylus cleaning brush, overall size 7¼" x 6" only
- ★ Automatic stop-start
- ★ Completely battery operated
- ★ Attractive two-tone rexine covered case
- ★ Construction simplicity itself
- ★ Components available separately if required
- ★ Instruction Book 1/6

## THE ARGONAUT

AM—FM MW—VHF  
TUNER—RECEIVER

First published in the March and April 1956 issues of this magazine this high quality tuner-receiver has aroused considerable interest. In this reprint the text has been revised and enlarged, and additional diagrams, including a map of present and projected coverage areas, have been included as a result of suggestions by readers

28 pp. plus stiff card cover  
Price 2/- postage 4d.

Published by

# DATA PUBLICATIONS LTD

57 MAIDA VALE · LONDON W9

Telephone CUNningham 6141 (2 lines)

Telegrams Databux London

## Radio Control Mechanisms

by

RAYMOND F. STOCK

A new publication—and the first devoted entirely to the subject of radio control linkage mechanisms. Complementary to *Radio Control for Model Ships, Boats and Aircraft* and to other books on radio control.

64 PAGES

ART BOARD COVER

70 ILLUSTRATIONS

4/6 postage 4d.

# Yours the easiest way!

## 21 RANGES

covering  
 10-1000 d.c. volts  
 10-1000 a.c. volts  
 100 Microamps to  
 500 Milliamps d.c.  
 100 Microamps a.c.  
 0 to 1 Megohm  
 0 to 10,000 ohms

\*There is also the  
**SERIES 90 MULTI-RANGE TEST SET**  
 having 19 SELF-CONTAINED Ranges, ac/dc Volts up to 1000V dc current .. 500mA ac .. 230µA Resistance 0-200,000Ω  
 Deposit 35/- and six monthly payments of 28/10 (Cash price £9.15.0)  
 GD20



## MULTI-RANGE TEST SET - SERIES 100

To MEASURING INSTRUMENTS (Pullin) Ltd  
 Electrin Works, Winchester Street,  
 Acton, London, W.3

Please send illustrated leaflet of the Series 100 Test Set with details of new easy payment scheme  
 Ditto Series 90 .....


\*Please indicate instrument required

NAME .....

ADDRESS .....

F958

### MULTI-PURPOSE NEON TESTER

(Page 135 this issue)

Complete kit. Containing resistors, condensers, special sub-miniature neon, fully insulated safety colour coded crocodile clips; sub-miniature jack and socket for output. Price complete 9/8 (Or with standard coax output 10/-)

GENERAL ITEMS. Miniature neons (as used in mains testers) 1/10. Resistors, carbon from 3d., wire-wound from 1/3, hi stabs from 6d. (Send list of requirements for quotation—stocks are always changing). Mixed Carbon 50 for 7/-. Capacitors, paper from 10d., 5/mica from 8d. 'Ajax' Crystal Kit complete, 14/6 (L.W. 15/-). Phones 14/- and 16/-. 'Ajax' Case with chassis, 5/9. Cored Solder 4d. yard, 19 ft reel 2/6, 11b reel 14/9. Fine gauge for printed circuits, 40 ft reel 2/6. Switches, s/p from 2/3, d/p from 3/6. Ferrite Rods 8" x 1/4" diam., 2/-. Mains neon indicators with built-in resistor. Domed top, chrome bezel, 1" long 1/2" diam. Opal, red, amber, 3/10; green 4/7. Mullard 3-valve 3 watt Amplifier, wired and tested. Limited number at £9.15.6.

### The TRANSIDYNE RECEIVER

(Page 119 this issue)

We guarantee all components to be exactly as specified by designer & approved by Messrs. Teletron  
 Drilled case, printed circuit, battery holder, dial, nuts, screws £15.0  
 Complete coil and aerial kit £2.2.0  
 Resistor kit (with circuit references) 6/-  
 Condenser kit (with circuit references) £1.5.0  
 Rola speaker (tax paid) £1.8.2  
 J.B. tuning condenser with centre screen 10/6  
 Ardente D131 & D132 per pr. £15.6  
 Ardente volume control (R15) 12/6  
 Slider wavechange switch 3/6  
 GEX34 diode 4/-  
**COMPLETE KIT AS ABOVE AT THE SPECIAL PRICE OF £8.15.6**  
 Transistors—  
 Red/Yellow (r.f.) £1 each  
 Green/Yellow (audio) 9/6 each  
**COMPLETE KIT WITH TRANSISTORS AT THE SPECIAL REDUCED PRICE OF £11.19.6**  
 FREE—Special 'printed circuit' solder with each kit

TRANSISTOR KITS. Companion £5.15.6. Leaflet 6d. 'Mini-7', £12.10.0, Envelope 1/6

### JACK PLUGS AND SOCKETS

(by Bulgin)

Miniature type 3/8" diameter, panel space. 3/8" behind panel. With optional closed circuit leaf.  
 Plug 3/- Socket 2/6

Sub-miniature type 1/4" x 1/2" panel space. 1/2" behind panel, 3/8" projection.  
 Plug 9d. Socket 1/3

TRANSISTOR ITEMS. Electrolytics 8µF 6V, 16µF 12.5V, 32µF 3V, 5µF 12.5V, 5µF 40V, 2.5µF 40V, 1.6µF 6V. All 3/3 each: 100µF 6V 3/-; Paper 0.01, 0.001, 0.002, 0.005µF, all 8d. each. Transistor Holders 1/- each, 6 for 5/9, 11/- doz. Ardente T.1065 transformers (page 911—July), 12/- Subminiature Speakers 1 1/2" round, 27/-; 2" x 3" elliptical, 33/-; Output Transformers, single-ended or p/p, 12/6. Volume Controls, button type (totally enclosed), 47k and 1MΩ, 2/6; preset skeleton type 5k 2/6; spindle type 1/2M, 1M, 2M, 4/3 (page 705—'R.C.' May). Ardente Catalogue 6d.

We recommend the 'LITESOLD' soldering iron for all fine work. Mains or battery. 21/6 complete (state mains voltage)

QUOTATIONS gladly given (S.A.E. please)

## R. FAGELSTON (MAIL ORDER)

Please add Postage to above prices

••••• 46 HARDWICKE ROAD • LONDON N13 •••••

# EMI

"HIS MASTER'S VOICE"  
MARCONIPHONE · COLUMBIA

Announce

## NEW PRACTICAL WAY OF LEARNING AT HOME

**NEW**— completely up-to-date methods of giving instruction in a wide range of technical subjects specially designed and arranged for self-study at home under the skilled guidance of our teaching staff.


**NEW**— experimental outfits and lesson manuals are despatched on enrolment and remain the student's property. A tutor is allotted to each student for personal and individual tuition throughout the course.

Radio and television courses, with which specially prepared components are supplied, teach the basic electronic circuits (amplifiers, oscillators, detectors, etc.) and lead, by easy stages, to the complete design and servicing of modern Radio and T/V equipments.

If you are studying for an examination, wanting a new hobby or interest, commencing a career in industry or running your own full-time or part-time business, these practical courses are ideal and may be yours for moderate cost. Send off the coupon to-day for a free Brochure giving full details. There is no obligation whatsoever.
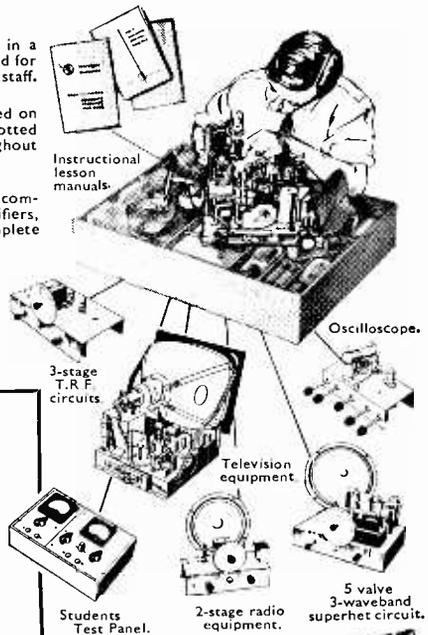
### Courses with Equipment

**RADIO · SHORT WAVE RADIO  
TELEVISION · MECHANICS  
CHEMISTRY · PHOTOGRAPHY  
ELECTRICITY · CARPENTRY  
ELECTRICAL WIRING · 'HI-FI'  
DRAUGHTSMANSHIP · ART, etc.**



E.M.I. Factories  
at Hayes,  
England.



# EMI INSTITUTES

Fill in for **FREE BROCHURE**  
E.M.I. INSTITUTES, Dept. 179X, London, W.4.

Name..... Age.....  
(If under 21)

Address.....

I am interested in the following subject(s) with/  
without equipment.....  
(We shall not worry you with personal visits)



BLOCK  
CAPS  
PLEASE

IC-107  
Senr '55

*The only Home Study College run by a World-wide industrial organisation.*

---

# *There's nothing so good*

## AND IT'S BEST IF IT'S A

**Jason**kit

When good circuitry and design are presented with straightforward, easily followed instructions, it becomes relatively simple to build technically advanced items of radio, audio and electronic equipment. There are already years of specialised experience in kit design and production behind the new Jasonkit programme. From it, the constructor can choose stereo amplifier and pre-amp designs, first-class fm tuners, and soon, a number of items of valuable electronic test equipment. Such is the quality of Jason designs that even to-day, the popularity of the original f.m. tuner, which was the first Jasonkit to be produced, is as great as ever and large numbers continue to build it with complete success.

No special tools or experience are required to build Jasonkits. To the satisfaction of building your own apparatus is added the knowledge that its performance will be the finest possible in its class. Kits are complete, too, down to the last detail, and include chassis and panels punched and drilled to size. Only valves are extra except where otherwise stated.

### *BRITISH THROUGHOUT*

*Details of kits in which you are interested gladly sent on request*

## THE JASON MOTOR & ELECTRONIC SALES CO

---

# as building it yourself



FM tuners  
 am/fm tuners  
 fm/ty tuners  
 stereo amplifiers  
 stereo pre-amplifiers  
 electronic instruments

## AUDIO

STANDARD FM TUNER in chassis form **£5.5.0**  
 Power Pack Kit **£2.1.9**

- ARGONAUT AM/FM TUNER.** As tuning unit only ... .. **£10.10.0**  
 As complete receiver ... .. **£11.11.0**
- MERCURY SWITCHED FM TUNER** including front end complete with  
 two valves ... .. **£9.0.0**
- STEREO AMPLIFIER** (10+10 watts) Power Amplifier with 7 valves ... **£17.8.0**
- STEREO PRE-AMP J.4-4** with case, but less valves ... .. **£16.10.0**
- STEREO PRE-AMP J.3-3** with valves and case ... .. **£16.15.0**
- STEREO PRE-AMP J.3-3** with valves, less case ... .. **£16.0.0**

**AVAILABLE SHORTLY**—Simplified Stereo Amplifier with FM Tuner to match: also switched FM/TV Sound Tuner

## INSTRUMENTS

**for release shortly**

**VALVE VOLTMETER; WOBBULATOR; STABILISED POWER PACK;  
 OSCILLOSCOPE:**—For all who wish to build and experiment to a high degree of accuracy.  
 These kits have attractive uniformly styled front panels and may be built with or without  
 the standardised cases.

**3-4(E) GT. CHAPEL STREET OXFORD STREET LONDON W1**

(between Tottenham Court Road and Oxford Circus Station Underground)

Telephone GERrard 0273/4

# ◆ ◆ ◆ ◆ REPANCO ◆ ◆ ◆ ◆

## HIGH GAIN COILS and QUALITY COMPONENTS for the constructor

### TRANSISTOR COMPONENTS

- FERRITE SLAB AERIAL TYPE FS2.** A new super-sensitive aerial, Long and Medium Wave, specially designed for transistor portable receivers. Complete with fixing brackets. Length  $5\frac{1}{2}$ " 12/6
- COMBINED OSCILLATOR AND 1st I.F. TRANSFORMER TYPE OT1** (315 kc/s), fully screened,  $1\frac{1}{2}$ " x  $1\frac{1}{2}$ " x  $1\frac{1}{2}$ " ... .. 11/6
- 2nd I.F. TRANSFORMER TYPE TT2** (315 kc/s),  $1"$  x  $\frac{3}{8}"$  dia. ... .. 5/-
- 3rd I.F. TRANSFORMER TYPE TT3** (315 kc/s),  $1"$  x  $\frac{3}{8}"$  dia. ... .. 5/-
- PUSH-PULL INTER-STAGE TRANSFORMER TYPE TT4.** Ratio 1:1 ct. Stack  $1\frac{3}{8}"$  x  $1\frac{1}{16}"$  x  $\frac{7}{16}"$  8/6
- PUSH-PULL OUTPUT TRANSFORMER TYPE TT5.** Ratio 15:1 ct. Stack  $1\frac{3}{8}"$  x  $1\frac{1}{16}"$  x  $\frac{7}{16}"$  8/-

### MINIATURE RANGE—For pocket receivers

- FERRITE SLAB AERIAL TYPE FS3.** Medium Wave only. With fixing grommets. Size  $3"$  x  $\frac{3}{8}"$  x  $\frac{3}{32}"$  7/6
- OSCILLATOR COIL TYPE XO8.** Medium Wave only. Overall size  $\frac{1}{2}"$  dia. x  $1"$ . Enclosed in Ferrite pots ... .. 5/-
- I.F. TRANSFORMER TYPE XT6.** Suitable for 1st and 2nd I.F. 455 kc/s. Size  $\frac{1}{2}"$  sq. x  $\frac{1}{16}"$  ... 10/-
- I.F. TRANSFORMER TYPE XT7.** Designed for 3rd I.F.T. or detector I.F.T. 455 kc/s. Size as XT6 ... .. 10/-
- PUSH-PULL INTERSTAGE TRANSFORMER TYPE TT9.** Ratio 1:1 ct. Radiometal Core. Size  $\frac{3}{4}"$  x  $\frac{3}{8}"$  x  $\frac{1}{16}"$  ... .. 12/6
- PUSH-PULL OUTPUT TRANSFORMER TYPE TT10.** Ratio 8:1 ct. Matched to 3 ohm speaker. Size as TT9 ... .. 12/6
- Practical and Theoretical circuits enclosed with each Repanco Transistor Component*

### COILS AND TRANSFORMERS FOR TRANSISTORISED CAR RADIO

- |  |   |   |
|--|---|---|
| Medium Wave Aerial Coil Type XMA16... 10/- | } | Interstage Transformer Type TT11 ... 10/-               |
| Medium Wave H.F. Coil Type XMF17 ... 10/-  | } | Output Transformer (12 volt Radio) Type TT12... .. 12/6 |
| Long Wave Aerial Coil Type XLA18 ... 6/9   | } | Output Transformer (6 volt Radio) Type TT13... .. 12/6  |
| Long Wave H.F. Coil Type XLF19... .. 6/9   | } |   |
| Oscillator Coil Type X015 ... .. 5/-       | } |   |

All this range boxed with circuit and practical diagram of all-Transistor Car Radio

### REPANCO EASY-TO-BUILD RECEIVERS

Constructors' Envelopes of easy wiring plans, instructions and detailed price lists of components

- THE HIWAYMAN** ... .. Envelope 1/6 (post 3d.)  
Four-valve superhet Dual-range Portable using Ferrite Rod Aerial
- REPANCO ONE-VALVE** ... .. Envelope 9d. (post 3d.)  
Beginner's Dual-range Radio Set for use with headphones
- REPANCO FM TUNER UNIT** ... .. Envelope 1/6 (post 3d.)  
Using 4 EF91, 1 EB91, 1 EM80 Valves, Ratio Detector
- REPANCO "THREE DEE"** ... .. Envelope 9d. (post 3d.)  
Dual-range Transistor Radio using 3 Transistors and Crystal Diode. Amazing loudspeaker reception from  $7\frac{1}{2}$  volt battery supply
- REPANCO "TRANSEVEN"** ... .. Envelope 1/6 (post 3d.)  
A new 7 Transistor superhet Portable with preset station tuning using Repanco transistor components
- REPANCO "MINI-7"** ... .. Envelope 1/6 (post 3d.)  
The amazing new transistor pocket portable radio with all the technical features of a standard receiver. Seven transistors, superhet circuit, fully tunable over medium wave. Size  $5\frac{1}{8}"$  x  $3\frac{1}{8}"$  x  $1\frac{1}{8}"$

MAIL ORDER and TRADE—

**RADIO EXPERIMENTAL PRODUCTS**  
LIMITED  
33 MUCH PARK STREET COVENTRY  
Telephone 62572

WHOLESALE and EXPORT—

**REPANCO LTD**  
O'BRIENS BUILDINGS  
203-269 FOLESHILL ROAD COVENTRY  
Telephone 40594

# Wanted!

**QUALIFIED MEN AND WOMEN**

Industry and Commerce offer their best posts to those with the qualifications — appointments that will bring personal satisfaction, good money, status and security. As part of a modern industrial organisation, we have skilled knowledge of what is required and the best means of training personnel for its present day and future requirements. We specialise also in teaching for hobbies, new interests or part-time occupations in any of the subjects listed below. Write to us to-day for further information. There is no obligation of any kind.

## PERSONAL & INDIVIDUAL TRAINING IN—

Accountancy	Electronics	Production
Advertising	Electronic	Planning
Aeronautical Eng.	Draughtsmanship	Radar
A.R.B. Licences	Eng. Drawing	Radio
Art (Fashion, Illustrating, Humorous)	Export	Radio Amateur's (C&G) Licence
Automobile Eng.	General Certificate of Education	Radio & Television Servicing
Banking	Heating & Ventilating Eng.	Refrigeration
Book-keeping	High Speed	Sales Management
Building	Oil Engines	Sanitary Eng.
Business Management	Industrial Admin.	Salesmanship
Carpentry	Jig & Tool Design	Secretaryship
Chemistry	Journalism	Shorthand & Typing
City & Guilds Exams	Languages	Short Story Writing
Civil Service	Management	Short Wave Radio
Commercial Subjects	Maintenance Eng.	Sound Recording & Reproduction
Commercial Art & Drawing	Mathematics	Telecommunications
Customs Officer	M.C.A. Licences	Television Time & Motion Study
Draughtsmanship	Mechanical Eng.	Tracing
Economics	Metalurgy	Welding
Electrical Eng.	Motor Eng.	Workshop Practice
Electrical Installations	Painting & Decorating	Works Management and many others
	Photography	
	P.M.G. Cert.	
	Police	
	Production Eng.	

### OUR BACKGROUND!




The E.M.I. Factories at Hayes, England.

Also courses for GENERAL CERTIFICATE OF EDUCATION, A.M.I.H.&V.E., A.M.S.E., A.M.Brit.I.R.E., A.M.I.Mech.E., A.M.I.E.D., A.M.I.M.I., A.F.R.Ae.S., A.M.I.P.E., A.M.I.I.A., A.C.C.A., A.C.I.S., A.C.C.S., A.C.W.A., City & Guilds Examinations, R.T.E.B.Serv. Cert. R.S.A. Certificates, etc.

The only Home Study College  
operated by a world-wide  
manufacturing organisation

**NEW!** Courses with PRACTICAL EQUIPMENT

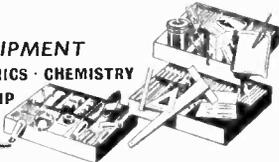IN RADIO · TELEVISION · MECHANICS · CHEMISTRY  
ELECTRICITY · DRAUGHTSMANSHIP  
PHOTOGRAPHY, ETC., ETC.



# EMI

## INSTITUTES

**POST THIS TODAY**

E.M.I. INSTITUTES, Dept. 179K, London, W.4

NAME  AGE (if under 21)

ADDRESS

I am interested in the following subject(s) with/without equipment

Sept/58

(We shall not worry you with personal visits).

**FREE**


BLOCK  
CAPS  
PLEASE

IC 92

*The only Home Study College run by a World-wide industrial organisation*

# HOME RADIO OF MITCHAM MIT 3282

for **HI-FI**

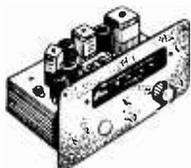

## JASON FM TUNER

The most popular and successful FM tuner ever. Full constructional data 2/4 post paid. Full kit of parts down to last nut and bolt, £7.7.6, post 1/-

## PYE "MOZART"

Brilliant new 10 watt high fidelity amplifier. Compact and easy to install. Holds a commanding lead in technical quality and modern streamlined appearance.



Full specification on request or call for demonstration  
**PRICE 22 gns.**

## KITS

We stock all the parts for the following popular constructional kits. Detailed price lists of any of these available on request: 3d. stamp.

**MINI-7** 7-transistor pocket portable. Data 1/9 post paid.

**BAND III PRE-AMPLIFIER** improves your I.T.V. Data 1/3 post paid.

**ONE VALVE RADIO** for the beginner. Data 1/- post paid.

Jason **"MERCURY"** switch tuned FM tuner Data 1/9 post paid.

**HIWAYMAN** 4-valve all-Dry portable. Data 1/9 post paid.

**MULLARD 510** amplifier including pre-amps, etc. Book 4/- post paid.

Teletron 3-transistor receiver. Strong signal areas. Data 9d. post paid.

**THREE DEE** 3-transistor bedroom set. 5" speaker. Data 1/- post paid.

**MULLARD 'A,' 'B,' and 'C'** tape amplifiers.

**VERSATILE** 2-VALVE AUDIO PRE-AMPLIFIER. Data 1/3 post paid.

**COMMUNICATIONS PRE-SELECTOR.** See April R.C.

## JASON STEREO

All component parts in stock and detailed price list on request. Ronnette Stereo pick-up insert in stock, price £3.9.6



1958 Edition of the HI-FI YEAR BOOK now available. All you want to know about hi-fi and equipment. PRICE 10/6 plus 1/3 post

Add life and realism to your sound with the Lorenz LPH65 tweeter. Amazing results. Price 39/6 plus cross-over condenser 3/-, post 1/-

Full range of DULCI and ARMSTRONG amplifiers and chassis, etc., always in stock. We also stock BERON chassis. New demonstration room now open. Callers welcome.

Dept. C · 187 LONDON ROAD · MITCHAM · SURREY

Shop Hours: 9-6.30 p.m. Wednesdays 9-1 p.m.

## HI-FI ENTHUSIASTS ALL OVER THE WORLD are building the . . .

## COOPER-SMITH Model BPI\*

The "B.P.I." is not just another amplifier kit, but a Hi-Fi amplifier equal to anything on the market for quality and styling and better than most much-advertised amplifiers costing pounds more. Designed originally for the home constructor, it can also be supplied laboratory built and tested.

• Demonstrations at address below

All orders and enquiries to

**H. L. SMITH & CO. LTD**

## Why not you?



### DIRECT FROM MAKER TO USER

Send 2/8 for this profusely illustrated booklet which contains full constructional details, articles on choosing associated equipment, a reprint of the review by G.W.T. in Hi-Fi News and a price list of components (any part may be purchased separately).

Complete Kit of parts for Amplifier (incl. valves) **£12.12.0**

Complete Kit of parts for Control Unit (incl. valves) **£8. 3.0**

Amplifier, Built and Tested **£14.17.0**

Control Unit Built and Tested **£11. 3.0**

\* **Balanced Phase Inversion** Carriage free in U.K.

287/289 Edgware Road London W2  
Telephone PADdington 5891

The

# Radio Constructor

incorporating THE RADIO AMATEUR



VOL. 12 No. 2

SEPTEMBER 1958

ANNUAL SUBSCRIPTION 25/- (including postage)

## CONTENTS

*Editor*  
C. W. C. OVERLAND, G2ATV

*Associate Editor*  
A. C. GEE, G2UK

*Business Manager*  
J. H. BURROWS, A C A

*Advertising Manager*  
F. A. BALDWIN, A M I P R E

*Offices*  
57 MAIDA VALE LONDON W9

*Telephone*  
CUNNINGHAM 6141  
(2 lines)

*Telegrams*  
DATABUX, LONDON

- 94 Suggested Circuits: Two and Three-Stage Sequential Neon Circuits, *by G. A. French*
- 98 In Your Workshop
- 103 Understanding Television, Part 9  
*by W. G. Morley*
- 109 Can Anyone Help?
- 110 A Pre-Tuned Superhet Receiver  
*by S. E. Keeley*
- 113 Radio Miscellany, *by Centre Tap*
- 116 A Multi-Range Electrostatic Voltmeter  
*by B. K. Poulson and J. D. Ward, G3HDW*
- 119 The Teletron "Transidyne" 6-Transistor Pocket Portable Superhet, Part 1  
*described by Edwin Marshall*
- 126 Models for Radio Control—The "Wavemaster" Kit, Part 2, *by Raymond F. Stock*
- 129 A Corner Reflector Aerial—for Band 3  
*by J. C. Belcher, G3FCS*
- 132 Loudspeaker Cross-over Networks,  
*by C. M. Pearson, B.Sc.*
- 135 A Multi-Purpose Neon Tester, *by M. J. Rogers*
- 136 A New Detector and Audio Amplifier  
*by K. E. Marcus*
- 139 A Stabilised Audio Oscillator  
*by G. K. Fairfield*
- 142 Book Reviews

## NOTICES

THE CONTENTS of this magazine are strictly copyright and may not be reproduced without obtaining prior permission from the Editor.

ARTICLES appearing in this magazine which describe kits are inserted only on condition that such kits, or special components thereof, are freely available at a trade discount to all retail advertisers.

OPINIONS expressed by contributors are not necessarily those of the Editor or proprietors.

THE EDITOR invites original contributions on construction of radio subjects. All material used will be paid for. Articles should preferably be typewritten, and photographs should be clear and sharp. Diagrams need not be large or perfectly drawn, as our draughtsmen will redraw in most cases, but all relevant information should be included.

ALL MSS must be accompanied by a stamped addressed envelope for reply or return. Each item must bear the sender's name and address.

TRADE NEWS. Manufacturers, publishers, etc., are invited to submit samples or information of new products for review in this section.


QUERIES. We regret that we are unable to answer queries, other than those arising from articles appearing in this magazine: nor can we advise on modifications to the equipment described in these articles.

ALL CORRESPONDENCE should be addressed to THE RADIO CONSTRUCTOR 57 Maida Vale London W9

REMITTANCES should be made payable to "DATA PUBLICATIONS LTD."
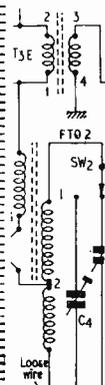
# Suggested Circuits

No. 94 Two & Three-Stage Sequential  
Neon Circuits



*The circuits presented in this series have been designed by G. A. FRENCH, specially for the enthusiast who needs only the circuit and essential relevant data*

**V**ERY FAMILIAR IN THE ELECTRONIC FIELD are devices which continually change from one state to another and back again. Typical of such devices is the multivibrator, in which two valves are interconnected such that either valve alternately passes current or is cut off. It is possible to employ neon bulbs in circuits which similarly alternate between one state and another, neon bulbs being suitable for this application due to the fact that their striking potentials are higher than those at which they burn. What is, perhaps, of more interest is the point that, by taking advantage of the properties of neon bulbs, it becomes possible to have *three* neon bulbs interconnected such that they ignite sequentially.

In this month's contribution the writer describes two- and three-stage sequential neon circuits, both of which he has developed with the aid of working prototypes. The three-stage circuit is that most worthy of attention, but the two-stage arrangement still has its uses. An understanding of two-stage operation is, in any case, helpful when the three-stage circuit comes to be discussed.

## The Two-Stage Circuit

The two-stage sequential circuit is illustrated in Fig. 1. Two neons are shown in this

diagram, and the purpose of the circuit is to cause them to be ignited alternately at a regular frequency.

To understand the functioning of the circuit, let us assume that the device is running and that neon NE<sub>1</sub> is illuminated and neon NE<sub>2</sub> is extinguished. Due to the fact that condenser C<sub>1</sub> has been previously charged from the negative supply line via R<sub>2</sub>, the current maintaining illumination in NE<sub>1</sub> flows from this condenser. The current from C<sub>1</sub> flows, also, through resistor R<sub>1</sub>, with the result that the bottom end of this resistor has a potential lower than that of the positive supply line. At the same time condenser C<sub>2</sub> charges up via resistor R<sub>3</sub>.

During the time that NE<sub>1</sub> draws current from C<sub>1</sub>, the potential across the plates of this condenser decreases. After a period this potential falls to too low a value to maintain illumination and neon NE<sub>1</sub> becomes extinguished. In consequence no further current is drawn through R<sub>1</sub>, and the potential at the bottom end of this resistor rises very rapidly to the potential of the positive supply line. When it reaches a potential which is sufficiently high above that on the lower plate of C<sub>2</sub>, neon NE<sub>2</sub> strikes. After striking, NE<sub>2</sub> remains illuminated, drawing current from condenser C<sub>2</sub> and causing, once more, a voltage drop in R<sub>1</sub>.

As soon as  $NE_1$  became extinguished no further current was drawn from  $C_1$ , whereupon this condenser is now in process of charging up via resistor  $R_2$ . When the potential across  $C_2$  becomes too low to maintain illumination in neon  $NE_2$ , this neon extinguishes, causing the bottom end of resistor  $R_1$  to rise once more to the potential of the positive line. Immediately it has risen sufficiently high above the potential held by the lower plate of  $C_1$ , neon  $NE_1$  strikes and a new cycle commences.

Summing up the above description, it may be said that each neon, when it is illuminated, draws current from its attendant condenser, this current being maintained until the potential across the condenser is too low to sustain illumination. Also, if a neon is not illuminated, its attendant condenser recharges, ready for the next period of illumination, via the resistor which connects it to the negative supply line. Due to the presence of  $R_1$  the extinguishing of one neon causes a striking potential to be applied to the other, its attendant condenser having in the meantime acquired sufficient charge to maintain illumination.

In practice, the circuit of Fig. 1 should not prove very difficult to get into working order. The writer employed G.E.C. Button Tuneons in the prototype and these gave reliable results. When neons of this type are used it is important to ensure that their tips are connected as shown and that the polarity of the supply is that indicated in the diagram. If these points are not observed, the device may not function satisfactorily.

Resistor  $R_1$  is not very "critical" so far as value is concerned. Due to what appears to be differences between neons it may, however, be necessary to adjust the values of  $R_2$  or  $R_3$  in order to get approximately 50:50 periods of illumination. In the writer's prototype different pairs of neons gave times of illumination between the approximate limits of 30:70 and 50:50. The process of adjusting the values of  $R_2$  or  $R_3$  is quite simple. If, for instance, neon  $NE_1$  remains illuminated for longer periods than does neon  $NE_2$  the value of  $R_2$  should be increased, in steps of  $0.5M\Omega$ , until approximately 50:50 operation is obtained. Similarly, the value of  $R_3$  should be increased if the period of


illumination of  $NE_2$  is longer than that of  $NE_1$ .

The condensers  $C_1$  and  $C_2$  may be conventional  $\pm 20\%$  components, as changes in value here do not seem to have as great an effect on illumination times as do discrepancies between neons. The reason for this may be that these condensers are charging and discharging over a potential range which is low compared to the total potential applied by the supply. It is, of course, necessary to ensure that the components employed in the  $C_1$  and  $C_2$  positions have good insulation resistance.

Using the component values given in Fig. 1 the frequency of operation is approximately 1.5 cycles per second. Should it be desired, this frequency may be altered, this being done by varying the values of  $C_1$  and  $C_2$ . Increasing capacity should cause a reduction in frequency, and vice versa. The writer has not checked the circuit with condenser values other than those shown in Fig. 1, and would like to pass on the hint that, if large differences in condenser values are tried, it may be necessary to experimentally alter the value of  $R_1$ .

### The Three-Stage Circuit

Fig. 2 illustrates the three-stage circuit. As may be seen, this is basically similar to that of Fig. 1 with the exception that all the resistive sections are made partially variable in value. As will be explained later, it is not entirely necessary to employ variable resistors in the  $R_4$ ,  $R_6$  and  $R_8$  positions. However, it is helpful to include them during construction

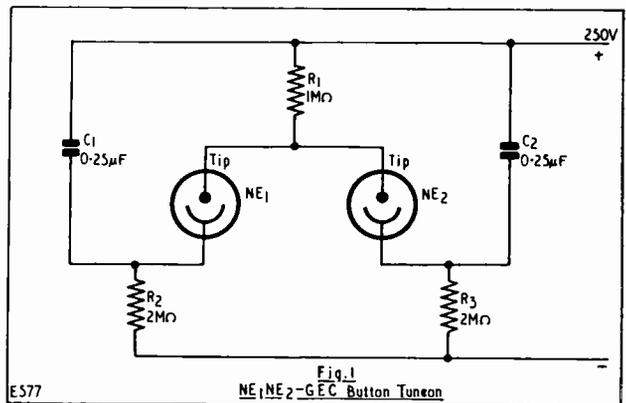

of the device as they assist considerably in initial setting-up.

To describe the operation of the circuit of Fig. 2 it is desirable to assume that the neons are igniting in the order  $NE_1$ ,  $NE_2$ ,  $NE_3$ , and


that we commence our examination at a time when neon NE<sub>1</sub> is illuminated.

Due to the fact that it is illuminated, neon NE<sub>1</sub> draws current from its associated condenser C<sub>1</sub>, causing thereby a potential drop across the two resistors R<sub>1</sub> and R<sub>2</sub> in series. (These two resistors carry out the same function as did R<sub>1</sub> in Fig. 1.) When condenser C<sub>1</sub> is sufficiently discharged, neon NE<sub>1</sub> becomes extinguished, and current flow through R<sub>1</sub> and R<sub>2</sub> ceases. In consequence the lower end of R<sub>2</sub> rises very rapidly to the potential of the positive supply line. When the lower end of R<sub>2</sub> rises sufficiently high above the potential held by the bottom plate of either C<sub>2</sub> or C<sub>3</sub>, the associated neon strikes and the potential at the bottom end of R<sub>2</sub> drops again. Of the two condensers, the bottom plate of C<sub>2</sub> has a lower potential than has that of C<sub>3</sub>, and so it is NE<sub>2</sub> which strikes. The lower potential on the bottom plate of C<sub>2</sub> is due to the fact that this condenser has been charging during the period when NE<sub>3</sub> and NE<sub>1</sub> were, consecutively, illuminated, whilst C<sub>3</sub> has been charging only during the time when NE<sub>1</sub> was illuminated.

charge whereas C<sub>1</sub> has had only one (that given by NE<sub>2</sub>). As a result NE<sub>3</sub> strikes and remains illuminated. When NE<sub>3</sub> extinguishes, condenser C<sub>1</sub> will have acquired sufficient charge to cause NE<sub>1</sub> to strike, and the next cycle commences.

It will have been noted that, in the description of circuit operation just given, it is assumed that the neons ignite in the order NE<sub>1</sub>, NE<sub>2</sub>, NE<sub>3</sub>. In practice, the application of the supply voltage may cause the neons to ignite either in the order NE<sub>1</sub>, NE<sub>2</sub>, NE<sub>3</sub>, or in the reverse order, the initial choice being random. However, as soon as the order of ignition has shown itself it remains constant until the supply is switched off.

As was mentioned above, the potentiometers R<sub>4</sub>, R<sub>6</sub> and R<sub>8</sub> are included in the circuit to simplify the process of setting up. In Fig. 1 it was possible to take up apparent discrepancies between neons by simple variations in the values of R<sub>2</sub> and R<sub>3</sub>, this being due to the fact that the circuit should still give sequential operation even if neons with widely varying characteristics are used. In the case of Fig. 2, however, circuit operation is somewhat more complicated and the

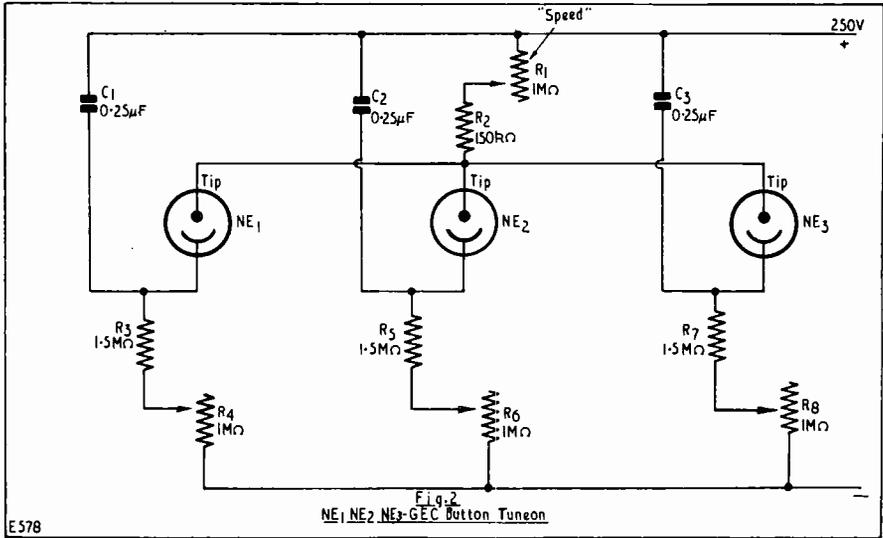

When, in its turn, condenser C<sub>2</sub> becomes sufficiently discharged, neon NE<sub>2</sub> extinguishes and the bottom end of R<sub>2</sub> once more rises towards the positive supply potential. Of the two remaining condensers, C<sub>3</sub> has a lower potential on its bottom plate than has C<sub>1</sub> because it has now had two illumination periods (given by NE<sub>1</sub> and NE<sub>2</sub>) in which to

device may not give sequential operation until the resistors connected between the charging condensers and the negative supply line have been given suitable values. It must be emphasised that this point should not be interpreted to infer that the settings of R<sub>4</sub>, R<sub>6</sub> and R<sub>8</sub> are at all "critical," because this is by no means the case. The reason for the

inclusion of variable resistors at these positions is that the values required for practical operation are liable to be widely variant.

To set up the circuit of Fig. 2, the power supply should be initially switched on and  $R_1$  set to a central position. The neons should then commence to flash in order, whereupon  $R_4$ ,  $R_6$  and  $R_8$  should be adjusted to ensure that the neons remain illuminated for approximately equal periods of time. Increasing the resistance inserted by any of the three variable resistors causes the associated neon to flash for a shorter period of time, and vice versa. If it is found that the neons do not flash consecutively, that which flashes most frequently should be identified, and the resistance inserted by its associated variable resistor increased. Similarly, it may be necessary to decrease the resistance inserted by the remaining variable resistors in order to allow the other neons to flash more frequently. Once the neons are running consecutively it will be found that the final settings of  $R_4$ ,  $R_6$  and  $R_8$  fall within quite broad limits. The variable resistors should be set such that reliable operation is obtained for all positions of the "Speed" control  $R_1$ .\* After  $R_4$ ,  $R_6$  and  $R_8$  have been set up, the resistance arms in which they appear may be replaced by single fixed resistors, should this be desired.

The "Speed" control,  $R_1$ , enables the

---

\* The values for  $R_4$ , to  $R_8$ , shown in Fig. 2 were found to provide adequate control in the writer's prototype for all neons checked in the circuit. Should it appear that sufficient resistance range does not appear to be offered by  $R_4$ ,  $R_6$ , or  $R_8$ , the value of the associated series fixed resistor may be increased, or decreased, accordingly.

frequency at which the circuit runs to vary, approximately, from 0.5 to 2 c/s. If frequencies outside this range are required, these would probably best be obtained by varying the values of  $C_1$ ,  $C_2$  and  $C_3$ . The writer has not, however, checked operation with condensers having values other than those shown in Fig. 2.

As with the device of Fig. 1, it is important to ensure that the neons (when Button Tuneons are employed) are connected as illustrated in the diagram and that the power supply is applied with correct polarity. The charging condensers must, of course, have good insulation resistance.

#### Applications

Apart from the novelty of the circuits of Figs. 1 and 2 from the theoretical point of view, the devices have certain functional applications. Probably the most obvious of these is that they can be used as very effective warning indicators. It will be realised that a continually changing flashing signal is much more liable to catch attention than is a steadily illuminated light. The circuit of Fig. 2 may also lend itself very well to decorating displays, wherein the impression of movement of a light source may be conveyed. Such an impression is heightened if the neon bulbs are mounted close together in a circle.

For more serious applications, both circuits are capable of offering control voltages, these appearing across the condensers associated with each neon. Also, sharp-fronted pulses appear across  $R_1$  in Fig. 1, and across  $R_1$  plus  $R_2$  in Fig. 2, these occurring when each neon strikes.

---

---

## Brussels Exhibition—Amateur Radio Station ON4UB

It would be quite impossible to even attempt to mention all of interest to the radio enthusiast to be seen at the great Brussels Exhibition. Such is the magnitude of this spectacular show that it would be quite impossible to see all that is on view.

On the radio side your reporter has singled out the things of particular interest to the radio constructor. It was, for instance, interesting to see some quite elaborate radio control equipment on a stand devoted to model aircraft, some of it being by our English firm of E.D. Electronics. The Dover-Ostend shipping line had some good working models of their ships, radio controlled and being expertly manoeuvred on a wide stretch of water. Just round the corner from the main Radio TV Building was to be found the Exhibition's Amateur Radio Station ON4UB, in charge, at the time of your

reporter's visit, of ON4IT and ON4IZ. The station is well displayed and is a real credit to those Belgian Amateurs who have organised it, and it has been visited by amateurs from all over the world. YV, W's, KH, LU are just a few of the DX prefixes to be seen in the visitor's book. The TX is a rebuilt 1131, using two 814's in the final, and feeding a long wire antenna on all bands. The receiver in use was an AR88, and we were soon working G2YJ in Croydon on 7 Mc/s. A Geloso TX and RX were also a prominent feature of the station, amongst numerous other items of interest.

Any other radio enthusiasts, be they Amateurs or not, will be given a real welcome, should they call in on ON4UB whilst visiting the Brussels Exhibition, a visit to which is very well worth the effort and expense incurred.

A.C.G.

# IN YOUR WORKSHOP



*This month Smithy the Serviceman, aided by his able assistant Dick, deals with an elusive h.t. short-circuit, and crosses figurative swords with our contributor G. A. French*

"I THINK," SAID DICK THOUGHTFULLY TO nobody in particular, "that I have a ground on my B-plus."

Smithy the Serviceman looked up and regarded his assistant gravely.

"I am strongly tempted," he said, heavily, "to remark that I hope it isn't catching. However, I know what you mean. Whence the correct American usage?"

Dick chuckled. It was always a little difficult to catch Smithy's attention during the first few hours of a Monday morning; the Serviceman always started his week with a feverish concentration which was probably caused by the fact that most weekends produced a large crop of sets, and Smithy hated having a wall\* behind him.

"Well, now I have your attention," laughed Smithy's assistant, "I shall proceed to translate. What I meant to say was that I have a short-circuit to chassis on the h.t. positive line in the t.v. set I'm working on. To which remark I will add that I'm hanged if I can trace where it's occurring."

## An Intermittent Short?

Smithy tut-tutted a little and wandered over to Dick's bench, where he noted that his assistant had taken the faulty television chassis out of its cabinet. Dick had not removed the speaker, this being connected to the chassis via a pair of flexible p.v.c. leads.

\* "Wall": a slang term used in manufacturing circles to define an excess of units for repair, or for a particular production operation.—EDITOR.

"This is a little surprising," commented Smithy at length, "I should have thought that an h.t. short was the easiest of all animals to track down. Anyway, let's hear what happened."

"Well," responded Dick, "when I first looked at the set I saw it was suffering with an acute attack of h.t. metal rectifier burn-up. The rectifier was easy to get at without removing the chassis from the cabinet, and so I swapped it straightaway. However, before connecting the chassis up to the mains I made a quick check with the meter to see if any obvious short-circuits to chassis had caused the original trouble." Smithy nodded approvingly. "On applying the testmeter prods I found that there was a short and that its resistance, as measured between the smoothed h.t. line and chassis, was of the order of twenty ohms or so. To my mind twenty ohms pointed to a component failure, such as would be given by the smoothing electrolytic."

"That's a reasonable enough diagnosis," observed Smithy, "and I must certainly add that you were very sensible in trying to evaluate the short circuit in terms of ohms, because this often gives a valuable clue to its nature and position. If you had had a really dead short-circuit with negligible resistance you could have assumed physical contact between chassis and, say, a tag connected to the h.t. positive line. Plus, of course, the possibility of breakdown in the h.t. electrolytic or any other component connected directly across the h.t. supply. Whilst it

would be silly to attempt to lay down hard and fast rules here, the existence of your twenty ohms does rather argue against such things as tags touching chassis, although it still allows suspicion to fall on broken-down electrolytics and the like. If your h.t. short had shown up as having a resistance of several thousand ohms, I would have suspected tracking across a tag-strip, or something of that nature. When the surface insulation of a tag-strip breaks down and a spark travels across that surface, the resultant carbon track often shows a resistance of several thousand ohms or so when checked with an ohmmeter. At the same time, when h.t. is applied to the tag-strip the effective resistance is very liable to drop and cause quite heavy currents to flow. I've seen carbon tracks on faulty tag-strips glowing red quite brightly on occasion."

"Wouldn't a resistance of several thousand ohms also indicate that there was a short to chassis on the other side of a decoupling resistor?" asked Dick. "Decoupling resistor values around two thousand ohms are very common in t.v. chassis, you know."

"I don't think so," replied Smithy, "mainly because such decoupling resistors usually have low wattage ratings, and they would burn out, themselves, long before the rectifier packed in. Anyway, we're getting off the subject of the particular receiver we have in mind. I presume you checked for a short on the rectifier side of the smoothing choke?" (See Fig. 1.)

"I next discovered that I would have to remove the chassis from the cabinet before I could reach its tags. This component was not so easy to get at as the rectifier. Consequently, and in pursuance of my duties, I duly proceeded to remove said cabinet, only to find, on re-checking, that the short had disappeared! Indeed, so well did it disappear that I even connected the set to the mains to try and get it back again. Instead, the set worked perfectly: I got a beautiful picture and excellent sound, with not a single puff of smoke to be seen anywhere. Nor was there the slightest suspicion of the delicate odour of cooking h.t. rectifier."

"Hmmm," commented Smithy. "It sounds as though this may be one of those awkward ones. I presume you checked that there was no risk of the chassis securing bolts touching any h.t. point when the chassis was boxed."


"That was one of the first things I did when I found that the short had cleared," declared Dick. "But no dice."

"A pity," remarked Smithy. "I don't like these indeterminate faults. Of course, the short *might* have been caused by a blob of solder or a bit of wire in the works, this becoming dislodged when you handled the receiver."

Smithy ceased conjecture and decided to examine the chassis. He carefully followed the red h.t. positive line on its route along the chassis, looking for traces of previous sparking.

"Well, everything seems to be above-

*Fig. 1. A short-circuit between h.t. positive and chassis could have occurred on either side of the smoothing choke, or in the choke itself. By taking quick resistance readings, such as those shown here, it is possible to locate the short-circuited section with a reasonably high degree of certainty*

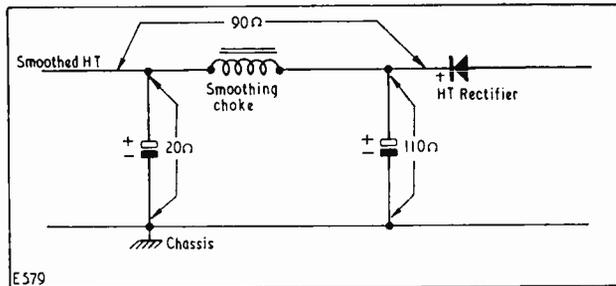

"I did, indeed," confirmed Dick, "and the resistance to chassis here was about 110 ohms. Also, the resistance of the choke winding is 90 ohms, so that almost certainly confirms that the short to chassis is on the smoothed h.t. line."

"O.K.," said Smithy. "What happened next?"

"Having decided that the smoothing condenser might be faulty," continued Dick,

board," he remarked eventually. "If an h.t. short in a t.v. set causes sparking it usually leaves quite noticeable traces, such as blackening of the chassis and so on. But there's nothing like that here."

Smithy leaned back and looked once more at the faulty chassis and its cabinet.

"Hey, wait a minute," he said. "I think you forgot something when you unboxed this chassis."

The Serviceman pulled out from inside the cabinet a flexible lead fitted with a solder tag.

"What about this?"

"Oh, that," said Dick, carelessly. "That's just the lead from the speaker frame to chassis. I didn't bother to re-connect it after I had taken out the chassis."

"That was a silly thing to do," commented Smyth.

"Why?" queried Dick, a little hotly.

"Just think," said Smyth.

Dick frowned.

"I'm sorry," he remarked at length, "but I just can't understand why disconnecting the speaker bonding lead should cause an h.t. short to disappear."

Smyth looked impatient.

"Well, I'm not going to argue about it," he said, somewhat stiffly, "firstly, because you may be right and, secondly, because I always hate arguments about the rightness or wrongness of technical points. So I'll just ask you to carry out the simple and practical act of connecting your ohmmeter between that speaker frame lead and the h.t. positive line of the chassis."

"As you like," said Dick.

He made the connection and looked at the scale of the instrument.

"Well, I'll be jiggered," he remarked, surprised. "My old friend, the twenty ohm leak, has returned!"

assumptions. Don't forget that, in this game, *nothing* is above suspicion."

### Tracing the Fault

Smyth drew Dick's attention to the wiring of the receiver. (Fig. 2.)

"Now, first of all," said Smyth, "we want to trace the route between the speaker bonding lead and the h.t. positive line. As you can see, the lead connects to the speaker frame at a solder tag which is held under a wood screw. Also connected to that tag is one of the two leads from the chassis to the speaker voice coil. We follow these leads back to the chassis whereupon we find ourselves at the speaker transformer. There is no sign of either of the leads to the voice coil having poor insulation, or showing signs of having touched any h.t. point, so it looks as though the transformer itself is at fault." Smyth picked up a soldering iron and disconnected the speaker leads from the transformer.

"As you can now see," he continued, "the secondary tags are connected to no external circuit at all. I next apply the ohmmeter, and what do we find?"

"Twenty ohms resistance between h.t. positive and the secondary," responded Dick dutifully.

"Exactly," remarked Smyth. "In other words a short between primary and secondary. And I should imagine that the twenty

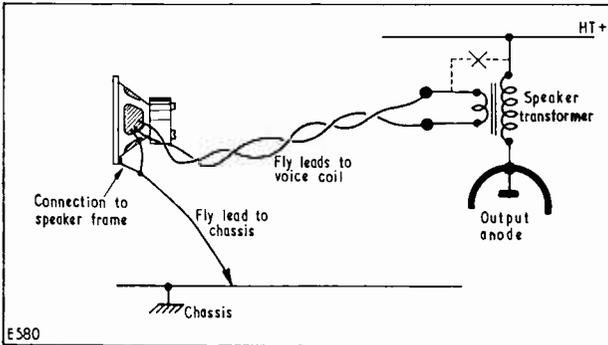


Fig. 2. According to production methods, the manner in which a loudspeaker frame is connected to chassis may vary from receiver to receiver. The slightly unusual method shown here assisted in drawing attention away from a faulty speaker transformer

"Which means?" prompted Smyth.

"Which means," continued Dick, thoughtfully, "that, if I were to re-connect this speaker frame lead to chassis, the h.t. short would re-appear. I'm sorry, Smyth, but you were quite right about that lead after all."

"To be quite frank," said Smyth, "it was more luck than anything. But it does make the point that, in servicing, it's much better to actually check every point, however remote some of them may be, than to rely on

ohms is appearing in the carbon which constitutes part of the short. It *could* happen that there is twenty ohms-worth of primary winding between h.t. positive and the actual short itself, but this is a little doubtful as the wire would probably have burnt out in quite a short time. Anyway, these points needn't worry us, as all we need to do is to fit a new transformer."

"One sound output tranny coming up," said Dick, who was already at the spares cupboard.

Smithy paused a moment to watch Dick fit the new transformer, and he pulled out his cigarettes. Before he could put one between his lips, however, his assistant had offered him one from a packet which was lying on a bench.

me that we're due for a rag-chew ourselves very soon. Over a cup of tea."

Smithy filled the battered Workshop kettle, placed it on its ring, and returned to his own work, leaving Dick to finish repairing the faulty t.v. set.

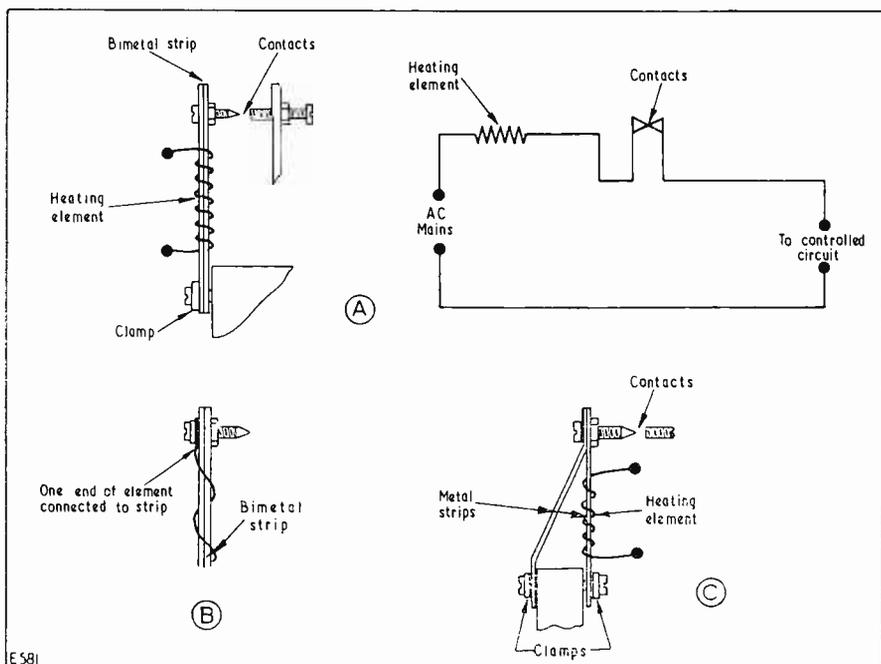


Fig. 3. A simple timing switch, which is described fully in the text. The switch is capable of continually switching on and off equipment running from a.c. mains

"Have one of mine," said Dick, "they're 6dB down!"

"6dB down?"

"That's right," replied Dick, "each cigarette has its own built-in attenuator."

Smithy examined the cigarette Dick had offered him, chuckling a little at Dick's description of its filter tip.

"Since when," he commented, lighting up, "have you been smoking snouts with spats on? And American snouts at that?"

"If by snouts and spats you mean cigarettes and filter tips," replied Dick, primly, "I've been smoking these American versions off and on since Saturday. We had a visit from an American who was billeted on us during the war. He's something of a Ham back in the States and so, apart from swapping cigarettes, we had quite a rag-chew together."

"Which explains the American terminology earlier on," said Smithy. "And that reminds

### Simple Devices

When, later, Smithy and his assistant sipped their tea, Dick became more and more ruminative.

"You know, Smithy," he said, at length, "my experience this morning makes me feel that most of the things we bump into in electronics are really very simple."

"I suppose that's true enough," commented Smithy, "although that h.t.-short snag wasn't as obvious as all that. The method employed for earthing that speaker frame was not entirely conventional, but it was by no means untypical of the way some commercial receivers are wired up."

"However, your talk of the simplicity of some aspects of electronics reminds me of something which appeared in *The Radio Constructor* for last March. I don't know if you can remember it, but in that issue G. A. French published a Suggested Circuit in

which a relay functioned as a periodic circuit timer in company with a condenser and a resistor. He stated, in his article, that "if it were possible to make a periodic relay switch any simpler he would be very interested to hear of it."\*

"Oh yes," Dick remarked, "I remember that circuit quite well. G. A. French certainly cut everything down to the bone."

"True enough," replied Smithy. "Yet at the same time, there is another type of simple periodic switching device which can be used for a.c. mains circuits and which, whilst not being truly a *relay* gadget, certainly runs neck and neck with G. A. French's from the simplicity point of view.

"This switching gadget† consists of a bimetal strip clamped at one end, and which is heated by means of a coil of asbestos-covered resistance-wire, such as is available from line cords and the like. (Fig. 3 (a).) Alternatively, the bimetal strip could be heated by ordinary resistance wire, this being insulated from the strip by asbestos tape; or, again, if the circuit to be switched carries a heavy current, the heating element could be ordinary copper wire.

"The heating element is connected in series with the device to be switched. When the current is first switched on, a circuit is made to the controlled equipment via the heating element, the bimetal strip and its contact. The bimetal strip then warms up, breaks its contact, and the equipment switches off again. When the strip becomes

cool the contacts make once more, and we start another cycle. Dead simple, isn't it?"

"It is indeed," remarked Dick, "but aren't you liable to lose a lot of volts in the element?"

"Not necessarily," replied Smithy. "At worst it should be some five volts for low current devices which take 200mA or so. You can, incidentally, shunt the element if you want to get a finer control of the voltage it drops and, in consequence, the length of each timing cycle."

"What about the insulation between the heating wire and the bimetal strip? Asbestos tape doesn't seem to me to be very effective in this direction."

"It doesn't need to be," replied Smithy. "One end of the element is permanently connected to the strip and the only voltage difference given is that between the other end of the element and the strip. You can, in fact, connect one end of the wire to the strip at the point where the latter does most wagging, thereby keeping the voltage difference lowest at the point where most physical movement occurs. (Fig. 3 (b).)

"A useful alternative to the bimetal strip consists of using two strips of the same material and of heating one of them. (Fig. 3 (c).) Small hacksaw blades would cope quite nicely here."

"Very neat," remarked Dick approvingly. "I especially like the hacksaw blade idea, because that uses parts which are easy to obtain. I shall have to think about knocking up one of these gadgets for Christmas."

"If you hurry," remarked Smithy, gently, "you'll get it done in time for Thanksgiving."

\* Suggested Circuits No. 88, *The Radio Constructor*, March 1958, page 542.

† This device is due to reader J. B. Leonard, of Oxford.

## NEW ANTENNAS FOR RADIO AMATEURS

Amateurs throughout the world soon will be able to buy Mosley Trapmaster rotary and vertical antennas for fixed and mobile stations everywhere.

Carl Mosley, president of Mosley Electronics, Inc., of St. Louis, Missouri, U.S.A., a leading American manufacturer of short-wave antennas and other electronic equipment, has announced that Mosley will begin operations in England soon.

"We are opening an English manufacturing plant," Mosley said, "in order to satisfy the great demand from all parts of the world for Mosley antennas."

O. J. Russell, G3BHJ, prominent English authority on electronics and nucleonics manufacturing and exporting, has been appointed manager of the Mosley plant in England, which will be located at 15 Reepham Road, Norwich, Norfolk, England. Russell has contributed many articles to leading American and English electronic publications.

## RADIO AMATEUR'S EXAMINATION

Grafton Radio Society announce that they have again made arrangements with the Islington L.C.C. Men's Evening Institutes for official courses in the RADIO AMATEUR'S EXAMINATION and MORSE (both for beginners) to be held this winter at the Montem School, Hornsey Road, Holloway, London, N.7. The classes will meet on Mondays, with a repeat lecture on Wednesdays, commencing 22nd September for the R.A.E., 7-9 p.m. (instructor S. H. Iles—G3BWQ), followed by the Morse 9-10 p.m. (instructors L. Barber and A. Ralph). The fee is 20s. for either course, or 22s. 6d. for the two, and application in the first instance should be made to the Hon. Secretary of the Grafton Radio Society, A. W. H. Wennell (G2CJN), 145 Uxendon Hill, Wembley Park, Middlesex, at once so that a place may be assured. In last May's City and Guilds examination 26 passes were obtained, making a grand total of 85 in the five years this course has been run.



# UNDERSTANDING TELEVISION

PART 9

By W. G. MORLEY

*The ninth in a series of articles which, starting from first principles, describes the theory and practice of television*

**W**ITHIN THE FIRST EIGHT ARTICLES IN THIS series we have considered the television system in very basic terms, starting with the system itself and the information it contains. We have also spent some time on a detailed discussion of the cathode ray tube, our treatment of this particular subject terminating in last month's issue of *The Radio Constructor*.

Logically, we should now turn to the circuits which cause the television signal to be applied to the cathode ray tube and which keep the receiver deflection circuits in synchronism with those at the transmitter. Unfortunately, it is difficult to discuss the video signal when it is in a form suitable for application to the cathode ray tube without a prior understanding of the processes to which it has previously been subjected. In consequence it now becomes necessary to deal with the r.f. and i.f. stages of the receiver, as these handle the television signal after it has been picked up by the aerial. In this month's issue, therefore, we shall commence right at the "front-end" of the television receiver, and shall introduce one of its more important parts—the tuner unit.

## Television Tuners

When, in this country, television receiver production commenced after the end of the

war, there was no necessity for sets to have complex tuning arrangements in the aerial input circuit. The very simple reason for this state of affairs was that there was, at that time, only one transmitter. This transmitter—sited at Alexandra Palace—broadcast on what is now described as Channel 1. In consequence, earlier televisions were designed to receive this transmitter only, no facility being provided for reception on any other channels. Indeed, many early post-war receivers were of the t.r.f. (tuned radio frequency) or "straight" variety, wherein all the tuned circuits before the video and sound detectors were aligned at signal frequencies. A second station, Sutton Coldfield, later commenced transmissions on what is now called Channel 4, but even this event did not materially affect commercial production; receivers, including a proportion of t.r.f. models, being still marketed for reception of a single channel only. Superhet receivers of this period were normally capable of adjustment from one channel to the other, but this usually necessitated the receiver being handled by a service engineer.


A little later, however, receivers began to appear which had some means of simple adjustment from Channels 1 to 5, and it was at this period that the television tuner unit began to take form as a sub-assembly in its

own right. Also, this was the period which marked the final demise of t.r.f. receiver production. Despite the fact that more transmitters later became available in Band 1, there was still, incidentally, no necessity for the viewer to change channels, as only one programme (that radiated by the B.B.C.) was available. As a result, controls for channel selection were rarely brought out to the front panel. Usually, the channel selector control was situated at the rear of the chassis and it was, in many cases, simple enough to be operated by most laymen.

As we already know, the tuners employed at this time were intended for reception of Channels 1 to 5 only, these lying within the Band 1 frequency range of 41 to 68 Mc/s. Without devoting too much space to them, it would now be instructive to examine the techniques employed in two of the more typical examples of these early Band 1-only tuners as, apart from their own interest, they are of assistance in leading up to the techniques currently employed in 13-channel tuners.

circuit form the device could be depicted as consisting of three tuned circuits having a "three-gang" adjustment of inductance. When the arrangement of Fig. 46 was employed in a television receiver the three coils were connected into the aerial input circuit, the r.f. circuit (that between the r.f. amplifier valve and the mixer valve), and the oscillator circuit. Especial care in design was needed to ensure that accurate tracking was given. ("Accurate tracking" defines the condition when the three coils are all tuned to the correct frequency at all points in the range of the tuner unit.)

Another, and mechanically simpler, method of obtaining channel selection in Band 1 was provided by "incremental inductance" tuner units. In these units selection was obtained with the aid of a rotary switch, this causing small values of inductance to be put into circuit for each switch position. A circuit diagram showing the basics of an incremental inductance tuner is given in Fig. 47. In this diagram we have three sets of variable inductances, these being connected, as with

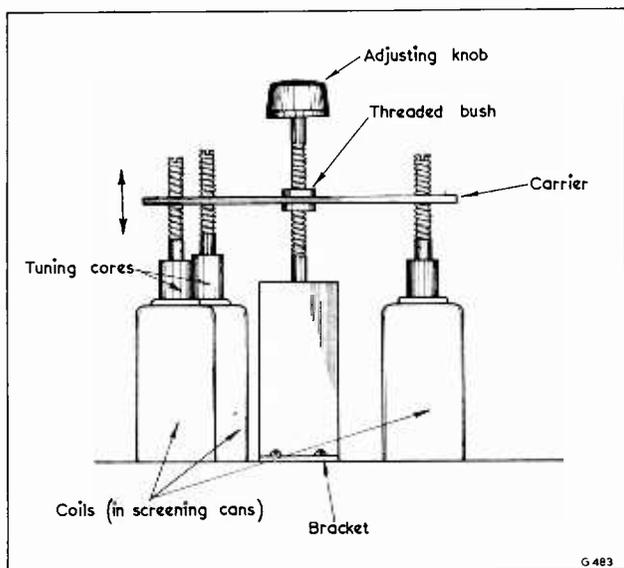

*Fig. 46. An example of a Band 1 tuner unit coil assembly. Rotating the knob causes the three cores to be inserted into, or withdrawn from, the coils. The positions of the three cores relative to the carrier are themselves adjustable (for purposes of initial setting up) with the aid of their threaded stems*

Fig. 46 illustrates a Band 1 tuner in which the inductances of three coils are varied by means of tuning cores fitted to a common carrier. A simple screw device enables the carrier to be raised or lowered, thereby causing the three tuning cores to be inserted into, or withdrawn from, the three coils. In

the device of Fig. 46, into the aerial, r.f. and oscillator circuits of the associated television receiver. When the switch of Fig. 47 is set to Channel 5, as it is in the diagram, the inductance put into each of the three circuits is that inserted by L<sub>1</sub>, L<sub>6</sub> and L<sub>11</sub>. These coils are provided with adjustable cores so

that their inductances may be raised or lowered, as desired. All the remaining inductances, those shown connected across the switch contacts, are short-circuited by the switch. When the switch is set to Channel 4, coil  $L_2$  is connected in series with  $L_1$ , coil  $L_7$  is connected in series with  $L_6$ , and coil  $L_{12}$  is connected in series with  $L_{11}$ . In consequence, the inductance presented to the associated receiver circuits increases, and the lower-frequency Channel 4 is selected. Setting the selector switch to positions 3, 2 and 1 inserts further inductance into the three circuits, thereby enabling these channels, whose frequencies become progressively lower, to be selected.

When the incremental inductance tuner unit is initially aligned, the coils  $L_1$ ,  $L_6$  and  $L_{11}$  are adjusted for correct inductance on Channel 5. These three coils should then present the required inductance for all the remaining channels, it being assumed that, provided they are wound with the correct number of turns, etc., the incremental inductances have so relatively low a value that the total inductance obtained is sufficiently accurate for correct tuning.<sup>1</sup> In practice the incremental inductance coils were very often self-supporting, being solder-

<sup>1</sup> In some cases small adjustments of incremental inductance might be achieved by opening or closing the turns of any particular coil.

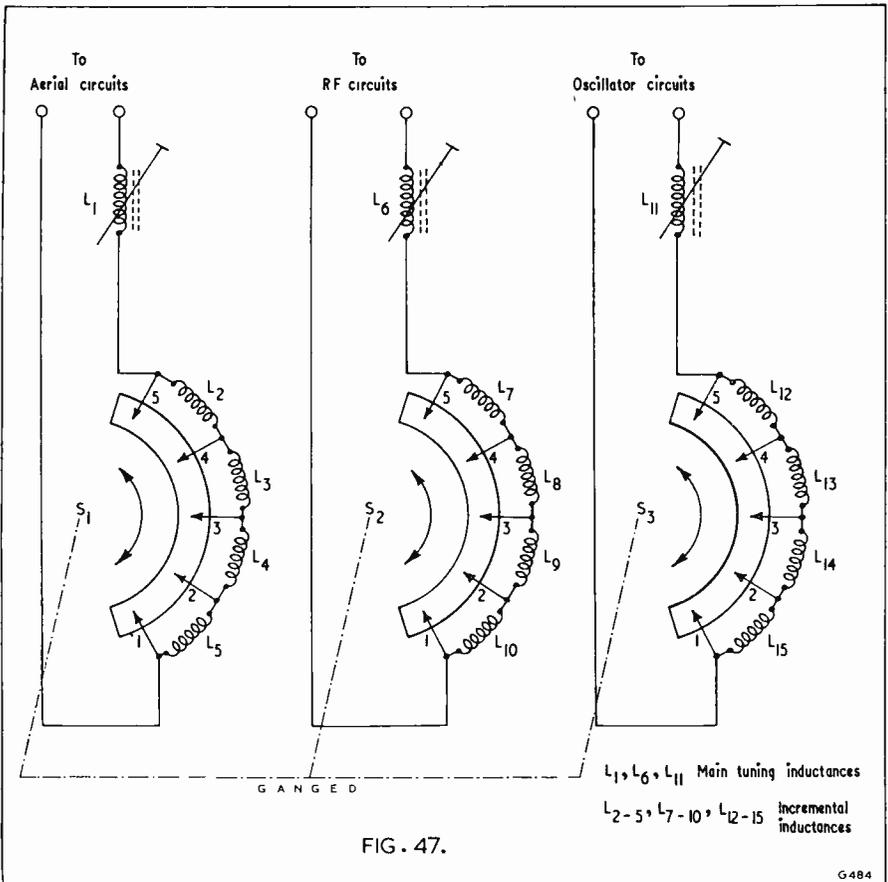


Fig. 47. The basics of an incremental inductance Band 1 tuner unit. The three switch "short-circuiting bars" are in the Channel 5 position. On switching to Channel 4,  $L_2$  is connected in series with  $L_1$ ,  $L_7$  with  $L_6$ , and  $L_{12}$  with  $L_{11}$ . If a coupling winding were required for any of the coil circuits, this could be fitted to the main inductance section

It should be noted that the incremental inductance type of tuner required some degree of oscillator fine frequency control, as it would be difficult to ensure that each discrete step in inductance provided by the switch would allow the oscillator to be set to the exact frequency required on all channels. A fine control of oscillator

amplified by the relatively highly selective intermediate frequency stages of the receiver. Whilst a small amount of de-tuning is permissible in the aerial and r.f. circuits, the oscillator must always function at the correct frequency.)

The tuner units of Figs. 46 and 47 are representative of early Band 1-only design and they are of especial interest here because they represent the first instance, in this country, of the tuning circuits of a television receiver being fitted in a separate sub-assembly. As sub-assemblies, these tuner units were similar in design to the more complex Band 1-Band 3 tuner units which followed later, insofar that the Band 1 units carried their own valves and circuitry, the connections to the main part of the receiver chassis consisting of h.t. and heater supplies, automatic gain control and contrast control wiring,<sup>2</sup> and the aerial and i.f. output circuits. The first i.f. coil of the receiver, that connected in the anode circuit of the mixer valve, might also be fitted in the tuner unit. It is worth mentioning that these tuner units were, in some cases, manufactured by specialist firms for general sale to set-makers.

### Band 3

When Band 3 transmissions commenced in Great Britain, the tuner unit situation altered considerably. There were two main reasons for this change. Firstly, equipment intended for operation at Band 3 frequencies requires special components, valves and design techniques if adequate amplification and stability are to be achieved. Secondly, since the domestic television receiver was now capable of presenting an alternative programme, the tuner unit fitted to the receiver had to become a simple foolproof device capable of customer control. This latter point carries with it the corollary that the tuner unit would be switched from one channel to another very frequently, with the result that such details as contact and mechanical wear had to receive much greater attention in the design stages.

If an attempt were made to classify the various types of Band 1-Band 3 tuners which have been employed in Great Britain since the inception of Band 3 transmissions, it could be said that these have consisted, in the main, of incremental inductance switching devices, of units wherein channel selection is achieved by ganged core insertion methods (similar to those shown in Fig. 46) and of turret tuner units. It is interesting to note that the incremental inductances fitted to switch type units frequently consisted of straight pieces of wire or flat metal tape between the Band 3 contacts. Fig. 48 shows

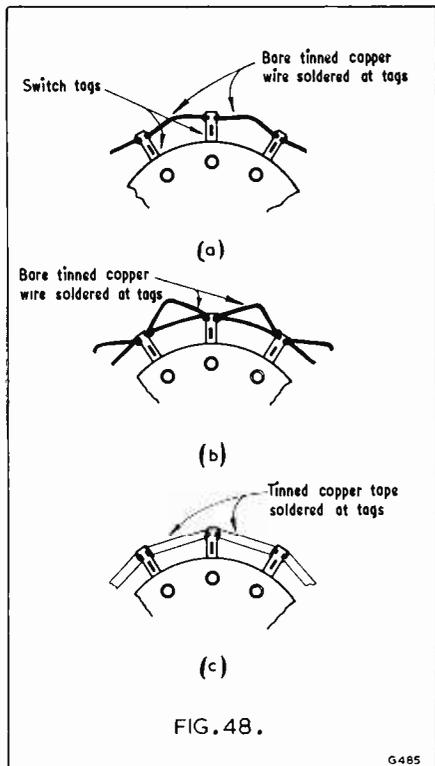


Fig. 48. When incremental inductance techniques are employed at Band 3 frequencies, very small values of incremental inductance are required when changing from one channel to the next. As examples, a single piece of tinned copper wire provides the inductance in (a), whilst two wires "in parallel" are employed in (b). Tinned copper tape is used in (c)

frequency would be provided by adjustment of the core of  $L_{11}$ . (The necessity of providing a fine frequency control for the oscillator is due to the fact that it is the oscillator frequency which, by beating with the incoming signal, causes the latter to be applied to and

<sup>2</sup> To be discussed in a later article.

three typical examples. The ganged core insertion units employed switching circuits which ensured that the large gap in inductance occurring between Band 1 and Band 3 was automatically allowed for when the selector passed from Channel 5 to Channel 6.

on the original design, almost universally employed. The reason for this fact is that the turret tuner offers, both electrically and mechanically, the best possible answer to the conflicting requirements of Band 1 and Band 3 reception, together with the feature

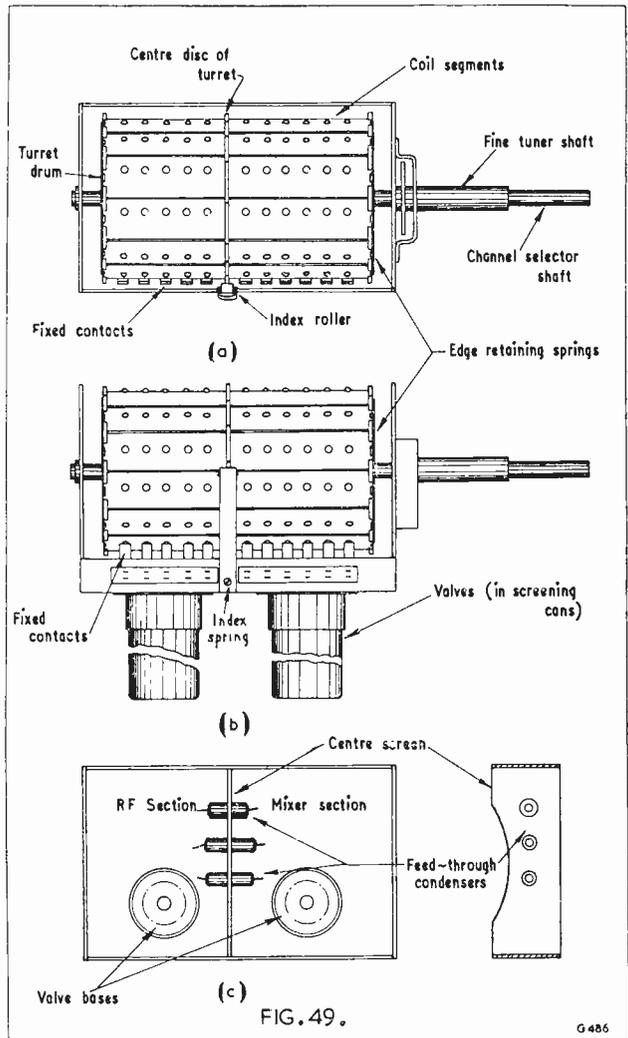


Fig. 49. (a) and (b) The basic construction of a typical turret tuner. (c) The internal screen of the tuner, visible when the drum is removed. The inset shows a side view, illustrating the curved edge which approaches the underside of the drum. The screen usually passes across the r.f. amplifier valve base, so that the anode tag may be isolated from the input circuit. Feedthrough condensers are frequently employed for coupling together supply circuits (h.t., heater, etc.) on either side of the screen

FIG. 49.

G 486

Of the three main types of television tuner, the turret unit has always been used most frequently. At the time being, indeed, it has practically ousted the other types of tuner unit, and it is now, with some slight variants

of considerable adaptability. Since, in most designs, turret tuner coils are capable of being individually fitted or removed, it becomes possible for a turret tuner to select channels in any order with no alteration in

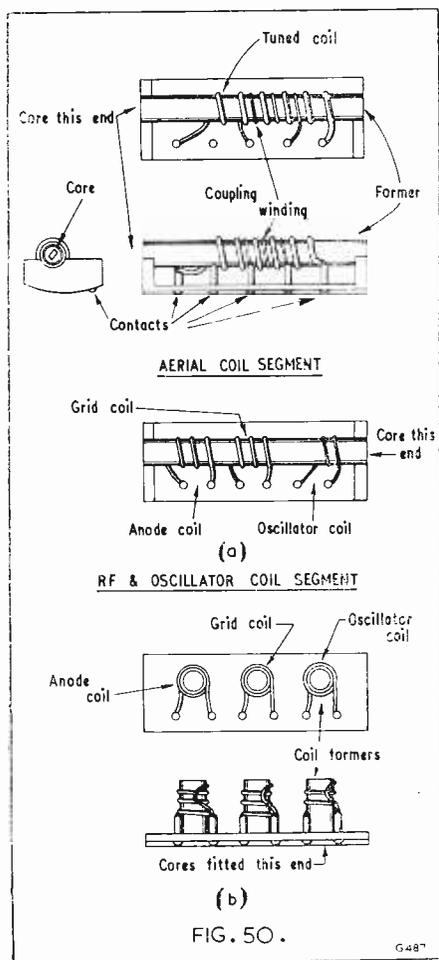


FIG. 50.

Fig. 50 (a). This diagram gives top, side and end views of a typical aerial coil segment, and a top view of an r.f. and oscillator coil segment. The aerial coil is tuned by an adjustable core, as is the oscillator coil of the lower assembly. The anode and grid coils of the latter are tuned by moving the turns of the coils along the former

Fig. 50 (b). It is possible for one or more of the coils on an r.f. and oscillator segment to be mounted radially (i.e. with their axes pointing inwards towards the actuating shaft when the segment is mounted in the turret), in the manner shown here. In such a case each radially mounted coil may be tuned by its own adjustable core

basic design at all. A typical example of turret tuner adaptability is the fact that these units may be fitted with coils suitable for reception of f.m. signals in Band 2 (v.h.f.) should this be desired, the basic layout remaining unchanged.

### The Turret Tuner

Since the turret tuner is by far the most important tuner unit currently employed, we shall now deal with it in greater detail. A typical turret tuner is illustrated in Fig. 49. In this diagram we see the turret "drum," this being the rotating section of the turret which contains the coil segments. The coil segments are held in position on the drum by means of edge springs, and they are readily capable of being fitted or removed. The coil segments connect into the tuner circuits via a row of fixed contacts mounted on the chassis. An internal screen is also fitted to the chassis in order to isolate the aerial circuits from the r.f. and mixer circuits and this screen, together with the centre disc of the drum assembly, provides almost complete shielding between the two sections. The shaft which rotates the tuner drum, and which thereby provides channel selection, is normally concentric with a second shaft which controls the "fine tuner." The centre disc of the turret drum usually has a serrated edge, this engaging with a roller on an indexing spring to ensure that positive location is provided at each channel setting.

A pair of typical turret coil segments is illustrated in Fig. 50 (a). One of these segments is an aerial coil, this consisting of an r.f. transformer which is tuned by an internal core. The core is usually brass or aluminium, but it might be iron-dust at Band 1 frequencies. An r.f. and oscillator segment is also shown in Fig. 50 (a). The oscillator coil is tuned by means of a brass or aluminium core (or, possibly, iron-dust core at Band 1 channels), the turret mechanical design being such that it is possible to adjust this core readily without the necessity for disassembly of the tuner unit.<sup>3</sup> In segments of the type shown in Fig. 50 (a) cores are not fitted to the two r.f. coils. This is due to the fact that access to a core in the right hand coil would be impeded by the oscillator core, and access to a core in the left hand coil would be impeded by the aerial core (when both aerial and r.f. coil segments were fitted on the drum). Because of the absence of cores, the r.f. coils are tuned by physically moving the turns on the formers. Since these coils function in a

<sup>3</sup> In many designs the oscillator cores are accessible through the front of the tuner chassis, allowing adjustment to be made, when the tuner is fitted to a receiver chassis, without removing the latter from its cabinet.

band-pass circuit the distance between them is of considerable importance, and this distance is also adjusted by moving the coil turns along the former.

Coil segments intended for r.f. and oscillator circuits may be designed differently from those shown in Fig. 50 (a). In some cases the coils may be mounted radially (so that their axes point towards the actuating shaft), whereupon cores can be fitted which are readily adjustable when the segment is fitted to the turret drum. See Fig. 50 (b). Coils mounted in this manner are then tuned with the aid of these cores and not, normally, by moving individual turns.

### Next Month

In next month's contribution we shall commence a study of the circuitry employed in Band 1-Band 3 tuners.

### BAND 1, 2 AND 3 CHANNEL FREQUENCIES (BRITISH)

Band	Channel	Vision	Sound
		Carrier (Mc/s)	Carrier (Mc/s)
1	1	45.0	41.5
1	2	51.75	48.25
1	3	56.75	53.25
1	4	61.75	58.25
1	5	66.75	63.25
2	F.M. Band	(87.5—100 Mc/s)	
3	6	179.75	176.25
3	7	184.75	181.25
3	8	189.75	186.25
3	9	194.75	191.25
3	10	199.75	196.25
3	11	204.75	201.25
3	12	209.75	206.25
3	13	214.75	211.25

# Can Anyone Help?

*Requests for information are inserted in this section free of charge, subject to space being available*

M. J. BALDWIN, "Eveden Cottage," Hook Green, Meopham, near Gravesend, Kent, wishes to obtain a copy of the April 1958 *Practical Wireless* containing information on converting the Mk. 19 No. 2 for amateur band use. Any expenses involved will be covered.

\* \* \*

P. WOOLARD, 10 Brookside, Glapthorn, Oundle, Peterborough, Northants, wishes to buy or borrow the circuit and/or servicing manual, or any data such as instructions, aerial and power supply details, etc., of the U.S.A. Collins TCS.12 type 52245 radio transmitter.

\* \* \*

W. LOWE, 28 Allenby Road, Cadishead, Manchester, wonders if any reader can supply him with data on the Kolster Brandes "Rejectostat" receiver type 510 or the K.B. battery personal receiver model F.P.11, serial O1956.

\* \* \*

J. JOHNSTONE, 118 Hertingsfordbury Road, Hertford, Herts, needs the circuit diagram or service sheet for the Haynes Tuner Unit type B.12 and Amplifier type B.9. All letters will be answered and all information paid for.

W. WINTER, 10 Siding Street, Bacup, Lancs, would like to buy or to borrow the service manual or any information on the R.1475 set, receiving unit type 88, and also the conversion data for the BC.348.N.

\* \* \*

G. C. BARROW, 45 Old Oscott Hill, Kingstanding, Birmingham 22C, wishes to borrow, hire or purchase the circuit, manual, or any relevant data on the U.S.A. communications receiver SCR.291A (Rx.1147).

\* \* \*

D. R. COAD, 14 Sandy Lane, Fair Oak, Eastleigh, Hants, wishes to obtain data on the following: BC-624-A receiver, BC-625-A transmitter, R.5019 receiver, T.5017 transmitter, Buzzer-oscillator pattern 2207, R.1132.A receiver, the type 71 receiver, and handbook (on loan or willing to purchase) and capacitance calibration charts for the Test Set TS.27/TSM.

\* \* \*

R. H. CLIFTON, 278 London Road, Staines, Middlesex, asks if anyone can supply the circuit connections, frequency coverage, and alignment details of the Denco type C.T.3 6-waveband, aerial, h.f. and oscillator coil-pack manufactured in 1946. The makers can no longer supply this data.

*(continued on page 125)*

# A PRE-TUNED SUPERHET RECEIVER

by S. E. KEELEY

MARY, A BACHELOR GIRL, IS SHORTLY moving into a flat of her own. "I'd be very grateful," she said to me the other day, "if you would build me a radio. I can't afford to spend much more than £7 or £8, so perhaps if you made me one that would get only the three B.B.C. programmes, nice to listen to, and fixed so that I can use my record player with it . . ."

I thought about it. Three stations . . . they could be pre-tuned and switched. Easy with a T.R.F. But that would bring a few snags in its train. Feeding a pick-up into a T.R.F. is always a bit messy, I think. And with no a.v.c., the stations always seem to be unbalanced in volume when you switch them.

A superhet? Yes, but a 465 kc/s superhet is not easy to pre-tune. The oscillator tuning is critical: you get the receiver on line, screw the chassis into the cabinet and switch on. Bump, bump, bump goes the bass notes . . . and in a few weeks' time the set needs re-aligning.

So it would have to be 1.6 Mc/s i.f. This would give a bandwidth allowing pleasant quality, no trouble in lining-up, stability once it was adjusted, ample selectivity to separate local signals, easily arranged gram input, and the a.v.c. would keep the volume of the stations balanced.

When I came to sketch out the circuit, I found that it was going to be both interesting and inexpensive. With 1.6 Mc/s i.f. the coil situation could be somewhat unorthodox.

For the Light Programme (200 kc/s) the local oscillator would have to operate on 1,800 kc/s; for the Third Programme (647 kc/s) the frequency would be 2,247 kc/s; and for the Midland Region (1,088 kc/s) 2,688 kc/s. For any other medium wave station, the oscillator would still lie within the 1.8–3.0 Mc/s range. This frequency range is covered by Wearite "P" coil PA6.

This meant that three coils, Wearite PA1 and PA2 on the mixer side and one oscillator coil—PA6, not PO6—would do the job.

Components List

<b>Condensers</b>		<b>Resistors</b>	
C1	0.01 $\mu$ F	R1	100k $\Omega$
C2	0.01 $\mu$ F	R2	22k $\Omega$
C3, 4, 5	See text	R3	15k $\Omega$
C6	0.1 $\mu$ F	R4	470 $\Omega$
C7	0.1 $\mu$ F	R5	47k $\Omega$
C8	100pF	R6	10k $\Omega$
C9, 10, 11	See text	R7	4.7k $\Omega$
C12	0.01 $\mu$ F	R8	100k $\Omega$
C13	0.01 $\mu$ F	R9	68k $\Omega$
C14	0.1 $\mu$ F	R10	330 $\Omega$
C15	0.1 $\mu$ F	R11	4.7k $\Omega$
C16	0.1 $\mu$ F	R12	47k $\Omega$
C17	0.01 $\mu$ F	R13	470k $\Omega$
C18	100pF	R14	500k $\Omega$ pot
C19	100pF	R15	2.2k $\Omega$
C20	0.1 $\mu$ F	R16	1M $\Omega$
C21	0.1 $\mu$ F	R17	1M $\Omega$
C22	25 $\mu$ F	R18	220k $\Omega$
C23	50pF	R19	220k $\Omega$
C24	0.1 $\mu$ F	R20	50k $\Omega$ pot
C25	50 $\mu$ F	R21	220 $\Omega$
C26	0.05 $\mu$ F		
C27	16 $\mu$ F	<b>Valves</b>	V1 EK32
C28	8 $\mu$ F	V2 EFC39	V3 EBC33
C29	0.1 $\mu$ F	V4 6V6	V5 Rect.

Miscellaneous

- L1, L2 PA2 (Osmor QA8)
- L3, L4 PA1 (Osmor QA9)
- L5, L6 PA6 (Osmor QA4)
- IFT<sub>1</sub>, IFT<sub>2</sub> 1.6 Mc/s I.F. trans. (see text)
- T<sub>1</sub> Main trans. 250–0–250V 6.3V and rectifier winding
- Sl, S<sub>2</sub>, S<sub>3</sub>, S<sub>4</sub>, S<sub>5</sub> 2 wafer Yaxley, each wafer 4-pole 3-way



I stripped a pair of 465 kc/s i.f. transformers down to 1.6 Mc/s. approximately. (The frequency is not really critical.) If you would like to know how I did this, the drill was as follows:

1. Unsolder the outside connection of one of the i.f. coils, strip off about six or eight feet of wire, cut it off and resolder the end of the coil wire back where it came from.

2. Connect one end of the i.f. coil to an aerial, and plug a lead from the other end of the i.f. coil into the aerial input socket of your domestic receiver. (The i.f. coil is now working like a wave trap or whistle filter—a rejector circuit offering great resistance to signals of a frequency equal to that of the resonant frequency of the i.f. coil/condenser tuned circuit.

3. Switch the set to the medium waves, and tune in the B.B.C. regional stations in turn, beginning with North Region. At each station, adjust the trimmer attached to the stripped i.f. coil, and see if you can “peak it” so that it blots out, or reduces, the volume of the station. Somewhere along the medium waveband, you will note this effect, and you will know what frequency you have stripped the coil to.

4. Carry on stripping and testing in the manner described until you can “peak out” the Third Programme on 1,546 kc/s. A few more turns off and you will have a 1.6 Mc/s

bobbin. If you have noted how much wire you stripped off one coil, you will know how much to take off the other three bobbins, and the job can be finished in minutes. (As a guide, I might mention that I had to strip 19 feet off each bobbin of a pair of Wearite 465 kc/s i.f. transformers to bring them down to 1.6 Mc/s.)

I used the TR1196 line-up for the valves—EK32, EF39, EBC33. A two-wafer Yaxley is used for switching the stations and the EBC33 grid circuit from radio output to gram. In the “gram” position, the coils are earthed.

For the mixer signal grid trimming condensers, I used the trimmers from defunct i.f. transformers. For the oscillator trimmers, 100pF for the Home Service, 200pF for the Third Programme and 250pF for the Light Programme served admirably. They can be bought in these values mounted in pairs on ceramic blocks which bolt neatly to the chassis.

The rest of the circuit is standard superhet practice and calls for no comment.

After a few hours with the soldering iron, the job was done. The results far exceeded my expectations—high sensitivity, most excellent quality, the three stations, correctly tuned in, at a flick of a switch. The cost—including the 10in speaker—was only £8 10s.

It's a pity it's so good, really—we can't bear to part with it!

---

## *Audio Has Big Place in*

# Britain's SILVER JUBILEE Radio Show

### Forecast of Features and Trends

The British radio industry, through the Radio Industry Council, is putting all its knows into the organisation and presentation of its annual National Radio and Television Exhibition to be held at Earls Court, London, from 27th August to 6th September, 1958, with a preview for overseas visitors and other special guests on 26th August.

It is the 25th National Radio Show and will be distinguished by very attractive designs in radio and television receivers and radiograms, making use of the latest transistor and printed circuit techniques, with some special emphasis on export models, as well as by lively demonstrations of all kinds, some technical and some for entertainment.

Audio equipment for high fidelity reproduction of sound, always included among

the exhibits, is being given a hall to itself this year, occupying a huge area on the first floor previously used by the B.B.C. for its exhibition studio, scenery dock, dressing-rooms and executive offices. Forty-five firms will have sound-proof rooms for demonstrating the equipment in the manufacture of which Great Britain excels, and which accounts for more than 20 per cent of British radio exports, the U.S.A. being the biggest buyer. The exhibits and demonstrations will include microphones, speakers, amplifiers, gramophone components, disc and tape recordings. The new stereophonic records will be demonstrated for the first time, and for the first time in an exhibition in Britain there will be a studio for stereophonic recording on tape.

# Radio



# Miscellany

**T**HIS COLUMN'S INTEREST IN STEREOPHONIC sound brings to light an anecdote told by W. E. Thompson (G3MQT). The name might not at first ring a bell as strongly as some of the others associated with *The Radio Constructor*, so perhaps it would be helpful if I reminded you that he does the Book Reviews.

At the time of the slump in the early 'thirties he was "axed" under an economy drive, from the technical development section of Standard Telephones and Cables, so he went to help out his mother who had recently acquired a business near Southend. The shop carried a fair stock of gramophone records and a few quite-good-for-their-period cabinet gramophones.

Surrounded by such a galaxy of material it wasn't long before Bill hit on the idea of playing two discs of the same recording simultaneously in an endeavour to obtain a stereophonic effect. His experiments along these lines were as a matter of personal interest rather than with any idea of exploiting it commercially. Naturally he had fun and games keeping the clockwork motors in step and getting the discs to start off exactly together. Even when he acquired the knack it required so much attention to operate, that little or no time was left for listening to the resultant distribution of sound. Improving on the idea, he swapped the mica-diaphragmed sound-boxes for electric pick-ups. Incidentally, the early pick-ups were often heavier than the sound-boxes they were intended to replace. Generally they were used in conjunction with the old-fashioned tone arm. Combined, they acted on the record surface rather like a miniature drill, penetrating deep in the grooves. The facetious types used to swear they threw their records away because after a few playings they alleged the loud passages from the other side would start breaking through! Nevertheless, record wear had to be sacrificed to the slightly wider frequency range and the possibility of having effective forms of tone and volume controls.

Bill, of course, being progressive, soon added pick-ups and separate amplifiers using

LS6A triodes plus mains-energised speakers mounted on 3ft square baffles. In the early 'thirties, anything less than nine square feet of baffle was distinctly non-U. To simplify synchronisation he mounted two turntables and pick-ups, one mounted above the other; the turntables were coupled by means of a key-way on the spindle to keep them in step, and one of the pick-ups was adjustable through a small arc. It was then only necessary to locate the records so that the run-in grooves came in roughly the same place. Adjustment of the upper pick-up arm forwards or backwards enabled perfect synchronisation or stereophonic reproduction to be obtained at a touch.

Bill used this scheme for a long time and it created a great deal of customer interest. When the discs were timed to be slightly out of step, the variation in the stereophonic effect was most marked—the source of sound appearing to shift from one speaker to the other, or it could be made to sound as if coming from the space between the two. This scheme was, of course, a complete basis of the latest innovation in stereo-gramophone reproduction except that Bill was using two discs instead of a dual recording on one—nearly thirty years before its commercialisation.

Perhaps the ironic part of this little story is that he wrote up a description of it and sent it to one of the radio magazines of the period. They did not even reply, let alone publish it! This was by no means a unique experience with certain periodicals of that era, due possibly to a form of prejudice by "professionals" disdaining the work of mere amateurs. Or, maybe, the idea of anybody wanting to wear out their records two at a time, even for the sake of stereo, was too much for some unimaginative editorial assistant.

By the way, Bill mentions two of the old type wax double-sided twelve-inchers which showed up on his coupled-turntable stereo to advantage. They were recordings of "Finlandia" (Tone Poem) and "Petite Suite de Concert" (two 12in discs). How about

these titles for our Aberdonian friend's quest for an ideal Test-cum-pleasure record? No one has mentioned them yet.

### Double Decker

While on the subject of "E.P. Test" records, a further letter covering several interesting points comes from our old friend J.G. of Rickmansworth who, it will be remembered, sent along a couple of useful suggestions. He starts off by asking if our Aberdonian reader found any of the titles put forward were to his satisfaction. Well, I haven't heard from Aberdeen since. Apparently he is a canny lad, and when he does finally settle on one to his liking I'll bet it will be a winner!

J.G. is once again able to be helpful in the matter of keeping garden workshops dry, and he expresses surprise that the mailbag was so light on a subject that must be something of a problem to many enthusiasts. His den is an underground brick-built air raid shelter with a concrete roof, situated half-way down the garden. It offers the obvious advantages that one can hammer and saw, making as much noise as one likes, without inconveniencing anyone. Before he got to work on it, the dampness and condensation made it uncomfortable to stay in and anything left in it was ruined within a few days. He overcame the problem by making alcoves in each of the end walls and installing burner paraffin lamps (cottage lighting type) in each, with a vent slightly to the side and about 18in above the lamps. Three-inch metal tubing runs from above the lamps to the vents. It is now beautifully dry and cosy. The floor was concreted and the ceiling and walls were lined with roofing felt and distempered, and light and power laid on. It is fitted with a lathe, workbench and a couple of old chests of drawers strengthened and adapted for storage. It sounds a most attractive proposition, and will no doubt put ideas into other readers' heads. He finds that it seldom needs extra heat, and an extractor fan is being fitted for summer use.

serve as camouflage if used for its original purpose—an air raid shelter—but they become rather an eyesore when you have to live with them. Hence he plans to make it a two-storey affair, and the upper part is to become a smartly painted greenhouse—with automatic ventilation! Thus he has applied his lively mind to the problem and has been good enough to send along details of the scheme he has devised.

The idea, although perhaps a little complicated, is very sound, but rather dependent on one or two important factors, namely, a sizeable collection of odds and ends including a synchronous clock, a suitable motor and gearing, plus a well equipped workshop and a natural aptitude for improvisation.

I am afraid my gardener friend lacks these, although quite a number of readers might well meet the requirements. In fact, Joe, your letter really scared him and I suspect he is still wondering if he wasn't born a couple of centuries too late. At least, he became quite eloquent about the good old days when life was far less complicated and grape-growers had plenty of time to stroll round in a leisurely manner screening their vines from variable winds by the simple expedient of opening and shutting the windows by hand.

J.A.C. (Polegate) is also helpful in throwing a little more light on the question of automatic ventilation, in which I gather he has a professional interest. In Britain, apparently, large scale grape growers have changed over to less exacting crops, being unable to find nimble-footed youngsters to scamper round opening and closing windows whenever the wind refuses to settle in one direction. In the U.S.A. a system using compressed air as its operating power is extensively used. The "sensing" is done by a valve controlled by a weathervane, and apparently it is an uncanny experience the first time one sees all the vents on one side of the house close down to the accompaniment of hissing air while those on the other side open whenever the wind changes direction.

## **Centre Tap** talks about items of general interest

Now Joe is a tidy sort of bloke—after my own heart—and having such an efficient and comfortable interior to his den he feels more than a little uneasy about the appearance of the outside, especially as it is right in the middle of the garden. At present it is a jungle of mint and other profuse growing vegetation with a few potted tomatoes, etc., thrown in for luck. Such things may well

### Brotherhood

In recent weeks threats of war, racial hatreds and political tyranny have dominated the news. It is thus doubly nice to feel that despite the evil-doing of violent minorities the world is still largely populated by peaceful and kindly people. Perhaps it is through one's hobbies that one can most easily get to know and understand the other fellow better,

and radio serves us well in this respect. Following my recent illness I was deeply touched by friendly letters from readers, many of whom said I was not to trouble to reply. If only statesmen had more time for hobbies, what a friendly place the world would become.

The mention of readers' letters reminds me that once again I am in a sorry mess with postal replies, but I would most earnestly assure the writers that their letters were greatly appreciated. The Old Timers' Brigade were well to the fore. Is it that they are mostly retired and have more time to spare, or do radiomen become more sentimental with advancing years?

Once or twice suggestions have been made that an Old Timers' Club should be formed, and I have recently begun to wonder if they ought not to have a distinguishing mark. Possibly the chap sitting opposite to you in the train is an Old Timer too, and neither of you realises that you have so much in common. What a wasted opportunity when no doubt you would both have enjoyed swapping yarns, news and views.

### Altruism

Each month I receive a copy of *Radial*—the monthly magazine produced by invalid hobbyists for other invalid hobbyists. Its cheerful chattiness gives me much pleasure, and I am sure it comes as a wonderful antidote against the depression and boredom of enforced idleness. As a contrast to the gloom of international suspicion, it is cheering to learn that *Radial* is now being printed for them by Denco (Clacton) Ltd. A very nice gesture. Even in a Welfare State, bedfast amateurs haven't much money to spare for hobbies and it is heartening to know that the directors of a firm have an interest in the hobby itself not simply confined to the business side. I often wonder how many of the helpers I see mentioned in *Radial* are Old Timers.

As for the Old Timers' letters, most of them seem to be busy building up sets such as they used in the early 'twenties, using genuine period parts. There must be something very fascinating in this "vintage" business. Indeed, I see one American firm is actually making "genuine brand new vintage" cars! Apparently there aren't enough old crows to go round. I wonder if the idea will spread to radio receivers.

### More of Yore

I am afraid we have but little space left for the rest of the Old Timer news which seems to have become almost a regular feature nowadays, so I must try to deal with their letters collectively. This month several have touched on an aspect previously overlooked

—the early craze for miniature receivers. This, of course, is one of the delights denied the modern enthusiast. What with transistors and miniaturised components, tiny sets are comparatively easy to design nowadays and unless one manages to compress it to the size of a wrist-watch no-one is very greatly impressed. In the old days, to design a working set of really diminutive dimensions demanded considerable ingenuity on the part of the constructor. The first real midget I saw was fitted into a teacup, over which many hours of patient and loving care had been spent. Then came the matchbox receivers. This size somehow grew to be the accepted standard. All real enthusiasts used actual matchboxes. They were not content to simply keep it to matchbox size.

H.R.N. (Northwick Park Road, Harrow) has a really early claim and still has his Bornite-Zincite combination using the outer and inner parts of the box to form the variometer for tuning, with the rest packed away in the inner slide.

The other predominant subject this month was (a) the more favourable position of Old Timers in regard to component prices, and (b) their less favourable position in the same respect. At first this seems flatly contradictory, but I suppose a lot depends on just what period is under review.


Is the newcomer really proportionally better off in this respect or not?

Personally, I should say that in the early days one could do quite a lot for a small expenditure. Then came the 1922-1930 period. One simply had to buy valves, etc., and they were mighty dear. This period in my opinion made by far the heaviest demands on the constructors' pocket, yet strangely enough home-construction proceeded on an enormous scale. Practically every household had a set built by one of the members, a friend or a neighbour. Sets were straightforward to make and were supplied in kit form so simplified that anyone who could read and use a pair of pliers became a "constructor." They were expensive (judged by comparative modern costs) but the real enthusiast could make most of his own parts cheaply.

In the 'thirties, mass production of domestic receivers began to get into its stride and vast quantities of manufacturers' "surplus" found its way on to the market. This was often sold at knock-down prices. It was too much for the handyman type to design his own set and hence, with a diminishing number of buyers for a swelling quantity of manufacturers-type over-produced components, prices fell sharply and enthusiasts bought shrewdly. These were happy days for the amateur with a lean purse.

*continued on page 118*

# A MULTI-RANGE

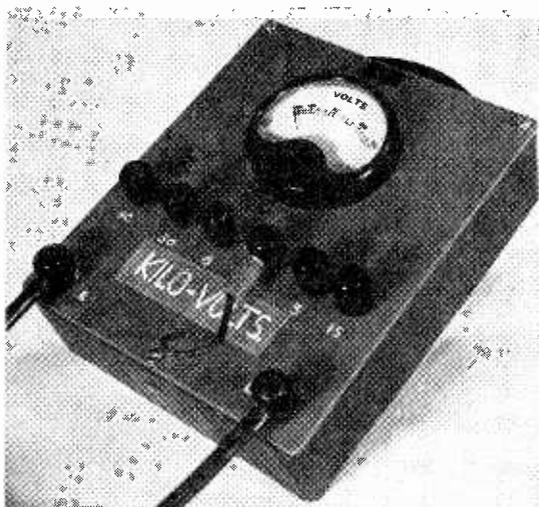

# ELECTROSTATIC VOLTMETER

By **B. K. POULSON** and **J. D. WARD, G3HDW**

**A** USEFUL AND INEXPENSIVE VOLTMETER can be made by utilising one of the electrostatic voltmeters which are now being sold for a moderate sum.

An electrostatic meter has the advantage of requiring almost zero current for its operation, unlike a conventional moving coil meter. Ordinary multi-range testmeters are not usually suitable for measuring high source impedance e.h.t. supplies, since the current taken by the meter loads the supply and reduces the voltage, thus giving an inaccurate reading.

The electrostatic meter overcomes this problem, and also has the advantage of measuring d.c. and a.c. without the use of a rectifier. The instrument is particularly suited to the measurement of e.h.t. supplies in t.v. receivers.

## Description

The instrument to be described has an input resistance of  $100M\Omega$  but if necessary this can be increased by modifying the value of resistors as described later. The basic movement consists of an 0-1.5kV meter and range selection is carried out by means of a wander plug which can be plugged into any one of six sockets; a switch was not used, due to the difficulty of obtaining one which would withstand the high voltages encountered. The ranges available are as follows:—


- 0-1.5kV
- 0-3.0kV
- 0-7.5kV
- 0-15kV
- 0-30kV
- 0-60kV

### Construction

The instrument can be built into any convenient size case, but the writers found that a neat and compact instrument could be built by using a case made of wood  $5\frac{1}{2}$ in x 7in x 2in x  $\frac{3}{8}$ in thick and a front panel made of  $\frac{1}{4}$ in paxolin.

ratings are applicable to resistors; the maximum voltage rating must not be exceeded. If in doubt, the manufacturer's data should be consulted.

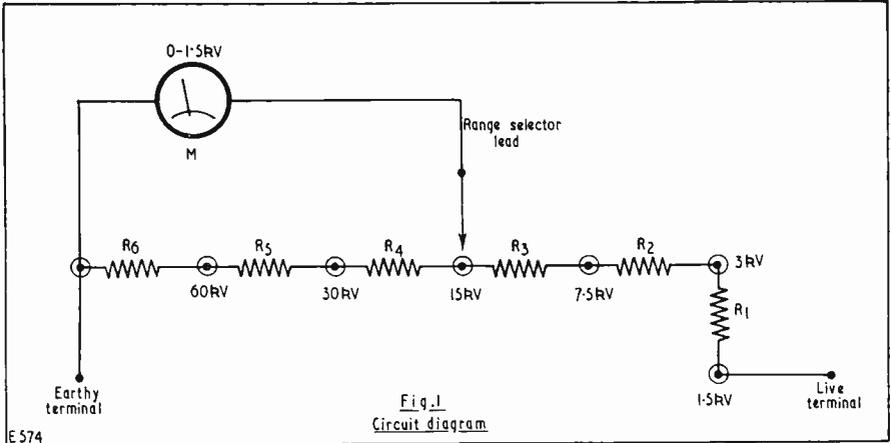Providing the precautions mentioned are observed, the wiring of the instrument should present no difficulty.



### Components

$R_1$  50M $\Omega$   
 $R_2$  30M $\Omega$   
 $R_3$  10M $\Omega$   
 $R_4$  5M $\Omega$   
 $R_5$  2.5M $\Omega$   
 $R_6$  2.5M $\Omega$

Made from a number of smaller value resistors connected in series if high voltage ones are not available.\*

M 0-1.5kV Electrostatic Meter  
 Eight Insulated Terminals  
 One Wander Plug

\* The voltage drop across each resistor must not exceed its voltage rating. This can be calculated by simple Ohms Law.


The panel should be drilled to accommodate the meter, six range selector terminals, range selector lead, test lead terminals and case fixing screws. A few holes must also be drilled to enable the resistor supports to be fixed to the reverse side of the panel.

Due to the very high voltages encountered special consideration must be given to the insulation of components. Resistors should be supported away from the front panel by the use of good quality ceramic insulators; components and wiring should be well spaced; and the insulation of leads, particularly the test leads, must be good enough to withstand the maximum voltage to be encountered. No sharp points should be allowed on soldered joints; this is to prevent corona discharges.

If high voltage type resistors are not available, the value required can be made up by connecting resistors in series. It is not generally realised that maximum voltage
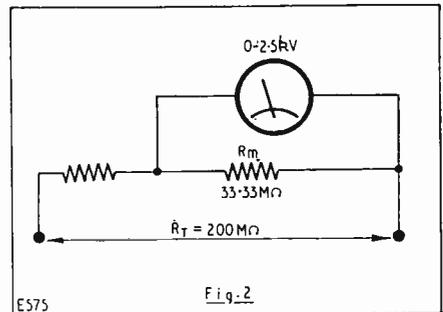
### Alternative Circuit Values

If the reader wishes to use a different meter, increase the input resistance, or use




different range multiples the component values can easily be calculated from the

following formula:  $R_m = \frac{R_T}{V_m}$ . Where  $R_m$  is the value of resistance that the meter is tapped across,  $R_T$  is the total value of resistance in the series resistor chain, and  $V_m$  is equal to the voltage range required divided by the f.s.d. voltage of the meter.
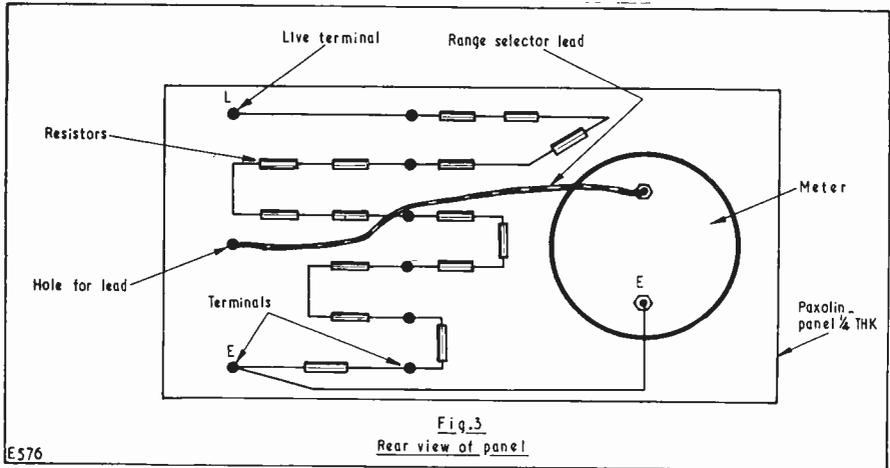
### Warning

The instrument and connecting leads must never be handled whilst connected to a supply. The range selector should be set to the appropriate range before use and should not be altered while measurements are being made. The earth terminal of the meter should be



E576

Example:  $R_T = 200M\Omega$ ; the meter reads 2.5 kV. f.s.d.; the voltage range required = 0-15kV; therefore,  $V_m = \frac{15}{2.5} = 6$ . Thus, the value of the resistance required for this range =  $\frac{200M\Omega}{6} = 33.33M\Omega$ . See Fig. 2.

connected to the earthed side of the supply irrespective of its polarity.

Providing the precautions mentioned are strictly observed, the reader will have at his disposal a safe, reliable, and inexpensive instrument which will give many years of useful service.

## Radio Miscellany

continued from page 115

The immediate post-war years saw tons of ex-W.D. stuff at junk prices, and knowledgeable amateurs had the time of their lives. Beginners weren't always so lucky. They often bought useful looking stuff only to find that it was of a highly specialised nature quite unsuited to their requirements. Still, it was a period in which you got a lot for your money, and generally speaking money was plentiful.

In more recent years prices have hardened again, but there are still plenty of bargains to be had—if you study the advertisement pages carefully. Modern conditions demand a much more complicated type of set and

many new components and the later type valves and transistors are expensive, and I should say the latest newcomers aren't having quite such a good time of it as some groups of the older hands did when they built up the basis of their stock.

In radio, as with most other hobbies, if you want the latest and best of everything you can soon run through a three-figure bank balance. But you can still get lots of fun for the outlay of only a few shillings, and generally speaking I suppose this was true whatever period you entered the brotherhood of radio hobbyists.

# The Teletron

# “TRANSIDYNE”

## 6 Transistor Pocket Portable Superhet Receiver

— described by EDWIN MARSHALL —

### PART I

IT IS A SOBERING REFLECTION THAT FOR many long years radio enthusiasts struggled—both with components and designs—to produce a really small pocket receiver of reasonable efficiency. To the best of the writer’s knowledge, none of us ever really succeeded with such a project. The comparatively large size of pre-war components effectively ruled out any hope of attaining a small and compact size and while portable designs did, of course, exist, the batteries were generally large and bulky. Various ingenious methods were tried and mooted, among them being unorthodox chassis shapes designed to pack the proverbial quart into the pint pot, frame wound aerials, batteries of smaller physical size but having less working life and even headphone reception! The portable of those days was, generally speaking, of a similar size to the small suitcase. Although the pocket portable superhet eluded the home designer and constructor, many hobbyists did succeed in producing a reasonably small “straight” receiver using the then new 1.5V valves.

With the advent of the transistor, a comparatively recent component to the home constructor, new and vast horizons began to appear, opening up new ways of thought, a fresh outlook of design and setting many of

us blazing new trails with this latest acquisition. In support of this, several of the firms specialising in the supply of components to the home constructor, and the industry, developed and designed the necessary miniature components consistent with transistor usage. These small items, coupled with the introduction of ferrite rod aerials, laid wide open the road to the small pocket superhet so sought after by most of us in the past.

The design about to be described—the “Transidyne”—is a six-transistor pocket portable superhet receiver having a class “B” push-pull output stage. It is tunable over the entire Medium waveband and has semi-variable tuning for reception of the 1500 metres Light programme. In addition to all the advantages imparted by the inclusion of small and compact components, the whole assembly is built up around a printed circuit board. This latest method of assembly has, in the opinion of the writer, great advantages for the home constructor as against the more normal method of wiring in a receiver of such small dimensions. Perhaps the greatest of these advantages is that the greater portion of the wiring is already in existence in impeccable and faultless form as received by the purchaser. In turn, this obviates several bugbears common to the more orthodox

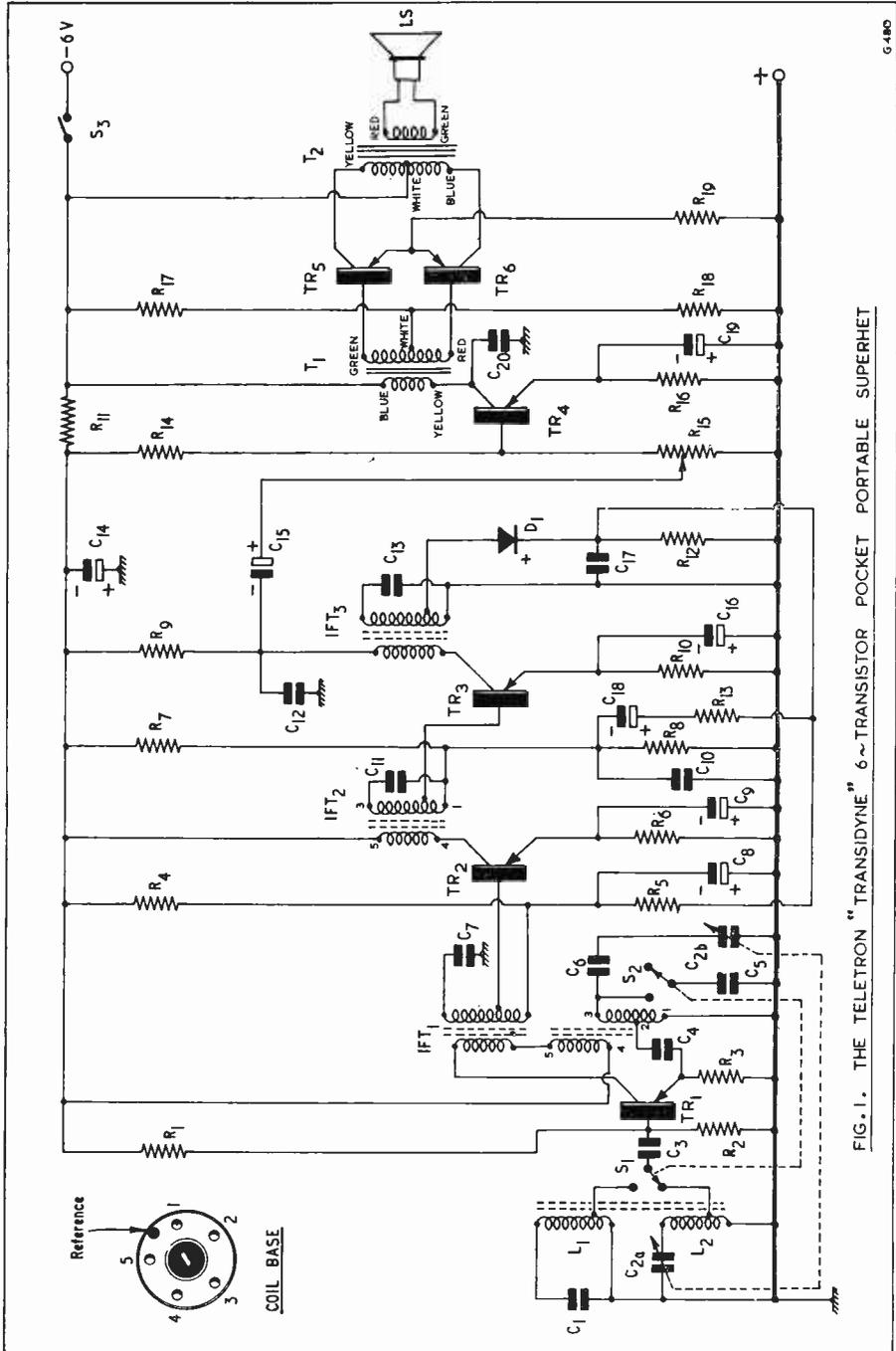


FIG. 1. THE TELETRON "TRANSIDYNE" 6-TRANSISTOR POCKET PORTABLE SUPERHET

G 480

presentation in that wiring errors are, as far as possible, eliminated; bad joints, at this stage, non-existent; a bad component layout impossible and long unsightly wires, together with all the associated troubles thereof, entirely absent. In addition to these very obvious advantages, a great saving of time and trouble is imparted to the constructor, it being merely necessary to solder into the printed circuit—hereafter termed the chassis—the required components as specified within the instructions.

### Circuit

The circuit of the Transidyne is reproduced in Fig. 1, and a study of this is well worth while before commencing the actual constructional details of the receiver. As previously stated, the receiver is tunable over the entire Medium wave range, this being effected in the input stage by C<sub>2a</sub> in parallel with the winding L<sub>2</sub>. Semi-variable tuning is used on the Light programme channel, the fixed condenser C<sub>1</sub> across the winding L<sub>1</sub> being the r.f. tuning components. Some variation is obtained on this band by switch-

ing into circuit C<sub>5</sub> across the oscillator winding. Rotation of C<sub>2b</sub> slightly varies the oscillator tuning, to enable "dead-on" tuning to be achieved.

The ferrite rod aerial used is the Teletron type FML22. Both the windings L<sub>1</sub> and L<sub>2</sub> are so fitted to the ferrite rod material that they may be moved along it, thus enabling some variation of tuning inductance to be achieved. The switches S<sub>1</sub> and S<sub>2</sub> are ganged and are, in fact, the wavechange control.


The transistor TR<sub>1</sub> functions as the frequency changer. L<sub>3</sub> primary functions as the feedback winding, while the secondary winding operates as the oscillator tuned coil. On the Medium waveband, this secondary is tuned by the gang half-section C<sub>2b</sub> in series with the padding condenser C<sub>6</sub>. The Light programme is pre-tuned by the fixed component C<sub>5</sub> and varied slightly by the C<sub>6</sub>-C<sub>2b</sub> combination. The padding component C<sub>6</sub> assists in ensuring that good tracking is achieved over the frequency coverage.

The collector of TR<sub>1</sub> feeds the selected signal via the 1st i.f.t. primary winding into the i.f. stages, these operating at a frequency

### Component List

Set out for easy reference to Fig. 1

<b>Resistors</b>	R1	47kΩ	±10%		
	R2	3.3kΩ	±10%		
	R3	1kΩ	±10%		
	R4	47kΩ	±10%		
	R5	4.7kΩ	±10%		
	R6	1kΩ	±10%		
	R7	4.7kΩ	±10%		
	R8	4.7kΩ	±10%		
	R9	560Ω	±10%		
	R10	1kΩ	±10%		
	R11	220Ω	±10%		
	R12	4.7kΩ	±10%		
	R13	8.2kΩ	±10%		
	R14	22kΩ	±10%		
	R15	5kΩ	pot w/switch (S3)		
	R16	220Ω	±10%		
	R17	3.3kΩ	±5%		
	R18	120Ω	±5%		
	R19	10Ω	±10%		
<b>Transistors</b>	TR1	Red/Yellow spot			
	TR2	Red/Yellow spot			
	TR3	Red/Yellow spot			
	TR4	Green/Yellow spot			
	TR5	Green/Yellow spot			
	TR6	Green/Yellow spot or equivalents			
	D1	GEX34 or equivalent			
<b>Inductances</b>	L1	Teletron type FML22			
	L2	Teletron type FT04			
	L3	Teletron type FT4E			
	IFT1	Teletron type FT4E			
	IFT2	Teletron type FT4E			
	IFT3	Teletron type FT4D			
<b>Condensers</b>	C1	100pF	±10%		
	C2a/b	Variable "OO"		2-gang, Jackson type	
	C3	0.01μF		Hunts type W99, 150V wkg	
	C4	0.01μF		Hunts type W99, 150V wkg	
	C5	200pF	±5%		
	C6	300pF	±5%		
	*C7	500pF	±5%		
	C8	25μF		electrolytic	
	C9	4μF		electrolytic	
	C10	0.01μF		Hunts type W99, 150V wkg	
	*C11	500pF	±5%		
	C12	0.01μF		Hunts type W99, 150V wkg	
	*C13	500pF	±5%		
	C14	25μF		electrolytic	
	C15	4μF		electrolytic	
	C16	25μF		electrolytic	
	C17	0.05μF		Hunts type W99, 150V wkg	
	C18	4μF		electrolytic	
	C19	25μF		electrolytic	
	C20	0.01μF		Hunts type W99, 150V wkg.	
				(* Supplied with i.f. transformers)	
<b>Transformers</b>	T1	Ardente type D131			
	T2	Ardente type D132			
<b>Miscellaneous</b>	Speaker	Celestion C25			
	S1/S2	Wavechange switch			
		Printed Circuit Panel (Teletron)			
		Cabinet (Teletron)			
		Dial (Teletron)			
		2 No. 8 batteries			
		Ferrite Rod mounting bracket (Teletron)			

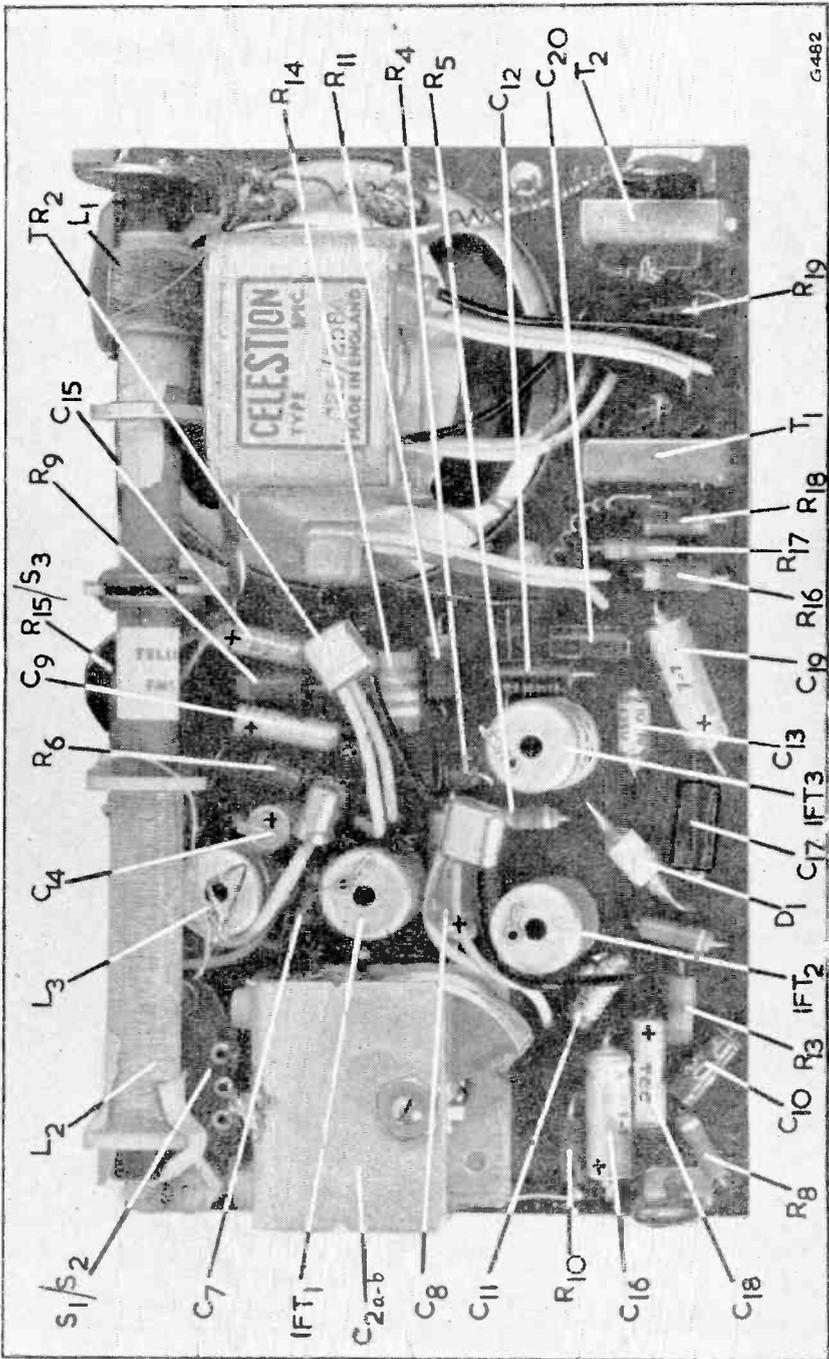

G482

Photograph of underside of prototype—compare with Fig. 2

of 470 kc/s. I.F. amplification is provided by both TR<sub>2</sub> and TR<sub>3</sub>, each operating in the earthed emitter mode. It will be noted here that each of the three i.f. transformers consists of an aperiodic winding coupled inductively to a tapped, tuned secondary, these having been so designed as to produce optimum performance at the low impedances occurring with transistor applications. The second i.f. stage is reflexed in order to provide some measure of additional audio gain.

The secondary of IFT<sub>3</sub> feeds into the diode detector circuit, the diode rectifying the applied signal and also providing an a.g.c. voltage. This voltage, together with the impressed a.f. signal is fed back into the respective bases of TR<sub>2</sub> and TR<sub>3</sub> via the i.f. secondary windings and associated decoupling components. The reflexed audio component is passed by C<sub>18</sub> into TR<sub>3</sub>, but prevented from reaching TR<sub>2</sub> by C<sub>8</sub>.

The amplified a.f. output is taken, via C<sub>15</sub> to the "first" a.f. amplifier TR<sub>4</sub>, being controlled by the potentiometer R<sub>15</sub>.

The amplified signal from TR<sub>4</sub> is then applied via the phase inverting transformer T<sub>1</sub> to the two class B output transistors TR<sub>5</sub> and TR<sub>6</sub>, these in turn driving the loudspeaker via the output transformer T<sub>2</sub>.

It will be gathered, from the details already given, that the Transidyne circuit is capable of providing a high degree of both i.f. and a.f. amplification, the degree of additional gain provided by the reflex arrangement allowing adequate audio reproduction with that reserve required for a satisfactory volume level when receiving distant Continental stations on the Medium waveband.

The power requirements of the Transidyne are very modest indeed, a six volt supply being required, which is provided by two 3-volt batteries series connected.

This completes the discussion of the actual circuit and it now remains to describe the assembly of the component parts, wiring of the receiver, and alignment procedure.

### Assembling and Wiring the Transidyne

The following operations should be carried out in the order and manner described. The order of both assembly and wiring has been very carefully planned so that even the not-so-far-advanced hobbyist may confidently undertake the construction of this receiver.

Firstly, fit the i.f.t.'s and the oscillator coil. When mounting these, note particularly that the reference mark on the base is intended to show the correct orientation of each component. A pencil mark, made on the side of the metal can, will greatly assist in this operation. The tags on the top of the cans must be earthed to the nearest point marked

"E" (Fig. 2). The use of 15A fuse wire is ideal for this purpose, and it may also be used in other positions when insulated with Imm. sleeving. The use of heavy gauge wire should be avoided as it may damage, by strain, the small components. The reason for fitting these components before any others is that some difficulty may be experienced in view of the fact that the short i.f.t. pin connections have to be first fed through the chassis holes and then soldered into position. Were other components to be mounted into position first, it would make the fitting and soldering of the necessary i.f.t. connections somewhat awkward and difficult to see.

The next items to be assembled are the loudspeaker and ferrite rod brackets. The 2½ inch speaker is first fitted into its position through the chassis with the flange being sited on the printed circuit side. The speaker is securely held into position by means of 6BA countersunk screws and nuts, the latter being fitted on the plain side of the chassis. Reference again to Fig. 2 will show that a solder tag and the ferrite rod mounting bracket are also mounted at the same time as the speaker.

Next, fix in position the variable tuning condenser C<sub>2a</sub>/C<sub>2b</sub>, but prior to so doing, ensure that the spindle is only some ⅜ of an inch in length. On some condensers this will already be the case, but it will be as well for the individual constructor to check this before finally securing the component in position. Only two 4BA x ¼in countersunk screws are used here—the third hole nearest to the wavechange switch is used for retaining the chassis in the cabinet.

We deal next with the volume control R<sub>15</sub>, securing this in position by an 8BA x ¼in countersunk screw and nut. The wavechange switch is next fixed by means of two 8BA x ¼in countersunk screws and nuts. Follow this by fitting the two a.f. transformers, these being positioned as shown in Fig. 2 and secured by inserting the lugs through their respective holes in the printed circuit chassis and berding them over so that a secure fixing is obtained. Fig. 2 also shows the correct terminations for the coloured lead-out wires which should be wound, in the manner of a spring, around a short length of 18 gauge wire. Removing the large gauge wire, the ends of these wires can then be cleaned and stretched in order to reach their respective termination points.

With the exception of the ferrite rod aerial and the transistors, the main components have now been fitted in position and we must now proceed to solder in the various resistors and condensers. Before doing so, however, a few words about soldering to a printed circuit board, for the benefit of those who

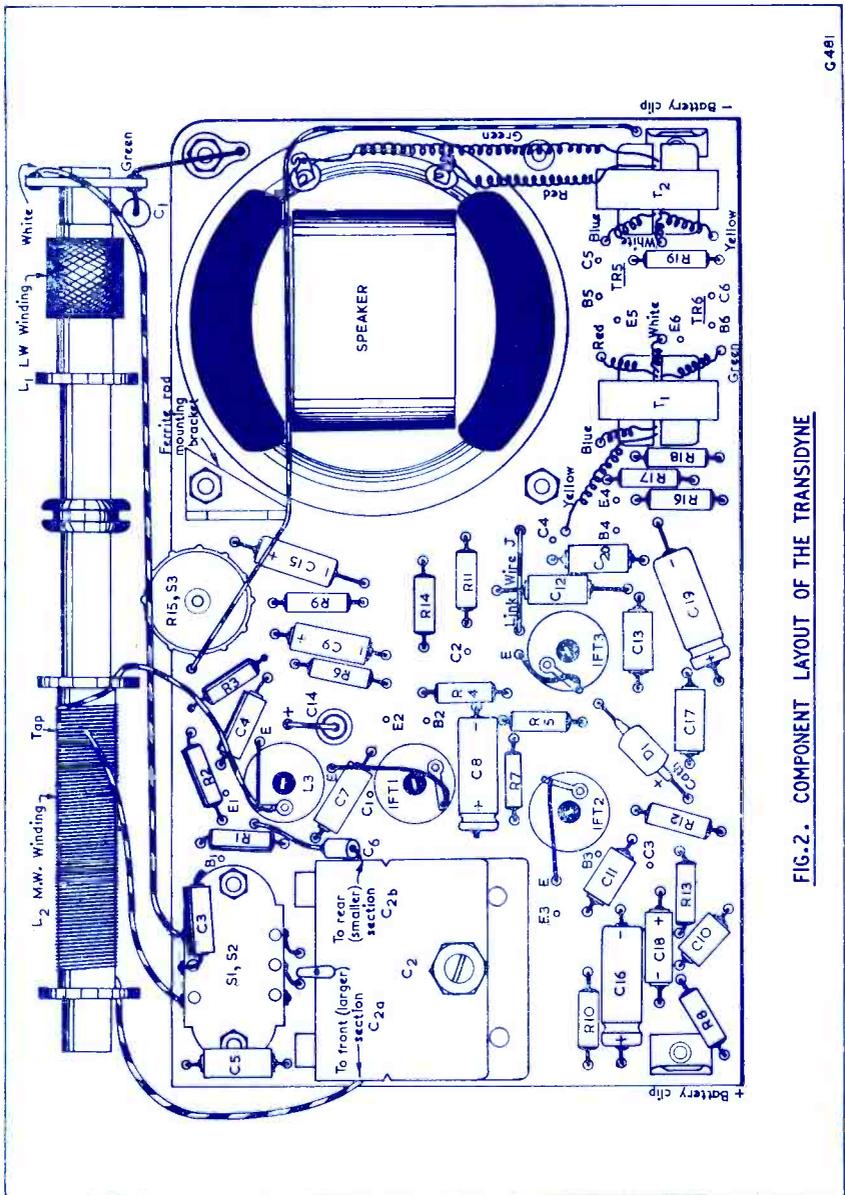


FIG. 2. COMPONENT LAYOUT OF THE TRANSIDYNE

G 481

have not undertaken this type of work before, may not come amiss.

When soldering components to the printed circuit board, the lead-out wires should be pushed through their respective holes, the ends cut off to a suitable length, a little *non-corrosive* flux applied and then, preferably

with a small 25 watt iron, soldered neatly. Surplus flux may afterwards be removed with a little methylated spirit and a small piece of clean rag. All components must be securely soldered to the printed wiring; large "blobs" of solder formed with a cold or untinned iron just will *not* suffice if the

outcome is to be at all successful.

The various resistors and condensers should now be soldered into their respective positions, omitting  $R_6$  at this stage, the value of this component being fully discussed later in this article under the heading "Biasing". Great care should be taken to observe the correct polarity of the electrolytic condensers and, where the metal cans of these are liable to be in contact with other components, they should be insulated with two layers of Sellotape material.

The correct positions of all resistors and condensers are clearly shown in the drawing of Fig. 2 and the accompanying photographic layout also greatly assists with the identification of the various components.

The condenser  $C_6$  is connected between the rear (smaller) section of the tuning condenser and the printed panel. In some cases, a small condenser, not included in the component list, having a value of between 5–10pF may be required to be fitted across  $C_{7a}$ .

$C_{14}$  is mounted so that the negative end is towards the chassis, the positive end being insulated with sleeving and soldered where shown in Fig. 2 (to the right of  $L_3$ ).

Having wired all these components into position, the remaining wiring links should now be soldered into the circuit, these being the two a.f. transformers, variable condensers, and the switch; leaving the transistors and the ferrite rod aerial still to deal with in the following manner.

The transistor lead-out wires should be first insulated with 1mm. sleeving, the wires themselves should *not be cut short*. The various leads should now be fed through the appropriate apertures, as shown in Fig. 2, and soldered to their respective terminations. A pair of pliers should be used here as a heat shunt when soldering these transistor leads into position. The transistors themselves may be positioned in any advantageous manner; but the output transistors  $TR_5$  and  $TR_6$  should not, under any circumstances,

touch the metal casing of the speaker as some transistors may have the collector internally connecting to the transistor outer casing.

Having wired the transistors into circuit, we deal next with the ferrite rod aerial. When mounting the aerial, the grommets may be required to be moved along the rod. The Medium wave winding is that positioned nearest to the ganged condenser. The connections of the Light programme winding are as shown in Fig. 2. The connections of the Medium wave winding are as follows: yellow to  $C_1$ ; white to  $S_1$ ; and green to earth (6BA solder tag held in position by the speaker fixing nut.)

### Biasing

The nominal value for  $R_6$ , which was referred to previously, is  $1k\Omega$ , but due to the somewhat wide variations of gain existing from transistor to transistor, this value may vary between that of  $500\Omega$  and  $2.2k\Omega$ . The best arrangement here would be for the constructor to temporarily connect into circuit a variable resistor of some  $10k\Omega$  in value during the alignment process, and to adjust this during alignment to a value which will maintain stability. Once this value has been found, the resistance of the variable component should be measured (disconnected from the set) and a fixed resistor of this value soldered into position.

### Battery

To provide power for the receiver, two No. 8 batteries should be inserted into the paxolin tube provided so that the brass cap of one is held into position against the zinc case bottom of the other battery. It is rather important to note here that the brass cap is the *positive* connection and that this must be in contact with the battery clip nearest to the *tuning condenser*. Intending constructors are warned that a reversal of the batteries will destroy the transistors.

In Part 2 of this series, to be published next month, alignment and fault finding procedure will be fully explained.

---

---

## Can Anyone Help (continued from page 109)

J. PATTERSON, 29 Leadale Road, Leyland, Lancs, requires information on the Test Set 43, in particular what it was specifically designed for, its sensitivity, and the timebase speeds.

\* \* \*

F. CORDING, 1 Stirling Buildings, Tavistock Street, London, W.C.2, wonders if any reader has any information or a manual, to lend or to sell, on the Synchroscope type P4E, serial 306.

J. F. PORTER, 448 Rochdale Road, Royton, Lancs. wishes to obtain the circuit and any other data concerning the 58 Mk. 1 Transmitter/Receiver, and is willing to purchase or pay for the loan of this.

\* \* \*

B. M. HALSTEAD, "Clovelly," Stubbing Drive, Hebden Bridge, Yorks, appeals for help in obtaining a service sheet or data (sale or hire) of the Pye Radio model 946 Console (1939).

## MODELS FOR RADIO CONTROL

# THE "WAVEMASTER" KIT

### Part 2


by Raymond F. Stock

THE "WAVEMASTER" COMES PACKED IN A strong cardboard box, which is 36in long to accommodate the main longitudinal members of the hull.

A clearly printed sheet of drawings is included in the kit and gives a full-size plan of the model, a full-size side elevation and a number of diagrammatic, exploded and cut-away views of detail to augment the instructions. The latter are printed in a separate 6-page leaflet which also carries a parts list.

true construction. In general, this also applies to the cabin structure—though one or two parts here need a little carving to shape; no difficulty should, however, be anticipated on this score.

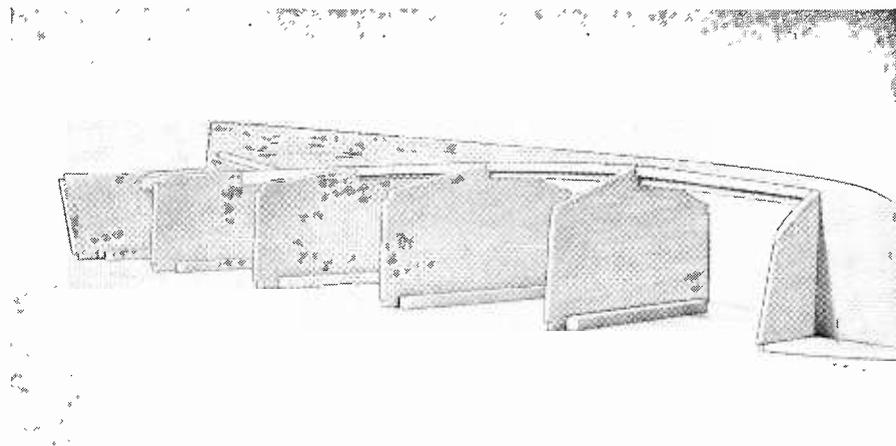Like most similar products, the "Wave-master" is a "dry" kit, i.e. it does not include glue or paint. This is quite reasonable since it avoids any possibility of deterioration during storage, and it gives the builder the choice of materials. It is suggested that the



*Early stage in assembling bulkheads and keel*

Most readers will have had some contact with kits of model aircraft, and the "Wave-master" might be considered to be a marine equivalent of this type of product. Unlike most aircraft kits, however, all the parts of the hull are prefabricated so that building the model is a matter of assembly rather than

instructions could usefully include some recommendations regarding the adhesive and perhaps some further notes on painting and finishing.

#### **Modifications**

Before commencing construction it is worth considering whether modifications to

the basic design might be included to permit greater versatility. The manufacturers of kits provide materials and a design which can be made up exactly as detailed into a very satisfactory model; but individual requirements vary so widely that builders invariably graft their own ideas on to the basic model.

being about  $\frac{1}{2}$  in. By cutting the frames in this way, chassis and other items of equipment need not be confined between bulkheads. Alternatively, as shown in Fig. 2 (right) the top part of the frame, acting as a deck beam, can be completely removed, in which case the verticals should be increased


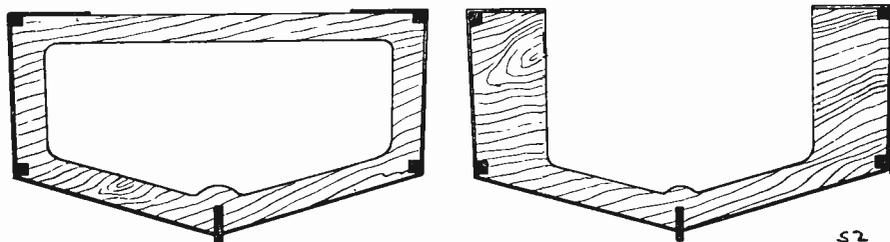


Fig. 2. Cutting away bulkheads to make open frames

As supplied, the hull is divided into six compartments by transverse bulkheads. This produces an enormously strong hull if properly made and is virtually indestructible.

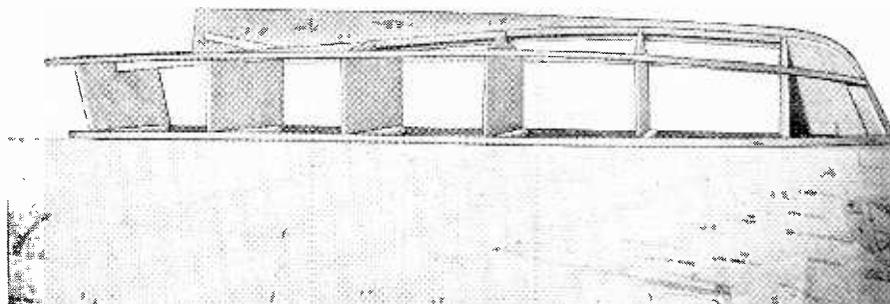in width—to the same width, in fact, as the deck at that point. This gives unobstructed access to the interior of the hull over a rectangle measuring about 25in by 6in. The



Stringers in position

It would be entirely reasonable to cut away the centre portions of the bulkheads so that they become open frames. Provided the wood is cut cleanly, and well radiused at the corners, the resulting structure would still have a wide margin of strength.

Fig. 2 shows (on the left) a typical frame shape, the average width of the plywood

strength of the hull would still be more than adequate.

A careful consideration of these points should be given, as it is extremely difficult to modify the hull in this way after building. When such work is decided upon, it should be carried out straight away, with the aid of a fretsaw and wood-cutting blades having not


fewer than 16 or so teeth to the inch, after which building can still be carried out exactly as detailed in the instructions.

Bulkheads should not, of course, be cut away needlessly, and there are at least two further reasons why complete transverse members may be a useful feature. When an internal combustion engine is fitted the builder is well advised to box it in so that the fuel is unable to attack the radio gear, and the most convenient method of doing so is to make one section of the boat, between bulkheads, a separate engine room, as indeed is indicated on the plans. Builders having no previous experience of miniature compression ignition and petrol engines will find that they are inclined to be "messy," though this vice can be cured by the appropriate treatment. Largely, this requires attention when filling the fuel tank to avoid spilling the liquid into the bilges, and needs a proper exhaust system to convey the unburnt fuel (always present) well outside the boat.

outside the hull by suitable extensions. The details must obviously be left to the ingenuity of the builder, but the aim must be to avoid joints which can leak oil into the hull. Such pipes can most easily be led straight out through the sides of the hull with a slight fall away from the engine, though a long exhaust pipe to the transom may be more typical of the class of hull.

These points must obviously be taken into account before starting work on the hull so that the appropriate holes may be cut into the bulkheads. Similarly, it is necessary to consider interconnection of control gear, some of which will almost certainly be sited both fore and aft of the engine. Small holes are provided in the bulkheads which may be opened out to take wires. It is a wise plan, however, to pass a  $\frac{1}{2}$  in diam. aluminium or paxolin tube through the engine room from bulkhead to bulkhead, thus providing a protected conduit for future use.

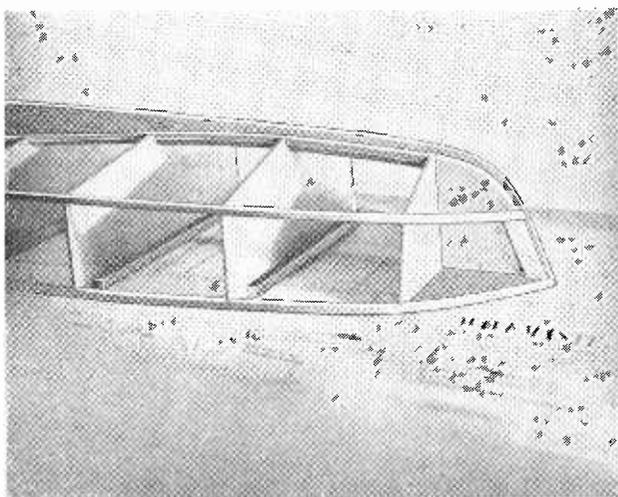It will be seen that it is advisable to pur-



*The completed structure ready for attachment of the side skins*

Generally speaking, the engines encountered will be basically aircraft motors. Some of these can be purchased in marine versions which have a water cooling jacket and exhaust stub pipes which must be continued

chase the engine before starting the construction, and this will also permit details of the mounting to be decided, and any special structure to be more easily fitted, at an early stage.

PLEASE NOTE: **We cannot undertake to answer queries over the telephone.**

See also Notice re queries on page 93

ERRATA: The following errors occurred in the Components List on pages 40, 41, last issue, of the Jupiter Stereo Amplifier: R15 should read 220 $\Omega$   $\frac{1}{4}$ W, EL34's should be EL84's, and ECC81's should be ECC83's.

# A CORNER REFLECTOR AERIAL

*Details of an efficient t.v. aerial specifically designed for Channel 10. Details are given which will enable a similar aerial to be constructed for any other channel*

By **J. C. Belcher, G3FCS**

THE WRITER'S HOUSE IS SITUATED IN A valley which runs in a direction at right-angles to the line of sight of the local television transmitting stations. A diagram showing the geography of the site is shown in Fig. 1. Now being in a zone of high field-strength, television reception is naturally marred by a large number of reflections or "ghosts." To complicate matters still further, as shown, about fifty feet from the foot of the house the ground rises fairly steeply to a

height of about 100 feet, and, being in the "shadow" of this high ground, the strength of the direct ray from each transmitter is severely attenuated. The problem presented is, therefore, one of extremes. A maximum of interference, and a minimum of signal from the transmitter.

The problem on Band I had previously been successfully overcome by providing a horizontal slot aerial with a mesh reflector in the under-drawing of the house, i.e. in the


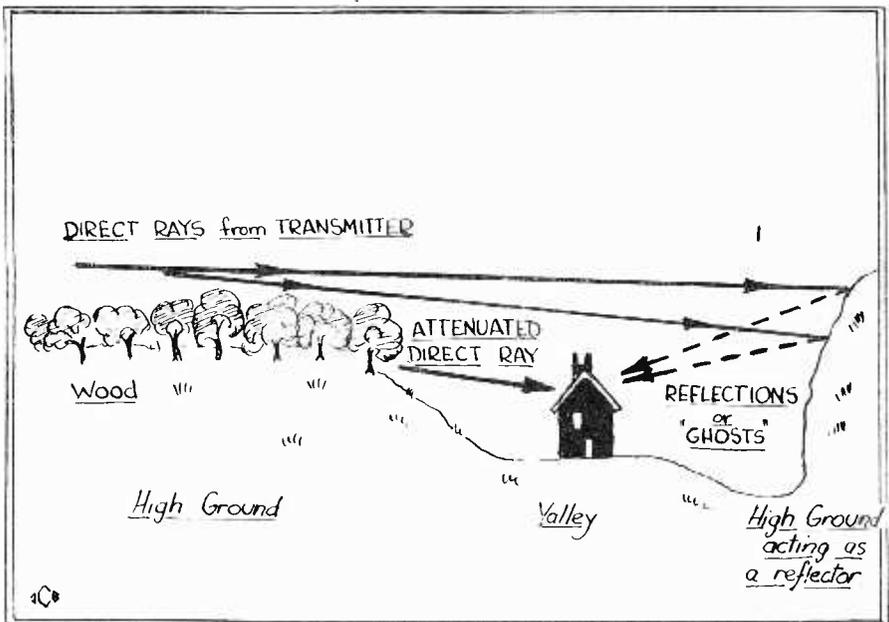


Fig. 1. Diagram showing production of "ghosts" and weak signal at the site in question

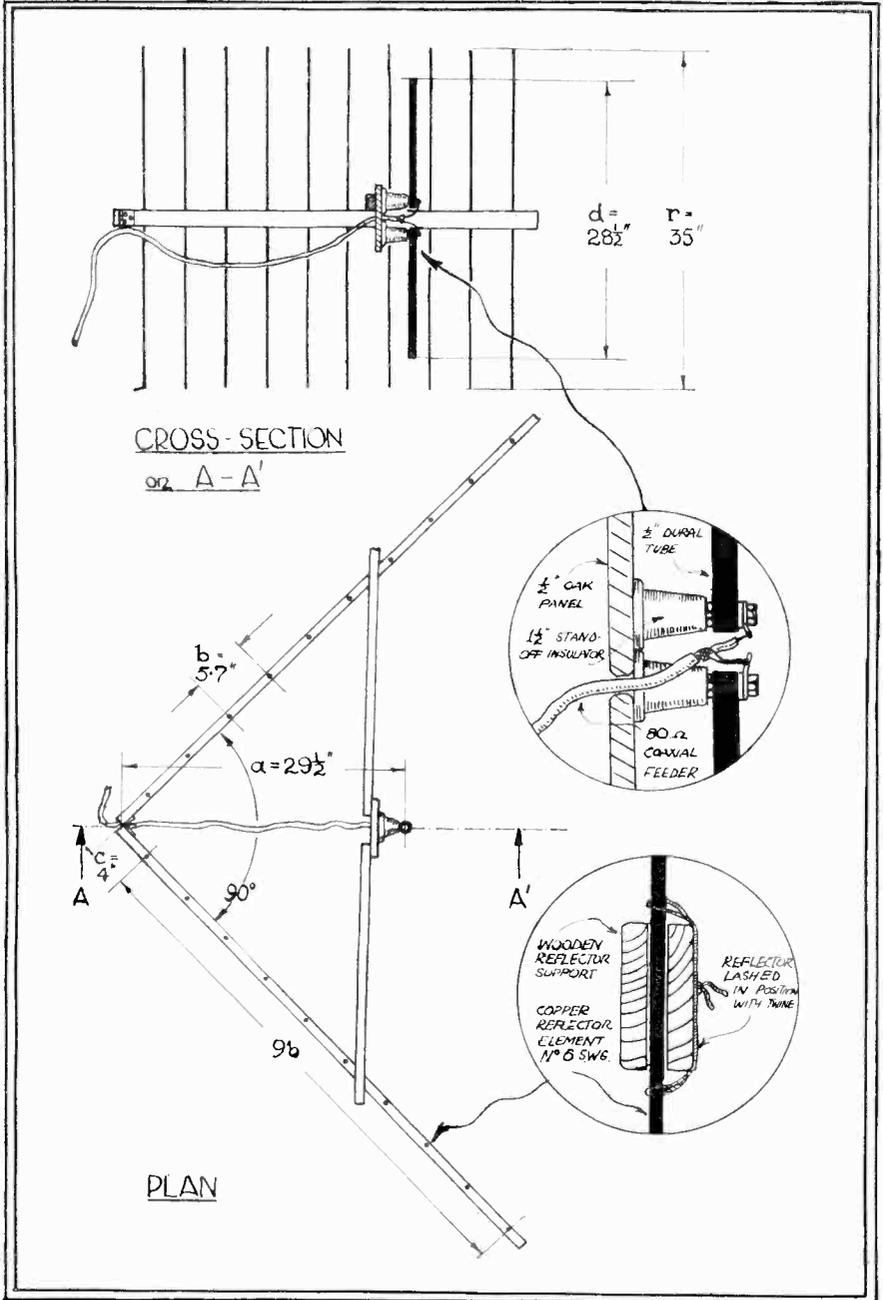

Note that the dimensions given in the above diagram refer to Channel 10.  
For other Channels see Table 1

roof-space. The resulting array of chicken-wire and bamboo may not have been particularly pleasing in the aesthetic sense. Nevertheless, its performance considerably out-pointed that of commercial multi-element external beams in the immediate neighbourhood.

When conversion to Band III became imminent, it was only natural, therefore, to consider the provision of a slot aerial with an added refinement in the shape of a completely enclosed hemispherical reflector. Although this proposal had considerable technical appeal, in practice, however, it was rejected on the subsequent grounds of lack of both time and small-mesh chicken wire.

The family was to blame. For once it was unanimous in presenting its ultimatum: "Channel 10 by tomorrow—or else." So the problem had to be considered anew. High gain together with a high front-to-back ratio was the specification, and the contract was to be completed within twenty-four hours.

The immediate solution which presented itself was a parabolic beam. The construction of a parabolic curve, however, involves certain difficulties which might not be easily overcome during the permitted time given. In addition, it was felt that the location of the dipole at the focus of the parabola might prove rather tricky, to say the least of it.

And so the idea of the corner reflector was born. The idea of using it, that is. Half-an-hour's figuring with pencil and paper produced a 21-element array with a theoretical performance which seemed to fill the requirements. A forward gain of about 10dB, and a front-to-back ratio of about 35dB. From the constructional point of view, the right-angled reflector is not at all complicated, and the only stipulation regarding the position of the dipole is that it must lie on a line bisecting the corner angle.

The next problem was that of raw materials. Armed with a torch, and protected by gumboots, a survey of the garden shed brought to light the following collection of loot—or junk, if you have a critical mind. One of those striped canvas garden shelter affairs yielded two lengths of wood, each 6ft x 1½in x ¾in. These were filched for the purpose of supporting the reflector elements, and normally wouldn't be missed by the family until the fine weather came. In any case they were due for replacement sooner or later. A third piece of wood of similar size would have been useful for supporting the dipole, but to wreck the shelter entirely was not considered to be good policy. Vandalism could be tolerated under the circumstances, but not sheer cannibalisation—especially when it involved a reconstruction job later on in the year! However, that problem was solved when an old clothes horse fell to

TABLE I

<i>Dimension</i>	<i>Length (inches)</i>
Overall length of dipole ( <i>d</i> ) ..	5480/f
Overall length of reflector ( <i>r</i> ) ..	6750/f
Distance of dipole from apex ( <i>a</i> ) ..	5650/f
Spacing between reflector elements ( <i>b</i> ) .. .. .	1095/f
Spacing between apex and first element ( <i>c</i> ) .. .. .	767/f

pieces in the writer's hands! A search in the wood pile disclosed an oak panel, 6in x 6in x ½in, quite suitable for mounting the dipole after very little modification. The next thing was the metalwork. One brass hinge, complete with six brass screws, seemed the very thing to fasten the two reflector supports together. Why brass? Well, iron or steel-work never does seem quite appropriate in an r.f. field. A pensioned-off Channel 2 H-array provided some lengths of ½in dia. dural tube; and, most useful of all—hung on a hook in the corner of the shed was a sizeable coil of hefty copper wire, about No. 6 s.w.g. Finally, a couple of ancient Raymart stand-off insulators—1½in size—were brought to light, together with some 4BA screws, washers, nuts, and soldering tags. Returning to the dining room via the kitchen, a reel of twine was successfully liberated from the household stores. Then, with the family safely out of the way in the living room in the company of Channel 2, the manufacturing process commenced with just twenty-three hours to go to zero hour.

The two 6ft lengths of wood were sawn off to a length of 60in and, commencing at 4in from one end, ½in dia. holes were drilled through the longer dimension of each piece at 5.7in intervals, a total of 10 holes being provided in each support. These were to take the reflector elements. The brass hinge was then used to join the two lengths together, and also allow the array to be folded up flat for carrying it through the trap door and up into the under-drawing. Another torch-and-gumboot expedition was made into the garden, where one end of the coil of wire was secured to a concrete gate-post. The coil was then unrolled to the far end of the garden, and fourteen stone of bone, muscle and blubber engaged in a tug-of-war with the gate-post. The verdict was given in favour of the B M and B as the wire gave a reluctant stretch of about eight inches and finished up free from kinks and wrinkles. Returning once more to the living room—via the french windows this time—a fifteen minutes stint with a pair of side-cutters resulted in the production of twenty reflector elements, each 35in in length. With the aid of two

chairs and the dining table as a support, the elements were threaded through the holes in the wooden supports, and lashed in position with liberated twine. So far, so good!

The two stand-off insulators were mounted next as close together as possible in the centre of the oak panel, and a  $\frac{1}{2}$ in dia. hole was drilled through the panel to take the coaxial feeder. A couple of lengths of dural tube—each about 15in long—were then drilled 4BA clearance at one end, and fixed to the insulators with the screws, washers and nuts—soldering tags being provided for the coax termination. As a final adjustment, the extremities of the dipole were trimmed off with hacksaw and file until the overall length of the dipole was 28 $\frac{1}{2}$ in. The two pieces of clothes-horse were then screwed to the oak panel in such a way that the centre of the dipole would lie in the same plane as the centre of the reflector elements when the assembly was finally fitted together. Next, the dipole support was laid across the reflector supports, the former providing the hypotenuse of the right-angled triangle thus described. The distance between the dipole and the vertex of the reflector was then adjusted to 29 $\frac{1}{2}$ in and the supports permanently lashed together with twine. A length of available—but, of course, very lossy—Channel 2 coax was finally soldered to the dipole terminations, passed through the hole in the oak panel, and lashed to the apex of

the reflector support.

A plug fitted, the t.v. set connected up, and with the corner antenna firing through the french windows, the writer settled back to sample his first taste of commercial telly—home-brewed! While it must be mentioned that the family's first reactions at the sight of the creation were not exactly complimentary, it is now pleasant to report that discipline is once more maintained and relations are on a more respectful footing!

The following day, the whole contraption was taken up into the under-drawing and suspended from the rafters with a length of twine at each corner of the reflector. With the installation of a diplexer unit the job was finished, the whole project taking only a total of four hours from picking up paper and pencil to closing down the trap-door. In spite of the losses over about 30ft of Band I coax, the signal was more than adequate—with plenty of contrast to spare, and absolute freedom from "ghosts."

The design of the array, together with constructional details, is shown in Fig. 2, the diagrams being more or less self-explanatory. Should the reader wish to design a similar aerial for a different channel—even on a different band—design formulae is scheduled in Table I,  $f$  being the mean channel frequency in Mc/s, and the lineal dimensions being in inches.

---

## AUDIO

# LOUDSPEAKER

# CROSS - OVER

By C. M. PEARSON, B.Sc.

# NETWORKS

IT IS ALMOST IMPOSSIBLE TO DESIGN AND manufacture a moving coil loudspeaker which will satisfactorily reproduce the range of frequencies required for high fidelity sound systems. For this reason, it is better to divide the audio frequency spectrum into two or more bands and to use a separate, optimally designed loudspeaker for each band. This division is usually accomplished by a loudspeaker cross-over network.

Consider, first of all, a two-speaker system comprising a bass and a treble unit. Suppose the bass unit is designed to operate from low frequencies with a level response up to, say,

10 kc/s, and the treble unit from 2.5 kc/s upwards. In order to drive these loudspeakers satisfactorily, we require a filter for each loudspeaker. The filter for the bass unit is required to pass all frequencies from zero to 5 kc/s and the filter for the treble unit is required to pass frequencies from 5 kc/s upwards, with a flat response and low attenuation in the pass region in each case. The cross-over frequency is chosen in this instance as 5 kc/s, since the change from pass to stop is not very sudden, and this frequency prevents overloading either speaker around the cross-over region.

These two filters are known as "low pass" and "high pass" filters, for obvious reasons. If the two loudspeakers have the same voice coil impedance, the design of these filters is quite a simple matter, the usual type being a single-section constant-k type as illustrated in Fig. 1. The values of L and C may be calculated from the formulae:—


$$L = \frac{Z_o}{\sqrt{2} \pi f c} \quad C = \frac{1}{2\sqrt{2} \pi f c Z_o}$$

where  $Z_o$  is the speech coil impedance and  $f$  is the cross-over frequency. Thus, for an impedance of  $15\Omega$  and a cross-over frequency of 5 kc/s,  $L_1 \approx 675\mu\text{H}$ ,  $C_1 \approx 1.5\mu\text{F}$ .

In use, the inputs of the two filters would be connected in parallel to the  $15\Omega$  amplifier output connections as shown in Fig. 2.

converting the  $3\Omega$  bass speaker impedance to  $15\Omega$  should be tapped at  $4/9$  of the winding (i.e.  $\sqrt{3/15}$ ). The actual number of turns required will depend on the power level, the lowest frequency to be handled and the core size of the transformer.

Consider now a three loudspeaker system, consisting of a bass speaker, a mid-range speaker and a treble speaker. Suppose that the cross-over frequency for the mid-range speaker is 750 c/s and for the treble speaker 5 kc/s as before. We now use what is in effect two cross-over networks, one designed for 750 c/s and one for 5 kc/s, as shown diagrammatically in Fig. 4 and in circuit form in Fig. 5.  $L_1$  and  $C_1$  are the components of the 5 kc/s cross-over network, with the same values as before, i.e.

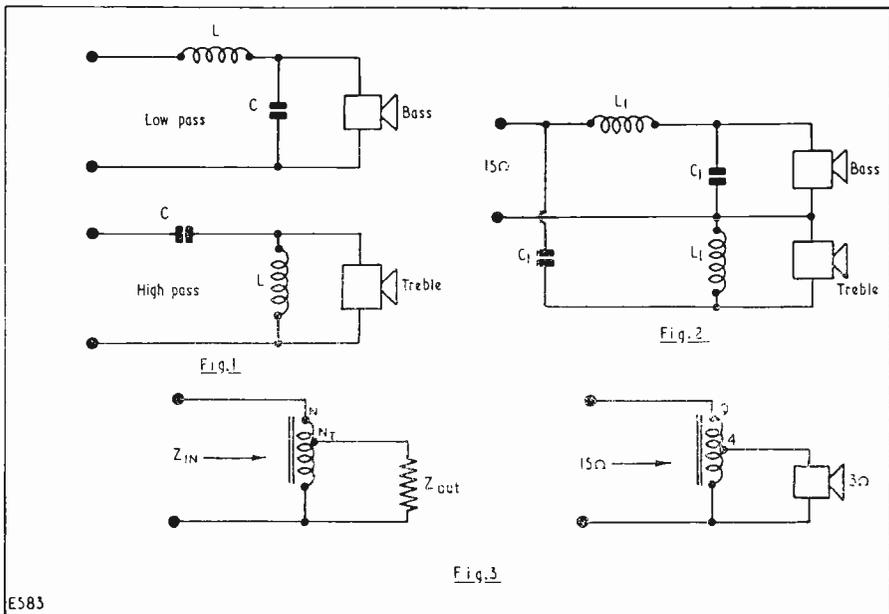

If the two loudspeakers have different speech coil impedances, a matching transformer will have to be used to make them alike. An autotransformer should be used and is best applied to the bass speaker. Referring to Fig. 3, if  $Z_{in}$  is the input impedance,  $Z_{out}$  is the output impedance,  $N$  is the total number of turns and  $N_t$  the number of turns to the tap, then

$$\frac{N_t}{N} = \sqrt{\frac{Z_{out}}{Z_{in}}}$$

In a system using a  $3\Omega$  bass speaker and a  $15\Omega$  treble speaker the autotransformer

$L_1 = 675\mu\text{H}$ ,  $C_1 = 1.5\mu\text{F}$ , and  $L_2$  and  $C_2$  are the components of the 750 c/s cross-over network and are  $L_2 \approx 4.5\text{mH}$ ,  $C_2 \approx 10\mu\text{F}$ .

It will probably be necessary to incorporate an attenuator in the treble and mid-range loudspeaker circuits in order to balance the overall response of the system to individual taste, since the efficiency of the mid-range and treble speakers will be rather higher than that of the bass speaker. A very simple attenuator is quite satisfactory, and a circuit and values for  $15\Omega$  speakers are given in Fig. 6.

The components used in cross-over net-


works are fairly critical. The capacitors, for instance, must be of the paper or mica variety, electrolytics being quite useless since there is no d.c. polarising voltage in the circuit. The inductances must be air cored or wound on a core of thin transformer laminations, stacked one way with a large air gap.

Cross-over chokes should not be mounted near metal since, being air-cored, the inductance value will be affected.

speakers may be obtained complete from Goodmans Industries Ltd., Axiom Works, Wembley, Middlesex, or through stockists of their products.

Goodmans also sell a 15Ω attenuator switched from 0-12dB in 2dB steps, and 4.5mH chokes suitable for home construction of the 750 c/s cross-over network.

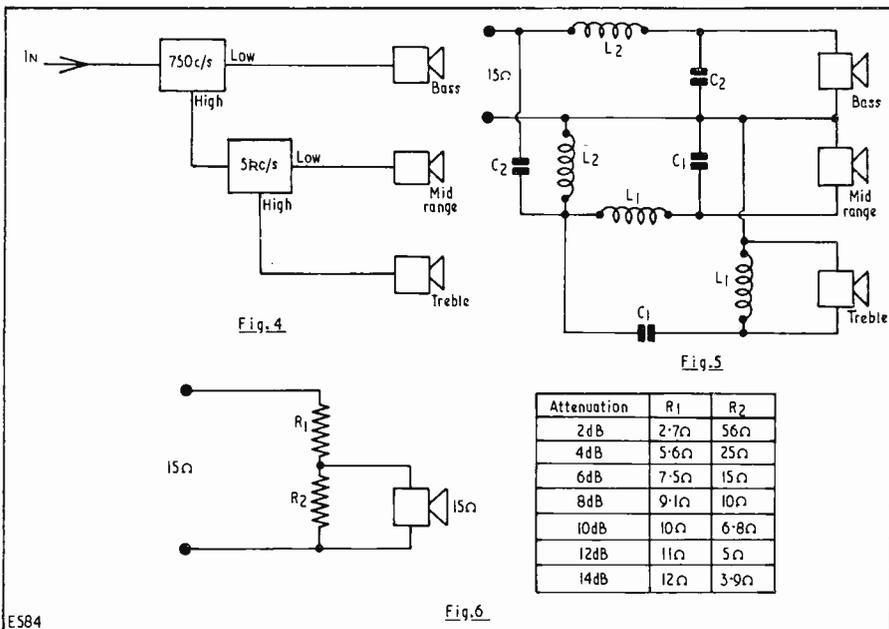Osmor Radio Products can supply both chokes; the 675μH one is their type QCO1, and 4.5mH is type QCO2.



The actual cross-over frequencies chosen depend on the loudspeaker design, and for any particular type of loudspeaker the manufacturers should be consulted. The examples worked out in this article are (1) for the twin loudspeaker system, Goodman's "Axiom 300" and "Trebax"; (2) for the triple loudspeaker system, Goodman's "Audiom 70", "Midax 400" and "Trebax." The cross-over network described for these

When connecting up in their cabinet, the phasing of the loudspeakers should be checked. This can be done by connecting a single cell battery in series with the output transformer secondary. There will be a "plop" and the cones of the speakers will move; check that they all move in the same direction. With 3Ω speakers it is wise to put a 10Ω resistor in series with the battery to limit the current.

*continued from facing page*

other fixture is the socket for the earth and positive leads. This socket has one large and one small diameter contact, and two-pin plug to suit, in order to prevent accidental reversal. All other components are floating.

The neon itself may be of nearly any type, and if unmarked it may be assumed to be an ex-W.D. type which will strike at around 90V.

If a variable tone is required, C<sub>1</sub> or R<sub>1</sub> may be variable components.

# A Multi-Purpose Neon Tester


by M. J. ROGERS

THE INSTRUMENT TO BE DESCRIBED IS compact, economical and versatile. It may be used for signal tracing, as a morse oscillator, and mains tester; it takes very little h.t. indeed; and it may be constructed in an old pen case.

The circuit is a conventional neon relaxa-

tion oscillator, where the voltage across the neon builds up as  $C_1$  is charged. At just over 90V the neon strikes and discharges the condenser. This cycle of operation is repeated.

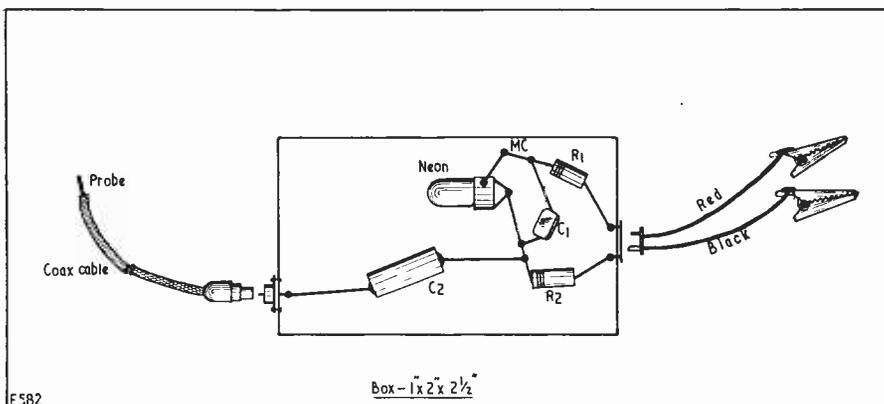
The construction will obviously vary from one constructor to another, and while the more experienced can easily build the



tion oscillator, where the voltage across the neon builds up as  $C_1$  is charged. At just over 90V the neon strikes and discharges the condenser. This cycle of operation is repeated.

instrument in a split pen case, it will be described as fitted in a box. A very useful type of case for this purpose is the small 2oz rectangular variety of tobacco tin.

The neon will be fitted in a holder with

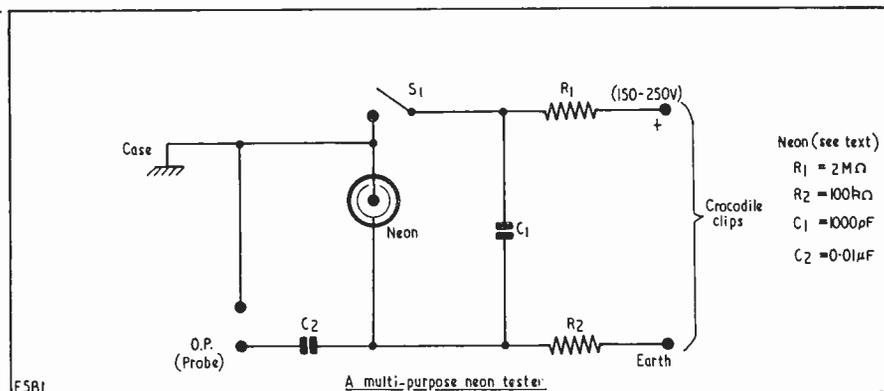

The output is taken from between  $C_2$  and case ("chassis"). When required to be used as a mains polarity tester, the switch  $S_1$  is

one side earthed to the case—to this one side of the coax socket is connected. The only

*continued at foot of page 134*

# A NEW DETECTOR AND AUDIO AMPLIFIER

*This article describes a new detector and audio amplifier of excellent quality. No claim for hi-fi reproduction is made, though the author has heard hi-fi systems which, to his ears, sounded worse.*

By **K. E. MARCUS**

**T**HIS NEW ARRANGEMENT OWES ITS development directly to the deplorable habit of the lady of the house, who likes to tune from one of her favourite stations to the next one with great rapidity, putting the tuning "somewhere" and turning up the volume control to compensate for the loss of sensitivity by her mistuning, and as the author cannot believe that Mrs. M. is the only offender in this respect, he settled down to design a receiver with the following qualities:

- (1) Pretuned to the three or four favourites on the medium wave band.
- (2) No volume control.
- (3) But roughly equal audio-output on all three or four channels.
- (4) Good quality of reproduction.

The first requirement was easily met by using a rotary switch which switches on and brings into circuit pre-set trimmers, which tune a normal medium wave coil to the favourites. A rotary switch was used as there were three circuits to be handled (r.f. grid, mixer grid, oscillator). However, push-buttons or "piano-keys," now so extensively used in Continental sets, will do just the same if one button moves three contacts and the difficulties of screening between them can be solved.

The other three requirements led to the system to be described here.

Fig. 1 shows the schematic circuit. Six things will be noted at once by the studious reader:

- (a) There is direct coupling from the detector load to the audio pre-amplifier,
- (b) There is no volume control.
- (c) Both valves have their cathodes tied to chassis; in fact, all the other three valves of the experimental station (r.f. amplifier, mixer and i.f. amplifier) have earthed cathodes as well.

- (d) One negative supply point is arranged in the power pack, from which all grids are supplied with their negative bias and with a.v.c.
- (e) There are two negative feedback loops.
- (f) There is extensive smoothing applied everywhere.

Let us take these points in order. In a conventional receiver the detector stage looks something like Fig. 2.

This rather cumbersome arrangement is too well known to merit a new description. Here are only a few details which may have escaped the casual observer: R<sub>c</sub> biases the audio amplifier triode and delays the a.v.c. production, while the demodulator load is returned to cathode so as not to delay the associated diode as well. The gain of the amplifier triode is usually around the 20 mark, so that with about 3V i.f. on the detector diode we can reckon with about 50V a.f. on the triode anode with the volume control full on.

Now compare this with the diode-pentode arrangement in Fig. 1. The grid of the pentode section is joined directly, via an h.f. filter, to the demodulator load. Therefore the pentode is a.v.c.-ed. The gain of the pentode would, without a.v.c., be about 60 times; therefore we would expect, again with 3V i.f. on the diode, about 150V a.f. on the anode. This, of course, will never occur because of the a.v.c. action and because of the negative feedback from the loudspeaker-speech coil into the bottom resistor (1kΩ) in the diode load. But it will now be clear why a volume control is unnecessary: with the amount of feedback required to "tame" the circuit, a "control" just does no controlling any more, and we are getting improved quality into the bargain.

The whole bias system of the new arrange-



ment needs now to be explained. For this refer to Fig. 3.



As can be seen, this is simply another way of drawing the relevant parts of Fig. 1, but it shows quite clearly how the different bias voltages are obtained.

Between the negative supply point ( $-18V$ ) and chassis there is round about  $18.5M\Omega$  resistance, therefore just under  $1mA$  will flow through this chain. In consequence there will be about  $-2V$  d.c. on the a.v.c. line, which is the usual no-signal bias of the previous stages. A bias of about  $-0.5V$  is applied to the detector diode, muting it nicely, while a little less (about  $-0.45V$ ) is applied to the grid of the pentode section.

amount of r.f. would be amplified in the pentode section and produce havoc in the output stage. And the screen grid voltage of the pentode section has to be stabilised by a bleeder resistance ( $47k\Omega$ ), as otherwise audio distortion would occur.

The coupling between the audio stages is quite conventional. Again the cathode of the output stage is earthed, and the negative supply is fed into the grid after smoothing through the  $100k\Omega/25\mu F$  filter. For safety's sake there is another r.f. filter  $220\Omega/250pF$  in the grid. Finally, there is a voltage feedback resistor ( $1.2M\Omega$ ) between the anodes of the pre-amplifier and the output stage.

The anode of the output stage is fed

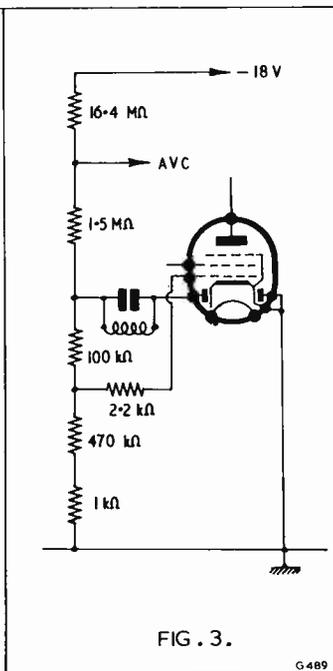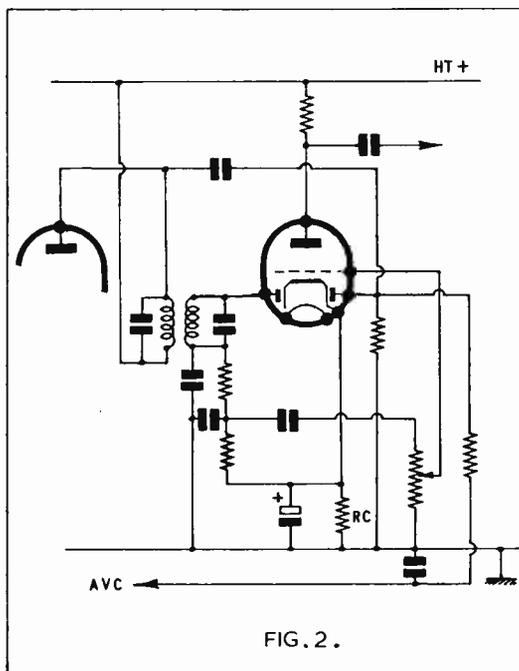

Now, with signals arriving the diode starts producing, across its load proper ( $100k\Omega + 470k\Omega + 1k\Omega$ ), a.v.c. which increases the negative supply to the previous stages in the usual manner, the  $1.5M\Omega$  acting as the audio filter resistor; and because of the high resistance ( $16.4M\Omega$ ) between a.v.c. line and negative supply point, no a.v.c. can leak away across it. The pentode section does, fortunately, not get the full a.v.c. but only, say,  $5/6$  of it.

Two further things in this stage need a short explanation: the  $2,200\Omega$  resistor in the grid is an i.f. stopper; without it a minute

through the output transformer from a higher voltage point ( $+320V$ ) of the power supply than the screen grid ( $+270V$ ). On the secondary side of the output transformer one side of the speech coil is earthed, whilst the other connects via a  $10k\Omega$  resistor to the bottom resistor ( $1k\Omega$ ) in the diode load. Experiment will show to which side of the speech coil this feedback loop has to be connected: the wrong side produces positive feedback and a mighty howl.

As stated at the beginning, the new detector-amplifier produces excellent quality. To achieve this only a minimum of hum can

be tolerated, and extensive smoothing and short connections are required.

In the experimental set (r.f. amplifier + mixer + i.f. amplifier + detector - amplifier + output) the whole h.t. consumption is 55mA, therefore a resistor of 330Ω in the negative h.t. line produces the required -18V bias. The valves used, as they were just available, are: for the detector-amplifier, 7R7 (6B8); for the output-stage, 7C5 (6V6);

for the rectifier, 7Y4 (6X5); but the valves in brackets can be substituted as they are equivalent in performance.

The lining up of the i.f. did not set up any problems. The r.f. alignment, however, produced a surprise: up to a quarter of a turn off-tune on the pre-set trimmers the set was so uncannily quiet that the author feared he would not hit the signal with the capacities provided. But then they romped in!

## TEST EQUIPMENT

# A STABILISED AUDIO OSCILLATOR

by G. K. FAIRFIELD

**T**HE ESSENTIAL EQUIPMENT FOR CARRYING out any serious audio-frequency work consists of a low-frequency oscillator, covering the range from 20 kc/s down to at least 25 c/s, and some means of accurately measuring the amplitude of the signal output from the piece of equipment undergoing test.

The set-up when making measurements (frequency response characteristics, input/output curves, etc.) will be as shown in Fig. 1. Although the meter can be switched to measure the input to the tested equipment at any given frequency setting, it is more convenient if the oscillator is arranged to give a constant amplitude of output, independent of frequency, and the meter switched permanently to the output during a frequency run.

One way of doing this is to arrange that the positive feedback network in the oscillator circuit contains some element which is independent of the frequency of oscillation but which remains sensitive to changes in the current through it, or potential developed across it. Such an element is found in the familiar tungsten lamp, the filament of which behaves as a resistance whose value is dependent on the current flowing through it (Fig. 2). We may arrange this to act as one arm of a positive feedback potential divider shown in the simplified diagram of Fig. 3.

Here  $V_1$  is an amplifier, the output of which is coupled to a cathode-follower  $V_2$ . The positive feedback loop is completed by the lamp L connected between the cathodes

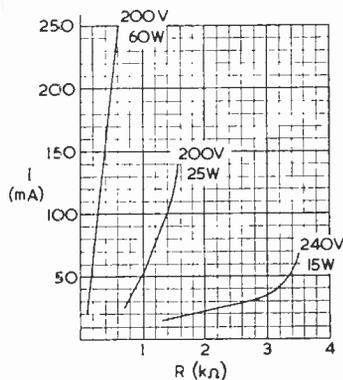
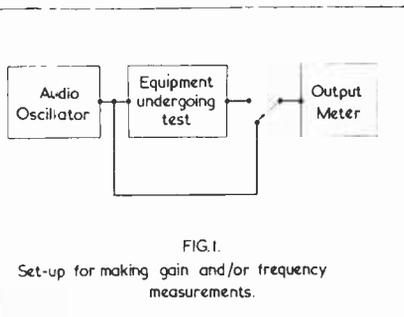


FIG. 2.  
Resistance characteristics of Tungsten Lamps. M541

of the two valves. There is also a negative feedback loop via a frequency-determining network N, but more will be said about this later.

The oscillator will resonate at a frequency fixed by N, due to the positive potential feedback from the output of V<sub>2</sub> to the cathode circuit of V<sub>1</sub>. As the oscillations build up so the resistance value of L increases and the amplitude of fed-back potential across R decreases. This in turn reduces the output from V<sub>1</sub> and an equilibrium state is quickly reached where the circuit is just maintained in a state of oscillation with a constant amplitude of oscillation developed across R<sub>1</sub>. The conditions for good waveform are at the same time automatically realised, for with V<sub>1</sub> handling the minimum amplitude of signal, overload conditions are avoided.

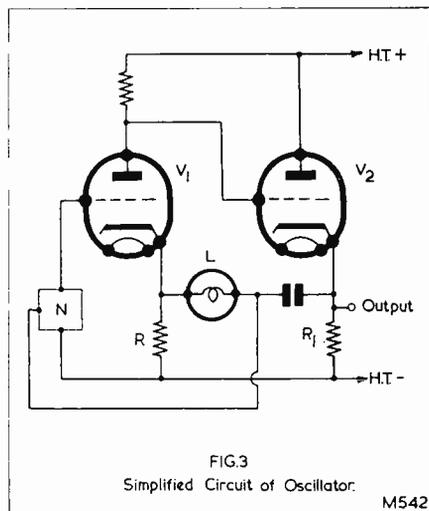


FIG.3  
Simplified Circuit of Oscillator.

M542

### Negative Feedback Loop

As mentioned previously, the frequency of oscillation is controlled by the network N connected between the output of V<sub>2</sub> and the grid circuit of V<sub>1</sub>. This is a resistance-capacity network arranged to supply a large negative feedback voltage to grid at all frequencies except the required oscillatory frequency. The amplitude of this feedback is normally arranged to exceed that due to positive feedback and oscillation prevented at all but this frequency.

Several networks are suitable for this purpose. We can use a Wien Bridge or a Twin-T network, but the one favoured by the writer is the asymmetrical circuit resembling that of a twin-T circuit shown in the complete

circuit diagram of Fig. 4. This has a considerable advantage over other networks in that control of frequency can be secured by the use of a single potentiometer R<sub>2</sub> and, apart from range-switching of capacitors C<sub>1</sub> and C<sub>2</sub>, the use of ganged potentiometer or capacitors avoided.

The circuit can be analysed and reduced to a twin- $\pi$  circuit where the series arm will be electrically equivalent to a parallel-tuned LC circuit. At the resonant frequency this will have a high impedance and very little of the output voltage from V<sub>2</sub> cathode will be fed back in antiphase to the grid of V<sub>1</sub>. At other frequencies the equivalent LC circuit is off-resonance and has a low impedance allowing a large amount of negative feedback to take place. The range of frequencies to be covered by variation of R<sub>2</sub> is governed by choice of capacity values for C<sub>1</sub> and C<sub>2</sub>. With the values shown continuous coverage is obtained from 18 c/s to 20 kc/s using three sets of capacity values.

### The Complete Circuit

In Fig. 4 is shown the complete circuit diagram for the oscillator. V<sub>1</sub> is the amplifying valve which is directly coupled to the cathode-follower V<sub>2</sub>. The lamp L is a 15W 200V pigmy lamp and is connected to the cathode of V<sub>2</sub> via a large capacitor C<sub>3</sub>. This should be at least 50 $\mu$ F if constant signal amplitude is desired down to the lowest frequencies.

The lower half of the feedback circuit R is made adjustable and in initial setting-up is adjusted until oscillation is just obtained at all points over the frequency range. This ensures minimum harmonic distortion of the output waveform.

In order to obtain a linear frequency/dial-reading calibration curve the frequency-determining resistor R<sub>2</sub> should have a logarithmic law (a suitable type is Dubilier type CD). Some cramping of frequencies at one end of the scale will be evident if a linear-law potentiometer is used, although this can be improved, at the expense of frequency coverage, by increase of the 330 $\Omega$  resistor in series with R<sub>2</sub>.

An output stage V<sub>3</sub> is shown following the oscillator. This has been arranged to function either as an amplifier having a fairly high impedance output at a maximum amplitude of 4.5 volts (r.m.s.); or as a cathode-follower giving 0.5 volts (r.m.s.) at a much lower impedance level.

Although small glass-based valves were used in the writer's equipment, it would be possible, by means of a few alterations to ensure correct bias conditions for V<sub>1</sub> and V<sub>2</sub>, to use easily obtainable "surplus" valves such as an EF50 for V<sub>1</sub>, 6V6 for V<sub>2</sub> and for V<sub>3</sub>, and a 6X5 for V<sub>4</sub>.



The layout used by the writer, and shown in Fig. 5 requires little comment. It is not critical, although care should be taken to avoid 50 c/s modulation of the output by suitable disposition of mains transformers and heater leads. Adequate smoothing of the h.t. supply is required for a similar reason.

Finally, in order to retain the advantage of the low output impedance when the instrument is switched to "cathode-follower" position, a large electrolytic capacitor is used to couple  $V_3$  to the output terminal. The polarity and voltage rating of this must be

borne in mind should the oscillator be connected to a circuit having a substantial and/or inverse polarity potential. This will rarely be the case, however, as it is more likely to be used fed into the grid circuit of amplifier valves, etc.

The amplitude of oscillations over the entire frequency range was found to be constant within  $\pm 0.5$  dB, and in order to fully utilise this a detecting instrument is required which is capable of measuring the output of the tested equipment accurately and independently of frequency. A suitable instrument will be described in a later article.

---

## BOOK REVIEWS

**HI-FI YEAR BOOK (1958 Edition).** Edited by Miles Henslow. 208 pages. 340 photographs and diagrams. Published by Miles Henslow Publications Ltd., 99 Mortimer Street, London, W.1. Price 10s. 6d.

Some people, when wishing to indulge in a spending spree on high fidelity reproducing equipment, dash into the nearest radio shop and buy the first thing they see (provided it is cheap enough), while others devote more time to comparing the merits and suitability of what is displayed and choose with more care. On the other hand, there are those who gather round them vast piles of leaflets, brochures, catalogues and such like, possibly with some considerable expense in postage for both themselves and those who supply the stuff; they then pore over it for hours on end and finish up by buying something entirely different because none of their precious catalogues shows exactly what they want.

Apart from those who may fall into any of the three broad categories listed above, there are those who, at some time or another, desire to augment or improve upon their present equipment; they, too, are then likely to adopt a similar approach to their intention to purchase. It is at such times, either for initial purchases or for supplementary acquisition, that a compendium of available equipment can be very useful, for its contents can be perused at leisure and a carefully considered choice made after stated performance, appearance and price have been studied.

This book seems to fill such a need, for it lists a considerable quantity of equipment and provides a great deal of information concerning it. Twenty pages are devoted to equipment suitable for stereo reproduction, and about a hundred pages to monaural equipment. Within this compass are contained details of amplifiers, pickups, microphones, speakers, radio tuners, motor units, speaker enclosures, hi-fi furniture, tape recorders, and so on. It is noted that transcription turntable units only are listed, so presumably auto-change mechanisms do not find a place in the hi-fi enthusiast's scheme of things. The publishers are also careful to point out that tape recorders are not necessarily hi-fi in the accepted sense of the term, even though they are included.

Several short articles are contributed by various writers in which different items of apparatus or equipment are discussed. Following some of these short but informative papers there are directories giving details of several manufacturers' products. The manufacturers are listed in alphabetical order for easy reference, and with a few exceptions all the products ascribed to them are depicted in clear photographs.

About a third of the book is given over to advertisements, though in fairness it must be said that many of these are concerned with equipment not listed in the text.

**AN ELECTRONIC ORGAN FOR THE HOME CONSTRUCTOR.** By Alan Douglas, M.I.R.E., M.A.I.E.E. 100 pages, 93 diagrams and illustrations. Published by Sir Isaac Pitman & Sons Ltd., Pitman House, Parker Street, Kingsway, London, W.C.2. Price 15s.

The contents of this rather unusual book make extremely interesting reading, and it is quite easy to imagine that the construction of the musical instrument described could form an absorbing undertaking, particularly during the longer evenings when more time could be given to the task. Provided that its constructor would be able to play it, he would have a fascinating new instrument upon which to exercise his talent for many years.

There does not seem to be a wasted word in the book, for it describes in full detail every stage of construction. It is to be noted that the author provides a comprehensive list of sources from which necessary parts can be obtained. The electronic circuits employed are simple in design and should not present any difficulty in construction to anyone who has had a fair amount of experience in such work. It would seem that the builder will need to possess a reasonably high standard of woodworking ability if he is to make a presentable job of the carpentry involved, though in all fairness it must be said that this aspect of the instrument's construction has also been reduced to the simplest possible terms.

The finished electronic organ is by no means a "one-finger" instrument, nor is it lacking in versatility. In the first chapter the author briefly discusses the musical basis of the design and his reasons for deciding on this particular one. It comprises two manuals, each having a compass of 61 notes, and a pedal board with 30 notes. The pedal specification is Major Bass 16ft, Bourdon 16ft, and Great to pedal; the Great manual has Tibia 8ft, Flute p.p. 8ft, Viole 8ft, Oboe 8ft, Trumpet 8ft, Harmonic key, Tremulant, Octave coupler and Swell pedal, while the Solo manual has Harmonic flue 8ft, Saxophone 8ft, Viole 8ft, Horn 8ft, Suboctaves I and II, Tremulant and Swell pedal.

The cost, though reduced to a minimum, would no doubt run into several pounds, but this would be spread over the period of construction and even then be far cheaper than a manufactured instrument.

W. E. THOMPSON

COME TO . . .

Open all day Sat.

# Burleigh's

for your "WAVEMASTER" BASIC KIT  
72/6 plus 3/6 p. & p.

We also keep in stock suitable Diesel and Electric Motors, Receivers & Kits, Actuators & Servos, Steering mechanisms and all requirements for a first class job.

**BURLEIGH of Edgware Road Ltd.**  
303 Edgware Rd W2 Telephone PAD 8827-8-9

## HIGH FIDELITY

Quality components of all types always in stock for the

**MULLARD 2-VALVE PRE-AMPLIFIER and MULLARD 3-VALVE 3-WATT AMPLIFIER**

Circuits free on request

510 AMPLIFIER FM TUNER	circuits 3/6
912 PLUS AMPLIFIER	" 4/-
912 PLUS FM TUNER	" 2/6
RADIO CONSTRUCTOR FM	" 2/-
MERCURY SWITCHED FM	" 2/-
DENCO FM TUNER	" 1/-

Price list available on request

**J. T. FILMER** 82 DARTFORD ROAD  
DARTFORD KENT  
Telephone Dartford 4057

# OSMOR

## Quality Components

are frequently recommended by "Radio Constructor" for use in their published circuits—a sure tribute to the reputation this company has built up for efficiency.

**PRE-TUNED SUPERHET RECEIVER**, p. 110. Osmor coils QAB, QA9 and QA4 are specially suited to this circuit.

**LOUDSPEAKER CROSS-OVER NETWORKS**, p. 132. Osmor chokes QCO1 and QCO2 have been specially designed for the circuits given and have been approved by the author.

## OSMOR RADIO PRODUCTS LIMITED

418 Brighton Road South Croydon Surrey  
Telephone Croydon 5148

# £2 DOWN will bring you enough parts to make a complete TRANSISTOR POCKET RADIO

(Size  $5\frac{3}{4} \times 3\frac{1}{4} \times 1\frac{1}{4}$ ) using a printed circuit

★ Send for **FREE PRICE LIST** (all parts sold separately) and/or 3/- for new simplified instruction booklet with suggested circuits and assembly details.

OUR CIRCUITS OFFER

**HIGH SENSITIVITY  
HIGH SELECTIVITY**

using

3 R.F. Transistors 1GN. each  
2 L.F. Transistors 10/- each

all specially selected to give  
HIGH OVERALL GAIN with A.V.C.

**FULL MEDIUM & LONG WAVE COVERAGE**  
for as little as **£9.19.6**

- Miniature loudspeakers, only  $2\frac{1}{2}$ " deep x  $2\frac{3}{8}$ " diam. **27/6**
- Miniature oscillator and i.f. coils,  $1\frac{1}{2}$ " high,  $\frac{3}{8}$ " diam. **8/-**
- Jackson 00 twin gang tuning condenser with intersection screen **10/6**
- Attractive high impact polystyrene cabinet with fittings for tuner, trimmers, speaker and circuit board **8/6**

MANY OTHER SUB-MINIATURE COMPONENTS AVAILABLE

**SPECIALISED ELECTRONIC COMPONENTS LTD** 8 Eccleston Square London SW1

MAIL ORDERS ONLY

## MEDRESCO HEARING AID

As supplied by National Health, completely overhauled and in good working order with six months guarantee. Only £2.15.0 plus 2/6 post and ins. Complete with earphone and new ear plug but not batteries. These can be supplied as an extra for 5/- per set. Instructions showing how to convert to pocket radio available free if requested.



## FLUORESCENT LIGHTS



These are complete fluorescent lighting fittings. Built-in ballast and starters—stove enamelled white and ready to work. Ideal for the kitchen, over the workbench and in similar locations.

**Single 40.** 4' 3" long, uses a 40 watt tube.

**Twin 20.** Uses two 20 watt standard tubes. Price 39/6 each, with tubes. Carriage and ins. up to 150 miles 5/6, up to 250 miles 7/6

## BAND III CONVERTER

Suitable Wales, London, Midlands, North, Scotland, etc. All



the parts including 2 EF80 valves, coils, fine tuner, contrast control, condensers, and resistors. (Metal case available as an extra.) Price only 19/6, plus 2/6 post and ins. Data free with parts or available separately 1/6

## TUBE TESTER & REACTIVATOR



We can supply all the main components for making this unit which will not only test cathode ray tubes but also will reactivate them. Supplied complete with full instructions. Price £3, plus 2/6 post and ins.

## TRANSISTOR TIMER

All the parts for making transistorised Enlarging or Process Timer with constructional details. £2.10.0, plus 2/6 post and packing

## LATEST AVO TEST METER



Can be yours for only 10/- deposit and 19 payments of 10/- weekly. Like all AVO meters it is a very fine instrument; it has a sensitivity of 10,000 ohms per volt and 19 most useful ranges as follows: d.c. volts 0-1,000 (7 ranges), a.c. volts 0-1,000 (5 ranges), d.c. current 0-1 amp (5 ranges), resistance 0-2 megs (2 ranges) (complete with test leads). Immediate delivery. Cash price £9.10.0

Non-callers please add 3/6 post and insurance

**FREE GIFT.**—All purchasers of the above item this month will receive the M.M. Range Extender which adds capacity 0.1µF in two ranges, inductance 0-100 henrys and decibel —20 to +36


## NOW TWO MODELS TURRET TUNER

Brand new stock, not surplus, with coils for Band I and III, complete with valves. Model 1: i.f. output 33/38 Mc/s, series heaters. Model 2: i.f. output 16-19 Mc/s, parallel heaters, with instructions and circuit diagram, 79/6. With knobs 3/6 extra, post and insurance 2/6

## INTRODUCING . . . THE INDUCTOR 80


80W 5ft fluorescent fitting with a 5-year guarantee—uses the latest type of impregnated induction (choke) control gear—absolutely quiet in operation—all-steel batten type construction stove enamelled white—suitable for direct mounting or for suspending. Undoubtedly the most modern fitting available. Will last a lifetime and will save its cost in lamps and electricity in about 12 months. Two models available—Type A: fixed voltage suitable for 200-240V, price 39/6. Type B: variable voltage suitable for 200-250V, price 45/-. Carriage and insurance up to 150 miles 5/6, up to 250 miles 7/6. Tubes, latest type which give more light for same electricity, daylight or natural to your choice, 14/6 each—no extra carriage if ordered with fitting.

## RECTIFIER BARGAINS

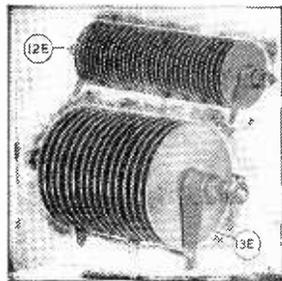

Selenium rectifier type 12. 500V ½A half-wave, easily rebuilt into full wave or multiple type, contains 30 35mm discs. Price 8/6, plus 1/6 post. Type 13. 36V 9A, easily rebuilt into six full wave charger rectifiers suitable for charging 6 or 12V batteries at 3A, contains 24 84mm discs. Real bargain at 19/6, plus 1/6 post. 9/15V 3A transformer to go with these 2/6 each
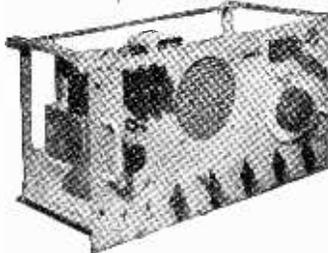
## SHORT WAVE COMMUNICATIONS RECEIVER R208



This is a super short wave receiver covering 5-30 metres (10-60 Mc/s). Uses 6 valves. Has r.f. stage, 2 i.f. stages, b.f.o., etc. Muirhead instrument drive, two internal power packs, mains and battery vibrator pack. Complete with own p.m. speaker. Provision for phones and speaker muting. Complete in metal transit case; size approx. 24" x 18" x 12", weight 70lb. Suitable a.c. mains, 100-250 and 6V battery. In perfect condition, practically

unused. Tested before despatch and guaranteed. Handbook free with each. Price £6.19.6, carriage and insurance 15/-. Or 10/- deposit, plus 15/- carriage, and 15 weekly payments of 10/-

## ELECTRONIC PRECISION EQUIPMENT LTD

For prompt attention post orders should be sent to our Eastbourne address marked Dept. 34

42/46 Windmill Hill  
Ruislip Middlesex  
Telephone RU1slip 5780  
Half-day Wednesday

66 Grove Road  
Eastbourne  
Sussex  
Half-day Saturday

29 Stroud Green Road  
Finsbury Park N4  
Telephone ARChway 1049  
Half-day Thursday

266 London Road  
Croydon  
Telephone CR0Ydon 6558  
Half-day Wednesday

*Technical  
training  
in radio  
television  
and  
electronics  
engineering  
with*

The decision is YOURS. To be a success in your chosen career; to qualify for the highest paid job . . . to control a profitable business of your own. ICS home-study courses put your plans on a practical basis; teach you theory and practice; give you the knowledge and experience to take you, at your own pace, to the top.

Choose the **RIGHT** course,  
RADIO AND TELEVISION  
ENGINEERING • RADIO AND  
TV SERVICING • RADIO SERVICE  
AND SALES • ELECTRONICS •  
VHF/1M ENGINEERING

ICS provides thorough coaching for professional examinations: AMBRIT.IRE, City and Guilds Telecommunications, Radio Servicing; Radio Amateurs PMG CERT. (MARINE).

**THERE ARE ICS COURSES TO MEET YOUR NEEDS AT EVERY STAGE OF YOUR CAREER.**



**The first step towards success is to fill in and post this coupon today:**

In return you will receive the FREE 60-page ICS Prospectus listing technical examinations and their appropriate ICS courses PLUS details of over 150 specialised subjects.

**AN EYE-OPENING SURVEY OF THE ICS WAY TO COMPLETE TECHNICAL TRAINING**

**LEARN AS YOU BUILD**

*Practical Radio Course*

Gain a sound up-to-professional-standards knowledge of Radio and Television as you build YOUR OWN 4 valve TRF and 5 valve superhet radio receivers, signal generator and high-quality multi-tester. At the end of the course you have three pieces of permanent and practical equipment and a fund of personal knowledge and skill . . . ICS Practical Radio courses open a new world to the keen radio amateur.

OTHER ICS COURSES INCLUDE: AGRICULTURE • HORTICULTURE ARCHITECTURE • WOODWORKING • SALESMANSHIP AND SALES MANAGEMENT • ART • PHOTOGRAPHY • MECHANICAL, MOTOR, FIRE AND CHEMICAL ENGINEERING, ETC. A WHOLE WORLD OF SKILL AND KNOWLEDGE FOR THE KEEN STUDENT.



INTERNATIONAL CORRESPONDENCE SCHOOLS  
Dept. 248B International Buildings Kingsway London WC2

NAME . . . . . AGE . . . . .

ADDRESS . . . . .

OCCUPATION . . . . . 9-58

# Build your own HI-FI

— with an  
entirely  
**NEW**  
range of  
Hi-Fi  
units and  
cabinets!



Imagine the pleasure of having this magnificent Hi-Fi equipment in its beautiful contemporary style furniture for your home . . . and experiencing an entirely new realism in sound reproduction. Yet the Emistructor Hi-Fi will save you money and give you all the *extra* fun and satisfaction of building it yourself—and being able to service and maintain it afterwards. Special instruction manuals guide you at each stage and teach you all about the equipment in simple terms as you build. No skill or experience is needed—only a few simple tools.

Emistructor equipment is made to the highest quality standards and is a product of E.M.I. Institutes Ltd.—part of a Company world famous for sound recording and reproducing equipment.

There is a wide variety of equipment and cabinets at different price levels to suit individual tastes and requirements. The range varies from a complete HI-FI installation with separate speaker enclosures to a simple all-in-one compact system for those with more modest requirements. All equipment is suitable for stereo or non-stereo reproduction of records. Full details and complete specifications will be sent with our free Brochure.



Amplifier



Pre-Amplifier



AM/FM Tuner



Tape Recorder



Record Player



Speaker System



Cabinet

**FREE BROCHURE—POST TODAY**

To: "Emistructor," (Dept. H.F. 179)  
43, Grove Park Road, London, W.4.

Please send, without obligation, details of your  
Hi-Fi equipment.

NAME .....

ADDRESS .....

IC. 135

Sent/58

# EMISTRUCTOR

Associated with one of the World's largest recording  
organisations comprising—

**"HIS MASTER'S VOICE"**

**CAPITOL · COLUMBIA**

**PARLOPHONE · MGM · ETC.**

AN ELECTRONIC ORGAN  
FOR THE  
HOME CONSTRUCTOR

By Alan Douglas, M.I.R.E., M.A.I.E.E.  
Here is a do-it-yourself book which gives straightforward instructions for building an inexpensive electronic organ. Compact and easily transportable, the instrument has been specially designed for amateur use in church, hall or home. Detailed step-by-step instructions are given, as well as a complete list of materials and their suppliers. Illustrated with photographs and diagrams. From booksellers. 15/- net.

**PITMAN**

Parker St. Kingsway London WC2

**WALK-AROUND-SHOP  
BARGAINS**

**MAINS TRANSFORMERS.** 230-250 V 50 c/s. Heater 6.3V, 1.5A, 6/6 plus 1/- carr. **Miniature Mains** 230V at 40mA and 6.3V at 1.5A., 12/6, plus 1/- carr. Charging 9V and 17V at 3A, 15/6 p.p. **Mains Isolating** 250V - 220V or 250V - 110-0-110V out. OR double wound auto 250V in 110V out., 5/-, carr. 1/6. **BEAM ROTATOR.** Cowl Gill motors are powerful reversible split field motors with 600 to 1 reduction gears which will operate from any 6 to 30V a.c. or d.c. source. Consumption 3A at 12V. Size 12" long by 3 1/2" dia., 1/2" splined drive. Price 35/- post free with instructions. **12 VOLT SOLENOID.** Powerful solenoid with lever mechanism giving a mechanical advantage of approx. 4:1 (1/2" travel = 3 1/2" arm). Consumption 350mA. Ideal for remote controls, model railways and mechanical indicators. Bargain offer. 3 for 10/- post free. **MICROPHONES.** Acos crystal inserts. 4/6 post paid. American throat microphones type T.S.30, including socket 3/- post paid. Aircrew type electro magnetic microphones with switch, 2/- post paid. Carbon type in black crackle case. 12/6, post paid. **GEIGER MUELLER TUBES.** These low voltage halogen quenched tubes are brand new and manufactured by a well-known company, individually tested and fully guaranteed. Price 55/- each. Send S.A.E. for specification. **PENCIL SOLDERING IRONS.** Genuine SOLON 230/250V 65W pencil bit soldering irons, 16/6 post free. Interchangeable angle bit, 1/6 extra. **CONNECTOR BLOCKS.** G.E.C. 12-way standard "chocolate block" type connectors, 3 for 6/6 post free **ROTARY TRANSFORMER.** Made by Hoover. Input 12V, output 310V 30mA. Size 4" x 2 1/2" dia. 15/- p.p. **PROOPS BROS. LTD.** Open all day Saturday Dept. R, 52 Tottenham Ct. Rd. W1 Hours 9-6 p.m. Thursday to 1 p.m. LAngham 0141



**I.F. Strips  
Power Packs**

**Sound & Vision Strip 10/6.** S/het. Takes 6 EF91, 1 6D2, 1 6F14 (valves 62/- extra). Not tested. Free drawing. Post 2/6.

**Sound & Vision Strip 25/6.** Plessey s/het. Takes 6 6F1, 2 6D2 (valves extra). I.F.s 10.5 Mc/s sound, 15 Mc/s vision. Post 2/6, free drawing.

**12-Channel Turret Tuner £6.17.6.** To fit above, supplied with any two channels (Band I and Band III). With 2 valves thus replacing 2 6F1. Post FREE.

**Timebase 4/9.** Including scanning coils (35 mm will stretch to 38 mm), focus magnet, line o.p. trans. and extras. Less valves. Post 3/6.

**Power Pack & Amplifier 19/6.** A MUST in every workshop. The basis of nearly every experiment or electronic instrument you make. Smoothed h.t. 325V 250mA, I.t.s 4V-6.3V and 4V (centre tapped). Also o.p. stage (pentode) with o.p. trans., less valves. Carr. 5/6

**MAINS POWER TRANSFORMERS**

**15/9.** 325-0-325V 250mA, 4V 5A, 6.3V 5A, 4V 5A (centre tapped), post 3/9. ALSO at 9/9. 350-0-350V 250mA, 22V 3A, 6.3V 4A, 6.3V 0.0A, 4V 2.8A, 4V centre tapped at 3.6A. Post 3/9

**Mains Trans. 5/9.** 280-0-280V 80mA, 6V 2A, 4V 2A, 4V 2A. Drop through type. Post 3/3

**Mains Trans. 3/9.** 350-0-350V 80mA, 4V 5A, 4V 2.5A. Post 2/9

**Mains Auto Trans. 12/6.** 0-205V 225V 245V 300mA. Heaters 6.3V 2.6A, 6.3V 3.6A, 2V 1.4A. Post 3/9

**O.P. Trans. 1/3.** Salvage guaranteed. 2-5 ohms. Standard size. Post 1/-, 20 for £1, post 5/6

**SPEAKERS 5/9  
8" P.M.**

Limited quantity of these modern type speakers. All tested and 'money back guarantee.' They have a slight cone fault that is repaired. Not affecting the quality. Post on 1, 2/6; 2, 3/6



**Focus Magnet 3/9.** Plessey salvage, 35 mm. Permanent magnet. Post 1/9 **Elac Focus Magnet 5/9.** 35-38 mm. Permanent magnet, salvage. Post 1/9. **Frame Output Trans. 3/9.** To match low impedance coils. Post 1/3. **Elac Focus Magnet 12/9.** Brand new. 35-38 mm. Post 1/9. **Visconal Condensers 5/9.** 0.1-7kV and 0.001µF 12.5 working. Post 6d. **Resistors 1/9.** 1 meg, 1 watt, 1% accuracy. Wire wound. Post 6d. **Co-ax Cable 6d.** yard. Good quality. Cut to your required length. Post on 20 yds 1/6, 45/- per 100 yds, post 3/6 **CAR AERIAL 6/9**

Whip antennae. Plated. 50" long, collapsing to 11." 1-hole fixing. Post 1/-

**Ganged Condensers 1/9.** 2-gang and 3-gang 0.0005 (500pF). Salvage, guaranteed. Standard size. Post 1/3 **Rectifiers 2/9.** 250V 100mA. Full or half-wave. Salvage, guaranteed. Post 1/3

**Insulating Tape 1/6.** 75 ft x 1/2" wide in sealed tins. The electrician's friend. Post 9d. Post on 6 tins 2/-

**Solder Reels 1/6.** 60-40, 3-core Ersin. 20 ft on plastic spool. No amateur can be without this. Post 6d.

**Chassis 1/-** each. 6 or 8-valve. Latest type midgeet valve design for a.m. or f.m. NEW. Cadmium plated on s.w.g. steel. 12 1/2" x 7 1/2" x 2 1/2". Post 1/9. Post on 4 3/-; 12 for 10/-, carr. 5/-

**Volume Controls 2/6** doz. Assorted parcel of volume and tone controls. Removed from working sets. Post 1/9

**Cine Film 6d.** roll. Fast, unexposed, 16 mm. Perforations 1 side only. NEG-Ilford. Out-dated, but reports good from sound and silent home cine enthusiasts.

**6d.** for 25 ft spool. Unopened tins of 12 rolls 5/-.

Post on 1 roll 6d. On 1 tin 1/6

**Coil Packs 3/9.** BARGAIN OFFER of 3 w/band coil pack, pair 465 i.f.s., and 2-gang condenser. Printed data. Post 2/3

**P.P. Components Ltd**

(Dept. C.8) Stamp for revised Catalogue  
219 ILFORD LANE ILFORD ESSEX ILF 0295  
Closed Thursday 1 p.m.

## Ask "ARTHURS" First

NOTE NEW ADDRESS AT  
125 Tottenham Court Road  
London WCI  
Close to Warren Street Station

You will have the same service and obtain all your requirements in Radio Components, Electrical Goods, Accessories and Television as previously.

Test Instruments in stock include Avo, Taylor, Cossor and Advance List on request.

VALVE MANUALS AVAILABLE  
Mullard 10/6 Brimar No.7 6/-  
Osram Part 1, 2nd Edition 7/6  
Post and packing 9d. each extra

# Arthurs first

Est.  
1919

Proprietors ARTHUR GRAY LTD

Gray House  
125 Tottenham Court Road  
London WCI  
Telephone EUSton 5802/3/4

## The Teletron TRANSIDYNE

Portable 6-Transistor Superhet  
Receiver with printed circuit

(See leading article in this issue)

Circuit diagram with  
instructions available  
from most advertisers  
in this magazine, 1/-  
post free

## SAM MOZER LTD

288 Hedge Lane London N13

Telephone PALmers Green 1748

Sole Distributors to the Trade

## TV FAULT FINDING

Data Book Series No. 5

### Again Enlarged and Revised



This latest edition now includes, for the first time, information and fault-finding details of both the B.B.C. and I.T.A. transmissions. Completely revised and enlarged, and especially useful in that it is lavishly illustrated by photographs taken from the screen of a television exhibiting the faults under discussion. A comprehensive fault-finding guide is included, and this is cross referenced to the book itself.

OVER 100 Illustrations and Diagrams

NOW 104 pages, high quality paper  
with laminated heavy art  
board cover

PRICE 5s. Available from your usual supplier, or direct Postage 5d.

"... A book that should be in every television dealer's service workshop, and in every home-constructor's, for that matter."

*Journal of the Television Society*

"... The book will undoubtedly be of value to TV service engineers, particularly those who are not fully experienced in translating the appearance of faulty pictures into the necessary adjustments or receiver fault location."—*Wireless and Electrical Trader*.

Published by

## DATA PUBLICATIONS LTD

57 MAIDA VALE · LONDON W9

Telephone CUNningham 6141 (2 lines)

Telegrams Databux London

**The Teletron TRANSIDYNE**  
6-Transistor Pocket Portable



**COMPLETE KIT**  
as specified  
**£11.19.6**  
1/6 postage

Teletron **COMPANION** complete kit including printed circuit **£5.5.0**, postage 1/3

**ELEC-RADIO**

172a BLACKSTOCK ROAD HIGHBURY  
LONDON N5 Telephone CANonbury 1672

**Res/Cap Bridge**

FOR  
**35/- ONLY**

P. & P. 2/-

For checking all types of resistors and condensers

**BUILT IN 1 HOUR!**  
**READY CALIBRATED!!**

Stamp for details of this and other instruments

**RADIO MAIL** Dept. CA Raleigh Mews  
Raleigh Street Nottingham

RADIO AMATEURS . . .

get your Licence in

**Half The Usual Time!**

You must be a good Morse operator!

A "slap-dash" 12 w.p.m. neither satisfies the authorities, yourself, nor your operator friends. Morse operating is an exacting art unless your training is made simple and is based on sound fundamentals. For this reason, the Candler System was invented to take the "grind" out of Code tuition, turning a tricky subject into a pleasurable pursuit.

★ Send 3d. stamp for the "Book of Facts"

**CANDLER SYSTEM CO**  
(Dept. 55 RC) 52b Abingdon Rd London W8  
Candler System Company Denver Colorado U.S.A.

**from one source**

Denco, Repanco, J.B., T.C.C., Woden, Elac, McMurdo, Radiospares, Eddystone, Elstone, Bulgin, Belling & Lee, Henley, Aco. Brown, Mullard, Igranic, Cossor, Taylor, Avo.

Orders dealt with day received

56 page illustrated catalogue No. 11, with 108 photographic illustrations. Over 2,000 new lines by leading makers. 9d. post free.

**SOUTHERN RADIO**  
**and ELECTRICAL SUPPLIES**

SORAD WORKS . REDLYNCH . SALISBURY . WILTS

**DALY**  
**MINIATURE**  
**ELECTROLYTICS**



Actual size H5

Send for descriptive leaflet giving full details of complete new range

**DALY (CONDENSERS) LTD**

West Lodge Works, The Green,  
Ealing, London, W5.

Telephone: EALing 3127/8/9



Let us supply  
**your new**  
**PULLIN**  
SERIES 100  
**MULTI-RANGE TEST SET**  
on easiest of terms

Completely restyled with new Diakon meter cover giving wide angle of vision and very clear scales. Carrying handle and ingenious three-position stand incorporated. Printed circuit gives a rugged accurate instrument. 21 ranges and sensitivity 10,000 ohms per volt. Full data on request.

**CASH PRICE £12.7.6**

Deposit £2.10.0 (delivery by return) and balance by Nine Monthly Payments of £1.4.6.

We also stock the full range of Test gear and instruments by Grayshaw, Avo, Taylor, Advance.

**STOP PRESS** Brand new 1200' PVC recording tape on plastic spools. Boxed. 20/- each plus 1/- post.

**HOME RADIO**  
(MITCHAM) LTD

Telephone  
Mitcham 3282

187 LONDON ROAD • MITCHAM • SURREY



## TELETRON MINIATURE TRANSISTOR 42/-

Superhet coil kit (as illustrated)

470 kc/s I.F. Transformers and Oscillator coil in screening cans  $\frac{3}{4}$ " x  $\frac{1}{2}$ " dia. Dual wave Ferrite rod aerial  $5\frac{1}{2}$ " x  $\frac{5}{16}$ " dia. Designed for the TRANSIDYNE miniature superhet receiver. Descriptive folder with circuit and assembly instructions Price 9d.

## TELETRON Type FX.25

Self-tuned, dual wave  
Ferrite rod aerial. 15/- each




Specified for the "Companion" 3 Transistor regenerative pocket receiver.  
Type 24 Inductor ... .. 3/6 each



## TRANSISTOR I.F. TRANSFORMERS

High Q "potted" construction, with Ferrite screw cores. Mounted in screening cans  $1$ " x  $\frac{3}{4}$ " dia., 6/6 each. Oscillator coil, 6/6. Transistor type Ferrite rod aerial for MW band 10/-. Selective crystal diode coil type HAX, 3/- each. Type HAX.L (for LW band), 3/6. Dual wave TRF coils, type A/HF, matched pair, 7/-, with adjustable iron dust cores.

## FERRITE ROD AERIALS

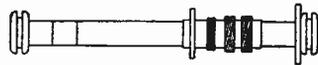

Wound on high permeability Ferroxcube rod. No external aerial required. Full sensitivity. Ideal for battery portable receivers. Medium wave, type FRM  $4$ " x  $\frac{5}{16}$ ", 8/9. Dual wave type FRD,  $8$ " x  $\frac{5}{16}$ ", 12/9. Miniature R.F. Chokes, wound on iron dust cores, with wire end terminations. 2.5 and 5mH, 3/- each; 10mH, 3/6

## BAND III PRE-AMP COIL SET

(as featured in March issue)

Types 20T, 21T and 22T 9/- per set

Send 5d. in stamps for complete data and circuits. All types available from advertisers in this Magazine and local component stockists

## THE TELETRON COMPANY LIMITED

112b Station Road . Chingford . London E4

Telephone SIL 0836

Trade enquiries to sole distributor


S. Mozer Ltd 288 Hedge Lane N13 Telephone PAL 1748 or EDM 7707

# THE **FAMOUS** BENNETT COLLEGE

## can train your mind to **SUCCESS**

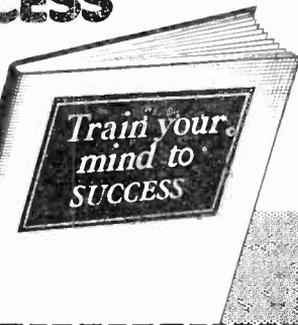**THROUGH PERSONAL POSTAL TUITION**

A **FREE** book vital to your career! Read how the famous Bennett College can help you to success! Send now for this recently published **FREE** book "Train your mind to **SUCCESS**," which tells you about The Bennett College proven success in postal tuition and how it can help you to success in your career.



### WHAT CAREER DO YOU WANT?

Building  
Carpentry  
Commercial Art  
Diesel Engines  
Draughtsmanship  
Electrical Eng.  
Fine Engineering  
Mechanical Eng.  
Quantity Surveying  
Radio Engineering  
Surveying  
Telecommunications  
Wireless Telegraphy  
and Telephony

Accountancy Exams  
Book-keeping  
Civil Service  
Journalism  
Languages  
Mathematics  
Modern Business  
Methods  
Police Methods  
Salesmanship  
Secretarial Exams  
Shorthand  
Short Story Writing  
and many others


**GEN. CERT. of EDUCATION**

**FREE**

To The Bennett College (Dept 1 162N), Sheffield

Please send me, without obligation, a free copy of 'Train your mind to **SUCCESS**' and the College Prospectus on:

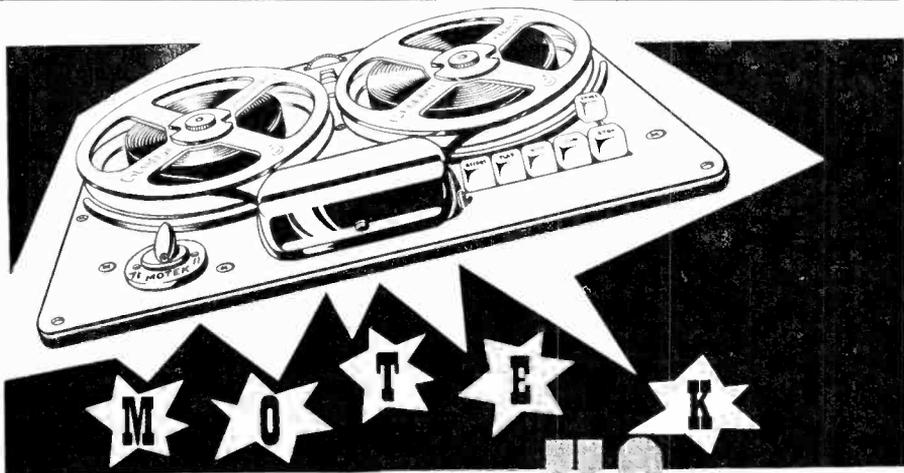SUBJECT.....  
NAME.....  
ADDRESS.....  
AGE (if under 21)..... Please write in **BLOCK** letters



The safety record button is only one of the features which keeps this famous tape-deck way out ahead. It is designed especially to combine all that is best with the minimum of maintenance. Illustrated literature on request. Patents Pending.

## The Five Star Tape Deck

List 21 gns.

### **MODERN TECHNIQUES**

WEDMORE STREET LONDON N19  
DHB/5894

Telephone : ARCHway 3114

# EDDY'S (NOTTINGHAM) LTD

(DEPT. RC) • 172 ALFRETON ROAD • NOTTINGHAM

Telephone NOTTINGHAM 74015

**B.S.R. MONARCH 4-SPEED AUTOMATIC CHANGER.** Complete with high fidelity turnover head H.G.P.37-1. Capacity of 10 records. Plays 12", 10", 7" intermixed in any order, 78, 45, 33 and 16 r.p.m. For a.c. mains 100-250 volts. With full instructions. Special price £6.19.6, post, etc., 5/- . Brand new

**ACOS CRYSTAL MIKES.** List price £2.10.0. Our price 29/11 plus 3/- post. Excellent for tape recorders, baby alarms, amplifiers, etc. Brand new and boxed

**ACOS MIKE INSERTS,** 4/11 each, high quality. Can be used for tape recorders, baby alarms, musical instruments, etc. Post, etc., 8d. extra. Brand new and boxed

1D5	10/-	6F15	9/-	757	9/11	35L6GT	9/11
1H5GT	10/-	6J5G	2/11	7Y4	7/11	35W4	7/6
1N5GT	9/9	6K7G	2/11	10F9	11/6	35Z3	13/6
1R5	7/6	6K8G	7/6	12AH7	7/6	35Z4G	7/6
1S5	7/6	6L6G	6/11	12AH8	9/11	807(B)	3/9
1T4	6/6	6L18	12/6	12K7	7/6	807(USA)	
3Q5GT	9/6	6Q7G	8/6	12Q7	7/6		5/6
5U4G	6/6	6SK7GT	6/-	12SH7	5/6	954	1/6
5Y3G	8/-	6SN7GT	5/9	12SK7	7/6	955	3/11
5Z4G	9/-	6V6G	5/11	14S7	15/6	956	2/11
5Z4M	10/-	6X4G	5/11	25A6G	12/11	AZ1	12/11
6B8G	2/11	6X5GT	6/6	25L6G	9/11	AZ31	12/11
6F1	13/11	7C6	8/-	25Z4G	9/11	CY31	12/11
6F13	12/6	7H7	8/-	35A5	10/6		

**MIDGET BATTERY ELIMINATORS** to convert all types battery portables to mains operation, 57/6 plus 2/6 post. Smaller than h.t. battery alone. Size 3.7" x 2.5" x 1.8". Please state make and model no. Brand new and boxed

**ACOS CRYSTAL TURNOVER PICK-UPS** (2 sapphire styli), 29/11, post 2/6 extra. Brand new and boxed

**MORSE TAPPERS.** Good quality, 3/6 each, post, etc., 9d. extra

**25 x 25 CONDENSERS** (midget), 1/3. Brand new. Post and packing 4d. each extra

DAF96	9/6	ECL80	13/6	EZ81	9/11	PY81	8/6
DF96	9/6	EF40	13/11	GZ32	12/6	PY82	8/6
DH77	7/11	EF41	9/6	KT33C	8/6	TDD4	12/6
DL96	9/6	EF42	12/6	KT66	15/-	UCH42	8/11
DM70	7/11	EF80	8/-	L63	6/-	UAF42	10/6
EB34	1/11	EF91	7/6	PCC84	9/-	UF41	8/-
EB91	5/11	EF92	6/6	PCF80	10/-	UF42	14/6
EBF80	9/11	EL41	10/6	PCL83	15/6	UL41	9/6
ECC81	8/-	EL42	10/6	PL38	19/6	UL84	9/6
ECC82	8/-	EL91	5/-	PL81	16/-	UY85	8/11
ECC83	8/11	EL84	9/11	PL82	9/6	VT52	2/11
ECC84	8/11	EY86	14/6	PL83	10/6	Z63	10/6
ECC85	8/11	EZ80	8/3	PY80	8/3	Z66	18/6

ANY PARCEL insured against damage in transit for only 6d. extra per order. All uninsured parcels at customer's risk

**SURPLUS, NEW AND GUARANTEED VALVES**

All tested before despatch  
C.O.D. or C.W.O. only

Postage and packing 6d. per valve extra. Over £3 Free.

S.A.E. with enquiries

## ★ VALVES NEW TESTED AND GUARANTEED ★

1R5	8/-	6SL7GT	8/-	DH77	8/-	EF85	10/6
1S5	7/6	6SN7GT	8/6	DK91	8/-	EF91	7/-
1T4	7/6	6V6G	7/6	DK92	9/-	EF92	5/6
3S4	7/6	6V6GT	7/6	DK96	9/-	EK32	8/6
3V4	8/-	6X4	7/6	DL92	7/6	EL41	10/-
5U4G	8/6	6X5GT	7/6	DL94	8/-	EL84	10/6
5Z4G	9/6	12AT7	9/-	DL96	9/-	EL91	7/6
6AM6	7/-	12AU7	9/-	EA50	1/6	EY51	11/6
6AL5	6/6	12AX7	9/-	EB91	6/6	EZ35	8/-
6AT6	8/-	12K8GT	13/6	EBC41	8/-	EZ40	8/-
6B8G	7/6	12K7GT	8/6	EFB80	10/-	KT33C	9/6
6BA6	8/6	12Q7GT	8/6	ECC81	10/6	PCF82	11/-
6BE6	7/6	35Z4GT	8/6	ECC84	11/6	PL82	10/6
6BR7	10/6	35L6GT	9/6	ECH82	11/-	PY81	9/-
6BW6	8/6	53K U	11/6	ECH81	10/6	PCC84	10/6
6J5G	5/6	807	6/9	ECH42	10/-	U76	8/6
6J5GT	6/6	5763	10/6	ECL80	13/6	UBC41	10/-
6I7GT	8/6	DAF91	7/6	EF36	7/6	UCH42	10/-
6K7G	5/6	DAF96	9/-	EF37A	14/6	UF41	10/-
6K8G	9/6	DF91	7/6	EF39	5/6	UL41	10/-
6L6G	9/6	DF96	9/-	EF41	10/-	UY41	8/-
6Q7GT	8/6	DH76	8/6	EF80	9/6	W76	8/6

**Matched Pairs.** EL84, 23/-; 6V6G & GT, 17/-; 6BW6, 18/-; KT33C, 19/6; 807 14/6 pair

1R5, 1T4, 1S5, 3S4, 3V4, DK91, DK92, DF91, DAF91, DL92, DL94, any four, 27/6 per set

**P.P. Op. Transformers.** MR 3-15 ohms for EL84, 6V6, 6BW6, etc., 18/6; Op. Pen. 50mA, 5/6; 30mA, 4/6

**Volume Controls.** All valves, long spindle 1/5 3/-, s.p. 4/-, d.p. 4/9, ext. spkr. control 3/-

**W.W. Pots.** Pre-set 3/-; 3W long spindle 5/6, s.p. 6/6

**P.M. Speakers.** 3 ohm. 5" 16/6, 6 1/2" 17/6, 8" 21/-, 10" 25/-, 12" 30/-

**Coaxial Cable.** 75 ohm 1/2" stranded, 8d. yd; semi-air spaced, 9d. yd; screen cable single and twin, 9d. yd

**Coaxial Plugs** 1/- each; **Sockets** 1/- each

P. and p. 9d. to £1; 1/6 to £2; over £2 post free. C.O.D. 2/6

**C.R.T. Isolation Transformers** with 25% boost. Low capacity, a.c. mains 200/240V. For 2V, 4V, 63.V and 13V tubes. All 12/6 each; 1-1 for H.C. shorts 10/6

**Valueholders.** 4, 5, 7 pin English and U.S.A. B7G, B9A, 1.0 Mc. B8G, 9d. each; B7G, B9A with screening can, 1/6; B12A, 1/3. Aladdin formers 1/2" with core, 8d. each

**Scotch Boy Recording Tape,** 1,200ft reels, 27/-

**Jack Plugs,** miniature standard, 3/-; **Sockets** 3/-

**2-Gang Condensers,** .0005 small size, 7/6

**I.F. Transformers,** 465 kc/s, small size, 7/6 pair

**Capacitors,** small mica, 5% 1pF to 100pF, 8d.; 120pF to 1,000pF, 9d.; 1,000V wkg. .01, .0015, .0025, .004, .005, 1/- each

**Crystal Diodes,** G.E.C., 1/6 each

**Headphones,** lightweight, 4,000 ohm, 16/6 pair

**Ceramic Capacitors,** close tol. 500V for V.H.F., 9d.

**Paper Capacitors,** tubular, .01, 1,900V, 1/-; 0.1 to 1.5 500V, 10d.

**Paper Blocks,** 4uF, 1,000V wkg., 3/6

**Rectifiers,** contact cooled, 250V 50mA, 7/6; 85mA, 9/6

**Reaction Condensers,** .0001, .0003, .0005, 4/6 each

**Heater Trans.** 200/240V, 6.3V, 1.5A, 7/6

**Resistors,** 1/2 and 1/4W, insulated, 4d. and 6d.; 1W, 8d. 6W W.W., 1/-; 10W, 2/-

**Electrolytics.** Wire ends. 25/25V, 1/6; 50/50V, 2/-; 12/50V, 9d.; 8/450V, 2/-; 16/450V, 2/9; 16/500V, 3/6; 32/450V, 4/-; 8+8/450V, 4/6; 8+16/450V, 4/6; can types: 16/450V, 3/6; 16+16/500V, 6/-; 32/500V, 6/6; 32/450V, 6/6; 20+20/450V, 4/6; 64+120/275V, 7/6

**Wavechange Switches,** midget: 1p 12V, 2p 6V, 3p 4W, 4p 3W, 4p 2W, long spindles, 4/6


**Toggle Switches.** QMB, s.p.s.t., 2/-; s.p.d.t., 3/3; d.p.s.t., 3/6; d.p.d.t., 4/-

**Chokes,** 80mA, 15H, 8/6; 100mA 10H, 10/6; 150mA 10H, 14/6

**Solder, Multicore,** 4d. yd; **Sleeving** 2mm, 3d. yd

## R. COOPER G8BX 32 SOUTH END CROYDON SURREY CROYDON 9186

## TERMS AVAILABLE

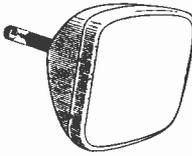

### REGETTERED IMPROVED VACUUM TV TUBES

**17" £7.10.0 12 MONTHS GUARANTEE 14" £5.10.0**

6 months full replacement, 6 months progressive. Made possible by the high quality of our tubes. Ins. carr. 15/6. 9", 10", 14", 15" and 16" round tubes. Our special offer of these sizes £5; 12" TV Tubes £6. Three months guarantee on round tubes. Ins. carr. 15/6 **14" RECTANGULAR TV TUBES** with burns 30/-. Ideal as a stand-by or testing. Carriage 10/-


### 17" TV Chassis Tube and Speaker £19.19.6

17" Rectangular Tube on modified chassis. Supplied as single channel chassis covering B.B.C. channels 1-5 or incorporating Turret Tuner which can be added as an extra, at our special price to chassis purchasers 50/-, giving choice of any 2 channels (B.B.C. and I.T.A.). Extra channels can be supplied at 7/6 each. I.F.s 10.5-14 Mc/s. Chassis size 12" x 14½" x 11". Less valves. Similar chassis were used by well-known companies, because of their stability and reliability. With tube and speaker, £19.19.6. With all valves £25.19.6. Complete and working with Turret Tuner £28.9.6. 12 months guarantee on the tubes, three months guarantee on the valves and chassis. Ins. carr. (including tube) 25/-


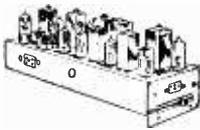
### BEAUTIFUL EXTENSION SPEAKERS—29/9

Fitted with 8" p.m. speaker, W.D. or Goodmans, of the highest quality. Standard matching to any receiver (2-5 ohms). Switch and flex included. Unrepeatable at this price. Money back if not completely satisfied. Ins. carr. 3/6 **8" p.m. SPEAKERS 8/9**. Those extra speakers are required for STEREPHONIC SOUND. With o/p transformer fitted, 10/-, post 2/9



### PLESSET SOUND AND VISION STRIP—25/6

Superhet. Tested. I.F.s 10.5 Mc/s sound, 15 Mc/s vision. 8 valve basis (6 6F1's and 2 6D2's, not included). Size 8½" x 5" x 4½" high. Post and packing 2/6.


The Turret Tuner plugs directly into this chassis. Complete vision strip. Less valves. Not tested. Drawings free. Postage 2/6.

**POWER PACK AND AMPLIFIER 19/6**. Output stage 6V6 with o/p trans. Smoothed h.t. 350V 250mA, 6.3V at 5A, 22V at 3A, 6.3V at 4A centre tapped. Less valves. Free Drawings. Ins. carr. 5/6

**POWER PACK AND AMPLIFIER 19/6**. Output stage PEN45, o/p trans., choke. Smoothed h.t. 325V at 250mA, 4V at 5A, 6.3V at 5A, 4V at 5A centre tapped. Less valves. Ins. carr. 5/6

**TIMEBASE 4/9**. Complete, including scanning coil, focus unit, etc. Less valves. Post and packing 2/6 **HEADPHONES 1/9**. Single earphone and band, CL-R type. Ideal for crystal sets, extension on radio. Post 1/3.

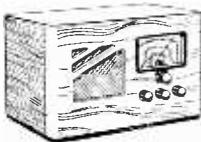**CHASSIS 1/-** each. 6 or 8 valve. Latest type midge valve design for a.m. or f.m. Brand new cadmium plated. Size 12½" x 7½" x 2½". Post 1/9. 4 for 4/-, post 3/-; 12 for 10/-, carr. 5/-



### HOME RADIO 79/6

5 valve (octal) superhet. 3 waveband receiver. Can be adapted for your gram. p.u. at a little extra cost. Two a.c./d.c. sizes: 9½" x 18½" x 11½" and 9" x 20½" x 12". Wooden cabinets. Ins. carr. 4/6. Please state size required when ordering.

**MAINS TRANSFORMERS 9/9**. 350-0-350V 250 mA, 6V at 5A, 4V at 4A, 22V at 6A, extra winding for 2V or 4V tubes. Primary 200-250V 50 c/s. Postage and packing 3/9

**MAINS POWER TRANS. 15/6**. 350-0-350V 250 mA, 6V heater at 5A, 4V at 5A, 4V centre tapped. Drop through type. Primary 200-250V (4½" x 5" x 5"). Post 3/9

**MAINS TRANS. 3/9**. 350-0-350V 80mA, 4V, 4V heaters. 200-250V prim. Post 2/3

**MAINS TRANS. 5/9**. 280-0-280V 80mA, 6V, 4V heaters. 200-250V prim. Post 2/3

**O.P. TRANS. 1/3**. Standard size. 2-5 ohms. Post 1/-, 20 for £1, post 5/6

**MAINS TRANS. 12/9**. 425V 300mA. Single secondary. 6.3V at 12A, 6.3V at 0.6A. 200-250V screened primary. Post and packing 3/6

**TV MASKS 14/9**. 17" brand new. Grey or white plastic. Good quality. Postage 2/-

**COAX CABLE 6d. yd.** Good quality, cut to any length. 1/6 post on 20 yds. 45/- per 100 yds, post 3/6 **INSULATING TAPE 1/6**. Finest quality, 75" x ½" wide. Post 9d.


**GANG CONDENSERS 1/9**. 2 and 3 gang, 500pF. Standard salvaged. Tested. P. & p. 1/3


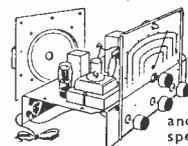
### SOLO SOLDERING

**TOOL 19/6**. 110V or 6V (special adaptor for 200/240V 10/- extra). Automatic solder feed, including a 20ft reel of ERSIN 60/40 solder and spare parts. It is a tool for electronic soldering or car wiring.


Revolutionary in design. Instantly ready for use and cannot burn. In light metal case with full instructions for use. Post 2/9


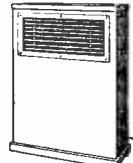
### SUPER CHASSIS 99/6

5-valve superhet chassis, including 8" p.m. speaker and valves. Four control knobs (tone, volume, tuning, w/ change switch). Four w/bands with position for gram, p.u.

and extension speaker. A.C. Ins. carr. 5/6



### ELECTRIC CONVERTER HEATER 99/6

A.c./d.c. Switched for 1 or 2kW. Illuminated grille. Size 26" x 18" x 7½" deep. Ins. carr. 10/6

Send for FREE 1958 Catalogue

Liverpool St. to Manor Park Stn. 10 mins.


OPEN SATURDAY ALL DAY THURSDAY CLOSED 1 p.m.

**DUKE & CO** (Dept. 1) 621/3 ROMFORD ROAD MANOR PARK EI2 Telephone ILF 6001/3

# TRANSISTOR NEWS FROM HENRY'S RADIO

ANNOUNCING THREE COMPLETELY NEW EASY-TO-BUILD POCKET TRANSISTOR RECEIVERS

## THE MINOR (Supersedes Mini-2)

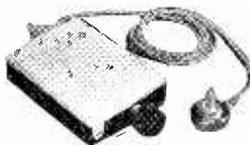

- ★ Size 3" x 2" x 1/2"
- ★ Less than 2 oz. weight
- ★ Variable tuning over medium waves
- ★ Three stage reflex circuit
- ★ No aerial (in areas of reasonable reception)

- ★ Economical (less than 1mA)
- ★ Easy to build
- ★ Drilled and mounted chassis
- ★ May be built within half an hour
- ★ Complete layout diagrams

Complete set of components can be supplied for

**52/6** post free

All parts sold separately

Circuit diagram and shopping list FREE

CALL AND HEAR DEMONSTRATION MODEL

## THE MAJOR (Supersedes Homelight 2 and 3)

### STAR FEATURES

- ★ Variable tuning over medium waveband
- ★ Home, Light and Third programmes
- ★ Foreign stations (in areas of reasonable reception)
- ★ Drilled and mounted chassis
- ★ Four-stage reflex circuit
- ★ Highly efficient
- ★ No aerial or earth
- ★ Economical (1 1/2 mA)
- ★ May be assembled within an hour
- ★ Complete layout diagrams



We can supply all items including battery, case and personal earphone for **72/6** post free

All components sold separately

Circuit diagrams and shopping list FREE

CALL AND HEAR DEMONSTRATION MODEL

SEE NEXT MONTH'S EDITION FOR FULL WRITE-UP


## TRANSISTORS

JUNCTION TYPE P-N-P

RED SPOT 800 kc/s Audio Amp. 30mW diss	7/6
WHITE SPOT 2.5 Mc/s c/o Osc./mixer R.F. and I.F. Amp. ... ..	15/-
GREEN/YELLOW 500 kc/s Audio Amp. 100mW diss. ... ..	7/6
RED/YELLOW 1.8 to 6 Mc/s R.F. Osc./mixer	15/-
<b>MAZDA TRANSISTORS</b>	
XA102 8 Mc/s c/o Osc./mixer, R.F. Amp. ...	40/-
XA101 4 Mc/s c/o R.F. and I.F. Amp. ...	35/-
XB102 600 kc/s Audio Amp. ... ..	21/-
XB104 800 kc/s amplifier ... ..	18/-
XC101 for up to 325mW Audio ... .. pair	60/-
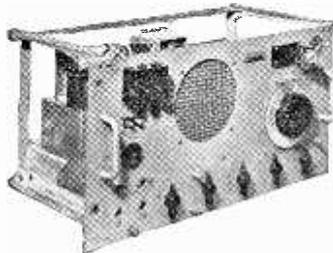
## SPUTNIK-SPECIAL

SHORT-WAVE RECEIVER 10-60 MC/S (5-30 Metres) RECEPTION SET TYPE 208



Complete with 6 valves, 2 6K8G, 2 EF39, 6Q7G and 6V6G. Internal mains power pack and 6V vibrator pack. Built-in 6 1/2" speaker. Muirhead slow-motion drive. B.F.O. and R.F. stage. I.F. freq. 2 Mc/s. Provision for phones and muting and 600 ohms. Input 110/250V a.c. 6V vibrator pack included for battery operation. All sets in new condition and air tested. £6.19.6 carr. 15/6


**NOW!** with stamped-out chassis and mounting brackets for aerial and battery.

Free colour code chart with every "EAVESDROPPER" "EAVESDROPPER"
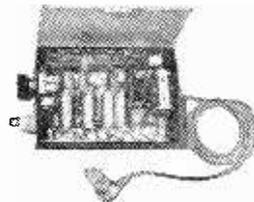
### THREE-TRANSISTOR POCKET RADIO

(No Aerial or Earth required)

Medium wave, Variable tuning. Total cost, as specified, including Transistors, Transformers, Coils, Condensers and Battery, etc., with circuit and plastic case. All items sold separately. 70/- POST FREE. With Min. Hearing Aid **86/-**



TRANSISTOR BASES ... .. 9d. each

## Mini-7 Pocket Transistor Portable

Seven-transistor Superhet, supplied with Plastic Case Size 5 1/2" x 2 1/4" x 1 1/4" and all Components as listed for **£9.19.6** P.P 2/6

All components sold separately. Send 1/6 for Plans and Price List

### TRANSISTOR SIGNAL TRACER

Complete Kit with 2 Transistors, components, phones, with circuit and plastic case ... .. 37/6

### PUSH-PULL AUDIO AMPLIFIER

An ideal miniature for transistor amplifier for baby-alarms, low volume crystal pick-ups and microphones. Output approx. 250mW from 4 1/2 volt battery. Cost of components less speaker, 69/6 post free. 325mW version 40/- extra

We stock transistors and components from the following manufacturers: Ediswan-Mazda, Ardente, Repanco, Telatron, Jackson Bros., G.B. Electrical, Hunts, B.T.S., etc. Send stamp for free list.

# Teletron "TRANSIDYNE" Superhet

## Six-Transistor Pocket Radio

As described in this issue

**CAN BE BUILT FOR £11.19.6**

### SPECIAL FEATURES

- T.C.C. Printed Circuit
- Medium and Long Waves
- Six Selected Transistors
- All Modern Components carded with Values shown
- Rola 2½" Speaker
- Attractive Plastic Case size 6¼" x 3½" x 1 11/16"
- Powered by two No. 8 Batteries
- Total weight 20 oz

This set is truly recommended as an ideal pocket portable containing all the latest features, giving not only simplicity in construction, but when built is really sensitive and selective, bringing in a host of foreign stations.



**ALL COMPONENTS FOR CONSTRUCTION, INCLUDING CABINET, CAN BE SUPPLIED FOR**

**£11.19.6 P.P. 2/6**

All parts sold separately. Send 9d. for Circuit, Plans and Prices  
**CALL & HEAR DEMONSTRATION MODEL**


**NOW!** COMPLETELY NEW CABINET IN VARIOUS CONTEMPORARY COLOURS

# The "TRANSISTOR - 8"

Push-Pull Portable Superhet

## COMBINED CAR RADIO & PORTABLE

**TWO SETS FOR PRICE OF ONE**

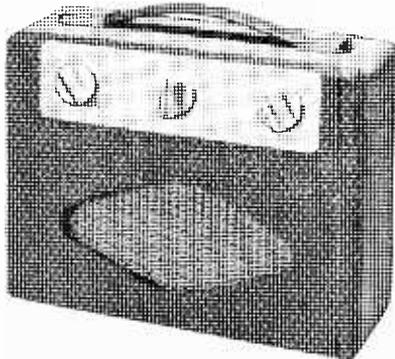

This Portable 8-Transistor Superhet is tunable for both Medium and Long Waves and is comparable in performance to any equivalent Commercial Transistor Set. Simplified construction enables this set to be built easily and quickly into an attractive lightweight cabinet supplied.

### TEN STAR FEATURES

- ★ 8 specially selected Transistors
- ★ 250 Milliwatts output push-pull
- ★ Medium and Long Waves
- ★ Internal Ferrite Rod Aerial
- ★ Highly sensitive
- ★ Drilled Chassis 8½" x 2½"
- ★ Point to point wiring and practical layout
- ★ Economical. Powered by 7½V battery
- ★ Ideal as a car radio
- ★ Attractive lightweight contemporary case

Send stamps for Instruction Booklet

All components as specified can be supplied at an inclusive price of **£11.10.0** p.p. 2/6

Car radio conversion components 8/- extra

All components sold separately

N.B.—Pair of XC101's for larger output supplied at additional cost of 40/- Call and hear demonstration model

**SEND 3d. STAMP FOR COMPLETE SET OF FREE TRANSISTOR CIRCUITS AND NEW TRANSISTOR COMPONENTS LIST**

**HENRY'S RADIO LTD • 5 HARROW ROAD • LONDON W2**

Telephone PADdington 1008/9

**FULL DISCOUNTS ON TRANSISTORS AND COMPONENTS TO THE TRADE**



Our specialised buying knowledge and reputation ensure a square deal and enables us to

**offer the best for your money!**

**BAND III TV CONVERTER**  
180 Mc/s—205 Mc/s

Suitable London, Birmingham, Northern, Scottish, Welsh & I.O.W. ITA transmissions  
**Mk. 2 Model.** Latest Cascade circuit using ECC84 and EF80 valves giving improved sensitivity (12 dB) over standard circuits, built-in power supply a.c. 200-250V. Dimensions only 6½" x 3", ht. 4". Simple and easy to fit—only external plug-in connections. Wired, aligned and tested ready for use. State channel required. Guaranteed. Bargain offer—good results or full refund, only **£3.19.6** Carr. and pkg. 2/6

Band I/Band III changeover switch and B.B.C. aerial socket can now be fitted and wired to the above converter for 8/- extra

**R.E.P. MINI-7.** Kit of parts for this popular pocket transistor portable, 9½ gns., p. and p. 2/6

**CONDENSERS.** Mica or S. Mica. All pref. values. 3pF to 680pF, 6d. each. Ceramic types, 2.2pF to 5,000pF, 9d. each. Tubulars, 450V, Hunts and T.C.C. 0.0005, 0.001, 0.005, 0.01 and 0.1, 350V, 9d.; 0.02, 0.05, 0.1, 500V Hunts, T.C.C., 1/-; 0.25 Hunts, 1/6; 0.5 Hunts, 1/9; 0.001 6kV T.C.C., 5/6; 0.001 20kV T.C.C., 9/6

**RESISTORS.** Pref. values 10 ohms 10 megohms, 20% col., ¼W, 3d.; ¼W, 5d.; 1W, 6d.; 2W, 9d.; 10% h-stab., ¼W, 5d.; ½W, 7d.; 5% tol., ¼W, 9d.; 1% h-stab., ¼W, 1/6

**PRE-SET W/P POT.** TV knurled slotted knob type. 25 ohms to 30,000 ohms, 3/-; 50,000 ohms, 4/-; 50,000 ohms to 2 Megohms (carbon), 3/-

**S.T.C. RECTIFIERS.** E.H.T. types, K3/25 2kV, 5/-; K3/40 3.2kV, 6/9; K3/45 3.6kV, 7/3; K3/50 4kV, 7/9; K3/100 8kV, 13/6, etc. Mains types: RM1 125V 60mA, 4/9; RM2 125V 100mA, 5/6; RM3 125V 120mA, 7/6; RM4 250V 250mA, 16/-; RM4B type 250V 275mA, 17/6, etc.

**LOUDSPEAKERS.** P.M. 3 ohm, 2½" Elac, 16/6; 3½" Goodmans, 18/6; 5" R. & A., 17/6; 6" Celest., 18/6; 7" x 4" Goodmans, 18/6; 8" Rola, 20/-; 10" R. & A., 25/-

**SPEAKER FRET.** Expanded bronze anodised metal; 8" x 8", 2/3; 12" x 8", 3/-; 12" x 12", 4/6; 12" x 16", 6/-; 24" x 12", 9/-, etc. **TYGAN FRET** (Murphy pattern): 12" x 12", 2/-; 12" x 18", 3/-; 12" x 24", 4/-, etc.

**RECORD PLAYER CABINETS**

Contemporary style rexine covered cabinet in two-tone fawn and brown. Size 18½" x 13½" x ht. 8½", fitted with all accessories, including speaker baffle-board and plastic fret. Space available for all modern amplifiers and auto-changers, etc. Uncut record player mounting board 14" x 11". Cut mounting boards available

**Cabinet Price £3.3.0** Carr. and ins. 3/6

**2-VALVE AMPLIFIER Mk. 1.** 200/250V a.c. modern circuit with high gain EL84 output and double wound mains transformer, variable tone and volume controls, wired and tested with 6" speaker and o/p trans., complete with knobs and drilled ready to fit baffle-board in above cabinet. Only **£3.12.6**. Carr. and pack. 2/6

**2-VALVE AMPLIFIER Mk. 2.** 200/250V a.c. Specification as above but a higher fidelity and greater output (approx. 3 watts) is obtained by using latest twin stage triode-pentode valve ECL82 and negative feedback tone control. Complete wired and tested as above, **£3.19.6**, carr. and pack. 2/6

We can only show a small selection from our vast stocks in this advert. Write now for full Bargain Lists, 3d.

**RECORD PLAYER BARGAINS**

**SINGLE PLAYERS.** 4-speed BSR (latest model, TU9), 92/6; 4-speed **COLLARO JUNIOR**, £4.10.0; 4-speed **GARRARD** (4 S.P.), £7.5.0, carr. & ins. 3/6

**AUTO CHANGERS.** Price reductions, 4-speed BSR (UA8), £7.19.6, 4-speed **COLLARO**, £7.19.6; 4-speed **GARRARD** (RC120/4H/2), £10.5.0, carr. and ins., 4/6. All above models brand new and guaranteed. Fitted latest style lightweight Xtal P.U. with turnover head and twin sapphire styli

**VOLUME CONTROLS**

Log. ratios, 10,000 ohms—2 Megohms. Long spindles. 1 year guarantee. Midget Edison type.  
No Sw. D.P.Sw.  
3/- 4/9

Linear Ratio, 10,000 ohms—2 Megohms. Less switch, 3/-, each. **Coax Plugs**, 1/- **Coax Sockets**, 1/-, **Couplers**, 1/3 **Outlet Boxes**, 4/6

**80 ohm cable COAX**

**STANDARD** ¼" diam. Polythene insulated. Grade "A" only. 8d. yd.

**Special.** Semi-air spaced polythene. 80 ohm. **Coax** ¼" diam. Stranded core. Losses cut 50%. Ideal Band III, 9d. yd

**C.R.T. HEATER ISOLATION TRANSFORMERS.**

New improved types—mains prim. 200/250V tapped. All isolation transformers now supplied with alternative no boost, plus 25%, and plus 50% boost taps at no extra cost, all in one transformer. 2V 2A type, 12/6; 6.3V 0.6A type, 12/6; 10.5V 0.3A type, 12/6; 13V 0.3A type, 12/6. P. and p. 1/6 Other voltages in course of production. Small size and tag terminated for easy fitting **L.F. CHOKES**—10H 65mA, 5/-; 15H 100mA, 10/6; 10H, 120mA, 10/6; 20H 150mA, 15/6

**OUTPUT TRANSF.**—Standard pentode, 4/6; push-pull 12 watt, 13/6. Small pentode, 3/9. Midget battery pentode (15A, etc.), 4/6

**ELECTROLYTICS—ALL TYPES—NEW STOCK**

Tubular—Wire Ends	Can Types, Clips 3d. each
25/25V, 50/12V	1/9 8+8/500V Dub. 4/6
25/50V T.C.C.	2/- 8+16/450V Hunts 5/-
50/50V, 4/500V	2/- 16+16/450V T.C.C. 5/6
100/25V, 2/450V	2/- 32/350V B.E.C. 4/-
8/450V T.C.C.	2/3 32+32/275V Hunts 4/6
8+8/450 B.E.C.	4/6 32+32/450V T.C.C. 6/6
8+16/450V T.C.C.	5/- 200/350V B.E.C. 8/6
8/500V Dub.	3/- 150+200/275V 12/6
16/450V B.E.C.	3/6 60+250/275V 12/6

**MIDGET TRANSISTOR TYPES.** 2½F, 4½F, 8½F, 6V, 3/6; 6½F, 10½F, 16½F 3V, 3/6; 32½F ¼V, 3/6

**8" P.M. SPEAKER** (3 ohms)

Ex-Mfrs. units: Rola, W.B., Celestion, etc. All reconditioned and guaranteed. Ideal ext. unit. Bargain, 7/6, carr. 1/6. Ditto with O/P trans. 9/6

**VALVES—NEW BOXED—ALL GUARANTEED**

1R5, 1T4, 7/6; 1S5, 1S4, 7/6; 3S4, 3V4, 9/-; 5Z4, 9/6; 6AT6, 8/6; 6K7, 6/6; 6K8, 8/6; 6Q7, 8/6; 6SN7, 8/6; 6V6, 7/6; 6X4, 7/6; 6X5, 7/6; 7C5, 9/-; 7Y4, 8/6; DAF96, 9/-; DF96, 9/-; DK96, 9/-; DL96, 9/-; 35L6, 10/6; EABC80, 9/6; EB91, 6/6; EBC41, 10/6; EVC33, 8/6; ECC84, 12/6; ECH42, 10/6; ECH81, 10/6; ECL80, 12/6; EF41, 10/6; EF80, 10/6; EF86, 13/6; EP91, 8/6; EY51, 12/6; EZ40, 8/6; EZ80, 8/6; MU14, 9/6; PCC84, 10/6; PCF80, 10/6; PCF82, 10/6; PCLB3, 12/6; PL81, 14/6; PLB2, 10/-; PLB3, 11/6; PY80, 9/6; PY81, 9/6; PY82, 8/6; U22, 8/6; U25, 12/6; UY41, 8/6

**SPECIAL**—1R5, 1T4, 1S5, 1S4 or 3S4 or 3V4 per set 27/6

Hours 9 a.m.—6 p.m., 1 p.m. Wed.



**RADIO COMPONENT SPECIALISTS**

70 Brigstock Road Thornton Heath Surrey Telephone THO 2188  
Terms: C.W.O. or C.O.D. Post and packing up to ¼lb 7d., 1lb 1/1, 3lb 1/6, 5lb 2/-, 10lb 2/9

## SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted at 3d. per word, including address, minimum charge 2/- . Trade advertisements will be accepted at 9d. per word, minimum charge 6/- . If a Box Number is required, an additional charge of 2/- will be made. Terms: Cash with order. All copy must be in hand by the 12th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of advertisers.

### PRIVATE

**WAVE METER** Type 1239, cal. 41.5 Mc/s to 51 Mc/s. Tun. ind. 250V, £3 10s. Wave meter Type CW-60AMB. Range 171.5 to 233.5 Mc/s. 115V input, offers? M.C.R.1, all coils, phs. mains unit, £5 10s.—Bishop, 64 Kippen Street, Glasgow N.2.

**ONE R3H18, TWO VCR97's**, two Indicators, e.h.t. trans. for VCR97, new. One new 1355 all valves with one copy Data Book No. 4, *Inexpensive Television*. S.A.E.—C. Coleman, Upper Ventnor, I.O.W.

**CR500 COMMUNICATIONS RECEIVER**. Lately checked by makers. Owner going abroad shortly. Best offer around £20 secures.—Boyd, 36 Egerton Gardens, Chelsea, S.W.3.

**FOR SALE**. Stromberg-Carlson amplifier with auto-transformer, £11. HRO receiver, £5. Pre-amplifiers, communications sets, valves, CRT's, etc., S.A.E. for list.—Box No. E.179.

**RADIO CONSTRUCTOR** Nov. 1956 to July 1958, 15s. Partridge Williamson output transformer with matched pair KT66's, £4. Power pack for same, £3. New ECL80, 8s. B.J. arm, 25s. Pre-set M.W. chassis, 25s.—9 Brenda Crescent, Thornton, Liverpool 23.

**TRIPLETT 1632 SIGNAL GENERATOR**, 100 kc/s—120 Mc/s, xtal check, r.f. level meter, £13. BCR139A tube in case, suit oscilloscope, 15s. Wave-meter W1649, 140-240 Mc/s, xtal check, 30s. A.C. power pack for same, 30s. D.C. motor generator, 6.5V to 20V and 300V, 30mA, 10s. Power pack 350V 200mA, 6.3V 5A, ex-modulator 67, 15s.—Meekums, 1 Clinton Road, London, N.15.

**TRANSISTOR-8**, built, tested, unused, less transistors and speaker, £9 12s. 6d.—Egan, 43 Hamilton House, Hogarth Lane, Chiswick, W.4.

**FOR SALE**. Repanco "Transeven" pre-set M/L wave 7-transistor superhet portable, complete, working, 10 gns. Post free.—Folds, "Maidwin," Lye Hill, Breachwood Green, Hitchin, Herts.

**OSCILLOSCOPE**, American, 3in tube, timebase 60 kc/s, good condition, £10. Power supply, 1,000V, 250mA, relay controlled. Canadian manufacture, £9. 64in speaker in communications style metal case, with transformer, 30s. 400 c/s audio oscillator, 3 EF91, 30s. New matched pair OC72, 17s. 6d. 6BA6, 4s. 12AT7, 4s. Please add postage.—Box No. E.180.

**COSSOR DOUBLE BEAM OSCILLOSCOPE** Type 339, cost £30, accept £20.—81 Eastfield Road, Waltham Cross, Herts.

**EDDYSTONE 358**, complete, £15 o.n.o.—R. C. Lambert, 1A New Broadway, Ealing, W.5.

**MAGNAVIEW S/V strips** with tuner, all specified parts. BBC only received, aligning assistance wanted; Midlands, will recompense.—Box No. E.177.

## NEW SURPLUS . . .

1A3	2/6	6H6M	3/6	446A	10/6	EF32	4/-
1L4	5/-	6L6G	9/-	801A	7/6	EL41	10/-
1R5	7/6	6L6M	10/6	803	17/6	EL84	9/-
155	7/6	6Q7GT	9/6	808	17/6	EM80	10/-
2A3	8/6	6SA7M	7/6	830B	15/-	EZ40	8/6
2X2	3/6	6SG7M	7/6	866A	12/6	EZ80	8/6
3A4	4/6	6SH7M	5/-	959	5/-	GT1C	10/-
3Q4	7/6	6SJ7M	7/6	1616	5/-	HK24G	25/-
354	8/6	6SK7M	6/6	1629	4/-	KT33C	9/6
5763	12/6	6SL7GT	7/6	EA50	1/6	PCC84	10/6
5B/254M		6SN7GT	6/6	EABC801		PCF82	10/-
	21/-	6SQ7M	7/6	EAC91	4/6	PL82	9/6
5Y4G	6/6	6XA	6/6	EAF42	10/6	PL83	10/6
6AC7M	5/-	6X5GT	7/6	EB34	2/6	PY80	9/6
6AG5	3/6	7B7	9/-	EB91	4/6	PY81	9/6
6AK5	5/-	7C5	9/-	EBC33	7/6	PY83	11/6
6AL5	6/6	7C6	9/-	EBC41	10/6	R19	12/6
6AM6	7/6	757	10/-	EBF80	10/-	SP61	3/-
6AQ5	8/6	7Y4	8/6	EBF89	10/-	TT11	4/6
6AT6	8/-	12A6M	7/6	ECC82	9/6	UAF42	10/6
6AU6	8/6	12AT6	8/-	ECC84	11/-	UBC41	10/6
6BBG	4/6	12AT7	9/6	ECC85	10/6	UBF89	10/6
6BA6	8/6	12AU6	9/-	ECCF80	12/6	UCB85	10/-
6BE6	7/6	12AU7	8/6	ECCF82	11/6	UCH42	10/6
6BH6	7/6	12BE6	8/6	ECH42	10/6	UF41	10/6
6BJ6	7/6	12CBM	7/6	ECH81	10/6	UF89	10/6
6BR7	11/6	12Q7GT	8/6	ECL82	12/6	UL41	8/6
6C4	5/-	12K7GT	8/6	EF36	4/-	UY41	8/6
6C5M	5/6	12SC7M	2/6	EF39	5/-	UY85	10/-
6F6M	5/6	12SK7M	5/6	EF41	10/6	UABC80	
6FBG	4/6	12SQ7M	8/6	EF50	3/-	VU39	9/6
6G6G	4/6	35L6GT	9/6	EF50(S)	4/6	VR150/30	
6J5GT	5/-	35Z4GT	8/6	EF55	7/6		
6J5M	6/-	35Z5GT	8/6	EF80	9/-	VR116	7/6
6J6	4/-			EF85	10/-	V570	3/-
6K7G	5/6			EF89	10/6	XP1.5	3/-
6K8G	7/6	50L6GT	9/6	EF91	7/6	Z77	7/6
6K8M	10/6	80	8/6				

### SPECIAL OFFER

#### Units of the Famous R107

- Complete Front End**, r.f. mix, osc., 3 bands 1.2-18 Mc/s with large half-moon calibrated dial and slow-motion drive
- Power Pack** for either 12V d.c. or 100-250V a.c. input. You only need an i.f. strip and output stage to make a first-class Short Wave Receiver. We offer both units brand new and boxed (less valves and vibrator) for only 52/6 the pair, plus 7/6 carriage
- I.F. Unit** less valves, 35/-, or 30/- if ordered with units 1 and 2
- R.F. Unit** only 40/-, carr. paid

**Miniature Rotary Transformers**. Input 12V d.c., o/p 310/365V 30mA. Size 4½"x2½", 14/- each post paid

**Latest Model Acos Crystal Stick Microphones** MIC39-1. Frequency response flat to 6 kc/s, and within 5dB to 12 kc/s. List price £5.50. Our price 67/6 or 55/- les stand. Post paid

**Transistors**. Yellow/green, aud. 250mW, 7/6; OC70, 12/6; OC71, 15/-; yellow/red, r.f. to 8 Mc/s, 15/-

**Midget Mains Transformers** (same size as std. spkr. o/p). Input 230/250V, o/p 220V 20mA, 6.3V 0.6A. Ditto but 175V 25mA, both types 11/9 each, post paid

**Transmitter/Receivers**. Army Type 17 Mk. 2. Complete with h.r. phones, hand mike and valves. 44-61 Mc/s. In good used condition, 29/6 each. Carr. paid. Few only. New ones 45/- each

### SPECIAL OFFER

**Performance Meters No. 2**. Comprising 230V 50 c/s mains trans. 250-0-250V 30mA, 6.3V 1½A 5V 2A (60mA h.t. may safely be drawn), 20H choke, 5Z4, Y65 magic eye, 2 EF50, 1 EC52, 1 EA50, dozens of components, all in smart grey louvered case 10" x 9" x 9". Made by Parmeko. Brand new and boxed. Unrepeatable component value at only 27/6 each plus 5/- carriage (U.K. only)

Post 9d. Free over £2

S.A.E. Enquiries

## JOHN ANGLIN

385 CLEETHORPE ROAD GRIMSBY LINCS

Telephone 56315

continued on page 159

## G2AK FOR QUALITY AND SERVICE

**HEADPHONES, H.R. type.** 4,000 ohms. Very sensitive, only 12/6 pair, post 1/6. **C.L.R. type** (low res.) 8/6, post 1/6

**BRITISH BREAST MIKES** (carbon). Ideal for mobiles, 7/6, p.p. 1/6  
**12V MINIATURE ROTARY TRANSFORMERS.** Output 360/310V, 30mA c.c.s. or 70mA i.c.a.s. Only 4½" x 2½" overall. Only 21/- each or £2 for 2. P. & p. 2/-

**MULTI-WAY CABLE.** ⅜" diam. 7 coded wires. Ideal for inter-chassis connections or beam control. 1/3 per yard. Ditto, 10-way (5 pairs). Screened and plastic covered, 2/- per yard. P. & p. min. 1/6

**DUAL RANGE VOLTMETERS.** 0-5V and 0-100V, moving coil, 1,000Ω/V; ranges easily extended. Complete with leads and prods; solid leather carrying case 6½" x 5" x 2½". A gift at 25/-, post free

We stock the full range of Denco, Repanco and Eddystone coils and components, and the most comprehensive range of Hi-Fi equipment in the Midlands, including Quad, R.C.A., W.B., Leak, Rogers.

**ABSORPTION WAVEMETERS.** 3.00 to 35.00 Mc/s in 3 switched bands, 3.5, 7, 14, 21 and 28 Mc/s. Ham bands marked on scale. Complete with indicator bulb. A must for any ham shack. Only 17/6 each post free

**100 kc/s CRYSTALS.** American makes, in 3-pin based holder. New condition, worth £3.10.0. Our price only 25/-, post free

### SPECIAL OFFER!

ACOS MIC 33/2

**NEW**

in makers cartons

List 55/-

Our price 35/- p. & p. 1/6

**CHOKES.** 2.5mH, 120mA R.F. chokes. Pie wound, 2/- each. Three or more—post free

**NATIONAL TYPE R-300U Pillar Mounting R.F. Choke,** 1mH 300mA, 3/- each or 6 for 15/-

PLEASE PRINT YOUR NAME AND ADDRESS

**CHAS. H. YOUNG LTD** Dept. 'R',

110 DALE END BIRMINGHAM 4 Telephone Central 1635

### SHADED POLE MOTORS.

For tape recorders or gram units. Adjustable voltage, 3-hole fixing. Only 15/- each or 27/6 pair, p.p. 2/-

### RACK MOUNTING PANELS

19" x 5½", 7", 8½" or 10½" black crackle finish, 5/9, 6/6, 7/6, 9/- respectively, p. & p. 2/-

### AERIAL EQUIPMENT

**COPPER WIRE** 14g. h.d.; 140' 17/-; 70' 8/6; 7/25 stranded; 140' 10/-; 70' 5/- plus 2/- p. & p.  
**RIBBED GLASS INSULATORS,** 3" 1/6 each or 6 for 7/6. Postage and packing 1/6

**TWIN FEEDER.** 300 ohm twin ribbon feeder, similar K25, 6d. per yard. K35B Telcon (round), 1/6 per yard. Post on above feeder and cable, 1/6 any length



SEND 1/- (stamps)  
FOR FREE  
NUMEROUS  
CIRCUITS,  
PRICE LISTS,  
ETC., ETC.

Type S.M.  
with FERRITE  
CORE

5/- EACH

*New*

**SUB-MINIATURE  
HIGH Q COIL  
RANGE**

*"That's what I call  
stupendous performance"*

for SUPERHET — T.R.F. —  
TRANSISTOR CIRCUITS

**OSMOR**

(Dept. 26) 418 BRIGHTON RD. SOUTH CROYDON  
SURREY Telephone CROYdon 5148/9

## SMALL ADVERTISEMENTS

continued from page 157

PRIVATE—continued

### LAB QUALITY, CONSTRUCTORS' PRICES.

Amateur reducing spare units, components, offers duplicates Tx's, Rx's, test instrs., with full technical advice. Includes ADM, Army, A.M., Eddystone, Marconi, Advance, Weston, Bendix, Hallicrafter, National, Philips, RCA, and 50 cycle scopes, power packs and mobile. S.A.E. lists, specific enquiries.—Box No. E.181.

### TRADE

HUNDREDS of interesting items. List 2d.—Rogers' 31/33 Nelson Street, Southampton, Lanes.

SERVICE SHEETS for sale. Radio 3s., television 4s. All makes.—Sultan Radio (RC), 23n Albert Street, Tunbridge Wells, Kent.

ILLUSTRATED CATALOGUE No. 13 containing over 450 items of Government Surplus and Model Radio Control Equipment, 2s. 2d. Refunded on purchase of goods, 2s. 6d. overseas seamount.—Arthur Sallis Radio Control Ltd., Department R.C., 93 North Road, Brighton. Telephone 25806.

PANL, recognised for many years as the unique one-coat black crackle finish. Brush applied, no baking. Available by post in ½ pint cans at 3s. 9d. from G. A. Miller, 255 Nether Street, London, N.3.

LEARN as you do it—we provide practical equipment combined with instructions in Radio, Television, Electricity, Mechanics, Chemistry, Photography, etc. Write for full details to E.M.I. Institutes, Dept. RC47, London, W.4.

### JOIN THE INTERNATIONAL S.W. LEAGUE.

Free Services to members including Q.S.L. Bureau Translation. Technical and Identification Dept.—both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, "MONITOR" containing articles of general interest to Broadcast and Amateur SWL's, Transmitter page and League affairs, etc. League supplies such as badges, headed notepaper and envelopes. QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership, including monthly magazine, etc., 15s. per annum.—Secretary, ISWL, 86 Barenger Road, London, N.10.

FREE. Brochure giving details in Home Study Training in Radio, Television and all branches of Electronics. Courses for the hobby enthusiast or for those aiming at the A.M.Brit.I.R.E., City and Guilds, R.T.E.B., with other Professional examinations. Train with the college operated by Britain's largest Electronics organisation. Moderate fees.—Write to E.M.I. Institutes, Dept. RC28, London, W.4.

SERVICE SHEETS, radio and television, for sale and hire, s.a.e. enquiries. Valves and components cheap, list, s.a.e.—J. Palmer (RC), 32 Neasden Lane, London, N.W.10.

INCORPORATED Practical Radio Engineers home study courses of radio and TV engineering are recognised by the trade as outstanding and authoritative. Moderate fees to a limited number of students only. Syllabus of Instructional Text is free. *The Practical Radio Engineer*, journal, sample copy 2s. 6,000 Alignment Peaks for Superhets, 5s. 9d. Membership and Entry Conditions booklet, 1s., all post free from the Secretary, I.P.R.E., 20 Fairfield Road, London, N.8.

continued on page 160

## BRIDGE COMPONENTS

If you require a stockist of High Grade Components, we are the people for the job.

### If you are fitting converters, Why not fit the best?

The **Brayhead Turret Converter** available for all channels from stock. Price **£7.7.0**, with adaptor 7/6 each extra. Order, stating channels required (two as specified by you supplied with converter—extra channels **£1.1.0** extra) Normal trade discount—full fitting information available from:

## The High Fidelity Co

18 MELVILLE ROAD EDGBASTON  
BIRMINGHAM 16

(Proprietors Kendall & Mousley Ltd)

## REVACUUMED TV TUBES

### SIX MONTHS STRAIGHT GUARANTEE

Mullard		Mazda	
14" MW 36-22	£5.10.0	14" CRM 141	£5.10.0
14" MW 36-24	£5.10.0	14" CRM 142	£5.10.0
14" MW 36-44	£5.10.0	14" CRM 143	£5.10.0
16" AW 36-21	£5.10.0	15" CRM 153	£6.10.0
16" MW 41-1	£7. 0.0	17" CRM 171	£7.10.0
17" MW 43-43	£7.10.0	17" CRM 172	£7.10.0
17" MW 43-64	£7.10.0	21" CRM 211	£10.10.0
17" MW 43-69	£7.10.0	21" CRM 212	£10.10.0
21" MW 53-20	£10.10.0		
21" MW 53-80	£10.10.0		
Cossor		Brimar	
14" 141K	£5.10.0	14" C14BM	£5.10.0
17" 171K	£7.10.0	17" C17FM	£7.10.0
17" 172K	£7.10.0	17" C17JM	£7.10.0

14" Marconi, Emitron, Ferranti, G.E.C. £5.10.0  
17" Marconi, Emitron, Ferranti, G.E.C. £7.10.0

Carriage and Insurance 12/6 (U.K.) Cash with order  
Personal Callers Welcome

## VIDIO REPLACEMENT CO

HALES STREET DEPTFORD HIGH STREET  
LONDON SE8

Telephone TIDeway 4506

No connection with any firms of a similar name

# Forrest

Transistor Transformers  
for Quality Equipment

**H. W. FORREST (TRANSFORMERS) LTD**  
349 Haslucks Green Road Shirley Solihull  
Warwickshire Telephone SHrley 2483

## NYLON • P.T.F.E

ROD BAR SHEET TUBE STRIP WIRE  
No quantity too small List on application

BRASS COPPER BRONZE  
ALUMINIUM LIGHT ALLOYS

**H. ROLLET & CO. LTD.**

6 Chesham Place SW1 SLOane 3463  
Also at Liverpool, Birmingham,  
Manchester, Leeds

## GUARANTEED — Over 3,000 in stock VALVES

EF92, EAC91, 616, 6C4, 4/6; 6K7, EC91, 5/6; 6AL5,  
6SK7, R10, 3A4, 807, 6/-; 6AM6, EL91, 6X4, 6/6; 6BE6,  
6CH6, 6F17, 6F33, 7/6; 12A7, 12AX7, 12AU7, 6BA6,  
6BW6, 8/-; 6BR7, 12E1, 85A2, 2D21, 10/-; EF86, 6L6M,  
5B/225M, 5B/251M, 11/6

**A. A. W. SKILLMAN**

79A FRANCHISE STREET WEYMOU'JTH

## H.A.C. THE ORIGINAL SUPPLIERS OF SHORT-WAVE KITS

One-valve Kit, price 25/-, Two-valve Kit, price 50/-,  
improved designs with Denco coils. All kits complete  
with all components, accessories and full instructions but  
less valves. Before ordering, call and inspect a demonstra-  
tion receiver, or send stamped envelope for catalogue.

**H.A.C. SHORT-WAVE PRODUCTS (DEPT. R)**  
11 OLD BOND STREET LONDON W1

## SMALL ADVERTISEMENTS

continued from page 159

TRADE—continued

**MORSE CODE TRAINING.** Special course for  
Beginners. Full details from (Dept. RC), Candler  
System Company, 52 Abingdon Road, London,  
W.8.

### SITUATION VACANT

**TECHNICAL ASSISTANT** required in  
Service Dept. with a good working know-  
ledge of radio and allied subjects. Duties  
include the handling of technical correspon-  
dence, preparation of literature and liaison  
between dept. and factories. Should have a  
wide knowledge of English and good appear-  
ance. Education to O.N.C. or equivalent.  
Permanent staff position with good pros-  
pects. Apply Siemens Edison Swan Ltd.,  
Ref./JAR, 155 Charing Cross Road,  
London, W.C.2.

## SMALL ADVERTISEMENTS

Readers' small advertisements will be accepted  
at 3d. per word, including address, minimum  
charge 2/-, Trade advertisements will be  
accepted at 9d. per word, minimum charge 6/-.  
If a Box Number is required, an additional  
charge of 2/- will be made. Terms: Cash with  
order. All copy must be in hand by the 12th  
of the month for insertion in the following  
month's issue. The Publishers cannot be held  
liable in any way for printing errors or  
omissions, nor can they accept responsibility  
for the bona fides of advertisers.

# THE RADIO CONSTRUCTOR BOUND VOLUMES

Attractively bound in blue cloth, with gold-blocked spine

Vol. 10, August 56 to July 57 .. .. £1.5.0, postage 1/9

Vol. 11, August 57 to July 58 .. .. £1.5.0, postage 1/9

Where readers return all issues of a volume for exchange,  
the price is 12/6, plus postage 1/9

Please note:—we regret that we can no longer undertake to bind readers' own copies.  
(Many newsagents can arrange for books to be bound, and/or sell self-binding kits.)

**DATA PUBLICATIONS LTD 57 MAIDA VALE LONDON W9**

# SCOTTISH INSURANCE CORPORATION LTD



62-63 Cheapside  
London EC2

## TELEVISION SETS, RECEIVERS AND TRANSMITTERS

Television Sets, Receivers and Short Wave Transmitters are expensive to acquire and you no doubt highly prize your installation. Apart from the value of your Set, you might be held responsible should injury be caused by a fault in the Set, or injury or damage by your Aerial collapsing.

A "Scottish" special policy for Television Sets, Receivers and Short Wave Transmitters provides the following cover:

- (a) Loss or damage to installation (including in the case of Television Sets the Cathode Ray Tube) by Fire, Explosion, Lightning, Theft or Accidental External Means at any private dwelling-house.
- (b) (i) Legal Liability for bodily injury to Third Parties or damage to their property arising out of the breakage or collapse of the Aerial Fittings or Mast, or through any defect in the Set. Indemnity £10,000 any one accident.
- (ii) Damage to your property or that of your landlord arising out of the breakage or collapse of the Aerial Fittings or Mast, but not exceeding £500.

The cost of Cover (a) is 5/- a year for Sets worth £50 or less, and for Sets valued at more than £50 the cost is in proportion. Cover (b) and (ii) costs only 2/6 a year if taken with Cover (a), or 5/- if taken alone.

Why not BE PRUDENT AND INSURE your installation—it is well worth while AT THE VERY LOW COST INVOLVED. If you will complete and return this form to the Corporation's Office at the above address, a proposal will be submitted for completion.

NAME (Block Letters) .....

If Lady, state Mrs. or Miss

ADDRESS (Block Letters) .....

/JB

## YOU CAN RELY ON US



### The New AVO MULTIMINOR

A first quality pocket instrument

Sensitivity 10,000Ω/V 0 to 1A in five ranges, 0 to 1,000V in 7 ranges. A.C. volts 0-1,000 in 5 ranges. Resistance 0-2 Meg in two ranges.

**PRICE £9.10.0** Leather Case 32/6  
or 63/4 Deposit and 6 Payments of 22/2 or 9 monthly payments of 23/3

ALL AVO INSTRUMENTS IN STOCK

### COSSOR HI-FI AMPLIFIER KIT

3 valve 3W, Printed Circuit, twin speaker. Beautifully kitted by Cossor Radio and Television Ltd to the last nut and bolt.

**COMPLETE KIT** or 65/- Deposit and 6 monthly Payments of 23/4  
**£9.15.0** or 23/10 Deposit and 8 monthly Payments of 23/10

82 SOUTH EALING ROAD  
LONDON W5 Tel EAL 5737

# RADIO SERVICING CO

# RADIO



# BOOKS

**Tape and Wire Recording.** A selection of articles reprinted from the pages of *The Radio Constructor*, covering both the theory and practical applications. A really useful book on this latest development of the hobby.

4th Edition, 3/-. Postage 4d

**TV Fault Finding.** Profusely illustrated with photographs taken from a television screen depicting the faults under discussion, and containing a wealth of technical information, with circuits, enabling those faults to be eradicated.

5/-. Postage 5d

**FM Tuner Units for Fringe and Local Area Reception.** Including optional Tuning Indicator and circuit of Osram 912 Amplifier.

2/-. Postage 4d

**The Argonaut AM/FM MW/VHF Tuner Receiver.** Describing the construction, alignment, and other details of a high quality tuner (or complete receiver), together with map of present and projected coverage areas.

2/-. Postage 4d

**Radio Amateur Operator's Handbook.** An indispensable aid to the amateur transmitter and listener, containing all details of information which are constantly required. Prefix Lists, Zone Boundaries, Call Areas, Codes, and Mileage Tables, together with Maps and much other useful operating data.

1957/8 edition, 3/-. Postage 4d

**Mercury Switched Tuned FM Tuner Unit.** A stable unit employing automatic frequency control and a *ready built* front end.

2/-. Postage 2d

**Radio Control for Model Ships, Boats and Aircraft,** by F. C. JUDD, G2BCX. A comprehensive work on this fascinating subject.

Standard edition 8/6. Postage 7d

Cloth bound edition 11/6. Postage 8d

**The "Eavesdropper."** A miniature transistor local station receiver. Complete constructional details of this pocket portable.

1/6. Postage 2d

**Radio Control Mechanisms,** by RAYMOND F. STOCK. The only book dealing solely with this important part of radio control.

4/6. Postage 4d

All available from your local bookseller, or from

## DATA PUBLICATIONS LTD

57 MAIDA VALE LONDON W9

Telegrams **Databux London**

Telephone **CUNningham 6141 (2 lines)**

Published in Great Britain by the Proprietors and Publishers

Data Publications Ltd 57 Maida Vale London W9

Printed by A. Quick & Co. (Printers) Ltd 125 High Holborn London WC1 England also at Clacton-on-Sea

Obtainable abroad through the following Collets Subscription Service Continental Publishers & Distributors Ltd William Dawson & Sons Ltd Australia and New Zealand Gordon & Gotch Ltd South Africa Central News Agency Holland "Radio Electronica"

Registered for transmission by Magazine Post to Canada (including Newfoundland)