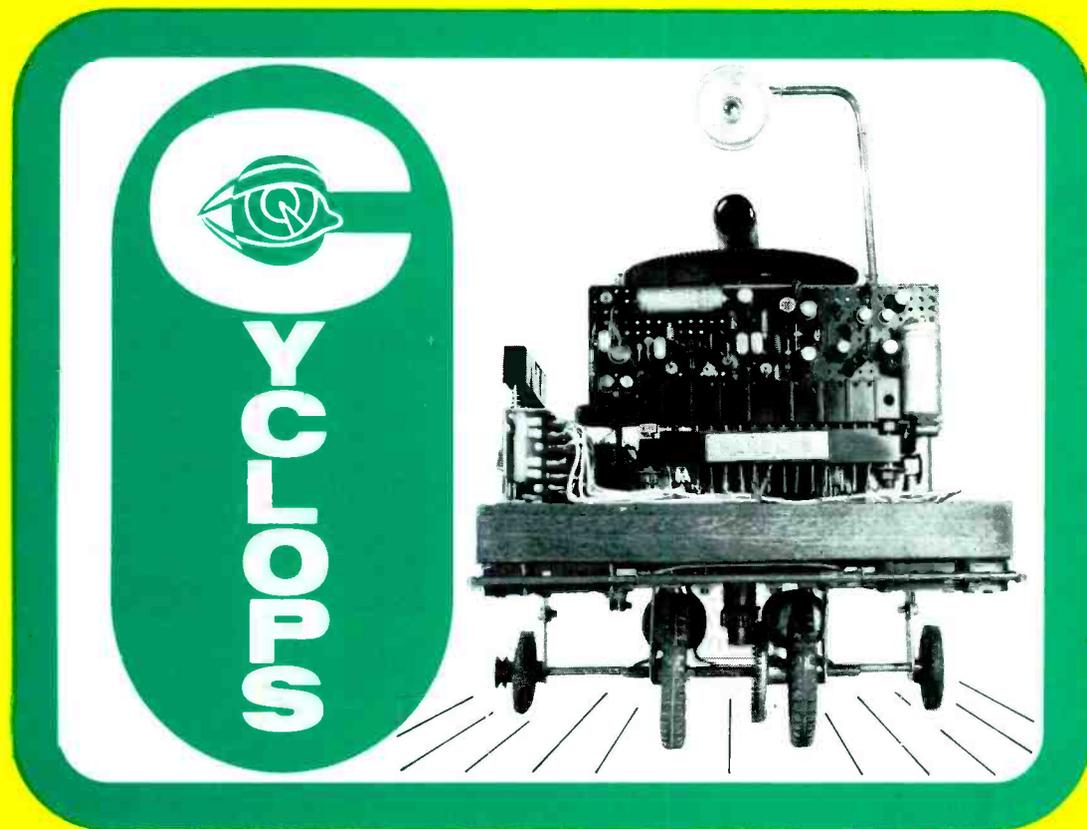


THE
RADIO CONSTRUCTOR

Vol. 25 No. 12

JULY 1972

20p



ELECTRONIC ROBOTS—Part 1

Describes various types of robot and introduces CYCLOPS — an electronic robot for home constructors

**FEATURED
IN THIS ISSUE**

Bedside Reflex Receiver
Winding Toroidal Coils

Index Volume 25, Aug. 1971 - July 1972



This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units

(or $\frac{1}{2}$ units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances And remember - as you buy more possessions just add more Home Units at any time.

THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD

Metropolitan House, 35 Victoria Avenue,
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way*.

Learn basic Radio and Electronics at home – the fast, modern way. Give yourself essential technical 'know-how' – like reading circuits, assembling standard components, experimenting, building – quickly and without effort, and enjoy every moment. B.I.E.T.'s Simplified Study Method and the remarkable **TECHNATRON** Self-Build Outfit take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

... and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors – even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again

You LEARN – but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build – and it's a good one – is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this Course – but it teaches the real thing. The easy to understand, practical projects – from a burglar-alarm to a sophisticated Radio set – help you master basic Radio and Electronics – even if you are a 'non-technical' type. And, if you want to make it a career, B.I.E.T. has a fine range of Courses up to City and Guilds standards.

New Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of 'OPPORTUNITIES IN TELECOMMUNICATIONS / TV AND RADIO'. This brand new booklet – just out – tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



FREE

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B9, ALDERMASTON COURT, READING RG7 4PF
Accredited by the Council for the Accreditation of Correspondence Colleges.

POST THIS COUPON FOR FREE BOOK

Please send book! and full information — free and without obligation.




NAME..... AGE.....
(BLOCK CAPITALS PLEASE)
ADDRESS.....
.....
OCCUPATION.....

To B.I.E.T. Dept. B9, Aldermaston Court, Reading RG7 4PF

JULY 1972

This remarkable catalogue

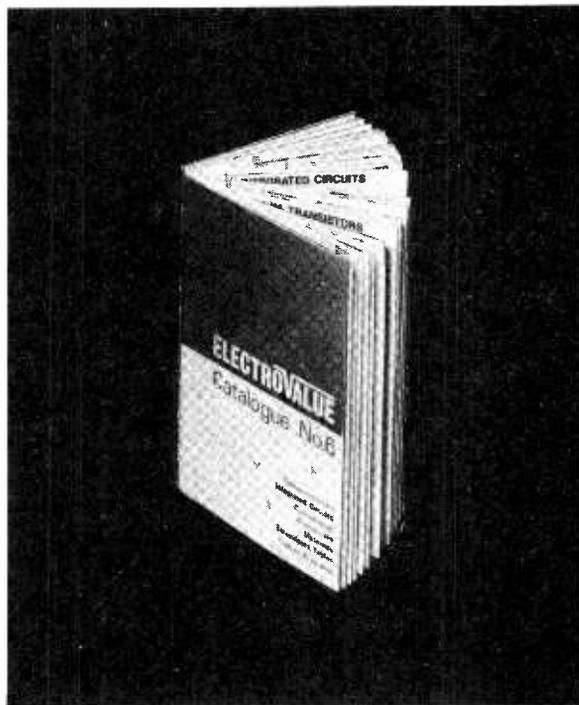

Comprises 96 pages, plus covers, packed with thousands of items of importance to every constructor. Also pages of I.C. diagrams, semi-conductor outlines, transistor characteristics and tables of equivalents. Hundreds of resistors and capacitors are detailed. Also included many other components, accessories, materials and tools. There is much other valuable information besides. The **Electrovalue Catalogue No. 6** costs but 10p post free. Orders for goods are dealt with very promptly and satisfaction guaranteed. Postage free for all orders over £2.00 in U.K.

- SUBSTANTIAL DISCOUNTS
- EVERYTHING BRAND NEW—
No seconds, 'surplus' or clearance bargains
- PROMPT DELIVERY
- SPECIAL TERMS FOR LARGE QUANTITY BUYERS

ELECTROVALUE LTD.

Dept FC.3

28 ST. JUDES RD., ENGLEFIELD GREEN, EGHAM, SURREY, TW20 0HB
Tel: Egham 3603 : Telex 264475 : Hours 9-5.30 : Sat. 1.0 p.m.

705

The largest selection

NEW LOW PRICE TESTED S.C.R.'s

PIV	1A	3A	7A	10A	15A	30A
	TO-5	TO-66	TO-66	TO-48	TO-48	TO-48
30	0.28	0.25	0.47	0.50	0.63	1.15
100	0.25	0.33	0.53	0.58	0.83	1.40
200	0.35	0.37	0.57	0.61	0.75	1.90
400	0.43	0.47	0.57	0.75	0.98	1.75
600	0.53	0.57	0.77	0.97	1.25	2.00
800	0.63	0.70	0.90	1.20	1.50	4.00

SIL. RECTS. TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
	TO-5	TO-5	TO-5	TO-5	TO-5	TO-5	TO-5
50	0.40	0.06	0.05	0.07	0.14	0.21	0.47
100	0.04	0.06	0.05	0.13	0.16	0.23	0.75
200	0.05	0.09	0.06	0.14	0.20	0.24	1.00
400	0.08	0.13	0.07	0.20	0.27	0.37	1.25
600	0.07	0.16	0.10	0.23	0.34	0.45	1.50
800	0.10	0.17	0.13	0.25	0.37	0.55	2.00
1000	0.11	0.25	0.15	0.30	0.46	0.83	2.50
1200	—	0.33	—	0.33	0.57	0.75	—

TRIACS

V _{BO}	2A	6A	10A
TO-1	TO-66	TO-88	TO-88
100	30	50	76
200	50	60	90
400	70	75	1-10

DIACS

FOR USE WITH TRIACS
BR100 (D32) 37p each

UNIJUNCTION

UT46. Eqt. 2N2646, Eqt. 1N843, BPN3090
27p each, 26-59 25p
100 UP 20p.

NPN SILICON PLANAR

PC107/108 10p each;
50-99 8p, 100 up,
8p each, 1-1000 off,
7p each. Fully tested
and coated TO-18 case.

FREE

One 50p Pak of your
own choice free with
orders valued \$4 or over.

SPECIAL OFFER

2N2926 (Y) (O)
10 for 50p, 25 for \$1
20,000 TO CLEAR

CADMIUM CELLS

ORP12 43p
ORP60, ORP61 40p each

GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18

SIM. TO 2N706-8, HSY27
(2N35A). All usable devices
no open or short circuits.
ALSO AVAILABLE in
PNP Sim. to 2N2906,
BCY70. When ordering
please state preference
NPN or PNP.
2p 100 For 1.75
20 For 0.50 500 For 7.50
50 For 1.00 1000 For 18.00

PHOTO TRANS.

OCP71 Type. 48p

SIL. G.P. DIODES 2p

300mW 30 .0-50
40V(1Min.) 100 .1-50
Sub-Min. 500 .8-90
Full Rate-1,000 .8-90
Ideal for Organ Builders.

DI8D1 Silicon Unilateral

switch 50p each.
A Silicon Planar, mono-
lithic integrated circuit
having thyristor electri-
cal characteristics, but
with an anode gate and a
built-in "Zener" diode
between rate and
cathode. Full data and
application circuits avail-
able on request.

FULL RANGE OF ZENER DIODES

VOLTAGE RANGE
2-33V. 400mV (DO-7
(Case) 18p ea. 10W (Top-
Hat) 18p ea. 10W (80-10
Stud) 25p ea. All fully
tested 5% tol. and
marked. State voltage
required.

10 amp POTTED BRIDGE RECTIFIER on heat sink

100 PIV. 90p each.

JUMBO COMPONENT PAKS

MIXED ELECTRONIC COMPONENTS
Exceptionally good value

Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs in weight. Price Incl. P & P \$1.50 only

Plus our satisfaction or money back guarantee.

BRAND NEW TEXAS GERM. TRANSISTORS

Coded and Guaranteed
Pak No. QCVT
T1 8 263713 OC7T
T2 8 1D1374 OC7E
T3 8 1D1218 OC81D
T4 8 21381T OC81
T5 8 21382T OC82
T6 8 26344B OC44
T7 8 26345B OC45
T8 8 26347A OC78
T9 8 26349A 2N1302
T10 8 26417 2N117
All 50p each pak

2N2906 NPN SIL. DUAL TRANS. CODE D1699 TEXAS. Our price 25p each.

120 VCB MIXIE DRIVER TRANSISTOR. Sim. 3BX21 & C407, 2N1933 FULLY TESTED A-D CODED ND 126. 1-24 27p each. TO-5 N.P.N. 15 up 15p each.

NEW LINE

Plastic encapsulated 2 amp Bridge Rects.
50 v RMS 32p each
100 v RMS 37p each
400 v RMS 46p each
Size 15 mm x 6 mm

KING OF THE PAKS Unequaled Value and Quality

SUPER PAKS NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak, or money back.

Pak No.	Description	Price
U1	120 Glass sub-min. general purpose germanium diodes	0.50
U2	60 Mixed germanium transistors AF/RF	0.50
U3	75 Germanium gold bonded diodes sim. OA5, OA47	0.50
U4	40 Germanium transistors like OC81, AC128	0.50
U5	60 200mA sub-min. Sil. diodes	0.50
U6	30 Silicon planar transistors NPN sim. BSY95A, 2N706	0.50
U7	16 Silicon rectifiers Top-Hat 750mA up to 1.000V	0.50
U8	50 Sil. planar diodes 250mA, OA 200/202	0.50
U9	20 Mixed volts 1 watt Zener diodes	0.50
U11	25 PNP silicon planar transistors TO-5 sim. 2N1132	0.50
U13	30 PNP-NPN sil. transistors OC200 & 2S104	0.50
U14	150 Mixed silicon and germanium diodes	0.50
U15	25 NPN Silicon planar transistors TO-5 sim. 2N697	0.50
U16	10 3-Amp silicon rectifiers stud type up to 1000 PIV	0.50
U17	30 Germanium PNP AF transistors TO-5 like ACY 17-22	0.50
U18	8 6-Amp silicon rectifiers BYZ13 type up to 600 PIV	0.50
U19	25 Silicon NPN transistors like BC108	0.50
U20	12 1.5-Amp silicon rectifiers Top-Hat up to 1,000 PIV	0.50
U21	30 A.F. germanium alloy transistors 2F300 series & OC71	0.50
U23	30 Mad's like MAT series PNP transistors	0.50
U21	20 Germanium 1-Amp rectifiers GJM up to 300 PIV	0.50
U25	25 300Mc's NPN silicon transistors 2N708, HSY27	0.50
U26	30 Fast switching silicon diodes like IN914 micro-min	0.50
U29	10 1-Amp SCR's TO-5 can up to 600 PIV CRS1 25 600	1.00
U31	20 Sil. Planar NPN trans. low noise amp 2N3707	0.50
U32	25 Zener diodes 400 mW DO7 case mixed volts, 3-18	0.50
U33	15 Plastic case 1 amp silicon rectifiers IN1000 series	0.50
U34	40 Sil. PNP alloy trans. TO-5 BCY26, 2S302 1	0.50
U35	25 Sil. planar trans. PNP TO 18 2N2906	0.50
U36	25 Sil. planar NPN trans. TO-5 BFY50 51.52	0.50
U37	30 Sil. alloy trans. SO-2 PNP, OC200 2S322	0.50
U38	20 Fast switching sil. trans. NPN, 400Mc's 2N3011	0.50
U39	30 RF germ. PNP trans. 2N1303 5 TO-5	0.50
U40	15 RF germ. trans. TO-1 OC45 NKT72	0.50
U42	10 VHF germ. PNP trans. TO-1 NKT667 AF 117	0.50
U43	25 Sil. trans. plastic TO18 A.F. BC113/114	0.50
U44	20 Sil. trans. plastic TO-5 BC115 116	0.50
U45	7 3-Amp SCR's TO-66 case up to 600V	1.00

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

NEW QUALITY TESTED PAKS

Pack	Description	Price
Q1	20 Red spot trans. PNP	0.50
Q2	16 White spot R.F. trans. PNP	0.50
Q3	4 OC77 type trans.	0.50
Q4	6 Matched trans. OC44/45/81/81D	0.50
Q5	4 OC75 transistors	0.50
Q6	4 OC72 transistors	0.50
Q7	4 AC128 trans. PNP high gain	0.50
Q8	4 AC126 trans. PNP	0.50
Q9	7 OC71 type trans.	0.50
Q10	2 AC127 128 comp. pairs PNP/NPN	0.50
Q11	3 AF116 type trans.	0.50
Q12	3 AF117 type trans.	0.50
Q13	3 OC171 H.F. type trans.	0.50
Q14	5 2N2926 sil. epoxy trans.	0.50
Q15	2 G17F880 low noise germ. trans.	0.50
Q16	3 NPN 1 ST41 & 2 ST140	0.50
Q18	4 Mad's 2 MAT 100 & 2 MAT 120	0.50
Q19	3 Mad's 2 MAT 101 & 1 MAT 121	0.50
Q20	4 OC44 germ. trans. A.F.	0.50
Q21	1 AC127 NPN germ. trans.	0.50
Q22	20 NKT trans. A.F. R.F. coded	0.50
Q23	10 OA202 sil. diodes sub-min.	0.50
Q24	8 OA81 diodes	0.50
Q25	6 IN914 sil. diodes 75PIV 75mA	0.50
Q26	8 OA95 germ. diodes sub-min. IN69	0.50
Q27	2 OA 600HV sil. rect. 1S458	0.50
Q28	4 Sil. power rect. BYZ13	0.50
Q29	4 Sil. trans. 2N696, 1 2N697, 1 2N698	0.50
Q30	7 Sil. switch trans. 2N706 NPN	0.50
Q31	6 Sil. switch trans. 2N708 NPN	0.50
Q32	3 PNP sil. trans. 2 N1131, 1 2N1132	0.50
Q33	3 Sil. NPN trans. 2N1711	0.50
Q34	7 Sil. NPN trans. 2N2369, 500MHZ.	0.50
Q35	3 Sil. PNP TO-5 2N2904 & 1 2N2905	0.50
Q36	1 2N3616 TO 18 plastic 300MHZ NPN	0.50
Q37	3 2N3053 NPN sil. trans.	0.50
Q38	7 NPN trans. 4 2N3703, 3 2N3702	0.50
Q39	7 NPN trans. 4 2N3704, 3 2N3705	0.50
Q40	7 NPN amp. 4 2N3707, 2 3N3708	0.50
Q41	3 Plastic NPN TO 18 2N3904	0.50
Q42	6 NPN trans. 2N5172	0.50
Q43	7 BC107 NPN trans.	0.50
Q44	7 NPN trans. 4 BC108, 3 BC109	0.50
Q45	3 BC113 NPN TO 18 trans.	0.50
Q46	3 BC115 NPN TO-5 trans.	0.50
Q47	6 NPN high gain 3 BC167, 3 BC168, 50	0.50
Q48	4 BCY70 NPN trans. TO-18	0.50
Q49	4 NPN trans. 2 BFY51, 2 BFY52	0.50
Q50	7 BSY28 NPN switch TO-18	0.50
Q51	7 BSY95A NPN trans. 300MHZ	0.50
Q52	8 BY100 type sil. rect.	1.00
Q53	25 Sil. & germ. trans. mixed all marked new	1.50

PRINTED CIRCUITS-EX-COMPUTER

Packed with semiconductors and components-10 boards give a guaranteed 30 trans and 30 diodes. Our price 10 boards, 50p. Plus 10p P & P. 100 Boards \$3. P & P 30p.

POWER TRANSISTOR BONANZA!

GENERAL PURPOSE GERM. PNP
Coded GP100 BRAND NEW TO-3 CASE, PORS.
REPLACE.—OC25-28-29-30-35-36. NKT 401-403-404-405-406-430-451-452-453. 13027-3028, 2N260A, 2N456A-457A-458A, 2N511 A & B, 3G220-222, ETC.
V_{CEO} 80V V_{CE0} 50V I_C 10A PT. 30 WATTS Hic 30-170.
PRICE 1-24 25-99 100 up
45p each 88p each

SILICON High Voltage 250V NPN TO-3 case, G.P. Switching & Amplifier Applications. Brand new Coded R 2400 V_{CEO} 250V/V_{CE0} 100IC 6A/30 Watts. HFE type 20/T 5MHZ.

OUR PRICE EACH: 1-24 25-99 100 up
50p 45p 88p

EX-STOCK TYPE EACH AS PRICED

OC20 50p OC28 40p AD149 43p BD131 70p BD139 75p
OC22 30p OC29 40p AL102 85p BD132 80p BD140 85p
OC23 33p OC35 35p AL103 85p BD135 70p BD156 75p
OC24 45p OC36 40p BD121 80p BD138 80p BU106 25
OC25 25p AD140 40p BD122 75p BD137 70p 2N305446p
OC26 25p AD142 40p BD124 70p BD138 80p

AD161 PNP AD162 PNP

M/P COMP GERM TRANS. OUR LOWEST PRICE OF 55p PER PAIR.

SILICON 50 WATTS MATCHED NPN/PNP BIP 19 NPN TO-3 Plastic. BIP 20 PNP. Brand new.

V_{CEO} 100V/V_{CE0} 50V/IC 10A. HFE type 100/Tc 3mHZ. OUR PRICE PER PAIR: 1-24 25-99 100 pps. 80p 55p 50p

SILICON PHOTO TRANSISTOR. TO-18 Lens end NPN Sim. to BP 25 and P01. BRAND NEW. Full data available. Fully guaranteed. Qty. 1-24 25-99 100 up Price each 45p 40p 35p

F.E.T.'S

2N3819	35p
2N3820	50p
2N3821	35p
2N3823	30p
2N3848	50p
2N3849	40p
BFW 10	40p
MPF105	40p

NEW EDITION 1971 TRANSISTOR EQUIVALENTS BOOK. A complete cross reference and equivalents book for European, American and Japanese Transistors. Exclusive to BI-PAK 90p each. Red cover edition.

A LARGE RANGE OF TECHNICAL AND DATA BOOKS ARE NOW AVAILABLE EX-STOCK SEND FOR FREE LIST

OUR STOCKS of individual devices are now too numerous to mention in this Advertisement. Send S.A.E. for our listing of over 1,000 Semiconductors. All available Ex-Stock at very competitive prices.

RTL Micrologic Circuits

Price each
Epoxy TO-5 case 1-24 25-99 100 up
uL300 Buffer 33p 33p 27p
uL914 Dual 1/2 1p
gate 55p 33p 27p
uL923 J-K flip-flop 50p 47p 45p
Date and Circuits Booklet for IC's Price 7p.

DUAL IN LINE SOCKETS

14 & 16 Lead Sockets for use with DUAL-IN-LINE IC's. TWO RANGES PROFES- SIONAL and NEW LOW COST
Prof. Type No 1-24 25-99 100 up
TSO14 pin type 30p 27p 25p
TSO16 pin type 35p 32p 30p
Low Cost No.
RPS 14 15p 13p 11p
RPS 16 16p 14p 12p

the lowest prices!

74 Series T.T.L. I.C.'S DOWN AGAIN IN PRICE

Check our 74 Series list before you buy any I.C.'s. Our prices are the lowest possible. All devices ex-stock. Full spec. guaranteed

BI-PAK Order No.	Price and qty. prices			BI-PAK Order No.	Price and qty. prices		
	1-24	25-99	100 up		1-24	25-99	100 up
BF00-8N7400	0.15	0.14	0.12	RP86-8N7486	0.92	0.80	0.28
BF01-8N7401	0.15	0.14	0.12	RP90-8N7490	0.87	0.64	0.58
BF02-8N7402	0.15	0.14	0.12	BP91-8N7491AN	0.87	0.64	0.78
BF03-8N7403	0.15	0.14	0.12	BP92-8N7492	0.87	0.64	0.58
BF04-8N7404	0.15	0.14	0.12	BP93-8N7493	0.87	0.64	0.58
BF05-8N7405	0.15	0.14	0.12	BP94-8N7494	0.77	0.74	0.68
BF07-8N7407	0.18	0.17	0.16	BP95-8N7495	0.77	0.74	0.68
BF08-8N7408	0.18	0.17	0.16	BP96-8N7496	0.77	0.74	0.68
BF09-8N7409	0.18	0.17	0.16	BP100-8N74100	1.75	1.65	1.55
BF10-8N7410	0.18	0.17	0.16	BP104-8N74104	0.87	0.64	0.68
BF13-8N7413	0.29	0.28	0.24	BP105-8N74105	0.97	0.94	0.88
BF16-8N7416	0.43	0.40	0.38	BP107-8N74107	0.40	0.38	0.36
BF17-8N7417	0.43	0.40	0.38	BP110-8N74110	0.55	0.53	0.50
BF20-8N7420	0.15	0.14	0.12	BP111-8N74111	1.25	1.18	1.00
BF30-8N7430	0.15	0.14	0.12	BP116-8N74118	0.90	0.85	0.60
BF40-8N7440	0.15	0.14	0.12	BP119-8N74119	1.85	1.25	1.10
BF41-8N7441	0.87	0.64	0.58	BP121-8N74121	0.87	0.64	0.58
BF42-8N7442	0.87	0.64	0.58	BP141-8N74141	0.87	0.64	0.58
BF43-8N7443	1.95	1.85	1.75	BP145-8N74145	1.50	1.40	1.30
BF44-8N7444	1.95	1.85	1.75	BP150-8N74150	1.90	1.70	1.60
BF45-8N7445	1.95	1.85	1.75	BP151-8N74151	1.00	0.95	0.90
BF46-8N7446	0.97	0.94	0.88	BP153-8N74153	1.20	1.10	0.95
BF47-8N7447	0.97	0.94	0.88	BP154-8N74154	1.80	1.70	1.60
BF48-8N7448	0.97	0.94	0.88	BP155-8N74155	1.40	1.30	1.20
BF50-8N7450	0.15	0.14	0.12	BP156-8N74156	1.40	1.30	1.20
BF51-8N7451	0.15	0.14	0.12	BP160-8N74160	1.80	1.70	1.60
BF53-8N7453	0.15	0.14	0.12	BP161-8N74161	1.80	1.70	1.60
BF54-8N7454	0.15	0.14	0.12	BP164-8N74164	2.00	1.90	1.80
BF60-8N7460	0.15	0.14	0.12	BP168-8N74168	2.00	1.90	1.80
BF70-8N7470	0.29	0.28	0.24	BP181-8N74181	2.75	2.60	2.40
BF72-8N7472	0.29	0.28	0.24	BP182-8N74182	0.97	0.94	0.88
BF73-8N7473	0.37	0.35	0.32	BP190-8N74190	3.50	3.25	3.00
BF74-8N7474	0.37	0.35	0.32	BP192-8N74192	2.10	1.95	1.75
BF76-8N7476	0.47	0.45	0.42	BP193-8N74193	2.10	1.95	1.75
BF78-8N7478	0.43	0.40	0.38	BP195-8N74195	1.10	1.05	0.95
BF80-8N7480	0.87	0.64	0.58	BP196-8N74196	1.80	1.70	1.60
BF81-8N7481	0.87	0.64	0.58	BP197-8N74197	1.80	1.70	1.60
BF82-8N7482	0.97	0.94	0.88	BP198-8N74198	5.50	5.00	4.00
BF83-8N7483	1.10	1.05	0.95	BP199-8N74199	5.50	5.00	4.00

PRICE-MIX. Devices may be mixed to qualify for quantity prices.
PRICES for quantities in excess of 500 pieces mixed, on application.
Owing to the ever increasing range of TTL 74 Series, please check with us for supplies of any devices not listed above, as it is probably now in stock. WARE 3442

LINEAR I.C.'s— FULL SPEC.

Type No.	Price		
	1-24	25-99	100 up
BP 201C-8L201C	63p	58p	45p
BP 791C-8L701C	63p	58p	45p
BP 792C-8L702C	63p	58p	45p
BP 722-72702	53p	45p	40p
BP 709-72709	53p	45p	40p
BP 709P-μA709C	53p	45p	40p
BP 710-72710	53p	45p	40p
BP 711-μA711	63p	50p	45p
BP 741-72741	75p	60p	50p
μA 733C-μA703C	45p	35p	27p
TAA 283	70p	60p	55p
TAA 293	70p	75p	70p
TAA 350	190p	158p	150p

LOGIC DTL 930 SERIES I.C.'s ROCK BOTTOM PRICES

Type No.	Price		
	1-24	25-99	100 up
BP930	12p	11p	10p
BP932	12p	12p	11p
BP933	12p	12p	11p
BP935	12p	12p	11p
BP936	12p	12p	11p
BP944	12p	12p	11p
BP945	25p	24p	22p
BP946	12p	11p	10p
BP948	25p	24p	22p
BP951	60p	60p	55p
BP962	12p	11p	10p
BP969	40p	35p	32p
BP904	40p	35p	32p
BP907	40p	35p	32p
BP909	40p	35p	32p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

NUMERICAL INDICATOR TUBES

MODEL	CD66	GR 116	3015F
Anode voltage (Vdc)	170	175	5
Cathode cur't(nmA)	2.3	1.4	
Numeral h'ght (mm)	16	13	9
Tube height (mm)	47	32	22
Tube diameter (mm)	19	13	12
I.C. driver rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All indicators 0.9" Decimal point: All side viewing: Full data for all types available on request.

STOP PRESS! NOW OPEN

BI-PAK'S NEW COMPONENT SHOP

A wide range of all types of electronic components and equipment available at competitive prices.

18, BALDOCK ST. (A10), WARE, HERTS. Tel.: 61593
OPEN 9.15-6 TUES. to SATS. FRIDAYS UNTIL 8 p.m.

BI-PAK DO IT AGAIN!

50W_{pk} 25w (RMS)

0.1% DISTORTION HI-FI AUDIO AMPLIFIER THE AL50



- ★ Frequency response 15Hz to 100,000 - 1dB. **ONLY £3.25p each**
- ★ Load - 3, 4, 8 or 16 ohms.
- ★ Distortion - better than 1% at 1kHz.
- ★ Signal to noise ratio 80dB.
- ★ Supply voltage 10 - 35 Volts.
- ★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and AL50 was conceived to fill the need for all your A.F. amplification needs. FULLY BUILT - TESTED - GUARANTEED.

STABILISED POWER MODULE

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (rms) per channel, simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Mains Transformer MT80, the unit will provide outputs of up to 1.5 amps at 35 volts. Size 63mm x 105mm x 30mm.

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications, including:- Disco Systems, Public Address, Intercom Units, etc, Handbook available 10p

STABILISED POWER MODULE SPM80 £2.95

TRANSFORMER BM780 £1.95 p & p 25p.
SPECIAL COMPLETE KIT COMPRISING 2, AL50's, 1, SPM80 & 1, BM780 ONLY £11, FREE p & p

DTL & TTL INTEGRATED CIRCUITS

Manufacturers "Fail outs"—out of spec. devices including functional units and part function but classed as out of spec. from the manufacturers' very rigid specifications. Ideal for learning about I.C.'s and experimental work.

Pak No.	μA	50p	Pak No.	μA	50p
UIC930	12 x μA 930	50p	UIC948	8 x μA 948	50p
UIC932	12 x μA 932	50p	UIC951	5 x μA 951	50p
UIC933	12 x μA 933	50p	UIC961	12 x μA 961	50p
UIC935	12 x μA 935	50p	UIC963	5 x μA 963	50p
UIC939	12 x μA 939	50p	UIC964	5 x μA 964	50p
UIC944	12 x μA 944	50p	UIC967	5 x μA 967	50p
UIC945	8 x μA 945	50p	UIC969	5 x μA 969	50p
UIC946	12 x μA 946	50p	UIC9 25 Assorted 930 Series		£1.50

Packs cannot be split but 25 Assorted Pieces (our mix) is available as Pack UIC930
Data Booklet available for the BP930 Series, PRICE 13p

UIC00	12 x 7400N	50p	UIC46	5 x 7446N	50p	UIC81	5 x 7481N	50p
UIC01	12 x 7401N	50p	UIC47	5 x 7447N	50p	UIC82	5 x 7482N	50p
UIC02	12 x 7402N	50p	UIC48	5 x 7448N	50p	UIC83	5 x 7483N	50p
UIC03	12 x 7403N	50p	UIC50	12 x 7450N	50p	UIC86	5 x 7486N	50p
UIC04	12 x 7404N	50p	UIC51	12 x 7451N	50p	UIC90	5 x 7490N	50p
UIC06	12 x 7406N	50p	UIC53	12 x 7453N	50p	UIC91	5 x 7491N	50p
UIC10	12 x 7410N	50p	UIC54	12 x 7454N	50p	UIC92	5 x 7492N	50p
UIC13	8 x 7413N	50p	UIC60	12 x 7460N	50p	UIC93	5 x 7493N	50p
UIC20	12 x 7420N	50p	UIC70	8 x 7470N	50p	UIC94	5 x 7494N	50p
UIC40	12 x 7440N	50p	UIC72	8 x 7472N	50p	UIC95	5 x 7495N	50p
UIC41	5 x 7441N	50p	UIC73	8 x 7473N	50p	UIC96	5 x 7496N	50p
UIC42	5 x 7442N	50p	UIC74	8 x 7474N	50p	UIC121	5 x 74121N	50p
UIC43	5 x 7443N	50p	UIC75	8 x 7475N	50p	UICX1	25 x Assorted	74's £1.50
UIC44	5 x 7444N	50p	UIC76	8 x 7476N	50p			
UIC45	5 x 7445N	50p	UIC80	5 x 7480N	50p			

All prices quoted in new pence Giro No. 388-7006
Please send all orders direct to warehouse and despatch department

BI-PAK

P.O. BOX 6, WARE - HERTS

Postage and packing add 7p. Overseas add extra for airmail.
Minimum order 50p. Cash with order please.

Guaranteed Satisfaction or Money Back

COMPONENTS

HOBBYIST - AMATEUR - DOMESTIC
SURPLUS INDUSTRIAL - BULK OFFERS

SELECTED PACKS 50p plus 10p Post/Pack

- 21 4 x 4 pole, 3 way, wafer switch.
- 22 20 x equipment phono plugs, metal.
- 23 4 x 5k log pots.
- 24 20 x pvc clip on mes bulb holder.
- 25 3 pair Bulgin 5mm switched jack socket and plug.
- 26 2 x 12volt solenoid and plunger.
- 27 4 x 3 pole, 7 way, wafer switch.
- 28 5 x 10k wirewound pots.
- 29 10 x 1k 10watt wirewound resistor.
- 30 15 x 15k 2%, ½ watt resistor.
- 31 15 x 150k, 2%, ½ watt resistor.
- 32 4 x 5k switched volume controls.
- 33 10 x 400 ohm, 10 watt wirewound resistors.
- 34 25 x 3.3pf 500v ceramic condenser.
- 35 10 x 330k, 1%, 2 watt resistors.
- 36 4 x 2 pole, 5 way, wafer switch.
- 37 5 x 50k wirewound pots.
- 38 15 x 500pf 5% condensers.
- 39 25 x 220k, 3 watt resistors.
- 40 150 pieces paxoline, 4 5/8 x 1/2 x 1/8".

SPECIAL: Packets of 12 carbon film 1 Watt 5% resistors, full range, but our selection 10p plus S.A.E.

THE RADIO SHACK MON-SAT
9AM-8PM

161 ST. JOHN'S HILL

BATTERSEA, S.W.11

01-223 5016

TECHNICAL TRAINING in Radio, Television and Electronic Engineering

Let ICS train You for a well-paid post in this expanding field. ICS courses offer the keen, ambitious man the opportunity to acquire, quickly and easily, the specialized training so essential to success. Diploma Courses in Radio, TV Engineering and Servicing, Colour TV Servicing, Electronics, Computers, etc. Expert coaching for:

- * C&G. TELECOMMUNICATION TECHNICIANS CERTS
- * RADIO AMATEURS EXAMINATION
- * GENERAL RADIOCOMMUNICATIONS CERTIFICATES
- * C&G. RADIO SERVICING THEORY

CONSTRUCTOR COURSES

Build your own transistor portable, signal generator, multi-test meter—all under expert guidance. Post THIS COUPON TODAY and find out how ICS can help YOU in your career. Full details of ICS courses in Radio, Television and Electronics will be sent to you by return mail.

Member of the ABCC.

Accredited by the C.A.C.C.

Name _____ Age _____
BLOCK CAPITALS PLEASE

Address _____

INTERNATIONAL CORRESPONDENCE SCHOOLS



NA 33

INTERTEXT House,
Stewarts Road,
London SW8 4UJ

ICS

Gets you there.

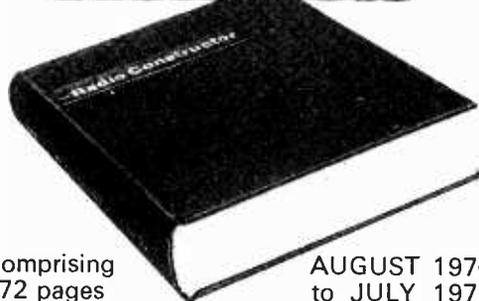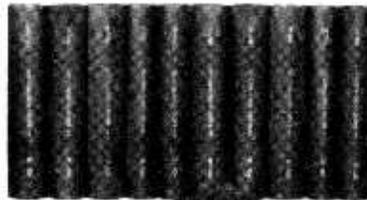Latest Bound Volume No. 24 of "The Radio Constructor" FOR YOUR LIBRARY



Comprising
772 pages
plus index

AUGUST 1970
to JULY 1971

PRICE £2.00 Postage 29p

BOUND VOLUME NO. 23

OF

"THE RADIO CONSTRUCTOR"
AUGUST 1969 to JULY 1970

Limited number of this volume still available

PRICE £1.88

Postage 29p

We regret all earlier volumes are now
completely sold out.

Available only from

DATA PUBLICATIONS LTD.,
57 MAIDA VALE, LONDON, W9 1SN

THE MODERN BOOK CO

NEWNES RADIO ENGINEER'S POCKET BOOK

£1.20

Postage 6p

GE Electronics Experimenters
Circuit Manual £1 Postage 5p
Integrated Circuit Pocket Book
by R. G. Hibberd £2.50 Postage 10p
Handbook of Transistor Equivalents
and Substitutes
by B. B. Babani 40p Postage 5p
99 Ways to Improve your Hi-Fi
by L. Buckwalter £1.50 Postage 5p
RCA Solid-state Hobby Circuits
Manual £1.05 Postage 10p
Practical Design with Transistors
by M. Horowitz £2.40 Postage 10p
GE Transistor Manual
£1.10 Postage 10p
F.M. Radio Servicing Handbook
by Gordon J. King £3 Postage 10p

110 Integrated Circuit Projects
for the Home Constructor
by R. M. Marston £1.20 Postage 6p
Audio Amplifiers
by Davies 52½p Postage 6p
The Manual of Car Electronics
by R. F. Graf £3.50 Postage 10p
Foundations of Wireless and Electronics
by M. G. Scroggie £1.80 Postage 15p
Practical Integrated Circuits
by McEvoy 90p Postage 10p
The Hi-Fi and Tape Recorder Handbook
by Gordon J. King £2 Postage 15p
ABC's of Electronic Power
by R. P. Turner £1.50 Postage 10p
Radio Valve and Transistor Data
by A. M. Ball 75p Postage 10p

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

RSGB BOOKS FOR YOU

RAE MANUAL

by G. L. Benbow, G3HB *Sixth (1972) edition*
The standard work for all would-be licensed radio amateurs studying for the Radio Amateurs' Examination. A completely re-written edition brought fully up to date to meet the present examination syllabus requirements.

96 pages

90p post paid

RSGB GREAT CIRCLE DX MAP

An invaluable aid to long-distance communications, showing the true bearing and distance from London of any position on the globe.

Supplied with a free copy of the latest Countries List showing world prefixes.

25 in. by 30 in.

65p post paid

RADIO DATA REFERENCE BOOK

Third (1972) edition

Compiled by G. R. Jessop, CEng, MIERE, G6JP
Completely revised and updated

An invaluable source of essential radio data conveniently gathered into one hard-bound volume.

150 pages

£1 post paid

These are three of a complete range of technical publications, log books and maps, all obtainable from:

RADIO SOCIETY OF GREAT BRITAIN
35 DOUGHTY STREET, LONDON, WC1N 2AE

REVERBERATION UNIT KIT Mk III

6 transistor reverberation chamber to which microphones, instruments, etc., may be connected for added dimensional effect. The output is suitable for most amplifiers and the unit is especially suitable for use with electronic organs. A ready-built spring and transistor assembly is used.
Complete easy-to-build kit, with constructional notes and circuits £7.50. Pre-drilled and printed case £2.00 extra. All parts available separately.



WAH-WAH PEDAL KIT Mk III

The Wilsic Wah-Wah pedal comprises a SELECTIVE AMPLIFIER MODULE KIT, containing all the components to build a two transistor circuit module, which may be used by the constructor for his own design or fitted to the FOOT VOLUME CONTROL PEDAL (as photo) converting it to Wah-Wah operation. This pedal is in strong fawn plastic and fitted with output lead and screened plug. Selective amplifier module kit £1.75. Foot Volume control pedal £5.13. COMPLETE KIT £6.50. Add 38p for assembly of module.



WILSIC VIBRATO UNIT

A new kit to build a self-contained vibrato foot switch unit. 4-silicon transistor circuit in tough grey hammered finish metal cabinet. Variable speed and depth controls and on-off foot switch. Ideal for guitars but unsuitable for high level inputs.
COMPLETE KIT £5.25, all parts available separately.



THE WILSIC BOOK OF CIRCUITS contains the full instructions for the Reverb unit, Wah-Wah pedal and our Vibrato unit.
PRICE ONLY 15p

SEND 5p in stamps for latest catalogue (Spring 1972) of Hi-Fi, components, guitars, etc., etc. Friendly, high-speed service.



WILSIC ELECTRONICS LTD.

6 COPLEY ROAD, DONCASTER, YORKS

PRECISION

POLYCARBONATE CAPACITORS

Fresh Stock – Fully Tested and Guaranteed

Close tolerance professional capacitors by well-known manufacturer. Excellent stability and extremely low leakage. All 63V D.C. Prices as follows:

0.47µF: ±5% 30p; ±2% 40p; ±1% 50p; Size $\frac{3}{8}$ " × $\frac{1}{2}$ " × $\frac{1}{8}$ "
 1.0 µF: ±5% 40p; ±2% 50p; ±1% 60p; Size 1" × $\frac{5}{8}$ " × $\frac{1}{2}$ "
 2.2 µF: ±5% 50p; ±2% 60p; ±1% 75p; Size 1" × $\frac{3}{4}$ " × $\frac{3}{8}$ "
 4.7 µF: ±5% 70p; ±2% 90p; ±1% 115p; Size $1\frac{1}{2}$ " × $\frac{3}{4}$ " × $\frac{3}{8}$ "
 10.0 µF: ±5% 110p; ±2% 140p; ±1% 180p; Size $1\frac{3}{8}$ " × $\frac{3}{4}$ " × $\frac{3}{8}$ "
 15.0 µF: ±5% 160p; ±2% 210p; ±1% 270p; Size $1\frac{3}{8}$ " × 1" × $\frac{3}{8}$ "

"DIRECT READING CAPACITANCE METER" DESCRIBED IN JUNE ISSUE

The 1mfd 63V polycarbonate listed above is recommended for use as timing capacitor C1. Extremely good stability with life and very low leakage. Our precision capacitors are also ideal for calibration purposes.

TRANSISTORS: BC107; BC108; BC109 (please state which), all at 9p each. 6 for 50p; 14 for £1.00; 100 for £6. May be mixed to qualify for lower price. All brand new to full manufacturer's specification.

RESISTORS: Carbon film $\frac{1}{2}$ watt 5%. Range 2.2Ω-2.2MΩ E12. Series i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades. All at 1p each. 8p for 10 of any one value; 70p for 100 of any one value. Special development pack 10 off each value 2.2Ω to 2.2MΩ (720 resistors) for £5.00.

440V A.C. CAPACITORS: 0.1µF: Size $1\frac{1}{8}$ " × $\frac{1}{2}$ ", 25p each
 0.25µF: Size $1\frac{3}{8}$ " × $\frac{5}{8}$ ", 30p each 0.5µF: Size $1\frac{3}{8}$ " × $\frac{3}{4}$ ", 35p each
 1.0 µF: Size 2" × $\frac{3}{4}$ ", 45p each 2.0µF: Size 2" × 1", 75p each

LIGHT DIMMERS: 440V A.C. capacitors listed above are ideal for dimming filament bulbs (unsuitable for fluorescent tubes). We suggest 1µF for dimming 25W bulb, 2µF for a 40W or 60W bulb.

5p post and packing on all orders below £5

V. ATTWOOD, Dept C.1., P.O. Box 8, Alresford, Hants.

To All Users of Industrial Electronics

Take advantage of our very competitive prices and high quality workmanship.

DESIGN AND CONSTRUCTION OF INDUSTRIAL ELECTRONICS EQUIPMENT. INDUCTION HEATING GENERATORS. METAL DETECTORS, POWER SUPPLIES, AUTOMATION AND CONTROL EQUIPMENT. HIGH QUALITY SHORT DELIVERY TIMES, TWO YEARS GUARANTEE

DESIGNS CONSTRUCTED TO CUSTOMERS OWN SPECIFICATIONS

WRITE FOR FULL DETAILS TO:

"E.B.E.H. A. KYPRIOTIS"

LABORATORIES OF INDUSTRIAL ELECTRONICS

OFFICE ANDROMAHIS 50, KALLITHEA ATHENS, GREECE

FACTORY PAPAFLISSA 3, TSAKOS AGHIA PARSKEVI ATHENS, GREECE

DENCO (CLACTON) LIMITED

355-7-9 OLD ROAD, CLACTON-ON-SEA, ESSEX

Our components are chosen by Technical Authors and Constructors throughout the World for their performance and reliability, every coil being inspected twice plus a final test and near spot-on alignment as a final check.

Our General Catalogue showing full product range	..	16p
DTB4 Transistor & Valve circuitry for D.P. Coils	..	16p
DTB9 Valve Type Coil Pack Application circuitry	..	16p
MD.1 Decoder Circuitry for Stereo Reception	..	20p

All post paid, but please enclose S.A.E. with all other requests in the interests of retaining lowest possible prices to actual consumers

BI-PRE-PAK



COMPLETE TELEPHONES
Normal household type as supplied to the Post Office, ex. G.P.O. Only **93p** each. p. & p. 35p each.



TELEPHONE DIALS
Standard Post Office type. Guaranteed in working order.
ONLY 50p
p. & p. 15p.

TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries. 0.3 to C.S.V. 0.5 to 2mA.	50p
B7	4	IN4007 Sil. Rec. diodes. 1,000 PIV lamp plastic	50p
B8	10	Reed Switches, mixed types large and small	50p
B9	200	Mixed Capacitors. Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors. Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors. Mixed types and values.	50p
H8	4	BY127 Sil. Recs. 1,000 PIV. 1 amp. plastic	50p
H9	2	OC771 Light Sensitive Photo Transistor	50p
H 1	50	NKT155/259 Germ. diodes. brand new stock clearance	50p
H 10	10	OC71/75 uncodded black glass type PNP Germ.	50p
H 19	10	OC81/61D uncodded white glass type PNP Germ.	50p
H 18	20	OC200/1/2/3 PNP Silicon uncodded TO-5 can	50p
H 19	20	OA47 solo. bonded diodes coded MCS2	50p

UNMARKED UNTESTED PAKS

B46	150	Germanium Diodes Min. glass type	50p
B63	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	50	Sil. Diodes sub. min. IN914 and IN918 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1 2N706A, BSY95A, etc.	50p
B91	50	Germanium Transistors PNP, A.F. & R.F.	50p
H4	40	250mW. Zener Diodes DO-7 Min. Glass Type	50p
H 10	25	Mixed volts. 1 1/2 watt Zeners Top hat type	50p
H 17	20	3 amp. Silicon Stud rectifiers, mixed 70Bts	50p
H 15	30	Top Max Silicon Rectifiers. 750mA. Mixed volts	50p
H 16	8	Experimenters' Pak of Integrated Circuits. Data supplied	50p
H 20	20	BY126/7 Type Silicon Rectifiers 1 amp plastic. Mixed volts.	50p

MAKE A REV COUNTER FOR YOUR CAR

The "ACHO BLOCK". This encapsulated block will turn any 0-1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system

£1 each



OUR VERY POPULAR 3p TRANSISTORS

TYPE "A" PNP Silicon alloy, TO-5 can.
TYPE "B" PNP Silicon, plastic encapsulation.
TYPE "E" PNP Germanium AF or RF.
TYPE "F" NPN Silicon plastic encapsulation.

FULLY TESTED AND MARKED SEMICONDUCTORS

4p		6p	
AC107	0-15	OC170	0-23
AC126	0-15	OC171	0-23
AC127	0-17	OC200	0-25
AC128	0-15	OC201	0-25
AC176	0-20	2G301	0-13
ACY17	0-20	2G303	0-13
AF239	0-30	2N711	0-50
AF186	0-20	2N1302-3	0-15
AF139	0-30	2N1304-5	0-17
BC154	0-20	2N1306-7	0-20
BC107	0-10	2N1308-9	0-22
BC108	0-10	2N3819FET	0.35
BF194	0-15	2N4416FET	0.35
BC109	0-10	Power Transistors	
BF274	0-20	OC20	0-50
BFY50	0-15	OC23	0-30
BSY25	0-13	OC25	0-25
BSY26	0-13	OC26	0-25
BSY27	0-13	OC28	0-30
BSY28	0-13	OC35	0-25
BSY29	0-13	OC36	0-37
BSY95A	0-10	AD149	0-30
OC41	0-15	AUY10	1-25
OC44	0-13	25034	0-25
OC45	0-10	2N3055	0-50
OC71	0-10	Diodes	
OC72	0-10	AA42	0-10
OC81	0-13	OA95	0-07
OC81C	0-13	OA79	0-07
OC83	0-18	OA81	0-07
OC139	0-13	IN914	0.06
OC140	0-15		

F.E.T. PRICE BREAKTHROUGH!!

This field effect transistor is the 2N3823 in a plastic encapsulation, coded as 3823E. It is also an excellent replacement for the 2N3819. Data sheet supplied with device. 1-10 30p each, 10-50 25p each, 50+ 20p each.



TRANSISTOR IGNITION! AS USED BY RACING DRIVERS!

NOW We introduce a Transistorised Ignition that is NOT a Kit at LESS than Kit price! The Super Spark, Mark II is ready to go. Installation time—10 minutes! It operates on a unique and newly discovered principle that drives a standard ignition coil with a fantastic peak of 400V. The solid impact gives 45,000 Volts right to the sparking plug and gives cooler running, longer plug life, more M.P.G. and greater B.H.P. Contact breaker life is extended indefinitely and no visible burning will ever take place. The circuitry is all silicon solid state and is engineered for top dependable performance on any car with standard ignition coil. Every unit is tested before despatch and each carries a full guarantee. Gives a full spark at up to 10,000 RPM!

Please state positive or negative earth on order.

SUPER SPARK

£10.95

P. & P. 25p.

FREE CATALOGUE



FOR TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS.

8 RELAYS FOR £1

VARIOUS TYPES P. & P. 25p.

COLOUR T.V. LINE OUTPUT TRANSFORMERS

Designed to give 25kV when used with PL509 and PY500 valves. As removed from colour receivers at the factory.

NOW ONLY 50p each post and packing 23p.

Quantity	1-10	10-50	50+
BB105 Varicap Diodes	10p	8p	6p
OC71 or 72 Fully Tested Unmarked	5p	5p	4p
Matched Sets 1-OC44 and 2-OC45, Per Set	25p	20p	15p
OA47 Gold-Bonded Diodes, Marked and Tested	3p	3p	2p
1-watt Zener Diodes 7.5, 24, 27, 30, 36, 43 Volts	5p	4p	3p
10-watt Zener Diodes 5-1, 8-2, 11, 13, 16, 24, 30, 100 Volts	20p	17p	15p
Micro Switches, S/P, C/O	25p	20p	15p
1-amp Bridge Rec's 25-volt	25p	22p	20p

INTEGRATED CIRCUITS

SL403D Audio Amp, 3-Watts	1.50	1.32
709C Linear Opp. Amp.	25p	20p 15p
Gates, Factory Marked and Tested by A.E.I.	25p	22p 20p
J. K. Flip-Flops Factory, Marked and Tested by A.E.I.	40p	35p 30p
5N7490 Decade Counter	50p	45p 40p
UL914 Dual 2 1/2 Gate	40p	35p 30p

LOW COST DUAL INLINE I.C. SOCKETS

14 pin type at 15p each
16 pin type at 16p each.

BOOKS

We have a large selection of Reference and Technical Books in stock. These are just two of our popular lines: **B.P.I. Transistor Equivalents and Substitutes:** 40p
This includes many thousands of British U.S.A., European and C.V. equivalents. **The Iliffe Radio Valve & Transistor Data Book 9th Edition:** 75p
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits. Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue.

NAME


ADDRESS

MINIMUM ORDER 50p. CASH WITH ORDER PLEASE. Add 10p post and packing per order. OVERSEAS ADD EXTRA FOR POSTAGE

BI-PRE-PAK LTD

DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX, SSO 9DF
TELEPHONE: SOUTHEND 0702) 46344

**May we draw
your attention**

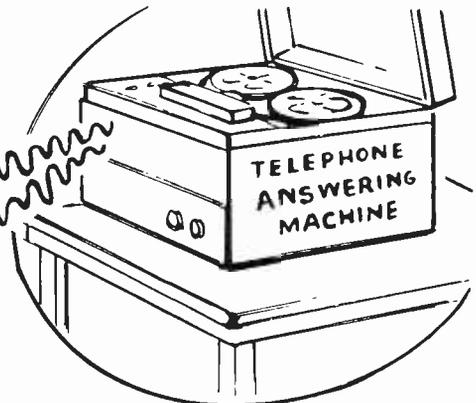

**to the
simplest way
of ordering goods**

from
**HOME RADIO (COMPONENTS)
LIMITED**

240 London Road, Mitcham. CR4 3HD Tel: 01-648 8422



It would help us considerably if we knew whether this was your first Home Radio Components Catalogue. If it is, please place a tick in the box.

It's late at night but that doesn't stop our young electronics enthusiast from ordering some urgently required components. He just dialled 01-648 8422 and telephoned his requirements, knowing that our Answering Machine will store his message ready for us to deal with next morning. As a seasoned member of our Credit Account Service he is well aware of the advantages it brings him. He has, for instance, a free supply of our pre-paid envelopes and order forms, for use when it suits him better to write his requirements rather than telephone them. This alone saves him quite a bit. He averages four orders a month and simply sends us a single cheque or postal order. *Without* our Credit Account Service his monthly cost would be: Four stamps at 3 pence each . . . 12p, four cheques or postal orders at 5 pence each . . . 20p., four envelopes 2p. Total, 34 pence. Over the year, quite an item! Not to mention his *time* spent in buying the stamps, envelopes and postal orders! We have well over 300 customers using our Credit Account Service – some sending us several orders every week, others just a few a year; but they *all* appreciate the fact that when they have been in the service for 12 months we send them up-dated catalogues and price lists *free of charge*.

Now – if *you* have not already got a copy of our famous Components Catalogue send the coupon with a cheque or postal order for 70 pence. More than 8,000 items clearly listed and indexed, over 1,500 of them illustrated.

Moreover, with the catalogue you get a sheet of 10 vouchers, each worth 5 pence when used as instructed.

If you call at our shop (open 9 to 5.30, Monday to Saturday inclusive, except Wednesday 9 to 1) you can buy the catalogue for 50 pence, thus saving the 20p packing and postage. Full details and entry forms for our Credit Account Service are included in each catalogue. Send today.

**POST THIS
COUPON
with your
cheque or
postal order
for 70p**

This is my first H.R. Components Catalogue

Name _____

Address _____

**HOME RADIO (COMPONENTS) LTD., Dept.RC
234-240 London Road, Mitcham, Surrey CR4 3HD.**

The price of 70p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.

THE Radio Constructor



Incorporating THE RADIO AMATEUR

JULY 1972

Vol. 25 No. 12

CONTENTS

Published Monthly (1st of Month)
First Published 1947

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141
Telegrams Databux, London

© Data Publications Ltd., 1972. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £2.70 (U.S.A. and Canada \$7.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.

BEDSIDE REFLEX RECEIVER	714
AUDIO FILTER FOR C.W.	716
NEWS AND COMMENT	718
ELECTRONIC EGG-TIMER (Suggested Circuit 260)	720
NOTES ON SEMICONDUCTORS (Further Notes – 8. Keep it Simple)	723
TRADE NEWS	724
USING THE U.J.T.	725
QSX	729
A TABLE-TOP WORK BENCH	730
WINDING TOROIDAL COILS	732
BALANCED DISTRIBUTION BOXES	734
CYCLOPS (Electronic Robot) – Part 1	736
DIGITAL FREQUENCY MONITOR Part 2	742
BOOK REVIEWS	747
SHORT WAVE NEWS	748
IN YOUR WORKSHOP	750
R.C. CROSSWORD	757
RADIO TOPICS	758
INDEX VOLUME 25 August 1971 – July 1972	766
RADIO CONSTRUCTOR'S DATA SHEET No. 64 (Copper Wire Data II)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

The Radio Constructor is printed by Carlisle Web Offset.

**AUGUST ISSUE WILL BE
PUBLISHED ON AUGUST 1st**

Bedside Reflex Receiver

by
A. Sapciyan

Circuit design for a low-cost 3-transistor medium-wave receiver

SIMPLE RECEIVERS ARE AMONG THE MOST INTERESTING projects for the home constructor. Receivers of this type frequently use the reflex principle, which provides a high gain with the minimum of components. The reflex receiver to be described in this article is capable of giving adequate loudspeaker volume for bedside listening without the need for an external aerial or earth. The sensitivity and selectivity are sufficient to enable several foreign stations to be tuned in after dark.

CIRCUIT DETAILS

The circuit is shown in Fig. 1. This has a variable resistor, VR1, which enables the set to be brought just below the oscillation level, thereby offering best sensitivity and selectivity for the reception of local and foreign transmissions. L1 is a ferrite aerial coil and is tuned by VC1. The signals picked up are passed to TR1 for r.f. amplification, the amplified signals being largely prevented by r.f. choke L2 from passing to the later stages. These r.f. signals then pass through C2 and are detected by D1, the resultant a.f. being reapplied to the base of TR1 via the electrolytic capacitor C9 and the lower end of L1. TR1 now functions as an a.f. amplifier and the amplified a.f. signals at its collector pass readily through the r.f. choke for application to TR2. C4 functions as a bypass capacitor for any r.f. signals that may still be present after the r.f. choke.

The a.f. signals next pass via C5 to TR2 and then via C7 to TR3. In the prototype, TR3 feeds a high impedance speaker directly but, as will be explained shortly, it may also couple into a 3Ω speaker via a step-down transformer.

The transistor in the first stage is an AF117 or AF127. The shield connection for either type is left open-circuit as this assists in providing regeneration. The current consumption of the first stage should be about 1.5mA.

The second stage uses an AC126 whilst the output stage employs an AC128. In the prototype, the output transistor coupled directly into a 150Ω speaker. However, speakers of this impedance are not widely available, and an alternative arrangement consists of coupling the collector of TR3 to the primary of a 9.2:1 step-down transformer (R.S. Components type T/T4), the secondary of which connects to a 3Ω speaker. The circuit incorporating the transformer is given in Fig. 2.

The total consumption of all three stages should not exceed 15mA, which is quite reasonable.

Sensitivity depends on the first stage providing a high gain. This stage can be checked for gain, if necessary, by

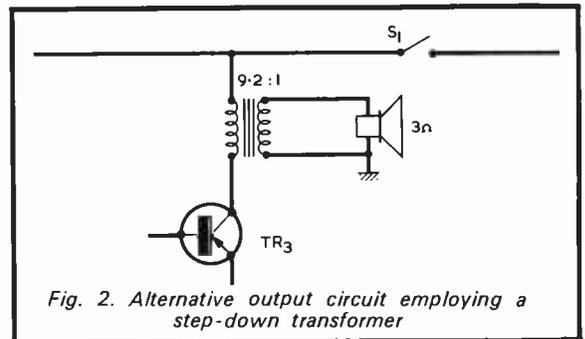


Fig. 2. Alternative output circuit employing a step-down transformer

connecting a pair of high impedance headphones in parallel with the load resistor, R2. R1, in series with VR1, controls the setting of the latter which allows oscillation to occur, and it may require adjustment in some cases for best results. R4 and C3 are decoupling components, and prevent motor-boating as the battery ages.

AERIAL COIL

The aerial coil is wound on a ferrite rod 4 in. long by $\frac{3}{8}$ in. in diameter, and consists of 75 turns close-wound on a paper sleeve that is free to slide along the rod. See Fig. 3. A tap is made at the 9th turn for the connection to the base of TR1, and the wire is 30 s.w.g. enamelled. Different grades of ferrite may give slightly varying values of inductance to the coil, and the constructor is advised to commence with 85 turns overall, still keeping the tap at the 9th turn. After the set has been completed and brought into working order, turns can then be

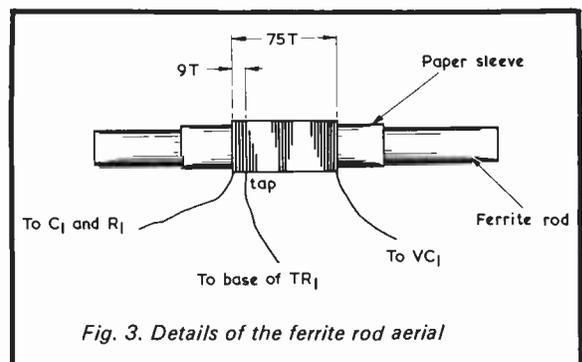


Fig. 3. Details of the ferrite rod aerial

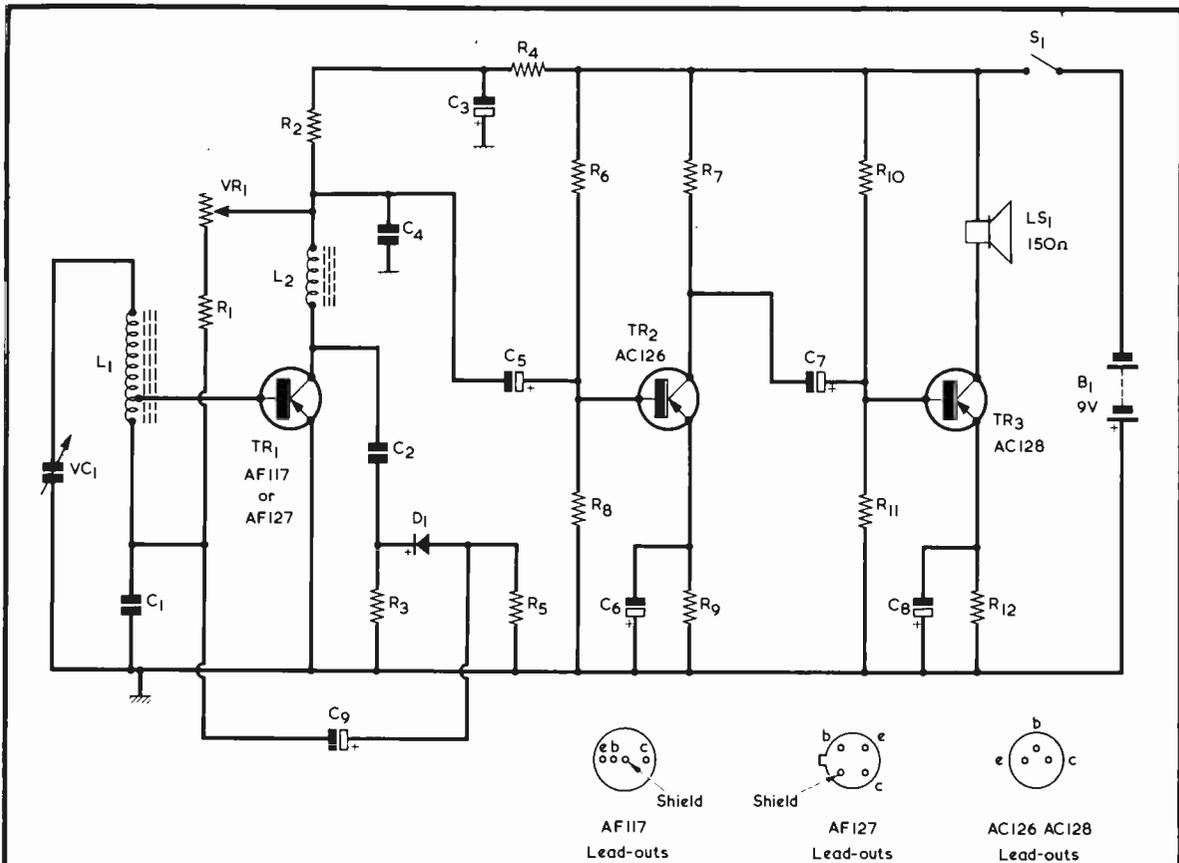


Fig. 1. The circuit of the reflex receiver

COMPONENTS

Resistors

(All fixed values ¼ watt 10%)

- R1 68kΩ (see text)
- R2 1kΩ
- R3 4.7kΩ
- R4 1kΩ
- R5 10kΩ
- R6 68kΩ
- R7 5.6kΩ
- R8 10kΩ
- R9 680Ω
- R10 33kΩ
- R11 5.6kΩ
- R12 150Ω
- VR1 100kΩ potentiometer, linear

Capacitors

- C1 0.01μF paper or plastic foil
- C2 330pF ceramic or silvered mica
- C3 50μF electrolytic, 10 V.Wkg.
- C4 0.01μF paper or plastic foil
- C5 5μF electrolytic, 10 V.Wkg.
- C6 50μF electrolytic, 6 V.Wkg.
- C7 5μF electrolytic, 10 V.Wkg.
- C8 100μF electrolytic, 6 V.Wkg.
- C9 10μF electrolytic, 2.5 V.Wkg.
- VC1 300pF variable, solid dielectric

Inductors

- L1 Ferrite aerial coil (see text)
- L2 2.5mH r.f. choke type CH1 (Repanco)

Semiconductors

- TR1 AF117 or AF127
- TR2 AC126
- TR3 AC128
- D1 OA85

Switch

- S1 s.p.s.t., toggle or rotary

Speaker

- LS1 Miniature speaker, 150Ω, or 3Ω with R.S. Components transformer type T/T4

Battery

- B1 9-volt battery

Miscellaneous

- Slow-motion drive and knob
- Chassis, as required
- Tagstrips or tagboard.

taken off at the end remote from the tap until the desired medium-wave coverage is obtained.

The receiver may be constructed on tagstrips or a tagboard mounted on a small metal chassis having a front panel for VC1, VR1 and, if desired, the speaker. VC1 should be provided with a simple slow-motion drive, such as is given by an epicyclic drive. VR1 is wired such that the resistance it inserts into circuit reduces as it is turned clockwise. The components should be laid out in roughly the same order as they appear in the circuit diagram, keeping the circuitry around TR3 well-spaced from that around TR1. The ferrite rod must be kept well away from the metal chassis or panel. The r.f. choke should not be connected permanently at this stage, as it may be necessary to alter its position with respect to the ferrite rod. It should be positioned about 2 in. from the rod.

When construction is complete, a battery may be connected and the receiver performance checked. After switching on, it should be possible to receive local stations by adjustment of VC1. VR1 functions as a reaction control and sensitivity is increased as it is turned clockwise, maximum sensitivity being given when it is set just below the oscillation point. VR1 will require different settings as the tuning is adjusted across the range. It may be found that the position of L2 relative to the ferrite rod affects the reaction and L2 should be rotated, if necessary through 180°, for best reaction performance.

As already mentioned, the value of R1 affects the setting of VR1 at which oscillation occurs, and R1 should have a resistance which enables VR1 to offer adequate control both with a new battery and with one whose voltage has fallen to some 7 volts or so. The value of 68kΩ employed in the prototype should be satisfactory in general, but it may need to be varied in some instances.

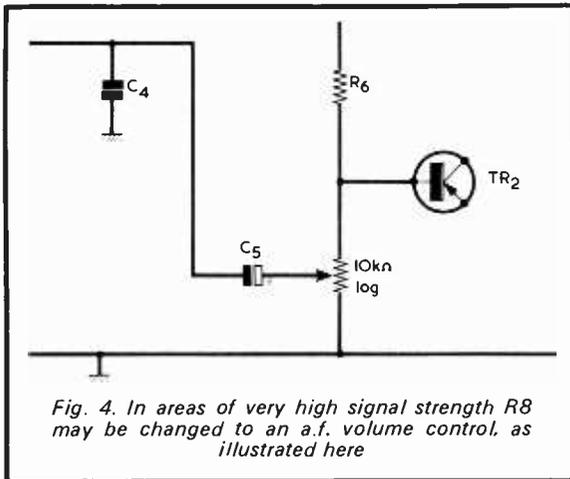


Fig. 4. In areas of very high signal strength R8 may be changed to an a.f. volume control, as illustrated here

No overloading problems were evident with the author's receiver, but they are feasible if the set should be employed close to a powerful station. Should overloading occur, resistor R8 may be replaced by a 10kΩ log potentiometer, connected as shown in Fig. 4. This will function as an a.f. gain control. It should be remembered that VR1 is a reaction control and is not a gain control, as such. VR1 should always be kept at a setting which provides adequate selectivity and sensitivity.



AUDIO

by

R. A. Penfold

THIS FILTER UNIT IS DESIGNED FOR USE WITH transistor short wave receivers, where it is used to greatly reduce the bandwidth of the receiver and thus reject unwanted transmissions together with atmospheric and other electrical interference. The bandwidth of the filter unit is very small and is far too limited for the reception of speech, but it is ideal for the reception of c.w. (morse code). The unit is inserted in the a.f. stages of the receiver after the detector and offers a high level of gain to audio frequencies at, or very near to, the frequency of the filter, and low gain to all other audio frequencies.

CIRCUIT DETAILS

Only a dozen components are used, and the cost of the unit is low. A single transistor is incorporated, this being a high-gain silicon type. Any extra noise introduced by the addition of the unit to the receiver is very small, and appears only at frequencies that lie within its passband. This small addition in noise should be more than compensated for by the reduction it provides in the noise from the earlier stages as well as by the increase in a.f. gain it gives at the filter frequency.

The circuit of the unit is given in Fig. 1, and it will be

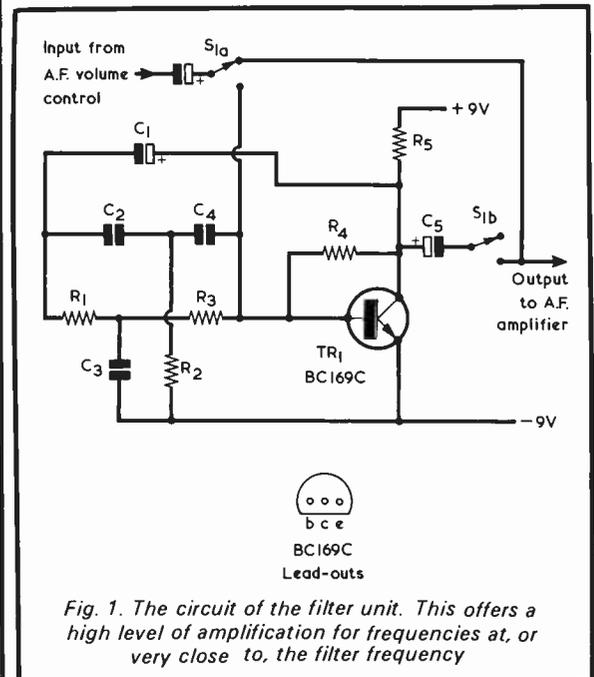


Fig. 1. The circuit of the filter unit. This offers a high level of amplification for frequencies at, or very close to, the filter frequency

FILTER FOR C.W. *

A simple but effective filter unit which may be inserted in the a.f. stages of a transistor short wave receiver

seen that it consists of a simple transistor amplifier employing TR1, R4 and R5, together with a parallel-T filter given by C2, C3, C4, R1, R2 and R3. This filter appears in a negative feedback path from the transistor collector to the base, and it offers very high attenuation to negative feedback signals at its operating frequency. Thus, signals at this frequency are not returned to the base of the transistor at any significant level, and the transistor is capable of offering the full gain of which it is capable. Full negative feedback is given to frequencies removed by any significant amount from the filter frequency and these are amplified at very much lower level by the transistor.

The filter unit is best inserted immediately after the slider of the a.f. volume control of the receiver. The electrolytic input capacitor shown in Fig. 1 without a component designation will normally be that already installed in the receiver which previously coupled to the base circuit of the following a.f. transistor. When the unit is installed, the output via C5 is passed to that base circuit. It will be noted that S1 (a) (b) enables the filter unit to be switched in or out, as desired.

It may be possible to add the parallel-T filter to the first audio stage of the receiver itself by coupling the network given by C2 to C4 and R1 to R3 between its collector and base circuits. This would make TR1, R4,

R5 and C5 unnecessary. However, the addition of the filter would cause a loss in the gain of the set, and in most cases it would be preferable to use the filter in an additional unit, as described here.

The operating frequency of the filter is about 4kHz. If this is thought to be rather high it can be reduced by altering the values of C2 and C4 to 0.02μF and that of C3 to 0.04μF. These changes will reduce the operating frequency to just over 2kHz.

Ideally, C2, C3 and C4 should have a tolerance of 5%, or better, but it will be difficult to obtain the values specified with a tolerance as close as this. In practice, good quality plastic foil components will work adequately. Avoid the use of ceramic capacitors, which may have very wide tolerances.

The power supply may be obtained from the receiver circuits, and it is left permanently connected to the filter unit. Since the current consumption of the unit will normally be less than 1mA, there is little point in providing it with an on-off supply switch.

COMPONENTS

Resistors

(All resistors ½ watt or ¼ watt)

R1	3.6kΩ 5%
R2	1.8kΩ 5%
R3	3.6kΩ 5%
R4	1.2MΩ 10%
R5	4.7kΩ 10%

Capacitors

C1	25μF electrolytic, 6.4V.w.kg.
C2	0.01μF plastic foil
C3	0.02μF plastic foil
C4	0.01μF plastic foil
C5	25μF electrolytic, 6.4 V.w.kg.

Transistor

TR1 BC169C

Switch

S1 (a) (b) d.p.d.t. toggle

Miscellaneous

Veroboard, 0.1 in. or 0.15 in. matrix, as required.


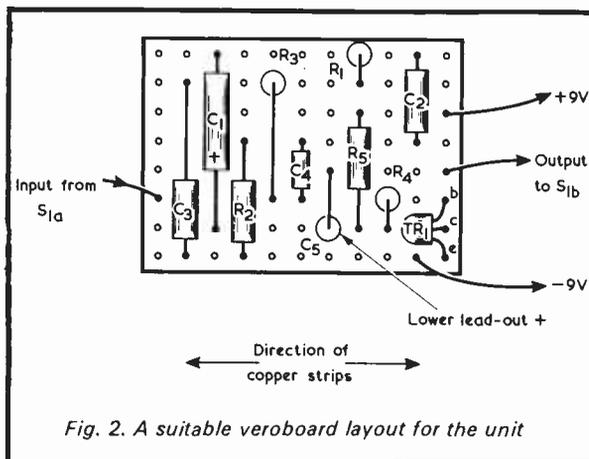


Fig. 2. A suitable veroboard layout for the unit

There will not be much space in most transistor receivers to accommodate the unit and, because of this, it must be made fairly small. Fig. 2 shows a suitable layout on a piece of Veroboard. In this layout, R1, R3 and C5 are mounted vertically. Veroboard with a matrix of 0.1 in. can be used if the physical size of the components allows this, otherwise a board of 0.15 in. matrix should be used. The switch S1 (a) (b) is external to the board and may be mounted at any convenient point in the receiver. It may be necessary to use screened wire for the input and output connections to the Veroboard and to the switch, the braiding of the wire being connected to the receiver chassis.

WORLD'S MOST POWERFUL VALVE

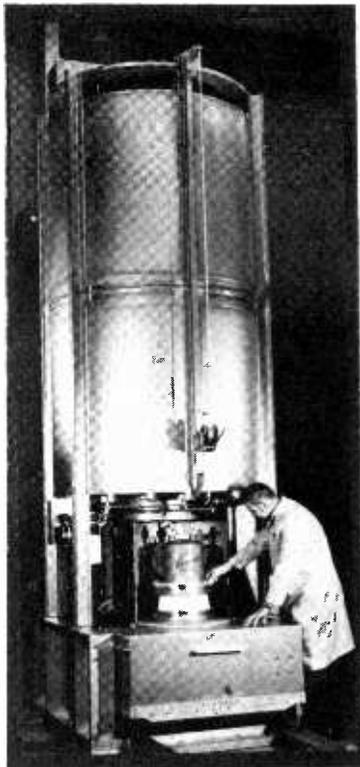

The world's most powerful radio transmitting valve is this two million-watt output super power tetrode pictured here in a test amplifier at the EIMAC Division of Varian Associates (San Carlos, Calif.). Generating more than two times the power of all the AM, FM and television stations in New York City, the 175-pound valve was developed for use in high-power transmitters in medium- and high-frequency broadcast service and for industrial and scientific uses as a 1,000-ampere, 60-kV switch. Costing \$20,000 each, the new two-megawatt valves permit a single stage amplifier to reach an output power level of 2,500 kW, 100 percent modulated - five times more powerful than any previous single amplifier ever built.

718

25 YEARS OLD AND STILL GOING STRONG

Observant readers will already probably have noticed that this issue of **THE RADIO CONSTRUCTOR** is Volume 25 No. 12. This means that the magazine has completed 25 years of publication.

Looking back over the years to our first issue, 28 small pages, we recall the hopes, fears and excitement that went into its production. Today, one of the few national magazines in this country published independently of the large publishing groups, we draw considerable satisfaction from our progress in this highly competitive field.

This progress has largely been due to the loyalty of our readers, many of whom look upon the "Constructor" with an almost proprietorial interest. We feel that this loyalty, which we greatly value, is in no small measure due to our policy of publishing, to the best of our ability, sound worthwhile articles of practical interest and giving good value for money.

As time goes on interests change, and a far greater proportion of our subject matter now deals with electronics over a broader field, but radio has not, nor will it be, neglected.

To commence our 26th year of publication, our Technical Editor, J. R. Davies, has especially designed the "Jubilee" 8 watt amplifier, to feature in our August and September issues; to be followed by a special October issue.

We have many exciting plans for the future, and the magazine will continue to evolve in the same practical friendly manner as it has done in the past.

If you are an established reader thank you for your support, and if our magazine is new to you we hope that you too will find pleasure and satisfaction in our pages and join the ranks of our regular readers.

NEW ELECTRONICS INSTRUMENT PLANT

Venner have just announced the opening, at their New Malden Works, of a new 5,000 sq.ft. Assembly and Test Unit for their range of electronic measuring instruments. This unit has been specially built and equipped to cater for a significant increase in instrument production, an increase which has become necessary in order to meet the ever growing demand for existing types and to handle the widening range of instruments now being developed.

Already recognised as one of the leading manufacturers of digital counting and timing instruments, Venner are now breaking into the communications test gear markets with their new ranges of p.c.m. and data line test instruments.

Commenting on this expansion, Mr. Derek Ashby, Venner's General Sales Manager, said "Our instrument sales in 1971 was an all-time record despite the apparent recession in the electronic industry, and our new assembly and test facilities are capable of producing over £1,000,000 worth of equipment each year".



COMMENT

ANOTHER NEW BRANCH FOR HENRY'S RADIO LTD

Ready for opening early July will be the new Electronics Centre for Henry's Radio Ltd, at 404-406, Edgware Road, London, W.2.

This large 32ft. frontage shop is the latest Henry's branch to be opened and will contain a comprehensive range of every conceivable item of electronic components - plus audio and test gear all offered at highly competitive prices.

In addition to the new branch Henry's Radio Ltd. have centres at 354/356 Edgware Road for Hi Fi and Tape Equipment, 309 Edgware Road for Disco, PA and Lighting equipment and 303 Edgware Road, London, W.2. deals with all mail orders, industrial sales and also stocks many clearance bargains at specially reduced prices.



IN BRIEF

● The English Electric Valve Co. Ltd., as well as THE RADIO CONSTRUCTOR, has also recently completed 25 years existence. Formed when The English Electric Co. Ltd., bought the controlling interest in Marconi's Wireless Telegraph Co. Ltd., the Company has expanded from 150 employees to more than 2,000. More than half the annual turnover of £10 million is exported.

● A group for the furtherance of FM operation in the VHF/UHF spectrum, and having the orderly growth of FM in the UK as one of its objectives, has recently been formed.

The group is known as U.K. FM Group, details from the Hon. Secretary, K. H. Kanalz G5AGX, Flat 6, Marzena Court, Whitton Dene, Hounslow, Middlesex.

● Advance warning of potentially dangerous rolling conditions, which could lead to a vessel's capsize, can be given by a roll period indicator a new electronic instrument introduced by Recording Designs (EMI) Ltd., of Camberley, Surrey.

● The Barking Radio Society will be operating an Exhibition Station at the Dagenham Town Show on Saturday and Sunday 8th and 9th July. All bands from Top Band through to 70 Centimetres.

Also on Sunday 9th July, the Cornish Radio Amateur Club is holding its annual mobile rally at the Truro Rugby Club.

● Lonsdale Technical's Printed Circuit company at Waterlooville, Hampshire, has been reconstituted as a separate company trading as Lonsdale Technical (Circuits) Ltd. They produce conventional and PTH circuit boards by modern plating techniques.

● An Honorary Fellowship of the Royal Television Society has been awarded to Dr. Gerhard Lubszynski. He was an original member of Sir Isaac Schonberg's pioneering team at E.M.I., and is a world authority on camera tubes and the author of 94 Patents in that field.

● Readers in South London who wish to purchase components locally, can do so from The Radio Shack, 161 St. John's Hill, Battersea. Shop hours are from 9am to 8pm Monday to Saturday.

● Vero Electronics announce what must be one of the largest export orders for printed circuit boards ever received by a U.K. company. The order, worth \$150,000 and won in fierce competition with American companies, is for the supply of standard universal wiring boards of their D.I.P. Board and Finger Board types.

● A new Vidor 14.74 volt mercury-zinc battery designed for radio microphone use has been developed by Crompton Parkinson Ltd., of Northampton. The battery consists of eleven KRK42 mercury-zinc round cells connected in series.


ITA TRANSMITTERS - A POCKET GUIDE

A new edition of the fold-out publication "ITA Transmitters - A Pocket Guide" has just been published by the ITA to assist television suppliers, aerial rectors and others concerned with television.

The Pocket Guide provides essential technical details of the ITA network of 47 VHF (Band III) transmitting stations and 149 existing or planned UHF (Bands IV and V) stations.

It includes details of channels, aerial polarization and recommended UHF aerial group, effective radiated power, aerial height above sea level, national grid references for 171 sites, programme company using each transmitter, reference information on channel frequencies, and a useful map. Where available, target dates are provided for those UHF stations not already in service, and an index to all stations is included.

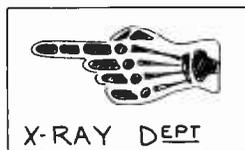
Copies of the new Pocket Guide, which measures approximately 8in. by 3½in. when folded, are available on request from: ITA Engineering Information Service, 70 Brompton Road, London, S.W.3. 1EY.



LETZ...

ELECTRONIC EGG-TIMER

by G. A. FRENCH

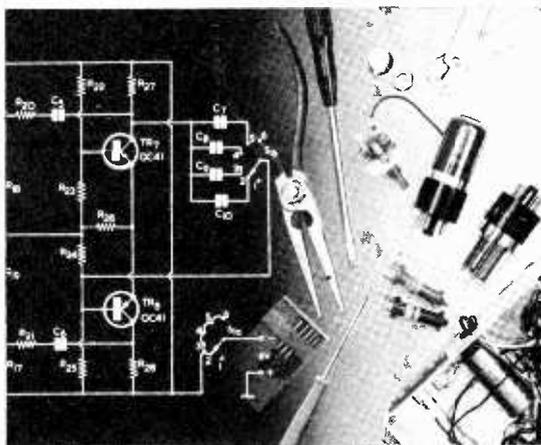

WHAT CAN ALMOST BE REFERRED to as the 'classical' type of egg-timer consists of a scaled-down version of the hour-glass in which the passage of sand from one section to the other indicates the time required for the boiling of an egg. This type of timer is set up by turning it through 180° so that the lower section, full with sand, becomes uppermost. The timing period is at an end when all the sand has flown through from this uppermost section.

The egg-timer concept offers an interesting challenge to electronic design. Obviously, an electronic 'egg-timer' has applications other than that of timing the boiling of an egg, and it could be employed for any operation where it is desired to indicate the timing of a process. If the egg-timer analogue is to be followed through in its entirety, the electronic version should be capable of being set in operation at any time and should require no attention other than that of being initially started.

The device to be described in this article meets both these requirements. It employs a battery-operated circuit which is normally in the 'off' condition and the only control is a push-button, this being pressed to start the timing period. At the end of the period an electric bell sounds, after which the unit automatically turns itself off again.

THE CIRCUIT

If complete switching-off at the end of a timing period is to be achieved with certainty, it is necessary to em-

ploy mechanically operated switching contacts. A semiconductor device could be cut off to prevent a circuit from operating but it would still allow a small leakage current, even if only of the order of a few microamps, to flow. For a definite and positive switching-off action mechanically operated contacts are essential, and this argues the use of relays. Two simple relays are employed in the timing unit to be discussed. Their specifications are not particularly critical and a fairly wide variety of relay types can be used.

In the accompanying circuit diagram for the timing unit the two relays are depicted in the so-called 'detached' method of presentation. Each relay coil is shown as a rectangle, alongside which is a letter over a number. The letter is the identifying letter for the relay, whilst the number indicates the number of contact sets that the relay possesses. The contact sets may appear anywhere in the diagram and are shown in the position they take up when the relay is de-energised. As an example, the coil of relay X can be seen in the collector circuit of transistor TR2. The legend alongside the rectangle indicates that this relay has 2 contact sets. These contact sets, X1 and X2, appear elsewhere in the diagram, in the de-energised position.

As the circuit stands, no positive connection is made to battery B1, and no current is drawn from it. To start the timing cycle, push-button S1 is pressed. This causes capacitor C1 to be almost immediately charged to about 8.2 volts, this voltage being con-

trolled by zener diode D1. At the same time, the positive supply potential is made available to the upper terminal of the coil of relay X by way of diode D2. As soon as C1 becomes charged, forward current flows from its positive plate via R4, D3 and D4 to the base of transistor TR1. This transistor becomes fully conductive and, in turn, makes TR2 similarly conductive. The voltage across the emitter and collector of TR2 is negligibly low and relay X energises. Its contact set X1 closes, causing the relay coil positive supply to be independent of the circuit provided by S1 and D2. This contact set also causes pilot lamp PL1 to be illuminated, thereby indicating that the circuit is ready to commence the timing cycle. At the same time, contact set X2 connects capacitor C2 across the 12 volt supply rails, causing C2 to become charged to the supply voltage.

The timing period commences when S1 is released. As soon as this occurs, capacitor C1 starts to discharge into R2 and R3 and the circuit given by R4, D3, D4 and the base-emitter junctions of TR1 and TR2. Diode D2 is now reverse-biased and plays no further part in circuit operation. After a period, the voltage across C1 falls below the level required to maintain forward current flow in D3, D4 and the base-emitter junctions of TR1 and TR2, with the result that TR2 becomes non-conductive. Relay X de-energises and its contact set X1 opens, extinguishing pilot lamp PL1. Contact set X2 changes over, connecting the coil of relay Y to the fully charged capacitor, C2. Current flows from C2

THE RADIO CONSTRUCTOR

into the coil of relay Y, whereupon it energises and its contact set Y1 causes the electric bell to be connected to battery B2. The bell sounds until the charge remaining in C2 is insufficient to maintain relay Y energised. Relay Y de-energises and the circuit reverts to its original condition, with no connection made to battery B1.

A further timing period may be initiated at any time by pressing push-button S1 again. This will cause C1 to be charged once more and the cycle of operation to be repeated, terminating in the ringing of the electric bell.

FURTHER POINTS

A few points concerned with circuit operation need to be discussed in more detail. Two transistors in tandem are employed to operate relay X, since the consequent high gain they provide enables the relay to energise with a relatively low current from capacitor C1. The use of two transistors also ensures that the fall in relay coil current before de-energising takes place is relatively swift, whereupon the length of the timing period is less dependent upon any changes in de-energising current in relay X which may take place. Mechanical performance is liable to cause the current at which relay de-energising takes place to vary with time, whereupon such variations could significantly


affect the accuracy of the timing period if they were not taken into consideration. Silicon diodes D3 and D4 are included in the forward current supply to the base of TR1 to enable relay de-energising to occur when the voltage across C1 is equal to about 2.4 volts, this being the total forward voltage drop across the diodes and the base-emitter junctions of the transistors. Relay de-energising thus takes place when the decrease in voltage across C1 is still proceeding at a reasonably steep region in the exponential voltage-time discharge curve, a factor which further ensures that a relatively swift fall in relay coil energising current takes place. In practice, coil current commences to fall after 95% of the timing period, which would seem reasonable in a simple timing circuit of this nature. The reduction in coil energising current is not so abrupt as to necessitate the usual diode across the relay coil to prevent the formation of back-e.m.f. voltages on de-energising, and such a diode is not employed in the present circuit.

The length of the timing period depends upon the gain of the particular transistors employed in the TR1 and TR2 positions and the coil resistance and de-energising current of relay X. Because of these factors it may be necessary to vary the value of R3 to suit the particular transistors and relay

employed. This procedure is carried out experimentally after the timer has been constructed. In the prototype circuit (in which the relays employed are discussed later) a value of 68kΩ in R3 provided a timing period of about 2½ minutes when R2 inserted minimum resistance into circuit and a timing period of about 4½ minutes when R2 inserted maximum resistance.

Zener diode D1 ensures that the voltage appearing across C1 is reasonably constant when S1 is pressed, and it prevents falling battery voltage from seriously affecting the length of the timing period. The 12 volt battery should, preferably, be discarded when its voltage falls below 10 volts.

The current drawn from the 12 volt battery when S1 is pressed consists of the initial charging currents for C1 and C2, plus some 27mA in R1, 1.2mA in R6, the current flowing in the coil of relay X, and 60mA in R8 and PL1. When the button is released, the current drawn is that flowing through R6, the relay coil and the pilot lamp circuit. The current falls to zero when the timing period ends. Relay Y draws no current directly from the battery since it is energised by the charge in C2. It is desirable to use a separate 3 volt battery for the bell circuit. Electric bells tend to draw a relatively heavy current and it would probably be necessary to insert series resistance if the bell were operated

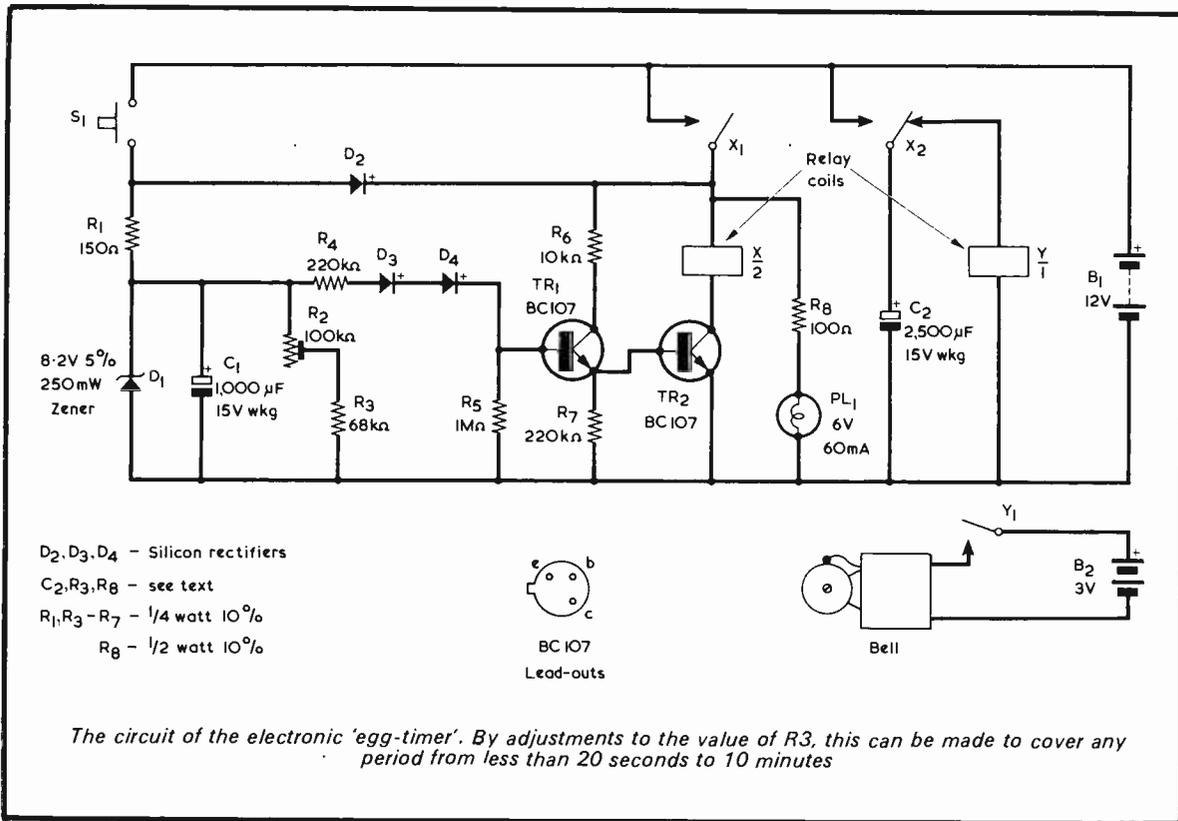

AUDIO AMPLIFIERS



16 Transistor & Valve Designs for the Home Constructor

Amplifiers for Tuner Units, Record Players, Tape Recorders, Public Address, etc., etc.

Includes contributions by such well-known authors as

A. S. Carpenter, A. Kinloch, E. Govier, G. A. French, F. G. Rayer, P. F. Bretherick, K. Jones, D. Aldous, R. Murray-Shelley, C. Swires, G. A. Stevens and V. E. Holley.

Edited by J. R. Davies

124 pages

PRICE 53p

Postage 6p

To: DATA PUBLICATIONS Ltd.,
57 Maida Vale London W9

Please supply copy(ies) of "Audio Amplifiers", Data Book No. 18. I enclose cheque/crossed postal order for.....

Name.....

Address.....

.....RC
BLOCK LETTERS PLEASE

from the 12 volt battery, with a consequent uneconomic demand on that battery.

It is necessary to have pilot lamp PL1 in circuit because this indicates that relay X has 'latched on' after S1 has been pressed. Should S1 be pressed and very quickly released the charge across C1 may not be sufficient to allow relay X to energise. If, however, S1 is held pressed until PL1 lights up, not only is the energising of the relay ensured but so also is the full charging of C1. Since the cold resistance of PL1 is much lower than its resistance when illuminated, the presence of series resistor R8 results in a very small but significant delay before the lamp becomes fully illuminated after contact set X1 closes. Thus, the operator of the timer presses S1 for the short period needed for PL1 to light up, and is then assured that the timer is in the correct condition for a timing period. To minimise battery drain PL1 needs to be a low-current type and the author employed a 6 volt 60mA m.e.s. type here, this being available from Home Radio under Cat. No. PL7. The Home Radio catalogue also lists a 6 volt 40mA m.e.s. bulb under Cat. No. PL5A. This could be used instead of the 60mA type if desired, with a consequent reduction in current consumption from the battery. With the 40mA bulb, R8 should be increased to 150Ω.

COMPONENTS

No great difficulties should be experienced in obtaining the components for the timer. The two transistors are a readily available standard silicon n.p.n. type. Diodes D2, D3 and D4 can be any small silicon rectifiers, such as the Lucas DD000. Zener diodes rated at 8.2 volts 5%, 250mW, are available in various constructions and makes, including the Mullard OAZ206. The resistors are standard components. Preset variable resistor R2 may be a skeleton potentiometer. Both the capacitors should be good quality modern types.

The relays used by the author were P.O. 3000 types having 500Ω coils and the contact sets indicated. P.O. 3000 relays having 500Ω coils and 3 change-over contact sets are available from G. W. Smith & Co. (Radio) Ltd., 3 Lisle Street, London W.C.2, and these could be employed with no connections made to the unused contacts. G. W. Smith & Co. will also make up relays to customer's specification as, similarly, will L. Wilkinson (Croydon) Ltd., Longley House, Longley Road, West Croydon, Surrey. As was mentioned earlier, however, the relays are not at all critical and any relays having the requisite contact sets, a coil resistance of 400Ω or more and the ability to energise reliably at 9 volts may be used in the circuit.

In the prototype, the 500Ω relay employed for relay Y energised for

about 4 seconds after the completion of the timing period, this being more than adequate for the ringing of the electric bell to attract attention. The bell-ringing period will be increased if a relay having a coil resistance higher than 500Ω and the same energising voltage is employed. Alternatively, the value of C2 could be reduced for the same bell-ringing period with such a relay.

The 12 volt battery, B1, can be made up with two 6 volt batteries, or four 3 volt batteries, in series as desired. If extensive use is to be made of the timer, four 3 volt cycle lamp batteries (Ever Ready type 800) could be used. A 3 volt cycle lamp battery would be a good choice, also, for B2.

CONSTRUCTION

The method of construction is left to individual choice. Probably the best approach would consist of housing all the parts in a small wooden case with S1 and PL1 on the front panel. The bell could be mounted on the side of the box. Component layout is in no way critical.

When wiring up, R3 and C2 should be connected into circuit temporarily only, as they may need to be changed. When wiring is completed the circuit should be given several test runs to ensure that it functions correctly. If C1 has been in store for a considerable period these test runs will also enable it to 'form' and settle down to its final value.

The length of the timing periods given with R2 first inserting zero resistance and then inserting full resistance should next be measured. If the circuit is to be employed as an egg-timer, the final timing period required will probably be, say, 3½ minutes. If the extreme settings of R2 result in periods on either side of 3½ minutes then R2 may be adjusted until this period is provided. Should it be found that the extreme settings of R2 result in periods that are both shorter than 3½ minutes the value of R3 should be increased, as required; whilst if the test periods are both longer than 3½ minutes the value of R3 should be reduced.

The timer can be used for other applications, and by suitable adjustments in the value of R3 may be made to cover any period from less than 20 seconds to 10 minutes.

The final process consists of checking the length of time during which relay Y energises at the end of the timing period. If this length of time is too long the value of C2 may be reduced. An insensitive relay may result in too short a length of time during which the bell rings, whereupon the value of C2 needs to be increased. Judging from the writer's experience with the prototype, however, it is doubtful whether an increase in the value of this capacitor will be required.

NOTES ON SEMICONDUCTORS

Further Notes-8 by P. WILLIAMS

KEEP IT SIMPLE

The current gain of silicon transistors can be determined with the aid of a circuit comprising two fixed resistors, a variable resistor and a voltmeter

THE CIRCUIT TO BE DESCRIBED THIS MONTH IS ALMOST sinful in its simplicity. It allows the measurement of current gain for a silicon transistor though under a somewhat restricted range of operating conditions.

EQUIPMENT NEEDED


The equipment needed for this transistor tester is:

- (i) a voltage supply capable of supplying a few mA, voltage not critical though 5 to 6V is quite convenient.
- (ii) a fixed resistor, typically $1k\Omega$.
- (iii) a resistor variable from about $10k\Omega$ to $500k\Omega$
- (iv) a sensitive voltmeter, calibration unimportant.

Thus the cost can be very low if there is such a meter available – such a one as might be used for detecting unbalance of a bridge circuit.

The procedure is as follows. Start with R_1 of Fig. 1 at its maximum value and then reduce until the meter *just* reads zero. At this point the collector voltage must have fallen to equal the base voltage. This condition for the large majority of silicon transistors still leaves the transistor with a current gain almost equal to its value at the more usual voltages of, say, 2 to 20V. This is illustrated in Fig. 2 with typical output characteristics where the spacing between the characteristics has barely started to narrow at $V_{ce} = 0.5V$, i.e. where $V_{ce} = V_{be}$.

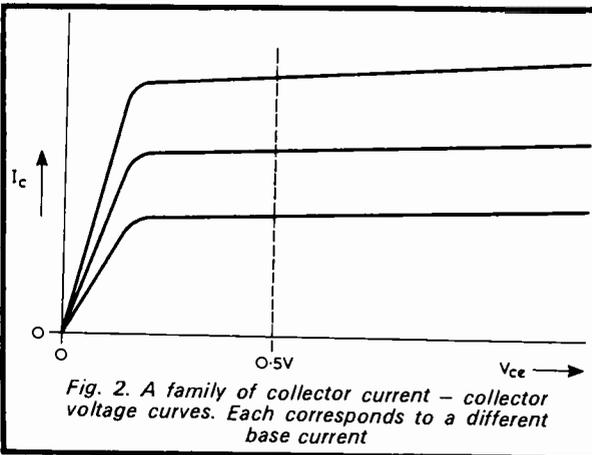To protect the meter against excessive current under fault conditions or where the collector current falls to zero for some reason, the meter should be switched to a higher voltage range until balance is almost reached. Alternatively any diode, either silicon or



germanium, may be placed in parallel with the meter as shown dotted in Fig. 1. This limits the meter p.d. to a few hundred millivolts even under fault conditions.

The variable resistor R_1 may be a calibrated potentiometer, preferably with a logarithmic law to prevent cramping of the scale by allowing a change of current gain of a given percentage to be as clear at low gains as at high gains. A limiting series resistor of say $1k\Omega$ in the base prevents excessive current. An interesting modification is to replace R_1 by a set of switched resistors of preferred values between say $10k\Omega$ and $470k\Omega$. This covers the gain range from 10 to 470, since at the balance point the voltages across R_1 and R_2 must be equal, i.e. $I_b R_1 = I_c R_2$.

But $I_c/I_b = hFE = R_1/R_2$. Hence (ignoring the base current limiting resistor) the current gain equals the value of R_1 in $k\Omega$ at which balance is achieved – provided $R_2 = 1k\Omega$. (The calibration of R_1 at low gain settings should take up the value of the series limiting resistor). If switched fixed resistors are used, no particular resistor will give exact balance but switching between one resistor and the next will cause the meter reading to change from positive to negative as balance is passed. Then the appropriate current gain can be estimated from these two values.

It must be noted that the current gain is measured at a fixed current of about 5mA. Other values of resistance and/or supply voltage may be used if testing at other currents is required. One snag of the switching method is that the meter reading jumps between switch positions. It remains the only method if the experimenter has no means of calibrating the variable resistor. While readings can only be made at 20% intervals using standard value resistors, this is good enough for most purposes. It may be worth while noting that the current gain at collector voltages up to 10V is likely to increase by less than this amount. ■

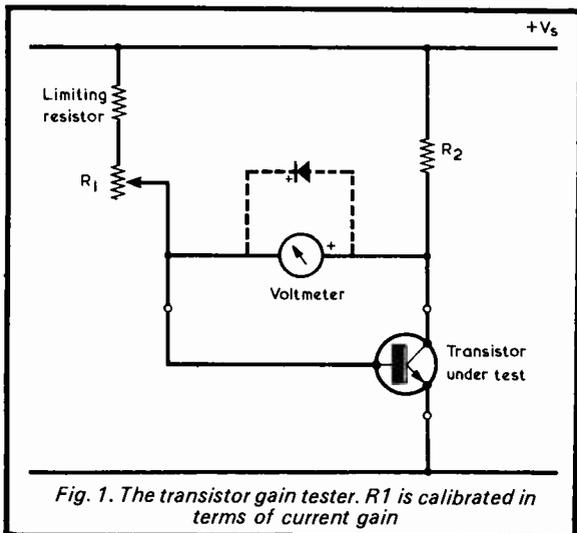


Fig. 1. The transistor gain tester. R_1 is calibrated in terms of current gain

BOURNS POTENTIOMETERS NOW ALSO MADE IN SCOTLAND

The Bourns Model 3700 and 3707 wirewound precision potentiometers are now made at their plant in Scotland



which backed up by their extensive production facilities in the U.S.A. supports their claim to be able to provide customers with two sources of supply for every popular model in their range. These 10-turn potentiometers are $\frac{1}{2}$ in. in diameter, bushing mount with a $\frac{3}{32}$ in. shaft.

Brief Specifications:

	3700	3707
Resistance Range:	50 Ω to 100K Ω	100 Ω to 100K Ω
Resistance Tolerance:	$\pm 5\%$	$\pm 5\%$
Independent Linearity:	$\pm 0.5\%$ max.	$\pm 1.0\%$
Effective Electrical Angle:	3600 $^{\circ}$ (+20 $^{\circ}$ -0 $^{\circ}$)	3600 $^{\circ}$ (+10 $^{\circ}$ -5 $^{\circ}$)
Power ratings:	1.0 watt @ 70 $^{\circ}$ C 0 watt @ 125 $^{\circ}$ C	1.0 watt @ 40 $^{\circ}$ C 0 watt @ 105 $^{\circ}$ C


HIGH QUALITY MINIATURE LOUDSPEAKERS

A high quality miniature moving coil loudspeaker with a frequency range of up to 5KHz is now available on the U.K. market from B. & Y. (Gates) Electronic Developments Limited, 26 Uxbridge Road, London W5 2BP.

The Company, members of the Interby Group, has already received full approval for the unit which is in use in Government Departments.

Mr. Anthony Young, Managing Director of B. & Y. (Gates) said that the loudspeaker had been designed and developed for all-purpose uses and was ideally suited for pocket paging systems.

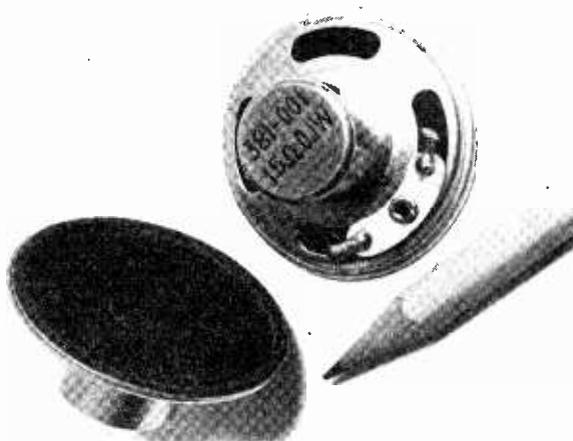It has a power output of 0.1 watt and an impedance of 15 ohms. Measuring 1.5in. diameter \times 0.65in. depth, the speaker can be supplied ex stock. Full technical specifications together with a typical frequency response graph may be obtained from the Company on request.



NEW FEATURES FOR AVO'S MULTIMINOR

Avo introduce the new pocket-size Multiminor Mark 5 which is designed to replace the popular Avo Multiminor Mark 4. It is similar in appearance and identical in size, but in this new model modern technology provides new improved features. Serviceability is simplified and reliability is increased by the use of thick film techniques.

The front panel and case of the Multiminor Mark 5 are black mouldings and the new range selector switch is in contrasting silver grey, with the ranges clearly marked with both conventional and international symbols.

The specification is unchanged, the sensitivity of 10,000 Ω /V and the accuracy of 2.25% on d.c. voltage and current and 2.75% on a.c. voltage ranges ensure that this compact, lightweight instrument is ideal for use by the radio and television service engineer.

Provision is made for the measurement of d.c. voltage between 100mV and 1000V, a.c. voltage between 10V and 1000V, and d.c. current between 0.1mA and 1A. Two basic scales are provided each approximately 70mm (2 $\frac{3}{4}$ in.) in length. The inner is used for resistance measurements up to 20m Ω and scaled 0 - 2k Ω , the outer scale, calibrated 0 - 25 and 0 - 100, is used for all a.c./d.c. voltage and d.c. current measurements.

The Mark 5 is supplied in an attractive black carrying case.

THE RADIO CONSTRUCTOR



USING THE U.J.T.

By
M. HARDING

This article discusses the basic operation of the unijunction transistor and its employment as a relaxation oscillator. It then describes a practical square wave generator which incorporates a unijunction transistor, and which has a wide frequency range and excellent output waveform.

THE UNIUNCTION TRANSISTOR (U.J.T.) HAS BEEN around now for quite some time, but not a great deal has been said about it. It is an interesting device with a primary application in relaxation oscillator and timing circuits. In order to become intelligent users of any semiconductor device it is necessary to acquire at least a brief insight into the way in which the device functions. Therefore the next section outlines the way in which the unijunction transistor works, and this is followed by a practical application in which a unijunction transistor is employed in a wide range square wave generator.

BASIC CHARACTERISTICS

The symbol for the U.J.T. is shown in Fig. 1(a) and the basic internal structure of the early devices is shown in Fig. 1(b).

Essentially, the device consists of a bar of n type silicon with non-rectifying, or ohmic contacts, attached to each end. These contacts are called 'base 1' and

'base 2'. Normally base 2 is made positive with respect to base 1 and a current flows through the base material, which forms a linear resistance. Typically, this resistance lies between 5 and 10k Ω . In addition to the two base contacts a third contact is made on the bar near the base 1 contact. This time, however, the contact is a rectifying contact and is in the form of a small piece of p type silicon. The contact is called the emitter and it will be fairly clear to see that if a potential of some 9 or 10 volts is applied between base 2 and base 1, then the bar will behave as a potential divider with respect to this emitter connection. Indeed, the proportion of interbase voltage which appears between base 1 and the emitter junction effectively reverse biases the emitter diode. It is this proportion which represents one of the most important device characteristics and it is called the 'intrinsic stand-off ratio'.

The most interesting characteristic of the U.J.T. is seen if we explore its behaviour when the emitter is made positive with respect to base 1. This can best be visualised by plotting a graph of emitter voltage against emitter current as seen in Fig. 2.

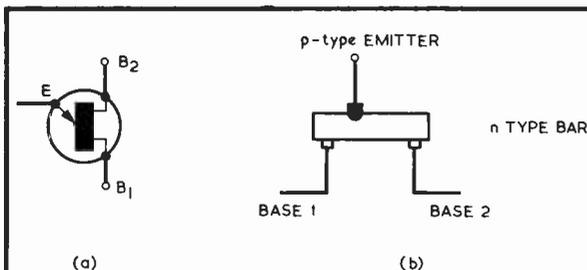


Fig. 1 (a). Circuit symbol for the unijunction transistor

(b). The basic construction of the transistor

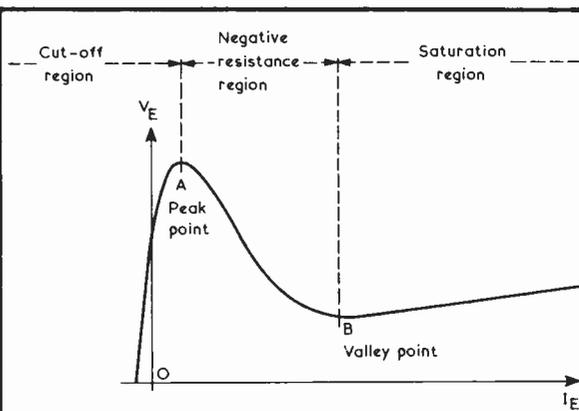


Fig. 2. Emitter voltage - emitter current characteristic of the unijunction transistor

Initially, as the emitter voltage rises the emitter current is very small indeed, usually just a few microamps. When the emitter voltage exceeds the reverse bias, point A is reached and the emitter injects current into the base. The point A is another important device parameter: it is called the 'peak point emitter voltage' and is denoted by V_p . The current flows in the direction of the applied electric field towards base 1 and thereby causes a decrease in the resistivity of that region. The consequence of this is that as the emitter current rises the emitter voltage drops and a region of negative resistance results. Eventually at point B, called the 'valley point', saturation sets in and a positive resistance characteristic exists once again.

It should be noted that in present-day devices a cube structure has been adopted in the manufacture of the device instead of the bar configuration, but the basic principle of operation remains unchanged.

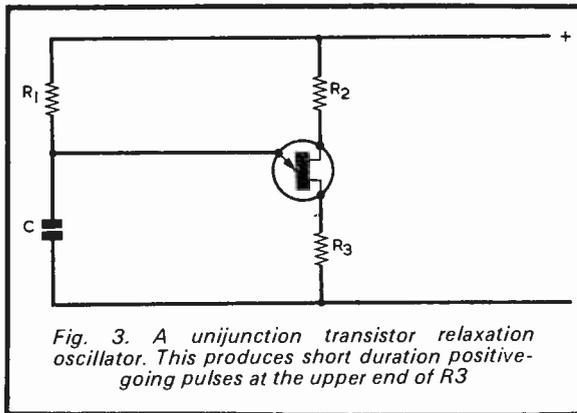


Fig. 3. A unijunction transistor relaxation oscillator. This produces short duration positive-going pulses at the upper end of R3

RELAXATION OSCILLATOR

The simplest circuit using a U.J.T. is shown in Fig. 3. This basic circuit produces an exponential sawtooth across the capacitor and a short duration positive-going pulse across the base 1 resistor R3. The way in which the circuit functions is quite simple to see. The U.J.T. is initially cut off and so the capacitor C charges through R1 until the emitter potential reaches the peak point value. The U.J.T. then fires, discharging the capacitor through the emitter diode. The current is limited by R3 and the discharge continues until the capacitor current reaches the valley point emitter current value. At this point the U.J.T. abruptly cuts off and the whole cycle repeats.

With regard to practical component values, R2 is usually 680Ω with a 9V supply and is included to help stabilize the emitter peak point voltage against temperature effects. R3 is not critical and a value of 120Ω is common. The period of oscillation is, of course, fixed by the combination of R1 and C. A lower limit to the value of R1 is set by the fact that the load line drawn on the V_e-I_e characteristic must intersect the region of negative resistance. A minimum value of $10k\Omega$ is typical. The maximum value of R1 is determined by the emitter drive requirements and $250k\Omega$ would be a safe maximum for devices in common use. An upper limit for the capacitor value would typically be $10\mu F$ in order to limit the amount of energy dissipated in the emitter diode during the discharge phase of the cycle.

Using the maximum values of R1 and C just indicated and by employing the popular U.J.T. type 2N2646, one will obtain a short positive pulse, produced across R3, about every 3 seconds. With a capacitor value of $1000pF$ and R1 around $10k\Omega$, an output pulse repetition frequency of some $100kHz$ would be produced.

It will be clear from the above discussion that this simple circuit could form the basis of a number of interesting designs. If R1 is made a variable resistor in series with a fixed resistor, and various values of C are switched into circuit, then we have a variable wide frequency range source of positive trigger pulses. We will now consider how this circuit may be used as the basis of a wide frequency range square wave generator.

PRACTICAL CIRCUIT

As many readers will know, square waves are very useful for checking the performance of an audio amplifier in conjunction with an oscilloscope. Indeed a square wave generator which can have its frequency continuously adjusted constitutes a useful addition to any home laboratory.

Fig. 4 shows the basic U.J.T. relaxation oscillator of Fig. 3 used to trigger a conventional divide-by-two bistable via an inverting stage. It will be seen at once that the fixed resistance of Fig. 3 has been replaced by a variable resistor in series with a fixed resistor. Four capacitor values may be switched into circuit by S1(a) which, together with VR1, enables the frequency to be continuously adjusted between upper limits determined by the value of the fixed resistor and lower limits determined by the maximum value of the potentiometer.

The positive-going pulse from R3 is coupled via C5 to the base of TR1 which is biased into its active region by R4. On each positive pulse TR1 conducts sharply and passes a negative-going pulse into the steering diodes D1 and D2. Initially the bistable, which is made up of transistors TR2 and TR3, takes up some arbitrary state. Either TR2 will be on and TR3 off or vice versa. The steering diodes D1 and D2 effectively route the negative-going pulse from TR1 to the base of the transistor that is on and flips the bistable into its complementary state, in which it remains until the next negative-going pulse arrives from TR1. The result is that the bistable changes state once for every pulse produced by the U.J.T. and in consequence anti-phase square wave outputs are available from the collectors of TR2 and TR3.

The table shows the frequency ranges obtained with the prototype. It should be noted that the frequencies listed refer to the output from the bistable which is, of course, dividing the pulse repetition frequency of the U.J.T. relaxation oscillator by 2.

In Fig. 4 the collector of TR3 is shown as being directly coupled to the output socket. This arrangement was used in the prototype in order to maintain a good

TABLE
Square wave generator frequency ranges for different values of C (C1 - C4 in Fig. 4)

Capacitor	Frequency Range
$1\mu F$	2Hz - 55Hz
$0.1\mu F$	20Hz - 550Hz
$0.01\mu F$	200Hz - 5.5kHz
$0.001\mu F$	2kHz - 55kHz

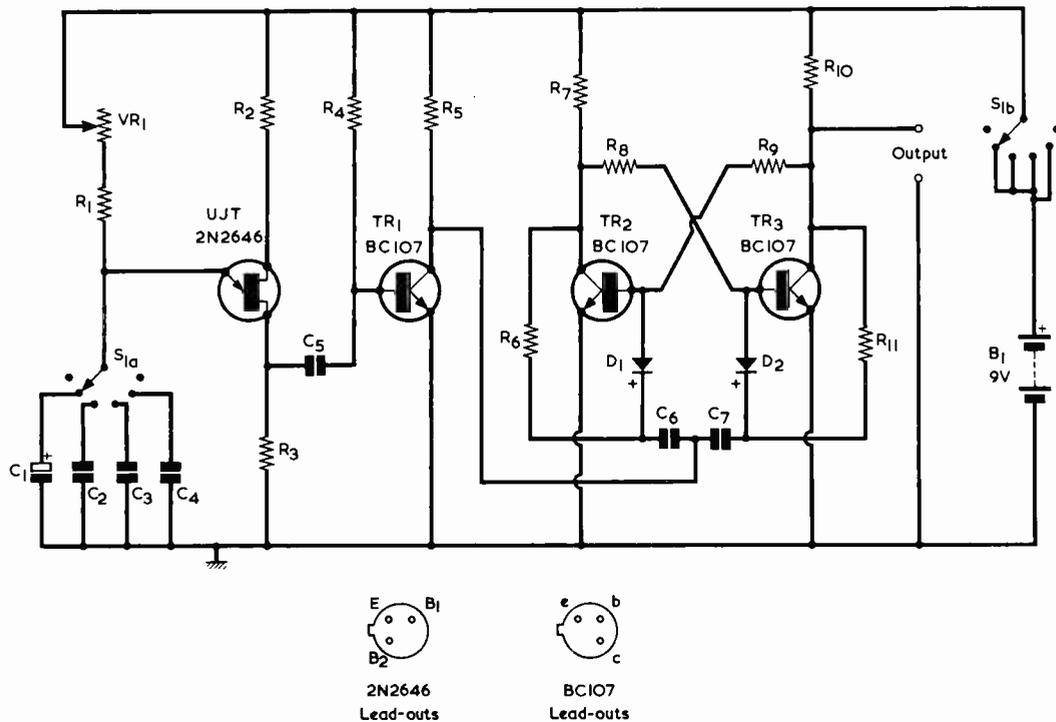


Fig. 4. A practical square wave generator incorporating a unijunction transistor relaxation oscillator for frequency control

COMPONENTS

Resistors

(All fixed values $\frac{1}{8}$ watt 10%)

R1	10k Ω
R2	680 Ω
R3	220 Ω
R4	1M Ω
R5	5.6k Ω
R6	15k Ω
R7	1k Ω
R8	5.6k Ω
R9	5.6k Ω
R10	1k Ω
R11	15k Ω
VR1	250k Ω potentiometer, linear

Capacitors

C1	1 μ F electrolytic, 40 V. Wkg., Mullard miniature
C2	0.1 μ F polyester
C3	0.01 μ F polyester
C4	0.001 μ F polyester
C5	0.001 μ F plastic foil
C6	0.001 μ F plastic foil
C7	0.001 μ F plastic foil

Semiconductors

U.J.T.	2N2646
TR1	BC107
TR2	BC107
TR3	BC107
D1	OA91
D2	OA91

Switch

S1	2-pole 6-way, miniature rotary
----	--------------------------------

Battery

B1	9-volt battery type PP3 (Ever Ready)
----	--------------------------------------

Miscellaneous

2 pointer knobs
 2 wander plug sockets
 Connectors for B1
 Veroboard, 0.1in. matrix (see Fig. 5)
 18 s.w.g. aluminium sheet (see Fig. 6)
 4 small grommets

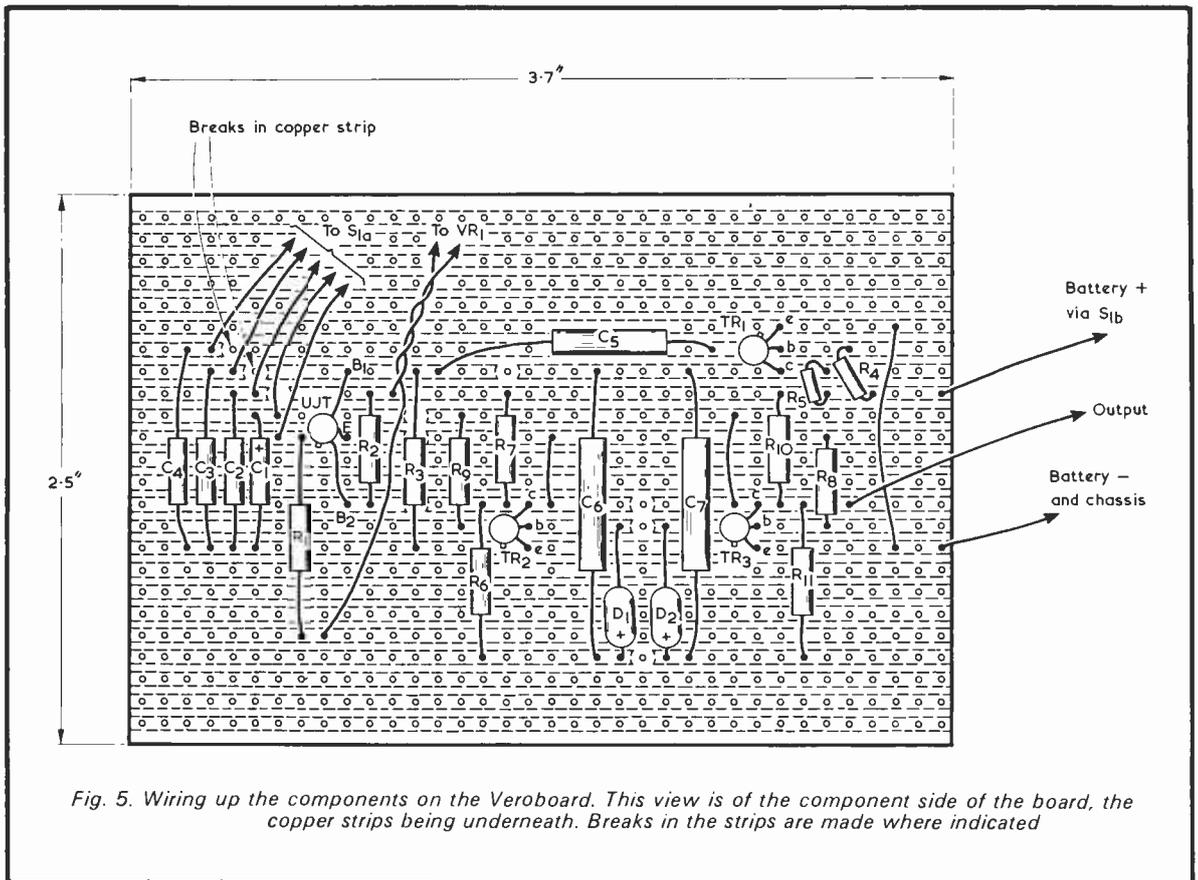


Fig. 5. Wiring up the components on the Veroboard. This view is of the component side of the board, the copper strips being underneath. Breaks in the strips are made where indicated

response down to the lowest frequencies. However, for many purposes d.c. isolation from the collector of TR3 would be desirable and an output coupling capacitor of 100 μ F would give acceptable results in most applications.

Although not employed in the prototype, a 250 μ F 10 V.Wkg. electrolytic capacitor could be added across the supply lines. This capacitor could improve performance when the internal impedance of the battery increases with age.

It will be seen that S1(a)(b) is a 6-way component. The four central positions select the frequency ranges by way of S1(a), whilst the two outside positions cause the generator to be switched off at S1(b).

The current consumption from the 9V battery is a nominal 12mA.

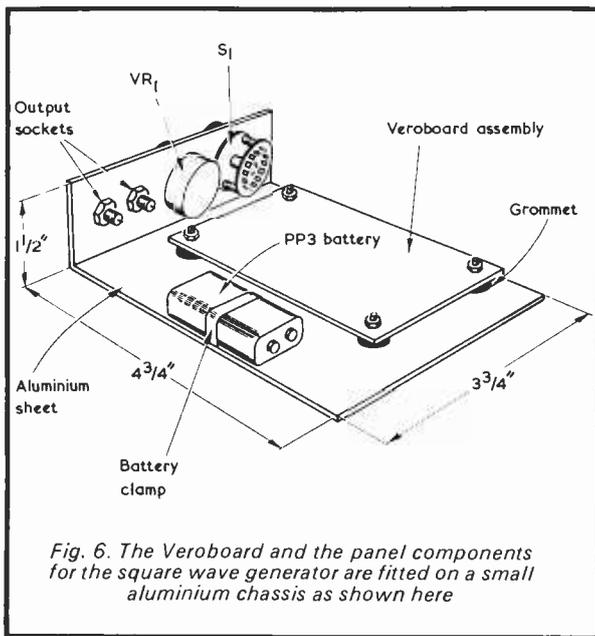


Fig. 6. The Veroboard and the panel components for the square wave generator are fitted on a small aluminium chassis as shown here

CONSTRUCTION

The layout of the generator is in no way critical and the original was wired up on a piece of Veroboard, with copper strips, measuring 3.7 by 2.5in. The Veroboard had a 0.1in. matrix. The layout details of the original are shown in Fig. 5.

Great care has to be taken when soldering on this fine matrix to ensure that the solder does not run across adjacent copper strips. The use of 22 s.w.g. solder and a soldering iron with a 2mm. bit has a lot to commend it.

The board was mounted on an aluminium plate using 0.5in. 6 B.A. bolts. The board was spaced away from the aluminium plate by small grommets as shown in Fig. 6. A small aluminium front panel carried the frequency controls together with the output sockets.

The unit as a whole forms a useful wide frequency range square wave generator module.

THE RADIO CONSTRUCTOR



Q S X

By
FRANK A. BALDWIN

(All Times GMT)

In the last QSX (May issue, page 607) mention was made of Radio Curom, Netherlands Antilles, broadcasting on a measured frequency of **20778**, reception here in the U.K. In this issue, we report reception of Radio Curom on **17513** by a BADX (British Association of Dx'ers) operator from 1500 through to 0400 on various days and times within the GMT limits mentioned. The frequency stated is subject to some variation from day to day.

However, there is some doubt about these transmissions and the theory has been put forward in 'Bandspread', the journal of BADX, that these programmes were those of Radio Curom and that they did, in fact, originate in Willemstad - their transmission on PTP frequencies being due to the whim of an engineer preferring such programmes instead of a marker or test tape when keeping the channel open - I am inclined to agree with this conclusion.

● UNID.

In dyed-in-the-wool S.W.L. language, this sub-head simply signifies 'unidentified', its appearance usually causing many operators to tune to the particular frequency mentioned, switch in the preselector, and to sharpen up the selectivity, the pencil and the ears. What are the top-flight operators trying to identify this time? Well, at the time of writing, attention is centred on two channels in the 60 metre band - details herewith.

On a measured frequency of **4968** we have logged a weak transmission in the Arabic language on several occasions during the time period 1930 to 2100. Now **4968** is an old channel of Radio Kuwait and the question is - is this Kuwait back on the channel as of yore? It seems the most likely answer.

The second unid. is on **4985** where we heard a weak signal in an unknown language from 1930 through to 2030, the signal being heard on several different occasions.

After a landline contact, two top-flight SWL's, Alan B. Thompson of Neath, and Glyn H. Morgan of Tredegar, brought themselves into action and suggested the possible answers after having logged these transmissions.

In the second case, the probable answer is that the unknown language is Malgache and that, after hearing the news in French at 2030, the transmission emanates from Radio Tananarive, this being a channel once used by this station in the past.

Can you, the reader, confirm or deny?

● MYSTERY SOLVED - AGAIN

In the last QSX, under the Mystery Solved sub-head, information was given on the **9020** transmission of Radio Teheran reported by B. Walsh of Romford and also heard by us. It would appear that we have to solve the mystery once more, for it appears that Radio Teheran is a confirmed wanderer, being logged by us on a measured **9004** around 2025 recently. According to BADX, this station has sojourned briefly on **7038**, **9020V** (V = varies) **12165** and **12176**. Just where it will be by the time these lines appear in print is anyone's guess!

● LATIN AMERICA

The LA's have been coming through quite well of late, two short sessions providing the following results:

4790 0240 HCVP2 Sistema de Emisora Atalaya, Guayaquil, Ecuador, with prolonged discussion in Spanish, YVON in the background with sports commentary. Schedule from 0100 to 0455, 10kW (62.63m).

4832 0530 TIHB Radio Capital, San Jose, Costa Rica, with LA music and several identifications, terrific signal. Schedule is 24 hours, 1kW listed (62.09m).

4880 0235 Radio Universo, Barquisimeto, Venezuela, with typical Latin American music and songs. Schedule 1000 to 0400, 10kW (61.48m).

4980 0228 Ecos del Torbes, San Cristobal, Venezuela, LA songs and music. Schedule not published, 10kW (60.25m).

5010 0545 HIMI Radio Cristal, Santo Domingo, Dominican Republic with music and songs of

Hispanic America. Schedule 24 hours, 1kW (59.88m).

5040 0225 YVQH Radio Maturin, Maturin, Venezuela, with identification followed by the inevitable LA music. Schedule 1000 to 0400, 1kW (59.55m)

● MOZAMBIQUE

Radio Clube Mozambique, in addition to being heard on **4762** (63.00m) as reported in "Short Wave News" this issue, has also been logged recently on **4855** (61.79m) with full station identification in Portuguese at 2100 and followed by a programme of dance music. The address is - P.O. Box 594, Lourenco Marques.

● YEMEN

Radio Sana'a has been reported on **5804** (51.68m) at 1930 with a talk in Arabic.

● SAUDI ARABIA

The Saudi Arabian Broadcasting Service is reported by BADX on **5987** (50.11m) at 2300 with identification in Arabic after a reading of the Koran, sign-off with National Anthem followed. Formerly on **6000**.

● CHINA

BADX reports Radio Peking on **9390** (31.93m) escaping the usual jamming when transmitting the Russian Service. Nothing unusual about the frequency or the programme content, the interest lies in the absence of jamming and more so in the fact that the tape was played forward and not backward - yes, backward - it is one of the mysteries of the short wave world. Why are the Russian programme tapes often run through in reverse?

● GAMBIA

Radio Gambia may be heard on **4820** (62.24m) at 2256 with identification and the news headlines in English and Madinka, sign-off at 2300 with the National Anthem.

● GUINEA

Radio Conakry can be heard on **4910** (61.48m) where it was logged by us at 1935 with a drama in an African dialect.

● CLANDESTINE



Radio Free Portugal is reported on **12010** (24.98m) at 1205 and also in parallel on **15480** (19.38m), both signals being jammed (as usual!).

A Table-Top Work Bench


By
Arthur C. Gee, G2 UK

★ ★ ★

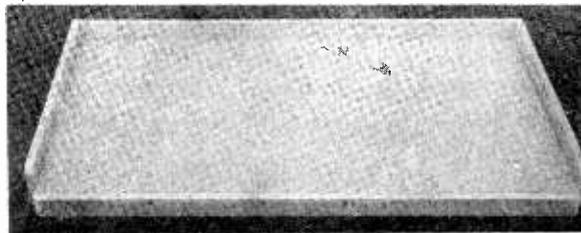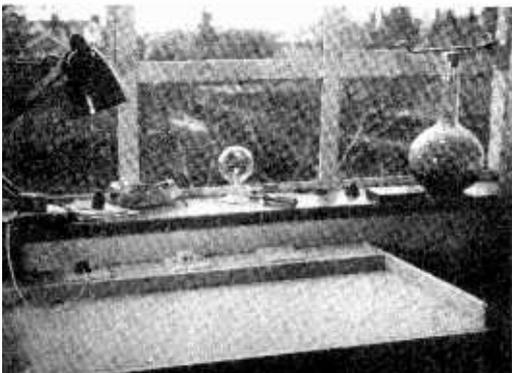*Completed work bench in position on top of a
"Z" bed*



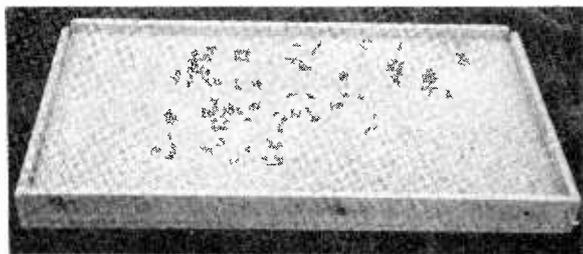Chipboard working surface, with strip wood each side and along the rear edge



Under-surface of the bench. Strip wood side-pieces are taken down all round to make a 'lip' to fit bench firmly on top of table, etc




The mains power supply points ready to be fitted to the bench

THE RADIO CONSTRUCTOR

WITH THE MINIATURISATION OF RADIO AND electronic equipment these days, what with printed circuit boards, transistors and integrated circuits, the large 'shack-size' work bench is hardly necessary for the hobbyist radio constructor now.

The writer recently made up a small work bench to fit on top of a 'Z' bed, and this has served its purpose so well that he felt other readers might be interested in the idea. Made to fit an occasional kitchen table, or even to go over one end of the proverbial kitchen table, with this table-top bench one can leave everything out on the bench without having to clear it away and simply stow it away under the bed or on top of the wardrobe until one has time to do a bit more to the project under construction.

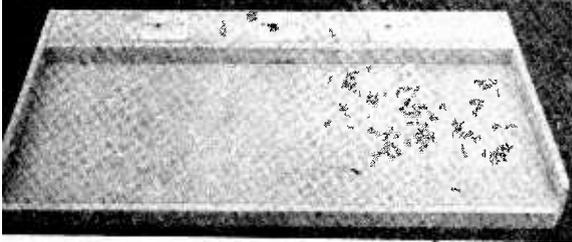

The work bench with power supply points fitted



Wiring completed on the power point sockets



Three switched sockets are fitted to a batten cut to fit the rear edge of the bench

The table-top work bench in use



A piece of chipboard, half an inch or so thick and cut to just cover the top of the table, has three side pieces of $\frac{1}{4}$ inch thick wood strip screwed to it as shown in the photos; one along the back and two down each side. These are wide enough to extend down around the edges of the table to just make a snug fit, so as to stop the work bench sliding off the top of the table. A fourth piece is fitted to the front edge of the work bench, but is only wide enough to complete the work bench edging in a downward direction. It prevents the work bench sliding backwards off the table top. In other words, do not have the back and sides type of 'edging' on the front of your work bench as well, as it will interfere considerably with easy working on the bench. The photographs make this point clear.

Along the back of the bench, three switched, three-pin mains sockets are fitted. These can be of the skirting board type as shown in the photos. This is a well worthwhile feature to incorporate, so that soldering iron, test equipment and the gear under construction can be easily plugged into the mains supply. These plugs are wired up in parallel with heavy duty flexible three-core electric cable, of sufficient length to go to the nearest power socket in the work room.

It had been intended to make an Anglepoise electric reading lamp a permanently fitted fixture to the work bench, but it was realised that to do so would make the bench much less easy to stow away when not in use. By keeping all tall items movable, it can more easily be stored away under the bed, chest of drawers, or other convenient out-of-the-way place, thereby pleasing the 'lady-of-the-house'!

There is little need to describe the construction of the bench further, since the photos illustrate well the various stages in its assembly. Since making up this little work bench, the writer has found that the old adage of 'building it on the kitchen table' to be a far less awkward procedure than hitherto. The new table-top work bench, which can be stowed away when not in use, is a far more acceptable item with the domestic side of the household than were his previous requests for a 'corner-of-the-kitchen-table-for-an-hour-or-so, please!'

WINDING TOROIDAL COILS

By
C. DICKSON

The unusual approach described here can ease the problem of winding these difficult coils.

OCCASIONALLY, THE HOME-CONSTRUCTOR FINDS IT necessary to wind a toroidal coil; that is, a coil which is wound on a core shaped like an American doughnut. Alternatively, he may find it necessary to wind a coil on a former which is so positioned on a chassis that it is impossible to wind the wire on directly. In either instance it is necessary to poke the wire through the centre of the toroidal core, or through the accessible section of the awkwardly placed former, and pull the whole length of the wire through for each turn until the coil is completed.

EASIER METHOD

If high coil voltages are not involved and a scramble-winding can be permitted, the process of winding a toroidal coil can be made considerably easier by taking advantage of the method to be described.

The explanation of this technique is best illustrated by a typical example. Let us say that we wish to scramble-wind 60 turns of wire on a toroidal core (or on a difficult-to-reach former). We first of all work out approximately the length of wire required for the coil by putting one turn on the core (or former) and measuring the length of wire involved. If the single turn requires 2in., then the total length of wire needed will, at a first approximation, be 60 times 2in., which works out at 120in. or 10ft. However, as the coil will be a scramble-winding some of the turns will rest on top of others and will require more than 2in. of wire. It would be best to allow a reasonable amount for this effect and, also, for the provision of lead-outs, and so it would be advisable to assume we will require an additional 25%, which means that we should allot 12½ft. of wire for the coil.

We next cut off 12½ft. of the wire to be used and double it back on itself, as in Fig. 1(a). This gives us a 6¼ft. length of double wire. We anchor the two 'open' ends of this double length of wire to the core and proceed to wind 30 turns of the double wire on to the core. There will be no greater difficulty in pulling the 'closed' end of the double wire through the core centre than there would be in putting a single wire through. Once the 30 turns have been wound on, the double wire at the end of the coil is secured to the core, and the coil has the appearance shown in Fig. 1(b).

Next, we cut the wire at the 'closed' end of the coil

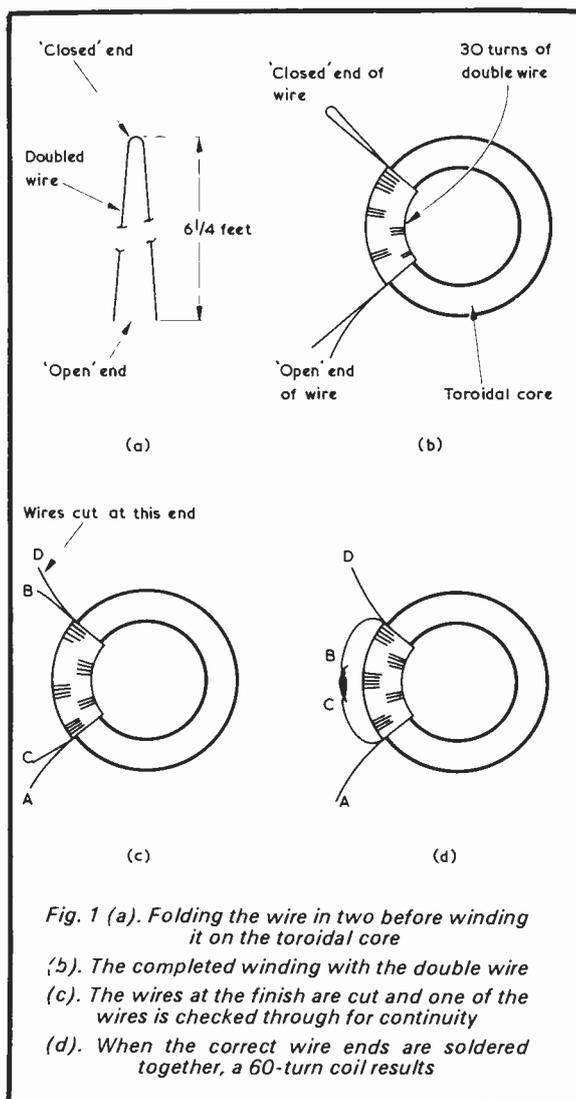


Fig. 1 (a). Folding the wire in two before winding it on the toroidal core
(b). The completed winding with the double wire
(c). The wires at the finish are cut and one of the wires is checked through for continuity
(d). When the correct wire ends are soldered together, a 60-turn coil results

whereupon there are two free wires at this end as well as two free wires at the start of the winding. We now have two 30-turn coils on the core and all we have to do, to obtain a 60-turn coil, is to connect them in series! Take up a continuity tester, such as a multi-testmeter switched to an ohms range, and connect it to one of the coil wires at the start of the winding. Then find the corresponding wire at the finish of the winding, and connect this to the other wire at the start. The two remaining free ends are now the connections to the 60-turn coil. The idea is illustrated in Figs. 1(c) and (d). In Fig. 1(c) the two wire ends with continuity between them are shown as A and B, the other two ends being C and D. Wire B is joined to wire C and the coil terminations are provided by A and D.

FURTHER DOUBLING

The approach can be taken a stage further by folding the original wire 4 times or 6 times. Fig. 2(a) shows the wire folded 4 times. Working from the previous example we now need to put only 15 turns of this 4-fold wire on the core to obtain an eventual 60-turn coil. The folded ends which are pushed through the core need to be

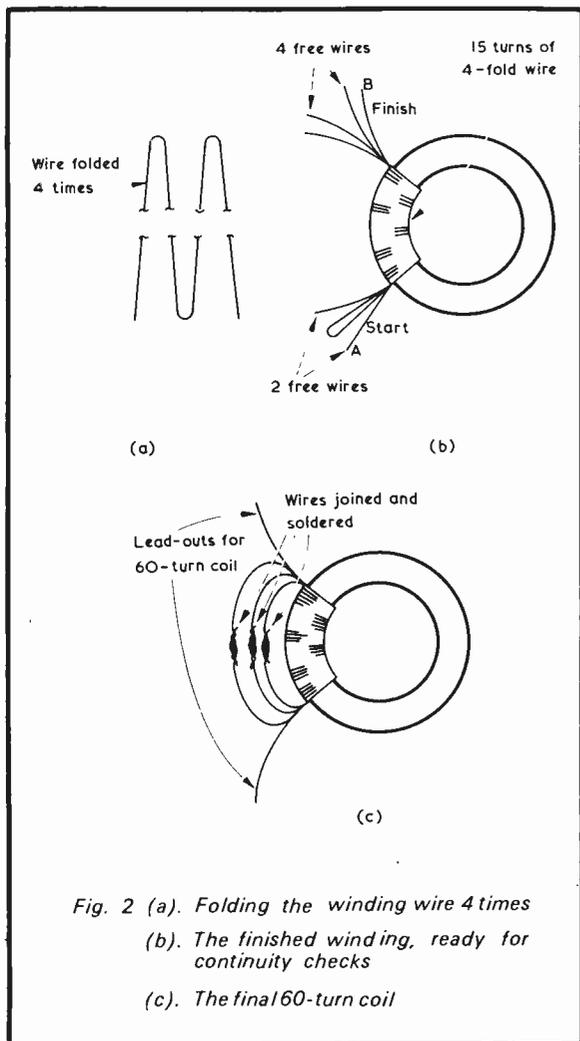


Fig. 2 (a). Folding the winding wire 4 times
 (b). The finished winding, ready for continuity checks
 (c). The final 60-turn coil

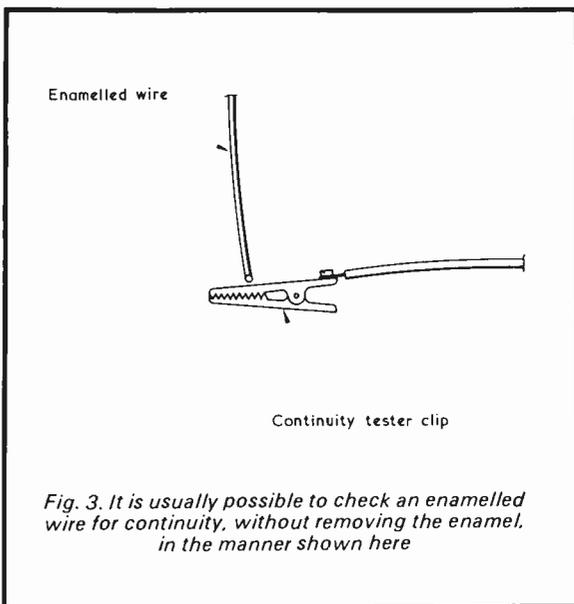


Fig. 3. It is usually possible to check an enamelled wire for continuity, without removing the enamel, in the manner shown here

twisted or soldered together to ensure that they can be handled easily.

When the 15 turns of the 4-fold wire have been wound on, the final coil is produced in the following manner. First, as in Fig. 2(b), cut the wires at the finish of the winding so that there are now 4 free wires here. Connect the continuity tester to one of the free wires at the start of the winding and find the corresponding wire at the finish of the winding. See Fig. 2(b), where the wire ends are shown as A and B. Next, cut the joined wires at the start of the winding and connect end B to either of these. Leaving the continuity tester still connected to wire end A, find the next free wire at the finish of the winding which indicates continuity. Connect this wire to any of the remaining free wires at the start of the winding, and repeat the process until the winding connections are complete, as shown in Fig. 2(c.)

The same procedure is followed with a 6-fold wire and, working to our example, only 10 turns of such wire would be required.

As may be gathered, there is an optimum number of folds in the wire for any particular coil, since the saving in coil winding time is offset by the time taken in tracing through the wire ends and suitably connecting them together afterwards. Usually, a 2-fold or 4-fold approach affords the best results. A further possible disadvantage is that a 4-fold or 6-fold winding could look a little more untidy than a winding made with single wire or with a 2-fold wire. However, a competent constructor should be able to make a neat job of any of the versions.

A few final tips may be of assistance. The solder joints between wire ends can be insulated by passing a length of sleeving over one of the wires before soldering. The sleeving is then pulled back along the wire to cover the joint. Another dodge is that it is often possible to trace out an enamelled wire by a continuity test without removing any of its enamel, this being especially true of the thicker wires. If the cut end of the enamelled wire is held against the clip of the tester, keeping the wire perpendicular as in Fig. 3, at least a momentary indication of continuity should be given.

Balanced

Distribution

Boxes

by
L. Simpson

How to calculate the resistor values needed in 75Ω distribution boxes

DISTRIBUTION BOXES FOR DOMESTIC AND RETAIL SHOP TV aerial installations are easy to make up, the main components needed being a small resistor for each input or output socket. The important point to remember is that the input and output impedance at any socket on the box must always be 75Ω . Otherwise, there is likely to be trouble and possible ghosting due to incorrectly matched runs of coaxial cable. Also, a poorly matched aerial feeder can give rise to changes in TV receiver performance if it is brought close to large metal objects or other cables. Most of us have seen the instance where a very badly matched cable is so 'hot' that the picture given by the TV set it feeds changes noticeably as people approach the aerial lead.

BASIC CIRCUIT

The conventional form of distribution box has a circuit of the nature shown in Fig. 1, which illustrates a box with 4 coaxial sockets. These sockets are positioned

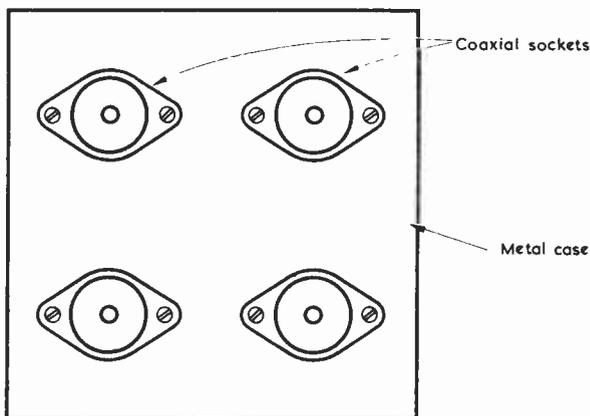
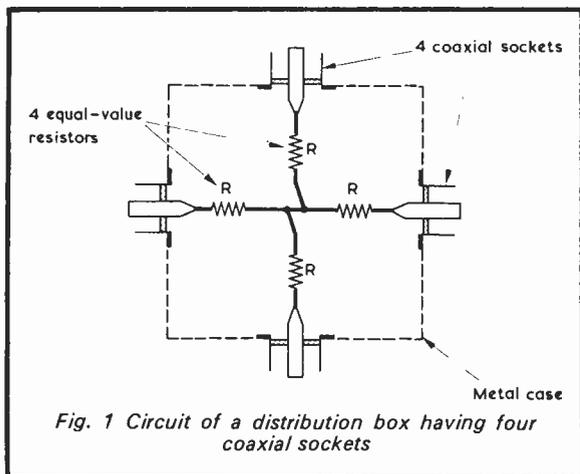


Fig. 2 In practice, the sockets of Fig. 1 are mounted on the front panel of a small metal box, the equal-value resistors being fitted inside. The wiring inside the box should be kept short

close together on the front panel of a small enclosed metal case, as in Fig. 2, their centre contacts being coupled together by equal-value resistors mounted inside the box. The outer connections of the sockets are all commoned via the metal of the box itself. In Fig. 1, an aerial may connect to any one of the sockets, whereupon three outlets are available at the other three sockets, all with impedances at 75Ω . Alternatively, two separate aerials may connect to two of the sockets, with the result that two outlets are available, these carrying the combined signals from the two aerials. Provided that all sockets are loaded by 75Ω , any socket can accept a 75Ω input or provide a 75Ω output.

If it is required to make up a box with 5 sockets, then 5 equal-value resistors are employed, one end of each resistor connecting to the centre contact of each socket.

THE RADIO CONSTRUCTOR

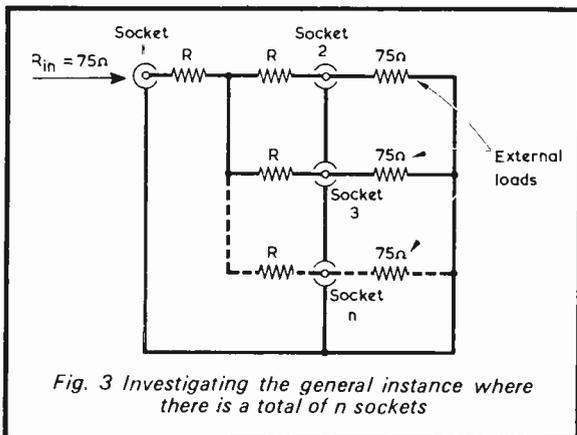


Fig. 3 Investigating the general instance where there is a total of n sockets

The other ends of all the resistors are joined together. With a box having 6 sockets, 6 equal-value resistors, similarly connected, are needed, and so on.

The value required in the equal-value resistors depends upon the number of sockets, and can be calculated by considering the instance where there are n sockets overall, as in Fig. 3. The distribution box shown here functions correctly if an external circuit 'looking into' socket No. 1 'sees' a resistance of 75Ω.

remaining socket, with the consequence that the resistance 'seen' at this socket is $37\frac{1}{2} + 37\frac{1}{2}\Omega$, or 75Ω.

Using the equation for a box with 6 sockets gives us a value, in R, of 75 multiplied by $\frac{2}{3}$, or 50Ω. Five branches, each of 50 + 75Ω, gives a total parallel resistance of $\frac{1}{5}(50 + 75)$, or 25Ω. A circuit connected to the sixth socket will then 'see' a resistance of 50 + 25Ω, which is the required 75Ω.

In practice it will be sufficient to use the 5% preferred value which is nearest to the calculated value, and the accompanying table lists values of R for distribution boxes having from 3 to 8 sockets. Where there is a choice of nearest preferred values, the resistors in the box should all be of the value chosen. Thus, in a box with 5 sockets, all the resistors may be 43Ω or 47Ω. They

TABLE

Total number of sockets	Value of R (calculated)	Nearest 5% preferred value
3	25Ω	24Ω
4	37.5Ω	36Ω or 39Ω
5	45Ω	43Ω or 47Ω
6	50Ω	51Ω
7	53.6Ω	56Ω
8	56.3Ω	56Ω

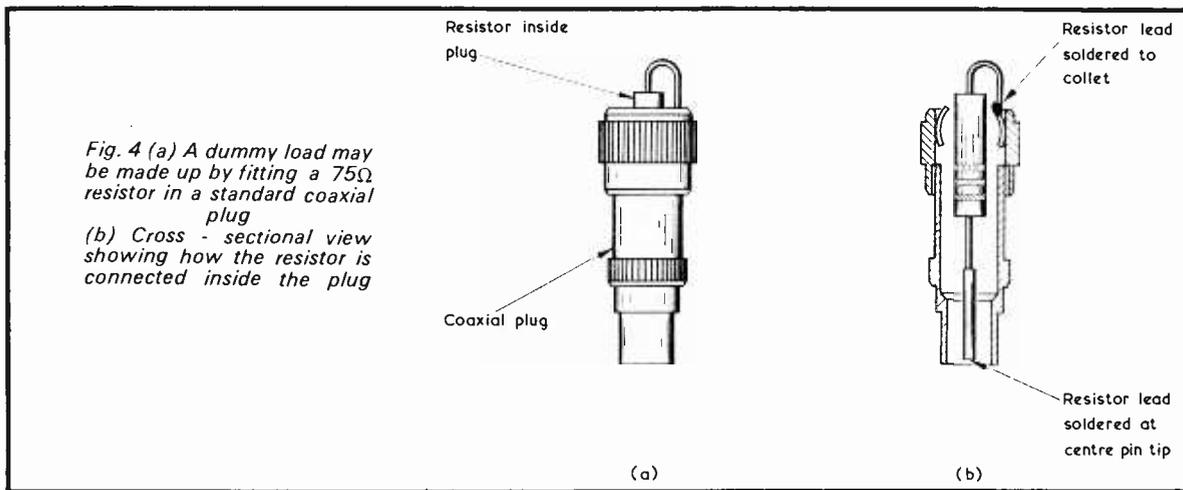


Fig. 4 (a) A dummy load may be made up by fitting a 75Ω resistor in a standard coaxial plug
(b) Cross-sectional view showing how the resistor is connected inside the plug

This resistance will be given by the resistance inserted by the resistor R connecting to the centre contact of socket No. 1 plus the parallel resistance of the (n - 1) remaining branches, each of which offers R + 75Ω.

Thus:

$$75 = R + \frac{1}{n-1} (R + 75)$$

This calculates out, for R in ohms, as


$$R = \frac{75(n-2)}{n}$$

To check the equation, let us take an example of an actual circuit, choosing as a start the 4-socket box of Fig. 1. Here, n is equal to 4, whereupon R is equal to 75 multiplied by $\frac{1}{2}$, or 37½Ω. If we consider three branches as being externally loaded by 75Ω, their resistance, in parallel, is $\frac{1}{3}$ of (75 + 37½)Ω, which works out at 37½Ω. This value will also be that of the resistor coupling to the

should not be a mixture of 43Ω and 47Ω. The resistors may be ½ watt carbon or high-stability, but *not* wire-wound.

Remember that the box introduces an inevitable loss in signal strength between any input and any output socket. With a box carrying one input and two outputs, each output receives half the input voltage. For one input and three outputs, each output receives one third of the input voltage, and so on.

Finally, any socket to which a connection is not made should still have a 75Ω load, as the distribution system will otherwise become unbalanced. If it is likely that sockets will be occasionally unloaded, an appropriate number of 75Ω dummy loads should be made up, these being fitted, when required, to unoccupied sockets. Each dummy load consists of a normal coaxial plug with a 75Ω resistor fitted internally, as shown in Figs. 4(a) and (b). A ½ watt resistor will fit comfortably inside a standard metal coaxial plug such as the Belling-Lee type L.734/P.

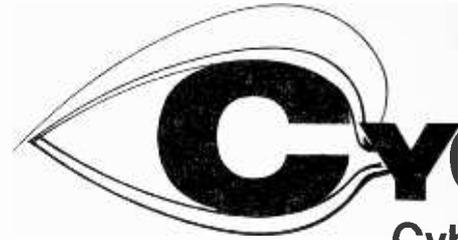

**Cybernetic
Light
Pov**

EXAMPLES OF THE USE OF CYBERNETICS WHICH IS the science of feedback control, have become prolific in recent years. In general, the wide field of Cybernetics may be divided into two main regions. The first is where a device is built to perform a number of specific pre-determined tasks, and devices of this nature are known as servo-robots. The other region encompasses devices which are built with a much more diversified approach, and have no specific purpose but to exist. They are usually much less specialised, and are known as auto-robots.

Examples of the former device are to be found everywhere. Computers, industrial control systems, traffic light systems and even common devices such as the motor car, the refrigerator and the washing machine are all servo-robots relying on feedback control.

The most common form of auto-robot is Homo Sapiens, a very generalised machine apparently having no specific purpose but to exist and better his environment. As mentioned in the author's earlier articles concerning 'Cynthia'¹, Man has had for a long time a compulsion to build something emulating himself. At present, his attempts in building various types of auto-robots have been fairly successful, the ultimate development to date having taken place in America with the programme at The Stanford Research Institute for developing a mobile automaton. Details of this device will be appearing in a later article. However, there is at present one limitation to the complexity of the systems that can be built, and that limitation is the finite speed of light.


The reason for this situation is as follows. When one compares the human brain to a computer, the latter, in certain aspects, is far superior. For instance, the rate of transfer of information, storage rate, and reset time of individual elements in a computer are all very much faster than the corresponding rates in the human brain. On the other hand, the human brain excels in storage capacity, and also in the fact that each element in the brain is connected to many more other elements than occurs in a computer. This rich interconnection in the human brain means that it can process information parallel with other information, as opposed to serially. The brain also has a very good filtering capability and, unlike the computer, can receive general information as opposed to pre-digested information. In the event of a component breakdown the brain appears to be 'holographic' in nature, in that it still gives the correct answer to a problem although sometimes to a lesser accuracy. In the event of a computer breakdown, a 'nonsense' answer usually results. Also, the brain can deal with general problems, whilst the computer is rather more limited.

The reason why the computer cannot at present have richer interconnection between elements is that, at the speeds computers operate, light (and therefore electricity) travels but a few feet per computer operation.

¹L. C. Galitz, 'Cybernetic Cynthia', *The Radio Constructor*, June, July, 1970.

This article is the first of a short series on cybernetic devices. One cybernetic device is described in detail. The present article deals with the differences between various types of robots.

P
A
R
T
O
N
E

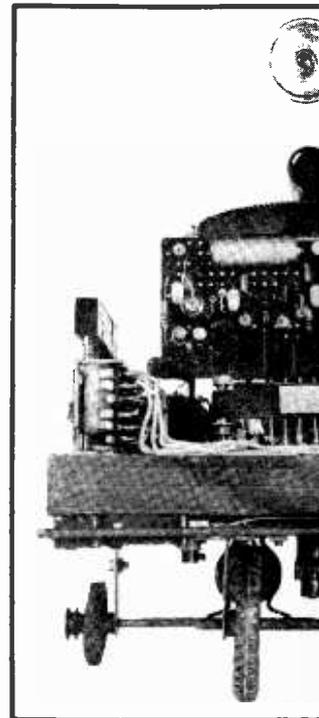


A general view of Cyclops from a front angle directly in front. The globe and the cylinder are at the top. The cylinder is the eye.

CYCLOPS

Magnetically Controlled
Orientated and
Controlled System.

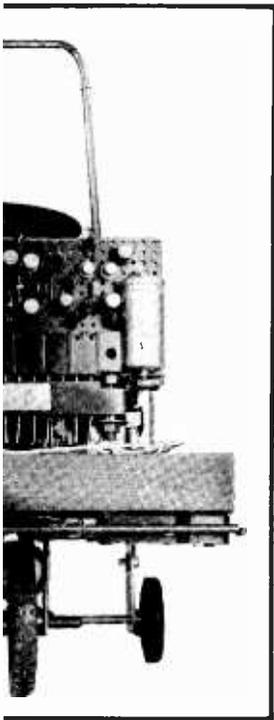This series devoted to robots and
the device, called Cyclops, will be
this article explains the differences
between a robot, and introduces Cyclops



Photograph taken from a low angle showing the light bulb and reflector immediately below the robot.

by
L. C. GALITZ



Therefore, in order that computer processing should operate in step, no two units in the central processing unit may be connected by a wire of more than two feet or so, otherwise pulses will arrive too late for any particular operation. At present, it is impossible for a machine to be built with all the relevant electronics in a sphere of radius less than about a foot, and with sufficient complexity to even approach that of the human brain. Nevertheless, we have still come a long way since Babbage's Analytical Engine.

CYCLOPS

One very useful way of finding out about something unknown is to build a model of it, and see how closely it imitates the real thing. In many cases this is the only way, and in some cases, such as solving the mystery of the human brain, it is the most practical way. Many auto-robots nowadays are mechanical equivalents of real animals, and such is the case with Cyclops, which is an approximate electro-mechanical equivalent of an animal in the amoeba family. Although most of Cyclops's behaviour is predetermined in the circuitry, one of the earlier prototypes surprised the author in imitating something which, although beneficial to both animal and machine, had not been intentionally put in!

Cyclops was designed with several criteria in mind. One of the most important of these was that he should explore his environment looking for things to happen, rather than passively wait for them to occur. Cyclops was to be positively tropic² towards light, and negatively tropic towards touch and bright lights. In other words, Cyclops is attracted by lights of a moderate intensity, and repelled by lights of dazzling intensity and also by obstacles into which it bumps. An advantage of using light as the sole attractive stimulus is that light, by way of solar cells, can mean food, i.e. electricity. In a perfect machine, the robot would be equipped with a bank of solar cells and, on finding a light, would pause to recharge its batteries. After its 'meal' it would then move off to explore further its environment. Thus, the perfect machine would show internal stability, and by reason of its positive tropism be self-perpetuating. Unfortunately, due to the prohibitive cost of a bank of solar cells providing sufficient power to recharge the machine's batteries within a reasonable length of time, another approach is needed for a practical device. A cheaper alternative would be for every light source to be equipped with a low tension supply, so that the machine would be capable of locating the light, homing into it, and plugging itself into the power source in order to recharge its batteries. Once these were recharged, the machine could move off again.

Returning to Cyclops in particular, other design requirements were that he should be able to recognise his reflection in a mirror, and that he should be able to recognise other members of his species.

² Derived from 'tropism', the response of protoplasm to stimulus.—Editor.

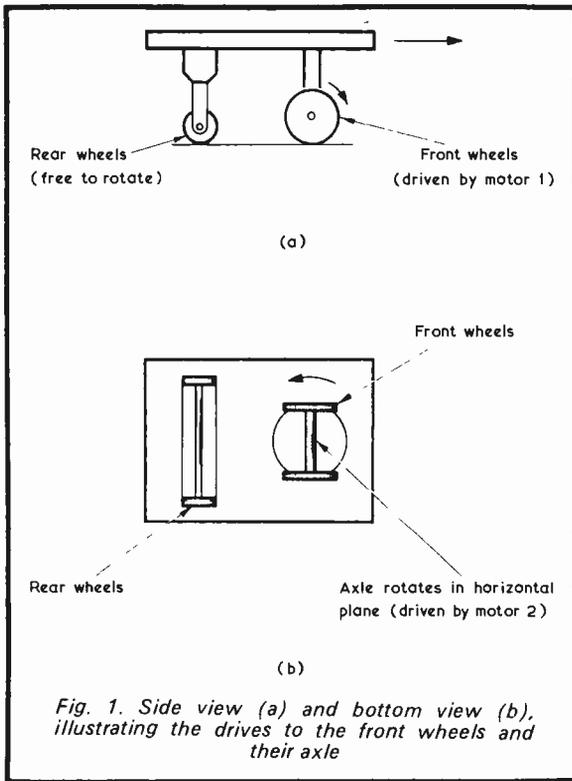


Fig. 1. Side view (a) and bottom view (b), illustrating the drives to the front wheels and their axle

To sum up, Cyclops will explore his terrain looking for light and, upon finding some will approach it and when sufficiently close, stop as if to recharge his batteries. Should he be dazzled, he will move off, and he will also avoid obstacles. This is sufficient to make him self-perpetuating. In order to be more realistic, a learning circuit was introduced, which enables Cyclops to make decisions concerning himself and his actions in relation to his environment.

BASIC DETAILS

The basis by which Cyclops works is by having the electronics control two motors. One motor drives the front wheels round to make Cyclops move. The other motor rotates the front wheels' axis through 360° and so changes the direction in which Cyclops moves. The drive from this second motor is in one direction only and cannot be reversed. The arrangement is shown in the side view of Fig. 1 (a) and the bottom view of Fig. 1 (b). The front wheels are caused to rotate by Motor 1, and their axis is rotated by Motor 2. The rear wheels are free to rotate and are not driven. Figs. 2 (a) to (d) illustrate how the rotating front axle changes the direction in which Cyclops moves.

With both motors running, Cyclops follows the path shown in Fig. 3. With the gear ratios incorporated the diameter of this pattern is approximately 6ft. Thus, quite a large area is traced out. The area would be larger if Motor 2 ran more slowly, but if this motor is geared down too much the robot will not home into light sources effectively. Hence, a compromise has to be reached.

Motor 2 not only rotates the front wheel unit but also a unit upon which the 'eye', which senses the presence of light, is mounted. The eye rotates at the same speed and in the same direction as the front wheel and thus always 'looks' in the direction in which Cyclops is moving. This rotation of the eye is referred to as 'scanning'.

When Cyclops sees a faint light, the electronics operate a relay which cuts the power to the scanning motor (i.e. Motor 2), causing Cyclops to move in the direction of the light. It will be appreciated that, unless the eye happens to be pointing straight ahead at the time Cyclops will tend to veer away from the light source, and the scanning motor will cut on. If the scanning stopped at an eye position such that, when the scan restarts, the eye turns in the direction which will bring it to the straight ahead direction sooner, the eye will be brought in line with the light source almost immediately after scanning starts again. Thus Cyclops will once more start heading for the light. He will then veer again for a shorter distance, after which the


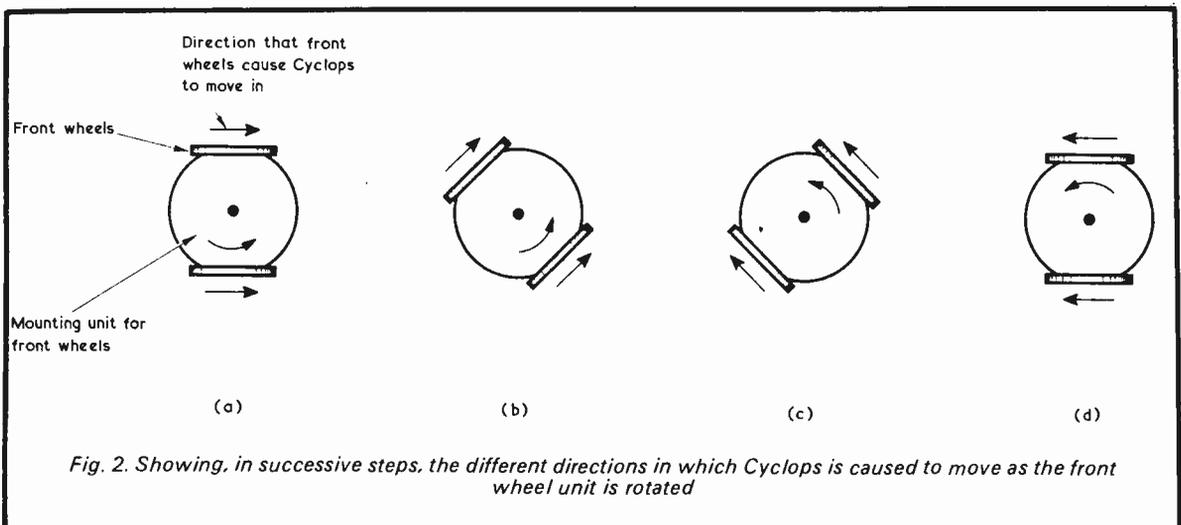


Fig. 2. Showing, in successive steps, the different directions in which Cyclops is caused to move as the front wheel unit is rotated

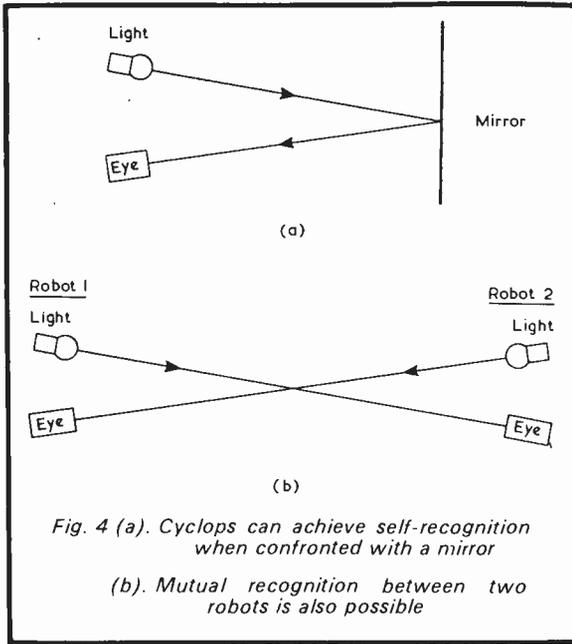

It is wired across the main drive motor with the result that, when the machine moves the lamp is illuminated, and when the machine stops the lamp extinguishes. If now a mirror is held up to Cyclops' eye such that he sees the lamp's image through the mirror, he will stop, the light being of sufficient brilliance to activate his 'stop to feed' circuitry. However, the action of this circuit is to cut the power to the motors, and this will extinguish the lamp. As Cyclops can now no longer see the lamp, his 'stop to feed' circuitry will revert to its normal state, and the power to his motors will be restored, and hence the lamp will light up again. This cycle of events will continue for as long as the mirror is held in front of Cyclops' eye, and he will linger in front of the mirror flickering, twittering, and jiggling like a clumsy Narcissus. This highly specific

behaviour towards his own reflection may be accepted as evidence that Cyclops has some degree of self-awareness. See Fig. 4 (a).

If we consider the result when two 'animals' of the same species as Cyclops encounter one another, we find that they home into one another owing to the attraction of the light. However, as this happens, the lamp and therefore the stimulus is cut off, but the removal of the stimulus restores the light which then becomes a stimulus again. Thus, the two animals dance about one another. See Fig. 4 (b).

With a colony of such creatures, the very fact that each animal extinguishes its own source of attraction in the act of seeking it in others means that the colony, when no other attraction is presented, must stick together. Such a colony will also attract other creatures of the same species due to the fact that the colony is giving off light. Unfortunately, the very gregariousness of creatures of the species of Cyclops is that species' downfall, because even though an external light source will attract several members of the colony, a good many will remain behind. It is not difficult to realise that the light source of the colony (the animals themselves) can never be sufficient to recharge the batteries of the animals therein, and eventually all the animals forming the colony must eventually die unless an external light source is available. An interesting point which arises here is that when an animal is reaching the end of its life its batteries will be low, and therefore the light it

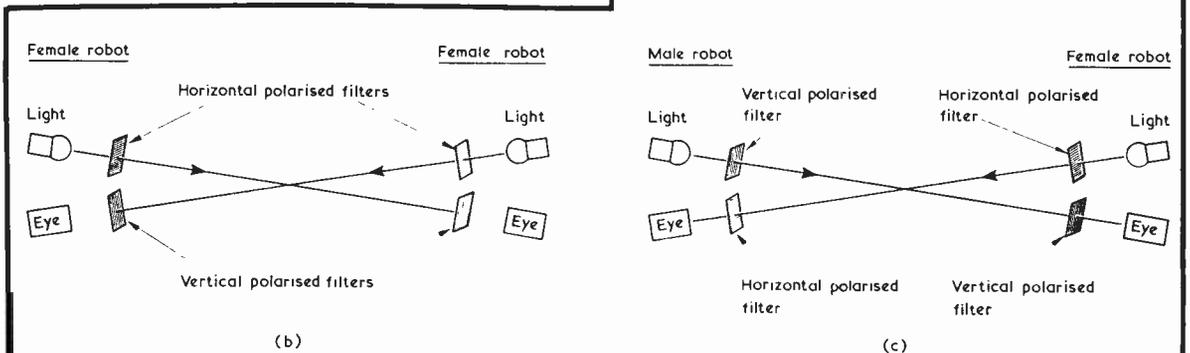
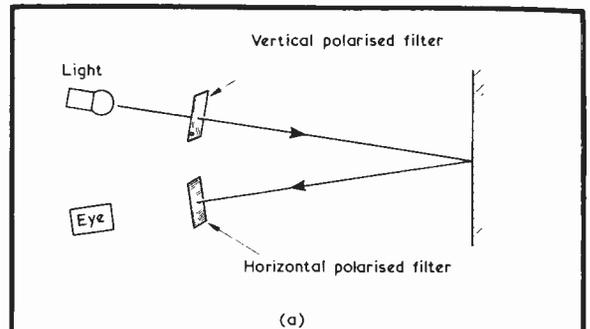


Fig. 5 (a). Although not incorporated in the present model, polaroid filters may be added to modify robot reactions. Here, a male robot is confronted by a mirror but the vertically polarised light cannot pass through the horizontally polarised filter and there is no reaction

(b). The filters ensure that one female robot is not recognised by another female robot

(c). Recognition is only achieved between a male and a female robot

emits will be dim. Therefore, there will be less likelihood of the animal going through the self-recognition response, and also the mutual recognition response, which would certainly be its downfall. The animal would rather look for light to replenish its waning power source than to participate in games with itself or with other animals of its own species.

One can be pedantic about this feature of mutual recognition and, at the expense of the self-recognition feature (which may be regarded as undesirable anyway) one could incorporate polaroid filters in front of the light source on each animal, and in front of the eye. These filters could create arbitrary males and females of the species. With this arrangement, a male will not react to itself or to another male; similarly, a female will not react to her reflection or to another female. However, males and females will react with the mutual recognition response upon encountering one another.

This feature can be accomplished by having a hori-

zontally polarised filter in front of the light of a female and the eye of a male robot; and a vertically polarised filter in front of the eye of a female robot and in front of the light of a male robot. Thus, when encountering a mirror, neither variety of animal is able to see its own light due to the fact that there are opposing filters on the light and eye. The same thing occurs when a male robot meets another male robot, or when a female robot meets another female robot. It is only when a female and a male robot meet that the filters are of the correct orientation for the female eye to see the light from the male's light, and for the male eye to see the light from the female's light. Naturally, the filter does not interfere with the light from unpolarised light sources, to which the animals are normally sensitive. Figs. 5 (a), (b) and (c) show the various situations.

Details of the construction of the mechanics of Cyclops will be given in the next article, which will appear in next month's issue.

(To be continued)

FEATURED NEXT MONTH



THE 'JUBILEE' 8 WATT AMPLIFIER

Part 1

By J. R. Davies

also

ZENER DIODE BUZZER

By R. J. Caborn


DIRECT READING CAPACITANCE METER

By F. Griffiths

etc. etc.

ORDER YOUR COPY NOW

RADIO CONSTRUCTOR

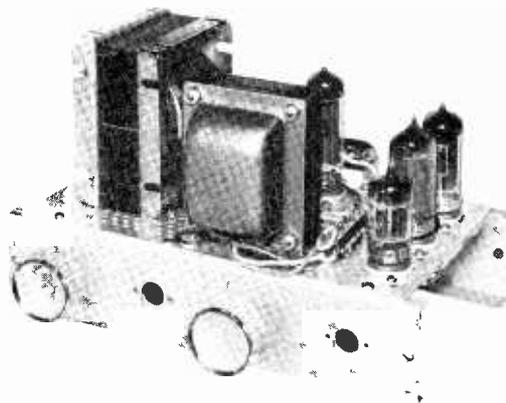

ON SALE AUGUST 1st
PRICE 20p

Copies may also be obtained direct from the Publishers, 26p. including postage. Published by Data Publications Ltd. 57 Maida Vale, London W.9

DIGITAL FREQUENCY MONITOR

PART 2

by

S. A. Money, M.B.C.S., G3FZX

This concluding article in our 2-part series completes the description of circuit operation and describes the process of setting up and final use.

THE CONTROL LOGIC

THE FUNCTION OF THE CONTROL LOGIC IS TO GOVERN the sequence of events required to carry out a single cycle of frequency measurement. Fig. 6 shows the circuit of this part of the system.

A four stage shift register circuit using two 7474 modules controls the timing sequence. This shift register is driven by the 250 Hz clock produced by the crystal controlled reference generator. At the start of the cycle the shift register is in a dormant state with the first three stages set at 'zero' and the fourth at 'one'. The clock is fed in via gates G1 and G2 which are controlled by the inverted output NQ of the fourth stage of the register. At the start of the cycle the clock gate is held closed because the fourth stage is at the 'one' level and hence its NQ output is at 'zero'.

To start a new cycle of operations a trigger pulse is applied to the preset and clear inputs of the four flip-flops so that the first stage is set at 'one' and the other stages are all set at 'zero'. Gate G1 will now open and allow clock pulses to be applied to the shift register.


At the first clock pulse after the gate has been opened the 'one' state will move along the register from stage 1 to stage 2. Stage 1 will reset to 'zero' again because its D input is permanently held at the 'zero' level. The output from stage 2 of the shift register is gated with the clock pulse in gate G3 to produce the presetting pulse for the main decade counter chain. Transistor TR2 inverts this pulse and also provides sufficient current drive to operate all of the decade stage reset lines in parallel.

When the next clock pulse occurs the 'one' state moves along to stage 3 of the register and stage 2 returns to 'zero'. The Q output of stage 3 is used to open the input gate circuit for exactly one period of the 250 Hz reference clock. The fourth clock pulse returns the shift register to its starting condition at which point gate G1 closes and cuts off the clock pulses. The control logic will now remain in this state until a new trigger pulse is applied to start another cycle.

In order to produce a continuously updated output display the trigger pulses which start the sequence need to be applied regularly. A convenient source of pulses is the 50 Hz power supply frequency. A half-wave rectified signal is applied via a resistor to the base of transistor TR3 which acts as a limiter and pulse shaper. The collector output drives the divide-by-five section of a 7490 and this in turn drives a short pulse monostable circuit made up from a 7400. The output from this stage is used to provide the trigger pulse which starts a new sequence in the control logic.

DISPLAY TUBE BLANKING

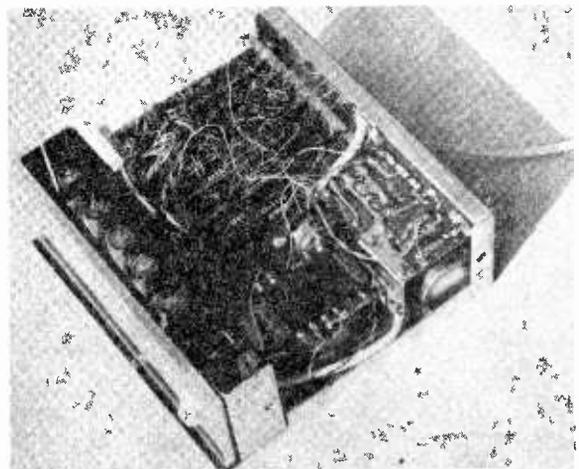During the period where the input frequency is being counted the display will change in sympathy with the count total since the indicators are connected to the counter output. This causes an objectionable flicker effect unless some form of blanking is applied to the indicator tubes.



Side view of the prototype

THE RADIO CONSTRUCTOR


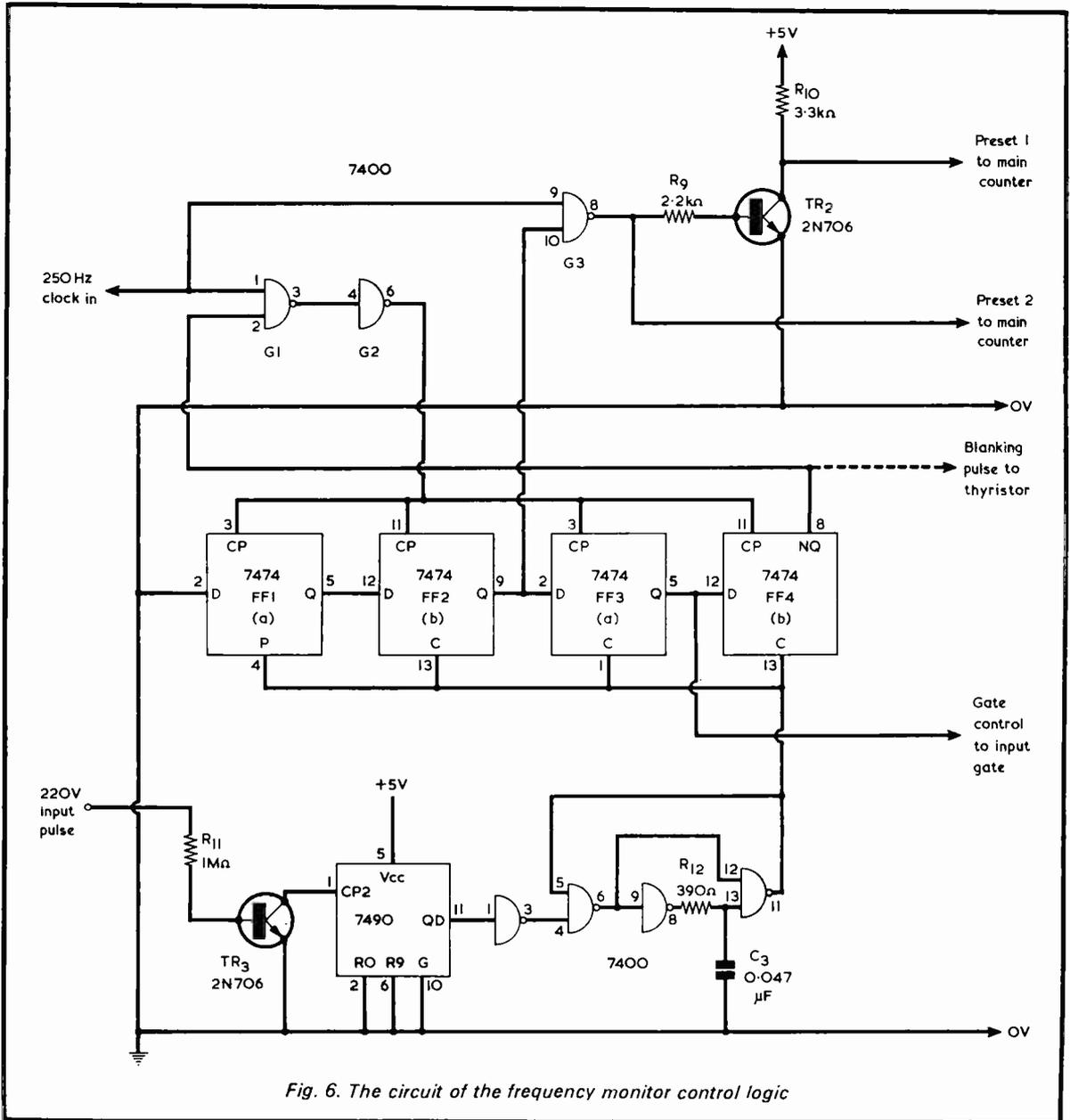


Fig. 6. The circuit of the frequency monitor control logic

The simplest method of achieving this is to feed the anodes of the indicators from a half-wave rectified supply and then to synchronise the control sequence to this same supply. If the control sequence is started as the anode voltage falls to zero the indicator tubes will be effectively switched off during the preset and count periods of the control sequence. During the half-cycle when the anode voltage is positive the counter output will be static and the indicators will display the current value of the frequency being measured. In fact the anode supply of the indicators may be used to drive transistor TR3 in the control logic.

Although this simple method of blanking works when the frequency is measured in units of 1 kHz it will be

necessary to use a more complex arrangement if hundreds of Hz are to be displayed. In this case the period for which the tubes must be blanked out is more than one half-cycle of the supply mains. A suitable circuit for this purpose is shown in Fig 10. In this arrangement a thyristor is used to provide the control of the anode voltage of the indicators. This thyristor is driven by the signal from the NQ output of the fourth stage of the shift register in the control logic. The thyristor will be turned on during the whole of the measurement sequence and effectively holds the anode voltage of the indicators below the striking level, thus blanking the display. To prevent excessive loading of the flip-flop stage a transistor emitter follower is included

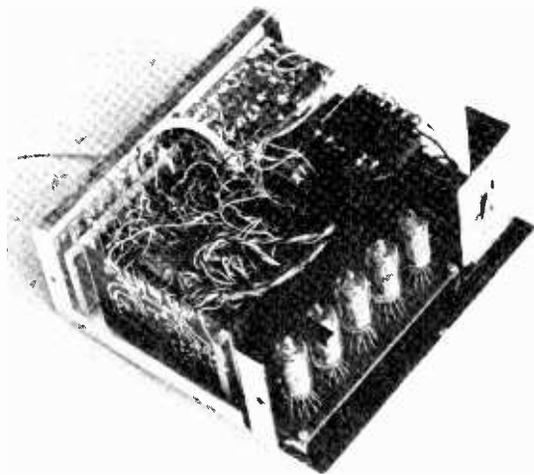

Another side view, illustrating the manner in which printed circuit boards were employed in the author's unit

to drive the gate of the thyristor. A resistor in the anode circuit of the thyristor limits the current when the thyristor is turned on.

THE POWER SUPPLY

A power supply is required to provide a d.c. supply stabilised at 5 volts for the logic circuits and a half wave rectified 220 volt supply for the indicator tubes.

A small transformer was used which had 220 volt 50mA, and 6.3 volt 1 amp secondaries, and a 240 volt primary. A 1N4005 rectifier supplies the 220 volt line for the indicator anodes and a bridge using four 1N4001 diodes is employed to provide the low voltage supply at about 750 mA. Using a 16,000 μ F reservoir capacitor, this circuit gives about 7 volts output at full load. A simple series stabiliser circuit is used to derive the 5 volt supply for the logic.


An OC28 germanium transistor was used as the series regulator because the voltage drop in silicon types did not permit the required 5 volts output to be maintained at full load current. Using an OC28 the output was stable up to 800mA load current. A 2 in. square heat sink of 16 s.w.g. aluminium will be required for this transistor.

Fig. 7 shows the circuit diagram of the power supply unit for the monitor unit.

DISPLAY INDICATOR TUBES

In the original unit Hivac type XN13 indicator tubes were used since these are readily available to the amateur constructor. The base connection arrangement is shown in Fig. 8. It should be noted that this type of tube has wire terminations instead of pins and the tube itself is about the size of an average B9A valve.

Each indicator tube has an 82k Ω anode resistor to limit the anode current to the recommended value. If other types of tube are used their data sheets should be consulted since they may require a different value limiting resistor. When thyristor blanking is used the value of the anode resistors may be reduced to 68k Ω to allow for the effect of the common series resistor in

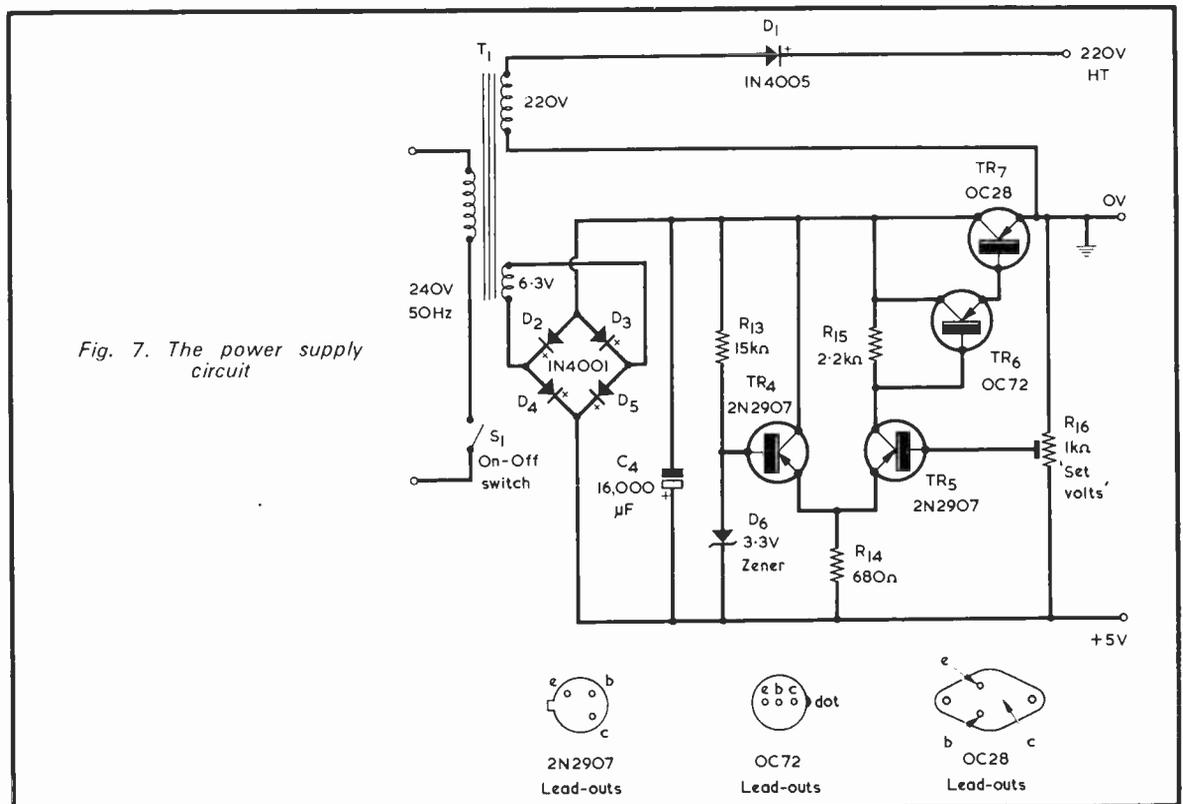

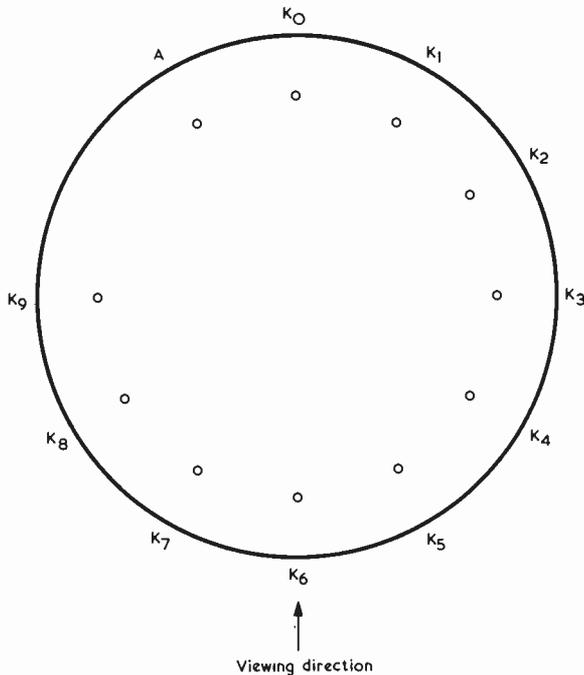


Fig. 8. Connections to the XN13 indicator tube

the anode circuit of the thyristor. The ten cathodes of the tube are connected directly to the ten outputs of the 7441 decoder module used to drive it.

RECEIVER MODIFICATIONS

A signal must be extracted from the receiver local oscillator in order to provide the input signal for the frequency monitor unit. A buffer amplifier and pulse shaper will be needed to provide the correct signal level. Since the frequencies involved are relatively high this circuit is best mounted in the receiver near the oscillator and must be capable of driving a short

length of coaxial cable.

The author's receiver is a Lafayette HE30 which uses a Hartley type oscillator. The most convenient pick-off point for this circuit was found to be at the cathode of the oscillator valve. For other receivers it will be necessary to find a pick-off point which causes least disturbance to the oscillator operation.

A buffer amplifier and limiter circuit as shown in Fig. 9 is used and should be mounted as close as is practicable to the oscillator circuit of the receiver. The transistor provides a buffering action and the two 7400 gates act as a limiter and cable driver. It should be possible to drive a coaxial cable of up to 3 ft. in length with this circuit.

The circuit requires a 5 volt supply which can be derived from the receiver heater supply in a valve type receiver by using a rectifier and zener stabilizer as shown in Fig. 9. If there is no convenient source of low voltage available in the receiver it will become necessary to feed 5 volts to the buffer unit from the frequency monitor itself.

CONSTRUCTION NOTES

It is not proposed to give detailed instructions on how the unit should be built since the majority of readers attempting this project will already be quite experienced in construction and will no doubt have their own ideas on the method of construction they intend to use. Some notes on the techniques used in building the prototype unit may however be of interest.

Home-made printed circuit cards were used with a separate card for each decade module and two further cards for the reference and control circuits. In making these cards the tracks were marked out on clean copper clad board using a cellulose enamel paint. For the etch a 50% solution of ferric chloride was used. After the etching stage the paint mask was removed with paint stripper such as Polystrippa. An alternative method of card construction would be to use 0.1 in. grid Vero-board.

The XN13 tubes are mounted on a single card and spaced at 1 in. intervals with the connection leads soldered directly to the card. The anode resistors may be mounted directly under the tubes they feed. A mask

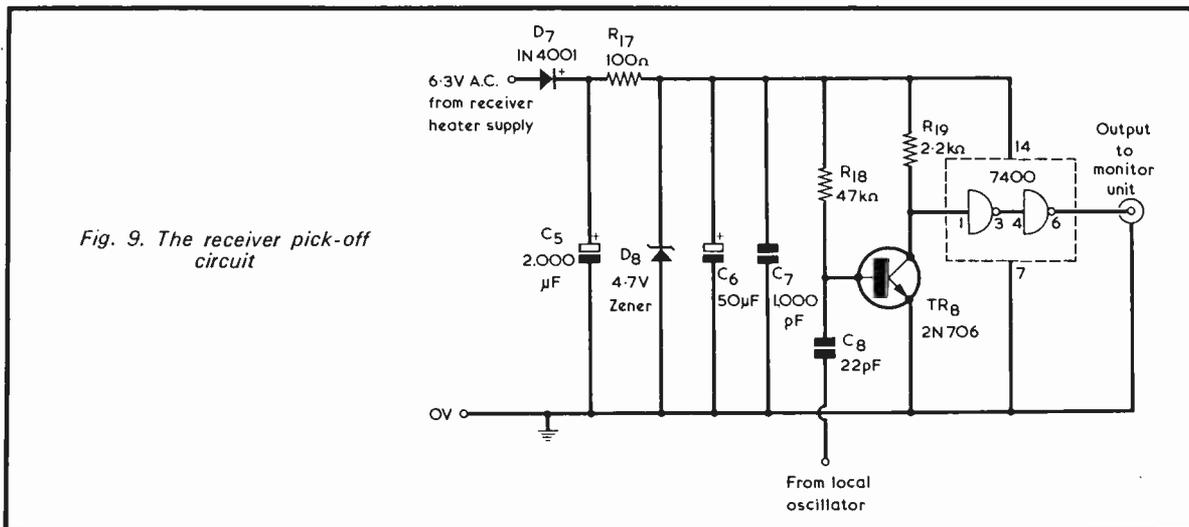


Fig. 9. The receiver pick-off circuit

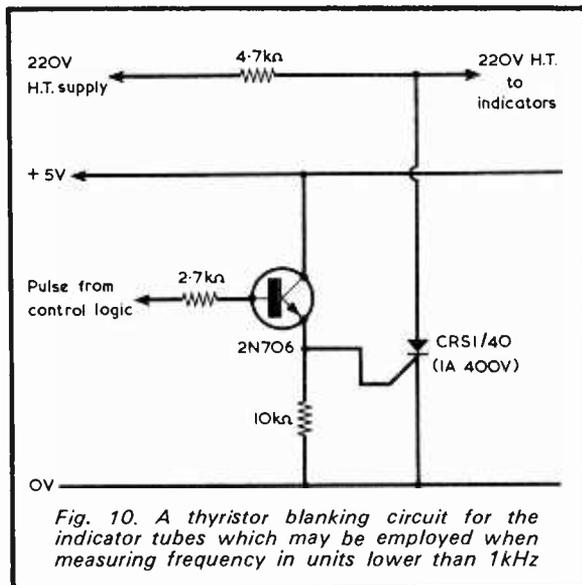


Fig. 10. A thyristor blanking circuit for the indicator tubes which may be employed when measuring frequency in units lower than 1kHz

plate of 22 s.w.g. aluminium with a suitable viewing aperture is mounted in front of the indicators and to give a reasonable finish to the unit a ¼ in. thick clear Perspex front panel is mounted in front of the masking plate. It is a good idea to mount the indicator tubes in a screened compartment as they tend to produce a certain amount of radio frequency interference. The surface behind the tubes and the front mask plate should be painted matt black to reduce reflections.

The whole unit should be mounted in a metal case which provides reasonably good r.f. screening. For the original unit a case of size 8 in. by 8 in. by 5 in. high was used. Since power dissipation is small no arrangements for ventilation are likely to be required.

The writer did not find it necessary in his unit (and in a subsequent monitor built up to the same circuit) to use bypass capacitors on the supply lines. It may, however, be worth-while to include a 0.1µF ceramic capacitor across the 5 volt lines, preferably on the card carrying the input divider stages, and also on the reference generator.

TESTING AND ADJUSTMENT

Although not essential, an oscilloscope will be very helpful in finding faults in the operation of the logic system. For most purposes, however, the only test instrument needed will be a multimeter.

For a start the power supply should be checked by itself using a 7Ω 2 watt resistor as a dummy load in place of the logic. Adjust the preset voltage control potentiometer to give an output of 5 volts. Check that when the dummy load resistor is removed the output stays at 5 volts. The logic circuits may next be connected and any final adjustment to the output voltage made. The indicators should now be illuminated and will probably be showing some random number at this stage.

With the power supply operating it is now possible to check the operation of the crystal oscillator and the reference divider chain. At this stage the series capacitor (Cs) in the crystal oscillator circuit should be 0.1µF and there should be no shunt capacitor (Cp).

With the case removed from the unit it should be possible to pick up the harmonics of the crystal oscillator on a receiver. The operation of the reference divider can readily be checked using an oscilloscope. If there is no oscilloscope available the output can be fed to a pair of high impedance headphones or an audio amplifier and loudspeaker. The 250 Hz tone is very nearly at Middle C in the musical scale and the earlier stages of the divider will give higher notes when they are operating correctly.

At this point the frequency of the crystal oscillator must be set up accurately. Tune in a standard or other known frequency station such as MSF on 2,500 or 5,000 kHz. The station chosen must have a frequency which is an exact harmonic of the crystal frequency. Adjust the receiver b.f.o. to zero-beat with the station. Switch on the monitor unit and check whether the harmonic of the crystal oscillator is also at zero beat with the b.f.o. If the resultant beat note is lower than about 50 Hz then no adjustment is needed.

In most cases it will be found that the beat note will be fairly high and it will be necessary to tune the crystal oscillator circuit to the precise frequency of 500kHz. Retune the receiver to bring the crystal harmonic to zero beat with the b.f.o. and note whether it was necessary to move higher or lower in frequency to achieve this. If the receiver had to be tuned higher then it will be necessary to add a small capacitor (Cp) across the crystal. This will need to be a few pF in value and should be increased until the crystal signal is as near as possible to zero beat with the signal from the standard frequency station. If the receiver has to be tuned lower in frequency the value of the series capacitor (Cs) will need to be reduced until the same result is achieved. The value of Cs may have to be reduced to the order of only a few picofarads. In both cases a variable trimmer capacitor may be helpful in setting the frequency accurately.

Once the crystal frequency has been adjusted to its correct value the presetting links in the decade counter may be set up to give the offset correction. Subtract the receiver i.f. frequency from 40 MHz to get the value to which the counter must be preset at the start of each measurement cycle. In the case of an i.f. of 465 kHz the counter must be preset to 39535.

The four links in each decade are set to Preset or Clear as shown in the Table in order to set the decade

TABLE

Link connections for presetting decade counters. (P=Preset, C=Clear).

Required State	Link Connections			
	S1	S2	S3	S4
0	C	C	C	C
1	P	C	C	C
2	C	P	C	C
3	P	P	C	C
4	C	C	P	C
5	P	C	P	C
6	C	P	P	C
7	P	P	P	C
8	C	C	C	P
9	P	C	C	P

to its required starting point. When all decades have been set up the readout should read 39535 for a 465 kHz i.f.

At this point the crystal oscillator signal may be fed in as a test input and the frequency readout should be 00035 for a 500kHz crystal and a 465 kHz i.f. offset. If this test works the receiver may be connected and a known frequency station on say the medium wave band tuned in. Check the frequency readout against the known frequency of the station. It may be necessary to do some experimenting with the pick-off circuit from the local oscillator in order to ensure that the monitor

unit gets a clean signal and operates properly on all bands. Due to the added stray capacitance of the buffer amplifier it may be necessary to slightly realign the oscillator circuits in the receiver. It may also be necessary to adjust the offset of the kHz decade if the receiver i.f. is not aligned exactly to the stated frequency.

Once the unit has been set up and is operating correctly it will be found that logging station frequencies and setting the receiver to given frequencies in the bands will be very easy, and the receiver main tuning dial may then be ignored. ■

BOOK REVIEWS



RADIO AND LINE TRANSMISSION, Vol. 2, Second Edition. By G. L. Danielson, M.Sc.Tech., B.Sc., C.Eng., M.I.E.E. and R. S. Walker, C.Eng., M.I.E.R.E.
301 pages, 5½ x 8½ in. Published by Iliffe Books. Price £1.60.

The first edition of this book appeared in 1963 and was intended to cover the syllabus of the City and Guilds of London Technician's Certificate examination in 'Radio and Line Transmission B'. This new edition is published with the same intention, and takes up changes in the syllabus which have occurred over the intervening period. Additions include details of transistor h-parameters, v.h.f. propagation and rectangular pulse waveforms. Also, the sections dealing with electronic voltmeters have been up-dated, a section dealing with Q-meters added and further material on transistor circuits incorporated. Finally, all units have been amended to S.I. and any traces of non-metric units removed.

The book commences with the subject of propagation, then carries on to lines and cables, communication channels, aerials, components, and logarithmic scales and units. Further sections deal with noise in communication systems, a.f. amplification, tuned circuits, r.f. amplification, oscillators, modulation and detection, and superhet reception. The final section discusses r.f. measurements, and there is an extensive index. Each of the sections ends with a number of test questions, many of which are taken from earlier City and Guilds examinations.

The book deals effectively with its subject-matter and offers a very useful text-book for the students for whom it has been primarily written. There are a large number of diagrams and the approach is at all times clear and concise.

INTRODUCTION TO VIDEO RECORDING. By W. Oliver, G3XT.
109 pages, 5½ x 8½ in. Published by W. Foulsham & Co. Ltd. Price £1.50.

This interesting book, on a subject which has not, perhaps, had as much information published about it as is due, is written for the layman and not for the technical expert. It introduces the reader to the various modes of video recording at present in use, dealing with these at elementary level so far as technicalities are concerned, but at the same time giving full details of operation and use, as offered by the commercial systems currently available. The manufacturers whose products are referred to include Ampex, E.M.I., Sony, Decca, Philips, EVR Rank-Bush-Murphy, National, R.C.A. and Akai. Also given is a list of agencies in the U.K. which handle video recording equipment, closed-circuit TV and allied apparatus.

After a preliminary outline the book compares sound and video recording, then carries on to video cameras, the choice of systems, video tape recorders, the EVR system, video disc systems, the laser and hologram in video recording, and video tape. Further chapters discuss closed-circuit TV systems, portable video recording systems, recording and playback transducers, applications and the cost of equipment. A final chapter deals with supplies and suppliers.

The book is well illustrated with photographs and will be of value to any reader contemplating the purchase of video recording equipment either for his own use or for commercial, entertainment or educational purposes.



SHORT WAVE NEWS

FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

The newly formed nation of Bangladesh (formerly East Pakistan) has a transmitter at the capital Dacca and has been operating a service in English from 1230 to 1300 daily on **11620** (25.82 metres) and **17925** (16.73m) although readers should be warned that the frequencies quoted are nominal – Bangladesh engineers are not noted for accuracy where frequencies are concerned. A transmission from Dacca recently logged by the writer was on a measured frequency of **17930**, the listed **11620** channel was, for some unknown reason, silent.

Another broadcast in English in the General Overseas Service of Radio Bangladesh is from 1715 to 1800 on **11650** (25.75m) according to recent station announcements heard here.

The most recent schedule of Radio Bangladesh is as follows – 0230 to 0300 in-English on **9690** (30.96m) and on **15520** (19.33m); from 1000 to 1030 on **11620** and **17925**; from 1230 to 1300 in English as listed above; from 1320 to 1350 in Nepalese on **7260** (41.32m) and on **9690**; from 1430 to 1530 in Bengali on **9680** (30.99m); from 1600 to 1630 in Hindi on **9680** and **11650** and in English from 1715 as listed above, according to the BBC Monitoring Service (BBCMS).

The programme from Radio Bangladesh usually consists of station identification and news about Bangladesh at 1230, press comments and native musical interludes, ending at 1300 with “Jai Bangla”.

● AFGHANISTAN

The evening broadcast to Europe in English from Radio Aghanistan, Kabul, is now from 1800 to 1830 on **11785** (25.46m) and on **15265** (19.66m).

● IRAN

Recently reported in these columns as operating on **9020**, Radio Iran, Teheran, has been recently logged here on a measured **9004** (33.31m) although for some weeks past (at the time of writing) the frequency has varied between the limits stated here. Radio Iran can also be heard on the ‘out-of-band’ channel of **12185** (24.62m), but listen on the **15084** (19.89m) channel for the taping of Iranian music.

● KUWAIT

The English Service of Radio Kuwait is radiated from 1830 until 2100 on **11845** (25.33m) replacing the **11925** outlet. (BBCMS).

● TUNISIA

The National Programme of the Tunsian Radio is now heard on **15216** (19.71m) from 0458 until 2330, replacing **9595**, according to BBCMS.

● ISRAEL

Kol Yisrael may now be heard in English from 2035

to 2115 on **6170** (48.62m), **9009** (33.30m) and on **9625** (31.17m) beamed to both Europe and Africa.

● SOUTH AFRICA

The English programme from RSA Johannesburg can now be heard from 1900 until 1950 on **15155** (19.80m) and on **21480** (13.97m). This programme is directed to the UK and is only part of the service in English.

● PAKISTAN

The English Service from Radio Pakistan, directed to the UK, may now be heard from 2000 to 2130 on **11672** (25.70m), **11860** (25.30m) and on **15520** (19.33m).

CURRENT SCHEDULES

● SRI LANKA

The Asian Indian Service from Radio Sri Lanka is currently from 0030 to 0430 on **6075** (49.38m), **9720** (30.86m) and **15120** (19.84m), also from 1230 to 1730 on **7190** (41.72m) and **9720**. The All Asia Hindi Service is heard from 0030 to 0430 on **7180** (41.78m) and on **11800** (25.42m); from 0630 to 0830 on **6075** and from 1330 to 1730 on **11800**. The All Asia Tamil Service also uses the two latter channels from 1030 to 1330. The latter Service is directed to South East Asia from 1030 to 1130 on **11740** (25.55m), **15120** and on **17830** (16.83m). Sri Lanka, formerly Ceylon.

● CANADA

The European Service in English is currently radiated as follows – from 1217 to 1313 on **11850** (25.32m) and **15325** (19.58m). From 2115 to 2152 on **11845** (25.33m), **15325**, **17820** (16.84m) and on **21595** (13.89m).

The Afro-European Service in English is from 0710 to 0745 on **9625** (31.17m), **11720** (25.60m), **15325** and **17820**, the last two frequencies being relays from Daventry.

The African Service in English is from 1831 to 1915 on **11845**, **15325** and **17820**.

Additionally, programmes to the Canadian Forces in Europe are radiated as follows – from 0558 to 0630 on **9625** and on **11725**. From 1055 to 1215 on **11850** and on **15325**. From 1630 to 1700 on **11850**, **15325** and on **17820**. From 2045 to 2115 on **11845**, **15325**, **17820** and on **21595**; also from 2158 to 2230 on **11845** and on **15325**.

● SWITZERLAND

Programmes in English from Berne are now as follows – from 0645 to 0730, from 1100 to 1130, from 1300 to 1345, from 1515 to 1600, from 1800 to 1815 and from 2100 to 2130 daily on **6165** (48.66m) and **9535** (31.46m) from 0645 to 1530 and on the additional channel of **3885** from 1530.

● PARAGUAY

According to BADX, the new high power (100kW) transmitter of Radio Nacional, on 5273 (56.89m) has commenced operations. Readers will recall that the low-powered experimental transmissions were reported some months ago.

● SWAZILAND

Swazi Radio is now on the air from 0400 to 1700 on 6155 (48.74m) and from 1600 to 2200 on 3223 (93.09m). The address is - Swaziland Commercial Radio (Pty) Ltd., P.O. Box 941, Mbabane, Swaziland or P.O. Box 23022, Joubert Park, Transvaal.

● U.S.S.R.

From 'Bandspread', we learn that contacts between the ground and manned spaceships can be heard on 18000 (16.66m) and on 18035 (16.63m)

● MAURITANIA

The Republic of Mauritania has a 30kW transmitter at Nouakchott operating on 4850 (61.86m) that can often be logged here in the UK. The weekday evening schedule is from 1800 to 2230 whilst on Sundays it is from 1700 to 2300. Listen around 2030 or so for this one, languages are French, Arabic or local vernaculars.

● ARAB AMIRATES

Dubai Radio is reported by BADX on 6040 (49.67m) around 1500 to 1700 daily. Identification is given as "Idahat el Dubai el Amirates al Arabia"; roughly translated as "This is Dubai, Arab Amirates, here".

● TURKEY

The Voice of Meteorology, Ankara, operates on 6900 (43.47m) and has been heard with Turkish vocal music at 1850. The station is operated by the Turkish State Meteorological Service and broadcasts Turkish music and weather reports on the hour during the periods as follows - from 0500 to 0700, from 0800 to 1000, from 1200 to 1600 and from 1800 to 1930. The address is - P.O. Box 401, Ankara.

The Turkish Home Service can be heard from 0355 to 0600 on 11880 (25.25m) and on 9515 (31.53m) from 0800 to 1100.

Broadcasts in English, according to the schedule, can be heard from 1330 to 1400 on 17820 (16.84m) and from 2200 to 2230 on 9515 and on 15195 (19.74m).

The clandestine Bizim Radyo (Our Radio) operates on 5915, 6200, 9500 and on 9585, according to BBCMS. All programmes are in Turkish, listen on either 6200 or 5915 (48.39m and 50.72m respectively) around 2030.

● NIGERIA

The Voice of Nigeria on 15185 (19.76m) may be heard with a programme in English at 0700 according to BADX.

Lagos on 4990 (60.12m) has been logged recently with an evangelical programme in English at 1940, complete with local preacher and choir.

● AUSTRALIA

Radio Australia can be heard daily at 0700 on 9570 (31.35m) when it was recently logged with 'Mailbag'.

Radio Australia can also be heard on 15240 (19.69m) around 2150 with a newscast.

The Pacific Islands Service was noted by us recently on 9590 (31.28m) at 2130 when the identification and intended target area were announced.

JULY 1972

● KUWAIT

Radio Kuwait can be heard on 15345 (19.55m) at 1615 with African and Arabic news in English followed by 'pops'.

● TANZANIA

Radio Tanzania is to be heard on 15435 (19.44m) at 1900 with the news in English.

● SEYCHELLES

FEBA can be heard in English on 15435 (19.44m) around 1730.

● SENEGAL

Ziguinchor on 3336 (89.95m) can occasionally be logged here in the U.K. if conditions are right. The 4kW signal was recently heard at 1955 when a programme of marches, with announcements in French, were heard - also the surrounding utility transmissions!

● CHINA

Radio Peking was heard recently on 9965 (30.11m) with news of Vietnam in English at 1955; also heard on 15165 (19.78m) with a programme in an Asian dialect at 1640, similarly on 9020 (33.26m) at 2035; also on 9030 (33.22m) at 2344 with a programme in English.

● ROMANIA

Radio Bucharest can be logged, with the English programme, on 11940 (25.13m) at 2100, also in parallel on 9690 (30.96m).

● ANGOLA

CR6RG Radio Commercial de Angola may be heard on 4795 (62.57m) where it was logged by us recently at 1825 with a musical programme, identification at 1830.

● FRENCH GUIANA

The latest schedule of ORTF Cayenne (just to hand) is - Monday to Friday from 0915 to 1130 on 3385 (88.63m) and 4972.5 (60.33m); from 1500 to 1730 on 4972.5 and 6170 (48.62m); from 2030 to 0115 on 3385 and 4972.5. Saturdays from 0915 to 1130 on 3385 and 4972.5; from 1500 to 0200 on 4972.5; from 1500 to 2030 on 6170; from 2030 to 0200 on 3385. Sundays from 1000 to 0115 on 4972.5; from 1000 to 1200 and from 2030 to 0115 on 3385; from 1200 to 2030 on 6170. All transmitters are 4kW except 4972.5 which is 1kW only. (BADX).

● U.S.A.

WINB Red Lion has been reported on 17720 (16.93m) at 2055 with "Mail Call" in English and requesting reports; off at 2100. WINB has been logged by us at 2115 on 15185 (19.76m) with a sectarian sponsored programme and full identification at 2130.

● MOZAMBIQUE

Radio Clube Mozambique may be heard fairly regularly here in the U.K. on 4762 (63.00m) where it was recently heard by us at 2020 with a musical programme and announcements.


● MALI

Bomako can be heard on 4783 (62.72m), often logged here around 1900 or so with announcements in French, transmitter is 18kW.

● ITALY

Rome was recently heard here on 9710 (30.90m) with identification and programme in English at 1945.

In your work shop

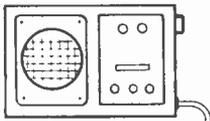

"WHAT WE WANT IN THIS WORK-shop," announced Dick, "is a microwave oven."

Smithy's assistant glanced down discontentedly at the last of his lunch-time sandwiches. Smithy, on the other hand, appeared to be entirely satisfied with his own mid-day fare, and he took a gargantuan bite out of his Wall's pork pie.

"What on earth," he asked indistinctly, "do we need a microwave oven for?"

"So that we can warm up things to eat."

"Such as?"

"Well," said Dick reflectively, "things like pasties or beefburgers or shish-kebabs. Things like that."

"Humph," grunted Smithy, taking a further bite and masticating vigorously. "I think it would be better to let matters stay as they are. Besides, these microwave ovens are a bit too expensive for just warming up odd pasties and beefburgers. What were those other things you mentioned?"

"Shish-kebabs."

READERS' HINTS

Smithy frowned, and a look of determination spread over his face.

"I don't think," he remarked resolutely, "that I'll take this conversation any further. I've got a funny feeling that, if I do, I'm liable to encounter things which are even more mind-bending. We shall now change the subject."

Smithy put the last of his pork pie into his mouth, poking it in to its entirety with the tip of his index finger.

"All right," returned Dick, hastily averting his eyes. "We'll talk about

750

This month Smithy the Serviceman, aided as always by his able assistant Dick, takes a respite from servicing work and discusses the latest batch of hints received from readers

something else, then. What do you suggest?"

But there was no response from the Serviceman, and Dick had to wait a full thirty seconds before, with one last prodigious swallow, Smithy finally despatched the remnants of the pie. He next proceeded to pick up his disgraceful tin mug, from which he drank noisily.

"Ye gods," exclaimed Dick, disgustedly. "The R.S.P.C.A. ought to put out special drinking bowls for people like you. Anyway, what do you suggest we talk about?"

"I can think of an excellent topic," responded Smithy, obviously refreshed by his repast. "What about readers' hints?"

Dick immediately forgot all his grievances about his lunch-time food.

"Readers' hints?" he repeated enthusiastically. "Why, that would be smashing, Smithy. It's ages since we last had a go at those."

"It is rather a long time," agreed Smithy. "As it happens, quite a few hints have come in since our last session, so if you'd be good enough to fill my mug for me I'll go and sort them out."

Eagerly, Dick took up Smithy's mug and carried it over to the sink, alongside which were ranged the cracked and battered culinary effects of the Workshop. Whilst Dick replenished Smithy's mug, that worthy opened a drawer in his bench and took out a sheaf of letters. He was already glancing through the uppermost letter in the

pile when Dick returned and placed Smithy's mug, now recharged with the precious fluid so necessary for the Serviceman's well-being, down on his bench. Drawing up his stool, Dick settled himself alongside the Serviceman.

"Here," remarked Smithy looking, more closely at the letter in his hand, "is a good one to start off with. It's an idea for a trimming tool, and there's a diagram of it in the letter."

Smithy showed Dick the diagram. (Fig. 1).

"I'll read out what the letter says," he continued, "When re-aligning or peaking coils or trimming capacitors in radio receivers, difficulty is sometimes encountered in accurately tuning these. This is particularly true if the final trimming position is very sharp, and it is often difficult not to over-adjust and go beyond the peak. In cases like these it isn't always possible to know whether the trimming is as accurate as it should be. A simple solution is to use a slow-motion drive as shown in the sketch. This can consist of a knob and a Jackson Brothers ball drive type 4511 or 4511/F coupled to a non-metallic trimming tool. It is an easy matter to use the device. Simply locate the trimming tool on the trimmer or coil core to be adjusted, then turn the body of the ball drive for initial rough trimming. Finally, hold the body of the ball drive stationary with one hand and turn the knob with the other to obtain fine adjustment. With the Jackson drive, the step-down ratio in rotation is 6:1. In circuits where hand-capacitance is evident an extra-long plastic trimming tool is required. The slow motion drive can, of course, be of a different type offering possibly a higher ratio, but the one used here is about the cheapest and simplest that can be obtained."

Smithy put down the letter and took up his mug, from which he drank deeply.

"That," remarked Dick warmly, "was a jolly good idea. What's the next hint, Smithy?"

Smithy placed his mug on the bench and examined the next letter.

"This," he chuckled, after some moments, "is another of the toothpaste tube hints."

"What d'you mean?"

"It's yet another scheme," grinned Smithy, "for using the screw tops from toothpaste tubes. I sometimes wonder whether the chaps who design these screw tops realise how many uses radio construction enthusiasts find for them! This present one is particularly neat and takes advantage

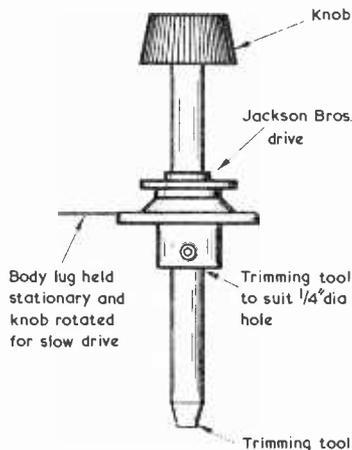


Fig. 1. An unusual trimming device which enables critical adjustments to be carried out

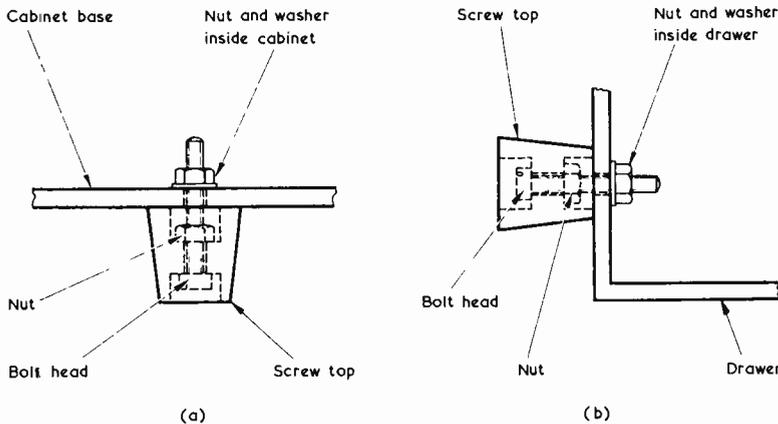


Fig. 2 (a). Toothpaste tube screw tops with recesses in the head make excellent cabinet feet

(b). The screw tops may also be used as knobs for small drawers

of the fact that many toothpaste tube screw tops nowadays have a tapered shape with a considerable recess in the top side. This makes it possible, after a hole has been drilled through the centre of the screw top, to fit a nut and bolt to it with the bolt head completely inside the recess. Four screw tops mounted in this way may then be employed as cabinet feet, whereupon they give a colourful finish to any cabinet with which they are used and also ensure that it doesn't scratch any surface it's placed on. If you keep components or nuts and bolts in small drawers, the screw tops can also be

used as drawer knobs. In this case, they're turned round so that the wider part is on the outside."

Smithy passed the letter over to Dick, who looked closely at the two sketches in it. (Figs. 2 (a) and (b).)

"And here," went on Smithy, picking up a third letter, "is an idea which, whilst not being entirely new, is certainly worthy of being more widely known and acted upon than it is. It's a safety precaution and it has to do with panel-mounting fuseholders."

"Panel-mounting fuseholders?" repeated Dick in some surprise, as he handed the previous letter back to

Smithy. "I shouldn't have thought you could have anything much safer than a panel-mounting fuseholder as it stands. So far as the front of the panel is concerned, all the fuseholder innards are covered and completely insulated. How is it that you need a safety precaution?"

"The innards are covered and completely insulated," Smithy corrected him, "only when the fuse is inserted and the cover is screwed up. The time when accidents are liable to happen is when you're inserting or removing the fuse."

Smithy indicated three sketches in the letter. (Figs. 3 (a), (b) and (c).)

"If the panel-mounting fuseholder is in a high voltage circuit," he went on, "you should never connect the source of voltage to the fuseholder contact which is nearer the panel. This is because the inside end of the fuse may touch the associated metal thread when it is being inserted or withdrawn. If the fuse is good the outer contact, which is not at this stage inside the housing, becomes connected to the source of voltage and the person handling the fuse can get a nasty or even dangerous shock. The source of voltage should connect to the rear fuseholder contact. The fuse cannot then make contact to it until it's nearly fully inserted, at which point all the internal connections are completely covered by the insulated parts of the fuseholder."

"Gosh," remarked Dick. "That's something I'd never thought of before. I'll be careful when wiring up these fuseholders in future. Particularly if they're in mains circuits."

"I should," recommended Smithy. "I know that you're usually supposed

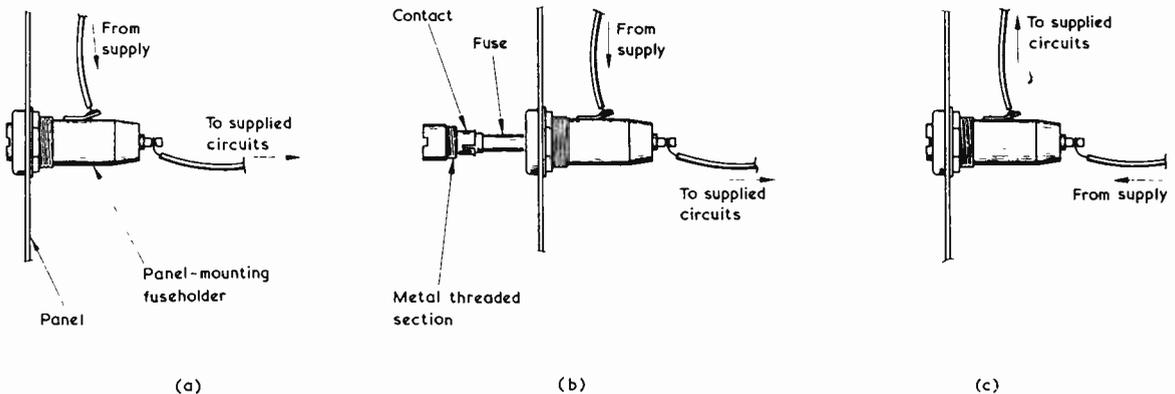


Fig. 3 (a). If a panel-mounting fuseholder is in a supply circuit having a high voltage with respect to earth, the method of connection shown here should never be used

(b). This is because, if the fuse is not blown, a large metal surface area outside the fuseholder can momentarily take up the high potential when the fuse is being fitted or withdrawn

(c). With the correct method of wiring the fuseholder shown here, in which the supply is applied to the rear contact, connection to the supply voltage is only given when the fuse is nearly fully inserted

Your Local Supplier

LONDON

Established 1910

H. L. SMITH & CO. LTD.

Comprehensive stocks of
components by
all leading makers

287-9 EDGWARE ROAD
LONDON W2 1BE

Tel: 01-723 5891

THE MODERN BOOK CO.

Largest selection of English &
American radio and technical
books in the country.

19-21 PRAED STREET,
LONDON, W2 1NP

Tel: 01-723 4185/2926

ST. HELEN'S RADIO

Hi-Fi Equipment
Tape Recorders
Radio Receivers
Television

SPECIALISTS IN RADIO
& ELECTRONIC TEXTBOOKS

ST. HELENS GARDENS
LONDON, W.10

Tel: 01-969 3657

NEW

15 watt Hi-Fi
plus 25p postage & packing
£3.75 each
AMPLIFIERS

**7 TRANSISTORS - GUARANTEED
PRINTED CIRCUIT - TESTED
DESIGN BUILT - INSTRUCTIONS**

A great new 15 watt HiFi amplifier is now available at the low cost of £3.75. Just look at the specification—Power 15 Watts R.M.S., frequency response 15-19000 c/s. Signal to noise ratio better than 70 db. Harmonic distortion 0.1%. Input sensitivity 750 mv into 2k. These make the H. Electronics HiFi amplifier the best at its price—order now.

H-ELECTRONICS.

105, Grange Road, London, S.E.25

to switch off before you fit or take out a fuse, but it's easy to forget to do this. Also, in some mains-operated equipment the fuse may appear on the mains side of the on-off switch."

SHUNT STABILIZER

Smithy put down the letter and took a further copious draught from his mug. A morose expression suddenly appeared on his features.

"It's no good," he sighed. "My curiosity, as always, is getting the better of me. What in heck are shish-kebabs?"

"Shish-kebabs?" repeated Dick.

"Why, a shish-kebab is a lot of bits of meat and stuff all impaled on a skewer. They eat shish-kebabs out in Egypt and places like that."

"Then," remarked Smithy, "even if we did have a microwave oven, I hardly think we'd be able to warm up exotic Eastern foods like shish-kebabs. So far as suppliers of cooked food are concerned, all we've got in this locality are a Wimpy, an Indian restaurant which serves Vesta curries and a take-away Chinese kitchen which just sells chicken and chips with noodles."

"You're forgetting Joe's Caff."

"Joe's Caff," repeated Smithy incredulously. "Isn't Joe the chap who keeps changing that scruffy old place of his around and who gives it a different name each time?"

"That's right."

"Since when has Joe been selling Egyptian food?"

"For quite a long time now," replied Dick. "He got the idea after hearing how popular this Egyptian Tooting Common show up in Smoke has been. He reckons that if people are as interested as that in Egyptian things he's going to cash in on it."

"I knew it," said Smithy regretfully. "I knew it! I should have had enough sense to have dropped this conversation at the shish-kebab stage. Now, I've got to keep on. At least, however, I can try to straighten things out as I go along. To start off with, that business up in London is not a show, it's an Exhibition and it's showing the treasures taken from Tutankhamun's Tomb. Tutankhamun, you should know, was a king of Egypt around 1400 B.C., and he died before he was twenty."

"Did he?" replied Dick politely, and without the slightest trace of interest. "Well, you know what Joe's like when he gets an idea into his head. He's changed his place round now so that it's all Egyptian. He's got Egyptian style pictures on the walls. Right queer pictures they are too, with geysers in smocks and dog's heads on them, and palm trees and oases in the background. Also, he's given new names to his regular dishes."

Smithy gritted his teeth.

"Tell me."

"Let's think now," said Dick. "Ah yes, well, there's Cairo Collation."

"What's that?"

"Egg and chips. Then there's Alexandria Appetiser."

"Go on."

"That's beans and chips. Then there's Sahara Special, which is pie and chips."

Dick paused, and a glint of naked voraciousness gleamed in his eyes.

"The best of the lot," he went on droolingly. "is Sarcophagus Supreme."

Smithy raised his eyes to the ceiling.

"I'll have to know," he groaned. "What's Sarcophagus Supreme?"

"It's egg, beans, pie and two lots of chips, together with three good dobs of chop sauce on the side of the plate!"

"That's enough," said Smithy hurriedly. "That's more than enough for now. Let's get back to those hints again."

"As you like," said Dick equably. "Still, you have to agree that old Joe does have a bit of style about him."

"I wouldn't argue about that," retorted Smithy. "Anyway, let's get on with the next letter."

Firmly, he turned his attention to the next letter in the pile on his bench. As he read it, all thoughts of the activities of the innovation-prone Joe passed from his mind.


"Ah," he said keenly. "This is a good one, too. You'd better have a look at the circuit that goes with it."

Smithy removed a circuit diagram which had been clipped to the letter and passed it over to his assistant. (Fig. 4 (a)).


"This circuit," he went on, "is for a novel stabilized power supply. The voltage on the zener diode is passed to the two transistors, each of which is connected as an emitter follower. TR1 is a power transistor, such as the OC28, whilst TR2 is a smaller transistor, and could be, say, an ACY18. Neither type is critical provided it can cope with the voltages and currents in the circuit. TR2 needs a reverse base-emitter voltage rating that is greater than the zener diode voltage. The zener diode voltage is present across the 400µF capacitor and will be applied as a reverse voltage to the base and emitter of TR2 if the stabilized output should be accidentally short-circuited. Incidentally, the maximum reverse base-emitter voltage for the ACY18 is 12 volts."

"I think I can see," said Dick frowning, as he concentrated on the diagram, "how this works. Since TR1 and TR2 are emitter followers, the zener voltage, plus the small forward voltage drops in the base-emitter junctions of the two transistors appears at the emitter of TR1."

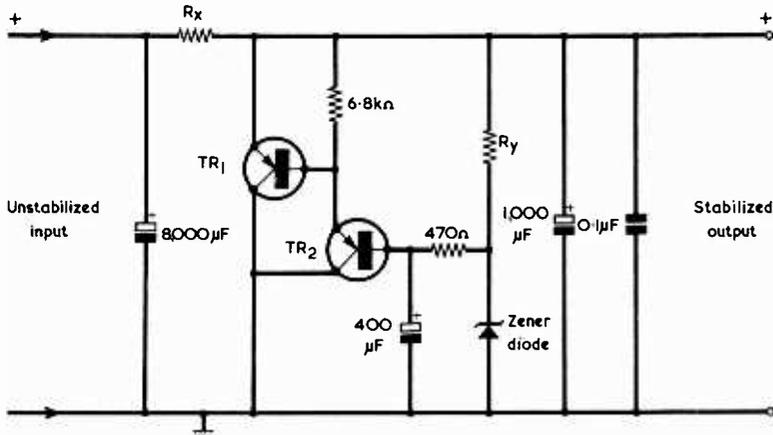"That's right," confirmed Smithy. "The series resistor Rx is given a value which causes slightly more than the maximum desired output current to flow through it. To take an example, let's assume that we want a stabilized output at around 10 volts with a maximum current of 100mA, and that the



(a)

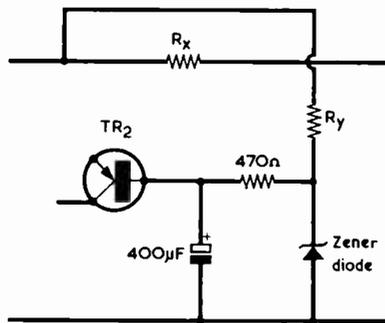

(b)

Fig. 4 (a). Experimental stabilized power supply circuit. The value of R_y should be chosen to suit the zener diode employed
(b). To ensure a greater voltage drop across it, R_y could, alternatively, be returned to the left hand side of R_x

unregulated input voltage is approximately 15 volts when, say, 125mA is drawn from it. We can choose a zener diode just below the 10 volt level, whereupon the emitter of TR1 is 10 volts above chassis. Let's next give R_x a value of 40Ω. This will cause our current of 125mA to flow through it. If no output load is connected, practically all this 125mA will flow through TR1. If an output load is connected, some of the 125mA will flow through it and the remaining current will flow through TR1, but the output voltage will still remain the same. If the maximum output current of 100mA is drawn, only 25mA will now flow through TR1, but the output voltage will still be the same."

"Blow me," said Dick enthusiastically. "That's neat! All the time you've got the same current flowing through R_x , which means that the load on the unregulated input remains constant."

"Exactly," confirmed Smithy. "This

factor will assist in obtaining good stabilization. With the figures I've used the dissipation in R_x is 5 volts multiplied by 125mA, which comes out to - let me see now - 0.625 watts. For zero output current the dissipation in TR1 is 10 volts multiplied by 125mA, which is equal to 1.25 watts. This would require TR1 to be mounted on a smallish heat sink, and an incidental advantage of the circuit is that the collector of TR1 is at chassis potential, whereupon it can be bolted direct to the power supply chassis. The chassis will then act as a heat sink."

"I see," remarked Dick, "that the zener diode series resistor, R_y , is returned to the output voltage. But that voltage will only be a little higher than the zener voltage itself."

"True enough," agreed Smithy. "The zener current is the sum of the current through this resistor plus the small base current for TR2, and in most practical cases the latter could be

Your Local Supplier

HAMPSHIRE

BOURNEMOUTH

LARGEST HI-FI AND
RADIO COMPONENT
STORE IN THE SOUTH

FORRESTERS NATIONAL
RADIO SUPPLIES LTD.

70-72 Holdenhurst Road
Bournemouth

Telephone 25232

SURREY

**WITWORTH
TRANSFORMERS**
TV Line out-put transformers

Manufacturers of the largest range in the
country. All makes supplied.

Free catalogue.

Modern
BAIRD, BUSH, GEC, PHILIPS
Replacement types ex-stock.
For "By-return" service, contact London
01-948 3702

Tidman Mail Order Ltd., Dept. R.C.
236 Sandycombe Road,
Richmond, Surrey TW9 2EQ

Valves, Tubes, Condensers, Resistors,
Rectifiers and Frame out-put Transformers,
Mains Transformers also stocked.
Callers welcome.

SUSSEX

E. JEFFRIES

For your new television set
tape recorder, transistor radio
and hi-fi equipment

PHILIPS, ULTRA, INVICTA
DANSETTE, MASTERADIO, PERDIO,
MARCONE, PHILCO FIDELITY

6A Albert Parade
Victoria Drive,
EASTBOURNE SUSSEX

EIRE

PEATS for PARTS

ELECTRONIC COMPONENTS
RADIO & TELEVISION

For the convenience of Irish
enthusiasts we supply

The Radio Constructor
Data Books and
Panel-Signs Transfers

Also a postal service

Wm. B. PEAT & Co. Ltd.
28 PARNELL STREET
DUBLIN 1

ignored. The circuit is in the experimental category, and it might be of interest to return the zener series resistor to the unstabilized end of Rx instead. It will, of course, require a value which does not cause zener diode dissipation to be excessive. In most cases the zener diode could be a 400mW type." (Fig. 4 (b)).

POLYSTYRENE TILES

Smithy put the letter to one side and picked up another, which he read carefully.

"Now this is another interesting one," he announced after some moments, "and I think that the best thing I can do is to read out the letter to you as it stands. 'Here are some suggestions,' our correspondent starts, 'which you might find of value and they concern the usefulness of polystyrene ceiling tiles in the construction of electronic devices. The large surface area of polystyrene tiles allows them to dissolve rapidly in solvents like xylenc or benzene, which are available from chemists. A strong tricky solution is given which, when painted on wires and on the underside of printed circuit boards, forms a quick-drying insulating film which prevents short-circuits.'"

"That," remarked Dick, "sounds to me like a jolly useful dodge. Those polystyrene tiles aren't all that expensive, either."

"There's more to come yet," commented Smithy, as he continued to read through the letter. "Another suggestion here points out that a polystyrene tile forms a useful components 'park' whilst one is constructing a project. Components can be jabbed into the tile by their wires instead of lying around and getting lost. A piece of thin paper placed over the tile can be written on to identify the components and the constructor can then easily tell what components have been used. Yet a further idea is that projecting wires on the underside of a printed circuit board can be exploited for anchoring the board to a polystyrene tile when the board is under test. This is far better than having the board flap around on a bench amongst bits of wire, beads of solder, and all the other things which tend to clutter up the surface of a bench."

"Stop me," remarked Dick elegantly. "Those ideas certainly take full advantage of polystyrene tiles. I particularly like the last one. Loose printed circuit boards can be an awful menace on the bench, particularly if they're small ones."

"They can be a nuisance," concurred Smithy, reaching for another letter. "Now, what have we here? Ah yes, this is one of those nice simple ones which often prove to be amongst the most useful of all. The idea is for an indoor Band I - Band III TV aerial. All it consists of is a half-wave dipole, and

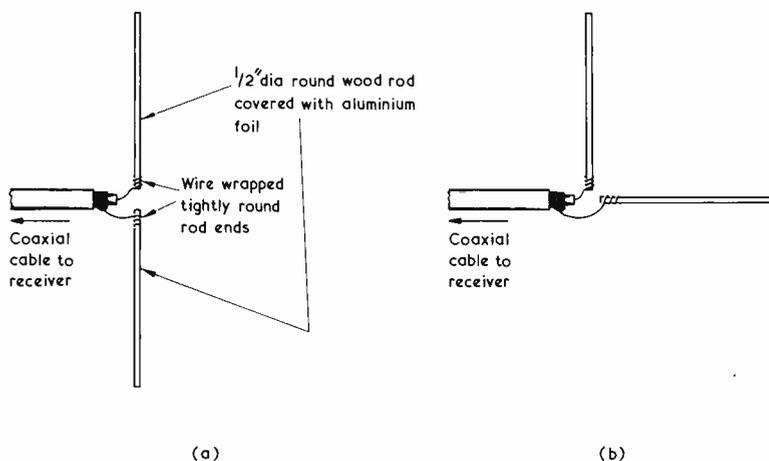


Fig. 5 (a). An indoor TV aerial for Bands I and III can be made as shown here. The aerial is a half-wave dipole
(b). If space is limited, the lower section may be at right angles to the upper section

each element is made up of $\frac{1}{2}$ inch diameter wooden rod around which is wrapped aluminium cooking foil."

Dick leaned over and examined two sketches which Smithy had taken from the letter and laid out on his bench. (Figs. 5 (a) and (b)).

"The advantage of this approach," Smithy continued, "is that each section of the dipole has an adequate width for reasonably broad band reception of the channel for which it is resonant. At the same time, the materials employed are inexpensive and easy to obtain. The foil can, of course, be secured at various points along the length of the wooden rods by Sellotape or similar adhesive tape. The bottom section of the aerial need not be vertical. If it is found more convenient, it can be at right angles to the top section."

"What about the lengths of the sections?"

Smithy stood up, leaned over his bench, and took a copy of "TV Fault Finding" from the shelf above it.

"Each section of the aerial," he replied, as he turned the pages of the book, "will be a little shorter than a quarter-wave. But there's no need to work out the lengths because they've been listed here in the chapter on aerials. Let's see now. Here we are: the length of each section should be 5 feet 2 inches for Channel 1, 4 feet 6 inches for Channel 2, 4 feet 3 inches for Channel 3, 3 feet 9 $\frac{1}{2}$ inches for Channel 4 and 3 feet 6 $\frac{1}{2}$ inches for Channel 5."

"What," asked Dick, "about Band III?"

"For Band III," replied Smithy, "the lengths are 1 foot 3 $\frac{3}{4}$ inches for Channel 6, 1 foot 3 $\frac{1}{4}$ inches for Channel 7, 1 foot 2 $\frac{1}{2}$ inches for Channel 8, 1 foot 2 $\frac{1}{4}$ inches for Channel 9, 1 foot 1 $\frac{1}{2}$ inches for Channel 10, 1 foot 1 $\frac{1}{4}$ inches for Channel 11, 1 foot 1 inch for

Channel 12 and 1 foot and $\frac{3}{4}$ inch for Channel 13. You'll probably find that an indoor aerial of this kind won't be so good at Band III as it is at Band I. If you're lucky, an indoor aerial made for a local Band I transmission will cope reasonably well at Band III, even though it won't be properly resonant at the Band III frequency. Blimey, all this talking has made me thirsty!"

POOL ALARM SYSTEM

Smithy reached over and took an enormous draught from his tin mug.

As he placed the mug back on his bench, a thought struck him.

"I know I'm tempting Providence," he said reluctantly, "but there's one final thing that I must know about Joe's Cuff before I finish."

"Oh yes," said Dick, "and what's that?"

"Well," continued Smithy, "when Joe changes his place round he always gives it a new name. Has he done so this time?"

"He has," confirmed Dick, "and what's more he's chosen a really smashing one, too. It sounds all Egyptian and mysterious."

"What's he called it?"

"He's called his place 'The Sphinx's Inscrutable Smile.'"

Smithy looked impressed.

"I must say," he remarked approvingly, "that sounds very effective. Is there any reason for this choice?"

"Oh, definitely," replied Dick. "Apparently there's some ancient Egyptian folklore involving the Sphinx, together with the sands of the Nile and the gloom of the camel."

"Is there?" commented Smithy. "I must say that you can always give Joe credit so far as the picking of names is

concerned."

His curiosity satisfied, Smithy returned to his letters.

"Now, here," he remarked, as he perused the next letter, "is quite an unusual one, and it comes from a reader who lives in Australia. Our correspondent has a swimming pool, and he wanted a device which would indicate when, during refilling, its level had reached a certain height. He took an old moving-coil meter, cut the pointer short and soldered a piece of hair spring wire onto it. Another contact was made from a brass pin inserted in a piece of Perspex, this being fixed so that the hair spring wire touched it when a current was passed through the meter coil. This sketch shows the idea."

Smithy pointed to a drawing in the letter. (Figs. 6 (a) and (b).)

"The water level sensing contact," he resumed, "is a brass tip sticking out of a piece of plastic tubing. This tip is held at the desired height by securing the tubing in one half of a pair of compasses, the tubing being passed through the part which normally holds the pencil. The level contact is wired to one side of the meter coil, which is sited some distance away from the pool. Only one wire between the level contact and the meter is needed, and the other side of the meter coil connects to a battery and thence to an earth connection."

"It's easy to see how this device works," broke in Dick eagerly. "When the water level reaches the brass tip a circuit is completed from the battery to the meter coil via earth and the water of the swimming pool. The

meter pointer then moves over and the brass hair spring wire touches the insulated brass pin on the modified meter, thereby causing the bell to ring."

"That's right," said Smithy. "As you can imagine, the process of modifying the meter is one which should only be tackled by those who are capable of carrying out fine work. Incidentally, this letter says that the prototype set-up has been in use successfully for a long time now. Since it is battery operated, there is no risk of any mains leakage into the pool."

"I wonder," queried Dick, "what sensitivity the meter should have."

"I would suggest that something like a 0-1mA movement would be the sort of thing required," replied Smithy. "The current through the meter coil when the water completes the circuit would be mainly limited by the resistance between the water and the contact tip. I would think also that it would be a good idea to measure that current by inserting an additional meter in series. If the current passing through the meter coil was well in excess of the f.s.d. value for the meter before it was modified it would be wise to insert a fixed resistor in series to limit it to, say, about twice the f.s.d. value."

"Are there any more hints?"

Smithy looked at the letters on his bench.

"There's just one I haven't dealt with," he remarked, picking up the final letter. "Now let's have a look at this."

Smithy read the letter carefully.

"This letter points out," he said, "that the construction of odd projects purely for fun tends to be rather expensive if Veroboard or printed circuit board is used. An alternative method is to make up the project on cardboard or similar material, the various connections being made to brass eyelets. The eyelets recommended have coloured heads and an inside diameter of slightly more than an eighth of an inch, and are available from most tool shops in packets of several hundred together with a pair of eyelet pliers. It is very easy to affix a number of these eyelets to a piece of cardboard, whereupon the components can be soldered to the unpainted brass sections. Here are a few samples which have come with the letter."

Smithy passed an eyelet, and some small pieces of cardboard to Dick, who examined them with interest. (Figs. 7 (a) to (d).)

"The brass parts of these eyelets," he remarked, "open out into six parts after the eyelet pliers have been applied."

"That's right," agreed Smithy. "You'll notice one of those sample cards has a circuit drawn out on it. If the eyelets are inserted at the drawn circuit junctions, the components corresponding to the circuit symbols can then be soldered to them."

"Blow me, that's neat," exclaimed Dick. "There's another piece of cardboard here which has the word 'Tag-strip' written on it."

"Ah yes," said Smithy, consulting the letter. "That's another application for the eyelets. The coloured heads on

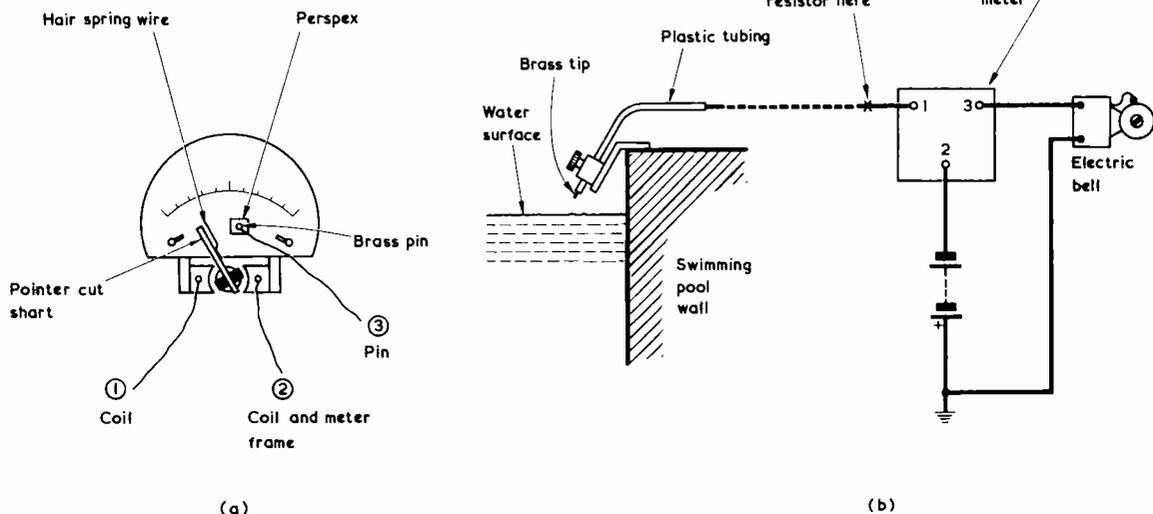


Fig. 6 (a). A water level sensing device incorporates a moving-coil meter modified in the manner shown here
 (b). The complete circuit of the water level sensing device. It is advisable to monitor current flow at the point marked with a cross and, if necessary, then insert a suitable current limiting resistor at this point


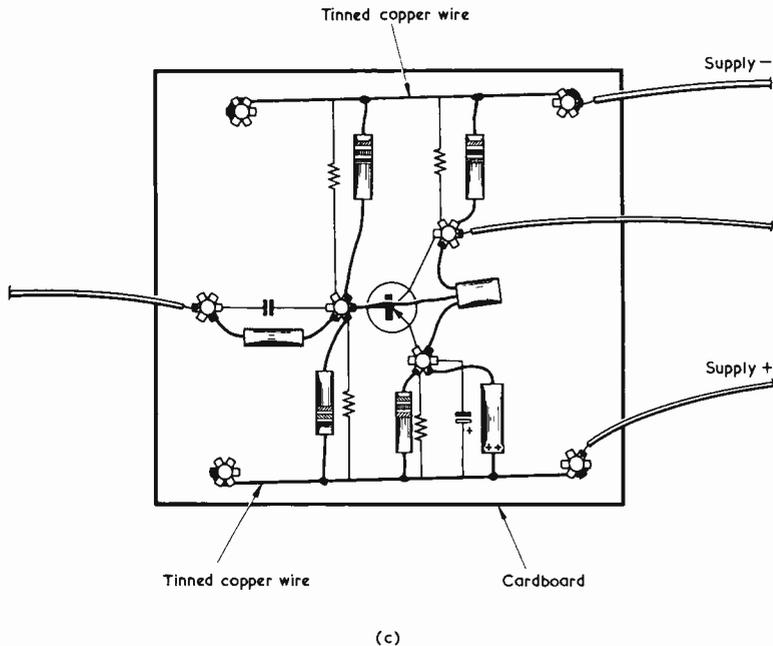
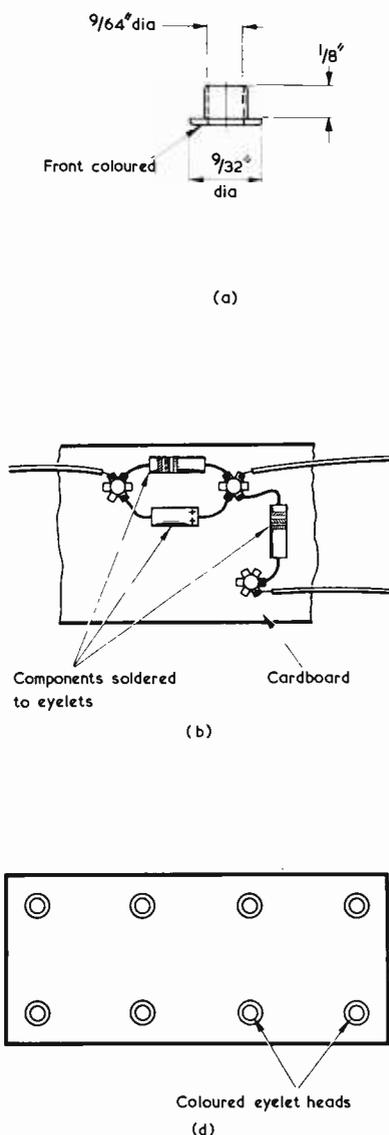


Fig. 7 (a). Brass eyelets mounted on cardboard may be employed for temporary circuits where a high level of insulation is not necessary. Approximate dimensions of a suitable eyelet size are given here

(b). Components are soldered to the turned-over sections of the eyelets

(c). A circuit can be initially drawn on the cardboard first, after which eyelets are inserted at circuit junctions and the components added to agree with the circuit. Tinned copper wires, each between two eyelets, provide negative and positive supply busbars

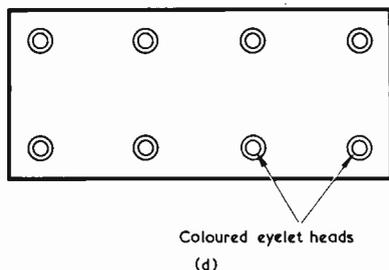(d). A 'tagstrip' can be made up using the eyelets. Their coloured heads may be employed to provide a wiring colour code



the other side can then be used to form a wiring code. Crafty, isn't it?"

LAST WORDS

"I'll say," replied Dick enthusiastically, "We've had some jolly good hints today, Smithy, haven't we?"

"Definitely," replied Smithy. "Still, we always do have useful hints sent in to us. I must confess I enjoy these hint sessions."

"So do I," said Dick warmly. "They make a real break from the normal run of things."

Smithy rose and, with an air of finality, gathered up the letters he had just read and returned them to the

drawer in his bench. He chuckled as a thought occurred to him.

"I wonder," he queried, "what will be the next craze old Joe gets up to."

"From what he was saying a couple of days ago," replied Dick, "he's already fed up with this Egyptian bit, and he's soon going to change his place over to something that he feels is more in keeping with the current scene."

"Why don't I keep my big mouth shut," groaned Smithy. "Now I've got to ask you what his next theme will be."

"It will be Women's Lib."

Smithy winced.

"And has he," he faltered, "chosen the new name for his place yet?"

"He has," replied Dick. "He's going to call it 'The Nonsuch Braserie'!"


EDITOR'S NOTE

The hints described in this episode of 'In Your Workshop' were submitted, in the order in which they appear, by I. G. Bennett, Vincent S. Evans, S. G. Peters, L. Cook, E. Switalski, F. Howard, B. A. Peach and B. K. Langley.

Further hints for this feature are welcomed and payment is made for all that are published.

The book 'TV Fault Finding' is published by Data Publications Ltd. ■

R. C. CROSSWORD

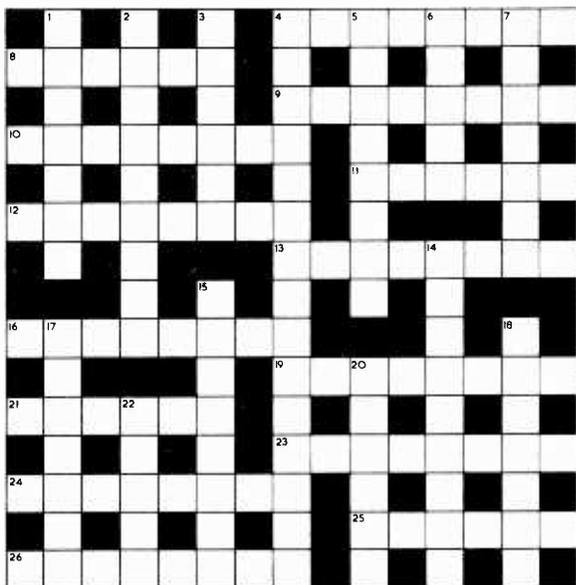

Clues Across


4. Shunt connection applicable also to bars. (8)
8. Bring on as a consequence. (6)
9. Too much of this feedback causes howls. (8)
10. Benders or twistors in crystal microphones. (8)
11. Even upset timers have their virtues. (6)
12. Ultimate demise of the transmitter p.a. section. (5, 3)
13. Complete harmony, despite having ac. or d.c. in a muddle. (2, 6)
16. Virtually, f.e.t. cut-off. (5-3)
19. Dielectric with permanent poles. (8)
21. Temporary circuit-checking assembly (if initially changed, can indicate frequent result!). (4-2)
23. Draws out (e.g. teeth). (8)
24. Resident engineers do this to equipment. (8)
25. The Yaxley switch is essentially this. (6)
26. Second dip in the solder-pot. (8)

Clues Down

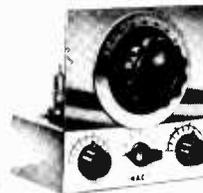1. Hold back, as at a gate input where output is suppressed. (7)
2. This receiver scans a wide frequency range. (9)
3. Pass away, as with time. (6)
4. Any number from zero to 360, lag or lead! (5, 10)
5. Add a square and this defines effective a.c. amps or volts. (4, 4)
6. In its early days was fondly referred to as 'lolly acquisition scheme for expensive research'. (5)
7. Points in for p.n.p., points out for n.p.n. (7)
14. What one of '18 Down' does after switch-off. (9)
15. Amplification in a closed path. (4, 4)
17. A diode can do this by passing signals in only one direction. (7)
18. The last things transistors want are these valve essentials! (7)
20. Complete. (6)
22. '18 Down' are inserted in cylinders made of this metal. (5)

(For Solution see overleaf)

H.A.C. SHORT-WAVE KITS WORLD-WIDE RECEPTION



Famous for over 35 years for Short-Wave Equipment of quality, "H.A.C." were the Original suppliers of Short-Wave Receiver Kits for the amateur constructor. Over 10,000 satisfied customers—including Technical Colleges, Hospitals, Public Schools, R.A.F., Army, Hams, etc.

NEW "DX" RECEIVER

Improved one-valve model "DX" mark 2. Complete kit—price £3.30 (post & packing 20p.).

Customer writes: "Australia, India and America at loud volume"—"I am 14 years of age and have logged over 130 stations, plus countless Amateurs from all over the world."

Send S.A.E. for test report.

This kit contains all genuine short-wave components, drilled chassis, valve, accessories and full instructions. Ready to assemble, and of course, as all our products—fully guaranteed. Full range of other S.W. kits, including the famous model "K" and "K plus" (illustrated above). All orders despatched by return (Mail order only). Send now for free descriptive catalogue & order form.

"H.A.C." SHORT-WAVE PRODUCTS
Dept. RC1, 29 Old Bond Street, London W.1

The RADIO CONSTRUCTOR

ANNUAL SUBSCRIPTIONS

to this magazine
may be obtained
through your
newsagent
or direct from the
publishers
ONLY £2.70
per year, post free

Please send remittance with name and address and commencing issue required to:

DATA PUBLICATIONS LTD
57 Maida Vale London W9 1SN

Radio Topics

By Recorder

MANY CONSTRUCTORS BUILD THEIR equipment direct from published designs, and obtain a considerable amount of satisfaction from the process. Others like to design all their equipment for themselves and this is an approach which gives even greater pleasure, since the enjoyment of construction is enhanced by a quality which more closely approaches the creative. I, myself, belong to both categories although, over recent years, I have devoted myself more to the assembly of home-brewed designs. Many of these have, however, been assisted by published designs including in particular, basic text-book circuits and manufacturers' Application Notes.

LOGICAL APPROACH

If you are going to design your own equipment it is well-nigh essential to adopt a logical approach. You must first say to yourself what exactly it is you are going to build and then sit down and work out its circuit. The circuit should be complete with component values. In some cases it is economical to use components, particularly the more expensive types, which are already on hand, and this can qualify one's approach to the design and its final specification. Such matters are, of course, the basic fundamentals of home construction.

No matter how keen you feel, it is always inadvisable to start an experimental project unless you have to hand *all* the components you think you'll need. It is frustrating, to say the least, to advance part-way with the construction of an item and then have to put it on one side until the missing parts can be obtained. It is far better to have all the components available, since the process of construction can then proceed unbroken.

Having acquired the parts, the next task is to work out the layout in which they will appear. This is another instance in which the wisdom of having all the components on hand becomes evident, since these can then be laid out physically and thus give a practical illustration of the dimensions required in the chassis, printed circuit board or Veroboard on which they are to be fitted. The layout must, of

course, follow the usual common-sense rules required for successful functioning. Amplifier inputs should be kept away from amplifier outputs, a.c. mains wiring should not too closely approach unscreened high impedance a.f. input circuits, and so on. If some of the circuitry is experimental, leave a little more space for it than is required by the components you *think* it will need. It may well be that, in the end, the experimental section requires one or more extra resistors or capacitors than had been originally anticipated.

Next proceeds the actual work of construction. Assuming that the parts are to be assembled on a metal chassis, it is a good plan to complete all the metal-work before any components are mounted and wired. Even so, it sometimes happens that an extra hole or holes has to be drilled to accommodate some part which hadn't been foreseen. Great care should be taken to avoid damaging components which have already been mounted if this additional metal-work has to be undertaken. Should any air-spaced variable capacitors be fitted on the chassis, their vanes should be closed whilst carrying out additional metal-work, since these components are especially vulnerable to physical damage. And, of course, all drill-shavings, etc., must be removed after the metal-work has been completed.

Eventually, the item is completed and is tried out. With luck, it will work satisfactorily at the first attempt, but it


is more than likely that one or two components, especially resistors and capacitors, may require adjustment in value. The experienced experimenter will have calculated what the most likely components in this respect are likely to be, and he will have connected them into circuit temporarily only. It is quite possible that the final value required in a resistor or capacitor is one which is not available in the spares box. Under these final circumstances it is then quite in order (provided there is no risk of incorrect operation in r.f. circuits) to make up the values, temporarily again, with several resistors or capacitors in series or parallel to ensure that the correct performance is given from the electronic point of view. The item of equipment is then nearly complete and its circuit operation is proven. It only remains to obtain, on the next component shopping expedition, correct resistors and capacitors to replace the temporary ones, after which these can be finally soldered into circuit.

One thing is essential for experimental work, and that is a testmeter. Fortunately, testmeters with quite a reasonable performance are available at low cost these days and, provided they are employed with care, can be of invaluable help. Experimental work without a testmeter is virtually impossible, since one is then working completely in the dark.

SPARE METERS

Talking of testmeters reminds me that one of the most useful buys I have ever made, so far as experimental work is concerned, consists of two Government surplus panel-mounting meters, one having an f.s.d. of 100 μ A and the other an f.s.d. of 1mA, which I obtained very cheaply some 20 years or so ago. I still occasionally use one or other of these to monitor current in an item of equipment if I require my testmeter for other tests in that equipment. But I use those two meters much more frequently as *voltmeters*.

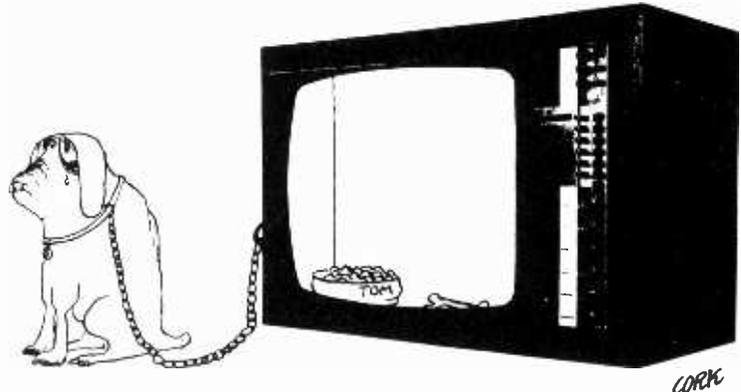A typical instance arises if I want to keep an eye on the voltage at any part of the equipment I'm checking and I can't spare the testmeter for the job.



THE RADIO CONSTRUCTOR

If, for instance, the voltage to be monitored is of the order of 6 to 7 volts, I take the 0-100 μ A meter, temporarily connect a 200k Ω variable resistor in series with it, and hook this combination across the two circuit points to be monitored. It is important to ensure, at this stage, that the variable resistor inserts maximum resistance into circuit. I also connect my testmeter, switched to an appropriate volts range, across the same circuit points; after which I reduce the resistance in series with the 0-100 μ A meter until it gives a reading corresponding to that in the testmeter, i.e. 60 μ A with 6 volts, 70 μ A with 7 volts, and so on. The 0-100 μ A meter may then be left in circuit to function as a 0-10V voltmeter. If the voltage to be monitored is less than 1 volt, I temporarily connect a 20k Ω variable resistor in series with the meter and carry out a similar adjustment to produce a 0-1V voltmeter.

Should the circuit being monitored be able to withstand a higher meter current, the 0-1mA meter can be employed in the same way. This time the series resistance required is one-tenth of that needed for the 0-100 μ A meter.

All of which goes to show just how easy it is to make up one's own test voltmeter incorporating a panel-mounting meter. One simply needs to fit the meter in an insulated case and provide series resistors for each voltage range required, each resistor being terminated in a separate socket. The other terminal of the meter is connected to a 'common' socket. A 0-100 μ A meter would be better than a 0-1mA meter for an application like this because, apart from the smaller current it draws, the series resistors dissipate an extremely low wattage. The series resistor for a 0-100V range would, for instance, be 1M Ω and, at meter f.s.d., this would dissipate only one-hundredth of a watt!

R.F. POWER TRANSISTORS

EMI-Varian announce the introduction of three new communications power transistors. These, shown in the accompanying photograph, are specifically designed for operation in broadband Class C or linear power amplifiers over the lower v.h.f. range, and are now available from EMI-Varian Limited, Hayes, Middlesex.

Operating from 28 volts and covering the frequency range of 30 to 80 MHz, the devices are the 3 watt type A3-28, the 25 watt type A25-28 and the 70 watt type A70-28. When used in a chain consisting of one 3 watt, one 25 watt and two 75 watt devices, a 140 watt output is achieved from an 0.2 watt input.

All the devices are 100% tested and guaranteed to withstand infinite v.s.w.r. at all phase angles when operated at 80 MHz, 28 volts rated power. Other features include reliable passiv-



Three new power transistors introduced by EMI-Varian for operation at 30-80 MHz. (See 'R.F. Power Transistors')

ated single chip construction, greater high frequency performance in low inductance hermetic stripline packages, and optimized power distribution via graded nichrome resistors.

PATIENT WEIGHING

From Finland comes an interesting story concerning electronic equipment for the weighing of hospital patients. As can be readily imagined, an important measurement in many intensive care situations is the stabilizing of a patient's weight, and this has been particularly difficult in the treatment of burns, pre- and post-operative therapy, pediatrics and geriatrics, dialysis and intravenous treatment. The patient under treatment can now, however, be weighed with a minimum of disturbance whilst still in bed with the aid of the Datex WM-104 Patient Weighing System.

The weighing system comprises four strain gauge load cells, which can be slipped under the legs of the bed, and an electronic control and display unit. Signals from the four load cell transducers are conducted to the control unit to tare and weight circuits and amplified to provide a readout on a panel meter. (Tare, in this case, is the weight of the bed and bedding without the patient). The patient's weight is determined in kilograms and grams

(after electronic cancellation of tare) by zeroing the meter panel deviation. Weight is displayed to six decimal figures with a maximum patient weight of 170kg, and a maximum tare-plus-patient weight of 370kg. The meter reading sensitivity is better than 10g, and with a separate suitable recorder the sensitivity is 1g.

Changes in weight can be shown directly on the panel meter, or from an external recorder, or they can be entered into a computer via a digital voltmeter. Several equipments can be connected to a central monitoring station and optional features include a weight change alarm system, a recorder, a carrying case for the transducers and a stand for the electronic control unit.

In Helsinki University Hospital the fluid balance of patients with 70% burns has been controlled successfully using this system. The readout is not seriously affected by patient movement or temperature fluctuations and the system can be installed in less than 30 seconds without disturbing the patient. The transducers can be sterilised by gas or liquids and, as they are connected only by cable, can be used with any bed or other equipment such as an incubator.

Further details on the equipment are available from Datex Oy, P.O. Box 10, 02100 Tapiola, Finland. ■

Solution to the puzzle on page 757.

ACROSS. 4, Parallel; 8, Entail; 9, Acoustic; 10, Bimorphs; 11, Merits; 12, Final end; 13, In accord; 16, Pinch-off; 19, Electret; 21, Mock-up; 23, Extracts; 24, Maintain; 25, Rotary; 26, Replunge.

DOWN. 1, Inhibit; 2, Panoramic; 3, Elapse; 4, Phase difference; 5, Root mean; 6, Laser; 7, Emitter; 14, Contracts; 15, Loop gain; 17, Isolate; 18, Heaters; 20, Entire; 22, Konel.

B. H. COMPONENT FACTORS LTD. DEPT. RC P.O. BOX 18, LUTON, BEDS. LU1 1SU

BARGAIN PRICES ALL GOODS GUARANTEED


ELECTROLYTIC CAPACITOR BARGAIN PACKS 80p each!			ELECTROLYTIC CAPACITORS			CERAMIC DISC		TRANSISTORS		ZENER DIODES		INTEGRATED CIRCUITS	
C1	C2	C3	0.64mfd 10V 2.5p	50mfd 25V 4p	5pF 500V 3p	2N706	3V3 BZ88C	1M7400N	15p				
1mfd 25V	1mfd 25V	4 1mfd 5V	1mfd 6V 2.5p	50mfd 40V 5p	5pF 750V 3p	2N708	3V9 BZ88C	1M7401N	15p				
2mfd 10V	2.5mfd 50V	10 2.5mfd 5V	1mfd 25V 2.5p	50mfd 50V 1p	10pF 750V 2p	2N1303	4V3 BZ88C	1M7410N	15p				
6 4mfd 50V	10mfd 50V	6 10mfd 5V	1mfd 50V 3p	64mfd 10V 4p	20pF 750V 2p	2N3866	5V6 IN752A	1M7430N	15p				
25mfd 25V	25mfd 25V	6 25mfd 2.5V	2mfd 10V 2.5p	64mfd 15V 4p	25pF 750V 2p	2N3055	6V8 BZ96C	1M7440N	25p				
50mfd 10V	32mfd 50V	32mfd 5V	2mfd 25V 2.5p	64mfd 25V 4p	40pF 750V 2p	BC108	7V5 BZ96C	1M7470N	30p				
100mfd 50V	3 300mfd 10V	3 100mfd 2.5V	2mfd 50V 3p	64mfd 40V 5p	60pF 750V 2p	BCY30	10V KS42A	5M7483N	80p				
			2.5mfd 5V 2.5p	100mfd 6V 1p	75pF 750V 2p	BFY51	13V BZ88C	1M7493N	80p				
			4mfd 10V 3p	100mfd 25V 4p	100pF 750V 2p	BFY56	20V BZ88C						
			4mfd 25V 2p	100mfd 50V 5p	120pF 750V 2p	BFX87	24V BZ88C						
			5mfd 25V 2p	200mfd 6V 4p	220pF 750V 2p	BSX21	30V MS255						
			6 4mfd 50V 3p	250mfd 6V 4p	4700pF 30V 3p	BSX60	BZ88 TYPE TESTED						
			8mfd 15V 3p	250mfd 10V 4p	10 0 1pF 30V 3p	C111	BUT UNMARKED						
			8mfd 25V 3p	250mfd 15V 4p	0 0 1pF 350V 2p	C407	ALL VALUES IN						
			8mfd 40V 3p	250mfd 25V 5p	0 0 22pF 30V 3p	C426	RANGE 2 13V 5p						
			10mfd 6V 1p	400mfd 10V 1p	0 0 22pF 30V 3p	P346A	OR 6 FOR 25p						
			10mfd 10V 3p	500mfd 10V 3p	0 0 47pF 30V 2p	V405A							
			10mfd 25V 3p	500mfd 12V 1p	1 1pF 25V 2p	OC35							
			10mfd 50V 4p	500mfd 25V 1p		OC36							
			16mfd 15V 3p	640mfd 10V 1p									
			16mfd 25V 3p	1000mfd 3V 1p									
			20mfd 25V 3p	1000mfd 6V 1p									
			25mfd 25V 3p	1000mfd 12V 1p									
			25mfd 40V 3p	1000mfd 25V 15p									
			25mfd 50V 4p	1000mfd 50V 35p									
			32mfd 25V 4p	2000mfd 12V 10p									
			32mfd 50V 4p	2000mfd 25V 25p									
			40mfd 6V 3p	2500mfd 12V 10p									
			40mfd 15V 3p	2500mfd 25V 25p									
			50mfd 10V 3p										

TERMS CASH OR CHEQUE WITH ORDER POST AND PACKING FREE ON ORDERS ABOVE £5 FOR SMALLER ORDERS PLEASE ADD 10p DISCOUNT ORDERS ABOVE £10—10% ABOVE £20—15% ALL GOODS ADVERTISED ARE TOP GRADE PROFESSIONAL COMPONENTS AND SUBJECT TO A MONEY REFUND GUARANTEE IF NOT SATISFIED WE HAVE MANY COMPONENTS NOT ADVERTISED AND ENQUIRIES ARE WELCOME. BUT MUST ENCLOSE AN SAE FOR REPLY PRICES LIST 5p. DATA SHEETS 5p. TRADE ENQUIRIES WELCOME



THE RADIO AMATEUR OPERATOR'S HANDBOOK

12 TH EDITION— FULLY REVISED

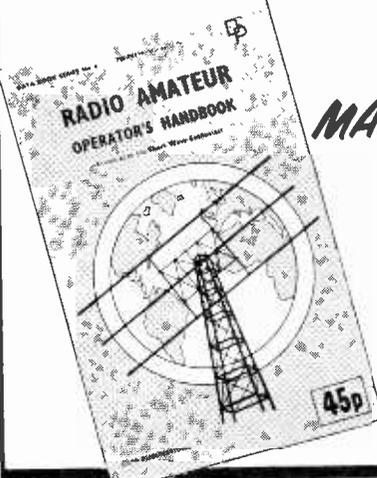

MAKE SURE OF YOUR COPY NOW!

80 PAGES ONLY 45p P. & P. 6p

Post this coupon, together with P.O. for 51p (to include postage) to DATA PUBLICATIONS, 57 MAIDA VALE, LONDON, W9 1SN

- ★ AMATEUR PREFIXES
- ★ AMATEUR CODES
- ★ LOCAL TIME CONVERSIONS
- ★ 8 MAPS
- ★ FREQUENCY/WAVELENGTH CONVERSION TABLES
- ★ POST OFFICE REGULATIONS
- MANY OTHER ESSENTIAL ITEMS

Please send me the New Edition of "THE RADIO AMATEUR OPERATOR'S HANDBOOK" DATA BOOK No. 6

I enclose cheque/crossed postal order for

NAME

ADDRESS

BLOCK LETTERS PLEASE

SMALL ADVERTISEMENTS

Rate: 4p (9d) per word. Minimum charge 60p (12/-),
Box No. 10p (2/-) extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W9 1SN)

NEW CATALOGUE NO. 18, containing credit vouchers value 50p, now available. Manufacturers new and surplus electronic and mechanical components, price 23p post free. Arthur Sallis Radio Control Ltd., 28 Gardner Street, Brighton, Sussex.

MECCANO FOR "CYCLOPS" - Special Pack of all Meccano parts required - £2.98 including postage. Send off today to *The Meccano Spare Parts Specialists* and start building! "Everything Meccano" at M. W. MODELS, 165 Reading Road, Henley-on-Thames, Oxon. Telephone 3342.

RECORD TV SOUND using our loudspeaker isolating transformer. Provides safe connection to recorder. Instructions included. £1 post free. Crowborough Electronics (R.C.), Eridge Road, Crowborough, Sussex.

SERVICE SHEETS (1925-1972) for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., by return post, with free Fault-Finding Guide. Prices from 5p. Over 8,000 models available. Catalogue 13p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 54 London Road, Bexhill, Sussex. Telephone: Bexhill 7097.

CHROMASONIC ELECTRONICS is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p. post free.

FOR SALE: VHF KIT, 80 - 180 MHz. Receiver, tuner, converter. World wide sales. Incomparable. £4.00 or s.a.e. for literature. Johnsons (Radio C), Worcester WR1 2DT.

FOR SALE: Cossor transistorised portable, LW, MW and VHF. Black leather. 6½ x 4 x 2in. £5. Box No. G179.

BUILD IT in a DEWBOX robust quality plastic cabinet 2 in. x 2½ in. x any length. S.A.E. for details. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. Write now - right now.

"GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK". Contains circuits, data, illustrations and valuable information for British/USA receivers, trans/receivers. Includes modifications to sets and test equipment. Price £2.85, p.p. 15p. Wanted all types of communications receivers and test equipment. Top Prices paid. What have you? Gerald Myers (RC), 18 Shaftesbury Street, Leeds LS12 3BT.

MEDICAL FORCEPS. Stainless steel 5 in. Ratchet locking. A real friend in the radio workshop. 55p. inc. postage. Send cash or cheque with order to: B. Mitchinson, 4 Fraser Close, Bexley, Kent.

STAMP COLLECTION for sale. Catalogue value £150. Offers? Box No. G180.

TUITION GIVEN in practical maths for Telecomms., and ordinary level maths. Telephone: 01-385-5288 evenings.

FOR SALE: Turmix Swiss kitchen mixer, with liquidiser and 3 sets stirring attachments. 240V, 50Hz. Full working order. £8. Box No. G182.

(Continued on page 763)

BENTLEY ACOUSTIC CORPORATION LTD.

38 Chalcot Road, Chalk Farm
LONDON, N.W.1.
01-722-9090

The Old Police Station
Gloucester Road
LITTLEHAMPTON Sussex
PHONE 6743

Please forward all mail orders to Littlehampton

OA2 .30	I2BE6 .30	ERC41 .48	EM81 .37	PL83 .30	UY41 .38
OB2 .30	I2BH7A	EB81 .29	EM83 .75	PL84 .28	UY85 .23
5U4G .30	I2K5 .27	EBF80 .30	EM84 .31	PL504 .60	X41 .50
5Y4C .33	I2K5 .50	EBF83 .38	EM87 .34	PL508 .90	AD165 .25
5Y4GT .25	19A05 .24	EBF89 .26	EM89 .34	PL509 .30	AD166 .36
5Z4G .33	20P4 .89	EC92 .34	EY81 .35	PL802 .75	AD149 .50
6/30L2 .53	30C15 .55	ECC31.50	EY83 .54	PX4 1.16	AD161 .45
6AQ5 .21	30C17 .74	ECC81 .16	EY876 .27	PY33/2 .50	AD162 .45
6AT6 .18	30C18 .58	ECC82 .19	EY88 .40	PY81 .24	AF114 .25
6AU6 .19	30F5 .61	ECC83 .21	EZ40 .40	PY82 .23	AF115 .15
6AV6 .28	30FL1 .58	ECC84 .28	EZ80 .19	PY83 .26	AF121 .30
6BA6 .19	30FL2 .58	ECC85 .32	EZ81 .20	PY88 .31	AF126 .18
6BE6 .20	30FL14 .66	ECC88 .35	EY501 .75	PY500 .95	BF107 .13
6BF6 .43	30L15 .55	ECF89 .27	EY51 .47	PY800 .31	BC108 .13
6B16 .39	30L17 .65	LCF82 .25	HVR2 .53	PY801 .31	BC113 .25
6BR7 .79	30P12 .69	ECF86 .64	KTW61 .63	QQV03/	BC118 .23
6BW6 .72	30P19 .55	ECH42 .57	KTW62 .63	10 1.20	BC211 .38
6BW7 .50	30PL1 .57	ECH81 .25	KTW63 .50	R19 .28	BF159 .25
6BZ6 .31	30PL13 .75	ECH83 .38	KT66 .80	U19 1.73	BF163 .20
6C4 .28	30PL14 .62	ECH84 .34	PC86 .44	U25 .62	BF180 .30
6C6U5 .30	30PL15 .87	ECL80 .28	PC88 .44	U26 .53	BY100 .18
6E16 .59	3516GT .42	ECL82 .28	PCF89 .46	U91 .35	BY126 .15
6F18 .45	38V4 .23	ECL83 .52	PC900 .29	U251 .62	BY127 .18
6F23 .65	35Z4 .24	ECL84 .54	PC884 .27	U301 .40	OA81 .79
6F28 .60	35Z5 .30	ECL86 .33	PC888 .39	U801 .76	OA91 .09
6HG6T .15	50L6GT .45	EF22 .63	PC889 .42	UABC80	OA95 .09
6K7G .10	DAF91 .20	EF41 .58	PCF89 .46	PCF81 .30	OC23 .38
6K8G .16	DAF96 .33	EF80 .21	PCF80 .26	UBC81 .40	OC24 .38
6L6GT .39	DF91 .14	EF83 .54	PCF82 .30	UBF80 .28	OC25 .38
6Q7GT .43	DF96 .34	FF85 .25	PCF84 .40	UBF89 .28	OC35 .32
6R16 .59	DM91 .26	FF86 .27	PCF86 .46	UCF82 .57	OC71 .11
6V6G .17	DK92 .15	FF89 .23	PCF801 .28	UCF84 .33	OC85 .11
6X4 .20	DK96 .35	FF91 .17	PCF802 .37	UCF83 .33	OC86 .15
7Y4 .60	DL92 .23	FF92 .28	PCF806 .55	UCF80 .31	OC70 .13
9A2V .78	DL94 .22	FF183 .25	PCL82 .70	UCH42 .57	OC71 .11
10F1 .75	DL96 .35	FF184 .27	PCL83 .54	UCH81 .59	OC71 .11
10F18 .35	DY87/6 .32	EH90 .34	PCL84 .32	UCH82 .30	OC74 .23
12A6 .63	DY802 .29	EL34 .44	PCL805 .37	UCL83 .48	OC75 .11
12AC6 .40	E88CC .60	EL41 .53	PL186 .36	UF41 .50	OC75 .15
12AD6 .40	E180F .90	EL42 .53	PD501 .44	UF80 .35	OC78 .15
12AE6 .48	EABC80	EL84 .21	PEN45 .40	UF85 .34	OC81 .11
12AT6 .23		EL91 .23	PFL200 .50	UF86 .63	OC81D .11
12AU6 .21	EAF42 .48	EL95 .32	PL36 .46	UF89 .27	OC82 .11
12AV6 .28	EB34 .20	EL180 .75	PL81 .42	UL41 .50	OC83 .20
12BA6 .30	EB91 .10	EM80 .37	PL82 .28	UL84 .28	OC84 .24

All goods are unused and boxed, and subject to the standard 90-day guarantee. Terms of business: Cash or cheque with order only. No C.O.D. orders accepted. Post/packing charge 3p per item subject to a minimum of 9p per order. Orders over £5 post free. All orders despatched same day by first class mail. Complete catalogue with conditions of sale 7p post paid. Any parcel insured against damage in transit for only 3p extra per order. Business hours 9 a.m.-5.30 p.m. Sats. 9 a.m.-1 p.m. Littlehampton closed Sats. No enquiries answered unless S.A.E. enclosed for reply.

FREE TO AMBITIOUS ENGINEERS

- THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

SEND FOR YOUR FREE COPY TO-DAY

NEW OPPORTUNITIES is a highly informative 76 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern Home Study Courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics Courses administered by our Specialist Electronics Training Division - explains the benefits of our free Appointments and Advisory service and shows you how to qualify for five years promotion in one year.

PRACTICAL EQUIPMENT INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with all the practical equipment you need, plus Basic Practice and Theoretical Courses for beginners in Radio, TV, Electronics, etc.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. (B10), Aldermaston Court, Reading RG7 4PF

SEND OFF THIS COUPON TO-DAY!

Tick subjects that interest you:

AMSE (Elec) City & Guilds Certificate RTEB Certificate
 Radio Amateurs' Exam DMG Certificate Colour TV
 Electronic Engineering Computer Electronics Radio and TV
 Servicing Practical Electronics Practical TV and Radio
Please send booklets & full information without cost or obligation.

NAME..... AGE.....
(BLOCK CAPITALS PLEASE)
ADDRESS.....
.....
.....
OCCUPATION.....

To: BIET Dept. B10, Aldermaston Court, Reading RG7 4PF
Accredited by the Council for the Accreditation
of Correspondence Colleges

RADIO OPERATORS

DO YOU HAVE

PMG I
PMG II
MPT
2 YEARS' OPERATING EXPERIENCE

?

POSSESSION OF ONE OF THESE QUALIFIES YOU FOR CONSIDERATION FOR A RADIO OFFICER POST WITH THE COMPOSITE SIGNALS ORGANISATION

On satisfactory completion of a 7 months specialist training course, successful applicants are paid on scale rising to £2365 pa; commencing salary according to age - 25 years and over £1664 pa. During training salary also by age, 25 and over £1238 pa with free accommodation.

The future holds good opportunities for established (i.e. pensionable) status, service overseas and promotion.

Training courses commence every January, April and September. Earliest possible application advised.

Applications only from British-born Male and Female UK residents up to 35 years of age (40 years if exceptionally well qualified) will be considered.

Full details from:

**Recruitment Officer,
Government Communications
Headquarters,**

**Room A/1105,
Oakley Priors Road,
CHELTENHAM,
Glos., GL52 5AJ.**


Tel: Cheltenham 21491. Ext. 2270.

NEW STYLE SELF-BINDER

for "The Radio Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

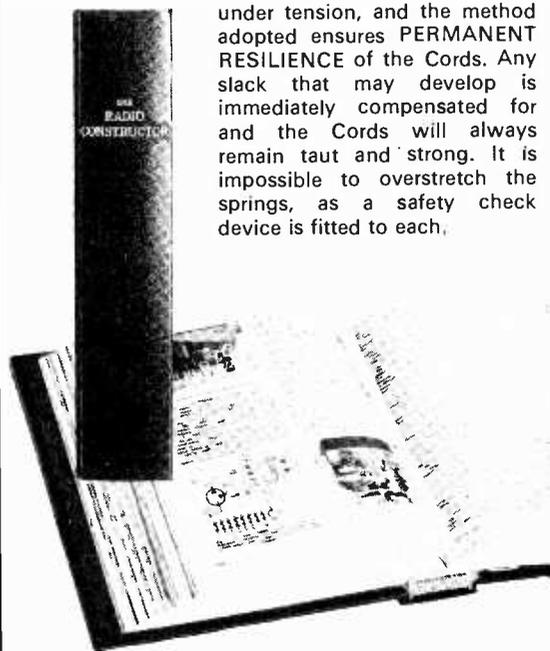

PRICE **75p** P. & P. 14p

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 ISN

SMALL ADVERTISEMENTS

(Continued from page 761)

'SHORTWAVE VOICES OF THE WORLD', £1.55; an exceptional book. *World Radio TV Handbook*, £2.80. *How To Listen to the World*, £1.35. Under £2 postage 10p worldwide. I.R.C./3p for price list. (Mail only). David McGarva, Box 114B, Head Post Office, Edinburgh, EH1 1HP. Closed June 20th - July 3rd.

FOR SALE: Ultraviolet light viewing cabinet. Suitable for stamp collectors for phosphor detecting. £3. Box No. G181.

MINI MAINS PACK KIT. Safe double-wound mini transformer, silicon rectifiers, 1000µF smoothing, instructions. Buildable to size of PP6 etc. 9V, 120mA. 90p, U.K. post 5p. Mail order only. AMATRONIX LTD., 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

MOSLEY DIPLOMAT 2, 2 metre 5/8 wave omnidirectional ground plane antenna. £3. Box No. G183.

"**MEDIUM WAVE NEWS**" Monthly during Dx season - Details from: K. Brownless, 7 The Avenue, Clifton, York.

BOOKS TO CLEAR: *Science Survey 3*, Vista Books, 50p. *Disease and its Conquest*, 25p. *Ski-ing for Beginners*, 25p. *Moscow, A Short Guide*, 30p. *Thyratrons*, Philips Tech. Lib., 20p. *The Colour of Canada*, 50p. Box No. G184.

FOR SALE: D.C., A.F., I.F. or R.F. amplifiers 50p (gain 3,600T, 3,600T, 24dB, 24dB respectively), size 1 cm. x 1 cm. x 1/2 cm., f - 200MHz max. IC12 £2.00; SN72741 40p; 2N706, 2N3702, 2N2926, 2N2501, 2N2412, all 5p each. All items 5p P. & P. M. Watterson, 28 Beltoy Road, Kilroot, County Antrim, N. Ireland.

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £2.00 per annum. (U.K. and British Commonwealth), overseas 6 Dollars or £2.50. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

ARE YOU A MOTORING ENTHUSIAST? The Seventy-Fifty Motor Club caters for all types of motor sport-racing, rallies, hill climbs, etc. Monthly Bulletin free to members. For full details write to: The General Secretary, Colin Peck, "Dancers' End", St. Winifred's Road, Biggin Hill, Kent.

MARINE TYPE SPEAKER, 7in. circular metal case, £1.50. Tannoy p/a type weather-proofed microphone, £1. Marine freq. xtals, 2009, 2306, 2381kHz 3in. pin spacing, £1. Box No. G185.

DUPLICATING FOR TRADE, Club newsletters, bulletins. Quick Service. S.A.E. with enquiries. G8FNJ Duplicating, 20 The Crescent, Stowmarket, Suffolk.

1920's BROWNIE CRYSTAL SET, loading coil, horn loudspeaker. Exchange for kit type Lissen or Eddystone receiver. Box No. G186.

HOLIDAY ACCOMMODATION. Burwood Lodge Hotel, Dawlish Road, Teignmouth, South Devon. Especially suitable for parents with young children. Facing south, on the cliffs, direct access by private path to the sea. Mothers' kitchen, automatic washing machines, baby listening service. Licensed lounge. Ample free parking.

(Continued on page 764)

A fascinating foundation for your child's future...

In Radio & Electronics with



Radionic Construction Kits



**NO SOLDERING
BATTERY OPERATED**

A teenager will enjoy many exciting hours constructing experiments with his Radionic Kit.

Not only is it entertaining and absorbing but the knowledge gained of the principles of electronics is invaluable in helping with general studies for higher education. So simple and practical to use - and there is no soldering whatsoever.

You couldn't choose a better gift for any occasion - or why not just buy one anyway?

Radionic Products Limited

St Lawrence House, Broad Street,
Bristol BS1 2HF. Tel. 0272 26351.

Write to: Philips, Dept. 11, Post Office, Milton Keynes.

PHILIPS

Please send me literature on Radionic radio and electronics construction kits.

NAME _____


ADDRESS _____

R.C.

PLAIN-BACKED NEW STYLE SELF-BINDERS

for your other magazines

(max. format 7½" x 9½")

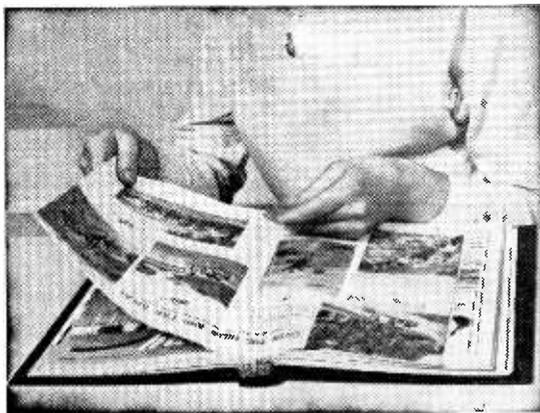

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE 70p P. & P. 14p

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 763.)

WORLD DX CLUB covers all aspects of SWLing on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.38 a year. Enquiries to Secretary, WDXC, 11 Wesley Grove, Portsmouth, Hants., PO3 5ER.

FOR SALE: *Wireless World* April 1964 to December 1971, *The Radio Constructor* June 1965 to December 1968. 8p per copy plus postage. Box No. G187.

FERRITE AERIALS. Litz wound M.W. 2½ x ¾ x ¼ in. with coupling coil, 30p. Miniature dynamic microphones, 2000Ω impedance, ¾ x ¾ x ¼ in., will also work as mini speakers, 45p post paid. Drew, 77 The Crescent, Southwick, Sussex.

FOR SALE: OSCILLOSCOPE, Ministry type CT52, miniature 2½ inch CRT. V.G.C. with handbook, £20. Marconi attenuator TF338 variable 0-100dB. V.G.C. £6. Offers, enquiries, S.A.E. Carriage extra. Box No. G188.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 1495.

FOR SALE: *Radio Constructor* June 1964 to December 1970. Offers? 33 Colne Road, Halstead, Essex.

FOR SALE: CODAR CR70A receiver and preselector. In excellent condition. Almost unused. Private sale. £20.00. Box No. G189.

ESSEX GARDENERS. Buy your bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

THE BRITISH AMATEUR ELECTRONICS CLUB. A club for all who are interested in electronics as a hobby. Quarterly Newsletter sent free to members. Subscription 50p per year. Details from Hon. Secretary, J. G. Margetts, 17 St. Francis Close, Abergavenny, Mon.

FOR SALE: Heathkit GC-1U communications receiver, £15. Harting tape deck, 3 heads, preamps, p.s.u., cabinet, £25. Hew Hansen transistor checker, £5. Portable valve tester, £5. New Audman Adroit F.M. front-end, silicon transistors, £4.50. Hi-Fi equipment cabinet, £5. Pye speaker, £2.50. Buyer collects (evenings). Hatch, 9 Glenwood Road, Hounslow, Middlesex.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:— The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

FOR SALE: A large number of *Radio Constructor*/*Practical Wireless*/*Practical Television*/*Wireless World* for disposal. Letters only in the first place. R. Hicks, 18 The Close, Dunmow, Essex.

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p, five sheets for 10p, postage 3p. Data Publications Ltd., 57 Maida Vale, London W9 1SN.

INDEX TO VOLUME TWENTY-FIVE

August 1971 - July 1972

AMPLIFIERS

A.F. Amplifier for Beginners, by <i>J. Hossack</i>	416	Feb. '72
Novel A.F. Amplifier, by <i>J. A. Brett</i>	330	Jan. '72
Second A.F. Input, by <i>S. L. Thomas</i>	540	Apr. '72
The 'F.E.T. Twin', by <i>Sir Douglas Hall, K.C.M.G., M.A. (Oxon)</i>	602	May '72

AMPLIFIER ANCILLARIES

Crystal Microphone Lead Extender, by <i>S. V. Jenkins</i>	679	June '72
High Impedance Transistor Pre-Amplifier, by <i>G. W. Short</i>	74	Sept. '71

ELECTRONICS

A.C./D.C. Mystery Bulb, by <i>A. L. Chivers</i>	30	Aug. '71
Alternative Multi-Voltage Circuit, by <i>B. E. Hawker</i>	22	Aug. '71
Automatic Thyristor Dimmer, by <i>G. D. Howat</i>	408	Feb. '72
Cyclops (Electronic Robot), Part 1, by <i>L. C. Galitz</i>	736	July '72
Electronic Egg-Timer, by <i>G. A. French</i>	720	July '72
GaAs Transistors in GHz Amplifiers, by <i>J. B. Dance, M.Sc.</i>	623	May '72
'Magic' Number Indicator, by <i>G. A. French</i>	467	Mar. '72
New Electrometer Device, MBH 1, by <i>M. J. Darby</i>	76	Sept. '71
Notes on Semiconductors, Further Notes 1, by <i>P. Williams</i>	273	Dec. '71
Notes on Semiconductors, Further Notes 2, by <i>P. Williams</i>	350	Jan. '72
Notes on Semiconductors, Further Notes 3, by <i>P. Williams</i>	405	Feb. '72
Notes on Semiconductors, Further Notes 4, by <i>P. Williams</i>	463	Mar. '72
Notes on Semiconductors, Further Notes 5, by <i>P. Williams</i>	532	Apr. '72
Notes on Semiconductors, Further Notes 6, by <i>P. Williams</i>	620	May '72
Notes on Semiconductors, Further Notes 7, by <i>P. Williams</i>	659	June '72
Notes on Semiconductors, Further Notes 8, by <i>P. Williams</i>	723	July '72
Solid-State "Relay", by <i>G. A. French</i>	151	Oct. '71
Sound Operated Camera Flash, by <i>M. G. Argent</i>	138	Oct. '71
The Surface Charge Transistor, by <i>J. B. Dance, M.Sc.</i>	88	Sept. '71
Thyristor Turn-off Methods, by <i>D. E. Vaughan</i>	682	June '72
Triggered Door Alarm, by <i>G. A. French</i>	210	Nov. '71
Versatile Successive Switch, by <i>G. A. French</i>	400	Feb. '72
"Vibratron" Vibrato Unit, by <i>R. J. Caborn</i>	288	Dec. '71

GENERAL

A Better Printed Circuit Resist, by <i>A. G. Blewett</i>	491	Mar. '72
A Table-Top Work Bench, by <i>A. C. Gee, G2UK</i>	730	July '72
Aerial Distribution Board, by <i>C. S. Johnson</i>	26	Aug. '71
An Enlarger Timer, by <i>B. E. Hunter</i>	244	Nov. '71
An Electrostatic Generator, by <i>D. P. Newton, B.Sc., Grad.Inst.P.</i>	12	Aug. '71
Automatic Morse Practice Keyer, by <i>A. G. Blewett</i>	84	Sept. '71
Binary Nim, by <i>G. A. French</i>	16	Aug. '71
Brake Light Failure Indicator, by <i>P. W. Hand</i>	78	Sept. '71
Communication & Electrolysis, by <i>D. P. Newton, B.Sc.</i>	169	Oct. '71
Coupling Capacitors Causes Complications, by <i>T. Burlman</i>	40	Aug. '71
D.C. Motor Controller, by <i>R. Wakeman</i>	488	Mar. '72
Dealing With High Tension Shorts, by <i>V. Capel</i>	475	Mar. '72
Diode Polarities, by <i>N. Stewart</i>	117	Sept. '71
Dodges with Diodes, by <i>P. T. Evans</i>	89	Sept. '71
Extracts from a Dotty Dictionary, by <i>B. H. Baily</i>	116	Sept. '71
Farad Electrolytic Capacitors, by <i>J. B. Dance, M.Sc.</i>	495	Mar. '72
Getting Started on Two Meters, by <i>A. C. Gee, G2UK</i>	86	Sept. '71
Half-a-Dozen Puzzlers, by <i>P. Manners</i>	539	Apr. '72
Half-a-Dozen Puzzlers (Answers), by <i>P. Manners</i>	568	Apr. '72
Home-Soldering Hint, by <i>R. L. Graper</i>	631	May '72
I.C. Intruder Alarm, by <i>Vincent S. Evans, G8EDM</i>	360	Jan. '72
Inexpensive Interphone, by <i>P. Bass</i>	656	June '72
Latin American Quest - 5	43	Aug. '71
Latin American Quest - 6	104	Sept. '71
Local Radio Transmitting Stations	214	Nov. '71
Mains Failure Indicator, by <i>G. A. French</i>	80	Sept. '71
Notes on Semiconductors - 6, by <i>P. R. Williams</i>	15	Aug. '71
Overload Trip Circuit, by <i>G. A. Miller and M. N. Pointing</i>	414	Feb. '72
Pilot Lamp Digital Display, by <i>G. A. French</i>	336	Jan. '72
1919 Radio Transmitter, by <i>F. Ashford</i>	490	Mar. '72
Removing Eliminator Hum, by <i>G. W. Short</i>	155	Oct. '71
Sensitivity Measurement of Portable Receivers, by <i>C. F. Dorey</i>	535	Apr. '72

Silicon Transistor Siren, by <i>J. Johnstone</i>	487	Mar. '72
Simplified Sequential Latching Circuit, by <i>M. G. Ashby</i>	108	Sept. '71
Subtraction Computing Circuit, by <i>D. Snaith</i>	537	Apr. '72
Transistor Stabilized Power Unit, Part 1, by <i>P. Cairns, M.I.P.R.E., G3ISP</i>	283	Dec. '71
Transistor Stabilized Power Unit, Part 2, by <i>P. Cairns, M.I.P.R.E., G3ISP</i>	345	Jan. '72
Winding Toroidal Coils, by <i>C. Dickson</i>	732	July '72

IN YOUR WORKSHOP

Aerials	689	June '72	Input and Output Impedances	431	Feb. '72
Aerial Mismatch	686	June '72	Latching Configuration	562	Apr. '72
A.F. Distortion	184	Oct. '71	Mains Transformer	180	Oct. '71
A.F. Output	375	Jan. '72	Mixer-Oscillator	433	Feb. '72
A.G.C. Circuit	46	Aug. '71	Operation With Coils	564	Apr. '72
A.M. Detector	505	Mar. '72	P.A. System	236	Nov. '71
A.M.-F.M. I.F. Stages	498	Mar. '72	Panel-Mounting Fuseholders	751	July '72
A.M. Valve Receiver	179	Oct. '71	Parallel Resistor	376	Jan. '72
Brass Eyelet Project	755	July '72	Polystyrene Tiles	754	July '72
Carbon Microphone	303	Dec. '71	Pool Alarm System	754	July '72
Capacitor Microphone	306	Dec. '71	Quadrature F.M. Detector	373	Jan. '72
Collector-Emitter Feedback	435	Feb. '72	Radio 2 Tuner	624	May '72
Contact Bounce	565	Apr. '72	Ratio Discriminator	502	Mar. '72
Contact Ratings	562	Apr. '72	Reference Voltage	437	Feb. '72
Crystal Microphone	237	Nov. '71	Ribbon Microphone	241	Nov. '71
Dry Reed Switch	560	Apr. '72	Rocking-Armature Microphone	304	Dec. '71
Dual-Standard TV	371	Jan. '72	Shunt Stabilizer	752	July '72
Earlier Symbols	114	Sept. '71	Sound Cell Microphone	240	Nov. '71
Electret Microphone	309	Dec. '71	Short Wave Aerials	691	June '72
Ferrite Aerial	627	May '72	Standing Waves	688	June '72
F.E.T. Head Amplifier	307	Dec. '71	Thermal Characteristics	110	Sept. '71
F.M. Front Ends	430	Feb. '72	Thermal Ohm's Law	111	Sept. '71
F.M. Overload Diode	499	Mar. '72	Transmission Line	687	June '72
Forward A.G.C.	46	Aug. '71	Trimming Tool	750	July '72
I.F. Instability	181	Oct. '71	Tuner A.G.C.	46	Aug. '71
Indoor TV Aerial	754	July '72	Tuner Construction	625	May '72

RECEIVERS

A Modern Homodyne Receiver, Part 1, by <i>G. W. Short</i>	492	Mar. '72
A Modern Homodyne Receiver, Part 2, by <i>G. W. Short</i>	552	Apr. '72
Bedside Reflex Receiver, by <i>A. Sapciyan</i>	714	July '72
Coil-Pack Communications Receiver, Part 1, by <i>F. G. Rayer, A.I.E.R.E., G30GR</i>	160	Oct. '71
Coil-Pack Communications Receiver, Part 2, by <i>F. G. Rayer, A.I.E.R.E., G30GR</i>	230	Nov. '71
D.R.C.3. Bandsread Short Wave Receiver, by <i>Sir Douglas Hall, K.C.M.G., M.A. (Oxon)</i>	665	June '72
"Easy" 2 Metre Receiver, by <i>F. G. Rayer, A.I.E.R.E.</i>	480	Mar. '72
Mark II Modification for the "Spontaflex" F.M. Receiver, by <i>Sir Douglas Hall, K.C.M.G., M.A. (Oxon)</i>	426	Feb. '72
F.E.T. Reflex Receiver, by <i>A. W. Whittington</i>	10	Aug. '71
Medium and Short Wave Reflex Receiver, by <i>A. Sapciyan</i>	292	Dec. '71
Parallel-T-Radio 2 Tuner, by <i>G. A. French</i>	276	Dec. '71
The Bandmaster, by <i>J. B. Willmot, A.I.P.R.E.</i>	32	Aug. '71
The "Bass-Boost" Portable, by <i>Sir Douglas Hall, K.C.M.G., M.A. (Oxon)</i>	522	Apr. '72
The "Doublet" Domestic Test Receiver, by <i>J. Hossack</i>	266	Dec. '71
The "Droitwich" Car Radio, by <i>Sir Douglas Hall, K.C.M.G., M.A. (Oxon)</i>	216	Nov. '71
The "Miniflex" Mark IV Portable Receiver, by <i>Sir Douglas Hall, K.C.M.G., M.A. (Oxon)</i>	172	Oct. '71
TR-2 Reflex Receiver, by <i>A. Sapciyan</i>	438	Feb. '72
2 Transistor M.W. Receiver, by <i>R. A. Penfold</i>	608	May '72

RECEIVER ANCILLARIES

Adding Regeneration, by <i>S. G. Wood, G5UJ</i>	212	Nov. '71
Audio Filter for C.W., by <i>R. A. Penfold</i>	716	July '72
Automatic Signal Generator, by <i>R. A. Butterworth, G8BI</i>	622	May '72
Digital Frequency Monitor, Part 1, by <i>S. A. Money, M.B.C.S., G3FZX</i>	672	June '72
Digital Frequency Monitor, Part 2, by <i>S. A. Money, M.B.C.S., G3FZX</i>	742	July '72
Pre-Selector Amplifier, by <i>F. G. Rayer, A.I.E.R.E., G30GR</i>	394	Feb. '72
The "Europaveter" 49-Metre Band Converter, by <i>D. Walsh</i>	300	Dec. '71
Transistor Crystal Marker Unit, by <i>P. Cairns, M.I.P.R.E., R.Tech.Eng., G3ISP</i>	458	Mar. '72
V.H.F. Wavemeter, by <i>F. G. Rayer, A.I.E.R.E., G30GR</i>	542	Apr. '72

TAPE RECORDING

Automatic Morse Practice Keyer, by <i>A. G. Blewett</i>	84	Sept. '71
---	----	-----------

TV

Balanced Distribution Boxes, by <i>L. Simpson</i>	734	July '72
---	-----	----------

TEST EQUIPMENT

Audible Continuity Tester, by <i>C. Dickson</i>	280	Dec. '71
Audio Frequency Meter, Part 1, by <i>J. T. Neill</i>	224	Nov. '71
Audio Frequency Meter, Part 2, by <i>J. T. Neill</i>	296	Dec. '71

Bench Current Monitor, by D. L. Simpson	232	Nov. '71
D.C. Voltmeter, by A. Russell	469	Mar. '72
Diode and Transistor Testers, by D. Salmon	29	Aug. '71
Direct-Reading Capacitance Meter, by G. A. French	661	June '72
Direct Voltage Calibrator, by J. K. Owen	650	June '72
General Purpose Transistor Signal Generator, by R. A. Penfold	202	Nov. '71
Meterless Beta Tester, by G. W. Short	92	Sept. '71
Multivibrator Capacitance Bridge, by G. A. French	596	May '72
Novel Alignment Aid, by G. A. French	533	Apr. '72
Semiconductor Gate-Dip Oscillator, by A. S. Carpenter, G3TYJ	96	Sept. '71
The "Doublet" Domestic Test Receiver, by J. Hossack	266	Dec. '71
The Transmatch, by H. T. Kitchen	20	Aug. '71
Transistor Tester, by A. G. Blewett	352	Jan. '72
Using the U.J.T., by M. Harding	725	July '72
Wide Range Linear Sawtooth Generator, Part 1, by D. Aldous, M.S.E.R.T.	544	Apr. '72
Wide Range Linear Sawtooth Generator, Part 2, by D. Aldous, M.S.E.R.T.	613	May '72
Wide Range Linear Sawtooth Generator, Part 3, by D. Aldous, M.S.E.R.T.	694	June '72
Wide Range Low Frequency Signal Generator, by P. Cairns, M.I.P.R.E., R.Tech.Eng., G3ISP	144	Oct. '71

TRANSMITTING

Small Transmitter for Two Metres, by A. S. Carpenter, G3TYJ	586	May '72
---	-----	---------

RADIO TOPICS

55 Aug. '71	119 Sept. '71	247 Nov. '71
310 Dec. '71	377 Jan. '72	440 Feb. '72
567 Apr. '72	632 May '72	696 June '72
758 July '72		

CAN ANYONE HELP?

79 Sept. '71	207 Nov. '71	528 Apr. '72
--------------	--------------	--------------

NEWS AND COMMENT

24 Aug. '71	82 Sept. '71	142 Oct. '71
208 Nov. '71	274 Dec. '71	334 Jan. '72
406 Feb. '72	464 Mar. '72	530 Apr. '72
594 May '72	654 June '72	718 July '72

QSX

91 Sept. '71	213 Nov. '71	349 Jan. '72
466 Mar. '72	607 May '72	729 July '72

NOW HEAR THESE

28 Aug. '71	95 Sept. '71	159 Oct. '71
223 Nov. '71	287 Dec. '71	

CURRENT SCHEDULES

39 Aug. '71	109 Sept. '71	171 Oct. '71
234 Nov. '71	295 Dec. '71	

SHORT WAVE NEWS

369 Jan. '71	423 Feb. '72	496 Mar. '72
558 Apr. '72	618 May '72	684 June '72
748 July '72		

RECENT PUBLICATIONS AND BOOK REVIEWS

54 Aug. '71	77 Sept. '71	154 Oct. '71
351 Jan. '72	399 Feb. '72	529 Apr. '72
658 June '72	747 July '72	

NEW PRODUCTS

107 Sept. '71	158 Oct. '71	235 Nov. '71
299 Dec. '71	333 Jan. '72	621 May '72
681 June '72		

TRADE NEWS

14 Aug. '71	118 Sept. '71	243 Nov. '71
279 Dec. '71	344 Jan. '72	425 Feb. '72
479 Mar. '72	536 Apr. '72	601 May '72
660 June '72	724 July '72	

RADIO CONSTRUCTORS DATA SHEET

No. 53 Time Frequency Table	iii	Aug. '71
No. 54 Potentiometer Track Currents	iii	Sept. '71
No. 55 Foreign Language Broadcasts	iii	Oct. '71
No. 56 Foreign Language Broadcasts	iii	Nov. '71
No. 57 Foreign Language Broadcasts	iii	Dec. '71
No. 58 Inch-Millimetre Table I	iii	Jan. '72
No. 59 Inch-Millimetre Table II	iii	Feb. '72
No. 60 Millimetre-Inch Table I	iii	Mar. '72
No. 61 Millimetre-Inch Table II	iii	Apr. '72
No. 62 Preferred Resistor Values	iii	May '72
No. 63 Copper Wire Data I	iii	June '72
No. 64 Copper Wire Data II	iii	July '72

Copper Wire Data II

Completing the Copper Wire Data series, the Table gives simplified data for wires from 25 to 39 s.w.g. The diameters given for enamelled wire are the mean of upper and lower tolerances for synthetic enamel 'M'. The minimum turns/in. figures are estimated, to the nearest quarter turn. All other values are nominal. The current figures are based on 1,000 amps per sq. in. (This augments Data Sheet 18, published December 1968).

S.W.G.	Diameter plain (in.)	Diameter plain (mm.)	Diameter enamelled (in.)	Min. turns/in. enamelled	Min. turns/in. enamelled s.r.c.	Resistance per 1,000 yds. at 20° C (ohms)	Current rating (amps)
25	0.020	0.5080	0.0223	44	42.5	77.78	0.3142
26	0.018	0.4572	0.0201	48.25	46.75	96.03	0.2545
27	0.0164	0.4166	0.0184	52.5	50.75	115.68	0.2112
28	0.0148	0.3759	0.0167	58.5	56.5	142.05	0.1720
29	0.0136	0.3454	0.0155	63	61	168.22	0.1453
30	0.0124	0.3150	0.0142	68.5	66.25	202.4	0.1208
31	0.0116	0.2946	0.0133	73.0	70.5	231.2	0.1057
32	0.0108	0.2743	0.0125	77.5	74.5	266.7	0.0916
33	0.0100	0.2540	0.0116	83.25	79.5	311.1	0.0785
34	0.0092	0.2337	0.0107	90	86	367.6	0.0665
35	0.0084	0.2134	0.0099	98	93.5	441.0	0.0554
36	0.0076	0.1930	0.0090	107.5	101	538.7	0.0454
37	0.0068	0.1727	0.0081	119	110	672.9	0.0363
38	0.0060	0.1524	0.0071	135	123.5	864.3	0.0283
39	0.0052	0.1321	0.0063	151.5	137	1,150.7	0.0212

HENRY'S RADIO LIMITED

ENGLAND'S LEADING ELECTRONIC CENTRES



HI-FI · ELECTRONIC COMPONENTS · TEST · P.A. · DISCOTHEQUE · LIGHTING · MAIL ORDER

BUILD THE TEXAN

20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER

FREE TEAK CABINET with complete kits
(As featured in "Practical Wireless" May to August 1972)

FEATURES New slim design with 6 - IC's, IC sockets, 10 silicon transistors, 4 rectifiers, 2 zenars. Special Gardener's low field slim line transformer. Fibre glass PC panel. Complete chassis work. HIGH QUALITY AND STABILITY ARE PROMINANT FEATURES - DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION.

FACILITIES On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector, Mag. P.U., Radio Tuner, Aux. Can be altered for Mic. Tape, Tape head etc.
(Parts list Ref. 20 on request)
Design approved kits only available from Henry's



SPECIAL KIT PRICE

£28.50 P&P 45p

(Complete with FREE TEAK CABINET)

SLIM DESIGN WITH SILVER TRIM.

Overall chassis size 14½" x 6" x 2" high

RECORD DECKS CHASSIS (Post 50p)		
SP25/3	£10.75	HT70 £15.00
MP60	£10.40	MP610 £14.15
AP78	£18.95	CL72 £22.25
WITH PLINTH/COVER (Post 70p)		
MP60	£17.20	T0150AB £41.46
HT70	£21.60	PL12AC £35.25
HL(GL75)	£35.25	BD2 £32.25
MP610	£20.35	
CART/PLINTH/COVER (Post 70p)		
(HL) AP78/G800/PC		£29.95
(HL) SP25-3/G800H/PC		£18.95
HT70/G800/PC		£27.00
(HL) 2025TC/9TAHCD/PC		£13.50
MP60/SC5MD/PC		£17.25
(HL) GL75/G800E/PC		£44.15
(HL) GL72/G800/PC		£34.50

ULTRASONIC TRANSDUCERS

Operate at 40kc/s up to 100 yds. Ideal remote switching and signalling. Complete with data and circuits.
PRICE PER PAIR £5.90 Post 10p

LOW COST HI-FI SPEAKERS

E.M.I. Size 13½" x 8½" Large Ceramic Magnet.

TYPE 150 6 watt, 3, 8 or 15 ohms £2.20. Post 22p.
TYPE 150TC Twin cone version £2.75. Post 22p.
TYPE 450 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms. £3.85. Post 25p.
TYPE 350 20 watt with tweeter and crossover, 8 and 15 ohms. £7.70. Post 28p.



POLISHED CABINETS For 150, 150TC and 450 £4.60. Post 30p.



NEW MW/LW TUNER TO BUILD ML-3

Uses Mullard Module. Slow motion tuning.


Built in battery. Ferrite aerial. Overall size 7" x 2½" x 3½".
TOTAL COST TO BUILD £4.85 Post 15p. All parts sold separately - Leaflet No. 6

"BANDSPREAD" PORTABLE TO BUILD



Printed circuit all transistor design using Mullard RF77 Module. Medium and Long Wave Bands plus Medium Wave Bandsread for extra selectivity. Also slow-motion geared tuning. 600mW push-pull output. Fibre glass PVC covered cabinet. Car aerial socket. Attractive appearance and performance. **TOTAL COST TO BUILD £7.98** p.p. 32p. (Battery 22p).

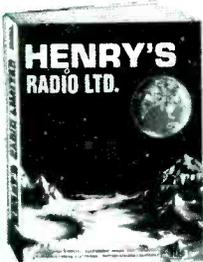All parts sold separately - Leaflet No. 2
"77" M & LW PORTABLE (as previously advertised) **£6.98** p.p. 35p. From stock (Leaflet No. 1).



CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics - plus data, circuits and information.

10,000 Stock lines at Special Low Prices and Fully Guaranteed.

PRICE **55p** Post Paid (40p FOR CALLERS)

PLUS FIVE 10p VOUCHERS

Send to this address - Henry's Radio Ltd. (Dept. RC), 3 Albemarle Way, London, E.C.1 - for catalogue by post only. All other mail and callers to "303", see below

TEST EQUIPMENT

SE250B	Pocket Pencil Signal Injector	£1.90
SE500	Pocket Pencil Signal Tracer	£1.50
TE15	Grid Dip Meter 440 KHz - 280 MHz	£13.45
500	30 K/Volt Multimeter	£5.25
	With leather case	£10.50
200H	20K/Volt Multimeter	£4.20
	With case	£4.95
AF105	50K/Volt Multimeter	£5.50
	With case	£9.50
U4341	AC/DC Multimeter with transistor tester with steel case	£10.50
TE20D	RF Generator 120KHz - 500MHz Carr 35p	£15.95
TE22D	Audio Generator 20Hz - 200KHz Carr 35p	£17.50
T03	3" Scope 1½Hz - 1½MHz Carr 50p	£39.00
CL 5	3" Pulse Scope 10Hz - 10MHz Carr 50p	£39.00
TE65	Valve Voltmeter 28 ranges Carr 40p	£17.50



BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BAND-WIDTH, PRINTED CIRCUIT, HIGH-FIDELITY REPRODUCTION, MONO AND STEREO. A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it - VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No. 3 & 7.

TOTAL £6.97, p.p. 20p. Decoder Kit **£9.97**.

Tuning meter unit **£1.75**
Mains unit (optional) Model PS900 **£2.47**, Post 20p.
Mains unit for Tuner and Decoder PS1200 **£2.62**, Post 20p.



PA-DISCO-LIGHTING

UK's Largest Range - Write phone or call in. Details and demonstrations on request.

DJ30L	3 Channel sound to light unit	3 Kw	£28.50
DJ40L	3 Channel Mic (built in) to light	3 Kw	£28.50
DJ70S	70 watt Disco amp/mixer		£37.50
DISCOAMP	100 watt Disco amp/mixer		£49.75
DJ105S	30 watt Disco amp/mixer		£67.50
Anti-Feedback Quality Mic			£31.00
SDL	12" 50 watt 8 ohm Full range Speaker		£11.50
DECKS	Use MP60 or SP25/3 see above.		£12.95
	Matching cartridge SC5M		£2.62



SINCLAIR PROJECT 60 MODULES

- SAVE POUNDS

.Z30	£3.57	Z50	£4.37
STEREO 60	£7.97	P25	£3.97
P26	£6.37	P28	£4.77
Transformer for P28	£2.95		
Active Filter Unit	£4.45		
Stereo FM Tuner	£16.95		
IC12	£1.80	Q16's	£1.5p
Post etc.	20p	per item	



PACKAGE DEALS Post 25p.

2 x Z30, Stereo 60, P25	£15.95
2 x Z30, Stereo 60, P26	£18.00
2 x Z50, Stereo 60, P28	£20.25
2 x Z50, Stereo 60, P28	£22.95
NEW PROJECT 605 KIT	£19.95

MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

All the parts you need plus Data and Circuits - Get a Catalogue - it's all in there!

Electronic Components, Audio and Test Gear Centre
404/406 EDGWARE RD., LONDON, W.2.
Tel: 01-402 8381/8382

High Fidelity & Tape Equipment Centre
354/356 EDGWARE RD., LONDON, W.2.
Tel: 01-402 4736/5854

Disco - PA - Lighting Equipment Centre
309 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 6963

Mail Order, Industrial Sales and Special Bargain Shop
303 EDGWARE ROAD, LONDON, W.2.
Tel: 01-723 1008/1009

"309", "354", "356", "404" & "406" OPEN SIX FULL DAYS A WEEK 9am to 6pm MONDAY TO SATURDAY