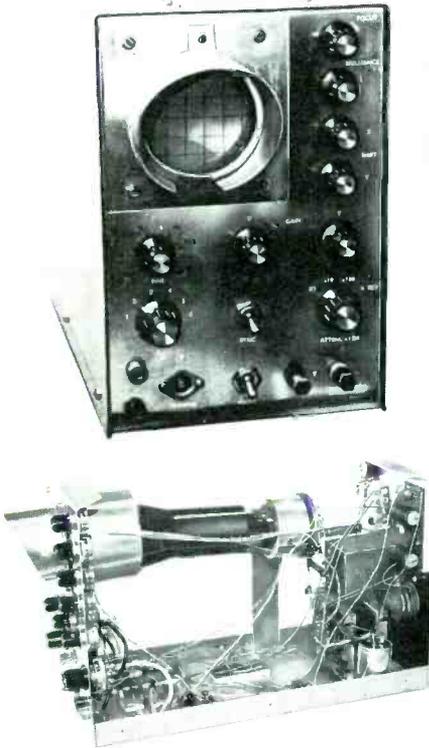


# RADIO & ELECTRONICS CONSTRUCTOR

Vol. 26 No. 5

DECEMBER 1972

20p



SPECIAL FEATURE

## TRANSISTORISED OSCILLOSCOPE

In this oscilloscope the only thermionic device is the cathode ray tube



**ALSO  
FEATURED**

**HIGH-GAIN SILICON  
REFLEX RECEIVER**



**Each £3 unit of Home Unit Insurance gives you protection up to the limit shown**

This is the simplified insurance you have been waiting for. Not just cover on the contents of your home but a package of personal protection you and your family need. And it's how we save you so much money: just ONE policy to issue instead of nine! You can build up to the cover you need by additional units

(or ½ units after the first) up to a maximum of five. So simple. So easy. Apply to your Broker, Agent or local office of a General Accident company. The Home Unit Policy can replace your existing insurances. And remember - as you buy more possessions just add more Home Units at any time.

**THE GENERAL ACCIDENT FIRE & LIFE ASSURANCE CORPORATION LTD**

Metropolitan House, 35 Victoria Avenue,  
Southend-on-Sea, Essex, SS2 6BT

It pays to be protected by a **General Accident** company

Please send me further particulars of the Home Unit Insurance.

Name.....

Address.....

20/9468

# THIS IS THE FIRST PAGE OF THE GREAT BI-PAK SECTION

## BRAND NEW FULLY GUARANTEED DEVICES

AC 107	20p AD 149	50p BC 143	30p BD 131	50p BF 179	30p C 444	35p 2G 301	2N 1613	20p 2N 2926(R)	10p 2N 3906	27p
AC 113	20p AD 161	30p BC 145	45p BD 132	60p BF 180	30p C 450	22p 2G 302	2N 1711	35p 2N 2926(B)	10p 2N 4058	12p
AC 115	23p AD 162	30p BC 147	10p BD 133	65p BF 181	30p MAT 100	19p 2G 303	2N 1889	32p 2N 3010	70p 2N 4059	10p
AC 117K	20p AD 161 and	BC 148	10p BD 135	40p BF 182	40p MAT 101	20p 2G 304	2N 1893	37p 2N 3011	14p 2N 4060	12p
AC 122	12p AD 162(MP)	55p BC 149	12p BD 136	40p BF 183	40p MAT 120	19p 2G 306	2N 2147	72p 2N 3054	44p 2N 4064	12p
AC 125	17p ADT 140	50p BC 150	18p BD 137	45p BF 184	25p MAT 121	20p 2G 308	2N 2148	50p 2N 3055	50p 2N 4284	17p
AC 126	17p AF 114	24p BC 151	20p BD 138	50p BF 185	30p MPF 102	42p 2G 309	2N 2160	60p 2N 3391	14p 2N 4285	17p
AC 127	17p AF 115	24p BC 152	17p BD 139	55p BF 188	40p MPF 104	37p 2G 339	2N 2192	35p 2N 3391A	16p 2N 4286	17p
AC 128	17p AF 116	24p BC 153	28p BD 140	60p BF 194	12p MPF 105	37p 2G 339A	2N 2221	20p 2N 3404	14p 2N 4287	17p
AC 132	14p AF 117	24p BC 154	30p BD 155	70p BF 258	14p OC 20	35p 2G 344	2N 2194	35p 2N 3395	14p 2N 4288	17p
AC 134	14p AF 118	35p BC 157	18p BD 175	60p BF 196	14p OC 22	42p 2G 345	2N 2218	20p 2N 3395	17p 2N 4290	17p
AC 137	14p AF 124	30p BC 158	12p BD 176	60p BF 197	14p OC 22	38p 2G 371	2N 2219	21p 2N 3402	21p 2N 4291	17p
AC 141	14p AF 125	25p BC 159	12p BD 177	65p BF 200	45p OC 23	42p 2G 371B	2N 2220	22p 2N 3403	21p 2N 4292	17p
AC 142	17p AF 126	28p BC 160	50p BD 178	65p BF 222	95p OC 24	56p 2G 373	2N 2221	20p 2N 3404	28p 2N 4293	17p
AC 143	14p AF 127	28p BC 161	50p BD 179	70p BF 257	45p OC 25	38p 2G 374	2N 2222	20p 2N 3405	17p 2N 4294	17p
AC 142K	17p AF 139	30p BC 167	13p BD 180	70p BF 258	80p OC 28	50p 2G 378	2N 2368	17p 2N 3414	15p 2N 4547	32p
AC 151	15p AF 178	50p BC 168	12p BD 185	65p BF 259	85p OC 28	50p 2G 378	2N 2369	14p 2N 3415	15p 2N 4548	32p
AC 154	20p AF 179	50p BC 169	12p BD 186	65p BF 262	55p OC 29	50p 2G 381	2N 2369A	14p 2N 3416	28p 2N 4549	40p
AC 155	20p AF 180	50p BC 170	12p BD 187	70p BF 263	55p OC 35	42p 2G 382	2N 2411	24p 2N 3417	28p 2N 301	50p
AC 156	20p AF 181	45p BC 171	14p BD 188	70p BF 270	35p OC 36	50p 2G 401	2N 2412	24p 2N 3525	75p 2N 302A	42p
AC 157	24p AF 186	45p BC 172	14p BD 189	75p BF 271	30p OC 41	20p 2G 414	2N 2646	47p 2N 1646	9p 2N 302	42p
AC 165	20p AF 239	37p BC 173	14p BD 190	70p BF 272	80p OC 42	20p 2G 414	2N 2711	21p 2N 1702	10p 2N 303	55p
AC 166	20p AL 102	65p BC 174	14p BD 195	85p BF 273	35p OC 44	15p 2N 388	2N 2712	21p 2N 1703	10p 2N 304	70p
AC 167	20p AL 103	65p BC 175	22p BD 196	85p BF 274	35p OC 45	12p 2N 388A	2N 2714	21p 2N 3704	11p 2N 305	84p
AC 168	24p ASY 26	25p BC 177	19p BD 197	90p BF 270	60p OC 70	10p 2N 404	20p 2N 3904	17p 2N 3705	10p 2N 306	84p
AC 169	14p ASY 27	30p BC 178	19p BD 198	90p BF X 29	27p OC 71	10p 2N 404A	2N 3904A	21p 2N 3706	9p 2N 307	84p
AC 176	20p ASY 28	25p BC 179	19p BD 199	95p BF X 84	30p OC 74	14p 2N 524	2N 3905	21p 2N 3707	11p 2N 321	56p
AC 177	24p ASY 29	25p BC 180	24p BD 200	95p BF 85	30p OC 74	14p 2N 524	2N 3905A	21p 2N 3708	7p 2N 322	42p
AC 178	28p ASY 50	25p BC 181	24p BD 205	80p BF X 86	22p OC 75	15p 2N 598	2N 2906	15p 2N 3709	9p 2N 322A	42p
AC 179	28p ASY 51	25p BC 182	10p BD 206	80p BF X 87	24p OC 76	15p 2N 599	2N 2906A	18p 2N 3710	9p 2N 323	56p
AC 180	17p ASY 52	25p BC 182L	10p BD 207	95p BF X 88	22p OC 77	25p 2N 696	2N 2907	20p 2N 3711	9p 2N 324	70p
AC 180K	20p ASY 54	25p BC 183	10p BD 208	95p BF X 89	20p OC 81	15p 2N 697	2N 2907A	22p 2N 3819	28p 2N 325	70p
AC 181	17p ASY 55	25p BC 184	10p BD 209	1.00 BF X 51	20p OC 81D	15p 2N 698	2N 2923	14p 2N 3820	50p 2N 326	70p
AC 181K	20p ASY 56	25p BC 184	12p BF 115	24p BF 52	20p OC 82	15p 2N 699	2N 2924	14p 2N 3821	35p 2N 327	70p
AC 187	22p ASY 57	25p BC 184L	12p BF 117	45p BF 53	17p OC 82D	15p 2N 706	2N 2925	14p 2N 3823	28p 2N 301	42p
AC 187K	20p ASY 58	25p BC 186	28p BF 118	70p BFX 25	85p OC 83	20p 2N 706A	2N 2926(G)	12p 2N 3903	28p 2N 40361	45p
AC 188	22p ASZ 21	40p BC 187	28p BF 119	70p BFX 19	15p OC 84	20p 2N 708	2N 2926(Y)	11p 2N 3904	30p 2N 40362	45p
AC 188K	20p ASZ 21	40p BC 187	28p BF 119	70p BFX 19	15p OC 84	20p 2N 708	2N 2926(Y)	11p 2N 3904	30p 2N 40362	45p
AC 189	25p BC 108	10p BC 207	11p BF 123	45p BSX 20	15p OC 139	20p 2N 711	30p 2N 2926(B)	10p 2N 3905	28p	
AC 17	25p BC 108	10p BC 207	11p BF 123	45p BSX 20	15p OC 139	20p 2N 711	30p 2N 2926(B)	10p 2N 3905	28p	
AC 18	20p BC 109	10p BC 209	12p BF 125	45p BSX 21	15p OC 169	25p 2N 718	50p AA 119	8p BY 130	16p OA 47	7p
AC 19	20p BC 113	10p BC 212L	11p BF 127	50p BSX 22	15p OC 170	25p 2N 718A	28p AA 120	8p BY 133	21p OA 70	7p
AC 20	20p BC 114	15p BC 213L	11p BF 152	55p BSX 28	15p OC 171	25p 2N 726	28p AA 129	8p BY 164	50p OA 79	7p
AC 21	20p BC 115	15p BC 214L	14p BF 153	45p BSX 29	15p OC 200	25p 2N 727	20p AA 130	7p BYX 38 30	42p OA 81	7p
AC 22	15p BF 116	25p BF 154	45p BSX 36	18p OC 201	28p 2N 744	20p AA 131	10p AAZ 13	35p OA 85	9p	
AC 27	18p BC 117	15p BC 226	35p BF 155	48p BSX 40	28p OC 203	25p 2N 914	14p BA 100	10p BYZ 11	30p OA 90	4p
AC 28	19p BC 118	10p BCY 30	24p BF 156	48p BSX 40	28p OC 203	25p 2N 914	14p BA 100	10p BYZ 11	30p OA 90	4p
AC 29	35p BC 119	30p BCY 31	24p BF 157	55p BSX 41	28p OC 204	25p 2N 918	30p BA 116	21p BYZ 12	30p OA 91	4p
AC 30	28p BC 120	80p BCY 32	30p BF 158	55p BSX 41	28p OC 205	35p 2N 929	21p BA 126	21p BYZ 13	25p OA 95	7p
AC 31	28p BC 125	12p BCY 33	22p BF 159	60p BSX 95A	12p OC 309	40p 2N 930	21p BA 148	14p BYZ 16	40p OA 200	6p
AC 34	21p BC 126	18p BCY 34	25p BF 160	40p Bu 105	42.00 346A	20p 2N 1131	20p BA 154	12p BYZ 17	35p OA 202	5p
AC 35	21p BC 132	17p BCY 34	14p BF 162	40p C 111E	50p P 357	43p 2N 1132	21p BA 155	14p BYZ 18	35p SD 10	5p
AC 36	28p BC 134	18p BCY 71	18p BF 163	40p C 400	30p OCP 71	43p 2N 1307	14p BA 156	13p BYZ 19	28p SD 19	5p
AC 40	17p BC 135	12p BCY 72	14p BF 164	40p C 407	25p ORP 12	43p 2N 1303	14p BF 100	15p CG 62	11p 34	7p
AC 41	18p BC 136	15p BCZ 10	20p BF 165	40p C 424	20p ORP 60	40p 2N 1304	17p BY 101	12p (Eq) OA 91	5p 1N 34A	4p
AC 42	35p BC 137	15p BCZ 11	25p BF 167	40p C 425	20p ORP 61	40p 2N 1305	17p BY 105	17p CG 651 (Eq)	11p 914	6p
AC 43	35p BC 139	40p BCZ 12	25p BF 173	40p C 426	35p ST 141	12p 2N 1306	21p BY 114	12p OA 70-OA79	6p 1N 916	6p
AD 140	48p BC 140	30p BD 121	60p BF 176	35p C 428	30p TIS 43	17p 2N 1307	21p BY 126	14p OA 55L	35p 1N 414B	6p
AD 142	48p BC 141	30p BD 123	65p BF 177	35p C 441	30p TIS 43	30p 2N 1308	21p BY 127	15p OA 55L	21p 1S 02B	10p
AD 143	38p BC 142	30p BD 124	60p BF 178	30p C 442	30p UT 46	27p 2N 1309	23p BY 128	15p OA 10	35p 1S 951	6p

## DIODES & RECTIFIERS

8p BY 130	16p OA 47	7p
8p BY 133	21p OA 70	7p
8p BY 164	50p OA 79	7p
7p BYX 38 30	42p OA 81	7p
35p OA 85	30p OA 85	9p
10p BYZ 11	30p OA 90	4p
21p BYZ 12	30p OA 91	4p
21p BYZ 13	25p OA 95	7p
14p BYZ 16	40p OA 200	6p
12p BYZ 17	35p OA 202	5p
35p SD 10	35p SD 10	5p
13p BYZ 19	28p SD 19	5p
15p CG 62	11p 34	7p
12p (Eq) OA 91	5p 1N 34A	4p
17p CG 651 (Eq)	11p 914	6p
12p OA 70-OA79	6p 1N 916	6p
14p OA 55L	35p 1N 414B	6p
15p OA 55L	21p 1S 02B	10p
15p OA 10	35p 1S 951	6p

Cut these 3 pages out and keep for reference

## NEW COMPONENT PAK BARGAINS

Pack No.	Qty.	Description	Price
C 1	250	Resistors mixed values approx. count by weight	0.50
C 2	200	Capacitors mixed values approx. count by weight	0.50
C 3	50	Precision Resistors .1%. .01% mixed values	0.50
C 4	75	1/4 W Resistors mixed preferred values	0.50
C 5	5	Pieces assorted Ferrite Rods	0.50
C 6	2	Tuning Gangs, MW/LW VHF	0.50
C 7	1	Pack Wire 50 meters assorted colours	0.50
C 8	10	Reed Switches	0.50
C 9	3	Micro Switches	0.50
C 10	15	Assorted Pots & Pre-Sets	0.50
C 11	5	Jack Sockets 3—3.5m 2 — Standard Switch Types	0.50
C 12	40	Paper Condensers preferred types mixed values	0.50
C 13	20	Electrolytics Trans. types	0.50
C 14	1	Pack assorted Hardware — Nuts/Bolts, Gromets, etc.	0.50
C 15	4	Mains Toggle Switches, 2 Amp D/P	0.50
C 16	20	Assorted Tag Strips & Panels	0.50
C 17	10	Assorted Control Knobs	0.50
C 18	4	Rotary Wave Change Switches	0.50
C 19	3	Relays 6 — 24V Operating	0.50
C 20	4	Sheets Copper Laminate approx. 10" x 7" 0.50	0.50

Please add 10p post and packing on all component packs, plus a further 10p on pack Nos. C1, C2, C19, C20. Component Lists for mail order available on request.

## JUMBO COMPONENT PAKS

MIXED ELECTRONIC COMPONENTS  
Exceptionally good value


Resistors, capacitors, pots, electrolytics and coils plus many other useful items. Approximately 3lbs in weight. Price incl. P. & P. £1.50 only

## BRAND NEW POST OFFICE TYPE TELEPHONE DIALS

ONLY 35p each
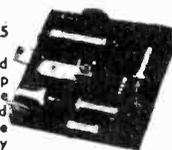
## THE NEW S.G.S. EA 1000 AUDIO AMP MODULE Guar. 3 Watts RMS. Module Tested and Guaranteed.

Qty. 1—9 £2.63; 10—25 £2.28. Price each. Larger quantities quoted on request. Full hook-up diagrams and complete technical data supplied free with each module or available separately at 10p each.



## SYSTEM 12 STEREO

Each kit contains two amplifier modules, 3 Watts RMS, two loudspeakers, 15 OHMS, The pre-amplifier, transformer, power supply module, front panel and other accessories as well as an illustrated stage-by-stage instruction booklet designed for the beginner. Further details available on request.

# The largest selection

## NEW LOW PRICE TEST S.C.R.'S.

PIV	1A	3A	5A	6A	7A	10A	16A	30A
706	T066	T066	T064	T048	T048	T048	T048	T048
50	0.33	0.25	0.35	0.35	0.47	0.50	0.53	1.15
100	0.35	0.33	0.47	0.47	0.50	0.58	0.63	1.40
200	0.35	0.37	0.49	0.49	0.57	0.61	0.75	1.60
400	0.43	0.47	0.56	0.56	0.67	0.75	0.93	1.75
800	0.53	0.57	0.68	0.68	0.77	0.97	1.15	—
800	0.63	0.70	0.80	0.80	0.90	1.10	1.50	2.00

## SILICON RECTIFIERS—TESTED

PIV	300mA	750mA	1A	1.5A	3A	10A	30A
	50	0.04	0.05	0.05	0.07	0.14	0.21
	100	0.04	0.06	0.06	0.13	0.16	0.23
	200	0.05	0.09	0.06	0.14	0.20	0.34
	400	0.06	0.13	0.07	0.20	0.27	0.37
	600	0.07	0.16	0.10	0.23	0.34	0.45
	800	0.10	0.17	0.11	0.23	0.37	0.55
	1000	0.11	0.25	0.14	0.30	0.46	0.63
	1200	—	0.33	—	0.38	0.57	0.75

TRIACS		
VBO	2A	10A
TO-1	TO-66	TO-88
	50	50
	100	30
	200	50
	400	70

FULL RANGE OF ZENER DIODES	
RANGE	5-33V
400mV (DO-7)	1W (Top-Hat) 18p ea. 10W (SO-16 Stud) 25p ea. All fully tested 5% tol. and rated. State voltage required.
50	RMS 32p each
100	RMS 37p each
400	RMS 46p each

**DIACS**  
FOR USE WITH TRIACS  
BR100 (D32) 87p each

10 amp POTTED BRIDGE RECTIFIER on heat sink  
100 PIV 90p each

**FREE**  
One 50p Pak of your own choice free with orders valued \$5 or over.

**NEW LINE**  
Plastic encapsulated 2 amp Bridge Rects.

**BRAND NEW TEXAS GERM. TRANSISTORS**  
Coded and Guaranteed  
Pak No. QVPT  
T1 8 234713 OCT1  
T2 8 11374 OCT5  
T3 8 11216 OCT8  
T4 8 23581T OCT8  
T5 8 21382T OCT8  
T6 8 21344B OCT4  
T7 8 21345B OCT4  
T8 8 21378 OCT8  
T9 8 21399A 2N1302  
T10 8 22417 AP117  
All 80p each pak

50 x RMS 32p each  
100 x RMS 37p each  
400 x RMS 46p each  
Size: 15mm x 6mm  
**JUNCTION**  
UT48 Evt. 2N2648, Evt. T1843, BEN3000  
87p each, 25-99 25p  
100 UP 20p.

**CADMIUM CELLS**  
ORP12 43p  
ORP60, ORP61 40p each

**GENERAL PURPOSE NPN SILICON SWITCHING TRANS. TO-18 SIM. TO 2N706 B, BSY27**  
28/95A. All usable devices no open or short circuits. ALSO AVAILABLE in PNP Sim. to 2N2906

**2N3060 NPN SIL. DUAL TRANS. CODE D1699 TEXAS.** Our price 25p each.

**120 VCB MIXIE DRIVER TRANSISTOR** 8 Sim. BSX21 & C407, 2N1993 FULLY TESTED AND CODED ND 120 1-24 17p each. TO-5 NPN 25 up 15p each.

BCY70. When ordering please state preference NPN or PNP  
Eq. 100 For 1.75  
20 For 0.50 500 For 7.50  
50 For 1.00 1000 For 18.00.

**SIL. G.P. DIODES 5p**  
300mV 30 0.50  
40PIV(Min.) 100 1.50  
Sub-Min. 500 5.00  
Full Tested 1,000 9.00  
Ideal for Organ Builders.

**F.E.T.'S**  
2N3819 85p  
2N3820 85p  
2N3821 85p  
2N3823 85p  
2N5458 80p  
2N5469 80p  
BFV 10 40p  
MPF105 40p

## POWER TRANS BONANZA!

**GENERAL PURPOSE GERM. PNP Coded GP100 BRAND NEW TO-3 CASE. P088. REPLACE—OC25 28 29 30 35-36. NKT 401-403-404-405-406-430-451-482-452. T13027-3028, 2N250A, 2N456A 457A-458A, 2N511 A & B 20220-222, ETC. VCB0 80V VCEO 50V IC 10A PT. 30 WATTS RTc 30-170.**  
PRICE 1-24 25-99 100 up  
45p each 40p each 35p each

**SILICON Hgh Voltages 250V PNP TO-3 case. G.P. Switching & Amplifier Applications. Brand new Coded R 2400 VCB0 250V VCEO 100/IC 6A/30 Watta. HFE type 20/IT 5MHz.**  
OUR PRICE EACH: 1-24 25-99 100 up  
50p 45p 40p

**2N3055**  
115 WATT SIL. POWER PNP  
50p EACH

**ADI61/ADI62 NPN**  
M/P COMP GERM TRANS. OUR LOWEST PRICE OF 55p PER PAIR.

**SILICON 50 WATTS MATCHED PNP/PNP BIP 19 NPN TO-3 FAIR**  
BIP 20 PNP. Brand new.  
1-24 25-99 100  
pr. pr. pr.  
80p 55p 50p

## KING OF THE PAKS Unequalled Value and Quality

# SUPER PAKS

### NEW BI-PAK UNTESTED SEMICONDUCTORS

Satisfaction GUARANTEED in Every Pak. or money back.

Pak No.	Contents	Price
U1	120 Glass Sub-Min. General Purpose Germanium Diodes	50p
U2	60 Mixed Germanium Transistors AF/RF	50p
U3	76 Germanium Gold Bonded Sub-Min. Like OA5, OA47	50p
U4	40 Germanium Transistors like OC81, AC128	50p
U5	60 200mA Sub-Min. Silicon Diodes	50p
U6	30 Sil. Planar Trans. NPN like BSY96A, 2N706	50p
U7	16 Sil. Rectifiers Top-Hat 750mA Vltg. Range up to 1,000	50p
U8	50 Sil. Planar Diodes DO-7 Glass 250mA like OA200/202	50p
U9	20 Mixed Voltages, 1 Watt Zener Diodes	50p
U10	20 BA756 charge storage Diodes DO-7 Glass	50p
U11	25 PNP Sil. Planar Trans. TO-5 like 2N132, 2N2904	50p
U12	12 Silicon Rectifiers Epoxy 500 mA up to 800 PIV	50p
U13	30 PNP/NPN Sil. Transistors OC200 and ZS 104	50p
U14	150 Mixed Silicon and Germanium Diodes	50p
U15	25 NPN Sil. Planar Trans. TO-5 like BFY61, 2N697	50p
U16	10 3AMP Silicon Rectifiers Stud Type up to 1,000 PIV	50p
U17	30 Germanium PNP AF Transistors TO-5 like ACY 17-22	50p
U18	8 6AMP Silicon Rectifiers BZY213 Type up to 600 PIV	50p
U19	25 Silicon NPN Transistors like BC108	50p
U20	12 1.5AMP Silicon Rectifiers Top-Hat up to 1,000 PIV	50p
U21	30 AF. Germanium Alloy Transistors 2G300 Series & OCT1	50p
U23	30 MADT's like Mhz Series PNP Transistors	60p
U24	20 Germanium 1 Amp Rectifiers GJM Series up to 300 PIV	60p
U25	25 300 MHz NPN Silicon Transistors 2N708, BSY27	60p
U26	30 Fast Switching Silicon Diodes like IN914 Micro-Min.	60p
U27	10 NPN Germanium AF Transistors TO-18 like AC127	60p
U29	10 IAMP SCR's TO-3 can. up to 600 PIV CR51/26-60	41.00
U30	15 Plastic Silicon Planar Trans. NPN 2N2926	50p
U31	20 Sil. Planar Plastic NPN Trans. Low Noise Amp 2N3707	50p
U32	25 Zener Diodes 400mV DO-7 case 3-18 volts mixed	50p
U33	15 Plastic Case 1 Amp Silicon Rectifiers IN4000 Series	50p
U34	30 Silicon PNP Alloy Transistors TO-5 BCY26 2S202/4	50p
U35	25 Silicon Planar Transistors PNP TO-18 2N2906	50p
U36	25 Silicon Planar NPN Transistors TO-5 BFY50/51/52	50p
U37	30 Silicon Alloy Transistors SO-2 PNP OC200, 28322	50p
U38	20 Fast Switching Silicon Trans. NPN 400 Mhz 2N8011	50p
U39	30 RF. Germ. PNP Transistors 2N1303/5 TO-5	50p
U40	10 PNP Germanium 6 lead TO-5 2N2080	50p
U41	25 RF Germanium Transistors TO-5, OC46, NKT172	50p
U42	10 VHF Germanium PNP Transistors TO-18 NKT1867, AF117	50p
U43	25 Sil. Trans. Plastic TO-18 A.F. BC113/114	50p
U44	20 Sil. Trans. Plastic TO-5 BC118/NPN	50p
U45	7.5A SCR. TO-68 up to 600 PIV	41.00

Code Nos. mentioned above are given as a guide to the type of device in the Pak. The devices themselves are normally unmarked.

**SILICON PHOTO TRANSDUCER TO-18 Lens and NPN Sim. to BP 25 and P21**  
BRAND NEW. Full data available. Fully guaranteed.  
Qty. 1-24 25-99 100 up  
Price each 45p 40p 35p

## DTL & TTL INTEGRATED CIRCUITS

### INTEGRATED CIRCUIT PAKS

Manufacturers "Fall Outs" which include Functional and Partial Units. These are classed as "out of spec" from the maker's very rigid specifications, but are ideal for learning about I.C.'s and experimental work.

Pak No.	Contents	Price	Pak No.	Contents	Price	Pak No.	Contents	Price
UIC00	12 x 7400	50p	UIC46	5 x 7446	50p	UIC86	5 x 7486	50p
UIC01	12 x 7401	50p	UIC47	5 x 7447	50p	UIC90	5 x 7490	50p
UIC02	12 x 7402	50p	UIC48	5 x 7448	50p	UIC91	5 x 7491	50p
UIC03	12 x 7403	50p	UIC50	12 x 7450	50p	UIC92	5 x 7492	50p
UIC04	12 x 7404	50p	UIC51	12 x 7451	50p	UIC93	5 x 7493	50p
UIC05	12 x 7405	50p	UIC53	12 x 7453	50p	UIC94	5 x 7494	50p
UIC06	8 x 7406	50p	UIC54	12 x 7454	50p	UIC95	5 x 7495	50p
UIC07	8 x 7407	50p	UIC60	12 x 7460	50p	UIC96	5 x 7496	50p
UIC10	12 x 7410	50p	UIC70	8 x 7470	50p	UIC100	5 x 74100	50p
UIC13	8 x 7413	50p	UIC72	8 x 7472	50p	UIC121	5 x 74121	50p
UIC20	12 x 7420	50p	UIC73	8 x 7473	50p	UIC141	5 x 74141	50p
UIC30	12 x 7430	50p	UIC74	8 x 7474	50p	UIC151	5 x 74151	50p
UIC40	12 x 7440	50p	UIC75	8 x 7475	50p	UIC154	5 x 74154	50p
UIC41	5 x 7441	50p	UIC76	8 x 7476	50p	UIC183	5 x 74183	50p
UIC42	5 x 7442	50p	UIC80	5 x 7480	50p	UIC199	5 x 74199	50p
UIC43	5 x 7443	50p	UIC81	5 x 7481	50p	UIC X1	25 Assort. 74's	11.50
UIC44	5 x 7444	50p	UIC82	5 x 7482	50p			
UIC45	5 x 7445	50p	UIC83	5 x 7483	50p			

Packs cannot be split, but 25 assorted pieces (our mix) is available as PAK UIC X1.

**BI-PAKS NEW COMPONENT SHOP NOW OPEN WITH A WIDE RANGE OF ELECTRONIC COMPONENTS AND ACCESSORIES AT COMPETITIVE PRICES**  
18, BALDOCK STREET (A10), WARE, HERTS. TEL: 61593.  
OPEN MON. - SAT. 9.15 a.m. to 6 p.m. FRIDAY UNTIL 8 p.m.

All Mail Orders please add 10p post and packing.  
Send all Orders to Bi-Pak P.O. Box 6, Ware, Herts.

# - the lowest prices!

## 74 Series T.T.L. I.C.'S

Bi-Pak Still Lowest in Price.  
Full Specification Guaranteed.  
All Famous Manufacturers.



	1	35	100		1	35	100
SN7400	0.15	0.14	0.12	SN7490	0.67	0.64	0.58
SN7401	0.15	0.14	0.12	SN7491	£1.90	0.95	0.90
SN7402	0.15	0.14	0.12	SN7492	0.67	0.64	0.58
SN7403	0.15	0.14	0.12	SN7493	0.67	0.64	0.58
SN7404	0.15	0.14	0.12	SN7494	0.77	0.74	0.68
SN7405	0.15	0.14	0.12	SN7495	0.87	0.84	0.78
SN7406	0.30	0.31	0.28	SN7496	£1.86	£1.60	£1.55
SN7407	0.30	0.31	0.28	SN7498	0.97	0.94	0.88
SN7408	0.18	0.17	0.16	SN7499	0.77	0.74	0.68
SN7409	0.18	0.17	0.16	SN7410	0.97	0.94	0.88
SN7410	0.18	0.14	0.12	SN74105	0.97	0.94	0.88
SN7411	0.25	0.24	0.23	SN74107	0.40	0.38	0.36
SN7412	0.25	0.31	0.29	SN74110	0.55	0.53	0.50
SN7413	0.29	0.26	0.24	SN74111	£1.25	£1.15	£1.10
SN7414	0.43	0.40	0.38	SN74118	£1.00	0.95	0.90
SN7417	0.43	0.40	0.38	SN74119	£1.35	£1.25	£1.10
SN7420	0.15	0.14	0.12	SN74121	0.40	0.37	0.34
SN7422	0.50	0.48	0.45	SN74112	£1.40	£1.30	£1.10
SN7423	0.50	0.48	0.45	SN74123	£2.80	£2.70	£2.60
SN7425	0.50	0.48	0.45	SN74180	0.67	0.64	0.58
SN7427	0.45	0.42	0.40	SN74185	£1.50	£1.40	£1.30
SN7428	0.70	0.65	0.60	SN74186	£3.00	£2.70	£2.50
SN7430	0.15	0.14	0.12	SN74181	£1.00	0.95	0.90
SN7432	0.40	0.42	0.40	SN74183	£1.20	£1.10	0.95
SN7433	0.60	0.75	0.70	SN74154	£1.80	£1.70	£1.60
SN7437	0.84	0.82	0.80	SN74155	£1.40	£1.30	£1.20
SN7438	0.54	0.52	0.50	SN74156	£1.40	£1.30	£1.20
SN7440	0.15	0.14	0.12	SN74157	£1.80	£1.80	£1.70
SN7441	0.67	0.64	0.58	SN74180	£1.80	£1.70	£1.60
SN7442	0.67	0.64	0.58	SN74181	£1.00	£1.70	£1.60
SN7443	£1.30	£1.25	£1.20	SN74182	£4.00	£3.75	£3.50
SN7444	£1.30	£1.25	£1.20	SN74183	£4.00	£3.75	£3.50
SN7445	£1.80	£1.77	£1.73	SN74184	£2.20	£2.15	£2.10
SN7446	0.97	0.94	0.90	SN74185	£2.25	£2.20	£2.15
SN7447	£1.00	0.97	0.95	SN74186	£2.50	£2.45	£2.40
SN7448	£1.00	0.97	0.95	SN74187	£2.50	£2.45	£2.40
SN7450	0.15	0.14	0.12	SN74174	£2.30	£2.20	£2.10
SN7451	0.15	0.14	0.12	SN74175	£2.30	£2.20	£2.10
SN7453	0.15	0.14	0.12	SN74176	£2.50	£2.40	£2.30
SN7454	0.15	0.14	0.12	SN74177	£2.50	£2.40	£2.30
SN7455	0.15	0.14	0.12	SN74180	£2.00	£1.90	£1.80
SN7470	0.29	0.26	0.24	SN74181	£5.50	£5.00	£4.75
SN7472	0.29	0.26	0.24	SN74182	£2.00	£1.90	£1.80
SN7473	0.37	0.35	0.32	SN74184	£3.00	£3.5	£3.00
SN7474	0.37	0.35	0.32	SN74190	£1.95	£1.90	£1.85
SN7475	0.45	0.43	0.42	SN74191	£1.90	£1.85	£1.80
SN7476	0.40	0.38	0.38	SN74192	£1.95	£1.90	£1.85
SN7480	0.67	0.64	0.58	SN74193	£2.00	£1.90	£1.75
SN7481	£1.30	£1.15	£1.10	SN74194	£2.00	£2.00	£2.50
SN7482	0.97	0.95	0.95	SN74195	£2.00	£1.90	£1.80
SN7483	£1.10	£1.05	0.95	SN74196	£2.00	£1.90	£1.80
SN7484	£1.00	0.95	0.90	SN74198	£1.90	£1.70	£1.60
SN7486	£3.60	£3.50	£3.40	SN74197	£1.90	£1.70	£1.60
SN7486	0.32	0.31	0.30	SN74198	£5.50	£5.00	£4.50
SN7489	£2.50	£2.25	£2.00	SN74199	£5.50	£5.00	£4.50

## BI-PAK DO IT AGAIN!


# 50W pk 25w (RMS)
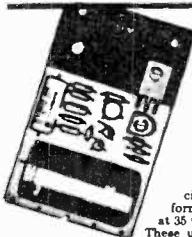
## 0.1% DISTORTION HI-FI AUDIO AMPLIFIER THE AL50



- ★ Frequency response 15Hz to 100,000 - 1dB. **ONLY**
- ★ Load - 3, 4, 8 or 16 ohms. **£3.25p each**
- ★ Distortion - better than 0.1% at 1KHz. ★ Supply voltage 10 - 35 Volts.
- ★ Signal to noise ratio 80dB. ★ Overall size 63mm x 105mm x 13mm.

Tailor made to the most stringent specifications using top quality components and incorporating the latest solid state circuitry and ALSO was conceived to fill the need for all your A.F. amplification needs. **FULLY BUILT - TESTED - GUARANTEED.**



## STABILISED POWER MODULE SPM80

AP80 is especially designed to power 2 of the AL50 Amplifiers, up to 15 watt (rms) per channel, simultaneously. This module embodies the latest components and circuit techniques incorporating complete short circuit protection. With the addition of the Main Transformer M780, the unit will provide outputs of up to 1.5 amp at 35 volts. Size: 62mm x 106mm x 30mm

These units enable you to build Audio Systems of the highest quality at a hitherto unobtainable price. Also ideal for many other applications including: Disco Systems, Public Address, Intercom Units etc. Handbook available 10p. **PRICE £3.95**

**TRANSFORMER BMT80 £1.95 p. & p. 25p.**

## STEREO PRE-AMPLIFIER, TYPE PA100

Built to a specification and NOT a price, and yet still the greatest value on the market, the PA100 stereo pre-amplifier has been conceived from the latest circuit techniques. Designed for use with the AL50 power amplifier system, this quality made unit incorporates no less than eight silicon planar transistors, two of these are specially selected low noise NPN devices for use in the input stages.

Three switched stereo inputs, and rumble and scratch filters are features of the PA100, which also has a STEREO/MONO switch, volume, balance and continuously variable bass and treble controls.



**SPECIFICATION**  
 Frequency Response 20Hz - 20KHz ± 1dB  
 Harmonic Distortion better than 0.1%  
 Inputs: 1. Tape Head 1.25 mV into 50KΩ  
 2. Radio, Tuner 35 mV into 50KΩ  
 3. Magnetic P.U. 1.5 mV into 50KΩ  
 All input voltages are for an output of 250mV. Tape and P.U. inputs equalised to RIAA curve within ± 1dB, from 20Hz to 20KHz.  
 Base Control ± 15dB @ 20Hz Treble Control ± 15dB @ 20KHz  
 Filters: Rumble (High Pass) 100Hz  
 Scratch (Low Pass) 8KHz  
 Signal/Noise Ratio better than - 65dB  
 Input overload + 26dB Supply + 35 volts @ 20mA  
 Dimensions 292mm x 82mm x 36mm **Price £11.95**

**SPECIAL COMPLETE KIT COMPRISING**  
 2 AL50's, 1 SPM80, 1 BMT80 and 1 PA100 **ONLY £33.00 FREE p & p.**

All prices quoted in new pence. **Giro No. 388-7006**  
 Please send all orders direct to warehouse and despatch department

# BI-PAK

**P.O. BOX 6, WARE · HERTS**

Postage and packing add 10p. Overseas add extra for airmail. Minimum order 50p. Cash with order please.

**Guaranteed Satisfaction or Money Back**

## LINEAR I.C.'s— FULL SPEC.

Type No.	1-34	25-99	100 up
BP 201C—SL201C	65p	55p	45p
BP 701C—SL701C	65p	50p	45p
BP 702C—SL702C	65p	50p	45p
BP 702—72702			
BP 709—72709	55p	45p	30p
BP 709F—μA709C	36p	34p	30p
BP 710—72710	44p	43p	40p
BP 711—μA711	45p	43p	40p
BP 741—72741			
μA 703C—μA703C	75p	60p	50p
TA A263	70p	60p	55p
TA A263	90p	75p	70p
TA A360	170p	160p	150p

## LOGIC DTL 930 SERIES I.C.'s ROCK BOTTOM PRICES

Type No.	1-24	25-99	100 up
BP930	12p	11p	10p
BP932	12p	11p	10p
BP933	12p	11p	10p
BP935	12p	11p	10p
BP936	12p	11p	10p
BP944	12p	11p	10p
BP945	12p	11p	10p
RP945	12p	11p	10p
BP948	25p	24p	20p
BP951	40p	39p	35p
BP962	12p	11p	10p
BP9093	40p	39p	35p
BP9094	40p	39p	35p
BP9097	40p	39p	35p
BP9099	40p	39p	35p

Devices may be mixed to qualify for quantity price. Larger quantity prices on application. (DTL 930 Series only).

## NUMERICAL INDICATOR TUBES



MODEL	CD66	GR 116	3015F
Anode voltage (Vdc)	170	175	5
min			
Cathode cur'nt(mA)	2.3	14	
Numeral height (mm)	16	13	9
Tube height (mm)	47	32	22
Tube diameter (mm)	19	13	12
I.C. driver rec.	BP41 or 141	BP41 or 141	BP47
PRICE EACH	£1.70	£1.55	£1.90

All indicators 0.9 + Decimal point: All side viewing: Full data for all types available on request.


## RTL MICROLOGIC CIRCUITS

	Price each
Epoxy TO-8 case	1-34 25-99 100 up
μL900 Buffer	85p 85p 87p
μL914 Dual 2/p gate	
μL923 J-K flip-flop	85p 85p 87p
Date and Circuits Booklet for IC's Price 7p.	50p 47p 45p

## DUAL IN LINE SOCKETS

Prof. Type No.	1-24	25-99	100 up
TS014 pin type	30p	27p	25p
TS016 pin type	35p	32p	30p
Low Cost No.			
BPS 14	15p	13p	11p
BPS 16	16p	14p	12p

**NOW AVAILABLE . . .**

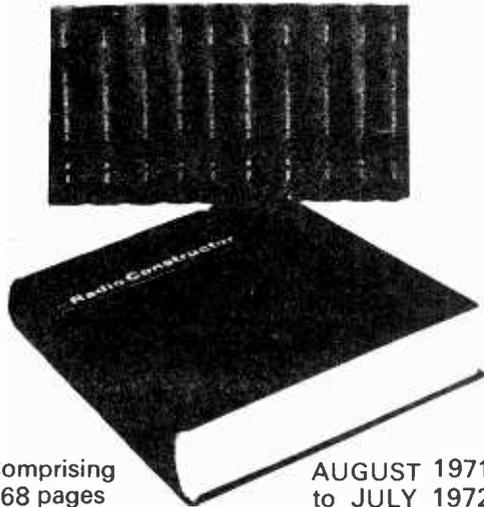

Comprising  
768 pages  
plus index

AUGUST 1971  
to JULY 1972

# LATEST BOUND VOLUME

## No. 25

of

### "The Radio Constructor" FOR YOUR LIBRARY

**PRICE £2.00 P&P 29p**

**BOUND VOLUME NO. 23 (August 1969 to July 1970)**  
**BOUND VOLUME NO. 24 (August 1970 to July 1971)**

Limited number of these  
volumes still available.

**PRICES Volume 23 £1.88 Postage 29p Volume 24 £2.00 Postage 29p**

We regret all earlier volumes are now completely sold out.

Available only from

**DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON, W9 1SN**

## Vary the strength of your lighting with a **DIMMASWITCH**



The DIMMASWITCH is an attractive and efficient dimmer unit which fits in place of the normal light switch and is connected up in exactly the same way. The white mounting plate of the DIMMASWITCH matches modern electric fittings. Two models are available, with the bright chrome knob controlling up to 300 w or 600 w of all lights except fluorescents at mains voltages from 200-250 v, 50Hz. The DIMMASWITCH has built-in radio interference suppression:  
600 Watt £3.20. Kit Form £2.70  
300 Watt £2.70. Kit Form £2.20

All plus 10p post and packing.  
Please send C.W.O. to:

**DEXTER & COMPANY**  
7 ULVER HOUSE, 19, KING STREET,  
CHESTER CH1 2AH. Tel: 0244-25883.  
As supplied to H.M. Government Departments.

## SAVE TIME AND MONEY

LIST  
PRICE **£6.25**

OUR  
PRICE **£4.84**



As supplied by us to **SCHOOLS, TECHNICAL COLLEGES, SHOPS, OFFICES AND INDUSTRY**. Silver grey stove enamelled steel cabinet with 48 transparent styrene drawers fitted with moulded handles and label slots. Dividers can be supplied at an extra charge to enable each drawer to be sub-divided into six compartments. Transparent drawers allow swift selection of components at a glance and eliminates duplication of stock. A really first class time saving unit. Size of cabinets 21" x 11 1/2" x 6 1/2". Size of drawers 6 1/2" x 2 1/2" x 1 1/2". Other sizes available.  
Callers welcome Mon.-Sat. 9 a.m.-1 p.m. -1 p.m.-6 p.m. NEW as illustrated **OUR PRICE ONLY £4.84** plus 35p carriage on orders less than £10. Money back guarantee. **SEND FOR FREE COLOUR BROCHURE.**

## TRADE AIDS

(DEPT. RC3) 11 CHILTERN DRIVE,  
BERRYLANDS, SURBITON, SURREY  
01-399 4383

100 yds. Berrylands Railway Station



## LOUDSPEAKER BARGAINS

Fane Pop 100 watt 18" 8/15 ohm	£19.50
Fane Pop 60 watt 15" 8/15 ohm	£11.15
Fane Pop 50 watt 12" 8/15 ohm	£ 9.25
Fane Pop 25/2 12" 25 watt 8/15 ohm	£5.40
Fane Pop 15 12" 10 watt 8/15 ohm	£4.00
Baker Group 25 12" 3.8 or 15 ohm	£6.60
Baker Group 35 12" 3.8 or 15 ohm	£8.00
Celestion PS8 for Unilex	£2.35
EMI 13 x 8 3.8 or 15 ohm	£2.25
EMI 13 x 8, 3.8 or 15 ohm	£2.60
EMI 13 x 8 twin/tw. 3.8 or 15 ohm	£3.60
EMI 13 x 8 type 350 15 watt 8 ohm	£8.00
Richard Allan 8" 3.8 or 15 ohm	£2.35
Richard Allan 12" dual cone 3 or 15 ohm	£2.50
Fane 8" d/cone 808T 8 or 15 ohm	£2.85
Fane 8" d/cone, roll surround, 807T 8 or 15 ohm	£3.50
Elac 9 x 5 59RM 09 15 ohm	£2.70
Elac 9 x 5 59RM 114 8 ohm	£2.70
Elac 6 1/2" dual cone 8 ohm	£2.25
Elac 6 1/2" d/cone, roll surround 8 ohm	£3.50
Elac 4" tweeter 8 ohm	£1.50
Crossover for above (p & p free)	£1.50
Goodmans 10P 8 or 15 ohm	£4.75
Goodmans 12P 8 or 15 ohm	£5.25
Goodmans 15P 8 or 15 ohm	£10.50
Goodmans 18P 8 or 15 ohm	£17.00
Goodmans 18P 8 or 15 ohm	£27.00
2" 2 1/2" or 3" 80 ohm	65
Philips 5" 8 ohm	£1.95
7 x 4 or 8" x 5" 3 or 8 ohm	£1.50
10" x 6" 3.8 or 15 ohm	£2.00

FREE with orders over £6.00 "Hi-fi loudspeaker enclosures" book.

All units guaranteed new and perfect.

Prompt despatch P & P 25p per speaker.

Send for our free booklet: "Choosing a speaker".

## WILMSLOW AUDIO (Dept. RC)

10 Swan St., Wilmslow,  
SK9 1HF, Cheshire

## PRECISION

### POLYCARBONATE CAPACITORS

**Fresh Stock - Fully Tested and Guaranteed**

Close tolerance professional capacitors by well-known manufacturer. Excellent stability and extremely low leakage. All 63V D.C.

0.47 $\mu$ F: $\pm 5\%$	30p: $\pm 2\%$	40p: $\pm 1\%$	50p: $\pm 1\%$
1.0 $\mu$ F: $\pm 5\%$	40p: $\pm 2\%$	50p: $\pm 1\%$	60p: $\pm 1\%$
2.2 $\mu$ F: $\pm 5\%$	50p: $\pm 2\%$	60p: $\pm 1\%$	75p: $\pm 1\%$
4.7 $\mu$ F: $\pm 5\%$	70p: $\pm 2\%$	90p: $\pm 1\%$	115p: $\pm 1\%$
6.8 $\mu$ F: $\pm 5\%$	95p: $\pm 2\%$	115p: $\pm 1\%$	150p: $\pm 1\%$
10.0 $\mu$ F: $\pm 5\%$	110p: $\pm 2\%$	140p: $\pm 1\%$	180p: $\pm 1\%$
15.0 $\mu$ F: $\pm 5\%$	160p: $\pm 2\%$	210p: $\pm 1\%$	270p: $\pm 1\%$

### NEW! - TANTALUM BEAD CAPACITORS

Values available .22, .47, 1.0, 2.2, 4.7, 6.8  $\mu$ F at 35V, 10  $\mu$ F 25V, 15  $\mu$ F 20V, 22  $\mu$ F 15V, 33  $\mu$ F 10V, 47  $\mu$ F 6V, 100  $\mu$ F 3V. All at 9p each; 6 for 50p; 14 for £1.00. Special pack, 6 off each value (72 capacitors) for £5.00.

**TRANSISTORS:** BC107; BC108; BC109 (please state which), all at 9p each, 6 for 50p; 14 for £1.00; May be mixed to qualify for lower price. All brand new to full manufacturer's specification.

**POPULAR DIODES:** IN914 - 7p each; 8 for 50p; 18 for £1.00  
IN916 - 9p each; 6 for 50p; 14 for £1.00. IS44 - 5p each; 11 for 50p; 24 for £1.00. All brand new and marked.

**400mW ZENER DIODES:** Values available 4.7, 6.8, 7.5, 8.2, 9.1, 10, 11, 12, 13.5, 15 volts. All new and marked. All at 10p each; 6 for 50p; 14 for £1.00.

**RESISTORS:** Carbon film  $\frac{1}{2}$  watt 5%. Range 2.2 $\Omega$ -2.2M $\Omega$  E12. Series i.e. 10, 12, 15, 18, 22, 27, 33, 39, 47, 56, 68, 82, and their decades. All at 1p each. 8p for 10 of any one value; 70p for 100 of any one value. Special development pack 10 off each value 2.2 $\Omega$  to 2.2M $\Omega$  (730 resistors) for £5.00.

**440V A.C. CAPACITORS:**  
0.1  $\mu$ F: Size 1 $\frac{1}{2}$ " x  $\frac{1}{2}$ ", 25p each  
0.25  $\mu$ F: Size 1 $\frac{3}{4}$ " x  $\frac{3}{8}$ ", 30p each  
1.0  $\mu$ F: Size 2" x  $\frac{3}{8}$ ", 45p each  
2.0  $\mu$ F: Size 2" x 1", 75p each  
Suitable for use on C.D. ignition, 250V A.C. motors, etc.

5p post and packing on all orders below £5

**V.ATTWOOD, Dept C.5., P.O. Box 8, Alresford, Hants.**

# Now! A FAST EASY WAY TO LEARN BASIC RADIO & ELECTRONICS



Build as you learn with the exciting new **TECHNATRON** Outfit! No mathematics. No soldering—you learn the *practical way.*

Learn basic Radio and Electronics at home - the fast, modern way. Give yourself essential technical 'know-how' - like reading circuits, assembling standard components, experimenting, building - quickly and without effort, and enjoy every moment. B.I.E.T.'s simplified study method and the remarkable **TECHNATRON Self-Build Outfit** take the mystery out of the subject, making learning easy and interesting.

Even if you don't know the first thing about Radio now, you'll build your own Radio set within a month or so!

and what's more, you will understand exactly what you are doing. The **TECHNATRON** Outfit contains everything you need, from tools to transistors - even a versatile Multimeter which we teach you to use. All you need give is a little of your spare time and the surprisingly low fee, payable monthly if you wish. And the equipment remains yours, so you can use it again and again.

You **LEARN** - but it's as fascinating as a hobby.

Among many other interesting experiments, the Radio set you build - and it's a good one - is really a bonus. This is first and last a teaching course, but the training is as fascinating as any hobby and it could be the springboard for a career in Radio and Electronics.

A 14-year-old could understand and benefit from this course - but it teaches the real thing. The easy to understand, practical projects - from a burglar-alarm to a sophisticated Radio set - help you master basic Radio and Electronics - even if you are a 'non-technical' type. And, if you want to make it a career, B.I.E.T. has a fine range of courses up to City and Guilds standards.

### Specialist Booklet

If you wish to make a career in Electronics, send for your **FREE** copy of "NEW OPPORTUNITIES". This brand new booklet - just out - tells you all about **TECHNATRON** and B.I.E.T.'s full range of courses.



## FREE

### BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY

Dept. B9, ALDERMASTON COURT, READING RG7 4PF

Accredited by the Council for the Accreditation of Correspondence Colleges.

**POST THIS COUPON FOR FREE BOOK**

B9

NAME..... AGE.....

(BLOCK CAPITALS)

ADDRESS.....

SUBJECT OF INTEREST.....

## THE 'PLUS' CATALOGUE

Technical data - Countless bargains + Discounts



+

25p

### REFUND VOUCHER

The Electrovalue Catalogue now costs 25p (post free, surface mail) and is well worth it for its technical information. But we include with it a 25p refund voucher for spending on orders for £5 or more. You will find this catalogue a great money saver in every way.

- 96 Pages. (4th printing)
- Transistors, with technical specs.
- I.Cs with working diagrams
- Resistors, capacitors, components
- Diagrams, tables, information
- **GENUINE DISCOUNTS**

**ELECTROVALUE LTD.** Dept. R.C. 12

28 St. Judes Rd., Englefield Green, Egham, TW20 0HB  
9-6 daily: 1.0 p.m. Sat. Telephone Egham 3603







# BI-PRE-PAK



**COMPLETE TELEPHONES**  
Normal household type as supplied to the Post Office, ex. G.P.O. Only **95p** each, p. & p. 35p each.



**TELEPHONE DIALS**  
Standard Post Office type. Guaranteed in working order. **ONLY 25p**  
p. & p. 15p.

## TESTED AND GUARANTEED PAKS

B2	4	Photo Cells, Sun Batteries 0.3 to 0.5V, 0.5 to 20mA	50p
B79	4	1N4007 Sil. Rec. diodes, 1,000 PIV lamp plastic	50p
B81	10	Reed Switches, mixed types large and small	50p
B99	200	Mixed Capacitors, Approx. quantity, counted by weight	50p
H4	250	Mixed Resistors, Approx. quantity counted by weight	50p
H7	40	Wirewound Resistors, Mixed types and values	50p
H9	2	OC71 Light Sensitive Photo Transistor	50p
H38	20	OC3001/313 PNP Silicon uncoated TO-3 can	50p
H30	20	1 Watt Zener Diodes, Mixed Voltages 6.8 - 43V	50p
H35	100	Mixed Diodes, Germ. Gold bonded, etc. Marked and Unmarked	50p
H38	30	Short Lead Transistors, NPN Silicon Planar types	50p
H39	10	Integrated Circuits: 6 Gates, BMC 962.4 Flip Flops, BMC 945	50p
H40	20	BFY50/2, 2N696, 2N1613, NPN Silicon uncoated TO-5	50p

## UNMARKED UNTESTED PAKS

B66	150	Germanium Diodes, Min. glass type	50p
B83	200	Trans. manufacturers' rejects all types NPN, PNP, Sil. and Germ.	50p
B84	100	Silicon Diodes DO-7 glass equiv. to OA200, OA202	50p
B86	100	Sil. Diodes sub. min. 1N914 and 1N916 types	50p
B88	50	Sil. Trans. NPN, PNP equiv. to OC200/1, 2N706A, BS195A, etc.	50p
B1	50	Germanium Transistors PNP, A.F. & R.F.	50p
H6	40	250mW Zener Diodes DO-7 Min. Glass Type	50p
H34	15	Power Transistors, PNP, Germ. NPN Silicon TO-3 Can	50p
H17	20	3 amp Silicon Stud rectifiers, mixed volts	50p
H13	30	Top Hat Silicon Rectifiers, 750mA Mixed volts	50p
H16	15	Experimenters' Pak of Integrated Circuits, Data supplied	50p
H30	20	BY126/7 Type Silicon Rectifiers 1 amp plastic, Mixed volts	50p

## MAKE A REV COUNTER FOR YOUR CAR

The 'TACHO BLOCK' This encapsulated block will turn any 0.1mA meter into a linear and accurate rev. counter for any car with normal coil ignition system.

**£1 each**



## OVER 1,000,000 TRANSISTORS IN STOCK

We hold a very large range of fully marked, tested and guaranteed Transistors, Power Transistors, Diodes and Rectifiers at very competitive prices. Please send for Free Catalogue.

## 600,000 Silicon Planar Plastic Transistors. Unmarked, untested - Factory clearance. A random sampling showed these to be of remarkably high quality.

Audie PNP, similar to ZTX500, 2N3702 3, BCY 70 etc.  
Audio NPN, similar to ZTX300, 2N3708 9, BC107 8 9, BC169 9 etc.  
R.F. NPN and Switching PNP  
Please state type of Transistor required when ordering.  
ALL AT 500 for £3.00, 1,000 for £5.00, 10,000 for £40.00

## OUR VERY POPULAR 3p TRANSISTORS

TYPE "A": PNP Silicon alloy, TO-5 can.  
TYPE "B": PNP Silicon, plastic encapsulation.  
TYPE "E": PNP Germanium AF or RF.  
TYPE "F": NPN Silicon plastic encapsulation.  
TYPE "G": NPN Silicon, similar ZTX300 range.  
TYPE "H": PNP Silicon, similar ZTX500 range.

## POWER TRANSISTOR PRICE BREAKTHROUGH!

PLASTIC CASED SILICON POWER TRANSISTORS OF LATEST DESIGN, 40 WATTS and 90 WATTS PNP & NPN TYPES.  
ALL TYPES AVAILABLE AT THE MOST SHATTERINGLY LOW PRICES OF ALL TIME. ALL ARE FULLY TESTED, MARKED AND GUARANTEED!

		1-12	13-25	26-50
40W	NPN	20p	18p	16p
40W	PNP	21p	19p	17p
90W	NPN	24p	22p	20p
90W	PNP	25p	23p	21p

PAK PAKS of complementary pairs  
MP 40 40W 40W 50p 48p 46p  
MP 90 90W 90W 60p 58p 54p



## A CROSS HATCH GENERATOR FOR £3.50 !!!

YES, a complete kit of parts including Printed Circuit Board. A four position switch gives X-hatch, Dots, Vertical or Horizontal lines. Integrated Circuit design for easy construction and reliability. This is a project in the September edition of Practical Television.

This complete kit of parts costs **£3.50**, post paid.

A MUST for Colour T.V. Alignment.

Our famous P1 Pak is still leading in value for money.

Full of Short Lead Semiconductors & Electronic Components, approx. 120. We guarantee at least 30 really high quality factory marked Transistors PNP & NPN, and a host of Diodes & Rectifiers mounted on Printed Circuit Panels. Identification Chart supplied to give some information on the Transistors.

Please ask for Pak P1, only 50p  
10p P & P on this Pak.

## FREE CATALOGUE

FOR TRANSISTORS, RECTIFIERS, DIODES, INTEGRATED CIRCUITS, FULL PRE-PAK LISTS.



## 8 RELAYS FOR £1

VARIOUS TYPES POST & PACKING 25p INTEGRATED CIRCUITS

THE LOWEST PRICES OF ALL FOR YOUR DTL

	LOGIC	1-12	13-25	26-50
Clocked Flip Flop	BMC931	20p	18p	16p
Ex. 2-4-input Buffer	BMC932	12p	11p	10p
2-4-input Expander	BMC933	12p	11p	10p
Hex. Inverter	BMC934	12p	11p	10p
Hex. Inverter	BMC935	12p	11p	10p
Hex. Inverter	BMC936	12p	11p	10p
Hex. Inverter	BMC937	12p	11p	10p
Decade Counter	BMC938	25p	23p	21p
Div. by 16 Counter	BMC939	25p	23p	21p
Hex. Inverter	BMC940	12p	11p	10p
Hex. Inverter	BMC941	12p	11p	10p
Type D, 4-input Flip	BMC942	20p	18p	16p
Ex. 2-4-input Power	BMC944	12p	11p	10p
Clocked Flip Flop	BMC945	20p	18p	16p
4/2 Input Nand Gate	BMC946	11p	10p	9p
Clocked Flip Flop	BMC948	20p	18p	16p
4/2 Input Nand Gate	BMC949	12p	11p	10p
Pulsed Trig. Binary	BMC950	20p	18p	16p
Monostable Mult. vib.	BMC951	25p	23p	21p
Dual J/K Flip Flop	BMC953	20p	18p	16p
Dual J/K Flip Flop	BMC955	20p	18p	16p
Dual J/K Flip Flop	BMC956	20p	18p	16p
Quad 2-input Power	BMC958	12p	11p	10p
2-4-input Gate	BMC961	12p	11p	10p
3-input NAND Gate	BMC962	11p	10p	9p
3-input NAND Gate	BMC963	12p	11p	10p
Audio Amp. 3-watts	SL403D	£1.50	£1.40	£1.36
Linear Op. Amp	709C	25p	20p	15p
Decade Counter	SN7490	65p	60p	55p

LOW COST DUAL IN LINE I.C. SOCKETS  
14 pin type at 15p each  
16 pin type at 16p each. Now new low profile type.

## BOOKS

We have a large selection of Reference and Technical Books in stock. These are just two of our popular lines:  
**B.P.I. Transistor Equivalents and Substitutes.** 40p  
This includes many thousands of British U.S.A., European and C.V. equivalents.  
**The Hi-Fi Radio Valve & Transistor Data Book 7th Edition P & P 21p** 75p  
Characteristics of 3,000 valves and tubes, 4,500 Transistors, Diodes, Rectifiers and Integrated Circuits.  
Send for lists of these English publications.

Please send me the FREE Bi-Pre-Pak Catalogue


NAME

ADDRESS

MINIMUM ORDER 50p CASH WITH ORDER  
PLEASE Add 10p post and packing per order  
OVERSEAS ADD EXTRA FOR POSTAGE
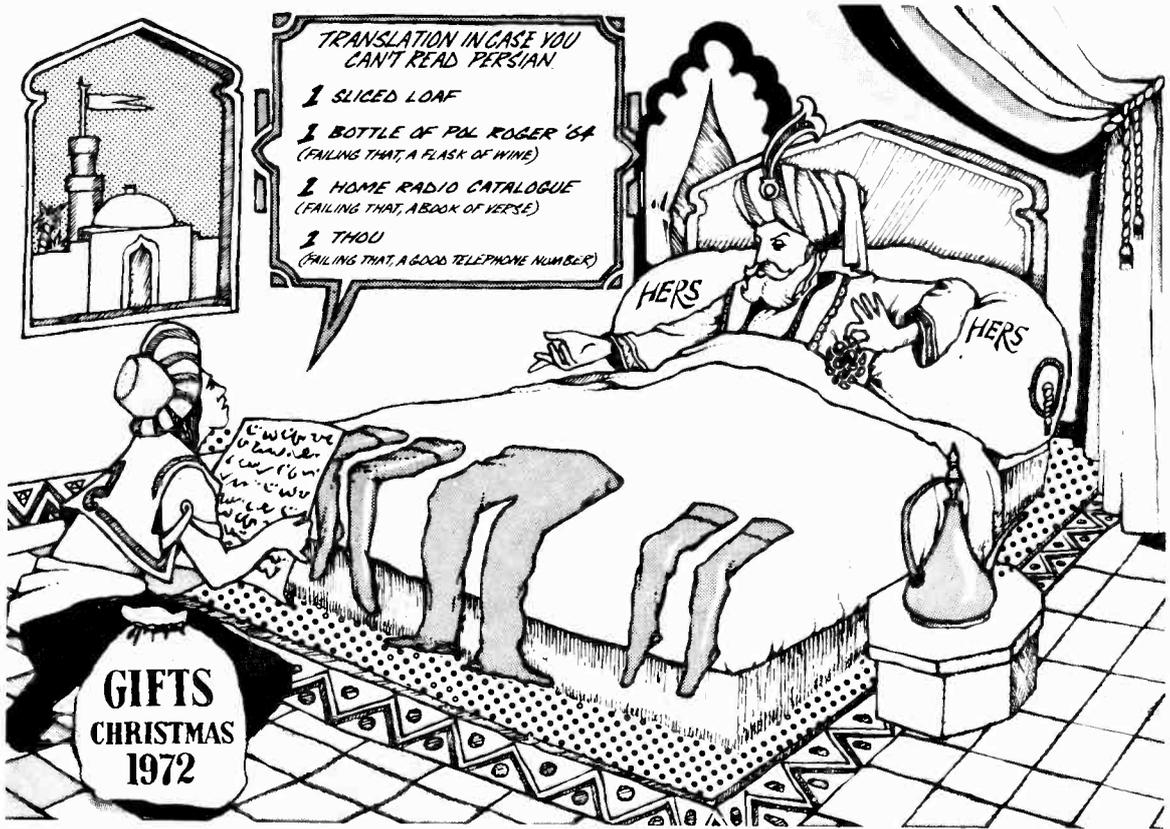
# BI-PRE-PAK LTD

DEPT. C, 222-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX, SSO 9DF  
TELEPHONE: SOUTHEND (0702) 46344



For the benefit of those who have a scientific rather than a literary bent, may we explain? Omar Khayyam was a Persian Tent Maker who lived in the 11th Century. He was also a Poet, Philosopher and Astronomer. Thanks to the fine translation by Edward Fitzgerald, his best known work is the exquisite "Rubaiyat." It was first produced in England as a pamphlet and offered at sixpence. It didn't sell and was reduced to twopence. As there are only three known copies left in existence you may imagine what they are worth today!

One of the best known verses runs as follows:

'Here with a loaf of Bread beneath the Bough,  
A Flask of wine, a Book of Verse and Thou  
Beside me singing in the Wilderness  
And Wilderness is Paradise enow.'

We hope that throws some light on our cartoon. If you read the poem you are bound to come to the conclusion that O.K. liked his tittle — obviously a thoroughly "good type."


What's all this to do with Electronics? you may well ask!!!

Nothing really, but after all this is the Christmas Number, so we should be able to let our hair down. In any case we are sure you must already know that we produce an excellent Components Catalogue which will make interesting holiday reading for you, listing as it does some 6,785 items (over 1,750 illustrated) and costing only 75p including postage and packing, (only 55p if you collect it). It also contains 10 vouchers (each worth 5p when used as directed). Are you convinced? No? Well you'd better go out and buy Omar's "Rubaiyat" instead!

Our "new look" catalogue is hot off the press! Larger pages, many new items and pictures. Now, more than ever, it is a "must" for every keen constructor.

Full details of our popular Credit Account Service are given in the catalogue.

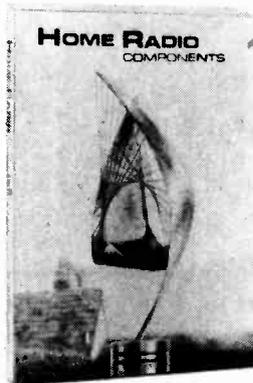The price of 75p applies only to catalogues purchased by customers in the U.K. and to BFPO addresses.



**POST THIS COUPON** with your cheque or postal order for 75 pence

Please write your Name and Address in block capitals

Name.....

Address.....



**HOME RADIO (COMPONENTS) LTD., Dept. RC**  
234-240 London Road, Mitcham, Surrey CR4 3HD.

RADIO & ELECTRONICS CONSTRUCTOR

# RADIO & ELECTRONICS CONSTRUCTOR

DECEMBER 1972

CONTENTS

Vol. 26 No. 5

Published Monthly (1st of Month)  
First Published 1947

*Incorporating The Radio Amateur*

*Editorial and Advertising Offices*  
57 MAIDA VALE LONDON W9 1SN

*Telephone*                      *Telegrams*  
01-286 6141                      Databux, London

© *Data Publications Ltd.*, 1972. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

*Annual Subscription:* £2.70 (U.S.A. and Canada \$7.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

*Technical Queries.* We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

*Correspondence* should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

*Opinions* expressed by contributors are not necessarily those of the Editor or proprietors.

*Production.*—Web Offset.

USING THE F.E.T. by M. Harding	288
SWITCH ABBREVIATIONS	292
TRADE NEWS	293
D.C. VOLTMETER (Suggested Circuit 265) by G. A. French	294
NEWS AND COMMENT	298
HIGH-GAIN SILICON REFLEX RECEIVER by G. W. Short	300
THE 'WYVERN' 160 METRE SOLID STATE TRANSMITTER – Part 2 by John R. Green, B.Sc., G3WVR	304
TRANSISTORISED OSCILLOSCOPE – Part 1 by R. A. Penfold	309
SHORT WAVE NEWS by Frank A. Baldwin	318
CYCLOPS (Electronic Robot) – Conclusion by L. C. Galitz	320
QUIZ DETECTOR by M. Jennings	327
BOOK REVIEW	328
RADIO TOPICS by Recorder	329
IN YOUR WORKSHOP	330
NEW PRODUCT	337
RADIO CONSTRUCTOR'S DATA SHEET No. 69 (Coil Data II)	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London, W9 1SN

Radio & Electronics Constructor is printed by Carlisle Web Offset.

JANUARY ISSUE WILL BE  
PUBLISHED ON JANUARY 1st

# USING THE F.E.T.

by  
M. Harding

Some notes on the functioning of the field effect transistor, together with a typical circuit application in which it may be employed.

ONE OF THE FIRST THINGS THAT ONE LEARNS ABOUT the field effect transistor or f.e.t. is that it has properties more like those of the thermionic valve than those of the ordinary transistor.

The f.e.t. is a voltage controlled device unlike the conventional transistor, which is current operated. One of the most important properties of the f.e.t. lies in its very high input resistance, although there are some other useful features which will be briefly discussed.

The f.e.t. is by no means a new device, for if one goes back to 1933 reference can be found to a patent taken out by J. E. Lilienfeld concerning a field effect device from which, in 1952, W. E. Shockley was able to develop the first practical f.e.t.

## INTERNAL CONSTRUCTION

In order to get to grips with any device it is necessary to briefly consider its internal construction together with its characteristic behaviour. In almost all accounts about the f.e.t. various terms turn up which tend to give the device a slight aura of mystery. Such terms are 'depletion layer' and 'enhancement mode'. A brief explanation of these aspects of the device will be given in order to enable the reader to make fullest use of the device.

Fundamentally there are two types of f.e.t. in common usage, these being

- (a) the *jugfet* or junction gate f.e.t.
- (b) the *igfet* or insulated gate f.e.t.

This latter device is more commonly called the *mosfet* or metal oxide silicon f.e.t., and therefore throughout the

rest of this article 'mosfet' will be used to describe the insulated gate type of f.e.t. For the most part we will be concerned with the *jugfet* and will conclude with a practical design for an a.f. buffer stage which illustrates the way in which the f.e.t. characteristics may be exploited. However, comparisons will be made with the *mosfet* because of the importance of the latter device.

## PRINCIPLES OF OPERATION


Fig. 1(a) illustrates the basic structure of the *jugfet*. Just like the ordinary transistor there are three electrodes, but this time they are called the gate, source and drain. The so-called channel is formed by the region of semiconductor material connecting the source and drain. In the diagram this is shown as being composed of n type silicon and the device would be referred to as an n channel f.e.t. In fact just as we have p.n.p. transistors to complement n.p.n. types, reverse polarity or p channel f.e.t.s also exist.

As shown in the diagram, with an n channel f.e.t. the gate region is p type silicon, and in this article only n channel devices are considered.


It should be noted that both drain and source contacts are non-rectifying or ohmic contacts and therefore the current flowing between them is proportional to the applied voltage across them.

As a useful guide it can be said that in general the source is the common electrode, the gate the input electrode and the drain the output electrode.

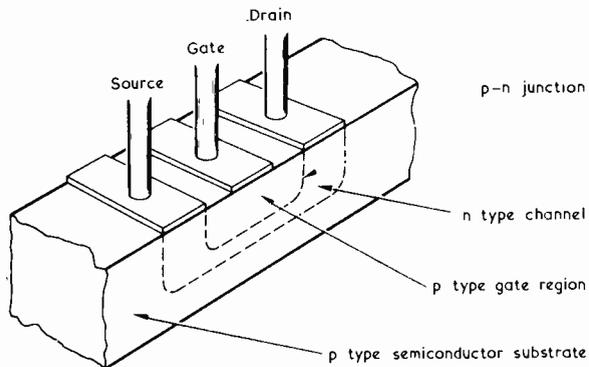Like the thermionic valve the majority current carriers in an n channel f.e.t. are electrons and they



(a)

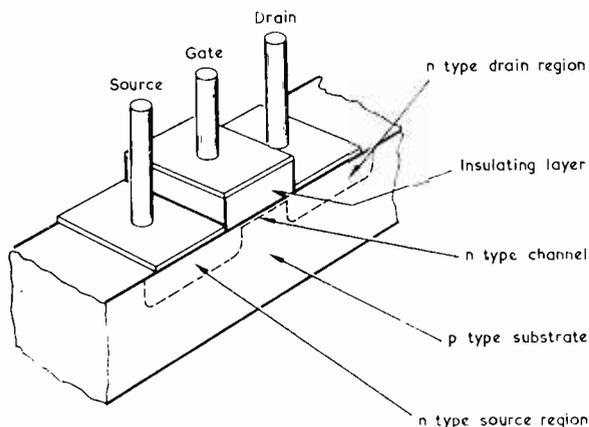

(b)

Fig. 1 (a). Basic construction of an n type channel junction gate f.e.t.  
(b). The n channel depletion mosfet

flow between source and drain - these electrodes being very aptly named. It is interesting to contrast this situation with the ordinary transistor which uses two types of current carrier, i.e. electrons and holes. In consequence the f.e.t. is often referred to as a unipolar device in order to distinguish it from the ordinary transistor which is then referred to as a bipolar device.

In normal operation the gate to source junction is reverse biased and therefore the input impedance can be very high indeed, some hundreds of megohms. With certain mosfets the figure can reach a million megohms. The basic structure of a mosfet is illustrated in Fig. 1(b).

To return to the jugfet we find that when the gate-source bias is increased the so-called depletion layer, in the region of the junction, extends into the channel and effectively reduces its width. (A short discussion on the depletion layer is included at the end of this article.) Accepting that this depletion layer is encroaching into the channel, the result is going to be a higher channel resistance and therefore a smaller channel current flow for a given potential between source and drain.

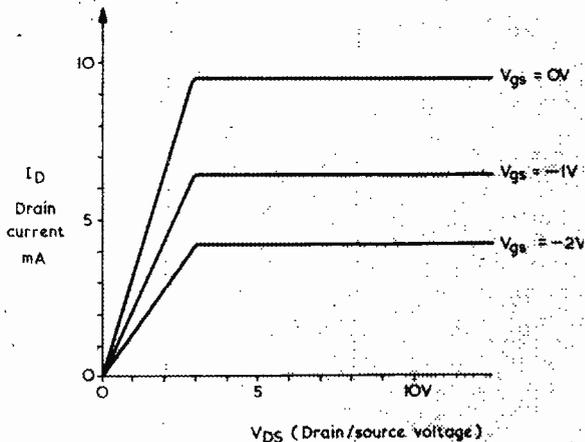


Fig. 2. Typical drain current-voltage characteristic curves for a jugfet

It is from this behaviour that the device gets its name, since changes in the transverse electric field of the junction region produces changes in the channel resistance. And so, we have a device which acts as a voltage controlled resistance. If we put a load resistance in series with the drain we have a direct current amplifier.

It is useful at this point to consider a graph showing the relationship between drain current  $I_D$  and drain-to-source voltage  $V_{DS}$  for three values of gate voltage. The result for a typical n channel f.e.t. is shown in Fig. 2. Valve men will at once see the similarity between the graph of Fig. 2 and the transfer characteristics of the pentode. The graph relating the drain current to gate-to-source voltage is shown in Fig. 3. For those with mathematical inclinations it can be shown that this characteristic has a square law relationship. This point

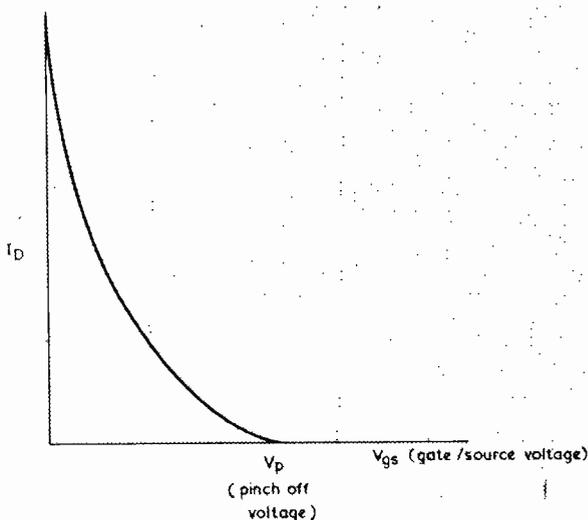


Fig. 3. Curve showing drain current against gate voltage

is of some importance when the f.e.t. is used as a mixer because it gives the device an excellent cross-modulation characteristic. This graph is also useful in showing the value of gate to source voltage required to completely cut off the source to drain current. This last parameter is called the pinch-off voltage  $V_p$  and varies, from device to device, from between as little as 3V to about 10V.

Of note is the fact that some jugfets are symmetrical, i.e. the drain and source are interchangeable, and the appropriate circuit symbol is shown in Fig. 4(a). However it should be noted that this symbol is sometimes used for a non-symmetrical jugfet and one should not take too much for granted in this respect. Fig. 4(b) shows the symbol which is normally used for a non-symmetrical jugfet. Both Fig. 4(a) and 4(b) show n channel devices. The arrow on the gate electrode is reversed for p channel devices. The symbol commonly used for the mosfet is shown in Fig. 4(c), a fourth lead being attached to the substrate. Fig. 4(d) shows the

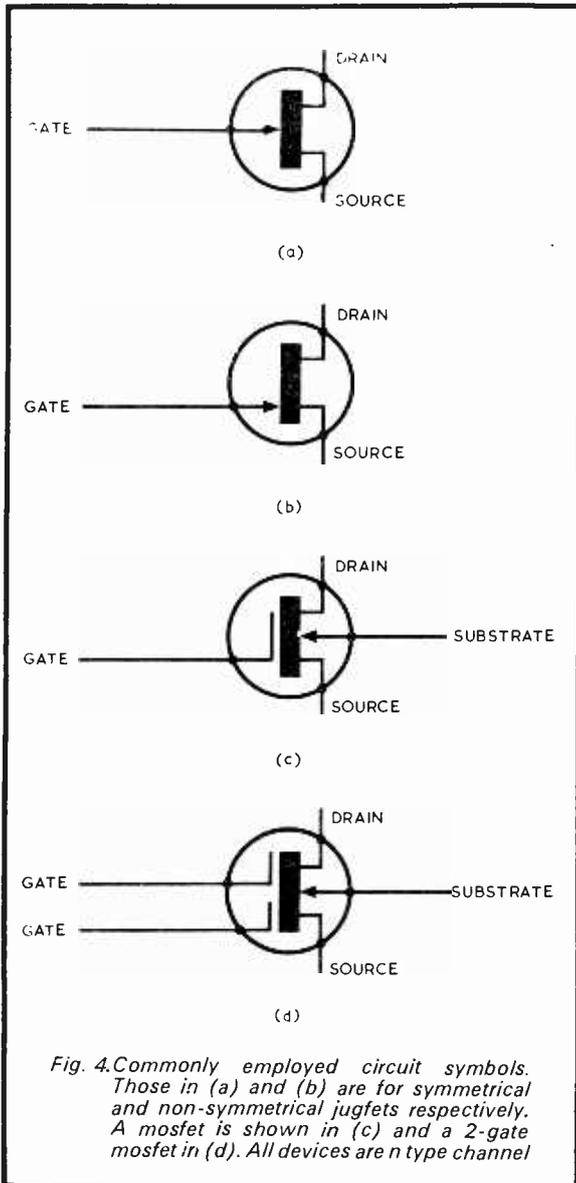


Fig. 4. Commonly employed circuit symbols. Those in (a) and (b) are for symmetrical and non-symmetrical jugfets respectively. A mosfet is shown in (c) and a 2-gate mosfet in (d). All devices are n type channel

symbol used for the dual gate mosfet, which has particular application in r.f. stages.

It should be realised that up to now we have been discussing the depletion layer type of jugfet. The depletion mosfet functions in the same manner as the depletion jugfet. A thin channel of n material appears between source and drain, and is affected by gate potential in the same way. However, using the mosfet technology it is also possible to produce an f.e.t. in which the channel is not present between source and drain until the appropriate gate bias is applied. This type of f.e.t. is called an enhancement device and has the useful property that it is normally non-conducting, i.e. with zero gate voltage no source-to-drain current flows. In fact it has to be turned on by the application of suitable gate bias. The main field of application is in the realms of logic circuitry because of the switch-like characteristics coupled with the fact that in manufacture many hundreds of these devices may be crammed onto a single chip of silicon. This means that complex functions such as large shift registers, which are encountered in computer engineering, may be built in a single package. Medium Scale Integration (M.S.I.) using bipolar transistors is, of course, already well established but mosfets offer the possibility of producing nearly all the electronics of say a digital voltmeter in a single multilead package. This is called Large Scale Integration (L.S.I.) and it is in this field where the enhancement mosfet is really coming into its own, but that's another story.

The proper symbol for the enhancement mosfet is shown in Fig. 5(a) and a simplified version of the same thing, which is commonly encountered, is shown in Fig. 5(b).

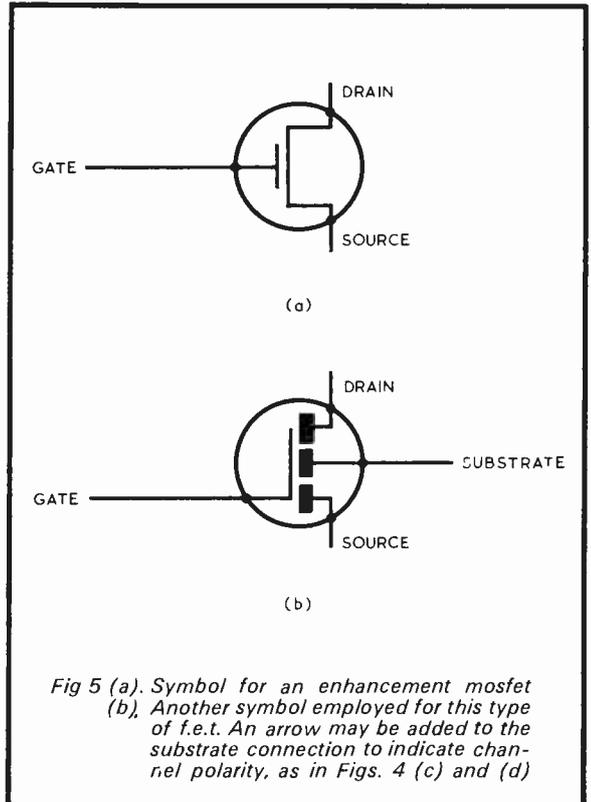


Fig 5 (a). Symbol for an enhancement mosfet (b). Another symbol employed for this type of f.e.t. An arrow may be added to the substrate connection to indicate channel polarity, as in Figs. 4 (c) and (d)

## SOME COMPARISONS

A lengthy discussion of the various attributes of the two basic types of f.e.t. and ordinary bipolar devices would be out of place but some important points must be brought out.

It has already been pointed out that the f.e.t. has a high input impedance which can be anything from 100 to 100,000 MΩ shunted by 1 to 10 pF. The f.e.t. has an output impedance similar to that of the bipolar transistor but, of course, the input impedance of the latter device is more typically 1kΩ shunted by a higher capacitance. For a typical jugfet type MPF105, an input capacitance of 4.5pF would be representative.

Looking at the mosfet we note that the device is capable of handling large positive and negative input swings without degradation of the input impedance due to diode current loading—this is very useful when a.g.c. is involved. Indeed the mosfet can offer a useful low noise amplification up to 250MHz. A typical R.C.A. device type 40603 has a 24dB power gain at 100MHz. The reverse transfer capacitance for a mosfet is typically 0.02pF compared with the jugfet 1.5pF. Because of these features, together with the advent of the dual-gate mosfet which features two separate channels each having an independent control gate, the mosfet is an attractive r.f. amplifier and mixer. Indeed the dual-gate device has applications as product detectors, balanced modulators and in colour demodulation circuitry, and as a bonus no neutralisation is required.

On a practical note, static charges produced when handling the device can cause permanent damage to the mosfet gate insulation although most modern devices have protection diodes connected to the gate to prevent damage.

We can see that mosfets are an attractive proposition to the designer of v.h.f. front ends and the like. Why do we not see the jugfet in common usage as a Class A low level amplifier more often than we do? If we consider a widely used jugfet such as the 2N3819, then without selection of devices one would have to compensate for a 10 to 1 variation in drain current which, with a self-biasing stage, is a bit tricky.

If we turn back to the jugfet's high input impedance, however, we find a very useful feature indeed. In general, with very large values of source resistance the noise performance of an f.e.t. can be better than that of a transistor. From this it will be realised that with transducers such as the ceramic or crystal pick-up type, the f.e.t. could offer some useful advantages.

Armed with this information we will look at a practical circuit for a buffer amplifier for use with a ceramic cartridge.

## PRACTICAL CIRCUIT

The simple circuit of Fig. 6 uses the jugfet in a source follower configuration which is similar in many ways to the emitter follower configuration given with bipolar transistors. The input impedance is substantially constant at 2MΩ from 15Hz to beyond 20KHz and the output impedance, with the 10μF coupling capacitor C2, is 500Ω at 1KHz. The voltage gain is just a little less than unity and the stage will handle signal swings of up to 2V peak to peak. The current consumption of the stage is some 1.5mA but will vary somewhat with individual f.e.t.'s dependent on manufacturing spreads.

The circuit is useful as a buffer stage between any high impedance transducer such as a crystal microphone


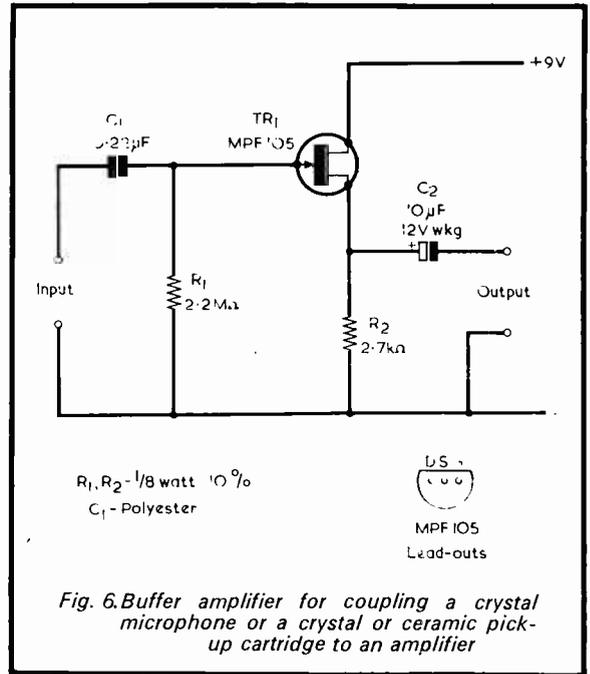


Fig. 6. Buffer amplifier for coupling a crystal microphone or a crystal or ceramic pick-up cartridge to an amplifier

or a ceramic cartridge. It is quite well known that these devices need to operate into a high impedance if the low frequency response is not to suffer. Because the circuit of Fig. 6 is so simple the entire array of components may be assembled in close proximity to the transducer; with a crystal microphone often within the case of the microphone itself. A simple Veroboard layout is shown in Fig. 7 and, as can be seen, using the 0.15 matrix board, the entire circuit less the battery only occupies a square inch or so.

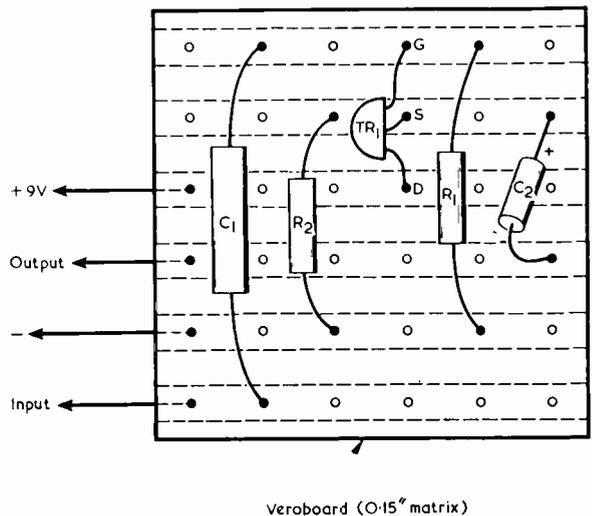

Veroboard (0.15" matrix)

Fig. 7. The components for the buffer amplifier may be mounted on a piece of Veroboard about 1 in. square. This diagram shows the component side of the board

The output impedance is low, as already stated, and therefore the output signal may be passed along quite a long length of cable without hum problems.

On a practical point, it should be noted that the usual heat shunt was applied when soldering the f.e.t. into circuit and, as an added precaution, the iron was unplugged from the mains supply to ensure that high static voltages were not inadvertently applied to the gate. This is a 'rather be safe than sorry' tactic and with jugsfets is usually unnecessary.

## DEPLETION LAYER

Before concluding, let us deal briefly with the all-important depletion layer, since this facet of transistor physics is not always fully understood.

What happens when p and n type materials are in close contact? If we take separate p and n type crystals and make their surfaces as flat as possible and then press them together the desired results expected of a p-n junction are not obtained. Instead both parts have to

be grown in one crystal and opposite impurities introduced so as to form zones with a junction between them. With no external connections made to the zones, electrons in the n zone cross the junction into the p zone, which is almost void of electrons. Similarly holes in the p zone diffuse into the n zone. Both of these migrations form a conventional positive current flow from p to n. A so-called 'potential barrier' is formed and a balance is established when the barrier is just sufficient to counteract the tendency to diffuse. The important bit is that we now discover that the migrating charges uncover, as it were, fixed ions—the atoms of impurities in the crystal lattice which have an electron each too many or too few. Therefore, at the junction a thin layer with fewer mobile charges than elsewhere exists. In consequence in the neighbourhood of the junction there is a small surplus of fixed charges which constitutes the depletion layer. In a conventional bipolar transistor the layer is only thousandths of a millimetre thick but in the f.e.t. it is the growth of this layer into the channel which gives the device its fundamental properties. ■

---

# SWITCH ABBREVIATIONS



There is, inevitably, a continual flow of newcomers to the hobby of radio construction, and it behoves the more experienced amongst us to do the courteous thing every now and again and explain points that to the initiated are obvious, but which are nevertheless very confusing for the novice.

One of the matters which perplex beginners has to do with the abbreviations employed for switches. These components are often referred to by the abbreviations 'd.p.s.t.' and the like, and for those who are not in the know these references can be mystifying, to say the least.

The four switch descriptions which are presented in abbreviated form are 's.p.s.t.', 's.p.d.t.', 'd.p.s.t.' and 'd.p.d.t.'. The letters 's.p.s.t.' stand for 'single-pole single-throw' and they refer to a switch which has two contacts only. On one position of the switch these contacts are open whilst on the other position of the switch they are closed. That simple on-off electric light switch on the wall is an s.p.s.t. switch.

The abbreviation 's.p.d.t.' means 'single-pole double-throw'. This applies to a switch whose arm (the moving contact) connects to one fixed contact in one position and to another fixed contact in the alternative position. A switch of this nature is also frequently described as a 'changeover' or 'c.o.' switch.

Some switches have two separate arms insulated from each other which move together as the switch is actuated, and these are the double-pole types. The contraction 'd.p.s.t.' stands for 'double-pole single-throw'. In one position the two arms connect to two separate fixed contacts whilst, in the other position, both sections of the switch are open. Finally, 'd.p.d.t.' refers to 'double-pole double-throw'. A d.p.d.t. switch is merely two s.p.d.t. switches ganged together, as it were.

These abbreviations are normally applied only to toggle and slide switches. They may occasionally be applied to simple 2-position rotary switches if these carry out the corresponding switching action. Normally, however, rotary switches offer more

complex functions, and these are referred to by such terms as '3-pole 4-way' and so on. A 3-pole 4-way rotary switch has 3 moving arms and 4 positions.

A very popular type of switch is the miniature rotary model having 12 fixed contacts. These switches are mass-produced and individual versions have variations in the moving arm section and in the stop mechanism which limits spindle rotation. All versions of the switch have the 12 fixed contacts, whereupon the switches are made up to employ all these and are available as 1-pole 12-way, 2-pole 6-way, 3-pole 4-way and 4-pole 3-way. Because of their low price it is often economic to employ miniature rotary switches in circuits where not all the poles (or arms) are used. Thus, if one required a 2-pole 4-way switch, one could use a 3-pole 4-way miniature rotary switch and merely make connections to two of the poles and their fixed contacts only. The remaining pole and fixed contacts are simply ignored. ■

## P.C.B. MARKING PENS


Decon Dalo P.C.B. Marking Pens, until now sold in dozens, and therefore restricted more to the larger electronics companies, are now available in half-dozens and single units, making them ideal for the smaller engineering department and laboratory engaged in small-scale and prototype p.c.b. production, and for the home amateur.

Model 33PC is a nylon-tipped marker pen that applies an etch-resist ink to copper laminated board, in line thicknesses down to  $\frac{1}{32}$  in. A spare nylon tip in the body of the pen can be trimmed by blade for even finer work. The attractive point about this method of working is the time and trouble it saves – no masking or taping is necessary. Simply draw the desired circuit, and after a few minutes drying time the ink tracks are impervious to ferric chloride and all normal etchant solutions.

The new small-quantity prices are £3.85 including postage for a box of six pens; £1.00 post-paid for single orders (cash with orders for one-off). Decon will quote separately for larger orders and can now arrange to print customers' own names on the pen barrel, making them an ideal agency line or Christmas gift. Details from Decon Laboratories Ltd., Ellen Street, Portslade, Brighton, BN4 1EQ.


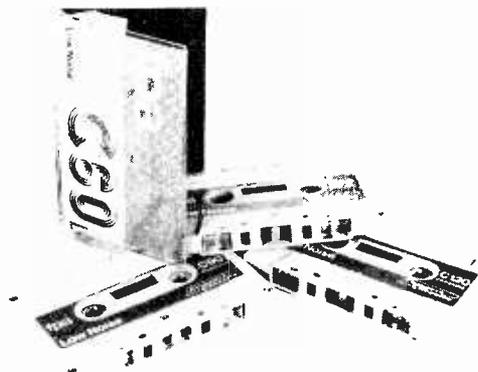
## DEMAND FOR NEW BRAND OF COMPACT CASSETTES



Fraser Peacock Associates Limited, the Wimbledon based audio-visual organisation have announced that demand for the range of compact cassettes which the company launched three months ago has "exceeded everyone's most optimistic forecasts".

The cassettes are available in 60, 90 and 120 minute versions.

David Tuckman, a director of Fraser Peacock Associates, said: "It was a logical development for us to go into our own brand compact cassettes since an increasing part of our business over the last few months has been in the tape duplicating field. Our cassettes do have a tremendous price advantage, and they are also fully guaranteed".

## ELECTRONICS KIT FOR STUDENTS

Limrose Electronics have announced their new Electronics Kit which has been specially developed to meet the requirements of the Nuffield 'A' Level Physics course.

The kit consists of a number of modules which can be plugged into each other in any order and carry their own power rails. Some of the modules can accept other modules in both directions which is particularly useful in setting up large experiments. Electronic components are mounted on the front panel so that students can see how the circuits they are using have been constructed. The modules can be supplied either in kit form or fully assembled. The modules are housed in sturdy wooden cabinets and are robust enough to withstand considerable misuse both electrically and mechanically.


All modules measure 124mm x 124 mm x 50mm and require 4mm patch leads for making interconnections.

In addition to the Basic Unit, Lamp Indicator, Switch (contact-bounce free), AND Gate, Multivibrator, Bistable and Beam Splitter Modules required to make up the Nuffield Starting and Working Kits, a number of extension modules such as Digital Readout, Triple

Lamp and Binary Counter are available.


Prices are from £2.00 for the Lamp Indicator module to £7.50 for the Digital Readout module in kit form.

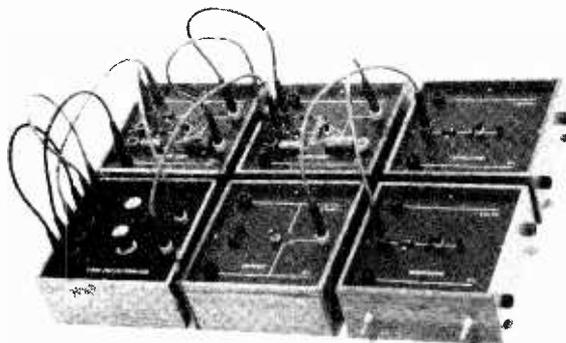Further information from Limrose Electronics Limited, 8-10 Kingsway, Altrincham, Cheshire, WA14 1PJ.



# D.C. VOLTMETER

by G. A. FRENCH

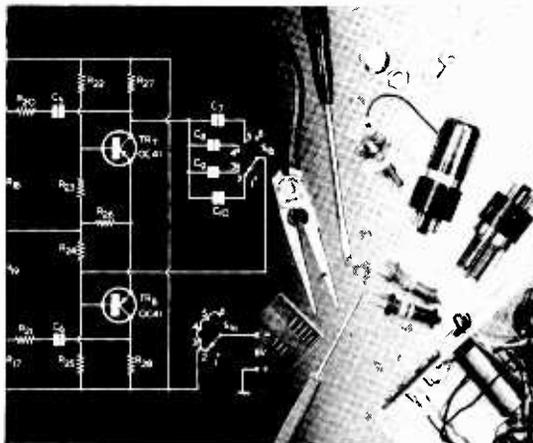

THE DEVICE WHICH FORMS THE subject of this month's 'Suggested Circuit' article is a d.c. voltmeter having a sensitivity of  $200k\Omega$  per volt. This is, of course, a much higher sensitivity than is provided by a standard testmeter, and it corresponds to a current, at full-scale deflection, of  $5\mu A$ . A feature of the circuit is that it can be made up, in one version, with standard 5% resistors in the input section. It incorporates a readily obtainable integrated circuit operational amplifier.

## CIRCUIT PRINCIPLE

To appreciate the basic manner in which the voltmeter functions it will be helpful to commence by examining Fig. 1(a). This diagram shows an operational amplifier, depicted by the triangle, with connections applied to it under theoretical conditions. The inverting input is identified by a minus sign and the non-inverting input by a plus sign, whilst the output appears at the right-hand apex of the triangle.  $R_2$  is a resistor applying negative feedback to the inverting input of the op-amp and  $R_1$  is a resistor in series between this inverting input and the input to the complete circuit. It is assumed that the source of input voltage has zero internal resistance. Under these conditions the voltage gain offered by the complete circuit is  $R_2$  divided by  $R_1$ .

In Fig. 1(b) we use the circuit of Fig. 1(a) to function as a voltmeter. Across the output from the op-amp is connected a current reading meter in series with a pre-set variable resistor, the pre-set resistor being set up such that the meter reads full-scale deflection when the voltage at the op-amp output is 1 volt.  $R_2$  and  $R_1$  are given the values shown. Since both these resistors have the same value,  $R_2$  divided by  $R_1$  becomes equal to unity, and the voltage gain of the complete circuit is similarly unity. If, therefore,

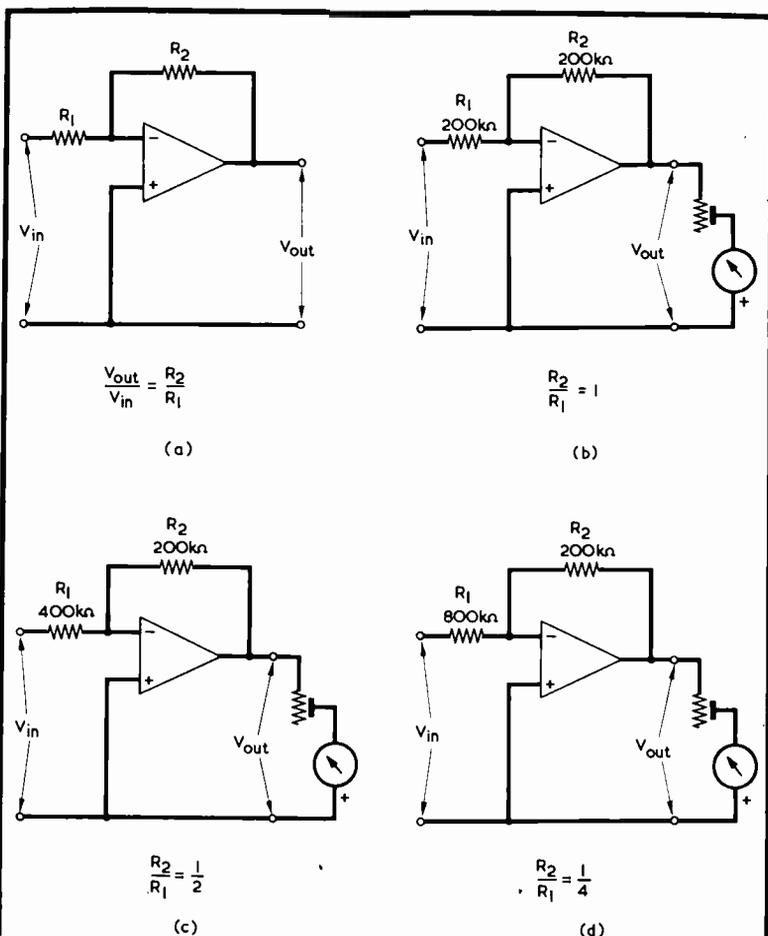


Fig. 1 (a). Basic operational amplifier circuit with feedback  
 (b). Amplifier circuit offering a voltage gain of unity  
 (c). An amplifier whose voltage gain is one-half  
 (d). Here, the voltage gain is one-quarter

we apply a voltage of 1 volt to the input, the output will also be 1 volt, and the meter will read full-scale deflection. The polarity of the input voltage is such that the upper input point is positive. Since this point is coupled to the inverting input of the op-amp, the op-amp output will be negative. This output polarity corresponds with the polarity ascribed to the meter in Fig. 1(b).

We turn next to Fig. 1(c), in which the conditions are the same as before, except that R1 has been increased to 400k $\Omega$ . R2 divided by R1 and, hence, the voltage gain of the circuit, is now one-half, and it follows that an input voltage of 2 volts will cause an f.s.d. reading to be given in the meter. In Fig. 1(d) R1 is increased to 800k $\Omega$ , whereupon the gain of the complete circuit becomes equal to one-quarter. The input voltage which produces f.s.d. in the meter is now 4 volts.

It will be obvious that we have, in Figs. 1(b), (c) and (d), an embryo

voltmeter having a sensitivity of 200k $\Omega$  per volt. As has been demonstrated, the voltmeter is capable of giving an f.s.d. reading for any input voltage provided that the value of R1, in kilohms, is 200 times that voltage. A further point which may now be taken into consideration is that the inverting input of the op-amp is a 'virtual earth', since its potential varies by a negligible amount despite large shifts in the input voltage applied to the complete circuit. The circuit becomes, in consequence, a true voltmeter because the right hand end of R1 terminates in a point which is, to all intents and purposes, connected to the lower input terminal by zero resistance. The circuit responds, nevertheless, to the current which flows in R1, and this current is the applied voltage divided by R1.

It is assumed here that, for zero input and zero output voltage, the inverting input of the op-amp is at the same potential as the non-inverting input. In practice there is a small offset voltage but, with the integrated circuit which is employed in the practical version, this is of the order of a few millivolts only, and should not noticeably influence circuit operation.

Brief mention of a minor point of detail may be included here for the benefit of newcomers to voltmeters of this nature. It was said, when Fig. 1(d) was discussed, that an applied voltage of 4 volts results in an f.s.d. reading in the meter. An input voltage of 2 volts will result in a half f.s.d. reading, and an input voltage of 1 volt will give a reading of a quarter of f.s.d. Thus, the arrangement of Fig. 1(d) is capable of measuring all voltages up to 4 volts. Similarly, the arrangement of Fig. 1(c) can measure voltages up to 2 volts and that of Fig. 1(b) voltages up to 1 volt.

Returning to the main theme, we may next consider R2. At first sight it might appear that this needs to be a close tolerance component, but such is not the case and a standard 5% resistor will be quite suitable here. If the resistor employed happens to be, say, on the upper limit of its tolerance, at 210k $\Omega$ , all the gain figures shown in Figs. 1(b), (c) and (d) become multiplied by a factor of 210 divided by 200. This discrepancy is taken up, quite simply, by adjusting the variable resistor in series with the meter accordingly. The variable resistor now becomes a 'Calibrate' component. The circuit of Fig. 1(b) could then be used to set it up, a known voltage of 1 volt being applied to the input of the complete circuit and the variable resistor then adjusted to give an f.s.d. reading in the meter. The circuit will still, under these circumstances, give its 200k $\Omega$  per volt performance. It is possible, even, to dispense with close tolerance resistors in the R1 position, the variable resistor in series with the meter being again adjusted to take up any discrepancies introduced thereby. This point is discussed at the end of the article, when a second version of the input circuit is discussed.


A final design point is concerned with that fact that it has been assumed up to now that the device, functioning as a voltmeter, gives an f.s.d. reading in the meter when the output voltage from the op-amp is nominally 1 volt. This assists in the explanation because it enables simple figures to be employed. But it would be possible to adjust the variable resistor in series with the meter to a setting which gave an f.s.d. reading for 0.5 volt, 2 volts, 5 volts or any other voltage, within reason, at the output of the op-amp. The complete circuit would still be capable of functioning as a voltmeter although, of course, it would then be necessary to recalculate the value of R2 to obtain an input sensitivity figure of 200k $\Omega$  per volt. It so happens, however, that in addition to easing the description of circuit operation, the nominal 1 volt figure represents a satisfactory practical value to work to, and it also enables a simple meter protection circuit incorporating two silicon diodes to be employed.

## WORKING CIRCUIT

The full working circuit of the voltmeter is given in Fig. 2. In this diagram R1 of Fig. 1 is replaced by whichever of R1 to R4 is switched in by the Range switch S1. R2 of Fig. 1 reappears in Fig. 2 as R7. The pre-set variable resistor and meter are now given by VR2, R8, R9 and M1. The two silicon diodes just mentioned are D1 and D2.

The integrated circuit is an ML741C and the numbers around its outline correspond to the 14 pin dual-in-line tag layout shown in the inset. Pin 4 of the i.c. is the inverting input and pin 5 the non-inverting input. Pin 11 is the connection for the positive supply and pin 6 is the connection for the negative supply. The similarity with Fig. 1 becomes very noticeable when it is remembered that the only major change introduced in Fig. 2 is the introduction of the battery supply which, of course, the i.c. must have in any case if it is to operate. The non-inverting input at pin 5 is not now returned to the 'zero line' as in Fig. 1, but to the potentiometer given by R5, VR1 and R6 connected across the supply lines. VR1 is the Set Zero control and it is adjusted for a zero reading in the meter when there is no input voltage at the test terminals, thereby causing the circuit to be balanced and taking up such things as differences in the voltages of the two batteries.

S1 provides four ranges, these being 0-1V, 0-2.5V, 0-10V and 0-25V. The corresponding series input resistors have values of 200k $\Omega$ , 500k $\Omega$ , 2M $\Omega$  and 5M $\Omega$  respectively. These values are each 200k $\Omega$  multiplied by the f.s.d. voltage figure of the corresponding range. Should it be desired to have ranges in the series 0-1V, 0-3V, 0-10V, etc., the series resistor for the 0-3V

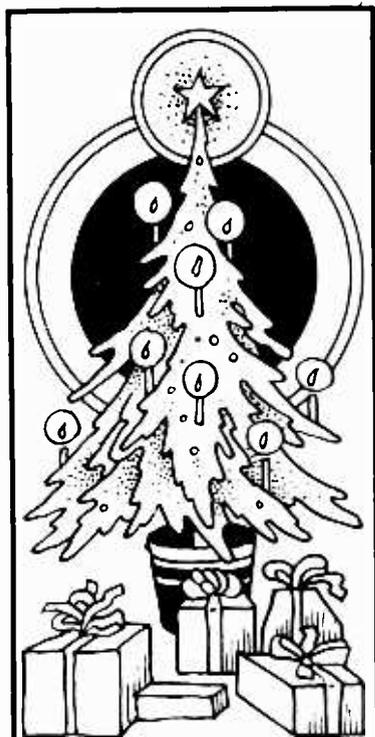

*We wish all our readers a very Happy Christmas and a Prosperous New Year*

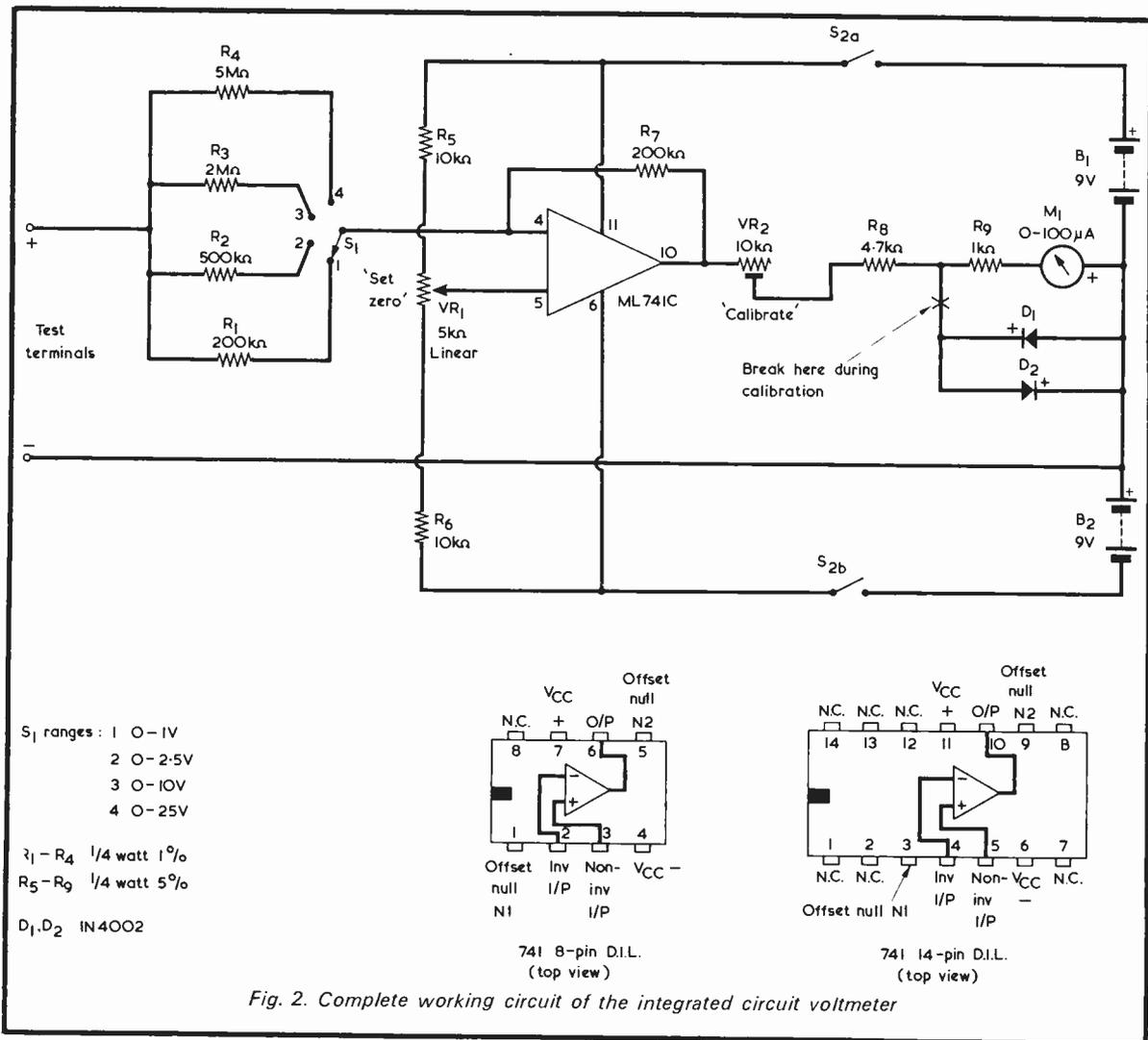


Fig. 2. Complete working circuit of the integrated circuit voltmeter

range would be 600kΩ. Any other ranges within reason can be incorporated by employing the appropriate multiplying factor for the series resistance required. In this version of the input switching circuit the series resistors should all have a tolerance of 1%.

In the meter section, diodes D1 and D2 provide protection when the voltage across the meter and R9 approaches the voltage at which forward conduction in the diodes takes place.

The ML741C integrated circuit was obtained from Henry's Radio, Ltd., by which firm it is advertised as a '741C (DIL)'. This i.c. has the 14 pin dual-in-line pin configuration shown, the rectangular identifying point between pins 1 and 14 being replaced by a paint dot. Other integrated circuits of the 741 type, such as SN72741, μA741, etc., could be employed instead, but it should be mentioned that the author

has only checked the circuit with the i.c. obtained from Henry's Radio. Some versions of the 741 are available in 8 pin d.i.l. and the tag layout of this type is included in Fig. 2. Note that both tag layouts are top views, with the pins pointing away from the reader.

The 741 is a development from the earlier 709 op-amp, and it is a particularly useful i.c. for amateur experimental and constructional projects since it has its own internal compensation and does not require any external capacitors to maintain stability. ('Compensation' defines the process where capacitance is employed to prevent instability in an i.c. due to excessive amplification at high frequencies). As will be seen from Fig. 2 it is necessary to make only five connections to the i.c. Also, the only components external to the i.c. are those which are directly involved in voltmeter operation. It is, incidentally, possible to obtain fine control of offset voltage by suitably

connecting a potentiometer to the two 'offset null' pins, but this is not needed in the present design and no connections are made to these pins.

## COMPONENTS AND CONSTRUCTION

Of the components, the series input resistors and the integrated circuit have already been discussed. VR1 is a panel-mounted potentiometer, whilst VR2 is a pre-set skeleton component. S2(a) (b) should be a double-pole toggle switch. The current drawn from each battery is 2mA only, and any small 9 volt batteries can be employed. They should be of the same type and both should be discarded at the same time when exhausted. The voltmeter should not be operated with one battery new and the other nearly exhausted. Diodes D1 and D2 can be any small silicon diodes or rectifiers. The author employed IN4002's, which happened

to be on hand.

All the components may be housed in a small case with VR1, S1, S2, M1 and the test terminals on the front panel. Wiring layout is not critical provided that R7 is fitted close to the i.c., and the i.c. output lead does not too closely approach the wiring to the two i.c. inputs. The connection between the junction of R8 and R9 and the junction of the positive lead-out of D1 and the negative lead-out of D2 should be of a temporary nature, as it is broken during the process of calibration. The author found it helpful to employ a d.i.l. holder for the i.c., wiring this up first and then inserting the i.c.

Calibration of the completed unit consists of checking it against another voltmeter, using the method shown in Fig. 3. In this diagram, the potentiometer should have a value which causes some 5 to 10mA to flow through its track. Thus, with a 12 volt battery the potentiometer could have a value of 2k $\Omega$ . Any suitable range is selected by S1 and the i.c. voltmeter is then switched on with VR1 slider at mid-track. VR1 is next adjusted for zero reading in the meter with the two test terminals short-circuited. The test terminals of the i.c. are then applied to the potentiometer shown in Fig. 3, after which that potentiometer is adjusted to give the f.s.d. value of the range selected, as indicated by the monitoring voltmeter. VR2 is then adjusted for f.s.d. in the i.c. voltmeter. After one range has been set up in this manner, all the other ranges will be correct.

Next, the i.c. voltmeter is switched off and D1 and D2 are disconnected from R9 and M1 as indicated in Fig. 2. The i.c. voltmeter is then switched on again. If the meter gives the same reading as before, all is well, and no further action is required other than the permanent connection of D1 and D2 into the circuit. If on the other hand, the meter gives a higher reading with D1 and D2 disconnected, the value of R9 will have to be reduced experimentally until D1 and D2 have no effect on meter reading. Each change in the value of R9 necessitates a re-setting of VR2. The check with D1

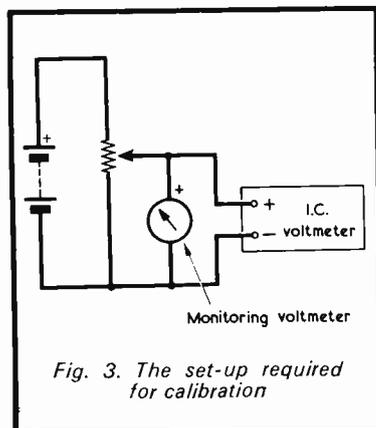


Fig. 3. The set-up required for calibration

and D2 is desirable because a few 0-100 $\mu$ A meters have relatively high internal resistance, and the voltage dropped across the meter and R1 may conceivably just fall within the level at which some diodes commence to pass forward current. It is improbable that this effect will be present in most units made up to the circuit, but it is worthwhile carrying out the check nevertheless.

#### ALTERNATIVE INPUT CIRCUIT

As was mentioned earlier, it is possible to dispense with close tolerance resistors in the input circuit, as discrepancies from the nominal resistance can be taken up by adjustment of the Calibrate potentiometer, VR2. An alternative input circuit employing 5% fixed resistors is illustrated in Fig. 4. The three pre-set potentiometers in this circuit may all be skeleton types.

The circuit of Fig. 4 is set up by

voltage range, since this means that the pre-set potentiometers will then, assuming a reasonable choice of ranges, be required to have values of 1M $\Omega$  or less.

It should be mentioned that it may be a little difficult to obtain close tolerance 1% resistors having values higher than 1M $\Omega$ , whereupon some of the resistors in the input circuit of Fig. 2 will need to be made up of a number of single close tolerance resistors in series. The alternative input circuit of Fig. 4 may, in consequence, be more attractive than that of Fig. 2, even though it does require three pre-set potentiometers.

The experienced constructor with a good stock of resistors may be able to make up the lower range series resistors in Fig. 4 by experimental selection, if necessary 'trimming up' individual resistances by inserting small value resistors in series. This process dispenses with the pre-set potentiometers.

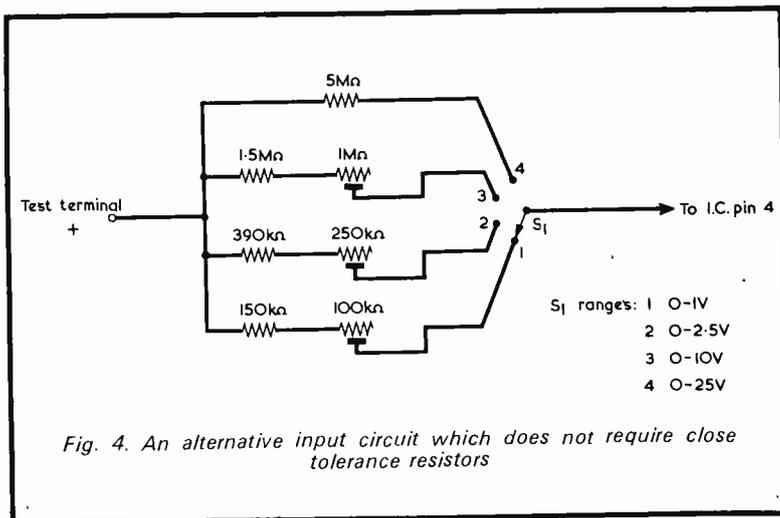


Fig. 4. An alternative input circuit which does not require close tolerance resistors

selecting Range 4 and connecting the unit to a source of voltage, monitored by another voltmeter as in Fig. 3, which is equal to f.s.d. value (i.e. 25V) on this range. VR2 is then set up for full-scale deflection in the meter. The test voltage is then reduced to the f.s.d. value for Range 3. Range 3 is selected, and the pre-set potentiometer in the Range 3 input circuit adjusted for an f.s.d. reading. The process is repeated with Range 2 and Range 1, after which the setting of the voltmeter is complete.

With the input circuit of Fig. 4, the input resistance of the i.c. voltmeter is not exactly 200k $\Omega$  per volt but only nominally so. If it should happen that the 5M $\Omega$  resistor is on the lower limit of its tolerance, at -5%, then the input resistance is 200k $\Omega$  - 5% per volt.

If ranges other than those shown in Fig. 4 are to be used, the values shown in this diagram may be changed accordingly. The single fixed series resistor in the input circuit should be that which is selected on the highest

#### RESULTS WITH THE PROTOTYPE

The prototype circuit gave an acceptable performance with good linearity over each range. It was found that the Zero Set control did not have to be re-set frequently, this being particularly the case when the batteries had settled down to a steady voltage, as opposed to the high voltage given in the brand-new state. Although it is preferable to have the test terminals short-circuited when adjusting the Zero Set control, it was found that this was not essential and that the meter reading remained at zero after the short-circuit had been removed. This indicates a high level of basic stability in the circuit, a factor which is not always evident in what are sometimes described as 'electronic voltmeters'.

As was stated earlier, the current drawn from each battery was 2mA only.

# NEWS . . . AND .

## EMI LOCIC PROBE CHOSEN AS STANDARD TEST DEVICE FOR

### ROYAL NAVY USE



The LP 500/1 probe is pictured here in use during final testing of the data processing units at the division's Hayes, Middlesex, plant.

Following its introduction 18 months ago, EMI's 5 volt logic probe – the type LP.500/1 – has now entered service with the Royal Navy under NATO number 6625-99-119-2584. The probe has been specified as standard test equipment for use with data processing equipment fitted in RN ships.

Both the probes and data processing units are being manufactured by EMI Electronics' Radar & Equipment Division, Hayes, Middlesex, and form part of a special purpose range of equipment covered by contracts with EMI totalling over £1 million.

Designed for testing DTL and TTL circuitry, the LP.500/1 probe can detect seven different types of logic signal, including the important 'open circuit' condition, which are identified by the lighting sequence of the probe's opal lame. The 18cm long device enables rapid functional tests to be carried out without the need for expensive test equipment such as

oscilloscopes. In many instances, the probe can be used to trace faults in less time than by employing an oscilloscope.

The EMI probe distinguishes between logic 1, logic 0, open circuit, +ve going pulses, -ve going pulses, square waves below 1MHz approx and pulse trains (including square waves) with a pulse recurrence frequency above 1MHz approx. It can be powered by the equipment under test, from a 4.5V battery or from a standard bench power supply.

To check that the probe is operating correctly, the 'open circuit' indication – a steady light for a.c. mode and a flashing light for d.c. – remains on until effective contact is made with the circuit under test. The device is protected against overload from input voltages up to  $\pm 100V$  and no damage can result from supply polarity reversal.

## NEW SOUND LEVEL METER

A Code of Practice for reducing the exposure of employed persons to noise has recently been announced by the Department of Employment.


To coincide with this important publication, which affects every noisy factory and office in the country, Dawe Instruments Limited, the leading British Manufacturer of noise measuring equipment, announce a new instrument, the Type 1405C Sound Level Meter, as a further addition to the already established and widely accepted Dawe range.

The Sound Level Meter Type 1405C provides a direct reading of sound level over the range 34dB to 130dB(A). The instrument consists of a ceramic microphone, weighting network, attenuators, high-gain amplifier, and an indicating meter. The highly stable and robust microphone is substantially non-directional; ageing and temperature effects are negligible.

The internationally standardised A-weighting frequency response is used because it provides measurements which correlate best with subjective noise ratings and is widely recommended for measurements relevant to hearing conservation and noise annoyance checks.

The instrument is battery powered, giving a typical operational life of 80 hours. The complete unit, with

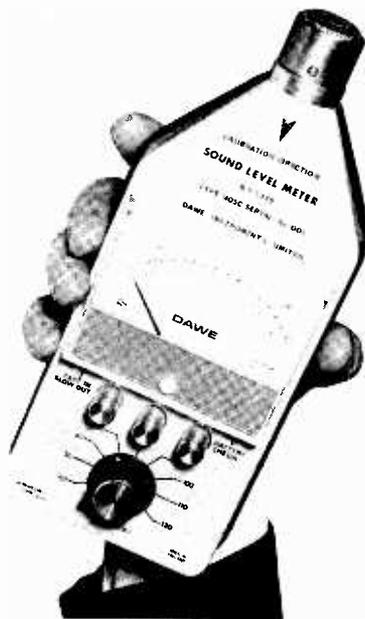battery, weighs less than 2lb and may be easily held in one hand. A carrying case is available as an optional extra.



## IEE TRAVELLING SCHOLARSHIP

An IEEE travelling scholarship of £300 is offered for visit(s) to foreign electrical or electronic research or manufacturing establishments by a postgraduate student.

The purpose is to promote an exchange of research and technological ideas and to foster a closer relationship between young engineers in different countries.

Candidates must submit a programme for their visit(s) by 31st December 1972, and the award will be made to the candidate whose programme is judged most likely to promote the objects of the scholarship.

The scholarship is financed by the UK and Republic of Ireland Section of the Institute of Electrical and Electronics Engineers, which is acting in collaboration with the Institution of Electrical Engineers and the Institution of Electronic and Radio Engineers. Entrants must be Student or Graduate Members of one of these three institutions.

Further information and entry forms from:

Prof. C. W. Turner  
Dept. of Electrical & Electronic Engineering

King's College  
Strand  
London WC2R 2LS.

RADIO & ELECTRONICS CONSTRUCTOR

# COMMENT

## ELECTROVALUE EXPANDS

David Longland started Electrovalue seven years ago, running his business from his home in Ascot. Before long he moved to comparatively larger premises, where in a partitioned off corner of somebody else's workshop, he took on staff and produced his first catalogue. Business increased and when a butcher's shop in Englefield Green became vacant, he moved in. More staff was taken on, and a teleprinter and a microfilm system were then installed. Now orders are individually microfilmed and the customer's original order returned with the goods for him to check for himself.

Electrovalue next installed an elaborately programmed full-size computer, programmed to provide stock control and processing information for instant stock position details and

forecasting forward renewal requirements. Now with Electrovalue's latest catalogue packed with thousands of different items, the computer's services have become vital.

Electrovalue's latest 96 page catalogue, No. 6 already in its 3rd printing, is typical of the thoroughness with which the company operates. It includes I.C. circuit and connection diagrams, semi-conductor outlines and considerable technical information, it is a most useful handbook for the home constructor as well as full time electronics worker; the catalogue now includes a purchase refund voucher for the 25p it costs to buy. Everything is brand new and sold in accordance with manufacturers' specifications.

Today, Electrovalue service customers all over the world, and behind the



facade of what appears to be a little village shop at 28 St. Judes Road, Englefield Green, Egham, TW20 0HB, is a complex specialist organisation geared, by use of some of today's most modern methods, to give good service to everyone.

## UK 2M BAND PLAN

A special meeting of the RSGB VHF Committee was held on 11th October at which *The Short Wave Magazine* and the RSGB Raynet and Mobile committees were represented.

Subject to the approval of Council of RSGB, it was agreed to recommend that the following band plan be adopted:

(a) the existing UK 2M band plan as published should be retained i.e. with specified geographical Zones and Mode frequencies.

(b) the following FM channels should be added to the band plan:

Zone A	FM Working	144.40 MHz
Zone B	FM Working	144.80 MHz
Zone C	FM Working	145.20 MHz
Zone D	FM Working	145.60 MHz
FM Calling - National		144.48 MHz

It was agreed to leave open the question of repeater channels until the end of the one-year experimental period with GB3PI currently operating on 145.15/145.75 MHz in conformity with the Region 1 Band Plan.

Those who have submitted views to the Committee are thanked for their valuable contributions. These were used as the basis of the discussion.


## QUOTE

"The BBC is an institution - a great institution, which can still to-day both inspire deep loyalty and provoke strong criticism. It has moved a long way from 'the Reith Era', 'the Golden Age of Radio' and the days of 'Auntie'. It has even moved on from pastures 'greene' and is tackling new horizons in this immensely challenging age." — Sir John Eden

DECEMBER 1972
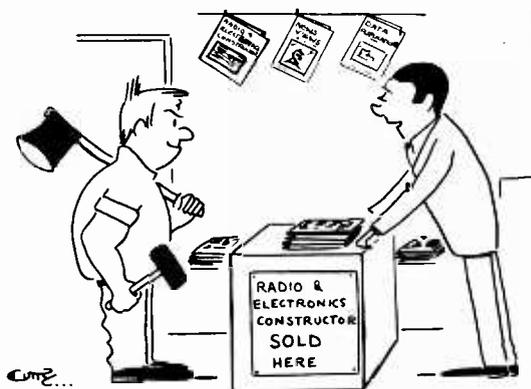
## IN BRIEF

- A new "Guide to Enthoven Solders & Fluxes" is now available upon application, from Enthoven Solders Ltd., Dominion Buildings, South Place, London, EC2M 2RE. It is designed as a "Pocket Guide" for research and production engineers.
- Following full stability tests, the Post Office has accepted the Ferranti microwave telecommunications equipment linking the Isles of Scilly with the mainland.
- Levell Electronics Ltd of Moxon Street, Barnet, Herts, have added to their range of portable electronic instruments a D.C. Microvoltmeter type TM10.
- A.P.T. Electronic Industries Ltd, of Byfleet, Surrey, have produced a two-page leaflet on their new TRU range of d.c. power supplies.
- A new inexpensive magnetron announced by Mullard has been developed for use in low-cost, small-boat radar equipment. Type YJ1390, it operates with a low anode voltage of only 2kV.



No Sir, as far as I know there is no publication called Radio & Electronics Destructor

# HIGH-GAIN SILICON REFLEX RECEIVER

by  
G. W. Short

**A sensitive 2-transistor receiver which requires few components and which can be adapted for a wide range of speaker impedances and battery voltages.**

**A** FEW YEARS AGO THE 'RADIO CONSTRUCTOR' PUBLISHED the writer's design for a simple but effective reflex t.r.f. receiver using silicon planar transistors. This proved to be a reliable circuit with a good performance. Several modifications have appeared, including a low-consumption version for use with a crystal earpiece and a version with an f.e.t. input stage.\*

The receiver described here is a new and improved version of the original circuit. Like the original, it has been kept very simple and straightforward. Nevertheless, it has proved possible to obtain a very useful increase in r.f. gain, and to provide enough audio output for low-volume loudspeaker listening indoors. The new circuit works from a 3 volt battery and is easily adapted to other voltages.

## CIRCUIT DETAILS

Referring now to the circuit diagram, which is shown in Fig. 1, the heart of the receiver is a 2-stage amplifier with direct coupling between stages and d.c. negative voltage feedback to stabilize the operating conditions of the two transistors. Each transistor operates as a common-emitter amplifier to both a.f. and r.f. signals, giving very high overall gain.

R.F. signals picked up by the ferrite rod aerial L1 are

stepped down and applied to the base of TR1 via L2, whose lower end, in the circuit diagram, is earthed to r.f. by C2. At the output of the 2-stage amplifier the r.f. signals are picked out and stepped up in voltage by an r.f. transformer (L3, L4) and applied to the detector D1, this being a point-contact germanium diode. The audio signals which appear across the detector load R4 (which is also the volume control) are fed back to TR1 and are then amplified by both transistors before application to the directly driven 75Ω loudspeaker.

A d.c. bias is applied to the diode by R5, which bleeds a little of the emitter current of TR2. Negative feedback at d.c. is taken via R4 from the emitter of TR2 to the base of TR1.

## CONSTRUCTION

There is nothing special about the ferrite rod aerial and tuning capacitor C1. The prototype employed a 300pF Jackson Bros. 'Dilemin' tuning capacitor. This covers the medium wave band when L1 consists of about 70 turns of 5/46 litz wire close-wound on a paper former at the centre of a 4in. by 3/8in. ferrite rod. The secondary winding has 4 turns of insulated wire wound over the earthy end of L1. The precise gauge of wire is not important. (A suitable rod is available from Amatronix Ltd., 396 Selsdon Road, S. Croydon, Surrey, CR2 0DE. The same company also stocks wound rods to suit a 300pF tuning capacitance, but the secondary has too many turns for this receiver and six turns should be removed.)

The r.f. transformer L3, L4 is made by winding 50 turns of 32 s.w.g. enamelled, silk or cotton insulated wire on top of the existing winding of a 2.5mH r.f. choke,

RADIO & ELECTRONICS CONSTRUCTOR

\* G. W. Short, "Silicon Transistor Reflex T.R.F.", *The Radio Constructor*, January 1968; G. W. Short, "Milliwatt' Silicon Reflex T.R.F. Receiver", *The Radio Constructor*, September 1969; A. W. Whittington, "F.E.T. Reflex Receiver", *The Radio Constructor*, August 1971.

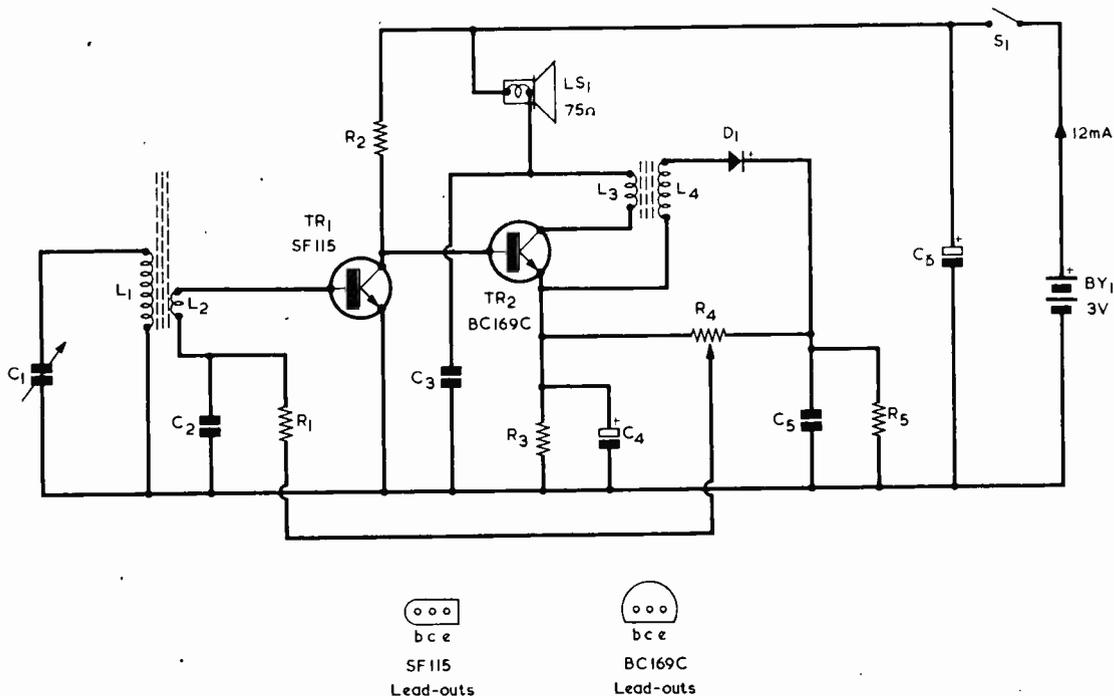


Fig. 1. The circuit of the high-gain silicon reflex receiver

## COMPONENTS

### Resistors

(All fixed values  $\frac{1}{10}$  watt 10%)

R1	3.3k $\Omega$
R2	1.2k $\Omega$
R3	68 $\Omega$
R4	10k $\Omega$ potentiometer, log track
R5	22k $\Omega$

### Capacitors

C1	Tuning capacitor, to suit L1 (see text)
C2	0.1 $\mu$ F
C3	0.1 $\mu$ F (see text)
C4	320 $\mu$ F electrolytic, 2.5 V.W/kg.
C5	0.01 $\mu$ F
C6	125 $\mu$ F electrolytic, 4 V.W/kg. (see text)

### Inductors

L1, L2	Windings on 4in. $\times$ $\frac{3}{8}$ in. ferrite rod (see text)
L3	Overwind on L4 (see text)
L4	R.F. choke type CH1 (Repanco)

### Switch

S1	s.p.s.t. switch (may be ganged with R4)
----	---

### Semiconductors

TR1	SF115
TR2	BC169C
D1	OA90

### Loudspeaker

LS1	75 $\Omega$ approx. (see text)
-----	--------------------------------

### Battery

BY1	3 volt battery
-----	----------------

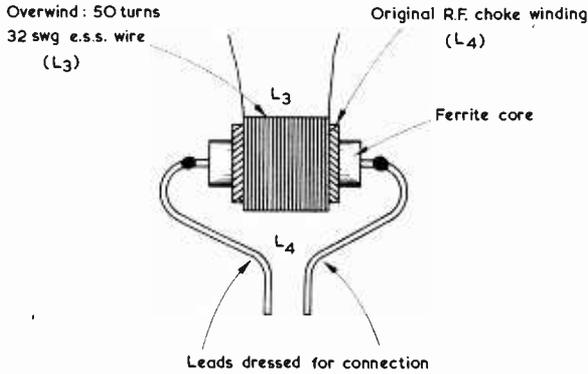


Fig. 2. Making up the r.f. transformer. L<sub>3</sub>, L<sub>4</sub>

Repenco type CH1. See Fig. 2. Do not use a different kind of choke – it may not be suitable for the present purpose. The gauge of wire used for the added 50-turn winding is not important and any moderately fine insulated wire may be used. The winding may be 'scramble-wound'.

A wiring diagram is given in Fig. 3. Apart from L<sub>1</sub>, L<sub>2</sub>, all the components may be fitted to a small piece of insulating material fitted with a front panel, on which are mounted C<sub>1</sub>, R<sub>4</sub> and S<sub>1</sub>. The components may be anchored to metal pins or tags at the positions indicated. For clarity, the transistors are omitted. The layout of the circuit should follow the circuit diagram and it is most important, in view of the high r.f. gain, to keep the output clear of the input or else screen the relevant portions.

A convenient means of providing the 3 volt supply consists of employing an Eagle battery holder type BH2, in which are fitted two U7 cells.

## OVERCOMING INSTABILITY

The receiver is wide open to two quite distinct forms of instability, fortunately both easily cured. First, there is a chance that a.f. will break through the r.f. transformer and set up a continuous howl. This is cured, if it occurs, by reversing the connections to L<sub>3</sub>. Secondly, it is inevitable, unless the r.f. transformer is put into a screening box, that it will couple with the ferrite aerial. This may cause positive feedback and instability or negative feedback and loss of sensitivity, depending on the winding directions. To minimise such undesirable interactions, the transformer should be kept as far away from the rod as possible, and it should be so oriented that the ferrite core of the CH1 choke is pointing broadside off to L<sub>1</sub> (like the down stroke of a capital T). Before connecting up L<sub>3</sub>, L<sub>4</sub>, dress the leads of the r.f. choke as shown in Fig. 2, so that the two ends of the leads can be soldered into circuit close together. This enables the choke to be twisted so as to re-orient it with respect to the ferrite aerial rod. In this way a position can be found where the coupling is zero or perhaps just slightly positive so that a useful improvement is obtained in selectivity. Varying the position of the ferrite aerial can also be helpful.

No other setting up adjustments are required. It will be found however that a sort of false instability occurs when the receiver is tuned in to a strong station with the volume too high. This is merely an overloading effect and the remedy is obvious – turn down the volume.

A simple test that the d.c. conditions are correct can be made by measuring the voltage drop across R<sub>3</sub>. This should be in the range 0.65 to 0.75V.

If desired, the on-off switch, S<sub>1</sub>, may be ganged to the volume control.

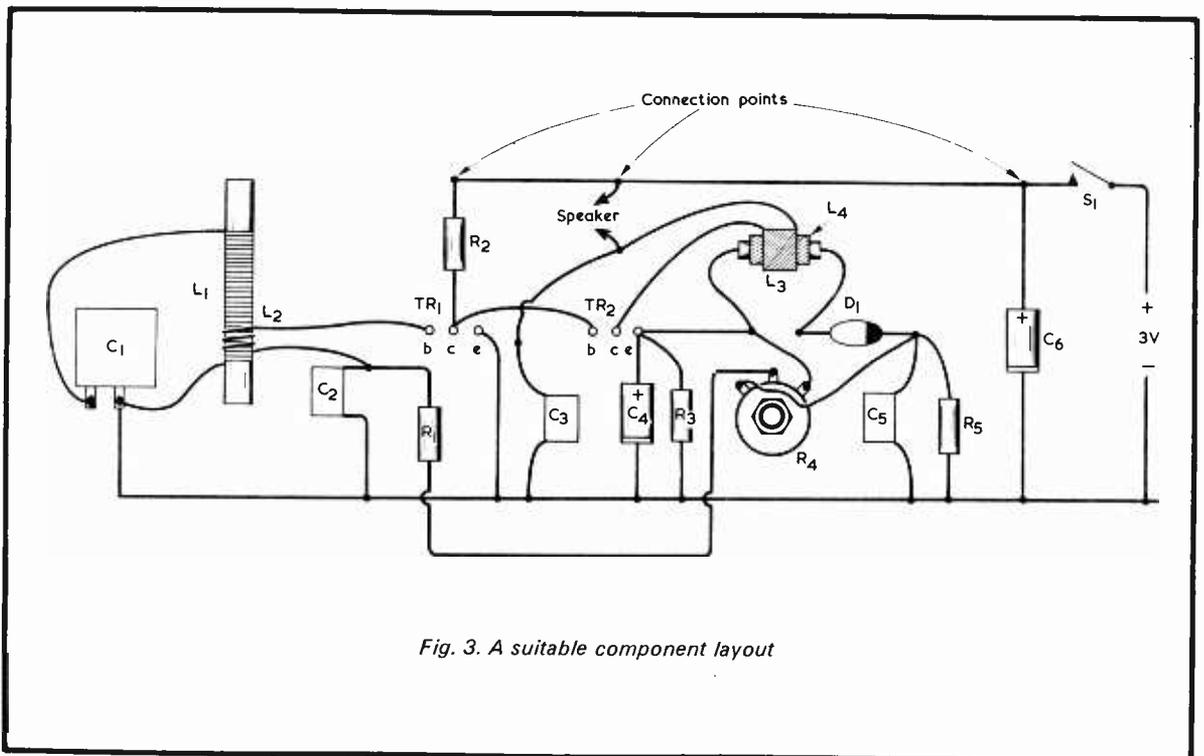


Fig. 3. A suitable component layout

## LONG WAVE RECEPTION

The circuit will work on long waves given a suitable ferrite rod with long wave windings. (There is not room on a 4in. rod for both medium wave and long wave windings.) Alternatively, a single long wave station could be received by switching a suitable fixed capacitor across L1 and using C1 for fine tuning, as shown in Fig. 4. For reception of the Radio 2 transmission on 200kHz the added capacitor should be 2,200pF. A polystyrene film or silvered mica capacitor should be used.

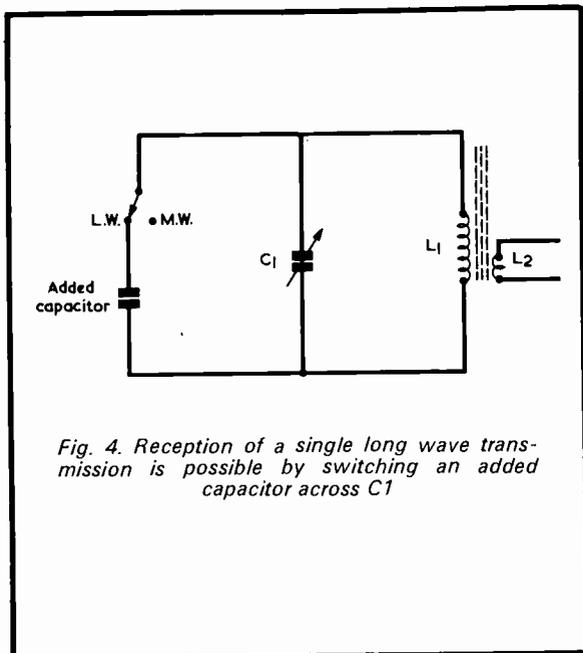


Fig. 4. Reception of a single long wave transmission is possible by switching an added capacitor across C1

## OTHER SUPPLY VOLTAGES AND LOADS

In this direct-drive circuit it is essential to use a high impedance loudspeaker. The preferred impedance is 70 to 80 $\Omega$  but speakers of somewhat different impedance may work: it depends upon how sensitive they are. A transformer may be used to match speakers of low impedance.

The voltage across R3 is stabilized at about 0.7 volt irrespective of the battery voltage. This makes it easy to set TR2 to take some particular collector current. At present, with R3 at 68 $\Omega$ , TR2 takes a little over 10mA. If it were required to set the current at 1mA to suit an earphone of around 500 $\Omega$  impedance in place of the speaker, R3 would be 680 $\Omega$ .

With a 75 $\Omega$  speaker, some increase in volume is obtainable by using the present resistor values but increasing the supply voltage to 4.5 volts. The circuit will go on working quite happily at higher voltages, up to 9 volts, but 75 $\Omega$  is not then the optimum speaker impedance. (This rises to about 800 $\Omega$  at 9 volts.)

Some constructors will want to use 3 $\Omega$  speakers, which must be matched with a transformer. It is then useful to tailor the current in TR2 and the supply voltage to suit the load and transformer ratio. Allowing

1 volt for the drop across R3 plus the d.c. drop across the transformer primary, we are left with 1 volt less than the battery voltage across TR2. This voltage, divided by the transformed speaker impedance, should equal the collector current. Suppose we have a 3 $\Omega$  speaker and a 10:1 transformer, giving a load impedance of 300 $\Omega$ . With a 3 volt supply, the optimum current in TR2 is then 2 volts divided by 300 $\Omega$ , which is 6.7mA. The required value of R3 is 0.7 volt divided by 6.7mA, or 106 $\Omega$ , and we could use 100 $\Omega$ , the nearest standard value.

Again, if we have a 20:1 transformer and a 5 $\Omega$  speaker, the transformed speaker impedance is then  $400 \times 5 = 2,000\Omega$ . With a 3 volt supply the optimum current is 1mA, but since the power input to TR2 would then only be 2mW the audio power output cannot exceed 1mW, which may well be inadequate. The remedy is to use a higher battery voltage. With a 9 volt supply, the optimum current becomes 8 volts divided by 2,000 $\Omega$ , or 4mA, and the d.c. input power to TR2 32mW, giving a possible 16mW of audio output (and a likely 8mW, assuming 50% transformer efficiency). The value of R2 for 4mA is 0.7 volt divided by 4mA, or 175 $\Omega$ , so the appropriate standard resistor in this case is 180 $\Omega$ .

When a high load impedance is used it may be necessary to reduce the value of the r.f. bypass capacitor C3, to avoid cutting the treble. Values down to 0.01 $\mu$ F may be used.

When working with supply voltages much above 3 volts it may be helpful, in the interests of battery economy, to reduce the current in TR1. This is done by increasing the value of R2. The voltage drop in R2 is held, by the d.c. feedback, at 1.4 volts less than the battery voltage, and a current in it of 1 to 2mA is adequate.

The working voltage of C6 must be increased for supply voltages greater than 3 volts. Constructors who intend experimenting with different supply voltages will find it useful to initially fit a capacitor here of 10 V.Wkg.

## SEMICONDUCTORS

It is essential to use silicon planar transistors. The types specified have been carefully selected to give a good performance. (The SF115 transistor can be obtained from Amatronix Ltd., as can the other semiconductors and components.) Other transistor types will probably work, but less well. The input transistor must be an r.f. type with a low feedback capacitance and the SF115 specified has the added advantage of low a.f. noise as well. It should be possible to substitute BF115, which is the same transistor in a metal case. The BF167 will also work in this position.

The requirement for TR2 is rather different. This transistor may have to handle peak currents of 20mA or more, which rules out some r.f. types. It should have a low input capacitance and a fairly low feedback capacitance as well, to avoid putting too great a stray capacitance across R2 and so reducing the r.f. gain. Fortunately the BC169C has these features, and also the added one of very high hfe: some other high-gain audio types are much worse in the matter of capacitances.

In principle any point-contact diode will be satisfactory for D1, but here again some are better than others, and the OA90 is very suitable.

# The


# 'WYVERN'

## 160 Metre

## Solid State

# Transmitter

— Part 2.

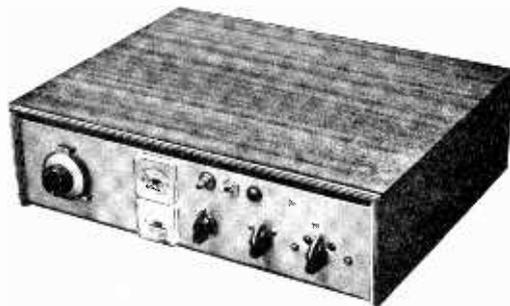

by

John R. Green, B.sc., G3WVR

The second article in our 3-part series which describes the construction of a comprehensive transmitter design incorporating semiconductors throughout.

IN LAST MONTH'S ISSUE THE OVERALL DESIGN OF THE transmitter was described as also, in detail, were the v.f.o., the wideband driver section and the doubler and driver stage. This month's article covers the power amplifier stage and the power supply. The concluding article, to be published next month, will deal with the modulator, VU meter driver and general assembly and testing.

### POWER AMPLIFIER

The circuit diagram for the p.a. stage is given in Fig. 11. This diagram also includes the power switching around S1(a) to S1(e).

The heart of the stage is the BD123 transistor, which has been chosen for three reasons:

(a) the frequency response cut-off  $f_T$ , of 85MHz gives a more than adequate performance at 2MHz,

(b) the power dissipation capacity of 45W gives a safeguard against overheating and damage,

(c) the VCE (collector-emitter maximum voltage) of 60 volts gives a reasonable safety margin since on modulation peaks the collector to emitter instantaneous voltage (peak) can be as much as four times the normal supply voltage, i.e. 48 volts.

304

The drive to the base of the BD123 is controlled by RV1, which is mounted on the front panel of the transmitter. TR7 is pulsed on by positive-going r.f. half-cycles. The consequent pulses of collector current passing through the 2 turn winding of L4 are shaped by the 20 turn tuning winding before radiation. Both windings are close-wound, direct on the rod using 20 to 24 s.w.g. enamelled wire.

Loading and tuning adjustments for the p.a. are as for a conventional valve transmitter, with the exception that the loading setting is far less critical, particularly if the aerial is not quarter wave resonant, and final loading adjustments are carried out by means of the drive potentiometer.

It is important to note that all drive components, i.e. RV1, L2 tuning and L3 tuning, are normally set for maximum p.a. current; whereas the p.a. tuning is adjusted for minimum p.a. current.

Always begin tuning operations with RV1 turned up only sufficiently to draw, say, 500mA of current through the p.a. meter, and then perform initial tuning and loading. Gradually increase the drive given by RV1 until the legal maximum (830mA at 12 volts) is achieved, then make final fine tuning adjustments. Failure to follow this procedure could cost an output transistor (about £1).

RADIO & ELECTRONICS CONSTRUCTOR

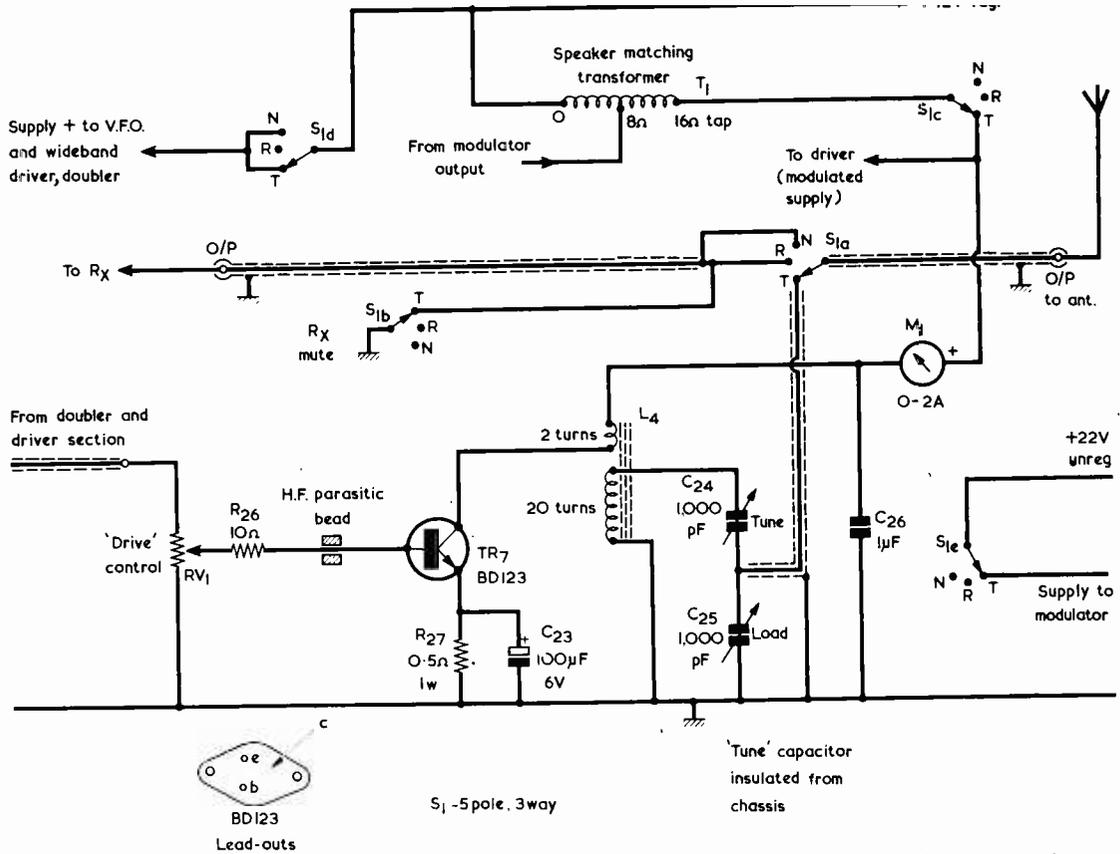


Fig. 11. The p.a. stage. Shown also are the Net, Receive and Transmit switching circuits and the modulation transformer, T1

## COMPONENTS

### Resistors

- (All fixed values ½ watt 10%, unless otherwise stated)
- R26 10Ω
  - R27 0.5Ω 1 watt
  - R28 1kΩ
  - R29 22kΩ
  - R30 1kΩ
  - R31 1kΩ
  - R32 220Ω
  - R33 0.25Ω 1 watt, see text
  - RV1 500Ω potentiometer, wire-wound

### Capacitors

- C23 100μF electrolytic, 6 V.Wkg.
- C24 1,000pF variable
- C25 1,000pF variable
- C26 1μF plastic foil
- C27 1,000μF electrolytic, 25 V.Wkg.
- C28 2,000μF electrolytic, 25 V.Wkg.
- C29 100μF electrolytic, 25 V.Wkg.

### Inductors

- T1 Speaker matching transformer, 8Ω and 16Ω or 8Ω and 15Ω, minimum rating 10 watts
- T2 Mains transformer, secondary 0-12-15-20-24-30 volts at 2 amps, Douglas type MT3AT
- L4 P.A. output coil, wound on ferrite rod 6ins. by ½in. diameter

### Semiconductors

- TR7 BD123
- TR8 BFY50/2N3053
- TR9 2N3053
- TR10 2N3250/2N3905/2N3702
- TR11 2N3055
- D1-D4 Silicon rectifiers, 2A 100 P.I.V.
- ZD2, 3 6.8V 200mW zener diodes

### Switches

- S1 5-pole 3-way, wafer
- S2 s.p.s.t. toggle

### Meter

- M1 0-2A meter

### Neon

- NE1 Panel-mounting neon assembly with integral series resistor

### Fuses

- F1-3 2 amp anti-surge, with holders

### Miscellaneous

- Ferrite lead
- 2 coaxial sockets
- 4-way tagstrip
- 3 pointer knobs
- Printed circuit board
- 16 s.w.g. aluminium
- Coaxial cable

The ferrite rod, on which is wound the output coil, is clearly visible here. The component to the left of the rod is the modulation transformer

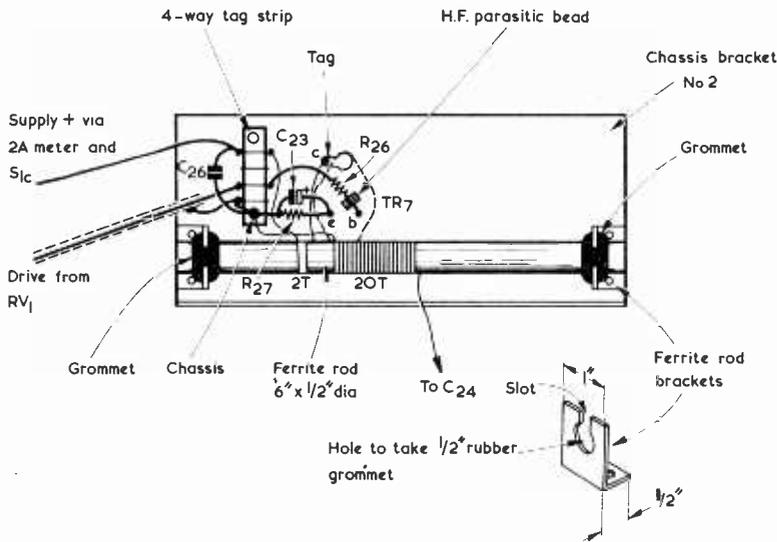
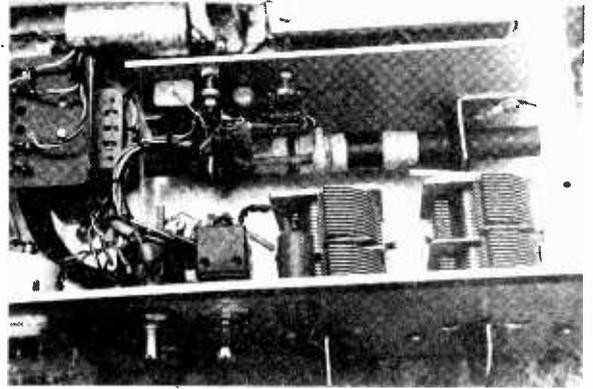


Fig. 12. Physical layout of the p.a. stage. The parts are mounted on Chassis Bracket No 2

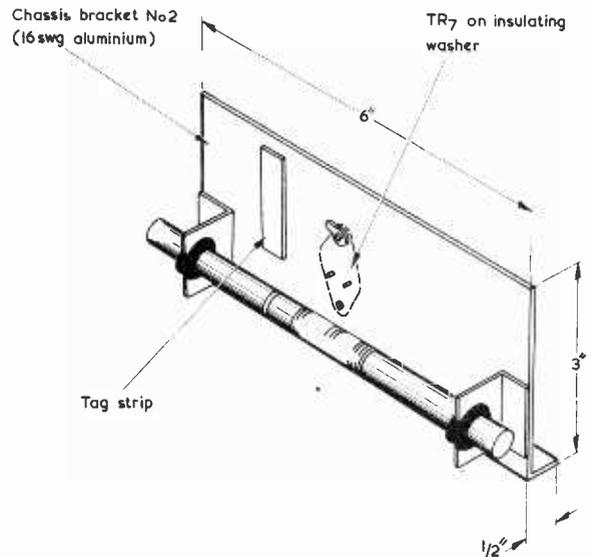


Fig. 13. Details of the Chassis Bracket No 2


Do not attempt to increase the p.a. efficiency (which is about 60%) by increasing the number of turns on the collector winding of L4, as this will cause 'jump tuning' and poor output waveform, resulting in TVI.

Also, do not use a smaller ferrite rod for L4 or saturation of the ferrite may result, destroying the transformer action. If desired, use a larger ferrite rod but *do* ensure that it is suitable for operation at 2MHz, as many ferrite grades are not. The rod used by the author is 6ins. long by 1/2in. diameter, and was obtained from G. W. Smith & Co. (Radio) Ltd., 3 Lisle St., London, W.C.2.

The construction of the p.a. stage is shown in Fig. 12. The output transistor is fitted to Chassis Bracket No. 2, the dimensions of which are given in Fig. 13. The transistor is insulated from the bracket by means of the usual mica washer and insulated mounting bushes, and its body is on the opposite side of the bracket to the ferrite rod. The latter is secured by two brackets with slots in the holes through which the rod passes. The slots prevent shorted-turn action. The earthy end of the 20 turn winding is that which is closer to the collector winding. A 4-way tagstrip is also mounted on the bracket.

Fig. 11 also shows the switching carried out by S1(a) to (e). This is quite simple and straightforward and the circuits controlled at each switch position can be readily traced through. The modulation transformer T1 is a speaker matching transformer having taps at 8Ω and 16Ω. A transformer having taps at 8Ω and 15Ω could alternatively be employed if this should prove easier to obtain. Whatever transformer is employed *must* have a power capability of at least 10 watts audio handling.

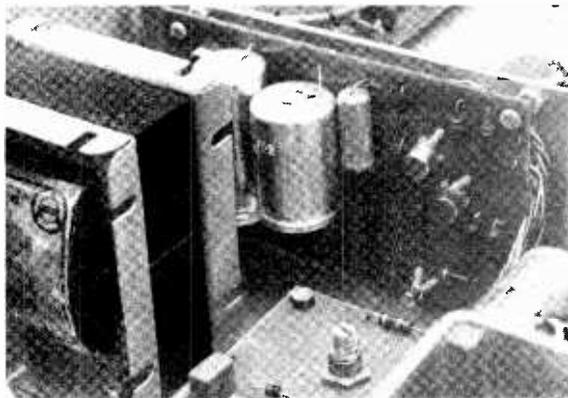As will be illustrated in greater detail in next month's article, in which the general assembly will be dealt



A view of the power supply board. This is partly obscured by the mains transformer

with, switch S1, driver potentiometer RV1 and meter M1 are all mounted on the front panel of the transmitter. So also are C24 and C25, the 'Tune' and 'Load' capacitors. The frame of the 'Tune' capacitor is insulated from the chassis by mounting it on a sheet of Paxolin. The frame of the 'Load' capacitor is bolted direct to the panel. In practice both capacitors consist of 2-gang 500 + 500 pF components with the two sections in parallel.

The modulation transformer, T1, is positioned between the v.f.o. box and Chassis Bracket No. 2.

## POWER SUPPLY

The circuit diagram of the power supply is shown in Fig. 14. The design incorporates the simplest form of regulation for the 12 volt supply, using zener diodes

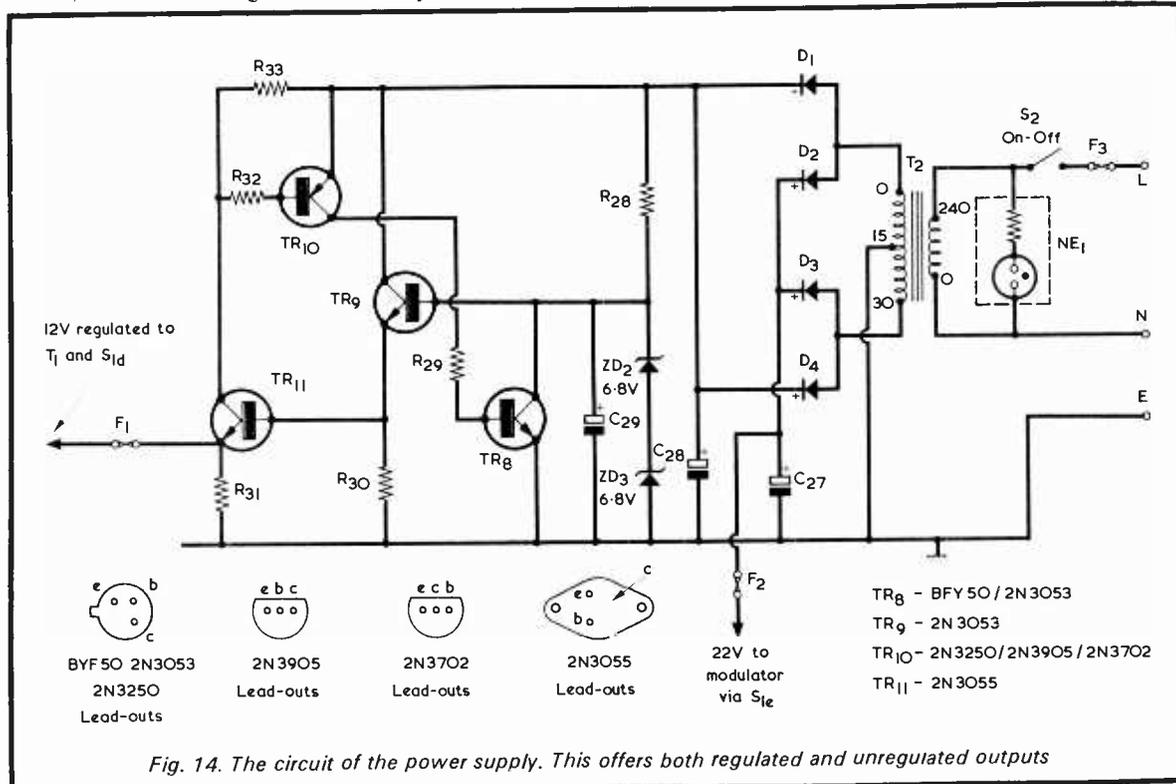


Fig. 14. The circuit of the power supply. This offers both regulated and unregulated outputs

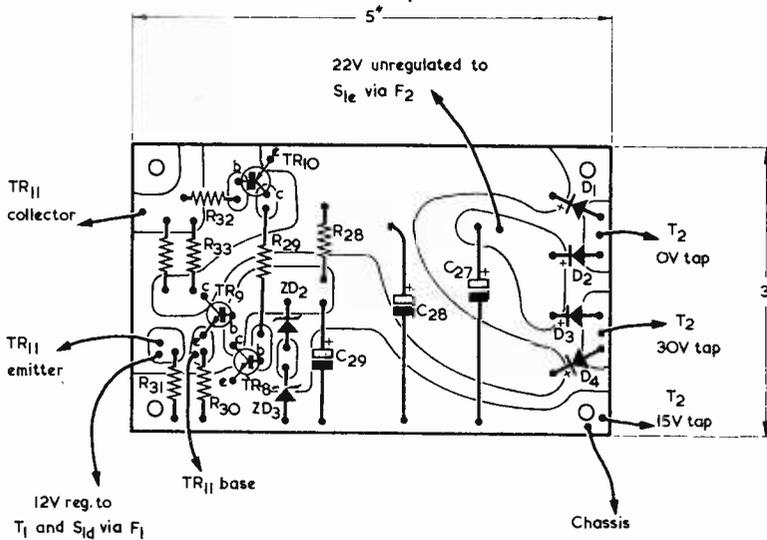


Fig. 15. The power supply printed circuit board, as seen from the component side.

ZD2 and ZD3 and the emitter followers TR9 and TR11. Overload protection is given by TR10 and TR8. If the current drawn through R33 causes a voltage to appear across it which is sufficiently high to allow base current to flow in TR10, this transistor becomes conductive. Its collector current flows in the base

circuit of TR8, whereupon TR8 causes a reduction in the voltage across ZD2 and ZD3 and, in consequence, in the regulated output. The current limit is 2.5 amps.

A 22 volt unregulated supply is also provided for the Class B modulator.

The mains transformer, T2, has a number of secondary windings, of which only the 0, 15 and 30 volt windings are employed here. The 15 volt winding becomes the earthed centre-tap in this arrangement.

The use of fuses in the mains input and regulated and unregulated output circuits is recommended, and they can be located in any available space in the transmitter. A neon mains indicator lamp with integral series resistor may be fitted, if desired.

The printed circuit board for the power supply is reproduced, full size, in Fig. 15. The view is from the component side of the board. In the prototype R33 is made up of two ½ watt 0.5Ω resistors in parallel and two resistors are shown, in Fig. 15, in the R33 position. The board is mounted, with spacing stand-off washers to Chassis Bracket No. 3, which is illustrated in Fig. 16. The bracket also acts as a heat sink for TR11, the body of which is on the opposite side of the bracket to the board. TR11 is insulated from the bracket by a mica washer and insulated mounting bushes.

The whole power supply (both 12 and 22 volt outputs) may be replaced by a car battery or other 12 volt accumulator (but *not* by dry batteries, which cannot supply the current required). The author's transmitter incorporates additional sockets and switching to achieve this. It should be pointed out, however, that when running from a 12 volt supply the modulator will not supply the output required for 100% modulation. Incidentally, the 22 volt output from the mains power supply will, of course, drop in voltage under load but this is not detrimental to the modulation quality unless excessive bass frequencies are present.

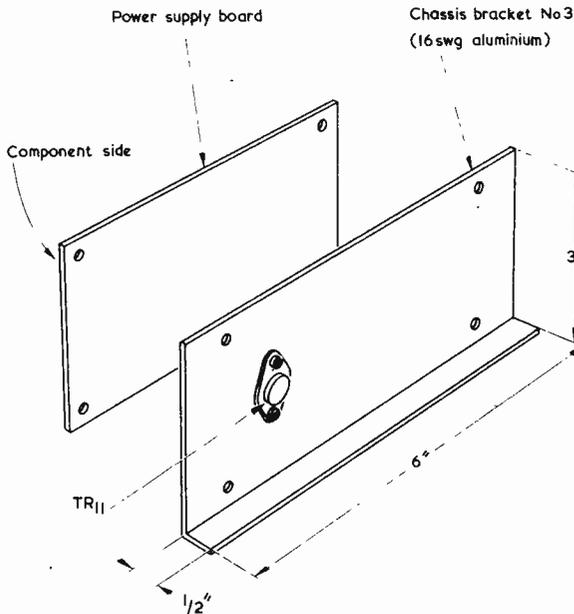


Fig. 16. Fitting the power supply board to Chassis Bracket No 3

(To be concluded)

RADIO & ELECTRONICS CONSTRUCTOR




# TRANSISTORISED OSCILLOSCOPE

Part 1  
by R. A. Penfold

In this oscilloscope the only thermionic device is the cathode ray tube. The present article describes the mechanical construction of the instrument, the power supply and display section, and the X amplifier module. The remainder of the circuit will be covered in a concluding article, which will be published next month.

**A**N OSCILLOSCOPE IS PROBABLY THE MOST USEFUL piece of test equipment an electronics enthusiast can possess (with the exception perhaps of the multi-range meter), even if it is only a very simple instrument. Unfortunately, an oscilloscope is also one of the most expensive pieces of equipment to buy. The instrument which is the subject of this article is quite inexpensive when compared with the cheapest commercially manufactured oscilloscopes, but it has to be pointed out that quite a considerable amount of work is involved in building it.

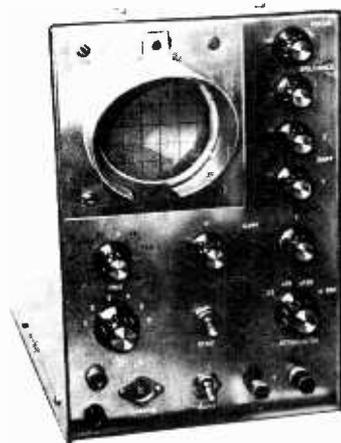It is suitable for most applications, except very specialised ones such as television servicing, where a very wide bandwidth is required. As the instrument was designed mainly for audio work, a high sensitivity was considered to be more desirable than a wide bandwidth, although as shown in the specification table, the useful bandwidth of the oscilloscope stretches to beyond 2MHz.





## METALWORK

The unit is housed in a home-made case, the outside dimensions of which are 14 ins. deep by 6 ins. wide by 9 ins. high. The accompanying photographs will assist in demonstrating how the parts of the case are assembled together. Construction of the case should commence with the front and rear panels, details of which are given in Fig. 1. The material is aluminium and the exact gauge is not critical, although a fairly thick gauge should be used for all parts of the case. The aluminium employed for the front and rear panels of the prototype was 20 s.w.g.


For those without the proper equipment for bending the metal, it will be found easier if a slightly thinner gauge of aluminium is used, although this will mean sacrificing some of the stiffness of the case.

On the front panel the holes for the control bushes should have diameters of  $\frac{3}{8}$  in. with the exception of the holes for S4 and S1, which are toggle switches. The hole marked 'T/B' is for a flush-mounting coaxial socket, and the two pairs of holes marked 'X' and 'Y' take 3mm. insulated sockets. Note that VR8 is fitted on the rear panel and that this also requires a  $\frac{3}{8}$  in. hole. The rear panel mains lead hole should be fitted with a rubber or p.v.c. grommet to prevent damage to the lead. The method of mounting the other parts fitted to the rear panel will become clear when these are discussed.

In Fig. 1 the front panel is seen from the front and the rear panel from the rear. In both cases the 1 in. sections at top and bottom are bent down away from the reader. The  $\frac{1}{2}$  in. side sections shown in dotted outline are optional and, as is explained shortly, are only incorporated if a cover different to that used by the author is employed. They should also be bent down, away from the reader.

The bottom of the case is made next, and this is shown in Fig. 2. The two 1 in. flanges are bent up, towards the reader. Fig. 2 also shows the positioning of components and circuits which will later be fitted to the bottom. The lower flanges of the front and rear panels pass under the case bottom and are secured by 4BA bolts and nuts fitted at the holes marked 'X' in Fig. 2.

To ease assembly the corresponding holes in the front and rear panel flanges are best marked out from those in the bottom after all the bending has been carried out. The holes in the top flanges of the front and rear panel can be  $\frac{1}{2}$  in. from the flange edge and  $1\frac{1}{2}$  ins. from each side: They are drilled to take self-tapping screws for securing the cover. If the side flanges on the front and rear panels are incorporated, they may also have holes drilled to take self-tapping screws. Four rubber feet

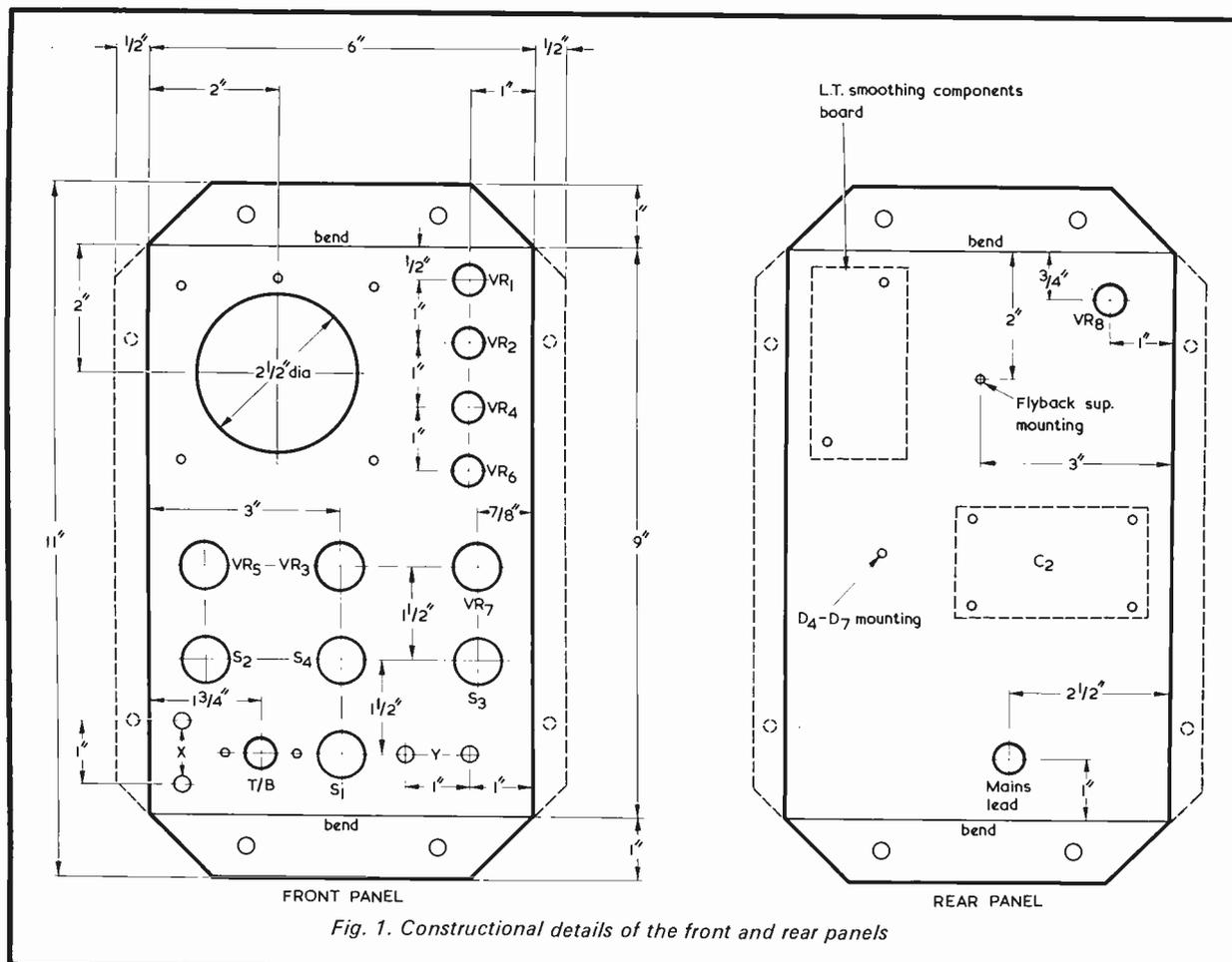



## C.R.T. MOUNTING

are fitted to the bolts at the holes marked 'X'.

An outer casing is very desirable to prevent dust from entering the unit and to improve appearance. With the prototype, the casing was made from a single sheet of aluminium suitably bent, but this was found to introduce a magnetic field to the c.r.t. from the mains transformer, resulting in a wider trace than was otherwise obtained. If the tube were fitted with a magnetic screen this effect would no doubt disappear. On the prototype it was eliminated by glueing thin pieces of steel sheet at strategic points on the inside of the case.

Alternatively the outer casing could be constructed from a non-metallic substance such as Perspex or Formica. It would be necessary to use three separate pieces, and this would require the addition of the two extra flanges on the front and rear panels shown in dotted line in Fig. 1.

For the best appearance the cover should overlap the front and rear panels by about  $\frac{1}{8}$  to  $\frac{1}{4}$  in. The outer casing is fastened in place by ten self-tapping screws (eighteen if it is made of three separate pieces). With the outer casing added the unit will have greatly increased stiffness.

The c.r.t. mounting comprises three sections, a metal tube fastened to the front panel into which the front of the c.r.t. is passed, a bracket which fits around the tube base, and an L-shaped bracket fixed to the bottom of the chassis to which the second bracket is coupled. All parts are made from 22 s.w.g. aluminium.

The metal tube holding the front of the c.r.t. is illustrated in Fig. 3. A piece of aluminium measuring 12 by 2 ins. is bent round to form a tube with an internal diameter of  $3\frac{1}{2}$  ins. To prevent the metal from opening up once it has been bent to shape, two  $\frac{1}{4}$  in. 6BA countersunk bolts, with the heads on the inside, are passed through the holes illustrated. A small angle bracket, made from a piece of aluminium 1 in. by  $\frac{1}{2}$  in., is mounted on one of these bolts, and a second by means of a countersunk 6BA bolt at a hole on the opposite side of the tube. The holes in Fig. 3 are not dimensioned as it will probably be found best to mark them out with the aid of the actual parts. The hole in each half of the angle brackets is central. The tube is fitted to the front panel at two holes, which are next drilled for it. These are two of the holes diagonally opposite each other which are shown outside the  $2\frac{1}{2}$  in. hole in Fig. 1. When these holes have been drilled, the remaining two diagonally opposed holes may be marked up to balance them and drilled out also.

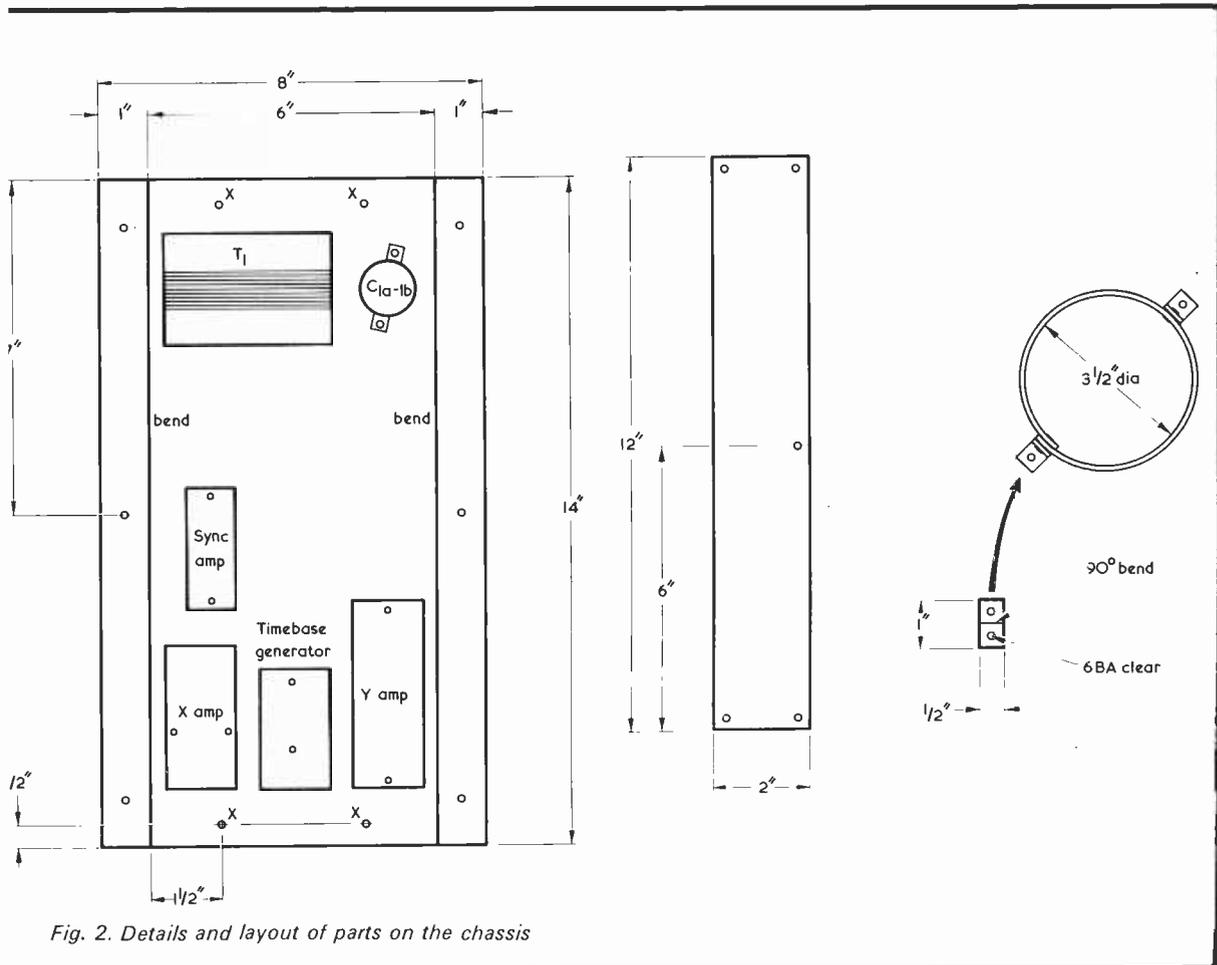


Fig. 2. Details and layout of parts on the chassis

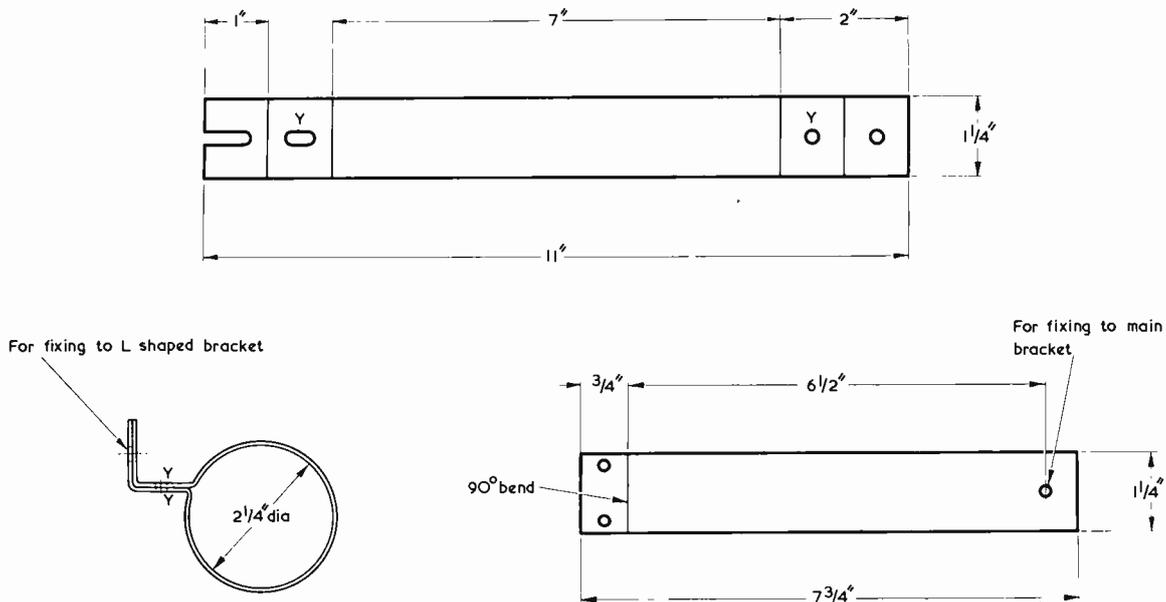


Fig. 4. The sections which form the rear mounting for the c.r.t.

Fig. 4 gives details of the mounting arrangement at the rear of the tube. A piece of aluminium, 11 by 1 1/4 ins. is drilled as shown and bent to shape. The L-shaped bracket is next made, from a piece of aluminium measuring 7 1/4 by 1 1/4 ins. The first bracket is fitted around the c.r.t. base and loosely bolted to the L-shaped bracket. A 2 in. 6BA bolt is passed through the holes marked 'Y' and is tightened until the bracket holds the c.r.t. base firmly. It is advisable to wrap a couple of bands of sticky-backed foam rubber or foam plastic strip (sold as draught-excluder) side by side around the c.r.t. base, as this will assist in causing the base to be held firmly by the bracket. Care must be taken not to overtighten the 2 in. 6BA bolt, as this could damage the c.r.t. The L-shaped bracket is bolted to the chassis by two 6BA screws at the point which allows the c.r.t. to take up a correct position. The tube should be orientated such that its pins 8 and 9 are uppermost.

To prevent the c.r.t. from being damaged through vibration, several layers of the foam rubber strip should be wound around the front of the c.r.t. on the area between the phosphor and graphite coatings. A couple of layers should also be wound around the inside of the metal tube at the extreme front.

When the c.r.t. is mounted finally, the two brackets of Fig. 4 are bolted securely together. Obviously, great care must be taken when handling the c.r.t. during these operations. It should be removed from its mounting after the positioning of the mounting parts has been satisfactorily established, and placed on one side, since further drilling operations have to be carried out on the chassis.

## VISOR AND GRATICULE

In strong lighting conditions, a visor to shield the screen from external light is a decided asset. A suitable visor is quite easy to construct and may be made from a piece of aluminium having the dimensions shown in

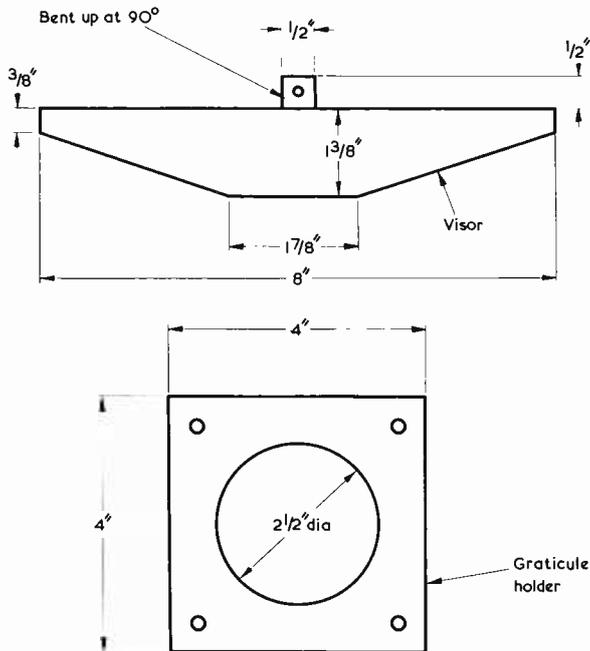


Fig. 5. The visor, before bending, and the graticule holder

Fig. 5. After cutting out, this is bent round to have a diameter slightly greater than the 2 1/2 ins. hole in the front panel. It is secured to the front panel by a single 6BA bolt in a hole which is marked out from the visor itself.

On the prototype, the visor was left with a natural finish, but it can be made more efficient by being painted matt black. The visor is fitted after the escutcheon which holds the graticule (next to be described) has been mounted.

When using the oscilloscope to measure signal voltages a graticule is required. This is merely a piece of transparent material such as Perspex which is marked with the X and Y centre axes. Graticules also have lines parallel with these axes, and these are usually marked off at 1mm. intervals with heavier lines at 1cm. intervals.


A suitable graticule can be constructed by cutting a piece of Perspex 2½ins. square. This is then marked as required by scribing it as deeply as possible with a sharp pointed instrument. To calibrate X and Y axes at 1mm. intervals by hand is extremely difficult, and it is very much easier if 2 or 2.5mm. divisions are used.

The graticule is held in place by an aluminium escutcheon, details of which are given in Fig. 5. This is bolted to the front panel by four 6BA bolts, two of which are already present as part of the tube mounting. The graticule is trapped between the escutcheon and the front panel. The four mounting holes for the escutcheon correspond with the four holes already drilled in the panel. A fifth hole, not shown in Fig. 5, takes the bolt which holds the visor in position.
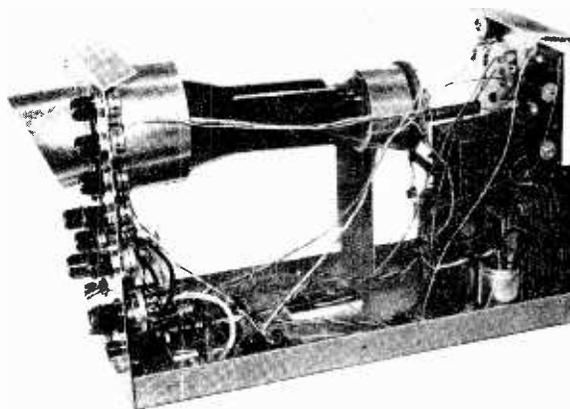
## POWER SUPPLY

The circuit of the power supply section is shown in Fig. 6. This circuit provides four voltages, these being approximately 500 volts e.h.t., 124 volts stabilized, 12 volts stabilized, and 6.3 volts a.c. for the tube heater.

The 250-0-250 volt secondary of the mains transformer has the chassis connection made to one end, causing it to provide 500 volts. This is of course 500 volts r.m.s., and the peak voltage is in the region of 700 volts. In consequence, despite losses in the half-wave rectifier and smoothing circuit given by D1, D2, R2 and C2, 500 volts is still available at the output. It should be



A view inside the oscilloscope. Most of the components are wired up on small printed circuit modules

noted that this output is negative with respect to chassis, whereas the other two d.c. outputs are positive with respect to chassis. Capacitor C2 was a 4µF 500 V.Wkg. paper component in the prototype. A component with a slightly higher working voltage could be employed here and it is noted that Home Radio advertise a 4µF 600 V.Wkg. capacitor under Cat. No. 2EG55.

A second half-wave smoothing circuit is used for the 124 volt h.t. supply. The power is taken from the centre tap of the h.t. secondary of T1, which now offers 250 volts, and is rectified by D3. C1(a) and C1(b) are the reservoir and smoothing capacitors, whilst R1 and the zener diodes D9 and D10 reduce the output voltage to a nominal 124 volts. The ZL100 specified for D10 is a 100 volt 5%, zener diode rated at 1 watt, and it is available from Henry's Radio. Other series combinations of zener voltages may be used to obtain the 124 volt figure, and typical instances are given by two 62 volt diodes or a 56 volt and a 68 volt diode in series. Each diode should be rated at 1 watt.

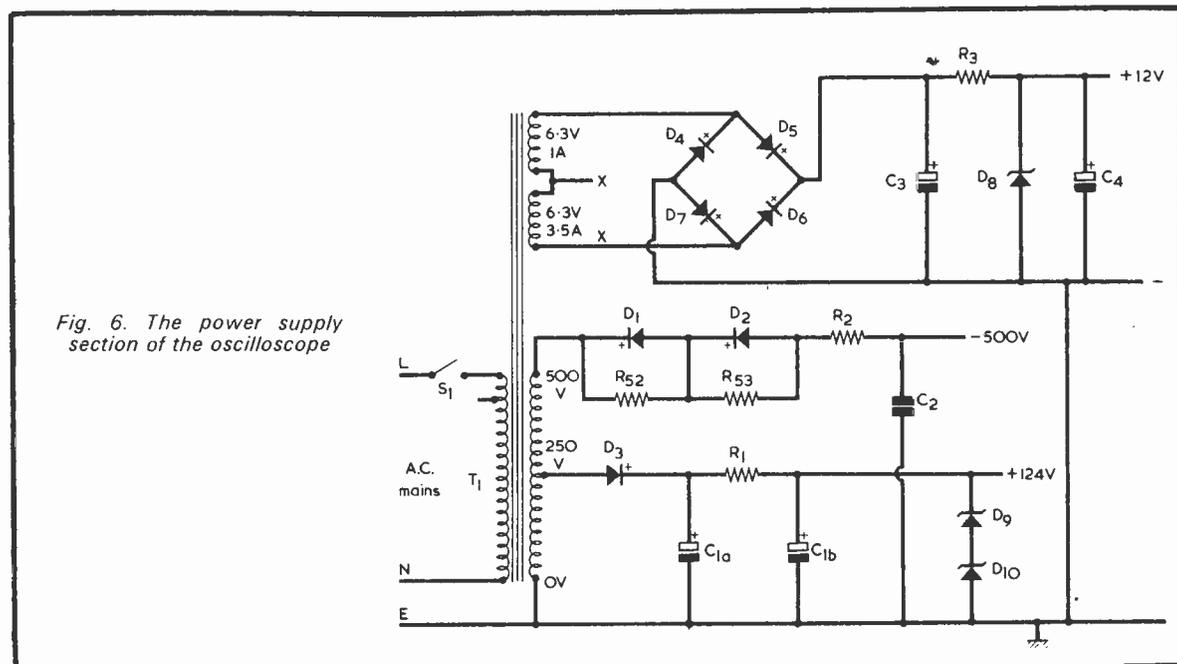


Fig. 6. The power supply section of the oscilloscope

The two 6.3 volt secondaries of the transformer are connected in series to provide the 12 volt output, the alternating voltage being rectified by the bridge selenium rectifier, D4 to D7. This rectifier should be rated at 12 volt 0.5 amp or more. Zener diode D8 stabilizes the supply at 12 volts. The cathode ray tube heater requires 6.3 volts at 1 amp and this is taken from the 6.3 volt 3.5 amp winding of the transformer at the points marked 'X'. The only disadvantage with this method of supplying the c.r.t. heater is that it causes a high voltage to appear between the tube cathode and the heater, and there is a consequent risk of breakdown in the cathode-heater insulation. No trouble was experienced on this score with the prototype, but constructors who would prefer to avoid the risk of damage to the c.r.t. are advised to supply its heater from a separate small 6.3 volt transformer, which can be mounted at the rear of the chassis.

The power supply section is mainly wired up using point-to-point wiring. The positioning of T1 and C1(a) (b) is shown in Fig. 2. C2 and the bridge rectifier D4-D7 are mounted on the rear panel, as illustrated in Fig. 1. D1, D2, R52, R53 and R2 may be wired between the transformer and C2 in any convenient manner, such as would be given by using a small tagstrip bolted to one of the slots in the transformer frame. R3, C3, C4 and D8 are mounted on a Paxolin board measuring 3 3/8 by 1 1/2 ins. The layout on this board runs along very much the same lines as the circuit diagram. The board is mounted to the rear panel, as in Fig. 1, and it must be spaced away from the panel by stand-off washers. Alternatively, a piece of polystyrene tile, cut to the same dimensions as the board, may be sandwiched between the board and the panel.

After thoroughly checking the completed power supply wiring for mistakes, the unit should be switched on and the various output voltages checked. The 124 and 12 volt outputs should have voltages that are within 5% of their nominal values since they are controlled by zener diodes. The e.h.t. should be somewhat higher, at 600 volts or more, as it is not under load conditions as it stands.

## DISPLAY UNIT

Fig. 7 shows the circuit diagram of the display unit. This is very straightforward, and uses standard circuitry. The astigmatism control is required to ensure that the beam is properly focused, whatever part of the screen it is aimed at.

No special insulation was used on the brilliance and focus controls as is sometimes done due to the high voltages involved, and this was found to be quite satisfactory. Point-to-Point wiring is used. R7 can be conveniently mounted between pin 3 and pin 6 of the c.r.t. base, as there is no internal connection to pin 6.


The 3BP1 c.r.t. employed is available from a number of suppliers, including Henry's Radio. Although this tube is intended to operate from a 1,500 volt supply, it gives perfectly satisfactory results at the lower voltages employed here. The only effect of using a lower voltage is a slight loss of trace brightness and an increase in deflection sensitivity.

To test that the display unit is functioning correctly, the X and Y plates should be temporarily earthed to chassis. The unit should then be switched on, and after a brief warm-up period for the c.r.t., a spot should appear on the screen. It should be possible to adjust the intensity of the spot with the brilliance control, while adjustment of the focus control should enable the spot to be reduced to about 1mm. diameter.

For the time being the astigmatism control should be set at its mid-point. This control can be given the correct adjustment later, after the X and Y deflection amplifiers have been installed.

When these are installed, the astigmatism control should be tried at various settings, with the focus control being re-adjusted for each new setting. The X and Y shift controls are then employed to move the spot to the extremities of the screen and thereby check how well the spot remains focused.

The control is left finally at a setting which gives a properly focused spot at any part of the screen.

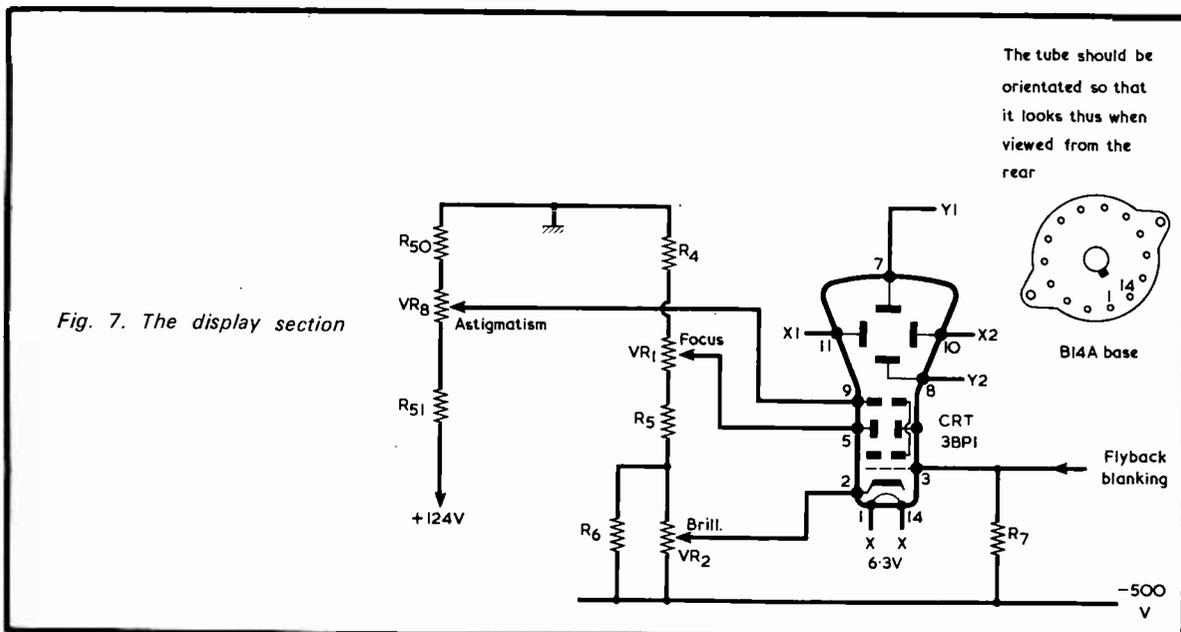

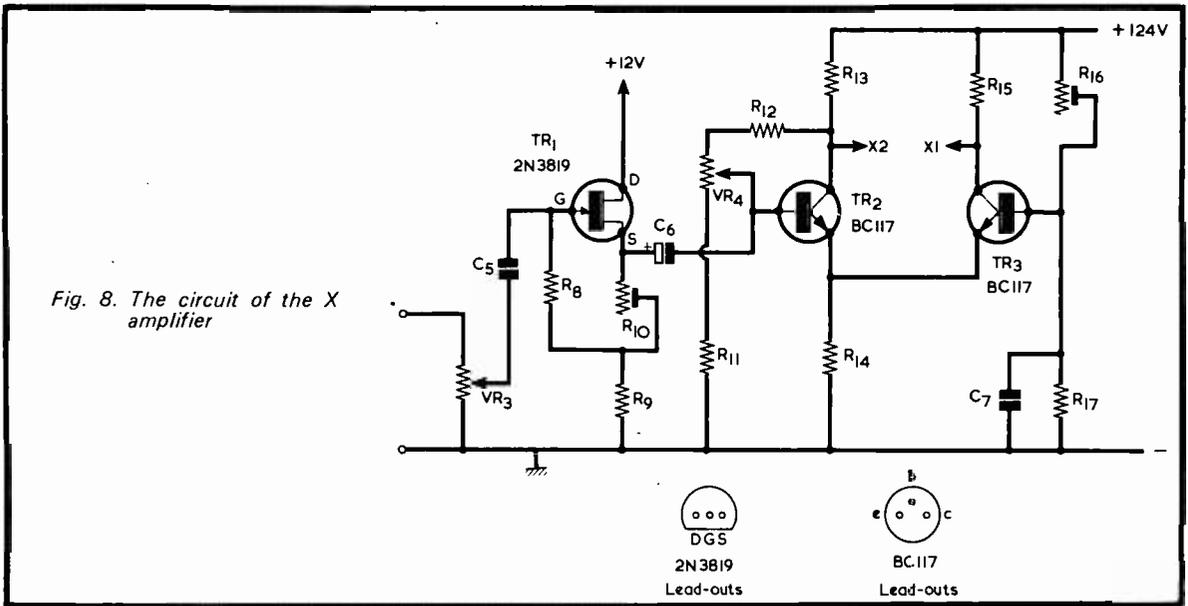


Fig. 8. The circuit of the X amplifier

### X AMPLIFIER

The X amplifier uses a very simple circuit incorporating only three transistors, including an f.e.t. input stage. The circuit diagram is given in Fig. 8.

TR1 is a 2N3819 field effect transistor operated in the source follower mode (the f.e.t. equivalent of the emitter or cathode follower circuits). Pre-set resistor R10 is adjusted to give approximately half the supply potential at TR1 source. The  $6.8\text{M}\Omega$  gate biasing resistor, R8, is given a certain amount of bootstrapping by being taken to a tap in the source load resistance. Because of the high input impedance of the f.e.t. and the very high effective resistance offered by R8 the circuit achieves an extremely high input resistance, but this is shunted by the gain control, VR3. A source follower gives a very low input capacitance (a few picafarads) and the actual input capacitance of this section of the oscilloscope will depend largely upon the stray capacitance in the input wiring.

TR2 and TR3 are operated as a paraphase amplifier. This is a form of phase splitter. The easiest way to consider the operation of this circuit is to regard TR2 as a common emitter amplifier, and TR3 as a common base amplifier. Signals at TR2 base will appear amplified, but  $180^\circ$  out of phase, at TR2 collector. These signals will also appear, at a low impedance and in phase, at TR2 emitter.

TR3 is operated as a common base amplifier. In such a circuit the input is taken to the emitter of the transistor, and so the signals at TR2 emitter are coupled to the emitter of TR3. Here they are amplified, appearing at TR3 collector and again having undergone no phase change. Out-of-phase signals therefore appear at TR2 and TR3 collectors.

The output of the amplifier is directly coupled to the c.r.t. X deflection plates.

Capacitor C7 is used to give high frequency boost to the amplifier by bypassing R17 at high frequencies, at which it has a low reactance. VR4 is the X Shift control. Pre-set resistor R16 is adjusted to enable the X shift control to deflect the spot equally either side of centre. A shift of approximately 2 cm. either side of centre should be possible.

The X amplifier is constructed on a printed circuit board measuring 3 by  $1\frac{1}{2}$  in. A diagram giving etching details of the board is shown in Fig. 9, and a second diagram of the board showing the component layout is given in Fig. 10. In common with all the other printed circuit board etching diagrams in this article, Fig. 9 is reproduced full size and may be traced.

The X amplifier board is mounted to the chassis in the position indicated in Fig. 2, being insulated from it by stand-off washers or by sandwiching a piece of polystyrene tile cut to the same dimensions between it and the metal. The input to the X amplifier is at the two sockets on the front panel marked 'X' in Fig. 1, and also at the coaxial socket, which is connected in parallel.

All leads at the input of the X amplifier must be screened. The capacitance to earth of the lead coupling the slider of VR3 to C5 should be kept low. The mains lead to the on-off switch on the front panel must be kept well clear of the f.e.t. and the input wiring, to prevent pick-up of mains hum.

When completed and checked for mistakes, the unit should be turned on, having first set R16 for maximum resistance (turned fully anti-clockwise). R10 should be

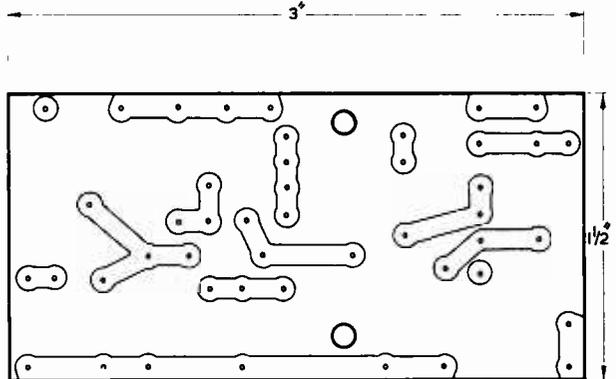


Fig. 9. The copper side of the X amplifier printed circuit board

This is reproduced full size and may be traced

# COMPONENTS

## Resistors

(All fixed values  $\frac{1}{2}$  watt 10%, unless otherwise stated)

R1	15k $\Omega$ 5 watt
R2	33k $\Omega$ 2 watt
R3	56 $\Omega$ 1 watt
R4	220k $\Omega$
R5	39k $\Omega$
R6	12k $\Omega$
R7	1M $\Omega$
R8	6.8M $\Omega$
R9	4.7k $\Omega$
R10	1k $\Omega$ vertical skeleton pre-set
R11	82k $\Omega$
R12	3.9M $\Omega$
R13	39k $\Omega$
R14	470 $\Omega$
R15	39k $\Omega$
R16	100k $\Omega$ horizontal skeleton pre-set
R17	1.2k $\Omega$
R18	270k $\Omega$
R19	3.3k $\Omega$
R20	15k $\Omega$
R21	680 $\Omega$
R22	82 $\Omega$
R23	12k $\Omega$
R24	10M $\Omega$
R25	10M $\Omega$
R26	15k $\Omega$
R27	5.6k $\Omega$
R28	1k $\Omega$ vertical skeleton pre-set
R29	27k $\Omega$
R30	27k $\Omega$
R31	2.2k $\Omega$
R32	1.2M $\Omega$
R33	56k $\Omega$
R34	10M $\Omega$ 5%
R35	1M $\Omega$ 2%
R36	100k $\Omega$ 2%
R37	11k $\Omega$ 2%
R38	110 $\Omega$
R39	47k $\Omega$ horizontal skeleton pre-set
R40	1.5M $\Omega$
R41	3.9M $\Omega$
R42	120k $\Omega$
R43	2.2k $\Omega$
R44	2.2k $\Omega$
R45	47k $\Omega$
R46	47k $\Omega$
R47	10k $\Omega$ 2%
R48	10k $\Omega$ 2%
R49	8.2k $\Omega$
R50	15k $\Omega$
R51	15k $\Omega$
R52	1.5M $\Omega$
R53	1.5M $\Omega$
VR1	100k $\Omega$ potentiometer, linear
VR2	25k $\Omega$ potentiometer, linear
VR3	2M $\Omega$ potentiometer, linear
VR4	500k $\Omega$ potentiometer, linear
VR5	500k $\Omega$ potentiometer, linear
VR6	100k $\Omega$ potentiometer, linear
VR7	2M $\Omega$ potentiometer, linear
VR8	100k $\Omega$ potentiometer, linear

R.R.V.  
Q.W.O.  
B.A.R.O.  
B.R.B.C.

## Capacitors

C1(a)(b)	32 + 32 $\mu$ F electrolytic, 350 V.Wkg.
C2	4 $\mu$ F paper, 500 V.Wkg. (see text)
C3	1,000 $\mu$ F electrolytic, 16 V.Wkg.
C4	1,000 $\mu$ F electrolytic, 16 V.Wkg.
C5	0.047 $\mu$ F plastic foil
C6	100 $\mu$ F electrolytic, 16 V.Wkg.
C7	5,000pF plastic foil
C8	1 $\mu$ F plastic foil
C9	0.1 $\mu$ F plastic foil
C10	0.01 $\mu$ F plastic foil
C11	1,000pF silvered mica
C12	100pF silvered mica
C13	200 $\mu$ F electrolytic, 10 V.Wkg.
C14	0.15 $\mu$ F plastic foil
C15	10 $\mu$ F electrolytic, 16 V.Wkg.
C16	2,000pF plastic foil or silvered mica (see text)
C17	120pF silvered mica (see text)
C18	10 $\mu$ F electrolytic, 16 V.Wkg.
C19	0.22 $\mu$ F plastic foil
C20	2,000pF paper, 500 V.Wkg.
C21	0.1 $\mu$ F disc ceramic
C22	0.1 $\mu$ F disc ceramic
C23	0.5 $\mu$ F electrolytic, 12 V.Wkg.

## Transformer

T1 Mains transformer. Secondaries. 250-0-250V at 80mA, 6.3V at 3.5A, 6.3V at 1A, Douglas type MT1

## Semiconductors

TR1	2N3819	TR9	BC117
TR2	BC117	TR10	BC169C
TR3	BC117	TR11	BC117
TR4	TIS43	TR12	XB113
TR5	BC169C	TR13	XB113
TR6	BC169C	D1	1N4007
TR7	BC109	D2	1N4007
TR8	BC117	D3	1N4006
D4-D7	Selenium bridge rectifier. 12V 0.5A		
D8	12V 3 watt zener		
D9	BZY88C24		
D10	ZL100		
D11	BAY31 or similar		
D12	BAY31 or similar		

## Tube

Cathode ray tube type 3BP1

## Switches

S1	s.p.s.t. toggle
S2	2-pole 6-way rotary
S3	3-pole 4-way rotary
S4	s.p.s.t. toggle

## Miscellaneous


10 control knobs  
B14A c.r.t. base  
Flush-mounting coaxial socket  
4 3mm. insulated sockets  
5-way tagstrip, centre tag earthed  
Capacitor clip (for C1)  
Printed circuit board  
Aluminium for case, chassis and c.r.t. mounting  
Veroboard panel  
Perspex for graticule  
Screened lead  
4 rubber feet

**Table I  
Specification**

Cathode Ray Tube. 3BP1, giving 2½ in. viewing area.  
Timebase. 6-position switch plus fine frequency control.  
Ranges: 1, timebase off; 2, 5-50Hz; 3, 50-500Hz;  
4, 500Hz-5kHz; 5, 5-50kHz; 6, 50-500kHz.  
X Amplifier. Input impedance, 1.8MΩ. Sensitivity,  
15mV/cm. Bandwidth, less than 5Hz to 250kHz at  
-3dB. X input provided.  
Y Amplifier. Input impedance, 1.5MΩ. Sensitivity,  
10mV/cm. Bandwidth, less than 5Hz to approx. 1MHz  
at -3dB. Useful response to beyond 2MHz. Four  
position attenuator, X1, X10, X100, X1000.  
Sync. Internal sync.


**Table II  
Control Functions**

S1 Mains on-off  
S2 Timebase range  
S3 Y attenuator  
S4 Sync. on-off  
VR1 Focus  
VR2 Brilliance  
VR3 X amplifier gain  
VR4 X shift  
VR5 Timebase fine frequency  
VR6 Y shift  
VR7 Y input gain  
VR8 Astigmatism

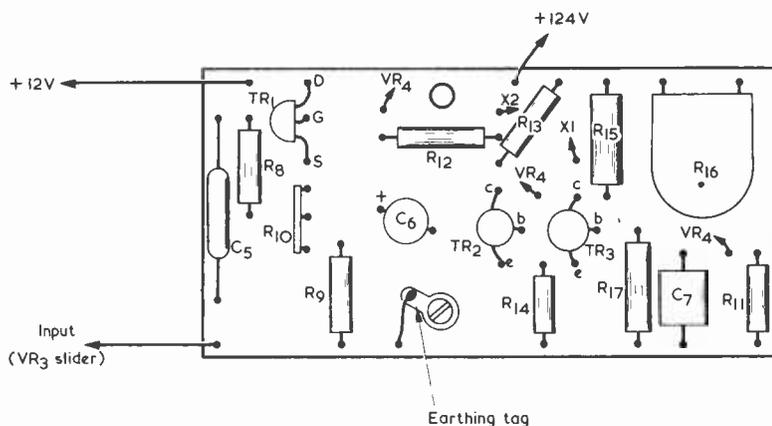

*Fig. 10. The component layout on the X amplifier board*

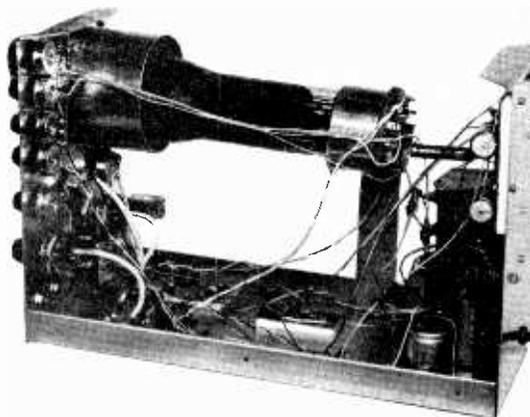*Another view inside the oscilloscope. The use of circuit modules represents an attractive constructional approach*



adjusted for half resistance at the outset, and then adjusted to give 6 volts (plus or minus 1 volt) at TR1 source.

After the tube has had time to warm up, it should be possible to bring the spot on the screen by adjusting the X shift control. R16 should now be reduced in resistance until the X shift control can move the spot an equal distance on either side of centre.

The circuit is very sensitive, and if it is working properly, touching the positive X input terminal will produce a line across the screen, the length of which can be controlled by the X gain control.

**NEXT MONTH**

The remainder of the constructional details of the oscilloscope will be discussed in the concluding article, to be published next month. The Components List accompanying the present article includes all the parts that are required. Some of the components will, in consequence, be referred to next month.

(To be concluded)

# SHORT WAVE NEWS

## FOR DX LISTENERS



By Frank A. Baldwin

Times = GMT

Frequencies = kHz

After some time spent searching for a clear 49 metre band outlet, Lakeland Radio, Blantyre, Malawi is reported by BADX (British Association of Dxers) operating on **9510** (31.55 metres) and signing-off at 2200. The schedule is from 0330 to 0430 (latter time is subject to some variation) and from 1845 to 2100 sign-off, also apparently liable to alteration. All programmes are in English from this 100kW transmitter.

### AROUND THE DIAL

#### ● LEBANON

Beirut has been heard signing-on with the National Anthem, station identification in English and a newscast in the same language at 1800 on **15170** (19.78m).

#### ● AUSTRALIA

The best time to hear transmissions from this country is, of course, in the early mornings around 0700 but it can be logged during the afternoons on occasions. We logged Radio Australia at 1520 on **7235** (41.47m) when a programme in English to S.E. Asia "Politics in Australia" was being radiated.

#### ● SOUTH AFRICA

Radio South Africa from Johannesburg may be heard during the evenings at 1900 on **15175** (19.77m) when radiating station identification and a newscast in the English programme.

For a more difficult exercise in the reception of South Africa, try the Internal English Service on **4965** (60.42m) from around 1930 onwards. Logged recently at 2100 with a programme of dance music records.

#### ● ECUADOR

If you are interested in Dx, why not listen to "DX Party Line" broadcast every Tuesday in the English programme which commences at 1930 from HCJB Quito on **17755** (16.90m) and in parallel on **15155** (19.80m) and **11715** (25.61m). The programme is mainly supported by listener reports from the USA but is nevertheless of interest to SWL's in the UK.

#### ● CUBA

Havana can be heard, in English, from 2015 on **15140** (19.81m) but do not be surprised if you later hear Hanoi, Vietnam on the same channel in English – it is merely a relay.

#### ● EGYPT

The Arab Republic of Egypt can be heard every evening with station identification and the news in English at 2200 on **9805** (30.59m) in the European Service. Address your reports to – European Service, P.O. Box 566, Cairo.

#### ● YUGOSLAVIA

Radio Belgrade may be heard with identification and a newscast in English at 2200 on **9620** (31.18m).

#### ● U.S.A.

WINB Red Lion is currently signing-on in English at 2100 on **15185** (19.75m).

#### ● INDIA

All India Radio, Delhi, can be logged if conditions are right on **4860** (61.72m). We heard it at 2200 with the news in English until 2210, a talk on Indian affairs until 2215 when, after station identification, local songs and music were radiated. Also logged on another occasion at 1930 with a programme of local music.

AIR Bombay has also been logged at 1840 on **15080** (19.89m) with programme of Indian music. Station identification and news in English at 1945.

#### ● ITALY

The news in English from Rome can be heard, after identification, at 1930 on **11800** (25.42m), but see below.

#### ● SRI LANKA

The **11800** channel also carries a programme of local music and songs from Colombo which may be heard around 1530, recently logged by us from 1520 through to 1550.

#### ● ROUMANIA

Bucharest radiates the news in English at 1930 and can be heard on **11775** (25.47m).

#### ● MALAYSIA

The BBC transmitter at Tebrau may be heard with the news in English at 2200 on **9570**.

#### ● PAKISTAN

Radio Pakistan, Karachi, may be heard with the local news in English from 1915 to 1920 on **9460** (31.71m).

#### ● CHINA

Some loggings of Radio Peking in recent weeks have been – **4865** (61.66m) at 2210, talks in a local dialect; **4905** (61.16m) at 2220, female in Chinese dialect; **7256** (41.34m) at 1435, dialogue in Chinese; **9020** (33.25m) at 2020, in Chinese; **9365** (32.03m) at 1500, sign-on with "East is Red" then into Russian – soon jammed; **11770** (25.48m) at 1542, female still talking; and on **15030** (19.96m) at 2005, programme in English about Chinese achievements.

#### ● BRAZIL

If the LF bands are reasonably 'open', ZYX2 Radio Brasil Central, Goiania, on **4995** (60.06m) can be heard from around 2100 or so. Logged here recently at 2120 with Latin American music and announcements in

Portuguese.

Another Brazilian station to look for is ZYR56<sup>W,4</sup> Radio Excelsior, Sao Paulo, on **9585** (31.29m) around 2200. We logged it at 2210 with a sports commentary.

● **BOTSWANA**

Radio Botswana, Gaborone, can sometimes be heard in the U.K., conditions permitting, on **4845** (61.91m) around 1830. We logged it recently at 1850 when African drums and native musical instruments were blended in a rhythmic sequence which went on, and on, and on!

● **ANGOLA**

Radio Clube do Huambo has a 10kW signal that is worth searching for on **5060** (59.28m) around 2230, programming is in Portuguese. Our last two loggings of this station however were marred by a continuous heterodyne on the channel – but we live in hope!

● **CAMEROON**

Radio Garoua on **5010** (59.88m) is more often than not blotted out by teletype transmissions but we did manage to hear the station at 2220 recently on a clear channel for a change. African chants by a chorus (!) of young ladies delighted our ears. Local 'pops' presumably!

GMT	Freq.	Stn.	Rcvd.
1435	7256	R. Peking	
1500	9365	R. Peking	
1520	7235	R. Australia	
1520	11800	Colombo	
1542	11770	R. Peking	
1800	15170	R. Beirut	
1830	15485	R. Libre	
1840	15080	Bombay	
1845	9510	Lakeland Radio	
1850	4845	R. Botswana	
1900	15175	Johannesburg	
1915	9460	R. Pakistan	
1925	4926	EAJ206 Bata	
1930	4965	Johannesburg	
1930	11715	HCJB Quito	
1930	15155	HCJB Quito	
1930	17755	HCJB Quito	
1930	4860	Delhi	
1930	11800	Rome	
1930	11775	Bucharest	
1945	15080	Bombay	
2005	15030	R. Peking	
2015	15140	R. Havana	
2020	9020	R. Peking	
2100	15185	WINB Red Lion	
2115	15105	R. Grenada	
2120	4995	ZYX2 R. Brasil	
2200	9585	ZYR56 R. Excelsior	
2200	9805	Cairo	
2200	9620	R. Belgrade	
2200	4860	Delhi	
2200	9570	Tebrau	
2210	4865	R. Botswana	
2220	4905	R. Peking	
2220	5010	R. Garoua	
2230	5060	R.C. do Huambo	

● **CLANDESTINE**

Radio Libre, with identification and talk in Portuguese, was recently logged by us on **15485** (19.37m) at 1830.

● **WINDWARD ISLANDS**

Radio Grenada operates on **15105** (19.86m), where we recently heard a programme in English at 2115 about tourism in the West Indies.

● **EQUATORIAL GUINEA**

EAJ206 Bata, Rio Muni, may be heard on **4926** (60.90m) during the evenings here in the U.K. Programming is mainly in Spanish and we logged it at 1925.

**TIME-CHECK**

The transmissions featured in *AROUND THE DIAL* are listed here on a time-check basis for the convenience of readers.

**NOW HEAR THESE**

● **INDONESIA**

"The Voice of Indonesia", Jakarta, currently radiates a programme in English, directed to the U.K., Europe and New Zealand, from 1900 to 2000 on **11715** (25.60m).

● **SRI LANKA**

The English Service from Colombo may be heard from 1230 to 1730 on **7190** (41.72m), **9720** (30.85m) and on **15120** (19.84m).

● **BRAZIL**

The Brasilia International Service beams an English programme to Europe from 2200 to 2300 on **11720** (25.59m) and on **15447** (19.42m). but, according to reports, the time schedule is subject to variation.

● **IRAN**

Radio Iran is now back (at the time of writing) on **9030** (33.22m) and has vacated the **12180** channel.

● **FINLAND**

Broadcasts in English to Europe daily from Finland may be heard from 1400 to 1430 and from 1800 to 1830 on **15185** (19.75m) and from 2030 to 2100 on **9550** (31.41m).

● **KUWAIT**

The English programme from Radio Kuwait has been logged at 1710 on **15415** (19.46m). Current schedule in English is from 1630 to 1900, also in parallel on **9750** (30.76m).

● **CONGO REPUBLIC**

Brazzaville may be heard in the evenings on **15190** (19.74m) we logged it at 1950 when a programme of typical African music was being broadcast, identification in French at 2100. "The Voice of the Revolution" carries the local domestic service and is on the air from 0600 to 1300 and from 1500 to 2130.

● **INDIA**

AIR Delhi can be heard with a programme in English from 2100 on **11620** (25.81m). We logged it at 2110 and learned about the 5-year village improvement scheme.



# CYCLOPS

## PART SIX

by L. C. Galitz

**This is the sixth and concluding article in the series concerning robots and cybernetic devices, and it describes the circuit operation and construction of the conditioned reflex circuits. Also dealt with is the battery charger unit.**

**I**N LAST MONTH'S ISSUE THE BASIC OPERATION OF THE conditioned reflex circuitry was described, after which the circuit for the conditioned reflex unit was published, as Fig. 27, together with the Components List. Fig. 27 should now be consulted, since its operation will next be discussed in detail.

### CIRCUIT OPERATION

In Fig. 27, the area enclosed by the dotted line is built on the new Veroboard panel, and above and below the dotted line are existing components such as RLA/4, RLB/1, RLC/1 and their contacts. There are also new components such as X2, the magnetic sensor, S4 and S3. The operation of the circuit is fairly straightforward, apart from a few details which are somewhat unusual – these are explained below.

The output from the inhibit Ss gate triggers the differential monostable via R26 and C6. The two monostables in this circuit have a diode in the collector of the transistor which is normally turned off. This is to ensure that if there is a momentary reduction in the supply rail voltage, these diodes will be reverse biased, and the potential on the collectors of TR17 and TR22 will be held up by the charge across C7 and C9 respectively. This prevents spurious triggering of the monostables.


The extension monostable is fired directly by X2, a reed switch acting as a magnetic sensor, via C8. R37 holds the X2 end of C8 negative until the switch is triggered. The output of this monostable passes to the base of TR20, whilst the output of the differential monostable passes to TR19. These two transistors, along with R30, form the coincidence And-gate, using the current sinking logic principle. In other words, the emitters of the transistors are kept near the earth potential unless *both* transistors cut off, and this only happens when both bases are negative, which in turn only occurs when both monostables have fired at the same time. At all other times, the current through R30

is sunk to earth via either or both transistors. The output of the gate passes via D5 and R31 to the summing capacitor. D5 prevents the capacitor discharging through the gate when it is closed, and R31 allows the capacitor to charge up only by a certain amount every time the gate opens. S4 is wired across the summing capacitor and is labelled 'Forget' – it is used when one wishes to erase Cyclops' memory of previous experiences and start afresh on a new experiment.

TR23 in the common collector mode acts as a current amplifier for the summing capacitor. In the emitter circuit of this transistor is wired a potentiometer which sets the threshold level of the Schmitt trigger formed by TR24, TR25 and associated components. It so happens that all three outputs from the Schmitt trigger require the inverted function rather than the normal one, and therefore the output is taken from the first collector.

It will be noticed that the time-constant resistor for the extension monostable is split into two halves, R34 and R35. The junction between the resistors is connected via D7 to the output of the Schmitt trigger. When the Schmitt trigger is in its unfired state the cathode of D7 is negative and the diode conducts, reducing the effective overall time-constant resistance. When the Schmitt trigger fires, this diode is reverse biased, and both resistors come into normal operation. In the prototype, the two monostable quasi-stable periods were seven and ten seconds respectively.

The first output And-gate, the inhibit En gate, consists of TR26, and TR27 and R44. This gate operates in similar fashion to the coincidence And-gate. The output of this gate passes directly to TR28, the relay driver, and it has the usual diode to prevent relay transients damaging the driving transistor. The bases of the transistors forming the And-gate couple directly to the Schmitt trigger output and the monostable output respectively. This is possible because the transistors operate in the common collector mode and therefore have a high input impedance.

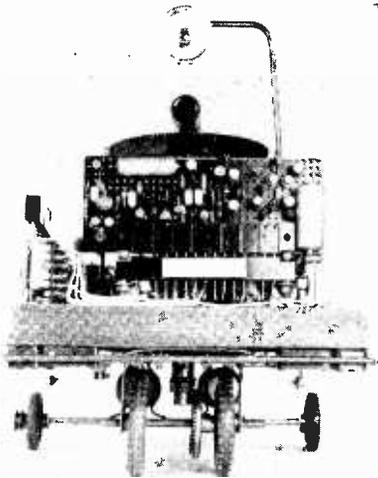

On the other hand, the transistors forming the 'instigate conditioned response' gate, TR29 and TR30, are in the common emitter mode, and they connect to the Schmitt trigger output and the S<sub>n</sub> input via resistors. As with the previously mentioned gate there is a relay driver, TR31, wired directly to the output of the gate, again with the usual protection diode. From the output of this gate passes a wire to S3(c), and from this switch to the base of TR15 in the inhibit S<sub>s</sub> gate, so that the automatic reinforcement feedback loop is inhibited when the switch is set to the 'magnetism means light' mode.

The other two sections of S3, which is the mode selector switch, occur in the input switching of S<sub>s</sub>, and in the output switching of E<sub>s</sub>, in the 'touch' mode, S<sub>s</sub> is connected via S3(a) to the make contact of RLA2, of which the common contact and the break contact are already in the basic reflex circuitry. (See Fig. 14, published in Part 3). At this point it should be noted that the positive lines of both the learn circuitry and the basic reflex circuitry are joined together. In the 'light' mode, S<sub>s</sub> connects to the make contact of RLC1; the common contact connects to the earth line via RLA2. (This is just for convenience when wiring – it could connect straight to the earth line).

When switched to the 'touch' mode the E<sub>s</sub> output passes to pin 6 of the basic reflex circuitry socket via S3(b), i.e. to the base of TR1, which operates RLA/4; and, when switched to the 'light' mode, the E<sub>s</sub> output passes directly to RLC/1 coil. The output from En always goes to RLB/1 so that, when En is activated, Cyclops' motors cut off until the extension monostable reverts to its normal state.

It can now be appreciated why relays RLB/1 and RLC/1 were specified as having dual coils – in each case, one relay coil appears in the basic reflex circuitry and the other coil appears in the conditioned reflex circuitry. The isolation of the two coils helps keep the two sets of circuits separate.

The arm of S3(a) connects to the base of TR16, one of the two transistors in the 'inhibit S<sub>s</sub>' gate. Resistor R23 keeps this transistor cut on until the appearance of the pulse from either RLA2 or RLC1.

DECEMBER 1972

## COMPONENTS

All resistors and capacitors are standard components as specified in the Components List, which was published last month. The diodes are all silicon, and D5 should be chosen to have a high back resistance to limit discharging of the summer capacitor. Transistors TR19 and TR20 are n.p.n. silicon planar, with the leads having the e-c-b sequence. TR26 and TR27 are normal n.p.n. transistors, whilst all the others are p.n.p. transistors. The monostable transistors may have to be selected, as some cause spurious triggering of the circuit – in other words, some transistors have a property of being more susceptible to noise than others. The writer encountered this problem with some of the transistors he had on hand, but quite a number worked quite satisfactorily, giving no trouble at all. It is possible that the risk of spurious triggering could be reduced by adding a bypass capacitor, of around 0.047μF, across the supply rails, although this was not found necessary by the writer, who had little difficulty in finding suitable transistors.

TR23 should be selected for low leakage – a transistor with too high a leakage would cause C10 to discharge too quickly. This capacitor may also have to be selected for low leakage, and although capacitors working well below their rated voltage have in general a lower leakage figure, the author found no trouble with the several samples tried, which were working at half rated voltage in the circuit.

### COMPONENTS

#### Resistors

R1	2.2kΩ ½ watt
R2	27Ω ½ watt (see text)
R3	330Ω 1 watt
R4	2.2kΩ ½ watt
R5	27Ω ½ watt (see text)
VR1	15Ω potentiometer, wirewound, preset

#### Capacitor

C1	1,000μF electrolytic, 20 V. Wkg.
----	----------------------------------

#### Transformer

T1	Mains transformer, secondary 12V at 0.5A. Douglas type MT111AT
----	--

#### Semiconductors

TR1	AC127
TR2	AD161
TR3	AC127
D1-D6	Silicon diodes (see text)
W1	Bridge rectifier 24-36V, 1A

#### Switches


S1-S4	s.p.s.t. toggle
-------	-----------------

#### Neon


NE1	Neon bulb assembly with integral series resistor.
-----	---

#### Miscellaneous

	Mica washer and insulating bushes (for TR2)
	Multi-way cable
	Chassis, tagboard, etc., (see text)

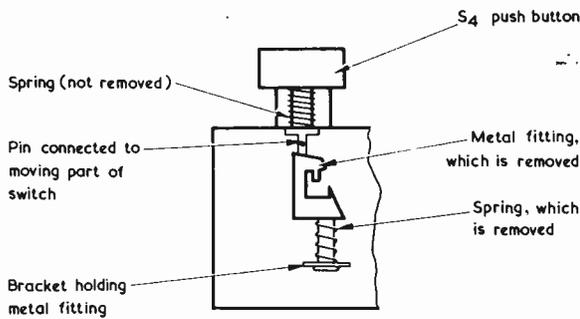

(a)

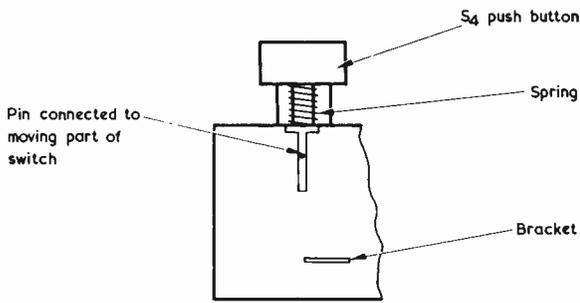

(b)

Fig. 28 (a). Switch S4 before modification  
(b). How the switch appears after modification

X2 is an R.S. Components reed switch, and the Veroboard connector used by the author was a Painton 15-way component. If difficulty is experienced in obtaining this connector a 16-way edge connector (Home Radio Cat. No. BTS45) could be employed with a 16-

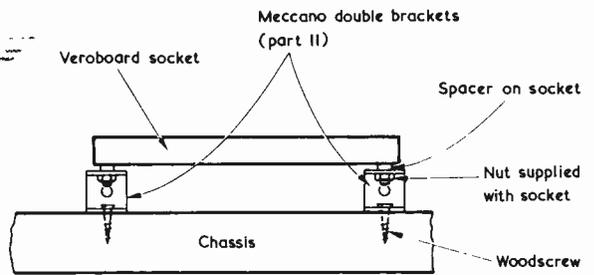



Fig. 29. Mounting the 15-way Veroboard socket. This is a view from the front of Cyclops

way piece of Veroboard, as was suggested for the board that is already fitted to Cyclops. The 16th way would, of course, be ignored when wiring up. Details of the relays RLB/1 and RLC/1, and of S3 and S4, were given in Part 3 of this series. However, although S3 is of the press-to-changeover, press-to-changeback, as on the switch-bank obtained, S4 is of the press-to-changeover, release-to-changeback variety, and was modified by removing a small metal fitting and a spring on the back of the switch. Details of this modification are shown in Fig. 28. Alternatively, separate switches can be obtained and mounted on the main control panel.


Battery BY3 is exactly the same as BY1, a Deac 6V 225mA/H rechargeable battery, but, as mentioned in Part 3, could be an Ever Ready PPI.
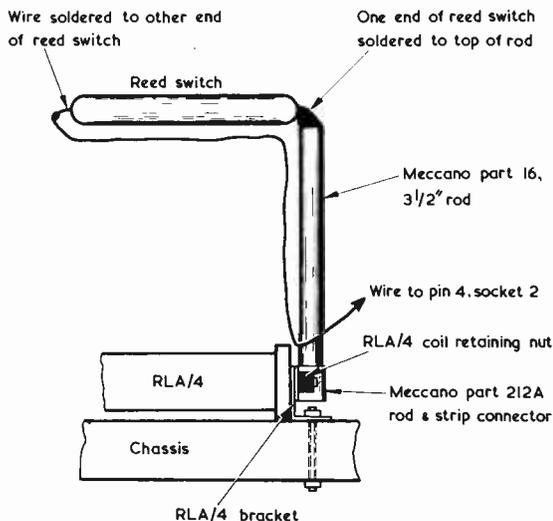
### CONSTRUCTION

If the reader has obtained the Painton 15-way connector, this is mounted on the baseboard using a pair of Meccano double brackets as shown in Fig. 29. If the alternative 16-way connector is employed, this may be fitted in the same way as was the connector for the first board. The reed switch is next mounted using a Meccano rod, and rod and strip connector. Details of



(a)

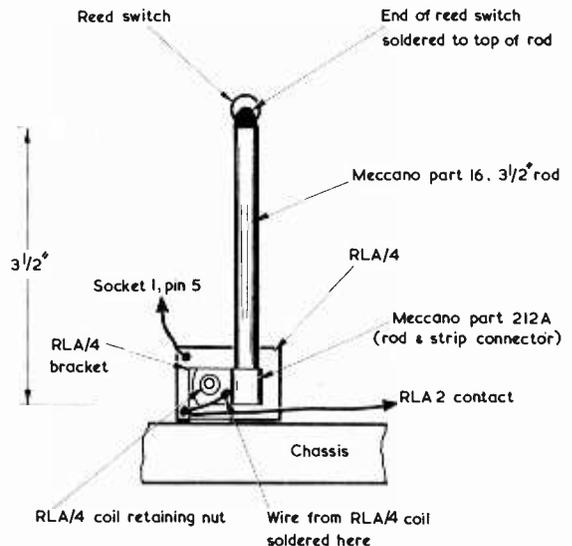

(b)

Fig. 30 (a). View from rear, showing the method of mounting the reed switch  
(b). Another view, from the right side, of the reed switch mounting

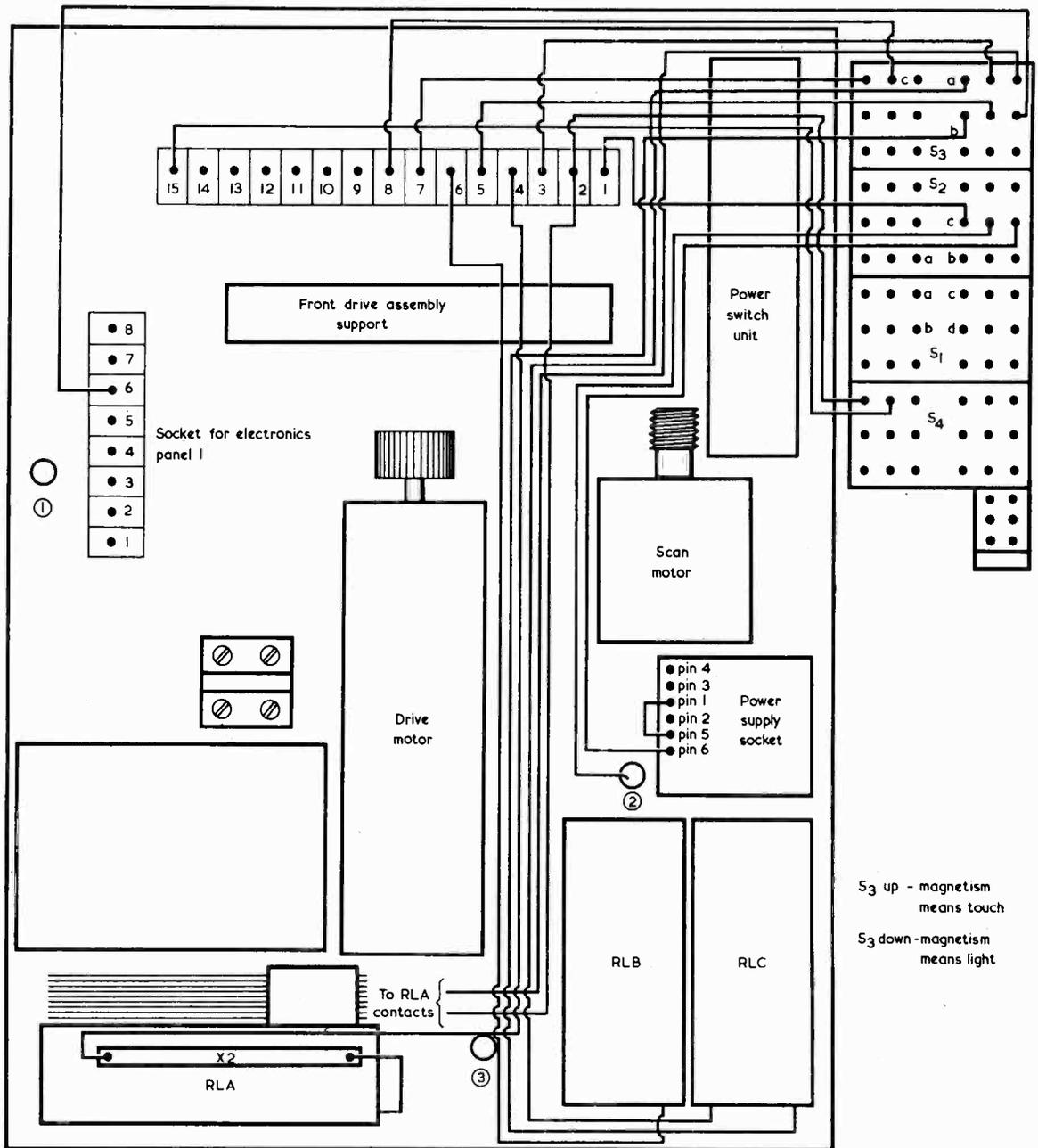


Fig. 31. The additional wiring on the main baseboard. As it is difficult to interpret diagrams in which the wires run closely together, as here, it is advisable to check against the circuit of Fig. 27 during wiring

how this assembly is built, and how it is mounted on the coil retaining nut of RLA/4 are given in Figs. 30(a) and (b).

The additional wiring can be carried out according to Fig. 31. Fig. 32 gives details of the wiring to the pins of the relays, which is not shown in sufficient detail in Fig. 31. It should be noted that the centre contact of RLC1 must be connected to the electronics earth, and the make contact of RLC1 should be connected to S3 (a). If the reverse is done, the circuit will not function correctly.

DECEMBER 1972

At this stage the Veroboard panel may be dealt with. This measures 2 by 5 in. and has 13 strips, each with 33 holes. If the Painton 15-way connector is to be used, the area bounded by the holes K7, M7, K27 and M27 must be cut out, after which the connector can be mounted by enlarging the holes L6 and L28. These holes are illustrated in Fig. 33 and 34, which show the component and copper sides of the board respectively.

Next, cut the strips as indicated in Fig. 34. In wiring the board several points need to be observed. One of the lead-outs of R46 passes through the hole F17 (at which

323

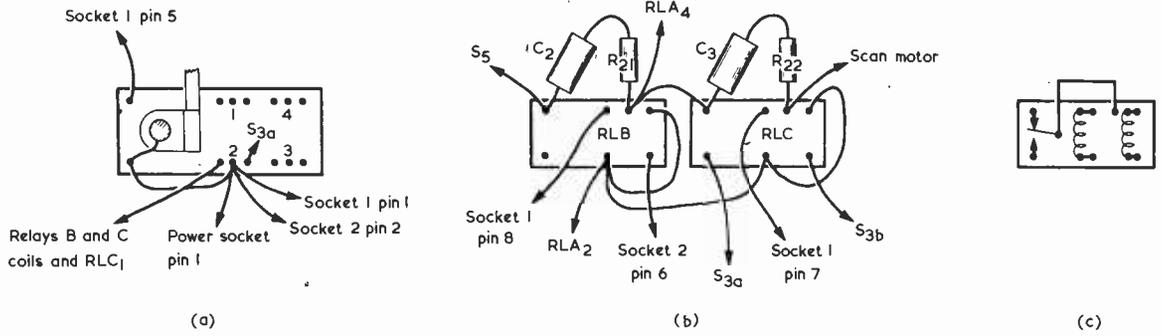


Fig. 32 (a). Wiring at RLA<sub>2</sub>. The additional connections are to S<sub>3</sub> (a) and RLC<sub>1</sub> (b). Connections to relays RLB and RLC. This includes existing wiring. RLB and RLC are wired in the mode shown here so that fields from separate coils assist each other. (It may be necessary to alter the existing wiring to the coils to achieve this)

(c). Pin designation for relays RLB and RLC

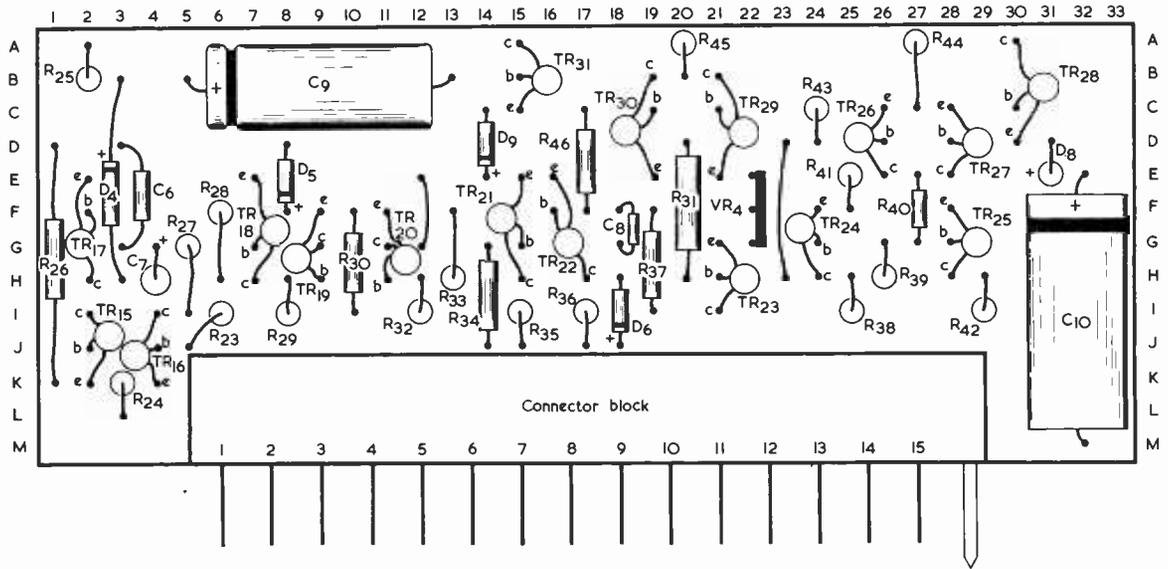


Fig. 33. Components side of Veroboard panel No. 2

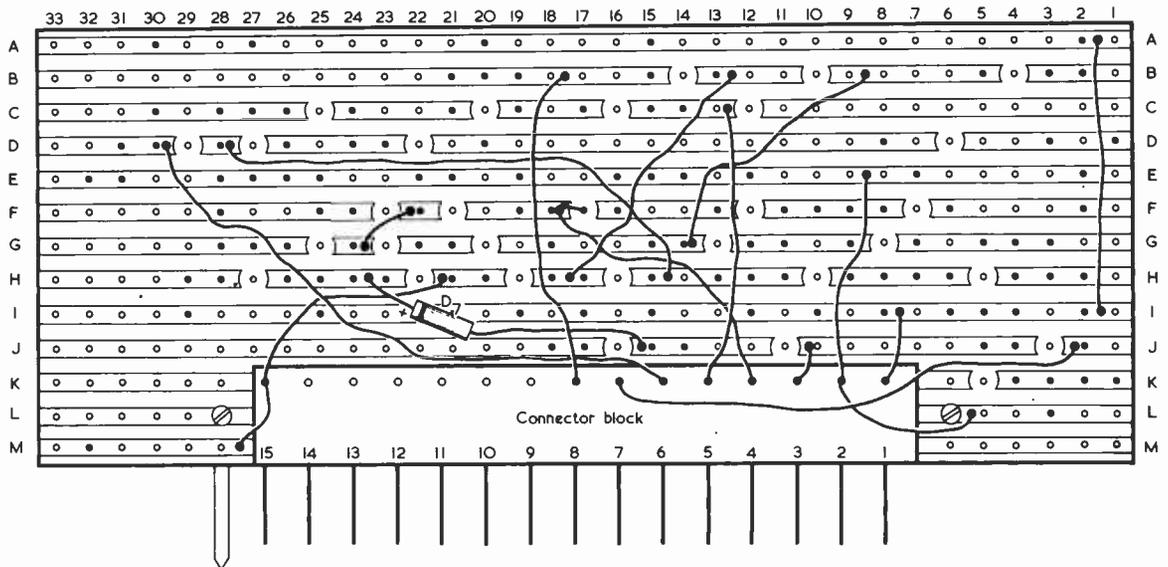


Fig. 34. The copper side of the Veroboard panel

the copper strip has been cut) and connects to the copper strip adjacent to F18. Diode D7 is mounted on the copper side of the board. There are, also, a number of links on the copper side of the board, these consisting of insulated wires soldered direct to the copper strips. Where possible, component lead-outs adjacent to the link connection points should be soldered before the links are fitted.

It is recommended that the circuit be built in stages; firstly the two monostables, then the coincidence gate and the inhibit Ss gate. Following this, the summer, Schmitt trigger, and finally, the output gates should be built. As each stage is completed the circuit can be tested. Any errors can be checked easily, because any faults that develop must be in the stage after the one previously tested. The polarities of the capacitors, diodes and transistors should be carefully checked before testing. When the circuit has been fully built and tested, the final setting up can take place.

## SETTING UP

It may be found that minor difficulties occur during testing, and these may crop up due to tolerance spreads in the components used. There is only one resistor specified in the Components List which may need its value slightly changed, and that is R26. If this value is too small, Ss will not inhibit; if the value is too large, Ss will not trigger reliably. The author found that it was easiest to start with the resistor too small in value. Connect TR15 base to the negative rail via a 1kΩ resistor, and trigger the Ss input, increasing the value of R26 until the differential monostable does not fire. If, then, TR15 base is connected to the positive rail by a 10kΩ resistor, the differential monostable should trigger reliably every time Ss input is applied.

The monostable resistors governing the time-constant in the prototype were 6.8kΩ for the differential monostable, and two 15kΩ in series for the extension monostable. These give monostable quasi-stable periods of 0.6 seconds calculated, against 0.8 seconds in actual fact, for the differential monostable; and 8.6 seconds calculated, against 10 seconds in fact, for the extension monostable with the Schmitt trigger fired. With the Schmitt trigger in the normal unfired state, the monostable period is 7 seconds.

In the prototype, with R31 at 1kΩ, the summer needs six coincidences to give an output of 4 volts, at which potential the threshold of the Schmitt trigger is set. However, this figure is based on measurements obtained with coincidences made one immediately after the other. In normal operation, approximately ten coincidences are required before the Schmitt trigger fires. Constructors may wish to vary the value of R31 to make the number of coincidences required more or less. VR4 sets the Schmitt trigger threshold, and in the prototype this potentiometer was set to operate the trigger upon receiving an output of 4 volts from the summer.

Now the conditioned reflex unit should be complete, and Cyclops should behave in a more intelligent manner, modifying his actions to suit his environment, and he should be enjoying himself more than he did during his uneducated days.

## CHARGING UNIT

In one of the photographs accompanying Part 1 of this series, Cyclops was shown having his batteries charged by a special charging unit coupled up to the 6-way power socket. Although any suitable method of charging the batteries may be employed, readers may prefer to use the charging unit employed by the author.


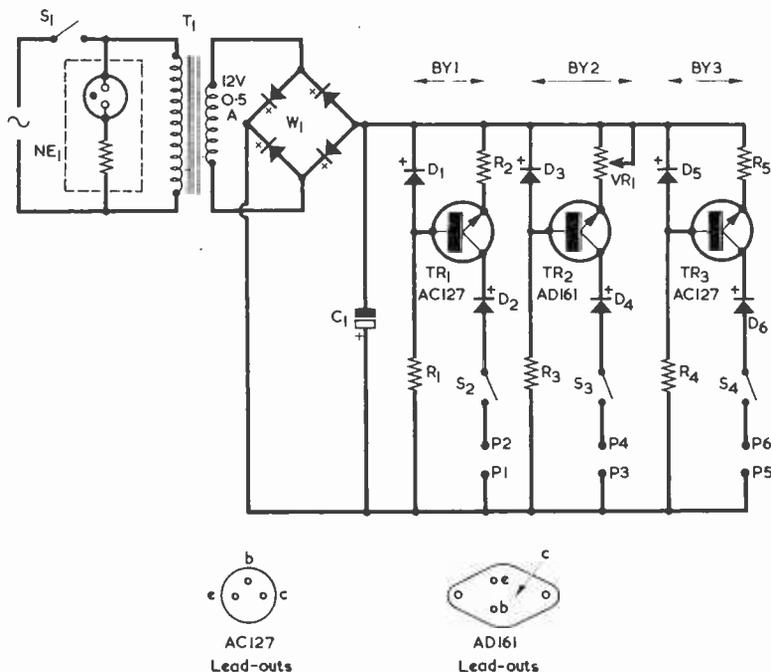


Fig. 35. The circuit of the battery charging unit

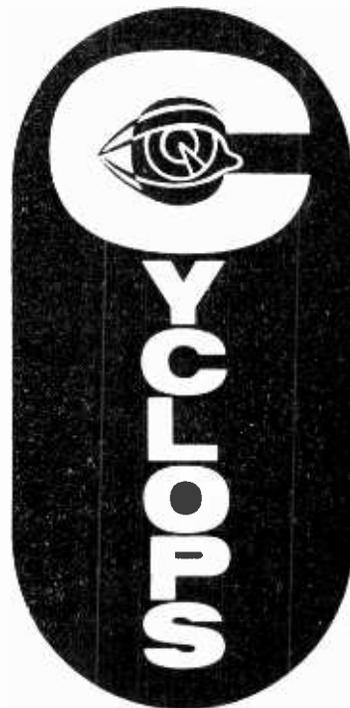

Brief details of this unit will now be given.

The circuit of the unit appears in Fig. 35. The a.c. mains input to T1 primary is switched by S1. The secondary output of 12 volts is rectified by W1 and smoothed by C1. The rest of the circuit consists of three constant current devices, one for each battery to be charged.

Considering the first constant current device, TR1 is germanium; therefore D1, a silicon diode with a voltage of about 0.7 volt across it, is sufficient to provide a constant voltage to TR1 base, TR1 being wired in the common base mode. R1 supplies sufficient current through the diode to swamp the current taken by TR1 base even when TR1 is passing the full constant current. As TR1 is in the common base mode, the constant current is set by the emitter resistor R2. S2 allows the charging current to be switched on and off. Diode D2 is in circuit to isolate the battery should the unit be disconnected from the mains. When this occurs D2 becomes reverse biased.

The same circuit description applies to the two other constant current devices.

The sections charging the Deac batteries BY1 and BY3 are set to give 27mA by adjusting the resistors R2 and R5. In the prototype the value required for these two resistors happened to be 27 $\Omega$  exactly. The transistors used are AC127's. The section charging BY2 is set to 200mA by adjusting VR1. This section uses an AD161 power transistor.

The charging unit is built in a 6 by 4in. aluminium chassis, with S1 to S4 and the neon indicator mounted on the front panel. The electronics is built on a 2 x 10-way tagboard. The AD161 is bolted direct to the chassis, employing a mica washer and two insulating bushes for insulation of its collector in the usual manner. Each AC127 (which has an isolated envelope) is secured to chassis with the aid of a heat clip, which also functions

as a bracket. The preset variable resistor, VR1, is mounted inside the chassis so that, once set, it cannot be accidentally disturbed. This component should be adjusted to insert maximum resistance before it is initially set up. Its resistance is then reduced until the desired 200mA charging current is achieved. A multi-way cable from the unit connects to a 6-way plug matching the power socket on Cyclops.

The mains transformer T1 is a Douglas MT 111AT offering 12 volts at 0.5amp. This is available from G. W. Smith & Co. Ltd., 3 Lisle St., London, W.C.2. Diodes D1 to D6 are any silicon diodes, but it must be remembered that D4 has to be able to pass 200mA.

The reason for including switches S2, S3 and S4 is simple. Sometimes the Cyclops electronics are run to test them without the motors, or the learn circuitry is not switched on. In either case, one battery has not been used and is still fully charged from the last time it was plugged into the charging unit. That battery is not then charged during the next charging period, it being switched out of the charging circuit by the appropriate switch.

The accompanying Components List shows the parts required for the charging unit.

## CONCLUSION

The present series of articles on Cyclops is now concluded. However, further work has been carried out since these were written, and modifications are available which teach Cyclops how to earn his living and how to give him fits of neurotic depression when encountering hard times! These modifications will be described in a few months' time and it is suggested that readers retain the copies of *Radio & Electronics Constructor* in which the present series has appeared since reference will be made to the diagrams in these. ■

## OUR NEXT ISSUE FEATURES

### Telephone Amplifier & Baby Alarm

ALSO

### Comprehensive Transistor Analyser

★ ★ ★

### Reflex Transistor V.H.F. Portable

PLUS

MANY OTHER ARTICLES BOTH CONSTRUCTION & GENERAL

ORDER YOUR COPY **NOW**


ON SALE 1st JANUARY  
PRICE 20p

**RADIO & ELECTRONICS  
CONSTRUCTOR**

Copies may also be obtained direct from the Publishers, 26p. including postage. Published by Data Publications Ltd. 57 Maida Vale, London W9

# QUIZ

# DETECTOR

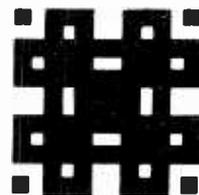

by

M. Jennings


**A reliable device which indicates, by electronic means, which of a number of switching circuits has been closed first.**

**T**HIS CIRCUIT INDICATES WHICH OF TWO PUSH-BUTTONS has been pressed first and can, in consequence, be used in a game where two contestants match their reflexes in response to a stimulus, or in a quiz in which, after a question has been posed, the first team to press its button has the first option of answering. Circuits carrying out this second function are commonly used in B.B.C. sound radio quiz programmes. There are more serious applications also, since the circuit can determine which of a pair of contacts has closed first, and can thereby evaluate the comparative performance of two relays or similar switching devices. As will be explained later, the system can be extended to any number of push-buttons or external contact sets.

## USE OF THYRISTORS

The circuit employs two thyristors (or silicon controlled rectifiers). It will be recalled that a thyristor is non-conductive until a positive pulse, relative to cathode, is applied to its gate. The thyristor then 'fires' and allows conventional current (from positive to negative) to flow through it from the anode to the cathode. Under this condition, about 0.6 volt is dropped across the thyristor. The thyristor remains conductive both in the presence or absence of a positive supply at its gate, and may only be made non-conductive again by switching off the source of anode-cathode current, or by short-circuiting the anode and cathode together.

In Fig. 1, two small thyristors type CRS1/05 are connected as shown. All the diodes in the circuit are silicon types. A 6 volt supply, which can be provided by a battery, is applied to the circuit. Let us assume that on-off switch S3 is now closed. Neither thyristor will conduct as there is no positive supply fed to either gate. Let us next say that push-buttons S1 and S2 are both pressed, with S1 closing momentarily before S2. As soon as S1 closes, a positive supply is fed to the gate of TH1 via R1, S1, R2 and the two forward biased diodes D2 and D3. A current flows in the gate-cathode circuit of the thyristor and it immediately fires, causing pilot lamp PL1 to be illuminated and the potential on the anode of the thyristor to fall to about 0.6 volt

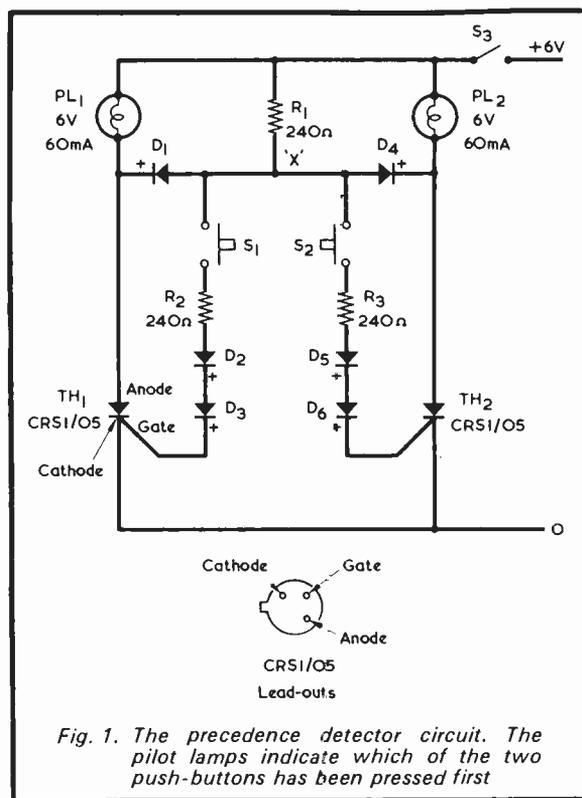

*Fig. 1. The precedence detector circuit. The pilot lamps indicate which of the two push-buttons has been pressed first*

positive of the negative supply rail. Diode D1 now conducts, bringing point 'X', at the junction of R1, D1 and D4, to a level which is positive of the negative supply rail by about 1.2 volts, this being the sum of the forward voltage drops across TH1 and D1. Diode D4 is reverse biased and no current flows through it.

With point 'X' at about 1.2 volts positive of the negative supply rail, it becomes impossible for push-button S2 to trigger TH2, because diodes D5 and D6,

being silicon types, are unable to pass any significant forward current to TH2 gate. Thus, even if S2 is closed only a split-second after S1, it will only be lamp PL1 which will become illuminated, whilst PL2 will remain extinguished. If, on the other hand, S2 is closed a split-second before S1, it is TH2 which will fire, whilst TH1 will remain non-conductive. PL2 will then light up to indicate that it is S2 which, on this occasion, has been pressed first.

To bring the circuit back, to its original condition with both lamps extinguished it is necessary to open on-off switch S1 and then close it again.

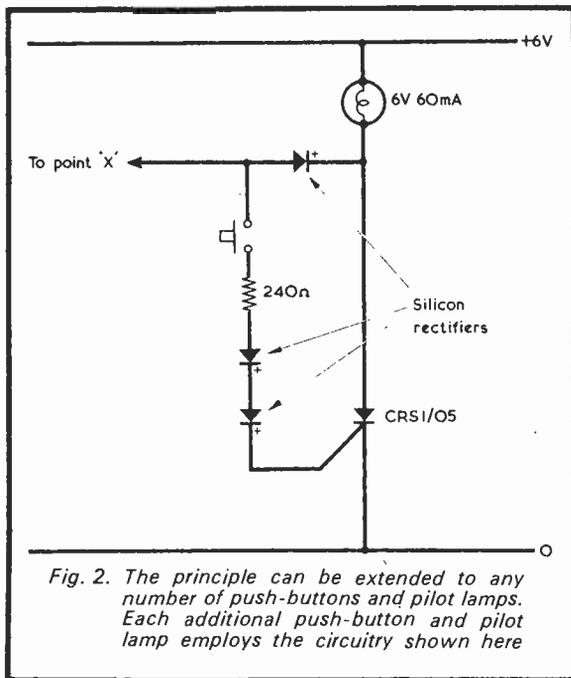


Fig. 2. The principle can be extended to any number of push-buttons and pilot lamps. Each additional push-button and pilot lamp employs the circuitry shown here

## COMPONENTS

In the author's circuit S1 and S2 were push-buttons, as shown. Alternatively, two pairs of terminals can be provided for connection to external contact sets whose performance is to be evaluated. Diodes D1 to D6 can be any silicon rectifier diodes. The author used rectifiers type 1N4002, which happened to be on hand. The resistors are ½ watt 10% types.

The author employed low-consumption m.e.s. pilot lamps rated at 6 volts 60mA (Home Radio Cat. No. PL7) in order to keep battery drain reasonably low. Lamps drawing a slightly larger current may be substituted, if desired, but care should be taken to ensure that their cold resistance (which can be many times greater than their hot resistance) is not so low as to cause an initial current in excess of 1 amp to flow in the associated thyristor at the instant of firing. The cold resistance of the bulbs to be used should be measured with an ohmmeter, and if it is less than 6Ω (which, of course, allows 1 amp to flow at 6 volts), a fixed resistor should be inserted in series with each bulb to bring the total resistance up to, or slightly greater than, this figure. The voltage dropped across the series resistor will be low when the bulb is lit and has attained its hot resistance value. Series resistors are not required with the 6 volt 60mA bulbs.

The circuit is not limited to merely two push-buttons and can, if desired, be expanded to accommodate any number of push-buttons (or external contact sets). Fig. 2 shows the circuit required for each additional push-button. This is identical to the existing individual push-button circuits in Fig. 1 and is connected across the same positive and negative supply rails. The diode in the anode circuit of the additional thyristor connects to point 'X' of Fig. 1. Circuit operation is the same as before. Whichever push-button is pressed first causes its associated thyristor to fire and its pilot lamp to light up, whilst at the same time bringing point 'X' down to about 1.2 volts positive of the negative supply rail and thereby disabling all the other gate circuits.

# BOOK REVIEW



**RADIO DATA REFERENCE BOOK, Third Edition.** Compiled by G. R. Jessop, C.Eng., M.I.E.R.E., G6JP. 150 pages, 5½ x 8¾ins. Published by Radio Society of Great Britain. Price £1.00.

Intended mainly for the amateur transmitter and short-wave listener, this book nevertheless contains information that is of value to the constructor and experimenter. Its function is to provide equations, curves, abacs, tables and circuits for assistance in the design and use of equipment, together with short descriptions where applicable.

Typical of the topics dealt with are transmission line resonators, Yagi aerial design curves, folded dipole calculations, self-resonant frequencies of capacitors, coil winding turns, great circle calculations, meteorological data, SI units and the fundamental frequencies of FT241 crystals. However, these are just a few of the matters covered, which range from logarithm tables to the SINFO signal-reporting code.

"Radio Data Reference Book" provides a comprehensive and compact source of technical facts, and will be a useful addition to the shelves of any serious experimenter, especially if the major field of interest lies in short-wave transmission and reception. The author was assisted in his compilation of the book by G. C. Fox G3AEX, R. F. Stevens G2BVN, G.M.C. Stone G3FZL and H. L. Gibson G8CGA.



# Radio

## Topics

### By Recorder



I SEE THAT THESE NOTES WILL APPEAR in the December issue, at a time when most people are turning their thoughts to the choosing of Christmas presents. If anyone were to ask me what would probably be the most useful present for the radio construction enthusiast these days my answer would be immediate – a magnifying glass!

It's true, too. Transistors and all the other semiconductor devices are getting smaller and smaller as the years go by. The type markings on some of the tinier plastic devices are nowadays so microscopic that I'm sure that even the keenest sighted have difficulty in deciphering them. It may not be long before we follow in the footsteps of the watch makers and work with an eye-glass permanently in position.

#### MINIATURISATION

All this miniaturisation is of course a good thing, since there isn't much point in making devices that are larger than they need be. In the very early days of transistors, when the common types were the OC70 and OC71, I well remember reading in a journal for the deaf a plea for the manufacture of smaller transistors for use in deaf aids. The journal pointed out that the transistors then current consisted of minute junctions which were housed in what were relatively whacking great cans. A perceptive plea indeed, and one that was answered in later years.

With semiconductors becoming smaller, what other components are also undergoing a continual process of shrinkage? Resistors, for a start.

DECEMBER 1972

Obviously, a resistor has to have a certain minimum volume in relation to the power it has to dissipate. But the transistor circuits in which the resistors are used tend, themselves, towards reduced dissipation in the associated components, whereupon it becomes possible for resistors to become more and more diminutive as development proceeds. Capacitors also become smaller, if only because the voltages associated with transistors are so low.

The ultimate in miniaturisation is, to date, the integrated circuit. This is already ousting individual transistors in many items of domestic electronic equipment, including in particular radio and television receivers. There is some way to go before all the components of a receiver, apart from the controls and speaker, etc., can be packed into a few integrated circuits but progress towards that end is nevertheless under way. In computers the Integrated circuit gained precedence over the transistor many years ago and we now see the situation where each generation of integrated circuits is being superseded by more efficient and even smaller types.


Perhaps one of the fascinations of electronics is that it never stands still. Every year brings forth its crop of exciting new devices and principles, and nearly all of these lead the way to equipment of more Lilliputian dimensions. I can visualise the day when a low cost mass-produced radio is encompassed in the same space as a wrist watch, and when an inexpensive mass-produced TV set has dimensions which are not very much greater than the screen which reproduces the picture.

#### AUTOMATED RADIO

When the little green men finally overtake the world they may find that many of our activities are being run by machines. The accompanying photograph illustrates an example of this trend and shows a radio broadcasting system that is fully automated.

The equipment is a typical item in the Schafer 900 series of modular broadcasting units and it consists of tape playback decks, both reel-to-reel and cartridge, which are controlled by prior programming in the memory store of the system control unit.

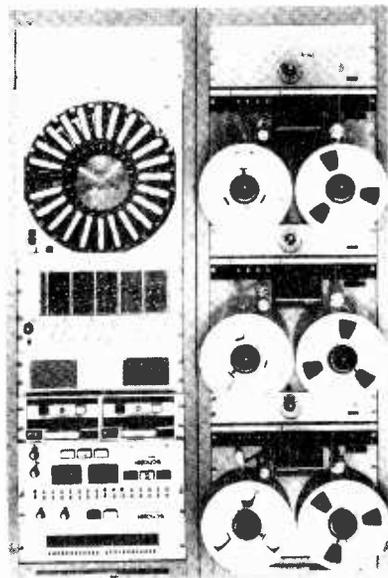EMI Electronics and Industrial Operations, Hayes, Middlesex, now have exclusive marketing rights (outside North America and Mexico) for these systems, which are stated to be the most flexible series of a.m. and f.m. radio automation equipments available.



*An automatic broadcasting system, marketed by EMI Electronics and Industrial Operations, which can be operated completely un-manned. Both reel-to-reel and cartridge tape playback facilities are available*


#### YEAR'S END

These represent my final jottings for 1972. Looking back, it has been, I feel, quite an outstanding year for this journal. We certainly intend to keep up the standard in 1973 and already have some really appetising radio and electronic constructional goodies lined up for publication.

In the meantime take advantage of the Festive Season, go easy on the pud and, above all else, have a truly Happy and Merry Christmas.

See you next year!

# In your workshop

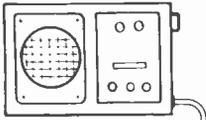

"Ah," said Dick lazily, as he settled himself more comfortably on his stool. "now this really is nice and Christmassy."

It was the afternoon of the last working day before Christmas. Both he and Smithy had been toiling feverishly in order to clear the rush of faulty receivers which inevitably appeared in the Workshop just before the Yuletide holiday. The "Repaired" racks now bulged with serviceable receivers, whilst the "For Repair" racks were gratifyingly empty.

An atmosphere indicative of the festive season pervaded the Workshop. Its utilitarian bleakness had already been relieved by the setting up, by Dick of a number of gaily coloured paper chains across the ceiling together with the application of red and mauve crepe paper to the walls behind the benches. An improbable series of imitation drops of snow garnished the windows in neat horizontal rows, and gave evidence of Dick's adroit application of judiciously controlled squirts from a Gillette Foamy Shaving Cream aerosol.

"Yes," spoke up Smithy, similarly relaxing at his own bench, "you're dead right, Dick. I can already feel the Christmas spirit soaking into my bones."

The pair grunted contentedly.

## LOGIC CIRCUIT

"Do you know," said Dick, "there's something about Christmas that fits exactly into the logic of life. It seems to be perfectly logical that the Christmas Holiday should commence just before the end of the year, and just before we go into the worst of the winter."

"True enough," agreed Smithy. "It's funny, though, that you should

Dick and Smithy are relaxing in the last few hours before the Christmas holiday when we join them this month. During their welcome break from servicing Smithy re-introduces Dick to the fascinating world of digital logic, and demonstrates to him the number of different gate functions which can be provided by the quadruple NAND gate type 7400.

have mentioned the word 'logic'."

"Why's that?"

"Because I was also thinking of logic," replied Smithy, "but in a completely different sense. I was thinking of those logic integrated circuits which are all the rage these days. As it happens, I've bought a selection of these devices and I was going to play around with them during the holiday. I've already knocked up a stabilized power supply for them."

Dick's ears pricked up.

"Logic i.c.'s, eh?" he said keenly.

"Have you got them with you here?"

Smithy opened a drawer in his bench and took out a small cardboard box. Dick rose eagerly from his stool and hurried over to Smithy's side.

"Here you are," stated the Serviceman, taking the lid off the box, "take a look at these."

Dick gazed into the box, which contained about a dozen dual-in-line integrated circuit modules, in company with an equal quantity of integrated circuit holders.

"Gosh," he said, picking up one of the modules and examining it closely. "Are all these integrated circuits digital types?"

"They are."

"I always look upon digital i.c.'s as coming close to black magic," confessed Dick. "When you look at circuit diagrams incorporating digital i.c.'s all you can see are individual blocks with lines joining them. There are hardly any external components in the circuit diagrams at all."

"That's one of the charms of working with digital integrated circuits," stated Smithy. "You simply connect the output of one integrated circuit

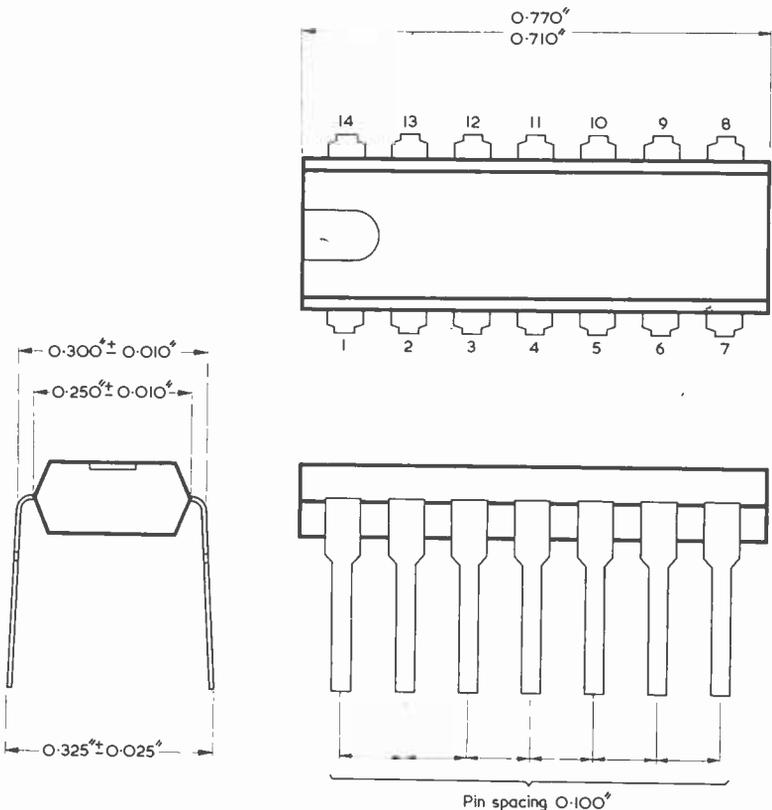


Fig. 1. The principal dimensions of a 14 pin dual-in-line plastic integrated circuit

section direct to the input of another integrated circuit section. You can look upon each i.c. section as a 'black box' and you don't need to think too much about what's inside it at all. So far as circuit diagrams incorporating i.c.'s are concerned, another unfamiliar aspect is that the power supply connections are usually omitted. Each i.c. has a tag for positive and negative supplies and it is automatically assumed that these are connected to the supply circuit."

"Would the i.c.'s you've got here," asked Dick doubtfully, "be what are known as t.t.l. types?"

"They would," confirmed Smithy. "The letters 't.t.l.' stand for 'transistor transistor logic' and the term arises from the fact that t.t.l. devices are a development from the earlier diode transistor logic or d.t.l. devices, and resistor transistor logic or r.t.l. devices. These t.t.l. circuits are capable of working faster than the older types. The ones I've got here are from the well-known 74 series. This name arises because the Texas Instruments type numbers for the series consist of 'SN74' plus two or three other numbers according to function. Also, there's usually a suffix letter to denote the type of case and terminals employed. With Texas Instruments i.c.'s, the letter 'N' indicates a plastic case and dual-in-line terminal pins, and this is by far the best version to use for home-constructor work."

"I suppose," said Dick, returning the integrated circuit to the box, "that the pins are spaced out in a standardised manner."

"That's true," confirmed Smithy. "There's 0.1 inch spacing between pin centres, and there's 0.3 inch spacing between the two lines of pins. Amongst other things, this pin spacing allows dual-in-line i.c.'s to be fitted directly to 0.1 inch Veroboard." (Fig. 1.)

"I wonder," asked Dick eagerly, "if we could try out one of these i.c.'s. Just so that I can get the feel of them."

Smithy looked at the Workshop clock.

"All right," he agreed. "We've got a couple of hours to spare, so I can see no harm in trying out some simple logic set-ups here and now. Let me think for a moment."

Smithy stroked his chin reflectively and studied the contents of the cardboard box. Eventually, he took out one of the integrated circuits.

"This will be a good one to start you off with," he remarked. "The i.c. I've selected is an SN7400, and it is a quadruple 2-input positive NAND gate."

Dick's face fell.

"I knew that this logic business just couldn't be all that easy," he sighed. "What on earth does 'quadruple 2-input positive NAND gate' mean?"

"All it means," replied Smithy soothingly, "is that the i.c. has four separate NAND gates, and that each of these has two inputs. The positive

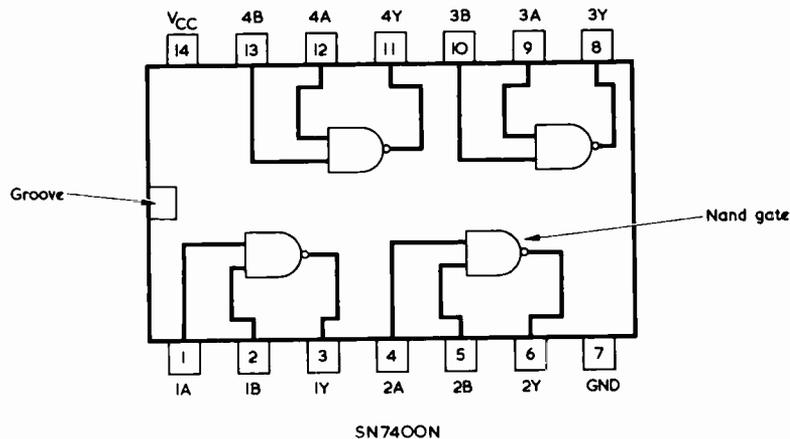


Fig. 2. Top view showing the pin layout for the 7400 integrated circuit in dual-in-line. A small groove identifies the end at which pins 1 and 14 appear

bit arises from the fact that the gates work on positive logic."

"And what's that?"

"It's logic in which the figure 1 is represented by a high voltage and in which the figure 0 is represented by a low voltage."

"Well," said Dick, brightening visibly, "that doesn't sound too bad after all. I suppose that the figures 1 and 0 came into the picture because all these digital i.c.'s work in binary notation."

"That's right," confirmed Smithy. "There are only the two figures, 1 and 0, in binary. Now, I've got a data sheet for the 7400 somewhere around so I'll show you the pin layout."

Smithy looked through some papers and extracted the data sheet in question. He laid it on his bench and indicated the pin layout diagram to his assistant. (Fig. 2).

"There you are," he remarked. "This diagram uses logic symbols and you can see the four NAND gates all

drawn out separately. Pins 1 and 2 are the inputs for the first gate and pin 3 is the output of the first gate. There are three other groups of three pins for the remaining gates. Pin 7 is the 'ground' pin and the negative side of the supply is coupled to this. At the same time, pin 14 is the Vcc pin, and it takes the positive side of the supply. These two pins supply power to all the gates in the i.c. but, as I said earlier, this fact is not indicated in the logic diagram, in which the supply connections are assumed. Don't forget, by the way, that this is a top view of the integrated circuit. The pins point away from you."

### INTERNAL CIRCUIT

"I wonder," mused Dick, "what the internal circuit of each of the NAND gates looks like."

"There's a diagram showing this on the data sheet," replied Smithy, pointing to the circuit. (Fig. 3). "It's a standard t.t.l. NAND circuit."

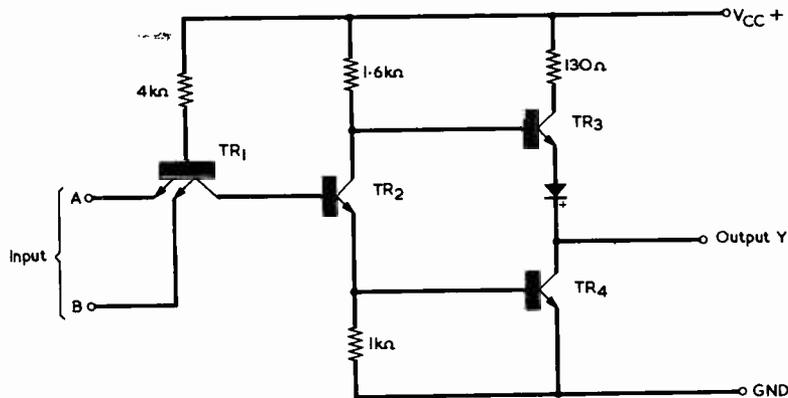


Fig. 3. Internal circuit of one of the NAND gates in a 7400 integrated circuit. The resistance values are nominal

"It looks rather familiar," commented Dick as he peered at the circuit. "I seem to remember having seen something like this before."

"You saw it several years ago," replied Smithy,\* "when we had a discussion on different types of NAND gate. However, it will do no harm to go quickly through the theory of the t.t.l. NAND gate once more. Don't forget that a NAND gate is the same as an AND gate with the output inverted. With an AND gate you get an output 1 only when *all* the inputs are 1. So, with a NAND gate you get an output 0 only when all the inputs are 1. For all other input conditions the NAND gate output is 1. Now, if you look at the two inputs of the gate circuit you'll see that these go to two separate emitters in transistor TR1. If both of these inputs are at a low positive potential corresponding to 0, they hold the base of TR1 down at a low potential too. Under these conditions the transistor is turned hard on and its collector voltage is only a little higher than its emitter voltage. Because of this, TR2, is turned off and TR3 draws base current via the 1.6kΩ resistor. TR3 is turned on and the output of the gate is at a high positive potential, corresponding to 1."

"What happens if one of the inputs goes positive, up to 1?"

"Transistor TR1 still remains hard on by virtue of the remaining emitter," said Smithy. "It only needs one emitter at a low voltage to keep TR1 hard on and its base at a low potential. If *both* the emitters go positive to 1, then quite a different state of affairs takes place. The voltage at the base of TR1 rises and a collector current now flows into the base of TR2. This transistor comes on and draws current through the 1.6kΩ resistor, thereby causing TR3 to turn off. TR2 also allows current to flow into the base of TR4, which comes hard on. As a result, the output of the gate goes down to a low potential, corresponding to 0, and the NAND function has been carried out. The particular NAND gate we're looking at has two inputs only. You can get NAND gates with more than two inputs, each connecting to a separate emitter at TR1. These gates operate in the same manner and *all* the inputs have to go up to 1 before the output falls to 0. Okay?"

"Sure," said Dick confidently. "Can you connect the output of a NAND gate to the input of another NAND gate?"

"Oh yes," confirmed Smithy. "The only thing you mustn't do is to connect the output of a NAND gate of this type to the output of another NAND gate of similar type. The output circuit of this type of NAND gate is referred to as a 'totem pole' output because the two transistors and the associated components are all in a vertical line in the circuit diagram, just

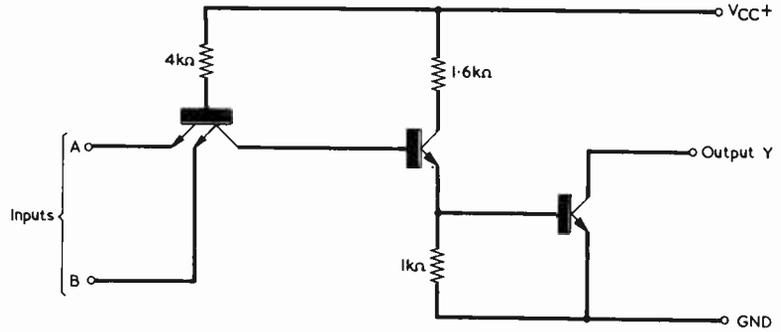


Fig. 4. A NAND gate with open-collector output. Four gates of this nature appear in the 7401 integrated circuit

like a totem pole. The output of a totem pole circuit is at low impedance for both the high and the low conditions and, if two output circuits were connected together, heavy currents could flow if they were in different states. There is, however, a version of the NAND gate having what is called 'open-collector output', and the outputs of two NAND gates of this type can be connected together. With the open-collector output, the second transistor simply couples into a third transistor which comes hard on when the second transistor conducts. The collector circuit to Vcc for the open-collector output has to be completed via an external resistor." (Fig. 4.)

"I see," said Dick reflectively. "What is the Vcc voltage, by the way?"

"For 74 series i.c.'s," said Smithy, "It's 5 volts nominal, and it is recommended that it should not be greater than 5.25 volts or lower than 4.75 volts. With the 7400 gate, the maximum Vcc voltage must not exceed 7 volts, and the input voltages must not exceed 5.5 volts. Well now, let's start getting practical and think of wiring up an actual gate circuit. As I mentioned earlier, I've already knocked up a power supply for these i.c.'s, so we

might as well bring it into use."

Smithy reached over to the back of his bench and produced a small neatly assembled power supply. (Fig. 5.)

"There's nothing out of the ordinary in this supply," he went on. "It uses a standard zener diode and emitter follower arrangement, and the output current is about 1 amp maximum. The mains transformer can be any 6.3 volt heater transformer offering a secondary current of 1 amp or more."

"Blimey, Smithy," said Dick excitedly, "I'm just itching to try my hand out at making up a NAND circuit."

"You can start right now," remarked Smithy, reaching for his note pad. "Here's a circuit for a NAND gate using the gate which connects to pins 1, 2 and 3 of the 7400. You needn't worry about the other gates; and they can just be left disconnected. If you had unused gates in a permanent working set-up it might be preferable to have their inputs all commoned and coupled to the positive supply line via a 1kΩ resistor. But for a temporary application such as we have here the unused gates may be ignored."

Smithy scribbled out the circuit for the single NAND gate. (Fig. 6.)

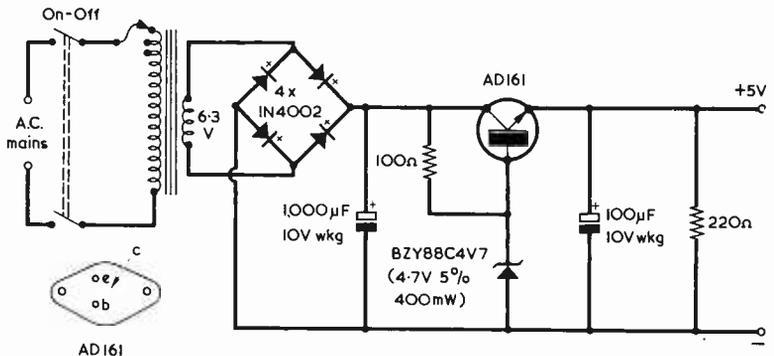


Fig. 5. The stabilized power supply constructed by Smithy. Both resistors are ½ watt. The AD161 may be mounted on a small heat sink about 1½ ins. square

\* 'In Your Workshop', *The Radio Constructor*, October 1970.

"What," asked Dick, "are the two switches for?"

"To give you your two input signals," explained Smithy. "If a switch arm connects to the negative zero voltage line this corresponds to an input signal of 0, and if it connects to the positive line it corresponds to an input signal of 1. I'd suggest that you next hunt out an odd bit of chassis with holes in it of the right size for two changeover toggle switches. You'll need to mount a few tagstrips on it for the other connections as well."

As Dick searched hastily for the requisite hardware, Smithy looked around him musingly.

"I must confess," he remarked cheerfully, "that this is an excellent way of spending the last few hours before the Christmas holiday."

"I'll say it is," replied Dick enthusiastically, as he returned with a small piece of metal and proceeded to mount two toggle switches and several tag-strips on it. "Working on stuff like this is a holiday in itself."

Smithy's assistant soon had the switches and tagstrips mounted, and then he turned expectantly to the Serviceman.

"Well," replied Smithy, "there are the obvious ones of using narrow gauge solder and a small soldering iron bit. Oh yes, and there's another important one I nearly forgot. The connecting wire to the holder, or to the i.c. itself if you were wiring directly to it, should consist of a very thin flexible wire. Don't use single strand solid wire. The pins of an i.c. and the pins of most i.c. holders are not at all strong and can easily be bent out of position or even broken off if you use wire that isn't sufficiently flexible. If the wire is stiff, the pin just bends over as the wire is moved."

"Righty-ho," said Dick. "Well, I'm starting off this moment. Hey, wait a minute, though! What about that voltmeter you included in your circuit?"

"You can use the bench testmeter switched to a voltage range for that," stated Smithy. "Wire the gate output to a tag on one of the tagstrips and clip the positive testmeter lead to that tag."

#### INVERTER FUNCTION

Pecring closely at the integrated circuit holder Dick commenced the

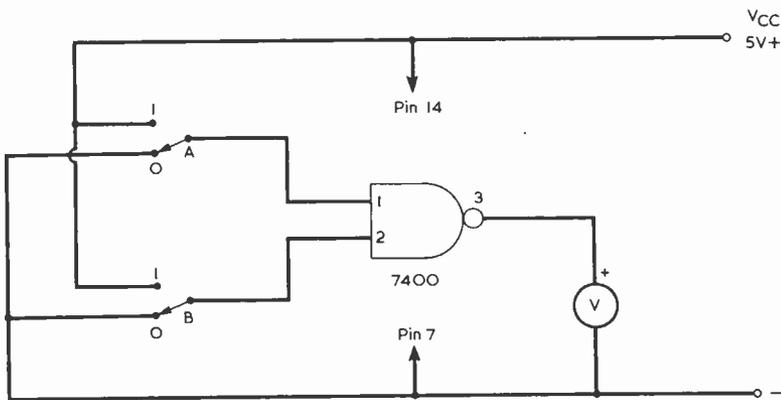


Fig. 6. Using the NAND gate which connects to pins 1, 2 and 3 of the 7400. Note also the supply connections to pins 14 and 7 of the integrated circuit

"You can next," pronounced that worthy, "wire up the NAND circuit. I must pass on a few words of warning here, though. To start off with, and seeing that this is your first attempt at wiring to a dual-in-line i.c., I'd advise that you use an integrated circuit holder instead of wiring directly to the integrated circuit itself. The terminal pins are very close together and they are quite fragile, and it's less expensive if you wreck a holder than an integrated circuit! You can insert the integrated circuit after you've completed the wiring to the holder. For the present exercise the holder can be suspended in the wiring or rested on a piece of Paxolin; it need not be mounted firmly."

"Any other points to watch?"

wiring.

"Stap me," he remarked, "These pins aren't half close together!"

"They are rather," chuckled Smithy, as he watched him. "They don't represent the sort of wiring-up job you'd welcome first thing on New Year's Day!"

"You must speak for yourself there," remarked Dick airily. "I myself am always full of vim and vigour on January the First. I like to start the New Year fresh and clear-eyed."

By now Dick had completed the few connections that were needed to the integrated circuit holder and was wiring his test circuit to Smithy's 5-volt power supply.

"All I can say," commented Smithy drily, "is that in the past I must have

## Your Local Supplier

LONDON

### THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET,  
LONDON, W2 1NP  
Tel: 01-723 4185/2926

## ST. HELEN'S RADIO

Hi-Fi Equipment  
Tape Recorders  
Radio Receivers  
Television  
SPECIALISTS IN RADIO  
& ELECTRONIC TEXTBOOKS  
ST. HELENS GARDENS  
LONDON, W.10  
Tel: 01-969 3657

CORNWALL

### DE-SOLDERING Made Easy

UNSOLDERING BITS - release component leads in one operation.  $\frac{1}{16}$ " diam, shanks.  
Dual-in-line (0.3"), I.C. 85p.  
Long line of leads 75p.  
T 0.5 outline 55p.  
Finepoint non-seize 30p.  
MATCHING SOLDERING  
IRON £1.80  
SOLDER-ABSORBING WICK 40p.

ORIENTATION LTD.  
Mayfield, Coverack, Cornwall

DEVON

### COMPUTER PANELS

Panel contains 2 x Mullard OC23 Transistors and 5 other Transistors etc. 2 panels 50p p.p. 15p.  
Panel contains 2 x Mullard OC28 Transistors 2XBCY34, etc. 2 panels 50p p.p. 15p.  
Assorted Computer Panels contains many useful Transistors, Diodes, Trim Pots, etc. 4 panels for £1 post free.  
Assorted Panels contains minimum of 10 integrated circuits, also Transistors, Diodes etc. £1 p.p. 15p.  
Electrolytic Capacitors UF/V. 2000/35, 10,000/15, 10,000/25, 12,500/35. All at 30p each p.p. 6p.  
2,000/50, 2,500/50, 5,000/50, 10,000/50, 12,500/50, 50,000/15 all at 40p each p.p. 10p.  
Also available wide range motor start capacitors also block paper, etc. Send our exact requirements.

Assorted miniature and subminiature Electrolytic Capacitors, 100 for £1.20 p.p. 15p.  
Send your exact requirements  
**XEROZA RADIO**  
1, East Street, Bishops Tawton, Devon

encountered you on the wrong New Year's Days."

"There must always, of course," responded Dick carelessly, "be exceptions to even the strictest of rules."

"In your case," replied Smithy. "I'd have thought that the exceptions were the rule."

"I've finished wiring up now," said Dick, bringing this unprofitable topic of conversation to an abrupt end. "What do I do next?"

"Fit the integrated circuit into its holder," said Smithy. "Be careful while you're doing this, as it's a bit of a fiddling process and you have to hold the i.c. pins in a little. You'll soon get the hang of it after you've done it a couple of times. And don't put it in wrong way round!"

Frowning with concentration, Dick succeeded in inserting the integrated circuit in its holder.

"Right," said Smithy. "We're off. Put both the input switches to 0 and turn on the 5 volt supply."

Dick carried out Smithy's instructions. The needle of the testmeter measuring the output voltage at once rose to 3.6 volts.

"Good," commented Smithy. "That's the high output and it corresponds to 1. Now put one of the input switches to 1."

Dick turned the switch. The meter reading was unaltered.

"Return the switch to 0," said Smithy, "and put the other switch to 1."

Dick clicked the switches over. Again, the meter reading remained the same.

"Now put both switches to 1."

Dick did so. At once the meter needle dropped to a reading just above zero volts.

"Gosh," said Dick impressed. "That gate's working right first go! It's only when *both* inputs are 1 that the output is 0."

"Excellent, excellent," enthused Smithy. "We can now make up a truth table for that NAND gate. A truth table is, of course, simply a table that indicates the state of affairs existing in a logic circuit."

Smithy drew out the truth table on his note-pad. (Fig. 7.)

A	B	OUTPUT $\overline{AB}$
0	0	1
1	0	1
0	1	1
1	1	0

Fig. 7. Truth table for the circuit of Fig. 6. The term  $\overline{AB}$  means 'A and B', whilst the horizontal line above these letters indicates 'not'

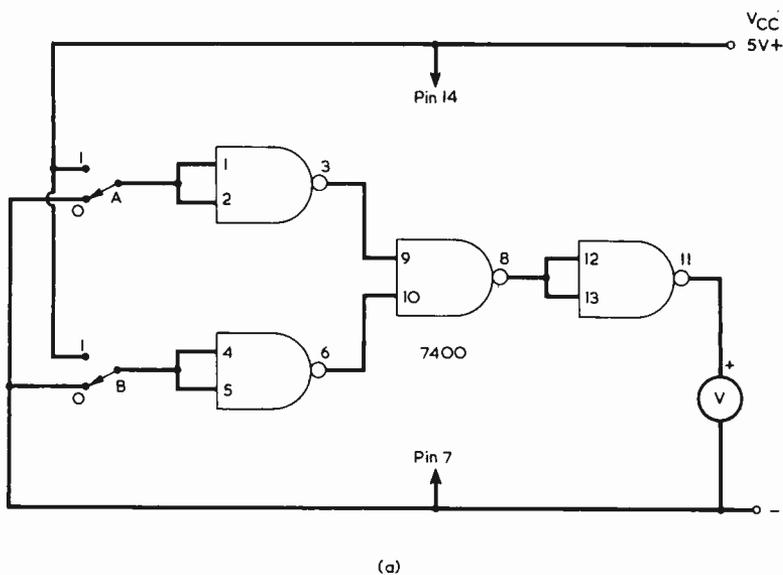


Fig. 8 (a). Two NAND gates connected together to form an AND gate. The second gate functions as an inverter (b). Truth table for the AND gate

A	B	OUTPUT AB
0	1	0
1	0	0
0	1	0
1	1	1

(b)

"This table," he went on, "Tells us that the output is 1 when either both or one input is at 0, and that it goes down to 0 when *all* inputs are 1."

"Why," asked Dick, "didn't the output go all the way up to 5 volts when it was in the high condition?"

"Because of voltage drop in the upper output transistor of the gate, in the resistor above it and in the diode below it," explained Smithy. "This voltage drop varies from i.c. to i.c. and it also varies according to the load which is connected to the output. If used under proper conditions, the high output voltage of a 7400 is typically 3.3 volts and is never less than 2.4 volts. The low output voltage is more closely defined because it corresponds to the lower output transistor being turned hard on, and it has a maximum of 0.4 volts."

"Is this important?"

"It can be," said Smithy, "if the output of a NAND gate is coupled to the input of another NAND gate. More input current flows to the second NAND gate when its input is at 0 than when it is at 1, because the input current then has to pull down the base of the first transistor in the second NAND gate. That higher current can be supplied very reliably when it is derived from a hard-on transistor in the first gate."

"Oh, I see," said Dick. "Is there anything more we can do with this NAND gate?"

"Yes," said Smithy promptly. "we can turn it into an AND gate!"

"Blimey," expostulated Dick. "How on earth do we do that?"

"By coupling the output of the NAND gate to another NAND gate wired up as an inverter," said Smithy. "If you join all the inputs of a NAND gate together you get an inverter. This is obviously the case because, when all the inputs of a NAND gate are at 0, the output is at 1, and when all the inputs of a NAND gate are at 1 the output is at 0. A NAND gate can also act as an inverter if you simply apply the input signal to one input and leave the other input or inputs floating. However, it's not always good practice to leave gate inputs floating and so we'll make up our own inverter with both inputs of the second gate connected together."

Smithy scribbled out a circuit on his note pad. (Fig. 8(a).)

"Here you are," he said, "there's only a few more connections to make."

Dick soon carried out the new wiring required and he then checked the result. When either or both of the input switches was at 0 the output of the second gate, as indicated by the testmeter, was also at 0. The output only

rose to 1 when both inputs were at 1. Smithy drew out a truth table for this new set of circumstances. (Fig. 8(b).)

### OR AND NOR GATES

"Gosh," said Dick, as he watched Smithy completing the truth table. "This is *fascinating*. You just connect up these i.c.'s in the correct way and they do any logic function you want. Is there any other sort of gate you can make up with this 7400?"

"You can," replied Smithy, "use three of its gates to make up an OR gate. Here's the circuit."

Smithy pulled the top sheet from his pad and drew out the circuit on the fresh page underneath. (Fig. 9(a).)

"This looks fairly easy," said Dick, glancing at the circuit cautiously. "So far as I can see, the first two gates are wired as inverters."

"That's right," confirmed Smithy. "We'll draw the truth table for this before you wire it up. We need three columns once more, these now being 'A', 'B' and 'A+B'. The last column represents the output, and you may recall that the plus sign in logical calculations means 'or'."

Smithy drew up the columns on his note-pad. (Fig. 9(b).)

"Now," he went on, "let's say that both inputs are at 0. The outputs of

the two inverters will be at 1, whereupon the output of the third gate, which functions as a true NAND gate, is 0. Let's next put input A to 1 and input B to 0. The inverter outputs will be 0 and 1 respectively and the output of the third gate will be 1. The same will happen if input A is at 0 and input B is at 1. When both inputs are at 1 the inverter outputs will both be at 0 and the third gate output will remain at 1."

Smithy showed Dick the completed truth table.

"Let's see now," said Dick concentrating. "What the table tells us is that the output is at 1 when either one input or both inputs are at 1."

"Correct," replied Smithy, "and that is exactly what is required of an OR gate. Wire up the circuit and see if this truth table works out in practice."

Dick set to work energetically and after some ten minutes or so announced that the new circuit was completed. With eager figures he tried it out.

The circuit functioned exactly as Smithy had predicted. With both switches in the 0 position the output was similarly 0. When either switch or both switches was set to the 1 position the output rose to 1.


"This is incredible," pronounced Dick as he continually tried the

**Your Local Supplier**  
 HAMPSHIRE  
**BOURNEMOUTH**  
 LARGEST HI-FI AND  
 RADIO COMPONENT  
 STORE IN THE SOUTH  
 FORRESTERS NATIONAL  
 RADIO SUPPLIES LTD.  
 70-72 Holdenhurst Road  
 Bournemouth  
 Telephone 25232

**WITWORTH TRANSFORMERS**  
**TV Line out-pot transformers**  
 Manufacturers of the largest range in the country. All makes supplied.  
 Free catalogue.  
 Modern  
 BAIRD, BUSH, GEC, PHILIPS  
 Replacement types ex-stock.  
 For "By-return" service, contact London  
 01-948 3702  
 Tidman Mail Order Ltd., Dept. R.C.  
 236 Sandycroft Road,  
 Richmond, Surrey TW9 2EQ  
 Valves, Tubes, Condensers, Resistors,  
 Rectifiers and Frame out-pot Transformers,  
 Mains Transformers also stocked.  
 Callers welcome.

SUSSEX  
**E. JEFFRIES**  
 For your new television set  
 tape recorder, transistor radio  
 and hi-fi equipment  
 PHILIPS, ULTRA, INVICTA  
 DANSETTE, MASTERADIO, PERDIO,  
 MARCONI, PHILCO FIDELITY  
 6A Albert Parade  
 Victoria Drive,  
 EASTBOURNE SUSSEX

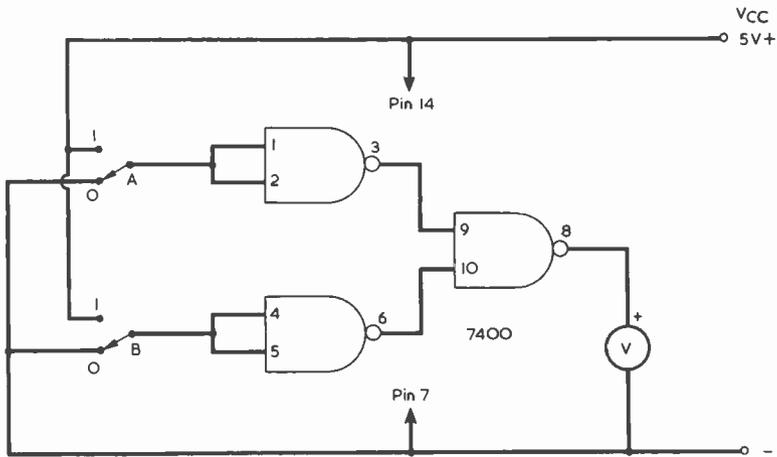EIRE  
**PEATS for PARTS**  
**ELECTRONIC COMPONENTS  
 RADIO & TELEVISION**  
 For the convenience of Irish  
 enthusiasts we supply  
 The Radio Constructor  
 Data Books and  
 Panel-Signs Transfers  
 Also a postal service  
**Wm. B. PEAT & Co. Ltd.**  
 28 PARNELL STREET  
 DUBLIN 1



(a)

Fig. 9 (a). Three NAND gates connected to provide an OR gate

(b). Truth table for the gate of (a). The plus sign indicates 'or'

A	B	OUTPUT A + B
0	0	0
0	1	1
1	0	1
1	1	1

(b)

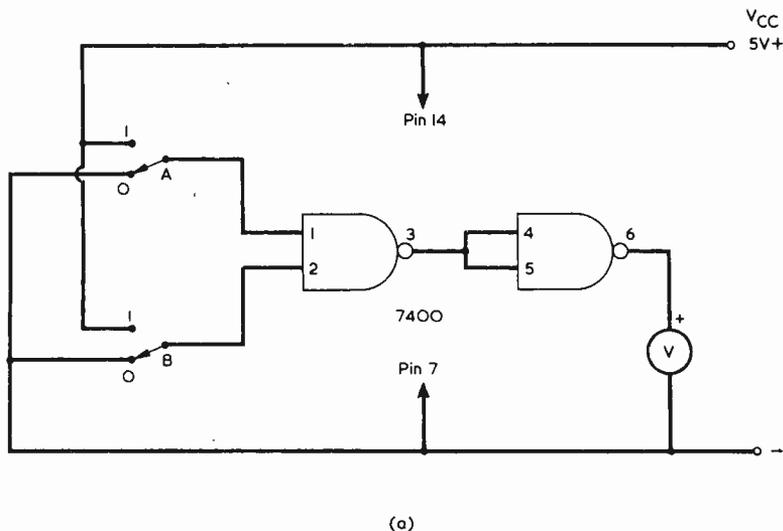


Fig. 10 (a). All the gates of a 7400 integrated circuit may be connected together to form a NOR gate (b). The NOR gate has the truth table shown here

A	B	OUTPUT $\overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0

(b)

switches in their different settings. "We've already made up a NAND gate, an AND gate and an OR gate. There's only a NOR gate left."

"That can be obtained quite easily," said Smyth, again busy with his notepad. (Figs. 10(a), and (b).) "All we have to do here is stick another inverter on the output of our OR gate. This will automatically change it to a NOR gate."

Dick quickly set to work wiring in the fourth NAND gate, now functioning as an inverter, of the integrated circuit. He transferred the positive lead of the testmeter to its new circuit position and checked circuit operation. In this case the output was at 1 when both switches were at 0, and fell to 0 when either one or both switches was set to 1.

#### LAMP INDICATOR

"There you are," said Smyth. "That performance corresponds to the truth table for a NOR gate."

"Well, I've certainly discovered a few new things today," said Dick happily. "I've first of all learned that these logic circuits aren't half as frightening as they look once you've started wiring them up in practice. The second thing I've found out is this

truly delightful business of directly coupling gates together by pieces of wire so that they give exactly what is theoretically expected of them. It's like drawing diagrams with a soldering iron! The third thing I've discovered is that after you've been playing with these logic i.c.'s for even a very short time you start thinking in terms of gates as complete entities without worrying at all about what goes on inside them. And the fourth thing I've learned is that you can wire up NAND gates to form inverters and any other forms of gate."

"It's the adaptability of NAND gates that has made them so popular," said Smyth. "NAND gates are probably the simple gates that are most commonly used, with NOR gates coming next. AND gates and OR gates aren't so useful because they can't be combined to form other gates as readily as can NAND and, for that matter, NOR gates. There are, of course, all sorts of other gates in t.t.l. integrated circuits but the simple ones you've been playing with here make a good introduction to this particular branch of electronics. I think we've done enough for today so far as logic integrated circuits are concerned, but it's a subject we could usefully turn to again in the future."

"I hope we do," said Dick. "I've really enjoyed myself this afternoon. There's only one thing I'm not too happy about."

"What's that?"

"This business of showing an output with the aid of a voltmeter. Isn't it possible to have something with a slightly more dramatic effect to show when an output is 1?"

Smyth thought for a moment.

"Well," he said, "you could have a bulb that lit up when an output was at 1 and which was extinguished for an output of 0. This idea can be carried out quite easily with the aid of an n.p.n. transistor. Its emitter would connect to the negative line and its collector to the positive line via the bulb. The base connects to the output that being monitored via a 2.2kΩ resistor."

Smyth picked up a box of spare transistors that was lying on his bench, and poked a finger through its contents.

"We'll need a small power transistor," he continued. "Ah, this one will do! I've got an AC127 here, and this can be used in conjunction with a 6 volt 60mA or 6 volt 100mA bulb." (Fig. 11.)

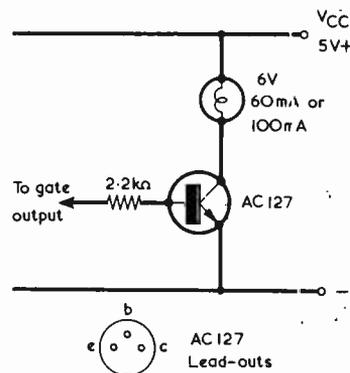


Fig. 11. Smyth used an AC127 to control a bulb which became illuminated when a gate output was 1. Any small n.p.n. power transistor of reasonable gain may be employed instead of the AC127

Dick took the transistor from Smyth, walked over to the spares cupboard for a suitable bulb and bulbholder, then wired up the lamp circuit. He next checked it out and found that the bulb lit up when the output to which the 2.2kΩ resistor was coupled was high, and became extinguished when the output was low.

#### YEAR'S END

"That," he remarked cheerfully, "works very nicely, too."

"Yes," concurred Smyth, "it's a pretty fool-proof arrangement. Any small n.p.n. transistor of reasonable

gain which is capable of handling the bulb current could, of course, be used instead of an AC127. If you liked, you could add further transistor and bulb circuits to the outputs of the intermediate gates which form a composite gate. They would then tell you the condition of each section in the logic chain."

"That's quite a good idea," said Dick, as, with an air of finality, he switched off the 5-volt power supply. "Well, it looks as though this is the end of electronics for us before Christmas. These gate circuits have certainly rounded things off nicely."

"Perhaps," commented, Smithy mysteriously, "there's something further that's needed to finally carry us through to the holiday period."

Whilst Dick raised a quizzical eyebrow, Smithy walked over to the filing cabinet where the service sheets were kept. As he returned there was a pleasant chink of glass against bottle.

"Good old Smithy," chuckled Dick.

"That filing cabinet was as good a hiding-place as any."

"It was the best place I could think of," chuckled Smithy as he carefully started to fill the glasses. "Knowing you, the last place you'd go to would be the service manual cupboard!"

He handed a charged glass to Dick and then picked up his own.

"Well, my lad," he said warmly, "a Merry Christmas to you."

"And the same to you," responded Dick, sipping appreciatively. "Come on, Smithy, let's be upstanding."

The pair rose.

"Let's next," said Smithy, raising his glass, "also wish a very Merry Christmas and a truly Happy New Year to all the readers who've put up with our antics during 1972."

They drank.

"And," concluded Dick, "let's finish, as we have done on so many previous Christmasses, by saying 'God Bless Us, Every One!'"

## The New Styled "MULTI-MINI" TWIN VICES



An extra "Pair of Hands" for those tricky jobs

ASSEMBLY - SOLDERING -  
GLUING - WIRING - DRILLING  
ETC.

- ★ INDEPENDENT ADJUSTMENT OF THE TWO VICE HEADS TO ANY ANGLE WITH POSITIVE LOCKING.
- ★ JAWS WILL FIRMLY GRIP, ROUND, FLAT, SQUARE OR HEXAGONAL PARTS.

TWIN VICE: £8.95 (25p - p&p)

ALSO AVAILABLE

SINGLE VICE: £5.45 (21p - p&p)

CANLEY ENGINEERING (SALES) LTD.


Dept. C/RC2

OSBORNE ROAD, COVENTRY

Tel. (0203) 77163/4

CV5 6EA

# NEW PRODUCT

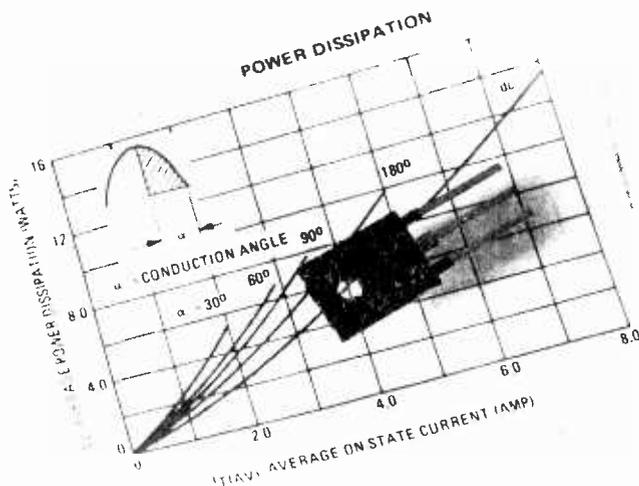

The above photograph illustrates the new Motorola thyristor type 2N4441. This appears in the 2N4441 to 2N4444 range of 8 amp thyristors in low-cost plastic housings and is now available, off-the-shelf, from Jermyn Distribution.

The junction-to-case thermal resistance of these thyristors is only 2.5°C per watt, a feature which simplifies heat-sink mounting requirements, and they have been designed for incorporation into consumer and other equipment manufactured in large quantities. The devices have peak reverse blocking voltages of 50 to 600 volts, a turn-on time of 1µs and a turn-off time of 15µs. They are in consequence suitable for phase and switching control at mains frequencies and above.

Phase control applications exist in the control of electric motors for food mixers, hand drills and the like, as well as in heater and lighting control. Typical switching operations lie in motor ignition and starting systems, voltage regulators, vending machines and lamp drivers. A surge current rating of 80 amps enables the thyristors to control tungsten lamps and similar loads up to a maximum rating of 1kW.

Versatility and ease of circuit design are assured by a worst-case triggering requirement (at 25°C) of only 30mA at 1.5 volts. The typical 'on' voltage is 1 volt at 5 amps, the holding current being only 40mA. Forward and reverse peak blocking currents are both 2mA.

Further details and prices can be obtained from Jermyn Distribution at Vestry Estate, Sevenoaks, Kent.

## RADIO & ELECTRONICS CONSTRUCTOR

**ANNUAL  
SUBSCRIPTIONS**  
to this magazine  
may be obtained  
through your  
newsagent  
or direct from the  
publishers  
**ONLY £2.70**  
per year, post free

Please send remittance with name and address and commencing issue required to:

**DATA PUBLICATIONS LTD**  
57 Malda Vale London W9 1SN



# SMALL ADVERTISEMENTS

Rate: 4p (9d) per word. Minimum charge 60p (12/-).  
Box No. 10p (2/-) extra.

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of advertisers. (Replies to Box Numbers should be addressed to: Box No. —, *The Radio Constructor*, 57 Maida Vale, London, W9 1SN

**CHROMASONIC ELECTRONICS** is well and living at 56 Fortis Green Road, London N10 3HN. 40 page illustrated catalogue 20p. post free.

**SERVICE SHEETS** for Televisions, Radios, Transistors, Tape Recorders, Record Players, etc., from 5p. with free Fault Finding Guide. Catalogue 15p. Please send S.A.E. with all orders/enquiries. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex.

**MECCANO FOR "CYCLOPS"** - Special Pack of all Meccano parts required - £3.39 including postage. Send off today to *The Meccano Spare Parts Specialists* and start building! "Everything Meccano" at M. W. MODELS, 165 Reading Road, Henley-on-Thames, Oxon. Telephone 3342.

**BUILD THE MULLARD C.C. TV CAMERA.** Complete kits now available from Crofton Electronics. Send large s.a.e. for details to: 15-17 Cambridge Road, Kingston-Upon-Thames, Surrey. Reply by post. No callers please.

**CATALOGUE NO. 18,** containing credit vouchers value 50p, now available. Manufacturers new and surplus electronic and mechanical components, price 23p post free. Arthur Sallis Radio Control Ltd., 28 Gardner Street, Brighton, Sussex.

**BUILD IT in a DEWBOX** robust quality plastic cabinet 2 in. x 2½ in. x any length. S.A.E. for details. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset. Write now - right now.

**FOR SALE: VHF KIT, 80 - 180 MHz.** Receiver, tuner, converter. World wide sales. Incomparable. £4.00 or s.a.e. for literature. Johnsons (Radio C), Worcester WR1 2DT.

**FOR SALE: Widescreen Cine Outfit.** 9.5mm Prince cine camera fitted with Zenoscope Anamorphic lens, 9.5mm Specte projector with adaptor for Zenoscopic lens, widescreen 60 in. by 30 in., six 9.5mm cassettes for camera. £50. Box No. G192.

**VISCONOL CATHODRAY CONDENSERS** 0.0025 mfd. 2.5kV 30p each, 0.002 mfd 15kV 60p, 0.02 mfd 12.5kV 65p, 0.025 mfd 5kV 40p, 0.1 mfd 6kV, 0.5 mfd 2.5 kV, 1 mfd 2kV, £1 each. CAPACITORS 0.1 mfd 150 volt £1 per 100, 44,000 available. MORSE KEYS precision type 50p each. STROBOSCOPE FORKS 124 cycles 80p each. JACK PLUGS 2 point screw on cover 15p each. Send for Lists. L. Wilkinson (Croydon) Ltd., Longley House, Longley Road, Croydon, Surrey.

**FOR "R. & E. C." PROJECTS:** CA3020 i.c. amp. £1. AD161, 30p. AD162, 30p. AF239, 35p. BC107, 12p. BC168B, 10p. BC169C, 10p. SF115, 15p. 1N4002, 100 p.i.v. 1A Si diode, 5p. Bias diode for FET TWIN, 3p. 2N2926G, 12p. 2N3702, 10p. 2N3707, 17p. 2N3819, 25p. 2N4289, 15p. 2N4291, 15p. Transformer LT700, 30p. Repanco CH r.f. chokes: 1.5mH, 20p; 2.5mH, 22p; 5mH, 23p; 7.5mH, 24p; 10mH, 25p. New, first grade. Mail order only. P. & P. 5p. Amatronix Ltd., 396 Selsdon Road, South Croydon, Surrey, CR2 0DE.

(Continued on page 341)

POTENTIOMETERS Lin or Log, 12p; with DP Switch, 23p; Dual Ganged, 36p; Special Offer, 5K with DP switch, 15p; WAVECHANGE SWITCHES, 22p; Special Offer, Miniature. 4P3W 16p; AMPLIFIERS: 1 Valve (EL84), £3; ½W Transistorised £1; 10W Transistorised, £3-75. JB3 Junction Box, £1-20. 5" Plastic Library Cases, 10p. 500uA TUNING METERS, 50p. CARTRIDGES: Compatible ACOS GP91-3SC, 90p; Stereo GP93-1, £1-15; Ceramic with Diamond Stylus, £1-80. CAPACITORS 100mF 25V, 5p; 220mF 25V, 5p; 400-200-50-16mF 300V, 30p; 0.1 500VDC, 300VAC, 3½p. MINIATURE INDICATOR LAMPS (5 colours), 11p; 6 or 12V Bulbs for above, 4p. MAINS NEONS panel mounting (red, green, clear), 15p. 100 MIXED RESISTORS, 45p. ROTARY SWITCHES (on/off) 250V 2A, 10p. PLUGS: Jack Standard, 10p; Screened, 13p; 2.5mm and 3.5mm, 6p; Screened, 8p. HEADPHONES: High Impedance (2,000 ohm), 90p; STEREO 8 ohm, £1-95; STEREO 8/16 ohm, £2-10. MICROPHONES: Lapel, 28p; ACOS MIC. 45, 90p; Dual Impedance Dynamic 600 ohm and 50k, £4-50. RECORDING TAPE: 5" LP 900ft., 45p; 5½" LP 1,200ft., 60p; 7" LP 1,800ft., 81p. RESISTORS: carbon film 5%, 1½p. ALUMINIUM CHASSIS from 6" x 3" to 16" x 10", all 2½" deep. Transistors, Rectifiers, etc. Large S.A.E. for list No. 4. Special Prices for quantity quoted on request. Add 10p for P&P on orders under £5.

**M. DZIUBAS**

158 Bradshawgate, Bolton, BL2 1BA. Lancs.

## Learn to understand electronics for your hobbies

### 1. Lerna-Kit course

Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered.

- (1) BUILD AN OSCILLOSCOPE.
- (2) READ, DRAW AND UNDERSTAND CIRCUIT DIAGRAMS.
- (3) CARRY OUT OVER 40 EXPERIMENTS ON BASIC ELECTRONIC CIRCUITS AND SEE HOW THEY WORK.

### 2. Become a Radio-Amateur

Learn how to become a radio-amateur in contact with the wide world. We give skilled preparation for the G.P.O. licence.

Brochure, without obligation to:

**BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL**

P.O. BOX 156, JERSEY, CHANNEL ISLANDS.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

BLOCK CAPS PLEASE

# THE MODERN BOOK CO

## HAM RADIO

A BEGINNER'S GUIDE by R. H. Warring

£1.60

Postage 10p

Transistor Pocket Book  
by R. G. Hibberd £1.40 *Postage 12p*  
Beginner's Guide to Television  
by Gordon J. King £1.60 *Postage 10p*  
Beginner's Guide to Radio Control  
by R. H. Warring £1.60 *Postage 12p*  
Field Effect Transistors  
by Mullard £1.80 *Postage 10p*  
T.V. Fault Finding 405/625 Lines  
by J. R. Davies 50p *Postage 8p*  
Television Timebase Circuits  
Principles & Practice  
by C. H. Banthorpe £1 *Postage 8p*  
Creative Tape Recording  
by Vivian Capel £3.50 *Postage 10p*  
VHF-UHF Manual  
by G. R. Jessop £1.60 *Postage 15p*  
The Mazda Book of Pal Receiver  
Servicing  
by D. J. Seal £3.50 *Postage 15p*

Transistor Audio & Radio Circuits  
by Mullard £1.80 *Postage 12p*  
Transistorized Radio Control for Models  
by D. W. Aldridge £2.50 *Postage 10p*  
Servicing Transistor Radio Receivers  
by F. R. Pettit 75p *Postage 6p*  
Understanding Electronic Components  
by Ian R. Sinclair £3.50 *Postage 10p*  
Transistor Substitution Handbook No. 12  
by Foulsham-Sams £1.40 *Postage 10p*  
Digital Logic Basic Theory & Practice  
by J. H. Smith £1.50 *Postage 8p*  
Colour T.V. With Particular Reference  
to the Pal System  
by G. N. Patchett £3 *Postage 10p*  
Transistor Manual  
by General Electric £1.10 *Postage 12p*  
Solid-State Hobby Circuits Manual  
by RCA £1.05 *Postage 12p*

We have the Finest Selection of English and American Radio Books in the Country  
**19-21 PRAED STREET (Dept RC) LONDON W2 1NP**  
Telephone 01-723 4185

## NEW STYLE SELF-BINDER

for  
"The Radio Constructor"



The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

PRICE  
**75p**

P. & P. 14p

Available only from:—

**Data Publications Ltd.**

**57 Maida Vale London W9 1SN**

## SMALL ADVERTISEMENTS

(Continued from page 339)

**FOR SALE:** "Jane's Fighting Ships" 1965/66 edition. £5.00. Box No. G195.

**"HOW TO LISTEN TO THE WORLD" 1973, £1.90.**

"WORLD RADIO TV HANDBOOK", published December, £2.80. "SWL ADDRESS BOOK", station's QSL policies, £1.45. Post (first class) 10p each. GIRO: 17-412-0001. David McGarva, Box 114G, Edinburgh EH1 1HP.

**FOR SALE:** 50 resistors 16p. 50 capacitors 40p. Magnetic counters 10p. 100 6BA bolts 10p. 50 nuts 10p. Intercoms. £2.20. Stereo headphones £1.99. Lists and samples 20p. Postage extra. Derwent Radio, 28 Hillcrest Avenue, Scarborough, Yorks.

**Q MULTIPLIER COILS.** High efficiency pot core assemblies for use in the range 50kHz - 2MHz. Other frequencies to order. 50p. each plus 5p. p. & p. State frequency required and whether p.c. or single hole mounting. Overseas enquiries invited. Storey, 145 The Knares, Basildon, Essex.

**COMPONENTS TO CLEAR:** Woden Mic. transformer, M.T.101, £1.50. E.C.C. Miniature relay type 2,5A, £1.00. 8 in. speaker, 30p. Eddystone 5 pin coil formers, 10p. Metal rectifiers, type SETT 2 W.B., 30p. Capacitors: 5mfd 3000V d.c., 30p. 2mfd 1000V d.c., 20. 1mfd 1000V d.c., 15p. 4mfd 500V d.c., 10p. Box No. G196.

**TAPE-HEADS RECONDITIONED.** Guaranteed satisfaction. Send worn head enclosing £2 to Sara Electronics, Fawkham Avenue, Longfield, Kent.

**VALVES TO CLEAR:** VR91, 171DDP, 801, U14, HP4106, 6B4-G, 6AG5. All at 20p each. Box No. G197.

**COMPUTER PANELS 3p.** Micro-switches (suitable for CYCLOPS), reed switches, 8p. 3V motors 15p. 40 hi-stabs 25p. Add 5p P. & P. Also hundreds of unusual items for the experimenter. Catalogue 5p. Mail order only. Grimsby Electronics, 64 Tennyson Road, Cleethorpes, Lincs.

**WANTED:** Early books on wireless, pre-1925. Details to Box No. G198.

**JOIN THE INTERNATIONAL S.W. LEAGUE.** Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £2.00 per annum. (U.K. and British Commonwealth), overseas 6 Dollars or £2.50. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

(Continued on page 343)

## MORSE MADE EASY!!!

**FACT NOT FICTION.** If you start RIGHT you will be reading amateur and commercial Morse within a month. (Normal progress to be expected.) Using scientifically prepared 3-speed records you automatically learn to recognise the code RHYTHM without translating. You can't help it, it's as easy as learning a tune. 18-W.P.M. in 4 weeks guaranteed. Beginner's Section only £3.30. Complete course £4.50 (Overseas £1 extra). Details only, 4p stamp. 01-660 2896

G3HSC/Box 38, 45 GREEN LANE, PURLEY, SURREY.

## SYNTHESISER MODULES

Voltage-controlled modules for synthesiser construction and other musical MIRACLES! Catalogue 15p. D.E.W. Ltd., 254 Ringwood Road, Ferndown, Dorset.

## Hi Fi CABINETS



In Teak Veneer finish with Dark Grey Vynair Padded removable frame front.

Strongly constructed tuned reflex system with built in tunnel. Cut outs to take two 8in Units but may be modified to use other Units or Tweeters.

2ft 7in HIGH  
1ft 2in WIDE  
9½in DEEP

**£10 each**

Packing and Carriage £1.

Some are slightly marked, first orders have first selection. Suitable Units can be supplied if required.

## AMDIO LTD.

26 Reading Road South  
Fleet, Hants.

Callers welcome 9-5 Monday to Friday.

## FREE TO AMBITIOUS ENGINEERS

- THE LATEST EDITION OF ENGINEERING OPPORTUNITIES

### SEND FOR YOUR FREE COPY TO-DAY

NEW OPPORTUNITIES is a highly informative 76 page guide to the best paid engineering posts. It tells you how you can quickly prepare at home for a recognised engineering qualification and outlines a wonderful range of modern home study courses in all branches of Engineering. This unique book also gives full details of the Practical Radio & Electronics courses administered by our Specialist Electronics Training Division - explains the benefits of our free Appointments and Advisory service and shows you how to qualify for five years promotion in one year.

### PRACTICAL EQUIPMENT INCLUDING TOOLS

The specialist Electronics Division of B.I.E.T. NOW offers you a real laboratory training at home with all the practical equipment you need, plus basic practice and theoretical Courses for beginners in Radio, TV, Electronics, etc.

BRITISH INSTITUTE OF ENGINEERING TECHNOLOGY  
Dept. (B10), Aldermaston Court, Reading RG7 4PF

### SEND OFF THIS COUPON TO-DAY!

Tick subjects that interest you:  
 AMSE (Elec)  City & Guilds Certificate  RTEB Certificate   
 Radio Amateurs' Exam  DMG Certificate  Colour TV   
 Electronic Engineering  Computer Electronics  Radio and TV   
 Servicing  Practical Electronics  Practical TV and Radio   
 Please send booklets & full information without cost or obligation.

NAME..... AGE.....  
(BLOCK CAPITALS PLEASE)

ADDRESS .....



OCCUPATION.....

To: BIET Dept. B10, Aldermaston Court, Reading RG7 4PF  
Accredited by the Council for the Accreditation of Correspondence Colleges

## NEW BOOKS

<b>ABC'S OF INDUSTRIAL ELECTRONICS</b> by J. A. Wilson	£1.50
<b>1-2-3-4 SERVICING STEREO AMPLIFIERS</b> by Forest H. Belt	£2.50
<b>TRANSISTOR-T.V. SERVICING GUIDE</b> by Robert G. Middleton	£2.25
<b>SOLID-STATE SERVICING</b> by A. N. Slood	£2.50
<b>MODERN DICTIONARY OF ELECTRONICS</b> New 4th Edition by Rudolf F. Graf	£6.50
<b>101 QUESTIONS AND ANSWERS ABOUT AM, FM AND SSB</b> by Leo G. Sands	£1.75
<b>99 WAYS TO IMPROVE YOUR SHORTWAVE LISTENING</b> by Len Buckwalter	£1.75
<b>HANDBOOK OF BASIC ELECTRONIC EQUIPMENT</b> by W. Oliver	£1.75
(Published: Foulsham Technical)	
<b>TRANSISTORIZED RADIO CONTROL FOR MODELS</b> by D. W. Aldridge	£2.50
<b>MAKING AND USING ELECTRONIC OSCILLATORS</b> by W. Oliver	£2.00
<b>SEMI-CONDUCTOR DIODE LASERS</b> by R. W. Campbell and F. M. Mims	£1.90

### FOULSHAM-SAMS TECHNICAL BOOKS

(W. FOULSHAM & CO. LTD.)

YEOVIL ROAD, SLOUGH, BUCKS, ENGLAND

## V.H.F. EQUIPMENT

Manufacturers of the highest performance V.H.F. and U.H.F. equipment for five years. All this gear is from stock.  
**THE SENTINEL DUAL GATE MOSFET 2 METRE OR 4 METRE CONVERTER**

- ★ Low noise figure 2dB.
- ★ Gain 30dB.
- ★ Dual gate MOSFETs in RF and mixers for excellent overload and cross modulation characteristics.
- ★ 9-18 volts 15mA operation.
- ★ Size only 2½" x 3" x 1½" aluminium case.
- ★ 2 metre stock I.F. outputs: 2-4MHz, 4-6MHz, 9-11MHz, 14-16MHz, 18-20MHz, 23-25MHz, 24-26MHz, 28-30MHz.

★ 4 metre: 28-28.7MHz.  
A very popular and well thought of unit at only £13.75.  
**THE SENTINEL LOW NOISE 2 METRE PRE-AMPLIFIER**

- ★ Low noise figure 1dB.
- ★ Gain 18dB.
- ★ Size the same as converter.
- ★ 12 V. 5mA. supply.
- ★ Price £6.50.

### THE SENTINEL M.F.

A double conversion 2 metre converter to medium wave. Ideal for mobile use with a car radio or any medium wave radio with an aerial socket.

- ★ Performance as the Sentinel above.
- ★ I.F. output 0.5MHz to 1.5MHz.
- ★ Tunes 2 metres in two switched ranges, 144-145MHz and 145-146MHz. When switched 'OFF' MW is switched straight through.

- ★ Size 5" x 1½" front panel 4" deep. 9-18 V operation.
- ★ Price £18.75.

We do many converters and pre-amplifiers, some from stock, for use outside amateur bands, e.g. satellite band. Please enquire.

### SOLID STATE MODULES

63 Woodhead Road, Solid, Lockwood, Huddersfield. HD4 6ER.  
Telephone 0484 23991

## PLAIN-BACKED NEW STYLE SELF-BINDERS

The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

**PRICE 70p** P. & P. 14p

Available only from:—

**Data Publications Ltd. 57 Maida Vale London W9 1SN**

for your other magazines  
(max. format 7½" x 9½")



**COLOURS: MAROON OR GREEN**

(If choice not stated, colour available will be sent)

# SMALL ADVERTISEMENTS

(Continued from page 341)

**MINI MAINS PACK KIT.** Safe double-wound mini transformer, silicon rectifiers, 1000uF smoothing, instructions. Buildable to size of PP6 etc. 9V, 120mA. 90p, U.K. post 5p. Mail order only. AMATRONIX LTD., 396 Selsdon Road, South Croydon, Surrey CR2 0DE.

**FOR ALL YOUR ELECTRONIC COMPONENT** requirements. Send for free list to:- B. C. Electronic Supplies, 7 Regent Road, Huddersfield, HD1 4NR.

**FOR SALE:** Cossor 1035 double beam oscilloscope ext. & int. trigger or synch. £21. Telephone: 01-444 8216 evenings.

**"MEDIAN WAVE NEWS"** Monthly during Dx season - Details from: K. Brownless, 7 The Avenue, Clifton, York.

**THE BRITISH AMATEUR ELECTRONICS CLUB.** A club for all who are interested in electronics as a hobby. Quarterly Newsletter sent free to members. Subscription 50p per year. Details from Hon. Secretary, J. G. Margetts, 17 St. Francis Close, Abergavenny, Mon.

**TRANSISTORS TESTED.** All transistors no matter what type tested to full SPEC. Any type. Specification given in full, shown on typewritten sheet. Sent by express post for same day service if required. I.C.'s rudimentarily tested. Cost to you: 3 for 2p. Singles 1½p each. 5 for 4p. Quantities at 25 for 22p. 30 for 24p. Harrington, 25 Poynter Road, Enfield, Middlesex.

**FOR SALE:** Cossor sine/square wave generator. Offers? Gallop, 58 Burtleigh Road, Hertford, Herts. Telephone: 7093.

**UNTESTED GOLD BONDED DIODES:** BA144 type Germanium OA91 type 200 for 50p, Zeners BZY88 type 100 for 50p. Post free. J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

**IF YOU HAVE ENJOYED A HOLIDAY** on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:- The Hon. Membership Secretary, The Broads Society, "Icknield", Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

**FOR SALE:** Advance constant voltage transformer, input 190/260V, output 240V 500W. As new. £20. Edwards, 2 Newlands Lane, Culverston, Gravesend, DA13 0RD. Telephone: Fairseat 822503.

**WORLD DX CLUB** covers all aspects of SWLing on Amateur and Broadcast Bands through its monthly bulletin "Contact". Membership costs £1.38 a year. Enquiries to Secretary, WDXC, 11 Wesley Grove, Portsmouth, Hants., PO3 5ER.

**WANTED:** *Wireless World* issues wanted July 1971 to April 1972 inclusive, together with June 1972. Also *Radio Constructor* Volume 16. J. R. Ault, 23 Newton Street, West Bromwich, Staffs.

**TELSEN, LISSEN, GRAHAM FARISH** bakelite phenolic components with terminals required. Birkinshaw, 219 Teagues Crescent, Telford, Salop., TF2 6RA.

**RECITALS OF RECORDED MUSIC.** The second Saturday evening of each winter month. Next recital: December 9th, 1972, 8 p.m. at Woodford Green United Free Church Woodford Green, Essex. Bus routes 20, 20A, 179 and 275 - alight at "The Castle" stop. Programme consists of works by Bach, Handel, Ravel & Gabrieli.

**POSTAL ADVERTISING?** This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. - The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 1495.

# BENTLEY ACOUSTIC CORPORATION LTD.

The Valve Specialists

The Old Police Station, Gloucester Road, LITTLEHAMPTON Sussex. PHONE 6743

OA2 .30	I2BE6 .30	EAF801.50	ELL80 .75	PFL200.50	UL41 .54
OB2 .30	I2K5 .50	EB34 .20	EM80 .37	PL36 .46	UL84 .28
5Y4G .30	I2S07 .50	EB91 .10	EM81 .37	PL81 .42	UY41 .38
5Y4G .33	I2Q05 .24	EB81 .25	EM83 .75	PL82 .28	UY85 .23
5Y3GT .25	20P4 .89	EBC81 .29	EM84 .31	PL83 .30	X41 .50
5Z4G .33	30C15 .55	EBF80 .30	EM87 .34	PL84 .28	AC165 .25
6/30L2 .53	30C17 .54	EBF83 .38	EY51 .24	PL504 .60	AD140 .36
6A0Q5 .21	30C18 .58	EBF89 .26	EY81 .35	PL508 .90	AC113 .25
6AT6 .18	30S5 .61	ECC82 .25	EY83 .54	PL509 .130	AD161 .45
6AU6 .19	30FL1 .58	ECC331.50	EY87/6 .27	PL802 .75	AD162 .45
6AV6 .28	30FL2 .58	ECC81 .16	EY88 .40	PY33/2 .50	AF114 .25
6BA6 .19	30FL14 .66	ECC82 .19	FZ40 .40	PY81 .24	AF115 .15
6BF6 .20	30L15 .55	ECC83 .21	EZ80 .14	PY82 .23	AF121 .30
6BH6 .43	30L17 .65	ECC84 .28	EZ81 .20	PY83 .26	AF126 .18
6BL6 .39	30P12 .69	ECC85 .32	GY501 .75	PY88 .31	BC107 .13
6BR7 .79	30P19 .55	ECC88 .35	GZ34 .47	PY500 .95	BC108 .13
6BW6 .72	30P1 .57	ECCF80 .27	HVR2 .53	PY800 .31	BC113 .25
6BW7 .50	30PL13 .75	ECCF82 .25	KTW61 .64	PY801 .31	BC118 .23
6BZ6 .31	30PL14 .62	ECCF86 .64	KTW62 .63	QVQV3.	BC211 .38
6C4 .28	30P115 .87	ECH35 .50	KTW63 .50	10 120	BF159 .25
6CU5 .30	35A3 .48	ECH42 .57	KT66 .80	19 28	BF160 .20
6E5 .55	35L6GT .42	ECH81 .22	PC86 .44	U19 .173	BF180 .30
6F1 .59	35W4 .23	ECH83 .38	PC88 .44	U25 .62	BY100 .18
6F18 .45	35Z4 .24	ECH84 .34	PC97 .26	U26 .53	BY126 .15
6F23 .65	35Z5 .30	FCH80 .28	PC900 .29	U191 .56	BY127 .18
6F28 .60	50C5 .35	FCL82 .28	PC884 .27	U251 .62	OAS1 .09
6H6GT .15	50L6GT .45	ICL83 .52	PCC88 .49	U301 .60	OA91 .09
6K7G .10	90C1 .59	ECL84 .54	PCC89 .42	U801 .76	OA95 .09
6K8G .16	90C2 .70	ECL86 .33	PCC189 .46	UABC80	OC23 .38
6L6GT .39	DAF91 .20	F122 .63	PCF80 .26	URC41 .30	OC25 .38
6O7G .43	DAF96 .33	L141 .58	PCF82 .30	URC45 .45	OC25 .38
6O7(M) .41	DF91 .34	F180 .21	PCF84 .40	URC41 .30	OC35 .32
6D4GT .60	DF96 .34	F183 .54	PCF86 .34	URF80 .28	OC44 .10
6V6G .17	DK91 .26	F185 .25	PCF802 .28	URF89 .28	OC45 .11
6X4 .20	DK92 .35	F186 .27	PCF802 .37	URF82 .37	OC46 .15
7Y4 .60	DK96 .35	F189 .35	PCF86 .35	URC81 .29	OC75 .11
9D7 .78	DI92 .23	EF91 .17	PCF86 .35	URC81 .29	OC75 .11
10I1 .75	DL96 .35	EF92 .28	PCF86 .35	URC81 .29	OC75 .11
10F18 .35	DY87/6 .22	EF183 .25	PCF86 .35	URC81 .29	OC75 .11
12A6 .63	DY88 .29	EF184 .27	PCF86 .35	URC81 .29	OC75 .11
12AC6 .40	E80C1 .65	EH90 .54	PCF86 .35	URC81 .29	OC75 .11
12AD6 .40	E801 .120	EL34 .44	PD500 .144	UC183 .48	OC78D .15
12A6E .48	F88CC .60	F141 .53	PEN45 .47	UF41 .50	OC81 .11
12AT6 .23	F180F .90	L142 .53	PEN45DD	UR60 .35	OC81 .11
12A26 .21	EABC80 .51	L189 .21	UF85 .34	UR85 .34	OC82 .11
12A26 .28	EL91 .33	EL91 .33	UF86 .63	OC82 .11	OC82 .11
12BA6 .30	EAF42 .48	EL95 .32	43DD.*8	UF89 .27	OC84 .24

All goods are unused and boxed, and subject to the standard 90-day guarantee. Terms of business: Cash or cheque with order only. No C.O.D. orders accepted. Post/packing charge 3p per item subject to a minimum of 9p per order. Orders over £5 post free. All orders despatched same day by first class mail. Complete catalogue with conditions of sale 7p post paid. Any parcel insured against damage in transit for only 3p extra per order. Business hours 9 a.m.-5.30 p.m. Mon.-Fri. Closed Sats. Please enclose S.A.E. with all enquiries.

## QUALITY COMPONENTS - BUDGET PRICES

<b>TRANSFORMERS</b>		
Hygrade Filament 0-245V tapped primary, 2 x 6 3V, 1 8A secondaries		£1.95
Miniature Mains 0-250V primary, 2 x 12V, 6VA secondaries		£1.10
Sub-Miniature Mains 0-240V primary, 2 x 12V, 50mA secondaries		£1.25
<b>RESISTORS</b>		<b>VOLUME CONTROLS</b>
10% Carbon, E12 values, 10-10M, ½ watt 1p		Small size, LOG or LIN.
1 watt 3p		5, 10, 25, 50, 100, 250.
5% Hystab, E24 values, 10 1M, 1/2 watt 2p		500KΩ, 1MΩ
1 watt 3p		Only 16p each
2% M.O. E24 values, 10 1M, ½ watt 4p		
<b>CAPACITORS</b>		
Tantalum - µF/V 0 1/35, 0 22/35, 0 47/35, 1 35, 2 2/35, 4 7/35, 10/63, 10/25, 17p		
10/16, 22/16, 47/6 3, 100/3, All at one price		
Moulded Polyester 250V, 0-01, 0 022, 0-C33, 5p, 0 047, 0-068, 0-1, 7p, 0 22, 10p, 0 33, 12p, 0 47, 15p, 0 68, 18p, 1 0 22p, 2 2, 35p, 10/63, 10/25, 17p, 47/40, 7p, 47/40, 10p, 100/63, 13p, 100/10, 7p, 220/40, 470/16, 13p, 1000/16, 15p.		
<b>FIXED VOLTAGE REGULATORS</b>		
TO3 case. Gives stabilized supply MVR 5 volt, MVR 12 volt, MVR 15 volt. All at £1.50.		
<b>STRANDED CABLE</b>		
16/0 2mm, 3p per metre, 11 colours, 1 metre of each		33p per pack
21 colours, 1 metre of each		60p per pack
Extra Flexible Wire, for testmeter leads, Red or Black		4p per metre
Probe Clips, for testmeters, Red or Black		12p each
Lightweight Screened Wire		Single 7p per metre, Twin 10p per metre.
<b>TRANSISTORS</b>		
AC 107 28p	AC 176 20p	BC 147 20p
AC 126 27p	AD 149 47p	BC 148 20p
AC 127 23p	BC 107 12p	BC 168 22p
AC 128 20p	BC 108 12p	BC 169 20p
AC 132 19p	BC 109 12p	BD 112 44p
		BFY 51 23p
		OC 81D 19p
		OC 28 52p
		OC 71 14p
		OC 72 19p
		OC 162 75p pr.
		OC 75 22p
		OC 75 22p
<b>PRINTED CIRCUIT BOARD</b>		
Approximate size 12" x 8" Bargain at only 25p per board		
<b>VEROBOARD</b>		<b>SERVICING AIDS - AEROSOLS</b>
0-1	0-15	Freezer
2 1/2" x 3 1/2"	20p 16p	Contact Fluid
3 1/2" x 5"	24p 26p	Insulating Lacquer
		60p
		75p
		80p

The above shows only a very small selection from our CATALOGUE price 25p post free by return  
All orders over 50p POST FREE IN U.K. S.A.E. with all queries  
We can supply ALL R. S. COMPONENTS, mostly by return of post

**CELETRON-E**  
P.O. Box No. 1, Llantwit Major, Glamorgan, CF6 9YN

# INTERNATIONAL SHORT WAVE LEAGUE



Membership £2.00 per annum (U.S.A. \$6.00) including 12 monthly issues of "Monitor" – the League journal. Including free use of all Services, QSL Bureau etc.

**THE LARGEST S.W.L. ORGANISATION  
IN THE WORLD**

For full details write to:  
The Secretary, I.S.W.L., 1 GROVE ROAD, LYDNEY, GLOS. GL15 5JE.

## ESSENTIAL BOOKS

**HOW TO MAKE WALKIE-TALKIES FOR LICENSED OPERATION.** Only 40p post free. **MOBILE RADIO TELEPHONES.** Important reference book for users of commercial mobile communications equipment. Includes chapters on installation, operation and maintenance. Contains photos and diagrams etc. Price £2.60, including post. **AN ELECTRONIC ORGAN FOR THE HOME CONSTRUCTOR.** Simple and straightforward instructions for building an inexpensive organ for use in church, hall or home. 100 pages. £1.25, postage 15p. **RADIO UPKEEP AND REPAIRS.** A practical handbook on servicing principles and receiver maintenance. £1.25, incl. postage. **GOVERNMENT SURPLUS WIRELESS EQUIPMENT HANDBOOK.** Contains circuits, data, illustrations and valuable information for British/USA receivers, transmitters, trans/receivers. With modifications to sets and test equipment. Latest impression £3.25, incl. postage. Available from: Dept. RC. GERALD MYERS, 18 SHAFTESBURY STREET, LEEDS LS12 3BT.

## FREQUENCY LIST TRANSFERS

We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500kc/s points. Each frequency is repeated. Two sheets for 5p, five sheets for 10p, postage 3p.

**DATA PUBLICATIONS LTD.,  
57 Maida Vale, London W9 1SN.**

## DATA BOOK SERIES

- DB5 TV FAULT FINDING**  
124 pages. Price 50p, postage 6p.
- DB6 RADIO AMATEUR OPERATOR'S HANDBOOK**  
80 pages. Price 45p, postage 6p.
- DB16 RADIO CONTROL FOR MODELS**  
192 pages. Price 75p, postage 8p.
- DB17 UNDERSTANDING TELEVISION**  
512 pages. Price £2.10, postage 25p.
- DB18 AUDIO AMPLIFIERS**  
128 pages. Price 53p, postage 6p.
- DB19 SIMPLE SHORT WAVE RECEIVERS**  
140 pages. Price 80p, postage 6p.

I enclose Postal Order/Cheque for \_\_\_\_\_ in payment for \_\_\_\_\_

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

(BLOCK LETTERS PLEASE)

*Postal Orders should be crossed and made payable to Data Publications Ltd.*

*Overseas customers please pay by International Money Order.*

*All publications are obtainable from your local bookseller.*

**Data Publications Ltd., 57 Maida Vale, London W9 1SN**

**Please mention THE RADIO CONSTRUCTOR when writing to advertisers**

## COIL DATA II

The Table gives calculated inductance values, in microhenrys, of single-layer air-cored coils having diameters of  $\frac{1}{4}$  in. and  $\frac{1}{8}$  in. and lengths (l) as shown. Thus, a 14-turn coil of diameter  $\frac{1}{4}$  in. and length  $\frac{1}{4}$  in. has a calculated inductance of 1.3 $\mu$ H.

Turns	Dia. $\frac{1}{4}$ in.			Dia. $\frac{1}{8}$ in.		
	l = $\frac{1}{4}$ in.	l = $\frac{1}{2}$ in.	l = 1 in.	l = $\frac{1}{4}$ in.	l = $\frac{1}{2}$ in.	l = 1 in.
4	0.21	0.14	0.10	0.29	0.20	0.15
6	0.47	0.31	0.23	0.63	0.45	0.34
8	0.84	0.55	0.41	1.2	0.80	0.60
10	1.3	0.86	0.64	1.8	1.3	0.93
12	1.9	1.2	0.92	2.6	1.8	1.4
14	2.6	1.7	1.3	3.6	2.5	1.8
16	3.4	2.2	1.6	4.7	3.2	2.4
18	4.3	2.8	2.1	6.0	4.5	3.1
20	5.3	3.4	2.6	7.4	5.0	3.8
25	8.2	5.4	4.0	12.0	7.8	5.9
30	12.0	7.8	5.8	17.0	11.0	8.3
35	16.0	11.0	7.8	22.0	15.0	12.0
40	21.0	14.0	10.0	29.0	20.0	15.0
50	33.0	22.0	16.0	46.0	31.0	24.0

# U.K.'s LARGEST ELECTRONICS CENTRES!

## HENRY'S RADIO LTD. EDGWARE ROAD, LONDON, W.2.




**NOW OPEN!**

404-406 ELECTRONIC COMPONENTS & EQUIPMENT 01-402 8381  
 354-356 HIGH FIDELITY & TAPE EQUIPMENT 01-402 5854/4736  
 309 PA - DISCO - LIGHTING HIGH POWER SOUND 01-723 6963  
 303 BARGAIN STORE SPECIAL OFFERS All Mail to: 303, Edgware Rd., London, W2 1B W

ALL YOUR ELECTRONIC REQUIREMENTS WITHIN 200 YARDS. CALL IN AND SEE FOR YOURSELF.

### BUILD THE TEXAN
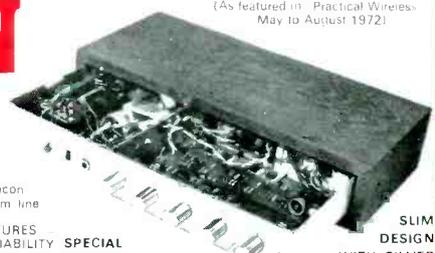
#### 20 + 20 WATT INTEGRATED I.C. STEREO AMPLIFIER



(As featured in Practical Wireless May to August 1972)

**FREE TEAK CABINET** with complete kits  
**FEATURES** New slim design with 6 ICs IC sockets, 10 silicon transistors, 4 rectifiers, 2 zeners. Special Gardeners low field slim line transformer. Fibreglass PC panel. Complete chassis work.  
**HIGH QUALITY AND STABILITY ARE PREDOMINANT FEATURES** DEVELOPED BY TEXAS ENGINEERS FOR PERFORMANCE, RELIABILITY AND EASE OF CONSTRUCTION  
**FACILITIES** On/off switch indicator, headphone socket, separate treble, bass, volume and balance controls, scratch and rumble filters, mono/stereo switch, input selector, Mag. P.U. Radio Tuner Aux. Can be altered for Mic. Tape. Tape head etc. (Parts list Ref. 20 on request) (Parts list Ref. 20 on request)  
 Constructional details Ref. No. 21 30p  
 Designed approved kits distributed by Henry's Radio Ltd.

**SPECIAL KIT PRICE £28.50** P&P 45p  
 Overall chassis size 14 1/2" x 6" x 2" high

RECORD DECKS CHASSIS (POST 50p)		
SP25/3	£10 25	H770 £14 50
MP60	£9 95	MP610 £12 95
AP76	£17 95	GL75 £28 60
PLINTH COVERS (State Model)		
SP25/MP60/610	£3 30	(Post 40p)
AP76	£4 50	(Post 40p)
CART PLINTH COVER (Post 70p)		
(HL) MP60/G800/PC		£18 50
MP610/SC5MD/1PD2/PC		£19 95
AP76/M7565M/PC		£32 50
AP76/M7565M/PC		£39 95
(HL) AP76/G800/PC		£28 25
(HL) SP25/G800/PC		£18 95
H770/G800/1PD1/PC		£24 50
(HL) 2025/STANCO/PC		£13 95
MP60/SC5MD/PC		£17 25
(HL) GL75/G800E/PC		£41 95
(HL) GL75/G800/PC		£38 95

**ULTRASONIC TRANSDUCERS**  
 Operate at 40kc/s up to 100 kc/s. Ideal remote switching and signalling. Complete with data and circuits.  
**PRICE PER PAIR £5.90** Post 10p

### LOW COST HI-FI SPEAKERS

E.M.I. Size 13 1/2" x 8 1/2" Large Ceramic Magnet  
**TYPE 150** 6 watt, 3, 8 or 15 ohms £2.20, Post 22p  
**TYPE 150TC** Twin cone version £2.75, Post 22p  
**TYPE 450** 10 watt with twin tweeters and crossover, 3, 8 or 15 ohms £3.85, Post 25p  
**TYPE 350** 20 watt with tweeter and crossover, 8 and 15 ohms £7.70, Post 28p

**POLISHED CABINETS** 150 150TC 450 £4.60 Post 30p  
 ASSEMBLED IN POLISHED CABINETS (8 mm) Series 6 (Assembled 150TC) per pair £16.50 post 70p  
 Series 8 (Assembled 450) per pair £18.95 post 70p

### TEST EQUIPMENT

**JUST A SELECTION**  
 SE250B Pocket Pencil Signal Injector £1.90  
 SE500 Pocket Pencil Signal Tracer £1.50  
 TH330D Rugged ZK Volt £4.55 With case £4.99  
 TE15 Grid Dip Meter 640 KHz - 280 MHz £13.45  
 500 30 K. Volt Multimeter £9.25. With leather case £10.50  
 200H 20K Volt Multimeter £4.20 With case £4.95  
 AF105 50k Volt Multimeter £8.50 With case £9.50  
 U4341 AC DC Multimeter with transistor tester with steel case £10.50  
 TE30D RT Generator 120kHz - 500kHz Carr 35p £15.95  
 TE22D Audio Generator 20kHz - 200kHz Carr 35p £17.50  
 CI 5 3 Pulse Scope 10kHz - 10MHz Carr 60p £39.00  
 TE65 Valve Voltmeter 28 ranges Carr 20p £17.50  
**ALL NOMBREX MODELS IN STOCK**

**POWER INTEGRATED CIRCUITS**  
 Plessey SL403D 3 watt with 8-page data, favours and circuits £1.50. P.C. Board 60p. Intel Sim 14p  
 Sinclair IC12 - 6 watt with data and circuits £1.80  
 TH913P - 20 Watt Power Amp Module £4.57  
 TH9014P - IC Preamp £1.50  
 Data/Circuits for above No. 42 10p

### NEW MW/LW TUNER TO BUILD ML-3

Uses Mullard Module. Slow motion tuning.  
 Built in battery. Ferrite aerial. Overall size 7" x 2 1/2" x 3 1/2"  
**TOTAL COST TO BUILD £4.85** Post 15p All parts sold separately. Leaflet No 6

### BUILD THIS VHF FM TUNER

5 TRANSISTORS 300 kc/s BAND-WIDTH, PRINTED CIRCUIT. HIGH FIDELITY REPRODUCTION. MONO AND STEREO  
 A popular VHF FM Tuner for quality and reception of mono and stereo. There is no doubt about it—VHF FM gives the REAL sound. All parts sold separately. Free Leaflet No 3 & 7.  
**TOTAL £6.97, p.p. 20p. Decoder Kit £5.97.**  
 Tuning meter unit £1.75.  
 Mains unit (optional) Model PS900 £2.47. Post 20p.  
 Mains unit for Tuner and Decoder PS1200 £2.62. Post 20p.

### MARriot TAPE HEADS

4 TRACK MONO or 2 TRACK STEREO  
 '17 High Impedance £2.00  
 '18 Med Impedance £2.00  
 '36 Med Low Imp £2.50  
 Erase Heads for above 75p  
 '63 2 track mono - Hi Imp £1.75  
 '43 Erase Head for above 75p

### "BANDSPREAD" PORTABLE TO BUILD

Printed circuit transformer design using Mullard RF 77 Module. Medium and Long Wave Bands plus Medium Wave. Bandspread for extra selectivity. Also slow motion geared tuning, volume push pull output. Fibreglass PVC covered cabinet, car aerial socket. Attractive appearance and performance. **TOTAL COST TO BUILD £7.98** p.p. 32p. (Battery 22p)  
 All parts sold separately. Leaflet No 7


### PA-DISCO-LIGHTING

UK's Largest Range. Write phone or call in. Details and demonstrations on request.  
 DJ301 3 Channel sound to light unit 3Kw £29.75  
 DJ401 3 Channel Mic (built in) to light 3 Kw £38.75  
 DJ705 70 watt Disco amp/mixer £49.95  
 DISCOAMP 100 watt Disco amp/mixer £67.95  
 DJ105S 30 watt Disco amp/mixer £32.75  
 Anti-Feedback Quality Mic. £11.50  
 DJ500 50 watt PA Amp £56.25  
 DJ300 150 watt rms Group Valve Amp £99.50  
 ● Portable Discos - Details on request  
 ● Credit terms for callers

FIBRE OPTICS LIGHTING £29.75  
 EFFECTS MICS £38.75  
 PROJECTORS £49.95  
 SPOTS SPKRS £32.75  
 DIMMERS £11.50  
 MIXERS STANDS £56.25  
 Everything for PA Disco Lighting. Free Stock List Ref. No 16
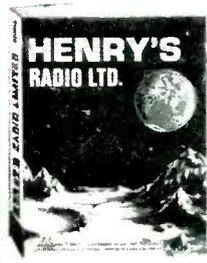
### 7 SEG & NIXIE TUBES

(Post 15p net 1 to 6)  
 XN3, XN13 GN40 9 Side view with data 85p  
 GNP 7, GNP B 0 9 Side view with decimal points and data 95p  
 3015F 7 segment £2 each, £7 per 4 with data  
 12 and 24 hour clock circuits for above. Ref. No 31 15p.



### CATALOGUE

Fully detailed and illustrated covering every aspect of Electronics - plus data, circuits and information.  
 10,000 Stock lines at Special Low Prices and Fully Guaranteed.  
**PRICE 55p** Post Paid (40p FOR CALLERS)  
**PLUS! FIVE 10p VOUCHERS**

Send to this address - Henry's Radio Ltd. (Dept. RC) 3 Albemarle Way London E.C.1 - for catalogue by post only. All other mail and callers to 303 see above.

### SINCLAIR PROJECT 60 MODULES - SAVE POUNDS

Z30 £3.57 250 £4.37  
 STEREO 60 £7.97 PZ5 £3.97  
 PZ6 £6.37 PZ8 £4.77  
 Transformer for PZ8 £2.95  
 Active Filter Unit £4.45  
 Stereo FM Tuner £16.95  
 IC12 E1 80 Q16 £15.15 p  
 Post etc 20p per item

PACKAGE DEALS Post 25p  
 2 x Z30, Stereo 60, PZ5 £15.95  
 2 x Z30, Stereo 60, PZ6 £18.00  
 2 x Z50, Stereo 60, PZ8 £20.25  
 Transformer for PZ8 £2.95  
 PROJECT 60S KIT £19.95

### MINIATURE AMPLIFIER

5 transistor 300mW o/p. Fitted volume and sensitivity control 9 vlt operated.  
**£1.75 each P/P 15p**

### QUALITY SLIDER CONTROLS

60mm stroke singles and ganged. Complete with knobs 5K, 10K, 25K, 100K, 250K, 500K 1 meg. Log and Lin. 45p each. 10K, 25K, 50K, 100K, 250K Log and Lin ganged 75p each.

### HI-FI & TAPE EQUIPMENT

As knowledgeable as UK's largest stockists with lowest prices plus 12 months guarantee. Write or call for FREE 16 page lists (Ref 17)

## MORE OF EVERYTHING AT LOW PRICES ALWAYS FROM HENRY'S

All the parts you need plus Data and Circuits. Get a Catalogue - it's all in there!  
 Prices subject to change without notice. E & Q.E.

309-354-356-404-406 Open 6 days a week 9am - 6pm (303 closed Thurs.) All Stores open all day Saturday

**H MORE OF EVERYTHING AT THE RIGHT PRICE ALWAYS AT HENRY'S H**