

RADIO & ELECTRONICS CONSTRUCTOR

AUGUST 1977
Volume 31 No. 1

Published Monthly (1st of Month)
First Published 1947

Incorporating The Radio Amateur

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone 01-286 6141 *Telegrams*
Datbux, London

© Data Publications Ltd., 1977. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £6.00 (U.S.A. and Canada \$12.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that such queries cannot be answered over the telephone; they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production.—Web Offset.


L.E.D. VU METER	12
by A. P. Roberts	
ULTRAVIOLET DEPOLYMERIZATION	17
by Michael Lorant	
NEWS AND COMMENT	18
12-NOTE TONE GENERATOR	20
by I. R. Sinclair (Special Series — Blob-a-job No. 3)	
TIMES PAST	24
by H. Ross Macdonald	
LOW VOLTAGE ZENERS	26
by R. J. Caborn	
AUTOMATIC POLARITY/BASE RESOLVER	27
(Suggested Circuit) by G. A. French	
SHORT WAVE NEWS—For DX Listeners	30
by Frank A. Baldwin	
MEDIUM WAVE POCKET RADIO	32
by R. A. Penfold	
VARIABLE OSCILLOSCOPE CALIBRATOR	36
by N. R. Wilson	
THE 'JUBILEE' A.M.-F.M. RECEIVER	38
Part 2 (Conclusion) by Sir Douglas Hall, K.C.M.G.	
SIMPLE QUADRAPHONIC AMPLIFIER	42
Part 3 (Conclusion) by R. A. Penfold	
IN YOUR WORKSHOP — Car Radio Repair	45
TRADE FUNCTION	50
R.S.G.B. AT ALEXANDRA PALACE	51
COLLECTOR SPECIFICATIONS	54
(Notes For Newcomers) by F. T. Jones	
RADIO TOPICS	56
by Recorder	
NEW PRODUCTS	58
ELECTRONICS DATA No. 25	iii
(For The Beginner — Potential Dividers)	

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN

The *Radio & Electronics Constructor* is printed by Swale Press Ltd.

THE SEPTEMBER/OCTOBER ISSUE
WILL BE PUBLISHED ON
1st SEPTEMBER


Blob-a-Bit-of-Better Board

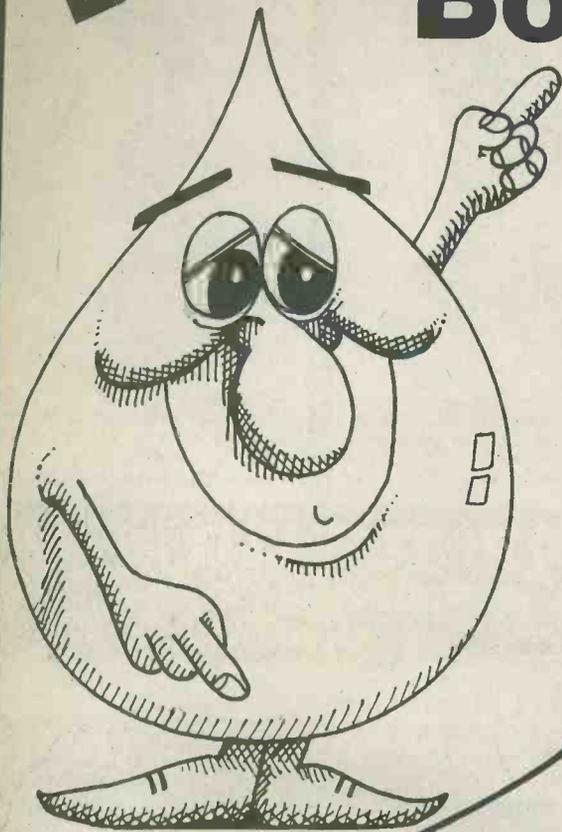

"Been a Blob-a-jobbing? Tried Blob-board, the new circuit board that needs only two hands to use, and doesn't come apart when you take the components off? Any circuit that can be built on a circuit board can be built more easily on a Blob-Board. Simply number the circuit junctions in the same way as the examples in the Blob-a-job series and **build**, no layout drawings needed. Components are butt soldered to one side, you can see the components and the track connectors without turning the board over. Now Blob-a-Bit-of-Better-Board.

Last Month's project was the Square wave generator built on ZV2V5 Blob Board. This month's project is the 12-note generator built on ZB 2IC Blob-Board. Next month's Blob-a-job is a Microphone pre-Amplifier built on a ZB 2v5 Blob-board.

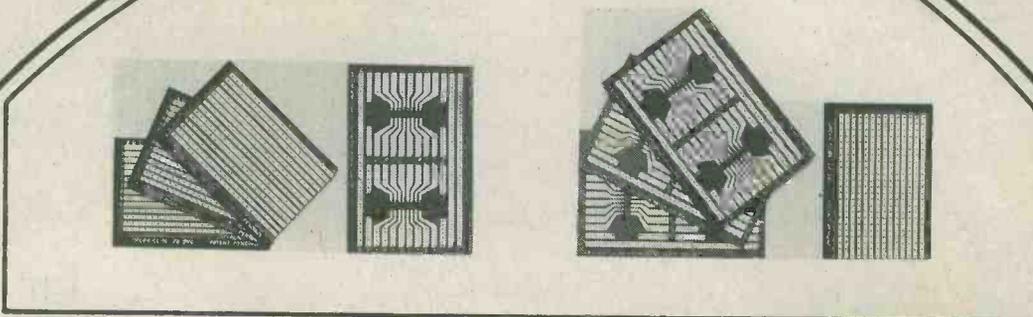As
a special
offer to
Radio and Electronics
Constructor readers



Buy pack of 3 2V5 Blob-Boards
and Get 1 2-IC Blob-Board Free
Please rush me

.....Packs of 3 2V5 + My Free 2-IC Blob
For only £0.62 per pack of 3.
Please add 20p for Post +VAT for all orders

Buy pack of 3 2-IC Blob-Board
and Get 1 2V5 Blob-Board Free.
Please rush me

.....Packs of 3 2-IC + My Free 2V5 Blob
For only £1.01 per pack of 3.
Please add 20p for Post +VAT for all orders

All goods are ex-stock delivery. Please enclose cheque,
postal order payable to PB Electronics (Scotland) Ltd.
Offer Available from All Good Component Stockists. Save on Post!



P.B. Electronics (Scotland) Ltd.
57 High Street, Saffron Walden, Essex CB10 1AA England.
Telephone: Saffron Walden (0799) Telex: 817185.

NEW for electronic design engineers!

FIX-PRINT for printed circuits



Invaluable for holding P.C.B.'s and other panels when inserting and soldering components. Can be adjusted to suit work up to 280mm, rotating to gain access to reverse side and locks in any position. All metal.

Price **£10** inc. VAT. p&p £1


Write or phone for full details

S2 Drill Stand



Robust, all metal with ample throat dimensions. Adjustable height cantilever with lever actuated feed. Spring return. Will accept both P1 & P2 drills
Price **£18.50** inc. VAT. p&p 106p

S1 Drill Stand

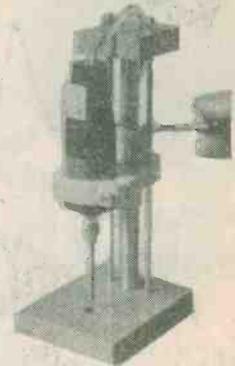

Constructed to take the popular P1 drill and ensure a high degree of accuracy in all types of electrical precision work.

Price **£5.13** inc. VAT. p&p 38p




PRECISION PETITE LTD

119a HIGH STREET TEDDINGTON MIDDLESEX TW11 8HG

TEL: 01-977 0878

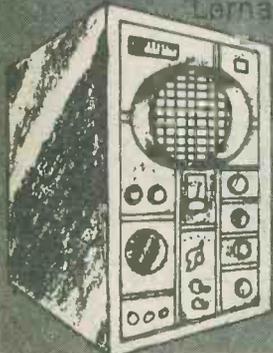1. Understand electronics.


Step by step, we take you through all the fundamentals of electronics and show you how easily the subject can be mastered using our unique Lorna-Kit course.



- (1) Build an oscilloscope.
- (2) Read, draw and understand circuit diagrams.
- (3) Carry out over 40 experiments on basic electronic circuits and see how they work.

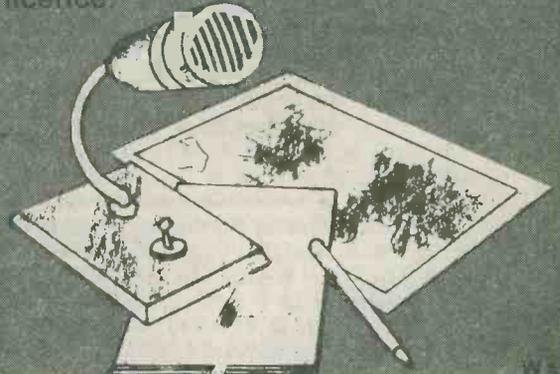2. Become a radio amateur.

Learn how to become a radio-amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.



Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

P.O. Box 156, Jersey, Channel Islands

NAME _____

ADDRESS _____

Block caps please

REC 87

REVOR OPTICAL & TECHNICAL

42 TAVISTOCK STREET
LONDON W.C.2
Tel. 01-836 4536



4" dia. lens

£10.00

**POST
FREE**

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE,
PRECISION GROUND AND
POLISHED LENS, CHROME PLATED
FRAME AND FLEXIBLE TUBE.
IDEAL FOR HOBBIES, AND
DETAILED WORK WHICH REQUIRES
BOTH HANDS FREE.

CALLERS WELCOME

(Subject to price ruling at the time of issue)


NEW STYLE SELF-BINDER

for "Radio & Electronics Constructor

(Max format 7½" x 9½")

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

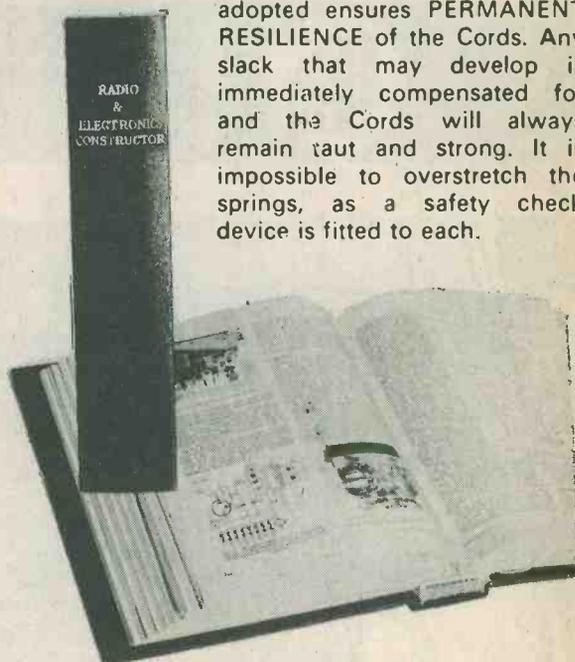

PRICE **£1.20** P.&P. 30p
including V.A.T.

BINDERS FOR THE NEW FORMAT
NOT YET AVAILABLE

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN



Wilmslow Audio

THE firm for speakers!


SEND 10P FOR THE WORLDS BEST
CATALOGUE OF SPEAKERS, DRIVE UNITS
KITS, CROSSOVERS ETC. AND DISCOUNT
PRICE LIST

ACT ● AUDAX ● BAKER ● BOWERS &
WILKINS ● CASTLE ● CELESTION ●
CHARTWELL ● COLES ● DALESFORD ●
DECCA ● EMI ● EAGLE ● ELAC ● FANE ●
GAUS ● GOODMAN'S ● HELME ● I.M.F. ●
ISOPHON ● JR. ● JORDAN WATTS ● KEF ●
LEAK ● LOWTHER ● MCKENZIE ● MONITOR
AUDIO ● PEERLESS ● RADFORD ● RAM ●
RICHARD ALLAN ● SEAS ● TANNAY ●
VIDEOTONE ● WHARFEDALE

WILMSLOW AUDIO DEPT REC

SWAN WORKS, BANK SQUARE, WILMSLOW
CHESHIRE SK9 1HF

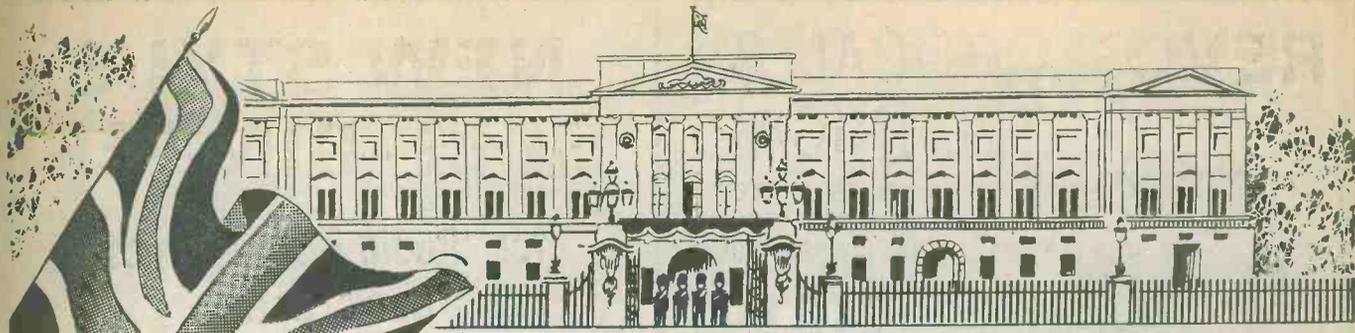Discount HiFi Etc. at 5 Swan Street and 10 Swan Street
Tel: Wilmslow 29599 for Speakers Wilmslow 26213 for HiFi



JUBILEE SALE

74 SERIES TTL IC's

Type	Quantity 100			Type	Quantity 100			Type	Quantity 100		
1	£	p	£ p	1	£	p	£ p	1	£	p	£ p
7400	0.09	0.08		7448	0.70	0.68		74122	0.45	0.42	
7401	0.11	0.10		7450	0.12	0.10		74123	0.65	0.62	
7402	0.11	0.10		7451	0.12	0.10		74141	0.68	0.65	
7403	0.11	0.10		7453	0.12	0.10		75145	0.75	0.72	
7404	0.11	0.10		7454	0.12	0.10		74150	1.10	1.05	
7405	0.11	0.10		7460	0.12	0.10		74151	0.65	0.60	
7406	0.28	0.26		7470	0.24	0.23		74153	0.70	0.68	
7407	0.28	0.25		7472	0.20	0.19		74154	1.20	1.10	
7408	0.12	0.11		7473	0.26	0.22		74155	0.70	0.68	
7409	0.12	0.11		7474	0.24	0.23		74156	0.70	0.68	
7410	0.09	0.08		7475	0.44	0.40		74157	0.70	0.68	
7411	0.22	0.20		7476	0.26	0.25		74160	0.95	0.85	
7412	0.22	0.20		7480	0.45	0.42		74161	0.95	0.85	
7413	0.26	0.25		7481	0.90	0.88		74162	0.95	0.85	
7416	0.28	0.25		7482	0.75	0.73		74163	0.95	0.85	
7417	0.26	0.25		7483	0.88	0.82		74164	1.20	1.10	
7420	0.11	0.10		7484	0.85	0.80		74165	1.20	1.10	
7422	0.19	0.18		7485	1.10	1.00		74166	1.20	1.10	
7423	0.21	0.20		7486	0.28	0.26		74174	1.10	1.00	
7425	0.25	0.23		7489	2.70	2.50		74175	0.85	0.82	
7426	0.25	0.23		7490	0.38	0.32		74176	1.10	1.00	
7427	0.25	0.23		7491	0.65	0.62		74177	1.10	1.00	
7428	0.36	0.34		7492	0.43	0.35		74180	1.10	1.00	
7430	0.12	0.10		7493	0.38	0.35		74181	1.90	1.80	
7432	0.20	0.19		7494	0.70	0.68		74182	0.80	0.78	
7433	0.38	0.36		7495	0.60	0.58		74184	1.50	1.40	
7437	0.26	0.25		7496	0.70	0.68		74190	1.40	1.30	
7438	0.26	0.25		74100	0.95	0.90		74191	1.40	1.30	
7440	0.12	0.10		74104	0.40	0.35		74192	1.10	1.00	
7441	0.60	0.57		74105	0.30	0.25		74193	1.05	1.00	
7442	0.80	0.70		74107	0.30	0.25		74194	1.05	1.00	
7443	0.95	0.90		74110	0.48	0.45		74195	0.80	0.75	
7444	0.95	0.90		74111	0.76	0.72		74196	0.90	0.85	
7445	0.80	0.76		74118	0.85	0.82		74197	0.90	0.85	
7446	0.80	0.75		74119	1.30	1.20		74198	1.90	1.80	
7447	0.70	0.68		74121	0.28	0.26		74199	1.80	1.70	

Devices may be mixed to qualify for quantity price. Data is available for the above series of IC's in booklet form Price 35p

CMOS ICs

Type	Price	Type	Price	Type	Price
CD4000	£0.18	CD4022	£0.80	CD4046	£0.95
CD4001	£0.18	CD4023	£0.18	CD4047	£0.75
CD4002	£0.18	CD4024	£0.64	CD4048	£0.46
CD4006	£0.80	CD4025	£0.18	CD4050	£0.46
CD4007	£0.18	CD4026	£1.85	CD4054	£0.95
CD4008	£0.80	CD4027	£0.48	CD4055	£1.60
CD4009	£0.50	CD4028	£0.80	CD4056	£1.15
CD4010	£0.50	CD4029	£0.95	CD4069	£0.32
CD4011	£0.18	CD4030	£0.46	CD4070	£0.32
CD4012	£0.18	CD4031	£1.80	CD4071	£0.20
CD4013	£0.42	CD4035	£1.40	CD4072	£0.20
CD4015	£0.80	CD4037	£0.78	CD4081	£0.20
CD4016	£0.42	CD4040	£0.78	CD4082	£0.20
CD4017	£0.80	CD4041	£0.68	CD4510	£1.10
CD4018	£0.85	CD4042	£0.68	CD4511	£1.25
CD4019	£0.46	CD4043	£0.78	CD4516	£1.10
CD4020	£0.95	CD4044	£0.78	CD4518	£1.10
CD4021	£0.85	CD4045	£1.15	CD4520	£1.10

ORDERING

Please word your orders exactly as printed not forgetting to include our "J" numbers

V.A.T.

Add 12½% to prices marked * add 8% to all others

POSTAGE AND PACKING

Add 25p for postage and packing unless otherwise shown. Add extra for Airmail. Minimum Order £1.00

TESTED TRANSISTOR PAKS

All devices brand new, tested and coded

J1	3 each AC128/AC176	J16	2 each BFY50/51/52
J2	10 off BC107	J17	6 x OC71
J3	10 off BC108	J18	4 each ZTX108/9 2 x ZTX107*
J4	10 off BC109	J19	2 each ZTX301/2 4 x ZTX300*
J5	3 each BC148/149-2 BC147*	J20	2 each ZTX500/1/2
J6	3 each BC163/171/172*	J21	4 each 2N706/2N708
J7	2 each BC177/8/9	J22	1 each 2N2218/19/21/22
J8	2 each BC182/3/4*	J23	2 each 2N2904/05
J9	2 each BC212/213/214*	J24	3 x 2N2907 2 x 2N2906
J10	2 x BC327 3 x BC328*	J25	7 x 2N2926 G*
J11	2 x BC337 3 x BC338*	J26	4 x 2N3053
J12	2 each BF115-BF167-BF173	J27	2 x 2N3055
J13	2 x BF194/5/6*	J28	3 each 2N3702/03/04*
J14	2 x BF258	J29	3 each 2N3904/06*
J15	2 x BFX29 3 x BFX84		

PRICE 60p PER PAK

TESTED DIODE PAKS

J30	12 x OA81	J34	15 x IN4148	J38	8 x IN4007
J31	12 x OA91	J35	20 x IN4001	J39	5 x IN5400
J32	12 x OA200	J36	15 x IN4002	J40	5 x IN5401
J33	12 x OA202	J37	10 x IN4004	J41	4 x IN5404
				J42	3 x IN5408

PRICE 60p PER PAK

OPTOELECTRONICS

J43	4 x DL707 + Data	£2.80
J44	5 x .125 Red LED	£0.50
J45	5 x .2 Red LED	£0.60
J46	5 x 2 and .125 LED's mixed colours	£0.50
J47	3 x ORP12 equivalent	£1.20
J48	5 x OCP71	£1.00

THYRISTOR PAKS

J49	1amp SCR's 2 x 50V, 1 x 400V, 1 x 600V	£1.00
J50	5amp SCR's 1 x 50V, 2 x 400V, 1 x 600V	£1.50

UNIJUNCTION/F.E.T. PAKS

J51	6 x TIS43/UT46	£1.00
J52	4 x 2N3819	£0.60

P.C.B. PRODUCTS

J53	2 x Etch resist pens	£1.00
J54	2 x Etchant paks	£1.00

D.I.Y. PRINTED CIRCUIT KIT

CONTAINS 6 pieces copper laminate, box of etchant powder and measure, tweezers, marker pen, high quality pump drill, Stanley knife and blades, 6" metal rule.

FULL easy-to-follow instructions

J59 SALE PRICE £5.50

RESISTOR PAK

J55	240 first quality ¼w resistors-mixed from 100ohm - 820k	£1.60*
J56	160 first quality ¼w resistors-mixed from 100ohm - 820k	£1.80*

ELECTROLYTIC PAK

J57	54 first quality miniature electrolytics from .47uF - 1000uF	£1.20*
-----	--	--------

CERAMIC PAK

J58	93 first quality ceramic capacitors-mixed from 22pF - .047uF	£1.60*
-----	--	--------

I.C. SOCKET PAKS

J60	11 x 8 pin D.I.L. Sockets	£1.00
J61	10 x 14 pin D.I.L. Sockets	£1.00
J62	9 x 16 pin D.I.L. Sockets	£1.00

ZENER PAKS

J63	20 mixed value 400mW zener diodes 3-10V	£1.00
J64	20 mixed value 400mW zener diodes 11-33V	£1.00

BI-PAK

Dept. R.C.8, P.O. Box 6, Ware, Herts
COMPONENTS SHOP: 18 BALDOCK
STREET, WARE, HERTS

TRADE COMPONENTS

JUST A FEW BARGAINS ARE LISTED - SEND STAMPEO ADDRESSED ENVELOPE FOR A QUOTE ON OTHER REQUIREMENTS. PAY A VISIT. OVER 90% OF STOCK BELOW QUANTITY WHOLESALE PRICE. ALL PRICES INCLUDE THE ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. MINIMUM ORDER GOODS VALUE £1.00.

Goods sent at customer's risk, unless sufficient payment for registration (1st class letter post) or compensation fee (parcel post) included.

VALVE BASES	
Printed circuit B9A-B7G	5p
Chassis B7-B7G	9p
Shrouded chassis B7G-B9A-B8A	10p
Octal chassis B12A tube	10p

Speaker 6" x 4" 5 ohm ideal for car radio 70p

TAG STRIP - 6 way 3p	
5 x 50pF or 2 x 220pF trimmers	20p
9 way 5p Single 1p	

BOXES - Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 32½p

Clear perspex sliding lid, 46 x 39 x 24mm 10p

ABS, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 48p; 80 x 150 x 50mm black 70p; 109 x 185 x 60mm black £1.10

ALUMINIUM

2½" x 5¼" x 1½"	45p	10" x 4½" x 3"	£1.02
4" x 4" x 1½"	45p	12" x 5" x 3"	£1.20

Pole	Way	Type	
4	2	Sub. Min. Slide	18p
6	2	Slide	20p
1	3	13 amp rotary	6p
2	1	2 Amp 250V A.C. rotary	20p
2	3	Miniature Slide	16p

S.P.S.T. 10 amp 240v. white rocker switch with neon. 1" square flush panel fitting 20p
S.P.S.T. dot 13 amp, oblong, push-fit, rocker 15p

Sidleen/AFA Very High Security barrel Key Switch. 2 tubular keys £1.50

AUDIO LEADS

3 pin din to open end. 1½ yd twin screened 35p
Phono to Phono plug, 6ft. 35p

COMPUTER & AUDIO BOARDS/ASSEMBLIES VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKES ETC.

3lb for 85p + £1.00 post and packing
7lb for £1.95 + £1.40 post and packing

1k horizontal preset with knob	3p	3" Tape Spools	3p
		1" Terry Clips	4p
		12 Volt Solenoid	30p

TV KNOB

Dark grey plastic for recessed shaft (quarter inch) with free shaft extension 5p

ENM Ltd. cased 7-digit counter 2½ x 1½ x 1½" approx. 12V d.c. (48 a.c.) or mains 75p

ZM1162A INDICATOR TUBE

0-9 Inline End View. Rectangular Envelope 170V 2.5M/A £1

REGULATED TAPE MOTOR

9v d.c. nominal approx 1½" diameter 60p

12v 8 amp Transformer £2.50 (p&p £1.00)

Ferric Chloride, Anhydrous mil. spec. 1lb bag 40p

Whiteley Stentorian 3 ohm constant impedance volume control way below trade at 80p
RS Yellow Wander Plug. Box of 12 25p
18 SWG multicore solder 2½p foot

Car type panel lock and key 40p
18 volt 4 amp charger, bridge rectifier 79p
GC10/4B £3.00

Aluminium Knobs for ½" shaft. Approx. ⅝" x ⅞" with indicator Pack of 5. 50p

RESISTORS
¼ - ½ watt 1p
1 watt 2p
Up to 15 watt wire wound 6p
1 or 2% five times price.
Cinch 8 way std 0.15 pitch edge connector 20p

Semiconductor Data Book 171 pages. Covers Japanese types 25A12 through to 2SD335. Type/connection/parameter details £1.50
No VAT

POTS

Log or Lin, single or dual, switched carbon or wire-wound, rotary or slider. All types 16p
1.5m Edgetype 3p

Skeleton Presets Slider, horizontal or vertical standard or submin. 5p

THERMISTORS

VA1008, VA1034, VA1039, VA1040, VA1055, VA1066, VA1082, VA1100 } 10p
VA1077, VA1005, } 15p

RELAYS

12 volt S.P.C.O octal mercury wetted high speed 40p
P.O. 30J0 type, 1,000 OHM coil, 4 pole c/o 40p
Mains or 12v d.p.c.o heavy duty octal 50p
3.5mm metal stereo plug 20p

JAP 4 gang min. sealed tuning condensers 20p

ELECTROLYTICS MFD/VOLT. Many others in stock 70- 200- 300- 450-
Up to 10V 25V 50V 75V 100V 250V 350V 500V MFD

10	4p	5p	6p	8p	10p	12p	16p	20p
25	4p	5p	6p	8p	10p	15p	18p	20p
50	4p	5p	6p	9p	13p	18p	25p	—
100	5p	6p	10p	12p	19p	20p	—	—
250	9p	10p	11p	17p	28p	—	85p	£1
500	10p	11p	17p	24p	45p	—	—	—
1000	13p	22p	40p	75p	—	£1.50	—	—
2000	23p	37p	45p	—	—	—	—	—

As total values are too numerous to list, use this price guide to work out your actual requirements

8/20, 10/20, 12/20 Tubular tantalum 20p each
16-32/275V. 100-100/150V. 100-100/275V 30p;
50-50/385V. 12,000/12V. 32-32-50/300V. 20-20-20/350V 60p; 700 mfd/200V £1.00; 100-100-100-150-150/320V £2.00.

RS 100-0-100 micro amp null indicator Approx. 2" x ¾" x ¾" £1.50

INDICATORS

Bulgin D676 red, takes M.E.S. bulb 30p
12 volt or Mains neon, red pushfit 18p
R.S. Scale Print, pressure transfer sheet 10p

CAPACITOR GUIDE - maximum 500V

Up to .01 ceramic 3p. Up to .01 poly 4p.
.013 up to .1 poly etc. 5p. .12 up to .68 poly etc. 6p. Silver mica up to 360pF 8p, then to 2,200pF 11p, then to .01 mfd 18p.
8p. .1/600; 12p. .01/1000, 8/20. .1/900, .22/900, .4/16. .25/250 AC (600vDC) 40p.
5/150, 10/150, 40/150.

Many others and high voltage in stock.

FORDYCE DELAY UNIT

240 volt A.C./D.C. Will hold relay, etc., for approx. 15 secs after power off. Ideal for alarm circuits, etc. £1

CONNECTOR STRIP

Belling Lee L1469, 4 way polythene. 6p each

1½ glass fuses 250 m/a or 3 amp (box of 12) 6p
Bulgin. 5mm Jack plug and switched socket (pair) 30p

Reed Switch 28mm. body length 5p

Aluminium circuit tape, ¼" x 36 yards—self adhesive. For window alarms, circuits, etc. 60p

MAINS DROPPERS

66+66+158 ohm, 66+66+137 ohm
17+14+6 ohm, 266+14+193 ohm 5p
285+575+148+35 ohm } 5p
25+35+97+59+30 ohm }

5½" x 2½" Speaker, ex-equipment 3 ohm 30p

2 Amp Suppression Choke 8p

3 x 2½ x 1½" } PAXOLINE 4p

4½ x 1½ x 1½" } 1p

PCV or metal clip on MES bulb Holder 4p

VALVE RETAINER CLIP, adjustable 2p

OUTPUT TRANSFORMERS

Sub-miniature Transistor Type 25p
Valve type. 40p

STYLII 15p

ER5SB/5MX/HC1/HC2/ER2. Compact X2/X/C/SX. Garrard

GCM21T/22T/GKM24T/GKS25/GP59. B.S.R. C1/FX1M/

ST3/CS80/TC8/OP and T, and many other sapphire types.

Send sample required with payment and s.a.e if in doubt.

KEY EDIT and display boards with up to 132* 12V bulbs, 38 d.t.l. and t.t.l. i.c.'s and other components. (*A few bulbs may be broken). £2.00 plus 75p p&p

Crouzet 30-minute timer-programmer, multi-variable contacts £6.00 plus £1.00 p&p

ACOS DUST JOCKEY record Automatic cleaner £1.00

Wood cased 8-12V buzzer £1.50 plus 80p p&p

McMurdo 8 or 12 or 18-way plug and socket, ex-equipment 36p

THE RADIO SHACK

161 ST. JOHNS HILL, BATTERSEA, LONDON S.W.11

Open 10 a.m. till 7 p.m. Tuesday to Saturday. VAT receipts on request.

Terms: Payment with order Telephone: 01-223 5016

SEMICONDUCTORS

Full spec. marked by Mullard, etc. Many other types in stock

AC128/176	8p	BCX32.36	12p	BFW10/11 F.E.T.	40p
ACY28	19p	BCY40	50p	BRW30	£1
AD149	40p	BCY70/1/2	12p	BRW57/58	17p
AF116	16p	BD113	50p	BFX12/29/30	20p
AF124/6/7	25p	BD115/6	31p	BFX84/88/89	17p
AF139	20p	BD131/2/3	35p	BFY50/51/52	13p
AF178/80/81	30p	BD135/6/7/9	30p	BFY90	50p
AF239	30p	BD140/142	30p	BR101	30p
ASY27/73	30p	BD201/2/3/4	80p	BR39/56	26p
BC107/8/9 + A/B/C	6p	BD232/4/5/8	49p	BSV64	30p
BC147/8/9 + A/B/C/S	6p	BDX77	£1	BSV79/80 F.E.T.s	80p
BC157/8/9 + A/B/C	6p	BD437	50p	BSV81 Mosfet	90p
BC178A/B, 179B	12p	BF115/167/173	15p	BSX20/21	14p
BC184C/LC	9p	BF178/9	20p	BSY40	27p
BC186/7	20p	BF180/1/2/3/4/5	15p	RSY95A	12p
BC213U/214B	10p	BF194/5/6/7	6p	CV7042 (OC41/44 ASY63)	5p
BC261B	8p	BF194A, 195C	6p	GET111	40p
BC327/8, 337/8	8p	BF200, 258, 324	20p	ON222	20p
BC547/8/8A/8C	10p	BF202/3	30p	TIP30/3055	45p
BC555/6/7/8/9	9p	BF336	27p	TIS88A F.E.T.	23p
		BFS28 Dual Mosfet	£1	ZTX300/341	7p

BRIDGE RECTIFIERS			
Amp	Volt		
1	1,600	BYX10	30p
1	140	OSM01-200	26p
1.4	42	BY164	40p
0.6	110	EC433	6p
5	400	Texas	90p

RECTIFIERS			
Amp	Volt		
IN4004/5/6	1	4/6/800	5p
IN4007/BYX94	1	1,250	5p
BY103	1	1,500	18p
SR100	1.5	100	7p
SR400	1.5	400	8p
REC53A	1.5	1,250	14p
LT102	2	30	10p
BYX38-300R	2.5	300	40p
BYX38-600	2.5	600	45p
BYX38-900	2.5	900	50p
BYX38-1200	2.5	1,200	55p
BYX48-300R	2.5	300	26p
BYX49-600	3	600	35p
BYX49-900	3	900	40p
BYX49-1200	3	1,200	52p
BYX48-300R	6	300	40p
BYX48-600	6	600	50p
BYX48-900	6	900	60p
BYX48-1200R	6	1,200	80p
BYX72-150R	10	150	35p
BYX72-300R	10	300	45p
BYX72-500R	10	500	55p
BYX42-300	10	300	30p
BYX42-600	10	600	65p
BYX42-900	10	900	80p
BYX42-1200	10	1,200	95p
BYX46-300R*	15	300	£1.00
BYX46-400R*	15	400	£1.50
BYX46-500R*	15	500	£1.75
BYX48-600*	15	600	£2.00
BYX20-200	25	200	60p
BYX52-300	40	300	£1.75
BYX52-1200	40	1,200	£2.50

*Avalanche type

Amp	Volt	TRIACS	
6	800	Plastic RCA	£1.20
25	900	BTX94-900	£4.00
25	1200	BTX94-1200	£6.00

RS 2mm Terminals
Blue & Black 5 for 40p

Chrome Car Radio fascia 15p
Rubber Car Radio gasket 5p

DLI Pal Delayline 50p

Relay socket
Take miniature 2PCO relay 10p

B9A valve can 5p

0-30, or 0-15, black pvc, 360° dial, silver digits, self adhesive, 4 1/2" dia. 10p

OPTO ELECTRONICS			
Diodes	Photo transistor		
TIL209 Red	12p	BPX29	80p
BPX40	50p	OC71	34p
BPX42	80p		
BPY10	80p		
(VOLIAC).			
BPY68	80p	BIG L.E.D. 0.2"	
BPY69		2v 50mA max.	
BPY77		ORANGE 14p	
		YELLOW 14p	
		RED 14p	

PHOTO SILICON CONTROLLED SWITCH BPX66 PNP 10 amp £1.00

3" red 7 segment L.E.D. 14 D.I.L. 0-9+D.P. display 1.9v 10mA segment, common anode 61p

Minitron 3" 3015F filament £1.10

CQY11B L.E.D. Infra red transmitter £1 One fifth of trade

Plastic Transistor or Diode Holder 1p

Transistor or Diode Pad 1p

Holders or pads 50pper100

Philips Iron Thermostat 15p

McMurdo PP108 8 way edge plug 10p

TO3 HEATSINK

Europlec HP1 TO3B individual 'curly' power transistor type. Ready drilled 12p

Tested unmarked, or marked ample lead ex new equipment

ACY17-20	8p	OC200-5	8p
ASZ20	8p	TIC44	24p
ASZ21	30p	2G240	£1
BC186	11p	2G302	5p
BCY30-34	8p	2G401	5p
BCY70/1/2	8p	2N711	25p
BY126/7	4p	2N2926	4p
HG1005	10p	2N598/9	6p
HG5009	3p	2N1091	8p
HG5079	3p	2N1302	8p
L78/9	3p	2N1907	£1
M3	10p	Germ. diode 1p	
OA81	3p	GET120 (AC128 in 1" sq. heat sink	15p
OA47	3p	GET872	12p
OA200-2	3p	2S3230	30p
OC23	20p		

KLAXON 12-24v 2-tone transistorized Alarm Sounder. Note, pitch and duration variable. Weatherproof alloy case. £10.00 p&p £1.30

2N2401	30p
2N2412	70p
2N2483	23p
2N2904/5/6/7/7A	15p
2N3053	14p
2N3055 R.C.A.	50p
2N3704	8p
2N3133	20p
2N4037	34p
2N5036 (Plastic 2N3055)	30p
2SA141/2/360	31p
2SB135/6/457	20p
40250 (2N3054)	30p

NEW B.V.A. VALVES

EB91	34p
ECL80	34p
PCC84	34p

TRANSFORMER

Ferromag C core. Screen-95-105-115-125-200-220-240v input: output 17v 1/2 A x 2 + 24-0-24v 1.04A + 20v 1mA. These current ratings can be safely exceeded by 50%. £3.50 + £1.00 p&p.

WOODS 240V A.C. Approx. 2,500 r.p.m. continuous rated 5 or 6in. FAN (ex-computer) £3.60 plus £1 p&p

Amp	Volt	THYRISTORS	
1	240	BTX18-200	30p
1	400	BTX18-300	35p
1	240	BTX30-200	30p
15	500	BT107	£1
6.5	500	BT101-500R	90p
6.5	500	BT109-500R	£1.00
20	600	BTW92-600RM	£3.00
15	800	BTX95-800R Pulse Modulated	£8.00
30	1000	28T10 (Less Nut)	£3.00

PAPER BLOCK CONDENSER

0.25MFD	800 volt	30p
1MFD	250 volt	15p
2MFD	250 volt	20p
4MFD	250 volt	20p

I.C. extraction and insertion tool 32p

CHASSIS SOCKETS

Car Aerial 9p, Coax 3p, 5 pin 180° 9p, 5 or 6 pin 240° din 6p, speaker din switched 5p, 3.5 mm switched 5p, stereo 1/2" jack enclosed 10p.

CRAZY OFFERS

2000 mfd.	50v	16p
2500 mfd.	40v	30p
8 mfd.	500v	6p
400 mfd.	16v	4p
.1 mfd.	350/500v	1p
1 mfd.	1500v	2p
2200 mfd.	25v	30p
1000 mfd.	200v	25p
10000 mfd.	15v	12p
1250 mfd.	35v	10p
6800 mfd.	10v	6p
32+32 mfd.	275v	8p
16+32 mfd.	350v	12p
8+8 mfd.	350v	8p
150 mfd.	35v	41p
100 mfd.	70v	41p
1 mfd. non-polar	350v	3p
680 mfd.	100v	10p
15 mfd.	160v	3p
4/00 pf. sub min	500v	1p
4700 mfd.	63v	70p
250 mfd.	300v	16p
4700 mfd.	40v	35p
25000 mfd.	25v	20p
1000 mfd.	63v	30p
1500 mfd.	70v	16p

Philips electronic engineer kits add on series E1004 75p each

G.E.C. 5% Hi-stab. capacitors .013, .056, .061, .066, .069, .075, .08, .089 2p each

OTHER DIODES	
1N916	6p
1N4148	2p
BA145	14p
Centercel	24p
BZV61/BA148	10p
BB103/110 Varicap	15p
BB113 Triple Varicap	37p
BA182	13p
OA5/7/10	15p
BZY88 Up to 33 volt	7p
BZX61 11 volt	15p
BR100 Diac.	15p

INTEGRATED CIRCUITS

TAA700	£2.00
TBA800	£1.00
741 8 pin d.i.l. op.	24p
SN76013N	£1.20
TAD100 AMRF	£1
CA3001 R.F. Amp	50p
CD4013 CMOS	36p
TAA300 1wt Amp	£1
TAA550 Y or G	22p
TAA263 Amp	65p
7400	10p
7402/4/10/20/30	14p
7414	56p
7438/74/86	24p
7483	69p
LM300, 2-20 volt	£1
74154	90p
TBA550Q	£1.50

ENAM. COPPER WIRE

SWG.	PER YD.
24	3p
26 to 42	2.5p

GARRARD

GCS23T Crystal Stereo Cartridge 66p

Mono (Stereo compatible), Ceramic or crystal 60p

HANDLES

Rigid light blue nylon 6 1/2" with secret fitting screws 5p

Belling Lee white plastic surface coax outlet box 20p

Miniature Axial Lead Ferrite Choke formers 2p

RS 10 Turn Pot 1% 250, 500 Ω, 1K, 50K £1

Copper coated board 10" x 9" approx 25p

TIE CLIPS

Nylon self locking 3 1/2" 2p

Geared Knob 8-1 ratio 1 1/2" diam, black 70p

KLIPPON 25A 440v TERMINAL BLOCKS professional leaf spring clamp, strip of 12 for 15p or twin with clip-over cover 7p

POSTAL ORDERS means quicker service — unless a fee is paid for special clearance it is 15 days from banking to ensure cheques are not returned 'unpaid'. Postal order poundage charge is offset by it now costing you 16p (reference Barclays Bank June 1977) bank charges on every cheque written out.

SMALL ORDERS. ENCLOSE SUITABLE STAMPED ADDRESSED ENVELOPE

LARGE ORDERS. ADD SUFFICIENT FOR POSTAGE, PACKING, INSURANCE, ETC.

TOTAL GOODS PLUS CARRIAGE, ADD V.A.T.

MAIL ORDER CUSTOMERS ONLY ADD 8% VAT-I PAY BALANCE ON 12 1/2% ITEMS

ALL ENQUIRIES, ETC., MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE


DIRECT SUPPLY SERVICE TO READERS . . .

TOWERS INTERNATIONAL TRANSISTOR SELECTOR

(NEW REVISED EDITION)


This is dead!

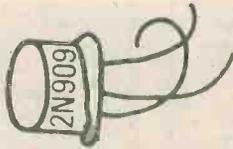If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. Its one of the most useful working books you will be offered this year. And probably the cheapest!



Japanese. And we think that they will solve 90% of your transistor enquiries.

Would this replace it?

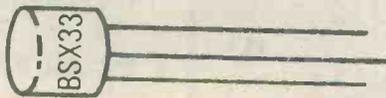

In it you will find a really international selection of 10,000 transistor types - British, Continental European, American and

Current and widely used obsolete types were carefully selected and arranged in order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Look at the entry for 2N909

TRANSISTOR NUMBER	PA LT	PACK-AGE	LEAD INFO	V _{CB} MAX	V _{CE} MAX	V _{EB} MAX	I _C MAX	T _J MAX	P _{TOT}	F _T MIN	C _{OB} MAX	H _{FE}	H _{FE} BIAS	USE	MFR	EURO EQVT	USA EQVT	ISS
2N909	NS	TO18	LO1	60V	30V	5V	200MA	175°C	500mW	50M	25P	110MN	50MA	AMG	SGI	BSX 33	2N731	0

This is what you will learn from it

TYPE NO	POL & MAT	OUTLINE	LEAD IDENT	V _{CB} MAX	V _{CE} MAX	V _{EB} MAX	I _C MAX	T _J MAX	P _{TOT}	F _T MIN	C _{OB} MAX	H _{FE}	H _{FE} BIAS	USE	MFR	EURO EQVT	USA EQVT	ISS
EXAMPLE 1 2N909	NS	TO18	LO1	60V	30V	5V	200 MA	175°C	500mW	50M	25P	110 MN	50 MA	AMG	SGI	BSX 33	2N 731	0

NUMERO ALPHABETIC LISTING

N NPN
P PNP
G GERMANIUM
S SILICON

REFER TO CASE OUTLINES APPENDIX C

REFER TO LEAD DETAILS APPENDIX B

MAXIMUM PERMISSIBLE COLLECTOR BASE VOLTAGE WITH EMITTER OPEN CIRCUIT

MAXIMUM PERMISSIBLE COLLECTOR EMITTER VOLTAGE WITH BASE OPEN CIRCUIT

MAXIMUM PERMISSIBLE EMITTER BASE VOLTAGE WITH COLLECTOR OPEN CIRCUIT

MAXIMUM PERMISSIBLE COLLECTOR CURRENT

MAXIMUM PERMISSIBLE JUNCTION TEMPERATURE

MAXIMUM PERMISSIBLE DEVICE DISSIPATION F IN FREE AIR AT 25°C C WITH CASE SURFACE HELD AT 25°C H IN FREE AIR AT 25°C WITH METAL HEAT SINK ATTACHED TO DEVICE

MINIMUM FREQUENCY CUT OFF F_c INDICATED IN K KILOHERTZ M MEGAHERTZ G GIGAHERTZ

F_c FREQUENCY AT WHICH COMMON EMITTER CURRENT GAIN DROPS TO UNITY TYPICAL F_c CAN BE TAKEN AS ROUGHLY TWICE F_c

FOOTNOTE

SUGGESTED EIA-JEDEC 2N STANDARD POSSIBLE SUBSTITUTE

SUGGESTED PROELECTRON STANDARD POSSIBLE SUBSTITUTE

CODE INDICATION POSSIBLE SUPPLIER OF DEVICE - SEE SUPPLIER APPENDIX F

CODE INDICATION OF APPLICATION USAGE - SEE APPENDIX A

BIAS CURRENT AT WHICH CURRENT GAIN H_{FE} IS CHARACTERISED

CURRENT GAIN NORMALLY DC (BUT SOMETIMES RELATED AC GAIN) AT I_C BIAS SPECIFIED - WHERE I_C (IN MN) ONLY IS SPECIFIED TYPICAL I_C P CAN BE TAKEN AS TWICE MIN AND VICEVERSA

MAXIMUM COLLECTOR CAPACITANCE (TYPICAL USUALLY 1/2 TO 1/3 MAX) - NORMALLY EMITTER OPEN-CIRCUIT AND INDICATED BY P PICOFARAD OR N NANOFARAD FOR HF DEVICES C_{in} IS GIVEN AND PICOFARADS THEN INDICATED BY R INSTEAD OF P

Tower's International Transistor Selector

by **T. D. TOWERS**
MBE, MA, BSc, C Eng, MIERE

£5.00

inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME


ADDRESS

(Block capitals)

ambit INTERNATIONAL Trade Mark

The Wireless Specialists for components & modules.

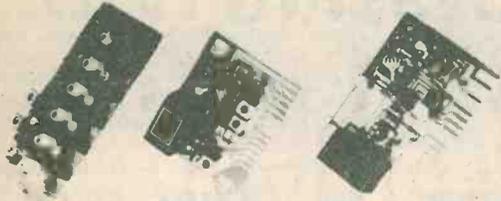EF5800, 7030 & 91196 - .9uV/30dB S/N., 0.2% THD
Our top three FM tuner modules. (EF5800 shown with can off).



From left to right, the EF5800 6 circuit varicap FM tunerhead with the 7030 linear phase IF and the 91196 PLL stereo decoder with integral 55kHz 'birdy' filter. The system provides afc muting, meter drives, agc, auto stereo switch, & a specification that exceeds broadcast requirements. Now available with a new EF5801 tunerhead, with FET buffered oscillator output for synthesiser/frequency readout facilities.

EF5801...£17.45; EF5800...£14.00; 7030...£10.95; 91196...£12.99

Complete FM tuner kits/systems (Carriage £3 extra.)

The Mark 8 Signalmaster - by Larsholt Electronics

This tuner is based on the popular 7252 tuner set, and provides an incomparable combination of style and performance that can be built by even the relatively inexperienced constructor. Complete kit...£85.00; matching 25+25W amplifier...£79.00.

International Mark 2 Tuner kits:

Complete tuner kit, based around the 7253 tuner set, £65.00. Or just the chassis, cabinet, heavy aluminium front panel — for your own choice of modules— see our new info. leaflet on the International Tuner. (SAE please)

NEW NEW NEW NEW NEW NEW NEW NEW BIONIC FERRET METAL LOCATOR

Ambit has designed a new approach to cost effective sensitive metal locators, and now we proudly present the first of the family of 'Bionic Ferrets'. Details OA, but we can say it will detect a 10p piece at 8-10 inches. Coupled with low power consumption and many innovations, this is the first radically advanced detector that can be made from a kit. £37.99

Radio module selection: (Prices for kits in our catalogue & PL)

EF5800	Ambit 6 stage varicap 88-108MHz tunerhead	£14.00
EF5600	TOKO 5 stage varicap	£12.95
EC3302	TOKO 3 stage varicap	£7.50
7020	Dual ceramic filter FM IF system module	£6.95
92310	MPX decoder, with stereo filter and preamp	£6.95
93090	MPX decoder with CA3090AQ + filter stage	£7.35
91197	MW/LW varicap AM tuner module	£11.35
771	New 'Off-Air' UHF varicap TV sound tuner module with mute, AFC, dual conversion, PSU	£27.00
9014	MW/LW/Stereo FM tuner chassis, Mech. tuned	£26.00

Components: ICs, coils, filters, trimmers diode law pots etc.

HA1137W/3089E FM IF	1.94	TOKO AM IFTs:	
TBA120 FM IF and demod	0.75	455/470kHz types	0.30
MC1350 FM IF preamp	0.97	10.7MHz types	0.33
SN76660N FM IF and det.	0.75	(10mm square, with int. cap.)	
MC1310/4400 PLL MPX	2.20	455kHz Mechanical filters	
CA3090AQ PLL MPX	3.75	4 or 7 kHz bandwidths	1.95
HA1196 PLL MPX	4.20	455kHz ceramic IF filters	
uA720 AM radio system	1.40	6 or 8 kHz bandwidth CFT	0.55
TBA651 AM radio system	1.81	SFD455 (Murata)	0.75
HA1197 AM radio system	1.40	455kHz dual ceramic CFX	1.80
LM1496 balanced mixer	1.25	10.7MHz filters for WBFM:	
11C90 600MHz decade ctr	14.00	3132A 6 pole lin phase	2.25
LM380N 2-W Audio	1.00	3125N 4 pole lin phase	1.30
LM381N audio preamp st.	1.81	CFS ceramic filters	0.50
TDA2020 20W audio amp	2.99	Pilot tone (MPX) filters:	
TCA940 10W audio amp	1.80	BLR3107N stereo	1.90
NE723 voltage reg IC	0.80*	BLR2007N	1.95
TDA1412 12v 600mA reg	0.95*	BLR3152/mono	0.97
78M20 20v 500mA	1.20*	BLR3172N tape bias trap, with	0.50
TAA550B varicap regulator	0.50	85 or 100kHz pole	0.97
NE560/1/2B PLL ICs	3.50*	various chokes etc. see price list	
ICL8038C function gen	4.50*		

22turn 100k diode law trim pots, with integral knob 40p
270° rotary 100k diode law tuning pot 32p
Also...meters for tuners, AM tuning varicaps, MOSFETs etc....

—post/packing 22p per order - except where indicated—

General: All prices shown here exclude VAT, which is generally 12½%. (Except where marked*). The latest price leaflet is available FOC with an SAE. Please send a (large) SAE with any enquiries. Full catalogue still 40p.

37 High Street, Brentwood, Essex. CM14 4RH.
TELEPHONE (0277) 216029 - after 3pm if possible please.

Double Economy Deal for Car Drivers

IT'S THE STIRLING SOUND


Super Spark MK 5

CAPACITY DISCHARGE IGNITION UNIT

DIRECT FROM THE MAKERS!

- LOWER PRICES AND REDUCES RUNNING COSTS
- MADE AND SOLD DIRECT BY OUR OWN FACTORY
- ADAPTABLE TO + or — EARTH AS REQUIRED
- REV. LIMITING CONTROL
- INSTANT REVERT SWITCH TO NORMAL IGNITION
- ON-OFF SWITCH TO IMMOBILIZE ENGINE
- EASY TO INSTALL
- FULLY GUARANTEED

Nothing extra to buy!

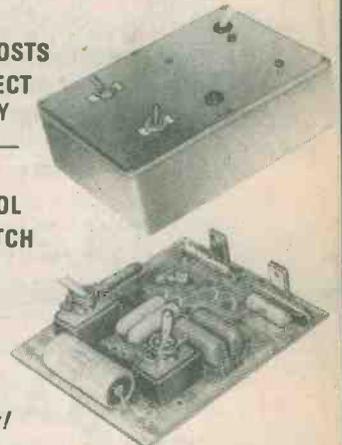

With Super Spark Mk. 5 you get all the well known advantages of electronic ignition for your car — year-round easier starting, fuel economy, better working life from the engine. PLUS essential features which come as extras in other makes. Built in our own factory in Essex from heavy duty transformer and components on improved fibre glass circuit board, now in heavy gauge aluminium case 6½ in. x 4½ in. x 2 in. (172 x 124 x 50 mm) with neon indicator and colour coded leads (approx. 27 in. — 68cm) ready to connect to your car.

OVER 14,000 SUPER SPARK UNITS HAVE ALREADY BEEN SOLD.
FOR DELIVERY BY RETURN S.A.E. BRINGS LEAFLET.

READY BUILT AND GUARANTEED INC. VAT


£12.75

POST PAID U.K.

COMPLETE KIT OF GUARANTEED PARTS INC. VAT

£10.50

POST PAID U.K.

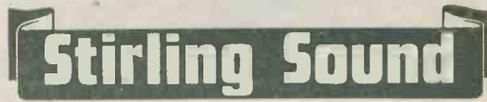

Factory and Offices:

37 VANGUARD WAY, SHOEBURYNNESS, ESSEX

Telephone: (03708) 5543

Shop: 220-224 WEST ROAD, WESTCLIFF-ON-SEA, ESSEX SS09DF

STIRLING SOUND, 37 VANGUARD WAY, SHOEBURYNNESS, ESSEX

Please send Super Spark Mk.5 Built @£12.75.....

Kit @ £10.50

My car is (year)..... (Pos. Earth) (Neg. Earth)

NAME

ADDRESS

(Block letters please)

RC877



UNDERSTAND DATA PROCESSING

DATA PROCESSING, by Oliver & Chapman, is now in its Third Edition — first published 1972.

200 pages 9 $\frac{3}{4}$ " x 6 $\frac{3}{4}$ " **PRICE £2.50**
Inclusive of postage

The primary aim of this outstanding manual is to provide a simplified approach to the understanding of data processing — (previous knowledge of the subject is not necessary).

The 40 chapters and appendices cover the following topics: Introduction to Data Processing; Organisation and Methods; Conventional Methods; Introduction to EDP and Computers; Hardware; Computer Files; Data Collection and Control; Programming and Software; Flowcharts and Decision Tables; Systems Analysis; Applications; Management of EDP, etc.

Available from:

D.P. PUBLICATIONS
 4 AMPORT CLOSE, WINCHESTER, HANTS SO22 6LP

LATEST BOUND VOLUME No. 29



of
**"Radio & Electronics
 Constructor"**

FOR YOUR LIBRARY

Comprising
 776 pages
 inc. index

AUGUST 1975
 to JULY 1976

PRICE £3.10 P&P 90p

BOUND VOLUME No. 27 (August 1973 to July 1974)
BOUND VOLUME No. 28 (August 1974 to July 1975)

PRICE £2.40 p. & p. 90p
 PRICE £2.75 p. & p. 90p

Limited number of these volumes still available

We regret all other volumes are now completely sold out.
 Available only from

DATA PUBLICATIONS LTD., 57 MAIDA VALE, LONDON, W9 1SN

THE MODERN BOOK CO

RADIO COMMUNICATION HANDBOOK by R.S.G.B. Vol 1 Price: £9.00 Vol 2 Price: £8.00

MAKE THE MOST OF YOUR
POCKET CALCULATOR

by L. Jansson PRICE: 95p

THE POCKET CALCULATOR GAME
BOOK

by E. Schlossberg PRICE: £1.10

ADVANCED APPLICATIONS FOR
POCKET CALCULATORS

by J. Gilbert PRICE: £3.90

INTRODUCTION TO COMPUTERS

by K. London PRICE: £1.35

BUILD YOUR OWN WORKING ROBOT

by D. L. Heiserman PRICE: £3.60

INTRODUCTION TO MICRO-
PROCESSORS

by D. Aspinall PRICE: £5.30

MICROPROCESSORS/MICRO-
PROGRAMMING HANDBOOK

by B. Ward PRICE: £4.00

UNDERSTANDING MICRO-
PROCESSORS

by Motorola PRICE: £3.75

T.V. ENGINEERS' POCKET BOOK

by P. J. McGoldrick PRICE: £5.10

COLOUR T.V. PICTURE FAULTS

by K. J. Bohlman PRICE: £2.80

COLOUR T.V. WITH PART REF. TO
THE PAL SYSTEM

by G. N. Patchett PRICE: £5.60

THE CATHODE-RAY
OSCILLOSCOPE & ITS USE

by Patchett PRICE: £3.90

THE OSCILLOSCOPE IN USE

by I.R. Sinclair PRICE: £2.80

SERVICING WITH THE
OSCILLOSCOPE

by G. J. King PRICE: £4.95

BASIC ELECTRONICS I-V

Schools Council PRICE: £7.60

BEGINNER'S GUIDE TO
ELECTRONICS

by T. L. Squires PRICE: £2.60

OP-AMP CIRCUIT DESIGN &
APPLICATIONS

by J. Carr PRICE: £3.90

99 ELECTRONIC PROJECTS

by H. Friedman PRICE: £2.65

110 OPERATIONAL AMPLIFIER
PROJECTS FOR THE HOME
CONSTRUCTOR

by R. M. Marston PRICE: £2.80

T T L COOKBOOK

by D. Lancaster PRICE: £8.60

ELECTRONIC CLOCKS & WATCHES

by M. Robbins PRICE: £5.00

BEGINNER'S GUIDE TO AUDIO

by I. R. Sinclair PRICE: £3.00

IMPROVING YOUR HI FI

by J. Earl PRICE: £3.65

CASSETTE TAPE RECORDERS

by J. Earl PRICE: £5.20

RADIO CONSTRUCTION FOR
AMATEURS

by R. H. Warring PRICE: £2.75

STEREO F.M. RADIO HANDBOOK

by P. Harvey PRICE: £2.90

RADIO SERVICING POCKET BOOK

by V. Capel PRICE: £3.25

ILLUST. TEACH YOURSELF RADIO

by D. Gibson PRICE: £1.90

FOUNDATIONS OF WIRELESS &
ELECTRONICS

by M. G. Scroggie PRICE: £4.40

THE PRACTICAL AERIAL HANDBOOK

by G. J. King PRICE: £8.20

RADIO & AUDIO SERVICING
HANDBOOK

by G. J. King £5.45

WORLD RADIO TV HANDBOOK

by J. M. Frost PRICE: £5.70

THE RADIO AMATEUR'S
HANDBOOK 1977


by A.R.R.L. PRICE: £8.70

PRICES INCLUDE POSTAGE

We have the Finest Selection of English and American Radio Books in the Country

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone 01-723 4185

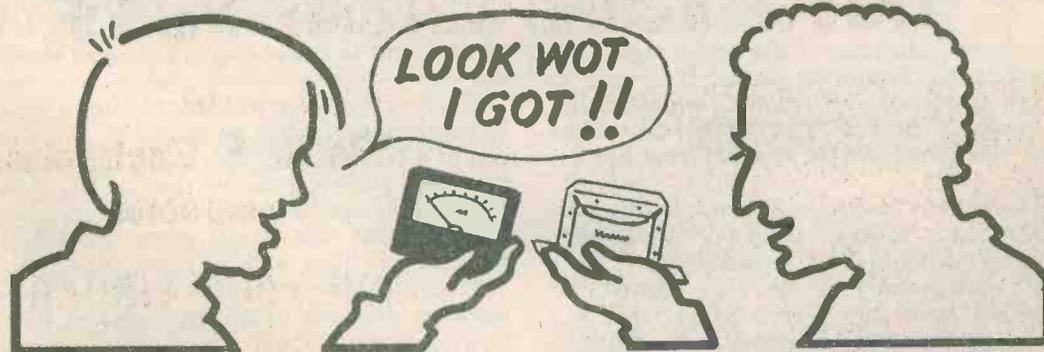

I bought this beautiful little milliamp-meter through the special Bargain List that Home Radio sent me when I bought a copy of their famous Components Catalogue. I reckon I saved a good £1.50 on this one item alone—more than the catalogue itself cost. If I'm not mistaken, you got

that natty transformer the same way, so no doubt you're as familiar as I am with the scores of bargains they're offering.

But have you noticed that there are quite a few bargains in the main catalogue itself? That Resistor Pack SP22 for instance—400 preferred value $\frac{1}{4}$ watt 5% resistors for only £6, beautifully arranged for easy selection. If that's not a bargain, what is?

For those readers who have not yet caught on to the advantages of dealing with Home Radio let us explain. Purchase a Home Radio Catalogue, £1.40 including postage and packing, or £1 over the counter. It has over 200 pages, listing about 5,000 items, nearly 2,000 of them illustrated.

With every catalogue Home Radio give you free an up-to-date Bargain List. Why wait? Send the coupon with a cheque or P.O. for £1.40 to Home Radio Components, 240 London Road, Mitcham, Surrey.

Please write your Name and Address in block capitals

NAME

ADDRESS



POST THIS COUPON
with cheque
or p.o. for
£1.40

HOME RADIO (Components) LTD., Dept. RC
234-240 London Road, Mitcham, Surrey CR4 3HD

Regd No 912966 London

HOME RADIO (Components) LTD. Dept. RC, 234-240 London Road, Mitcham, CR4 3HD. Phone: 01-648 8422

L.E.D. VU METER

By A. P. Roberts

THIS INGENIOUS DESIGN INCORPORATES TWO QUAD NORTON AMPLIFIER I.C.'S TO CONTROL SEVEN L.E.D.'S.

The latter give comparative signal level indications ranging from -18dB to $+3\text{dB}$, the 0dB level being pre-set to suit the associated audio equipment.

Probably most readers will be familiar with a device known as a peak level indicator, and these are now fitted to a substantial proportion of the cassette decks and recorders that are currently available. The purpose of the indicator is to provide a visual indication if the audio signal exceeds a certain amplitude on peaks. It is used to augment an ordinary VU meter, which is an average reading device and therefore lacks reliability when rather spiky waveforms are involved.

The device which forms the subject of this article is really just a form of peak level indicator. However, whereas most peak level indicators have only one, or occasionally two indicator lamps, the unit described here has seven. Thus it is not necessary to use it in conjunction with an ordinary VU meter; it can be used to replace it. Furthermore, it provides more reliable results since it is a peak reading rather than an average reading indicator. Peak reading VU meters are the type that are employed in professional recording establishments.

Of course, the unit is not only suitable for tape recording applications, and it is increasingly common for some form of volume unit indicator to be fitted to other types of audio equipment, such as amplifiers or mixers.

QUAD NORTON AMPLIFIERS

Only two active devices are employed in the circuit, and these are both quad Norton amplifiers. The prototype has been constructed as a completely self-contained unit which is powered from an internal 9 volt battery, but in many cases it would be possible for an experienced constructor to build the

unit into the main equipment. The seven indicator lamps light up at the following levels: -18dB , -12dB , -9dB , -6dB , -3dB , 0dB and $+3\text{dB}$. The sensitivity of the unit is pre-set, and when it is at maximum only about 350 to 400mV r.m.s. is required at the input to cause all the indicator lamps to turn on.

Each of the seven indicator lamps appears in the basic circuit which is given in Fig. 1. Here the output of a Norton amplifier is fed to a light-emitting diode via current limiting resistor R_L . The Norton amplifier is used as a form of electronic switch, and the indicator will be off when the output of the amplifier is high, and on when it is low.

Which of these states the output of the amplifier assumes depends upon the levels of the currents flowing into its inputs. Like a standard operational amplifier, a Norton amplifier has both inverting


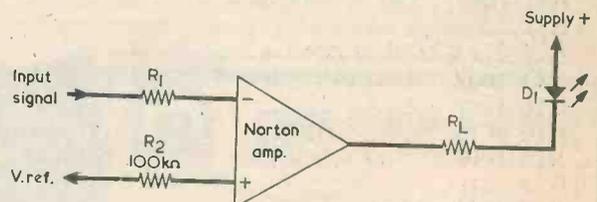


Fig. 1. The basic switching circuit which operates each l.e.d. in the VU meter. Sensitivity is controlled by the value of R_1 .

TER

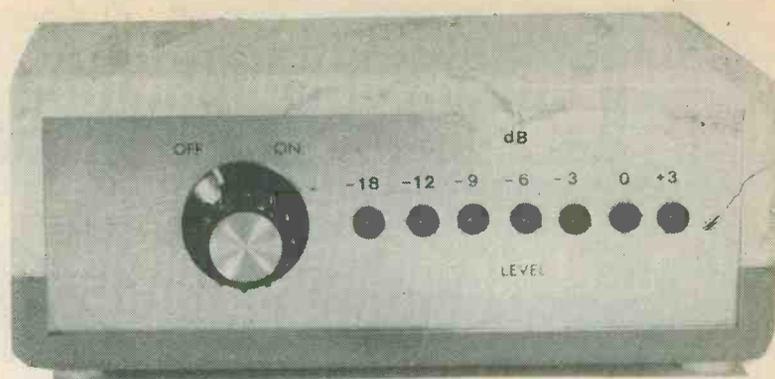

Housed in a 2-tone plastic case with an anodised aluminium front panel, the l.e.d. VU meter has a striking presentation

(-) and non-inverting (+) inputs. If the current which flows into the inverting input is significantly higher than the one which flows into the non-inverting input, then the output goes low. If, on the other hand, the current flow into the inverting input is less than the flow into the non-inverting one, then the output takes up the high state.

The non-inverting input is taken to a stabilised reference voltage via a $100\text{k}\Omega$ resistor, and the input signal is coupled to the inverting input via a resistor whose value determines the sensitivity. If, for example, this resistor has a value of $100\text{k}\Omega$ the indicator lamp will not come on until positive input signal peaks exceed the reference voltage. The

current flow in R1 will then exceed that in R2, since the voltage across R1 will be higher than that across R2 for the duration when the input signal exceeds the reference voltage. The output of the amplifier thus goes low, and supplies current to the l.e.d. indicator lamp.

If the value of R1 were reduced to $50\text{k}\Omega$ the sensitivity of the circuit would be doubled, as now only half the previous signal voltage would be required across R1 in order to produce the same level of current flow. Increasing R1 to $200\text{k}\Omega$ would obviously halve the sensitivity. The sensitivity of the circuit can thus be varied over a wide range by choosing a suitable value for R1.

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated. See text for close tolerance resistors).

- R1 $120\text{k}\Omega$
- R2 $1.2\text{M}\Omega$
- R3 $150\text{k}\Omega$ close tolerance
- R4 $100\text{k}\Omega$ close tolerance
- R5 $1\text{k}\Omega$
- R6 $110\text{k}\Omega$ close tolerance
- R7 $100\text{k}\Omega$ close tolerance
- R8 $1\text{k}\Omega$
- R9 $100\text{k}\Omega$ close tolerance
- R10 $75\text{k}\Omega$ close tolerance
- R11 $1\text{k}\Omega$
- R12 $2.2\text{k}\Omega$
- R13 $51\text{k}\Omega$ close tolerance
- R14 $100\text{k}\Omega$ close tolerance
- R15 $1\text{k}\Omega$
- R16 $36\text{k}\Omega$ close tolerance
- R17 $100\text{k}\Omega$ close tolerance
- R18 $1\text{k}\Omega$
- R19 $100\text{k}\Omega$ close tolerance
- R20 $27\text{k}\Omega$ close tolerance
- R21 $13\text{k}\Omega$ close tolerance
- R22 $1\text{k}\Omega$
- R23 $100\text{k}\Omega$ close tolerance
- R24 $1\text{k}\Omega$
- VR1 $100\text{k}\Omega$ pre-set potentiometer, standard skeleton, horizontal

COMPONENTS

Capacitors

- C1 $0.1\mu\text{F}$ type C280 (Mullard)
- C2 $100\mu\text{F}$ electrolytic, 10 V. Wkg.

Semiconductors

- IC1 CA3401E or LM3900N
- IC2 CA3401E or LM3900N
- D1 small l.e.d., red, with mounting bush
- D2 small l.e.d., yellow, with mounting bush
- D3-D7 small l.e.d., green, with mounting bush
- D8 BZY88C3V9

Switch

- S1 s.p.s.t., rotary

Socket

- SK1 3.5mm. jack socket

Miscellaneous

- Verobox type 75-1238D
- Veroboard, 0.1 in. matrix
- 2 i.c. sockets, 14 way (optional)
- Control knob
- 9 volt battery type PP6 (Ever Ready)
- Battery connector.

Looking into the case from the rear. A PP3 battery appears in this photograph, but a PP6 is recommended for general usage

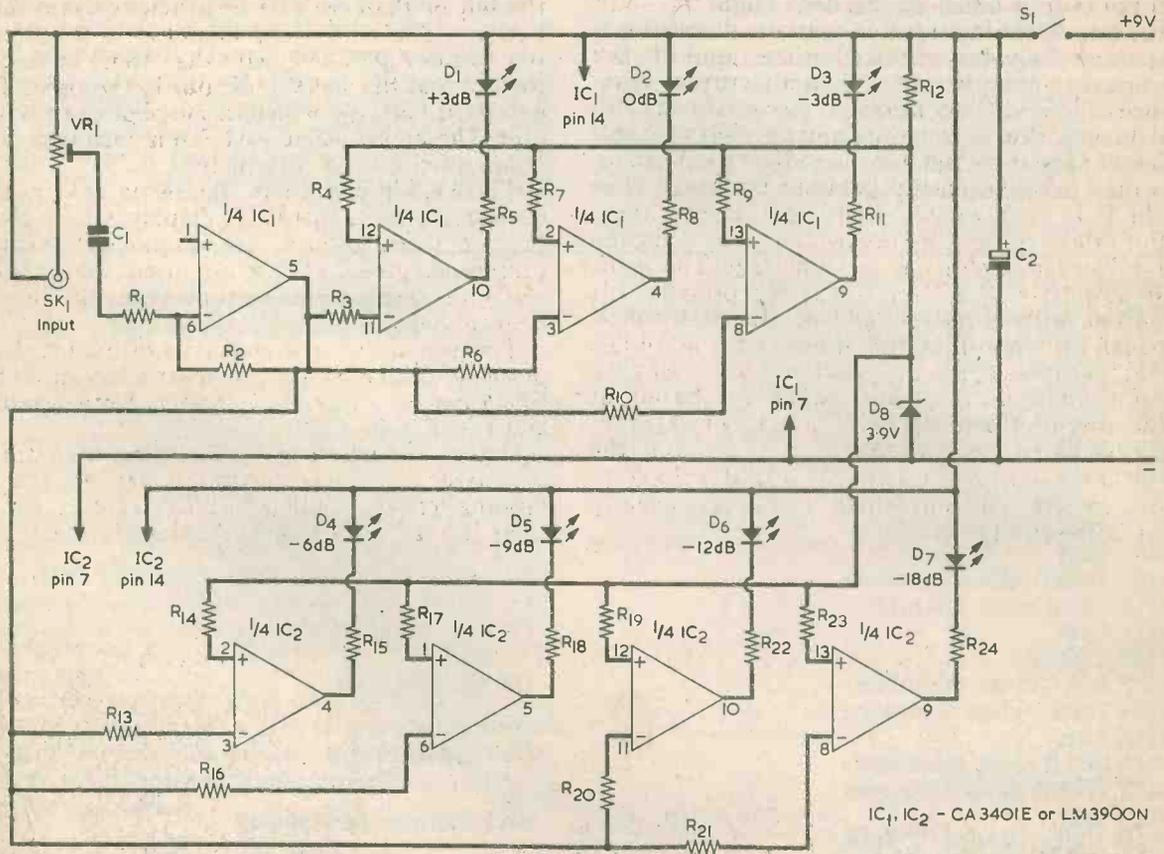
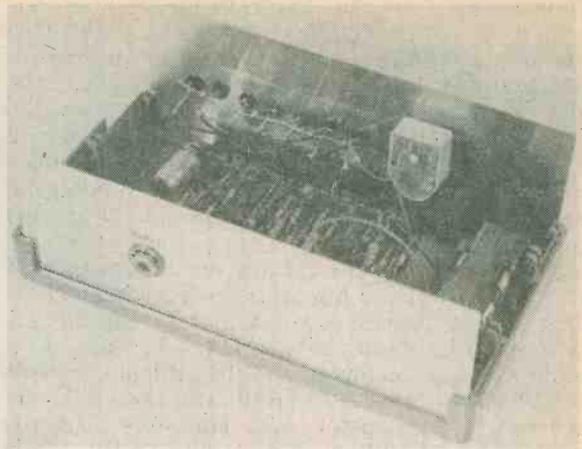


Fig. 2. The complete circuit of the 1.e.d. VU meter. The 1.e.d.'s light up at the decibel levels shown alongside them

PRACTICAL CIRCUIT

The complete circuit diagram of the l.e.d. VU meter is shown in Fig. 2, and it will be seen that seven of the Norton amplifiers are used in the configuration just described. They are all fed from the same reference voltage source, which is provided by a simple zener circuit incorporating R12 and D8. It is essential that a stabilized voltage be used here, since any changes in the reference potential result in similar changes in the sensitivity of each indicator.

All the inverting inputs are fed from pin 5 of IC1, and the series input resistors have been given values which provide approximately the correct relationship between the various indicators. As a simple example of this, the -3dB indicator circuit has a 75k Ω series resistor (R10) and the +3dB circuit has a 150k Ω resistor (R3). Therefore the -3dB indicator has double the sensitivity of the +3dB one, and the correct 6dB difference in sensitivity is obtained.

In some cases the required resistor values do not coincide with preferred values, and so the nearest value in the E-24 series is used. This provides perfectly adequate accuracy in practice. It is necessary to use close tolerance components for both sets of input resistors, and 5% should be regarded as the widest acceptable tolerance. Ideally, 2% or, better, 1% types should be employed.

One problem with the very simple indicator circuits is that they are not very sensitive, with a peak input of over 5 volts being needed to light the +3dB indicator. Another and more serious drawback is that about 0.6 volt is required at the input of each Norton amplifier before any input current commences to flow. This makes it necessary to both add an amplifier at the input and provide a 0.6 volt quiescent input voltage for the indicators. Without this bias the relationship between the sensitivities of the indicators would be seriously inaccurate.

Both these difficulties are overcome by using the eighth Norton amplifier as an input stage. This is the first amplifier of IC1. R1 and R2 provide this amplifier with a voltage gain of about 10 times. Normally the non-inverting input of the amplifier would be connected to the positive supply rail via a resistor having a value which would bias the output of the amplifier to about half the supply rail potential. However, by omitting this resistor the amplifier assumes a quiescent output voltage of approximately 0.6 volt, which is of course exactly what is required.

C1 provides d.c. blocking at the input, and VR1 is a pre-set sensitivity control. The input impedance of the circuit is quite high, and varies from approximately 55k Ω at maximum sensitivity to about 100k Ω at minimum sensitivity. S1 is the on-off switch, and C2 is the only supply decoupling component which is required.

The circuit has a quiescent current consumption of about 12mA, and this rises to some 30mA when all the l.e.d. indicators are illuminated. Bearing in mind that each l.e.d. has a current limiting series resistor of 1k Ω , it might at first appear that the 30mA current consumption figure is surprisingly low. It has to be remembered, however, that the l.e.d.'s are only illuminated when positive signal half-cycles are applied to the indicator circuits, with the result that they are alight for only half or less than half of the time. If desired, the brightness of the l.e.d.'s can be increased by reducing the value of the 1k Ω series resistors to about 470 Ω , but this will considerably increase the current consumption of the unit.



CONSTRUCTION

The prototype l.e.d. VU meter is housed in a Verobox which has outside dimensions of 154 by 60 by 85mm., but any case of a similar size should be satisfactory. The battery fits inside the case at the extreme left hand side. S1 is mounted to the left on the front panel; it must not be mounted too far to the left or there will be insufficient space for the battery. The l.e.d.'s are mounted in a horizontal row to the right of S1, with the -18dB indicator to the left and the +3dB indicator to the right. These details are clearly shown in the photographs of the unit. The input socket is a 3.5mm. jack type, and it is mounted on the rear panel.

The l.e.d.'s can all be the same colour, but a clearer and more attractive display will be given if two or three colours are employed. With the prototype, green l.e.d.'s are used for -18dB to -3dB, the 0dB l.e.d. is a yellow type and the +3dB l.e.d. is red.

The remaining components are mounted on a piece of Veroboard of 0.1 in. matrix having 37 holes by 24 copper strips. Full details of this board are given in Fig. 3.

Cut out the board with a hacksaw, then drill the two mounting holes clearance size for the self-tapping screws supplied with the Verobox (or 6BA clear if a different case is employed). Next, make

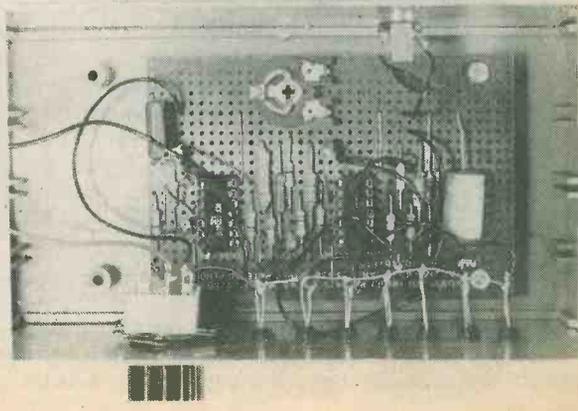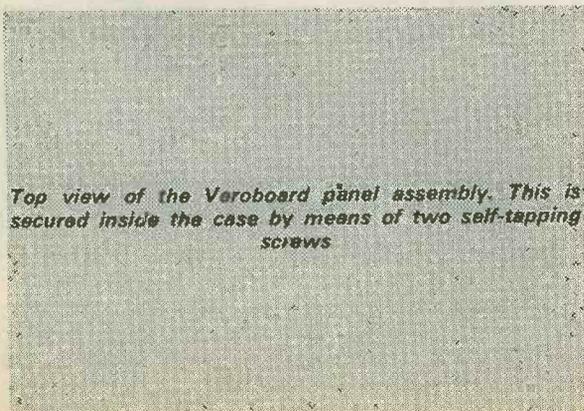

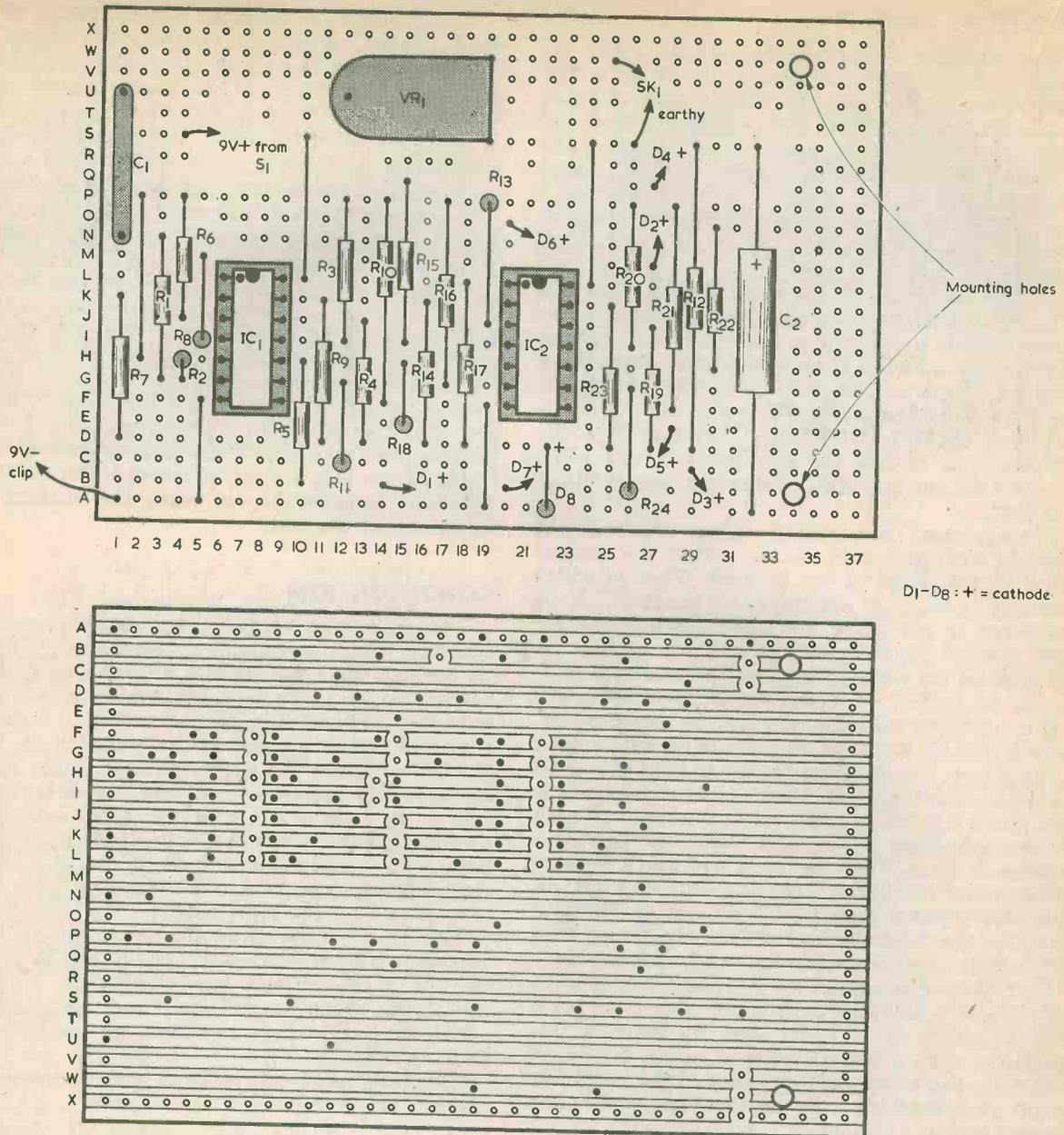


Fig. 3. Nearly all the components are assembled on a Veroboard panel. The component and copper sides are shown here

the breaks in the copper strips as shown in the diagram. The components and link wires are then soldered into circuit. The author used two 14 way integrated circuit holders, these being soldered to the Veroboard and the i.c.'s plugged in afterwards. However, the i.c. holders can be dispensed with and the integrated circuits soldered directly to the board if this is preferred. With some potentiometers, the slider tag of VR1 may need to be fitted to a different hole along strip U than is shown in the diagram.

The Veroboard is wired up to the other components, by means of thin stranded p.v.c. covered wire, before it is mounted in the case. It is secured to the two mounting pillars on the right hand side which are moulded into the case, using two of the self-tapping screws.

There are several connections which are not shown in Fig. 3. The positive battery lead connects to the unused tag of S1. The anodes of the l.e.d.'s are all wired together and are then connected to the tag of S1 which connects to the board. The wiring at S1 should then conform with the circuit diagram of Fig. 2.

ADJUSTMENT

Only one adjustment needs to be made to the finished unit before it is ready for use, and that is to set the correct sensitivity by means of VR1. The prototype unit is used to monitor the output from a mixer which has a nominal output level of 500mV. In order to set up the l.e.d. VU meter a 500mV r.m.s. signal (at a frequency of 1kHz) was fed to SK1. VR1 was then adjusted to a point at which


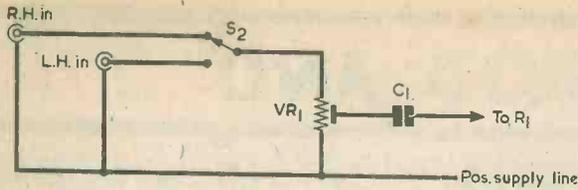


Fig. 4. A simple input switching circuit can be added for monitoring stereo signals

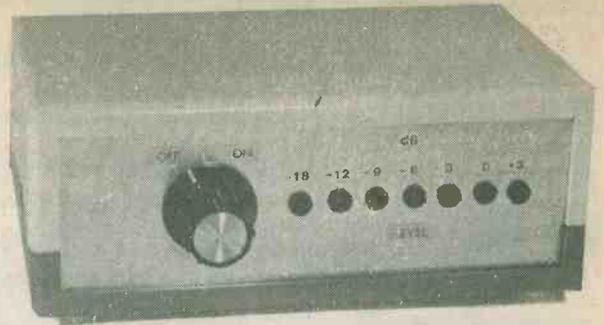

Another view of the VU meter. The legends on the front panel are all taken from Panel Signs, Set No. 4

the 0dB l.e.d. was just noticeably illuminated.

The same basic method of calibration can be employed whatever type of equipment the unit is used in conjunction with. The audio level of the equipment is adjusted to that which it is desired should correspond to an indication of 0dB, and VR1 set up accordingly.

As described here the unit is only suitable for


monitoring mono equipment. For stereo operation two circuits can be used, one monitoring each channel. Alternatively, switching could be added at the input so that the unit could be switched to monitor one or other of the channels. All that are required are an s.p.d.t. switch and an extra socket connected in the manner shown in Fig. 4. There is plenty of space for these on the rear panel. ■

Ultraviolet Depolymerization

By Michael Lorant

Dr. Donald E. Bolon, electronic research scientist of General Electric Research and Development Center, Schenectady, New York State, has developed a unique process called "Ultraviolet Depolymerization" which uses intense ultraviolet light to speed and simplify the fabrication of semiconductor wafers.

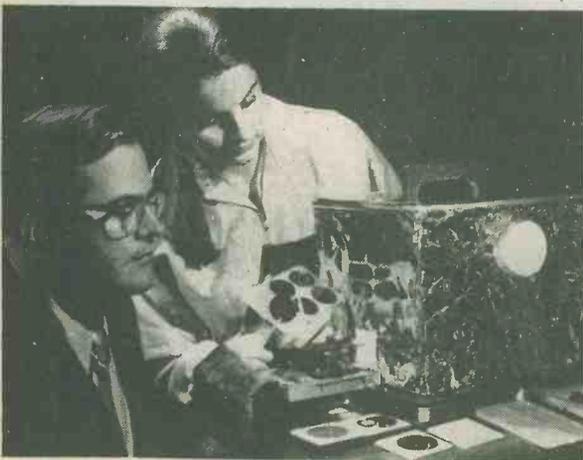With the process, ultraviolet irradiation cleans excess photoresist from semiconductor wafers, thereby solving a long-standing problem in the semiconductor processing industry. The photoresist, a polymer film sensitive to light, is used in etching microscopic circuit patterns onto the wafer. After etching takes place, the left-over plastic film has to be completely removed.



Depolymerization of semiconductor wafers by ultraviolet light. Dr. Bolon, developer of the process, prepares to run sample wafers through a test chamber. The process is continuous and does not have the disadvantages inherent in other methods of polymer removal.


The photoresist is exposed to intense ultraviolet light in the presence of air, causing the material to break down and vaporise. A typical film of photoresist plastic (depending upon its composition and thickness) can be completely removed from a semiconductor wafer in 25 to 40 minutes. The process is the first that lends itself to the continuous removal of excess photoresist material. All other techniques require the processing of wafers in batches, and are thus inherently slower.

In addition, ultraviolet depolymerization is the first dry process that operates at atmospheric pressure and at modest temperatures (about 250°C). The most widely used alternative methods for removing photoresists involve soaking the polymer films, either in a solvent which causes it to swell after which it is shaken or abraded off, or in acid solvent which destroys the polymer.

In many cases, however, a semiconductor processor desires to remove the photoresist without subjecting the substrate to solvents or acids. This is especially important where there are soft metal overlays which would be damaged by abrasion or by corrosive solvents, or where the presence of carbon contaminants would interfere with subsequent fabrication steps.

In tests, Dr. Bolon has found that ultraviolet depolymerization of photoresists proceeds at a rate of about 1,000 Angstroms per minute. But the process can be made to operate ten times faster simply by injecting two per cent ozone gas into the processing chamber.

Semiconductor wafers subjected to the ultraviolet depolymerization process have been inspected with Auger-emission spectroscopy, and this has confirmed that their surfaces are extremely clean and are free of any carbonaceous residue. Furthermore, the process is non-polluting as its only byproducts are carbon dioxide and water. ■

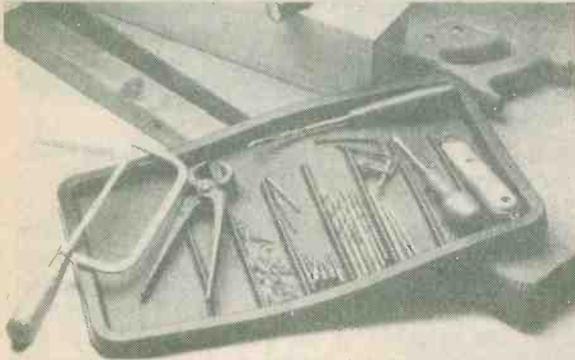RUBBER TRAY FOR YOUR TOOLS

Lost tools, scratched paintwork and bad temper should be saved by a new rubber tool tray, just introduced by Cannon Rubber Ltd. of Ashley Road, Tottenham, London.

The 'Autotidy', made from flexible, non-slip rubber, can be draped over an irregular surface such as a car wing, or laid flat on a polished table top. Internal dividers and a 1-in. lip around the tray provide for a variety of small tools and hardware to be kept conveniently sorted and near at hand, very useful when you are engaged on a constructional project.

Recommended price of the 'Autotidy' is £1.38 including VAT, from motor accessory, hardware and DIY stores.

INAUGURAL MONTREUX ACHIEVEMENT GOLD MEDAL AWARD

An IBA engineer — John L. E. Baldwin — recently received the inaugural Achievement Gold Medal Award at the 10th International Television Symposium at Montreux, Switzerland, for 'the development of the world's first digital intercontinental standards converter'. We extend to him our congratulations on winning this 'first'.

This is the first time that an Achievement Gold Medal Award has been presented at the Montreux technical symposia. At the same time a 10th Anniversary Gold Medal was presented to a French engineer, Claude Mercier.

John Baldwin is Head of the Video and Colour Section of IBA's Experimental and Development Department and was responsible for the conception and successful design of DICE (Digital Intercontinental Conversion Equipment). This equipment has greatly improved the exchange of programmes between countries using different television standards.

100 YEARS OF RECORDED SOUND

Edison invented sound recording 100 years ago this year. The prospect of 'storing up' the human voice, particularly of great men and women, was as sensational in the 19th century as stepping on the moon was in the 20th.

Edison's talking machine established the principle of sound recording. The quality of it had yet to be proved. Meanwhile Edison was diverted for ten years from this discovery to experiment with systems of electric lighting, and two Englishmen, Bell and Tainter, renewed interest in the project by replacing tin foil with wax and producing the gramophone.

Joe Pengelly recalled the tremendous technical achievements and played some of the best recordings of those early days in two Radio 4 programmes — 'The Centenary of Recorded Sound'. Broadcast in June, the programmes included the speech by Lord Stanley, Governor General of Canada, at the Toronto Exhibition in 1888, the voice of Caruso, who demanded, and got, a staggering £100 for recording ten songs in 1902, and the incredible falsetto of the last of the Sistine Chapel castrati.

COVER DATE

The cover date on our next issue, to be published 1st September, will be September/October. The issue to be published in October will be dated November and future issues will continue to be pre-dated.

The revision of cover dates will bring us into line with other radio and electronic journals.

Subscribers will, of course, continue to receive 12 issues per year.

ELECTRIC PIANO FEATURED IN 'TOMORROW'S WORLD'

A musical trio starring a conventional pianoforte, presenter Mike Rodd on flute, and General Instrument Microelectronics' electric piano featured in the BBC's 'Tomorrow's World' recently.

The prototype electronic piano was built round GIM's new AY-1-1320 microcircuit which simulates the sound and touch of hammer action instruments.

In the picture, Mike Rodd compares a sustaining flute note with a decaying piano note simulated by the AY-1-1320.

We gave a short technical description and general notes on this electronic piano in 'News and Comment' in our May issue.



COMMENT

'AMBISONICS' TEST BROADCAST

The first experimental 'on-air' tests of a British-developed surround-sound system known as 'Ambisonics' or 45J were made recently on an Independent Local Radio station — Radio City in Liverpool. As part of the celebrations of the Queen's Jubilee visit to Liverpool, Radio City broadcast a specially commissioned performance of Mahler's Eighth Symphony, the 'Choir of a Thousand Voices', from Liverpool Anglican Cathedral.

This test, formed part of a continuing investigation by engineers of the Independent Broadcasting Authority into a number of systems for broadcasting sound radio programmes for reproduction as 'surround sound' in the home. The system to be used during these experimental broadcasts is known as Ambisonics and has been developed by Michael Gurzon of Oxford University, Professor Fellgett of Reading University and J. S. Wright, D. Brown and J. Hayes with the support of the National Research Development Council.

During the past few years a number of different systems have been proposed for broadcasting additional directional information on stereophonic VHF/FM transmissions. Such systems are usually known as 'quadraphony' (four-channel stereo) or 'surround sound' to distinguish them from existing two-channel stereophony. The systems differ in the manner of carrying or encoding the additional information on the transmitted signal. Some systems use matrixing techniques to allow the additional information to be carried on the conventional two channels of a stereo transmission; others use either one or two additional subcarriers.

Many variations have been proposed for using stereo channels in this enhanced way, each offering some desirable, some less desirable, features.

Details of BBC Quadraphonic broadcasts were given in 'N & C' June issue.

NORTHERN RADIO SOCIETIES EXHIBITION



Along with the RSGB's Alexandra Palace event and the ARRA exhibition at Leicester — it looks as if Belle Vue is now one of the "big three" national amateur radio events of the year.

The exhibition of amateur radio equipment, both commercial and home built, was the largest and best attended of these annual events ever staged by the NRSA. All the well known trade names were represented as well as most of the amateur radio societies in the North West of England. The photograph shows part of the scene inside the exhibition hall, and indicates the large attendance.

The Club Stand Trophy was won by the South Manchester Radio Club and the Inter-Club Quiz was won by the Bury Radio Society.


The date provisionally booked for the NRSA Belle Vue Convention & Exhibition in Manchester next year is Sunday, 2nd April, 1978. Discussions have already taken place regarding the use of an even larger hall at Belle Vue for the 1979 exhibition.


INTERNATIONAL BROADCASTING CONVENTION 1978

The 7th International Broadcasting Convention — IBC 78 — will take place in London, 25-29 September 1978.

IBC 78 will be held at the new Wembley Conference Centre instead of Grosvenor House which has been the venue for the past five of the six IBCs. This move, heralded in May last year, to London's first purpose-built convention centre will enable the IBC to benefit from the first class facilities at Wembley while still being based in London, one of the main centres of broadcasting in the world, and be able to offer all the amenities of the Capital.

IBC 78 is the seventh in a series of biennial broadcasting conventions which have become firmly established as an international forum for new techniques in broadcasting and allied services and one of the world's leading international market places for the latest broadcasting equipment and systems. Each of these events has shown a dramatic growth in the number of delegates attending and countries participating. Records were again broken at IBC 76 when more than 2,600 delegates from 51 countries attended and at the complementary exhibition, 72 exhibitors representing leading manufacturers of the world displayed and demonstrated the latest professional broadcasting equipment and services. It is expected that this continued growth will again be highlighted at IBC 78.

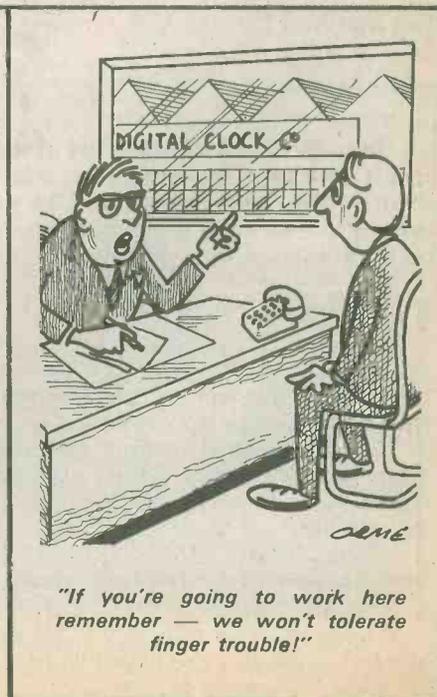

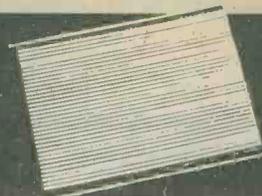

No. 3

12-NOTE TONE GENERATOR

CAN FORM THE BASIS OF AN ELECTRONIC KEYED OR STYLUS ORGAN.

Incorporating two t.t.l. integrated circuits, this very simple circuit offers twelve pre-set tones which are set up to form a complete twelve note scale.

This tone generator is designed to produce a complete set of twelve notes for a musical scale. By itself, it can be used as the basis of a simple "stylus organ", or it can be combined with dividers and filters to form the basis of quite a useful electronic organ. The number of components that are needed is remarkably small, only two i.c.'s, twelve capacitors and twelve skeleton pre-set potentiometers for a complete twelve note scale. The penalty for all this simplicity is rather a large current consumption of about 200mA, so that a mains supply or a large capacity battery is needed.

HEX SCHMITT INVERTER

The type of i.c. used is the 7414 hex Schmitt inverter. The 7414 has a set of six high gain inverting amplifiers with a snap-over action, each of which can be used as an oscillator by simply connecting output to input via a resistor, and the input to earth by way of a capacitor. The waveshape is a series of pulses with unequal mark-to-space ratio; the mark-to-space ratio can be improved

but the additional components that are needed hardly make the effort worthwhile, and the tuning then becomes much more difficult.

Since these are t.t.l. circuits, the supply voltage should be limited to 5 volts. In practice the tone generator will work from a 4.5 volt battery, and in the type of circuit used will not be damaged by operation from 6 volts (via a diode), but the frequency of operation is rather sensitive to voltage, so that a stabilized supply (see "Blob-A-Job No. 1" in the June 1977 issue) should be used if a complete organ is to be built up. For a portable stylus organ a 4.5 volt battery of large capacity will serve fairly well, and a very simple output stage will be enough to drive a speaker.

Fig. 1 shows the pin connections for the 7414, whilst Fig. 2 gives the circuit of the 12-note generator. All the potentiometers are 1kΩ standard vertical mounting skeleton types and all the capacitors are 6.8μF electrolytic. These are specified in the Components List as 10 volts working but, if difficulty is experienced in obtaining this working voltage, a higher voltage is satisfactory. Mullard miniature 6.8μF 40 volt capacitors with a diameter of 4.8mm. and a length of 12.5mm. can be employed, and these are quite readily available. It may be necessary to alter the capacitor values for some notes.

BLOB BOARD

The circuit is built on a ZB-2-IC Blob Board, with the components arranged as shown in the assembly diagrams. The twelve pre-sets should be mounted so that each can be easily adjusted to obtain the correct note from each inverter. Because of capacitor tolerances it may sometimes be necessary to substitute capacitor values if the range of the pre-sets is insufficient; this is easily done when Blob Board is used for construction. A larger value of capacitance will give a lower note, a

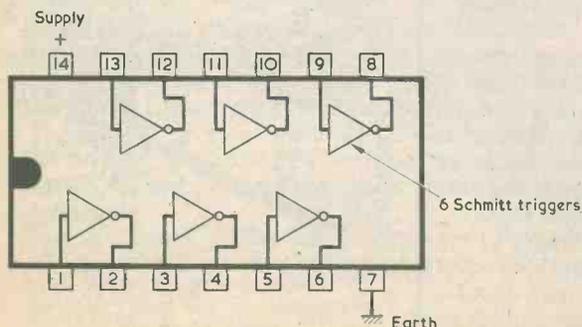


Fig. 1. Pinout diagram of the 7414 i.c.

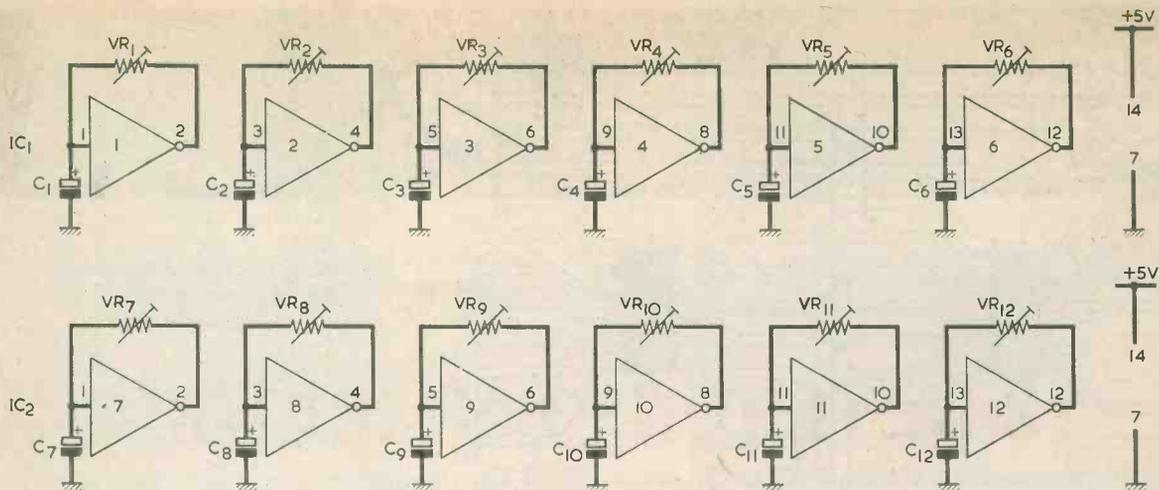


Fig. 2. The circuit of the tone generator. All six Schmitt trigger inverters of each i.c. are employed

COMPONENTS

Resistors

VR1-VR12 1k Ω pre-set potentiometer, standard skeleton, vertical

Capacitors

C1-C12 6.8 μ F electrolytic, 10 V. Wkg.

Semiconductors

IC1 7414
IC2 7414

Blob Board

Blob Board type ZB-2-IC

smaller value a higher note. The cheapest skeleton pre-sets should be used; those employed in the prototype were taken from a mixed bag offered at low cost.


Start construction by soldering the 7414's to the Blob Board. See Fig. 3. Tin the end of each of the i.c. pins, and place the i.c. on the bench with the index mark facing away from you. Set down the Blob Board such that the maker's name is at the bottom and the type number is at the top as you look at it on the bench. Now place each i.c. on its solder pads, with the top set of pads left unused, so that pin 1 of the i.c. is placed on pad 7 and pin 1 of IC2 is on pad 28. This leaves two spare mounting pads above each integrated circuit.

Once you are satisfied that the i.c.'s are correctly placed, line up one i.c. on its solder pads and solder pin 1 to its pad by bringing up a hot iron freshly charged with a blob of solder. When the iron is touched against the i.c. pin and the solder pad, a blob-joint will form almost immediately, and the iron can be taken away. Now check the i.c. again. If all is well, solder on pin 8 in the same way, and check again. At this stage the i.c. can be easily removed; any removal later will have to be carried out with solder braid. Solder pins 1 and 8 of the second i.c.

Now solder on the remaining pins of the two i.c.'s. With a bare wire connect pads 19 and 21 to 23, and

similarly connect pads 40 and 42 to 23, both as shown in Fig. 3. Using an insulated wire, link together tracks 2 and 23. Track 2 is the earth line and takes the negative supply. Track 1 is the 5 volt positive supply line.

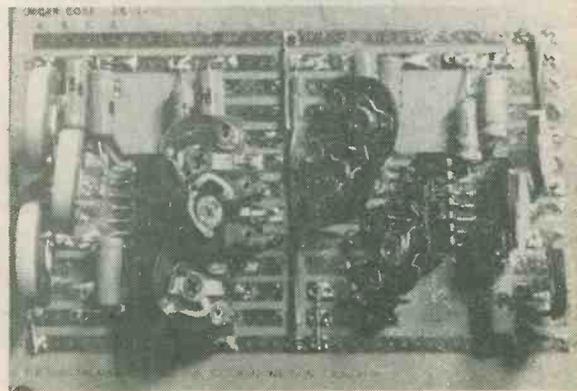Next, solder capacitor C1 from pad 7 (connected to pin 1 of IC1) to earth, at track 2. Keep the capacitor close to the i.c., as we shall want to



The completed 12-note generator. The six central pre-set potentiometers are mounted at an angle for ease of adjustment


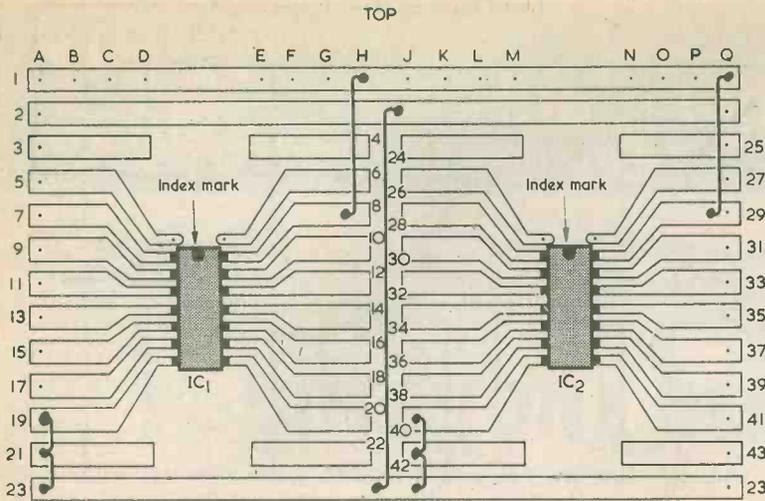


fig. 3 Positions of the integrated circuits on the board. If the i.c.'s are not mounted in these positions the pad numbers in the text will not apply

Fig. 4. Fitting capacitors C1 to C6 to the Blob Board. Capacitors C7 to C12 are not shown; these are positioned similarly around IC2

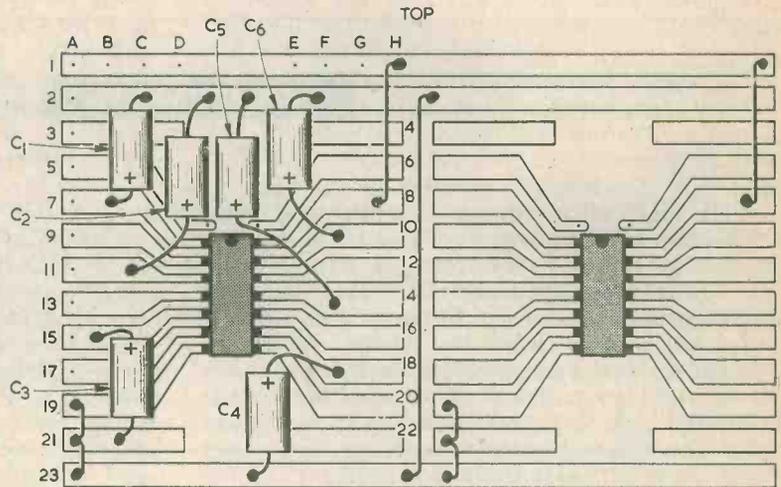

mount the pre-sets nearer to the edge of the board where they are more easily adjusted. Solder C2 from pad 11 to earth at pad 2, and C3 from pad 15 to its nearest earth, pad 21. Note that we can leave the leads of these capacitors long, or trim them, as we please. Using long leads has the advantage that we can adjust the positions of the capacitors to make the assembly look neater when all the construction is finished. The negative leads of all capacitors connect to earth.

Now use a piece of insulated wire to connect pad 8 (pin 14 of IC1) to the positive 5 volt supply line on track 1. The wire is shown in Fig. 3 and should be routed as illustrated. Now solder in the remaining capacitors for IC1, between pad 10, pad 14, pad 18, and earth, as in Fig. 4. This completes the capacitor connections for IC1.

After this, the pre-sets are prepared for soldering. Only two of the three legs of each pre-set will be used and the spare leg, which may be either of the outer legs, should be bent up out of the way. We may have to splay the two legs which are used slightly apart to fit the Blob Board pads. One pre-set connects between pads 7 and 9, another between pads 11 and 13, and a third between pads 15 and 17. See Fig. 5. On the other side of the i.c.

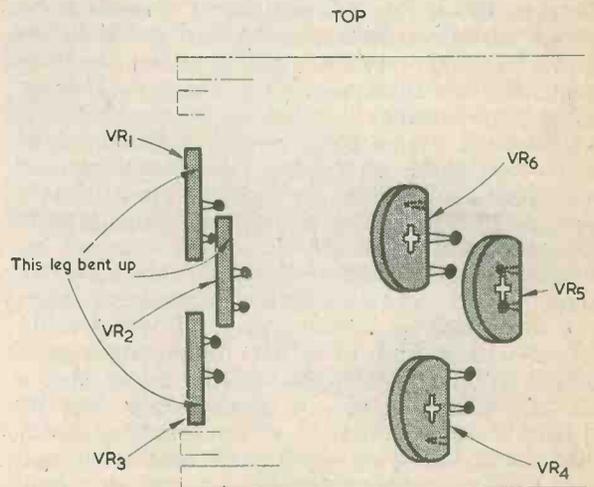


Fig. 5. The six skeleton pre-set potentiometers are soldered as shown here. They must be mounted so that they can be easily adjusted.

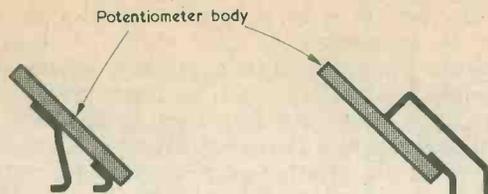


Fig. 6. Two methods of bending the legs of VR4 to VR9 so that they may be mounted at a suitable angle

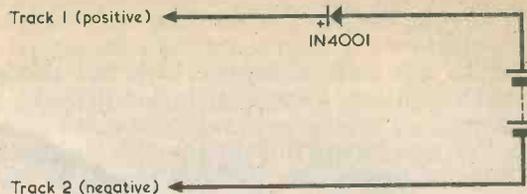


Fig. 7. Connecting a silicon rectifier, such as the 1N4001 or equivalent, in series with track 1 will ensure that the battery cannot be applied with incorrect polarity

the pre-sets are fitted between pads 10 and 12, 14 and 16, 18 and 20. Pre-sets VR1 to VR3 are mounted vertically in normal manner so that they may be adjusted from the edge of the board. VR4 to VR7 need to be mounted at an angle so that their adjustment slots are available from above the board. This is achieved by suitably bending their legs using either of the methods shown in Fig. 6.

Now repeat these assembly methods for IC2. We start with capacitors C7 to C12, soldering each capacitor between an input pin and earth as before. An insulated link wire connects pad 29 to pad 1. The pre-sets are attached as for IC1, with the three soldered between pads 28 and 30, pads 32 and 34 and pads 36 and 38 mounted at an angle which permits adjustment from above the board. The assembly is completed by soldering on the supply (battery) leads, and these should be arranged so that their polarity cannot be accidentally reversed. If this is impossible, then a silicon rectifier should be inserted in the positive line as shown in Fig. 7. The rectifier will drop the voltage slightly, enough to make operation from a 6 volt accumulator which is not charging safe, but making operation from a 4.5 volt battery possible only when the battery is fresh. Never use a 6 volt accumulator which is still on charge.

TESTING AND TUNING

An amplifier, earphone or headphones is needed for testing and tuning, and care is needed here on two counts. The first of these is that connecting a

low resistance load to a 7414 output will damage the i.c., and the second is that the output level will overload most amplifier inputs. Fig. 8 shows three suitable methods of coupling to the i.c. outputs. An earphone with an impedance lower than 250 Ω must not be connected to an i.c. output without a series resistor.

Start by setting all the pre-sets to maximum resistance, with the sliding contact on each pre-set touching the track end at the leg which has been folded up. Clip the earth lead of the headphones, earphone or amplifier to the negative (earth) line of the Blob Board, and clip the other lead to the output from the first oscillator of IC1, on pad 9. Listen to this note, which will be the lowest on your scale. If there is no note to be heard, adjust the pre-set, VR1, until oscillation starts (oscillation is not possible with too high a resistance value, and some 7414's will not oscillate with 1k Ω in circuit). Check that the oscillator will start again reliably when the power supply is switched off and on again. With this oscillator now running at the lowest frequency of the scale, take the headphone, earphone or amplifier lead from pad 9 to pad 13 to hear the next note. Adjust this by means of its pre-set, VR2, so that the note is a semitone higher than the note from the first oscillator. If you have a reasonably musical ear you should find this process not too difficult, but if not you will need a piano to help you. Locate the note of the lowest oscillator on the piano, and adjust the oscillator to match exactly the piano note. Now sound the next

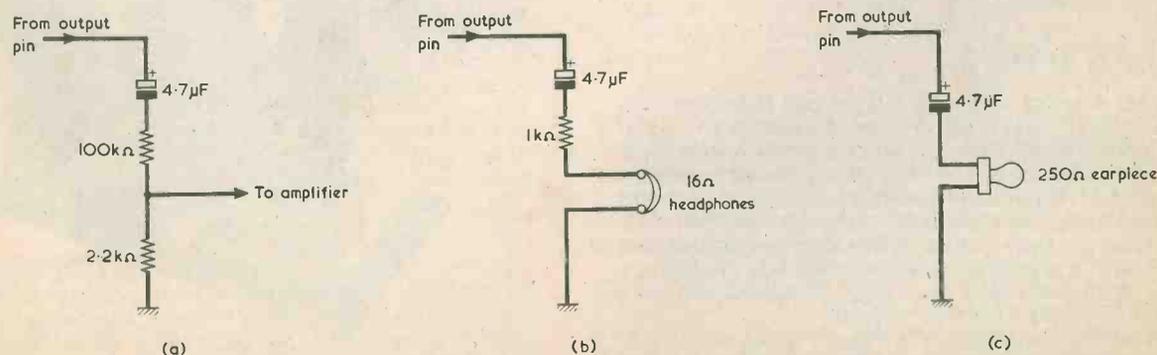


Fig. 8. Suitable methods of coupling an output to (a) an a.f. amplifier, (b) low resistance headphones and (c) a high resistance earphone

piano key on the right of the first note (black or white, whichever is nearer) and tune the second oscillator to this note. Continue with this process, with each oscillator a semitone higher than the one before until all twelve oscillators are at the correct pitch. You now have a full chromatic scale of notes. The range of frequencies available cannot be stated precisely as there are so many tolerances in the circuit. It should, however, be possible to obtain a scale where the first oscillator starts at, say, the C below middle C or at middle C itself. Other starting notes may be chosen.

To incorporate the 12-note generator into a stylus organ, you need a small amplifier whose in-

put connection is to a metal stylus, and whose earth is connected to the earth of the tone generator. Each output from the tone generator can be coupled to a strip, such as those given by the tracks of a piece cut out from a ZB-2V5 Blob Board, by way of a $1k\Omega$ $\frac{1}{4}$ watt resistor. Twelve $1k\Omega$ resistors in all, one for each output, are required and they ensure that no damage to the i.c.'s can occur if two strips are short-circuited together.

For an organ a set of keys operating microswitches could couple the generator outputs to the amplifier. Again, a $1k\Omega$ resistor should be inserted in series with each output and the corresponding switch. ■

A nostalgic glance back to the early 1920's.

Times Past

by

H. Ross Macdonald

It is compact in its walnut box, utilitarian, even a little sad-looking, enlivened only by the reflections on its shiny valves. Yet this, the Marconiphone V2, was one of the most advanced radio sets of its time.


In 1923 it was so contemporary that it almost hurt to look at it. The first commercial wireless set that looked and really was functional, while most of its competitors were covered in engraved dials and switches hinting at the most complex adjustments and calling for deft operational skills.

But with this magic little brown box you just switched on, turned the two knobs, and at once there were music and strange voices in the room. As one ad-writer of the period stated with unconscious humour: "You could even hear foreigners speaking in real foreign voices."


REFLEX SYSTEM

This wireless set — we did not call them radios in those days — was the first Marconiphone to enjoy real popularity and many thousands must have been sold. It was designed in late 1922 by the almost legendary Capt. J. H. Round and, considering the state of the art at that time, it remains a tribute to his enormous skill. He used the then popular reflex system but discarded the use of a crystal detector and ended up producing a very stable set that was easy to adjust and gave reliable results over long periods.

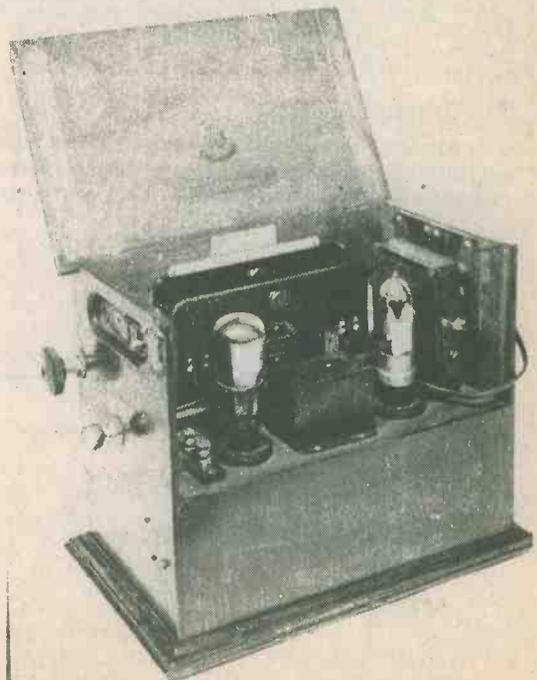A normal experience of a listener in the early twenties was that when one switched off a station programme say at seven o'clock in the evening, there was no guarantee that it would be present at the same volume or even dial indication when one switched on



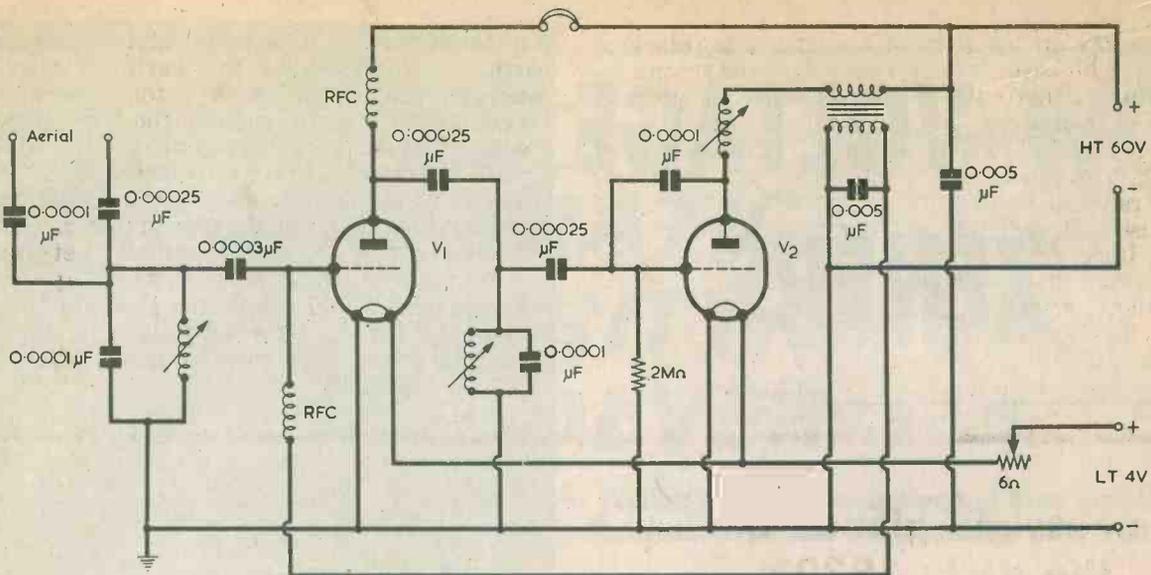The Marconiphone V2 receiver. Produced in 1923 this 2-valve set was in the forefront of domestic receiver design of the period



The basic circuit of the V2 receiver. Valve V1 provides a measure of r.f. amplification whilst V2 functions as a grid leak detector. The detected signal at V2 anode is coupled via the a.f. transformer back to V1, which then also amplifies the a.f. signal

again to hear the nine o'clock news. By contrast this particular receiver (providing the batteries were charged) always gave repeatable results.

Owning a valve operated wireless set in 1923 was quite an expensive affair. The basic set, valves and royalty for this model cost £16.3.6d; with headphones, h.t. battery, 4 volt accumulator and aerial and earth installation the cost rose to some £24.

Now, £24 was a great deal of money in 1923. When one remembers that about 65 per cent of the population were earning under £2 per week and paying rent and bringing up a family on this salary, £24 for a wireless set was indeed a lot of money.

There were of course cheaper alternative family entertainments. If you lived close enough to a broadcasting station you could get results with a crystal set costing £1 to £3 complete, but then you were stuck with one programme as well as endless fiddling with the cat's whisker. Should you want to hear music of your choice the alternative was a wind-up gramophone and lots of records (78's of course). You could buy a nice noisy gramophone for about £3, not of course an H.M.V., which were always nice and seldom noisy.

The ownership of a valve set, especially if it would operate a loudspeaker, was for the lucky few something special indeed, equivalent to today's ownership of colour TV, central heating and double glazing. Captain Round may have supplied the technical magic but it was left to Colonel Stanley of the Marconiphone Company to make the magic easy for people to acquire, for he made it possible to own this wireless set on hire purchase. I think this was another first for the Marconiphone Company. It was the first domestic receiver to be sold on H.P. directly from the manufacturer.

EARLY MEMORY

My first encounter with this set was in the North of Scotland in 1924, where it performed as well as could be expected in a place so far distant from broadcasting stations. The owner was a choleric Irishman and a retired Sergeant Major who had spent some 25 years in India. He was a large man, a loud man, and

was accustomed to always being right! He wanted to hear Dublin on his "machine" as he called it. After consulting what at that period passed for expert advice, he was told he needed a bigger aerial. So for the not inconsiderable sum of 2 shillings I was inveigled on to the roof of his house and erected more than 150 feet of wire pointing, according to his exact instructions, towards Dublin. When I suggested that according to my school atlas and Scout's compass there was some variance between his sense of direction and mine, he brushed my advice aside. He was accustomed to being always right.

We did not get Dublin on that occasion but, due to the fact that the Grand Fleet was stationed off Cromarty, the set got more than its fair share of messages in morse code at 600 metres. However, the Sergeant Major brushed this interference aside and said it was due to the machinations of his ever-present enemies who had always been jealous of his military career and his advancement.

However, his receiver and several others in the district continued to give good and useful service for many years. The set in the photograph was acquired by me some 10 years ago. When I rescued it, the set was covered in grime in a cellar where it had stood for 15 years. After restoration and finding some valves of the period, it was connected up to batteries and a horn speaker of like vintage and it worked moderately well. During the BBC 50 year Jubilee programme, at the request of some friends it was again put to work. Despite its 50 years of age it again acquitted itself favourably.

To my mind the Marconiphone V2 represents a tribute to its designer and to the assemblers who built it. The individual components have scarcely departed from their original values, the soldered joints are still sound and the cabinet, despite the damp cellar, shows no sign of warping or cracks.

The Marconiphone Company made many other sets after this period until in 1929 they joined with Columbia and H.M.V. to form the grand triumvirate of E.M.I. After that date the name of Marconiphone still continued to appear before the public on the fronts of many successful radio and television receivers.

LOW VOLTAGE ZENERS

By R. J. Caborn

Some care is needed when using zener diodes with voltages lower than 6 volts.

We tend to look upon zener diodes as useful voltage stabilizing devices which drop almost exactly the voltage with which they are credited. This is fairly true with zener diodes rated at 6 volts or more, but does not apply so readily with zener diodes of lower voltage.

CHARACTERISTICS

Fig. 1 shows static voltage-current curves for three diodes from the popular 400mW BZY88 range. These

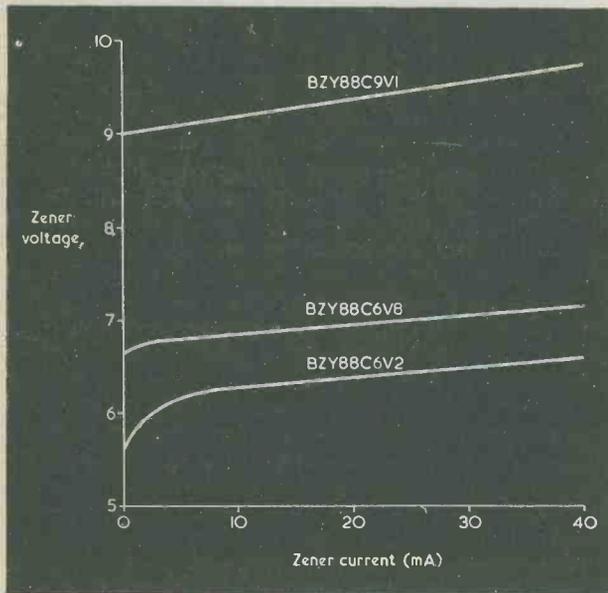


Fig. 1. Voltage-current curves for three BZY88 zener diodes. The onset of curvature at low zener currents becomes noticeable with the lowest curve.

TABLE 1
ZENERS VOLTAGES

Zener Current	BZY88C9V1			BZY88C6V2		
	Min.	Typ.	Max.	Min.	Typ.	Max.
1mA	8.55	9.0	9.5	5.7	5.9	6.5
5mA	8.6	9.1	9.6	5.8	6.2	6.6
20mA	8.7	9.4	9.7	5.95	6.4	6.7

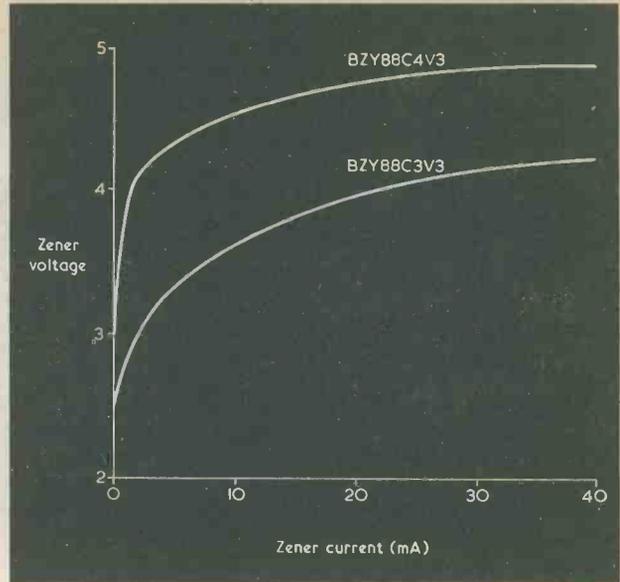


Fig. 2. The curvature becomes very pronounced with lower zener voltages. The curves here apply to diodes with nominal zener voltages of 4.3 and 3.3 volts

TABLE 2
ZENERS VOLTAGES

Zener Current	BZY88C4V3			BZY88C3V3		
	Min.	Typ.	Max.	Min.	Typ.	Max.
1mA	3.3	3.6	3.9	2.4	2.75	3.0
5mA	4.0	4.3	4.5	3.1	3.3	3.5
20mA	4.45	4.7	4.95	3.5	4.0	4.2

are the BZY88C9V1, the BZY88C6V8 and the BZY88C6V2. Note that the 9.1 and 6.8 volt diodes commence a straight slope as soon as they pass a zener current of 2mA or even less. With the BZY88C6V2, on the other hand, we see quite a pronounced curvature until zener current reaches about 8mA. Above 8mA the curve becomes linear. Table 1, which is taken from Mullard data, lists the characteristics of the BZY88C9V1 and the BZY88C6V2 for zener currents of 1mA, 5mA and 20mA.

We turn, next, in Fig. 2, to curves for two lower voltage diodes, these being the BZY88C4V3 and the BZY88C3V3. Here, curvature is extremely pronounced for all zener currents up to some 30mA. Table 2, also taken from Mullard data, gives the characteristics for these two diodes at the three currents of 1mA, 5mA and 20mA, and fully demonstrates the story implicit in the curves. With a typical BZY88C3V3, zener voltage at 1mA is only 2.75 volts whilst at 20mA the voltage is as high as 4 volts.

The tables tell us also that all the diodes are typically at their nominal voltages at 5mA, and this current is, indeed, that recommended by the manufacturer for acceptance testing purposes.

The moral is simple. When using lower voltage zener diodes expect quite wide variations in zener voltage at different zener currents. If you want a low voltage BZY88 zener diode to stabilize at a voltage within its tolerance, operate it at 5mA. ■

SUGGESTED CIRCUIT

AUTOMATIC POLARITY/BASE RESOLVER

By G. A. French

In the "Suggested Circuit" article which appeared in the April 1977 issue the author described a very simple piece of test equipment which was capable of indicating whether a bipolar transistor was n.p.n. or p.n.p. and of also identifying its base lead-out. The circuit is extremely useful for sorting out unbranded transistors such as those which have been purchased as job lots at low cost.

The circuit of the polarity/base resolver is reproduced in Fig. 1. The unknown transistor is connected to the three test terminals and the unit is switched on at S2. S1 is then taken through its three positions. If all three l.e.d.'s light up at one switch position and only one l.e.d. lights up at the remaining two positions then the test transistor is n.p.n. and the switch position at which all three l.e.d.'s are alight corresponds to its base lead-out. Should all three l.e.d.'s light up at two positions of the switch and only one l.e.d. lights up at the third position the test transistor is p.n.p., and the position of S1 which causes the single l.e.d. to be illuminated corresponds to the transistor base.

A full explanation of circuit operation was provided in the previous article, and only a quick summary will now be given. When an n.p.n. transistor is connected to the test terminals and the switch arm connects to its base, forward current flows in both the base-emitter and base-collector junctions, causing all three l.e.d.'s to be illuminated. At the other two switch positions there is no current flow through the transistor, which presents a reverse biased emitter-base or collector-base junction to the current. A p.n.p. transistor presents reverse-biased junctions when the switch connects to its

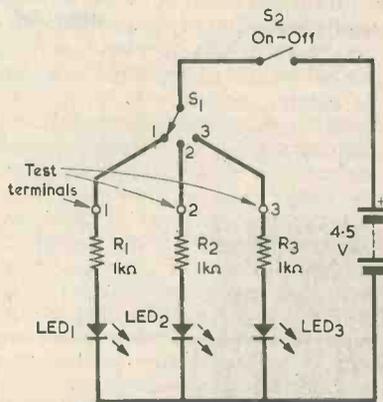


Fig. 1. The circuit of the polarity/base resolver in its initial form

base. When the switch arm connects to its emitter the transistor functions as an amplifying transistor in the common emitter mode, and when the switch arm connects to its collector the transistor functions as an amplifying transistor with the collector acting as an emitter and the emitter functioning as a collector. This assumes that the transistor has a current gain of at least unity when operated in this manner, and the author has not yet found a transistor which does not offer this performance.

Regrettably, the diagrams for Figs. 5(b) and 6(b) were transposed in the earlier article.

AUTOMATIC OPERATION

Since writing this article, it has occurred to the writer that performance would be enhanced if the 3-way switch of Fig. 1 could be dispensed with and the positive supply


applied successively to the test terminals by an automatic switching circuit. It would then be necessary merely to connect up the transistor and observe the lighting of the l.e.d.'s. In some instances the transistor leads could simply be touched against the terminals, giving an even quicker means of checking.

The automatic switching circuit would have to apply the positive supply to the test terminals following the sequence 1,2,3,1,2,3,1, etc., and it would be essential for there to be a significant gap between the cessation of voltage at one terminal and the application of voltage to the next. If this were not done the two situations with a p.n.p. transistor where all three l.e.d.'s are alight would merge into each other, as also would the two situations with an n.p.n. transistor where only one l.e.d. is alight, and it would be more difficult to differentiate between a p.n.p. and an n.p.n. transistor.

A simple oscillator circuit capable of offering the sequential switching required is shown in Fig. 2. This oscillator has appeared in earlier "Suggested Circuit" articles and was described in the May and June 1975 issues. The oscillator is self-starting and offers reliable performance for electrolytic coupling capacitor values between some $10\mu\text{F}$ and $500\mu\text{F}$. It will also run with capacitor values from $10\mu\text{F}$ down to $2\mu\text{F}$ provided the capacitors have very low leakage current. When the capacitors are $47\mu\text{F}$, as they are in Fig. 2, it is only necessary that they be good quality modern components. The author employed Mullard miniature electrolytic capacitors in the prototype circuit.

Between the instants of changeover, one transistor in the oscillator is always off and the other

Fig. 2. A 3-step oscillator capable of offering automatic operation of the resolver

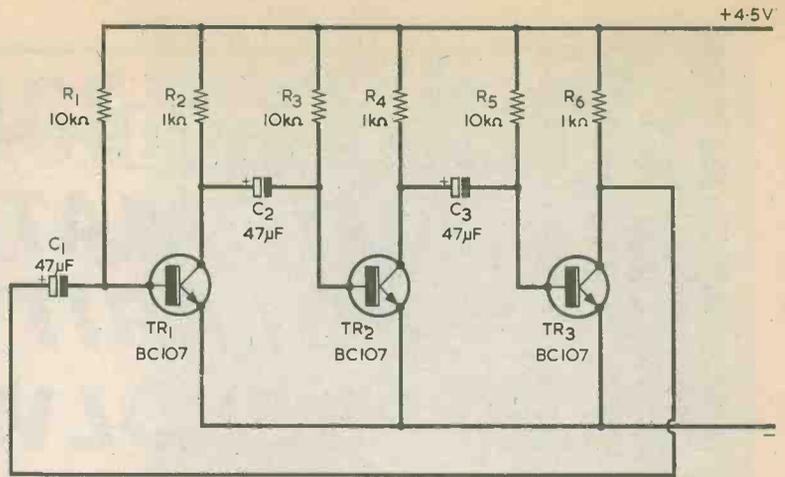

two are always on. Let us examine the circuit at a moment when TR1 is changing from the off to the on condition. At this instant C2 will be charged up to the supply potential

less the 0.6 volt dropped across the base-emitter junction of TR2. As TR1 turns on its collector potential falls from that of the positive rail to a value which is about 0.2 volt positive of the negative rail.

Because of the presence of C2, the base of TR2 is taken negative by a similar voltage, whereupon TR2 turns off. The circuit now remains in this condition as C2 discharges via R3. After a period C2 discharges


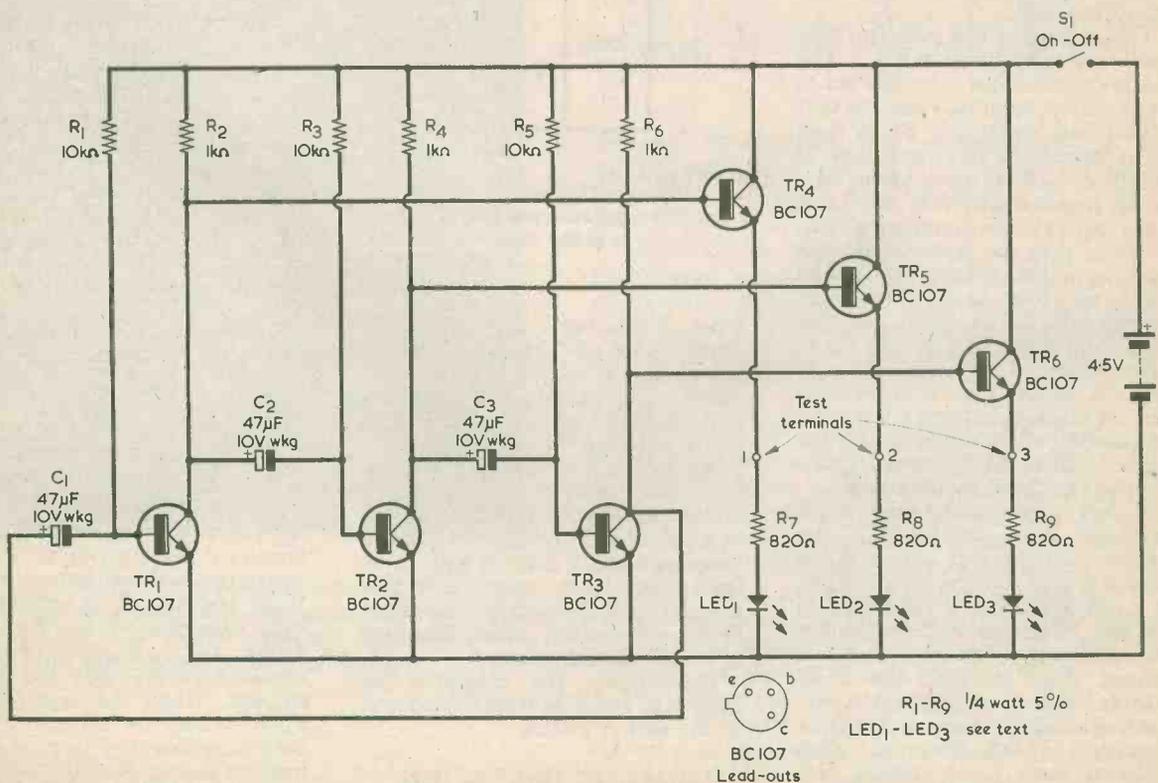


Fig. 3. The complete circuit of the automatic polarity/base resolver. It is merely necessary to switch on at S1, connect the transistor to be checked and observe the l.e.d.'s

Fig. 4. The resolver can be assembled in a small plastic case. A suggested front panel layout is shown here

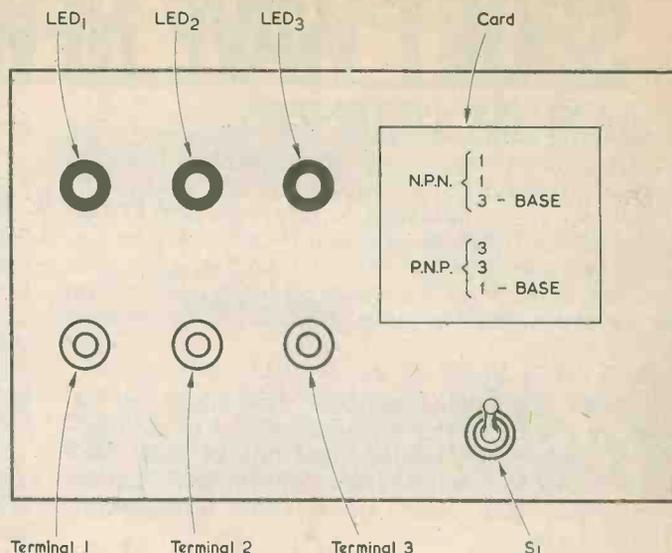

sufficiently for the base of TR2 to become some 0.6 volt positive of the negative rail, whereupon TR2 turns on. Its collector voltage falls rapidly, with the result that the base of TR3 is taken negative by way of the charged C3, and TR3 turns off. When C3 has discharged sufficiently into R5, TR3 turns on again and, in so doing, causes TR1 to turn off. The cycles proceed in this manner with each transistor turning off in turn. Using the component values shown, the length of a complete three-transistor cycle, from TR1 turning off to TR1 turning off the following time, is approximately 1.25 seconds.

It will be seen that the oscillator is capable of controlling the application of a positive voltage to the test terminals of Fig. 1. What has not been mentioned so far, with respect to Fig. 2, is that the collector of any transistor does not rise to the potential of the positive rail immediately after the transistor turns off. When, for instance, TR2 turns off its collector potential rises relatively slowly because C3 charges via R4 and the forward biased base-emitter junction of TR3. This slow rise in collector potential can provide the gap between periods of l.e.d. illumination which was referred to earlier.

Before leaving the circuit of Fig. 2 it should be pointed out that, when two successive transistors are on, the coupling electrolytic capacitor between them has a small reverse polarity applied to it. When, for example, TR2 and TR3 are on, C3 has a potential of 0.6 volt on its negative plate and a potential of about 0.2 volt on its positive plate. This small reverse voltage does not appear to affect circuit operation in practice with the component values

specified. In the 1975 articles on the oscillator the transistors were germanium, whereupon there is no application of a reverse voltage to the electrolytic coupling capacitors. Experimenters who wish to use the oscillator circuit with alternative capacitor values may find it desirable to employ germanium transistors if any difficulties are experienced with silicon transistors. Whatever transistors are used, the supply rail voltage must not be greater than the maximum reverse base-emitter voltage rating of the transistors concerned. With the BC107 this rating is 6 volts.

COMPLETE CIRCUIT

The complete circuit of the automatic polarity/base resolver appears in Fig. 3. Here, TR1, TR2 and TR3 are in the oscillator circuit of Fig. 2, with emitter followers TR4, TR5 and TR6 coupled respectively to their collectors. The emitters of TR4, TR5 and TR6 connect to test terminals 1, 2 and 3. Thus, when a transistor in the oscillator turns off its collector goes (relatively slowly) positive, causing the corresponding emitter follower to apply a positive supply to the test terminal to which it connects. If, during the cycle and with no transistor connected to the test terminals, TR1 is turned off, test terminal 1 is at a positive potential and LED1 is alight. When TR1 turns on, LED1 extinguishes immediately. LED2 does not, however, light up until the collector of TR2 has gone sufficiently positive for the l.e.d. forward voltage to be present at the emitter of TR5. The l.e.d.'s light up successively, with a perceivable gap between the extinguishing of one l.e.d. and the lighting of the next.

The series l.e.d. resistors, R7, R8 and R9, have a slightly lower value than the series resistors in Fig. 1. This is because the positive voltage applied to the test terminals is 0.6 volt lower, due to the presence of the emitter followers. The l.e.d.'s should be red types and the author employed Doram type 4 components, which have good sensitivity at the low currents appearing in the circuit. With these particular diodes the anode lead-out is shorter than the cathode lead-out. The latter connects to the negative rail.


If a p.n.p. transistor is connected to the test terminals the l.e.d.'s take up the rhythm 3-3-1, the figures signifying the number of l.e.d.'s which are alight. When the single l.e.d. lights up, this indicates the base lead-out of the test transistor. With an n.p.n. transistor the rhythm is 1-1-3. The base is indicated by the l.e.d. which has not been lit up on its own during the sequence. Since the l.e.d.'s light up in order, that l.e.d. is the one which would have lit up next on its own had not all three l.e.d.'s turned on.

There is no need to keep S1 switched off when connecting a test transistor, as the voltages and currents at the test terminals are quite low. No damage will result if the test terminals are inadvertently short-circuited together. The current drawn from the 4.5 volt battery is about 11mA with one l.e.d. lit, rising to approximately 17mA when all three l.e.d.'s are alight.

The circuit can be assembled in a small plastic case having a front panel layout similar to that shown in Fig. 4. A card glued to the cover shows the rhythms resulting from the two kinds of transistor and acts as a reminder of these.

SHORT WAVE NEWS

FOR DX LISTENERS

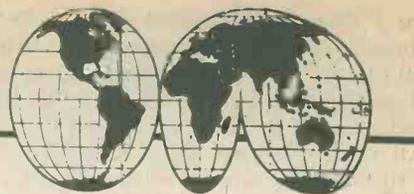

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

In the last issue, mention was made in the opening gambit of this series of articles to the logging of clandestine stations and one in particular that is back to front, but more of that later. Let us commence with more news about clandestine transmitters.

The "Voice of the One Lebanon" (in Arabic "Sawt Lubnan al-Wahid") operates from 1030 to 1130 and from 2030 to 2130 in Arabic on **6170** and on **9510**. Broadcasts are anti-Syrian and against the Syrian presence in Lebanon.

The "Voice of Arab Syria" (in Arabic "Sawt Suriya al-Arabiya") is on the air from 0400 to 0500, 0700 to 0800 and from 1700 to 1800 on (surprise, surprise) **6170** and **9510**. According to the BBC Monitoring Service, to whom I am indebted for the foregoing information, programmes include a newscast, press quotations and anti-Syrian regime talks.

The back to front programmes? Oh yes, not strictly speaking clandestine but perhaps the nearest one can get, and certainly very interesting to those of us who are aware of the current 'battles' being fought on the short wave bands. I refer of course to the broadcasts from Radio Peking on reversed tape which are always in Russian. Several theories have been advanced by Dxers as to just why these broadcasts are carried out in such a mode, the current favourite being that it is done to avoid Russian jamming, such radiations being intended for Chinese provincial stations near the Soviet border, not equipped with landline facilities, who promptly record the programme and retransmit 'right way up'. However, more about this next month, meanwhile listen on **6550** from 1830 to 1925, you'll hardly be expected to understand Russian backwards but you can always tape it and do the reversing bit yourself!

CURRENT SCHEDULES

● ETHIOPIA

The "Radio Voice of Revolutionary Ethiopia", Addis Ababa, lists a transmission in English from 1630 to 1700 on **6015** and on **7180**.

● HUNGARY

"Radio Budapest" has an External Service in which the following broadcasts, in English to Europe, are made. From 1200 to 1240 (not on Saturdays or Sundays) on **7155**, **9585**, **11910**, **15160**, **17785** and on **21525**; from 1515 to 1530 on Tuesdays and Fridays a Dx programme is featured; from 2130 to 2200 on **5965**, **7200**, **9655**, **11910**, **15415** and on **17780**.

● ISRAEL

"Kol Yisrael", Jerusalem has the following frequency schedule for its service in English to Europe. From 1200 to 1230 on **11655**, **15100**, **15405** and on **17815**; from 2000 to 2030 on **9815** and **11655**.

● CHINA

"Radio Peking" radiates programmes in English to Europe from 2020 to 2130 on **5090**, **6590**, **6860**, **7590** and on **9030**; from 2130 to 2230 on the same channels.

● NETHERLANDS

"Radio Nederland Wereldomroep", Hilversum, is in English to Europe at the following times — from 0930 to 1050 on **5955**, **6045**, **7240**, **9660** and on **9895**; from 1400 to 1520 on **5955**, **6045**, **9895**, (11740 Madagascar Relay), **15185** and on **17810**; from 1830 to 1950 on **6020**, **11730** and on **17700**; from 2000 to 2120 on **11730** from Madagascar Relay.

● NIGERIA

The Domestic Service National Programme from Lagos may be heard from 0700 to 1630 on **7255**; from 0430 to 1000 and from 1500 to 2305 on **4990**. Most of the programmes are in English.

AROUND THE DIAL

● CHINA

Radio Peking on **7080** at 1930, OM with a newscast in English in a programme directed to North and West Africa, scheduled from 1930 to 2030.

Radio Peking on **3920** at 2039, YL in Chinese, orchestral music in local style in the Domestic Service 1, scheduled on this channel from 2000 to 0100 and from 1100 to 1735.

Radio Peking on **9020** at 1920; OM with a talk in Chinese in the Domestic Service 2, scheduled from 2100 to 1600 except Wednesdays and Fridays when the schedule is from 2100 to 0600 and from 0950 to 1700.

Checking on the PLA (Peoples Liberation Army) Fukien Front transmissions recently the following were logged — **2490** at 2025, YL in Chinese in Network 1, scheduled from 1200 to 0118; **3000** at 2030, Chinese orchestral music in Network 1, scheduled from 1227 to 2314; **3400** at 1847, OM in Chinese, scheduled from 1120 to 1900; **3535** at 1950, YL in Chinese and local music in Network 1, scheduled from 1300 to 2244; **4045** at 1945, OM in Chinese and local music in Network 1, scheduled

from 1000 to 0530; 4330 at 1943, YL with songs, orchestral music in Network 1, scheduled from 1100 to 0158; and, last but not least, 4380 at 1843, OM and YL alternate in Chinese in Network 2, scheduled from 0230 to 1900.

All transmissions from the PLA Fukien Front are directed to the Offshore Islands and Taiwan and are in Standard Chinese or Amoy.

● NORTH KOREA

Radio Pyongyang on a measured 6398 at 2050, YL's in chorus, local music in a programme directed to South Korea, scheduled from 2000 to 2130.

Radio Pyongyang on a measured 6398 at 2050, OM in French in the programme of that language directed to the Near and Middle East and Africa, scheduled from 2000 to 2150 on this channel.

● KUWAIT

Radio Kuwait on the out-of-band frequency 12085 at 1837, OM with a talk on Zionism in English.

● EGYPT

Radio Cairo on 15475 at 1331, Islamic chants in a "Voice of the Arabs" programme, scheduled from 0800 to 1400 and from 1500 to 1900.

● USSR

Radio Moscow on 15100 at 1325, OM with identification "Radio Station Peace and Progress" in the English programme directed to Asia.

● ALBANIA

Radio Tirana on 9375 at 1450, YL in Polish to Europe, scheduled from 1430 to 1500.

● MALAWI

Blantyre on 3380 at 1800, OM with station identification and a newscast in English.

● SRI LANKA

Colombo on a measured 4902 at 1939, Buddhist chants on a full-moon day. To log this one, consult the calender and then, hopefully, listen!

● NIGERIA

Lagos on 15140 at 1945, YL in English, local pops on records.

● ECUADOR

This country is easy to log by virtue of the HCJB transmissions but Dxer colleague Gordon Bennett of Stockport has brought to notice, in a recent letter, that some readers may care to try for the following Ecuador stations on the lower frequencies.

Radio National Espejo, Quito, on 4679 at 0200 (and often through to 0700).

Radio Splendit, Cuenca, on 5025 at 0355, LA music programme with several identifications interspersed.

Emisoras Progreso, Loja, on 5060 at 0410, local music with station identification. All these loggings by G.B.

● HONDURAS

La Voz Evangelica, Tegucigalpa, on 4820 at 0417, OM in English presenting a religious

programme. G. Bennett also mentions this station, having logged it on several occasions during the 0300-0430 English programme.

● PERU

Radio Atlantida, Iquitos, on 4790 at 0530, local style pop music. G.B. finds this station interesting in that it features hardly any typical Andean music of the type regularly heard when tuned to R. Andina, Chinchaycocha or Libertad.

Radio Andina, Huancayo, on 4996 at 0434, YL with song in Spanish, OM announcer, local style music. The schedule is from 0100 to 0600 but has been reported closing as early as 0450; the power is 1kW.

Radio Eco, Iquitos, on 5010 at 0340, dance music Latin American style, YL with songs in Spanish. The Schedule of this one is from 1100 to 0500 (Sundays 0400) but often operates around the clock and sometimes identifies as "Radio El Sol"; the power is 1kW.

● VENEZUELA

Radio Universidad, Merida, on 3395 at 0221, OM with songs in Spanish, guitar music. Schedule is from 1000 to 0400 and the power is 1kW.

Radio Bolivar, Ciudad Bolivar, on 4770 at 0240, OM with songs in Spanish, local style dance music. Schedule is from 1000 to 0400 and the power is 1kW.

Radio Difusora Venezuela, Caracas, on 4890 at 0250, OM with identification, songs in Spanish. The schedule is from 1000 to 0400, the power is 5kW and the identification is given as "La Estacion de la Alegria".

Ecos del Torbes, San Cristobal, on 4980 at 0318, Latin American dance music, announcements and jingles in Spanish. Schedule is from 1000 to 0400 and the power is 10kW, making this (and the three that follow) the easiest of Venezuelans to log.

Radio Juventud, Barquisimeto, on 4900 at 0301, OM with announcements in Spanish, local style music. Schedule is from 1000 to 0400 and the power is 10kW.

Radio Rumbos, Caracas, on 4970 at 0535, local style recorded pops, announcements, jingles. Schedule is from 0830 to 0400 and the power is 10kW.

Radio Continente, Caracas, on 5030 at 0340, Latin American dance music, identification at 0345 as "Radio Reloj Continente". Schedule is from 1000 to 0500 and the power is 10kW.

● COLOMBIA

Radio Colosal, Neiva, on 4945 at 0312, OM announcer, ballads in Spanish, light music. Schedule is on a 24-hour basis and the power is 2.5kW.

Radio Sata Fe, Bogota, on 4965 at 0316, OM with songs in Spanish, guitar music. Schedule is also around the clock and the power is also 2.5kW.

● BRAZIL

Radio Tabajara, Joao Pessoa, on 4795 at 2040, excited OM with an excited commentary on an exciting futebol match! Schedule is from 0800 to 0400 and the power is an exciting 2kW.

● DOMINICAN REPUBLIC

Radio Norte, Santiago, on a measured 4807 at 2113, songs in Spanish, pops in local style. Schedule is continuous and the power is 1kW.

MEDIUM WAVE POCKET R

By R. A. Penfold

Covers standard medium wave band
after construction

Although perhaps not as numerous as they once were, pocket radio sets still seem to be quite prevalent. Ready-made receivers of this type are usually electrically much the same as larger sets, with the small physical size being accomplished by means of special miniature components and almost unbelievably compact layouts. It is virtually impossible for the amateur constructor to emulate these sets, and so home-made pocket receivers tend to use circuitry which is as simple as possible, and this often results in a comparatively poor performance.

However, such need not be the case and with the integrated circuits that are now available it would seem to be quite feasible to produce a simple high performance medium wave receiver circuit. Bearing this in mind, the radio which forms the subject of this article was designed.

Only two semiconductor devices, both integrated circuits, are used in the set, which has outside dimensions of approximately 114 by 76 by 36mm. excluding control knobs. The sensitivity of the receiver is good, and even during daylight hours it is possible to receive quite a number of stations on the prototype. The audio quality is also surprisingly good, the main limitation on quality and volume being the comparatively poor performance of the miniature speaker which has to be used. There is only one tuned circuit and so the selectivity is not as high as would be given with a more complex superhet design.

The receiver is completely self-contained, with an internal ferrite rod aerial and 9 volt battery.

THE CIRCUIT

An obvious choice for the r.f. and detector circuitry is the well-known ZN414 i.c., and it is indeed this device which is used here. The popular LM380N i.c. provides the a.f. amplification for the receiver. The complete circuit diagram appears in Fig. 1.

Basically, the ZN414 is a high gain r.f. amplifier which has a high input impedance. This enables the ferrite aerial coil, L1, and tuning capacitor, VC1, to be coupled direct into the input of the i.c. without employing the usual low impedance win-

ding on the aerial. C1 is an earth return capacitor and R2 is a bias resistor. The i.c. includes a transistor detector and a.g.c. circuitry. The audio output is developed across R3, with C3 acting as an r.f. filter capacitor. The i.c. requires a supply potential of about 1.3 volts, and this is derived from the main 9 volt supply by means of the voltage divider circuit consisting of R1, R4 and R5. R5 is adjusted to provide the correct supply voltage.

If instability is to be avoided it is essential that no significant r.f. signal is allowed to reach the audio amplifier section. Therefore, additional r.f. filtering is provided at the output of IC1 in the form of R6 and C5. C4 provides d.c. blocking.

The LM380N i.c. is ideal for the present application since it requires very few discrete components.

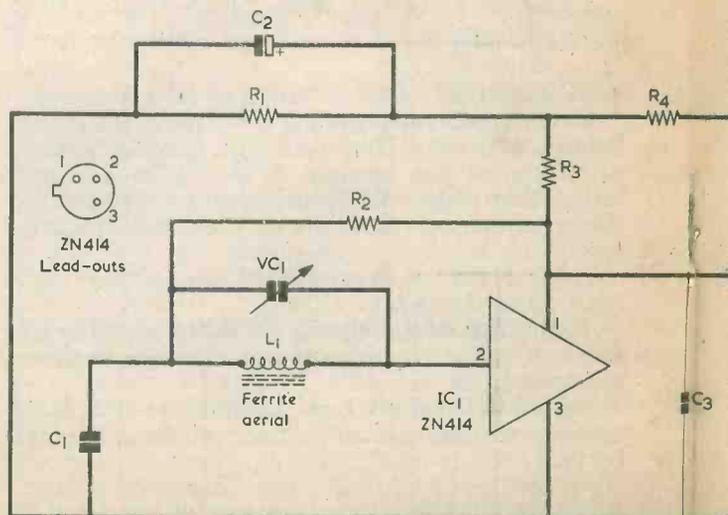


Fig. 1. The circuit of the medium wave pocket radio receiver. Requires few discrete components.

MEDIUM WAVE POCKET RADIO

By R. A. Penfold

Covers standard medium wave band and requires no alignment after construction.

us as they once
n to be quite
f this type are
e as larger sets,
accomplished by
nponents and
ts. It is virtual-
uctor to emulate
t receivers tend
as possible, and
ly poor perfor-

se and with the
ailable it would
e a simple high
r circuit. Bear-
rms the subject

ices, both in-
which has out-
114 by 76 by
ne sensitivity of
during daylight
te a number of
o quality is also
tion on quality
ly poor perfor-
ch has to be us-
uit and so the
be given with a

contained, with
9 volt battery.

nd detector cir-
c., and it is in-
e. The popular
ification for the
ram appears in

in r.f. amplifier
e. This enables
ning capacitor,
input of the i.c.
mpedance win-

ding on the aerial. C1 is an earth return capacitor and R2 is a bias resistor. The i.c. includes a transistor detector and a.g.c. circuitry. The audio output is developed across R3, with C3 acting as an r.f. filter capacitor. The i.c. requires a supply potential of about 1.3 volts, and this is derived from the main 9 volt supply by means of the voltage divider circuit consisting of R1, R4 and R5. R5 is adjusted to provide the correct supply voltage.

If instability is to be avoided it is essential that no significant r.f. signal is allowed to reach the audio amplifier section. Therefore, additional r.f. filtering is provided at the output of IC1 in the form of R6 and C5. C4 provides d.c. blocking.

The LM380N i.c. is ideal for the present application since it requires very few discrete components.

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

- R1 680 Ω
- R2 100k Ω
- R3 820 Ω
- R4 2.7k Ω
- R5 2.2k Ω pre-set potentiometer horizontal skeleton
- R6 560 Ω
- VR1 5k Ω potentiometer, log, w text)


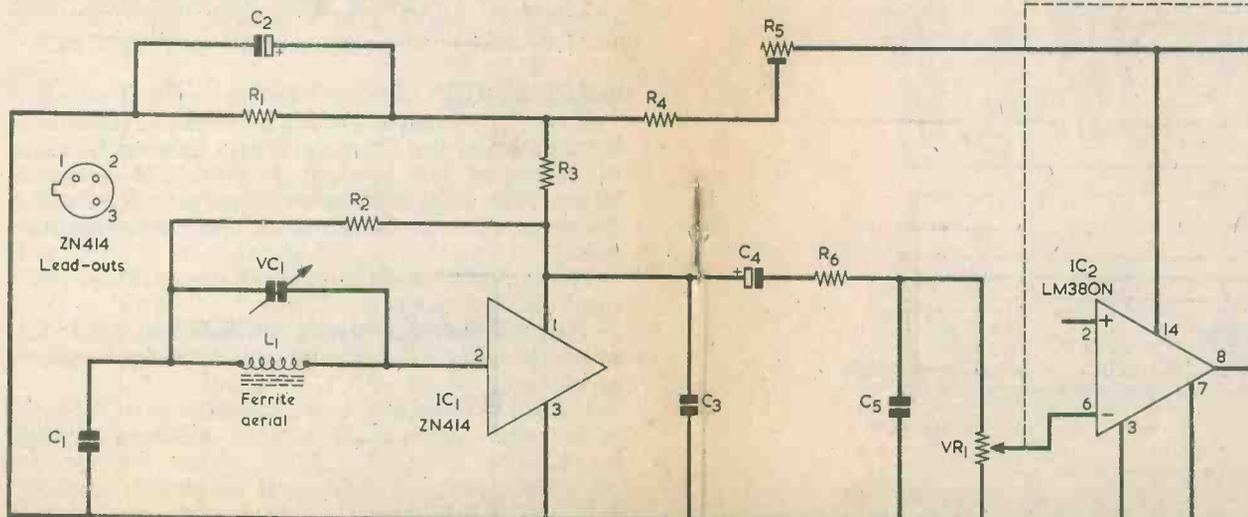


Fig. 1. The circuit of the medium wave pocket radio. Due to the use of two integrated circuits this requires few discrete components

RADIO

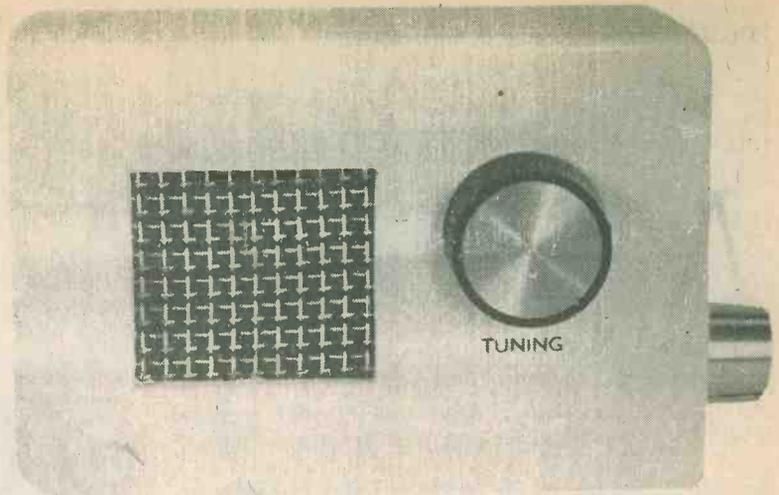

Simplicity is the keynote of this little radio. The two controls are for tuning and volume/on-off

band and requires no alignment
struction.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5%)

- R1 680 Ω
- R2 100k Ω
- R3 820 Ω
- R4 2.7k Ω
- R5 2.2k Ω pre-set potentiometer, 0.1 watt, horizontal skeleton
- R6 560 Ω
- VR1 5k Ω potentiometer, log, with switch S1 (see text)

Capacitors

- C1 0.01 μ F type C280 (Mullard)
- C2 6.8 μ F electrolytic, 10 V. Wkg.
- C3 0.1 μ F type C280 (Mullard)
- C4 1 μ F electrolytic, 10 V. Wkg.
- C5 0.047 μ F type C280 (Mullard)
- C6 47 μ F electrolytic, 10 V. Wkg.
- C7 220 μ F electrolytic, 10 V. Wkg.
- VC1 20-250pF mica trimmer (see text)

Semiconductors

- IC1 ZN414
- IC2 LM380N

Speaker


- LS1 8 Ω speaker, 45mm. (see text)

Switch

- S1 s.p.s.t., part of VR1

Miscellaneous

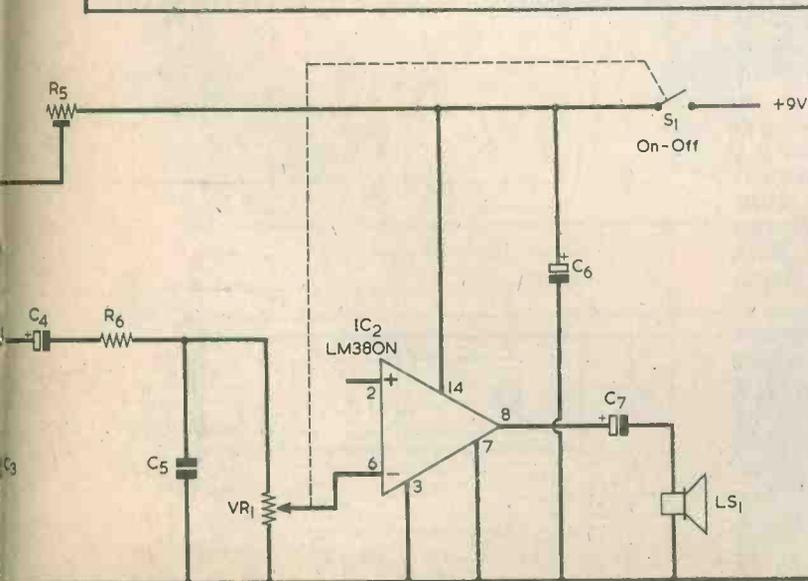- Plastic case type PB1
- Veroboard, 0.1 in. matrix
- Trimmer converter (see text)
- Ferrite rod, 110 x 8mm. diameter
- 28 s.w.g. enamelled copper wire
- PP3 battery
- Battery connector
- 2 control knobs
- 14 pin i.c. holder (optional)
- Speaker fabric
- 18 s.w.g. aluminium
- Insulation tape, wire, etc.




radio. Due to the use of two integrated circuits this re-
discrete components

In fact, the only external component which is used is the output d.c. blocking capacitor, C7. There is no need to use an input d.c. blocking capacitor, and the inverting input of the device connects direct to the slider of the volume control, VR1. The LM380N also has a non-inverting input, but this is simply ignored.

The voltage gain of the LM380N is fixed at a typical figure of 50 times, and with the ZN414 providing an audio output level of about 30mV r.m.s., this is just about the required level.

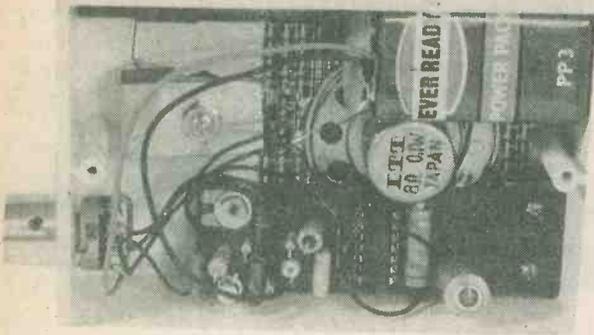C2 and C6 are supply decoupling capacitors and S1 is the on-off switch. The latter is ganged with the volume control. The quiescent current consumption of the receiver is about 7mA, but the output stage is a Class B type and at high volume levels the consumption can rise to some 25mA.



The components fit comfortably inside the small plastic case

COMPONENTS

Most of the components are standard readily available items, but some are special miniature types. VR1/S1 is a "Japanese Volume Control" which is available under this description from Maplin Electronic Supplies. The miniature 45mm. diameter 8Ω speaker is available from the same source, as also is the plastic case type PB1.

VC1 is not an ordinary variable capacitor, and it is actually a modified trimmer. The trimmer is a type TP4 (20-250pF) which has its adjustment screw replaced by a trimmer converter. The latter is a cylinder of 1/4 in. diameter, on which a knob can be fitted, terminated in a threaded section. Both this and the trimmer are available from Home Radio.

The resistors and capacitors are all miniature types, and C280 capacitors should be used where specified. The pre-set potentiometer, R5, is a miniature component having 0.2in. spacing between track tags and 0.4in. spacing between track and slider tags. The low value electrolytic capacitors C2 and C4 are specified as 10 V. Wkg., but in practice it may be difficult to obtain them in this voltage. It is quite in order to use capacitors with a high working voltage such as 40 or even 63 volts. Mullard miniature electrolytic capacitors will be found suitable.

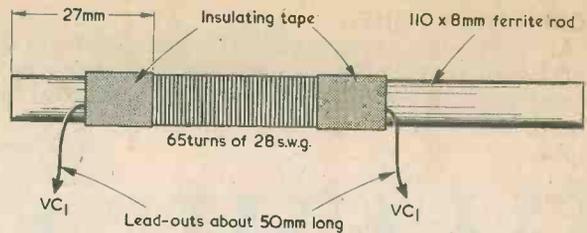


Fig. 2. The ferrite aerial coil is close-wound with enamelled copper wire.

FERRITE AERIAL

The ferrite aerial is home constructed, and the coil is wound on a 110 by 8mm. ferrite rod using 28 s.w.g. enamelled copper wire. Details are provided in Fig 2.

It is unlikely that a rod of suitable length will be available, and it will be necessary to break a 110mm. length from a longer rod. Ferrite is very hard and brittle, and it is not practicable to cut right through the rod using an ordinary hacksaw. A V-cut should be filed all round the rod at the point where it is desired to break it, and it may then be tapped against the edge of the bench.

The winding starts 27mm. from one end of the rod, and the lead-out wire is held in place by a band of insulating tape. The coil consists of 65 turns of wire close-wound in a single layer. Due to the relatively thick wire that is used it is easy to make a neat job of the coil. When the winding has been completed, the second lead-out wire is taped in place.

MOUNTING BRACKET

VC1 cannot be mounted in the usual manner because the mounting bush and nut are situated at the rear of the component. A mounting bracket is constructed from 18 s.w.g. aluminium, and details of this are shown in Fig. 3. The aluminium is bent along the lines indicated to produce a U-shaped bracket. VC1 is mounted on the larger of the two holes, and the smaller one is used to enable the bracket to be bolted to the front panel of the set by means of a short M3 or 6BA countersunk screw.

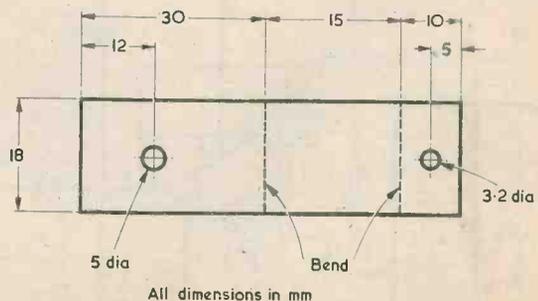


Fig. 3. A simple bracket is required for mounting the tuning capacitor, VC1. This has the dimensions shown here.


COMPONENT PANEL

All the small components are assembled on a Veroboard panel of 0.1in. matrix. The componet layout and other details of this panel are shown in Fig. 3. Start by cutting out a panel which has 9 copper strips by 32 holes, using a hacksaw. Then the two mounting holes are drilled to take small woodscrews. Next, the breaks in the copper strips are made, making quite sure that none of these are accidentally overlooked. After this, the components and link wires are soldered into position. In the prototype a 14 pin i.c. holder was soldered to the Veroboard and the LM380N fitted into this later. Alternatively, the LM380N can be soldered directly to the board.

Flexible insulated leads leave the board for connection to VR1 (at points A, B and C), S1, VC1 and the speaker. It is advisable to make these a little longer than will eventually be required and cut them to length when the connections are later made to the external components. A further lead from the board connects to the negative battery clip.

CASE LAYOUT

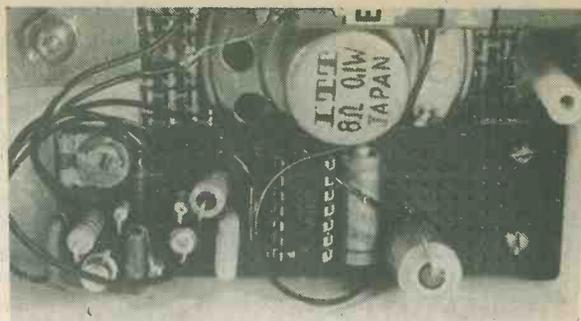Reference to the accompanying photographs should help to clarify the general layout of the receiver inside the case. VR1/S1 is mounted towards the bottom of the right hand side panel, and it requires a 7mm. diameter mounting hole. VC1 is mounted on the front panel towards the right hand side, slightly above centre. The speaker is situated to the left of this, and it requires a cut-



The Veroboard panel fits below the speaker and is mounted by means of two small woodscrews

out which measures about 36 by 40mm. This can be made with either a fretsaw or a miniature round file. A piece of speaker fret or material is glued in position behind the cut-out, and then the speaker is glued onto this. A good quality adhesive must be used, and care must be taken to apply only a conservative amount to the rim of the speaker, ensuring that none gets on to the speaker cone or surround. The speaker should be positioned such that there is space above its magnet for the PP3 battery and space below it for the Veroboard panel.

The ferrite aerial is glued in place at the top and towards the front of the case. A high quality gap filling adhesive must be used here, and the author employed an epoxy resin. The coil is to the right, i.e. at the VC1 end.

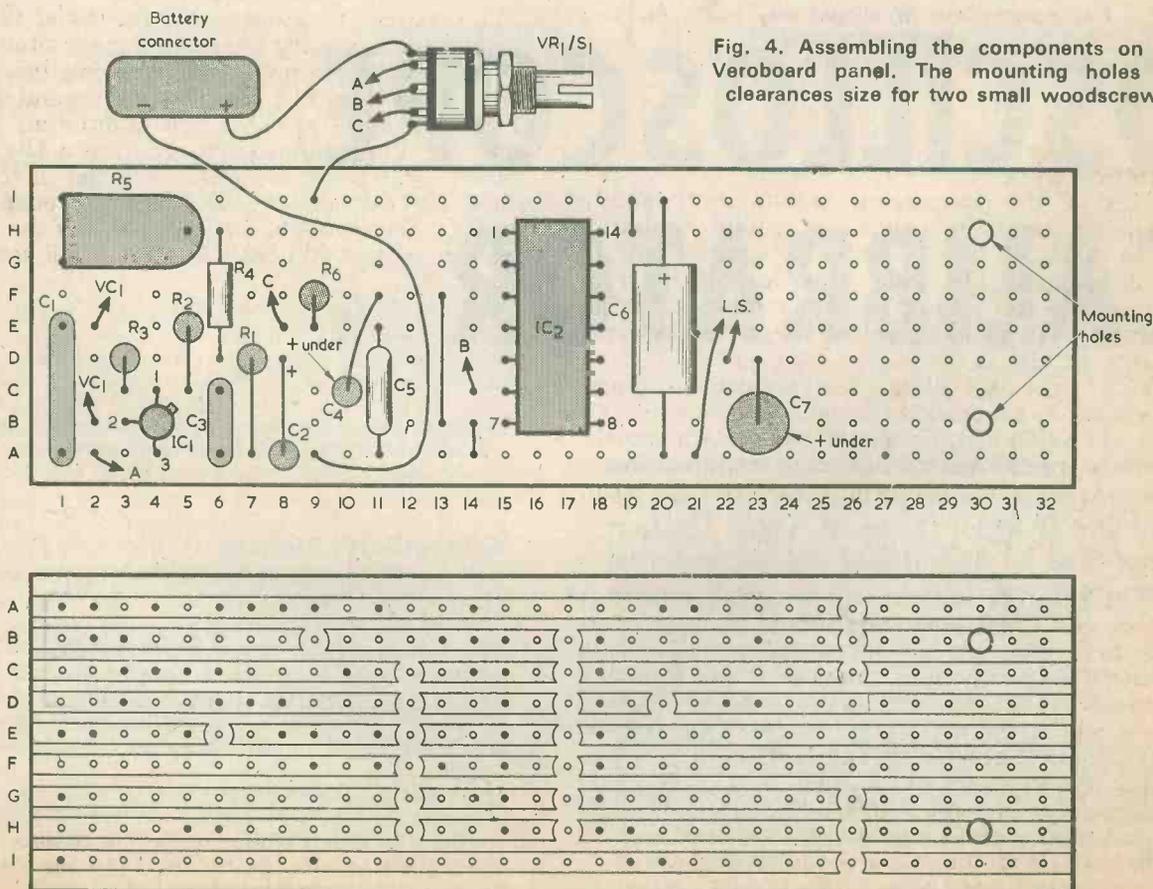


Fig. 4. Assembling the components on the Veroboard panel. The mounting holes are clearances size for two small woodscrews.

The component panel fits into the bottom of the case, and it is mounted on a small block of wood which measures approximately 27 by 12 by 6mm. using two small woodscrews. The block of wood is glued to the inside face of the front panel at the bottom left hand corner, as viewed from the front of the case. The component panel is not finally mounted until it has been wired up to the remainder of the set. If there is any risk of the connections under the Veroboard panel touching the speaker frame apply insulating tape to the frame at the appropriate place. At this stage the two lead-outs of the ferrite aerial coil are soldered to the tags of VC1.

There is space for the battery in the top left hand corner of the case, again as viewed from the front. It should be placed as far to the left as possible, since it will otherwise have a slight screening effect on the aerial coil, and this would result in a loss of performance. A piece of sponge rubber or fabric is fitted between the battery and the speaker frame and inside front of the case, whereupon the battery is held in place when the back of the case is screwed on.

ADJUSTMENT

Before switching on the completed receiver, thoroughly check the wiring for errors and set R5 at about half its maximum resistance. The set requires no alignment, and so it should work properly

immediately after switching on. If a multimeter having a sensitivity of 10k Ω per volt or more on its voltage ranges is available, this can be set to the 0.5 volt range (or a similar low voltage range) and then used to measure the voltage between the negative supply rail and the junction of R1 and R3. R5 is then adjusted to produce a reading of 1.3 volts in the meter.

If a multimeter is not available, perfectly adequate results should be obtained if R5 is simply left at its central setting. Do not adjust R5 up to or near the fully anticlockwise setting if a meter is not used as this could inadvertently cause too high a voltage to be applied to the ZN414.

The tuning of the set is broad, and there should be no difficulty in tuning in stations accurately even when these are at the high frequency end of the band. One reason for this is the fairly wide bandwidth of the set, but it is mainly due to the unconventional tuning capacitor. Whereas the capacitance swing of an ordinary tuning capacitor is covered by a 180 degree turn of the spindle, about three complete turns are required with the present capacitor.

Subminiature speakers are not very efficient and they are not capable of handling more than very modest output powers. This means that the volume from any set of this type is not very high, although it is perfectly adequate for most purposes. ■

VARIABLE OSCILLOSCOPE CALIBRATOR

By N. R. Wilson

This oscilloscope voltage calibration generator can have its output level set for any value from 1 to 5 volts. Output amplitude is monitored by an external testmeter switched to an appropriate voltage range.


Home-constructed oscilloscope voltage calibration generators are not normally complicated items of equipment. Frequently, they employ a multivibrator whose output is fed into a clipping circuit given by a zener diode or a pair of silicon diodes connected back to back. The generator to be described is basically of this simple nature, but it has the unusual feature that

its peak-to-peak output amplitude is continuously variable between 1 and 5 volts and can be monitored by an external testmeter switched to a suitable d.c. volts range.

CIRCUIT OPERATION

The calibration generator circuit appears in the accompanying diagram, in which the multivibrator consists of a 555 timer i.e. in a standard configuration. This runs at a frequency of approximately 350Hz. Its output is not a true square wave because C1 has to charge via R1 and R2 in series and to discharge via R2 on its own. As a result, the positive part of the output waveform at pin 3 is slightly longer than the negative section.

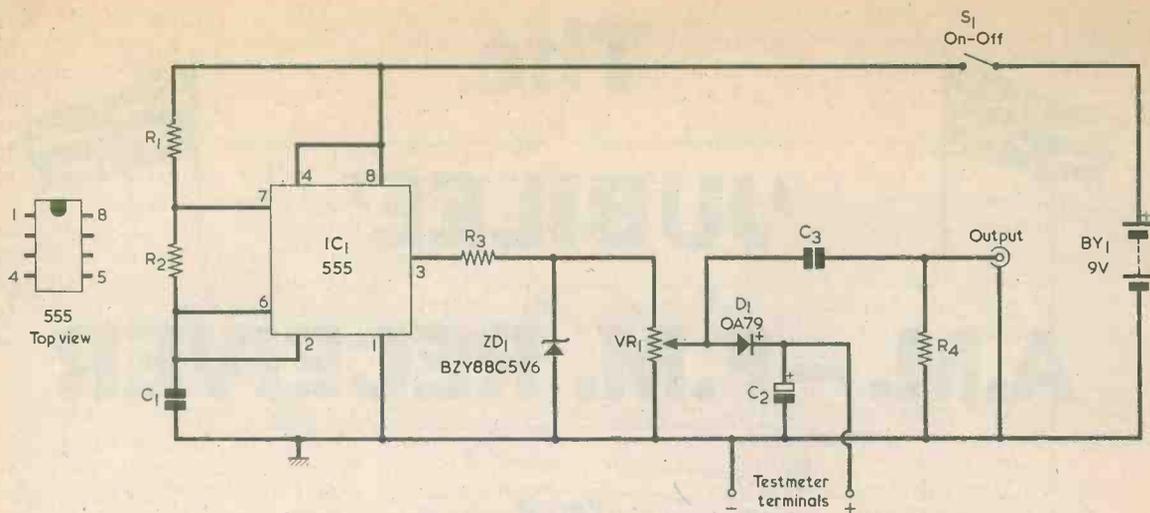The output couples to the zener diode ZD1 via R3. The output of a 555 does not rise close to the positive rail when it is high, and it is usually about 1.5 volts below that rail in this condition. In consequence about 12mA flows in R3 when the 555 output is high.



The circuit of the oscilloscope voltage calibration generator. The output is continuously variable by means of VR1, and its amplitude is measured by a voltmeter connected to the testmeter terminals

Resistors

(All fixed values $\frac{1}{2}$ watt 10%)

- R1 10k Ω
- R2 100k Ω
- R3 150 Ω
- R4 470k Ω
- VR1 10k Ω potentiometer, linear

Capacitors

- C1 0.022 μ F polyester
- C2 10 μ F electrolytic, 10 V. Wkg.
- C3 0.47 μ F polyester

Semiconductors

- IC1 555
- ZD1 BZY88C5V6
- D1 OA79

COMPONENTS

Switch

- S1 s.p.s.t. toggle

Battery

- BY1 9 volt battery

Miscellaneous

- Case (see text)
- Battery connector
- Control knob
- Output socket (see text)
- Insulated terminal, red
- Insulated terminal, black

This current takes the slope resistance of the zener diode down to about 10 Ω , ensuring hard clipping and a low impedance for the positive part of the waveform. When the 555 output goes low its pin 3 is very close to the potential of the negative rail, with a low output impedance. The impedance for the negative part of the waveform is virtually that of R3.

The voltage across the zener diode appears across VR1 and a proportion is then tapped off by this potentiometer and applied by way of C3 to the output socket. R4 ensures that the output waveform is approximately symmetrical about the negative supply rail.

VOLTAGE MONITOR

The voltage tapped off by the slider of VR1 is applied to the simple half-wave rectifier circuit comprising D1 and C2. An external testmeter switched to a volts range is connected across C2 and will give a reading slightly lower than the peak-to-peak amplitude of the generator output signal. If the meter were a relatively insensitive type having a resistance of 1k Ω per volt it would present a resistance of 10k Ω if it were switched to, say, a 0-10 volt range. C2 has a value of 10 μ F and the time constant of 10 μ F and 10k Ω

is 0.1 second, which is considerably longer than the length of each cycle in the signal. C2 can, therefore, be assumed to charge almost fully to the peak value of the signal. The time constant with more sensitive meters will naturally be longer. If VR1 is quickly adjusted from a high setting to a low setting the meter may take a short time to produce the new reading as C2 discharges into it.

To be precise, the reading indicated by the testmeter is the peak-to-peak voltage less about 0.1 volt forward voltage drop in diode D1. For accurate calibration, VR1 should therefore be set for a voltmeter reading 0.1 volt below the desired output voltage.

The current drawn from the 9 volt battery is 10mA. Any type of 9 volt battery, from PP3 to PP9, would be suitable. The output socket may be a coaxial type or a jack socket, as preferred.

The circuit can be assembled in any small case, which may be either metal or plastic. If the case is metal it is made common with the negative supply rail, as indicated by the chassis symbol in the diagram. This symbol is ignored if the case is plastic. Mounted on the front panel are VR1, S1, the output socket and the two terminals for the testmeter. ■



The 'JUBILEE'



A.M.—F.M. RECEIVER

Part 2

By Sir Douglas Hall, K.C.M.G.


Constructional details are completed and the simple process of setting up is described.

In the last month's issue we examined the circuit of this receiver and then commenced its construction. We now continue with this, after which we deal with the process of setting up and making a case. References will be made to Figs. 1, 2 and 3; these were published in Part 1.

SPEAKER PANEL

We turn next to Fig. 4, which shows the back of the speaker panel. Cut out piece of $\frac{1}{4}$ in. plywood to the dimensions shown. Also to be cut out is a smaller piece of plywood which functions as a battery platform. When all the holes in the main plywood panel have been cut out, the battery platform is secured to the bottom right of the panel, at right angles; employing thin wood screws.

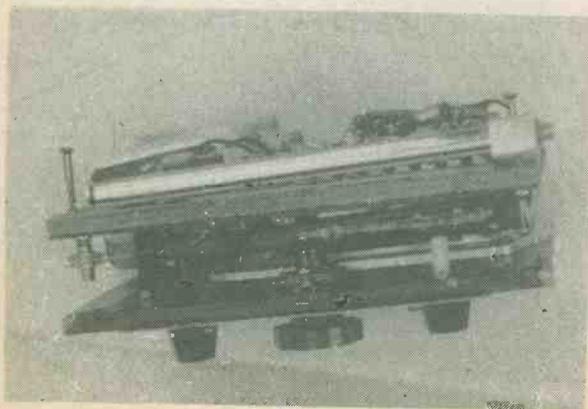Cut out the three holes at the top and drill hole G. The central hole takes the epicyclic ball drive



Looking down at the receiver assembly from the top

flange, with its spindle pointing away from the reader and its body on the reader's side of the panel. Temporarily place the drive in position and use it to mark out a 6BA clear hole for a screw which will secure its anchor lug. Drill the hole.

The left hand edge of the speaker is flush with the left hand side of the panel, and its lower edge is similarly flush with the bottom of the panel. Cut out a suitable speaker aperture and secure the speaker with four countersunk bolts, the nuts being on the same side as the speaker. Note that the heat clip of TR5 is secured under one of the speaker mounting nuts, whereupon the speaker frame acts as a heat sink for this transistor.

Cover the upper front of the panel, down to the speaker aperture, with Fablon of a suitable colour.

Next, cut out a piece of s.r.b.p. 4 by $2\frac{1}{2}$ in. and prepare a hole in this which will pass tightly over the speaker magnet. As was mentioned last month, the speaker obtained should be similar to that employed by the author, and panel dimensions are modified to suit if there are any serious discrepancies. Cut out a 5 way and a 6 way tagstrip from the tagboard, and secure these to the s.r.b.p. panel as shown in Fig. 4, using small screws passing through the centres of the end tags. Make certain that none of the screws or their nuts can touch the frame of the speaker and, if necessary, apply insulating tape here. The panel is passed over the speaker magnet and secured with adhesive.

Fit and wire up the components as shown. The leads identified as H, J, K and L will connect, later, to similarly identified points in Fig. 3. Fit the epicyclic drive in position, and pass a 2 in. 4BA countersunk bolt through hole G in Fig. 4, with its head underneath. Secure it with a nut, then place another nut over the bolt. Assemble the panel of Fig. 3 to that of Fig. 4 by having the 4BA bolt pass through its hole G and by inserting the spindle of VC2 into the epicyclic drive. Tighten up the drive grub screws and fit a further nut over the 4BA screw. Tighten up the two nuts such that the panel

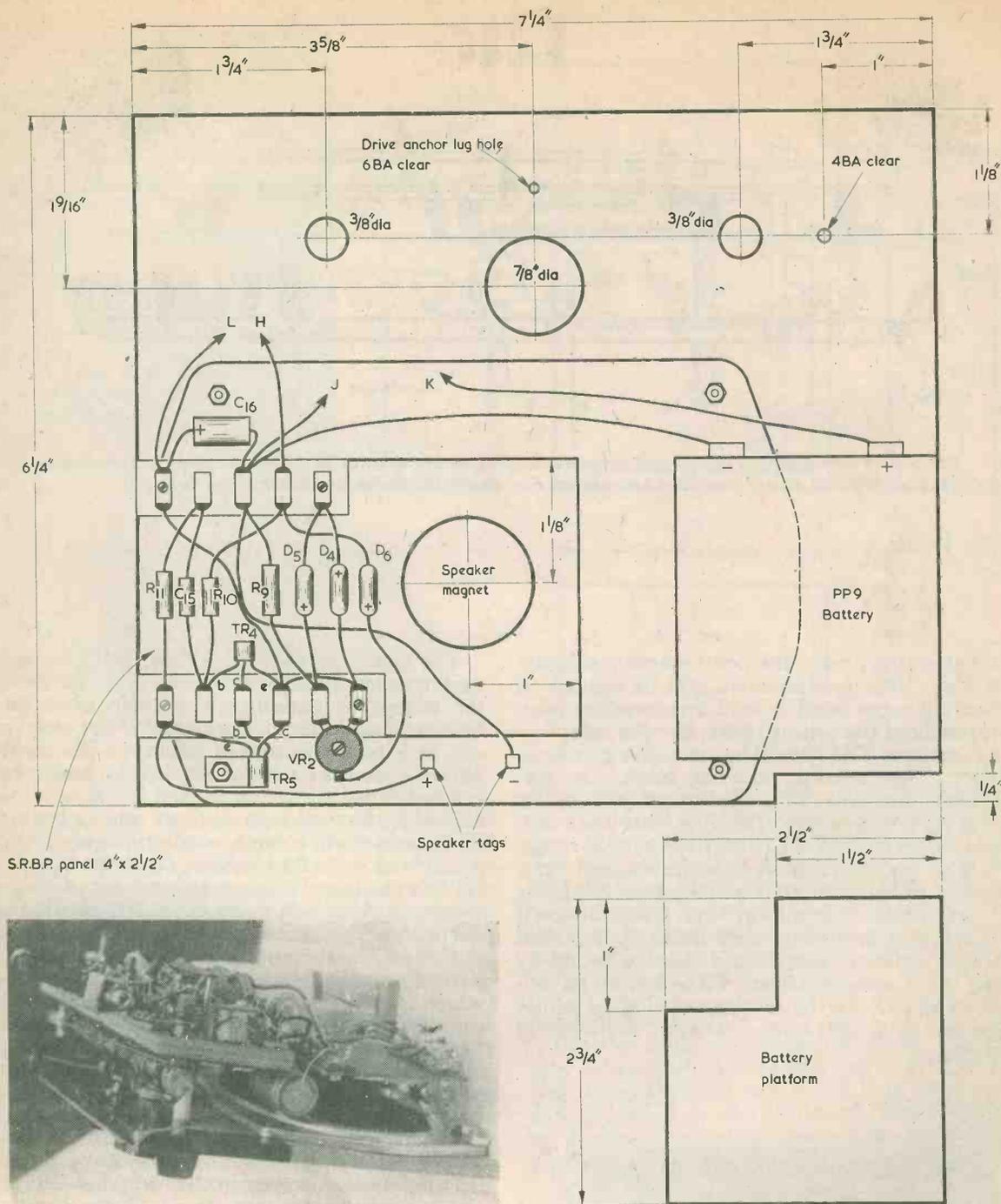


Fig. 4. Dimensions and wiring on the speaker panel. The s.r.b.p. panel fits over the speaker magnet. TR5 has its heat clip secured under one of the speaker mounting nuts.

of Fig. 3 is parallel with the panel of Fig. 4. The two panels are thus secured together by the 4BA bolt and the epicyclic drive and spindle of VC2, as is illustrated in the top view of Fig. 5. Complete the connections H, J, K and L.

SETTING UP

The receiver may now have VR2 set up, and this should be done with a new battery and no signal input. The slider of VR2 is turned fully anticlockwise, as shown in Fig. 4. Insert a meter,

switched initially to a high current range, in series with the positive battery connection and switch the receiver on. If the initial reading indicates that it is safe to do so, switch off, select a range that will enable a clear reading of 12mA to be taken, and switch on again. Slowly advance VR2 for a reading of 12mA. Repeat this procedure once more after the battery has been in use for about 20 hours. No further adjustment to VR2 is required.

For the most sensitive reception of stations on the medium and long wave bands VR1 should be

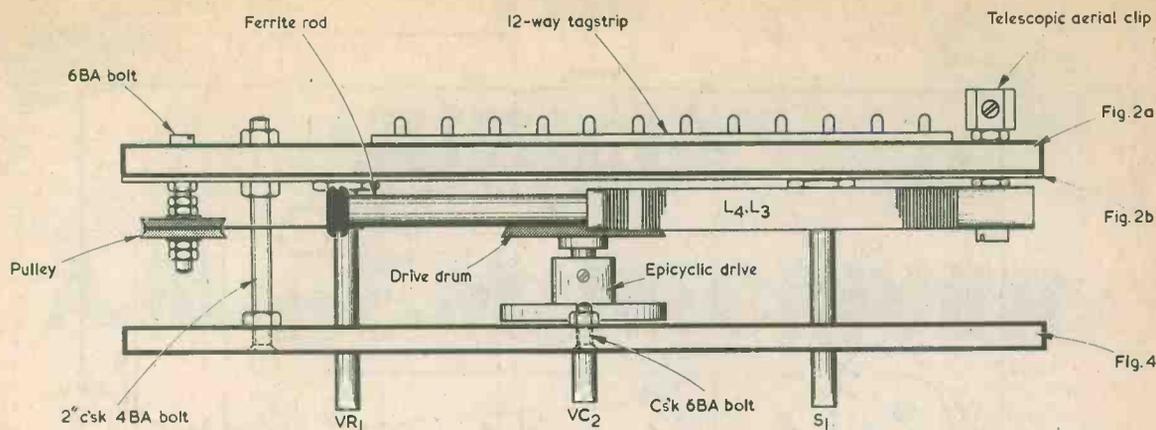


Fig. 5. Top view showing the disposition of parts between the speaker panel and the panel on which the r.f. and detector components are assembled. For simplicity, these components are omitted.

set just at, or very near, the point where oscillation starts. Very little readjustment will be needed on the medium wave band to hold this sensitive position throughout the tuning range. For the reception of v.h.f. stations VR1 should be set to give gentle oscillation. This setting will be back, i.e. anticlockwise, somewhat from the critical position for medium and long waves. In order that the v.h.f. stations appear correctly within the tuning range, set VC2 to near maximum capacitance and tune, by means of an insulated screwdriver adjusting VC1, until Radio 2, or a local v.h.f. transmission if this is lower in frequency than Radio 2, is picked up. Other transmissions should then be found by turning VC2 anticlockwise. VR1 should be adjusted so as to keep the receiver oscillating gently — denoted by a light hiss — as v.h.f. stations are tuned in.


The components, as specified, will allow a good performance to be given. If, however, the constructor wishes to experiment a little after he has become used to the performance of the receiver, he can look for an optimum value for R6. As is apparent from the circuit of Fig. 1, this resistor causes a small forward current to flow in D3, and it only affects performance on medium and long waves. If R6 has too small a value, oscillation may prove impossible at some frequencies. If, on the other hand, R6 has too large a value, adjustment of VR1 may cause a sudden and noisy burst into oscillation. In particular, R6 settles the constancy of the reaction setting on the medium wave band. It can be temporarily replaced by a 47kΩ pre-set potentiometer which is adjusted for maximum constancy of setting of VR1 for full sensitivity over the whole of the medium wave band. The potentiometer is then removed, the resistance it inserted into circuit is measured, and a fixed resistor of the appropriate value fitted in the R6 position.

If necessary, C7 may have its value varied to ensure full coverage of the medium wave band, and C8 may need changing in the same way for proper coverage of the long wave band. These changes will most probably be required if the ferrite rod is other than orange grade.



RECEIVER CASE

A case for the receiver can be made as illustrated in Fig. 6, which shows the front, sides, top and bottom before assembly. Note that the dimensions defining case height, width and depth are tentative only, as they assume that the "chassis" has been made exactly to dimensions and can be inserted in the case without clearance. In practice, slightly increase the appropriate dimensions so that the case will take the particular chassis which has been assembled. It may be necessary, also, to modify the depth if the speaker employed differs significantly from that used by the author.

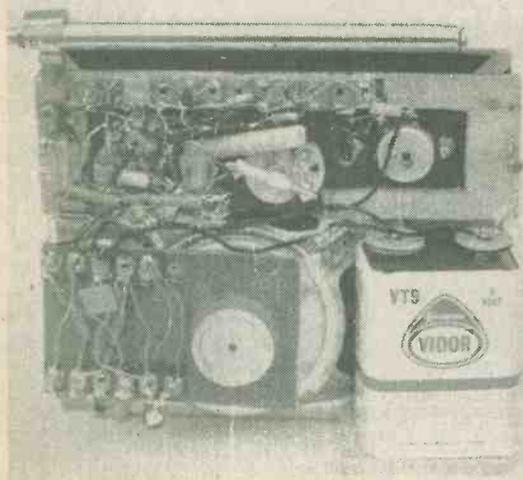The front section has two apertures, one for the controls and one for the speaker. The top, bottom and sides are screwed together, and the front is



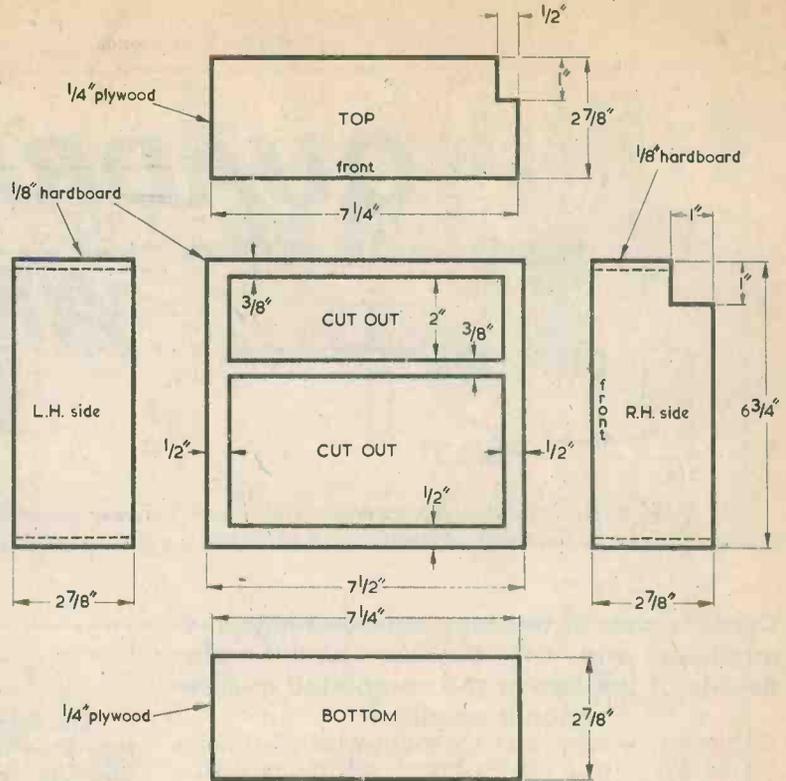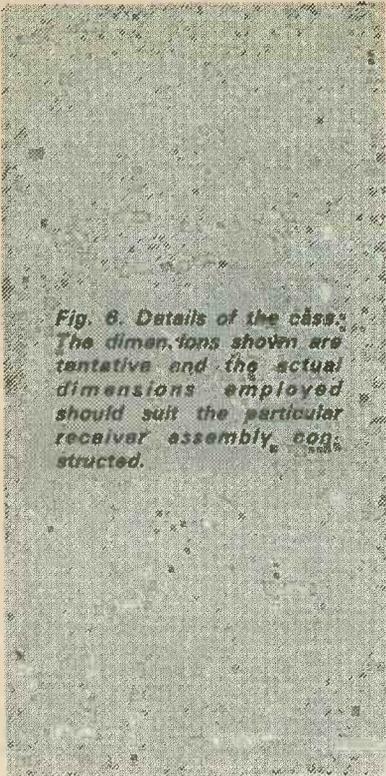Another view of the receiver assembly, as seen from the rear



then screwed to the top and bottom. Note the opening at back right for the telescopic aerial bracket and clip. The case is covered with Fablon of the same type as that already applied to the speaker panel. A rectangular white card with suitable holes may be passed over the spindles and marked up with control functions and a tuning scale. The flange of the tuning drive has two 8BA tapped holes, by means of which a tuning cursor can be attached.

A piece of metal speaker gauze is dropped into place behind the lower front aperture and the receiver is then pushed in from the rear.

The case back consists of a piece of $\frac{1}{8}$ in. pegboard and, working to the dimensions in Fig. 6, measures $6\frac{1}{4}$ by $7\frac{1}{4}$ in. Again, these dimensions may be modified slightly as required in practice. The two woodscrews shown in Fig. 3 as "to be fitted later"

are now screwed into position such that their heads are $\frac{1}{8}$ in. inside the open rear of the case. These ensure that the back will fit in flush at the top. The rear edge of the battery platform should ensure that the back fits flush at the bottom. The back is held in place by two small solder tags screwed to the case top rear and a further tag screwed to the case bottom rear. These are swivelled to press against the pegboard.

BASS RESPONSE

Because of its very high selectivity, the receiver may cause attenuation of the higher audio frequencies when listening to distant long wave stations with the reaction well advanced. This can result in an apparent excess of bass when speech is being reproduced.

Constructors who anticipate listening to such stations can, if they desire, add a bass cut control. The modification required is very simple and is illustrated in Fig. 7. The negative lead of C2 is disconnected from its tag and a $10\mu\text{F}$ electrolytic capacitor inserted between that lead and the tag from which it has been disconnected. The positive lead of the $10\mu\text{F}$ capacitor connects to the negative lead of C2. A small toggle switch short-circuits the $10\mu\text{F}$ capacitor when it is not required and this can be fitted to the back of the receiver close to the added capacitor, being wired to the appropriate tag with a stiff wire. The mounting nut of the switch is unscrewed when the back of the case is removed. Other means of mounting the switch can also be devised.

With the switch open, bass cut takes place due to negative feedback. With the switch closed, full bass is reproduced.

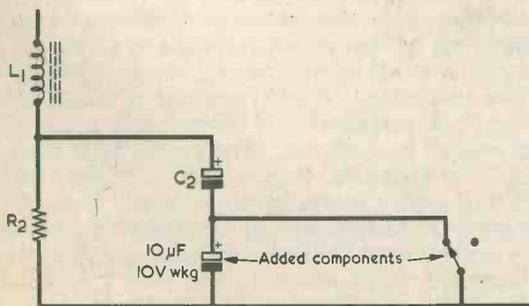


Fig. 7. A modification which offers bass cut when the added switch is opened. This improves reproduction of weak signals on the long wave band.

(Concluded)

SIMPLE QUADRAPHONIC AMPLIFIER

Part 3

(Conclusion)


By R. A. Penfold

Construction of the magnetic cartridge pre-amplifier and SQ decoder circuit, plus details of the use of the completed quadraphonic amplifier.

In the previous two articles we described the construction of the power supply section of the amplifier, then carried on to the power amplifiers and a description of the magnetic cartridge pre-amplifier and SQ decoder circuits. In this concluding article we proceed next to the construction of the board on which are assembled the pre-amplifier and decoder components.

PRE-AMPLIFIER AND DECODER

A single printed circuit board measuring $6\frac{1}{2}$ by $2\frac{1}{2}$ in. holds both the pre-amplifier and decoder circuitry. A full size diagram showing the copper pattern and component layout of this board appears in Fig. 10. This is constructed in the usual fashion. The holes in the board for the MC1312PQ decoder i.c. have the spacing applicable to a quad-in-line package. Should a constructor wish to fit an MC1312P, the hole positioning may be modified for dual-in-line pins. Pin numbering is the same for both versions of the device.

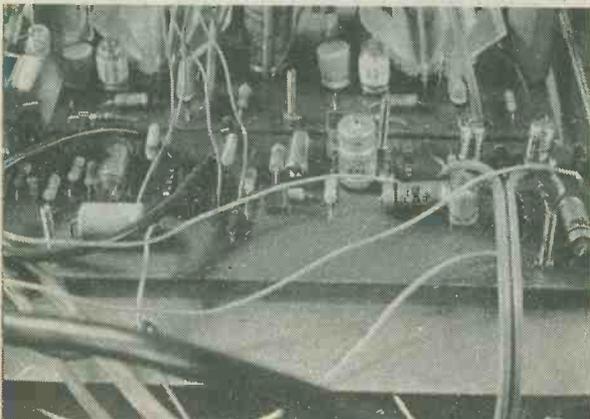

Internal view giving a close-up of the magnetic cartridge pre-amplifier and SQ decoder board

The board is mounted in the same way as the previous two boards, and is positioned on the underside of the chassis as close to the power amplifier board as possible, with IC2 towards the rear of the case. This positioning puts the decoder components well away from T1, and results in a low level of mains hum pick-up. As with the other boards, the present board is mounted by M3 (or 6BA) bolts and nuts, and it takes up its chassis connection by way of the metal spacers on these bolts. The board is not finally mounted until all the external connections to it have been completed.

The outputs from the decoder to the C7 capacitors on VR1 are at low impedance and do not need to be screened. Make sure that these outputs connect to the correct channels and that each of the four outputs carries through to the appropriate speaker socket.

The two C22 capacitors are mounted at SK3 and do not appear on the board. Two screened leads connect the magnetic cartridge inputs to the board, the braiding being connected to chassis at the appropriate points on the boards. The braiding is connected to the earthy contact or contacts of SK3 but, to avoid hum loops, should not connect to chassis at this point on the rear panel. This should raise no problems if a DIN socket is employed. However, with a double phono socket, as was used in the prototype, it is necessary to insulate the earthy metal part of the socket from the rear panel. This can be achieved by means of p.v.c. insulating tape.

The two output leads from the pre-amplifier to S3 are not screened. All the remaining wiring to this switch is screened. The leads from SK1 and SK2 have their braiding earthed to chassis at these sockets, and the braiding is also connected to chassis at the switch end. This chassis connection is to a solder tag secured under the adjacent nut holding the front panel and chassis together. (The resistors R6 are already connected to this tag.) The screened wires from S3 arms to the R'1 and L'1 inputs of the decoder on the board also have their braiding connected to chassis at this solder tag. There is no connection to their braiding at the board end.

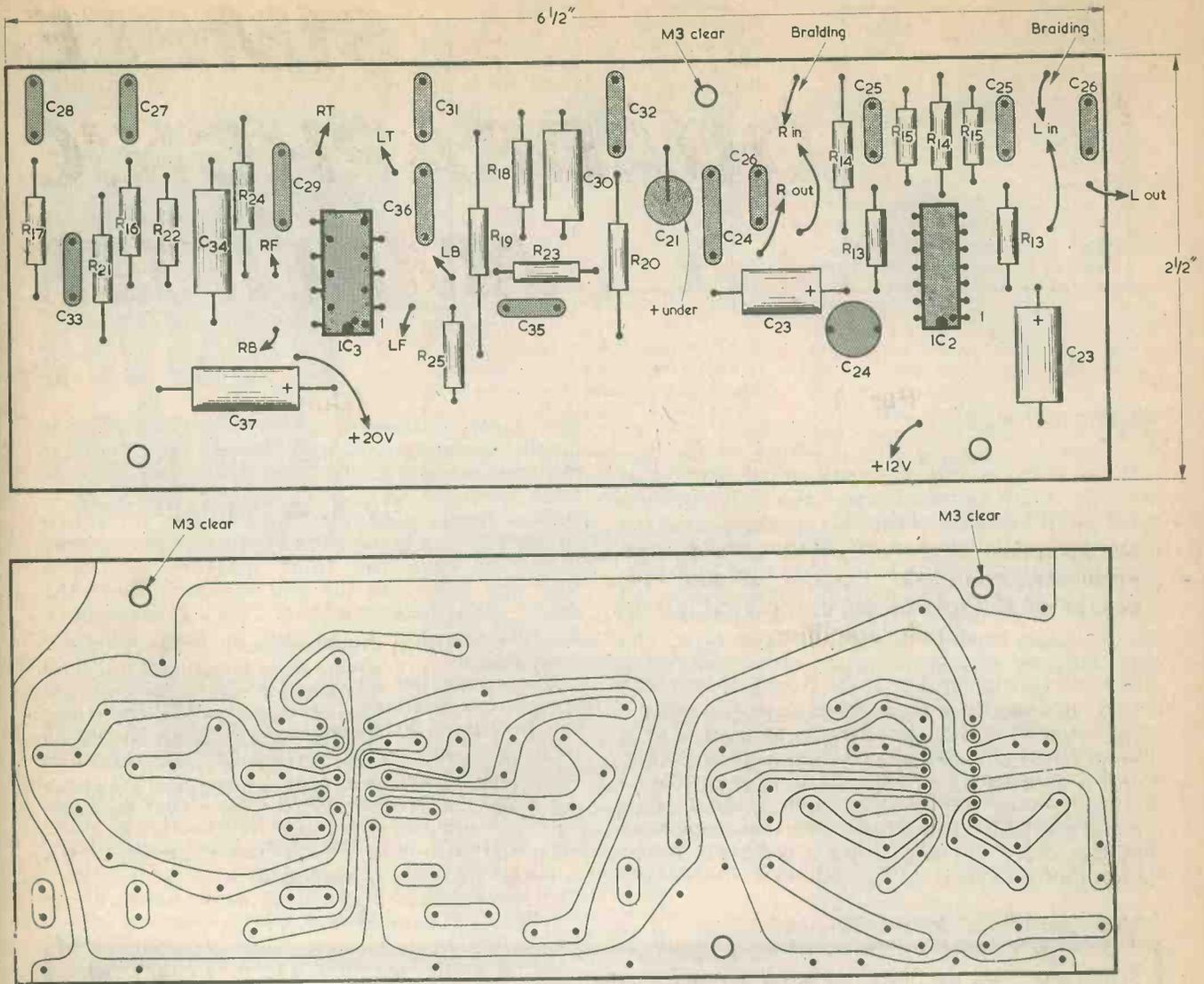


Fig. 10. Illustrating the layout of components and the copper pattern on the pre-amplifier and SQ decoder board

Fig. 11 shows the connections to S3 as seen from the rear. Before making the connections, check the three outer tags which correspond to the centre tag of each pole. With some rotary switches the relative positioning may differ from that shown in the diagram. It will be noted that S3 is a 4-pole 3-way switch with two of the poles unused.

The only two remaining leads to the board are those which carry the 12 volt and 20 volt supplies from the power supply section. These pass over the chassis edge at the mains transformer end. Take great care to ensure that these leads are correctly connected and are not accidentally transposed, as the maximum supply voltage rating for the MC1339P is only 16 volts.

After a final check of the wiring the amplifier is finished and ready for use.



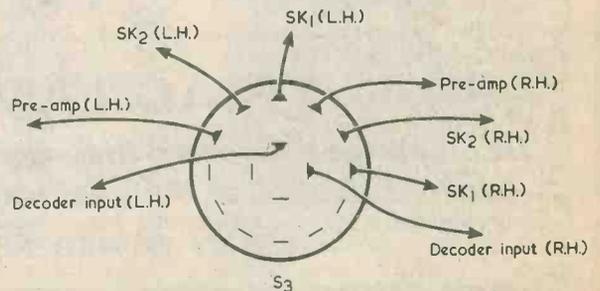


Fig. 11. The connections to input selector switch S3. Details concerning the connections to screened wire braiding are given in the text

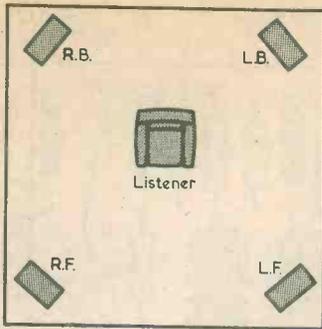

(a)

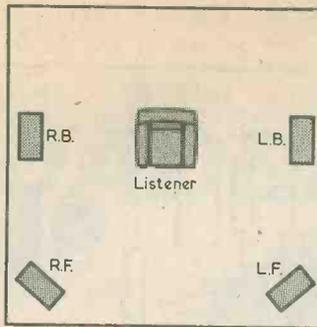

(b)

*Fig. 12(a). The classic speaker arrangement for a quadraphonic system
(b) An effective alternative arrangement for the speakers*

NOTES ON USE

When using simple surround sound systems of the type which employ synthesisers only, and not decoders, the quality of the rear speakers is not too important, and they can be inferior to the front speakers without significantly detracting from performance. With a true quadraphonic system, on the other hand, this is not the case and ideally the four speakers should all be of the same type. The quadraphonic system will work quite well using different types of speaker at the front and rear, but it will not then be giving optimum performance.

Any type of matrix decoder can be used to synthesise a four channel output from a stereo source of two channels only, and the SQ decoder employed in the present amplifier has been found to give quite an effective performance in this respect. If the user of the amplifier prefers to have a stereo source reproduced in a two channel format rather

than have synthesised four channel sound, it is merely necessary to operate S2 so that the two rear channels are muted. The result is perfectly acceptable stereo sound from the front speakers.

The classic placing of the speakers for a four channel system is shown in Fig 12(a). Many people prefer to have the front speakers positioned relatively low, with the rear speakers above the height of the listener's head. This arrangement is, also, fairly easy to set up in most domestic situations.

There are other speaker arrangements which can provide good results, and it is worthwhile experimenting a little here to see if a set-up suiting both the room layout and the listener's personal tastes can be found.

The arrangement shown in Fig. 12(b) is often used, and is one that the author considers very effective. There are, of course, many other possibilities.


(Concluded)

IN NEXT MONTH'S

RADIO & ELECTRONICS CONSTRUCTOR

PORTABLE F.M. RADIO

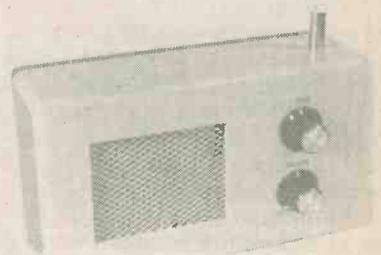- *Easy to construct*
- *5 Transistors*
- *High gain audio amplifier integrated circuit*



TRIAC LAMP DIMMER

Incorporates a standard triac-diac circuit configuration — Offers continuous control of the brightness of an a.c. mains filament bulb


MANY OTHER PRACTICAL ARTICLES

ORDER NOW!

ON SALE 1st SEPTEMBER

PRICE 40p

In your workshop

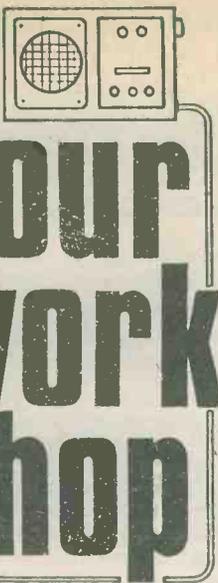

As is their custom every August, Dick and Smithy leave the confines of the Workshop to take a day out together. On this occasion they choose to drive out into the country, well away from the bustle and hurry of their normal urban life.

"Ye gods," called out Dick in alarm, "you aren't going to overtake *that*, are you?"

"Of course I am," replied Smithy confidently, "hang on to your seat."

Ahead of them in the bright August sun raced an enormous articulated lorry, carrying on its back a large mobile crane secured with a network of cables and chains. The entire equipage rattled and clattered deafeningly and the crane swayed ominously from side to side as the lorry scorched along.

Smithy pressed resolutely on the accelerator. Looking out of the window a quaking Dick watched the manifestly superfluous legend "Long Vehicle" gradually draw past. He closed his eyes, and attempted to close his ears to the clamorous metallic clangour which was now inching back alongside them. Eventually the sound was behind them and Dick blinked briefly. They had passed the mobile crane but still had what appeared to Dick to be several cricket pitches of articulated lorry to overhaul. Dick gave a furtive side glance at the Serviceman. Smithy was crouched over the wheel with the grim determination of the driver who is going to get in front if it kills him which, given the odd loose nut in the steering system, it could one day very well do.

Eventually they were alongside the driving cab of the immense speeding vehicle. Smithy gave a last spurt and they were then, at last, clear of the multi-wheeled monster. With a smile of satisfaction Smithy continued for a safe distance then crept back into his previous lane.

DAY OUT

"What about that, then," he stated proudly. "That's just about made my day."

"It's ruined mine," retorted Dick aggrievedly. "I've secreted so much adrenalin it will take me ages to get back to normal again. I can never understand what gets into you, Smithy, when you get on to a motorway. You change from an easy-going quiet sort of a bloke into a fiend incarnate."

"Nonsense," snorted Smithy. "Here am I, taking you out for a day in the country away from the Workshop, and all you do is complain. Anyway, we're getting near the turn-off point."

"Thank goodness for that!"

Smithy reduced speed and then steered away from the motorway. It was not long before they were driving, much more sedately, along a road more reminiscent of G. K. Chesterton's rolling English drunkard than the soulless soaring strip of six-segment cement stretching from nowhere to nowhere along which they had previously been hurtling.

Dick sighed contentedly.

"This is more like it," he said happily. "A complete break from radio and electronics. Hey, how about putting the radio on?"

"I thought we were having a break from radio."

"Ah, but this time we'll just be listening to it."

Obligingly, Smithy extended his left hand and turned on the little medium and long wave car radio fitted under the dashboard. He selected Radio 2 on long waves and the strains of a light classical melody became audible from the speaker.

The car drove over a bump and the music stopped.

Smithy frowned and adjusted the controls of the radio. It was completely silent, not only on long waves but also on the medium wave band as well. Irritably, Smithy switched it off.

Shortly afterwards he turned off unexpectedly down a narrow deserted side road. They were now well out into the country and he eventually found a space where he could pull off from the road. Smithy favoured large cars, and this fact often made it difficult to find suitable parking places. He slowed down and stopped the car, positioning it close to, and parallel with, a gate behind which was a big

empty field.

"What," enquired Dick, "is all this about?"

"It's that darned radio," replied Smithy. "I want to see why it stopped working."

"You've got to be joking," expostulated Dick incredulously. "You've only just now said that we're supposed to be getting away from radio. Dash it all, it's our annual day out together and now you want to waste it fixing radios."

"I can't help it," replied Smithy irritably. "It's just that I can't drive along knowing there's something wrong with that set. I like everything around me to be fully serviceable."

"A fine outing this is going to be," grumbled Dick. "What are you going to use for a meter?"

"I'm going to see if there are any obvious faults."

"Perhaps it's got a fuse that's blown."

Smithy switched on the set again. The bulb illuminating its tuning scale lit up but there was no other sign of life.

"If the fuse had gone," stated Smithy, "that bulb wouldn't light up."

"How do you know that?" persisted Dick. "That bulb could be wired across the supply lines before the fuse."

Vexedly, Smithy plunged his hand into the glove compartment and produced a number of papers. He glanced through these, extracted one and returned the rest to the compartment.

"This is the service manual for the set," he announced. "I keep it in the car because that seems to me to be the most obvious place to have it. If you look at the circuit you'll see what I mean about the fuse and the bulb."

Dick opened the manual and studied the circuit for a short while, after which he concentrated on the supply input section. (Fig. 1)

"Well, you're right about the lamp being after the fuse," he conceded, "and I'll agree with you that the fuse can't be blown. This circuit is rather interesting, though. For a start there are no fewer than three chokes after the fuse before you even get to the on-off switch."

"Those chokes are needed to prevent noise from the car electrics getting into the set. As you can see, there are two $0.1 \mu F$ capacitors providing decoupling to the receiver chassis."

"That's funny," remarked Dick. "I'd have thought you'd have needed a nice fat electrolytic there."

"A capacitance of $0.1 \mu F$ is enough to kill off most r.f. noise," replied Smithy, "and you couldn't have electrolytics in that part of the circuit anyway because the 12 volt input could be either positive or negative, depending upon whether the car has a negative or positive

Your Local Supplier

LONDON

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country

19-21 PRAED STREET
LONDON W2 1NP
Tel: 01-723 4185/2926

HAMPSHIRE

MORSE IMPROVEMENT

C90 Cassettes 1-12 w.p.m. with simple exercises. 12-14 w.p.m. computer produced professional level operator material including international symbols.

Price: complete with instruction and exercise booklets £4 including postage. Overseas £1 extra.

Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price £4 including postage. Overseas £1 extra.

MHEL ELECTRONICS (R)
12 Longshore Way, Milton
Portsmouth (UK), PO4 8LS

SUSSEX

JEFFRIES

For
Hi-Fi Equipment
Tape Recorders
Television
Transistor Radios

6A ALBERT PARADE
VICTORIA DRIVE
EASTBOURNE, SUSSEX

PEATS for PARTS ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics
Constructor Data Books
Panel Signs
Transfers

Also a postal service

PEATS
the world of electronics
25 Parnell Street, Dublin 1. Telephone 749972

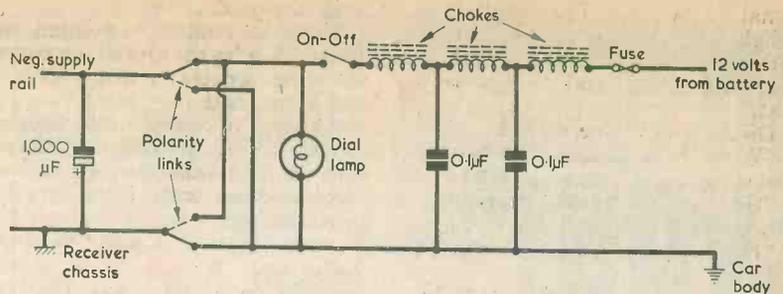


Fig. 1. The power supply circuit of Smithy's car radio. The polarity links are set up to cater for positive or negative earth. The receiver has a negative upper supply rail

earth. Immediately after the on-off switch are the tuning scale lamp and the polarity selection links. You set the links up to suit the car the radio is installed in."

CLASS A OUTPUT

"Oh, I see," stated Dick. "Ah, it's *after* the polarity links that we get the electrolytic. There's a nice big 1,000µF one connected across the supply rails."

Dick beamed at the capacitor symbol in the circuit. Smithy looked round at him.

"You're really happy about finding that electrolytic, aren't you?"

"I am," responded Dick. "No radio supply circuit should be without one!"

He turned to the a.f. and output stages of the receiver. (Fig. 2)

"Hey," he said, "this a.f. section is a bit unusual, isn't it? The first transistor is transformer coupled to

the output transistor, and the output transistor is transformer coupled to the speaker. Most transistor output stages these days don't use transformers at all, you just have two output emitter followers, one above the other, with the emitters coupling to the speaker."

"This set of mine," confessed Smithy, "is not quite as recent as all that, as you can tell by the fact that the a.f. transistors are germanium types. But a.f. transformers still keep cropping up in a surprising number of fairly recent ordinary transistor radios, appearing between the driver transistor and the two Class B output transistors."

"There's only one output transistor here."

"I know," retorted Smithy. "It's operating in Class A. It draws a standing collector current under no-signal conditions and this current increases or decreases in sympathy with the signal when a

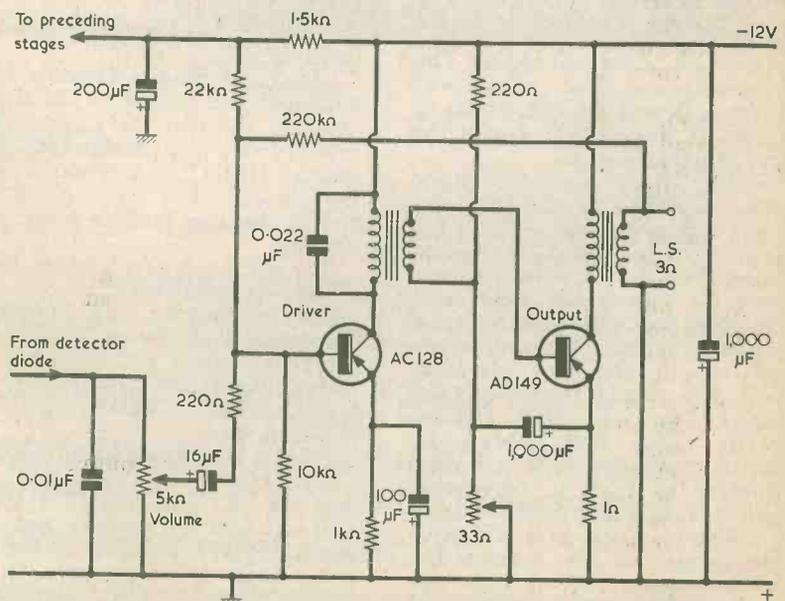


Fig. 2. The a.f. stages of the receiver comprise a driver and an output transistor functioning in Class A. The 1,000µF capacitor across the supply rails is the same component as that which appears in Fig. 1

signal is applied. The result is a delightfully simple output circuit with no problems at all about cross-over distortion and things like that."

Dick gazed at the circuit. "What," he enquired, "would that standing collector current be?" "Oh," replied Smithy carelessly, "about half an amp." "Half an amp? You're having me on!"

"No, I'm not. This is a car radio drawing current from a car battery, and to a car battery half an amp is a mere drop in the ocean. The current is set up by adjusting the 33 Ω pre-set. Despite the fact that the amplifier has two transformers in it the circuit still gives quite good quality. You will note that there's negative feedback from the secondary of the second transformer back to the base of the driver transistor via a 220k Ω resistor."

But Dick's attention had now wandered to another section of the receiver circuit.

"Here, this is crazy," he remarked. "There's no tuning capacitor in the mixer-oscillator stage at all!"

Smithy glanced at the r.f. and oscillator stage in the circuit of the receiver.

"There won't be a tuning capacitor," he stated. "Most car radios use permeability tuning instead. They are tuned by having iron-dust cores going in and out of the aerial and oscillator coils."

"Why's that, Smithy?" "Mainly because car radios have to withstand a lot of vibration and bumping around, and a permeability tuning assembly is more robust mechanically than is a tuning capacitor. The usual idea is to have the tuning spindle coupled to a coarsely threaded rod on which is affixed a carriage for the iron-dust cores. As the threaded rod rotates the carriage moves along it and the iron-dust cores go in or out of the coils."

"Humph," commented Dick as he digested this information. He was struck by a sudden inspiration.

"I've just thought about something! If variable capacitors aren't robust enough for car radios, why not use varicap diodes instead?"

"Why not, indeed? Varicap diodes having a capacitance swing wide enough to tune the medium and long wave bands have been available for several years now, and they are the obvious choice for tuning car radios. We haven't had any very recent car radios in for servicing at the Workshop, but it could well be that the latest versions are already incorporating varicap diodes."

An expression of bewilderment spread over Smithy's face, and he looked at the pastoral scene around him.

"What in the world am I doing, talking about the Workshop?" he

said bemusedly.

"You started it," pointed out Dick. "You're the one who wants to do radio repairs in the middle of the countryside."

"Ah yes, of course," said Smithy. "Well, I'll just get this car radio out and see if I can see anything obviously wrong with it."

He got out of the car, opened the boot and selected a small spanner. Returning, he got back in the driver's seat and proceeded to fumble under the dashboard. Dick opened his door and got out of the car to allow the Serviceman more room.

A VISITOR

Dick stood and leaned against the gate, savouring the fresh rural air. Looking down the road he espied a small figure walking towards them. As it approached, the figure revealed itself to be a little boy. As the distance between them decreased, Dick was able to observe him with greater resolution and he noted that he appeared to be a singularly dirty little boy. When the boy was very close to him Dick revised his opinion: the boy was an unbelievably dirty little boy. The little boy stopped at the car and gazed inside with interest. A rich country smell, redolent of the Augean stables, wafted across the top of the car.

"What yer doing there?" said the little boy.

Surprised, Smithy looked up then sniffed unconsciously.

"Why, who are you?" "I live here. What yer doing there?"

"If you must know," said Smithy with some asperity, "I'm trying to get this radio going."

By now he had removed the set from under the dashboard and had it resting on his lap. The back of the radio was towards the boy, who looked at it keenly.

"There's a wire off," he pronounced.

"Now, be a good boy," stated Smithy patronisingly, "and run along."

He sniffed again, then grimaced.

"Funny," he remarked. "That smell wasn't here before."


"It's me," remarked the boy proudly. "When I've been helping with mucking-out, I pong something vile. I'm famous for it; I'm the strongest ponger in these here parts."

"No doubt that's very creditable," said Smithy hastily. "But please go away. I want to see what's wrong with this set."

"There's a wire off," repeated the boy.

He leaned in and pointed a black-nailed finger at the back of the radio. Smithy recoiled and glanced, whilst attempting to cease breathing, at the radio. A wire was indeed off.

MORSE MADE EASY

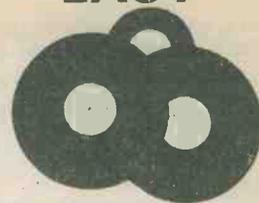

BY THE RHYTHM METHOD!

These courses, which have been sold for over 23 years, have been proved many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words.

Using scientifically prepared 3-speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 W.P.M. in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books. For Complete Course send £5.00 including P.P.E. etc. (overseas surface mail £1 extra).

Now available Shrouded Morse Keys £2.50

THE MORSE CENTRE

Box 8, 45 Green Lane, Purley, Surrey.

Enclose £5.00 or large s.a.e. for explanatory booklet.

Name

Address

GAREX

2-metre RECEIVER NR56: fully tunable 144-146 MHz, also 11 xtal positions for monitoring specific channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v DC operation. £54.00 inc. VAT. Crystals, if required: £2.41 each. All popular 2m. channels in stock. Credit terms available. s.a.e. details. Experimenters' H.T. transformer; multitap primary, 5 sec. windings: 35V 200mA, 75/115V 150mA, 50V 500mA, 150V 300mA, 170/220V 300mA, Wt. 6kg. £5.50
Relays: GPO type 2400 (medium size): 200+200 Ω coil (12-24V), 8A contacts. 4PCO+1M Type 3000 (large): 2k Ω coil (12-24V) 1B+3M, 2k Ω coil (24V) 2PCO, 8A contacts. 100+100 Ω coil (3-12V) 4PCO.

All new, 60p each, any 5+: 40p
Neons min. wire end. 55p/10; £4/100
Slide Switches min. DPDT 18p ea; 5+: 14p
2 pole, 3 position 22p each; 5+: 18p

Resistor Kits E12 series, 22 Ω to 1M Ω
57 values, 5% carbon film, $\frac{1}{4}$ W or $\frac{1}{2}$ W.
Starter pack, 5 each value (285) £2.40
Mixed pack, 5 each $\frac{1}{4}$ W + $\frac{1}{2}$ W (570) £4.65
Standard pack, 10 each (570) £4.65
Giant pack, 25 each (1,425) £11.65

I.C.'s (new full spec.) CD4001AE 25p
SN76660 75p NE555 55p 723(T05) 75p
709 (T05), 741 (DIL-8) Op. amps 30p each
BNC Cable mtg socket 50 Ω 20p; 5+: 15p
PL259 UHF Plug & Reducer 68p; 5+: 60p
SO239 UHF Socket panel mtd. 55p; 5+: 45p
Nicaid rechargeable cells HP7 size £1.05 each; 4: 95p; 10: 88p. Brand new.
We stock amateur V.H.F. equipment and mobile aeriels, s.a.e. details.

Distributors for J. H. Associates Ltd. (switches and lamps)

PRICES INCLUDE UK POST, PACKING & VAT
Mail order only Sole Address:

GAREX ELECTRONICS
7 NORVIC ROAD, MARSWORTH,
TRING, HERTS HP23 4LS
Cheddington (STD 0296) 668684

"Well, well, well," said Smithy with attempted joviality. "You have now found for me what was wrong."

"If I was running a shop and you brought in that set," said the little boy, "I'd have charged you a quid for finding that loose wire."

"Perhaps so," remarked Smithy. "But seeing as how we're out in the open, like, I reckon 50p would be all right."

Resignedly, Smithy reached into a pocket and produced a 10 pence piece.

"50p."

The boy came closer to Smithy, who blenched visibly. Furiously, he reached into his pocket again, this time to produce a 50 pence piece. Shuddering, he dropped it into the little boy's filthy outstretched hand.

"Ta, skip," said the boy. "I've really saved you 50p, you know. If you'd taken that set to someone who knows how to mend radios he'd have charged you a quid."

The boy circled round the car and approached Dick, who retreated rapidly. The boy unfastened the clasp of the gate and opened it wide, pushing it into the field.

"You and your grand-dad," he said, "had better get moving soon."

With which remark he left the pair and proceeded leisurely up the road. The air gradually cleared and Dick and Smithy breathed deeply.

"I'll have to get the car fumigated," complained Smithy. "What did he say to you?"

"He said that me and my grand-dad should get moving soon."

"Cheeky little devil. Do you know, he spotted the fault on this set and made me give him 50 pence for doing so?"

"And you paid him?"

"I had to. It was either that or asphyxiation."

"Well," said Dick, "we won't see him again. Did he truly find the fault?"

"Yes, truly," confessed Smith ruefully. "That output transistor is a T03 type and it's bolted to the back of the set chassis, which acts as a heat sink. Also, it's insulated from the chassis by a mica insulating washer. A wire comes through a hole alongside and connects to the collector, which is of course the transistor case, by way of a solder tag held under one of the insulating bushes. As that horrible little boy noticed, that wire had broken away from the tag." (Fig. 3.)

Dick examined the broken wire and the tag.

"Blimey," he remarked, "you certainly had an obvious fault there. But you still can't fix it. Not unless you've got a 12 volt soldering iron."

"I haven't," admitted Smithy, "but I can still make a temporary

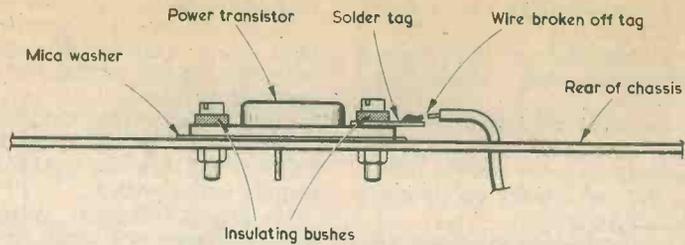


Fig. 3. The output transistor in the radio is mounted, with mica washer and insulating bushes, to the rear of the chassis, which functions as a heat sink. A lead to a solder tag in contact with the transistor case had broken off at the solder tag.

repair. All I need to do is to strip off a bit of the insulation at the end of the wire and trap it between the solder tag and the transistor case."

A. F. STAGES

Deftly, Smithy proceeded to carry out the temporary repair, after which he returned the radio to its position under the dashboard. He switched on, and a pleased expression spread over his face as the radio once more operated correctly. He checked both wavebands then switched off again.

"Phew," he said, pulling out a handkerchief and mopping his brow. "It's hot working in here. I'll cool off a bit before we get going."

He got out and leaned against the bonnet of the car, leaving the driver's door open. The front passenger door was also open and Dick was now leaning on the bonnet as well.

"I think," said Smithy, "it would be a good idea to leave the two rear doors open as well. I fancy I can still smell that stinking little kid, so we'll give the car a complete airing."

Dick and Smithy opened the rear doors wide then returned to the bonnet. Smithy noticed that Dick had the service manual in his hand.

"Oh no," he groaned, "don't tell me that you're going to start on about the circuit of that set again."

"It's just the permeability tuning bit," said Dick. "When you're used to r.f. stages with tuning capacitors, it throws you a bit when you bump into something which is so entirely different."

"Permeability r.f. tuning circuits can be a little difficult to understand," admitted Smithy. "Let's have a look at this one and see if we can sort it out."

Dick walked round to Smithy's side of the car and laid out the service sheet circuit on the bonnet. He pointed to the aerial and mixer-oscillator section of the receiver circuit. (Fig. 4.)

"Ah yes," said Smithy. "Well, this is fairly straightforward once you start digging into it. L2 and L4 are the permeability tuned coils and their inductance is altered as the tuning control is adjusted. L3 and L5 are coils with pre-set iron-dust cores. The easiest part of the circuit is the oscillator section and the coils for this are L4 and L5."

Smithy traced out the oscillator connections. (Fig. 5(a).)

"Positive feedback," he went on, "is from the collector of the mixer-oscillator back to its emitter, the feedback path being via part of the first i.f. transformer primary, R6 and C10. Don't forget that the collector and emitter of a transistor are in phase, and so there's no need to introduce phase reversal as would be needed if the feedback was from the collector back to the base."

"When the wavechange switch is set to medium waves," broke in Dick quickly, "it short-circuits L5. Presumably, then, the frequency of oscillation is governed by L4, C8 and C9."

"That's right," agreed Smithy. "C9 is the oscillator trimmer for medium waves. The circuit is unusual by normal standards but it obviously works. When the wavechange switch is set to long waves, L5 is inserted in series with the medium wave tuned circuit. The added inductance then lowers oscillator frequency to the range required for long wave coverage."

"That seems to be fair enough," commented Dick slowly. "Now, what about the signal frequency part?" (Fig. 5(b).)

"That," stated Smithy, "is more complex, but only because we're used to the more simple circuits involved with tuning capacitors. On medium waves, the aerial signal is applied via C2 to C1 and C3 in parallel. C3 is the medium wave aerial trimmer. This is a form of bottom-end coupling in which the aerial is applied to a tap in the capacitive part of the tuned circuit

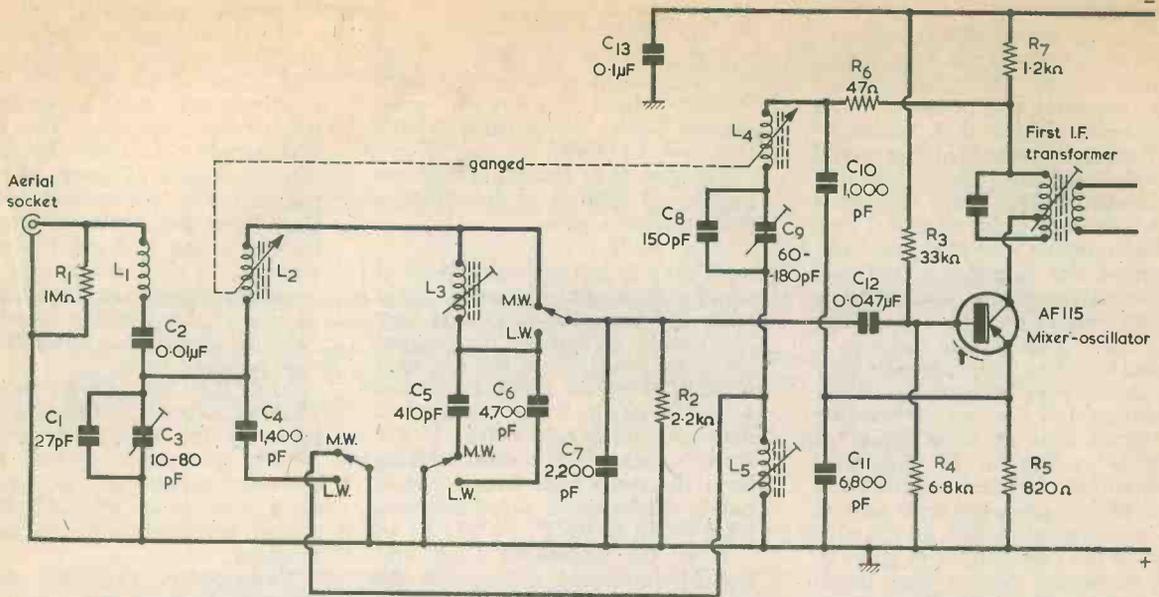



Fig. 4. The signal frequency and oscillator circuits of the radio. L2 and L4 are permeability tuned. This, and the circuits of Figs. 1 and 2, are slightly simplified versions of the circuits employed in the Pye model 2040 car radio. The three switches are sections of the medium-long wavechange switch.

instead of to a tap in the inductance part. The overall resonant frequency on medium waves is governed by the inductances of L2 and L3, the capacitors C1, C3, C5 and C7, and the capacitance of the aerial to earth, which is the car body of course, together with the self-capacitance of the screened aerial feeder wire. The aerial to earth capacitance has quite a significant effect, especially at the high frequency end of the medium wave band. Admittedly, it's odd to find two inductors in a frequency selective circuit, but there's no reason why there shouldn't be. We think nothing of having two or more capacitors in such a circuit."


"What happens," queried Dick, "when we go to long waves?"

"Well," said Smithy, "one thing that happens is that C4 is connected in parallel with C1 and C3. The next thing is that L3 is connected in series with L2, and the base of the mixer-oscillator transistor is transferred to the other end of L3. Also, C5 is taken out of circuit and replaced by the higher value C6. All these changes bring the resonant frequency down to the range needed for long waves. A complicated circuit, admittedly, but the complications will be due to the necessity for getting good tracking both on medium and on long waves."

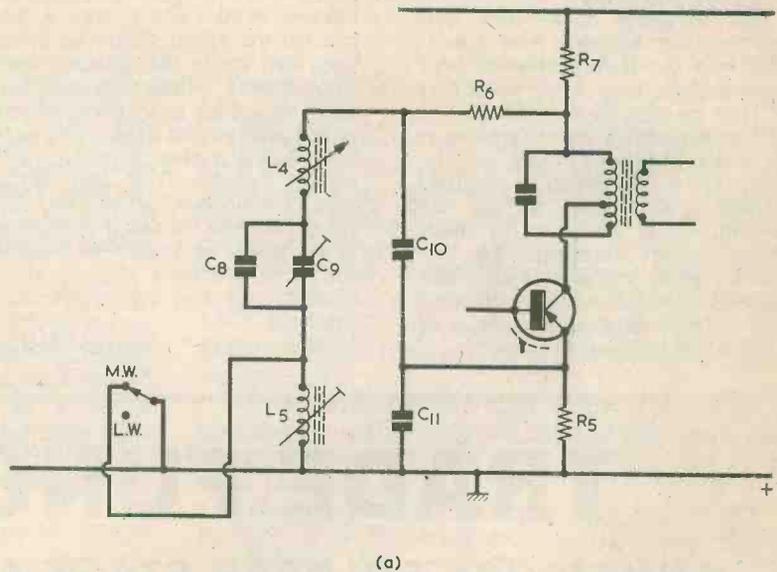A perceptive listener could have heard a very faint bleating from the direction in which the mendicant and malodorous little boy had disappeared. But Dick and Smithy were too preoccupied with the circuit of the car radio to be aware of



(a)

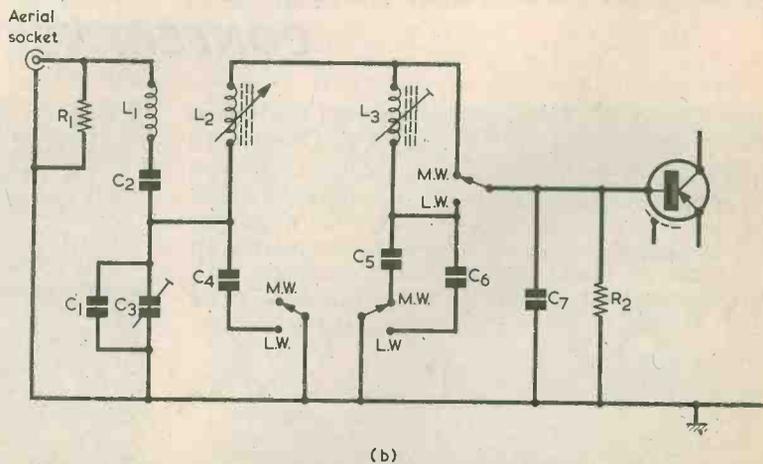

(b)

Fig. 5(a). The essential components in the oscillator section of Fig. 4

(b). The signal frequency circuitry. Taking an input for the transistor base from a relatively high value capacitance in the tuned circuit is equivalent to taking a low impedance tap from a coil

the sound.

"You say," stated Dick, "that the aerial to earth capacitance plays an important part, particularly at the high frequency end of the medium wave band. Why is that, Smithy?"

"Because a standard car aerial provides very little signal pick-up," explained Smithy. "You only have about six feet or so of aerial rod, and at medium and long wave frequencies the impedance between the aerial and the car body is almost entirely capacitive. The aerial is coupled to the radio by a special screened cable having a very low capacitance between the centre conductor and the outside braiding to ensure that as little signal as possible is lost in it. The total capacitance between aerial and earth is then assumed to be part of the input tuned circuit. In practice most of the capacitance is given in the screened cable. The usual procedure when installing a new radio in a car is to trim the medium wave tuned circuit to suit the particular aerial and screened lead which are employed."

The bleating noise had now become more distinct. Also discernible was the faint clatter of very many tiny hooves.

"How do you do that, Smithy?"

"You tune in to a weak station at the high frequency end of the medium wave band," replied Smithy, "and then adjust the medium wave trimmer for maximum signal strength. In our receiver that trimmer is C3. The trimmer only has to be readjusted if, at a later date, a new aerial or aerial screened lead is fitted."

STATIC VOLTAGE

"That seems to cover all I want to know about this circuit," commented Dick. "No it isn't! What's that coil, L1, for?"

"It's an r.f. choke. It reduces pick-up of impulsive interference from the car engine."

"And R1?"

"That's to prevent a build-up of static voltage on the aerial. On a very dry day it's surprising how much static voltage can be acquired by a car aerial when the car is in motion. Some car radios even have a little neon bulb connected between aerial and earth. If the static voltage rises to neon striking level the neon bulb turns on and partly discharges it. Good heavens, what's that racket?"

Even the engrossed Dick and Smithy could not now ignore the animal hubbub which impinged on their ears. They turned round and gazed open-mouthed at a vast army of sheep running busily towards them and completely filling the narrow road. There was a purposeful air about them, as though they had made this journey many times before. When they were level with the open gate they wheeled round to enter the field, those in the front being pushed forward by the masses behind. Dick and Smithy found themselves jostled away from the car bonnet by sheep determined to exchange, as quickly as possible, the hard confined surface of the road for the lush open softness of the field.

"The doors," shouted Smithy.

"Shut the car doors!"

But it was too late. One sheep had already been forced past the outside rear door of the car, to find a relatively easy entry to the field by way of the other door. This leader was at once followed by a continuous retinue of sheep, all pressing their way behind each other as they crowded through the car. Several sheep had got themselves trapped in the front and were bleating helplessly as they struggled against the unfamiliar hazards of steering wheel, gear lever and the now repaired radio.

And still the sheep came on. Fuming helplessly as he was thrust back by the volume of animals, Smithy groaned in despair at the devastation wrought in his car. Dick gave up the unequal struggle and sat at the roadside, roaring with laughter.

Eventually, the end of the column of sheep came into view. Behind them was the dirty little boy, whistling tunelessly and waving a stick at the stragglers in the rear. Smithy watched with hapless resignation as the last sheep forced its way through the rear of the car. The boy poked at the sheep trapped in the front and these, too, at last made their way out and into the field. The boy followed them, closed the gate and then leaned over it to address the shattered Serviceman.

"Don't blame me, grand-dad. I said you ought to move on."

"But," spluttered Smithy, "what about my car?"

"You was lucky," said the boy. "Last week it was cows I brought into this field." ■

TRADE FUNCTION

MULTICORE SOLDERS STAGE A WORLD SALES CONFERENCE

London Airport's Heathrow Hotel was the venue recently of the first ever World Sales Conference held for overseas Distributors by Multicore Solders Limited. Over 40 delegates representing 30 countries flew in for the two day Conference which included lectures by senior Multicore executives on all aspects of Soldering and Solder products.

Many delegates' wives accompanied their husbands, and guided sightseeing and shopping ex-

peditions were arranged for them during Conference hours.

Other highlights included a gala dinner at the hotel and a tour of the Multicore plant.



The assembled delegates pose for a happy souvenir of the conference

R.S.G.B. at Alexandra Palace

The RSGB International Radio Communication Exhibition and Convention, held at Alexandra Palace, London, was officially opened at noon on Friday, May 6th by Councillor Vic Butler, Mayor of Haringey and closed at 1700 the following Sunday. This ambitious 3 day event was visited by some 6,000 people which fully rewarded both the RSGB and its organiser, John Hitchins.

AROUND THE STANDS

By David Gibson

Pots of gold are commonly found (so we are reliably informed) at the end of rainbows. Fantastic radio and electronics bargains, on the other hand, are found underneath TV transmitting aerials; and without the need for a metal detector! The truth of this can be verified by all who visited the RSGB International Radio Communication Exhibition and Convention.

Bargains were interspersed with the unusual and, often, unexplicable. One dealer offered an oscilloscope with a clockwork mechanism which gave a pulse trace once a minute for eight days! The cost was £15 and the mind boggled. In a more simple vein, Future Scientist transistor radio kits were offered at £1 complete and were seen clutched in the hot little hands of more than a few prospective radio 4 listeners.

The exhibition was certainly a place for opportunists and evidence of their presence was rife. Even the walls of the gents loo bore advertisements for various items on sale. In place of the customary graffiti, one was caught staring at a colour brochure urging the purchase of a Trio TS-700G 2 metre all-mode transceiver. While next to it was an assurance that six TIL 209 LEDs could be had for only 50p if one applied at the "undermentioned stand".

For the constructor, the show was an absolute gold mine. Four-gang 500pF variable capacitors were offered at only 80p, and the Amateur gardener was catered for by one company displaying 240V 1.5A soil heaters for 25p each.

Even eccentrics could find items of interest, such as an enormous moving coil meter with two scales marked in microseconds and thousands of feet. Just the thing for your mantlepiece and cheap at half the price.

Even nostalgia was catered for by the showing of items like EF50 valves and Type 2G barretters not to mention an original Mullard VP4B. Contrasting with these ancient friends were newer brothers in components.

People who went looking for quartz crystals were in luck, many types were on display.

One stand doing continually brisk trade was that of J. Birkett. Dealing in a wide range of components there was a constant stream of money going one way and packages going the other across the counter. Silicon solar cells were on sale, a smile from the sun would encourage them to give 0.5V at up to 5mA. Not a huge power, but three would give 1.5V which is more than enough for a solar powered MW receiver using the popular ZN414 Ferranti IC.

There seemed to be a huge quantity of very large electrolytic capacitors on sale everywhere. Ten thousands microfarads was average, but many were larger!

Exhibitions within exhibitions were also a feature. The Havering and District Club gave a convincing demonstration of 3cm television transmitted live from Ilford. In demand on the



A general view at the exhibition



Tom Hook, talking with other 10 GHz enthusiasts about some of the equipment he has constructed

Havering stand was Tom Hook, who despite being partially blind, manufactures all the plumbing necessary for 10.1GHz and displayed some directional coupler ports, 10GHz wavemeters and other items he's made at home. Anyone wanting to get started on 10GHz but is put off by the plumbing should contact Tom.

Best component bargain spotted on the Garex stand was a pack of resistors (preferred values) from 22Ω to 1MΩ for only £4.50p. Oh yes, there were 10 of each value, too!

New products were also in evidence. Some were so new that you could only look — but not actually purchase! Just such an item was the new Datong active antenna. Connect the receiver to one side, and two pieces of wire each only 2 metres long and you're in business. Ideal for receiving — especially if you want an extremely tiny aerial, the device is broadbanded from below long waves to 30MHz. On the stand, David Tong claimed that even Rugby on 16kHz was received well and the device works just as efficiently at 30MHz. The new active antenna should be available in about three months' time.

Some people break records but one stand marked "Home Test" sold them. One was even able to find "A nightingale sang in Berkely Square" by the Glenn Miller orchestra (number BD 5850) nestling comfortably next to a large heap of G401 transistors offered at only 2p each. At that low price, the transistor bargain must have been a record, too!

This years' exhibition can claim contrasts if nothing else. In among stands offering the very latest in sophisticated Amateur Radio transceivers was an unnamed stand showing semi-rusty handles at 10p each complete with even more rusty fixing nuts. Also shown was a pile of Stylophone records at 10p each. Now there's variety for you!

One stand owner commented that the "Black Box Boys" were here and this had helped the show. Most noticeable in this area was the number of sophisticated Amateur Stations now offered for sale. The Icom IC-240 for example, is a 22 channel synthesised 144MHz transceiver requiring no crystals. This entirely solid state unit runs from 13.8V and has a 10W power output of FM. Receiver sensitivity is at least 0.4μV and there's an audio output of 1.5W.

Interesting, too, that many units are now appearing with auto-scanning facilities. An example here is the Multi-U11 432MHz transceiver with a scanning speed of 4 channels per second. This unit costs £249 complete with 9 channels and auto tone burst. The receiver has three IFs; 45MHz, 10.7MHz and 455kHz with a receiver sensitivity of 0.5μV. As the man said in Fiddler on the Roof; "If I were a rich man."

For visitors interested in scanning, Modular Electronics showed its FM 10A sequential scanner module. This little unit, ready built and tested, is designed to automatically switch between each of up to 10 channels of a crystal controlled receiver,

The lovely Brenda demonstrates an Icom 144MHz transceiver on the Amateur Radio Exchange stand



*Caught in the act — your actual knob-twiddler.
One of many who twiddled on the Lowe Elec-
tronics stand.*



stopping on receipt of a signal for as long as the signal is present.

In one corner was the RAIBC stand. The Radio Amateur Invalid Bedfast Club now has some 1,000 members. Listen for their net on 3.5MHz at 1000hrs Tuesdays, and 1400hrs Wednesdays. If you know of anyone who is bedridden and interested in radio, why not drop the secretary a line at 14 Queen's Drive, Bedford MK41 9QB.

For anyone interested to learn more about some aspect of Amateur Radio, there were many lectures taking place each afternoon. These covered most popular interests such as getting started as an SWL, aerials, synthesisers and phase locked loops — and even one intriguing talk entitled, "Some confessions of a VHF columnist". I wonder if this will appear in paper-back version, "Forty years before the Mast"?

If you missed this year's show, make a note in your diary for next year.

AT THE CONVENTION

By Ron Ham

On Saturday evening, it was praise all the way for the Society as about 180 members and guests listened to the after dinner speakers in the Palace Suite, presided over by Lord Wallace of Coslany, the Society's President.

Mr. R. W. Cannon, Technical Director, Cable and Wireless Ltd., proposing the toast to the Society, referred to amateur radio as one of our national assets, because, by introducing young people to amateur radio it often spurs them on to take up a career in a similar field. The speaker was very impressed with the large exhibition and admired the way in which the "trade" had produced some very technical equipment at prices which most amateurs could afford. The RSGB, he said, shaped the amateur effort in the same way that the technical institutes helped the professional engineers.

Replying, Dr John Allaway, Immediate Past President, mentioned the many countries where Cable and Wireless staff had used their own amateur stations to keep in touch with the UK, and he took this opportunity to thank Cable and

Wireless for supplying the monthly HF Predictions table which appears in *Radio Communication*. Dr. Allaway stressed the need for the RSGB to work with other national societies in persuading new countries to accept amateur radio. Among the dinner guests were representatives from France, Belgium, Yugoslavia, and USA and they all joined in the spontaneous applause when Dr. Allaway congratulated Lord Wallace on his appointment as first Lord in waiting to Her Majesty the Queen.

Proposing the toast to the Guests, Dr. Dain Evans, Executive Vice-President, spoke of the many sides to amateur radio and referred to Ed Tilton, who had given a lecture in the afternoon, as "a legend in amateur radio".

Replying for the Guests, Dr. J. A. Saxton, Director, Appleton Laboratory, and past President of the Society, emphasised his well worn theme that every amateur in the UK should give his wholehearted support to the RSGB. It was obvious, he said, that this event had been well supported, and he congratulated all who were responsible for its organisation.

BACK NUMBERS

For the benefit of new readers we would draw attention to our back number service.

We retain past issues for a period of two years and we can, occasionally, supply copies more than two years old. The cost is 40p plus 12p postage.

Before undertaking any constructional project described in a back issue, it must be borne in mind that components readily available at the time of publication may no longer be so.

We regret that we are unable to supply photo copies of articles where an issue is not available. Libraries and members of local radio clubs can often be very helpful where an issue is not available for sale.

NOTES FOR NEWCOMERS

COLLECTOR SPECIFICATIONS

By F. T. Jones

How to ensure that small transistors are operated within their collector voltage, current and dissipation ratings.

Bipolar transistors are liable to break down if their voltage, current and wattage dissipation ratings are exceeded. With small transistors (as opposed to large power transistors which are designed to be mounted on a heat sink) it is, fortunately, a simple matter to ensure that these ratings are not exceeded. A general procedure will be described here.

VOLTAGE RATINGS

The maximum collector voltage rating for a transistor is usually specified in terms of V_{ce0} max. and V_{cb0} max. V_{ce0} refers to collector-emitter voltage with the base open-circuit whilst V_{cb0} applies to collector-base voltage with the emitter open-circuit. Sometimes the voltages are simply referred to in transistor data as V_{ce} and V_{cb} respectively. Where there is a difference between the two voltage ratings the V_{cb0} (or V_{cb}) figure is usually higher than the V_{ce0} (or V_{ce}) value. Neither figure should be exceeded, and in general it is a good plan to ensure that a transistor does not approach more than say, 75% of its maximum voltage rating. In most instances a transistor is employed in the common emitter configuration, as in Fig. 1(a), whereupon the supply voltage should preferably be lower than 75% of the V_{ce0} or V_{cb0} figure. With most practical circuits the supply voltage will be considerably below the maximum collector voltage rating.

The transistor of Fig. 1(a) will in many cases be passing a steady collector current, whereupon the actual voltage across its collector and emitter will be the supply voltage less the voltage dropped in the collector load resistor. Such a state of affairs should not tempt the designer into employing a supply voltage

higher than the maximum rated voltage for the transistor unless circuit requirements make this absolutely unavoidable; accidents can happen and a sudden large input signal, a faulty connection or the onset of instability can cause the transistor to be cut off, whereupon no voltage is dropped across the collector load and the full supply voltage is applied across the transistor. With all transistor ratings it is wise to anticipate the worst-case effect.

We do not normally, of course, choose a supply voltage to suit a particular transistor. Instead, the supply voltage is usually given and we select a transistor to suit that voltage. With most home-constructor projects the supply is limited to about 9 to 18 volts or so, with the result that the choice of a transistor with an adequate collector voltage rating raises few problems.

A different aspect arises when the collector load is not resistive but has a relatively high value of inductance. The most common example here occurs when the collector load is the coil of a relay. When the transistor cuts off to release the relay the lines of magnetic force in the relay coil collapse, to generate a back-e.m.f. of opposite polarity which can be much greater than the supply voltage. In the circuit shown in Fig. 1(b) the collector voltage of the transistor would go well positive of the positive supply rail. We overcome this problem by connecting a diode across the relay coil, as in Fig. 1(c), with a polarity which causes it to be non-conductive when the transistor is turned on and energises the relay. When the transistor cuts off the relay coil attempts to produce its high back-e.m.f., but the diode then conducts and prevents the e.m.f. rising above the diode forward conducting voltage.

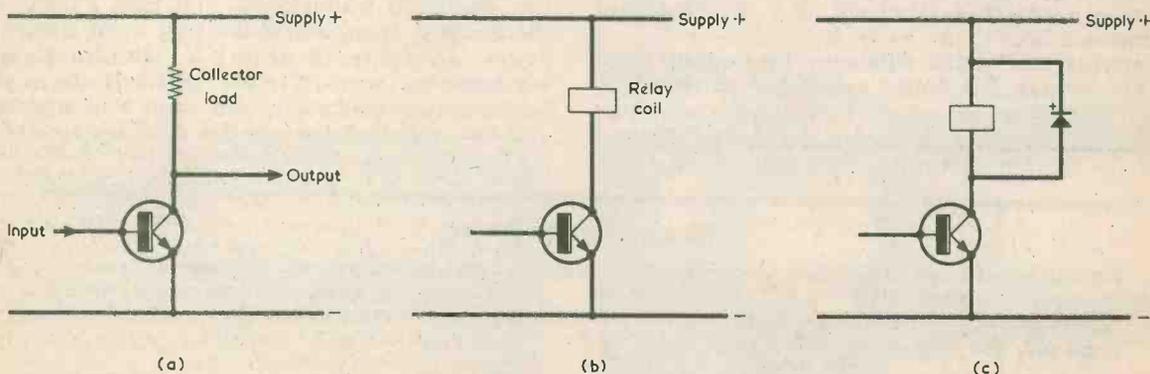


Fig. 1(a). A simple common emitter amplifier with bias components omitted. An n.p.n. transistor is assumed here and in the succeeding diagrams
(b). In this circuit the collector load is a relay coil
(c). A diode across the relay coil prevents the formation of a high back-e.m.f. when the relay releases

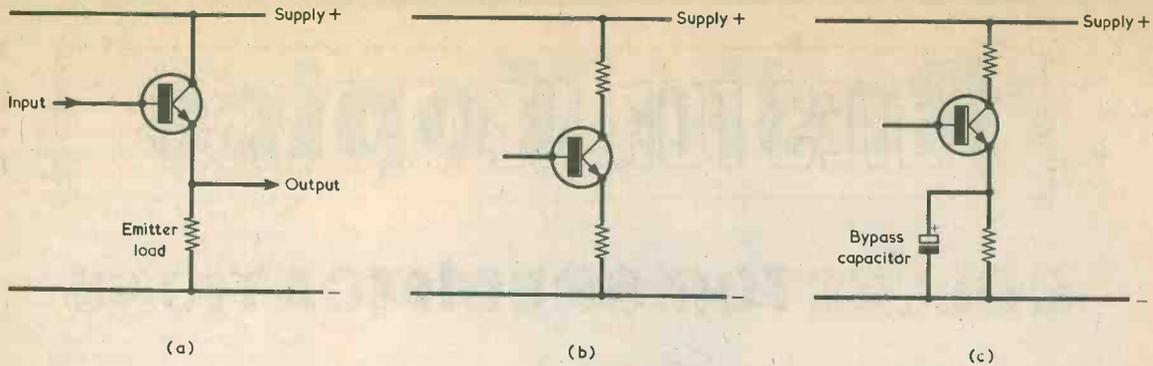


Fig. 2(a). With an emitter follower the resistive load is in series with the emitter
 (b). Here there are resistors in both the collector and emitter circuits
 (c). Frequently, a high value bypass capacitor is connected across one of the resistors

COLLECTOR CURRENT

The maximum collector current rating for a transistor is normally expressed as $I_c \text{ max.}$ There is another term, I_{cbo} , which applies to collector-base current when the emitter is open-circuit. This is not a limiting rating and merely defines the collector-base leakage current.

A circuit should always be designed so that the transistor maximum collector current rating cannot be exceeded for any foreseeable circuit condition. In Fig. 1(a) the maximum collector current which can flow is given when the transistor is turned hard on, whereupon the highest possible voltage appears across the collector load resistance. A little exercise in Ohm's Law soon settles the situation here, and we assume that there is zero voltage across the transistor when it is hard on. If, for example, the supply voltage is 10 volts and the load resistance is 100 Ω the maximum collector current which can flow is 0.1A (10 divided by 100) or 100mA. We would select a transistor with a maximum collector current rating of at least 150mA, and preferably 200mA or more, for use in such a circuit. Happily, most collector load resistance values are much higher than 100 Ω and transistors can be employed more than comfortably within their maximum collector current ratings. A minor exception here is given by such items as a.f. output transistors. It would be in order to take these up to, but not beyond, the maximum current rating during part of the a.f. cycles they handle.

If the transistor is an emitter follower, as in Fig. 2(a), we say that the emitter current is the same as the collector current. We then treat the value of the

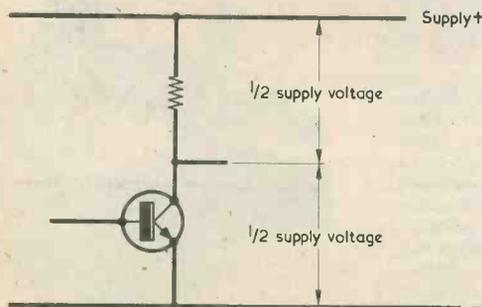


Fig. 3. The situation when half the supply voltage appears across a collector load resistor and the remaining half appears across the transistor

emitter load resistor in the same way as we did with the collector load resistor. Should there be resistive loads in both the collector and emitter circuits, as in Fig. 2(b), we add their values and treat the result as a single collector (or emitter) resistor. When there is a high value bypass capacitor across one of the resistors, as in Fig. 2(c), it is advisable to assume that this will be discharged and act as a short-circuit at the instant of switch-on. The collector current is then limited, at that instant, only by the resistor which does not have the capacitor across it.

POWER DISSIPATION

Maximum power dissipation is referred to as $P_t \text{ max.}$ or $P_{tot} \text{ max.}$ and requires a different type of calculation. The dissipation is equal to the voltage across the transistor multiplied by its collector current. If a transistor is connected in the manner illustrated in Fig. 3 it can be demonstrated that maximum power is dissipated in the transistor when half the supply voltage appears across it. Obviously, half the supply voltage will then also appear across the collector load resistance. Since the same current passes through the transistor and the resistor, the same power is dissipated by both.

It is an easy process to find the maximum possible transistor dissipation which the circuit can cause. If we once more assume that the supply voltage is 10 volts and the collector load resistance is 100 Ω , maximum dissipation in the transistor occurs when the load resistance has 5 volts across it. The dissipation given by 5 volts across 100 Ω is 0.25 watt (5 squared divided by 100) or 250mW. For our circuit we would be wise to choose a transistor with a $P_{tot} \text{ max.}$ rating of say 350mW or, preferably, higher. With power output transistors we could allow the maximum dissipation figure to be approached but not exceeded.

In the emitter follower circuit of Fig. 2(b) we find the maximum dissipation figure by working out the dissipation when half the supply voltage appears across the emitter load resistor. When there are resistors in both the emitter and collector circuits we add their values and find the dissipation which occurs when half the supply voltage is applied across a single resistor having their total value.

These approaches are also applicable to power transistors which are intended for mounting on a heat sink. The only difference is that the power dissipation figures for the latter type of transistor assume that the transistor is mounted on a heat sink of adequately large dimensions and low thermal resistance to air.

Radio Topics

By Recorder



RESISTORS AND CAPACITORS

These make up the grist for the electronic mill and, as the years go by, they become smaller and smaller and more and more delightfully simple to handle. My stock of resistors goes back to the early 1960's and what we used to treat as $\frac{1}{2}$ watt types in those days are almost ten times the volume of the tiny little $\frac{1}{4}$ -watt types we deal with nowadays. Especially pleasing are the lead-out wires, which tin and solder immediately the iron is placed on them. In the old days resistor lead-outs used to tarnish quite noticeably if they were held in stock for any length of time, and sometimes it was even necessary to scrape and tin them before they could be soldered into a circuit.

SMALL SIZE

The small size of modern resistors has some disadvantages because, of necessity, the width of the colour coding bands reduces in proportion. The human eye has a reduced perception of colour as the size of the object diminishes, which explains why colour television has been able to flourish in its present form. Particularly difficult to distinguish in small areas are orange and red or orange and some of the shades of brown which resistor manufacturers employ. I recently had a mixed batch of 47k Ω (yellow, violet, orange) and 4.7k Ω (yellow, violet, red) resistors to sort out, all of these being identical in size and general body colour and differing only in the orange and red third bands. After a little practice I was able to sort them out visually, but I had to rely on the meter when I started, just to make certain that I wasn't making any errors. Rather a similar happening occurred with a mixture of 22k Ω (red, red, orange) and 220 Ω (red, red, brown) resistors with which the brown of the 220 Ω resistors had a strong orange tinge, although these weren't so bad as the 47k Ω and 4.7k Ω resistors.

When dealing with resistors sold on the home constructor market it is a good plan to assume that the wattage rating is the absolute maximum that the resistor can stand without burning out. It's always best to play safe in matters of this nature, and I never knowingly allow a resistor to dissipate

more than half its rated wattage. Fortunately most modern transistor circuits involve extremely low resistor dissipations and these are an almost minute fraction of $\frac{1}{2}$ watt.

WATTAGE RATING


As an example of what a resistor may be called upon to dissipate, assume that we have a 470 Ω transistor emitter bias resistor and that a current of 3mA passes through it. The voltage across the resistor will be just a little short of 1.5 volts, whereupon the power dissipated by the resistor is 3mA times 1.5 volts, or 4.5 milliwatts. Since $\frac{1}{2}$ watt is equal to 250 milliwatts the resistor, in a typical transistor application, is obviously running more than comfortably within its dissipation figure.

The ease with which resistor leads can be soldered pays off an unexpected bonus when you are making up a quick experimental circuit in "lash-up" form. If relatively long lead lengths can be tolerated, it is a good idea to solder the first few resistors to their tags or circuit points with their leads uncut. Quite a few other components and wires can then be readily soldered to the resistor leads themselves. The result admittedly looks extremely untidy and the technique should never be employed for any permanent assembly. But it pays off with quick experimental circuits and allows rapid changes of components and wiring.

Turning to capacitors, these have undergone a similar diminution in size accompanied by a corresponding ease of lead soldering. With the introduction of plastic dielectrics, the modern capacitor is almost completely leak free, whereas the old paper dielectric capacitors were always a possible cause of trouble here. A word of warning is necessary with respect to working voltages. Since nearly all electronic equipment these days is low voltage solid state we have got into the habit of using capacitors with maximum working voltages in the order of 100 to 160 volts without bothering a great deal about such voltages. If it becomes necessary to fit a replacement capacitor to, say, a TV set having valves it is advisable to check the voltage the capacitor will be subjected to. Quite often this may be well in excess of 250 volts immediately after switch-on and before the valves have warmed up and started drawing current. A low voltage capacitor which would be perfectly happy in a transistor circuit would soon break down at such voltages.

Newcomers are sometimes a little puzzled by the working voltages specified for electrolytic capacitors. In general it is always safe to employ an electrolytic capacitor having a working voltage higher than the specified voltage. If, for instance, a components list in a magazine quotes a value of 100 μ F at 10 volts it is quite in order to use instead a 100 μ F 16 volt capacitor or even a 100 μ F 25 volt capacitor.

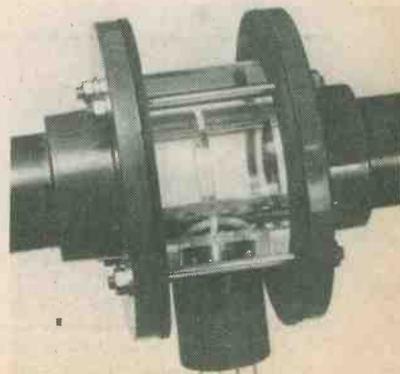One of a range of Metre Meter fluid flowmeters manufactured by Litre Meter Ltd. By adapting a small turbine and orifice plate an output is obtained which is directly proportional to fluid flow. Also the range of flow measurement is considerably increased



Provided, of course, that there is space for the larger component.

FLUID FLOW

The accompanying photograph shows a flowmeter, which is a device for measuring the flow of a fluid, and is one of a range which has been introduced by Litre Meter Ltd., Ryefield Crescent, Northwood, Middlesex, HA6 1NN. The Northwood air must be conducive to alliteration because the flowmeter is referred to as a Metre Meter.

The old and most commonly used method of flowmetering is by means of an orifice plate where a flow produces a differential pressure on the plate which is proportional to a square of the flow across the orifice. The typical flow range which can be measured is 6:1, producing a 36:1 pressure change. This pressure is expensive to measure accurately and it is even more expensive to extract the square root for display.

However, engineers at Litre Meter Ltd. have found that the flow through a modified Litre Meter turbine flowmeter has an interesting characteristic, in that the flow caused by the differential pressure obeys a square law. If this is combined with an orifice plate the square root is extracted at source and a linear digital output is obtained. Not only is this extremely useful in itself, but in addition the dynamic flow range measurable becomes increased from 6:1 to 60:1, an impossible range with a normal orifice plate. The converted orifice plate has in fact become a complete Linear Digital Orifice Plate.


The Litre Meter turbine flowmeter has a tiny rotor which revolves in the fluid flow, sending pulses according to its speed of rotation through a simple electronic device, which then sends signals to appropriate recording instruments. The rate of rotation indicates the rate of flow, and the total of rotations the total flow. The associated instruments can display rate and/or total.

The combination of this cost-effective system with the established orifice plate method has resulted in the new Metre Meter appearing in a highly versatile set of flow rate transmitters, all of which employ the same miniature turbine and simple electronics. The range of the Metre Meter flowmeters now being marketed by Litre Meter Ltd. has been correspondingly increased enormously and are together capable of metering fluid flow from 1 drop per second to 5 tonnes per minute, a ratio of over 500,000:1.

HIGH VOLTAGE RELAY

My second photograph shows what I can only describe as two really man-sized relays. Manufactured by Walmore Electronics Ltd., the relays can switch exceptionally high voltages and currents.

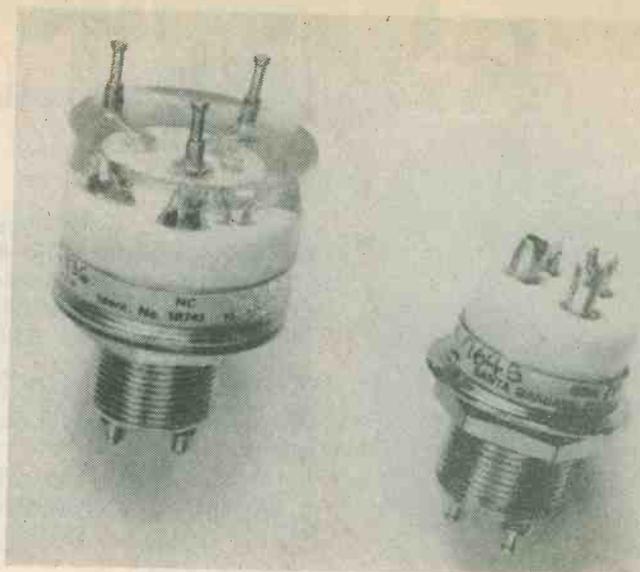The larger relay is a newly introduced version of the Kilovac HC-1 vacuum dielectric ceramic relay, of which the small relay is a standard example. The large relay is the type HC1/S43, and it retains the advantages of light weight, small size, high-strength ceramic housing, 6 millisecond operating speed and low contact



Two vacuum dielectric ceramic relays in the Walmore Electronics HC-1 series. The larger relay has been recently introduced and it can switch voltages up to 8kV at 18 amps maximum

resistance exhibited by its predecessors in the HC-1 range. However, design modifications, including the potting of the relay housing, have enabled the voltage rating to be increased from the normal 2.5kV to 8kV. The r.f. ratings have also been enhanced. Current carrying capacity is 18 amps maximum, contact resistance is 0.01Ω maximum and the coil resistance is 335 Ω

All HC-1 Series relays are suitable for high voltage and high peak current applications such as are given in radar, communications, pulse forming networks and aerial tuning units. They exhibit high reliability and long life, and their low dielectric loss and the use of high conductivity, non-magnetic materials in the switching circuit make them particularly suitable for r.f. applications.

Further details are available from Walmore Electronics Ltd., 11-15 Betterton Street, Drury Lane, London WC2H 9B3.

NUTS AND BOLTS

I suppose that the day is coming when we shall see the end of BA nuts and bolts as we go more and more metric. The metric nuts and bolts are denoted by the letter "M" followed by a number which gives an idea of the full diameter in millimetres. Common sizes available at the time being are M2.5, M3, M4 and M5. For the record, the M2.5 is just slightly smaller in diameter than 6BA, the M3 is about half-way between 6BA and 4BA, the M4 is half-way between 4BA and 2BA whilst the M5 is approximately midway between 2BA and 1BA. They're covered by British Standards, that for the screws being B.S.3643 and that for the nuts being B.S.3692.

TRANSFORMERS

There are some very small mains transformers creeping onto the scene, including in particular those offering low voltage outputs at currents of 100mA or even 50mA for transistor equipment. Some of these little transformers tend to be of the "no-name" variety, and I must confess that I look upon them with a little distrust.

If you are using one of these transformers near its maximum secondary current rating you may find that it runs quite warm, particularly if it is mounted on an insulating material such as s.r.b.p. Should a metal chassis be in use for the equipment concerned it is probably a good idea to mount the transformer on this, as the chassis will then act as a heat sink. I may be a little over-fussy here but I never feel quite happy with unbranded components of this nature and, in any case, I always like to keep things cool!

My colleagues on this journal receive a few queries from time to time about suitable output transformers for valve receivers. Most valve transformers have now been discontinued, of course, but some retailers are still retaining stocks of multi-ratio types. The usual queries are concerned with output valves of the 6V6 and 6BW6 type. The 6V6 is on an octal base whilst the 6BW6 is on a 9-pin B9A base and, electrically, the two valves are virtually identical. For the benefit of readers who wish to know the best output transformer ratios for these two valves, the information is that a 40:1 ratio is suitable for working into a 3 Ω speaker and a 20:1 ratio can be used with a 15 Ω speaker. The ratios are not very critical, and ratios close to those I have just mentioned will be quite satisfactory. ■

New Products



DALESFORD LOUDSPEAKER DRIVE UNITS

A range of loudspeaker drive units of interest to professional and amateur constructors alike has recently been announced by Dalesford Speakers Ltd. All the models are Bextrene coned and fitted with high power voice coils.

All HiFi bass and midrange applications are covered by nine models ranging from 4in to 12in diameter.

Details are available from the sole distributors: Wilmslow Audio, Swan Works, Bank Square, Wilmslow, Cheshire.

THE NEW PROSSER PS1 1211 FUNCTION GENERATOR


Market research in the function generator field exposed the following criticisms of some existing instruments: limited waveforms available; limited attenuation; single output impedance; need for a "floating" instrument in many applications.

The PSI 1211 claims to satisfy all these requirements in addition to providing many

negative ramp, with variable duty cycle pulses. The main output is 20V pk-pk from two output impedance sources: 50ohm and 600ohm.

A front panel control provides full adjustment of the pulse duty cycle from 10% to 90% independent of frequency.

The main output level is controlled by a

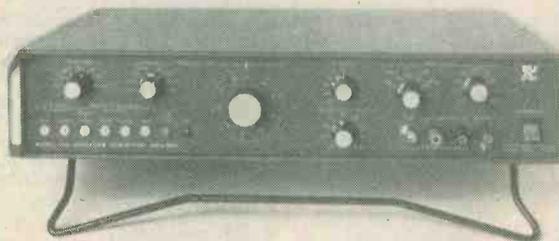

The Prosser 1211 5MHz Function Generator

other refinements. It is an all-purpose function generator which provides a wide choice of precise output waveshapes and amplitudes while simultaneously offering monitor outputs of all the other functions.

The instrument has a significant edge, both technical and costwise over comparable competitive types. It combines many functions in a single package thereby eliminating the need for several different instruments with a consequent cost saving.

British designed and manufactured, the PSI 1211 has a frequency range from 0.04MHz to 5MHz. It offers output functions of sine, square, triangular, positive ramp,

high accuracy attenuator which provides five fixed levels from 20V down to 200mV. Additionally, a further fine attenuator control allows fully continuous attenuation down to 40mV yet still retains the same signal purity.

The PSI 1211 is fully protected against damage should any output be inadvertently shorted. An internal DC offset control permits all waveshapes to be referenced to a DC level, in addition the maximum level of DC offset is $\pm 10V$. The instrument has been designed to be fully floating.

Auxiliary outputs on the PSI 1211 all have TTL compatibility and there is provision for external frequency sweeping.

SMALL ADVERTISEMENTS

Rate: 10p per word. Minimum charge £1.50
Box No. 25p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the *bona fides* of Advertisers. (Replies to Box Numbers should be addressed to: Box No. —, **Radio and Electronics Constructor**, 57 Maida Vale, London, W9 1SN.

SERVICE SHEETS for Radio, Television, Tape Recorders, Stereo, etc. With free fault-finding guide. From 50p and s.a.e. Catalogue 25p and s.a.e. Hamilton Radio, 47 Bohemia Road, St. Leonards-on-Sea, Sussex.

ELECTRONIC DEVICES and Semiconductors. Component kits for this month's projects. S.A.E. for lists. Export welcome. NKM, P.O. Box 65, Eastbourne, Sussex.

TREASURE HUNTERS! Construct 11-transistor metal detector giving £300 performance. 10 page illustrated plans, send £1. C. H. Lucas, 241 Upminster Road South, Rainham, Essex.

BOOKS TO CLEAR: *Introductory Radio — Theory and Servicing*, 1948. (With Teacher's manual) by H. J. Hicks, £1.50. *Klystron Tubes*, by A. E. Harrison, 1947, £1.50. *An Approach to Audio Frequency Amplifier Design*, 1957, G.E.C. Publication, £1.25. *Television Engineers' Pocket Book*, 1954, by Molloy & Hawker, 50p. All prices include postage. — Box No. G329.

WANTED: Large and small quantities of transistors, I.C.'s, displays, etc., etc., Call any Saturday to: 306 St. Paul's Road, London N.1. Telephone: 01-359 4224.

300 PAIRS OF S/H SPEAKERS in 9" x 14" teak cabinets. From £3.50. Edwards, 103 Goldhawk Road, London W12. Telephone: 743 6996.

ANTIQUE WIRELESS: For valves, radios, components and service sheets, 1920 to 1950. Contact The Vintage Radio Shop, 1977 Full Catalogue 70p. 64 Broad Street, Staple Hill, Bristol BS16 5NL. Telephone: (0272) 565472.

TV REPAIRS SIMPLIFIED. Full repair instructions individual British sets £4.50; request free circuit diagram. Stamp brings details of unique TV publications. Auserec, 76 Churches, Larkhall, Lanarkshire.

RESISTORS: E12, 5% 1/3 W — 1p. Diodes 4148 — 3p, 4004 — 5p, LM555CN — 38p. VAT inclusive. 15p postage. Cleveland Supplies, P.O. Box 20, Redcar, Cleveland.

OUTSTANDING HI-FI FM TUNER. Comprises 7 transistor superhet design with vericap tuning, AFG. Latest silicon circuitry, full coverage 88-102MHz. Supplied built and tested with metal front panel and instruction sheet. Only £9.95 + 30p P. & P. Gregg Electronics, 86-88 Parchmore Road, Thornton Heath, Surrey.

(Continued on page 61)

FANTASTIC GOLDRING SAVINGS

GOLDRING G103 Belt Drive Turntable


Famous name turntable slashed to near half price. Complete with plinth, cover and leads. Accepts any standard cartridge (not included)

FULL 12 MONTH GUARANTEE

OUR PRICE
£29.95

R.R.P. £54 (+p/p & Ins £2.25)

SAVE OVER £24

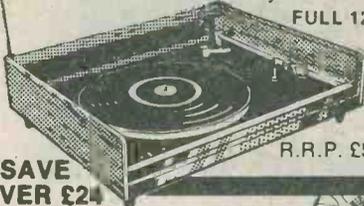

Build your own GOLDRING CK2 Belt Drive Turntable

Beautifully engineered unit from the famous Goldring company, comes complete with instructions and all necessary parts. Ready to incorporate into your design plinth and cover. The pleasure of assembling your own deck.

(Plinth, cover and cartridge not included).
Usually sold for £54.95 with plinth and cover.
Call in or send cheque; P.O., M.O., Access, Barclaycard, Diners Club or American Express Number.

ONLY
£16.95

(+ p.p & Ins. £1.50)

ALL PRICES
INC. VAT

Sonic Sound Audio

248/250 TOTTENHAM COURT ROAD, LONDON W1. TEL: 01-637 1908

RADIO MODELLER

ELECTRONIC BOOKS

● **MODEL RADIO CONTROL**
Detailing both Theory and Practice, this book, by leading authority Paul Newell, has become the standard reference work. A brief historical survey leads up to a detailed description of proportional systems, with over 100 illustrations, including theoretical circuits and p.c. layouts for an advanced digital system.
134 pages Price £2.25

U.K. Packing & Postage 32p

ON SALE NOW
at all leading shops
or direct from:—

**RADIO MODELLER
BOOKS DIVISION,
84 High Street,
teddington, TW11 8JD.**

theory and practice of
**MODEL
RADIO
CONTROL**

development of a stem-proportional expanded digital system design practical examples and full circuit details

TV

FAULT FINDING MANUAL for 405/625 LINES



90p

P. & P. 18p

REVISED & ENLARGED

EDITED BY J. R. DAVIES

132 pages

Over 100 illustrations, including 60 photographs of a television screen after the appropriate faults have been deliberately introduced.

Comprehensive Fault Finding Guide cross-referenced to methods of fault rectification described at greater length in the text.

UNDERSTANDING TELEVISION



by
J. R. DAVIES

Over 500 pages
300 diagrams

£3.25

P. & P. 60p

UNDERSTANDING TELEVISION deals with:

- Principles of 405 line reception
- Principles of 625 line reception
- Nature of the television signal
- Receiver tuner units
- A.F. and video amplifiers
- Deflector coil assemblies
- Automatic gain and contrast control
- Receiver aerials
- The cathode ray tube
- Receiver i.f. amplifiers
- Vertical and horizontal timebases
- Synchronising
- Power supply circuits
- Colour television
- **COLOUR TELEVISION** – 80 page comprehensive introduction to the subject

The reader is required to have only a basic knowledge of elementary radio principles. The treatment is non-mathematical throughout, and there is no necessity for any previous experience in television whatsoever. At the same time UNDERSTANDING TELEVISION is of equal value to the established engineer because of the very extensive range it covers and the factual information it provides.

To Data Publications Ltd., 57 Maida Vale, London, W9 1SN

Please supply the 4th revised edition of TV FAULT FINDING, Data Book No. 5.....

Please supply UNDERSTANDING TELEVISION; Data Book No. 17.....

I enclose cheque/crossed postal order for.....(Tick which book is required)

NAME.....

ADDRESS.....

(BLOCK LETTERS PLEASE)

SMALL ADVERTISEMENTS

(Continued from page 59)

JOIN THE INTERNATIONAL S.W. LEAGUE. Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. — both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £3.75 per annum. (U.K. and British Commonwealth), overseas \$10.00 or £4.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

WANTED: Desk-FAX machine, complete or spare parts, with literature, manuals, etc., in the series TR100/1 and TR102/1, made by Creed & Co. Ltd. Details to Box No. G335.

FOR SALE: Complete 9.5mm cine "Wide screen" outfit — Cameras, projector, screen, etc. S.A.E. for details. Box No. G336.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. — The Holborn Direct Mail Company Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

SEND 10p IN STAMPS for latest list of aids for DX Listening, tuners, filters, etc. Stephens-James Ltd., 47 Warrington Road, Leigh, Lancs, WN7 3EA.

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. Rita Shepherd, 59 Paintain Road, Loughborough, Leics., LE11 3LZ.

WANTED: Radio & Electronics Constructor wave-winding machine copy. Replies to Box No. G337.

WANTED URGENT: Power Supply unit or circuit for frequency meter BC221. Hamilton, 67 Caswell Close, Farnborough, Hants.

FOR SALE: Copies of "Hi-Fi News" January 1975 to October 1975 inclusive, plus December 1975 and January 1976. Mint condition. Offers? Box No. G338.

FOR SALE: R/E, E/E, P/W. 75 in all. From October 1974. Best offer. R. Plant, 5 Molyneux Place, Stoke, Plymouth, Devon.

FOR SALE: Four volumes "Newnes Complete Wireless" about 1935 in very good condition. Offers wanted including carriage. Box No. G339.

-BOOKS TO CLEAR: *The Radio Constructor* Vol. 15 August 1961 to July 1962, Bound, £2.30. *Practical Wireless*, Bound, Vol. 28, January to December 1952, £2.20. *Short Wave Magazine*, Bound, Volume VIII, March 1950 to February 1951, £2.00. *Newnes Television & Short Wave Handbook*, by F. J. Camm, 1935, £2.00. All prices include postage. Box No. G340.

(Continued on page 62)

PHILIPS



YOU & PHILIPS HI-FI KITS

The top sellers for home assembly in Europe — now available in the U.K.

Now — read all about the Philips range of quality kits for home assembly — mixers, amplifiers, speakers, etc, etc. Send today to S.S.T. Distributors (Electronic Components) Ltd., West Road, Tottenham, London N17 ORN

Please send me, quickly, the new colour catalogue. REC 81

Name _____

Address _____



Postcode _____

free SEND TODAY!
S.S.T. Distributors is a member of the Philips Group of Companies.

Become a radio amateur.

Learn how to become a radio amateur in contact with the whole world. We give skilled preparation for the G.P.O. licence.

Free!

Brochure, without obligation to:
BRITISH NATIONAL RADIO & ELECTRONICS SCHOOL

REK 87

P.O. Box 156, Jersey, Channel Islands


NAME _____

ADDRESS _____

(Block caps please!)

PLAIN-BACKED NEW STYLE SELF-BINDERS

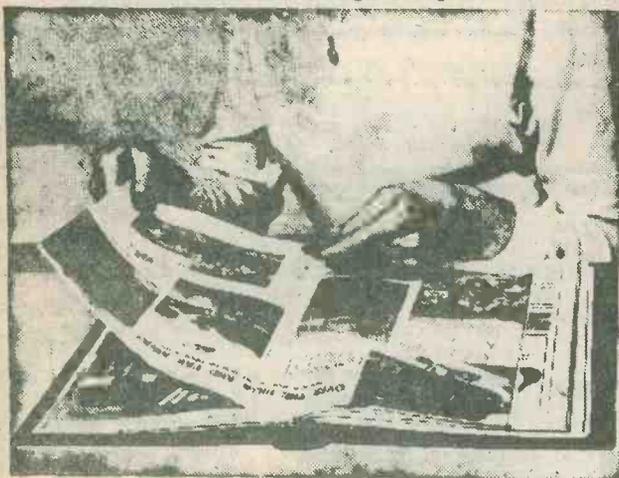for your other magazines
(max. format $7\frac{1}{2}$ " x $9\frac{1}{2}$ ")



The "CORDEX" Patent Self-Binding Case will keep your copies in mint condition. Issues can be inserted or removed with the greatest of ease. Specially constructed Binding cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for, and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

COLOURS: MAROON OR GREEN

(If choice not stated, colour available will be sent)

PRICE **£1.15** P. & P. 30p

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 61)

FOR SALE: A loft full of surplus components. Speakers, uniselectors, wire etc. Must be cleared. Also Fidelity tape recorder, Meccano set and electronics construction kit. Offers? Telephone: 01-455 0248 evenings.

FREQUENCY LIST TRANSFERS. We have a limited supply of sheets of Dial Frequency Transfers in black. Short Wave frequencies 1.8Mc/s to 32Mc/s and 144Mc/s and 146Mc/s. Includes amateur band marker frequencies at 100kc/s points and other short wave frequencies from 2 to 32Mc/s at every 500Kc/s points. Each frequency is repeated. Two sheets for 5p., five sheets for 10p., postage 7p. Data Publications Ltd., 57 Maida Vale, London, W9 1SN.

FOR SALE: 108-136MHZ Receiver. Size 5in. x 3in. x 2in. Pocket size. Easily adjusted to tune over 144MHZ band with good sensitivity. £16.50 post and packing paid. Romak Engineering Ltd., Dept. RE, 10 Hibel Road, Macclesfield, Cheshire SK10 2AB.

FOR SALE: Clearing out back issues of *Radio Constructor* to 1950's. Projection TV lens and tube, etc. Offers? Telephone Medway 408427.

MICRO SWITCHES button type, 3A 250V. Minimum quantity 5 for £1 all inclusive. Cobra Electronic Systems Ltd., 83 Greenfields Avenue, Alton, Hants.

FOR SALE: 1949-71 *Wireless World*, and *Radio Constructor* Volumes 3-28. Offers to: Mr. Hanson, 67 Pine Walk, Carshalton, Surrey.

60kHz MSF RUGBY RECEIVERS BCD time-of-day output. High performance PLL 5V operation, pulsating LED. Kit or assembled instrument available. Prices £14.08-£23.47. Details: Toolex, Sherborne, Dorset.

JUBILEE PACKS. Contains diodes, transistors, capacitors, resistors, plus odd items. Average 80 items per pack, £1 plus 25p P. & P. Cheque or P.O. to: A. Callow, 61 Coniston Way, Bewdley, Worcs.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

ESSEX GARDENERS. Buy your Bedding and rock plants, shrubs, etc., also cacti from May's Nurseries, 608 Rayleigh Road, Hutton, Brentwood, Essex. Callers only. Monday to Saturday.

SPONSORS required for exciting scientific project. Norwich Astronomical Society are building a 30" telescope to be housed in a 20' dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational, Educational. You can be involved. Write to: NAS Secretary, The Manse, Back Lane, Wymondham, Norfolk.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from:— The Hon. Membership Secretary, The Broads Society, "Icknield," Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

THE OPEN DOOR TO QUALITY



4th ISSUE INCLUDES NEW METERS AND SWITCHES as well as items from advanced opto-electronic components to humble (but essential) washers. Many things listed are very difficult to obtain elsewhere. The company's own computer is programmed to expedite delivery and maintain customer satisfaction. Attractive discounts continue on many purchases, Access and Barclaycard orders are accepted.

SEMI-CONDUCTORS ● COMPONENTS ● ACCESSORIES ● TOOLS
 • **FREE POSTAGE** on all C.W.O. mail orders over £2 list value (excluding VAT) in U.K., add 15p handling charge.

144 pages
40p
 Post paid
 inc. refund
 voucher
 worth
40p

All communications to Head Office, Dept. RCB 28 ST. JUDES ROAD, ENGLEFIELD GREEN, EGHAM, SURREY TW20 0HB. Phone Egham 3603 Telex 284475, Hours 9-5.30 daily: 1 pm Sats. NORTHERN BRANCH: 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone 061-432 4945. Hours 9-5.30 pm, 1 pm Sats.

ELECTROVALUE LTD

PRINTED CIRCUITS AND HARDWARE

Comprehensive range Constructors' hardware and accessories. Sheet aluminium and lightweight sections. Selected range of popular components. Printed circuit boards for individual designs. Drawing materials for printed circuits. Resist coated laminate, epoxy glass for the d.i.y. man. Full processing instructions, no unusual chemicals required.

Send 15p for catalogue

Ramar Constructor Services

Masons Road · Stratford-on-Avon · Warwks CV37 9NF

MULLARD FERRITE CORES — LA3 100 to 500 kHz, 75p; LA5 30 to 100 kHz, 100p; LA7 10 kHz, 100p LA13 for W.W. Oscilloscope, £2.00.

SPECIAL OFFER — Metallised Polyester Capacitors by Erie, Mullard, etc. Values include: .01/160V, .01/250V, .015/160V, .022/160V, .033/160V, .047/160V, .068/160V, .1/160-250V, .22/160V, etc. This is a bargain not to be missed. 100 for £3.00. 1N4148 **SWITCHING DIODES**, 10 for 30p; 50 for £1.25; 100 for £1.50; 1,000 for £12.50.

TRANSISTORS — All branded BC147, BC148, BC149, BC157, BC158, BC159, BF194, BF195, BF196, BF197, 10p each or 100 for £7.50.

Please note all prices include UK Postage and appropriate VAT @ 8% or 12½%

XEROZA RADIO

306 ST. PAUL'S ROAD, Highbury Corner, LONDON N1
 Tel: 01-226 1489

SMALL ADVERTISEMENTS

Use this form for your small advertisement

To: The Advertisement Manager, Data Publications Ltd., 57 Maida Vale, London W9 1SN

Please insert the following advertisement in theissue of RADIO & ELECTRONICS CONSTRUCTOR

➔			

15 words at 10p
 = £1.50

**ALL WORDING
 IN
 BLOCK LETTERS
 PLEASE**

I enclose remittance of being payment at 10p a word. **MINIMUM £1.50**
 Box Number, if required, 25p extra

NAME

ADDRESS

Copy to be received four weeks prior to publication. Published on the 1st of every month.

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 40p each, postage 12p

Issue(s) required

Annual Subscription

Price **£6.00**, post free, commence with.....issue

Bound Volumes:

Vol. 27. August 1973 to July 1974

Price **£2.40**, post & pkg 90p

Vol. 28. August 1974 to July 1975

Price **£2.75**, post & pkg 90p

Vol. 29. August 1975 to July 1976

Price **£3.10**, post & pkg 90p

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price **£1.20**, post & pkg 30p

With no title on spine, maroon

Price **£1.15**, post & pkg 30p

With no title on spine, green

Price **£1.15**, post & pkg 30p

Max. Format 7½" x 9½"

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages

Price 90p, P. & P. 20p

DB6 Radio Amateur Operator's Handbook,
88 pages

Price 70p, P. & P. 13p

DB17 Understanding Television, 504 pages

Price **£3.25**, P. & P. 70p

DB19 Simple Short Wave Receivers
140 pages

Price 80p, P. & P. 20p

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording — White

Price 75p, P. & P. 8p

Set 4: Wording — Black

Price **£1.00**, P. & P. 8p

Set 5: Dials

Price 38p, P. & P. 8p

Prices include V.A.T. on Panel Signs

I enclose Postal Order/Cheque for.....in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS