

WALLACE

RADIO & ELECTRONICS CONSTRUCTOR

JULY 1980
55p

**80 METRE
AMATEUR BAND
RECEIVER**

*Expressly
designed for
s.s.b. and c.w.
signals*

**CAPACITANCE
MEASURING
ADAPTOR**


SIMPLE DEVICE ENHANCES
USE OF ANALOGUE
MULTIMETER

**ALSO
FEATURED**

**OSCILLOSCOPE VOLTAGE CALIBRATOR
31-DAY TIMING CIRCUIT**

DIRECT SUPPLY SERVICE TO READERS

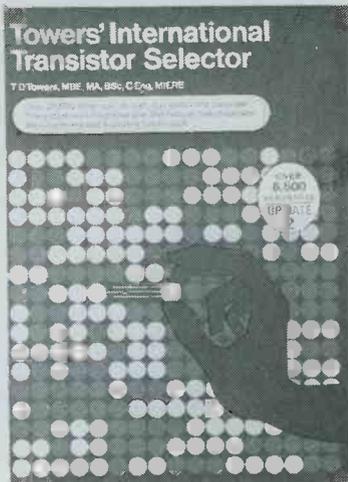TOWERS INTERNATIONAL TRANSISTOR SELECTOR (NEW REVISED EDITION)



This is dead! 

Would this replace it?



If it takes you longer than 1 minute to find out all about these transistors then you need a copy of TOWER'S INTERNATIONAL TRANSISTOR SELECTOR. It's one of the most useful working books you will be offered this year. And probably the cheapest!

In it, you will find a really international selection of 13,000 transistor types — British, Continental European, American and Japanese. And we think that they will solve 90% of your transistor enquiries.

Current and widely used obsolete types were carefully selected and arranged in Numero-Alphabetical order by an author who was uniquely qualified to do the job. With his compendium, all you need to know is the type number and you can learn all about a transistor's specification; who made it and where to contact them; or what to use to replace it.

Price £10.35 inc P&P

TOWERS INTERNATIONAL FET SELECTOR



If you deal with field effect transistors, or fet's — whether as a student, a hobbyist, a circuit engineer, a buyer, a teacher or a serviceman — you often want data on a specific fet of which you know only the type number.

Specifications apart, you may be even more interested in where you can get the device in question. And perhaps more important still (particularly with obsolete devices), you may want guidance on a readily available possible substitute.

This fet compendium, a comprehensive tabulation of basic specification, offers information on:

1. Ratings
2. Characteristics
3. Case details
4. Terminal identifications
5. Applications use
6. Manufacturers
7. Substitution equivalents (both European and American)

The many fet's covered in this compendium are most of the more common current and widely-used obsolete types.

It is international in scope and covers fet's not only from the USA and Continental Europe, but also from the United Kingdom and the Far East (Japan).

Price £4.00 inc P&P

(Please allow 21 days for delivery)

Tower's
International
Transistor
Selector by **T. D. Towers**
MBE, MA, BSc, C Eng, MIERE
£10.35
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

(Block capitals)

Tower's
International
FET
Selector by **T. D. TOWERS**
MBE, MA, BSc, C Eng, MIERE
£4.00
inc. post and packing

To:—DATA PUBLICATIONS LTD.
57 MAIDA VALE
LONDON W9 1SN

Please send me copy/copies
to the address shown below

NAME

ADDRESS

(Block capitals)

RADIO & ELECTRONICS CONSTRUCTOR

JULY 1980
Volume 33 No. 11

Published Monthly

First published in 1947

*Incorporating The Radio
Amateur*

Editorial and Advertising Offices
57 MAIDA VALE LONDON W9 1SN

Telephone
01-286 6141

Telegrams
Databux, London

c Data Publications Ltd., 1980. Contents may only be reproduced after obtaining prior permission from the Editor. Short abstracts or references are allowable provided acknowledgement of source is given.

Annual Subscription: £8.50, Eire and Overseas £9.50 (U.S.A. and Canada \$20.00) including postage. Remittances should be made payable to "Data Publications Ltd". Overseas readers, please pay by cheque or International Money Order.

Technical Queries. We regret that we are unable to answer queries other than those arising from articles appearing in this magazine nor can we advise on modifications to equipment described. We regret that queries cannot be answered over the telephone, they must be submitted in writing and accompanied by a stamped addressed envelope for reply.

Correspondence should be addressed to the Editor, Advertising Manager, Subscription Manager or the Publishers as appropriate.

Opinions expressed by contributors are not necessarily those of the Editor or proprietors.

Production – Web Offset.

OSCILLOSCOPE VOLTAGE CALIBRATOR – Suggested Circuit by G. A. French	644
KEEPING CURRENTS LOW by R. J. Caborn	646
NEWS AND COMMENT	648
CAPACITANCE MEASURING ADAPTOR – Neat add-on unit allows your testmeter to measure capacitance – by R. A. Penfold	650
THE LM3909 I.C. – 8 Pin i.c. with both useful and novelty applications – by A. P. Roberts	655
IN NEXT MONTH'S ISSUE	657
SHORT WAVE NEWS – For Dx Listeners – by Frank A. Baldwin	658
80 METRE AMATEUR BAND RECEIVER – Expressly designed for s.s.b. and c.w. amateur signals – by M. V. Hastings	660
BCD ENCODER SWITCH – Trade Review	667
COMPUTING LANGUAGES – Databus Series No.11 (Conclusion) by Ian Sinclair	668
GENERAL PURPOSE 8 WATT AMPLIFIER – Part 2 by A. P. Roberts	671
31-DAY TIMING CIRCUIT – In Your Workshop	675
ARIANNE SUCCESSFULLY LAUNCHED – Report by Arthur C. Gee	680
TRADE NEWS	682
VOLTAGE MULTIPLIERS Electronics Data	iii

Published in Great Britain by the Proprietors and Publishers, Data Publications Ltd, 57 Maida Vale, London W9 1SN.

The *Radio & Electronics Constructor* is printed by LSG Printers, Portland Street, Lincoln.

OUR NEXT ISSUE
WILL BE PUBLISHED
EARLY AUGUST

BI-PAK

SEMICONDUCTORS

DEPT. RC. 7, PO Box 6, WARE, HERTS.

Visit our Shop at: 3 Baldock Street, Ware, Herts.

GIRO NO. 3887006

TEL: 0920 3182

TELEX: 817861

EXPERIMENTOR BREADBOARDS

CONTINENTAL SPECIALITIES CORPORATION

FROM 

No soldering breadboards. Simply plug components in and out of letter number identified Nickel-silver contact holes. Start small and simply snap-lock boards together to build a breadboard of any size.

All EXP Breadboards have two bus-bars as an integral part of the board. If you need more than two buses, simply snap on 4 more bus-bars with the aid of an EXP 48.

EXP 325 The ideal breadboard for 1 chip circuits. Accepts 8, 14, 16 and up to 22-pin IC's

ONLY £1.84
48mm (1.9")

EXP 350/270 contact points with two 20-point bus-bars.

ONLY £3.62
91mm (3.6")

EXP 300/550 contacts with two 40-point bus-bars.

ONLY £8.81
152mm (6.0")

EXP 650 For Micro-processors.

ONLY £4.14
91mm (3.6")

EXP 48

ONLY £2.85
152mm (6.0")

EXP 600 As EXP 300 but accepts 24 pin DIL and over.

ONLY £7.25
152mm (6.0")

All EXP 300 Breadboards mix and match with 800 series.

ANTEX IRONS

1943 15 watt quality soldering Iron with 3/32" bit £5.12

1947 Replacement element for 1943 £2.33

1944 Iron coated bit 3/32" for 1943 £0.58

1945 Iron coated bit 1/8" for 1943 £0.58

1946 Iron coated bit 3/16" for 1943 £5.12

1948 18 watt iron with iron coated bit £2.22

1952 Replacement element for 1948 £0.58

1949 Iron coated bit 3/32" for 1948 £0.58

1950 Iron coated bit 1/8" for 1948 £0.58

1951 Iron coated bit 3/16" for 1948 £0.58

1931 X25 25 watt iron, ceramic shaft and another shaft of stainless steel to ensure strength £5.12

1935 Replacement element for 1931 £2.00

1932 Iron coated bit 1/8" for 1931 £0.58

1933 Iron coated bit 2/16" for 1931 £0.58

1934 Iron coated bit 3/32" for 1931 £0.58

1953 SK1 soldering Kit - contains 15 watt soldering iron with 3/16" bit plus two spare bits, a reel of solder, heat-sink and a booklet 'How to Solder' £7.28

1939 ST3 iron stand made from high grade bakelite - chrom plated steel spring, suit all models - includes accommodation for six bits and two sponges to keep the iron bits clean £1.89

1724 Model MLX as X25 iron but 12 volts £5.59

CASES AND BOXES

VERO plastic case box. These boxes consist of top and bottom sections which include fixings points for horizontal mounting PC boards/chassis plates, the two sections are held together by four screws which enter through the base and are concealed by plastic feet.

No.	Length	Width	Height	Price
170	140mm	40mm	205mm	£4.35
171	140mm	75mm	205mm	£4.85
172	140mm	110mm	205mm	£6.30

INSTRUMENT CASES in two sections vinyl covered top and sides, aluminium bottom, front and back.

No.	Length	Width	Height	Price
155	8in	5 1/2in	2in	£1.72
156	11in	6in	3in	£2.92
157	6in	4 1/2in	1 1/2in	£1.79
158	9in	5 1/2in	2 1/2in	£2.43

ALUMINIUM BOXES made from bright anodized, folded construction each box complete with half inch deep lid and screws.

No.	Length	Width	Height	Price
159	5 1/2in	2 1/2in	1 1/2in	£0.85
160	4in	4in	1 1/2in	£0.85
161	4in	2 1/2in	1 1/2in	£0.85
162	5 1/2in	4in	1 1/2in	£0.97
163	4in	2 1/2in	2in	£0.87
164	3in	2in	2 1/2in	£0.60
165	7in	5in	2 1/2in	£1.43
166	8in	6in	3in	£1.63
167	6in	4in	2in	£1.18

SLOPE front aluminium boxes with black vinyl base and sides & aluminium back, top & front - strong construction easily accessible.

169	2 1/2in	5 1/2in	2 1/2in	3 1/2in	8in	£5.45	
168	2 1/2in	7 1/2in	4in	16in	4 1/2in	11in	£8.21

AUDIO MODULES

AMPLIFIERS

AL10	3 watt Audio Amplifier Module 22-32v supply	£3.53
AL20	5 watt Audio Amplifier Module 22-32v supply	£4.11
AL30A	7-10 watt Audio Amplifier Module 22-32v supply	£4.78
AL60	15-25 watt Audio Amplifier Module 30-50v supply	£5.92
AL80	35 watt Audio Amplifier Module 40-60v supply	£9.28
AL120	50 watt Audio Amplifier Module 50-70v supply	£15.11
AL250	125 watt Audio Amplifier Module 50-80v supply	£22.54

STEREO PRE-AMPLIFIERS

PA12	Supply voltage 22-32v input sensitivity 300mv suit AL10/AL20/AL30	£9.83
PA100	Supply voltage 24-36v Inputs - Tape, Tuner, Mag P.U. Suit AL60/AL80	£20.30
PA200	Supply voltage 35-70v inputs - Tape, Tuner, Mag P.U. Suit AL80/AL120/AL250	£20.98

MONO PRE-AMPLIFIERS

MM100	Supply voltage 40-65v inputs: Mag. P.U., Tape Microphone Max. output 500mv	£14.29
MM100G	Supply voltage 40-65v inputs: 2 Guitars, Microphones Max. output 500mv	£14.29

POWER SUPPLIES

PS12	24v Supply suit 2 - AL10, 2 - AL20, 2 - AL30 & PA12/S.450	£1.90
SPM80	33v Stabilised supply - suit 2 - AL60, PA100 to 15 watts	£5.57
SPM120/45	45v Stabilised supply - suit 2 - AL60, PA100 to 25 watts	£7.34
SPM120/55	55v Stabilised supply - suit 2 - AL80, PA200, 1 - AL250, PA200	£7.34
SPM120/65	65v Stabilised supply - suit 2 - AL120, PA200, 1 - AL250, PA200	£7.34
SG30	15-0 16 Stabilised power supply for 2 - GE100MKII	£4.37

MISCELLANEOUS

MPA30	Stereo Magnetic Cartridge Pre-Amplifier input 3.5mv Output 100mv	£2.76
S.450	Stereo FM Tuner Supply Voltage 20-30v - Varicap tuned	£29.39
STEREO30	Complete 7 watt per Channel Stereo Amplifier Board - includes amps, pre-amp, power supply, front panel, knobs etc. - requires 2050 Transformer	£24.25
BP124	5 watt 12v max - Siren Alarm Module	£4.43
GE100MKII	10 channel mono-graphic equaliser complete with sliders and knobs	£26.45
VPS30	Variable regulated stabilised power supply 2-30V 0-2amps	£8.74

TRANSFORMERS

No.	Description	P&P
2034	1.7 amp 35v suit SPM80	£6.21 £1.21
2035	2 amp 55v	£7.30 £1.47
2036	750mA 17v suit PS12	£3.68
2040	1.5 amp 0-45v-55v suit SPM120/45, SPM120/55v	£5.98 £1.21
2041	2 amp 0-55v-65v suit SPM120/55, SPM120/65v	£7.82 £1.47
2050	1 amp 0-20v suit Stereo 30	£3.74 £0.75
1725	150mA 15-0-15v suit SG30	£2.04

ACCESSORIES

139	Teak Cabinet suit Stereo 30, 320 - 235 - 81mm	£8.05
140	Teak Cabinet suit STA 15 425 - 290 - 95mm	£9.78
FP100	Front Panel for PA100 & PA200	£2.07
BP100	Back Panel for PA100 & PA200	£1.84
GE100FP	Front Panel for one GE100MKII	£2.05
2240	Kit of parts including Teak Cabinet, chassis sockets, knobs to build 15 watt stereo amplifier	£22.94

SPECIAL OFFERS

MINIDRILL 12v hand held battery-operated mini drill, 7,500 r.p.m. Collet chuck ideal for drilling printed circuits or model making. No. 1402. Complete with 2 drills 1 and 15

TRANSFORMER 240v Primary 0-20v at 2A Secondary. By removing 5 turns for each volt from the secondary winding, any voltage up to 20v at 2A is obtainable. Ideal for the experimenter. No. 2042. £150 + 86p P & P

ANTEX MLX Soldering Iron. Sturdy 25 watt iron complete with: 4j metres of 2 core cable. Works off a 12 volt battery. ideal for Car. Boat. Caravan. No. 1724. £5.99

METAL FOIL CAPACITOR PAKS

16204 - Containing 50 metal foil capacitor like Mullard C280 series. Mixed values ranging for 01uf - 2.2uf. Complete with identification sheet £1.38

TRIACS

2 amp volts	T05 case No.	Price	10 amp volts	Price	
100	TR12A/100	£0.56	100	TR110A/100	£0.88
200	TR12A/200	£0.59	200	TR110A/200	£1.06
400	TR12A/400	£0.62	400	TR110A/400	£1.29
6 amp volts			10 amp volts		
100	TR16A/100	£0.59	400	TR110A/400P	£1.29
200	TR16A/200	£0.70			
400	TR16A/400	£0.88			

SILICON RECTIFIERS

200mA	Price	3 Amp	Price
IS920 50V	£0.07	IN5400 50V	£0.16
IS921 100V	£0.08	IN5401 100V	£0.17
IS922 150V	£0.09	IN5402 200V	£0.18
IS923 200V	£0.10	IN544 400V	£0.20
IS924 300V	£0.12	IN5406 600V	£0.24
		IN5407 800V	£0.25
		IN5408 1000V	£0.35
1 Amp		10 Amp	
IN4001 50V	£0.05	IS1050 50V	£0.22
IN4002 100V	£0.06	IS10100 100V	£0.24
IN4003 200V	£0.07	IS10200 200V	£0.26
IN4004 400V	£0.08	IS10400 400V	£0.40
IN4005 600V	£0.09	IS10600 600V	£0.48
IN4006 800V	£0.10	IS10800 800V	£0.59
IN4007 1000V	£0.12	IS101000 1000V	£0.69
		IS1012000 1200V	£0.79
1.5 Amp		30 Amp	
ISO15 50V	£0.10	IS3050 50V	£0.64
ISO20 100V	£0.12	IS30100 100V	£0.79
ISO21 200V	£0.13	IS30200 200V	£1.07
ISO23 400V	£0.15	IS30400 400V	£1.44
ISO25 600V	£0.16	IS30600 600V	£2.02
ISO27 800V	£0.18	IS30800 800V	£2.23
ISO29 1000V	£0.23	IS301000 1000V	£2.66
ISO31 1200V	£0.29	IS301200 1200V	£3.31
60 Amp		IS70400 400V	£2.01
IS7050 50V	£0.86	IS70600 600V	£2.59
IS70100 100V	£0.97	IS70800 800V	£2.88
IS70200 200V	£1.38	IS701000 1000V	£3.45


THYRISTORS

600ma	TO 18 Case	7 amp	TO 48 Case
Volts No.	Price	Volts No.	Price
10 THY600/10	£0.17	50 THY7A/50	£0.55
20 THY600/20	£0.18	100 THY7A/100	£0.59
30 THY600/30	£0.23	200 THY7A/200	£0.66
50 THY600/50	£0.25	400 THY7A/400	£0.71
100 THY600/100	£0.29	600 THY7A/600	£1.14
200 THY600/200	£0.44	800 THY7A/800	£1.06
400 THY600/400	£0.51	10 amp	TO 48 Case
		Volts No.	Price
		50 THY10A/50	£0.59
		100 THY10A/100	£0.66
		200 THY10A/200	£0.71
		400 THY10A/400	£0.81
		600 THY10A/600	£1.14
		800 THY10A/800	£1.40
		15 amp	TO 48 Case
		Volts No.	Price
		50 THY15A/50	£0.62
		100 THY15A/100	£0.67
		200 THY15A/200	£0.71
		400 THY15A/400	£0.89
		600 THY15A/600	£1.04
		800 THY15A/800	£1.60
		30 amp	TO 94 Case
		Volts No.	Price
		50 THY30A/50	£1.38
		100 THY30A/100	£1.64
		200 THY30A/200	£1.87
		400 THY30A/400	£2.06
		600 THY30A/600	£4.03
5 amp	TO 66 Case		
Volts No.	Price		
50 THY5A/50	£0.41		
100 THY5A/100	£0.52		
200 THY5A/200	£0.58		
400 THY5A/400	£0.66		
600 THY5A/600	£0.79		
800 THY5A/800	£0.93		
		110	Price
		BT110/500R	£0.92
		BT102/500R	£0.92
		BT106	£1.44
		BT107	£1.07
		BT108	£1.13
		2N3228	£0.81
		2N3525	£0.89
		BTX30/50L	£0.38
		BTX30/400L	£0.53
		600 THY5A/600P	£0.79
		C106/4	£0.69
		800 THY5A/800P	£0.93
		BT116	£1.73

ZENER DIODES

400 mw (Bz

Complete Audio/Tuner Kits

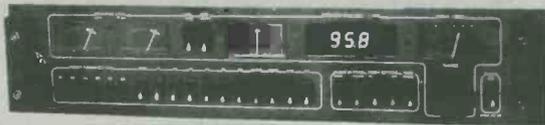

Mk III FM Tuner series

Carriage for Mk III tuner £3 inc

The Mark III series FM tuner has been updated, and now includes a centre zero tuning meter as standard. The instruction manual has been meticulously revised, enabling easy assembly by constructors of various levels of experience - a preview copy may be purchased for £1.00.

Mk III A series 'Reference series' tuner modules£171.35 inc.
Mk III B series 'Hyperfi' modules, with switched IF BW, pilot cancel decoder£198.95 inc.

A matching synthesiser unit will be made available later this year, and can be retrofitted to either version. All versions include digital frequency readout/clock, VU deviation meters, 6 preset stations, 10 turn pot manual tuning, toroidal PSU, output level adjustment, 110/240v AC input. Full alignment service available.

Power Amplifier

Style and performance - with a real 'belt and braces' PSU design.

After a couple of previous comments, it seems that many of you are waiting to hear about the matching HMOSFET power amplifier for the Mk III tuner. Well, it's out at last - complete with twin toroidal PSUs for comfortable 80W RMS per channel, over 100W peak, but limited by thermal shutdown of the HMOS. 10W-100W log LED output peak indicator, DC offset protection and switch-on pause relay. AC or DC input coupling, direct or relay protected output terminals. The works. Only one version of this item: Complete kit£178.25 inc. Carr. £5.

Preamplifier

More features and facilities, thanks to DC switching and control design

Featuring the most comprehensive audio preamplifier yet..... DC switching of 7 inputs, plus two tape in/out's. 2 low pass, 2 high pass active filters, genuine volume related loudness, 1dB channel matching, with DC volume, balance, bass and treble controls. Suitable for bus/remote control, tape dubbing, switched monitor etc. 80dB S/N+, THD -75dB or better. Pluggable PU equalization boards, tone control override. Price for complete unit about £149 ex VAT.

Semiconductors

Radio/Communications IC's

FOR COMPLETE LISTINGS - SEE OUR NEW PRICELIST



CA3089E	2.11	HA1197	1.61	SD6000	4.31
CA3189E	2.53	CA3123E	1.61	TDA4420	2.59
HA1137W	1.95	TDA1072	3.09	MC1330P	1.38
HA11225	2.47	TBA651	2.53	MC1350P	1.38
HA12412	2.81	TDA1090	3.51	KB4412	2.24
KB4420	1.96	TDA1220	1.61	KB4413	2.24
TBA1205	1.15	TDA1083	2.24	KB4417	2.53
KB4406	0.80	TDA1082	2.24	MC3357P	3.16

SL1610	1.84	SL1626	2.80
SL1611	1.84	SL1630	1.86
SL1612	1.84	SL1640	2.17
SL1613	2.17	SL1641	2.17
SL1620	2.50	SL6900	4.31
SL1623	2.80	SL6640	3.16
SL1624	3.77	SL6690	3.68
SL1625	2.50	MC1498	1.44

VARICAP DIODES.....

A section from our PL:

BA102	0.35	16:1 ratio AM tuning	2.93
BB204	0.41	KV1215 9v triple	2.01
BB105	0.41	KV1211 9v dual	2.01
BB109	0.31	KV1225 25v triple	3.16
MVAM2	1.93	BB212 9v dual	2.25

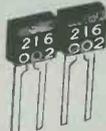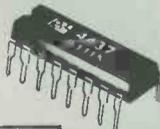

POWER MOSFETS

100W PA's made simple

Since pioneering the 100W complementary MOSFET technique - Hitachi have developed a range of output devices and drivers that ought to revolutionise opinions and attitudes towards the design of all LF amplification systems. We have a new 48 page application note (£1.50 inc) and complete sets of parts, modules and now the new complete PA system (see above).
25K133 120v N-ch 100W MOSFET £6.33 2S/48 Pch complement £6.33
25K135 160v N-ch 100W MOSFET £7.29 2S/50 Pch complement £7.39
PA1018 Kit for 100W MOSFET PA less Heatsink £16.10. (£23 inc heatsink/bkt)

ULTRA LOW NOISE PU PREAMPLIFIER

The HA12017 is the last word in PU preamps, and general low noise audio design. It is an SIL IC, with 86dB S/N in RIAA configuration, 10v RMS output capability, 0.002% typ THD at 10v RMS output (imagine the overload margin !!). It comfortably exceeds discrete circuit designs in terms of price/performance, and takes the art beyond the TDA1042's capabilities. [Replaces HA1457] £1.80 each - or an RIAA applications PCB with two ICs for £5.75. Complete with Rs&Cs £9.95.

Radio Control ICs

We have various RC ICs, including NE544 NE5044, and two new ones from OKI

KB4445 - 4 channel dig. prop. FM TX IC. 30mW out (amplifiable) -£2.30 inc
KB4446 - 4/5 ch. dig. prop FM RX IC. Suits KB4445 or RCME syst. £2.65 inc
KB4445/6 pair: £4.75. New 8 page data sheet 35p + SAE. More RC ICs in list

CMOS, LPSNTTL, TTL, MPU:

Most CMOS is available in low volume - also LPSN. Standard linears and TTL OK.

Listings in the new pricelist.

Things like ICM7216B, ICL8038, 8080A, 6800P, 2708, NE555, NE556, etc

Coming Soon..... Contain yourselves, RF fans I Not yet ready for a full launch until autumn, but previewed here:-

SSB transceiver system : 10kHz to 1000MHz !!

A modular VLF to UHF SSB TX/RX system at last. With the correct first mixer, the basic PCB covers 10kHz to 1000MHz - using LO fed from ext. source (Our 2 IC Mullard synth for instance) and RF PA for TX. OP. 0.2uV basic sensitivity in HF, Typ cost for HF synth SSB RX will be less than £200. Add an RF PA for full TRX for another £50. See one in our foyer, and marvel.

CATALOGUES, etc. etc. all shown for £1.60
PRICES SHOWN HERE INCLUDE VAT
POSTPACKAGE CHARGES NOW 50p

Please send an SAE with all enquiries. Phone orders by ACCESS - but minimum £5 Callers welcome

ambit
INTERNATIONAL

200 North Service Road, Brentwood, Essex


TELEPHONE (STD 0277) 230909 TELEX 995194 AMBIT G POSTCODE CM14 4SG

Parts 1-3
AMBIT catalogues
60p ea, or
£1.60 the lot.

Radio/Audio/Communications Modules

LW-MW-SW-SW DC tuned and switched

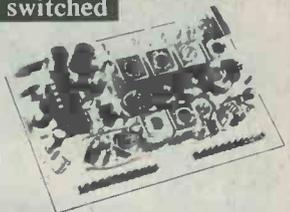91072- All switching of bands by a single pin to gnd. Varicap tuned, with LO output for synth. MW/LW version or MW/LW plus 1 or 2 SW bands MW/LW: £15.58 +1SW £16.73



VHF Tunerheads

Europe's largest stock range for broadcast and communications. Probably also the world's - details in the catalogues and PL. Specials are also supplied in the region 30-220MHz.

Pilot Cancel PLL Stereo decoders

Again, Europe's widest range of stereo decoders including pilot cancel PLL types. The pic shows the 944378 - pilot cancel including post decoder 26/38kHz filtering and muting preamp output

944378-2
£26.45



Switched bandwidth FM IF strips

Broadcast FM IF strips for all occasions, including the new 911225 - with diode switched narrow filter option, ultra linear phase ceramic filters, 84dB S/N, and 0.04% THD (40kHz deviation). Plus usual things like AGC, AFC, dev. mute, level meter drive. £23.95 (supplied in screen can with 0.1 edge connection system) Also the 7230 hyperfi series - as the 911225, but with slope controlled AFC that operates in conjunction with signal level - and an extra IF amp stage for DXing.

Various digital frequency displays

The World's largest range of receiver DFM's is now joined by the DFM7 (shown) - and L shaped version of the DFM3 with remote display mount connector possibility. 1kHz SW resolution with 455kHz or 10.7MHz offsets, 100Hz res up to 3.9999MHz, and VHF to 299.99 MHz in 10kHz steps : £41.75



Components

Crystal Filters

Most popular types are available - ex-stock, and in quantity.

10.7MHz	25kHz Channel spacing 8pole	£16.67
	12kHz	£17.82
	2.4kHz SSB	£19.78
	Monolithic dual roofing filter	£2.30
34.5MHz	1.3dB loss, 80dB stopband HF first filter in synth. RX	£36.80
RC XTALS	FM pairs (no spilt's)	£3.74
	AM pairs ..	£3.57
USB/LSB	Xtals for 10.7SSB filter	£2.88 ea



Piezo Sounders

The most efficient warning sounders yet

The latest thing in electro-acoustic efficiency. 1mA of drive from CMOS will give an SPL of 83dB - 10v RMS drive from CMOS uses 3mA for 100dB SPL at 4.8kHz (88dB at 1.65kHz) The data sheets shows various drive circuits, and give full specifications with regard to broadband responses and power consumption etc. 1 off 44p inc. 100 off 28.75p (25p ex vat)



Keyboard switches and caps

From the world's most widely used switch manufacturers - ALPS - come the biggest and best range of keyswitches, and data entry keyboard switches. The SCMB1101 is shown here, with the KTS 2-part cap (with clear top, to enable easy fitting of your chosen legend. Other types are available with built in LED, 90° mounting etc. SCMB1101 : 17p, KTS : 16p - or 29p/pair



LCD CLOCKS

Clocks use 7.5v at 15uA only - DVM 9v/1mA

LCD DVM

CM161:	7mm LCD 12/24hr, alarms etc	£11.44 each
CM172:	13mm, 12hr, alarms, timer etc	£14.32 each
CM174:	13mm, 12hr, min/sec stopwatch	£14.32 ea
DVM 176:	ICM7106 based LCD 3 1/2 digit	£22.36 each



WHAT'S NEW at AMBIT

NEW PRICELIST/SHORTFORM:- 28 pages, FOC with A5 SAE pse

Bigger print than our recent one page list - and vastly extended

If you still need convincing to invest £1.60 in the cats, be mean and get this first.

POWER MOSFET APPLICATIONS HANDBOOK by HITACHI :

£1.50 each - or free with pairs of HMOS and the PA1018.

Everything you should know about HMOSFET devices theory and applications.

Conquer the chip.

Be it career, hobby or interest, like it or not the Silicon Chip will revolutionise every human activity over the next ten years.

Knowledge of its operation and its use is vital. Knowledge you can attain, through us, in simple, easy to understand stages.

Learn the technology of the future today in your own home.

ELECTRONICS



Build your own oscilloscope

Learn to draw and understand circuits.

Carry out over 40 experiments.

DIGITAL TECHNIQUES

From watches to sophisticated instrumentation, Digital Electronics adds scope to hobby or career.



COMPUTER TECHNOLOGY


Learn to operate and programme your own home computer.



FREE BROCHURES



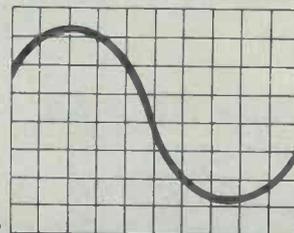No previous knowledge is necessary.
— Just clip the coupon for a brochure



TUTORCOURSE ELECTRONICS

Please rush me details of your ELECTRONICS COURSE

Name

Address

RER/7

Block Caps. Please

Post now, without obligation to:

British National Radio & Electronics School.

P.O. Box 156, Jersey, Channel Isles

THE MODERN BOOK CO

UNDERSTANDING MICROPROCESSORS Texas Ins. £4.25

For the newcomer to Microprocessors. An in-depth look at the magic of the solid-state chips that are affecting our lives. Written in everyday language. Ideal for self-paced individualised learning.

ELECTRONIC FAULT DIAGNOSIS
By I. R. Sinclair Price £3.15

ELECTRONIC PROJECTS IN AUDIO
by R. A. Penfold Price £2.50

OP-AMPS THEIR PRINCIPLES & APPL.
by J. B. Dance Price £2.50

PRINTED CIRCUIT ASSEMBLY
by M. J. Hughes Price £2.10

ELECTRONIC SECURITY DEVICES
by R. A. Penfold Price £1.65

UNDERSTANDING DIGITAL ELECTRONICS
by Texas Inst. Price £4.00

UNDERSTANDING MICRO-PROCESSORS
by Motorola Price £4.30

THE FIRST BK OF MICROCOMPUTERS
by R. Moody Price £3.35

HOW TO BUILD YOUR OWN SOLID STATE OSCILLOSCOPE
by F. G. Rayer Price £1.70

THE OSCILLOSCOPE IN USE
by I. R. Sinclair Price £2.85

AUDIO AMPLIFIERS FOR THE HOME CONSTRUCTOR
by I. R. Sinclair £2.55

REPAIRING POCKET TRANSISTOR RADIOS
by I. R. Sinclair Price £2.55

MAKING & REPAIRING TRANSISTOR RADIOS
by W. Oliver Price £2.30

WORLD RADIO TV HANDBOOK
by J. M. Frost Price £9.25

PROJECTS IN RADIO & ELECTRONICS
by I. R. Sinclair Price £2.50

ELECTRONIC PROJECTS IN THE HOME
by O. Bishop Price £2.50

SIMPLE CIRCUIT BUILDING
by P. C. Graham Price £2.20

110 SEMICONDUCTOR PROJECTS FOR THE HOME CONSTRUCTOR
by R. M. Marston Price £3.20

HAM RADIO
by K. Ulllyett Price £5.00

UNDERSTANDING SOLID-STATE ELECTRONICS
by Texas Inst. Price £3.95

A SIMPLE GUIDE TO HOME COMPUTERS
by S. Ditlea Price £4.00

HOW TO BUILD A COMPUTER-CONTROLLED ROBOT
by T. Loofbourrow Price £5.30

THE CATHODE-RAY OSCILLOSCOPE & ITS USE
by G. N. Patchett Price £4.00

HOW TO GET THE BEST OUT OF YOUR TAPE RECORDER
by P. J. Guy Price £1.90

A GUIDE TO AMATEUR RADIO
by P. Hawker Price £1.70

RADIO CONSTRUCTION FOR AMATEURS
by R. H. Warring Price £2.80

MAKING TRANSISTOR RADIOS A BEGINNER'S GUIDE
by R. H. Warring Price £2.90

We have the Finest Selection of English and American Radio Books in the Country

PRICES INCLUDE POSTAGE

19-21 PRAED STREET (Dept RC) LONDON W2 1NP

Telephone: 01-402 9176

20Hz to 100MHz - £77.55

(+ VAT 15% & P & P. £90.91) Export + 10%



It's an incredible price for a very credible frequency counter . . . Continental's MAX-100.

It comes to you from a major American corporation and has one operating range, and one only: 20Hz to 100MHz, minimum. (Guaranteed.)

So we've pensioned off the range selector, and fitted the sharpest of LED displays. (Sheer brilliance.)

We've also designed the MAX-100 around the latest in LSI technology; and built-in high sensitivity, with a 30mV trigger level; protection against high transients; and an outstanding accuracy of 3ppm. (What performance!)

But, most importantly, the MAX-100 is totally automatic — and available now. In fact, you could have one tomorrow.

Hesitating? Just take a look at the spec. Then, if you're ready to order immediately, call us on (0799) 21682. And

your MAX-100 could be on its way, today! (Continental's are great performers, too.)

For data, please use our enquiry number.

Specification * Frequency range 20Hz to 100MHz * Input impedance 1 megohm shunted by 56pF * Sensitivity 30mV to 300mV r.m.s., from 20Hz to 100MHz * Timebase accuracy 3ppm * Temperature stability 0.2ppm per °C * Max. ageing rate 10ppm per year * Overfrequency indication * Low battery power alarm * Operates from a.c. mains, dry or rechargeable cells, or 12Vd.c. auto battery * Dimensions 45 x 187 x 143 mm. * Options: 12V auto. cigar lighter adaptor; battery eliminator/charger; r.f. antenna; low-loss r.f. tap; and carrying case.

Quality. At a low, low, price.



C.S.C. (UK) Limited, Dept. 16D
Unit 1, Shire Hill Industrial Estate,
Saffron Walden, Essex CB11 3AQ.
Tel: Saffron Walden (0799) 21682
Telex: 817477.

TRANSISTORS

AC126	16p	BD235	35p	MPP131 Dual	2N2586	15p	
AC127	16p	BD238	25p	MOSFET	2N2614	4p	
AC128	5p	BD239C	29p	MPU131 Prog. Uni. J.	2N2887	£2	
AC153	11p	BD244/A/C	30p		2N2894	11p	
AC176	11p	BD246	32p	MRF502 Improved	2N2904	9p	
AC188	10p	BD253	44p	BFY90	2N2905	15p	
ACY20	30p	BD375	35p	16A Russian	2N2906	9p	
ACY21	20p	BD437	35p	42A Russian	2N2907/A	9p	
ACY28	22p	BD438	28p	NKT A49	2N2926	4p	
AD161/162		BD678 Pwr. Darl.	50p	NKT A52	2N2920	25p	
match pair	70p	BDX33B Pwr Darl.	44p	NKT B54	2N3053	16p	
AF116	21p	BDX77	97p	NKT152	2N3054	35p	
AF119	35p	BDY20	86p	NKT153	2N3055RCA	68p	
AF124	27p	BF115	18p	NKT154	24p	2N3133	24p
AF126	27p	BF137	11p	NKT251	18p	2N3283	25p
AF127	27p	BF167	18p	NKT775	16p	2N3418	15p
AF139	23p	BF173	18p	NKTME2	13p	2N3553	56p
AF178	35p	BF178	23p	OC41	4p	2N3583	18p
AF180	35p	BF179	23p	OC43	55p	2N3645	3p
AF181	33p	BF180	12p	OC44	4p	2N3703	3p
AF239	35p	BF181	8p	OC45	13p	2N3704	4p
ASV60	35p	BF182	18p	OC71	4p	2N3707	3p
ASV63	35p	BF183	18p	OC72 (XK120)	15p	2N3711	3p
ASV73	35p	BF184	18p	OC76	46p	2N3714 80v 150w	54p
ASZ21	4p	BF185	18p	OC77	46p		
AU110	£1.43	BF194/A	5p	OC84	30p	2N3794	14p
AU113	£1.18	BF195/C/D	5p	OC200	41p	2N3799	18p
AU110	70p	BF196	5p	OC201	66p	2N3823	25p
BC107/A/B	6p	BF197	5p	OC202	66p	2N3904	3p
BC108/A/B/C	6p	BF198	5p	OC603	50p	2N3906	8p
BC109/B/C	6p	BF200	13p	OC701	50p	2N4000	15p
BC125B	3p	BF224	4p	ON222	23p	2N4026	15p
BC140	15p	BF244C	7p	P348A	24p	2N4031	15p
BC141	11p	BF245	6p	P7029	30p	2N4062	4p
BC147/A/B/C	5p	BF256	4p	PXB103	25p	2N4285	17p
BC148/A/B/C	5p	BF256B/LC	3p	R1039 (2010)	54p	2N4891	30p
BC149/A/B/C/S	5p	BF257	20p	R2008B	£1.18	2N4898 40v 25w	36p
BC154	7p	BF262	29p	R2101B	£1.18	2N4900 80v 25w	36p
BC157/A/B	5p	BF263	29p	R2540	£1.70	2N4918	15p
BC158/A/B	5p	BF274	8p	S3017	25p	2N5147	15p
BC159/B/C	8p	BF324	34p	SB240	26p	2N5247	40p
BC171B	8p	BF336	16p	SFT357	28p	2N5248 FET	3p
BC172	6p	BF355	15p	SJE5039	8p	2N5293	30p
BC172c	7p	BF394B	3p	SL102	40p	2N5295	30p
BC173	4p	BF416	6p	TE886	£1	2N5449	3p
BC177A	14p	BF434	10p	TIP30	22p	2N5484	37p
BC178A/B/C	14p	BF615	27p	TIP31	24p	2N5927	36p
BC179B	14p	BF617	27p	TIP32C	26p	2N5954 P, 80v, 40w	36p
BC182/AL	5p	BFQ35	15p	TIP48	33p		
BC182L	3p	BFQ37	15p	TIS60GY	3p	2N6027/8 P.U.J.T.	3p
BC183/A/AL/LC/B	3p	BFQ85	15p	TIS73L	3p	TIS61	24p
		BFR34A	36p	TIS90	4p	2N6254	36p
		BFR38	68p	TIS91	3p	2N6385 Pwr. Darl.	54p
		BFR86	19p	TIS92GY	14p	2S701	18p
		BFS21 FET pair	£3	TIS98	3p	2SA12	42p
		BFS28 Dual MOS FET	50p	TK24	20p	2SA50	36p
BC184L	3p	BFT30	15p	TOR04	1p	2SA80	36p
BC186	21p	BFT31	15p	TOR37	1p	2SA83	36p
BC187	8p	BFT39	15p	TOR45A/B	1p	2SA141	36p
BC204	11p	BFT41	15p	TOR47	1p	2SA142	36p
BC212/L/B	5p	BFT43	15p	TOR50	1p	2SA234	50p
BC213L	4p	BFT60	6p	TOR57	1p	2SA235	50p
BC213LA	3p	BFT71	15p	V435	20p	2SA354	38p
BC213LB	4p	BFT71	15p	U14710	20p	2SA360	34p
BC214B	5p	BF170	15p	ZT403P	3p	2SA367	56p
BC214L	3p	BF171	15p	ZT1486	£1.10	2SA518	38p
BC237A	7p	BFW10 FET	46p	ZTX300	9p	2SA634	80p
BC238	5p	BFW11 FET	46p	ZTX327	18p	2SB56	18p
BC238B/C	7p	BFW31	15p	ZTX341	9p	2SB77	25p
BC239C	7p	BFW57	18p	ZG103	33p	2SB134	25p
BC251	3p	BFX12	23p	ZG302	12p	2SB135	25p
BC257B	7p	BFX29	15p	ZG309	30p	2SB136	25p
BC258B/C	7p	BFX30	16p	ZG339A	20p	2SB156	60p
BC259C	7p	BFX37	16p	ZG371	18p	2SB175	20p
BC302	15p	BFX42	23p	2N456A	71p	2SB176	20p
BC304	15p	BFX48	14p	2N597	16p	2SB187	25p
BC307	7p	BFX85	20p	2N598	16p	2SB457	25p
BC308B/C	7p	BFX88	20p	2N601	£1.50	2SD315D	80p
BC309B	7p	BFY39	20p	2N644	22p	40313 N, 35w, 300v	54p
BC327	5p	BFY50	13p	2N706A	12p	40235	50p
BC328	6p	BFY52	13p	2N706	9p	40250	36p
BC338	5p	BFY75	15p	2N914	15p	40816	30p
BC382L	7p	BFY90	40p	2N918	12p		
BC384B	7p	BLY10	23p	2N929	16p		
BC384L	7p	BR101	20p	2N984	28p		
BC384/A/B	5p	BR139	29p	2N987	45p		
BC384/B/C	5p	BRY56	29p	2N1091	16p		
BC390	5p	BSV64	36p	2N1132	14p		
BC395	5p	BSV79	50p	2N1302	16p		
BC612L	4p	BSV80	50p	2N1303	16p		
BCW71R	1p	BSV81	75p	2N1395	25p		
BCX32	10p	BSX19	15p	2N1484	£1.15		
BCX34	10p	BSX20 VHF Osc.	10p	2N1487	90p		
BCX36	10p	BSX21	10p	2N1490	£3		
BCY11	28p	BSX78	8p	2N1500	30p		
BCY31	59p	BSY40	30p	2N1507	18p		
BCY56	10p	BSY95A	10p	2N1711	13p		
BCY70	8p	BU105	64p	2N1716	15p		
BCY71	8p	BU105/04	78p	2N1748	28p		
BCY79B	15p	BU204	63p	2N2192A	15p		
BCZ11	32p	BU208	90p	2N2217	15p		
BD113	57p	BUX 66P, 150v, 35w,	54p	2N2219	14p		
BD115	35p	D1693	£2.85	2N2221A	9p		
BD(BRC)116	45p	GET102	46p	2N2222A	8p		
BD133	28p	GET111	45p	2N2369	10p		
BD135	25p	GET120	30p	2N2401	7p		
BD136	25p	M103G MOSFET	30p	2N2412	27p		
BD137	28p	M393	25p	2N2483	28p		
BD138	28p	MD7000	£2.25	2N2484	10p		
BD137/8	45p	ME2	13p				
match pair	60p	ME0412	13p				
BD139	17p	ME8003	20p				
BD140	26p	MJ481 (BDY23)	23p				
BD142	35p	MJE371	40p				
BD156	50p	MJE2371	80p				
BD201	50p	M 15 Russian	25p				
BD202	64p	M 15 Russian	25p				
BD203	86p	M 15 Russian	25p				
BD204	86p	M 15 Russian	25p				
BD232	52p	M 15 Russian	25p				
BD233	20p	M 15 Russian	25p				
BD234	13p	M 15 Russian	25p				

ELECTROLYTICS - Hundreds more in catalogue Value/Voltage

Tant Bead .033/35v 3p. .22, 47/35v 6p. .1, 1/35v, 8p. .22/20v. 3.3/16v, 4.7/35v, 10/25v, 22/16v 9p. 10/3v 10p. 2.2/50v 11p. 3.3/35v 12p.

Wire End
63v 2.2, 31p. 4.7, 4p. 10, 33, 5p. 2.5 3p. 1.5, 22, 47 6p. 68, 100, 220 8p. 150 71p. 330 8p. 470 12p. 1000 29p. 25v 6, 6.4, 10, 12, 16, 22, 25, 30, 33, 40, 47, 50, 64 4p. 100, 150, 160, 330 6p. 220 7p. 250, 300, 470 8p. 680 11p. 1000 11p. 22/16. 3.3/50, 10/50 4p. 100/10, 47/16 5p. 100/16, 100/35, 220/16 6p. 470/6.3, 10/350, 470/16 8p. 1000/16 10p. 1500/6.3, 71p. 2200/10 20p. 4700/10 9p. 15/160 7p. CANS 250/300, 45p. 25,000/25 50p. 100/275 14p. 2000/100 82p. 1000/100 70p. 8 plus 8/450 9p. 10,000/16 36p. 2000/50 35p. 2000 plus 2000/50 40p. Full range in catalogue.

CAPACITORS: up to 500v: Ceramic up to 4700pF 2p. to .047 21p. to .15p. to 1mfd 8p. Silvermica up to 5000pF 5p. to .01 21p. Poly, etc up to 820pF 3p. to 0.1 2p. to .27 5p. to .47 5p. 5.9p. 68 11p. 047/630V 11p. .1, .22/900v 15p. .3/600v 4p. .97/160v 71p. 1mFd up to 2.5m 10p. 1.5/100 9p. 2.2mFd up to 100v 14p. 4/16v 25p. 4.7/63 10p. 6.8/63, 25/50 10p. 10/100 30p. 8/20v 40p. CAN 1/350 12p. 8/660 vac £2. 3/660 vac £1.75. 5/150 70p. 6/450 vac 98p. Pulse Tube: 8-12kv, 10, 47, 56, 82, 100, 120, 300pF 2p each. Hundreds of others in Catalogue

MARKED FULL SPEC DIGITAL I.C.'s
Branded - New 25 for £1 Mixed

TV MAINS DROPPERS
5 assorted multiple units for 45p

16 Watt Power Amp. Module
35v 1A power required, giving 16 watt RMS into 8 £3.65
RS neg. volt regulator 103, 306-099 (equiv. MPC900) 10A, 100 watt 4-30v. Adjustable short circuit protection. Sacrifice at 75p

RESISTORS
1/8 1/4 1/2 watt . . . 1p
1 watt 11p
1 or 2% 11p
Up to 15W w/wound 10p, 10 same value 75p

Skeleton Presets
Slider, horizontal or vertical standard 7p or submin 5p.

RELAYS
RS/Alma reed relay, 1K12v or 3k 12-18-30v d.c. coil, normally open 36p
12v d.p.c.o. heavy duty 60c
octal £1
600 4 p/co min sealed 75p. Base 10p.
D.I.L. 3.7-12V S.P. £1.00

THERMISTORS and V.D.R.'s
CZ1/2/6/11/14, KR22, KT150, VA1005/6/8/1010/1033/4/7/8/9 1040/1053/5 /1066/7/1074/6/7/1082/6/1091/6/7/8/1100/3/8/8602. 338 / 340 / 350 / 352 / YF020 . E220Z2 /02 KR100C . KR150 . E23 glass bead . YG150-S534 bead . KB13 E299 DHP230 . 300K 2 Glass bead All 7p each

POTS
Wirewound 38p. Log or Lin rotary 22p, or slide 30p. With switch 40p, Dual 45p. Dual switch 55p 1.5m. Edgetype 10 for 40p.

END OF LINE STOCK ITEMS AND COMPUTER & AUDIO BOARDS/ASSEMBLIES WITH VARYING CONTENTS INCLUDE ZENER, GOLD BOND, SILICON, GERMANIUM, LOW AND HIGH POWER TRANSISTORS AND DIODES, HI STAB RESISTORS, CAPACITORS, ELECTROLYTICS, TRIMPOTS, POT CORES, CHOKE, INTEGRATED CIRCUITS, ETC.
3lb for £2.30 7lb for £4.30

1k horizontal preset with knob 10 for 40p | 3" Tape Spools 5p | 12 Volt Solenoid Box of 3 £1.20

ENM Ltd. cased 7-digit counter 21 x 11 x 1 1/2" approx. 12V d.c. (48 a.c.) or mains £1.10

Motorola ex-equipment (unused) 2N3055 28p

SAPPHIRE STYLII. 10 different; dual and single point, current and hard to get types. My mix £1

INDICATORS
Bulgin D676 red, takes M.E.S. bulb 38p
12 volt, or Mains neon, red pushfit 23p
R.S. Scale Print, pressure transfer sheet Pack 4 48p

HUGHES MICRO ELECTRONICS 400MW ZENER DIODES 200 IN CLEAR PLASTIC HINGED LID COMPONENT BOX £2.30
3V, 3.6V, 3.9V, 4.3V, 4.7V, 11V or 13V

RESISTOR PACKS

10 for 4p	100 for 40p	200 for 80p
5K6 1w	68 1w	1w 5% Carbon film
100K 1w	12K 1/2w 2%	100, 100K, 9K1
1K8 1w	560 1/2w 2%	1K2, 47K
1M7 1w	2K 1w	
2M7 1w	10K 1w	
10 for 9p	100K 1/2w	1/2w 5% Carbon Film 100 for 20p
3K3 1w	22M 2w	5.6, 180, 360, 560, 3K6, 1K2, 8.2.
22M 2w	1M8 1/2w	
3M3 2w	3M9 1/2w	
1M5 1w		

TRADE COMPONENTS
 ESTABLISHED 23 YEARS
 PAY A VISIT - THOUSANDS MORE ITEMS BELOW WHOLESALE PRICE. CALLERS PAY LESS ON MANY ITEMS AS PRICES INCLUDE POSTAGE. PRICES INCLUDE VAT AND ADDITIONAL DISCOUNT IN LIEU OF GUARANTEE. GOODS SENT AT CUSTOMERS' RISKS UNLESS SUFFICIENT ADDED FOR REGISTRATION OR COMPENSATION FEE POST.

TRADE COMPONENTS

BRIAN J. REED</

VAT & POST PAID

UK - Postal Orders for same day service. Cheques require 8 days from a Monday banking to ensure clearance. Export - bank's draft (sterling) same day service. Foreign currency money orders etc. can lose value and take 4-6 weeks to clear. VAT content becomes documentation charge.

Due to lack of space, items (i.e. pots, caps, etc) can only be collectively priced. Catalogue often shows much lower individual value price. ALL ENQUIRIES, ETC. MUST BE ACCOMPANIED BY A STAMPED ADDRESSED ENVELOPE

BOXES - Grey polystyrene 61 x 112 x 31mm, top secured by 4 self tapping screws 6p; Clear perspex with sliding lid, 46 x 39 x 24mm 11p. **ABS**, ribbed inside 5mm centres for P.C.B., brass corner inserts, screw down lid, 50 x 100 x 25mm orange 69p; 80 x 150 x 50mm black £1.09; 110 x 190 x 60mm black £1.62. **DIECAST ALU** superior heavy gauge with sealing gasket, approx. 6 1/2" x 2 3/8" x 1 3/8" £1.60; 3 3/4" x 2 3/8" x 1 3/8" £1.10. **VARIABLE CAMM PROGRAMMER** 10, 12 or 15 pole 2 way, 50VAC motor—series with 1mfd, or 3k 10W or 15W pygmy bulb for mains operation. Ex equipment £3.10

CATALOGUE

5300 ITEMS AT PRICES YOU WOULD NOT BELIEVE BEFORE INFLATION, YOUR MONEY MUST GO TWICE AS FAR 75p PLUS 30p POST.

OPTO ELECTRONICS

Photo Diodes: BPX40, BPX42, BPY10, CQY77, CQY17, BPY68, BPY69, BPY77 36p.

Wire end neons 4p. Photo transistors: BPX29, BPX43, BP103, 2N5777 Darlington, 36p. OCP71 40p. LED's (Mullard Seimens) Red .2" 8p. .125" 9p; Green .2" 11p; .125" 12p; Micro Yellow LD481 7p. **PHOTO SILICON CONTROLLED SWITCH** BPX66 PNP 10 amp 36p

7 SEGMENT L.E.D. DISPLAYS

.3" Red com. anode 81p
.5" Red FND 500 C.C. 72p
.5" Green R.S.C.A. £1.77
5082-7650 Red com. anode
5082-7653 Red com. cath
5082-7600 Yellow com. anode
H.P. Highbrilliance .43" 72p

HEWLETT PACKARD MULTIPLEXED .12" 7 SEGMENT LED DISPLAYS

3 Digit HP 5082 7413 45p
4 Digit HP 5082 7414 45p
5 Digit HP 5082 7415 45p
Minitron 0.3in 3015F filament £1.25
Infra red transmit diodes, CQY11B or LD27 High power 1.6-2v or 3-3.5v Pulse 53p
LD242 36p

H15B Photon coupled isolator I.R. diode and NPN Photo-Darlington amp 26p
Data Sheet 10p
CNY17/1 opto coupler 70p
Cold cathode tubes I.T.T. G517A or 5870L 60p

Wet Tantalum Capacitor. Plessey A Series 250 MFD 15 Volt Pack of 5 70p

Magnetic Cartridge Diamond Stylus Price per pack of 3 G800 £5.62 G800E £10.45 G850 £5.51 MC100 Cartridge £5.16 MC150 Cartridge £7

DIODES

AA113	9p	QA5	25p
AA119	7p	OA7	25p
AAZ15	15p	OA10	25p
B1	11p	OA47	7p
BA116	30p	OA70	10p
BA128	21p	OA75	11p
BA145	21p	OA79	11p
BA148	12p	OA81	3p
BA182 Varicap	6p	OA95	8p
BAX14	21p	OA200	21p
BAX54	8p	OA202	21p
BAY36P	21p	IGP7	11p
BB103 Varicap	6p	IGP10	11p
BB104 Varicap	16p	IN662	21p
BB109 Varicap	24p	IN914	11p
BB110B Varicap	24p	IN916	21p
BB113 Triple Varicap	43p	IN935B	71p
		IN936B	71p
BB139	£1	IN937B	71p
BY206	71p	IN941B	71p
BY207	23p	IN942B	71p
BY402	21p	IN943B	71p
BY403	21p	IN3064	21p
Centercell	3p	IN3716 Tunnel	
CG651	9p	Diode	30p
CR HG/3	10p	IN4009	21p
CSD117YLZ	40p	IN4148	1p
CV7095	21p	IN4150	21p
CV7098	21p	IN4151	21p
D3202Y Diac.	11p	IN4446	21p
DC2845 Microwave	20p	IN4449	21p
DOG53	11p	IN5456	15p
FSY28A	40p	5082 2900 RF Schotky Barrier	20p
HG1012	10p		
HS2091	11p		
MPN3401	30p		

RECTIFIERS

Type	Volt	Amp	Price
BY127	1250	1	4p
BY212	EHT	6p	6p
BY235	600	1 1/2	71p
BY236	900	1 1/2	71p
BY238	1200	1 1/2	9p
BY264	300	3	12p
BY265	600	3	11p
BY266	900	3	15p
BY274	300	5	14p
BY275	600	5	17p
BY277	1200	5	27p
BY299	800	2	4p
BY1202	2kV	10mA	6p
BYX20-200	200	25	72p
BYX22-200	300	1 1/2	25p
BYX38-300R	300	2 1/2	48p
BYX38-600	600	2 1/2	52p
BYX38-900	900	2 1/2	60p
BYX38-1200	1200	2 1/2	65p
BYX42-300	300	10	36p
BYX42-900	900	10	92p
BYX42-1200	1200	10	£1.07
BYX46-300R	300	15	£1.19
BYX46-400R	400	15	£1.75
BYX46-500R	500	15	£2.00
BYX46-600	600	15	£2.30
BYX48-300R	300	6	47p
BYX48-600	600	6	60p
BYX48-900	900	6	70p
BYX48-1200R	1200	6	92p
BYX49-300R	300	3	35p
BYX49-600	600	3	42p
BYX49-900R	900	3	47p
BYX49-1200	1200	3	60p
BYX52-300	300	40	£2.05
BYX52-1200	1200	40	£2.90
BYX72-150R	150	10	42p
BYX72-300R	300	10	52p
BYX72-500R	500	10	65p
BYX94	1250	1	5p
E250C50	250	1	14p
LT102	30	2	15p
M1	68	1	5p
MR56	600	3	24p
OA210	400	5	33p
RAS3 (OAF) Avalanche	1250	1 1/2	48p
REC53A	1250	1 1/2	16p
S10BR30	1000	3	£2.00
SKE4G	200	6	30p
SR100	100	1 1/2	9p
SR400	400	1 1/2	10p
IN3254	400	1	4p
IN4002	100	1	3p
IN4004	400	1	4p
IN4005	600	1	6p
IN4006	800	1	6p
IN4007	1250	1	6p
IN5059	200	1 1/2	10p
IN5402	200	3	11p
IS138	800	1	21p
IS921	100	1	8p
25G100	100	60	£4.35

TRIACS

Amp	Volt		Price
0.1	40	7W84	3p
25	100	BTX94-100	£2.25
25	1200	BTX94-1200	£5

Astec UM 1663E36 Pal Encoder and UHF Modulator Video £2.50

BRIDGE RECTIFIERS

Amp	Volt		Price
1	1,600	BYX10	34p
1	140	OSH01-200	25p
0.6	110	EC433	20p
5	400	Texas I.R.	85p
2 1/2	100	B40C 3200	40p
3 1/2	60V	BC30 C350	58p
2 1/2	350V	9F2	23p
2 1/2	500V	9E4	70p
			85p
Miniature	Meter	Type	Price
1	400V	WO4	28p
1	400V	MDA104	29p
1	200V	WO2 Ex Equip	15p
1	50V	WO5	19p
1	800V	WO8	27p
1 1/2	75V	IBIBY234	11p
1 1/2	150V	IBIBY235	15p

Thyristors

Amp	Volt		Price
1	240	BTX18-200	35p
1	240	BTX30-200	35p
1	400	BTX18-300	41p
4	500	40506	58p
4	600	2N3228	36p
6.5	500	BT109/SCR957	71p
20	600	BTW92-600RM	£3.40
15	800	BTX95-800 Pulse Modulated	£1
0.8	50	2N5061	3p
0.8	200	2N5064	18p
3	600	T3N06C00	53p
3	100	T3N1C00	36p
110	20	72RC2A	£3
75	800	71CG80	£6
150	1000	151RA100	£10
150	1200	151RA120	£11
12	1000	CR121103-RB	£8
2.5	600	2N5757	36p
10	200	S2800B	54p
5	600	S5800M	44p
8	600	S112M	54p
5	400	S3700D	44p
BT 106		70p BT 107	£1
BT 121		70p	

ZENER DIODES

4/500MW. BZY88, BZX97, etc.	5p
2v. 2v7. 3v. 3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 9v1. 10v. 11v. 12v. 13v. 13v5. 15v. 18v. 20v. 22v. 24v. 27v. 30v. 33v. 43v.	
1.3/1.5WT BZX61, BZY97, etc.	11p
2v4. 2v7. 3v6. 3v9. 4v3. 4v7. 5v6. 6v2. 6v8. 8v2. 9v. 10v. 11v. 15v. 18v. 27v. 33v.	
2.5WT BZX70, etc.	13p
v75. 1v. 2v4. 3v6. 3v9. 5v6. 6v2. 7v. 7v5. 8v. 9v. 10v. 11v. 14v. 15v. (8p). 20v. 22v. 24v. 26v.	
5WT BZV40, etc.	15p
3v3. 3v6. 3v9. 4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 8v7. 9v1. 10v. 11v. 12v. 15v. 33v. 68v. 120v.	
10WT Z5D, ZX, etc.	20p
4v3. 4v7. 5v1. 5v6. 6v2. 6v8. 7v5. 8v2. 11v. 12v. 13v. 16v. 18v. 21v. 22v. 33v. 36v. 39v. 68v. 150v.	
BZY61 Laboratory Standard 400MW 7v5. Voltage Regulator Diode	12p
20WT BZY93, etc.	44p
8v2. 12v. 39v.	

METAL-CASED SOLID TANTALUM CAPACITORS ONLY 12p ANY VALUE. (A few values are ample lead ex unused equipment) Despite World Tantalum Shortage.

PROFESSIONAL ELECTROLYTIC

MFD/VOLT	Price	
.0068/35	4.7/35	33/10
.01/35	4.7/50	33/20
.022/35	4.7/75	33/35
.022/50	5.6/35	39/30
.056/50	6.8/6	40/10
.1/35	6.8/35	40/50
.1/63	6.8/50	45/30
.22/35	8.2/20	47/10
.22/75	10/20	47/20
.33/200	10/25	47/25
.68/35	10/35	47/35
.82/20	12/20	56/6
1/35	15/12	56/20
1.2/20	15/20	56/35
1.5/20	18/15	68/15
1.5/35	18/50	82/10
2.2/15	22/15	100/10
2.2/20	22/25	100/20
2.2/35	22/35	120/15
2.3/10	22/50	150/6
2.5/25	25/35	150/25
3.3/15	25/50	220/10
3.3/35	27/20	560/6
4.7/10		

BRIAN J. REED

SEE PRECEDING PAGES FOR ORDERING INSTRUCTIONS
Cut out and keep these 3 pages. Over the months they will bring to you some of the 6,000 items stocked.

INTEGRATED CIRCUITS

542 Servo Amp	18p	74180	12p	MC862P	4p	ZN414 AM Radio	79p
555 Timer	20p	74192	33p	MC863P	4p	ZST131A	8p
702 CL	25p	74LS192	60p	MC1306P	40p		
709/72709	18p (14 pin 10p)	74193	38p	MC1307P	35p		
710	28p	74196	36p	MC/CA/BRC 1310P St. Dec.	35p		
724	20p	74S196/82590	65p	MC1312P Stereo Decoder	40p		
741 OP Amp	16p	74197	50p	MC1314P	35p		
747	44p	74LS221	52p	MC1315P	35p		
748	30p	74LS290	47p	MC/BRC1330	85p		
9300DC	4p	74293	80p	MC1350P	35p		
933DC	4p	74298	£1	MC1351P	35p		
936DC	4p	74490	£1.30	MC1357P	35p		
937DC	4p	7805 (TO3) plus 5v Reg.	64p	MC1358PQ	35p		
946DC	4p	7905 - 5v Reg.	54p	MC1596L	35p		
949DC	4p	8080A C.P.U.	£3.60	MC3302L	75p		
953 - 42300 Triple 2 Input NAND	4p	82S129	£5	MC4044P	£1		
961DC	4p	9093DC	4p	MC4344P	£3.50		
962DC	4p	9112DC	4p	MIC7C	25p		
963DC	4p	93S10	£1	MK2686	36p		
1315P2	36p	9311	£1.20	MK4012 Memory	38p		
2102 Memory	73p	93L16	35p	ML237B	£1		
2716 Eprom	£14	9370	25p	MM5233 C.P.U.	36p		
3351-2DC 40 x 9 Bit FIFO 2MHZ	£1.07	930399-256 Bit Shift Register	4p	MM5235D C.P.U.	36p		
7400	10p	930399-480 Bit Shift Register	4p	MM5387N	£3		
74H00	26p	930399-500 Bit Shift Register	4p	MM6008 C.P.U.	36p		
74LS00	13p	930399-512 Bit Shift Register	4p	MPG900 10A - 4 to 30v Reg.	75p		
74S00	18p	AJ371-002	4p	MT300 Volt Reg.	8p		
7401	7p	AY38500 TV Game	£2	MT305 Volt Reg.	8p		
74H01	26p	AY58300 Ch/Time Display	36p	SAA661	36p		
7402	11p	BRCM300 Volt Reg.	£1.40	SAA1010	34p		
7404	11p	BTT822	£1.73	SAA1025	£4		
54/7406	15p	C500 Calculator	37p	SAS580	18p		
7408	13p	CA139AG Quad Volt Comp.	54p	SAS590	18p		
74LS08	15p	(T)CA270AE	£1	SGS308 Op. Amp	4p		
7410	10p	(T)CA270CW/AW	35p	SL403A 3Wt. Amp	38p		
74L10	25p	CA3001 RF Amp	86p	SL442	36p		
74H10	26p	CA3028A	75p	SN7528	11p		
7411	8p	CA3044	£1.20	SN15836	25p		
5413	16p	CA3046	40p	SN15844P	4p		
7414	39p	CA3054	69p	SN15845	50p		
7417	18p	CA3060	72p	SN15846	37p		
7420	11p	CA3065	36p	SN15851	50p		
74S20	50p	CA3083	65p	SN15858N	55p		
74S22	18p	CA3086	29p	SN15862	6p		
7425	18p	CA3089	54p	SN75107	£1.15		
7426	16p	CA3093	36p	SN75108	46p		
5430	12p	CA3123	73p	SN75110	18p		
7430	11p	CA3132EM	£2.22	SN75150	11p		
74L30	11p	CA3146E	90p	SN75235N	36p		
7432	13p	CA3183	80p	SN75451	36p		
54/7437	13p	CA3189	73p	SN76001	36p		
7438	14p	CA3401 (LM3900)	36p	SN76003 5Wt. Amp	36p		
74H40	26p	CD4001	14p	SN76003N 5Wt. Amp	£1.10		
7442	26p	CD4002	12p	SN76013 5Wt. Amp	36p		
74LS42	40p	CD4009	19p	SN76013ND 5Wt. Amp	£1.18		
7445	42p	CD4011	14p	SN76023 5Wt. Amp	36p		
7450	11p	CD4012	13p	SN76110P	35p		
74H50	26p	CD4013	23p	SN76115N	35p		
7451	7p	CD4014	36p	SN76131	35p		
7454	11p	CD4018	43p	SN76226	58p		
74L54	11p	CD4019	25p	SN76227	58p		
54/7472	20p	CD4022	36p	SN76228N	59p		
74L72	25p	CD4023	36p	SN76228N	£1.60		
5473	12p	CD4028/MC14028	19p	SN76396 (TBA396)	35p		
7473	17p	CD4029	42p	SN76630	18p		
74H73	26p	CD4033	72p	SN76650N	50p		
7474	13p	CD4035	54p	SN76660N	35p		
74L74	25p	CD4040	54p	SN76666N	35p		
7475	24p	CD4046	54p	SN158093	35p		
54/7476	19p	CD4050	36p	SN158097	50p		
7480	22p	CD4066	25p	SN158099	4p		
7482	35p	CD4069	27p	TAA263 Amp	50p		
7483	45p	CD4078	13p	TAA300 1Wt. Amp	75p		
74LS83	47p	CD4094	19p	TAA320	£1		
54/7486	18p	CD40194	72p	TAA550 Volt Reg.	35p		
7489	40p	CD4502	72p	TAA700	23p		
54/7490	25p	CDP1802 Cosmac	44p	TAD100 AM Radio	£2.30		
7493 Binary Counter	25p	CDP1833 Cosmac	£3.60	TBA120S/CQ/SB/B TV Amp	£1.22		
54/74L95	25p	D3624	£3.60	TBA240	25p		
74LS98	£1.25	DM8214 C.P.U.	36p	TBA395Q	£3.90		
74107	20p	FCH111	8p	TBA396	£1.50		
74LS107	26p	FCH201	18p	TBA550	36p		
74S112	38p	FCJ101	50p	TBA560C	£1.61		
74118	75p	FPQ/MPQ3725 4 Tr. Array	45p	TBA800 Amp	52p		
74121	12p	FZH151	18p	TBA810 Amp	70p		
74122	18p	FZH191	18p	TBA920	70p		
54/74123	35p	FZH201	18p	TCA270Q/SA/AE/OS	£1		
74132	44p	JM5623 C.P.U.	36p	TCA270SQ	55p		
74141	42p	LM300 Volt Reg.	86p	TCA440	£1.25		
74LS145	93p	LM309 (Ex Equip.) 5v Reg.	60p	TCA830S Ex. Equip.	18p		
74150	12p	LM326 Volt Reg.	20p	TCA830S	37p		
74151	32p	LM340T6 6v Reg.	36p	TCA4401	£1.25		
74154 16 Way Dist.	35p	LM343 Amp	4p	TCEP100	£1		
74155	12p	LM1303N	65p	TDA/MC1327	18p		
74157	12p	LM/MC1458N	19p	TDA2610	71p		
74165	58p	LM3900 Quad Op. Amp	36p	TDA2680	71p		
74167	23p	MC830P	4p	TDA2690	71p		
74173	44p	MC833P	4p	TL720	28p		
74176/8280	30p	MC837P	4p	TMS4034 Memory	£1.08		
		MC846P	4p	TYA0171	4p		
				XR215	£2		

ROTARY WAFER SWITCHES

Pole	Way	
1	3	23p
1	4	40p
1	8	40p
1	11	23p
1	12	23p
1	20	23p
2	2	40p
2	3 plus Mains D.P.	25p
2	4	23p
2	5	48p
2	6	40p
3	7	23p
3	11	23p
4	2	23p
4	3	45p
4	5	47p
6	3	23p
7	4 plus Mains D.P.	23p
12	3 plus Off	23p
24	2	60p
Makaswitch 1" diam. small centre, 1 pole, 10 way wafer		5p

7 MILLION CARBON FILM RESISTORS PURCHASED

1/4 - 1/2 - 1/2 - 3/4 - 1 - 1 1/2 Wt.
Iskra and Piher, mainly 5%, few 2%. Lucky Dip as the packs come (will not duplicate under 20 packs) due to cartons packed tight and on top of each other to ceiling of warehouse.

PACK OF 100 FOR 20p

Gents 3" 4-6 Vac Dome Bell
£1.50

I.C. SOCKETS

Low Profile
8 Dil 9p. 14 Dil 11p. 16 Dil 11p.
28 Dil 22p. 14 Dil to Q 8p
Standard
14 Dil to Q 8p. 16 Dil to Q 11p

SLIDE POTENTIOMETERS

60mm Track		
LOG	LIN	
250 Ω	30p	500 Ω 30p
1K	30p	1K 30p
5K	29p	2K2 27p
47K	23p	5K 30p
50K Neg.	30p	10K 30p
100K	23p	22K 25p
250K	36p	47K 24p
470K	24p	50K 17p
1M	25p	100K 30p
2M	30p	250K 18p
		500K 19p
40mm TRACK		
LOG	LIN	
10K	30p	
22K	30p	470K 30p
50K	7p	
100	30p	
30mm TRACK		
LOG	LIN	
5K	30p	1K 30p
22K	30p	5K 30p
50K	20p	
100K	30p	

ELECTROVALUE

SUPPLIERS OF COMPONENTS THAT COUNT



SIEMENS SEMI-CONDUCTOR CAPACITORS FERRITES	NASCOM MICRO COMPUTERS AND ANCILLARIES	VERO BOARDS CASES & KITS
ISKRA RESISTORS	RADIOHM POTENTIOMETERS	BREADBOARDS SOLDER TOOLS
	OPTO-ELECTRONICS	SWITCHES CATALOGUE 10

OUR MINI-SELECTION POINTS THE WAY!

EXAMPLE ONE - SOLDERING IRONS

Aryx 50	£12.08 net	Antex x 25	£4.83 net
Isotip	£25.90 net	Desolder tool SR3A	£7.48 net
Antex C	£4.83 net	500 gm reel solder	£6.61 net

EXAMPLE TWO - PRINTED CIRCUIT MATERIALS

PCB's 300 x 150 mm	Ech Resist Pen	£1.14
SRBP S/S £1.38	Breadboards	
D/S £2.13	Bimboard	£9.23
F/Glass S/S £1.96	Eurobreadboard	£6.56 net
Positive resist 75cc	T-DeC	£5.18
Ferric Chloride 500 g		

EXAMPLE THREE - SWITCHES

Chrome toggle	13A time switch adaptors	
Std. SPDT 65p	Smiths TS100	£14.43 net
Min. SPDT 66p	Wavechange, Lorlin, 1P12W, 2P6W, 3P4W, 4P3W	46p each
DPDT 89p		
DPDT 92p		

EXAMPLE FOUR - CAPACITORS BY SIEMENS

Polyester 7.5mm PCM
1, 1.5, 2.2, 3.3, 4.7µF, 10, 15, 22, 33, 42µF 8p each, .1µ 12p, .15µ 15p, .22µ 18p, .33µ 21p, .47µ 27p, .68µ 34p, 10mm PCM 1µ 37p.
Electrolytic, axial, (µF/V)
1/40 24p, 1/100 15p, 2.2/25 24p, 2.2/63 15p, 4.7/16 24p, 4.7/40 15p, 10/25 15p, 10/40 18p, 22/25 18p, 22/40 18p, 22/63 19p, 47/10 18p, 47/25 18p, 47/40 16p, 47/63 20p, up to 1000/16V 36p, then 1000/25V 49p to 47/16 65p.
Also full supporting ranges of other ceramic, plastic and electrolytic caps.

EXAMPLE FIVE - POTENTIOMETERS BY RADIOHM

Single gang lin or log	34p	(Twin types stereo matched)
Twin gang lin or log	93p	Slider knobs 10p each.
Mono slider lin or log	83p	Presets lin, horiz, or vert at 10p
Twin slider lin or log	136p	

EXAMPLE SIX - RESISTORS

1/4, 1/2, 1/2W 2.3p 1W 6p
Wirewound from 21p

AND AS FOR SEMI CONDUCTORS . . .

1N914	6p	40673	99p	MU481	£1.70	T1P41A	69p
1N4007	9p	AC128	36p	MJ491	£1.88	T1P41C	74p
1N4148	5p	AC176	67p	MJ2955	97p	T1P42A	69p
1N5402	19p	AD136	£4.25	MJE2955	£1.13	T1P42C	74p
2N1599	£1.01	AD149	£1.01	MJE3055	£1.00	T1P2955	69p
2N2369A	24p	AD161	40p	MPSA12	42p	T1P3055	69p
2N3055	81p	AD162	52p	MPSA63	44p	T1S43	40p
2N3702-11	11p	AF127	43p	OA47	14p	W02	35p
2N4443	£1.78	AL102	£1.84	OA90	8p	2T x 107, 9	14p
2N4444	£2.28	BA379	29p	OA91	8p	2T x 300	14p
2N4991	98p	BB103	43p	OA202	16p	62T x 500	16p
2N5457-9	45p	BB104	70p	OC29	£1.23		
40HF40	£2.25	BB105	37p	OC36	£1.18	This list is	
40361	49p	C106D1	52p	T2800D	£1.20	but a fraction	
40362	49p	E1110	92p	T1P31A	52p	of what we	
40636	£1.69	E1210	97p	T1P32A	52p	carry.	


INFORMATION - To show everything we supply would take about seven pages of closely packed type in this journal - the range is enormous including not only opto devices and very advanced sophisticated items, but all the everyday things you need as well down to nuts and washers! IT'S ALL IN CATALOGUE 10 - OUR 120 PAGE CATALOGUE FREE FOR THE ASKING. **PRICES AND V.A.T.** - All prices quoted here include V.A.T. for U.K. orders. Overseas buyers deduct 13% when ordering.

POSTAGE - For orders up to £5.75 value (U.K.) please add 40p for p/p. If over, orders sent post free in U.K. Overseas orders sent at cost (Min. 40p). **DISCOUNTS** - 5% allowed on non-net items if order value exceeds £11.50, 10% if order value exceeds £29. Quantity discount prices on most components.

ELECTROVALUE LTD. Dept. 28(A), St. Judes Road, Englefield Green, Egham, Surrey TW20 0HB. Phone Egham 33603 Telex 264475. Northern Branch (Personal Shoppers only) 680 Burnage Lane, Burnage, Manchester M19 1NA. Phone (061) 432 4945.

TUNE IN!

Build the World Famous
CHROMA-CHIME

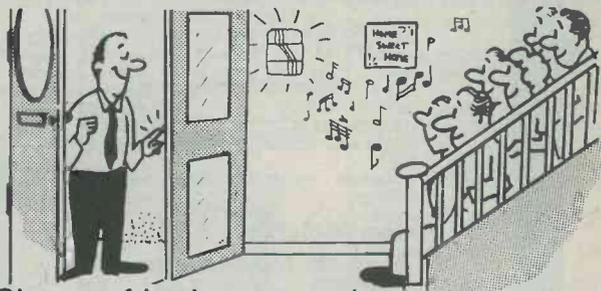

Give your friends a warm welcome


This kit has been carefully prepared so that practically anyone capable of neat soldering will have complete success in building it. The kit manual contains step by step constructional details together with a fault finding guide, circuit description, installation details and operational instructions all well illustrated with numerous figures and diagrams.

- Handsome purpose built cabinet
- Easy to build and install
- Uses Texas Instruments TMS1000 microcomputer
- Absolutely all parts supplied including I.C. socket
- Ready drilled and legended PCB included
- Comprehensive kit manual with full circuit details
- No previous microcomputer experience necessary
- All programming permanently retained is on chip ROM
- Can be built in about 3 hours!
- Runs off 2 PP3 type batteries.
- Fully Guaranteed

ONLY £11.95
+ 75p p&p
UK ONLY

* Save pounds on normal retail price by building yourself.

TMS 1000N

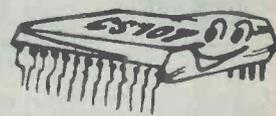

-MP0027A Micro-computer chip available separately if required. Full 24 tune spec device fully guaranteed.

This unique chip can be used not only for electronic door chimes but for other projects requiring musical output: New low price only

£4.95 inc. p & p.
Free applications manual and data supplied with device! (Or 30p separately.)

ALL CHROMATRONICS PRODUCTS SUPPLIED WITH MONEY BACK GUARANTEE PLEASE ALLOW 7-21 DAYS FOR DELIVERY

Please send me:
TO: CHROMATRONICS, RIVER WAY, HARLOW, ESSEX.

NAME _____
ADDRESS _____

I enclose cheque/PO value £ _____
or debit my ACCESS/BARCLAYCARD account no. _____

Signature _____ R.E.C. 780

CHROMATRONICS

ALL PRICES INCLUDE V.A.T. AND P. & P.

L.E.D.s

Red .2	12p
Green .2	21p
Yellow .2	21p
Red .125	12p
Green .125	21p
Yellow .125	21p

uA 741 8 pin	26p
NE555	32p

Sub-min Transformers

6-0-6v 100mA	£1.05
9-0-9v 75mA	£1.05
12-0-12v 100mA	£1.15

Chassis mounting fuse holders. 20mm	8p
--	----

5 pin 180 Din Plugs	13p
---------------------	-----

5 pin 180 Din Sockets. Standard metal type	15p
---	-----

Printed.Circuit Board bonded paper,
copper cald single sided.

Approx. 2 x 8½	15p
----------------	-----

Approx. 4½ x 9	31p
----------------	-----

Etch Resist Pen	£1.07
-----------------	-------

PP3 Battery Clips	7p
PP9 Battery Clips	16p

Crocodile clips with vinyl insulation sleeves, Red or Black	6p
--	----

4mm Banana Plugs Red or Black	12p
-------------------------------	-----

4mm Banana Sockets Red or Black	14p
---------------------------------	-----

4mm Terminal Posts Red or Black	30p
---------------------------------	-----

13 amp Plugs

White plastic plug fitted with 13 amp
fuse and cable grip.

Price:	48p
--------	-----

White unbreakable plug with a
rubber outer cover and hard plastic
insert. Fitted with 13 amp fuse and
cable grip.

Price:	52p
--------	-----

High Quality Desolder tools £4.75

Mains tester screwdriver with neon
indicator in handle. Tests 100 to 500
volts.

Price:	52p
--------	-----

Seven section Telescopic Aerials,
Chrome finish, with swivel. Collar
fixing.

82p

2 pole 2 way Latchswitches 10p

40mm dia. 8 ohms .2 watts

Speakers.

Price:	£1.00
--------	-------

Extra Flex. Flexible wire ideal for test
leads. Max. current 6A. Black or Red.

Price:	13p per metre.
--------	----------------

Magnetic earpiece, 8 ohm im-
pedance, with 1m lead and 3.5mm

jack plug	15p
-----------	-----

Push to make Switches	16p
Push to break Switches	22p
DPDT Slide Switches, Fixing centres 29mm	15p
Sub min DPDT Slide Switches	15p
Standard DPDT Toggle Switch with chrome dolly	49p
Sub min toggle switches, Fixing hole dia: 5mm	
SPST Toggle	68p
SPDT Toggle	72p
DPDT Toggle	80p
Rotary Switches	
1p 12w, 2p 6w, 3p 4w, 4p 3w	All 53p each

2.5 Jack Plugs Plastic body	11p
3.5 Jack Plugs Plastic body	11p
2.5 Open framed Jack Sockets	10p
3.5 Open framed Jack Sockets	10p

Sub-min Presets

Horiz: 100 ohms, 220 ohms, 470 ohms, 1k, 1k5, 2k2,
4k7, 10k, 22k, 47k, 100k
Vert: 470 ohms, 2k2, 4k7.

All price 7p each

Heatsinks

4 inch long, for use on printed circuit boards and
suitable for external mounting on equipment. Un-
drilled. Black anodised finish.

Price:	85p
--------	-----

Cast aluminium, approx: 4½ x 2 x 2, drilled to take one
TO3 transistor in the centre. Sprayed Black.

Price:	80p
--------	-----

Cast aluminium, approx: 3½ x 5½ x 1½, takes two flat
plastic type transistors on rear side of fins. Ideal for
mounting at the edge of P.C. boards and on the rear of
chassis. Sprayed Black.

Price:	85p
--------	-----

Black plastic self adhesive insulation tape. ¾" wide 18m
long.

Price:	42p
--------	-----

14mm square self adhesive feet, brown only. Set of
four

	16p
--	-----

Low profile d.i.l. I.C. Sockets

8 pin	10p	20 pin	16p
14 pin	12p	22 pin	18p
16 pin	13p	24 pin	19p
18 pin	15p	28 pin	24p
		40 pin	34p

Mixed pack ¼ watt Resistors, E12 series 10 off each
value.

Price:	£7.75
--------	-------

Mixed Pack ¼ and ½ watt Resistors approx. 500
items.

Price:	£3.50
--------	-------

Mixed pack ceramic tube, ceramic disc, polystyrene,
silver mica, ceramic plate, mixed dielectric, etc. ½ kg.

Price:	£1.50
--------	-------

Pack of 50 mixed rubber grommets

42p

6mm dia. Wire Neons 90 volts

6p

Two pin Loud speaker plugs

12p

Two pin Loud speaker sockets, plastic

10p

57mm dia. 8 ohms .1 watts Speakers.

Price:	75p
--------	-----

Three core, blue, brown, green/yellow P.V.C. insulated
13/0.2mm copper conductors sheathed overall in
White P.V.C. Nominal O.D. .9mm. Nominal current
rating: 2.5 amps.

Price:	20p per metre
--------	---------------

Crystal earpiece, with 1m lead and 3.5mm jack plug

40p

Please add £1.00 handling charge to all orders
OUR NEW CATALOGUE IS NOW AVAILABLE.
SEND 22p FOR YOUR COPY

HARRISON BROS. P.O. Box 55, Westcliff-on-Sea
Essex SS07LQ

Telephone: Southend-on-Sea (0702) 32338

TRADE ENQUIRIES WELCOME

SAME DAY SERVICE

QUALITY COMPONENTS

MOTORS

1.5-6VDC Model Motors 22p. Sub. Min. 'Big Inch' 115VAC 3rpm Motors 32p. 6 volt standard cassette motors new £1.20. 8 track 12V Replacement Motors 55p. Cassette Motors 5-8VDC ex. equip. 70p. Geared Mains Motors (240V) 2.5 rpm 75p. 115VAC 4rpm Geared Motors 95p.

SEMICONDUCTORS

LM340 80p. BY103 10p. 2N5062 100V 800mA SCR 18p. BX504 Opto Isolator 25p. CA3130 95p. TBA800 50p. 741 22p. 741S 35p. 723 35p. NE555 24p. 2N3773 £1.70. AD161/2 70p. ZN414 75p. BD238 28p. BD438 28p. IN4005 10 for 35p. TIL305 alpha numeric displays £2.50. TIL209 Red Leds 10 for 75p. Man3A 3mm Led Displays 40p.


PROJECT BOXES

Sturdy ABS black plastic boxes with brass inserts and lid. 75 x 56 x 35mm 65p. 95 x 71 x 35mm 75p. 115 x 95 x 37mm 85p.

MOTOROLA PIEZO CERAMIC TWEETERS
No crossover required



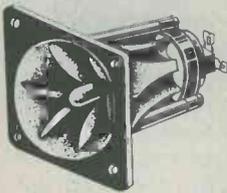2.5" Direct Radiating Tweeter, maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8kHz-28kHz, £3.65



3.5" Super Horn (flush mounting), maximum rating 25 volts R.M.S. 100 watts across 8 ohms. Freq. range 3.8-2.8kHz, £4.50

MORSE KEYS

Beginners practice key £1.05. All metal full adjustable type. £2.60

MINIATURE LEVEL METERS

1 Centre Zero 17 x 17mm 75p. 2 (scaled 0-10) 28 x 25mm 75p. 3 Grundig 40 x 27mm £1.25.

JVC NIVICO STEREO CASSETTE MECHANISM. Music centre type. Rev. counter, remote operation £13.50 and £1.00 p&p.

JUMPER TEST LEAD SETS

10 pairs of leads with various coloured croc clips each end (20 clips) 90p per set.

TRANSFORMERS

All 240VAC Primary (post-age per transformer is shown after price). MINIATURE RANGE: 6-0-6V 100mA, 9-0-9V 75mA and 12-0-12V 50mA all 79p each (15p). 0-6, 0-6V, 280mA £1.20 (20p). 6V 500mA £1.20 (15p). 12V 2 amp £2.75 (45p). 15-0-15V 3 amp Transformer at £2.85 (54p). 30-0-30V 1 amp £2.85 (54p). 20-0-20V 2 amp £3.65 (54p). 0-12-15-20-24-30V 2 amp £4.75 (54p). 20V 2.5 amp £2.45 (54p).

TRIAC/XENON PULSE TRANSFORMERS

1:1 (ppo style) 30p. 1:1 plus 1 sub. min. pcb mounting type 60p each.

MICROPHONES

Min. tie pin. Omni, uses deaf aid battery (supplied), £4.95. ECM105 low cost condenser, Omni, 600 ohms, on/off switch, standard jack plug, £2.95. EM507 Condenser, uni, 600 ohms, 30-18kHz., highly polished metal body £7.92. DYNAMIC stick microphone dual imp., 600 ohms or 20K, 70-kHz., attractive black metal body £7.75. EM506 dual impedance condenser microphone 600 ohms or 50K, heavy chromed copper body, £12.95 CASSETTE replacement microphone with 2.5/3.5 plugs £1.35. INSERT Crystal replacement 35 x 10mm 40p. GRUNDIG electric inserts with FET pre-amp, 3-6VDC operation £1.00.

LIGHT DIMMER

240VAC 800 watts max. wall mounting, has built in photo cell for automatic switch on when dark £4.50

RIBBON CABLE

8 way single strand miniature 22p per metre.

SPECIAL OFFER TAPE HEAD DEMAGNETIZER



240VAC with curved probe suitable for reel to reel or cassette machines. £1.95.

STEREO FM/GRAM TUNER AMPLIFIER CHASSIS, VHF and AM. Bass, treble and volume controls, Gram. 8-track inputs, headphone output jack, 3 watts per channel with power supply. £14.95 and £1.20 p&p (CCT supplied).

MULTIMETER BARGAINS



Pocket Multimeter, 1,000 opv sensitivity. Ranges 1KV AC/DC Volts, 150ma DC current, resistance 0-2.5K, 0-100K, £4.50



20,000 opv., 1,000 volts AC/DC, DC current to 500ma, 5 ranges, resistance 4 ranges to 6 meg. Mirror scale, carrying handle, £975.

MURATA MA401

40kHz Transducers. Rec/Sender £3.50 pair.

TELEPHONE PICK UP COIL

Sucker type with lead and 3.5mm plug 62p.

RELAYS

Plastic Encap. Reed Relay, 0.1 matrix. 1k Ω coil., 9-12VDC normally open, 35p. Miniature encapsulated reed relay 0.1 matrix mounting, single pole make, operates on 12VDC 50p each. Continental series, sealed plastic case relays, 24VDC 3pole change over 5 amp contacts, new 65p. Min. sealed relay, P.C. mounting, 6-9vdc operation changeover 3 amp contacts, new 85p. Metal Cased Reed Relay, 50 x 45 x 17mm, has 4 heavy duty make reed inserts, operates on 12VDC 35p each. Magnets 1/2" long 1/4" thick with fixing hole, 10 for 40p.

Dalo 33PC Etch Resist printed circuit maker pen, with spare tip, 79p.

TERMS:

Cash with order (Official Orders welcomed from colleges etc). 30p postage please unless otherwise shown. VAT inclusive. S.A.E. for illustrated lists

TMK500 MULTIMETER



TMK500 30,000 ohms per volt. 1KV AC/DC., D.C. Current to 12 amps. Resistance to 60 meg in 4 ranges, mirror scale, with built in buzzer for continuity testing £20.95

YN360TR MULTIMETER



YN360 M/Meter. 20,000 ohms per volt. 1KV AC/DC volts, 250ma dc current, 4 resistance ranges to 20meg, also has built in transistor tester with leakage and gain ranges. £12.50

CRIMPING TOOL

Combination type for crimping red blue and yellow terminations also incorporates a wire stripper (6 gauges) and wire cutter, with insulated handles only £2.30.

POWER SUPPLIES

SWITCHED TYPE, plugs into 13 amp socket, has 3-4.5-6-7.5 and 9 volt DC out at either 100 or 40 0mA, switchable £3.45. HC244R STABILISED SUPPLY, 3-6-7.5-9 volts DC out at 400mA max., with on/off switch, polarity reversing switch and voltage selector switch, fully regulated to supply exact voltage from no load to max. current £4.95.

AMPHENOL CONNECTORS

(PL259) PLUGS 47p. Chassis sockets 42p. Elbows PL259/SO239 90p. Double in line male connector (2XPL259) 65p. Plug reducers 13p. PL259 Dummy load, 52 ohms 1 watt with indicator bulb 95p.

BUZZERS

MINIATURE SOLID STATE BUZZERS, 33 x 17 x 15mm white plastic case, output at three feet 70db (approx), low consumption only 15mA, voltage operating 4-15VDC, 75p each. LOUD 12VDC BUZZER, Cream plastic case, 50mm diam. x 30mm high 63p. Carters 12 volt Minimize Alarm sirens £7.65p. 12VDC siren, all metal rotary type, high pitched wail, £6.25.

TOOLS

SOLDER SUCKER, plunger type, high suction, teflon nozzle, £4.99 (spare nozzles 69p each).

All Antex irons still at pre increase prices, order now as new stock will be going up next month.

Antex Model C 15 watt soldering irons, 240VAC £3.95

Antex Model CX 17 watt soldering irons, 240VAC £3.95

Antex Model X25 25 watt soldering irons, 240VAC £3.95

ANTEX ST3 iron stands, suits all above models £1.65

Antex heat shunts 12p each.

Servisol Solder Mop 50p each.

Neon Tester Screwdrivers 8" long 59p each.

Miyarna IC test clips 16 pin £1.95

SWITCHES

Sub. miniature toggles: SPST (8 x 5 x 7mm) 42p. DPDT (8 x 7 x 7mm) 55p. DPDT centre off 12 x 11 x 9mm 77p. PUSH SWITCHES, 16mm x 6mm, red top, push to make 14p each, push to break version (black top) 16p each.

G.P.O. Telephone handsets £1.95. Electrolytic Caps, can type, 2,200mfd and 2,200mfd 50VDC 35p each.

RES. SUB BOX



Resistance Substitution Box. Swivelling disc provides close tolerance resistors of 36 values from 5 ohms to 1 meg. £3.95.




Signal Generator. Ranges 250Hz-100MHz in 6 Bands, 100MHz-300MHz (harmonics) internal modulator at 100Hz. R.F., output Max. 0.1vRMS. All transistorised unit with calibrating device. 220-240VAC operation, £48.95.

TAPE HEADS

Mono cassette £1.75. Stereo cassette £3.90. Standard 8 track stereo £1.95 BSR MN1330 1/2 track 50p. BSR SRP90 1/2 track £1.95. TD10. tape head assembly - 2 heads both 1/2 track R/P with built in erase, mounted on bracket £1.20

PROGRESSIVE RADIO

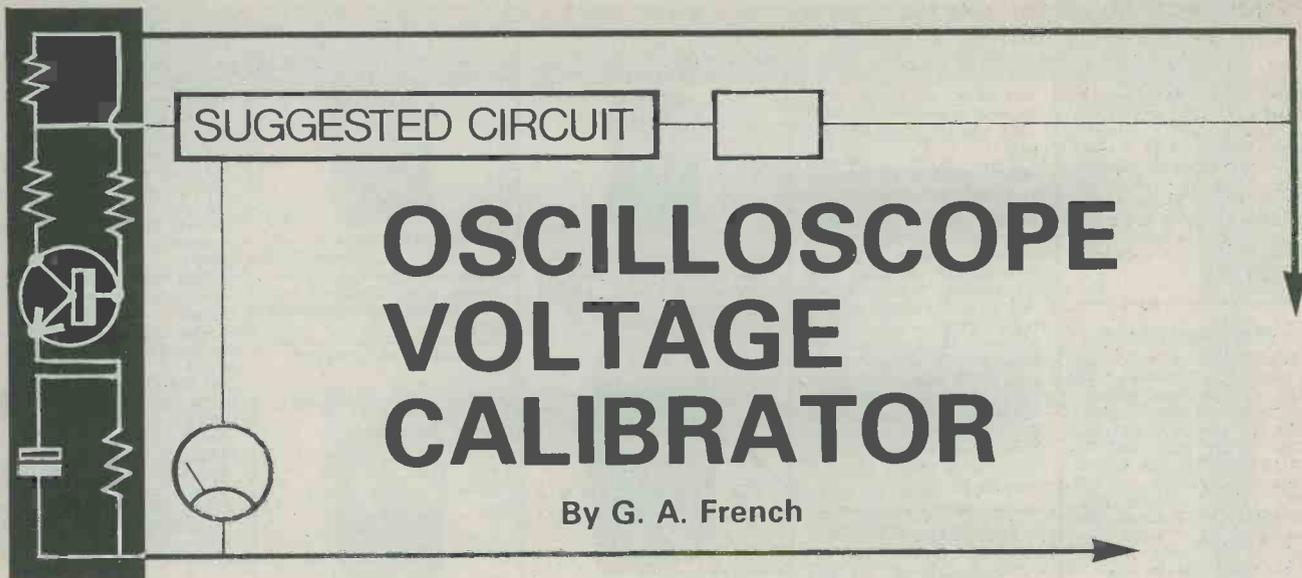31 CHEAPSIDE, LIVERPOOL 2.
ALL ORDERS DESPATCHED BY RETURN POST



SUGGESTED CIRCUIT

OSCILLOSCOPE VOLTAGE CALIBRATOR

By G. A. French

A number of requests from readers have been received recently asking for the publication of a voltage calibrator design for oscilloscopes. In consequence, this article in the "Suggested Circuits" series will be devoted to a practical calibrator circuit which employs basic principles and should offer few difficulties in assembly and setting up. The process of setting up, it may be added, requires no test equipment other than a multimeter having a low d.c. volts range capable of giving a clear indication of 1 volt.

Normally, oscilloscope voltage calibrators are not used frequently by amateurs and should not, in consequence, incorporate expensive components. However, high accuracy is needed, and this requirement can be satisfied by the use of a few readily available close tolerance resistors. The calibrator to be described produces square waves of known voltage amplitude and at very low impedance, and it meets the convention that the pulses be positive-going with reference to a common earthy output terminal.

SQUARE WAVE GENERATOR

A suitable square wave generator for use in the calibrator is the CMOS timer type ICM7555. However, this i.c. has

rather a poor output source current performance (i.e. the current it can pass to the negative voltage rail with a high output is limited) and the possibility of using this output to produce square waves directly is not attractive. It is, nevertheless, a simple matter to use the ICM7555 low output to drive a constant current transistor, with the transistor producing positive-going pulses. When this combination

is fed from a regulated voltage supply, output pulse amplitude becomes virtually constant over a wide range of unregulated supply voltages.

The circuit of the oscilloscope voltage calibrator is given in Fig.1. Here, the ICM7555 functions as an astable multivibrator running at around 450Hz with timing components R1, R2, R3 and C1.

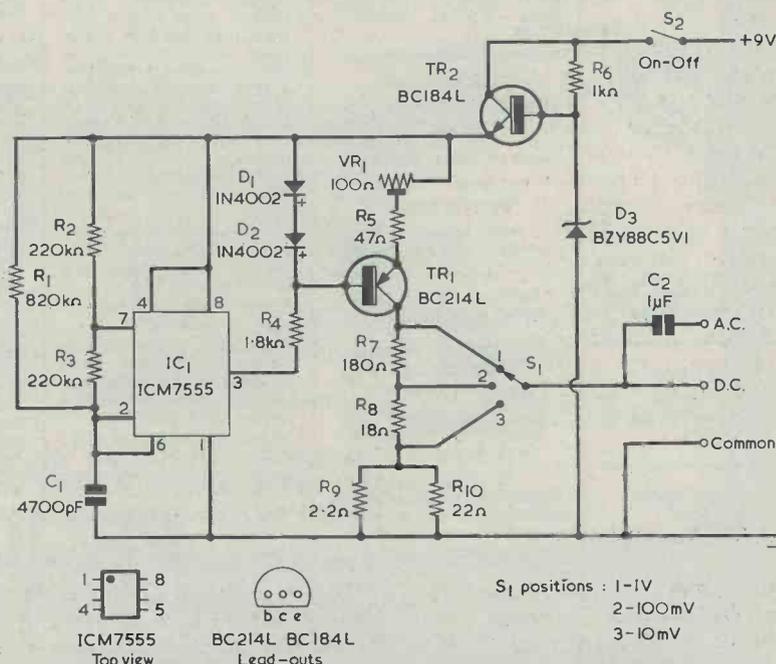


Fig.1. Circuit of the oscilloscope voltage calibrator. Switch S1 selects square waves having the voltage amplitudes shown, and these are applied to the input of the oscilloscope being calibrated

value, and the added resistor R1 has about 4 times that value, the timer produces a square wave with a (calculated) mark-space ratio of 50:50. This neat circuit trick was described by J.R. Davies in the article "50:50 Output From The 555" which appeared in the April 1978 issue of this journal.

The 50:50 square wave output at pin 3 of the ICM7555 is applied via R4 to the two diodes D1 and D2, and to the base of the p.n.p. transistor TR1. When the pin 3 output is high TR1 is cut off and no current flows in its collector circuit through R7 to R10 inclusive. As a result, no voltage appears across these resistors. When the pin 3 output of the i.c. goes low, diodes D1 and D2 conduct and a relatively stable reference voltage of around 1.1 volts is applied to the base of TR1. Pre-set potentiometer VR1 in the emitter circuit of TR1 is set up so that the collector current of the transistor is precisely 5mA. As we shall see shortly, this current enables S1 to tap off positive-going square wave pulses having a high degree of accuracy in terms of voltage amplitude.

TR1 is a constant current generator with an output current which, in practice, remains stable for fairly large changes in supply voltage. Since it is intended that the calibrator be battery driven, whereupon high changes in battery voltage are possible, the circuit as so far described is supplied by the voltage regulator consisting of zener diode D3, R6 and pass transistor TR2. With the prototype circuit this combination of voltage regulator and constant current transistor produces a performance in which there is no noticeable change in output pulse amplitude even when the battery voltage of 9 volts nominal falls well below 7 volts.

POTENTIAL DIVIDER

The 5mA collector current from TR1 which is produced when the pin 3 output of IC1 is low flows through the potential divider consisting of R7, R8, R9 and R10. These are all close tolerance 1% resistors. The parallel combination of R9 and

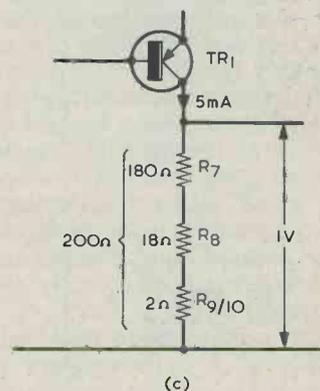
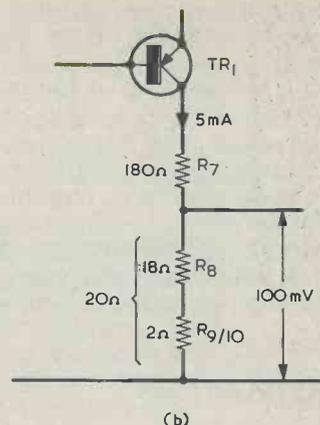
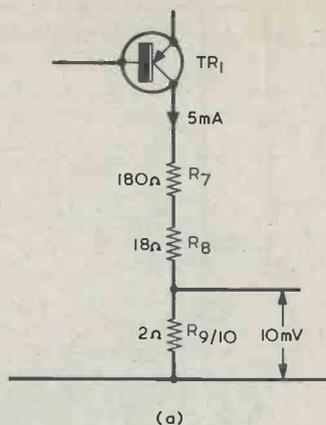


Fig.2(a). With S1 in position 3, the output pulses are produced by the 5mA collector current of TR1 flowing through a resistance of 2Ω

(b). Setting S2 to position 2 produces pulses built up across a 20Ω resistance

(c). 1 volt pulses are given across the total potential divider resistance of 200Ω

R10 produces a resistance of 2Ω. The four values shown can be obtained in 1% tolerance from several component suppliers (e.g. Maplin Electronic Supplies) and may be available with ratings of $\frac{1}{2}$ or $\frac{1}{4}$ watt. Either rating is suitable. If a 2Ω 1% resistor can be obtained this may be used instead of the parallel combination of 2.2Ω and 22Ω which is shown in the diagram.

When S1 is set to position 3, the output pulse is obtained from the combination of R9 and R10, as shown in Fig.2(a). The 5mA from TR1 collector which flows in the 2Ω combination produces a voltage of 10 millivolts. Fig.2(b) shows the situation with S1 in position 2. The 5mA current now flows through a total resistance of 20Ω, producing a voltage amplitude of 100 millivolts. In position 1, S1 selects the voltage dropped across all the potential divider resistors. As is illustrated in Fig.2(c) the resistance now totals 200Ω, giving an output voltage of 1 volt.

Thus, S1 selects square wave pulses having the amplitudes indicated in Fig.1.

These pulses may be directly coupled to the oscilloscope to be calibrated if this is connected to the "Common" and "D.C." output terminals. An a.c. output, given via C2, is provided when the oscilloscope input is connected to the "Common" and "A.C." terminals. All the output impedances are very low, the highest impedance being 200Ω when S1 is at position 1.

Since the 5mA collector current provided by TR1 is only present for half the time, as also is the current flowing through R4 to D1 and D2, this part of the circuit only draws an average current of about 3 to 3.5mA. The total current consumption of the calibrator at 9 volt battery voltage is 7mA, a high proportion of which flows through R6.

The components are all standard parts, and the close tolerance potential divider resistors have already been dealt with. The remaining fixed resistors are all $\frac{1}{4}$ watt 5%. VR1 may be a 0.1 watt skeleton potentiometer, but it will probably be found that greater resolution in setting up, and

improved long term stability, is given if a larger 0.25 watt potentiometer is employed. C1 can be polystyrene or polycarbonate, and C2 polycarbonate or polyester. The frequency of the square waves produced by IC1 can be altered by changing the value of C1. The frequency is inversely proportional to C1, so that if its value is halved the frequency is doubled, and so on.

CONSTRUCTION

The circuit may be assembled in any conventional manner. Layout is not critical provided that interconnecting wiring is kept reasonably short. A suitable housing would be given by an inexpensive plastic case with the two switches and the three output terminals mounted on the front panel. If a metal case is used this should be made common with the negative rail.

After construction has been completed it is necessary to adjust VR1. Initially this potentiometer should be set to insert maximum resistance into cir-

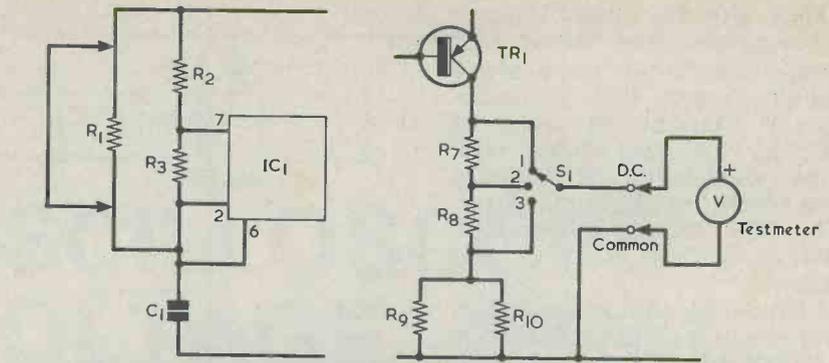


Fig.3. Setting up the calibrator. R1 is temporarily short-circuited, whereupon the pin 3 output of the ICM7555 goes low, turning on the constant current transistor TR1. VR1 in the emitter circuit of TR1 is then adjusted to produce a measured voltage across the potential divider of 1 volt.

cuit. Selector switch S1 should be in position 1 and a testmeter switched to a low volts range connected across the "Common" and "D.C." output terminals, as shown in Fig.3. A temporary short-circuit is connected across R1 so that, when the calibrator is switched on at S2, pins 2 and 6 of the ICM7555 are taken high and its output

forced low.

After switch-on, a voltage of less than 1 volt will be indicated by the meter. VR1 is then adjusted until the meter reads exactly 1 volt. The temporary short-circuit across R1 is next removed, after which the calibrator is fully set up and ready for use.

Keeping Currents Low

By
R. J. Caborn

*Flea-power
oscillator
for CMOS.*

Many CMOS circuits incorporate an oscillator for clock or timing purposes. Since CMOS devices draw exceptionally low supply currents, a minor challenge to the experimenter is given in the designing of low current oscillators for CMOS circuitry.

OSCILLATOR CIRCUITS

The well-known CMOS relaxation oscillator illustrated in Fig. 1 is often employed. When running at audio frequencies, this type of oscillator can draw a surprisingly high current of several hundred microamps at 9 volts. It has to be remembered that a CMOS gate only draws a significant current when its input passes through the voltage range at which linear amplification takes place, and that the quicker the input passes through this range the lower is the overall average current. With the oscillator of Fig. 1 at least one of the gate inputs goes through its transition at a relatively slow rate; hence the high overall current. The ICM7555 (the "CMOS 555") is more attractive. This draws a current of about $70\mu\text{A}$ at 9 volts and has the further advantage that its output changes extremely rapidly from the high to the low


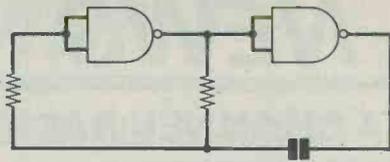


Fig. 1. A common CMOS relaxation oscillator using two NAND gates acting as inverters. Two NOR gates, similarly connected, would give the same performance

Fig. 2. The multivibrator consisting of the circuitry around TR1 and TR2 draws an extremely low supply current. However, supply voltage is restricted to 4.5 volts.

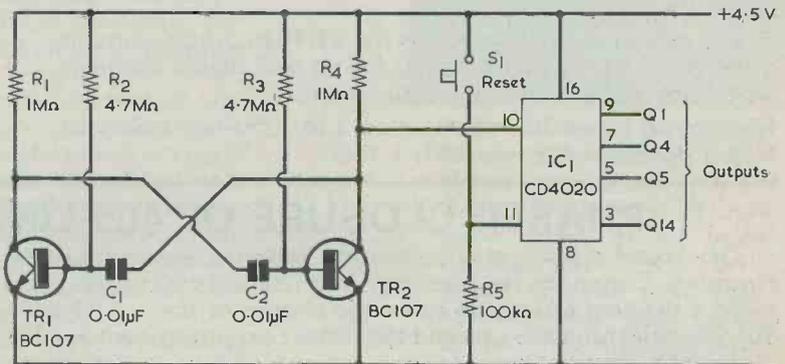

state and vice versa. This very fast output transition results in very low current-demands in CMOS gates whose inputs are connected to the ICM7555 output.

An alternative oscillator circuit which the author has used offers even lower consumption than the ICM7555, provided certain requirements peculiar to the circuit are satisfied. It consists of the multivibrator shown in Fig. 2, in which an output is fed to the pulse input of a CD4020. The latter is a 14-stage binary divider, and its Q14 output at pin 3 offers division by 2 to the power of 14, or 16,384 times. However, the device following the multivibrator is incidental to the present discussion as we are interested in the multivibrator itself. The device it drives can be any CMOS gate or divider.

The multivibrator is made to draw a low current by the simple expedient of using high value collector and base resistors. The current flowing in either R1 or R4 from the 4.5 volt supply cannot exceed $4.5\mu\text{A}$ and, since only one transistor is turned on at a time, total collector current has to be around this level. Immediately after the multivibrator changeover the current in R2 or R3 is about $2\mu\text{A}$, falling to about $1\mu\text{A}$ as the appropriate cross-coupling capacitor discharges. The multivibrator runs at about 16Hz and, without the CD4020 in circuit, the measured current consump-

tion is $7\mu\text{A}$. When the CD4020 is connected into circuit the total current consumption rises to $10\mu\text{A}$. It follows from this that the output transitions at TR2 collector are a little slow, and not as fast as those from an ICM7555. Nevertheless, overall performance in terms of current consumption is better than would be given with an ICM7555.

Although the two transistors are operating at very low current levels the multivibrator works well with all transistors checked in it and has been found to be reliably self-starting.

Note that the supply voltage is 4.5 volts only. This low voltage is necessary because the maximum reverse base-emitter voltage rating for the BC107 is 5 volts. If the base-emitter junction is taken to breakdown level it zeners and upsets multivibrator operation. In consequence the multivibrator, using the circuit as shown, should only be run at supply voltages below the base-emitter voltage rating of the transistors.

As proof of this fact the circuit of Fig. 2 was run at 9 volts. With the CD4020 out of circuit, current consumption was $14\mu\text{A}$, but it rose to as much as $100\mu\text{A}$ when the CD4020 was added. This high increase was due to a distorted output from TR2 collector causing slow switching in the input gate of the CD4020. ■

NEWS . . . AND

4 CHANNEL RADIO CONTROL IN ONLY TWO ICs.

The increasing interest in electronic toys has led to a considerable upsurge in remote control in applications previously considered to be the province of the 'toy' manufacturer. The majority of the current toys are crude non-proportional control systems, using AM transmissions with superregenerative receivers in the 27MHz radio control band.

TOKO have announced a new approach to the production of low cost digital proportional radio control system for the 27MHz to 50MHz radio control bands.

The KB4445 is a complete 4 channel encoder, with crystal oscillator and FM modulator system, giving approx. 30mW RF output, which is readily boosted to a watt or more with a single transistor stage.

The companion receiver IC is the KB4446, which contains a complete RF Decoder system for up to 5 digital channels with a total of less than 25 components.

Distributed by Ambit International Ltd., 200 North Service Road, Brentwood, Essex CM14 4SG.



PHASED CLOSURE OF 405-LINE TV NETWORK

The Home Secretary in a written reply in the House of Commons on Tuesday, May 20th, 1980 made a detailed statement about the closure of the 405-line television services and the further extension of the 625-line services.

His statement began: "The 405-line VHF television services of the BBC and the IBA transmit BBC-1 and ITV in black and white only and are now substantially duplicated by the 625-line UHF services which transmit BBC-1, BBC-2 and ITV in colour, and which will in due course transmit the fourth channel service. Phase II of the current UHF engineering programme for extending the 625-line services to communities with populations of 500 or more (over

99% of the population) should be completed by about 1984.

"I have, therefore, agreed with the broadcasting authorities on a timetable for the closure of the 405-line services. Closure will begin in 1982 and will be phased over a period of about 4 years."

The BBC and the IBA are co-operating closely in the implementation of these engineering programmes in order to minimise any inconvenience to the public. As far as possible they plan to close down their 405-line services in Bands I and III at the same time in particular areas, although this will not be possible everywhere since the BBC have 110 transmitters on 405-lines while the IBA have 47.

NEW BRITISH MADE MONOCHROME TV's



The new 12 inch monochrome portable television designed and produced by Fidelity Radio Limited of London, NW10.

Fidelity Radio Limited, London, NW10 have become, it is claimed, the first British manufacturer to enter the monochrome television market for many years with a totally new 12 inch portable, designed and produced exclusively by themselves.

The latest TV technology and the company's long experience of value-for-money volume production in the radio and audio field, where they are Britain's leading manufacturer, will enable their new television to be one of the lowest priced quality models available.

Features of the new 12 inch monochrome television, designed to claim a substantial share of the market currently running at about 1.2 million units per annum are an essentially simple design, hence good reliability, easy operation and servicing and the provision of a two year guarantee.

Powered by 12v battery mains the white moulded cabinet houses circuitry employing the latest techniques. Programme selection is by rotary tuning and a single control combines on/off and volume. A brightness control and ear-phone socket are included together with a loop aerial and battery leads.

The new Fidelity television is expected to reach shops by the autumn.

... COMMENT

TEXAS HOME COMPUTERS FOR UK MARKET

Low cost multi purpose domestic computers have hit the UK at last. Sussex based Scan Computers has launched on to the market a home computer costing about £1,000 all-in; a price made even more incredible by the fact that the VDU monitor doubles as a second household colour TV, receiving all normal TV channels.

The new incredibly compact computer is the Texas Instruments TI-99/4, manufactured in the USA and marketed by Scan Computers under an agreement newly signed with Texas Instruments in the UK. It consists of a compact keyboard and processor unit plus a colour TV monitor. Unique solid-state command modules plug into the processor to program the machine for personal finance, home records, educational purposes and entertainment. Readily available solid-state pre programmed modules can be purchased for all these functions from as little as £16.95.

Alternatively, easy to follow instruction booklets teach you to program the machines yourself. The home computer is capable of keeping the accounts for a small business, of charting sales results – you name it, the TI-99/4 can probably do it.

The home computer can even speak – synthesising a human voice with a Solid State Speech synthesiser. You type in the word – the computer speaks it or tells you that you have spelt it wrongly. This capability is an invaluable teaching aid for children, particularly those with learning difficulties.

Scan Computers' Managing Director Steve Russell is delighted with the agreement that enables his company to market the TI Domestic Computer. He said "We're marketing this amazing machine direct to the public or to any retail outlet that expresses interest. People are going to love it."



The T1-99/4 Domestic Computer being marketed for under £1,000 by Scan Computers. It can keep track of all your house accounts, will teach you to spell correctly, and can even speak! The monitor doubles as a second household colour TV set, receiving all normal TV channels.

DIGITAL-VIDEO ON IBA'S SMALL-DISH SATELLITE TERMINAL

The first reception on a small-dish satellite terminal of digital-video television transmissions through a European space satellite has been successfully achieved at the IBA Engineering Centre at Crawley Court, Winchester.

This was in the course of experimental work being carried out with the assistance and co-operation of the British Post Office and the European EUTEL-SAT organisation, using the OTS experimental geostationary satellite launched in May 1978.

The first digitized pictures – of excellent quality – were received by IBA engineers on April 25, 1980 and were transmitted to the satellite from the Post Office's 14 GHz satellite terminal at Goonhilly

Downs, Cornwall, where an experimental IBA digital encoder had been installed for the purpose. The downcoming signals were received and decoded on the IBA's 11GHz space terminal which was built in 1977 and which has a dish-aerial only three metres in diameter.

For these experiments, a conventional 625-line analogue television picture was encoded and transmitted through the 120MHz-bandwidth OTS transponder using a bandwidth of some 40MHz and modulated by means of quadrature phase-shift keying. The pictures were initially sampled at four times the frequency of the colour sub-carrier (142Mbit/s) and then digitally converted to the equivalent of twice sub-carrier frequency sampling (71 Mbit/s). This data rate is then further reduced by means of bit-reduction techniques including the use of differential pulse code modulation and, when error-protection and 'house-keeping' bits are added the system has a bit rate of 60Mbit/s.

The purpose of the experiments is to establish the relative merits of digital (QPSK) and analogue (FM) modulation techniques for international distribution of television pictures and to determine the minimum size of dish aerial for a given satellite power needed for the reliable reception of good quality pictures when using digital techniques.

The digital sampling rate and techniques used in these trials are for experimental purposes only and are not being proposed as an international standard.

LATE PUBLICATION

We apologise to our readers for the late publication of this issue, and the preceding one, due to the recent dispute in the printing industry. Such disruption, unfortunately, adversely affects print schedules for some time ahead.

The next issue should be available by mid July and future issues will be published a little earlier each month until the normal publication date is achieved.

We regret the inconvenience caused to readers which is through no fault of ours or that of the distributive trade.

CAPACITANCE MEASURING ADAPTOR

by
R.A. Penfold

Neat add-on unit allows your testmeter to measure capacitance. Five switched ranges from 0-2,500pF to 0-5 μ F.

When used in conjunction with an analogue multimeter set to a 0-50 μ A range, this simple device provides the following five ranges of capacitance measurement: 0-2, 500pF, 0-5,000pF, 0-0.05 μ F, 0-0.5 μ F and 0-5 μ F. Most multimeters do not have provision for measuring capacitance and their usefulness will be considerably enhanced by the use of this add-on instrument.

Many multimeters have a 0-50 μ A range, but the unit can also be used with multimeters not having such a range, as is explained at the end of the article. All that is required is a modification to two of the resistor values in the unit.

The output of the add-on adaptor does not consist of a straightforward direct current, but is instead a series of pulses. These pulses are averaged in an analogue meter to give a single steady reading. Because of the nature of the output, the unit cannot be employed with a digital multimeter.

If preferred, the adaptor could be built as a completely self-contained capacitance measuring instrument having its own 0-50 μ panel-mounted meter. However, the cost of good quality panel meters is relatively high these days, and an obvious saving is given by employing the unit with a multimeter which will already be on hand.

OPERATING PRINCIPLE

The method of operation is quite conventional and is shown in block diagram form in Fig.1. A clock oscillator running at a fixed frequency triggers a monostable, which produces a positive output pulse


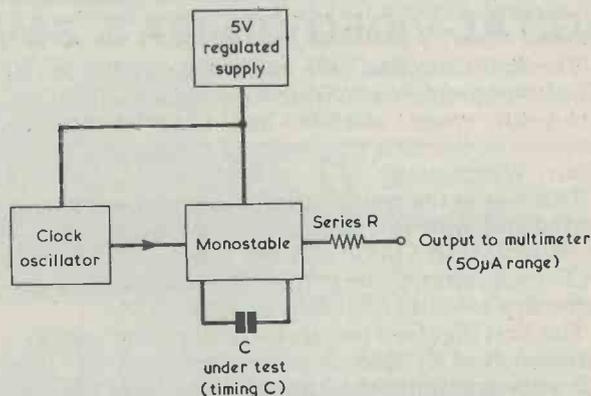


Fig.1. Block diagram illustrating the operating principle of the adaptor. This is employed in conjunction with an existing multimeter switched to a low current range

at each cycle from the oscillator. These pulses are applied to the multimeter, switched to a 0-50 μ A range, via the series resistor shown. The duration of each monostable pulse is controlled by a timing resistor and a timing capacitor, and is proportional to the values of both. The timing capacitor is the capacitor being measured whilst the timing resistor is, in practice, one of five different resistances which is switched in to provide the required capacitance range.

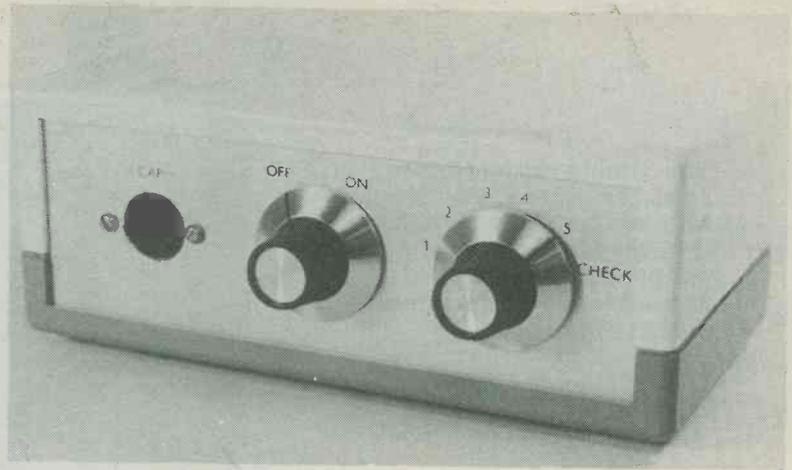Housed in an attractive Verobox, the add-on adaptor presents a tidy and neat appearance



The circuit values are arranged such that the multimeter gives full-scale deflection for the maximum capacitance in each range. In, for example, the last of the ranges just referred to, a $5\mu\text{F}$ test capacitor will give a reading in the multimeter of $50\mu\text{A}$. If the $5\mu\text{F}$ test capacitor is replaced by a $2.5\mu\text{F}$ capacitor the same number of output pulses will be produced in a given time but each will have half the duration of the previous ones. The multimeter, measuring the average current, will then give an indication of $25\mu\text{A}$. Similarly, a $1\mu\text{F}$ capacitor will give a reading of $10\mu\text{A}$ and so on.

Since the output current indicated by the multimeter is directly proportional to test capacitance, the overall effect is that of a linear scale capacitance meter. The existing meter calibration does not require any alteration. The use of a $0-50\mu\text{A}$ scale on a multimeter is particularly useful here as this scale corresponds directly to four of the five capacitance ranges provided. It would, of course, be nearly as easy to interpolate readings from a multimeter having, say, a linear scale calibrated from 0 to 100.

The unit is powered by its own 9 volt battery which


couple into a 5 volt monolithic regulator i.c. to give a very stable supply voltage to both the clock oscillator and the monostable. In consequence, the oscillator frequency is not altered due to changes in battery voltage, nor is the voltage amplitude of the pulses from the monostable. Readings are not therefore affected by falling battery voltage. The unit also has a position of the range switch which allows the battery voltage to be checked by the multimeter.

FULL CIRCUIT


The full circuit is shown in Fig.2. In this a CA3140E operational amplifier is employed as the clock oscillator, and a 555 timer as the monostable.

Dealing first with the oscillator, the non-inverting input of the CA3140E has a potential which is controlled by R1, R2 and R3. All of these resistors have the same value of $47\text{k}\Omega$ with the result that, if the output of the op-amp is high the voltage at the non-inverting input is two-thirds of the supply voltage and, if the output is low, the non-inverting input voltage is one-third of supply voltage. Capacitor C2 is connected between the inverting input and the negative


Fig.2. The circuit of the adaptor. The full type number of IC3 is given in the Components List and it is shown inset here with the lead-outs pointing towards the reader

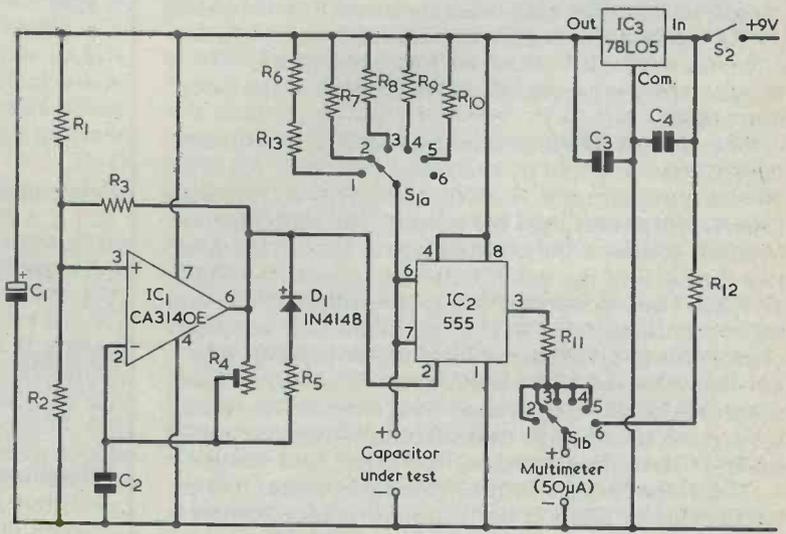

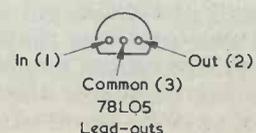- S₁ positions :
- 1 - 0 - 2,500pF
 - 2 - 0 - 5,000pF
 - 3 - 0 - 0.05µF
 - 4 - 0 - 0.5µF
 - 5 - 0 - 5µF
 - 6 - Battery check



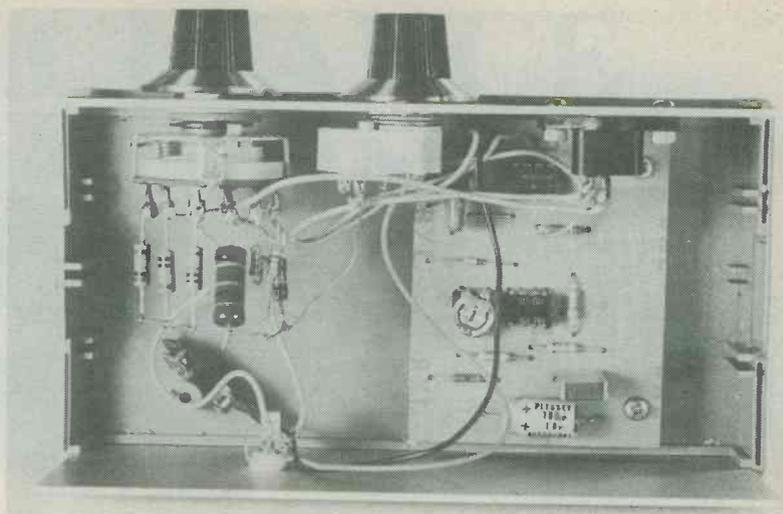The timing resistors are soldered direct to the tags of the range switch, whilst the remaining small components are assembled on a printed circuit board



rail. Immediately after switch-on it will be discharged, whereupon the op-amp output will be high. The capacitor charges via R4 until the voltage across it reaches and marginally passes two-thirds of the supply voltage. The op-amp passes two-thirds of the supply voltage. The op-amp output will then swing low, whereupon the capacitor discharges via R4, R5 and the now forward biased D1 until the voltage across it falls to very slightly less than one-third of the supply voltage. The op-amp output then swings high again, the capacitor starts to charge to two-thirds of the supply voltage once more and the clock oscillator cycles then continue. The hysteresis effect in the circuit is the same as that given with a Schmitt trigger, and is essential for the operation of this type of oscillator.

Because R5 has a very much lower value than R4 (after the latter has been set up) the length of the negative-going pulse from the clock oscillator is extremely short, and is very much shorter than the positive pulse. It is this negative pulse which triggers the 555 monostable and it has to have almost negligible duration because the monostable cannot produce an output pulse shorter than the negative pulse which triggers it. Since R5 has a value which should be less than one-three hundredth of the value of R4 after adjustment, the unit offers resolution down to very low values of test capacitance which would hardly cause significant deflection of the meter movement.

The monostable is a standard 555 circuit with timing resistors selected by the range switch S1 (a). The 555 output connects via R11 and S1(b) to the multimeter which monitors the output. The sixth position of S1(b) connects the multimeter via R12 to the positive terminal of the 9 volt battery to check its voltage on load. The clock frequency is controlled by R4, and this potentiometer is set up after the unit has been completed to give the required meter reading with a known value of test capacitance. If all the timing resistors are close tolerance components the setting up process needs to be carried out on only one range and will then hold good for the other four ranges.

The value chosen for R12 causes the meter to have a full-scale deflection corresponding approximately to 10 volts. The battery should be replaced when its voltage falls to 7.5 volts or less.

The 5 volt stabilized supply is provided by IC3, which is a small 100mA monolithic regulator. C3 and C4 are bypass capacitors which ensure stability in the regulator. S2 is the on-off switch. The current drawn

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt unless otherwise stated. See text for values indicated as close tolerance)

- R1 47k Ω
- R2 47k Ω
- R3 47k Ω
- R4 220k Ω pre-set potentiometer, 0.1 watt, horizontal
- R5 330 Ω
- R6 10M Ω close tolerance
- R7 10M Ω close tolerance
- R8 1M Ω close tolerance
- R9 100k Ω close tolerance
- R10 10k Ω close tolerance
- R11 82k Ω
- R12 200k Ω
- R13 10M Ω close tolerance

Capacitors

- C1 100 μ F electrolytic, 10V Wkg.
 - C2 0.1 μ F type C280
 - C3 0.1 μ F type C280
 - C4 0.1 μ F type C280
- Setting up capacitor (see text)

Semiconductors

- IC1 CA3140E
- IC2 555
- IC3 μ A78L05AWC (+5V 100mA regulator)
- D1 1N4148


Switches

- S1(a)(b) 2-pole 6-way rotary
- S2 s.p.s.t. toggle rotary

Miscellaneous

- Verobox type 75-1238-D (see text)
- 3.5mm jack socket
- 3.5mm jack plug
- 2-way DIN socket
- 2-way DIN plug
- 2 crocodile clips
- 9-volt battery type PP3
- Battery connector
- 2 control knobs
- Printed circuit board
- Wire, solder, etc.

Fig.3. Component and copper sides of the printed circuit board

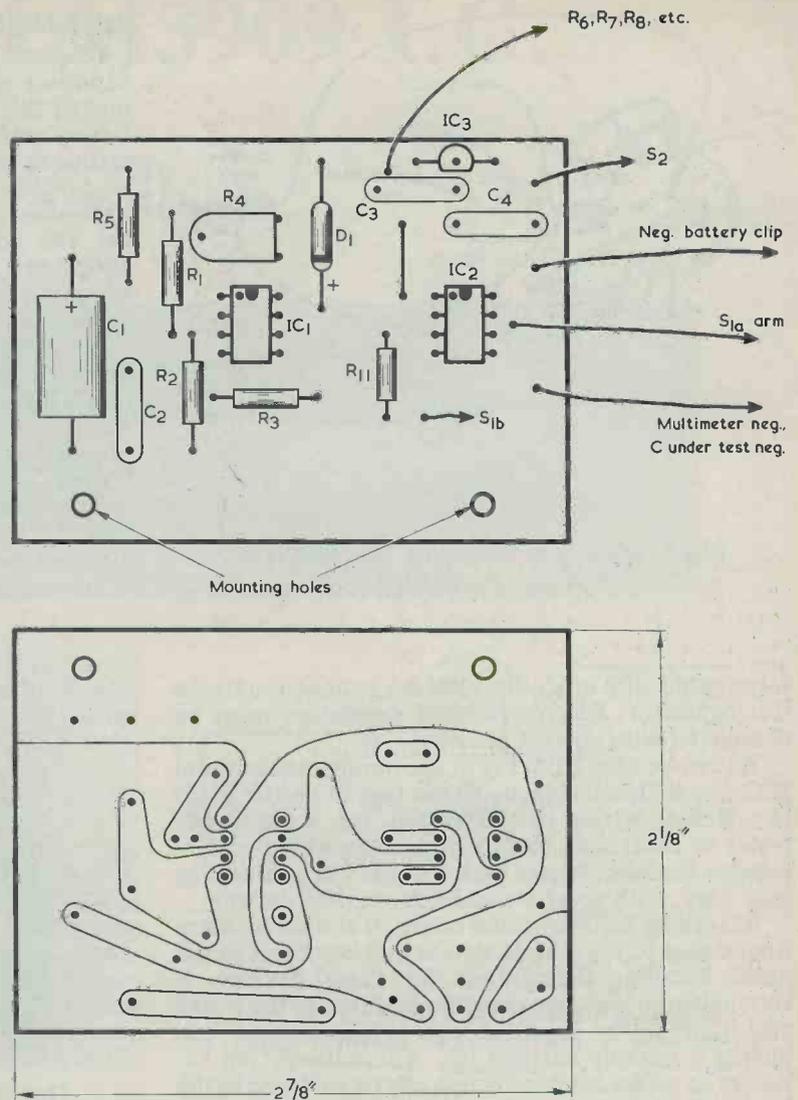

from the 9 volt battery is about 9mA, and this gives a reasonably long life from a PP3 battery, as is used in the author's unit. If it is intended that the add-on adaptor be employed extensively rather than occasionally, as would normally be the case in an experimenter's workshop, a larger battery would represent a more economic choice, and it might then be necessary to employ a larger case than that used for the prototype. This case is a Verobox type 75-1238-D with nominal outside dimensions of 153 by 84 by 59mm.

The timing resistors, R6 to R10 and R13 should be close tolerance types, and values up to and including 1MΩ are readily available in 2% or, better, in 1%. The closest tolerance in which the 10MΩ resistors R6, R7 and R13 are generally offered is 5% and, if a slight lack of accuracy on Ranges 1 and 2 can be accepted, these three resistors may have that tolerance. In this case, setting up should be carried out on Range 3, 4 or 5. Readers who are fortunate enough to have access to accurate resistance measuring equipment may be able to select resistors for the three 10MΩ positions. It is, of course, perfectly in order to use timing resistors having a higher wattage rating than the ¼ watt figure given in the Components List. The maximum permissible timing resistance for the 555 is 20MΩ, and this limits the minimum capacitances which can be measured to those given with Range 1.

CONSTRUCTION

Many of the components are assembled on a small printed circuit board which is shown full size in Fig.3. This board is prepared in the usual manner. The specified Verobox has two mounting pillars and the board is secured to these by means of two of the self-tapping screws supplied with the case. For optimum accuracy, the positions of the two mounting holes in the board should be checked physically against the mounting pillars in the Verobox before drilling them. The board is not finally mounted until it has been wired up to the remainder of the components.

The wiring external to the board is illustrated in Fig.4. A 2-way DIN socket is used for the connections to the test capacitor and this socket, together with S1(a) (b) and S2, is mounted on the front panel. A 3.5mm. jack socket mounted on the rear panel is used for the connection to the multimeter. The jack plug which fits into this has the negative connection at its "sleeve" and the positive connection at its "tip".

Most small capacitors can have their lead-outs passed into the contacts of the DIN socket on the front panel without difficulty. For other capacitors, a test lead assembly must be made up. This simply consists of a DIN plug with a short red flexible lead connected to the positive contact and a short black flexible lead connected to the negative contact. The two leads are


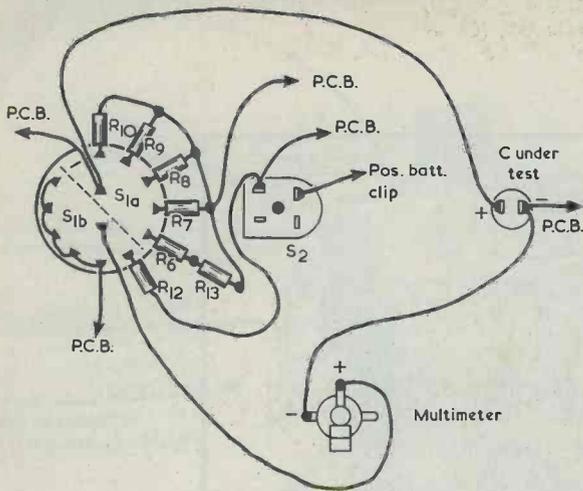


Fig.4. Wiring external to the board is carried out as shown here

terminated with crocodile clips for connection to the test capacitor. Electrolytic test capacitors must be connected with correct polarity.

As can be seen from Fig.4, the timing resistors and R12 are soldered directly to the tags of switch S1(a) (b). Before wiring to this switch, use a continuity tester to determine the six outer tags which correspond to the inner tags of each section. Tag positioning may vary, with some switches, from that shown.

Returning to the printed board, it should be mentioned that IC1 is a MOS device and is subject to the usual handling precautions for these devices. It should be the last component to be fitted to the board and it should be soldered into circuit with an iron having a reliably earthed bit. Alternatively, an i.c. holder or soldercon connectors can be soldered to the board and the i.c. fitted afterwards. (The photograph of the board does not, incidentally, show the lead which takes the stabilized 5 volt supply to the timing resistors. The photograph was taken before the design was finally developed.)

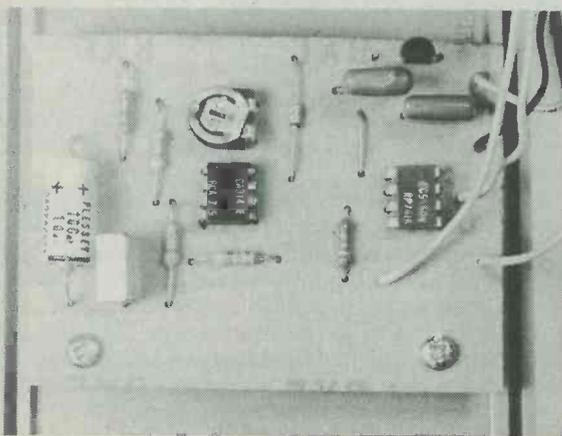


The three i.c.'s and their immediate components are wired up on the printed board

SETTING UP

The unit is set up with the aid of a close tolerance capacitor whose value is near the maximum value of one of the ranges. If, as was mentioned earlier, 5% timing resistors are used for Ranges 1 and 2, the setting up process should be carried out on Range 3, 4 or 5. Close tolerance capacitors are fairly easy to obtain and, for instance, Maplin Electronic Supplies list 1% polystyrene capacitors with values from 100pF to 0.022 μ F. Two 0.022 μ F capacitors in parallel would give a test capacitance of 0.044 μ F, which could be used on Range 3.

R4 is initially set fully anti-clockwise and the multimeter and the test capacitor are connected to the unit. This is switched on at S2 and R4 is next carefully adjusted for the appropriate meter reading. Setting up is then complete and the add-on adaptor is ready for use.

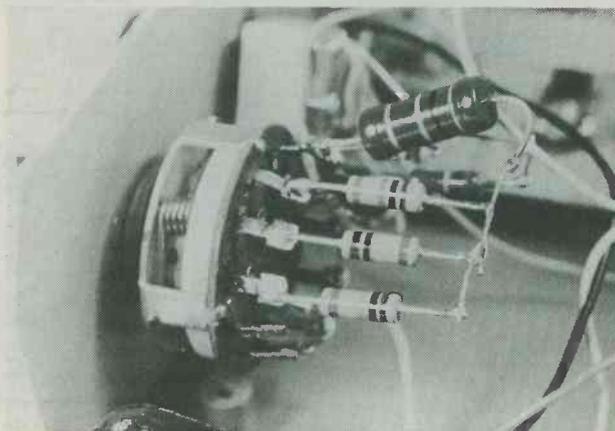The completed adaptor should be found to have excellent linearity and accuracy. Despite the simplicity of its design it should give results that are more than accurate for normal amateur requirements.



The timing resistors. These are close tolerance types and it may be necessary to obtain some or all of them with wattage ratings greater than 1/4 watt

OTHER METER CURRENTS

The unit can be used with meters having current ranges other than 0-50 μ A by changing the value of R11. This value, in kilohms, is equal to 4 divided by the f.s.d. current of the meter in milliamps. A 0-100 μ A meter would require R11 to have a value of 4 divided by 0.1, or 40k Ω . Similarly, a 1mA meter would need a value of 4k Ω in R11. In practice the nearest preferred value in 5% (39k Ω and 3.9k Ω in the two examples just given) would be employed, since slight differences here are taken up in the setting up procedure.

The value of R12 would also need to be altered. This, in kilohms, is equal to 10 divided by the meter current in milliamps, and for a 0-100 μ A meter would require a 100k Ω resistor for R12, and a 0-1 mA meter would require a 10k Ω resistor. The battery voltage measurements are intended to be approximate only, but purists who require high accuracy here can first find empirically a value for R12 which takes in the voltage dropped across the multimeter and then fit this value to the printed board. ■

THE LM3909 I.C.

By
A. P. Roberts

8-pin i.c. with both useful and novelty applications

Although it is one of the simplest i.c.'s currently available, the LM3909 has many useful home-constructor applications. Contained in a standard 8-pin d.i.1. encapsulation, it is primarily designed to act as a low frequency low power oscillator.

INTERNAL CIRCUITRY

Fig. 1 shows the internal arrangements of the device and the method of using it in a simple l.e.d. flasher circuit. When power is initially connected to the circuit the discrete capacitor C1 will obviously be in a discharged state. Due to the relatively low value of R4 in the potential divider consisting of R4, R2 and R3, nearly the full positive supply voltage is then applied to the voltage detector. The detector passes a signal to the electronic switch which keeps it in the open condition.

C1 commences to charge whereupon the voltages across R4, R2 and R3 fall accordingly. When the

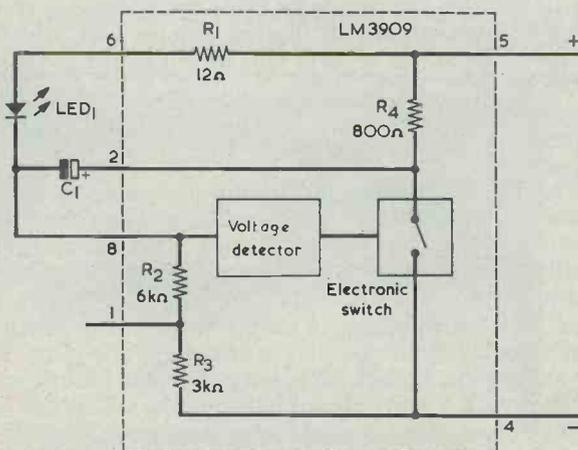


Fig. 1. The internal functions of the LM3909 (shown inside the broken line) and its use as an l.e.d. flasher.

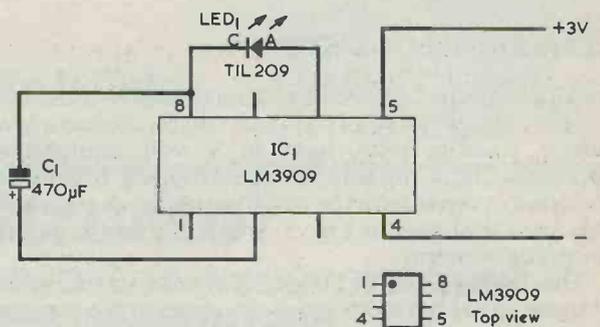


Fig. 2. Practical 3 volt circuit giving an approximate flashing rate of one per second.

voltage across R2 and R3 in series drops to a predetermined low level the voltage detector triggers the electronic switch on. This takes the positive terminal of C1 down to the negative rail whereupon the charge voltage in C1 is effectively connected in series with the supply voltage. A voltage which is higher than the supply voltage is therefore applied across the l.e.d. and current limiting resistor R1.

The l.e.d. flashes and C1 discharges rapidly. The altered voltage conditions cause the voltage detector to open the electronic switch and C1 charges once more via R4, R2 and R3. When C1 is sufficiently charged the electronic switch closes again to give another flash in the l.e.d. The cycles then proceed in the same manner, giving a series of l.e.d. flashes. As will be gathered, the circuit is really a form of relaxation oscillator.

TORCH FINDER

A typical application for the LM3909 is as a torch finder or as a flasher to show the location of important items at night time. A suitable circuit is given in Fig. 2, where C1 is given a value which provides a flash rate of roughly one per second, although the actual rate can vary from one circuit to another due to the wide

tolerance on value of electrolytic capacitors and other factors such as supply voltage. The flashing light enables the torch or other item to be easily found in the dark, and the circuit can be left on continuously with only a low current drain from the battery.

The average current consumption of the Fig. 2 circuit is $500\mu\text{A}$. This is an average figure as the actual consumption varies considerably during the oscillation cycle. The circuit will also function from a 1.5 volt supply, even though 1.5 volts is not sufficient in itself to turn on a light-emitting diode. As was just explained, an extra voltage is obtained from the charged C1. The operating frequency becomes lowered as the supply voltage decreases to this level and, with a 1.5 volt supply, the value of C1 should be changed to $220\mu\text{F}$ to maintain the flashing rate at about one per second. The average current drawn from the 1.5 volt supply is only of the order of $300\mu\text{A}$.

The circuit of Fig. 2 can be employed, without modification, with a 4.5 volt supply. The average current demand is then approximately $800\mu\text{A}$.

FLASHING PILOT LIGHT

Although the LM3909 has a maximum permissible supply voltage rating of 6 volts, it can be used as a low power flashing pilot light in 9 volt equipment provided that a suitable voltage dropping resistor is included in series with the positive supply. A circuit of this type is shown in Fig. 3, where R1 is the series dropping resistor.

The flashing circuit proper functions in the same manner as has been described. Because of the varying current demands during the flashing cycle it is essential to include the bypass capacitor C2, which smooths out voltage variations and ensures that the voltage applied to the i.c. always stays within acceptable levels. C2 must on no account be omitted as device operation would then be upset, and the supply voltage applied to the i.c. could exceed the maximum permissible level.

The Fig. 3 circuit gives a flashing rate of around one per second, and the average current consumption from the 9 volt supply is only about $300\mu\text{A}$. The circuit will also work from a 12 volt supply, with a slightly higher current consumption of approximately $500\mu\text{A}$.

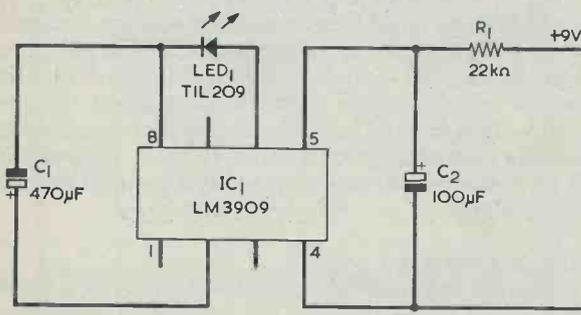


Fig. 3. The circuit arranged to operate from a 9 volt supply.

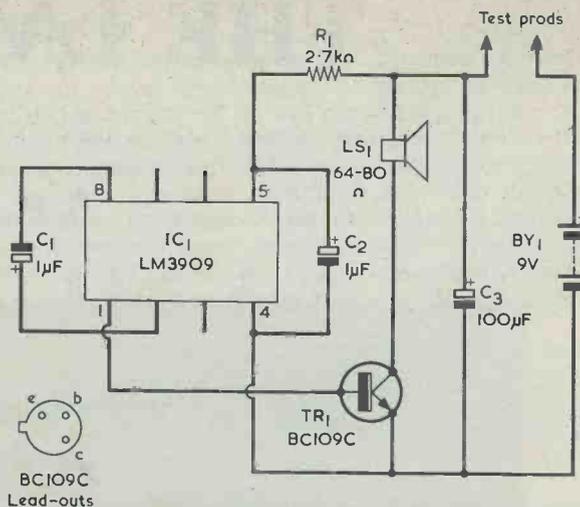


Fig. 4. The LM3909 may also be employed as an audio frequency oscillator. In this circuit it functions as an a.f. continuity tester.

CONTINUITY TESTER

A device as versatile as the LM3909 is not, of course, confined to l.e.d. flasher applications. It can be employed for other low frequency oscillator applications including sound generator circuits. An example is the continuity tester shown in Fig. 4.

The oscillator circuit is much the same as in the previous examples but as the l.e.d. is not now required this component is omitted. The discharge path for the timing capacitor, C1, is through two internal resistors in the i.c. (R2 and R3 of Fig. 1). C1 is given a much lower value than before, so that the operating frequency is raised to a few hundred Hertz. R1 is a voltage dropper resistor and is necessary because the circuit is powered by a 9 volt battery. C2 ensures that the voltage across the i.c. supply pins is maintained at a satisfactorily low level during the oscillatory cycle.

TR1 is a high gain common emitter amplifier with a high impedance speaker as its collector load. Its base couples to pin 1 of the LM3909 which, as was shown in Fig. 1, connects to the junction of R2 and R3 inside the i.c. During the oscillator cycle the voltage at this junction rises sufficiently high to turn on TR1, which causes a current of several tens of milliamps to flow in the speaker. These pulses of current in the speaker produce a loud audio tone. Between the pulses TR1 is turned off. Capacitor C3 is merely a supply bypass capacitor.

The circuit functions as a continuity tester because power is only applied to the oscillator when there is continuity between the test prods. The circuit still oscillates when there is a resistance between the two test prods but, because operating frequency varies a great deal with changes in supply voltage, this condition causes a readily apparent change in the pitch of the audio tone. In fact, there is a noticeable difference in the note if a short-circuit between the test prods is changed to a resistance of just a few ohms. The current drawn by the continuity tester from the 9 volt supply is 20mA.

In all the circuits, the electrolytic capacitors should have a working voltage higher than the supply voltage employed.

IN OUR NEXT ISSUE

PORTABLE SHORT WAVE RADIO

- Suitable for newcomers
- Employs only one i.c. and one transistor
- Covers 25, 31, 41 and 49 metre bands



The INSTRUCTOR


A FULLY CONSTRUCTIONAL PROJECT INCORPORATING
AN INS8060 MICROPROCESSOR CHIP

- *A Practical introduction to microprocessor functioning*
- *Relatively small number of components required*
- *An instructional project*

Featured in our new 8-part series, the INSTRUCTOR is a fully constructional project incorporating an INS8060 microprocessor chip which provides a practical introduction to microprocessor functioning. Where previously you read about microprocessors you will now be able to handle a working microprocessor i.c. with power applied. Clock frequency is considerably reduced to enable inputs to be applied by push-buttons and by a 10-way digital slide switch. Readout is given by light-emitting diodes. The relatively small number of components required are wired up in breadboard form and most can be used in other projects later. The INSTRUCTOR is not a mini-computer – it is an instructional project which illustrates in slow-motion form exactly how a microprocessor deals with its input data and program commands.

A. F. MILLIVOLT METER


Small
Self-contained
Unit

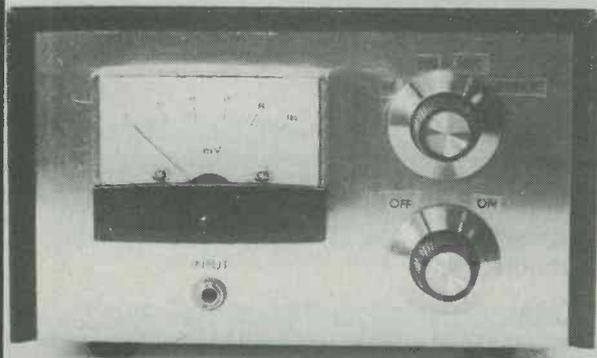

PLUS MANY OTHER ARTICLES

SHORT WAVE NEWS

FOR DX LISTENERS

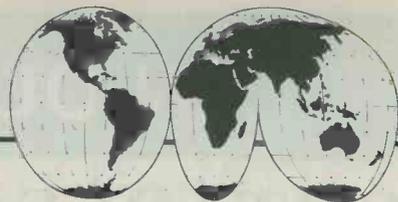

By Frank A. Baldwin

Times = GMT

Frequencies = kHz

Just recently a brief survey was made of that most difficult of bands – the 90 metre part of the dial (3200 to 3400 kHz) – simply to assess the current situation. The brief period amounted to a couple of hours on three evenings of the month; the following being most of the results obtained.

● SOUTH AFRICA

“Radio Five”, Johannesburg on **3250** at 1805, pops on records, OM announcer in English. Radio Five closes at 2200, at which time the All Night Service begins.

● BURUNDI

Bjumbura on **3300** at 1810, OM with a newcast in French. This is a good time to log this one – later in the evening the channel is covered by commercial QRM.

● CHINA

CPBS Peking on **3220** at 2046, YL with a song in Chinese in the Domestic Service 1 programme which closes at 2200 on this channel.

● GHANA

Ejura on **3350** at 2053, OM and YL with a discussion in vernacular.

Accra on a measured **3367** at 2056, OM with announcements in English followed by a programme of local pops.

● NIGERIA

Lagos on a measured **3326** at 1925, OM with a talk in English about national defences.

● RWANDA

Kigali on **3330** at 1813, OM with a newcast in French.

● MALAWI

Blantyre on **3380** at 1818, OM with the local news in English.

AROUND THE DIAL

In which are listed some of the interesting loggings recently made on the various bands covered – use these as a general guide for those countries you wish to hear and/or QSL.

● FINLAND

Helsinki on **15400** at 1325, OM and YL with a discussion on Finnish internal affairs in the English programme announced here from 1300 to 1330. Also logged in parallel on **15265**, this latter channel providing the best reception here in the U.K.

● SWITZERLAND

Berne on **21570** at 1345, recorded dance music 1950 style in the English programme scheduled here from 1315 to 1345.

● PORTUGAL

Lisbon on **21495** at 1348, OM with a talk in Portuguese to the Cape Verde Islands.

● CZECHOSLOVAKIA

Prague on **17840** at 1730, YL with station identification and programme details at the commencement of the English transmission to Africa, followed by OM with a newcast. The English programme ended at 1825.

● HOLLAND

Hilversum on **17605** at 1740, OM with news of internal affairs in the Dutch programme for Africa and Europe.

● ROMANIA

Bucharest on **17720** at 1750, OM with station identification and “Radio Review” in the English programme announced for Africa, scheduled from 1730 to 1800.

● BULGARIA

Sofia on **11720** at 1731, OM with station identification and announcements at the commencement of the German programme for Europe, on the air from 1730 to 1800. A newcast of world events followed.

Sofia on **11765** at 1724, OM with a talk in Arabic for the Middle East.

● POLAND

Warsaw on **11840** at 1735, YL with news of Poland in the Italian programme which ended at 1800.

● YUGOSLAVIA

Belgrade on **11735** at 1738, OM with a newcast in Arabic, presumably for Arabian consumption.

● **CUBA**

Havana on **15385** at 1937, OM with identification and a talk in Spanish.

● **MALTA**

Cologne Relay on **17825** at 1735, YL with a talk about German internal affairs in an English programme which ended at 1750.

● **NETHERLANDS ANTILLES**

Bonaire on **17810** at 1730, OM with station identification and a talk in Arabic obviously for the Arabian areas.

● **AUSTRALIA**

Melbourne on **21630** at 1858, OM with station identification, announcements, time-check for 1900 GMT then some local news followed by news of events in the Pacific area.

Melbourne on **21680** at 0801, OM with a newscast in English which was also logged soon after on **21570** in parallel. The latter channel provided the best reception conditions here in the U.K.

Melbourne on **21890** at 0405, OM with a newscast of world events, followed by the local news read by a YL announcer – all in English.

● **TURKEY**

Ankara on **9515** at 1646, OM with the local news – many place-names mentioned – then YL with songs, all in the Turkish Service for those overseas.

● **AFGHANISTAN**

Kabul on **15075** at 1709, YL and OM in Arabic until several station identifications were made at the commencement of the German programme at 1830.

● **ECUADOR**

HCJB Quito on **15250** at 0430, OM with the station identification in English in a programme obviously directed to North America – judging from the announcements.

● **EAST GERMANY**

Radio Berlin International on **6040** at 0500, OM with the station identification and announcements with programme details at the commencement of a Spanish programme.

● **VATICAN**

Vatican City on **11700** at 2050, YL with the English programme all about the Greek and Roman gods of classical times, followed by details of other programmes for Africa.

● **BRAZIL**

Radio Nacional Brasil, Brasilia, on **15445**, at 1904, OM and YL announcers in Portuguese in a programme for internal consumption.

Radio Nacional Brasil, Boa Vista, on **4835** at 0208, OM with pops in Portuguese, OM announcer. The schedule is from 0900 to 0400 and the power is 10kW.

Radio Cultura do Para, Belem, on **5045** at 0243, OM announcer in Portuguese, followed by a programme of light orchestral music – quite a change from the eternal pops or LA (Latin American) music! The schedule here is from 0900 to 0600 but it has been reported by some listeners closing as early as 0300 or so. The power is 10kW.

● **COLOMBIA**

Radio Colosal, Neiva, on **4945** at 0237, OM announcer with some of the local pops on records. This one has a 24-hour schedule and it is one of the easiest Colombian stations to receive here in the U.K. The power is 2.5kW.

● **VENEZUELA**

Radio Mundial Bolivar, Bolivar, on **4770** at 0159, OM songs in Spanish, full identification at 0200. The schedule is from 1000 to 0400 and the power is 1kW.

Radio Lara, Barquisimeto, on **4800** at 0203, YL's in chorus with local ballads, piano solo. The schedule here is from 1000 to 0400 and the power is 10kW.

Radio Universo, Barquisimeto, on **4880** at 0220, YL with local pop song, OM with a programme of pops on records. The schedule of R. Universo is from 1000 to 0400 and the power is 10kW.

Radio Juventud, Barquisimeto, on **4900** at 0227, OM announcer with the inevitable local pops. The schedule is from 1000 to 0400 and the power is 10kW.

● **PERU**

Radio Loreto, Iquitos, on **5050** at 0248, OM with a sports commentary in Spanish – all very excitable stuff, complete with many trilled R's. The schedule is from 1100 to 0650 and the power is 2kW.

Radio Atlantida, Iquitos, on **4790** at 0430, OM identification in Spanish, local-style songs and music. Quite a change from pops. The schedule is from 0900 to 0600 but sometimes transmits around the clock. The power is 1kW.

Radio Chinchaycocha, Junin, on **4860** at 0425, local songs and music, identification in Spanish at 0430. The schedule is from 1100 to 0700 but has been reported closing around 0500. Just to confuse us all, it sometimes operates a 24-hour schedule. The power is 0.5kW.

● **MAURITANIA**

Nouakchott on **4845** at 1950, OM with a newscast in French. The schedule is from 0600 to 0900 and from 1830 to 2400 (on Sundays the second session opens at 1700). The power is 100kW.

● **CAMEROON**

Radio Yaounde on **4850** at 1908, OM with a newscast in French. The schedule is from 0430 to 0800 and from 1700 to 2300. The power is 30kW.

● **EQUATORIAL GUINEA**

Radio Ecuatorial, Bata, on **5005** at 2200, station identification in Spanish, the National Anthem and off. This station now seems to be permanently on this channel – formerly on **4926**. The schedule is from 0430 to 0630, 1000 to 1600 and from 1700 to 2200. The power is 5kW and it is a much easier station to log now it is on the present channel; I hope that it is still on **5005** when this is published!

● **TOGO**

Togblekope on **5047** at 2320, local songs and music in typical style, OM announcer. The schedule is from 0530 to 0800 and from 1700 to 2400. The power is 100kW.

80 METRE AMATEUR BAND RECEIVER

By M. V. Hastings

*Expressly designed for
s.s.b. and c.w. amateur
signals.*

Minimal alignment

This easily built and fairly inexpensive receiver has been specifically designed for beginners who want to get started on amateur band reception. Unfortunately, most broadcast receivers having one or more short wave bands are not suitable for reception on any amateur bands which fall within their frequency coverage. This is because the two modes of transmission most commonly employed on the amateur bands are single sideband (s.s.b.) and morse (c.w.), neither of which can be resolved with an ordinary a.m. receiver. Communications receivers are obviously ideal for amateur bands reception but these are relatively expensive even when home-built. Quite good results can be obtained employing a much simpler receiver using the "homodyne" or "direct conversion" principle. Such a receiver is described here and it will provide reception of British and other European amateur stations, as well as reception of stations from further afield when conditions are suitable. A considerable simplification in design is given by having the receiver operate on a single band only, this being the popular 80 metre band.

In most countries, including the U.K., the 80 metre band extends from 3.5 to 3.8MHz. In the U.S.A. and a few other countries it extends from 3.5 to 4.0MHz. This set covers slightly more than the second of these two ranges whereupon little difficulty will be experienced in aligning it for the required frequency coverage. Alignment, in any case, merely consists of adjusting the cores of two coils, one to give the correct frequency coverage and the other to give maximum sensitivity over this range. No test equipment of any type is needed for the alignment. The receiver is not intended for the reception of ordinary a.m. signals.


Power is obtained from an internal 9 volt battery type PP6, and the output is suitable for high impedance magnetic headphones ($2k\Omega$ or $4k\Omega$) or a crystal earphone. An external aerial is required. However, a short indoor aerial will give reasonably good results, and an outdoor aerial is by no means essential.

DIRECT CONVERSION

An s.s.b. transmitter is basically an a.m. transmitter with the carrier and one sideband removed. If the s.s.b. signal is to be resolved the missing carrier must be re-inserted at the receiver and this and the signal passed through a suitable detector. Normally, a product detector will be used. In a superhet receiver the locally generated carrier can be inserted into the i.f. amplifier. With a receiver of the type described here, the locally generated carrier has the same frequency as would the carrier of the received signal.

The transmitted signal can be upper sideband (u.s.b.) or lower sideband (l.s.b.). If a 1kHz audio modulating tone were fed to a u.s.b. transmitter tuned to 3.6MHz, the corresponding upper sideband of 3.601MHz would be transmitted, whilst with an l.s.b. transmitter it would be the lower sideband of 3.599MHz which would be radiated. In either case the modulating tone of 1kHz can be resolved at the receiver by injecting a locally generated carrier frequency of 3.6MHz. When the 3.6MHz s.s.b. transmitter is modulated by a speech signal, the speech can similarly be resolved by injecting the local carrier of 3.6MHz. It is important, however, that the local oscillator be tuned as precisely as possible to 3.6MHz or

TEUR ER

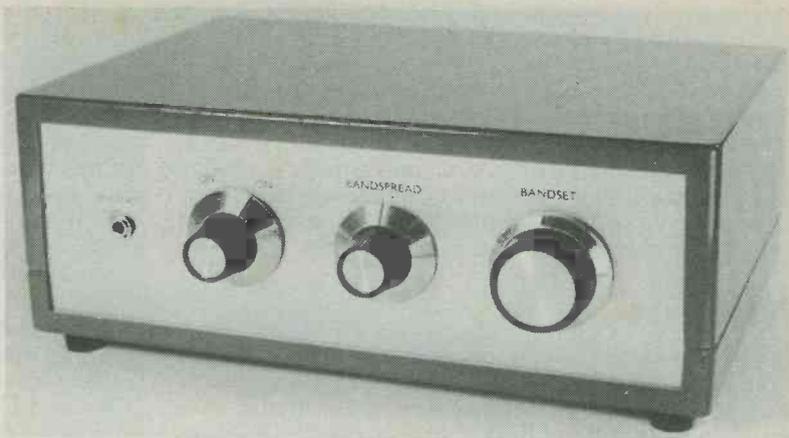

Simple homodyne design for the beginner.

nt requirements.

all the components of the speech signal will be raised or lowered in frequency. Only slight detuning can make the received speech signal difficult to comprehend.

A c.w. signal merely consists of a radio frequency signal which is keyed on and off. A local oscillator at the receiver can then be adjusted to beat with the signal and produce an audible heterodyne note. The locally generated signal used for s.s.b. reception can also be employed here, its frequency simply being adjusted to produce a comfortable tone.

The basic line-up of the receiver is shown in Fig. 1. The aerial is connected to an r.f. amplifier with a tuned output filter, the latter being set to the centre of the 80 metre amateur band. This filter stops breakthrough from signals outside the band. The r.f. amplifier output is fed to a product detector, as also is an output from a variable frequency oscillator. The v.f.o.

provides the missing carrier with s.s.b. signals or gives a heterodyne with c.w. signals. A second function of the r.f. amplifier and filter stage is to prevent signals from the v.f.o. being passed to the aerial, where they would be radiated and cause interference with other receivers.

The product detector couples into an r.f. filter which passes the detected audio signal to the a.f. amplifier whilst removing the r.f. signals present at the detector output. These r.f. signals, consisting of the received signal and the v.f.o. signal, are at a much higher frequency than the audio signal and can easily be filtered out by a single RC circuit.

The audio output from the product detector is very weak, and a considerable amount of audio amplification is required to bring it up to headphone level. The majority of the gain in the receiver is provided by the high gain a.f. amplifier which follows the r.f. filter.

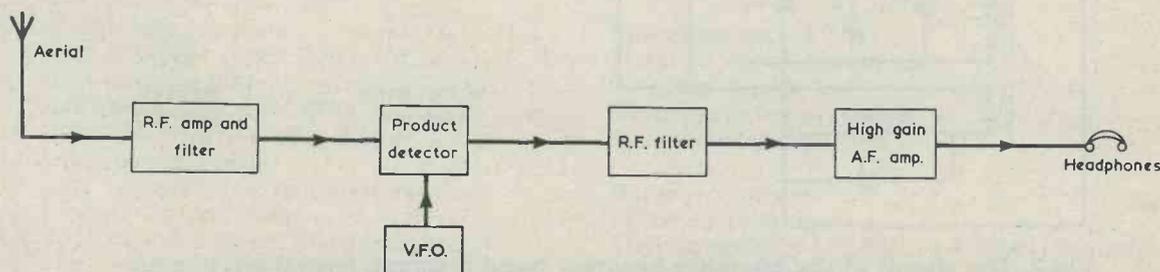


Fig. 1. Block diagram representing the stage line-up of the receiver

The receiver is tuned by adjusting the v.f.o. frequency. This selects the s.s.b. signal to be received by inserting the missing carrier. The tuning here is much more critical than is given with ordinary a.m. reception because, as was just explained, a slight inaccuracy in v.f.o. frequency can make the detected signal incomprehensible. With c.w. signals tuning is similar to a.m. reception, however, as it is merely necessary to set the v.f.o. to a frequency which produces an acceptable heterodyne note.

THE CIRCUIT

The full circuit of the receiver is shown in Fig.2. TR1 is the r.f. amplifier and is used in the common emitter mode with an untuned base input circuit. Two aerial sockets, SK1 and SK2 are provided. SK2 couples direct to TR1 base and is used with short indoor aerials. SK1 couples to the base via trimmer TC1 and is employed with longer and more efficient aerials, which could cause the r.f. amplifier to be overloaded by strong signals if the aerial were connected direct to the transistor base. TC1 is adjusted to suit the particular aerial used.

The collector of TR1 connects to a coupling winding of coil L1. The winding between pins 1 and 6 is tuned by C2, and the core of the coil is adjusted so that this tuned circuit is resonant at the centre of the 80 metre amateur band. A second coupling winding on the coil connects to the product detector, consisting of D1, D2 and R2. The v.f.o. signal is introduced, via capacitor C3, at the junction of the two diodes. R2 is adjusted to minimise breakthrough of out-of-band signals.

The variable frequency oscillator is provided by the circuitry around TR4. This is a Jfet device used in the source follower mode. The gain from gate to source is somewhat less than unity, but there is a voltage step-up from the source coupling winding to the tuned winding of L2., which ensures that there is sufficient positive feedback to produce strong and reliable oscillation. Tuning is controlled by VC1 and VC2. VC1 is the bandset capacitor and VC2 the bandspread capacitor. Because of its low value and the fact that C11 is in series with it, VC2 can tune over only a small part of the band, but fine tuning is much easier to carry out with this capacitor. The oscillator signal is taken from TR4 source and passes to the product detector through C3.

R4 and C4 constitute the low pass r.f. filter which follows the product detector, and the remaining audio signal is coupled via C5 to the high gain low noise a.f. amplifier given by TR2 and TR3. These are both employed in the conventional common emitter configuration. C6 and C8 provide negative feedback of the higher audio frequencies, and thus roll off the high frequency response of the receiver. This is beneficial as it gives an improved signal-to-noise ratio and decreases adjacent channel interference. A good audio frequency response is of no benefit at all in a receiver of this nature since s.s.b. amateur transmitters normally incorporate filtering which limits the audio frequencies to a range suitable for good communications quality speech, with frequencies above 3kHz being virtually eliminated. C9 couples the output of the amplifier to SK4, the phones socket.

On-off switching is provided by S1, and C1, R3 and C10 are the only supply decoupling components


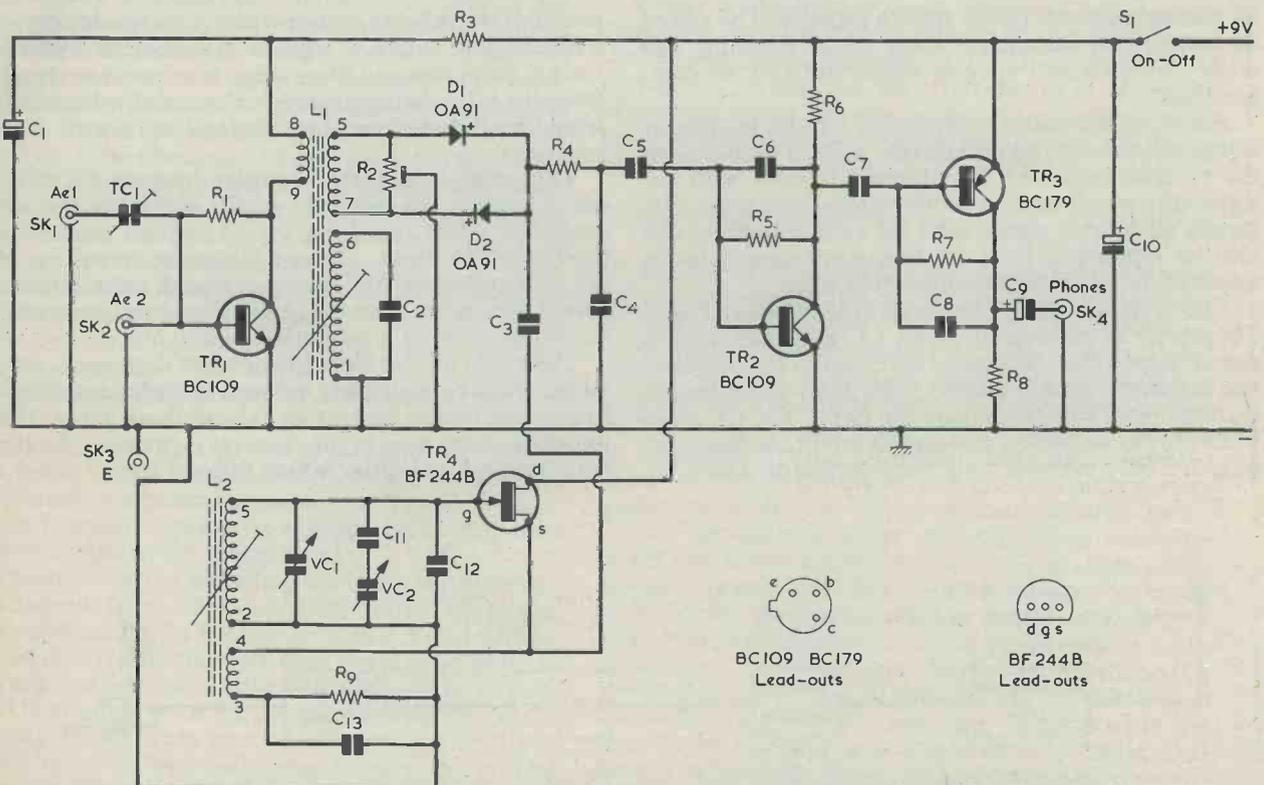


Fig.2. The circuit of the 80 metre amateur band receiver. Reception of s.s.b. signals is achieved by "direct conversion" with the output of oscillator TR4 inserting the missing carrier at the product detector stage

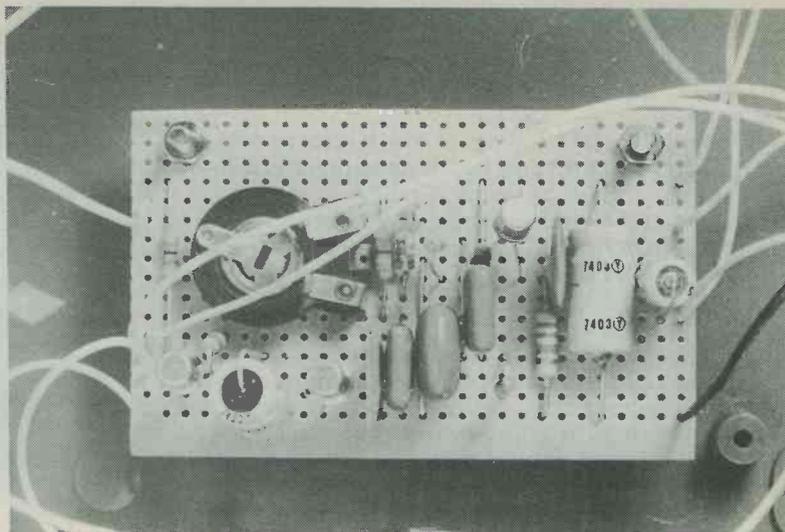The components on the veroboard panel. This takes transistors TR1, TR2 and TR3 and their immediate components



which are required. Current consumption from the 9 volt battery is approximately 7mA only.

A few notes need to be made concerning components. SK4 should be a 3.5mm. jack socket of open construction, i.e. it should not have an insulated body. This is because a chassis connection to the front panel of the receiver is made by way of its mounting bush and nut. If difficulty is experienced in finding a source for the coil specified for L2, this may be obtained (as may also L1) direct from the manufacturer at Denco

(Clacton) Limited, 355-7-9 Old Road, Clacton-on-Sea, Essex, CO15 3RH. The coil has a third winding, incidentally, which connects between pins 8 and 9. This winding has no effect on circuit operation and is not shown in Fig.2.

Trimmer TC1 can be any small trimming capacitor having a maximum value of about 20pF. The BF244B specified for TR4 is available from a number of suppliers, including Greenweld, 443 Millbrook Road, Southampton, S01 OHX.

COMPONENTS

Resistors

(All fixed values $\frac{1}{4}$ watt 5% unless otherwise stated)

- R1 1M Ω
- R2 470 Ω pre-set potentiometer, 0.25 watt, horizontal
- R3 470 Ω
- R4 3.9k Ω
- R5 1.8M Ω 10%
- R6 4.7k Ω
- R7 1.2M Ω 10%
- R8 2.2k Ω
- R9 3.3k Ω

Capacitors

- C1 100 μ F electrolytic 10V Wkg.
- C2 56pF ceramic plate or polystyrene
- C3 27pF ceramic plate
- C4 0.01 μ F polyester type C280
- C5 0.1 μ F polyester type C280
- C6 1,000pF ceramic plate
- C7 0.1 μ F polyester type C280
- C8 390pF ceramic plate
- C9 10 μ F electrolytic, 10V Wkg.
- C10 100 μ F electrolytic, 10V Wkg.
- C11 3.9pF ceramic plate
- C12 22pF ceramic plate or polystyrene
- C13 4,700pF ceramic plate
- VC1 25pF variable type C804 (Jackson)
- VC2 10pF variable type C804 (Jackson)
- TC1 20pF trimmer (see text)

Coils

- L1 Dual purpose, coil, transistor usage, Blue, Range 3T (Denco)
- L2 Dual purpose coil, valve usage, Green, Range 3 (Denco)

Semiconductors

- TR1 BC109
- TR2 BC109
- TR3 BC179
- TR4 BF244B
- D1 OA91
- D2 OA91

Switch

- S1 s.p.s.t. toggle, rotary

Sockets

- SK1 insulated socket, red
- SK2 insulated socket, red
- SK3 insulated socket, black
- SK4 3.5mm. jack socket

Miscellaneous

- Verocase type 75-1411-D
- 3 control knobs
- Veroboard, 0.1 in. matrix
- 9-volt battery type PP6

Battery connector

- 2B9A valveholders
- High impedance (2,000 Ω or 4,000 Ω) headphones or crystal earphone with 3.5mm. jack plug
- Wire, solder, etc.


CONSTRUCTION

A Verocase type 75-1411-D with dimensions of 205 by 140 by 75mm. makes an excellent housing for the receiver.

This has a metal front panel which screens some of the circuitry and prevents hand capacitance effects on the tuning.

The general layout of the set can be seen from the photographs. On the front panel, from left to right, are SK4, S1 VC2 and VC1. On the rear panel are mounted L1, L2, the two aerial sockets and the earth socket. Looking at the receiver from the front, L1 is to the left, with SK2 next to it, followed by SK1, SK3 and, at the right, L2. Each of these coils requires a $\frac{1}{4}$ in. mounting hole and is held in place by a plastic nut provided with it. It is important that these nuts be tightened by hand only as excessive force here could easily strip the plastic thread on the nut or the former. Soldered connections can be made directly to the pins of the two coils, but these are held in plastic which melts readily when heated. In consequence, a B9A valveholder is passed onto the pins of each coil and connections are made to the valveholder tags.

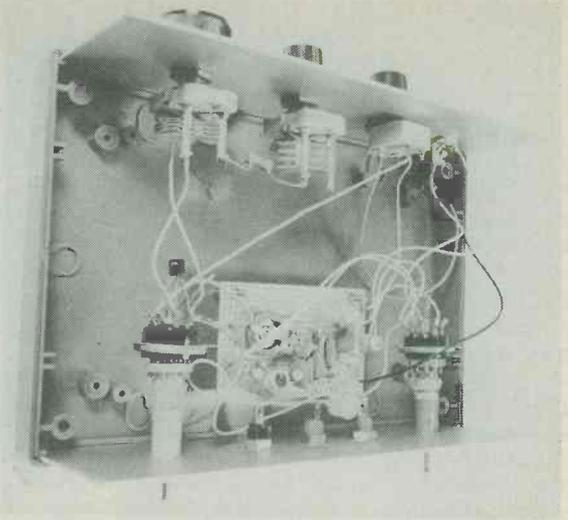A Veroboard panel of 0.1in. matrix having 28 holes by 16 copper strips takes most of the components, and this is cut down from a larger panel. The Veroboard layout is shown in Fig.3. The two mount-



Looking into the receiver from the L2 end. Each of the coils has a B9A valveholder fitted over its pins, and connections are made to the valveholder tags

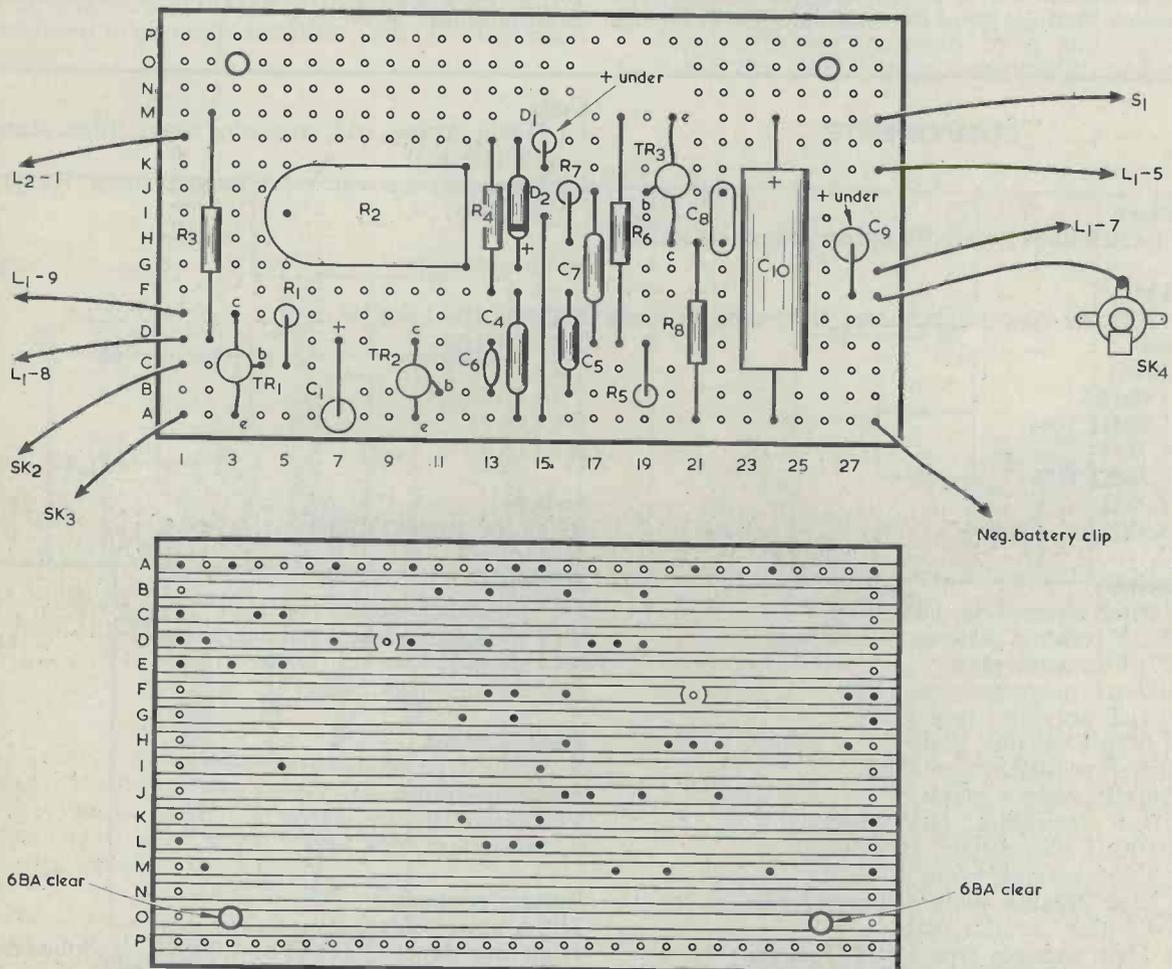


Fig.3. The component and copper sides of the Veroboard assembly. Wiring to components on the rear and front panels is also shown in Fig.4

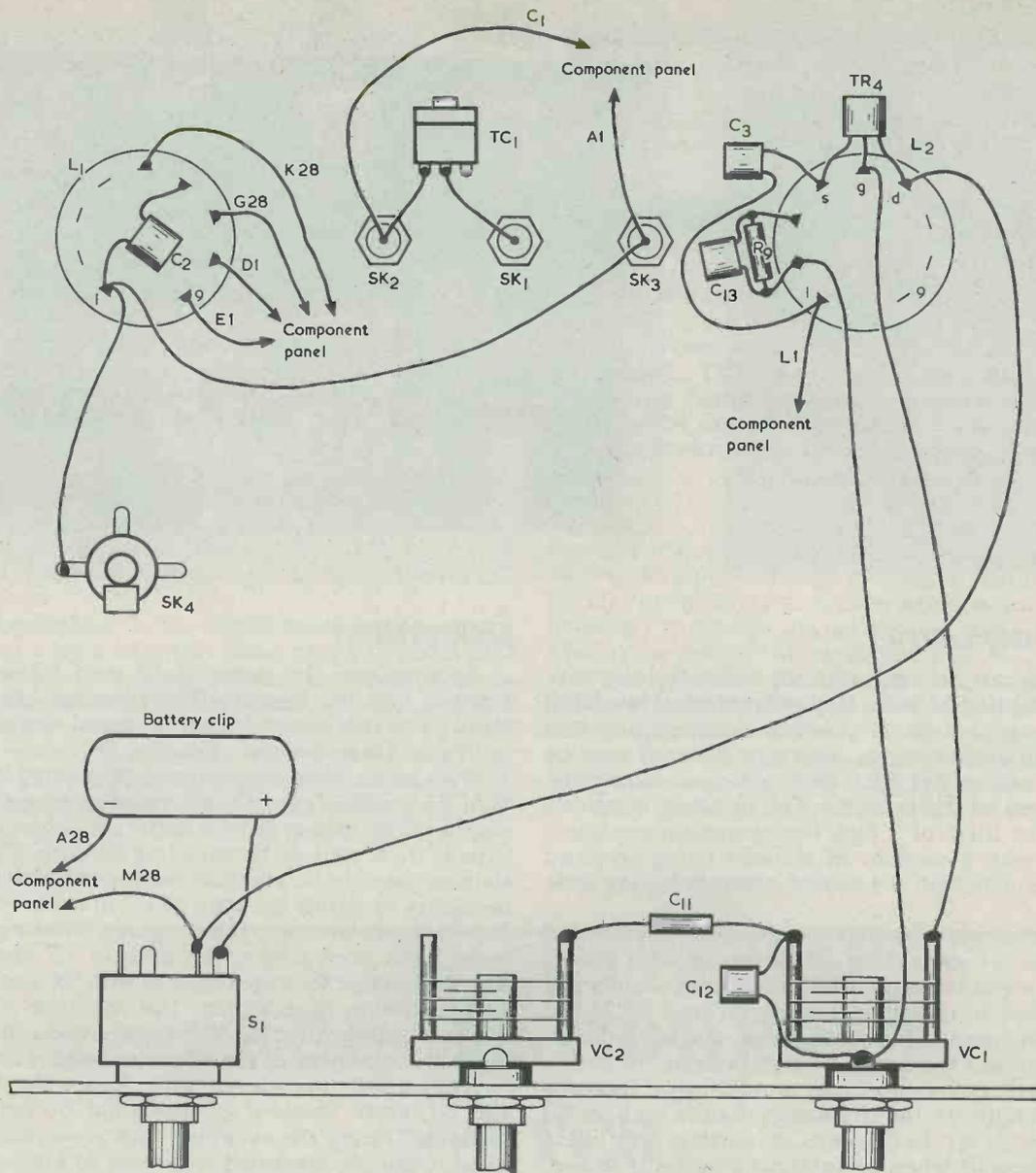



Fig.4. Point-to-point wiring. The letter and number references apply to the corresponding Veroboard holes. This diagram shows the remaining connection to SK4, shown removed from the front panel for clarity

ing holes have to be drilled out, and the two breaks made in the copper strips before soldering components to the board. Note that there is a link wire near the centre of the board. The two diodes should be the last components to be soldered to the board. The soldering of these diodes should be carried out fairly quickly as they are germanium types which can be damaged by excessive heat.

The panel is mounted on the base of the case just in front of the aerial and earth sockets. The two mounting holes are to the front. Two 6BA bolts and nuts are employed here, with spacing washers to keep the panel underside clear of the case bottom.

Before it is finally mounted in place, the Veroboard panel must be wired up to the components on the front and rear panels. The point-to-point wiring is shown in Fig.3. and 4. All the wiring should be kept reasonably short and direct. TC1 is connected directly between SK2 and SK1, being supported here by two stout pieces of tinned copper wire soldered to the socket tags. Some of the oscillator circuitry is connected to the valveholder fitted over the pins of L2. Pins 1 and 6 of this valveholder are used as anchor tags and do not connect to any coil windings. The letter and number references in Fig.4 apply to the corresponding Veroboard holes in Fig.3.

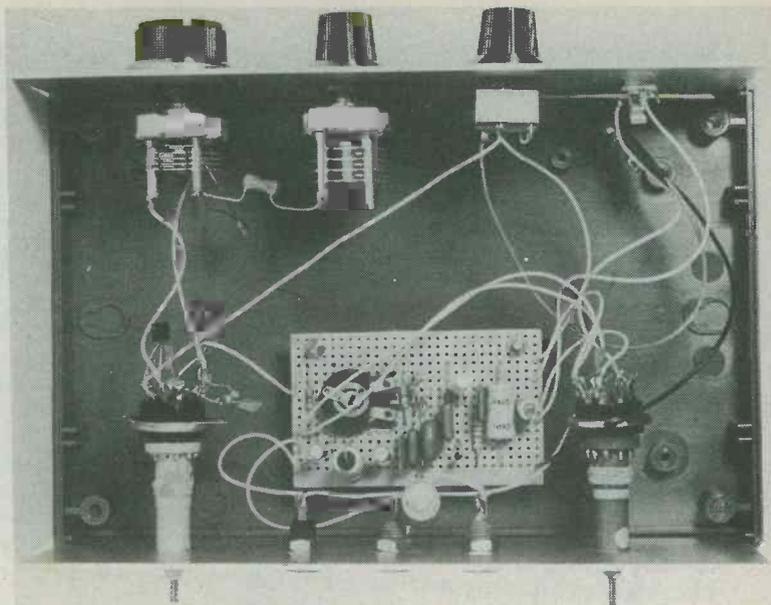Another view into the receiver interior. Transistor TR4 is mounted on the valveholder tags at L2. The battery is positioned behind S1 and SK4



AERIAL AND EARTH

The set can be used with an ordinary long wire aerial consisting of some 10 to 40 metres of insulated wire strung as high as possible between any two convenient anchor points. This type of aerial must be plugged into socket SK1 to avoid overloading the input stages of the receiver. Overloading manifests itself in the form of a high background noise level, together with a number of stations being received simultaneously with the tuning controls having little effect.

An indoor aerial will give quite good results and can consist of some 3 to 10 metres of wire strung around a room or in an attic. Satisfactory results will be obtained by plugging this aerial into SK2, but overloading may still occur at times, making it necessary to connect the aerial to SK1 instead.


An earth connection can considerably increase signal strength on low frequency bands such as 80 metres. However, in this case, an earth is only likely to be of benefit when an inefficient aerial is in use. The set does not require a very strong input signal and can be overloaded by such a signal. The best type of earth connection is provided by a metal pipe buried or pushed into moist earth, with a lead which is as short as possible connecting it to the receiver.

ADJUSTMENT


As supplied, the cores of L1 and L2 are fully screwed into the formers. The cores should be unscrewed so that about 10mm. of metal screw thread protrudes from the end of each coil.

With an aerial and headphones connected it should then be possible to tune in a number of stations of some kind by means of VC1 and it should be possible to peak these stations by adjusting the core of L1. The stations may not be amateur ones, and it will then be necessary to adjust the core of L2 in order to locate the 80 metre amateur band signals. When some of these have been found, the core of L2 should be adjusted so that they are tuned in with VC1 at around half maximum capacitance. The coverage provided by VC1 should then be sufficiently wide to ensure that all or nearly all of the 80 metre band is covered.


After a little experience with the set the limits of the 80 metre amateur band should become fairly obvious. During the evenings, and at weekends, the band is usually crammed from end to end with stations, and the band limits can then be located quite easily. If necessary, the core of L2 can be given a final slight adjustment to centralise the band in the range covered by VC1. VC1 is then adjusted to the centre of the band and the core of L1 finally adjusted for max-

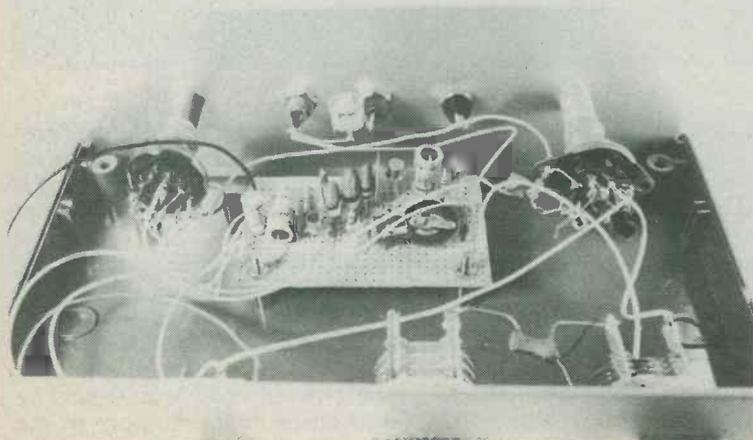

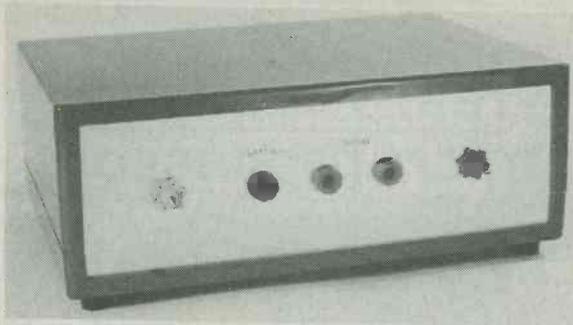The rear panel wiring. Trimmer TC1 is wired between sockets SK1 and SK2



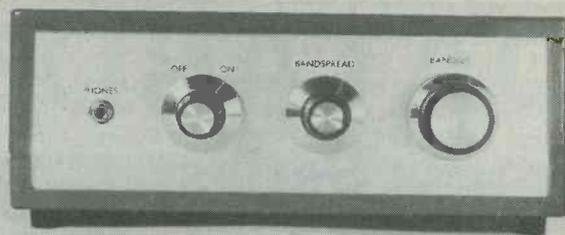The coils and aerial and earth sockets are assembled on the rear panel. The coils are held in position by plastic nuts which are supplied with them, and care must be taken not to overtighten these nuts



On the front panel socket SK4 is to the left with the on-off switch next to it, followed by VC2. VC1 is to the extreme right. The panel legends are taken from Panel-Signs Set No. 4. It will be found convenient to fit VC1 with a larger knob than is employed with the other two controls

imum sensitivity. The bandwidth of the L1 tuned circuit is wide enough to give good sensitivity over the entire band.

During daylight hours the 80 metre band provides reception over a relatively short range of about 200 miles, but after darkness has fallen the range becomes very much greater and quite distant stations can often be received.

Two remaining adjustments concern R2 and TC1. The set will work perfectly well with R2 at any setting. It may occasionally be found that strong broadcast signals or possibly other transmissions are breaking

through whereupon R2 should be adjusted in an attempt to null the interfering signal. Adjustment of R2 may not always remove the signal, whereupon it is necessary to change the aerial input to SK1 if it is at SK2, or to reduce the capacitance of TC1.

When only a modest outside aerial is being used, TC1 will probably give best results when set for maximum capacitance. However, with longer aerials the set may be overloaded unless the capacitance of TC1 is reduced somewhat. This is really a matter of finding a setting which gives good sensitivity without overloading problems. ■


BCD ENCODER SWITCH

A miniature 10-position rotary switch, introduced by Impectron Limited, has five connection pins and produces a binary-coded decimal output (i.e. a four digit binary group representing decimal 0 to 9) at each position. One signal pin is for voltage supply whilst the others represent decimal 1, 2, 4 and 8. No contacts are made on position "0" but as the switch is taken through the remaining 9 positions the four output pins present the number of the position selected in BCD form.

Known as the type BCM23, and measuring only 23 by 23 by 19mm. overall (excluding mounting pins and spindle), the switch will enable designers of mechanical-electrical interfaces to fit a low cost encoder into tight corners. The device will prove particularly useful where manual controls or mechanical assemblies have to be interfaced to electronic logic such as microprocessor circuits.

There are two fixing tabs for mounting to printed circuit boards and also a threaded spindle and nut for front panel mounting. Power rating is 3 watts maximum, with maximum voltage and current ratings of 200 volts and 500mA. The manufacturers are Impec-

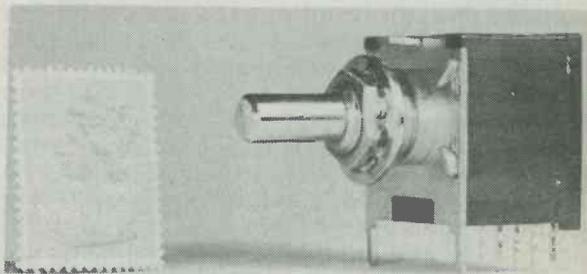tron Limited, Foundry Lane, Horsham, W. Sussex, RH13 5PX.



The Impectron type BCM23 10-position rotary switch. This offers BCD outputs for switch positions corresponding to decimal numbers from 0 to 9. The spindle may be continuously rotated whereupon the switch functions as a shaft encoder with 36 degree resolution

DATABUS

Series
No. 11

(Part 10 appeared in our May issue)

really explains
microprocessors

By Ian Sinclair

COMPUTING LANGUAGES

This concluding article examines current computing languages and ends with a glimpse into the exciting future world of microprocessors.

Whatever a microprocessor system is used for, the CPU action is always that of a number-cruncher, loading bytes of binary digits from memory and processing them. In some applications, all that the CPU ever does is to shift data bytes from one place to another; in other applications, quite extensive operations may be carried out on each byte.

MONITOR PROGRAM

Whatever the action, though, programming in binary code is never easy nor straightforward, so that the first essential for any programming that goes beyond the stage of finding out what a microprocessor can do is a monitor program in ROM. A suitable monitor program (and it must be one which suits the CPU exactly – you can't use a 6502 monitor to run a Z80) will enable addresses and data bytes to be entered in hex or octal form rather than in binary, and will allow the data byte in each memory location to be displayed when the memory address is keyed. All of this *can* be carried out by hardware, but if you have ROM in your microprocessor system it makes sense to program it so as to do this work, thus making the hardware simpler. Many monitor programs (or BUGS) do considerably more than these simple requirements, of course, but these are essentials.

Development systems, such as the MK14, the KIM 1, and others consist of the CPU with monitor ROM, RAM for your own programs, and I/O ports coupled to a keyboard and a hexadecimal display. Such development systems allow programs to be written in hexadecimal code so that

machine control, or any other programs, can be tried out in RAM, and modified until they do what is required. The program can then be transferred to a PROM (using a PROM programmer circuit), written out in hex form, stored on tape or otherwise recorded for later use.

These development systems are excellent educational tools. Even if they taught nothing else they would certainly teach you how much programming is needed for even the simplest operations. For professional use, however, the time that is needed makes it necessary to use other methods of programming if a system is to be designed quickly. This involves the use of assembler language or of higher level languages.

An assembler is a device which "translates" letters, symbols and numbers typed on a keyboard into binary code which can be used to program the microprocessor. The important point here is "program" – lots of development units include full, alphabetical keyboards, but that doesn't mean that they can be used to write programs. An assembler allows the operator to type out the mnemonics in place of the binary codes. If this were its only task it would still be useful, because a program written out as a series of mnemonics is easier to follow and less liable to error than one written in hex or binary codes. A good assembler allows much more than this to be done, however, because several steps of machine code can be generated by one assembler statement, and much of the tedious work of hex or binary coding can be carried out more easily.

HIGHER LANGUAGES

This is one step towards the use of higher computing languages. The ideal computing language would be "normal" English, so that a description of what the program is to do could be typed on a keyboard, and thus automatically translated into a program. The nearer the programming "language" gets to this ideal the higher its level is said to be. The use of an assembler makes it possible to substitute groups of letters and words for the binary or hex numbers which have to be used for machine-code programs, so that assembler language is a step in the right direction. The assembler may be in hardware, meaning that logic circuits exist to perform the conversion, or in software, a program which makes the microprocessor carry out its own conversions. A hardware assembler is expensive and cannot easily be modified. A software assembler which might be a magnetic tape of a program written out to be placed in RAM by the user, is more adaptable, but is going to use up valuable memory space. An assembler program could very well use up so much of the precious RAM of a small microprocessor system that there would be no memory left for the user to write programs. A third option is the "firmware" one, which uses the assembler program on a ROM or PROM chip; this is the most usual form of assembler.

A variation of assembler that few of us are likely to encounter is the "cross-assembler". A cross-assembler allows a program written for an existing (large) computer to be translated into machine language for a micro. This is a very attractive proposition for the professional engineer who has access to a main-frame or mini computer. The programs can be written and tested on the large computer, then translated by the cross-assembler, loaded into the microprocessor and tested again. There is an impressive saving of time by using this method, but you need a few tens of thousands of pounds invested in a computer and again in a cross-assembler.

The next step to a genuine high level language is a compiler, which allows the use of one of the genuine higher level computing languages, such as FORTRAN, ALGOL or COBOL. These lan-

guages are as close to English as any computing language gets at the moment, are internationally understood, and are standard on large main-frame computers. When we use one of these languages with a compiler, we can say goodbye to all the tedious business of calculating relative displacements for memory addresses, because the compiler does this automatically; some assemblers will also do this. Readers who have followed the "Tune-In To Programs" series in this journal will appreciate that the TI-57 programmable calculator uses a simple form of compiling, since no displacements have to be calculated to label a memory point - if we could just marry a TI-57 or a CBM P50 to a microprocessor, we would have a computer worth writing home about.

The use of a compiler allows any programmer to use a computer; whereas the use of machine code is possible only if the workings of the CPU, and also its circuit arrangement (the hardware), are well understood by the programmer. Once again, though, a compiler takes up a lot of memory space, so much that a FORTRAN compiler is of little use in a computer with less than 2^{14} bytes of memory - this is 16,384 bytes, often referred to as 16K bytes.

BASIC AND PASCAL

High level languages such as FORTRAN, ALGOL, and COBOL are seldom used for computer systems which are built around microprocessors. A compromise between assembler language and a genuine higher-level language is probably the best bet for small computer systems, and two such languages are BASIC and PASCAL. BASIC is the language which has been used in most of the first generation of home computers; the letters stand for Beginners' All-purpose Symbolic Instruction Code, but it exists in a wide variety of shapes and sizes, so that the BASIC which is used on one computer may not completely suit another; we also have size variations such as Tiny BASIC, Extended BASIC, and so on. PASCAL is a language which has not yet appeared on any machine offered in this country, but which may appear in the future when the competition hots up a bit. At the time of writing, the announcement that the first home computers

The Tandy TRS-80 Model I Microcomputer System. Shown in the photograph are a 12in. video monitor, keyboard, battery/a.c. cassette recorder and the User's Manual for Level I. The Manual is intended for the novice, and its 232 pages explain the capabilities of the computer



The Model II TRS-80 System. Particular attention has been paid to making the keyboard as simple as possible, with as few "special" keys as are necessary. As with the Model I the Model II is fully expandable. Further details can be obtained from Tandy Corporation (Branch UK), Bilston Road, Holyhead Road, Wednesbury, Staffordshire



from Hong Kong are coming out of the factories has led to some sudden price-cuts, and those who bought the larger kits are seeing a hundred pounds or so being clipped off the prices they have just paid. At first sight, it all looks like the sort of thing which happened with pocket calculators – if you want a calculator keyboard, it's now cheaper to buy a £3.99 calculator from Woolies than it is to try to buy the bits.

Remember, though, that items such as QUERTY (typewriter style) keyboards, printers, video displays and cassette mechanisms can never reach the same low prices as i.c.'s so that there must be a lower level to the prices which can be reached, and it doesn't pay to wait too long if you genuinely have a need for a computer.

At the moment, BASIC is the main language for these machines, and is well worth learning before your sons and daughters start to teach it to you. Like all computing languages, though, BASIC is best learned on an actual computer, so that you can find out at once if you've made a mistake. Readers who have followed the "Tune-In" series will know what I mean. If you're tempted to take evening classes in BASIC, make sure that the college or school which offers the course has a computer, and not just a terminal or a card punch. One of the quickest ways of being turned off programming is to fill in a program on punched cards this week and to find next week that there was a fault in it, and that it can't be run again for yet another week. The ideal arrangement is to have one micro-computer (PET or similar) for each two or three learners, so that you can program and run, then retire to find out what went wrong.

THE FUTURE

What of the future? Well, the sixteen-bit microprocessor is already with us, and every major CPU manufacturer has announced his own version of this particular beast. At the moment prices are high, waiting times are long, and few of us have had a chance to see one, let alone play with one. In fact, at the time of writing, there is a scarcity of all the chips associated with microproces-

sors, caused by the rush of everyone eager to update to this comparatively new technology. We needn't wait for the sixteen-bit machines – the difference is in speed of operation, which is the least important of factors for the amateur user. In any case, anyone who has mastered 8-bit machines will have no trouble adapting to a sixteen-bitter from the same manufacturer, so that 8-bit micros are not going to vanish overnight; though some of the prices being asked for the more advanced 8-bit chips (like the Z-80) might drop.

The most interesting hint to the future, though, in my view is the announcement of analogue microprocessors by INTEL, followed by several other manufacturers. This isn't quite so revolutionary as it sounds – it's basically a digital microprocessor fitted with a built-in analogue-to-digital and digital-to-analogue converter system, but it could make a lot of microprocessor applications a lot easier. For example, many car manufacturers would welcome microprocessor control of carburettor and ignition to ensure that an engine always worked at maximum efficiency. The snag has always been the interface circuits – how to generate the right input signals for the microprocessor, and to make use of the digital output signals from the microprocessor. For example, inputs might include signals of engine temperature, r.p.m., load torque, air temperature, air humidity, throttle opening, and so on. To make a digital transducer for each of these quantities, so that each quantity would be converted into digital signals, would be prohibitively expensive. Even in the USA, where manufacturers are highly efficient and trim costs to the bone, the average price for each transducer would have to be around 25p to make the whole proposition worthwhile. The chances of producing digital transducers at this sort of price, even in the 20-million batches which would be needed, looks a bit remote.

Continued on Page 681

GENERAL PURPOSE 8 WATT AMPLIFIER


Part 2

by A.P. ROBERTS

Final steps in constructing this versatile design.

MAIN P.C.B.

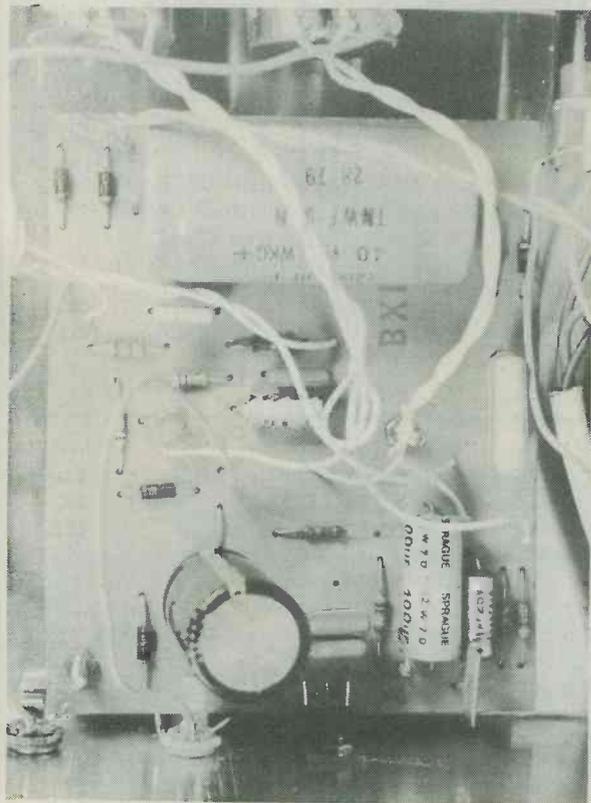A single circuit board is used to accommodate the components associated with the power amplifier section and the power supply rectifying circuit, and this is reproduced actual size in Fig.4. The board is etched, drilled and completed in the conventional manner.



A closer look at the power amplifier section board

The lead-outs of IC1 are bent at right angles so that its heat tab surface is just very slightly outside the board edge at which it is mounted. This enables the heat tab to be bolted to the rear panel of the case whilst the board is mounted horizontally to the bottom of the case. After the board has been completed and the components fitted, it is used to mark out the hole for IC1 heat tab and the two mounting holes in the case bottom. The board should be just to the right of T1. It will be mounted with short metal spacing washers on the two 6BA bolts so that the board underside is well clear of the metal bottom of the case. The board takes up its chassis connection by way of one of the spacing washers as well as via the heat tab of IC1. Socket SK3 obtains its chassis connection by way of its own mounting bush and nut.

Before finally mounting the board in position, the connections to the external components must be made. These are illustrated in Fig.5. The lead from the board taking the positive supply to the pre-amplifier board can, at this stage be about 6in. long. It will be connected, shortened as necessary, to the pre-amplifier board after the latter has been completed and made ready for mounting. The pre-amplifier board, incidentally, measures 1½ by 2 5/8in. The lead from VR1 to the pre-amplifier board will also be fitted later. Note that all the signal-carrying leads in the amplifier can be unscreened, as the metal case provides all the screening required. It is desirable, however, to keep the output lead to SK3 reasonably well spaced from the input leads to SK1 and SK2 when these leads are later fitted.

The mains lead should be clamped inside the case. The earth wire connects to the solder tag under the securing nut for T1, whilst the live and neutral wires connect to the on-off switch tags. If the mains transformer has tags at the top which could be fairly close to the inside surface of the lid when the latter is fitted, secure a piece of thin s.r.b.p. sheet to the lid on the area over which the transformer tags appear. The s.r.b.p. should be held in place with a strong adhesive such as an epoxy resin.

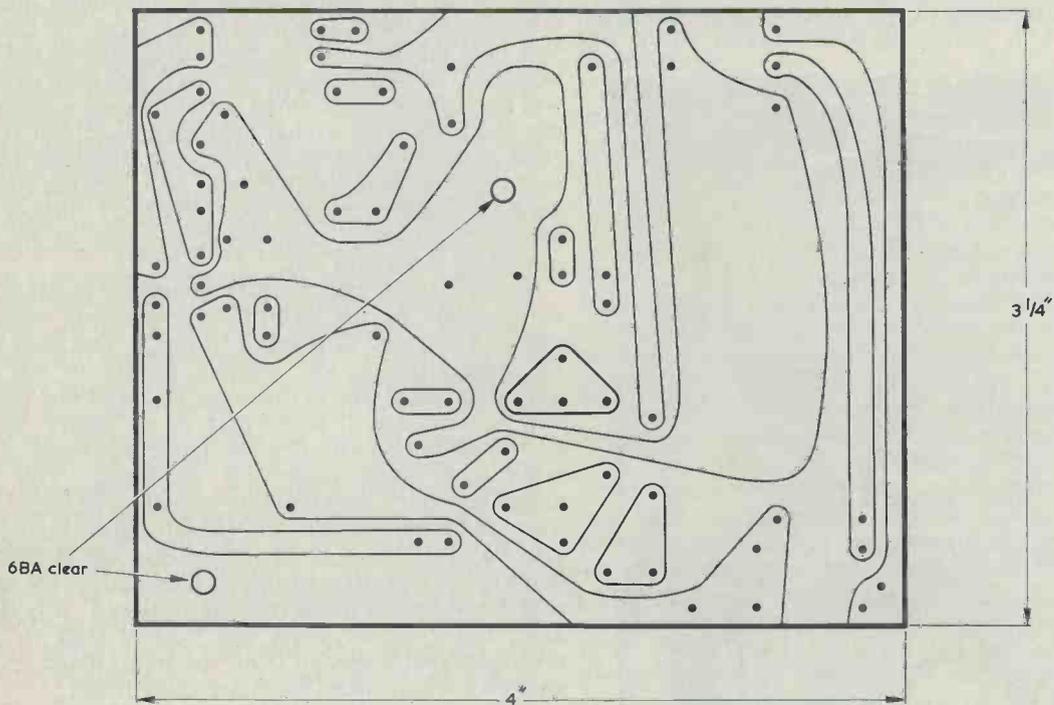
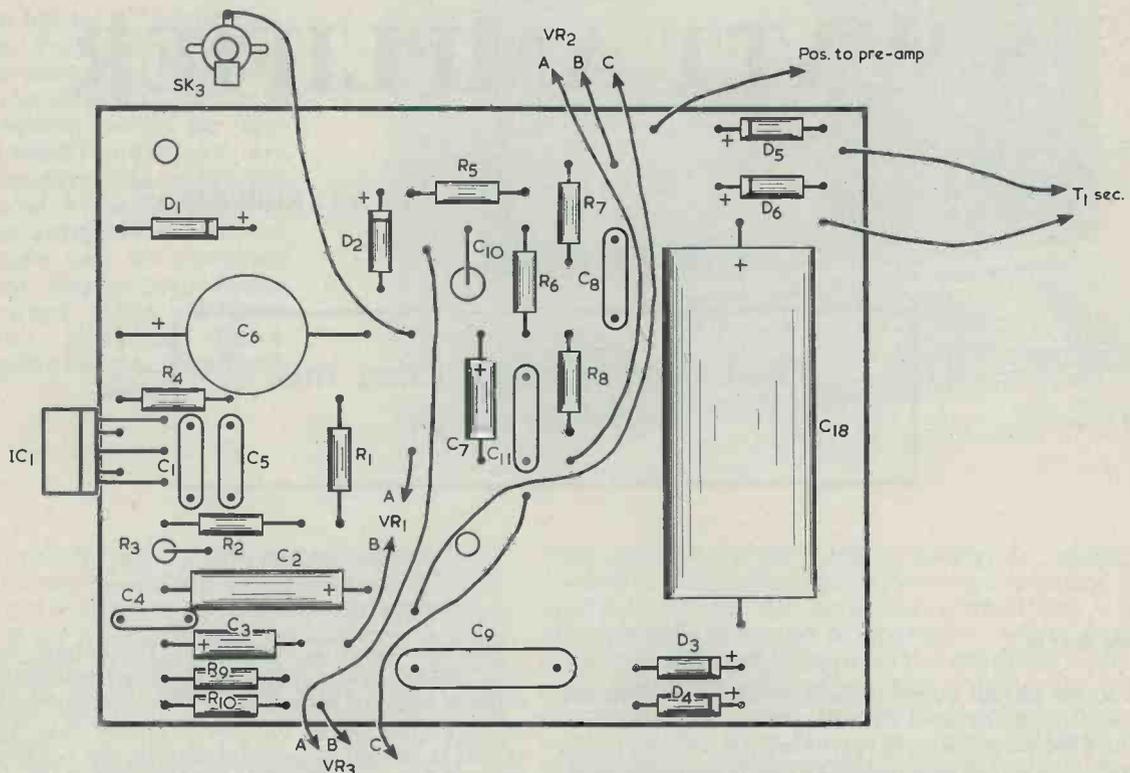


Fig.4. The power amplifier and supply rectifier circuitry is assembled on a printed board, reproduced here full size. See the text for details of the mounting of IC1

The wiring around the mains transformer and the on-off switch


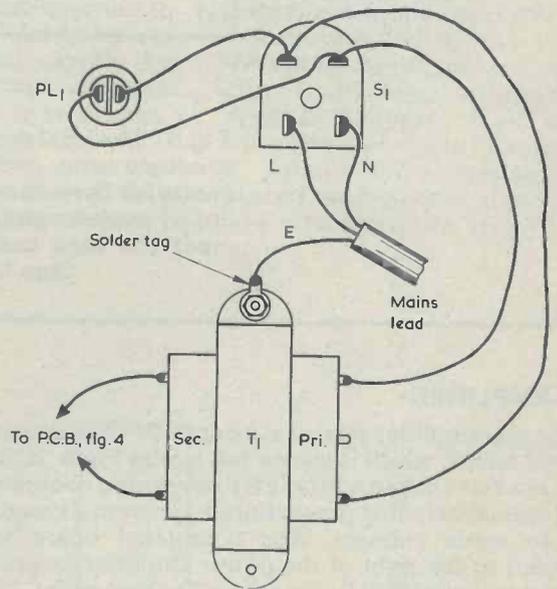
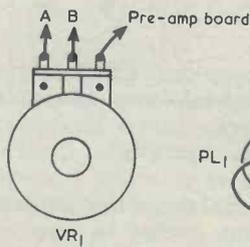
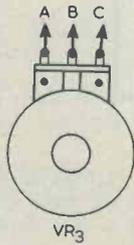
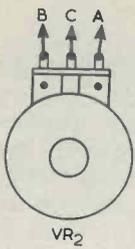
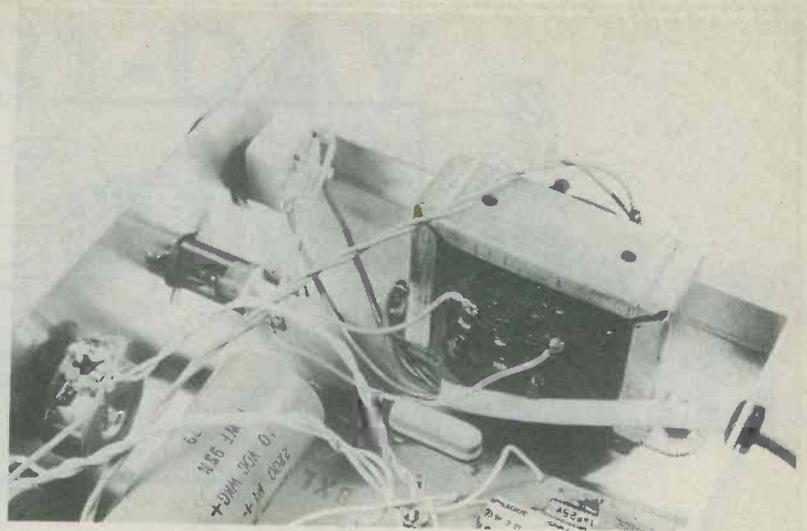


Fig.5. Wiring external to the board of Fig.4. Note that the connections to VR2 are in the order B, C, A

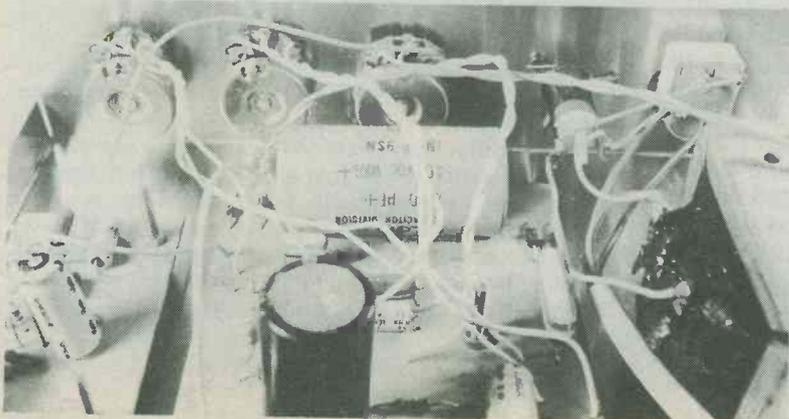

Looking at the front panel wiring from the rear

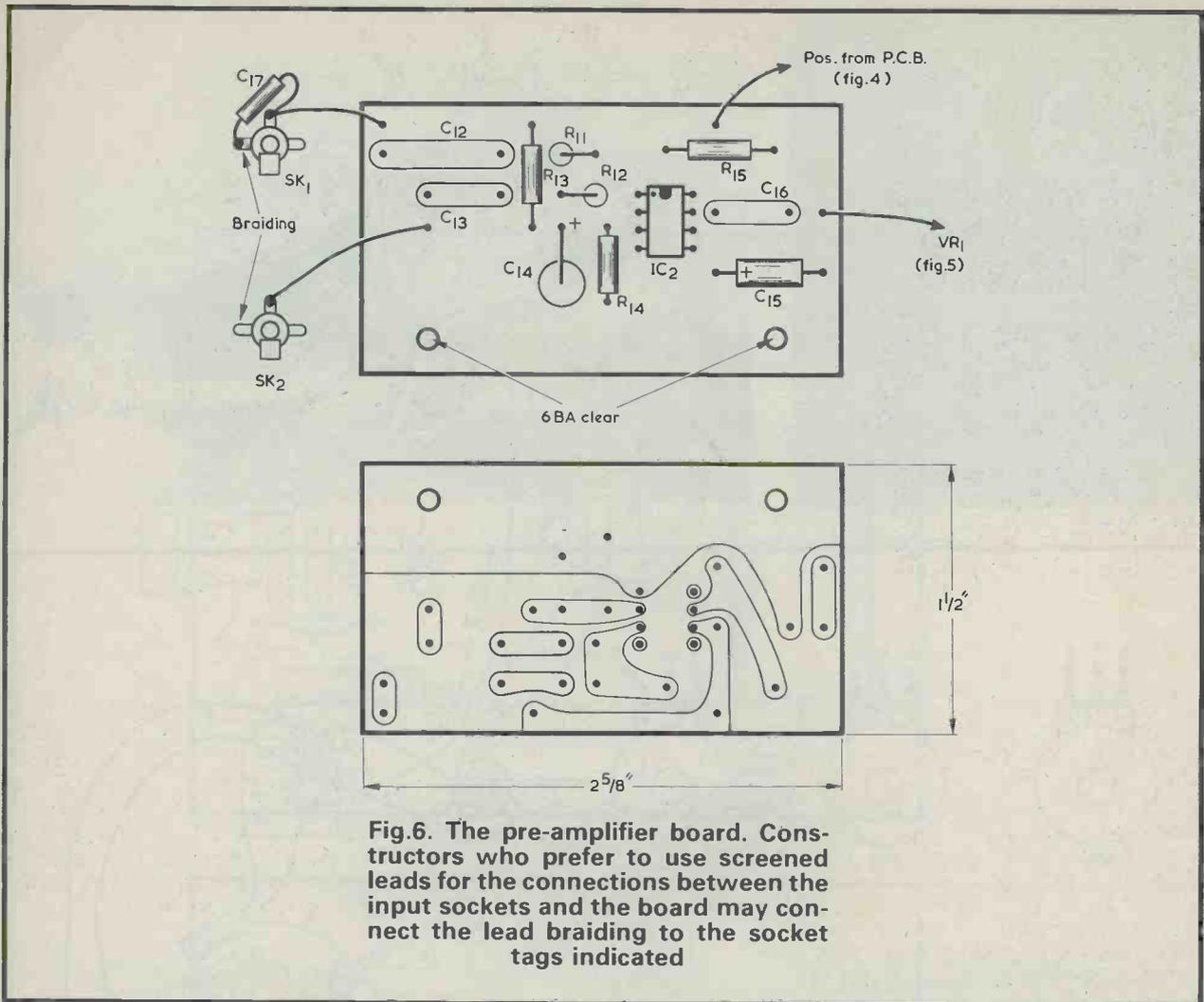


Fig.6. The pre-amplifier board. Constructors who prefer to use screened leads for the connections between the input sockets and the board may connect the lead braiding to the socket tags indicated

PRE-AMPLIFIER

The pre-amplifier section is assembled on a second printed board, which is shown full size in Fig.6. IC2, here, is a Jfet and not a MOSFET device and does not need special handling precautions to prevent damage due to static voltages. The completed board is mounted to the right of the power amplifier section and is positioned well to the rear of the case with C15 and C16 nearer the front, so that the input leads to SK1 and SK2 are kept short. As was stated last month, these two wires do not need to be screened. If, nevertheless, the constructor would prefer to use screened wires here, the braiding can be connected to the appropriate tags of SK1 and SK2 as indicated in Fig.6. The board is mounted by means of 6BA bolts with metal spacing washers, and picks up its chassis connection by way of these washers. It is not finally mounted until the connections to SK1, SK2, VR1 and the power amplifier section board have been completed. As will be noted, C17 is not mounted on the pre-amplifier board but is connected across the tags of SK1. This socket, in company with SK2, obtains its chassis connection from its own mounting bush and nut.

TESTING

Before switching on and testing the completed amplifier, give all wiring a thorough check for errors.

Since printed circuit construction is used it is unlikely that any disastrous wiring errors will occur, but it is as well to be on the safe side.

The input to the amplifier should be connected by the usual screened cable, the braiding of which connects to the "sleeve" tag of the jack plug employed. The output should be applied to a good quality 8Ω loudspeaker capable of handling the power provided and which is housed in a proper enclosure. The use of speaker impedances below 8Ω is not recommended. Speakers with impedances higher than 8Ω may be used but with an inevitable loss in maximum output power.

It is quite in order to have a switched-off item of equipment connected to one input whilst a second item of equipment is connected to the other input. This will have no adverse effect on the performance of the amplifier.

The amplifier may seem to be lacking in sensitivity when used with some items of equipment having slightly low output levels. This problem can be resolved by simply increasing the value of R15 to 1MΩ. The resultant doubling of amplifier gain will increase the r.m.s. sensitivity of Input 1 to about 12mV, and that of Input 2 to about 250mV.

(Concluded)

In your workshop-shop

31-DAY TIMING CIRCUIT

Smithy's timer runs for just over a month

"Hi-ya, Smithy!"

Smithy, standing on the Workshop doorstep, turned round in surprise.

"Don't tell me," he gasped, "that you've actually got to work *before* time. And on a Monday morning, too!"

"Come off it, Smithy," replied Dick indignantly. "When am I ever late for work?"

"Virtually every day," stated Smithy positively as he put his key in the door. "What you usually do is rush in at about five to ten minutes past nine with any possible excuse you can dream up."

"Well," said Dick, following the Serviceman into the Workshop, "I'm good and early today at any rate." He glanced at the clock on the wall. "Look, it isn't even five to nine yet. Hey, just wait a minute!"

"What's up?"

"You must have left something switched on on your bench. There's a little light glowing away over there."

LONG DISTANCE TIMER

And, indeed, a small light was plainly visible on Smithy's bench. Intrigued, Dick walked towards it, to find that the light emanated from a small l.e.d. which, with its series resistor, was coupled to a relay and a twin-cell 3 volt cycle lamp battery. The relay coil connected to a neat Veroboard assembly

which, at first sight, seemed to be bristling with Veropins. As Dick looked more closely he saw that, mounted on the Veroboard, were three diodes, two transistors, two 16 pin d.i.l. integrated circuits, an electrolytic capacitor and a few resistors. A flexible lead termi-

nated in a small crocodile clip was connected to one of the Veropins, and the crocodile clip itself was clipped to another Veropin. Two wires from the Veroboard passed to a small mains transformer placed on the other side of the board to the relay. (Fig.1.)

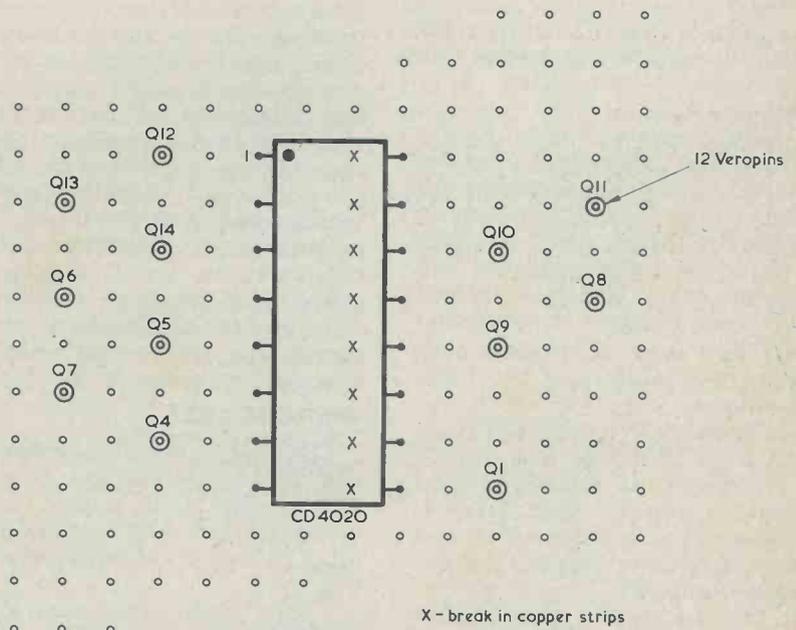


Fig.1.

The CD4020 i.c.'s employed by Smithy in his timing circuit have 12 output pins. Each i.c. is mounted on part of a Veroboard panel, as in this top view, with the outputs connected to Veropins in a staggered layout. A small crocodile clip can be clipped to any pin to select a particular output. The crosses indicate cuts in the copper strips below the board.

"Don't touch anything there," warned Smithy sharply, coming up behind Dick.

"What is it?"

"It's a little experiment in timing which I'm carrying out," stated Smithy proudly. "In a few minutes, if all goes well, that l.e.d. should extinguish. In fact, it should go out almost precisely at five minutes after nine o'clock this morning."

Dick looked incredulously at the Veroboard assembly.

"I don't believe it," he said flatly. "When did you set it up?"

"Yesterday morning," replied Smithy. "I popped in yesterday morning to start the timing run, and I did so at exactly 9.47."

"And the l.e.d. has been lit up all the time since?"

"It was lit up when I left yesterday and it was certainly still lit up when we came in just now."

Dick looked at the Workshop clock. It indicated two minutes past nine.

"Well," he stated in an unconvinced tone, "I've never heard of an electronic timer being as accurate as that over what is nearly a 24 hour period."

"We'll see," returned Smithy confidently, "what this particular timer does, anyway."

The minute hand of the Workshop clock crept past the fourth minute graduation on the clock face then moved imperceptibly until its tip started to merge with the five minute mark. The hand tip and the mark became convergent.

There was a sudden click from the relay, and the l.e.d. went out.

"Ye gods," exclaimed Dick, startled, "it did go out, too!"

"It went out exactly when I said it would," said Smithy. "Now do you believe that this timing circuit operated just as I said it would?"

The successful demonstration had changed Dick's scepticism to an attitude of intense interest.

"Yes, I'll go along with that," he replied keenly. "But how on earth do you manage to get an electronic timing circuit to be as accurate as that?"

"Simply by using a couple of

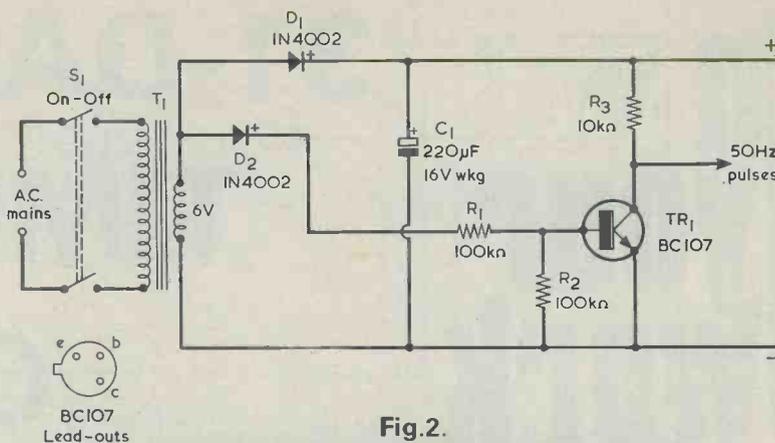


Fig. 2.

A suitable circuit for obtaining pulses at a repetition frequency of 50Hz for driving a CD4020 divider. A half-wave rectified supply is also provided.

CD4020 divide-by-two counters and driving them from the a.c. mains supply," explained Smithy. "My old colleague, G.A. French, has been playing around with CD4020's lately, and so I thought I'd get a few in for myself and see what they could do. If you've been following G. A. French's 'Suggested Circuits' you'll know that the CD4020 is a multi-stage divide-by-two device. It has one input and twelve outputs. The first output is called Q1, after which the remaining outputs are Q4 to Q14 inclusive. Each output corresponds to a division by 2 to the power of the Q number concerned. For example, the Q4 output corresponds to a division by 2 to the power of 4, or 16 times. It's when you get to the higher Q numbers that you hit the really big divisions. The Q14 output gives the biggest dividing number of the lot and it corresponds to a division by no less than 16,384 times."

MAINS PULSES

"Blimey," said Dick, impressed. "I'm beginning to see how you can get such a very long timing period. And you get the input to the circuit from the a.c. mains?"

"The input pulses are derived from the 50Hz a.c. mains," confirmed Smithy. "Which means that you can get timing periods having the same accuracy as an a.c. mains analogue or digital synchronous clock. Here's a suitable circuit for obtaining the 50Hz pulses."

Smithy reached to the back of his bench and picked up a sheaf of papers. He selected one and passed it to his assistant. Dick looked down at the circuit which had been sketched out on it by Smithy. (Fig. 2.)

"This seems pretty simple," he remarked. "For a start, you've got a mains transformer with a 6 volt secondary, and this couples to a standard half-wave rectifier circuit consisting of D1 and C1. Does that circuit power the timer?"

"It does," confirmed Smithy. "The rest of the circuit produces the pulses. When the transformer secondary voltage passed to D2 is negative of the negative rail, transistor TR1 is cut off and its collector voltage is the same as that of the positive rail. When, on the alternate half-cycle, the voltage passed to D2 starts to go positive of the negative rail, TR1 conducts as soon as that voltage overcomes the forward voltage delay in the diode and the base-emitter junction of the transistor. As the positive voltage applied to D2 increases, TR1 turns hard on and its collector voltage falls nearly to zero. The result is that there is very nearly a square wave at TR1 collector, with TR1 turned on for a slightly shorter time than it is turned off, and with a fairly rapid transition from one output voltage state to the other. This square wave is at 50Hz, and it's just the job for passing into the input pin of a CD4020."

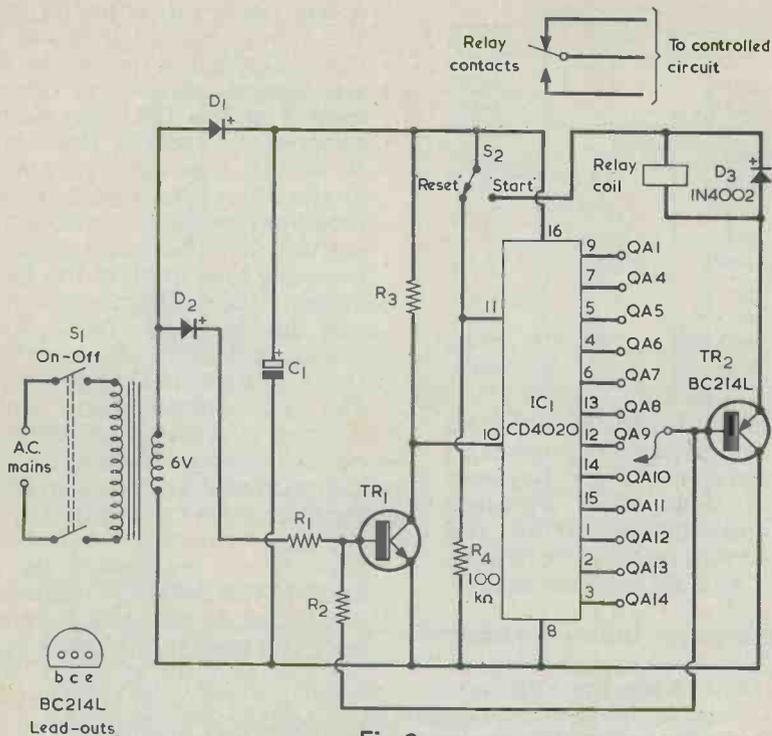


Fig.3.

The main part of the CD4020 timing circuit. The base of TR2 can be connected to any of the outputs of IC1 (although in practice the outputs below QA7 are not used). C1 and R1 to R3 have the same values as in Fig.2, but R2 is now returned to the base of TR2 instead of to the negative rail

Dick looked at the circuit a little dubiously.

"Is that diode really necessary?" he asked. "I mean the one you've marked as D2."

"It's not needed with the circuit as I've described it so far," replied Smyth. "But it serves a purpose in the complete circuit. Here's the main part of that circuit."

Smyth handed over another piece of paper to his assistant. This had a larger circuit drawn out on it, and Dick studied this with interest. (Fig.3.)

"As you can see," continued Smyth. "We've now introduced one of the two CD4020's which are used in the complete timing circuit. The 50Hz pulses are fed to pin 10, which is the input pin of the CD4020. On the right there are the twelve QA outputs, which I've labelled QA1, QA4, QA5 up to QA14."

"Why d'you put in the 'A'?"

"Because we'll be bumping into another lot of Q outputs in a few minutes, and I'll be calling these QB1, QB4, QB5 and so on. Now, pin 11 of the CD4020 is the reset pin, and when this is taken positive it

causes all the outputs to go to zero and stay there, even if there is a pulse input at pin 10. When switch S2 in the diagram is at 'Reset' it connects pin 11 to the positive rail. And when S2 is put to 'Start' pin 11 is taken negative by R4 and the i.c. starts to divide."

"Giving," queried Dick, "divided pulses at the outputs?"

"That's right," said Smyth.

"Just consider what happens at the QA1 output, which is simply a divide-by-2 output. The divider is advanced one count on each negative-going transition at the input, so let's assume for the moment that S2 is put to 'Start' at an instant immediately after the collector of TR1 goes negative. The QA1 output will then be low. Now, the length of the 50Hz cycle is 0.02 second, and so the next negative-going transition at pin 10 will be 0.02 second later. This will cause the QA1 output to go high. After another 0.02 second there will be another negative-going excursion at pin 10 and this will cause the QA1 output to go low again. So

the length of the QA1 output cycle under these conditions is 0.04 second, or twice the length of the 50Hz cycle." (Fig.4.)

"Go on," said Dick cautiously.

"So," said Smyth, "at the QA1 output we have a voltage which is low for 0.02 second after which it goes high. For timing purposes we use the first 0.02 second part of the output cycle."

RELAY TRANSISTOR

Dick frowned.

"There's something fishy here," he remarked, "but I can't quite place my finger on it!"

"Don't worry about it," advised Smyth cheerfully.

"Turn your attention next to the relay transistor, TR2. This is a p.n.p. transistor with its collector connected to the negative rail, its emitter connected to the relay coil and its base connected to a flying lead terminated in a small crocodile clip which connects to any QA output. Let's say, for the sake of explanation, that this clip is applied to the QA1 output. What happens now, when S2 is put to 'Start', is that the positive supply is applied to the relay coil. At the same time the QA1 output is low whereupon TR2, acting as an emitter follower, causes the relay to energise. This situation continues until, after 0.02 second, the QA1 output goes high. So also does the base of TR2, and the relay de-energises. But another important thing happens because, in this circuit, I haven't returned R2 to the

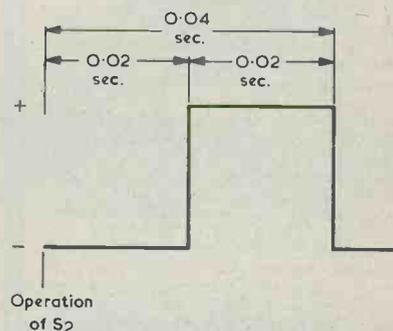


Fig.4. Theoretical consideration of the output at QA1, with the assumption that S2 is set to "Start" immediately after a negative transition at TR1 collector

GAREX

V.H.F. Receivers SR-9 for 2-metres F.M., fully tunable 144-146MHz, 2-speed slow-motion dial, also 11 xtal controlled channels. Compact, sensitive, ideal for fixed or mobile listening. Built-in L.S., 12v D.C. operation £47.15 inc. VAT. Crystals, if required: £2.60 each. All popular 2m. channels in stock. Marine band version (156 162MHz) £47.15 (xtals £2.90). Mains psu for above £11.95. Pocket VHF Receiver 12 channel xtal controlled complete with nicad and charger. 4MHz bandwidth in range 140-175MHz £57.95. Amateur and Marine xtals in stock, prices as SR-9.

Amplifier module new, fully assembled 6W IC unit, 12v D.C. Low impedance (4-8Ω) input and output for extrn. speaker amplification, with circuit £2.75. Neons min wire end 70p/10: £4.50/100

Slide switches min DPDT 20p ea; 5 plus: 16p Resistor Kits E12 series, 22Ω to 1MΩ 57 values, 5% carbon film, 1/4W or 1/2W Starter pack, 5 each, value (285) £3.10

Mixed pack, 5 each 1/4W plus 1/4W (570) £5.55 Standard pack, 10 each (570) £5.55

Grant pack, 25 each (1,425) £13.60

BNC Cable mtg socket 50Ω 25p; 5 plus: 20p;

PL259 UHF Plug and Reducer 75p; 5 plus: 67p;

SO239 UHF Socket panel mtd. 60p; 5 plus: 50p;

Nicad rechargeables physically equiv. to zinc-carbon types: AAA (016) £1.80; AA(U7) £1.30;

C(U11) £3.35; PP3 £5.55. Any 5 plus: less 10%. Any 10 plus less 20%.

We stock V.H.F. & U.H.F. mobile aerials s.a.e. details.

Access - Barclaycard

PRICES INCLUDE UK POST, PACKING & VAT

Mail order only

Sole Address

GAREX ELECTRONICS
7 NORVIC ROAD, MARSWORTH.
TRING, HERTS HP23 4LS
Cheddington (STD 0296) 668684

QA TIMING PERIODS

Output	Minutes	Seconds
QA1		0-02
QA4		0-16
QA5		0-32
QA6		0-64
QA7		1-3
QA8		2-6
QA9		5-1
QA10		10-2
QA11		20-5
QA12		41-0
QA13	1	22-0
QA14	2	44-0

Fig.5. Table showing the timing periods for the QA outputs of Fig.4. Because of their short duration and starting errors, the timing periods from QA1 to QA6 are not used

negative rail but to the base of TR2."

"What does that do?"

"When the QA1 output goes high so also does the lower end of R2. This causes TR1 to stay turned on all the time, so that its collector voltage remains low and no further 50Hz pulses are fed to the CD4020 input. In consequence, dividing stops and the circuit remains fixed in this state until S2 is put back to 'Reset'."

Dick's furrowed brow cleared momentarily.

"That does at least explain," he said, "why you put diode D2 in the circuit from the transformer secondary to TR1 base."

"It does," agreed Smithy. "The diode ensures that TR1 still remains turned on during the mains half-cycles when the upper end of the transformer secondary is negative."

"Well, that seems okay," said Dick, clearly still unhappy. "But there's something else that's bothering me."

"Yes?"

Dick concentrated.

"Ah, now I know what it is," he exclaimed suddenly. "It's the assumption you made just now when you said that S2 is put to the 'Start' position immediately after a negative-going transition at TR1 collector. But, dash it all, S2 can be put to 'Start' at any time during the cycle at TR1 collector."

"Very good," commended Smithy approvingly. "And, of course, my assumption cannot hold true in practice, although

it has helped in showing that the timing period is equal to half a CD4020 output cycle. So we cannot rely on the timing output at the QA1 pin being exactly 0.02 second. There will be similar starting errors with all the other QA outputs, but as these get higher in number the starting error becomes proportionately less until, at the QA7 output, it is negligibly low and can be ignored. Now, I've made up a table showing the QA outputs from QA1 to QA14. The QA1 output is the input divided by 2 and the QA4 output is the input divided by 16, and so the QA4 timing period is the QA1 period multiplied by 8. All the successive timing periods are multiplied by 2, ending with the QA14 output at 2 minutes 44 seconds. If I connect TR2 base to the QA14 output and put S2 to 'Start' the relay will energise and remain energised for 2 minutes and 44 seconds. After this period it will de-energise and the timing run will be over." (Fig.5.)

"That means, then," said Dick slowly, "that you can select any of the timing periods in your table simply by clipping the base of TR2 to the appropriate QA output."

"You've got it," confirmed Smithy. "In practice we wouldn't bother about the QA1 to QA6 outputs because of starting errors and also because the periods are too short for a relay operated circuit anyway."

SECOND DIVIDER


"That's definitely a neat circuit," said Dick approvingly. "But it only goes up to 2 minutes 44 seconds."

"I know," said Smithy. "And so I add another CD4020! All I do is connect its pin 10 input to the QA14 output and provide pins for all its outputs. These I have called QB1 to QB14."

Smithy selected another piece of paper and showed the circuit on it to his assistant. (Fig.6.)

"This is the final CD4020 set-up," he continued. "I've omitted the QA1 to QA6 outputs, but I've included all the QB outputs. You can now connect the base of TR2 to any QA or QB output that's available and you will get the corres-

MORSE MADE EASY

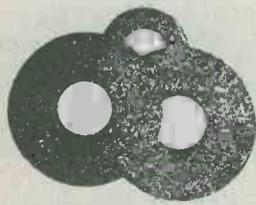

BY THE G3HSC RHYTHM METHOD!

These courses which have been sold for over 25 years, have been proven many times to be the fastest method of learning Morse. You start right away by learning the sounds of the various letters, numbers, etc., as you will in fact use them. Not a series of dots and dashes which later you will have to translate into letters and words. Using scientifically prepared 3 speed records you automatically learn to recognise the code, RHYTHM without translating. You can't help it. It's as easy as learning a tune. 18 WPM in 4 weeks guaranteed.

The Complete Course consists of three records as well as instruction books.

Complete Course £5.50 U.K. p/p 75p. (Overseas postage sufficient for 750grm). Details only s.a.e.

THE G3HSC MORSE CENTRE
S. Bennett, (Box 8), 45 Green Lane,
Purley, Surrey.

Name

Address

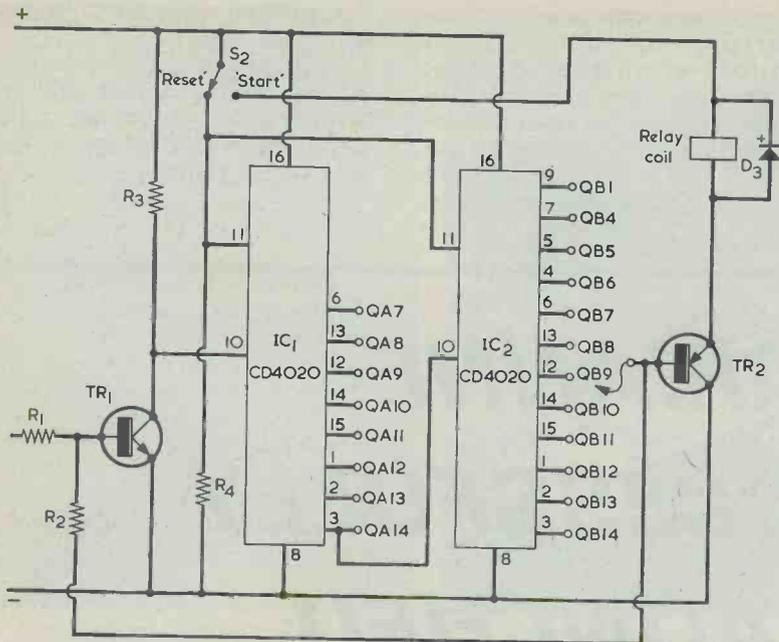


Fig.6. The final version of the circuit incorporates a second CD4020. This has its reset pin connected to the reset pin of the first CD4020. Timing periods can be selected by connecting the base of TR2 to any of the available QA or QB outputs

ponding timing period."

"With all this further division," observed Dick, "I can understand how you were able to get that timing period of nearly 24 hours we saw today. I mean the one which started yesterday morning and which ended this morning."

Smithy kept his face straight.

"And here," he said carelessly, "is a table showing the timing periods available at the QB outputs. The period I selected for today's little demonstration was the one given by the QB9 output." (Fig.7.)

QB TIMING PERIODS

Output	Days	Hours	Minutes	Seconds
QB1			5	28
QB4			43	41
QB5	1	27	23	
QB6	2	54	46	
QB7	5	49	32	
QB8	11	39	3	
QB9	23	18	6	
QB10	1	22	36	
QB11	3	21	12	
QB12	7	18	25	
QB13	15	12	50	
QB14	31	1	40	

Fig.7. The timing periods available at the QB outputs. These are corrected to the least significant figure shown

Dick took the table from the Serviceman and glanced at it. As he scanned the figures near the bottom his jaw dropped.

"What's this?" he stuttered. "31 days! You've just got to be joking, Smithy!"

"No I'm not," chuckled Smithy. "If you select the QB14 output you'll get a timing period of 31 days, 1 hour and 40 minutes. What's more, the period should be accurate to within a minute or so and, as I said at the beginning, the accuracy will be the same as is given with a synchronous mains analogue or digital clock."

"Well, stap me," spluttered Dick, "you've certainly got a real long distance timing circuit here."

"It's partly a novelty circuit," admitted Smithy, "but at the same time it can have quite serious applications because of the accuracy of the timing periods. The only snag is that there is no continuously variable control of these periods, and you have to select one of the periods which appears in the tables. But, apart from that, it's a very simple little project and is not at all expensive."

"What about components?"

"Well, the transformer can be any mains transformer having a 6 volt secondary rated at

MORSE IMPROVEMENT

C90 Cassettes (A) 1-12 w.p.m. with simple exercises. Suitable for R.A.E. preparation. (B) 12-24 w.p.m. computer produced professional level operator material including international symbols.

Price each: complete with instruction and exercise booklets £4.75 including postage. Morse Key and Buzzer Unit suitable for sending practice and DIY tape preparation.

Price £4.75 including postage

Overseas Airmail £1.50 extra.

MHEL ELECTRONICS (Dept. R)
12 Longshore Way, Milton,
Portsmouth (UK), PO4 8LS

THE MODERN BOOK CO.

Largest selection of English & American radio and technical books in the country.

19-21 PRAED STREET
LONDON W2 1NP
Tel: 01-402 9176

ELECTRONIC TUTOR KITS

Learn electronics the effective way by experiments. Each kit contains an illustrated handbook, which takes you step by step through the fundamentals of electronics, plus all the components needed. No soldering. Safe and instructive for even the young enthusiast. Kit 1, £5.85. Kit 2, £5.95. Kit 3, £6.15. SAE for leaflets on this and other RXG products.

RXG ELECTRONICS LTD.

15 Walnut Tree Crescent,

Sawbridgeworth, Herts, CM21 9EB.

PEATS for PARTS

ELECTRONIC COMPONENTS RADIO & TELEVISION

For the convenience of Irish enthusiasts we supply:

Radio & Electronics Constructor Data Books Panel Signs Transfers

Also a postal service

peats

the world of electronics
25 Parnell Street, Dublin 1. Tel 749972

100mA or more. The relay can be one of those Maplin 'Open Relay' jobs with a 410Ω coil and changeover contacts. All the remaining parts are quite standard."

And with these words Smithy closed all further dis-

cussion and chivied Dick into starting on his normal trouble-shooting duties. However, before finally embarking on his own servicing work Smithy connected the base of TR2 in his timing circuit to the QB14 output and

thoughtfully selected "Reset" and then "Start".

Which means that the relay in the timing circuit will be de-energising at just about the same time as we have our next little get-together. ■

ARIANNE SUCCESSFULLY LAUNCHED

Report by
Arthur C. Gee

The European Space Agency's rocket Ariane has been developed to gain independence from the U.S.A. for launching commercial satellites. Some estimates suggest that as many as two hundred satellites may need to be launched in the next ten years and the ESA hopes to get a share of this market with its Ariane launchers.

From its inception, the Ariane development programme has provided for a ground-testing phase, followed by a test-flight phase. The latter comprises four launches, to prove that the launchers can execute the missions foreseen and thus offer an operational launch facility to customers from the late 1980's onward. The first test flight was scheduled for July 1979 and the last for October 1980.


All went well until an incident affecting the rocket's 3rd Stage upset the programme. An explosion on a test stand,

attributable to malfunctioning of a safety system, damaged the only 3rd Stage available at the time for final development testing.

However, it was possible to ship a completed rocket to the launch site at Kourou, French Guiana by the end of Sep-

tember 1979, and the launching programme sequences were started on 1st October. It was planned that this phase should last for 56 days, giving a launch date of 15th December.

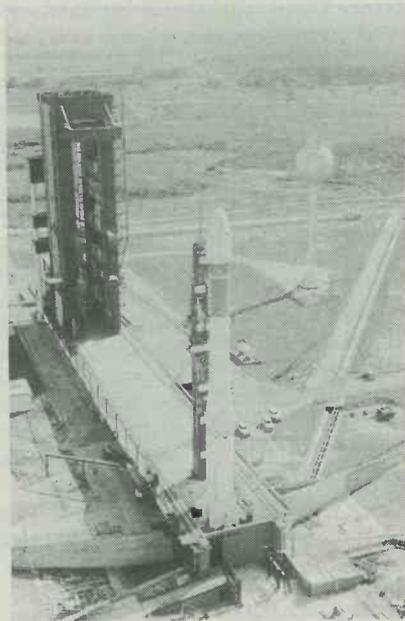On the 14th December, the countdown for a launch schedule for the next day was



Ariane "propellant mock-up" erected on the launch site for testing of launch procedures in February 1979, Kourou French Guiana.

Launch Centre E.L.A.



started. All went well, until the ignition of the First Stage engines, after which one of the pressure sensors in the First Stage propulsion system shut down the computer controlling the automatic launch sequences, indicating a malfunction somewhere in the system and the launch sequence was thus interrupted.

Evaluation of the telemetry data showed that the engines had been functioning correctly and that the shut down had

been caused by malfunction of the pressure sensor itself.

The countdown was therefore resumed on the 22nd December for a launch on 23rd December. Once again during the automatic pre-launch sequence a minute or so before firing, a false signal at the instant of switching from ground to on-board electric power supply followed by the detection of insufficient pressure in the Third Stage helium bottle, led to the launch

being postponed to the following day. Finally on the 24th December at 17 h. 14 min. 38 s. U.T. after a countdown interrupted by a number of comparatively minor incidents, the launcher lifted off for a totally successful flight.

No actual satellite was flown on this first test flight, but a simple "Technological Capsule" was put into orbit to make trajectory and environmental measurements.

Databus series No. 11 Continued from Page 670

With a microprocessor which has analogue inputs and outputs all of these problems are eased. Temperature, for example, can be measured with thermistors, since a digital signal is no longer needed. Since all of the analogue-to-digital conversion takes place inside the microprocessor, the differences between different types of transducer become less important. At the other end, the analogue signal out of the microprocessor is better adapted to control quantities such as fuel and air supply than a digital signal, and again avoids conversion chips. Even before this announcement, General Motors had ordered 5 million 6802 micros from Motorola and Fairchild, so as to cope with the new US laws on fuel economy and pollution – and these new car designs could very well be the biggest threat we've ever seen to what's left of the British car industry.

I have a sneaking feeling, too, that the

analogue micro may be of more than passing interest to audio designers, too! The analogue microprocessor, of course, still carries out all its operations in binary bytes, and has to be programmed in the same way as the digital version.

The important point about all this is that the microprocessor bandwagon is moving very fast indeed, and the quicker we all hop on the better. It's like the valve-transistor switch – if you didn't get in early you had great difficulty in adjusting your thinking fast enough. We don't necessarily need to build or buy computers, or design machine-control systems to keep up to date, but we do need to be able to speak the language of microprocessing and to understand how they do what they do. That has been the aim of this series, and I hope that each reader has been able to derive benefit from it.

(Concluded)

(The series "Tune-In To Programs", by Ian Sinclair, appeared in *Radio & Electronics Constructor* for February to September 1979 inclusive and November 1979).

TRADE NEWS

VIDEO TAPE ERASER CUTS HEAD WEAR

Now being marketed by the Broadcast and Closed Circuit Television Equipment Division of S.G.I. is a video eraser which will erase video and audio cassettes and tapes in seconds.

Called the Videoraser, it is used instead of the recorder's own internal mechanism and thereby leads to a reduction of video head wear and replacement frequency.

It also erases 100 times better than a recorder thus enabling higher re-recording standards to be achieved and prolongs the usable life of the tape.

Although used extensively by broadcasting organisations in North America, its price £49.50 plus V.A.T., makes it a worthwhile investment for the domestic video user.

With a magnetic flux of 1,400 gauss, it is the most powerful of its type and can erase a two inch cassette.

It measures 120mm x 114mm, weighs 2 kilos and is designed for 220-240 volts A.C. operation.

Further information can be obtained direct from: S.G.I. Limited, Broadcast & Closed Circuit Television Equipment Division, Fircroft Way, Edenbridge, Kent, TN8 6HA.



HOME RADIO ELIMINATOR KIT

With PP9 batteries hovering around the £1 mark use of battery eliminators becomes increasingly attractive. The newly introduced Home Radio Battery Eliminator Kit, at only £2 (plus 30p VAT and 50p postage) and with a running cost of approximately 500 hours for 1p, will in consequence be welcomed by owners of radios requiring a 9 volt supply. Included in the kit are a 6-0-6V 100 mA mains transformer, two high value electrolytic capacitors, smoothing and dropping resistors, 1N4002 rectifier, 9.1V zener diode and PP9 and PP3 style connectors. The

kit can be assembled without soldering by the use of small terminal blocks which are also supplied. The output is suitable for all standard 9V portable radios.

The components can be assembled inside the radio or in a suitable case, such as the Home Radio BX53. The eliminator kit is available from Home Radio (Components) Ltd., 234-240 London Road, Mitcham, Surrey, CR4 3HD. Incidentally, Home Radio will be closed from 1st to 9th August for part of the Summer holidays.

NEW STEREO DESK FOR BBC LOCAL RADIO

BBC Local Radio's first 16-channel stereo studio desk is called the Mark 3(N). It came into operation in April in the Local Radio Training Unit's new studios just completed in The Langham, Portland Place.

First to use the equipment will be the production staff currently being trained as the broadcasting team for BBC Radio Norfolk, the station due to go on the air in stereo on 11 September. They will be followed by the staff of Radio Lincolnshire, who start broadcasting in November.

The Mark 3(N) is designed to the same operational principles as the present BBC Mark 3 but is as compact as the old Mark 1 with a number of new features added.

Said Robert McLeish, Head of BBC Local Radio Training: "This is an exciting development for the new BBC stations - a compact, self-op stereo desk with full production facilities.



SMALL ADVERTISEMENTS

Rate: 12p per word. Minimum charge
£2.00
Box No. 30p extra

Advertisements must be prepaid and all copy must be received by the 4th of the month for insertion in the following month's issue. The Publishers cannot be held liable in any way for printing errors or omissions, nor can they accept responsibility for the bona fides of Advertisers. Where advertisements offer any equipment of a transmitting nature, readers are reminded that a licence is normally required. (Replies to Box Numbers should be addressed to: Box No. —, Radio and Electronics Constructor, 57 Maida Vale, London, W9 1SN.

ANY REQUESTED SERVICE SHEET £1 (Plus large s.a.e.). Full repair data any named TV £5.50 (with circuits, layouts, £7). Large s.a.e. brings newsletter, bargains, etc. Ausrec, 76 Church Street, Larkhall, Lanarkshire, ML9 1HE.

£5 OSCILLOSCOPE. Standard junk box components plus approx. another £5 (Total components approx £12). This unit plugs into TV aerial socket and converts TV to oscilloscope. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge, CB4 4BL.

FOR SALE: "Challenge of the Stars" by Patrick Moore and David A. Hardy £2.00. "Destroyers" by Antony Preston £4.00. Box No. G376.

FREE 1980 AMTRON CATALOGUE with new range of kits and equipment cabinets. Send s.a.e. Amtron UK Ltd., 7 Hughenden Road, Hastings, Sussex, TN34 3TG. Telephone: Hastings 436004.

COLLECTORS' ITEMS. Nearly 50 copies of Radio Society of Great Britain's *Bulletins* covering period 1945 to 1949. In reasonable condition. Offers to: Box No. G377.

COMPONENTS, Items, Bargains. Various lists 15p or s.a.e. Sole Electronics (REC), 37 Stanley Street, Ormskirk, Lancs., L39 2DH.

INTERESTED IN OSCAR? Then join AMSAT-UK. Newsletters, OSCAR NEWS Journal, prediction charts, etc. Details of membership from Ron Broadbent, G3AAJ, 94 Herongate Road, Wanstead Park, London, E12 5EQ.

PEN TYPE SIGNAL INJECTOR available for £2.50 including air freight. Business Promotion Bureau, 376 Lajpat Rai Market, Delhi 110006, India.

(Continued on page 685)

LIGHTING & AMPLIFIER MODULES FROM L&B

01-689 4138

YOU'VE ALL HEARD OF OUR SUPERB MODULES, AND IF YOU HAVEN'T, IT'S TIME YOU DID, SO READ ON! SHOWN HERE ARE A RANGE OF THE MOST RELIABLE SYSTEMS ON THE MARKET.

LB31000SLC
£29.90



19 x 9.5 x 3cm.


LB31000SL SOUND TO LIGHT. A SUPERB PERFORMING SYSTEM AT AN INCREDIBLY LOW PRICE.

3 channels. 1000w each. Fully fused. Very high input impedance. Operates from ¼ to 300w sound input. Third order filters. Zero voltage fired. Master Vol/Bass/Mid/Treble controls.

LB31000SLC SOUND TO LIGHT/CHASER. THE MOST ADVANCED SOUND TO LIGHT MODULE AVAILABLE, WITH AUTOMATIC SWITCHING TO CHASE UPON ABSENCE OF A MUSIC INPUT.

3 Channels, 1000w each. Fully fused. Very high input impedance. Electronic filters. 5HZ to 70KHZ bandwidth. Operates from ¼ to 300w sound input. Triac zero voltage triggering. Master Vol/Bass/Mid/Treble/Chase speed controls

LB31000SL £21.40

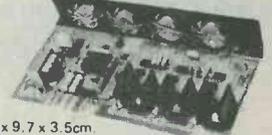

20 x 9.7 x 3.5cm.

LB31000LC CHASER A FULLY DIGITAL 8 CHANNEL CHASER, ALLOWING VARIATION OF CHASE SPEED AND CHASE RETURN DELAY.

1000w per channel. CMOS circuitry. Zero voltage fired. Can be footswitch triggered. Additional modules can be cascaded to form 16, 24, 32 chan. ect.

£26.50

LB81000LC
19 x 9.5 x 3cm.

LB41000LS SEQUENCER LOGIC RANDOM SEQUENCER, WITH TWO SPEED CONTROLS OFFERING A WIDE RANGE OF EFFECTS. 4 channels, 1000w each. CMOS circuitry. Zero voltage fired.

LB31000LD



20 x 7.8 x 3.5

POWER AMPS, 250, 100 & 25W RMS. RUGGED TOUGH DEALING AUDIO POWER AMP MODULES.

LB250	LB150	LB100	LB25
10HZ to 25KHZ	10HZ to 25KHZ	10HZ to 25KHZ	10HZ to 25KHZ
S/N 110 dB	S/N 110 dB	S/N 110dB	S/N 90 dB
THD 0.1%	THD 0.1%	THD 0.1%	THD 0.007%
0.5v SENS	0.5v SENS	0.5v SENS	0.5v SENS
£39.50	£26.50	£18.20	£11.20


LB41000LS
£17.50

20 x 9.2 x 3.5 cm

LB31000LD and 11000LD DIMMERS. FULL POWER 3 & SINGLE CHANNEL LIGHTING DIMMERS FOR USE IN CLUBS/PUBS/THEATRES/SCHOOLS, ETC.

1000w per channel. Fully fused phase controlled. Full input and individual Triac filters.

LB31000LD £14.70 LB11000LD £6.70

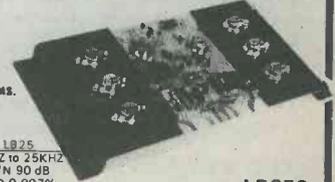

LB250
31 x 15 x 3.5cm

PREAMPS

LBPA3. Complete stereo disco preamp system. Comprising of L&R deck mixers, mic mixer, deck and mic tone stages, mic auto fade over decks, PFL, output drivers and its own regulators.

LBPA2. General purpose 4 chan, mixer/tone stage.

LBPA1. Stereo Hi-Fi System



LBPA1 £19.50

LBPA2 £17.20

LBPA3-M (magnetic deck inputs) £30.70

LBPA3-C (ceramic deck inputs) £30.70

LBPA3-M

20.4 x 9.5cm

POWER SUPPLIES


Four types of powerful supply units for our power amps. Consisting of a varnish-impregnated mains transformer and rectifier board (fuse protected).

LB250PS £24.50

LB150PS £18.00

LB100PS £14.70

LB25PS £11.20

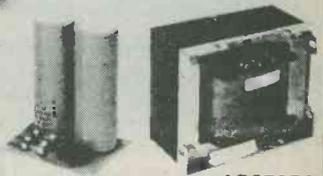

LB250PS

YOU REQUIRE A BOARD THAT'S MIGHTY COMPETITIVE, RELIABLE, MANUFACTURED FROM THE HIGHEST QUALITY COMPONENTS, OF HIGH PERFORMANCE, TESTED AND INSPECTED, SUPPLIED WITH CONNECTION AND CCT, DGM AND GUARANTEED. IN TWO LETTERS YOU REQUIRE L & B.

All prices shown are inclusive of VAT.

For your FREE catalogue, with full spec. Send a 12p stamp.

Trade and Overseas inquiries welcome

P/Packing 50p in the UK except power supplies (£1.00).

→ L & B

45 WORTLEY ROAD
WEST CROYDON
SURREY CR0 3EB
TEL. 01-689 4138



Wilmslow Audio

THE firm for speakers!

SEND 50p FOR THE WORLDS BEST CATALOGUE OF SPEAKERS, DRIVE UNITS KITS, CROSSOVERS ETC. AND DISCOUNT PRICE LIST

AUDAX ● AUDIOMASTER ● BAKER ● BOWERS & WILKINS ● CASTLE ● CELESTION ● CHARTWELL ● COLES ● DALESFORD ● DECCA ● EAGLE ● ELAC ● EMI ● FANE ● GAUSS ● GOODMAN'S ● HARBETH ● ISOPHON ● I.M.F. ● JORDAN ● JORDAN WATTS ● KEF ● LOWTHER ● MCKENZIE ● MISSION ● MONITOR AUDIO ● MOTOROLA ● PEERLESS ● RADFORD ● RAM ● ROGERS ● RICHARD ALLAN ● SEAS ● SHACKMAN ● STAG ● TANNOY ● VIDEOTONE ● WHARFEDALE ●

WILMSLOW AUDIO DEPT REC
SWAN WORKS, BANK SQUARE, WILMSLOW
CHESHIRE SK9 1HF

Tel: 0625-529599 for Mail Order & Export of Drive Units, Kits, etc.,
Tel: 0625-526213 (Swift of Wilmslow) for Hi-fi and complete speakers

A CAREER IN RADIO

Start training *today* and make sure you are qualified to take advantage of the many opportunities open to the trained person. ICS can further your technical knowledge and provide the specialist training so essential to success.

ICS, the world's most experienced home study college, has helped thousands of ambitious men to move up into higher paid jobs — they can do the same for *you*.

Fill in the coupon below and find out how!

There is a wide range of courses to choose from, including:

CITY & GUILDS CERTIFICATES

Telecommunications Technicians'
Radio TV Electronics Technicians'
Electrical Installations Technicians'
Electrical Installation Work
Radio Amateurs'
MPT Radio Communications Cert
EXAMINATION STUDENTS —
GUARANTEED COACHING
UNTIL SUCCESSFUL

TECHNICAL TRAINING

ICS offer a wide choice of non-exam courses designed to equip you for a better job in your particular branch of electronics, including:
Electronic Engineering & Maintenance
Computer Engineering/Programming
Radio, TV & Audio Engineering & Servicing
Electrical Engineering Installations & Contracting

COLOUR TV SERVICING

Technicians trained in TV Servicing are in constant demand. Learn all the techniques you need to service Colour and Mono TV sets through new home study course approved by leading manufacturer.

POST THIS COUPON OR TELEPHONE FOR FREE PROSPECTUS

I am interested in

Name Age

Address

Occupation



Accredited
by CACC
Member of
ABCC


To
International Correspondence Schools
Dept W278, Intertext House, LONDON
SW8 4UJ or phone 01-622 9911 (anytime)

Self-Binder

for "Radio & Electronics Constructor"

The "CORDEX" Patent Self-Binding Case will keep your issues in mint condition. Copies can be inserted or removed with the greatest of ease. Rich maroon finish, gold lettering on spine.

Specially constructed Binding Cords are made from Super Linen of great strength, very hard twisted and twice doubled. They are attached to strong RUSTLESS Springs under tension, and the method adopted ensures PERMANENT RESILIENCE of the Cords. Any slack that may develop is immediately compensated for and the Cords will always remain taut and strong. It is impossible to overstretch the springs, as a safety check device is fitted to each.

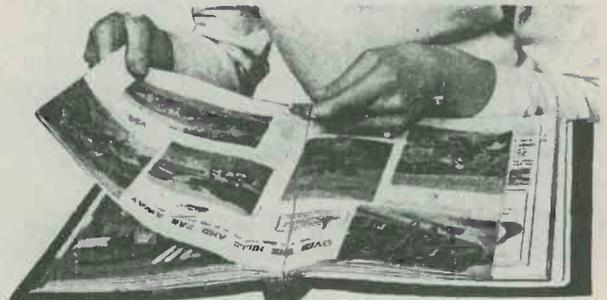

PRICE £2.25 P. & P. 50p
including V.A.T.

For your other magazines
Plain-backed in Maroon or Green
(Please state colour choice)

PRICE £2.25 P. & P. 50p
including VAT

Available only from:—

Data Publications Ltd.
57 Maida Vale London W9 1SN

SMALL ADVERTISEMENTS

(Continued from page 683)

MODULES: Mullard LP1164 AM/FM I.F. Unused and guaranteed. £1.50. P.&P. C.W.O. BA screws, hardware, components, manufacturers' clearance. S.A.E. lists. Tennex Ltd., Stock Road, Southend-on-Sea, Essex, SS2 5QF.

FOR SALE: Wide angle 9.5mm cine equipment: camera, projector, screen, etc. Also several other 9.5mm cine cameras. S.A.E. for details Box No. G388.

JOIN THE INTERNATIONAL S.W. LEAGUE.

Free services to members including Q.S.L. Bureau, Amateur and Broadcast Translation, Technical and Identification Dept. - both Broadcast and Fixed Stations, DX Certificates, contests and activities for the SWL and transmitting members. Monthly magazine, *Monitor*, containing articles of general interest to Broadcast and Amateur SWLs, Transmitter Section and League affairs, etc. League supplies such as badges, headed notepaper and envelopes, QSL cards, etc., are available at reasonable cost. Send for League particulars. Membership including monthly magazines, etc., £6.00 per annum. (U.K. and British Commonwealth), overseas \$12.00. Secretary ISWL, 1 Grove Road, Lydney, Glos., GL15 5JE.

FOR SALE: Sinclair MK14 mini-microprocessor with power supply. £45.00 o.n.o. Box G389.

ELECTRONIC COMPONENTS & ACCESSORIES: We offer you a first class service at the right price, all orders processed the same day. Send now for 1980 catalogue 30p refundable on first order over £1.00 or return catalogue within 10 days for full refund to: Lightning Electronic Components (RE), Free post, Tamworth, Staffs., B77 1BR.

BOOKS TO CLEAR. "Solid State Design for the Radio Amateur" ARRL. £3.50. "The Radio Amateur's Handbook" by Frederick Collins, £3.00. "Amateur Radio Antennas" by Harry Hooton, £1.00. "Ham Antenna Construction Projects" by J. A. Stanley, 75p. "All about Cubical Quad Antennas" by W6SAI, £1.00. "Astronomy" by David Evans, £1.25. Box No. G390.

THE RADIO AMATEUR INVALID & BEDFAST CLUB is a well established Society providing facilities for the physically handicapped to enjoy the hobby of Amateur Radio. Please become a supporter of this worthy cause. Details from the Hon. Secretary, Mrs. F. E. Woolley, 9 Rannoch Court, Adelaide Road, Surbiton, Surrey, KT6 4TE.

WANTED: Service Manual circuit of R1155A receiver. To buy or borrow copy. All expenses refunded. Box No. G.391.

(Continued on page 686)

RADIO & ELECTRONICS Constructor Projects

Following the announcement last month of our component kit service, we list below the kits which are now available.

RING OF LEDS PRINT TIMER January 1980 £7.80

LOGIC TESTER February 1980 £3.05

TELEPHONE BELL REPEATER February 1980 (Excludes screened cable which is supplied as required). £5.80

INFRA-RED INTRUDER ALARM March 1980 (Relay 2p 2w £3.20 extra) £6.10

STEREO MIXER UNIT March 1980 £7.60

GENERAL PURPOSE 8 WATT AMPLIFIER May 1980 (Excludes etched p.c.b. Plain board can be supplied at 55p extra). £12.75

LABORATORY POWER SUPPLY May 1980 £12.80

DUAL POLARITY VOLTMETER May 1980 (Case differs from that shown). £9.60

All kits include parts as specified in the article except where indicated. Batteries and solder are not supplied with any kit. We hope to add to the range at approximately two monthly intervals. Prices include VAT but do not include postage, for which we make a standard charge of 50p per kit. Allow 10 days for delivery. Remember we also sell a wide range of components, etc. send 30p in stamps for details on the above kits and our components. Mail order only.

T & J ELECTRONIC COMPONENTS

98 Burrow Road, Chigwell, Essex. IG7 4HB

BUILD YOUR OWN

P.A., GROUP & DISCO SPEAKERS by R. F. C. Stephens

Save money with this practical guide. Plans for 17 different designs, Line source, I.B., Horn and Reflex types, for 8"-18" drive units. £3.95 post free (\$8 overseas).

THE INFRA-BASS LOUDSPEAKER by G. Holliman

(full constructional details for versions using 15", 12" and 10" (drive units). £2.95 post free (\$6 overseas).

THE DALESFORD SPEAKER BOOK by R. F. C. Stephens

This book is a must for the keen home constructor. Latest technology DIY designs. Plans for I.B., and Reflex designs for 10-100 watts. Also unusual centre-bass system. £2.20 post free (\$5 overseas).

VAN KAREN PUBLISHING

5 Swan Street, Wilmslow, Cheshire



Top Priority for every constructor - HOME RADIO CATALOGUE

- Over 2,000 items clearly listed
- Profusely illustrated throughout
- Over 100 A-4 size pages
- Bargain list included free

Send cheque or P.O. for £1.30

HOME RADIO Components LTD
Dept. RC, P.O. Box 92, 215
London Road, Mitcham, Surrey.
01-648 8422

Strip-fix Plastic PANEL SIGNS



- ★SET 3-Wording-WHITE
- ★SET 4-Wording-BLACK

Over 1,000 words and symbols,
covering more than 300 terms, in
each set

Illustration of actual size equals RADIO

★SET 5-DIALS

6 sheets containing one Large and two
Medium scales, Large Horizontal Tuning
scale, Frequencies, 12 Control Panels

6 SHEETS IN EACH SET

PRICE: **£1.50** per set including VAT.
p.&p. 11p per set.

**To DATA PUBLICATIONS LTD.,
57 Maida Vale, London, W9 1SN**

Please supply Panel Signs as follows: Set 3.....Set 4.....Set 5.....

I enclose cheque/crossed postal order for
(Tick which set is required)

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

SMALL ADVERTISEMENTS

(Continued from page 629)

FREE! 12" x 6" Veroboard, with first 50 orders for our compilation pack of components. Hundreds of common and exotic use devices plus pcb's thermistors, etc. This is really an offer not to be missed. Send P.O. or cheque for £8.20 immediately to: R.E. Norman, Portbuild Limited, 57 Amberwood Rise, New Malden, Surrey. Or send s.a.e. for list.

INGENIOUS GAMES to distract and tantalise – and to construct. Three original designs by me in kit form, pocket sized with a top quality finish to grace your coffee table and deceive your friends. From £4.25. Send s.a.e. for details of all three to: H. S. Houston, 12 Harlech Avenue, Leeds 11 Yorkshire.

WANTED: FAX equipment, manuals, service sheets, etc. G2UK, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk. NR32 3PJ

FOR SALE: Video Tape recorders, need attention. £25.00-£75.00. Also C.C.T.V. Cameras. Box No. G392.

OSCILLOSCOPE FOR £12. Easy build converter plugs into TV aerial socket and converts to large screen oscilloscope. Components cost approx £12. Circuit and plans £3. Kerr, 27 Coles Road, Milton, Cambridge, CB4 4BL.

BE PROFESSIONAL! Use our P.C.B. equivalent to old-fashioned 8/way group boards. Incorporates locations for additional components if required. Pack of three in high-quality fibreglass – includes special services catalogue and price list – only £2.00 post paid (Mail Order only). M. J. Evans, 7 Shap Drive, Warndon Estate, Worcester, WR4 9NY.

POSTAL ADVERTISING? This is the Holborn Service. Mailing lists, addressing, enclosing, wrapping, facsimile letters, automatic typing, copy service, campaign planning, design and artwork, printing and stationery. Please ask for price list. – The Holborn Direct Mail Company, Capacity House, 2-6 Rothsay Street, Tower Bridge Road, London, S.E.1. Telephone: 01-407 6444.

FOR SALE: 2000 diodes £2.50. 25 mixed voltage zeners £1.00. LCD 1/100 sec. stopwatch £12.00. LCD watch £7.50. Voice control ladybird toy £15.00. 3 dimensional hologram pendants £12.50. 10" x 8" holograms £30.00. S.A.E. for details. Damaged video tape recorders and CCTV cameras £25.00 to £75.00. Nicad battery chargers £1.50. Light powered calculator, needs no batteries, £20.00. Credit card calculator. C60 tapes 25p, 10 – £2.00, 100 – £15.00. Chess challenger 10 level £150, 7 level £100. Draughts challenger 4 level £90. 2 level £75. Football table plans £5.50. Pair walkie talkies £15.00 J. Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

(Continued on page 687)

SMALL ADVERTISEMENTS

(Continued from page 686)

SHACK CLEARANCE. Large selection of good components. Everything must go so selling cheaply. S.A.E. for details. Box No. G393.

INTERESTED IN RTTY? You should find the "RTTY Journal" of interest. Published in California, U.S.A., it gives a wide outlook on the current RTTY scene; RTTY-DX; DXCC Honour Roll; VHF RTTY news; and up to date technical articles are included. Specimen copies 35p from: The Subscription Manager, RTTY Journal, 21 Romany Road, Oulton Broad, Lowestoft, Suffolk, NR32 3PJ.

BOOKS FOR SALE: *Master Transistor/I.C. Substitution Handbook*, by Tab Books, £1.75. *The Fabulous Phonograph 1877-1977* by Roland Gelatt, £2. *Linear I.C. Applications Handbook*, by George Clayton, £1. *John Logie Baird & Television*, by Michael Hallett, £2. *110 Semiconductor Projects for the Home Constructor*, by R. M. Marston, £1.20. *The Cat's Whisker — 50 years of Wireless Design*, by Jonothan Hill, £2.00. *Experiments with Operational Amplifiers*, by George B. Clayton, £3.75. *Digital I.C. Equivalents & Pin Connections*, by Adrian Michaels, £1.20. All prices include postage. Box No. G.394.

FOR SALE: Cassette tapes 6 — £5.00. Classical, rock, disco, country, party time or easy listening. J Fulton, Derrynaseer, Dromore, Co. Tyrone, N. Ireland.

PERSONAL

JANE SCOTT FOR GENUINE FRIENDS. Introductions to opposite sex with sincerity and thoughtfulness. Details free. Stamp to: Jane Scott, 3/Con North St. Quadrant, Brighton, Sussex, BN1 3GJ.

IF YOU HAVE ENJOYED A HOLIDAY on the Norfolk Broads, why not help to preserve these beautiful waterways. Join the Broads Society and play your part in determining Broadlands future. Further details from: — The Hon. Membership Secretary, The Broads Society, "Ickniel," Hilly Plantation, Thorpe St. Andrew, Norwich, NOR 85S.

SPONSORS required for exciting scientific project Norwich Astronomical Society are building a 30" telescope to be housed in a 20" dome of novel design. All labour being given by volunteers. Already supported by Industry and Commerce in Norfolk. Recreational. Educational. You can be involved. Write to: NAS Secretary, 195 White Woman Lane, Old Catton, Norwich, Norfolk.

BROADLANDS RESIDENTIAL CLUB for elderly people. Are you recently retired and looking for a home? We have a delightful top floor room overlooking Oulton Broad, facing south. Write to: The Warden, Broadlands Residential Club, Borrow Road, Oulton Broad, Lowestoft, Suffolk.

REVOR OPTICAL & TECHNICAL

6 SICILIAN AVENUE
LONDON W.C.1
Tel. 01-836 4536

£14.91

POST FREE



4" dia. lens

FLEXIBLE MAGNIFIER

WITH CAST IRON BASE, PRECISION GROUND AND POLISHED LENS, CHROME PLATED FRAME AND FLEXIBLE TUBE. IDEAL FOR HOBBIES, AND DETAILED WORK WHICH REQUIRES BOTH HANDS FREE.

CALLERS WELCOME

(Subject to price ruling at the time of issue)

MARCO TRADING

To obtain a free copy of our 35 page list simply send a 20p postage stamp or a large SAE. This advertisement shows only a part of our range. (Our new list includes Tants, Electrolytics, Disc ceramics, etc.)

400m/w ZENOR DIODES

Low Price
3V6, 3V9, 4V3, 4V7, 5V1, 5V6, 6V2, 6V8, 7V5, 8V2, 9V1, 10V, 11V, 12V, 13V, 13V5, 15V, 16V, 18V, 20V, 22V, 24V, 27V, 30V, 33V
Price: 8p each 100 any mix £6.00

RESISTORS

1/4W at 40°C 5% tol., 2.2 Ω to 2M2, E12 2p each.
Resistor Pack — 2.2 Ω - 2M2, 10 each value (730 resistors) £6.00

1 watt

ZENER DIODES

3V3 to 200V Full range
Price 15p each 100 any mix £12.50
8 DIL 10p 22 DIL 23p
14 DIL 13p 24 DIL 24p
16 DIL 15p 28 DIL 28p
18 DIL 18p 40 DIL 40p
20 DIL 22p

VEROBOARD (Copper Clad)

Size Inch 0-1" 0.15
2.5 x 1 20p N/A
2.5 x 5 55p 56p
2.5 x 3.75 46p 50p
Vero Wiring Pen (including spool of wire) £2.84

CONNECTING CABLE

Black, Blue, Green, Grey, Orange, Pink, Red, White, Violet, Yellow, Brown. Singles 5p per metre
7/0.2mm 5p per metre
16/0.2mm 8p per metre

SPECIAL OFFERS

Power Amplifier Sanyo STK015 Brand New Full Spec, etc. 10 watts into 8 Ω.
Free Spec sheet with every order. Our price: £2.50 each.
Radio Spares Edge Meter Type MR100 (259-562). All new and boxed. RS price over £4.00 each. Our Price: £2.50 each.

Send your orders to:

DEPT DP12, MARCO TRADING, THE OLD SCHOOL,
EDSTASTON, Nr. WEM, SHROPSHIRE SY4 5RJ
Tel: Whixall (094872) 464/465

Please add 30p postage and packing to each order and add 15% VAT to your total order. Export add NO VAT but add postage. Air/Sea at cost

TANT. BEAD CAPS

0.1/35v	12p	4.7/35v	12p
0.22/35v	12p	33/6.3v	25p
1.0/35v	12p	47/10v	30p

SUB. MIN. TOGGLE SWITCHES

SPST —	70p
SPDT —	78p
DPDT —	82p
DPDT —	90p

(C-OFF)



BRIDGE RECTIFIERS

50V	32p	400V	50p
400V	43p	6.0 Amp 50V	70p
800V	58p	200V	78p
2.0 Amp 50V	35p	400V	85p
100V	42p		

0.1W SUB. MINIATURE PRE-SETS

100 Ω to 1 Meg Vertical or Horizontal
Price: 6p each. 100 any mix £4.50

AC128	20p	BC125	10p	BC184	9p
AD149	58p	BC147	8p	ZN3055	48p
BC107	10p	BC153	10p	BY127	12p
BC108	10p	BC172	8p	IN4007	8p
BC109	10p	BC183	9p	IN4148	2p

Full range of Panel Meters available
£6.25 each

RADIO & ELECTRONICS CONSTRUCTOR

Single Copies

Price 55p each, p&p 18p

Issue(s) required

Annual Subscription

Price £8.50 inland, £9.50 overseas (including Eire)

post free, commence with issue

Bound Volumes:

Vol. 27.	August 1973 to July 1974	Price £3.00, post & pkg £1.30
Vol. 28.	August 1974 to July 1975	Price £3.20, post & pkg £1.30
Vol. 29.	August 1975 to July 1976	Price £3.50, post & pkg £1.30
Vol. 30.	August 1976 to July 1977	Price £3.70, post & pkg £1.30
Vol. 31.	August 1977 to August 1978	Price £5.20, post & pkg £1.30
Vol. 32.	September 1978 to August 1979	Price £5.50, post & pkg £1.30

CORDEX SELF-BINDERS

With title, 'RADIO & ELECTRONICS CONSTRUCTOR' on spine,
maroon only

Price £2.25, post & pkg 50p

With no title on spine, maroon

Price £2.25, post & pkg 50p

With no title on spine, green

Price £2.25, post & pkg 50p

Prices include V.A.T.

DATA BOOK SERIES

DB5 TV Fault Finding, 132 pages

Price £1.20, P.&P. 27p

DB6 Radio Amateur Operator's Handbook,

New edition in course of preparation

DB17 Understanding Television, 504 pages

Price £3.95, P. & P. £1.00

DB19 Simple Short Wave Receivers

Price 80p, P. & P. 27p

140 pages

STRIP-FIX PLASTIC PANEL SIGNS

Set 3: Wording – White

– 6 sheets

Price £1.50, P. & P. 11p

Set 4: Wording – Black

– 6 sheets

Price £1.50, P. & P. 11p

Set 5: Dials

– 6 sheets

Price £1.50, P. & P. 11p

Prices include V.A.T.

I enclose Postal Order/Cheque for in payment for

NAME

ADDRESS

(BLOCK LETTERS PLEASE)

Postal Orders should be crossed and made payable to Data Publications Ltd.

Overseas customers please pay by International Money Order.

All publications are obtainable through your local bookseller

Data Publications Ltd., 57 Maida Vale, London W9 1SN

PLEASE MENTION THIS MAGAZINE WHEN WRITING TO ADVERTISERS


VOLTAGE MULTIPLIERS

In (a) the a.c. generator, with a peak voltage of E volts, is shown at an instant when its lower terminal is at peak positive. D_1 conducts and C_1 charges to E volts. D_2 and C_2 are added in (b), and the generator upper terminal is at peak positive. The anode of D_2 is $2E$ volts positive with respect to earth and so D_2 conducts, to charge C_2 to $2E$ volts. D_1 is reverse biased.

D_3 and C_3 are introduced in (c), with the generator lower terminal positive. The left hand side of C_3 is at earth potential, because the left hand side of C_1 is made E volts negative of earth by the generator, whilst the anode of D_3 is $2E$ volts positive of earth because of C_2 . D_3 conducts and C_3 charges to $2E$ volts. D_2 is reverse biased. In (d) a fourth diode and capacitor are added. With the generator upper terminal positive, $4E$ volts (generator voltage plus C_1 voltage plus C_3 voltage) is applied to the anode of D_4 , which conducts to charge C_4 to $2E$ volts. Diodes D_1 and D_3 are reverse biased.

The circuit of (d) is a Cockcroft-Walton voltage multiplying rectifier circuit and it produces 4 times the peak voltage of the a.c. generator. The series can be extended further and a Cockcroft-Walton sextupler circuit is shown in (e).


For purposes of illustration, the capacitors in (a) to (d) were shown as electrolytic. Non-electrolytic capacitors can, of course, also be used. As in any capacitor input rectifier circuit, the rectified output voltage falls from peak value when current is drawn. Multiplier circuits of this type are usually employed in high voltage low current applications, such as the provision of e.h.t. voltage for cathode ray tubes.

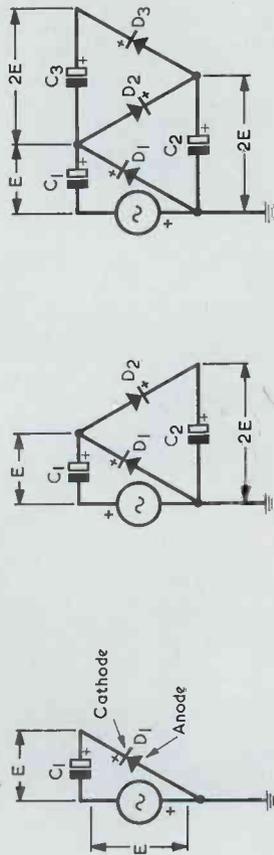

(a)

(b)

(c)

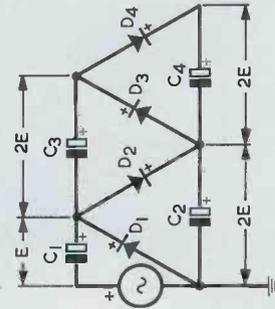

(d)


(e)

STEP INTO A NEW WORLD WHEN YOU DISCOVER **MAPLIN**

For beginners or professionals, the Maplin catalogue will help you find just about everything you need for your project.

Over 5,000 of the most useful components — from resistors to microprocessors — clearly described and illustrated.

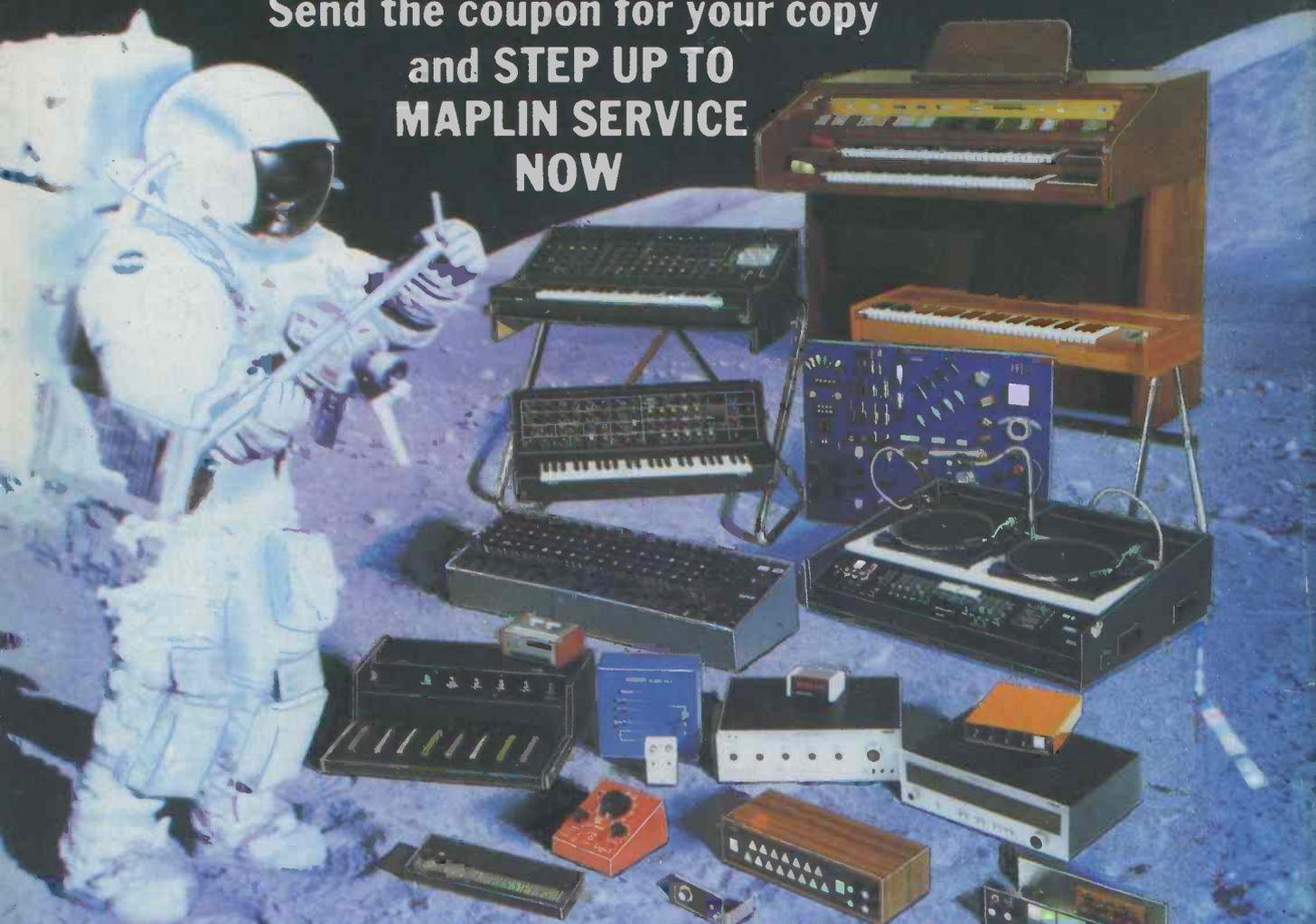Send the coupon for your copy
and **STEP UP TO
MAPLIN SERVICE
NOW**




Post this coupon now for your copy of our 1979-80 catalogue price 70p.

Please send me a copy of your 280 page catalogue. I enclose 70p (plus 46p p&p). If I am not completely satisfied I may return the catalogue to you and have my money refunded. If you live outside the U.K. send £1.35 or ten International Reply Coupons. I enclose £1.16.

NAME _____
ADDRESS _____

R.E.C. 780

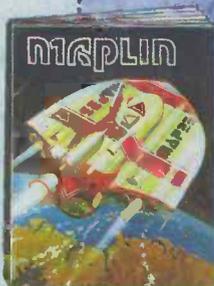

MAPLIN

ELECTRONIC SUPPLIES LTD

All mail to:
P.O. Box 3, Rayleigh, Essex SS6 8LR.
Telephone: Southend (0702) 554155.
Shop: 284 London Road, Westcliff-on-Sea, Essex. (Closed on Monday).
Telephone: Southend (0702) 554000.

Catalogue now available in all branches of WHSMITH  Price £1.00