

RADIO — ELECTRONICS

MARCH 1952

LATEST IN TELEVISION • SERVICING • AUDIO



**EFFICIENT TV SERVICE
IN THE CUSTOMER'S HOME**

See page 4

30¢

U. S. and
CANADA

***In this issue:* Servicing Oscillator Circuits •
TV Conversion Details • Improving Listenability**

CYLINDRICAL reflection-free

21 inch

245 sq. in.

the largest 21" CRT
available!

21KP4A



Selfocus Teletron.
Maintains focus
automatically
at all times.
Requires no focus
coil or control.

21EP4A



Magnetic focus-
ing and deflection.
Utilizes Du Mont
bent-gun for
edge-to-edge
focus.

21FP4A



Low-voltage
electrostatic
Teletron. Focuses
in range of -65
to +350v. at
16 kv anode
voltage.

DU MONT

*Teletrons**

Cathode-ray Tube Division,
Allen B. Du Mont Laboratories, Inc.,
Clifton, N. J.

*trade mark

You Practice COMMUNICATIONS

I send you parts to build this transmitter

As part of my Communications Course you build this low power broadcasting transmitter, learn how to put a station "on the air," perform procedures demanded of Broadcast Station operators, make many tests.




This is just part of the equipment my students build. You keep all parts I send.

You Practice Radio SERVICING

on this modern radio you build with parts I send

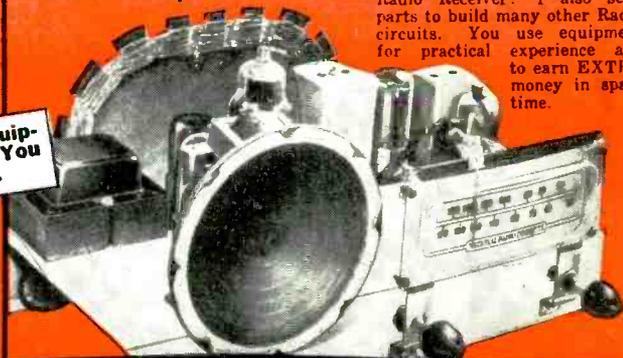As part of my Servicing Course, I send you the speaker, tubes, chassis, transformer, loop antenna. EVERYTHING you need to build this modern, powerful Radio Receiver! I also send parts to build many other Radio circuits. You use equipment for practical experience and to earn EXTRA money in spare time.



BE A RADIO-TELEVISION TECHNICIAN

NOW! Advanced Television Practice

New, special TV kits furnished to build high-definition SCOPE . . . RF OSCILLATOR with flyback power supply . . . complete TV set . . . many other units. You see pulse, trapezoidal, saw-tooth wave forms. Get valuable PRACTICAL EXPERIENCE locating and correcting TV troubles. Mail coupon for facts, pictures and prices!

Learn Servicing or Communications Practice at Home in Spare Time



J. E. SMITH, President National Radio Institute

Do you want good pay, a job with a bright future and security? Would you like to have a profitable shop or store of your own? If so, find out how you can realize your ambition in the fast growing, prosperous RADIO-TELEVISION industry. Even without Television, the industry is bigger than ever before. 90 million home and auto Radios, 21st Broadcasting Stations, expanding use of Aviation and Police Radio, Micro-wave Relay, Two-way Radio for buses, taxis, etc., are making opportunities for Servicing and Communications Technicians and FCC-Licensed Operators.

Television is TODAY'S Good Job Maker

In 1950, over 5,000,000 TV sets sold. By 1954, 25,000,000 TV sets estimated. Over 100 TV Stations now operating. Authorities predict 1,000 TV Stations. This means more jobs, good pay for qualified men all over the United States and Canada.

Many Make \$10 Extra a Week in Spare Time

Keep your job while training. Hundreds of successful RADIO-TELEVISION TECHNICIANS I trained had no previous experience, some only a grammar school education. Learn Radio-Television principles from illustrated lessons. Get PRACTICAL EXPERIENCE—build valuable multimeter—experiment with circuits common to Radio and Television. Keep all equipment. Many students make \$5, \$10 extra a week fixing neighbors' Radios in spare time. SPECIAL BOOKLETS start teaching you the day you enroll.

Send Now For 2 Books FREE—Mail Coupon

Send now for my FREE DOUBLE OFFER. You get actual Servicing lesson to show you how you learn at home. Also my 64-page book, "How to Be a Success in Radio-Television." Read what my graduates are doing, earning; see equipment you practice with at home. Send coupon in envelope or paste on postal. J. E. SMITH, President, Dept. 2CF, National Radio Institute, Washington 9, D. C. Our 38th Year.

I TRAINED THESE MEN



"I have been operating my own Servicing business. In two years I did \$14,000 worth of business; net profit \$6,850. Have me full time employee, an NEI student."—PHILLIP G. BOGAN, Louisville, Ky.



"Four years ago, I was a bookkeeper, with a hand-to-mouth salary. Now I am a Radio Engineer with a key station of the American Broadcasting Company network."—NORMAN H. WARD, Ridgefield Park, New Jersey.



"When halfway through the NRI course, I made \$5 to \$8 a week fixing sets in my spare time. Am now selling and installing Television sets and antennas."—E. J. STREITBERGER, New Boston, O.



"My first job was operator with KDLR, obtained for me by your Graduate Service Dept. I am now Chief Engineer of Police Radio Station WQOX. I never hesitate to endorse NRI."—T. S. NORTON, Hamilton, Ohio.



EXTRA PAY IN ARMY, NAVY, AIR FORCE

Knowing Radio, TV, Electronics can help you get extra rank, extra prestige, more interesting duty at pay up to several times a private's base pay. You are also prepared for good Radio-TV jobs upon leaving service. Mail Coupon TODAY.

Have Your Own Business

Many N.R.I. trained men start their own Radio-Television sales and service business without capital. Let me show you how you, too, can be your own boss, have a good income from your own shop. Send coupon for FREE book now!

Tested Way to Better Pay

Good for Both—FREE

MR. J. E. SMITH, President, Dept. 2CF, National Radio Institute, Washington 9, D. C.

Mail me Sample Lesson and 64-page Book about How to Win Success in Radio-Television. Both FREE. (No Salesman will call. Please write plainly.)

Name.....Age.....

Address.....

City.....Zone.....State.....

Approved for training under G. I. Bill

The ABC's of SERVICING

How to Be a Success in RADIO-TELEVISION

RADIO - ELECTRONICS

Formerly RADIO-CRAFT • Incorporating SHORT WAVE CRAFT • TELEVISION NEWS • RADIO & TELEVISION*

CONTENTS

MARCH 1952

Hugo Gernsback,
Editor-in-Chief

M. Harvey Gernsback
Editorial Director

Fred Shunaman
Managing Editor

Robert F. Scott
W2PWG, Technical Editor

I. Queen
Editorial Associate

Angie Pascale
Production Manager

Wm. Lyon McLaughlin
Tech. Illustration Director

Sol Ehrlich
Art Director

Lee Robinson
General Manager

John J. Lamson
Sales Manager

G. Aliquo
Circulation Manager

Robert Fallath
Promotion Manager

Editorial (Page 21)

Microwave Evolutionby Hugo Gernsback 21

Television (Pages 22-35)

TV Marries the Moviesby Aaron Nadell 22
 TV Conversion Details 24
 Beyond the Fringesby T. W. Morgan and R. J. Buchan 27
 The TV "Service Aid"by Charles G. Buscombe 28
 Everything Does Happen in TV Service 29
 TV Control Troublesby DeLoss Tanner 30
 Pedro and the Incentive Planby Guy Slaughter 32
 TV Service ClinicConducted by Matthew Mandl 34

Audio (Pages 36-42)

Improving Listenabilityby Nathan Grossman 36
 Electronics and Music, Part XXIby Richard H. Dorf 38
 Compact Multi-Purpose Amplifierby John W. Straede 40
 Playback Response Curves 42

Servicing-Test Instruments (Pages 43-53)

Servicing Oscillatorsby Robert M. Field 43
 A Practical Multitesterby William C. Stoecker 44
 Maintaining 2-Way Radioby Hardin G. Stratman 46
 Efficient TV Service in the Customer's Home
 (Cover Story)by W. M. Tomlin 48
 Accent on Space (Service Bench Contest Second Prize) ...by C. J. Whitton 49
 Fix It Yourselfby Eric Leslie 51
 Variable Line Voltageby Phil Hiner 53

Broadcasting & Communications (Pages 54-55)

Operating TV Studio Equipment, Part IIby Harold Ennes 54

Foreign (Pages 58-60)

Automatic 150 KW Stationby T. W. Dresser 58

Electronics (Pages 62-69)

Subminiature Germanium Photodiodesby R. P. Turner 62

New Design (Pages 78-80)

Tubes of the Month 78

Theory and Engineering (Page 83)

Varying the Bandwidthby Wilbur Hantz 83

Amateur (Pages 84-90)

Bandswitching Receiver for the Novice Amateur ...by Homer L. Davidson 84

Construction (Pages 92-107)

Putting New Life in Midget Setsby C. E. Cohn 92
 Sensitive R. F. Voltmeterby A. Stratmoen 95
 A Visual Alarm for Hard of Hearingby Richard H. Houston 97

Departments

The Radio Month .. 8	With the Tech- .. 111	Technotes	122
Radio Business.. 15	nician	Miscellany	123
New Devices .. 70	Radio-Electronic ..	People	130
New Patents ... 108	Circuits	Communications ..	132
Try This One .. 113	Question Box .. 120	Book Reviews ..	135

ON THE COVER:
 Technician Ed Walter, of the RCA Service Company's Bushwick (Brooklyn) branch, adjusts a TV receiver in the customer's home (See P. 48).



MEMBER Audit Bureau of Circulations

RADIO-ELECTRONICS

Published monthly by Radcraft Publications, Inc., at Erie Ave., F to G Streets, Philadelphia 32, Pa.

Vol. XXIII, No. 6

EXECUTIVE, EDITORIAL AND ADVERTISING OFFICES: 25 West Broadway, New York 7, N. Y. Telephone REctor 2-8630. Hugo Gernsback, President; M. Harvey Gernsback, Vice-President; G. Aliquo, Secretary.
SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., Erie Avenue, F to G Sts., Philadelphia 32, Pa., or 25 West Broadway, New York 7, N. Y. When ordering a change please furnish an address stencil impression from a recent wrapper. Allow one month for change of address.
SUBSCRIPTION RATES: In U. S. and Canada, in U. S. possessions, Mexico, South and Central American countries, \$3.50 for one year, \$6.00 for two years; \$8.00 for three years; single copies 30c. All other foreign countries \$4.50 a year, \$8.00 for two years; \$11.00 for three years. Entered as second class matter September 27, 1948 at the post office at Philadelphia, Pa., under the Act of March 3, 1879. Copyright 1952 by Radcraft Publications, Inc. Text and illustrations must not be reproduced without permission of copyright owners.
BRANCH ADVERTISING OFFICES: Chicago: 100 E. Ohio St., Telephone SCenter 7-1796. Los Angeles: Ralph W. Harker, 1127 Wilshire Blvd., Tel. MA 6-1271. San Francisco: Ralph W. Harker, 582 Market St., Tel. GARfield 1-2481. **FOREIGN AGENTS:** Great Britain: Atlas Publishing and Distributing Co., Ltd., London E.C.4. Australia: McGill's Agency, Melbourne. France: Brentano's, Paris 2e. Holland: Trilectron, Heemstede. Greece: International Book & News Agency, Athens. So. Africa: Central News Agency, Ltd., Johannesburg. Capetown; Durban, Natal. Universal Book Agency, Johannesburg. Middle East: Steimatzy Middle East Agency, Jerusalem. India: Broadway News Centre, Dadar, Bombay #14, K. L. Kannappa Mudaliar, Madras 2. Pakistan: Paradise Book Stall, Karachi 3.
POSTMASTER: If undeliverable send form 3578 to: RADIO-ELECTRONICS, 25 West Broadway, New York 7, N. Y. *Trademark registered U.S. Patent Office.

RADIO-ELECTRONICS

TRAIN for Security! Good-Paying Jobs!

MAKE THE MONEY YOU'VE ALWAYS DREAMED OF!



LEARN RADIO -TELEVISION AND ELECTRONICS BY EASY SHOP METHOD TRAINING AT HOME!

You get all the parts—even tubes!—for this modern Superheterodyne Receiver. You learn to build it step by step. And you keep it! Get all the facts. Mail coupon now.

Let **NATIONAL SCHOOLS**—a resident-training school for nearly 50 years—train you at home for today's unlimited opportunities in Radio-Television-Electronics. National Schools is one of the largest schools of its kind. It is located in Los Angeles—the center of Radio and TV world! It has four large buildings of modern shops and labs. Its faculty is considered tops in the business.



You learn from lessons prepared by experienced instructors and engineers. Men who are successful Radio and Television technicians. Men who have trained 1000's of men like YOU!



FREE BOOK TELLS YOU HOW!

Page after page—in color—tells you everything you want to know. Mail the coupon. Get this valuable book today. And if you hurry—YOU GET A FREE SAMPLE LESSON, TOO! Shows how easy National Schools Home Training is. Mail the coupon today.

You Train At Home—In Your Spare Time

National Schools Shop Method Home Training gives you basic and advanced instruction in all phases of Radio-TV-Electronics. And remember—your training is based on resident school training principles. You learn fast from hundreds of diagrams and pictures. All instructions are written by experienced technicians who work in Radio and TV every day. All instructions have been developed and tested in National Schools' own labs and studios, which are equipped with the latest RCA equipment. No wonder this National Schools course is so up-to-date, practical, interesting. And so easy to learn! And no wonder it is held in such high regard by leaders of American industry! Approved for eligible Veterans.

We Teach You How To Make Welcome Extra Money—While You Learn!

Many National Schools students—men like you—make plenty of extra dollars each week in spare time! Fixing neighbors' radios, appliances—and other ways we teach you. You start learning and earning from the day you enroll. From the very first lesson!



Only National Schools Gives You This Professional Multi-Tester!

You get this amazing, new testing instrument—factory-made and tested—complete—ready to use! Simple to operate. Accurate and dependable. An instrument every Radio-TV man needs. Light enough to carry around—so you can use it at home or on service calls. You'll be proud to own this valuable equipment.

Here are only a Few of the Good-Paying Jobs You Can Choose

Radio Station Engineer, District Service Manager, Aircraft Radio Inspector, Own Your Own Repair Shop, Inspector Technician, Service Specialist, Special Government Jobs, Complete TV Service, Sound Truck Operator. Many more! National Schools graduates have secure, good-paying jobs like these! So don't wait—mail the coupon today. Now—while you're thinking about it!

WE SEND YOU LOTS OF PARTS LIKE THIS!



With National Schools Shop Method Home Training, you get basic principles and plenty of practical training. You learn by doing. No wonder you learn so fast! We send you many parts—all of professional, modern quality. You do lots of practical experiments. You advance day by day, step by step. Until you can even build the modern Superheterodyne Receiver you see above—plus other important testing units. The free book tells you all about it. The free sample lesson shows how easy the training is. Use the coupon. Send today—without fail!

Today's Shortage of Trained Technicians Creates Chance of a Lifetime For You!

Think of it! With guided missiles, radar, and other electronic devices so important to national defense! With big, new developments in TV. With over 90,000,000 home and auto radios, over 12,000,000 TV sets. With more than 3100 radio stations...over 100 TV stations—and more building every day...yes, imagine the great opportunity you have today!

YOU are wanted in Radio-Television-Electronics! America's fastest-growing field. High-pay jobs—the kind you've always wanted—are waiting for YOU!

Job Security! Big Money! For YOU! in Today's Expanding Industries!

Trained Radio and Television technicians really make important money these days. Thousands of National Schools graduates—men just like you—are earning good money all over the country. Why not you? And—National Schools graduates get the personal satisfaction of being highly-skilled technicians. Men people respect. Men who enjoy their work—rather than having to drag along in just any old job.

National Schools Has Trained 1000's of Successful Men! Why Not YOU?

In almost every state—and many foreign countries—National Schools graduates are filling big jobs with famous companies. Or running their own successful businesses. What are YOU waiting for? National Schools training is complete training. So when you graduate you can take advantage of today's big opportunities in Radio-Television-Electronics—fast.

DON'T PUT IT OFF! GET THE BIG SALARY YOU HAVE ALWAYS WANTED!

Attention! Men Going into Service Soon!

National Schools' course quickly prepares you for many important jobs in the Armed Services. With National Schools Training you have an opportunity to get into special service classifications—with higher pay and grade—immediately!

FREE SERVICE FOR GRADUATES

National Schools uses its great influence and prestige to help you find your place in the field of your choice. Don't put it off! Start yourself toward a skilled trade! Get the big pay you've always wanted!

NATIONAL SCHOOLS

LOS ANGELES 37, CALIFORNIA • ESTABLISHED 1905

MAIL THIS COUPON TODAY—WITHOUT FAIL!

NATIONAL SCHOOLS, Dept. GR-32
4000 South Figueroa Street
Los Angeles 37, California

Mail in envelope or paste on penny post card.

Mail me FREE the book mentioned in this ad. Also a free sample lesson. I understand no salesman will call on me.

NAME _____ AGE _____

ADDRESS _____

CITY _____ ZONE _____ STATE _____


Check here if you were released from the Service less than 4 years ago.

Be Sure of Your Installations

Get the *Aptitude-Tested*
**RG/U TRANSMISSION
 LINE CABLES**

• You know what you are doing when you use Belden RG/U Transmission Line Cables—they're aptitude rated. They are designed to provide desirable electrical characteristics, and rigid control assures constant quality. Specify Belden Radio Wires.

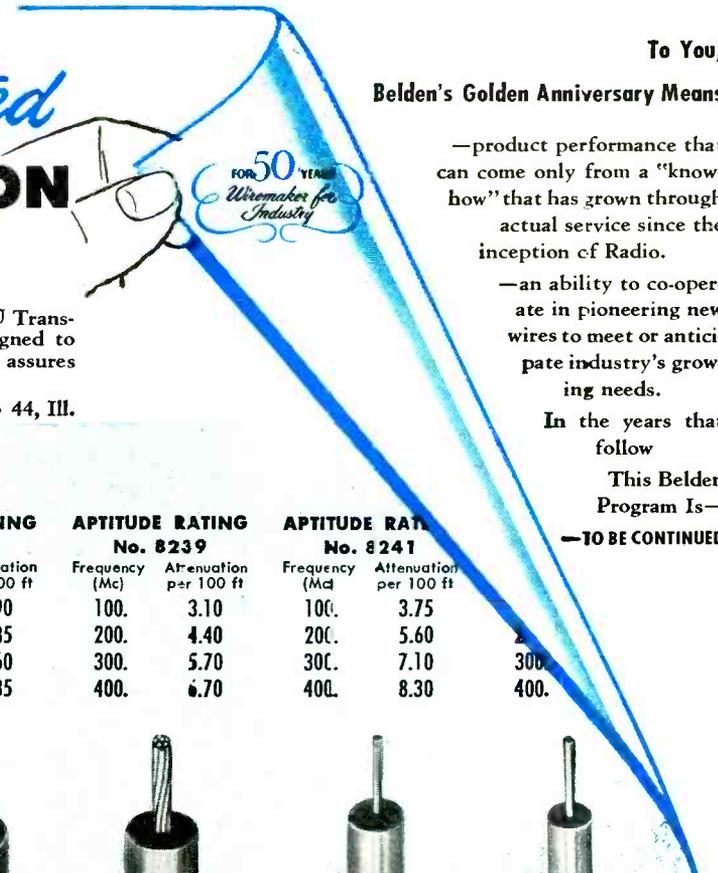Belden Manufacturing Co., 4623 W. Van Buren St., Chicago 44, Ill.



To You,

Belden's Golden Anniversary Means

—product performance that can come only from a "know-how" that has grown through actual service since the inception of Radio.

—an ability to co-operate in pioneering new wires to meet or anticipate industry's growing needs.

In the years that follow

This Belden Program Is—


—TO BE CONTINUED

APTITUDE RATING No. 8236		APTITUDE RATING No. 8237		APTITUDE RATING No. 8238		APTITUDE RATING No. 8239		APTITUDE RATING No. 8241	
Frequency (Mc)	Attenuation per 100 ft								
100.	2.65	100.	2.10	100.	1.90	100.	3.10	100.	3.75
200.	3.85	200.	3.30	200.	2.85	200.	4.40	200.	5.60
300.	4.80	300.	4.10	300.	3.60	300.	5.70	300.	7.10
400.	5.60	400.	4.50	400.	4.35	400.	6.70	400.	8.30



Belden
Radio WIRE

The *Aptitude-Tested* **LINE**

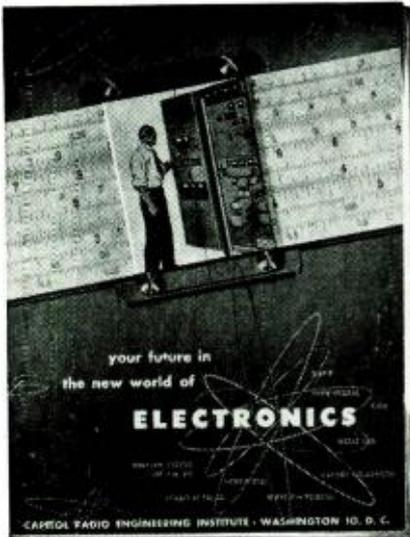

*How far ahead can you be
next year . . .*

IN TV AND ELECTRONICS?

◀ **Send for this free CREI booklet today...
and find out!**

T HIS BOOKLET can mean the difference between small, w-i-d-e-l-y s-p-a-c-e-d salary increases—and rapid advancement. Between routine work—and challenging opportunity. Between constantly defending your job against better-trained men—and dynamic confidence. Between short-circuited hopes—and high-powered ambition.

An exciting new world has opened up with such super-speed that even the most optimistic electronic experts fall short in their predictions of expansion.

Think of the 1,500 TV stations within the next 5 years and the 2,500 stations within 10 years, as predicted by the Chairman of the FCC. Think of the 14,496,000 TV sets now in use. *Remember that we weren't supposed to reach that figure until 1954.* Think of the 100,000,000 radios in current operation. (95% of the nation's homes have one or more sets.) Think of the tremendous defense orders now being placed for electronic equipment and installations.

Think of the thousands of radio-equipped fire and police departments throughout the U.S. Of the many radio-equipped railroads, of the hundreds of cities with 2-way radio service for cars and cabs. Think of the wide-ranging field of aviation communications—radio-controlled aircraft, navigation-and-traffic control, airport stations.

Think of the maritime world with its navigational aids, fathometers, ship-to-shore and ship-to-ship communications and radar. Think of electronic heating, fax and ultra-fax, of electronic medicine, and all the other applications of electronic know-how.

Countless positions must be filled—in development, research, design, production, testing and inspection, manufacture, broadcasting, telecasting and servicing. Who will get those positions? You—if you prepare today—if you are alert and have the ambition to advance your knowledge. You—if you take 2 minutes to send for a free copy of "Your Future in the New World of Electronics."

This helpful book shows you how CREI Home Study leads the way to greater earnings through the inviting opportunities described above.

However, being an accredited technical school, CREI does not promise you a "bed-of-roses." You have to translate your willingness to learn into saleable technical knowledge

—via *study*. Since its founding in 1927, CREI has provided thousands of professional radiomen with technical educations. During World War II, CREI trained thousands for the Armed Services. Leading firms choose CREI courses for group training in electronics at company expense, among them United Air Lines, Canadian Broadcasting Corporation, Trans Canada Airlines, Sears Roebuck & Co., Bendix Products Division, All-American Cables and Radio, Inc., and RCA-Victor Division.

CREI courses are prepared by recognized experts, in a practical, easily-understood manner. You get the benefit of time-tested materials, under the personal supervision of a CREI Staff Instructor. This complete training is the reason why CREI graduates find their diplomas keys-to-success in Radio, TV and Electronics. CREI alumni hold top positions in America's leading firms.

At your service is the CREI Placement Bureau, which finds positions for students and graduates. Although CREI does not guarantee jobs, requests for personnel currently exceed supply by far.

Talk to men in the field and check up on CREI's high standing in electronics instruction. Determine for yourself right now that your earnings are going to rise with your knowledge—and that you get your rightful place in the Age of Electronics. All this CREI can promise you, provided you sincerely want to learn. Fill out the coupon and mail it today. We'll promptly send you your free copy of "Your Future in the New World of Electronics." The rest—the future—is up to you.

MAIL COUPON FOR FREE BOOKLET

CAPITOL RADIO ENGINEERING INSTITUTE

Dept. 143D, 16th & Park Rd., N.W., Washington 10, D. C.

Send booklet "Your Future in the New World of Electronics" and course outline.

CHECK FIELD OF GREATEST INTEREST } TV, FM & Advanced AM Servicing Aeronautical Radio Engineering
 Practical Television Engineering
 Broadcast Radio Engineering (AM, FM, TV)
 Practical Radio Engineering

Name.....

Street.....

City..... Zone..... State.....

If residence school in Wash., D. C. preferred, check here

It's
Tung-Sol
for radio
and tv



Quality

-that keeps pace with the growth of the electronic industry

Quality

-that meets fully the performance requirements of all radio and tv set manufacturers

Quality

-that safeguards dealer service work

TUNG-SOL ELECTRIC INC.

Newark 4, N. J.

Sales Offices: Atlanta • Chicago • Culver City (Calif.) • Dallas • Denver • Detroit • Newark

Tung-Sol makes all-glass sealed beam lamps; miniature lamps; signal flashers; cathode ray, radio, TV and special purpose electron tubes.

TUNG-SOL

RADIO, TV TUBES, DIAL LAMPS

HIDDEN VALLEY is at last to receive the benefits of "hidden valley" television. The valley with the name so familiar to persons interested in TV distribution systems is located near Lafayette, California, and is to receive signals via an antenna on an 800-foot hill in full range of signals from the San Francisco area.

Jerrold community antenna equipment will be used to bring the signals from the hilltop tower to viewers in Hidden Valley and the adjacent Acalanes Valley. The signals will be boosted on leaving the antenna, and again after being piped 2,200 feet through coaxial cable to the floor of Hidden Valley.

An interesting feature of the project is that cables will run underground instead of overhead, as is more common in such installations.

TV BROADCASTING IN BRAZIL

has been reinforced by a new 5-kilowatt station operating on Channel 5 in Sao Paulo, "the Chicago of South America." The station services an estimated 20,000 TV sets in the Sao Paulo area and is housed in a new 12-story building on Avenida Reboucas 62 overlooking the residential section.

A portable TV microwave link and equipment for the station, owned and operated by Radio Televisao Paulista, S.A., was supplied through International Standard Electric Corporation, New York, an associate of the International Telephone and Telegraph Corporation.

A COLOR TELECAST linking Los Angeles, Chicago and New York over a closed circuit, lasting for one hour, enabled hundreds of doctors to watch a delicate operation performed at the Los Angeles County Hospital. This first transcontinental color telecast was sponsored by the Columbia Broadcasting System laboratories division and Smith, Kline and French, a Philadelphia pharmaceutical concern.

Doctors said the colors of nerves and tissues were accurately transmitted. At the American Medical Association convention, Dr. John W. Cline, president, said that the telecast was a "milestone" in helping isolated practitioners.

TAPE RECORDING network for the benefit of sick and disabled veterans in VA hospitals has proved to be an excellent morale-booster. Tape records of special programs by nationally known entertainers and celebrities visiting a hospital are circulated among the 50 or so member hospitals of the network. Presentations written, acted and directed by talented veteran-patients have been recorded and circulated and enjoy a wide popularity. Patients confined to their beds listen to the programs over receiving units placed right by the pillows.

PILFERAGE of television parts and equipment was held to be one of the main causes of the dramatic failure of Conlan Electric of Brooklyn. The firm declared itself in bankruptcy in January. It held more than 20,000 television service contracts.

Less dramatic but possibly more significant was the statement made by the company's attorney, Nathan Korn, that the financial difficulties resulted almost entirely from the television installation and service contract phase of the firm's activities. Other activities of the 48-year-old firm have always made a profit, but losses on TV contracts were too great to be absorbed by the other branches of the business, he said.

Of the 20,000 contracts, more than 17,000 are bonded, according to Mr. Korn. It is expected that with the co-operation of the bonding companies, a new organization may be formed to service these and possibly the other 3,000 sets covered by unexpired contracts.

"TV ATTENDANCE" is greater in actual time than schoolroom attendance, according to a survey of sixth and seventh grade school children conducted by Xavier University, Cincinnati, Ohio, in co-operation with the Crosley Broadcasting Corporation. The study of 998 children revealed that the average pupil spends 30 hours a week watching TV as compared with 25 hours spent in school.

There was no appreciable difference in the school work of children with TV sets at home compared with those not having TV sets. The child whose television habits are controlled by parents (not as common as originally believed) did not manifest superior scholarship to the uncontrolled child.

Since the report was concerned only with the present complexion of TV programs—recreational—there was no implication drawn concerning special TV programs designed to aid learning.

The report showed that the children in TV homes had a later bedtime, and that children with lower IQ's were avid watchers of mystery-crime and wrestling programs.

AN ALUMINUM SHEATH is used in a new type of coaxial cable which is cheaper and, reportedly, more efficient than that usually used for microwave transmission. The applications to remote pickup TV transmission lines are held promising.

The aluminum pipe is made by a new continuous extrusion process invented by Heinz Horn of Cologne and further developed in Germany. The cable already is used in 150 installations in Europe and is being marketed in this country by the Phelps Dodge Copper Products Corporation under agreement with the Cologne manufacturers.

IRE'S NATIONAL CONVENTION and Radio Engineering Show will be held in New York City, March 3rd through 6th. Convention headquarters will be at the Waldorf-Astoria Hotel. The Show has been expanded to include four floors of exhibits at the Grand Central Palace. Over 350 exhibitors will occupy booth space. RADIO-ELECTRONICS will again have a display at Booth S-2 on the mezzanine floor.

Charles E. Wilson, Director of Defense Mobilization, will be the guest speaker at the annual banquet.

RADIO-ELECTRONICS


**NOW... GET EVERYTHING YOU
NEED TO LEARN AND MASTER
TELEVISION
RADIO-ELECTRONICS
...AT HOME!**

**Use REAL commercial-type equip-
ment to get practical experience**

Your future deserves and needs every advantage you can give it! That's why you owe it to yourself to find out about one of the most COMPLETE, practical and effective ways now available to prepare AT HOME for America's billion dollar opportunity field of TELEVISION-RADIO-ELECTRONICS. See how you may get and keep the same type of basic training equipment used in one of the nation's finest training laboratories... how you may get real STARTING HELP toward a good job or your own business in Television-Radio-Electronics. Mail the coupon today for complete facts — including 89 ways to earn money in this thrilling, newer field.

D.T.I., ALONE, INCLUDES BOTH MOVIES and HOME LABORATORY In addition to easy-to-read lessons, you get the use of HOME MOVIES — an outstanding training advantage — plus 16 big shipments of Electronic parts. Perform over 300 fascinating experiments for practical experience. Build and keep real commercial-type test equipment shown at right

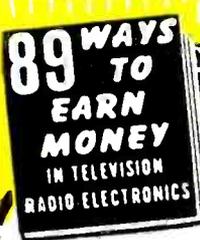**Get BOTH of these
information packed
publications FREE!**



MODERN LABORATORIES
If you prefer, get all your preparation in our new Chicago Training Laboratories—one of the finest of its kind. Ample instructors, modern equipment. Write for details!

MILITARY SERVICE!
If you're subject to military service, the information we have for you should prove very helpful. Mail coupon today.

ACT NOW! MAIL COUPON TODAY!

DE FOREST'S TRAINING, INC., Dept. RE-3-1
2533 N. Ashland Ave., Chicago 14, Ill.

Without obligation, I would like your Opportunity News Bulletin showing "89 Ways to Earn Money in Television-Radio-Electronics"; also, the folder showing how I may prepare to get started in this thrilling field.


Name.....Age.....
Address.....Apt.....
City.....Zone.....State.....

ABOVE: Build and keep a real 17 INCH commercial TV receiver. Optional after completing regular training at moderate added cost.



17 INCH TUBE

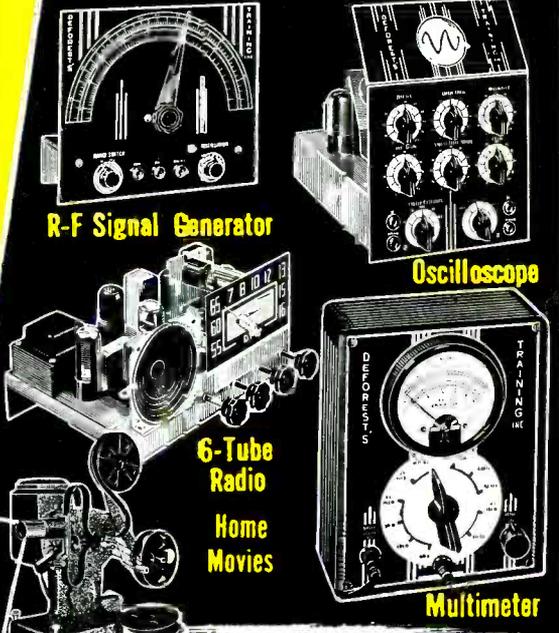**Here's the
REAL THING!
SET UP YOUR OWN
HOME LABORATORY**



R-F Signal Generator

Oscilloscope

**6-Tube
Radio
Home
Movies**


Multimeter

**"ONE OF AMERICA'S FOREMOST
TELEVISION TRAINING CENTERS"**

De FOREST'S TRAINING, INC.
CHICAGO 14, ILLINOIS
A DeVRY INSTITUTION

The New Astatic "TWIN CAC"

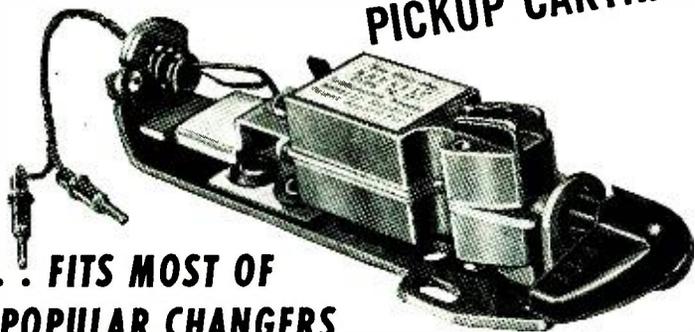THE INDUSTRY'S FIRST MAJOR ADVANCEMENT IN TURNOVER TYPE PICKUP CARTRIDGES



... FITS MOST OF
THE POPULAR CHANGERS

INTERACTION between the two needles has long reduced the performance quality of conventional designs in turnover pickup cartridges. Another difficulty has been that, if output and response characteristics are made ideal on one side, for one record type, reproduction on the other side is poor; so a compromise has to be made. It took a revolutionary new design in turnover cartridges to eliminate these problems . . . and that is exactly what Astatic engineers have come up with. The new "Twin CAC," Astatic cartridge model CAC-D-J, is the first turnover unit offering unlimited reproduction clarity, fidelity and brilliance of tone. It is the equal of the finest single-needle cartridge of them all, Astatic's own famous CAC-J.

LIST PRICE \$10.50

Code ASXDJ

FEATURES

- 1 Basic design principle combines two complete CAC assemblies, back to back, on a common plate.
- 2 Output and response characteristics of each side established independently of the other: 0.8 volt at 1 kc. on Audiotone 78-1 Test Record and 0.7 volt on RCA 12-5-31-V Test Record. Frequency range, 30 to 11,000 cycles.
- 3 Needles are, of course, entirely independent of each other, free of interaction. Needle pressure, 10 grams.
- 4 Unique but simple switching device in turnover mechanism connects only the cartridge or side being used to amplifier phonograph input.
- 5 Furnished complete with turnover bracket and knob assembly, with standard 1/2" mounting holes. Wiring terminating in pin connectors, graduated for two dimensions now standard on lead wire connectors. Easily installed without soldering.
- 6 Equipped with Type Q (3-mil) and Type Q-33 (1-mil), sapphire tipped needles.

Write for complete details on the new Astatic "TWIN CAC" turnover cartridge. Ask also about the three new Astatic Pickup Models now available complete with this superb new cartridge.

EXPORT DEPARTMENT
401 Broadway, New York 13, N. Y.
Cable Address: ASTATIC, New York



MISLEADING TV SET ADS are expected to be curbed by the plan set forth by the Better Business Bureau of New York City. The plan, also affecting home appliances, implements the enforcement of the advertising and selling standards adopted by the trade over 18 months ago. A five-man, industry advisory panel consisting of three TV and appliance advertisers, one non-advertiser and one wholesale distributor will review advertising practices with the bureau and conduct hearings when an advertiser disputes a BBB charge of violation of the standards.

An advertiser whose copy is considered in violation of the standards will be notified by registered mail and requested to give written assurance within 72 hours that it will be discontinued. It places responsibility on the advertiser to substantiate with proof any advertised claims deemed questionable. Further action could mean publicity and referral to law-enforcement authorities.

FARSIGHTED ENTERPRISE has been shown by the Capitol Appliance Co. of Boise, Idaho, in advertising the sale of 161 nationally known, quality brands, traded-in TV sets. The prices quoted ranged from \$1 up for table models, \$3 up for consoles, and \$10 up for radio-phonograph-TV combinations!

Since Boise is far from the nearest TV station, there may have been some question in the minds of the residents as to what they could do with the 161 used sets from Salt Lake City, Utah. The ad settled this natural query by stating that when TV *does* come to Boise the advertiser will allow the full purchase price of the traded-in set as a trade-in allowance on a new TV set.

The ad resulted in "a lot of interest and a few sales."

A £50,000 AWARD, tax free, was made to Sir Robert Watson-Watt, president of Britain's Royal Meteorological Association and the Institute of Navigation, for his pioneer work in developing radar before and during World War II. Nine of his research associates are to receive an additional £37,900 government award. In a joint claim last year, the ten stated that "without radar the Battle of Britain would have been lost and these islands invaded."

This prize is the largest since 1948 when Sir Frank Whittle received £100,000 for inventing the jet engine.


1952 ELECTIONS AND TV will be closely linked, according to statements by David Sarnoff, and Dr. Allen B. Du Mont. General Sarnoff indicated that TV has a great destiny in providing "an open forum in which every home has a front-row seat in the discussion of national and international problems." Dr. Du Mont believed that television's quality of honesty in separating the wheat from the chaff had its effect in recent elections. He indicated that it is up to the candidates to use television's "unerring ability to distinguish the demagogue from the statesman."

—end—

RADIO-ELECTRONICS



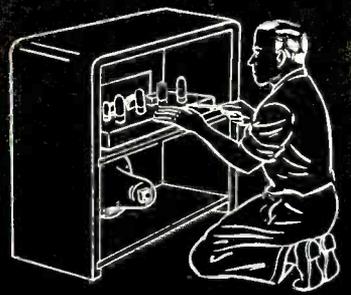Where Will You be
in **ELECTRONICS**
6 Months from Today?



ADD TECHNICAL TRAINING TO YOUR PRACTICAL EXPERIENCE

GET YOUR FCC LICENSE IN A HURRY!

Then use our Amazingly Effective
JOB-FINDING SERVICE

Get this Valuable Booklet **FREE**



TELLS HOW YOU CAN GET A
FREE TELEVISION ENGINEERING COURSE

TELLS HOW —

WE GUARANTEE
TO TRAIN AND COACH YOU AT HOME
IN SPARE TIME UNTIL YOU GET
YOUR FCC LICENSE

If you have had any practical experience—Amateur, Army, Navy, Radio repair, or experimenting.

TELLS HOW —

Employers make
JOB OFFERS like These
to Our Graduates Every Month

Letter, October 11, 1951, from Chief Engineer, Broadcast Station, North Carolina. "Need men with radiotelephone 1st class license, no experience necessary. Will learn more than at average station for we are equipped with Diesel Electric power, transmitting and studio equipment."

Telegram, October 2, 1951, from Chief Engineer, Broadcast Station, Wyoming. "Please send latest list available first class operators. Have November 10th opening for two combo men."

These are just a few examples of the job offers that come to our office periodically. Some licensed radiomen filled each of these jobs . . . it might have been you!

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR Coaching AT HOME in Spare Time.

Name and Address	License	Lessons
Lee Worthy, 2210 1/2 Wilshire St., Bakersfield, Calif.	2nd Phone	16
Clifford E. Vogt, Box 1016, Dania, Fla.	1st Phone	20
Francis X. Foerch, 38 Beucler Pl., Bergenfield, N. J.	1st Phone	38
Sgt. Ben H. Davis, 317 North Roosevelt, Lebanon, Ill.	1st Phone	28
Albert Schoell, 110 West 11th St., Escondido, Calif.	2nd Phone	23

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RE-39, 4900 Euclid Bldg., Cleveland 3, Ohio

MARCH, 1952

TELLS HOW —

Our Amazingly Effective
JOB-FINDING SERVICE
Helps CIRE Students Get Better Jobs
Here are a few recent examples of Job-Finding results:

GETS JOB WITH CAA

"I have had a half dozen or so offers since I mailed some fifty of the two hundred employment applications your school forwarded me. I accepted a position with the Civil Aeronautics Administration as a Maintenance Technician. Thank you very much for the fine cooperation and help your organization has given me in finding a job in the radio field."

Dale E. Young, 122 Robbins St., Owosso, Mich.

GETS FIVE JOB-OFFERS FROM BROADCAST STATIONS

"Your 'Chief Engineer's Bulletin' is a grand way of obtaining employment for your graduates who have obtained their 1st class license. Since my name has been on the list I have received calls or letters from five stations in the southern states, and am now employed as Transmitter Engineer at WMMT."

Elmer Powell, Box 274, Sparta, Tenn.

GETS CIVIL SERVICE JOB

"I have obtained a position at Wright-Patterson Air Force Base, Dayton, Ohio, as Junior Electronic Equipment Repairman. The Employment Application you prepared for me had a lot to do with me landing this desirable position."

Charles E. Loomis, 4516 Genesee Ave., Dayton, Ohio.

OURS IS THE ONLY HOME STUDY COURSE WHICH SUPPLIES FCC-TYPE EXAMINATIONS WITH ALL LESSONS AND FINAL TESTS.

Your FCC Ticket is recognized in all radio fields as proof of your technical ability.



Get All 3 FREE

MAIL COUPON NOW

CLEVELAND INSTITUTE OF RADIO ELECTRONICS
Desk RE-39—4900 Euclid Bldg., Cleveland 3, Ohio
(Address to Desk No. to avoid delay)

I want to know how I can get my FCC ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examinations" (does not cover exams for Amateur License), as well as a sample FCC-type exam and the amazing new booklet, "Money-Making FCC License Information."

Tell me how I can get your Free Television Course.

Name

Address

City Zone State

Paste on penny postcard or send air mail.

What
kind
of
men?



What kind of men are the 2500 scientists and engineers of Bell Telephone Laboratories?

They are men of many types, yet they work well together, for all have good minds as a foundation, years of study in the fundamentals of their science and in the methods of research and design. Vital, too, is their teamwork — for without the co-operation of many individuals the products of research and development could never be perfected.

Above all else these men have “the spirit to adventure, the wit to question, and the wisdom to accept and use.”

Such men can develop the world’s finest telephone systems — and have done so.

Perhaps there is a place among them for you. Write the Employment Director, Bell Telephone Laboratories, New York 14.




BELL TELEPHONE LABORATORIES

• EXPLORING AND INVENTING, DEVISING AND PERFECTING FOR CONTINUED IMPROVEMENTS AND ECONOMIES IN TELEPHONE SERVICE

RADIO-ELECTRONICS

the only complete catalog
for everything in Radio,
TV & Industrial Electronics

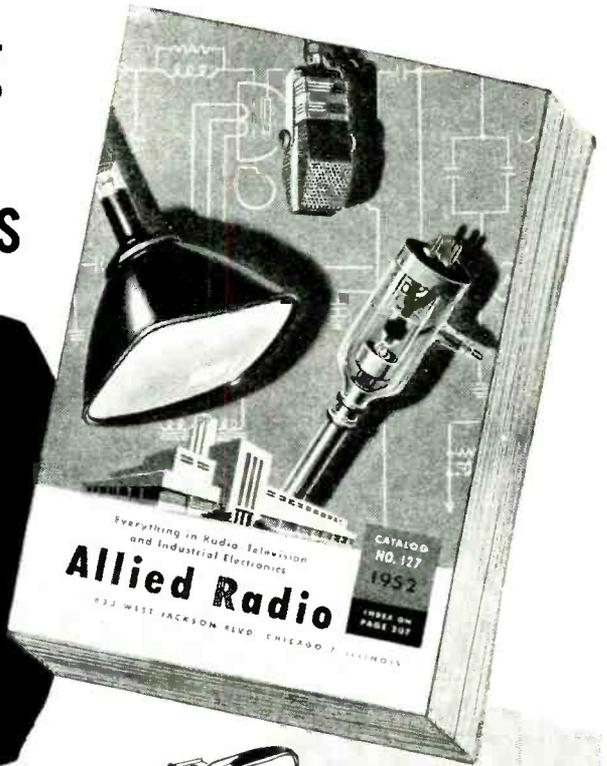
your 1952 **free!**
ALLIED 212-page
value-packed catalog




Send for it today!

Here's the *one* authoritative, complete, up-to-date Buying Guide to TV, Radio and Industrial Electronics. Make your selections from the world's largest stocks of quality equipment at lowest, money-saving prices. See the latest and most complete presentation of electronic apparatus: new TV, AM and FM receivers; High-Fidelity Custom Sound components; latest P.A. Systems and accessories; recorders; fullest selections of Amateur receivers and station gear; specialized industrial electronic equipment; test instruments; builders' kits; huge listings of parts, tubes, tools, books—the world's *most complete stocks* of quality equipment.

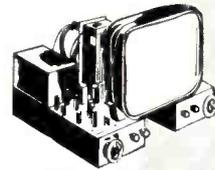ALLIED gives you *every* buying advantage: speedy delivery, expert personal help, lowest prices, liberal time payment terms, assured satisfaction. Get the latest 1952 ALLIED Catalog. Keep it handy—and save time and money. Send for your FREE copy today!



**the world's
largest stocks**

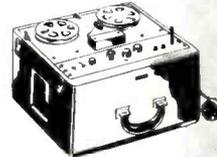

- Radio Parts Unlimited
- Test Instruments
- Television & Home Radios
- P.A. and Hi-Fi Equipment
- Amateur Station Gear
- Builders' Supplies
- Equipment for Industry



quick, expert service



ALLIED IS YOUR TV and HI-FI HEADQUARTERS

TV **HI-FI**

Count on ALLIED for the latest in TV! If it's made—we have it for quick delivery. We specialize, too, in High-Fidelity sound components—everything in amplifiers, speakers, tuners, phono gear and accessories. For TV or Hi-Fi—think of ALLIED!



free

**SEND TODAY FOR RADIO'S
LEADING BUYING GUIDE**

ALLIED RADIO

the World's Largest Radio Supply House

EVERYTHING IN ELECTRONICS


**ALLIED RADIO CORP., Dept. 2-C-2
833 W. Jackson Blvd., Chicago 7, Illinois**

Send FREE 212-page 1952 ALLIED Catalog No. 127.

Name _____

Address _____

City _____ Zone _____ State _____

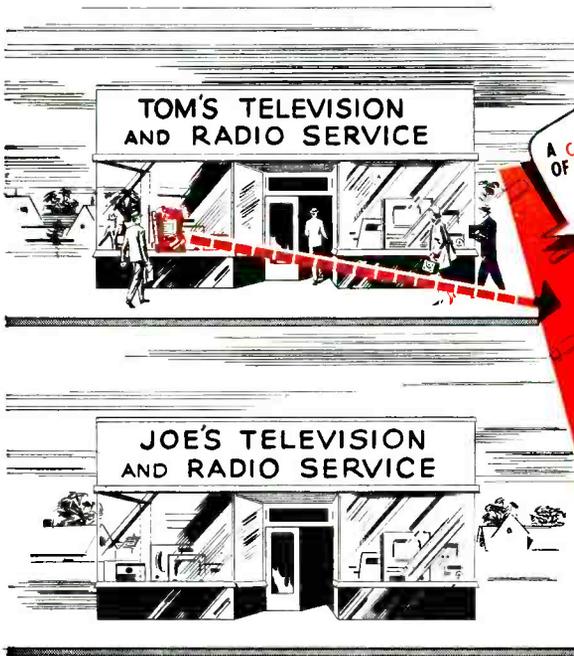


A CASH BOND OF PROTECTION for You!

To Guarantee Efficient Operation, Reliability and Good Repair Work.

- THIS REPAIR SHOP IS BONDDED...**
- 1 Guarantee all radio and television repair work for 90 days.
 - 2 Use only parts of recognized quality.
 - 3 Charge not over established prices for parts.
 - 4 Test customers' tubes as accurately as possible.
 - 5 Keep labor charges at a reasonable level.
 - 6 Perform only such work as is necessary.
 - 7 Maintain proper equipment for good repair work.
 - 8 Maintain high quality service.



Right for Sound and Sight

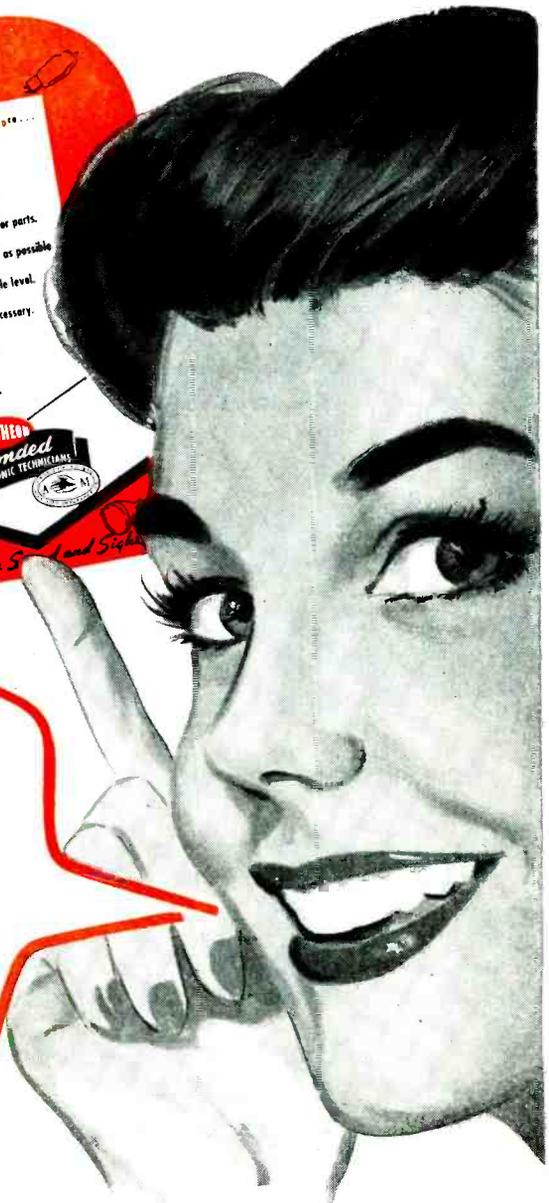

"Here's why Tom gets my service business!"

Today's wary customers want to know *how you do business* as well as *how capable a technician you are*. That's why thousands of Radio and Television Service Dealers across the nation are discovering that, all other things being equal, their status as RAYTHEON Bonded Electronic Technicians tips the scales in their favor.

If you don't know how this exclusive Raytheon Bonded Program builds customer confidence and good will by cash-protecting your radio and television service 90-day guarantee, *at no cost to you*, you'd better get in touch with your Raytheon Tube Distributor. He'll be happy to tell you whether you can qualify for this important sales aid.



RIGHT... FOR SOUND AND SIGHT



RAYTHEON MANUFACTURING COMPANY

Receiving Tube Division

Newton, Mass., Chicago, Ill., Atlanta, Ga., Los Angeles, Calif.

Excellence in Electronics

RECEIVING AND PICTURE TUBES • RELIABLE SUBMINIATURE AND MINIATURE TUBES • GERMANIUM DIODES AND TRANSISTORS • RADIAC TUBES • MICROWAVE TUBES

RADIO-ELECTRONICS

Merchandising and promotion

Allen B. Du Mont Laboratories, Cathode-Ray Tube Division, Clifton, N. J., issued a new weatherproof three-color decalcomania for use in store windows,



truck panels, etc. The decals are available to distributors, dealers, and service technicians.


General Electric's Tube Department is conducting a mail survey of radio and TV service technicians. Upon completion of the survey, G-E will tabulate the information and supply it to service technicians so that they may compare their operations with those of others in the servicing industry. The Tube Department also announced that its recent "Hit the Trail" sales promotion campaign directed to distributor personnel was one of the most successful in its history.

Brach Mfg. Corp., Newark, N. J., launched a TV lecture program in cooperation with its TV parts distributors for the benefit of TV service technicians throughout the country. The illustrated lectures are given by Ira Kamen, Brach director of TV sales, on the subjects: "TV Antennas and Installations" and "Making Profitable Master TV Antenna Installations." Brach also announced the publication of a jobber-dealer booklet, "How to Sell Brach Products," covering the company's complete line.

Sprague Products Co., North Adams, Mass., developed a new "Service Package" system which, it states, makes it easy for service technicians to carry complete stocks of the proper replacement capacitors for the brand of TV sets they most frequently service. Each of 22 of the most popular makes of TV sets are represented in the "Service Package" system.

Jensen Industries, Inc., Chicago, released a mailing piece describing the sales aids it issues backing its line of phonograph needles.

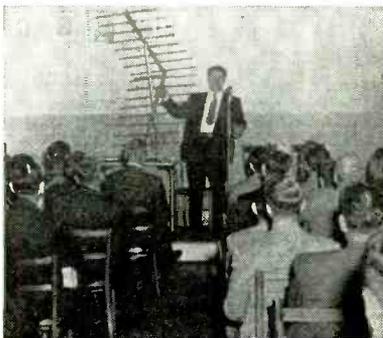Radio Merchandise Sales, Inc., (RMS) New York City, is continuing its series



MARCH, 1952



PERMOFLUX ROYAL EIGHT" WITH THE FAMOUS BLUE CONE

Permoflux ROYAL EIGHT"

Balanced
tone

... from the flashing sunlight of Mozart to the storm of Shostakovich

AUDIOPHILES the country over acclaim the clean, brilliant, life-like musical reproduction of the Permoflux Royal Eight"...the 8" Speaker comparable to any 12"! Combined with the new Permoflux Corner Baffle, Model CB-8-M, the Royal Eight" re-creates original programs with even superior sensitivity and fidelity—every instrument in full-range tonal balance. Here's Big Speaker Performance in a small, easy-to-install frame at a sensible price. (\$22.50 List, less Baffle).

See your Radio Parts Distributor or write to Permoflux today for full information about the complete Royal Blue Line of 6" to 15" Speakers and Baffle Combinations. Ask for Permoflux Catalog -202.

"Sound in Design!... Sound in Price!"
PERMOFLUX CORPORATION 4912-A W. GRAND AVE., CHICAGO 39, ILL.
236 S. VERDUGO RD., GLENDALE 5, CALIF.

Canadian Licensee—Campbell Mfg. Company, Toronto, Canada

**"I'm tough and rugged.
but the SWEETEST mike you ever owned!"**



TOUGH?

Yes, the Turner Model 99 Dynamic is the greatest mike in the world for taking hard knocks...yet retains the perfect response and sensitivity that make the 99 an outstanding microphone value.

Indoors or outdoors — for ham rig, broadcast remotes, sound installations — the Turner 99 is completely dependable. For mobile public address systems, paging systems, communications or recording machines, the 99 delivers crisp, clear results. Its smooth response is not affected by heat, cold or humidity.

Specify the Turner Model 99 Dynamic microphone with confidence. Use it with pride. Order from your Turner dealer or representative, or write direct for complete microphone literature.



**TURNER
Model 99**

Response: 60 — 9000 c.p.s.
Level: 52 db below 1 volt/dyne/
sq. cm. at high impedance
Impedance: 50, 200, 500 ohms
or high impedance
List Price -----\$36.00

THE TURNER COMPANY

IN CANADA:

Canadian Marconi Co., Ltd.
Toronto, Ont., & Branches

EXPORT:

Ad. Auriema, 89 Broad Street
New York 4, N. Y.




933 17th Street N.E.

Cedar Rapids, Iowa

of forums on ultra-high frequencies and techniques and accessories for improved fringe-area television. Discussions were recently held in Dallas, Fort Worth, Austin, San Antonio, and Amarillo, Texas, under the sponsorship of local service associations. The forums are conducted by Martin Bettan, RMS sales manager.

JFD Manufacturing Co., Inc., Brooklyn, N. Y., released a new brochure describing its "Tuck-Away" line of single-channel TV boosters.

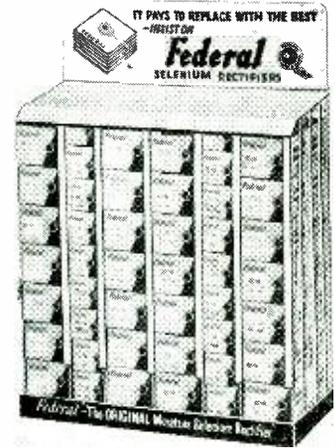Federal Telephone and Radio Corp., Selenium-Intelin Division, Clifton, N. J., has launched a sales promotion campaign aimed at the replacement market



for its selenium rectifiers. The campaign includes a selenium rectifier dispenser offered to distributors and a handbook and replacement guide containing technical information for the service technician.

M. A. Miller Mfg. Co., Chicago, designed a plastic leatherette wallet phone needle carrier which holds one dozen individually-carded replacement needles. The wallet and 12 needles sell for \$7.95.

Production and sales

The NBC Sales Planning and Research Department reported that as of January 1, 1952, there were 15,787,000 TV sets in the United States. New York City was first with 2,800,000 followed by Los Angeles and Chicago with 1,090,000 each, Philadelphia 1,001,000 and Boston 848,000.

The RTMA reported that 4,062,375 TV picture tubes valued at \$97,937,583 were sold during the first 11 months of 1951. The Association also announced that 4,415,422 TV sets had been sold to dealers in the first 11 months of 1951.

New plants and expansions

Raytheon Manufacturing Co., Waltham, Mass., leased a one-story building, now under construction. The new building will provide Raytheon with 50,000 square feet of space on a 100,000-square-foot tract, it will be used for the company's expanding Research and Manufacturing Divisions and is expected to be ready early in May.

RADIO-ELECTRONICS

Over 43,000 Technicians Have Learned
**HOW TO GET THE MOST OUT
OF BASIC TEST EQUIPMENT**
Why Not You, Too?

SERVICING by SIGNAL SUBSTITUTION
A BEST SELLER FOR OVER 9 YEARS! (NEW, UP-TO-DATE, 12TH EDITION)

The Simple, Modern, Dynamic Speed Approach To Receiver Adjustment and Alignment Problems, AM-FM-TV.

- Nothing complex to learn
- Universal — non-obsolete
- No extra equipment to purchase
- Employs Only Basic Test Equipment

Ask for "S.S.S." at your local Radio Parts Jobber or order direct from factory.

only 40¢

100 pages. Invaluable information that will help you re-double the value of your basic test equipment.

PRECISION APPARATUS COMPANY, INC. • 92-27 Herace Harding Blvd., Elmhurst 4, N. Y.

Ohmite Manufacturing Co., Chicago, manufacturer of resistors announced plans for a new and larger manufacturing plant in Skokie, Illinois. The new plant will provide for the company's expanded activities in defense work.

The RTMA moved its offices to larger quarters in the Wyatt Building, 777 Fourteenth St., N. W., Washington, D. C.

Electronic Instrument Co., Inc., Brooklyn, N. Y., manufacturer of Eico test equipment and kits, moved to a new 6-story factory building at 84 Withers St., Brooklyn, N. Y.

Kay-Townes Antenna Co., Rockmart, Ga., has relocated its plants and offices in larger quarters in Rome, Ga.

Hoffman Radio Corp. acquired a one-story building immediately adjacent to its No. 5 plant in Los Angeles.

Lowell Manufacturing Co., St. Louis manufacturer of low-volume ceiling-type loudspeakers, moved to a new and larger plant at 330 Laclede Station Road.

Synthane Corp., Oaks, Pa., opened an Indianapolis sales office under the direction of Duane W. Roland, formerly of the New York sales staff. The new office will provide service for industrial users of Synthane plastics in southern Indiana, southwest Ohio, and Kentucky.

Chatham Electronics Corp., Newark, N. J., has contracted to purchase a 17-acre tract in Livingston, N. J., as a site for a one-story plant to be devoted to the manufacture of electronic products.

Multi-Tron Laboratory, Chicago, moved to larger quarters which will be devoted to research and manufacture in electronic and nuclear physics.

Business briefs

... Raytheon Mfg. Co. in conjunction with the Massachusetts State Division of Employment Security worked out a recruitment plan for skilled technical personnel. The plan has been in operation for over six months and has been hailed as highly successful by both the company and state officials.


... Lion Mfg. Corp., Chicago, manufacturer of coin-operated amusement devices, announced plans to manufacture television sets. Paul H. Eckstein, previously with Hallcrafters Co., has been named general manager of Lion's new Television Division.

... Pacific Mercury Television, Van Nuys, Cal., Trutone Electronic Engineering Co., Hollywood, and Davis Electronics, Los Angeles, were elected as new members to the Los Angeles Council of the West Coast Electronic Manufacturers Association.

... The RTMA Engineering Department released a 14-point chart on electronic equipment reliability for the use of equipment designers. The association also scheduled its annual fall radio meetings for 1952 and 1953. The 1952 meeting will be held in Syracuse, N. Y., and the 1953 meeting in Toronto, Canada.

... The 1952 Electronic Parts Show, Educational Committee, mailed out a

MARCH, 1952

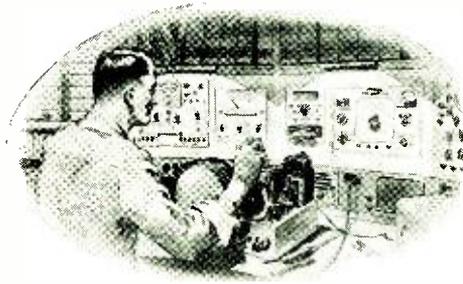

Send 10c to Sprague for window-size blow-ups of this message

ARE SERVICEMEN GYPS?

Every so often, some national magazine sounds off about radio-television servicemen.

"Servicemen are a bunch of gyps," is the general theme. "They'll clip you if you don't watch out."

They might just as well write the same thing of doctors, lawyers, storekeepers, auto mechanics—or anyone else. There are gyps in every line. Actually, the percentage in radio is far lower than in most.

The average serviceman—and I have met thousands during 30 years in radio parts manufacture—is a hard-working, straight-shooting individual. Rather than gyp customers, he is far more likely to spend more time on a job than he knows he will be paid for—simply as a matter of personal pride in doing things right.

The other evening, a friend's TV set went bad. A serviceman called for it in his truck and returned it in good working condition within 48 hours. His bill came to \$10 for service plus \$2.68 for replacement parts.

My friend argued that this was too much—yet he would never dream of complaining to the medical specialist who charged him \$10 for a 15-minute office visit; the lawyer whose bill for writing a simple will was \$75; or the garage man who, as my friend laughingly admits, charges \$5 for "just raising the hood" of his car.

In a large Eastern city having over 800,000 TV receivers, the Better Business Bureau received complaints about service on only 1/10 of 1% of the sets in a year. Investigation showed that most of these came from folks who

expected first-class reception in doubtful fringe areas; who tried to operate their sets without suitable antennas, or who had bought sets "wholesale" or at ridiculously low prices from cut-rate dealers who could offer little or no service.

Actually, it takes almost as long to become a good serviceman as it does to train for any other profession. Beyond this, it calls for regular study to keep up with the constant stream of new developments. Also, it requires a surprisingly big investment in test instruments, manuals and other shop equipment. The modern radio or TV receiver is by far the most intricate piece of equipment the average person ever owns or uses.

Servicemen are not fly-by-night businessmen. Ninety-nine out of 100 radio-television servicemen run their businesses properly. The other one per cent—the gyps—can usually be spotted a mile away. Nine times out of ten, they are the shops that feature "bargain" prices and ridiculously liberal service contracts. And their victims are generally set owners who expect to beat the game by "getting something for nothing."

Good television sets or good TV service are not things to be bought on a "bargain counter" basis. Set owners who recognize this aren't likely to get gyped.

Instead, they'll find that they get more real value for their television entertainment dollars than for almost any other dollars they spend!

Harry Nathan
PRESIDENT

SPRAGUE PRODUCTS COMPANY
(Distributors' Division of the Sprague Electric Company)
North Adams, Mass.



WORLD'S LARGEST CAPACITOR MANUFACTURER

MERIT

TV full-line* Components For Improvement, Replacement, Conversion



SELL IMPROVED RECEPTION

MERIT "TV" Kit #1000 for edge to edge focus—contains MDF-70 Cosine Yoke, HVO-7 Universal Flyback and MWC-1 Width Linearity Control. Keep a Kit handy—you'll get plus business and a reputation for "know-how."



MDF-70 . . . original of the "cosine" series—low horz, high vert inductance. Used by such famous sets as Radio Craftsman. Cosine Yokes will improve 10,000,000 sets now in use!

MERIT... HQ for TV Service Aids

MERIT's 1952 Catalog #5211 now available . . . introducing MERIT IF-RF Coils, includes Coil & Transformer data, listings. Other MERIT service aids: TV Repl Guide #404, Sept. '51 issue—covers 3000 models, chassis of 82 mfrs; Cross Ref Data on IF-RF Coils, Form #14. Write: Merit Coil and Transformer Corporation, 4425 North Clark Street, Chicago 40.

These three MERIT extras help you:

- Exclusive: Tape-marked with specs and hook-up data
- Full technical data packed with every item
- Listed in Howard Sams Photo-facts



* Merit is meeting the TV improvement, replacement and conversion demand with a line as complete as our advance information warrants!



HORTON & BROWNE ADVERTISING

questionnaire to distributors in an effort to determine what problems they want discussed at the seminars and educational meetings to be held in conjunction with the Show in Chicago, May 20 and 21. The plan was announced by Jack A. Berman, chairman of the Show Educational Committee.

. . . The Institute of Inventive Research, San Antonio, Texas, has acquired exclusive patent development rights for the Western Hemisphere on the Ionophone—the inertialess loudspeaker—developed by the French inventor Siegfried Klein. The Ionophone was described in the November and December issues of RADIO-ELECTRONICS. A public demonstration is planned.

. . . Park Metalware Co., Inc., Orchard Park, N. Y., maker of hand tools for the mechanical, electrical, and electronic fields, changed its name to Xcelite, Inc.

. . . Raytheon Manufacturing Co. announced that Interstate Supply Co., St. Louis distributor of Raytheon tubes, held a series of meetings announcing the sponsorship of the Raytheon Bonded Electronic Technician Program. The firm also has announced the publication of "Raytheon News," a monthly newspaper distributed among employees. It is a revival of an earlier publication bearing the same name, which was discontinued in 1945.

. . . Snyder Manufacturing Co., Philadelphia, announced that it would continue its highly successful consumer advertising campaign. New media are being spot tested. The company used national advertising in consumer newspapers for the first time last fall to introduce its "Directronic" antenna system to TV owners. New advertising will be in the form of news articles advising the layman of the function of the antenna in TV reception. The articles will be written by Edward M. Noll, consulting engineer at Snyder and a faculty member of Temple University.

. . . The G-E Tube Department announced plans for a campaign designed to promote more efficient use of three types of industrial tubes. The first stage of the campaign includes an eight point program aimed at lengthening the life of thyratrons, the most widely used industrial tubes.

. . . Sylvania Electric Products Inc. announced a new Glass Allowance Program by which radio-TV service technicians will be given a trade-in allowance of from \$2.25 to \$5.25 on used television picture tubes. Under the terms of the plan, one new Sylvania picture tube of any type must be purchased to earn the credit for each used tube returned. It operates through Sylvania's 450 radio and TV tube distributors.

. . . The National Electronic Distributors Association prepared a four-page brochure outlining the structure and functions of electronic parts distributors' organizations. The booklet was prepared as an answer to the many queries of people outside the industry, particularly in government circles, as to just what constitutes an electronic parts distributor.

—end—

NEW! 2ND EDITION
of the only complete
reference on AUDIO!

"The Recording & Reproduction of SOUND"

by OLIVER READ



Completely revised and vastly enlarged new edition

OVER 800 PAGES

A "Must" for Sound Engineers, Hi-Fi Enthusiasts, P. A. Men, Broadcasting Stations, Recording Studios, Students

largest selling book in its field

CONTENTS:

A Partial List of Authoritative Chapters:

Behavior of Sound Waves; Basic Recording Methods; Lateral Disc Recording; Microgroove Recording; The Decibel; Phono Reproducers; Styli; Microphones; Loudspeakers and Enclosures; Dividing Networks and Filters; Attenuators and Mixers; Home Music Systems; P.A. Systems; Amplifiers; AM and FM Tuners—PLUS HUNDREDS OF OTHER SUBJECTS

Now you can have all the right answers to any subject in the field of Audio. Learn how to select and get the most out of recording equipment. Tells you how to select the proper amplifier for given applications, how to test amplifier performance, how to eliminate hum. Explains microphone, speaker and pickup principles and selection factors. Shows how to utilize inverse feed-back, expanders and compressors. Covers hundreds of subjects—a vast wealth of reliable information found in no other single volume. If you work in the field of Audio, this book belongs in your library. Order your copy today!


6" x 9" **ONLY \$7.95**
Hard Covers
800 pages 700 illustrations

ORDER TODAY

Order from your Parts Jobber, or write direct to
HOWARD W. SAMS & CO., INC.
2201 E. 46th St., Indianapolis 5, Ind.
My (check) (money order) for \$.....
is enclosed.
Send copy(ies) of *The Recording & Reproduction of Sound (RR-2)*. \$7.95 per copy.

Name.....
Address.....
City.....State.....

Here's your Opportunity

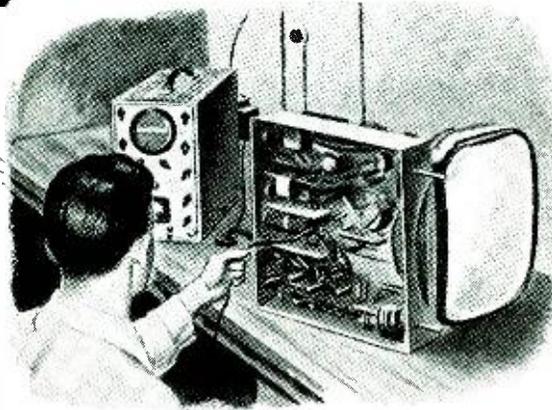

to prepare for a good job or a business of your own in TV SERVICING

There are today more good jobs open in TV Servicing than there are trained and experienced men to fill them. Yes, thousands of opportunities exist now for good-pay jobs offering employment security for years and years to come. Thousands of TV Servicing jobs are going begging. Do you want one of them?

Experts agree, that because of the critical shortage of trained and experienced TV Servicemen, and the tremendous future growth of the industry, no vocational field today offers more opportunities than TV Servicing.

The Big New Industry with a Great Future

Television is just in the beginning stages of its big industrial boom. Look at these amazing facts:

- Lifting the freeze on new TV stations will open many new TV areas and will improve the coverage of existing areas. The result will be an enormous demand for TV receivers.
- Within a few years over 1000 TV stations will be telecasting compared with 108 TV stations now on the air.
- Nearly one-half of all families living within the present TV areas do not yet own TV receivers.
- The new trans-continental video network plus better and more interesting programs plus larger viewing screens and color TV will increase the installation of new receivers, will induce present owners of 12-inch and smaller size viewing screens to buy newer model receivers.
- The power increases of many existing stations and improved reception range of current receivers will result in receivers being installed and serviced in the fringe areas of present stations.
- Under the FCC proposal, over 70 per cent of all communities will be served by UHF channels exclusively. This means TV servicemen must know UHF receivers before the new UHF stations in their area are opened.
- No one yet knows how great the industrial TV market will be.

RCA Institutes Home Study Course prepares you for a Career in TV Servicing

The addition of the RCA Institutes TV Service Training to your present radio-electronics experience will qualify you to step out and grasp the golden opportunities that now exist in television—America's fastest growing industry.

Learn at home—in your spare time—while you study the practical *how-to-do-it* techniques with *how-it-works* information. Easy-to-read and easy-to-understand lessons under the supervision of RCA engineers and experienced instructors quickly train you to qualify for the many good jobs now waiting for trained TV servicemen. Don't pass up this lifetime opportunity for financial security and a bright future in TV. Learn TV Servicing from RCA—pioneers and leaders in radio, television and electronic developments.

RCA Institutes conducts a resident school in New York City offering day and evening courses in Radio and TV Servicing, Radio Code and Radio Operating, Radio Broadcasting, Advanced Technology. Write for free catalog on resident courses.

Send for FREE BOOKLET

Mail the coupon—today. Get complete information on the RCA INSTITUTES Home Study Course in Television Servicing. Booklet gives you a general outline of the course by units. See how this practical home study course trains you quickly, easily. Mail coupon in envelope or paste on postal card.



MAIL COUPON NOW!

RCA INSTITUTES, INC., Home Study Department RE-352
350 West Fourth Street, New York 14, N. Y.

Without obligation on my part, please send me copy of booklet "RCA INSTITUTES Home Study Course in TELEVISION SERVICING." (No salesman will call.)

Name _____
(please print)
Address _____
City _____ Zone _____ State _____

RCA INSTITUTES, INC.
A SERVICE OF RADIO CORPORATION of AMERICA
350 WEST FOURTH STREET, NEW YORK 14, N. Y.

MARCH, 1952

EICO

TEST INSTRUMENTS

Guards

Majestic
HIGH STANDARDS OF
TELEVISION PRODUCTION QUALITY



In the Majestic design laboratories, Frank J. Dieli and assistant, Paul Smith, discuss with Harry R. Ashley, some important prototype-circuit measurements just taken with the 425 Oscilloscope, #221 VTVM and #MVP-1 HV Probe.

Frank J. Dieli, Majestic's Chief Engineer, and Harry R. Ashley, President of EICO, inspecting the use of the EICO Model 425 5" Push-Pull Oscilloscope, Model 221 Vacuum Tube Voltmeter and Model MVP-1 High Voltage Probe at the important Final Test Position on the Majestic Television production lines.

KITS - Wired Instruments

For Laboratory Precision at Lowest Cost—the Leaders Look to **EICO!**

WHY does The Majestic TV Division of The Wilcox-Gay Corp., another one of America's leading TV manufacturers, specify EICO Test Instruments on both its production lines and in its design laboratories?


BECAUSE—like Emerson, Tele-King, Tele-Tone, CBS-Columbia, and many another famous TV manufacturer coast to coast, Majestic knows that

ONLY **EICO** TEST EQUIPMENT DELIVERS ALL 10 **EICONOMICAL** FEATURES

1. Laboratory Precision
2. Lowest Cost
3. Lifetime Dependability
4. Speedy Operation
5. Rugged Construction
6. Quality Components
7. Latest Engineering
8. Super-Simplified Assembly and Use Instructions
9. Laboratory-Styled Appearance
10. Exclusive EICO Make-Good Guarantee

Before You buy any higher-priced equipment, be sure You look at the **EICO** line—in **Wired** as well as **Kit form!** Each **EICO** product is jam-packed with unbelievable value. **YOU** be the judge—compare, see **EICO** instruments today—in stock at your local jobber—and **SAVE!** Write **NOW** for **FREE** newest Catalog 3-C.

FOLLOW THE LEADERS... INSIST ON EICO!

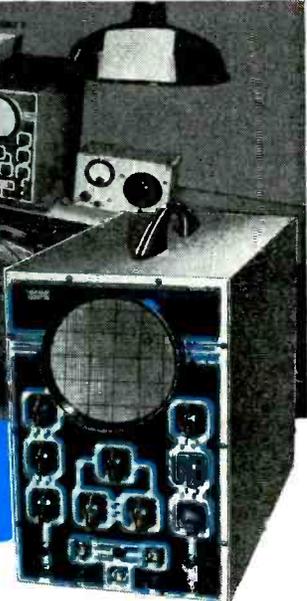

NEW 425K 5" PUSH-PULL SCOPE KIT \$44.95. WIRED \$79.95



NEW 221K VTVM KIT \$25.95 WIRED \$49.95



HIGH VOLT-AGE PRCBE \$6.95



NEW 555K MULTIMETER KIT \$29.95. WIRED \$34.95
20,000 ohms/volt



NEW 950K R-C BRIDGE & R-CL COMP. KIT \$19.95
WIRED \$29.95



320K SIG. GEN. KIT \$19.95. WIRED \$29.95

NEW 322K SIG. GEN. KIT \$23.95. WIRED \$34.95



NEW 1040K BATTERY ELIM. KIT \$25.95. WIRED \$34.95



511K VOM KIT \$14.95
WIRED \$17.95



NEW 625K TUBE TESTER KIT \$34.95
WIRED \$49.95



NEW 315K DELUXE SIG. GEN. KIT \$39.95
WIRED \$59.95



340K SWEEP GEN. KIT \$34.95
WIRED \$49.95



NEW 524K MULTIMETER KIT \$13.90 WIRED \$16.90
1000 ohms/volt

NEW 1171K RES. DECADE BOX KIT \$19.95 WIRED \$24.95



145K SIG. TRACER KIT \$19.95
WIRED \$29.95



ELECTRONIC INSTRUMENT CO., INC.
84-86 Withers Street, at Mosker Ave., Brooklyn 11; New York

©1951

Prices 5% higher on West Coast. Due to unstable conditions, prices and specifications are subject to change without notice

MICROWAVE EVOLUTION

. . . *New means for quick, efficient, low-price communication.* . . .

By HUGO GERNSBACK

INDUSTRY and commerce today more and more require ultrafast communication. This is particularly true of our big industries and corporations which must have instantaneous service between branches, their factories, and elsewhere, when seconds saved are often of the utmost importance. The telephone, the telegraph are no longer quick enough and in some ways are too costly. Even radio communication through independent communication companies has become far too slow.

Hence, many of our larger corporations have installed their own communication systems, taking advantage of the flexibility and comparative low cost of modern microwaves. These microwave (u.h.f.) private networks operate on frequencies from about 950 to 5000 mc.

Nearly 150 of our large corporations, many of which are oil companies, use the u.h.f. networks not only for communications but also to telemeter, run teletypes, open and close distant switches, operate direct phone networks and many other similar services. The corporations have their own private operators and their systems therefore are self-contained in all respects. Many of them maintain twenty-four-hour microwave service, every day of the week.

Microwaves are highly attractive because their use is far more economical than using telegraph or telephone lines, as was the case in older private communication systems. The cost per mile is less than half with microwaves and the maintenance cost is very low. During sleet storms and hurricanes wire-line damages run high, whereas with microwaves the communication towers are anywhere from twenty-five to fifty miles apart, cutting maintenance costs sharply.

It is interesting to note that even old-time corporations such as Western Union, which at one time relied mainly on pole wire lines and for years operated in the red, finally began making a profit when they switched to microwaves. Western Union is now busily engaged in extending its microwave system throughout the country, at a huge saving in maintenance and operating costs.

To date, the American Telephone and Telegraph Company is the largest user of the microwaves, having pioneered in it over many years. The recent successful completion of their coast to coast network uses microwaves not only—as is often erroneously thought—for television, but more for multiplex phone communication from coast to coast besides other services of the corporation. Microwaves are so flexible that a single channel can carry up to 2500 simultaneous messages, against 1800 on the older (and more costly) coaxial cable.

But microwave channels are not used solely by our large corporations. One of the important new users is the recently opened *New Jersey Turnpike*, operated by the State of New Jersey. This new toll superhighway operates its own statewide network on 960 mc. The system now has seven microwave towers, each about one hundred and fifty feet high. These have been erected near Newark, New Brunswick, Trenton, Bordentown, Moorestown, and

Swedesboro. Two towers have been erected near Newark.

The system consists of a voice channel which monitors the entire system. There is also a dial phone for administrative calls as well as two voice channels used for communication with state police cars and maintenance trucks. In addition to this, there is also a teletype one-party line. An innovation is that it is possible to cover the entire length of the new turnpike with two-way mobile coverage for instant communication. This is effected by having a number of v.h.f. base stations at five of the system's seven microwave towers for communicating with the vehicles. The system is so well integrated that the dial phones and teletypes can link the police for the entire length of the turnpike with one another as well as with the state police headquarters in Trenton. The same is the case with state troopers, maintenance trucks and all toll gates along the road. Over \$100,000 has so far been expended on this new microwave communication network.

Another highway system now making use of microwave communication is the Pennsylvania Turnpike Commission, whose system is similar to that of the New Jersey Turnpike.

Another user, at present experimenting with microwaves in the Northwest, is the Bonneville Power Administration. The versatile waves will be used by Bonneville to monitor its power lines, compute the location of line breaks, and automatically record the time of the failure.

The Atomic Energy Commission is another newcomer which requires microwaves chiefly for remote control purposes. Due to the fact that atomic workers cannot be exposed to dangerous radiations, many atomic plants must be operated from a distance. This is a most complex undertaking, because many of the operations must be checked and doublechecked without any human being on the spot to supervise plant operation and other facilities. Through a variety of interlocking devices, microwaves furnish the key for safe operation. In fact they can do anything that humans do—and often do tasks impossible for humans. This particular branch of microwaves is due for great future expansion.

But to date, numerically the oil companies are in the advance guard as users of microwaves. In the telemetering and supervision of their long pipelines, opening and closing distant valves, controlling pressures in pipes, starting and stopping pumps, getting reports on distant oil flow, the oil companies have found a most versatile tool in microwaves. Such companies as the Peoples Gas Light and Coke Company obtains automatic reports on distant gas pressure, gas flow, metering, etc., by microwave. The Transcontinental Gas Pipe Line Corporation is now considering installation of a microwave system for its new 1,800-mile pipeline from Texas to New York. Most of the large pipelines are certain to follow suit in the near future.

All in all, microwaves for industry and commerce are bound to expand enormously in the foreseeable future, with expenditures for installation alone running into tens of millions of dollars.



TV marries the MOVIES

By AARON NADELL

TELEVISION and the motion picture theater are getting married. Theater owners do not wish their two and a half billion dollar investment jeopardized by video, so they are taking the gal right into their family. Equipment manufacturers have found amazingly ingenious ways of encouraging the match.

Theaters equipped for TV do more than just pick standard telecasts out of the air. They all do that; but some of them also maintain camera crews and buy exclusive rights to special events, thus giving their paying customers programs that cannot be seen at home. By pooling their resources, theaters in different cities now are linked by coaxial or microwave nets to handle sports events or other special features on an exclusive basis.

Programs obtained from either of these sources are placed before theatergoers through any of five general types of equipment.

Three of the five general types of TV installations now in theater use provide enlarged, projected images up to 24 feet wide. A fourth, similar to one of the three just referred to, supplies projected images not more than 8 or 9 feet wide. It is used principally in the "television lounges" that showmen are now installing as a sort of theater within a theater. The fifth type of theater system is merely a home receiver, set up in a lobby, foyer or television lounge.

Only this last type, it should be noted, is likely to offer the average television dealer or service technician much opportunity in a business way. The first four systems, which are priced up to \$25,000 each, have been put on the market through established theater-supply dealers, not through television dealers. Their maintenance and repair has been arranged for, by their manufacturers, through organizations that now service theater projection and sound equipment. Sale and maintenance of a home-type unit for lobby use is a wide-open field that anyone may enter.

Theaters use TV for a number of different purposes, all considered important. A lobby set diverts patrons who cannot find seats immediately. A TV lounge encourages attendance by those who prefer to see their movies from the beginning and might not come in to wait if there were no other entertainment to keep them amused until the next show starts. Reproduction of reg-

ular telecasts by either of these means attracts those who would not come to the theater if that meant missing some favored video program. The lounge enables family groups to separate while attending the same theater: thus, Papa can watch the boxing matches while Mama sobs through the drama; or both parents can watch TV while the kiddies sit through a Western.

Further, TV is used to attract patrons by showing special events not available in the home or tavern, as mentioned above. Showmen located in or beyond fringe areas have put up receiving antennas that mere home-owners can't afford.

Photo A shows essentially home-type equipment giving direct-view presentation on a standard picture tube. The minor problem of keeping patrons from fiddling with the controls is met by mounting the tube in a wall so only its face is visible, the controls being elsewhere in a locked room and adjusted with the help of a monitor tube.

Photo B shows a lounge-type installation delivering an optically projected image that can be as much as 8 or 9 feet wide. The optical arrangements are similar to those invented for astronomical work. They are called Schmidt optics, after their inventor. A small picture tube—usually 3 or 5 inches across—faces a spherically curved mirror. The stem of the tube protrudes through a hole centrally located in a thin *correcting lens*, also called *corrector plate*. The mirror projects the image to the 9-foot screen through this lens, which counteracts and neutralizes the spherical aber-

ration. The "optical barrel" that houses the tube and optical system is atop the cabinet at the front of the center aisle (Photo B). The rest of the TV receiver is in the cabinet.

A larger C-R tube and optical system projects theater images up to 24 feet wide. The picture tube is 7 inches in face diameter and operates at an anode potential of 80 kv. The spherical mirror is 30 inches in diameter. Picture brilliance in general approaches but does not equal the standard set some years ago by the Society of Motion Picture Engineers.

Film storage system

The fourth and fifth kinds of theater TV in current use are variations of the so-called *film storage* or *film intermediate* method of enlargement and projection.

In this system the image on the picture tube is reversed to present a negative—black where white should be, and vice versa—and photographed by a motion picture camera. The film runs continuously from the camera through automatic high-speed development and thence directly into a motion picture projector. It is thus shown like any other film, and can be given the theater's standard image width and brightness. Because the developing solutions operate at elevated temperature, the time lag between photographing the image and projecting it before the audience may be as little as 40 seconds. The fourth standard is 35-mm film and standard theater projection equipment; the fifth is a similar system using 16-mm

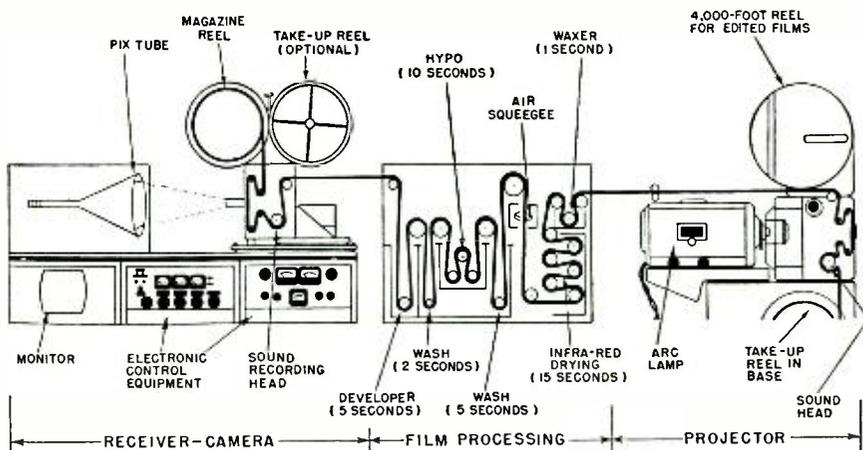


Fig. 1—The film's course from kinescope through developer and to the projector.

RADIO-ELECTRONICS

film and a 16-mm projector. Photo C shows some control equipment and a part of the film-processing equipment.

It is in these systems that the 30-frames-per-second of television must be converted to the 24-frames-per-second for standard movie projectors. Several effective but intricate methods for doing this have been worked out. Some are mechanical. The one associated with Fig. 1 is completely electronic.

This arrangement includes what is, in effect, an electronic counter. The C-R tube remains dark until the camera film has been pulled down one frame and is motionless behind the lens. Then a circuit associated with the camera mechanism turns on the tube. The electronic counter goes into action immediately, and after the 525th horizontal scanning pulse has been counted, darkens the tube again. It remains dark until the camera once more turns it on, after the next frame of film has been pulled down. This cycle is repeated 24 times a second. Each time, $\frac{1}{4}$ TV frame is lost out of every $1\frac{1}{4}$ TV frames. Thus 24 images per second are photographed, regardless of the fact that 30 are supplied to the tube. Sound is recorded simultaneously.

Film produced in this way remains a permanent record that can be shown again in the same theater or "bicycled" to affiliated theaters for subsequent showings. This was done during a recent Presidential broadcast. The telecast was piped over coax to the New York Paramount and projected there with a time lag of about 60 seconds, then rushed across the river to the Brooklyn Paramount.

Other theaters, in New York and elsewhere about the country, took the telecast from the air.

Smaller theaters, using home-type or lounge equipment, show nothing but commercial telecasts. Larger theaters may have their own TV camera crews, or several noncompetitive theaters may share the cost of one crew. Equalized coaxial lines or the theater's own microwave links may be used to get the program to its destination. These processes were begun in 1948, were expanded in 1949, and still further expanded in 1950. Plans announced before the imposition of government restrictions called for ballooning expansion in 1951-52. Whether that will now be possible remains doubtful at this moment.

But there is no doubt at all that television and the motion picture theater are definitely getting married. Whatever may happen with respect to the larger equipments during this emergency, the smaller ones seem destined to become as common a theater facility as the popcorn machine. Their advantages are many and evident; their price is low, and operation costs almost nothing. As a final endorsement on the marriage license, it may be noted, the Society of Motion Picture Engineers has changed its name to Society of Motion Picture and Television Engineers, and now admits to membership persons whose backgrounds lie in either field.

—end—



Photo A.—Moviegoers don't mind waiting for seats in the homelike TV lounge.

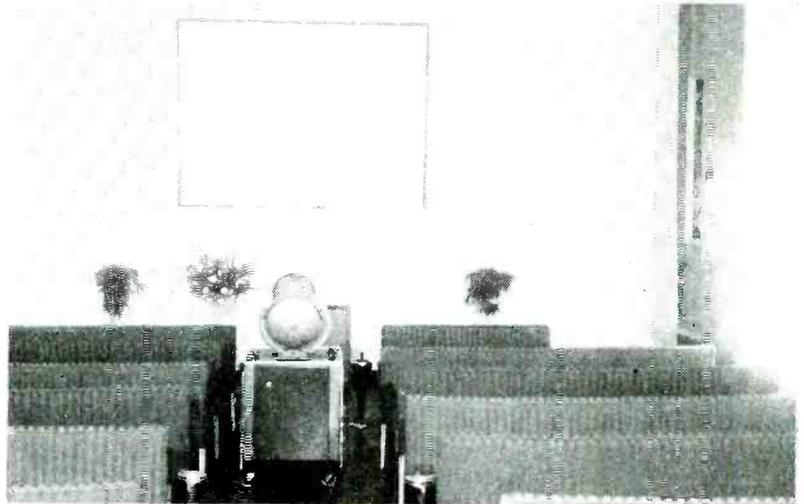


Photo B.—Projection unit provides a large TV picture for waiting audience.

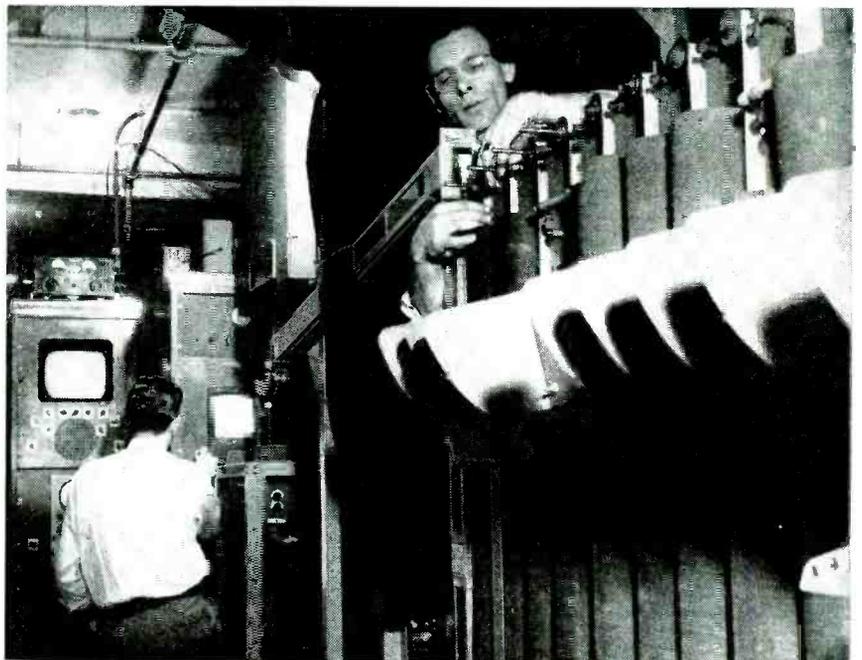


Photo C.—Control and film-processing equipment in large theatre installation.

TV CONVERSION DETAILS

For the past year we have been sending a brochure on big-tube conversion to all readers who requested it. The brochure was prepared originally by Walter Buchsbaum and later revised by Matthew Mandl. The demand for it has been increasing regularly, so we are printing it herewith for the benefit of all our readers.

THIS article on conversion deals with the electromagnetically deflected receivers. Electrostatic 7-inch receivers require major design changes and conversion is not recommended. Slave units are much more satisfactory for such receivers (see page 22 of RADIO-ELECTRONICS for August, 1951).

Complete kits, containing all matching components as well as an accompanying instruction sheet, make conversions easier. These are available and occasionally advertised in the pages of RADIO-ELECTRONICS.

Three primary factors must be considered in any conversion: The cabinet size, the tube type, and the necessary circuit changes. If the cabinet is not to be changed, the tube will be limited to the next larger size unless the cabinet is very roomy. Mechanical problems include changing the picture-face cabinet aperture and mask, mounting the picture tube on new brackets to raise it to the required height, and extending leads to the socket and neck assemblies. Such factors depend on the size of picture tube required and whether or not a new cabinet is to be utilized, therefore only the electrical aspects of conversion will be discussed here.

Changing a 10-inch to a 12-inch tube usually requires no major electrical modifications. Tubes often can be replaced without yoke change if the larger tubes do not have deflection angles in excess of 65 degrees. When rectangular tubes or large round picture tubes are to replace 10- and 12-inch ones, major changes must be made in the horizontal flyback section of the receiver. A new yoke, a matching transformer, and often a new width coil and focus coil are needed. Besides this, second-anode

voltages must be higher, and changes in the vertical-sweep section may be necessary to secure the required additional height for the larger tube.

Horizontal-sweep section

In most modern receivers the horizontal-sweep system uses a flyback transformer for horizontal output and high voltage. If the radio-frequency type high-voltage system is used it would be advisable to rewire the high-voltage compartment for the flyback deflection system.

There are a number of different components as well as circuit variations for conversion to the large-screen picture tubes. In many cases the set's original circuit can be used, with some modifications for the higher voltages and greater sweep.

The yoke must match the flyback transformer. For this reason it is preferable to secure a transformer and yoke recommended by the manufacturer for use together. Thus, for conversion to the 14- or 16-inch tubes with a deflection angle of 70 degrees, the Merit HVO-6 flyback transformer can be used with the Merit MDF-70 yoke. In addition, a Merit MWC-1 width coil can be used and a Merit MF2 focus coil. A general Electric RTO-085 kickback transformer can be used in conjunction with the G-E RLD-024 yoke. An RLD-017 or 019 width coil can be used. If the original focus coil is inadequate, an RLF-038 focus coil can be used.

The same holds true for the 19- or 20-inch tubes which have a deflection angle of 66 to 70 degrees. An RCA 225T1 transformer can be used with a 209D1 or 211D1 yoke. An RCA 202D2 focus coil can be used in conjunction with this combination. A Ram X053

transformer can be used with Y70F10 yoke. This combination will furnish approximately 17,000 volts as compared with the 16,000 for the previously mentioned transformer. A Ram 201R11 width coil will work with these. A Quam QFC focalizer can be used instead of the focus coil, or the RCA 202D2 can be utilized. Merit also has a combination for the 20-inch tubes which uses a cosine wide-focus yoke such as the MDF-70. An HVO-7 flyback transformer can be used in connection with a Merit MWC-1 width coil.

For the 24-inch tubes a Merit HVO-8 transformer can be used with an MDF-30 cosine yoke. Ram also has a transformer for direct-drive circuits in the X035. The matching yoke is the Y70F10 and the width coil is the 201R4.

A typical circuit for a 14- or 16-inch conversion is shown in Fig. 1. This uses a minimum of new components and does not require any more filament or B-power than most of the 10- or 12-inch receivers already have. The 6BQ6-GT tube is recommended because it is somewhat more efficient than the 6BG6-G. The 6CD6-G can be used as a direct replacement for the 6BG6-G, though greater filament current is required. Care should be taken that the 6CD6-G does not exceed the rating of the power transformer. Otherwise an additional filament transformer must be installed. When using the 6BQ6-GT the socket will have to be rewired as shown in Fig. 1. If the 6BG6-G is to be retained, increase the screen voltage by using a lower value of screen-dropping resistor. The maximum screen rating of the 6BG6-G is 350 volts; the 6CD6-G 175; and the 6BQ6-GT 200. All these can be exceeded by approximately 25 volts without damaging the tube.

WARNING!

We have received requests for conversion information from persons who state they have had little radio training. Conversion is no job for the unskilled man! Unless you are an experienced technician, familiar with the precautions necessary in handling picture tubes, and with some knowledge of television circuits, keep away from it! You face danger of injury or death from high voltage or possible tube implosion, and the set or tube may be damaged by wrong adjustments of ion traps or wrong connections. Let a qualified service technician do the job.

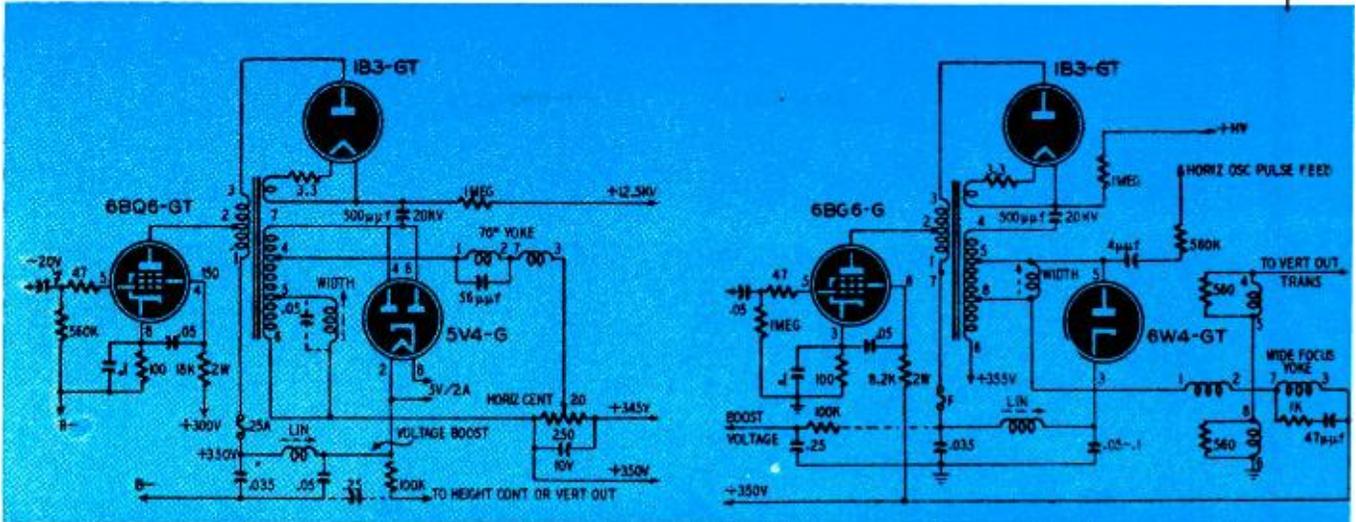


Fig. 1—Diagram of horizontal output for 14- or 16-inch jobs. Fig. 2—A circuit useful for 19- or 20-inch conversions.

The circuit of Fig. 1 uses a Ram X030 high-efficiency output transformer which usually mounts in the same holes and space as most of the older transformers such as the RCA 211T1, 211T3, etc. The same width and linearity coils can be used as in the original circuit. Thus, the width coil is an RCA 201R1 and the linearity coil an RCA 201R3. This circuit incorporates a horizontal centering control similar to the type used in the RCA 630 receivers as well as many others. If mechanical centering is used, a 20-ohm, 2-watt resistor may be connected between the deflection yoke lead and the B-plus terminal of Fig. 1.

The damper tube shown in Fig. 1 is a 5V4-G. It requires 5 volts for the heater connections. A 6W4-GT, which requires 6.2 volts, can be used as shown in Fig. 2. It is a more rugged tube and preferable.

A 1X2 miniature rectifier can be used instead of the 1B3-GT shown. The wiring is identical except that the anode connector clip must be changed to fit the 1X2. The deflection yoke should be a 70-degree type. For rectangular tubes or other short-necked picture tubes the length of the yoke is very important. If the yoke is too long the focus coil and ion-trap magnet will not fit properly and a dim or partly cut-off picture will result. The total length of the coils should not exceed $2\frac{3}{8}$ inches. Otherwise neck shadows and other faults will result.

A suitable circuit for the 20-inch tubes is shown in Fig. 2. It uses a Merit HVO-7 output transformer with a matching MFD-70 deflection yoke. An MWC-1 width coil is used with this combination. Fig. 2 is for receivers in which the chassis is the ground, as compared with the RCA 630 types which use a B-minus as in Fig. 1. The first voltage-boost capacitor below the damper tube can be changed from .05 to 0.1 or to some intermediate values to minimize linearity defects and reduce transient oscillations caused by improper damping. The latter will sometimes produce white vertical bars to the left of the screen. The 47-ohm resistor

in series with the grid circuit of both systems illustrated is to reduce Barkhausen oscillations which will produce dark vertical bars to the left of the screen. In Fig. 2 a connection for feeding a pulse to the horizontal oscillator is shown. This connection is required in some sync-lock circuits.

If the new tube does not have an outer conductive coating, an additional filter capacitor may have to be placed beyond the 1-megohm series resistor in the high-voltage line. This should be a 500- μ f, 20,000-volt filter.

Vertical-sweep section

Many older receivers have a vertical-sweep system with sufficient reserve power to give the necessary increase in height for the large tubes. Unless the sweep amplitude on the old tube was barely sufficient for full height, no changes should be made until the horizontal system has been completed. If increased vertical sweep is necessary the voltage to the plate of the vertical-output tube can be increased, or the vertical-output tube can be changed to one giving a greater output. If, for instance, a 6SN7-GT tube is used as a combination oscillator and vertical output, a 6BL7-GT can be substituted without circuit change. A 12BH7 is a direct substitute for the 12AU7 and will give increased height. When a 6K6 tube is used, substituting a 6V6 will usually help.

These substitutions will function only in sets with filaments wired in parallel. If a pentode is used but connected as a triode, rewire the tube socket and connect the screen grid to a well-filtered B-plus point in the low-voltage power supply. Check with the tube manual for proper screen voltage.

If tube substitution is not possible or does not increase height enough, connect the B-plus side of the height control to the boost voltage as shown in the dotted line sections of Fig. 1 or Fig. 2. The 100,000-ohm resistor and 0.25- μ f capacitor are a decoupling network. If the height is still insufficient, connect the B-plus side of the vertical-output transformer to the boost voltage

instead of the height control. For this change use a 5,000-ohm, 2-watt resistor and an 8- μ f, 600-volt filter capacitor in place of the 0.25 shunt. However, this will tend to reduce the high voltage and width slightly. Experiment with different values of resistors and capacitors for maximum efficiency in both the vertical and horizontal circuits.

Focus coil and ion trap

All the larger tubes beyond the 14-inch size require a greater magnetic field in the focus coil. The easiest change is to substitute a new focus coil in place of the old one. For Fig. 1 the RMA 109 (Tech-Master 2D2, Stancor FC-11, Quam QF2, RCA 202D2, etc.) can be used. It is larger than the old types and has a round steel case. Its resistance is approximately 470 ohms. If focus cannot be obtained with the new coil, reverse the connections and note the results.

Focus-coil current can be increased when needed by changing the associated resistor values around the focus control. A shunt resistor can be removed or any resistor which is in series with the focus coil can be shunted. Make sure such resistors are in the focus-coil circuit only and do not affect other circuits. For instance, in the Admiral 30A1 chassis, a decreased resistance in the focus network will also increase the voltage to grid 2 of the picture tube because the focus network is a resistor in series with the B-plus supply. (This increased voltage to grid 2 of the picture tube is all right in this case because most of the large tubes require about 50 volts more on grid 2 than do the smaller types.)

Receivers which use a combination of electromagnetic and permanent-magnet focus coils may require a new coil or else a full PM focus ring. If high voltage is raised above 15,000, some PM focus devices don't have enough field strength to focus the picture.

Three types of electrostatic tubes are being manufactured: The one requiring high voltage on the focus electrode; the type which uses low voltage from the B supply; and the self-focus type re-

quiring no focus electrode voltage. The high-voltage type appears to be going out, and is not recommended.

For low-voltage types like the 17HP4 and 20HP4, voltage for the focusing electrode can be obtained from the low-voltage power supply, using a potentiometer for the control. Voltage values depend on tube type and should be those recommended by the manufacturer. Focus coil is not used, but the old focus coil would not be placed on the neck. The focus coil should be left in the circuit or replaced with a resistor having the same value as the d.c. resistance of the coil. Make the necessary socket changes.

For the newer self-focusing C-R tubes, direct replacement can be made without use of focus coil. (The latter should be left in the circuit, however, as described above.) No focus control is used, though the old one can be left in circuit or replaced with a resistor.

Practically all of the newer large-screen tubes use either a single- or double-magnet ion trap. If the old receiver used an electromagnetic ion trap of two coils, it can be left in the circuit by removing it from the tube and taping it to the chassis. A PM ion trap then can be placed on the new tube. Be sure to use the correct type of trap for the new tube, because damage to the screen material can result from an incorrect ion trap. (See "Ion Burns" in the February, 1952, issue.)

In converting sets several years old, change all tubes from the horizontal oscillator through to the deflection-coil circuit. Also replace the low-voltage rectifiers. Tubes used for a long time have lower output. Installing a new discharge tube, horizontal output, high-

voltage rectifier, and damping tube will give the increased efficiency necessary for the larger-sized picture tube.

Corona or arcing: Because of the new higher voltages the high-voltage section may have corona or even arc-over. To avoid it, keep all high-voltage connections smooth. Avoid sharp bends and keep high-voltage wires away from each other and from the chassis. Clean all insulating surfaces with carbon tet. If necessary, paint the high-voltage socket with Glyptal or polystyrene coil dope. Coat grounded parts near high-voltage points with the same material. If there is no corona ring on the high-voltage socket, connect all unused tube pins together with No. 18 bare wire. Leave smooth, well-soldered joints.

Insufficient width: Check all low voltages (except that at the plate of the horizontal-output tube—there are 6,000-volt pulses there!). If there is not enough bias on the output tube (about 18 volts for a 6BQ6) increase the value of the grid-coupling capacitor. Also increase the voltage on the horizontal oscillator or discharge tube by decreasing series plate resistance. In the synchro-lock circuits, reduce the discharge capacitor and increase the resistor in series with it experimentally. Connect a .05- μ f capacitor across the width coil as shown by the dotted lines in Fig. 1. This reduces high-voltage supply but increases width. Increasing the screen voltage of the horizontal output tube (as previously mentioned) also helps. Also check the low-voltage power-supply system because in some instances a gradual decrease in the low-voltage output over the years may have been compensated for by increasing the height and width-control settings. Re-

place the low-voltage rectifier tubes and check the filter capacitors for leakage.

Picture blooming: Blooming is caused by too low second-anode voltage. This decreases beam velocity and the electron stream is more strongly influenced by the magnetic fields of the yoke. It is therefore swept too much. If the high voltage is too low and the preceding measures have not helped, a voltage-doubling circuit may be needed.

Excessive high voltage will reduce the picture size because the magnetic fields of the yoke cannot sweep the beam fully because of increased velocity. High voltage tests should be made in such an instance to discover whether the insufficient picture size is caused by increased high voltage or by insufficient sweep. A defective low-voltage supply will also decrease picture size.

Many special points—mechanical as well as electrical—have been discussed in articles and short items in this magazine. They contain detailed information on conversion of various models, hints on the furniture aspects of conversion, and other information useful in converting sets for bigger tubes. The more important articles are listed below.

References:

Big-Tube Conversions Are Profitable..... Jan., 1951
 Converting to Bigger TV Tubes..... May, 1951
 Slave Unit for 7-inch Conversions..... Aug., 1951
 Special Problems in TV Conversions..... Aug., 1951
 TV Conversion Components..... Aug., 1951
 Profitable Conversion with
 Rectangular Tubes..... Aug. and Sept., 1951
 630 to 17 inches..... Jan., 1952
 —end—

TV DX FOR MARCH

TV receiving conditions during March will be generally similar to those of February over most of the country, though there will be some evenings of fairly good propagation that will be a foretaste of better things to come as spring advances. As warmer weather comes to the Gulf states and the Southwest, the average quality of fringe-area reception will improve appreciably.

Sporadic-E dx will be rare in March, as in February, though years of experience have shown that this phenomenon that brings us low-band TV signals from 600 to 1,300 miles away can happen anytime. The openings observed during March are not likely to be of long duration, nor is the reception apt to be of "program quality" for long.

For viewers in the northern states and adjacent Canadian areas there will be pronounced auroral activity, with the likelihood that the disturbances will be strong enough to affect the lower TV channels. This is most commonly seen as co-channel interference on channel 4, as it is most heavily saturated with stations, and to a lesser extent on other low-band channels.


To what extent aurora is capable of affecting the high-band channels is still a matter of conjecture, and may be answered by discerning TV dx observers.


—end—

CORRECT "630 TO 17 INCHES" DIAGRAM


In a large number of the copies of the January issue, the diagram on page 56 was printed badly out of register, making it difficult or impossible to under-

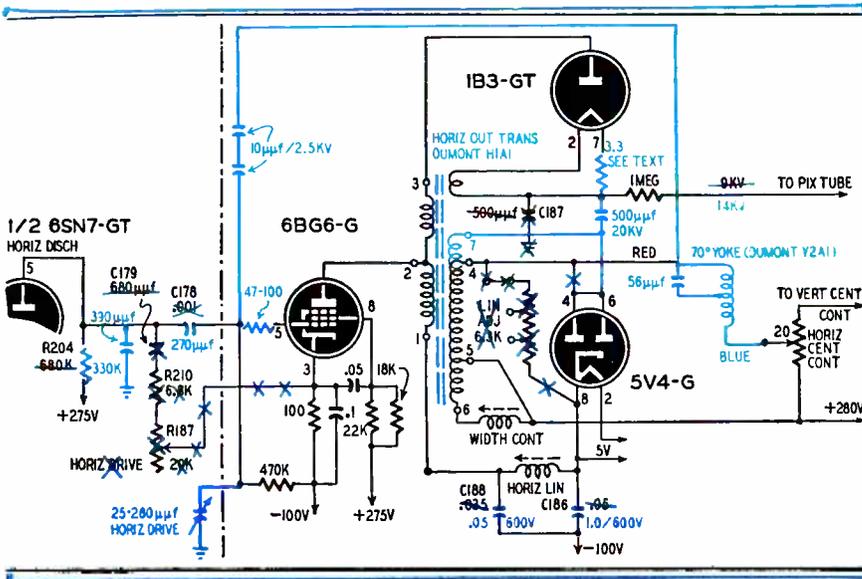stand. The corrected diagram is below. The changes in the circuit are printed in blue, while the original parts are shown in black.



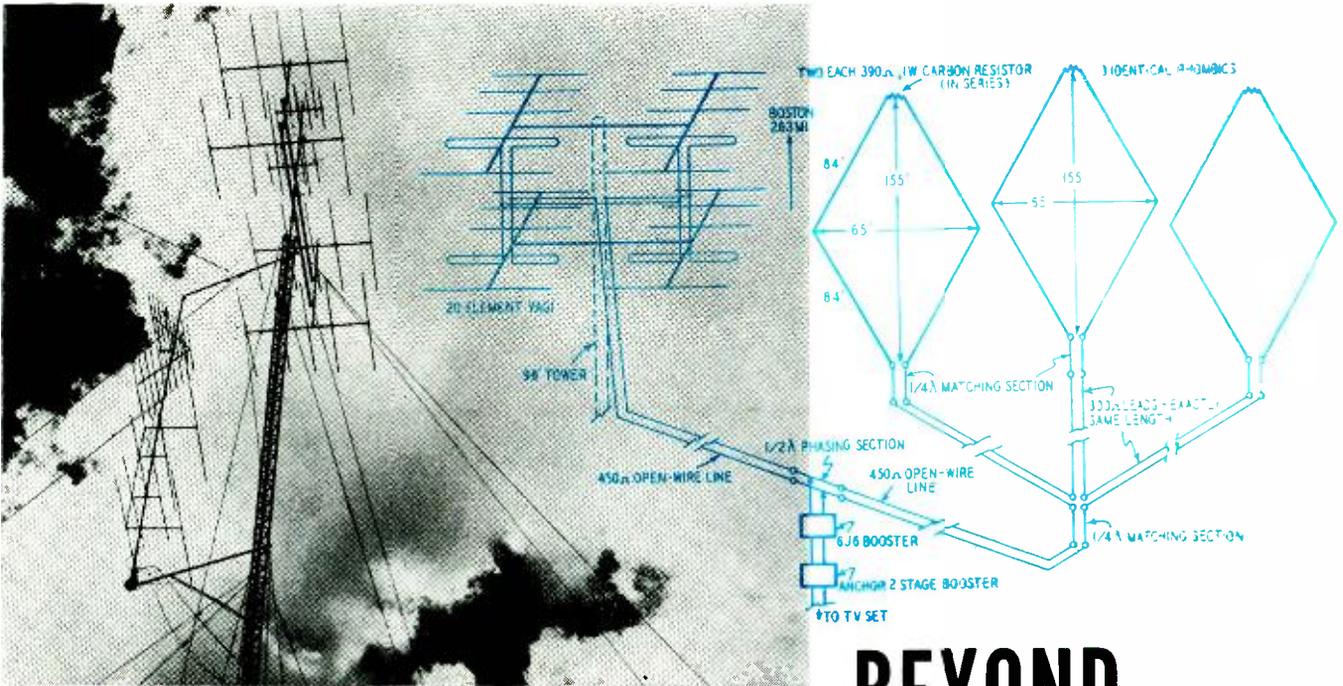

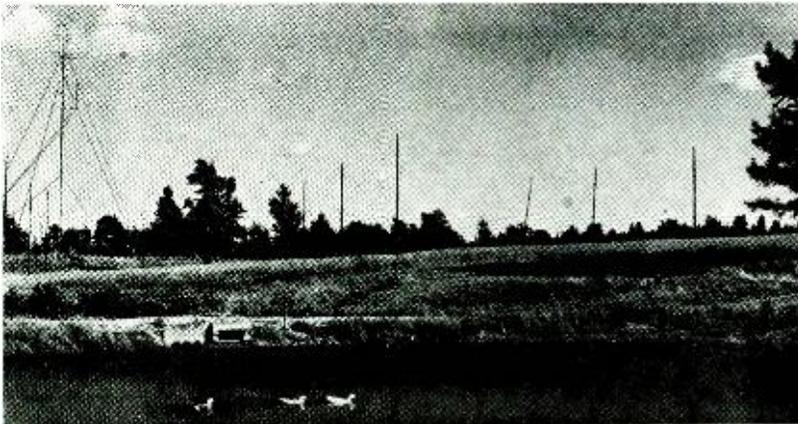Above—The Yagi arrays for 4 and 7. Below—The “ten-acre-field” rhombic array.



BEYOND THE FRINGES

by
T. W. MORGAN
and
R. J. BUCHAN

IMPROVEMENTS in antennas and receivers, plus increased transmitter power, have stretched the range of TV signals so that 75 to 150 miles is considered “fringe” by many stations. Thomas W. Morgan at West Pembroke, Maine, has succeeded in stretching this distance with an elaborate antenna system to an almost unbelievable 263 miles. Three large rhombics, 84 feet to a leg, in parallel with a 20-element Yagi, mounted on a 98-foot tower, for channel 4, plus an assortment of three arrays for channel 7 should qualify as the world’s largest antenna receiving installation.

The system of connecting the three rhombics, which are in parallel with the 20-element Yagi, is shown in the figure. The quarter-wave matching sections connecting the rhombics to the twin lead are 42 inches in length, and constructed of No. 14 wire, spaced two inches. The quarter-wave matching section at the junction of the three leads from the rhombics matches the 100-ohm resultant impedance of the three leads

in parallel to the 450-ohm open wire line. It has an impedance of 210 ohms, and is constructed from $\frac{3}{8}$ -inch outside diameter copper tubing 42 inches in length, spaced $1\frac{1}{4}$ inches. The impedance of the quarter-wave phasing section between the two antennas is not critical, and can be made of bare wire or tubing. If made 42 inches long, it may be necessary to reverse the lead from one antenna in order to cover a 180-degree phase difference so that the signals from the two antennas will add. It can be made 84 inches long. In this case moving the connections to the booster between the two ends should result in a point of maximum brightness—when the correct point is found—without reversing one antenna lead.

If an antenna having a small amount of gain is connected to a high-gain antenna, very little, if any, differences will be noted as the connections are varied along the phasing strip. However, the situation changes when two antennas having equal gain are phased out. At a point 180 degrees out of

phase, the signal will be zero, and at a point in phase, it will be 3 db better than with either antenna when used alone. The signal received with the entire system is definitely better than either the 20-element Yagi or the rhombic alone. This shows that more than one antenna can be connected to a set, provided they are properly phased out and impedances are matched.

A 30-foot gin pole has been permanently set back of the 98-foot tower so that, with the use of two blocks and tackles (the second one as a safety measure), the tower can be lowered or raised in a few minutes.

Two boosters are normally used—a custom-built one first, using the well-known 6J6 neutralized triode circuit, plus an Anchor two-stage booster for additional amplification. Various sets have been used. The present one is a 20-inch Sheraton with which sound is received 75% and a picture about 30% of the time the set is tuned in from WBZ-TV, channel 4, Boston, Mass.

—end—



This simple TV Service Aid may be as useful as much more expensive apparatus.

A pocket-size device using no meters or other expensive components, this is an excellent TV test unit for student use and service in the home

By

CHARLES G. BUSCOMBE*

THE TV "SERVICE AID"

THERE is no disputing the value of accurate test equipment such as the sweep and marker generator, oscilloscope, tube checker and vacuum-tube voltmeter for fast, efficient, complete TV receiver servicing.

But there are times when the technician is called upon to service a set without any of these instruments. The amount of apparatus that can be carried into a customer's home is strictly limited, to give one example. When regulation type test instruments are not readily available, the *skilled* technician can do nicely with nothing more than a kit of replacement tubes, an R-C decade box or an assortment of resistors and capacitors, plus the usual hand tools. His greatest asset in such work is a plentiful supply of down-to-earth "know-how" and a good knowledge of circuit theory.

To supplement the above, the writer has designed and constructed the simple *Service Aid* described in this article. It is cheaper and more rugged than the standard v.t.v.m. or multimeter, and because it is specifically designed for television set testing, may be even more useful. With this instrument and the intelligent use of suitable techniques, it is possible to locate close to 90% of the troubles encountered in any section of the TV receiver.

The TV Service Aid is a tubeless, meterless instrument of vest-pocket size, that will enable a capable technician to perform all the tests normally performed in a customer's home with reasonable accuracy and speed.

It was originally constructed experi-

mentally and put to use with some reservations as to its ultimate value, considering its utter simplicity. But over a period of several months it has more than lived up to expectations.

Such a Service Aid can be of great value to the busy technician on house calls, or even in the shop when his regular equipment is tied up on other jobs. It can be used:

For measuring plate and screen voltages and taking other readings in low-voltage supplies. The hot lead is connected to terminal B (See circuit diagram) with black ground lead clipped to chassis. The control potentiometer is then slowly varied until the neon bulb just barely fires. Voltage is read directly from the calibrated scale, which is graduated from 80 to 1,000 volts. (It was found after considerable experimentation that the average neon lamp could not be made to fire at less than about 70 volts. This of course prevents it being used for bias tests.) Its reliability over the calibrated range is extremely good, as proven by continued accuracy over several months of use.

For measuring output of high voltage power supplies. Use terminal A and ground lead. Readings are taken as for low voltages. *Be careful not to touch bared ends of hot leads because of the shock hazard.* Scale is calibrated from 1 to 50 kv. Negligible loading is imposed on the circuit under test (multiplier totals over 70 megohms and firing current of bulb is only a few microamps.

Audio signal generator, using conventional relaxation-type oscillator circuit. Terminal B is connected to a convenient B-plus point in the set under test. Audio signal of approximately

1,000 cycles is taken from terminal C. It can be used for signal tracing in both audio and video amplifier circuits. Control is varied until desired tone at proper level is obtained. The setting will vary according to the amount of B-voltage used.

Signal tracing of all stages (front end, pix i.f. video, sound i.f., a.f., sync and sweep circuits). Uses a 1N34 crystal diode.




Probe lead is taken from terminal C and applied to circuit under test. Signals can be monitored by plugging phones into the jack or—what is usually more convenient—making use of the audio amplifier in the set. This is done by connecting terminal D to the volume control or to first a.f. grid. To prevent possible overload to crystal when tracing high amplitude signals, probe should be connected to terminal E, using potentiometer as an attenuator.

For tracing inaudible horizontal sync and sawtooth voltages, use a lead to jump test pulses to the a.f. amplifier input. Then use the neon voltage tester for visual indication by connecting C to the a.f. output plate. A little practice will enable the user to recognize the control setting which indicates approximately correct pulse levels. The setting at which the neon tube fires will of course vary somewhat with different amplifiers.



Control voltage for a.g.c. and sync stabilization. To obtain a small amount of negative voltage to stabilize a.g.c. during alignment, connect A or B to some negative voltage point in set, with black lead to chassis. Stabilizing voltage is taken from terminal E, and varied with control.

*Western Radio Television Inst.
Los Angeles, Calif.

2 3 4 5 6 7 8 9 10 11 12 13

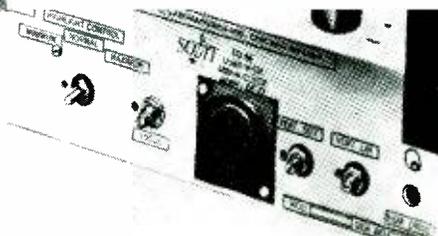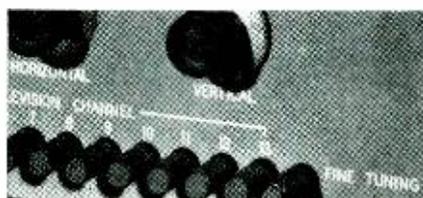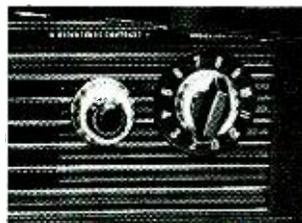

VERT. HOLD

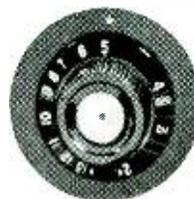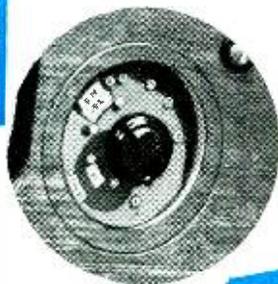

TV CONTROL TROUBLES

By DeLOSS TANNER

TV RECEIVERS often leave the factory with some of their controls giving best results when set close to one end of their range. Slight aging of tubes or components can then cause the correct constants to fall outside the range of these components (usually variable resistors). Then customers are dissatisfied and extra service calls result.

All the controls (especially the "user-adjust" ones at the front of the receiver) of course should reach correct settings at approximately the center of their ranges. (Incidentally, some of the control settings—such as focus—vary with the line voltage, and the service technician will find it worth while in these cases to try to duplicate the customer's evening line voltage when adjusting these controls.)

This article will be confined to controls on modern magnetically deflected sets. Some of the older sets had circuits

not used today. For example, the potentiometer as a horizontal drive control has been largely displaced by the variable trimmer capacitor. Some manufacturers still use a variable trimmer-type capacitor as a width control.

Before making any changes in control adjustments, check all parts in the circuit! Some component may be going bad and throwing the adjustment off.

Vertical hold control

If the picture does not sync in vertically or syncs in at the end of the control's range, first try replacing the vertical oscillator tube. If this makes no difference, check all components as above, especially the resistance of the hold control and the resistor (R1) in series with it (Fig. 1). If everything is approximately normal, increase or decrease the series resistance. If all or most of the resistance in the hold control is used to get the best setting, ob-

viously the series resistance should be increased, and if the control is "all out" for best results, it should be decreased. Try different values till the hold control syncs in near the center of its range. In some cases, the value of C1 may be incorrect. This will affect hold range, too.

Vertical height control

Values of parts in this circuit being normal, check line and B-voltages. Too low voltages can cause insufficient height (and width). Correct these troubles if present. If height is still insufficient, decrease the resistor R2 in series with the height control.

Notice that the height control has its largest effect on the bottom of the picture. This is normal. The vertical linearity control (Fig. 2) usually has its greatest effect on the top of the picture. Before varying the resistor in series with the linearity control check the vertical output tube by substitution.

RADIO-ELECTRONICS

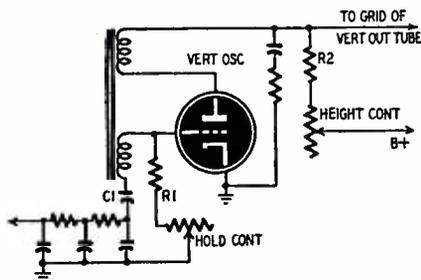


Fig. 1—A type of vertical oscillator.

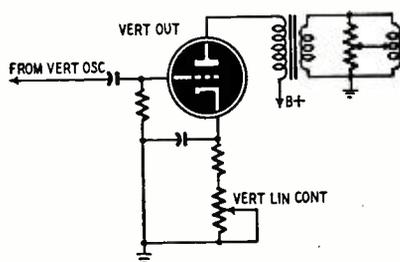


Fig. 2—Basic vertical output circuit.

Horizontal hold and lock

Read the article, "Servicing Horizontal Locks," on page 50 of the January issue. Follow manufacturers' instructions for adjusting the circuit. Since almost any component in the horizontal oscillator could be responsible for inadequate control range, the components check is especially important. Try replacing the horizontal oscillator tube first, then check the value of the hold control and its series resistor. Next in line for checking are the coils and capacitors.

Width control

Insufficient width with the control slug all in may be caused by low line voltage, poor tubes, low B voltages, or incorrectly adjusted horizontal drive control (Fig. 3). If there is not enough width with all voltages correct, try placing a paper bypass capacitor across the width coil. Use the smallest that will do the job, as the bigger it is, the lower the high voltage will be. A typical value would be .005 μf.

Horizontal linearity

This control usually has a limited effect on the picture. It will usually suffice to just leave it alone when adjusting the set. If adjustment is necessary, remember that the width and horizontal drive controls may have more effect on horizontal linearity than the linearity control itself. Using a test pattern, adjust all three controls alternately till linearity is good.

Focus controls

If a set comes into the shop with poor focus or with correct focus at one end of its rotation, check the voltage across the coil while rotating the control toward the end where best focus is obtained. If the voltage increases, the coil has too little current through it; if it decreases, it has too much.

Check the coil's resistance. It may be partly shorted out. If O.K., too much current may be due to high voltage, caused by having the drive control trimmer set too far out. If there are no drive lines in the picture throughout the pull-in range of the horizontal hold control, the drive adjustment is probably O.K. and it will be necessary to check further.

Lack of current through the focus control may be due to decreased current through stages whose return path is through it. Try replacing the audio-output tube, the horizontal-output tube

and the low-voltage rectifier, in that order. Other tubes may be guilty—as may be other components. Irregularities in the values of horizontal oscillator components may cause poor focus, along with decreased brightness and decreased picture width. If everything seems O.K. but the position of correct focus is near one end of the control setting, increase or decrease the resistance in series with the focus control (Fig. 4) or shunt an additional resistor across the coil.

Remember also that poor focus can be caused by a bad or gassy picture tube (though this is not common). In sets using a PM focus unit, poor focus may be due to too strong or too weak magnets. Where the unit is doubted, check with an exact replacement.

Brightness control

If the brightness control cannot be turned far enough up or down (or both) check it and other resistors between the video amplifier output and the picture tube before going ahead with a general components check. In sets where the video output is coupled through a d.c. resistance path to the cathode-ray tube, the resistor values may be critical.

In some sets the control's brightest setting may be limited excessively by design. Try a slight decrease of the resistance between the control and B-plus, but don't overdo it! Lack of brightness may be due also to incorrect ion trap adjustment, which may also damage the tube.

Centering controls

If a set uses electrical centering controls and the picture cannot be correctly centered with them, it will be necessary to adjust the focus coil and possibly the ion trap and yoke. Turn both centering controls to their center setting and shove the yoke as far ahead as it will go. Next adjust the ion trap. Read "Ion Burns" on page 34 of the February issue very carefully before attempting such adjustment. Next, adjust the focus coil by moving and tilting it till the picture is centered. After adjusting the focus control be sure to recheck the ion trap for maximum brightness.

Do not use the ion trap to eliminate shadows. Do it with the focus coil. If shadows persist and it is impossible to get rid of them while keeping the picture centered, try rotating the tube a little.

Sets with no electrical centering controls and without the centering attach-

ments or levers commonly found on the best modern receivers are harder to center, but the job can be done with care and patience. Remember that when the focus coil is moved the electron beam moves in a line perpendicular to the direction of movement.

Before attempting to center the picture it is often good to position the focus coil or magnet assembly so that its inner surface is equidistant from the outside of the neck all the way round.

Other controls

If you cannot get enough volume or contrast when these controls are all the way up it is usually not the fault of the control but of some other component or adjustment which is preventing the video or audio signal from being amplified normally.

Weak sound or video may be due to a poorly adjusted fine-tuning control, poor alignment, and of course, to weak tubes or defective components.

From the customer's point of view, the fine tuning control settings are the most important ones on the receiver. It is essential that they be adjusted so that stations come in best at or near their center settings. This is a question of oscillator adjustment and front-end alignment, and is covered in great detail in manufacturers' service data.

Control adjustment may seem a minor part of servicing, but it is very important in cutting service costs on future calls by reducing a situation that might otherwise call for pulling the chassis for a simple adjustment. And centered adjustments in controls accessible to the user are unparalleled prestige builders!

—end—

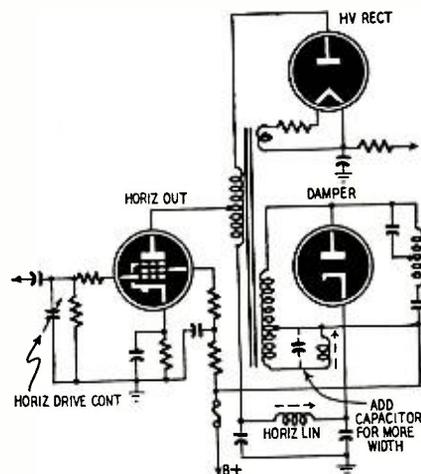


Fig. 3—A conventional flyback circuit.

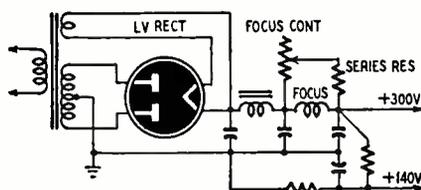


Fig. 4—Focus circuit used in some sets.



PEDRO and the INCENTIVE PLAN

By GUY SLAUGHTER

HE'S a little short guy in a beat-up felt hat, and his tiny mustache twitches like a rabbit's nose. He stands just inside the door for a long moment, the radio tucked under his arm, while his eyes dart about the store.

"Good morning," I say, leaning on the counter and wondering what he's looking for. "Got some radio trouble?"

His eyes stop on my face, then drop to the floor, and he shuffles up to me.

"Yeah," he says, in a high, whiney voice. "You the boss?" He looks almost disappointed when I nod, then taps the radio with his free hand. "It's got a whistle in it." He sets it down on the counter.

"Birdies, hunh?" I undo the line cord and plug it in. I flip it on and give it the quick once-over while it's warming up. It's a conventional little a.c.-d.c. job in a plastic cabinet, and it looks good for its three or four years of age; the cabinet isn't cracked, the dial glass is clean, and even the cardboard loop cover is intact.

The little set comes on and I tune the band. It isn't particularly hot, especially on the high end of the dial where the sensitivity falls way off, but it sounds pretty good. No trace of a birdie.

"Do you get the whistle all over the dial?" I ask, cutting the volume.

The little guy shakes his head, crinkles up his thin face, and his mustache twitches violently.

"Unh-uh!" he gurgles. "Just on WLW. You can hear the station okay, but there's a whistle on it."

"All the time?"

"Evenings, mostly. Not all the time." I flip the dial pointer to the 700 mark, and run the gain up. WLW is clear.

"Sounds okay," I say. "It's probably local interference in your area."

"Yeah?" the guy yeahs vaguely.

"Yup. But the set needs aligning anyway, so why don't you leave it a day or so? Then if the whistle shows up, we can fix that too."

The customer licks his lips, looks at the floor, and lets his mustache twitch twice.

"Okay," he agrees finally. "That'll be okay."

I reach under the counter for a job ticket.

"Name?"

"Hunh?" The mustache twitches.

"Your name?" I repeat.

"Oh. Yeah. Alverson. Frank Alverson."

I write it down, ask for his address, wait while the mustache twitches a couple more times, and write *it* down. The guy starts for the door, stuffing his claim stub into a worn wallet. But he pauses with his hand on the knob, turns back toward me, his eyes darting about the store again.

"I'm interested in a television," he whines. "Those for sale?" He jerks his head at the line of consoles along the wall.

"Sure," I say. "And I've got a good selection in back, too. If you'd care..."

"Not now," he interrupts me. "In a hurry. You here all the time?"

"Mornings," I nod. "And sometimes afternoons. Usually, though, I do my outside work in the afternoons."

"Anybody here then?"

"Oh, sure," I say. "We're open all day, and evenings by appointment. If I'm not here myself, Pedro can give you a demonstration."

The mustache twitches twice, he eyes one of the TV consoles for a moment while he digests this, and then he jerks the door open and shuffles out.

"Okay," he throws back over his shoulder at me. "Be seeing you."

I carry the little set back to the service bench, plug it in, and let it play while I dive into the line-up of chassis waiting there for me. It's still going strong with no sign of a birdie when Pedro shows up after lunch.

"Hi, Herk," he greets me, bustling in with a beat-up, sorry-looking chassis under his arm.

"Hi, Pedro," I return. I straighten up, grateful for an excuse to take a breather, and reach for a cigarette. "Where'd you get the relic?"

"It's home-made," he says, grinning at me and laying the alleged radio on the bench.

"No kidding." I try to ignore the messy-looking little two tuber, but the gobs of hookup wire hanging from its

innards finally get the better of my curiosity, and I give it the quick scan. Evidently it's been wired by a left-handed baboon with nine thumbs. Every soldered joint looks like a wad of crumpled-up tinfoil.

"Got to fix it," Pedro reports. "Noisy volume control. Carbon tet, hunh?"

"Depends," I say. "If it's just dirty, carbon tet'll do it. But if the resistance element is worn through in spots you'll have to replace the control."

Pedro's forehead wrinkles.

"Seems to me I read someplace you can fix 'em with a lead pencil."

"Not recommended. The graphite treatment is an emergency measure. Wartime stuff when you can't get controls."

Pedro jerks his thumb at his two-tuber, grins at me.

"It's a regenerative set," he confides. "You got two windings on the coil, and one of 'em feeds back part of the signal from the plate to the grid and that gives it lots of amplification."

"Well whattaya know," I breathe, playing it straight. "Clever, hunh?"

Pedro beams and nods.

"Lots of kids make 'em. We got a club."

"Great," I say. "Look, Pedro, lug these carcasses out to the truck, will you? I'm about ready to take off."

"Sure, Herk," he says, starting to pick up one of the chassis. Then he pauses, clears his throat, and I can tell something is coming. He fixes his big eyes on me and clears his throat again.

"Okay, kid," I say resignedly, leaning back against the bench. "What now?"

"I figure . . . I mean I think I should get a commission on sales," he says. "I got no kick on my wages, Herk, but I been reading about the 'incentive plan' and I'm for it."

"You would be," I laugh.

"No, I mean it Herk," he says seriously. "If I've got a personal interest in making a sale, I'll do a better job. See, Herk?"

I chuckle again, in spite of myself.

"Yeah, I see. But maybe it's a good idea at that. Okay, Pedro, you're on commission as of now. How does one percent of retail price suit you?"

RADIO-ELECTRONICS

"I figured on five. . . ." he begins, but I cut him off.

"That's settled, then," I say quickly. "Two percent commission you get on every set you sell, radio, TV, or whatever. Now lug those chassis out before I change my mind."

"Sure, Herk," Pedro says happily. "They're practically loaded."

"And Pedro," I add. "Keep your ear on that little a.c.-d.c. job while I'm gone. See if it develops a whistle on WLW."

"Roger," Pedro says, a chassis under each arm. "Can do, Herk."

I spend a few minutes on mustache's a.c.-d.c. set the next morning, checking for a loose or intermittently-open capacitor, or maybe a corroded chassis tie-lug. But I don't really expect to find anything, since the whistle only bothers WLW, so I finally settle for a realignment job.

"Tell this guy there's nothing wrong



with his radio," I instruct Pedro when he comes in. "Must be local interference on WLW in his neighborhood. And if he wants to look at a TV set you give him a demonstration, will you?"

"Sure will, Herk. For two percent I'll give him a good one."

"Load up the truck, then, so I can take off. I've got lots of stops today." I climb into my coat, fiddle around collecting call cards and mentally planning my itinerary, and he's all through by the time I get back to the bench again. "How's your regenerator?" I ask.

"Fine. Carbon tet did it."

"Glad to hear it. See you later, kid."

But it's late when I get back, and Pedro has already gone. The first thing I see is a note he has propped up on the cash register that almost gives me heart failure. It says I owe him nine dollars and thirty cents, and I cuss incentive plans whole-heartedly while I jerk open the cash drawer, a premonition of disaster nudging me. Sure enough there's a check inside, signed by one Frank Alverson. It's for four hundred sixty five dollars. Across the bottom Pedro has printed "payment in full for one RCA TV console combination."

So now I know why Frank Alverson has such shifty, darting eyes, why his mustache twitches, and why he has been careful to find out when I'm not in store.

I scramble through the job tickets in the day's pile, grab the one with Alverson's name on it, and head for the address it lists as fast as the truck can travel. It's a vacant lot. . . .

The cop is still there when Pedro comes into the shop the next day. He stares at the uniform with big, round eyes, and then fixes his gaze on me.

"In trouble again, Herk?" he asks.

"Yeah," I snap. "But not like you think. How'd he haul the TV set away?"

"Who?" Pedro asks. Suddenly comprehension dawns on his face. "Oh, him. He had a truck."

The cop goes to work on Pedro, then, throwing questions right and left. Did he get the license number? Didn't he suspect the guy of being a rubber check artist? Did he have any scars or marks that might make identification easy? Had he ever seen him before? Did he have any kind of an accent? What did it say on the side of the truck? Finally he turns back to me, shoulders hunched.

"What've we got to go on?" he asks sadly. "It's prob'ly the same gee that's been passin' checks for TV sets all over town, but he don't leave a trace."

"You've got a description," I say wearily. "That should help."

"Sure," the cop growls disgustedly. "A little guy in a beat-up felt hat and a mustache. I should have a buck for every guy in town who looks like that."

"Yeah," I say. "I'll go through it again. Maybe I missed something." So I tell the whole incident of his coming into the shop with the radio, and describe every move either of us made, every word either of us said. When I finish Pedro is looking at me queerly.

"Hey, Herk," he says. "You going to pay me my commission?"

I draw my hand back into firing position, but he jumps out of reach.

"Well, then, if we find the guy and get the set back will you pay me my commission?"

"Yeah," I snort. "The day we find him you get paid."

"Tomorrow, maybe today yet," Pedro says smugly. "I'll find him. See you later, Herk," he calls back over his shoulder, and then the door slams shut behind him.

"—he worked for me I'd can him," the cop mutters darkly. "Takin' a bum check like that."

I wave a hand wearily.

"My own fault. I should have spotted the guy for a phoney when I first saw him. Besides, Pedro's just a kid, and this incentive plan made him too eager for a sale. I should have warned him about things like that."

"Yeah," the cop says. "Well, we'll let you know if anythin' turns up." He smiles feebly and leaves.

"Fine," I say without enthusiasm. "Do that." I wander back to the bench and dive into a chassis. Pedro doesn't show up again, so I work there until closing. After that I stop off for a hamburger and fiddle around uptown a while, so it's late when I get home. There is a figure waiting for me on the porch. It's Pedro.

"Hi, Herk," he says with elaborate casualness. "Nice evening."

"Yeah," I return suspiciously. "Ain't it."

"Herk," Pedro goes on, gazing up at the streetlight, "let's get it straight. If I find the guy I get my commission. Right?"

"Forget it, kid," I say gruffly. "We

just ain't going to find that bozo."

"But if," Pedro insists. "If I find him, I get paid, hunh?"

"Sure," I nod. "Sure. But. . . ."

"I found him," Pedro cuts in proudly. "And I called the cops and they took him down to the station. You got to identify him and claim your TV set."

"Look," I say severely. "If you're pulling my leg, I'll break every bone. . . ."

"No kidding, Herk," Pedro assures me solemnly. "It was easy. You said the whistle on his radio was local interference in his neighborhood, so we found his neighborhood."

"How?" I demand. "And who's 'we'?"

"My radio club. We got guys all over town. So I called a meeting and told everybody to monitor WLW. Three guys finally heard the whistle come on about seven o'clock, and phoned me."

"Yeah," I say. "But. . . ."

"So I rode my bike over to their bailiwick and tracked down the whistle with my portable radio."

I just nod my head dumbly, and Pedro goes on.

"Where the whistle was the loudest there was a house with a big, long aerial running to a tree, and through the window I could see a kid listening to a home-made set. I beat on the door. A lady came, and I asked for her boy."

"Yeah," I say again. "But. . . ."

"I asked the kid if he always listened to WLW, and he said that was the only station his regenerator could get any good." Pedro shakes his head pityingly. "He was a dumb kid, Herk. He had his aerial coupled too tight, and he didn't know how to tune his rig right. Anyway, I asked him if he ever saw a little short man with a mustache and a funny hat around the neighborhood."

"Hey," I breathe reverently, a bell ringing in my head. "Pedro, that was smart figuring."



"Yup," he agrees, matter-of-factly. "So the kid said a guy that looked like that lived right across the street. I called the cops, and there he was. Our TV set was in the garage, and there were half a dozen more, too."

"Pedro," I mumble, my head starting to spin again. "You're a genius."

"I wouldn't say that, exactly," he says, staring modestly down at his shoe. "I'm just on the ball." Then he holds out his hand, fixes his eyes on my face, and breaks into a big grin. "For a commission, of course. Great stuff, this incentive plan, hunh Herk?"

"Yeah," I say reverently, digging deep for a ten-dollar bill. "Yeah, Pedro. Damned if it ain't!"

—end—

TV SERVICE CLINIC



Conducted by MATTHEW MANDL

ALL television receivers in use today are unfortunately not designed for the ideal 4-mc i.f. bandpass. If the video i.f. amplifier consists of only two or three stages, bandwidth is sacrificed in order to get adequate gain. This poses an impossible problem for the servicing technician when the customer insists on better picture quality.

If slight defects in the receiver are contributing to the poor definition, corrective measures can often be taken. Careful checks should be made on the focus control system, the video i.f. alignment, the r.f. tracking, and the antenna system. With these working at peak performance, remarkable improvement is often realized.

Initial checks should be made on the focus control circuit. If the focus control requires an extreme setting, or is entirely ineffective, the voltage across the focus coil as well as the current through the resistive network of the control should be tested against manufacturers data. Changes in resistance values in the focus control circuit or a defective focus coil can bring about inability to secure good focus. Low or abnormal high voltage can also produce defocusing.

If the focus control gives best results at around mid-range but the picture is not satisfactory then the trouble, most likely, is elsewhere. This could include improper alignment of the i.f. system or poor tracking in the tuner. Improper alignment gives poor picture quality on all stations, while improper tracking may affect only some stations. This depends on the tuner used. Poor tracking is sometimes encountered in the drum type tuners using plug-in coils.

A contributing cause to poor picture quality would be standing waves on the transmission line. A mismatch between the line and the receiver input means that all the energy is not absorbed by the receiver's r.f. stage. The unabsorbed energy is reflected back to the antenna and sent back down the line again. Simultaneous reception of the direct signal and the reflected sig-

nal of the lead-in can displace picture line structure enough to blur the picture. The length of the line may not be sufficient to cause severe displacement—such as occurs during ghost reception. A small displacement will, however, blur the picture. This is shown in the photo above in which line reflections were present. The photo at the left on the opposite page shows the same receiver on another channel which, due to the difference in frequency, allows a better match between the antenna and receiver. Matching the transmission line to the receiver impedance will help a great deal on blurry channels. Of course, any mis-orientation of the antenna to the station being received will ordinarily make any further work on the picture in vain (photo at the right).

"Ringing" or a slight "echo" effect which causes repeats to the right of sharp vertical lines due to transient oscillations in the picture system can also cause poor picture quality. This calls for a check of the peaking coils in the video amplifier and, in addition, the r.f. tracking and i.f. alignment. If the video response curve favors the high-frequency sideband components, r.f. or i.f. stages can easily be pulsed into damped oscillations.

An oval beam within the picture tube instead of a perfectly round beam will cause poor definition. This can be ascertained by rotating the picture tube approximately 90 degrees. In such a case, if the horizontal wedge is slightly obscured but the vertical wedge is clear the opposite would be true after the tube is turned. This immediately gives an indication of an incorrectly formed electron beam which cannot be focused to a circular pin-point on the phosphor screen. Tube replacement is, of course, necessary in correcting this condition.

Intermittent Ghost

In a Tech-Master receiver the picture seems to have a ghost after the first fifteen minutes of warm-up. The picture also becomes slightly blurred. If the station selector is turned the ghost disappears. Within fifteen to twenty minutes, however, the ghost re-

appears. Twisting the station selector always causes the ghost to disappear. The condition exists on all stations and is affected by fine tuning. I have checked all tubes. J. A., Brooklyn, N. Y.

True ghost reception can only be caused by receiving a reflected signal as well as a direct signal from the station simultaneously. What often appears as a ghost, however, is the condition known as echo effect in which picture displacement is very small at all times. Ghosts may show a picture displacement from a small separation to as much as an inch or two, depending on arrival time and screen size. Your condition appears to be caused by a defective component which changes the resonant condition of your tuner and blurred picture and echo effect.


An intermittent shunting resistor such as the 3,900-ohm resistor across the grid coil of the r.f. amplifier can bring this about. Inasmuch as there also are resistors across the primary and secondary of the transformer between the r.f. amplifier and the mixer, these *could* give trouble. Check these as well as tubes and other parts in the tuner. A change of value and a reduction of bandwidth would increase the Q of the circuit. The narrowed bandpass would destroy fine detail and cause "ringing." A change in the high-frequency sideband components would also cause some echo effect due to excess amplification in that part of the picture spectrum.

Narrow Focus

On an Admiral 10-inch receiver I have trouble getting good focus over most of the tube face. Adjusting the focus control causes the center focused area to split into two sections. How can I extend the focus across the face of the tube? B. M., Buffalo, N. Y.

The focus conditions you describe can be improved somewhat by careful positioning of the focus coil with respect to the yoke. Make sure the latter is snug against the flare of the tube. With improper positioning, narrow focus is obtained as you describe. Adjustment of the focus control will split up the

RADIO-ELECTRONICS

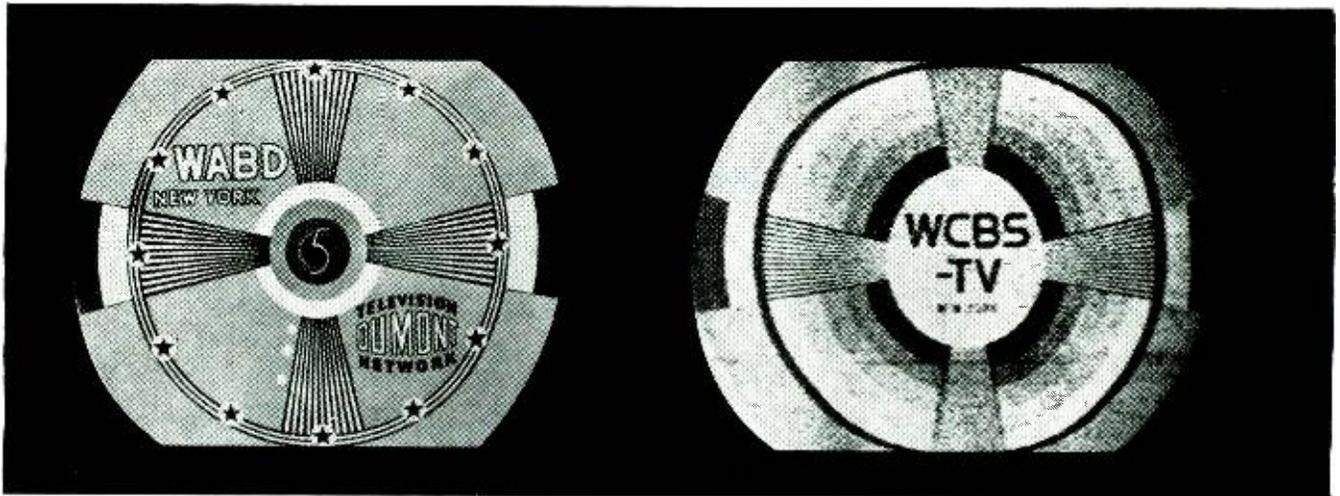

focus as you observed, giving sharp focus at the edges and not at the center, or vice-versa.

Only by using special types of yokes such as the "cosine" type specially designed for full focus, can you get sharp focus over the entire tube face up to the very edges. By carefully experimenting with the focus coil setting, however, you should be able to get some improvement.

Poor Vertical Linearity

In a Trav—ler 16G50A receiver, the vertical linearity is very poor and cannot be corrected with the controls. Also, on fine tuning or contrast adjustments the picture pulls sharply to the side. Tube replacements have not helped the pulling condition. H. C., New Orleans, La.

You should try a new 6S4 vertical output tube. If this does not improve vertical linearity try a new 100- μ f capacitor in the cathode circuit of the output tube. After the new capacitor is installed, readjust the linearity control to see whether or not good linearity can be secured. If the control is still ineffective, check the series resistor associated with it as well as the control itself.

If the picture pulls when the fine tuning or contrast is adjusted it would indicate troubles in the a.g.c. system. If a new 6AL5 detector a.g.c. tube does not help, check all resistors and capacitors in the a.g.c. feed line to the r.f. and i.f. amplifier tubes.

X-Ray Radiation

What is the danger of X-Rays from picture tubes during servicing procedures? I. G., Lonsdale, R. I.

X-Ray radiation is more of a factor with projection type picture tubes in which second anode voltages of 20,000 to 30,000 are encountered. Consequently—aside from the glaring image—projection tubes should not be viewed directly during servicing. In actual service these tubes are housed in a metal barrel which eliminates radiation hazard.

The larger 24- and 30-inch picture tubes using anode voltages in excess

of 20,000 volts exhibit some X-Ray radiation; but it is of such low intensity that the protective panel glass filters it out.

With the protective glass removed, as when the set is on the bench, the danger is of course increased, especially for long and repeated exposure. The best rule is to keep out of the beam path as much as possible.

Repeated Rectifier Failure

In a Zenith Model H-2352 receiver the high voltage rectifier 1X2 constantly goes bad. I have changed the rectifier to a 1B3-GT with the same results. There is arcing within the tube if the horizontal drive is advanced, but a reduction of drive results in loss of brightness and insufficient width. I have changed the horizontal output tubes as well as the high-voltage filter capacitor but this did not help. The line voltage is normal in this area. H. F., Anderson, Ind.

Excessive drive will shorten the life of the high-voltage rectifier tube. The fact that the reduction of drive decreases your brightness may be caused by an improperly adjusted ion trap. Adjust the ion trap with a rotary, back and forth movement for maximum brilliancy. If this fails to give you sufficient brilliance and it is necessary to advance the drive control to the point of arcing, place a 4.7-ohm, $\frac{1}{2}$ -watt wire-wound insulated resistor in series with the filament lead of the 1X2 rectifier tube.

On some Zenith receivers a 2.2 ohm resistor was used but this value may not be high enough. A 5.6 ohm can also be used, though the 4.7 is preferable. As a last resort try decreasing the plate voltage to the horizontal output tubes by approximately 30 volts.

Picture Bounce

In an Arvin receiver, Model 2160, the picture has a continuous jump. It does not roll but has a bounce for all stations. I have checked tubes and parts in the vertical oscillator. R. P., Clio, S. C.

This would indicate defective components in the vertical sweep system.

Inasmuch as you have checked tubes as well as the components, the trouble may lie in the integrating network which pulses the vertical sweep oscillator. Check the sync separator tubes and parts also for these could contribute some instability in the vertical circuit not apparent in the horizontal system due to the lock stabilization. You do not state whether you replaced any resistors in the vertical system; however, any of them off by more than 10% of rated value should be replaced. The trouble, probably, is in the integrating network of resistors and capacitors at the input of the vertical sweep oscillator.

Reduced Width

On a Capehart TV receiver the picture is compressed at both sides and I am unable to correct this condition. This model (CX-33L) has no width control and the picture width can only be changed by the horizontal drive. Previous models included a width control. How can I correct the reduced width? H. S., Baltimore, Md.


The reduction of width can be caused by a defective 6BG6-G horizontal output tube or a defective 6SN7-GT horizontal oscillator-discharge tube. You should try these tube substitutions first. If replacement fails to correct the trouble check the .1- μ f, 200-volt capacitor in the cathode circuit of the 6BG6-G output tube.

If the trouble persists the following changes recommended by the manufacturer should be tried. On some Capehart CX-33L models these changes have already been made:

1. Add a .1 μ f, 200 volt capacitor across the R-291 cathode resistor of the 6BG6 tube.
2. Change R-286 (this may be 150,000 ohms in some early models) to 47,000 ohms.
3. Connect a 30- μ f, 6,000-volt capacitor from the cathode of the 6W4-GT to ground. If additional width is needed, connect the capacitor from the 6BG6-G plate to ground.
4. Interchange coupling capacitors C253 and C257, .0047 and .001 μ f, respectively.

—end—

...IMPROVING

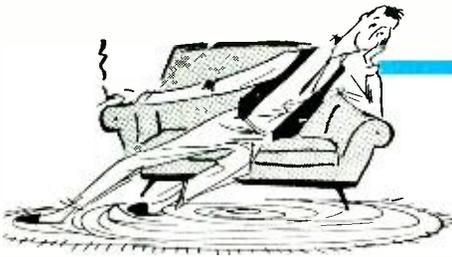

By **NATHAN GROSSMAN**

AUDIO enthusiasts and sound men often complain that amplifiers and speaker systems, despite theoretical excellence, fail to come up to expected standards in "listenability." Sometimes there is a lack of upper treble response, or bass, or the presence of some undesirable effect on the ear. Many audio installations have to be modified to get optimum results.

The need for modification arises from differences in listener preferences, room conditions, speakers, speaker housings and positions, and also from inadequate compensation for Fletcher-Munson effects (loss of bass and treble at lower listening levels). Many amplifiers, including some of the better ones, do not provide enough or proper bass or treble boost to cope with these effects. Bass boost should begin as high as 800 cycles and be able to furnish as much as 20 db compensation at the low-frequency end; treble boost should begin above 1500 cycles and be able to furnish as much as 15 db compensation at the higher frequencies.

Much of the desired range compensation can be made in the amplifier and some with the speaker. Sometimes it is necessary to make adjustments to both simultaneously.

Fig. 1 shows the principal points where changes in the audio amplifier can be made. These are:

1. the de-emphasis capacitor in the FM receiver;
2. the RC constant of the d.c. blocking capacitor and the grid resistor of the interstage coupling in resistance-coupled amplifiers;
3. the cathode bypass capacitors;
4. the R-C constant of the bass boost

- (R2, C1) and the amount of the boost;
5. the R-C constant of the treble boost (R5, C2) and the amount of the boost;
6. the d.c. blocking capacitor in the plate circuit of the interstage audio transformer (Fig. 2).

7. the R-C constant of the inverse feedback circuit (R3, C3);

8. the speaker treble pass capacitor;
9. the potentiometer across the tweeter controlling the amount of energy fed into this speaker.

The frequencies emphasized or depressed will influence the pleasantness or realism of the sound. Emphasis at about 2,000 cycles will cause shrillness without real improvement in the treble, whereas, emphasis above 4,000 cycles will tend to overcome Fletcher-Munson effects and produce realism in speech and in the sound of metal musical instruments, or metal-stringed ones. If the starting point of the de-emphasis in the output of the FM tuner, at point 1 of Fig. 1 is too low, say, 500 cycles or lower, it will cut out much *edge*. If bass boost starts too high, say 1,500 cycles, and is used in conjunction with a record player employing a crystal pickup, *boominess* will result.

The resistor and capacitor combinations at points 2, 3, 4, 5, and 7, will determine the frequency of the point at which the boost or depression begins to operate. The following table lists these:

R (in ohms) × C (in uf)	Starting frequency
80	2,000
100	1,600
333	500
400	400
800	200
1600	100
8000	20

If we want bass boost below 500 cycles, then the resistor and capacitor at points 4 or 7, in Fig. 1 should result in a product of 333. The maximum amount

of boost will be determined by the ratios of the resistors which form the voltage divider in these two circuits. At point 4 the voltage divider is roughly R2 plus reactance of C1 divided by R1 plus R2 plus reactance of C1. As the reactance of the shunt capacitor increases with the lowering of frequency, the ratio of the voltage step-down decreases so that bass is boosted. We can increase the amount of boost by decreasing either R2 or C1. However, a change in either of the latter without a corresponding change in the other will change the frequency at which the bass boost begins to operate. At point 7 the voltage divider is roughly R4 divided by R4 plus R3 plus reactance of C3, and operates in the same way that the voltage divider at point 4 does. Since the ratio of R3 to R4 is determined by other considerations, an increase in bass boost can be obtained by decreasing the value of C3; by doing so there will be less inverse feedback as the reactance of C3 increases with lowering frequency.

In many commercially built amplifiers the bass response may be improved by adding capacitors across the bias resistors at point 3 in Fig. 1, or increasing the values of the ones already in the amplifier. In practice the R-C of the bias circuit of the amplifier and output stages should equal 25,000 for full bass response.

In the older amplifiers bass can be improved by removing the direct current from the primary of the interstage transformer, by using parallel feed such as at point 6 (Fig. 2). This change will produce an improvement of from 2 to 5 db in the low register.

Where it is desired to cut down bass, the capacitors at points 2, and 3, in Fig. 1 should be reduced in value so that the product of the resistor and capacitor combination is below 8,000. The value of the capacitor at point 7, in Fig. 1, on the contrary has to be increased to reduce bass. This will shift the frequency at which a boost of about 2 db generally occurs, to a point lower in the bass spectrum and below the audible range, where cutting-off factors may be operating.

Suppose that we want treble boost of only the extreme highs. In such a case the product of the resistor and capacitor combination at point 5 in Fig. 1 should be about 80. The boost obtained at this point is also through a voltage divider, which is roughly R6/R6 plus R5. As the reactance of the capacitor shunting R5 decreases with rise in frequency the effective impedance of the combination becomes smaller until there is no longer a voltage divider and no

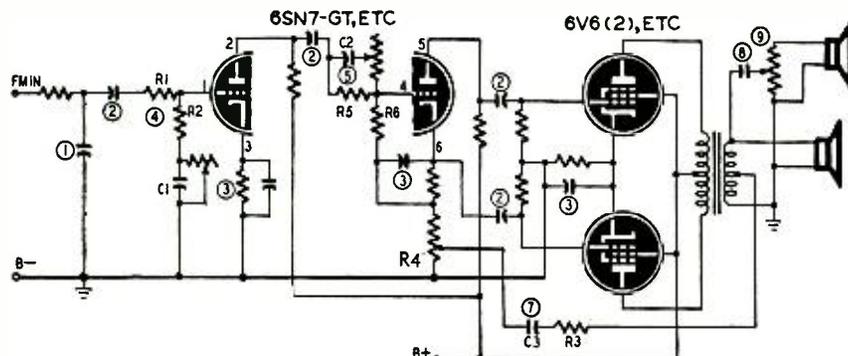


Fig. 1—The diagram of an amplifier with separate bass and treble compensation.

"LISTENABILITY"

loss on the higher treble frequencies. Treble boost can be increased by decreasing R6, increasing R5, or increasing the value of the capacitor across it. When either is changed without a corresponding change in the other, the treble boost is started at a lower frequency.

It is possible to use the volume control to get some treble boost without any loss in gain. The volume control in an audio amplifier is a voltage divider (Fig. 3). When the usual operation of the amplifier is such as to permit the arm of the volume-control potentiometer to be set at mid-position or lower, considerable gain in higher treble frequencies can be obtained by placing a small shunting capacitor across the input and arm. The resistance between the input and the usual setting of the arm should be regarded as similar to R5 at

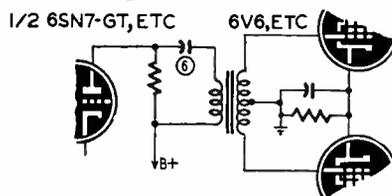


Fig. 2—Bass is improved by this change.

point 5. By measuring the resistance of this part of the volume control, the size of the shunting capacitor can be calculated. To overcome the loss of highs from Miller effect due to the input capacitance of high- μ triode amplifier tubes the R-C should be about 40; to compensate for falling off of high frequencies in output transformers or speakers the R-C should be between 60 and 120; and where clarity and crispness of speech is desired the R-C should be between 150 and 300. We have used the circuit in Fig. 3 with a low-priced speaker and crystal microphone in a system used for voice amplification and occasional dance music from a record player. When the microphone was used the switch was closed, and considerable treble boost was obtained, although the bass boost control was not touched.


Despite the excellence of published response curves some speaker systems may seem to lack treble or "edge". This loss is often due to the way the tweeter or speaker is mounted in the baffle. Placing the tweeter low in the speaker housing will direct the treble frequencies where they will be absorbed by furniture and carpets. Interesting but annoying to many sound men has been the loss of edge when a tweeter with a multicell horn is mounted so that the entire mouth of the tweeter is recessed behind the line of the front panel of the speaker cabinet. In one such cabinet the pub-

lished curve showed a 10-db drop at the very high audio frequencies. This can be corrected by moving the tweeter forward so that the entire mouth of the horn is out of the cabinet. An effective way to secure edge from a horn-type tweeter is to take it entirely out of the cabinet and place it on top. By doing so, not only is the bad effect of the speaker cabinet upon the tweeter overcome, but in addition the axis of projection of sound from the tweeter is raised slightly from the horizontal. The result is that most of the sound energy goes directly into the area of the room where the listening is usually done, and is not dissipated on furniture and rugs. However, separating the tweeter and woofer too much will cause loss of presence. Some critical listeners may be dissatisfied with this solution. Where a single broad-range, or coaxial speaker is used, the highs may be lost by placing the speaker near a cloth-covered chair, or on a floor which tilts the speaker cabinet so that sound is projected slightly downward. In the first case, adjustments in the amplifier were of no avail. However, when the speaker cabinet was accidentally moved but six inches further away from this chair, high treble was heard again. The effect of the tilted floor was overcome by placing thick coasters under the front legs of the speaker cabinet; and in one instance, by tilting back about two inches the upper edge of the panel on which the speaker was mounted, allowing a still greater rise to the speaker axis.

Maximum bass can be obtained from a speaker when it is placed on the floor and in the corner of the room. The three sides of the corner act as a continuation of the baffle. Conversely, of course, moving the speaker from such a position reduces excess bass rendition. The writer has seen installations where the speakers were mounted near the ceiling and tilted upwards. This caused bass almost to disappear.

When a reflex housing is used, bass can be reduced by closing the port.

Students of speaker characteristics have found that the same speaker in various positions in the room gives different response curves. Differences in the shapes of rooms, placement of furniture, and sound-reflecting and sound-absorbing materials in the listening area, affect speaker response. For this reason sound men will often say that in some rooms all speakers, regardless of their original tonal characteristics, will sound too bassy, or on the other hand too shrill. On one occasion we tried the same sound system in two adjoining rooms; in one of these the higher

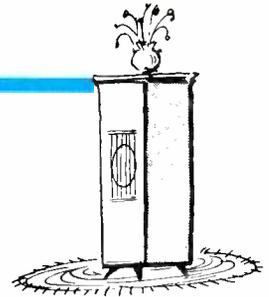

treble frequencies were attenuated to the vanishing point. On another occasion, we tried the same system in two meeting rooms of about the same size. In one room the speaker was pointed across the room width. About 70 persons were present. Speech was clear and distinctly heard throughout the room. In the other room, one side of which was heavily draped, the speaker was pointed down its length. Only 20 persons were present. Yet with the treble control set at maximum, speech was muffled and indistinct.

The output of the tweeter may be cut

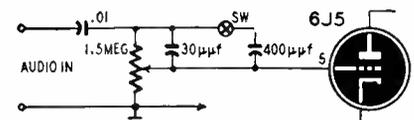


Fig. 3—A useful treble boost circuit.

by reducing the size of the capacitor at point 8, in Fig. 1. Even where a crossover network is employed, an effective method is to use a 5-50-ohm potentiometer across the tweeter as shown at point 9 in Fig. 1. This is often a necessity with a horn type of tweeter as it is generally more efficient than the direct-radiator woofer.

Connecting the tweeter out of phase with the woofer may depress some frequencies.

Speaker phasing sometimes produces tricky effects. We once made an installation in which a considerable amount of bass without sacrifice of tone range was desired, to furnish dance music in the social hall of a summer resort. A loud speaker capable of handling a considerable amount of power but with a limited tone range and inadequate bass already was in use. This speaker had been mounted on a large celotex baffle at the juncture of wall and ceiling, with the speaker aimed down the length of the room. We placed a wide-range speaker in a bass-reflex cabinet on the floor about 15 feet away from the first speaker facing the width of the room. This speaker was connected in series with the first speaker. Only a slight improvement in over-all and bass response resulted. There was, however, good distribution of sound throughout the room. The leads of the new speaker were then reversed, and the over-all range and bass improved considerably.

—end—

ELECTRONICS and MUSIC



Part XXI—Second half of a discussion of the Consonata—keying, mixing, and tremolo injection circuitry.

By RICHARD H. DORF

LAST month I showed in Fig. 3 how a single oscillator may be keyed. The actual system, however, is more complex because of the couplers, each of which is a 73-pole, single-throw relay.

The circuit is diagrammed in Fig. 1. The figure shows only the seven C's of the swell manual, but the same switching system and the same relays are used for all the 61 notes of the swell manual. Another complete system is used for the great.

Each key operates a 5-pole, single-throw, normally open switch. One side of all poles is a common so that when the key is pressed all contacts come together. There are 5 relay coils at the left. Each of these, when energized, attracts all 73 contacts (only 7 of which are shown).

Seventy-three oscillators are provided for each manual. Sixty-one of them correspond to the 61 keys of the 5-octave manual and the other 12 are

added to obtain 4-foot tones (one octave above the key pressed). Each oscillator grid resistor junction is wired to a bus to which the relay contacts are closed.

To see how this operates, let us concentrate on the key switch corresponding to middle C, which is labeled C3 in Fig. 1. Assume that we have closed the SWELL UNISON switch, energizing the swell unison relay. This causes contact A of the relay to make with the bus connected to the oscillator generating note C3. It also causes all the relay contacts in a horizontal line with contact A to close with their respective oscillator buses.

Now, pressing key C3, the right-hand key switch contact connects the rest of the contacts either to ground or to the tremolo generator output, depending on the position of the tremolo switch. The second-from-right switch contact goes to a relay contact which is not touching its bus. But the center switch contact goes to relay contact A, which is touch-

ing its bus. The grid of oscillator C3 is now grounded for d.c. and that note is routed to the amplifier circuits.

The same is true for any other key switch. Pressing key C5, for instance, connects ground through relay contact B, which is also touching its bus, to oscillator C5. Hence, pressing any key will produce a tone of the pitch corresponding to that key.

Let us also close the SWELL 16 switch. This energizes the swell 16 relay and presses all contacts in a horizontal line with that relay to their busses. Now when we press key C3, the left-hand contact of the key switch connects ground, through contact C of the relay, to oscillator C2, and we hear not only the tone of C3 but also that of C2 one octave lower. Thus we have added the 16-foot register to the tones we are playing. Similarly, closing the SWELL 4 or SWELL 2 switches adds tones one and two octaves above our middle C. Of course, the same will happen with

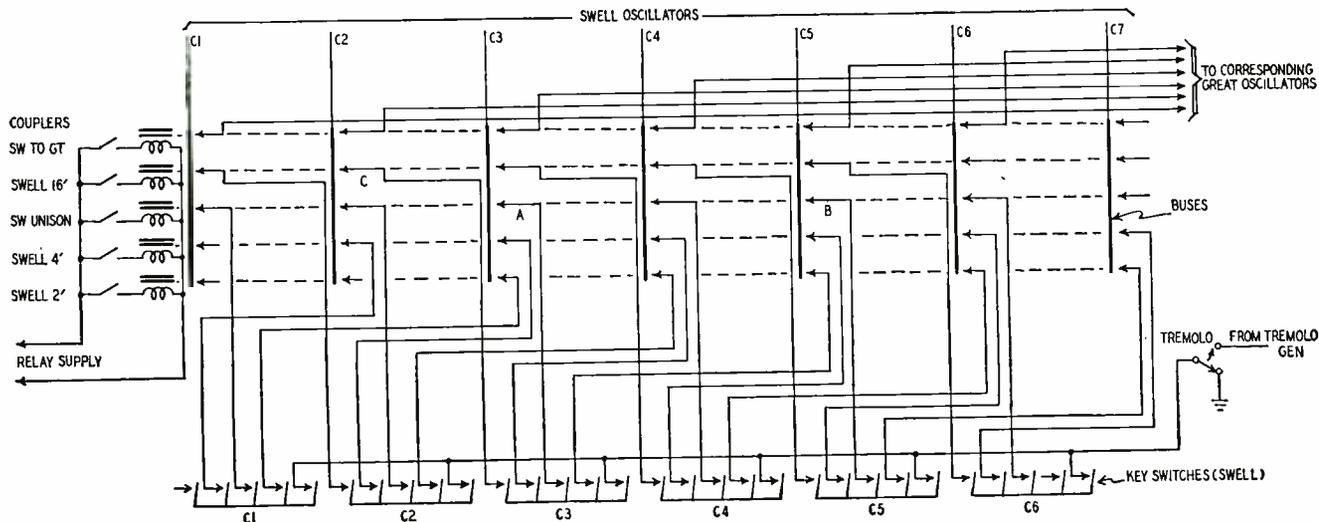


Fig. 1—The swell manual keying system. Each of the five coupler relays (shown at left) is connected to 73 oscillators.



Front view. Tube sockets act as jacks for speaker and cutter.

COMPACT MULTI-PURPOSE AMPLIFIER

By JOHN W. STRAEDE

THE amplifier described here is a very compact job suitable for public address work, recording and playback. It is high powered for its size, yet reliable because of the comparative simplicity of its circuit.

Constants are so chosen that either 6V6's or 6L6's (or English or Dutch EL5G tubes) can be used for the push-pull output stage, the power output being 15 or 22 watts for 6V6 or 6L6 tubes respectively. Even with the small 6V6 tubes (there's enough room for glass envelope 6L6's), sound can be projected up to a mile or more if efficient longhorn type speakers are used.

Although the circuit is very similar to that of the simpler conventional three-stage amplifiers, there are several slight additions. Each one is small but nevertheless adds to the value of the complete job. Electrolytic capacitors are connected in series on the high-voltage side of the filter circuit for increased reliability. Low-voltage electrolytics are completely avoided.

Some of the controls are in the form of toggle switches as it is thought that four knobs are quite enough adjustments for any operator to worry over—a switch is something definite!

A simple output filter consisting of a rotary switch and an assortment of high-voltage capacitors is connected across the primary of the output transformer and provides a more rapid attenuation of the highs than does the usual capacitor and variable resistor in the plate circuit of a previous tube. The reasons for this greater effectiveness are in the inductance and the leakage reactance of the output transformer. This output filter (together with a bass-attenuation or speech-music switch), is the only provision for controlling the tone of reproduced sound when the microphone input is used. It seems quite adequate, possibly because when using a microphone you are at least starting with real and therefore 100% fidelity sound, while when playing from a disc you may be starting with almost anything under the sun.

Speech-music control

One toggle switch, the speech-music switch S3 (so called because lower fre-

quencies are often deliberately attenuated when reproducing speech), acts in two ways. The switch is a double one—it breaks one circuit while closing another. When switched to **SPEECH** an extra .001- μ f capacitor is placed in series with the grid of the top 6V6. This small capacitor has a high reactance at low frequencies, attenuating them greatly. This is a distinct advantage in recording and in public address work, particularly if a ribbon microphone is used. The attenuation is limited by a 1.5-megohm resistor. In the other position, the capacitor is shorted out, but a peculiar network comes into operation in the phase-changing circuit.

Phase inverters often suffer from a false shift at lower frequencies, so that the two output signals are not quite 180 degrees out of phase. Also the "second" signal to the lower output tube is often smaller at the lower frequencies. The simple phase-shift network shown helps to compensate for the deficiencies. At high frequencies the reactance of the 0.25- μ f capacitor is negligible and the 10,000 and 22,000-ohm resistors are effectively in parallel, equivalent to about 7,000 ohms. At low frequencies, the impedance rises (becoming 10,000 ohms at zero frequency). This gives the lower output tube more signal. If you are interested in experimenting, try interchanging the 10,000 and 22,000-ohm resistors—you'll get quite a bass-boost effect.

Two other toggle switches (S1 and S2) are ON-OFF and CUTTER-SPEAKER controls. The first is a simple s.p.s.t. in the line; the other connects a high-impedance cutting head to the primary of the output transformer or a pair of low-impedance dynamic speakers to the secondary. Like the **SPEECH-MUSIC** switch it breaks one circuit while closing another.

Recording monitor

It will be noted that one pair of contacts is shunted by a small resistor, so that the speakers are operating faintly while the cutter is in action. This provides either a monitor action or extra reverberation, depending upon whether or not the speakers are located

in the same room as the microphone. 56 ohms, ½ watt is usually suitable though the optimum value depends on the voice-coil impedance.

If the speaker field coils are used as B+ filter chokes, at least one speaker must be plugged in at all times.


When using a pick-up, tone is controlled in three ways: Not only can the output filter be used to give a sudden "chop" (preferably just below the needle resonant frequency if a wide-range pick-up is used), but the bass can be attenuated by the speech-music switch (handy if you're using some cheap crystal pick-up with no decent high-frequency response). The general balance between "highs" and "lows" can be adjusted by a simple variable resistance connected in the pick-up filter. When the pick-up tone control is set at one end an extra bypass capacitor (Cd in the circuit diagram), is connected across the pick-up input causing a reduction of the high frequency response. When set at the opposite end, the bass boost network is put out of action by the shorting of capacitor Cc. At the midway position the tone control affects neither the highs nor the lows.

Bass compensation

The pick-up "filter" is practically a standard bass-boost network (see Bibliography for reference), consisting of resistors Ra and Rb and capacitor Cc. There are also two fixed capacitors Ca and Cb, the former to give moderately sharp cut-off at the highest frequency to be reproduced, the latter to balance the customary treble-boost found in most modern records.

The values of Ca, etc., depend upon the type of pick-up used and average characteristics of the records most often played. Typical values are given in Table I for two English pick-ups, one American and the writer's own needle-armature magnetic.

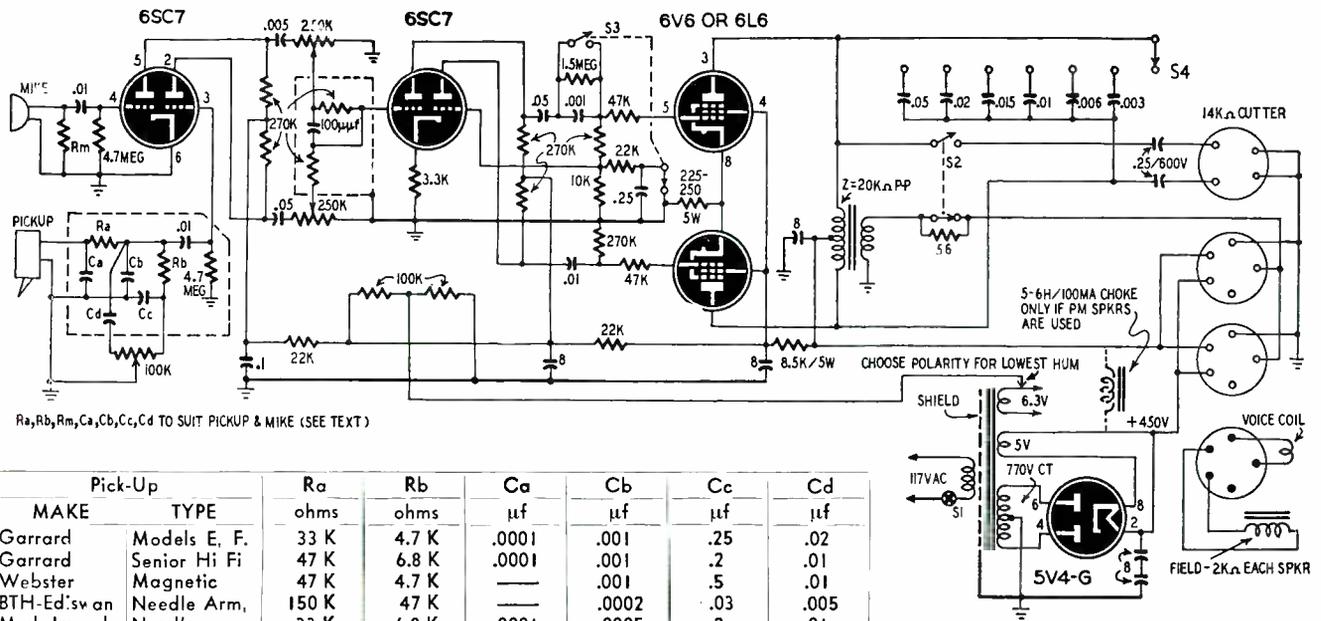Although the basic amplifier circuit is standard, there are a few small points worth considering: Two-in-one tubes are used thus keeping the layout compact and wiring short, resulting in low hum level. Both microphone and pick-up pre-amplifiers (the first 6SC7 tube), are grid-leak biased to keep



Ra, Rb, Rm, Ca, Cb, Cc, Cd TO SUIT PICKUP & MIKE (SEE TEXT)

Pick-Up		Ra	Rb	Ca	Cb	Cc	Cd
MAKE	TYPE	ohms	ohms	μf	μf	μf	μf
Garrard	Models E. F.	33 K	4.7 K	.0001	.001	.25	.02
Garrard	Senior Hi Fi	47 K	6.8 K	.0001	.001	.2	.01
Webster	Magnetic	47 K	4.7 K	—	.001	.5	.01
BTH-Ed'svan	Needle Arm,	150 K	47 K	—	.0002	.03	.005
Med. Imped.	Needle	33 K	6.8 K	.0001	.0005	.2	.01
Armature.							

N.B: Rm is to suit microphone, approx. .5 megohm for crystal.

Schematic of the multi-purpose amplifier is above and Table I at left.

down the hum. Further reductions in hum-level are provided in several ways. All connections to the chassis are made at one place—where the common cathode of the first tube is grounded. No other connection is made to the chassis—even the power transformer and output transformer are insulated from the chassis. Separate leads to the common ground point are run from the can over the pick-up filter and from the metal shields over the volume controls. Even the metal case is not connected directly to the chassis. Instead, a screw at the extreme left of the front panel connects the metal case to a solder lug connected also to the common ground. Metal shielding braid over hook-up wire is insulated (with adhesive tape), where it passes through the chassis.

Two other hum-prevention ideas that are included are the separation of power transformer and speaker transformer (at opposite ends of the chassis), and the connecting of one side (select the side giving lowest hum) of the filament supply to a positive potential of about 100 volts, thus preventing any emission from the filaments themselves. As far as possible, all resistors and capacitors are as compact as can be obtained.

One extra precaution against hum may be necessary in some locations—a small capacitor, say .002-uf and 600 volt rating connected between one side of the A.C. line and the chassis. Reversing the A.C. line plug also helps to cut down some types of hum.

Output circuit

The load for the output tubes is something of a compromise, first because speaker and cutting head impedances vary considerably with frequency and operating conditions, and second because sometimes one and sometimes two speakers may be used. About 10,000 ohms is correct so an output trans-

former labelled "20,000 ohm" is about right—this used with two speakers gives ½ of 20,000 or 10,000 ohms, the correct load at the time when greatest power is needed. The mismatch of 2:1 when a single speaker is used is of little consequence.

Some high impedance magnetic cutting-heads require small adjustments of the circuit, usually either a shunt resistor of about 10,000 ohms or a .25-μf capacitor in series. Crystal cutters require shunt resistors to limit the output voltage to a safe figure.

Constructional details and layout are fairly obvious from the photographs. The front panel of quarter-inch Masonite is the sole support of the 18-gauge steel chassis. Edges of the panel are bevelled and the whole panel is crackle painted with a black paint containing a rubber emulsion. Lettering on the panel is done by smoothing the paint where necessary, moistening slightly and writing with white show-card ink. A light spray of shellac or clear duco helps to anchor the dried white ink.

As panel size is only 10 x 7¼ ins. and chassis size only 9 x 6 x 2 ins. it is suggested that parts first be tried in various positions until a nice uniform spacing is devised.


A fourth toggle switch, to the left of the speech-music switch, is a dummy. Originally it was intended to vary the bias resistor when changing from 6V6 to 6L6 tubes, but this was found unnecessary in practice—the bias resistor was not critical, even 300 ohms being satisfactory so far as the ear could tell.

What is obtained from the amplifier depends to a very large extent on the efficiency of the output transformer.

Best results in recording speech are obtained with the speech-music switch S3 set to SPEECH and the output filter S4 to OFF. Simply throw the switch to MUSIC for music recording. For playing speech records or for PA work, set the switch to SPEECH and the output filter for moderate attenuation. For music, try various settings of both input and output networks.


—end—

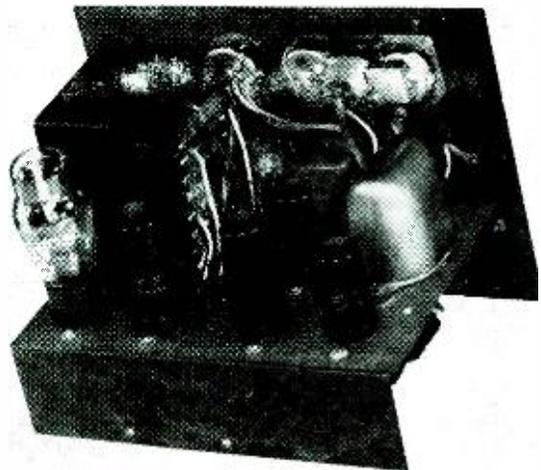Rear view. This job has a distinctly Australian appearance to the American reader, but has the advantages of compactness and portability.



Playback response curves


for LP, 45 and 78 r.p.m. records

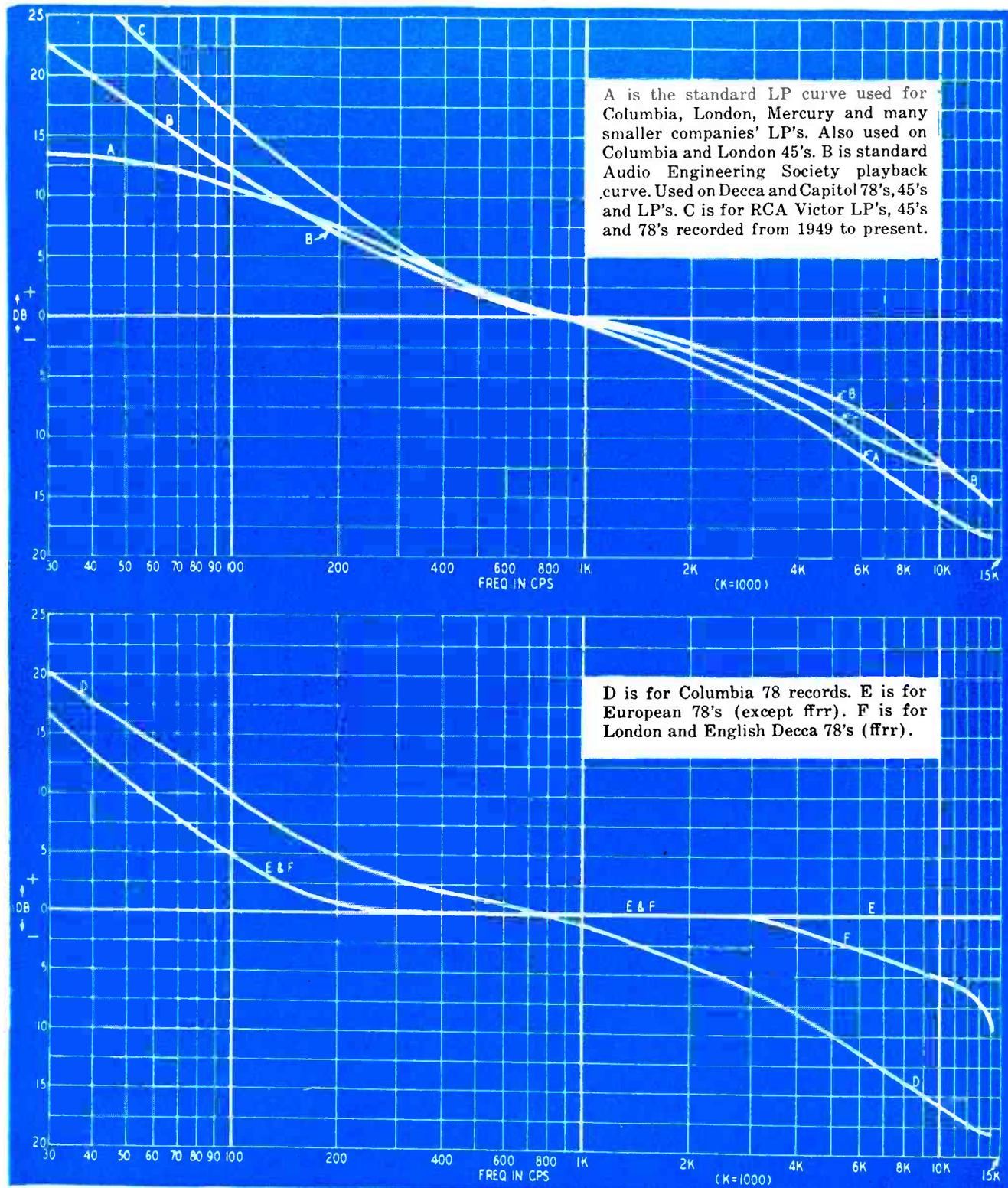

NOTE: Although these curves are *electrically* correct, *acoustic* balance at time of recording may make additional equalization necessary on some records. Older 78 r.p.m. records were recorded with a number of different curves, depending on date and manufacturer. In general, prewar 78's had a lower crossover (250-400 cycles) than current 78's.

Curves prepared from information supplied by record manufacturers.

RADIO-ELECTRONICS

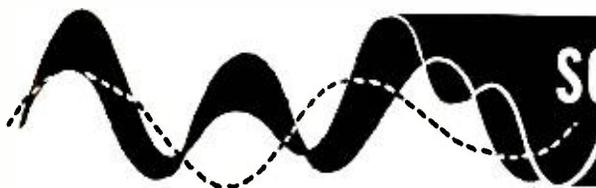

servicing OSCILLATORS

By ROBERT M. FIELD

THE oscillator of a superheterodyne is, ordinarily, the most difficult section of a receiver to service. If its oscillator is not working properly, there rarely is a signal to trace through the set.

A simple check may be made to determine whether or not the oscillator stage is working. Having first determined that a signal does pass through the i.f. section with a circuit-disturbance test or by using a signal generator, short out the oscillator tuning capacitor with a screwdriver. If the oscillator is working, a thump should be heard from the speaker. Touching a finger to the oscillator grid, or the hot side of the oscillator coil, should cause the same result. The oscillator is not working if there is no sound from the speaker. A more positive indication of oscillation, and one not dependent upon the operation of any other stage in the set, is a v.t.v.m. reading of the voltage across the oscillator grid leak. The grid should be negative with respect to ground. A typical reading at the low end of the broadcast band is 6 volts. On sets for which you have no circuit diagram, or the grid bias reading is not listed, look up the typical operation characteristics of the oscillator tube in a tube manual. In older sets that have no grid leak, the voltage drop across the cathode resistor gives a clue to its operation.

Most oscillator trouble is caused by faulty tubes. Low transconductance, especially in battery-operated tubes, is a common source of trouble. A customer who lived where no power lines were available, brought in her battery set. She had purchased a new long-life battery a few weeks before, but her set was fading out after the first few minutes of operation. The set worked steadily on a new battery in the shop, so I checked the 1A7 converter tube. Its transconductance was down only about 15% in the tester, but the tube looked old, so I replaced it. I explained to the lady that without her own battery there to check the set, I couldn't be certain that a new tube would fix it; I told her to bring the tube back for a refund if it didn't work. It must have been all right, for she never brought it back. Many instances of apparently shortened battery life are not due to faulty batteries, but to low emission (or transconductance) of the oscillator portion of the mixer.

Low filament voltage (when the set is operated from the a.c. line) is a common source of oscillator trouble in 3-way portables. Check the B-voltage at the input filter capacitor; it should be the same, or slightly higher, than the

line voltage. A poor rectifier or input filter will cause a substantially lower reading. Many new sets use selenium rectifiers, and low B-voltage can be traced, in many cases, to defects in this rectifier. They may be tested with an ohmmeter: The forward resistance should not exceed a few hundred ohms, and the reverse resistance should be a hundred or more times greater. One selenium rectifier I came across had a front-to-back ratio of about 2; the resultant a.c. current flow blew the current-limiting resistor (in series from rectifier to input filter).

In sets where the filaments are in series with the cathode circuit of an a.c.-d.c. audio-output tube and where a new tube does not bring the filament voltage up, try a shunting resistor from screen to cathode of the output tube—20,000 ohms at 1 watt is a good starter—and work up or down from that value as necessary.

Loss of plate voltage is a common cause of oscillator failure in sets where this voltage is obtained through a series resistor. It was once the practice of some set manufacturers to bypass this resistor with a 200-volt paper capacitor. With age the capacitor breaks down under the strain, and then the series-dropping resistor goes too.

A less common cause of no plate voltage is an open plate winding of the oscillator coil. The break is usually near either end of the coil, and unwinding a turn or two and resoldering the wire to its terminal lug will often fix it. In this connection it might be mentioned that a small percentage of oscillator coils have rosin joints or fault from some simple error, such as leaving the enamel on or neglecting to solder the connections during assembly and manufacture. A steady ohmmeter reading usually indicates a good coil. A grid-dip meter will give an excellent indication of the condition of the tuned circuit as a whole.

Grid capacitors give little trouble, as a rule, but are tough to locate when they do act up. A simple check may be made by shunting a 100- μ mf mica across the suspected capacitor. Some sets use an extra winding on the oscillator coil as a coupling capacitor. Since this is an open winding, no satisfactory check can be made with an ohmmeter. If in doubt, try a small mica capacitor from oscillator grid to the hot side of the oscillator coil.

Paper padding capacitors have given me trouble; bad ones are almost always intermittent. Variable mica pads occasionally become shorted (due to a

broken piece of mica) but they may be easily spotted by turning the adjusting screw while measuring the grid bias. I have replaced a few fixed mica pads that were noisy or intermittent, in fact, a silver mica pad that I put into a communication receiver caused an intermittent frequency shift, noticeable when receiving code, due to just a single plate making and breaking connection.

I have heard of a case in which a customer adjusted the trimmers on the ganged capacitors and caused the mica and screw to fall off. On replacing the pieces he put the mica over the trimmer and tightened down the screw! The tuning capacitor thereupon was shorted and the set was *very* dead.

I have yet to find an open grid leak, but during either the assembling or servicing of a set, the pigtail going to grid sometimes gets pushed against another lead and shorts the grid to ground.

Trouble with tuning capacitors is mainly confined to bent plates or metal filings (or dirt) between the plates. In personal portables, if the batteries are left in the set after they are exhausted, battery goo may get to the tuning capacitor and short out the plates. A simple remedy is to flush the goo off with warm water and dry the capacitor with compressed air. Only in extreme cases is it necessary to replace the capacitor. My customers get a gentle lecture on the folly of leaving dead batteries in their radios, together with a set of "sealed" dry cells, when a job of that kind comes in.

In case you think that oscillators aren't so tough: Just recently a set came in. "Must be some simple little thing," said the customer, "it just goes off and on."

"It's always something simple," I thought, but said merely, "Yes sir." At first it *did* look easy; bending the chassis just right would stop the set. It didn't take long to discover that the oscillator was the culprit—but I spent a good hour, with the chassis upside down, checking and rechecking every piece of the oscillator circuit. After there was nothing else left, I decided it had to be the tuning capacitor, although a quick look previously had indicated that all was well. Turning the chassis right side up disclosed the trouble. The capacitor was shock-mounted on rubber grommets, and the grounding connection (a little soldering lug) had a rosin joint. It goes to show that when it comes to oscillators, you just can't trust a thing.

—end—



Useful as a primary or auxiliary tester, this economical unit will give valuable service

By WM. C. STOECKER

A Practical Multitester

MANY experimenters and service technicians seem to overlook the possibility of making their own test equipment. Construction of a volt-ohm-milliamperemeter is feasible and can be an economical project. Furthermore, the experience to be gained from making such a unit is not to be underestimated.

This multitester employs a 0-1 milliamperemeter and is a reliable and convenient instrument for many general testing purposes. A meter with a 1,000 ohms-per-volt sensitivity can be inexpensive and fairly rugged, and may be used with wire-wound resistors at a cost much lower than would be possible with a meter of higher sensitivity. The only calibration required is a check with another a.c. voltmeter at a few points. Some voltage measurements, of course, require higher sensitivity, but those are commonly made with a vacuum-tube voltmeter. This instrument is built around an ordinary 0-1 ma meter hav-

ing an accuracy rating of 2% at full scale and an internal resistance of approximately 45 ohms. The tester provides 8 d.c. voltage ranges, 7 a.c. voltage ranges, 4 d.c. milliamperemeter ranges, and 2 ohmmeter ranges.

No attempt was made to mark scales on the meter directly. D.c. voltage and d.c. milliamperemeter ranges use simple multipliers and shunts. Ohms and a.c. volts are read from the meter scale with the aid of tables. For accuracy wire-wound 1% precision resistors were used as multipliers and shunts. D.c. measurements on any range are nearly as accurate as the meter itself at the particular part of the scale where the reading falls. The limiting factor for accuracy in resistance measurement is the linearity of the scale.

Construction details

The general layout is indicated by the photo above. All parts except the internal batteries were mounted on the

$\frac{3}{16}$ -inch Masonite panel. The usual milliammeter is not shielded, and accuracy will be affected if ferro-magnetic material is mounted close to it. Therefore a clearance of approximately 1 inch was provided between the meter and parts. The voltage multipliers were mounted on the rear section of the rotary switch; the front section was used as the ohmmeter range selector. The rectifier and fuse holder were mounted on small pieces of Masonite, providing insulation for these items. Heavy-duty toggle switches (3 amperes) were used in the milliamperemeter section, since contact resistances must be kept low. This section should be wired with No. 18 wire, or heavier, and the shunt leads should be kept as short as possible.

The assembly was mounted in a sturdy oak box the bottom of which was a piece of $\frac{1}{8}$ -inch Masonite with rubber feet attached to its corners. The overall dimensions of the box with panel and bottom attached are $8\frac{3}{4} \times 8\frac{3}{4} \times 3\frac{3}{4}$ inches. This plan of construction facilitates assembly and wiring, and allows space for adjustments and replacements. The arrangement of parts is not critical and any desired layout can be used according to the preference of the constructor. Fig. 1 shows the circuit.

Voltmeter section

The required resistance for each d.c. range was calculated from Ohm's law, assuming a current of 1 milliamperemeter for full-scale deflection. On selector point 1, for example, a 950-ohm resistance (theoretically 955) was added to the meter resistance to provide a circuit resistance of 1,000 ohms, and on point 2 an additional 4,000 ohms brought the circuit resistance to 5,000 ohms. Since a 950-ohm precision resistor was not

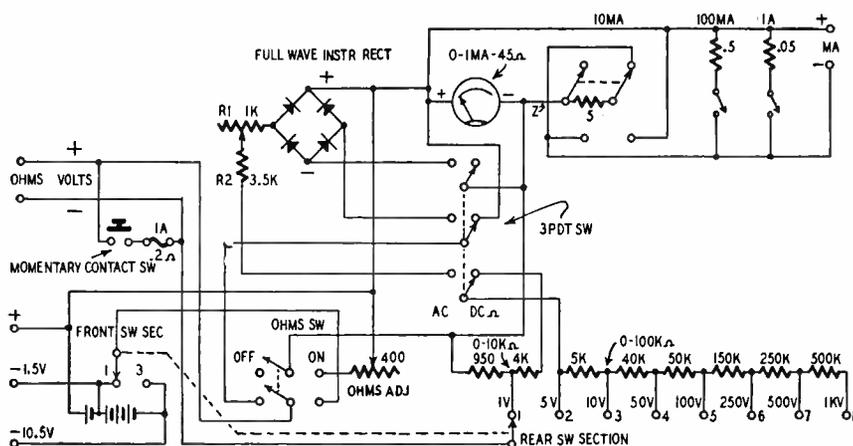


Fig. 1—Diagram of the tester. Positions 1 and 3 are the two ohmmeter ranges.



The technician watches the field strength meter when adjusting the transmitter.

MAINTAINING TWO-WAY RADIO

By HARDIN G. STRATMAN

Part I — Equipment and installation kinks, plus a few servicing problems

RECENT improvements in the design, installation, and maintenance of mobile two-way radio have greatly increased the role that vehicular communication plays in our society. Besides police and fire departments, taxis, buses, many utilities, factories, and farmers co-operatives have adopted this facility as an aid in their operations.

With these advances have come improved radio communications. This applies especially to the 152- to 162-megacycle band. The increased familiarity with the higher frequencies brought about by the war, and increased interest in TV and FM have helped make this so. With just a few watts frequency modulated on this band, good, clear reception can be had over a distance of approximately 10 miles. On several occasions, while repairs were being made on a 3-watt transmitter, the control station was contacted from inside a garage constructed of steel and concrete over a distance of about 3 miles. With some of the larger units whose output is approximately 30 watts, excellent reception was obtained up to about 50 miles of hilly terrain.

The control or master station

Setting up and maintaining the fixed station will not present any great problem. The antenna installation, however, may involve considerable work before the desired coverage and radiation pattern is achieved. If satisfactory transmission and reception is desired over a large area, the highest spot that the local terrain allows is picked for the antenna. This often turns out to be the town's water standpipe. After the somewhat difficult job of properly mounting the antenna is accomplished, future trouble with this item will be rare.

The fixed station may be either locally or remotely controlled. There are pros and cons to either type. If locally controlled, it is not likely that the antenna has been placed in the best spot. However, if trouble occurs, all parts of the equipment will be immediately accessible. If the unit is remotely controlled a good spot has probably been chosen for the antenna but a special line is required for the transfer of intelligence and relay control voltages from the operating point to the transmitter. Trouble may be caused by power failure at either one of the two points. A gasoline-driven generator unit is a valuable asset in maintaining uninterrupted operation. The extra line used when operating remotely will invariably be an ordinary telephone line with a line amplifier at the operating position. Besides acting as a preamplifier for the microphone and amplifying the incoming signals from the receivers, the line amplifier sometimes contains a tone oscillator which is used on occasion to attract the attention of the listeners to important messages. The line amplifier contains a B-plus supply and voltage-divider system to actuate specific relays for shifting to different frequencies.

The method used to shift from one frequency to another may be of interest. When the operator presses the microphone button, a voltage of say, plus 70 volts is applied to the line controlling the transmitter. This actuates the B-plus relay, energizing the transmitter, and at the same time another relay closes, switching in a specific crystal. If a different frequency is desired, the operator turns a switch and presses the mike button, and a voltage of approximately plus 120 volts is applied to the line feeding the transmitter. This again closes the B-plus relay but the added

voltage will cause a different crystal relay to switch in. If a third frequency is desired, the voltage feeding the transmitter may be reversed, switching in still another crystal. In almost all cases these frequencies will be channeled through the same tubes and circuits with no retuning required since the bandpass is very wide. No loss of power will be noticed. The range of transmitting frequencies will usually cover 200 to 300 kc. It could be considerably less since most of the receivers are double superheterodynes and, consequently, very selective.

The most troublesome components of the fixed station are the frequency-shifting relays, as many of them are multicontact units. If they are under a dust cover, clean the contacts only when they commence giving trouble since any slight bend in the reeds throws them off. A considerable amount of servicing time will be involved with tubes, especially rectifiers.

Mobile units

The mobile radio communication equipment is installed in the trunk of the car, thereby maintaining cruising comfort in the car. Instead of drilling a number of holes in the floor of the trunk to mount the main units and using the sheet metal screws supplied with the equipment, a board straddling the gas tank is recommended. Mount it with four stove bolts, clearing the gas tank on both sides to eliminate the danger of puncturing the gas tank. The possibility of the bolts loosening through vibration will be minimized if the bolts are double-nutted. Since mobile units are subject to constant vibration, secure mounting will prevent trouble later. A mounting board can give shock-absorbing action and allow provision for additional shock

mounts if deemed necessary. As a rule, shock mounts will lengthen tube life and reduce stress on the units' components. Since the radio units usually outlast the cars many times over, having the units already mounted on a board will speed up reinstallation in other cars. Over a period of several years many hours will be saved in equipment change-over. The chassis must be bonded to the frame of the car. Half-inch-wide copper strap or braid has proven completely satisfactory. Although the first few units had the bonding brazed to the car frame, self-tapping screws were later tried and found to work just as well. It is easier to drill a hole through the copper braid, if some solder is flowed onto the ends first.

Installation entails running cables to the battery under the hood and to the control panel on the dashboard. For best results separate the cables into two equal sets, usually two cables to each set, and run them along each side of the car under the floor matting close to the doors instead of next to the transmission housing. The cables are easily run along the side and behind the back seat to the trunk but if placed next to the transmission housing, the back seat will refuse to fit properly in the catches and will be a continuous source of annoyance. Furthermore, placing cables next to the transmission housing will interfere with the proper operation of the clutch, brake, and gas pedals, as the cables will drift around after a time.

A roof-mounted antenna will be the touchiest and toughest part of the mobile installation. The coaxial feed line to the trunk will present some unique problems. A roof installation, besides the extra height, provides a large radiating plane free of obstructions. The best spot is on the center line of the car slightly back of the front and back door center post and between roof ribs. It is practically impossible to get the coaxial line from the antenna mounting hole to the trunk in one operation without marring and disturbing the upholstery. After the mounting hole has been drilled, the upholstery immediately above one of the rear windows should be loosened for about a foot and a length

of semiflexible wire, such as No. 8 or 10 copper bus, should then be inserted down the channel just above the window and run down along the side of the car where the wires to the ceiling light of the car will probably be found. The bus wire should be poked down the channel till the end reaches the trunk compartment. One end of the antenna coax lead can then be taped or tied to the end of the bus in the trunk and then pulled back to a point above the window. The coax lead is loosened from the bus wire which is then inserted through the hole in the top of the car and worked over to the side of the car above the window where the end of the antenna coax protrudes. It is again fastened to the end of the bus wire and pulled through the hole in the roof and connected to the antenna. Soldering the coaxial lead to the antenna must be carefully done or the center conductor may short to the outer shield if allowed to get too hot.

The loosening and refitting of the upholstery above the window can be neatly done, as follows: With a wide-blade screwdriver, pry up slightly the metal strip along the top edge of one rear window and unhook the upholstery from the teeth on the strip, leaving the molding still attached to the frame. Loosening about one foot should give ample working room. After the installation of the antenna has been completed, the metal strip should be forced firmly back along the window frame and the upholstery tucked under the metal strip. A little clear varnish around the antenna mounting hole will prevent moisture from seeping into the car and ruining the upholstery.

A *must* in every good mobile installation is that the car have an oversize generator. Some of the larger radio units draw as much as 40 amperes and the battery must be kept up or it will be continually going dead. It is especially important that the battery terminals be kept clean, as a very slight resistance developing here due to corrosion can cause a lot of trouble. It often does not show up except under load while transmitting; checking across the terminals with a voltmeter will show no trouble. If the entire outfit, one fine day, should


suddenly go dead when the mike button is depressed, the trouble can usually be traced to corroded battery terminals. After cleaning them, a small amount of vasoline on the terminals will retard further corrosion.

Complaints of intermittent operation in mobile equipment will often be traced to tubes not properly seated in their sockets. Lower-powered transmitters and receivers use vibrator type power supplies. They will be subject, of course, to the usual limited life of about six months of almost continuous service.


When the fuse on a particular receiver is continually blowing for no apparent reason, the logical thing to suspect is the vibrator. Replacing it will usually clear up the trouble. Speaker hum can almost always be traced to a bad filter capacitor in the power supply, just as in any conventional radio receiver. Buffer capacitors with a 1,600-volt rating will very seldom break down. An operator will occasionally complain of distortion, and if the transmitter tubes all check okay and all stages meter properly, the modulator tubes are a sure bet to be somehow at fault. A lot of outfits use a 2E24 or 2E26 tube in the driver and power amplifier stages and if the drive to the grids is not kept high considerable trouble results. If the driver tube of a transmitter becomes even slightly weak, it is a good idea to replace it to protect the final stages from burning out. In the long run this will pay off in less expense and trouble. The brushes in the motor-generator of the more powerful mobile units should be checked regularly and cup grease kept on the bearings. After approximately three or four years, the motor and generator commutators will require turning down on a lathe to eliminate arcing and noise.

Since the plate relay which supplies B-plus to the output tubes passes considerable current through its contacts, they will become burned and pitted. They can be filed and cleaned just so often before the relay must be replaced. Its life can be extended by operating the power output tubes well within their limits.

(to be continued)

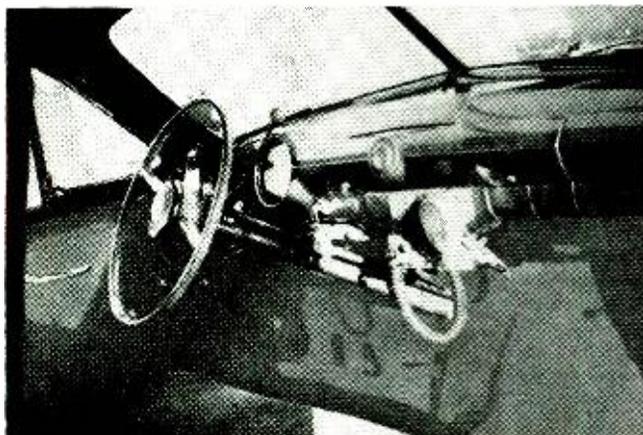

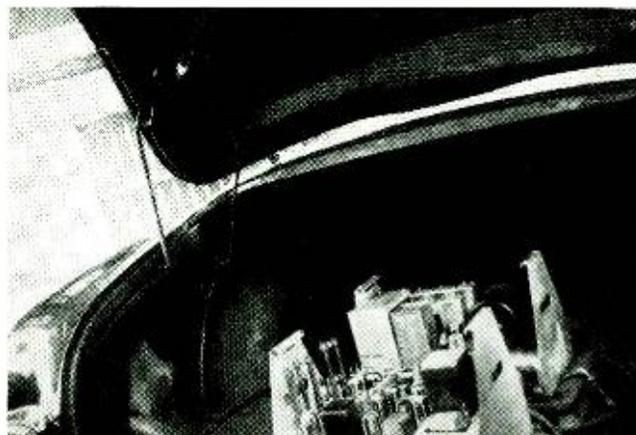Mobile control panel. Speaker is on firewall under the dash.



Units with covers off. Transmitter uses a motor generator.

Efficient TV Service in the Customer's Home

By W. M. TOMLIN*



Explanations to the customer are an important part of in-the-home servicing.

EFFICIENT and satisfactory television servicing can be performed almost entirely in the customer's home. In fact, RCA Service Company television service branches handle more than 90% of their service work in the home.

While our methods of operation may differ somewhat from the other service organizations, they at least typify the many factors involved in rendering efficient and satisfactory service to our many customers, whether the chassis is repaired in the home or brought to the shop for repairs.

The high cost of bringing the chassis to the shop makes it necessary that every effort be made to handle in the home such repairs as replacement of tubes, capacitors, resistors, and similar defective parts. Conversely, the chassis that are brought to the shop for repairs are those that would be too costly to service in the field.

These chassis usually are the ones that require replacement for major parts or have certain intermittent conditions that involve the use of special shop testing equipment. No r.f. and i.f. alignment is performed in the field, so these sets end up in the shop.

The most important factor in home service is the original diagnosis of the trouble. The use of test points found in most chassis, of course, expedites diagnosis. These test points are located at converter grid, i.f. bias bus, second detector output, and in the video amplifier circuit. Once the trouble has been isolated to a particular circuit, it is necessary to explore only this circuit to find the cause of trouble.

The trained technician usually handles from eight to ten service calls per day. Therefore, it is important that he

waste no time exploring other circuits which obviously do not contribute to the trouble. The so-called "know-how" in television service is knowing, from the symptoms observed, the exact part of the receiver to check, and quickly locating the trouble by systematic check and analysis of the circuit. The experienced technician usually knows the eccentricities of individual chassis and can locate these troubles readily.

Proper tools for the job

For field service, our technicians are equipped with a volt-ohmmeter (20,000 ohms per volt) which is satisfactory for analyzing the common troubles encountered in home service. The necessary hand tools, screw drivers, socket wrenches, adjusting tools, soldering iron, line cord, drop cloth, etc., are neatly arranged in a tool box so that they can be easily located when needed. This also includes such convenience items as extension cables, picture tube and yoke cables, etc. (usually made up by the service technician on his own, to expedite his work).

Besides the tools, the technician carries a complete kit of tubes and parts normally required. These parts usually consist of an assortment of resistors, capacitors, and other specific components known to be sources of trouble in the various chassis.

If the technician finds that a part needed is not in his kit, the part number is obtained from the parts list of the service data for the model being serviced and ordered when he returns to the branch at the end of the day. The part is placed in his personal parts bin in the shop by the stockman, for delivery to the customer the next day.

Because of the increase in the number of different sizes and types of picture

tubes, it is impossible for the technician to carry all types and sizes, unless his calls are scheduled on similar models. If a picture tube replacement is needed and is not available from the technician's kit of tubes, it is usually handled the same as other parts not normally carried by the technician, and delivered the following day. However, sometimes special delivery of picture tubes can be obtained by a phone call to the branch. The tube is dispatched to the customer's home and installed by a follow-up technician from a truck equipped with a complete stock of all sizes and types of picture tubes.

Why do they go wrong?

Any successful servicing operation calls for a periodic review of the "causes of need for service." Just what happens to a television receiver when it becomes inoperative? An analysis of 3,000 service calls made during November, 1951, in 15 different locations throughout the country revealed the following facts:

Reason for Failure	% of Calls
Tubes	44.3
Minor picture adjustments, centering, size, a.g.c., etc.	18.8
Component parts, capacitors, resistors, transformers, etc.	10.8
Miscellaneous—interference, nuisance calls, duplications, minor rechecks, instruction, checkup, etc.	22.9
Antenna work—reorienting, repairs, transmission lines, etc.	3.2

(These figures also include replacements on older receivers when life expectancy enters into the problem)

Among this group of 3,000 calls, it was found necessary to return only 120 receivers to the shop for repairs—46 of these for realignment, the remainder for troubles not easy for the technician to diagnose in the home.

These figures are very interesting

RADIO-ELECTRONICS

*Engineering Dept., RCA Service Company, Inc.

and refute the popular belief that realignment is a major problem in TV receiver servicing. The figures also support the claims of major servicing agencies that more than 80% of the receivers can be serviced *in the home*.

Customer handling, basic training in the shop of the service technician, proper scheduling and briefing before making the call, and adequacy of tools, tubes, and parts, are the prerequisites that help solve many home servicing problems. To this must be added the initiative and the will-to-try of the technician. This combination will work in most any size servicing operation.

Formula for efficiency

What then is the *formula* for successful servicing of television receivers? Any successful operation starts with the initial conversation with the customer reporting that his receiver is inoperative. The handling of the customer at this moment is just as important as the technical excellence of the man assigned to the job, or the complexity of the equipment that he uses. The customer *has* a legitimate complaint—he has reason to be annoyed. His major form of entertainment has been interrupted. He is to be treated with respect and sympathy—not irritability or argument. Right here, in 99% of the cases, is determined whether the service technician can fix that receiver in the home. Psychology at this moment is of much more value than a B.S. degree.

The next step toward solving this particular complaint is in selecting the technician who will handle the call. Avoid clash of personalities wherever possible. The nature of the complaint should be outlined fully on the job card handed the technician, so he can equip himself with the expected tubes and parts that may be at fault. Scheduling this call with other calls in the vicinity—and if possible, on similar models—is a *must* in the interest of economy and efficiency. If he needs coaching on how to handle this particular trouble—give him such assistance. Needless to say, he should have the necessary schematics and case histories that go with that particular model receiver. One minute briefing in the shop may save thirty minutes in the home. Make sure he knows the location of the customer's residence, and that the customer will be at home.

A very important part of the successful servicing program is explaining to the customer what was done, and demonstrating the improved performance. Time permitting, it is also an admirable point of professional courtesy to call the customer the next day to check on the work that was done.

In handling almost all our service work in the home, we do not use any secret or miraculous methods, but rather the down-to-earth common-sense practices that have been relied on by good technicians of the radio service industry for years.

—end—

RADIO-ELECTRONICS

Service Bench Contest

Second Prize



Mr. Whitton's panel design permits maximum utilization of the working space.

ACCENT ON SPACE

By C. J. WHITTON*

LIKE most service technicians, our preferences in a test bench were divided between the flexibility and convenience of individual unmounted instruments and the solid and impressive appearance (to the customer) of a symmetrical mounted panel. This test bench and panel was designed to meet both these requirements.

As you will note from the photograph, we have used the accepted patch-cord method of making instruments available at all positions on the bench, without having to move the chassis or other instruments being used. Obsolescence was also considered in the arrangement and construction of the panel. The large center panel contains instruments least apt to become obsolete, while instruments such as the tube tester and others whose life is likely to be short are mounted in the smaller end panels. These panel sections are made of quarter-inch tempered Masonite and are painted with auto enamel (with the color code recorded so they


may be accurately matched when replacement is necessary).

Another feature that has proven very convenient in use, is the mounting of the panel to the work bench. The lower edge of panel projects 10 inches over the work top and is raised 12 inches above the bench top. This places all controls within easy reach and still leaves ample bench area for the average chassis.

The frame for the panel support is made of 1 $\frac{3}{4}$ x 1 $\frac{3}{4}$ (2 x 2) material. There are two end supports as shown in the drawing. Stringers run across the bench at the rear top and bottom (see photo), along the front of the top and along the lower edge of the panel at the front. There is another stringer at the back about 8 inches from the bench—just so placed that it and the panel would make two sides of a square.

The center brace on each end piece runs between these two lower stringers, and a piece of 1-inch shelving runs the length of the bench on top of them,

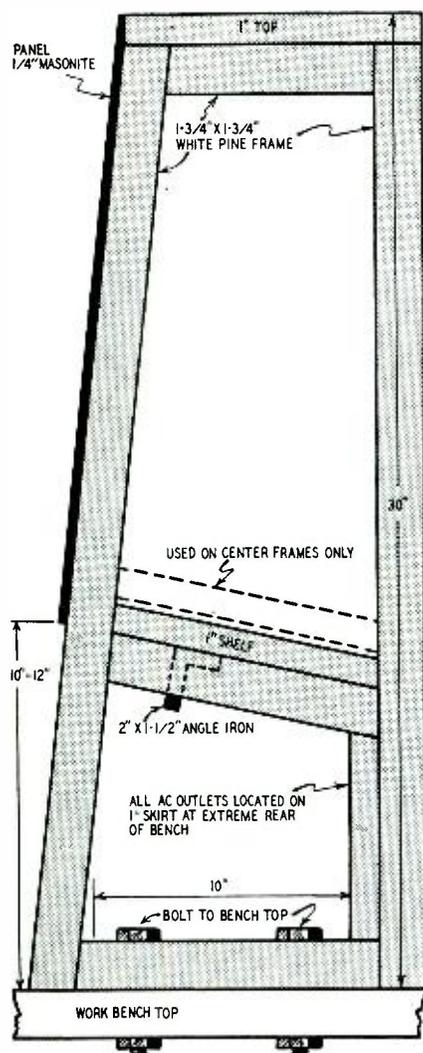making a floor for the panel section. Two middle support sections are also made. They are like the end section, but have no lower leg section. One of these is placed at each panel break. The



End section of the panel support frame.

bottom edges rest on the shelf and are screwed firmly to it.

For better center support, a length of 1-inch angle iron runs the full length of the panel (see photo). It is externally grounded and serves as a convenient grounding bus that cannot be accidentally contacted but may be used along the length of the bench by using alligator-clip leads.

The work bench proper is simple in design. The base consists of two identical drawer sections. Work top trusses are of 2- x 4-inch material with a 1-inch top covered with tempered Masonite and painted with a good grade floor enamel. Drawer sizes may vary with individual requirements, but ours were designed to hold small bench tools and small parts not easily stocked on open shelving.

The choice of instruments and their grouping was not due to haphazard decision but was the result of eight years of study, and planning what we wanted in a permanent test bench:

The left panel section consists of an audio-control panel, a vibrator analyzer, voltage control for d.c. supply, and a row of patching jacks.

The right panel section contains the tube tester and a row of patching jacks.

The center panel contains a resistance bridge, two volt-ohmmeters, a 15-volt d.c. meter, a 30-amp d.c. meter, polarized d.c. metered output jack (for auto radios), patch network jacks, Analyst, a 150-volt a.c. meter, a 75-watt a.c. wattmeter (this meter is on single a.c. outlet skirt under panel), and an FM-AM signal generator.

All instruments are standard commercial units and require no description other than the fact that each unit has its own red-jeweled indicator. The entire panel is controlled by a 20-amp automatic circuit breaker which has a green-jeweled indicator in top center of main panel.

As you may note in the photo, there is a row of patch jacks within easy reach of all instruments. Each end section carries five standard tip and sleeve jacks. The two top jacks in each section are connected in parallel with low-loss coaxial shielded cable with shields commonly grounded to sleeve connection of jacks. Each of the lower three jacks is horizontally connected with its opposite number on the other end panel with parallel cord with no common connections. Thus an instrument on one end panel may be plugged into the jack near it with a jumper cord and may be used

at the other end of the bench by plugging into the corresponding jack. When the photograph was taken only four jacks were in use. A fifth jack was added later.

The audio panel consists of an a.c. control switch; pilot light; input jacks for standard phono plug, microphone, and electrical instrument pickups; and output jacks for external speaker. All shielded input leads, speaker leads, and a.c. supply leads from this panel terminate at one of our standard 25-watt rental PA amplifiers, which is mounted under the back edge of the bench with controls accessible to the technician. This amplifier may be easily removed when peak PA rentals demand its use. The panel test speaker may be switched to the amplifier's output or to bottom row of patch jacks, thus making test speaker connections available at any point along the bench.

Another customer-convincing feature of this panel is the use of the noise test jack usually incorporated in the present-day tube checker. Plug the noise test jack on tester to shielded patch jack, then jumper the corresponding jack to input of audio panel, switch the test speaker to output, and presto! the noises that may appear in the tube under test will sound convincing indeed to the customer. To make this test more usable and to generally increase the efficiency of the entire panel, all instruments should be properly phased and grounded. —end—

Corona a Problem With Big Tubes

A number of service organizations find an undue amount of corona and arcing in the high-voltage power supplies of new large-screen receivers. In these sets, especially those using the 19-inch and larger tubes, the high voltage power supply develops between 12-18 kv for the picture tube. At these high voltages the tendency toward arcing or corona is much greater than at the 8-9 kv commonly used for smaller picture tubes. It is especially bothersome in damp locations and during humid weather. Near the ocean and the Great Lakes where the air has a large moisture content, corona is one of the most frequent reasons for service calls on large screen receivers.

Corona is apparent usually in reduced brightness and a buzzing sound, regardless of volume control setting. The decrease in brightness is caused by the extra loading which the corona presents to the high-voltage circuit, and which decreases the second-anode potential. Corona occurs when the po-

tential at one point is so great that it forces all free electrons to the surface, and the surface is so small that electrons are "crowded out" and pushed into the air where they change oxygen molecules into ozone molecules. Ozone is the clean-smelling gas present after severe electrical discharges. Often one can smell the ozone at the back of the receiver as a sure indication of corona. In addition, corona can be seen in the dark as a bluish glow around a thin wire or sharp point.

One of the cures for corona is to smooth out sharp points by applying solder and letting it flow smoothly. Painting all exposed metal surfaces with polystyrene coil dope or Glyptal will also help, especially when the corona source is hard to locate exactly. Dust and dirt on insulating material often form a leakage path for corona or arcing. A good cleaning with carbon tetrachloride and subsequent application of coil dope will clear it up. —end—

Have you had an interesting servicing experience recently? Or learned something new about the business end of servicing? Or maybe you have built a better TV service instrument, shortwave receiver or what have you? If so, chances are RADIO-ELECTRONICS readers would like to hear about it. We pay excellent rates for good down-to-earth articles. Let us know what you are thinking of writing about and ask for an Author's Guide.

FIX IT YOURSELF

By ERIC LESLIE

THE TV repairman is suffering from a rash—a rash of “fix-it-yourself” TV books. They are announced by radio and TV broadcast, in newspaper advertising, and even in the windows of TV and parts dealers (some of whom should know better). The TV technician is rightly troubled because his profession is being belittled by the shouted suggestion that anyone with a fifty-cent book can be a fair TV repairman. Even more he resents the implication that the average TV repairman is a racketeer which dominates much of the advertising (though far less prominent in the books themselves). Just how useful or harmful are these works? What will be their impact on the TV service technician?

Four representative specimens appear in the photograph. They may be a little better than average, since at least two of them were sent to this magazine in good faith, with a request for review.

The cheapest of these, “How to Adjust Your Television” sells for 50c. It has 47 pages in four chapters. The theme of the book is: “Eighty-five percent of the things that require servicing a TV set are repairable by ADJUSTMENTS or TUBE REPLACEMENTS.” Chapter I describes adjustments, telling the set owner how to vary horizontal and vertical amplification, center the picture, adjust the ion trap (!), etc. The second chapter discusses the antenna and lead-in, the third, common tube failures, and the fourth is a short lesson on television theory. Then follows some useful information on possible modifications (color, big-tube conversion, etc.) and an order blank with which the set owner can obtain a tube layout for his set for \$1.00.

The book is obviously written by someone familiar with television. Its chief fault is ambition. More than one set owner is going to get in wrong making some of the adjustments. Much of the material will be over the reader's head. There seems to be little reason for giving the set owner a glossary of technical terms, though chapter IV “How You Get a TV Picture” may be interesting if not useful. The service technician is mentioned in the introduction, which states that due to the shortage of technicians “. . . in many cases boys who should be installing antennas are sent out as ‘repairmen.’ This is costly both to the repair dealer and the set owner.”

Two code-type books

Of an entirely different type is “Now You Can Fix Your Own TV Set.” It makes no attempt to instruct the owner in the principles of television, but simply prints tube layouts of 107 TV re-

ceivers, with a list of trouble symptoms below. Each symptom is given one or a series of code numbers. These code numbers appear as callouts on the layouts above, with lines running from the tubes that might be responsible.

A set owner *might* be able, with this book and a spare set of tubes, to fix a fair proportion of the troubles in his receiver. A spare set of tubes, however, would make the book unnecessary. All the owner would have to do is replace *all* his tubes when his set goes wrong. Then he could put the old ones back one by one, till the symptoms show up again. The last tube in would be the guilty one.

The owner would probably be at a loss in the numerous cases where tube failure is a symptom of some other trouble. These books should carry a note: “If the new tube goes bad a few hours after installing it, call a service technician.” Such a note would cover a large percentage—but not all—of such cases.

“Now You Can Fix” contains some introductory information, including instructions on removing and replacing tubes safely. The inexperienced set owner is warned against touching the controls on the back of the set. (“Adjustments” have no place in the picture, apparently.) According to the preface “. . . up to 75% of all troubles in television sets are caused by either defective tubes or faulty antennas.”

The other code-type book is written by another familiar to service technicians. It is “The Television Doctor” by H.G. Cisin, well known electronic engineer and author of articles in this and other magazines. This book sells for \$1. The set owner is asked to check three things: the picture, the raster (called “bright area”) and the sound. Various conditions of each of these are given in three lists on the inside front cover. There are 69 picture conditions and a smaller number of the other two. Each is numbered or indicated by a letter.

The set owner runs down the lists to the symptoms that describe his troubles, combines their numbers and letters into a phone-number-like code and searches for the remedy under this code. For example, the code for “no picture” is 1, that for “no bright area” is A and for “weak sound” is 11. Hence the code combination for this condition is 1A11. Next step is to turn to the second chapter “Trouble Location Guide” to identify the code symbol and find what's wrong. It's disappointing to find no 1A11—in fact nothing between 1A7 and 2A7. This may be one of the troubles a set owner cannot repair, and possibly this code appears in “Rapid Trouble Shooting”, a companion book for TV



service technicians. The symptoms given in the three lists can be combined into more than 35,000 different codes, so it might be too much to expect them all in *any* one book!

Cisin quite plainly has had first-hand experience in TV servicing, and one of his difficulties is dropping into terms not familiar to the set owner. The third chapter explains many of these terms, and the fourth goes into tube replacement. Even picture tube replacement is covered, and the owner is given detailed instructions, including how to adjust the ion trap, and even disposing of the old tube.

Unlike some authors, Cisin does not represent the TV technician as a racketeer, but as a good-natured individual who will be rather pleased if he finds the set owner intelligent enough to make small adjustments or replace burnt-out tubes: "As a matter of fact, he prefers not to be called on trivial matters," because then "he is obliged to charge you what may seem to you an unreasonable price, but you must remember that his time is valuable and he must be recompensed for it." A point of view which is original even to some service technicians!

A smoother job

A book which takes a somewhat different view is "TV Owner's Guide to Operation and Repair" an ambitious-looking job that sells for \$1.98. Apparently written by a non-technical writer to help non-technical readers to purchase, operate, and install their own televisions, it is a mixture of common-sense advice and delicious nonsense, with the latter predominating.

On the one hand, the author performs a real service by printing genuine copies of warranties, purchase and service contracts, and points out many pitfalls which the customer can avoid if forewarned.

On the other hand, the reader might lose all these advantages by following the instructions for installation and repair. The author shows—as an example—a picture of an antenna installation which looks for all the world like a combination of two pictures published by a fire protection association to show how an antenna should *not* be installed. "To ground the mast" for instance, "simply wind a wire round the bottom of the mast, then wind that same wire firmly around a pipe or other metal fixture on the roof."

He is careful to warn the reader to be sure the carton is sealed when he receives his set, and after opening it, to make sure the serial number is intact. But he does not warn that ion traps are often moved out of position for shipping, an important fact for the owner who would like to make his picture tube last.

It is in the chapters on servicing that the "Guide" is most erratic. Aiming—apparently in good faith—to protect the set owner, its instructions would cause him to reject the honest service organization and search for gyps.

"You yourself can fix 90% of all the things that go wrong . . .," the book says, in a chapter headed "If You Must Send Your Set to a Repairman." (This chapter trains the reader "to diagnose major repairs" and know "how much any one repair should cost you.") It goes on: "We are going to let you in on some of the most vicious repair rackets—not because most repairmen are dishonest, which they are certainly not—but because we don't want you to be one of the unfortunates who pay these gyp artists' salaries."

Some good advice follows. The customer is warned against fly-by-nighters, "membership plans," and "club discount houses," as well as picture tube insurance, and given some hints on how to find a good service technician.

Once the technician is in the home, however, the picture is different. Mind you, our skilled customer has already exhausted the "90%" of faults that can be repaired in the home. The trouble is obscure. Yet, if the technician cannot tell what is wrong with the set or "tells you that he'll have to take it to his shop for further experimentation—call another serviceman!"


If the service technician *can* tell what's wrong, "MAKE HIM TELL YOU IN ADVANCE HOW MUCH HE THINKS THE REPAIR WILL COST YOU." This estimate is to be checked with a "chart" which contains exactly five items:

Defective picture tube	\$50.00-\$60.00
Not enough electronic power	6.50- 7.50
Shorted picture tube	50.00- 60.00
Burnt-out condenser	6.00- 10.00
Burnt-out resistor	6.00- 12.00

(The spelling of "condenser" is consistent throughout the book.)

If by some chance it agrees with the chart "MAKE HIM GIVE YOU AN EXACT DAY" (when he will return the set).

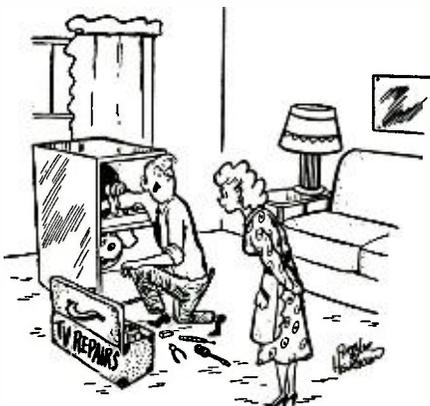Only the gyp, endowed by nature with X-ray vision and a mental analog computer for simultaneously (and instantly) evaluating "electronic power", a bill of materials, and the customer's bank balance, can glibly tell the owner what troubles shop examination will turn up, estimate exact charges, and predict the return date. The honest service techni-



Suggested by Arthur Henrikson, Chicago, Ill.

"Oh yes. Of course it's simple!
I just replace the tube that isn't hot!"

cian is virtually excluded by this interesting technique. And, unless something is wrong with the picture tube, the only defect that justifies removing the set to the shop is "insufficient electronic power" (whatever that may be).

The book winds up with a chapter on repairing your AM radio. Instructions for repairing one common trouble—a defective line plug—are clear, detailed, and correct. Information on curing other troubles is not as accurate.

What impact will they have?

What effect are these books going to have on television servicing? The best guess is: "none." They *will* give the set owner a better idea of the complexities of TV receiver servicing. The explanations of TV theory will so confuse him that he will likely believe that the TV technician—who presumably understands these mysteries—is a superintellect.

They are going to produce their crop of service calls, some of which may be distressing. (There is no meaner customer than the man who has to replace a picture tube, and does not intend to admit to his family—or even to himself—that he is responsible for the damage.) On the other hand, the better books may channel the incurable experimenter's tinkering into non-destructive channels. The "TV Doctor" warns about turning trimmers, and tells the set owner exactly how they look. The more intelligent T-viewer may even learn to make certain minor repairs and replacements which the service technician would otherwise be called on to do.

Books like these cannot help the prestige of the repair technician. Only one of the four studied suggests that he is a capable man whose time is worth money. The others, while giving lip-service to the "near-miracles" of the TV service industry and the "thousands of conscientious repairmen," justify their existence by the assumption that the industry is so largely made up of incompetents and high-school boys, if not racketeers, as to make it worth the set owner's while to try to make his own repairs.

Even worse than the books is some of the advertising heard on the radio. This however is not a new problem to the technician and service organization, and is one which must be met by counter-publicity and counter-advertising.

In the long run, the amount of business lost to TV set owners making their own repairs should be balanced almost exactly (at least dollarwise) by the amount of additional business gained from owners who try—without sufficient knowledge—to apply the instructions of some of these books. And any loss in prestige will be more than overbalanced by the increased respect readers will have for anyone who really understands television. The total result should be a greater understanding of the TV technician's problems by the set owner.

—end—

VARIABLE LINE VOLTAGE

By PHIL HINER

A VERY practical aid in radio and television servicing that has been generally overlooked is the power line transformer with manually-controlled, variable output voltage. With the very rapid increase of TV servicing in the metropolitan areas, a device for instantly varying the input voltage to a set under test has become almost a necessity.

The experienced service technician is aware that line voltage varies greatly from district to district in most of our cities, and also varies from hour to hour within the same district. These variations affect the operation of many electrical appliances—but particularly radio and television. We have frequently seen line voltage drop so low in a large Illinois city that normal battery-electric radios became inoperative due to cutting-out of the sets' local oscillators.

Television servicing requires a much closer check on line voltage than does normal radio servicing. A few volts variation in line voltage may make considerable difference in required size, focus, and picture linearity adjustments. As a result, a picture that was adjusted with loving care at the shop may be away off when it is turned on in the customer's home. This annoyance is now being obviated by some technicians simply by checking the line voltage in the customer's home when picking up the set and then setting the variable transformer in the shop test panel to that same voltage before aligning the set and adjusting the picture. (Note: Remember that in areas where the voltage varies at different times during the 24-hour period the peak-load evening voltage is the one that must be used, as the owner will do most of his viewing at that time.) Very little, if any readjustment then will be necessary in the customer's home.

In actual bench servicing, innumerable tests can be made on both TV and radio sets by varying the input voltage. As an example, suppose a TV set has a normal raster but no sound or picture and you suspect the r.f. oscillator. Arrested oscillation is most frequently caused by either low emission of the oscillator tube, a tired rectifier, or defective electrolytics across the low-voltage rectifier. As a quick check, a slightly raised input voltage is useful, as it will for a brief period counteract any of these conditions and artificially restore oscillation.

Most battery-electric portables derive their filament current from a voltage-dividing network in the B-plus supply, consequently, a substantial drop in line voltage means a drop in filament voltage below the level necessary to sustain

oscillation. With a variable line voltage it is possible to determine quickly and precisely at what voltage the set signal fades and whether such trouble is due to low line voltage or to defects within the set such as electrolytic filter capacitors that have dropped in efficiency below the point that will maintain proper B-plus voltage.

Frequently, it is desirable to make voltage tests on a set when an excessive wattmeter reading or some other evidence of overload indicates a B-plus short. This can be done for a brief period, minimizing the danger of injuring good parts, by decreasing line voltage 20 to 30 volts below normal. Some sort of wattage indicating device is a very valuable addition to any test panel. A variety of such circuits are available and can easily be constructed in the shop. A low-cost, satisfactory wattage indicator can be built around an electron ray 6E5 or 6U5 indicating tube, using a circuit similar to that found in the RCA Chanalyst.

A simple hookup is shown in the drawing. A low-value resistor is inserted in the line and the voltage across it is measured with a low-range a.c. voltmeter. The meter may have a range of 3 volts, and the resistor should have a drop of about 1 to 1.5 volts with apparatus most commonly tested. Thus for television receivers, a $\frac{1}{2}$ -ohm resistor would be good, and for midgets a 2- or 3-ohm resistor would give best indications. Many technicians use a 1-ohm resistor as a compromise.


The device is actually an a.c. ammeter, not a wattmeter, though in practical application the number of amperes flowing through it multiplied by the line voltage will give the approximate wattage. With a line voltage of 120, for example, and a $\frac{1}{2}$ -ohm resistor, 1 volt on the meter would indicate 2 amperes, or 240 watts.

A chart can be drawn up, based on ordinary line voltage, to show watts against voltage readings on the meter. The line should also be frequently checked (as suggested in the figure).

There are, of course, several methods of attacking the problem of intermittents, one of the most satisfactory being the use of momentary surges of high line voltage. The voltage is increased to 125 to 130 volts, but only for a short time. Many old-time service technicians use momentary applications of high line voltage to polish off worn parts on the theory that the components that go west are borderline and should be replaced. Some prefer to remove all tubes but the rectifier, thereby impressing high voltages across capacitors. On occasion the writer has successfully

used this technique in breaking down and locating leaking capacitors. The practice is controversial, however, and it places abnormal stress upon good parts as well as bad.

An ideal device for varying line voltage is an isolation-type transformer constructed with either a continuously variable secondary or a switch-controlled multitapped secondary, and a built-in voltmeter. Several such transformers are now available. A transformer that has suitable characteristics is the Staco model LR-5. This transformer is metered and has a continuously variable secondary from 70 to 140 volts. A similar transformer by the same manufacturer, model LRL-5, has a continuously variable secondary, from zero to 140 volts, available at a slightly

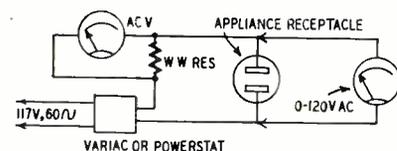

higher cost. An autotransformer variac such as Stancor's testing transformer, model P-6299, also may be used, but it does not provide the isolation from the power line that is particularly advantageous in working with a.c.-d.c. sets. The "hot chassis" is a long-standing source of annoyance to service technicians and a possible source of real danger when plugging directly into a power receptacle. This hazard is completely eliminated by using an isolation transformer with the set under test. The RCA Isotap provides such isolation with variable voltage.

Other types of variable-output transformers or autotransformers are obtainable, with a wide range of power-handling capabilities, number of taps, and prices. Among these are the Merit P-3177, UTC's Varitran V-1, the Stancor PV-6443, and a number of others.

Much commercial test equipment is dependent to some degree upon a constant input voltage for accuracy. Since line voltage in metropolitan areas may drop as much as 5 to 15 volts during periods of heavy power consumption, many modern shops have found it advisable to energize their test equipment through a separate variable transformer or variac, making it possible to maintain a constant input voltage at any hour of the day or night.

While not literally a test instrument, the variable line transformer does afford control over an ever-present variable in electronic trouble-shooting. The ability to control or reproduce certain conditions results in more effective and economical servicing.

—end—



Scene of action in studio of television station WRGB.

Operating TV

Part II—Equipment, techniques and practice in the TV studio

THE operating techniques of a TV camera are briefly as follows: **Depth of field.** If inadequate depth of field is apparent, three possible corrective adjustments may be made:

1. Camera may be moved back. The farther the object is from the lens (for a given focal length and iris opening), the greater the depth of field, also the smaller the image.

2. Use of smaller iris opening. The smaller the opening (for a given focal length and distance), the greater the depth of field. It must be borne in mind also that the illumination required increases with the *square of the ratios* of the f: numbers of the diaphragm as the lens is "stopped down."

3. Use of a lens with shorter focal length. This increases the depth of field, widens horizontal and vertical angles, and reduces the image size. Use of a shorter focal length, however, complicates the problem of obtaining good pictorial quality, due to the smallness of the image and a *flat field*.

Focusing. The image is focused by a knob on the right-hand side of the camera, which moves the image orthicon tube and yoke assembly in respect to the lens. Inspection of Fig. 4 in the February issue shows that the field *in focus* is about twice as great to the rear of the object upon which the camera is focused than in front of the object. This characteristic has a direct bearing on focusing technique as practiced by the cameraman. When he adjusts the focusing of the camera on the subject or scene, the lens is focused on a plane about one-third of the distance between the limit of the depth of field closest to the lens and the rear limit farthest from the camera. In this way the camera is properly focused for activity within the *depth of field* of the area likely to be used.

Special effects are sometimes called for which require the cameraman to use the focus control in an unorthodox manner. One common example is a de-

liberate defocusing (blurring of the entire scene), and then refocusing to impart the illusion of a transition of time.

Using the Iris. The iris controls the stop openings or aperture of the lens, and is adjustable from the rear of the camera, or in some cases, is motor-driven from the camera-control unit. This adjustment is a vital part of camera technique.

The *lens stop* is usually engraved on the rim of the iris and on remote iris controls, and is prefixed with a small letter f. The lens speed is rated by its widest stop, such as f:1.9; f:2.7; f:3.5 for a *fast* lens, or f:16 or f:22 for a comparatively *slow* lens. The iris enables the operator to use a smaller aperture (higher stop number) than the maximum available. The wider the aperture, the more light gets through to the photocathode of the tube. The smaller the aperture, the less light but the greater the depth of field. The scene composition, lighting facilities, and the scenic effects desired are contributing factors in determining the iris adjustments. In practice, adequate light is used so that the lens may be stopped down to the f: number allowing the maximum depth of focus necessary for the sequence of operations.

Panning. Turning the pickup head right or left to follow movement across a scene requires considerably more practice than one would think. The movement must be smooth and even. Motion that is too fast causes a breakup of the image in the horizontal lines. Proper

technique requires one thing: *practice*. Panning is done by grasping the lever at the rear which swivels the pickup head on the tripod or dolly, and moving it easily in the direction the pan is to be made.

Dollying. This term refers to the action of moving in, out, or around a scene. A camera dolly mounted on wheels and sometimes operated by a dolly man is used. It is obvious that the cameraman must continually adjust his focusing control if the movement is in or out.

The above discussion of course is only an outline of camera technique. Several electrical adjustments yet remain in the cameraman's bag of tricks which affect picture quality and produce the special effects that may be called for.

Final image orthicon adjustments

After the initial focus and alignment adjustments have been made, the remaining settings are *beam current* and *target potential*. These adjustments are made simultaneously and only when the scene composition and lighting conditions are known.

In order to better understand these adjustments, consider for a moment the nature of the video signal currents. The electron gun emits a stream of electrons which constitute the *beam current*. Before scanning, this beam current is a direct current. The image focused upon the photocathode creates a varying target charge. Upon scanning, the electrons are attracted to the target, partially neutralizing the target image charge, subtracting from the original

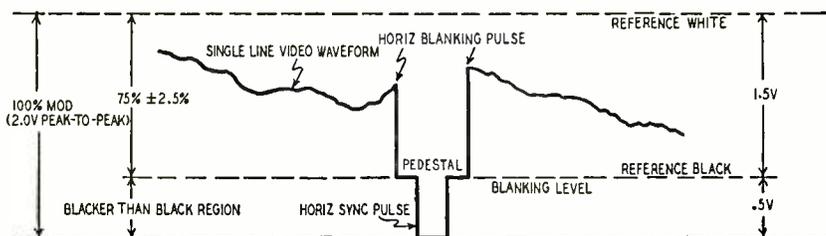


Fig. 1—Parts of two single video lines separated by horizontal blanking pulse.

Studio Equipment

By HAROLD ENNES



Photo of the Du Mont field-type monitor.

beam current, and causing modulation of the returning beam. (See Fig. 1 in last issue). This returning beam undergoes current multiplication in the electron multiplier, flows through the output load resistor, and creates the video signal for the wide-band video preamp.

When no light (a dark portion of the scene) is impressed upon the photocathode, all of the scanning electrons return to the multiplier section. When a comparatively large amount of light is present (such as highlights of a scene), few electrons will return, since most of them are removed from the original beam in neutralizing the charge on the target.

If the beam current is increased excessively, the excess electrons not required to neutralize the target charge will be returned to the multiplier section along with those of the black portion of the scene, resulting in a relative loss of detail. Also, the *beam noise* is proportional to the square root of the beam current, so that the higher the beam current, the lower will be the signal-to-noise ratio.

It is the operator's job to adjust beam current and target potential so that the highest highlights are just adequately discharged, while maintaining highest signal-to-noise ratio possible.

The target voltage may be varied in practice over a range of from minus 3 to plus 3 volts d.c. If the target voltage is gradually reduced (made more negative), the operator notices a point where the picture disappears. This is known as *target cutoff voltage*. If the target is

operated at a potential just slightly higher than this value, the greys are deteriorated and the blacks compressed, with very poor detail and low signal-to-noise ratio.

With higher target voltage, however, more beam current is required to discharge the strongest highlights in the scene. In order to attain a high signal-to-noise ratio, the operator must use only enough target potential to provide good resolution. In practice this occurs at a target potential of 1.8 to 2.2 volts *above cutoff potential*.

Beam current is adjusted to the point where good resolution of the strongest highlights is obtained. In practice, if the operator encounters an unforeseen excess of light in a scene, he does not hold it down by a more negative target voltage or by more beam current, but by *stopping down the lens iris*.

After the target potential and beam current adjustments have been made, the video amplifier gain controls may be adjusted for proper level.

Interpreting the camera monitor

Referring back to Fig. 1 in last month's issue, it is noted that each camera is connected to its own camera control and monitor unit, and that all of these units feed a mixer-amplifier monitor unit. Each of these units contain a cathode-ray tube used as a picture monitor (usually 7-inch), and a cathode-ray tube (usually 3-inch) used to monitor either line waveform (7,875-cycle sweep), or frame (30-cycle sweep) waveform.

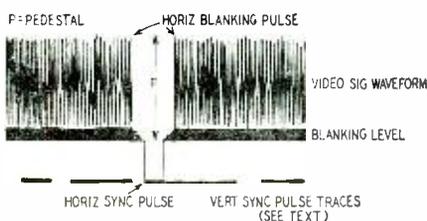


Fig. 2-a—Waveform of horizontal lines.
MARCH, 1952

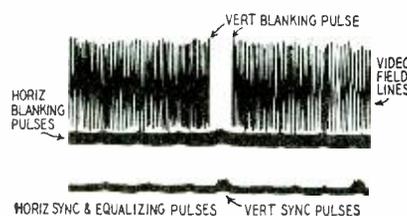



Fig. 2-b—Waveform at field frequency.

The interpretation of the waveform monitor warrants some description.

Fig. 1 is a representation of the composition of the video line. Since the waveform monitor may show the control pulses either on top or bottom, depending upon which stage it is connected in, we have arbitrarily chosen to show the blacker-than-black region at the bottom. The picture signal is shown by a varying line representing the varying light content from left to right of the scene. Television standards call for a maximum of 75% of the total signal to be allowed for this signal level, allowing 25% for sync and control pulses. The horizontal blanking voltage (pedestal) blanks out the return trace of the horizontal sawtooth in monitor and receiver scanners, making the return trace invisible to the viewers. During this time, the horizontal sync pulse is transmitted. After each line is scanned a horizontal pedestal voltage is applied.

The pedestal voltage and the various sync and control pulses for the pickup head are usually injected at the camera-control unit. The small waveform scopes on camera and line monitors supply the information needed for proper adjustment of video and pulse amplitudes. In practice, 100% modulation of the transmitter is usually referred to 2.0 volts (peak-to-peak) on this monitor screen. This includes the sync pulse peaks as shown in Fig. 1.

Fig. 2-a is a representation of a typical pattern as observed on the waveform monitor when the sweep is set to observe the horizontal line waveform. Two horizontal lines will be traced out on the screen for each scope sweep. A single horizontal pedestal is observed marking the end of one line of picture information and the beginning of the next. This screen image, however, needs some explanation since the horizontal line picture information is not a simple line of varying amplitude as in Fig. 1. The scope should be considered as scanning the video signal of all the lines of the

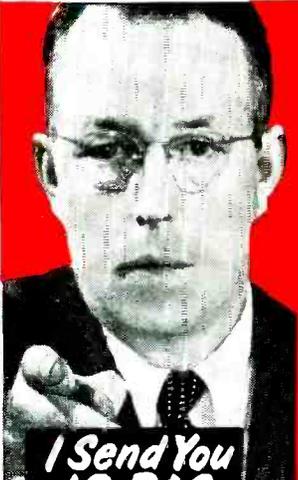


Learn RADIO TELEVISION

**- New Package Unit Plan - PAY AS YOU LEARN
NO MONTHLY PAYMENT CONTRACT TO SIGN!**

**I Send You
18 BIG
KITS
OF RADIO-
TELEVISION
EQUIPMENT**

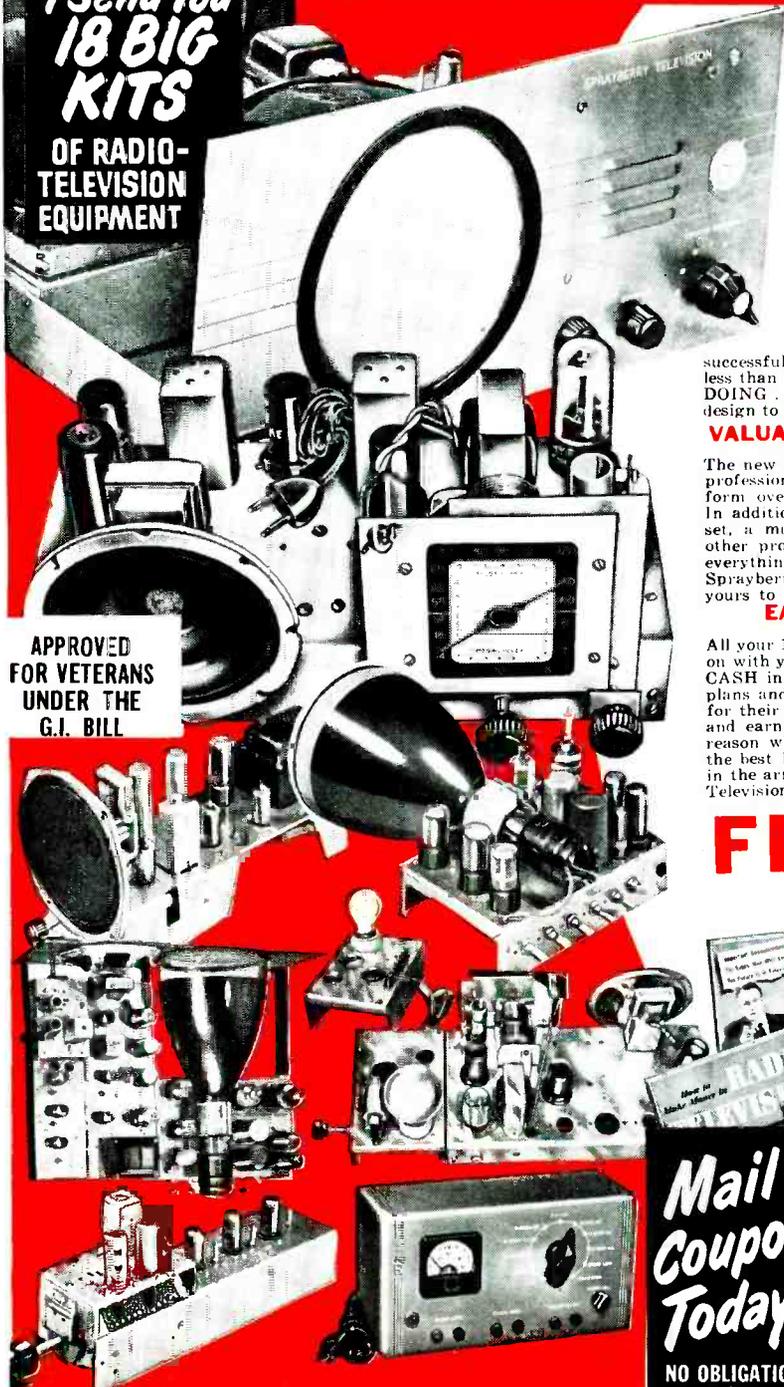**APPROVED
FOR VETERANS
UNDER THE
G.I. BILL**



**TRAIN IN 10 MONTHS OR LESS
At Home in Your Spare Hours**

Now . . . be ready for Radio-Television's big pay opportunities in a few short MONTHS! Frank L. Sprayberry's completely new "Package" training unit plan prepares you in just 10 MONTHS . . . or even less! Equally important, there is NO monthly payment contract to sign . . . thus NO RISK to you! This is America's finest, most complete, practical training - gets you ready to handle any practical job in the booming Radio-Television industry. In just 10 months you may start your own profitable Radio-Television shop . . . or accept a good paying job in this fascinating expanding field at work you've always wanted to do. Mr. Sprayberry has trained hundreds of successful Radio-Television technicians—and stands ready to train you in less than one year, even if you have no previous experience. You learn by DOING . . . actually working with your hands with equipment of special design to illustrate basic theory instead of relying on books alone.

VALUABLE EQUIPMENT INCLUDED WITH TRAINING

The new Sprayberry "package" plan includes many big kits of genuine, professional Radio-Television equipment. While training you actually perform over 300 demonstrations, experiments and construction projects. In addition, you build a powerful 6-tube standard and short wave radio set, a multi-range test meter, a signal generator, signal tracer, many other projects. All equipment is yours to keep . . . you have practically everything you need to set up your own service shop. The interesting Sprayberry book-bound lessons and other training materials . . . all are yours to keep.

EARN EXTRA MONEY WHILE YOU LEARN!

All your 10 months of training is AT YOUR HOME in spare hours. Keep on with your present job and income while learning . . . and earn EXTRA CASH in addition. With each training "package" unit, you receive extra plans and ideas for spare time Radio-Television jobs. Many students pay for their entire training this way. You get priceless practical experience and earn generous service fees from grateful customers. Just one more reason why the Sprayberry new 10 MONTH-OR-LESS training plan is the best Radio-Television training in America today. If you expect to be in the armed forces later, there is no better preparation than good Radio-Television training.

FREE 3 BIG RADIO-TELEVISION BOOKS

I want you to have ALL the facts about my new 10-MONTH Radio-Television Training —without cost! Act now! Rush the coupon for my three big Radio-Television Books: "How to Make Money in Radio-Television," PLUS my new illustrated Television Bulletin PLUS an actual sample Sprayberry Lesson—all FREE with my compliments. No obligation and no salesman will call on you. Send the coupon in an envelope or paste on back of post card. I will rush all three books at once!

SPRAYBERRY ACADEMY OF RADIO
Dept. 20-G, 111 N. Canal St., Chicago 6, Ill.

**Mail
Coupon
Today!**
NO OBLIGATION
No Salesman
Will Call

**IF YOU ARE
EXPERIENCED IN RADIO**

Men already in Radio who seek a short intensive 100% TELEVISION Training with FULL EQUIPMENT INCLUDED are invited to check and mail the coupon at the right.

SPRAYBERRY ACADEMY OF RADIO, Dept. 20-G
111 North Canal St., Chicago 6, Ill.

Please rush to me all information on your 10-MONTH Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me.

Name.....Age.....

Address.....

City.....Zone.....State.....

Please check Below About Your Experience

Are You Experienced? No Experience

Automatic 150-kw Station

World's largest remotely switched transmitter has some new design features


By T. W. DRESSER

LAST summer marked the opening of a new BBC high-power transmitter and mast radiator at Daventry, England, for the Third Program on the present wavelength of 464 meters (647 kc).


With a power of 150 kilowatts the new transmitter is more than twice as powerful as its predecessor, and has also been provided with a more efficient aerial, specifically designed to give as large a fading-free service area as possible.

Daventry has the longest history of any BBC transmitting station. Just over 26 years ago (in 1925) the BBC's first high-power transmitter for long-wave broadcasting—Daventry 5XX—was installed there, to be followed two years later by the high-power medium-wave transmitter 5GB. In 1932 the station was rechristened the Daventry Empire Station, following the installation of transmitters for broadcasting to the Empire on short waves. By 1937 the number of short-wave transmitters had increased to six, with a further increase to 11 by 1940, making Daventry at that time the BBC's most powerful short-wave broadcasting station. Meanwhile the long- and medium-wave services had been transferred to new and more powerful transmitters at Droitwich.

The new transmitter, designed and manufactured by Marconi's Wireless Telegraph Co., Ltd., is in the building that originally housed the 5XX transmitter. It consists of two identical transmitter units which can work in parallel, each complete in itself and each capable of an unmodulated carrier output power of 100 kilowatts. To conform with the Copenhagen wavelength plan the actual power used will be limited to 150 kilowatts. All the tubes—including those in the output stage—are air-cooled, a new departure for a BBC transmitter of this power and one that makes maintenance and remote control easier, for the transmitter is designed so that it will ultimately be possible to operate it from a remote point—from another building at Daventry or from Broadcasting House, London, for example—by means of signals sent over a single telephone channel. The BBC has had low-power remotely controlled

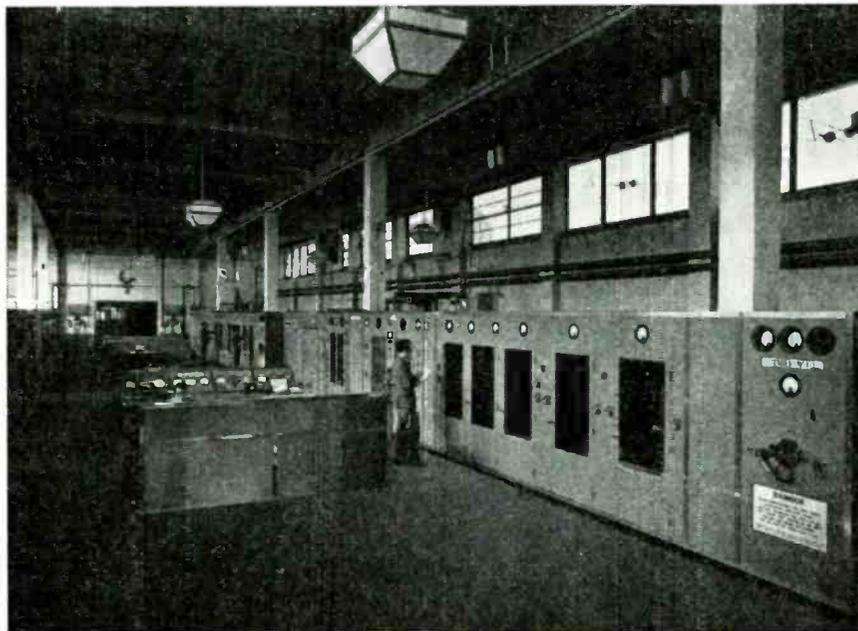


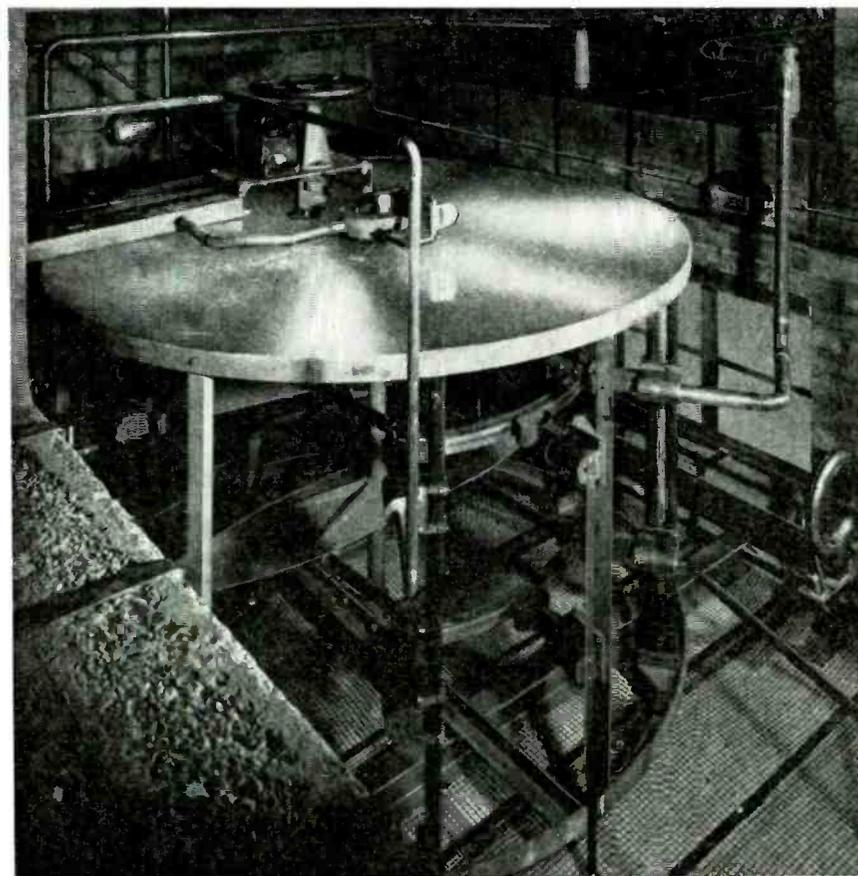The automatic station's main transmitting hall, showing four 100-kw transmitters.




With this switch the antenna may be remotely connected to either transmitter.

RADIO-ELECTRONICS

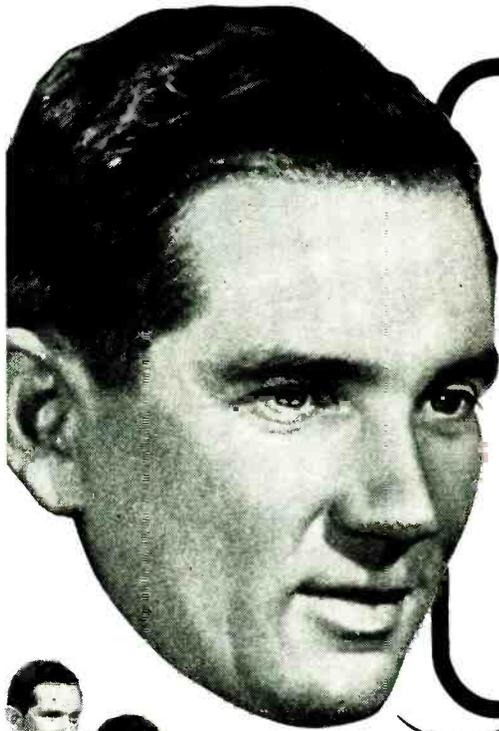

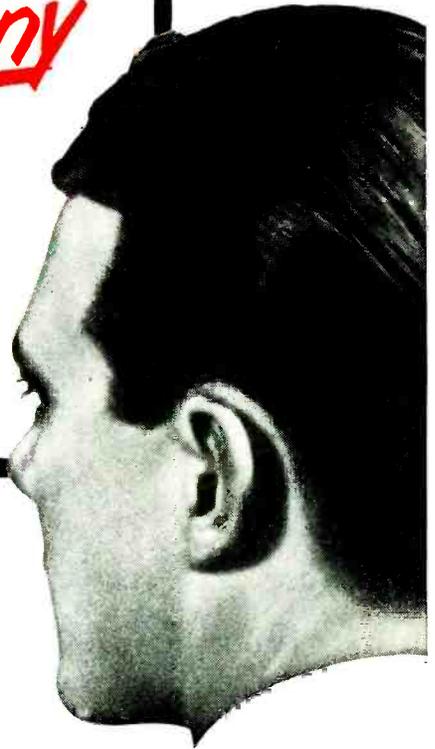How come you sell so many picture tubes, Sam?



"I'm using the CBS-Hytron Easy Budget Plan, Joe. My CBS-Hytron distributor gave it to me."



"Tell me more."

"Well, CBS-Hytron's Plan helps me sell TV picture tubes and service to many a customer who just doesn't have \$50 cash. Now I make sales I'd lose otherwise. My customer pays for the job painlessly a few dollars a month. Yet I get my cash right away — and can discount my bills with my distributor."



"Fine! How does it work, Sam?"

"Simple. I introduce my customer to the finance company authorized by CBS-Hytron. The finance company does the rest. Acts as my credit department to secure me against losses. Takes care of all the details . . . paper work, collections, etc. My customer gets his tube and I get my cash — at once."




"That's swell, Sam. Now I can see why you always have plenty of working capital."

"That's right. And talk about service! This CBS-Hytron Easy Budget Plan has even brought me immediate cash from old accounts I'd written off as bad debts. CBS-Hytron is perfectly willing, too, that my regular budget loans include my service work and other components besides CBS-Hytron tubes. I owe my CBS-Hytron distributor a vote of thanks for letting me in on this wonderful Plan."



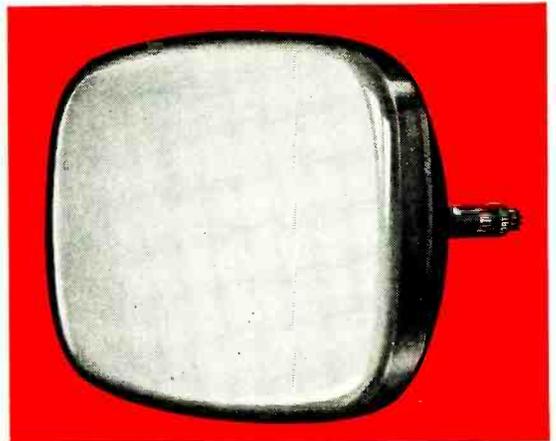"Fair enough! I've sure been losing sales I shouldn't, Sam. I need the CBS-Hytron Easy Budget Plan. CBS-Hytron tubes are tops, too. Thanks for the tip. I'll see my CBS-Hytron distributor today."



SAVE THE SALE No need for *you* to miss a single profitable picture-tube sale . . . just because your customer does not have the cash. Get the details on this original CBS-Hytron service for you. See *your* CBS-Hytron jobber . . . or mail this coupon . . . today!



MAIN OFFICE: SALEM, MASSACHUSETTS

HYTRON RADIO & ELECTRONICS CO.
SALEM, MASSACHUSETTS

Please rush me details on the CBS-Hytron Easy Budget Plan.

NAME.....
(Please print)

STREET.....

CITY.....STATE.....

FOR THOSE
HOT SPOTS

**AEROVOX AFH
ELECTROLYTICS**



Especially for elevated temperatures and high ripple currents, particularly in TV applications.

Light weight. High capacitance. Compact container. And of course the handy twist-prong mounting and easily-wired terminals.

Single, dual, triple- and quadruple-section units. Connections clearly indicated on rear label. Expanded listings provide outstanding selection of voltages, capacitances, combinations.

Ask your distributor for Aerovox AFH electrolytics. Consult the Aerovox expanded listings.



**FOR RADIO-ELECTRONIC
INDUSTRIAL APPLICATIONS
AEROVOX CORPORATION
NEW BEDFORD, MASS., U. S. A.**

In Canada: AEROVOX CANADA LTD., Hamilton, Ont.
Export: 41 E. 42nd St., New York 17, N. Y.

transmitters in service for some time, but this is the first time that an attempt has been made to apply remote control to one of its high-power transmitters.


About 1¼ miles east of the transmitter building on a site 460 feet above sea level a 725-foot mast radiator has been erected for the new transmitter, the tallest mast yet installed by the BBC for a medium-wave transmitter.

The mast is of lattice-steel construction and is triangular in cross-section, each face being 9 feet across. The base of the mast is poised on an insulator shaped like two truncated cones placed apex to apex. It is capable of withstanding a peak voltage of over 100 kilovolts without flashing over, even when wet. Between the two halves of the insulator is a ball joint which permits the mast to deflect several degrees from the vertical.

At a point 460 feet above the base the mast is divided into two sections by an insulator similar to the one at the base. Thus the lower section extends up to a height of 460 feet, then comes the insulator at the "nodal" point, and above it is the top section extending up another 265 feet. At the masthead there is a capacity top load consisting of a number of spokes projecting out to a distance of 35 feet, with their extremities connected together by wires. The spokes are hinged close to the mast so that they can be folded down if the capacity top is not required.

The most interesting feature about this mast radiator is that the radio-frequency power is fed into it across the insulator at the 460-foot level instead of at the base. This method is expected to reduce fading by minimizing the effect of the feed current, which with a conventional base feed distorts the vertical polar diagram by increasing the high-angle radiation.

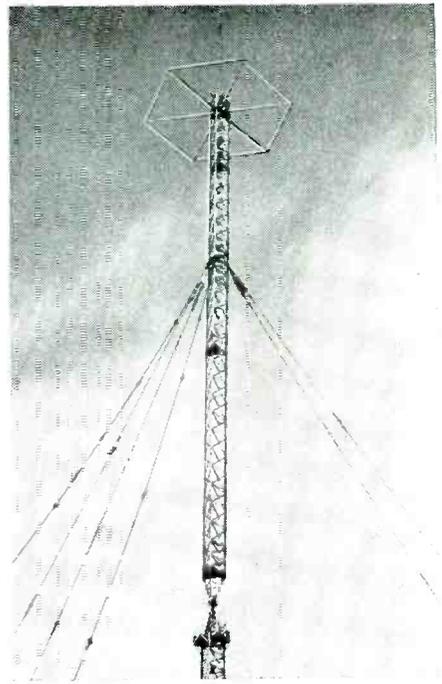
The transmitter output is connected to the antenna tuning house at the



Upper section of the 725-foot top-loaded radiator. The insulator near bottom of photo is 460 feet from the ground.

base of the mast by a 12-wire unbalanced open-wire transmission line supported on steel poles 18-feet high and spaced at 150-foot intervals. The outer conductor of the line is formed by eight wires on a pitch circle having a diameter of 1 foot 6 inches, and the inner by four wires on a circle of ½-inch diameter. The length of the feeder is 2,640 yards, and the loss is approximately 0.35 db. The ground system consists of a 90-foot square screen of wires and a spider's web of wires radiating out to a distance of 750 feet at 5 degree intervals, and buried nine inches underground.

—end—

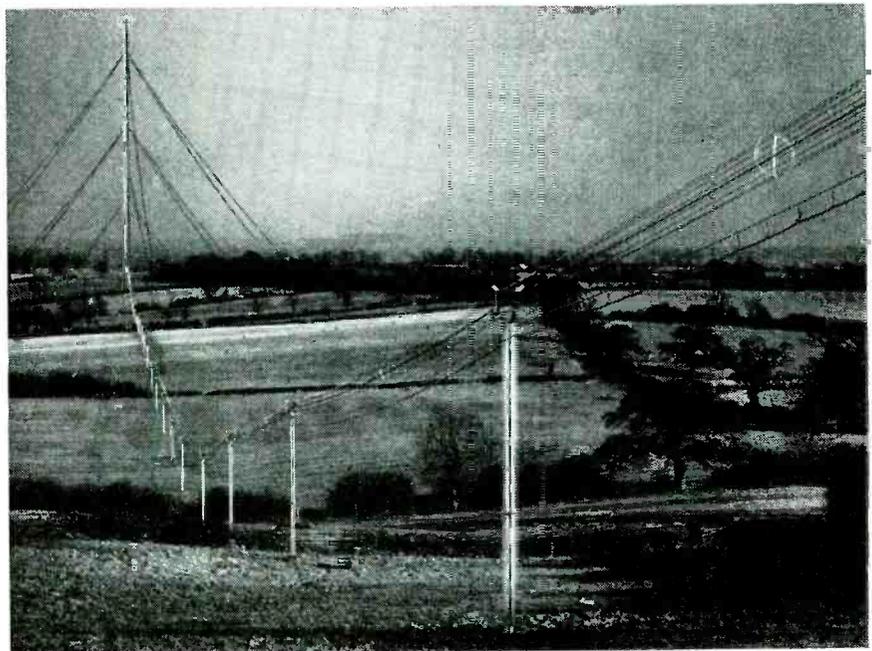

A twelve-wire unbalanced line runs between the transmitter and antenna tuning house.

All photos courtesy British Broadcasting Co.

RADIO-ELECTRONICS

STIKIT-UP!

*the NEW
AMAZING*

INDOOR Directronic TV AERIAL SYSTEM

- ALL CHANNELS
- ANYONE CAN INSTALL
- ADHERES TO ANY SURFACE
- 360° ELECTRONICALLY-SWITCHED BEAM
- FLICK OF SWITCH CLEARS PICTURE

**9⁹⁵
LIST**






SNYDER MFG. CO. PHILADELPHIA

DALIS, New York • ALMO, Philadelphia • RADIO PARTS, Chicago

FRESHMAN, Cleveland • WHOLESALE RADIO, Baltimore • KAEMPER & BARRETT, San Francisco

VAN DER HOUT, Canada • Export: ROBURN AGENCIES, New York • AND OTHER DISTRIBUTORS, EVERYWHERE

MARCH, 1952

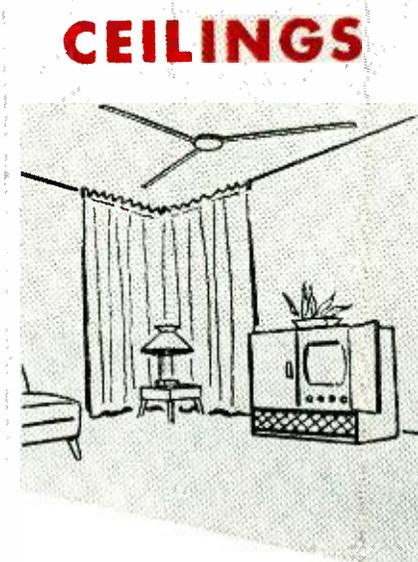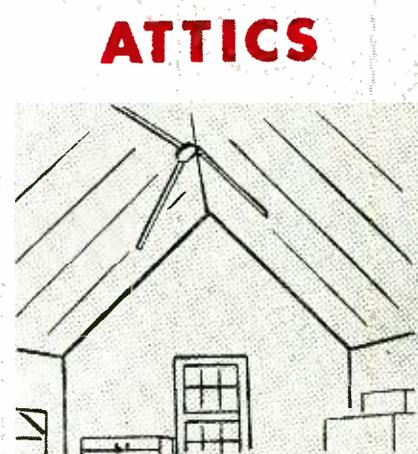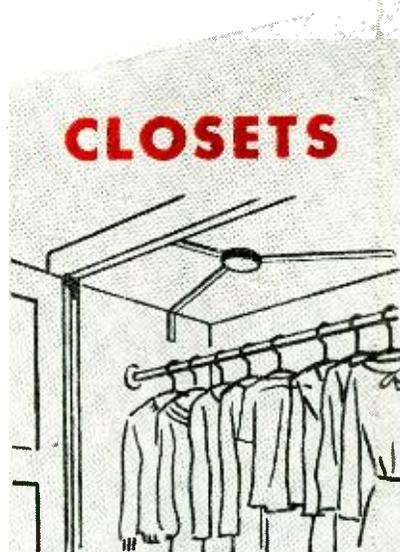

NEW a "must" book
for every
TV Service Technician

**"Servicing TV
in the
Customer's Home"**



**SAVES TIME
SAVES WORK**
Earns More
for You
on Outside
Service Calls

shows how
to diagnose trouble using
capacitor probe and VTVM

Here's the book you've been asking for—practical, proved help to make your outside TV servicing really effective and profitable. Saves time, work and chassis hauling . . . shows you how to make successful repairs on the spot. You learn the following: 1. A simple, effective method for tracing down trouble, using your VTVM and a simple capacitor probe. 2. Methods for finding your way around a strange circuit—shows you how to "pull tubes" and diagnose trouble by observing audio and picture effects. 3. How to judge TV set performance by analysis of the test pattern. 4. Methods for making adjustments in the field. You'll want this essential, profit-building book. Handy pocket size; sturdy cover. **\$1.50**

ORDER TC-1. Only
Pays for itself on the very first job.

HOWARD W. SAMS & CO., INC.

Order from your Parts
Jobber, or write direct to
HOWARD W. SAMS & CO.,
2201 E. 46th St., Indianapolis 5, Ind.

**ORDER
TODAY**


Send . . . copy(ies) of "SERVICING TV IN THE
CUSTOMER'S HOME," \$1.50 per copy.

(Check) (money order) for \$ enclosed

Name

Address

City State

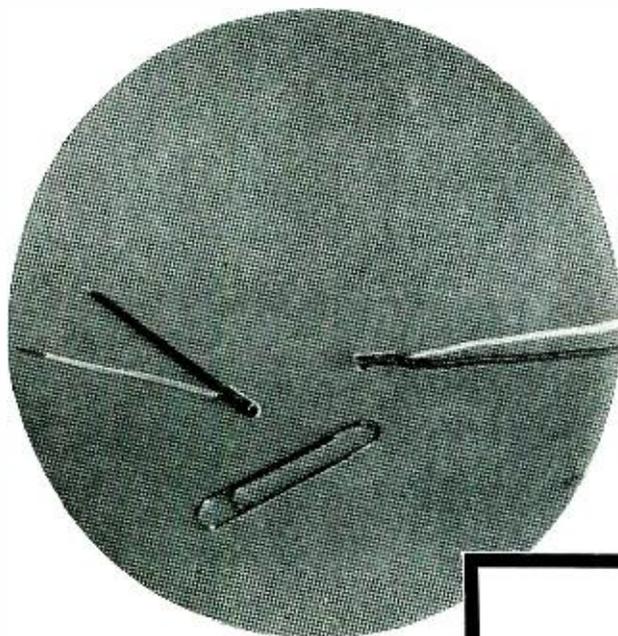

Two of the diminutive
type 1N77 photodiodes.

Subminiature Germanium Photodiodes

By **RUFUS P. TURNER**

THE relatively large size of photo-cells and phototubes often hinders miniaturization of photoelectric equipment. Even the *small-sized* phototubes which have made their appearance in recent months are too big for many projected applications. Nor has the situation been improved materially by reducing the area of selenium and copper-oxide photocells, since the internal shunting capacitance of these cells remains high and the frequency response correspondingly poor.

The recent development of the Syl- vania type 1N77 germanium photodiode makes available a light-sensitive device of very small proportions. The rod-shaped, molded transparent plastic housing of the 1N77 is only $\frac{5}{16}$ -inch in diameter and $\frac{3}{16}$ -inch long. This small over-all size adapts the photodiode es-

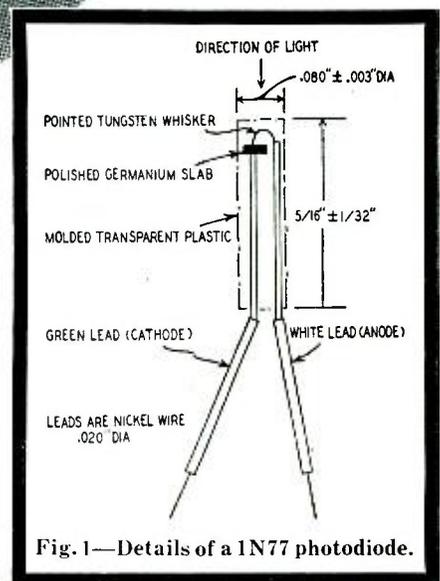


Fig. 1—Details of a 1N77 photodiode.

They may open many
new applications
in photoelectricity


pecially to subminiature light-sensitive apparatus. The 1N77 may be mounted directly in the tip of a pencil-type light probe for evaluating the illumination of small areas. The sensitive area of the device is approximately *one ten-thousandth of a square centimeter*. The capacitance accordingly is low, of the order of 2 μ f, and the frequency response therefore high—greater than 100 kc. The wide frequency range of the 1N77 makes it suitable for operations involving chopped or modulated light, such as sound reproduction, facsimile, and similar processes in which high-frequency operation is important.

Constructional details

The small size of the 1N77 may be noted from the photograph. Two of the

A Guiding Beacon For
Quality Electronic Parts

Your Local
RADIART
Distributor

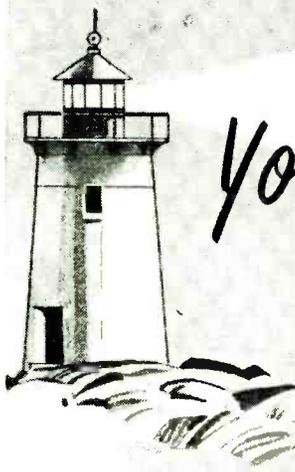

RADIART Sales Offices Across The Nation



These Are The Cities With RADIART Distributors in Illinois, Kansas, Missouri and Wisconsin.

ILLINOIS

- ARLINGTON HEIGHTS
- AURORA
- BELLEVILLE
- BENTON
- BLOOMINGTON
- CHAMPAIGN
- CHICAGO
- DANVILLE
- DECATUR
- JACKSONVILLE
- JOLIET
- KANKAKEE
- MOLINE

OAK PARK

- PEORIA
- QUINCY
- ROCKFORD
- ROCK ISLAND
- SPRINGFIELD
- TUSCOLA
- WAUKEGAN

KANSAS

- PITTSBURGH
- SALINA
- TOPEKA
- WICHITA


MISSOURI

- BUTLER
- CAPE GIRARDEAU
- JEFFERSON CITY
- JOPLIN
- KANSAS CITY
- POPLAR BLUFF
- SPRINGFIELD
- ST. JOSEPH
- ST. LOUIS

WISCONSIN

- MADISON
- MILWAUKEE
- RACINE

BUY OF THE MONTH

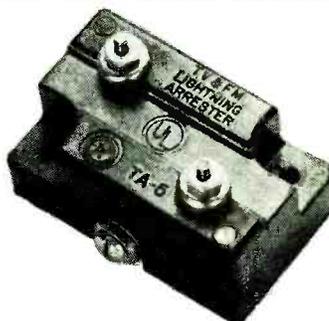

THE RADIART FULL SIZE LIGHTNING ARRESTOR is the talk of the industry. Here is a FULL SIZE arrestor at the price of a midget... and now handles OPEN WIRE TRANSMISSION lines—it fits anywhere... handles all size twin leads and its sharp toothed cup washer eliminates wire stripping. Real protection—yet does not unbalance the line. Permanently sealed against temperature changes and humidity. So why pay more—get the best for less! See your RADIART DISTRIBUTOR... or write us—

FOR NAME OF YOUR NEAREST RADIART DISTRIBUTOR

USE COUPON BELOW

RADIART SALES CO. 177 Sunset Avenue • Glen Ellyn, Illinois

.....Please send names of the Radiart Distributors in my area stocking the following Radiart products in which I am interested: Tele-Rotors, Vibrators, TV and FM Antennas, "Spee-Dee" Chimney Mounts, Lightning Arresters, Auto Aerials, Power Supplies

.....Please have a Radiart Distributor call on me.

Name _____

Address _____

City _____ State _____



THE RADIART CORPORATION CLEVELAND 2, OHIO

VIBRATORS • AUTO AERIALS • TV ANTENNAS • ROTATORS • POWER SUPPLIES

Put across that PERSONALITY

WITH AN **E-V** MIKE



Model 950
CARDAX
Crystal
Cardioid
with Dual
Response
List, \$42.50



Model 636
Slimair
High Fidelity
Dynamic
List, \$70.00



Authorized
Distributors
Everywhere

Model 630
High Fidelity
High Output
Dynamic
List, \$42.00


REPRODUCE VOICE AND MUSIC... ACCURATELY!

The microphone makes a difference in the sound you hear! As a radio ham, sound specialist, or home recording fan, you are certain to reproduce the individual quality and personality of speech or song or orchestral music... with a research-engineered E-V mike! Send today for illustrated bulletin.

NO FINER CHOICE THAN

Electro-Voice

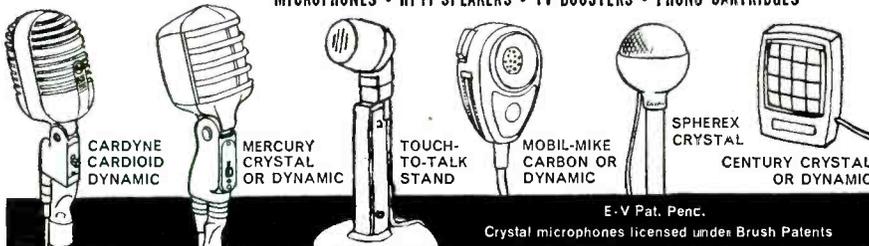421 CARROLL STREET • BUCHANAN, MICHIGAN
Export: 13 East 40th St., New York 16, N.Y., U.S.A. Cables: Arlab
MICROPHONES • HI-FI SPEAKERS • TV BOOSTERS • PHONO CARTRIDGES



CARDYNE
CARDIOID
DYNAMIC

MERCURY
CRYSTAL
OR DYNAMIC

TOUCH-
TO-TALK
STAND

MOBIL-MIKE
CARBON OR
DYNAMIC

SPHEREX
CRYSTAL

CENTURY CRYSTAL
OR DYNAMIC

E-V Pat. Penc.

Crystal microphones licensed under Brush Patents

units are shown beside a paper clip for comparison.

Fig. 1 shows structural details of the 1N77. The photodiode is similar in construction to the simple crystal diode. In the 1N77, a sharply pointed tungsten whisker is placed in firm contact with the polished surface of a processed germanium slab. The assembly is molded in a colorless, transparent plastic, with the diode elements close to one end of the molding. Leads of .020-inch diameter nickel wire, from the germanium and whisker, are brought out of the other end. The extended portions

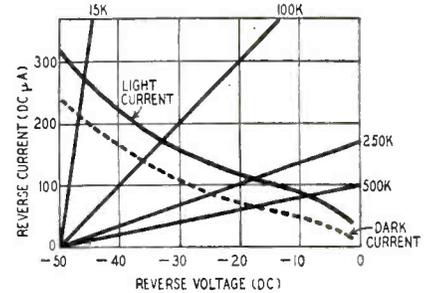


Fig. 2—Static characteristics, 1N77.

of the leads are insulated. For identification the cathode lead which is connected to the germanium slab is covered with green spaghetti wire; the anode lead connected to the whisker is insulated with white spaghetti. The anode lead is approximately 4 inches long, while the cathode lead is approximately 4½ inches.

The 1N77 may be mounted and operated in any position, provided the actuating light rays are allowed to enter the end nearest the diode assembly and perpendicular to the "outside" face of the germanium slab, as shown in Fig. 1.

Operating principle

The photodiode uses an effect long known to workers with germanium diodes—that illumination of the whisker-germanium contact area momentarily changes the conduction characteristics of the diode. When a polarizing voltage is applied to the diode, the current

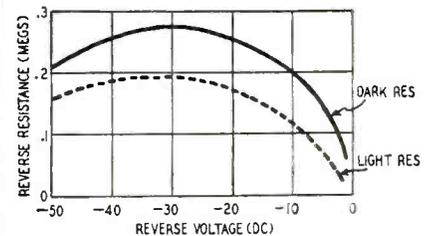


Fig. 3—D.c. resistance characteristics.


flowing through it increases when the contact area is illuminated. This is the result of a decrease in the diode resistance—a complex effect in the atomic structure of the germanium. Both forward current (anode positive) and reverse current (anode negative) may be increased by means of illumination. However, experimental results indicate that the device works best by using the reverse characteristic. The germanium diode also possesses a small photovoltaic property—that is, in the ab-

the most convenient TV tower ever made

THE TEL-A-RAY

SWING-OVER* TOWER

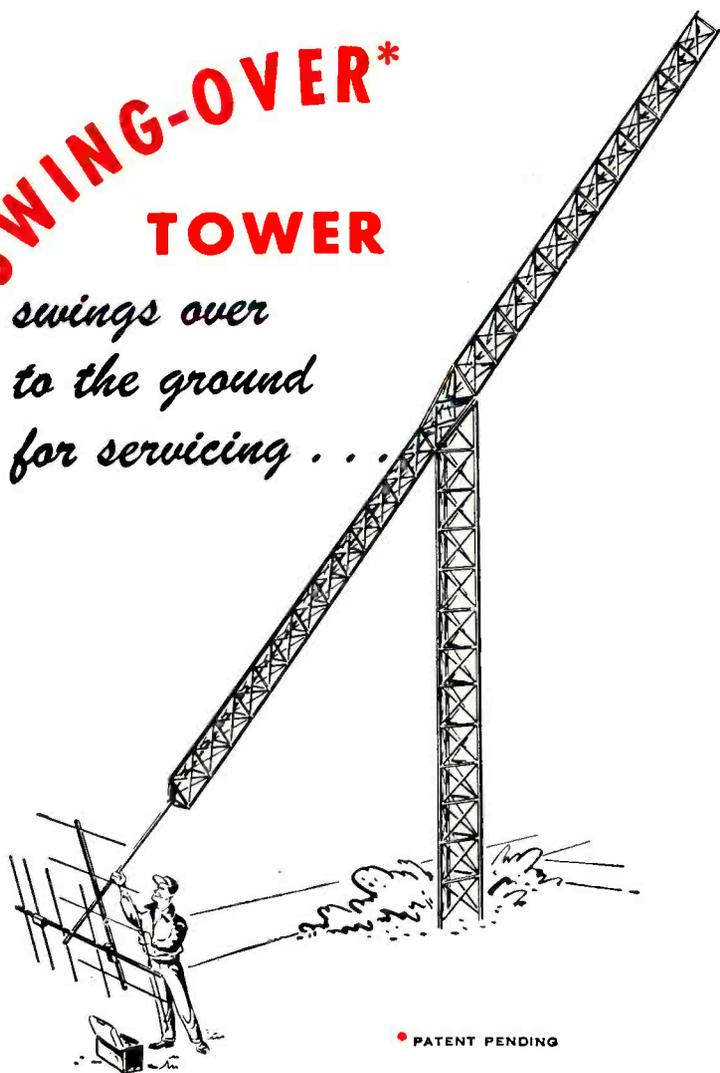*swings over
to the ground
for servicing . . .*



The biggest new idea in television — the Tel-a-Ray Swing-Over Tower* — swings over to the ground for easy servicing! One man can raise or lower this counterbalanced tower in three minutes!

Model TT1, for ground installations, is 50 feet high when a recommended 10 feet of water pipe is added — can be quickly erected with no guy wires.

Model TT2 is designed for roof tops, reaches up 24 feet with the addition of an eight-foot pipe.

Although light in weight, the Swing-Over Tower is ruggedly built with steel angles and welded construction.

Simple to assemble . . . no machinery necessary . . . low in price.

Write today for information.

MARCH, 1952

FOR WONDERFUL
TV RECEPTION
WHEREVER YOU ARE




The weatherproof Model T antenna . . . brings in wonderful reception up to 200 miles.



Only low-priced Pre-Amplifier on the market, the TB. Multiplies signal gain . . . holds noise to a minimum.



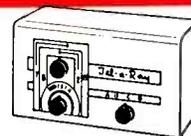Butterfly Swivel-Positioned TV and FM antenna . . . designed to give the finest reception in primary areas.



Tel-a-Ray's new Switching Booster (Model PTB1) — one switch changes channels and antennas. Eliminates the need for a separate booster for each antenna . . . for as many as four antennas. Automatic features make this outstanding.

FOR COMPLETE INFORMATION WRITE

Tel-a-Ray

ENTERPRISES, INC.



BOX 332E
HENDERSON, KY.

Some Plain Talk about Making More Money

HOW WE CAN HELP

...with the RCA Battery Line

As Radio men, we can do it by working together


Here's how we'll help you build a more profitable business with RCA BATTERIES:




1 We will advertise you, the Radio Service-Dealer on national network radio and TV programs. We'll tell millions of listeners that you are best qualified to sell and install RCA Radio Batteries.



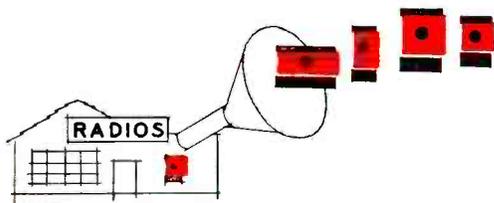2 We will help you advertise for repeat sales on the RCA Battery carton. Millions of volume-type RCA Batteries will carry a printed message directing the user to come back to you for replacements. Below this message will be a space where you can stamp your own name with a personalized stamp which you may obtain from your RCA Battery Distributor.



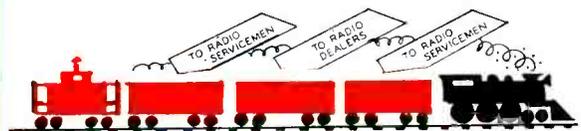3 We will continue to channel our principal battery distribution to you as a Radio Dealer and Serviceman which means that you get profitable repeat business with RCA BATTERIES.



4 We will continue to provide speedy, dependable service backed by the only nation-wide warehousing and distribution organization geared to the needs of the radio trade.

DOESN'T THIS MAKE SENSE TO YOU?

As a Radio man, you should handle the Radio Battery line of the Radio Company that wants to help you prosper. By doing this, you get extra help . . . four-way help. And you make more money. It's as simple as that.

for Local Radio Dealers and Servicemen:

YOU MAKE MORE MONEY

With the RCA line you get ALL THESE EXTRA BENEFITS, TOO

You get **TREMENDOUS BRAND ACCEPTANCE** . . . because RCA is the best-known, most-advertised name in the radio field. This means your battery sales are fast, easy, profitable with RCA.

You get **COMPETITIVE PRICES**. RCA Batteries are priced to sell against the toughest competition.

You get **TERRIFIC SELLING AIDS** . . . signs, banners, displays, kits, merchandisers that are unique . . . to mark your store as headquarters for RCA Batteries.

You get **RADIO-ENGINEERED BATTERIES** . . . power-packed for *extra* listening hours . . . and built to exacting standards of quality. They represent the combined skills of both battery engineers and radio engineers.

You get a **ROUNDED LINE** to fill virtually every portable and farm radio requirement. Seven popular types will fill about 80% of your needs. You cut down on stocking problems . . . are sure to have the right batteries on hand—at the right time!

Get started with RCA Batteries . . . NOW

Let us help you make this your banner year for battery sales. Call your RCA Battery Distributor right now. Get set with the *Radio Battery* for the *Radio Trade* . . . RCA. And *let us help you make more money . . . starting TODAY.*

Why YOU are so important to us.

You're in the *Radio Business*. So are we.


You're interested in promoting the sale and use of *Radio products*. So are we.

If you prosper, so do we!

That's why we channel our battery distribution to *you as a Radio outlet*.

That's why we advertise *you, the Radio-Service Dealer* on national radio and TV programs. That's why we help promote your store right on the actual RCA Battery.

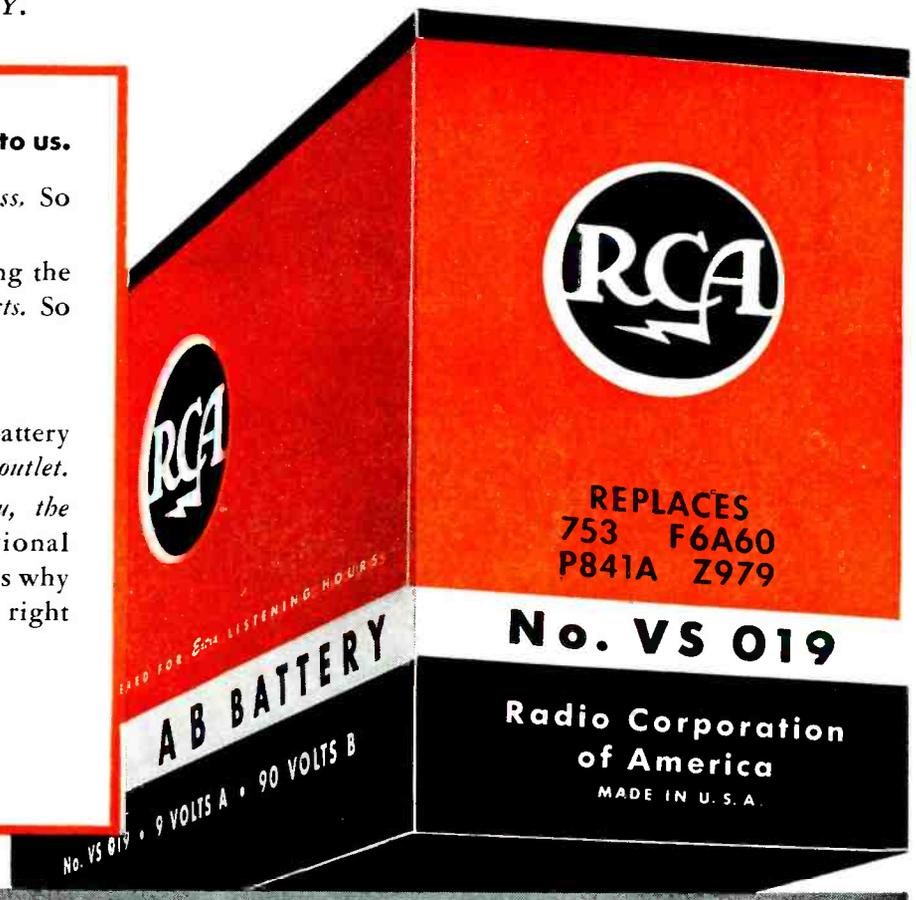*You're a Radio Man.
We're a Radio Company.
Let's prosper together!*




RADIO CORPORATION of AMERICA

RADIO BATTERIES

HARRISON, N. J.

MARCH, 1952

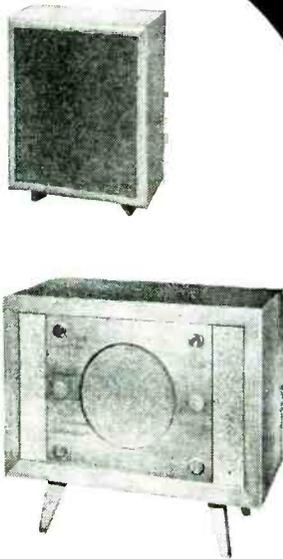TYPE C BLONDE OR MAHOGANY FINISH—FOR 8", 12" OR 15" SPEAKERS



acoustically-correct
handsomely styled
durably constructed

**BASS REFLEX
CABINETS** by

Jensen

JENSEN MANUFACTURING COMPANY
DIVISION OF THE MUTER COMPANY
6601 S. LARAMIE AVENUE • CHICAGO 38, ILLINOIS

WRITE FOR
DATA SHEET 152

TYPE D WALNUT—FOR 12" OR 15" SPEAKERS



TYPE B BROWN LACQUER FINISH—FOR 12" SPEAKERS



TYPE H BROWN LACQUER FINISH FOR 8" SPEAKERS



TYPE J WALL OR POST MOUNTING—BROWN LACQUER FINISH—FOR 6" OR 8" SPEAKERS



(FERIDYNAMIC TOTAL ENCLOSURE)

sence of any polarizing voltage, it will generate a voltage under the influence of illumination, the anode (whisker) becoming positive and the cathode (germanium) negative.

Fig. 2 shows the reverse-voltage-reverse-current curves for the 1N77 operated with various values of load resistance. Fig. 3 shows a typical reverse-resistance curve. Fig. 2 assumes that a circuit similar to the one given in Fig. 4 will be employed; i.e., with photodiode, d.c. voltage, and load resistance connected in series. Fig. 4 illustrates response of the 1N77 circuit to pulsed light at 1,000 cycles.

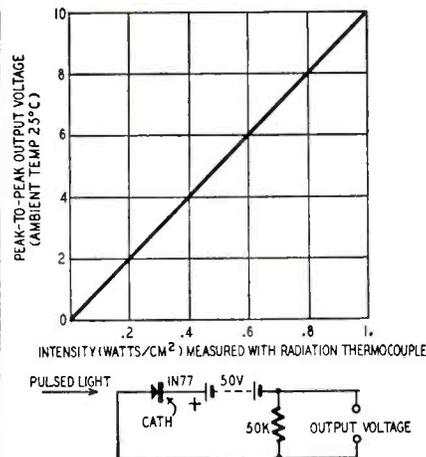


Fig. 4—The output with pulsed input at 1,000 cycles. Circuit at bottom of figure was used to obtain the curves.

In electrical characteristics, the 1N77 is similar to the 1N34 crystal diode, except that the peak reverse voltage of the photodiode is somewhat higher. Special germanium processing makes the reverse resistance of the 1N77 especially sensitive to illumination.

The 1N77 is most sensitive to radiation in the infra-red and near infra-red regions. The spectral response peak is at 1.7 microns. Response is negligible in the ultra-violet region.

Maximum voltage output is obtained with the higher values of load resistance, while maximum power output results with low load resistance values. In production units, the dark current (as measured with a 50-volt d.c. supply and zero load resistance) is kept below 0.5 ma. In pulsed-light operation (See Fig. 4), the output voltage has the same waveform as that of the applied light.

The actual mechanisms whereby the diode resistance is varied by radiation intensity and also through which current is generated by photovoltaic action in germanium-tungsten point contact devices may be explained only in the complex terms of semiconductor physics. Such an explanation is beyond the scope of this article. The reader who desires a complete exposition of this process is referred to any of the textbooks on the modern theory of semiconductors and electrical conduction in solids.

Higher light intensities are required with the germanium photodiode for a given voltage output than with photo-

260
260
260
260



Simpson

volt-ohm-milliammeter that
outsells all others combined.

260
260

Hi-Fidelity Crystal Hand Mike . . . Hi-impd. Moulded bakelite case; 6 ft. cable. ONLY \$3.95
ALNICO MAGNETS . . . Set of two 3/4" O.D. 2.29
 Bar Magnets, 4 1/4" & 1-5/16" boxed . . . 2.29
 Flat Bar Magnet . . . 1 7/8" x 1/2" x 5/16"79
 Round Bar Magnet . . . "U" Magnet . . . 1/2" x 3/4" x 5/8" . . . 59c 10 . . . 5.50
 Alnico Magnet Kit . . . Power-ful Bar, Block, "U", Rod, etc. Kit of 10 assorted. . . 1.98

Leotone

HEARING AID PARTS . . . MIDGET OUTPUTS. (3x1/2) 50B5, 35B5 to V.C. . . . 49c 6/2.49
 Midget Audio Chokes . . . (3x1/2) . . . 49c 6/2.49
 4500 DC 49c 6/2.49
 Hearing Aid Amplifier (2 tube) . . . MAKE A REAL VEST POCKET RADIO adding simple tuner, 1/2" x 2 1/2" x 5" WITH SCHEMATIC FOR 2 or 3 TUBE SET. Less tubes, case. 2.49
 Hearing Aid Tubes . . . set of for amplif. 2.98
 Hearing Aid Bone Conduction Receiver (1/2" x 3/4" x 1 3/4" Excl. MUSICAL CONTACT MIKE, DETECTAPHONE, MINI-SPKR. Lo-impd. . . 2.49



20 Push-Back Wire . . . Red, Yel., Blue or Blk. 100 ft.1.89
!! SWITCH SPECIALS !! . . . DPT BAT TOGGLES (AHH). 6A/125V. Bakelite cased. Set. Role 49c 12/5.49
 Rotary Switches . . . deck 1/2" shaft. 3 Pos. D.P., or 6 Pos. S.P. . . . ea. 39c 6/1.98
 DPT Flush Plate Bat Toggle (C-H 8715K2) . . . Lum. tip. 1 3/4" mtr. Sprng. Ret. . . . 59c 6/3.25

Variable Condensers . . . four 250mmf sects. 1/4" shaft. 7 1/2" x 1 3/4" 3/2.98
 2 Gang Superhet or TRF Variables69
 W-110B Field Fire . . . rolls 100-400 ft. ONLY 1c
 220V/110V Step-Down Ballast . . . 60W . . . per ft. 1.39
 Gun Sync. Control Box (F-childMk3) . . . "GOLD MINE" of new Relay, Toggle, Fuses, etc. . . . 2.95
"BUY OF THE MONTH" . . . 60 CYCLE SYN. CHRONOUS MOTOR . . . 110V. Part of Watt-Hour Meter check full of Matched Gears, Worms, Dials, etc. 1.98
 Portable Metal Utility Box . . . 6x6x6 3/4". Hinged lid. Web carrying strap. 69c 3/1.98
 Polystyrene . . . 12" length. 10D. 1/4" -10c; 3/8" -20c; 1/2" -36c; 5/8" -55c; 3/4" -79c; 1" -1.29
 Tubing . . . (O.D.): 1/4" -10c; 3/8" -12c; 1/2" -17c; 5/8" -23c; 3/4" -27c; 1" -36c; 1 1/4" -49c
 Amber Jewel Assy. . . LC Mtg. base. 39c
 5" Leather Scope Visor . . . rubber eye-piece.79

BARGAINS IN KITS . . . JUMBO RADIO PARTS KIT. 17 PDLB. of: COILS, SOCKET, WIRE, RESISTORS, CONDENSERS, CHASSIS, SWITCH, ETC., ETC. Shpg. Weight 21 lbs. 3.95
 Radio Hardware Treasure . . . FULL LB. CAN of Nuts, Screws, Washers, Lugs, etc. . . 1 lbs./1.98
 Moulded Bakelite Condensers00001 to .2 mfd., 200-600V. Kit of 50 assd. 1.98
 Rotary Selector Switches . . . multi-point contact. Kit of 6 assd. 1.75
 Knobs . . . screw, spring. Kit of 25 assd.98

FACTORY SPEAKER REPAIRS SINCE 1927"
 Min. Order \$3.00 20% deposit on all COD's
 Please add sufficient postage. Excess refunded
 Full remittance with foreign orders

LEOTONE RADIO CORP. . . . 67 Dey Street, New York 7, N. Y.

Replace Your Old TV Aerial With The NEW Snyder

360° MOTORLESS TV AERIAL

SAME CLEAR PIX AS MOTOR ROTATING AERIAL SYSTEMS COSTING TRIPLE THIS PRICE

Only \$18.95

Complete with 3 1/2" mast sections, 75 ft. of 3 cond. cable. Electronic beam selector switch. Connecting stubs, guy ring mounting base.

For Ultra Fringe Electronically beams in complete 360° rotation to give clear picture on all channels. You choose direction with Directronic selector switch. Mounted on or near TV set. 18 hi-tensil 3/8" aluminum alloy elements. Complete ready to install.

AX-599 DIRECTRONIC ARRAY FOR FRINGE Same as TX-599 less mast 16.95
 AX-56 DIRECTRONIC ARRAY FOR CITY AREA 6 element array with switch, lead-in less mast \$9.50

STEEL MAST SECTIONS weather treated.
 10 Ft. 1 1/4" dia. \$2.19
 5 Ft. 1 1/4" dia. 1.35
 Chimney Mount Brackets CM-100 1.59
 Wall Mount Brackets WB-2. Adj. to 18" Heavy Duty 3.75

Order from Dept. RE-12, or call Mulberry 2134
 WRITE FOR FREE F.Y.I. BULLETIN

WHOLESALE RADIO PARTS CO., Inc.
 311 W. Baltimore St.
BALTIMORE 1, MD.

MARCH, 1952

cells and phototubes of other types. This is not necessarily a drawback, since sufficient illumination is available at close range in many applications. Such applications include counters, communication and recording devices employing punched tape, sorters, densitometers, turbidity meters, sound-track pickup, etc. Lens systems and filters may be employed to advantage with the 1N77.

Applications

The basic direct-current photodiode circuit is shown in Fig. 4. When this circuit is employed with steady, unmodulated illumination, output voltage may be applied to the input terminals of a d.c. amplifier, which in turn may actuate a rugged relay, counter, or indicating meter.

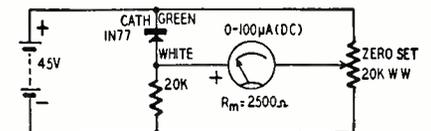


Fig. 5—Bridge type light meter circuit.

Fig. 5 shows a bridge-type light meter employing the 1N77. In this arrangement, the cell is darkened and the potentiometer is adjusted to zero the meter. Illumination then will cause the meter to deflect upscale. If the meter is zeroed, on the other hand, under illumination, interruption or attenuation of the light will produce downscale deflection. If desired, the meter may be removed from the circuit and the output terminals of the bridge circuit connected to the input of a d.c. amplifier.

Fig. 6 shows how the 1N77 may be connected to an a.c. amplifier when the photodiode is operated from pulsed, chopped, or modulated light and more voltage or power is required than the diode alone can furnish. A power-out-

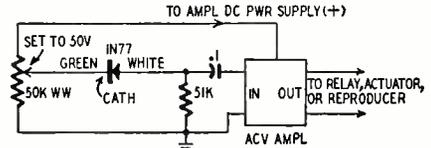


Fig. 6—Amplifier for modulated light.

put stage in the amplifier may drive an electromechanical device or reproducer. Possible interrupted light sources for operation of this circuit include shutters, film sound tracks, punched tape, and flasher tubes such as Strobotrons and glow modulators.

The 1N77 is adaptable to other conventional circuits in which other types of photocells commonly are specified. When operated within its limits, the germanium photodiode affords the best compromise between size and sensitivity available up to this time.

This photodiode—or even smaller modifications of it—may have future applications not now foreseeable. The possibility of building up a relatively fine mosaic out of these units is only one example of the possibilities which may open up entirely new fields not now occupied by phototubes.

—end—

BOOK SHELF



ENCYCLOPEDIA on CATHODE-RAY OSCILLOSCOPES and THEIR USES
 by Rider and Uslan

1. The most complete source of practical, usable knowledge concerning the oscilloscope ever published. Covers practically every kind of scope manufactured during the past ten years. Hundreds of pages alone are devoted to actual application plus complete, detailed treatments of auxiliary equipment, measurements, wave-forms, visual alignment of AM-FM-TV receivers and more, much more. A "must" for anyone using an oscilloscope. Completely indexed, with 992 pages (8 1/2 x 11") 3,000 illustrations. \$9.00

2. **VACUUM-TUBE VOLTMETERS**, by Rider & Barber. Completely revised. Covers theory, functions, operation and applications of the VTVM in detail. Typical chapters: Triode Vacuum-Tube Voltmeters; Probes for DC & RF; Calibration and Testing. 432 pp. (5 1/2 x 8 1/2") ill. \$4.50

3. **TV AND OTHER RECEIVING ANTENNAS**, by Bailey, is a source book on antennas of all types. Typical chapters: The Center Fed Zero DB Half-Wave Antenna; Parasitic Element Antennas; The TV Signal and Its Bandwidth; Vertically Polarized Antennas. 606 pp. (5 1/2 x 8 1/2") ill. \$6.00

4. **TV INSTALLATION TECHNIQUES**, by Marshall. A practical timely "how-to-do-it" book on antenna installation and receiver adjustment. Typical chapters: Materials and Methods Used in Installations, High Mast and Tower Installations; Municipal Regulations Governing TV Installations. 336 pp. (5 1/2 x 8 1/2") 270 ill. \$3.60

5. **TV MASTER ANTENNA SYSTEMS**, by Kamen & Dorf, covers all popular distribution systems now in manufacture, with schematics, performance figures and design data. Typical chapters: Installing Master Antenna Systems; Basic TV Antenna Systems; The Need for Master Systems. 356 pp. (5 1/2 x 8 1/2") ill. \$5.00

6. **RECEIVING TUBE SUBSTITUTION GUIDE BOOK**, by Middleton. Lists 2,500 radio, TV and electronic tube substitutions in numerical sequence for quick reference. Gives performance ratings and any necessary wiring changes. Also RTMA color codes, transformer and condenser substitutions. 225 pp. (8 1/2 x 11") \$2.40

6a. **FIRST SUPPLEMENT TO ORIGINAL GUIDE BOOK** lists 650 completely new and different tube substitutions. Includes wiring instructions and illustrations of original and substitute tube sockets. 48 pp. (8 1/2 x 11") \$0.99

Buy these books now at your jobbers... leading bookstores... or—

MAIL THIS COUPON—TODAY

JOHN F. RIDER, Publisher, Inc.
 480 Canal Street, New York 13, N. Y.

Please send me book(s) circled. I understand, if not satisfied, I may return them within 10 days for full refund.

1 2 3 4 5 6 6a

NAME _____
 ADDRESS _____
 CITY _____ ZONE _____ STATE _____

(Please Print) RE-3

New Devices

RESONATORS FOR TVI

Motorola, Inc., 4545 W. Augusta Blvd., Chicago 51, Ill., has announced production of precision selector cavity resonators available in several degrees of selectivity depending upon application and frequency separation. These units minimize television interference by highly attenuating spurious and harmonic radiation of transmitter antenna systems of base station two-way radio communications equipment. The cavity resonator, a very high "Q" circuit which can be inserted into a line, makes it possible to use two or more transmitters on the same antenna without mutual interference.


Motorola cavities, designed for the 30-48 mc, 72-76 mc, 122-132 mc, and 132-180 mc communication bands, are compensated for optimum performance over wide temperature ranges. Each unit has an input and output impedance of 50-72 ohms at a 250 watt maximum power rating. They are designed for optimum impedance match and a low voltage standing wave ratio.

position, including upside down. The high-gain amplifier, requiring no preliminary warm-up, will pick up a normal speaking voice 100 feet from the microphone. A tape speed of 1 7/8 inches per second with a frequency response to 3,000 cycles allows two full hours of recording time on a single 5-inch reel of standard 1/4-inch wide tape.



SEALING COMPOUNDS

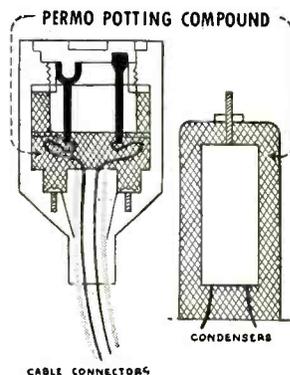H. V. Hardman Co., Inc., 571 Cortlandt St., Belleville, N. J., announces production of a new line, known as




Permo Potting and Sealing Compounds, especially designed for use where high electric insulation and low moisture absorption is required. These compounds are not to be mistaken for ordinary tars as they have a wide temperature tolerance and maintain viscosity at higher temperatures.

8-ELEMENT YAGI

LaPointe Plascomold Corp., Windsor Locks, Conn., has announced the "Long John", a new Vee-D-X single bay antenna for more powerful single channel fringe area reception. This 8-element Yagi (Model LJ) produces 41% more gain than the best 5-element Yagi and is equivalent to any 5-element stacked array. Higher front-to-back ratio eliminates co-channel interference, yet the LJ has the same wide bandwidth as the Vee-D-X JC.

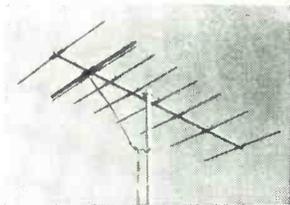Standard pre-assembled construction, lower cost, installation ease, better appearance, and a reinforced boom for extra sturdiness on the low channels are some of the features.




U.H.F. SWEEP GENERATOR

Radio Corp. of America, Harrison, N. J., has developed two new u.h.f. sweep generators of particular interest to research workers and engineers engaged in the development of u.h.f. TV receivers, tuners, filters, antennas, etc. The model WR-40A and WR-41A instruments feature continuous tuning from 470 to 890 mc with operation entirely on fundamentals. No beats or harmonics are used. Sweep width is continuously variable from 0 to 45 mc.

RADIO-ELECTRONICS

TV AUTOTRANSFORMER

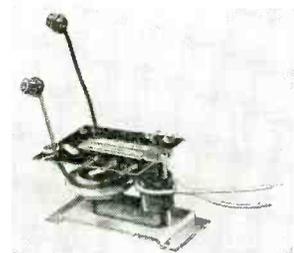RAM Electronics Sales Co., 7 South Buckhout St., Irvington-on-Hudson, New York, has added a new high-efficiency replacement and conversion TV autotransformer to its line of TV parts. The RAM X054 requires less driving power than a true transformer while



providing ample high voltage and sweep for tube sizes up to 21-inch rectangular. It features a high-permeability ferrite core and special precision-pattern windings resulting in excellent regulation and linearity. In sets using selenium-rectifier voltage-doubler circuits with 250 volts plate supply, it produces 13.5 kv with a boost voltage of 430; with standard power supplies, 15 kv with 500 volts boost.

PORTABLE RECORDER

Amplifier Corp. of America, 398 Broadway, New York 13, N. Y., has announced full scale production of the Magnemite, a battery-operated portable tape recorder-playback unit. Weighing only 9 3/4 lbs. and measuring 11 1/2 x 8 1/2 x 5 1/2 inches, the unit will operate for 100 hours at an operating cost of 2 1/2 cents per hour using self-contained dry batteries. A noiseless and vibrationless spring wound motor will run 15 minutes on a single winding; during operation a light indicator flashes a warning two minutes before rewinding is necessary.

When closed, the Magnemite's two-tone leatherette covered case gives no hint of the function of the unit, which may operate in motion and in any

AMPHENOL INLINE ANTENNA

Be Sure
ANTENNA INSTALLATIONS
are *Safe*

Safety is a factor too often overlooked in many TV antenna installations. Bent or broken antennas are a constant menace and antennas that break off or topple over under any undue strain can cause serious damage. Installing an Amphenol Inline Antenna is your guarantee of all-around quality! Not only does the Inline Antenna present the best possible TV picture, but it is safe! The Inline Antenna is constructed of aluminum for light weight and strength, and is engineered to withstand winds up to 70 miles per hour. In addition, it will bear up to one-half inch annular ice loadings without bending or breaking.

LIGHTNING ARRESTOR

Using an Amphenol Lightning Arrestor on the lead-in from your Inline Antenna makes your antenna installation secure in all ways. It provides real protection to your home and TV set from lightning damage and carries off the minor static discharges which interfere with good picture reception. The Amphenol Lightning Arrestor is of the type approved by the National Electric Code and is also approved by the Underwriters' Laboratories.



See your regular Amphenol Distributor now for your copy of this 20-page book containing all the factors which determine Better TV Picture Quality and safe antenna installation.

AMERICAN PHENOLIC CORPORATION
1830 SOUTH 54th AVENUE • CHICAGO 50, ILLINOIS

AMPHENOL


BUY TEST EQUIPMENT ON THIS RADICALLY NEW TIME PAYMENT PLAN

NO INTEREST!! - NO CARRYING CHARGES!!

USE CONVENIENT TIME PAYMENT ORDER BLANK BELOW

Superior's New JUNIOR SUPER-METER

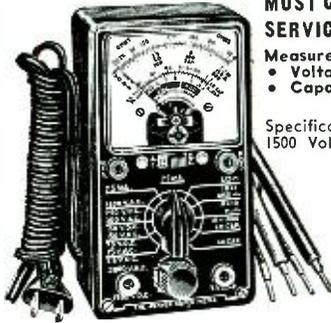MOST COMPLETE AND COMPACT MULTI-SERVICE INSTRUMENT EVER DESIGNED



Measures:
 • Voltage • Current • Resistance
 • Capacity • Reactance • Inductance
 • Decibels

Specifications: D.C. Volts: 0-7.5/75/150/750/-1500 Volts. A.C. Volts: 0-15/150/300/1500/3000 Volts. Resistance: 0-10,000/100,000 ohms. 0-10 Megohms. D.C. Current: 0-7.5/75 Ma. 0-7.5 amps. Capacity: .001 Mfd.—.2 Mfd..1 Mfd.—20 Mfd. Electrolytic Leakage: Reads quality of electrolytics at 150 Volt test potential. Decibels: -10 Db to +18 Db. +10 Db to +38 Db. +38 Db. to +58 Db. Reactance: 15 ohms—25 K ohms. 15 K ohms—2.5 Megohms. Inductance: .5 Henry—50 Henries. 30 Henries—10 K Henries. Plus Good-Bad scale for checking the quality of electrolytic condensers.

Handsome round cornered molded bakelite case 3 1/2" x 5 3/4" x 2 1/4" complete with all test leads and instructions.

\$21.40
NET

Superior's New Model TV-11 TUBE TESTER



Operates on 105-130 Volt 60 Cycles A.C. Hand-rubbed oak cabinet complete with portable cover **\$47.50** NET

* Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary. * Uses no combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket. * Free-moving built-in roll chart provides complete data for all tubes. * Phono jack on front panel for plugging in either phones or external amplifier detects microphonic tubes or noise due to faulty elements and loose external connections.

Superior's New Model CA-12 SIGNAL TRACER



The well known model CA-12 is the only signal tracer in the low price range including both meter and speaker !!!

SPECIFICATIONS: * Comparative Intensity of the signal is read directly on the meter—quality of the signal is heard in the speaker. * Simple to Operate—only one connecting cable—no tuning controls. * Highly Sensitive—uses an improved vacuum-tube voltmeter circuit. * Tube and Resistor Capacity Network are built into the detector probe. * Built-In High Gain Amplifier—Alnico V Speaker.

Completely Portable—weighs 8 pounds—measures 5 1/2" x 6 1/2" x 9".

Model CA-12 comes complete with all leads and operating instructions **\$33.95** NET

Superior's New TV BAR GENERATOR



THROWS AN ACTUAL BAR PATTERN ON ANY TV RECEIVER SCREEN!!

Two Simple Steps

1. Connect Bar Generator to Antenna Post of any TV Receiver.
2. Plug Line Cord into A. C. Outlet and Throw Switch.

RESULT: A stable never-shifting vertical or horizontal pattern projected on the screen of the TV receiver under test.


Power Supply: 105-125 Volt 60 Cycles. Power Consumption: 20 Watts. Channels: 2-5 on panel, 7-13 by harmonics. Horizontal lines: 4 to 12 (Variable). Vertical lines: 12 (Fixed). Vertical sweep output: 60 Cycles. Horizontal sweep output: 15,750 Cycles.

TV Bar Generator comes complete with shielded leads and detailed operating instructions. Only **\$39.95** NET

Superior's New Model 660—AN AC OPERATED SIGNAL GENERATOR

Provides Complete Coverage for A.M.—F.M. and TV Alignment

* Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 240 Megacycles on powerful harmonics. Accuracy and stability assured by use of permeability trimmed Hi-Q coils. * R.F. available or modulated by the internal audio oscillator. * Built in 400 Cycle sine wave audio oscillator used to modulate the R.F. signal also available separately for audio testing of receivers, amplifiers, etc. * Oscillator Circuit: Uses a miniature high frequency type of acorn triode in a Hartley circuit to insure a high degree of stability. By using the same type of triode as a buffer amplifier, complete and positive isolation between the R.F. oscillator and the attenuator is attained. * Attenuator: a 3 step ladder type of attenuator is used. Each step of the attenuator is controlled by a separate attenuator control thus providing intermediate level steps. * Tubes used: 955, as R.F. Oscillator, 955 as Modulated Buffer Amplifier, 6SN7 as Audio Oscillator and Power Rectifier.

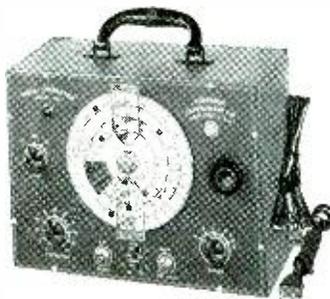

The Model 660 comes complete with coaxial cable test lead and instructions. **\$42.95** NET

NEW TIME PAYMENT PLAN ORDER BLANK

Moss Electronic Distributing Co., Inc.
Dept. B-18, 38 Murray Street, New York 7, N. Y.

Please send me the units checked below. I am enclosing the down payment with order and agree to pay the monthly balance as shown. It is understood there will be no carrying, interest or any other charges, provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

- JUNIOR SUPER METER Total Price \$21.40 \$5.40 down payment. Balance \$4.00 monthly for 4 months.
- MODEL TV-11 Total Price \$47.50 \$11.50 down payment. Balance \$6.00 monthly for 6 months.
- MODEL CA-12 Total Price \$33.95 \$9.95 down payment. Balance \$4.00 monthly for 6 months.
- TELEVISION BAR GENERATOR Total Price \$39.95 \$9.95 down payment. Balance \$5.00 monthly for 6 months.
- MODEL 660 Total Price \$42.95 \$12.95 down payment. Balance \$5.00 monthly for 6 months.
- I enclose \$_____ as down payment.
- Ship C.O.D. for the down payment.

Signature _____

Name _____

Address _____

City _____ Zone _____ State _____

High score every time with "Safe Centers!"



In Basketball there's no better assurance of victory than a lengthy lad jumping center . . . and there is nothing that scares higher in radio, TV and other electronic circuits than SELETRON miniature rectifiers with "Safe Center" plates.

When you specify SELETRON Selenium Rectifiers you eliminate arc-over danger, short circuits and heating at the center contact point. Assembly pressure, or pressure applied in mounting the rectifier cannot affect its performance — a SELETRON feature accomplished by deactivating the area of the plate under the contact washer.

The millions of SELETRON Selenium Rectifiers in satisfactory service as original equipment in the products of leading manufacturers are millions of reasons why you can specify SELETRON and be safe!


Look for Howard W. Sam's Red Book Supplement listing SELETRON replacements . . . and write for Bulletin No. 104-R-1



SELETRON DIVISION
RADIO RECEPTOR COMPANY, INC.
Since 1922 in Radio and Electronics
Factory: 84 North 5th St., Brooklyn 11, N. Y. • Sales Department: 251 West 15th St., New York 11, N. Y.

with amplitude variation of 0.1 db per mc or less throughout the swept range. Maximum output is 0.5 volt across a 50-ohm load. Facilities for matching to 72- or 300-ohm loads are provided.

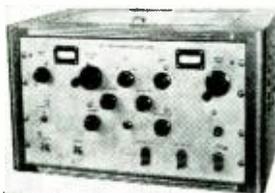The WR-40A is a laboratory-type instrument. It has a built-in crystal calibrator and a variable-frequency marker oscillator. Other features in-




clude attenuator controls for varying amplitudes of the sweep output, response input, marker pips, and calibrating pips; built-in detector for direct monitoring of the sweep-oscillator output, a front-panel blanking control, and a marker injection system which prevents distortion of the response curve.

The WR-41A has the same sweep-generator mechanism as the WR-40A but does not include the calibrator or marker circuits.

5-INCH OSCILLOSCOPE

Triplet Electrical Instrument Co., Bluffton, Ohio, has replaced the model 3440 with their new model 3441, designed for TV, FM, and industrial testing requirements. An illuminated calibration meter makes it possible to view the percentage of positive and negative peak-to-peak volts in addition to reading peak-to-peak voltage directly in 8 ranges from 0 to 1000 volts. The push-pull horizontal amplifier is flat within $\pm 20\%$ from 20 cycles to 150 kc. and its deflection sensitivity is 0.15 r.m.s. volt inch. The push-pull vertical amplifier is usable beyond 4 mc. Its sensitivity is .01 r.m.s. volt inch with switch in 2-mc position; .02 r.m.s. volt inch with switch in 4-mc position. A high-gain amplifier system is available for tracing audio circuits and checking for noisy com-

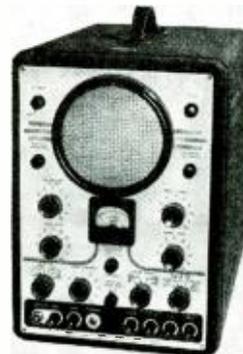ponents. A phone jack on the panel makes a convenient way to associate the visual pattern with the familiar sounds. Furnished in black suede-finished metal case, 15-11/32 x 11-1/32 x 16 inches. Accessories include coaxial cables, probe, and instructions. A crystal signal-tracing probe is available as an extra accessory.



HI-FI SPEAKERS

Oxford Electric Corp., 3911 So. Michigan Ave., Chicago 15, Ill., has announced a number of new high-fidelity loudspeakers. Among them are



LEARN Practical RADIO AT HOME



COMPLETE
ONLY . . .

\$19⁹⁵

BUILD 15 RADIOS

ABSOLUTELY NO PREVIOUS TRAINING NEEDED
EXCELLENT BACKGROUND FOR TELEVISION

10-DAY MONEY-BACK GUARANTEE

WHAT THE 1952 PROGRESSIVE RADIO "EDU-KIT" OFFERS YOU:

This is a practical home radio course. You learn theory, construction, operation, trouble shooting, code. You build RECEIVERS, TRANSMITTERS, AMPLIFIERS, CODE OSCILLATOR, SIGNAL TRACER.

You start with a simple radio circuit, and gradually advance to more complex circuits. No previous background is required. No instructor is needed. All parts and instructions are included and every single step is clearly explained.

All parts are guaranteed, individually packaged, identified, and explained. There is nothing extra to buy. You receive all parts, tools and instructions at once. You keep everything; there is absolutely nothing you return to us.

You can easily pay for the kit in a short time by repairing radios. Use the tester and signal tracer for servicing. The signal tracer alone is worth more than the price of the entire kit.

USED BY RADIO SCHOOLS AND GOVERNMENT AGENCIES!

The Progressive Radio "Edu-Kit" includes tubes, paper condensers, mica condensers, electrolytic condensers, variable condensers, selenium rectifiers, chassis, hardware, tie strips, tube sockets, solder, wire, soldering iron, tubing, coils, instruction book, radio trouble-shooting guide, radio tester, television trouble-shooting manual, etc.; in brief, everything you need in a practical radio course.

Order your "Edu-Kit" today, or send for further information.
Postage prepaid on Cash orders—C.O.D. orders accepted in U.S.A.

PROGRESSIVE ELECTRONICS CO.

497 UNION AVE. DEPT. RE-57 BROOKLYN, NEW YORK

FREE RADIO TESTER & SOLDERING IRON

GET A WELL-PAYING JOB



GO INTO A PROFITABLE BUSINESS
AND PLAN FOR A FUTURE



RADIO-ELECTRONICS

IMPORTANT NOTICE TO READERS!

Today's ever-shifting defense and civilian demands are bringing rapid-fire changes in radio, television and audio. A subscription to RADIO-ELECTRONICS now, is your assurance of getting important topical information on servicing, construction, theory and new developments every month, at the lowest cost, no matter what the future brings in the way of prices, paper shortages or defense demands.

SUBSCRIBE TODAY

3 Years \$8.00 2 Years \$6.00
1 Year \$3.50



more TV set outlets
per dollar!

with easy-to-install

Blonder-Tongue

**ALL-CHANNEL
MASTER
ANTENNA
SYSTEMS**



Distribution Amplifier
8 TV Set Outlets
Model #DAB-1-M List Price \$87.50



Distribution Amplifier
2 TV Set Outlets
Model #DA2-1-M List Price \$39.50



Commercial Antensifier (30 Times
Gain) Use As Pre-Amplifier, Line
Amplifier or de-luxe Booster
Model #CA-1-M List Price \$77.50

More Gain Per Dollar!

8-T Home Antensifier Model HA-2-M
Finest All-Channel TV Booster. Fully
Automatic, 16 Times Gain. In Metal
Cabinet List Price \$57.50



Literature on Request write Dept. D3

Blonder-Tongue Labs., Inc. Mt. Vernon, N. Y.

the 8-inch HF8JB, 10-inch HF10JB, and 12-inch HF12JB. These units handle 10 watts maximum, and have 6.8-ounce magnets and 1-inch voice coils. The HF12LN, a 12-inch model, has a 14-ounce magnet, 1 1/2-inch voice coil, and handles 25 watts.

Also included in the line is the C012JB coaxial speaker which has a frequency range of 65 to 15,000 cycles with crossover at 4,000 cycles. The combination handles 10-12 watts. The 12-inch woofer has a 6.8-ounce Alnico V magnet and the 3-inch tweeter has a 1.47-ounce Alnico V magnet.

All the speakers have 8-ohm input impedances and are finished with hardemtone lacquer.

TV ANTENNA TOWERS

Channel Master Corp., Ellenville, N.Y., is distributing a new line of steel towers. Available in 10-foot sections, they have a built-in ladder on one side with no obstructions to interfere with easy climbing. The other two sides feature truss construction for added strength. Tower legs are made of steel tubing and are spaced, 8 1/2 inches apart, for greater rigidity and twist-resistance. All tower sections are com-


pletely interchangeable, because only one type of section is used. No different top, middle, or bottom sections are required, and base mount and mast brackets fit all sections.

All three tower legs are swaged on one end for easy assembling. Additional sections are merely slipped into each preceding section and fastened. Masts and rotators are mounted internally for greater support and protection.

Also available is a universal base mount which is adaptable for all types of installations—peaked, sloping, and flat surfaces. Special dual-purpose mounting brackets, for use both as mast supports and rotator bearings, are also available with the towers.


ROTATOR ADAPTOR KIT

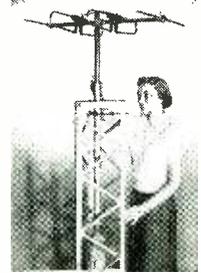Alproco, Inc., Kempton, Ind., and Mineral Wells, Texas, is producing a new antenna rotator adaptor kit de-



signed to make it possible to install any commercial antenna rotator on its antenna towers. The RK-1W kit consists of a pre-drilled adaptor mounting plate which takes any well-known rotator, a 1-foot mast pole to connect the rotator to the antenna, a 24-inch-long bearing for the pole, and a 3-piece assembly which holds the mast bearing securely to the tower. This protects the rotator by permitting the tower to absorb all wind thrust.

—end—

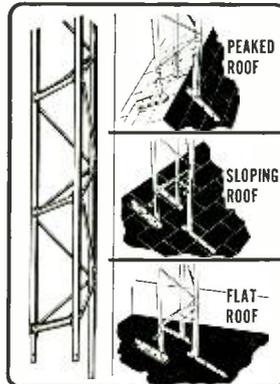

SAVE \$ ON \$UN \$URPLUS AND \$TANDARD \$PECIALS!

LOW FREQ. XTALS-FT 241A

For SSB, lattice filter, etc. 1/2" spc. 54th or 72nd harmonic channels listed by fundamentals. Fractions omitted.

372 404 436 506	400 462	5910	2030 2435
374 405 437 507	440 463	6370	2045 2442
375 406 438 508	441 464	6450	2105 2532
377 407 481 509	442 466	6470	2125 2545
379 408 483 511	444 468	6497	2145 2557
380 409 484 514	446 470	6522	2155 3202
381 411 485 515	447 472	6547	2220 3215
383 412 487 516	448 474	6610	2258 3237
384 413 488 518	450 475	7350	2280 3250
385 414 490 519	451 476	7480	2282 3322
386 415 491 520	452 477	7590	2290 3510
387 416 492 522	457 479	7810	2300 3520
388 418 493 525	461 480	7930	2305 3550
390 419 494 526			2320 3580
391 420 495 530	99c ea.		2360 3945
392 422 496 531	10 for	\$1.29	2390 3955
393 423 497 533		each	2415 3995
394 424 498 537	\$9.00		
395 425 503 538			
396 426 504			
397 427			
398 429	49c ea.		
401 431	10 for		
402 433			
403 435	\$4.50		

SPECIAL
200 Kc xtals
without holders
99c each
3 for \$2.00

SCR 522

Xtals
1/4" ins
1/2" spc.

5910	2030 2435
6370	2045 2442
6450	2105 2532
6470	2125 2545
6497	2145 2557
6522	2155 3202
6547	2220 3215
6610	2258 3237
7350	2280 3250
7480	2282 3322
7590	2290 3510
7810	2300 3520
7930	2305 3550
	2320 3580
	2360 3945
	2390 3955
	2415 3995

**SPECIAL PURCHASE
FM RADIO CHASSIS**



88-108 MC Complete with 6 tubes. Built-in Antenna and Speaker. Product of Famous Radio & TV Manufacturer whose name we promised not to mention.

TUBE LINE-UP Regularly \$29.95
1-12BA7 1-12S8
2-12BA6 1-35W4
1-35B5
Brand New
May also be used as an FM Tuner by picking signal off detector.
\$16.95

**SPECIAL PURCHASE
RECORD CHANGER
GENERAL INSTRUMENTS
3-SPEED AUTOMATIC**



Reg. \$34.95
Brand New
\$19.97

With all purpose cartridge. Plays 33 1/3-45 and 78 RPM records automatically.

VARIABLE CONDENSERS

From SCR-522
2 GANG - 25
MMF
per section
\$1.29



3 GANG - 25
MMF
per section
\$1.59



BRAND NEW with CONCENTRIC AIR TRIMMERS

BC-306A ANTENNA TUNING UNIT


Contains - antenna variometer heavy duty 3 pole 5 pos. ceramic switch, velvet vernier dial. Standoff insulators housed in heavy aluminum case
\$2.95



BC-221T FREQ. METERS BRAND NEW

complete with XTAL—spare tubes. manual and calibration book with cases carrying
\$125.00

RL-42B ANTENNA REEL

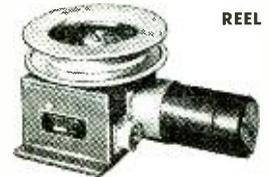


24 V D C — can work on A C convert to antenna rotator. Only.....
\$3.95

1-82A RADIO COMPASS INDICATOR



Compass indicator with built-in syn only—
\$3.95

VARIABLE CONDENSER

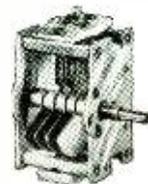

26 MMF—.10 spacing only
99c

CQ TO ALL HAMS DE W3PPQ

Handle here is "Pick" . . . call or write me for anything you need in ham gear or parts—Will be happy to expedite your order with best quality merchandise. 73's

HAM XTALS-FT 243 HOLDERS—1/2" pin spc.

4190 6773 7840	1015 5800 6306 6573 7506 7673
5030 6873 7873	1129 5806 6325 6575 7540 7706
5485 6906 7906	2045 5825 6340 6600 7573 8240
6040 6973 7940	3735 5840 6373 6606 7606 8340
6073 7740 7973	5305 5850 6406 6625 7840 8400
6106 7773 8273	5677 5873 6440 6640 7650
6125 7806 8306	5706 5875 6450 6673
6140	5725 5906 6473 6706
6173	5740 5940 6475 6740
6175	5760 5973 6506 7440
8206	5773 6273 6540 7473

99c ea. 10 for \$9.00

Add 20c for each 10 xtals or less for postage and handling.
TERMS: All items F.O.B., Washington, D.C. All orders \$30.00 or less, cash with order. Above \$30.00, 25 per cent with order, balance C. O. D. Foreign orders cash with orders, plus exchange rate.


SUN RADIO
OF WASHINGTON, D. C.
938 F STREET, N. W. WASH 4. D. C.

TERMS All items F.O.B., Washington, D. C. All orders \$30.00 or less, cash with order. Above \$30.00, 25 per cent with order, balance C.O.D. Foreign orders cash with orders, plus exchange rate.

ANCHOR BOOSTERS

bring the "fringe"

the BEST in TV reception

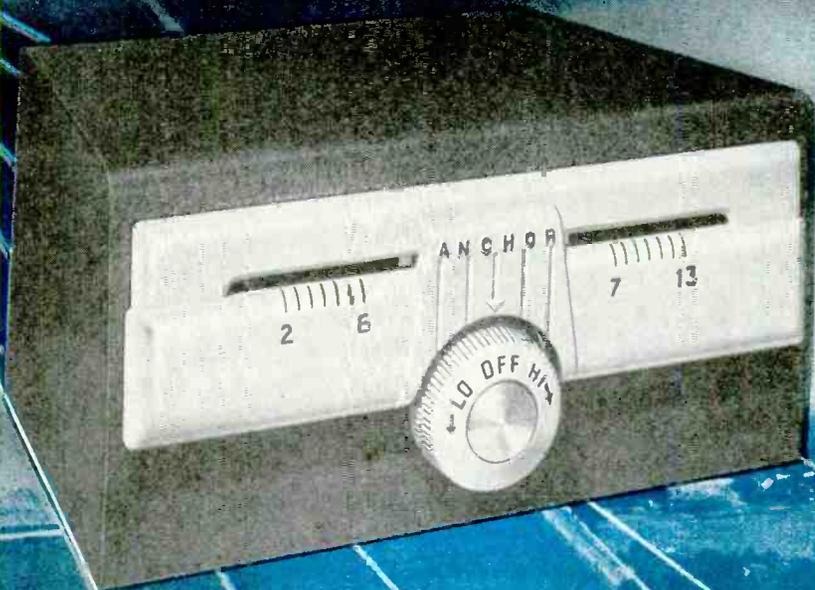

Ask your Distributor about Anchor's
Easel Presentation on successful fringe installations

ANCHOR RADIO CORP.

2215 South St. Louis Avenue, Chicago 23, Illinois

ANCHOR ENGINEERING ALWAYS A YEAR AHEAD



TRAIN AT HOME FOR



DO BETTER WORK..MAKE MORE MONEY with modern service methods!

A complete,
1-volume service
training course in
time-saving
professional
methods . . .

only
\$6.75

Here's the book you've been waiting for . . . *the new Ghirardi guide to servicing by professional methods!*

In a way that could only be matched by having one of the world's greatest instructors at your side, it explains every phase of modern servicing procedure. Fully modern, profusely illustrated, RADIO AND TV TROUBLESHOOTING AND REPAIR covers all TV, FM, AM, Phonograph and recorder servicing procedures. For the beginner, it is a complete training course. For the busy serviceman, it is a quick way to brush up on specific types of work or to find fast answers to puzzling service problems.

THE GREATEST HOW-TO-DO-IT SERVICE BOOK EVER WRITTEN!

First you get a full analysis of components and why they fail. Next you learn the most modern servicing methods—from static tests to dynamic tests using signal tracing and injection techniques. You'll learn how to set up a basic servicing procedure and to interpret performance data. Four big chapters show how to realign TV, FM, and AM receivers with a minimum of tools and equipment. Now that components are becoming scarce, you'll appreciate the chapters on how to repair as well as to replace defective

transformers, chokes, loudspeakers, coils, controls, resistors, etc.

You learn how a glance at a TV receiver may quickly tell you what is wrong; how to understand 3-way portable radio filament circuits; what to do about intermittent troubles; how to check ac/dc and transformerless power supply heaters professionally; how to handle fading and propagation troubles; . . . and dozens of others. In short, no really practical service procedure has been omitted from this great book—and all are handled so that you can't fail to understand them!

The
New
Ghirardi

RADIO & TELEVISION RECEIVER Troubleshooting and Repair

820 pages, 417 clear illustrations, price only \$6.75



Money-saving Combination Offer

Have the service data you need at your fingertips *when you need it!* Make your service library complete! Get both the new Ghirardi Radio & Television Receiver TROUBLESHOOTING AND REPAIR (\$6.75) and the Ghirardi Radio & Television Receiver CIRCUITRY AND OPERATION (\$6.00) at the special price of only \$12 for the two books. Check **SPECIAL COMBINATION OFFER** in coupon for 10-day examination privilege. You don't risk a cent.

PASS SERVICE LICENSE EXAMINATIONS!

Many cities now require servicemen to pass rigid license examinations. Let these two great new Ghirardi books help prepare you today to pass any such examinations with flying colors!

LEARN BASIC RADIO AND TV CIRCUITS FROM A to Z . . . and watch service troubles disappear


Actually, there are only a few really basic circuits in radio and TV receivers. Learn these from A to Z and even the most complicated of the countless modern circuit variations won't bother you. You'll work faster, better—and a lot more profitably!

**HANDLE TOUGH JOBS IN
½ THE USUAL TIME!**

Backed with what you can learn from A. A. Ghirardi's great new book, RADIO AND TELEVISION RECEIVER CIRCUITRY AND OPERATION, you'll find that nine out of ten difficult service jobs are tremendously simplified.

Starting with a clear explanation of AM and FM processes and char-

acteristics, it progresses to a complete understanding of ALL basic circuits, shows how they operate, teaches you to recognize them quickly. Guesswork is eliminated. Laborious testing is greatly minimized. By making it easy for you to understand each circuit and its relation to other circuits, Mr. Ghirardi helps you go right to the seat of the trouble with far less time and effort. You'll know what to look for—and you'll have what it takes to enable you to repair troubles faster and more efficiently.

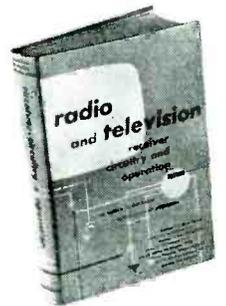

Ghirardi's New RADIO AND TELEVISION RECEIVER Circuitry and Operation

669 pages, 417 illustrations, price \$6.00


COMPLETE BASIC TRAINING for BEGINNERS

More people now in Radio-TV got their basic training from this book than any other book or course of its type!

"The most complete training course in radio fundamentals ever offered"—that's what the experts say about Ghirardi's world-famous RADIO PHYSICS COURSE. More widely used by Signal Corps, Navy, etc. in World War II, than any other basic radio training text. Everything is explained so clearly that you can understand every word without previous radio training of any kind.

Ghirardi's Radio Physics Course starts with Basic Electricity. Then it takes you step by step through the entire field of Radio-Electronics from simple circuits showing the basic functions of resistors, condensers, coils, transformers, etc., to the final

applications of these circuits in home, auto, and aircraft radios, public address systems, sound motion pictures, etc. Subjects covered include Sound, Speech, Music, Electron Theory, Electric Circuits, Current, Resistance, Capacitance, Inductance, Transformers, Filters, Radio Waves, Vacuum Tubes, Radio Circuits, Loudspeakers and dozens of others. You get exactly the training you need—at a price you can afford to pay. If broken into "course" form and sent as monthly lessons, you'd regard it as a bargain at \$50.00 or more. Instead you buy it for only \$5.00—and you progress as fast as spare reading time permits.

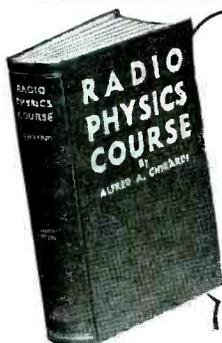

36 COURSES IN ONE!

Ghirardi's world famous
**RADIO PHYSICS
COURSE**

972 pages, 508 illus.

856 self-test review
questions.

Price only \$5

Let these great books give **YOUR** earning power

RADIO-ELECTRONICS

HIGHER PAY in 1952!

Read any of these 12 great money-making books for 10 days **AT OUR RISK**. You be the judge!

IT PAYS TO KNOW HOW TO USE THE OSCILLOSCOPE



Modern Oscilloscopes and Their Uses

by Jacob H. Ruiter, Jr.

326 pages, 370 illustrations, dozens of pattern photos. \$6.00

Don't let the oscilloscope "stump" you!
Learn to use it fully for top notch service efficiency

Now you'll really know how to use the greatest, most versatile service instrument of all—the oscilloscope! MODERN OSCILLOSCOPES AND THEIR USES gives you expert knowledge of scopes, helps you work faster, more accurately and more profitably on all sorts of service and laboratory jobs. No involved mathematics or theory! First, the author explains the construction and operation of cathode ray tubes and basic oscilloscope circuits. Then he gets right down to earth in telling exactly how to use a scope for AM, FM and TV service work—from locating receiver troubles to aligning and adjusting the most complicated circuits. Dozens of actual pattern photos plus an unusually descriptive text teach you exactly how to analyze and interpret various patterns.

MAKES AUTO RADIO REPAIR twice as easy!

SERVICING THE MODERN CAR RADIO

by A. L. Hurlbut

2nd Edition, 702 pages, 222 illus., 8 1/2 x 11. Price \$7.50



Used either as a text book or bench manual, Hurlbut's famous SERVICING THE MODERN CAR RADIO is a complete, easily understood guide to fast, accurate installation and servicing of all types of auto radios. Covering every type of auto radio from the mid-1930's, this compact book gives you complete installation, troubleshooting and repair procedures plus tips on how to set up shop and get business. Subjects include differences between car and ordinary radios; antennas; antenna input circuits; power supplies; circuit features; automotive electrical systems; installations; loudspeakers; interference; vibrator maintenance; alignment; push-button tuning and many others. Over 500 actual circuit diagrams and mounting drawings for car radios alone can save you many times the cost of the book.

Includes OVER 500 CAR RADIO CIRCUIT DIAGRAMS and mounting drawings

CUT SERVICE TIME IN 1/2 on hundreds of jobs

RADIO TROUBLESHOOTER'S HANDBOOK

by A. A. Ghirardi

744 Manual-size pages, Over 4800 Radio Models listed, Price \$5.00



This big book makes it easy to make prompt repairs on over 4800 radio models WITHOUT expensive test equipment, or long hours of study. Ghirardi's RADIO TROUBLESHOOTER'S HANDBOOK lists Home and Auto receivers and Automatic Record Changers of 202 manufacturers, together with common trouble-symptoms and exactly where to locate and how to repair the defects. This is not a "study" book. Simply look up the make, model, and trouble symptom of the set you want to repair and go to work. Ideal for older sets where data is so often lacking. Hundreds of additional pages contain valuable data on tubes, parts and equipment, plus graphs, diagrams and money-making service hints.

Get off the beaten path! Start training now for the more interesting Radio-TV jobs that most students overlook! Let the following four books teach you at home. Each is complete, fully authentic. Each is endorsed by leading experts and educators in its field.

BE A SOUND EFFECTS EXPERT!

... The noise of a creaky door—wind—rain—wagon wheels—and dozens of other sound effects play big parts in almost every radio and TV program. This unique book, RADIO AND TV SOUND EFFECTS tells the whole story of sound effects—even down to showing you how to make creakers, "boing" boxes, glass crashers, splashes, rain machines, thunder machines and much other special equipment for this work. Written by Robert B. Turnbull, of the Don Lee-Mutual Broadcasting System, it is a complete guide to this fascinating phase of Radio-TV work. 334 pages—profusely illustrated. Price \$4.50. (Order RADIO AND TV SOUND EFFECTS in coupon.)

LEARN RADIO-TV ANNOUNCING

Let the big, manual-size RADIO ANNOUNCERS' HANDBOOK by Ben G. Henneke help you train for this interesting, well-paid work! Subjects include The Announcers Qualifications; The Announcers Skills; The Announcers Work; Audition Tests; Vocabulary Exercises—and over 300 pages of actual radio copy, commercials; newscasts and script shows for test and practice. More widely used than any other book of its kind. Price \$4.25. (Use coupon to read RADIO ANNOUNCERS' HANDBOOK for 10 days at OUR RISK.)

FREQUENCY MODULATION

... Ever increasing uses for FM in mobile radio, television sound, and home receivers open new fields for profitable service work. Written by a well-known expert, this book simplifies a clear understanding of FM fundamentals, equipment and servicing procedures. You'll learn basic FM theory, transmitters, circuits and their peculiarities. R-F, I-F, limiters, discriminators, ratio-detectors, squelch, AFC circuits, and tuning indicators are fully explained. Equally important is a thorough description of antenna construction, troubleshooting methods, alignment, repair and other servicing procedures. 448 pages, over 300 illustrations. Price \$5.00.


LEARN ELECTRIC MOTOR REPAIR

... There's big money in installing, maintaining and rewinding electric motors—and here is a big book to help you train for this fast-growing field! Every type of motor work is explained both in text and also by more than 900 helpful drawings, photos and diagrams. ELECTRIC MOTOR REPAIR book includes complete details of troubleshooting, repair and rewinding of all a-c and d-c motor types in common use plus motor control systems. Quick reference guides show how to handle specific jobs. Practice from this book for 10 days at our risk. Order ELECTRIC MOTOR REPAIR in coupon. Price \$6.00.

Get this COMPLETE GUIDE TO TELEVISION SERVICE

PRACTICAL TELEVISION SERVICING

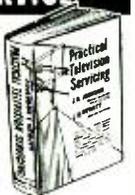by J. R. Johnson & J. H. Newitt
334 pages, 253 illustrations, \$4.00



Here—at only a fraction of the price you might expect to pay—is complete, intensely practical training in every phase of television receiver service procedure. You learn how TV differs from radio; how receivers operate; how to locate troubles quickly with a minimum of testing and how to make repairs fast and profitably.

SERVICE CASE HISTORIES

Dozens of actual service case histories help simplify your training, make even the most puzzling jobs far easier to handle. Clear illustrations and pattern photos explain details step by step. Other subjects include component replacement data, wiring details, tips on testing, and a wealth of data on fringe area reception, improving picture linearity and many other vital TV service subjects.

All about TV Components-Construction-Operation-Trouble-shooting-Servicing- In language YOU can understand.

THERE'S FUN AND PROFIT in Magnetic Recording



MAGNETIC RECORDING

by S. J. Begun

242 pages, 146 illustrations
6 x 9, Price \$5.00

LEARN NEW USES FOR MAGNETIC RECORDING IN:
High-Fidelity Sound
Broadcasting
Industrial Measurements
Sound Pictures
Home Entertainment

Get started on the "ground floor" of this fast-growing business that will eventually replace the modern phonograph. MAGNETIC RECORDING brings you specific details on every phase of wire and tape recording from its history, basic acoustic and magnetic theories, through the components, circuits, and equipment in current use. Then, the author describes the many applications of magnetic recording and its use for home entertainment, motion pictures, broadcasting, amateur radio, secret communications (speech scrambling), and the rapidly expanding field of industrial sound and noise measurements. Standard equipment is fully discussed along with the instruments needed to evaluate recording performance.

Mail Order—10 DAY EXAMINATION OFFER

Dept. RE-32, RINEHART BOOKS, Inc., Technical Division
232 Madison Ave., New York 16, N. Y.

Send the books checked below for 10-day FREE examination. In 10 days, I will either remit the price indicated or return books postpaid in good condition and owe you nothing

- Ghirardi's Radio & TV Receiver TROUBLESHOOTING & REPAIR, \$6.75
- Ghirardi's RADIO TROUBLESHOOTER'S HANDBOOK, \$5.00
- Ghirardi's Radio & TV Receiver CIRCUITRY & OPERATION, \$6.00
- PRACTICAL TELEVISION SERVICING, \$4.00
- MAGNETIC RECORDING, \$5.00
- COMBINATION OFFER: Both of above new Ghirardi books, \$12.00 (Outside U.S. \$13.00)
- FREQUENCY MODULATION, \$5.00
- Ghirardi's RADIO PHYSICS COURSE, \$5.00
- RADIO & TV SOUND EFFECTS, \$4.50
- ANNOUNCERS' HANDBOOK, \$4.25
- Ghirardi's MODERN OSCILLOSCOPES AND THEIR USES, \$6.00
- ELECTRIC MOTOR REPAIR, \$6.00
- SERVICING THE MODERN CAR RADIO, \$7.50

TO ORDER BOOKS OUTSIDE U.S.A.—Add 50c to price of each book for handling through customs, etc. Cash only. Same 10-day return privilege with money refunded.

Name

Address

City, Zone, State

Employers' name & address

a big boost!

MARCH, 1952

more than

2,000,000

set owners use

jfd panorama

indoor tv antennas

triple-chrome plated dipoles

absolutely tip-proof

- MODEL TA135 DELUXE 6.95 list
- MODEL TA136 STANDARD COMPANION 5.95 list
- MODEL TA137 ECONOMY COMPANION 5.50 list
- COMPLETE WITH TWIN LEAD



JFD MFG. CO., BENSONHURST 6-9200 • BROOKLYN 4, N. Y.

SOUNDTRONICS SPECIALS

Hi-Frequency Components

TOP BRAND 557 CERAMIC TRIMMERS 15-65 mmfd. or 1.5 to 7 mmfd. 15¢ ea.

CENT. STYLE 823 AN TRIMMERS 20-125 mmfd. 34¢

TUBULAR TYPE TRIMMERS

.5-5 mmfd. 9¢

TOP BRAND BUTTON MICA

Type CB 500 mmfd. 9¢ type FA 2000 mmfd 14¢

MUTER CERAMIC CONDENSERS

15, 22, 33, 56, 75, 82, 180, 220 mmfd. 5¢ each \$4.50 per M.

NEW STANDARD BRAND RESISTORS

1/2 W 2.5¢ 1 W 3.9¢ 2 W 4.9¢

No Min. Order Req. Quantity Discounts

TOP BRAND

1 mfd 1000 W. V. D. C. 6¢ ea. 5 for 25¢

HAIR FELT FOR SOUND WORK

12 x 24" 12¢ ea.

SPECIAL ASSORTMENTS

50 new pop. type 1/2, 1 & 2W coded resistors
 50 small pop. type ceramic conds. All voltages and cap. 50 postage stamp mica conds. **Your Choice \$1.49 ea.**

ARC-5 RECEIVER

IF strip—6.9 meg. IF. Contains the following circuits: mixer, 1st IF amp, 2nd IF amp, det., AVC, squelch neut, 1st AF & Squelch amp, 2nd A.F. complete wired IF strip, less tubes & output trans. 2.49

Terms—25% w/order, balance C.O.D.

SOUNDTRONICS LABS.

632 Arch St., Phila. 6, Pa. MA 7-2775

When writing advertisers please mention RADIO-ELECTRONICS

New Design

TUBES OF THE MONTH

The leading tube manufacturers have produced a bumper crop of new tube types during the last month. These types include cathode-ray tubes for TV, radar, and oscilloscopes; receiving and transmitting tubes, as well as types for industrial and special-purpose applications.

The Rauland Corporation announces the 27QP4, a new 27-inch electrostatically focused and magnetically deflected metal rectangular picture tube. Because it has a 90° deflection angle the tube has a shorter over-all length than a standard 20-inch tube. The picture area is about 390 square inches with a gray filter face plate treated to minimize surface reflections. The tube uses a tilted offset electrostatic gun with an indicator-type ion trap which requires a single-field magnet. The gun design provides for improved detail in the corners as well as in the center of the screen. The 27QP4 can be used as a zero-voltage




Rauland 27QP4 has a 90-degree deflection angle and can be used with zero or low-voltage electrostatic focusing.


focus tube or can be focused for maximum sharpness with a low voltage taken from the set's power supply.

RCA is producing two new picture tubes—the 17HP4 and 7TP4.

The 17HP4 is a 17-inch glass rectangular picture tube using a Filter-glass faceplate; low-voltage electrostatic focus, and magnetic deflection (65° horizontal). A single-field ion-trap magnet is required. An external conductive bulb coating forms a supplementary filter capacitor. The focusing electrode (grid No. 4) has its own base-pin terminal allowing optimum setting with a potentiometer from the boost voltage to ground. Focusing potential varies from 0 to 350 volts with 14 kv on the ultor. The screen size is 14 1/4 by 11 1/16 inches with slightly curved sides

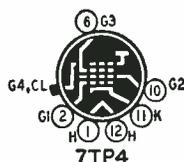

TRIO the TROUBLE PROOF TV ROTATOR

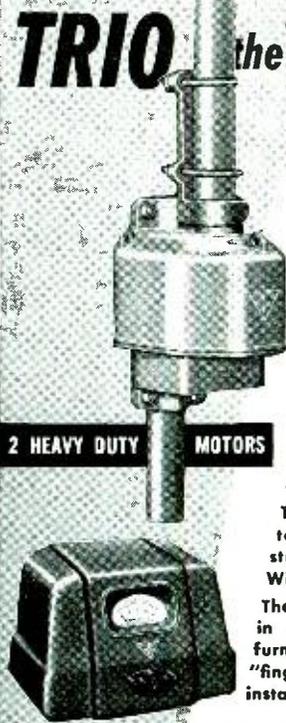

For years of dependable, unflinching service—in good weather and bad—you can't beat the new TRIO Model TR-2M TV ROTATOR and DIRECTION INDICATOR.

Sturdy and completely weatherproof, the TRIO ROTATOR will support the heaviest TV arrays—even in 80 MPH winds! Its sound design and construction has been proven by three years of extensive field testing under every extreme of weather. The TRIO ROTATOR will not freeze up!

Two 24 volt motors are used—one for each direction of rotation. Thus, each motor operates just 50% of the time —cannot burn out! Positive electrical stops at both ends of 360° turn eliminates lead damage.

The TRIO ROTATOR is precision built to extremely close tolerances. Housing is die-cast aluminum for greater strength, lighter weight and perfect alignment of parts. Will fit any mast, 1" to 2" diameter.

The smartly styled TRIO DIRECTION INDICATOR is housed in a sturdy plastic cabinet that harmonizes with any furniture style. Easy operation is assured by the new "finger-tip" control and the easy-to-read dial that clearly, instantly indicates exact antenna position.

See the new TRIO ROTATOR at your jobber today! It's tops for TV—ideal for ham arrays too!



Trio MANUFACTURING COMPANY
GRIGGSVILLE, ILLINOIS

2 new exclusive important advancements.....

GET THEM NOW
ON THE

National **V**ideo **C**orp.

TELEVISION PICTURE TUBES

Demand the
N.V.C. trade mark
on every picture tube.

1

**A MAGNETICALLY
FOCUSED TUBE WHICH
ELIMINATES A COSTLY
FOCUSING COIL**

2

**A BETTER GLARE-PROOF
FACE WHICH ELIMINATES
PRACTICALLY ALL DISTURBING
REFLECTED LIGHTS**

Three plants with over 17 acres of co-
ordinated machinery and personnel.



**THESE TWO ADVANCEMENTS YOURS—
BECAUSE OF N.V.C.'S INDEPENDENT
UNHAMPERED AND FORWARD THINK-
ING ENGINEERING.** Through every step of
manufacturing—perfection—that's why the N.V.C.
picture-tube delivers the better performance. Designed
for conversion and replacement in every standard
make television set and engineered to give even a
clearer, better and more lasting picture. Producing the
world's finest television picture and receiving tubes.

Write for name of Representative nearest you
3019 West 47th Street, Chicago, Ill.

National Video Corporation

3019 W. 47th St.
Chicago

Grays Lake
Illinois

901 W. Huron St.
Chicago

Perfection TV Components

*Now-
Individually
Packaged!*



More Popular Than Ever!

The new Perfection **Kine-Center** for finger-tip picture centering in electrostatic tubes — the **BeamaJuster** for 3-second centering of pictures in focus-coil tubes — the **B. O. Eliminator** for removing black lines caused by Barkhausen Oscillation—and easily installed Perfection **Ion Traps**—all are now available in handy individual cartons at no extra cost.

Order Today from Your Supplier!

PERFECTION ELECTRIC COMPANY
2635 South Wabash Avenue, Chicago 16, Illinois
MAKERS OF PERFECTION SPEAKERS AND TELEVISION COMPONENTS



and rounded corners. The over-all length is approximately 19¼ inches. Maximum ultor (collector) voltage is 16,000, maximum focusing-electrode voltage is 500, maximum accelerator anode (grid No. 2) voltage is 500.

The 7TP4 is a 7-inch round tube intended for monitor service in TV broadcast systems. It produces a 5¾ x 4



The RCA electrostatically focused 17HP4.

inch picture on a metal-backed screen which improves brightness and definition and eliminates the need for a beam-bender. It employs high-voltage electrostatic focusing and 50-degree electromagnetic deflection. Maximum ratings are 12 kv for the ultor, 2 kv on grid 3, and 410 volts on grid 2. Grid 1 voltage for visual extinction of un-deflected focused spot is -22 to -52 volts.

The 17RP4/17HP4 and 17VP4 are G-E's new low-voltage electrostatic focused glass rectangular picture tubes. They have cylindrical face plates. The 17RP4/17HP4 is a single type designation used for a tube which can be used as a direct replacement for either the 17RP4 or 17HP4. The manufacturer recommends operating the focusing electrode at zero voltage with respect to the cathode. Slightly sharper focusing may be obtained by applying a potential be-

RADIO ENGINEERING DEGREE IN 27 MONTHS

Intensive, specialized course including strong basis in mathematics and electrical engineering, advanced radio theory and design (inc. TV and Electronics). Modern lab. Low tuition. Self-help opportunities. Also 27-month courses in Aeronautical, Chemical, Civil, Electrical, and Mechanical Engineering. Approved for G.I.'s. Enter June, Sept., Dec., March. Catalogue.

INDIANA TECHNICAL COLLEGE

154 E. Washington Blvd., Fort Wayne 2, Indiana

REDI-VOLT MODEL 60 PLUG-IN D.C. POWER SUPPLY

Furnishes 60 ma. filtered D.C. at 140 V. with 115 V. A.C. input.


A thousand uses, makes building neat equipment easier. Use like a tube, plug into socket on radio, amplifier, or other chassis.

Price \$2.95 Satisfaction guaranteed.


Post paid U.S.A.
Z-LAB CO. Box 48, Grand Rapids, Mich.

Largest Selling Booster

AT ANY PRICE !

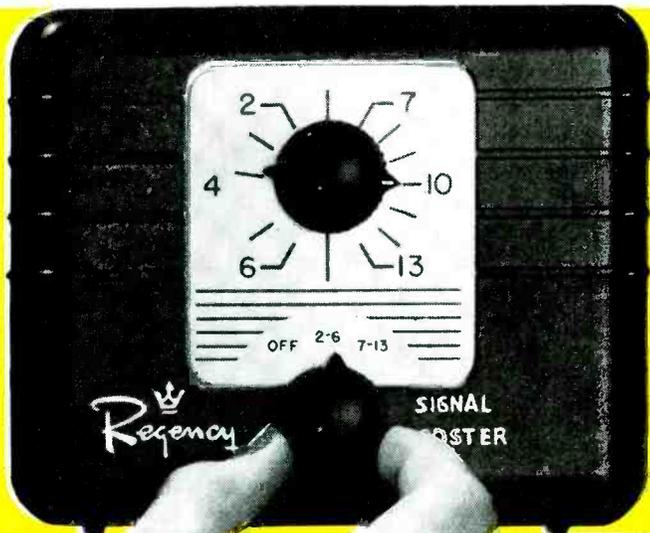

Regency

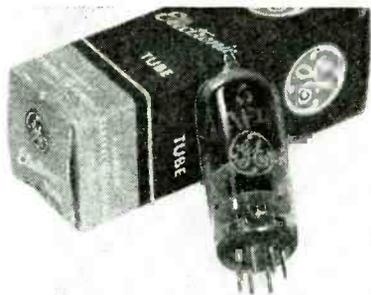

G-E 6AF4, intended for oscillator duty in u.h.f. TV sets, the tube has dual pins for grid and plate connections.

tween -50 and +300 volts to the focusing electrode. The 17VP4 is mechanically and physically equivalent to the 17LP4.

U.H.F. oscillator

The new General Electric 6AF4 is a 7-pin miniature type triode intended for local oscillator use in ultra-high-frequency reception from 470 to 890 mc. Operating data: plate voltage, 150; plate current, 28 ma; input, 2.5 watts; dissipation, 2.25 watts; heater, 6.3 volts at 0.225 amperes.

Oscilloscope and radar tubes

The 7MP7, 7MP14, and 16ADP7 are new RCA oscillograph tubes employing magnetic focus and deflection and are designed for radar and similar applications where a pulse-modulated signal on grid 1 causes high beam currents. Their gun structure includes a limiting aperture which produces a sharper spot at high beam currents. The 7MP7 and 7MP14 are identical except for the characteristics of their phosphors. The P7 and P14 phosphors are long- and medium-long-persistence types, respectively. Both may be used with Wratten No. 15 (G) yellow filters to suppress the blue fluorescence while observing slow traces or with Wratten 47A (C5) blue filters to suppress the yellow phosphorescence when observing fast traces. They have 6.3-volt, 0.6-amp heaters.

The 7-inch tubes have round glass envelopes 7¹/₁₆ inches in diameter and are 13¹/₄ inches long. Typical operating conditions are 4-7 kv on the ultor, 250 volts on grid 2, and bias on grid 1 varying from -27 to -63 volts. The 16ADP7 has a metal shell 16 inches in diameter. Its overall length is 22 inches. Its typical operating conditions are similar to the 7-inch types above except for the ultor voltage which is 12 kv.

Special and industrial types

The RCA 6080 is a low-mu, high-perveance, power, twin triode, similar in characteristics to the 6AS7-G and with pin connections identical to the 6SN7-GT. Smaller in size and mechanically sturdier, it has been designed primarily for use as the regulator tube in stabilized d.c. power-supply units and is useful in projection television scanning applications where high pulsed plate voltages are encountered.

Other special tubes include the u.h.f. triode 5893, the 5822 ignitron, the GL-5727 thyatron and the 6038 ATR tube. These may be described later.

—end—

WHAT is TEK-FILE

- 1** Tek-File is Rider service data in package form.
- 2** New Tek-File packs are available every month.
- 3** Tek-File's contents are grouped according to manufacturers.
- 4** All Tek-File data is the official, complete factory-issued data direct from the manufacturer.
- 5** Tek-File folders are packed one or more to a box . . . a minimum of 128 (8¹/₂ X 11") pages for only \$2.00. The cumulative index covering all issued Tek-Files is available *free* from your distributor.
- 6** With Tek-File you buy only the servicing data you need to match the set you're working on . . . and it's complete data! Includes chassis views, voltages, resistance readings, troubleshooting test patterns, complete alignment procedures, waveforms, circuit action descriptions, complete parts lists and values, coverage of all models and circuit changes, plus all unpackaging and installation data . . . and much, much more.
- 7** Tek-File gives you *extras!* A free coupon, 15 of which entitle you to a free hard-cover, permanent Rider manual binder for Tek-File shelf use . . . plus Tek-File Handies, 3 X 5" index cards containing trouble cures based on manufacturer's changes for his set.

Remember all this for only \$2.00 — buy it from your jobber today!



The man who uses Tek-File finds servicing easier



JOHN F. RIDER

PUBLISHER, INC.
480 Canal St., N. Y. 13, N. Y.

Rauland—the Original

LOW FOCUS VOLTAGE ELECTROSTATIC TUBE

Perfected in Rauland Electronics Laboratories, this tube that gives edge-to-edge sharpness of focus without coils and magnets is proved and ready as the materials pinch becomes painful

BETTER in all ways! Gives better over-all focus—hair-line sharpness from edge-to-edge—with NO critical materials for focusing . . . and **STAYS SHARP** under considerable variation in line voltages.

REQUIRES NO re-engineering of present television chassis . . . NO added high voltage focus circuit . . . NO added receiver tubes . . . NO additional components except an inexpensive potentiometer or resistor.

FOCUSES by using D.C. voltage already available in the receiver.

ELIMINATES focusing coils and magnets . . . saves critically scarce copper and cobalt.

• • •

This new Rauland development is now available in substantial quantities in 17 and 20 inch rectangular tubes. For further information, address . . .

THE RAULAND CORPORATION



Perfection Through Research

4245 N. KNOX AVENUE • CHICAGO 41, ILLINOIS



RADIO-ELECTRONICS

VARYING THE BANDWIDTH

By WILBUR HANTZ

COMMUNICATIONS and other high-quality receivers may use several double- or triple-tuned i.f. transformers to obtain a specific selectivity curve. Triple-tuned transformers are excellent, but their cost prevents the average constructor from using them.

You can build your own i.f. channels for any passband within reason from standard commercially available i.f. transformers. The intermediate frequency is not too critical and may be anything from 175 to 2,000 kc.

Several methods may be used to vary the coupling in intermediate-frequency stages. Some receivers use a mechanical arrangement which changes the distance between the primary and secondary windings of the i.f. transformer for different degrees of selectivity, but the mechanical difficulties deter the average home constructor.

Fig. 1 shows a coupling arrangement using two i.f. transformers. Reactance

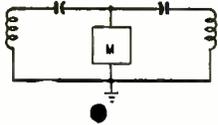


Fig. 1—Setup for varying selectivity.

of coupling component M controls the width of the selectivity curve.

Figs. 2, 3, and 4 show three variable coupling arrangements using two standard output i.f. transformers. In Fig. 2 the coupling component is a tapped inductance connected to a single-pole, five-position switch for selecting the passband. The coupling inductance used here is made by winding a form 2½ inches long and 1 inch in diameter with 50 turns of No. 22 enameled wire, tapped at 9, 16, 23, and 35 turns from ground. The passband of this unit is variable from 7 to 12 kc.

In Fig. 3 the coupling components are from left to right, .003-, .007-, .01-, .03-, and .07-µf capacitors. The passband of this unit is the same as above.

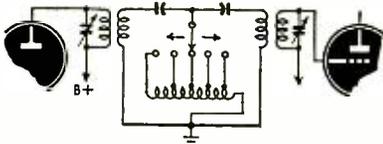


Fig. 2—Reactance using a tapped coil.

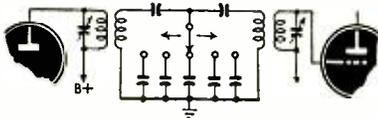


Fig. 3—Selected capacitors may be used.

The coupling in Fig 4 is varied by switching resistors of different values. Resistors present a uniform impedance or coupling factor at all the frequencies within the passband, while the effect of an inductance or capacitance is a little greater at one side or the other.

When resistors are used as the cou-

pling component, they tend to decrease the Q of the coils. A small series resistance is equivalent to a high value of shunt resistance. A medium value, 100 ohms, used in the circuit of Fig. 4 has the same effect as shunting the coil with about 700,000 ohms. This circuit has the advantage of giving both steeper and broader selectivity than the above circuits. The resistors are 5, 15, 25, 50, and 100 ohms.

In Fig. 5, the selectivity is varied by switching another coil in series with either the primary or secondary winding of a single i.f. transformer. An output-type i.f. transformer can be altered slightly to provide two different passbands of 10 or 20 kc.

When the switch is thrown to the sharp position, inductance is added to the secondary winding. In the broad position, the extra coil on the secondary

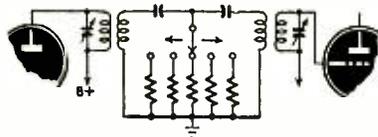


Fig. 4—A symmetrical curve is possible.

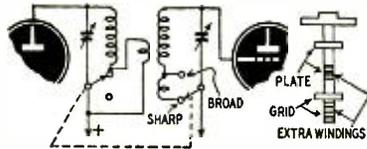


Fig. 5—An alternate 2-position circuit.

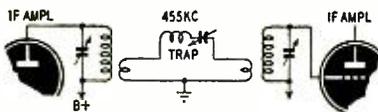


Fig. 6—A circuit of high versatility.


side is removed while inductance is added to the primary winding. The extra windings are 15 turns of No. 30 enameled wire wound in the same direction as the transformer windings.

In Fig. 6 two 455-kc. transformers are used in a bottom coupling arrangement. This circuit is effectively a triple-tuned intermediate transformer and has a straight-sided selectivity curve. As the coupling is low-impedance, the leads between the two transformers can be any convenient length. The wave-trap is tuned to the intermediate frequency. The coupling coils are 15 turns of No. 30 enameled wire close-wound.

The variable-selectivity types should be aligned in the sharp position. All units with the exception of Fig. 6 introduce some loss of gain and may require an additional i.f. stage.

All the information on these coupling arrangements was obtained by oscilloscope measurements. Meissner Ferrocart type 16-5742 output transformers were used. The values given are for a frequency of 455 kc but values for other frequencies can be calculated readily.

—end—

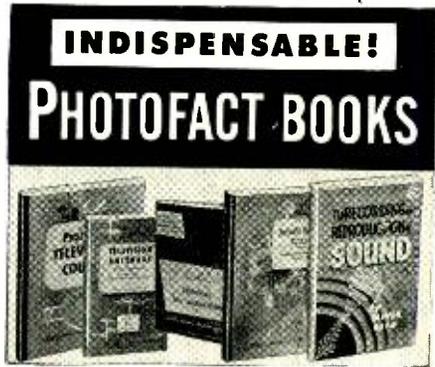

Photofact Television Course. Covers TV principles, operation and practice. 216 pages; profusely illustrated; 8½ x 11". Order TV-1.....Only \$3.00

Television Antennas. New 2nd edition. Describes all TV antenna types; tells how to select, install, solve troubles. Saves time; helps you earn more. 200 pages; illustrated. Order TAG-1.....Only \$2.00

Television Tube Location Guide. Volume 2. Accurate diagrams show position and function of all tubes in hundreds of TV sets; helps you diagnose trouble without removing chassis. 224 pages; pocket-size. Order TGL-2. Only \$2.00

Television Tube Location Guide. Vol. 1. Over 200 pages of TV receiver tube position diagrams on hundreds of models. Order TGL-1.....Only \$1.50

Making Money in TV Servicing. Tested proved methods of operating a profitable TV service business. Covers all important phases. Authoritative, valuable guide to success. Over 130 pages. Order MM-1.....Only \$1.25

Servicing TV in the Customer's Home. Shows how to diagnose trouble using capacitor probe and VTVM. Shortcut methods help save time, earn more on outside service calls. Order TC-1.....Only \$1.50

1949-1950 Record Changer Manual. Vol. 3. Covers 44 models made in 1949, including multi-speed changers and wire and tape recorders. Original data based on actual analysis of equipment. 286 pages; 8½ x 11"; paper-bound. Order CM-3.....Only \$3.00

1948-1949 Changer Manual. Vol. 2. Covers 45 models made in 1948-49. Paper bound. Order CM-2. Only \$4.95

1947-1948 Changer Manual. Vol. 1. Covers 40 post-war models up to 1948. Order CM-1.....Only \$3.95

Recording & Reproduction of Sound. 2nd Edition. New, completely revised and vastly enlarged edition of the outstanding original volume. The most authoritative treatment of all phases of recording and amplification ever written. Over 800 pages. 6 x 9". Order RR-2. Only \$7.95



Audio Amplifiers. Vol. 3. Clear, uniform, accurate data on 50 important audio amplifiers, plus full coverage of 22 FM and AM tuners, produced during 1950. 362 pages, 8½ x 11". Order AA-3.....Only \$3.95

Audio Amplifiers. Vol. 2. A complete analysis of 104 well-known audio amplifiers and 12 tuners made 1949-50. 368 pages, 8½ x 11". Order AA-2.....Only \$3.95

Audio Amplifiers. Vol. 1. 102 amplifiers and FM tuners made through 1948. 352 p. Order AA-1.....Only \$3.95

Auto Radio Manual. Complete service data on more than 100 post-war auto radio models. Covers over 24 mfrs. 350 pages, 8½ x 11". Order AR-1.....Only \$4.95

Communications Receiver Manual. Complete analysis of 50 popular communications models. 246 pages, 8½ x 11". Order CR-1.....Only \$3.00

Radio Receiver Tube Placement Guide. Accurate diagrams show where to replace each tube in 5500 radio models, covering 1938-1947 receivers. 192 pages, pocket-size. Order TP-1.....Only \$1.25

Dial Cord Stringing Guide. Vol. 2. Covers receivers made from 1947 through 1949. Shows you the one right way to string a dial cord in thousands of models. Pocket-size. Order DC-2.....Only \$1.00

Dial Cord Guide. Vol. 1. Covers sets produced 1938 through 1946. Order DC-1.....Only \$1.00

Order from your Parts Jobber or write direct to
HOWARD W. SAMS & CO., INC., 2201 E. 46th St., Indianapolis 5, Indiana

HOWARD W. SAMS & CO., INC.

Specified by Manufacturers*
for Servicing
2-Way Mobile Radios



Model "B"

FILTERED
DC POWER SUPPLY

Leading Manufacturers Say . . . "It's the only one to withstand continuous high overloads, so we specify the Model "B" for servicing." Exclusive application of selenium rectifiers, aided by conduction cooling, doubles rectifier power rating, dissipates over 3 times the heat with lowest cost per ampere output. 1 to 20 amperes continuous duty with peak instantaneous rating of 35 amperes. Operates 2 auto radios with push-button solenoids simultaneously. Net \$49.80.

Other Uses—Phone circuits, relays, instruments, low voltage devices. Battery charging and electroplating.

* Names on request.

Model "BJ" Low Cost Power Supply
6 Volts DC 1 to 12.5 Amperes Net \$37.50



Model "S"

Converts Battery Radios to All-Electric

Plug into AC outlet. Hum-free reception from any 1½ volt 4-6 tube battery radio. Uses less than ¼ the power of cheapest AC radio. Fits battery space. Guaranteed 3 years.


Many Others Available



FREE BULLETIN
ON BATTERY ELIMINATORS

See Your Distributor!

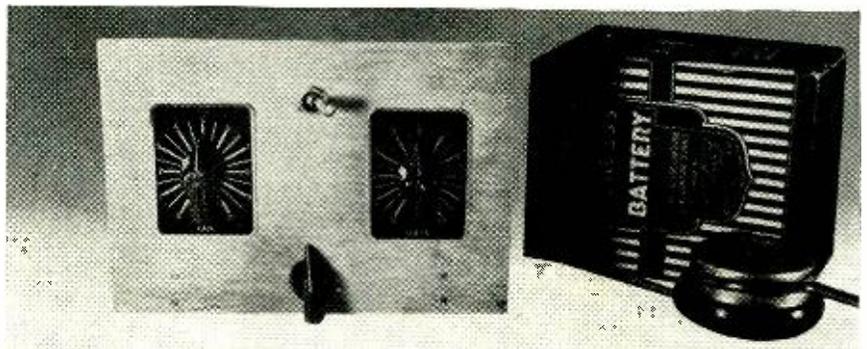If he cannot supply you write to
ELECTRO PRODUCTS LABORATORIES
4501-Rb Ravenswood Ave. Chicago 40, Illinois
In Canada: Atlas Radio Corp., Ltd., Toronto



Front-view photograph of the battery-operated, bandswitching novice receiver.

Bandswitching Receiver For The Novice Amateur

By HOMER L. DAVIDSON

THE little "ham novice" receiver described in this article is very simple to build, but will provide shortwave reception for the inexperienced constructor. Only two battery tubes are used in this amateur receiver. One is an r.f. pentode 1N5-GT, which is used as a regenerative detector. The other tube is a 1A5-GT audio power amplifier. The receiver operates from A- and B-batteries only. The plate supply is a small 45-volt B-battery, while the A-battery supply can be a flashlight cell or a No. 6 dry cell. A good pair of magnetic headphones with a resistance of 2,000 ohms or better will work satisfactorily.

The receiver is mounted in a Masonite and plywood cabinet, to be described later in the text. The set has three operating controls: tuning, regeneration, and band-switching.

The frequency range is from 1.8 to 15 mc. A tapped coil and switch provides a simple method of band changing. Switching eliminates the need for plugging coils in and out for different bands. The regeneration control is a tickler which slides in and out of the grid coil. Regeneration is smooth over a wide range, and there are no variable resistors to introduce noise into the regeneration circuit.

Tube line-up

The regenerative detector 1N5-GT requires a filament voltage of 1.5 at .05 ampere and is hooked in parallel with the 1A5-GT. The grid coil of 70 turns is tapped at 20, 40, and 60 turns. (See Fig. 2-a.) These taps were made by winding 20 turns on the coil form and then twisting the wire around in a tight loop for a tap, then continuing the winding. All the taps were made this way. The last ten turns were spaced to about one full inch for the 20-meter band. It is important to mount

the grid coil with the 1.8-mc coil tap away from the front panel. Thus the 14-mc coil winding will be nearest to the chassis or front panel. By doing so the regeneration can be varied over all bands.

The band switch is mounted on the right, and the tuning capacitor on the left side of the front panel. The ceramic trimmer is mounted on the chassis between the 1N5-GT tube and the tuning capacitor. Binding posts for antenna and ground connection may be mounted at the rear of the chassis. The grid coil is tuned with a small 140- μ f variable capacitor. The tuning is very sharp and one should be able to learn to fish in shortwave and ham stations. This will come with experience after you've played with the set a bit.

A grid leak and grid capacitor is wired in the lead to the control grid of V1. After the signal passes through the tickler coil, it goes through a small r.f. choke RFC to the .01- μ f coupling capacitor. The choke consists of 100 turns of No. 28 enameled wire on a ¼-inch form. The screen grid is kept at a lower potential than the plate by inserting a 470,000-ohm carbon resistor in series with it and the B-battery. A 100,000-ohm carbon resistor is the plate load for the 1N5-GT.

By hooking a coupling capacitor to

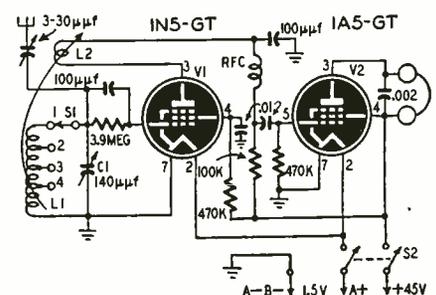


Fig. 1—Diagram of the all-wave 2-tube.

RADIO-ELECTRONICS

Deciding Factors . . .

**SINGLE SOURCE MEANS
MORE PROFIT**
WITH ANTENNAS



AUTO ANTENNAS



TELEVISION

ANTENNAS

Tops for the fringe and super-fringe areas . . . WARD Yagi antennas have universal acceptance. WARD also provides you with the exclusive Para-Con and other TV antennas for city, country and fringe.

*T. M.



There is a WARD antenna for every auto need, featuring the famous 8-ball. WARD auto antennas are the world's most popular and fastest selling.

Only WARD offers a complete line of antennas . . . TV . . . auto . . . FM and mobile communications . . . there is a WARD antenna for every job.

WARD, the best known name in the industry, is the world's oldest and largest manufacturer of antennas. When you concentrate on WARD you can be sure of highest quality . . . that they are stocked by your distributor . . . and that you are selling a nationally famous brand.

So specify WARD whatever your problem . . . a TV antenna for every need, world's fastest selling auto antennas and the most complete line for mobile communication in the industry. One source . . . more profit . . . let "BUY WARD be your BY-WORD"

THE WARD PRODUCTS CORPORATION


Division of The Gabriel Co.

1523 East 45th Street

Cleveland 3, Ohio

In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.

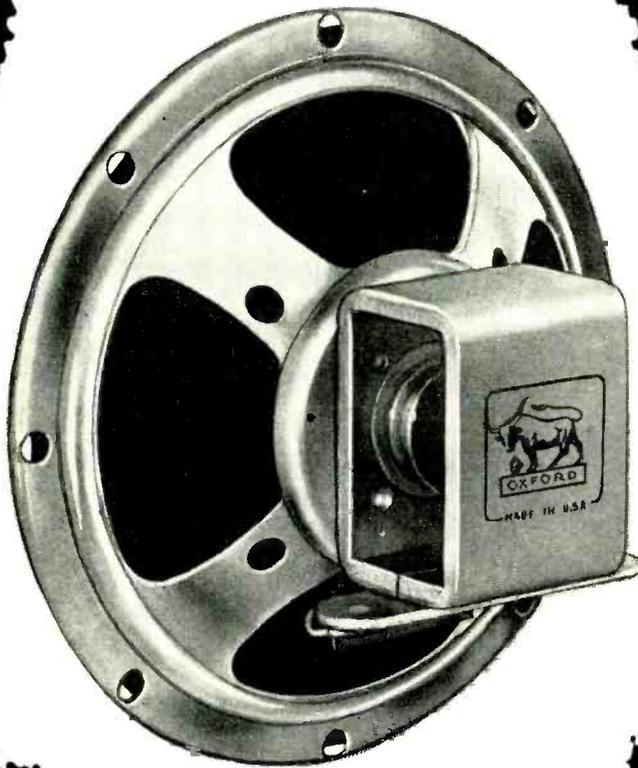for Outdoor and
Weatherproof
Applications



it's
OXFORD
Speakers

Preferred for original equipment
... Proven for replacement!

Other Oxford Speakers for: Radio and Television •
Portable Sets • Auto Radios • P.A. Systems • High
Fidelity • Intercom

OXFORD
ELECTRIC CORPORATION

3911 S. Michigan Ave. • Chicago 15, Ill.
EXPORT: ROBURN AGENCIES, NEW YORK CITY

A copy of our
latest catalog
will be sent
upon request.

Available at
leading jobbers!



the plate load, the signal is transferred to the control grid of V2. A 470,000-ohm resistor is tied in as a grid resistor. The plate and screen grid of the 1A5-GT tube are soldered directly to the phone jack pins. A .002- μ f paper capacitor is wired across the phones. At first, this was not included and one could vary the regeneration by touching the phone cord. This annoying condition can be easily eliminated with the bypass capacitor as shown in Fig. 1.

The 45-volt B-battery is switched off and on with a d.p.d.t. switch. In one leg of this switch the A-supply is switched simultaneously. A connection common to A- and B-batteries is made to ground. These batteries are external.

The regeneration control L2 contains 40 turns of Litz wire and is wound on

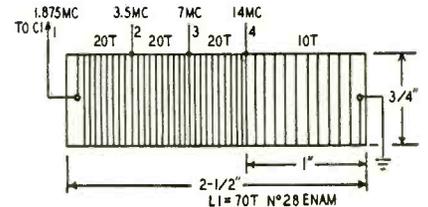


Fig. 2-a—Details on L1, the tuned coil.

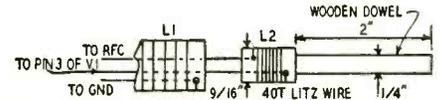


Fig. 2-b—L2 slides inside L1 as shown.

a 9/16-inch coil form. (See Fig. 2-b.) If you can't find a coil form this size, wind paper around a smaller one until it becomes the required diameter. A wooden dowel could be whittled from a larger piece of wood stock, leaving 9/16 inch diameter for the coil form. The Litz wire was taken from an old i.f. transformer and wound tightly around the coil form. Ordinary fine wire (No. 36 or so) will also work well. The form should be as short as possible. Leave about three inches of long leads on the tickler winding so that movement through L1 will be unimpeded.

When the winding is finished, brush on some coil dope for firmness. With a piece of wrapping paper, pad up a 1/4-inch-diameter wooden dowel and place it inside this coil. A spot of coil cement at each end will keep it into place. Let it dry overnight. It is best to build your chassis and wind the coils the first night, then start wiring the receiver later.

In operation this tickler coil is adjusted by slowly inserting coil L2 (middle lower knob) into coil L1 until the threshold point of oscillation is reached. The most sensitive reception is at this point. This setting varies, however, with tuning capacitor and range-switch setting. Be careful not to operate the receiver in an oscillating condition (when you can hear whistles as you tune to and away from a station). This ruins the quality of reception. Pull the tickler back and start building up regeneration very slowly again.

Mounting and wiring


A few words should be said about mounting the various components of



ALL RANGES WITH THIS ONE CONTROL

**Model
630**

Just *one* knob—extra large—easy to turn—flush with the panel, controls all ranges. This one knob saves your time—minimizes the chances of “burn-outs” because you don’t have to remember to set another control. You can work fast with Model 630 with your eyes as well as your hands. Look at that scale—wide open—easy to read, accurately. Yes, this is a *smooth TV* tester. Fast, safe, no projecting knobs, or jacks, or meter case. Get your hand on that single control and you’ll see why thousands of “Model 630’s” are already in use in almost every kind of electrical testing

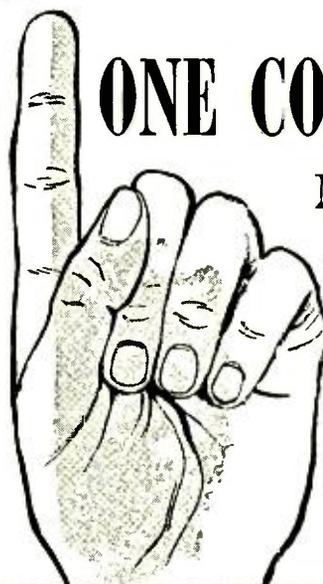

ONLY \$39.50 AT YOUR DISTRIBUTOR


In Canada: Triplett Instruments of Canada, Georgetown, Ontario

FOR THE MAN WHO TAKES PRIDE IN HIS WORK

Triplett

TRIPLETT ELECTRICAL INSTRUMENT COMPANY • BLUFFTON, OHIO, U.S.A.

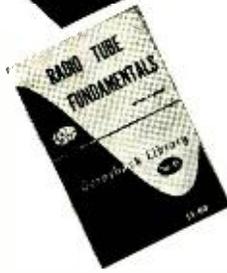Practical, Popular-priced Books on
RADIO•AUDIO•SERVICING



A NEW BOOK ON RADIO TUBES!

RADIO TUBE FUNDAMENTALS—No. 45. By George J. Christ. 96 pages, 74 illustrations. **Just off the press**—the first and only low-priced book to give you such a complete picture of the how, what and why of radio tubes—the heart of any set. The author, an engineer and teacher, gives the radio man the information he wants about tubes in the way he's accustomed to using it. Here's a practical book that will increase your understanding of radio whether you're a 25-year man or just starting out. Covers tubes from the electron theory to a working analysis of the different types of tubes. You'll find this new Gernsback Library Book as valuable as your soldering iron! Order your copy today. Only \$1.00.

TWO TOP-FLIGHT \$1.00 BOOKS

MODEL CONTROL BY RADIO—No. 43. By Edward L. Saford, Jr. 112 pages. An authority in the field of radio control gives you the first complete book on the subject. For beginner and expert. Tells you what radio control is, how it works and how to construct not only component parts but a complete system as well. Illustrations explain each step.

HIGH-FIDELITY TECHNIQUES—No. 42. By James R. Langham, 112 pages. You've never seen a technical book like it! Just as he'd talk to you across the work bench, RADIO-ELECTRONICS' popular audio writer tells you how to design your own equipment and how to get top performance from it. Takes the double talk out of high-fidelity work.



THREE IMPORTANT 75¢ BOOKS



PUBLIC-ADDRESS GUIDE—No. 41. 80 pages. This handy book shows the service technician the way to extra income in big-paying PA work. Covers installation, maintenance and construction.

THE CATHODE-RAY OSCILLOSCOPE—No. 40. 112 pages. A "must" for servicing TV, FM and AM receivers and in amateur operation! Tells in simple, but technically sound language, how the scope works and how to use it.

PRACTICAL DISC RECORDING—No. 39. 96 pages. Tells you how to make good disc recordings. Covers every phase, theory as well as technique. A full chapter is devoted to each component.

6 POPULAR 64-PAGE BOOKS — 50¢ EACH

HANDY KINKS AND SHORT CUTS—No. 29. A treasury of time savers! Antennas, power supplies, test equipment, phonographs, amplifiers. Easy reference. Illustrated.

UNUSUAL PATENTED CIRCUITS—No. 30. A gold mine of important hook-ups. Control circuits, detectors, amplifiers, power supplies, foreign circuits.

RADIO QUESTIONS & ANSWERS—No. 31. Answers the tough ones on circuit diagrams, amplifiers, receivers, transmitters, meters and test equipment.

ADVANCED SERVICE TECHNIQUE—No. 32. A "must" for the advanced service technician! Covers specialized problems of servicing not usually found in ordinary textbooks.

AMPLIFIER BUILDER'S GUIDE—No. 33. For the designer and builder of audio equipment. Covers a variety of amplifiers with power outputs from 8 to 30 watts.

RADIO TEST INSTRUMENTS—No. 36. Practical construction data on signal tracers, capacity meters, portable and bench multi-checkers, voltmeters, etc.

THE GERNSBACK LIBRARY

SEE YOUR DISTRIBUTOR OR MAIL THIS COUPON TODAY

RADCRAFT PUBLICATIONS, INC.
 25 West Broadway, New York 7, N. Y.

Enclosed is \$..... for which please send me postpaid, the books checked below.

- | | | | | | |
|-----------------------------|-----------------------------|-----------------------------|-----------------------------|-----------------------------|-----------------------------|
| <input type="checkbox"/> 29 | <input type="checkbox"/> 30 | <input type="checkbox"/> 31 | <input type="checkbox"/> 32 | <input type="checkbox"/> 33 | <input type="checkbox"/> 36 |
| <input type="checkbox"/> 39 | <input type="checkbox"/> 40 | <input type="checkbox"/> 41 | <input type="checkbox"/> 42 | <input type="checkbox"/> 43 | <input type="checkbox"/> 45 |

Name.....
 Street.....
 City..... Zone..... State..... **32**

the receiver. After all the holes are drilled, mount the larger parts first. Then connect the smaller parts such as capacitors and resistors, when wiring up the receiver. The diameters of holes are shown in Fig. 3 a and b.

The receiver is very simple to wire. Here are a few wiring *don't's*: Do not use acid-core solder because it will cause corroded, high-resistance joints. Use only rosin-core solder. Don't forget to check the wiring twice before trying

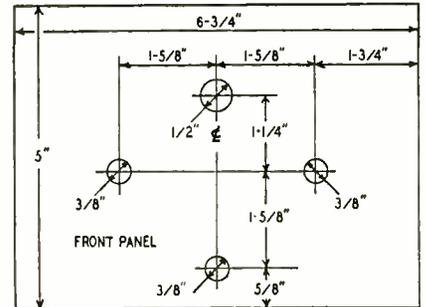


Fig. 3-a—Details of the plywood panel.


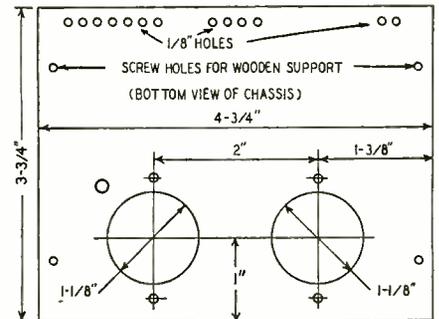


Fig. 3-b—Space chassis holes as shown.

it out. It is very discouraging not to have it work at once. Don't forget to scrape the ends of the Litz wire clean and tin them, because the outside of the wire is enameled. It is also very easy to break the wire while scraping, so be as careful as possible. Use fine emery cloth. Do not use long r.f. lead wires. A neat soldering and wiring job should be done, as long straggling wires are poison to high frequencies. Do not forget to reverse the tickler leads if the receiver fails to oscillate the first time. A proper regenerative condition is indicated by a smooth rushing sound, culminating in a plopping noise as the

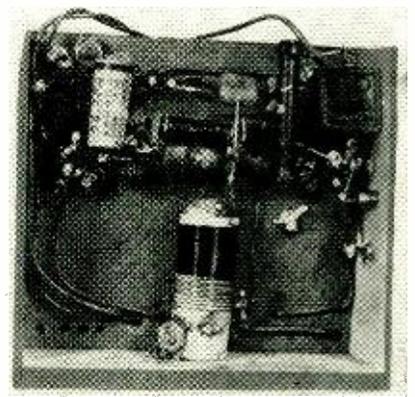


Under-chassis photograph of the receiver. The grid coil L1 is shown in the center. Note the tapered section of the winding.

FOR POSITIVE PROTECTION

YOU'RE SAFE...YOU'RE SURE

with VEE-D-X LIGHTNING ARRESTERS

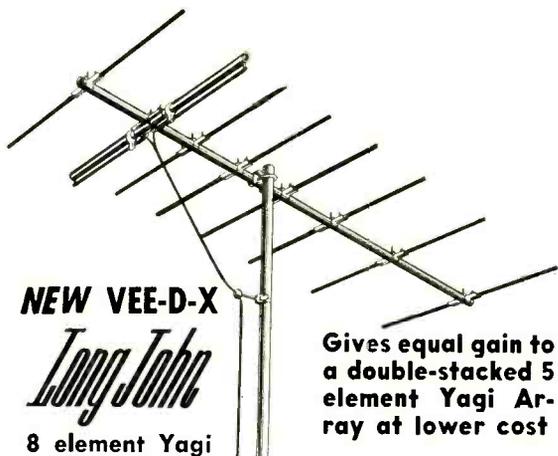

NEW VEE-D-X
Tong John
8 element Yagi

Gives equal gain to a double-stacked 5 element Yagi array at lower cost

A new 8 element Yagi that provides 41% more gain than the best 5 element Yagi, or equal gain to a double-stacked 5 element Yagi array — yet is lower in cost, is easier to install, and provides better roof-top appearance. Famous VEE-D-X pre-assembled construction. The ideal antenna for fringe area operation.

(LESS MAST)
\$12.50 LIST
For Channels 7-13

VEE-D-X OUTBOARD BOOSTER

Out of sight . . . out of the way . . . fits snugly against back panel of any TV set. This single channel booster delivers powerful 18 db gain with full 5 megacycle band width. Install it — forget it! Botherome tuning completely eliminated.



Only
\$19.95 LIST



a sensational
NEW VEE-D-X antenna

MODEL RW-200

\$1.25 LIST

COSTS NO MORE THAN A MIDGET

Most popular full size arrester for standard two-wire transmission line. Exclusive saw-tooth contact points assure positive electrical connection without wire stripping. Exclusive case cover prevents pulling and straining of transmission line against contact — seals out moisture — adds to appearance.



MODEL RW-204

\$1.50 LIST


The first and still the finest arrester ever made to accommodate four-wire rotator line as well as standard two-wire transmission line. Exactly the same in size and appearance as Model RW-200.



MODEL RW-300

\$2.00 LIST

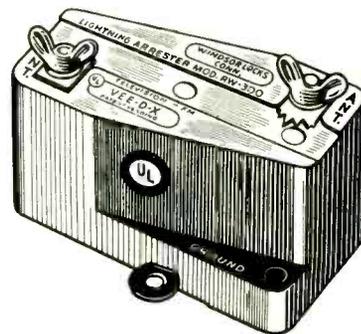For extra heavy duty. First arrester to be introduced to the television trade. It is the time-accepted standard with TV installation men everywhere. Air gap plus resistors provide double protection.



All models available with strap for mast or pipe mounting as well as standard models for wall or window ledge. No wire stripping required on any VEE-D-X arrester.

THE LaPOINTE-PLASCOMOLD CORPORATION
Windsor Locks, Connecticut

Gentlemen:

Send me information on the following _____


NAME _____

STREET _____

CITY _____ ZONE _____ STATE _____

For Direct Drive Circuits... New STANCOR

TELEVISION REPLACEMENT COMPONENTS

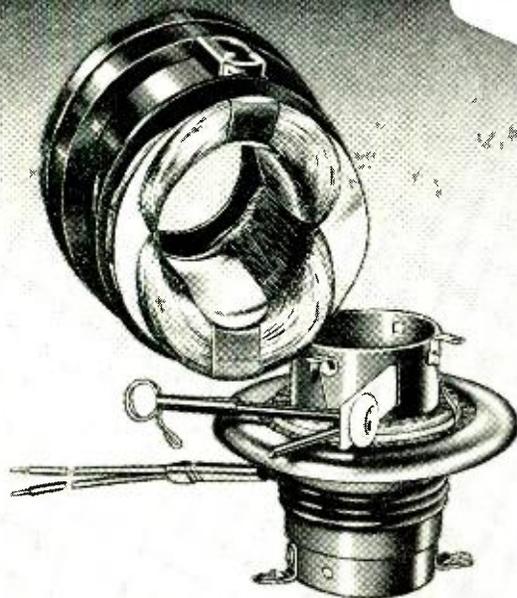

DY-10 ANTI-ASTIGMATIC DEFLECTION YOKE


A high efficiency yoke with cosine distributed windings, ferrite core and nylon bobbins. Replacement in 34 RCA TV models, 30 Emerson models and 7 Capehart models.

A-8131 AIR CORE "FLYBACK"

Companion unit to DY-10 in direct drive circuits and used in some models. See Stancor Bulletin No. 389 for a complete list of these 71 models.

A-8140 VERTICAL OUTPUT TRANSFORMER

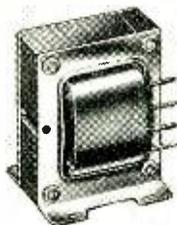Has primary:secondary ratio of 44:1. Replaces RCA No. 74950 in 35 TV models, Emerson No. 738044 in 30 models and Capehart No. 650238A-1 in 7 models. These models are listed in Stancor Bulletin No. 390. Ask your distributor for a free copy.



Stancor transformers are listed in Howard Sams' Photofacts Folders

STANDARD TRANSFORMER CORPORATION

3592 ELSTON AVENUE • CHICAGO 18, ILLINOIS

PARTS LISTS

Bills of material for most of the pieces of equipment described in RADIO-ELECTRONICS construction articles are on hand at all radio parts jobbers and distributors who sell the magazine. See your dealer for a complete parts list of any of this apparatus you wish to construct.

feedback coil, L2, is inserted into the grid coil, L1.

Chassis and front panel

The chassis is made from ¼-inch Masonite. It is 4¾ inches long by 3¾ inches deep. Two small wooden pieces 3¾ inches long and 1 inch high support the chassis; the front panel is screwed tightly or nailed to these wooden strips. All holes were drilled and cut before the chassis was put together. The phone jack holes were drilled in the wooden side support. If the holes are very snug the phone tip jacks may be screwed in and no locknuts are needed.

A piece of mahogany veneer plywood was secured for the front panel. It is 6¾ inches long by 5 inches high. Drill the holes for the tuning capacitor, regeneration control, and S1 control first. Before mounting any parts on the front panel, sand the surface down. Then nail the front panel onto the chassis with four small brads. The panel was not painted but could be shellacked to keep its original color.

The little receiver has two attractive black dial plates with matched red pointer knobs. When operating the receiver, a good 75-foot antenna should be used. Be sure it is as high as possible and clear of all objects. Also use a good ground such as a cold water pipe for best results.

Materials for receiver

Resistors: 1—100,000, 2—470,000 ohms; 1—3.9 meg-ohms, ½ watt.

Capacitors: 1—140 µuf, midget variable; 1—3.30 µuf, ceramic trimmer; 2—100 µuf, mica; 1—.002, 2—.01 uf, paper.

Miscellaneous: 1—1N5-GT and 1A5-GT tube and octal sockets. Coils (see text). 1—single-pole 4-position rotary switch, 1—double-pole single-throw toggle switch, 2—pin jacks, 3—bar knobs, 2—black dial plates, 1—45-volt battery, 1—flashlight cell, 2—binding posts, phones, ¼-inch plywood and masonite board, hardware, solder, and wire.

—end—



Suggested by Leslie Boisen, Indianapolis, Ind.
"Sometimes I wish I had a motor driven antenna!"


NOW...Chassis Superiority in an unbeatable combination!

1 World Famous
**630TS
CHASSIS**
Licensed by
R. C. A.
30 Tubes With
C. R. T. Chassis

2 Fabulous new
Rectangular 21"
"Cylindrical"
Picture Tube
With tilted
face plate

3 New Miracle
**CASCADE
TUNER**

4 Provision
for
**UHF
and COLOR**

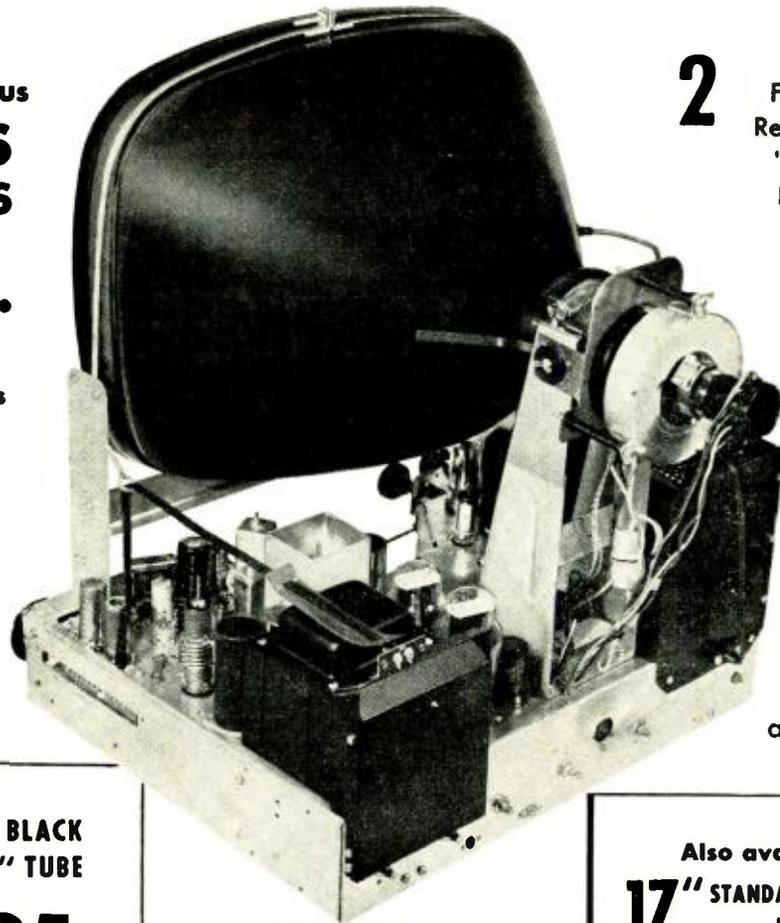

**21" RECTANGULAR BLACK
"CYLINDRICAL" TUBE**
\$179⁹⁵

Complete Chassis Including Speaker
F.O.B. E. Newark, N. J.

Also available with
**17" STANDARD RECTANGULAR
BLACK TUBE**
\$159⁹⁵

Complete Chassis Including Speaker
F.O.B. E. Newark, N. J.

Get the world's most powerful TV chassis unit... combined with the industry's latest advance in the elimination of glare, reflection and distortion. A combination that is incomparable in the field!

- Best for fringe area reception
- Improved keyed A. G. C.
- Full 4 megacycles 14,000 to 16,000 output
- A. F. C. Sync Separator Syncrolok Improved
- 25 Microvolts or better
- Complete chassis with tubes aligned
- Use 70° to 90° deflection yoke coil
- Cascade tuner F.M. Radio,
- 6-inch 'True-to-Life' speaker

NO EXTRA CHARGES—

R. M. A. guarantee on all parts

IMMEDIATE DELIVERY—


15% Down — Balance C. O. D. Remit in full—save C.O.D. charges

(Chassis equipped with 12-inch speaker, \$5.00 additional)

Export Orders Filled

GEM RADIO & TELEVISION CORPORATION

900 Passaic Avenue • East Newark, N. J.

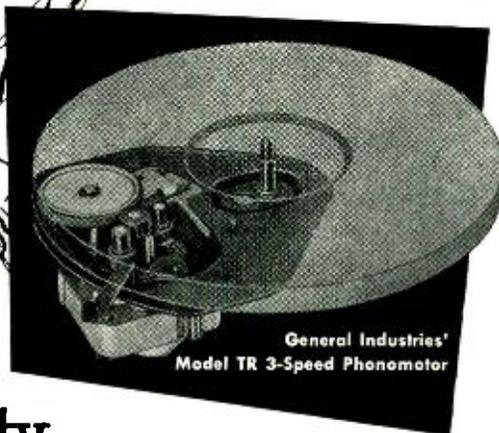

Dependability...

an important reason why leading manufacturers prefer General Industries' 3-Speed Phonomotors

Year after year, General Industries' *Smooth Power* Phonomotors provide trouble-free performance—backing up fine radio, television and record-changer engineering with highest quality motor design and construction.

Write for complete information, including specifications, design features and dimensions. Quantity price quotations available on request.



THE GENERAL INDUSTRIES CO.
DEPARTMENT ME • ELYRIA, OHIO

NEW CONDENSER TESTER



Finds Intermittent Condensers Instantly

Pres-probe's sliding tip with variable resistance prevents condenser heating. Tests with power on. Requires no adjustment. Stops guesswork. Saves time. Convenient probe size (7 1/2" long). Satisfaction guaranteed.

NET **795**
Postpaid U.S.A.

See Your Dist. or Order Direct

PRES-PROBE CO.

4034 N. Sixth St., Milwaukee 12, Wisc.

HAVE YOU A JOB FOR A TRAINED TECHNICIAN?

We have a number of alert young men who have completed intensive training in Radio and Television Repairing. They learned their trades thoroughly by working on actual equipment under personal, expert supervision. If you need a trained man, we invite you to write for an outline of our course, and for a prospectus of the graduate. No fees, of course. Address:

Placement Manager, Dept. P108-3

COMMERCIAL TRADES INSTITUTE

1400 Greenleaf

Chicago 26

PUTTING NEW LIFE IN MIDGET SETS


By C. E. COHN

The circuit shown here is a simple way of squeezing a little more performance out of those ordinary 2-gang superhets which do not already have an r.f. stage, and which use an external antenna. It is essentially an r.f. stage with an aperiodic input circuit, and requires only a tube, socket, and one resistor.

Connecting it to the receiver is simple. First, find a suitable place to install the tube socket, as close to the antenna coil as possible, either on the main chassis or on a subchassis. Disconnect the primary of the antenna coil from its present connections, and connect one end to the B-plus and the other end to the plate of the new tube. The screen of the new tube goes to the converter screen terminal. Make the rest of the connections as shown, connecting the bottom end of the grid resistor to the bottom end of the antenna coil secondary to get a.v.c. Any remote-cutoff r.f. pentode can be used here.


This stage is extremely easy to put in operation, and because of the resistance in the grid circuit, cannot possibly oscillate. There is no cross-modulation that would be caused normally by the use of a remote-cutoff tube. However, it will induce modulation hum into the signal if there is any trace of hum on the chassis. This can be easily eliminated in an a.c. set—with a good ground connection. In a transformerless set, try the plug both ways and use the polarity that gives best operation, since a ground connection is not permissible.

The circuit improves the performance of the set in almost every respect. There is a slight increase in gain and in noise figure, and there is a decided improvement in a.v.c. action. However, the greatest improvement which this set gives is in image rejection. If you tune an ordinary 2-gang superhet across the lower part of the broadcast band from 550 to about 700 kc, you are likely to notice a number of whistles, which are caused by image interference from stations in the upper part of the band. These image stations are so far away from the signal you would think that the antenna tuned circuit could separate them, but in many sets it does not. The effective Q and the selectivity of the mixer circuit are greatly increased,

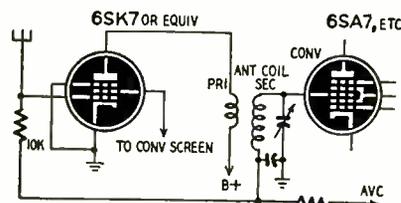

An untuned r.f. stage improves the set.
RADIO-ELECTRONICS

New Supreme 1952 TV Manual

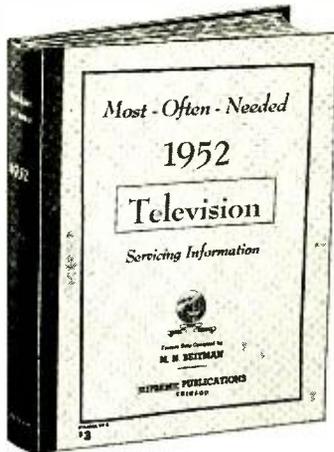

INCLUDES ALL POPULAR SETS

The new 1952 TV manual has complete service material on every popular television set of every important manufacturer. Here is helpful, practical, factory-prepared data that will make servicing and adjustment easy for you. This new giant manual, as well as the previous volumes listed at left, has complete circuits, alignment facts, test patterns, response curves, service hints, voltage charts, waveforms, recommended changes for improvement, and many double-spread diagram blueprints. Here is your TV service material to help you become an expert, and at only \$3 and \$2 per manual.

AMAZING BARGAIN OFFER

The new 1952 TV manual is the most remarkable value offered by Supreme Publications in their 17 years of business. This giant-size television servicing manual at only \$3, or the TV manuals for previous years for only \$3 and \$2 each, are amazing bargains and defy competition. There is nothing else like them. Each manual is a virtual treatise on practical television repairs. By normal standards, each such large manual packed as it is with practical facts, hundreds of illustrations, diagrams, charts, photographs, and expensive extra-large blueprints, should sell for \$10—but as SUPREME special values they are priced at \$3 and \$2 each. Only a publisher who sold over one million TV and radio manuals can offer such bargains based on tremendous volume-sales.

FIND—FIX ALL TV FAULTS

Use the new 1952 TV manual and the earlier volumes (see listing at left) to help you with all TV repairs. Cuts hour-wasting jobs to pleasant moments. Use test patterns for quick adjustment, or look up probable cause of trouble in the pages of hints after simply observing fault in video picture. No equipment needed with these tests. Or use your voltmeter and compare values with many voltage charts included. With an oscilloscope you can get waveforms similar to hundreds illustrated using test points suggested and in a flash locate what used-to-be a hard-to-find fault. Order at our risk for a 10-day trial. Use coupon at bottom of page.

YOURS TO USE ON TRIAL

Be ready to repair any TV set by having in your shop all five Television Manuals described at left. Or try the new 1952 TV manual to see what an amazing bargain you get for only \$3. Order on no-risk trial by using coupon at bottom of page.

1952 TV Manual. New, giant volume gives everything you need to repair and adjust all present-day sets. Double-page schematics, needed alignment, patterns, waveforms, voltage charts, hints. Manual opens flat; 192 pages, large size, 8½x11". Price, only **\$3**

1951 TV Manual. Covers most of the seven million TV sets of this period. Includes 53 mammoth work-bench diagrams. Only... **\$3**

1950 TV Manual. Includes service information on all popular TV sets of all makes from Admiral to Zenith. Large size; 8½x11", plus ten mammoth 11x15" blueprints. Amazing SUPREME bargain at only... **\$3**

1949 TV Manual. Similar to the volume listed above. Has 192 extra-large pages, plus 9 double-spread giant blueprints. To order **\$3** see no-risk trial coupon below. Only... **\$3**

1948 TV Manual. Earlier volume has material on all popular TV sets of this period. Large size; 8½x11". Remarkable value. Including 8 fold-out blueprints, only... **\$3**


1947 FM and TV Manual. Data covers all needed FM and television sets including popular R.C.A. 6307S. Size: 8½x11". Service material on 192 pages. Only... **\$2**



All Supreme Publications TV and Radio manuals are compiled by M. Beitman, radio engineer, teacher, author, and serviceman.

SUPREME RADIO MANUALS

Just out

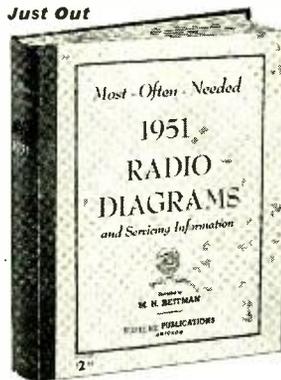

New 1951 Radio Diagrams

Now you can benefit and save money with Supreme amazing manual scoop. This one giant volume has all the service data you need on all recent radio sets. Here you have clearly-printed large schematics, needed alignment data, parts list, voltage values, and information on stage gain, location of trimmers, and dial stringing illustrations. This is the help you need to find tough faults in a jiffy. The new 1951 radio manual is a worthy companion to the 10 previous volumes used to an advantage by over 132,000 shrewd radio men.

BIGGEST BARGAIN IN SERVICE DATA

Wise servicemen know that Supreme Publications manuals have all the material needed at the lowest prices. For the remarkable bargain price (only \$2 for most volumes) you are assured of having on hand needed diagrams and all other essential repair facts on almost all sets you will ever service. Every popular radio of all makes, from old-timers to new 1951 sets is covered. Select manuals wanted, see list below.

RADIO-ELECTRONICS HOME-STUDY COURSE

ONLY \$3.95 COMPLETE 3 VOLUMES 53 Lessons

NEW AMAZING OFFER

Here is the most amazing bargain in radio training. The price scoop of the year. For only \$3.95 (full price) you receive a complete radio-electronics course of 53 large, fact-packed lessons. Covers every topic of radio fundamentals, practical servicing, TV, FM, audio, and industrial electronics. Published in three giant books, bound in one super-mammoth volume. Printed in 1951. Compares lesson by lesson with the best \$200 home-study correspondence courses; but here you get all lessons at one time at the unheard-of bargain price of only \$3.95; nothing further to pay or buy.

THREE COURSES IN ONE

The complete training of these 53 large lessons is really THREE distinct courses on: (1) Practical Radio, (2) Applied Electronics, and (3) Radio Servicing. The lessons are clear, practical, easy to master and use. Early lessons will make fundamentals clear even to a beginner, while other lessons will give you the practical "know-how" of an expert. Notice in the illustration of the manuals, at top, that the wide column on each page has the text, while the narrow column contains pertinent explanations usually supplied by a teacher. These teacher comments guide you over the hard parts, stress points of importance, tell you how to perform practical experiments using any home radio. There are hundreds of review self-testing questions, 427 drawings, pictures, diagrams, and over a thousand service hints.

SUPREME RADIO MANUALS for PREVIOUS YEARS



1950	1949	1948	1947	1946	1942	1941	1940	1939	1926-1938
SUPREME Most-Often-Needed RADIO DIAGRAMS									RADIO DIAGRAMS
Each Manual only \$2 (*50, *49, \$2.50); 192 pages of diagrams, alignment data, voltage, values, parts lists, and service hints; large size, 8½" x 11". To order see coupon below.									240 PAGES
									PRICE \$2.50

YOURS TO TRY FOR 10 DAYS

Just send no-risk coupon, at right, and receive the 3-volume COURSE for a free examination. Use all this material a full 10 days in your own home. Read a few lessons, examine the hundreds of illustrations, apply some of the hints to fix a couple of radios. Only then, if you are pleased, the complete course of 53 lessons, in three volumes, is yours to keep for only \$3.95, full price; otherwise, it costs you nothing for the use and examination. Fair enough? Please rush coupon or ask your jobber while your special price for the 3-in-1 volume 53-Lesson course is still only **\$3.95**

Supreme Publications

Sold by all Leading Radio Jobbers

NO-RISK TRIAL ORDER COUPON

SUPREME PUBLICATIONS, 3727 W. 13 St., Chicago 23, ILL.

Send on trial the manuals checked below and at right. You guarantee complete satisfaction.

<input type="checkbox"/> New 1952 Television Service Manual.....\$3. <input type="checkbox"/> 1951 TV...\$3. 1950 TV...\$3. 1949 TV...\$3. <input type="checkbox"/> 1948 TV...\$3. <input type="checkbox"/> 1947 TV & FM, only...\$2. <input type="checkbox"/> Radio & Electronics Course, 53 Lessons...\$3.95 <input type="checkbox"/> I am enclosing \$..... Send postpaid. <input type="checkbox"/> Send C.O.D. I am enclosing \$..... deposit.	Radio Diagram Manuals <input type="checkbox"/> 1951 <input type="checkbox"/> 1950 <input type="checkbox"/> 1949 <input type="checkbox"/> 1948 <input type="checkbox"/> 1947 <input type="checkbox"/> 1946 <input type="checkbox"/> 1942 <input type="checkbox"/> 1941 <input type="checkbox"/> 1940 <input type="checkbox"/> 1939 <input type="checkbox"/> 1926-38 Manual, \$2.50
---	--

EACH ONLY \$2.50

PRICED AT ONLY \$2 EACH

Name:

Address:

ANOTHER *Editors and Engineers* **PUBLICATION**

**RADIOTELEPHONE
LICENSE
MANUAL**

RADIOTELEPHONE OPERATOR'S
QUESTIONS AND ANSWERS
STUDY GUIDE

**GET YOUR
COMMERCIAL
RADIOTELEPHONE
LICENSE**

WITH THIS BRAND NEW BOOK

Now in one convenient volume,
everything you need to obtain
your license. Contains the
following elements:

- ELEMENT I:
Questions On Basic Law
- ELEMENT II:
Basic Operating Practice
- ELEMENT III:
Basic Radiotelephone
- ELEMENT IV:
Advanced Radiotelephone

\$3.75 FROM YOUR DISTRIBUTOR

ADD 10% ON DIRECT MAIL ORDERS TO

EDITORS AND ENGINEERS, LTD., 1305 KENWOOD ROAD, SANTA BARBARA, CALIF.

Bookstores order from BAKER AND TAYLOR CO., Hillside, New Jersey

and the whistles practically disappear.

Replacing the original antenna coil with a matching r.f. coil may give a slight increase in gain. This is especially true if the antenna coil has a low-impedance primary. If the primary winding is high-impedance (a large universal-wound coil) it may be well matched to a pentode plate. Experiment will tell. Even more gain may be obtained (especially at the low-frequency end of the dial) by using a choke (or untuned antenna) coil in place of the grid resistor. This coil should be trimmed till it resonates just beyond the low-frequency end of the band. There is some danger of oscillation with this hookup. Increasing the grid resistor from 10,000 to 50,000 may increase volume.

This circuit can be used in an all-wave set, being fully effective to the highest ranges. In such receivers, the plate and B-plus connections previously made to the antenna winding will now be made to the antenna and ground connections on the bandswitch respectively. In most cases, this circuit gives added performance.


Some commercial sets use an arrangement in which the antenna coil (or built-in loop) is used in the grid circuit of a tuned r.f. stage whose plate is fed through an r.f. choke coil. A .0001- μ f capacitor couples the r.f. plate to the control grid of the mixer. A 1/2-megohm resistor from the mixer grid to the a.v.c. line allows bias control.

—end—

GIANT TV SALE

Save on Chassis, Tubes, Cabinets, Accessories, etc.

NEW—THE SENSATIONAL 630-DX CHASSIS

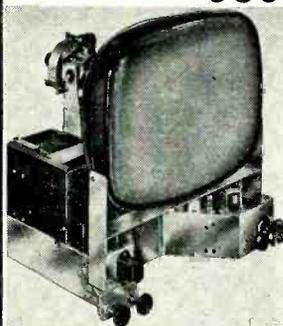

Amazing Low Price!
1952 Model—30-Tubes—
RCA lic.—For 16" to 24"
Picture Tubes.
FINEST CHASSIS AVAIL-
ABLE At Any Price! For long
range and best reception up to
200 miles without a complicated
booster or antenna, this new,
advanced 630 DX Chassis gives
3-times normal reception. Special
extra-high gain standard
coil tuner offers greater sensi-
tivity, top performance on any
channel; aligned & tested for 5
hours; molded condensers; 4
microvolts sensitivity; Arm-
strong FM sound system; hori-
zontal & linear lock and is di-
rectly adaptable for color and
UHF. This is the very best
Chassis buy—order NOW at this
low-low price! You can't beat it!

RMA Guaranteed—Factory Wired \$159.95 (Incl. Fed. Tax—less CRT)
Complete, ready to play including 12" speaker, hardware and knobs: \$144.50 (Incl. Fed. Tax—less CRT)

630 Standard Chassis, complete **Now! \$144.50**

FREE! With any chassis, a copy of the famous "TV Trouble Shooting Method," locate all troubles in a jiffy. Complete with illustrations and hundreds of rapid checks. Get yours NOW—FREE!

TV TUBE ACCESSORIES—ANTENNAS

Each Specially Priced!

- Universal Mounting Bracket, \$6.97
- Sleeve & Ring for 16" Metal 3.85
- Sleeve & Ring for 19" " 4.04
- Sleeve & Ring for 24" " 7.95
- All Aluminum Conical Antennas \$3.29 ea.
- Lots of 12—\$2.69 ea.
- All Aluminum "Vee" Type Antenna \$3.29 ea.
- Lots of 12—\$2.69 ea.

LUXURIOUS, NEW TV CABINETS

For 630 Chassis, 17", 19", & 20" Picture Tubes

Model
100
Reduced
to

\$39.95



Save
45%!
Custom
Styled

Model
200
Now
only

\$49.50



Blonde finish add \$10

Every beautiful cabinet, in richly finished, hand rubbed mahogany will stand out in any room. Made special to house the 630 chassis, they will carry a 17", 19" or 20" picture tube. Every cabinet is custom styled, made by craftsmen and guaranteed perfect. Includes safety glass, mask & mounting brackets. Order Now and Save 45%!

**All Prices Reduced!
CRYSTAL CLEAR
LUCITE MASKS**

Framed in Rich Gold Leaf Finish

RO—Round Tubes	RE—Rect. Tubes
11" RE 10 1/2" x 13 1/4"	\$4.49
16" RE 12 1/2" x 15 3/4"	5.79
16" RO 13 1/2" x 17"	5.89
17" RE 13 1/2" x 17"	5.89
19" RO 15 1/2" x 20"	7.69
20" RE 16 1/2" x 20 1/2"	7.69
21" RO 21" x 25"	13.95

TV PICTURE TUBES

6-Months Guarantee—non pro-rata
Black Face—Brand New—Standard Brands—
Sealed Cartons

10BP4 RO-Glass ... \$24.95	16HP4 RO-Glass ... \$33.95
12LP4 RO-Glass ... 24.95	17BP4 RE-Glass ... 29.95
14BP4 RE-Glass ... 24.95	19AP4A RO-Metal ... 37.95
16GP4 RO-Metal ... 31.95	20CP4 RE-Glass ... 37.95
	24AP4 RO-Metal ... 69.95

NOW! Write for FREE! Catalog including new complete line of tubes, parts, accessories for radio & TV, plus test instruments.

MINIMUM ORDER: \$5.00. 25% deposit with order, balance C.O.D. Include postage with order. All merchandise subject to prior sale. F.O.B. New York City. Prices subject to change without notice.



THE ROSE COMPANY

100 Park Place

Dept. E-3, New York 7, N. Y.

Cortlandt 7-6195

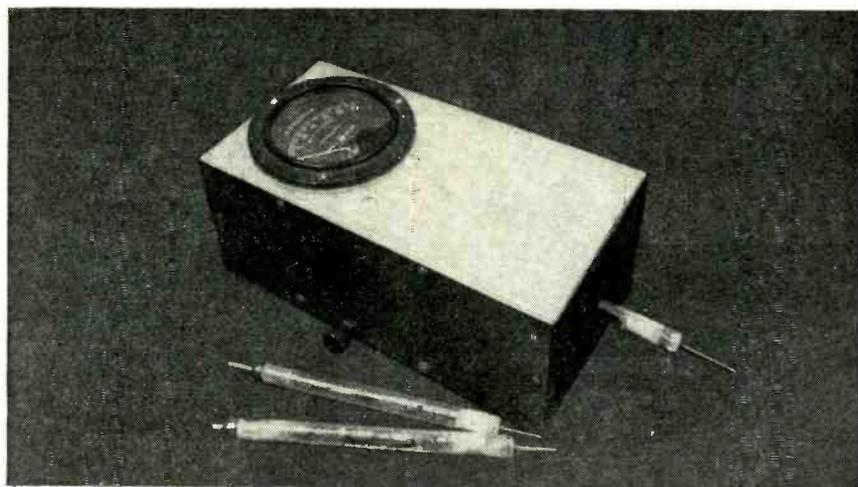


Photo of the trim-looking unit and the associated plug-in multiplier probes.

SENSITIVE R. F. VOLTMETER

By A. STRATMOEN

A GOOD vacuum-tube diode type voltmeter costs a good deal of money. It also requires power to operate the diode. The one illustrated can be constructed for about ten dollars and be designed to cover many ranges by increasing the case size and multiplier resistance. It is ready to operate instantly and requires no connection to the power line. It isn't even necessary to have a ground connection as body capacitance is enough to provide a return path. But for safety's sake it is best to ground it, especially if there is high-voltage d.c. around. Where d.c. is present in the circuit an external blocking capacitor is necessary.


Originally built for amateur use, this circuit can be used to measure relative values of the voltage (with a more sensitive meter and a higher voltage multiplier) at the plate of horizontal output tubes or high voltage rectifiers in TV sets. The meter should present about the same load as the picture tube and the filter capacitor.

The popular germanium diode probe used for measuring r.f. voltage is usually limited to 30 volts maximum, as more than this might exceed the back voltage rating of the crystal, especially if the waveform is not a sine wave.

Some crystal diode rectifiers can be used up to 150 volts, and with a capacitance-type multiplier will safely read almost any voltage.

The unit to be described has been used for quantitative tests on transmitters and open-wire feeder lines to antennas. The illustrations show that the case is used as a three-section shield—two sections around the probe which is also the multiplier, and one around the meter and rectifier assembly. The shield around the probe must have a low capacitance to the resistors or some of the current will pass directly to ground without registering on the meter. The multiplier must be shielded to prevent the sensitive low-voltage end of the multiplier from picking up r.f. both from the source and from the high-voltage end through distributed capacitance. The two-section box shield does this without introducing too much capacitance to ground. The capacitive effect is minimized further by using a fairly large meter current. A 0-1 ma meter is used but the over-all sensitivity is about 450 ohms per volt. This does load the circuit somewhat but for transmitting work this is not undesirable.

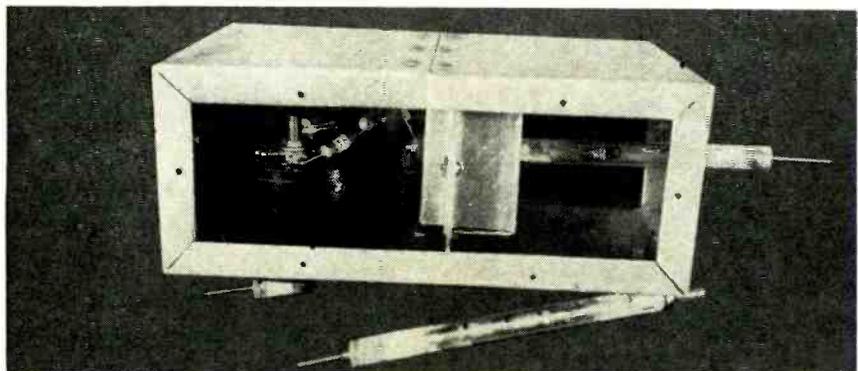The case is constructed of 52S½H aluminum sheet. This alloy combines



View of the inner construction, showing the resistor shielding and the components.

It's **NEW**... It's a **MONEY MAKER**
for
Every Serviceman!

2 Service Instruments
for the price of **1**



TRANSVISION CR TUBE TESTER-REACTIVATOR

performs 2 vital functions:

- Tests Picture Tubes
- Renews Brightness of Many Dim Picture Tubes

It's a **TESTER**:

Without removing picture tube from set, you apply this precise instrument to:—

- Measure Cathode emission
- Locate shorts between elements
- Locate high resistance shorts or leakage as high as 3 megohms

It's a **REACTIVATOR**

for dim CR Picture Tubes

Revives dim TV Picture Tubes, without removal of tubes from sets. Works on a great many tubes with low light output, if there's no mechanical defect in tube, 110 V—60 cycles. Portable, weighs only 3 lbs. One or two applications pays for instrument.

SATISFACTION GUARANTEED or money refunded if you return the instrument in 10 days in good condition. **\$19.95** NET

RUSH THIS COUPON—

TRANSVISION, INC.
DEPT. RC NEW ROCHELLE, N. Y.

Send me ___ CR Tube Tester-Reactivator(s).

Enclosed find \$___ deposit. Balance C.O.D.

Enclosed find \$___ in full. Send prepaid.

Name _____

Address _____

City _____ State _____

only \$67⁵⁰
for this
"Challenger"
tube tester
by JACKSON



As the name implies, we ask you to compare our "Challenger" instruments with any and all others at anywhere near the price.

In the Model 115 "Challenger" Tube Tester, the famous Jackson *Dynamic*® test principle is employed. Separate voltages are applied to each tube element. Tests can be made under actual use conditions.

A feature of this instrument is the high voltage power supply. It affords more accurate results because of high plate voltages—over 200 v. for some types of tubes.

Spare socket positions are pro-

vided for future use, thus avoiding obsolescence. Push-button and selector switch controls simplify operation. The 4-inch-square meter is easy to read. The instrument gives complete short tests. It is applicable to over 700 types of tubes including TV amplifiers and rectifiers. The built-in roll chart is frequently revised to provide data on new tubes. This service is free for one year.

Finish is attractive Challenger Green with harmonizing knobs, meter cover, and push-buttons. Size, as of all "Challenger" instruments, is 13" x 9½" x 5½". Weight, 11 lbs.

Each of these "Challenger" instruments

\$59⁵⁰



Condenser Tester Model 112



Test Oscillator Model 106

Push-button controlled. Provides quick positive range selection for capacity and leakage tests. Shows up all types of faulty condensers, using a new method for detecting leakage. No need to count flashes on the electron ray tube indicator! Test voltages from 20 v. to 500 v. in six steps. Glass-enclosed dial with Jackson "Scale Expander" pointer which doubles effective scale length. Power factor measured on Direct Reading Scale calibrated from 0 to 60%. Ranges from .00001 to 1000 mfd in four steps.

Here's a "Challenger" instrument for testing AM and FM radios. It is also used as an auxiliary TV marker generator. Range of fundamental frequencies is 100 kc to 54 mc . . . Harmonics calibrated 54 mc to 216 mc. Two-circuit attenuator controls signal strength. 400 cycle audio modulation, or may be used for straight RF unmodulated signal. Accuracy is ½ of 1% in all ranges. Same finish and dimensions as other "Challenger" instruments. Compare this instrument with any low-priced signal generator or with any so-called kit.

stiffness and workability. For an 8x4x3-inch case, sheeting of .025 gauge is about right. The sides, however, could be heavier since it isn't necessary to bend them. One side is riveted permanently and the other one is fastened with self-tapping screws. Two partitions reinforce the sides, shield the multiplier, and divide the case into three sections. The construction of the inner shields and banana jack support should be completed before assembling the case.

The multiplier resistance for each range may be determined by using an audio-frequency voltage and an accurate a.c. voltmeter. Start with about 450 ohms per volt. The multipliers would be accurate only for sine waves as most voltmeters read r.m.s. values. The multiplier should have at least three resistors, especially for the higher ranges. On the 1,500-volt range the resistors may dissipate a little over 3 watts so the total wattage should be adequate. It is preferable to have the resistors in a multiplier as near identical as possible in wattage and ohmage.

The probe-multipliers are made of Amphenol polystyrene tubing and rods. ¼-inch rods just fit into ⅜-inch tubing, so these sizes are used. A ½-inch length of rod is drilled axially and tapped for the 6-32 thread of standard banana plugs. It is difficult to drill this straight unless the rod is placed in the drill chuck and the drill bit clamped in a vise. This rod is then cemented in the end of a piece of tubing with polystyrene cement and allowed to harden. Then a ¼-inch hole is drilled alongside the threads for the resistor lead. After the resistor string is made up use a length of ¼-inch brass welding rod at one end for the probe tip. The resistors should be so spaced that about half of the last one will be inside the inner shield when the probe is plugged in. After making a final check of the multiplier for accuracy, seal the probe end with a section of rod drilled to fit the welding rod, and cement it in place.

The meter illustrated use four probes to give 0-3, 30, 300, and 1,500-volt

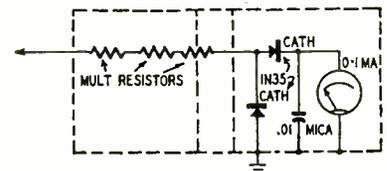


Diagram of the diode-type voltmeter.

ranges. The circuit was selected because it gives linear readings on all but the 3-volt scale, allowing d.c. meter scales to be used. A 1N35 dual crystal (having matched characteristics) is used in preference to the 1N34 types.

Materials for Voltmeter

One 0-1 ma meter, one .01-µf mica capacitor, one 1N35 germanium crystal, some ¼-inch polystyrene rods, several lengths of ⅜-inch polystyrene tubing 5½ inches long, several pieces of brass welding rod, several banana plugs, a jack with insulating washers, three matched 1-watt 5% tolerance resistors (see text), per multiplier-probe, and solder. Several .025-gauge 52S½H aluminum sheets, binding posts, hardware, etc.

—end—

JACKSON ELECTRICAL INSTRUMENT CO.
"Service Engineered" Test Equipment DAYTON 2, OHIO In Canada: The Canadian Marconi Co.

A VISUAL ALARM FOR HARD-OF-HEARING


By RICHARD H. HOUSTON

One member of our household is somewhat hard-of-hearing, although not enough so to be considered really deaf. On numerous occasions he is left to hold the fort alone for an evening as general custodian and baby sitter. While not a professional, he enjoys the family TV receiver in true sitter style. Now this is where a problem arises. With the receiver volume at a fairly high level, the telephone bell is not sufficiently loud to attract the sitter's attention if he is absorbed in a TV program. This difficulty caused several evenings of anxiety when a call home produced no response.

Some kind of signal or alarm with more attention-getting power was needed. We considered using a mike, amplifier, and speaker which would make the sound of the phone bell much louder. The baby sitter would hear it, but so would the baby! Some other method would have to be used.

A little thought brought up the idea of using a light as the signal. The following system was developed quickly. A microphone picks up the sound of the telephone bell and an electronic circuit operates a relay, which in turn flashes a light near the TV screen. It works every time.

The control unit shown in the diagram is built in a conventional chassis to be mounted in a wooden cabinet. A two-stage resistance-coupled amplifier raises the voltage from the microphone to a level of 20 volts or more (depending on the mike output). The amplifier output is rectified by the 6AL5, producing a positive voltage at the cathodes. This positive potential is present only when sound is being picked up by the mike.

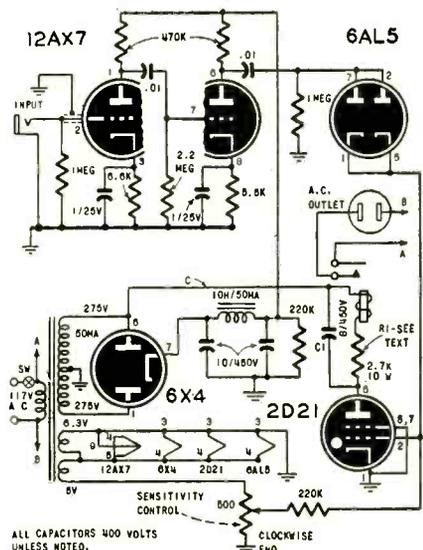

Schematic of the sound-operated alarm.
MARCH, 1952



"CONICAL-V-BEAMS"

*REGISTERED TRADE MARK

CHECK! your antenna requirements

WITH THESE THREE

Telrex FEATURES:

1. CONSERVATIVE FACTORY RATINGS
2. EXCEPTIONAL PICTURE QUALITY
3. WEATHER-DURABLE CONSTRUCTION

There's no finer antenna at any price! Every model — whether for high signal areas or remote locations — assures full audio and video bandpass, high gain and high signal to noise ratio. All materials used in their construction are weather-tested to insure maximum service life under the most grueling climatic conditions. For finer pictures and lasting installations, install genuine Telrex "Conical-V-Beams"—your key to complete antenna satisfaction. Write for new catalogs, today!

Guessing is costly on FRINGE AREA installations!

Make sure of picture quality in remote areas by installing the "famous for high gain" Telrex 8X-TV. IF THE 8X-TV does not provide a usable signal, TV reception is impractical!

"CONICAL-V-BEAMS" are covered by Patent No. 23,346
CANADIAN and FOREIGN PATENTS PENDING

Telrex INC.

CONICAL-V-BEAMS

AMERICA'S OUTSTANDING TELEVISION BEAM

Be sure it's a "CONICAL-V-BEAM" — look for the Telrex TRADEMARK

ASBURY PARK 9, N. J.

EASY TO LEARN CODE

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes for beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.



ENDORSED BY THOUSANDS!

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

INSTRUCTOGRAPH COMPANY

4701 Sheridan Rd., Dept. RC, Chicago 40, Ill.

Every RADIOMAN can use these SERVICE HINTS!

Valuable Manual Yours—FREE Write today—no obligation

FEILER ENGINEERING CO. Dept. 3RCZ-1
8026 N. Monticello Ave., Skokie, Ill. (Suburb of Chicago)

Every page of "How to Simplify Radio Repairs" is packed with on-the-bench, practical ideas.

PARTS—TUBES—KITS

50L6—88; 35Z5—59; 6SN7—88; 5V4G—99; 6J6—\$1.06. Standard Brand—Fully Guaranteed. Stanwyck TV Coll Kit—List \$12.95—Special \$3.95. 20" TV Kit \$65.00 Less Tubes. Write for free catalogue. Minimum order \$5.00 F.O.B. N. Y. Money-back guarantee. Send 20% with order. CERTIFIED TELEVISION LABORATORIES Dept. C, 5507-13th Ave., Brooklyn 19, N. Y.



ONE OUTSTANDING FEATURE:

**LOWER IN COST THAN OTHER LEADLINES
PURPORTED TO GIVE YOU THE SAME RESULTS
OTHERS EQUALLY IMPORTANT—**

- Sharp, clean "snow-free" pictures.
- Correct impedance for "ghost-free" reception. Nominal 300 ohms.
- Correct spacing for minimum radiation loss. Less than 1% of operating wave length.
- Fully insulated—approved by safety experts.
- Pure, unadulterated polyethylene insulation—specially treated by our chemists for extreme weather.
- High-efficiency conductors: Flexible, stranded—to insure long life.
- Easily installed—with standard insulators.
- Packaged in convenient lengths: 100', 250', 500', 1,000', 2,500'.
- AT YOUR DEALERS, or Write For Free Samples and Literature.

*Patent Pending *Trade Mark U.S. and Foreign Patents Pending
EXCLUSIVE LICENSEE AND SOLE MANUFACTURER

Don Good, INC.

1014 FAIR OAKS AVENUE
SOUTH PASADENA, CALIFORNIA

OTHER OUTSTANDING GOODLINE PRODUCTS:

VARIABLE TELETRAPS—2: Highly effective for *eliminating interference* from FM STATIONS, and DIATHERMY and AMATEUR SIGNALS within its tuning range.

HI-PASS FILTER: *Eliminates or greatly reduces interference* picked up by I. F. AMPLIFIER or TV RECEIVER—interference arising from strong, local low-frequency fields: X-Ray, Diathermy Equipment, Neon Lights, Etc., Etc.

The positive voltage from the 6AL5 is applied to the grid of a 2D21 thyatron, causing it to conduct and operate the relay in its plate circuit. The contacts of the relay are in series with the a.c. line and the ac output receptacle. Thus when a sound of sufficient intensity is picked up by the microphone, the relay contacts close and turn on a lamp plugged into the a.c. output receptacle. The lamp is placed so that it could not fail to attract attention, using an extension cord if necessary. (Use a small *Photoflood* lamp—it will be seen anywhere in the room.—*Editor.*)

Most circuits of this type need a source of negative voltage to keep the thyatron from firing during no-signal intervals. A negative-voltage power supply would do the trick, but it would increase the size and cost. Fortunately another source of bias is already at hand, since we may use a.c. voltage as bias. The voltage of the filament windings of the power transformer, reverses polarity at the same time as that of the high-voltage winding. If this low voltage is tied to the control grid so the grid goes negative when the plate goes positive, no arc will occur during this half-cycle. When the grid goes positive, the plate will go negative, and still no plate current will flow. Thus we have an a.c. bias doing essentially the work of a constant negative d.c. bias.

The positive voltage from the 6AL5 rectifier is added to this a.c. bias at the grid of the 2D21. When the positive voltage becomes sufficient to cancel the action of the negative a.c. grid swing, the 2D21 conducts on each half-cycle that its plate is positive, since the grid is no longer negative during this period. Thus, each time the microphone picks up sound of sufficient intensity, the thyatron fires and its plate current closes the relay and energizes the a.c. output receptacle.

Since the plate-current flow through the winding of the relay is a series of pulses, capacitor C1 was added to prevent the relay from chattering. Note the polarity indications on C1. The relay may be any type whose contacts will handle 2 or 3 amps. and which will close on a current of 35 to 50 ma. The value of resistance of R1 is best determined experimentally, but will be roughly 3,000 ohms less the resistance of the relay. Omit R1 if the relay resistance is 3,000 ohms or more.

Potentiometer R2 is a sensitivity control. It controls the a.c. bias applied to the grid of the 2D21. The clockwise end of R2 should be grounded. Note that the 5-volt winding is tied in series with the 6.3-volt winding on the power transformer to supply the a.c. bias across the control. This is necessary because 6.3 volts was too low to provide reliable operation. Make sure the two filament windings are in series *adding*, not *bucking*. An a.c. voltmeter will show when the two are adding by indicating a total voltage of about 11.3.

(Continued on page 107)

Unlimited Opportunities in RADIO ENGINEERING

DEGREE IN 27 MONTHS

Complete Radio Engineering course including Telev., U. H. F. and F. M. Bachelor of Science Degree also in Mech., Civil, Elect., Chem., and Aero. Eng.; Bus. Adm., Acct. Extensive campus, modern buildings, well equipped labs. Low cost. Prep courses. Personalized, practical instruction. Founded 1888. Placement service. Growing shortage of engineers. Prepare now for unlimited opportunities ahead. Enter September, January, March, June. Write for catalog.



TRI-STATE COLLEGE

2432 College Ave. ANGOLA, IND.

WANTED TO BUY

Large and small quantities of new or used electronic government or manufacturers' surplus tubes and equipment. Highest prices paid. State quantity, condition and best price in first letter.

Box No. F-2 c/o Radio-Electronics
25 West Broadway
New York 7, N. Y.


Features OF THE NEW 1952



PROOF OF THE NEW O-7 OSCILLOSCOPE'S OUTSTANDING PERFORMANCE


Below are actual, unretouched photographs showing the outstanding frequency response characteristics of the NEW 1952 HEATH-KIT OSCILLOSCOPE, MODEL O-7. To the left is a 10 KC square wave — to the right a 4 MC sine wave as they actually appear on the screen.

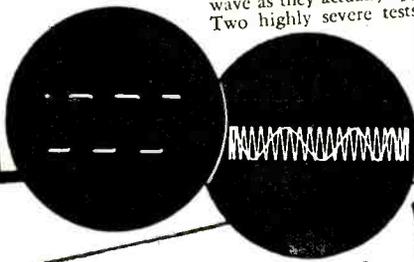Two highly severe tests to make on any scope (only the best of scopes will show traces like these) — and the O-7 really comes through.




COMPANION VACUUM TUBE VOLTMETERS

Here are the two NEW 1952 VACUUM TUBE VOLTMETER COMPANION PIECES. Matched instruments of new design to open up the whole field of DC, AC, and resistance measurements for you. The new greatly reduced size combines style, beauty, and compactness — The V-5 and AV-1 have the new panel and cabinet construction as shown on the right. A tremendous pair of voltmeters. Small in size but virtual giants in the range of measurements they make.

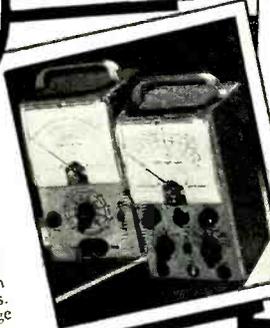

NEW STYLE AND BEAUTY


Style that's modern, yet functional — that's the trend of today — and Heathkits are right up to the minute. Note the cut showing the new V-5 and AV-1 cabinet and panel construction. The front panel and rear cover slide right over the recessed flange of the case thereby eliminating sharp edges and pointed corners. The voltmeter kits aren't "shelf" or "mounted" instruments — they're moved about on the bench a lot and thus the new compact size and specially designed cabinets — Another 1952 Heathkit feature.

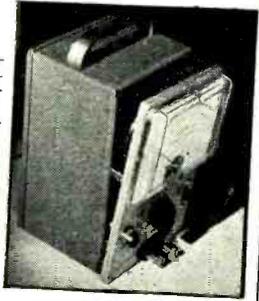

A STATEMENT FROM SIMPSON ELECTRIC CO.

In choosing Simpson Meters for their Heathkit VTVM, the Heath Co. has set a new high standard of kit meter quality. The same high quality of material, workmanship and design that has given Simpson the reputation for building "Instruments That Stay Accurate" is found in the Heathkit Meter Movement.

SIGNED
SIMPSON ELECTRIC CO.

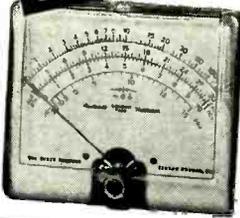

A STATEMENT FROM CHICAGO TRANSFORMER

It is indeed gratifying to note the outstanding sales records you are building with your Heathkits.

This sales success is readily understandable, since we are cognizant of the high quality standards you have established for your component suppliers.

We at Chicago Transformer are proud that our product has contributed to the recognized quality and increasing popularity of Heathkits.


CHICAGO TRANSFORMER DIVISION
Essex Wire Corporation

L. S. RACINE *L. S. Racine*
Vice-President and Sales Manager




HEATHKIT PRECISION RESISTORS

Where exact resistance values are required for instrument accuracy, the Heath Co. has spared no effort in supplying the finest resistors available. Precision resistors as manufactured by Continental Carbon Inc., and Wilcor Corp., meet the rigorous JAN (Joint Army-Navy) specifications and are small in size, extremely non-inductive, highly stable, have a low temperature coefficient, and can be held to great accuracy. You'll find quality components in Heathkits.

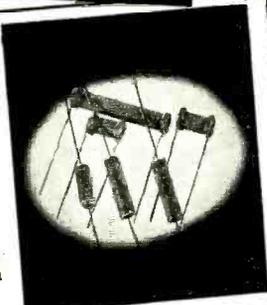

COLLEGES USE HEATHKITS

Colleges and Universities throughout the country are using Heathkits in their electrical engineering, radio, and physics laboratories — Heathkits are the answer to good test equipment at low cost, plus being rugged, dependable, and accurate. Trade schools are having their students build Heathkits to obtain a first hand working knowledge of test equipment and to get the practical experience gained by construction. Heathkits fill school needs.

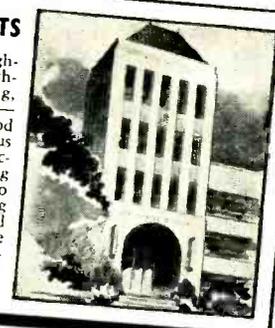

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARLAB-N.Y.


The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

THE *New* 1952
Heathkit
**OSCILLOSCOPE
 KIT**

MODEL O-7
 SHIPPING WEIGHT 24 LBS.

\$43⁵⁰

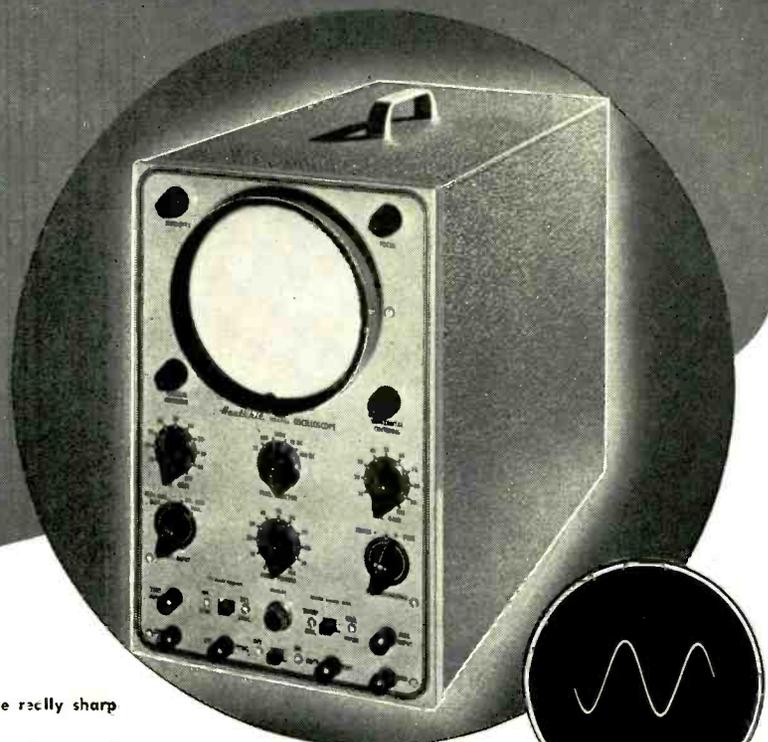

Features

- New "spot shape" control for spot adjustment — to give really sharp focusing.
- A total of ten tubes including CR tube and five miniatures.
- Cascaded vertical amplifiers followed by phase splitter and balanced push-pull deflection amplifiers.
- Greatly reduced retrace time.
- Step attenuated — frequency compensated — cathode follower vertical input.
- Low impedance vertical gain control for minimum distortion.
- New mounting of phase splitter and deflection amplifier tubes near CR tube base.
- Greatly simplified wiring layout.
- Increased frequency response — useful to 5 Mc.
- Tremendous sensitivity .03V RMS per inch Vertical — .6V RMS per inch Horizontal.
- Dual control in vernier sweep frequency circuit — smoother acting.
- Positive or negative peak internal synchronization.

The performance of the NEW, IMPROVED, HEATHKIT 5" OSCILLOSCOPE KIT is truly amazing. The O-7 not only compares favorably with equipment costing 4 and 5 times as much, but in many cases literally surpasses the really expensive equipment. The new, and carefully engineered circuit incorporates the best in electronic design — and a multitude of excellent features all contribute to the outstanding performance of the new scope.

The VERTICAL CHANNEL has a step attenuated, frequency compensated vertical input which feeds a cathode follower stage — this accomplishes improved frequency response; presents a high impedance input, and places the vertical gain control in a low impedance circuit for minimum distortion. Following the cathode follower stage is a twin triode — cascaded amplifiers to contribute to the scope's extremely high sensitivity. Next comes a phase splitter stage which properly drives the push-pull, hi-gain, deflection amplifiers (whose plates are directly coupled to the vertical deflection plates). This fine tube lineup and circuitry give a sensitivity of .03V per inch RMS vertical and useful frequency response to 5 Mc.

The HORIZONTAL CHANNEL consists of a triode phase splitter with a dual potentiometer (horizontal gain control) in its plate and cathode circuits for smooth, proper driving of the push-pull horizontal deflection amplifiers. As in the vertical channel, horizontal deflection amplifier plates are direct coupled to the CR tube horizontal deflection plates (for improved frequency response).

The WIDE-RANGE SWEEP GENERATOR circuit incorporates a twin triode multivibrator stage for producing a good saw-tooth sweep frequency (with faster retrace time). Has both coarse and vernier sweep frequency controls.

And the scope has internal synchronization which operates on either positive or negative peaks of the input signal — both high and low voltage rectifiers — Z axis modulation (intensity modulation) — new spot shape (astigmatism) control for spot adjustment — provisions for external synchronization — vertical centering and horizontal centering controls, wide range focus control — and an intensity control for giving plenty of trace brilliance.

The Model O-7 EVEN HAS GREAT NEW MECHANICAL FEATURES — A special extra-wide CR tube mounting bracket is provided so that the vertical cascade amplifier, vertical phase splitter, vertical deflection amplifier, and horizontal deflection amplifier can mount near the base of the CR tube. This permits close connection between the above stages and to the deflection plates; distributed wiring capacity is greatly reduced, thereby affording increased high frequency response.

The power transformer is specially designed so as to keep its electrostatic and electromagnetic fields to a minimum — also has an internal shield with external ground lead.

You'll like the complete instructions showing all details for easily building the kit — includes pictorials, step-by-step construction procedure, numerous sketches, schematic, circuit description. All necessary components included — transformer, cabinet, all tubes (including CR tube), completely punched and formed chassis — nothing else to buy.

NEW INEXPENSIVE *Heathkit*
ELECTRONIC SWITCH KIT

The companion piece to a scope — Feed two different signals into the switch, connect its output to a scope, and you can observe both signals — each as an individual trace. Gain of each input is easily varied (gain A and gain B controls), the set (gain A and gain B) frequency is simple to adjust (coarse and fine frequency controls) and the traces can be superimposed for comparison or separated for individual study (position control).

Use the switch to see distortion, phase shift, clipping due to improper bias, both the input and output traces of an amplifier — as a square wave generator over limited range.

The kit is complete; all tubes, switches, cabinet, power transformer and all other parts, plus a clear detailed construction manual.



Model S-2
 Shipping Wt. 11 lbs.

Only
\$19⁵⁰

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
 13 E. 40th ST.
 NEW YORK CITY (16)
 CABLE: ANLAB N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

THE *New* 1952

Heathkit VTVM KIT

MODEL V-5
SHIPPING WT. 5 LBS.

\$24.50

Features

- New styling, — formed case for beauty.
- New truly compact size. Cabinet 4 1/8" deep by 4-11/16" wide by 7 3/8" high.
- Quality 200 microamp meter.
- New ohms battery holding clamp and spring clip — assurance of good electrical contact.
- Highest quality precision resistors in multiplier circuit.
- Calibrates on both AC and DC for maximum accuracy.
- Terrific coverage — reads from 1/2V to 1000V AC, 1/2V to 1000V DC, and .1 to over 1 billion ohms resistance.
- Large, clearly marked meter scales indicate ohms, AC Volts, DC Volts, and DB — has zero set mark for FM alignment.
- New styling presents attractive and professional appearance.

A real beauty — you'll have only highest praise for this NEW MODEL VACUUM TUBE VOLTMETER. Truly a beautiful little instrument — and it's more compact than any of our previous models. Note the new rounded edges on the front panel and rear cover. The size is greatly reduced to occupy a minimum of space on your workbench — yet the meter remains the same large size with plainly marked scales.

A set of specially designed control mounting brackets permit calibration to be performed with greatest ease — also makes for ease in wiring. New battery mounting clamp holds ohms battery tightly into place, and base spring clip insures a good connection to the ohms string of resistors.

The circuitry employs two vacuum tubes — A duo diode operating when AC voltage measurements are taken, and a twin triode in the circuit at all times. The cathode balancing circuit of the twin triode assures sensitive measurements, and yet offers complete protection to the meter movement. Makes the meter burn-out proof in a properly constructed instrument.

Quality components are used throughout — 1% precision resistors in the multiplier circuit — conservatively rated power transformer — Simpson meter movement — excellent positive detent, smooth acting switches — sturdy cabinet, etc.


And you can make a tremendous range of measurements — 1/2V to 1000V AC, 1/2V to 1000V DC, .1 to over 1 billion ohms, and DB. Has mid-scale zero level marking for quick FM alignment. DB scale in red for easy identification — all other scales a sharp, crisp black for easy reading.

A four position selector switch allows operator to rapidly set the instrument for type or reading desired — positions include ACV, DC+V, DC-V, and Ohms. DC — position allow negative voltage to be rapidly taken. Zero adjust and ohms adjust controls are conveniently located on front panel.

Enjoy the numerous advantages of using a VTVM. Its high input impedance doesn't "load" circuits under test — therefore, assures more accurate and dependable readings in high impedance circuits such as resistance coupled amplifiers, AVC circuits, etc. Note the 30,000 VDC probe kit and the RF probe kit — available at low extra cost and specially designed for use with this instrument. With these two probes, you can make DC voltage measurements up to 30,000V, or make RF measurements — added usefulness to an already highly useful instrument.

The instruction manual is absolutely complete — contains a host of figures, pictorials, schematic, detailed step-by-step instructions, and circuit description. These clear, detailed instructions make assembly a cinch.

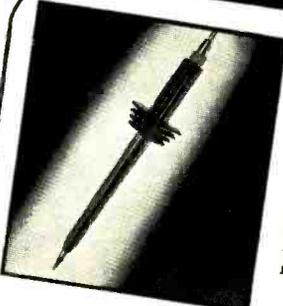And every part is included — meter, all controls, pilot light, switches, test leads, cabinet, instruction manual, etc.




Heathkit 30,000V DC PROBE KIT

A new 30,000 V DC Probe Kit to handle high voltages with safety. For TV service work and all other high voltage applications. Sleek looking — and color molded plastic — Red body and guard — jet black handle. Comes with connector, cable, and PL55 type 300V plugs into Heathkit VTVM so that 300V scale is conveniently multiplied by 100. Can be used with any standard 11 megohm VTVM.

\$550

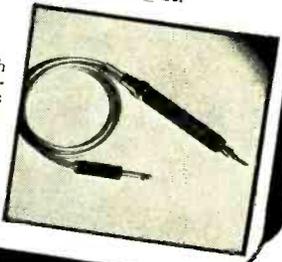No. 336 High Voltage Probe Kit
Shipping Wt. 2 lbs.



Heathkit RF PROBE KIT

This RF Probe Kit comes complete with probe housing, crystal diode detector, connector, lead and plug and all other parts plus clear assembly instructions. Extends range of Heathkit VTVM to 250 Mc. ± 10%. Works on any 11 megohm input VTVM. Specify No. 309 RF Probe Kit.

\$550

Ship. Wt. 1 lb.

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
12 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARLAB-N.Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

Heathkit SIGNAL GENERATOR KIT

Model SG-6
Shipping Wt. 7 lbs.

The new Heathkit Signal Generator Kit has dozens of improvements. Covers the extended range of 160 Kc to 50 megacycles on fundamentals and up to 150 megacycles on useful calibrated harmonics; makes this Heathkit ideal as a marker oscillator for TV. Output level can be conveniently set by means of both step attenuator and continuously variable output controls. Instrument has new miniature HF tubes to easily handle the high frequencies covered.

Uses 6C4 master oscillator and 6C4 sine wave audio oscillator. The kit is transformer operated and a husky selenium rectifier is used in the power supply. All coils are precision wound and checked for calibration making only one adjustment necessary for all bands.


New sine wave audio oscillator provides internal modulation and is also available for external audio testing. Switch provided allows the oscillator to be modulated by an external audio oscillator for fidelity testing of receivers. Comes complete, all tubes, cabinet, test leads, every part. The instruction manual has step-by-step instructions and pictorials. It's easy and fun to build a Heathkit Model SG-6 Signal Generator.



Heathkit CONDENSER CHECKER KIT

Only
\$19.50

Model C-2
Shipping Wt. 6 lbs.

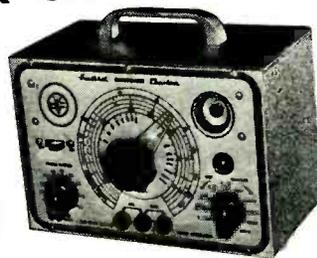

Checks all types of condensers — paper — mica — ceramic — electrolytic. All condenser scales are direct reading and require no charts or multipliers. Covers range of .00001 MFD to 1000 MFD. A Condenser Checker that anyone can read. A leakage test and polarizing voltage for 20 to 500 V provided. Measures re-power factor of electrolytics between 0% and 50% and reads resistance from 100 ohms to 5 megohms. The magic eye indicator makes testing easy.

The kit is 110V 60 cycle transformer operated and comes complete with rectifier tube, magic eye tube, cabinet, calibrated panel and all other parts. Has clear detailed instructions for assembly and use.

NEW Heathkit SIGNAL TRACER AND UNIVERSAL TEST SPEAKER KIT

\$19.50

Model T-2
Shipping Wt. 7 lbs.



The popular Heathkit Signal Tracer has now been combined with a universal test speaker at no increase in price. The same high quality tracer follows signal from antenna to speaker — locates intermittents — finds defective parts quicker — saves valuable service time — gives greater income per service hour. Works equally well on broadcast, FM, or TV receivers. The test speaker has an assortment of switching ranges to match either push-pull or single output impedances. Also tests microphones, pickups and PA systems. Comes complete: cabinet, 110V 60 cycle power transformer, tubes, test probe, all necessary parts, and detailed instructions for assembly and use.



Model TC-1
Shipping Wt. 12 lbs.

\$29.50

Heathkit TUBE CHECKER KIT

The Tube Checker is a MUST for radio repair men. Often customers want to SEE tubes checked, and a checker like this builds customer confidence. In your repairing, you will have a multitude of tubes to check — quickly. The Heathkit tube checker will serve all these functions — it's good looking (with a polished birch cabinet and an attractive two color panel) — checks 4, 5, 6, 7 prong Octals, Loctals, 7 prong miniatures, 9 prong miniatures, pilot lights, and the Hytron 5 prong types. AND IT'S FAST TO OPERATE — the gear driven, free-running roll chart lists hundreds of tubes, and the smooth acting, simplified switching arrangement gives really rapid set-ups.

The testing arrangement is designed so that you will be able to test new tubes of the future — without even waiting for factory data — protection against obsolescence.

You can give tubes a thorough testing — checks for opens, shorts, each element individually, emission, and for filament continuity. A large BAD-?-GOOD meter scale is in three colors for easy reading and also has a "line-set" mark.

You'll find this tube checker kit a good investment — and it's only \$29.50.

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARLAR, N.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

New LABORATORY LINE HEATHKITS



MODEL AV-1
Shipping weight 5 lbs.

\$29⁵⁰

Now — as a Heathkit — at a price anyone can afford, an AC VTVM. A new kit to make possible those sensitive AC measurements required by audio enthusiasts, laboratories, and experimentors. Here is the kit that the audio men have been looking for. Its tremendous range of coverage makes possible measurements of audio amplifier frequency response — gain or loss of audio stages — characteristics of audio filters and attenuators — hum investigation — and literally a multitude of others. Ten ranges consisting of full scale .01, .03, .1, .3, 1, 3, 10, 30, 100, 300 volts RMS assure easy and more accurate readings. Ten ranges on DB provide for measurements from -52 to +52 DB. Frequency response within 1 DB from 20 cycles to 50 KC.

The ingenious circuitry incorporates precision multiplier resistors for accuracy, two amplifier stages using miniature tubes, a unique bridge rectifier meter circuit, quality Simpson meter with 200 microampere movement, and a clean layout of parts for easy wiring. A high degree of inverse feedback provides for stability and linearity.

Simple operation is accomplished by the use of only one control, a range switch which changes the voltage ranges in multiples of 1 and 3, and DB ranges in steps of 10.

The instrument is extremely compact, cabinet size — 4 1/8" deep x 4-11/16" wide x 7 3/8" high, and the newly designed cabinet makes this the companion piece to the VTVM. For audio work, this kit is a natural.

NEW Heathkit AUDIO FREQUENCY METER KIT

MODEL AF-1
Shipping weight 12 lbs.



\$34⁵⁰

A NEW Heathkit Audio Frequency Meter — the ideal instrument for determining frequencies from 20 cycles to 100 KC. Set the selector switch to the proper range — feed the signal into the input terminals — and read the frequency from the meter — completely simple to operate, and yet dependable results.

Quality Simpson 200 microampere meter has two plainly marked scales (0-100 0-300). These scales, read in conjunction with the seven position selector switch, give full scale readings of 100, 300, 1000, 3000, 10,000, 30,000, and 100,000 cycles. Convenient ranges for fast and easy readings.

For greatest accuracy, the 1-3-10 ratio of ranges is maintained and each range has individual calibrating control.

Input impedance is high (1 megohm) and a change in signal voltage between 2 and 300V can be fed directly into the instrument reading. In addition, input wave shape is not critical (the unit will read the frequency of either sine wave or square wave input).

The tube complement consists of a 6SJ7 amplifier and clipper, 6V6 amplifier and clipper, 6H6 meter pulse rectifier, 6X5 power supply rectifier, and OD3/VR150 voltage regulator.


Construction is simple, and quality components are used throughout.

NEW Heathkit INTERMODULATION ANALYZER KIT

Intermodulation testing of audio equipment is rapidly being accepted by more and more engineers and audio experts as the best way to determine the characteristics of audio amplifiers, recording systems, networks, etc. — shows up those undesirable characteristics which contribute to listening fatigue when all other methods fail.

The Heathkit Intermodulation Analyzer supplies a choice of two high frequencies (3000 cycles and a higher frequency (60 cycles) and one low frequency (60 cycles). Both 1:1 or 4:1 ratios of low frequencies can be set up for IM testing, and the ratios are easily set by means of a panel control and the instrument's own VTVM. An output level control supplies the mixed signal at the desired level with an output impedance of two thousand ohms. The Analyzer section has input level control and proper filter circuits feeding the instrument's VTVM to read intermodulation directly on full scale ranges of 30%, 10% and 3%. Built-in power supply furnishes all necessary voltages for operating the instrument.

You won't want to be without this new and efficient means of testing.

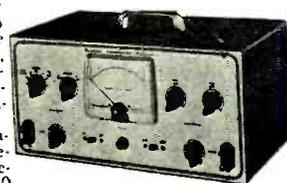

MODEL IM-1
Shipping wt. 18 lbs.

\$39⁵⁰

NEW Heathkit SQUARE WAVE GENERATOR KIT

The new Heathkit Square Wave Generator Kit with its 100 KC square wave opens an entirely new field of audio testing. Square wave testing over this wide range will quickly show high and low frequency response characteristics of circuits — permit easy adjustment of high frequency compensating networks used in video amplifiers — identify ringing in circuits — demonstrate transformer characteristics, etc.

The circuitry consists of a multivibrator stage, a clipping and squaring stage, and a cathode follower output stage. The power supply is transformer operated and utilizes a full wave rectifier tube with 2 sections of LC filtering.

As a multivibrator cannot be accurately calibrated, a provision is provided to allow the instrument to be accurately synchronized with an accurate external source when extreme accuracy is required.

The low impedance output is continuously variable between 0 and 25 volts and operation is simple. You'll really appreciate the wide range of this instrument, 10 cycles to 100 kilocycles — continuously variable. Kit is complete with all parts and instruction manual, and is easy to build.



MODEL SQ-1
Shipping wt. 14 lbs.

\$29⁵⁰

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARKAP, N. Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

Heathkit IMPEDANCE BRIDGE KIT



Model 1B-1B
Shipping Wt. 15 lbs.

\$69⁵⁰

This Impedance Bridge Kit is really a favorite with schools, industrial laboratories, and serious experimenters. An invaluable instrument for those doing electrical measurements work. Reads resistance from .01 Ohms to 10 meg., capacitance from .00001 to 100 MFD, inductance from 10 microhenries to 100 henries, dissipation factor from .002 to 1, and storage factor from 1 to 1000. And you don't have to worry about selecting the proper bridge circuit for the various measurements—the instrument automatically makes the correct circuit when you set up for taking the measurement you want. Bridge utilizes Wheatstone, Hay, Maxwell, and capacitance comparison circuits for the wide range and types of measurements possible. And it's self powered—has internal battery and 1000 cycle hummer. No external generator required—has provisions for external generator if measurements at other than 1000 cycles are desired. Kit utilizes only highest quality parts, General Radio main calibrated control.

Mallory ceramic switches, excellent 200 microamp zero center galvanometer, laboratory type binding posts with standard 3/4 inch centers, 1% precision ceramic-body type multiplier resistors, beautiful birch cabinet and ready calibrated panel. (Headphones not included.)

Take the guesswork out of electrical measurements—order your Heathkit Impedance Bridge kit today—you'll like it.

Heathkit LABORATORY RESISTANCE DECADE KIT



\$19⁵⁰

Shipping Wt. 4 lbs.

An indispensable piece of laboratory equipment—the Heathkit Resistance Decade Kit gives you resistance settings from 1 to 99,999 ohms IN ONE OHM STEPS. For greatest accuracy, 1% precision ceramic-body type resistors and highest quality ceramic wafer switches are used.

Designed to match the Impedance Bridge above, the Resistance Decade Kit has a beautiful birch cabinet and attractive panel. It's easy to build, and comes complete with all parts and construction manual.

Heathkit LABORATORY POWER SUPPLY KITS

Limits:

No load	Variable	150-400V DC
25 MA	Variable	30-310V DC
50 MA	Variable	25-250V DC

Higher loads: Voltage drops off proportionally



\$29⁵⁰

Model PS-1... Ship. Wt. 20 lbs.

Every experimenter needs a good power supply for electronic setups of all kinds. This HV supply and a 6.3 V filament voltage source. Voltage control allows selection of HV output desired (continuously variable within limits outlined), and a Volts-Ma meter scale indicates either DC voltage output in Volts or DC current output in Ma. (Range of meter 0-500V D.C., 0-200 Ma. D.C.) Instrument has convenient stand-by position and pilot light.

Comes with power transformer, filament transformer, meter, 5Y3 rectifier, two 1619 control tubes, completely punched and formed chassis, panel, cabinet, detailed construction manual, and all other parts to make the kit complete.

Heathkit ECONOMY . . . 6 WATT AMPLIFIER KIT



Model A-4
Ship. Wt. 8 lbs.

\$12⁵⁰

No. 304 12 inch speaker . . . **\$6.95**

This fine Heathkit Amplifier was designed to give quality reproduction and yet remain low in price. Has two preamp stages, phase inverter stage, and push-pull beam power output. Comes complete with six tubes, quality output transformer (to 3-4 ohm voice coil), husky cased power transformer and all other parts. Has tone and volume controls. Instruction manual has pictorial for easy assembly. Six watts output with response flat $\pm 1\frac{1}{2}$ db from 50 to 15,000 cycles. A quality amplifier kit at a low price. Better build one.

Heathkit HIGH FIDELITY . . . 20 WATT AMPLIFIER KIT



\$33⁵⁰

Shipping Wt. 18 lbs.

Our latest and finest amplifier—the model A-6 (or A-6A) is capable of a full 20 Watts of high fidelity output—good faithful reproduction made possible through careful circuit design and the use of only highest quality components. Frequency response within ± 1 db from 20-20,000 cycles. Distortion at 3 db below maximum power output (at 1000 cycles) is only .8%. The power transformer is rugged and conservatively rated and will deliver full plate and filament supply with ease. The output transformer was selected because of its exceptionally good frequency response and wide range of output impedances (4-8-16-150-600 ohms). Both are Chicago Transformers in drawn steel case for shielding and maximum protection to windings. The unit has dual rone controls to set the output for the tonal quality desired—treble control attenuates up to 15 db at 10,000 cycles—bass control gives bass boost up to 10 db at 50 cycles.

Tube complement consists of 5U4G rectifier, 6SJ7 voltage amplifier, 6SN7 amplifier and phase splitter, and two 6L6's in push-pull output. Comes complete with all parts and detailed construction manual. (Speaker not included.)

MODEL A-6: For tuner and crystal phono inputs. Has two position selector switch for convenient switching to type of input desired.

MODEL A-6A: Features an added 6SJ7 stage (preamplifier) for operating from variable reluctance cartridge phono pickup, mike input, and either tuner or standard crystal phono pickup. A three position selector switch provides flexible switching. **\$35.50**

Shipping Wt. 18 lbs.

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (16)
CABLE: ARLAB-N.Y.

The HEATH COMPANY

. . . BENTON HARBOR 20, MICHIGAN

RADIO-ELECTRONICS

NEW 1952 *Heathkit* BATTERY ELIMINATOR KIT



\$24.50

Model BE-3
Shipping Wt. 17 lbs.

- Can be used as battery charger.
- Continuously variable output 0 - 8 Volts — not switch type.
- Heavy duty Mallory 17 disk type magnesium copper sulfide rectifier.
- Automatic overload relay for maximum protection. Self-resetting type.
- Ideal for battery, aircraft and marine radios.
- Dual Volt and Ammeters read both voltage and amperage continually — no switching.

The new Heathkit Model BE-2 incorporates the best. Continuously variable output control is of the variable transformer type with smooth wiper type contacts. There are no switches or steps and voltage between 0 and 8 Volts is available at 10 Amperes continuous and 15 Amperes intermittent. Maximum safety from overloads and shorts provided by automatic overload relay which resets itself when overload is removed.

The new rectifier is a 17 plate Mallory magnesium copper sulfide type. This is the most rugged type available for long trouble-free use. Output is continuously metered by both a 0 - 10 Volt Voltmeter and a 0 - 15 Amp Ammeter. Shorted vibrators indicated instantly by ammeter.

Equip now for all types of service — aircraft — marine — auto and battery radios — this inexpensive instrument vastly increases service possibilities — better be ready when the customer walks in.

NEW *Heathkit* SINE AND SQUARE WAVE AUDIO GENERATOR KIT

Designed with versatility, usefulness, and dependability in mind, the AG-7 gives you the two most needed wave shapes right at your fingertips — the sine wave and the square wave.

The range switch and plainly calibrated frequency scale give rapid and easy frequency selection, and the output control permits setting the output to any desired level.

A high-low impedance switch sets the instrument for either high or low impedance output — on high to connect a high impedance load, and on low to work into a low impedance transformer with negligible DC resistance.

Coverage is from 20 to 20,000 cycles, and distortion is at a minimum — you can really trust the output wave shape.

Six tubes, quality 4 gang tuning condenser, power transformer, metal cased filter condenser, 1% precision resistors in the frequency determining circuit, and all other parts come with the kit — plus, a complete construction manual — A tremendous kit, and the price is truly low.



Model AG-7
Shipping Wt. 15 lbs.
\$34.50

THE NEW *Heathkit* HANDITESTER KIT

A precision portable volt-ohm milliammeter. Uses only high quality parts — All precision 1% resistors, three deck switch for trouble-free mounting of parts, specially designed battery mounting bracket, smooth acting ohm adjust control, beautiful molded bakelite case, 400 micro-amp meter movement, etc.

DC and AC voltage ranges 10 - 30 - 300 - 1000 - 5000V. Ohms range 0 - 3000 and 0 - 300,000. Range Milliamperes 0 - 10 Ma, 0 - 100 Ma. Easily assembled from complete instructions and pictorial diagrams.



\$13.50
Model M-1
Shipping Wt. 3 lbs.

NEW *Heathkit*

T.V. ALIGNMENT GENERATOR KIT

Here is an excellent TV Alignment Generator designed to do TV service work quickly, easily, and properly. The Model TS-2 when used in conjunction with an oscilloscope provides a means of correctly aligning television receivers.

The instrument provides a frequency modulated signal covering, in two bands, the range of 10 to 90 Mc. and 150 to 230 Mc. — thus, ALL ALLOCATED TV CHANNELS AS WELL AS IF FREQUENCIES ARE COVERED.


An absorption type frequency marker covers from 20 to 75 Mc. in two ranges — therefore, you have a simple, convenient means of frequency checking of IF's, independent of oscillator calibration.

Sweep width is controlled from the front panel and covers a sweep deviation of 0-12 Mc. — all the sweep you could possibly need or want.

And still other excellent features are: Horizontal sweep voltage available at the front panel (and controlled with a phasing control — both step and continuously variable attenuation for setting the output signal to the desired level — a convenient instrument stand-by position — vernier drive of both oscillator and marker tuning condensers — and blanking for establishing a single trace with base reference level. Make your work easier, save time, and repair with confidence — order your Heathkit TV Alignment Generator now!

Model TS-2
Shipping Wt. 20 lbs.

\$39.50

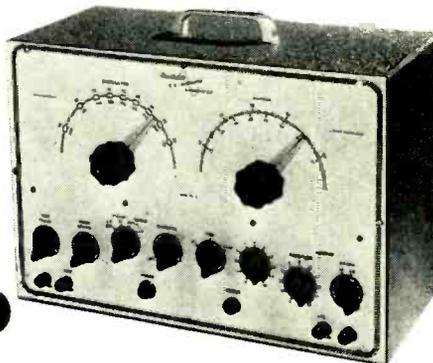

YOU SAVE BY ORDERING DIRECT FROM MANUFACTURER—USE ORDER BLANK ON LAST PAGE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
15 E. 40th St.
NEW YORK, CITY (16)
CABLE: ARIRAN.Y.

The **HEATH COMPANY**

... BENTON HARBOR 20, MICHIGAN

Heathkit RECEIVER & TUNER KITS for AM and FM



Model BR-1 Broadcast Model Kit covers 550 to 1600 Kc. Shipping Wt. 10 lbs.

\$19.50



Model AR-1 3 Band Receiver Kit covers 550 Kc. to over 20 Mc. continuous. Extremely high sensitivity. Shipping Wt. 10 lbs.

\$23.50

TWO HIGH QUALITY *Heathkit* SUPERHETRODYNE RECEIVER KITS

Two excellent Heathkits. Ideal for schools, replacement of worn out receivers, amateur and custom installations.

Both are transformer operated quality units. The best of materials used throughout—six inch calibrated slide rule dial—quality power output transformers—dual iron core shielded. I.F. coils—metal cased filter condenser. The chassis has phono input jacks. 110 Volt output for phono motor and there is a phono-radio switch on panel. A large metal panel simplifying installation in used console cabinets is included. Comes complete with tubes and instruction manual incorporating pictorials and step-by-step instructions (less speaker and cabinet). The three band model has simple coil turret which is assembled separately for ease of construction.



Model FM-2
Ship. Wt. 9 lbs.

\$22.50

TRUE FM FROM *Heathkit* FM TUNER KIT

The Heathkit FM Tuner Model FM-2 was designed for best tonal reproduction. The circuit incorporates the most desirable FM features—true FM.

Utilizes 8 tubes: 7E5 Oscillator, 6SH7 mixer, two 6SH7 IF amplifiers, 6SH7 limiter, two 7C4 diodes as discriminator, and 6X5 rectifier.

The instrument is transformer operated making it safe for connection to any type receiver or amplifier. Has ready wound and adjusted RF coils, and 2 stages of 10.7 Mc IF (including limiter). A calibrated six inch slide rule dial has vernier drive for easy tuning. All parts and complete construction manual furnished.



MAIL TO THE
HEATH COMPANY
BENTON HARBOR 20,
MICHIGAN

ORDER BLANK

From _____

SHIP VIA

- Parcel Post
- Express
- Freight
- Best Way

Quantity	Item	Price	Quantity	Item	Price
	Heathkit Oscilloscope Kit — Model O-7			Heathkit H.V. Probe Kit — No. 336	
	Heathkit VTVM Kit — Model V-5			Heathkit R.F. Signal Gen. Kit — Model SG-6	
	Heathkit FM Tuner Kit — FM-2			Heathkit Condenser Checker Kit — Model C-2	
	Heathkit Broadcast Receiver Kit — Model BR-1			Heathkit Handitester Kit — Model M-1	
	Heathkit Three Band Receiver Kit—Model AR-1			Heathkit Power Supply Kit — Model PS-1	
	Heathkit Amplifier Kit — Model A-4			Heathkit Resistance Decade Kit — Model RD-1	
	Heathkit Amplifier Kit — Model A-6 (or A-6A)			Heathkit Impedance Bridge Kit — Model IB-1B	
	Heathkit Tube Checker Kit — Model TC-1			Heathkit A.C. VTVM-KIT — Model AV-1	
	Heathkit Audio Generator Kit — Model AG-7			Heathkit Intermodul. Analyzer Kit—Model IM-1	
	Heathkit Battery Eliminator Kit — Model BE-2			Heathkit Audio Freq. Meter Kit — Model AF-1	
	Heathkit Electronic Switch Kit — Model S-2			Heathkit Square Wave Gen. Kit — Model SQ-1	
	Heathkit T.V. Alignment Gen. Kit — TS-2				
	Heathkit Signal Tracer Kit — Model T-2				
	Heathkit R.F. Probe Kit — No. 309				

On Parcel Post Orders, include postage for weight shown and insurance. (We insure all shipments.)

On Express Orders, do not include transportation charges—they will be collected by the Express Agency at time of delivery.

Enclosed find Check Money Order for _____

Please ship C.O.D. Postage enclosed for _____ lbs.

ALL PRICES SUBJECT TO CHANGE WITHOUT NOTICE

EXPORT AGENT
ROCKE INTERNATIONAL CORP.
13 E. 40th ST.
NEW YORK CITY (10)
CABLE: ARLAS-N.Y.

The HEATH COMPANY

... BENTON HARBOR 20, MICHIGAN

If no a.c. voltmeter is obtainable, you can find the correct connection by determining which of the two possible connections produces the loudest hum in a pair of headphones connected across R2.

Voltage on the plate of the 2D21 must be out of phase with the a.c. bias voltage across R2. That is, plate voltage is positive when grid bias is negative, and vice versa. Set R2 at the extreme counterclockwise position. Be sure no signal is coming from the amplifier 12AX7 tube. Under these conditions, the 2D21 will fire (relay operates and tube glows blue) when the lead C from the relay is connected to one end of the high-voltage winding, but will not fire when the lead is connected to the other end. Leave the lead on the latter connection. Advancing R2 to the extreme clockwise end should now cause the thyatron to fire. In practice, the control is set so that the 2D21 thyatron almost fires, making the unit quite sensitive.

A word about the microphone—almost any high-level output mike will work nicely. We used the transmitter from an otherwise defective sound-powered handset. An old earphone would do the same job, as would a small loudspeaker with an output transformer attached. A carbon mike (old telephone transmitter) would be O.K., but a mike transformer and battery would be necessary. Constant drain on the battery necessitates frequent replacements. Shield the microphone lead.

An experimenter who has several large tubes in his junk box, but no miniatures, could build the alarm without additional purchases. A 6SL7 or two 6F5's would replace the 12AX7, with different circuit constants as given in the resistance-coupled amplifier section of a tube handbook. An 884 or a 2050 could replace the 2D21, and a 6X5 would do the same job as the 6X4. A 5Y3, 80, or other such rectifier could be used if an additional 6.3-volt winding were available on the transformer to substitute for the 5-volt winding in the bias circuit.

In addition to its function as a telephone alarm, the unit may be used in several other ways. It can be used to signal the ringing of the doorbell, the crying of the baby, or even the arrival of the family car in the garage. Frankly, though, our most enthusiastic user so far is the little two-year-old for whose protection the unit was designed. Does he appreciate our efforts in his behalf? Does he realize the security this little device affords? We wonder—he likes to chatter into the mike and watch the light wink back!

Materials for telephone alarm

Resistors: 1—2.2, 2—1 megohm, 1/2 watt; 2—470,000, 2—220,000, 2—5,600 ohms, 1/2 watt; 1—(Potentiometer) 500 ohms, wire-wound; 1—R1 (see text).
Capacitors: (Paper) 2—0.1 µf, 400 volts; (Electrolytic) 2—10 µf, 450 volts; 1—8 µf, 450 volts; 2—1 µf or larger, 25 volts.
Miscellaneous: Tubes: 1—12AX7, 1—6AL5, 1—2D21, 1—6X4. 4—Tube sockets. 1—A.C. receptacle. 1—Microphone jack. 1—Power transformer, 550 volts c.t., 50 ma; 6.3 volts, 2 amp, 5 volts, 2 amp. 1—Choke, 10 henries, 50 ma or more. 1—Relay, s.p.s.t. normally open contacts (see text). Hookup wire, chassis, hardware, etc.

—end—

WE'RE TELLING THE WORLD ABOUT FEATHERIDE PICK-UP CARTRIDGES


...to build more sales for YOU!

For the first time in pick-up cartridge history, the 5,000,000 readers of two great national magazines... Better Homes & Gardens and Time... will be told that their phonograph or record player needs a new pick-up installed from time to time and that you are the man whom they should seek to furnish and install Webster Electric Featheride Pick-up Cartridges.

Your service problems can be greatly minimized by standardizing on Webster Electric Featheride Pick-up Cartridges. Only two models are required for most replacement jobs; no charts, no manuals are needed. Both models are handsomely packaged in Webster Dri-Pack containers.

A special metal foil seal, which we call Dri-Seal, protects the crystal, adding life to the cartridge and making it practically impervious to moisture. Both models are completely assembled units. They are the most versatile, most competitively priced and practical pick-up cartridges on the market today.

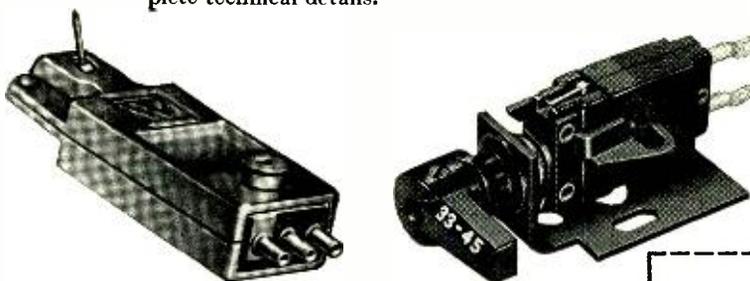The features of these two models are briefly described below. Send the coupon for complete technical details.



Featheride

MODEL WS
Pick-up Cartridge
for 78 RPM

1. Special 3-terminal construction provides dual output... 4.0 v. or 1.5 v.
2. Factory assembled, ready for use.
3. Matching osmium-tipped needle furnished.
4. Fits any standard 1/2-in. RTMA mounting.

Featheride

MODEL AX
Pick-up Cartridge
for 33 1/2, 45 and 78 RPM

1. Completely factory assembled in positive-action twist bracket.
2. Bracket easily removed for integral-twist-mechanism tone-arm installation.
3. Two matching osmium-tipped needles furnished.
4. Fits standard 1/2-in. RTMA mountings.

WEBSTER ELECTRIC
RACINE • WISCONSIN

"Where Quality is a Responsibility and Fair Dealing an Obligation"

Webster Electric Company, Clark and DeKoven Sts., Racine, Wis.
 Please send me technical data on Featheride Pick-up Cartridges for replacement use.


Name _____ (Please print)
 Address _____
 City _____ State _____ Zone _____
 Jobber Service Technician Other

MATTISON SILVER ROCKET 630 CHASSIS With • TUNEABLE • BUILT-IN BOOSTER for Better DX Reception

Featuring NEW Super CASCODE
Tuner and 70° COSINE YOKE
for edge to edge focus!

Tube
Complement:
28 tubes
3 rectifiers
1 CRT

32

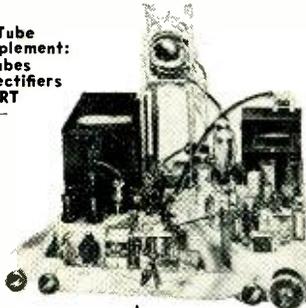


All Channel Booster

- Broad band—single knob control pre-amplifier built in to eliminate long leads which may cause regeneration and attenuation of signal.
- ONLY THE MATTISON 630 CHASSIS HAS AN ALL CHANNEL TUNEABLE BUILT-IN BOOSTER THAT INCREASES SIGNAL STRENGTH UP TO 10 TIMES. THE SILVER ROCKET WILL OUT-PERFORM ANY CHASSIS MADE AND IS PRICED RIGHT TO SELL FAST WITH AN EXTRAORDINARY MARGIN OF PROFIT FOR YOU. WRITE FOR CONFIDENTIAL PRICE SCHEDULE.

All
CABINETS
MADE IN
MATTISON'S
OWN
CABINET
FACTORY!

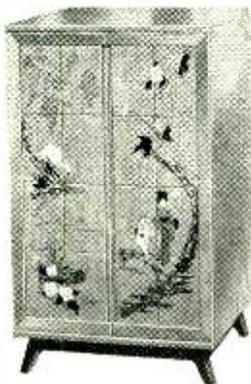The "Chinese
Quadrille" is
only one of 36
breath-taking
cabinets.



FREE! Write for MATTISON'S mer-
chandising portfolio explaining:
"THE MATTISON
UNASSEMBLED PLAN"
and
"THE MATTISON
\$1,000,000 FLOOR PLAN"



Manufactured with integrity

Write for the name
of your MATTISON
distributor nearest
you. NO OBLIGA-
TION!

Mattison Television & Radio Corp.
893 Broadway, Dept. E, N. Y. 3, N. Y.

EARLY WARNING PLANE DETECTION SYSTEM

Patent No. 2,571,386

David Sarnoff, New York, N. Y. (assignor to
the Radio Corporation of America).


The purpose of this invention is to obtain information on enemy raiders or guided missiles at a sufficiently early moment to permit intercepting raiders, jamming the control signals of guided missiles, sending out counter-aircraft, or otherwise deflecting or destroying the attackers.

It provides a system wherein a number of radio-relay carrying aircraft are to follow each other at regular intervals over a given course (say between Newfoundland and England). They would be kept on the same beam by directive transmitters at the shore stations at each end of the flight course and by directive receivers and transmitters on each plane. Thus a straight line would be maintained over the whole course, though planes near the center of the flight would be out of range of the shore stations. A typical defense setup of this type could consist of a

stream of planes in which each would fly about 250 miles behind the other.

Each of these planes would carry radar detection apparatus, and could relay information picked up on the radar equipment immediately to the shore station by way of the other planes in the string, thus warning of attackers much earlier than could any shore-based station.

The patent, which covers six pages of text and seven pages of drawings, suggests a number of other possibilities, such as parasite planes attached to the patrol craft. Should enemy planes or missiles approach, the parasites would be launched to intercept them. The use of Ultrafax and Teleran is also mentioned as means of obtaining more rapid or complete information on given strategic situations, and relaying it to its final destination with the utmost efficiency.

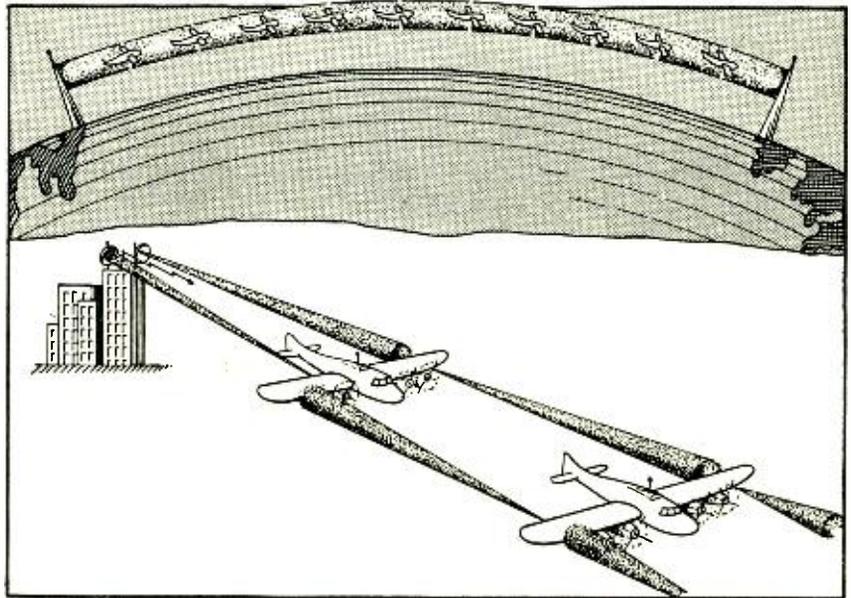

COSMIC RAY ALTIMETER

Patent No. 2,573,823

John W. B. Barghausen, Mt. Rainier
and James A. Van Allen, Silver Spring, Md.


(Assigned to the U.S. Government
as represented by the Secretary of the Navy)

This instrument is effective at heights of 3 to 20 miles above sea level. Geiger counters measure the cosmic ray intensity which increases with height and becomes nearly constant 20 miles up. Results are accurate within 1,000 ft. An ordinary barometric altimeter is unreliable above 3 miles due to the low and nearly constant pressure.

The Geiger counters (GC) are arranged in two groups, one above the other. The groups are sepa-

rated by a lead barrier (L) about 3/4 inch thick. Several counters are used to average out possible error. Each anode is polarized by a positive 1,000-volt source (not shown). The upper group of counters feeds through channel V1 and V3. The lower group is connected through V2 and V4. Tubes V1 and V2, cathode followers, do not reverse the polarity of a signal.

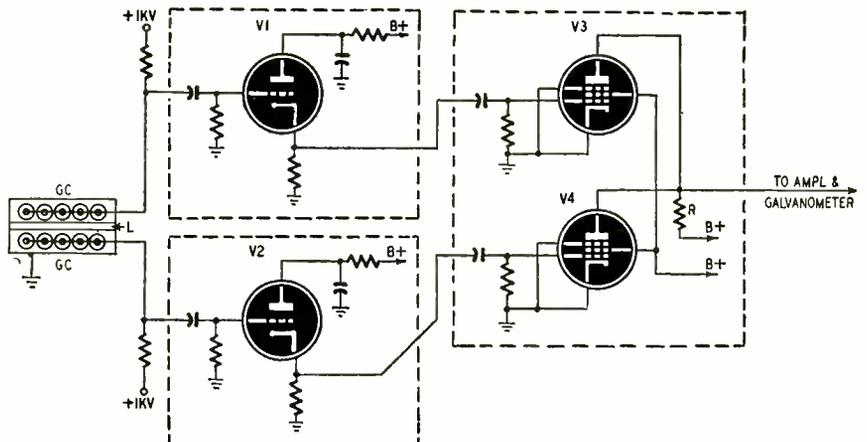A Geiger counter output consists of negative



pulses. These are fed, as shown, to separate tubes. The negative pulse outputs of these tubes are connected to pentodes V3, V4 which comprise a coincidence stage. If either tube is pulsed, there is practically no change in the plate current through R. For example, if V3 is pulsed negatively, this tube is blocked but there is a rise in plate voltage at V4. Therefore the latter tube passes more current and there is little net change in the voltage drop across R. However, when V3 and V4 are pulsed *simultaneously* both are blocked and a positive pulse is transmitted. The pulse is amplified and indicated on a damped galvanometer to show the average count.

Cosmic rays penetrate the lead barrier at high speed so both groups of counters are energized almost simultaneously. But if other types of radiation are also present they will not register.


MAGNETIC TAPE REPRODUCER

Patent No. 2,574,708

Michael Rettinger, Encino, Calif.

(Assigned to Radio Corp. of America)

This pickup works capacitively rather than by the conventional magnetic method. The usual reproducer includes a playback winding in which a voltage is induced as the tape moves past. This voltage is proportional to frequency. With the same magnetization, for example, the output voltage is greater at higher frequencies. Therefore an equalizer is needed to restore acoustic balance. The new pickup does not need an equalizer.

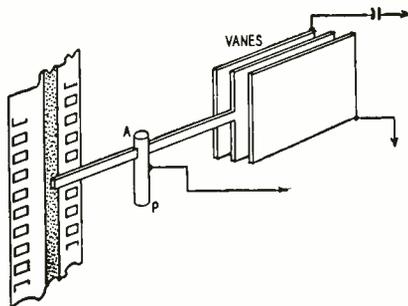

An iron armature A is pivoted at P and carries a flat vane at the far end. Two fixed plates are on either side of the movable vane. When a magnetized tape (shown with sprocket holes) moves past A, the armature vibrates. The motion of the center vane produces a varying capacitance proportional to the tape magnetization.

An oscillator-discriminator transforms the capacitance changes to variations of voltage. The present patent does not cover such a circuit. If desired, the capacitance changes may be used to frequency-modulate an oscillator. This produces FM which may be detected in the usual way.

TV SOUND SEPARATOR


Patent No. 2,574,259

Harold Goldberg, Towson, Md.

(Assigned to Bendix Aviation Corp.)

This network rejects the sound channel while passing a wide video band. Rejection is greater than 40 db at the undesired frequency. The network may be aligned without a sweep generator. The adjustments are not interdependent.

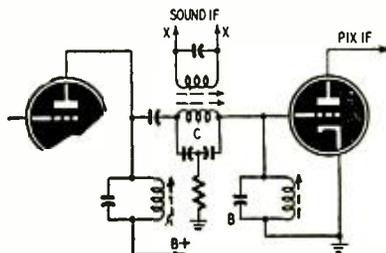A and B are parallel-resonant circuits. One is tuned slightly higher than the center of the pix i.f., and the other slightly lower. This extends the pix pass-band. C is a bridged-T circuit tuned to the sound channel. When set for null, the bridged-T eliminates the sound from succeeding pix stages. However, this sound energy appears across C and terminals X which feed the sound i.f. strip.



WELCOME, BROTHER 'VARI'!
Many Servicemen want your New Micrometer Adjustment and Snap-in Mount!

GLAD TO JOIN THE CAUSE, BROTHER 'FERRI'!
You've done a wonderful job for 100,000 sets in only 5 months!

NOW THERE ARE 2 GRAYBURNE Loopsticks!

FERRI-LOOPSTICK and VARI-LOOPSTICK

Grayburne Loopsticks, with magic Ferrite cores, obsolete conventional radio loops, improve reception amazingly over entire broadcast band, and pull in hard-to-get stations that normally can't be heard with ordinary loops.

Highest Sensitivity: Average Q is 250, unaffected by adjacent metallic or inductive elements.

Omni-Directional: Equally sensitive and efficient at every angle. No more turning or moving receivers to get better reception.

Greater Receiving Range: Greater, more uniform amplification over a wider frequency range—all at higher signal-to-noise ratio.

Performance-Proved: After comparative tests, service dealers coast to coast have bought 100,000 Loopsticks in only 5 months!

FERRI-LOOPSTICK: Just set and forget! For permanent installations, new or replacement, where user desires to make no further changes once Loopstick has been set for maximum overall efficiency. **List 75¢.**


VARI-LOOPSTICK: Has advantages of Micrometer Adjustment and one-hole Snap-in Mount! For peaking efficiency on several stations consecutively, station jumpers and DX tuners. Peak resonance for any station is quickly obtained. **List \$1.00.**

Write for name of your nearest Grayburne distributor and free booklet "Ferrites and Their Applications."

the world's most sensitive, compact and efficient **Small Radio Antennas at Low Cost!**

shown actual size

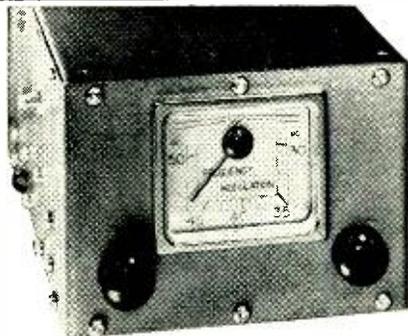GRAYBURNE CORPORATION, 103 Lafayette St., New York 13, N. Y.



Model M-51

for emergency communications

USED BY HUNDREDS OF MUNICIPALITIES FROM BOSTON, MASS., TO ALHAMBRA, CAL.

POLICALARM MONITORADIO

Says S. L. Grant, City Manager, Winchester, Virginia . . .

"I think you have a receiver that is well built, and I see no reason why it should not be in demand by all public works departments that have a transmitter available."



Users of FM 2-Way Radio Communications equipment throughout the entire nation, find Polic-Alarm and Monitoradio a welcome innovation to low-cost mobile communications radio .

5 Models For All Systems

6 VOLT MOBILE
M-51 Tuneable 30-50 MC
M-8 Tuneable 152-163 MC

115 VOLT AC-DC
PR-31 Tuneable 30-50 MC
PR-8 Tuneable 152-163 MC
AIRCRAFT
AR-1 AM Tuneable 108-132 MC
115 Volt AC-DC

For Complete Information: See Your Jobber—Or Write Us Today

RADIO APPARATUS CORPORATION

55 N. NEW JERSEY ST., INDIANAPOLIS 4, IND., PHONE: ATLANTIC 1624

for flawless reproduction
NO OTHER CARTRIDGE CAN PERFORM LIKE A PICKERING
Pickering patented design
 provides **DYNAMIC COUPLING***
 throughout the entire audible range

*** DYNAMIC COUPLING ASSURES**

- constant stylus contact with the record grooves over the entire audio spectrum (20-20,000 cps)
 - full frequency response
 - full transient response
- NO RESONANCES
 NO MISTRACKING
 NO GRINDING OF GROOVE WALLS**

Pickering Cartridges transmit all of the sounds in the musical spectrum, without loss of definition, just as a fine optical lens passes all of the colors in the rainbow.

For literature address Dept. P

Well-informed engineers and technicians, schooled in the science of electro-mechanics, know that only wide-range frequency response provides full transient response; the electronic phenomena which enables the reproduction of orchestral music with all the subtle sounds that give each musical instrument its individual character.

Pickering engineers and designers have but one objective . . . to produce products that will please the music lovers' insatiable appetite for the flawless recreation of recorded music . . . for the utmost in quality insist upon Pickering Audio Components.

Pickering
 & COMPANY, INCORPORATED
 OCEANSIDE, NEW YORK

NOW—Get this expert SELF-TRAINING in RADIO SERVICING

by ABRAHAM MARCUS



co-author of famous "Elements of Radio" which has sold over 800,000 copies!

Here is every detail you need to know about radio repair, replacement, and readjustment. Easy-to-understand, step-by-step self-training handbook shows you how to locate and remedy defects quickly.

Covers: TRF Receivers; Superheterodyne Receivers; Short-Wave Receivers and Converters; Multiband Receivers; Portable Receivers; Automobile Receivers; Communication Receivers; F-M Receivers; Power Supplies operated from AC, DC, Batteries, Motor Generators, etc.

Tells you the HOW and WHY of: **Electron Tubes** (Diode, Triode, Pentode, Beam Power, Thyatron, Phototube, Cathode Ray, etc.); **Rectifier Circuits** (Half-wave, Full-wave, Bridge, Voltage-Doubler, etc.); **Detector Circuits** (Diode, Triode, Regenerative, Superregenerative, Infinite-Impedance, etc.); **Amplifier Circuits** (Audio, Radio, I-F, Video, D-C, etc.); **Oscillator Circuits** (Hartley, Colpitts, Crystal, Transistron, Multivibrator, Sweep-circuit, etc.); **Control Circuits** (Volume, AVC, DAVC, Tone, Noise-Suppression, Automatic Tuning, Automatic Frequency Control, etc.).

All in one big volume — easy to read. 16 Big Chapters. 121 Sections. 400 "Show How" Diagrams. 775 pages of practical radio instruction.

Explains how to use testing instruments such as meter, vacuum-tube voltmeters, ohmmeters, bridges, multimeters, signal generators, tube checkers, cathode-ray oscilloscopes, etc. Over 100 pages and 69 illustrations in this section alone!

Get this authoritative radio repair handbook today! Coupon below brings you "Radio Servicing" on FREE trial for 10 days. Mail it NOW.

PRENTICE-HALL, Inc., Dept. M-RE-352
 70 Fifth Ave., New York 11, N. Y.

Send me, for 10 DAYS' FREE TRIAL, "Radio Servicing," by Abraham Marcus. I will return it in ten days and pay nothing—or keep it and send \$1.95 down (plus postage) and \$2 monthly for 2 months.

Name _____
 Address _____
 City _____ State _____
 () SAVE! Send \$5.95 WITH COUPON—we pay postage.

There is Nothing for us to Add...

...when BROOK AMPLIFIER owners tell the story so much better.

"...absolutely transcendent"
 "It is excellent—better than I had anticipated."
 "10 years of building amplifiers, trying out almost every quality unit on the market, I still have yet to find any unit that even comes close to performance and pure enjoyment—consistent enjoyment to the BROOK."
 "I still think there is nothing quite like the BROOK."

May we suggest that you assemble your home music system around

THE **BROOK**
 ALL TRIODE HIGH QUALITY
AUDIO AMPLIFIER

Write for detailed information, free booklet, "Better Listening," and name of dealer in your locality, Dept. EC-2

BROOK ELECTRONICS, INC.
 34 DeHART PLACE, ELIZABETH 2, N.J.


FM GENERATOR

Patent No. 2,574,647

Robert Lorenzen, New York, N. Y.

(Assigned to Electronic Systems Corp.)

Magnetostriction is utilized to modulate frequency in this generator. It seems to be applicable to phone transmitters, sweep generators, etc. The figure shows a single triode employed as an FM oscillator. A bar of nickel or magnetostrictive alloy is shown near or partly within the tank coil (L). One end of the bar is firmly fixed in position. The other end carries an iron slug (P) insulated from the bar. Two windings magnetize the bar. One carries an a.f. signal, the other uses d.c.

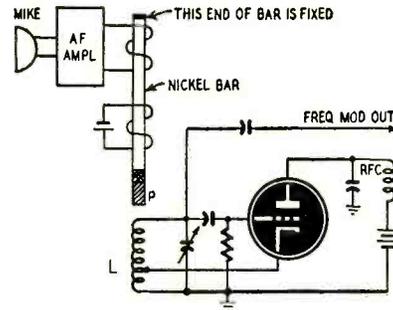

The bar shown here will vibrate longitudinally at an a.f. rate in a magnetic field. The d.c. merely biases the bar magnetically for linear operation. As P vibrates into and out of L, the oscillator frequency varies and produces an FM signal.

If desired, capacitance may be controlled instead of inductance. In this case P is then a high dielectric material and is placed between metal plates. When the nickel bar expands, P moves deeper into the capacitor formed by the metal plates, changing the capacitance.

IMPROVED TRANSISTOR

Patent No. 2,570,978

William G. Pfann, Chatham, N. J.

(Assigned to Bell Telephone Laboratories, Inc.)

This transistor is designed for greater gain, higher input impedance and better efficiency. It may be used as an amplifier or oscillator. The germanium crystal is partly N-type and partly P-

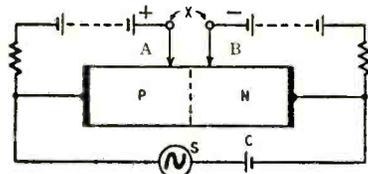


Fig. 1—Transistor used as amplifier.

type as illustrated. Each point contact functions as a combination emitter-collector. A metal plating (shown as a thick line) is used as the base of the transistor. Either separate bases (Fig. 1) or a common element (Fig. 2) may be used.

In Fig. 1, A is biased to emit holes. These positive charges pass through the crystal and are collected by B. On the other hand, B is biased to emit electrons which are collected at A. An a.c. signal S and a d.c. source C control the output across terminals X. The d.c. aids the passage of holes from P to N and of electrons in the opposite direction. The a.c. signal S modulates the flow of both charges.

Fig. 2 shows a transistor connected as an oscillator. The point contacts are coupled by an LC circuit which determines the oscillating frequency. R may be adjusted to control output amplitude.

In both circuits, the boundary between N and P (dotted line) is photo-sensitive. Light falling on this barrier liberates electron-hole pairs and adds to the output.

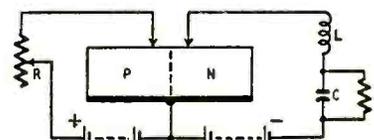


Fig. 2—Transistor oscillator circuit.

ARTSNY RECEIVES GIFT

The Associated Radio-Television Servicemen of New York (City) received a complete set of Oak Ridge test equipment from that company. The gift, which was on hand and formally accepted at their meeting of January 17, will be of great assistance in their work in the new shop-class-clubroom at 165 East Broadway.

The new headquarters has been fitted up with a stage, benches for spectators and a test bench 40 feet long. A couple of old chassis have been obtained, and more test equipment is expected.

The meeting on January 17 was largely occupied with a discussion of the pending licensing legislation. The bankruptcy of Conlan Electric, which had more than 20,000 contracts, was another of the main topics of discussion. Newspaper reports of statements made by Conlan's legal counsel that the company had lost more than \$1,000,000 since going into television, and that the reason for failure was that the rates charged under the contracts were not sufficient to meet the costs of service, attracted special interest.

LONG BEACH ELECTS

Officers of the Long Beach (Cal.) RTA for 1952 are: Fred S. Abrams, president; Les Huckins, vice president; H. L. Brown, secretary; and Clarence Spencer, treasurer.

Elwyn W. Ley was chosen program chairman, and Harry Ward continues as public relations officer, with the assistance of Col. J. C. Hughes and Rod McIntire. Frank Gregson is the new chairman of the membership committee, and Joe Martin was again selected as the association's technical adviser.

A new post, sergeant-at-arms, was created, with Merlyn (Speedy) Cochems at the first incumbent. The past president, Hal Meyers, is handling the job of technical guidance in customer relations. An official photographer, Bob Hayden, was designated.

NESA APPROVES US

We received the following much appreciated letter from the Nebraska Electronic Service Association (NESA) of Lincoln, Nebraska.

"The members of the Nebraska Electronic Service Association very heartily endorse the efforts of RADIO-ELECTRONICS and all its staff for what they are doing for the electronic industry today and also for the information we have received from you in the past."

NESA is now sponsoring a TV service school for the service technicians of the community.

The officers for 1952 are: Eddie Kohl, president; H. M. Tanquary, vice-president; Leslie Ryman, secretary; and Paul Eddy, treasurer.

MOCH PRESIDENT OF TISA

Frank Moch, president of NATESA, has been elected for the fifth time to the presidency of Chicago's Television Installation and Service Association (TISA). Morton Binder was reelected vice president, Reuben Saxner, secretary, and Martin Reese, treasurer.


BUILD THESE RCP KITS!

THEY'RE EASY! . . . PROFESSIONAL! . . . SAVE MONEY!
COMPLETE KITS • NOTHING ELSE TO BUY!

MODEL 345K SUPER VACUUM TUBE VOLTMETER

Features long scale 4 1/2" meter in burn out proof meter circuit—electronic balanced bridge type push pull circuit—negligible current drawn due to high input impedance of 25 megohms—Isolation Probe—center of ohm scale 10 ohms—5 ohmmeter ranges reading from 2 ohms to 1 billion ohms (1000 megohms). 20 voltage ranges 0-1000 volts including AC and DC—Complete D.B. meter.

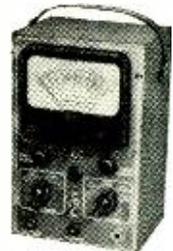Discriminator alignment scale with zero center permitting operation in both directions. Operates on 105-130 volts. 50-60 cycles—Extra heavy panel, case and chassis. Size 10" x 6" x 5". Weight 8 1/2 lbs. Shipping weight 11 lbs. **\$25⁹⁵**



MODEL 322AK TUBE TESTER KIT

Fully engineered to test all recently developed tubes and television types. Has provisions for checking individual sections of multi-purpose tubes as well as miniature and subminiature receiving tubes. Jack for head-phone noise test to check noisy swinging or high resistance internal tube connections. Neon lamp for rapid short and leakage tests between elements. **\$27⁹⁵**



MODEL 447BK MULTI-TESTER KIT

3" square D'Arsonval meter. DC Voltmeter: 0-5-50-250-2500 Volts at 1000 Ohm per Volt. AC Voltmeter: 0-10-100-500-1000 Volts. Output Voltmeter: 0-10-100-500-1000 Volts. DC Milliammeter: 0-1-10-1000 MA. DC Ammeter: 0-1-10 Amperes. Ohmmeter 0-10,000 Ohms—1 Megohm—10 Megohms Ext. Decibel Meter: —8 to +55 decibels. Complete with batteries. **\$13⁹⁵**



ORDER THESE KITS TODAY!

AVAILABLE AT YOUR DISTRIBUTOR—INSIST ON RCP INSTRUMENTS • WRITE FOR CATALOG RE-3

RADIO CITY PRODUCTS CO., INC. 
152 WEST 25th ST — NEW YORK 1, N. Y.

LEARN
Television-Radio Electricity
REFRIGERATION-ELECTRONICS
IN THE GREAT SHOPS OF **COYNE**

TRAIN QUICKLY! OLDEST, BEST EQUIPPED SCHOOL of ITS KIND in U.S.
Young and Older Men . . .

Come to the Great Shops of Coyne in Chicago. Get practical training in TELEVISION-RADIO or ELECTRICITY—vital in Defense Program. Prepare now for a better job or better service rating.

START NOW—PAY LATER
You can finance most of your tuition, pay for it later in easy monthly payments. Special plan for men of Draft Age. Part time employment service available.

FREE BOOK Clip coupon for Big Free Illustrated Book. Indicate below, course that interests you. No salesman will call. Act NOW.

COYNE 
ELECTRICITY ★ TELEVISION
RADIO ★ REFRIGERATION ★ ELECTRONICS

B. W. COOKE, Pres.
COYNE School
500 S. Paulina St., Chicago 12, Ill. Dept. 32-51H

Send FREE BOOK and full details on:
 TELEVISION-RADIO ELECTRICITY

NAME
ADDRESS
CITY STATE

ASTRON CAPACITORS

pay

No shelf-warmers; no comebacks—for smooth, sweet SERVICE all the way, use ASTRON capacitors on your next job—they DO MORE!

Have YOU sent for our new Catalog AC-3 with its wealth of educational data? Write for this helpful material today.


ASTRON CORPORATION
255 Grant Ave. East Newark, N. J.

Now! HERE'S EVERYTHING YOU WANT TO KNOW TO
Pass FCC Radio Exam
FOR COMMERCIAL OPERATORS



IT'S GREAT TO HAVE AN FCC LICENSE WITH SO MANY BIG-PAY JOBS OPEN!

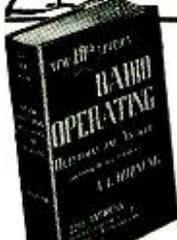2218 ANSWERS to FCC Study Guide Questions—Covers the Requirements Needed to Pass Commercial Radio Operator's Examination in ANY Class



PARTIAL CONTENTS
 • Basic Law • Operating Practice • Basic and Advanced Radiotelephone • Radiotelegraph • Aircraft Radiotelegraph • Ship Radar Techniques • International Morse Code —PLUS 185 ANSWERS for new and revised questions listed in current FCC Study Guide • NEW Information on Television Antenna Systems, Radar, Loran, Aircraft Radio Telegraph, Marine Operational Procedure—and much more!

Here's the *tested* way to prepare for commercial radio operator's exams. Get your FCC License in ANY class. Prepare for big jobs and big money. This brand-new, revised, and enlarged book ANSWERS 2218 questions in the FCC Study Guide. Used successfully by thousands of beginners to prepare for basic exams —helps experienced operators get better ratings, top jobs!

Brand-New 10th Edition
 668 Pages
 131 Illustrations

668 pages crammed with NEW FCC examination requirements. Answers latest technical and legal questions. 69 questions and answers cover the NEW Element 8 on ship radar. NEW and revised list of important Q signals, standard abbreviations, changes in use of International Morse Code.

A gold-mine of reference data on radio communication, apparatus, circuits, regulations, etc. Includes 46 special problems given in new FCC guide on antenna systems, loran, radar. PLUS easy-to-follow diagrams for all questions where diagrams are required.

SEND NO MONEY—EXAMINE FREE

Just mail coupon below to get the new, supplemented 10th Edition "Radio Operating Questions and Answers" on 10 DAYS' FREE TRIAL. If not satisfied that it will help you pass FCC Radio Exams—just return it, owe nothing. Otherwise, send only \$6.50, plus a few cents delivery, as full payment. Mail coupon TODAY.

McGraw-Hill Book Co., Inc., Dept. RE-3-52, 327 West 41st St., New York 18, N. Y.
 Send me "Radio Operating Questions and Answers" for 10 days' FREE EXAMINATION. If fully satisfied I will send you \$6.50 plus delivery as full payment. Or I will return book postpaid in ten days and owe nothing.

Name.....
 Address.....
 City..... State.....
 Employed by.....
 SAVE DELIVERY COST—Check here if enclosing \$6.50 WITH coupon. Then WE prepay postage. Money back if you return book.

ST. LOUIS EXPOSE

St. Louis has joined the cities making investigations into television service. The Better Business Bureau of that city submitted three sets—two with a defective tube and one with a blown fuse—successively two or three times to different branches of the same service company. The prices for repair ranged from \$5.30 (fuse 30 cents, labor \$5.00) to \$32.60. In all cases where a high charge was made, various resistors and tubes were replaced, but the major charge was for labor in each case. The labor charge tended to run between \$20 and \$25. In at least one case a repair charge of \$30.40 was charged for repairing a set which had been returned a few days before by another branch of the same company, presumably in perfect operating condition.

The Bureau concludes that the "unnecessary replacement of good parts and high labor charges indicate sharp practices or gross incompetence."

Two interesting points stand out in the investigation. One is that all parts listed as having been replaced were replaced in fact. (In many cases, where concerns have been engaged in gyp practices, the bills have been padded with many items not actually supplied.) The other is that the "trivial gimmick" angle is not as applicable in television as in radio repair, since the customer is trained to pay \$5.00 for a service call, even when the trouble is a blown fuse.

Otherwise the faults in these receivers might be classified as trivial, in one case consisting of a loose wire, and in others single bad tubes.

UNETHICAL ADS BANNED

The *Courier Journal* and *Louisville Times* of Louisville, Ky., have announced a set of rules which television dealers must abide by to be permitted to advertise in those papers.

Advertisements must contain accurate descriptions, carry the featured price next to illustrations of the featured receiver, use exact illustrations, state whether equipment shown with sets must be paid for separately, state only the actual retail price, state what additional charges are to be made for warranty, tax, service contract, etc., refrain from using such terms as "no money down," without the necessary qualifications regarding trade-ins, and make all guarantees quite clear and specific.

The advertising manager of the two papers states that the code is no pious statement, but that all copy is actually checked to see that it complies. If it does not, it is returned to the advertiser for revision.

CHANGE OF NAME

The Nebraska-Iowa Television & Electronic Service Association has changed its name to Television & Electronics Service Association, according to a recent *NATESA Bulletin*. Jim Husted, secretary-general of NATESA, has been elected to the T&ESA presidency for a second term.

—end—

The Book that takes Drudgery out of Mathematics
 Only **\$1.** postpaid
 SOLVES EVERYDAY PROBLEMS HELPS YOU GET AHEAD IN LIFE

How many times have you lost money because of a mistake in figuring? Do you know how to figure quickly and correctly? Can you figure discounts, interest rates, taxes and all the other calculations you meet up with in your daily life?

Are you having trouble qualifying for Civil Service Exams or Armed Services Promotions, because you're not up on mathematics?

ILLUSTRATED

Here is the book that gives you a good background in mathematics; that takes all the irritation and drudgery out of it; that you don't need to be scared of mathematics, because here's the subject explained without frills, without useless computations. Here's the book for men in radio jobs; for business men; technicians and craftsmen, explaining and answering everyday mathematic problems in easy-to-understand words and illustrations.

A BOON TO EVERY RADIOMAN

The Radio Technician will find information on the following: Ohm's Law—Resistance—Reactance—Capacities—Inductances.

The valuable tables are multiplication and division table. Squares; Square Roots; Cubes and Cubic Roots Tables. Areas of Circles Table. Common Fractions reduced to Decimal Table. Factors and Prime Numbers Table. Table of Multiples.

Yes, it's the key to a simple understanding of mathematics. It's a real home-study course in mathematics for the man who's alert to its importance in the world today.

ELEMENTARY MATHEMATICS

• EASY — SIMPLIFIED — PRACTICAL •

CONTENTS OF BOOK

CHAPTER I. Arithmetic—Addition—Subtraction—Multiplication—Division.
CHAPTER II. Factoring and Cancellation—Fractions—Decimals—Percentage—Ratio—and Proportion.
CHAPTER III. The Metric System.
CHAPTER IV. How to Measure Surfaces and Capacity (Geometry).
CHAPTER V. Powers and Involution—Roots and Evolution.
CHAPTER VI. Mathematics for the Manual and Technical Craftsman—Thermometer conversions—Graphs or Curve Plotting—Logarithms—Use of the Slide Rule.
CHAPTER VII. Special Mathematics for the Radio Technician.
CHAPTER VIII. Commercial Calculations—Interests—Discounts—Short Cut Arithmetic.
CHAPTER IX. Weights and Measures—Useful Tables.

STAMPS, CASH OR MONEY ORDER ACCEPTED
 Send Today for Your Copy of This Indispensable Book. It Can Be Carried Readily in Your Pocket. (Size 6 x 9 in.)

ONLY **\$1.** POSTPAID

TECHNIFAX; 100 East Ohio St. Chicago 11, Ill.

Enclosed find \$1.00 for which send me ELEMENTARY MATHEMATICS prepaid.

Name.....
 Address.....
 City & State.....

PRESELECTOR FROM T.R.F. SET

Old t.r.f. broadcast radios which have been dismissed from active service can be used as preselectors for broadcast dx. (Also for short wave if the set has a short-wave switch.) We used a set which had two 6K7's in the r.f. stages and a 6F6 in the audio. The .01- μ f capacitor which went from the plate of the detector to the grid of the 6F6 was removed, and a 100- μ f mica capacitor was soldered from the plate of the 6K7 detector to a tie lug. A shielded wire was brought from the tie lug and attached to the antenna post of a broadcast set. The shield was grounded in the t.r.f. preselector and near the antenna of the broadcast set to which it was attached. Both these sets had transformer-type power supplies. If two a.c.-d.c. sets are to be hooked together, polarity must be observed. No feedback was noticed with the sets in their cabinets. If feedback is present, it may be necessary to put wire screen inside the cabinet of the preselector.

With the preselector in operation after midnight when there is little congestion on the band, the results were astounding. Stations all over the country never before heard came in with good signals.—*C. Tierney*

AUDIO AMPLIFIER HINT

If oscillations do not respond to the usual remedies in a high-gain amplifier which does *not* have inverse feedback, try reversing the leads to the primary of the output transformer. If the amplifier has a push-pull output stage, reverse the plate connections to the output transformer and keep these leads isolated as much as possible from grid and plate leads of preceding stages. Shielding these may be necessary.—*John Crouch*

TV CHANNEL INDICATOR

Some TV sets, such as the Motorola VT-71M-A, have only a small dot as the indicator on the channel-selector knob. This makes it difficult to tell which channel is tuned in when viewing from a distance in a dimly lit room.

To solve this problem, I use a piece of cardboard as a pointer. Using the rear circumference of the knob as a guide, I trace the outline on the cardboard, then add a small projection for the pointer. After trimming around the outline and punching out the center for the control shaft, I cement the pointer to the back of the knob so it is directly behind the small indicator dot.—*B. W. Welz*



A KINK FOR D.C. RELAYS

In the small broadcast station where I am employed, several d.c. relays are operated by microphone switches on the control console. Every time a mike was turned off the VU meter kicked and a click could be heard in the audio system. This was probably caused by the inductive kickback current in the relay coil. We cleared up the trouble by shunting a .05- μ f capacitor across the coil of each relay.—*Charles Erwin Cohn*

SUPERCHARGED TV!

when results count...

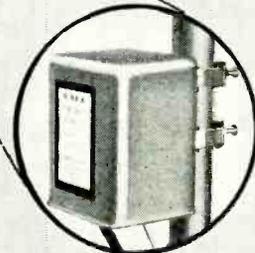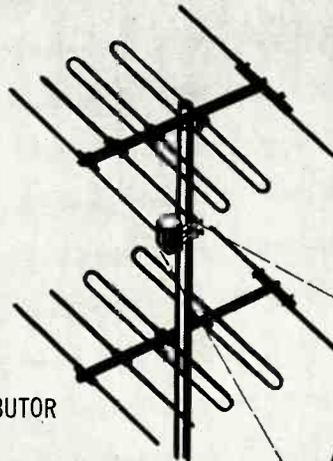For the highest signal-to-noise ratio try this winning combination. Taco Super 980 Yagi and Taco Antenna Supercharger provide 25db gain plus rejection of noise due to sharp directivity of the antenna and sharp frequency tuning of the combination. (For high-band channels use the Taco 5-element Yagi)



ASK YOUR DISTRIBUTOR



TECHNICAL APPLIANCE CORPORATION,
ONE TACO AVE., SHERBURNE, N. Y.
Manufacturers of Tacoplex Master Antenna Systems
In Canada: Stromberg-Carlson Co., Toronto 4, Ont.

WORLD'S FASTEST SELLING VOLT-OHM MILLIAMMETER



Sensitivity
1000 ohms per volt

- ★ Uses latest design 2% accurate 1 Mil. D'Arsonval type meter.
- ★ Same zero adjustment holds for both resistance ranges. It is not necessary to readjust when switching from one resistance range to another. This is an important time-saving feature never before included in a V.O.M. in this price range.
- ★ Housed in round-cornered, molded case.
- ★ Beautiful black etched panel. Depressed letters filled with permanent white, insures long-life even with constant use.

The Model 770 comes complete with self-contained batteries, test leads and all operating instructions. **\$14.90 NET**

- Specifications:
- 6 A.C. VOLTAGE RANGES:
0-15/30/150/300/1500/3000 Volts.
 - 6 D.C. VOLTAGE RANGES:
0-7.5/15/75/150/750/1500 Volts.
 - 4 D.C. CURRENT RANGES:
0-1.5/15/150 MA. 0-1.5 Amps.
 - 2 RESISTANCE RANGES:
0-500 Ohms 0-1 Megohm.


Model 770
is an accurate pocket-size V.O.M.
Measures only 3 1/8" x 5 7/8" x 2 1/4".

Write Dept. RE-3 for catalog of complete line.



Manufactured and Guaranteed by
SUPERIOR INSTRUMENTS CO.
227 Fulton Street • New York 7, N. Y.

AT YOUR RADIO PARTS JOBBER

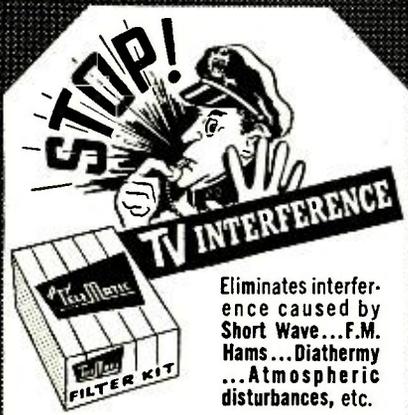

Eliminates interference caused by Short Wave...F.M. Hams...Diathermy...Atmospheric disturbances, etc.

With a TELEMATIC Full Range FILTER KIT

SIMPLE — SPEEDY — EFFICIENT


- Eliminates antenna-fed interference!
- Covers full-range both I.F. and R.F. Sharper, steadier picture!
- Fewer service recalls!
- Any filter in kit replaceable separately!

FILTER KIT
contains 2 Hi-Pass Filters, 4 WAVE TRAPS covering full range of interference signals.

Send for FREE Booklet on TV-INTERFERENCE



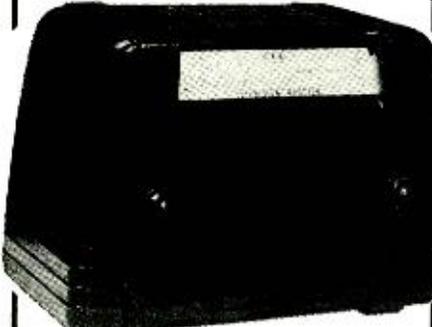NEW OAK BOOSTER
Precision Engineered!
for TV-FM
by OAK ELECTRONICS
\$39.95



The booster that finally satisfies your demands by succeeding where others have failed. The OAK BOOSTER uses Mallory INDUCTUNER same as used in Dumont, Crosley and Stromberg Carlson TV sets) in a newly engineered circuit on which patent is pending. Provides variable bandwidth to control adjacent channel interference and reduce noise to a minimum. Uses new "Q" multiplier circuit to increase gain enormously.

- ✓ Highest gain of any booster
- ✓ Gain adjustable from front knob
- ✓ Dual Input
- ✓ Automatic On-Off
- ✓ Dual Output
- ✓ Variable bandwidth controllable from front panel

Order Oak Booster from your jobber today
Write for specifications and discounts

OAK ELECTRONICS
150 Oak Street, Buffalo, N. Y.

CLEANING VARIABLE CAPACITORS


Many of the younger service technicians use carbon tet, compressed air, and other gimmicks to remove dust, metal filings, etc. from between the plates of tuning capacitors. When it comes to stubborn cases which do not respond to these treatments, the youngsters would do well to borrow a trick from an old-timer.

Disconnect the leads from the tuning capacitor, apply 800-1,000 volts a.c. across the plates, and slowly turn the rotor through its range. Arcing in the narrow air gap will quickly burn out any foreign material.

The secondary of an old power transformer is a convenient source of voltage. Connect a 200-ohm, 25-watt resistor or a 25-watt, 115-volt bulb in series with the primary and one side of the power line. This limits the current and keeps the transformer from burning out. When the bulb starts to light, leave the rotor set at this point until the condition clears up as indicated by the lamp going out. Use well-insulated leads and test clips to connect the transformer across the capacitor.—*A. Ivanivsky*

AUDIO MIXING SYSTEM

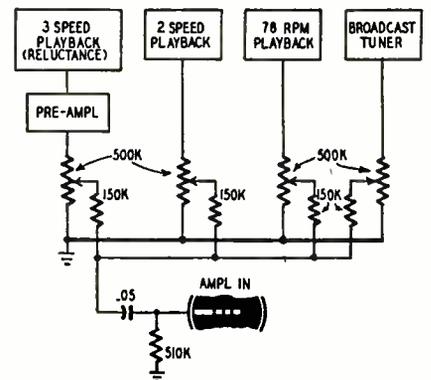I am a high-fidelity fan with quite an array of audio equipment which includes a playback amplifier, tuner, and three turntables. We wanted to avoid using a channel-selector switch on the amplifier because of the clicks and pops which usually occur when a switch is thrown, so we used the mixer circuit shown in the diagram.




The volume control at the input of the amplifier was replaced with a 510,000-ohm resistor. The amplifier was then coupled to individual 500,000-ohm volume controls through 150,000-ohm isolating resistors. These resistors introduce some loss into the individual circuits, but they enable me to set the unused controls in any position without noticeably changing the level of the particular channel in use.—*Robert G. Masching*

TRANSFORMER LEAD MARKING

Ordinary pricing tags—such as are used by stores—are useful when replacing multilead transformers. Check each lead when removing the old transformer, and slip a properly marked tag on it. When the new transformer arrives, the job of checking need not be done again.—*Eric Leslie*

Heavy on experience—light on theory?

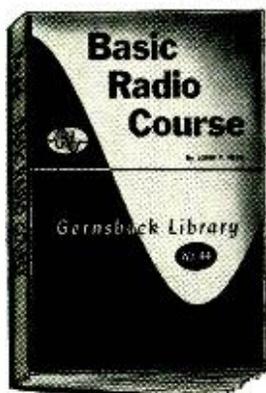

Basic Radio Course by John T. Frye
Answers all your questions on fundamentals from Ohm's Law to advanced service techniques
Completely • Humorously • Economically
176 Pages 120 Illustrations
Only \$2.25

Popular writer, John T. Frye, himself a 25-year veteran in servicing, clears away every bit of haze that may cloud your knowledge of why tubes, capacitors, resistors and other components act as they do in radio circuits. He packs every single chapter with the kind of information that will make you know and understand what you're doing instead of just guessing or following formula.

Order your copy from your distributor or MAIL THIS COUPON TODAY

Radcraft Publications, Inc., Dept. 32
25 West Broadway
New York 7, N. Y.
My remittance for \$2.25 is enclosed. Please send me a copy of Book No. 44, BASIC RADIO COURSE postpaid.

NAME _____
STREET _____
CITY _____ ZONE _____ STATE _____

TWENTY-SIX BIG CHAPTERS
Covers:—Electron Theory • Ohm's Law • Resistance • Inductance • Capacitance • Reactance • Impedance • Resonant Circuits • Transformers • Tubes • Sound and Loudspeakers • Power Output Stage • Voltage Amplifiers • Demodulating the R.F. • Selectivity • Oscillators • Service Techniques • Other important subjects.

AUTOMATIC M-90 AUTO RADIO



- Six Tube Superheterodyne • Three Gang Condenser • Powerful, Long-Distance Reception • Fits All Cars, Easy Installation
 - Mounting Brackets Included
 - 6 Tube model M90\$34.97
 - 5 Tube Model A-15..... \$28.76
- *Above price includes Federal Excise Tax
Approx. shipping weight either radio (11) eleven pounds
- MAIL US YOUR ORDERS**
All orders filled within 24 hours.
Standard Brand tubes 50% off list

Bill Sutton's Wholesale Electronics
Fifth at Commerce Fort Worth, Texas

LOW FACTORY PRICES

Sensationally New for 1952!

MIDWEST TELEVISION
and 5 Wave Band RADIOS

Mammoth **20-inch** Rectangular PICTURE

FACTORY TO YOU EASY TERMS

A sensational new 1952 line of beautiful consoles and complete chassis, Mammoth 20-inch Televisions and powerful 5 Wave Band Radios—at Low Factory Prices.

30 DAYS TRIAL

MIDWEST RADIOS AM-FM

WE PAY TRANSPORTATION CHARGES.

Special Bonus Gift!

Illuminated TELEVISION CLOCK

Given With Every Purchase of a MIDWEST RADIO or TELEVISION

LIMITED TIME ONLY!

Phone For FREE 1952 MIDWEST CATALOG

IN NEW YORK Murray Hill 2-6810 IN CHICAGO State 2-5600
IN CLEVELAND Prospect 1-7450 IN PITTSBURGH Grant 1-0609
IN DETROIT Woodward 3-1233 IN ST. LOUIS Grand 1161
IN PHILADELPHIA LOcust 4-1035 ... or send coupon below

SEND THIS COUPON For FREE MIDWEST 1952 Catalog

MIDWEST RADIO & TELEVISION CORP.
Dept. 388, 909 Broadway, Cincinnati 2, Ohio

NAME _____
ADDRESS _____
CITY _____ ZONE _____ STATE _____

QUIETER VOLUME CONTROLS

Standard replacement volume controls have been shrinking in physical size for the past several years. While these controls have a low enough noise level for replacement use in radios, they are noisy in low-level stages of amplifiers and equalizers. Here are some ways to substantially reduce this noise.

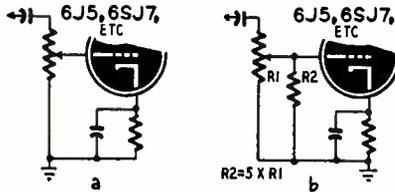


Fig. 1—The circuit at *b* lessens noise.

A large part of volume-control noise is a result of the grid not having any return to ground when the contact passes over an eroded or dirty portion of the control. This is the case in Fig. 1-a. By adding a resistor R2 between grid and ground, a d.c. return for the grid is insured at all times. This resistor should have a resistance about five times the volume-control resistance R1. See Fig. 1-b.

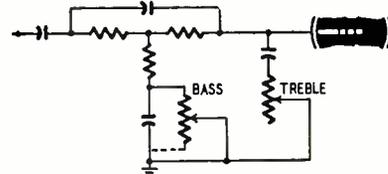


Fig. 2—Quieting tone-control circuits.


Fig. 2 is the basic tone-control circuit used in many tuners and radios. Only two terminals of the bass control are usually wired into the circuit. After a few months the control becomes more noisy. The simple cure is to ground the third terminal as shown by the dashed lines. This establishes a grid return through the potentiometer regardless of variable arm contact irregularities.

The procedure is simple, yet it is a sure cure for this cause of control noise.

—Edwin Bohr

ADAPTER FOR TUNING SHAFTS

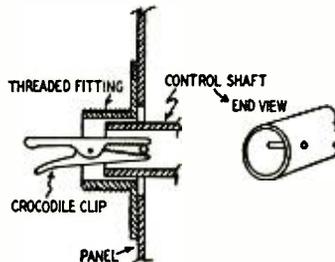Many automobile radios have volume, tone, and tuning controls equipped with special fittings designed to be operated through slotted-end flexible shafts. This type of control is difficult to adjust when the control shafts are removed while the set is being serviced.



I use thin-nose crocodile clips to simplify adjusting the controls. The drawing shows the type of fitting and the use of the clip as an extension shaft.

—Nate Silverman

—end—

The New

Mandl's Television Servicing

- gives you detailed, illustrated trouble-shooting procedures for every flaw or failure you're likely to encounter.

A COMPLETE MASTER INDEX and separate lists of trouble symptoms for each circuit defect make it easy to locate any particular trouble and the exact procedures for correcting it. Unusual, hard-to-find flaws as well as all common trouble are dealt with.

THE LATEST CIRCUITS are explained and illustrated, including servicing techniques for UHF and VHF.

ORIGINAL PHOTOGRAPHS show actual symptoms that appear on the TV screen when defects occur. Hundreds of circuit diagrams, illustrations of station defects, scope patterns, and other illustrations aid in the identification and location of circuit faults

and these are only a few of the features that make this the most helpful, practical, and complete service manual yet to be published.

Are these outstanding radio & TV aids on your working reference shelf?

Radio and TV Mathematics

by Fischer. Step-by-step solutions for hundreds of typical problems, arranged under radio and electronic headings for quick reference. Shows what formulas to use, what numerical values to substitute, how to solve each.

Television for Radiomen

by Noll. Very clear, non-mathematical explanation of all principles and full instruction on installation, alignment, adjustment, and trouble-shooting.

Television & FM Antenna Guide

by Noll & Mandl. A basic course on theory plus a complete handbook on all types of antennas and installation procedures.

Movies for TV

by Battison. Practical information on all equipment and experienced advice on the do's and don'ts of making newsreels, commercials, features, titles, special effects, cartoons, etc.

SEE THEM ON APPROVAL

The Macmillan Co., 60 5th Ave., N. Y. 11

Please send me copies of the books checked. I will either remit in full or return the books in 10 days.

- Mandl's TV Servicing \$5. (prob.) Signed
- Radio & TV Math. \$6.75
- TV for Radiomen \$7.75 Address
- TV & FM Antenna Guide \$6.25
- Movies for TV \$5.00

Compare!

**PROVE
EMC
SUPERIORITY!**





Model 104
(20,000 ohms per volt meter)

- 4 1/2" SQUARE METER (50 micro-amperes-Alnico magnet)
- Includes carrying strap
- 5 DC Voltage Ranges at 20,000 ohms volt to 3,000 V.
- 5 AC Voltage Ranges to 3,000 V.
- Resistance Ranges to 20 megohms
- Also 3 AC & DC Current Ranges at 5 DB Ranges

\$26.95

Model 102
(1000 ohms per volt meter)

- 3" SQUARE METER
- 3 AC CURRENT RANGES (0-30/150/500 ma.)
- Same zero adjustment for both resistance ranges (0-1000 ohms, 0-1 meg-ohms)
- 5 DC & 5 AC Voltage Ranges to 3,000 Volts
- Also 4 DC Current Ranges

\$14.90

Model 103
(1000 ohms per volt meter)

- 4 1/2" SQUARE METER
- 3 AC CURRENT RANGES (0-30/150/500 ma.)
- Same zero adjustment for both resistance ranges (0-1000 ohms, 0-1 meg-ohms)
- Same Ranges as Model 102.
- Also 5 DB Ranges

\$18.75

Model 103-S with plastic carrying strap **\$19.25**

All of the above have molded bakelite cases.
Write Dept. RE for Free Complete Catalog of these and other Instruments.
— See them at your Jobbers —


EMC

Electronic Measurements Corp.

280 Lafayette St., New York 12, N. Y.
Export Dept., 303 W. 42nd St., N. Y. C.


NOVEL OUTPUT STAGES

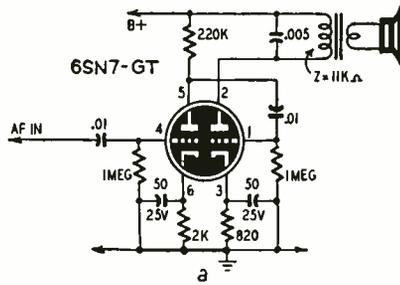From time to time, we have seen circuits of small European receivers which




use 6C5's, 6SK7's, and similar voltage amplifier triodes and pentodes driving speakers in the output stage. We haven't seen any claims as to the power delivered, but if they can drive a small speaker, the saving in drain on the B-supply should certainly make them useful in some types of sets.

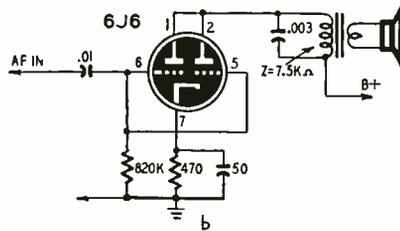Three circuits designed for twin-triodes were described in *Radio Ekko*



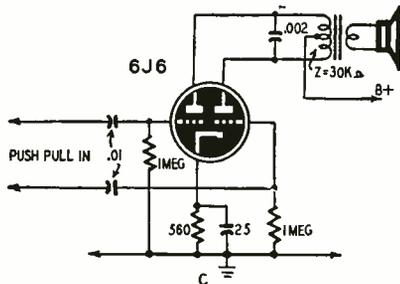
(Denmark). The circuit at *a* shows how a 6SN7-GT may be used as a cascade-coupled amplifier with the second section driving the speaker. The circuits at *b* and *c* are for 6J6's and similar tubes. These show connections for single-ended and push-pull output stages.



WOBBULATED SIG GEN

Most broadcast sets are aligned by peaking the i.f. transformer windings for maximum output. This method is not particularly suited to high-fidelity tuners and some communications receivers. The ideal method is to adjust the tuned circuits for the desired response curve on an oscilloscope. A circuit of a wobulated oscillator for visual alignment of broadcast sets is described in *Wireless World* (London, England). Its circuit is shown in the diagram.

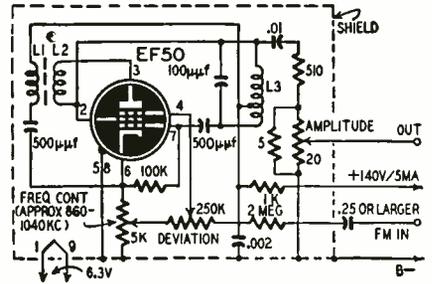This circuit, which uses a single EF50 tube as combined oscillator and reactance tube, is a development of a system described by K. C. Johnson in the April and May, 1949, issues of *Wireless World*. The EF50 is obtainable in this country as a surplus tube.



The oscillator circuit consists of L1 and the 500-µmf capacitor in series. Feedback between the grid and plate is developed through the autotransformer L3 which is broadly resonant throughout the tuning range—about 860 to 1040 kc. L2 carries the plate current and is tightly coupled to L1. A change in plate current changes the mutual inductance and shifts the operating frequency. The change in frequency is determined by the ratio of plate current to cathode current. Since changing the voltage on the suppressor causes a large change in plate current without greatly affecting the total cathode current, the oscillator may be frequency-modulated by applying a varying voltage to the suppressor.

A sawtooth voltage is applied to the suppressor grid to provide the necessary sweep voltage. This is obtained by connecting the FM input terminal to the horizontal deflection amplifier output of the 'scope. The output of the generator is coupled directly to the grid of the mixer tube in the receiver or to the antenna posts through a dummy antenna. The signal for the vertical amplifier of the 'scope may be tapped off the hot end of the volume control. The a.v.c. line should be grounded during alignment.

L1 consists of 30 turns of No. 31 enameled wire close-wound on a 1-inch form. L2 is an identical winding wound in the same direction on top of L1. The cathode and screen-grid connections should be made to corresponding ends of L1 and L2. L3 is 100 turns of No. 31 wire on a 1-inch form with a tap 40 turns from the end which connects to L2. L3 should be mounted at right angles to L1-L2 with the tube or a shield between them to minimize coupling. The unit should be carefully shielded to minimize leakage.

When using the wobulator, adjust the receiver to a quiet spot around 1000 kc on the dial, then adjust the frequency control until the signal is tuned in. Set the sweep speed of the scope to a fairly low rate so there is no difference between the forward and backward traces.

BEAM KILLER

This circuit modification prevents formation of the intense spot of light that appears in the center of many TV screens immediately after the set is turned off. In most TV sets the picture tube first anode is supplied from some point in the power supply proper. The diagram shows how a popular RCA circuit can be modified so the first anode is supplied directly from the arm of the

WANTED

WE PAY TOP \$\$\$ FOR:

- ★ RADIO RECEIVERS
- ★ TRANSMITTERS
- ★ ARC-1
- ★ ARC-3
- ★ ART-13
- ★ CONTROL BOXES
- ★ INDICATORS
- ★ AN CONNECTORS

- ★ CLAMPS
- ★ PLUGS
- ★ CORDS
- ★ RELAYS
- ★ TELEPHONE MATERIALS

WE BUY ANYTHING!!


Write, Wire Today!

Tell us what you have

TALLEN COMPANY, INC.

Dept. RE, 159 Carlton Ave.
Brooklyn 5, New York

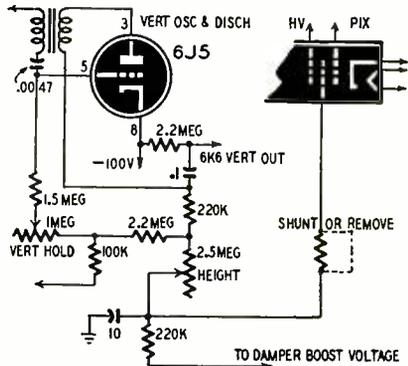height control which usually obtains its voltage from the damper-boost circuit. If the original circuit has a resistor in




series with the first anode, remove it. This circuit also aids in eliminating the brown spot seen on kinescope screens after some use. Although the circuit shown is applied to the 630-type set, there is no reason why it cannot be applied in other receivers.—*Wilbur J. Hantz*

(Take care when adding this circuit to sets having large picture tubes, because the boosted voltage may exceed the maximum voltage which may be applied to grid 2. If the voltage exceeds 400, use a voltage divider.—*Editor*)

KEYING MONITOR

A keying monitor must be simple to construct and trouble-free in its operation if it is to become a permanent fixture in the average amateur station. Such a monitor is described in *Short Wave Magazine* (London, England).

The r.f. input terminal of the monitor is coupled loosely to the output of the transmitter. A foot or so of wire or bus bar will work nicely. When the transmitting key is up, the triode section of the tube conducts heavily so the voltage on its plate is too low to permit the neon-tube relaxation oscillator to fire. When the key is closed, the diode section rectifies the incoming r.f. signal and develops sufficient negative voltage to greatly reduce the plate current of the triode. The plate current rises enough to permit the neon lamp to oscillate.

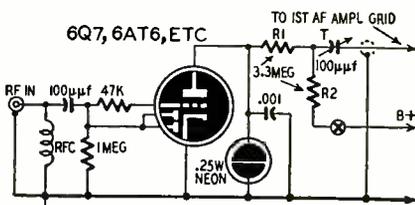

A 6SQ7, 6Q7, 6AT6, or similar tube may be used in the circuit. The output of the monitor is fed directly to the grid of the a.f. power amplifier in the receiver, so the setting of the receiver's volume will not disturb the level of the output from the monitor. Monitor volume is controlled by the 100-µf trimmer and by the ratio of R1 to R2. Operating voltage may be taken from the receiver. The receiver's standby switch should not disable the a.f. amplifiers when the monitor is used. If the switch is in the negative leg of the power supply, modify the circuit so it is in the r.f. and i.f. B-plus lead.



COMPLETE LINE OF WHEELER SOUND POWERED PHONES

Up to 25 Miles without Batteries or Power Supply

The Finest! 12 Intercom Master Stations

WRITE FOR FREE WHEELER CATALOG

MODEL SPT-102 (Illustrated)

WITH TEST CLIPS \$962 EACH

National SW-54

\$4995

Sleek, Low-Priced, Beauty in a Compact General Coverage Receiver.

11" x 7" x 7"

NATIONAL SW-54 IN STOCK

WRITE FOR FREE LITERATURE

REMOTE CONTROL FOR THE THING!!

(PLUS \$1.00 BOOK FREE)

The answer to the "Remote Control" experimenter's dream. A completely wired, 3 tube remote control unit, originally used as an Electronic Brain for remote thermo-static control of electric blankets. Can be used, with slight modification, to control model trains, planes, trucks, remote on-off for radios, open and close garage doors from your car, or to remotely control any device in accordance with your own ingenuity.

And that's not all! With each unit we will give you absolutely free, one copy of Germsback Library's popular new book "Model Control by Radio," 112 pages, containing more than 125 illustrations, diagrams, crammed full of theory and practical uses for Elec-
tronic Remote Control.

Remote Control Unit, including Fil. Xfmr., 300 ohm plate circuit "trigger" relay, completely wired, circuit diagram and above described book—
less tubes.....

ALL FOR ONLY.....

Shipping Wgt. 3 Lbs.

\$5.50

ASTATIC BOOSTER

MODEL BT-1

A simplified high gain booster using the famous Mallory inducto-tuner for continuous tuning over entire TV and FM spectrum. Gives exceptional improvement on all channels. Single tuning knob. Mahogany finished metal case. Low noise. For either 72 or 300 ohm line.

Wgt. 5 lbs.

SPECIAL! \$18.45

MODEL AT-1

Astatic four-tube deluxe models—no other booster can do so much in improving TV picture contrast and clarity, in improving sound, in eliminating interference. Feature exclusive variable gain control and dual-tuning.

Model AT-1 in fine furniture finish mahogany.

Special \$29.10

HEART OF THE BC-221 FREQ. METER

This VFO Sub-Assembly, used in BC-221 Freq. Meter, FULLY WIRED and mounted on sturdy aluminum sub-chassis, ready for installation. Brand new—in original packing. Very special.

Each \$4.95

A HIGH PRECISION VTVM KIT By

TEICO

TOPS ON ANY WORK BENCH

Versatility plus! 15 different ranges. Resistance ranges from .2 ohms to 1000 megohms in 5 steps! Exceptionally accurate. Big 4 1/2" fused meter. Dozens of features too numerous to mention. Sum it up in one word, TERRIFIC!

TEICO VTVM Kit No. 221K \$25.95

TEICO VTVM, wired and tested \$49.95

Write for Free TEICO Catalogue

WEBSTER-CHICAGO NEW MODEL 100-75

AUTOMATIC RECORD CHANGER WITH "FLIP-OVER" CARTRIDGE

One of their latest models. Plays 12, 10 or 7 inch records at 33 1/3, 45, or 78 R. P. M. New spindle carefully lowers unplayed record stack. Balanced arm assures light needle pressure and long wear. Needle-tip (included) for standard or micro-groove records. Inside-out records played without any adjustment. Pickup arm comes to rest position after last record has played. Complete factory packed and sealed record changers, normally listing at \$47.50—While they last.

\$2485

Shipping Wgt.

ONE OF AMERICA'S GREAT RADIO STORES

Niagara

RADIO SUPPLY CORP. Dept. 3-E2


160 Greenwich Street, New York 6, N. Y.

Digby 9-1132-3-4

TELLS HOW TO SOLVE TV TROUBLES AND ANSWERS TV QUESTIONS

AUDEL'S TELEVISION SERVICE MANUAL covers T.V. information at your finger ends. Shows good receiver adjustment and How to Get Sharp, Clear Pictures, How to Install Aerials—Avoid Blurs, Smears, Interference and How to Test. Explains Color Systems and Methods of Conversion. IT PAYS TO KNOW! Over 380 PAGES & 225 ILLUSTRATIONS explaining operating principles of Modern Television Receivers.

Just Out!

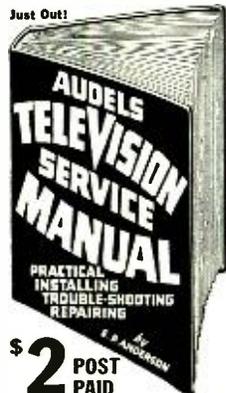

1001 FACTS 19 CHAPTERS
 Placement of Television Receivers—Receiver Controls; Test Patterns & Adjustments—Television Interference—Interference Traps—Television Antennas & Transmission Lines—Master Antenna Systems—Antenna Installation Procedure—Television Broadcasting—Television Receiver Fundamentals—Circuit Description of Typical Receiver—Television Picture Tubes—Projection Type Receivers—Television Testing Instruments—Television Servicing—Trouble Shooting—Color Television—Television Terms.

\$2 POST PAID

7 DAYS FREE TRIAL
 GET THIS PRACTICAL ASSISTANCE FOR YOURSELF—MAIL COUPON TODAY—

AUDEL, Publishers, 49 W. 23rd St., N. Y.
 Mail me postpaid for 7 Days examination
AUDEL'S TELEVISION SERVICE MANUAL (Price \$2).
 If O. K. I will mail you \$2, otherwise I will return book.

Name.....

Address.....

Employed by..... **TV16**

DID YOU GET IT? IF NOT
SEND NOW FOR B-A'S 136 BIG PAGE FREE CATALOG



BURSTEIN-APPLEBEE CO.
 1012-14 McGee St.
 Kansas City 6, Mo.

Send your 1952 catalog to:

FREE

Name.....

Address.....


City.....State.....

BURSTEIN-APPLEBEE CO.

SELECTIVE I.F. AMPLIFIER

Adequate selectivity is often a major problem in communications receiver design particularly in sets designed for c.w. reception. In most cases, a network of one or more quartz crystals acts as a selective coupler between two i.f. stages. The filter network can be considered as a very high-Q series-resonant circuit tuned to the intermediate frequency.

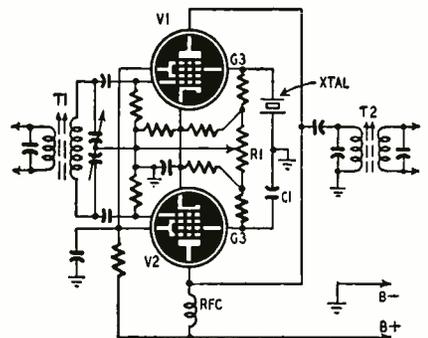A different type of crystal-controlled variable-selectivity circuit is described in patent No. 2,533,802 issued to Donald L. Hings, and assigned to Cornell-Dubilier. This method of obtaining a high degree of selectivity is based on the operation of the push-push selective amplifier



shown in the diagram. Transformers T1 and T2 are tuned to the frequency to be passed. This may be the i.f. of a standard receiver. The secondary of T1 is tuned by a split-stator capacitor which provides a balanced input to the push-pull grids of amplifier tubes V1 and V2. The plates of these tubes are connected in parallel.

The injector grid G3 of V1 is connected to ground through a crystal cut to the center frequency of the amplifier. The injector grid of V2 is bypassed to ground through C1, in the injector grid circuit of V2.

If it were not for the crystal in the circuit of V1, the voltages at the plates of V1 and V2 would be equal and 180 degrees out of phase and would cancel each other. However, when a signal to which the crystal is resonant is fed into T1, the crystal oscillates at its natural frequency. The injector grid of V1 becomes sufficiently negative to bias the tube to cutoff or greatly reduce its output. V2 amplifies the signal in a normal manner so the voltage developed across the primary of T2 is the differential of the two plate voltages. The curve of the developed voltage is similar to the response characteristic of a conventional crystal filter, as commonly used in communications receivers.

The selectivity of the circuit can be varied by adjusting the setting of R1 which controls the bias on the injector grids.

V1 and V2 are obviously mixer-type tubes which have two grids that can be used as independent control elements. Such tubes as the 6AS6, the 6SA7, or better, the 6BA7 can probably be used in this circuit. Another feasible tube might appear to be the 6L7, provided that the grid cap on the top is properly shielded.

SPECIAL!! 6 TUBE AC-DC KIT

At Last! A low-priced kit designed for high sensitivity, excellent selectivity and good tone quality. Uses 25L6, 25Z6, 6SQ7, 6SA7, 6SK7, 6SK7 in an easily constructed circuit. The 6 Tube Kit is shipped with all parts, including punched chassis, resistors, condensers, coil, sockets, PM Speaker, hardware, etc.

And at a closeout price of only **\$6.95**
 X182 less tubes and cabinet

X183 Extra for matched set of six tubes for kit **\$3.25**

5 TUBE AC-DC SUPERHET KIT

Five tube superheterodyne kit, A.C.-D.C. contains all components required to construct this latest design, highly sensitive superheterodyne broadcast receiver complete with black bakelite cabinet (excludes wire and solder) Price \$7.95
 Extra for a kit of 5 tubes (12A6, 12BA6, 12BE6, 35WA, 50C5). Price \$3.25.

YOUR MONEY RETURNED IN FULL—

If the New Regency Television Booster fails to improve your television enjoyment! Bring your picture out of the snow and reduce interference!

- Push-Pull Neutralized triode design assures high gain without adding snow.
- No external impedance matching devices required.
- Inductive tuning assures same high-gain wide-band operation on all channels.
- Single knob tuning control.
- Underwriters approved with 90 day RMA guarantee.

LOWEST Price—ONLY **\$19.11**

MODEL NFRD—RADIO NOISE FILTER

If it doesn't work, send it back!

We absolutely guarantee that our Model NFRD will eliminate all line noises when properly connected to radios, television sets, short wave sets, motors, electric shavers, refrigerators, vibrators, oil burners, transmitters, and all other sources of interference. This unit will carry up to 12 amperes or 1 1/4 KW of power and may be used right at the source of interference or at the radio.

Small size only 2 1/2" x 1 3/4" x 4 1/2". Very low price only
 Each **\$1.95**

A SCIENTIFICALLY DESIGNED PHONO SCRATCH FILTER

Resonated at approximately 4500 cycles effectively reducing objectionable needle scratch without altering the brilliancy of reproduction.

Contains a HI-Q SERIES resonated circuit. Tested by means of an audio oscillator and an oscilloscope to give 22 db attenuation with very low signal loss.

EASY TO ATTACH

Just two wires to clip on. Compact
 Price..... **\$1.98**

THREE TUBE PHONO AMPLIFIER

An assembled unit ready for installation using tone and volume control and six feet of rubber **\$2.95**
 cord.....

(Not including Tubes)

With Complete Set of Tubes..... **\$3.95**

PHONO OSCILLATOR

Wireless phono oscillator transmits recording for crystal pick-ups or voice from carbon mike through radio without wires. Can also be used as an intercomm by using P.M. speaker as mike.

Price (excluding tubes)..... **\$2.95**

With Complete Set of Tubes..... **\$3.95**

Grab Bag Special, 10 pounds of Misc. Electronic Material—Transformers Condensers, resistor, wire, etc. Price **\$1.95 ea.**

Satisfaction guaranteed on all merchandise
 All prices subject to change without notice.

RADIO DEALERS SUPPLY CO.

154 Greenwich St. New York 6, N. Y.

7 HARD TO GET ITEMS AT BIG SAVINGS TO YOU

AMAZING BLACK LIGHT



250-watt ultra-violet light source. Makes fluorescent articles glow in the dark. Fits any lamp socket. For experimenting, entertaining, unusual lighting effects. Ship. wt. 2 lbs. ITEM NO. 87 A SAVING AT **\$2.45**

POWERFUL ALL PURPOSE MOTOR



Sturdy shaded pole A.C. induction motor. 15 watts, 3000 rpm. 3/4" x 1 1/4" mounting studs; 7/8" shaft, 3/16" diameter; 110-120 volts, 50-60 cycles. A.C. only. When geared down, this unit can operate on 18" turntable with a 200 lb. dead weight. Use it for fans, displays, timers and other purposes. Ship. wt. 2 lbs. ITEM NO. 147 UNUSUAL BUY **\$2.45**

WATTHOUR METER

Leading makes — completely overhauled, ready for service. 100-110 volts, 60 cycles, 2-wire A.C. 5 amp. Heavy metal case 8 1/2" x 6 1/4" x 5". Easy to install. Ship. wt. 14 lbs.



ITEM NO. 33 NOW ONLY **\$4.50**

WESTERN ELECTRIC BREAST MIKE



Lightweight 1 lb. carbon microphone. Aircraft type. Breastplate mounting, adjustable 2-way swivel. Easily fastened straps. For home broadcasts, communications etc. Complete with 6 foot cord, hard rubber plug. Shaded plate, non-rusting finish. Ship. wt. 2 lbs. ITEM NO. 152 NEW LOW PRICE **\$1.75**

TELEPHONE TRANSMITTERS

Genuine transmitters made by Kellogg Western Electric, Stromberg Carlson. Work on two dry cells. For P.A. systems, intercoms other practical uses. Shipping weight 1 lb.



ITEM 160 REAL VALUE **\$4.75**

HUDSON SPECIALTIES CO. 40 West Broadway, Dept. RE-3-52 New York 7, N. Y.

1 am enclosing full remittance for items circled below. (Be sure to include shipping charges.)

OR, my deposit of \$..... Ship balance C.O.D. MINIMUM C.O.D. ORDER \$5.00. C.O.D. ORDERS ACCEPTED ONLY WITH 20% DEPOSIT INCLUDE SHIPPING CHARGES.

Circle Items Wanted 87 147 33 152 160

Name..... Please Print Clearly

Address.....

City..... Zone..... State.....

NATIONAL EMERGENCY

If you have any scrap iron, steel, copper, bronze, aluminum, lead, zinc or other metal, turn it over to co-operating scrap-collecting agencies. The defense effort needs it more than you do.


THE SYNCHROSCOPE

The principal component of this small stroboscope is a 1C21 cold-cathode rectifier, used as a moderately strong source of light.

The plate and the cathode of the tube are connected to the a.c. line with about 800 ohms in series to limit the current to about 100 ma.

The starter anode (grid) is connected to the plate through a resistance of about 100,000 ohms.

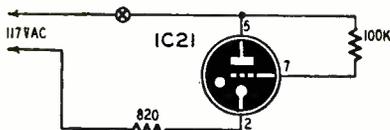The tube rectifies the line voltage and gives off a pulse of light during each positive half of the a.c. cycle. Thus one visual pulse per cycle of line frequency is given.





This pulse of light will stroboscopically stop the motion of a synchronous motor or any device that is operating in synchronism with the line frequency. Its ready application in the testing of synchronous motors, electric clocks, phonograph motors, time switches, timing devices, generators, business time machines etc., is apparent.—Harry Peach and Edward Spierer

NEW CIRCUITS IN FM SET

If you are an experimenter looking for interesting circuits to try, or are an engineer looking for a chance to develop new circuits, study the circuits of some of the new FM-AM combinations. They are full of interesting tricks.

Two unusual circuits are used in an FM receiver described by J. G. Spencer of the BBC, in *Wireless World* (London, England). The high-frequency oscillator circuit is shown at a. (The tube is the triode section of a converter similar to the 6K8.) This is a conventional tuned-plate oscillator with a 68-ohm resistor-heater in contact with the negative-coefficient temperature compensating capacitor, C1, in series with C2 added across the tuned circuit to compensate for the rapid drift which usually occurs during the initial warm-up period. A 1-watt resistor is ok.

—end—

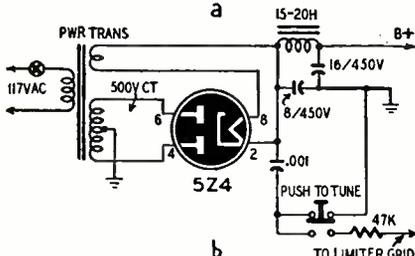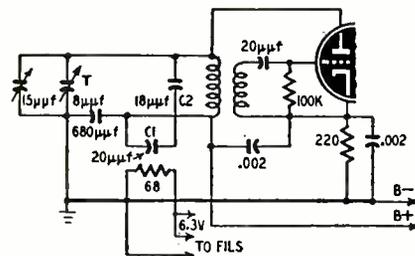

SAVE UP TO 53% ON COMPLETE ANTENNA KITS

Why search for parts? We put everything you need for a perfect installation in one kit. No forgotten parts. No wrong sizes. By prepacking these kits, we save handling costs. These savings are passed on to you. That's why you buy at such sensational prices, many below wholesale cost. All kits guaranteed to satisfy you or your money back.

Rocket 5 Element YAGI KITS


Excellent Pictures in Fringe Areas
HIGH GAIN. Clearer, sharper, sturdier pictures. PERFECT PICTURES IN FRINGE AREAS. Minimum interference from ghosts and noise due to a directive pattern. Five elements include one folded dipole, three directors, and one reflector. MATCHES 300 OHM IMPEDANCE. Molded insulator provides additional strength. Exclusive design must clamp prevents antenna curving or canting under any conditions. STURDY, TROUBLE-FREE CONSTRUCTION. No return calls. No broken elements. Stands the test of severest weather. Elements of heavy aluminum—top and bottom. QUICK RIG. Completely pre-assembled. Just swing elements into line and tighten wing nuts. Simple and quick to install. Available for any channel, high or low band.

FRINGE AREA YAGI KIT	
For people over 30 miles from station	
2 Yagi Antennas for Channels 7, 8, 9, 10, 11, 12, 13	\$19.00
1 Pair Stacking Bars (Tie Rods)	2.00
2 5-foot Mast Sections (Sweated)	4.50
75 Feet 300 Ohm Twin Lead @ 5c foot	3.75
60 Feet Galvanized Guy Wire @ 1 1/2c foot	.90
3 No. 4 Guy Wire Screw Eyes @ 5c each	.15
2 Mast Standoffs @ 5c each	.10
1 Guy Ring for 5c foot	.325
3 Screw Eye Insulator Standoffs @ 6c each	.18
1 Lightning Arrestor	1.25
1 Instruction Sheet	.15
Channels 7 to 13 Total Value	\$32.58
Channels 7, 8, 9, 10, 11, 12, 13 Kits, You Pay	\$ 9.25
Channels 4, 5, 6 Kits, You Pay	14.25
Channels 2 or 3 Kits, You Pay	17.25
Channels 7, 8, 9, 10, 11, 12, 13 Kits, You Pay	\$15.25
Channels 4, 5, 6 Kits, You Pay	22.25
Channels 2 or 3 Kits, You Pay	25.25

EACH CHANNEL requires a DIFFERENT Yagi antenna. When ordering, specify exact channel number desired. Any merchandise listed above may be purchased separately at prices shown.

SOLD ONLY BY MAIL BY NATIONAL ELECTRONICS

Rocket DIRECTRONIC MOTORLESS TV ANTENNA

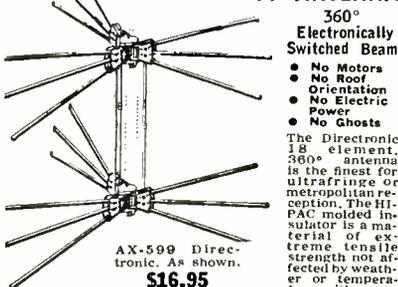

360° Electronically Switched Beam
• No Motors
• No Roof Orientation
• No Electric Power
• No Ghosts

The Directronic 18 element, 360° antenna is the finest for ultrafringe or metropolitan reception. The Hi-PAC molded insulator is a material of extreme tensile strength not affected by weather or temperature, either mechanically or electrically.

Included in the AX-599 "Servicemen's Array" are:
18 hi-tensile aluminum alloy elements
1 set of connecting stubs (3)
Universal U Clamps for masts to 1 1/2"
Directronic Beam Selector
75 feet of Tri-X Cable
1 stacked array per carton

AX-566 Directronic, 6 element Single	\$ 9.50
AX-566 Directronic, 12 element Stacked	14.25
AX-599 Directronic, 9 element Single	10.35

All above antenna prices include Tri-X Cable and Switch.

SOLD ONLY BY MAIL BY NATIONAL ELECTRONICS


Rocket All Channel CONICAL KITS

This sturdy, all-aluminum constructed TV antenna is designed for broad-band reception on all TV channels, plus FM. High Gain, 4 to 1 front to back ratio. For use with 72-150-300 ohm lines. Low inception angle.

METROPOLITAN KIT F-44 FRINGE AREA KIT F-44X
No. 1 \$8.95 No. 2 \$13.95
Rocket Conical Kits contain same accessories as Yagi Kits above.
Any merchandise listed above may be purchased separately at prices shown.

SOLD ONLY BY MAIL BY NATIONAL ELECTRONICS
Prices subject to change without notice. All prices F.O.B. Cleveland—Do not remit more than complete purchase price. Pay shipping charges on receipt of goods. 25% on C.O.D. orders, please. Money back guarantee.

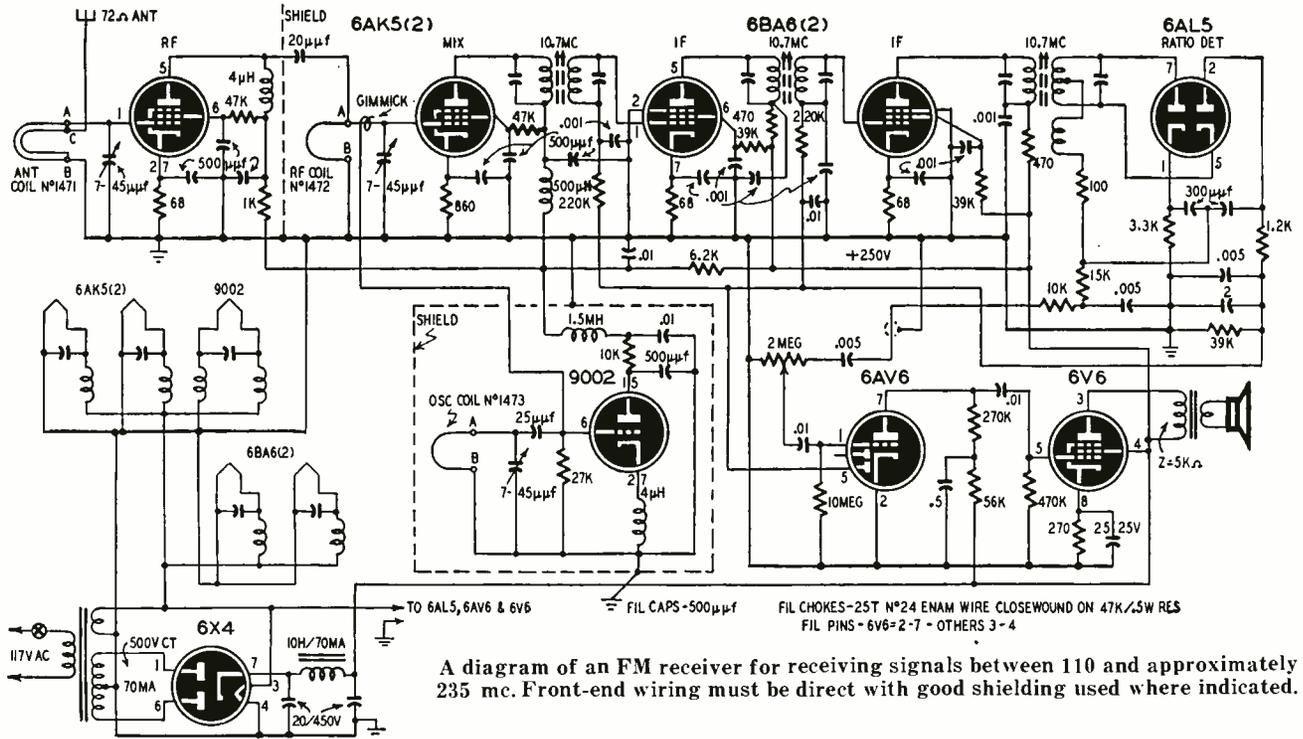National Electronics OF CLEVELAND
THE HOUSE OF TV VALUES
203 Delco Bldg. • Cleveland 3, Ohio



A diagram of an FM receiver for receiving signals between 110 and approximately 235 mc. Front-end wiring must be direct with good shielding used where indicated.

150-MC EMERGENCY RECEIVER

? Please prepare a diagram of a sensitive superhet receiver for receiving the signal from a 156.57-mc police transmitter. Please show how the frequency of this receiver may be shifted to receive another station near 130 mc.—A. R. S., Stockton, Calif.

A. The diagram can be used for any FM receiver as long as the coils in the tuner section cover the required band. The coils specified are made by J. W. Miller Co. and are suitable for use in the range from 110 to 235 mc. The tuning capacitors specified are for use in the 150-mc range. Other sections of this band can be covered by using larger or smaller tuning capacitors.

Shielding must be used between the r.f. amplifier, mixer, and oscillator circuits to prevent interaction and feedback. The set is designed for spot-frequency work, so the tuning capacitors may be ceramic trimmers. If continuous tuning is desired, a 3-gang tuning capacitor is recommended. In this case, you may have to pad the oscillator circuit to provide proper tracking. The i.f. amplifier may be aligned more sharply than for conventional FM broadcast sets. This provides more gain, so take care to avoid oscillation in the i.f. strip.

PREAMP AND EQUALIZER UNIT

? I have an old Philco receiver which has a triode-connected 6F6 as a driver for push-pull power amplifiers in a dual-channel audio output system. I like the performance of the audio channel and would like to convert it into an amplifier for high-fidelity music and public-address work.

Please draw a circuit of a preamplifier, mixer, and equalizer for two crystal microphones and a crystal pickup. Please include an input circuit for a radio tuner when the mikes and pickup are not being used. I want separate high- and low-frequency tone controls and a simple loudness control.—C. J. M., Broad Channel, N. Y.


A. The diagram shows a 6SJ7 used as mixer and preamplifier for the microphones and pickup. The output of the preamplifier or the input from a tuner is fed through bass and treble controls to cascade-connected 6J5 voltage amplifiers. These two stages provide the required gain while compensating for the insertion losses of the equalizer and the IRC loudness-control circuits.

A single 6SN7-GT may be substituted for the pair of 6J5's. The driver and output transformers which you have are probably satisfactory. However, if


you replace the driver transformer, be sure to select a unit which supplies a minimum plate load of 10,000 ohms.

ADDING HEADPHONES

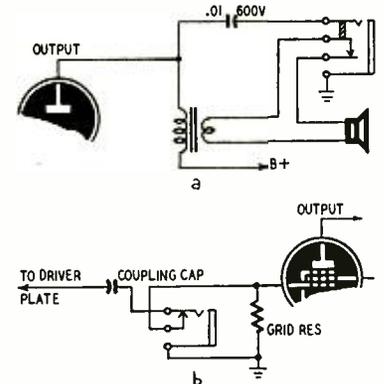? I would like to add a pair of headphones to my receiver, which has a single 47 in the output stage. The jack must be wired so the speaker is cut out when the phones are plugged in.—J. M., La Grangeville, N. Y.



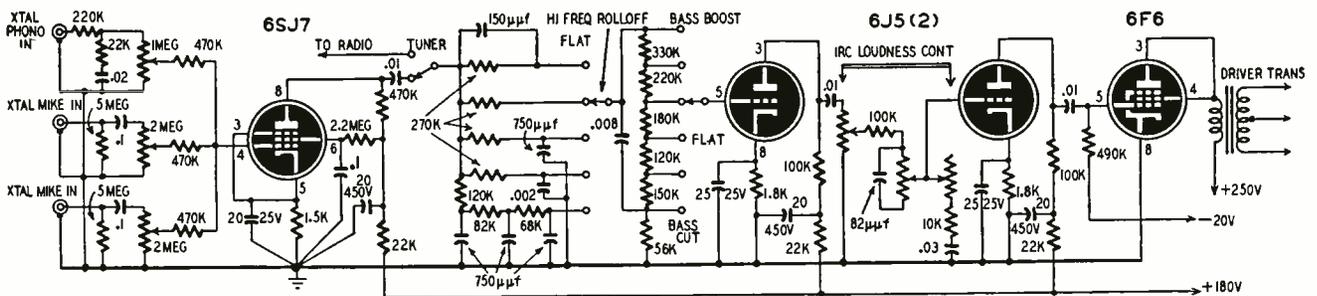A. The phone jack can be installed in the plate or grid circuit of the output tube. The volume will be somewhat greater when the phones are inserted in the plate circuit as shown at a, but the




This unit can be used with most amplifiers by omitting the 6F6 and using coax to couple the last 6J5 to the amplifier.

volume obtained with the circuit at *b* is usually adequate for most purposes. These circuits can be used for most sets having single-ended output stages. If the receiver is an a.c.-d.c. model, a .006- μ f, 600-volt capacitor should be used between the frame of the jack and ground.

OSCILLATOR-MIXER CIRCUIT


? I am planning to use parts from a small a.c.-d.c. set (Hallicrafters S-41G) to construct an a.c. receiver. I would like to use a 6SA7 mixer and a 6J5 as a separate oscillator. Please draw a circuit showing how the antenna and oscillator coils of the S-41 can be used in this type of circuit.—A. B., New York, N. Y.

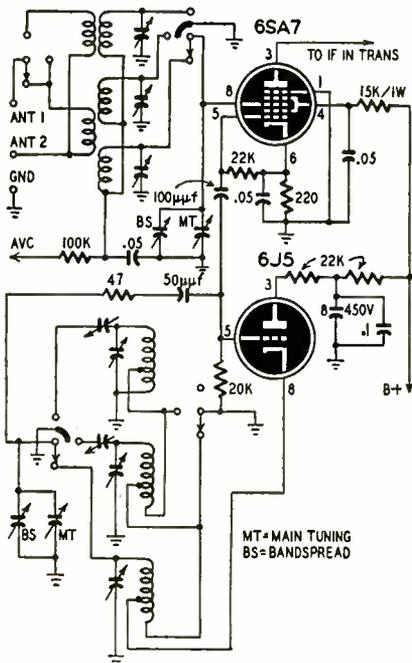A. The diagram shows how the coils can be used in the oscillator-mixer circuit. Compare this circuit with the original schematic to determine the proper connections to the coil and band switch.



SCOPE SWEEP GENERATOR

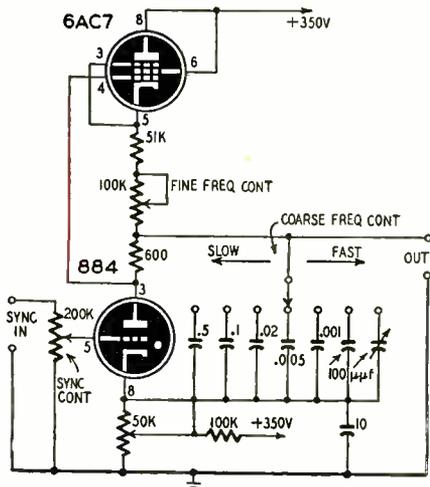? I am modifying a BC-412 radar indicator so it can be used as an oscilloscope. I have not been able to find a circuit of a sweep generator which has



the required linearity. Can you recommend a circuit?—N. C. O., Seattle, Wash.


A. Having experimented with a number of different oscillators as sweep generators, we believe that the circuit described by Eugene L. Langbergh (*Electronics*, November, 1946) to be more linear and easier to operate than most of the others which we have tried. Tubes and components are not critical.

Vary the 50,000-ohm variable resistor for greatest linearity with the generator delivering 8 to 13 volts at its output terminals. Varying the setting of this control causes some shift in calibration of the fine frequency control, so adjust this before calibrating the sweep circuit.

QUERY ON S-38 RECEIVER

? My Hallicrafters S-38 receiver has a defective b.f.o. circuit. When the shield of the coil is completely on or completely off, I cannot get a beat with incoming signals. However, the unit works properly when the shield is covering about half the coil. I am using a small piece of metal foil wrapped around half the coil as a temporary repair. Can you tell me what is wrong and how I may repair it.—R. L. E., Ambler, Pa.

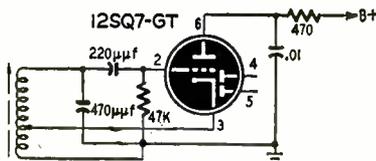A. If the set is properly aligned and you cannot get the b.f.o. to operate properly by adjusting the C. W. PITCH CONTROL, the trouble is probably caused by a change in the value of the 220- or 470- μ f capacitors or the 47,000-ohm grid resistor. Try replacing these components with others known to be of the correct value. The position of these parts is shown on the diagram.




ANTENNA PROBLEM

? For the last four years, my 75-meter transmitting antenna has been a dipole fed with 75-ohm transmitting-type ribbon line. Up until a week ago, the antenna resonated at 3990 kc and worked out nicely. Overnight, it refused to take a load anywhere in the band. There was no measurable change in the length of the Copperweld flat-top. The feeders checked good with an ohmmeter. Checking the antenna with a grid-dip meter and with a v.f.o., we found that it resonated sharply at 4400 kc. Since there were no changes in the installation or operating conditions, we cannot explain this change. Can you offer any suggestions?—H. R. C., New York, N. Y.

A. Since all conditions are the same, we suspect that the feeders are the source of the trouble. According to an Amphenol bulletin, the life of ribbon-type lines is not more than 16 months when exposed to sunlight. Deterioration of the polyethylene changes the power factor and characteristic impedance of the line. Since the line is much too old to perform at its best, we believe that replacing it will clear up the trouble.

—end—

Become an Electrical Engineer

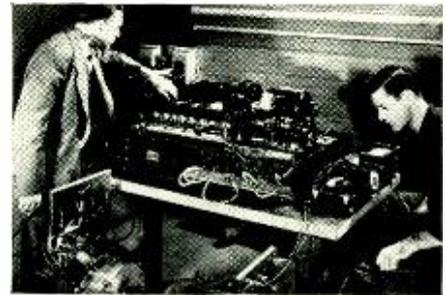

MAJOR IN ELECTRONICS



- B. S. Degree in 36 Months
- Radio-Television Technician Certificate in 18 Months

By 1954 there will be at least two positions for every engineering and technician graduate. This College offers a tested plan that permits you to enter these vast employment opportunities at an early date. First—you save a valuable year through optional year-round study. Second—you can receive advanced credit for prior training gained in the armed forces, other schools or field experience.

Enter Both Radio and Television Through This Plan

12 months or one-third of the B. S. degree course (Electronics major) — also brings you the Radio Technician's certificate. An added 6-month course qualifies you for the Radio-TV Technician's Certificate.

The Proven "UNIT CHASSIS SYSTEM"



of teaching was developed here. It "breaks down" the TV set by stages. You learn every component of all types and makes — and are prepared for future design changes, including the advent of color.

SPECIAL! Television Clinics

Ambitious Radio and TV Servicemen can enrol now in special one-month spring or summer clinics — to handle latest field service problems. Combine vacation with education.

Over 48,000 former students from all states and 23 overseas countries. Faculty of trained specialists. Modern laboratories and equipment. Nonprofit technical institute and college. 49th year.

MILWAUKEE

SCHOOL OF ENGINEERING
Founded 1903 • Milwaukee, Wis.

Terms open April, July, October, January

FREE — Write for "Occupational Guidance Bulletin," "Your Career" booklet, and Catalog.

- Milwaukee School of Engineering
Dept. RE 352, 1025 N. Milwaukee
Milwaukee, Wisconsin
- Without obligation send Catalog for
Electrical Engineering, B. S. Degree,
major in Electronics Power; Your
Career"; Occupational Guidance Bulletin
on: Radio-TV; Electrical Power;
 Welding; Heating, Refrigeration Air Conditioning.
 TV Service Clinic.

Name.....Age.....

Address.....

City.....Zone.....State.....

If veteran, indicate date of discharge.....

ALWAYS REPLACE WITH

QUAM

Adjust-A-Cone

SPEAKERS



THEY ARE
FIRST in
REPLACEMENT
FIELD

FIRST for
ORIGINAL
EQUIPMENT

The Speaker with the U-Shaped Coil Pot and the Adjustable Voice Coil.
A Complete Line with a Speaker for every Radio and TV set from 3" to a 15" coaxial; P.M. and Electro-Dynamic.

Write for Complete Catalog!

ALSO QUAM FOCALIZERS, ION TRAPS AND TRU-MATCH OUTPUT TRANSFORMERS

QUAM-NICHOLS COMPANY

521 E. 33rd Place, CHICAGO 16, ILL.

MAKERS OF QUALITY SPEAKERS FOR 27 YEARS, UNDER THE SAME MANAGEMENT

AN/APR-4 COMPONENTS WANTED

In any condition. Also top prices for: ARC-1, ARC-3, APR-1, APR-5A, etc.; TS-34 and other "TS-" and standard Lab Test equipment, especially for the MICROWAVE REGION; ART-13, BC-348, BC-221, LAE, LAF, LAG, and other quality Surplus equipment; also quantity Spares, tubes, plugs and cable.

ENGINEERING ASSOCIATES

438 Patterson Road Dayton 9, Ohio

PEN-OSCIL-LITE

Extremely convenient test oscillator for all radio servicing; alignment • Small as a Pen • Self powered • Range from 700 cycles audio to over 600 megacycles u.h.f. • Output from zero to 125 v. • Low in cost • Used by Signal Corps • Write for information.


GENERAL TEST EQUIPMENT
38 Argyle Ave. Buffalo 9, N. Y.

RETRACE LINES IN ADMIRAL SETS

In weak-signal areas, the best pictures are often obtained by operating the set with contrast reduced and brightness turned up. Under these conditions, several bright retrace lines may be visible in the picture. By feeding a portion of the vertical oscillator voltage to the grid or cathode of the picture tube, the brightness control can be turned up without retrace lines appearing.

On the 20A1, 20B1, 20T1, 20V1, 21A1, 21B1, and similar chassis, connect a 270,000-ohm, 1/2-watt resistor in series with the lead going from the grid (pin 2) of the picture tube to the junction of the arm of the brightness control and its bypass capacitor (see *b* in the figure). Connect a .05- μ f capacitor from the grid of the picture tube to the junction of wave-shaping network shown at *a*.

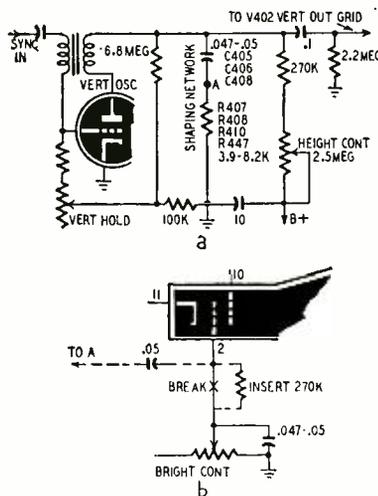On the 24D1, -E1, -F1, -G1, and -H1 chassis, connect the 270,000-ohm resistor as shown at *b*. Reverse the connections of the vertical wave-shaping network (R410 and C406) so the capacitor connects to the grid of V402 and the resistor connects to ground. Connect a .05- μ f capacitor from the grid of the picture tube to the junction of R410



Diagrams of typical Admiral vertical oscillator and brightness-control circuits. Pertinent codes used in the models discussed are:

- C405—Models 20A1, -B1, -T1, 20V1 and 21A1.
- C406—Models 24D1, -E1, -F1, -G1, and 20H1, and 21B1.
- C408—Models 20X1, 20Y1 and 20Z1.
- R408—Models 20A1, 20B1, and 21A1.
- R410—Models 24D1, -E1, -F1, -G1, and 24H1.
- R447—Models 20X1, 20Y1, and 20Z1.

and capacitor C406 to the wave-shaping network as described in the paragraph above.

To modify the 20X1, 20Y1, and 20Z1, connect the 270,000-ohm resistor as shown at *b* in the illustration. Replace the 3,900-ohm vertical wave-shaping resistor (R447) with an 8,200-ohm, 1/2-watt unit. Connect a .05- μ f capacitor between the grid of the picture tube and the junction of C408 and R447.

In the 30A1, 30B1, and 30D1 chassis, insert a 47,000-ohm, 1/2-watt resistor in

series with the lead from the cathode (pin 11) of the picture tube to the arm of the brightness control and the cathode bypass capacitor C325. Connect a .05- μ f capacitor between the cathode of the picture tube and the green lead of the vertical output transformer.—*Admiral Radio & TV Service Bulletin*

BLOWN FUSES IN SENTINELS

Blown fuses may be encountered in the Sentinel models 438, 439, 440, 441, 443, and 446 using chassis marked YA, YB, YC, and YD. Take a look at the 1-inch-long No. 8 self-tapping screw which holds the back to the chassis near the interlock plug. This screw may be long enough to short to one of the filament pins of the 6W4 or 6BY5-G rectifiers. If so, you can eliminate the condition by placing a 1/8-inch washer or washers under the head of the screw. If the set has a 2 1/2-ampere Slo-Blo fuse, replace it with a 3-ampere Slo-Blo unit.

A few chassis have a 1/2-ampere Slo-Blo fuse in the secondary circuit of the power transformer. If the screw touches the rectifier socket on this type chassis, the 1/2-ampere fuse will not blow. Check this possibility if the power transformer overheats.—*Sentinel Service Bulletin*

ASTORIA (R. H. MACY) 816

I had difficulty with horizontal sync phase at the 6AL5 phase detector tube. The picture was split down the middle by a gray bar, and the right and left-hand sides of the picture were transposed. This set has no centering controls. I discovered that the feedback capacitor between the horizontal flyback transformer and the phase detector was leaking under load. It checked O.K. in a capacitor checker with 500 volts on it, but when it was in the set, it allowed enough high voltage to leak through to disturb the comparison voltage at the phase detector. Replacing this capacitor corrected the phase shift.—*G. McVity*

HIGH-VOLTAGE FAILURE

When checking TV receivers for lack of high voltage on the picture tube, it is a good idea to check the setting of the horizontal-drive trimmer capacitor. In many new sets, this trimmer has been turned all the way in to eliminate vertical overdrive lines at the left of the picture. When the receiver ages, there is a lack of horizontal drive on the output tube. This results in little or no high voltage. Sometimes, you may find the trimmer completely shorted to ground.—*Wilbur J. Hantz*

EMERSON 664B (CHASSIS 120133B)

If the horizontal sync is unstable and cannot be corrected by changing the sync amplifier and horizontal oscillator tubes, check the plate voltage at pin 5 of the horizontal oscillator tube. If the voltage is incorrect, check the 150,000-ohm resistor R78 in the plate circuit. This resistor sometimes increases to 200,000 ohms or more. Replacing it with a resistor of the correct value restores the set to perfect operation.—*Peter Hickey*

—end—




**THE FUND REACHES
\$9,274.00**

**HELP -
FREDDIE-WALK
FUND**

Readers from all over the world—from Spain, Italy, Sweden, and Hawaii, to mention a few spots—are still responding enthusiastically to our appeal for funds to "help Freddie walk." Freddie, the young son of radio technician Herschel Thomason, of Magnolia, Arkansas, was born without arms or legs, and contributions from RADIO-ELECTRONICS readers are largely responsible for making available the means by which he will become a useful member of society when he grows older.

This month the "Freddie" fund reaches a grand total of almost \$9,300.00. We are particularly pleased to note two "group" contributions from the members of the U.S. Navy. \$72.00 was received from the Enlisted Electronic Technicians of the "U.S.S. Midway," who express the hope that "if our contribution was noticed by other men in the fleet it might instigate further contributions from Navy men in our field of work."

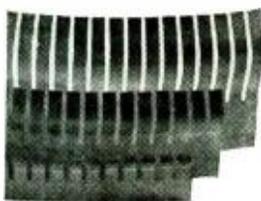And from Gyro & Battery Repair, 9th Division, "U.S.S. Delta" comes \$13.70, with the following note attached: "Everything once it is started should have a purpose. Well, about six weeks



FINGER STOCK

**Electrical Weather-Stripping
by Eimac —**

Now Available!

Silver-plated, spring alloy, pre-formed finger stock especially suited for electrical "weather-stripping" for TVI-proofing cabinet access doors, etc. Also ideal for making coaxially constructed tube connections and many other uses. Available in 17/32", 31/32", and 17/8" widths.

Write for new Eimac Catalogue
Summary showing Eimac tubes
and other accessories.



EITEL - McCULLOUGH, INC.
San Bruno, California



NOW AVAILABLE

**TO THE SERVICEMAN
AND EXPERIMENTER**

**THE FAMOUS
K-TRAN**



• THE FINEST
MINIATURE
I. F. TRANSFORMER
EVER
MANUFACTURED!

• ONLY 2 1/4" HIGH
BY 3/4" SQUARE

• SHELL CORE PERMEABILITY TUNED STABLE SILVER
MICA FIXED CONDENSERS — NOT MICA COM-
PRESSION TUNED.

CAT. NO.	ITEM	NET PRICE
12-H1	262 KC INPUT I.F. TRANS	51 50
12-H2	262 KC OUTPUT I.F. TRANS	1 50
12-H6	262 KC OUTPUT I.F. TRANS WITH DIODE FILTER CAPACITORS	1 59
12-C1	455 KC INPUT I.F. TRANS	1 32
12-C2	455 KC OUTPUT I.F. TRANS	1 32
12-C6	455 KC OUTPUT I.F. TRANS WITH DIODE FILTER CAPACITORS	1 41
1463	10.7 MC INPUT OR INTERSTAGE F.M. TRANS.	1 65
1464	10.7 MC F-M DISCRIMINATOR	1 98
1465	10.7 MC F-M RATIO DETECTOR	1 98



The "K-TRAN" is distributed
nationally to the jobber only
by J. W. Miller Company.

* Manufactured under K-TRAN Patent
Numbers 2435a30 and 2429a08 of Automatic
Manufacturing Corp.

J. W. MILLER COMPANY
5917 S. MAIN ST. LOS ANGELES, CALIF.

Get This Valuable Book

Just for Examining COYNE'S New 6-Volume Set

FREE



Applied Practical Radio-Television

Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Just off the press! Gives complete wiring circuits and diagrams on the latest Radio and Television Sets. Easy-to-read, large 8 1/2 x 11" pages, with full instructions on how to read and use the diagrams. A "must" in every Radio and Television service-man's repair kit. You get this valuable book as a FREE Gift for asking to see Coyne's great new 6-book set, "Applied Practical Radio-Television"!

**ON 7 DAY
FREE
TRIAL!**



Here's "Know-How" That Makes You Worth More!

You'll get into the big money faster in TELEVISION-RADIO if you know where to find the answer to servicing problems. Coyne's great new 6-volume set gives you all the answers—quickly! For basic "know-how" that is easy to understand, you'll find everything you want in volumes 1 to 5 which contain over 5000 practical facts and data. They cover every step from principles to installing, servicing, trouble-shooting and aligning all types of radio and TV sets. So up-to-date it includes COLOR TV and UHF adapters and converters.

762-Page Television Cyclopedic Included

And then, for speedy on-the-job use, you get volume 6—the famous Coyne TELEVISION CYCLOPEDIA. It answers today's television problems on servicing, alignment, installation and others. In easy-to-find ABC order, cross indexed. Use this 6 volume TV-RADIO LIBRARY free for 7 days; get the valuable Servicing Book ABSOLUTELY FREE!

SEND NO MONEY!

Just mail coupon for 6-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$23.00 plus postage is paid. (Cash price \$22.00). Or you can return the library at our expense in 7 days and owe nothing. YOU BE THE JUDGE. Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

FREE BOOK — FREE TRIAL COUPON!

COYNE ELECTRICAL & TELEVISION-RADIO SCHOOL, Dept. 32-T1
500 S. Paulina St., Chicago 12, Ill.

YES! Send 6-volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name.....Age.....

Address.....

City.....Zone.....State.....

Where Employed.....

() Check here if you want library sent COD. You pay postman \$22 plus COD postage on delivery. 7-day money-back guarantee.

COYNE

ELECTRICAL & TELEVISION-RADIO SCHOOL
500 S. Paulina St., Dept. 32-T1 Chicago 12, Ill.

**for dependable sound,
INDUSTRY relies on
ATLAS**



DR Double-Reentrant Projectors



Paging & Talk-Back Speakers



ALNICO-V-PLUS Driver Units



Dual Speakers



FULL-GRIP, VELVET-ACTION Mike Stands

DEPENDABLE QUALITY:

The latest electro-acoustic research and engineering—and over 20 years of manufacturing know-how—are behind every ATLAS product.

DEPENDABLE SERVICE:

Coast-to-coast and around the world today—in every Industrial, Marine, Railroad, Military, Educational, Civic, U.S. and Foreign Government application—under every kind of climate and noise condition—ATLAS sound equipment is famous for highest efficiency and durability. That's the proof of ATLAS performance dependability.

DEPENDABLE DELIVERY:

Yes, ATLAS gives our Government highest priority. And yes, we too feel the pinch of material shortages. But our customers will continue to get our usual dependable delivery—because we believe in equitable and dependable distribution to all ATLAS users.

DEPENDABLE PROFITS:

Completeness of line, excellence of product, dependable delivery, right prices—that's the ATLAS combination that means high, steady Industrial Sound profits for you!

JUDGE for yourself. COMPARE ATLAS at your local Jobber today. See why ATLAS is the preferred line for utmost dependability. Write NOW for FREE latest Catalog 551.

ATLAS SOUND CORP.
1443-39th Street, Brooklyn 18, N. Y.
In Canada: Atlas Radio Corp., Ltd., Toronto, Ont.



ON-THE SPOT BATTERY RECORDER

WALKIE-RECORDALL 8 lb. miniature BATTERY RECORDER-PLAYBACK Continuous, permanent, accurate, indexed recording at only 5¢ per hr. Instantaneous, permanent playback. Picks up sound up to 50 ft. Records conferences, lectures, dictation, 2-way phone & sales talks; while walking, riding or flying. Records in closed briefcase with "hidden mike"! Write for details.

MILES REPRODUCER CO., INC.
812 BROADWAY Dep't RE-3 NEW YORK 3, N. Y.

Miscellany

before Christmas we started putting odd amounts of change in a large glass jug every time we had a cup of coffee. And everyone knows the Navy drinks coffee pot after pot all day. All this money and no reason, but then the newspaper piece about Freddie was pasted up on the jug. I don't know if we drank 1,370 cups of coffee, but here we are . . ."

Also of special note is a contribution of \$17.00 from the Young Women's Society of Christian Service of the Methodist Church of Centralia, Pa., collected through the efforts of Mrs. Larry Minnish, Secretary, who writes they all "want to help a little, most of us having little boys, too."

Contributions are still urgently needed; and no contribution is too small for our notice and acknowledgment. Please continue to send them from time to time whenever you are able. Make all checks, money orders, etc., payable to Herschel Thomason. Please address all letters to:

Help-Freddie-Walk-Fund
c/o RADIO-ELECTRONICS
25 West Broadway
New York, N. Y.

FAMILY CIRCLE CONTRIBUTIONS

Balance as of December 19, 1951 . . .	\$511.50
Miss Ann Albino, New Haven, Conn. . .	1.00
Mary Krull, Passaic, N. J.	1.00
Mrs. M. J. Pagliaro, Richmond, Calif. . .	2.00
Mrs. S. Weinzimer, New York City . . .	2.00

FAMILY CIRCLE Contributions received to January 18, 1952 \$517.50

RADIO-ELECTRONICS CONTRIBUTIONS

Balance as of December 19, 1951 . . .	\$8,594.60
Anonymous, No. Hollywood, Calif. . .	5.00
Anonymous, Palo Alto, Calif.	1.00
Anonymous, Lake Odessa, Mich.	1.00
Walter J. Bluhm, Jamaica Plain, Mass. . .	5.00
Dominic & Mary Cacciola, Phila., Pa. . .	1.00
V. L. Daniels, W91ZL, Racine, Wisc. . . .	5.00
Meyer Dumanis, New York City	6.00
Enlisted Electronic Technicians of the U.S.S. Midway, c/o F.P.O., New York City	72.00
William Evans, Jr., McLean, Va.	1.00
A Friend, Knoxville, Tenn.	1.00
Friends of Freddie, Worcester, Mass. . .	2.00
Lt. Louis J. Frketic, c/a F.P.O., New York City	2.00
Gyro & Battery Repair, 9th Division, U.S.S. Delta, c/o F.P.O., San Francisco, Calif.	13.70
C. T. Haley, Chicago, Ill.	1.00
Johan Jensen, Goteborg, Sweden	1.00
William F. Klein, St. Louis, Mo.	5.00
Harry Khosrofan, Washington, D. C. . . .	1.00
John L. Knoerl, Buffalo, N. Y.	1.00
C. J. Loramie, Marquette, Mich.	2.00
"Merry Christmas from out Texas"20
Morris Moses, Baldwin Township, Pittsburgh, Pa.	5.00
Joe Rackey, Milwaukee, Wisc.	1.00
Gray Trembly, Somerville, Mass.	10.00
G. Carrol Utermahlen, W3HVD, Baltimore, Md.	1.00
Mr. & Mrs. David W. Wothe, Green Bay, Wisc.	1.00
Young Women's Society of Christian Service, Centralia Methodist Church, Centralia, Penn.	17.00

RADIO-ELECTRONICS Contributions	\$8,756.50
FAMILY CIRCLE Contributions	517.50

TOTAL RECEIPTS to January 18, 1952 \$9,274.00

We Helped . . .

WON'T YOU?



A message from **ALBERT FINKEL** Vice-President of



. . . "It was very easy to arrange a blood donor program for our people at JFD. All we did was phone our local Red Cross Office. They did the rest. And everyone, from top management to employee wanted to contribute, to help our boys in Korea."

DON'T HESITATE!

Call your **LOCAL RED CROSS OFFICE TODAY!**



New WIRE CUTTER AND STRIPPER

Big TIME SAVER

Snips wire to 18 gauge . . . gets in hard to reach places . . . perfect for holding wire or other small parts. Contact your radio parts jobber or Jim Handy representative.

H jim HANDY
EASY ACTION WIRE CUTTER
C & G Mfg. and Sales Co.
Box 1525 Columbus, O.

HAM WINS SUIT!

YUP! Hundreds of hams all over the U.S. have earned free suits of clothes just by selling their new and used radio gear for cold, hard cash. Why don't you?

Round up everything you have in electronics. Tell us what you've got.

WARNING: We can't be held responsible if you faint with surprise when you see the high prices we pay!

DO IT UP RIGHT—WRITE RIGHT NOW!
COLUMBIA ELECTRONICS SALES
522 S. San Pedro St. Los Angeles 13, Calif.

THE PRICES SPEAK FOR THEMSELVES!

RADIO & TV TUBES

At Better Than 50% Off List Price!

STANDARD BRANDS—FULLY GUARANTEED

OZ4 \$.77	6SG794
1A5G994	6SH7 1.04
1A7GT 1.03	6SJ7GT77
1B3GT 1.27	6SK7GT84
1H5GT77	6SL7GT 1.14
1LA6 1.27	6SN7GT 1.04
1LB4 1.27	6SQ7GT69
1LC5 1.27	6SS794
1LC6 1.27	6T8 1.39
1LD5 1.27	6U594
1LE3 1.27	6V6GT94
1LH4 1.27	6W4GT84
1LN5 1.27	6X469
1N5GT94	6X5GT69
1Q5GT 1.27	7A5 1.04
1R594	7A884
1S4 1.03	7B484
1S584	7B584
1T494	7B684
1T5GT 1.27	7B784
1U494	7C584
1U584	7C684
1X2 1.27	7F7 1.04
3Q4 1.04	7F8 1.54
3Q5GT 1.14	7Q784
3S494	7Y484
3V494	12AH7GT 1.27
5T4 1.16	12AL594
5U4G69	12AT669
5V4G 1.14	12AT7 1.39
5W477	12AU7 1.14
5Y3GT52	12AX7 1.14
5Y4G69	12BA684
6A7 1.04	12BE684
6A8GT 1.04	12J5GT69
6AB494	12K7GT 1.04
6AB7 1.56	12SA7GT84
6AC7 1.39	12SF594
6AG5 1.27	12SF794
6AG7 1.54	12SG794
6AH6 1.89	12SJ7GT77
6AK5 1.89	12SK7GT84
6AL594	12SL7GT 1.14
6AL7GT 1.27	12SN7GT 1.04
6AQ594	12SQ7GT77
6AQ684	12SR7 1.04
6AQ7GT 1.14	14A7 1.04
6AS7G 3.98	14B6 1.04
6AT669	14Q7 1.04
6AU684	19BG6G 2.94
6AV669	19T8 1.39
6AX5GT77	25A6 1.27
6BA684	25L6GT84
6BE684	25W4GT94
6BG6G 2.32	25Z577
6BC594	25Z6GT69
6BH694	35A584
6BQ6GT 1.54	35L6GT84
6C477	35W462
6C5GT77	35Y484
6C6 1.04	35Z384
6CD6G 2.94	35Z5GT62
6D6 1.04	4194
6E5 1.04	4294
6F5GT77	4394
6F6GT77	4594
6H6GT84	47 1.39
6J5GT69	50A5 1.04
6J6 1.39	50B594
6J7GT94	50L6GT77
6K6GT77	7577
6K7GT 1.04	7677
6L6G 1.72	7794
6N7GT 1.14	7894
6Q7GT84	8061
6SA7GT84	117L7GT 1.89
6SC794	117N7GT 1.89
6SF5GT84	117Z369
6SF794	117Z6GT 1.14

ASSORTED TUBULAR 100 CONDENSERS

All Are Standard Brands
All Are Desirable Sizes

\$15.00 Value

Only **\$4.69**

ASSORTED 100 PILOT LIGHTS

#44, 46, 47 & 51 only **\$4.83**

ASSORTED 100 SOCKETS

Octal, Loctal & Miniature, only **3.92**

ASSORTED 100 KNOBS

Screw & Push-on only **2.97**

TUBE CARTONS in Lots of 100

SMALL PEANUT 1" x 1" x 2 1/8" **\$.89**

LARGE PEANUT 1" x 1" x 2 3/4" **.98**

GT TYPE 1 1/4" x 1 1/4" x 3 3/8" **1.06**

SMALL G 1 1/2" x 1 1/2" x 4 1/2" **1.39**

LARGE G 2" x 2" x 5" **1.59**

EXTRA LARGE 2 1/4" x 2 1/4" x 6 1/2" **2.97**

PM SPEAKERS (ALNICO #5)

Brand New Factory Guaranteed Stock
1 oz. mag. on 3" to 6", heavier mag. on 8" & 12"

3" **\$.98** | 6" **1.98**

4" **1.29** | 8" **3.97**

5" **1.49** | 12" **6.94**

LATEST **RADIOS** Complete Ready to Play

1952 MODEL

DEWALD—ROUND THE WORLD PORTABLE

3-Way, A.C.-D.C. & Batteries.
3-Bands, Broadcast, Short Wave, Foreign.
Beautiful leatherette case, whip antenna **\$39.84**

STANDARD BRAND RADIO

5-TUBE SUPER, TABLE-MODEL

A.C.-D.C. built-in antenna.
Streamlined plastic cabinet in Walnut or Ivory. **14.32**

STANDARD BRAND RADIO

WITH SESSIONS CLOCK

Goes ON & OFF automatically.
Style, Quality & Performance **18.97**

CUSTOM-BUILT AUTO RADIOS

FORD 1949-50-51 | PLYMOUTH 1949-50-51

DODGE 49-50-51 | CHEVROLET 49-50-51

STUDEBAKER 50-51 | HUDSON 48-49-50-51

HENRY J. 51

All List at \$59.95

Your Price (Any Model)
Complete ready to install
Including Easy Instructions. **\$36.97**

AUTO ANTENNA, fits all cars \$2.49

ASSORTED 1/2 WATT 100 RESISTORS

Just what you use in Radio & TV Repairs.

\$12.00 Value

Only **\$3.97**

TV CONDENSERS — 85° — C

.05 MFD — 2500 Volts **\$.27**

.1 MFD — 2500 Volts **.29**

.05 MFD — 3000 Volts **.36**

.003 MFD — 6000 Volts **.28**

.01 MFD — 6000 Volts **.37**

.05 MFD — 6000 Volts **.39**

.0005 MFD — 7500 Volts **.29**

.005 MFD — 7500 Volts **.32**

.003 MFD — 7500 Volts **.34**

.03 MFD — 7500 Volts **.39**

Worth 4 times as much, for example the .05-6000V condenser lists for \$1.60.



SUPERIOR POCKET SIZE VOLT-OHM MILLIAMMETER

SENSITIVITY—1000 ohms PER VOLT
SIX—A.C. VOLTAGE RANGES
0-15/30/150/300/1500/3000 volts
SIX—D.C. VOLTAGE RANGES
0-7.5/15/75/150/750/1500 volts
FOUR—D.C. CURRENT RANGES
0-1.5/15/150 MA 0-1.5 Arms
TWO—RESISTANCE RANGES
0-500 Ohms 0-1 Megohm
PLASTIC CASE—3 1/4" x 8 7/8" x 2 1/4"

Complete with batteries, test leads, instructions and factory guaranty. **\$14.90**

\$5.00 SAPPHIRE PHONO NEEDLE **\$.58**

WEBSTER 3-SPEED CHANGER **24.96**

PHONO MOTOR, 78 RPM, complete **3.18**

PHONO MOTOR, 78, 45, 33 RPM, **4.97**

UNIVERSAL PICKUP, 78, 45, 33 RPM **4.63**

FAMOUS MAKE CRYSTAL PICKUP **2.44**

CRYSTAL CARTRIDGE, popular type **1.42**

PHONO AMPLIFIER, incl. 3 tubes **3.87**

BROOKS INVERTER, DC to AC, 50 W **8.95**

QUALITY STAND MICROPHONE **5.76**

GRILL CLOTH, gold, 14" x 13" **.49**

OUTPUT TRANSFORMER (50L6) **\$.36**

OUTPUT TRANSFORMER (6K6) **.52**

UNIVERSAL OUT. TRANS. (any tube) **.89**

IF TRANSFORMER, 456KC **.49**

IF TRANSFORMER, FM-10.7MC **.58**

VARIABLE COND., 2 gang, super **.59**

VOL. CONT. L/S, 1/4, 1/2, 1, 2 meg. **.24**

VOL. CONT. W/S, 1/4, 1/2, 1, 2 meg. **.47**

AC-DC OVAL ANTENNA LOOPS **.19**

ANTENNA HANK, 15' on handy spool **.08**

RESISTANCE CORD, 150 ohms **.19**

6' LINE CORD, complete with plug **.16**

1 POUND ROSIN CORE SOLDER **\$.59**

UNIVERSAL BALLAST TUBES, (3) **1.18**

67 1/2 V. BATTERY, 3 3/8" x 2 3/4" x 1 3/8" **1.69**

TOGGLE SWITCH, DPDT **.46**

SELENIUM RECTIFIER, 75 mills **.59**

SELENIUM RECTIFIER, 100 mills **.69**

300 OHM TWIN-LEAD WIRE, 100' **1.98**

TV POWER TRANSFORMER, 295 ma **6.11**

72 OHM CO-AX CABLE WIRE, 100' **4.84**

TV TABLE ANTENNA **1.99**

TV WINDOW ANTENNA, Gyro Tenna **4.97**

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N. Y.

MARCH, 1952

BE "ECONOMY-WISE" WITH

GREYLOCK

TERRIFIC TUBE BUYS!

All tubes listed below carry 6 month Guarantee—exception only burnouts and breakages. At these sensationally low prices, these tubes must be ordered in quantities of AT LEAST 10 ASSORTED TYPES add 10% for orders under 10 tubes. All individually boxed in attractive Greylock Cartons.

1L4	6AT6	6J5GT	12AUG
1S5	6AUG	6J7GT	12A8GT
1U4	6AV6	6S4	12BA6
1U5	6BA6	6SK7GT	12F5GT
3Q4	6BE6	6V6GT	12BE6
3V4	6C4	6W4GT	25Z5
5Y3GT	6C5GT	6X4	35W4
6AL5	6C6	6X5GT	35Z5GT
6AQ5	6CB6	12AT6	117Z3

YOUR NET COST EACH **49^c**

0Z4M	6AR5	12AUG	35B5
1R5	6R7GT	12AV6	35C5
1T4	6S7GT	12AX7	50C5
3S4	6SN7GT	12SK7GT	50L6GT
5X4G	6U4GT	25L6GT	

YOUR NET COST EACH **59^c**

1V2	6BC5	12AX4GT	12SQ7GT
5U4G	6SA7GT	12BA7	25Z6GT
6AB4	6SL7GT	12J5GT	35Y4
6AQ6	12AL5	12Q7GT	50B5
6AS5	12AV7	12S8GT	80

YOUR NET COST EACH **69^c**

1LC5	6BA7	7A7	12K8GT
6AG5	6BQ6	7E5	12SA7GT
6AK5	6T8	7N7	12SN7GT
6AK6	6Y6G	7X7	25B6GT
			35L6GT

YOUR NET COST EACH **79^c**

1LA4	1N5GT	6BH6	6J6
1LN5	1X2	6BJ6	6SG7
			7A8
			12AT7

YOUR NET COST EACH **89^c**

12BH7	6AC7	14C5	7C7
19T8	32L7GT	1A7GT	5Z3

YOUR NET COST EACH **99^c**

SPECIAL! 6AR6 \$2.49



SPEAKER SPECIALS

Permanent Magnet—Alnico No. 5 Slugs	
3" PM..... .88 oz.....	\$1.09
4" or 3" PM..... .68 oz.....	1.29
6" PM..... 1.0 oz.....	1.59
6"x9" PM..... 3.16 oz.....	3.49
8" PM..... 2.15 oz.....	3.69
10" PM..... 6.8 oz.....	5.95
12" PM..... 3.2 oz.....	4.95

AUTO SPEAKERS

7/4" 4-ohm dynamic less output.....	\$2.19
7/4" PM less output.....	4.95



HIGH VOLT. FLYBACK TRANSFORMER 14K VOLTS

Used for 16", 17" round or rectangular tubes. Good for conversion and replacement use. Many set mfrs. used this flyback transformer in their sets and paid more than this for them! Order #B-2612 **\$2.99**

GREYLOCK "BONDED" ELECTROLYTIC CONDENSERS

Guaranteed Fresh Stock

LOTS OF 10 YOUR ASSORTMENT					
Mfd.	W.V. DC	Net each	Mfd.	W.V. DC	Net each
16	150	.29	40 x 40	150	.45
24	150	.35	50 x 30	150	.45
30	150	.35	8	450	.29
40	150	.39	8 x 8	450	.49
20 x 20	150	.39	16	450	.39
20 x 40	150	.39	30	450	.44
30 x 30	150	.44	40	450	.49

Above prices are for minimum quantities of 10 asstd. condensers. Deduct additional 10% discount in lots of 100 assorted condensers.

WHILE THEY LAST! FAMOUS MAKE TV BOOSTER
List \$2.50—Order #Q-001 **16.95**
MANY ADDITIONAL VALUES!
Write for our latest supplement and complete catalog C-3.

4 ELEMENT CONICAL ANTENNAS

Constructed of reinforced butt seam aluminum elements and strong steel cross bars; ruggedized insulators.

SINGLE Order #P-003 **\$3.99**
STACKED Order #P-004 **\$8.29**

Extra elements for conicals make fan-flector type.

P-009 Low Band Elements, each **49¢**
P-010 High Band Elements, each **35¢**

CHIMNEY MOUNTS #E-1585.....Only 99¢

TERMS: Net C.O.D., F.O.B. New York City. 25% Deposit on all C.O.D. orders.

"A Trusted Name in Radio"
GREYLOCK ELECTRONICS SUPPLY CO.
115 Liberty Street - New York 6, N. Y.

Radio Thirty-Five Years Ago

In Gernsback Publications

HUGO GERNSBACK Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some of the larger libraries still have copies of ELECTRICAL EXPERIMENTER on file for interested readers.

MARCH, 1918 ELECTRICAL EXPERIMENTER

- President's Speech to World Via Cable and Radio
- How U-Boats Send Radio 1,000 Miles, by H. Winfield Secor
- A War-Time Suggestion To Radio Amateurs, by Howard S. Pyle, U.S.N.
- Women Now Study Wireless
- An Exceptional Amateur Radio Station Visiting Arlington via the Talo Club, by W. J. Howell
- The Design and Use of the Wave-Meter, by Morton W. Sterns
- "Secret Service" Pocket Radio Receptor, by Harry E. Fuchs
- Hy-Tone Tester for Minerals and Code Practice, by Curtis Kissell
- The How and Why of Radio Apparatus, by H. Winfield Secor
- A Good Substitute for a Practice Buzzer, by Paul G. Watson
- An Improved Radiophone Arc Gap, by Seefred Bros.

AUDIO FEEDBACK DESIGN

A number of readers have asked for a list of reference texts to supplement the series of articles which appeared in RADIO-ELECTRONICS between October, 1950, and November, 1951. There is, unfortunately, no book which I would recommend that the average reader buy just for its treatment of negative feedback. If there had been, the series of articles would not have been presented. The books mentioned below are not being condemned when I say this, because they do not claim to deal exclusively with negative feedback, which occupies only the place taken by bread on Falstaff's bill at the inn. Examine these books and decide for yourself whether they contain too much mathematics, and whether the other material in them is what you want.

The following list is not complete. These are only the books in my office, on my desk at home, or remembered from past reading.

1. **Network Analysis and Feedback Amplifier Design**, H. W. Bode: Van Nostrand. Bode knows more about feedback than most of us will ever want to know. This book was planned as a course of lectures to Bell Laboratories engineers and I would say was for "college graduates only."

2. **Radio Engineers Handbook**, F. E. Terman: McGraw-Hill. The handbook seems to me to be a better value for the money than Terman's *Radio Engineering*. Feedback is dealt with in two instances—under circuit theory, pp. 218-

CODE SENDING RECEIVING SPEED

Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay, adventure. Interesting work. Learn at home quickly through famous Candler System. Quality for Amateur or Commercial License. Write for FREE BOOK. **CANDLER SYSTEM CO.**
Dept. 3-C, Box 928, Denver 1, Colo., U.S.A.

Another Outstanding Jobber
Almo Radio Co.
COR. 6th & ORANGE, WILMINGTON, DEL.

has all 17 KITS & INSTRUMENTS in stock!
EICO
1040K BATTERY ELIM KIT \$25.95
See EICO ad on Page 20

answer the call

1932 RED-CROSS FUND

226, and under amplifiers, pp. 395-406. I do not like the "Bode Step" design discussed in the first section, because it seems too complicated for the noncritical audio problems. The treatment, on page 401, of the response peaks is definitely misleading, because the responses shown are only just stable.

3. **Reference Data for Radio Engineers** (3rd Ed.). Federal. This is worth \$3.75 of anybody's money. Feedback is discussed on pages 256-261 and (for the long-haired ones) on pages 533-545.

4. **Vacuum Tube Circuits**, L. B. Arguimbau: Wiley. This book contains a very clear discussion of the effect of feedback on the amplifier impedances.

5. **Vacuum tube Amplifiers**, Valley and Wallman: Radiation Lab Series, McGraw Hill. Deals mostly with band-pass amplifiers.

6. **Electronic Instruments**, Companion volume to the above (5). Contains a short discussion of the template method described in the Radio-Electronics series.

7. **Radio Receiver Design, Vol. II (Low Frequency)**, K. R. Sturley: Wiley. This book has a good reputation. Sturley is head of the BBC training department.

In addition to the above books, and a number of others, some of the following articles should help the reader. The *Proceedings of the I.R.E.* paper is a good general survey, with a number of references. The *Wireless Engineer* papers (W.E.) are rather mathematical, the *Wireless World* papers (W.W.) are the easiest reading.

"The Stability Problem in Feedback Amplifiers," W. A. Lynch: *Proc. I.R.E.* Vol. 39, p. 100, September, 1951.

"Audio Amplifier Damping," R. M. Mitchell: *Electronics*, Vol. 24, No. 9, p. 128, September, 1951.

"Relations between Attenuation and Phase in Feedback Amplifier Design," H. W. Bode: *Bell System Technical Journal*, XIX, 421, July, 1940.

"When Negative Feedback Isn't Negative," "Cathode Ray": *W.W.* LV, 189, May, 1949.

"Output Impedance Control," T. Roddam: *W.W.* LVI, 48, February, 1950.

"Negative Feedback: Its Effect on Input Impedance and Distortion," E. Griffiths: *W.W.* LVI, III, March, 1950.

"More About Positive Feedback," T. Roddam: *W.W.* LVI, 242, July, 1950.

"Stabilizing Feedback Amplifiers," T. Roddam: *W.W.*, LVII, 112, March, 1951.

"Negative-Feedback Amplifiers: Conditions for Maximal Flatness," C. F. Brockelsby: *W. E.*, XXVI, 43, February, 1949.

"Feedback Amplifier Design," H. Mayr: *W. E.*, XXVI, 297, September, 1949.

"Feedback Amplifiers and Servo Systems," E. E. Ward: *W. E.*, XXVII, 146, May, 1950.

"Negative-Feedback Amplifiers: Conditions for Critical Damping," J. E. Flood: *W. E.*, XXVII, 201, July, 1950.

SYNCHRO SWEEP

Trade Mark Reg.

PROVIDES

- LINEARITY PATTERN
- SYNC PULSES
- SWEEP SIGNALS

A NEW INVENTION!

Pat. Pend.



OAK RIDGE "MINIATURE" Model 104 in Bakelite Case 5 3/4" x 4" x 2 1/4"

TELEVISION SERVICING "ON-THE-SPOT"

With or Without Test Pattern, Scope, or Bench Equipment!

Synchro-Sweep* is the FIRST and to date the ONLY TV Test Instrument to provide its own sync and sweep signals for fast trouble-shooting of sync, sweep and high voltage circuits. It supplies:

1. Direct and/or Transmitted Vertical and Horizontal Sync Pulses simultaneously.
2. Vertical and Horizontal Saw Tooth Signals.
3. Transmitted Vertical and Horizontal Linearity Pattern Bars, (Cross Hatch). This marvelously compact new precision instrument is acclaimed by leading Servicing Organizations, Parts Jobbers, Technical Schools, as a much needed invention for ON-THE-SPOT Television Servicing!

NEWLY IMPROVED!

PROVIDES Stable horizontal and vertical linearity pattern for linearity adjustments.



See the entire Oak Ridge line of precision portable Television Test Instruments at your Jobber's. Send today for your copy of our complete catalog.

OAK RIDGE PRODUCTS

37-01 Vernon Blvd. Long Island City 1, N. Y.
Mfg. Division of VIDEO TELEVISION, INC.

Oak Ridge Products, Dept. C
37-01 Vernon Blvd., Long Island City 1, N. Y.
Please send your complete new OAK RIDGE Catalog at once, to:

Name.....
Address.....
City..... State.....

HUGO GERNSBACK'S

GREAT SCIENCE FICTION NOVEL IS MUST READING

Listen: "NO BOOK in two generations, no book since Jules Verne, has undertaken to do what Hugo Gernsback in the first decade of our century has here so outstandingly achieved."

LEE DE FOREST, Father of Radio.

Forty years ago, Hugo Gernsback, Father of Modern Science Fiction, in this book, **RALPH 124C 41+**, predicted and described in startling detail, radar, the learn while you sleep method, television, televised operas, plastics, night baseball, blood transfusion, wire recording, micro film and a host of other scientific achievements—all undreamed of in 1911—but part of everyday life today.

All of these and scores more, not as yet realized, are found in his remarkable prophetic book. For Hugo Gernsback's prophecies are based not on

fantasy but on the logical projections of established scientific facts.

RALPH 124C 41+ is the first and most remarkable true science fiction novel ever written! A whacking good adventure story that takes place in 2660 AD—but it is far more than fiction!

To technically minded people, **RALPH 124C 41+** is the most complete and accurately documented catalog of scientific prophesy ever published. It was originally written in 1911 and published in book form in 1925. Now, because of its tremendous importance as a work of accurate, scientific prediction of the future, it has been reissued in a new, second edition.

Hugo Gernsback's writings were the spark that started many of today's top radio engineers and scientists on their way. Now again, this new edition of **RALPH 124C 41+** may well be the inspiration for a new generation of pioneers of science.

RALPH 124C 41+ is the kind of book you should read. Order your copy now, only \$2.50 postpaid. The supply is limited.

RADIO PUBLICATIONS

25 West Broadway New York 7, N. Y.

MAIL THIS COUPON TODAY

RADIO PUBLICATIONS

25 West Broadway, New York 7, N. Y.


Gentlemen:

Send me a copy of **RALPH 124C 41+** postpaid, at once. My remittance of \$2.50 is enclosed.

NAME.....


STREET.....

CITY..... ZONE..... STATE.....

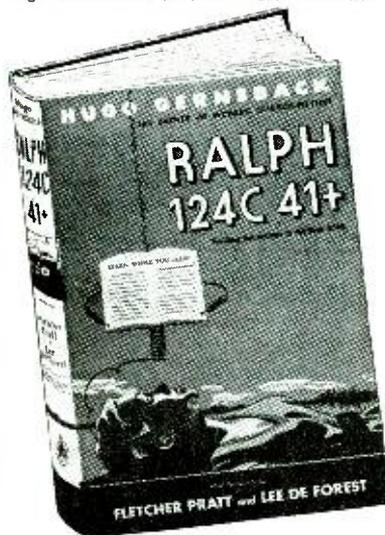


For GREATER TV ENJOYMENT . . .

Install a MOSLEY 3-WAY ANTENNA SWITCH

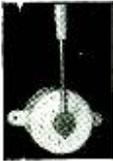

Cat. No. F-20
List \$3.75

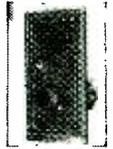

Cat. No. F-10
List \$3.75

Here's convenience! MOSLEY TV Antenna Switches give instant, easy selection of any one of three antennas. Special rotary type switch, making silver-to-silver contact, assures low loss, constant impedance.

Cat. No. F-10 is Flush Mounted Switch and Lead-in Socket combination for neat, concealed-in-wall installation in standard electrical box. Cat. No. F-20 is enclosed in attractive plastic case for mounting on wall or back of set. If mounting on back of set, attach special extension lever provided and install in position for easy accessibility.

At leading Radio Parts Jobbers everywhere

MOSLEY ELECTRONICS 2125 Lackland Road
Overland, Missouri

TUBES

Every
Critical
Type

WE BUY FIRST QUALITY TUBES FOR CASH!

Fully Guaranteed • Brand New • Immediate Delivery

.59

5U4G
5Y3GT
6AL5
6AU6
6AV6
6BE6
6J5GT
6K5GT
6K6GT
6W4GT
35W4
35Z5GT

.69

1R5
1U4
354
3V4
6BA6
6SA7GT
6SK7GT
6V6GT
6X5GT
6BJ6
12AT6

.79

1B3GT
3Q4
6SN7GT
12AU7
12SA7GT
12SK7GT
12SN7GT
12SQ7GT
35L6GT
50L6GT
6CB6
6BM6
25L6GT

.99

1X2A
5V4G
6BC5
6AG5
6AC7
6J6
6T8
6AB4
12AV7
12BH7
12SC7
12SG7

1.29

6AH6
6BG6
6CD6
6BQ6
6BN6
6AK5
12AT7
19C8
19T8
25BQ6
198G6
70L7GT

300-ohm twin lead, pure copper and polyethylene, \$19.50 per thousand feet, 1500 feet to a roll.

TERMS: Orders for less than \$25.00, add 10% to above prices. 25% deposit with order, balance C.O.D. F.O.B. New York City.

All Merchandise Subject to Prior Sale.

Supreme Radio & Television Co.

136 Liberty Street, New York 6, N. Y.

You can't beat RADIO-ELECTRONICS

for complete coverage of

RADIO, TELEVISION and AUDIO

Free NEW
BIG RADIO
CATALOG



Ready now. Complete with everything in radio, television and electronics. Newest parts, as well as old, standard lines. Paste coupon on penny postcard and mail today!

Lafayette Radio

DIVISION: RADIO WIRE TELEVISION, INC.

NEW YORK 13 100 Sixth Ave. NEWARK 2 24 Central Ave. BOSTON 10 110 Federal St. BRONX 58 542 E. Fordham Rd.

LAFAYETTE RADIO,
Dept. JC
100 Sixth Avenue, N. Y. 13

Please rush Free catalog to:

Name.....

Address.....

City..... State.....

PASTE ON PENNY POSTCARD

"Amplifier of Variable Output Impedance," R. Yorke and K. R. McLachlan: *W. E.*, XXVIII, 222, July, 1951.

"Amplifier Characteristics at Low Frequencies," G. W. Edwards and E. C. Cherry: *Journal of the Institution of Electrical Engineers Proc. W. Section* 15, 204, September, 1940.

"Some Considerations in the Design of Negative-Feedback Amplifiers," W. T. Duerdath: *J.I.E.E.*, Vol. 97, III, 138, May, 1950.

Finally, for the armchair rather than the desk:

The Human Use of Human Beings, and Cybernetics, both by Norbert Wiener: Houghton Mifflin.

Even if you do not agree with Wiener, he will make you think about the implications of feedback in economics and politics. And if you won't take an interest . . . —George Fletcher Cooper

ELECTRONIC LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. All literature offers void after six months.

RADIO-TV CATALOG

The new 1952 Catalog No. 86 has been issued by Radiolab. Comprising 118 pages, the issue features a wide variety of ham equipment, communications receivers, tubes, test equipment, TV and sound equipment, books, tools, and TV antennas.

Gratis from Radiolab, 1608-14 Grand Ave., Kansas City 8, Mo.

DIAGRAM AID

A four-page bulletin giving tips to the technicians on how to get more efficiency in consulting diagrams has been put out by Supreme Publications. Also included is a list of the various manuals issued by them.

Gratis from Supreme Publications, 3727 W. 13th St., Chicago 23, Ill.

RADIO-TV CATALOG

The 1952 catalog of Edlie Electronics, Inc., features a wide variety of parts, accessories, test equipment, sound units, auto sets, books, and antennas.

Gratis from Edlie Electronics, Inc., 154 Greenwich St., New York 6, N. Y.

WINDOW-SIZE BLOWUP

"Are Servicemen Gyps?" is the title of a blowup of the advertisement on page 17 of this issue, currently being offered to service technicians by Sprague Products Co., for exhibition in their windows.

The text deals with the customer who protests a television repair bill while accepting without comment much larger bills from his garageman, and the complaints from persons in fringe areas who expect excellent reception, or those

RADIO-ELECTRONICS

in better areas who have bought bargain sets and are getting reception that is no bargain. It ends with an exhortation directed at the service technician's customer and is signed by the president of the company.

Available from Sprague Products Co., North Adams, Mass., for 10 cents to cover costs.

METALLIC RECTIFIER BOOKLET

Radio Receptor Co. has issued a 16-page booklet reviewing the background of metallic rectifiers and clarifying the various applications factors with many drawings, diagrams, and charts. It is useful to the engineer with specialized experience as well as to the novice.

Copy gratis from Radio Receptor Company, Inc., Seletron Rectifier Division, 251 West 19th St., New York 11, N. Y.

TUBE SUBSTITUTION GUIDE

The first supplement of Receiving Tube Substitution Guide Book, by H. A. Middleton, is now available. Wiring instructions and illustrations cover 750 tube substitutions in AM-FM-TV receivers. The supplement contains 48 pages, 8½ x 11 inches, and is bound with a heavy cover.

John F. Rider Publisher, Inc., 480 Canal St., New York 13, N. Y., or any of the organization's distributors. Price 99¢.

RIDER HAS NEW FOLDERS

A new TV schematic folder service is announced by John F. Rider Publisher, Inc., with the issuance of the TEK-FILE. Each TEK-FILE (to be issued monthly) is in a box containing a number of folders of alphabetically arranged TV schematics. The makeup of the new service is similar to the Rider Manuals in organization and emphasis on servicing details. Each pack has at least 128 8½ x 11-inch pages.

The files contain factory authorized information, circuit action descriptions, unpacking and installation data, trouble-shooting waveforms, production changes, alignment data, chassis views, and voltage and resistance readings. Included in the pack is an index of manufacturers and model numbers. A TEK-FILE cumulative index is available for dealers from Rider distributors.

LABORATORY INSTRUMENTS

Polarad is issuing its new enlarged catalog on laboratory instruments, including all-band spectrum analyzers, and microwave signal sources.

Available from Polarad Electronics Corp., 100 Metropolitan Avenue, Brooklyn 11, N. Y. Gratis.

REPLACEMENT NEEDLE GUIDE

Recoton is issuing a 17-page replacement needle guide containing handy needle charts and manufacturers' cross index. Punched for binder insert.

Available from Recoton Corp. 25 4th Ave., New York, N. Y. Gratis.

—end—



HEAVY WEB TV LEAD-IN WIRE CUTS DOWN COSTLY "CALL-BACKS"

Have you seen the new SYNKOTE 300 ohm TV lead-in? It has a .100 web with a maximum variance of five thousandths of an inch! Tough polyethylene construction that stands up against sun, snow, rain, cold and abrasion.

Ask your jobber to show you this as well as the complete SYNKOTE line of dependable wires . . . used and recommended by leading manufacturers everywhere.

Synkote

DEPENDABLE

HOOK-UP WIRE • COAXIAL CABLE • TV LEAD-IN WIRE

"manufactured by the mile — tested by the inch"

SYNKOTE—Reg. Trademark of PLASTOID CORP., Long Island City 1, N. Y.

So You Want To Be A Writer!

That idea you may have for writing a technical book is absolutely no good unless you do something about it. If you're dying to reveal all you know about TV; if you feel the world is wasted without your words on servicing, or if you nurture a secret ambition to out-theorize all the books on TV theory, then start your writing career by writing to us. Just send us a letter outlining your ideas. Our reply will contain a copy of our author's guide and details of royalty payments.

**Book Dept.
RADCRAFT PUBLICATIONS, INC.**

**25 West Broadway,
New York 7, N. Y.**

Solderless Cable Fittings



By Workshop

Whenever you need a cable fitting for RG-8 U, RG-11 U and RG-59 U, specify **WORKSHOP . . . Solderless silver plated connectors, receptacles, junctions and adaptors.** Look for the complete line at your distributor's on the red and white display card.



THE WORKSHOP ASSOCIATES
Division of the Gabriel Co.
135 Crescent Road
Needham Heights 94, Mass.

Douglas Y. Smith, a veteran of almost 25 years of service in the engineering, merchandising, and sales activities of RCA, was promoted to manager of sales operations for the Tube Department, according to an announcement by



D. Y. SMITH

L. S. Thees, general sales manager of the department. Mr. Smith was most recently plant manager of the Tube Department's Lancaster, Pa., plant. Earl M. Wood, former manager of manufacturing at Lancaster, succeeds Mr. Smith as plant manager.

Wickham Harter, sales manager of Mechanical-Electronic Products of the CENTRALAB DIVISION of GLOBE-UNION INC., Milwaukee, died of a heart ailment in St. Mary's Hospital, Milwaukee, at the age of 58. Mr. Harter was a pioneer sales executive in the radio field and at one time vice-president of Solar Manufacturing Co. He was a member of the Sons of the Revolution and the Princeton Club of New York.



W. HARTER

Floyd J. Van Alstyne was appointed jobber sales manager of PERMOFLUX CORP., Chicago. He will direct the sales of loudspeakers, baffles, headsets, and other jobber items manufactured by Permoflux. Also announced was the appointment of Howard Roth, Eugene Roeske, and George Adams as industrial sales representative, head of the New



F. J. VAN ALSTYNE

Transformer Core Division and factory superintendent, respectively. Mr. Roth came to Permoflux from American Steel and Wire; Mr. Roeske from S & C Electric Co.; and Mr. Adams from RCA.

John Giltner Twist, former assistant sales manager of the CAPACITOR DIVISION of SANGAMO ELECTRIC CO., was promoted to sales manager of the division at Marion, Ill. William W. Taylor was named sales promotion manager of the division.



W. W. TAYLOR



J. G. TWIST

SENSATIONAL VALUE!

±630 SUPER 30 TUBE CHASSIS
Mfr. Licensed under R. C. A. Patents

Complete with 21" first quality tube

AND Beautiful hand-rubbed Mahogany Console Cabinet.

COMPLETE PRICE \$259.95 slightly higher with full doors



the latest 1952 model with all the newest electronic improvements . . .

- peak sensitivity for fringe areas
- synchrolock tuning
- keyed A G C
- 15,000 volts under load
- 12-inch RCA speaker
- can be adapted to color & UHF
- high quality parts

A set—NOT A KIT

Completely wired, Factory Engineered, aligned and tested. RMA Guaranteed

1 YEAR GUARANTEE ON TUBE

A half-hour to mount; ready for operation. Saves up to \$150.

Compare this anywhere for high quality—low price!

Write Dept. H for further information. Phone and mail orders filled on receipt of money order for 25% as deposit . . . the balance C.O.D., f.o.b. N. Y.

NEW ENGLAND TELEVISION CORP.
75 CHURCH STREET NEW YORK, N. Y.

TUBES at Mfr's. COST

Standard Brands—Unbranded—Guaranteed

11B3	\$1.35	6B86	\$2.70	12AT6	\$4.50
11L	.60	6B86G	1.48	12AT7	.95
11L6	.60	6B86	.94	12AU6	.46
11LNS	1.05	8C1	.60	12AU7	.75
1U4	.60	6C06	.56	12AV7	.95
1U5	.50	6C06G	1.93	12AX7	.65
2X3	.85	6J5W	.75	12AY7	2.85
2X2	.60	6J6	.73	12BA7	.80
3Q4	.68	6J6	1.09	12BE6	.49
3V4	.62	6K6	.65	12CG7	.60
5U4Q	.75	6J7GT	.85	12SA7GT	.75
5V4	1.20	6L6GA	1.05	12SF5M	.70
5V3GT	.53	6M5G (M&G)	1.10	12SQ7	.90
5Z3	.85	6R6	1.50	12SK7GT	.65
6AB4	.65	6S4	.51	12SQ7	.75
6AC7	.90	6S7M	1.05	12SN7GT	.75
6AG5	.57	6S7GT	.75	12SW4	.65
6AG7	1.85	6SC7	1.10	14BE6	.95
6AH6	1.75	6T	.70	19T8	.86
6AK5	1.10	6S7	.70	25L6GT	2.50
6AK6	1.20	6S7GT	.53	25W4	.90
6AL5	.44	6L7G1	.65	35L6GT	.53
6AQ5	.65	6S7GT	1.45	50C5	.53
6AT8	.40	6S07GT	.65	35Z5GT	.39
6AU6	.65	6H	.86	50B5	.53
6AV6	.65	6S7GT	1.51	50C5	.53
6B85/GNS	1.25	6W4GT	.49	50L6GT	.53
6B86	.48	6X4	.36	*59	1.50
6BC5	.56	6B4	.46	*89Y	.75
6BE6	.65	*7AD7	1.25		
6BF5	.65	*12A6	.70		

UNBRANDED—*STANDARD BRANDS
Minimum Order \$15.00

SPECIAL PURPOSE TUBES

1838	\$9.95	703A	\$2.45	9002	\$1.50
1N23A	2.75	807	7.10	9003	1.75
1N23B	3.75	813	7.60	9005	1.75
2E25	5.95	812	7.50	CK70	4.95
3047L	10.50	837	1.25	KKR73	1.50
3047M	10.50	866	1.25	VR10	1.50
3B24	5.50	931A	6.75	VR105	1.15
757M	6.75	5670	5.95	VR150	1.00
211/VT4C	5.50	5814	4.95	TUF20	3.95
350B	5.50	8025	5.75	TZ20	2.25
394A	5.50	9001	1.75	TZ40	3.25

IMMEDIATE DELIVERY!

Write for quotations, many other types available. 20% Deposit with order, balance C.O.D. All tubes subject to prior sale. Prices subject to change without notice.

WRITE, WIRE, CALL—TODAY!


We Buy Anything in Electronics—large or small Quantities!

Nat Adelman

168 Washington St. New York 6, N. Y.
CO, 7-6091

500 FORMULAS TO SUCCESS

MANY million dollar firms started with a single formula, for which they paid a big price. Here you have 500—no less—tried and tested formulas, recipes and processes for making things . . . all at the ridiculously low price of 25¢. Here is your opportunity to start a business with but a few dollars capital and with undreamed of profits in prospect. You can also use these formulas in your own home to cut household expenses to the bone. Or you can put them to use in your workshop to cut costs as much as 100%.

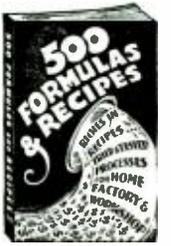

Quit paying out many dollars in profits to manufacturers, wholesalers, and dealers, when you can make the same thing yourself for a few cents. It's so easy when you follow our simple instructions.

66 PAGES. 47,000 WORDS IN TEXT

Send for "500 FORMULAS AND RECIPES" today. Enclose 25¢, that's all! You won't be asked for another cent now or later. Sold on a money-back guarantee.

NATIONAL PLANS COMPANY

1966 Broadway, New York 23, N. Y.



\$3.00 FOR CARTOON IDEAS

RADIO-ELECTRONICS prints several radio cartoons every month. Readers are invited to contribute humorous radio ideas which can be used in cartoon form. It is not necessary that you draw a sketch, unless you wish.

Address
RADIO CARTOONS, RADIO-ELECTRONICS
25 West Broadway, New York 7, N. Y.

RADIO-ELECTRONICS

STAN-BURN ELECTRONICS

★ ANTENNAE SPECIALS ★

★ DOUBLE V 3/4" Dowel	1-11	12 or more
★ DOUBLE V 3/8" Dowel	\$2.98	\$2.20
★ DOUBLE V 1/2" Dowel	3.45	2.45
★ 19 Element Conical 3/4" Dowel	3.95	2.95
★ Folded Hi Straight Low Quick	3.55	2.55
★ Rig 1/2" elements	4.25	3.25
★ WINDOW CONICALS	4.95	3.75
★ 5 FOOT SWEGDED MASTS	.89	.69
★ 10 FOOT PLAIN	1.59	1.29
★ 42 Mil. 300 OHM	\$15.95	M Ft.
★ 55 Mil. 300 OHM	17.95	M Ft.
★ 72 OHM COAXIAL	52.50	M Ft.

★ CATHODE RAY TUBE SPECIALS ★

★ 7JP4	\$15.00	16RP4/KP4 N.U.	\$23.00
★ 10BP4	14.95	16RP4A	26.00
★ 10BP4 N.U.	14.95	17BP4A	27.00
★ 10BP4A N.U.	19.95	20CP4	39.95
★ 12LP4	19.95	20CP4 Sheldon	37.00
★ 12LP4A	19.95	19AP4A	47.95
★ 14BP4	19.95	19DP4A	47.95
★ 16DP4A	26.00	24AP4A	73.00
★ 16GP4	33.00	Single ion traps	.39
★ 16AP4A	39.00	Double ion traps	.59

★ CHASSIS 630 K38 VIDEO	\$139.50
★ OPEN FACE CABINET	39.00

★ RCA type for 16" to 24" X032	\$3.85	★ DEFLECTION YOKES	
★ G.E. Type for 16" to 24" X045	\$3.85	★ Cosine Ferrite Todd Yoke 70"	\$4.20
★ These are very special prices while they last!		★ Regular 70" Yoke	3.85

★ Condenser specials BY PASS— ALL GUARANTEED	★ Speaker Specials ALL GUARANTEED	
★ 20x20-150 Stan Burn	4" P.M.	\$1.64
★ 50x30-150 Stan Burn	5" P.M.	1.75
★ 20x150 Stan Burn	6" P.M.	2.41
★ 8-450 Stan Burn	8" P.M.	3.41
★ 16-450 Stan Burn	12" P.M.	6.33
★ 4 Prong Vibrators each \$1.29	4 x 6 P.M.	2.19
★ Lots of 12 or more \$1.19	5 x 7	3.43
★ Standard TV Tuners \$18.95	10" P.M.	5.48

★ RCA Guaranteed Tuners (with tubes) Special, while they last. \$12.00

★ AUTHORIZED DISTRIBUTORS for General Electric, Konrad, Tung-Sol, National Union, Jewel, De Waid, Regal, Automatic and Satchel Carlson.

★ We carry a complete line of popular makes of radio and TV tubes at 50% discount. Also many other special purpose and transmitting types, and all electronic parts and equipment at lowest prices. Send us a list of your requests for quantities and prices. Terms: 20% with order. Balance COD All prices FOB, New York Warehouse. Minimum order \$5.00

★ Write for our latest price list to Dept. RE-3

STAN-BURN RADIO and ELECTRONICS CO.
(C.B.S. THEATRE BLDG.)
1697 BROADWAY • NEW YORK 19, N.Y.

★ OPPORTUNITY AD-LETS ★

Rates—35¢ per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount for 6 issues, 10% for 12 issues, 20%. Misleading or objectionable ads not accepted. Copy for May issue must reach us before March 21, 1952.

Radio-Electronics, 25 W. Broadway, New York 7, N. Y.

RADIO OFFICERS, \$7,200-\$10,000 annual earnings, top union conditions, 6 months Radio Operating experience US Merchant ships on FCC License since Jan., 1935, can get emergency FCC License to sail at once. Also experienced CSSN Radiomen with 2d class Radiotelegraph license plus 6 months sea radio time. Phone, write, wire, American Radio Association, C10, 5 Beekman St., New York, CO 7-6397.

SPEAKERS, REPAIRED at wholesale prices. Guaranteed workmanship. Past service, Amprite Speaker Service, 70 Vesey St., New York 7, N. Y.

SEND ME A BUCK: I'll send you my book—RAPID RADIO REPAIR. John D. Burke, 88-14 168th Street, Jamaica 3, N. Y.

MINIATURE RADIO, weight 8 oz. with batteries. Write for prices. Also plans all wave radio using hearing aid parts. 25¢. Glen Ecker, 10 East Orange Grove, Pasadena, California.

USED BUT EXCELLENT SNABER AUDITORIUM 20x26 Projection TV. List \$1495.00. Sacrifice \$398.00. Details, Porter, Essex, Middleton, Mass.

WE REPAIR, EXCHANGE, SELL, ALL TYPES OF electrical instruments, tube checkers and analyzers. Hazleton Instrument Co. (Electric Meter Laboratory), 128 Liberty Street, New York, N. Y. Telephone—BR 4-1239.

FIVE ONE-TUBE "LOUDSPEAKER" RADIO CIRCUITS 25¢. Radio Kit price list with each order. Master Kit Company, Post Office Box 206, Belleville, Ontario, Canada.

WANTED RG-8-U, RG-11-U, RG-50-U COAXIAL Cable; any lengths, any quantities Write: Television Service Co., 249 North 48 St., Lincoln, Neb.

AMATEURS — RADIO ENGINEERING QUESTIONS answered \$1.00. With Schematics \$2.50. Henry Twillmann, RR. #1, Chesterfield, Missouri.

TV AND FM ANTENNAS, YAGI, CONICAL, BOW-TIE. Mounts accessories. Lowest prices. Wholesale Supply Co., Lunenburg 2, Mass.

20' TELEVISION TOWER, AMERICA'S FAVORITE "TUFFY" now six at \$29.95 complete with saddle hinged mount. Easy to erect, safe to climb, may be made 40' by telescoping pipe through tower. (Cartoned). Youngstown Steel Towers Co., 1825 Wilson Ave., Youngstown, Ohio.

Personnel notes

... Robert E. Lee was appointed assistant manager of the cathode-ray tube operations of GENERAL ELECTRIC'S Tube Department at Schenectady, N. Y. He was formerly manager of finance for the department. Other Tube Department promotions include S. Norman Crawford, designing engineer for power electronic equipment; C. Curtis Herskind and Walter R. Kettingring, section engineers.

... Albert A. La Pointe, vice-president of LA POINTE-PLASCOMOLD CORP., Windsor Locks, Conn., died in West Hartford, Conn.

... John J. Doyle was appointed manager of power tube sales for the Electronic Tube Division of WESTINGHOUSE at Elmira, N. Y.

... John M. McGuire joined NATIONAL UNION RADIO CORP. as district manager for the up-state New York territory of the Renewal Sales Division. He previously held a sales position with the General Electric Credit Corp.

... Manfred E. Philip was appointed controller and director of purchases for TELREX, INC., Asbury Park, N. J. He was formerly with a firm of certified public accountants.

... S. I. Neiman and Kenneth C. Prince were named executive secretary and general counsel, respectively for RADAR-RADIO INDUSTRIES of Chicago, a trade group of radio, television, and parts manufacturers engaged in defense work.

... J. E. O'Donnell was named to the post of Chicago warehouse manager of the WALTER L. SCHOTT CO., Los Angeles.

... J. A. Myers, Jr., and P. E. Coolbaugh were appointed departmental sales managers for the CHICAGO TRANSFORMER DIVISION of the ESSEX WIRE CORP. Mr. Myers will be responsible for broadcast and transmission equipment and Mr. Coolbaugh for radio, television, and industrial equipment.

... Thomas M. Blake, vice-president and treasurer of LITELFUSE, INC., Chicago, has written a treatise, "Formula for Peace," which he has published in booklet form at his own expense. The booklet is available free upon request from Mr. Blake.

... H. A. Gumz, production manager of WEBSTER-CHICAGO, was named vice-president of the firm.

... Leon B. Ungar, vice-president and general manager of UNGAR ELECTRIC TOOLS, INC., was elected chairman of the Los Angeles Council of the West Coast Electronic Manufacturers Association.


... Warren E. Albright, former manager of the General Materials Division of RCA's Home Instrument Department, was appointed general plant manager of the department.

... H. S. Zebly joined SNYDER MANUFACTURING CO., Philadelphia, as sales manager of the Military Division. Ben Henig joined Snyder as sales representative of the same division. Mr. Zebly was formerly with Major Distributing Co., and Mr. Henig with U.S. Metal Products Co.

—end—

FOR FRINGE AREA & DX the New DAVIS SUPER-VISION ANTENNA

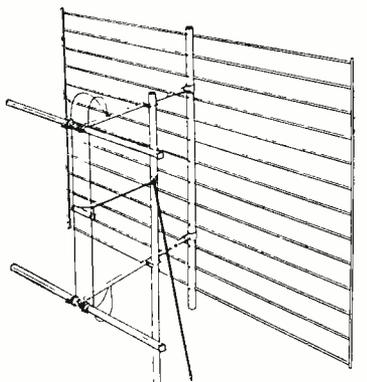Built to the same Davis High-Quality Reception Standards which have made Davis Electronics Products so popular with users and the trade. Backed by over a quarter of a century of electronic experience.



MANY OUTSTANDING FEATURES:

- Broad-Band Receiving—Channels 2 to 13.
- Eliminates or Greatly Reduces "Ghosting" Problems.
- Provides 10 DB or More Gain on High Channels—where gain is most needed.
- Excellent Front-to-Back—on all channels.
- Minimizes Interference: Airplane Flutter—Diathermy and Ignition—F. M.—Neon Signs—X-Ray—Industrial—Etc.
- Can Be Tipped WITHOUT Tilting Mast.
- Jiffy Assembly. Light-weight rugged construction.

AT YOUR JOBBERS, OR WRITE TO:

DAVIS ELECTRONICS 1-4
3047 W. Olympic Blvd., Los Angeles 6, California

SIRS: RUSH INFORMATION TO ME AS CHECKED BELOW:

Send Free Technical Data on new SUPER-VISION ANTENNA.

Send Name and Address of NEAREST JOBBER.

Name _____

Street _____

City _____ State _____

WE JUST GOTTA BUY THIS STUFF!

We're tearing our hair out to buy desperately needed equipment, such as ART-13, BC-348, BC-224, BC-342, BC-312, ARC-1, BC-221, RS/ARN-7 or components. In fact, we'll buy any parts or accessories, no matter how small. For speedy, efficient service and a real honest deal, phone, wire or write:

V & H RADIO & ELECTRONICS SUPPLY CO.
2033 W. Venice Blvd., Los Angeles 6, Calif.
Telephone: REpublic 3-1127

RADIOS
1, 2 & 3 band Electric and/or Battery

TELEVISION
AC/DC Operation

TEST INSTRUMENTS
Write for FREE Catalog

ARKAY—Radio Kits, Inc.
120 Cedar St., New York 6, N. Y.



Low Cost Powerful P.A.!

COMPLETE • READY TO USE

Tops for powerful indoor-outdoor use; ideal for electioneering. Easy portability. Covers 4,000 persons indoors, up to 25,000 sq. ft. outdoors. Full 30 watts usable output; 2 high-imp. mike inputs, 1 phono input, each with separate volume control; tone control; fidelity ± 2 db from 40-20,000 cps. Complete system includes: 30 watt amplifier and tubes, Electro-Voice "Cardax" unidirectional mike with adjustable floor stand and 20' cable; 2 General Electric 12" PM speakers, each with 30' cable; portable carrying case holds all, 16 $\frac{3}{4}$ x 12 $\frac{3}{4}$ x 25". For 110-130 v., 60 cy. A.C. Shpg. wt., 75 lbs. Complete, less only phono top.

93-372. Complete 30 Watt System. Only \$119.75
93-340. 3-Speed Phono Top for above. Only \$16.95
Available on Easy Terms—write for details

FREE See the 212-Page ALLIED Catalog for other Sound Systems, ranging from 8 to 80 watts. Write for Free copy of Radio's leading Buying Guide today.

ALLIED RADIO

833 W. Jackson Blvd., Dept. 2-CC-2, Chicago 7, Ill.

SHOOT TV TROUBLE FAST!

With H. G. Cisin's Copyrighted RAPID "TV TROUBLE SHOOTING METHOD"

Without experience or knowledge, this *guaranteed* new method of servicing TV sets enables you to DIAGNOSE TV troubles as rapidly as an expert. **NO THEORY—NO MATH**—you can locate all faults in record-breaking time, regardless of make or model.

"TV TROUBLE SHOOTING METHOD" is the most valuable aid to TV servicing ever written. Be a TV Trouble Diagnostician. Increase your present earnings. Open your own Profitable Business or get a high-paying skilled job.

It's all in this book . . .

Nothing more to Pay—Nothing else to Buy

Alphabetically listed, there are 85 picture troubles, over 58 raster and 17 sound troubles and by this unique copyrighted method you know EXACTLY WHERE the trouble is; plus step-by-step instructions, including the RAPID CHECKS, enabling you to find the faulty part.

13 IMPORTANT PRELIMINARY CHECKS NEED NO INSTRUMENTS! Of the 69 Rapid Checks, OVER 65 ALSO REQUIRE NO INSTRUMENTS! Rapid checks include emergency checks for distorted pictures, defective tubes including PIN tube, plus 57 others. ALL EXPLAINED IN SIMPLE LANGUAGE, PERFORMED WITHOUT INSTRUMENTS. MANY CHECKS USE THE PICTURE TUBE AS A GUIDE.

H. G. Cisin, the author, is the inventor of the AC/DC midjet radio. He licenses RCA, AT&T, etc. He has also trained thousands of technicians now owning their own prosperous TV service organizations or holding highly paid TV positions. His years of experience are embodied in this remarkable new TV TROUBLE SHOOTING METHOD.

Guaranteed. Money Back in 5 Days if Not Satisfied!

If you use coupon below you will receive, **ABSOLUTELY FREE**, a copy of H. G. Cisin's new book "TV Terms Simply Explained including Picture Guide" which sells for \$1. **ACT NOW** and get both books postpaid at the cost of only one.

RUSH COUPON NOW!

H. G. CISIN, CONSULTING ENGINEER, (Dept. E-11)
200 Clinton Street, Brooklyn 2, N. Y.

Name.....
Address.....
City.....Zone.....State.....

CONVERSIONS DANGEROUS?

Dear Editor:

No technician has any business making any major changes in a radio or TV. Converting to bigger picture tubes, u.h.f., or color is the manufacturer's business, not the technician's. In a good many cases the manufacturer is wisely shying away from it, yet the technician, with very limited technical and financial resources, steps in and undertakes these conversions. "Television technicians rush in where angels fear to tread," or something to that effect!

Purpose of this letter is to ask you to put a headnote on these conversion articles warning that when, as and if the conversion jobs start coming back a few months or a year from now, the technician may be faced with a choice, either to make good and go bankrupt, or to deny paternity and leave the customer with an orphan on his hands, to work out his own salvation as best he can.

The garageman confines his activities to replacing worn or broken parts with exact duplicates, and if he does make any major changes it is with the authority of, and with parts furnished by, the manufacturer. He believes in "Cobbler stick to your last."

If the television man will do likewise, all will be well. That is, confine his activities to replacing defective parts with exact duplicates. Leave research, radio engineering and experimentation and the headaches and financial losses that go with them, to the manufacturer who has a special department to handle all that and a way of collecting for its maintenance!

CLARENCE J. RICHARDSON
Buffalo, N. Y.

(The above represents the highlights of a carefully written but very long letter, which covered a number of details and brought up supporting arguments for the statements made. Our set conversion specialists will no doubt be interested. Comment is invited. —Editor)

BENEFICIAL DISTORTION

Dear Editor:

It has come to my attention recently that my use of the word "distortion" in my November article on the Baldwin Electronic Organ has been misinterpreted (either deliberately or through ignorance) by rival sales organizations, and used for attacks on the Baldwin.

As I clearly stated in that article and the two following ones, the special kind of "distortion" referred to was Baldwin's deliberate changes in the shapes of sawtooth waves, using formant filters. As any technician must have understood, and as anyone who has ever heard the Baldwin knows, the results, far from being deleterious, are a wide variety of tones so like those of a pipe organ and so pleasing in musical quality that it is often hard to believe that there are no pipes!

I know you would not want the magazine quoted incorrectly, especially

when it can unfairly harm a high-quality product. I hope you will publish this letter, therefore, to assure anyone who may have been misled that sometimes "distortion"—at least the kind I described—is good, not bad. To misquote a phrase myself, "What's an amplifier's poison may be an electronic organ's meat!"

R. H. DORF

New York, N. Y.

WORST TYPE OF TVI?

Dear Editor:

Your magazine has devoted hundreds of articles to improving and servicing TV receivers. Included among them have been many about television interference. But nobody has yet done anything about the most important television interference problem existing today. All magazines, books, and other sources that cover TV blithely ignore it.

I refer to the nerve-wracking, insanity-producing *audio* whistle heard on all TV sets. I have heard this high-frequency whistle on practically every set I have been near. Cost of a set is no criterion—they all seem to have it.

You may ask, "Is this a special condition?" No, it isn't. About half the people under 30 are affected by it and complain bitterly about it when asked. Many have specifically stated that the whistle is the reason they will not own a set, even though they desire and can afford to. I assume that much business is lost because of this.

I even dislike visiting friends who own a TV set. This is embarrassing because they can't hear the whistle. (They wouldn't have bought the set if they could!) I have asked children about it. They have indicated that they thought the whistle was part of the program. They hear it, of course, but somehow become oblivious to its effects. (Is this the reason why some claim that kids get groggy listening to a TV set?)

The effect caused by this noise is a splitting headache. Prolonged exposure will cause a headache that will last for days. The fact that most people are to a degree deficient in hearing and therefore cannot hear this 15,750-cycle note, is no reason for the rest of us to suffer. I am against TV till this most important difficulty is solved and cured (for new sets and old alike). Can you include an article on this in your magazine? Can any of your readers find a cure?

LEO W. MAKI

Los Angeles, California

LET'S HAVE MORE THEORY

Dear Editor:

Your recent series "Audio Feedback Design" and your articles on electronic brains were very stimulating. Let's have more of this sort of theory—it makes fine material for the technical readers to sink their teeth into. Keep up the good work!

ALLEN BRUCE

Halifax, Nova Scotia

—end—

Brooks LIFE-SIZE Edition

630 TV KIT BUILDER - SET OF INSTRUCTIONS

Step By Step Instructions by **WALTER H. BUCHSBAUM**
 Layouts And Artwork by **GEORGE MILLER**
 Practical Applications by **IGNAZIO MERCANTE**
 Compiled and Edited by **MORRIS BROOKS**

TRULY AS NEW AS TOMORROW!—One streamlined version that covers all #630's from the ORIGINAL 29-tube 10" SET to the latest SUPER DELUXE 31-tube 16" to 24" TV RECEIVER.


NO MORE FUMBLING!—The diagrams, layouts and easy to follow step by step instructions are all neatly arranged on GIANT 25"x38" charts, showing everything at a glance.

LIFE-SIZE!—All illustrations of parts on the layout charts such as chassis, parts, tubes, wires, etc. are in actual LIFE SIZES, *you just can't make mistakes.*

SPECIAL TV FOLDER!—Shows the parts arrangements and enumeration, makes adjustments and alignment procedures simple and provides all the other necessary information to afford you pleasure and success in building your #630 TV RECEIVER.

Popular priced at only **\$2.49** ... Plus postage, First Class 36¢, Air Mail 72¢

#630 SUPER DELUXE 31-TUBE TV CHASSIS

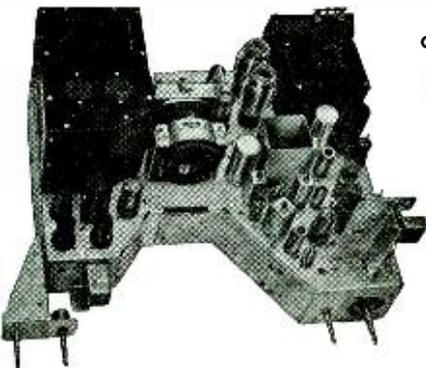

KNOWN MFR. **16" TO 24"** LICENSED BY RCA
 OPERATES ALL **16" TO 24"** PICTURE TUBES

Engineered in strict adherence to the genuine
 RCA #630, plus added features ★ ★ ★ ★ ★

NOTHING BETTER AT ANY PRICE!

- Standard Turret Tuner (Cascode) for DX
- Original 630 Synch. Chain for Stability
- 16.5 KV for Clarity and Brilliance
- 4 Megacycle Bandwidth for Definition
- Fast Action Pulse Keyed AGC
- Large Concert-tone 12" PM Speaker

Complete ready to play with all tubes,
 hardware, knobs, etc. (less CRT) **\$167.97**

#630 Standard 29-TUBE TV KIT

COMPLETE SET OF PARTS
 for the FAMOUS ORIGINAL RCA #630
 29-TUBE 10" TO 12½" CHASSIS

Complete with all tubes,
 hardware and the new LIFE-
 SIZE builder's instructions
 (less CRT & wire)

\$99.99

#630 Super Deluxe 31-TUBE TV KIT

SAME AS FEATURED TO LEFT
 WITH VOLTAGE DOUBLER & AGC

OPERATES ALL **16" TO 24"** PICTURE TUBES

Complete with all tubes,
 hardware and the new LIFE-
 SIZE builder's instructions
 (less CRT & wire)....

\$119.44

#630 TV BASIC PARTS KIT

(Totals over \$100 if purchased separately at list prices)

- PUNCHED & DRILLED CHASSIS PAN
- BRACKET & SHIELD KIT (18 items)
- VIDEO & I.F. KIT (19 items)
- POWER TRANSFORMER #20T6
- VERTICAL OUTPUT TRANSFORMER
- VERTICAL BLOCKING TRANSFORMER
- FLYBACK TRANS. #211T3 or #211T5
- FOCUS COIL, #202D1 or #202D2
- DEFLECTION YOKE, 60° or 70°

All for Only **\$39.49** Incl. the new
 LIFE-SIZE
 builder's instructions

FINEST STANDARD GUARANTEED PICTURE TUBES

Most desirable 3 sizes. Choice of DUMONT 6-mos. guaranty or SHELDON blue label 1-yr. guaranty.

17" Rect. **\$34.63**

20" Rect. **\$49.74**

24" Round **\$79.49**

CUSTOM-BUILT CABINETS - FROM FACTORY TO YOU

4 leading styles in genuine mahogany or walnut (Blonde 10% extra). WINDSOR or NEW YORKER when open look like STREAMLINER. Ready drilled for #630 chassis and any 16" to 20" picture tube at no extras in price. Also supplied with blank panel to fit any make TV set. Delivered complete as pictured including hardware, supports and safety glass. Information on cabinets for the 24" picture tube, on request.

THE MANHATTAN
 It Has Everything
 Style, Quality, Price

THE STREAMLINER
 Center Drop Panel
 Conceals Tuning Knobs.

THE NEW YORKER
 A Deluxe Cabinet
 With a Piano Finish.


THE WINDSOR
 Aristocrat of Cabinets
 Doors in Genuine Leather
 Hand Tooled In Gold




H-41", W-25", D-23"
\$59.37



H-42", W-26", D-25"
\$74.98

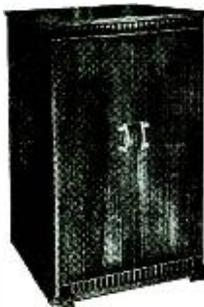

H-42", W-26", D-24"
\$96.87

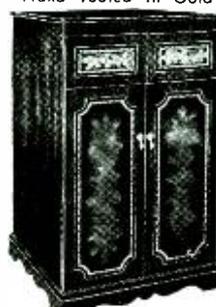

H-42", W-26", D-25"
\$117.46

SPECIAL COMBINATION OFFERS

MANHATTAN CABINET, SUPER DELUXE CHASSIS & 17" CRT* \$235.78

MANHATTAN CABINET, SUPER DELUXE CHASSIS & 20" CRT* 249.37


For same combination offer, substituting the STREAMLINER, NEW YORKER or WINDSOR cabinet simply add difference in cost of cabinet. For BLONDE finish add 10% above cost of cabinet. *CRT is the abbreviation for picture tube.

BROOKS RADIO & TV CORP.

84 Vesey St., Dept. A, New York 7, N. Y.

AMPERITE

Studio Microphones at P.A. Prices

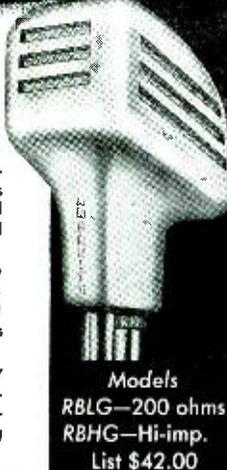

Ideal for BROADCASTING RECORDING PUBLIC ADDRESS

"The ultimate in microphone quality," says Evan Rushing, sound engineer of the Hotel New Yorker.

- Shout right into the new Amperite Microphone—or stand 2 feet away—reproduction is always perfect.
- Not affected by any climatic conditions.
- Guaranteed to withstand severe "knocking around."

Models
RBLG—200 ohms
RBHG—Hi-imp.
List \$42.00

"Kontak" Mikes
Model SKH, list \$12.00
Model KKH, list \$18.00

Special Offer: Write for Special Introductory Offer, and 4-page illustrated folder.

AMPERITE Company, Inc.
561 BROADWAY • NEW YORK 12, N. Y.
Canada: Atlas Radio Corp., Ltd., 560 King St. W., Toronto

TWIN-TRAX* TAPE RECORDERS



...give you more

MORE MODELS
the most complete variety of recorders for professional, semi-professional and experimenter use.

MORE FEATURES
for better quality, smoother performance and easier operation.

MORE VALUE
because our direct sales policy saves you dealer markups.

Send today for our catalog 5109 which lists complete technical specifications and performance ratings for all recorder models and accessories. *Trademark Reg.

AMPLIFIER CORP. OF AMERICA
398 Broadway New York 13, N. Y.

BE A RADIO AMATEUR!

A profitable hobby that can lead to better-paying jobs, preferred positions and ratings in the armed forces, worldwide friendships with "hams" in U.S. and foreign countries.

Start-out course teaches you quickly, easily, all you need to know to pass F.C.C. Amateur Radio Operators license. Low cost, money-back guarantee. Write for details.

STREAMLINED SELF STUDY COURSES
509 Fifth Ave. Dept. B New York, N. Y.

RADIO SCHOOL DIRECTORY

Learn Easily at Home

- CONSTRUCTION OF ROBOTS
- COMPUTING MACHINERY

—and Many Other Scientific Subjects

Complete, comprehensive courses or guided study, by mail, for beginners or advanced students. Individuals or Study Groups. Courses fitted to your own interests and needs. Your questions answered promptly. Cost—\$9. to \$35. Write for complete information.

EDMUND G. BERKELEY & ASSOCIATES
INVENTORS OF THE ELECTRIC ROBOTS:

"SIMON"—The Midget Brain
"SQUEE"—The Robot Squirrel

Berkeley is Author of:
"Great Brains or Machines that Think"—Wiley, 1949

36 West 11th St., R-3, New York 11, N. Y.

TELEVISION

Big demand for graduates

B.S. DEGREE IN 27 MONTHS in radio including TV engineering—VHF, UHF, AM and FM. New TV lab. Over \$100,000 worth of equipment. Also new modern physics lab. Intense specialized course includes strong basis in mathematics, advanced design in radio and in TV.

Hundreds of young men each year are earning engineering degrees in this recognized institution. Start any quarter. Many earn a major part of expenses in this industrial center. Low tuition. Competent instruction. Thorough, intense, practical program.

Also B.S. degree in 27 mo. in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. Approved for veterans. Enter March, June, Sept. and Dec. Send for free catalog. **ENROLL NOW**

INDIANA TECHNICAL COLLEGE
1732 E. Washington Blvd., Fort Wayne 2, Indiana

RADIO & TELEVISION
... TRANSMITTERS
LAB. WORK EVERY DAY
LEARN BY EXPERIENCE

REHRIG SCHOOL
11-13 S. GAY ST.
BALTIMORE 2, MD.
Lex. 3195

AUDIO (SOUND) ENGINEERING COURSE
HOME STUDY TRAINING

Prepare yourself, in your spare time for a BIG PAY JOB as an AUDIO ENGINEER. Practical, easy-to-understand lessons, written by nationally recognized Audio Engineers and Educators.

Prepare for a SUCCESSFUL CAREER in the TELEVISION, RADIO, DISC AND TAPE RECORDING, ELECTRONICS AND MOTION PICTURE INDUSTRIES.

Training will not interfere with present employment.

EARN WHILE YOU LEARN
WRITE FOR COMPLETE DETAILS—TODAY

B. M. Klekner, D.Sc., Ph.D.
President

HOLLYWOOD TECHNICAL INSTITUTE
3359 Cahuenga Boulevard
Hollywood 28, California

TELEVISION

LEARN AT HOME! America's newest and most sensational method of home training in television maintenance and repair. Low cost; easy terms. Act now! Write...

TELEVISION TRAINING 531 S.W. 12th Avenue
PORTLAND 5, OREGON

ATTENTION...

A NEW department of the DON MARTIN SCHOOL OF RADIO AND TELEVISION ARTS AND SCIENCES ... for instruction and training in TELEVISION incorporating:

Production Writing, Directing, Producing, Acting, Staging, Lighting

Engineering, Transmission, Receiving, Camera and Studio, Operation, Theory of Video, Pickup and Reproduction.

Approved for veterans.

THE DON MARTIN SCHOOL OF RADIO AND TELEVISION ARTS AND SCIENCES
1655 No. Cherokee, Hollywood 28, Calif. HU. 23281.

RADIO ENGINEERING
FM—Television—Broadcast

Police Radio, Marine Radio, Radio Servicing, Aviation Radio and Ultra High mobile applications. Thorough training in all branches of Radio and Electronics. Modern laboratories and equipment. Old established school. Ample housing facilities. 7 acre campus. Small classes, enrollments limited. Our graduates are in demand. Write for catalog.

Approved for Veterans

VALPARAISO TECHNICAL INSTITUTE
Dept. C VALPARAISO, INDIANA

LEARN TELEVISION

ELECTRONICS and RADIO
Engineering Laboratory and Classroom Training. Day and Evening Classes.

Write for illustrated Catalog

ELECTRONICS INSTITUTE, Inc.
21 HENRY, DETROIT 1, MICH.

RCA RADIO and TELEVISION ELECTRONICS

Thorough Training For Men and Women in All Technical Phases
New Classes (Day & Eve.) Start MARCH 3, 1952
FREE PLACEMENT SERVICE FOR GRADUATES
For Free Catalog Write Dept. RC-52

RCA INSTITUTES, Inc.
A Service of Radio Corporation of America
251 WEST 4TH STREET NEW YORK 14, N. Y.

F.C.C. COMMERCIAL RADIO OPERATORS LICENSE

CRITICAL SHORTAGE OF LICENSED OPERATORS EXISTS!!!

A wonderful future is yours with an F.C.C. commercial radio telephone or telegraph operators license, leading to top-salaried jobs in aviation, broadcasting, transportation and Civil Service. Sensational new simplified HOME STUDY course teaches you in the shortest possible time at lowest possible cost. NO OTHER COURSE LIKE IT! Proven valuable during World War II in speedy training thousands of men, eliminates tedious schooling, exam, papers, wading through books. Each page of text directly related to official F.C.C. exam, questions, thus assuring you of all theory requirements.

The entire up-to-date course, nothing else to buy, containing 250 pages of complete material, diagrams, etc., yours for only \$9.95. Send check or money order; or pay postman \$9.95 upon receipt, plus C.O.D. charges. Complete satisfaction or money refunded within ten days.

STREAMLINED SELF STUDY COURSES
509 5th Ave. Dept. A New York, N. Y.

RADIO COURSES

- RADIO OPERATING • CODE
- RADIO SERVICING • ELECTRONICS
- F.M. TELEVISION

Preparation for Civilian, Maritime, Army and Navy license requirements.

Write for Catalog TE

TRADE & TECH. SCHOOL 15 W. 63 St., N. Y. 23
INDICENT 2-8117

PHYSICAL PRINCIPLES OF WAVE GUIDE TRANSMISSION AND ANTENNA SYSTEMS, by W. H. Watson. Published by Oxford University Press, 114 Fifth Ave., New York 11, N. Y. 6 x 9 1/2 inches, 207 pages. Price \$7.00.

This is an advanced text suitable for physicists and theoretical-minded engineers. It deals with v.h.f. exclusively. Rectangular wave guides are covered in detail. There is also material on various antennas, notably the slot radiator. One chapter describes measurements of frequency, power, standing waves, phase, antenna gain, etc.

Through most of the book, matrix algebra is relied upon to discuss wave phenomena. This method entails less work equation-wise than differential equations, but a knowledge of matrices is presupposed.—IQ

AMPLIFIERS, by N. H. Crowhurst. Published by Norman Price (Publishers) Ltd., 283, City Road, London, E.C. 1, England. 5 1/2 x 8 1/2 inches, 64 pages. Price three shillings sixpence.

There has been a gap in audio literature between the practical material on audio amplifier construction, installation and use, and the engineering treatises on theory and design. Evidently that gap exists on the other side of the Atlantic, too, for the author describes this work as a book to fill the gap between *theory* and *practice*.

Explanations of such things as load lines, oscillation, and matching are therefore given in greater detail than in the standard engineering work, but with more of a theoretical slant than the average build-this-amplifier type of book.

Negative feedback is excepted from the theoretical approach, and little explanation of the "why" is given. The "how" is dealt with in considerable detail, making a complete and concise compendium of information on what negative feedback will *not* do, what it will do, and what circuit arrangements will supply it.

In spite of its small size, this book contains more easily accessible information on amplifiers than any other this reviewer has seen.—FS

RECORD KEEPING FOR SMALL STORES, by Charles H. Welch and Charles H. Sevin. Printed by the U.S. Government Printing Office, Washington, 25, D.C. 6 x 9 inches, 94 pages. Price 65¢.

A book aimed at persuading the small businessman of the necessity of keeping records and training him to do so. Although it is directed to the retailer rather than to the service type of business, and therefore ignores a whole class of records necessary to the owner of a radio or television service business, its style and approach may make it more valuable than many more inclusive bookkeeping texts. For this is by no means a textbook—it is a straightforward how-to-do-it book intended for the practical man.


Can be ordered from the Superintendent of Documents, Government Printing Office. Contains information worth at least the 65¢ it costs.—FS

MARCH, 1952

FREE GIFT

4 in 1 SCREW DRIVER

(Four different drivers in one holder)

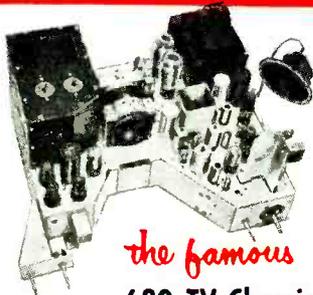

the famous
630 TV Chassis
World's Finest
TV RECEIVER

The New and Improved Super Famous "630" T.V. Chassis, is a 30 tube high quality television receiver (including 3 rectifiers) manufactured under license by the Radio Corporation of America. This chassis is the standard by which all other T.V. chassis are measured.

Standard R.M.A. Guarantee! FREE replacement on all defective tubes and parts.

FEATURES: • Full channel coverage • Discriminator-type FM sound system • Improved picture brilliance • AFC horizontal hold • Keyed AGC • Stabilized vertical hold • 3 stage sync. separator and clipper • Automatic brightness control • 4 Mc band width • Highest quality parts used. All standard tubes • For all Cathode Ray tube sizes and types. 16", 17", 19", 20", 24" Tubes. Perfect for Fringe Area Reception.—Will work where most sets fail to operate.

With HiGain standard coil tuner and R.C.A. Hi-Fi 12" Speaker, complete with knobs and hardware. Complete with Fed. Taxes Paid. Less Cathode Ray Tube **\$141.50**

630 DX Chassis—Extra power for fringe areas. Can be operated without booster or complicated antenna. Complete with Fed. Taxes Paid. Less Cathode Ray Tube. **\$151.50**

Available with DuMont Input Tuner FM Radio, less Cathode Ray Tube.... **\$148.50**

Chassis Mounting Brackets when ordered with chassis..... **\$4.95**



BRAND NEW STANDARD BRAND TUBES— Individually Boxed and Guaranteed

0Z4	.59	6BN6	1.32	7J7	1.19
1A3	.89	6BQ6	1.44	7K7	1.19
1A6	.89	6C4	.76	7L7	1.19
1A7	.98	6C5	.79	7N7	.99
1B3	1.02	6C6	.85	7Q7	.89
1B5 25S	1.09	6CB6	.86	7T7	1.19
1H5	.89	6CD6	2.49	7Y4	.86
1J6	.74	6D6	1.09	7Z4	.84
1L4	.74	6D8	1.39	12A6	.79
1LA4	1.12	6F6	.88	12A8	.86
1LA6	1.12	6F8	1.39	12AL5	.86
1LC5	1.12	6H6	.76	12AT6	.65
1LC6	1.12	6J5	.59	12AT7	1.09
1LD5	1.12	6J6	1.09	12AU6	.89
1LN5	1.12	6J7	.81	12AU7	.96
1N5	.87	6K6	.66	12AV6	.79
1R5	.82	6K7	.74	12AV7	1.24
1S5	.79	6L5	1.39	12AX7	.99
1T4	.83	6L6GA	1.69	12BA6	.79
1U4	.79	6L7	1.19	12BE6	.79
1U5	.78	6N7	1.19	12H6	.89
1V2	.69	6Q7	.59	12AU7	.96
1X2A	.88	6S4	.76	12Q7	.79
2A1G	.84	6SA7	.76	12SA7	.77
2A5	.84	6SF7	.99	12SJ6	.78
3A4	.89	6SG7	.99	12SK7	.77
3Q4	.89	6SH7	.89	12SL7	1.09
3Q5	1.02	6S17	.76	12SN7	1.09
3S4	.88	6SK7	.79	12SQ7	.68
3V4	.89	6SL7	1.10	14A7	1.03
5U4	.65	6SN7	.89	14B6	1.03
5V4	1.10	6SR7	.86	14B8	1.03
5W4	.83	6SQ7	.72	14N7	1.07
5Y3	.47	6T8	1.19	12SL7	1.02
5Y4	.75	6V6	1.69	14R7	1.09
5Z3	.89	6V6GT	.86	19T8	1.34
5Z4	1.12	6W4	.66	25A6	1.09
6A3	1.59	6W6	.89	25BQ6	1.49
6AB7	1.39	6X4	.74	25L6	.85
6AC7	1.21	6X5	.74	25W4	.88
6AF6	1.18	6Y6	.96	25Z6	.74
6AG5	.86	7A4	.89	32L7	1.49
6AG7	1.59	7A5	.99	35L6	.86
6AH6	1.49	7A6	.86	35W4	.58
6AK5	1.49	7A7	.86	35Y4	.80
6AL5	.68	7AD7	1.92	35Z5	.57
6AQ5	.72	7AF7	.89	47	1.34
6AR5	.67	7AG7	1.05	50A5	.96
6AS5	.99	7B5	1.05	50B5	.86
6AS7	5.39	7B6	.89	50C5	.86
6AT6	.68	7B8	.99	50L6	.72
6AU5	1.59	7C4	.79	50Y6	.99
6AU6	.76	7C5	.89	56	.66
6AV6	.67	7C6	.99	70L7	1.69
6BA6	.69	7E3	.99	80	.89
6BA7	1.16	7E6	.99	80	.79
6BC5	.86	7E7	.99	117Z3	.78
6BE6	.82	7F7	.99	2051	1.22
6BG6	1.76	7H7	.96	117N7	1.79
6BH6	.86	7G7	1.21		

TV CONSOLE CABINETS



Designed and built by master cabinet makers. Genuine Mahogany wood with hand-rubbed piano finish. All panels 1/2". Supplied complete with tube mounts, speaker grille and back. (Masks extra, see below for prices). Dimensions—23" wide x 39 1/2" high x 23" deep.

No. 1 Cabinet—For 630 chassis with all holes drilled on front panel for controls and 17" or 20" tube opening (Specify size wanted)

No. 2 Cabinet—Blank front panel to accommodate any make TV chassis. Tube openings for 17" or 20" (Specify size wanted)

Special Price **\$47.95**

17" LUCITE MASK **\$5.95**
20" LUCITE MASK **6.95**

TERMS: 20% cash with order, balance C.O.D. Prices F.O.B. N.Y. City warehouse. Min. order \$5 (allow for postage). Prices in this ad supercede all others published.

TV PICTURE TUBES

ONE YEAR UNCONDITIONAL GUARANTEE
All black faced-non glare—SHELDON, ZETKA and other famous makes.

10BP4A \$22.95	17BP4 \$25.90
12LP4A 22.95	17HP4 27.90
14BP4 23.95	19AP4 35.90
16HP4 31.95	19EP4 35.90
16KP4 28.95	19DP4 55.00
16GP4 31.95	20CP4 35.95
16LP4 31.95	24AP4 69.90

free

CATALOG

UP-TO-THE-MINUTE selection of merchandise including TV antennas, cabinets, parts, hardware and accessories

STEVE-EL ELECTRONICS CORP.

VISIT OUR NEW STORE

Dept. E-3

61 Reade St., New York 7, N. Y.

CR-Hand 7-3886

TAB That's A Buy!

"WILLIAMSON" 10W HI-FI KIT
 10 to 20000 cycles with Ease! Internationally Famous! For HI-FI enthusiasts. Incl Pwr supply, selected parts; Balanced resistors. . . . \$29.95
 W/mson Preamp Kit & Tone boost Amplifier, chassis parts, pwr supply. . . . \$34.95
SUPER-Wide-Range Hi-Fi TRIODE 10W KIT. 10 to 20000 cycles 4B4G's, Max Harmonic Distortion 1/34% at full output & only 1/2% at 3W output. Includes Bass & Treble tube boost & Tone ckt's 4 PreAmp G.E. Pickup 5 dual and 2 output (7) tubes, Parts, RCA chassis & info., less shipping. . . . \$29.95
UTC Hi-Fi Output Xfmr for P.P. 2A3, 6B4, 6A5, & 6L6. Csd cap 30W; Sec 3 taps 2 1/2 to 250 ohms. \$6.98
GE Reluc Cartridge perm needle. . . . \$1.98
GE Dual Reluc Cartridge RPX 050. . . . \$7.29
GE Reluc Cartridge RPX040 or 041. . . . \$7.29
GE S201D Hi-Fi Hvy dty 12" PM Spkr. . . . \$18.98
 Sensational 10" Hi-Fi Spkr Ideal 10 Watt Home Size, Concentric, Separate Driver Woofer & Horn Driver Tweeter—30 to 16000 cps English Mfg. . . . \$18.98
Electro Voice EV16H dual twilt cart. . . . \$3.98
"LP" Anti-Static fluid GUD 1000 plays. . . . 69c
 Extra dual needle for "Twilt" Cart. . . . \$1.98
Phono Motor & Turntable 78RPM 110VAC. . . . \$3.98

TRANSFORMER

TV & CR Pwr Xfmr for 7" to 20" Tubes. HI Volt's, PL & FIL wdg's divrg: 300 VDC/275Ma Full-Wave, 6.4V/10.3A, 5.4V/8A, 2.5V/3A Heater Cove, Oil Impreg. \$7.98
 2500V for CRT, 6.3V/6A, 4V/1.5A 400V.
YON BC412 Replmt. . . . \$7.98
 1320V & 375V/110ma, 5V/3A 2.5V/3.25A, 6.3V/7.275A H'Sid HVins, 2530V/21ma 2x5V/3A 6.3V/1A, 1100VCT/200Ma, 6.3VCT/4A, 5V/3A. . . . \$5.98
 1000VCT/125ma, 500VCT/100ma, 2x5V/3A 18V/1A, 6.3V/8A, 100V. . . . \$5.98
 1000VCT/45ma, 795VCT/80ma & 360VCT/55ma, 3x 5V/3A, 6.3VCT/1A, 6.3VCT/3A Csd HVins can be used 2x rating. Includes U.S. N. rates. Hipersl'd. 1000V/45ma, 2x2.5V/2A, Excellent! 1800V/ DBLR 200 2x2 Fil. Wdg's H'Sid, HVins. . . . \$3.49
 840VCT/110ma, 2530VCT/21ma 2x5V/3A 6.3V/1A, 6.3V/3A Csd HVins Rayth. . . . \$4.98
 770V/2.5ma, 2.5V/3A, HVins incl'd Fltr parts. \$3.69
 750VCT/650MA, 500V Tap. . . . \$11.95
 700VCT/120MA, 2x8.3V/3A, 6.3V/1A. . . . \$4.49
 570V/150ma, 5V/3A, 12V/4A, H'Sid. . . . \$4.49
 500VCT/60ma, 6.3V/4A H'Sid. . . . \$2.98
 420VCT/60ma, 6.3V/1.8A, w/Imp'd 12-24, 115VDC & 115 230VAC VIB Trans. . . . \$1.98 2 for \$3.49

FILAMENT TRANSFORMERS

2x5V 30A ea. Wdg'd 12.5Kv Ins. . . . \$10.98
 6.3vct/4A, 6.3vct/5A, 6.3vct/5A HVins. . . . 2.58
 6.3vct/1A, 3.9vct/1.5A, 3.9vct/1.5A HVins. . . . 3.98
 2.5vct/2A, 79c; 7.5vct/12A 15Kvins. . . . 10.98
 12.6vct/1.25A, \$1.98; 1.8vct/1.25A csd. . . . 1.98
 Phil. 13V/300mA, 12.6V/300mA, 12.6V/300mA
 18, 12, 9-0-9, 12, 18 BRIDGE or CT. . . . 7.70

PLATE TRANSFORMERS

7500V or 15000V dblr/35ma V.E. . . . \$19.95
 3000V/100Ma, 1000V/100Ma, 1000V/100Ma
 5500vct/650ma wstrngs esd. . . . 69.95

SELENIUM POWER SUPPLY

0-12 VDC/2amps Variable DC supply, cased & completely built. 115 V. input. Usable for lab. jammed DC. Plating, batt charging model railroad. Includes voltage or speed control w/center off reversing switch. Ideal for two "H" locomotives.
 "TAB" Special . . . each \$10.95 2 for \$20.00

SOLDERING IRON GUN

Sensational value, light weight, heavy duty soldering gun. W/removable alloy tip will not corrode. Tip is flat, can be used for soldering small and large joints.
 "TAB" special. . . . \$8.98 2 for \$15.98

RECTIFIERS

30Vin/26Vout/150Ma Selen w/mtg flange, 2 units can connect in C. Full Wave. . . . \$5.98
 Full Wave Bridge Selen for relays or Pwr, Inpt 115 to 130 vac; Outpt 115vdc/40Ma. Ea. 69c; 10 for . . . \$5.98

Current (Cont)	18/14	26/18	36/28	54/40
	volts	volts	volts	volts
1 amp	2.20	1.95	1.95	6.50
2 amps	3.65	3.50	3.50	8.75
4 amps	5.40	5.40	5.40	14.00
6 amps	6.70	8.10	10.75	24.00
10 amps	7.50	14.00	14.00	23.25
20 amps	12.75	16.20	20.25	47.50
24 amps	14.00	24.30	26.00	59.50
30 amps	18.50	24.30	29.00	59.50
36 amps	25.00	40.50	42.50	105.50
50 amps	39.50	40.50	59.50	105.50
70 amps	50.00	80.00	84.00	

CT rectifier 100amp 10-30-10 volts
 180-18V @ 70Amp \$2.75; 360-36V @ 70Amp. . . . \$35.00
 Full Wave Selen Rect & Trans. with Ageing Taps in Kit form, at Fraction of usual price. All 115V/60cy up to 16VDC at 12 amps. . . . \$2.95
 up to 32VDC at 12 amps. . . . 36.50
 up to 32VDC at 48 amps. . . . 149.50
 up to 24VDC at 6 amps. . . . 16.98
 up to 24VDC at 10 amps. . . . 16.98
 * This 6 amp & 10 amp supply has no ageing taps.
 We Specialize in Power Supplies to Your Specification.

KITS FOR THE BENCH

Silver & Mic Cndrs. . . . 30 for \$2.50
 Controls, 50 ohms to 2 Megs. . . . 10 for 2.98
 Resistors, 1/2 & 1W, to 2 Megs. . . . 100 for 3.98
 Vitreous MW Res. for 100. . . . 69
 Sockets: Asstd, 8, 7, 5, 4P. . . . 25 for 2.49
 Rotary Switches, Asstd. . . . 6 for 1.75
 Coil Forms, Th'd Sm HF. . . . 50 for 1.00
 Iron Core Slug & Screw. . . . 50 for 1.00
 Elastic Stop Nuts, Asstd. . . . 50 for 1.00
 Knobs, Asstd. w/Insert. . . . 10 for .98
 Spaghetti Sleeving. . . . 75 ft for 1.00
 Ceramicon Cndrs, Asstd. . . . 12 for 1.00
 Grommets, Rubber, Asstd. . . . 50 for 1.00
 Resistors, 2 Watt Asstd. . . . 25 for 3.69
 Tie-Point Lugs, Asstd. . . . 25 for .98

INFRARED SNOOPERSCOPE

Image-Converter Tube HiSensitivity simplified design 2 1/2" tube. . . . \$29.95
 Resolution up to 350 lines/in. Complete data & tube. Each \$4.98; 2 for \$9.49
CODE PROBE . . . Unexcelled for MW Loss VHF testing. Ultrasensitive subminiature-envelope, App. 1 1/4"x3/8". Element and probe at 1/2" center hit.
 Brand New, w/data VR92. . . . 25c; 5 for \$1.

NEW TV COMPONENTS

HW Horiz dAen Outp Xfmr Sim RCA 211T5. . . . \$1.98
 15-16" Picture Tube. . . . 39c
 Width Control Sim 201R4. . . . 1.69
 UTC88662 VBOXfmr H'Sid. . . . 79c
 ERIE HW Condns 500mm. . . . 89c
 JEFFERS Condns 500mm/20KV. . . . 98c
 ION Trap Permimagnet Type. . . . 98c
 12 of 12 1/2" Tube Picture Frame Mask. . . . 2.49
 TWINEX TV 3000ft Cable 100 ft. . . . \$1
 Vert Integrating Netwk CPR3 3 Res & 3 Cndrs only con 29c.
 2X 00AMID 600V 23c. . . . \$1
TV CONICAL ANTENNA (Dubi-X) elements & 100 ft. All-Copper TwineX, Cross Bar & Hd ware. . . . \$8.49
 Dual-Stacked Conical Ant. Similar above, but 10" elements plus 2 crossbars & 100 ft. TwineX. \$12.98

Prices Subject to Change.
 Dept. 3RE, 6 Church Street
 New York 6, N. Y., U. S. A.
 Cor. Church & Liberty Sts.
 Room 200, Phone Worth 2-7230

ADVERTISING INDEX

Adelman, Nat	130
Aerovox Corporation	60
Allied Radio Corp.	13
Almo Radio Company	132
American Phenolic Corp.	70
Amperite Company, Inc.	134
Amplifier Corporation of America	75
Anchor Radio Corp.	135
Arky Radio Kits, Inc.	124
Astak	111
Astron Corporation	111
Atlas Sound Corp.	124
Audio Publishers	118
Barry Electronics Corp.	136
Belden Manufacturing Co.	6
Bell Telephone Labs.	6
Blonder-Tongue	74
Brook Electronics, Inc.	110
Brooks Radio & Television Corp.	125
Burstein-Applebe	118
C & G Mfg. & Sales Co.	124
Candler System Co.	126
Capitol Radio Engineering Institute	137
Certified Television Labs.	97
Crisin, H. G.	132
Columbia Electronics	11
Columbia Electronics Sales	124
Commercial Trades Institute	132
Communication College	137
Coyne Electrical & TV Radio School	111, 125
Davis Electronics	131
DeForest's Training, Inc.	9
DeMont Labs., Allen B.	Inside Front Cover
Editors & Engineers	94
Electro-Culionics, Inc.	123
Electro-Products Labs.	84
Electro-Video, Inc.	60
Electronic Instrument Co., Inc.	116
Electronic Measurements Corp.	122
Engineering Associates	97
Feiler Engineering Co.	91
Gem Radio and Television Corp.	92
General Industries Co.	122
General Test Equipment	109
Don Co., Inc.	98
Grayburn Corporation	126
Greylock Electronics Supply Corp.	109, 101, 102, 103, 104, 105
Heath Company	99
Hudson Specialties Co.	109
Hytron Radio & Electronics Co.	59
Indiana Technical College	97
Instructograph Company	78
JFD Manufacturing Co., Inc.	78
Jackson Electrical Instrument Co.	117
Jensen Manufacturing Co.	112
Lafayette Radio	128
LaPointe-Plascomold Corp.	69
Leotone Radio Co.	115
Macmillan Company, P. B.	Inside Back Cover
Mallory & Co., Inc.	108
Matison Television & Radio Corp.	112
McGraw-Hill Book Co.	118
Merit Coil & Transformer Corp.	118
Midwest Radio & TV Corp.	124
Miles Reproducer Co., Inc.	124
Miller Company J. W.	121
Milwaukee School of Engineering	123
Mosley Electronics	131
Moss Electronics	119
National Electrical Institute of Cleveland	130
National Plans Co.	5
National Radio Institute	3
National School	130
National Video Corp.	79
New England Television Corp.	117
Niagara Supply Corp.	116
Oak Electronics	127
Oak Ridge Products	114
Oxford Electric Corp.	131
Opportunity Adlets	80
Perfection Electric Co.	95
Perrin Electronics	110
Pickering & Company	129
Plastoid Corp.	110
Precision Apparatus Co., Inc.	110
Prentice-Hall, Inc.	92
Pres-Probe Co.	92
Progressive Electronics Co.	122
Quam-Nichols Co.	19
RCA Institutes, Inc.	65, 67, Back Cover
RCA Victor Division (Radio Corporation of America)	65, 67, Back Cover
Radiart Corporation	63
Radio Apparatus Corp.	109
Radio City Products	111
Radio Dealers Supply	137
Radio Merchandise Sales, Inc.	137
Radio Receptor Co., Inc.	72
Berkeley & Associates, Edmund C.	14
Electronics Institute, Inc.	14
Hollywood Technical Institute	131
Indiana Technical College	69
Martin School	78, 77
RCA Institutes, Inc.	65, 67, Back Cover
Rohrig School	74
Streamlined Self Study Courses	78
Television Training	78
Valparaiso Technical Institute	128
YMCA Trade & Technical School	116
Rauland Corporation	82
Raytheon Manufacturing Corp.	80
Regency Div. (I.D.E.A., Inc.)	80
Relay Sales	130
Rider-John, Publisher, Inc.	69
Fincham Books	78, 77
Rose Company	94
Sams & Co., Inc., Howard W.	21, 62, 83
Sarnet, Robert	83
Simpson Electric Co.	68
Snyder Manufacturing Co.	61
Soundcraft Labs.	78
Sprague Products Co.	17
Sprayberry Academy of Radio	57
Supreme Radio & Electronics Corp.	131
Standard Transformer Corp.	90
Steve-El Electronics Corp.	135
Supra-El of Washington, D. C.	113
Superior Instrument Co.	113
Supreme Publications	93
Supreme Radio & Television Co.	115
Sutton's Wholesale Electronics, Bill Tab	136
Talbot Electronics, Inc.	116
Technical Applience Co.	113
Technifax	112
Tel-A-Ray Enterprises, Inc.	114
Telematic Industries, Inc.	97
Telrex, Incorporated	97
Transvision, Inc.	65
Trio Mfg. Co.	127
Triplet Electrical Instrument Co.	87
Tri-State Electronics	91
Tung-Sol Electric, Inc.	8
Turner Company	16
Vee-D-J	131
V. H. Radio & Elec. Sup. Co.	89
Vard Products Corp.	85
Webster Electric Co.	107
Wholesale Radio Parts Co., Inc.	139
Workshop Associates, Inc.	80
Z-Lab. Co.	80

SELENIUM RECTIFIERS—Full-Wave Bridge Types

Current (cont.)	18/14	36/28	54/40	130/100
	Volts	Volts	Volts	Volts
2 Amps	\$2.40	\$3.75	\$6.95	\$10.50
4 Amps	3.85	7.00	9.00	
6 Amps	5.65	9.00		33.00
10 Amps	6.95	10.95		48.00
12 Amps	7.50	14.00		58.00
20 Amps	13.25	20.50		
24 Amps	14.00	26.00		
30 Amps	19.00	30.00		
36 Amps	25.50	35.00		

All our Rectifiers are new & Guaranteed one year. We manufacture special types of rectifiers and rectifier supplies to your specs. . . . FAST DELIVERY.

• Selenium Rectifier Specials
 110 V., 1/2 Wave. . . . 65 ma. . . . only 59c each
 110 V., 1/2 Wave. . . . 450 ma. . . . only \$1.65 each

• New, Selenium Rectifier Transformers
 PRI: 110V, 60 cycle in. . . . 4 Amps. . . . \$ 8.75
 SEC: 18, 24, and 36 12 Amps. . . . 16.75
 Volts 24 Amps. . . . 35.75
 Made to Our Specs. for Continuous, Heavy-Duty Use

• 110 V. PRI.—36 V. @ 50 Amp. SEC. . . . \$39.95
 • 110 V. PRI.—5 V. @ 190 Amp. SEC. . . . 75.00

QUALITY TUBES TESTED

Large stocks available, new and guaranteed in stock now; many others not listed—complete line of receiving tubes at low prices. In ordering tubes listed below, you may also order types not listed, at about same prices. Buy in full confidence on 100% guaranteed merchandise. Submit your requirements on any types for our quotation. Call us on Westinghouse and other types of industrial and special-purpose tubes. Large stocks of germanium crystals. Before you buy, let us quote.

0A2	\$1.00	6BE6	.50	12AT7	\$1.00
0B2	1.10	6BG4	1.20	12AU7	.75
0Z4	.65	6BH6	.80	12AV6	.55
1A7GT	1.00	6BK7	1.40	12AY7	2.75
1B3GT	.85	6BQAGT	.70	12BA6	.70
1A4E	1.10	6C4	.65	12BA7	.90
1N21	.80	6C8G	.70	12BE6	.70
1N21B	3.50	6CR8	.85	12BH7	1.00
1N23	1.45	6CDAG	1.75	12SH7	.95
1N23A	2.50	6F7	.98	12SJ7	.75
1N23B	3.75	6F8G	.98	12SK7	.75
1N34	.65	6H6	.75	12SL7	.75
1R5	.65	6J5GT	.55	12SQ7	.75
1U4	.65	6J6	.75	2580AGT	.98
2B7	.75	6J7	.95	25L6GT	.65
2E24	4.75	6K6GT	.79	35C5	.60
2E26	3.25	6K7	.75	35Z5GT	.55
3A4	.85	6K8	.80	50C5	.60
3A5	1.10	6L7	.98	50L6GT	.60
3D4	.50	6R8	.90	80	.60
3Q4	.55	6SA7	.75	304TL	9.95
3Q5GT/G	1.00	6SF5	.85	304TH	9.95
354	.90	6SG7	.98	717-A	.98
5FP7	1.95	6SH7	.70	807	1.65
5U4G	.59	6SK7	.75	955	.45
5V4G	1.05	6SL7GT	.75	956	.37
5X4G	.85	6SN7GT	.65	1616	.75
5Z3	.95	6SQ7	.75	1624	1.40
6AB4	.75	6T8	1.25	1625	.40
6AC7	.98	6U4GT	.80	1626	.40
6AJ5	1.65	6VAGT	.60	1629	.30
6AK5	.95	6V6M	1.50	5608-A	3.95
6AK6	1.30	6W4GT	.60	5910	.75
6AL5	.55	6X4	.45	9004	.44
6AG5	.85	6X5GT	.45	9005	1.50
6AH6	1.50	7A6	.65	9006	.44
6AN5	2.95	7H7	.80	VR-90	1.00
6AU6	.65	12A6	.75	VR-105	1.25
6AV6	.55	12C8	.85	VR-150	.90
6BA6	.70				

NEW! Bromeco 10 or 20 meter DeLuxe Compact AM Mobile XMTR, 50 watts, complete @ . . . \$89.95 net
 • TV "Cheater" Cord—6 Ft. Complete, U.L. App'd, Reg. net 59c. Special39c

• Mazuire 75 meter Mobile AM XMTR. Only 6"x6" w/built-in Pwr. Pack. New @ \$25.00 complete.

• AR-II—Complete Radio Station in a Suitcase! Superhet RCVT, and 33 watt CW XMTR Built-in AC Supply. Write for Details.

• CARTER, 6 Volt Dynamotors Brand New—400 VDC @ 375 ma. List \$71.40—Special. . . . \$28.00

"NOTE: COLLEGES, UNIVERSITIES, INSTITUTIONS, LABS, M'FRS, IND

POWER TRANSFORMERS

Comb. Transformers—115V/50-60 cps input.

CT-77B	5500V/0.02A, 2.5V/2A 12KV TEST	
	6.3VCT/6A—4600V TEST	\$12.95
CT-75B	1200VCT/600MA, 2X3VCT/6.2A	
	6.3VCT/3A, 6.3VCT/3A	14.95
CT-825	360VCT	3.10
	6.3VCT/3A	3.95
CT-626	1500V	.160
	2.5/12, 30/100	9.95
CT-15A	350VCT	.070
	6.3/6, 6.3/1.8,	2.95
	3 lbs.	
CT-071	110V	.200
	33/200, 5V/10,	4.95
	2.5/70	6.95
CT-378	2300V	4 MA
	2.5/70	6.95
CT-721	550VCT	.100
	6.3/1, 2.5VCT/2,	2.95
CT-99A	2x110VCT	.010
	6.3/1A, 2.5VCT/	
	7A	3.25
CT-403	350VCT	.026 MA 5V/3A
	2.5V/2.1A,	2.75
CT-610	1250	.002 MA 2.5V/1.75A
	2.5V/1.75A	4.95

Plate Transformers—115V/50-60 cps input.

Item	Rating	Each
PT-919	1200-0-1200 200 MA	\$8.95
PT-31A	2x300V/5 MA	.79
PT-033	4150/400 MA	49.95
PT-403	Auto: 70V/1A	2.29
PT-160	1120VCT/70 MA, 590VCT/82 MA,	
	25 lbs.	24.95
PT-170	Auto: 156/146/136/128—71A	3.29
PT-31A	2x300V/5 MA	.79
PT-976	120VCT/10 MA	.79
PT-12A	260VCT/1.2A	2.95
PT-611	4730VCT/500 MA 12KV INS	29.95

Filament Transformers—115V/50-60 cps input.

Item	Rating	Each
FTG-31	2.5V/2.5 7V/7A (Tape @	
	1.5V/2.5A), 16 lbs.	\$9.95
FT-674	8.1V/1.5A	1.10
PT-157	4V/16A, 2.5V/1.75A	2.95
PT-101	6V/.25A	.79
PT-924	5.25V/21A, 2x7.75V/6.5A	17.95
PT-104	6V, 5A	4.79
PT-824	2x20V/2.5A, 10.5V/1A, 7.2V/7A,	
	6.4V/10A, 6.4V/2A	12.95
PT-357	9VCT/45A	14.75
PT-463	6.3VCT/1A, 5VCT/3A, 5VCT/3A	5.49
PT-55-2	7.2V/21.5A, 6.5V/6.85A, 5V/6A,	
	5V/3A	8.95
FT-986	16V @ 4.5A or 12V @ 4.5A	3.75
PT-384	6.3/2.5A, 2.5/1.5V/7A	4.19
PT-A27	2.5V/2.5A, 7V/7A TAP 2.5V/2.5A	
	16KV TEST	18.95
PT-340	2 x 2.5V/3A, 7V/7A—23KV TEST	24.95
PT-038	63V/500A WELD	29.45

KLYSTRON TRANSFORMER

PRI: 115V, 60 CY.
SEC: 1050V/10MA, MINUS 625V/5MA, 26.3V/
4.5MA, 2x2.5V/3A, 6.3V, 3A.
Stock No. CT-311. Only a few left at... **\$22.45**

Send M.O. or CHK. Mdse. Guard. Shpg. Charges
Sent C.O.D. Price F.O.B. N.Y.C. Phone Di. 9-4124

COMMUNICATIONS EQUIPMENT CO.

131 Liberty St. Dept. C-3 New York City 7, N. Y.

THIS AD MAY BE SMALL—BUT IT CAN MEAN B-I-G MONEY TO YOU!

I want to buy BC-348, BC-342, BC-312, ARC-1, ART-13, BC-221 or any parts thereof, no matter how small. In fact, I'll buy anything. I'm not kidding! Let me prove it!

Wire or write: ROBERT SANETT
4668 Dockweiler, Los Angeles, Calif.
Telephone: YOrk 4637



EVERY RADIOMAN Can Use These SERVICE HINTS!

Valuable Manual Yours—FREE!

Every page of "How to Simplify Radio Repairs" is packed with on-the-bench, practical ideas. Contains photos, charts, diagrams—no fluff—no vague theory. In plain every-day language it gives you priceless suggestions—new servicing ideas, you'll use and benefit from the experience of experts. Partial list of contents: How to Localize Trouble; How to Service Amplifiers; How to Test for Distortion; How to Test Audio Circuits; How to Test Speakers; How to Find Faults in Oscillators; How to Test Radio Parts—and it's all yours—FREE! No obligation.



SEND COUPON OR PENNY POSTCARD FOR YOUR FREE COPY TODAY!

FEILER ENGINEERING CO., Dept. 3RC2
8025 N. Monticello Ave.,
Skokie, Ill. (Suburb of Chicago)

Please RUSH my FREE copy of "How to Simplify Radio Repairs."

Name.....
Address.....
City.....Zone.....State.....

SHORT-WAVE RADIATION PHENOMENA, by August Hund. Published by McGraw-Hill Book Co., Inc., 330 W. 42 St., New York, N. Y. 6 x 9 inches, 1382 pages. Price \$20.00, in 2 volumes (not sold separately).

This work is a comprehensive, modern description of h.f. radiation from 30 mc upward. It is a combination handbook, textbook and guide for self-study. Numerous graphs, equations and tables appear throughout both volumes. The author has spared few details of this subject which he knows so well. Most descriptions are rather lengthy.

The first volume is divided into six chapters. The first touches basic fundamentals in theory and calculation. Reference is made to Ampere's and Faraday's laws, Maxwell's equations, vectors, gradients, curl, etc. Many numerical examples are worked out. The treatment is largely descriptive and without rigor.

Succeeding chapters discuss fields of elementary dipoles, propagation, transmission lines and space radiation. A full chapter is devoted to mathematical methods and their application to electromagnetic problems.

The second volume has three chapters and supplementary material. It continues with a discussion of radiation where obstructions are present, diffraction phenomena, wave guides and cavities. A large appendix covers special math functions and their use. It is easy to find a desired subject in the detailed index, which covers 74 pages.—IQ

AUDIO AMPLIFIERS AND ASSOCIATED EQUIPMENT, Vol. 3 (AA-3), compiled and published by Howard W. Sams & Co., Inc., 2201 E. 46th St., Indianapolis 5, Ind. 8½ x 11 inches, 362 pages. Price \$3.50.

This manual—the third in the Audio Amplifier series—gives clear, concise technical details on 50 audio amplifiers and over 20 AM, FM, and FM-AM tuners produced by leading manufacturers during 1950. Like the two earlier volumes, this book is a compilation of folders which have been published previously in Photofact sets. It includes detailed photographs, drawings, schematics, parts lists, and voltage and resistance charts.


This volume is a good buy for technicians, custom builders, instructors, and audio enthusiasts who desire detailed information on the latest audio equipment.—RFS

GUIDE TO BROADCASTING STATIONS (sixth edition, 1951) Published by *Wireless World*, Dorset House, Stamford St., London, S.E. 1. 4 x 5½ inches, 94 pages. Price two shillings twopenny postpaid.


A complete listing of European broadcasting stations by frequency and geographical location occupies the first third of this little book. A listing of shortwave stations of the world—first by frequency, then by geographical location—follows. Other material includes a listing of European television stations, with some operating particulars, and a list of European stations operating above 30 mc. Most of these are frequency modulated.

They're here

THE LATEST RMS ANTENNAS

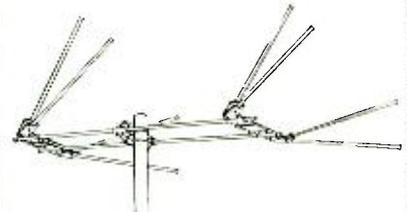

Conical V Fringe Mast Sr.
Model CVA-500
(stacked—CVA2-500; 4-Bay—CVA4-500)

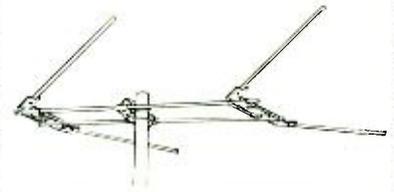

Conical V-Beam Fringe Mast Jr.
Model VA-100
(stacked—VA-200; 4-Bay—VA-400)



Fantenna Super-Fan Array
Model FA-1
(stacked—FA-2; 4-Bay—FA-4)

RMS ANTENNAS



Powerful is the word for these new RMS Antennas. Remarkably advanced in signal-getting ability . . . Each model incorporates new construction features to assure their ability to withstand rigorous service. In addition to single-bay models, units are also supplied for double-bay and 4-bay operation.

Write for descriptive brochure. See your local jobber.

RADIO MERCHANDISE SALES INC.
1165 Southern Blvd., New York 59, N. Y.

TELEPHONE TYPE RELAYS



RELAYS

This list represents only a small part of more than a million relays in our stock—one of the world's largest. All relays are standard, brand new in original packing, and fully guaranteed by Relay Sales. Send us your relay requirements. If the items are in stock we can make immediate delivery at substantial savings in cost to you.

STANDARD TELEPHONE RELAYS

STK. NO.	VOLTAGE	OHMAGE	CONTACTS	UNIT PRICE
R-806	115 VAC	900	1A	\$2.05
R-161	6 VDC	10	2B&1A	1.10
R-873	6 VDC	12	3C-3A MICALEX	3.00
R-305	12 VDC	50	2A Split Cerm.	1.35
R-360	24 VDC	200	1C	1.50
R-484	24 VDC	200	2A, 1C	1.35
R-337	24/48 VDC	1200	1A, 2B Split	2.65
R-101	24 VDC	1300	2A	2.50
R-868	30/162 VDC	3300	1C	1.90
R-365	52/162 VDC	3300	4C	3.95
R-518	85/125 VDC	6500	1C	3.60
R-918	52/228 VDC	6500	1C	3.60
R-852	52/228 VDC	6500	1C, 1A	3.00
R-341	75/228 VDC	6500	4C @ 4 Amps	3.65
R-633	180/350 VDC	10,000	1C @ 5 Amps	2.90
R-344	72/300 VDC	11,300	3A, 1B	2.45
R-332	100/350 VDC	40,000	2A	3.50
R-664	110 VAC	-	2B&1A/OCT.SOCKET	2.45
R-667	6 VDC	.75	1B/10AMP. 1A/3AMP.	1.45
R-632	6 VDC	12	5A&1C	3.25
R-154	6/12 VDC	200	1A	1.50
R-517	12 VDC	250	2A	1.50
R-116	85 VDC	3000	1B	3.05
R-631	100/125 VDC	3300	2A	1.90
R-545	110/250 VDC	7000	1C	2.40
R-124	300 VDC	12,000	1A	1.55
R-511	24 VDC	200	W/MICRO N.O.	3.05
R-160	6 VDC	12	3C&3A	3.00
R-851	52/228 VDC	6500	1C, 1A	3.00
R-591	6 VDC	40	1B&1C	1.35
R-155	12 VDC	100	4A&4B	1.45
R-520	200/300 VDC	14,000	2C	3.45
R-159	6 VDC	50	2A	1.35
R-158	6 VDC	50	4A Cerm.	1.85
R-381	6/8 VDC	100	1A Split	2.50
R-382	6/12 VDC	200	1B Split	2.50
R-153	12 VDC	200	1C&1A	1.55
R-304	12 VDC	200	4A Split Cerm.	2.50
R-383	6/12 VDC	500	1A Split	2.50
R-385	6/12 VDC	500	1B Split	2.50
R-384	6/12 VDC	500	3A Split	3.00
R-576	12 VDC	200	2A	2.50
R-316	24 VDC	200	1C	1.50

SHORT TELEPHONE RELAYS

STK. NO.	VOLTAGE	OHMAGE	CONTACTS	UNIT PRICE
R-635	12 VDC	100	1C&1B	\$1.35
R-308	12 VDC	100	2C @ 4 Amps	1.85
R-343	12 VDC	100	1C	2.00
R-826	12 VDC	150	2C, 1B	1.55
R-770	24 VDC	150	1A/10 Amps	1.45
R-368	8/12 VDC	200	1B	1.40
R-771	24 VDC	200	1A/10 Amps	1.45
R-603	18/24 VDC	400	2A	1.55
R-575	24 VDC	500	2C	2.40
R-764	48 VDC	1000	1C&2A	2.00
R-417	5.5 ma	5800	2C	2.50
R-563	60/120 VDC	7500	1A	2/3.10
R-213	5/8 VAC 60 Cy.	2A	2.50
R-801	115 VAC	NONE	1.45
R-589	12 VDC	125	2A	1.30
R-113	12 VDC	150	4A	1.55
R-689	12/24 VDC	255	1C	1.55
R-799	24 VDC	500	NONE	1.00
R-115	24 VDC	500	1C	1.70
R-110	24/32 VDC	3500	1C	2/3.45
R-121	150 VDC	5000	2A&1C	2.05
R-122	150 VDC	5000	2C/Octal Base	2.50
R-634	150/250 VDC	6000	1A&1B	2.45
R-369	8/12 VDC	150	2A, 2B	1.60
R-908	6 VDC	15	4A @ 4 Amps	1.50
R-800	12 VDC	150	2C&1A	1.55
R-537	12/24 VDC	150	2C&1B	2.00
R-750	24 VDC	400	1A	1.60
R-367	10/16 VDC	195	2C	2.50
R-335	20/30 VDC	700	2A, 1C	2.00
R-366	30/120 VDC	4850	1C	2.50

OTHER RELAY TYPES IN STOCK

- Keying Relays
- Voltage Regulators
- Rotary Relays
- Differential Relays
- Contactors
- Sealed Relays
- Midget Relays
- Special Relays

WRITE FOR CONTACT DATA

Telephone


Manufacturers and Distributors:

Write for the new Relay Sales Catalog.

SEELEY 8-4146

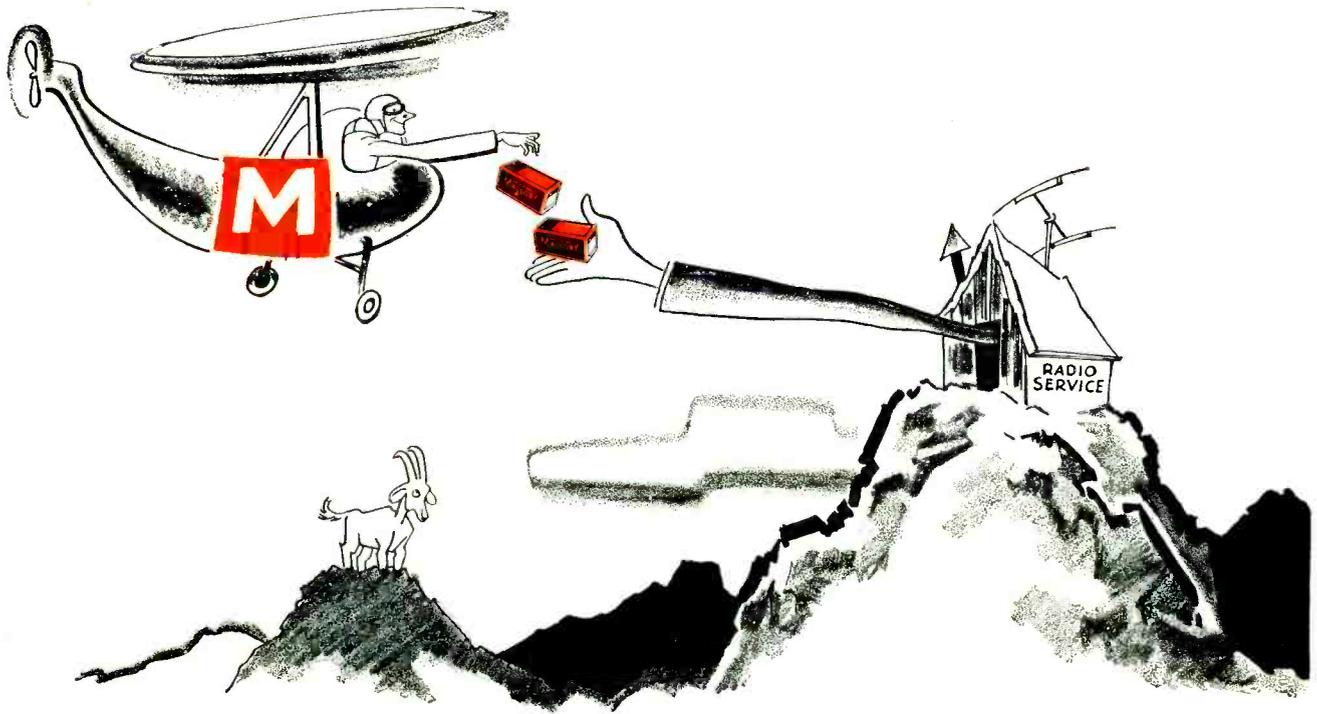833 W. CHICAGO AVE., DEPT. 10, CHICAGO 22, ILL.






TOPS with Servicemen Everywhere . . .

MALLORY VIBRATORS

That's right! In a recent survey, more servicemen preferred Mallory vibrators than all other brands combined. And manufacturers use more Mallory vibrators as original equipment than all other brands combined. Here are the reasons . . .

- 1— Slow contact impact for minimum wear
- 2— High contact pressure for low resistance
- 3— Fast contact break for reduced arcing, pitting

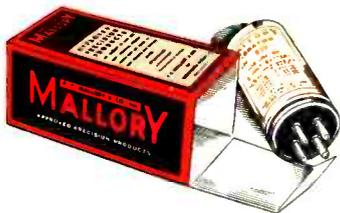You get that vibrator combination *only* from Mallory—thanks to a patented, tuned mechanism. That's why Mallory vibrators give you and your customers long, trouble-free service. When you order vibrators, always . . .



With Just ONE of Mallory's Special Vibrator Deals You Can Service 47 Different Makes of Radios

Think what that means from the standpoint of fast service for your customers . . . and smaller inventory for you—6 Mallory vibrators are all it takes to fix 47 radio makes. When you purchase one of these Mallory vibrator deals at *your regular discount price*, you get a handy parts cabinet at no additional cost. See your distributor today.

Make Sure! Make it Mallory!


P. R. MALLORY & CO. Inc.
MALLORY

CAPACITORS • CONTROLS • VIBRATORS • SWITCHES • RESISTORS
• RECTIFIERS • VIBRAPACK* POWER SUPPLIES • FILTERS

*Reg. U.S. Pat. Off.

APPROVED PRECISION PRODUCTS

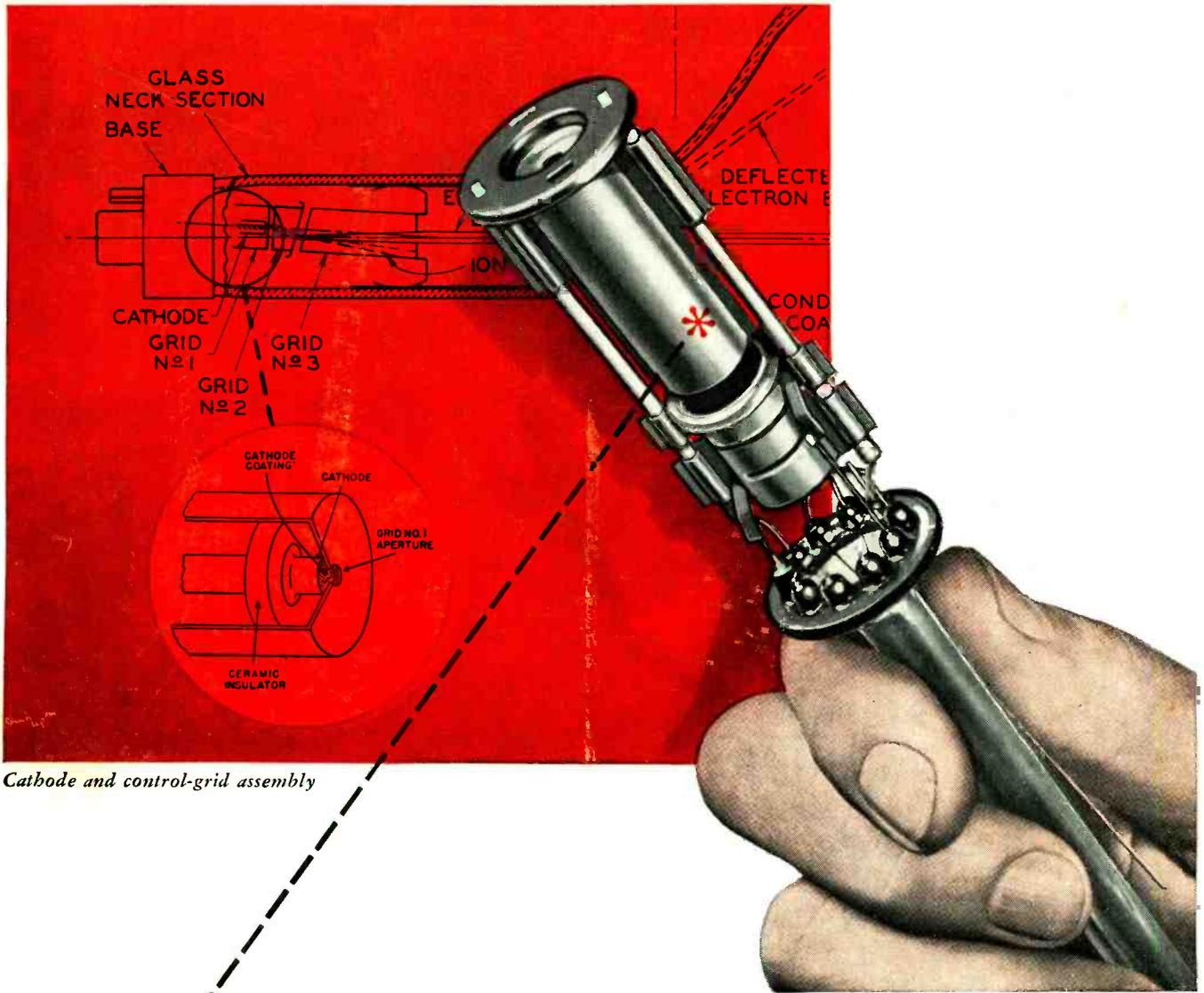P. R. MALLORY & CO., Inc., INDIANAPOLIS 6, INDIANA



Cathode and control-grid assembly

The gun that looked 100% "perfect" ...yet never "fired a shot"

The electron gun you see looks perfect, but actually it "never fired a shot." You see, RCA rejected it because the spacing between grid No. 1 and the cathode was out of bounds. Only a 0.001" departure from the design value for this spacing is sufficient cause for gun rejections in RCA factories.

Why does RCA prescribe such a close tolerance? Simply because RCA engineers have found that if the cathode-to-grid spacing is too small, or too large, the grid would have faulty "control." Such tubes, when installed in TV receivers, may be

the cause of poor picture performance, and may result in troublesome and time-consuming service problems and call-backs.

RCA takes no chances with its reputation for quality. You get the benefit of RCA's quality reputation when you use RCA tubes. Constant vigilance and quality control at all stages of manufacture assure meeting RCA standards on the final production line. That's why RCA picture tubes are unmatched for reliability and uniformity.

In RCA picture tubes, the difference is

top-quality control. That's why, dollar for dollar, RCA picture tubes have no equal.

With RCA Receiving Tubes, as well as RCA kinescopes, **TOP-QUALITY CONTROL** makes the difference.



RADIO CORPORATION of AMERICA
ELECTRON TUBES
HARRISON, N. J.