

15 PAGES OF MOST USEFUL 1955 TV CIRCUIT DIAGRAMS

JANUARY 1956

# RADIO - ELECTRONICS

TELEVISION • SERVICING • HIGH FIDELITY

HUGO GERNSBACH, Editor

9th Annual  
TV Issue

Special Articles  
and Features

•  
Adapt Your Set  
To Receive Color

•  
Trends in Recent  
TV Receivers

•  
Whistle Your Set  
On and Off

•  
Color Television  
Test Equipment

•  
Easily Constructed  
Antenna Orienter  
Uses Transistor



50¢  
U. S. and  
CANADA

Installing a Color TV Receiver  
(See page 4)




Consider ONLY a

# PERFECT REPLACEMENT

when original quality disappears

When the *original* goes, the substitute should be a *Perfect Replacement*. Ordinarily there is only one perfect replacement—something that looks and works as good as the original when new—*or better*. When the original picture tube goes, the *perfect* replacement is a Du Mont Twin-Screen Hi-Lite<sup>®</sup>. The set will sparkle with new picture life... you'll have "new set" quality—*or better*. A Du Mont Twin-Screen Hi-Lite picture tube *replaces* age with "like new" performance.

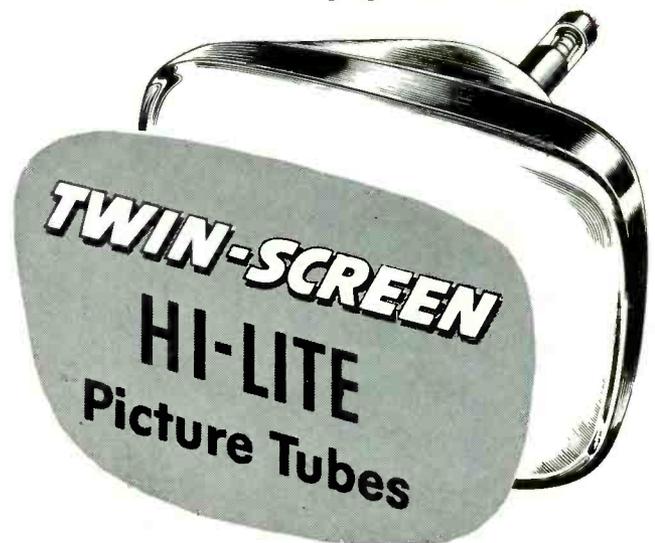
<sup>®</sup>the ultimate in aluminized picture tubes.



## DU MONT<sup>®</sup>

CATHODE-RAY TUBE DIVISION, ALLEN B. DU MONT LABORATORIES, INC., CLIFTON, N. J.
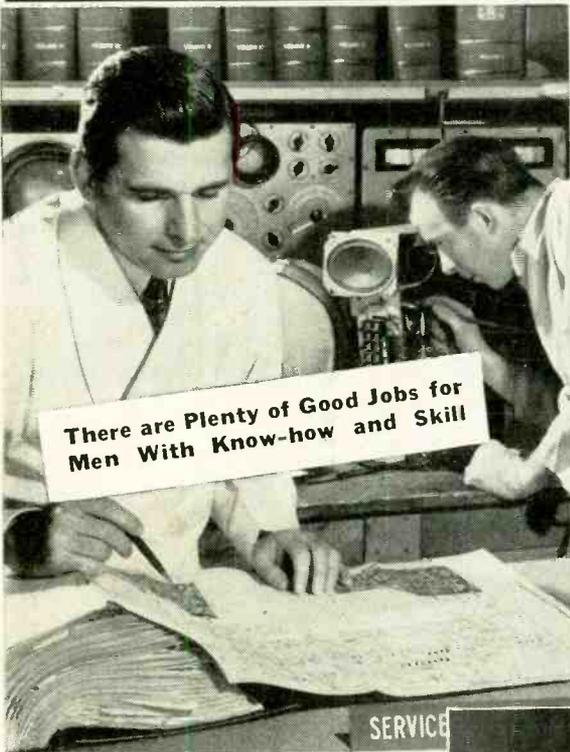
# Learn to Service TV Sets—any make or model—Quickly



There are Plenty of Good Jobs for Men With Know-how and Skill

## New ALL PRACTICE Method trains you at home to become a Professional TV Serviceman


*You learn the time saving techniques, methods used by top TV Servicemen*

This is 100% learn-by-doing, practical training. NRI supplies all necessary equipment, all tubes, including a 17-inch picture tube; and comprehensive manuals covering a thoroughly planned program of practice. You learn how experts diagnose TV receiver defects quickly. You easily learn the causes of defects—audio and video—and how to fix them accurately.

You get actual experience aligning TV receivers, isolating complaints from scope patterns, eliminating interference, using germanium crystals to rectify the TV picture signal, adjusting the ion trap and hundreds of other valuable Professional techniques.

17" Picture Tube, Components for a TV Receiver, Scope, Signal Generator, HF Probe—all included in introductory price under \$200—Easy Terms

If you want to go places in TV servicing, you will act quickly to find out what you get, what you practice, what you learn and how NRI's new course in Professional Television Servicing will help you advance through better technical knowledge and training. See pictures of equipment supplied, read what you practice in book offered FREE to ambitious men with some knowledge of Radio or TV fundamentals. Find out about this ALL PRACTICE Professional TV Servicing Course now.

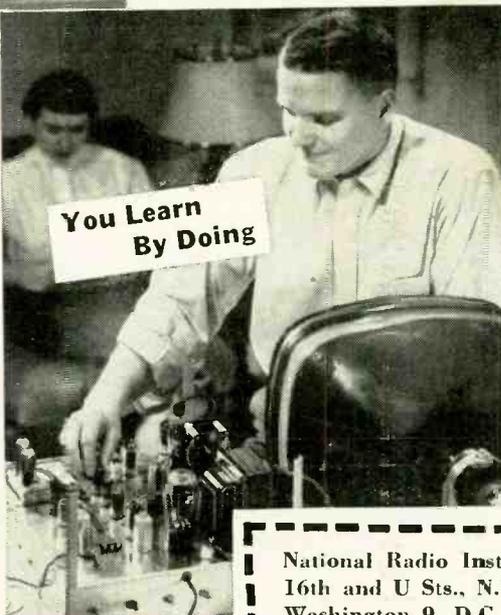

You Learn By Doing

## UHF and COLOR Create Growing Opportunities

To cash in on the present UHF and the coming COLOR TV boom you'll need the kind of knowledge and experience NRI's Course gives. You'll get practice installing front-end channel selector strips in modern UHF-VHF receivers. You learn UHF servicing problems and their solution. Mail the coupon now. Discover how NRI's new course in PROFESSIONAL TELEVISION SERVICING meets the needs of the man who wants to get ahead in TV Servicing.

## Not for Beginners

If you have some knowledge of Radio-TV fundamentals, or have had some Radio Shop experience or some Radio school training, this course IS FOR YOU. Mail coupon today.

Address National Radio Institute, Dept. 6AFT, 16th and U Sts., N. W., Washington 9, D. C.

**MAIL NOW**

## COUPON BRINGS IMPORTANT BOOK FREE

HOW TO REACH THE TOP IN TV SERVICING

Get this book and judge for yourself how this course will further your ambition to reach the top in TV Servicing or help to build a more secure business of your own in TV. Many of tomorrow's top TV Servicemen . . . men who can service any make, any model, UHF, VHF or Color TV . . . will be graduates of this training. Mail the coupon now. There is no obligation.

National Radio Institute, Dept. 6AFT, 16th and U Sts., N.W. Washington 9, D.C.

Please send my FREE copy of "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name..... Age.....

Address.....

City..... Zone..... State.....

Approved Member National Home Study Council

# RADIO - ELECTRONICS

Formerly RADIO CRAFT • Incorporating SHORT WAVE CRAFT • TELEVISION NEWS • RADIO & TELEVISION\*

Hugo Gernsback  
Editor and Publisher  
M. Harvey Gernsback  
Editorial Director  
Fred Shunaman  
Managing Editor  
Robert F. Scott  
W2PWG, Technical Editor  
Jerome Kass  
Associate Editor  
I. Queen  
Editorial Associate  
Matthew Mandl  
Television Consultant  
Elizabeth Stalcup  
Production Manager  
Angie Pascale  
Editorial Production  
Wm. Lyon McLaughlin  
Tech. Illustration Director  
Sol Ehrlich  
Art Director

Lee Robinson  
General Manager  
John J. Lamson  
Sales Manager  
G. Aliquo  
Circulation Manager  
Adam J. Smith  
Director, Newsstand Sales  
Robert Fallath  
Promotion Manager

## GERNSBACK PUBLICATIONS, INC.

Executive, Editorial and Advertising Offices, 25 West Broadway, New York 7, N. Y. Telephone REctor 2-8630.

Hugo Gernsback  
Chairman of the Board  
M. Harvey Gernsback  
President  
G. Aliquo  
Secretary

## ON THE COVER

Our cover this month depicts RCA Service Co. technician Samuel R. Fairbanks, Jr. completing the installation of a color receiver in our Editorial Director's living room—a scene that will be reenacted in many thousands of homes this year.

Color original by Dan Rubin



Average Paid Circulation over 175,000

**JANUARY 1956**

**Vol. XXVII, No. 1**

**9th ANNUAL TV ISSUE**

<b>Editorial (Page 35)</b>			
The Future of Color TV .....	by Hugo Gernsback 35		
<b>Television (Pages 36-92)</b>			
Trends in 1955-56 TV Receivers .....	by Robert F. Scott 36		
Colordapter, Part I .....	by Perry H. Vartanian and Robert W. DeGrasse 40		
Viewing Cyclotron Targets .....	by A. A. Schulke 44		
1956—Television's Year of Decision .....	by David Lachenbruch 45		
New "Rainbow" Tuner .....	by E. D. Lucas, Jr. 48		
TV Receiver Designs in 1955 .....	by H. P. Manly 51		
It's a Matter of Psychology .....	by Guy Slaughter 55		
Whistle Your TV Set On or Off .....	by R. W. L. Mark 58		
Color TV Receiving Tubes .....	by Jerome Kass 59		
Improving Your TV Audio .....	by Norman H. Crowhurst 64		
Britain Takes on Commercial TV .....	by T. W. Dresser 68		
TV Service Clinic .....	Conducted by Jerry Kass 70		
Licensing—Bad or Good? .....	by John A. Wheaton 72		
TV DX in 1955 .....	by E. P. Tilton, WHDQ 74		
Intermittent Foldover .....	by Charles E. Thomas 75		
TV Station List .....	Compiled by Iris Fenster 76		
Most Useful TV Schematics of 1955 .....	77		
<b>Test Instruments (Pages 105-124)</b>			
Color TV Test Equipment .....	by Matthew Mandl 105		
Chroma Signal Generator .....	by Charles W. Rhodes 112		
Electronic Compass Orients TV Antennas .....	by Rufus P. Turner 113		
<b>Audio—High Fidelity (Pages 127-136)</b>			
For Golden Ears Only: Pilot AF-850 AM-FM tuner; Pilot AA-904 audio amplifier; H. H. Scott 710 stroboscopic turntable .....	by Monitor 127		
Table Radios into Hi-Fi Tuners .....	by Joseph Marshall 134		
<b>Miscellany (Page 138)</b>			
Our Abbreviations of Electronic Terms .....	138		
<b>Radio (Pages 139-148)</b>			
Making Photoetched Circuits in Your Workshop, Part II— Sensitizing the laminate, exposing the panel; developing the image; etching .....	by Richard H. Dorf 139		
<b>DEPARTMENTS</b>			
Books .....	194	Question Box .....	175
Business .....	183	Radio Month .....	8
Correspondence .....	4	Radio-Electronic Circuits .....	171
New Devices .....	155	Technical Literature .....	192
New Records .....	152	Technicians' News .....	149
New Tubes and Transistors .....	165	Technotes .....	178
Patents .....	169	Try This One .....	180
People .....	188		



Associate Member of Institute of High Fidelity Mfrs., Inc.

RADIO-ELECTRONICS, January, 1956, Vol. XXVII, No. 1. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-class mail privileges authorized at Mt. Morris, Ill. Copyright 1955 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions.

**SUBSCRIPTIONS:** Address correspondence to Radio-Electronics, Subscription Dept., 404 N. Wesley Ave., Mt. Morris, Ill., or 25 West Broadway, New York 7, N. Y. When ordering a change please furnish an address stencil impression from a recent wrapper. Allow one month for change of address.

**SUBSCRIPTION RATES:** U. S., U. S. possessions and Canada, \$3.50 for one year; \$6.00 for two years; \$8.00 for three years; single copies 35c. Pan-American countries \$4.00 for one year; \$7.00 for two years; \$9.50 for three years. All other countries \$4.50 a year; \$8.00 for two years; \$11.00 for three years.


**BRANCH ADVERTISING OFFICES:** Chicago: 1413 Howard St. Tel. ROGers Park 4-8000. Los Angeles: Ralph W. Harker and Associates, 600 South New Hampshire, Tel. DUnkirk 7-2328. San Francisco: Ralph W. Harker and Associates, 582 Market St., Tel. GArdfield 1-2481. **FOREIGN AGENTS:** Great Britain: Atlas Publishing and Distributing Co., Ltd., London E.C. 4. Australia: McGill's Agency, Melbourne. France: Brentano's, Paris 2e. Belgium: Agence et Messageries de la Presse, Brussels. Holland: Trilectron, Heemstede. Greece: International Book & News Agency, Athens. So. Africa: Central News Agency Ltd., Johannesburg; Capetown, Durban. Natal. Universal Book Agency, Johannesburg. Middle East: Steimatz Middle East Agency, Jerusalem. India: Broadway News Centre, Dadar, Bombay #14. Pakistan: Paradise Book Stall, Karachi 3.

**POSTMASTER:** If undeliverable send form 3578 to: RADIO-ELECTRONICS, 25 West Broadway, New York 7, N. Y.

\*Trademark registered U. S. Patent Office.



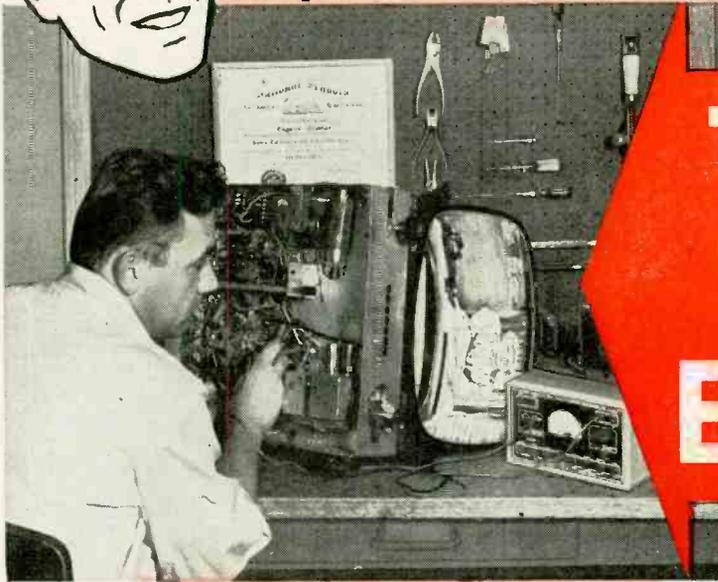**Get more money!  
More security! More out of life!**



# Learn TELEVISION • RADIO • ELECTRONICS

**Get the best!**

## Get National Schools' SHOP-METHOD HOME TRAINING!


Start now! Why wait around for that raise or promotion that may never come? Get started *now* in high-paying TV-Radio-Electronics! National Schools' SHOP METHOD Home Training prepares you for success in a top-salary job or in your own business. You learn *all three*... Television, Radio, Electronics... in one complete course. Our Shop-Tested lessons and manuals help you master all phases in shortest possible time! Send coupon, find out today!

### WHY NATIONAL SCHOOLS LEADS THE FIELD

Located in the "Television Center" of the world, our staff is in close touch with latest developments and opportunities. We give you personalized job placement assistance. We also give you confidential help with both technical and personal problems relating to your training. We show you how to make Part Time Earnings as you progress. Whether you live 30 miles away, or 3,000, you will always be pleased with our prompt, friendly service!

**DRAFT AGE?** Our home training helps you achieve specialized ratings and higher pay grades if you go in service.

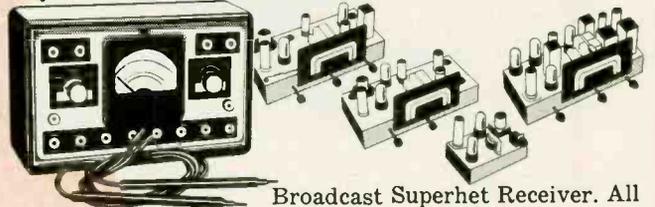We send you this precision-tested Multitester! Plus parts to build Oscillators, Receivers, Signal Generator, Continuity Checker, Combination Short Wave and Standard



Broadcast Superhet Receiver. All this equipment is part of your National Schools course. **NO EXTRA CHARGES!** Send coupon for free books!

**NATIONAL SCHOOLS,** world-famous technical trade school. Now in our 50th year!



## NATIONAL SCHOOLS


**TECHNICAL TRADE TRAINING SINCE 1905**  
LOS ANGELES 37, California · CHICAGO: 323 West Polk St.  
IN CANADA: 811 West Hastings Street, Vancouver, B. C.

- APPROVED FOR G. I. TRAINING
- BOTH HOME STUDY AND RESIDENT COURSES OFFERED

### 30 MILLION TV SETS

need regular repair! Color TV means more sets than ever before. NOW is the golden opportunity to cash in on this multi-billion-dollar industry. Or "write your own ticket" in broadcasting, manufacturing, and other specialized phases!

**YOUR AGE  
IS NO  
OBSTACLE!**

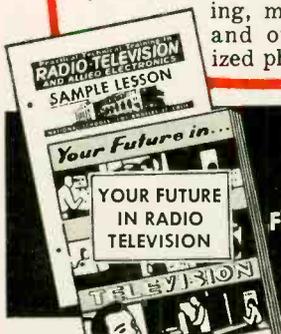

**Send for  
FREE LESSON!**  
FREE BOOK & SAMPLE LESSON  
will convince you!  
**SEND COUPON TODAY!**

### MAIL NOW TO OFFICE NEAREST YOU!

(mail in envelope or paste on postal card)

**NATIONAL SCHOOLS, Dept. RG-16**

4000 SOUTH FIGUEROA STREET OR 323 WEST POLK STREET  
LOS ANGELES 37, CALIFORNIA CHICAGO 7, ILLINOIS

Please rush **FREE BOOK**, "My Future in Radio-Television-Electronics," and **FREE LESSON** at once. I understand there is no obligation, and no salesman will call.

NAME \_\_\_\_\_ BIRTHDAY \_\_\_\_\_ 19\_\_


ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

Check if interested. ONLY in Resident Training at Los Angeles.

VETERANS: Give date of discharge \_\_\_\_\_

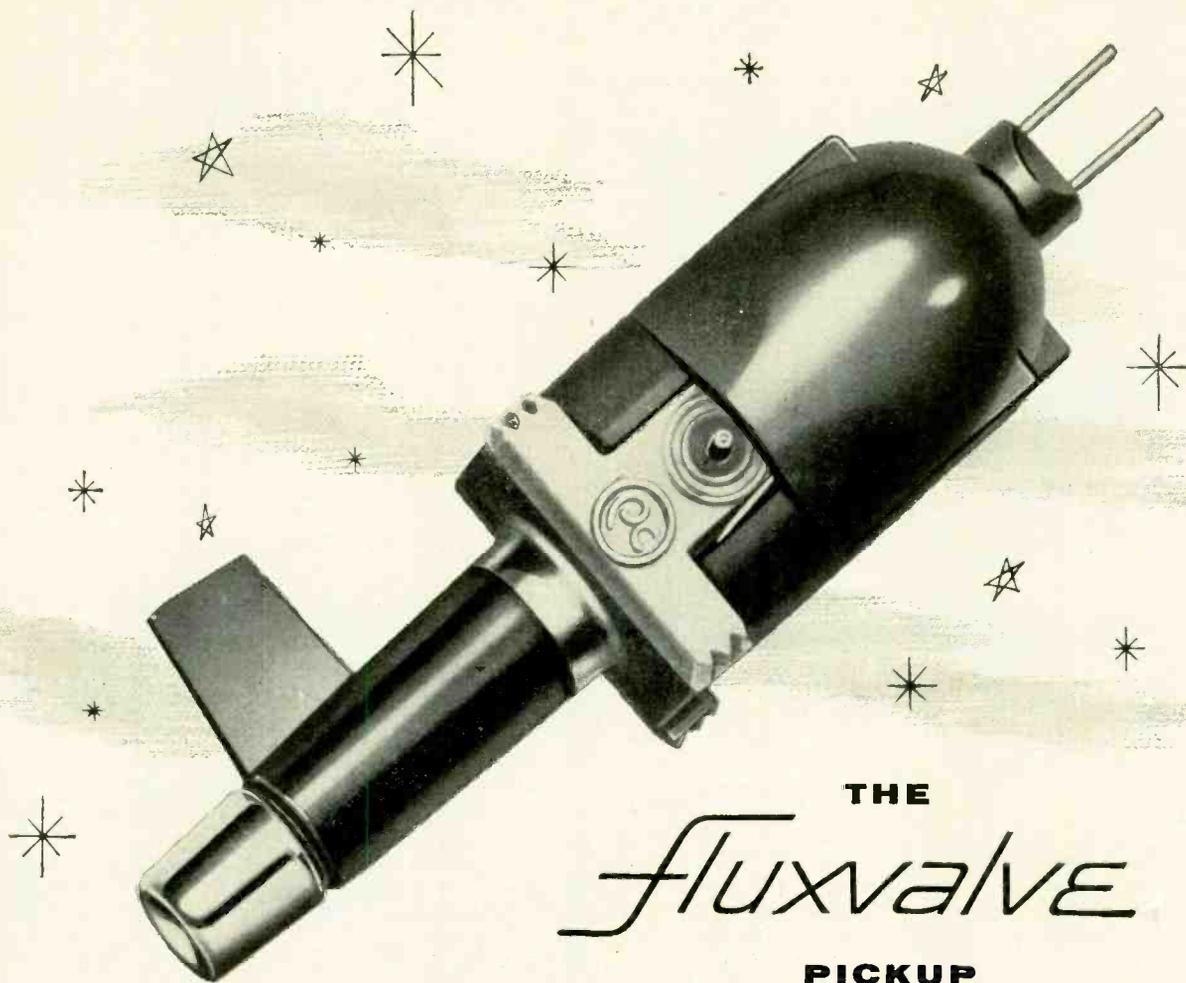*the first really new pickup in a decade*



THE  
*Fluxvalve*  
PICKUP


**Made by perfectionists—for perfectionists.** The FLUXVALVE is literally the cartridge of the future, its unique design meets the demands of all presently envisioned recording developments, including those utilizing less than 1 mil styli.

**There is absolutely nothing like it!** The FLUXVALVE Turnover Pickup provides the first flat frequency response beyond 20kc! Flat response assures undistorted high frequency reproduction — and new records

retain their top "sheen" indefinitely, exhibiting no increase in noise . . . Even a perfect stylus can't prevent a pickup with poor frequency characteristics from permanently damaging your "wide range" recordings.

With this revolutionary new pickup, tracking distortion, record and stylus wear are reduced to new low levels.

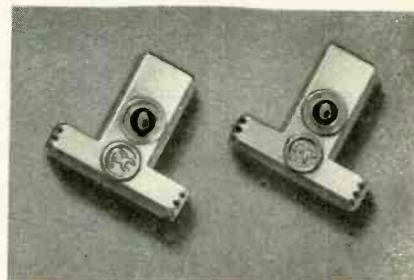The FLUXVALVE will last a lifetime! It is hermetically sealed, virtually impervious to humidity, shock and wear...with no internal moving parts.



The FLUXVALVE has easily replaceable styli. The styli for standard and microgroove record playing can be inserted or removed by hand, without the use of tools.

For a new listening experience, ask your dealer to demonstrate the new FLUXVALVE...words cannot describe the difference...but you will hear it!

**"FOR THOSE  
WHO CAN  
HEAR THE  
DIFFERENCE"**



**PICKERING & CO., INC.**  
OCEANSIDE, LONG ISLAND, N. Y.  
PIONEERS IN HIGH FIDELITY

... Demonstrated and sold by Leading Radio Parts Distributors everywhere. For the one nearest you and for detailed literature: write Dept. W-9.

# Here's an amazingly effective way to learn TELEVISION RADIO and ELECTRONICS in spare time AT HOME... or at DTI's big Chicago training center

What will mailing the coupon below do for YOU? First, you will get . . . absolutely free . . . the valuable publication, "89 Ways to Earn Money in Television-Radio-Electronics." You'll find out about scores of exciting, good paying opportunities in this vast, billion-dollar industry . . . one of the largest, most promising opportunity fields in America today. Best of all, you will find out exactly how you may prepare to get into this good paying work that is so interesting . . . that enables you to start your own business almost "on a shoestring," if you prefer this to a job opportunity.

## NOW . . . get EVERYTHING you need!

You'll also see WHY so many employers ask for DeVry graduates. You'll see that DeVry Tech provides every major training advantage you may need . . . in your spare time at home . . . or in our big million-dollar training center in Chicago. In our home program, you (1) learn-by-reading from easy-to-read, well illustrated lessons, (2) learn-by-seeing from home movies—a wonderful advantage that helps make important points picture clear, and (3) learn-by-doing from 16 shipments of Electronic parts, enabling you to work over 300 fascinating projects.



HOME MOVIES  
VACUUM TUBE  
VOLT-METER  
5 INCH  
OSCILLOSCOPE  
21 INCH

Build and keep this BIG DTI Engineered TV set—easily converted to U.H.F. DTI offers another home training, but without the TV set!

## Valuable Test Equipment Helps You "Earn While You Learn"

As part of your home laboratory projects, you build and keep a top-quality Vacuum Tube Voltmeter and a 5-inch Oscilloscope—two of the most useful pieces of test equipment. No need to buy this expensive equipment later. Little wonder so many DeVry students tell us they are able to earn all, or a good part of the cost of their training, servicing TV and Radio equipment in their spare time.

## MODERN LABORATORIES

If you prefer, get all your preparation in DeVry's new Chicago training center—one of the finest, best equipped of its kind. Write for details!

## EMPLOYMENT SERVICE

Upon completing your training, you can get the full benefit of the same effective employment service that has already helped thousands of DeVry graduates to start earning good money.

## MILITARY SERVICE

If you are subject to Military service, the information we have should be very helpful to you. Mail coupon today.

## MAIL COUPON TODAY!

**89 WAYS TO EARN MONEY IN TELEVISION RADIO ELECTRONICS**

DeVry Technical Institute  
4141 Belmont Ave., Chicago 41, Ill. Dept. RE-1-M

I would like complete facts including "89 Ways to Earn Money in Television-Radio-Electronics."

Name \_\_\_\_\_ Age \_\_\_\_\_  
Street \_\_\_\_\_ Apt. \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_  
6 \_\_\_\_\_ State \_\_\_\_\_

DTI's Training is available in Canada



**DeVry**  
**TECHNICAL INSTITUTE CHICAGO 41, ILLINOIS**  
"One of America's Foremost Television Training Centers"  
Formerly DeFOREST'S TRAINING, INC.





## TUNG-SOL®

### Magic Mirror Aluminized PICTURE TUBE

That electronic miracle, your TV set, picks a world of entertainment out of the air at the fantastic speed of 120 pictures a second!



Leading TV set manufacturers depend upon Tung-Sol Magic Mirror Aluminized Picture Tubes and Receiving Tubes to deliver the exacting performance their engineering standards demand.

This use is indicative of the quality and dependability of Tung-Sol Tubes . . . products of America's largest independent electron tube manufacturer.

TUNG-SOL ELECTRIC INC.  
Newark 4, N. J.

Sales Offices: Atlanta, Chicago, Columbus, Culver City, Dallas, Denver, Detroit, Newark, Seattle, Canada: Montreal.
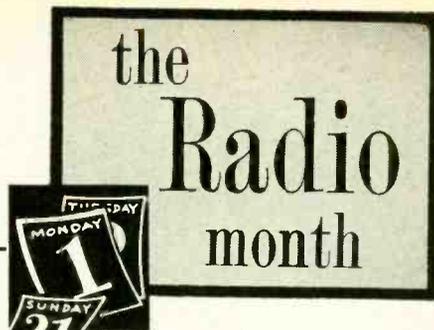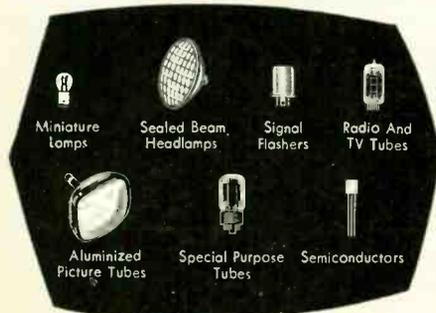
### Tung-Sol Automotive & Electronic Products



**SHALLOWER PICTURE TUBE** is now the subject of concentrated experimentation by television receiver and tube manufacturers, the goal being a smaller and lighter TV set. To date, the industry has come up with a developmental 21-inch 120° tube approximately 3 to 4 inches shorter and from 1.6 to 2 pounds lighter than its 90° counterpart.

The "miniaturization" process has created some major problems: It is more costly and difficult to apply the screen to the tube and aluminize it. Greater input power is required to deflect the electron beam over the wider angle; this means improved and possibly more expensive driving circuitry and transformers. The new wide-angle tube may have to use a narrower neck diameter to place the deflection yoke closer to the electron beam for more efficient deflection.

To minimize these troubles, some tube manufacturers are also experimenting with 110° tubes. Some companies—Westinghouse, Sylvania, Thomas Electronics, Tung-Sol and others—are already sampling prospective customers on a limited basis.

**AWARD TO RCA** in recognition of its lengthy and consistent cooperation with the entire radio and television service industry was made by the Philadelphia Radio Service Men's Association. Presentation of the award, a plaque (see photo), was made by Richard G. Devaney (left), president of PRSMA, and accepted in behalf of RCA by Charles M. Odorizzi, executive vice president, corporate staff, RCA.



Charles M. Odorizzi—left—of RCA receives award for cooperation from Richard Devaney, PRSMA's president.

In accepting the award from the nation's oldest association of electronic service technicians (founded in 1928), Mr. Odorizzi cited RCA's longtime close association and cooperation with independent service organizations in providing them with up-to-the-minute technical information.

**THUNDERSTORMS** send signals all the way round the earth, in the form of low-frequency waves that travel between the earth and the ionosphere. A research team headed by Drs. Holzer, Dean and Ruttenburg of the Institute of Geophysics, UCLA, installed a radio receiver in a remote area of the Borrego desert of southern California and recorded signals for correlation with known major thunderstorm activity throughout the world. Signals so far received appear to have been produced by lightning flashes occurring in the great thunderstorm centers of Africa and South America.

Low-frequency signals produced by a bolt of lightning are apparently of the same type that produce radio static but are much too low in frequency to be picked up on a broadcast receiver. Vertical loop antennas were used for determining signal direction.

The isolated California desert was used to minimize interference from power lines. Research was carried out during a period when local thunderstorms were at a minimum.

### Calendar of Events

Montreal Audio Show. Jan. 18-20. Windsor Hotel, Montreal, Canada.

Toronto Audio Show. Feb. 1-3. Prince George Hotel, Toronto, Canada.

1956 Los Angeles High Fidelity Music Show. Feb. 8-11. Alexandria Hotel, Los Angeles.


**ALL-COLOR TV STATION**, the nation's first, will be WNBQ, Chicago. Beginning about April 15 all its local programs will be in color. Including the color programs on its regular NBC network broadcasts, WNBQ will transmit approximately 10 hours of color per day.

The announcement was made by David Sarnoff, board chairman of RCA and NBC, in a closed-circuit color TV press conference held simultaneously in New York and Chicago. Work on replacing the present monochrome TV equipment with color facilities is already well under way.

free
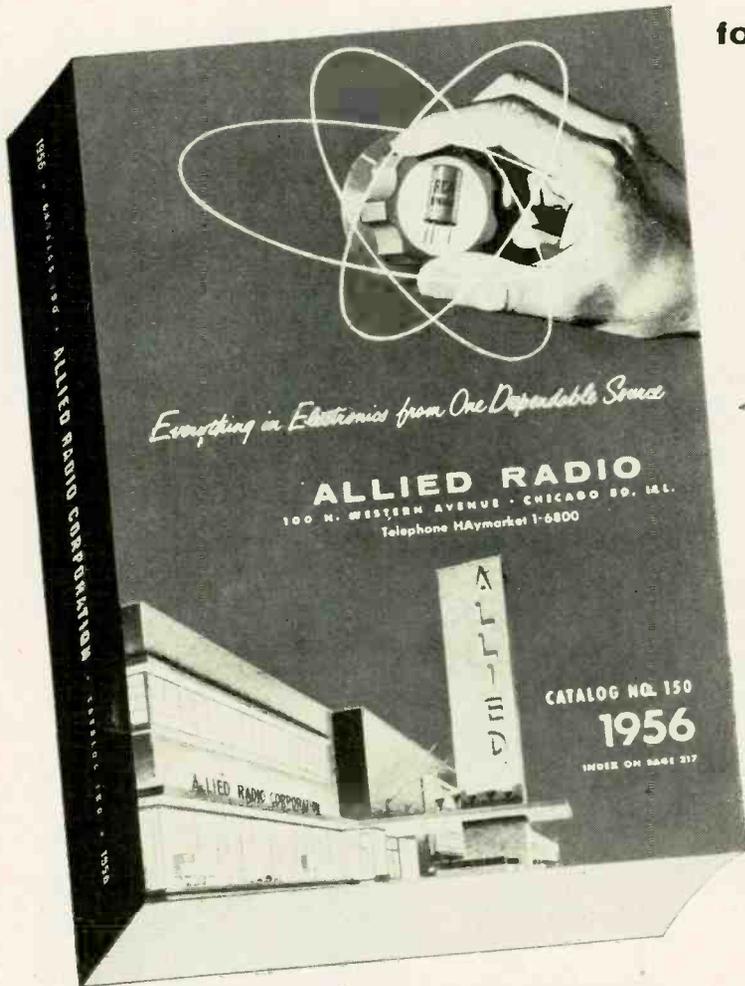
# ALLIED'S 1956 value-packed 324-PAGE CATALOG

the only **COMPLETE** catalog  
for everything in TV, Radio, Hi-Fi  
and Industrial Electronics



Get ALLIED's 1956 Catalog—it's *complete*, up-to-date—324 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get *every* buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, assured satisfaction. Send today for your **FREE** copy of the big 1956 ALLIED Catalog.

## World's Most Complete Stocks

- Latest Hi-Fi Systems and Components
  - P.A. Systems and Accessories
- Recorders and Supplies • TV Tubes, Antennas, Accessories • Amateur Receivers, Transmitters, Station Gear
- Specialized Industrial Electronic Equipment • Test and Lab Instruments
- Huge Listings of Parts, Tubes, Transistors, Tools, Books

**Featuring Super-Value Knight-Kits—**  
top quality electronic equipment  
in precision-designed kit form  
**BUY DIRECT AND SAVE**

### EASY-PAY TERMS

Use our liberal Easy Payment Plan—only 10% down, 12 months to pay—no carrying charges if you pay in 60 days. Available on Hi-Fi and P.A. units, recorders, TV chassis, test instruments, kits, Amateur gear, etc.

### HI-FI SPECIALISTS

To keep up with the latest and best in High Fidelity, look to ALLIED. Count on us for *all* the latest releases and largest stocks of Hi-Fi equipment. We specialize, too, in TV supply—and are foremost in the field of Builders' Kits.

free

send for the leading  
electronic supply guide

ALLIED RADIO CORP., Dept. 2-A-6  
100 N. Western Ave., Chicago 80, Ill.

Send **FREE** 324-Page 1956 ALLIED Catalog.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_




## ALLIED RADIO

World's Largest Electronic Supply House

JANUARY, 1956

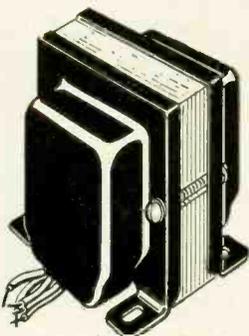MERIT, first in exact and universal replacement transformers, yokes, coils—the only manufacturer of transformers, yokes and coils who has complete production facilities for all parts sold under their brand name.




You find MERIT's leading quality and MERIT's original engineering developments throughout the entire Merit catalogued items—the only single source for all your transformer and coil requirements.
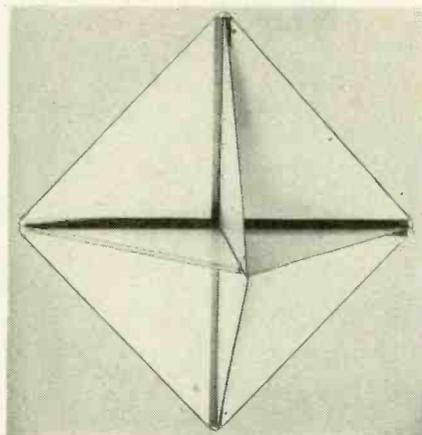
# Merit

MERIT COIL & TRANSFORMER COMPANY  
4427 NORTH CLARK STREET  
CHICAGO 40, ILLINOIS



**ELECTRONIC RED FLAG** designed to make small boats highly conspicuous to the searching eye of radar from larger vessels is being marketed by Raytheon. The unit is a folding device made of sheet aluminum. It can be opened like an umbrella (see photo)



and raised to the top of a mast or held aloft at the end of an oar.

Radar, searching for a small boat, is much more likely to pick up a pip on its screen from the aluminum radar reflector than from a low-lying small craft in the water.

**AURAVISION**, a photographic process that combines sound with printed matter for use in recordings, has been announced by Columbia Records. Using specially treated printed surfaces, recorded speech or music can be transcribed on postcards, instructional brochures, etc. Records of any speed can be produced and played on standard phonographs.

The process requires that the printed matter be limited to four colors. Columbia then photographs the illustration and manufactures the recording, perforated around the edges so that it can be easily removed. Because of cost and quality factors, playing time is limited to 2 minutes. The record may be used about 50 times without appreciable wear.

**RADIO - CONTROLLED TRAFFIC** signals have been installed at 13 busy street intersections in Chicago. Designed and built by General Electric, the central control station is located at City Hall and a transmitter and antenna on the roof of the Board of Trade Building. The control station is linked to the antenna by existing underground cable. This is believed to be the first time such a system has been used under large-city conditions. (For a small-city installation, see **RADIO-ELECTRONICS**, November 1955, page 58.)

The transmitter provides remote control of electronically equipped stop-and-go signals through coded radio tones. Existing stop-and-go lights have been adapted to radio control by equipping them with antennas, receivers, decoders and electronic mech-


anisms. Immediately after a decoder receives its signal, it actuates the timing mechanism of its traffic signal as directed by central control. The most desirable signal timing is put into operation automatically each day but is modified as often as necessary to facilitate the movement of traffic.

**TV HOTEL REGISTRATION** permits motorists to register for rooms without having to leave their cars. Convenient and fast, it allows a guest to go to his room without having to stop at a desk inside the hotel.

A TV drive-in service has been installed by Du Mont for the Temple Hotel in Pendleton, Ore. Cars, driving to a special curbside booth at one side of the hotel, trigger a signaling device which alerts a room clerk inside the hotel. At the same time, the car enters in view of a two-way Du Mont closed-circuit television system, flashing a picture of the driver on a screen inside the hotel. The clerk sees the driver and in turn his picture can be seen by the driver on a screen in the curbside booth. The two can then talk and make the necessary room arrangements through an audio system.

A bellboy then brings a registration sheet to the car, gives the guest the room key, takes his baggage and directs him to parking space in the garage. The TV system does away with traffic jams in front of the hotel.

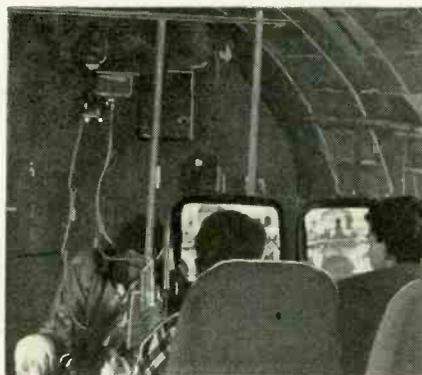
**AIRPLANE RELAY TELECAST** conducted by NBC and the Cuban TV network, CMQ, sent live pictures from Havana into the homes of millions of American viewers. As part of NBC's *Wide Wide World* program of Nov. 13, 1955, the first controlled telecast from an overseas foreign land was relayed



from a plane. The aircraft, flying in a series of tight figure-8's at 11,000 feet and 60 miles from the initial receiving point atop the Fontainebleau Hotel in Miami Beach, Fla., carried the receiving and transmitting relay equipment.

The Havana transmitting post was located atop a 35-story apartment building where TV cameras viewed local points of interest. Other cameras, in the historic Cathedral Square, picked up a portrayal of 1830 Cuban customs and dances.

END

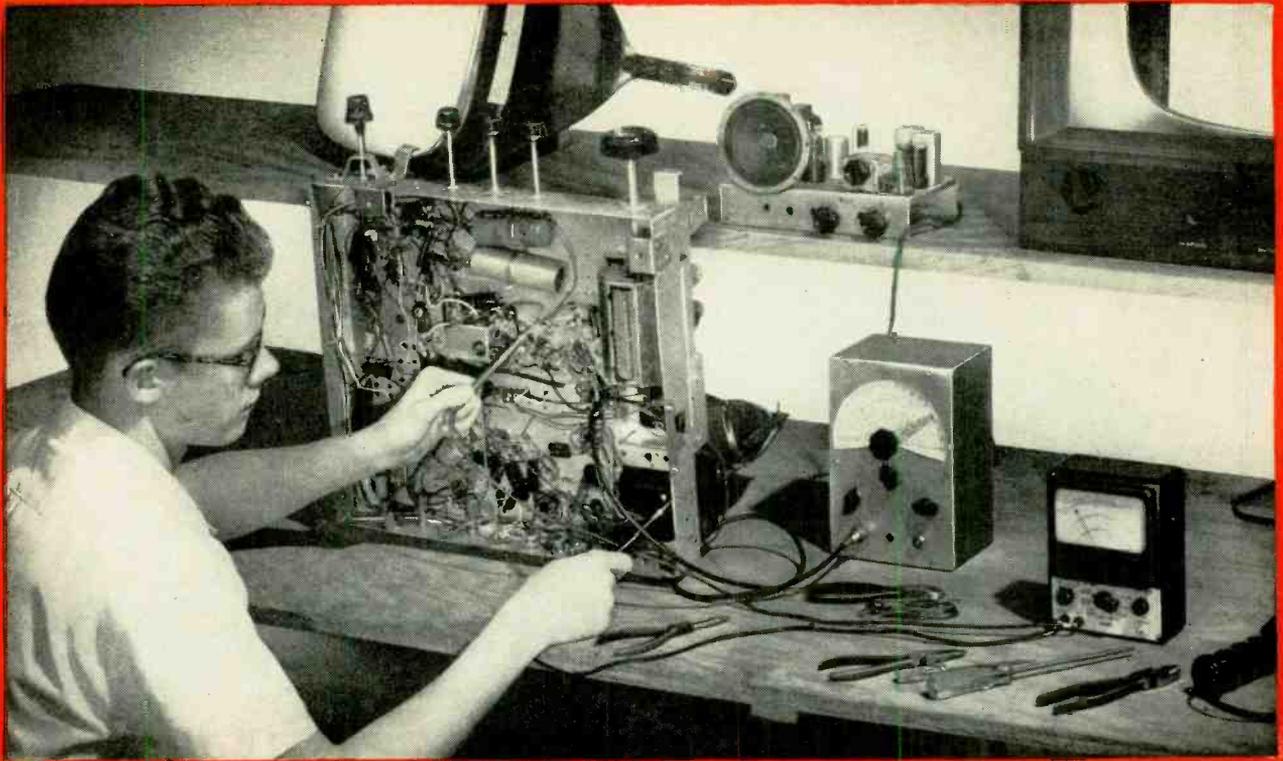

# NOW... RCA trains you at home to be an expert technician in...

**RADIO-TV ELECTRONICS**

**TV SERVICING**

**COLOR TV SERVICING**

**NOW THREE HOME STUDY COURSES...** prepared by instructors of RCA Institutes, engineers from RCA Laboratories, and training experts of the RCA Service Company. Clearly written... easy to understand... the same high caliber instruction as given in the resident classrooms of RCA INSTITUTES.

● **COURSE I—RADIO-TELEVISION ELECTRONICS**—starts you from the ground up to a solid working knowledge of electronics. Without any previous experience, you get a thorough training in radio theory and servicing techniques for AM, FM, home and car radios... plus an introduction to the fundamental theory and practices of television.

● **COURSE II—TELEVISION SERVICING**—prepares you to advance from radio into the expanding field of television servicing as a well-trained service technician. If you have completed Course I or are now working in

the field of radio or TV, Course II will show you the many special techniques of troubleshooting, aligning, checking, and repairing modern black and white TV sets.

● **NEW TV KIT AVAILABLE WITH COURSE II**—there is no better way to learn than by *doing* and RCA Institutes has developed a large-screen TV KIT available to home study students to build while taking Course II. It has the most modern up-to-date circuitry, actually enabling you to apply at home all the latest servicing techniques.

● **COURSE III—COLOR TELEVISION SERVICING**—covers all phases of color servicing techniques. It is a practical, down-to-earth course in color theory as well as how-to-do-it servicing procedure. A natural move "up" from Course II or for those now employed in TV.


**SINCE 1909, RCA INSTITUTES** has trained thousands for successful careers in elec-

tronics. Many graduates have established their own paying business. Now this opportunity is available to you at home.

● **"PAY-AS-YOU-LEARN" PLAN**... you pay for one study group at a time, as you progress through the course. Tuition costs are amazingly low. For full details, mail coupon.

**A SERVICE OF RADIO CORPORATION OF AMERICA—RCA INSTITUTES** is licensed by the N. Y. State Education Department... recommended by radio and television service organizations.

**SEND FOR  
FREE  
CATALOG  
NOW**

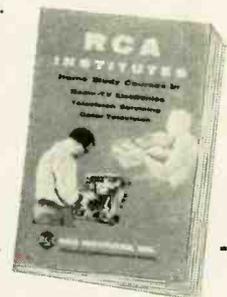

**RCA INSTITUTES, INC.**  
A SERVICE OF RADIO CORPORATION of AMERICA  
350 WEST FOURTH STREET, NEW YORK 14, N.Y.

RCA Institutes, Inc., Home Study Dept. E-16  
350 West Fourth Street, New York 14, N. Y.  
Without obligation, send me FREE CATALOG on Home Study Courses in Radio, TV and Electronics. No salesman will call.


Name \_\_\_\_\_ Please Print

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

only

# C.D.R. Rotors






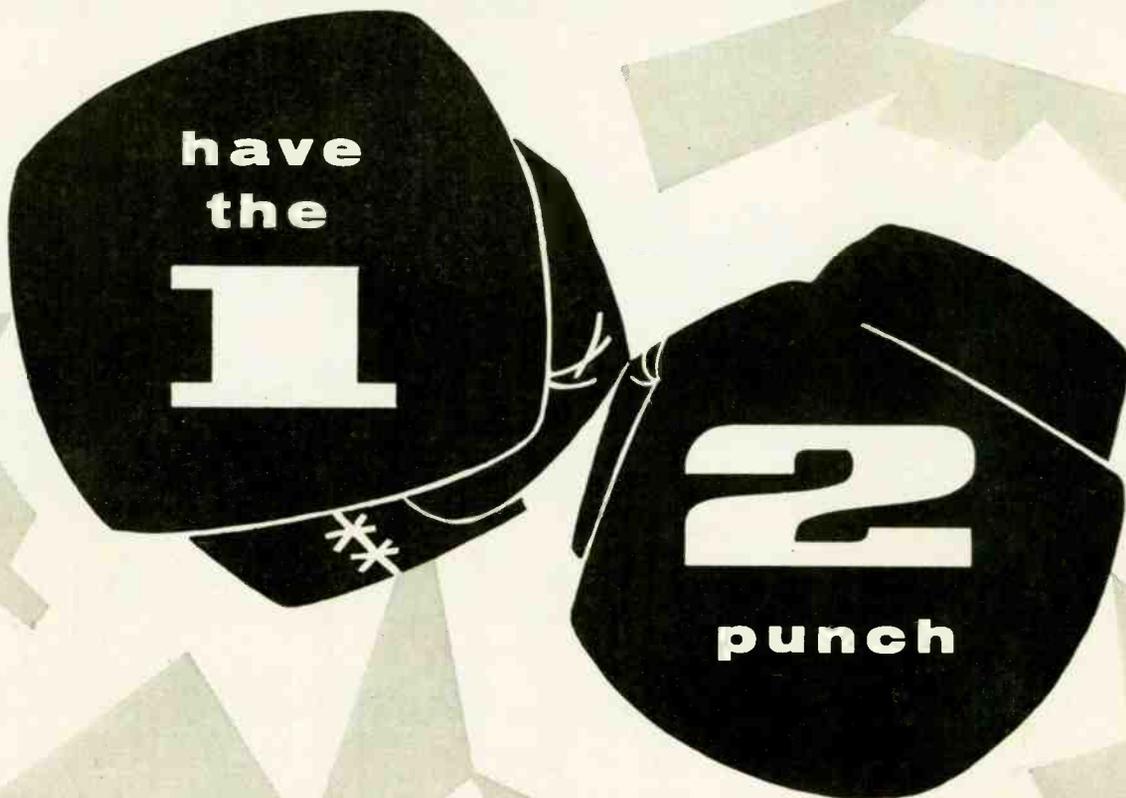


## 1. The Most Complete Line

The CDR Rotor line is COMPLETE to every detail, with a model for every application! A distinct selling advantage because YOU can give your customer EXACTLY what is required! The RIGHT CDR Rotor for the RIGHT job

## 2. Pre-SOLD For You on TV

to millions of viewers through an extensive coverage of audiences in every important TV market. Capture this pre-sold market by featuring these nationally advertised CDR ROTORS.

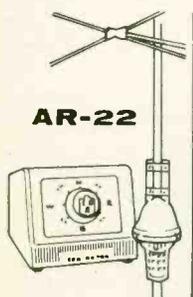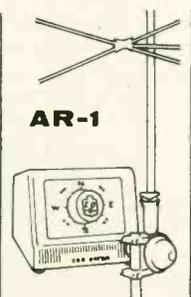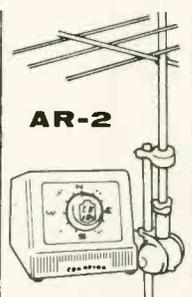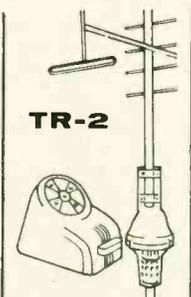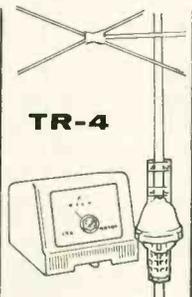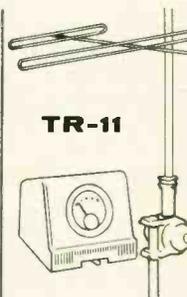 <p><b>AR-22</b></p>	 <p><b>AR-1</b></p>	 <p><b>AR-2</b></p>	 <p><b>TR-2</b></p>	 <p><b>TR-4</b></p>	 <p><b>TR-12</b></p>	 <p><b>TR-11</b></p>
<p>Completely AUTO-MATIC version of the TR-2 with all the powerful features that made it famous.</p>	<p>Completely AUTO-MATIC rotor, powerful and dependable. Modern design cabinet. 4 wire cable.</p>	<p>Completely AUTO-MATIC rotor with thrust bearing. Handsome cabinet, 4 wire cable</p>	<p>Heavy-duty rotor with plastic cabinet. "compass control" illuminated perfect pattern dial, 8 wire cable</p>	<p>Heavy-duty rotor, modern cabinet with METER control dial, 4 wire cable</p>	<p>Combination value complete rotor with thrust bearing. Modern cabinet with meter control dial, uses 4 wire cable.</p>	<p>Ideal budget all-purpose rotor, new modern cabinet featuring meter control dial, 4 wire cable</p>



**CORNELL-DUBILIER**

SOUTH PLAINFIELD, N. J.



**THE RADIART CORP.**

CLEVELAND 13, OHIO

# An Excellent Way to Test Your Understanding of Music

Will you accept **WITHOUT CHARGE** the

Music-Appreciation Recording of

## Brahms' VIOLIN CONCERTO IN D MAJOR

WALTER GOEHR, conducting the LONDON SYMPHONY ORCHESTRA • Endre Wolf, violinist

ON TWO RECORDS (a 12-inch and a 10-inch disc)\*



First play the 12-inch PERFORMANCE record and see how much—and what—you hear in it . . .



Then play the 10-inch ANALYSIS record—and see how much you may have been missing

**\*IMPORTANT, PLEASE NOTE:** Unlike most MUSIC-APPRECIATION RECORDS (see below), this recording, because of the length of the Brahms' concerto, is on two records—a 12" disc with the uninterrupted performance only, and a 10" disc presenting the analysis, written and conducted by Thomas Scherman, Musical Director of MUSIC-APPRECIATION RECORDS.

### SPONSORED BY THE BOOK-OF-THE-MONTH CLUB

THIS NEW IDEA is designed for those who enjoy good music but who are aware, too often, that they do not listen to it with complete understanding and appreciation. There is no doubt about the reason: most of us are not properly primed about *what to listen for*. MUSIC-APPRECIATION RECORDS meet this need—for a fuller understanding of music—better than any means ever devised. This enjoyable form of self-education is comparable to the Music Appreciation courses given in many universities.

**YOU SUBSCRIBE BUT TAKE ONLY THE RECORDS YOU WANT . . .** A new Music-Appreciation Record is issued—for subscribers only—every month. You receive a descriptive Announcement about each record, written by the noted composer and music commentator, Deems Taylor. After reading this Announcement you may take the record or not. You are not obligated to take any specified number of records. And you may stop the subscription at any time!

**TWO TYPES OF RECORDS . . .** All Music-Appreciation Records are high-fidelity, long-playing records of the highest quality—33½

R.P.M. on Vinylite. They are of two kinds: first, a so-called Standard Record—a *twelve-inch* disc—which presents the uninterrupted performance on one side, featuring orchestras and artists of recognized distinction, and on the other side an illuminating analysis of the music with the themes and other main features played separately, with running explanatory comment, so that you learn what to listen for. This standard record is sold for \$3.60 to subscribers only. When the selection, because of its length, requires two records, as in the case of Brahms' *Violin Concerto*—a 12-inch record giving the performance and a 10-inch record giving the analysis—the price is \$4.90 for the two. (A small charge is added to the prices above to cover postage and handling.)

**TRY A ONE-MONTH SUBSCRIPTION — WITH NO OBLIGATION TO CONTINUE . . .** Why not make a simple trial, to see if these records are as pleasurable and as enlightening as you may anticipate? The Brahms recording will be sent to you at once—without charge. You may end the subscription immediately after hearing this recording, or you may cancel any time thereafter. In any case, the gift recording is yours to keep.

PLEASE RETURN ONLY IF YOU HAVE A 33½ R.P.M. RECORD PLAYER

MUSIC-APPRECIATION RECORDS R39-1  
c/o Book-of-the-Month Club, Inc.  
345 Hudson Street, New York 14, N. Y.

Please send me at once the Music-Appreciation recording of Brahms' *Violin Concerto in D major*, without charge, and enroll me as a Trial Subscriber to Music-Appreciation Records, with the privilege of canceling at any time. I understand that, as a subscriber, I am not obligated to buy any specified number of records, but may take only those I want. Also, I may cancel my subscription after hearing the first recording, or any time thereafter at my pleasure, but the gift offer is free in any case.

Mr. }  
Mrs. } .....  
Miss } (PLEASE PRINT)

ADDRESS .....

CITY ..... Postal Zone No. .... STATE .....  
(if any)

MAR 60

Used the World Over  
more than any other  
Microphone!



THE  
**SHURE**

**"UNIDYNES"**

are the only small size, all-purpose moving coil Dynamic Microphones that reduce the pickup of random noise energy by 67%.

The Unidynes, 55s and 556s, simplify P. A. installation . . . enhance your reputation . . . insure customer satisfaction by eliminating or reducing callbacks due to critical gain control settings—often necessary when conventional microphones have been installed.


No wonder the Unidynes are used the World over—more than any other microphones—for finest quality public address . . . theater stage sound systems . . . professional recording . . . remote broadcasting.

**SHURE**

**SHURE BROTHERS, Inc.**

Microphones and Acoustic Devices  
225 W. Huron St., Chicago 10, Illinois  
Cable Address: SHUREMICRO

## Correspondence

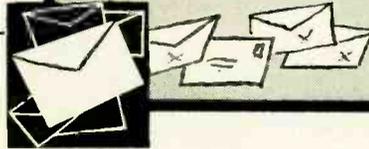

### BRIGGS SPEAKS UP

Dear Editor:


I have recently come across Mr. Augspurger's article "Horn Type Speaker Systems" (May, 1955), a subject on which I too have made many experiments.

The technical press in Britain has often deplored the fact that technicians in the U. S. A. are not always kept informed of what goes on over here, and I am sure that Mr. Augspurger is not aware of developments which took place in this country before the war. I refer to his comments about the Voigt corner horn, which he stated had been developed as the complement of the Lowther P.M.2 driver. This driver is a postwar development; the Voigt corner horn was well known long before the war. I myself heard demonstrations of the Voigt corner horn during lecture tours by Mr. Voigt in the 1930-1938 period. Mr. Voigt then used his excited, high-flux-density field magnet and twin diaphragm in conjunction with his horn and Lowther amplifiers. This combination undoubtedly set the standard in pre-war Britain.

In the Voigt corner speaker the horn which dealt with the middle and upper frequencies used the walls as part of the system while the bass, after expanding through an elongated folded and outwardly expanding air passage, radiated into the room from the corner, using both walls and floor as part of the system. The theory showing the advantages of radiating into one-eighth sphere in this way is clearly set down in Mr. Voigt's British Patent No. 447749 dated October, 1934. In my own little book *Loudspeakers*, published in 1948, I included an illustration of the

Voigt design and described it as an example of the study of room acoustics which was well ahead of its time. The accompanying diagram was published by courtesy of *Wireless World*, who reviewed the Voigt speaker over 20 years ago—in their issue of Dec. 28, 1934.

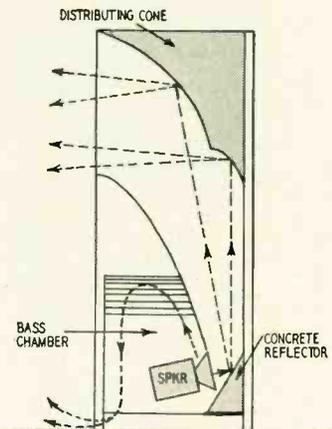When I saw Mr. Voigt in Toronto last year, I was indeed sorry to learn that his business in England had come



to a standstill, but I think it is only fair that he should be given full credit for his original work in the field of corner horn loading of loudspeaker units.

It is nice to learn from articles such as the one by Mr. Augspurger that his fundamental work, not forgotten in England, is also coming to be recognized on your side of the Atlantic.

G. A. BRIGGS  
Managing Director

Wharfedale Wireless Works Ltd.  
Yorkshire, England

### VOIGT AND LOWTHER


Dear Editor:

Mr. Felix' letter (November, 1955) directed me to that of Mr. Chave (July, 1955) which I had missed. Reading the latter indicates that the situation should be cleared up and I hope what follows will do so:

I have known Voigt since before he ever designed a speaker, at the time when he was chief recording engineer for the long-defunct Edison Bell Record Co. of London. As a friendly competitor I watched his progress as an independent speaker designer and manufacturer with the greatest interest

and our diverging views never interfered with our friendship. In my article on speakers (March, 1954) I gave a picture of the twin-cone Voigt unit, which at that time had an electromagnet. This unit was used in conjunction with regular exponential horns of straight form as well as the Voigt corner horn, the latter being a domestic type of loading which worked very well. At a later date Voigt found the need for using permanent magnets. To get the flux and field he wanted some changes were made to the design of the pole pieces; he also cleaned up the gen-
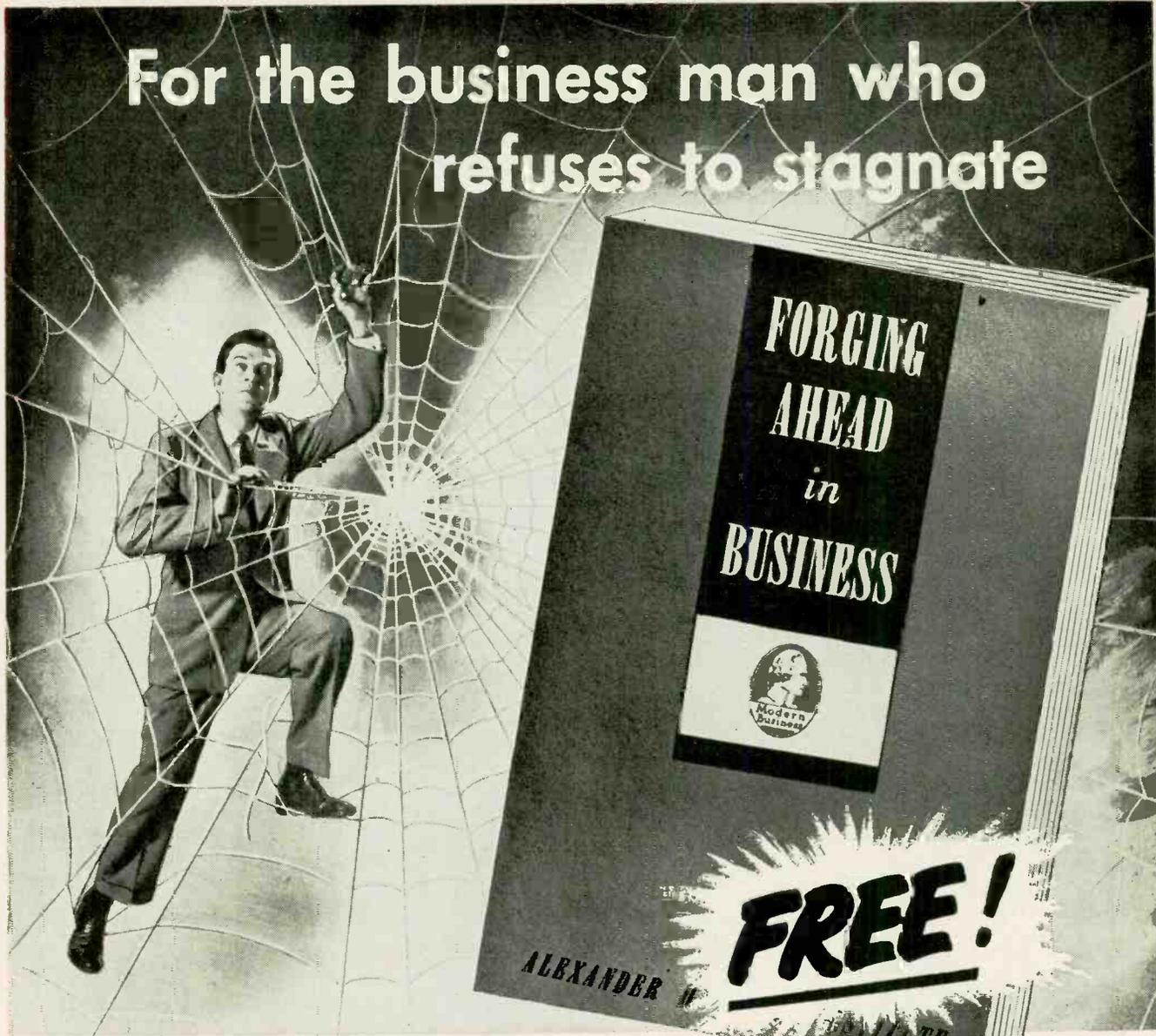
# For the business man who refuses to stagnate



**H**ALF the world is half asleep! Men who could be making *twice* their present salaries are coasting along, hoping for promotions but doing nothing to bring themselves forcefully to the attention of management.

They're *wasting* the most fruitful years of their business lives . . . throwing away thousands of dollars they may never be able to make up. And, oddly enough, they don't realize—even remotely—the tragic consequences of their failure to forge ahead while time is still on their side.

These are the men who are unknowingly headed for the frustrations and the disappointments of mediocrity. They'll go part way up the ladder and down again by the time they're fifty years old. They'll be executive material in their twenties and thirties—and clerks in their fifties. They'll have high hopes for themselves and their families while they're young; but only struggling, skimping and regret later on when their earning power should be at its height.

### Send for Your Free Copy of "Forging Ahead in Business"

If you want to discover how to succeed while you are still young—if you want to avoid the heartbreak of failure in later years—send today for "Forging Ahead in Business" . . . one of the most practical and realistic booklets ever written on the problems of personal advancement.

Here you will find—not a "pep talk," not an academic lecture—but cold, hard facts on how to improve your position and increase your income. You will be told what the qualifications of an executive are in today's competitive market . . . what you must *know* to make \$15,000, \$20,000 or more a year . . . what you must *do* to accumulate this knowledge.

"Forging Ahead in Business" was written for mature, ambitious men who seriously want to get down to bed-rock in their thinking about their business future. If you feel it is meant for you, simply fill in and return this coupon. Your complimentary copy will be mailed to you promptly.



**Mail  
Coupon  
Now!**

#### ALEXANDER HAMILTON INSTITUTE

Dept. 413, 71 W. 23rd Street, New York 10, N. Y.

In Canada: 57 Bloor St., W., Toronto, Ontario, Canada

Please Mail Me, Without Cost, a Copy of Your 48-Page Book—

**"FORGING AHEAD IN BUSINESS"**

Name.....

Firm Name.....

Business Address.....

Position.....

Home Address.....

Problem:

2 TV Sets  
1 Antenna

Answer:



## 2-SET COUPLER

Model TV-42  
Approved for Color TV  
UHF, VHF and FM



Cost: ONLY \$2<sup>95</sup> LIST

### Features:

- Matched resistive circuit
- Flat response—0 to 900 megacycles
- 12db inter-set isolation
- Easy to install
- Couples 2 TV sets without ghost or smear

### Application:

In class A signal areas the B-T 2-Set Coupler provides the ideal low cost solution to the problem of operating two receivers from one antenna. There are other applications. For example, the TV-42 can couple a TV set and FM receiver to one antenna—or it can be used, in reverse, to couple or mix 2 antennas to one receiver.

Write for FREE BOOKLET—"TV for 2 or 3...or More"  
Covers all types of Multiple TV Systems

Sold by Radio-TV Parts Distributors and Jobbers

**BLONDER-TONGUE LABORATORIES, INC.**

Depr. LA-3 Westfield, New Jersey



Manufacturers of TV Cameras,  
TV Amplifiers, Boosters,  
UHF Converters, TV Accessories  
and Originators of the Masterline  
and 'Add-A-Unit' Master TV Systems.

### CORRESPONDENCE

eral chassis design and made it a much tidier looking unit. It was clearly, however, a development of his original design which appeared in my article.

After I had established a skeleton distribution in the U. S. A. for my own speakers I approached Voigt and said that as his design did not compete with mine, I would be very glad to introduce his units to the American market. He said that much as he would like to do that, he had found the strain of running his own business, Voigt Patents Ltd., too much for his rather delicate health and had sold his interests to the Lowther Manufacturing Co. He had, therefore, no jurisdiction over the sale of his speakers anywhere in the world.

At a later date I heard that the Lowther Manufacturing Co. had come to terms with my good friend Victor Brociner to represent them in the U. S. A. But between the time that Voigt had sold out to Lowther and the appearance of Voigt speakers on the American market it is a fact that these speaker units were advertised in the London *Wireless World* as "Lowther-Voigt" speakers. I think this shows beyond dispute that the Voigt designs were acquired by Lowther.

Last winter, during a friendly dis-

cussion with Mr. Brociner on other matters, he asked if I would like to see the latest units he was getting from England. I said I would and had an opportunity of inspecting what Mr. Chave refers to as P.M.2 and P.M.4 units. It would be most improper for me to make any comment on the performance of any other manufacturer's speakers, but from my nearly 30 years' experience of designing speakers I can say that my unhesitating opinion of what I saw was that these units were virtually Voigt speakers of the permanent-magnet type. There may have been some slight modification of the speakers I knew came from the original Voigt factory, but I did not see them. The speakers looked alike and to my ears they sounded alike.

I cannot see why Mr. Chave should take up the attitude so clearly displayed in his letter of July. When all is said and done Voigt's is an honored name in the roll of speaker designers, and I would have thought the attachment of his name to the Lowther output would have been a commercial asset. But this, of course, is Mr. Chave's business, not mine.

H. A. HARTLEY

London, England

### THE VOCATROL

Dear Editor:

Last August I was delighted to find your write-up on the Vocatrol. I have been looking for such an article and trying to devise a Vocatrol ever since I saw one demonstrated at the IRE convention in New York in 1951. Mr. R. C. Jones described how he developed it. He also demonstrated it, even differentiating between a singing commercial and the singing portion of an opera. The loud and lengthy enthusiasm evinced by that overflowing hall of staid engineers was heartwarming.

Calmer consideration with the passage of time caused a little nagging doubt to exist as the performance of the gadget seemed too good, and his name with those initials seemed too appropriate. He said he had applied for a patent, but to date it has not been issued. And having built the Vocatrol described, my doubts grow larger.

I'm not able to make the thing work but, if everyone gets together and points out the gimmicks found in it, maybe they will add up to a workable circuit. Below are those I found:

1. I do not believe that stage V3-a in conjunction with V2-a is a logarithmic amplifier as V3-a is not a variable-mu tube and positive bias developed by V2-a is the wrong polarity.

2. In applying audio to the circuit,

it was found to disappear at the grid of V3-a. This is due to V2-a giving a positive output causing the V3-a grid to draw current and have a conductive resistance small compared to the 10-megohm series resistor. Eliminating this, and then the entire filter, does not help. Reversing V2-a produces a voltage across the 2- $\mu$ f capacitor (about -50 at full gain measured with a 20,000-ohm-per-volt meter on the 300-volt scale) that is usually larger for voice than for music but not reliably so. This is as the article stated. For reversing V2-a causes the device to be actuated by the increases rather than the decreases of signal level. Adding a phase-reversing stage of unity gain following V3-a gave no difference in voltage level across the 2- $\mu$ f capacitor.

Incidentally, the connection shown to the receiver requires that the grid resistor in the receiver be at least several megohms or the 22 megohms be reduced, as the plate voltage of V5 only goes to -80 when the tube conducts.

EDWARD E. PREDMORE

New York, N. Y.

(The item referred to was printed in good faith, using all the information available from the manufacturer. We would be interested in hearing of other readers' experiences with it.—Editor)

### CONVERSION CORRECTION

Dear Editor:

There are, unfortunately, some mistakes in my letter as printed in the November, 1955 issue, which, I am sure, will cause dissatisfaction to anyone at-

tempting to make this conversion.

Item 1 should read:

Remove V104, T111, T112 and input circuitry associated with V104.

Item 2 should read:

**Electronics Boom Seen**

**Need For Television Technicians To Rise**

**Industry Warned About Shortage Of Trained Men**

**TV SALES SET NEW RECORD**

**Sylvania Head Expects Huge Electronic Gains**

**Transistor Radios Developed**

**RCA HEAD PREDICTS SALES BOOM FOR COLOR TV SETS**

**VETERANS - - NON-VETERANS**

# Get Into The Field That's Making Headlines



I. C. Lane, B.S., M.A.  
President, Radio-Television Training Association,  
Executive Director, Pierce School of Radio & Television.

All over the nation the Television-Radio-Electronics industry is making News — News that means opportunity for YOU. You can cash in on the headlines.

**I WILL TRAIN YOU AT HOME FOR A TOP-PAY JOB IN TELEVISION**

I will prepare you for a spot in America's fastest-growing industry. You can become a trained technician in your spare time without giving up your present job or social life. No experience needed.

## LEARN BY DOING

As part of your training I give you the equipment you need to set up your own home laboratory and prepare for a top-pay job or set up your own business. You build and keep an Electromagnetic TV RECEIVER designed and engineered to take any size picture tube up to 21-inch. (10-inch tube furnished. Slight extra cost for larger sizes.) . . . also a Super-Het Radio Receiver, AF-RF Signal Generator, Combination Voltmeter-Ammeter-Ohmmeter, C-W Telephone Transmitter, Public Address System, AC-DC Power Supply. Everything supplied, including all tubes.

Combination Voltmeter-Ammeter-Ohmmeter



C-W Telephone Transmitter

Super-Het Radio Receiver



AF-RF Signal Generator



Public Address System

## STUDY NEWEST DEVELOPMENTS

My training covers all the latest developments in the fast-growing Television-Radio-Electronics industry. You learn about FM — RADAR — COLOR TV — TRANSISTORS — PRINTED CIRCUITS, etc.

## CHOOSE FROM THREE COMPLETE COURSES covering all phases of Radio, FM and TV

1. Radio, FM and Television Technician Course — no previous experience needed.
2. FM-TV Technician Course — previous training or experience in radio required.
3. TV Cameraman and Studio Technician Course — advanced training for men with Radio or TV training or experience.

## EXTRA TRAINING IN NEW YORK CITY AT NO EXTRA COST!


After you finish your home study training in Course 1 or 2 you can have two weeks, 50 hours, of intensive Lab work on modern electronic equipment at our associate resident school, Pierce School of Radio & Television. THIS EXTRA TRAINING IS YOURS AT NO EXTRA COST WHATSOEVER!

## FCC COACHING COURSE

Important for BETTER-PAY JOBS requiring FCC License! You get this training AT NO EXTRA COST! Top TV jobs go to FCC-licensed technicians.
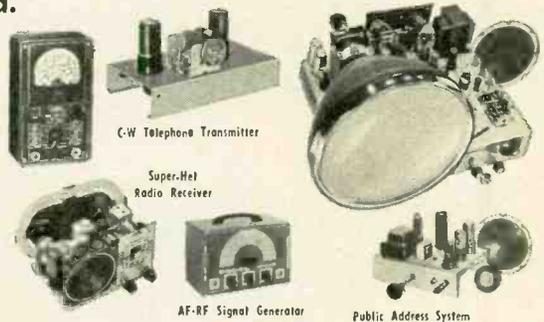
## VETERANS

My School fully approved to train Veterans under new Korean G. I. Bill. Don't lose your school benefits by waiting too long. Write discharge date on coupon.



## EARN WHILE YOU LEARN

Almost from the very start of your course you can earn extra money by repairing sets for friends and neighbors. Many of my students earn up to \$25 a week . . . pay for their entire training with spare time earnings . . . start their own profitable service business.

**FREE** I'll send you my new 40-page book, "How to Make Money in Television-Radio-Electronics," a Free sample lesson, and other literature showing how and where you can get a top-pay job in Television.

**FREE** HOW TO MAKE MONEY IN TV

**FREE** SAMPLE LESSON

## MAIL THIS COUPON TODAY!

Mr. Leonard C. Lane, President  
RADIO-TELEVISION TRAINING ASSOCIATION  
Dept. R-1C, 52 East 19th Street, New York 3, N. Y.

Dear Mr. Lane: Send me your NEW FREE BOOK, FREE SAMPLE LESSON, and FREE aids that will show me how I can make TOP MONEY IN TELEVISION. I understand I am under no obligation.

(PLEASE PRINT PLAINLY)

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

I AM INTERESTED IN:

- Radio-FM-TV Technician Course
- FM-TV Technician Course
- TV Cameraman & Studio Technician Course

## VETERANS!

Write discharge date

# Radio Television Training Association

52 EAST 19th STREET • NEW YORK 3, N. Y.

Licensed by the State of New York • Approved for Veteran Training

## NO OBLIGATION!



Model 5M36 Mahogany  
Chairside High Fidelity Phonograph


**Admiral** . . . famous manufacturer of  
Hi-Fi Phonographs, Television, Radio

**CHOOSES GENERAL INDUSTRIES**

*Smooth Power*

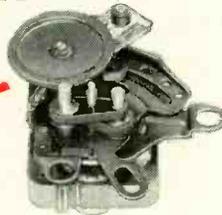**PHONOMOTORS**

**A**dmiral chooses GI phonomotors for original equipment in its famous line of phonographs because experience has proved that *it costs less to buy the best!* GI phonomotors have shown, by years of trouble-free performance, that GI is always the one best choice. When you need phonomotors, take your cue from Admiral, you'll find that *it pays to rely on GI!*



4 SPEED HI-FI MOTOR

Other General Industries AC Induction type motors for applications ranging from 1/40 HP to 1/1100 HP.

Write for specifications and quantity-price quotations today.



**THE GENERAL INDUSTRIES CO.**

DEPT. GE • ELYRIA, OHIO

**50 WATTS** from your **WILLIAMSON**  
New **DYNACO A-430**



**\$29.95**

at your Electronic  
Parts Distributor  
or Audio Jobber

Output transformer and simple circuit modifications let you raise the power of your Williamson-type amplifier to over 50 watts at less than 1% I M distortion. This super-fidelity output transformer will give you *double power and double listening pleasure* with very low distortion and unequalled transient bandwidth. Its unique design uses para-coupled windings, the first basic advance in quality transformer design since the introduction of interleaved windings.

Write for details of new Dynaco output transformers, circuits, and conversion data for Williamson Amplifiers.

**DYNA COMPANY, 5142 Master St., Phila. 31, Pa.**

PAT.  
PENDING

**CORRESPONDENCE**

(Continued)

Install a 4.5-mc pickup coil in the circuit connecting the 6AL5 video detector to the grid of V105.

V105 is necessary as a limiter for the following discriminator stage.

Although noise rejection may be poorer in fringe areas, I doubt that this circuit is any less sensitive than that suggested in Mr. Bierman's article.

It should also be kept in mind that oscillator drift, so troublesome when using u.h.f. converters, is not a problem restricted to fringe areas.

The RCA T120 converts in a similar manner, but all sound tubes must be retained in this circuit since it has one less stage than the 630. Here it is necessary to remove the original input circuitry of the first stage and introduce the 4.5-mc pickup coil instead.

FREDERICK J. NORVIK  
Albany, N. Y.

**ADDING A "SQUARER"**

Dear Editor:

The wide-range oscillator described by Mr. Graham in July, 1954, was an interesting little test instrument. I see in the November, 1955, issue (page 143) that a correspondent wished to add to the circuit to produce square waves in addition to the sine waves of the original instrument.

As I had space on my chassis, I added a "squarer" similar to the one you published. I also installed an extra tube and tuning capacitor to give me an oscillator tuning from TV channels 2 to 6. This gadget adds two controls to the front panel—the tuning capacitor and a switch in the heater of the oscillator tube, but it gives dandy bars, vertical and horizontal, for checking linearity of a TV set.

The output, coupled from the cathode of the new oscillator tube to the grid of the original output tube, is available at the same output terminals from which the audio is obtained.

The bars are clean black-and-white with no smears. In addition, varying the audio produces fantastic patterns on the TV screen. My 2-year-old enjoys them as much as some of the programs.

JOHN DEWAR

RCAF Station  
Clinton, Ontario  
Canada

**TRANSISTOR SYMBOLS**

Dear Editor:

I find your suggestion of using a square or triangle (October, 1955) around transistors better than using a circle. However, I prefer no enclosure. Space should be occupied with factual matter such as voltages, pin numbers, etc.

Circles are not needed around tubes. Anyone not capable of distinguishing a grid from a resistor would not be able to understand any circuit, no matter how drawn.

A. W. CLEMENT  
Galion, Ohio

END

Prepare for a Good Paying Job—Or Your Own Business

Learn PRACTICAL RADIO-TV  
with 25 BIG KITS

of equipment I send you while  
you train with me . . . for valuable  
shop bench experience . . .





17" to 24"  
PICTURE TUBE

This is the new Sprayberry Training Television receiver, built and tested in sections for greatest instruction value.

I now offer this fine modern oscilloscope to help you learn practical Television servicing.

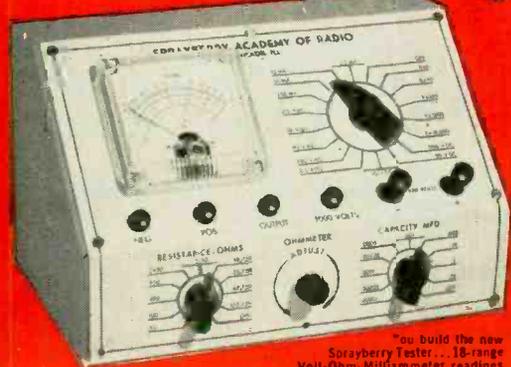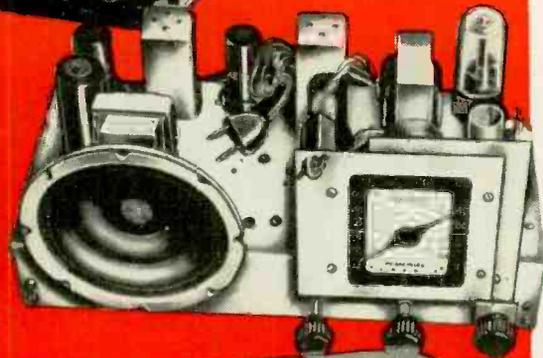You will build this powerful short wave and broadcast superhet radio receiver for valuable shop instruction practice.



You build the new Sprayberry Tester . . . 18-range Volt-Ohm-Millimeter readings plus output meter and condenser and resistor substitution selector.

In addition to modern lesson training, I also give you plenty of home practice on actual Radio-Television equipment . . . you will build and use the units shown here plus many more. All this equipment is yours to keep . . . keep everything you need to set up your shop.

"I Will Train You at Home in  
**RADIO-TELEVISION**  
On Liberal No Obligation Plan!"

New Equipment! New Lessons! Enlarged Course! The true facts are yours in my big new catalog . . . YOURS FREE . . .

JUST MAIL COUPON!

I can train and prepare you in as little as 10 months to step into the big opportunity Radio-Television service field. Train *without* signing a binding contract . . . without obligating yourself to pay any regular monthly amounts. You train entirely at home in spare hours . . . you train as fast or as slowly as you wish. You'll have your choice of THREE SPRAYBERRY TRAINING PLANS . . . planned for both beginners as well as the more experienced man. Get the true facts about the finest most modern Radio-Training available today . . . just mail the coupon for my big new 56 page fact-filled catalog plus sample lesson—both FREE.



Frank L. Sprayberry  
President, Sprayberry  
Academy of Radio

Train the Practical Way—with Actual Radio-Television Equipment

My students do better because I train both the mind and the hands. Sprayberry Training is offered in 25 individual training units, each includes a practice giving kit of parts and equipment . . . all yours to keep. You will gain priceless practical experience building the specially engineered Sprayberry Television Training Receiver, Two-Band Radio Set, Signal Generator, Audio Tester and the new Sprayberry 18 range Multi-Tester, plus other test units. You will have a complete set of Radio-TV test equipment to start your own shop. My lessons are regularly revised and every important new development is covered. My students are completely trained Radio-Television Service Technicians.

NEWEST DEVELOPMENTS

Your training covers U H F, Color Television, F M, Oscilloscope Servicing, High Fidelity Sound and Transistors.

See for Yourself . . . Make Your Own Decision . . . Mail Coupon Today!

The coupon below brings you my big new catalog plus an actual sample Sprayberry Lesson. I invite you to read the facts . . . to see that I actually illustrate every item I include in my training. With the facts in your hands, you will be able to decide. *No salesman will call on you.* The coupon places you under no obligation. Mail it now, today, and get ready for your place in Radio-Television.

**SPRAYBERRY ACADEMY OF RADIO**  
111 North Canal Street, Dept. 20-G, Chicago 6, Illinois

Mail This Coupon For Free Facts and Sample Lesson



SPRAYBERRY ACADEMY OF RADIO  
Dept. 20-G, 111 N. Canal St., Chicago 6, Ill.

Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# The "K.O." is Fantastic!

Features the highest front-to-back ratios ever recorded for any TV antenna:


- **Low band:** from 20:1 to 50:1 relative VOLTAGE.
- **High band:** Up to 13:1 relative VOLTAGE.

**High gain:** Low band, 7 to 9 DB. High band, 8.5 to 10.5 DB. (Single bay figures). Balanced for COLOR.

**Ends co-channel interference!**  
**Knocks out "Venetian Blinds"!**

Channel Masters "K.O." puts an INVISIBLE BARRIER in the path of rear signals, preventing co-channel interference. The "K.O." is completely preassembled with time-saving "Snap-Lock" Action. 100% aluminum.

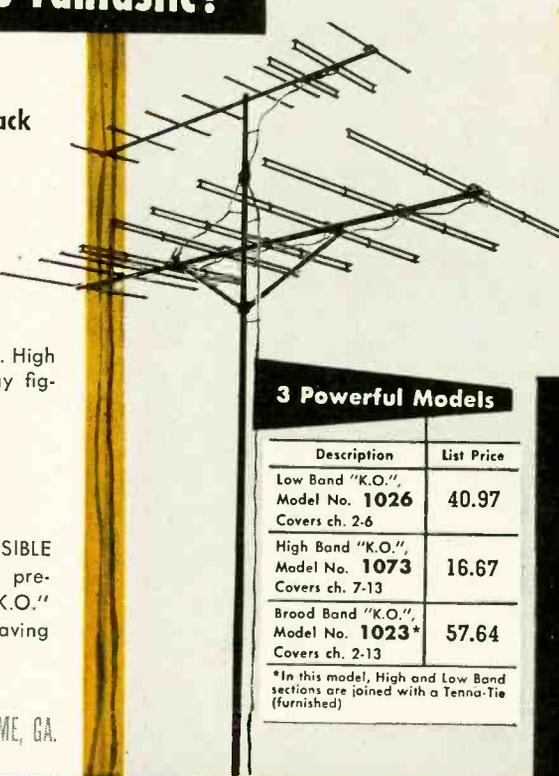LICENSED BY KAY-TOWNES ANTENNA CO., ROME, GA.



### 3 Powerful Models

Description	List Price
Low Band "K.O.", Model No. <b>1026</b> Covers ch. 2-6	40.97
High Band "K.O.", Model No. <b>1073</b> Covers ch. 7-13	16.67
Brood Band "K.O.", Model No. <b>1023*</b> Covers ch. 2-13	57.64

\*In this model, High and Low Band sections are joined with a Tenna-Tie (furnished)


**New Antennas!**

**New Accessories!**

# CHANNEL MASTER

now provides you

## The <sup>new</sup> Super Fan

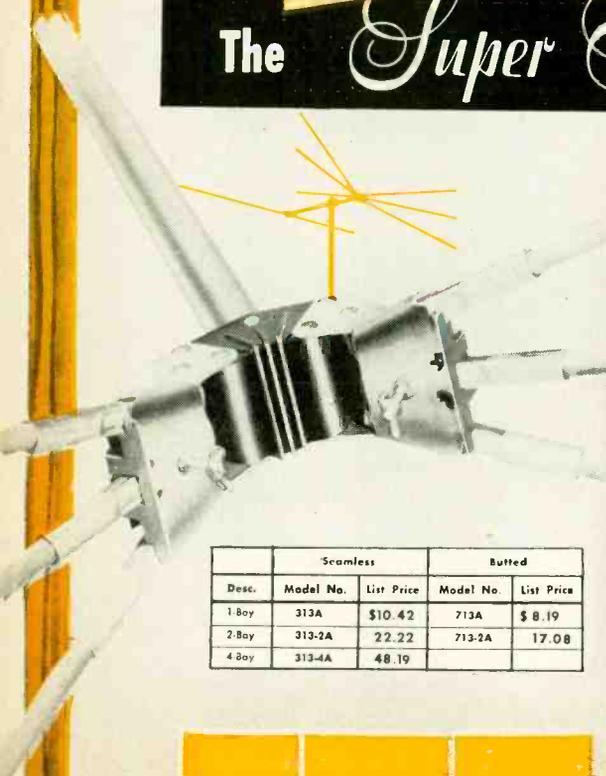

- "Super-Sembled"!
- Re-designed!
- Better than ever!

Channel Master's Super Fan is the original fan antenna. Famous for its superb quality, it has been in continuous demand for six years. Millions are in current use.

- Assembles with NO HARDWARE or tightening.
- Massive, heavy-duty, molded fan head. Unaffected by moisture and extreme temperatures.
- Reinforced elements. External sleeves prevent breakage.

	Seamless		Butted	
Desc.	Model No.	List Price	Model No.	List Price
1-Bay	313A	\$10.42	713A	\$ 8.19
2-Bay	313-2A	22.22	713-2A	17.08
4-Bay	313-4A	48.19		



**CHANNEL MASTER CORP.** ELLENVILLE, N. Y.

the world's largest manufacturer of television antennas and accessories

# CHANNEL MASTER'S

new

## TV TRANSMISSION LINE

The first TV wire to give you the benefits of

**20**

strands per conductor (20/33 pure copper).



it's got  
**FLEX-APPEAL!**



Channel Master wire — at REGULAR prices — is the finest, most flexible transmission line you have ever handled. Complete range of web thicknesses available. Colorful display packaging.

with  
**EVERYTHING**  
but the roof!

### Two outstanding lines:

(both featuring exclusive 20-strand conductor):

#### "TWIN TWENTY"

- Marked every 10 feet. Saves time, ends waste.
- Full width. Available in silver or brown.
- Pure VIRGIN polyethylene.

#### "CHALLENGER"

Fine quality transmission line at today's VERY LOWEST PRICES.

installation. From now on, guarantee customer satisfaction with a COMPLETE CHANNEL MASTER INSTALLATION — FROM TOP TO BOTTOM.

new


## STANDOUT insulators

Featuring this revolutionary new **2 in 1** screw thread design!


Eliminates the need for stocking separate machine and wood screws. Cuts your inventory investment in standoffs by more than 65%.

- Needle sharp point, made possible by finer thread. Easier to work in wood. Prevents slipping on mast.
- STANDOUT buckle has 8 machined threads.
- Convenient "Taper-Tip" strapping, available in galvanized or stainless steel.

It's a wood screw insulator

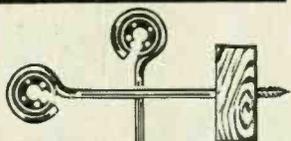

It's a machine screw insulator

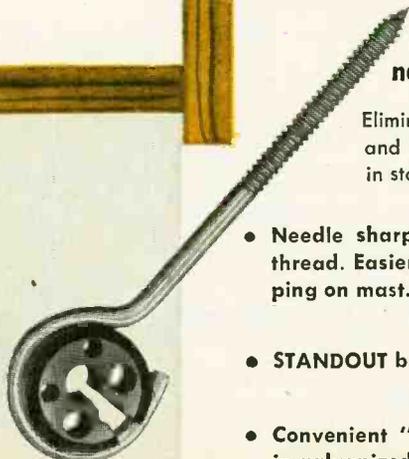

All popular types and sizes available, including full assortment of specialized hardware. See your Channel Master distributor

Copyright 1955, Channel Master Corp.



*It's your  
reputation  
that's  
in the air  
now...*

This is the test that counts —  
Your reputation is at stake.

For consistent performance,  
always select an antenna with  
'staying power' — one that pro-  
vides uniformly excellent results,  
day and night, month after  
month. And remember, the an-  
tennas with 'staying power' are  
the Taco Trapper, Super Trapper  
and Trapper Royal. Don't risk  
your reputation on less . . .




Your distributor has complete details on these fine antennas

Flat across-the-channel performance inherent in the  
Trapper design assures best results on black-and-white and color.

**TACO** TECHNICAL APPLIANCE CORPORATION  
SHERBURNE, N. Y.

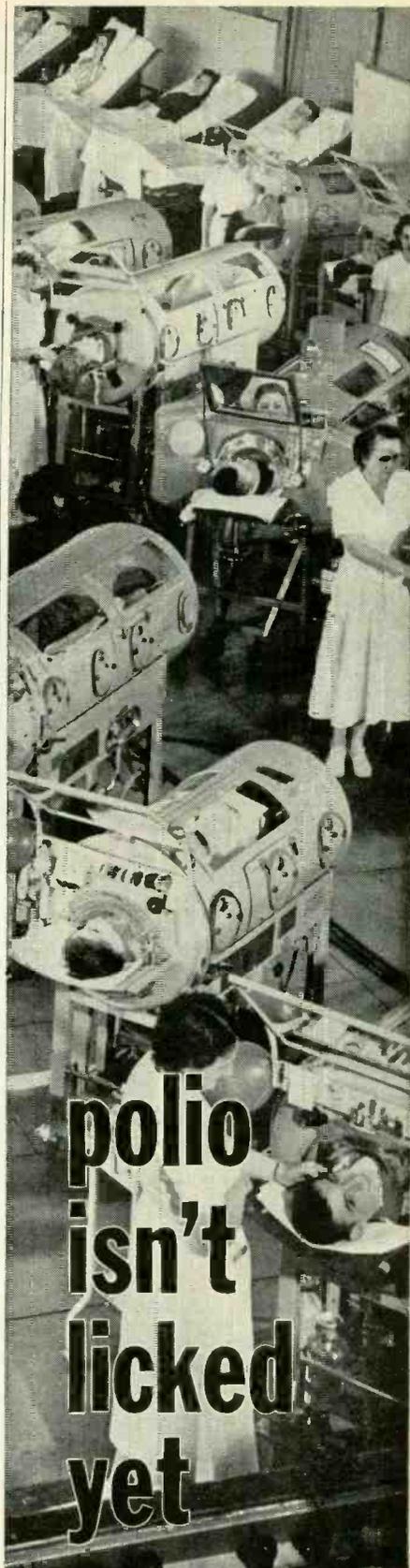In Canada: Hackbusch Electronics, Ltd., Toronto 4, Ont.



**polio  
isn't  
licked  
yet**

*Join the*  
**MARCH OF DIMES**  
*January 3 to 31*

For ALUMINIZED TUBE PERFORMANCE, *plus* EXCELLENT TUBE LIFE . . . Replace with

**RAYTHEON**



Thanks to LUMILAC, Raytheon Aluminized Picture Tubes provide sharper pictures, high light output and superior contrast — *plus excellent tube life*. LUMILAC, — a lacquer especially blended and used exclusively by Raytheon — is the secret of superiority. This amazing lacquer produces an extra smooth, unbroken surface for the pure aluminum coating, yet leaves no gas-producing residues which could impair cathode emission and shorten tube life.

What's more, the quality of Raytheon Aluminized Picture Tubes is safeguarded by Raytheon's great ultra-modern Cathode Ray Tube Plant in Quincy, Mass. — a plant designed and built solely for the manufacture of first quality picture tubes.

*Replace with Raytheon Aluminized Picture Tubes — they are best for you and your customers, too.*

## RAYTHEON "Lumilac" ALUMINIZED PICTURE TUBE REPLACEMENT GUIDE

RAYTHEON "Lumilac" ALUMINIZED PICTURE TUBE	REPLACES STANDARD TYPE	NECESSARY ADJUSTMENTS OR CHANGES	RAYTHEON "Lumilac" ALUMINIZED PICTURE TUBE	REPLACES STANDARD TYPE	NECESSARY ADJUSTMENTS OR CHANGES	
12KP4A	12KP4	None.	21AUP4A	21AUP4	None.	
	12QP4	Ground conductive coating. Remove ion trap.		21AUP4B	None.	
	12QP4A	Ground conductive coating. Remove ion trap.		21AVP4A	21AVP4	None.
	12RP4	Ground conductive coating. Remove ion trap.			21AVP4B	None.
16KP4A	16KP4	None.	21EP4B	21EP4	Ground conductive coating.	
	16QP4	Ground conductive coating. Change ion trap.		21EP4A	None.	
	16RP4	Check conductive coating contact.	21FP4C	21FP4	Ground conductive coating.	
	16TP4	Space may not be sufficient in some cases.		21FP4A	None.	
	16XP4	Ground conductive coating. Change ion trap.		21YP4A	21AFP4	Ground conductive coating.
17BP4B	17BP4	Ground conductive coating.	21YP4		None.	
	17BP4A	None.	21ZP4B	21ZP4	Ground conductive coating.	
	17BP4C	None.		21ZP4A	None.	
	17JP4	Do not exceed voltage rating.	24CP4A	24CP4	None.	
17HP4B	17HP4	None.		24QP4	None.	
	17HP4A	None.		24TP4	None.	
	17RP4	None.		24XP4	Ground conductive coating.	
17LP4A	17LP4	None.	24DP4A	24DP4	None.	
	17VP4	None.		27EP4	27GP4	None.
20DP4C	20DP4A	None.	27NP4		Add filter condenser.	
	21ALP4A	21ALP4	None.	27RP4	27GP4	Ground conductive coating.
21ALP4B		None.	27NP4		None.	
21ANP4		Ground conductive coating.				
21ANP4A		Ground conductive coating.				



### RAYTHEON MANUFACTURING COMPANY

Receiving and Cathode Ray Tube Operations

Newton, Mass. • Chicago • Atlanta, Ga. • Los Angeles, Calif.

Raytheon makes all these } Receiving and Picture Tubes, Reliable Subminiature and Miniature Tubes, Semiconductor Diodes, Power Rectifiers and Transistors, Nucleonic Tubes, Microwave Tubes



Excellence in Electronics



# HERE'S ELECTRONIC 'KNOW-HOW' - the quick, easy way!

for  
**Technicians, Industry, Experimenters,  
Students, Hobbyists, Hams...**

**"BASIC ELECTRICITY"  
"BASIC ELECTRONICS"  
"BASIC SYNCHROS  
and SERVOMECHANISMS"**

3 NEW "PICTURE BOOK"  
COURSES DERIVED FROM THE  
U. S. NAVY'S ELECTRICITY-  
ELECTRONICS TRAINING  
PROGRAM

With these remarkable picture books, the Navy teaches the basics of electricity-electronics -synchros and servomechanisms faster, easier, and more economically than ever before! Regardless of previous education, students master these vitally important subjects in record time. Now these picture book courses are available to everyone!

Each course features easy-to-understand "show-how" drawings that make up more than 50% of the entire material (a total of over 2,000 illustrations). They present and explain every topic; make everything picture clear.

Subjects are taken up in the order of need, with a complete idea on every page. Each point is discussed clearly, accurately, concisely. On that same page, at least one big "show-how" drawing illustrates and explains the topic in question. Then, review pages at the end of every section highlight the material just covered. In this thorough, step-by-step way, a solid foundation of knowledge is built, enabling the reader to grasp instantly the following portion of the course. There is no finer basic material for schools, industrial training programs or home study!

**"BASIC ELECTRICITY"**  
No. 3 Paper bound: 5 volumes, 624 pages, 6" x 9" only \$9.00 per set  
No. 4 Cloth bound: all 5 volumes in a single binding...only \$10.50  
**"BASIC ELECTRONICS"**  
No. 5 Paper bound: 5 volumes, 550 pages, 6" x 9" only \$9.00 per set  
No. 6 Cloth bound: all 5 volumes in a single binding...only \$10.50

**"BASIC SYNCHROS & SERVOMECHANISMS"**

No. 7 Paper bound: 2 volumes, 270 pages, 6" x 9"...only \$5.50  
No. 8 Cloth bound: both volumes in a single binding...only \$6.95

**COLOR TELEVISION  
RECEIVER PRACTICES**

by the Hazeltine Corporation Laboratories Staff.

World famous for their contributions in the field of electronics, the Hazeltine Corporation Laboratories Staff has prepared a thorough exposition of color television receivers, based on years of extensive research and design.

Every chapter deals with a separate portion of the receiver, and is written by a different Hazeltine Laboratories expert, a specialist in the operation of that particular section. Thus, "Color Television Receiver Practices" presents the thinking of eight leading authorities in present-day electronics. Every major aspect of color receivers is analyzed and thoroughly explained, including the latest 21" picture tube and its required circuitry.

For the convenience of the reader, each chapter contains a summary of the salient points in that chapter.

This significant book, destined to become a standard reference work on the subject, will be of tremendous value to educational institutions, technicians, engineers... to everyone who understands monochrome television, and now wants a solid grounding in color. An ideal book to use as a text on color television!

**CHAPTERS:** Introduction to Color Television... The Color TV Signal... Display Devices... Three-Gun Shadow-Mask Kinescope... Decoders... Color Synchronization in the Receiver... I-F and Video Amplification... Laboratory Apparatus... Index

No. 1 Soft Cover...only \$4.50  
No. 2 Cloth Bound...only \$6.00

**HANDBOOK OF 630-TYPE  
TV RECEIVERS**

Covers all 630-types - from the earliest to the latest! Gives the "whys" and "hows" of each section; analyzes and explains the many changes and modifications made by various manufacturers. 26 pages of troubleshooting charts - plus complete schematics of the original "630" and typical revisions. A must for everyone in servicing.

No. 15...only \$3.50

**"RADIO OPERATOR'S LICENSE  
Q & A MANUAL"**

by Milton Kaufman  
5th edition (including elements 1 through 8-1955 ed.). An indispensable reference volume that systematically lists questions and answers of past FCC exams for all classes of communications tickets - plus a simplified follow-through discussion of each answer (so necessary for complete understanding). Over 240 illustrations.

No. 16...cloth only \$6.60

**ADVANCED TV SERVICING  
TECHNIQUES**

by RETMA Teaching Staff  
A practical, step by step course developed by the Radio-Electronics-Television Manufacturer's Association, to provide uniform servicing standards throughout the nation. This course treats each major section of the receiver separately - shows how to service every part - how to pinpoint the trouble by using all types of test equipment. Adopted by schools all over America, "Advanced Television Servicing Techniques" is endorsed by leading educators, the electronics industry, and the National Better Business Bureau. There is no finer advanced TV servicing course!

No. 17 Main Text...only \$3.60  
No. 18 Lab Workbook...only 95¢

**PICTURE BOOK OF TV  
TROUBLES**

Each volume in this series covers a different part of the TV receiver! Based on troubleshooting done in the Rider lab, each shows you dozens of typical troubles, their symptoms (picture tube patterns and waveforms) and their causes. There's also a handy pull-out section in each book that shows you what the RIGHT waveforms should look like. Actually does your troubleshooting for you!

No. 9 Vol. 1: Horiz. afc-osc. ccts. ....only \$1.35  
No. 10 Vol. 2: Vert. sweep-def. ccts. ....only \$1.80  
No. 11 Vol. 3: Video i-f & amp. ccts. ....only \$1.80  
No. 12 Vol. 4: AGC ccts. ....only \$1.80

**OBTAINING & INTERPRETING  
TEST SCOPE TRACES**

A complete explanation of waveforms appearing on the 'scope screen, with over 800 waveform illustrations to show the ideal, practical, and distorted versions of the most commonly encountered 'scope traces: am & fm radio receivers, tv receivers, audio amplifiers, power supplies, test equipment. Tells and shows how to apply the 'scope!

No. 13...only \$2.40

**"FUNDAMENTALS OF  
TRANSISTORS"**

by Leonard Krugman  
A clear, easy to understand explanation of transistor characteristics and operation, by one of the pioneers in transistor development.

No. 14...only \$2.70

**RECEIVING TUBE  
SUBSTITUTION GUIDEBOOK**

Vital replacement data to help you do every servicing job faster, easier, more economically! You'll refer to these invaluable guides every day... there's no finer, more complete tube substitution information available anywhere! Every item listed in numerical order, with original and substitute socket illustrations and wiring instructions wherever needed.

No. 19-2,500 am-fm-tv tube substitutions .....only \$3.00

**FIRST SUPPLEMENT**

No. 20-750 new, completely different am-fm-tv tube substitutions .....only 99¢

**SECOND SUPPLEMENT**

No. 21-324 new, completely different am-fm-tv tube substitutions...including 134 PICTURE TUBE substitutions .....only 99¢

**ENCYCLOPEDIA ON  
CATHODE-RAY OSCILLOSCOPES  
AND THEIR USES**

(enlarged, up-to-date 1955 edition)

1,008 pages... 3,000 illustrations... half a million words that tell you everything you should know about scopes! Fully and clearly describes the oscilloscope - its construction, its capabilities, its applications in servicing, engineering, research... with thousands of time-saving, labor-saving references, waveforms, charts.

Here are just a few examples of the wealth of information this fabulous book gives you: theory of operation of the cathode-ray tube... what's inside your present scope, or the one you're planning to buy... getting your money's worth from the scope... understanding the amplifier, sweep, and synchronizing circuits used in scopes... scope applications... interpreting scope patterns... composition of complex waveforms... visual alignment of am, fm, and tv receivers... determining phase and frequency of unknown signals... and much, much, more!

The most complete, authoritative reference book on scopes ever available to schools, technicians, engineers, industry!

No. 22 Cloth bound...only \$11.50

**COMING SOON**

**"HI-FI LOUDSPEAKERS  
AND ENCLOSURES"**

by Abraham B. Cohen, Eng. Mgr., University Loudspeakers, Inc.

Every hi-fi fan's been waiting for a book like this! Answers all your questions about loudspeakers and enclosures so clearly, in such an easy-to-grasp way that everyone can understand! Includes complete construction information on all types of loudspeaker enclosures... profusely illustrated with almost 200 clear, "here's-how" photos and drawings... each one a complete story in itself.

**WATCH FOR THIS BOOK -  
IT'S COMING SOON!**



**RIDER BOOKS HELP YOU  
DO MORE,  
LEARN MORE,  
EARN MORE...**

**JOHN F. RIDER**

**PUBLISHER, INC.**

480 Canal Street, New York 13, N. Y.

**RIDER MANUALS**

The world's finest reference library on radio and TV receivers. Rider manuals provide official, factory-authorized service data on more radio and TV receivers than any other source! Famous for accuracy, these outstanding manuals have become the standard reference in all fields where the servicing and maintenance of radio and TV receivers is required. Complete information on all radios made from 1934 on... all television sets—from the very earliest models right up to the newest! There is no finer, more reliable data!

**RADIO**

Vol.	Cat.	No.	Pages	Year	Price
23	1023	1,152	51-53	15.00	
22	1022	1,529	50-51	18.00	
21	1021	1,648	49-50	21.00	
20	1020	1,776	1949	21.00	
19	1019	2,122	48-49	22.50	
18	1018	2,036	1948	22.50	
17	1017	1,648	47-48	19.80	
16	1016	768	46-47	9.90	
15	1015	2,000	42-46	22.50	
14	1014	1,376	1942	19.80	
13	1013	1,672	41-42	19.80	
12	1012	1,648	40-41	19.80	
11	1011	1,652	39-40	19.80	
10	1010	1,664	38-39	19.80	
9	1009	1,672	37-38	19.80	
8	1008	1,650	36-37	19.80	
7	1007	1,600	35-36	19.80	
6	1006	1,240	34-35	15.00	

**TV**

Vol.	Cat.	No.	Pages	Coverage	Price
16	2016	2,100	4'-55 7/8"	24.00	
15	2015	2,100	1'-55 3/8"	24.00	
14	2014	2,200	5'-54 1/2"	24.00	
13	2013	2,320	8'-53 5/8"	24.00	
12	2012	2,000	3'-53 7/8"	24.00	
11	2011	2,200	10'-52 1/2"	24.00	
10	2010	2,350	3'-52 9/8"	24.00	
9	2009	2,136	10'-51 7/8"	24.00	
8	2008	2,688	6'-51 7/8"	24.00	
7	2007	2,352	9'-50 6/8"	24.00	
6	2006	2,320	8'-50 1/8"	24.00	
5	2005	2,320	3'-50 7/8"	24.00	
4	2004	2,296	10'-49 2/8"	24.00	
3	2003	2,032	1'-49 10/8"	24.00	
2	2002	1,896	1'-48 1/8"	24.00	
1	2001	2,000	Up to 1'-48"	19.80	

Please order Manuals by Vol. number

**GENERAL**

**TV & ELECTRONICS AS A CAREER**  
An authoritative guide to a profitable career in electronics. No. 36 Cloth bound...only \$2.50


**BROADCAST OPERATOR'S HANDBOOK**  
2nd edition. A complete presentation of the practical considerations of radio broadcasting and the equipment required. No. 35 Cloth bound...only \$5.40

**SELLING YOUR TV-RADIO SERVICE**  
Advertising, window and store display for the service shop. No. 63...only \$1.00

Whether it's Radio, TV, Sound, Servicing, Test Equipment, Theory, or Beginner's Books—you're sure to find a RIDER BOOK on the subject that interests you most!

Written by experts, in clear, easy-to-understand language—profusely illustrated—every RIDER BOOK you buy is a sound investment that pays big dividends in increased know-how and greater earning capacity.

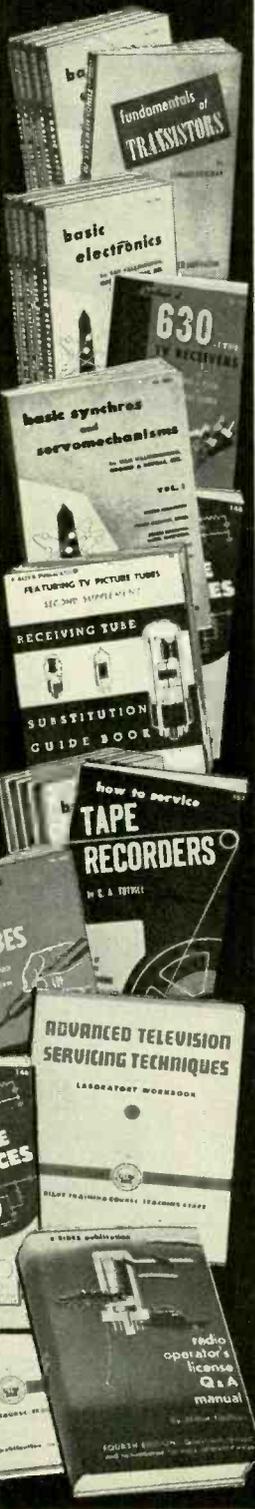Listed here are some of the valuable books we've published recently. Pick the ones you want most!



**SERVICING**

**TV REPAIR QUESTIONS & ANSWERS (front ends)**

135 specific, practical questions and their answers (including follow-through discussions where needed) on servicing TV front ends. No. 23...only \$2.10

**TV REPAIR QUESTIONS & ANSWERS (video circuits)**

135 questions and answers on servicing all types of video circuits. No. 24...only \$2.10

**TV REPAIR QUESTIONS & ANSWERS (sync & sweep circuits)**

116 questions and answers on servicing all types of sync and sweep circuits. No. 25...only \$2.10

**TV FIELD SERVICE MANUAL WITH TUBE LOCATIONS**

Tube locations plus over 30 different trouble symptoms for each model, tubes and parts to check, adjustments to make. 7 years coverage in each volume. VOL. 1: Admiral, Artone, AMC, Air King, Air Marshall, Allied Purchasing, Andrea, Arvin, Automatic. No. 26...only \$2.10  
VOL. 2: Bendix, Capehart, CBS-Columbia, Crosley, DuMont. No. 27...only \$2.40  
VOL. 3: Emerson, Fada. No. 28...only \$2.10  
Vol. 4: GE, Hallicrafters, Hoffman. No. 29...only \$2.40  
VOL. 5: Motorola, Philco. No. 30...only \$2.40  
No. 31  
COMING SOON: Vol. 6: RCA

**TV TROUBLESHOOTING AND REPAIR GUIDEBOOK**

VOLUMES 1 & 2  
How to do quick, accurate tv receiver troubleshooting and repairing. Completely practical... down-to-earth information. No. 37 Volume 1...only \$3.90  
No. 38 Volume 2...only \$3.30

**TV MANUFACTURERS' RECEIVER TROUBLE CURES**

Positive cures for tv troubles! Factory authorized data direct from receiver manufacturers. 7 volumes covering over 60 different manufacturers. No. 41...only \$1.80 per volume

**HOW TO USE METERS**

Explains everything about using meters of all types: what, when, where, and how. No. 42...only \$2.40

**TV SWEEP ALIGNMENT TECHNIQUES**

Alignment and response curve shaping techniques for front end, video, i-f systems. Accurate, time saving! No. 43...only \$2.10

**HOW TO USE SIGNAL & SWEEP GENERATORS**

A how-to-do-it book that clearly explains the use of these important testing devices. Covers every major type. No. 44...only \$2.10

**RADIO TROUBLESHOOTING GUIDEBOOK**

Explicit information about troubles and their causes in a-m and f-m radio receivers—with full troubleshooting procedures. No. 46...only \$2.40

**SERVICING TV VERTICAL & HORIZONTAL OUTPUT SYSTEMS**

Complete, easy to understand explanations of these systems; covers circuits, waveforms, components, troubleshooting. Tells the whole story! No. 47...only \$2.40

**HOW TO TROUBLESHOOT A TV RECEIVER**

A step-by-step guide for quick, easy troubleshooting. No. 48...only \$1.80

**SERVICING**

**HOW TO LOCATE & ELIMINATE RADIO & TV INTERFERENCE**

Explains the sources of interference, and what to do about them. No. 52...only \$1.80

**HOW TO INSTALL AND SERVICE AUTO RADIOS**

Practical, detailed instructions to help you do the job right. No. 53...only \$1.80

**TECHNICIAN'S GUIDE TO TV PICTURE TUBES**

Down-to-earth coverage of care handling, replacement, maintenance, and operation of picture tubes. No. 54...only \$2.40

**HOW TO USE TEST PROBES**

Clear, understandable explanation of all-types of meter and scope test probes and their uses. No. 56...only \$2.90

**HOW TO INSTALL TV ANTENNAS**

An illustrated "antenna bible" you'll refer to every time an installation job comes in. No. 62...only \$2.50

**COLOR TV INTRODUCTION TO COLOR TV**

Clear, understandable—explains everything you need to know. No. 50...only \$2.10

**HIGHLIGHTS OF COLOR TV**

A quick summary of how color tv works—for the man who already knows black and white tv. No. 51...only 99¢

**COLOR TV DICTIONARY**

Complete explanation of color tv terminology, with over 50 illustrations. No. 55...only \$1.25

**SOUND-HI-FI HIGH FIDELITY SIMPLIFIED**

How to get best sound reproduction in your own home. Covers tuners, amplifiers, loudspeakers, tape recorders, record players and changers. No. 40...only \$2.50

**GUIDE TO AUDIO REPRODUCTION**

Design, construction, assembly, testing of sound reproduction systems. Explains circuitry of pre-amps, amplifiers; also covers speakers, enclosures. No. 45...only \$3.50

**HOW TO SERVICE TAPE RECORDERS**

The complete story—including recording heads, drive mechanisms, circuits—with practical suggestions for troubleshooting. No. 59...only \$2.90

**SPECIALIZED HI-FI—AM-FM TUNER MANUAL**

Factory-accurate service data on 20 popular makes of tuners between 1950 and 1955—tells everything you need to know. No. 64...only \$3.50

**SPECIALIZED TAPE RECORDER MANUAL, VOL. 1**

Complete, factory-accurate service data on 88 different tape recorder models made between 1950 and 1954. No. 65...only \$4.50

**THEORY**

**CRYSTAL OSCILLATORS\***

Discusses all types of crystal cuts and their characteristics; Reviews all types of crystal oscillator circuits.

**FREQUENCY MODULATION\***

Reviews basic principles of f-m transmitters and receivers.

**LIMITERS & CLIPPERS\***

Reviews all basic types of diode, triode, and pentode limiter circuits, along with practical applications.

**A-M DETECTORS\***

A comprehensive review of diode, grid-leak, power, and regenerative detectors, including circuit operation and characteristics.

**FM TRANSMISSION & RECEPTION**

2nd edition. Complete f-m story—receiving and transmitting; everything from basic principles to circuits and applications. No. 32 Cloth bound...only \$4.95

**UNDERSTANDING VECTORS & PHASE**

A simple, non-mathematical approach to the relationship between sine-wave currents and voltages in electronic networks, in terms of rotating vectors. No. 33 Paper bound...only 99¢

**UNDERSTANDING MICROWAVES**

A basic study of microwaves and radar, with minimum of mathematics. No. 34 Cloth bound...only \$6.00

**UHF PRACTICES & PRINCIPLES**

A thorough explanation of UHF—including transmitting and receiving equipment. No. 39 Cloth bound...only \$6.60

**UHF TELEVISION ANTENNAS & CONVERTERS**

A simple explanation of the most commonly used UHF antennas and conversion systems. No. 49...only \$1.80

**R-C/R-L TIME CONSTANT**

Complete, understandable explanation of time constant, and how it affects circuit operation. No. 57...only 99¢

**FM LIMITERS & DETECTORS**

Reviews basic concepts of circuits as well as complete operation of these devices. No. 58...only 90¢

**BASIC VACUUM TUBES AND THEIR USES**

Simplified step-by-step explanation of all the basic tube types—and their applications. No. 60 Paper bound...\$3.00  
No. 61 Cloth bound...\$4.50

\*Watch for these books—coming soon



**RIDER BOOKS HELP YOU!**

ORDER TODAY! Look for this Rider Book Seller at your electronic parts jobber or book store. If your dealer doesn't have them, mail this coupon for prompt delivery. Add state and city sales tax where applicable. In Canada, prices approximately 5% more.

1	2	3	4	5	6	7	8	9	10	11	12	13
14	15	16	17	18	19	20	21	22	23	24	25	26
27	28	29	30	31	32	33	34	35	36	37	38	39
40	41	42	43	44	45	46	47	48	49	50	51	52
53	54	55	56	57	58	59	60	61	62	63	64	65





JOHN F. RIDER PUBLISHER, INC.  
Dept. RN-12, 480 Canal Street, New York 13, N. Y.  
Enclosed is \$\_\_\_\_\_ Please rush the books checked here:

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City and State \_\_\_\_\_

## FIELD REPORT NO. 8
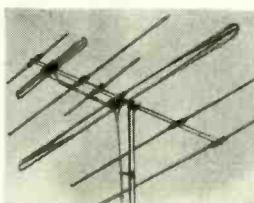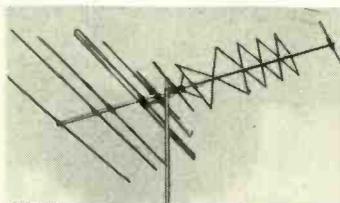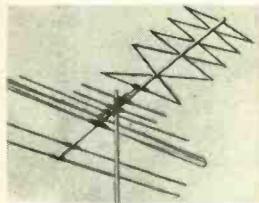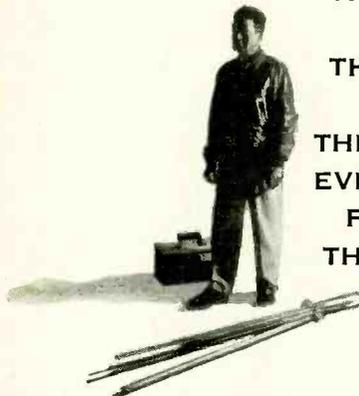
# The voice of the serviceman is the voice of Experience . . .

... AND THESE DEALERS ARE SPEAKING FROM PERSONAL EXPERIENCE. THEY REPRESENT THOUSANDS OF ENTHUSIASTIC SERVICEMEN THROUGHOUT THE COUNTRY. THESE MEN MUST PROVIDE THEIR CUSTOMERS WITH STEADY, SHARP RECEPTION ON EVERY CHANNEL RECEIVED IN THEIR AREA. THEIR REPUTATIONS DEPEND ON THE QUALITY OF THEIR ANTENNA INSTALLATIONS. SO THEY RUN THEIR OWN FIELD TESTS. AND THEY'RE MORE THAN SATISFIED. THEY KNOW THAT THERE'S A JFD ANTENNA FOR EVERY PROBLEM, FOR EVERY PURSE. THEY'VE SEEN FOR THEMSELVES. YOU CAN, TOO.



### STAR-HELIX

**SX711** single \$25.50  
**SX711S** stacked \$52.50  
**SX711S-96\*** \$55.00  
 96" stacked

\*for added ch. 2-6 gain

†for areas with co-channel and cross-channel interference

### SUPER-STAR HELIX

**SX13** single \$35.00  
**SX13S** stacked \$72.50

### FIREBALL

**FB500** single \$17.35  
**FB500S** stacked \$36.65  
**FB500S-68†** \$36.65  
 68" wide stacked  
**FB500S-96\*** \$38.60  
 96" wide stacked

*YOUR REPUTATION GOES UP  
WITH A JFD ANTENNA!*



**MANUFACTURING CO. INC.**  
**BROOKLYN 4, N. Y.**

INTERNATIONAL DIVISION, 15 MOORE ST., N. Y., U. S. A.

**GO FORWARD WITH JFD ENGINEERING!**



CARL KOWA  
KOWA ELECTRIC  
OLNEY, ILLINOIS

WE HAVE USED JFD ANTENNAS FOR SEVERAL YEARS AND HAVE FOUND THEM SUPERIOR TO ALL OTHERS THAT WE HAVE TESTED. WE WERE THE FIRST TO USE JET213 AND WHEN SX711 WAS RELEASED WE STARTED USING IT. TO DATE WE HAVEN'T HAD A SINGLE COMPLAINT AND HAVE INSTALLED APPROXIMATELY TWO OR THREE HUNDRED.



FRANK A. MARZANO  
MARS APPLIANCE CO.  
HARTFORD, CONNECTICUT

I AM CONVINCED THAT THE STAR-HELIX ANTENNA IS THE HIGHEST GAIN ANTENNA ON THE V. H. F. CHANNELS I HAVE EVER USED IN ALL MY EIGHT YEARS IN THE BUSINESS. CUSTOMERS ARE ENTHUSIASTIC ABOUT RECEPTION FROM NEW YORK, OVER ONE HUNDRED MILES AWAY.



FRED LOREMAN  
LOREMAN SERVICE  
BARSTOW, CALIFORNIA

WE ARE IN AN EXTREME FRINGE AREA. WE HAVE RECENTLY PURCHASED YOUR NEW STAR-HELIX ANTENNA FROM ELECTRONIC SUPPLY CORP., RIVERSIDE, CALIF. WE ARE QUITE HAPPY WITH THEIR PERFORMANCE AND ALSO THEIR CONSTRUCTION.



AL ADAMS  
HOLMES REFR. ELECT. SERVICE  
MYRTLE BEACH, SOUTH CAROLINA

WE USE AND RECOMMEND THE JFD STAR-HELIX ANTENNA IN THIS AREA AS IT NOT ONLY GIVES THE BEST PERFORMANCE POSSIBLE FROM OUR DISTANT STATIONS BUT WILL WITHSTAND EXTREME WEATHER CONDITIONS AND EFFECTS OF SALT SPRAY.



WILLIAM F. PETERSON  
WANK'S FURN. & APPLIANCE MART  
SOUTH HAVEN, MICHIGAN

WE LIKE THE JFD STAR-HELIX ANTENNA BECAUSE OF ITS EXCELLENT FRONT-TO-BACK RATIO. CO-CHANNEL INTERFERENCE IS LESS THAN WITH ANY OTHER ANTENNA WE HAVE TRIED. WE RECEIVE STATIONS FROM FOUR DIRECTIONS AND WE CONSISTENTLY BRING IN THE FIVE (5) CHICAGO STATIONS WHICH ARE OVER 75 AIR-MILES DISTANT. WE ALSO USE THIS ANTENNA WITH OUR COLOR RECEIVER FOR DEMONSTRATION.



H. H. FIGFORD  
BURGAW RADIO & T.V. SERVICE  
BURGAW, NORTH CAROLINA

I HAVE TRIED MANY DIFFERENT ANTENNAS BUT I FIND THAT THE JFD STAR-HELIX GIVES BEST PERFORMANCE IN A FRINGE AREA OVER ALL THE REST OF THE ANTENNAS I HAVE TRIED.

# I Will Train You at Home

## For Good Pay Jobs, Success in

# RADIO-TELEVISION



**J. E. SMITH**  
President  
National Radio  
Institute  
Washington, D. C.  
40 years of success  
training men at  
home in spare time.



I'll Prove It Is Easy And Practical To Learn At Home. Sample Lesson FREE.





To See Equipment I Send You For Practical Experience... Get Illustrated Book FREE.

### Practice Broadcasting with Equipment I Send

It's practical to train at home for good Radio-TV jobs and a brighter future. As part of my Communications Course I send you kits of parts to build the low-power Broadcasting Transmitter shown at the left. You use it to get practical experience performing procedures demanded of Broadcasting Station Operators. An FCC Commercial Operator's License can be your ticket to a better job and a bright future; my Communications Course gives you the training you need to get your license. Mail card below and see in my book other valuable equipment you build. Get FREE sample lesson.
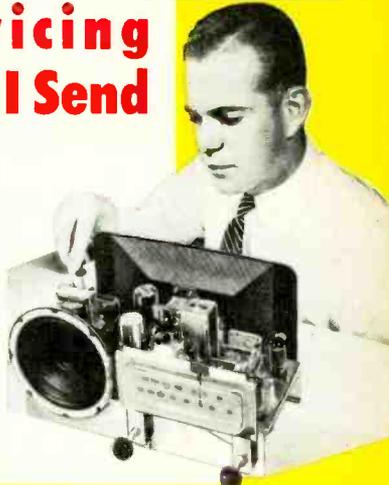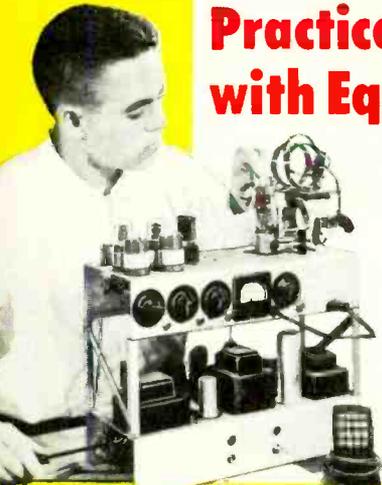
### Practice Servicing with Equipment I Send

Self-confidence, security, earning power come from knowing-how and from experience. Nothing takes the place of PRACTICAL EXPERIENCE. That's why NRI training is based on LEARNING BY DOING. You use parts I furnish to build many circuits common to Radio and Television. With my Servicing Course you build a modern Radio (shown at right). You build a Multitester, use it in conducting experiments, fixing sets in spare time starting a few months after enrolling. All equipment is yours to keep. Card below will bring book showing other equipment you build. Judge for yourself whether you can learn at home in your spare time.



### Television Is Growing Fast Making New Jobs, Prosperity

More than 30 million homes now have Television sets and thousands more are being sold every week. Well trained men are needed to make, install, service TV sets and to operate hundreds of Television stations. Think of the good job opportunities here for qualified technicians, operators, etc. If you're looking for opportunity, get started now learning Radio-Television at home in spare time. Cut out and mail postage-free card. J. E. Smith, President, National Radio Institute, Washington, D. C. Over 40 years' experience training men at home.

AVAILABLE TO  
**VETERANS**  
UNDER G.I. BILL

Good Jobs  
Good Pay **See Other Side**

Get My **SAMPLE LESSON** and  
**64-Page Illustrated Book**  
**BOTH FREE**

Cut out and mail card NOW!

This card entitles you to Actual Lesson on Servicing, shows how you learn Radio-Television at home. You'll also receive my 64-page Book, "How to Be a Success in Radio-Television." Mail card now!

**NO STAMP NEEDED! WE PAY POSTAGE**

**Mr. J. E. SMITH, President**  
National Radio Institute, Washington 9, D. C.

Mail me Lesson and Book, "How to Be a Success in Radio-Television." (No Salesman will call. Please write plainly.)


NAME.....AGE.....

ADDRESS.....

CITY.....ZONE.....STATE.....

**VETS** write in date of discharge.....

K L

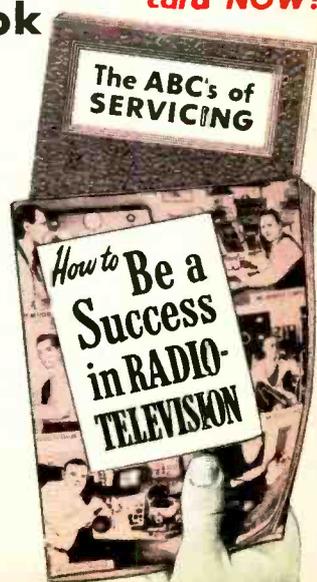

# Train at Home to Jump Your Pay as a RADIO-TV Technician



J. E. Smith, President

National Radio Institute

The men whose messages are published below were not born successful. Not so long ago they were doing exactly as you are now... reading my ad! They decided they should KNOW MORE... so they could EARN MORE... so they acted! Mail card below now.

## Get a Better Job—Be Ready for a Brighter Future in America's Fast Growing Industry

Training PLUS opportunity is the PERFECT COMBINATION for job security, good pay, advancement. When times are good, the trained man makes the BETTER PAY, GETS PROMOTED. When jobs are scarce, the trained man enjoys GREATER SECURITY. NRI training can help assure more of the better things of life.

Radio-Television is today's opportunity field. Even without Television, Radio is bigger than ever before. Over 3,000 Radio Broadcasting Stations on the air; more than 115 million home and Automobile Radios are in use. Television Broadcast Stations extend from coast to coast now with over 30 million Television sets already in use. Over 400 Television stations are on the air and there are channels for hundreds more.

Use of Aviation and Police Radio, Micro-Wave Relay, Two-way Radio communication for buses, taxis, trucks, etc., is expanding. New uses for Radio-Television principles coming in Industry, Government, Communications and Homes.

### My Training Is Up-to-Date You Learn by Doing

Get the benefit of our 40 years' experience training men. My well-illustrated lessons give you the basic principles you must have to assure continued success. Skillfully developed kits of parts I furnish "bring to life" the principles you learn from my lessons. Read more about equipment you get on other side of this page.

More and more Television information is being added to my courses. The equipment I furnish students gives experience on circuits common to BOTH Radio and Television.

### Find Out About this Tested Way to Better Pay

Read at the right how fellows who acted to get the better things of life are making out now. Read how NRI students earn \$10, \$15 a week extra fixing Radios in spare time starting soon after enrolling. Read how my graduates start their own businesses. Then take the next step—mail card below.

You take absolutely no risk. I even pay postage. I want to put an Actual Lesson in your hands to prove NRI home training is practical, thorough. I want you to see my 64-page book, "How to Be a Success in Radio-Television," because it tells you about my 40 years of training men and important facts about present and future Radio-Television job opportunities. You can take NRI training for as little as \$5 a month. Many graduates make more than the total cost of my training in two weeks. Mailing postage-free card can be an important step in becoming successful. J. E. Smith, President, National Radio Institute, Washington 9, D. C. Training Men for Over 40 years. Approved Member, National Home Study Council.

## I TRAINED THESE MEN



### Lots of Spare-Time Jobs

"I do a lot of spare-time Radio and TV servicing. It was fun learning and I don't know how to thank you." B. Goede, Plainview, Minn.



### Now TV Trouble Shooter

"I had only gone to 7th grade when I started course. Now have job as TV troubleshooter, also fix sets spare time." M. R. Lindemuth, Fort Wayne, Ind.



### Engineer with WHPE

"Thanks to NRI, I operated a successful Radio repair store. Then I got a job with WPAQ and now am an engineer for WHPE." V. W. Workman, High Point, N. C.



### NRI Course Can't Be Beat

"Am with WCOG. NRI Course can't be beat. No trouble passing 1st class Radio-Phone license examination." Jesse W. Parker, Meridian, Mississippi.



### Quit Job for Own Business

"I decided to quit my job and do TV work full time. I love my work and am doing all right financially." William F. Kilne, Cincinnati, Ohio.



### Extra Money in Spare Time

"I am a police captain and also have good spare-time service business. Just opened my new showrooms and shop." C. W. Lewis, Pensacola, Fla.

## Start Soon to Make \$10 to \$15 a Week Extra Fixing Sets



Keep your job while training. Many NRI students make \$10, \$15 and more a week extra fixing neighbors' Radios in spare time, starting a few months after enrolling. The day you enroll I start sending you special booklets that show you how to fix sets. The multimeter you build with parts I furnish helps discover and correct troubles.

## SEE OTHER SIDE

FIRST CLASS

Permit No. 20-R

(Sec. 34.9, P. L. & R.)

Washington, D. C.

BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed In The United States

POSTAGE WILL BE PAID BY

NATIONAL RADIO INSTITUTE

16th and U Sts., N. W.

Washington 9, D. C.

**SAMPLE LESSON**  
and 64-Page BOOK  
**BOTH FREE**  
CUT OUT AND MAIL  
POSTAGE-FREE CARD

## Have Your Own Business

Many NRI trained men start their own successful Radio-Television sales and service business with capital earned in spare time. Joe Travers, a graduate of mine, in Asbury Park, N. J., writes: "I've come a long way in Radio and Television since graduating. Have my own business on Main Street."




*New!  
Revolutionary!*



- ★ The GENERAL has a closely spaced screen (7 inches) to minimize pick up off the rear. With more and more stations coming on the air, on the same channel, this is a major problem of today and tomorrow.
- ★ The GENERAL is completely pre-assembled. By simply tightening three wing nuts, the antenna is ready to mount.
- ★ The GENERAL is light in weight with low wind resistance. Not only easy to put up, but easy to KEEP up.
- ★ The GENERAL is packed in a small carton. This makes the antenna more economical to ship, store, and handle.
- ★ The GENERAL sells for less than comparable products. This gives YOU a better mark up and faster moving merchandise.

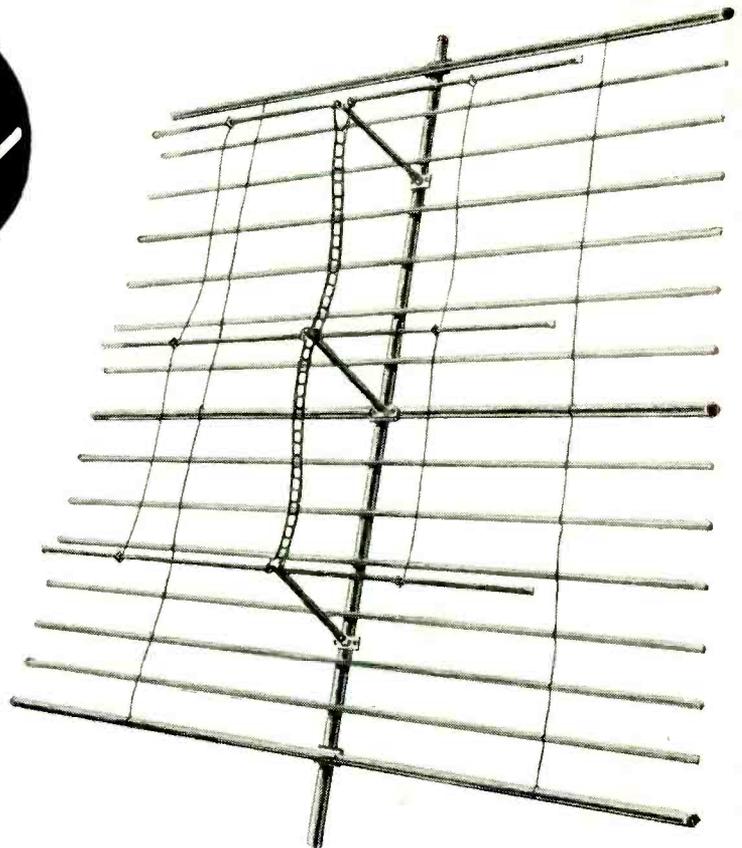**Some Exclusive Territories Available  
To Aggressive Jobbers.**




★ The GENERAL is low enough in price to use in the most competitive market and is recommended for all locations.


The GENERAL combines 6 dipoles in a phased collinear array for super gain on channels 7 to 13 and features an interpolated dipole arrangement on channels 2 through 6 for a small physical size, high gain array on these channels. The GENERAL has peak gains of over 15 D.B. and is recommended for use in the most difficult reception areas.

LIST PRICE 24.95

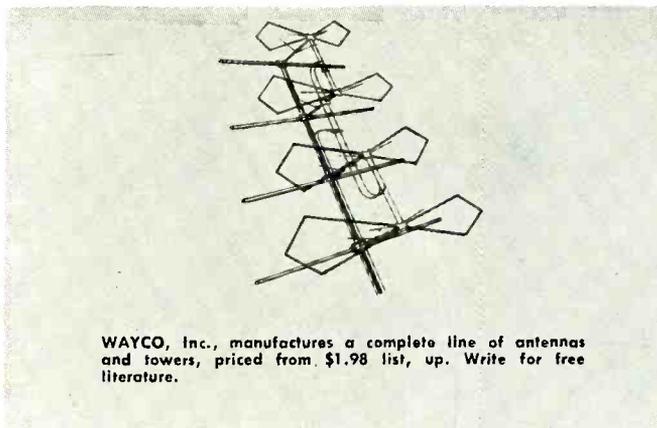**World's Finest TV Antennas and Towers**



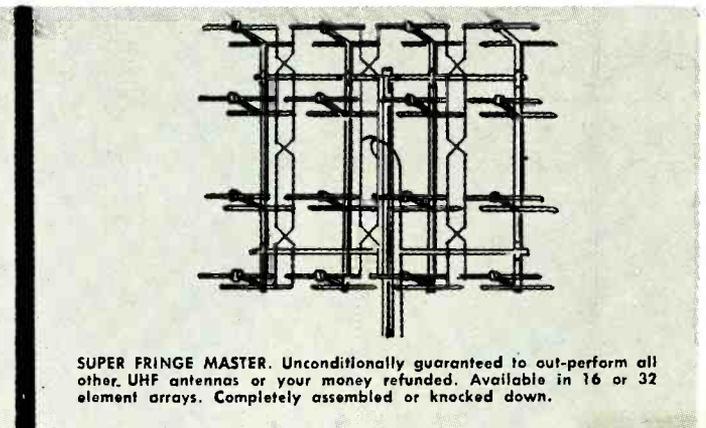WAYCO, Inc., manufactures a complete line of antennas and towers, priced from \$1.98 list, up. Write for free literature.



SUPER FRINGE MASTER. Unconditionally guaranteed to out-perform all other UHF antennas or your money refunded. Available in 16 or 32 element arrays. Completely assembled or knocked down.

P. O. Box 115  
Phone 7-2981

**WAYCO, Inc.**

WAYNESBORO  
TENNESSEE



# Silver Vision

## THE ALUMINIZED TUBE THAT IS PRE-SOLD

Sure, *you* are already sold on the advantages of aluminized tubes. You know that the CBS Silver Vision aluminized screen with its silver-activated phosphors and the CBS small-spot gun mean clearer, sharper, brighter pictures.

But your woman customer (76.9% of TV service customers are women) doesn't understand electronics or CBS advanced-engineering as you do.

She does know and respect the name CBS . . . she has confidence in Garry Moore and in the Good Housekeeping Guaranty Seal.

So all you have to do is take advantage of Garry's pre-selling over the CBS Television Network. Just remind her that there are no finer tubes made than CBS Silver Vision tubes . . .

And, like all CBS tubes, they have the Good Housekeeping Guaranty Seal. She's already pre-sold by Garry Moore and national magazine advertising. You build profitable customer confidence and sales every time you recommend CBS Silver Vision tubes.



Garry Moore  
famous CBS  
Television Star




Show the CBS carton with the Good Housekeeping Guaranty Seal

**CBS-HYTRON**  
Danvers, Massachusetts  
A DIVISION OF  
COLUMBIA BROADCASTING SYSTEM, INC.  
RADIO-ELECTRONICS

I chose **COYNE TELEVISION**

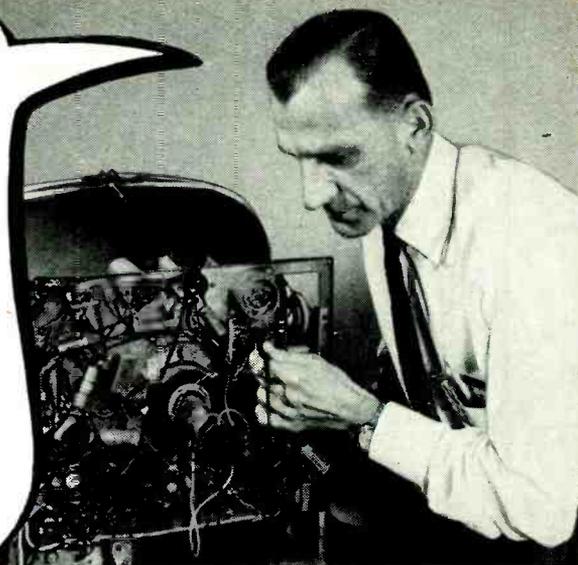**RADIO-ELECTRONICS** home training because they have been preparing men quickly for good jobs for over 56 years



Giant opportunity field! Join the thousands Coyne Home Training is preparing for success in TV—open the door to big-pay jobs, or your own business! Coyne is the oldest, largest, best-known school of its kind—established 1899.

Experts call this the finest home training


ever developed—to standards that have made Coyne famous. As result of Coyne's greater background, you learn TV servicing **faster, easier, learn it right!** No previous experience or advanced education necessary. **Coyne training includes UHF and COLOR TV.**

I chose **COYNE** because their new method costs less than half what most others do!



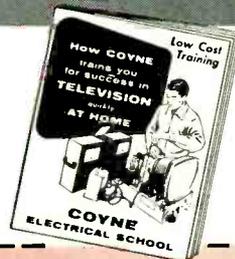**SEND COUPON FOR FREE BOOK**

Send coupon below for all-new fully-illustrated book and full details including **EASY PAYMENT PLAN. NO COST OR OBLIGATION—NO SALESMAN WILL CALL**



Modern, up-to-the-minute. Easy to follow, step-by-step instructions—fully illustrated with 2150 photos and diagrams. So practical you can quickly earn extra money in TV-Radio Sales and Service. Not only the finest training, but costs *half* what you'd expect to pay because you **pay only for training—no costly extras.** Free life-time employment service.

**B. W. COOKE**  
President

**COYNE** Founded 1899  
**ELECTRICAL SCHOOL**


A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT  
500 S. Paulina, Dept. 16-HT4, Chicago 12, Illinois

**B. W. COOKE, President**  
**COYNE ELECTRICAL SCHOOL**  
500 S. Paulina St., Chicago 12, Ill.  
Dept. 16-HT4

Send **FREE** Book and details of your Television-Radio-Electronics Home Training offer.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

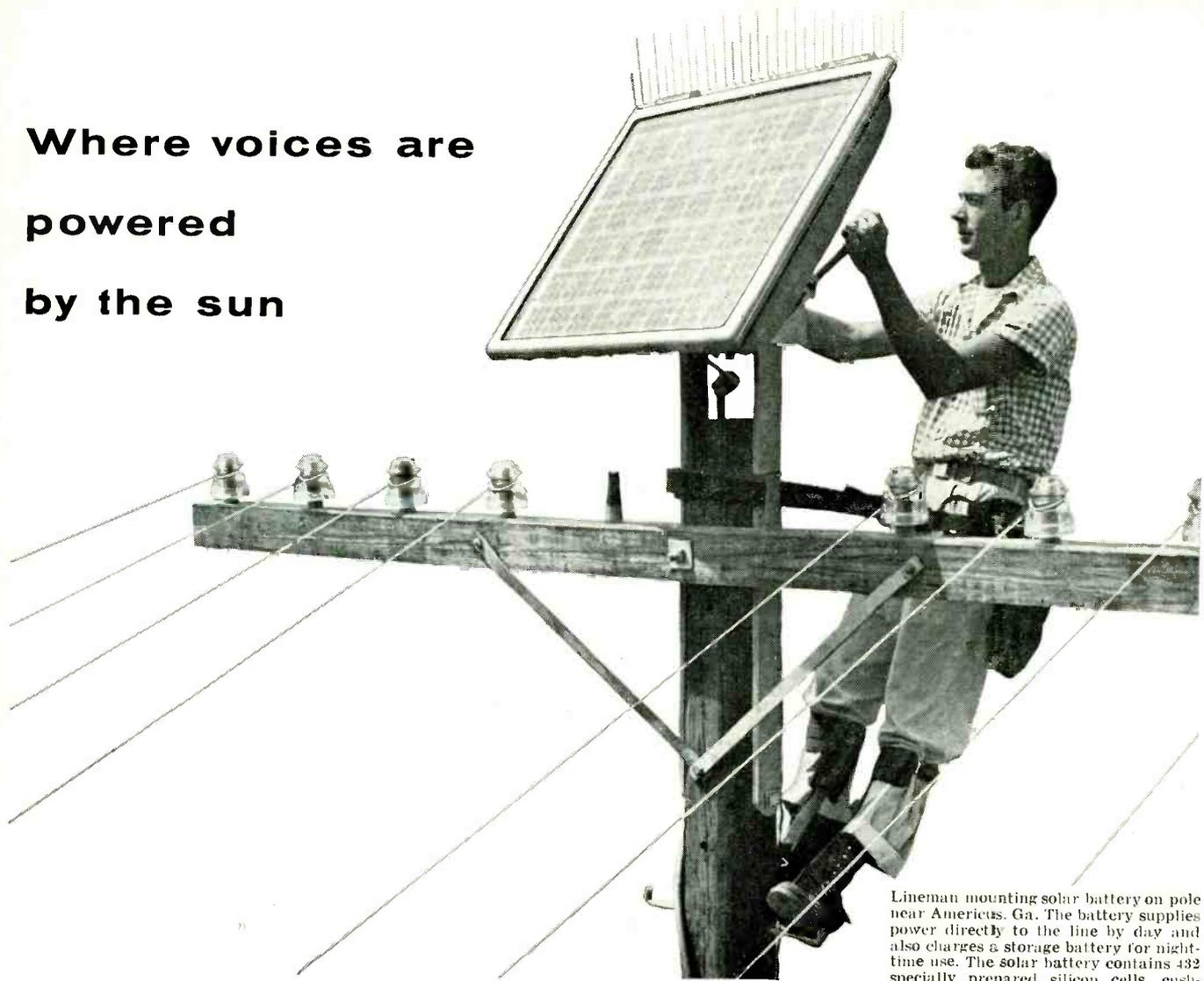**Where voices are  
powered  
by the sun**




Lineman mounting solar battery on pole near Americus, Ga. The battery supplies power directly to the line by day and also charges a storage battery for nighttime use. The solar battery contains 432 specially prepared silicon cells, cushioned in oil and covered by glass.

A new kind of telephone system developed by Bell Telephone Laboratories for rural areas is being operated experimentally by electric current derived from sunlight. Electric current is generated as sunlight falls on the Bell Solar Battery, which a lineman is seen adjusting in position.


The exciting achievement is made possible by two Laboratories inventions—the solar battery and the transistor. The new system uses transistors to the complete exclusion of electron tubes.

Transistors require little power and this power can be easily supplied by the solar battery.

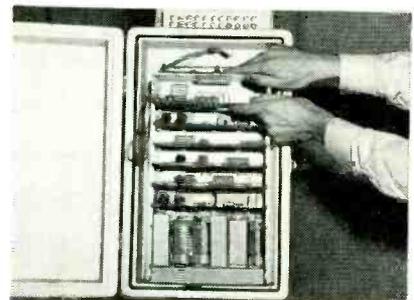Compact and economical, the transistorized system can carry several voices simultaneously without interference. It has proved its ruggedness by standing up to heat, cold, rain and lightning. It promises more and improved telephone service for rural areas and it typifies the Laboratories' continuing efforts to make American telephony still better each year.



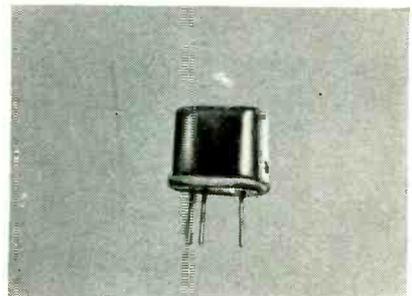In sending and receiving terminals, transistors are used as oscillators, amplifiers and regulators, and for signaling.



One of the transistors (actual size) used in the new system. New ideas, new tools, new equipment and new methods had to be developed for this project.

**BELL TELEPHONE LABORATORIES**

IMPROVING AMERICA'S TELEPHONE SERVICE PROVIDES CAREERS  
FOR CREATIVE MEN IN SCIENTIFIC AND TECHNICAL FIELDS



everyone's

# Looking for



## "STAMINIZED"\* CAPACITORS!

\*"Staminized" is Astron's name for the special, extra-rugged construction of *all* their capacitors . . . it's why smart service technicians are installing more and more fabulous Astron Blue • Point® molded plastic paper tubulars . . . their unsurpassed reliability builds consumer satisfaction and repeat business. Install dependable Blue • Points with absolute confidence, their exclusive bonded shell and seal form an impenetrable shield against heat and moisture damage.

You'll find Blue • Points are being used by leading set manufacturers because . . . a new solid thermosetting impregnant insures high capacitance stability over the entire operating range of -40°C to +85°C . . . continuous 85°C operation *without derating*.

Each Astron Blue • Point is clearly marked for fast identification . . . individually tested and guaranteed to prevent call-backs!

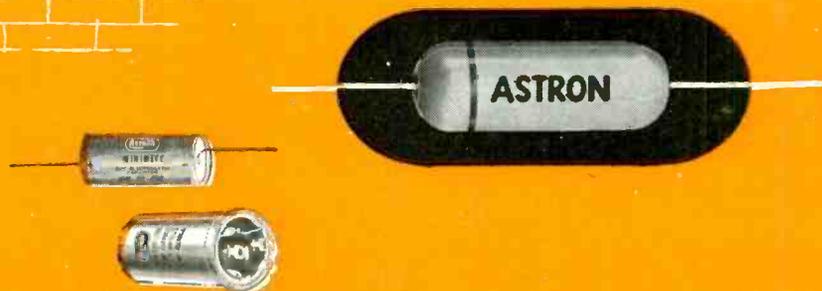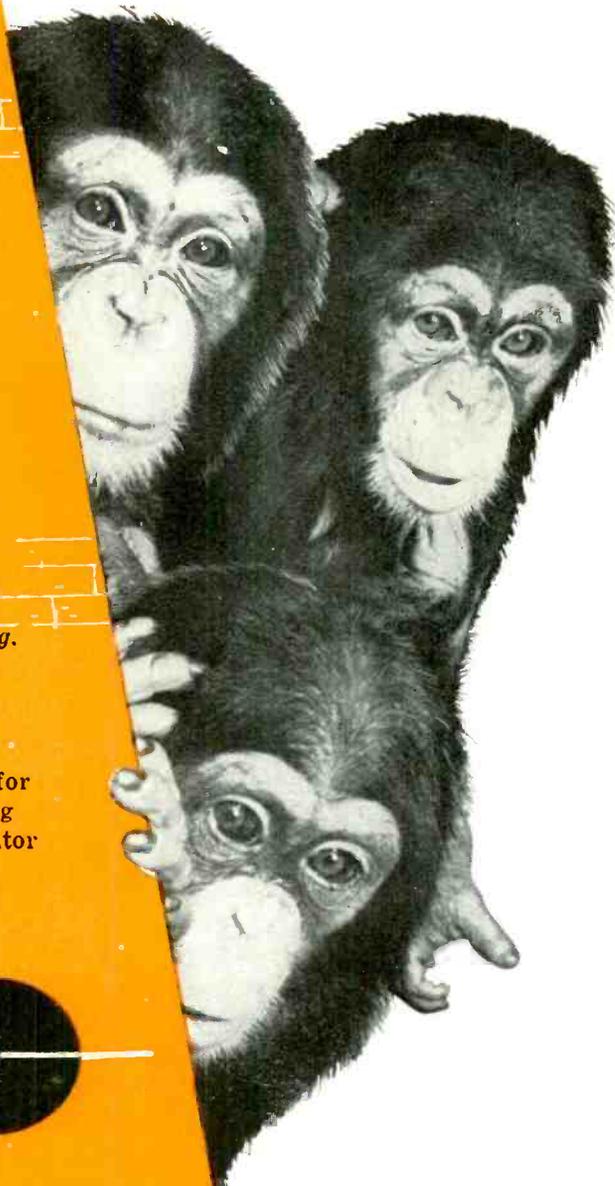There's a dependable Astron replacement capacitor for superior performance in *every* radio and TV servicing requirement . . . send for Astron Replacement Capacitor Catalog AC-4D today!



# ASTRON

C O R P O R A T I O N

255 GRANT AVENUE, E. NEWARK, N. J.



Export Division: Rocke International Corp., 13 East 40th St., N. Y., N. Y. In Canada: Charles W. Poitron, 5 A. King Ave., Toronto 10, Ontario

**Do you OVERPAY  
for QUALITY  
instruments?**

EICO's mass purchasing and world-wide distribution, together with advanced electronic design, produce values never before possible . . . to give you **Laboratory Precision at Lowest Cost!**

**GET the MOST for YOUR MONEY!** Don't buy ANY test instrument till you put the **EICO INSTRUMENT** (kit or wired) equivalent before you—and . . .

Compare advanced electronic design: see the latest in circuitry and features.

Compare finest components: see the famous brands you know and trust, such as GE, Centralab, Mallory, etc.

Notice ease of construction and operation: Exclusive "Beginner-Tested" Manuals make assembly and operation step-by-step, quick, crystal-clear. "You build them in one evening—they last a lifetime!"

Check **5-Way Guarantee**: Only EICO gives you this exclusive complete protection! EICO guarantees components, instructions and satisfactory operation — AND guarantees service and calibration for the **LIFETIME** of the instrument, at less than cost of handling.

Compare feature for feature, dollar for dollar.

There's an EICO distributor right nearby in your own neighborhood — over 1200 coast-to-coast. EICO planned it that way so that you can easily examine EICO **BEFORE YOU PUT DOWN ONE CENT OF YOUR MONEY!**

**COMPARE** any of EICO's 46 models **SIDE BY SIDE** with ANY competitor. Then YOU judge who's giving you the **MOST** for your money.

Over 500,000 EICO instruments in use . . . You'll agree EICO gives you **LABORATORY PRECISION AT LOWEST COST.**



## FREE 1956 EICO CATALOG!

Tells you how to **SAVE 50%** on your test equipment costs!

### NEW RF SIGNAL GENERATOR #324



**KIT \$26.95**  
**Wired \$39.95**

Ill. dial

150 kc-435 mc; 6 fund. bands.



**NEW WIDE BAND DC-5MC 5" OSCILLOSCOPE #460**

**KIT \$79.95**  
**Wired \$129.50**

Designed for color TV servicing & laboratory use. DC vert. amplifier, flat DC-4.5 mc.



**5" PUSH-PULL OSCILLOSCOPE #425**  
**KIT \$44.95**  
**Wired \$79.95**

**7" PUSH-PULL OSCILLOSCOPE #470**  
**KIT \$79.95**  
**Wired \$129.50**



**VACUUM TUBE VOLTMETER #221**

**KIT \$25.95**  
**Wired \$39.95**

**DELUXE VTVM #214 (7 1/2" METER)**  
**KIT \$34.95**  
**Wired \$54.95**



**#232 Peak-to-Peak VTVM with AC/DC UNI-PROBE (pat. pend.)**

**KIT \$29.95**  
**Wired \$49.95**

**Deluxe #249 with 7 1/2" Meter**  
**KIT \$39.95**  
**Wired \$59.95**



**TUBE TESTER #625**

**KIT \$34.95**  
**Wired \$49.95**

• tests 600 mil series string type tubes  
illuminated roll-chart


Pix Tube Test Adapter .....\$4.50



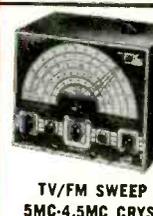**#944 FLYBACK TRANSFORMER & YOKE TESTER**

**KIT \$23.95**  
**Wired \$34.95**

• fast check all flybacks & yokes in or out of set.  
• spots even 1 shorted turn!



**TV/FM SWEEP GENERATOR #360**  
**5MC-4.5MC CRYSTAL .....\$3.95 ea.**

Range 500 kc-228 mc on fund. Cont. sweep width control, 0-30 mc.

**KIT \$34.95**  
**Wired \$49.95**



**DELUXE RF SIGNAL GENERATOR #315**

1% accuracy on all 7 ranges. Range 75 kc-150 mc. Volt reg.

**KIT \$39.95**  
**Wired \$59.95**



Sep. volt-meter & ammeter

**KIT \$29.95**  
**Wired \$38.95**

**6V & 12V BATTERY ELIMINATOR & CHARGER #1050**



**DELUXE MULTI-SIGNAL TRACER #147**

Sep. hi-gain RF & lo-gain audio inputs. Special noise locator. Calibrated wattmeter.

**KIT \$24.95**  
**Wired \$39.95**



**R-C BRIDGE & R-C-L COMPARATOR #950B**

Reads 0.5 ohms -500 megs, 10 mmfd-5000 mfd power factor.

**KIT \$19.95**  
**Wired \$29.95**



**NEW! High Fidelity Amplifier #20**  
**KIT \$49.95**  
**Wired \$79.95**

20-20,000 cps  $\pm$  0.5db IM distortion 1.3%. Harmonic distortion 0.3%. All at 20 watts. Ultra Linear Williamson, 5 pos. equal., tone & loudness controls.



**20,000 Ohms/Volt MULTIMETER #565**  
**KIT \$24.95**  
**Wired \$29.95**



**1000 Ohms/Volt MULTIMETER #536**  
**KIT \$12.90**  
**Wired \$14.90**



**VTVM PROBES**

Peak-to-Peak	<b>KIT \$4.95</b>	<b>Wired \$6.95</b>
RF	<b>\$3.75</b>	<b>\$4.95</b>
High Voltage Probe-1		<b>\$6.95</b>
High Voltage Probe-2		<b>\$4.95</b>

**SCOPE PROBES**

Demodulator	<b>\$3.75</b>	<b>\$5.75</b>
Direct	<b>\$2.75</b>	<b>\$3.95</b>
Low Capacity	<b>\$3.75</b>	<b>\$5.75</b>

For FREE 1956 catalog, mail coupon NOW!



84 Withers St. • Brooklyn 11, N. Y.

Prices 5% higher on West coast and subject to change without notice. ©55

EICO, 84 Withers Street  
Brooklyn 11, New York

C-1

Send FREE 1956 Catalog and name of neighborhood EICO jobber.

Name.....

Home Address.....

City.....Zone.....State.....

Occupation.....

1945 to 1955: a decade of Know-How & Value Leadership in Kits & Instruments—over 1/2 million sold to date!

## THE FUTURE OF COLOR TV

*... A glimpse and forecast of coming multichrome TV ...*

**C**OLOR television has been with us for a number of years, most of them spent in the developmental stage. It has been an extraordinarily difficult and brilliantly conducted engineering and research undertaking on which tens of millions of dollars have been expended by the industry—the lion's share certainly by RCA. 1956 seems to be slated as the first year when color receivers will be manufactured in appreciable quantities.

If no large quantities of color receivers have been manufactured up to now, the reasons are simple to find: 1. The great complexity of the sets and particularly of the color picture tube. 2. The relatively high cost of the receiver compared to black-and-white sets. 3. The scarcity of color programs on the air.

The latter reason is now being rapidly remedied. In late 1955 we already had a number of daily network programs, whereas up to October, 1955, we had only a few programs a week and no day programs.

As of Nov. 1, 1955, there was an average of 11¼ hours of color network studio programs per week by NBC and CBS. Of this total NBC accounted for about 10 hours per week, CBS 1¼ hours. Outdoor sports events in color are not included in these figures.

It would seem elementary that even the well-to-do would not rush to buy color sets that would have to stand idle 90% of the week as was the case in early 1955. True, while color receivers are compatible and receive black-and-white programs—or, to be accurate, bluish-black-and-white—an overwhelming percentage of TV color set owners already have black-and-white sets. Hence the color demand is not so acute as it would be if there were no TV receivers. This condition will probably continue for a while until more people become better acquainted with color. It is a truism that, once you have watched a color television program for several hours, your black-and-white screen appears drab and takes on qualities of an old Ford Model T.

The evolution of color receivers will parallel that of black-and-white ones in many respects. 1956 will probably not be a year of multimillion set sales. Up to now only RCA has made color sets in any sizable quantities. Much of the industry has sat on the sidelines content to let the pioneer take the hot chestnuts from the fire. The exceptions were Westinghouse, Motorola, Raytheon and CBS.

This situation is certain, however, to change drastically, probably before the end of 1956. It has never been the habit of the electronic industry to stay out of a good thing once it has become convinced that good opportunities are in the offing. Already one small manufacturer has announced his intention to produce a "color receiver that could retail for \$500."—a cut of \$200 below the present market. This set would use the Lawrence color picture tube, so far not manufactured in quantities. Even this price will not prevail for perhaps a year or more.

When prices of color sets reach \$400 or \$350—possibly in 1957—then we will see production of tens of millions of sets a year. (There are now 40 million black-and-white TV sets in the U. S.)

Another reason why the television industry has not rushed into color-set manufacture is twofold. First there is the great complexity of manufacturing the present-day receiver and the comparative lack of know-how. Secondly, every color set must be installed by a factory-trained technician, inasmuch as the average service technician has had practically no experience with color. It will take them time to familiarize themselves with the new required techniques. It could not be otherwise if we reflect

that up to Nov. 1, 1955, a total of only 41,500 color receivers had been manufactured. By Jan. 1, 1956, a figure of 51,500 was expected. RCA intends to sell more than 200,000 color sets in 1956.

It may be news to most service technicians that color sets are sensitive to such outside influence as, for instance, the earth's magnetic field. Hence placement of the receiver in the owner's home often poses a problem. So are ghosts much more annoying in color than in black-and-white. The owner, too, must be instructed more thoroughly in color tuning than was the case with black-and-white sets.

All this is to be expected in any new product, particularly in a truly miraculous one like color television, possibly man's greatest electronic technical triumph. We certainly are privileged to live in this age of wonders, and it therefore behooves us to overlook petty flaws.

As time goes on, we know that color television's present complexities will vanish. Already the 1955 color receiver has been simplified. It has only 26 tubes (most of them dual purpose types) against 37 tubes in 1954.

To be sure the picture tube, the heart of color TV, is still and will remain for some years the supreme technical crux. It is here that invention, engineering skill and simplification will cut the Gordian knot of manufacturing and production economics. Small wonder if we remember that today's list price of the 21-inch color tube is \$175 against an average of \$45 for a black-and-white one.

In the meanwhile, we should not forget that present-day color sets are excellent, even if the price is still somewhat high. Nor will it be too easy to buy them in 1956 in many localities. They are certain to be scarce for some time to come, and deliveries will often be slow.

Let us now turn to the future. We may be positive that in years to come a color picture tube will sell for only a fraction of today's cost. In our opinion, the present three-gun tube will not prevail. We may not even use one gun—and we will probably not scan at all the way we do now.

Take the animal eye. Look steadily at a color painting on the wall. Your eye does not scan. It uses no three-color "gun." It receives all the colors in the rainbow reflected by light from the picture. These color rays pass through the lens of your eye and are focused on your retina, i.e., the "screen." You perceive colors because of the difference of frequencies of the incoming light rays.

In our opinion it should be possible to eliminate all scanning and even cathode rays, in the manner in which they have been used up to now.

We can imagine a flat rectangular vacuum glass or metal-glass tube 2 to 4 inches thick. The screen on the inside will be covered with a pattern of thousands of phosphors, each of which will react to its selected color of red, green or blue. The phosphor screen is bombarded by electrons from the rear. The high-voltage supply, the sound equipment, etc., remain more or less standard television receiver procedure. The screen now lights up brilliantly and the colors appear on the front of the screen as at present.

There is no actual direct scanning inside of the flat picture tube, no moving cathode ray—special electron tubes or transistors do all the work in sequential or pulsing electronic switching.

The above is a rough theoretical outline of a possible future TV color screen. We know it will take many years to perfect it. But it will come.

—H. G.

# Trends in 1955

By ROBERT F. SCOTT  
TECHNICAL EDITOR

WE cannot foresee the various circuit innovations and improvements in TV receiver circuitry during 1956 but the chances are good that the new models will be pretty much like those produced during the latter months of the past year. This article describes some of the more novel circuits in late 1955 sets. Whether these circuits are sufficiently important to gain wide acceptance is yet to be seen. But there is always the chance that at least one of them will receive the universal acceptance accorded the flyback transformer, keyed a.g.c. and cascode r.f. amplifier.

Tuners, transformers, tubes and other components will be improved, making it possible to decrease the weight and number of tubes in a set and in some cases reduce the number of controls. For example, a number of recent sets use a high-efficiency flyback transformer and horizontal output circuit that enables the designers to eliminate the horizontal linearity and width controls.

Although many of the better TV sets have, for the last few years, included circuits designed to eliminate or attenuate noise pulses so they will not affect the stability of deflection circuits, the search is still on for simpler and more effective circuits. Usually special noise-cancelling circuits are inserted at a point between the sync take-off and the input to the deflection generators. Recently several manufacturers have developed circuits to attenuate noise in the i.f. circuits. (See "Motorola Frame-Lock Circuit," page 56, November, 1955.)

Crosley attacks noise in both the i.f. and sync circuits. Fig. 1 shows the feedback circuit used to attenuate noise in the i.f. amplifier circuits of the 466 and 467 chassis. Noise pulses appear as amplitude modulation on the video i.f. carrier. This circuit acts as a com-

pressor to clamp the positive half-cycles of the noise signal that are strong enough to drive the grid of the third i.f. amplifier positive.

Fig. 2-a shows the video carrier envelope, with noise pulses superimposed, at the input to the third i.f. amplifier. The first five or six positive half-cycles drive the grid positive. They are rectified and produce negative pulses across the 470-ohm grid resistor (Fig. 1). These pulses are tapped off and fed through the 6.5- $\mu$ h choke, 0.1- $\mu$ f

video amplifier and are considerably weaker at the sync take-off point.

Although the noise pulses are clamped at or slightly above the level of the sync tips by the i.f. feedback circuit, some may still get through and cause picture tearing and rolling. Fig. 3 shows the circuit that Crosley uses to immunize the sync circuits further against noise in the 466 and 467 chassis.

A bleeder resistor consisting of R122, R128, R176, R193 and R178 is connected between the 260-volt B-plus line

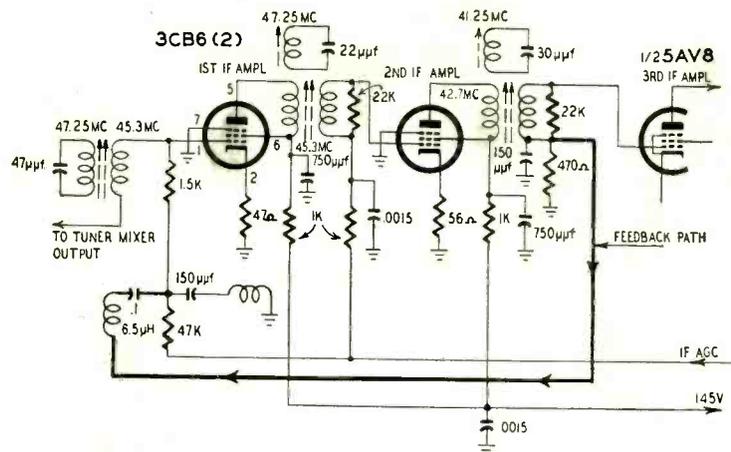


Fig. 1—Schematic of noise attenuator circuit in Crosley 466 and 467 chassis.

pressor and the 1,500-ohm resistor to the grid of the first i.f. stage. The feedback is so fast that the pulses act as a negative bias that momentarily reduces the gain of the first i.f. stage for the remainder of the noise pulse shown in dashed lines 2-b.

The first few cycles of the noise signal that do get through to the video detector correspond to frequencies above 5 mc so they are greatly attenuated by the bandpass characteristics of the

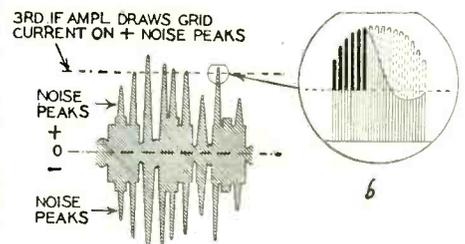


Fig. 2—Noise pulses on carrier signal



and 24 volts negative tapped off the horizontal output tube grid resistor. The grid of the noise inverter tube is tapped on the bleeder at a point that biases it to or slightly below cutoff. The exact bias is determined by R128, the NOISE GATE control. This is set so the noise inverter is cut off for all signals below the sync tips.

The cathode of the noise inverter is fed with negative noise pulses tapped off the video detector load (R118 and R190). Its plate is tied directly to the sync take-off point where noise pulses have positive polarity. When noise pulses arrive simultaneously at cathode and plate, the tube conducts and shorts the positive pulses to ground, preventing their reaching the sync clipper.

The AREA SWITCH varies the overall sensitivity of the receiver for best operation in areas of different signal strengths. In the LOCAL position, the tuner plate voltage is taken off the arm of the LOCAL AREA CONTROL con-

nected as a voltage divider between the 150-volt line and ground. Normally this control is set for maximum voltage and gain. But, when the signals are exceptionally strong, the tuner plate voltage is reduced so a good sharp picture can be obtained without overloading on the area's strongest signal.

When the switch is set to NORMAL, the tuner B plus line is disconnected from the variable 150-volt source and tied directly to the fixed 260-volt line. The sync noise eliminator circuit is disabled in the NORMAL and LOCAL positions of the switch by grounding the junction of R176 and R193 and allowing the noise-inverter grid to rise to cutoff (-24 volts).

In the DISTANT position of this switch, the tuner a.g.c. voltage is reduced approximately one-half and the short is removed from the junction of R176 and R193 to allow the bias on the noise-inverter grid to rise to the normal operating level set by the NOISE GATE.

This control varies the screen voltage on the video amplifier to set the clipping level and simultaneously varies the bias on the noise inverter so it conducts on noise pulses of a predetermined amplitude. The NOISE GATE control is open and out of the circuit when turned to its extreme counter-clockwise position. In any other position, it controls the clipping level of the video amplifier and is highly effective in all three position of the AREA SWITCH.

### Triode sound i.f. amplifiers

Set manufacturers frequently use a large number of dual-purpose tubes in a TV set to reduce the total number of tubes without impairing performance. In some instances, it is necessary to use a triode in the sound i.f. amplifier circuit. This presents a design problem because a triode will oscillate because of feedback through the grid-plate capacitance when its plate and grid

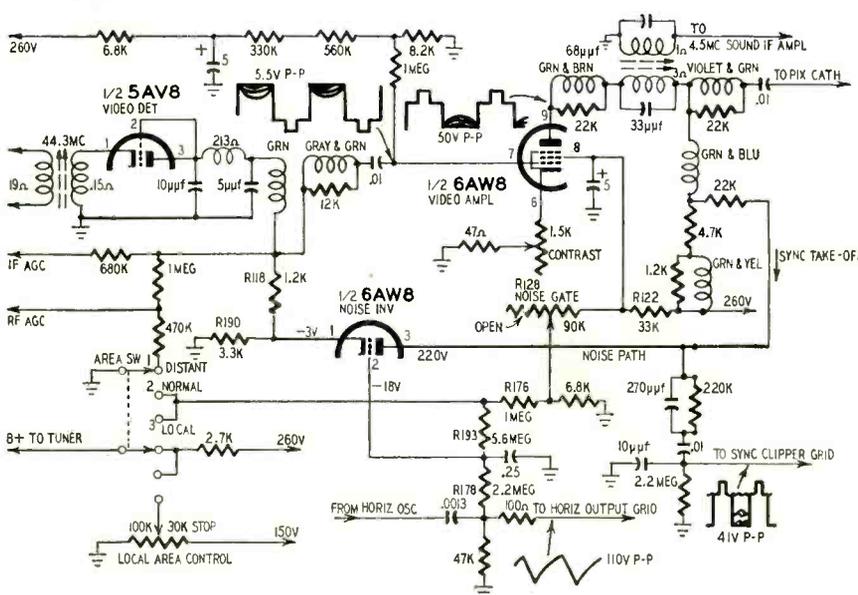


Fig. 3—Schematic of the video and noise inverter circuit in Crosley 466, 467.

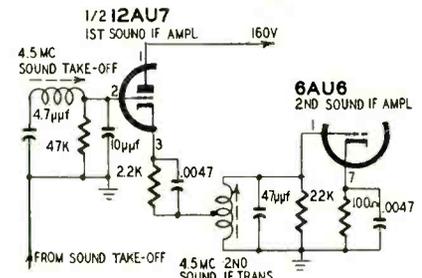


Fig. 4—Sylvania 1-521-1 sound i.f.

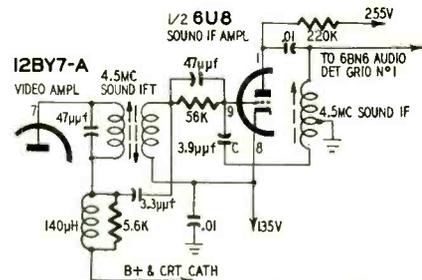


Fig. 5—Capehart CX-38S sound i.f.

# TELEVISION

are tuned to the same frequency. Fig. 4 shows the triode first sound i.f. amplifier in the Sylvania 1-521-1 chassis. In this circuit the need for neutralization is eliminated by operating the triode as a cathode follower. In the usual cathode follower circuit the output voltage is less than the input. To overcome this, Sylvania uses an autotransformer type second i.f. coil. The signal voltage developed in the cathode circuit appears between the tap and ground. A signal voltage much higher than the input is developed across the entire winding and is fed to the grid of the second i.f. amplifier.

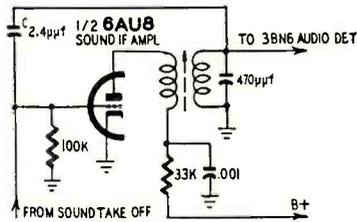


Fig. 6—Zenith T1814R sound i.f.

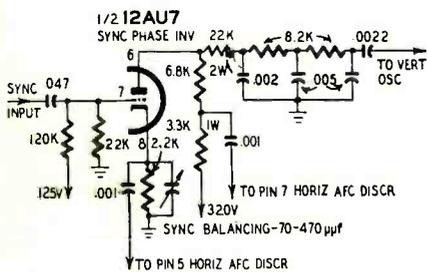


Fig. 7—Sync phase inverter circuit.

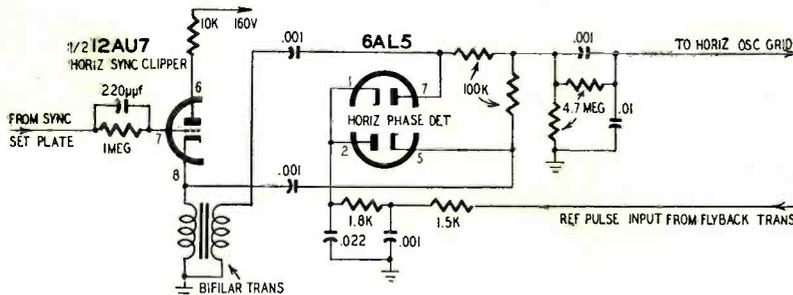


Fig. 8—Horizontal sync clipper and phase detector in Sylvania 1-521.

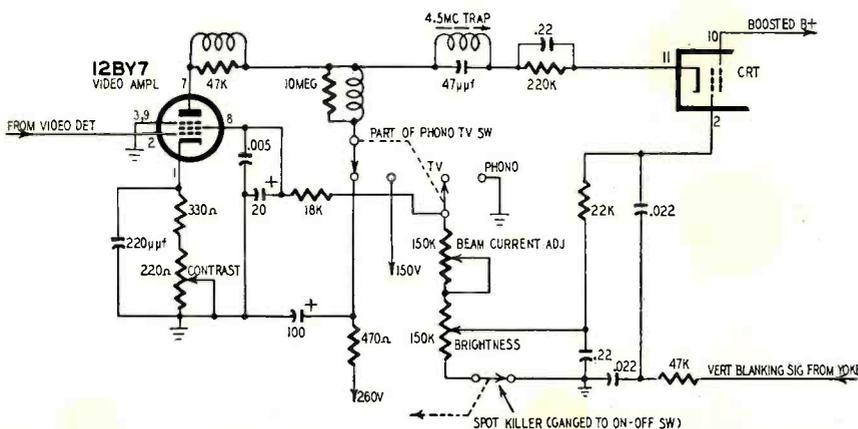


Fig. 9—Video amplifier and picture-tube input of Hoffman Mark V 415, 416.

Fig. 5 shows the scheme used in the Capehart CX-38S chassis. The 4.5-mc sound i.f. signal is tapped off the plate circuit of the video amplifier by a high-impedance i.f. transformer that also acts as a sound trap in the signal circuit to the picture tube. Maximum transfer of signal to the grid of the first sound i.f. amplifier is provided by capacitive coupling through the 3.3-µf capacitor and magnetic coupling in the transformer.

In this circuit oscillation is prevented by feeding back to the grid, through an external circuit, a voltage equal to and 180° out of phase with that reaching the grid through the grid-plate capacitance of the tube. This neutralizing signal voltage is obtained from one end of the 4.5-mc sound i.f. coil common to the plate circuit of the 6U8 and the grid of the 6BN6 discriminator. Neutralization is obtained by carefully adjusting the value of C and the position of the tap on the coil. (Old-timers will recognize the neutrodyne circuit, so popular in t.r.f. radios 30 years ago.)

The triode section of a 6AU8 is used as the sound i.f. amplifier in the Zenith model T1814R in Fig. 6. Here, the neutralizing voltage is obtained from the secondary of the i.f. transformer. This winding is polarized so the voltage on the grid of the gated-beam discriminator is out of phase with that on the plate of the 6AU8. When the voltages on the primary and secondary are equal, the voltages on the grid are equal and the stage is neutralized when the capacitance of C equals the sum of the stray and internal grid-plate capacitances.

## Horizontal sync balance

Positive and negative horizontal sync pulses of equal amplitude are required for proper operation of a horizontal phase detector. Conventionally, the positive pulses are taken from the plate and negative pulses from the cathode of a sync phase inverter or clipper. Vertical sync pulses are also taken from the plate circuit. The frequency responses of the plate and cathode circuits differ because of differences in stray circuit capacitance. This often makes it hard to balance the amplitudes of the sync pulses applied to the phase detector.

If the circuit is adjusted so the horizontal sync pulses balance, the differences in circuit response may unbalance the vertical sync pulses on the phase discriminator diodes and reduce the stability of the horizontal sweep circuit. Sylvania uses two schemes to balance the sync signals fed to the phase detector.

Fig. 7 shows the circuit used in the 1-520 chassis. A 70-470-µf trimmer capacitor is used in the cathode circuit of the sync phase inverter to improve balance between the positive and negative sync pulses. This capacitor is set to balance the frequency responses of the plate and cathode circuits for equal horizontal pulses.

In some chassis, circuit parameters are such that this particular balancing scheme would result in a larger vertical pulse appearing on one diode of the horizontal phase detector when the horizontal sync pulses are balanced. This would reduce horizontal stability. To eliminate this trouble in the 1-521 chassis, a bifilar-wound transformer is used as a phase inverter in the cathode circuit of the sync clipper (Fig. 8). In this circuit negative sync pulses are taken from the cathode and positive pulses from the secondary of the transformer. Since the impedances of the transformer windings are equal, the negative and positive sync pulses are balanced, regardless of frequency. The transformer has a low Q so the pulses will not cause ringing or oscillation.

## Beam afterglow

An intense spot of light often appears on the screen of a picture tube when the TV set is turned off. This spot can sometimes cause a permanent stain that looks something like an ion burn. After a set is turned off, the cathodes of the tubes may retain enough heat

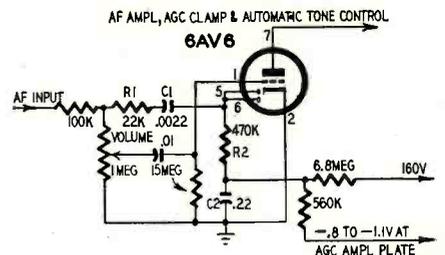


Fig. 10—The Automatic Audio Ranger.

to continue to emit electrons for 30 seconds or longer. The low-voltage filter capacitors discharge almost immediately through the various voltage dividers and bleeders and through the tubes whose cathodes are still emitting.

The high-voltage filter capacitor, usually a 500- $\mu\text{f}$  unit or the capacitance between the inner and outer Aquadag coatings on the picture tube, can discharge only through stray leakage and the electron beam. The time constant of this circuit is long and the spot remains on the screen until the high-voltage capacitor is discharged to the point where its voltage is not sufficient to attract electrons from the cathode. Whether a TV screen is burned by this spot of light depends on the beam intensity and the time that it remains undeflected. A high-intensity beam can strike the screen for several seconds without damaging it while a much weaker one will burn it if undeflected for a much longer period.

Fig. 9 shows the spot-killer circuit in the Hoffman Mark V 415 and 416 chassis. A switch—ganged to the on-off switch in the power line—is connected between ground and the low end of the brightness control. When this switch is opened, the grid of the picture tube is around 45 volts positive with respect to cathode. This positive grid bias accelerates the residual electron beam and causes a heavy beam current that quickly discharges the high-voltage capacitor. The high beam current does not last long enough to burn the screen.

The beam-current adjustment is another innovation in this receiver. Its purpose is to prevent blooming when the brightness control is advanced. It limits the positive voltage that can be applied to the grid of the picture tube and thus limits the loading on the high-voltage supply when brightness is turned toward maximum.

To adjust this control check the position of the ion-trap magnet, set the brightness control to maximum and then set the beam-current control for the brightest raster without blooming. This control must be readjusted each

time the video amplifier, high-voltage rectifier, horizontal output or picture tubes are changed.

### Automatic tone control

A high-frequency hiss or frying sound may be heard in the background of a TV receiver's audio channel when the incoming signal is not strong enough to overcome the antenna and circuit noises. To eliminate hiss in some of its chassis, Sylvania uses an automatic high-cut tone control (*Automatic Audio Ranger*) that reduces the high-frequency response of the audio circuit when signal-to-noise ratio is low. This necessarily cuts out some of the higher audio frequencies but results in a sound free from background noise.

The circuit of the *Automatic Audio Ranger* used in the 1-522 chassis is shown in Fig. 10. Fig. 11-a is a conventional high-cut type manual tone control and Fig. 11-b is the basic circuit of the electronic equivalent. In Fig. 11-a high-frequency attenuation increases as the value of R is decreased or the capacitance of C is increased.

In Fig. 11-b, the diode replaces R in Fig. 11-a. The series resistance in the tone control is controlled by varying the conduction in the diode. The diode plate is connected to a voltage divider between the a.g.c. and 160-volt B-plus lines. The circuit values are adjusted so the diode plate is slightly negative when the a.g.c. voltage is low and highly negative when signal strength and a.g.c. voltage are high.

We usually consider a diode cut off when its plate voltage is zero or negative with respect to the cathode. However, this is not the case when the plate is only a few volts negative. In this case, current flow in the tube is due to the high velocity of the electrons leaving the cathode. The graph in Fig. 12 shows the current flow with a low negative voltage on the plate. The straightness of the curve indicates that the internal resistance of the diode is comparatively linear in the negative plate-voltage region.

In the practical circuit (Fig. 10) C1 and the diode (pins 2 and 6) form the high-frequency attenuator. The voltage divider consists of the 6.8-megohm and 560,000-ohm resistors between the B-plus and a.g.c. lines. Since the a.c. signal voltage is applied to the diode plate, the internal resistance will change in step with it. R1 is added in

series with C1 to increase the total resistance in the circuit and minimize the effects of resistance change with signal voltage.

If R1 is omitted, the resistance will vary greatly with signal voltage and the high-frequency end of the audio range will be distorted. C2 filters out sync buzz and prevents it from entering the audio circuit through the connection to the a.g.c. line. R2 decouples C2 from the tone-control circuit and prevents it from short-circuiting the audio signal to ground.

### Deflection output circuits

The vertical and horizontal output circuits in many receivers have been greatly simplified. Fig. 13 shows the vertical output and oscillator circuit used in the Muntz 474A chassis. Feedback required for oscillation is developed in a special winding on the output transformer. Pulses for blanking vertical retrace lines are tapped off the screen grid and shaped by the .01- and .022- $\mu\text{f}$  capacitors and the 47,000-ohm resistor.

Fig. 14 is the vertical oscillator and output circuit in the Crosley 445 chassis. An autotransformer couples the tube to the yoke. Vertical linearity is improved by negative feedback through the .005- $\mu\text{f}$  capacitor and height control to the grid of the output stage. END

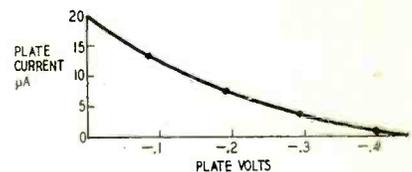


Fig. 12—Diode characteristic curve.

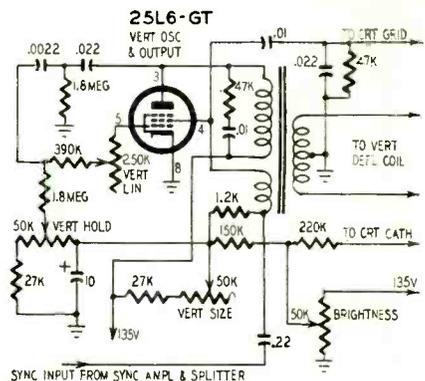


Fig. 13—Vertical oscillator and output circuits in the Muntz 474A chassis.

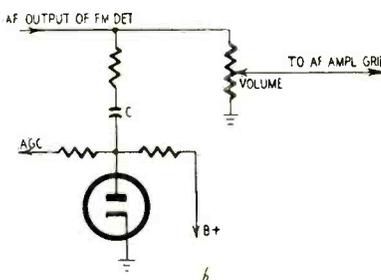
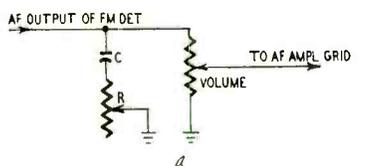


Fig. 11—High-cut tone controls.


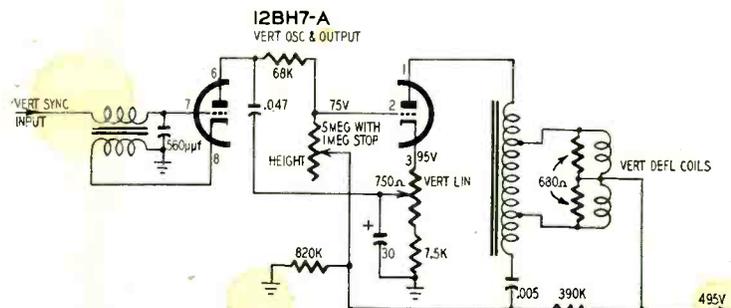
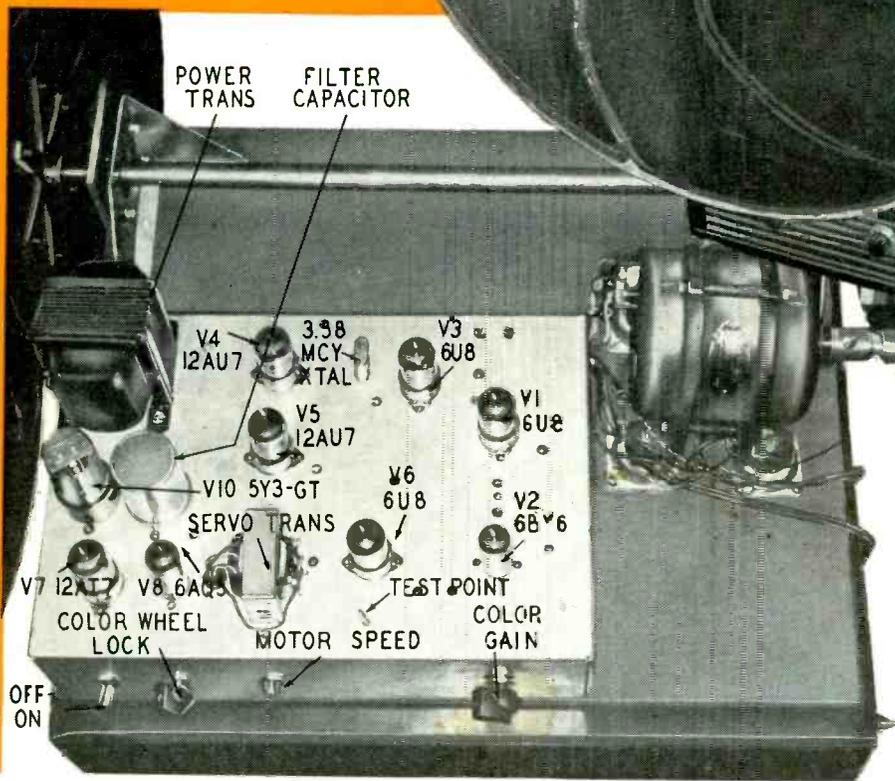


Fig. 14—Vertical oscillator and output circuits in the Crosley 445.
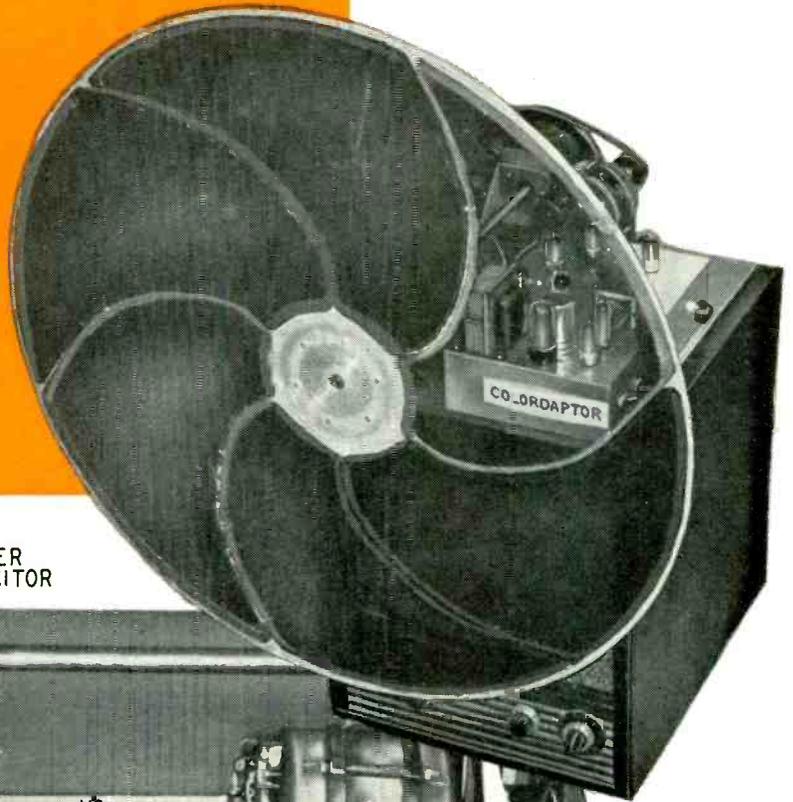
# COLOR DAPTOR

*Part I—Color reception with black-and-white TV receiver for \$85 and up—junkbox owner might do it for \$50*

By PERRY H. VARTANIAN and ROBERT W. DEGRASSE



Above, the complete Colordaptor installed. Left, top view shows major components.

**A**LTHOUGH rapid advances are being made in commercial color TV, as yet most circuits are complex and require expensive, difficult-to-obtain components such as the tricolor kinescope. For the experimenter interested in color TV, the Colordaptor offers a method of obtaining good color TV from present black-and-white receivers at a minimum of expense and complexity.

The Colordaptor system uses a

simple nine-tube circuit and a rotating color wheel to convert any black-and-white TV set to color operation.

The decoder, with only six tubes, is the heart of the Colordaptor system. This circuit converts the NTSC compatible dot sequential color signal, now standard in the United States, into a field sequential signal. This signal is supplied to the black-and-white picture tube and, when viewed through the rotating color wheel, a full color picture results.

The Colordaptor can be built from parts most experimenters have on hand. Tubes are standard receiving types and all the coils may be handwound. The Colordaptor decoder has undergone extensive development to simplify all circuits and remove critical adjustments. The completed system has only two color adjustments, hue and saturation. An r.f. signal generator and a standard volt-ohmmeter are the only test instruments required for alignment.

The color wheel (see photo) is mounted on a removable unit on top of the TV set. The Colordaptor chassis may be permanently attached to the rear of the set since, when left connected, it does not affect normal black-and-white reception. The color wheel may be removed when desired.

The rotating color wheel, when used with standard picture tubes, eliminates the need for an expensive color tube and associated deflection and high-voltage circuits. It is driven with a 1/50- (or less) horsepower motor and is constructed of lightweight materials. A simple two-tube synchronizer circuit locks the color-wheel speed to the TV picture rate automatically.

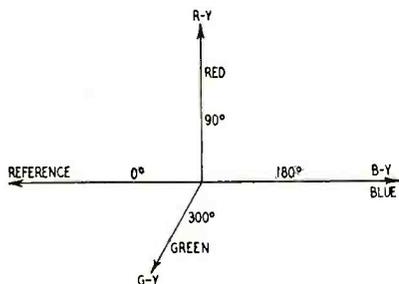


Fig. 1—Demodulator color phases.

Numerous articles have described the NTSC compatible color television signal and the reader should be reasonably familiar with its makeup. The color signal is transmitted as sidebands of the 3.58-mc subcarrier. The color information is separated into two parts, hue and saturation. Hue is the color, saturation is the depth or dilution of color, that is, bright red as compared to pink. At the color receiver the hue of the picture is determined by the phase of the received color signal, saturation by the amplitude. The reference phase is transmitted during the horizontal retrace as an eight-cycle burst.

As is shown in Fig. 1, a certain phase angle corresponds to each of the primary colors. That is, 90° from the reference phase is the red information, 180° the blue and 300° the green. In the conventional color TV set, two synchronous demodulators are used which measure the amplitudes of two phases 90° apart. The I and Q system is a special choice of demodulation angles which permits a greater color bandwidth to be obtained. The most common system now used is the R - Y B - Y system. All these systems have the common characteristic that there

are three color signals being produced at all times.


In the Colordaptor system only one signal at a time is required. When the red filter is in front of the TV tube, the Colordaptor demodulates along the 90° phase, for blue it switches to 180° and for green it switches to 300°. The switching operation continues automatically from red to blue to green and the color wheel is locked in with the switching operation. Consequently, a complete red picture is followed by a complete blue picture and finally a complete green picture. The switch operates at 60 cycles so that a set of three color pictures is produced each 1/20 second. The eye then superimposes these pictures to give the full color effect. That is all there is to the principles of operation of the Colordaptor (Fig. 2) system.

**Operation of the Colordaptor**

The video is taken off at the second detector and after going through a stage of preamplification (Fig. 3) is fed into high-gain chroma amplifier V1-a. This stage is designed to discriminate against both the low-frequency black-and-white video signal and the high-frequency 4.5-mc sound

channel. The output of the chroma amplifier is fed to demodulator V2 and burst gate V3-a. The burst gate is normally biased off until the horizontal sync pulse drives it into conduction. This occurs toward the end of the horizontal flyback which is exactly when the eight cycles of 3.58-mc reference occur. Thus the burst-gate output consists of bursts of 3.58-mc reference signal. The crystal filter with associated V3-b drive tube converts these bursts into CW 3.58-mc r.f. reference voltage.

The reference phase shift network then supplies exactly the correct delay so that reference phases for the three colors, as shown in Fig. 1, are generated and fed into the tritch (tristable switch). The tritch, made up of triodes V4-a, -b and V5-a, is essentially a three-position rotary switch "rotating" at 20 cycles. It is triggered among its three stable conditions by the vertical sync pulse via V5-b. The output of the tritch is then 3.58 mc which has a phase of alternately 90°, 180° and 300° relative to the reference signal. After amplification and limiting in reference amplifiers V6-a and V6-b, the tritched reference signal is then applied to V2.

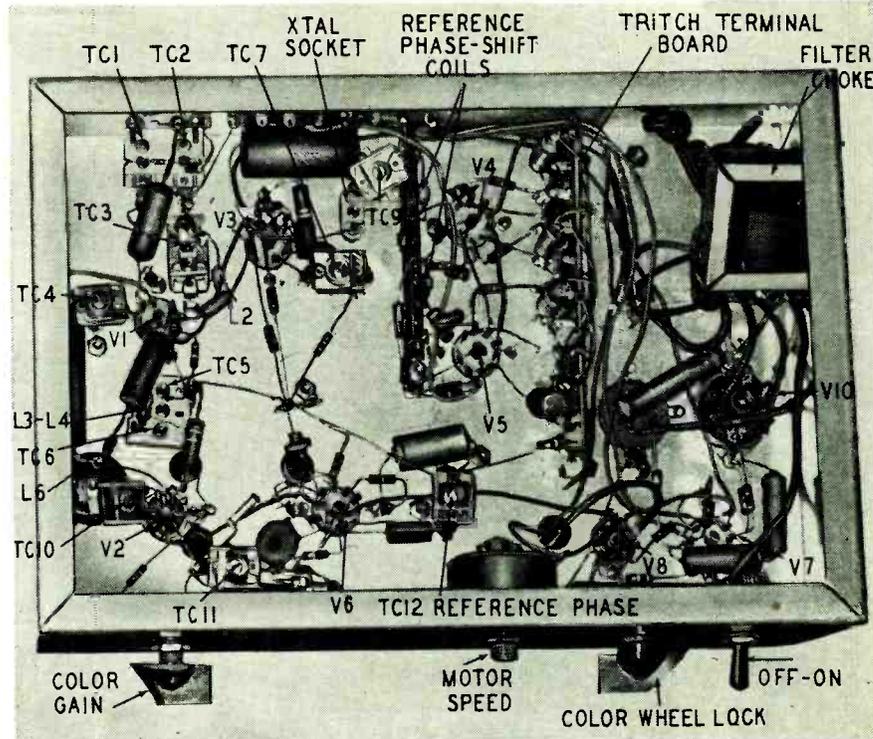

Underchassis layout of Colordaptor. TC8 was omitted from this unit.

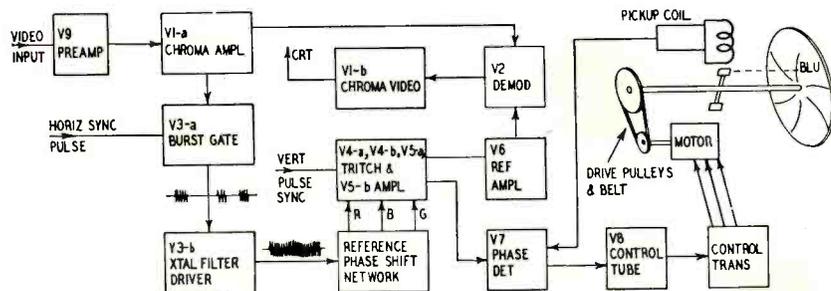


Fig. 2—Block diagram shows circuit distribution in the Colordaptor.

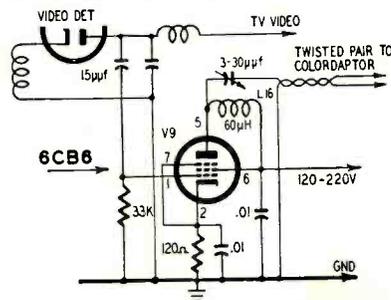


Fig. 3—Schematic of the preamplifier.

# COLORDAPTER SCHEMATIC AND CONNECTIONS

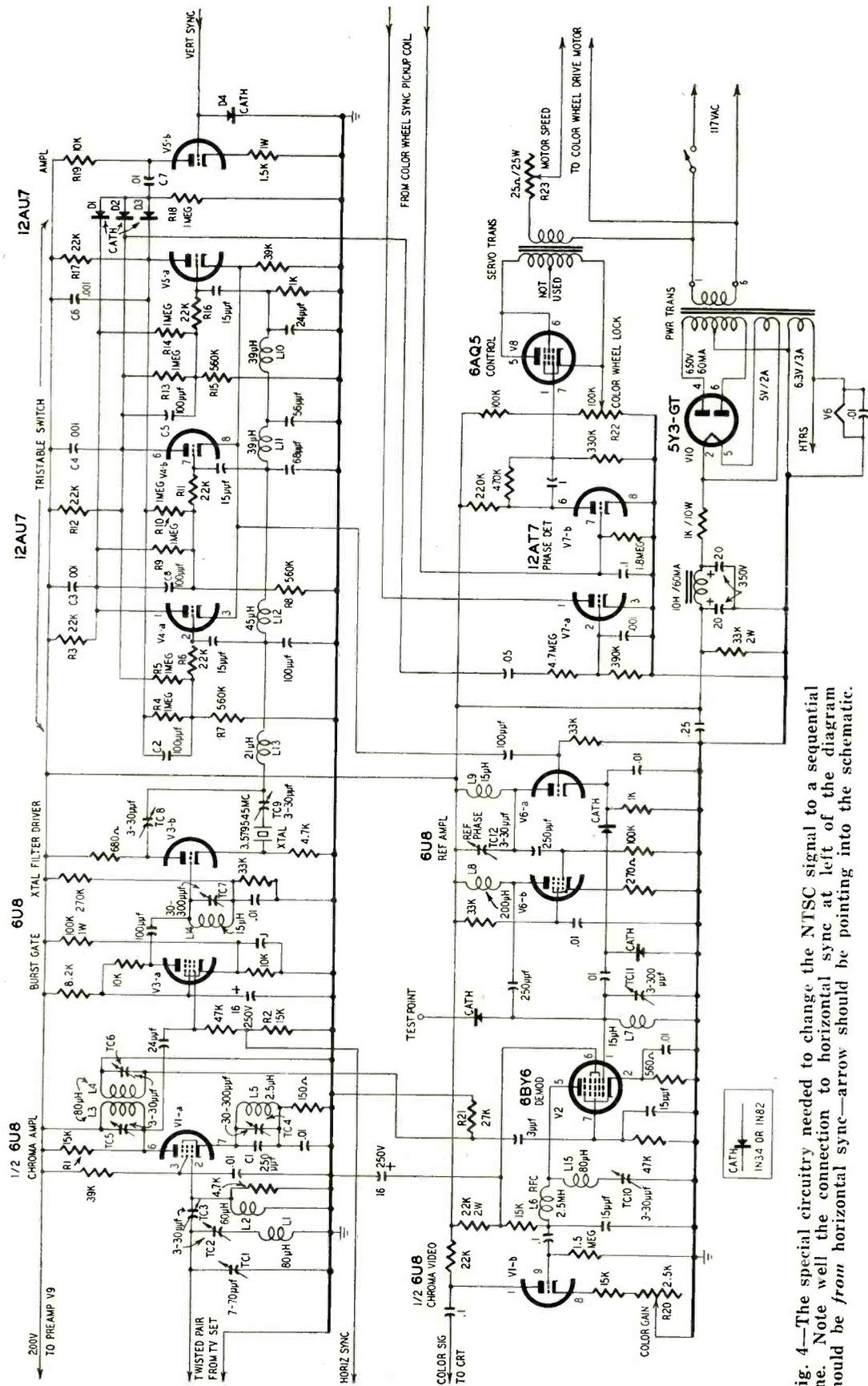


Fig. 4—The special circuitry needed to change the NTSC signal to a sequential one. Note well the connection to horizontal sync at left of the diagram should be *from* horizontal sync—arrow should be pointing into the schematic.

The output of the demodulator is then amplified in V1-b and applied to the picture-tube grid (monochrome video on the cathode) or cathode (monochrome video on the grid).

A delay line is added in the black-and-white video circuit so that the black-and-white and color signals arrive at the picture tube at the same time. Connections are made to the vertical and horizontal sweep circuits to provide synchronizing signals for the Colordaptor.

The color wheel and associated drive mechanism include a small magnetic pickup which gives a voltage pulse once for each set of red, blue and green filters. This synchronizing pulse is compared with the plate waveform of the blue triode and the phase difference detected by V7. The resulting control signal is applied to control tube V8 which in turn controls the motor speed through the control transformer.

**Constructing the Colordaptor**

Chassis layout is shown in the photos. The circuit is shown in Fig. 4. A 3 x 12 x 8-inch chassis is large enough to hold the entire system including power supply and synchronizer.

A suggested procedure for construction is to locate all socket, transformer and trimmer capacitor holes first. After these are drilled and cleaned, mount all large components in place. Wire the tube heater leads using the chassis as common ground. The heater lead should be bypassed to ground at V6 with a .01- $\mu$ f capacitor. Using tie points, run a B-plus bus.

Since most of the components associated with V4 and V5 are not critical as to wire lengths it is advisable to mount them on a terminal board (Fig. 5). Then mount the terminal board (see photo).

Mount and wire in place all inductors and trimmers. These should be placed

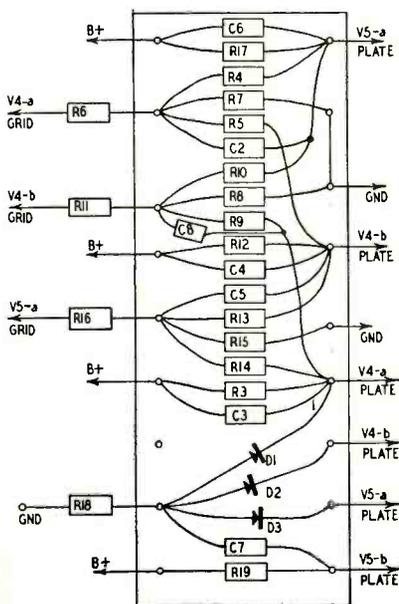


Fig. 5—The tritch terminal board.

approximately as shown in the photo. The dimensions of the coil forms are given in Fig. 6 and the winding data in the parts list. It is important that L7, L8 and L9 be well separated since oscillation is possible in the high-gain reference amplifier.

For those not wishing to wind their own coils, special machine-wound coils are available in kit form from the Colordaptor Co., 3471 Ramona, Palo Alto, Calif. The 3.58-mc color crystal is also available as well as all other components individually or in complete kit form.

If external controls are desired for the Colordaptor, COLOR GAIN R20 and REFERENCE PHASE TC12 may be located on the TV set front panel. The connection to R20 should be kept away from any high-voltage pulses, but otherwise is not critical as to length. The connection to TC12 may be run through a shielded cable for a length up to about 4 feet. The additional capacitance of the cable reduces the amount of capacitance which must then be added as the reference control. A 100- $\mu$ f variable capacitor should be satisfactory.

The connections which attach the Colordaptor to a TV set are shown in Fig. 7. All connections except the twisted pair and the color signal connection to the picture tube may be run in a cable.

The vertical sync pulse required is taken from the grid of the vertical output tube of the TV set. It is a negative pulse of about -10 to -30 volts.

The horizontal sync pulse is taken from the plate of the horizontal output tube. This pulse has a positive amplitude of about 3,000 to 5,000 volts,

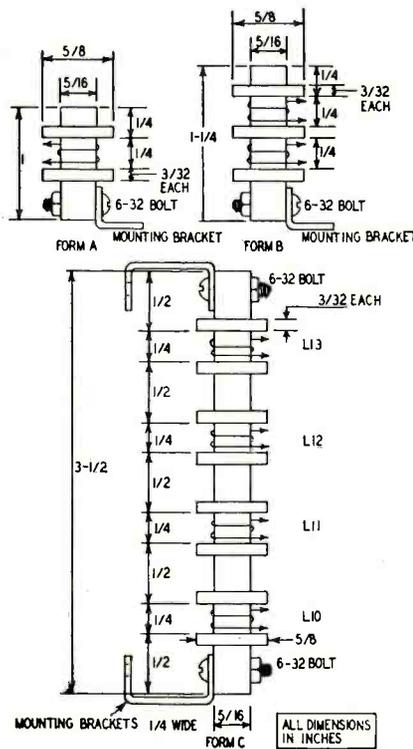


Fig. 6—Dimensions of coil forms.

reduced in amplitude by the divider network to approximately 30 volts. An alternate connection is to wind about 10 turns of wire about the horizontal output transformer core. One side of this winding is grounded at the TV set and the other connected directly to the Colordaptor. The divider is not needed when this is done.

The chroma signal for the Colordaptor is amplified by 6CB6 V9 (Fig. 3). The power for V9 may be obtained either from the Colordaptor or, preferably, from the TV set. The addition of V9 to the set makes it possible for the Colordaptor system to operate from any standard TV since the preamplifier may be adjusted to compensate for insufficient i.f. amplifier bandwidth. The chroma preamplifier 6CB6 can be mounted on the TV chassis or on a bracket near the video detector. The trimmer should be mounted in such a manner that it is accessible for tuning when the chroma amplifiers are to be aligned.

A delay line (Fig. 8) is added to the video amplifier of the TV set in the plate circuit of the output video amplifier. This line has a delay of about 1.3  $\mu$ sec and an impedance of 5,000 ohms. The delay line winding should be made about 6 1/2 inches long. After the set is operating its length can be trimmed to align the color and black-and-white pictures accurately. Since approximately 113 turns of No. 32 enameled wire occupy 1 inch of winding length, the lathe feed is set for .0039 inch per revolution so the turns tend to overlap and form roughly two layers in a single pass of the lathe. The delay line is also available from the Colordaptor Co.

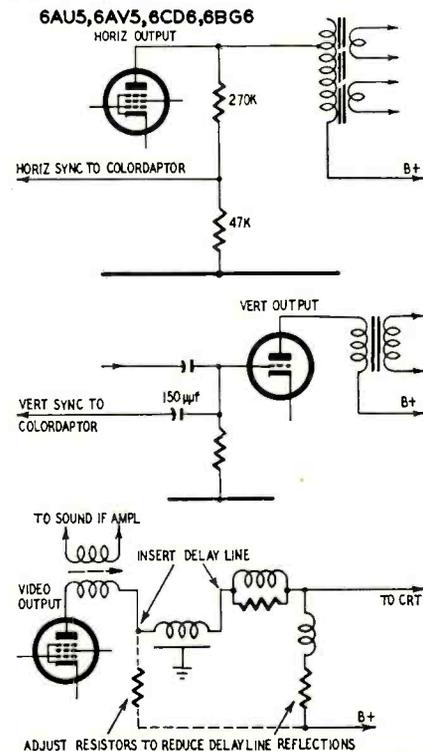


Fig. 7—The diagrams show TV receiver attachments to the Colordaptor.

## TELEVISION

In addition, vertical and horizontal retrace blanking signals are added, depending on the method of connection of the black-and-white video to the picture tube. The proper retrace connections are shown in Fig. 9. The connections shown in Fig. 9-a apply

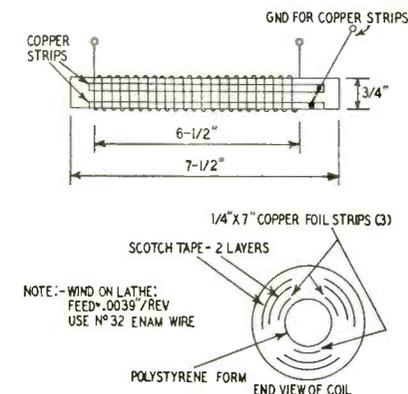


Fig. 8—Construction of delay line.

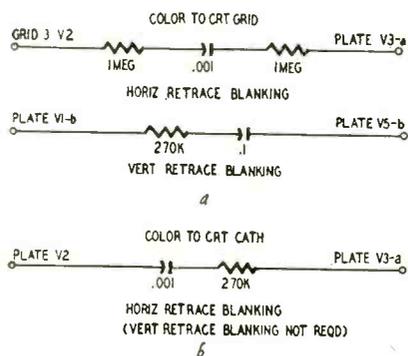


Fig. 9—Retrace blanking circuits.

when the video is on the cathode of the picture tube; Fig. 9-b when the video is on the grid.

Next month the color-wheel mechanism and synchronizer will be described, together with alignment and operation data. **TO BE CONTINUED**

### Parts for Colordaptor


**Resistors:** 1—120, 1—150, 1—270, 1—560, 1—680, 2—1,000, 2—4,700, 1—8,200, 3—10,000, 4—15,000, 6—22,000, 1—27,000, 4—33,000, 2—39,000, 3—47,000, 2—100,000, 1—220,000, 1—270,000, 1—330,000, 1—390,000, 1—470,000, 3—560,000 ohms; 7—1, 1—1.5, 1—1.8, 1—4.7 megohms, 1/2 watt; 1—1,500, 1—100,000 ohms, 1 watt; 1—22,000, 1—33,000 ohms, 2 watts; 1—1,000 ohms, 10 watts; 1—25 ohms, 25 watts, potentiometer; 1—2,500 ohms, 1—100,000 ohms, potentiometers.

**Capacitors:** 1—3, 6—15, 2—24, 1—56, 1—68, 6—100, 1—150, 2—250  $\mu$ f; 4—.001, 11—.01, 1—.05, 4—0.1, 1—0.25, 1—1  $\mu$ f; 2—16  $\mu$ f, 250 volts, electrolytics; 2—20  $\mu$ f, 350 volts, electrolytics; 9—3—30, 1—7—70, 5—30—300  $\mu$ f (shunt TC4 with 250- $\mu$ f capacitor C1).

**Coils and transformers:** L1, L15—80  $\mu$ h, 100 turns No. 2-38 or 5-44 litz wire (form A); L2, L16—60  $\mu$ h, 85 turns No. 2-38 or 5-44 litz wire (form A); L3-L4—80  $\mu$ h, 100 turns each No. 2-38 or 5-44 litz wire (both on form B); L5—2.5  $\mu$ h, 12 turns No. 28 enamel wire, 1/4-inch diameter form; L6—2.5-mh r.f. choke; L7, L9, L14—15  $\mu$ h, 40 turns No. 28 enamel wire, 1/4-inch diameter form; L8—200- $\mu$ h peaking coil; L10, L11—39  $\mu$ h, 64 turns No. 2-38 or 5-44 litz wire (form C); L12—45  $\mu$ h, 73 turns No. 2-38 or 5-44 litz wire (form C); L13—21  $\mu$ h, 51 turns No. 2-38 or 5-44 litz wire (form C); 1—power transformer, 650 volts c.t. @ 60 ma, 6.3 volts @ 3 amps, 5 volts @ 2 amps; 1—choke, 10 h @ 60 ma; 1—servo transformer (Stancor A-3852 to be described in following article).

**Tubes:** 3—6U8, 1—6BY6, 2—12AU7, 1—12AT7, 1—6AQ5, 1—6CB6, 1—5Y3-GT.

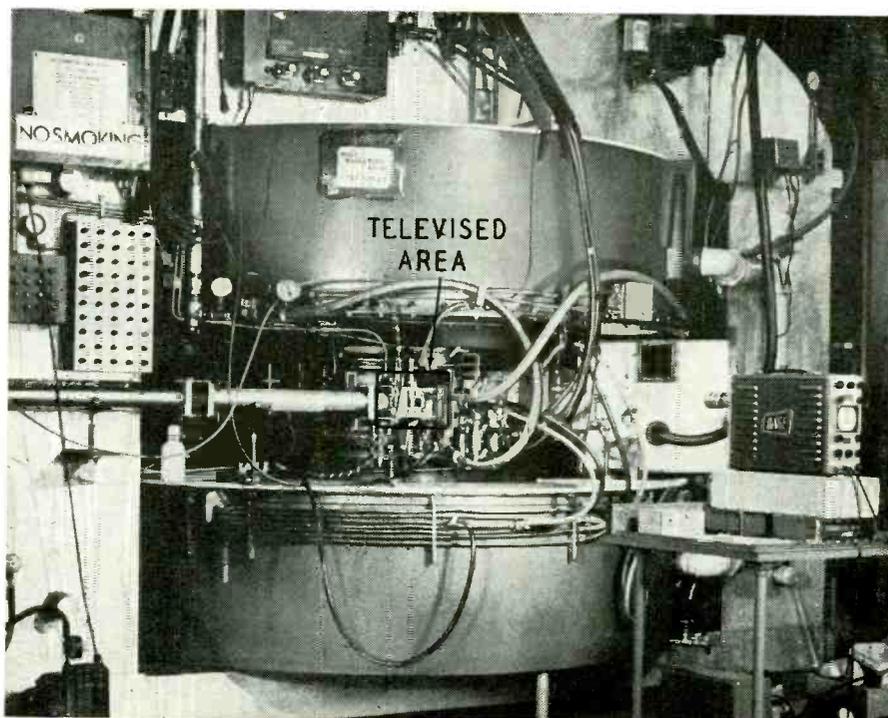**Miscellaneous:** 5—diodes, 1N34, 1N82 or other general-purpose type; 1—crystal, 3.579545-mc series-resonant type; 1—s.p.s.t. switch; 1—chassis, approximately 3 x 8 x 12 inches; 1—color wheel (to be described in following article); 6—9-pin miniature socket; 2—7-pin miniature socket; 1—octal socket.



Camera setup to televise important information from the cyclotron.

## VIEWING CYCLOTRON TARGETS

By A. A. SCHULKE

**A**N unusual application of industrial television has been made at Washington University, St. Louis. A TV camera (see photo) faces the target side of a cyclotron and is focused on the irradiation chamber containing the target. The video output of the camera is coupled to a standard TV receiver (see photo) at the control desk through a single 72-ohm coaxial cable about 180 feet long. The line is tapped at other points for monitors used in different parts of the laboratory.

The camera uses a standard movie camera lens but was equipped with a 3-inch f1.9 telephoto lens to keep it far enough away from the stray field of the cyclotron magnet and still have a close-up view of the target. A magnetic field as weak as 15–20 gauss produced objectionable picture distortion.

Initially, the scientists were concerned that the intense neutron and gamma radiation from the cyclotron might cause scintillations in the camera phosphor, but that did not occur.



The viewing position. An ordinary television receiver is used as monitor.

# 1956

## TELEVISION'S YEAR OF DECISION

By DAVID LACHENBRUCH\*

**T**ELEVISION ends its first decade of commercial existence with a success story unmatched in any industry. Starting from zero in 1946, in 10 years it has become a major industry. There are now more than 36,000,000 TV sets in the hands of the public, representing a total investment—when you count initial cost, antennas, installation, servicing—of nearly \$16,000,000,000. And today well over 90% of the American population is within viewing range of at least one of the nearly 500 television stations.

Impressive as TV's report card is, it's not an all-A average. There have been failures along with the successes. Some important decisions must be made in 1956, and they may determine the extent of American television's future growth. These decisions, which will be made in Washington by the Federal Communications Commission, will directly affect the future character of television, the design of TV sets and the number of channels which will be available in your own home town or city.

This question will challenge the FCC in 1956: Is the television allocation plan a failure? The allocation plan, a blueprint for TV's growth adopted in 1952 after years of study, contains geographical assignments for more than 200 stations on 82 channels. But the rapid growth of new transmitting stations seems to be slowing down to a walk at around the 500-mark. And worse—even during TV's "boom" period, more than 50 stations have been forced to leave the air.

### The "good" and "bad" channels

By 1955, it had become obvious that there were "good" and "bad" television channels. A "good" channel is a v.h.f. channel in a market with enough population to support a station of the relatively elaborate design required by the FCC.

Channels 14 to 83 in the ultra-high

\* Associate editor, *Television Digest With Electronic Reports*

territory were opened to TV settlement in 1952 because the FCC realized that in television—as in any industry—there must be competition to maintain economic health. It wanted competition between stations and between networks for the viewer's favor, and it wanted to give the viewer a choice between as many channels as possible.

But this competition didn't come, in most areas—because a u.h.f. station just cannot compete with v.h.f. outlets. The public just will not bother to buy converters or new sets to receive the u.h.f. channel. It was the lesson of FM all over again, as John Q. Public demonstrated his distaste for converters, gadgets and extra installation charges. And without the big audiences made possible by mass set circulation, neither the networks nor the advertisers found it profitable to use many of the u.h.f. stations.

There have been some notable exceptions to this rule, however. U.h.f. stations were welcomed by the public wherever there was no v.h.f.—and hence no conversion problem. Some u.h.f. stations have gained a good foothold where they have one v.h.f. competitor. But where there are two or more v.h.f. stations—zowie!

In 1954, 31 ultra-high stations went broke and quit operating; in 1955 about 20 more. Nevertheless, there are still more than 100 u.h.f. outlets on the air. A recent FCC study found only 18 of these operating at a consistent profit, most of them in areas without any v.h.f. stations.

Should u.h.f. be encouraged or abandoned? Is there an available substitute for u.h.f. or is time the only cure for television's biggest headache? No one has come up with an answer.

### Congress, RETMA & FCC

The problem is being tackled at three different levels. The FCC has asked for industry's advice on whether to scrap the old allocation plan and substitute a new one. With the FCC's blessing, the

Radio-Electronics-Television Manufacturers Association set up its Frequency Allocation Study Committee to investigate the whole allocations situation and advise the FCC. In a preliminary report, RETMA's study committee urged the commission to save u.h.f. and refuse to scrap the allocation plan. Serving on this committee are seven top executives of TV transmitter and receiver manufacturers, under the chairmanship of General Electric's electronics vice president, Dr. W. R. G. Baker. He is known for his work as chairman of the first and second National Television System Committees, which devised the present standards for both black-and-white and color TV.

Attacking the problem from the engineering standpoint is the Allocations Engineering Study Committee, headed by Prof. Edward Bowles of MIT and comprising the industry's top engineers. This committee was established by Senator Warren G. Magnuson, chairman of the Senate Interstate and Foreign Commerce Committee. He has promised full-scale hearings on allocations early in 1956.

While a number of proposed solutions have been advanced, they all boil down to three basic plans. The FCC must choose between them or perhaps select a combination. Each has its drawbacks.

### Solution by "de-intermixture"


Proponents of "de-intermixture" point out that there's nothing wrong with u.h.f. except when it's placed in *direct competition* with v.h.f. Their proposal: Rejigger the allocation plan so that each market is either all u.h.f. or all v.h.f.

Opponents of this proposal say that to be effective it would require a completely new allocation plan, with tremendous expense to the public and to existing stations—and that even then it wouldn't work very well, because there will always be areas where high-

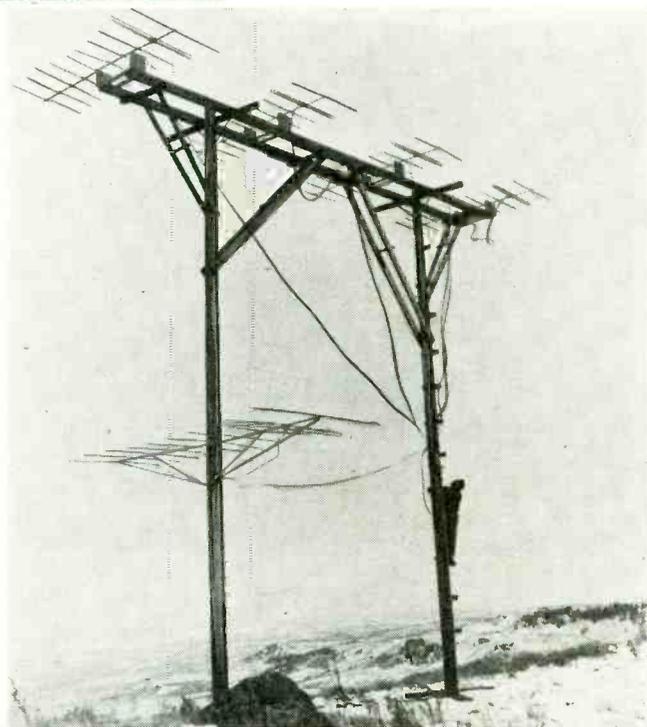
## TELEVISION



This unlicensed booster serves Bridgeport, Wash. Note complete transmitter on pole.



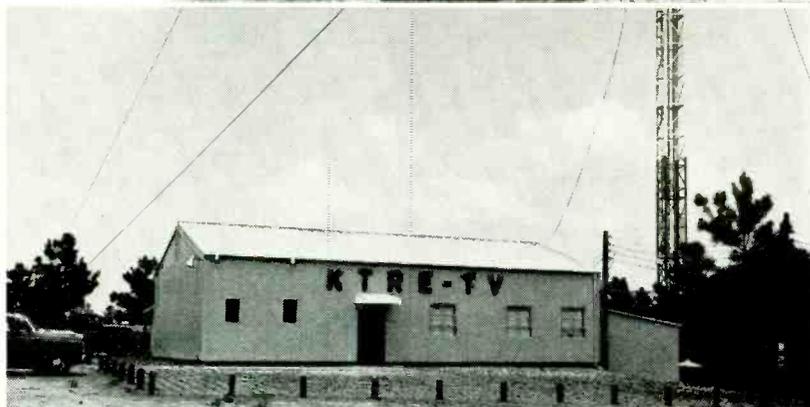This array of Yagis cut to Spokane's frequency feeds illegal booster transmitter.



KTRE-TV, channel 9 Lufkin, Tex., one of the country's most elaborate repeaters. A satellite of KPRC-TV of Houston, its power is 25 kw, antenna height 540 feet.

powered v.h.f. signals will come barging into "u.h.f.-only" territories. For example: Though Allentown, Pa., might be a "u.h.f.-only" area, a good signal from "v.h.f.-only" Philadelphia could easily be received there.

The FCC has already rejected all pending petitions to "de-intermix" individual areas, insisting that de-intermixture should not be attempted on a piecemeal basis.

### New v.h.f. channels?

Another school of thought—which has two of the seven FCC commissioners as adherents—argues that the only long-term solution is to abandon u.h.f. and get hold of more v.h.f. channels. They would pick up part of the spectrum immediately above channel 13, and carve out anywhere from 12 to 40 new v.h.f. channels. They argue that this band is largely occupied by Government and public service radio, much of which could be moved to the u.h.f. band.

Experts on military radio say this plan is doomed. FCC has no direct control over Government use of the radio spectrum and it is almost inconceivable that the Armed Forces would let go of their v.h.f. channels, which are becoming increasingly useful to national defense as a result of the development of new ultra-reliable long-distance v.h.f. radio communications techniques. Another strong argument against the "new channels" plan is that it would have the same major drawback as u.h.f.: existing receivers would have to be converted to get the new television channels.

Nevertheless, leaving no stone unturned, the FCC has already asked the Office of Defense Mobilization how many v.h.f. channels the military can spare—if any.

A proposal which has gained some favor recently is the "v.h.f. drop-in" or "shoe-horn" plan. This would involve putting more stations on the current 12 v.h.f. channels, squeezing them into locations where they are not now assigned. To minimize interference with existing stations, the "drop-ins" would be forced to use low power, directional antennas and perhaps vertical antenna polarization. Existing v.h.f. outlets wouldn't be changed, but existing u.h.f. stations might be given first priority on the new v.h.f. "shoe-horn" assignments.

Some drawbacks are apparent in this plan, too. It would almost certainly mean writing off u.h.f. as dead. Stations on the same channel would be located nearer to each other than at present—and there would be an interference problem. There still would be no equality among stations, since the newer "dropped-in" stations would be limited to powers as low as 5 kw, while the older outlets could continue at maximum power. But perhaps the plan's biggest deficiency is that it wouldn't provide enough channels to give most viewers a choice between three different stations.

### Boosters and satellites

As a partial answer to the problems of u.h.f. and the demand for television service in areas too small to support full-fledged stations, the FCC in 1955 paved the way for small "repeater" stations which can be set up for a fraction of the cost of a complete TV station.

For the first time, it authorized "satellite" stations—outlets which don't have their own studios but pick up the signals of a "mother" station and re-broadcast them on another channel at effective radiated powers as low as 100 watts. Satellites are now permitted on both the v.h.f. and u.h.f. bands. A handful have already gone on the air in relatively sparsely settled areas. A slow but steady increase in satellites may account for the larger part of TV station expansion in 1956.

An even less expensive type of repeater service has been proposed by the FCC and may be inaugurated within the next few months. This is the "booster station" or "amplifying transmitter," which re-broadcasts on the same frequency as the mother station (see "Booster Transmitter Increases TV Station Range" *RADIO-ELECTRONICS*, January, 1954). To help u.h.f. stations, the FCC has proposed that boosters be used to fill in holes and shadow areas within normal coverage circles of u.h.f. outlets only.

Boosters and satellites may be the key to a new TV expansion boom—into the smaller towns. A complete booster station will sell for as little as \$12,500, as compared to about \$100,000 for a not-very-elaborate full-fledged TV station equipped with studio, live cameras, etc.

One leading manufacturer estimates that nearly 1,400 low-power repeaters may be built in the next five years—including 375 satellites with powers up to 10 kw or more, 600 of 100–200 watts, and another 140 low-powered boosters.

### "Unlicensed radiator" headache

There's no question that low-priced and low-powered boosters have a tremendous potential. Proof is easily found in the epidemic of "unlicensed radiators," which have sprung up in the far Northwest. Though the FCC has tried to crack down on these tiny TV boosters, they continue to multiply like rabbits—and it's a good guess that there are now as many as 200 of them in operation in Washington and Oregon alone.

A typical illegal booster might be found on a hilltop near a small isolated town and might consist of a Yagi receiving antenna, a small low-power transmitter (often less than 1 watt and of the type used by wired community TV systems) and a transmitting antenna—just enough to pull the signal over the mountain top and aim it at town. They operate completely unattended.

Their origin is in the desire of people in small and remote communities to have television. They are generally

operated by public-spirited citizens; often they are financed by community subscription.

So important have these "TV coffeepots" become that Senators and Congressmen from the far Northwest are spearheading a drive to legalize them. The FCC argues, however, that these stations can't be licensed because they are operating on frequencies not allocated to their areas, they may be causing interference to other radio services and they don't conform to the high engineering standards required of TV stations.

### Pay-as-you-see television

The FCC is determined to try to cure its allocation headache before it gets around to such issues as subscription television—which, despite heavy publicity, isn't considered a particularly pressing item on the agenda. But because the whole idea of fee TV is highly controversial, it may well be decided in Congress rather than by the FCC. At any rate, this issue isn't likely to be decided this year.

### A colorful 1956

Though allocations problems may

well slow down television's expansion into new outlets in 1956, another dimension of expansion will be just beginning. After several false starts, color TV may really begin to roll by the end of the year.

More than 75% of the population is now within range of a color TV signal, and the networks are providing more than two hours of color programming a day. This should be enough to spur the traditional American demand for something better.

The high price tag on color sets is the major barrier. While sales of color sets in 1956 won't be impressive except by comparison with 1955, they will be sufficient to make possible real mass production. As a result, prices of color receivers should drop to more realistic levels in 1957.

As 1955 closes and 1956 begins, television's biggest problems rest squarely on the shoulders of the FCC. The industry's past has been impressive and its future looks colorful. But the pattern of television's expansion into a multiple-channel service for all the towns and villages of America is due to be determined in 1956 by the regulators in Washington. END

## UNUSUAL SYNC TROUBLE

**T**he set was a Motorola TS88. The owner phoned and said that his set worked well except for the picture tube going blank intermittently. This would occur once or twice an evening for a period of about 30 seconds. All horizontal sweep circuit tubes were replaced, including the damper and high-voltage rectifier. A few days later the owner reported the same trouble, and the set was removed to the shop.

Routine voltage measurements revealed nothing out of the ordinary. The set was allowed to run, and the next day the screen went blank. Touching the cap of the 1B3 indicated very little high voltage, and before any other checks could be made the picture returned. At least, this ruled out an intermittent picture tube.

I then checked the voltage at the grid of the 6BQ6—it matched that indicated in the service information. A few minutes later the trouble recurred and I noticed the 6BQ6 grid voltage increased (became more negative) 8 volts while the screen and cathode voltages remained normal. I suspected the trouble might be in the flyback transformer. This was replaced and a careful check was made of the deflection yoke and its associated components. The set played 2 days and then it happened again.

Deciding to move the chassis to the work bench, I removed the antenna—instantly the picture appeared. I then connected the antenna and the picture disappeared. As I repeated this procedure several times, the picture came on and off as if controlled by a switch.

Fortunately, this time the inter-

mittent lasted for a few minutes, long enough to determine that, when the set was tuned to an unused channel, the picture would appear; when tuned to an active channel, the screen would go blank. Since the trouble occurred with a signal, it appeared that the sync circuit might be affecting the horizontal oscillator.

A scope was placed at the grid of the 6BQ6 with the antenna connected. Picture and waveform were normal. When the intermittent occurred, the horizontal sweep frequency rose to about three times its normal rate; switching to an unused channel restored normal waveform. It was apparent that the defect was in or applied to the horizontal oscillator.

This set uses a 6AL5 phase detector. The scope was applied to pins 5 and 7—only one had the sync signal. I then checked the plate and cathode of the preceding sync splitter—both had sync signals. The trouble had been found. The coupling capacitors from the sync splitter to the phase detector were replaced and the picture was perfect.

Out of curiosity, the capacitors were tested on a capacitor bridge. They checked very well except one would cause the 6E5 "eye" to flicker occasionally. The increase in horizontal frequency was so great that the flyback transformer functioned poorly, developing very little high voltage. Had I observed the grid of the 6BQ6 with a scope instead of making voltage measurements with a v.t.v.m., a great deal of time would have been saved.—*Henry S. Connolly*

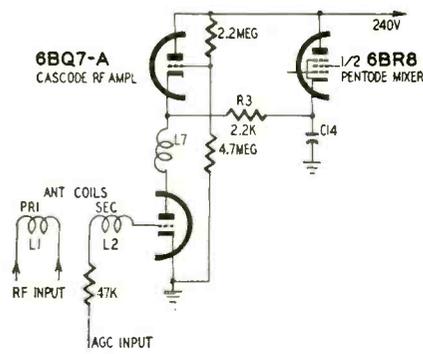


Fig. 1—Simplified schematic diagram of the Standard Coil Rainbow tuner.

*Circuitry and analysis of Standard Coil's new color TV tuner*


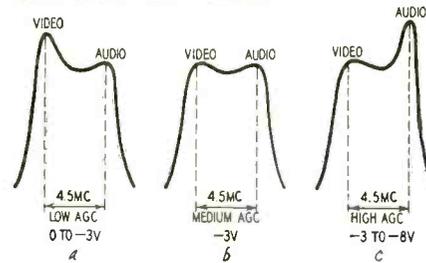


Fig. 2—Diagram shows the tilt characteristics of earlier tuner designs.

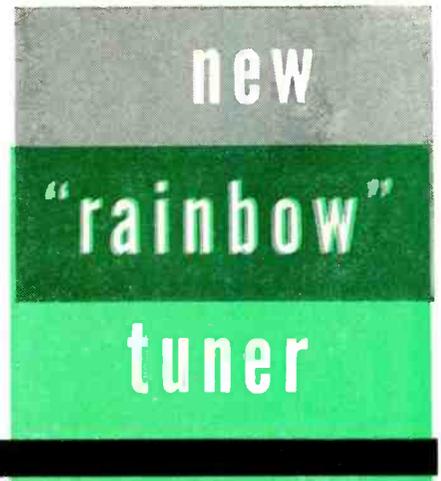

By E. D. LUCAS, Jr.

FRONT ends of television receivers have long been identified by colorful code names both within the industry and in consumer advertising. Thus it is no surprise that Standard Coil Products should introduce a new TV tuner called the "Rainbow."

What is surprising is that just one simple refinement in the well known cascode tuner circuitry should achieve such notable improvements in performance. There are many engineering advances in the Rainbow design. But the major feature is a novel circuit which ties the cathode of the second triode of the cascode amplifier to the cathode of the pentode mixer stage (Fig. 1) so that the two stages operate in parallel so far as d.c. level is concerned and in series with the first input triode of the 6BQ7-A cascode amplifier. As a result, a.g.c. applied directly to the grid of this first triode is also applied indirectly to both the second triode and to the mixer.

The r.f. signal input from the secondary of the antenna coil strip (L2) and the a.g.c. voltage are both applied to the grid of the first triode. As the amount of a.g.c. voltage is increased, over a range from about 0 to -8 volts, the plate voltage of this triode rises while the amplification or gain of this stage is reduced. Since this first triode plate is tied through L7 to the cathode of the second cascode triode and thence through R3 to the cathode of the pentode mixer section of the 6BR8, the two cathodes will also rise in voltage. Consequently the voltage across both the second triode and the pentode will be reduced and the gain of these two stages lowered in proportion.

Thus the basic advances in the Rainbow circuitry consist of relatively simple modifications which result in the indirect application of a.g.c. voltage for gain reduction of both the second cascode stage and the mixer.

**Advantages of new circuit**

1. Improved tilt characteristic over the entire a.g.c. range. Fig. 2 shows typical response curves of previous

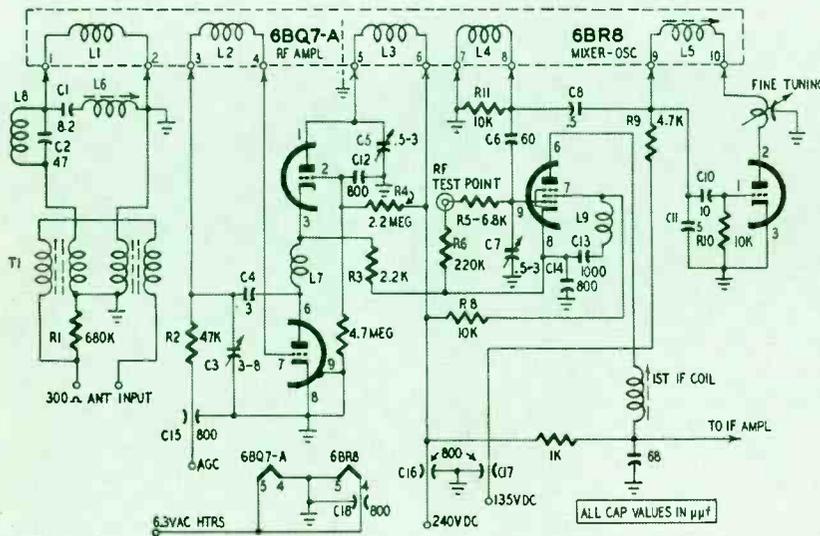


Fig. 3—Schematic diagram of the Standard Coil type TD-B Rainbow tuner.

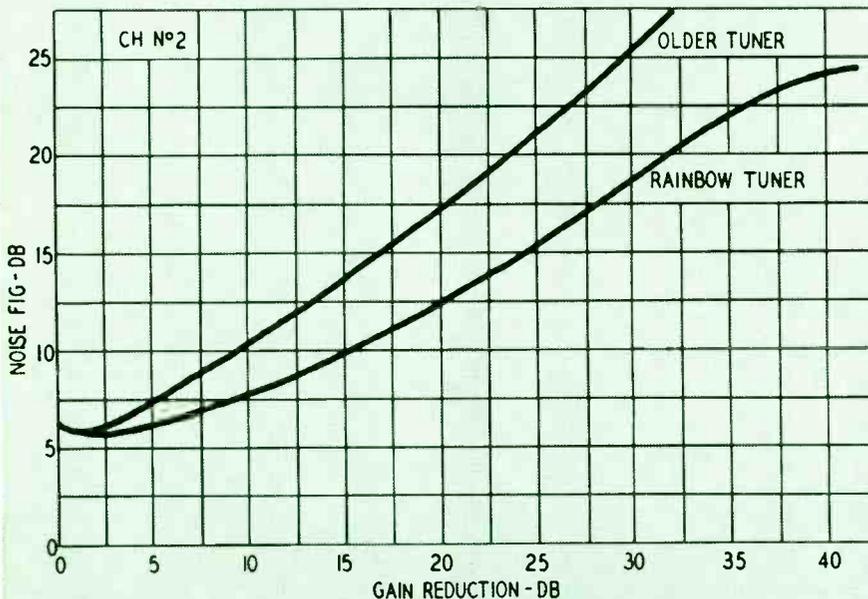


Fig. 4—Graph of noise figure vs. gain reduction in Standard Coil tuners.

tuner designs. With a low level of a.g.c. signal, less than -3 volts, there has been a tendency to peak the video carrier as indicated by the left hump of Fig. 2-a. At the typical alignment bias level of -3 volts there is the desired response characteristic (Fig. 2-b) with two minor peaks for video and audio carriers. Still higher a.g.c. voltage has produced a response like that of Fig. 2-c where there is a marked tilt at the audio end of the curve.

Specifications of color TV receivers require that the amount of tilt be held to within  $\pm 15\%$  over the entire range of a.g.c. voltages. As indicated in Fig. 2 conventional tuner designs have met this specification only in the middle of the a.g.c. range, with resulting deterioration of color reception in areas having either very strong (maximum a.g.c.) or weak (minimum a.g.c.) signals.

The Rainbow circuit limits tilt with bias so that the response curve is maintained well within the required 15% limits. This is accomplished because the new circuit maintains better loading on the first triode grid over the full a.g.c. bias range. Thus, the frequency of the first tuned circuit is not shifted nearly as much as in previous cascode or pentode circuits.


While the Rainbow circuit is among the first to meet the frequency response requirements of good color TV reception, it also has advantages in black-and-white reception, especially where there are wide variations in signal level.

2. Improved voltage standing wave ratio vs. a.g.c. Maintaining a low v.s.w.r. is important; particularly in color reception. Installations with long antenna lead-ins often make the problem of receiving acceptable color pictures acute, since the bandpass characteristics of the receiver's front end may be badly distorted by reflections.

A separate antenna primary coil L1 is tuned for minimum v.s.w.r. and noise. As shown on the detailed schematic (Fig. 3) separate primary and secondary antenna coils L1 and L2 are used and the loading is increased by 47,000-ohm damping resistor R2. Another achievement is maintenance of better v.s.w.r. with high, medium and low a.g.c. bias.

Tests indicate that the v.s.w.r. of the new design does not exceed 3 to 1 at any a.g.c. bias, while at most signal levels the ratio is no greater than 2.5 to 1. This is helpful not only in maintaining good response to color signals but also in eliminating the smear often apparent in black-and-white reception with changes in signal strength.

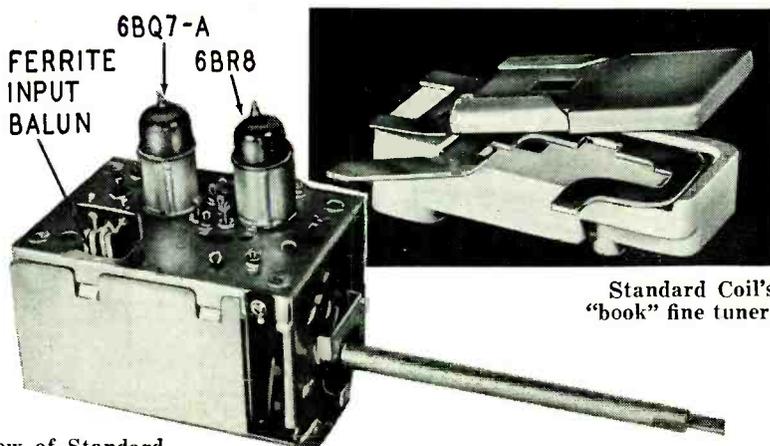3. Improved noise figure vs. gain reduction. This measurement of a tuner's performance is considered by leading engineers to represent a better yardstick than the more frequently used criterion of noise figure vs. a.g.c. The novel a.g.c. circuit in the new Rainbow makes possible lower noise values as the bias increases. With conventional



Overall view of Standard Coil's Rainbow television tuner.

a.g.c. action it has been apparent in cases where the r.f. signal input level was 500 to 1,000 microvolts, for example, that the noise figure of the tuner has increased too rapidly as more a.g.c. is applied—that is, under typical conditions where signal levels are fluctuating and stronger signals result in the appearance of more noise while increased a.g.c. voltage is applied. The Rainbow circuit, by applying a.g.c. not only to the first cascode triode but also indirectly to the second cascode stage and the mixer, limits the noise level so that the noise figure does not rise nearly as rapidly with gain reduction as in previous tuners. (See Figs. 4 and 5.)

This advance helps produce cleaner pictures in both black-and-white and color, except possibly in deep fringe areas.

4. Improved a.g.c. characteristic and much higher maximum gain reduction. With TV stations increasing their effective radiated power, one problem in receiver design has been to maintain good reception characteristics where the signals are extremely strong. Expressed somewhat differently, while TV

reception has been pushed out into fringe areas, much emphasis has been on increased sensitivity, high gain and low noise of the receiver front end. Now the same tuner must be capable of handling very high signal levels for receivers close to transmitters which have stepped up their power.

Previous tuners have been able to produce a maximum gain reduction of about 54 db with maximum a.g.c. signal applied. By comparison, the Rainbow circuit with a.g.c. applied to both parts of the cascode and the mixer achieves a gain reduction of 80 db and higher. (See Figs. 5 and 6.)

In a recent test with a popular 1956 television receiver, the i.f. a.g.c. was deliberately shorted and a relatively tremendous input signal of 0.2 volt r.f. (200,000 microvolts) was fed into two identical receivers, identical except that one tuner was conventional and the other the new Rainbow. With the old-style tuner this signal level literally swamped the picture, sync was lost and the set was completely overloaded. The Rainbow presented a clean picture.

One advantage which Standard Coil

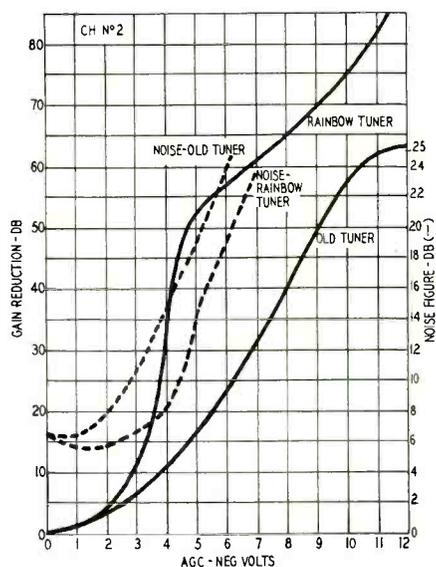


Fig. 5—Gain reduction and noise figure vs. a.g.c. in Standard Coil tuners.


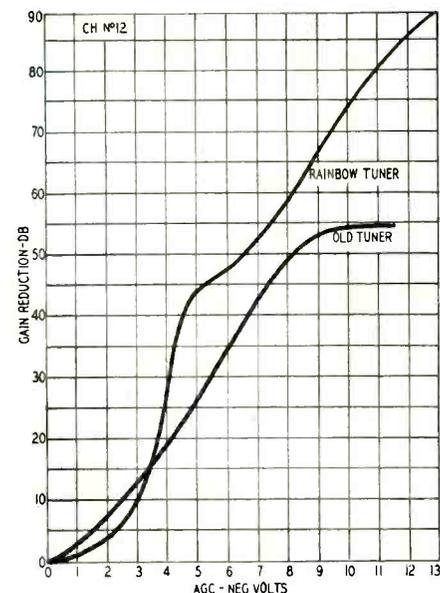


Fig. 6—Graph of gain reduction vs. a.g.c. in Standard Coil tuners.

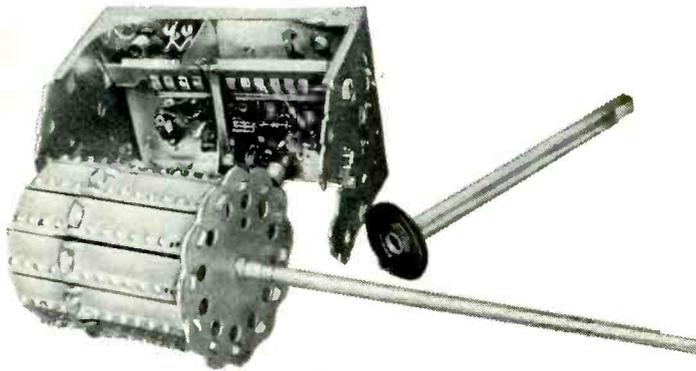
## TELEVISION

Below—Underside of Rainbow tuner showing the coil drum and fine-tuning control.

Right—Closeup of the Rainbow underchassis.



## BALUN

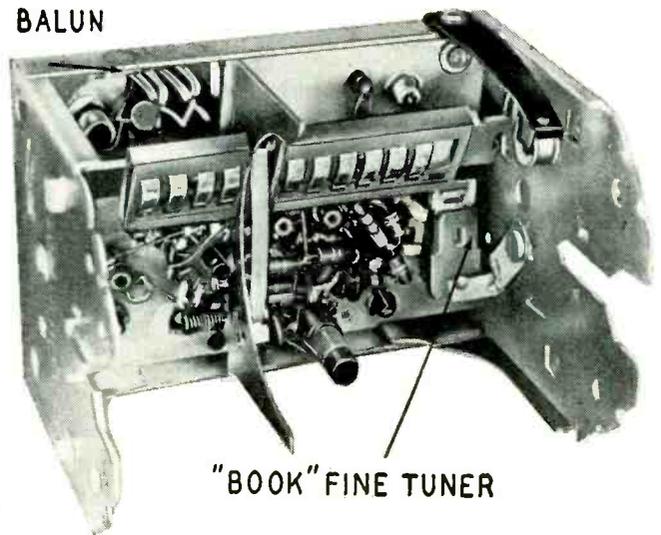

"BOOK" FINE TUNER

engineers believe will result from this feature of increased maximum gain reduction is that TV set manufacturers can probably simplify their i.f. amplifier design. While it has not been desirable to use a two-tube i.f. amplifier strip because a.g.c. can be applied only on the first stage, and hence very strong signals have overloaded the previous tuners and two-stage i.f. designs, the fact that the Rainbow offers up to 80 db or more of gain reduction in the presence of extremely high inputs means that it should now be possible to get good reception with a two-stage i.f. strip.

5. Elimination of delayed a.g.c. in receiver i.f. design is now possible because of the marked improvement in noise figure vs. gain reduction achieved by the Rainbow circuit.

### Design details

Starting with the antenna input (Fig. 3), the input circuit consists of a novel ferrite balun—from the 300-ohm balanced antenna lead-in to an unbalanced 300-ohm input to the tuner. This circuit provides isolation from d.c. voltages or 60-cycle a.c. without the need for additional capacitors. Hence it is particularly useful with a.c.—d.c. receivers. (Standard Coil is now supplying the industry in quantity with similar ferrite baluns for 300-ohm balanced to 75-ohm unbalanced lines for coaxial cable installations such as community TV systems.)

From the input balun the signal goes through improved 41-mc i.f. traps, the parallel circuit of C1 and L6 and series circuit C2 and L8.

There is a separate antenna primary coil L1, for each channel.

Separate primary and secondary antenna coils L1 and L2 are inductively coupled so as to obtain the best v.s.w.r. and noise figure. The r.f. signal from secondary L2 is fed to the grid of the first cascode triode, pin 7 of the 6BQ7-A, along with the a.g.c. signal coming through grid damping resistor R2 and bypassed by C15, a bypass capacitor that prevents radio frequencies from

feeding back into the i.f. a.g.c. circuit.

Neutralizing capacitor C4 is used in this first triode stage to obtain an improved noise figure and to maintain minimum tilt with bias. Trimmer C3 compensates for variations in the input capacitance of the tube.

Peaking coil L7, connected between the plate (pin 6) of the first triode and the cathode (pin 3) of the second cascode triode, is used to obtain optimum gain on the high v.h.f. channels.

Isolating resistor R3 couples the cathode of the second triode with the cathode of the pentode mixer. Capacitor C14 grounds the mixer cathode for r.f. signals. Here is the circuitry which represents the major advance of the Rainbow design: the second cascode triode and mixer are in parallel so far as d.c. voltage is concerned, and the two are then in series with the first triode.

In the grid circuit of the second triode, R4 is a 2.2-megohm dropping resistor from B plus and an additional 4.7-megohm resistor is connected between the grid and ground to form a voltage divider. This second resistor was added to reduce the gain of the tuner more sharply with increase in a.g.c., since now this grid (pin 2) becomes negative with respect to the cathode (pin 3) when the cathode voltage exceeds about 164.

Bypass capacitor C12 grounds the grid of the second cascode stage for r.f. Trimmer C5 is similar in function to C3; it compensates for variations in output capacitance of the tube.

The coupling circuit, coils L3 and L4, provides inductive overcoupling controlled to obtain optimum bandpass characteristics. The signal from L4 goes through coupling capacitor C6 to the first grid (pin 9) of the pentode mixer, part of the 6BR8. This tube is a specially rebased 6U8 designed to facilitate the tuner wiring layout.

While discussing tubes, a version of the Rainbow tuner is being produced with the 4BQ7-A and 5BR8 instead of the 6BQ7-A and 6BR8, respectively, for TV receiver chassis with 600-ma series-heater circuits.

Loading resistor R11 in parallel with L4 is used to limit the peak-to-valley ratio of the response curve of the cascode amplifier output.

Resistors R5 and R6 form a voltage divider for the r.f. test point, to see this response curve. When looking at the r.f. bandpass at this test point, it is essential to use an 80- $\mu$ f electrolytic capacitor connected between the pentode mixer cathode and ground—that is, in parallel with C-14—to eliminate hum and distorted 60-cycle response. Capacitor C7, like C3, is a trimmer to compensate for varying input capacitance.

In the pentode screen grid circuit, C13 is a bypass capacitor for r.f. while L9 is an inductance that raises the input impedance of the mixer grid on high-band v.h.f. signals.

The B-plus supply for the oscillator is 135 volts instead of about 240. Compensating capacitors C10 and C11 in the grid circuit maintain a minimum of oscillator drift. The well-known slug-tuned oscillator coil L5, is adjustable from the front for each channel.

An innovation is the "book" type fine tuner (so called because it appears to open and close like a book, with its loop and flap) which provides both inductive and capacitive tuning (see photo). It is in the tuner chassis, and three finger springs are grounded on the center disc so that local oscillator radiation is maintained well within RETMA specifications. Another important advantage in performance is that, by providing both inductive and capacitive tuning, the book fine tuner has a range of 2.5 to 3.5 mc per channel over the whole v.h.f. band from channel 2 to 13. The inductance is particularly useful in restricting the fine-tuning range on the high channels; the capacitance helps restrict the fine-tuning range on the lows.

The author wishes to thank Robert Eland, chief engineer—research, for assistance with the text, and James Brown, chemical engineer, Standard Coil Products, Inc., for the photographs illustrating this article. END



# TV RECEIVER DESIGNS IN 1955

By H. P. MANLY

**T**HE accompanying bar graphs show a cross-section of monochrome television receiver design in 1955. Lengths of bars correspond to relative importance or popularity of 165 types of circuits and components.

The graphs are derived from chassis marketed as 1955 models by 28 major manufacturers. Where the same maker produced chassis with numerous important differences in design the types are considered separately. In arriving at percentages for picture tubes, tuners and some other features, consideration has been given to various kinds offered on either the same or different chassis. The minimum number of models analyzed for any one classification in the table is 60 and for some classifications the number of models approaches 100.

The number of times each design feature appears is represented as a percentage of the total number of chassis and by the length of a graph bar. Bars not so joined relate to minor features. Percentages are to the nearest values which avoid fractions.

In many classifications variations are not separately listed. As examples: Most a.g.c. rectifiers are tubes but some are crystal diodes. There are a number of varieties of plate-grid-coupled multivibrators for vertical deflection, differing in connection of hold and linearity controls as well as in other details.

There are simplified circuit diagrams for a number of features referred to. These illustrate easily recognized or distinctive characteristics but are not complete operative circuits. Numbered notes explain the meanings of some classifications.

It is interesting to pick out the most used design or component in each group, or for each function, and thus arrive at what might be called the average television receiver of

1955. A listing of designs least used might add up to the most obsolete composite or else the one most advanced, depending on whether the features are on the way out or in.

It is interesting also to look for once-familiar designs which have disappeared or nearly so. A few of these are shown by zero percentages. Even more important to the service technician or student is the appearance or the growth in popularity of designs looked upon as novelties not too long ago. These include such things as contrast control on the picture-tube input, new sound take-offs and gated-beam demodulators, pentagrid tubes in the sync section and many others.

DESIGN FEATURES	Percentages
<b>Picture Tube</b>	
Nominal size	
14 inches	2
17 inches	18
21 inches	69
24 or 27 inches	11
Envelope	
All glass	99
Metal cone	1
Face shape	
Rectangular	100
Round	0
Face plate	
Spherical	91
Cylindrical	9
Viewing screen	
Aluminized, metal-backed	50
Others	50

# TELEVISION

## DESIGN FEATURES

## Percentages

Focus	Percentage
Electrostatic	
Fixed voltage	36
Voltage choice (Note 1)	18
Adjustable voltage	10
Magnetic (Note 2)	36

Small Tubes (Exclusive of Power Rectifiers)	Percentage
Number of tubes	
14 to 16	48
17 to 20	44
21 or more	8
Sections in tubes (Note 3)	
18 to 21	24
22 to 25	50
26 to 30	26
Tuners	
Channel selection	
Turret	58
Incremental or switch	42
Frequency bands	
V.h.f. only	46
V.h.f. and u.h.f. (Note 4)	54
R.f. amplifiers	
Cascode	79
Pentode	21
Triode	0
Mixers (Note 5)	
Pentode	67
Triode	33

## DESIGN FEATURES

## Percentages

I.f. Amplifier Section	Percentage
Number of amplifier tubes	
Two	2
Three	90
Four	8
Interstage couplings (Note 6, Fig. A)	
Trans., single-tuned	77
Trans., double-tuned	6
Single coils, impedance	2
More than one type	15
Intermediate frequencies (mc)	
40 to 50	75
20 to 30	25
Trap type (Note 7)	
Accompanying sound	41
Adjacent sound	48
Adjacent video	11
Traps, total per receiver	
None	15
One	39
Two	26
Three	15
Four	3
Five	2
Automatic Gain Controls	
Voltage obtained from:	
Video detector load	48
Keyed or gated a.g.c. tube	40
A.g.c. rectifier	10
Ratio detector capacitor	2
Auxiliaries	
Clamp or delay (Note 8)	32
Sensitivity adjustment	17
Video detector	
Crystal diode	59
Diode tube (Note 9)	41
Video amplifier stages	
One	80
Two	20

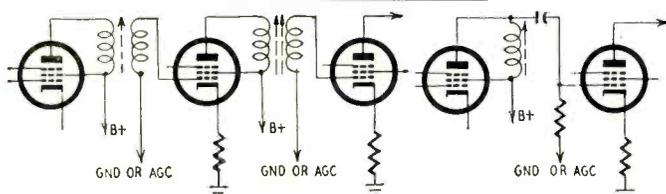


Fig. A—Types of interstage coupling.

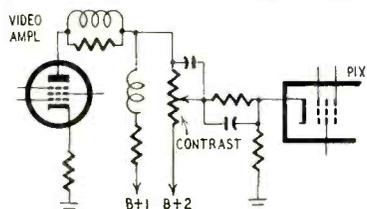


Fig. B—Contrast in input circuit.

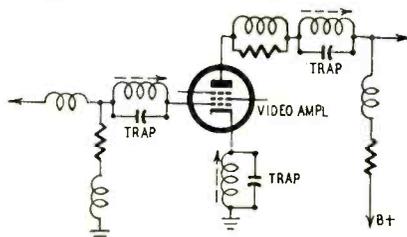


Fig. C—Various 4.5-mc parallel-resonant traps in grid, cathode and plate circuits.

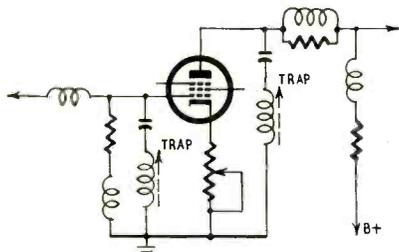


Fig. D—Diagram shows series traps.

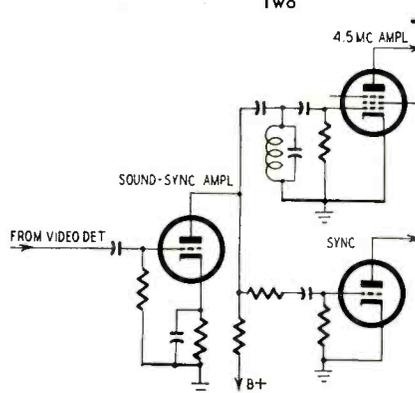


Fig. E—Sound-sync amplifier circuit.

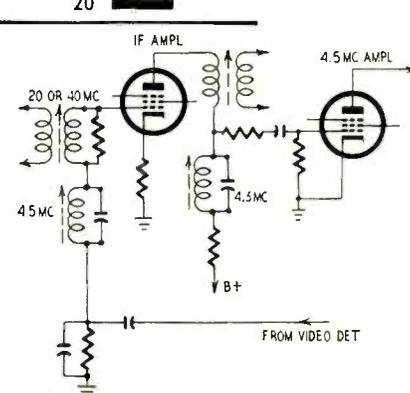


Fig. F—I.f. amplifier reflex circuit.

### Notes

1. Convenient terminals are provided for connection of the focus anode to either of two or more voltages for obtaining optimum performance.
2. The great majority of magnetic focusing devices are of the adjustable permanent-magnet type.
3. The distinction between number of tubes and number of tube functions is desirable because of numerous dual and twin types built into a single envelope. For example, a diode-pentode is one tube and is so counted, but this one tube serves two functions: it may be a video detector and also an i.f. amplifier. As a further example, a receiver might have a total of 18 small tubes, but if 5 of these are dual or twin types, these 5 tubes may serve 10 functions. Then the total number of tube functions in that receiver will be 23, made up of 10 functions served by the 10 duals plus 13 functions served by the remaining single-section tubes.
4. Classification refers to u.h.f. tuners or u.h.f. sections of v.h.f. tuners used as standard equipment. A given chassis with u.h.f. tuning

often serves for one group of models; a chassis otherwise similar except without u.h.f. tuning may be used for other models.

5. A pentode mixer in present-day sets usually is one section of a dual tube whose other section is a triode r.f. oscillator. A triode mixer ordinarily is one section of a dual-triode whose other section is a triode r.f. oscillator.

6. References are to couplings between i.f. amplifier tubes and from the final i.f. amplifier to the video detector.

7. Percentages are based on a count of the total number of each kind of trap in all the receivers taken together. This indicates that there are more i.f. traps for adjacent-sound than for other interferences. But in any particular receiver there might be no adjacent-sound trap while other i.f. traps would be present. In a given receiver there may be almost any combination of kinds of traps.

8. A tube or a tube section commonly called either a clamp or a delay most often is a diode, but sometimes a triode. In most cases the purpose is to maintain a suitable bias on the r.f. amplifier more or less independently of a.g.c.

DESIGN FEATURES Percentages

Contrast control	
Video ampl. cath. resistor	87
Pix-tube signal input (Fig. B)	13
Peakers	
Adjustable	5
Nonadjustable	95
D.c. restorer tube	3
Picture-tube signal input	
To cathode	80
To control grid	20
4.5-Mc Traps	
Parallel resonant (Fig. C)	
Video amplifier plate	44
Video amplifier grid	5
Video amplifier cathode	2
Series resonant (Fig. D)	
Video amplifier plate	2
Video amplifier grid	13
Sound take-off transformer (Note 10)	29
No 4.5-mc trap	5
Transformer (Note 11)	
Video amplifier plate	25
Video amplifier cathode	2
Video detector	2
Capacitor or direct from	
Video amplifier output	34
Video detector output	29
Sound-sync amplifier tube (Fig. E)	5
Reflex in i.f. amplifier (Fig. F)	3

Sound Take-off

Transformer (Note 11)	
Video amplifier plate	25
Video amplifier cathode	2
Video detector	2
Capacitor or direct from	
Video amplifier output	34
Video detector output	29
Sound-sync amplifier tube (Fig. E)	5
Reflex in i.f. amplifier (Fig. F)	3

Intercarrier Sound Section

Amplifiers, 4.5 mc	
None	2
One triode	6
One pentode	64
Two pentodes	28
Demodulators	
Ratio detector	62
Gated beam (Fig. G)	36
Discriminator	2

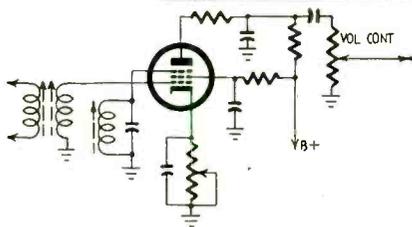


Fig. G—Gated-beam demodulator circuit.

bias on i.f. amplifiers, especially during reception of weak signals.

9. A triode with grid and plate connected together is classed as a diode. Also, a triode in which cathode and grid are used as a diode is classed as a diode. Other diode tube detectors include one section of twin-diodes and the diode section of a diode-pentode.

10. There is trap action in the primary of a sound take-off transformer connected in series with a video amplifier plate lead. Both primary and secondary are tuned to 4.5 mc.

11. The primary of the sound take-off transformer is in series with the tube elements. The secondary connects to the signal input of the 4.5-mc sound amplifier.

12. Other than pentagrid tubes listed below, nearly all sync tubes are twin-triodes or are triode section of other multisection tubes. This classification refers to the total number of such triode sections per receiver.

13. Pulses for horizontal retrace blanking may be obtained from a tap on the horizontal output transformer. Sometimes these pulses pass through an amplifier-inverter tube. Horizontal blanking pulses may be applied to any of the picture tube elements listed for vertical pulses.

DESIGN FEATURES Percentages

Amplifiers	
Beam power tube only	43
Triode and beam tubes	57
Speakers	
Permanent magnet	93
Field coil	7
Audio Section	
Sync Section	
Triodes, total sections (Note 12)	
One	5
Two	47
Three	13
Four	5
Five	2
Pentagrid tube (Fig. H)	
With one triode	24
Used alone	4
Take-off for triodes	
Video amplifier output	82
Video detector output	9
Sound-sync amplifier (Fig. E)	7
D.c. restorer plate	2

Vertical Deflection System

Blocking oscillator (Fig. I)	
Plate trans. feedback	41
Cathode trans. feedback	11
Others	2
Multivibrator oscillator	
Plate-grid-coupled (Fig. J)	38
Cathode-coupled	8
Height control	
Oscillator plate voltage	100
Output amplifier	
Triode	75
Beam or pentode	25
Linearity control	
Amplifier cathode resistor	84
Amplifier grid (Fig. K)	13
Others	3
Output transformer	
Autotransformer	77
Insulated secondary	23

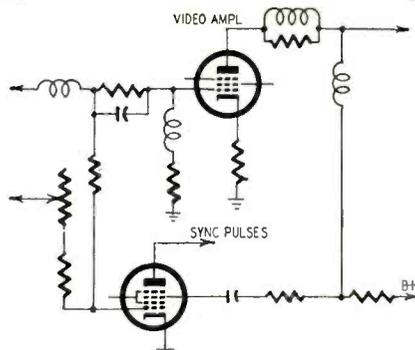


Fig. H—Partial pentagrid sync circuit.

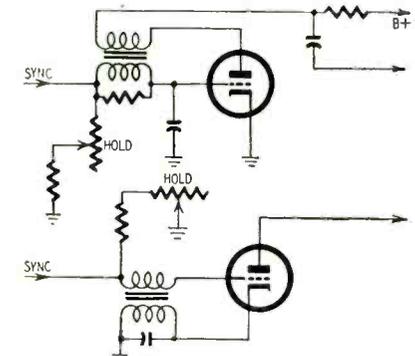


Fig. I—Vertical blocking oscillators.

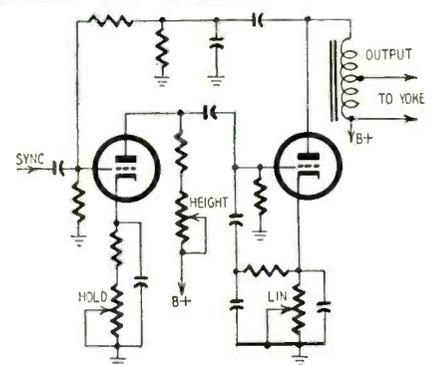


Fig. J—Plate-grid-coupled oscillator.

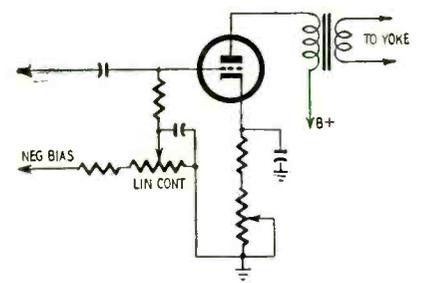


Fig. K—Grid circuit linearity control.

# TELEVISION

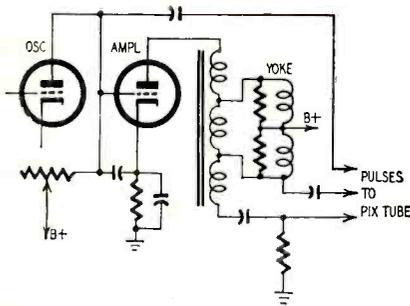


Fig. L—Take-off for retrace blanking.

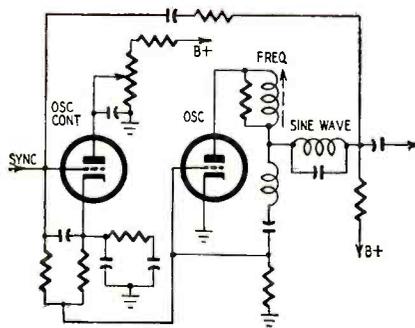


Fig. N—Variable-pulse-width a.f.c.

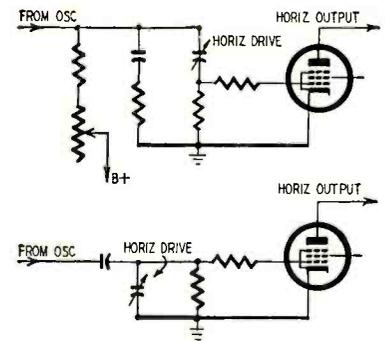


Fig. O—Horizontal drive controls.

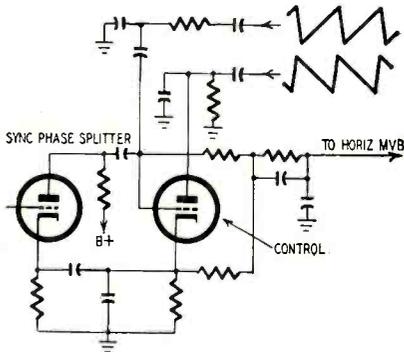


Fig. M—A triode phase detector.

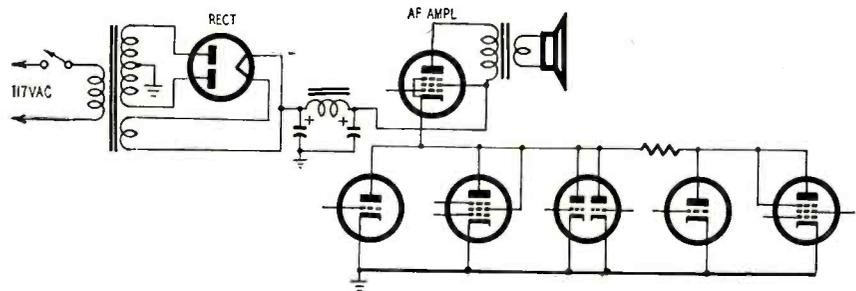


Fig. P—Series type B distribution.

## DESIGN FEATURES Percentages

DESIGN FEATURES	Percentages
<b>Retrace Blanking</b>	
Tracos blanked:	
Only vertical	95
Vertical and horizontal (Note 13)	5
Take-off for vertical (Fig. L):	
Yoke coil	63
Output transformer tap	10
Amplifier circuit	14
Oscillator circuit	13
Vertical pulses to:	
Picture-tube cathode	21
Picture-tube first grid	68
Picture-tube second grid	11
<b>Horizontal Deflection System</b>	
Automatic frequency control:	
Phase det. diodes	33
Phase det. triode (Fig. M)	24
Phase det., reactance (Note 14)	5
Variable pulse-width (Fig. N)	38
Oscillator:	
Multivibrator	57
Blocking	38
Hartley	5
Drive control (Fig. O):	
Voltage-divider capacitors	21
Series capacitor to ampl.	10
Oscillator plate voltage	4
Negative peaking resistor	3
No separate control	62
Output transformer:	
Autotransformer	90
Insulated secondary	10
Width control:	
Inductor on output trans.	48
Amplifier screen voltage	8
Various others	10
No separate control	34

## DESIGN FEATURES Percentages

Linearity control:	
Induction damper circuit	33
Others	5
No separate control	62
<b>High-Voltage Supply</b>	
Type:	
Flyback or pulse	100
Radio-frequency	0
Rectifier tube:	
Octal	74
Miniature	26
Anode kv (approx.):	
12 to 14	29
14 to 16	56
16 to 18	11
18 to 20	4
<b>Low-Voltage Supply</b>	
Power rectifier tubes:	
One	44
Two, paralleled	17
Two, different voltages	3
Selenium power rectifiers:	
One	5
Two, voltage doubler	31
Power filter:	
Choke	84
Spkr. field or focus coil	8
Resistance-capacitance	8
B current distribution:	
Direct to all tubes	46
Series plates-cathodes (Fig. P)	54
Tube heaters:	
Parallel on power trans.	64
Parallel on heater trans.	10
Series, ordinary tubes	6
Series, controlled warmup (Note 15)	20

14. This method is similar to the earlier one using a discriminator, reactance tube, Hartley oscillator and discharge tube, but has a phase

detector instead of a discriminator for correction voltage.

15. This classification includes tubes designed

especially for series heater strings. All cathodes reach normal emission within approximately the same time after voltage is applied. END

By GUY SLAUGHTER



it's  
a  
matter  
of

# Psychology

I COULD hardly believe my eyes when Buzz Maloney walked into my shop. We'd been swapping Christmas cards ever since we got out of service, but we hadn't seen much of each other in all that time. Right now, his face was as long as a channel-2 dipole. He was wearing a sharp-looking tweed suit, but his shoulders drooped under the padding.

"What brings you to my town?" I asked, after the first greetings were over, "and what's eating you?"

"I'm dead, Sid," Buzz informed me, pushing a TV chassis aside and sitting down on my bench. He stared at me mournfully. "An hour ago I got off the train a happy and carefree advertising man. Now I'm a bum and I'm dead."

"Okay," I said, reaching for a cigarette and hoisting myself onto my high stool. "When you get around to it fill me in and we'll both weep."

"Please, no comedy," Buzz moaned. "I'm not in the mood. You familiar with the Mister Typical TV Tech promotion?"

I told him I was. Every radioman in the country had entered the thing a couple of months ago. It was written up in all the technical magazines and the prizes were worth trying for. There was service equipment, hi-fi apparatus, ham gear and even a trip to Hawaii for the winner, if winner is the right word. It seems that all the entries were to be run through IBM analyzing machines and qualifications of the entrants averaged. Then the one guy in the United States who most nearly represented a compromise among all TV technicians in age, height, weight, background, education and a hundred other things—a sort of root mean square of the industry—would be crowned Mr. Typical TV Tech and win the jackpot.

"It was my brainchild," Buzz said. "I dreamed it up and sold the idea to

my own agency and then to all the major electronic manufacturers in the country." As a promotion, he went on, up to now it had been a huge success, one of those naturals that—according to Buzz—comes along just once in an advertising man's lifetime! The only trouble was, now that the payoff was in sight, it had pooped out!

The preliminary campaign had been completed, entries received from the forty-eight states, the statistical work done and the winner determined. His name had been released to the sponsoring organizations as well as to the newspapers, magazines, TV and radio news bureaus and even the wire services. All the vast machinery of publicity had been set in motion. The press releases were dated this very day and inside of a few hours the name of Mr. Typical TV Tech would be a household word.

## An uncooperative winner

Buzz—the guiding genius of the whole thing—had just called upon the winner to advise him of his good fortune and to prepare him for the ceremonies coming up tomorrow and had got what amounted to a kick in the stomach. Because the guy, Buzz said, had thought about it for a minute, then coolly announced he didn't want any.

"So here I am," Buzz finished, almost choking by now. "I'm a bum, because the minute the word gets out my agency'll can me. And I'm dead, because every sponsor and every magazine in the country will blacklist me!

"I don't blame 'em," I said. "Everybody involved'll be the laughing stock of the century. Who ever heard of a contest winner refusing his prizes?" I thought about it a minute. "But why? He must be nuts. What reason did he give?"

"It's the trip, mainly," Buzz ex-

plained. "He claims he can't take three weeks off because he's got sets to fix."

"He's got a point, there," I said. And I went on to explain how it is with us shop owners. You've got a good business, you have to take care of it. Get a few customers teed off at you for slow service and pretty soon you're out picking up crumbs with the chickens.

Buzz said he could understand that so he'd promised to hire a technician for the guy and see that business went on as usual in the shop while Mr. Typical TV Tech spent a few days receiving awards and getting his picture taken a couple hundred times and then went off on his trip. But it didn't work. The joker, Buzz sputtered, just insisted he didn't want any other man doing his work and wasn't interested in going to Hawaii anyway. When I suggested they drop the trip and just give the guy the other prizes, Buzz nixed that idea. It was an all-or-nothing deal, he said. Sort of a package affair.

Suddenly I thought of something. "Hey!" I exclaimed. "If all this happened in the last hour and you're here now, this clown must be a local boy. Who is he?"

"Character named George Myers. He's got a shop over on third . . ."

"Yeah, yeah," I cut him off. "I know George casually. He'd rather fix TV sets than eat. Really loves his work." I thought about that for a minute, and then I grinned. "You know what, Buzz? I think I can solve your problem. All we have to do is make him change his mind."

"Sure," Buzz said grimly. "That's all. But I got the impression he's like a three-legged baby. Awful hard to change."

"Leave it to me," I declared. "It's going to cost you some money, though. You've got to hire some people to carry TV sets into George's shop and pay

## TELEVISION

some repair bills that may run into a little moola."

Buzz looked me squarely in the eye for a minute. Then, for the first time since he'd been there, he grinned at me. He said, "Old buddy, I don't know what's running through that nasty mind of yours but if it'll work I'll pay through the nose."

"You probably will at that," I said. "Go hire half a dozen people while I fix up some repair jobs."

While Buzz was gone I rounded up some of the table-model loaners and trade-ins I had in the place and looked them over with a speculative eye. Then I started pulling chassis and gimmicking them. Inside the first one, I soldered a bypass from plate to ground of the second i.f. stage. The next one I modified by carefully dripping a blob of solder between the grid and cathode terminals of the high-frequency oscillator tube socket. I studied the third one for a little while, then removed the can from one of the video i.f. transformers, soldered a jumper between the B plus and plate lugs inside and replaced the can. Inside the high-voltage compartment of the next set, I drew a line with a soft lead pencil across the ceramic between the hot and ground terminals of the filter condenser. I tore into the vertical integrating network in the next chassis, inter-



"... soldered a jumper between B plus and plate leads and replaced the can."

changed two resistors and two leads. I took the back off a sixth set, sprayed insulating compound inside the controls along the rear apron and replaced the back.

By the time I had all the chassis back in their cabinet, Buzz showed up with a string of people in tow. There were four men and two women. I briefed them carefully, assigned them definite times, half an hour apart, to carry their respective sets into George's shop and told each one to absolutely insist on waiting for his set to be repaired then and there. If George told them he

couldn't handle it that way, they were to make a scene, raise the devil and stalk out. They were to report back here with their sets as soon as they finished their assignments. Buzz fixed each of them up with twenty bucks for repair money, promised them generous rewards when they returned and shooed them out the door. Then he turned to me.

### Frustration the answer

"Okay, master mind, what's the gimmick? This George joker refused the jackpot because he had too much work to do. So why do we give him more?"

"Relax, junior," I said, grinning. "We're using psychology on the lad. Do you know what frustration is?"

"Do I know what frustration is?" Buzz bit off, looking sour. "What you suppose this deal has done to me, given me an ego lift?"

"This is different," I assured him. "Give a TV man a coupla dog jobs in a row, it goofs him up. He'll poke around trying to find the trouble and the more he looks the less he finds and the more frustrated he gets. By and by, if he doesn't solve the problem, he's ready to cut his throat. You offer a guy in a spot like that a trip to Hawaii, he'll grab it. Believe me, I know."

"I get it," Buzz said. He looked at me with awe in his eyes. "And those six sets we're sending him are dogs?"

"They're dogs," I said. "Real bowwows. A sharp bench man could fix them all in good time. But likely George'll go batty with six of them lined up on the bench and six customers out front pacing the floor."

"Sid," Buzz said with feeling. "You're a pal." He stuck out his hand, shook mine solemnly.

"Yeah," I said. "Ain't I though? Now you get the heck out of here and hire that helper you promised George, while I get some of my own work done. When you find a man, go offer George that trip again. And this time he'll break his neck accepting."

Buzz left and I dove into my bench work, whistling. It makes you feel pretty good to come up with an idea in the clutch that helps a buddy out of a spot.

I was still feeling good a couple of hours later when Buzz stalked in again. The six fake customers had come in during the interim, one at a time, and I had just waved them into chairs in the front of the shop, not even taking time to talk to them. Now Buzz walked up to me and shook his fist under my nose. I could see his plate current was zooming.

"Thanks a million," he was snarling, his voice thick with sarcasm. "Boy, what a brainy idea that was! I should have known better than to listen to you. Now I'm *really* dead."

"Hey, wait a minute. You mean it didn't work? George didn't fall all over himself accepting when you showed up again?"

"You bet he didn't," Buzz shouted.

"He said he'd been tempted to change his mind right after I left the first time. But he had so much fun and cinched himself so many new customers this afternoon that he wouldn't think of going anywhere now."

"Hold it," I said, sticking up my hand like a traffic cop. "Calm yourself, junior. You mean he... he didn't blow his cork over those six dog jobs?"

In answer, Buzz jerked his thumb at the four men and two women just going out my front door. They had left my six sets in a neat pile in the middle of the room. It seems Buzz had paid them off and dismissed them. It seems, too, that each of them had got his particular set fixed while he waited and that altogether George had collected nearly a hundred bucks of Buzz's money from them. Buzz slammed down the repair bills George had made out. I leafed through them, my mouth open—high-voltage filter condenser, plus 14-minute service charge, \$12... new i.f. transformer, 11 minutes; \$10.90... Six controls replaced, 35 minutes; \$18.75. I laid down the bills, tried to grin at Buzz, didn't make it.

"So thanks for nothing," Buzz was saying. He glowered at me a minute, then spun on his heel and headed for the door.

"Hey," I called. "Where you going?"

"Outer Mongolia, where else?" He grabbed the knob, not looking back, stalked out into the street.

I ran after him. I caught him at the corner, held him by one padded shoulder until he stopped trying to shake free. Then I tried to grin at him again. This time I made it.

"Okay, so I fumbled. I merely underestimated this character, that's all. And you boys missed the boat, too. He's no more an average TV man than you are."

That got Buzz's attention. He looked at me kind of funny, said, "Hunh?"

"Oh, he may be average age," I went on. "And average height and average everything else in the tangible things. But he's head and shoulders above most of us in the upstairs department evidently. That boy's a real technician, maybe the best there is."

Buzz found his voice. "Great," he said without enthusiasm. "And that helps me a lot, doesn't it?"

"Maybe," I answered. "Maybe it does, at that. I didn't know George well enough to realize he was such a hot bench man. Apparently he thrives on tough ones, just loves to work on them."

"Obvious, so I'm dead. He won't leave his work for fear he'll miss some fun. So excuse me while I go bury myself."

### Changing strategy

"Hold it, junior," I said. "Now we know how our boy operates, we can figure it better. I got the deal for you this time."

"Hah!" Buzz looked at me coldly. "Forget it. I dropped a wad of dollars out of my own pocket on your last brainstorm. And real soon my salary stops. Thank you, friend, but no more ideas, please."

"Look, Buzz," I pleaded. "I know TV men. They fall into two general categories, the lazy and mediocre ones like me, and the eager geniuses like this George character. You go along with me on this thing and I guarantee he'll accept your Mr. Typical TV Tech title and the trip to Hawaii. I guarantee it!"

That got him. I led him back still hooked to the shop, briefed him on how many people to hire this time and what instructions to give them. Then I started taking the backs off every operating TV set in the place. I dug up a carton full of discarded tubes, shuffled through them looking for 6SN7's and sorted them into a pile. Then I started switching tubes. I took one out of each set, replaced it with one from the discard pile. When I finished and put the backs on, I had 17 TV sets lined up in front of me. I sat down on my tall stool, lighted a cigarette and waited for Buzz to come back with his little army.

★ ★ ★

I had dinner with Buzz that evening. His face shone like an indirectly lighted dial and he radiated happiness like WLW does r.f.

"So tomorrow morning," he finished,

"when the photogs and PR men move in, George'll be ready for them."

"And the Hawaiian jaunt?" I asked.

"All set. He leaves next Saturday."



"... trip to Hawaii—as spectacular a change as any soul could long for."

Buzz leaned back in his chair, and grinned. "Tell me the gimmick."

"Same gimmick, different twist. My psychology was sound on that first try, but I didn't know my subject well enough. When I found out what kind

of a guy he was, I just had to change strategy a little bit."

"Okay, okay," Buzz responded sweetly. "And pray what was this new tactic that turned the trick?"

"Same tactic, different method. Frustration was the answer, like I said. But this guy is different from most of us and doggy sets don't goof him up. So I figured routine would."

"I don't know what you're talking about," Buzz said. "But rave on, Macduff."

"Routine," I repeated. "Monotony. You know, one-two-three-kick. I sent him 17 TV sets to fix—dull jobs."

"Dull jobs?"

"The dullest," I said. "At least for that type of eager genius. Every set had the same symptoms, which in itself might be interesting. But every one had the same cure, too, and that's the dullest kind of routine. None of the sets had any horizontal deflection. And a new tube cured each one. To any technician 17 consecutive sets with a single and obvious tube defect are dull—to this particular one—downright frustrating! And as I pointed out before, frustration craves change and a free trip to Hawaii is as spectacular a change as any soul could long for."

Buzz sat silent for a long moment. Then he grinned. "You know," he said, finally, "All you TV guys are nuts."

"We don't have to be," I grinned back. "But it helps, Buzz." END

## RADIO-ELECTRONICS readers FOR YOUR PROTECTION—

We will not knowingly permit the advertising pages of RADIO-ELECTRONICS to be used to deceive you! Our success depends on your faith and confidence. Unfortunately, within the past year that confidence has been abused by a few mail-order advertisers.

Therefore, to protect our readers, and the overwhelming majority of honest advertisers who use space in RADIO-ELECTRONICS, this letter was recently sent to all mail-order tube advertisers. It advised them that effective with the January 1956 issue, all their advertising copy must warrant that tubes advertised are

- 1) New and unused
- 2) Not mechanical or electrical rejects
- 3) Not washed and/or rebranded

These regulations will be strictly upheld. We will not accept advertising which fails to comply. We ask the cooperation of both readers and advertisers in calling to our attention any abuses.

**RADIO -  
ELECTRONICS**  
RUBO GERNERBACK, PUBLISHER

GERNERBACK PUBLICATIONS, INC.  
41 WEST BROADWAY • NEW YORK 9 • N. Y. • BR 6-1416

November 2, 1955

Mr. John Jones  
Jones Tube Company  
1024 West River Street  
New York, New York

Dear Mr. Jones:

One of RADIO-ELECTRONICS greatest plus values for advertisers is our readers' faith in the magazine and its advertising pages.

Unfortunately this faith has been abused by a few tube advertisers in the last year. To protect our readers as well as legitimate advertisers, the following advertising regulations will become effective with the January 1956 issue:

All mail-order tube advertisers must state in their advertisements that they warrant

- 1) tubes are new and unused.
- 2) tubes are not mechanical or electrical rejects.
- 3) tubes are not washed and/or rebranded.


We invite your fullest cooperation in carrying out these regulations and request that you instruct your advertising agency accordingly.

Sincerely yours,  
GERNERBACK PUBLICATIONS, INC.  
*M. Harvey Gernerback*  
M. Harvey Gernerback  
President


MAILING

PLEASE ADDIT BUREAU OF CIRCULATIONS

# WHISTLE your set ON or OFF

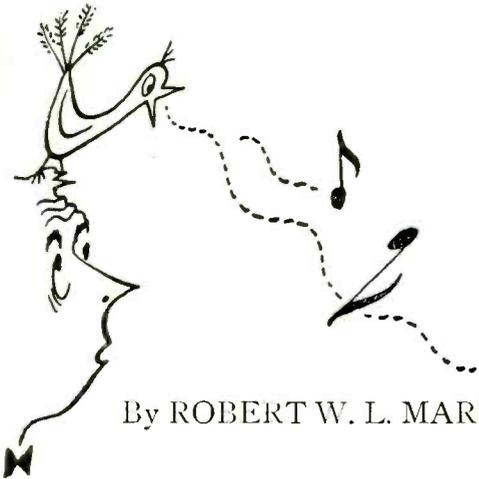

By ROBERT W. L. MARK

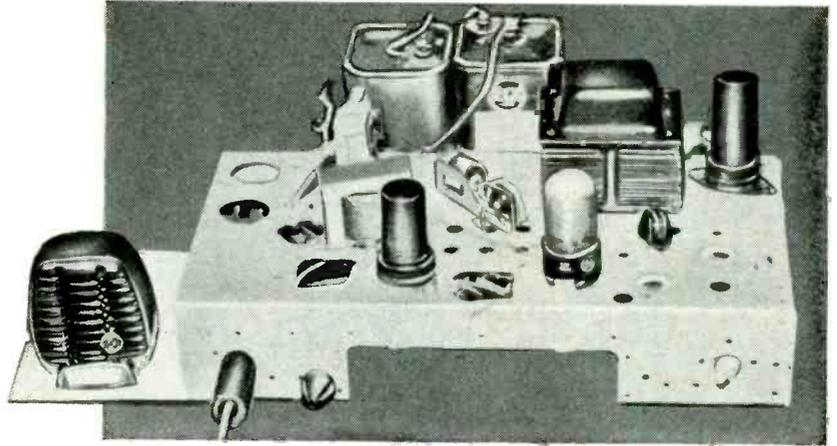

**H**AVE you often wanted to turn off those commercials without having to get out of your comfortable chair to do it? If you have—and who hasn't—here is an electronic remote-control device that will do just that. Give a short whistle and the audio on your set ceases; another short whistle brings it back. This amazingly sensitive device is a source of considerable pleasure and fun.

A crystal mike is placed on top of your TV set facing away from the loudspeaker and toward the audience. In back of the set on a small table or chair sits the electronic device that does the trick. (To make operation more amazing the mike can be placed off to one side so as to be practically hidden.)

The microphone picks up your whistle, which should have a pitch of between 950–1,050 cycles, and amplifies it to operate a relay in the last stage of the set. This relay activates another which makes and breaks a connection to the TV loudspeaker (see diagram).

The remote control device has a resonant audio circuit (L1–C1) between the first and second stages (V1 and V2-a) which makes it respond to the proper pitch of whistle and not to other

sounds in the room or from the TV set itself. L1 is the primary of a universal a.f. output transformer. Adjust the value of C1 for good tone discrimination.

The control unit may be built on an old receiver chassis approximately 12 x 6 inches and parts may be placed where most convenient. The mike may be an inexpensive, high-impedance crystal type.

Two controls are all that need adjusting: R1 for the mike input; R2 for current through RY1. Current through RY1 should be set for around 2 ma, just enough to make the relay close when the unit is turned on. The microphone input should be set to open, with a whistle of the proper pitch, from a distance of 15–30 feet. It may take a little experimenting to get the relay working O.K. The relay contacts may need adjusting too; the closer they are, the more sensitive. If they are too close, though, the relay may chatter.


The plate relay is a Potter & Brumfield type LM5. It has a 10,000-ohm coil and will close on approximately 3 ma and open on anything less than that. The ratchet relay is a 12-volt d.c. type. The contacts on it are connected so that when it moves the

ratchet, the loudspeaker connection is alternately made and broken. Two lantern type 6-volt batteries are hooked in series to provide the 12 volts. (If a.c. type relay is used, power may be obtained from transformer.) They will last a long time since current is taken from them only during each whistle.


One precaution is necessary. The batteries are hooked up so that when relay RY1 is open, current is drawn and the ratchet moves. Since RY1 is normally open, except when the remote control device is turned on and warms up, the batteries will draw up the ratchet relay and hold it there, draining the batteries, unless some way is provided to disconnect them except when the unit is in operation. An alligator clip on one battery terminal will make an easy way to open or close that circuit. Relay RY1 will not close until the power is turned on and all voltages reach their proper level.

To adjust RY1, turn up R2 until the relay closes. By adjusting the screw on the relay it can be made to close on as little as 1.5 ma and open on anything less than that. Mine is set to close on 2 ma, and the action is firm and sure.

END

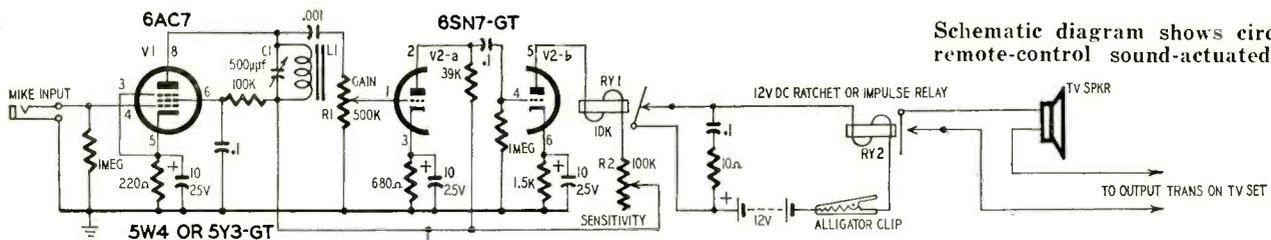

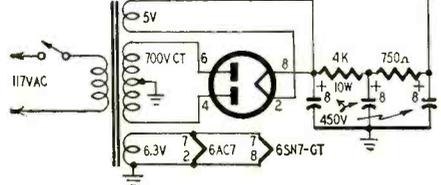Schematic diagram shows circuitry of remote-control sound-actuated switch.



Parts for a.c. remote unit

**Resistors:** 1—10, 1—220, 1—680, 1—1,500, 1—39,000, 1—100,000 ohms, 2—1 megohm, 1/2 watt; 1—750, 1—4,000 ohms, 10 watts; 1—100,000, 1—500,000 ohms, potentiometers.

**Capacitors:** 1—500  $\mu$ f, 1—.001  $\mu$ f, mica; 3—0.1  $\mu$ f, 400 volts; 3—10  $\mu$ f, 25 volts, electrolytics; 3—8  $\mu$ f, 450 volts, electrolytics.

**Relays:** 1—single-pole single-throw normally closed, 10,000-ohm coil, approximately 3-ma sensitivity (Potter & Brumfield LM5 or equivalent); 1—ratchet type,

6 or 12 volts d.c. d.p.d.t. (Potter & Brumfield APIID or equivalent. Suitable 12-volt ratchet relays may be obtained from Lionel Corp.)

**Miscellaneous:** 1—6AC7, 1—6SN7, 1—5W4, tubes; 3—octal sockets; 1—open-circuit microphone jack; 1—high-impedance crystal microphone; 1—power transformer, 700 volts ct. @ 30 or more ma, 5 volts @ 2 amps, 6.3 volts @ 2 amps; 1—s.p.s.t. switch; 1—500-ohm 14,000-ohm impedance audio coil (primary winding of a Stancor A-3823 output transformer or equivalent); 1—chassis.



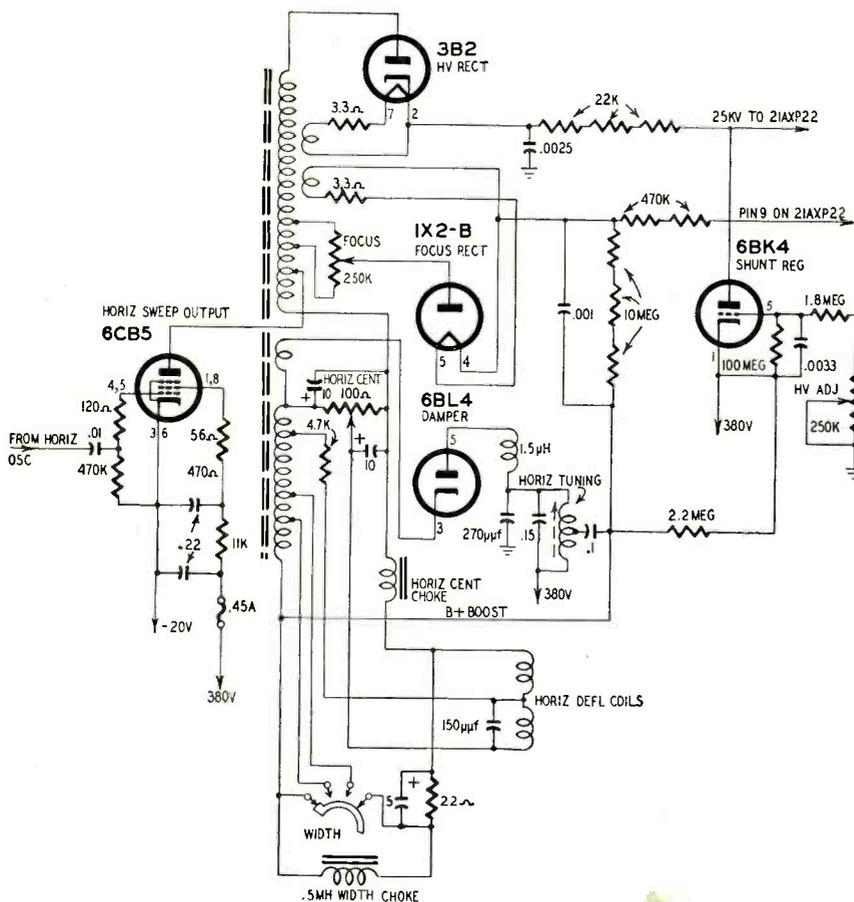


Fig. 2—New tubes in high-voltage circuit of the RCA model 21-CT-661U set.

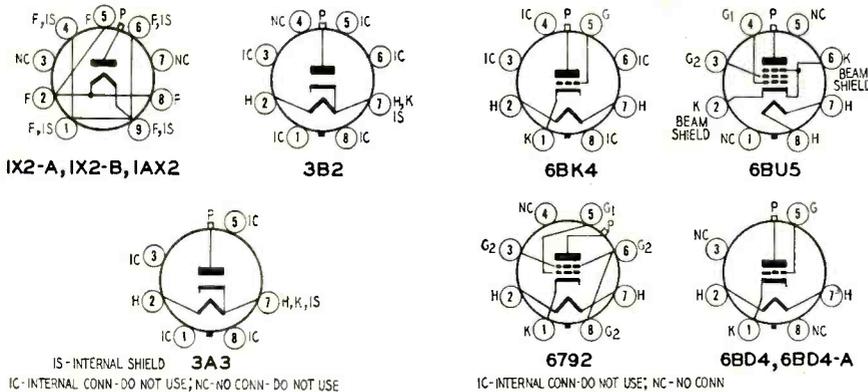


Fig. 3—Diagrams of new high-voltage and focus rectifiers for color TV sets.

Fig. 4—New high-voltage regulators.

and the larger tubes needing approximately 25,000 volts at 800 microamperes, the heretofore dependable 1B3-GT has given way to newer, more rugged types. In addition, it is very important that this high voltage remain fairly constant (good regulation) during beam current variations from cutoff to maximum brightness. This adds a new circuit to the high-voltage power supply, the shunt regulator. Another newcomer to this section is the focus rectifier, supplying a somewhat smaller high voltage.

**High-voltage tubes**

Some early (if we may call 1954 early) TV color receivers such as the Westinghouse model H-840CK15 (chassis V-2284-15), using the 15GP22,

obtained high voltage with voltage-doubler circuits using tubes such as the 1B3, 2V2 and 3A2. These had peak inverse voltage ratings of 21,000, 21,000 and 18,000 at a d.c. output current of 0.5, 1 and 1.5 ma, respectively. Fig. 1 shows the horizontal output and high-voltage circuits in the pioneer of color sets, the RCA CT-100 (chassis CTC2).

Appearing in the later larger-screen sets, the color-TV-designed 3A3 and 3B2 have taken over the task of supplying high voltage for 19- and 21-inch picture tubes. Fig. 2 shows the horizontal output and high-voltage circuits of the most recent RCA color set, the 21-CT-661 (chassis CTC4).

The 3A3 half-wave rectifier has a peak inverse plate voltage rating of 30,000 and can supply an average plate

current of 1.5 ma. The base pins (see Fig. 3) fit a standard octal socket. To reduce corona, the socket terminals for pins 1, 3, 5 and 8 may be connected to pin 7. The heater of the 3A3 requires 3.15 volts and draws 220 ma.


A still more rugged half-wave vacuum-tube rectifier is the 3B2, used in the high-voltage power supply of Fig. 2. This tube is rated to withstand a maximum peak inverse plate voltage of 35,000 while delivering a maximum average plate current of 1.1 ma. The base pins (Fig. 3) of the 3B2 also fit a standard octal socket.

To aid in corona reduction in the 3B2, pins 1, 3, 5 and 7 may be connected together. In addition, pins 2, 6 and 8 may be tied together, pin 4 may be connected either to pins 2 or 7 or used as a tie point for a heater voltage-dropping resistor. Pin 4 cannot be used as a low-potential tie point. Like the 3A3, the 3B2 has a 3.15-volt 220-ma heater. With present picture-tube design, it is very likely that the 3B2 will become the 1B3 of color television.

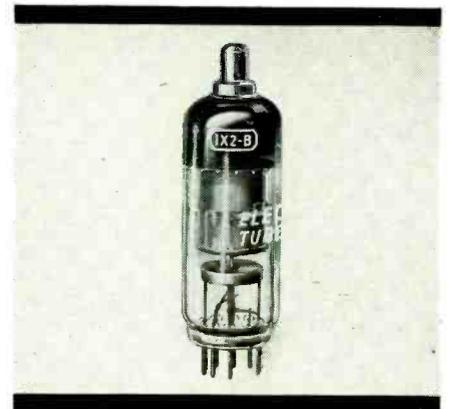**High-voltage regulators**

Used to stabilize the high-voltage output in color receivers, high-voltage regulators are connected in circuits shunting the power supply. Since TV high-voltage regulation is a relatively new function, only a few types have appeared—the 6BU5, 6BD4, 6BD4-A and 6BK4.

The 6BU5, a beam pentode (see Fig. 4), was used in the General Electric model 15CL100, an early color set using the 15GP22 picture tube. The tube is a low-current high-voltage pentode designed primarily for use as a shunt voltage regulator in color TV receivers. Its maximum ratings include a plate voltage of 20,000 and a plate dissipation of 20 watts. The plate lead is brought out of a top cap that has a



circular groove insuring a firm connection. The maximum cathode current rating for this sharp-cutoff pentode is 2.5 ma. Heater requirements are 6.3 volts at 150 ma.

A much more popular (though very expensive) type is the 6BD4, used in the RCA CT-100, Westinghouse H-840CK15, Arvin 15-550KB and Stromberg-Carlson K-1. This tube is a sharp-cutoff beam triode specifically designed for the regulation of high-voltage low-

current d.c. supplies. The 6BD4 has a maximum d.c. plate voltage rating of 20,000 and a plate dissipation rating of 20 watts.

The double-ended tube will pass a plate current of 1.5 ma and has an amplification factor of 1,650. The heater of the 6BD4 requires 6.3 volts at 600 ma. The 6BU5 and 6BD4 have similar electrical characteristics but the 6BD4, being a triode (Fig. 4) and making for simpler circuitry, has been much more widely used.

The 6BD4-A is similar to the 6BD4 with the exception of a few maximum ratings. It is interchangeable with the 6BD4. Its plate voltage is rated at a maximum of 27,000; maximum plate current is 1.5 ma. The plate carries a dissipation rating of 25 watts. The amplification factor of the 6BD4-A is 1,650. This tube, with its higher plate-voltage rating, is found in the CBS-Columbia 205 chassis using the 19VP22.

The most recent of the regulator type sharp-cutoff beam triodes is the 6BK4, used in the RCA 21-CT-661. Announced in late 1954 and designed specifically for color TV receivers, the tube has maximum ratings of: plate voltage, 25,000; d.c. plate current, 1.5 ma; plate dissipation, 25 watts. Its advantages over the 6BD4-A are its amplification factor of approximately 2,000 and its smaller heater requirement of 6.3 volts at only 200 ma (and its much lower cost).

Base pins 3, 4, 6 and 8 of the 6BK4 (Fig. 4) should not be used for tie points. The tube may show a blue glow on the upper half of the inner surface of the bulb wall under normal operating conditions—this is caused by fluorescence and should not be assumed to be the result of gas. This characteristic is also typical of the 6BD4 and 6BD4-A.

not reveal any unusual capabilities as compared to the previously mentioned types. However, the fact that it can be connected as either a triode or tetrode extends its characteristics and control features over a wide range. Thus, this tube type should be included among those the service technician will most likely come in contact with.

**Focus rectifier**

The d.c. focus voltage for color TV picture tubes varies from 4,000 to 8,000, depending upon the tube and its associated circuitry. While occasionally a 1B3-GT, 2V2 or 3A3 will be found in this application, the trend appears to be toward the almost exclusive use of the 1X2-B. This tube has evolved from an old standby, the 1X2 which has a maximum peak inverse voltage rating of 15,000 and a maximum d.c. output current of 1 ma.

The 1X2-A, having higher ratings than the 1X2, was designed specifically for use in television sets as a high-voltage rectifier in flyback type power supplies and became a sort of poor relative of the popular 1B3. The 1X2-A has a maximum peak-inverse plate voltage rating of 20,000 and carries a maximum d.c. output current rating of from 0.5 to 1.1 ma, varying with manufacturer's specifications.

The final product of this design to date, the 1X2-B, is rated to withstand a maximum peak inverse plate voltage of 22,000 and can supply a maximum average plate current of 0.5 ma. The basing connections of the 1X2-B (Fig. 3) are the same as for the 1X2-A. Pins 3 and 7 of this double-ended nine-pin miniature half-wave rectifier may be connected to the filament. The filament voltage of the 1X2-B is 1.25; the filament current, 200 ma.

In late 1954 still another high-voltage

pioneer damper in color TV circuitry. Virtually every 15-inch color set used this octal type half-wave vacuum rectifier that was first announced in late 1953 for use with 90° picture tubes. Its only competitor was the 6AX4-GT used (two in parallel) in the Westinghouse H-840CK15.

Reason for the choice of the 6AU4 over the 6AX4 can be seen in their comparative ratings. The maximum peak inverse plate voltage rating of the 6AU4 is 4,500 as against 4,000 for the 6AX4; maximum peak plate current 1.05 amperes as against 600 ma; maximum d.c. plate current 175 ma as against 125 ma for the 6AX4. Each tube requires a heater supply of 6.3 volts with the 6AU4 drawing 1.8

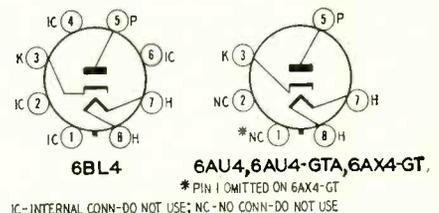


Fig. 5—New damper tubes for color TV.

amperes and the 6AX4 1.2 amperes. The socket connections (Fig. 5) for both tubes are identical.

The socket terminals for pins 1, 2, 4 and 6 should not be used for tie points, and the socket clips for these pins should be removed to reduce the possibility of arc-over and minimize leakage.

With the development of large-screen color TV, RCA announced the 6BL4 in late 1954. This extremely rugged tube was especially designed for use as a damper diode (Fig. 2) in color TV receivers. While having a peak inverse plate voltage rating of 4,500, the same as for the 6AU4, the 6BL4 can supply



Announced by CBS-Hytron in late 1955, the 6792 (Fig. 4) is the most recent development in the field of high-voltage regulator types. The 6792 is a beam tetrode designed for voltage stabilization from 3,000 to 25,000 volts and can be triode- or tetrode-connected.

Maximum ratings for the tube include: plate voltage, 25,000; plate dissipation, 25 watts; plate current, 1 ma; amplification factor, 1,515; heater, 6.3 volts at 450 ma.

The maximum ratings of the 6792 do

half-wave rectifier made its appearance. Used as a focus rectifier in the Westinghouse chassis, the 1AX2 may well give the 1X2-B some competition. Having the same base connections as the 1X2-B, the 1AX2 has a maximum peak inverse plate voltage rating of 25,000 with the usual average plate current rating of 0.5 ma. However, the 1.4 filament draws 650 ma.

**Damper diode**

The 6AU4-GT stands alone as the

a maximum peak plate current of 1.2 amperes and a maximum d.c. plate current of 200 ma. Furthermore, it carries a plate dissipation rating of 8 watts as against 6 watts for the 6AU4.

The price paid for using this tube is its heater consumption: 6.3 volts at 3 amperes, a husky 19 watts. The socket connections for the 6BL4 (Fig. 5) are the same as for the 6AU4.

A tube with a bright future in color TV is the 6AU4-GTA, an improved version of its namesake, the 6AU4-GT.

## TELEVISION

Both are identical in all respects except for two slightly higher ratings of the "GTA"—a maximum peak plate current of 1,150 and a maximum d.c. plate current of 190 ma. Thus while not as muscular as the 6BL4, its high ratings together with its comparatively low heater current of 1.8 amperes will probably make it a widely used tube. (In later production runs of the RCA 21-CT-661 this tube has replaced the 6BL4.)

### Horizontal output

The horizontal-deflection and high-voltage circuits in 15-inch color receivers required no driving power that couldn't be supplied by tubes used for monochrome reception—in parallel. Stromberg-Carlson and General-Electric used two 6CD6's, Westinghouse and Arvin two 6BG6-G's. In the CT-100, RCA drove a 6CD6 very hard and managed to turn the trick with

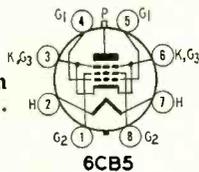


Fig. 6—Base diagram of the 6CB5 tube.

one tube. These beam-power tubes are very rugged, having maximum positive pulse plate voltage ratings of 6,600; a plate dissipation rating of 20 watts for the 6BG6-G and 15 watts for the 6CD6-G. Either could supply the driving power for the 15-inch color tubes, but not with ease.

In the recent CBS-Columbia 205 color TV chassis using the 19VP22, the horizontal sweep circuit is driven by two 6CU6's in parallel. This tube is a slightly heavier version of the 6BQ6-GT. It has a maximum positive pulse plate voltage rating of 6,000 but a plate dissipation rating of only 11 watts.

voltage rating of -1,500. The tube (Fig. 6) has a 6.3-volt heater drawing 2.5 amperes; a high mutual conductance of 8,800 micromhos; high operating ratio of maximum plate input wattage to screen wattage (150 to 3.6 watts); a plate resistance of 5,000 ohms. The 6CB5 will very likely become a widely used horizontal output tube in color TV receivers.

### The synchronous detector

No one tube has as yet dominated this application—various diode, triode and pentodes have been used. This circuit, receiving signals from the band-pass and subcarrier oscillator circuits, has mostly made use of the 6AS6 in early color receivers. The 6AS6 is a sharp-cutoff pentode designed so that grids 1 and 3 can each be used as independent control electrodes and has long found use in gated amplifier and mixer circuits.

Another tube commonly used in this application is the 6BY6, the I and Q demodulator in the RCA CT-100 and CBS-Columbia receivers. This tube is a pentagrid amplifier and its popularity seems to be gaining momentum. Announced by RCA in late 1953, the 6BY6 (Fig. 7) is a seven-pin miniature type intended especially for use as a gated amplifier in monochrome and color TV receivers. While presently being used as a demodulator (Fig. 8), it may very well find use as a combined sync separator and sync clipper.

Grids 1 and 3 have separate base terminals and can be used independently as control electrodes, each having sharp-cutoff characteristics. Grid 3 is designed to minimize secondary emission and the resultant possibility of blocking. Heater voltage is 6.3; current is 300 ma.

A considerable improvement in tube design for synchronous detection has been made with G-E's sheet-beam tube,

tive to variations in oscillator amplitude over a wide range. Its characteristics also made it useful in the burst gate circuit of color sets. Fig. 9 shows a typical application.

The heater of the 6AR8 requires 6.3 volts at 300 ma. In normal application, positive d.c. voltages are applied to the accelerator and plates.

The Westinghouse-designed 6DB6, intended for use as a color demodulator, was announced in 1954 but as yet has not made an appearance in color sets. It is a pentode capable of being driven harder and giving greater output than the 6AS6. The sharp-cutoff tube is a seven-pin miniature unit using grids 1 and 3 for signal application. The tube's output is linear for high levels of grid-3 drive. It features a minimum of interaction between the grids 1 and 3 circuits. The 6DB6 has a 6.3-volt, 300-ma heater.

### The d.c. restorer

Appearing within a few months of each other are the 6BC7 of RCA and


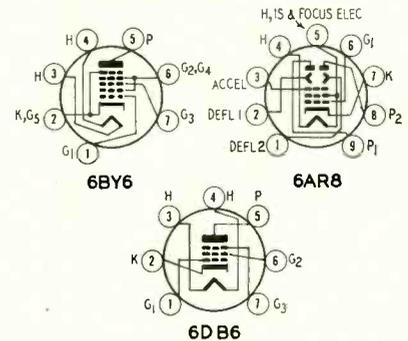


Fig. 7—Bases of new color detectors. the 6BJ7 of G-E, triple diodes widely used as d.c. restorers in color TV receivers. Both are nine-pin miniature units containing three high-perveance diodes. Each diode has its own plate and cathode base connections (Fig. 10),

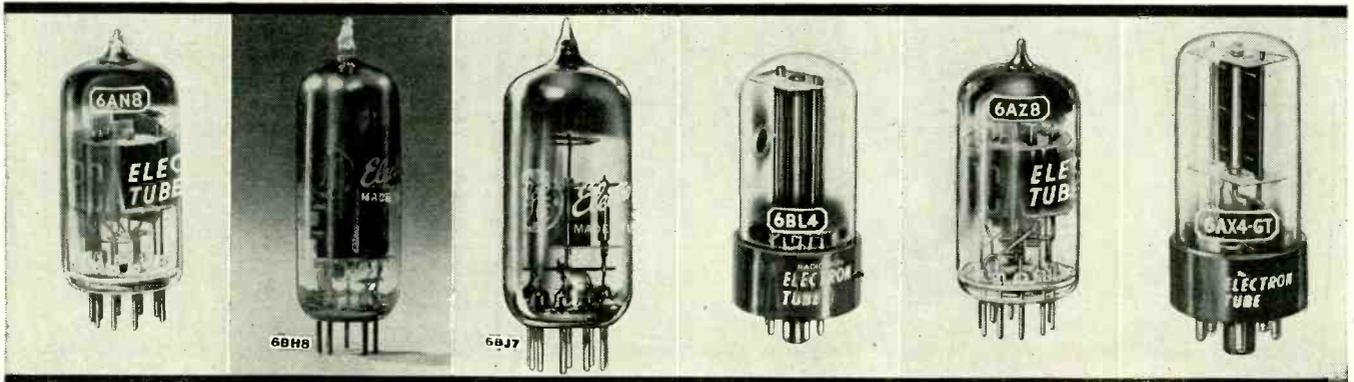

A tube specifically designed to supply the necessary 20 watts of regulated high-voltage power for the 21AXP22 is the 6CB5. This high-perveance beam-power tube was developed in late 1954 as a horizontal-deflection amplifier tube for color TV receivers—it does the job alone (Fig. 2).

The 6CB5 has a positive pulse plate voltage rating of 6,800 and a maximum plate dissipation of 23 watts. In addition, it has a peak negative-pulse plate

the 6AR8 (Fig. 7). It is a miniature double-plate unit having a pair of balanced deflectors to direct the electron beam to either of the two plates and a control grid to vary the intensity of the beam. This characteristic makes the 6AR8 especially suited as a synchronous detector in color TV sets.

The tube requires low oscillator injection power, is free from space-charge coupling effects common in dual-control pentodes and heptodes and is insensi-

is well shielded from the other units and either diode can be used independently.

The 6BC7 is somewhat more robust than the 6BJ7, having a peak inverse plate voltage rating of 300, a peak plate current per plate of 54 ma and a d.c. output current per plate of 12 ma.

The 6BJ7, while having a slightly higher peak inverse plate voltage rating of 330, has a peak plate current rating of only 10 ma and a d.c. output current

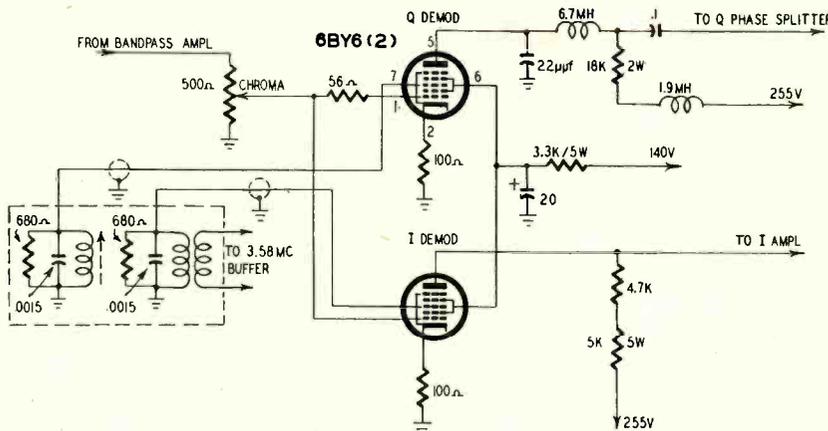


Fig. 8—6BY6's as I and Q demodulators.

rating of 1 ma. Fig. 11 shows 6BC7 circuitry in the CBS-Columbia 205 color chassis. Pin 3, connected to the internal shield, is grounded. The heater of each tube operates at 6.3 volts and 450 ma.

**Power pentode**

The 6CL6 (a miniature tube similar to the old 6AG7 metal), originally designed as a power pentode for use in the video output stage of TV receivers and as a wide-band amplifier tube for industrial equipment, saw comparatively little use in black-and-white TV. Not in its favor were its high heater requirements, 6.3 volts at 650 ma. How-

ever, as the first video amplifier in color TV sets it has come into its own. As such, it has the very responsible position of driving the second video (Y) and bandpass amplifiers.

The 6CL6 (Fig. 10) has a very high transconductance of 11,000 micromhos and provides a voltage gain of from 40 to 45 in wide-band video circuits. In typical operation in 4-mc-wide video amplifier circuits, the 6CL6 will provide an output voltage (peak to peak) of 132 with a control grid signal (peak to peak) of 3 volts. In some receivers the 6CL6 is also used as the second video amplifier.

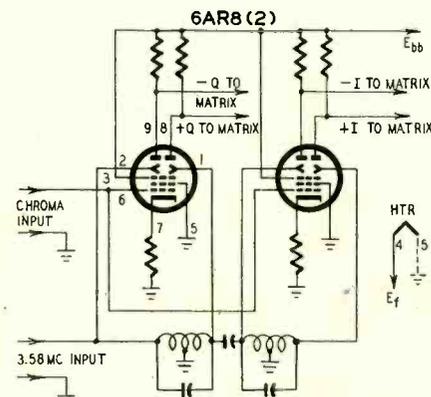


Fig. 9—6AR8 synchronous detectors.

**General-purpose 6AZ8**

This medium-mu-triode-semiremote-cutoff-pentode is fast becoming an electronic Available Jones. Announced in early 1955, it is one of many now appearing containing dissimilar units within one envelope, thus reducing the

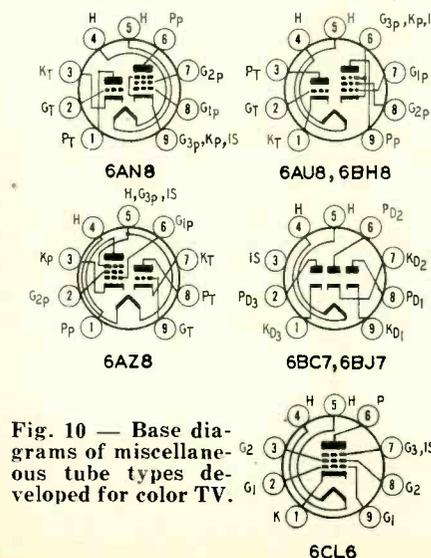


Fig. 10 — Base diagrams of miscellaneous tube types developed for color TV.

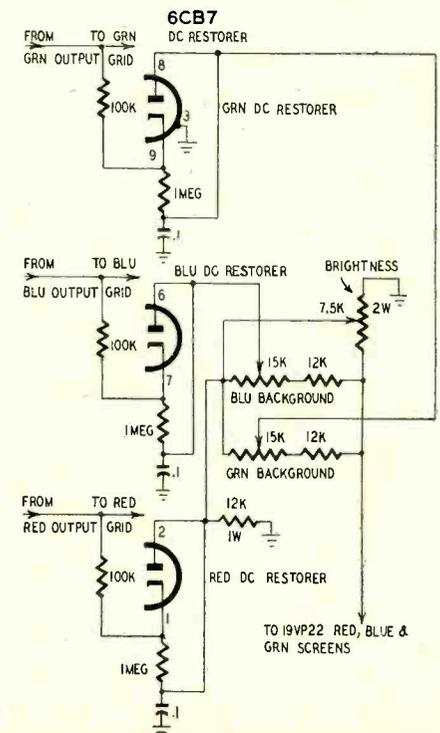


Fig. 11—Triple-diode d.c. restorer in the CBS-Columbia 205 color TV chassis.

number of tubes in TV receivers. The 6AZ8 was intended for a wide variety of applications in monochrome and color sets; it is a nine-pin miniature type and has proven highly versatile. In the RCA 21-CT-661, four 6AZ8's function as a second sync and second video i.f. amplifier, a vertical oscillator and first video i.f. amplifier, a bandpass amplifier and color killer, a 3.58-mc oscillator and B-Y amplifier.

The pentode unit has a high transconductance—6,000 micromhos—and its semiremote-cutoff characteristic minimizes cross-modulation effects and overload distortion in video i.f. stages. There are separate base pins for the cathodes. The suppressor grid and internal shield are connected to one of the heater leads.

The basing arrangement (Fig. 10) and internal construction of the 6AZ8 are designed so that coupling between the triode and pentode is virtually eliminated. Heater requirements are 6.3 volts and 450 ma.

**General-purpose 6AN8**

Staying right with the 6AZ8 as an all-around tube is the 6AN8, a medium-mu-triode-sharp-cutoff-pentode. The CBS-Columbia chassis uses six 6AN8's in such diverse applications as a reactance tube and 3.58-mc oscillator, I amplifier and I phase splitter, second video amplifier and Q phase splitter, a.g.c. amplifier and horizontal sync separator, 3.58-mc buffer and a.g.c. clamp, bandpass amplifier and color killer.

Intended for color TV receivers, the pentode section has a high transconductance of 6,200 micromhos. As with the 6AZ8, the coupling between the triode and pentode is virtually eliminated and their heater requirements are the same—their base connections (Fig. 10) are not.


**Odds and ends**

A major casualty of color TV has been the low-voltage rectifier tube. The very large B currents necessary have brought on the use of 600-700-ma selenium rectifiers in voltage-doubler circuits. Of course, color TV is not all to blame—the same trend exists in black-and-white television.

At this writing 600-ma series-string types are beginning to appear. Tubes such as G-E's 6AU8 and 6BH8, general-purpose sharp-cutoff-pentode-medium-mu-triodes (see diagram) are among the first of the controlled-warm-up units to be announced for color TV use. Certainly many more will follow. Base diagrams of these types are shown in Fig. 10.

Many old-timers still remain in the most recent of color sets. Units such as the 12BH7, 12BU7, 6U8, 6BL7, 6CB6 and 6AL5 perform important functions in color circuits. However, as color circuitry becomes standardized, it is more than likely that many of these will be replaced by units especially designed for color TV. END

## improving your

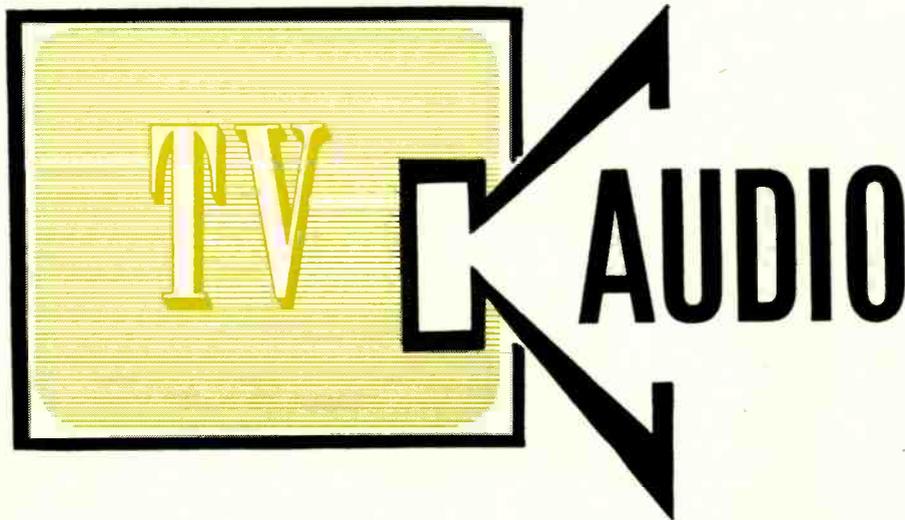

*Using feedback and multiple speakers  
for better-quality sound*

By NORMAN H. CROWHURST

THE televiewer is naturally more concerned about having a good picture to look at than about the quality of the sound that goes along with it. This fact seems to have been overemphasized in the minds of TV designers during the past several years, as shown by the audio section of the average TV receiver which has failed to keep pace with progressing audio techniques. True, some of the more recent models are now going to push-pull outputs and are feeding more than one loudspeaker, which is an improvement over the much more common single-ended output stage.

But designers seem reticent about making progress toward really high quality by introducing feedback which would reduce output stage distortion and provide better damping characteristics for feeding the loudspeaker. Sometimes even a little better speaker unit would produce considerable improvement. In other cases the addition of feedback, involving only one or two extra resistors and maybe a capacitor, will considerably improve sound-reproduction quality.

Many readers are high-fidelity enthusiasts as well as televiewers, and would appreciate knowing how to improve the audio quality of their own TV receivers. A number of things can be done. Your choice will depend on your facilities, how much work you want to put in and how much improvement you really want.

An improvement can be made simply by using a good external loudspeaker.

This merely entails locating the connection to the voice coil of the speaker in the set, disconnecting it and connecting a better speaker in its place. If the speaker in the set uses a field coil, do not disconnect it as it also serves as a filter choke in the receiver.

#### Using your hi-fi system

For the man with a high-fidelity setup a very simple method of bettering TV sound reproduction is to feed the audio through the hi-fi system in place of, or in addition to, the existing TV sound. To do this connect a two-wire conductor from the outside pair of terminals on the set's volume control (Fig. 1), using shielded lead, to the

only at the amplifier end of the cable.—*Editor*)

The volume control on the hi-fi system will then control the level from the system speaker; the set's volume control will determine the volume coming from the set. This gives independent control of volume from each. Leave the set control off, and all the sound will come from the hi-fi system. Adjust balance, and pleasing effects can be obtained.

Many will not want to tie up their hi-fi system in this way but will prefer to improve the quality delivered by the set's loudspeaker. Practically all television receivers have a two-stage single-ended audio amplifier using a triode for the first stage and a pentode for the output stage. The principal fault with this arrangement is that the pentode has a plate resistance of about 10 times its optimum load resistance. Hence the loudspeaker is fed from an amplifier having a damping factor of about 0.1. This means that the natural resonance of the loudspeaker with its enclosure—in this case the television cabinet—tends to be emphasized considerably. The rise at the high-frequency end of the response, due to the voice coil inductance, is usually offset to some extent by an equalizing capacitor connected across the primary of the output transformer.

#### Applying feedback

The best way to step up performance is to apply feedback so as to improve this damping factor, in which case the

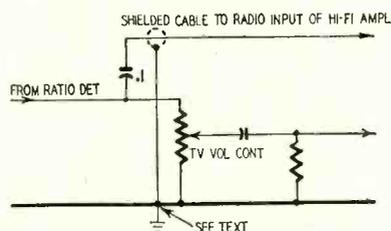


Fig. 1—Sound take-off from TV set.

"radio" input of your preamplifier or hi-fi amplifier. (It must be a high-impedance input.)

(If the TV set uses a voltage-doubler in the B supply or has a series heater string with one end connected to the chassis or B minus, connect a small 600-volt blocking capacitor between the low end of the volume control and the shield on the audio cable. Ground the braid

equalizing capacitor connected across the output transformer can be removed—feedback will take care of this function much more effectively.

If we apply enough negative voltage feedback to change the damping factor from 0.1 to some value greater than 1, the audio chain will have insufficient gain because the change will reduce gain over 20 db. But remember that positive current feedback, as well as negative voltage feedback, has the effect of *reducing* source impedance. Positive current feedback increases the gain; negative voltage feedback reduces it. If we use the same amount each of positive current and negative voltage feedback, we shall end up with the same gain we started with and improve the damping factor twice over.

Assume that we adjust the current feedback to give a gain just 4 times the original and then apply voltage feedback to reduce it again to its original value. This will increase the damping factor by 16 times which will considerably improve the response and performance of the loudspeaker in its enclosure. As the voltage feedback is over a longer loop than the current feedback, the distortion will show overall reduction too.

While audio circuits are very similar in all recent TV receivers, there are three principal variants that require separate consideration on how to apply this method, so we will take each in turn. The first thing to do in each case is to remove the capacitor connected across the output transformer primary.

**Variant one**

This is represented by the typical circuit in Fig. 2 and uses a 6V6, 25L6, 6K6 or 6AQ5 in the output stage, preceded by a 6AV6, 6SQ7, 6T8, 6AT6 or half of a 12AX7 or 6SL7 in the first audio stage. All these are high-slope tubes with an amplification factor of 70 or 100, and usually the circuit uses contact bias provided by a very large resistance (R1) in the grid circuit, the cathode being grounded.

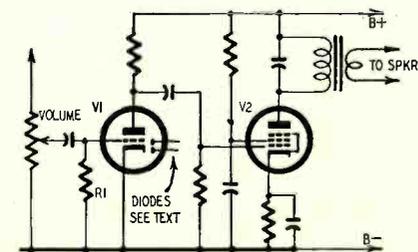


Fig. 2—Schematic diagram of the audio output circuit for variant one.

Most of these first audio stage tubes include diodes using the same cathode as the triode section. If these diodes are used for some other purpose in the circuit, consideration will need to be given as to what arrangements can be made to take care of their function. In many circuits, however, particularly those using the 6AV6, the diodes are not used, being either grounded along

with the cathode or left unconnected. In these circuits no problem arises about the diodes. But where the diodes are used the problem is discussed after variant two, which is similar in this respect.

The output tube (V2) in this variant uses a cathode bias resistor; in some instances it will have a bypass capacitor connected across it. To apply current feedback we want to use the cathode resistor unbypassed; so if a bypass capacitor is used, it should be removed.

Next, insert a 470-ohm resistor (Fig. 3) between the cathode of V1 and ground. This will produce a small bias voltage, but less than the full operating bias of the tube. So now the value of R1 can be reduced and the operating bias is correct. Probably a value of

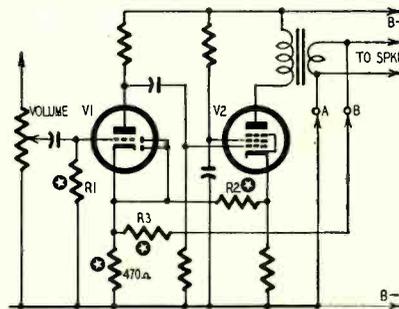


Fig. 3—Fig. 2 modified for positive current and negative voltage feedback.

2 or 3 megohms will suit in place of the 6.8 or 10 megohms used previously. The correct value can be checked by measuring the plate voltage on this tube which should be the same as in the original circuit.

Now we are ready to apply current feedback. Calculating the resistance value required is a little involved and the easiest method is: Connect a potentiometer of, say, 100,000 ohms between the two cathodes in the position shown as R2 in Fig. 3; adjust this pot until the amplifier just goes into oscillation. If oscillation starts as soon as the potentiometer is connected and adjustment will not stop it, put another fixed resistor of, say, 47,000 ohms in series with the pot and adjust until the oscillation stops. Then reduce the resistance until it just starts. Next, carefully remove the variable resistor (with the fixed one if used), taking care not alter its setting and measure its value (the two in series where a fixed one is added). This value causes oscillation. The value for positive feedback to give approximately four times the gain without feedback will be three-quarters of the value measured.

Obtain a resistor of this calculated value and connect it in the position shown as R2 (Fig. 3). For example, if the resistor that caused oscillation measured 90,000 ohms, the value required will be about 68,000 ohms. A close-tolerance component should be used or else the values selected with an ohmmeter or bridge to be as close as possible to the desired value.

We are now ready to apply the negative voltage feedback. This should be taken from the secondary of the output transformer by connecting one side of it to B minus and the other side, through a suitable resistor (R3), to the cathode of V1. The same variable resistor can be used to find the correct value by adjusting it until the gain is the same as without feedback connected. But first be sure the phase is correct: if *reducing* the feedback resistor *increases* gain instead of reducing it, or if the set oscillates in any position of the resistor, the phasing is wrong—reverse the secondary connections. Then adjust to give the same gain with both feedbacks connected as without either.

This adjustment can be made by unsoldering the two return points on the cathode of V1 (R2 and R3) connecting them, and tapping them both onto the cathode together; then adjust the variable (R3) until there is no change when the feedback resistors are contacted to the cathode—no change in level, that is. There may be an improvement in quality—in fact there should be! This will find the condition when voltage and current feedback are equal. Finally the resistance can be measured and the nearest standard value of fixed resistor wired in its place. The value of R3 is not as critical as that of R2, but the nearest standard preferred value should be used.

**Variant two**

The remaining two variants both use the output stage to provide a regulated voltage tapping for other points in the receiver, usually in the region of 125 to 150 volts (the exact voltage varies with individual receivers). This voltage is obtained from the cathode of the output stage and some method has to be used to insure that the d.c. grid

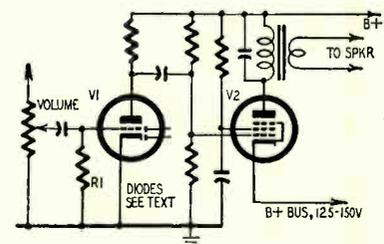


Fig. 4—V2 grid voltage established by voltage divider from B plus and ground.

voltage is just a few volts negative of the required cathode voltage, because this is what controls it. The difference between the remaining two variants is in the method of setting this d.c. grid voltage.

In the circuit of Fig. 4, this voltage is set by connecting the grid of V2 to the junction of two close-tolerance resistors connected from B plus to ground. The audio signal is then capacitively coupled from the plate of V1. In this circuit the tube used for the output stage is either a 6AS5, 6V6, 6W6 or 6Y6, and the first audio stage is usually one of the same group as for the first variant.

## TELEVISION

The first thing to do in this case, after disconnecting the capacitor on the output transformer primary, is to insert a cathode resistor in the output stage to provide current feedback and at the same time adjust the circuit so the voltage fed to the rest of the circuit is still correct. Values suggested for cathode resistor R5 in Fig. 5 are: 150 ohms for high-slope tubes such as 6W6, 25L6 or 6Y6; 330 ohms for the 6AS5 or 6V6. This resistor does not serve as

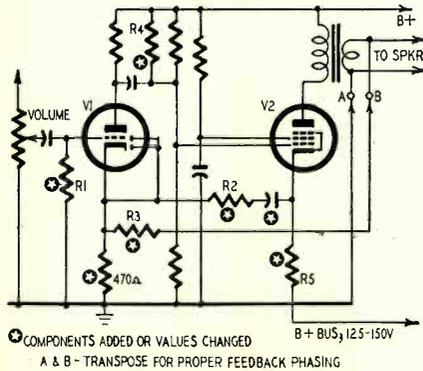


Fig. 5—Schematic diagram of the audio output circuit for variant two.

the normal bias resistor but provides an audio potential for current feedback.

Having inserted this resistor in the cathode return, the top end of the voltage divider arrangement should be shunted with a high-value resistance R4 of about 10 megohms. This is to raise the voltage at the grid of V2 so that the voltage at the bottom end of R5 is the same as the original cathode voltage. In this way the rest of the circuit gets the right working voltage, but the cathode and grid voltage on V2 have to be a little higher.

The first stage can now be modified in the same way as for the first variant by inserting a 470-ohm resistor in the V1 cathode return and modifying the grid resistor so the plate voltage is approximately the same as in the original circuit. This was described in variant one.

In connecting the current feedback for this and the final variant, a blocking capacitor is needed in series with R2 because the cathode of V2 is more than 100 volts higher in voltage than the cathode of V1. The value of this capacitor is not likely to prove critical. For good low-frequency response when the circuit is completed, a 4- $\mu$ f 200-volt electrolytic capacitor may be used.

The same method as described before can be used to find the correct resistance value. One observation, though: If oscillation, like motorboating, starts at a very low frequency it is due to a low-frequency phase shift effect and a different value blocking capacitor should be tried. But this is unlikely. The oscillation usually starts at a frequency somewhere in the middle of the audio band and is of rather poor waveform, indicated by a rough sound.

Finally, negative voltage feedback can be applied from the output transformer secondary to the cathode of V1

as described in variant one and the finished circuit will be as at Fig. 5.

### The diode problem

In both the foregoing variants, the first stage use a grounded cathode. And in many instances diodes, using the same cathode of V1, perform the a.g.c. or some other function in the set. The d.c. voltage drop and also the audio component caused by inserting the 470-ohm resistor between cathode and ground will interfere with the correct operation of these diodes, so some other arrangement will have to be made to take their place.

The exact replacement that can be made will depend upon the component values in the rest of the circuit to which the diodes are connected. Sometimes the two diodes are strapped together in parallel, so as to perform as only one diode. Then, of course, only one diode will be necessary to replace the original two.

In some circuits a crystal diode could be used, either one of the high-back-resistance germanium types such as a 1N63 or 1N65 or else a 1N21 silicon type. In fact, one of these or another should prove successful for most receivers. But in some cases even the high back resistance of these types will not be high enough for the rest of the circuit, so a leakage will upset the operation of the set.

In such cases a thermionic diode (tube) must be substituted. The problem then is where to put it and how to connect in its heater. If the set uses parallel heaters on 6.3 volts, a 6AL5 or 6AN6 should serve, provided the transformer will supply the extra 0.2 or 0.3 ampere necessary in addition to its present load. TV heater windings have to be liberal to supply the large number of tubes in the set, but there is a breaking point. The best way to check is to measure the voltage on the heaters and see if connecting the diode drops it seriously. The cathode should be connected to ground and the diodes to the wires removed from the original diodes. If a 6AL5 is used, both cathodes must be tied to ground. If a 6AN6 is used, two diodes can be strapped together to each wire.

If the set uses a series-connected heater arrangement, a suitable point will have to be found to connect in a heater for the diode, using a type with the correct heater current to suit the chain, such as a 12AL5 or 5AL5. The extra voltage required by this heater will mean that the other tubes will be running a shade low in heater volts. Check that this does not drop by more than a volt per tube (except for the heaters with a big voltage drop where a larger drop is permissible).

The miniature types mentioned can be hung in the wiring—or rather the socket can—if it is not possible to find space to make an additional hole or if you do not have facilities for making holes. If the set has to be transported at any time, it would be a good idea to

find some way of tying the tube down so it cannot break loose. The subminiature types are even easier to hang in the wiring and the British Mullard type EA50, taking a heater supply of 6.3 volts at 0.15 ampere, would serve excellently.

### Variant three

The final commercial circuit we shall consider here uses a different method of controlling the voltage on the grid of V2, shown in Fig. 6. First audio stage V1 is usually a 6AV6, 6C4 or half of a 6SN7 and is biased by a cathode resistor. The value of bias resistor, in conjunction with the plate resistor, controls the plate voltage reliably, and the grid of V2 is fixed by being direct-coupled to the plate of V1. Sometimes the cathode resistor of V1 is bypassed by a capacitor. If used, it will have to be removed before applying current feedback.

Some of these circuits also have a low-value resistor in the cathode circuit of V2 which will prove convenient for picking off the current feedback. However, sometimes this too has a bypass capacitor which will have to be removed. If no such resistor is provided, a suitable value will have to be inserted and the grid voltage adjusted so the bottom

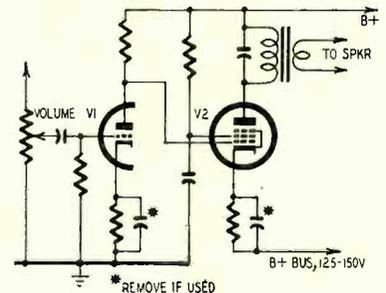


Fig. 6—V2 grid voltage established by direct coupling to plate of V1.

end of R4 (Fig. 7) shows the same voltage as the cathode of V2 did in the original circuit. This is done by connecting a high-value resistance R1 in parallel with the existing V1 plate resistor. Adjust the value until the right voltage appears at the bottom end of R4. A suitable value for R4 in this circuit is 150 ohms if V2 is a 6W6, 25L6 or 6Y6; 330 ohms for a 6AS5, 6V6 or 6K6.

The diode problem does not arise in

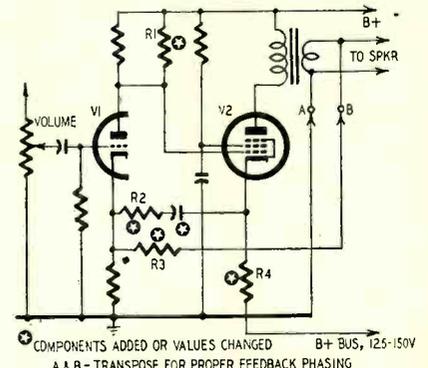


Fig. 7—Schematic diagram of the audio output circuit for variant three.

this circuit—the 6C4 and 6SN7 do not have diodes and where a 6AV6 is used for V1 its diodes are either tied to ground, cathode or left unconnected.

Positive current feedback is next applied as described for variant one, using the blocking capacitor as in variant two. Finally the negative voltage feedback is applied from the output transformer secondary as described in variant one.

### What improvement?

The foregoing discussion covers the great majority of television receivers at present in service, and the changes described will better the sound quality of the set. But it is nice to know just what sort of improvement to expect.

Most TV receivers have two very marked resonances in their response: one in the lower frequencies due to the resonance of the loudspeaker diaphragm with the cabinet acting as an enclosure; the other at a higher frequency due to the parallel resonance of the equalizing capacitor across the output transformer primary with the voice coil inductance. In TV audio designer's parlance, these resonances provide the "pleasing bass" and the "treble brilliance." But no hi-fi enthusiast is deceived!

The changes described in the foregoing three variants will give a true wide-range response in place of this phony two-resonance imitation because the speaker damping factor will be raised from the region of 0.1 to about 2.

But what about harmonic and intermodulation distortion? The current feedback will not appreciably increase this because its effect is to modify the operation of the output tube so that more second harmonic and less third are produced—which at least reduces the annoyance factor of the distortion. Then the voltage feedback brings the actual distortion value to a lower figure than the original. But an effect that normal distortion measurements will not show up is the reduction in the emphasis which the straight pentode circuit places on higher harmonics, both in program and distortion. This is caused by the speaker impedance characteristic in conjunction with the tube characteristic when no feedback is used, but the improved damping factor eliminates it to all intents and purposes.

If the loudspeaker is correctly matched to the output stage this modification should also result in considerably more output being apparent before overloading begins. By correct matching, we mean that its impedance in the region from 600 to 1,000 cycles should be matched to the optimum load value for the output tube. But often, to avoid producing distortion at the dominant frequencies (the pleasant bass and brilliant treble!), the impedance of the speaker at its low-frequency resonance and the dynamic impedance produced by tuning the voice coil inductance with the primary shunt capacitor, is what is matched to the optimum load for the tube. In this case, further improvement

by way of increased output can be achieved by changing the matching.

### Multiple speakers

A convenient way of killing two birds with one stone here is to add an extra speaker, identical to the one already in the set, and connect it in series with the existing one. This will give the advantage of two speakers in improved realism, increase the effective sound output and correct the matching at the same time.

Where the existing speaker is mounted in one side of the cabinet, the additional one can be mounted in the opposite side (Fig. 8). This will give

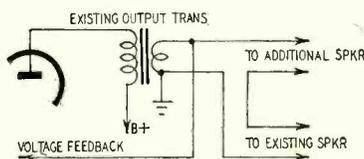


Fig. 8—Adding another loudspeaker.

balance to the reproduction and a surprising approach to stereophonic effect. Then the TV sound will be far more realistic than it ever was with the inferior reproduction over a single unit. But the question of phase comes in here. The extra unit must be connected properly to give correct phase in the combined reproduction.

With the loudspeakers mounted in opposite sides of the cabinet there is not a very ready way of checking phasing; the best way is to judge from the effect it produces on program presentation. Incorrect phasing will give the sound an unnatural effect, as if it has nothing to do with the picture—although, of course, it will be synchronized. Correct phasing will give sound that seems to "fit the picture" better.

Try it for a while with the extra speaker connected each way and decide which is best after careful listening.

A better method of connection, from the viewpoint of loudspeaker operation, is to connect the two units in parallel rather than in series. But this requires the use of a different output transformer. However, if you really want to go to town on improvement, you could use two slightly larger speakers than the 5-inch one the set probably came with. Then install a new output transformer designed to match the optimum load of the output tube to the impedance of the two units in parallel. Don't forget to check for phasing here also.

If you decide to change the speaker-matching arrangement by making any of these additions, the adjustment of current and voltage feedback, as described earlier, should be conducted *after* the new transformer and loudspeaker units have been installed—the loading of the output stage will alter both current and voltage feedback and throw the values out of balance.

When you have gone through this routine once, you will be familiar with it, so having made the set work successfully with the existing speaker, you will probably want to go on and try the effect of better speakers or speaker arrangement. As you have already the spare potentiometer with which you made the adjustment the first time, there will be no problem in going over the whole procedure again and setting the values to suit the new speaker arrangement.

The improvements described in this article will be found to be considerable when one considers the limitations imposed by having to get them into the existing set. END

## CASE OF THE SELF-TURNING TRIMMERS

THE owner of a nondescript table model a.c.-d.c. receiver came into the shop complaining of its sensitivity and selectivity. I went out to his house to inspect the five-tuber. With the volume control full on I could hear some local stations but that was about all. It looked like a case of bad alignment, and after taking the chassis from the cabinet I noticed that the iron slugs in the two i.f. transformers were turned down—nowhere near their correct setting.


Fortunately, the oscillator was in the truck and I aligned the receiver. The difference in performance was amazing and I made a slightly vinegary remark about tampering with the screws as I left.

I was very surprised the next day when the customer called to say that the set had played well for most of the previous evening but had become gradually weaker and was now as bad as ever. I made my way back to the house

expecting to find a bad tube. Instead, when I removed the chassis, I found the i.f. cores screwed all the way down. My thoughts were quite unprintable, but I was assured that the chassis was not touched.

About this time, I was struck by an awful thought and gingerly screwed the nearest slug up again with my fingers—the darned thing was loose as that. Up it came, first through one peak, then out of resonance again as it passed through the winding, then to the other and proper peak. I followed the same course with the other slug and then turned the volume up. The slugs, almost imperceptibly but very surely, began to dance themselves down with the vibration from the speaker. I fixed the trouble with a lump of paraffin.

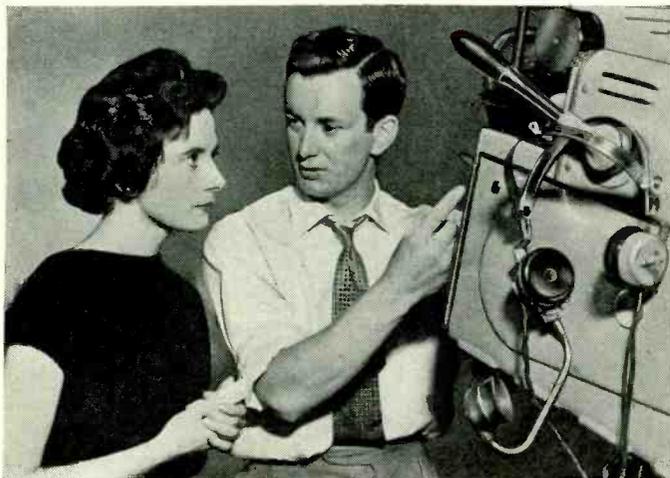Never again would I align a receiver without sealing the cores and trimmers when finished.—George R. Anglado



# BRITAIN TAKES ON COMMERCIAL TV

By T. W. DRESSER

Camera operator explains equipment to girl video mixer

**T**OLL TV, pay TV or whatever you like to call it, has for the past two years occupied the attention of the American public to the exclusion of many other important things. Over the same period the British public has been just as absorbed in the reverse of the same thing—whether the country should have free TV — TV paid for by the advertisements it carries. Britain has heard the same acrimonious debates and arguments that pay TV has roused in the States, the same gloomy forecasts that it would kill the entertainment business and the same threats that if it came about this and that organization would not touch it, which would automatically insure its failure. But, despite all the eloquence expended on the subject, Britain for the first time in its radio or TV history has been looking at and liking commercial programs.

In the States much depends, as far as pay TV is concerned, upon the FCC. If that body is agreeable, pay TV is on the air. In Britain it requires an act of Parliament. Only after that has gone through can the postmaster general grant frequency channels to a new broadcasting organization. Commercial TV was sanctioned on July 30, 1954.

The bill was put through only after a bitter debate in the House of Commons, in which the Socialist Party made it quite plain that if they secure power at a future election they will promptly remove the act from the statute book and kill commercial TV forthwith! Generally this is considered an idle threat. The fact that the people like it and now demand it would deter any politician from such a step.

The setup for the commercial network is considerably different from either current American practice or that of the BBC, which had a monopoly of all radio and TV services before the organization responsible for the new programs was formed. The Act of July 30, 1954 created a semi-official body named the Independent Television Authority, which is responsible for putting the programs on the air and used Government funds to the tune of \$8,000,000 to commence operations. The act stipulated that this loan has to be repaid

over the next 5 years. By its charter the ITA is empowered to:

1. Plan the overall setup of commercial TV in the country.
2. Insure the widest possible access to the new service in order to prevent the rise of another monopolistic body like the BBC.
3. Choose *program contractors*.
4. Design, build and operate the transmitters for the new service. These will remain the property of the ITA and neither the Government nor the program contractors have any hold on them.

5. Supervise the ethics and general standards of the programs originated by the contractors.

The ITA has nothing whatever to do with the origination of programs or the medium by which the video signals are piped to the transmitter building. These functions are solely the province of the program contractors who deal directly with the advertisers. These contractors originate the programs and while they have a free hand to a large extent they are prevented by law from devoting more than six minutes in every hour of program time to actual advertising material. Moreover, it is stipulated that advertising matter can be inserted only at the beginning and end of programs and during "natural breaks." Still further, advertisers have no say in the main program material whatever. They can stipulate the time they wish their ad to appear, and the actual advertising material—usually a 30-second or 1-minute film run—is largely left to them if it conforms to ITA's code of ethics. That is all they are permitted.

The charge for time has been fixed arbitrarily by all the contractors at around \$2,800 a minute for peak viewing hours with pro rata figures for off-peak times. Contractors have lined up a glittering galaxy of talent for their shows, including most of the top-flight American stars as well as all the leading figures in British show business. When the service first commenced, there was a prospect the BBC service would go off the air due to the pirating of their program stars as well as technicians by the commercials contractors.

One notable result of the opening of commercial service was this wholesale importation, on film, of popular American programs and personalities and the adaptation of anglicized versions of other U. S. shows, says the British Information Service in a release intended for American circulation. "I Love Lucy," "Dragnet," Roy Rogers and Liberace are well on the road to fame in London. The giveaway program, too, is creeping in. "Double Your Money," run by a lively young Canadian, Hughie Green, has a top prize for general knowledge answers rising to nearly \$3,000. "People Are Funny" has also migrated from Hollywood and, while its brash practical joking annoys some professional newspaper critics, there are grave suspicions that sections of the public enjoy it. Certainly the victims accept washing machines and TV sets as gifts with marked equanimity.

## Problems of conversion

The country was well blanketed with publicity advertising these attractions prior to the opening of the service but for some time public interest was difficult to assess. There were a number of reasons for the apparent apathy. To begin with, to convert his equipment to cover commercial TV as well as the BBC service involved John Citizen in a not inconsiderable financial outlay. He wanted to be sure he would get value for his money before he committed himself to that. The 14 BBC stations, ranging in power from 10 to 100 kw (ERP), all carry the same program. As a result TV receiver manufacturers have turned out only fixed-tuned models to cover the nearest station to the area in which they were to be sold.

These BBC stations operate in band I (41-65 mc). While the high-powered ones radiate a vertically polarized signal, the low-powered are horizontally polarized. The commercial stations, each of 100 kw, operate in band III (176-214 mc) and all use vertical polarization. Therefore the prospective viewer of commercials has either to purchase a converter (cost \$15 to \$30) or buy one of the new 13-channel receivers at \$180 to \$240. In both in-

stances he would also need an additional antenna at a cost of \$18 upward. If he also wished to get the new BBC FM transmissions in band II (87.5-100 mc) due to come into service this month, he would require still more elements tagged on to the weird erection surmounting his roof. His home, which used to be reckoned his castle, would begin to look more like a space ship than a miniature baronial hall!

Evidence that John Citizen was holding off came from a research survey—designed to test public enthusiasm—which came up with the following figures for the London area:

Receivers ready for the new service 19%

Viewers prepared to convert for commercial TV 25%

Waiting to see if programs are worth the cost of conversion 38%

Will not convert 17%

Three days before the London commercial station was due on the air these figures were made meaningless by a sudden rush on the part of the public to have their TV's converted for the new service. To date the dealers still have a backlog of two to three months' work on present orders.

#### The transmitting net

The first two of the commercial stations serve the London and Birmingham areas. The London antenna tower is 500 feet high and will be shared with the BBC, each party having a separate antenna mounted on it. A further station—to serve northwest England, parts of Wales and the Midlands—is scheduled for service next month or early March. This station will cost \$560,000 and the studios to feed it, which will be built in Manchester, will run away with another \$2,800,000. Like the Birmingham station, it will provide a program for something like 7,000,000 viewers. Other transmitters due to come into operation this year will extend the service to cover all thickly populated areas.

Eventually a network of 25 stations will cover the country from Land's End to John O'Groats, but the ITA does not propose to stop there. According to Sir Robert Fraser, ITA chief, they do not intend restricting competitive TV to one alternative to the BBC program. As long as advertisers believe in the medium of TV (and the tremendous success of American commercial TV shows no slacking off) there is no reason why there should not be two, three or even more commercial TV stations for each area of Britain, competing with the BBC and with each other, but all of them under the wing of the ITA.

The transmitters, antennas and most of the studio and film projection equipment of the commercial studio centers and transmitter buildings are of Marconi, EMI or Pye manufacture. A considerable amount of RCA apparatus has been purchased by Associated-Rediffusion, Monday-through-Friday

program contractor for London and one of the biggest organizations in the business. This firm also uses four outside broadcast vehicles, or remote telecast units as they term them (two of Marconi manufacture, one Pye and one RCA), all of them three-camera units. These vehicles require 8 kw of power for operation. This can be taken either from the nearest utility supply or from a mobile generator trailer.

Since the new service was first mooted a remarkable degree of cooperation has grown up between the program contractors and the TV dealers. Week by week until the commencement of the programs the contractors furnished new material for dealers' counters and displays. In addition, they advertised in towns in the service area extremely effectively. The dealers reciprocated by supplying the contractors with figures for receiver conversions and new installations which enabled them to form a fair estimate of the probable number of prospective viewers on opening day. A similar degree of cooperation has also been a feature of the relations between equipment manufacturers and contractors. As late as last May the only source from which the contractors could secure trained studio and outside broadcast van (truck) technicians was the BBC. Wholesale pirating from that source would have jeopardized that service (as indeed it did for a time about the middle of last year).

The alternative was to train their own crews under actual "on the air" conditions, but at that time there was neither a suitable place nor available spare equipment for the purpose. The Marconi Co., principal suppliers of equipment to the program people, filled the gap by furnishing a former theatre with cameras, control gear, mikes, trucks and sets and installing a typical control room set-up. This Marconi TV center with its stage of 2,000 square feet has since been used for training over 100 technicians for such jobs as video and sound mixing, camera and boom operation, floor management and lighting engineering. These technicians—selected from some 4,000 applicants—have been given an intensive course in

practical operation of TV gear. They have worked as teams in the studio, in the control room, on the film projection apparatus and with the mobile telecast van. As a result they went on the air for the first time like old hands, with the confidence which comes from familiarity with one's equipment, although a few short weeks before they had been complete greenhorns.

The commercial programs were welcomed from the first as good competition for the BBC and likely to stir that august body into some semblance of life. Apart from that the majority of British viewers kept an open mind, preferring to wait and see what sort of a show the commercials made before passing judgment. Now, it can be safely said that viewers are all for them. They provide a refreshing change to the BBC programs, although under the spur the latter have improved enormously. They have brought Burns and Allen and have started modest give aways with the maximum prize of a camera and scored a big success over their rivals by securing an Anglo-Russian boxing match. But the commercials can give viewers a wealth of varying programs it would be impossible for the BBC to put out on its restricted budget. And all this from the proceeds of advertising! The commercials get nothing out of the \$8.40 per annum each British viewer pays for the privilege of looking at TV; the BBC still gets it all. The viewer is happy though; for the first time in his life he is getting something for nothing (he thinks) and many figure that there is a chance, given time, of the commercials taking over completely and then it would all be for free.


As Roland Gillet, program chief of Associated-Rediffusion, succinctly put it, "The public are the bosses. If they like our programs, we go on. If they don't, we go off. But we'll take care that they do."

So far they do. The commercial audience increases each day and TV manufacturers have quit making fixed-tuned television receivers. Nobody wants them; they won't pick up the commercials!

END



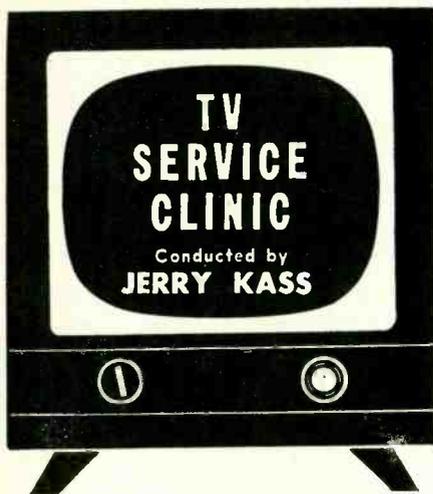A view of the control room in Associated-Rediffusion's Wembley studio. The operators are—left to right—the program producer and vision mixer.



THE audio-frequency range transmitted on the FM sound carrier of a television broadcast is considerably wider than that used in conventional AM broadcasting. Many local TV stations transmit an audio range of 50 to 15,000 cycles. (Cross-country lines carrying network programs will have a much lower audio range due to the frequency limitations of these cables.)

The higher audio frequencies are generally of lower amplitude than the low frequencies and thus produce comparatively little frequency deviation (in FM, frequency swing is proportional to the amplitude of the audio signal). Thus, interference (atmospherics and transmitter noise) would produce the greatest noise-to-signal ratio at the higher audio frequencies. To counteract this condition, FCC standards provide at each transmitter for a pre-emphasis network consisting of a high-pass filter having a time constant of 75 microseconds.

The amount of pre-emphasis applied at the transmitter ranges from a gain of 1 at 50 cycles to a gain of 7 at 15,000 cycles (Fig. 1). The rise is very slow to about 500 cycles; from there it increases rapidly. This pre-emphasis increases carrier swing at higher frequencies and minimizes the effects of atmospheric and transmitter noise reaching the receiver.

This procedure introduces tone distortion which, if not compensated for in the television receiver, produces accentuated treble. However, compensation consisting of a de-emphasis network—a low-pass R-C filter—also having a time constant of 75 microseconds is applied in the TV receiver.

De-emphasis can be applied at any point in the audio amplifier, but general practice has been to install the R-C filter at the output of the sound detector. This attenuates the higher audio frequencies immediately and reduces the possibility of regeneration in the sound section of the set.

The exact values of the R-C de-emphasis network vary with different receivers. With the low-pass filter connected across the output of the sound

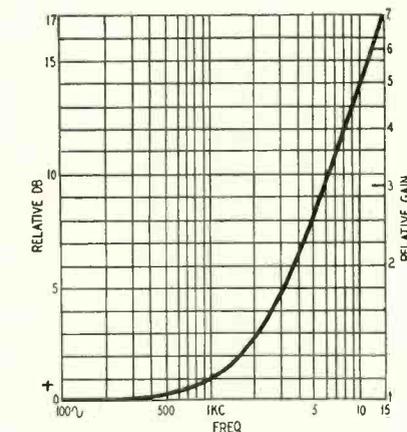


Fig. 1—Standard 75-microsecond pre-emphasis curve for FM and TV sound.

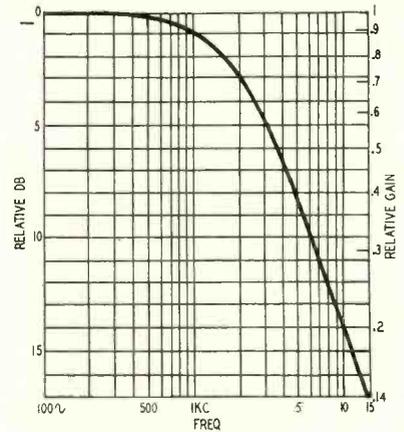


Fig. 3—An ideal de-emphasis curve.

detector, the time constant must also include the various shunt capacitances in the circuit. Thus, while a 75-microsecond time constant is used, the physical values of R and C vary with different receivers. In each case, however, the low-pass filter shunts the higher audio frequencies to ground to a greater extent than the lower ones.

Thus, the amplitude of the higher audio frequencies, that were increased before modulation at the FM transmitter to increase the signal-to-noise ratio, are now attenuated to the same extent.

It might appear that the pre-emphasis-de-emphasis arrangement is of no advantage because it leaves us where we started—however, that is just the idea. Since noise reaching the FM receiver is generated during and after

modulation, pre-emphasis is applied at a low-level audio stage before the interference is produced. Thus, the signal-to-noise ratio of the higher-frequency audio signals transmitted is increased. When the audio-frequency signals and noise are reduced by the de-emphasis network in the television receiver, the signal is restored to its original value while the noise is reduced to a below-normal value.

Commercial circuits

Fig. 2 shows several de-emphasis networks used in the audio section of present-day television receivers. Fig. 2-a is the circuit used in the Admiral chassis 21B1. Resistor R is 47,000 ohms, capacitor C is .001  $\mu$ f. Fig. 2-b is the circuit used in the G-E model 21C225. R is either 22,000 or 47,000 ohms, C is .004 or .002  $\mu$ f. Fig. 2-c is the network used in the Du Mont RA-166 chassis. Here R is 22,000 ohms and C .0033  $\mu$ f. Still another de-emphasis network, used in the Hoffman 195 chassis, is shown in Fig. 2-d. The resistor is 15,000 ohms and the capacitor .0047  $\mu$ f.

While the various resistance and capacitance values appear to be approximately the same, they vary considerably percentage-wise. The resistance values in the Fig. 2 examples ranged from 15,000 to 47,000 ohms and the capacitance .001 to .0047  $\mu$ f. These values are determined by the desired voltage output from the network and the distributed circuit capacitances.

Many readers have inquired as to the best sound takeoff point for feeding the audio signal from a TV receiver into a high-fidelity amplifier. Theoretically, it is the output of the de-emphasis network since the response of this network should reverse the pre-emphasis curve.

However, the vast majority of television sets work into small speakers, so the receiver's audio amplifier usually has a frequency response well below the range of the transmitted audio signal. Because of this, and to avoid possible regeneration in the audio amplifier and interference from the horizontal sweep, high-frequency suppression of most de-emphasis networks is excessive.

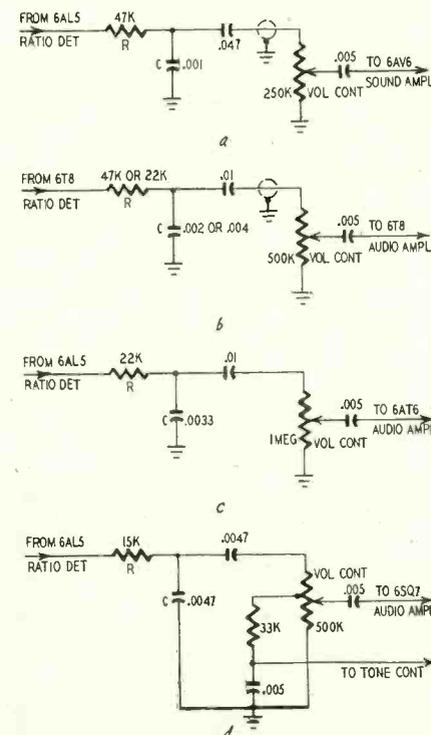


Fig. 2—De-emphasis networks in some Admiral, G-E, Du Mont and Hoffman TV sets are shown in circuits a through d, respectively.

Thus, a better solution is this: Connect a switch to remove the de-emphasis shunt capacitor and following circuitry from the circuit. With the audio cable connected to the hi-fi amplifier, feed the output of the de-emphasis resistor into the input of the cable. Connect a new de-emphasis capacitor of slightly lower value at the input to the audio cable. Now feed the input of the de-emphasis network with a signal from an audio signal generator, varying the frequency every 500 cycles from 500 cycles to 15 kc, maintaining a constant input voltage. Connect an oscilloscope or a.c. v.t.v.m. across the input circuit to the high-fidelity amplifier. Then vary the resistance and capacitance values (while observing the v.t.v.m. or scope at each check point) in the new de-emphasis network until the Fig. 3 response is obtained.

**Shorted yoke**

A Crosley chassis 431-2 came in with no vertical deflection. A resistance check revealed a short in the vertical deflection coils. When I removed the yoke, I noticed that the trouble was mechanical in that the vertical winding had broken through the insulation. I returned the deflection yoke to the Crosley distributor and he claimed that the yoke was improperly installed and that the yoke itself was not defective.

The unit appears as if it can be taken apart and possibly repaired. Who is responsible for the trouble and can the yoke be repaired?—J. C., Los Angeles, Calif.

The mechanical defect described sounds very much like the result of pressing the deflection yoke hard against the bell of the picture tube. Whoever installed the yoke may have pushed it forward in the hope of getting greater width. The insulation between the vertical winding and the core of the yoke will often break under these conditions.

If the yoke has not been damaged through overheating, it could probably be repaired as follows: Remove the yoke from its bracket. Then remove the core clamp and the four iron-core sections. Wrap a few turns of Scotch tape around the winding. This done, replace the cores and wrap more tape around them. Finally, replace the core clamp and tighten. When you replace the yoke in the bracket, do not apply too much pressure against the bell of the picture tube. This is a good rule to follow for all deflection yokes.

**Insufficient width**

I have a CBS-Columbia 1601 chassis about 1 inch shy in width. This set has no width control so I tried increasing the voltage on the screen grid of the horizontal output tube. The width increased but the picture was very non-linear. The set doesn't have a linearity coil either and with all my checking I can't seem to obtain the additional width. Would installation of some sort

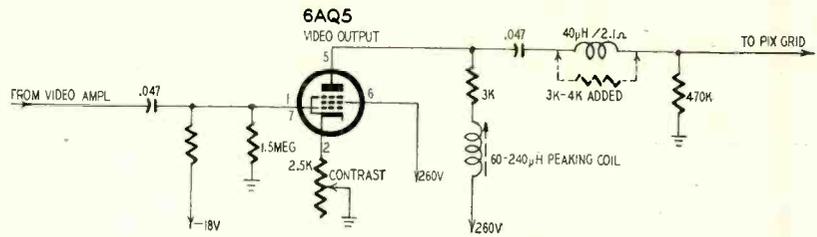


Fig. 4—Video output of Philco R-191. Addition of resistor prevents ringing.

of drive control help? At present there is a 100-µmf capacitor from the grid of the horizontal output tube to ground.—N. L., Erie, Pa.

You did not mention whether you replaced any tubes. If not, replace the horizontal oscillator and output tubes. If this doesn't help, remove the 100-µmf capacitor from the grid of the horizontal output tube to ground. Most likely this will give you more than enough width. If so, replace this capacitor with a trimmer with a range of about 25 to 100 µmf. It will act as a drive control and can then be adjusted for proper width.

**High-voltage fuse trouble**

A very bothersome condition exists in a Du Mont model RA-166. A ¼-amp fuse in the high-voltage section blows about every two weeks. I have replaced several fuses and have had it in the shop twice. All components check good and all voltages check with the manufacturer's service notes. Some component is probably critical but still good enough to check O.K. I would appreciate any service notes covering this trouble.—M. S., Fort Wayne, Ind.

Intermittent high-voltage and horizontal sweep troubles that blow this fuse are difficult to pin down, and I know of no characteristic trouble in this chassis causing this. Occasionally it is good service technique to increase the line voltage so as to hasten the breaking down of the defective component.

However, this places a burden on all the circuits and may do some harm.

A better plan in this receiver is to remove the 6W6-GT audio amplifier tube. With this tube out, the horizontal sweep pulse, the boost voltage and the high voltage increase. Thus, increased voltages are placed on the circuits with the possible defective component without increasing the B-plus voltage.


It is just possible that the fuse is blowing as the result of harmless voltage fluctuations. Try using a ¼-amp slow-blowing fuse.

**Oscillations in picture**

The complaint on a Philco R191, D191 was that when the contrast control was varied, various types of wavy lines would appear on the picture. I checked the video signal on the picture-tube grid and found that at certain settings of the contrast control oscillations would appear on the picture-tube grid and I got erratic readings. I then replaced every component in the video output stage—but still no improvement.—F. T., Fort Worth, Tex.

This circuit contains a 40-µh peaking coil between the plate of the 6AQ5 video output tube and the picture tube. See Fig. 4.

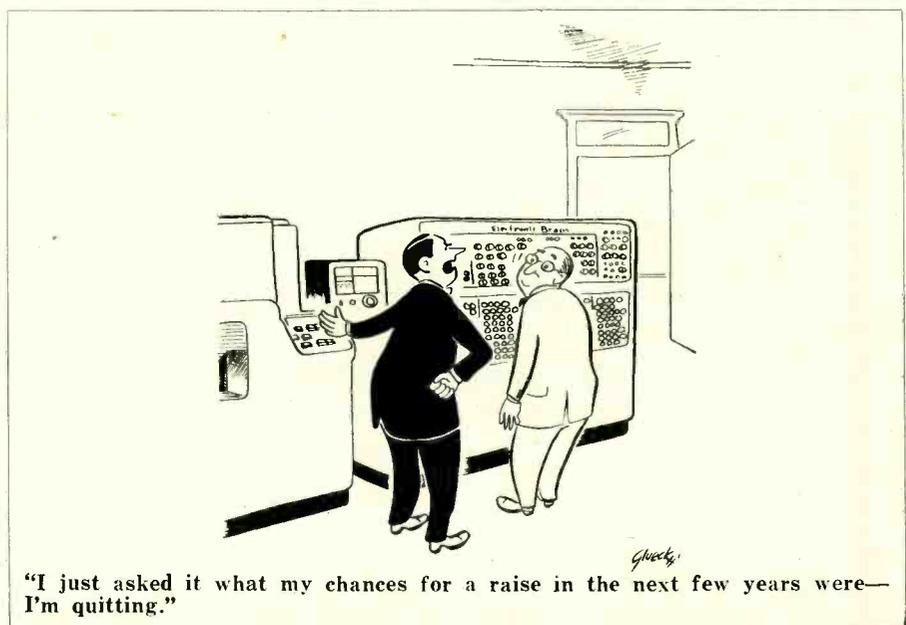Generally, the oscillation you describe is caused by insufficient dampening of this peaking coil. You can probably clear up the trouble by shunting the coil with a resistance of about 3,000-4,000 ohms. END



# LICENSING BAD or GOOD ?

By JOHN A. WHEATON\*

LET'S summarize some of the arguments for and against licensing and see who has or who wants licensing—and why. First, various points raised *against*:

- Possibility of regimentation
- Possibility of bureaucratic interference

\*Secretary, National Electronic Technicians & Service Dealers Associations.

Will not prevent fraud and malpractice

Will raise the service costs  
Next, various points expounded for:

If a license law is written *correctly* and enforced properly,

it establishes a minimum standard of qualification of competency;

it tends to raise the standards in the service business;

it provides an official body to deal with fraud and malpractice;

it tends to reduce fraud and malpractice by deterring persons for fear of losing a license.

At present, the only license law which provides a measure of the points itemized for licensing is that of Madison, Wis. It has been in effect since the early Forties. However, shortcomings are indicated in an inquiry made by the writer as secretary of National Electronic Technicians & Service Dealers Association (NETSDA). Ten shops in Madison were queried. Four answers were received. These mentioned the lack of apprenticeship provisions in the license law and pointed out that *anyone* was permitted to work for a licensed man. On the good side, indications were that malpractice was reduced and that a lot of part-timers with no genuine interest were discouraged from service activity.

Several groups around the country are pressing for a license law. Perhaps the longest in point of activity is the license law before the Council of the City of New York, sponsored and supported by Associated Radio Television Servicemen of New York (ARTS-NY) and their mentor, Max Liebowitz. More recently, Television Service Association in Detroit has been sponsoring a bill in that city.

On the state level, the Utah Association of Radio & Television Servicemen is trying to get a bill passed in Utah; the Radio-Electronic Technicians Associations of the South is trying for one in Louisiana and the Middle Tennessee Television Technicians Association is encouraging the passage of a bill for Tennessee. Several California groups are supporting a bill for that state.

Several of these bills have been reviewed and even reprinted in magazines as well as association papers. The *Guild News*, monthly publication of the Radio Television Guild of Long Island, published the New York City bill in toto, and also shortly thereafter published an article of mine comparing the Madison law and the Louisiana, Utah and the New York City bills. Sufficient response developed from this brief comparison to make it bear repeating.

To begin with, let's examine the purposes expressed in each of the four:

**Madison (in effect):** To provide minimum regulation to insure safety to persons and property, safe and stable design, and good workman-like methods of construction.

Utah: To regulate practice of servicing TV and radio receiving apparatus.

Louisiana: To protect public welfare by providing competent service technicians in all fields.

New York City: For correcting TV service contracting abuses.

The next point: who is required to have licenses? (Fees required vary from \$5 to \$25 per year)

Madison: Three licenses issued:

Radio and electronic technicians (all electronic devices)

Sound technicians (limited to devices operating on less than 100,000 cycles)

Radio and TV dealers

Utah: Four licenses:

Service contractor

Service dealer

TV-radio technician

TV-radio apprentice

Louisiana: Four licenses:

Technician, class B (specialty technician, must state service field in application)

Technician, radio and TV, class A (applicants must be qualified for radio and TV, public-address and intercommunications servicing)

Technician, industrial electronic

Technician, medical electronic

New York City: Three licenses, one permit and one temporary permit:

Television service contractor

Television service dealer

Television service technician

Television service apprentice

The type of license indicates the range of occupations covered by each: Madison covers servicing of radio and television as well as other electronic devices, sound cars and trucks, installation of various types of equipment. Utah adds the service contractor and apprentice groups to those required to have a license. Louisiana provides a more complete service technicians' requirement—in separating the licenses for the various fields of radio and TV industrial equipment and medical equipment servicing. New York City is chiefly concerned with TV servicing.

Common to all bills is the creation of an examining board to administer and regulate the license:

Madison: Five members, the first three having a two-year term:

a holder of both a radio and TV technician's license; radio and TV dealer's license and engaged in that business;

a holder of a radio and TV technician's license and an employee in that business;

a communications engineer;  
the city radio technician;  
the city electrical inspector.

Utah proposes to create a board of five members who shall have a two-year term. The makeup of the board is not specified in the bill, but is suggested by the Utah Associated Radio-TV Servicemen (ARTS):

an attorney from the state's legal department;

a member of the board of education;

a service contractor with a license under the bill;

a service dealer with a license under the bill;

a person engaged in business or occupation of servicing TV or radio equipment for two years preceding and with a license under the bill.

Louisiana goes a step further than any of the others: a State Board of Registration of seven members is to be created under the bill. Five of these would be selected from the general radio and television field, all duly licensed under the act. The other two must have at least six years' experience continuously as technicians in all phases of electronics and also be licensed under the act. They would serve a four-year term but no more than two to be replaced each year. The members of the board are to be selected by the Governor from nominees proposed by the Radio & Electronics Technicians Associations of New Orleans and Baton Rouge, sponsors of the bill, and any other state-chartered association.

New York City provides in its proposed license bill for an eight-man board more complete and diversified than the others, but indicates only the occupation of each:

a member of the Board of Education and designated by the Superintendent of Schools;

a person with a baccalaureate degree in physics or electrical engineering, and a member of the IRE engaged in electronics for five years previous to appointment;

a technician who has serviced electronic products for ten years and TV receiving apparatus the last three years;

a service contractor;

a service dealer;

a television distributor's service manager;

a distributor; the above four to have been in the business for three years prior to appointment.


All these bills have as their main purpose a desire to serve the public interest; they also express—between the lines—the desire of the electronic service technician to raise the standards of his profession and obtain a measure of prestige which does not exist to any degree at the present time. That many men in the business realize that fact is evidenced by the changing attitude of various groups during the last few years. NETSDA for some years has taken the stand that licensing was a local problem and offered assistance to any member association on whichever side that particular association might find its best interests lay; the National Alliance of Television & Electronic Service Associations (NATESA) for a

time not committed either way, has for some period now taken an identical stand. The National Appliance & Radio Dealers Association (NARDA) although at one time very definitely against licensing, now also has turned to a position of local option. The Empire State Federation of Electronic Technicians Associations (ESFETA) has for several years held that, if licensing became necessary, it would be preferred on the state level. As recently as last April ESFETA supported a decided trend toward licensing at a Consumer's Counsel discussion called by Governor Harriman of New York State and offered assistance to the state's legislative bodies in drawing up such a measure. The Federation of Radio Servicemen's Associations of Pennsylvania (FRSAP) has favored a state license and is supporting one, as are other state groups previously mentioned.

Some groups prefer an industry-sponsored accreditation program, evolved through a system of approved courses. The Minnesota Television Service Engineers group has formed a working arrangement with the Bureau of Apprenticeship of the State of Minnesota, with courses designed to raise the standards of service. The long-range benefits of such programs are obvious. But they do not provide immediate benefit beyond, perhaps, indicating to those who have the opportunity to take the courses the best way to run their business as well as to increase their knowledge of servicing.

As a sidelight on the aspects of licensing, consideration might be given to a license law which has been in effect in New York State since 1921 and concerns an occupation which might, like ours, be classified as a semiprofession: that of real estate brokers and salesmen. That it has benefitted the public as well as the sellers of real estate cannot be disputed. This law also provides for a board of men licensed under the act to advise the Secretary of State, under whose jurisdiction this law comes. It also provides for examination, as well as stipulating the field of activity in which real estate brokers and salesmen are permitted to work. To be worthy of support of all those engaged in a given activity, a licensing law must meet these minimum requirements: an examining board on which the licensed profession is represented, an examination to provide at least a minimum qualification of licenses and provision for all classifications of activity of the particular field to be licensed, with limitations provided for apprentice classifications. Any license law which omits any of these minimum requirements should be questioned.

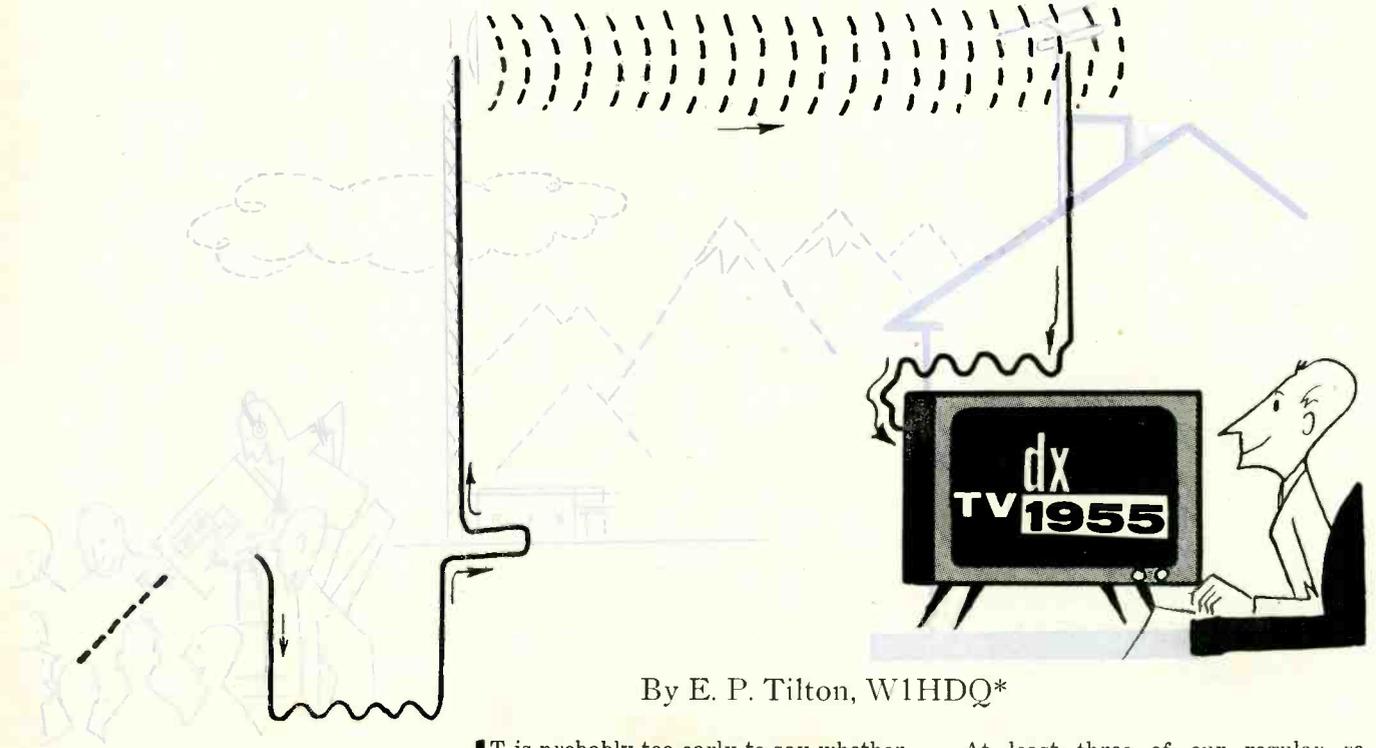As has been pointed out in *Guild News*, if any person (or group) says—without reference to a particular piece of legislation—that he is for or against licensing, he is committing himself to an unknown quantity. Consideration must be given to all aspects, and the specific type of licensing proposed, before making a decision. END



By E. P. Tilton, W1HDQ\*

It is probably too early to say whether it was the result of the rising curve of the new sunspot cycle we're just entering, but 1955 was a banner year for TV dx enthusiasts. The winter period ran longer and produced more dx per day and the summer season held on for weeks later than in some past years. There was more multiple-hop dx and more reception of South American stations than ever before.

\* V.h.f. editor, QST.

At least three of our regular reporters now have identified 200 or more TV stations. Robert Seybold (Dunkirk, N. Y.) tops the list with a total of 259. Bob has logged 45 of the 48 states and 6 countries. In his odd moments he has managed to photograph identifications of more than 150 of his catches!

Bedford Brown, Jr., Hot Springs, Ark., has received stations in 42 states and 9 countries in running up his 228-station list.

In addition to the tropospheric bending associated with weather, sporadic-E skip and other forms of propagation discussed many times in these pages, our sharper observers are finding that "burst" reception offers fine opportunities for catching new and difficult stations. Such bursts may come as the result of reflections from high-flying



Champion dx-er Louis Matullo's antenna system and some veris photographed by Matullo himself.



# INTERMITTENT FOLDOVER

By CHARLES E. THOMAS

aircraft, from ionized regions near lightning discharges or from the ionized trails left by meteors as they pass through the E region of the ionosphere, to name some of the more likely sources.

Some typical catches (see photos) by veteran TV dx-er Lou's Matullo, Washington, Pa., are: Cuban CMQ and KFDX, Wichita Falls, Tex. (received by sporadic-E skip); WMBV, channel 11, Green Bay, Wis., 500 miles and WBKB, channel 7, Chicago, 450 miles (high-band tropospheric dx); WIN-T, channel 15, Waterloo, Ind., 200-mile u.h.f. reception (also tropospheric in nature). The antennas used are broadbanded Yagis for the high and low bands, with 12 bowties in phase stacked between the two bays. Matullo has photographed identifications of 136 of the 194 stations he has logged to date.

Distances over which burst reception is possible range from a few hundred miles to perhaps 1,500 miles or more. Individual bursts are usually of no more than a few seconds' duration, but several may overlap making possible reception of a signal for several minutes at a time. Several observers say that they get best results in burst hunting by turning their antennas in a likely direction and then simply monitoring a blank channel where a distant station is known to be operating. Western observers try this in the early morning hours before their local stations come on the air. As the average level of burst signals—particularly those of the meteor-scatter variety—is low, effective work of this kind calls for a sensitive receiver, a large antenna, a quiet location and not a little patience. But it does wonders for one's totals! Observer Schafer of Kenmore, N. Y., has added 19 stations that way.

The fall hurricane season along the Atlantic and Gulf coasts produced plenty of dx. (Practical example of ill winds blowing good!) The air circulation pattern associated with a tropical storm may set up sharp temperature and humidity gradients in the upper atmosphere for hundreds of miles around the storm. A hurricane in the West Indies, for example, may mean fine tropospheric dx for TV enthusiasts and v.h.f. hams from the Carolinas to Nova Scotia. It happened again and again in the fall of 1955 and observer Frank Greene, Roswell, N. M., reports that the weather fronts associated with tornado conditions in the West Texas plains bring similar results for him.

Reception of South American stations is increasing, with Venezuelan, Brazilian and Argentine stations being logged in nearly all parts of the country. Not only are more Latin American stations coming on the air, but the increasing sunspot activity is very likely helping things along. From the more southerly parts of North America, particularly, it will become increasingly easy to pick up our South American friends as the solar cycle rises higher. If it follows amateur

experience in the 50-mc band, South American TV reception should be most frequent in the afternoon and early evening hours of the spring and fall months, becoming more common in the next few years. This will be in addition to the multiple-hop sporadic-E skip that peaks in June and July.

Observer Machado of Mendoza, Argentina, reports almost daily reception of Caracas, Venezuela, on channel 2 in February, March, April, October and November. As will be seen, these periods do not coincide with our twice-yearly sporadic-E seasons. They do, however, check with 50-mc amateur observations in these countries taken during the higher part of the previous sunspot cycle. South Americans are worth plenty of watching!

## Over 50 TV DX Club

NAME	LOCATION	TOTAL UHF	BEST DX (miles)
Robert Seybold	Dunkirk, N. Y.	259	4,900
Bedford Brown, Jr.	Hot Springs, Ark.	228	5,200
Dorsey W. Akers	Charleston, W. Va.	202	1,200*
Louis A. Matullo	Washington, Pa.	194	35 2,000
Art Collins	Buffalo, N. Y.	175	28
Delwin D. Whitt	Grand Prairie, Tex.	171	
Fred Von Gunten	Berne, Ind.	154	20
Robert Weems, Jr.	State College, Miss.	144	1
John Betterworth	State College, Miss.	139	1,800
Richard Lowry	Temple, Tex.	135	5,800
Russell Ashworth	New Bedford, Mass.	121	22
Gary Cooper	South Bend, Ind.	121	7 5,400
Bob Cooper	Fresno, Calif.	118	8 6,600
Raymond Sloss	Baton Rouge, La.	117	
Billy Don Sevier	Corpus Christi, Tex.	115	2
Joseph Rombach	Arabi, La.	112	4
F. E. DeCrot	Salamanca, N. Y.	112	
Kingdon P. Schafer	Kenmore, N. Y.	108	
Edward Rugel	Independence, Kan.	108	
Parrissa C. Cox	Visalia, Calif.	103	2,400
Michael O'Rourke	Mesick, Mich.	103	
Roger Anderson	Madison, S. D.	99	26
Tommy Larkins	Clarksville, Tenn.	97	
Paul Swartz	Glynn, Ohio	90	
Sam Brooks	Boston, Ga.	90	
M. W. DeGeer	Tulsa, Okla.	88	
Gordon Simkin	Ft. Lee, Va.	88	9
Douglas Bryan	Otey, Tex.	86	
Walter Owens, Jr.	Springfield, Ohio	85	
Ronn DeNeuf	Ithaca, N. Y.	83	12
Ernest I. Smith	Clarksville, S. C.	81	2,300
Alton Caldwell	Brockton, Mass.	81	4
Paul Mitschler	Marysville, Kan.	81	
Toby Chambers	Miami, Fla.	76	1
B. H. Rauch	Peoria, Ill.	76	1,750*
Dick Mason	Menasha, Wis.	75	
Larry Veborn	Indianapolis, Ind.	73	14 1,460
C. P. Oberst	Richmond, S. C.	73	4,700
Joe Foyer	Westville, Ill.	72	15
Mrs. Wm. Callan	Altoona, Pa.	72	
Clyde C. Barber	Okmulgee, Okla.	71	
Kenneth C. Bush	Buffalo, N. Y.	71	
James M. Honan	Biloxi, Miss.	70	
D. B. Middleton	Sanford, Fla.	68	4,800
Larry Wash	Monroeville, Calif.	68	
Ross Brown	Lupperville, Ont.	66	
George A. Quay	Allentown, Pa.	66	
Danny Startzman	Bennington, Kan.	64	
Edward Fournier, Jr.	Bradford, R. I.	64	
Stanley Brown	Barstow, Calif.	63	2,400
R. A. Wilson	Detroit, Lakes, Minn.	62	
Frank Greene	Roswell, N. M.	62	
Carl F. Lupton	Shelbyville, Ill.	61	
Barry Rossum	Nohall, N. Dak.	61	
Don Martin	De Ridder, La.	60	
Donald G. Sanford	Viola, Wis.	59	
F. H. Schinakenburg	Honesdale, Pa.	59	
Harry Wieskamp	Holland, Mich.	58	14
Dennis Smith	Wasco, Calif.	55	7 2,200*
Kenneth M. Neal	Hamlin, Tex.	55	
Neil Stone	University Hts., Ohio	55	11
Irvin Englander and Tommy Mayo	Boston, Ga.	54	
Larry D. Whiting	Ilderton, Ont.	53	
Karl Kleintop	Bowmantown, Pa.	52	8
Richard Gleitz	York, Pa.	52	11
W. C. Staftard	Chambersburg, Pa.	50	
W. C. Sherman	Sinton, Tex.	50	

\*high band.

Once again we thank the hundreds of dx-ers who have taken the trouble to report their reception. The list is too long to permit running all names, so we list the more outstanding. If you report regularly and have more than 50 stations logged, include your total with each report and you'll automatically become a member of our "Over 50" clubs. END

THE complaint was "slow widening out." The set was an RCA model TC165, chassis KCS40. When I turned it on, a picture about 6 to 8 inches wide appeared on the 16-inch screen. The picture had a foldover right up and down the center of the screen, while the part of the picture on either side of the wrinkle was apparently normal in proportion. I had never seen anything like it. The beam moved across the screen in the normal manner until it got about halfway. Then it reversed, traveled back to the left a distance of about 2 inches where it again reversed itself and swept on to the right. You can imagine what such a picture looked like.


I took it to be horizontal output or horizontal oscillator trouble. The customer explained that the picture had been coming on this way each time the set was turned on but after a short while would suddenly snap out to full width. The foldover remained this way long enough for me to substitute a new 6W4, 6BG6, and 6SN7. No help.

I took the set into the shop and started checking with the scope. Every waveform from the input to the horizontal oscillator control tube to the plate of the horizontal output tube was distorted. I checked the sync input to the horizontal oscillator control tube—it was O.K. (I didn't check the peak-to-peak value of this pulse, but the shape was normal.) Since a part of the signal on the grid of the control tube is fed back from the output of the oscillator, I reasoned the trouble could still be anywhere in this circuit. One at a time each capacitor was substituted with a new one, each resistor was checked, and the horizontal oscillator transformer was replaced. Since the trouble was an intermittent one, this was a time-consuming job.

I consulted television books, service notes, and back issues of RADIO-ELECTRONICS for more information on this circuit. Some information was found but nothing gave me a clue to the trouble.

The next day the set refused to act up, and since other work was beginning to accumulate, I set the job aside for a time. When I resumed work on this set, I noticed a variation in the amplitude of the sync separator output. When it was larger than normal, the foldover appeared. This was traced to the sync limiter. This tube would open up occasionally, increasing the sync amplitude applied to the input of the control tube, the result being a distorted waveform from there to the deflection yoke. END






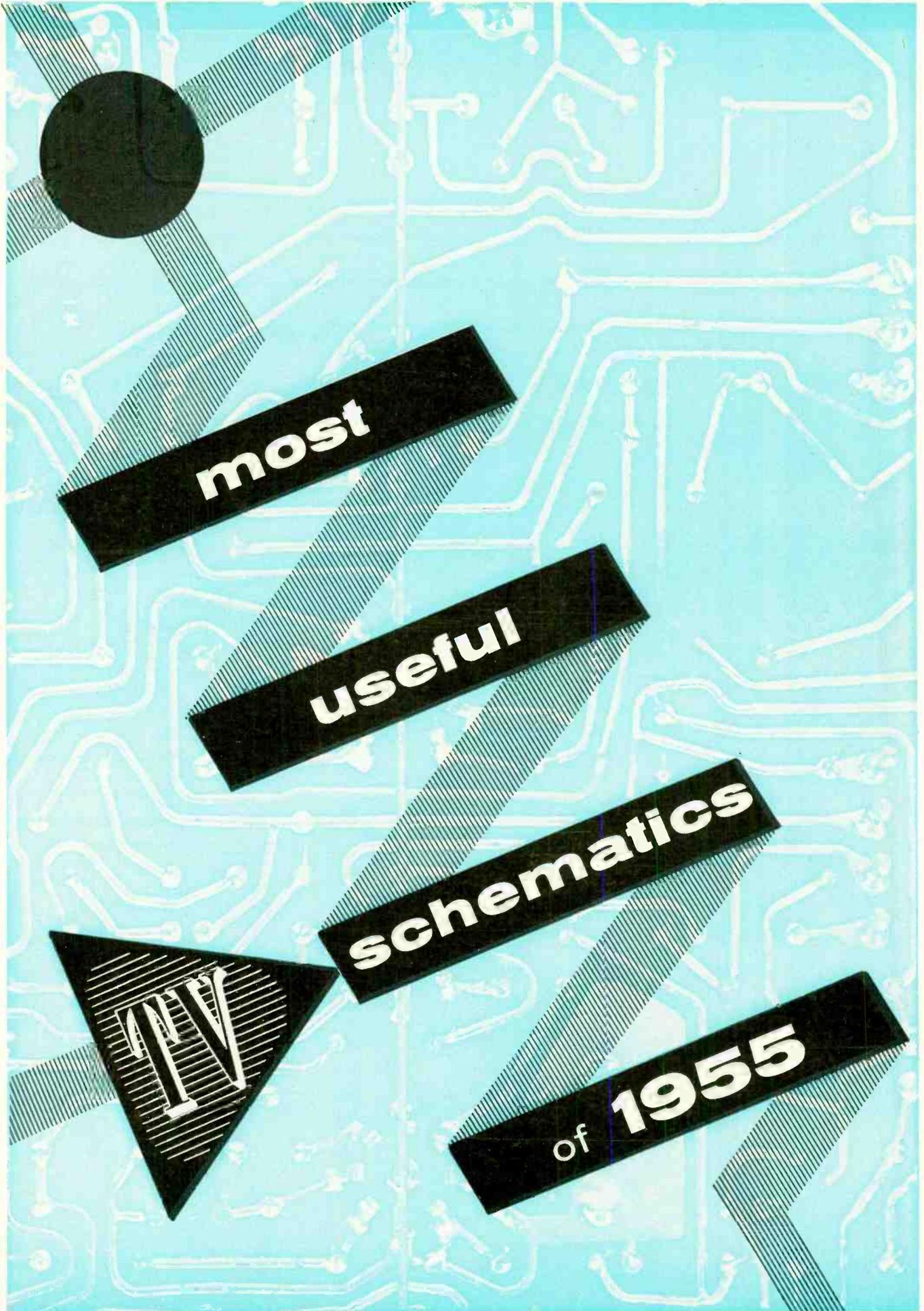

# ADMIRAL 20Y4- CHASSIS

Rear View 20Y4B Chassis.

Rear View 20Y4E, 20Y4F, 20Y4L Chassis.

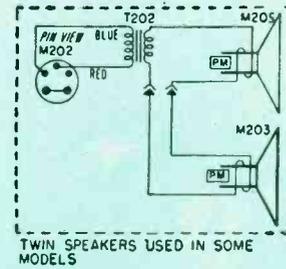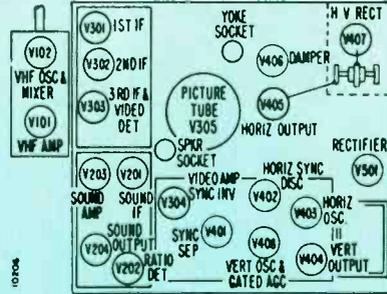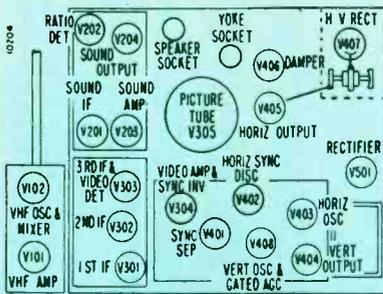


- V101-6BC8
- V102-6J6
- V201-6AU6
- V202-6AL5
- V203-6AV6
- V204-6BF5
- V301-6BZ6
- V302-6BZ6
- V303-6AM8

- V304-6AW8
- (21ALP4A
- (20Y4B,
- 20Y4E,
- 20Y4L)
- Z4DP4A
- (20Y4F)
- V401-6CS6
- V402-6AL5

- V403-12AU7
- V404-6S4
- V405-6CU6
- V406-6AU4CT
- V407-1B3GT
- V408-6BH8
- V501-5U4GA
- or
- 5U4GB

## VHF TUNER 94D92-7

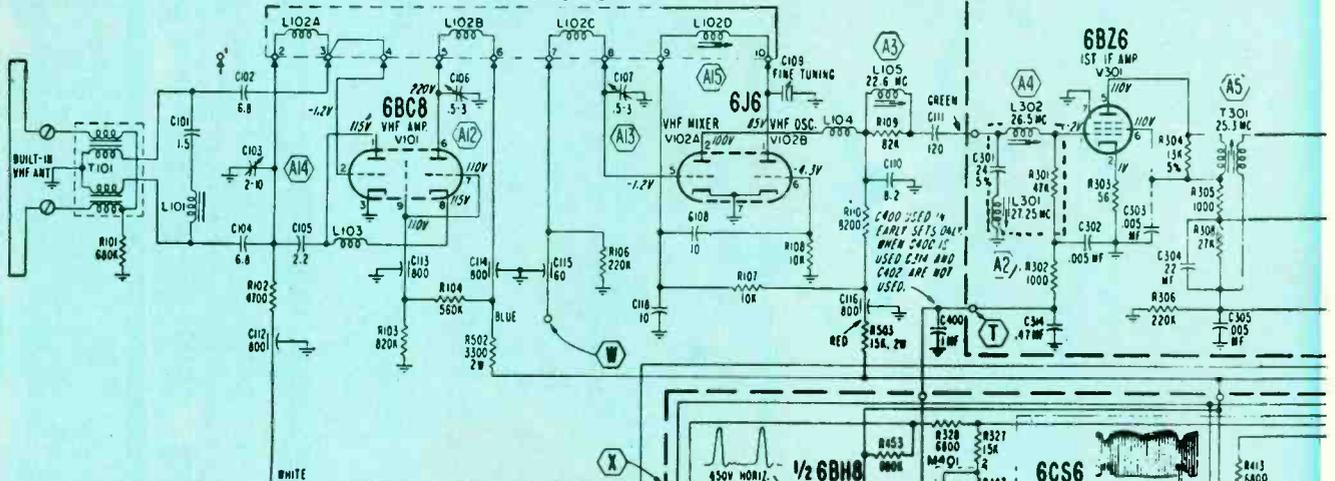

### SCHEMATIC NOTES:


Letters and numbers shown within hexagons indicate points that are adjusted during alignment and test points to facilitate voltage measurements and connecting the scope

Voltages are measured with the antenna disconnected, the antenna terminals shorted and the channel selector turned to an unused channel. The contrast control is turned fully clockwise. All other controls are fully counterclockwise. Do not disturb the horizontal lock and drive adjustments

D.c. voltages are measured between the socket terminal and chassis unless otherwise indicated. Use an adapter to measure tuner socket voltages from the top of the chassis with the tubes in place

NOTE: ARROW THROUGH VARIABLE ARM OR CONTROLS INDICATES COUNTERCLOCKWISE NOTATION AND MAXIMUM SETTING.


## SYNC BOARD A4868-1 (PRINTED WIRING)

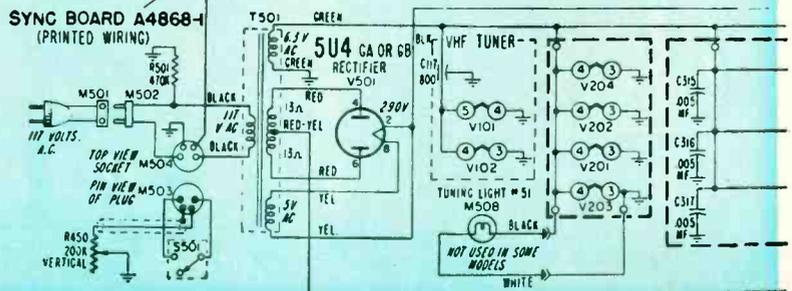

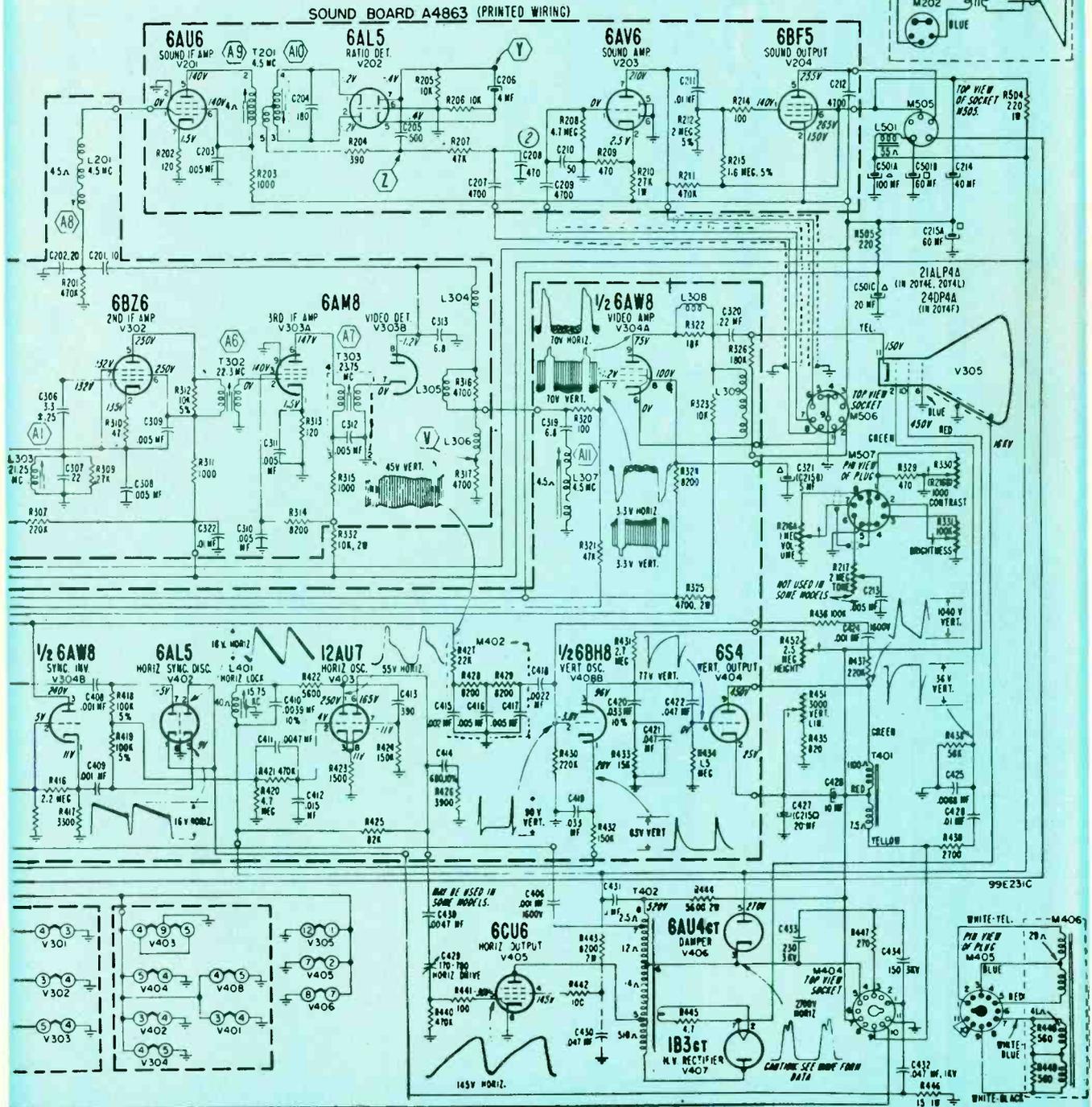
# Schematic for 20Y4B, 20Y4E, 20Y4F, 20Y4L Chassis

Conditions for Viewing Waveforms:  
Waveforms are taken with a signal input to the TV chassis. All controls are set for normal picture, NOISE GATE control fully counterclockwise. After the receiver is set

for normal picture, turn CONTRAST control fully clockwise. Set scope sweep at 30 cycles for vertical waveforms, at 7,875 cycles for horizontal waveforms, to permit observing two complete cycles



# CBS-COLUMBIA 1610 and 1611

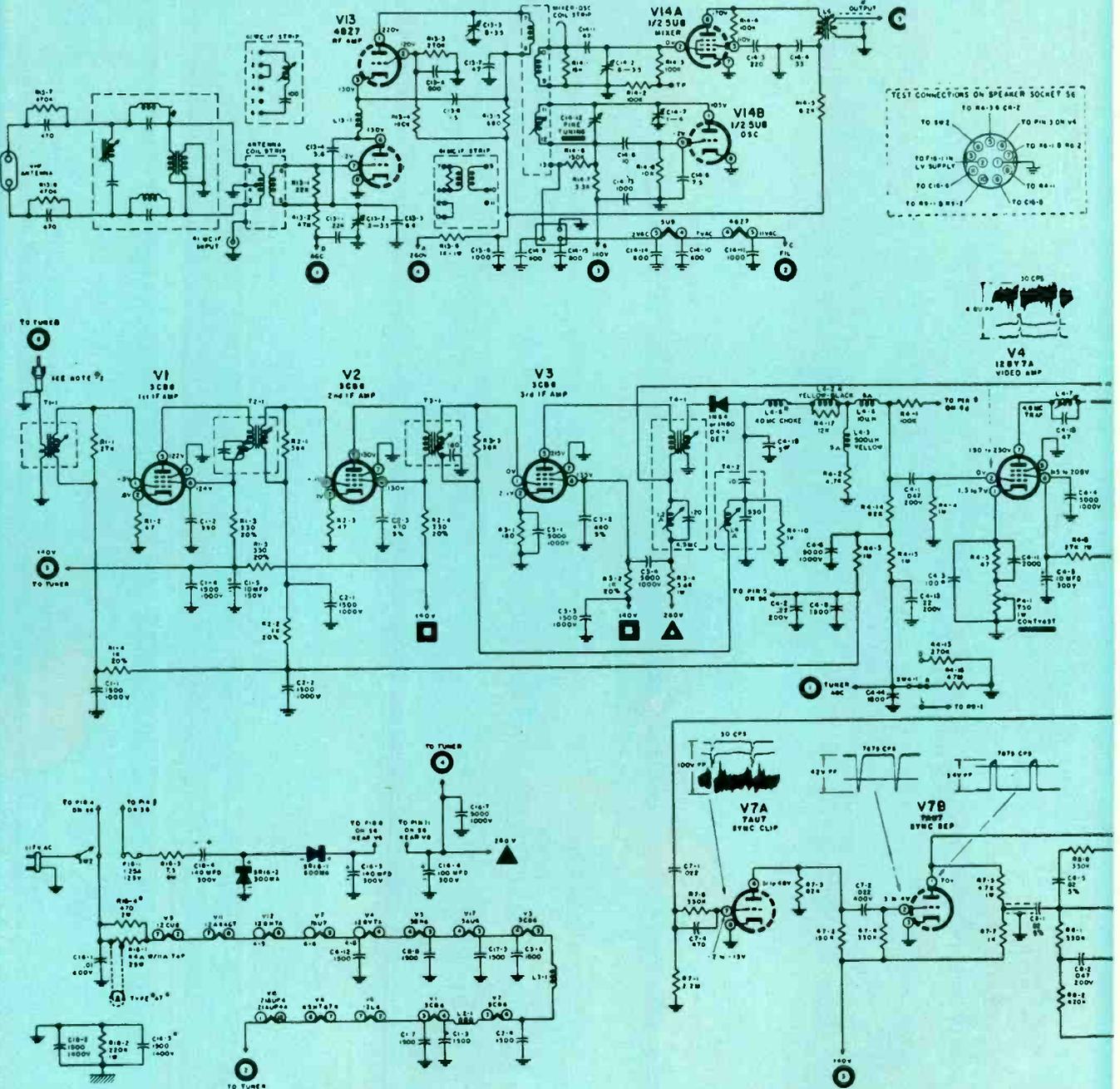

**Schematic notes:**

On the 1610 chassis, the i.f. input plugs into the tuner. In the 1611, a shielded lead that is a part of the tuner is soldered to the first i.f. transformer T1-1

Some chassis use the General Industries tuner (part 69 000 692) shown in the diagram. Others may have a GI tuner of the same general type (part 69 000 711) with the 41-mc i.f. strip, i.f. input jack, u.h.f. power receptacle and R14-6 omitted. The

remainder will have a Standard Coil tuner (part 69 000 721) using a 4BQ7-A cascode r.f. amplifier and a 5AT8 mixer-oscillator

The solid geometric figures such as the black triangle at the 260-volt line on the B plus supply at lower left and the solid square on the cathode return lead of the 12L6 audio output tube are B plus voltage sources. Similar open symbols indicate points to which the voltage is applied. Num-


bered circles are terminals for the various tuner leads

All d.c. voltages are measured with a v.t.v.m. between the socket terminals and chassis with the channel selector set between channels and the area control switch (SW4-1) set to NORMAL. When voltages depend on settings of the various controls, two readings are shown at pertinent points. One value is for clockwise and the other for counter-clockwise



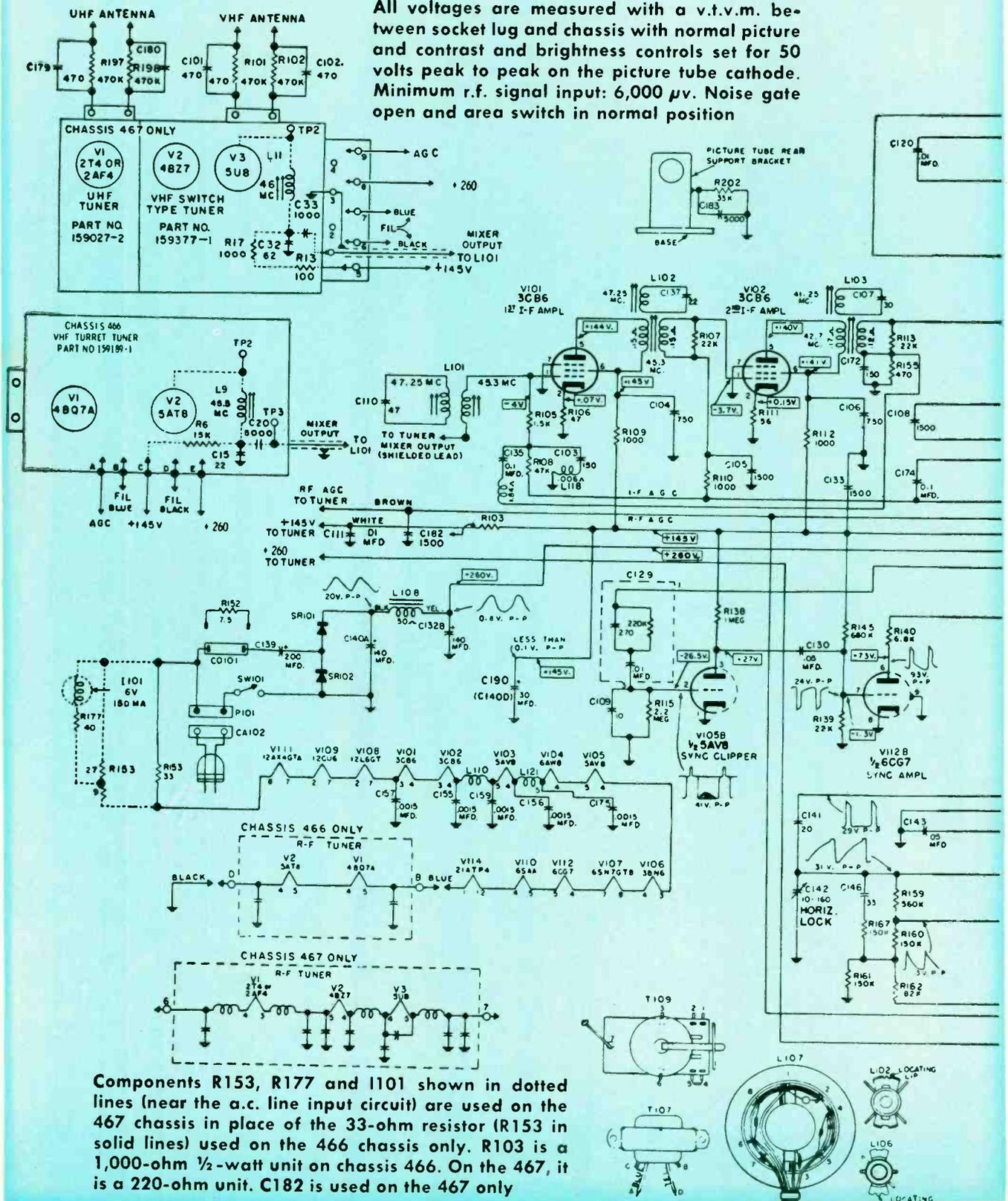
# CROSLEY CHASSIS 466 and 467 (Codes A and A1)

All voltages are measured with a v.t.v.m. between socket lug and chassis with normal picture and contrast and brightness controls set for 50 volts peak to peak on the picture tube cathode. Minimum r.f. signal input: 6,000  $\mu$ v. Noise gate open and area switch in normal position



Components R153, R177 and I101 shown in dotted lines (near the a.c. line input circuit) are used on the 467 chassis in place of the 33-ohm resistor (R153 in solid lines) used on the 466 chassis only. R103 is a 1,000-ohm 1/2-watt unit on chassis 466. On the 467, it is a 220-ohm unit. C182 is used on the 467 only

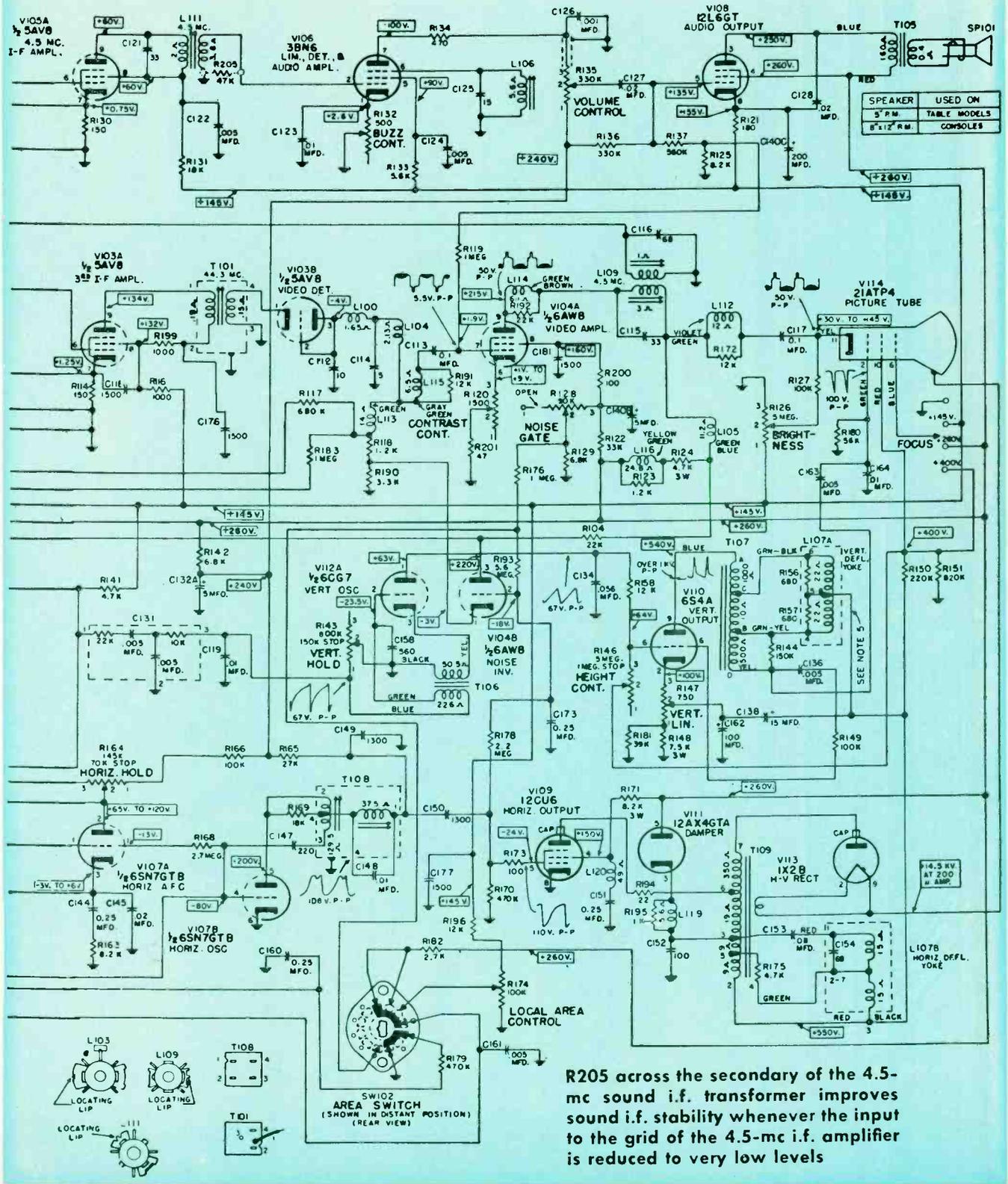**Models (466) H-21CKBF, H-21CKMF, H-21HKBF,  
H-21HKMF, H-21TKBF, H-21TKMF  
(467) H-21CKBU, H-21CKMU, H-21HKBU,  
H-21TKBU, H-21TKMU**




R205 across the secondary of the 4.5-mc sound i.f. transformer improves sound i.f. stability whenever the input to the grid of the 4.5-mc i.f. amplifier is reduced to very low levels


# MOTOROLA TV TS-525 SERIES

## VOLTAGE MEASUREMENTS:

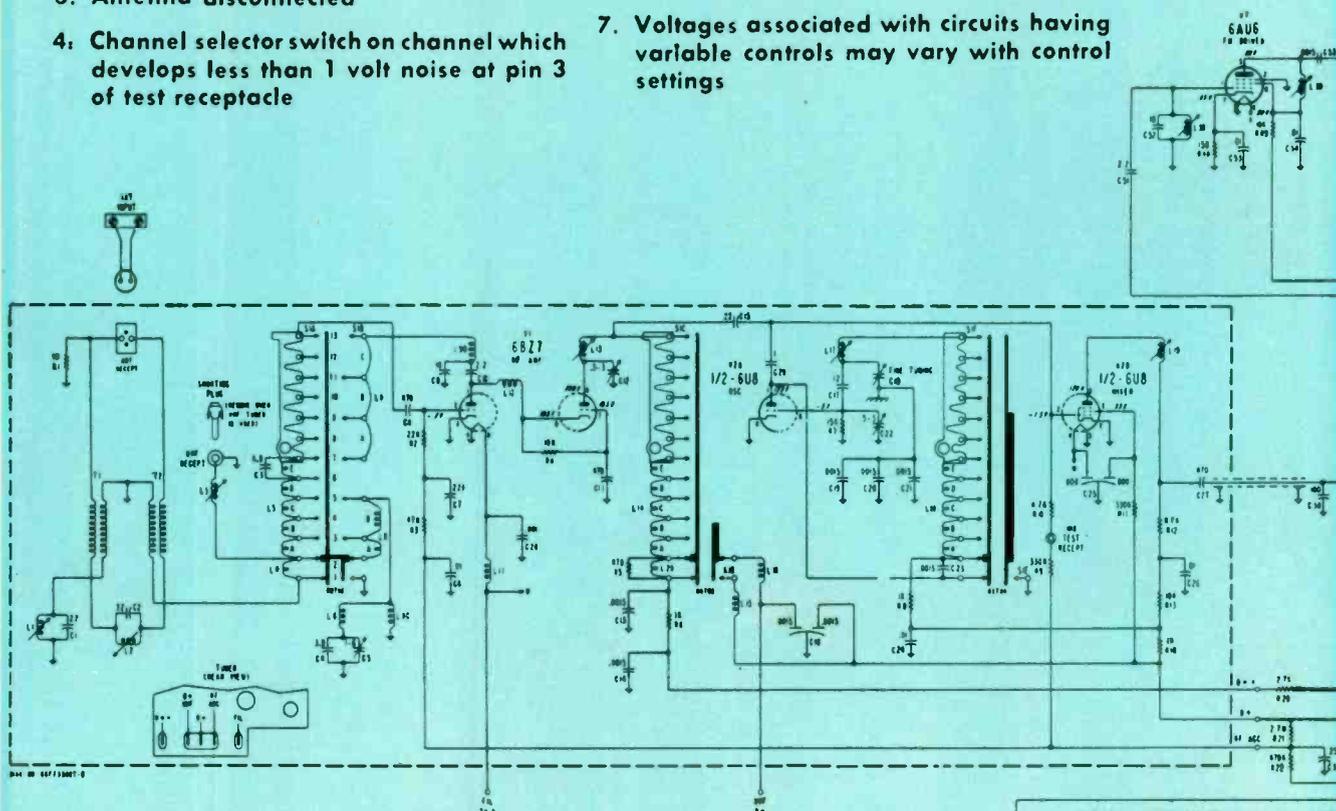1. Made with v.t.v.m. from point indicated to chassis
2. Line voltage 117
3. Antenna disconnected
4. Channel selector switch on channel which develops less than 1 volt noise at pin 3 of test receptacle
5. Contrast control maximum clockwise position
6. All other controls in normal operating position
7. Voltages associated with circuits having variable controls may vary with control settings




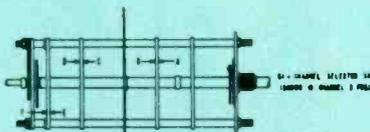CAPACITOR VALUES UNDER 1000 ARE IN PPF  
 ALL OTHERS IN MF UNLESS OTHERWISE SPECIFIED  
 ↓ - GND TO CHASSIS    ↗ - GND TO TUNER SHIELD




## WAVEFORMS:

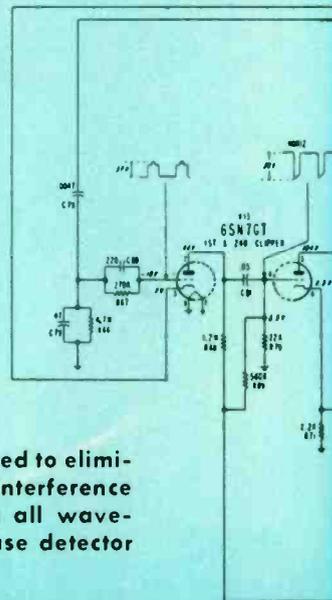1. Observed on Du Mont 241 oscilloscope
2. Contrast control set for signal of 45 volts peak-to-peak at plate of video amplifier tube
3. All other controls in normal operating position
4. Horizontal output tube removed to eliminate high-voltage pulse interference from scope when observing all waveforms except those from phase detector through horizontal circuit



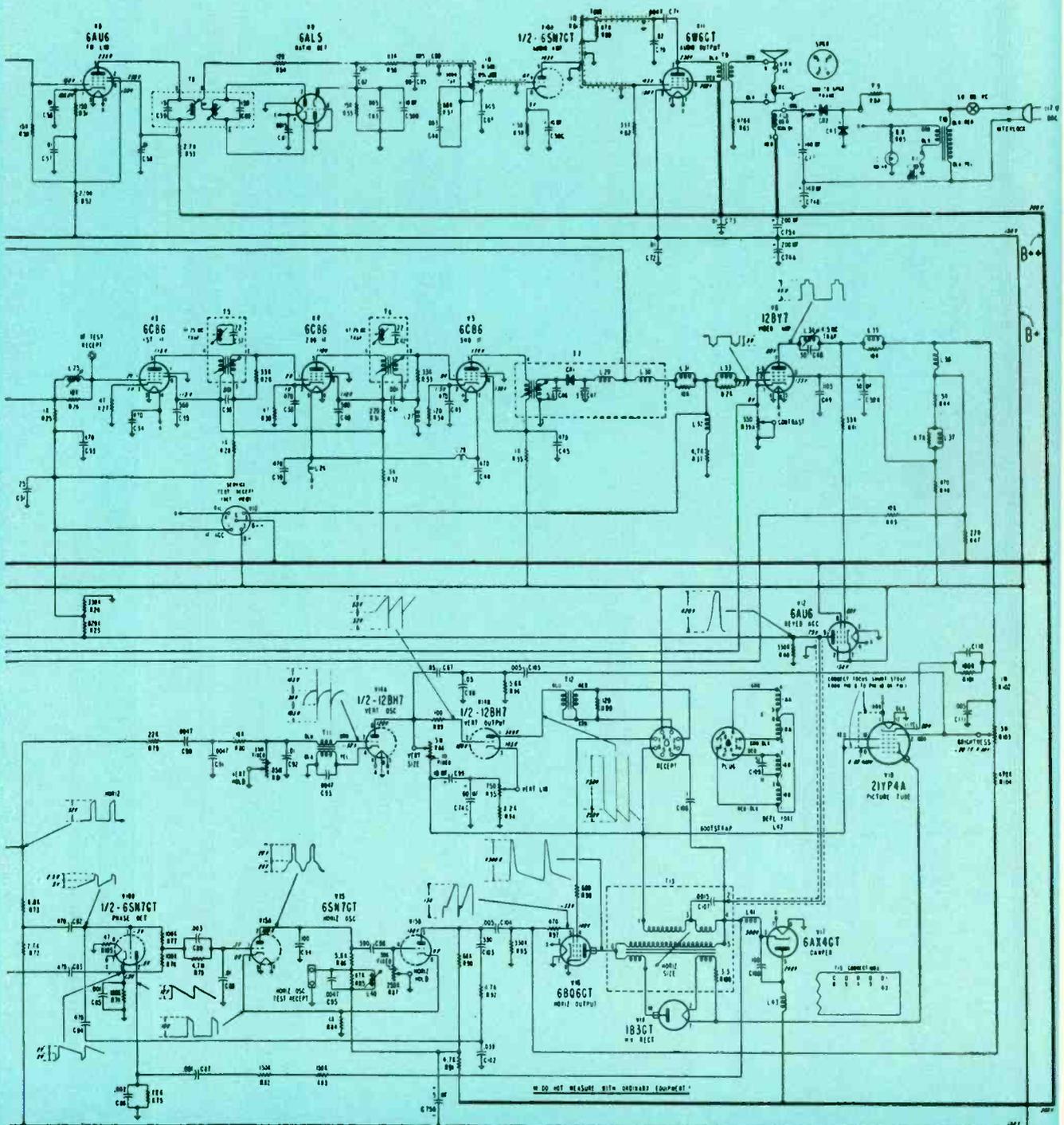
# Models 21K20, 21K20B, 21T18, 21T18B etc.

(Basic models have suffix -00.) First *minor* change makes the number 01. Example: 21K20A-01. First *major* electrical change changes suffix letter. Example: 21K20B. Additions to prefix indicate mechanical changes. Chassis TS has 21ALP4A 90° tube, RTS has 21YP4A 70° tube and WTS is same as RTS except picture tube is tilted 5%


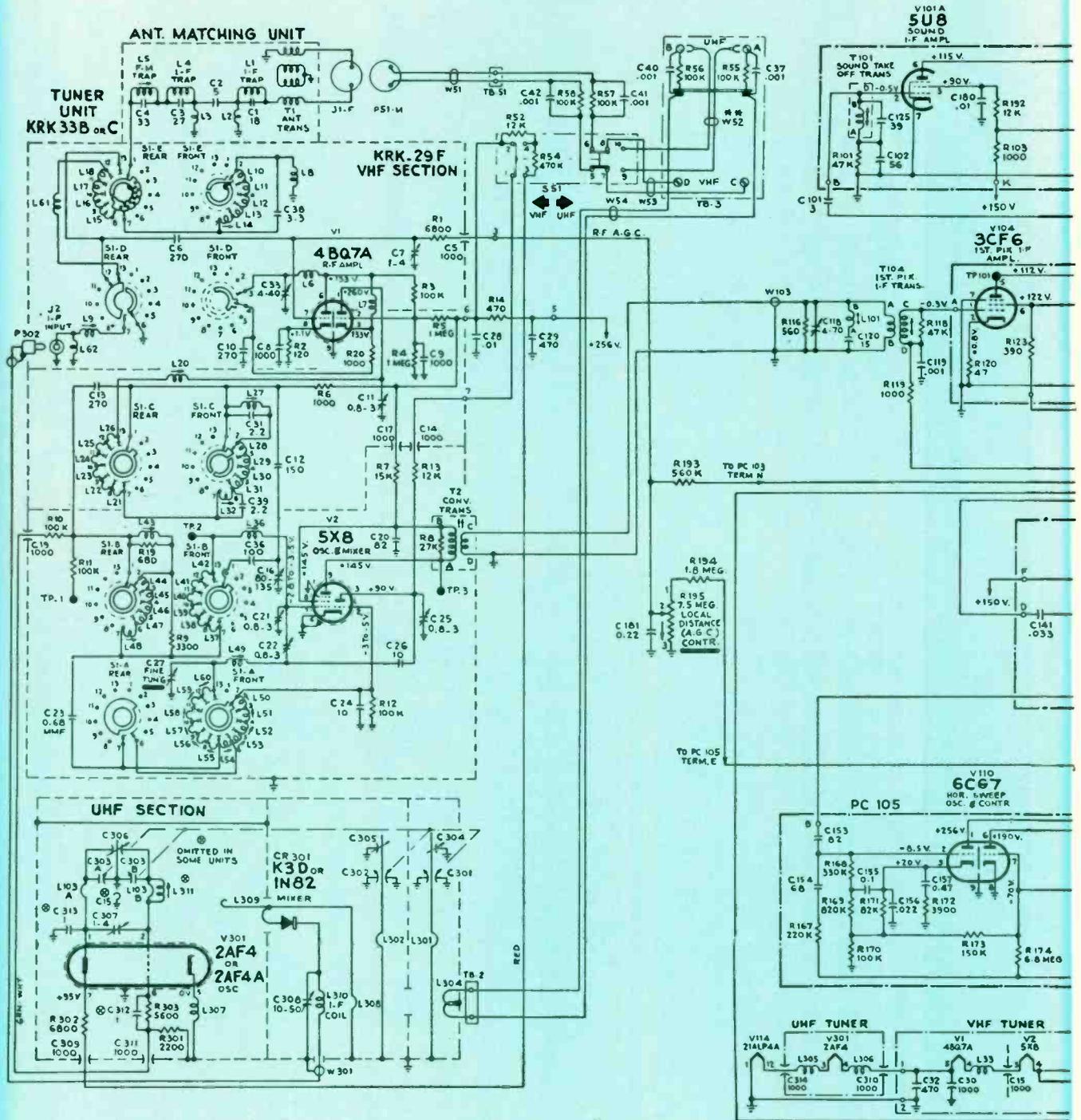
# RCA VICTOR CHASSIS KCS95B, -C

(Chassis 95 and 95A identical except that they have KRK32B v.h.f. tuner)



### IMPORTANT WIRING NOTICE


Many of the wiring connections in these receivers employ a new type solderless wire-wrap connection. These connections consist of six or seven turns of tightly machine-wrap-

ped wire around special square studs. They are both electrically and mechanically equal or superior to conventional soldered connections and should not be considered to re-

quire soldering. However, where re-wiring is required or the original tightly wrapped connection has once been unwound, conventional soldering methods must be used.

# Models 21-S-6052, 21-S-6052U, 21-S-6053 21-S-6053U, 21-S-632, 21-S-632U

(Models with suffix "U" are v.h.f.-u.h.f. receivers.)

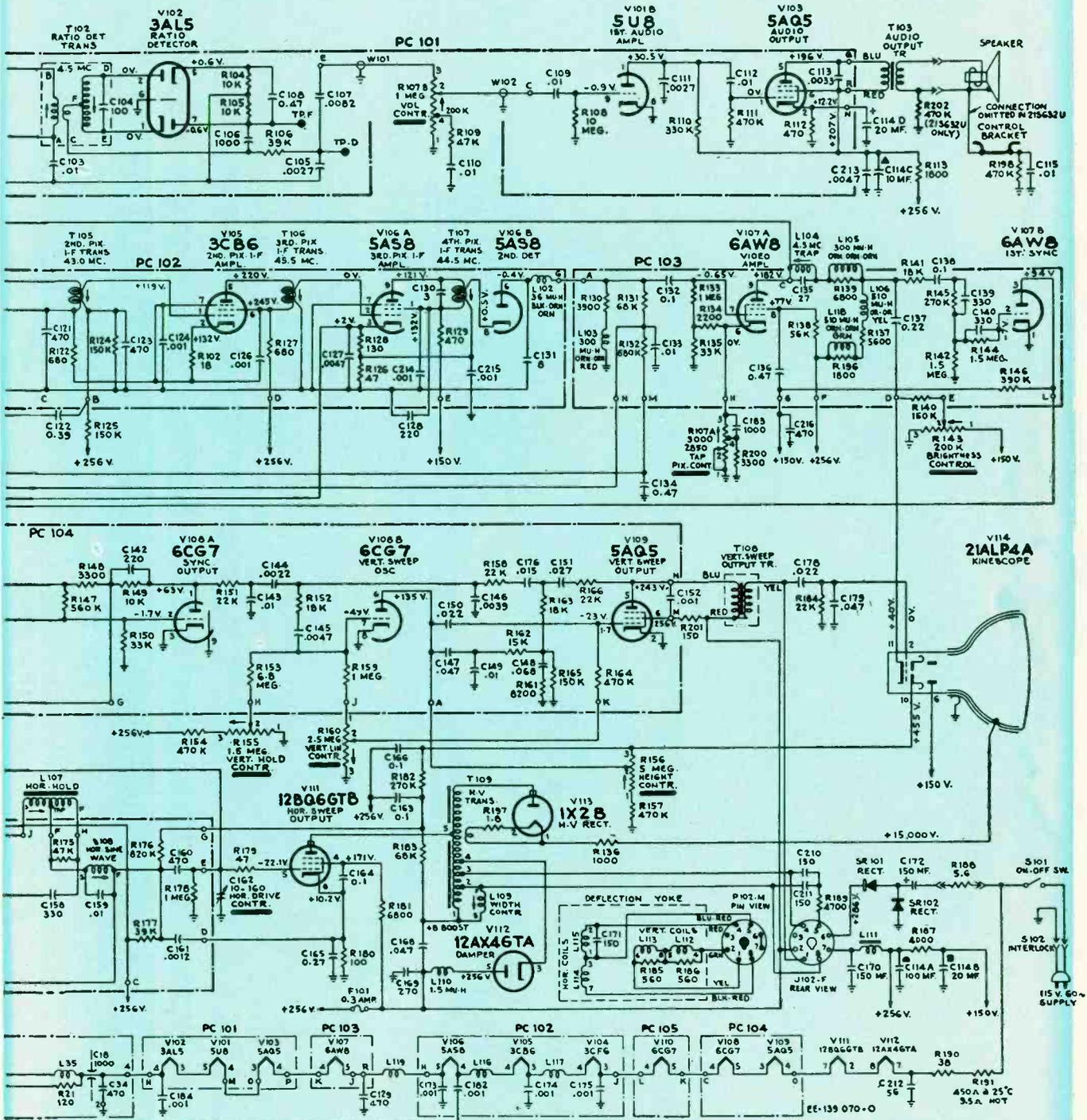


**Note 1:**

When using combination v.h.f.-u.h.f. antenna, connect transmission line to v.h.f. terminals. For separate v.h.f. and u.h.f. antennas, disconnect W52 and connect transmission lines to their respective terminals.

**Note 2:**

The channel selector switch is shown in the channel 2 position with both front and rear sections shown as viewed from the front.
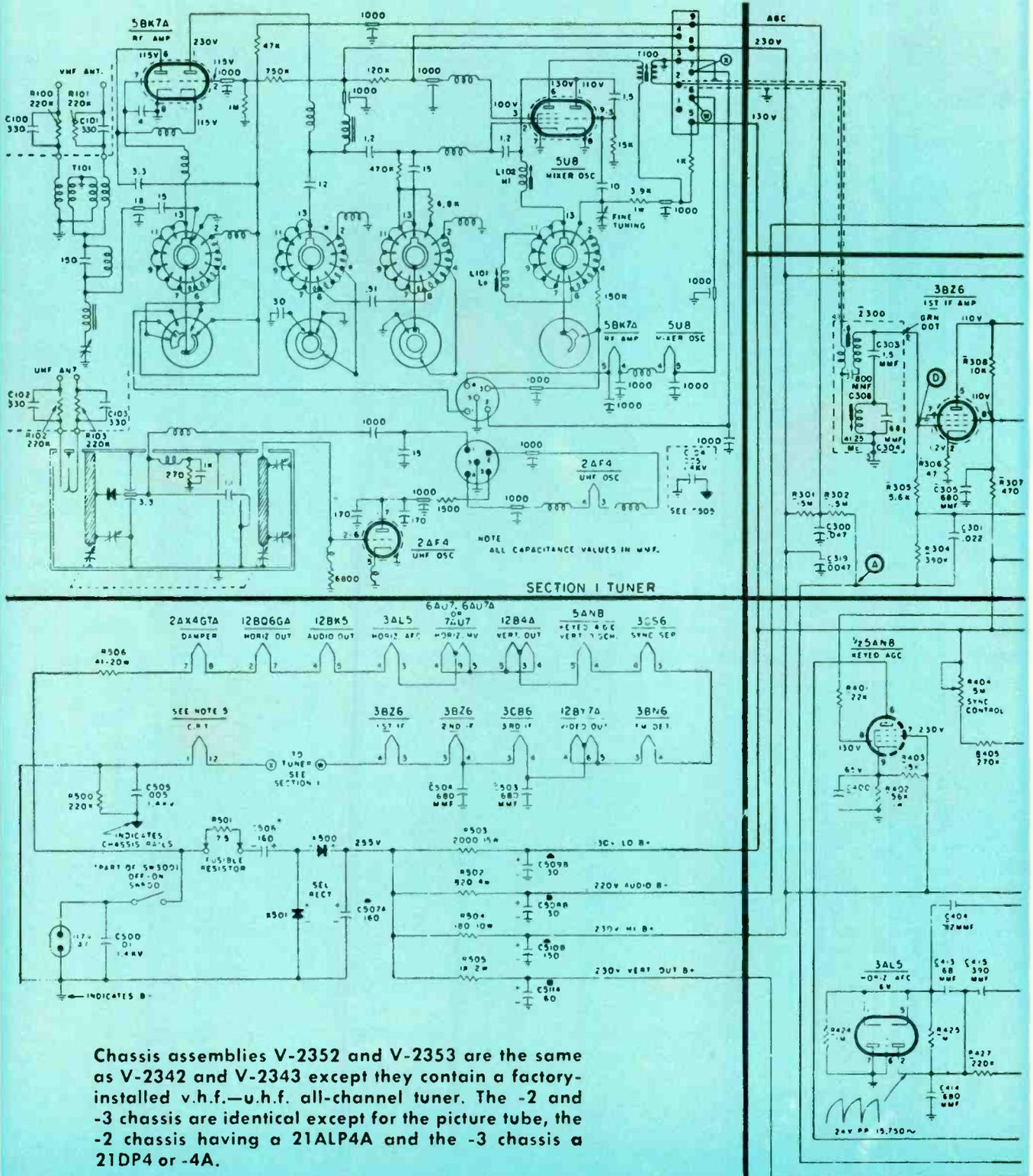
# WESTINGHOUSE V-2342, V-2352 V-2343, V-2353



Chassis assemblies V-2352 and V-2353 are the same as V-2342 and V-2343 except they contain a factory-installed v.h.f.—u.h.f. all-channel tuner. The -2 and -3 chassis are identical except for the picture tube, the -2 chassis having a 21ALP4A and the -3 chassis a 21DP4 or -4A.

Notes:


D.c. voltages measured from B minus with a v.t.v.m. and no signal applied. Peak-to-peak waveforms are taken with the picture control set for a 60-volt peak-to-peak signal at the picture tube cathode. All other controls set for a normal picture.

All capacitance values  $\mu\text{f}$ , all resistance values in ohms and all resistors  $\frac{1}{2}$  watt, unless otherwise specified.



A line above or below a code indicates the location of the part. Example: R305 is located on the i.f. board; R304 is on the sweep board. R505 (no line) indicates the part is located elsewhere.

Use 21ALP4 on V2342-14, V2352-104; 21ALP4A on V2342-24, V-2352-204; 24DP4 on V2343-14, V2353-104 and 24DP4A on V2343-24, V2353-204 chassis.

SECTION 2 SOUND I-F and AUDIO

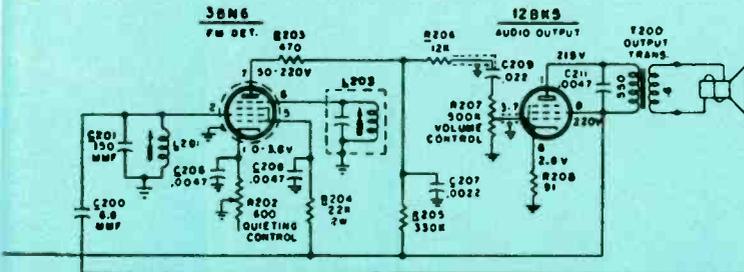

SECTION 3 VIDEO

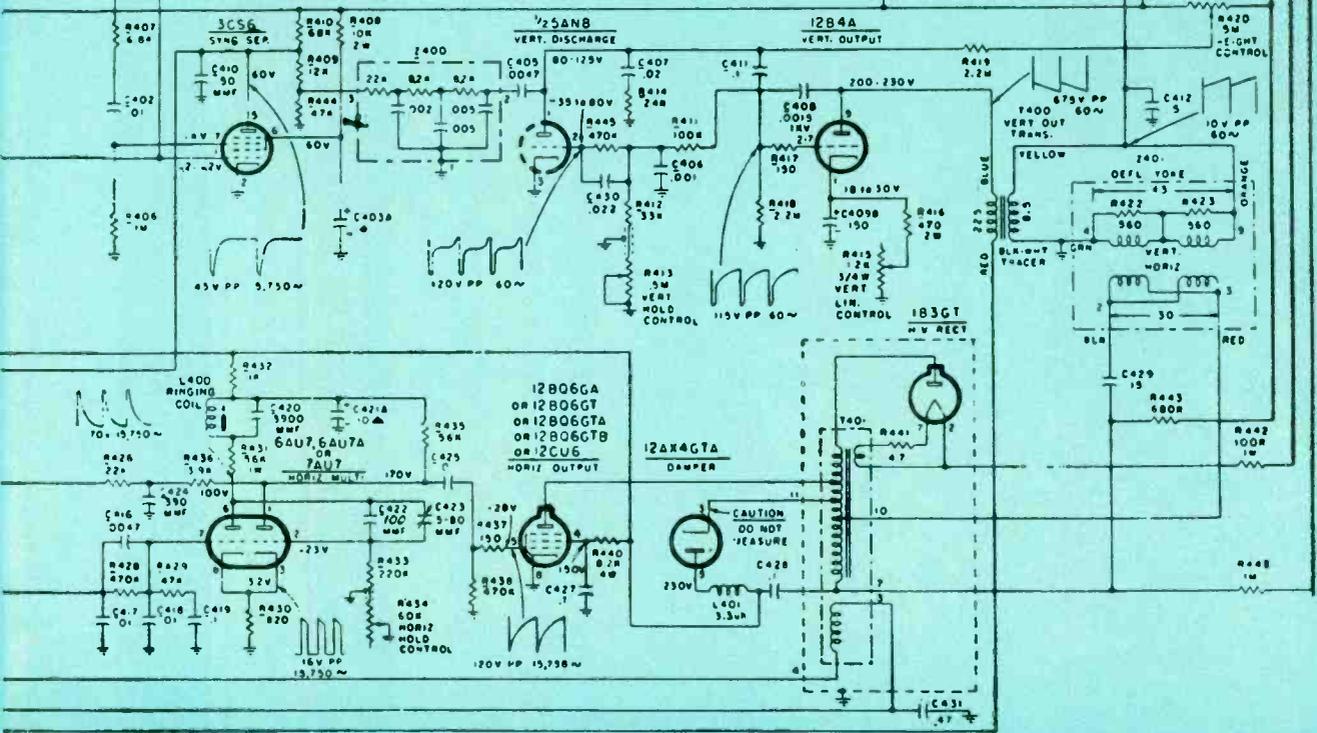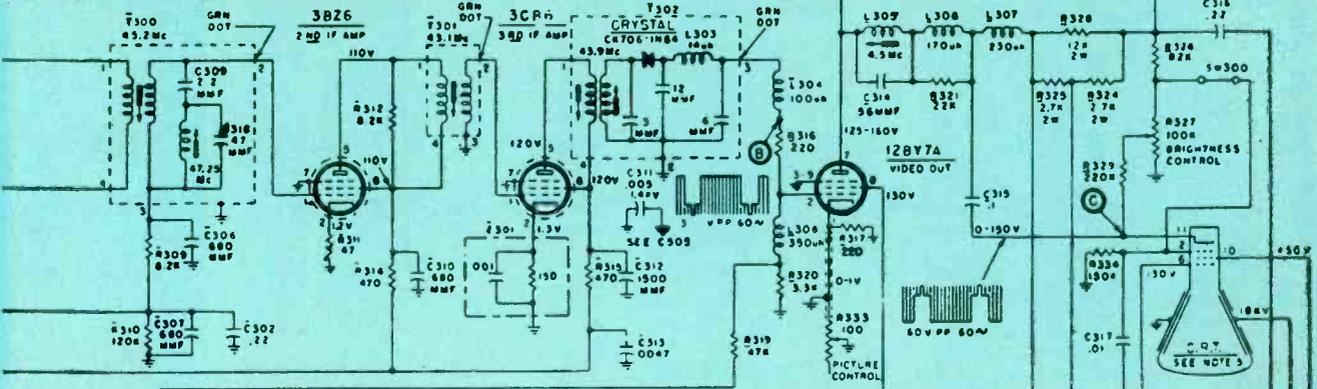

SECTION 4 SWEEP



# Used in Models X2229R, X2230E,R, X2256E,R

## NOTES

All voltages d.c. unless specified and measured from chassis to points indicated with a vacuum-tube voltmeter having 11 megohms input resistance.

Voltage measurements are made with no signal present, normal setting of controls and channel selector set to 2 unless otherwise specified.

All capacitor values in  $\mu\text{f}$  tolerances  $\pm 20\%$  unless otherwise specified.


All resistors 20% tolerance,  $\frac{1}{2}$ -watt carbon, unless otherwise stated. Resistance measurements shown with coils disconnected from the circuit.

Coil resistances not shown are under 1 ohm.

Picture tube 2nd anode voltage to be measured with electrostatic or 20,000 ohms-per-volt minimum high voltage meter.

Arrows on potentiometers indicate clockwise deflection.

TO 6AUG GRID

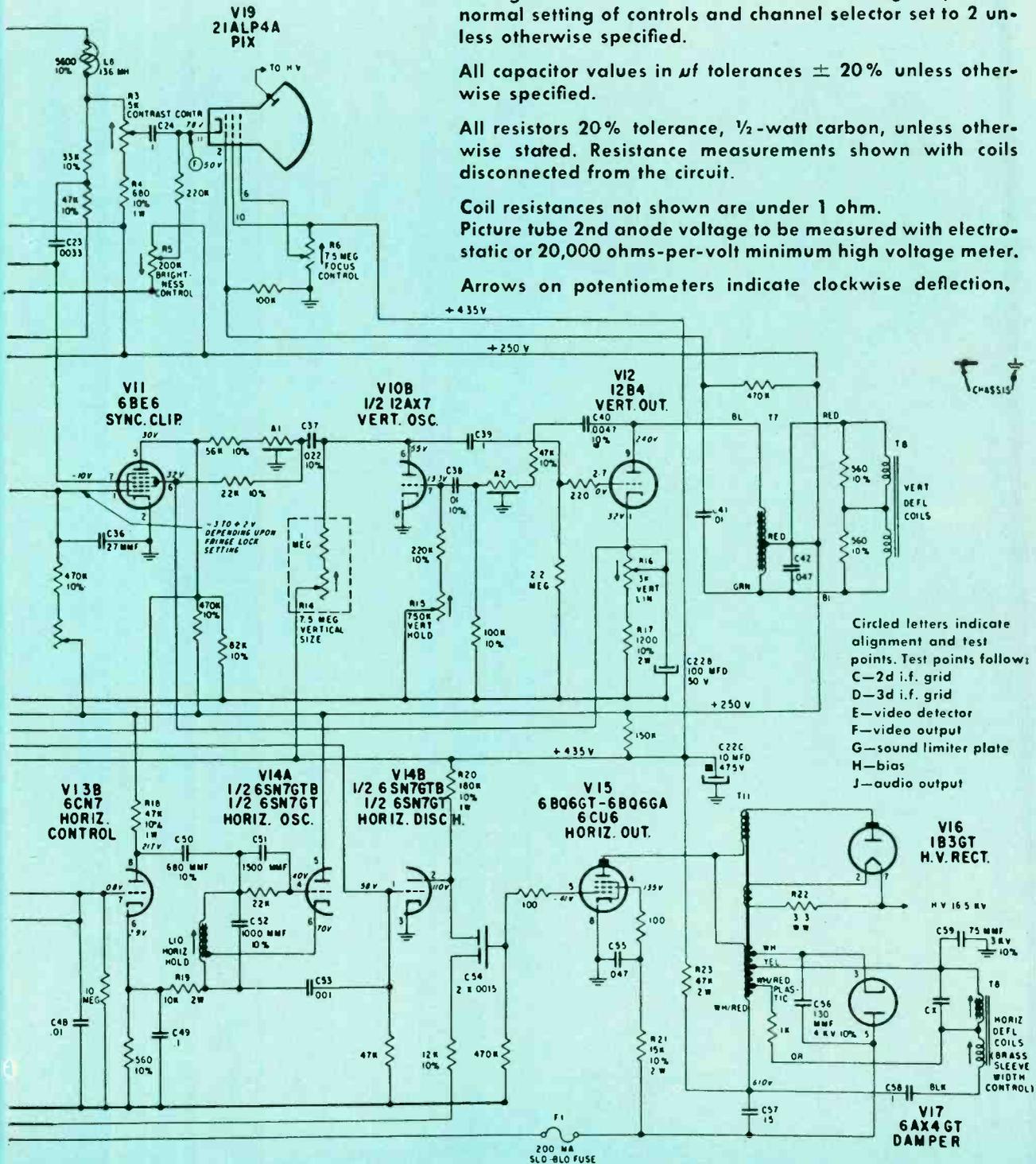

Circled letters indicate alignment and test points. Test points follow:  
 C—2d i.f. grid  
 D—3d i.f. grid  
 E—video detector  
 F—video output  
 G—sound limiter plate  
 H—bias  
 J—audio output



# Heathkits

FOR THE ENTIRE ELECTRONICS INDUSTRY

more than 65 top-quality models to choose from, including such outstanding kit designs as . . . . .

**V-7A VACUUM TUBE VOLTMETER:** Easily the world's largest selling VTVM. Features peak-to-peak scales—etched metal circuit board—1% precision resistors—full wave rectifier and AC input circuit—reads rms and peak-to-peak AC, DC, and ohms.

**O-10 LABORATORY TYPE OSCILLOSCOPE:** The world's largest selling oscilloscope kit, and the most successful oscilloscope in history. Designed especially for color and black-and-white TV service work. Its 5 megacycle bandwidth and new 500 Kc sweep generator readily qualify it for laboratory applications. Features easy-to-assemble etched metal circuit board construction.

**WA-P2 HIGH FIDELITY PREAMPLIFIER:** This is the world's largest selling hi fi preamplifier kit. Features complete equalization, 5 separate switch-selected inputs with individual pre-set level controls, beautiful modern appearance, high-quality components.

**HIGH FIDELITY AMPLIFIERS:** Five Heathkit Models to choose from at prices ranging from \$16.95 to \$59.75. Power output range from 7 to 25 watts.

**DX-100 TRANSMITTER:** A 100 watt phone and CW ham transmitter, offering the greatest dollar value available in the ham radio field today.

THE  
**WORLD'S LEADING  
MANUFACTURER  
OF ELECTRONIC  
KITS . . .**

AMATEUR  
RADIO



RADIO & TV  
SERVICEMEN



INDUSTRIAL  
LABORATORIES

TRAINING  
SCHOOLS



HI-FI  
ENTHUSIASTS



*Greatest Dollar Value Through Factory-To-You Selling!*

# Heathkits

**ONLY** **CAN GIVE YOU ALL**  
**OF THESE DISTINCTIVE ADVANTAGES!**

- *The Most Complete Construction Manuals for Easy Assembly.*
- *Originality of Design—Developed Through Pioneering in the Kit Instrument Field.*
- *Greatest Dollar Value—Finest Quality with Real Economy.*
- *Direct Contact with Manufacturer—Lower Price, Guaranteed Performance.*
- *Etched Metal, Prewired Circuit Boards—Save Construction Time, Improve Performance.*
- *High Quality Standard Components for Long-Life Service.*


**HEATH COMPANY** A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICHIGAN**




there is no substitute for  
**HEATHKIT QUALITY**

**YOU GET MORE:** All first-run, top quality parts—the latest in electronic design—complete and comprehensive step-by-step assembly instructions with large pictorial diagrams and assembly drawings. Proven performance through the production of thousands of kits.

MODEL O-10  
**1**

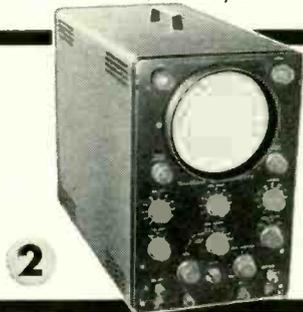

**2**

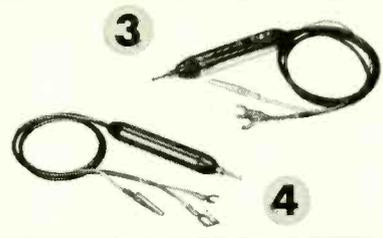

**3**

**4**

**5**



**1** *Heathkit* ETCHED CIRCUIT  
COLOR-TV  
**5" OSCILLOSCOPE KIT**

This deluxe quality oscilloscope has proven itself through thousands of operating hours in service shops and laboratories. Features the best in components—and the best in circuit design.

Features amplifier response to 5 Mc for color TV work, and employs the radically new sweep circuit to provide stable operation up to 500,000 cps. In addition, etched metal, pre-wired circuit boards cut assembly time almost in half, and permit a level of circuit stability never before achieved in an oscilloscope of this type.

Vertical amplifiers flat within +2 db -5 db from 2 cps to 5 Mc, down only 1½ db at 3.58 Mc. Vertical sensitivity is 0.025 volts, (rms) per inch at 1 Kc. 11 tube circuit employs a 5UP1 CRT.

Plastic molded capacitors used for coupling and bypass—preformed and cabled wiring harness provided.

Features built-in peak-to-peak calibrating source—retrace blanking amplifier—push-pull amplifiers and step-attenuated input.

MODEL O-10  
**\$6950**  
Shpg. Wt. 21 Lbs.

**3** *Heathkit* LOW CAPACITY  
**PROBE KIT**

Scope investigation of circuits encountered in TV requires the use of special low capacity probe to prevent loss of gain, circuit loading, or distortion. This probe features a variable capacitor to provide correct instrument impedance matching. Also the ratio of attenuation can be controlled.

NO. 342  
**\$350**  
Shpg. Wt. 1 Lb.

**4** *Heathkit* ETCHED CIRCUIT  
**SCOPE DEMODULATOR PROBE KIT**

Extend the usefulness of your Oscilloscope by observing modulation envelope of R.F. or I.F. carriers found in TV and radio receivers. Functions like AM detector to pass only modulation of signal and not signal itself. Applied voltage limits are 30 V. RMS and 500 V. DC.

NO. 337-C  
**\$350**  
Shpg. Wt. 1 Lb.

**2** *Heathkit* ETCHED CIRCUIT  
**5" OSCILLOSCOPE KIT**

This is a general purpose oscilloscope for the more usual applications in the service shop or lab, yet is comparable to scopes costing many dollars more.

Features full size 5" CRT (5BP1), built-in peak-to-peak voltage calibration—3 step input attenuator—phasing control—push-pull deflection amplifiers—and etched metal pre-wired circuit boards.

Vertical channel flat within ±3 db from 2 cps to 200 Kc, with 0.09 V. rms/inch, peak-to-peak sensitivity at 1 Kc. Sweep circuit from 20 cps to 100,000 cps. A scope you will be proud to own and use.

MODEL OM-1  
**\$4950**  
Shpg. Wt. 21 Lbs.

**5** *Heathkit* ETCHED CIRCUIT  
**3" OSCILLOSCOPE KIT**

This compact little oscilloscope measures only 9½" H. x 6½" W. x 11¾" D., and weighs only 11 lbs! Easily employed for home service calls, for work in the field or is just the ticket for use in the ham shack or home workshop. Incorporates many of the features of the Model OM-1, but yet is smaller in physical size for portability.



Employing etched circuit boards, the Model OL-1 features vertical response within ±3 db from 2 cps to 200 Kc. Vertical sensitivity is 0.25 V. RMS/inch peak-to-peak, and sweep generator operates from 20 cps to 100,000 cps. Provision for r.f. connection to deflection plates for modulation monitoring, and incorporates many features not expected at this price level. 8-tube circuit features a type 3GP1 Cathode Ray Tube.

MODEL OL-1  
**\$2950**  
Shpg. Wt. 14 Lbs.

**HEATH COMPANY** A Subsidiary of Daystrom, Inc. **BENTON HARBOR 20, MICHIGAN**
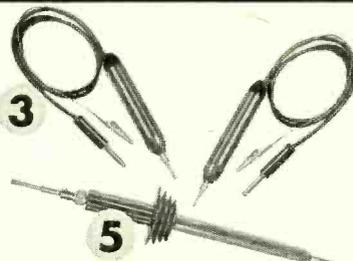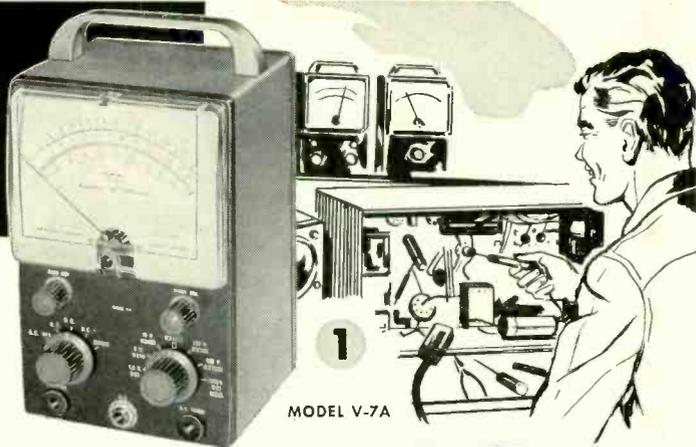
# fill your test requirements WITH HEATHKITS

DESIGNED FOR YOU: Heath Company test equipment is designed for the maximum in convenience. Besides being functional, Heathkits represent the very latest in modern physical appearance, and incorporate all the latest circuit design features for comprehensive test coverage.



## 1 Heathkit ETCHED CIRCUIT VACUUM TUBE VOLTMETER KIT

Besides measuring AC (rms), DC and resistance, the modern-design V-7A incorporates peak-to-peak measurement for FM and television servicing.

AC (rms) and DC voltage ranges are 1.5, 5, 15, 50, 150, 500, and 1500. Peak-to-peak AC voltage ranges are 4, 14, 40, 140, 400, 1400, and 4000. Ohmmeter ranges are X1, X10, X100, X1000, X10K, X100K, and X1 megohm. Also a db scale is provided. A polarity reversing switch provided for DC measurements, and zero center operation within range of front panel controls. Employs a 200  $\mu$ a meter for indication. Input impedance is 11 megohms.

Etched metal, pre-wired circuit board for fast, easy assembly and reliable operation is 50% thicker for more rugged physical construction. 1% precision resistors for utmost accuracy.

MODEL V-7A  
**\$24.50**  
Shpg. Wt. 7 Lbs.

## 2 Heathkit 20,000 OHMS/VOLT MULTIMETER KIT

The MM-1 is a portable instrument for outside servicing, for field testing, or for quick portability in the service shop. Combines attractive physical appearance with functional design. 20,000 ohms/v. DC, and 5000 ohms/v. AC. AC and DC voltage ranges are 0-1.5, 5, 50, 150, 500, 1500 and 5000 volts. Direct current ranges are 0-150  $\mu$ a., 15 ma., 150 ma., 500 ma., and 15 amperes. Resistance ranges are X1, X100, X10,000 providing center scale readings of 15, 1500 and 150,000 ohms. DB ranges cover -10 db to +65 db.

Features a  $4\frac{1}{2}$ " 50  $\mu$ a. meter. Provides polarity reversal on DC measurements. 1% precision resistors used in multiplier circuits. Not affected by RF fields.

MODEL MM-1  
**\$29.50**  
Shpg. Wt. 6 Lbs.

## 3 Heathkit ETCHED CIRCUIT RF PROBE KIT

The Heathkit RF Probe used in conjunction with any 11 megohm VTVM will permit RF measurements up to 250 Mc with  $\pm 10\%$  accuracy. Uses etched circuits for increased circuit stability and ease of assembly.

NO. 309-C  
**\$3.50**  
Shpg. Wt. 1 Lb.

## 4 Heathkit ETCHED CIRCUIT PEAK-TO-PEAK PROBE KIT

Now read peak-to-peak voltages on the DC scale of any 11 megohm VTVM with this new probe, employing etched circuit for stability and low loss. Readings made directly from VTVM scales, from 5 Kc to 5 Mc. Not required for Heathkit Model V-7A VTVM.

NO. 338-C  
**\$5.50**

Shpg. Wt. 2 Lbs.

## 5 Heathkit 30,000 VOLT D.C. HIGH VOLTAGE PROBE KIT

For TV service work or similar application for measurement of high DC voltage. Precision multiplier resistor mounted inside plastic probe. Multiplication factor of 100 on the ranges of Heathkit 11 megohm VTVM.

NO. 336  
**\$4.50**

Shpg. Wt. 2 Lbs.

## 6 Heathkit HANDITESTER KIT

The Model M-1 measures AC or DC voltage at 0-10, 30, 300, 1000, and 5000 volts. Measures direct current at 0-10 ma. and 0-100 ma. Provides ohmmeter ranges of 0-3000 (30 ohm center scale) and 0-300,000 ohms (3000 ohms center scale). Features a 400  $\mu$ a. meter for sensitivity of 1000 ohms/volt. Because of its size, the M-1 is a very handy portable instrument that will fit in your coat pocket, tool box, glove compartment, or desk drawer. Makes a fine standby unit in the service shop when the main instruments are in use, or is ideal for the hobbyist or beginner. An unusual dollar value.

MODEL M-1  
**\$14.50**

Shpg. Wt. 3 Lbs.

**HEATH COMPANY**

A Subsidiary  
of Daystrom, Inc.

**BENTON HARBOR 20, MICHIGAN**

*Heathkit*  
TV ALIGNMENT  
**GENERATOR  
KIT**



1



2



3



4

**HEATH  
COMPANY**  
A SUBSIDIARY OF DAYSTROM INC.

The Model TS-4 features a controllable inductor for all-electronic sweep, improved oscillator and automatic gain circuitry, high RF output, center sweep operation, and improved linearity. It sets a new high standard for sweep generator operation, and is absolutely essential for the up-to-date service shop doing FM, black-and-white TV, and color TV work.

Voltage regulation and effective AGC action insure flat output over a wide frequency range. Electronic sweep insures complete absence of mechanical vibration. Sweep deviation controllable from 0 up to 40 Mc, depending upon base frequency. Effective two-way blanking.

Fundamental output from 3.6 Mc to 220 Mc in 4 bands. Crystal marker provides markers at 4.5 Mc and multiples thereof. Crystal included with kit. Variable marker covers from 19 Mc to 60 Mc on fundamentals, and up to 180 Mc on harmonics. Provision for external marker.



MODEL TS-4  
**\$4950**  
Shpg. Wt. 16 Lbs.

1 *Heathkit* LINEARITY PATTERN  
**GENERATOR KIT**

The new-design Model LP-1 produces vertical or horizontal bar patterns, a cross-hatch pattern, or white dots on the screen of the TV set under test. No internal connections required. Special clip is attached to the TV antenna terminals. Instant selection of the pattern desired for adjustment of vertical and horizontal linearity, picture size, aspect ratio, and focus. Dot pattern presentation is a must for color convergence adjustments on color TV sets.

Extended operating range covers all television channels from 2 to 13. Produces 6 to 12 vertical bars or 4 to 7 horizontal bars.

MODEL LP-1  
**\$2250**  
Shpg. Wt. 7 Lbs.

2 *Heathkit* LABORATORY  
**GENERATOR KIT**

The Heathkit Model LG-1 Laboratory Generator is a high-accuracy signal source for applications where metered performance is essential. It covers from 100 Kc to 30 Mc on fundamentals in 5 bands. Modulation is at 400 cycles, and modulation is variable from 0-50%. RF output from 100,000  $\mu$ v. to 1  $\mu$ v. 200  $\mu$ a. meter reads the RF output in microvolts, or percentage of modulation. Fixed step and variable output attenuation provided.

Features voltage regulation, and double copper plated shielding for stability. Provision for external modulation. Coaxial output cable (50 ohms).

MODEL LG-1  
**\$3950**  
Shpg. Wt. 16 Lbs.

3 *Heathkit* CATHODE RAY  
**TUBE CHECKER KIT**

This new-design instrument holds the key to rapid and complete picture tube testing, either in the set, on the work-bench, or in the carton. Tests for shorts, leakage, and emission. Features Shadow-graph test (a spot of light on the screen) to indicate whether the tube is capable of functioning.

The Model CC-1 tests all electromagnetic deflection picture tubes normally encountered in television servicing. Supplies all operating voltages to the tube under test, and indicates the condition of the tube on a large "GOOD-BAD" scale. Features spring loaded test switches for operator protection.

The CC-1 is housed in an attractive portable case and is light in weight - ideal for outside service calls.

MODEL CC-1  
**\$2250**  
Shpg. Wt. 10 Lbs.

4 *Heathkit* DIRECT READING  
**CAPACITY METER KIT**


Not only is this instrument popular in the service shop, but it has found extensive application in industrial situations. Ideal for quality control work, production line checking, or for matching pairs.

Features direct reading linear scales from 100 mmf to .1 mfd full scale. Necessary only to connect a capacitor of unknown value to the insulated binding posts, select the correct range, and read the meter. The CM-1 is not susceptible to hand capacity, and has a residual capacity of less than 1 mmf.

MODEL CM-1  
**\$2950**  
Shpg. Wt. 7 Lbs.

**BENTON HARBOR 20, MICHIGAN**

RADIO-ELECTRONICS

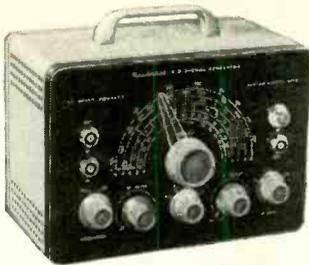

MODEL SG-8 **\$1950**  
Shpg. Wt. 8 Lbs.

This is one of the biggest signal generator bargains available today. The tried and proven Model SG-8 offers all of the outstanding features required for a basic service instrument. High quality components and outstanding performance.

The SG-8 covers 160 Kc to 110 Mc on fundamentals in 5 bands, and calibrated harmonics extend its usefulness up to 220 Mc. The output signal is modulated at 400 cps, and the RF output is in excess of 100,000 uv. Output controlled by both a continuously variable and a fixed step attenuator. Also, audio output may be obtained for amplifier testing. Don't let the

low price deceive you. This is a professional type service instrument to fulfill the signal source requirements in the service lab.


## 1 Heathkit . . . IMPEDANCE BRIDGE KIT

The IB-2 features built-in adjustable phase shift oscillator and amplifier, and has panel provisions for external generator. Measures resistance, capacitance, inductance, dissipation factors of condensers, and storage factor of inductance.

D, Q, and DQ functions combined in one control. 1/2% resistors and 1/2% silver-mica capacitors especially selected for this instrument. A 100-0-100 microammeter provides null indications. Two-section CRL dial provides 10 separate "units" with an accuracy of .5%. Fractions of units read on variable control.

MODEL IB-2 **\$5950**  
Shpg. Wt. 12 Lbs.

# Heathkit SIGNAL GENERATOR KIT

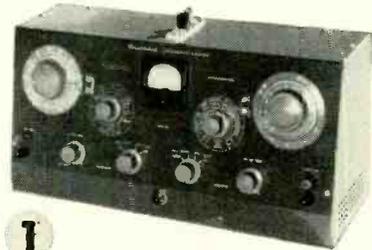

1

## 2 Heathkit "Q" METER KIT

The Heathkit Model QM-1 will measure the Q of inductances and the RF resistance and distributed capacity of coils. Employs a 4 1/2" 50 microampere meter for direct indication. Will test at frequencies of 150 Kc to 18 Mc in 4 ranges. Measures capacity from 40 mmf to 450 mmf within ± 3 mmf. Indispensable for coil winding and determining unknown condenser values. A worthwhile addition to your laboratory at an outstandingly low price. Useful for checking wave traps, chokes, peaking coils, etc. Laboratory facilities are now available to the service shop and home lab.

MODEL QM-1 **\$4450**  
Shpg. Wt. 14 Lbs.



2

## 3 Heathkit 6-12 VOLT BATTERY ELIMINATOR KIT

This modern battery eliminator will supply 6 or 12 volt output for ordinary automobile radios as well as 12 volts for the new models in the latest model cars. Output voltage is variable from 0-8 volts DC, or 0-16 volts DC. Will deliver up to 15 amperes at 6 volts, or up to 7 amperes at 12 volts. Two 10,000 microfarad filter capacitors insure smooth DC output. Two panel meters monitor output voltage and current. Will double as a battery charger. Definitely required for automobile radio service work.

MODEL BE-4 **\$3150**  
Shpg. Wt. 17 Lbs.



3

## 4 Heathkit DECADE RESISTANCE KIT

Twenty 1% precision resistors provide resistance from 1 to 99,999 ohms in 1 ohm steps. Indispensable around service shop laboratory, ham shack, or home workshop. Well worth the extremely low Heathkit price.

MODEL DR-1 **\$1950**  
Shpg. Wt. 4 Lbs.



4

## 5 Heathkit VIBRATOR TESTER KIT

Tests vibrators for proper starting and indicates the quality of the output on a large "GOOD-BAD" scale. Checks both interrupter and self-rectifier types in 5 different sockets. Operates from any battery eliminator delivering variable voltage from 4 to 6 volts DC at 4 amps. Ideal companion to the Model BE-4.

MODEL VT-1 **\$1450**  
Shpg. Wt. 6 Lbs.

5

## 6 Heathkit DECADE CONDENSER KIT

Provides capacity values from 100 mmf to 0.111 mfd in steps of 100 mmf. ± 1% precision silver-mica condensers used. High quality ceramic switches for reduced leakage. Polished birch cabinet. Extremely valuable in all electronic activity.

MODEL DC-1 **\$1650**  
Shpg. Wt. 3 Lbs.


6

# HEATH COMPANY

A SUBSIDIARY OF DAYSTROM INC.

BENTON HARBOR 20, MICHIGAN

# Heathkit TUBE CHECKER KIT

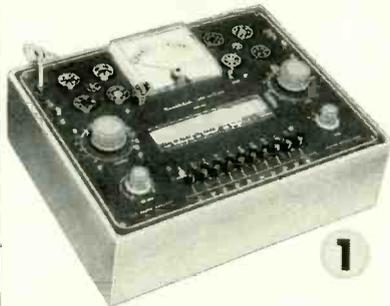

1

1 The Heathkit Model TC-2 is an emission type tube tester that represents a tremendous saving over the price of a comparable unit from any other source. At only \$29.50, you can have a tube tester of your own, even if you are an experimenter, or only do part time service work. Extremely popular with radio servicemen, it uses a 4½" meter with 3-color meter face for simple "GOOD-BAD" indications that the customer can understand. Will test all tubes commonly encountered in radio and TV service work.

Ten 3-position lever switches for "open" or "short" tests on each tube element. Neon bulb indicates filament continuity or short between tube elements. Line adjust control provided. The roll chart is illuminated.

Sockets provided for 4, 5, 6, and 7-pin, octal, and loctal tubes, 7 and 9 pin miniature tubes, and the 5 pin Hytron tubes. Blank space provided for future socket addition. Tests tubes for opens, and shorts, and for quality on the basis of total emission. 14 different filament voltage values provided.

MODEL TC-2

**\$29.50**

Shpg. Wt. 12 Lbs.

## 2 Heathkit PORTABLE TUBE CHECKER KIT

The Model TC-2P is identical to the Model TC-2 except that it is housed in a rugged carrying case. This strikingly attractive and practical two-tone case is finished in proxylin impregnated fabric. The cover is detachable, and the hardware is brass plated. This case imparts a real professional appearance to the instrument. Ideal for home service calls, or any portable application.

MODEL TC-2P

**\$34.50**

Shpg. Wt. 15 Lbs.

## 3 Heathkit TV PICTURE TUBE TEST ADAPTER

The Heathkit TV picture tube test adapter is designed for use with the Model TC-2 Tube Checker. Test picture tubes for emission, shorts, and thereby determine tube quality. Consists of 12-pin TV tube socket, 4 ft. cable, octal connector, and necessary technical data. (Not a kit.)

MODEL 355

**\$4.50**

Shpg. Wt. 1 Lb.

## 4 Heathkit . . .

### CONDENSER CHECKER KIT

Use this Condenser Checker to quickly and accurately measure those unknown condenser and resistor values. All readings taken directly from the calibrated panel scales without any involved calculation. Capacity measurements in four ranges from .00001 to 1000 mfd. Checks paper, mica, ceramic and electrolytic condensers. A power factor control is available for accurate indication of electrolytic condenser efficiency. Leakage test switch—selection of five polarizing voltages, 25 volts to 450 volts DC to indicate condenser operating quality under actual load conditions. Spring-return test switch automatically discharges condenser under test and eliminates shock hazard to the operator.

Resistance measurements can be made in the range from 100 ohms to 5 meg-ohms. Here again, all values are read directly on the calibrated scales. Increased sensitivity coupled with an electron beam null indicator increases overall instrument usefulness.

For safety of operation, the circuit is entirely transformer operated. An outstanding low kit price for this surprisingly accurate instrument.

MODEL C-3

**\$19.50**

Shpg. Wt. 7 Lbs.

## 5 Heathkit VISUAL-AURAL SIGNAL TRACER KIT

This signal tracer is extremely valuable in servicing AM, FM, and TV receivers, especially when it comes to isolating trouble to a particular stage of the circuit under test.

This visual-aural tracer features a high gain RF input channel to permit signal tracing from the receiver antenna input clear through all RF, IF, detector, and audio stages to the speaker. Separate low-gain channel provided for audio circuit exploration. Both visual and aural indication by means of a speaker or headphone, and electron beam "eye" tube as a level indicator. Also incorporates a noise locator circuit for DC noise checks, and a built-in calibrated wattmeter (30-500 watts). Panel terminals provided for "patching" output transformer or speaker into external circuit for test purposes. Designed especially for the radio and TV serviceman. Cabinet size: 9½" wide x 6½" high x 5" deep. A real test equipment bargain.

MODEL T-3

**\$23.50**

Shpg. Wt. 9 Lbs.

# HEATH COMPANY

A SUBSIDIARY OF DAYSTROM INC.

BENTON HARBOR 20, MICHIGAN

RADIO-ELECTRONICS



MODEL HD-1

Shpg. Wt. 13 Lbs. **\$4950**

Used with a sine wave generator, the Model HD-1 will check the harmonic distortion output of audio amplifiers under a variety of conditions. Reads distortion directly on the meter as a percentage of the input signal. Operates between 20 and 20,000 cps. High impedance VTVM circuit for initial reference settings and final distortion readings. Ranges are 0-1, 3, 10, and 30 volts full scale. 1% precision resistors. Distortion scales are 0-1, 3, 10, 30 and 100% full scale. Requires only .3 volt input for distortion test.

# Heathkit HARMONIC DISTORTION METER KIT

## 1 Heathkit AUDIO ANALYZER KIT

This instrument consists of an audio wattmeter, an AC VTVM, and a complete IM analyzer, all in one compact unit.

Use the VTVM to measure noise, frequency response, output gain, power supply ripple, etc. Use the wattmeter for measurement of power output. Internal loads provided for 4, 8, 16, or 600 ohms. VTVM also calibrated for DBM units. High or low impedance IM measurements made with built-in 6KC and 60 cps generators. VTVM ranges are .01, to 300 volts in 10 steps. Wattmeter ranges are .15 mw. to 150 w. in 7 steps. IM scales are 1% to 100% in 5 steps.

MODEL AA-1  
**\$5950**

Shpg. Wt. 13 Lbs.



## 2 Heathkit AUDIO GENERATOR KIT

This new Heathkit Model features step-tuning from 10 cps to 100 Kc with three rotary switches that provide two significant figures and multiplier. Less than .1% distortion. Frequency accurate to within  $\pm 5\%$ .

Output monitored on a large  $4\frac{1}{2}$ " meter that reads voltage or db. Both variable and step-type attenuation provided. Meter reads zero-to-maximum at each attenuator position. Output ranges (and therefore meter ranges) are 0-.003, .01, .03, .1, .3, 1, 3, 10 volts. Step-tuning provides rapid positive selection of the desired frequency, and allows accurate return to any given frequency.

MODEL AG-9  
**\$3450**

Shpg. Wt. 8 Lbs.




## 3 Heathkit AUDIO OSCILLATOR KIT

(SINE WAVE — SQUARE WAVE)

The Model AO-1 features sine wave or square wave coverage from 20-20,000 cps in 3 ranges. It is an instrument specifically designed to completely fulfill the needs of the serviceman and high fidelity enthusiast. Offers high level output across the entire frequency range, low distortion and low impedance output. Features a thermistor in the second amplifier stage to maintain essentially flat output through the entire frequency range. Produces an excellent sine wave for audio testing, or will produce good, clean, square waves with a rise time of only 2 microseconds.

MODEL AO-1  
**\$2450**

Shpg. Wt. 10 Lbs.

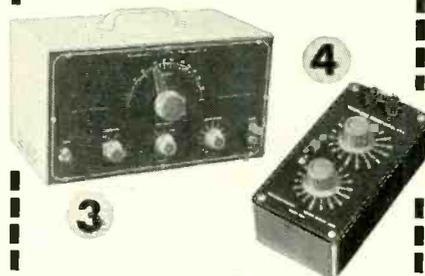

## 4 Heathkit RESISTANCE SUBSTITUTION BOX KIT...

Provides switch selection of 36 RTMA 1 watt standard 1% resistors ranging from 15 ohms to 10 megohms. Numerous applications in radio and TV work, and essential in the developmental laboratory.

MODEL RS-1  
**\$550**

Shpg. Wt. 2 Lbs.




## 5 Heathkit AC VACUUM TUBE VOLTMETER KIT...

The Heathkit AC VTVM features high impedance, wide frequency range, very high sensitivity, and extremely wide voltage range. Will accurately measure a voltage as small as 1 mv. at high impedance. Excellent for sensitive AC measurements required by laboratories, audio enthusiasts and experimenters. Frequency response is substantially flat from 10 cps to 50 Kc. Ranges are .01, .03, .1, .3, 1, 3, 10, 30, 100, and 300 v. RMS. Total db range -52 to + 52 db. Input impedance 1 megohm at 1 Kc.

MODEL AV-2  
**\$2950**

Shpg. Wt. 5 Lbs.

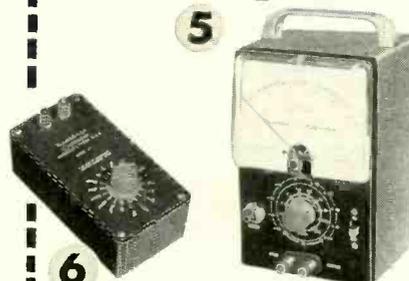


## 6 Heathkit CONDENSER SUBSTITUTION BOX KIT...

Very popular companion to Heathkit RS-1. Individual selection of 18 RTMA standard condenser values from .0001 mfd to .22 mfd. Includes 18" flexible leads with alligator clips.

MODEL CS-1  
**\$550**

Shpg. Wt. 2 Lbs.

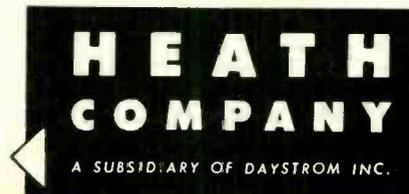

BENTON HARBOR 20, MICHIGAN

**HEATH  
COMPANY**

A SUBSIDIARY OF DAYSTROM INC.



# HEATHKIT HAM GEAR

for high quality at moderate cost

**DOLLAR VALUE:** You get more for your Heathkit dollar because your labor is used to build the kit instead of paying for someone else's. Also, the middleman's margin of profit is eliminated when you deal directly with the manufacturer.

1

MODEL DX-100



2



3



4

## 1 Heathkit DX-100 PHONE & CW TRANSMITTER KIT

The reception given this amateur transmitter has been tremendous. Reports from radio amateurs using the DX-100 are enthusiastic in praising its performance and the high quality of the components used in its assembly. Actual "on the air" results reflect the careful design that went into its development.

The DX-100 features a built-in VFO, modulator, and power supplies, and is completely bandswitching for phone or CW operation on 160, 80, 40, 20, 15, 11, and 10 meters. All parts necessary for construction are supplied in the kit, including tubes, cabinet, and detailed step-by-step instructions. Easy to build, and a genuine pleasure to operate.

Employs push-pull 1625's modulating parallel 6146's for RF output in excess of 100 watts on phone and 120 watts on CW. May be excited from the built-in VFO or from crystals (crystals not included with kit). Features five-point TVI suppression: (1) pi network interstage coupling to reduce harmonic transfer to the final stage; (2) pi network output coupling; (3) extensive shielding; (4) all incoming and outgoing circuits filtered; (5) inter-locking cabinet seams to eliminate radiation except through the coaxial output connector. Pi network output coupling will match 50 to 600 ohm non-reactive load. Illuminated VFO dial and meter face. Remote control socket provided.

The chassis is made of extra-strong #16 gauge copper-plated steel. It employs potted transformers, ceramic switch and variable capacitor insulation, solid silver loading switch terminals, and high-grade well-rated components throughout. Features a pre-formed wiring harness, and all coils are pre-wound.

High-gain speech amplifier for dynamic or crystal microphones, and restricted speech range for increased intelligence. Plenty of audio power reserve. Measures 20<sup>7</sup>/<sub>8</sub>" W. x 13<sup>3</sup>/<sub>4</sub>" H. x 16" D. Schematic diagram and complete technical specifications on request.

MODEL DX-100

**\$189<sup>50</sup>**

Shpg. Wt. 120 Lbs.

Shipped Motor Freight Unless Otherwise Specified  
\$50.00 Deposit Required on C.O.D. Orders

## 2 Heathkit VFO KIT

The Model VF-1 covers 160-80-40-20-15-11 and 10 meters with three basic oscillator frequencies. Better than 10-volt average RF output on fundamentals. Features illuminated and pre-calibrated dial scale. Cable and plug provided to fit crystal socket of any modern transmitter.

Enjoy the convenience and flexibility of VFO operation at no more than the price of crystals. May be powered from plug on the Heathkit Model AT-1 transmitter, or supplied with power from most transmitters. Measures: 7" H. x 6<sup>1</sup>/<sub>2</sub>" W. x 7" D.

MODEL VF-1

**\$19<sup>50</sup>**

Shpg. Wt. 7 Lbs.

## 3 Heathkit CW AMATEUR TRANSMITTER KIT

The Model AT-1 is an ideal novice transmitter, and may be used to excite a higher power rig later on.

This CW transmitter is complete with its own power supply, and covers 80, 40, 20, 15, 11, and 10 meters. Features single-knob bandswitching, and panel meter indicates grid or plate current for the final amplifier. Designed for crystal operation or external VFO. Crystal not included in kit. Incorporates such features as key click filter, line filter, copper-plated chassis, pre-wound coils, 52 ohm coaxial output, and high quality components throughout. Instruction book simplifies assembly. Employs a 6AG7 oscillator, 6L6 final amplifier. Operates up to 35 watts plate power input.

MODEL AT-1

**\$29<sup>50</sup>**

Shpg. Wt. 15 Lbs.

## 4 Heathkit ... ANTENNA COUPLER KIT

The Model AC-1 will properly match your low power transmitter to an end-fed long wire antenna. Also attenuates signals above 36 Mc, reducing TVI. 52 ohm coax. input—power up to 75 watts—10 through 80 meters—tapped inductor and variable condenser—neon RF indicator—copper plated chassis and high quality components. Ideal for use with Heathkit AT-1 Transmitter.

MODEL AC-1

**\$14<sup>50</sup>**

Shpg. Wt. 4 Lbs.

**HEATH COMPANY**

A Subsidiary  
of Daystrom, Inc.

**BENTON HARBOR 20, MICHIGAN**



# "AMATEUR-ENGINEERED"

## Equipment For The Ham

MODERN DESIGN: You can be sure of getting all the latest and most desirable design features when you buy Heathkits. Advanced-design is a minimum standard for new Heathkit models.



1 MODEL AR-3

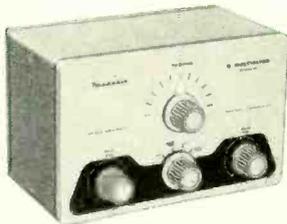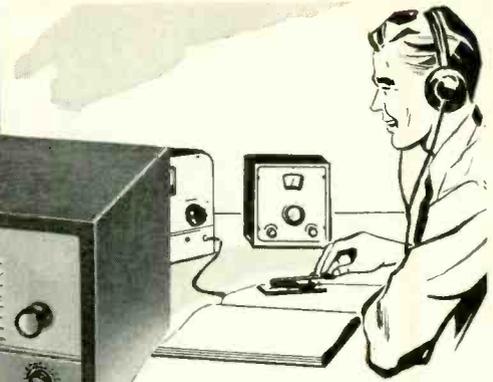

2



3



4



5

### 1 Heathkit COMMUNICATIONS-TYPE ALL BAND RECEIVER KIT

The new Model AR-3 features improved IF and RF performance, along with better image rejection on all bands. Completely new chassis layout for easier assembly, even for the beginner.

Covers 550 Kc to 30 Mc in four bands. Provides sharp tuning and good sensitivity over the entire range. Features a transformer-type power supply—electrical bandspread—separate RF and AF gain controls—antenna trimmer—noise limiter—AGC—BFO—headphone jacks—5½" PM speaker and illuminated tuning dial.

CABINET: Fabric covered cabinet with aluminum panel as shown. Part No. 91-15, shipping weight 5 lbs. \$4.50.

MODEL AR-3

**\$27<sup>95</sup>**

Shpg. Wt. 12 lbs.  
(Less Cabinet)

### 2 Heathkit "Q" MULTIPLIER KIT

Here is the Heathkit Q Multiplier you hams have been asking for. A tremendous help on the phone and CW bands when the QRM is heavy. Provides an effective Q of approximately 4,000 for extremely sharp "peak" or "null." Use it to "peak" the desired signal or to "null" an undesired signal, or heterodyne. Tunes to any signal within the IF band-pass of your receiver. Also provides "broad peak" for conditions where extreme selectivity is not required.

Operates with any receiver having an IF frequency between 450 and 460 Kc. Will not function with AC-DC type receivers. Requires 6.3 volts AC at 300 ma. and 150 to 250 VDC at 2 ma. Derives operating power from your receiver. Uses a 12AX7 tube, and special High-Q shielded coils. Simple to connect with the cable and plugs supplied. Measures only 4-11/16"H.x7¾"W.x4½"D. A really valuable addition to the receiving equipment in your ham shack.

MODEL QF-1

**\$9<sup>95</sup>**

Shpg. Wt. 3 lbs.

### 3 Heathkit VARIABLE VOLTAGE REGULATED POWER SUPPLY KIT

Provides well filtered DC output, variable from zero to 500 volts at no load and *regulated* for stability. Will supply up to 10 ma. at 450 VDC, and up to 130 ma. at 200 VDC. Voltage or current monitored on front panel meter. Also provides 6.3 VAC at 4A. for filament. Filament voltage isolated from B+, and both isolated from ground. Invaluable around the ham shack for supplying operating potentials to experimental circuits. Use in all types of research and development laboratories as a temporary power supply, and to determine design requirements for ultimate power supply.

MODEL PS-3

**\$35<sup>50</sup>**

Shpg. Wt. 17 lbs.

### 4 Heathkit ANTENNA IMPEDANCE METER KIT

Use in conjunction with a signal source for measuring antenna impedance, line matching, adjustment of beam and mobile antennas, etc. Will double as a phone monitor or relative field strength indicator. 100 µa. meter employed. Covers the range from 0-600 ohms. An instrument of many uses for the amateur.

MODEL AM-1

**\$14<sup>50</sup>**

Shpg. Wt. 2 lb.

### 5 Heathkit GRID DIP METER KIT

This is an extremely valuable tool for accomplishing literally hundreds of jobs on all types of equipment. Covering from 2 Mc to 250 Mc, the GD-1B is compact and can be operated with one hand. Uses a 500 µa. meter for indication, with a sensitivity control and headphone jack. Includes prewound coils and rack. Indispensable instrument for hams, engineers, or servicemen.

MODEL GD-1B

**\$19<sup>50</sup>**

Shpg. Wt. 4 lbs.

**HEATH COMPANY**

A Subsidiary  
of Daystrom, Inc.

**BENTON HARBOR 20, MICHIGAN**

*Heathkits*  
 PROVIDE THE  
 "CONSTRUCTIVE"  
 APPROACH TO  
**HIGH-FIDELITY**



**EASY TO BUILD:** *The assembly instructions supplied with Heathkits are so complete and detailed that anyone can assemble the kits without difficulty. Plenty of pictorial diagrams and step-by-step instructions. Information on resistor color codes, soldering, use of tools, etc. Build-it-yourself with confidence!*



1

1 *Heathkit* **ADVANCED-DESIGN**  
**HIGH FIDELITY** **AMPLIFIER KIT**

The 25 Watt Model W-5 is one of the most outstanding high fidelity amplifiers available today—at any price. Incorporates the very latest design features to achieve true "presence" for the super-critical listener.

Features a new-design Peerless output transformer, and KT66 output tubes handle power peaks up to 42 watts. The unique "tweeter-saver" suppresses high frequency oscillation. A new type balancing circuit results in closer "dynamic" balance between output tubes. Features improved phase shift characteristics and frequency response, with reduced IM and harmonic distortion. Color styling harmonizes with the Heathkit WA-P2 Preamplifier and the FM-3 Tuner.

Frequency response—within  $\pm 1$  db from 5 cps to 160 Kc at 1 watt. Harmonic distortion only 1% at 25 watts, 20-20,000 cps. IM distortion only 1% at 20 watts, using 60 and 3,000 cps. Output impedance 4, 8, or 16 ohms. Hum and noise—99 db below rated output. Uses two 12AU7's, two KT66's and a 5R4GY.


**KIT COMBINATIONS:**

W-5M Amplifier Kit: Consists of main amplifier and power supply, all on one chassis. Complete with all necessary parts, tubes, and comprehensive manual. Shpg. Wt. 31 lbs. Express only.

**\$59<sup>75</sup>**

W-5 Combination Amplifier Kit: Consists of W-5M Amplifier Kit listed above plus Heathkit Model WA-P2 Preamplifier Kit. Complete with all necessary parts, tubes, and construction manuals. Shpg. Wt. 38 lbs. Express only.

**\$79<sup>50</sup>**

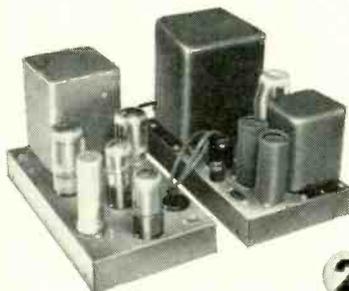

2

2 *Heathkit* **DUAL-CHASSIS WILLIAMSON TYPE**  
**HIGH FIDELITY** **AMPLIFIER KIT**

This is a very popular high fidelity amplifier kit that features dual-chassis type construction. The resulting physical dimensions offer an additional margin of flexibility in installation. It features the famous Acrosound TO-300 "ultra-linear" output transformer, and has a frequency response within  $\pm 1$  db from 6 cps to 150 Kc at 1 watt. Harmonic distortion only 1% at 21 watts. IM distortion at 20 watts only 1.3% at 60 and 3,000 cps. Rated power output is 20 watts. Output impedance 4, 8, or 16 ohms. Hum and noise—88 db below 20 watts. Uses two 6SN7's, two 5881's, and a 5V4G.

**KIT COMBINATIONS:**

W-3M: Consists of main amplifier and power supply for separate chassis construction. Includes all tubes and components necessary for assembly. Shpg. Wt. 29 lbs., Express only.

**\$49<sup>75</sup>**

W-3: Consists of W-3M Kit listed above plus Heathkit Model WA-P2 Preamplifier described on opposite page. Shpg. Wt. 37 lbs., Express only.

**\$69<sup>50</sup>**



3

3 *Heathkit* **SINGLE-CHASSIS WILLIAMSON TYPE**  
**HIGH FIDELITY** **AMPLIFIER KIT**

This is the lowest priced Williamson type amplifier ever offered in kit form, and yet it retains all the usual features of the Williamson type circuit. Main amplifier and power supply combined on one chassis, and uses a new-design Chicago output transformer. Frequency response—within  $\pm 1$  db from 10 cps to 100 Kc at 1 watt. Harmonic distortion only 1.5% at 20 watts. IM distortion at rated output, 2.7% at 60 and 3,000 cps. Rated power output is 20 watts. Output impedance 4, 8, or 16 ohms. Hum and noise—95 db below 20 watts. Uses two 6SN7's, two 5881's, and one 5V4G.

Instructions are so complete that the kit may be assembled successfully even by a beginner in electronics.

**KIT COMBINATIONS:**

W-4AM: Consists of main amplifier and power supply for single chassis construction. Includes all tubes and components necessary for assembly. Shpg. Wt. 28 lbs. Express only.

**\$39<sup>75</sup>**

W-4A: Consists of W-4AM Kit listed above plus Heathkit Model WA-P2 Preamplifier described on opposite page. Shpg. Wt. 35 lbs. Express only.

**\$59<sup>50</sup>**

**HEATH  
 COMPANY**

A SUBSIDIARY OF DAYSTROM INC.

**BENTON HARBOR 20, MICHIGAN**

RADIO-ELECTRONICS

ATTRACTIVELY STYLED: *Heathkit high fidelity instruments are not only functional, but are most attractive in physical design. Such units as the preamplifier and the W-5 main amplifier are designed for beauty as well as performance. They blend with any room decor and are the kind of instruments you will be proud to own.*



*enjoy....*  
**THE VERY BEST  
 IN AUDIO WITH  
 "BUILD-IT-YOURSELF"  
 HEATHKITS**

**1** *Heathkit* HIGH FIDELITY  
**PREAMPLIFIER KIT**

This outstanding preamplifier is designed specifically for use with the Heathkit Williamson type amplifiers. It completely fulfills the requirements for remote control, compensation and preamplification, and exceeds even the most rigorous specifications for high fidelity performance.

Features five separate switch-selected input channels (2 low level and 3 high level), each with its own input control. Full record equalization with four-position turnover control and four-position rolloff control.

Output jack for tape recorder — separate bass control with 18 db boost and 12 db cut at 50 cps. — treble control offering 15 db boost and 20 db cut at 15,000 cps — special hum control to insure minimum hum level — and many other desirable features. Overall frequency response (with controls set to "flat" position) is within 1 db from 25 cps to 30,000 cps. Will do justice to the finest available program sources. Beautiful satin-gold finish.

Power requirements from the Heathkit Williamson type high fidelity amplifier — 6.3 VAC at 1 amp., and 300 VDC at 10 Ma. Uses two 12AX7's and one 12AU7.

MODEL WA-P2  
**\$19.75**  
 Shpg. Wt. 7 Lbs.



1

**2** *Heathkit* 20-WATT HIGH FIDELITY  
**AMPLIFIER KIT**

This Heathkit Model offers you the least expensive route to high fidelity performance. Frequency response is  $\pm 1$  db from 20-20,000 cps. Features full 20 watt output using push-pull 6L6's, and incorporates separate bass and treble tone controls. Preamplifier and main amplifier are built on the same chassis. Four switch-selected compensated inputs and separate bass and treble tone controls provide all necessary functions at minimum investment. Features miniature tube types for low hum and noise.

Uses 12AX7, two 12AU7's, two 6L6G's and a 5V4G. A most interesting "build-it-yourself" project, and an excellent hi-fi amplifier for home use. Well suited, also, for public address applications because of its high power output and high quality audio reproduction. Another Heathkit "best-buy" for you!

MODEL A-9B  
**\$35.50**  
 Shpg. Wt. 23 Lbs.



2

**3** *Heathkit* 7-WATT  
**AMPLIFIER KIT**

The redesigned Model A-7D features a new type output transformer for tapped screen operation, and provides improved sensitivity, reduced distortion, and increased power output.

The full 7-watt output of the Model A-7D is more than adequate for normal home installations. Frequency characteristics are  $\pm 1\frac{1}{2}$  db from 20 to 20,000 cps. Potted output and power transformers employed. Push-pull output — detailed construction manual — top quality parts — high quality audio without great expense. Output transformer tapped at 4, 8, and 16 ohms. Bass and treble tone controls provided on the front chassis apron.

MODEL A-7D  
**\$16.95**  
 Shpg. Wt. 10 Lbs.



3


**HEATH  
 COMPANY**  
 A SUBSIDIARY OF DAYSTROM INC.

**BENTON HARBOR 20, MICHIGAN**

JANUARY, 1956



# Test Equipment

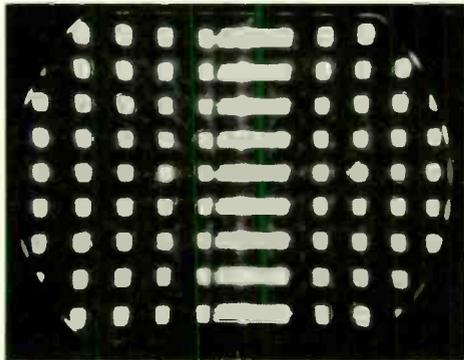

Pattern for convergence adjustment.

*A survey of instruments  
necessary for color TV  
servicing*

By MATTHEW MANDL\*

**Q**UESTIONS uppermost in the minds of technicians who intend servicing color television receivers are:

What type of new test equipment is needed?

How useful will my old equipment be?

Can my existing test gear be modified to be more useful in color television servicing?

First let's emphasize that your present equipment will be just as useful on color receivers as it is on black-and-white sets. The v.t.v.m. is still needed for voltage and resistance checks, and your tube checker can probably be brought up to date to test some of the newer color tube types. If your signal generators have been able to take care of alignment of the newer 45.75-mc video i.f. stages, they will do as good a job on color receivers. The oscilloscope can be used for waveform observation in the sweep circuits and other stages of a color receiver which duplicate those in black-and-white. For some special checks of the subcarrier oscillator, however, a good frequency response in the vertical system of the scope will be necessary.

Capacitor checkers, cross-bar generators and various other black-and-white testing devices also find similar applications in color.

Thus, color television servicing does not mean that black-and-white equipment is obsolete—but it does mean that *additional equipment of a specialized nature* must be obtained. Such test gear is a virtual necessity, not only to expedite troubleshooting, but for proper

adjustment of the various circuits handling the color signals.

### Circuit adjustments

An important aspect of color television servicing involves color circuit adjustments. These procedures require some equipment not used in black-and-white alignment and troubleshooting—color bar generators, white dot generators, etc.

A critical adjustment procedure is *convergence*, the process of adjusting the color receiver so the three beams of the picture tube cross over at the internal aperture mask. This crossover or convergence is necessary so each beam strikes the color phosphor dot which produces the right color. Incorrect colors will result, for instance, if the blue beam strikes the red phosphor or the green beam the blue phosphor dots.

Convergence at the center of the screen is not too difficult, but at the screen edges it becomes involved because of the increased distance which the beams travel. Initially, the center of the screen must be adjusted for good convergence (static or d.c. convergence) after which the magnetic fields of the convergence yoke must be adjusted so the properly shaped modified beam scans the screen. The modification consists of using a parabolic waveform shaped from the horizontal and vertical sweep signals.

A typical convergence circuit is shown in Fig. 1 and is used in the 21-inch RCA chassis CTC4 receiver. Note the number of controls. They indicate only the green beam convergence adjustments. Since three times as many are necessary for all three colors,

obviously adjustment can become complex when the system is considerably off true convergence.

A white dot generator is very useful for convergence adjustments. It produces a series of white dots or squares against a black background when convergence is correct. When the beam is misconverged, each white dot breaks up into *three* dots of different colors. It is for this reason that some of the black dot generators used for black-and-white linearity adjustments are not useful for convergence adjustments; a black dot represents the absence of light (beam cutoff) and could not reproduce the identifying color dots indicating misconvergence.

A center vertical segment of the screen is shown in Fig. 2-a. The center of the screen is converged because a white square is present, indicating that each beam in the picture tube is striking its respective phosphor. At the top and bottom there is a lack of convergence, and the white square is broken into three squares of individual colors.

Fig. 2-b shows a horizontal segment not converged and a vertical converged section. Note that convergence dis-

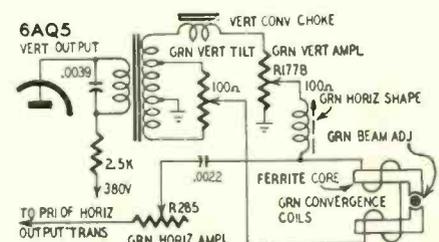



Fig. 1—Vertical and horizontal convergence adjustments for the green beam.

\* Author: Mandl's Television Servicing

# TEST INSTRUMENTS



RCA WR-61A color bar generator.

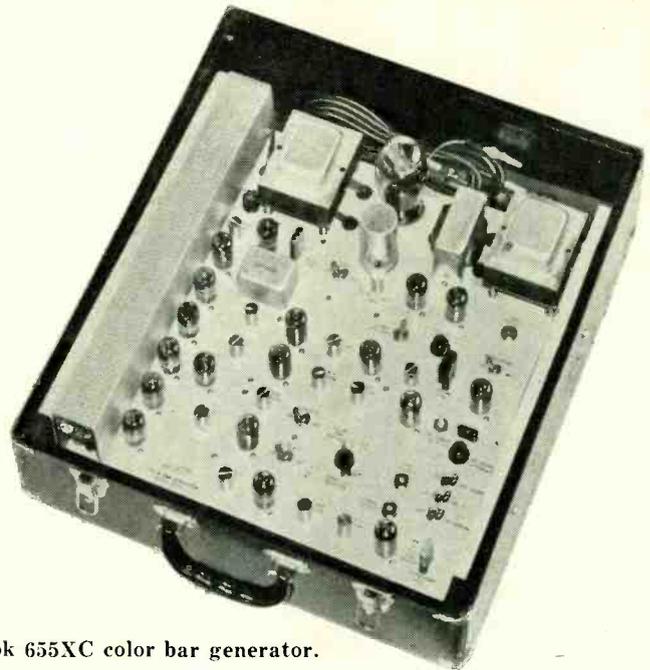

Hickok 655XC color bar generator.

placement of the squares increases at the edges. Center-screen convergence is made by adjusting the beam positioning in the newer receivers having convergence yokes. Dynamic convergence for screen edges is adjusted with the tilt, amplitude and shaping controls shown in Fig. 1.

White dot generators should be able to produce a fairly large dot or square. Small dots are not too clearly visible and the technician is apt to turn the brightness up too high, disturbing proper convergence settings. The generator should be stable so that the dots can be locked in for a stationary pattern. Adjustment of dot size and number is a desirable feature, though not necessary if initial size is adequate. From 10 to 12 dots should be visible

horizontally, about 8 to 10 vertically. When the receiver needs only slight retouching for convergence, it can be done by observing a televised scene; when extensive convergence is necessary, the white dot generator is indispensable. Most white dot generators duplicate the function of the cross-bar generator and have available a switch for selecting horizontal or vertical bars or both for linearity adjustments of black-and-white or color receivers.

Another very important service instrument for color television is the color bar generator which permits checking the color a.f.c. system, the matrix and other circuits shown in Fig. 3. True color reproduction depends on the phase of the incoming 3.58-mc burst with respect to the 3.58-mc oscillator in the receiver. Adjustment of gain in the color signal amplifier stages and matrix are also important for true color rendition.

The color bar generator produces a series of differently colored vertical bars conforming to the signals found in the receiver. A typical bar sequence is shown in Fig. 4. The sequence, number and color of the bars differ for the various commercially available generators. Hence the service technician must be familiar with the number and

color sequence of the particular instrument he uses, for various misadjustments of phase controls, fine tuning, etc., will disturb the color sequence. The color bars produced by color bar generators are not suitable for linearity checks.

Useful features of these generators include r.f. signal outputs of color sub-carrier frequency, sound carrier frequency and luminance signals. Of importance also are outputs providing for positive- and negative-polarity video signals. These features help servicing the various bandpass amplifier circuits, video amplifiers, color killer and burst gate stages.

Color bar generators should produce colors which conform to NTSC standards. Thus, they should include colors conforming to the I and Q signals as well as the R - Y and B - Y signals as shown in Fig. 4. Such color reproduction is necessary so that the generator may be used on receivers which demodulate on the I and Q axis or which have R - Y and B - Y demodulators. The color bars should be stable with true color lock-in so that they can be identified by the particular color sequence listed for the generator in the instruction manual. *The particular sequence of colors from left to right*

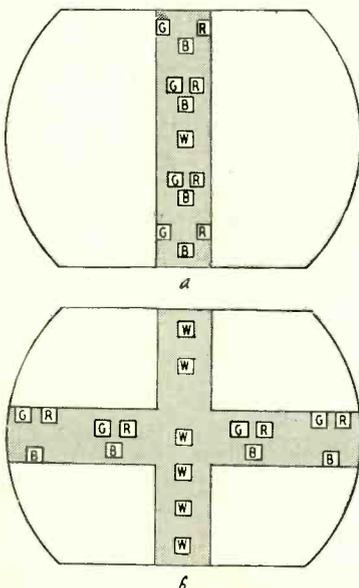


Fig. 2—Segments of screen showing lack of vertical and horizontal convergence.

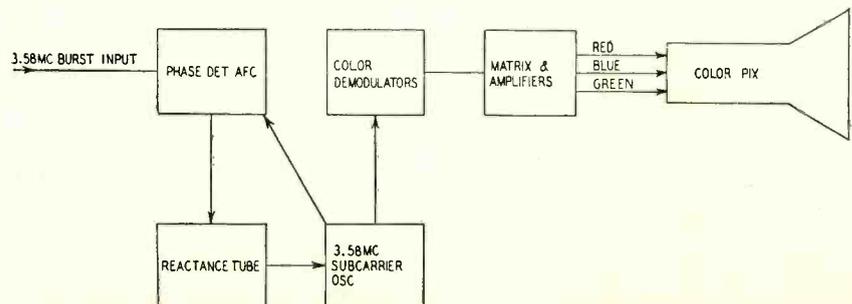


Fig. 3—Circuits that can be adjusted and serviced with a color bar generator.

*Always at your fingertips...*

## TV WIRE-WOUND CONTROLS

thanks to the

# CLAROSTAT PD-1 PACKAGE

Here's a versatile assortment of wire-wound controls with a selection of the most popular Pick-A-Shaft field-attached shafts, packaged in an attractive, convenient, hinge-cover box.

The PD-1 includes eight different values of the well-known Clarostat Series A10 (4-watt) wire-wound controls, eight Pick-A-Shaft\* shafts (two each of the four most popular types); and a handy mounting-nut wrench.

For focus controls alone, the assortment services over 2000 TV set models! Also provides for other functions such as width, linearity, balance and gain. Included is a data sheet listing TV manufacturers' part numbers with proper replacements from this assortment.

And of course the controls may be used in various test equipment, radios, hi-fi systems, industrial electronics, etc.



## and don't overlook those CLAROSTAT RESISTOR CARDS!

GK-1	20 most popular 10-watt wire-wounds	(1 ohm to 25K)
GK-2	32 most popular 2-watt wire-wounds	(5 to 2000 ohms)
GK-3	36 most popular 5-watt wire-wounds	(1 to 4000 ohms)
GK-4	54 most popular 5-watt wire-wounds	(1 ohm to 10K)
GK-5	50 most popular 10-watt wire-wounds	(1 to 9000 ohms)
GK-6	45 most popular 10-watt wire-wounds	(5 ohms to 50K)
GL-1	12 "Fuzohm"† 7.5-ohm fuse-type resistors	

### Order Your PD-1 Package Today!

Clarostat distributors have it waiting for you. Take advantage of this time- and money-saving assortment. Ask for latest Clarostat Catalog—or write us.

†Trade-mark.



\*Reg. U. S. Pat. Office

*Controls and Resistors*  
**CLAROSTAT MFG. CO., INC., DOVER, NEW HAMPSHIRE**  
 In Canada: Canadian Marconi, Co., Ltd., Toronto 17, Ont.

## TEST INSTRUMENTS

isn't important so long as identified NTSC colors are available.

The high-voltage and focus circuit adjustments are few. Focus and second-anode voltages can be read with a v.t.v.m. and high-voltage probe. Voltages up to 25,000 will be encountered.

### Commercial units

A variety of color test instruments is available in price ranges from below \$100 per unit to well over \$200. In general, the more expensive units feature precise crystal control and versatility with respect to the number of output signals available. A number of instruments, in addition to generat-

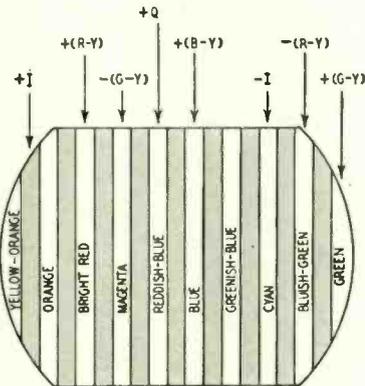


Fig. 4—Typical color bar sequence.

ing color bars or white dots, also duplicate some of the functions found in black-and-white television test equipment—provide r.f. or video signal outputs for alignment and cross bars for linearity checking. Hence, in some instances the technician may desire to obtain the lower-priced equipment if his black-and-white test gear is fairly modern. The higher-priced units will

be particularly desirable where black-and-white equipment is outmoded and no longer capable of servicing late-model receivers having i.f. stages with 45.75-mc video and 41.25-mc sound.

### Bar generators

RCA WR-61A. This color bar generator (see photo) produces 10 vertical color bars, including a number which correspond to the NTSC standard R - Y, B - Y, G - Y, I and Q signals as shown in Fig. 4. In addition, the instrument also provides a crystal-controlled picture carrier, color subcarrier and a sound carrier. The stability of the generator is maintained by crystal control. The output signals are those corresponding to channel 3. A separate video output signal is also provided, having either positive or negative polarity.

The radio-frequency output is approximately .01 volt peak to peak across a 300-ohm load. The video output from the HI output terminal is approximately 8 volts peak to peak across 4,700 ohms. Luminance signals are available which show up at the edges of the color bars for checking the registration of the luminance and chrominance signals. A special rectifier circuit is built in the instrument for use with an external v.t.v.m. for measuring and adjusting sync and subcarrier amplitudes.

The picture carrier output is modulated by a color subcarrier and a front-panel switch can be used to eliminate the sound carrier from the output signal for quick identification of sound interference in the bar pattern. The sound carrier signal permits precise tuning of the receiver and checking its sound-rejection and beat-interference characteristics with respect to the color subcarrier and the sound carrier.

Hickok model 655XC. This instrument (see photo) produces a series of eight vertical color bars—green, yellow, red, magenta, white, cyan, blue and black. The white bar is useful as a reference for setting up the colors. It is only when the receiver has proper convergence and correct signal amplitudes of red, blue and green that a white signal can be obtained.

The Hickok unit uses crystal control for the 3.58-mc signal and for the horizontal frame rate.

In addition to the color bar pattern, the generator produces an NTSC standard in-phase I signal and a Q (quadrature phase) signal besides R - Y and B - Y signals.

A 3.58-mc subcarrier of 1 volt peak to peak is provided for alignment and testing the color synchronizing stage. A video output signal is available of 2 volts peak to peak on open-circuit measurement, dropping to 1 volt across a 100-ohm load. The signal can be switched to either positive or negative polarity. An r.f. signal is available, modulated with the color-bar pattern. The r.f. signal can be tuned through channels 4, 5 and 6. A sound carrier output signal is also provided.

Triplet model 3439. The 3439 (see photo) produces 10 vertical color bars in the sequence, from left to right: yellow-orange, orange, red, blue-red, magenta, blue, green-blue, cyan, blue-green and green. The second, fifth and eighth vertical bars are fairly close to the NTSC standard I, Q, -I signals (3° off). To adjust I and Q circuits, the hue control of the receiver can be varied for the proper phasing of these three signals.

Crystal operation is provided for the signals and the output is set for channel 3. A sound carrier is available, as well



Triplet model 3439 generator.



Kay Electric Chromabar generator.



Win-tronix 150 rainbow generator.

as a video or a modulated r.f. signal. The video signal can be switched to either a positive or negative polarity output. To adjust and observe signal amplitudes, the Triplett unit has a built-in v.t.v.m. with the dial centered above the controls.

**Win-Tronix model 150.** Designated as a "Rainbow Generator" by the manufacturer, the unit (see photo) provides from one to eight vertical color bars with the main colors produced having the sequence: red, magenta, blue, cyan, green. It has provisions for modulating the r.f. carrier with a 60-cycle luminance signal and the 3.58-mc chroma subcarrier. The chroma subcarrier is phase-modulated with respect to the television receiver frequencies in a linear phase-sweep process. This method scans all the color phases from zero to 360°, a process similar to that used in sweep-frequency generators for TV and FM sideband alignment.

A 300-ohm output connector at the rear of the unit provides the 3.58-mc color signal or the r.f. signal modulated by the color signal. The modulated r.f. signal output is approximately 0.3 volt. Crystal control can be had by inserting a 3.58-mc crystal into the internally wired socket of the unit.

**Combination units**

While generators are available which produce white dots for convergence adjustments, some combination units on the market contain both the bar and dot generators in one unit. One of these is the **Chromabar generator** (see photo) manufactured by the Kay Electric Co. This unit provides six NTSC colors: green, yellow, red, magenta, blue and cyan, available individually with black-and-white. Other colors, including gray

shades or I and Q, are included on special order.

The output amplitude is continuously variable to a maximum of 1.4 volts peak to peak across a 75-ohm load. The phase-angle accuracy is within 3°.

Another unit combining the color bar and white dot generators into a single unit is the **Jackson model 712 color bar generator**. This instrument provides a positive or negative video signal and an r.f. signal on channels 3, 4 and 5.

The bar generator produces eight bars: white, yellow, cyan, green, magenta, red, blue and black. A switch permits selecting just the NTSC standard I and Q signals or the R - Y and B - Y signals. A sound carrier signal output is provided in addition to the r.f. and video signals. A switch selects either a luminance- or color-signal output. The video output is adjustable to a maximum of 2 volts peak to peak across a 90-ohm load resistance; the r.f. signal output has a maximum of 0.1 volt across a 300-ohm load.

In addition to the white dots for convergence checking, a white cross-bar signal can also be obtained. Jacks on the rear panel provide a 3.58-mc subcarrier burst signal output and a horizontal sync signal output.

**Dot generators**

**RCA WR-36A.** This dot generator (see photo) can be used with a channel selector set from channels 2 through 6. The maximum output voltage is .08. Approximately 10 to 13 vertical bars and 8 to 15 horizontal bars can be obtained. The same number of rectangular dots are available as well as a cross-hatch pattern.

The video signal output is 3.5 volts peak to peak on open circuit. It can


be made either positive or negative.

**Simpson model 434.** This Varidot white dot generator (see photo) produces from 6 to 15 vertical and from 6 to 14 horizontal dots. Controls vary dot width and height and horizontal and vertical retraces are blanked out. The r.f. output is adjustable for channels 2 through 6 and a balanced 300-ohm output is provided. The r.f. output is variable up to .05 volt r.m.s. on open circuit; the video output is adjustable to 3.5 volts peak to peak on open circuit. The internal sync and blanking provided by the generator eliminates the appearance of white smears between dot segments.

**Win-Tronix model 160.** The model 160 (see photo) white dot generator produces large and small white dots and vertical and horizontal bars for linearity checking. Approximately 10 horizontal and vertical dots are produced in the large-dot position; approximately 15 horizontal and 11 vertical in the small-dot position. The r.f. signal output is adjustable from channels 2 through 6. A jack is provided for external modulation of the r.f. carrier and another jack for increasing dot stability by sync injection from the TV receiver.

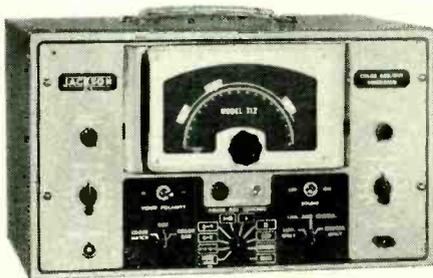**Other test equipment**

Instruments are available which provide specialized operations in the servicing and adjustment of color television receivers. One of these is the **Simpson Chromatic Probe** (see photo). It contains a crystal rectifier and several resistors, making up a nonlinear network for heterodyning. Thus, the probe can be used to produce the *difference* frequency when the outputs from an



Jackson bar-dot generator.



Simpson 434 white dot generator.



The RCA WR-36A dot-bar generator.

## TEST INSTRUMENTS




Left—the Win-Tronix model 160 white dot linearity generator.



Right — the Simpson model 406 Chromatic Amplifier.

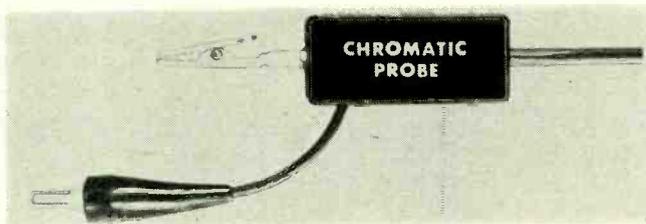Below — the Simpson chromatic probe—has crystal rectifier.



AM and an FM generator are fed to it. It is primarily designed to be used with a sweep generator providing two such signals simultaneously, such as the Simpson model 479 or 480. The probe is useful for checking the various frequency points on the response curve of the bandpass amplifier of a color TV receiver. It provides an equivalent detector source following the generators, thus eliminating the necessity for applying the generator signal through a preceding detector stage as is advisable when checking the response curve of video amplifiers.

An additional instrument, also manufactured by Simpson, is the Chromatic Amplifier model 406. It raises video signal levels to provide full-screen oscilloscope deflection when an insensitive scope is used.

The Chromatic Amplifier requires no

tuning and the front panel merely contains an on-off switch and the input and output terminals. It has a gain of 30 over a 4-mc band, with the output from the amplifier flat within  $\pm 0.5$  db from 80 kc to 4 mc. It has a high input impedance; the output impedance is approximately 2,200 ohms.

### Present equipment

As mentioned, black-and-white equipment can be used in TV servicing. Some can be modified for greater usefulness in servicing color receivers. For the technician about to begin color TV servicing, a high-voltage probe for the v.t.v.m. should constitute his initial purchase toward a future stock of color test equipment. The probe should be capable of extending the useful d.c. voltage range of the instrument above 25,000 (preferably to 30,000).

An oscilloscope should have good vertical sensitivity and wide-band vertical amplifier response. This means that the vertical sweep circuit of the scope should extend to approximately 4 mc to check the 3.58-mc subcarrier oscillator or to observe the signals in the burst amplifier, burst-gate circuits, etc. The less expensive scopes have a vertical frequency response to only 30 kc and are not suitable for test procedures on the subcarrier oscillator. Such scopes can be used for checking the vertical and horizontal sweep systems and similar circuits, in the color receiver which are also present in black-and-white sets. The sensitivity of an existing scope can be increased by using the Simpson Chromatic Amplifier or similar equipment.

Some test instruments can be altered to increase their usefulness for color TV servicing. The manufacturer should be consulted with respect to available data for making changes. Owners of the Hickok model 650 bar generator, for instance, can convert it to produce white dots with a kit available from the maker for under \$10. This attachment, not only produces white dots for convergence adjustments, but permits retaining the black dots available for use with black-and-white receivers.

If the present bar generator can't be converted, the purchase of a white dot generator is recommended. With a high-voltage probe, sensitive oscilloscope and white dot generator, a considerable amount of color TV servicing and adjusting can be done. As soon as possible, however, a color bar generator should be acquired.

### Use of equipment

The technician should study the operating manual furnished with an instrument so that he is thoroughly familiar with the manner in which it is to be used.

If a color bar generator, for instance, fails to produce a proper sequence of colors, it is not necessarily an indication that it is at fault but rather that the various controls of the receiver require proper adjustment. A single color or virtually all sorts of colors can be obtained by improper use of the bar generator or improper setting of the fine-tuning, phase, hue and other controls on the receiver.

Precautions must also be taken with respect to the dot-bar generator so that brilliancy and contrast controls are properly set for observing dots and adjusting of convergence. While a number of bar and dot generators can be connected directly to the antenna terminals of the receiver, other leads are also provided for coupling to the sweep circuits of the receiver to assure good stability and lock-in. If the technician understands that greater care in adjustments is necessary for proper operation of color test equipment, he will have overcome one of the big hurdles in getting the most from color TV test equipment. END

you can't argue with acceptance

proven quality  
100% inspected  
accurate replacement  
prompt delivery


the most  
complete  
line

of twist mount  
dry electrolytic capacitors

Better than any claims we could make is the unqualified and enthusiastic acceptance by engineers and servicemen alike. These are some of the features on which this acceptance is based:

- Aluminum containers provide maximum protection against moisture.
- Low leakage, long shelf life.
- Designed for 85° C. operation.
- Complete with metal and bakelite mounting plates.
- Easy to mount.
- Extremely compact—yet highly dependable.

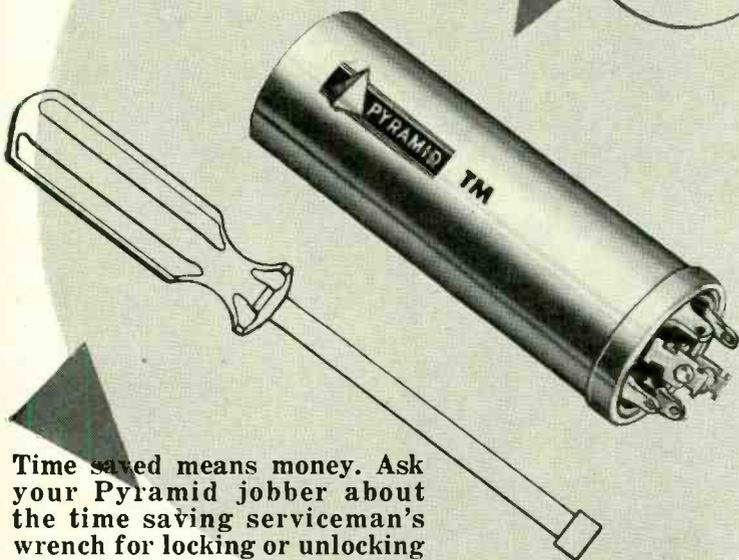Pyramid capacitors are listed in Sams' Photofacts



Time saved means money. Ask your Pyramid jobber about the time saving serviceman's wrench for locking or unlocking the mounting ears of Pyramid's twist mounts.

DISTRIBUTOR DIVISION

**PYRAMID**  
ELECTRIC COMPANY  
1445 Hudson Blvd., North Bergen, N. J.

# CHROMA SIGNAL GENERATOR

*An inexpensive portable signal generator for color TV servicing*

By CHARLES W. RHODES

**E**ITHER a color bar generator or a chroma generator is required to service color receivers. At present most commercial generators are rather expensive and heavy. This generator has been developed to fill the need for an inexpensive portable generator of high stability and accuracy. It can be used without a wide-band (0-5-mc) oscilloscope; the usual service instruments when equipped with a demodulator probe suffice.

In the absence of a color bar pattern from a TV station this instrument will show whether color reception can occur and if the entire chroma section of the receiver is working and properly adjusted. By signal-tracing techniques, a defective circuit may be quickly located. The very critical color a.p.c. (automatic phase control) system may be aligned completely. Lastly, it can provide a color bar pattern for color receivers on display in stores. A defect in the chroma or color a.p.c. circuits does not affect a color receiver tuned to a black-and-white program.

The instrument consists of two oscillators, a video carrier oscillator and a crystal-controlled chroma oscillator. The latter amplitude-modulates the video carrier oscillator as the plate of each oscillator (Fig. 1) is returned to B plus through a parallel resonant tuned circuit tuned to 3.5 mc. Link coupling from the carrier oscillator carries the output signal to the color receiver's antenna terminals via a length of 300-ohm line.

A small power transformer and selenium rectifier supply power and provide isolation from the a.c. lines. Two crystals are used: one, tuned to exactly 3.563795 mc by its shunt trimmer, will be referred to as the *offset* crystal; the other, tuned to the color subcarrier frequency, 3.579545 mc, is known as the *locked* crystal.

Construction is very simple, there being no critical lead dress. The use of short direct wiring as is customary in all r.f. equipment is desirable. An old TV booster unit makes a very handy starting point as it generally has the transformer, power supply and tube socket. The crystal trimmers should not be accessible except for initial adjustments. The carrier oscillator transformer is tuned to the video carrier frequency of an unused TV channel. Connect the chroma generator to any set tuned to the desired channel and, starting with the minimum value of inductance, adjust for maximum quieting of the snow level on the receiver and then increase inductance a little more. This is not at all critical. The 3.5 mc tuned circuit T1 is tuned for maximum grid-leak bias on the crystal oscillator. This also is a broad adjustment and covers both crystal frequencies.

The crystals used may be surplus or 75-meter amateur units. As they may be pulled in frequency only a few hundred cycles, they must be very close to the specified frequencies. For the locked crystal order either 3580 kc or 3579.5

kc. The other may be either 3564 kc or 3595 kc. I had no trouble with either of the surplus 3580-kc crystals purchased nor with an amateur 3564-kc crystal.

The exact crystal frequencies may now be adjusted by connecting the generator to a properly working color TV set. With the set receiving a program, switch to the generator's channel and turn up the chroma and contrast controls. Switch the *offset* crystal on and adjust its trimmer until one color band of red, blue, cyan, etc. appear. Momentarily switch off channel and then back—adjust the trimmer for fastest lock-in action. Switch the *locked* crystal on and adjust its trimmer to decrease the number of horizontal color bars until suddenly a locking action occurs, leaving only one hue on the screen. Again, try to lose sync by switching off chan-



Fig. 2—Output of the burst amplifier.

nel and back, adjusting for fastest lock-in action. (With the *locked* crystal, on some color sets, a very narrow bar will appear at the left edge of the screen and then a wider band of another hue at the right. A third hue will fill about two-thirds of the screen. This is immaterial.)

While the above procedure sets these crystals fairly accurately, enough so for signal tracing and matrix adjustment, there is an even more accurate method and it should be used before the color a.p.c. is aligned. Tune in either a color program or a station transmitting a color stripe. Short the a.p.c. voltage to chassis and adjust the coil shunting the crystal in the receiver to get the color to lock in at least momentarily. Now, with the a.p.c. still shorted, switch the receiver to the generator. Adjust the *offset* crystal until the colors just float left and right. Adjust the *locked* crystal in the same way. Remove the short on the receiver's a.p.c. This procedure may be done when convenient as the first is generally satisfactory.

The color a.p.c. can lock to this chroma signal generator because at the start of each line the burst amplifier


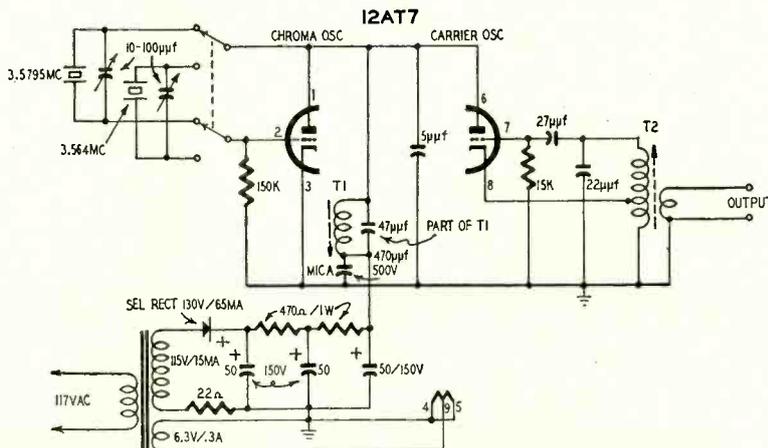


Fig. 1—Schematic diagram of the chroma signal generator—all values are given.

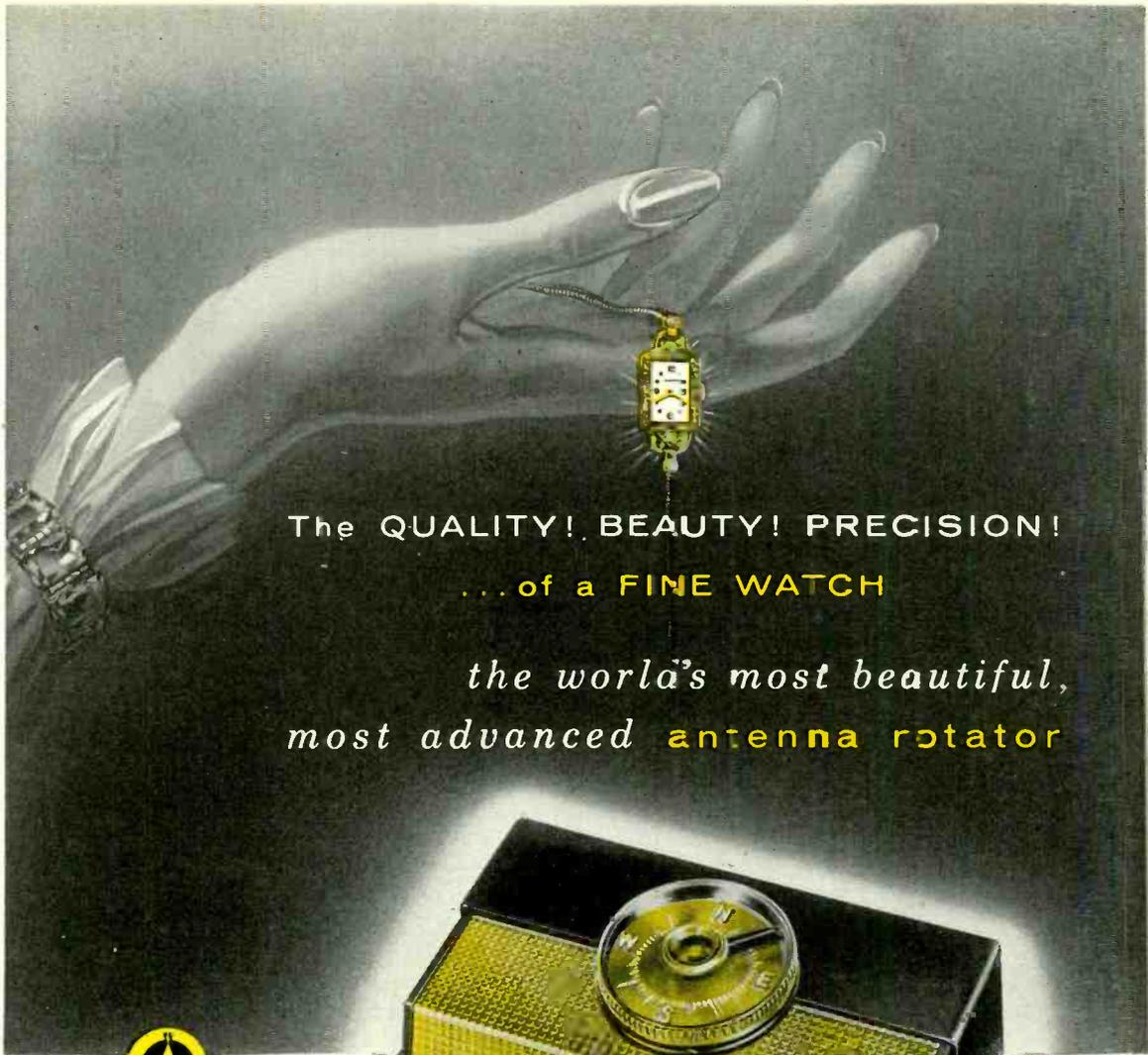

The **QUALITY! BEAUTY! PRECISION!**  
 ...of a **FINE WATCH**

*the world's most beautiful,  
 most advanced **antenna rotator***




**Thompson Products**

**Automatic  
 ELECTRONIC**

**Superotor.**

**F**or accuracy, dependability, and ease of control, the new Electronic Automatic Superotor is years ahead of any other antenna rotator on the market. Electronic VP\* Tuning, completely silent operation, and smooth, even rotation combine to bring you instantly, automatically, the finest TV picture you've ever enjoyed.

\* Vernier Precision

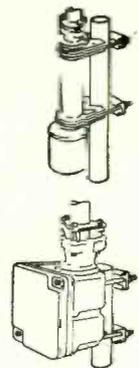

**INTERCHANGEABLE ROTATORS**

Famous Superotor models "100" and "500" have both been designed for automatic operation.

**OTHER THOMPSON PRODUCTS  
 ELECTRONIC AFFILIATES**

- Bell Sound Systems • Dage Television • Ramo-Wooldridge Corp.
- Pacific Semi-Conductors, Inc.


**ELECTRONICS DIVISION**

**Thompson Products, Inc.**




2196 CLARKWOOD ROAD • CLEVELAND 3, OHIO  
 Available in Canada thru Atlas Radio Corp., Ltd., 50 Wingold Ave., Toronto


TEST INSTRUMENTS

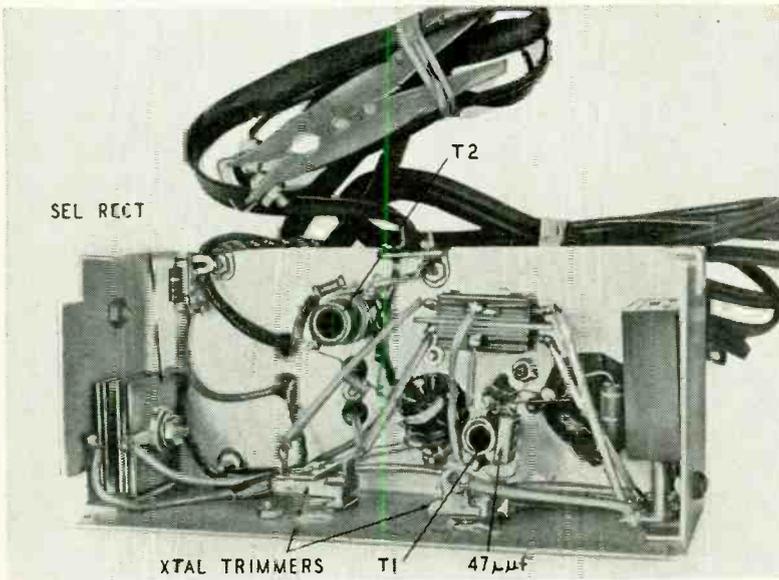

Underchassis view of the generator.

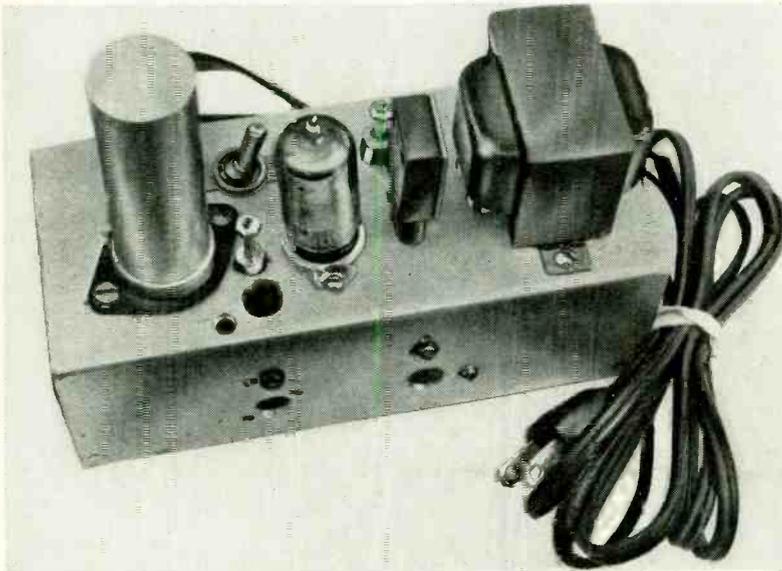

Unit mounted on 6 x 3 x 2-inch chassis.

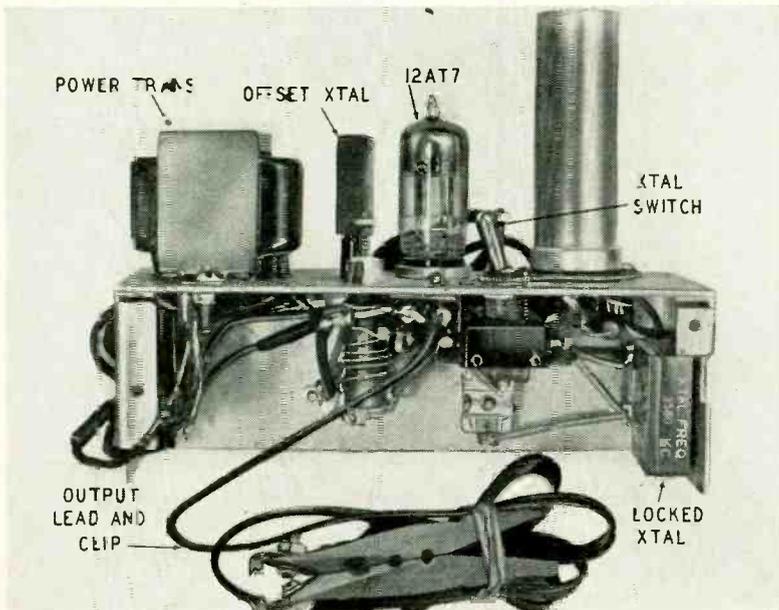

View shows overall layout of components.

conducts briefly (Fig. 2), feeding the generator's output to the a.p.c. detector. The burst amplifier therefore gates the incoming signal and creates the burst pulse. The bandpass amplifier is cut off during this *same* interval (Fig. 3) and hence delivers no chroma to the demodulators when the burst is sampled. Therefore we find that they have

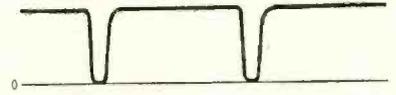


Fig. 3—Output of bandpass amplifier.

no outputs at that moment. In the demodulators, the chroma signal beats with the 3.58-mc subcarrier. The difference frequency is the a.c. output signal. As the *offset* crystal is 15,750 cycles higher or lower (it matters not which), the demodulators' outputs are sine waves (Fig. 4) at 15,750 cycles. Because during burst interval no chroma reaches the demodulators, a notch in the

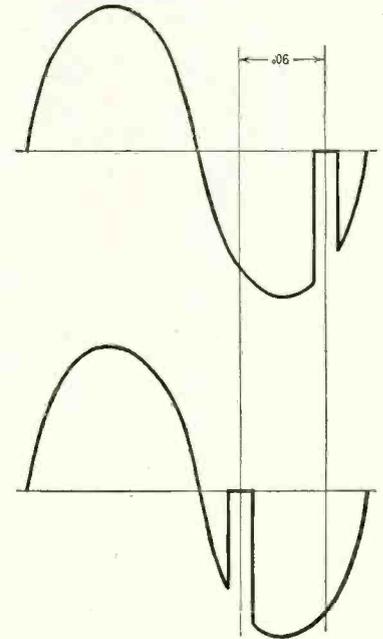


Fig. 4—Output of the two demodulators using the offset crystal.

sine waves will appear denoting burst. Since the subcarrier fed to the two demodulators is different in phase by 90° in the two circuits, the burst notch will be displaced 90° between the two sine waves.

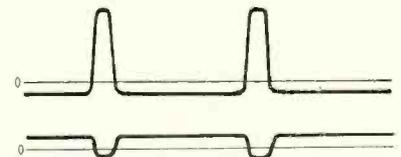


Fig. 5—Output of the two demodulators using the locked crystal.

The *locked* crystal, being of the same frequency as the subcarrier, produces only a d.c. output in the demodulator proportional to the cosine of the phase angle between the chroma and subcarrier. This d.c. voltage changes to that



# TRIO *Zephyr Royal*

**highest performance ever achieved in a TV antenna**


**MODEL ZR-1** PATENT NO. 2,703,840

**SUPERIOR IN**

- design
- workmanship
- performance

Now, the tests of TRIO engineers have been confirmed unanimously by scores of unsolicited reports from the field. Distributors, dealers and thousands of consumers have verified these tests, proving it's the best antenna ever designed. The ZEPHYR ROYAL's performance on ALL CHANNELS, 2 thru 13, is nothing short of miraculous, thanks to its revolutionary new WING DIPOLE PRINCIPLE and STAG-

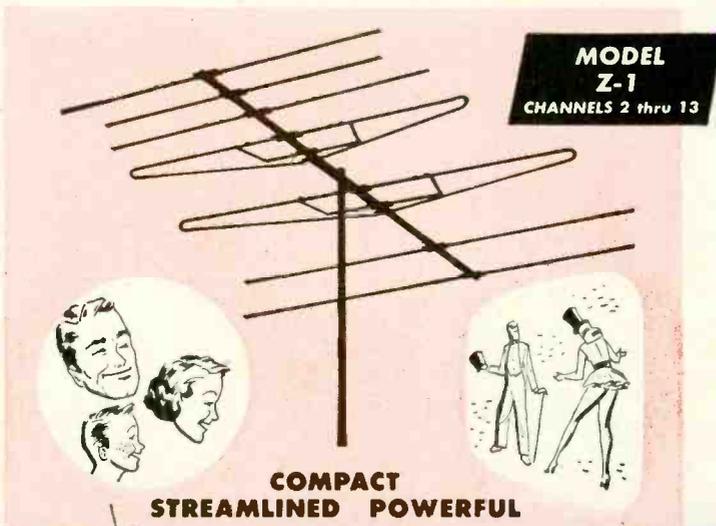GER-TUNING developed and introduced by TRIO engineers. It is pre-assembled—uses Instalok Clamps; fiberglass insulators and riveted construction, is lightweight, yet extremely rugged. For these reasons the ZEPHYR ROYAL is America's new favorite—the No. 1 Antenna—electrically and mechanically—and one bay does it!



**COMPACT  
STREAMLINED POWERFUL**

# TRIO *Zephyr*

**more performance per dollar than any other antenna!**


The TRIO ZEPHYR is the popular choice when the extra features of the ZEPHYR ROYAL are not required. Using two of the revolutionary new wing dipoles, the ZEPHYR will outperform any other antenna in its price range on the market. Needless to say—the ZEPHYR uses the same superior construction features found in the ZEPHYR ROYAL. For its size and weight, its performance also is nothing short of miraculous!

**TRIO** *Manufacturing Company*  
GRIGGSVILLE, ILLINOIS  
COPYRIGHT 1955—TRIO MANUFACTURING COMPANY

Export Sales Div.: Scheel International, Inc., 4237 N. Lincoln Ave., Chicago, U.S.A. Cable Address: Harscheel

for  
**RELIABLE  
TV  
PERFORMANCE**

**AMPHENOL  
ACCESSORIES**

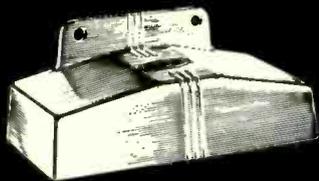

**TELE-COUPERS**

**TELE-COUPERS**

For effective coupling to one antenna in multiple-set installations, Tele-Couplers are a 'natural' for plus sales with the present trend toward two set families. Network is in an all weather protective case—may be mounted indoors or outdoors. UHF, VHF, VHF/UHF, FM.

114-088 2 SET TELE-COUPLER List \$3.75  
114-090 3 OR 4 SET TELE-COUPLER . . . List \$5.75

**ISOLATING NETWORKS**

Combine different frequency antennas into a single down-lead with an AMPHENOL Isonet, Duonet or Trisonet. Isonet: VHF/UHF; Duonet: Lo-VHF/Hi-VHF; Trisonet: Lo-VHF/Hi-VHF/UHF. All in durable, protective cases for mast mounting. Lowest-loss performance.

114-061 ISONET . . . . . List \$3.75  
114-094 DUONET . . . . . List \$3.50  
114-074 TRISONET . . . . . List \$4.50



**ISOLATING NETWORKS**

**HIGH PASS FILTER**

Interference below 50 mc which appears on the set as tearing lines, herringbone or dark bands will be eliminated with the AMPHENOL High Pass Filter. Easily attached, this accessory has been used to clear up low frequency interference in thousands of installations.

114-330 HIGH PASS FILTER List \$5.45



**HIGH PASS FILTER**

**TEST INSTRUMENTS**


which would be present without any input signal during burst time. Thus, with an oscilloscope, rectangular pulses (Fig. 5) at 15,750 cycles are observed at the demodulator outputs or on toward the picture tube.

The size and polarity of these pulses depend upon the hue control as it shifts burst phase.

If the demodulators are both dead, either the bandpass amplifier is defective (Fig. 3 won't appear) or the color killer has cut off the bandpass amplifier. The other possibility is that the color subcarrier oscillator is defective. An inoperative oscillator may be caused by a defect in the reactance tube circuits. If the oscillator is inoperative, Fig. 3 will be obtained but Figs. 2, 4 and 5 won't


One defective demodulator would be discovered when a sine wave of Fig. 4 is obtained from only one demodulator. The same applies for the color-difference amplifiers which follow the demodulators.

Fig. 6 is a vectorscope presentation. The output of the R - Y demodulator is connected to the oscilloscope vertical input, the B - Y demodulator to the horizontal input. The horizontal and

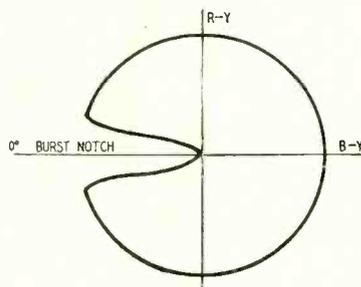

**Fig. 6—Pattern of the demodulator output in a color-difference receiver.**

vertical gain and positioning controls are adjusted to obtain a well centered circle. (The offset crystal is used.) This will be possible if the demodulators are both operating properly. Overloading may occur if the chroma control is advanced too far. The burst notch lies along the horizontal axis when the hue control is properly set. This notch should rotate about equally in both directions as the hue control is rotated, indicating its range is proper.

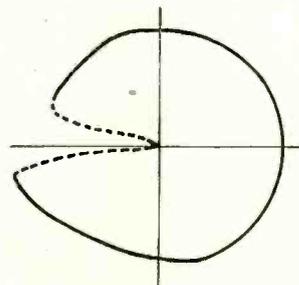

**Fig. 7—Pattern shows that the quadrature transformer is out of alignment.**

Where the best adjustments possible do not provide a good circle, but an ellipse as in Fig 7, the signals from the subcarrier oscillator are not at 90° as

AMERICAN PHENOLIC CORPORATION  
chicago 50, illinois  
AMPHENOL CANADA LIMITED  
toronto 9, ontario



## TEST INSTRUMENTS

they enter the demodulators and color fidelity is lost. Where the positive and negative outputs of either demodulator are not equal, clipping occurs and the demodulator tube is defective or its operating voltages are not correct. Too high a chroma control setting may cause overload, but this disappears with a reduced setting which still provides vivid colors on the color picture tube.

Fig. 8 shows the same presentation from the I and -Q test points in a CBS-Columbia color receiver which

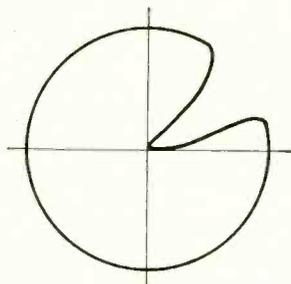


Fig. 8—Pattern of the demodulator output in an I-Q color TV receiver.

uses the I-Q wide-band system. The only difference is in the position of the burst notch. Here it is at about  $30^\circ$  to the -Q axis. When the hue control is properly adjusted on an I-Q receiver, the I gain control is also properly adjusted if the pattern of Fig. 6 appears when the red picture-tube grid is connected to the vertical input and the blue grid to the horizontal input. As there is no Y signal present, the matrix should have as outputs, R - Y and B - Y from I and Q. Adjusting the I gain control for a circle provides accurate adjustment.

### Parts for chroma signal generator

**Resistors:** 1—22, 1—15,000, 1—150,000 ohms,  $\frac{1}{2}$  watt; 2—470 ohms, 1 watt.

**Capacitors:** 1—5; 1—22, 1—27  $\mu\text{f}$ , NPO ceramic; 1—470  $\mu\text{f}$ , 500 volts, mica; 1—50-50-50  $\mu\text{f}$ , 150 volts; 2—10-100  $\mu\text{f}$ , trimmer, NPO ceramic.


**Miscellaneous:** 1—T1, 4.5-mc trap (J. W. Miller 4170 or equivalent); 1—T2,  $4\frac{1}{2}$  turns of No. 18 wire wound on  $\frac{1}{2}$ -inch form, turns spread over  $\frac{1}{2}$  inch on form, tap  $\frac{1}{2}$  turns from bottom, link 1 turn around bottom end, powdered-iron core; 1—power transformer, 1:1 turns ratio with 15-ma secondary, 6.3 volts @ 300 ma; 1—12AT7 and socket; 1—d.p.d.f. switch; 1—crystal, 3579.5 kc (see text); 1—crystal, 3564 kc (see text); 1—selenium rectifier, 130 volts @ 65 ma; 2—crystal sockets; 1—aluminum chassis, approximately 6 x 3 x 2 inches; 1—power cord; 1—length of 300-ohm line; 1—terminal strip.

In a color-difference receiver, the equivalent of the I gain control is the R - Y gain control. This may be adjusted or checked by first setting the gains of the horizontal and vertical amplifiers in the scope equal. Feed in, say, 6.3 volts a.c. and adjust for a  $45^\circ$  line or ellipse. Now reconnect the scope as before and adjust the gain control so that the vertical (R - Y) deflection is five-ninths the horizontal (B - Y) deflection.

Once properly aligned, the chroma generator provides a highly stable frequency source to align the color a.p.c. system and a means of checking its performance in accordance with the set manufacturer's instructions. **END**
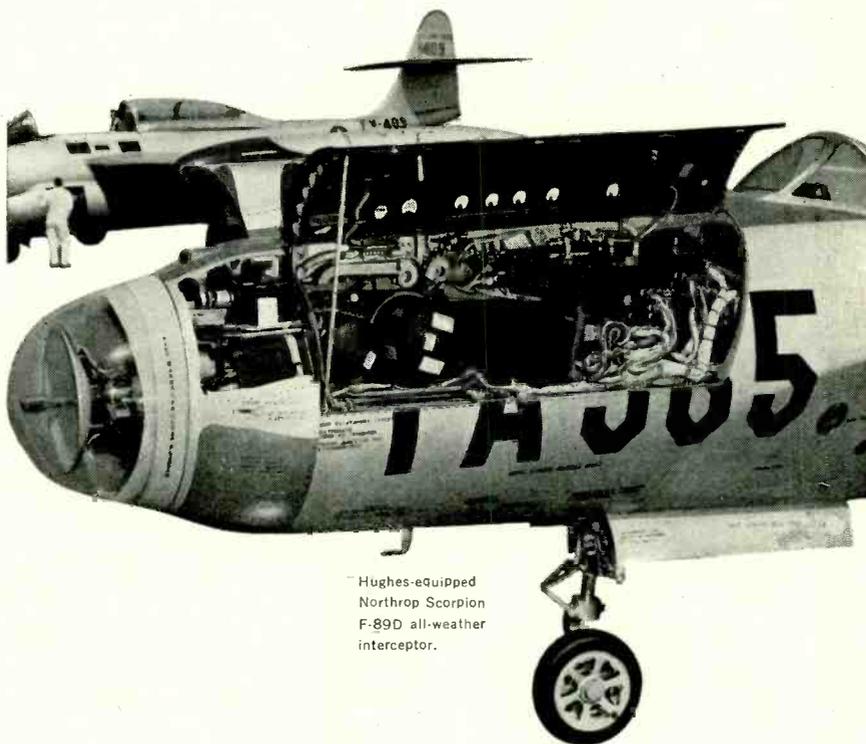
## Use Your Military Training

*The time was never  
more opportune than now  
for becoming  
associated with the field  
of advanced electronics.  
Because of military  
emphasis this  
is the most rapidly  
growing and  
promising sphere of  
endeavor for the young  
electrical engineer  
or physicist.*



Hughes-equipped  
Northrop Scorpion  
F-89D all-weather  
interceptor.

### E.E. or PHYSICS GRADUATES

*with experience in*

### RADAR or ELECTRONICS

*or those desiring to enter these areas...*

Since 1948 Hughes Research and Development Laboratories have been engaged in an expanding program for design, development and manufacture of highly complex radar fire control systems for fighter and interceptor aircraft. This requires Hughes technical advisors in the field to serve companies and military agencies employing the equipment.

As one of these field engineers you will become familiar with the entire systems involved, including the most advanced electronic computers. With this advantage you will be ideally situated to broaden your experience and learning more quickly for future application to advanced electronics activity in either the military or the commercial field.

Positions are available in the continental United States for married and single men under 35 years of age. Overseas assignments are open to single men only.

*Scientific Staff  
Relations*


# Hughes

RESEARCH AND  
DEVELOPMENT  
LABORATORIES

*Culver City  
Los Angeles County  
California*

# ELECTRONIC COMPASS ORIENTS TV ANTENNA

By RUFUS P. TURNER

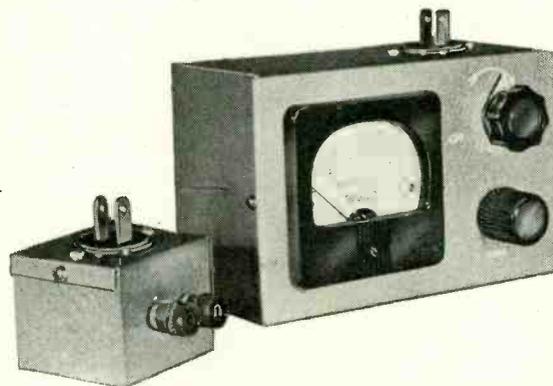

Two units make up the antenna orienter.

THE conventional TV antenna orientation meter consists of two parts: a diode rectifier capacitance-coupled to the video electrode (grid or cathode) of the picture tube right at the set, and a d.c. microammeter which is transported to the roof and is connected to the diode output through a long two-wire line. Many service technicians prefer the compass to a field-strength meter as an indicating instrument for placing and orienting antennas because it operates in conjunction with the receiver to be used with the antenna. Although the antenna compass has been in existence for 6 years, very little has been done to improve it.

The compass described in this article is eight times more sensitive than the conventional type. It has a more rugged indicating meter and loads the TV receiver less. The original compass circuit used a 0-200- $\mu$ a d.c. meter. My instrument has a 0-1-ma d.c. meter with a single-stage transistor d.c. amplifier for current gain. In this circuit, only 25 microamperes d.c. output from the pickup diode will deflect the milliammeter full scale. A single 1.5-volt size-D flashlight cell powers the amplifier, but this need for d.c. voltage is no inconvenience since the cost of replacing this cell is only 10 cents and (due to the low full-signal drain of 3 ma) over 1,000 hours of life can be expected on a basis of 8 hours of continuous use per day. This represents over 4 months of battery life at 8 hours a day! The part of the instrument taken to the roof weighs only 2 pounds.

The pickup section (see diagram) consists of capacitors C1 and C2, a

1N54 diode and resistor R1. These components are mounted in small box but might also be arranged in a probe. The video signal is picked up through clips connected to the receiver ground and to the video pin 2 or 11 of the picture-tube socket. The d.c. output of the pickup section is fed to a two-prong chassis type male plug. The 1N54 diode has been used because of its improved back resistance. A higher resistance R1 may be used without decreasing the rectification efficiency.

A two-wire line, which can be a length of lamp cord or 300-ohm ribbon, is run from the pickup box plug to the corresponding plug in the remote meter box. On each end of this line there is a female receptacle for connection with the male plugs.

The meter box contains the transistor amplifier circuitry, milliammeter and flashlight cell. The amplitude of the incoming direct current, and accordingly the meter swing, is adjusted by sensitivity control, R2. The meter is set initially to zero with potentiometer R3. This operation is the same as zeroing a vacuum-tube voltmeter.

With R2 set to its "zero"-resistance (maximum-sensitivity) position, 2.82 volts peak r.f. input to the diode circuit will provide full-scale deflection of the milliammeter. When R2 is at its "maximum"-resistance (lowest-sensitivity) setting, approximately 100 volts peak r.f. will be required. This covers the whole range of conditions likely to be met in practice. Settings of the sensitivity control have only slight disturbing effect on meter zero.

Since there are no tube heaters to warm up, the instrument is ready to

(Continued on page 124)

*A sensitive transistorized  
meter for placing and  
orienting antennas*

# ALLIED knight-kits

give you **MORE** precision quality... save you **MOST**  
**FINEST ELECTRONIC EQUIPMENT IN KIT FORM—FAMOUS FOR:**



**LOW COST**—huge buying power and **DIRECT SALE** pass biggest savings on to you. You do the easy assembly and your built-up instrument is equivalent in appearance and performance to equipment selling for several times the **KNIGHT-KIT** price.

**ADVANCED DESIGN**—months of research, development and field testing go into each **KNIGHT-KIT** for assurance of top performance.

**EASY ASSEMBLY**—all chassis and panels are punched for accurate assembly; all parts are fully identified. Instruction manuals are a marvel of simplicity and clarity.

**ALLIED**—the reliable name in Electronics—gives you the greatest value in **KNIGHT-KITS** through **DIRECT SELLING**

**NEWEST  
 PRINTED CIRCUITS**

## knight-kit PRINTED CIRCUIT 5" OSCILLOSCOPE KIT

Model F-144

**\$69<sup>00</sup>**

\$6.90 down,  
 12 months to  
 pay balance

New wide-band, full-size 5" Oscilloscope; equals or better the performance of commercially-wired scopes costing several times the price. Two printed circuit boards and exclusive laced wiring harness cuts assembly time to minimum. Ideal for the professional Laboratory, for color TV servicing and high frequency applications. Has 6 times the usual sweep range—from 15 to 600,000 cps. Locks in frequencies as high as 9 mc. Vertical response from 5 cycles to 5 mc.

Response:  $\pm 1$  db at 3.58 mc;  $\pm 3$  db at 5 mc. High vertical sensitivity of 25 rms millivolts/inch. Input capacitance 20 mmf. Outstanding features: cathode-follower vertical and horizontal inputs; 2nd anode provides 1400 volts for high-intensity trace; push-pull vertical and horizontal amplifiers; positive and negative locking; faithful square wave response; frequency-compensated input attenuator; Z-axis input for intensity modulation; one volt peak-to-peak calibrating voltage; internal astigmatism control; blanking circuit to eliminate retrace lines; DC positioning control. Complete with all tubes and parts, ready for easy assembly. Handsome professional case finished in blue, with gray control panel. Shpg. wt., 40 lbs.


Model F-144. Printed Circuit 5" Oscilloscope Kit. Net only... **\$69.00**  
 Model F-148. Demodulator Probe. Net... **\$3.45**  
 Model F-147. Low Capacity Probe. 12 mmf. Net... **\$3.45**

## YOU SAVE MORE BECAUSE YOU BUY DIRECT

Buy with confidence at lowest cost. You get the latest advances in electronic equipment design in **KNIGHT-KITS**. You get premium quality parts for absolute dependability. And you save the **MOST** because you buy **DIRECT**.

Build with confidence. **KNIGHT-KITS** are designed for easiest assembly—all you need is a soldering iron, screwdriver and pliers. Manuals are easy to follow—it's just like having a good instructor at your side.

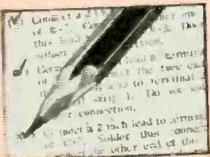**ALLIED** stakes its 35-year reputation in the Electronics field on your complete success and fullest satisfaction with **KNIGHT-KITS**.




### "STEP-AND-CHEK" ASSEMBLY METHOD

You just follow each step and check it off as you complete it. You always know where you are and what to do next with a **KNIGHT-KIT** Manual.


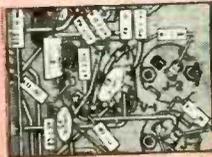
### "KING-SIZE" DIAGRAMS

Diagrams are duplicated in large wall size to hang conveniently over your work. Helps you see and understand the finest details clearly and easily.



### "SPOTLIGHT" PICTORIALS

Special two-tone treatment makes it easy for you to spot the circuit you're working on, separates it from work you've already completed. "You always know where you are."

ALL PRICES NET F.O.B. CHICAGO

**NEWEST  
 PRINTED CIRCUIT**

## knight-kit PRINTED CIRCUIT VTVM KIT

Model F-125

**\$24<sup>95</sup>**



New, extremely stable, highly accurate VTVM. Greatly simplified wiring—entire chassis is a printed circuit board. Features maximum convenience in arrangement of scales and controls. With peak-to-peak scale for FM and TV work. Ranges: AC peak-to-peak volts, C-4-40-140-1400-4000; AC rms volts and DC volts, 0-1.5-5-15-50-150-500-1500; ohms; 0-1000, 10K, 100K; 1-10-100-1000 megs; db scale, -10 to +5. Uses low-leakage switches and 1% precision resistors. Balanced-bridge, push-pull circuit permits switching to any range without

adjusting zero set.  $4\frac{1}{2}$ " meter, 200 microamp movement. Polarity reversing switch. Input resistance, 11 megs. Complete kit, ready to assemble. Shpg. wt., 6 lbs.

Model F-125. Printed Circuit VTVM Kit. Net only... **\$24.95**  
 Model F-126. Hi-Voltage Probe; extends DC range to 50,000 Volts. Net... **\$4.50**  
 Model F-127. Hi-Frequency Probe; extends AC range to 250 mc. Net... **\$3.45**

## EASY PAYMENT TERMS

If your total Knight-Kit order is over \$45, take advantage of our liberal Time Payment Plan—only 10% down, 12 full months to pay. Write for application form.

**ALLIED RADIO**

SEE FOLLOWING PAGES

# ALLIED knight-kits ....



Portable  
Tube Tester Model

Model F-143

**\$29<sup>75</sup>**

knight-kit

## EASY-TO-BUILD TUBE TESTER KIT—OUTSTANDING VALUE

Expertly designed, up-to-date, ideal for the laboratory or service shop. Remarkably low priced, yet it offers high accuracy, top versatility and convenience. Features provision for testing 600-ma tubes; roll-chart data for all popular series-string types. Tests 4, 5, 6 and 7-pin large, regular and miniature types, octals, loctals, 9-pin miniatures and pilot lamps. Tests for open, short, leakage, heater continuity and quality (by amount of cathode emission). 4½" square meter with clear "GOOD-?-REPLACE" scale. With line-voltage indicator and line-adjust control. Choice of 14 filament voltages from .63 to 117 volts. Blank socket for future type tubes. Universal-type selector switches for any combination of pin connections. Single-unit, 10-lever function switch simplifies assembly. Illuminated roll chart lists over 700 tube types. Complete kit, ready for easy assembly. Shpg. wt., 14 lbs.

Model F-143. Counter type Tube Tester Kit. Net only ..... **\$29.75**  
 Model F-142. As above, but with carrying case. Net only ..... **\$34.75**  
 Model F-141. TV Picture Tube Adapter for above. Net only ..... **\$3.75**

## QUALITY ELECTRONIC TEST EQUIPMENT IN LOW COST KIT FORM

### BUY WITH CONFIDENCE

- Advanced Electronic Design
- New Printed Circuits
- Easy-View, Hi-Legibility Panels
- Professional Streamlined Styling
- Matched Instruments
- Premium Quality Components



Model F-137

**\$31<sup>50</sup>**

knight-kit

## AUDIO GENERATOR KIT

Save money—have performance equal to instruments at many times the price! Provides an ideal audio frequency source for checking audio circuits of amplifiers and other hi-fi equipment; also checks speaker response. Frequency range: 20 cps to 1 mc in 5 ranges. Output voltage: 10 volts into 600 ohms impedance, ± 1 db to 1 meg. Generator imp., 600 ohms. Less than .25% distortion from 100 cps through the audible range; less than .5% when driving 600 ohm load at maximum output. Continuously variable step-attenuated output. Circuit as developed by U. S. Bureau of Standards. Complete kit with professional portable case, ready to assemble. Shpg. wt., 17 lbs.

Model F-137. Audio Generator Kit. Net only .... **\$31.50**



knight-kit  
**20,000 OHMS/VOLT  
VOM KIT**

Model F-140

**\$26<sup>50</sup>**

TOP VOM VALUE

Outstanding quality and performance at extremely low cost. Features 32 ranges; full vision 4½" meter; accuracy ± 2% of full scale; 50 microampere sensitivity for 20,000 ohms/volt input resistance on DC; front panel "zero adjust." Single switch selects function and range. Range: AC, DC and output volts, 0-2.5, 10-50-250-1000-5000; Resistance, 0-2000-200,000 ohms and 0-20 meg.; DC ma, 0-1-10-100; DC amps, 0-1-10; Decibels, —30 to +63 in 6 ranges. Uses precision 1% multipliers. Complete kit with bakelite case, batteries and test leads. Shpg. wt., 5 lbs.

Model F-140. 20,000 ohms/volt VOM Kit. Net only ..... **\$26.50**



knight-kit  
**1,000 OHMS/VOLT  
VOM KIT**

Model F-128

**\$14<sup>25</sup>**

Exceptional accuracy and versatility at amazing low cost. Ideal for service shop, lab and Amateur use. Uses 4½" meter (400 microamp movement) with separate scales for AC voltage and current, DC voltage and current, decibels and resistance. 38 ranges include: AC, DC and Output volts, 0-1-5-10-50-100-500-5000 (1000 ohms/volt sensitivity); Resistance, 0-1000-100,000 ohms and 0-1 meg.; Current, AC or DC, 0-1-10-100 ma and 0-1 amps; Decibels, —20 to +69 in 6 ranges. Uses 1% precision resistors. 3-position function switch and 12-position range switch. Complete kit with bakelite case, battery and test leads. Shpg. wt., 2½ lbs.

Model F-128. 1,000 ohms/volt VOM Kit. Net only ..... **\$14.25**



Model F-124

**\$18<sup>75</sup>**

knight-kit

## RESISTOR-CAPACITOR TESTER KIT

This new highly accurate tester meets the critical requirements of lab and service shop. Measures capacitance and resistance; checks for opens and shorts in paper, mica and ceramic capacitors; shows power factor of electrolytics. Large dial shows capacitance and resistance at a glance; balanced-bridge circuit with "magic eye" for correct dial setting. Direct-reading potentiometer and "magic eye" measure power factor from 0-50%. Tests capacitors with rated voltages applied. 5 test voltages: 50, 150, 250, 350, 450. Capacity ranges: 10 mmf to .005 mfd, .001 to .5 mfd, .1 to 50 mfd and 20 to 1000 mfd. Resistance ranges: 100 to 50,000 ohms and 10,000 ohms to 5 megs. Accuracy, ± 10%. Automatic discharge feature prevents after-test shock. Complete kit with professional portable case includes tubes, instructions and all required parts. Shpg. wt., 8 lbs.

Model F-124. Resistor-Capacitor Tester Kit. Net only ..... **\$18.75**

**EASY PAYMENT TERMS:** If your total kit order comes to over \$45, take advantage of our liberal Time Payment Plan—only 10% down, 12 full months to pay. Write for application form.

**BUY DIRECT AND SAVE!**

order from

**ALLIED RADIO**

100 N. WESTERN AVE., CHICAGO 80, ILL.

# better by far...easiest to build and YOU SAVE MORE\*

**IDEAL FOR SERVICE TECHNICIANS,  
INDUSTRIAL LABS, TRAINING SCHOOLS**

**\*YOU SAVE  
because you  
BUY DIRECT**

## BUILD WITH CONFIDENCE

- Crystal-Clear Instruction Manuals
- "Step-and-Chek" Building Method
- "King-Size" Diagrams
- "Spotlight" Pictorials

**SAVE MONEY! BUY DIRECT**—get top quality—get the most for your test instrument dollar.



Model F-135  
**\$23<sup>75</sup>**

**knight-kit**

### VISUAL-AURAL SIGNAL TRACER KIT

A remarkable value in a kit which permits visual and aural signal tracing of RF, IF, video and audio circuits—costs no more than an audio signal tracer alone. Traces the signal from the antenna to the speaker. Reproduces signal at plate or grid connection of any stage. Identifies and isolates "dead" stages. Features: high usable gain of 50,000; "magic eye" with calibrated attenuators for signal presence indication and stage-by-stage gain measurements; built-in 4" PM speaker; RF probe for checking all stages; special audio probe tip included; provides noise test; built-in watt meter calibrated from 25 to 1000 watts; provision for external scope or VTVM. Complete kit with portable case. Shpg. wt., 13 lbs.

Model F-135. Visual-Aural Signal Tracer Kit. Net only.....**\$23.75**



**knight-kit  
RESISTANCE  
SUBSTITUTION BOX KIT**

Model F-139  
**\$5<sup>95</sup>**

Supplies 36 standard 1 watt resistance values between 15 ohms and 10 megohms with an accuracy of 10%. Resistance values are readily substituted into any circuit to determine proper value of resistor required to do a particular job. Uses simple, single 18-position switch for resistance selection, plus a slide switch which multiplies all values by 1000. In attractive bakelite case, 5 x 3 x 2". Complete with all parts, including 18" leads with insulated alligator clips. Full instructions for easy assembly. Shpg. wt., 2 lbs.

Model F-139. Resistance Substitution Box Kit. Net only.....**\$5.95**

**ALL PRICES NET  
F. O. B. CHICAGO**



Model F-145  
**\$19<sup>75</sup>**

### knight-kit LOW-COST RF SIGNAL GENERATOR KIT

An extremely popular kit, noted for its wide range and exceptional stability—saves you two-thirds the cost of a comparable wired instrument. Delivers output on fundamentals from 160 kc all the way out to 110 mc; useful harmonic output to 220 mc. Ideal for aligning RF and IF stages and for audio equipment troubleshooting. Also serves as TV marker generator when used with any sweep generator. Features the famous Colpitts circuit for high accuracy with negligible drift. RF output rated over 100,000 microvolts. Output can be modulated at 400 cycles. Has built-in sine-wave audio oscillator with output jack for 400 cycle output. Maximum audio output, 10 volts. Jack for external modulation; step and continuous-type output attenuators. Complete kit with professional portable case, including punched chassis, tubes, pre-wound coils and all required parts. Shpg. wt., 10 lbs.

Model F-145. RF Signal Generator Kit. Net only.....**\$19.75**




Model F-119  
**\$11<sup>65</sup>**

### SAVE UP TO 70%! SUPER-VALUE knight-kit CAPACITOR CHECKER KIT

Tests capacitors while they are still wired in the circuit! Saves time and bother in testing the many capacitors in a set; it's an absolutely essential instrument for the service technician. Just press a button and the "magic eye" instantly shows opens and shorts. Checks by-pass, blocking,

coupling and filter condensers from 20 mmf to 2000 mfd, even when the capacitor under test is wired with a resistance as low as 60 ohms. Capacitors between .1 mfd and 2000 mfd may be tested even when in parallel with resistance as low as 2 ohms. Housed in the professionally styled Knight-Kit case, sturdy steel in blue wrinkle finish with gray control panel. Complete kit, ready for easy assembly. Shpg. wt., 5 lbs.

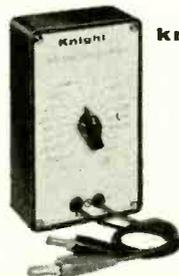Model F-119. Capacitor Checker Kit. Net only.....**\$11.65**



Model F-138  
**\$5<sup>50</sup>**

### knight-kit CAPACITANCE SUBSTITUTION BOX KIT

Provides 18 standard capacitor values from .0001 mfd. to .22 mfd., ± 20%. All values are 600 volt, with the exception of .15 and .22 which are 400 volt. A single 18-position switch selects all values quickly and easily—no need to touch the test leads. Saves hours of time and effort required to determine proper condenser value required. In bakelite case with anodized aluminum panel; 5 x 3 x 2". Complete with all parts, including 18" leads with insulated alligator clips. Easy to assemble in just minutes. Shpg. wt., 2 lbs.

Model F-138. Capacitance Substitution Box Kit. Net only.....**\$5.50**

**YOU SAVE MORE BECAUSE YOU BUY DIRECT • ORDER TODAY**

# ALLIED knight-kits ....

**LOW-COST  
QUALITY HAM GEAR**



**knight-kit**

## 50 WATT CW TRANSMITTER KIT

Model SX-255

**\$42<sup>50</sup>**

**Built-in Pi-Type Antenna Coupler**

Check the features packed into this new transmitter kit and you'll see why it's one of the greatest Amateur values ever offered. Compact and versatile, it is the perfect low-power rig for the beginning Novice or seasoned veteran. Features: 50 watts input to 807 final; high-efficiency 6AG7 modified-Pierce oscillator takes crystal or VFO without circuit changes; bandswitching coverage of 80, 40, 20, 15, 11-10 meters; pi-section antenna output matches line impedances from 50 to 1200 ohms—permits use with any type of antenna. Crisp, clean, cathode keying of oscillator and final. Power take-off plug supplies filament and B-plus voltages for other equipment. Copper-finished chassis and cabinet interior, filtering, shielding, bypassing, and coaxial SO-239 antenna connector provide excellent TVI suppression. Meter reads either plate or grid current of final. Jacks for VFO, crystal, and key. Supplied with all parts, tubes and step-by-step instructions. Less crystal and key. Size, 8 $\frac{1}{4}$ " x 11 $\frac{3}{8}$ " x 8 $\frac{3}{4}$ ". For 110-120 volts, 50-60 cycle AC. Shpg. wt., 18 lbs.

SX-255. 50-Watt Transmitter Kit. Net. .... **\$42.50**



**knight-kit  
SELF-POWERED  
VFO KIT**

Model S-725  
**\$27<sup>50</sup>**

Complete with built-in power supply! Careful design and voltage regulation assure high stability. Excellent oscillator keying characteristic for fast break-in without clicks or chirps. Full TVI suppression. Has plenty of bandspread; separate calibrated scales for 80, 40, 20, 15, 11 and 10 meters; vernier drive mechanism. 2-chassis construction keeps heat from frequency determining circuits. Output cable plugs into crystal socket of transmitter. Output on 80 and 40 meters. With Spot-Off-Transmit switch for "no swish" tuning. Extra switch contacts for operating relays and other equipment. Complete kit for easy assembly. Shpg. wt., 8 lbs.

Model S-725. Self-Powered VFO Kit. Net. .... **\$27.50**



**knight-kit  
CODE PRACTICE  
OSCILLATOR KIT**

Model S-239  
**\$4<sup>95</sup>** Transistorized—  
Powered by Flash-  
light Battery

An ideal new code practice oscillator. Uses transistor circuit. Extremely low current consumption—powered by single penlight battery. Provides crisp, clear tone (400 to 600 cps). Has input jack for earphone; screw-type terminal strip for key. In compact bakelite case (2 $\frac{3}{8}$ " x 3 $\frac{3}{4}$ " x 1 $\frac{1}{2}$ "") with anodized aluminum panel. Complete with all parts, battery and easy-to-follow instructions. Shpg. wt., 1 lb.

Model S-239. Code Practice Oscillator Kit .... **\$4.95**

**FAMOUS knight-kits FOR HOBBYISTS...**  
EASY-TO-BUILD... FEATURING EXCEPTIONAL PERFORMANCE AT LOW COST



Model S-243


**\$13<sup>95</sup>**

**knight-kit  
"SPACE SPANNER"  
BAND SWITCHING  
RECEIVER SET**

**DUAL BAND FOR THRILLING  
SHORT WAVE & BROADCAST**

All-new 2-band receiver in easy-to-build kit form at a very low price. Pulls in thrilling short-wave (6 to 17 mc) and standard broadcast, plus amateur, aircraft, police and marine radio. Features special regenerative circuit; highly sensitive on broadcast band. Band-switch selects broadcast or short wave. Has 4" PM speaker and beam-power output tube for plenty of volume; headphone connectors for weak signal listening; slide switch cuts out 35W4 rectifier. Six controls; Bandsread; Main Tuning; Antenna Trimmer; Bandwidth; Regeneration; Audio Gain. Panel finished in attractive gray with black knobs. Includes all parts, punched chassis and tubes. 7 x 10 $\frac{1}{2}$  x 6"; for 110-120 v. 50-60 cycles AC or DC. Shpg. wt., 4 $\frac{1}{2}$  lbs.

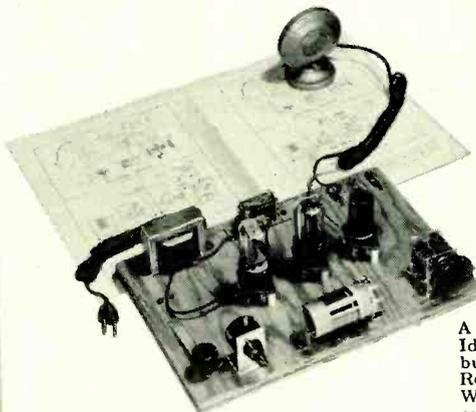Model S-243. "Space Spanner" Receiver Kit. Net. .... **\$13.95**



Model S-265

**\$12<sup>45</sup>**

**knight-kit  
10-IN-1  
LAB KIT**

**BUILD ANY OF  
10 FASCINATING  
ELECTRONIC PROJECTS**

A wonderfully instructive electronics kit. Ideal for experimenters, beginners—fun to build. Construct a sensitive Broadcast Receiver; Amplifier (for phono or mike); Wireless Phono Oscillator; Home "Broadcast Station"; Code Practice Oscillator; Capacity-Operated Relay, or any one of four other fascinating projects. Low voltages; safe to build and operate. Only tools needed are soldering iron, screwdriver and pliers. Perfect for self-instruction in circuit fundamentals, and packed with practical applications. Kit includes mounting board, tubes, all parts, hardware, microphone, and 12-page builders' manual. For 110-120 v., 50-60 cycle AC. Shpg. wt., 10 lbs.

Model S-265. "10-in-1" Kit. Net. .... **\$12.45**

Model P-003. Phototube for Photo Relay Project. Net. .... **\$2.00**

Model H-024. 4-Prong Socket for Phototube. Net. .... **8¢**



Model S-735

**\$14<sup>85</sup>**

**knight-kit  
"RANGER II"  
SUPERHET RADIO KIT**

Thousands have built and enjoyed the "Ranger" Broadcast Band Receiver. Carefully engineered for easy construction and powerful, sensitive performance. Latest Superhet circuit; tunes 540 to 1680 kc; covers entire broadcast band and exciting police calls. Features automatic volume control, built-in pre-formed loop antenna, ball-bearing tuning condenser. Develops excellent tone quality from Alnico V PM dynamic speaker. Supplied with following tubes: 12SK7GT IF amp.; 12SQ7GT det.-AVC- audio; 50L6GT audio output; 35Z5GT rect. Complete with handsome brown plastic cabinet, tubes, speaker, all parts, and instruction manual. For 110-120 v., 50-60 cycle AC or DC. Shpg. wt., 8 lbs.

Model S-735. "Ranger II" Superhet Radio Kit. Net. .... **\$14.85**

Receiver Kits Supplied Less Wire and Solder

Order from **ALLIED RADIO** 100 N. WESTERN AVE., CHICAGO 80, ILL.

# Top Quality Electronic Equipment in Kit Form

**SAVE MORE  
BUY DIRECT**

**FASCINATING, INSTRUCTIVE**  
USED BY MANY LEADING TRAINING SCHOOLS



**knight-kit**  
**"OCEAN HOPPER" RECEIVER KIT**

Model S-740 **BROADCAST, LONG WAVE & SHORT WAVE RECEPTION**

**\$10<sup>75</sup>**

The famous "Ocean Hopper" receiver kit—sensationally low-priced—tops for enjoyable broadcast, long wave and short wave reception. Highly sensitive regenerative-type circuit. Excellent head-phone reception; can be used with 3-4 ohm PM speaker on strong broadcast band stations. Supplied with plug-in coil for standard broadcast; covers long wave and popular short wave bands with coils below. Pulls in thrilling foreign broadcasts, police, amateurs and aircraft. Controls: Main Tuning, Bandspread, Antenna Tuning, Off-On-Regeneration. Handsome gray panel, logging type lucite main tuning knob. With all parts, tubes, instructions (less extra coils and headset). AC or DC operation. Shpg. wt., 5 lbs.

Model S-740. "Ocean Hopper" Receiver Kit. Net. **\$10.75**

**EXTRA PLUG-IN COILS**

- S-741. Long Wave, 155-470 kc. Net. .79c
- S-742. Short Wave, 1.65-470 kc. } Net
- S-743. Short Wave, 2.9-7.3 mc. } each .65c
- S-745. Short Wave, 7-17.5 mc. }
- S-744. Short Wave, 15.5-35 mc. }



**knight-kit**  
**TRANSISTOR RADIO KIT**  
**PRINTED WIRING—WORKS FROM FLASHLIGHT CELL**

Model S-765  
**\$3<sup>95</sup>**

Experiment with the marvel of transistors in this new transistorized, printed-circuit radio. No tubes—no crystal! Small enough to fit in the palm of the hand—yet it provides powerful reception over the complete AM broadcast band. Transistor provides extra audio power for loud, clear reception. Operates from single flashlight cell. Designed for use with headphones. Printed circuit eliminates wiring—just assemble and solder a few connections—that's all there is to it! Supplied complete with all parts, hardware, battery, and easy-to-follow instructions. Less antenna and headphone (use 3000 ohms or higher). Shpg. wt., 8 oz.

S-765. Transistor Radio Kit. Net. **\$3.95**

**RECEIVER KIT ACCESSORIES**

- 2000 Ohms Headset. Dual headset for use with "Space Spanner", "Ocean Hopper" and "10-in-1 Lab" Kits. J-110. Net. **\$1.79**
- 5000 Ohms Headset. Dual headset for Transistor Radio Kit. J-126. Net. **\$3.38**
- Antenna Kit. For use with all Knight-Kit receiver kits. C-100. Net. **\$1.05**

**ALL PRICES NET F. O. B. CHICAGO**

**BUILD-YOUR-OWN  
HIGH FIDELITY knight-kits**

**knight-kit**  
**BASIC 25 WATT  
ULTRALINEAR  
HI-FI AMPLIFIER KIT**

Model S-755

**\$41<sup>50</sup>**

**TOP CUSTOM QUALITY—  
ETCHED CIRCUIT WIRING**



This new super-quality hi-fi basic amplifier is designed to satisfy the most critical listener. Intended for use with tuners incorporating built-in preamp or with separate preamp. Uses latest Williamson type ultralinear circuit with potted, matched transformers. Delivers maximum output of 45 watts. Frequency response:  $\pm 0.5$  db, 10 cps to 120 kc, measured at 20 watts. Harmonic distortion is only .15% right up to 30 watts. IM distortion is only .27% at 10 watts and only 1% at 20 watts, using 60 cps to 7 kc, 1:4 ratio. Hum level is — 85 db below full rated output. Output impedance, 4, 8, 16 ohms. Input voltage for 25 watt output is 1.8 volts. Uses two 12AU7's, two 5881's, and a 5V4. Etched circuit is utilized in voltage amplifier and phase inverter stages. Has output tube balancing control, variable damping control, and on-off switch. Handsome chrome-plated chassis, 14" x 9" x 2". Overall height, 7". A deluxe true hi-fi amplifier in every detail—satisfying to build—equal in performance to amplifiers selling at over twice the price. Complete with all parts, tubes and construction manual. Shpg. wt., 27 lbs.

Model S-755. Basic 25 watt Hi-Fi Ultralinear Amplifier Kit. Net. **\$41.50**



**knight-kit**  
**10 WATT HI-FI AMPLIFIER KIT**

Model S-234  
**\$20<sup>95</sup>**

Famous for wide response and smooth reproduction at low cost. Only 0.5 volt drives amplifier to full output. Frequency response:  $\pm 1$  db, 30-20,000 cps at 10 watts. Harmonic distortion less than 0.5% at 10 watts. Intermod. distortion less than 1.5% at full output. Controls: on-off-volume, bass, treble. Input for crystal phono or tuner. Chassis punched to accommodate preamp kit. Matches 8 ohm speakers. Shpg. wt., 14 lbs.

Model S-234. Amplifier Kit. Net. **\$20.95**  
Model S-235. Preamp Kit for above. Net. **\$2.75**



**knight-kit**  
**20 WATT HI-FI AMPLIFIER KIT**

Model S-750  
**\$34<sup>75</sup>**

True hi-fi for less! Frequency response,  $\pm 1$  db, 20 to 20,000 cps at 20 watts. Distortion, 1% at 20 watts. Hum and noise level: tuner input, 90 db below 20 watts; phono, 72 db below 20 watts. Sensitivity: tuner input, 0.6 volt for 20 watts output; magnetic phono, .007 volts. 4 inputs: magnetic phono, microphone, crystal phono or recorder, and tuner. Controls: Bass, Treble, Volume, Selector. With compensation positions for 78 and LP records, controlled from front panel. 23 lbs.

Model S-750. 20-Watt Hi-Fi Amplifier Kit. Net. **\$34.75**

Amplifier Kits Supplied Less Wire and Solder

## ALLIED RADIO

*Everything in Electronics from One Reliable Source*

Allied Radio Corp., Dept. 2-A-6, 100 N. Western Ave., Chicago 80, Ill.

Ship me the following KNIGHT-KITS:

Quantity	Description	Model No.	Price

\$ . . . . . enclosed. For parcel post include postage (express is shipped collect).


Name \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**ORDER TODAY** →

## TEST INSTRUMENTS

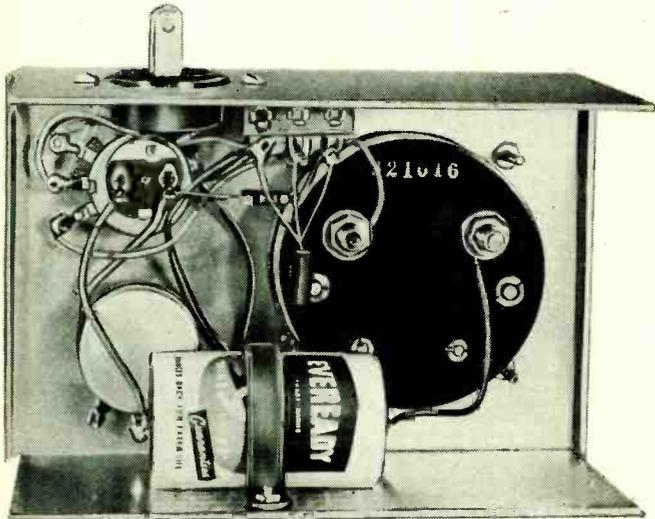

Underchassis view of the meter unit.

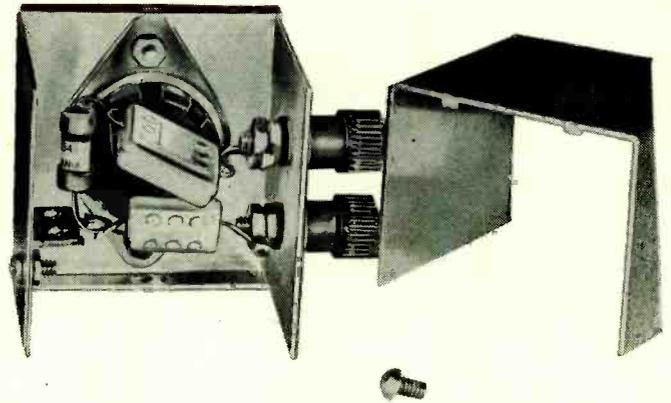

Underchassis view of the pickup box.

operate as soon as the on-off switch is closed. This makes the instrument as easy to use as a nonelectronic meter.

Temperature changes which reach the interior of the transistor will cause the no-signal meter current to change. Heat increases the current. The no-signal transistor collector current (initially about 10 microamperes) doubles approximately for each 18°F increase in temperature. This means that the meter must be reset to zero as the ambient temperature grows hotter or colder. However, the drift is not severe in normal field service and occasional resetting to zero is no more of a nuisance than the periodic readjustment of an ohmmeter. Furthermore, should the technician choose not to reset the meter, an initial deflection slightly off zero will not detract from the usefulness of the compass. For these reasons, the circuit has not been complicated nor its power drain increased by including temperature-compensating gimmicks.

The diode pickup circuit (pickup box) is connected to the output of the receiver video channel by connecting the lower clip (see diagram) to receiver ground and the upper clip to the picture-tube grid or cathode, which-

ever element receives the signal. If a sharp-pointed upper clip is used, the point will puncture the insulation of the video lead, obviating the need to clip to the picture-tube socket. Some of the modern, series-heater TV receivers operate with a hot chassis; that is, the chassis is connected *directly* to one side of the power line. Unless an isolating transformer is used when checking these receivers with any type of instrument used outdoors, the operator must exercise more than ordinary caution to protect himself from dangerous 60-cycle electric shock. *The two instrument boxes are not connected to any part of the circuitry.* The instrument and receiver are switched into operation and the antenna is positioned and rotated for maximum deflection of

the meter. When signal pickup is sufficient to slam the pointer, reduce the sensitivity with R2.

### Construction

The photos show details of construction. The circuit is not critical and the layout is flexible; other arrangements therefore can be used, if desired. A technician might, for example, prefer to build his instrument in a handle-type meter case.

The pickup section is built in an aluminum box 2 x 2 x 1½ inches. Two insulated binding posts (see photos) receive the clip leads from the TV set. A two-prong male plug is mounted in the top of this box for plug-in connection to the outgoing line.


The transistor in the meter box is mounted by soldering its three pigtails (each cut to a length of ¾ inch) to the terminals of a three-lug, insulated terminal strip (see photo). When soldering the transistor and diode leads, hold each lead with pliers to remove the heat. The flashlight cell is held to the bottom of the box with a short strap. Leads are soldered directly to this cell, since replacement is infrequent.

When wiring the instrument, observe carefully the polarities of the diode, transistor, meter and battery. Connect each of these components exactly as shown in the diagram. The two male plugs are polarized; that is, each has one large and one small prong. This prevents plugging in the interconnecting line in the wrong direction.

As much as 150 feet of lamp cord, 300-ohm ribbon or flexible coaxial line have been used successfully with this type of instrument. And there seems no reason why the compass will not operate with longer lines. **END**
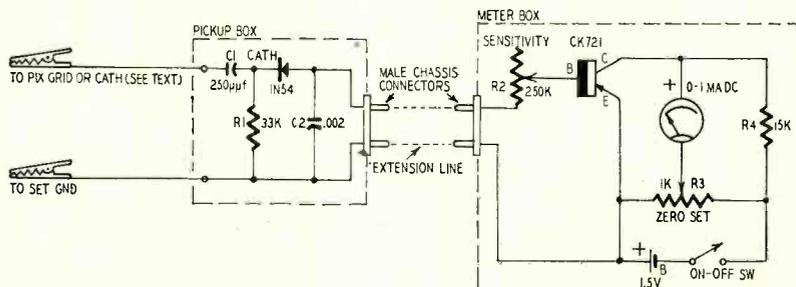
### Parts for TV compass

1—15,000, 1—33,000 ohms, ½ watt, resistors; 1—1,000-ohm potentiometer, wirewound; 1—250,000-ohm potentiometer with switch; 1—250 μmf, 1—0.002 μf, mica capacitors; 1—size-D flashlight cell; 1—0-1-ma d.c. meter (Triplet 327T or equivalent); 2—2-pole male plugs, polarized (Amphenol 61-MPI or equivalent); 2—2-pole female receptacles, polarized (Amphenol 61-MIP-61F or equivalent); 1—CK721 transistor; 1—1N54 germanium diode; 2—knobs; 1—1-lug, 1—3-lug, insulated terminal strips; 2—binding posts; 1—2 x 2 x 1½-inch aluminum box; 1—6 x 4 x 3-inch aluminum box.



Schematic diagram of the transistorized television antenna compass.



# If you're willing to lose your job tomorrow to a technically-trained man, don't read this, mister

But, if you're interested in an honest-to-goodness career in the vigorous young electronics industry, here's how you can step ahead of competition, move up to a better job, earn more money, and be sure of holding your technical job even if the brass is firing instead of hiring.

The "how" is CREI training in radio-television-electronics. You don't have to be a college graduate. You *do* have to be willing to study—at home. You can do it while holding down a full-time job. Thousands have. However, you must have some prior electronic experience, either in military service, professional employment, experimenting, or ham operating. Since 1927 CREI has provided alert young men with the technical knowledge that leads to more responsibility, more job security, more money. More than a quarter century of experience qualifies CREI to train you.

What qualifies *you* for CREI? If you have a high school education, you're off to a good start. If you have a knack for math, so much the better. If you are currently working in some phase of the electronics industry, you'll get going faster. But remember this: CREI starts with fundamentals and takes you along at your own speed. You are not held back by a class, not pushed to keep up with others who have more experience or education. You set your own pace. Your CREI instructors guide you through the lesson material and *grade* your written work personally. You master the fundamentals, then get into more advanced phases of electronics engineering principles and practice. Finally you may elect training at career level in highly specialized applications of radio or television engineering or aeronautical radio.

How good is CREI training? Here are a few ways to judge. Ask an electronics engineer, if you know one.

Ask a high-school or college physics teacher. Ask a radio station engineer. Check up on our professional reputation: CREI home study courses are accredited by the Engineers' Council for Professional Development; CREI is an approved member of the National Council of Technical Schools. Ask personnel managers how they regard a man with a CREI "ticket." Look at this partial listing of organizations *that pay CREI* to train their own personnel: All American Cables & Radio, Inc., Canadian Aviation Electronics, Ltd., Canadian Broadcasting Corporation, Columbia Broadcasting System, Hoffman Radio Corp., Machlett Labs., Glenn L. Martin Co., Magnavox Co., Pan American Airways, Atlantic Division, Radio Corporation of America, United Air Lines. Finally, ask a CREI graduate to tell you about our Placement Bureau, which currently has on file more requests for trained men than we can fill.

What's the next step? The logical one is to get more information than we can cram into one page. The coupon below, properly filled out, will bring you a fact-packed booklet called "Your Future in the New World of Electronics." It includes outlines of courses offered, a resume of career opportunities, full details about the school, and tuition details. It's free.

## MAIL THIS POSTAGE-FREE POSTCARD TODAY

### CAPITOL RADIO ENGINEERING INSTITUTE

Accredited Technical Institute Curricula

Dept. 141-C

3224 16th St., N.W., Washington 10, D. C.

(R. N. Feb. 55)

**IA**

Please send me your course outline and FREE Illustrated Booklet "Your Future in the New World of Electronics" . . . describing opportunities and CREI home study courses in Practical Electronics Engineering.

- CHECK FIELD OF GREATEST INTEREST
- Practical Radio Electronics Engineering
  - Broadcast Radio Engineering (AM, FM, TV)
  - Practical Television Engineering
  - Practical Aeronautical Electronics Engineering

Name \_\_\_\_\_ Age \_\_\_\_\_

Street \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Check:  Home Study  Residence School  Korean Veteran

To help us answer your request intelligently, please give the following information:

EMPLOYED BY \_\_\_\_\_

TYPE OF PRESENT WORK \_\_\_\_\_

SCHOOL BACKGROUND \_\_\_\_\_

ELECTRONICS EXPERIENCE \_\_\_\_\_

IN WHAT BRANCH OF ELECTRONICS ARE YOU MOST INTERESTED? \_\_\_\_\_

# CREI prepares you quickly for success in

**The future is in your hands!**

The signs are plain as to the future of the trained men in the electronics industry. It is a tremendous industry, and—at the *present time* there are more jobs than there are trained men to fill them. But—when there's a choice between a trained and untrained applicant, the trained man will get the job. Your biggest problem is to decide on—and begin the best possible training program.

## CREI Home Study . . . The Quick Way to Get There.




Since 1927, CREI has given thousands of ambitious young men the technical knowledge that leads to more money and security. The time-tested CREI procedure can help you, too—if you really want to be helped. CREI lessons are prepared by experts in easy-to-understand form. There is a course of instruction geared to the field in which you want to specialize. You study at *your* convenience, at *your* rate of speed. Your CREI instructors guide you carefully through the material, and grade your written work personally (not by machine).
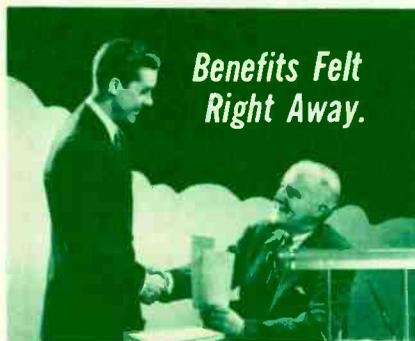
## Industry Recognizes CREI Training.

CREI courses are prepared, and taught with an eye to the needs and demands of

industry, so your CREI diploma can open many doors for you. Countless CREI graduates now enjoy important, good-paying positions with America's most important companies. Many famous organizations have arranged CREI group training for their radio-electronics-television personnel. To name a few: All America Cables and Radio, Inc.; Canadian Aviation Electronics, Ltd.; Canadian Broadcasting Corporation; Columbia Broadcasting System; Canadian Marconi Company; Hoffman Radio Corporation; Machlett Laboratories; Glenn L. Martin Company; Magnavox Company; Pan American Airways, Atlantic Division; Radio Corporation of America; Technical Appliance Corporation; Trans-Canada Air Lines; United Air Lines. Their choice for training of their own personnel is a good cue for *your* choice of a school.



**Benefits Felt  
Right Away.**

- BROADCASTING
- TELEVISION
- MANUFACTURING
- COMMUNICATIONS
- SERVICING
- AERONAUTICAL ELECTRONICS

Almost immediately you feel the benefits of CREI training. Your employer, when informed of your step toward advancement (only at your request), is certain to take new interest in you and in your future. What you learn in CREI Home Study can start helping you do a better job immediately.



## CREI also offers Resident Instruction

at the same high technical level—day or night, in Washington, D. C. New classes start once a month. If this instruction meets your requirements, check the coupon for Residence School catalog.

**PAYS FOR ITSELF QUICKLY.** Your very first raise could repay your investment in CREI training, and leave you a profit the very first year. Your increases in pay thereafter are all pure profit, and you'll be prepared for many more promotions and pay raises in the future years of your life.

## KOREAN WAR VETERANS

If you were discharged after June 27, 1950, let the new G.I. Bill of Rights help you obtain resident instruction. Check the coupon for full information.



**Get this fact-packed  
booklet. It's free.**

Called "Your Future in the New World of Electronics," this free illustrated booklet gives you the latest picture of the growth and future of the gigantic electronics world. It includes a complete outline of the courses CREI offers together with all the facts you need to judge and compare. Take 2 minutes to send for this booklet right now. We'll promptly send your copy. The rest—your future—is up to you.

1st Class

Permit No. 288-R

Sec. 34.9 P.L.R.

Washington, D. C.

### BUSINESS REPLY CARD

No Postage Stamp Necessary If Mailed in United States

3c Postage Will Be Paid By

**CAPITOL RADIO ENGINEERING INSTITUTE**

**3224 16th Street, N.W.**

**Washington 10, D. C.**

# FOR GOLDEN EARS ONLY

*The Pilot AF-850 AM-FM tuner;  
Pilot AA-904 audio amplifier;  
H. H. Scott 710 stroboscopic  
turntable*

By MONITOR

ONCE in a while one runs into a piece of equipment so unobtrusive about its virtues that one is inclined to underrate it. The Pilot AF-850, top tuner in the Pilot line, is an example. Its circuit is not only conventional but rather conservative, with the normal pentode r.f. stage and converter, two i.f. stages, two limiters, Foster-Seeley discriminator and a twin-triode type of reactance automatic frequency control. Its performance is steady, solid and completely uncritical. Casual use might well lead one to dismiss it as unremarkable. In actual fact, only two or three tuners surpass it in any single characteristic and I know of none which surpasses it in the net total of virtues and absence of vices.

Sensitivity of the FM section is close to the top category. Pilot's claim of 1.5  $\mu\text{v}$  for 20 db and 5  $\mu\text{v}$  for 40 db quieting appears to be realized. Two or three of the top tuners I have used had somewhat better sensitivity. In my location the AF-850 brought in all but one of the FM stations regularly receivable. This was done with complete limiting with my regular test antenna. The one exception could be received enjoyably with my horn antenna which has higher gain. For local use there is a built-in power-line "antenna." A folded-dipole ribbon-lead antenna is also included in the package.

The AF-850 shines with a unique brightness in ease of tuning and stability. It is remarkably free of drift — by far the best tuner in this respect I have ever used. The a.f.c. is continuously

and smoothly variable with a knob on the panel and in its maximum position appears to provide a tuning leeway of  $\pm 150$  kc or so. The tuning knob is especially pleasurable to use. The choice of ratio and the flywheel loading provide a smooth control which reminds me of the knob on a fine safe. Selectivity is excellent. Unless the station on the adjacent channel is extremely strong, there is no difficulty bringing in adjacent-channel stations. My family agrees that the AF-850 is the easiest FM tuner for unskilled hands of any we have had.

The sensitivity of 2  $\mu\text{v}$  on the broadcast band is just about tops in tuners and few communications receivers will surpass it. In most locations the built-in ferro-loopstick antenna will prove adequate. Two bandwidths are provided

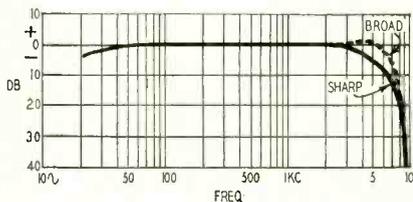


Fig. 1—Diagram shows response of the AM section at 1 mc—10% modulation.

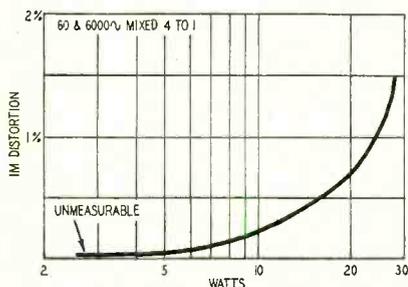


Fig. 2—Pilot AA-904 distortion curve.

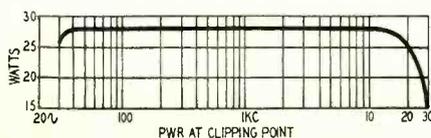


Fig. 3—Pilot AA-904 power curve.

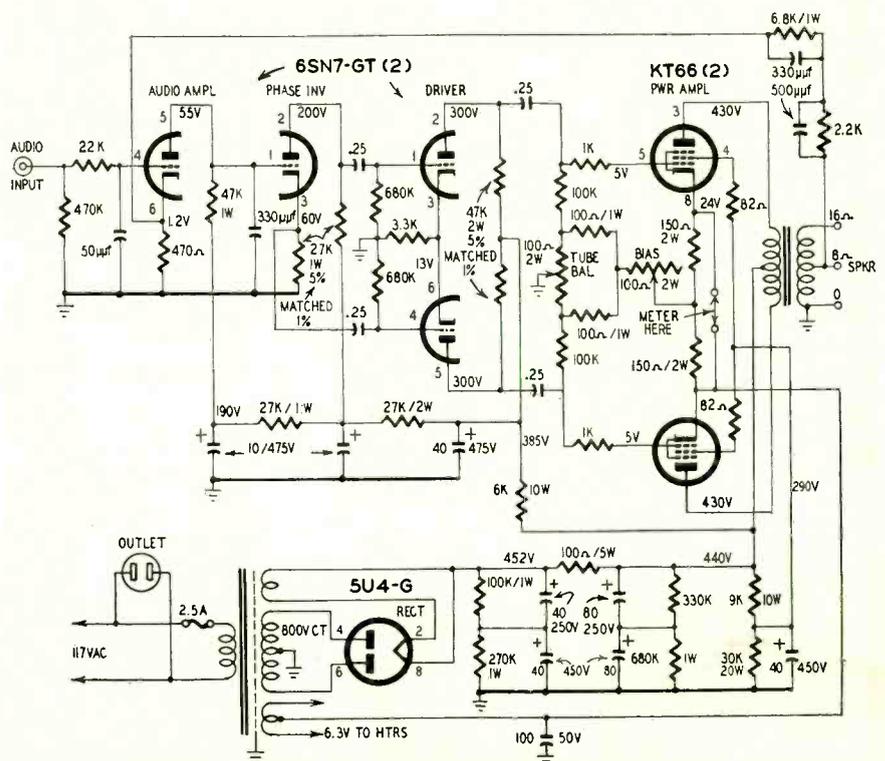


Fig. 4—Schematic of Pilotone AA-904 high-fidelity audio amplifier.

## AUDIO—HIGH FIDELITY

in the two-stage i.f. amplifier. The narrow or sharp bandwidth is about 8 or 9 kc wide at 6 db down, the broad about 15 kc wide. The loss at high frequencies in both positions is largely equalized by a network ahead of the whistle filter which in turn is very sharp and has little skirt effect beyond 10 kc. The response curves I obtained (Fig. 1) in both the sharp and broad positions agree with the manufacturer's curve within 1 or 2 db. The smooth tuning control and the meter make it very easy to tune for best fidelity and least interference.

The AF-850 provides three 500,000-ohm audio inputs: PHONO, TAPE and AUX. These work into a half section of a 12AU7 amplifier and only 150 mv of input is required for full rated output. The 1.5 to 2 volts required to drive most amplifiers to full output is obtainable with very low distortion, though the tuner can provide as much as 10 volts of output on the radio positions. The signal source in use is plainly indicated. The two radio dials are lighted independently and only the one in use is illuminated. The three audio channels have red pilot lights above the dial scales so they are also clearly indicated. The output is from a cathode follower, and hum level is inaudible. The tuner is compact (14½ inches wide, 7½ inches high and 9 inches deep) and has an excellent appearance worthy of its quality and price. For those who like to have a control unit combined with the tuner Pilot offers the AF-860, identical except for the addition of preamplifier, equalizer and tone controls.

### Pilot model AA-90 amplifier

Pentode and tetrode operation of power output tubes has been in dispute among high-fidelity experts for a generation. Even after feedback made it possible to reduce the internal resistance of pentode amplifiers to a point comparable with that of triodes and providing acceptable damping factors, many authorities continue to look askance at this more efficient mode of operation. Lately this prejudice has been suffering considerable erosion but it is still prevalent. For those who cherish it the curves of Figs. 2 and 3, which summarize the performance of the Pilot AA-904 amplifier (see photo),

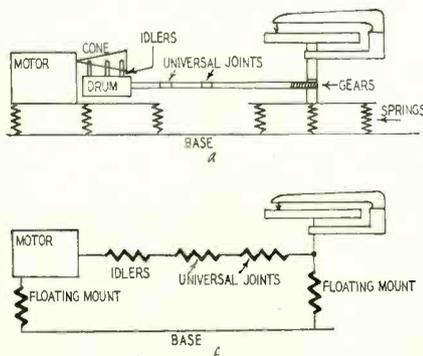


Fig. 5—Diagrams show the Scott turntable layout and equivalent circuit.

especially the IM distortion curve, will no doubt be a shock. The distortion of the specimen tested was so low that below 7 watts it was necessary to subtract the residual reading of my Heathkit AA-1 audio analyzer to obtain any measure at all. Though I do not claim any great accuracy below that point the curve could be 100% off and still be remarkable. As near as I could measure it the distortion was about .02% at the 5-watt level and less than .01% below 2 watts. The manufacturer avers this distortion curve is representative of production runs.

The other characteristics require no apologies either. About 24 db of feedback is applied in a single loop but this has been so well controlled that nothing short of .05  $\mu$ f or reactive load will set it off into oscillation. Below that and with no load it is fully and entirely stable. The power curve (Fig. 3) is down about 1 db at 20 and 20,000 cycles, though it slopes more severely beyond. The damping factor is 6, an excellent value for today's high-fidelity speakers which do not require as heavy damping as older models did.


The circuit (Fig. 4) is a conventional Williamson except in the use of pentode connection of the output tubes. Special care, however, is taken to maintain balance in all push-pull stages by using 1% resistors. Also, a simple and convenient means is provided for balancing the output stage and biasing it. Behind an easily removable escutcheon on the chassis there is a terminal board with two screws connected with a wire link. Removing the link opens the two cathodes, and a voltmeter attached to the two terminals can be used to obtain the zero-voltage-difference reading which indicates perfect balance. When the link is replaced, the same voltmeter applied to either terminal and ground will read the bias, which should be 24 volts. There are two phase-correcting networks in series in the feedback loop and two bypass networks within the amplifier to control high-frequency response. The reasons for the low distortion are: higher than usual feedback factor; since pentode operation requires less drive (24 volts instead of about 38), the drivers are not driven so hard; the bias and balance of the output tubes can be adjusted for lowest distortion with a given pair. If there is, between the sound of this pentode version and an Ultra-Linear or triode version of the Williamson, any difference which can be ascribed to the pentode operation, it is beyond the ability of my ears to perceive.

### H. H. Scott stroboscopic turntable

The H. H. Scott 710 turntable (see photo) was obviously aimed at the closest approximation of the ideal of turntable performance rather than merely to match current standards. Ideals are not approximated for peanuts and at \$130 (approximate audiophile net) the Scott will dig a noticeable hole in the best-furnished wallet.



The H. H. Scott type 710 turntable.

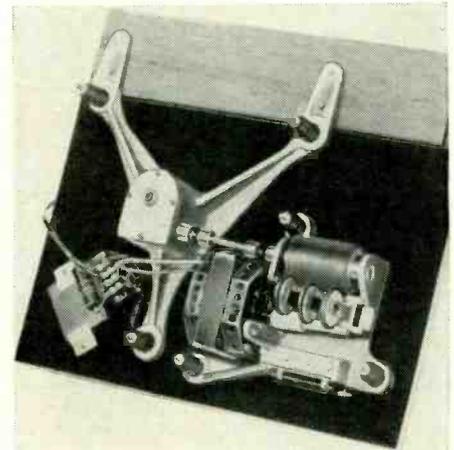

Underside of the Scott 710 turntable.



The model AA-904 Pilotone amplifier.

The big villain of turntable performance is rumble. And the better the system otherwise, the greater the price in quality and satisfaction this rude villain exacts. The 710 will not dispose of the rumble problem completely. Unfortunately, there is another turntable involved in every disc recording, that of the cutting lathe, and unfortunately few if any cutting lathes dispose of rumble as thoroughly as does the Scott. Still, with most of today's recordings you will have to own a speaker system really flat to 30 cycles or lower and add considerable loudness control or bass boosting to hear any rumble at all. Even then you'll have to operate at an uncomfortably high volume level.

A second and, to a critical musical ear, equally annoying villain is wow. Scott claims a figure of 0.1% for both wow and flutter combined and again I cannot quarrel. The Scott seems better in this respect than the best tape recorder I have used and yields as steady a pitch, even with piano music, as I have heard.


**ALLIANCE TENNA·ROTOR**  
*beats the biggest drum!*

**30,000,000**  
**TV VIEWERS**  
*week after week*



New

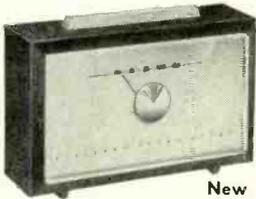**MODEL U-98** — fully automatic — incorporates 32 distinct improvements — eliminates all arcing and consequent picture distortion — points directly, positively, instantly to target station — "just set it and forget it"! . . . . . List Price, **\$39.95**



New

**MODEL T-12** — fingertip electrical operation. Rocker switch on top controls turning. Has direction indicator dial. Compact and smartly styled. Highly accurate! . . . . . List Price, **\$29.95**

**You can't miss with the "leader"!**


Seven years of continuous TV advertising pays off!

Millions know about Alliance . . . more users have Alliance Tenna-Rotor.

Millions of sales impressions in hundreds of TV markets week after week—year after year—give you the solid backing that no other TV accessory has even approached!

The **ALLIANCE Manufacturing Company, Inc.**, Alliance, Ohio

**Another Outstanding Profit-Maker!**

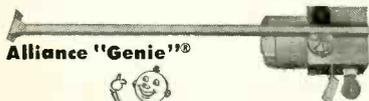

Alliance "Genie"™

**LIFT-A-DOR**  
 GARAGE DOOR OPERATOR

Radio-controlled (from car dash) automatic garage door operator—opens, closes, locks door, turns lights on and off. Factory-assembled for easy installation. Customers gleam when you tell them the low price! Models from **\$69.95** up.

**alliance**  
**TENNA·ROTOR**  
 (TV ANTENNA ROTATOR)

Of this  
you can be sure...

*there is no finer*

**Record  
Changer  
than the**

**Collaro  
RC-54**

*Automatic Intermix*

- + Supplied with pre-cut Mounting Board, Power Cord and Audio Cable.
- + Automatically Intermixes All Size Records without Presetting.
- + Rapid, 7-second Change-over Cycles ... and other outstanding features.



You can SEE it at your Sound Dealer.  
You can READ about it in our Folder.

*Mail This Coupon Today*

**ROCKBAR CORPORATION, Dept. WA-16**  
215 East 37th St., New York 16, N. Y.

*Please send Literature describing the  
Collaro RC-54 Record Changer.*

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

## AUDIO—HIGH FIDELITY

A somewhat related problem is that of synchronizing the speed of the playback turntable with the speed of the recording lathe and thus achieving the identical pitch used by the instruments or orchestra at the time of recording. The Scott deals with this problem as completely as I imagine it can be dealt with. A built-in stroboscope operates at all three standard speeds (33, 45 and 78 r.p.m.) making it possible to see to what degree these standard speeds are attained and maintained.

The stroboscope operates constantly, requires no special lighting or skill or knowledge to interpret, provides clear and positive information. There are adjustments to vary the speed either to correct for the error produced by differences in line voltage or loading of the turntable by the pickup or to change the pitch so that, for example, recordings played with instruments tuned to the Continental pitch will be in tune with ones tuned to the American pitch. The variation possible is  $\pm 5\%$  which amounts to just about a whole tone at 33 r.p.m. and even permits transposing to the next lower or higher key.

Each of the three speeds is adjusted individually by a separate knob without affecting the speed of the other two. The adjustment can be made any time without interfering with turntable performance. Thus, it is not only possible to obtain precise synchronization with the three standard speeds but also to make corrections in playback for small errors in the synchronization of cutting lathe with tape recorder and even to permit changing the pitch to suit one's own ear.

I was not aware of any hum problems with the Scott and experienced no difficulty even with such very-low-level cartridges as the Fairchild (without transformer) or the Electro-Sonic, Angel or even the Ferranti.

There are some additional fine points. The turntable is aluminum, so there is no magnetic pull even on cartridges with large and powerful magnets like the Angel. The pickup mounting board, as well as the turntable base, are large enough to accommodate the long transcription type arms and to permit a choice of orientation with the short home type arms.

Choice of operating speeds is positive and simple. There are four pushbuttons, one for each of the three speeds and the fourth for stop. Pushing any of the three starts the turntable revolving at the desired speed. Pushing the stop button stops the turntable and returns the depressed pushbutton to neutral. There is a slip-clutch between turntable and drive so records can be cued or placed and removed without stopping the turntable.

The performance of the Scott is achieved by a radically novel design (Fig. 5-a). The problem so far as rumble is concerned is to isolate the vibration of the motor from the turntable and pickup. In the Scott the system is divided into two entirely inde-


pendent sections: the motor and speed converter, the turntable and pickup. Each section is floated separately and independently with a combination of steel springs and sponge rubber. Thus, so far as the vibration is concerned, there are two floating mounts in series instead of the usual one. The turntable is gear-driven but the coupling between the gears and the motor is flexible and highly damped instead of solid and fixed. Two rubber or rubberlike universal joints in the drive shaft transmit the torque but tend to absorb the vibration. Furthermore, between this drive shaft and the motor itself idlers with rubber rims also absorb vibration. If we represent the damping elements by resistances, we get the equivalent diagram of Fig. 5-b with five damping elements in the loop.

Another interesting feature is that the pickup mounting board is rigidly mounted to the turntable frame but floats with it on the turntable mount. This is mechanically identical to using a common ground in an audio circuit — places the pickup at the same vibration potential, as it were, as the turntable. It has the incidental benefit of providing isolation of both turntable and pickup from shock transmitted to the base by footsteps, passing trucks or vibration from a speaker, and thus minimizes the thumps, bumps, skipping and jumping due to shock as well as acoustic feedback from the loudspeakers.


The drive system is equally novel. The motor drives a long narrow cone. The drive shaft from the turntable terminates in a drum of the same length as the cone and parallel to it in axis. The three idlers are exactly the same size but are placed between cone and drum so that one engages the cone at its larger diameter, another at its smaller diameter and the third in between. This forms a planetary transmission or, rather, three independent planetary transmissions. Obviously the speed of each idler will be proportional to the diameter of the portion of the cone that it engages. There is a linkage to move each idler a fraction of an inch along its portion of the cone and this movement provides the variation of speed.

At this point the two rubber universal joints perform another service, that of torque damping. The initial starting torque of the motor against the load of turntable puts a twist in the joints; once speed is attained and the turntable acquires momentum the twist is relaxed to a state of normal tension or torsion. However, any sudden increase or decrease in torque will be resisted by the torsion of the rubber and the back torque of the turntable which also loads the universal joints. This tends to dampen irregularities in torque and therefore in speed and — with the heavy flywheel effect of the turntable — accounts for the notable wow characteristics and low flutter of the unit. END

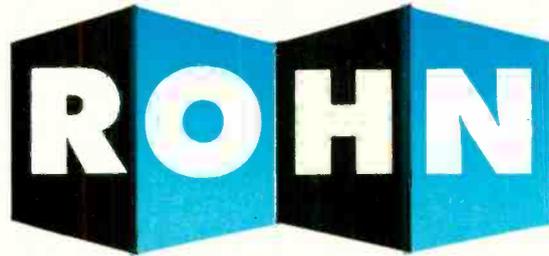these 3 hot dipped galvanized  
towers  
are exclusive with




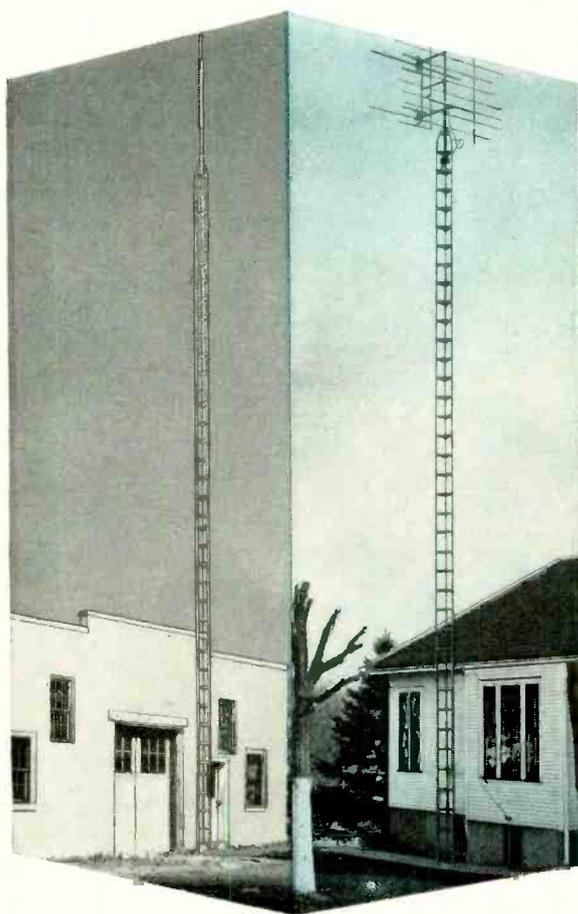*No guying needed to 40—50—or  
60 feet! Guyed heights safely  
up to 200—300 feet!*


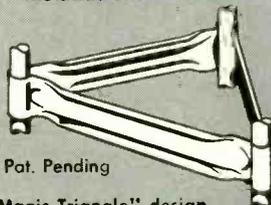
### NO. 6 TOWER

Features unexcelled 12½" equilateral "magic triangle" design with electric welding throughout. Self-supporting to 50', the Rohn No. 6 is ideal for home TV installation.



Pat. Pending

"Magic Triangle" design utilizes mass production machines — means sturdier towers, uniformity and lower costs!

### "PACKAGED" TOWER

Constructed for ease in shipping and storage. A 48' tower comes in six 8' sections bound together in a single 8' x 20" package! Self-supporting and available in 24' to 64' sizes.

and now, a new and completely hot-dipped galvanized, heavy duty

### NO. 40 COMMUNICATIONS TOWER

For extreme heights and communication purposes of all kinds, the Rohn No. 40 gives you strength and durability on which you can depend. The time tested and proven equilateral triangle design using extra heavy duty tubing and corrugated steel cross-bracing is utilized in this new Rohn Tower. The No. 40 is structurally sound so that you can install it for heights up to 300'; and is preferred for lesser heights when considerably greater strength is required because of excessive wind or antenna loading, etc. Check this tower for your requirements of this type. You'll find it just can't be beat, neither structurally nor price-wise!

Note: For lesser heights, use the Rohn No. 20 or No. 30 Tower . . . for experimental operation, use the Rohn "Fold-Over" Tower.

All Rohn Towers are quickly erected- shipped in easy-to-handle sections; and, Rohn-Designed accessories are available with each tower.

Check the complete line of Rohn Towers, including Roof Towers, Masts and Tubing . . . plus a full line of tower and TV installation products such as bases, house mounts, brackets, service tables, guy brackets and rings plus dozens of other items.

**ROHN** Manufacturing Company

116 LIMESTONE, BELLEVUE  
PEORIA, ILLINOIS

#### MAIL THIS COUPON FOR FREE LITERATURE!

Rohn Manufacturing Company  
116 Limestone, Bellevue  
Peoria, Illinois

Gentlemen: Please rush me complete details on the full line of Rohn Towers and Accessories.

Firm \_\_\_\_\_

Name \_\_\_\_\_ Title \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_



# Superior's New Model TC-55 TUBE TESTER

**FOR** The Experimenter or Part-time Serviceman, who has delayed purchasing a higher priced Tube Tester. The Professional Serviceman, who needs an extra Tube Tester for outside calls. The busy TV Service Organization, which needs extra Tube Testers for its field men.

Speedy, yet efficient operation is accomplished by:

1. Simplification of all switching and controls.
2. Elimination of old style sockets used for testing obsolete tubes (26, 27, 57, 59, etc.) and providing sockets and circuits for efficiently testing the new Noval and Sub-Minar types.

You can't insert a tube in wrong socket

It is impossible to insert the tube in the wrong socket when using the new Model TC-55. Separate sockets are used, one for each type of tube base. If the tube fits in the socket it can be tested.

"Free-point" element switching system

The Model TC-55 incorporates a newly designed element selector switch system which reduces the possibility of obsolescence to an absolute minimum. Any pin may be used as a filament pin and the voltage applied between that pin and any other pin, or even the "top-cap"

Checks for shorts and leakages between all elements

The Model TC-55 provides a super sensitive method of checking for shorts and leakages up to 5 Megohms between any and all of the terminals. Continuity between various sections is individually indicated. This is important, es-

pecially in the case of an element terminating at more than one pin. In such cases the element or internal connection often completes a circuit.

Elemental switches are numbered in strict accordance with R.M.A. specification.

One of the most important improvements, we believe, is the fact that the 4 position fast-action snap switches are all numbered in exact accordance with the standard R.M.A. numbering system. Thus, if the element terminating in pin No. 7 of a tube is under test, button No. 7 is used for that test.

The Model TC-55 comes complete with operating instructions and charts. Housed in rugged steel cabinet. Use it on the bench—use it for field calls. A streamlined carrying case, included at no extra charge, accommodates the tester and book of instructions.

**\$26<sup>95</sup>** NET



Superior's new Model TV-11

# TUBE TESTER

★ Tests all tubes including 4, 5, 6, 7, Octal, Lock-in, Peanut, Bantam, Hearing Aid, Thyatron Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity fuse types, etc.

★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TV-11 as any of the pins may be placed in the neutral position when necessary.

EXTRA SERVICE—The Model TV-11 may be used as an extremely sensitive Condenser Leakage Checker. A relaxation type oscillator incorporated in this model will detect leakages even when the frequency is one per minute.

★ The Model TV-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

★ Free-moving built-in roll chart provides complete data for all tubes.

★ Newly designed Line Voltage Control compensates for variation of any Line Voltage between 105 Volts and 130 Volts.

★ NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

The model TV-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover.

**\$47<sup>50</sup>** NET



Superior's New Model TV-12

# TRANS-CONDUCTANCE TUBE TESTER

TESTING TUBES

★ Employs improved TRANS-CONDUCTANCE circuit. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.

★ NEW LINE VOLTAGE ADJUSTING SYSTEM. A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.

★ SAFETY BUTTON—protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.

★ NEWLY DESIGNED FIVE POSITION LEVER SWITCH ASSEMBLY. Permits application of separate voltages as required for both plate and grid of tube under test, resulting in improved Trans-Conductance circuit.

TESTING TRANSISTORS

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only" meter scale.

The Model TV-12 will accommodate all transistors including NPN's, PNP's, Photo and Tetrodes, whether made of Germanium or Silicon, either point contact or junction contact types.

Model TV-12 housed in handsome rugged portable cabinet sells for only

**\$72<sup>50</sup>** NET

**ALSO TESTS TRANSISTORS!**

## ABOUT TESTING PICTURE-TUBES...

Of course you can buy an "adapter" which theoretically will convert your standard Tube Tester into a picture-tube tester. Sounds fine—but—it simply doesn't work out that way!

We do not make nor do we recommend use of C.R.T. adapters because a Cathode Ray Tube is a very complex device and to properly test it, you need an instrument designed exclusively to test C. R. Tubes and nothing else. As compared to a makeshift adapter, which sells for about five dollars, our Model TV-40 C.R.T. Tube Tester sells for \$15.85. But, if you believe

that Television is here to stay, then you must agree that the difference in price is more than justified by the many years of valuable service you will get out of this indispensable instrument.

Incidentally, the Model TV-40 is the ONLY low-priced C.R.T. Tube Tester, which includes a real meter. Neons are fine for gadgets and electro-line testers, but there is no substitute for a meter with an honest-to-goodness emission reading scale.



Superior's New Model TV-40

# C. R. T. TUBE TESTER

Tests ALL magnetically deflected tubes... in the set... out of the set... in the carton!!

- Tests all magnetically deflected picture tubes from 7 inch to 30 inch types.
- Tests for quality by the well established emission method. All readings on "Good-Bad" scale.
- Tests for inter-element shorts and leakages up to 5 megohms.
- Test for open elements.

EASY TO USE: Simply insert line cord into any 110 volt A.C. outlet, then attach tester socket to tube base (Ion trap need not be on tube). Throw switch up for quality test... read direct on Good-Bad scale. Throw switch down for all leakage tests.

Model TV-40 C.R.T. Tube Tester comes absolutely complete—nothing else to buy. Housed in round cornered, molded bakelite case. Only

**\$15<sup>85</sup>** NET


**EXAMINE BEFORE YOU BUY!**

**USE APPROVAL FORM ON NEXT PAGE**

Superior's new  
Model 670-A
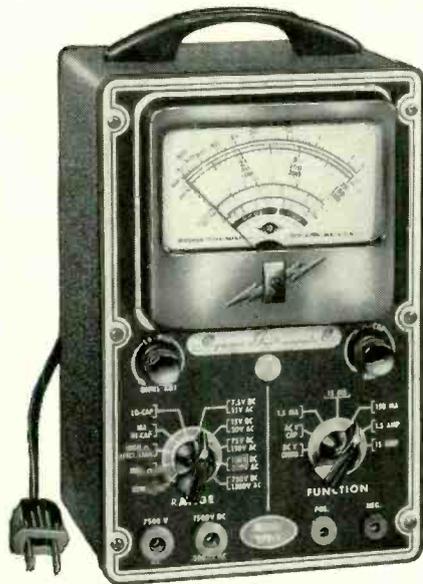
# SUPER METER

A COMBINATION VOLT-OHM MILLIAMMETER PLUS  
CAPACITY REACTANCE INDUCTANCE  
AND DECIBEL MEASUREMENTS



**SPECIFICATIONS:**

- D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500/7,500 Volts
- A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- OUTPUT VOLTS: 0 to 15/30/150/300/1,500/3,000 Volts
- D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes
- RESISTANCE: 0 to 1,000/100,000 Ohms 0 to 10 Megohms
- CAPACITY: .001 to 1 Mfd. 1 to 50 Mfd. (Good-Bad scale for checking quality of electrolytic condensers)
- REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms
- INDUCTANCE: .15 to 7 Henries 7 to 7,000 Henries
- DECIBELS: -6 to +18, +14 to +38, +34 to +58

**ADDED FEATURE:**


Built-in ISOLATION TRANSFORMER reduces possibility of burning out meter through misuse.

The Model 670-A comes housed in a rugged crackle-finished steel cabinet complete with test leads and operating instructions.

**\$28<sup>40</sup>**  
NET

Superior's New  
Model TV-50

# GENOMETER

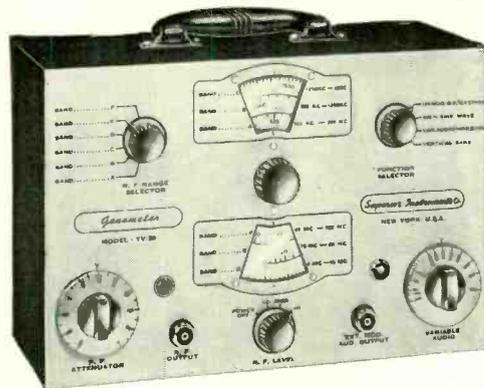

A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing:  
A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV  
**7 Signal Generators in One!**

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

**R. F. SIGNAL GENERATOR:** The Model TV-50 Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

**VARIABLE AUDIO FREQUENCY GENERATOR:** In addition to a fixed 400 cycle sine-wave audio, the Model TV-50 Genometer provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

**BAR GENERATOR:** The Model TV-50 projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

**CROSS HATCH GENERATOR:** The Model TV-50 Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

**DOT PATTERN GENERATOR (FOR COLOR TV)** Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50 will enable you to adjust for proper color convergence.

**MARKER GENERATOR:** The Model TV-50 includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency.)

THE MODEL TV-50 comes absolutely complete with shielded leads and operating instructions.

Only .....

**\$47<sup>50</sup>**  
NET

**SHIPPED ON APPROVAL  
NO MONEY WITH ORDER — NO C.O.D.**

Try any of the instruments on this or on the facing page for 10 days before you buy. If completely satisfied then send down payment and pay balance as indicated on coupon. **No Interest or Finance Charges Added!** If not completely satisfied return unit to us, no explanation necessary.

MOSS ELECTRONIC DISTRIBUTING CO., INC.  
Dept. D-198, 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked. I agree to pay down payment within 10 days and to pay the monthly balance as shown. It is understood there will be no finance, interest or any other charges. Provided I send my monthly payments when due. It is further understood that should I fail to make payment when due, the full unpaid balance shall become immediately due and payable.

- Model 670-A Total Price \$28.40  
\$7.40 within 10 days. Balance \$3.50  
monthly for 6 months.
- Model TV-11 Total Price \$47.50  
\$11.50 within 10 days. Balance \$6.00  
monthly for 6 months.

- Model TV-40 Total Price \$15.85  
\$3.85 within 10 days. Balance \$4.00  
monthly for 3 months.
- Model TV-50 Total Price \$47.50  
\$11.50 within 10 days. Balance \$6.00  
monthly for 6 months.

- Model TC-55 Total Price \$26.95  
\$6.95 within 10 days. Balance \$5.00  
monthly for 4 months.
- Model TV-12 Total Price \$72.50  
\$22.50 within 10 days. Balance \$10.00  
monthly for 5 months.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



*Modified a.c.-d.c. receiver makes economical AM tuner*



By JOSEPH MARSHALL

FM radio and LP recordings provide by far the greatest portion of the listening fare on most high-fidelity installations. However, even in metropolitan areas having several FM stations many desired programs are broadcast only on AM stations. Often, therefore, a need arises for an adequate and economical AM tuner either to supplement the FM tuner and record player or to serve as the primary source of program material. The ordinary table-model a.c.-d.c. radio can be converted very simply and economically into a satisfactory tuner. Since almost every household possesses one or more such radios, a conversion offers a means of saving a sizable portion of the investment in a hi-fi installation.

Most a.c.-d.c. radios consist of a converter, i.f., detector-a.v.c.—first audio and beam-power output stages. Most use vacuum-tube rectifiers; some the more compact, selenium rectifiers. In any case Fig. 1 is representative of the audio end of more than 90% of such receivers.

The a.c.-d.c. radio is more suitable

for conversion to hi-fi tuners than more elaborate models having an r.f. and additional i.f. stage. The bandpass of the simple receiver, while narrow enough to minimize the most serious interference, is sufficiently wide to pass most of the desired high frequencies. And for primary areas with hi-fi AM stations, it can be widened to provide about as much usable fidelity as AM broadcasting permits.

Even in primary areas so close to the transmitter that the desired signal swamps most or all electrical and radio interference, a bandpass of about 15 kc, which results in an audio response up to 7,500 cycles, is about the limit for enjoyable reception because a wider bandpass increases the noise level to the point where it produces outright annoyance or its amplitude is sufficient to effectively mask frequencies above 7,500 cycles.

On the fringe of the primary area and beyond, with conditions on the broadcast band as they are today, interference-free reception limits the bandwidth to only 10 kc and an audio

response which slopes rapidly beyond 5,000 cycles. The table-model radio can easily meet the bandwidth requirements of either situation with very slight modifications and little if any investment in additional parts.

The steps necessary for conversion are: provide a suitable takeoff point for the audio, disable the output stage and speaker, improve the frequency response, reduce the hum level sufficiently to make the additional low-frequency response usable.

### The hot chassis problem

Providing the audio takeoff point and connecting the tuner to the amplifier are not as simple as might appear at first thought. The trouble is that the audio amplifier will certainly have a transformer type power supply and the chassis will be the common ground for both the audio frequencies and the operating voltages. In the transformerless a.c.-d.c. radio the chassis serves as a common ground for r.f. and a.f. but the B-minus point is isolated from the chassis. Moreover, in the transformer type supply the chassis and B minus are isolated from the power line. In the a.c.-d.c. radio B minus is connected directly to one side of the power line and the chassis is also in the power-line circuit through a capacitor and high-value series resistor. Therefore, the chassis and common ground points of radio and amplifier are at different potentials with respect to the power line, operating voltages on the tubes and the desired audio frequencies. So that, in the interests of safety for equipment and persons, as well as in the interest of not disturbing the operating parameters of either radio or amplifier, it is necessary to isolate the chassis and B-minus points.

We can get the necessary isolation and still minimize hum pickup by using

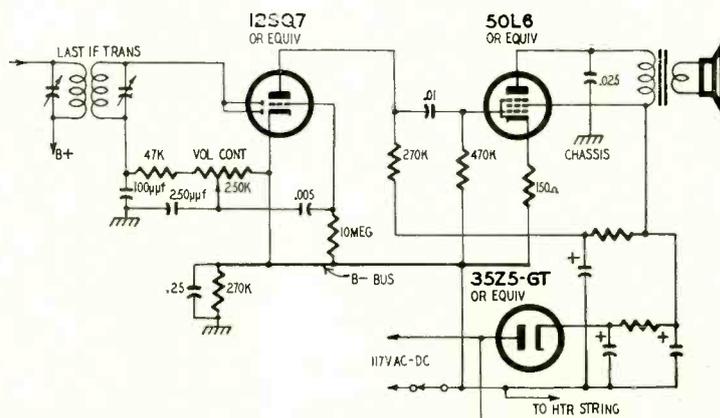


Fig. 1—Audio output stage and power supply of a typical a.c.-d.c. radio.

# SMASH THE "distance barrier"

—WITH *Telrex*


## THUNDERBIRDS

**new!** Telrex  
Hi-Frequency  
Yagis for Dual  
Channel  
Reception

Precision tuned and matched for super-performance. Featuring famous Telrex ruggedized all-aluminum construction and quick-rig design that saves you time and money on every installation!



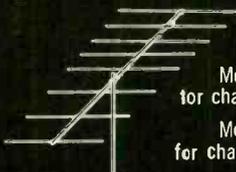Model Y7X1 (7-8-9)  
for channels 7, 8, and 9.




Model Y8X1 (10-11)  
for channels 10 and 11.

Model Y8X1 (12-13)  
for channels 12 and 13.

Producers of famous "BEAMED-POWER" Communication Rotaries. Call or write for new catalogs on TV Antennas, Commercial Arrays or Amateur Rotaries.

"Conical-V-Beams" are produced under U.S. Patent No. 23,346, Canadian Patent No. 500,436 and British Patent No. 69,435—other patents pending. Sold only through authorized distributors.

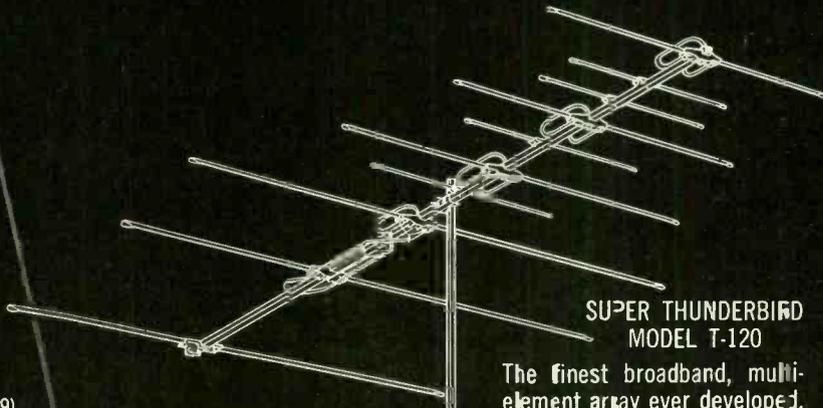- Duplexed Elements for Maximum Gain
- Compensated "Trombone" Matching Sections for Maximum Efficiency
- Full Video and Audio Bandwidth for Maximum Black and White and Color Fidelity
- Hi-Strength Aluminum, Quick-Rig Construction




SUPER THUNDERBIRD  
MODEL T-120

The finest broadband, multi-element array ever developed.
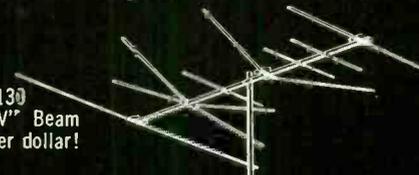
### New Distance Smashers for All-Channel TV!

These new multi-element Broadband "Beamed-Power" Arrays are Telrex-designed especially for fringe and sub-fringe area reception, wherever exceptional sensitivity and maximum directivity are required. For extra performance at low cost, install Telrex "Thunderbirds"—the "hurricane-designed" arrays that provide lasting installations! Call or write for complete catalog, today!

TELREX THUNDERBIRD Model T-130 features Conical Dipole and "V" Beam elements for maximum results per dollar!




*Telrex* INC.  
"CONICAL-V-BEAMS"

AMERICA'S  
STANDARD OF  
COMPARISON!

ASBURY PARK 7  
NEW JERSEY, U.S.A.  
Tel. PRospect 5-7252

Canadian Distributor:  
DELHI METAL PRODUCTS,  
LTD., Delhi, Ontario

## AUDIO—HIGH FIDELITY

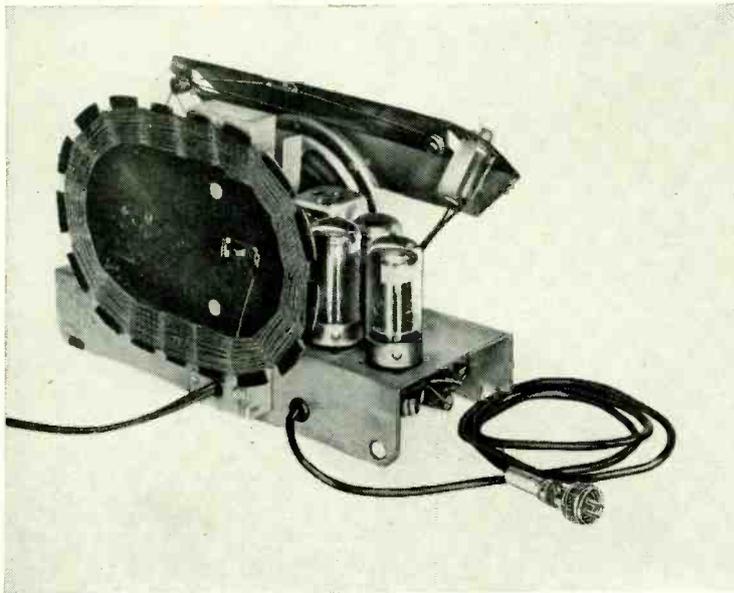

Typical a.c.-d.c. receiver modified for feeding a high-fidelity audio amplifier.

an insulated, shielded two-conductor microphone cable instead of the usual one-conductor shielded cable. The shield is grounded *only* to the chassis of the amplifier, the two inner conductors picking up the audio through blocking capacitors as indicated in Fig. 2. In this way the two units are isolated so far as d.c. operating and line voltages are concerned, and still provide adequate shielding of the connecting cable to minimize hum pickup. We also protect ourselves against shocks and the equipment against possible damage. To preserve isolation and consequent safety, the two chassis must not be permitted to touch each other or be connected together.

Although the chassis of the radio could be removed from its cabinet and placed in the same cabinet as the audio amplifier, it is simpler and more convenient, as well as safer, to keep the radio in its cabinet and connect it to the amplifier through a cable. If the cable length is held down to 5 feet or less there will be no significant loss of the high audio frequencies. Cable lengths as great as 10 feet will not be too serious and the high-frequency losses can be compensated for by some treble boosting in the amplifier. A location more remote than this, however, would require a cathode follower output on the tuner and, unfortunately, it is not easy to provide a cathode follower in an a.c.-d.c. radio because of the lack of suitable tubes with high-voltage filaments—although it might be possible to modify the output stage to a cathode follower.

### Receiver modifications

It is not possible to remove the output tube from an a.c.-d.c. radio because the filament chain would be broken. However, it can be disabled as far as the audio and d.c. voltages are concerned and still remain part of the filament chain. This is done simply by

disconnecting the following leads at the socket terminal: the lead from output transformer to the plate; the lead from the screen to B plus; the grid resistor; the cathode resistor. All these changes are indicated in Fig. 3. The speaker should also be disconnected from the secondary of the output transformer. The output tube will now serve simply as a ballast tube in the filament chain. It will draw no plate current and will not affect the audio signal.

The low-frequency response of a.c.-d.c. radios is very poor below 100 cycles and must be improved for hi-fi reception. This is very easily done by changing the coupling capacitor between the first audio stage and the output tube from its present value of about .01 to 0.1  $\mu$ f. The same value can be used as the blocking capacitor at the ground end of the connecting cable. It is highly probable that the first audio amplifier will use grid-leak bias—as indicated by a grid resistor of 5 to 10 megohms for the triode section of the 12SQ7 or equivalent tube. In this case, no change in the coupling capacitor of that stage is necessary since the .005- $\mu$ f capacitor will, in conjunction with the very high grid resistance, have a time

constant low enough to pass the desired low frequencies.

### Reducing hum level

Increasing the bass response, however, will almost certainly raise the 60-cycle hum level to an objectionable stage. Fortunately, there is a simple means of reducing the hum at no additional cost. The primary of the output transformer, now no longer being used, can be employed as a choke. If the receiver already uses one choke in the filter, the transformer can be inserted in series with the present choke to produce a two-stage filter. Some, if not most, receivers use a resistor instead of a choke. In that case the transformer primary can be used to replace the resistor. In either case, the addition of a choke will usually reduce the hum level to a point low enough to be tolerable. If further filtering is necessary, additional filter capacitance can easily be added.

If the receiver is used in a primary signal strength area, it may be desirable to widen the bandwidth of the i.f. amplifier. This is easily done by detuning the secondaries of the i.f. transformers slightly. For the most symmetrical response curve, an oscilloscope and sweep generator should be used. However, a v.t.v.m. connected across the a.v.c. line will serve as a good enough indicator and careful detuning to provide as nearly uniform deflection on both sides and as flat a

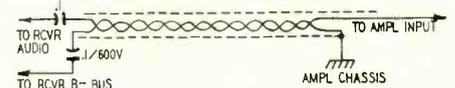


Fig. 2—Radio-amplifier connection.

top as possible can produce excellent results. A bandpass of 15 kc is easy to obtain even without a scope but a wider one with a suitable flat top requires the use of a scope.

By these very simple changes and modifications, it is possible to produce an AM tuner good enough for the very great majority of hi-fi installations at little or no cost beyond that of an hour or so of labor. END

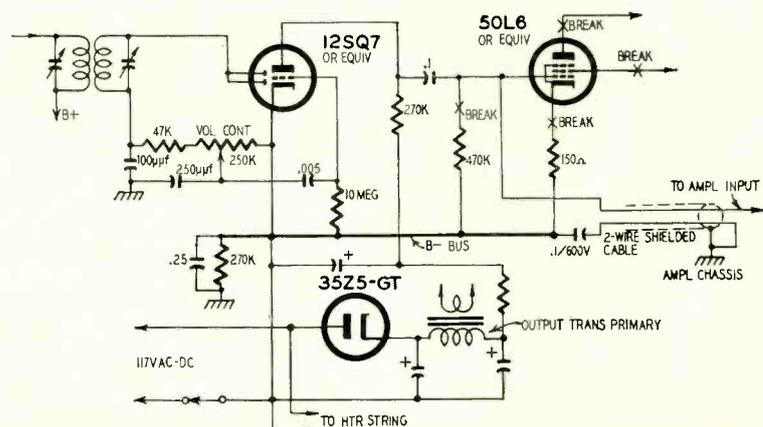


Fig. 3—Modified output circuit for connection to a hi-fi amplifier.

**FIRST** TO BREAK THE TV RECEPTION BARRIER...

**MOST POWERFUL SUPER FRINGE  
ANTENNA IN THE WORLD**

# NEW WALSCO WIZARD

with exclusive **PHASE REVERSER**

Distance is no barrier to the amazing new WALSCO WIZARD. Exclusive "Phase Reverser" delivers the sharpest, crystal-clear picture ever seen in the most difficult reception areas. No other antenna like it!

New WIZARD offers highest gain and sharpest directivity possible on all VHF channels. Installation in a jiffy... without complicated harnesses, phasing stubs, or extra dipoles. Guaranteed for 3 years!




**ELECTRONICS CORPORATION**  
A SUBSIDIARY of *Autograph* CORPORATION

3602 Crenshaw Blvd.,  
Los Angeles 16, California

**Model**  
Wizardette #4210  
Wizard #4220  
Wizard Imperial #4230

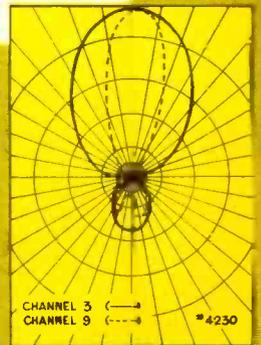**Price**  
\$14.90 list  
19.50 list  
34.90 list



WALSCO WIZARD Imperial equals reception of 10 element yagi on low channels, and equals a three stack 10 element (30 elements) yagi on channels 7 to 13.

Actual comparison of fringe antenna performance

Channels	Gain (db) Single Bay						
	2	4	6	7	9	11	13
Walseo Wizard Imperial	5.1	6.9	8.2	11.9	11.6	10.8	12.6
Antenna "A" With 3 Phase Reversing Dipoles	5.3	6.6	8.1	10.5	10.2	10.6	12.4
Antenna "B" - Yagi Type with Phasing Loops	5.1	5.5	6.8	7.5	9.6	8.3	11.2
Antenna "C" - Yagi Type with Loading Coils	5.9	6.9	8.6	9.1	8.6	9.5	7.8

**Guaranteed for 15 and 25 Years...**

All Columbia 300 ohm PERMALINE TV

TRANSMISSION LINE is backed by a written guarantee of 15 and 25 years (50 mil — 15 years; 80 mil — 25 years)

Extensive research on Permaline insulation has shown that it will far outlast any other type of television transmission line in average use today. This is based on reports of one of the largest testing laboratories in the country (name upon request).

Service men are rapidly learning that even though Columbia Permaline insulation is more durable, it strips easier due to the high molecular weight of Polyethylene . . . simplifies service jobs.

Available from leading jobbers

**WIRE & SUPPLY CO.**  
2850 Irving Park Road, Chicago 18, Ill.



**Another "Columbia" First...**

**MISCELLANY**

**OUR ABBREVIATIONS OF ELECTRONIC TERMS**

AS some of our readers have noted, RADIO-ELECTRONICS attempts to maintain a consistent style in its abbreviations.

Many of our readers have not been with us long enough to profit by our consistency. Others have requested a list of abbreviations to help them in their own writing. Therefore we are printing this list of abbreviations in the hope that they may be useful.

The list below represents a revision of abbreviations used in this magazine. Many are always spelled out in text but abbreviated in our art work—terms which appear only in art work—as well as those capitalized in text—appear in capitals. Other abbreviations used in drawings only are omitted since they are practically self-explanatory. Terms like *ft*, *lb*, etc., which are not electronic, are generally omitted. Note that in those (and other) abbreviations the period is used only where the abbreviation might be confused for another word: *ft*, for example, but *in*. for inch. Abbreviations in lower case are so printed in text; are capitalized in art-work.

ELECTRONIC TERM	ABBREVIATION
adjacent	ADJ
alternating current	ac
American wire gauge	AWG
ampere(s)	amp
amplifier	AMPL
amplitude modulation	AM
antenna	ANT
attenuator	ATTEN
audio frequency	af
audio-frequency choke	af choke
audio-frequency transformer	AFT
automatic chroma control	ACC
automatic frequency control	afc
automatic gain control	agc
automatic phase control	apc
automatic volume control	avc
autotransformer	AUTOTRANS
Barkhausen oscillation	BO
base (of transistors)	b or base
battery	BATT
beat frequency oscillator	bfo
blocking tube oscillator	BTO
broadcast interference	BICI
calibrate	CALIB
capacitor (capacitance)	C. CAP
cathode	CATH (K on tube diagrams)
cathode follower	CATH FOLL
cathode-ray (tube, etc.)	C-R
cathode-ray oscilloscope	CRO
channel	CHAN
charge	CHG
choke	CH (or CHOKE)
circuit	CKT
circuit breaker	CKT BRKR
coaxial	coax
coil	L
collector	c (of transistors)
common	COM
conductor	COND
connection	CONN
continuous wave	CW
control	CONT
convergence	CONV
converter	CONVTR
counter electromotive force	counter emf
crystal	xtal
current	I
decibel(s)	db
deflection	DEFL
demodulator	DEM0D
detector	DET
dielectric	DIELEC
direct current	dc
direct current restorer	DC REST
direction finder	df
discharge	DISCH
discriminator	DISCRIM
distance	dx
double cotton covered (wire)	dcc
double pole double throw	dpdtt
double pole single throw	dpst
double silk covered (wire)	dsc
dynamic	DYN
effective radiated power	ERP
electric	ELEC
electrode	ELECT
electromotive force	emf
emitter (transistor)	e
enameled (wire)	ENAM
equivalent	EQUIV
erase head	ERASE HD
external or extension	EXT
farad(s)	F (in combination)
filament	FIL (F in tube diagrams)
follower (ing)	FOLL

ELECTRONIC TERM	ABBREVIATION
frequency	f. FREQ
frequency modulation	FM
generator	GEN
grid	G (in tube diagrams)
grid dip oscillator	GDO
ground	GND
ground controlled approach	GCA
head	HD
heater	HTR (H)
henry	h
high frequency	hf
horizontal	HORIZ
impedance	Z
inches per second	ips
inductor	L
input	IN
instrument landing system	ILS
intermediate frequency	if
intermodulation	IM
inverter	INV
kilocycle	kc
kilowatt	kw
limiter	LIM
linearity	LIN
low frequency	lf
maximum	max
megacycle(s)	mc
megohm	meg
meter	M
micro- (one-millionth)	u
microfarads	uf
microhenry (ies)	uh
micromicrofarad(s)	uuf
microphone	mike
microseconds	usec
milliampere(s)	ma
millihenry(ies)	mh
minimum	MIN
modulation (modulator)	MOD
multiplier	MULT
multivibrator	NVB
narrow-band FM	NBFM
negative	NEG
negative-positive-negative (transistors)	n-p-n
neon	NE
network	NET
oscillator	OSC
output	OUT
peak-to-peak	PP
permanent	PERM
permanent magnet (speaker)	PM
phase modulation	PM
picture (TV)	pix
pilot lamp	PL
plan position indicator (radar)	PPI
plate	P
positive	POS
positive-negative-positive (transistors)	p-n-p
potential	POT
potentiometer	E
preamplifier	preamp
primary	PRI
public address	PA
pulse repetition frequency	prf
pulses per second	pps
reactance-resistance ratio	Q
regeneration	regen
quadrature	QUAD
radio frequency	rf
radio-frequency choke	RFC
radio-frequency transformer	RFT
reactance	X
recorder	RCDR
recording	RCDG
rectifier	RECT
regulator	REG
relay	Ry
resistance (resistor)	R
root mean square	rms
screen grid	SG
secondary	SEC
selenium (rectifier)	SEL (RECT)
separator	SEP
shortwave	SW
signal	SIG
single cotton covered (wire)	sec
single pole double throw	spdtt
single pole single throw	spst
single silk covered (wire)	ssc
speaker	SPKR
standing wave ratio	SWR
switch	S
synchronization	sync
tuned plate tuned grid	tpg
telegraph	TELEG
telephone	phone(s)
television interference	TVI
terminal	TERM
thousand	K
transformer	TRANS
transistor	often V
trimmer	T
tube	V
tuned radio frequency	trf
ultra high frequency	uhf
vacuum-tube voltmeter	vtvm
variable	VAR
variable frequency oscillator	VFO
vertical	VERT
very high frequency	vhf
vibrator	VIB
voice coil	VC
voltage	E (sometimes V in transistor diagrams)
volt(s)	v
volt-ampere	Va
volt-ohmmeter	vom
voltage standing wave ratio	vswr
volts ac, dc	vac, vdc
volume	VOL
volume unit(s)	VU
watt(s)	w

—END—

## MAKING

## PHOTOETCHED

CIRCUITS  
IN YOUR  
WORKSHOP

By RICHARD H. DORF\*

*Part II—Sensitizing the laminate;  
exposing the panel; developing the  
image; etching*

THE foil-clad laminate on which the circuits are etched consists of a base material of phenolic or some other substance. For most purposes the cheapest grade of phenolic (XP) is satisfactory, and it comes in several thicknesses beginning at about 1/64 inch. There are other base materials for critical applications but, unless it is absolutely necessary, steer clear of the glass-fiber-base substances. They ruin drills and saws. The base material is usually covered with copper foil .00135 inch thick. It is bonded to the base with a very effective adhesive and will generally "lift" only if excessive heat is applied. Use a piece of this laminate somewhat larger than the

final circuit for ideal results—the photo resist coating may tend to form a bead at the lower edge during the drip-dry time. Laminate is available with copper on either one or both sides; choose the proper type, trying to stick to one-side panels where feasible.

The laminate must be thoroughly cleaned before use. Do this with an abrasive type kitchen cleanser such as Kirkman's. The copper must be absolutely clean and of uniform light color. Once clean, *do not touch it with the fingers*. Run warm water over it for at least 2 minutes to be sure the last trace of cleanser is removed and finish with hot water alone for faster drying. Do not dry—let the water evaporate.

The next material required is Kodak Photo Resist, obtainable in quart bottles. Pour a little into a glass or enameled tray. Dunk the panel into the resist face up and give it a moment to spread uniformly over the copper. Then remove the panel from the tray and hang it up to drip dry.

For best results:

1. Be absolutely certain that all materials which come in contact with the Kodak Photo Resist are completely dry. The slightest bit of water causes the resist to solidify, making it useless.

2. Do not touch any part of the copper with the hands or with anything else (except the negative) between the initial cleaning and the time the laminate goes into the etching acid.

3. If the panel is larger than the final piece, drill a small hole near the center of one of the long edges and insert a wire a few inches long as a handle. This keeps fingers out of the liquids.


4. When drying the panel, hang it so an edge is parallel to the floor. If hung by a corner—normal with films—a diagonal streak of resist may cause the coating to be heavier along the streak and give imperfect results.

5. While a darkened room is not necessary, try to keep Kodak Photo Resist, Photo Resist Dye and Photo Resist Developer away from too much light, as light reduces the potency.

6. The photo resist is not cheap. Let the initial drops from the hanging panel drip into a tray, then pour it back into the bottle. Screw the cap on tight.

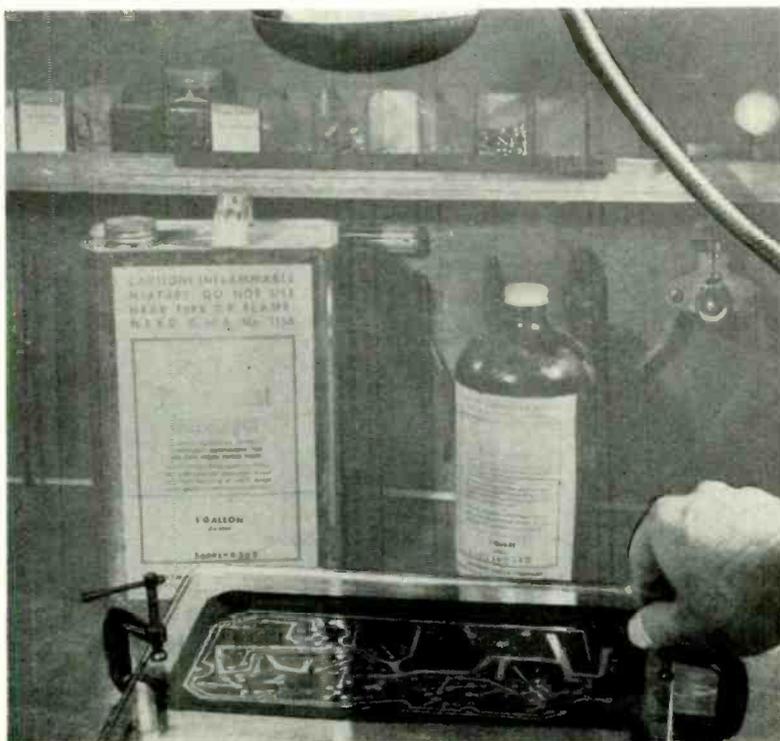7. Be sure the resist is thoroughly dry before exposing the panel. On one-sided laminate a good test is to stroke the noncopper side with a finger. No heat is needed, just a hanging time of 15 to 30 minutes in ordinary climates.

You are ready now to start the actual making of a printed circuit, using the  
(Continued on page 142)



Equipment and setup for exposing the sensitized laminate.



\*Electronics consultant, New York.

**precise**

**EXTRA!**


**EXCLUSIVE..**

*Who murdered the serviceman?*

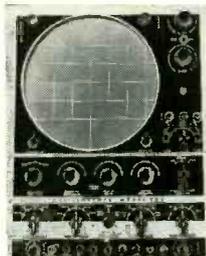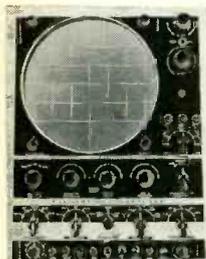

THE FIRST AND ONLY  
8 1/2" COLOR SCOPE  
308K ..... \$129.50  
308W ..... \$229.50

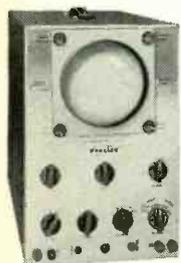THE FIRST LOW PRICED  
7" COLOR SCOPE  
300K ..... \$94.95  
300W ..... \$199.50



LOW PRICED 5" SCOPE  
315K ..... \$49.95  
315W ..... \$84.95



THE FAMOUS MODEL #111  
111K ..... \$69.95  
111W ..... \$139.95



LOWEST PRICED  
WIRED 4 1/2" VTVM  
909K ..... \$25.98  
909W ..... \$37.50



RF-AF-BAR GENERATOR  
with pre-assembled\* head  
630K ..... \$33.95  
630KA\* ..... \$38.95  
630W ..... \$53.95



THE FINEST VOLT, REG,  
7" VTVM KIT  
9071K ..... \$35.95  
9071W ..... \$49.95



LOW PRICED RF SIGNAL GENERATOR  
"BEST BUY" IN GEN. FIELD  
610K ..... \$23.95  
610KA pre-assembled head ..... \$28.95  
610W ..... \$39.95



UNIV. AF, SINE, SQ, & PULSE GEN.  
635K ..... \$33.50  
635W ..... \$52.50

OR at least the serviceman's confidence in tube testers. LOOK at the FACTS —A serviceman trusts his VTVM (like the Precise 9071 or 909); his signal generator (like the Precise 610 or 630 or 635); his oscilloscopes (like the famous 300 or 308 or 315).

**BUT . . . HE DOES NOT TRUST HIS TUBE TESTER (UNLESS IT'S A PRECISE 111).**

For the serviceman's sake, WHY?

Precise engineers recognize him as a logical, intelligent fellow. They knew he had good reasons and they looked into the matter with him in mind. Our electronic sleuths found that some manufacturers used an Em (emission) test, some a Gm (mutual transconductance), some a so-called combination, and some a sort of OUIJA board. Some manufactured tube testers that were fast—some slow—some tied almost all the elements together. In some you could cut off pins and the tube merrily read "good." Some didn't even connect all the pins. NO wonder our serviceman's confidence was being murdered!

What then has Precise done to prevent this mayhem. We went directly to the tube manufacturers before offering the serviceman a tube tester. We found out how the tube manufacturer gets the kind of check a serviceman wants . . . a 100% test! We wanted to offer a tube tester that simulates operating conditions in a set. WE HAVE DONE THIS. We added a lot of other requirements . . . A SHORT CHECK, GAS CHECK, Gm, Em, LIFE, FILAMENT CURRENT for 600 mil tubes, BIAS, NOISE and other checks.

**RESULT**, a tube tester with built in confidence . . . you can even see the tube characteristic curve on an oscilloscope. What's more you can operate this tube tester as simply as the ordinary testers. The Precise 111 has about the same number of controls . . . Remember! it uses rotary switches instead of lever type, because the rotary gives over twice the protection against becoming obsolete. Furthermore, several tests are listed for each tube (an Em and a Gm) with the 100% test started.

NOW YOU CAN TEST YOUR TUBES COMPLETELY. FOR PROOF OF WHAT WE OFFER SEE THE RESULTS OF AN INDEPENDENT SURVEY.

Prices slightly higher in the West. Prices and specifications subject to change without notice.

**precise**

THE FINEST KIT AND WIRED TEST EQUIPMENT

SEE THE MANY MORE PRECISE INSTRUMENTS AND PROBES AT YOUR JOBBER TODAY!

WRITE FOR CATALOG RE 1-6

DEVELOPMENT CORP. OCEANSIDE, NEW YORK, U.S.A.

# .. INDEPENDENT SCIENTIFIC SURVEY

## PRECISE MODEL #111 PROVED

### "BEST COMMERCIAL TUBE TESTER

### AT ANY PRICE" IN INDEPENDENT SURVEY



111K (kit form)

NOW ONLY

# \$69<sup>95</sup>

111W (factory wired) ..... \$139.95

Prices slightly higher in the West. Prices and specifications subject to change without notice.

# precise

## Model #111

### MUTUAL CONDUCTANCE AND EMISSION TUBE TESTER

An independent scientific survey conducted by an impartial testing laboratory confirms what purchasers already know: "The most advanced, the most complete tube tester and the best priced is made by PRECISE DEVELOPMENT CORP., Oceanside, N. Y."

#### NOW YOU CAN CHECK TUBES THE MANUFACTURER'S WAY

- Checks both emission and mutual conductance
- Checks all tubes including hearing aid, miniatures
- Six different plate voltages
- Different grid signals
- Simplified Short check
- Gas check
- New type switches
- Deeply etched aluminum panel
- Three different screen voltages
- Latest roll chart
- Measures filament current
- Measures grid bias

#### CHECK THESE ADDITIONAL 'specs' . . . TALK TO YOUR JOBBER AND TO ANYONE WHO HAS THIS OUTSTANDING TUBE TESTER . . .

The Model 111 is the only single commercial tube tester that checks all tubes for both EMISSION and MUTUAL CONDUCTANCE separately. Filament current is measured directly on large meter when checking a VOLTAGE SAPPER tube. NEW, MODERN DESIGNED ROTARY SWITCHES allow you to check each tube element individually. NEW TYPE Single Rotary switch for complete short checks. The 111 makes all BIAS,

FILAMENT VOLTAGE, GAS, LIFE checks visually on large meter . . . 5 individually calibrated ranges and scales for mutual conductance tests. NEWLY DESIGNED "NO BACKLASH" ROLL CHART lists all tubes including the new type 600 mil series tubes. Provisions are made for testing many color tubes. All CRT's can be checked with accessory adaptor, Model PTA.

SEE THE MANY MORE PRECISE INSTRUMENTS AND PROBES AT YOUR JOBBER TODAY!


WRITE FOR CATALOG RE 1-6

# precise

 THE FINEST KIT AND WIRED TEST EQUIPMENT

## DEVELOPMENT CORP. OCEANSIDE, NEW YORK, U.S.A.
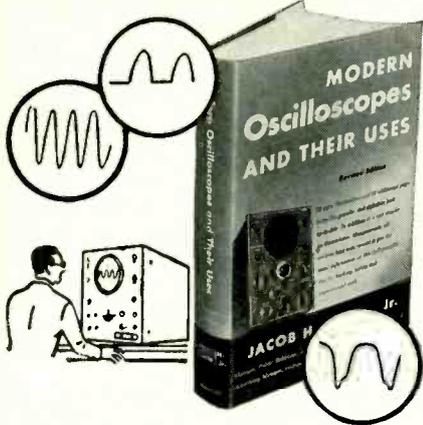
# HERE'S EVERYTHING YOU NEED TO KNOW ABOUT OSCILLOSCOPES!



## Service Any Radio-TV ever built EASIER-BETTER-FASTER

Oscilloscopes are gold mines for servicemen who learn to use them fast and accurately—and here, in a completely revised 2nd edition, is THE book that really shows you how.

In plain, easily understood language, MODERN OSCILLOSCOPES AND THEIR USES teaches you just when, where and exactly how to use your oscilloscope. You learn how to handle tough jobs easier and faster than you may have dreamed. Every detail is clearly explained—from making connections to adjusting circuit components and setting oscilloscope controls.

Equally important, you learn to analyze patterns accurately in far less time. Almost 400 illustrations including dozens of pattern photos make things doubly clear.

### 'SCOPES ARE "GOLD MINES" when you learn to use them fully!

This big book is more widely used than any other of its type—because it gets right down to "brass tacks." No involved mathematics. No complicated discussions. You learn exactly what the oscilloscope is and exactly how to use it on all types of AM, FM and television service (including color)—from locating troubles in a jiffy to handling tough realignment jobs.

Send coupon for 10-day free trial.

### PRACTICE 10 DAYS FREE!

Dept. RE-16, RINEHART & CO., Inc.,  
232 Madison Ave., New York 16, N. Y.

Send new 2nd edition of 370-page MODERN OSCILLOSCOPES AND THEIR USES for 10-day FREE EXAMINATION. If book is what I want, I will then send you \$6.50 promptly in full payment. If not, I will return book postpaid in good condition and owe you nothing.

Name.....


Address.....

City, Zone, State.....

OUTSIDE U.S.A.—Price \$7.00, cash only. Money back if you return book in 10 days.

Rinehart Books Are Sold by Leading Book Stores

## RADIO


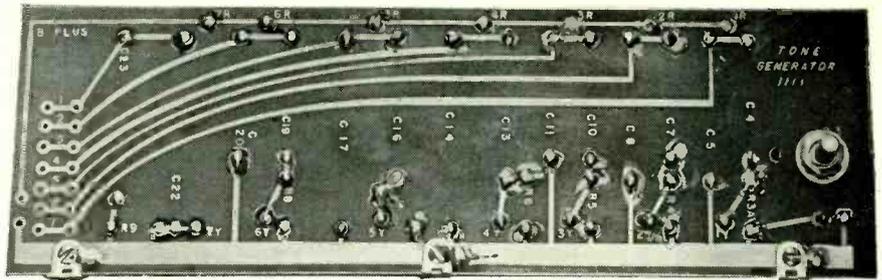


The completed printed circuit. Globules of solder are at the connection points.


panel which has just been coated. You may coat as many panels as you like at a time. Wrap any you are not going to use immediately in paper and store away from light; they will keep indefinitely and will be ready for use at any time.

You will need a table with a flat top, a piece of heavy glass and an exposure lamp. A mercury-vapor ultra-violet lamp especially made for photographic purposes by Hanovia is ideal. This lamp fits into an ordinary lamp socket which you can hang on the end of a cord above the table. When the switch is turned on, the lamp will light; after a few seconds it will momentarily re-

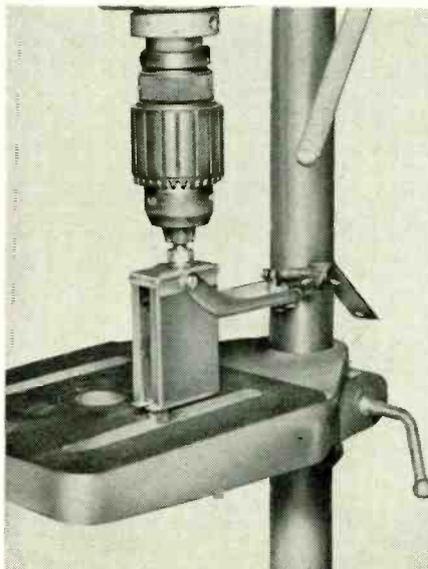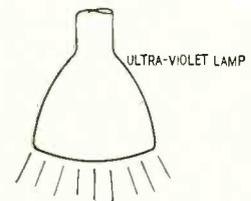materials. Be sure that the emulsion (dull) side of the film is down against the panel, a point you can check by seeing that the pattern reads right rather than in mirror fashion as viewed through the glass. There must be good contact at all points. If the panel is somewhat warped, use a piece of glass a good deal larger than the negative



Roto drill saw for cutting laminate.

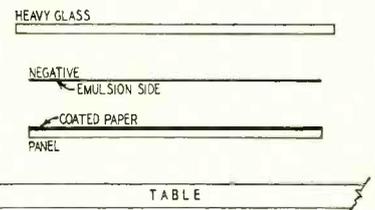

Showing how the equipment is assembled to expose the sensitized laminate.

and panel and weight it down at the edges with good heavy weights and leave it there till it straightens out.

Exposure time depends on such factors as distance from lamp to panel, line voltage and others. However, I have a standard which should be universally applicable. With the lamp at a distance of 12 inches from the table, the time is 6 minutes. A couple of test exposures on short strips cut from larger panels will make this clear. Try to place the materials directly under the lamp for most even exposure. If the panel is more than about 8 inches square, the lamp might be raised somewhat and exposure time lengthened. Once set for a given set of circumstances, all exposures can be made the same in the future. A person who has had some experience in developing his own negatives and making prints will find all the procedures strictly matters of routine.

### Developing the image

When the exposure is finished, turn off the light and remove the panel. Place it immediately in a tray of Kodak

duce its light output, then immediately go back to full brilliance and remain on until the switch is opened. After it is turned off, however, the lamp will not go on again for several minutes. So if you are in a hurry, do not turn on the lamp until you are actually ready to start using it. It gives off light in plenty but no heat is transmitted to the negative, which would tend to curl and even melt with an ordinary photoflood. These lamps can be obtained from Hanovia distributors—if you have none locally, any store handling health lamps will be in a position to give you information as to where one can be ordered.

The diagram shows how to set up the

*Exclusive!*

# The First **MULTI-CHANNEL** YAGI...PRE-TUNED TO CHANNELS OF YOUR CHOICE

*New!* **WINEGARD**



- ... Gives You More Gain on Channels in Your Area
- ... Because it's Peaked to Channels in Your Area


There has never been an antenna like the COMBO — the first MULTI-CHANNEL TV ANTENNA that is actually PRE-TUNED TO YOUR AREA. The Combo is factory peaked in 16 different channel combinations — one of which will give you the ultimate in performance on the specific channels you want.

This is the first logical, practical TV antenna development in years. The Winegard COMBO is guaranteed to give better performance on all channels in your area, regardless of size or number of bays of the antenna you are now using.

Another original by WINEGARD!

Available in 16 Factory Pre-Tuned Combinations

Custom-Combo Model No.	Channels Peaked for												
TC3-A	2	3	4	5	6	7	8	9	10	11	12	13	
TC3-B	2	3	4	5	6	7	8	9	10				
TC3-C	2	3	4	5	6	7	8	9	10				
TC3-D	2	3	4	5	6	7	8	9	10	11	12	13	
TC3-E	2	3	4	5	6	7	8	9	10	11	12	13	
TC3-F	2	3	4	5	6	7	8	9	10				
TC3-G	2	3	4	5	6	7	8	9	10	11			
TC3-H	2	3	4	5	6	7	8	9	10	11	12	13	
TC3-I		3	4	5	6	7	8	9	10	11	12	13	
TC3-J		3	4	5	6	7	8	9	10				
TC3-K		3	4	5	6	7	8	9	10	11			
TC3-L		3	4	5	6	7	8	9	10	11	12	13	
TC3-M		4	5	6	7	8	9	10	11	12	13		
TC3-N		4	5	6	7	8	9	10					
TC3-O		4	5	6	7	8	9	10	11				
TC3-P		4	5	6	7	8	9	10	11	12	13		

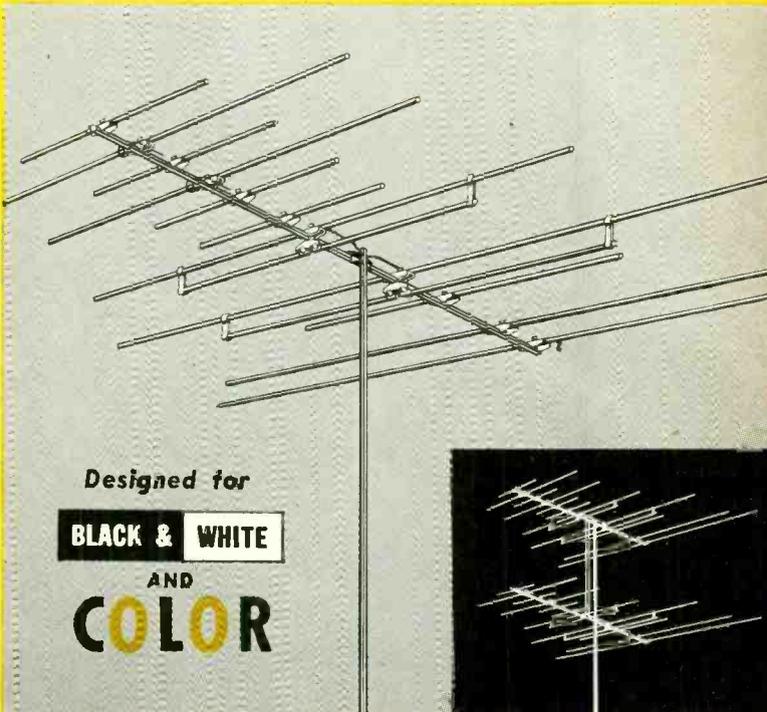

Designed for  
**BLACK & WHITE**  
AND  
**COLOR**

Single bay Combo — \$29.95    Double bay Combo — \$59.95

## 5 GOOD REASONS TO INSTALL THE COMBO:

1. Pre-Peaked to Your Channels
2. Electro-Lens\* Director System
3. Completely Pre-Assembled
4. Automatic Twin-Lock Hardware
5. All Aluminum and Stainless Steel Construction

**MAIL TODAY**

**WINEGARD COMPANY** 1.  
3000 Scotten Boulevard  
Burlington, Iowa

Please RUSH  COMBO Bulletin No. WL11135  
 Address of nearest distributor

---

NAME OF FIRM \_\_\_\_\_

---

ADDRESS \_\_\_\_\_

---

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

---

SIGNATURE \_\_\_\_\_



# Chicago Standard HI-FI OUTPUT TRANSFORMERS

**for a 100 WATT AMPLIFIER  
with 0.2% IM DISTORTION  
and a wide range of  
smaller amplifiers**

The new BO-14 Super-Range transformer is typical of the 43 high fidelity output transformers that CHICAGO STANDARD can supply. Used in a newly developed circuit with 6550 tubes, it provides a flat frequency response from 10 cycles to beyond 200,000 cycles and a power response, at 100 watts, of 15 to 30,000 cps,  $\pm 2$  db, with only 0.2% intermodulation distortion at 100 watts. The BO-14 is tapped for 8 and 16 ohm speakers and 70 volt sound systems and can be used for triode, pentode or ultra-linear operation.

**FREE** Detailed brochure on the BO-14 Super-Range Hi-Fi Amplifier and other Hi-Fi equipment, with complete parts lists and construction information.

**TRANSFORMERS FOR ALL TYPES OF HI-FI EQUIPMENT AND APPLICATIONS—in a variety of mounting styles—are available from CHICAGO STANDARD.**

Export Sales:  
Roburn Agencies, Inc.  
431 Greenwich Street,  
New York 13, N. Y.



**CHICAGO STANDARD  
TRANSFORMER CORPORATION**  
3592 ELSTON AVE. • CHICAGO 18, ILL.

**NEW ELECTRONIC  
GARAGE DOOR OPERATOR**

You can assemble your own operator and save almost half the cost. New Bellford-Matic kits are now furnished with quick-disconnect, automatic light and control box factory wired and tested—at no increase in price. Top quality components assure trouble-free operation. Detailed drawings and easy-to-follow assembly instructions with each kit. Post Controlled Kit, Model PCK-1L, only \$69.00. Radio Controlled Kit, Model RCK-1L, only \$119.00 F. O. B. Factory. Complete, nothing else to buy. Fully guaranteed. Send for folder of complete line.

**Dealer inquiries invited**  
**BELLFORD-MATIC, Inc.**  
Dept. R.E., Maurice Ave., Cleveland 27, Ohio

**\$69.00**

**BUY IT WHOLESALE!**

GET UP TO 40% OFF

Start a Buying Service at Home. SPARE TIME. GET BIG-NAME MERCHANDISE FOR LESS AND CLIENTS UP TO 40% LESS THAN REG. PRICES. SALES AS EASY AS YOU CAN GIVE. SCHEDULE DISCOUNTS. STILL MAKE FAT COMMISSIONS. Post Card brings FREE COPY The Wholesale Plan.

**FREE!** THE WHOLESALE PLAN

**American Buyers Service**

DEPT. RE, HERTEL STATION  
BUFFALO, NEW YORK

**Watch for February  
RADIO-ELECTRONICS**

**NOW IN STOCK at ALMO RADIO CO.**

550 Markley St. Murrinstown, Pa.

**EICO**

**COLOR & BLACK & WHITE  
5" — 5 MC SCOPE**

**KIT \$79.95 Wired \$129.50**

#460

## RADIO

Photo Resist Developer. The tray must be glass or enamel without any defects. Be sure to keep all water well out of the way since it will harm the developer. Agitate the tray constantly. Development time is at least 2½ minutes, but overdevelopment for a couple of minutes or more causes no harm and is a safety factor.

The developed image will not be visible. Developing simply dissolves away the resist which was not hardened by light; however, the resist is so transparent that this cannot be seen.

It is not necessary to see the developed pattern to etch it. It is a safety factor, however, a check to see that everything is as it should be. There are two ways to make the pattern visible.

The first and a good way is to use Kodak Photo Resist Dye. Pour some in a tray. Take the panel from the developer and immerse it in the dye for 30 to 60 seconds *without wetting it with water*. Then wash the panel under a light stream of warm water. After this washing the areas to which resist has stuck will be dense black and the areas to be etched will be clear copper. Wash the panel thoroughly (but don't rub it) to see that no dye sticks to undesired areas since the dye acts as a resist during etching. The wiring pattern will be clearly shown in black and can be checked. If any lines are imperfect they can be touched up by applying resist with a brush *after the panel is dry*, followed by an exposure to the light. If there is black where there should be none, it can be scraped away.

The second method does without the dye. Simply wash the panel after it comes out of the developer with warm water—around 120°F—for at least 1 minute until the pattern is visible. There will not be a great deal of visual contrast, but enough to see. This method has at least the advantage that the dye, which is rather messy and hard to clean, is absent.

## Etching

The final major step is the actual etching. The material used may be either ferric chloride or chromic acid. Ferric chloride is hard to get in any but liquid form and the liquid may present some difficulties in storage and handling—it cannot be mailed. Chromic acid can be had in chip form; it is mixed with water before use.

The tray in which the etching is done must be glass or enamel. If enamel, it must be unchipped since the acid will eat away the metal base of the tray where it is vulnerable. The acid should not get on clothes or face; if it does get on the skin it is not harmful if washed off immediately. It is not removable from clothes.

Immerse the panel in the acid and agitate the panel throughout the process. It is the mixture of air with the acid that does the etching so it is a good idea to immerse the piece, remove it and let it drip for a second or two, then immerse it again and keep up this

# SELLING OUT!

REGARDLESS OF COST.  
Prices Reduced Up to 80%

COMPLETE STOCK OF NATIONALLY ADVERTISED  
RADIO & TELEVISION TESTING INSTRUMENTS,  
PARTS AND ELECTRICAL APPLIANCES TO BE SOLD  
*This is the opportunity of a lifetime!*

Below mentioned units are not kits, but all factory wired and brand new. Some models have been discontinued by the manufacturer, but every one is factory sealed and carries a one year factory guarantee. Satisfaction or money refunded within 10 days.



Model 999 Combination  
F.M., A.M. and Television

## SIGNAL GENERATOR

A.C. operated, generates R.F. frequencies from 150 kc. to 50 mc. Positive action attenuator provides effective output control

at all times. R.F. is obtainable separately or modulated by the Audio Frequency. Complete with test leads, instructions. Reg. \$39.50; **now only \$19.50**



## TEST CRAFT

Model TC-10 Quality  
Multitester

AC and DC Voltage Ranges: 0-5/15/150/-1500/3000 Volts. DC Current Ranges: 0-5/50 ma. 0-1.5 Amps. Resistance Ranges: 0-100 ohms. 0-100 K.

Complete with batteries, instructions: **now only \$9.85**  
Size: 6"x3 1/2"x2"  
Reg. \$16.85



## TEST CRAFT

Model TC-75

### Combination Test Speaker and Signal Tracer

plus speaker substitution plus field substitutor plus condenser tester plus voice coil substitution plus output indicator

Complete with full instructions **now only \$24.50**  
Reg. \$39.50



## Famous-Make OHMMETER

Has a double range of 0-10 and 0-1000 ohms for accurate measurement of low resistance. Widely used for production testing, armature and field resistances of small motors relay and coil testing transformer winding tests, etc.

Complete with test leads, instructions, leather case. **now only \$14.95**  
Reg. \$36.50



## SUPREME

Model 543-S  
Multimeter

1% WIRE WOUND PRECISION RESISTORS

D.C. Volt Ranges: 0-150-300 D.C. Ma: 0-60-120-300-600. AC Volt Ranges: 0-150-300. Ohm Ranges: 0-1000/100,000. Complete with instructions.

**now only \$9.95**  
Reg. \$24.50



## SUPERIOR

Model PB-100

### Volt-Ohm-Milliammeter

Measures DC Voltages to 2500 Volts, AC Voltages to 1000 Volts, Resistance to 1 Megohm, 1000 Volts, Decibels to plus 55 D.B. Push Button Operation. Complete with instructions and test leads.

**now only \$15.00**  
Reg. \$28.40

	Model	Dealers Net Price	Selling-Out Price
SUPERIOR METROPOLITAN GENERAL ELECTRONICS	660-A Signal Generator	\$42.50	\$29.50
	111 Quality Multitester	21.50	9.95
	200, AM-FM & Television Signal Generator, AC operated	39.50	24.50
REINER ELECTRONICS	333, DC Volt-Ohm-Milliammeter	26.95	9.95
RADIO CITY PRODUCTS	668 Electronic Multitester	74.50	39.50
	665 AC-DC Volt-Ohm Capacity, VIVM	95.40	49.50
SHALLCROSS ELECTRONIC MEASUREMENTS CORPORATION	630 Wheatstone Resistance Bridge	145.00	75.00
	102, Voltmeter	14.90	11.90
	103	18.75	15.00
	104	26.95	21.50
	106 Vacuum Tube Voltmeter	35.90	28.75
	107	48.90	39.00
	205-P Tube Tester	47.50	37.50
	206-P Mutual Conductance Tube Tester	83.50	67.50
	600 Oscilloscope	99.50	79.50
GRUEN	2 1/2" DC, D'Arsonval Type, 1 Milliammeter, Meter	9.95	2.95
WESTON	Model 507, F.S. 1, 2 Milliammeter, Meter	12.95	3.95
TRIPLETT	331-JP 30 Amperes, Meter	12.95	4.95
MARION	3" D'Arsonval Type, 1 Milliammeter with calibrated Volt-Ohm Current Scale, Meter	12.95	3.95
ACRO	Radio & Phonograph Chassis Cradles	6.95	2.95
GRAF-O-TONE	8" Glass Recording Discs, sold only in cartons of 24 discs	.75 each	.15
MELODISC	12" Metal Recording Discs, sold only in cartons of 50 discs	1.50 each	.30
HOLYOKE	180 Ohm resistance line cords, 6 foot with plug	1.25 each	.35
	Electrical Iron Cords, 6 foot with plug	.95 each	.25
	Extension line cords, 9 foot with plug	.75 each	.30
	Extension line cords, 12 foot with plug	.95 each	.40
	Electrical Iron Cords, 6 foot with plug and on and off switch	1.25 each	.45
	No. 22, stranded, tinned, copper push-back wire, on 500' spools	5.75 ea. spool	2.50
SUPREME	3 speed recordplayers, with life time needle portable case, speaker and amplifier	Reduced to 14.95 each	
DUOSONIC	MODEL CAPRI, 3 speed recordplayers, with life time needle, plastic case, speaker and amplifier	Reduced to 16.95 each	
WEBSTER-CHICAGO	Model Webcor, 3 speed recordplayers, with life time needle, portable case, speaker and amplifier	Reduced to 19.95 each	
MAGUIRE	Automatic Recordchanger	Reduced to 9.95 each	
TELE-TONE	Table Radio, all colors	Reduced to 9.95 each	
MOTOROLA	Table Radio, 5 tubes, all colors	Reduced to 12.95 each	
	Clock Radios, all colors	Reduced to 18.95 each	
NELSON	Electrical Waffle Iron	Reduced to 4.95 each	
	Electrical Mixer	Reduced to 4.95 each	
CUCKOO CLOCK	Genuine, imported Black Forest, hand-carved, cuckoos every 15 minutes	Reduced to 4.95 each	
GLO	Electronic, oscillating massager with infra-red heat combined	Reduced to 3.95 each	
BROIL-QUICK CHEF	Fully automatic rotisserie and broiler combination, 7 way, with time clock, 3 heat element, double powered	Reduced to 24.50 each	
CAPITOL	Infra-red heat, automatic broiler	Reduced to 9.95 each	

All prices are f.o.b. New York, 20% deposit with order, balance C.O.D., or full remittance with order. QUANTITIES ARE LIMITED. WRITE, PHONE OR WIRE FOR IMMEDIATE DELIVERY.

## METROPOLITAN ELECTRONICS & INSTRUMENT CO.

106 Fifth Ave., New York 11, N.Y. Telephone: Oregon 5-1707 Cable Address: METRONICS




## SUPERIOR

Model 1553

### Volt-Ohm-Milliammeter

Meets U.S. Army requirements for accuracy and durability. Measures AC Voltages: 0-7.5/15/150/-750. D.C. Voltages: 0 to 2.5/15/150/750. D.C. Current: 0 to 7.5/75 ma. Resistance: 0 to 5,000/500,000 Ohms. Complete with leather case, instructions.

**now only \$14.50**  
Reg. \$29.25

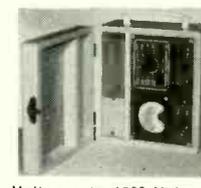

## SUPERIOR

5,000 ohms per Volt,

### Volt-Ohm-Milliammeter

D.C. Voltages to 1500 Volts, A.C. Voltages to 1500 Volts, Resistance to 2 Megohms, Output Volts to 1500 Volts, D.C. Current to 150 Ma., Decibels to plus 58 D.B. Complete with instructions and test leads.

**now only \$14.50**  
Reg. \$27.65



## TEST CRAFT

Model TC-50

### TUBE AND SET TESTER


Test all tubes up to date, incl. 4, 5, 6, 7L, octals, octals, television, magic eye, thyrtors single ended floating filament, mercury vapor, new miniatures, etc. Multimeter Specifications:

AC and DC Voltage Ranges: 0-1-100-1000-5000. DC Current Ranges: 0-10-100-1 Amp. Low Res. Range: 0-10,000 Ohms. Medium Re. Range: 0-100,000 Ohms High Res. Range: 0-1 megohm. Complete with test leads and instructions. **now only \$29.50**  
Reg. \$49.50

# E-Z WAY HURRICANE PROOF
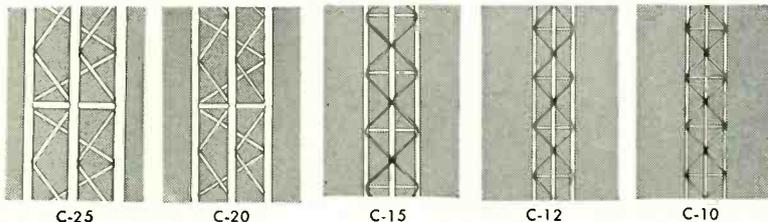
## COMMUNICATION TOWERS

Now you can have a tower that combines rugged strength with easy erection. E-Z Way Towers will stand a wind load of 40-60 lbs. per square ft. and with our new portable gin pole, it's easy to erect a 120 ft. tower in one piece. All work is done on the ground and this one shot erection method saves time, money and ends dangerous climbing. Find out about E-Z Way—the industry's new leader—now!



	C-25	C-20	C-15	C-12	C-10	C-7 not shown
Width	25"	20"	14"	10.5"	10"	6.5"
Weight per ft.	21 lb.	15 1/2 lb.	9 lb.	5.5 lb.	4.2 lb.	2.8 lb.
Max Height	400 ft.	330 ft.	230 ft.	160 ft.	120 ft.	80 ft.
Max Guy Space	60 ft.	50 ft.	50 ft.	40 ft.	27 ft.	35 ft.
Legs	2" pipe	1 1/2" pipe	1" pipe	3/4" pipe	1/2" pipe	1/2" rod
Horizontals	1 1/4" pipe	1" pipe	3/8" pipe	1/2" rod	1/2" rod	3/8" rod
Diagonals	3/4" pipe	1/2" pipe	3/8" rod	5/16" rod	5/16" rod	1/4" rod

When maximum height and guy spacing are not exceeded, towers are rated for 40 lb. wind load.

### TV TOWERS

Thousands are using E-Z Way TV Towers. Made in Florida to withstand the severest hurricanes. Patented ground post. No guy wires. Crank up and down, tilt over, for complete safety. Write for free TV Tower Catalog. No. TH

### TOWERS FOR HAMS

The answer to a ham's dream—crank up and down, tilt over. Heavy duty towers, yet easy to install and adjust antennas. Patented E-Z Way ground post. No guy wires required. Write for free Ham Tower catalog. No. HH

Write for free  
Communication  
Tower Catalog No. CH

When writing for catalog specify height of tower and type of antenna (make and model) you intend to use.

**E-Z WAY TOWERS INC.**  
5901 E. BROADWAY PHONE 4-3916  
P. O. BOX 5491 TAMPA, FLORIDA

## ELECTRONICS



Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. degree in 27 months at Indiana Technical College. Intensive, specialized course. Comprehensive training in math and electrical engineering, advanced radio theory and design, television, electronics, Modern laboratories. Low rate. Also B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical and Mechanical Engineering. G.I. approved. Enter December, March, June, September. Earn part of your expenses in Fort Wayne while studying. Write for catalog.

**INDIANA TECHNICAL COLLEGE**  
1716 E. Washington Blvd., Fort Wayne 2, Ind.

Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.

Electronics  Chemical  Aeronautical  
 Civil  Mechanical  Electrical

Name \_\_\_\_\_  
Address \_\_\_\_\_

## It's New!! It's Sensational!!

THE 1956 ALL-DIFFERENT "JUMBO  
RADIO-ELECTRONICS PARTS KIT"



Thousands of NEW & VALUABLE ELECTRONIC COMPONENTS are yours at a FRACTION OF ORIGINAL COST. You get 17 choicestful lbs. of: SWITCHES, TERMINALS, KNOBS, CONDENSERS, CONTROLS, RESISTORS, SAMPS, PHOTOFACTS, HARDWARE, SOCKETS, COILS, WIRE, PULS, DOZENS & DOZENS OF OTHER ITEMS. (SHIP. wt. 20 lbs.).....

**\$3.95**

25% Dep. Req. with order—Please add sufficient postage

**LEOTONE RADIO CORP.**  
67 Dey Street  
New York 7, N. Y.

## RADIO

routine. The time will vary from about 20 to 40 minutes; it is finished when all metal is removed from the blank areas.

Wash the acid off the piece when it is etched, then remove the dye if it has been used. The solvent for the dye is the developer which may also be used for any other cleanup of the dye, though sparingly for it is not cheap. Clean the piece of resist even if no dye was used. Kitchen cleanser can be used to save money in either case.

### Using the product

You now have a printed circuit equal in quality to any you can buy. You are not finished, however. You must drill the necessary holes. If the piece is 1/8 inch or more thick you can simply put it on the drill press or use a hand drill in the normal way. The rear may chip somewhat as the drill goes through, but that is not serious if you do not care about appearance. For professional results, however, always back the piece with wood. If you have the usual set of fractional drills, a 1/16-inch diameter hole is adequate for all the connection points. If you have drawn the concentric holes as instructed, the drill will center itself automatically.

Be very careful in drilling larger holes. Normal sizes, even as much as 3/8 inch for mounting potentiometers and the like, may be drilled. But note the tendency of phenolic to chip and work up to the final size by using a series of smaller drills. For holes to accommodate tube sockets, for example, use a fly cutter or hole saw. Do not try to use ordinary chassis punches. Phenolic can usually be punched, but not that way. To trim the piece to size, use a hacksaw with the finest teeth. A good device for this purpose if you have a drill press is a gadget like the Roto drill saw (see photo). This can be used with a drill press by adding a couple of pieces of metal in the form of a Y to keep it from rotating. The spring shown in the photo holds the pieces firmly enough to prevent rotation but slides up the post when desired.

Bare-copper printed circuits are rarely used in industry because a plated copper takes dip-soldering better, especially if the plating is solder. For hand-soldered pieces, the bare copper presents no problem at all. If you don't use it immediately, clean it before use with an abrasive kitchen powder. Use an Ungar or similar iron with a 20-watt chisel or pyramid tip. Get the foil just hot enough to make the solder flow and don't be afraid to touch the solder to the iron, despite normal practice. Too much heat will lift the foil, but normal care prevents that. The appearance of the panel (see Part I) after soldering is shown in one of the photos. The little blobs of solder at each connection point make a perfect job.


### Non-circuitry uses

Etched circuits are useful for many purposes other than simple wiring — as commutators, switches, etc. One rather


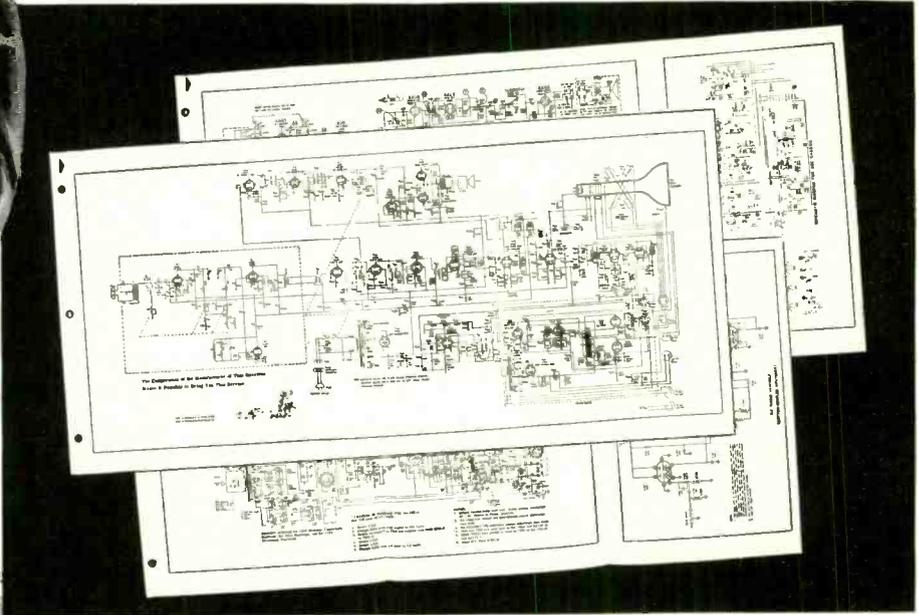
# NOW! PHOTOFAC BRINGS YOU EXTRA SCHEMATIC COVERAGE

*you get immediate coverage on leading receivers just as soon as they hit the market!*




## **IT'S AN "EXTRA" SERVICE— IN ADDITION TO REGULAR COVERAGE— AT NO EXTRA COST TO YOU**

The January issues of Sams' PHOTOFAC contain the first of a series of schematic diagrams covering the nation's top manufacturers' new model releases. Look for PHOTOFAC Sets 302, 303, and 304 at your Parts Distributor today! See for yourself how PHOTOFAC keeps you current with the present output of new TV and Radio Models. Be sure to enter your "standing order" for each new monthly release of Sams' PHOTOFAC Sets—they'll put you out ahead in service work.

**remember—you get the world's finest service data —  
you get it fastest in PHOTOFAC**

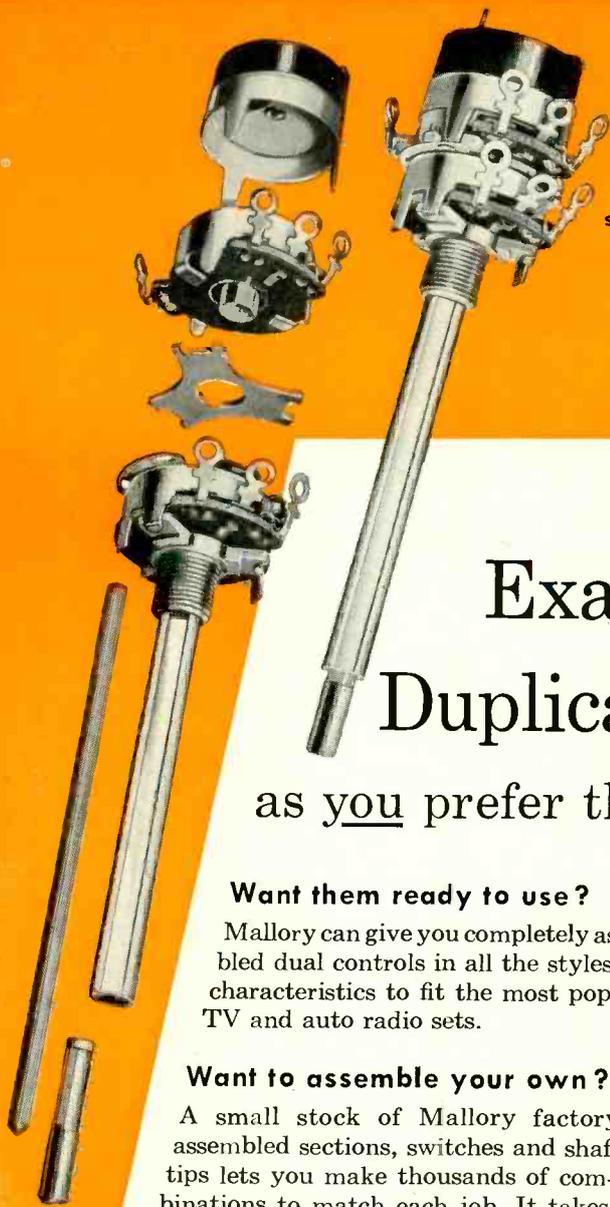**HOWARD W. SAMS & CO., INC., 2205 E. 46th St., Indianapolis 5, Indiana**



... another  
**MALLORY**  
 service-engineered  
 product

# Exact Duplicates as you prefer them

### Want them ready to use?

Mallory can give you completely assembled dual controls in all the styles and characteristics to fit the most popular TV and auto radio sets.

### Want to assemble your own?

A small stock of Mallory factory-assembled sections, switches and shaft tips lets you make thousands of combinations to match each job. It takes you only a few minutes to complete the control you need, and you save all the time of shopping for the right combination.

**You're right either way — with Mallory.** Mallory Dual Controls assure you of duplicating the exact characteristics you require . . . with noise-free, long-lasting, stable controls that assure customer satisfaction. Your Mallory distributor carries a full stock of both types. See him today!

P. R. MALLORY & CO. Inc.  
**MALLORY**

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Controls
- Vibrators
- Switches
- Resistors
- Rectifiers
- Power Supplies
- Filters
- Mercury Batteries

## RADIO

unusual use — distinctive nameplates, dials, and meter scales — gives intriguing and delightful effects.

There are several possible methods of making nameplates. For each it is necessary to make the master with the appropriate printing, writing or typing. A printer will furnish a "reproduction proof" of anything you like at very small cost, but you can save money and time by cutting out letters or whole words and phrases from magazines, using your letterhead for your name.

To make an etched nameplate simply go through the steps outlined exactly as if the master copy were a circuit drawing. This will give copper lettering on the phenolic background. However, you can have jet-black lettering on any material you like as long as it is not very porous — phenolic, any metal, chassis, rack panels and so on. To make these, carry through the process as far as development in the Photo Resist Developer exactly as though you were working on normal laminate. Then dip the piece in Photo Resist Dye, rinse with water and stop. You can use a reverse system to obtain bright metal letters on a black background simply by using a positive film (black lettering on a clear background) instead of the usual negative.

Using laminate to etch nameplates gives beautiful results — provided there are no very thin lines to reproduce. Thin lines tend to be damaged because the solution works on the unprotected edges of the letters as they are formed by etching away the background material. Thin lines are too easily obliterated in this way.

In any nameplate process, finish off the job by giving it a coating of Krylon or similar clear plastic spray to protect the dye from abrasion or to keep the copper gleaming.

Some of the materials mentioned in this article may not be easily obtainable everywhere or may be obtainable only in larger quantities than occasional experimental use warrants. A list of companies selling kits and materials in small quantities is given on page 36 of the September, 1955, issue. **END**



"These callbacks are a nuisance."

# Technicians News

## FRSAP TALKS OF UNITY

The question of unity was one of the most important discussed at the October meeting of the Federation of Radio Servicemen's Associations of Pennsylvania. After going into the matter in detail, it was resolved that the delegates take the question of joining NATESA back to their chapters or groups for discussion and approval or otherwise.

The system of self-licensing as advocated at previous meetings was another important matter taken up. The plan as proposed would be set up on a local level, but through the state federation. This was also referred back to the delegates to present to their locals for discussion.

Newsletter, plaque and lecture committees were appointed by president Bert Bregenzer, and reports on group insurance were considered.

## CINCINNATI LICENSING

A system of self-licensing is expected to take effect shortly in Cincinnati. It is sponsored by the Association of Television Service Companies and is limited to members of the association. Among the qualifications necessary for the association's license are: possession of adequate test equipment, service data and replacement parts; at least one qualified television technician; a business telephone; regular operation during standard business hours; adequate insurance on customers' property and a 90-day guarantee on parts furnished and work done.

A qualified *technician*, under the association rules, must have 8,000 hours of practical experience in TV servicing (about 4 years) and pass oral or written examinations. Alternatively, he may have 4,000 hours' experience plus credentials from an accredited service school, and pass the same examinations. A television *serviceman* will be certified if he has 2,000 hours of service and is otherwise qualified; an *apprentice*, if he has school training and 3 months' experience; a *trainee*, if he fails to qualify for apprentice. A licensing fee of \$15 per shop and \$2.50 per man will be levied.

## NEW STATE ASSOCIATION

A temporary board of 11 members was elected and a provisional constitution for a California state group ratified at a meeting held in October under the auspices of the Television Service Betterment Committee of California.

JANUARY, 1956

... another  
**MALLORY**  
service-engineered  
product



# Now Mallory Selenium Rectifiers in a convenient protective carton

Every service man who has found selenium rectifiers damaged when thrown together on a shelf or in a bench drawer will appreciate the new Mallory package. In each compact carton you get ten stacks . . . each one in a separate cut-out compartment . . . including all the mounting hardware you need.

Stacks stay in place during shipment and in your shop. They can't get chipped or bent. They're protected right up to the instant you install them in a set.

Just as the Mallory carton is a new high in convenience, so is Mallory rectifier performance a new high in service and uniformity. Mallory-developed manufacturing techniques assure you of extra long life and low forward voltage drop in every stack you use. Get your stock today, from your local Mallory distributor.

P. R. MALLORY & CO. Inc.  
**MALLORY**

P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

- Capacitors
- Vibrators
- Resistors
- Power Supplies
- Controls
- Switches
- Rectifiers
- Filters
- Mercury Batteries



Build your own

**SUPER DE LUXE  
31-TUBE  
#630 TV CHASSIS**

**#630 SUPER DELUXE 31-TUBE TV KIT**  
OPERATES 16" to 21" PICTURE TUBES. Engineered in strict adherence to the genuine RCA #630 plus added features • FULL 4MC BANDWIDTH • CASCODE TUNER • COSINE DEFLECTION YOKE • LARG. ER POWER TRANSFORMER • KEYED AGC • 12" SPEAKER • CONDENSERS and RESISTORS at rated capacities and tolerances. You receive a COMPLETE SET OF PARTS and TUBES, everything needed is included (less CRT & wire). All I.F. Coils and Transformers are factory pre-aligned and tuned. You will enjoy building it with "LIFE-SIZE" easy to follow step-by-step ASSEMBLING INSTRUCTIONS" included with each KIT.

Slashed to **\$99.99** Less CRT

Similar KIT for 24" or 27" CRT slashed to **\$110.39**

**#630 SUPER DE LUXE TV CHASSIS**

LICENSED UNDER RCA PATENTS  
COMPLETE READY TO PLUG IN AND PLAY  
Similar in features to the 16" to 21" TV KIT above.

Slashed to **\$142.27** (Less CRT)

**#630 B Y TECHMASTER**

COMPLETE LINE AT SPECIAL PRICES  
Catalog mailed on request

**STANDARD CASCODE TUNER**

For better all around performance  
Complete with tubes and Brooks CASCODE MANUAL with step-by-step instructions and all extra parts needed. **\$15.97**

**PULSE KEYED AGC KIT**

Finest, most accurate and the easiest Kit to install in any make TV RECEIVER including the No. 630. Improves performance and insures a steady picture on all channels.

COMPLETE SET OF PARTS **\$2.99**  
Including 6AU6 tube & Instructions

**FLYBACK TRANSFORMER**

This is the most terrific new sensation in Flyback Transformers. It is similar to the popular No. X-053 and goes up as high as 16KV. With it you receive easy-to-follow instructions and schematic diagrams that apply to improve practically all makes of TV Receivers. **\$4.86**

**COSINE DEFLECTION YOKE**

The latest achievement in the 70° type, with complete wired network. Will add new life to any TV Set. In brilliance, clarity and sweep. This is the same type we supply with our Kits, with it you receive easy-to-follow instructions and diagrams. **\$4.92**

**18KV FLYBACK TRANSF.**

This new Flyback Transformer now makes 90° conversions easy on any make TV Set. Customers report excellence on 24" and 27" TV Sets built or converted with this Transformer. Instructions and schematic diagrams included. **\$5.24**

**COSINE DEFLECTION YOKE**

NEW 90° TYPE, with complete wired network. It solves all problems formerly sought for, in 90° Yokes for undistorted clear pictures and ease of overall sweep. Instructions and schematic diagrams included for building, replacing and converting. **\$5.98**

**MICA & CERAMIC CONDENSERS**

Values up to 85c each  
5, 10, 51, 56, 82, 100, 120, 150, 220, 270, 330, 390, 470, 510, 680, 1000, 1200, 1500, 3900, 6800 MMF. Your choice **5c** each

Brooks LIFE-SIZE TV INSTRUCTIONS for building any #630 TV Receiver from the original 10" to the latest 27" **\$1.25** postpaid

90° TV CONVERSION MANUAL, how to convert any TV SET to 24", 27", etc. **50c** postpaid


**CUSTOM-BUILT CABINETS FROM FACTORY TO YOU**

**3 LEADING 1956 STYLES** in genuine Mahogany or walnut (blond) 100% extra ready drilled for any #630 TV chassis and cutout for any 16", 17", 19", 20" or 21" picture tube at no extras in price. Also supplied with undrilled knob panel for any other TV set. EVERYTHING NECESSARY for an easy perfect chassis and CRT assembly is included. Each cabinet is delivered complete as pictured with mask, safety glass, mounting brackets, backboard, backcup, hardware and assembling instructions. Each cabinet is shipped in an air cushioned carton from FACTORY to YOU!


**WESTCHESTER \$88.70**

**MANHATTAN \$53.43**

**GEM \$35.91**

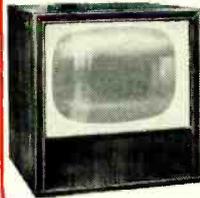

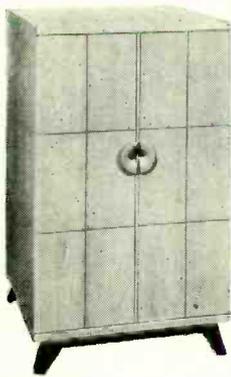**GEM** also available for 24" or 27" picture tube **\$59.54**



**MANHATTAN** also available for 24" or 27" picture tube **\$79.22**



**DUMONT OR THOMAS PICTURE TUBES**

BRAND NEW in Factory Sealed Cartons — With a Full Year Guarantee

17" #17BP4A **\$22.66** | 21" #21EP4B Aluminized **\$32.21** | 24" 90° #24EP4A Aluminized **\$48.99** | 27" 90° #27EP4A Aluminized **\$74.31**

**21" TV CONVERSION KIT**

Positively the HOTTEST item in CONVERSIONS. Customers tell us they even use it to bring a 21" Set up-to-date for greater power, brilliancy and clarity.

Convert ANY MAKE TV RECEIVER including #630 to operate the 21" or ANY 70° PICTURE TUBE

COMPLETE SET OF ESSENTIAL PARTS includes matched set of Todd 70° COSINE DEFLECTION YOKE and TODD HV FLYBACK TRANSFORMER


List Price **\$33.50**

Your price... **\$13.97** incl. CONVERSION MANUAL with Step-by-Step Instructions & Diagrams.

Similar Kit for 24", 27" or any 90° CRT **\$15.98**

**UNIVERSAL PICTURE TUBE MOUNTING BRACKETS**

Fits All 12 1/2" to 21" picture tubes

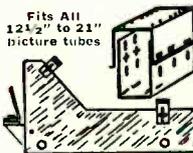

Complete — Including band that holds picture tube **\$4.97**

**#630 TV BASIC PARTS KIT**

PUNCHED & DRILLED CHASSIS PAN  
BRACKET & SHIELD KIT (18 items)  
VIDEO & I.F. KIT (19 items) All for Only  
POWER TRANSFORMER #20IT6 **\$29.97**  
VERTICAL OUTPUT TRANSFORMER  
VERTICAL BLOCKING TRANSFORMER  
FLYBACK TRANSFORMER #21IT5 Including Instructions  
FOCUS COIL, 470 ohms #202D2  
COSINE DEFLECTION YOKE 70°

**#630 Parts in COMPLETE SETS**

TV WIRE & SOLDER KIT, for any Set... **\$ 1.98**  
630-KIT, screws, nuts, rivets, washers, etc... **1.69**  
VIDEO AND I.F. KIT, 19 items... **4.99**  
VARIABLE CONTROL KIT, 9 controls... **3.97**  
CARBON RESISTOR KIT, 107 resistors... **4.98**  
WIREWOUND RESISTOR KIT, 4 resistors... **1.76**  
ELECTROLYTIC CONDENSER KIT, 6 cond... **4.96**  
TUBULAR CONDENSER KIT, 38 condensers... **3.63**

HINTS FOR BETTER PERFORMANCE **50c** postpaid on your #630 TV receiver.

70° TV CONVERSION MANUAL, how to convert any TV SET to 17", 21", etc. **50c** postpaid

**SELENIUM RECTIFIERS**

65 ma. . . . \$ .46	250 ma. . . \$1.08
75 ma. . . . .49	300 ma. . . 1.19
100 ma. . . . .62	350 ma. . . 1.26
150 ma. . . . .74	450 ma. . . 1.42

**PM SPEAKERS (ALNICO #5)**

Brand New Factory Guaranteed Stock  
1 oz. mag. on 3" to 6", heavier mag. on 8" & 12"

3" . . . . . \$ .98	6" . . . . \$1.58
4" . . . . . 1.17	8" . . . . 2.64
5" . . . . . 1.29	12" . . . . 4.67

**TUBULAR CONDENSERS — 85°C**

TOP QUALITY — Equally as good for TV or Radio Work. Example of value we offer . . . . . #047-600v lists at 36c

.005-400v . . . . 4c	.047-600v . . . . 9c
.01-400v . . . . 5c	.1-600v . . . . 12c
.02-400v . . . . 5c	.25-600v . . . . 14c
.047-400v . . . . 7c	.001-1000v . . . 11c
.1-400v . . . . 9c	.01-1000v . . . 14c
.25-400v . . . . 12c	.035-1000v . . . 16c
.005-600v . . . . 7c	.05-1000v . . . 18c
.01-600v . . . . 8c	.1-1000v . . . 22c
.02-600v . . . . 8c	.5-400v . . . . 28c

**CARBON RESISTORS**

Regular factory stock in. Stackpole, I.R.C. Sner. Order any ohmage from 2.2 ohms to 10 meg in the desired tolerance. Deduct 10% on lots of 100 or over.

1/2 WATT, 5% . . . . 5c	10% . . . . 4c	20% . . . . 3c
1 WATT, 5% . . . . 6c	10% . . . . 5c	20% . . . . 4c
2 WATT, 5% . . . . 9c	10% . . . . 7c	20% . . . . 5c

**ELECTROLYTIC CONDENSERS — 85°C**

40/10/80 mfd—450/450/150v . . . . . \$1.37	
40/40/10 mfd—450/450/450v . . . . . 1.49	
80/50 mfd—450/50v . . . . . 1.49	
40/10/10 mfd—450/450/350v . . . . . 1.37	
20/80 mfd—450/350v . . . . . 1.49	
250/1000 mfd—10/6v . . . . . .98	
20 mfd—150v . . . . . 27c	8 mfd—450v . . . . 26c
20/30 mfd—150v. 38c	20 mfd—450v . . . 42c
50/30 mfd—150v. 39c	30 mfd—450v . . . 49c

Brooks CASCODE MANUAL, how to install Cascode Tuner in any make TV Set. **25c** postpaid

A.G.C. STEP-BY-STEP INSTRUCTIONS, how to add A.G.C. to any make TV Receiver **25c** postpaid

**BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y.**

TELEPHONE  
CORTland 7-2359

RADIO-ELECTRONICS

The meeting was held in San Jose, with the Radio Television Association of Santa Clara Valley (RTASCV) as hosts. It was the third organizational session under the sponsorship of the committee; the first session was held last May.

Chairman Thomas Lawson of the TSBCC, acting chairman of the new group, stated they hoped to file articles of incorporation before the end of 1955 and to be ready for election of full-term officers and all other association activities before May.

**A NEW PAPER**

We have just received Vol. I, No. 1, of *RTA*, official publication of the Radio Television Association of Santa Clara Valley (Calif.). The new magazine is an attractive 6 x 9-inch, 16-page publication. Unlike many technician's journals, it is thoroughly advertising-conscious and presents itself as "a direct approach to the Valley's top dealer-service organization group . . . a highly flexible medium that will bring big returns to our advertisers." Direct results are three full-page ads (including the front cover) and several smaller ones.

Most interesting of the editorial features are an account of cooperation with station KNTV; a report on the state unity meeting; the RTASCV Standards of Practice, which includes a 16-item code of ethics, an editorial by the president of the association, H. Lawrence Schmidt.

**OHIO STATE GROUP**

A state TV service association for Ohio was formed at a November meeting in Columbus. It will be known as TESA (Television Electronic Service Association) of Ohio, and will be affiliated with the National Alliance of Television Electronics & Service Associations (NATESA).

Richard E. Miller, Sr. of Cincinnati was elected president; Marvin A. Miller of Springfield, Vern V. LaPlante of Toledo and Harry L. Hakes of Hillsboro, vice presidents; John T. Graham of Columbus, secretary-treasurer. The organization is expected to represent about 16 local groups.

**L. I. HAS DISTRIBUTORS**

The Long Island Guild informs us that they were in error in the statement that there is no bona fide Sylvania distributor in their territory. This statement was made in a letter to Sylvania, an abridgment of which was published in our December, 1955, issue on page 115.

The guild apologizes to Long Island Electric and Melville Radio, two distributors who have been cooperating with the guild program. The fact that they were Sylvania distributors was accidentally overlooked at the time the letter was written, the guild report stated. **END**



because Sangamo Telechief Capacitors still outperform all other paper tubulars

What do we mean when we say Sangamo Telechief Capacitors outperform all other molded paper tubulars?

Simply this: When it comes to moisture resistance . . . optimum operation in high temperatures . . . when it comes to holding rated capacity under all conditions, the Sangamo Telechief wins hands down.


Tests by major manufacturers and branches of the Armed Services—not our tests—have proven that Telechiefs outlive

all other molded tubular capacitors . . . that they have a final insulation resistance 10 to 15 times greater than any other paper tubular because they're molded in HUMIDITITE . . . the remarkable plastic molding compound developed by Sangamo.

HERE IS TRULY EXTRA VALUE AT NO EXTRA COST! Best of all, Telechief, the biggest value in molded paper tubulars, is available to you at the price of an ordinary capacitor.

SC55-9

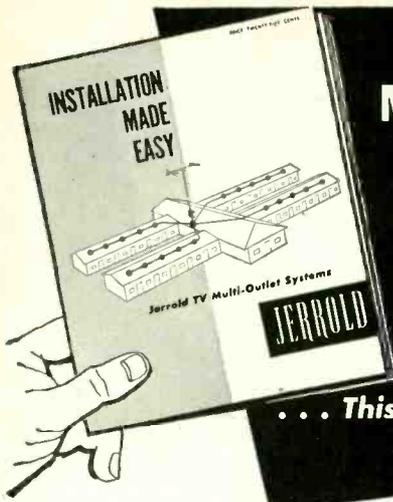**SANGAMO ELECTRIC COMPANY**  
MARION, ILLINOIS



# MAKE BIG MONEY SELLING MASTER TV SYSTEMS

... This Handy Guide Shows You How!

Cash-in on television's fastest growing market by selling master TV systems to motels, apartments, clubs, schools, and hotels. This big, data-packed booklet explains every step . . . from making cost estimates of each job and selling an installation to laying-out the system, calculating DB gain and loss, locating and installing equipment, maintenance, servicing, and much more. Every calculation is figured out for you—no complicated mathematics needed. Over 35 helpful photos, charts, diagrams, and schematics make things doubly easy to understand.

Learn how you can sell distribution systems in your area and boost servicing and TV set orders in the bargain. Send 25 cents for your copy of the Jerrold booklet, "Installation Made Easy." Use coupon below!


## The JERROLD TV Multi-Outlet SYSTEM



Distribution  
Amplifier



Line Splitter

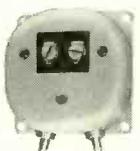

Line-Tap  
Impedance Matcher

### SEE WHAT THIS VALUABLE BOOKLET CONTAINS

Selling Multi-Outlet Systems • On-the-Spot Proposals • Distribution Amplifiers • Mixing Networks • Signal-Splitting Networks • Line Taps • Antennas • System Layout • Dollars & DB • What Amplifier Ratings Mean • Overcoming Cable Losses • Tap-Off Theory • The "Break-Even" System • Cascading Amplifiers • Mounting Equipment • Balancing & Adjusting Systems • Maintenance • Servicing Systems • Constructing Baluns • etc.



**JERROLD ELECTRONICS CORP., 23rd and Chestnut Sts., Phila. 3, Pa.**

Gentlemen:

Please rush \_\_\_\_\_ copies of your new booklet, "Installation Made Easy." I enclose 25 cents for each copy (35¢ outside U.S.A.)

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_



Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

### Spotlight on Percussion

Arnold Goldberg and Kenny Clark  
Vox DL-180

This Vox entry in the percussion sweepstakes has one fault: the voice narration is too loud for the level at which the record must be played. This is the more unfortunate because this excellent recording possesses many subtle nuances with high test value in weeding out merely fine from superb high-fidelity systems.

Extremely clean and well defined, it has a truly fine transient response. The drums are not particularly bigger or deeper, but the delicate qualities of the instruments are defined with great clarity and faithfulness. The rapid rolls of traps, drums, temple blocks, castanets and guiro (gourd with scraper) are highly exceptional test material for transient response; the individual staccato pulses are distinct even in the most rapid bursts. Any tendency to blur them indicates poor transient response, an unstable amplifier or speaker hangover.

The record will sound pretty good on just about any system worthy of the high-fidelity label; but there are several sure-fire measures of genuine response below 30 cycles and very severe tests of rumble, hum and overall noise figure. In the marimba passage an underlying rumble consists apparently of beat notes, striking transients, possibly a touch of mike blast and very likely a touch of tape-recorder flutter. On a system responding below 30 cycles this produces a sound as of a heavy and near diesel train. To some degree the same effect is found in the vibraphone passage. In other portions, where the gain was boosted in cutting the master, the tape-recorder flutter is plainly audible—provided the playback system has an extremely low noise figure. Finally, a faint groove-echo (or possibly tape print-through) in several spots ahead of the voice (perhaps 50 or 55 db down) will be audible only on systems with superb noise figures.

Xylophone and castanet transients are very well defined but if the system goes far enough down one can hear a touch of mike blast produced by the violent attacks. The curious "spit" of the whip (actually a mouse-traplike arrangement of two wooden blocks) is excellently reproduced. The very fine definition of the multi-track recording of *Anchors Aweigh* and the other selections by Goldberg and Clark provides exceptional material for testing playback definition. The accompanying booklet (by R. D. Darrell, Ward Botsford and Rudolph Van Gelder) does a fine job of covering the various musical and sound aspects. Teachers of music, as well as audiophiles, will find this a most useful recording.

### Easy Listening Vol. 3

Red Daugherty Sextette  
Audiophile AP-27 (AES)

Set your equalizer for AES bass and a flat or -6-db treble (the EUR curve isn't bad either), raise the volume so the piano is about as loud as it would be in your room and you can measure how far short your hi-fi system is of the best possible by measuring how far short of actually being there the effect is.

Assuming that your system is capable of producing a true "being-there" effect you can demonstrate that response above 10 kc is essential for realism by playing this with and without a 10-ke cutoff. A good part of the illusion is produced by the remarkably clean and sharp traps which require a very fine transient re-

(Continued on page 154)

# LEARN MORE! EARN MORE!

## WITH H. G. CISIN'S TV SERVICE BOOKS

### Facts About "SHOOT TV & RADIO TROUBLE FAST"

This newest Cisin book was written in response to the demands of thousands of radio-television servicemen. Mr. Cisin, inventor of the AC-DC radio circuit, has adapted his famous streamlined trouble shooting method to servicing of AC-DC radios, in the only book which combines both TV and radio trouble tracing. **SHOOT TV & RADIO TROUBLE FAST** also contains a section on **PRINTED CIRCUIT SERVICING**, of vital interest to all servicemen.

### FACTS ABOUT THE AUTHOR

H. G. Cisin, technical author and publisher, is also well-known as a radio and television inventor, electronic consulting engineer and educator.

Holder of six U.S. patents, perhaps the most famous of his inventions is the basic AC-DC circuit which makes present-day small radios possible. Among the concerns he has licensed under his patents are: RCA, AT&T, W.E. Co., Bell Telephone Co., and many others. He is also the inventor of the 3-way portable radio and of other important television and radio devices. He is the author of many technical books and also of hundreds of radio & TV technical articles.

Mr. Cisin learned practical television servicing the hard way by actually working at a test bench on hundreds of faulty TV sets. He has trained thousands of technicians, many now owning their own prosperous TV service concerns, or holding highly paid TV positions. A graduate of Cornell University, he has concentrated on teaching television and radio to men with little formal education. His years of study, practice and experience are embodied in his radio and television service books.

### WHAT TV SERVICEMEN & TECHNICIANS SAY ABOUT CISIN BOOKS

Send another copy. Have one, but am afraid I might mislay it. Can't afford to be without it.

As TV instructor, writer and technician, I can fully appreciate this fine book.

Enormously pleased with results obtained by using your book. Hasn't failed me yet.

Your book has taken the mystery out of TV servicing. Better than any book on the subject I have ever seen, but still the lowest priced.

Your book has helped me tremendously. Hold a top bench job with one of the largest servicing organizations here.

Please send me another book. Lent my copy to a friend, also a TV serviceman, and can not get it back. We both think it's great.

Unable to see how you can give so much for so little. Paid three times as much for other TV service books which didn't contain 1 percent of the information in your book.

Clear, concise handling of a complicated subject in a way the average serviceman can easily grasp it.

Hundreds of similar letters in our files.

### SHOOT TV & RADIO TROUBLE FAST



**NEW!** A complete section on Rapid Trouble Shooting of AC-DC radio sets combined with new edition of Rapid TV Trouble Shooting Method. Enables you to locate radio & TV faults in record-breaking time, regardless of make or model.

**Quickest Radio & TV Trouble Shooter—**  
No. T2.....\$1.50

### RCA TV MODELS



### 1947 to 1955 TUBE LOCATION GUIDES

Most complete compilation of RCA Trouble Indicating Tube Location Guides ever produced. Contains hundreds of RCA models from earliest 1947 sets to latest 1955 models including Color TV.

Each guide shows positions of all tubes and also by a copyrighted method indicates effect of each tube on operation of TV set. Scraps old-style fine-print function names such as AGC Gate, Sync Clip, Vert. Mult., etc. Instead tells plainly what each tube actually does. Tubes affecting picture are marked "P," sound "S," horizontal sweep "H," etc.

**Fits Every Tube Caddy—No. A1...\$1**

### TV DOCTOR



How to Diagnose and Remedy TV Troubles; Useful Info About TV Sets; Easy Trouble Checks; UHF Servicing; Antenna Know-How; Servicing Hints; Color TV; Troubles Due to Defective Tubes; How to Read Schematic diagrams. Practical hints for prospective TV servicemen.

**Beginner's Best Buy—No. D5.....\$1**

### NEW! TV & RADIO TUBE SUBSTITUTION GUIDE



Contains tube replacements for TV sets, radios and other electronic devices. All fit same socket and **NEED NO CHANGES IN WIRING**. Also contains complete data on

### TV PICTURE TUBE

replacements, many directly, others with only slight changes.

**Substitute with Certainty**  
No. S1.....Only 50c

### ABC OF COLOR TV

Takes mystery out of Color TV. Explains this fascinating new TV development in simple down-to-earth manner. Translates technical descriptions of research scientists into plain language. Covers basic color principles, color signal, transmission, color TV reception, plus practical pointers on color pix tubes, tests, etc.



**Color TV Simplified—No. R1.....\$1**

### TV CONSULTANT

**NEW**, easy to use way to solve toughest TV troubles. UHF and COLOR TV sections included. Modern alignment methods clearly shown, tell exactly **WHAT** to do and **HOW** to do it. Practical pointers on the use of all TV TEST INSTRUMENTS. Over 300 pix, raster and sound symptoms. Detailed directions tell where and how to find faulty parts. Over 135 **RAPID CHECKS**, many using pix tube as trouble locator. 125 illustrations of scope wave forms, diagrams, station patterns, show various defects. **NO THEORY—NO MATH—NO FORMULAS**—just practical service info covering all types of TV sets.



**TV Serviceman's Silent Partner**  
No. L1.....Only \$2

### TV TUBE LOCATOR

**TROUBLE INDICATING TUBE LOCATION GUIDES** over 3000 most popular models. Admiral to Zenith.

Shows PIX tubes used in many models. Covers products of over 110 different TV manufacturers. Over 135 common TV troubles are listed with explicit directions for locating defective tubes which cause each fault.



**Speed Servicing—No. K1.....\$1**

### NEW! TROUBLE SHOOTING PIX GUIDE incl. TV TERMS EXPLAINED

Each vol. has different TROUBLE INDICATING TUBE LOCATION GUIDES of hundreds of popular TV models. Each has over 70 illust. & Guides. 40 most common pix troubles illustrated.



**Pix Show Faults—No. G1.....\$1**

### TV TROUBLE TRACER

Each vol. has different TROUBLE INDICATING TUBE LOCATION GUIDES of hundreds of popular TV models. Each has over 70 illust. & Guides. 40 most common pix troubles illustrated.



Vol. 1 (No. TT1) older models;  
Vol. 2 (No. TT2) 1952-1953 sets;  
Vol. 3 (No. TT3) 1953-1954 sets;  
Vol. 4 (No. TT4) 1954-1955 models.

**Find It & Fix It.....Each Vol. 50c**

### RAPID TV TROUBLE SHOOTING METHOD

This unique servicing method has helped thousands to become expert TV diagnosticians. Pix, raster & sound troubles are listed and given code numbers. When these are combined they tell exactly where trouble exists. Then step-by-step directions enable you to find faulty part.



**Easy To Use—No. T1.....\$1**

**FREE: TV & RADIO TUBE  
SUBSTITUTION GUIDE**

with every purchase of \$5 or over

**FREE: TV & RADIO TUBE  
SUBSTITUTION GUIDE**

plus **TV TROUBLE TRACER, Vol. 4**  
with every purchase of \$8 or over

IF JOBBER IS OUT OF STOCK MAIL "NO RISK" TRIAL ORDER COUPON  
5-day Money Back Guarantee!

H. G. CISIN, Dept. E-37 AMAGANSETT, N. Y.

Enclosed find \$..... RUSH POSTPAID following books:

L1—\$2     D5—\$1     T2—\$1.50     TT2—50c     S1—50c    Order \$5 or over    Order \$8 or over  
 A1—\$1     G1—\$1     T1—\$1     TT3—50c     INCLUDE     SEND BOTH  
 K1—\$1     R1—\$1     TT1—50c     TT4—50c     FREE S1     FREE BOOKS

Name .....

Address .....

City .....

Zone.....State.....

sponse above 10 kc to be reproduced sharply and cleanly.

Aside from the notable high-highs there is a very nicely damped drum, a gutty double bass and easy-listening music (*Tailgate Ramble, I Never Knew, Some of These Days, Sheik of Araby, Ain't She Sweet*, etc.). I consider *Tailgate Ramble* one of the very finest showoff pieces available. To demonstrate good hi-fi or simply to enjoy some fine jazz, well-played and wonderfully recorded, this is required listening in my book.

#### Traditional Jazz Vol. 4

Doc Evans and Band

Audiophile AP-29 (78-r.p.m. micro-groove, AES bass, flat treble)

E. D. Nunn considers this the finest disc he has produced. Its high quality is less obvious and it doesn't have the peculiarly special demonstration value of AP-27, but it presents the jazz of the 'Twenties (*That's a Plenty, London Blues, Eccentric Blues* and *Bye and Bye*) with such faithfulness—both the music and original styles—and so complete an illusion of presence that it is enough to make anyone who lived the jazz age cry into his near-beer with nostalgia. Extremely fine tuba and drums.

#### Cornet Artistry

Doc Evans and Band

Audiophile AP-31 (AES)

More very fine and very real, mostly Chicago style, jazz featuring the silver-smooth, plaintive Doc Evans cornet in *Linehouse Blues, Don't Worry About Me, Melancholy Baby, Memories of You, Just a Gigolo, Old-Fashioned Love* and *Stars Fell on Alabama*, but offering also some fine drums and double bass, very fine wood-blocks, sharp percussive traps and handclapping. Very good test material for pickups and needle condition. If with AES equalization the cornet sounds at all strident, chances are the pickup has a peak or the needle is poor. With flat pickup and a good needle there should be little or no unnatural stridency even with flat treble.

#### Sounds of the Boudoir ERA EI 50001

Cook's *Burlesque* proved that when it comes to striptease the ear is no substitute for the eye, and this clinches the proof. It tries to bring a "Hollywood model's boudoir" to the living room and is supposed to "tell in sound how a lovely actress wakes up in the morning and a red-headed model goes to sleep at night." Eliminate the narrator's leering, smirking voice and the sounds might as well be ascribed to a greasemonkey washing, polishing and cleaning a car. The only thing the recording will test is the listener's gullibility, suggestibility and imagination.

#### HAYDN: *Missa Solemnis* (Lord Nelson Mass)

Vienna Academic Choir and Vienna State Opera Orchestra conducted by Mario Rossi Vanguard VRS-470

#### SPELLMAN: *The Vigil of Venus*

Vienna Academic Choir and Vienna State Opera Orchestra conducted by Zoltan Fekete MGM E-3085

Clearly among the busiest in the world, these two musical groups appear not only on these labels but several others and do a fine job for all of them. The combination of voices and orchestra can provide a spectacular demonstration of hi-fi and either of these records will do the job. The Haydn mass is especially notable for its unique scoring for strings, kettle drums and trumpets and is far more satisfying as music. If one forgets it is a mass, the general effect is rather like that of Beethoven's *Ninth* but much easier to take. The recording is very fine.

Spellman is an obscure American composer circa in the Twenties and Thirties and this is one of his most ambitious works. There is nothing remarkable about either the music or the hi-fi qualities, but the overall effect, played fairly loud, can be very imposing. END

Names and addresses of manufacturers of any items mentioned in this column may be obtained by writing Monitor, RADIO-ELECTRONICS, 25 West Broadway, New York 7, N.Y.



# 666 VOM


THE 666 IS THE ONLY  
VOM THAT OFFERS ALL  
OF THESE FEATURES

The MODEL 666 VOM is a completely self-contained, ready-to-use test instrument. Its accessories, probes, AC line cord (which serves to illuminate the dial) and instruction book all fit into the genuine California Saddle Leather carrying case that is furnished with the instrument.

### METER MOVEMENT PROTECTION AND FUSED OVERALL INSTRUMENT PROTECTION

- 43 Unduplicated Ranges
- AC Current Ranges
- Separate Range and Function Switches
- Only 2 Jacks for all Measurements
- Illuminated Dial (5000 hour self-contained lamps)
- Large, Easy-to-Read Scale 4 7/8" long
- Color Coded Scales: green—ohms; black—AC-DC volts, DC current; red—AC current; blue—output
- Die Cast Chrome Bezel
- Metal Case, unbreakable, ultra-compact
- Doubly Shielded, time proven 50 microamp movement
- Permanent Accuracy... 3% DC, 4% AC
- New High Style, Easy-to-Use Chrome Bar Knobs
- Dual Purpose Handle also serves as AC line cord reel

YOUR KEY  
TO  
EXCELLENCE

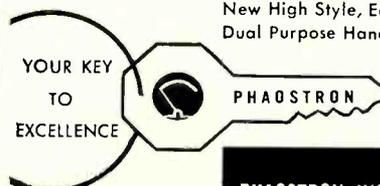

Complete with Probes,  
AC Line Cord and Leather Case  
at your PARTS DISTRIBUTOR


**\$59<sup>50</sup>**

PHAOSTRON INSTRUMENT AND ELECTRONIC COMPANY

151 PASADENA AVE., SOUTH PASADENA, CALIF.
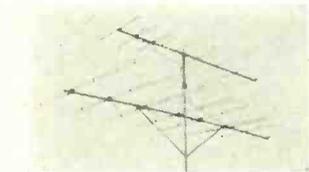
# new Devices


**ANTENNA, K.O.** Front-to-back ratios from 20:1 to 50:1 relative voltage on low band; to 13:1 on high. High gain characteristics from 7 to 9 db on low band, 8.5 to 10.5 db on high.



(Figures for single bay.) K.O. is driven end-fire array of two individual antennas.

*Model 1026* (6 driven elements covers channels 2-6; *model 1073* (2 driven elements) channels 7-13; broadband *model 1023* entire v.h.f. band.—**Channel Master Corp.**, Ellenville, N. Y.

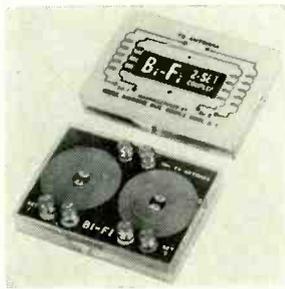
**2-SET COUPLER, Bi-Fi 2-Set Antenna Coupler**, for connecting two TV or FM sets to a



common antenna. Provides high audio and video signal transfer. Improves matching, reduces ghost and interest interference. Bifilar printed circuit construction. Polystyrene case eliminates losses due to impedance changes. Mounts in any convenient location between sets or near or behind one set.—**Federal Electronics Sales**, Federal Electronics Bldg., Rockville Centre, N. Y.

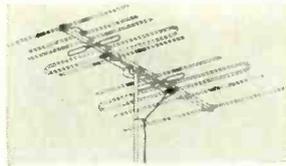
**V.H.F. ANTENNA, Finco Twin-**

**Driven model B-8 Geomatic.** Very high front-to-back ratio eliminates venetian blinds, back ghosts, etc. No sacrifice of gain on low or high bands. Multiple



reflectors and directors, including combination and collinear elements, produce sharp directivity normally found only in Yagis cut for single channel.—**Finney Co.**, 4612 St. Clair Ave., Cleveland 3, Ohio.

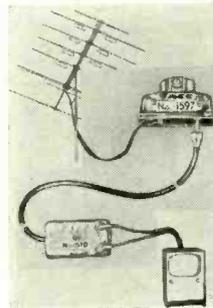
**COAXIAL TV COUPLER Taco models 1597 and 1570** permit use of 72-ohm coaxial cable as TV lead-in to reduce man-made static and running antenna lead without regard to proximity to metal gutters, etc. *Model 1597* matches antenna to 72



ohms and *1570* matches 72-ohm lead to 300-ohm receiver termi-


nals.—**Technical Appliance Corp.**, Sherburne, N. Y.

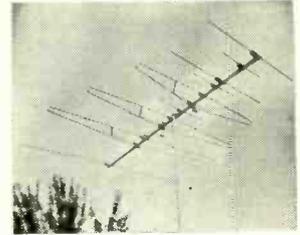**TV ANTENNA, Zephyr Royal**, stagger-tuned to 6 pre-determined frequencies—channels 2, 4, 6, 7, 10, 13—giving flat re-



sponse over v.h.f. band. Optimum phasing for maximum forward gain.—**Trio Mfg. Co.**, Griggsville, Ill.

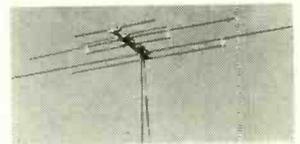**TV ANTENNA, Color-Beam**, unfolds like an umbrella. Elements snap and lock into place



automatically. Support mast and one end of lead-in wire attached to antenna. Other end of wire has clip for fastening screws on back of set.—**Winegard Co.**, Burlington, Iowa.

**20-WATT AMPLIFIER, model**



Get This Valuable Book

# FREE



Yes, you get this big, brand new book, "150 Radio-Television Picture Patterns and Diagrams Explained", absolutely FREE! Just off the press! Gives complete 11x22" Schematic Diagrams on leading models Radio and Television Sets. Easy-to-read, large 8½x11" pages, with full instructions on how to read and use the diagrams. A "must" in every Radio and Television service-man's repair kit. You get this valuable book as a FREE Gift for asking to see Coyne's great new 6-book set, "Applied Practical Radio-Television"!

**At Last! Money-Making "Know-How" on Transistors, Color TV and Servicing**

Coyne's great new 6-volume set gives you all the answers to servicing problems—quickly! For basic "know-how" that is easy to understand, you'll find everything you want in volumes 1 to 5 which contain over 5000 practical facts and data. They cover every step from principles to installing, servicing, trouble-shooting and aligning all types of radio and TV sets. So up-to-date it includes COLOR TV and UHF, adapters, converters. Also covers latest data on TRANSISTORS.

**Extra! 900-Page Television Cyclopedic Included**

And then, for speedy on-the-job use, you get volume 6—the famous COYNE TELEVISION CYCLOPEDIA. It answers today's television problems on servicing, alignment, installation and others. In easy-to-find ABC order, cross indexed. Use this 6 volume TV-RADIO LIBRARY free for 7 days; get the valuable Servicing Book ABSOLUTELY FREE!


Educational Book Publishing Division

**COYNE ELECTRICAL SCHOOL**  
500 S. Paulina St., Dept. 16-T1, Chicago 12, Ill.

Just for Examining COYNE'S New 6-Volume Set

# "Applied Practical Radio-Television"

ON 7 DAY  
FREE  
TRIAL!

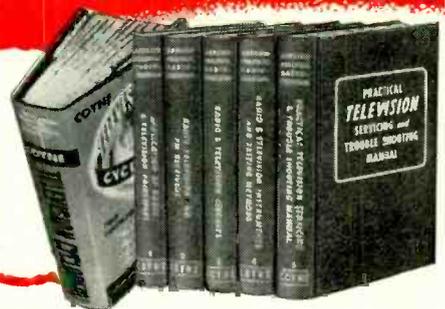

**SEND NO MONEY!** Just mail coupon for 6-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$2 in 7 days and \$2 per month until \$22.50 plus postage is paid. (Cash price \$20.95). Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE.** Either way, the book of TV-Radio Patterns is yours FREE to keep! Offer is limited. Act NOW!

**FREE BOOK—FREE TRIAL COUPON!**

Educational Book Publishing Division

**COYNE ELECTRICAL SCHOOL, Dept. 16-T1**  
500 S. Paulina St., Chicago 12, Ill.

YES! Send 6-volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.


Name ..... Age .....

Address .....

City ..... Zone ..... State .....

Where Employed .....

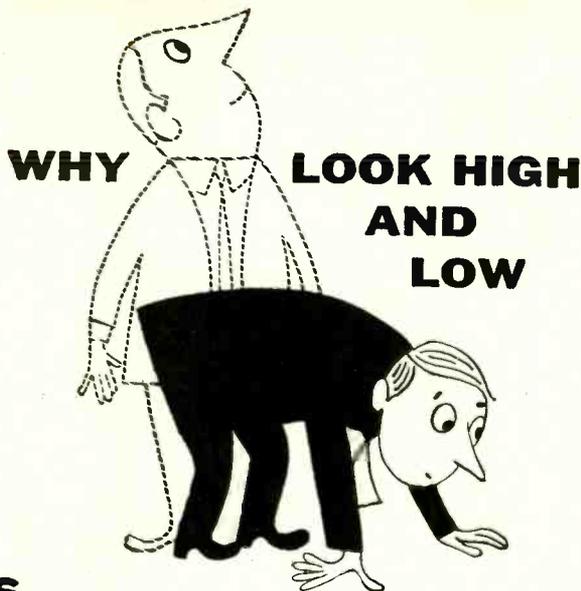( ) Check here if you want library sent COD. You pay postman \$20.95 plus COD postage on delivery. 7-day money-back guarantee.



## C-D IS THE ONLY COMPLETE LINE OF ELECTROLYTICS

No matter what you need in electrolytic capacitors—C-D has it. Every type, shape and rating . . . all of consistent high quality proven by outstanding field performance. C-D capacitors are always reliable . . . and readily available—because Distributors *who know*, carry the complete Cornell-Dubilier line.

Free! TV Capacitor "Replacement Guide"—and C-D Twist Prong Cross Index from your C-D Distributor. He's listed in your local Classified Telephone Directory.

C-D's "Up" twist prong



There are more C-D capacitors in use today than any other make.



## CONSISTENTLY DEPENDABLE CORNELL-DUBILIER CAPACITORS

PLANTS IN SOUTH PLAINFIELD, N. J.; NEW BEDFORD, WORCESTER AND CAMBRIDGE, MASS.; PROVIDENCE AND HOPE VALLEY, R. I.; INDIANAPOLIS, IND.; SANFORD AND FUGUAY SPRINGS, N. C.; SUBSIDIARY: THE RADIART CORPORATION, CLEVELAND, O.

## SERVICE TECHNICIANS . . .

# MAKE UP TO 50% MORE MONEY!

\$\$\$\$\$\$\$\$\$\$\$\$\$\$\$\$

Take home more money than ever before . . . increase your business . . . handle jobs faster and easier! For the first time, you can quickly figure out even the toughest servicing problems . . . know all the short cuts, all the latest technical information . . . have the world's smartest experts working for YOU!

Never before has every phase of servicing been covered in such practical, easy-to-understand language—with complete and detailed diagrams! Now you can have the advice of experts in the handy, beautifully bound, hard-cover books of the GERNSBACK TECHNICIANS LIBRARY . . . you will own such books as the V.T.V.M., written by Rhys Samuel, RCA test instrument engineer and technical writer. The up-to-the-minute book that gives you dozens of new uses for the Vacuum-Tube Voltmeter . . . tells you how to pin-point hidden trouble spots in seconds . . . gives you all the info to make better and more efficient use of this "electronic workhorse".

Other books we will send to you every three months for your FREE trial include: RAPID TV REPAIR, SERVICING AUTOMATIC RECORD CHANGERS, SERVICING COLOR TV CIRCUITS, LOCALIZING TUBE TROUBLES, and many many more.

### And You Can Save 25%

You may buy any of these books at the low retail price of only \$4.00. OR, as a member of the Library Plan you pay the special member's price of only \$3.10—YOU SAVE 25%

### How the Library Plan Works

- 1) Each book is sent to you for a 10 day FREE EXAMINATION. If you don't like it, return it . . . doesn't cost a penny!
- 2) One new book will be sent to you for your FREE TRIAL every three months.
- 3) You pay only \$3.10 per book if you agree to take a total of 4 out of the 12 or more books.

### JOIN TODAY

Hurry! Get all the up-to-date, inside dope you need to make more money, faster! Fill out the coupon and mail it NOW!

- - - NO-RISK COUPON - - -

GERNSBACK LIBRARY, INC., Dept. 156  
25 West Broadway, New York 7, N.Y.

Please send me postpaid the deluxe, hard-cover edition of The V.T.V.M. Enclosed is \$4.00.

Enroll me now as a member of the GERNSBACK TECHNICIANS LIBRARY. Send me postpaid the deluxe, hard-cover edition of The V.T.V.M. If I keep it I will promptly send you the special price of \$3.10. I agree to take at least 4 books.

I would like to know more about the books I may have as a member of the TECHNICIANS LIBRARY—Send me full information.

Name..... (Please print)

Street.....

City..... State.....

**ATTENTION!**  
SCHOOLS, HOBBYISTS,  
RADIO TECHNICIANS!

**CATHODE RAY SCOPE TUBE**

3API, made by famous tube maker - Jan type! Electrostatic focus and deflection. Medium 7 pin base. Individually cartoned. Packed for export.

Regular net \$15.75  
ea. Lots of 4  
individ. packed  
4 to a carton

**79¢**

**SINGLE 99¢ EA.**

Send for FREE catalog RE-1 with over 400 tube types at savings!

**Rad Tel TUBE CO.**

115 COIT ST., IRVINGTON II, N. J.

**RT-24/APX-2 IFF EQUIPMENT**

44 tube transceiver with usable parts, tube sockets, relays, coax fittings, condensers, resistors, etc. 24 volt Blower motor, 24v gear train motor. Power transformer 400 to 2400 cycles. Original govt. cost \$750.00 Less \$5.95 ea.

Shipping weight 45 lbs.

**SPECIAL**

Same RT-24/APX-2 in sealed overseas carton complete with 44 tubes: 11-6AG5; 19-6C4; 1-OD3/-VR150; 1-2C26; 7-6J6; 4-9006; 1-5Y3; 1-2D21.

List price of tubes alone \$81. Ship by railway only. Approx. weight 46 lbs.

**\$17.95 each**

**Lots of 3 \$16.95 ea.**


Allow for postage and shipping charges. Send for our complete list of over 400 tube types from 70% to 80% off list!

NEW DEVICES

(Continued)

**1520 Golden Crest:** frequency response  $\pm 0.5$  db, 20 to 40,000 cycles; harmonic distortion not more than 0.5%, 1M less than 0.5% at listening level, less than 2% at rated output; variable damping control. 5 inputs for VR and ceramic pickups, tuner, tape and microphone. Selection of inputs, 3 crossovers and 4 rolloffs. Separate bass, treble, volume and contour (loudness) controls. Record compensation: EUR, AES, frr, RIAA, 78 and Quiet (scratch reduction). Input for rated output: magnetic cartridge .015 volt, tape and tuner 0.4 volt. Tubes: 3—12AX7, 2—5581, 1—5U4-G. 15½ inches wide, 11 inches deep, 4 inches high.—**Rauland-Borg Corp.**, 3515 West Addison St., Chicago 18, Ill.

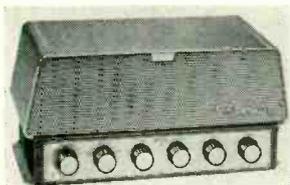**HIGH-FIDELITY AMPLIFIERS** self cabineted G series, 2122-C, 2199-B, and 2200-C. Satin-finish gold cover houses entire deck area. Amplifiers



available with chassis deck exposed. Entire front face of perforated metal grill; back open for maximum ventilation.—**Bell Sound Systems**, 555 Marion Rd., Columbus 7, Ohio.

**TAPE RECORDERS, Crown Imperial, Broadcaster and Deluxe.** Flat response  $\pm 2$  db, 20-18,000 cycles at 7½ i.p.s.; at



3¾ i.p.s., +3 db, 20-8,000 cycles. Uses 10½-inch reels.—**International Radio & Electronics Corp.**, S. 17 St. & Mishawaka Rd., Elkhart, Ind.

**TUBELESS HI-FI AM TUNER, model 595 high-fidelity AM tuner,** has crystal detector with negative mutual coupled band-pass circuit. Audio output from .07 to 0.7 volt on broad-




cast stations within 20-25 miles. Connects to TV antenna and plays through audio circuit of TV set or uses a good antenna and high-quality audio system. 4 x 7 x 3½ inches.—**J. W. Miller Co.**, 5917 South Main St., Los Angeles 3, Calif.

**CONVERSION KIT** for converting all RCA sets from 21-inch metal picture tubes to 21-inch glass picture tubes.—

**Colman Tool & Machine Co.,** Amarillo, Tex.

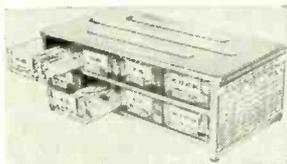**PISTON CAPACITOR KIT, PK85,** 85 quartz and glass precision piston capacitors, 10 basic types, for experimental



purposes. Compact metal cabinet, with double row of compartment drawers, holds capacitors.—**JFD Mfg. Co., Inc.**, 6101 16 Ave., Brooklyn 4, N. Y.

**TV REMOTE CONTROL UNIT, Magic Brain:** control knobs for fine tuning, picture control, on-off and volume; a dial for all v.h.f. channels. Installable in most RCA Victor TV sets without u.h.f. tuners manufactured since 1951. 5½ x 2¼ x 2 inches. Connected to receiver by 30-foot flat cord with pro-



tective cover. Subchassis and motor inside receiver. Change-over from local to remote control by turning tuning knob on receiver fully clockwise.—**RCA Victor Television Div.**, Camden, N. J.

**C-R TESTER, model 400,** replaces B & K model 350. 4½-inch plastic meter. Checks and corrects most TV picture-tube troubles without removing tube from set. Locates and repairs inter-element shorts and open circuits, stops leakage, reactivates picture-tube cathode and restores emission. Life test



checks gas content, predicts probable useful life expectancy. Model 200 with 3-inch meter performs many functions of former model 350.—**B & K Mfg. Co.**, 3726 N. Southport Ave., Chicago 13, Ill.

**V.O.M. Volometer model 102.** 3½-inch 800  $\mu$  D'Arsonval type meter, accurate to within 2%. Combines 5 a.c. voltage ranges: 0-3,000; 5 d.c., 0-3000; 3 current ranges a.c., 0 to 600 ma; 4 current ranges d.c., 0 to 130 maximum, 0 to 1.2 amps; 2 resistance ranges, 0 to 1,000 ohms, 0 to 1 megohm.—**Electronic** (Continued on page 163)

**BUILD 16 PRINTED CIRCUIT AND METAL CHASSIS RADIO CIRCUITS only \$19.95 complete**

With the New Deluxe 1956 PROGRESSIVE RADIO "EDU-KIT"

Build 16 Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector Circuits



Reg. U.S. Pat. Off. Pend.

- No Knowledge of Radio Necessary
- No Additional Parts Needed
- Excellent Background for TV
- Learn High Fidelity
- Used in 79 Countries
- School Inquiries Invited
- Learn Practical Radio Theory and Construction

**FREE RADIO and TELEVISION SERVICING LITERATURE ON REQUEST (See Coupon Below)**

**WHAT THE "EDU-KIT" OFFERS YOU**

Our Kit is designed to provide a fundamental background in radio, with the basic facts of Radio Theory and Construction Practice expressed simply and clearly. You will gain a knowledge of basic Radio Principles involved in Radio Reception, Radio Transmission and Audio Amplification.

You will learn how to identify Radio Symbols and Diagrams; how to build radios, using regular radio circuit schematics; how to mount various radio parts; how to wire and solder in a professional manner. You will learn proper chassis layout. You will learn Printed Circuitry. You will learn how to service and trouble-shoot radios. You will learn code. You will receive training for F.C.C. Novice License. You will learn High Fidelity.

In brief, you will receive a practical basic education in Radio, worth many times the small price you pay.

**THE KIT FOR EVERYONE**

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The Kit has been used successfully by young and old in all parts of the world. It is not necessary that you have even the slightest background in science or radio.

The Progressive Radio "Edu-Kit" is used by many Radio Schools and Clubs in this country and abroad. It is used by Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. All parts are individually boxed, and identified by name, illustration and diagram. Every step in building these sets is carefully explained.

**"LEARN BY DOING"—PROGRESSIVE TEACHING METHOD**

The Progressive Radio "Edu-Kit" comes complete with instructions. These instructions are arranged in a clear, simple and progressive manner. The theory of Radio Transmission, Radio Reception, Audio Amplification and servicing by Signal Tracing is clearly explained. Every part is identified by illustration and diagram. You will learn the function and theory of every part used.

The Progressive Radio "Edu-Kit" uses the principle of "Learn by Doing." Therefore you will build radio circuits, perform jobs, and conduct experiments to illustrate the principles which you learn. These circuits are designed in a modern manner, according to the best principles of present-day educational practice. You begin by building a simple radio. The next set that you build is slightly more advanced. Gradually, in a progressive manner, you will find yourself constructing still more advanced multi-tube radio sets and doing work like a professional Radio Technician. Altogether you will build Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector Circuits—16 in all. These sets operate on 105-125 V. AC-DC. For use in Foreign Countries having 210-250 Volt Source, an Adaptor for 210-250 V. AC-DC is available.

**THE PROGRESSIVE RADIO "EDU-KIT" IS COMPLETE**

You will receive every part necessary to build 16 different radio circuits. Our "Edu-Kit" contains all tubes, tube sockets, variable, electrolytic, and paper condensers, resistors, slide switches, coils, hardware, tubing, Instruction Manuals, Printed Circuit Materials, etc. No solder or wire included.

Every part that you need is included. These parts are individually packaged, so that you can easily identify every item. A soldering iron is included, as well as an Electrical and Radio Tester. Complete, easy-to-follow instructions are provided. All parts are guaranteed, brand new, carefully selected and matched.


In addition, the "Edu-Kit" now contains lessons for servicing with the Progressive Signal Tracer and Signal Injector, F.C.C. Instructions, quizzes, High Fidelity Instructions.

**TROUBLE-SHOOTING LESSONS**

Trouble-shooting and servicing are included. You will be taught to recognize and repair troubles. You will build and learn to operate a professional Signal Tracer and Signal Injector. You will receive an Electrical and Radio Tester, and learn to use it for radio repairs. While you are learning in this practical way, you will be able to do many a repair job for your neighbors and friends, and charge fees which will far exceed the cost of the "Edu-Kit." You can learn radio quickly and easily and have others pay for it.

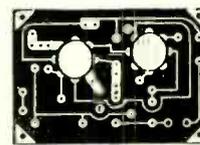**PRINTED CIRCUITRY Now Included**

You build a Printed Circuit Signal Injector, a servicing instrument that can detect many Radio and TV troubles. A Printed Circuitry is a special insulated board on which has been deposited a conducting material which takes the place of wiring. Various parts are plugged in and soldered to terminals. This new process is now popular in commercial radios, TV, hearing aids, etc.



**FREE EXTRAS**

- RADIO & ELECTRICAL TESTER
- TESTER INSTRUCTION MANUAL
- QUIZZES
- ELECTRIC SOLDERING IRON
- TELEVISION BOOK
- CONSULTATION SERVICE
- HIGH FIDELITY GUIDE


**30-DAY UNCONDITIONAL MONEY-BACK GUARANTEE**

"MAIL TODAY—ORDER SHIPPED SAME DAY RECEIVED"


- Send "Edu-Kit" Postpaid. I enclose full payment of \$19.95.
- Send "Edu-Kit" C.O.D. I will pay \$19.95 plus postage.
- Send me FREE additional information describing "Edu-Kit." Include FREE valuable Radio and TV Servicing Literature. No obligation. (Outside U.S.A.—No C.O.D.'s. Send check on U.S. bank or Intern'tl M.O. "Edu-Kit" for 105-125 V. AC/DC \$20.95; 210-250 V. AC/DC \$23.45.)

Name \_\_\_\_\_  
Address \_\_\_\_\_

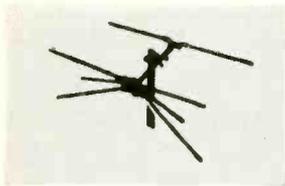
PROGRESSIVE "EDU-KITS" INC.  
497 Union Ave., Room 112G, Progressive Bldg., Brooklyn 11, N.Y.



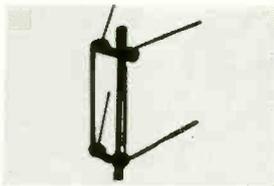
**TELCO SCOUT 3 ANTENNA**  
Eight elements; for low channels.  
No. A-180 NET \$3.30



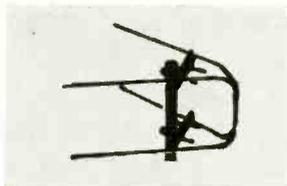**TELCO DOUBLE V ANTENNA**  
Adjustable UHF & VHF... Channels 2-83.  
No. A-9010 NET \$3.75



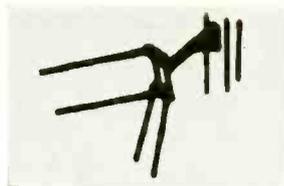**TELCO U-TYPE DOUBLE V ANTENNA**  
Adjusts to any V angle; VHF-UHF.  
No. A-9017 NET \$3.57




**TELCO DOUBLE V WINDOW-TENNA**  
UHF-VHF; mounts on window frame.  
No. A-9057 NET \$5.37



**TELCO STAND-OFF "EYE-OPENER"**  
Handy tool for faster installing.  
No. 8450 NET \$0.75



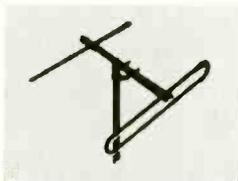
**TELCO UHF GOLDEN YAGI**  
16-element style, cut to channel.  
No. A-325 NET \$4.92




**TELCO HI-LOW DIPOLE ANTENNA**  
Pre-assembled; VHF chs. 2-13.  
No. A-250 NET \$5.22



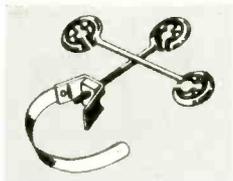**TELCO E-Z STAND-OFF**  
UHF-VHF; 3 1/2" machine screw.  
EZ-8031 NET \$4.80/C



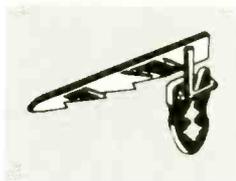
**TELCO E-Z KANT-STRIP STAND-OFF**  
7 1/2" 3-way; 9" stainless strap.  
EZ-8396 NET \$0.33



**TELCO E-Z DRIVE-IN STAND-OFF**  
Hardened metal 3/16" drive.  
EZ-8751 NET \$0.15



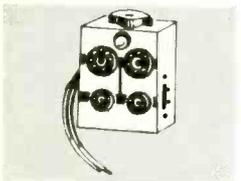**TELCO DUPLEX STAND-OFF**  
7 1/2" in-line duplex wood screw.  
No. 8225 NET \$0.15




**TELCO POCKET TUBE CHECKER**  
Series fil. and continuity tester.  
No. 9270 NET \$2.75

*Ask For These*




# SERVICE AIDS


*...at Your Jobber*

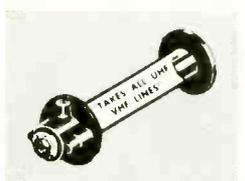

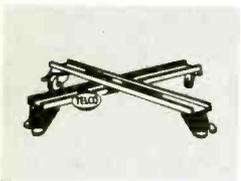
**TELCO UNIVERSAL LEAD-IN TUBE**  
Fits 3/4" hole, 1/4" wall; brown.  
No. 8958 NET \$1.17



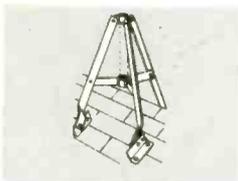
**TELCO TV SET ROLL-AROUND**  
Fits all sets, easy to install.  
No. 8957 NET \$5.97



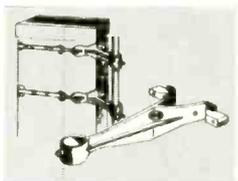
**TELCO TRIPOD TOWER BASE**  
Supports 10' masts without guys.  
No. 9063 NET \$4.17



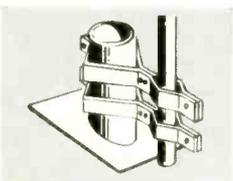
**TELCO CHIMNEY MOUNT BRACKETS**  
Cast alum. pair for 1 1/4" masts.  
No. 8001 NET \$4.05



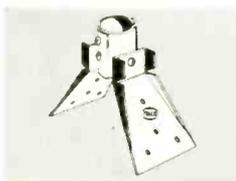
**TELCO VENT MOUNT**  
Holds mast to 2" to 4" vents.  
No. 8802 NET \$1.35



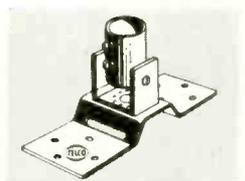
**TELCO UNIVERSAL RIDGE MOUNT**  
Adjustable to peaks, flat roofs.  
No. 8906 NET \$1.17



**TELCO FITZ-ALL MOUNT**  
Use anywhere; masts to 2".  
No. 8804 NET \$1.77

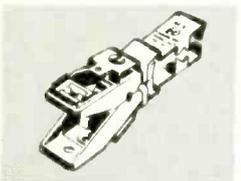

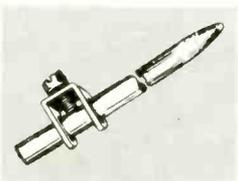**TELCO 3-WAY TV LINE KLIP**  
For straight, side, plug-in (RCA).  
No. 9015 NET \$0.13




**TELCO GROUND ROD**  
4 ft. long; 3/8" diameter.  
No. 8929 NET \$0.81



**TELCO UNIVERSAL LIGHT ARRESTOR**  
UL approved; UHF and VHF.  
No. 9242 NET \$0.45



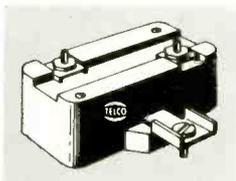**TELCO ACRYLIC SPRAY-KOAT**  
Fast-drying outdoor-indoor use.  
No. 8665 NET \$1.19




**TELCO SPECIAL LIGHT ARRESTOR**  
For 300-450-ohm open line; UL.  
No. 8640 NET \$0.60




**TELCO DELUXE LIGHT ARRESTOR**  
For all types TV lines, VHF & UHF.  
No. 8642 NET \$0.75



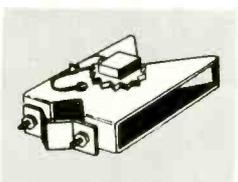**TELCO RIGID-TYPE TV BASE**  
Smart wrought black finish.  
No. 9082 NET \$3.57



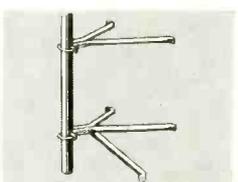**TELCO RATCHET CHIMNEY MOUNT**  
Galvanized straps; masts to 1 1/2".  
No. 9218 NET \$2.37



**TELCO TUBULAR WALL MOUNT**  
15" mount; masts to 1 1/2".  
No. 9243 NET \$3.00

**FREE!**

Your copies of all current TELCO Catalogs. Send postcard today!






# TELEVISION HARDWARE MFG. CO.

Division of General Cement Mfg. Co. • 910 TAYLOR AVENUE • ROCKFORD, ILLINOIS

Let me send you the entire story—FREE


Just fill out the coupon and mail it. I will send you, free of charge, a copy of "How to Pass FCC License Exams," plus a sample FCC-type Lesson, and the valuable booklet, "Money-Making FCC License Information."



CARL E. SMITH, E. E.  
President

I can train you to pass your FCC License Exams in a minimum of time if you've had any practical experience—amateur, military, radio servicing, etc. We can put you on the road to success.

# How to Pass FCC

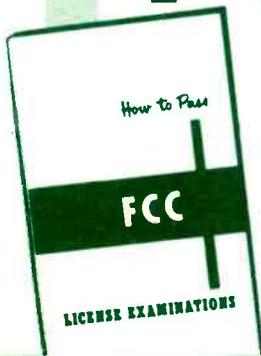

## FREE

Tells where to apply and take FCC examinations, location of examining office, scope of knowledge required, approved way to prepare for FCC examinations, positive method of checking your knowledge before taking the examination.

GET YOUR FCC TICKET IN A MINIMUM OF TIME

## Get this Valuable Booklet FREE

TELLS HOW

# WE GUARANTEE YOUR FCC LICENSE

TO TRAIN AND COACH YOU AT HOME IN SPARE TIME UNTIL YOU GET YOUR FCC LICENSE.

If you have had any practical experience—amateur, military, radio repair, experimenting, etc.

### HERE IS YOUR GUARANTEE

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind, until you successfully obtain your Commercial license.

TELLS HOW

Our Effective JOB FINDING Service Helps CIRE Trainees Get Better Jobs —

Here are a few recent examples of Job-Finding results.

#### ELECTRONICS TECHNICIAN:

"I am now employed by the Collins Radio Company as a Lab Technician. (This job was listed in your bulletin). I have used the information gathered from your course in so many ways and I know that my training with CIRE helped me a great deal to obtain this job."

Charles D. Sindelar, Cedar Rapids, Iowa

#### AIRLINES

"I replied to the Job Opportunities you sent me and I am now a radio operator with American Airlines. You have my hearty recommendation for your training and your Job-Finding Service."

James A. Wright, Beltsville, Md.

#### INDUSTRIAL ELECTRONICS

"Upon my discharge from the Navy I used your Job-Finding Service and as a result I was employed by North American Aviation in electronic assembly (final checkout)."

Glen A. Furlong, Fresno, Calif.

TELLS HOW

Employers make JOB OFFERS

Like These To Our Graduates Every Month

#### Broadcast Station in Illinois:

"We are in need of an engineer with a first class phone license, preferably a student of CIRE; 40 hour week plus 8 hours overtime."

#### West Coast Manufacturer:

"We are currently in need of men with electronics training or experience in radar maintenance, and we would appreciate if you will refer interested persons to us."

HERE'S PROOF FCC LICENSES ARE OFTEN SECURED IN A FEW HOURS OF STUDY WITH OUR COACHING AT HOME IN SPARE TIME.

	License	Time
A/1C Ronald H. Person, St. Louis 20, Mo.	1st	25 weeks
Carl Verboomen, Wrightstown, Wis.	1st	18 weeks
Marvin F. Kimball, Lafayette, Ind.	2nd	21 weeks
L. M. Bonino, Harlington AFB, Tex	2nd	16 weeks
John E. Hutchison, Bluefield, W. Va.	1st	27 weeks

An Approved Member



TV ENGINEERING INCLUDED IN OUR TRAINING & COACHING

THE ONLY HOME STUDY COURSE WHICH SUPPLIES FCC TYPE EXAMINATIONS WITH ALL LESSONS AND FINAL TESTS.

Your FCC ticket is recognized by employers in all phases of Electronics as proof of your technical ability.

Mail This Card Now NO POSTAGE REQUIRED

Get All 3 FREE



CLEVELAND INSTITUTE OF RADIO ELECTRONICS  
4900 Euclid Bldg., Cleveland 3, Ohio

RE-85A

I want to know how I can get my FCC ticket in a minimum of time. Send me your FREE booklet, "How to Pass FCC License Examination" (does not cover exams for Amateur License), as well as a Sample FCC-type lesson and the amazing new booklet "Money-Making FCC License Information." Be sure to tell me about your Television Engineering Course.

PLEASE PRINT CAREFULLY

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

Special tuition rates to members of the U. S. Armed Forces. Electronic Training Available To Canadian Residents.

CLEVELAND INSTITUTE OF RADIO ELECTRONICS

CARL E. SMITH, Consulting Engineer, President

4900 Euclid Bldg., Cleveland 3, Ohio

www.americanradiohistory.com

See our ad on next page

Six months from today

# Which Will You Hold?

this-

REGRET TO ADVISE  
YOU FAILED YOUR  
FCC EXAMINATIONS-

or this

1<sup>ST</sup> CLASS  
RADIO TELEPHONE  
OPERATOR'S LICENSE

Add Technical Training  
To Your Practical Experience -

## GET YOUR FCC LICENSE IN A HURRY!

Then use our Amazingly Effective  
JOB-FINDING SERVICE

Money-Making  
FCC  
Commercial  
Radio Operator  
LICENSE  
Information

Get This  
Valuable Booklet

TV ENGINEERING  
INCLUDED IN OUR  
TRAINING & COACHING

FREE!

**IMPORTANT**  
SEE OTHER SIDE FOR MORE INFORMATION

TELLS HOW—

### Here Is Your GUARANTEE

If you fail to pass your Commercial License exam after completing our course, we guarantee to continue your training without additional cost of any kind until you successfully obtain your Commercial License.

## WE GUARANTEE

TO TRAIN AND COACH YOU  
AT HOME IN  
SPARE TIME UNTIL YOU GET

## YOUR FCC LICENSE

If you have had any practical  
experience—amateur, Army, Navy,  
radio repair, or experimenting.

If You're in the Armed Forces PLAN NOW for

### PRESENT and FUTURE SECURITY

- 1 Use your spare time, NOW, while you are in the armed forces, to prepare for the FCC license examinations, and get your FCC Commercial License.
- 2 Shortly before discharge, use our EFFECTIVE JOB-FINDING SERVICE to get your choice of good-pay jobs.

Special tuition rates to members  
of the U. S. Armed Forces.

### FORMER NAVY MAN GETS JOB AT COLLINS RADIO

"Since my discharge from the Navy, I have been working for Collins Radio Company at Cedar Rapids, Iowa, one of the job opportunities you listed. I am giving a lot of credit to your course for helping me in passing the qualifications exam at Collins."  
Howard Johnson, Marion, Iowa

### NORTH AMERICAN EMPLOYS EX-ARMY MAN

"I am employed by North American Aviation as an electronic technician. Their name was received from you while I was in the service overseas. The lessons I completed played a big part in helping me pass their screening examinations.  
Vernon Skovgaard  
Los Angeles 6, Calif.

TEAR OUT AND MAIL THIS CARD NOW!

Postage  
Will Be Paid  
by  
Addressee

**BUSINESS REPLY CARD**  
FIRST CLASS PERMIT No. 8685, Sec. 349, P.L.A.R., Cleveland, Ohio

Cleveland Institute of Radio Electronics  
4900 EUCLID AVENUE  
CLEVELAND 3, OHIO

No Postage Stamp  
Necessary  
If Mailed in the  
United States

Desk RE-85A

# CONCORD MONEY SAVING VALUES!

## 15 WATT HIGH FIDELITY AMPLIFIER

- Built-in Pre-amp
- 4 Inputs



Reg. \$69.50 Value!

\$24.50  
Kit Form

**\$29.50**  
Wired

Superb mirror-like reproduction at an absolutely unbelievable price! Concord's "CELEBRATION" Amplifier has a frequency response of 20 to 20,000 cycles. Push-bull 6L6's give a full 15 watts of undistorted (less than 1%) power. Seven tube circuit uses 2-6L6's to give 40 db bass boost attenuation range, and 30 db treble boost-attenuation range. Noise level is better than 50 db below rated output. Other tubes include 6SQ7 pre-amplifier, 6SN7 phase inverter and 5Y3 rectifier. Controls include mike volume, phono volume, bass control, treble control and function selector. Output transformer will drive 8 ohm speaker. Adjustable hum balance control assures minimum hum as tubes age. Chassis is finished in grey vitreous enamel. Size 14" L x 8" D x 7 1/4" H. For 110-125 V, 60 cycle AC. Shpg. wt. 18 lbs. Complete with tubes. Kit includes all necessary components, complete pictorial step-by-step instructions and tubes. Less wire and solder.

Stock No. K-CA15K. 15 Watt Kit Only \$24.50  
Concord's "CELEBRATION" Amplifier described above, completely wired and tested: Stock No. K-CA15W. Worth \$69.50. Only \$29.50

## DELCO 8 TUBE-PUSH BUTTON AUTOMOBILE RADIO

Will outperform any Auto Radio on the market today!

Reg. \$125.00



Now **\$29.95**

Complete with 9 section 82" solid brass whip antenna. Measures only 14" collapsed. Worth \$9.20

Here's the auto radio with all the excellent features every car owner wants in his auto. Covers full broadcast range with powerful 10 watt push-pull output. Has 5 push-buttons and a sensitivity control in addition to manual tuning! Selective 8 tube circuit includes 2-6SK7's, 2-6V8's, 1-6SQ7, 1-6SA7, and 1-0Z1. Large 6"x9" speaker, push-pull output, and wide range tone control guarantee that this radio will outperform any competitive model on the market. It's ideal for tractors, trucks, boats and vacation camps as well as your automobile... truly the finest money can buy. Size: 9" high x 10" wide x 7 1/4" deep. Control shaft centers are 6-11/16" apart and require 1/2" diameter holes. Shpg. wt. 19 lbs. Complete with owners' installation manual, all necessary hardware, brackets and knobs. With tubes, less escutcheon.

Stock No. 99-P8T..... Reg. \$125.00..... Only \$29.95



## HIGH FIDELITY COAXIAL SPEAKERS

Worth \$19.90

12" are built especially for Concord \$9.70 ea.

These superb instruments by one of the leading audio manufacturers in the country. Acoustically designed for finest reproduction, quality built into every component for years of enjoyable performance. Sold at prices that are really exceptionally low! All of these fine speakers have remarkable power handling capacity with lowest distortion. One piece molded cones in both woofer and tweeter. Has cross-over network. Response uniform 50-13,000 cps. Speakers use extremely heavy Alnico magnets



## FAMOUS BRAND 25 WATT 12" HI-FI SPEAKER

Reg. \$19.95

Only **\$7.50** ea.

Highly recommended hi-fi 12" speaker with 9 oz. Alnico V magnet. Powerful 25 watt rating and freq. response of 50 to 12,000 cycles make this the best speaker buy available. Ideal for PA work where power and fidelity are a must. Voice coil impedance 6-8 ohms. Will perform at full rated power without significant loss of bass or treble or distortion. Precision engineering and superior materials put this speaker in a class by itself.

3 for \$20.85

## PM SPEAKER VALUES

Class "A" replacement speakers at Bargain Basement prices. All have heavy Alnico V magnets and are constructed to give a lifetime of trouble-free performance. Stock up now while the supply lasts!



Size	Price Ea.	Price Ea.	Lots of 3
4"	\$1.55		\$1.45
5"	\$1.65		\$1.55
6"	\$2.15		\$2.05
4"x8"	\$2.05		\$1.95
5"x8"	\$2.35		\$2.10
6"x8"	\$3.10		\$2.95
8"	\$3.30		\$3.15
12"	\$4.90		\$4.65

## SPECIAL BUY-8" and 10" PHILCO SPEAKERS

Complete With 50L6 Output Transformer and AC-DC Choke Mounted on Frame! Extra Heavy Alnico V Magnets.

8"—\$2.95 ea.—3 for \$8.50  
10"—\$3.49 ea.—3 for \$9.95

## ELECTRO-DYNAMIC SPEAKERS

Made for Philco, Individually boxed. Excellent frequency response and power output. Ideal for replacement use or for original equipment design.

3"	3000 Ohm	79c	6"	2500 Ohm	\$1.05
5"	4 Ohm	79c	8"	1700 Ohm	\$1.15
5"	2500 Ohm	89c	8"	2500 Ohm	\$1.25
4x6	450 Ohm	98c	10"	1700 Ohm	\$1.49
6"	1700 Ohm	\$1.05	10"	2500 Ohm	\$1.49

## DIAMOND STYLI SALE

Famous Brand Diamond Stylus designed to fit into new GE Heluctance Cartridge RPX-050A or old RPX-050. Replacement for GE #RPJ-013A. Has individually replaceable slide-in stylus. Diamond and Sapphire.

Reg. \$31.00..... Only \$11.95 ea.  
New Slide-in type diamond stylus for RPX-011A or RPX-040. Complete assembly. List \$27.50..... \$10.95 ea.

## INDOOR TV ANTENNAS 6 for \$1.00

Unmatched Value! Expertly designed indoor TV antennas attach in seconds. Mount invisibly on back of TV set. No unsightly rabbit ears or wings to spoil the appearance of the room. And what's more, they work! Buy them by the dozen and solve many of your TV antenna problems.

## MOBILE WHIP ANTENNA

REG. \$12.50

Only **\$1.98** ea.

One of the most sensational Whip Antennas ever offered. 9 section solid brass construction. 82" fully extended, only 14" collapsed. Can be adapted to a hundred different uses. Designed originally for bumper mounting with a removable base clamp. Can be used on 2, 6, 10 or 11 meters. Removable mast makes it possible to base load this antenna for 20, 40 or 75 meters. Simplified construction makes it possible to use 6 of the whips as a low priced beam antenna, or 4 as a ground plane.

Stock No. R-AN75D..... 3 for \$5.45

## BUILD YOUR OWN SNOOPERSCOPE

### INFRA-RED SNOOPERSCOPE TUBE AND FILTER

Reg. \$39.50  
Only **\$7.95**

Now you can see in the dark with this ingenious infra-red viewing device. Made famous by Armed Forces during World War II. Simple to construct with parts easily obtained. Snooperscope tube and filter supplied are the only specialized parts required. Complete with instructions schematic and information sheet. Stock No. SCR124



## GERMANIUM DIODE KIT

10 for \$3.45

Worth \$12.50

Here's a sensational kit value that has never been offered before. An assortment of 10 of the most modern and widely used germanium diodes. Complete with their specifications and interchangeability chart. Included are such currently used TV numbers as 1N34A, 1N87A, 1N51A, 1N56A, 1N38A and the latest Goldbond diodes TS6, TS3, and TS1. The retail value of these brand new, famous brand diodes is over \$12.50. Order several kits to be sure of an adequate supply.

Stock No. R-GDK10..... \$3.45

## FILTER CHOKE VALUES

TV REPLACEMENT CHOKE—2.5 henry at 150 MA. 60 ohms DC Res. Size 2 1/2" x 3 1/4" x 2". Mtg. Ctrs. 2 1/2" apart. Stock No. R-25H6. 59c ea.—3 for \$1.59

250 MA SWINGING CHOKE—Rated at 4.5 henrys at 250 MA to 8.5 henrys at 50 MA. DC res. 150 ohms. Open frame mounting—2" H. x 2" W. Mtg. Ctrs. 3-5/16" apart. Stock No. R-SWK45. 69c ea.—3 for \$1.95

JEFFERSON DUAL CHOKE—Two separate 8 henry 80 MA chokes in one case. JAN specs. Hermetically sealed. 6" H. x 2 1/2" x 3". Worth \$10.00. Stock No. R-004105. \$1.49 ea.—3 for \$3.95

## TV POWER TRANSFORMER SPECIAL

Worth \$17.25  
Only **\$4.95**

An outstanding power transformer value. 350-0-350 volts at 250 MA. 5 Volts at 6 Amps, 6.3 Volts at 6 Amps, and 6.3 Volts at 1.2 Amps. Size 1 1/2" x 3 1/2" x 4 1/2". Mtg. Ctrs. 3" x 3 1/2". Shpg. wt. 11 lbs. Stock No. R-TVP15..... \$4.95

## 6.3 VOLT FILAMENT TRANSFORMER

6.3 V @ 1.2 Amps  
Worth \$2.95  
IAN SPECS  
3 for \$2.95

## TUBE SPECIALS

### FAMOUS BRAND—GUARANTEED

304TH—\$3.95 ea. 304TL—\$7.95 ea.

616's—6 for \$3.00 6SN7—5 for \$3.00

Send for Bargain Tube Sheet No. 114—

Thousand of Fabulous Tube Values!



## HEAVY DUTY DUAL BLOWER

BLOWS HOT OR COLD!!

WORTH \$29.50

Only **\$14.95**

Made by famous manufacturer. Has AC shaded pole motor, dual multi blade fans and dual outlet blowers. Heating elements are built into each blower outlet. 3 way switch blows hot or cool air. Has UL approved line cord. Operates at 2800 RPM. 2850 fpm velocity. Has a million uses, photo dark rooms, cooling xmt tubes, humidifiers, hair dryers, kitchen ventilators, etc. Black lower finish. wt. 11 lbs. 8 1/2" long x 6" H. Vent openings 2" diam. Stock No. R-5107B.

## LATEST SARKES TARZIAN CASCADE VHF TUNER

Another exceptional tuner value from Concord! Latest 3 tube Sarkes Tarzian Cascade tuners for less than manufacturer's cost! Covers all 13 VHF channels with unusually high sensitivity and low co-channel interference. Designed to last a lifetime and give terrific fringe area reception. Ideal low cost replacement unit. Guaranteed Brand New and in excellent operating condition. Available for either 21 or 41 mcx-cycle use. Please specify.

Stock No. R-STD-3..... \$8.95 ea.



Reg. \$24.40

Only **\$8.95**

## KIT OF USED SARKES TARZIAN TUNERS

IDEAL FOR EXPERIMENTING OR REPLACEMENT PARTS. LESS TUBES. 3 for \$1.98

## WESTINGHOUSE UHF TUNERS

CONVERT TO UHF **\$1.95** For Only

Worth \$24.95




It's Fabulous!! The opportunity of a lifetime. Now you can convert to UHF for only \$1.95. Sensational Westinghouse UHF Tuners are designed to operate in conjunction with your present VHF tuner to give you complete ALL-CHANNEL coverage. Tunes 450 to 870 Mc. Output 43 Mc. Regular 300 ohm input. The ideal basic element for building tuner, converter, booster or for experimenting on UHF. Convenient size for installation in TV chassis. (5 x 2 1/4 x 5 1/2") Complete with 6AF4 and crystal easy-to-follow schematic. Shpg. wt. 2 lbs. Stock No. 99-G-VI1390

## WESTINGHOUSE UHF RECEPTOR

Complete with 6AF4 Tube, Crystal Diode. Schematic and Instructions

What more can we say! You get this highly miniaturized UHF receptor complete with tube, germanium diode, resistors, condensers, coils, variable condenser, plug and socket, all for LESS THAN THE PRICE OF THE TUBE ALONE!! In addition we throw in a schematic diagram and installation instructions. Quantities are limited, so buy now and save!!

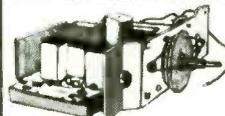Stock No. WTC-2 Whatta Buy! **\$1.25** ea.



## FAMOUS CROSLY UHF TUNERS

Only **\$4.95** ea. \$4.45 ea. Lots of 3

Worth \$29.50 in Parts Alone!

Uses famous Mallory continuous tuning inductor. Covers all UHF channels 14 thru 82. Original replacement for Crosley part 151698-1-1 used in Crosley series E7 chassis 392 and 391. Ideal for building UHF converters, etc. Output feeds into channel 5 I.F. Concentric shaft includes fine tuning. Built-in antenna switch operates off tuning shaft. Comes complete with 1N72 diode, 6B27 and stock mounted 6AP4 tubes. Size: 8 x 5 x 3 1/2". Shpg. wt. 5 lbs. Stock No. R-CMD15..... \$4.95 ea.



## REPLACEMENT PHONO MOTORS

Only **\$1.49** ea.—3 for \$4.15

Worth \$4.50

- Limited Quantity Available
- Single Speed 78 RPM
- Rim Drive—Brand New

All Merchandise Money Back Guaranteed. \$5.00 Minimum Order F.O.B. N.Y.C. 25% Deposit for C.O.D.'s—Prices subject to change without notice.

## SEND FOR FREE CATALOG

CONCORD RADIO Dept. E16  
45 Warren Street, N. Y. 7, N. Y.

Please, send me your Special Bargain Catalog free of charge.

Name

Address

City

State

**Concord Radio** 45 WARREN STREET New York 7, N. Y.

Telephone: DIgby 9-1132

# N A Reliable, Stable, O BATTERY OPERATED W VTVM



## NEW PRECISION MODEL 78

Metal Cased • Modestly Priced

- ★ 6 True Zero-Center DC Voltage Ranges: 13 1/3 Megohms constant input resistance. 0 ±1.5 ±6 ±30 ±150 ±600 ±1500 volts.
- ★ 5 Wide-Spread Electronic Ohmmeter Ranges: 0-1000-100,000 ohms. 0-1-100-1000 Megs.
- ★ 5 Extra-Hi Impedance RMS AC Voltage Ranges: 0-3-12-60-300-1200 volts. 8 Megs. input resistance; 67 mmfd. input cap.
- ★ High-Frequency Probe Facilities available thru use of accessory crystal probe, Model RF-12.
- ★ One Coaxial, 3-Way VTVM Probe for all functions except High Frequency Probe RF-12.
- ★ Complete, Self-Contained, Battery Operation engineered for long-lived battery performance.
- ★ Built-in Battery Compartment: All batteries conveniently replaced via removable cover plate.
- ★ Uses Standardly Available Commercial Batteries.
- ★ 5 1/4" Wide-Angle PACE Meter: 100 microamperes sensitivity, ±2% accuracy.
- ★ 1% Wire and Deposited-Film Type Resistors.
- ★ Deep-Etched, Satin-Brushed Aluminum Panel.

**MODEL 78:** In rugged, blue-grey ripple-finished steel cabinet. Dimensions: 5 7/8" x 7 3/4" x 3 1/2". Complete with tubes, one set of batteries and detailed instruction manual. Net Price: \$57.50

### ACCESSORIES AVAILABLE FOR MODEL 78

**Model RF-12:** High Frequency Crystal Probe complete with low capacity x10 multiplier head. Frequency range to 250 Mc. Net Price: \$10.95

**Model TV-4:** High Voltage Safety Test Probe for ranges to 60 KV. Net Price: \$14.75

*Precision Test Equipment is available and on display at leading Electronic Parts Distributors. Write directly to factory for new 1955 catalog.*

**PRECISION** Apparatus Company, Inc.  
70-31 84th Street, Glendale 27, L. I., N. Y.  
Export: 458 Broadway, New York 13, U. S. A.  
Canada: Atlas Radio Corp., Ltd., 50 Wingham Ave., Toronto 10

# All From One Source

These four quality lines of Electronic Components may be obtained quickly and conveniently from Distributors who stock **ERIE RESISTOR CORPORATION** products.



ERIE Electronic Components enjoy the reputation of having the highest quality and make up the most complete line of Ceramic Replacement Capacitors. Distributor Stock items are representative of the most common types used by dealers, servicemen, experimenters, amateurs, laboratories, project engineers, and industrial.



CORNING Glass Electronic Components include the complete line of Fixed Glass Capacitors, Direct Traverse and Midget Rotary Glass Trimmer Capacitors, and various types of Low Power, Precision and High Power Glass Resistors.



ERIE-Chemelec Teflon Electronic Components are made of the most nearly perfect insulating material available, and are ideally suited to withstand high humidity, high or low temperatures, high altitudes, high voltages, and high frequency operation. It is serviceable at any temperature from -110° to 550°F for long periods with negligible change in critical electrical characteristics.



GRIGSBY-ALLISON Switches are known throughout the industry for dependable quality and smooth performance. They include a complete variety of styles for all types of applications.

ORDER NOW  
From Your  
ERIE  
DISTRIBUTOR



ERIE ELECTRONICS DISTRIBUTOR DIVISION  
ERIE RESISTOR CORPORATION  
Main Offices: ERIE, PA.  
Factories: ERIE, PA. • LONDON, ENGLAND • TRENTON, ONTARIO

## WRITE FOR THIS

**FREE**  
LIFETIME  
HI-FIDELITY  
Sales Kit

**DEALER SALES KIT**  
MAKE BIG  
HI-FI PROFITS

Sell the finest HI-FI Units for custom building or in BEAUTIFUL CABINETS... Sell BELOW REGULAR WHOLESALE PRICES with full dealer mark-up and with price protection.

TRANSVISION Hi-Fi Equipment is  
SOLD THRU SELECTED DISTRIBUTORS

TRANSVISION, INC., NEW ROCHELLE, N. Y.  
In Canada: 1336 Queen St. W., Toronto 3, Ont.

TRANSVISION, INC., New Rochelle, N. Y. RE-1  
Rush FREE Dealer SALES KIT on HI-FI and name of nearest distributor.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_

## TEST and REPAIR

CRT TUBES

"RIGHT on  
the Job"

with

CENTURY'S  
CRT

TESTIVATOR

MODEL 103 \$14.95  
ONLY net



New Profits! More Calls! Save Time! Save Trouble! Here is a key to a whole new field of profits for you. With the #103 CRT TESTIVATOR you can repair picture tubes right in the set in a matter of minutes. The TESTIVATOR TELLS YOU INSTANTLY where the trouble is and then fixes it! Here are some of the major advantages of the TESTIVATOR—it TESTS: Cathode emission, Shorts and leakage between elements, then elements. Probable useful life of the tube. It REPAIRS: Activates the CRT cathode by removing surface contamination. Restores emission giving life to weak and dim tubes. Clears inter-element shorts and leakage. So easy to use... you just plug in, attach the TESTIVATOR socket to the base of the CRT and the accurate, easy-to-read indicators tell you what you must know. (Complete instructions with every unit.)

**FREE BONUS OFFER**—Order your #103 now and receive a handy, valuable booklet listing radio and TV tubes including CRT's which are interchangeable with no wiring changes. Another profit maker for you. Now you can always leave 'em with a picture. The TESTIVATOR IS MONEY BACK GUARANTEED.

### — NO RISK TRIAL ORDER COUPON. —

If Jobber is out of Stock mail order to  
CENTURY ELECTRONICS CO., Dept. RE-1  
111 Roosevelt Ave., Mineola, N. Y.

Please send the Model 103 CRT TESTIVATOR on 10-day money-back guarantee.

Send Postpaid... I am enclosing full payment of \$14.95.


Send C.O.D. . . . I will pay \$14.95 plus postage.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

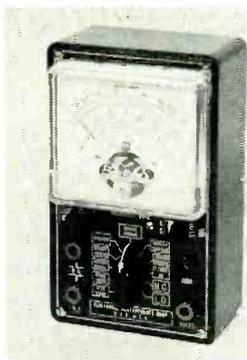SAVE! We pay postage on all prepaid orders




Measurements Corp., 280 Lafayette St., New York 12, N. Y.

**C-R TUBE CHECKER KIT, CC-1**, tests for shorts, leakage and emission. Shadowgraph test (spot of light on screen) indicates whether all electromagnetic deflection picture tubes are capable of functioning; indicates condition on good-bad scale. Supplies all operating




voltages to tube under test. Protective spring-loaded test switches. **Heath Co.**, a subsidiary of Daystrom, Inc., Benton Harbor 20, Mich.

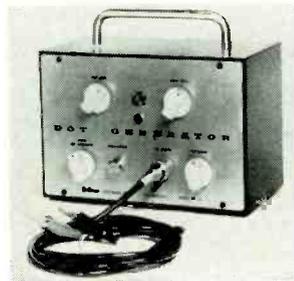**WHITE DOT GENERATOR, model CD**, in kit form. Preriveted sockets and terminals. Generator output can be fed directly to antenna terminals of color receiver. Weighs 6½



pounds, measures 5 x 9 x 6 inches. — **Hoffman Electronics Corp.**, 3671 S. Hill St., Los Angeles 7, Calif.

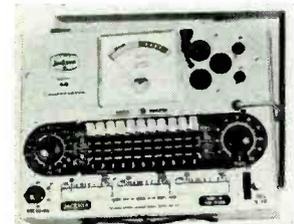**TUBE TESTER, model 49**, features number of plug-in accessories, using basic meter and



power supply for additional tube and components tests. Includes high-resistance shorts tester measuring interelement leakage to 2 megohms, heater current tester, selenium rectifier checker. Lever-action switches. 4½-inch meter indicates tube condition on a colored good-bad scale which is also marked in percent of normal quality.—**Jackson Electrical Instrument Co.**, 16-18 S. Patterson Blvd., Dayton 2, O.

**V.T.V.M., Phaotron 777**, self-contained, with 42 ranges, illuminated 4¾-inch scale color-coded green for ohms, black for a.c. and d.c., red for peak-to-peak volts; 2 zero-center scales for FM alignment; double-



shielded 200-µa movement; separate range and function switches; unbreakable nonmagnetic metal case. Accuracy: 3% d.c., 5% a.c. Accessories include high-frequency coaxial cable, d.c. probe and leather carrying case.—**Phaotron Co.**, 151 Pasadena Ave., South Pasadena, Calif.


**V.T.V.M., model 68** (illustrated), a.c.-operated, wide-range, general-purpose electronic test set. 5¼-inch wide-angle meter, ±2% accuracy. 1% multipliers and shunts, wire and deposited film types. Has 5 plus and 5 minus d.c. voltage ranges: 3, 12, 60,



300, 1,200 at 13½ megohms constant input resistance; 5 resistance ranges to 1,000 megohms; 5 peak-to-peak voltage ranges: 8, 32, 160, 800, 3,200; 5 stabilized zero-center reference ranges for FM discriminator balancing.

**Model 78**, battery-operated wide-range general-purpose electronic test set. Uses same meter as **model 68**. Contains one No. 477 (67.5 volts), 2 No. 950 (1.5 volts) batteries. 6 zero-center d.c. voltage ranges at 13½ megohms constant input resistance: ±1.5, ±6, ±30, ±150, ±600, ±1,500; 5 resistance ranges to 1,000 megohms; 5 high-impedance r.m.s. a.c. voltage ranges at 8 megohms input resistance and 67 µf input capacitance: 3, 12, 60, 300, 1,200. — **Precision Apparatus**

Just Out

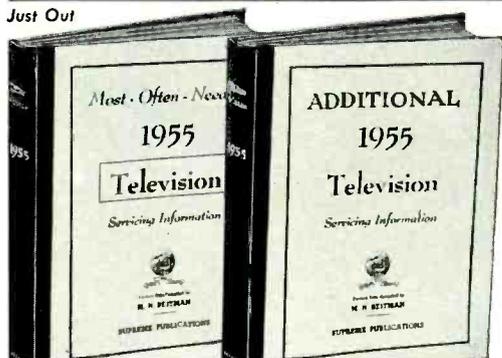

These twin 1955 TV volumes cover practically all sets of all makes. The new **ADDITIONAL 1955 TV** manual includes material almost to the minute. Each giant manual has 192 large pages of service data, changes, double-size circuits, service hints. Special price, each manual only

\$3

## New ADDITIONAL 1955 TV Volume LARGE MANUAL COVERS NEWEST 1955 TV SETS EARLIER TV VOLUMES STILL SOLD AT ONLY \$3 AMAZING BARGAIN

**Supreme** twin 1955 TV manuals are the scoop of the year. Cover all sets of all important makes. New **ADDITIONAL 1955 TV** volume gives you the very latest material. Your price for this mammoth manual is only \$3. **Supreme** super values defy competition. Each prior-year manual (at only \$3) has a whole year of service material. Each volume covers different material, from 1947 to latest 1955 sets. Include circuits, alignment, waveforms, voltage charts, service hints, changes, and double-spread diagrams.


### ALL NEEDED TV DATA

**Supreme TV** manuals supply all needed service material on every TV set of every important manufacturer. Here is helpful, practical, factory-prepared data. It will really make TV servicing and adjustment easy for you. Join 146,000 servicemen who use, benefit, and save with **SUPREME** service manuals. In these manuals you get correct factory-checked circuits, alignment procedure, response curves, service hints, recommended changes, voltage charts, waveforms, and dozens of double-page diagrams. Here is your TV service material to help you do expert work double-quick; and priced at only \$3 per annual volume. Be ready to repair any model by carrying in your car all ten TV volumes listed in coupon below. Or try one of the new 1955 TV manuals to see what an amazing bargain you get for only \$3. Send coupon for prompt shipment or ask your jobber.

Practically tell you how to make every repair. More pages, more diagrams, more service data per dollar of cost. Get the best for less. Get **SUPREME**.

**TELEVISION SERVICING COURSE**  
Let this new course help you in TV servicing. Amazing bargain, complete, only \$3, full price for all lessons. Giant in size, mammoth in scope, topics just like a \$200.00 correspondence course. Lessons on picture faults, circuits, adjustments, short-cuts, UHF, alignment facts, hints, antenna problems, trouble-shooting, test equipment, picture analysis. Special, only

\$3

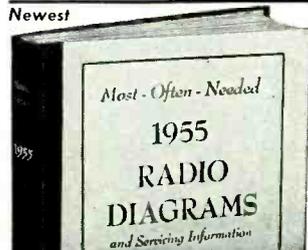

### RADIO DIAGRAMS

Here is your complete source of all needed **RADIO** diagrams and service data. Covers everything from most recent radios to pre-war old-timers; home radios, auto sets, combinations, changers, and portables. Sensational values. Still sold at pre-Korean prices. Only \$2 for most volumes. Every **Radio** manual contains large schematics, all needed alignment facts, parts lists, voltage values, trimmers, dial stringing, and helpful service hints. All volumes are large in size, 8½x11 inches, about 190 pages. See coupon at right for a complete list of these low-priced manuals.

### NO-RISK TRIAL ORDER COUPON

**SUPREME PUBLICATIONS, 1760 Balsam Rd., Highland Park, ILL.**

#### Radio Diagram Manuals

- New 1955 Radio Manual, \$2
- 1954 Radio Manual, \$2.50
- 1953 Diagrams
- 1952 Radio
- 1951 Diagrams
- 1950 Manual
- 1949 Radio
- 1948
- 1947
- 1946
- 1942
- 1941
- 1940
- 1939
- 1926-1938 Manual, \$2.50
- Radio and TV Master Index, 25¢

PRICED AT ONLY \$2 EACH

Rush today TV manuals checked  below and Radio manuals at left. Satisfaction guaranteed.

- Additional 1955 TV, \$3.
- 1954 TV Manual, \$3.
- 1952 Television Manual, \$3.
- 1948 TV, \$3.
- New Television Servicing Course, complete... \$3.
- Early 1955 TV, \$3.
- 1953 TV Manual, \$3.
- 1951 TV, \$3.
- 1949 TV, \$3.
- 1947 TV & FM, only \$2.

- I am enclosing \$..... Send postpaid.
- Send C.O.D. I am enclosing \$..... deposit.

Name: .....  
Address: .....

**Supreme Publications**  
Sold by All Leading Parts Jobbers

# EXTRA VALUES AT LESS COST

with **EMC TEST EQUIPMENT**

## EMC MODEL 102

**HIGH QUALITY—LOW PRICE, POCKET SIZE VOLOMETER\*—NEW EXPANDED SCALE.** Sturdy, pocket-size case. Large clear 3 1/2" — 1000 ohms per volt D'Arsonval-type voltmeter—2% accurate. 5 AC & DC voltage ranges, 0-3000V. 4 DC current ranges, 0-6000 MA. Two resistance ranges with same zero adjustment.

**ALSO AVAILABLE:**

EMC model 104 Multi-meter 4 1/2" meter at 20,000 ohm per volt DC. Only \$26.95. Kit \$19.25



**\$14.90**

102 Kit \$12.50

## EMC MODEL 205 P

**ACCURATELY CHECKS ALL TUBES BY STANDARD EMISSION METHOD**

All tubes with filament volts between 75 and 117V are accurately checked by standard emission method. Individual sockets. Compensates for line variations between 105-135V. Flexible four-position lever type switches positively protect against obsolescence. Checks continuity, shorts, opens and leakages. Large, clear, 4 1/2" Three-color "reject-good" scale meter.

**ALSO AVAILABLE:**

Model 206P dynamic mutual conductance tube checker \$83.50 4 1/2" meter in portable oak case. (Lowest price in the market.)



**\$47.50**

205P Kit \$36.20

## EMC MODEL 107

**DIRECTLY MEASURES CAPACITY, RESISTANCE AND COMPLEX WAVEFORMS PEAK TO PEAK**

Measures directly in 6 ranges. All peak to peak voltages of complex waveform, between .2 volt and 2800 volts—RMS values of sine wave voltages, between .1 volt and 1,000 volts. Capacity of condensers between 50 MMFD to 5000 MFD—resistance from .2 ohms to 1000 megohms. Inductance from 1.4 henries to 140,000 henries.

**ALSO AVAILABLE:**

EMC regular VTVM model 106 with carrying strap only \$35.90. In kit form model 106 K only \$23.90.



**\$48.90**

107 Kit \$34.50

Electronic Wholesalers 1419 N. 3rd St. Harrisburg, Pa.

Please send me:

EMC Style \_\_\_\_\_ Quantity \_\_\_\_\_

EMC Style \_\_\_\_\_ Quantity \_\_\_\_\_

EMC Style \_\_\_\_\_ Quantity \_\_\_\_\_

25% Deposit enclosed, balance C.O.D.

Full Amount enclosed—Freight prepaid

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

## NEW DEVICES


Co., Inc., 70-31 84th St., Glendale 27, N. Y.

**FIBERGLAS DROP CLOTH** protects floors and rugs against hot solder, scratches, etc. 37 x 48 inches, fire resistant. Used as rainproof chassis cover.



Folds compactly into a tube caddy.—**CBS-Hytron**, Div. of Columbia Broadcasting System Inc., Danvers, Mass.

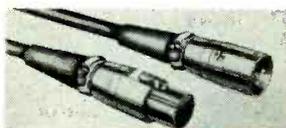**AUDIO CORD CONNECTORS, XLR**, shockproofed for quiet connection by use of insulating material of resilient synthetic rubber (polychloroprene). Positive cable clamp for even grip on cable through a rubber bushing. Two insert arrangements available—one with three 15-ampere contacts for No. 14




wire, other with four 10-ampere contacts for No. 16 wire. Solder pots pretinned; standard finish satin nickel. Panel style rectangular flange receptacle provides closer mounting for crowded installations.—**Cannon Electric Co.**, 3209 Humboldt St., Los Angeles 31, Calif.

**OUTPUT TRANSFORMER, Dynaco A-430**, high-fidelity audio output unit matching 6550 or 6CA7/EL34 tubes in circuits delivering 50 to 100 watts, for converting Williamson-type amplifiers to 50 watts output. Response  $\pm 1$  db from 6 to 60,000



cycles. Undistorted power output rating, 50 watts from 20-20,000 cycles; 100 watts from 30-15,000 cycles. Phase characteristics permit substantial feedback without amplifier instability.—**Dyna Co.**, 5142 Master St., Philadelphia 31, Pa.

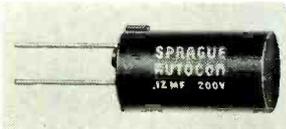**SINGLE-ENDED CAPACITORS**, Sprague type SE Autocon molded-paper replacements for single-ended types in printed circuits. Tiny standoff feet eliminate dust and moisture



All specifications given on these pages are from manufacturers' data.

(Continued)

traps under capacitors and prevent printed wiring shorts. Leads 1-inch long. Type HXC solid dielectric for high insulation resistance, low power factor and flat temperature-capacitance curve. Plastic shell excludes moisture. 47 types with values from .001 to 0.47  $\mu$ f at 200, 400 and 600 volts.—**Sprague Products Co.**, 81 Marshall St., North Adams, Mass.

**ANTI-STATIC SPRAY, No-Fog NF-102**, a colorless, odorless liquid sprayed on tube or mask and wiped with clean dry cloth. Leaves microscopic film



as insulation against static. Good for cleaning phonograph records, plastic products, etc.—**Tele-Matic Industries Inc.**, 16 Howard Ave., Brooklyn 21, N. Y.

**FLYBACK TRANSFORMERS**, five Triad types, correct replacements for use in RCA, Traveler and Zenith TV receivers. Electrically and mechanically interchangeable with original



equipment. Complete line of TV replacement transformers listed in catalog TV-155.—**Triad Transformer Corp.**, 4055 Redwood Ave., Venice, Calif., or Triad distributors.

**4-SPEED RECORD PLAYER, Quartet**, plays new 16 r.p.m. Talking Book records and all other speeds automatically. Accessory to all Hoffman 21- and 24-inch table or console models with Super Mark 10 or Mark 5 chassis. Can be plugged into radio, amplifier and TV receivers equipped with phono input jack. Dual sapphire needles, ceramic long-life car-



tridge, automatic shutoff after last record. Featherweight tone arm. Model W120 walnut base; model M120 mahogany; model B120 blond.—**Hoffman Radio Div., Hoffman Electronics Corp.**, 3761 S. Hill St., Los Angeles 7, Calif. END

## new Tubes & Transistors




### 3CE5 and 6CE5

High-mutual-conductance sharp-cut-off pentodes, the 3CE5 and 6CE5, have been announced by CBS-Hytron. They are designed for use in v.h.f. tuners and as i.f. amplifiers and feature a very sharp cutoff characteristic. Electrically and mechanically the tubes resemble types 3CB6 and 6CB6.
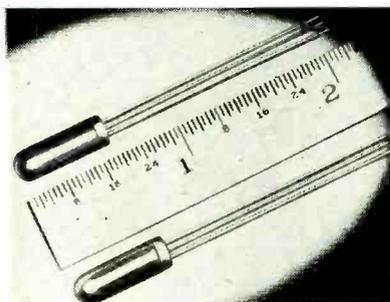
### 2-OC72 transistor

Announced by Amperex, the 2-OC72 (see photo) is a matched-pair high-current low-voltage power type designed for such applications as portable



phonographs and radios and similar portable equipment. The p-n-p push-pull units can deliver 200 mw from a 6-volt battery supply.

### 6810 phototube

This head-on type multiplier phototube is intended for use in scintillation counters and other applications involving low-level, large-area light sources. Announced by RCA, the 6810 features fast response, high current gain, relative freedom from after-pulses and small spread in electron transit time. Since the tube can deliver pulse currents of up to 0.5 ampere with good linearity, there is generally no need for associated wide-band amplifiers.

The 6810 has high sensitivity to blue-rich light and negligible sensitivity to red radiation. Design features include 14 electrostatically focused multiplying (dynode) stages and a focusing electrode with external connection for shaping the field which directs photoelectrons from the cathode onto the first dynode.


### Silicon rectifier

Development of a silicon power rectifier capable of operating at ambient temperatures up to 200°C was announced by Hoffman Electronics. The
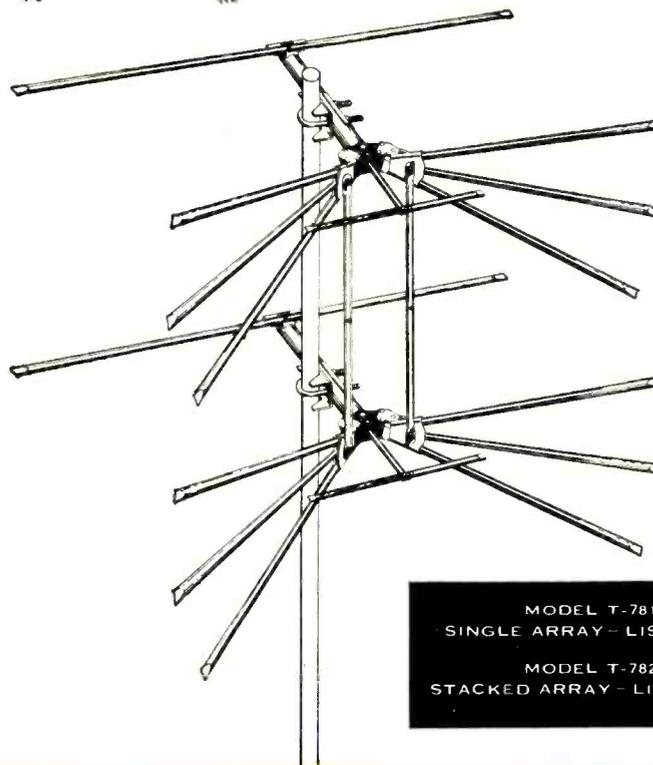
## CHAMPION of all Fan-Type CONICALS



- ★ BETTER LOW BAND PERFORMANCE!
- ★ BETTER HIGH BAND PICKUP!
- ★ GUARANTEED SUPERIOR TO ANY CONICAL ON THE MARKET TODAY!



MODEL T-781  
SINGLE ARRAY - LIST \$5.56  
MODEL T-782  
STACKED ARRAY - LIST \$11.53

## An Exclusive Tenna Development

Now, Tenna has combined all of the better features of the BAR-X conical and the fan-type conical into a single model to give you the ultimate in both high band and low band performance. The NEW Tenna T-781 and T-782 are guaranteed superior to any other conicals. Try this NEW Tenna conical under the toughest reception conditions and you'll be astonished with its performance. All aluminum, full size and completely pre-assembled . . . and at a low, low price.

**TENNA** Manufacturing Co.

7580 GARFIELD BLVD. • CLEVELAND 25, OHIO

PACKED WITH BARGAINS

# FREE!

## LAFAYETTE

132 PAGE ELECTRONIC CATALOG

SAVE ON EVERYTHING IN ELECTRONICS



**Big Money Saving Values!**

### NEW LAFAYETTE CATALOG GET YOURS NOW IT'S FREE

Packed with the largest selection of Electronic, Radio and T.V. Parts, and equipment, PA, Hi-Fi systems, tubes, antennas, Transistor Kits, parts and components, Test Equipment, new build your own kits, tools, books, Microscope, drafting equipment, Binoculars, Telescopes, All Radio, TV and Ham supplies — ALL AT GREAT SAVINGS — For the economy minded servicemen, dealer, engineer and technician. **CHUCK FULL OF BUYS! SEND FOR YOUR FREE COPY TO-DAY.**

**Lafayette Radio** 100 SIXTH AVE. NEW YORK, N.Y. DEPT. JA  
Include postage with order

**LAFAYETTE RADIO**  
100 SIXTH AVE., NEW YORK, N.Y.  
Send FREE 132-Page 1955 Lafayette Catalog

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

BOSTON, MASS.  
110 Federal St.

BRONX, N.Y.  
542 E. Fordham Rd

NEWARK, N.J.  
24 Central Ave.

PLAINFIELD, N.J.  
139 West 2nd St.

#### HIGH-FIDELITY TURNOVER CARTRIDGE



● 40-14000 CYCLE  
● NEVER BEFORE AT SUCH A PRICE!  
Lafayette brings you one of the finest high-fidelity turnover cartridges, AT AN UNBELIEVABLE PRICE! Frequency response from 40-14000 cycles — +2 db. Has 2 sapphire styli to play all speeds. Needle pressure only 5 grams on LP cond 12-15 gram on 78. Output is 5 volts. Complete with turnover mechanism and knob, fits Webster, Garrard, VM, Collaro and tone arms of leading manufacturers of record changers and players.

2.75  
Reg. Price 8.50  
PK-79

Singly, Each 2.75  
In lots of 3, Each 2.50

#### CRYSTAL MICROPHONE



COMPARE IT WITH ANY MIKE AT 2 to 3 TIMES THE PRICE  
A quality crystal Microphone for PA systems, house recorders, etc. Frequency response 30 to 10,000 cycles. Output level —52 db. Provides ample output for use with low gain amplifiers. Complete with 5 ft. of shielded cable. Shpg. wt. 3 1/2" lbs.

PA-24 — In lots of 3, each ... 3.95 singly, each 4.25

#### SLIM HIGH OUTPUT DYNAMIC MICROPHONE



Reg. Price 11.50 Net \$9.95

A pencil-slim design, high output PA Dynamic Microphone of exceptional quality, at a price that is 1/3 of the price of any comparable microphone on the market today. Very smooth response, 50-11,000 cycles. Omnidirectional, tiltable head. Switch on side gives choice of either high impedance (50,000 ohms) or low impedance (250 ohms). Instantly removable bracket permits use either on stand or as hand mike. Features exceptional mechanical strength. Cast case with satin chrome finish, 3/8" x 27 thread, Acoustically-treated grille head, 8" long; 1 1/4" barrel diameter. Shipping weight 2 lbs.

PA-29 — In lots of 3, Each \$9.25  
Singly, Each \$9.95

#### TELEPHONE PICKUP



FOR RECORDING TELEPHONE CONVERSATIONS

Induction telephone pickup. Telephone conversations can now be picked up with no tapping of wires or special telephone circuits. Simply place the phone base, either cradle or upright type, on the pickup platform and connect the leads to the high impedance input of any medium gain audio amplifier, or directly to any tape disc or wire recorder.

MS-16 ..... 2.95

#### A NEW LIGHT WEIGHT DYNAMIC EARPHONE



Fits right into the ear. Ideal for use with radio sets, for private listening. DC resistance 2000

ohm impedance 5000 ohm with 3 ft of Plastic Cord.  
MS-72 ..... Net 1.95  
MS-100 — Impedance 8 ohm for silent radio or TV viewing. Net 1.95

MS-260 — FOR TRANSISTOR CIRCUITS, Special high output for low power circuits; DC resistance 2000 ohm, impedance 8000 ohm. Net 3.95


#### TRANSISTOR 455 KC I.F.



Specially designed for transistor circuit, only 1/2" square by 3/4" high.  
MS-126 —  
In lots of 10, each 79¢  
Single, Each ..... 89¢

#### RAYTHEON TRANSISTOR

CK722  
P-N-P  
99¢

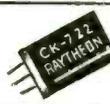

#### TRANSISTOR LOOP ANTENNA



Fixed inductance tapped to match 800 ohm input. Covers 540-1650 kc with 385 mmf variable cond. size 9/16 x 4 1/4".  
MS-166 Net 1.25

1.25

#### TRANSISTOR TYPE 2N107

P-N-P  
\$1.25

#### TRANSISTOR OSCILLATOR COIL



Supplies local OSC. energy to mixer stage. IF 455 KC. Use with 385 mmf cond. 5/8" x 1 1/4" high.  
MS-165 ..... Net 49¢

New Price!

4.65

RAYTHEON TRANSISTOR CK-760 (2N112)

#### HIGH SENSITIVITY AC-DC MULTITESTER

20,000 OHMS PER VOLT DC and 10,000 OHMS PER VOLT AC

The New Lafayette High Sensitivity Multitester is a complete instrument (not a kit) packed with every desirable feature found in instruments costing twice as much. One of the most sensitive multitesters ever offered: 20,000 ohms per volt DC and 10,000 ohms per volt AC; having a highly sensitive 35 microamp meter. Check these full scale readings: DC Volts: 0-6; 0-12; 0-60; 0-300; 0-1200; 0-6000 volts at 20,000 ohms per volt. AC Volts: 0-6; 0-12; 0-60; 0-300; 0-1200 at 10,000 ohms per volt. DC current ranges: 60 microamp, 0-6; 0-60; 0-600 milliamperes. Resistance ranges: 0-4; 0-40; 0-400K; 4 meg. ohms. Decibel: —20 to +17 db (0 = 774 volt). Capacity: 250 mmf-10 MF. Inductance: 20-1000 millihenry. Extreme versatility and accuracy; 1% precision resistors. 3/4" meter; plastic front with metal bottom for ruggedness. Size: 5 3/4" x 3 3/4" x 2 3/4"; complete with batteries and test leads. Shipping weight 4 lbs.



RW-30A ..... In lots of 3, Each \$19.25  
Singly, Each \$19.95

#### IMPORTED BINOCULARS



All have coated lenses — clamped in prisms — light weight all metal bodies. Complete with case and straps.

F-182 — 6x.13 I.F.	NET 10.75
F-105 — 8x.30 I.F.	NET 17.95
F-115 — 7x.35 I.F.	NET 17.95
F-183 — 7x.35 C.F.	NET 20.95
F-103 — 7x.50 I.F.	NET 21.50
F-104 — 7x.50 F.F.	NET 24.95
F-117 — 10x.35 C.F.	NET 23.95
F-104 — 12x.50 I.F.	NET 27.95
F-118 — 18x.50 C.F.	NET 31.50
F-185 — 20x.50 C.F.	NET 37.50

FULLY GUARANTEED FOR A YEAR AGAINST MECHANICAL AND OPTICAL DEFECTS.  
ADD 10% PER. TAX TO PRICES



rectifier (see photo), designated NS-P1, is housed in a rugged, vibration-proof case measuring approximately 1 1/8 inches in diameter and 1 1/4 inches in height.

The maximum reverse working voltage is 60 and the forward current density at 1 volt is in excess of 600 amperes per square inch of junction area.

**6562 pencil type oscillator**

This triode is a fixed-tuned u.h.f. oscillator having pencil type construction



tion (see photo) and is intended for transmitting service in radiosonde applications. The 6562, produced by RCA, has two resonators: one is fixed-tuned and connected between grid and cathode; the other, connected between grid and plate, is loop-coupled to a coaxial r.f. output terminal and can be tuned to 1,680 mc. The useful power output of the tube is approximately 600 milliwatts.

**6806 beam power tube**

Another RCA announcement concerns the high-power 6806, designed for operation as a grid-driven power amplifier at frequencies up to 1,000 mc. It has a maximum plate-dissipation rating of 35 kw.

In color or black-and-white television service the 6806 can deliver a synchronizing-level power output of 30 kw at 550 mc or 25 kw at 750 mc. As a CW amplifier in class-C telegraphy service the 6806 is capable of giving a useful power output of 25 kw at 400 mc.

**6786 rectifier**

A new mercury-vapor grid-controlled rectifier, the 6786 (see photo), has been announced by Amperex. The tube has a peak inverse voltage rating of 15 kv and an average plate current of 10 amperes. For intermittent operation, a



A. A. Ghirardi

J. R. Johnson



**...here's how to LEARN SERVICING R-I-G-H-T!**  
 Complete training in modern professional methods . . . only \$12 . . . 3 months to pay!

**FIX ANY RADIO OR TV SET EVER MADE...easier...better...faster**

**Radio & TV Receiver TROUBLESHOOTING AND REPAIR**

by Ghirardi & Johnson

822 pages, 417 illustrations  
 Price \$6.75

(See special offer in Coupon)

This big, 822-page book brings you the kind of PROFESSIONAL training that helps you handle the toughest radio-television-electronic service jobs as slick and as accurately as you now do the easy ones!

For service beginners, Radio & Television Receiver TROUBLE-SHOOTING AND REPAIR is a complete, easily understood professional training course. For experienced servicemen, it is the ideal way to "brush up" on specific jobs; to develop better troubleshooting methods and shortcuts; and to find quick answers to puzzling service problems.

Step by step, it takes you through each service procedure . . . from locating troubles quicker and with less testing to repairing them faster and better.

You learn to deal with any kind of trouble in any kind of receiver. No guesswork. No aimless testing.

Here are just a few of the subjects covered: Components and Their Troubles; Basic Troubleshooting Methods; "Static" and "Dynamic" Testing; Practical Troubleshooting Tips and Ideas; AC/DC, 3-way Portable and Battery-set Problems; Servicing Communications Receivers; A Complete Guide to Television Service; AM, FM and TV Realignment Made Easy; Resistor, Capacitor, Inductor and Transformer Problems; Servicing Tuning, Selector and Switching Mechanisms; Loudspeakers; Servicing Recorders and Record-playing Equipment . . . and dozens more. Use coupon. Read it for 10 days at our risk.

**LEARN BASIC CIRCUITS...and watch service "headaches" disappear!**

**Radio & TV Receiver CIRCUITRY AND OPERATION**

by Ghirardi & Johnson

669 pages, 417 illustrations  
 Price \$6.50

(see special offer!)

It's amazing how much easier you can repair radio and television sets and even industrial electronic equipment when you know all about its circuits. You locate troubles in a jiffy because you know what to look for and where to look. You handle jobs lots faster, better . . . and more profitably.

Radio & Television Receiver CIRCUITRY AND OPERATION gives you a complete understanding of basic circuits as well as their variations. It teaches you to recognize them . . . to understand their peculiarities . . . to

know their likely "troubleshooting" . . . and how to eliminate guesswork and useless testing.

Throughout, this new book brings you the kind of above-average professional training that fits you for the bigger, better-pay jobs. Covers all circuits used in modern television and radio receivers, amplifiers, phono pick-ups, record players, etc.

Price only \$6.50 . . . or see money-saving combination offer in coupon. 10-day FREE examination.

**Save \$1.25!**

**Make your training library complete. Have ALL the latest data at your fingertips. Get both these books at only \$12.00 for the two . . . YOU SAVE \$1.25.**

**FREE EXAMINATION . . . easy terms!**

Dept. RE-16, RINEHART & CO., INC.  
 232 Madison Ave., New York 16, N.Y.

Send books indicated for FREE EXAMINATION. In 10 days, I will either remit price indicated plus a few cents postage or return books post-paid and owe you nothing.

Radio & TV CIRCUITRY AND OPERATION (Price \$6.50)     Radio & TV TROUBLE-SHOOTING AND REPAIR (Price \$6.75)

COMBINATION OFFER . . . Both books only \$12.00 (Regular price separately \$13.25 . . . you save \$1.25)  
 (Combination offer is payable at rate of \$3 (plus postage) after 10 days if you decide to keep books, and \$3 a month thereafter until \$12 has been paid.)

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City, Zone, State \_\_\_\_\_

**OUTSIDE U.S.A. . . . \$7.25 for TROUBLESHOOTING AND REPAIR; \$7.00 for CIRCUITRY AND OPERATION; \$13.00 for both books; Cash with order, but money refunded if you return books in 10 days.**

RINEHART BOOKS ARE SOLD BY LEADING BOOK STORES

## NOW... model SX-100

Selectable side band receiver

BUILT TO THE SPECIFICATIONS OF  
1,000,000 FIELD EXPERTS

See it at your Jobber—only \$295.00



Model SX-100. Amateur Net \$295.00  
Matching R-46B Speaker \$17.95  
Frequency Range 538kc-1580kc  
1720kc-34mc

Hallicrafters 22 years of production know-how, the engineering experience of developing over 100 different major receiver designs, plus the advice of over 1,000,000 field experts operating Hallicrafters receivers all are combined to bring you this outstanding new receiver—the SX-100! Hallicrafters alone, long recognized as the leading designer and manufacturer of quality communications equipment, can offer you the dependability and performance of this great new SX-100 at the amazingly low price of just \$295.00

Look at these features you enjoy with the SX-100... before, they were available only on receivers costing a great deal more!


1. SELECTABLE SIDE BAND OPERATION.
2. "TEE-NOTCH" FILTER—This new development provides a stable non-regenerative system for the rejection of unwanted heterodyne. The "Tee-Notch" also produces an effective steepening of the already excellent 50 K.C. i.f. pass band (made famous in the SX-96) and further increases the effectiveness of the advanced exalted carrier type reception.
3. NOTCH DEPTH CONTROL for maximum null adjustment.
4. ANTENNA TRIMMER.
5. PLUG IN LABORATORY TYPE EVACUATED 100 KC QUARTZ CRYSTAL CALIBRATOR—included in price.
6. LOGGING DIALS FOR BOTH TUNING CONTROLS.
7. FULL PRECISION GEAR DRIVE DIAL SYSTEM.
8. SECOND CONVERSION OSCILLATOR CRYSTAL CONTROLLED—greater stability through crystal control and additional temperature compensation of high frequency oscillator circuits.

### CONTROLS

Pitch Control  
Reception  
Standby  
Phone Jack  
Response control (upper and lower side band selector)  
Antenna Trimmer  
Notch Frequency  
Notch depth  
Calibrator on/off  
Sensitivity  
Band Selector  
Volume  
Tuning  
AVC on/off  
Noise limiter on/off  
Bandspread  
Selectivity

**hallicrafters**  
CHICAGO 24, ILLINOIS

## NEW TUBES AND TRANSISTORS (Continued)

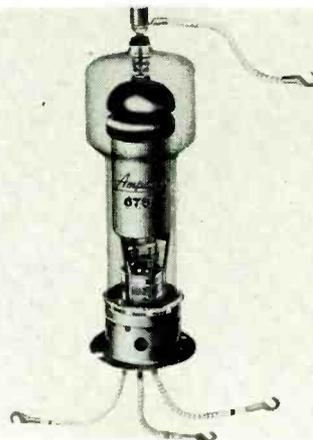


maximum plate current of 15 amperes may be used.

The 6786 is designed for high-current power supplies in radio transmitters and industrial r.f. generators. Under normal ambient temperature conditions, no forced-air cooling is necessary.
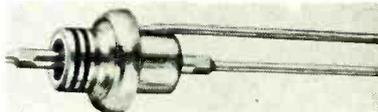
### HA5001, 2, 3 transistors

The Semiconductor Division of Hughes Aircraft has announced three new n-p-n fused-junction germanium transistors, the HA5001, HA5002, HA5003. These are medium-power units having high gain and low noise figures. They show a negligible alpha-crowding effect at high currents, making them especially suitable for high-current medium-power amplifiers. All three types have a maximum collector current of 100 ma and a collector dis-




sipation of 500 mw. With suitable heat sinks these ratings can be increased.

For the HA5001, HA5002 and HA5003, respectively, maximum current amplification (alpha) is 1.0, 0.965 and 0.99; maximum collector-to-base voltage is 30, 15 and 20; collector cut-off current is 5, 12 and 10 $\mu$ a.
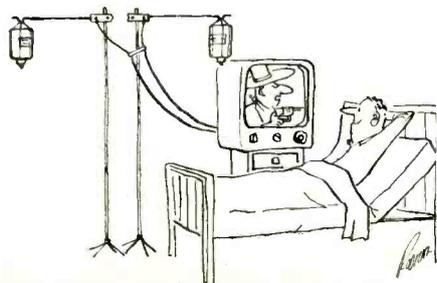
### 5AHP4 picture tube

A universal picture tube, the 5AHP4, has been announced by La Salle Tube Co., Chicago. It does not require a focus device or ion-trap magnet. To observe set performance it is necessary only to connect the high-voltage lead and the regular picture-tube socket to the 5AHP4. END



## HERSHEL SPECIALS

**All New MYSTERY PACKAGE**  
of ELECTRONIC PARTS

Worth \$40.00  
Our Price **\$3.95**  
Ship Wt. 20 lbs.

It's the surprise of your life! 20 pounds of brand new usable Govt. surplus. The ideal gift for hams, etc.  
We save the price! post to save the more money!

**KIT SPECIALS**

<b>KIT 1. HARDWARE</b> Over 1,000 pcs. Assorted For Radio & TV	<b>99c</b>	<b>HI GAIN DYNAMIC MIKE KIT</b> Uses UTC Transformer and Western Electric Mike. Ideal for Hams, PA. CAP, Recording, Mobile Equip.—50 DB/80. 7500 CPS. Diagram Furnished	<b>\$1.95</b>
<b>KIT 2. CERAMICONS</b> 100 Assorted 75 mmfd. to 6,000 mmfd.	<b>\$2.50</b>	<b>PHOTO ELECTRIC CELL</b> 95¢ CE Vacuum Cell used in AMPRO Sound Projector. Also useful for opening garage doors and Alarm Systems.	
<b>KIT 4. Rotary Switches</b> 25 Assorted Terrific Buy!	<b>\$2.50</b>		
<b>KIT 5. RESISTORS</b> 100 Assorted 1 ohm to 15 meg. 1/2 to 5 watts	<b>\$1.75</b>		

**SWING CHOKE**

<b>2H-7H-550 MA Thordarson T48003 \$5.95</b>	<b>KIT 10. MICAS AND SILVER MICAS</b> 100 Assorted Range from 10mmfd. to 7500mmfd.	<b>95c</b>	<b>\$2.50</b>
<b>KIT 6. RF CHOKES</b> 25 Assorted Range from 5MH to 25MH	<b>KIT 11. BATH-TUB OIL CONDENSERS</b> 25 Assorted Range from .1 Mfd. to 2 Mfd. up to 600 VDC	<b>\$3.25</b>	<b>\$1.50</b>
<b>KIT 7. DOGGLE AND SLIDE SWITCHES</b> 25 Assorted D.P.S.T.—D.P.D.T. S.P.S.T., etc.	<b>KIT 12. HI WATTAGE RESISTORS</b> 25 Assorted Range from .75 ohm to 20,000 ohm, 10 up to 200 watts	<b>\$2.75</b>	<b>\$3.25</b>
<b>KIT 8. PAPER AND CAN CONDENSERS</b> 25 Assorted Range from 4Mfd.—150V to 80Mfd.—450V.	<b>KIT 13. TUBE SOCKETS</b> 50 Assorted 1-10-7-8-9 pin types	<b>\$1.75</b>	<b>\$2.50</b>

**ALL-PURPOSE FIL. TRANSFORMER**  
PHI 117VAC 60CY. SEC. 6.4V 12A 6.4V 10A 5.0V 3A 5.0V 3A 5.0V 1.75A

**\$4.95**

**VARIABLE CONDENSERS YOUR CHOICE**  
TYPE A 100 MMFD. Double Spaced size 2 1/2" W x 1 1/2" H Hummerbund Mfg. Veeta Root Counter 1/4" Shaft 0.10 Manual for coil tuning. 1.00. 3 for \$1.00

**95c**

**OIL CONDENSER**  
2 Mfd. 3000 VDC Pyranol Oil W Mounting Brackets 1-1 Mfd. 3000 VDC. New, removed from equip. Size 4 3/4" x 4 1/4"

**\$1.65**

**ARC-5 COMMAND TRANSMITTER YOUR CHOICE**  
2.1 to 3 MC. 7 to 9.1 MC. Brand New in Cases with subet.

**\$6.95**

**HOTTEST BUY IN THE COUNTRY**

**AUDIO CHOKE**  
4500 ohm ideal for radio control air. business boats. etc. Size 1 1/4" x 5/8" x 5/8" Wt. 1/2 oz.

**95c**

**TERMS: Cash with order or 25% DOWN—BALANCE C.O.D. ALL PRICES NET F.O.B. DETROIT MINIMUM ORDER \$2.00**

**HERSHEL RADIO CO.** 5249 GRAND RIVER  
Detroit 8, Michigan Phone TYler 8-9400


## TAPE RECORDERS

**Tapes—Accessories**  
Nationally Advertised Brands  
**UNUSUAL VALUES**  
Send for Free Catalog  
**DRESSNER**  
Box 66RE, Peter Stuyvesant Sta., New York 9, N. Y.

**MERITAPE**  
Low Cost. High Quality Recording Tape—in boxes or cans.

**KARL F. ROSS**  
Registered Patent Agent  
(U. S. and Canada)  
Specializing in electronic patent matters  
305 Broadway, New York 7, N.Y. WO 2-3449

# Patents

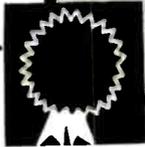

## COLOR KINESCOPE

Patent No. 2,711,493

Ernest O. Lawrence, Berkeley, Calif. (Assigned to Chromatic Television Labs., Inc., San Francisco, Calif.)

This patent is awarded to a researcher who has done much previous work on color kinescopes (see RADIO-ELECTRONICS, June, 1955, page 110).

As shown in Fig. 1, the new tube differs in several respects from conventional tubes. The green gun is centrally located and its beam passes straight through the tube. The red gun is above. Its beam is deflected by plates D1. The beam from the lower blue gun is deflected by plates

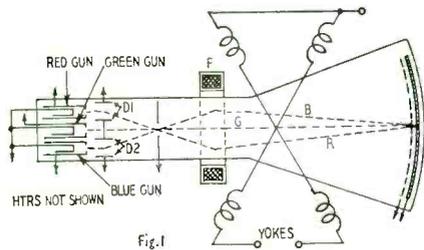


Fig. 1

D2 as shown. These blue, green and red beams (marked B, G and R) are focused by coil F so that they arrive at the target together.

Fig. 2 is a magnified diagram which shows how the beam angle of incidence controls color. Just in front of the target is a wire grid with individual wires W. These are biased negatively

with respect to the target. Each wire corresponds to a group of three color phosphors which are deposited on the target in thin horizontal strips. They appear as R (red), G (green) and B (blue). For example, the green

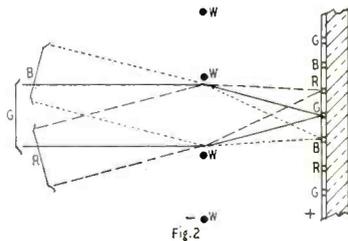


Fig. 2

phosphor strip is always deposited midway between any two wires. Of course, each negative wire repels electrons near it.

The beam from the blue (B) gun arrives at a downward angle. It is shown by dotted lines. Note how repulsion by the negative wire grid focuses this beam accurately on the blue (B) phosphor. The red (R) beam (dashed lines directed upward) is focused on the red phosphor. The green (G) beam (continuous lines) arrives head on and is focused midway between the wires.

## 3-GUN KINESCOPE

Patent No. 2,719,241

(Assigned to Westinghouse Electric Corp., John W. Coltman, Pittsburgh, Pa.)

This new invention, it is claimed, simplifies the construction of a 3-color kinescope tube, while permitting better color registration.

Fig. 1 shows the general layout of the new tube. It has two screens: S1 a photoelectric and S2 a picture screen. They are shown in greater

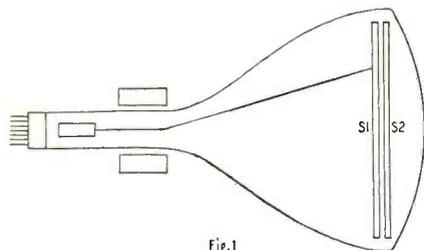


Fig. 1

detail in Fig. 2. High-velocity electrons from the gun penetrate the aluminum backing of S1 and strike a phosphor layer which emits light. The light passes through a transparent medium and a thin layer of tin oxide, a semiconductor. It excites the photoemissive surface. The latter emits electrons. Note that strips of conducting material lie between the emissive surface and the tin oxide. Naturally light cannot pass through the conducting strips, therefore electrons are emitted only at the gaps between strips.

Now for S2. This includes phosphor layers as shown in Fig. 2. R, G, B denote red, green and blue. Note that a green layer occurs between each of the other colors. Also, the green

layers are opposite to and parallel with each gap in S1.

Electrons coming from the gap between strips of S1 normally fall on each green phosphor in S2, since the green phosphor strips are in front of the gaps. Normally, therefore, only green would be visible on the picture screen.

A high voltage is connected between S1 and S2 as shown. It biases S2 positive so that electrons coming from the photoelectric screen are

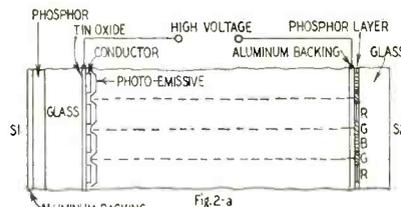


Fig. 2-a

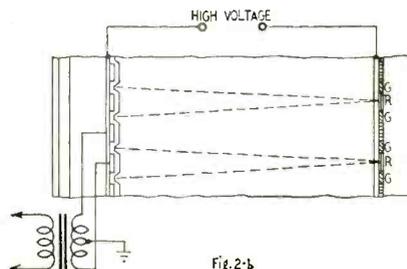


Fig. 2-b

## COMPLETE HI-FI

"Golden Ensemble"  
by Rauland

Tuner, Preamp and Amplifier in a single, compact BALANCED HI-FI unit at extremely low cost . . .

*The Very Best for Less!*



Here's the quality unit for simplest installation—merely add speaker and record changer and have your complete, superb FM-AM-Phono home music system. No cabinet required—saves money, space, installation problems. You get the ultimate in wide-range musical enjoyment and you pay less for it. Features are outstanding. Response: FM  $\pm 0.5$  db, 20 to 20,000 cps; AM,  $\pm 3.0$  db, 20 to 5,000 cps; Phono,  $\pm 0.5$  db, 20 to 20,000 cps. Sensitivity: FM, 3 mv. for 20 db of quieting; AM, 5 mv. for 0.5 watt output. Harmonic distortion: Radio input, less than 2%; Phono input, less than 0.7%. Separate front ends for AM and FM; tuned RF stage on FM; discriminator with dual limiters; AFC with defeat on function switch; FM dipole antenna; AM has RF stage, ferrite loop. Separate bass, treble controls; RIAA record equalization; choice of standard or equal loudness control; full 12 watts output, etc. Ultra-compact design, only 5 $\frac{3}{4}$ " high; decorator-styled in handsome charcoal black with marbled gold finish. Fits anywhere beautifully. See and hear the "Golden Ensemble" soon.

## NEW! HI-FI SOUND FOR TV!



EXCLUSIVE RAULAND  
TV55 TELEVISION  
SOUND TUNER

Designed for use with the "Golden Ensemble". Makes your TV sound "come alive" for thrilling listening or tape recording. Just plug in, tune and enjoy Hi-Fi audio on any VHF channel, played through your RAULAND music system! See it—hear it now.

Visit your Hi-Fi dealer for a personal RAULAND Hi-Fi audition. See and hear the "Golden Ensemble" and TV 55 Sound Tuner—and you'll know you're getting the very best for less.

Write for full details covering the complete RAULAND Hi-Fi line

**Rauland**

RAULAND-BORG CORPORATION  
3515 W. Addison St., Dept. A, Chicago 18, Ill.

**INTRODUCING YOUR NEW PROFIT MAKER**

**SAVE SERVICE TIME  
SELL MORE TUBES**

**SECO**  
GRID CIRCUIT  
TUBE TESTER

MODEL GCT-5

**\$29<sup>95</sup>** Slightly higher West

Now quickly and accurately detect "positive grid" conditions in amplifier tubes used in circuits employing a high value of grid return resistance. **EXCLUSIVE!**



**"HARD TO FIND" TV TUBE FAULTS LOCATED FAST!**

- Poor picture contrast
- Grainy picture
- Twisting, bending or pulling of the picture
- AGC, RF, IF and Sync. Group tube faults
- Vertical jitter or bounce
- Sync. Buzz in the sound
- Any or all symptoms caused by sync. pulse compression.

Stop guessing and substitution checking, test and sell tubes with conviction on the first call, avoid embarrassing and costly callbacks.

Filament Selector Switch accommodates all the latest tubes for TV and INDUSTRIAL uses.



Another Seco Exclusive!  
**FLY BACK INTERVAL & INDUCTANCE ANALYZER**

Checks horizontal circuits without disconnecting!

For specialized applications to meet your specific need, contact:



**SECO MFG. CO.**  
5015 Penn Ave. So.  
Minneapolis, Minn.

PATENTS

(Continued)

attracted and accelerated towards S2. In addition, a.c. is applied to the conducting strips of S1. See Fig. 3, where alternate strips are shown tied together and connected to the color signal. Thus during one half-cycle of this signal, the even numbered strips will be more positive than the odd. This polarity is reversed during the next half-cycle.

Fig. 2-a shows that when the color signal voltage is zero, electrons move in straight lines from S1 to S2 and strike the green phosphors. When the odd-numbered strips are more negative than the even-numbered, the electrons are deflected as shown in Fig. 2-b. Then each beam falls on the red phosphors. One-half cycle later

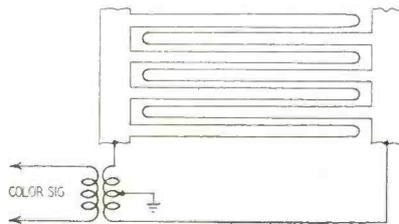


Fig. 3

the beams will be deflected in the opposite directions and they will scan only the blue phosphors.

Fig. 4 shows the shape of the color signal applied to alternate conducting strips of S1.

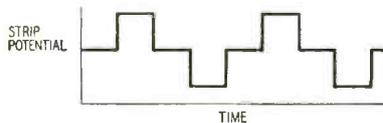


Fig. 4


It is a complicated square wave. When its voltage is zero, green is scanned so this color appears more often than either of the others. For that reason the green phosphors must be narrower than the others.

**AIDING THE BLIND**

Patent No. 2,721,316

Joseph D. Shaw, Cincinnati, Ohio

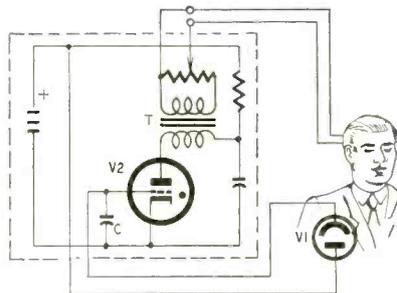Though the vision area of a brain is undamaged, the eyes and optic nerves may be unable to transmit the necessary impulses to the brain. This device generates and sends a signal to the brain so that the sensation of light occurs. According to this inventor, it is possible to place plastic sockets within the skull to contact the sensitive brain areas for the purpose described.



The diagram shows a phototube V1 whose output charges C. When this capacitor is charged to a predetermined level, it fires the gas thyratron V2 which transmits the brain pulse (via transformer T). When this occurs, the blind person receives the sensation of light.

With such an arrangement, a person can see whether an object in front of his photocell is light or dark and can judge its brilliance. In a more complicated form of the invention several cells are used with a corresponding number of terminals at the brain. Then the person can scan several areas at once and perhaps perceive a rough outline of the object.

For finer detail, of course, the sensitivity of the system will have to be improved. However, even in its present form it represents a significant aid to the blind.

END

**Now there are 2**

*Rondine Jr.*

**2-SPEED 12" TURNTABLES by REK-O-KUT**



Model L-34 for 45 and 33 1/3 rpm records

And the **NEW**

Model L-37 for 78 and 33 1/3 rpm records



**\$49<sup>95</sup>**

Slightly higher on West Coast

**SEE THEM BOTH AT YOUR SOUND DEALER**

or write for complete details to Dept. LA-13

**REK-O-KUT COMPANY**  
38-01 Queens Blvd., Long Island City 1, N.Y.

# radio-electronic Circuits



## MULTIPLE WAVETRAP


The usual wavetramp with a single resonant circuit is not very effective in eliminating interference whose frequency is close to that of the desired signal. Its response curve is so broad that it attenuates the desired signal too much. Here is a multi-resonant wavetramp that overcomes this disadvantage. I live close to the transmitting towers of a broadcast station and use the trap to prevent interference to another station a few channels away.

A tuned circuit is reactive at all frequencies off resonance. A parallel-tuned (antiresonant) circuit appears as an inductive reactance at all frequencies below resonance and as a capacitive reactance above resonance. The reactive effects are just the opposite for a series-tuned circuit.

The trap shown at *a* in the illustration is used to receive a signal whose frequency is lower than that of the interference. The parallel-tuned network (L1-C1) is tuned to the interference frequency (F1). This network appears as an inductance at frequencies lower than F1 so C2 can be used to tune this inductive reactance to F2, the frequency of the desired signal. The signal voltage developed across

C2 is fed to the antenna post on the receiver.

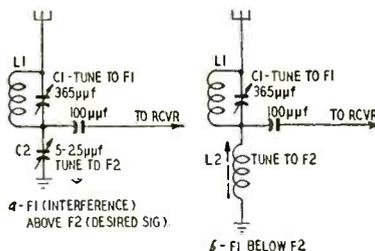If the signal is above the interference frequency, L1-C1 appears as a capacitor to the signal frequency when tuned to F1. In this case, C2 can be replaced by a variable inductor (L2) and the com-




bination tuned to F2 as at *b* in the illustration.

L1 is approximately 110 turns of No. 28 enameled wire closewound in a single layer on a 1½-inch diameter form. L2 is a variable inductor whose value is determined experimentally. You can try various horizontal linearity and width coils and ferrite-core broadcast and shortwave coils to find one that will peak the desired signal at about the center of its range.—*L. David Oliphant*
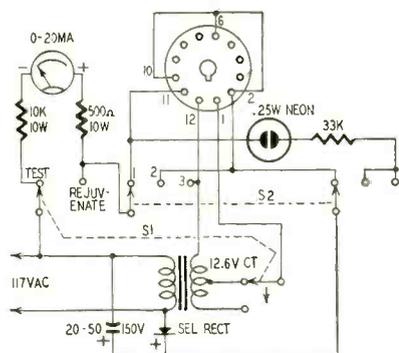
## IMPROVED CRT TESTER

Mr. Cavaseno's cathode-ray tube tester and rejuvenator (August, 1955) is a handy and useful instrument. The diagram shows how I have increased



its versatility by modifying the circuit to provide a test for shorts. The 10-ohm potentiometer in the original was eliminated by using a 12.6-volt center-tapped transformer and making S1 a double-pole switch connected as shown. The auxiliary power supply feature was left out because it was not needed here.

A ¼-watt neon lamp, a 33,000-ohm resistor and a double-pole 3-position switch (S2) provide the short test. Position 1 of S2 is used for testing emission and rejuvenating. Position 2 checks for shorts between cathode and control grid and position 3 shows shorts between heater and cathode. The neon lamp glows in positions 2 and 3 when the resistance between the shorted elements is from zero to over 2 megohms.—*W. G. Eslick*


## NEW R-C OSCILLATOR

Twin-T (also called parallel-T) networks provide almost infinite rejection of one particular frequency. They are commonly used as notch or rejection filters and as tuned peaking circuits when connected in the negative-feedback loop around an amplifier. In the latter application, feedback is minimum at the resonant frequency and amplifier gain is maximum. Noticing that a

badly unbalanced network may cause oscillations when connected in a feedback loop, M. J. Tucker developed a new type of R-C oscillator producing good waveform and requiring only a single-stage low-gain amplifier.

The oscillator is described in detail in *Electronic Engineering* (London, England). The oscillator proper consists of the twin-T network and V1-a.

# Hand size... Voice size...

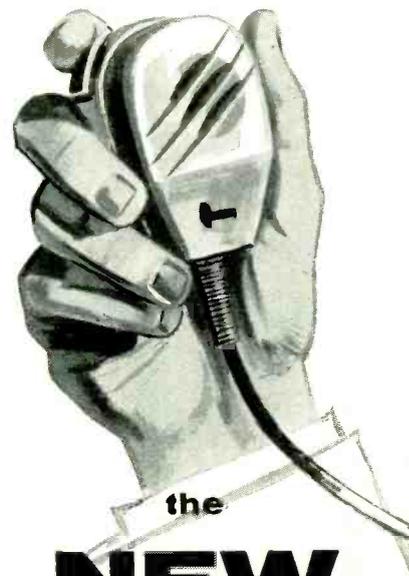

the  
**NEW**

## American "501" Series Microphones

Lightweight, rugged, easy to handle... true-to-life in fidelity of voice pickup. The new American "501" Series presents a complete line of dynamic or carbon hand microphones to improve all types of voice communications.

The attractive styling is completely functional... the gently curved case fits easily into the hand. Positive operation under all conditions is provided by a specially designed cantilever switch. The case is made of die cast aluminum to assure durability and minimum weight.

There's a model for every need:

- Mobile Communications
- Police
- Ship-to-Shore
- Aircraft
- Amateur

To be heard and understood... start with an American Microphone. Write for complete details and specifications today. Ask for Bulletin 501.



**AMERICAN**  
microphone  
company

370 South Fair Oaks Ave., Pasadena 1, Cal.

AN ELGIN NATIONAL WATCH  
COMPANY AFFILIATE

*Sure-Cure  
for  
Replacement  
Headaches:*



# Replace with the **BEST** **OXFORD** **SPEAKERS**

"No more worrying after you've completed your replacement jobs" . . . that's the saying of more and more servicemen every day because they've switched to OXFORD REPLACEMENT SPEAKERS.

We GUARANTEE you products that are built to be replacement speakers. We stand behind each and every speaker with a 100% guarantee against any mechanical or electrical defects for one full year.

OXFORD Replacement Speakers undergo a rigid inspection to make certain that they are as good or better than the original speaker. That's why more servicemen are switching to OXFORD . . . the replacement speakers for a better job.

*Illustrated literature is available without obligation.*

*. . . at better jobbers!*




## OXFORD ELECTRIC CORPORATION

3911 SOUTH MICHIGAN AVENUE  
CHICAGO 15, ILLINOIS

EXPORT — ROBURN AGENCIES, NEW YORK CITY  
IN CANADA — ATLAS RADIO CORP. LTD., TORONTO

## AVAILABLE AT LAST! METAL-TO-GLASS CONVERSION KITS

FROM THIS — TO THIS

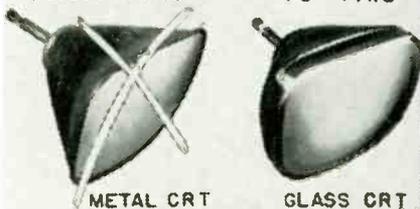

METAL CRT

GLASS CRT

for  
**RCA 21"**  
**TV SETS**  
QUICK — EASY

ONLY **\$5.95** LIST

**ONE MAN — ONE HOUR — IT'S DONE!**

*In Stock at All Leading Parts Distributors*


*Ask Your Jobber*

**COLMAN TOOL & MACHINE CO.**  
Box 6001  
**AMARILLO, TEXAS**

## RADIO-ELECTRONIC CIRCUITS (Continued)

V1-b is the cathode-follower output stage. Output is controlled by the 1-megohm potentiometer in the grid circuit.


The waveform is purest when the

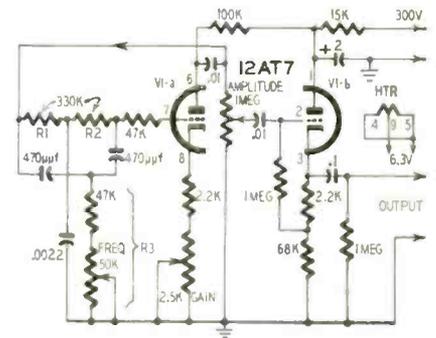

amplifier gain—controlled by the 2,500-ohm potentiometer—is just sufficient to sustain oscillations. The frequency can be varied over a limited range by varying either R1 or R3 alone and readjusting the gain. When R3 is 68,000 ohms, the frequency range is approximately 1,500 to 800 cycles as R1 is increased from 100,000 to 700,000 ohms. Decreasing R1 below 100,000 ohms places an excessive shunt load on V1-a and oscillations cannot be maintained. When R3 is varied between 20,000 and 150,000 ohms, the frequency range is approximately 1,400 to 800 cycles. The 47,000-ohm grid resistor prevents parasitic oscillations.
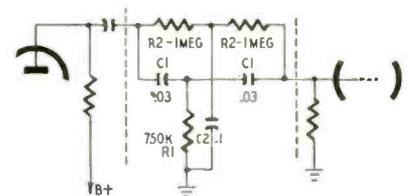
## RUMBLE FILTER FOR 45's

The popular little 45-r.p.m. record changers often produce an annoying rumble when connected to a wide-range audio system. A simple rumble filter will often prevent having to turn down the bass control. L-C filters that completely eliminate the rumble frequency are difficult to design and even harder to get working satisfactorily. They also have a tendency to pick up hum



and introduce it into the audio system.

The filter shown between the dashed lines in the diagram will reduce rumble to a tolerable level and does not readily pick up hum. It is inexpensive and easy to construct. Although designed especially for RCA 45-r.p.m. changers, it can be used with any type. In these cases, it may be necessary to experiment with capacitor values to obtain maximum attenuation.

Connect the filter between the pre-amplifier and amplifier input terminals or between first and second stages of the main amplifier. Insertion loss is low and extra amplification is not needed.

—R. D. Sandison

(The design of a parallel-T network

like that in the rumble filter requires that  $R2$  equal  $2R1$  and  $C2$  equal  $2C1$ . These relationships were not followed closely in this circuit so we assume that the constants were altered to provide optimum performance in this application. The formula for the null frequency of a parallel-T in cycles is  $159,000/R2 \times C1$  or  $159,000/R1 \times C2$ ; where capacitance is in microfarads and resistance in ohms.—Editor)

**A.F. OUTPUT METERS**

Audio fans often need an output meter when an amplifier or receiver is used for feeding a disc or tape recorder. Judging from the letters we have received, many have tried to use standard VU and db meters without much success because they have connected them across voice coil circuits instead of the 500- or 600-ohm circuits for which they are usually designed and calibrated.

The diagrams in Figs. 1 and 2 show simple output meters that can be added to existing equipment. Fig. 1 uses a d.c. milliammeter which may have a full-scale range up to 10 ma, a half-wave instrument rectifier and a pair

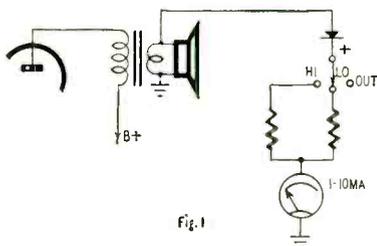


Fig. 1

of calibrating resistors. The values of the resistors are determined experimentally for high and low amplifier outputs.

The circuit in Fig. 2—reprinted from *The Radio Constructor* (London, England)—shows a vacuum-tube diode in

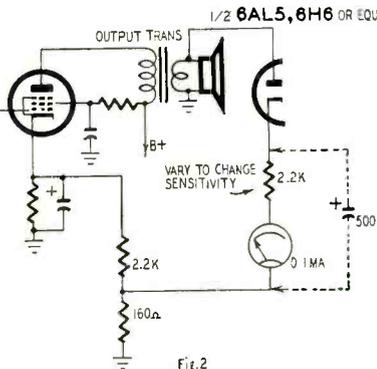


Fig. 2

place of the instrument rectifier. Contact bias in the diode is bucked out by returning the diode cathode to a voltage divider across the cathode of the output stage. The meter can be zeroed by replacing the 160- and 2,200-ohm resistors with a wirewound potentiometer of about 2,500 ohms. A capacitor of several hundred microfarads can be connected as shown by dashed lines to damp the meter movement. END



**TRANS-CONDUCTANCE TUBE TESTER**  
Also Tests Transistors

• Employs improved TRANS-CONDUCTANCE circuit. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers, and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one

meter reading.

• SAFETY BUTTON — protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.

• TESTS ALL TRANSISTORS—including NPN's, PNP's, Photo, Tetrodes, etc. Transistor quality is read on separate meter scale.

Model TV-12 comes housed in rugged portable case. Complete with all instructions — Only **\$7250** NET

Now at your local radio parts jobber.




**SUPERIOR INSTRUMENTS CO.**  
2435 White Plains Road Dept. RC-1, New York 67, N. Y.

**ELECTRONIC ENGINEERS**

To work on engineering problems in development of new Regulated AC and DC supplies, transistors, semi-conductor circuitry and magnetic amplifiers. BEE, or BS with physics or math major, plus some allied experience.

**SORENSEN & COMPANY, INC.**  
375 Fairfield Avenue Stamford, Conn.

**World's First F-M Pocket Radio**

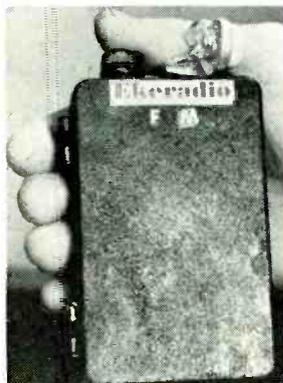

(THIS IS THE 5th year) USING A PRINTED CIRCUIT. Tunes 88 to 107.6 megacycles, self contained, operates on miniature batteries inside the case. NO ANTENNA OR GROUND NEEDED. CAN BE USED AS A TUNER WITH YOUR CAR RADIO OR ANY AMPLIFIER. BE THE FIRST IN THE NEIGHBORHOOD TO OWN ONE. THE COMPLETE KIT WITH A HIGH FREQUENCY TUBE AND A CLEAR PLASTIC CASE.

**ONLY \$9.95**

**SPECIAL EARPIECE \$5.95 BATTERIES \$3.50**

new now a printed CIRCUIT T-V ANTENNA

(smaller than a TRANSISTOR ONLY \$1.98. ALL WAVE RADIO KIT TUNES BROADCAST AND 160 to 10 meters ONLY 4 1/2 oz. \$5.95. TWO BAND 8 oz. BATTERY EMERGENCY RADIO RECEIVER ONLY \$24.95 READY TO PLAY WITH BATTERIES AND EARPIECE.

**EKERADIO ELECTRONIC DEVELOPMENTS**  
646 N. Fair Oaks Ave., Dept. "G", Pasadena, California

TO INTRODUCE YOU TO THE MIRACLE OF TRUE HIGH FIDELITY RECORDINGS  
**10 Major Works**

**BACH**

Tecato and Fugue in D Minor

**CHOPIN**

Ponte-Isle-Les-Bains, Opus 66

**BEETHOVEN**

Piano Sonata No. 24 in F Sharp, Opus 78

**MUSSORGSKY**

Night on Bald Mountain

**VIVALDI**

Concerto in C for Two Trumpets and Orchestra

**MOZART**

Symphony No. 26 in B Flat, K. 184

**BRAHMS**

The Academic Festival

**BERLIOZ**

The Roman Carnival

**WAGNER**

Die Meistersinger, Prelude, Act 1

**DUKAS**

Sorcerer's Apprentice

COMPLETE TO THE LAST NOTE!

Yes, all works complete on two EXTRA-Long Playing discs.

**\$1**  
Take all 10 for just one dollar!

try them **FREE**

Don't pay until AFTER you've heard them. No Strings Attached! No purchase obligation ever. Full membership privileges.

Performed by world-famous artists and orchestras. Custom recorded on quiet vinylite with full range high-fidelity—50 to 15,000 cycles! Now, take all these 10 Masterpieces for free home trial! After 5 days send only \$1 as payment in full for all 10, or return them. We make this amazing offer to show you the quality of our recordings and acquaint you with our no obligation Membership plan. See coupon for details, and mail today — without money — for your 10 Masterpieces.

The Musical Masterpiece Society, Dept. 52-1  
43 West 61st Street, New York 23, N.Y.  
Rush 10 Masterpieces for free trial. After 5 days I'll send only \$1 plus shipping or return them. Enroll me as Trial Member. Privileges: No purchase obligation ever. Advance notice of releases. Free trial or any disc. May return any disc. May cancel membership at any time. For future l.p. discs I keep I'll pay only \$1.65 each plus shipping.

Name.....  
Address.....  
City..... Zone..... State.....  
Canada: 105 Bond Street, Toronto 2, Ont.

## OPPORTUNITY ADLETS

Rates—45c per word (including name, address and initials) Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for March issue must reach us before January 15, 1956.

**Radio-Electronics, 25 W. Broadway, New York 7, N. Y.**

**ENGINEERING DEGREES** earned through home study. American College of Engineering, Box 27724 (AD), Hollywood 27, Calif.

**HIGH-FIDELITY SPEAKERS REPAIRED.** Amprite Speaker Service, 70 Vesey St., New York 7, N.Y. BA7-2550.

**MAKE** an easier living tape recording. Write **BILINA STUDIOS**, Ridgefield Farm, New Jersey.

**BUY** Surplus Radio, Electronic Equipment direct from Government. List \$1.00. Box 169RAC, East Hurd 8, Conn.

**SPEAKER RECONING:** Guaranteed workmanship. C&M Becone Co., 255 Tioga St., Trenton 9, N.J.

**RCA, Motorola, Link, GE and Kaar** new and used two-way radio equipment bought and sold. Communications Associates, 138-17 Springfield Blvd., Springfield Gardens, N. Y. Phone LA 7-2727.

**RULE OTHERS WITH THOUGHTS.** (Full course.) \$2. Delmar Wisdom, 846-85, Sunnyside, Chicago 40.

**"LESS COMPLAINTS,"** report television engineers everywhere, comparing the **OCTO-TENNA** with other antennas. Sample \$2.50, Postpaid. **DERR**, 1018 Taylor, Vallejo, Calif.

**DIAGRAMS FOR REPAIRING RADIOS \$1.00.** Television \$2.00. Give Make, Model, Diagram Service, Box 672-RE, Hartford 1, Conn.

**BIG MAILS—ALL TYPES OF OFFERS:** Your name in our Directory. Once 10c; 3 listings 25c. **DON ENTERPRISES**, Box 186-A, Hialeah, Fla.

**U.S. CIVIL SERVICE TESTS!** Training until appointed. Men—Women, 18-55. Start high as \$350.00 month. Many jobs open. **Qualify NOW!** Get **FREE** 36-page illustrated book showing salaries, requirements, sample tests. **WRITE:** Franklin Institute, Dept. L-54, Rochester, N.Y.

**TV FM ANTENNAS, ALL TYPES.** Mounts, accessories. Lowest prices. Wholesale Supply Co., Lunenburg 2, Mass.

**HI-FIDELITY SPECIALS:** Collaro RC-51, Ronnette Flip Cartridge, Mounting Board—\$28.75 prepaid. Monarch of England, Top Quality 4 pole Motor Changer, GE RPX-950—\$38.75 prepaid. Any Diamond Stylus, \$13.75. Boxed, Year Warranty, LP Records, Fresh, Sealed RCA, Columbia, all brands, 20% off, prepaid, send list. Our best buy HI-FI System—\$225.50 prepaid, write for details. **FIDELITY UNLIMITED**, 65-03 39th Ave., Woodside 77, N.Y. Latest Webeor Changer-Flip Astatic Cartridge, \$28.75 prepaid.

**TUBES—TV, RADIO, TRANSMITTING, AND SPECIAL PURPOSE TYPES BOUGHT, SOLD AND EXCHANGED.** Send details to R. E. Gensler W2LNI, 512 Broadway, N.Y. 12, N.Y.

**FOREIGN JOBS—Latin America, Alaska, Canada,** up to \$1500 monthly. Up-to-date 1956 Foreign Service Directory gives complete information; hot list of firms hiring for Military and Civilian Construction, Aircraft, Oil, Exporters—Importers, Mining, \$1.00. How-When-Where to apply. 9th successful year! **GLOBAL REPORTS**, Box 883-RE, Hollywood 28, Calif.

**POCKET** Rubber Stamp, plastic case, self inking, \$1.00 air mailed postpaid, **HADFIELD STAMPS**, Dept. RE, 205 W. Cross-timbers, Houston 18, Texas.

**ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING** equipment repaired. Write for free catalogue on new and used instruments at a savings. **Hazelton Instrument Co.**, 128 Liberty Street, New York, N. Y.

**1,000 BUSINESS CARDS**, \$2.99, Samples free. **HONTZ**, 1069-R Hill, Phillipsburg, N.J.

**TRADIN TV SETS \$14.** Jones TV, 1115 Ramber, Pottstown, Pa.

**TAPE RECORDERS**, tapes; Wholesale prices. **KARSTAN**, 215 E. 88 St., New York 28, N.Y.

**WHOLESALE RECORDERS, TAPES,** Radios, Phonographs. Catalog. **TOWERS**, Box 155, Philadelphia 5, Pa.

**INVENTORS:** If your invention is adaptable to promoting we will contract on cash or royalty. If not, we will attempt selling it for you. Special booklet free. **KESSELER Corporation**, 171, Fremont, Ohio.

**WANTED: AN/APR-4, other "APR.", "TS-", "TE-", ARC-1, ARC-3, ART-13, BC-348, etc.** Microwave Equipment. Everything Surplus, Special tubes, Test Manuals, Lab Quality Equipment, Meters, Fast Action, Fair Treatment, Top Dollar! **Littell**, Fairhills Box 26, Dayton 9, Ohio.

**BUY WHOLESALE**, 25,000 Items, Catalog 25c. Matthews, 1472-14, Broadway, N.Y.C. 36.

**DIAGRAMS:** Professional Model Timers, Counters, Intercous, Organs, etc. \$1.00 each, List free. **Parks**, 101 S.E. 57th, Portland 13, Oregon.

**PRINTING—Letterheads, 6 1/2 envelopes, statements, 250 for \$2.50, Postpaid, FOOT BOY RE**, Box 1053, Little Rock, Ark.

**RADIO, RADAR, TELEVISION** instruction leading to Licenses. Port Arthur (Texas) College.

**FOREIGN** jobs list. Technicians needed. \$1. **BATHE**, Box 173, New Orleans 3, La.

**CODE** speed information free. **DON ROGERS**, Debois Ave., Island, Pa.

**"Build juvenile ORGAN, 30 keys, 3 tubes, 2 watts. Use with HI-FI. Complete plans only \$1.00. Dept. RE. SOLOTRON CO.** Farmington, Mich.

**PARTS** and Equipment, List free. **ART SORRELL**, Riverdale, Maryland.

**UNEQUALLED** promotion service for patented or unpatented inventions. Particulars, Forms, Invention Recording, advice, etc. Free. **SUPERIOR**, 342-344 North Rodeo, Beverly Hills, Calif.

*High Fidelity Magic...*



from **EICO®**

**KIT \$49.95**  
Factory Wired \$79.95

### NEW! 20-WATT HIGH FIDELITY AMPLIFIER #HF20

Due to its Ultra-Linear output stage with its conservatively-rated Ultra-Linear output transformer, the #20 features negligible distortion & increased power-handling capacity at both extremes of the audio spectrum. Costliest, complete equalization facilities—plus low-distortion, wide-range tone controls & Centralab Compentrol loudness control—create a preamplifier and control section unsurpassed even in units ticketed at much higher prices.

- Power Response (20W): ±0.5 db 20-20,000 cps; ±1.5 db 10-40,000 cps.
- Frequency Response (1/4W): ±0.5 db 13-35,000 cps; ±1.5 db 7-50,000 cps.
- Rated Power Output: 20 w (34 w peak).
- IM Distortion: (60 cps; 6 kc/4:1) at rated power: 1.3%.
- Mid-Band Harmonic Distortion at rated power: 0.3%.
- Maximum Harmonic Distortion (between 20 & 20,000 cps at 1 db under rated power): approx 1%.
- Speaker Connection Taps: 4, 8 & 16 ohms.
- High quality preamp-equalizer & control section plus complete 20-watt Ultra-Linear Williamson-type power amplifier. Output transformer in compound-filled seamless steel case.

See and HEAR it at your neighborhood distributor. Write for **FREE** Catalog CA-1

**EICO®** 84 Withers St., Brooklyn 11, N. Y.  
Prices 5% higher on West coast © 56

# ATTENTION . . .

## Service Technicians' Associations Club Members Student Groups

Special subscription rates to **RADIO-ELECTRONICS** are available to associations, clubs, schools, employee groups, etc. For information write—

G. Aliquo  
**RADIO-ELECTRONICS**  
25 West Broadway  
New York 7, N.Y.

**CLOSED CIRCUIT  
and INDUSTRIAL  
TELEVISION**  
By Edward Noll

**COMMERCE! INDUSTRY! EDUCATION!**

*The Future of Television*

The television camera is moving out of the station and studio and into industry. Make the knowledge you already have really pay-off. Get ahead in a growing field!

Complete Technical Details on:

- Transmission Systems
- Sync & Deflection Generators
- Scanning Processes
- Closed-Circuit Cameras
- Composite Picture Signals
- Video Amplifier Systems

- Learn How To:
- Construct
  - Install
  - Operate
  - Service
- Closed-Circuit Systems

NOT A HANDBOOK! NOT A GUIDE! A COMPLETE EDUCATION!

**CLOSED-CIRCUIT AND INDUSTRIAL TELEVISION: by Edward Noll \$4.95 (Prob. Price)**

Send your order today. If not completely satisfied within 10 days, return without any obligation.

*The Macmillan Company*  
Department RE, 60 Fifth Avenue, New York, New York

# Question Box

## CONVERTING 6-VOLT RADIOS FOR 12-VOLT MOBILE OPERATION

Please print details for converting 6-volt auto radios and 2-way mobile equipment to operate from 12-volt batteries.—E. E. P., Pittsburgh, Pa.

Most manufacturers of two-way radio equipment will now convert the units for 12-volt operation at a nominal charge. This is the most practical method. If the equipment is to be transferred back and forth between vehicles with 6- and 12-volt ignition systems, you can use one of the new converters that deliver 6 volts d.c. output with 12 volts input. One of these is the Carter *Change-A-Volt* dynamotor and the other is a synchronous vibrator and transformer arrangement made by Motorola.

Of course, you can also replace the tubes with 12-volt equivalents or wire their heaters in series-parallel for 12-volt operation and replace the B supply with a 12-volt type.

The most practical method of converting auto receivers is to replace the tubes, vibrator and vibrator transformer with equivalent 12-volt types. Suitable transformers with a wide range of voltages and currents are made by such manufacturers as Hall-dorson, Merit, Stancor and Thordarson. Cornell-Dubilier, James, Mallory, Radiart and others make 12-volt vibrators.

If you don't want to replace the tubes with 12-volt types, you can rewire the heater circuits in series-parallel strings as shown in the diagrams. Figs. 1, 2 and 3 show possible revisions in the


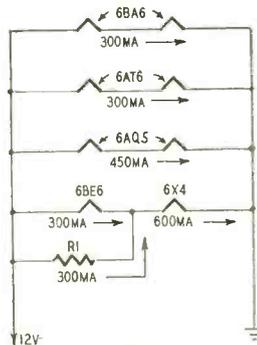


Fig. 1

heater circuit of a typical 8-tube auto radio. Wherever possible, divide the tubes into series strings that draw the same current. In Fig. 1, the 6AQ5's with their 450-ma heaters are in one string, the 6BA6's with 300-ma heaters in another and so on. The 6X4 with its 600-ma heater is connected in a
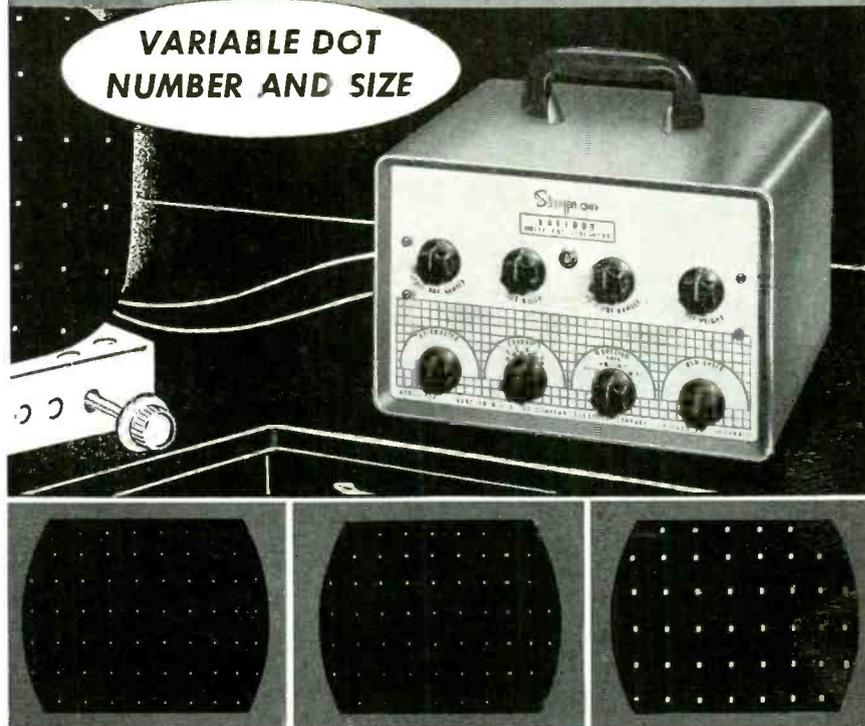
# NEW! NEW! NEW! Simpson VARIDOT WHITE DOT GENERATOR model 434



(Actual Photographs)

Provides white dot patterns with VARIABLE dot size (from 1 to 8 scanning lines, with corresponding dot widths), and variable dot number from 6 to 12 horizontal dots, and 6 to 12 vertical dots. Modulated RF output is available, operating on fundamentals from Channel 2 to Channel 6.

## THE ONLY WHITE DOT GENERATOR THAT LETS YOU MATCH ANY RECEIVER MANUFACTURERS' RECOMMENDATIONS

You can make convergence adjustments on color-TV receivers faster and better with the new Simpson Varidot. Use for linearity adjustments on both color and black and white.

Vertical and horizontal synchronization assures you of correct aspect ratio . . . ample attenuation . . . 300 ohm RF output.

Adjustable dot size provides a check of receiver transient response. Positive or negative video

output is excellent for accurate and fast checking of transient response of video amplifiers.

Use the new Simpson Varidot for hum checking both color and black and white receivers—a rare feature in test equipment at this price.

Portable: Approx. 11½ lbs. Housed in Simpson gray case.

Complete with Output Cables and Operating Instructions **\$147<sup>50</sup>**

See Your Electronics Parts Distributor, or write


**Simpson ELECTRIC COMPANY**

WORLD'S LARGEST MANUFACTURER OF ELECTRONIC TEST EQUIPMENT

5200 W. Kinzie St., Chicago 44, Illinois  
Phone: Estebrook 9-1121  
In Canada: Bach-Simpson Ltd., London, Ontario

# CROWN

## Professional Tape Recorder

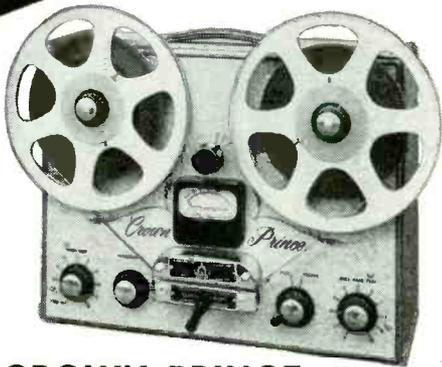

**CROWN PRINCE**

**Breaks Sound Barrier**  
**20-20,000 CPS usable at 7 1/2 IPS**

The only Complete Professional Recorder as a single easily portable unit using 10 1/2" reels . . . Three speeds: 15, 7 1/2, 3 3/4 IPS . . . 10 1/2" Reels—can be rack mounted . . . Hi-Z Mike and Phono Input . . . Cathode Follower Output . . . Size: 19" x 14" x 7 1/2". Wt., 38 lbs.

**Dual Track—\$349.50 Full Track—\$399.50**

Complete less case  
Write for literature.  
Address Dept. RE-1

**SPECIFICATIONS**

- "Micro-Linear" Heads
- Three Speeds
- Three Motors
- Meets NARTB Standards
- "Micro-Sync" Timing
- Straight Line Threading
- 4" Dual Lighted Meter
- Magnetism Braking
- Perfect Erasure

★ ★ ★ ★

**GUARANTEED**

Record & Playback Performance

IPS	15	7 1/2	3 3/4
% WOW	.12	.18	.25
DB	±2	±2	±3
CPS	20 to 22,000	30 to 16,000	30 to 10,000
NOISE RATIO	55	52	44

for Full Track Heads

**INTERNATIONAL RADIO & ELECTRONICS CORP.**

Elkhart Indiana

**GET INTO ONE OF THESE GREATER OPPORTUNITY FIELDS**

# Electricity or Radio-Television

**TRAIN IN THE GREAT SHOPS OF COYNE**

OLDEST, BEST EQUIPPED SCHOOL OF ITS KIND IN U. S.

Prepare for your future NOW. Get practical training in TELEVISION—RADIO—ELECTRICITY—ELECTRONICS—all vital in Industry. Prepare now for a better job that also offers a real future in the years ahead. Learn on real equipment at Coyne—no advanced education or previous experience needed.

**Approved for Veterans—finance plan—enroll now, pay most of tuition later. Part time employment service while training if needed.**

**FREE BOOK** Clip coupon for Big Free Illustrated Book. No Salesman will call. Act NOW.

**B. W. COOKE, President**

## COYNE ELECTRICAL SCHOOL

A TECHNICAL TRADE INSTITUTE OPERATED NOT FOR PROFIT

500 S. PAULINA, CHICAGO, Dept. C16-81H

ELECTRICITY • TELEVISION • RADIO • REFRIGERATION • ELECTRONICS

**B. W. COOKE, Pres.**  
COYNE ELECTRICAL School  
500 S. Paulina St., Chicago 12, Ill. Dept. C16-81H

Send FREE BOOK and details on:

RADIO-TELEVISION  ELECTRICITY

NAME.....  
ADDRESS.....  
CITY..... STATE.....

Need a Tube Tester?

## FOLLOW THE LEADER...

Buy **EICO**



© 1955

**TUBE TESTER #625**  
**KIT \$34.95 Wired \$49.95**

- Tests latest 600-mil series string type tubes.

**More Servicemen buy EICO TUBE TESTERS**—in KIT and wired form—than any others sold through distributors. Why? Because EICO gives you the MOST value at LOW-EST cost.

- Test all conventional & TV tubes and pilot lights.
- 10 individual lever-type element switches.
- Illuminated anti-backlash rollochart kept up-to-date by EICO's Engineering Dept.
- 4 1/2" meter, 3-color "Good-Bad" scale.
- Line-adjust control. Blank socket for new tubes. Protective overload bulb.



**In stock at your local jobber. Write for free Catalog CT-1** Prices 5% higher on West Coast.

**ELECTRONIC INSTRUMENT CO., INC.**  
84 Withers Street • Brooklyn 11, N. Y.

**QUESTION BOX** (Continued)

series string with a 300-ma 6BE6 so a shunt resistor (R1) is added to carry the excess current (300 ma) around the 6BE6.

Fig. 2 shows an arrangement that eliminates the shunt resistor. Here, two 300-ma tubes are paralleled and connected in series with the 6X4 across

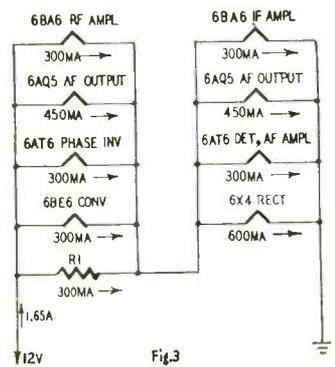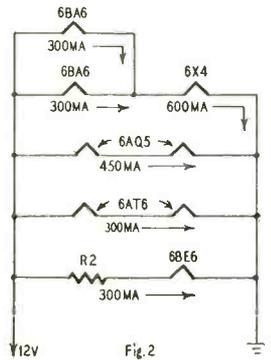


the 12-volt circuit. Resistor R2 provides a 6-volt drop in series with the 6AV6.

Fig. 3 is a third arrangement in which the tubes are divided into two parallel strings that are then connected in series. The sum of the heater currents must be equal in each branch so shunt resistor R1 is added to one side to balance the excess current drawn by the 6X4.

Fig. 4 is a possible heater circuit in a typical 5-tube auto radio. Both series and shunt resistors are needed here. R1 bypasses excess current drawn by the 6AS5 and R2 drops the voltage to 6.3 for the 6AV6.

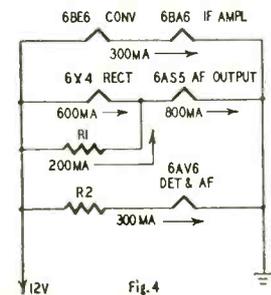A shunt resistor (R1 in the diagrams) is always used across the heater of a tube (A) whose current rating  $I_A$  is less than the maximum flowing in a series circuit. This maximum current ( $I_B$ ) is drawn by tube B. The resistance of R1 in ohms is found from the formula  $E_A / (I_B - I_A)$  where  $E_A$  and  $I_A$  are heater voltage and cur-



rent (in amps), respectively, of tube A and  $I_H$  is the heater current of tube B in amps.

For example, if a 300-ma heater is in series with one drawing 600 ma as in the case of the 6BE6 and 6X4 in Fig. 1, the resistance of R1 is  $6.3/0.6 - 0.3$  or 21 ohms and the wattage dissipated is  $E_A(I_H - I_A)$  or  $6.3 \times 0.3$ . In practice, a 20-ohm 5-watt resistor can be used.

Voltage-dropping resistors R2 are determined by the formula  $(E_{supply} - E_{tube})/I_{tube}$ . In Figs. 2 and 4, R2 is  $(12.6 - 6.3)/0.3$  or 21 ohms. The wattage is computed in the same way as R1.

**POWER SUPPLY CIRCUIT**

Please print the circuit of a power supply using a transformer with a 220-volt 50-ma secondary. I want to use full-wave rectification to simplify filtering.—H. L., Chicago, Ill.

The diagram in Fig. 1 shows a full-wave bridge type selenium rectifier. You can purchase a composite bridge

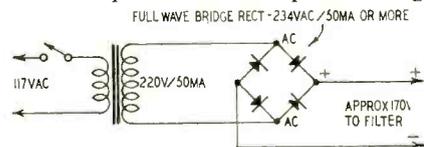


Fig. 1

or you can make up one with 130-volt 50-ma selenium rectifiers. It is desirable to use two such rectifiers in series (plus terminal of one to the minus terminal of the other) in each arm of the bridge to increase the safety factor. This circuit will deliver approximately 170 volts to the filter. The output

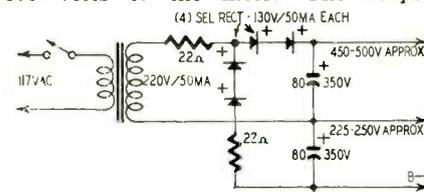


Fig. 2

voltage will then rise to around 240, depending on the value of the input filter capacitor and the load current.

Fig. 2 is a full-wave voltage doubler type supply delivering maximum voltages of around 250 and 500 at two output terminals. END

**Radio Thirty-Five Years Ago**  
In Gernsback Publications

**HUGO GERNSBACK, Founder**

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of ELECTRICAL EXPERIMENTER on file for interested readers.

**In January, 1922 Science and Invention**  
(formerly Electrical Experimenter)

- Shall I Take Up Engineering?, by H. Winfield Secor
- Ultra High Speed Atoms—and Their Effects, by Rogers D. Rusk, M. A.
- Radio Central, by Arthur H. Lynch
- Jazz From the Air, by Robert E. Lacault



14th EDITION

**RADIO**  
*Handbook*

The most extensive list of equipment descriptions ever bound between two covers!

- A-C & D-C CIRCUITS
- SEMI-CONDUCTORS
- V. T. PRINCIPLES
- V. T. AMPLIFIERS
- OSCILLOSCOPES
- R-F V. T. AMPLIFIERS
- SPECIAL V. T. CIRCUITS
- RECEIVER FUNDAMENTALS
- R-F ENERGY GENERATION
- AMPLITUDE MODULATION
- FM TRANSMISSION
- SSB TRANSMISSION
- TRANSMITTER DESIGN
- TV & BC INTERFERENCE
- TRANSMITTER KEYING
- WORKSHOP PRACTICES
- ANTENNAS, H-F, V-H-F, U-H-F & BEAMS
- RADIATION, PROPAGATION & TRANSMISSION LINES

- MOBILE EQUIP. & INSTALLATION
- 1-Tube Mobile Converter for 75 Meters
- Mobile Transmitters
- 12-Watt All-Band Mobile Transmitter
- Universal Modulator and Power Unit
- 832-A Transmitter for 144 Mc.
- 12-Watt Fixed/Mobile X-mitter for 225 Mc.
- 1-Kilowatt SSB Mobile Transmitter
- Antennas for Mobile Work
- Constr. & Installation of Mobile Equip.
- Vehicular Noise Suppression

- RECEIVING EQUIPMENT
- "Super-Gainer" Receiver
- Universal Q-5'er
- Simple Preselector for 15 and 10 Meters
- All-Triode Converter for 144 Mc.
- De Luxe 2-Meter Superheterodyne
- C-W Man's Superheterodyne

- EXCITERS & LOW POWER TRANSMITTERS
- 40-Watt All-Band Transmitter
- High Stability VFO Unit
- 220-Mc. Transceiver
- 20-Watt 2-Meter Transmitter
- 75-Watt 2-Meter Transmitter
- 120-Watt 2-Meter Exciter for Use with the Collins & Viking Transmitters
- Versatile VFO-Exciter Unit

- SPEECH & A.M. EQUIPMENT
- Design of Speech Amplifiers & Modulators
- 120-Watt Modulator with Triode 807's
- General Purpose Class B Modulator
- Outboard Clipper-Filter
- 10-Watt Amplifier-Driver
- De Luxe 15-Watt Amplifier-Driver
- 200-Watt 811-A Modulator
- 500-Watt 810 Modulator
- 500-Watt 304TL Modulator

- HIGH FREQUENCY POWER AMPLIFIERS
- Power Amplifier Design—Choice of Tubes
- Push-Pull Triode Amplifiers
- Push-Pull 811-A Triode Amplifier
- Push-Pull Kilowatt Triode Amplifier
- Push-Pull 250-TH Amplifier
- Push-Pull 144 Mc. 4X-150A Amplifier
- Push-Pull 813 Amplifier
- Push-Pull 4-250A Kilowatt Amplifier
- Pi-Network Amplifier Using a 4-125A
- Kilowatt Pi-Network Amplifier
- 4-1000A Pi-Network Amplifier
- 1-Kilowatt Triode Pi-Network Amplifier

- TRANSMITTER CONSTRUCTION
- 350-Watt P.A. for Ranger Transmitter
- The Ranger as Driver for Tetrode Amplifier
- Vikina II as Exciter for 1-Kw. Transmitter
- 300-Watt Phone/C. W. Transmitter
- Other Transmitter Assemblies

- POWER SUPPLIES
- Power Supply Design
- Rectification Circuits
- Standard Power Supply Circuits
- Simple Transformer-type Power Supplies
- Power Supply Components
- Transformer Design
- Special Power Supplies

- TEST EQUIPMENT
- Voltage, Current and Power
- Measurement of Circuit Constants
- Capacitance-Inductance Meter
- Measurements with a Bridge
- Frequency Measurements
- The Grid-Dip Meter
- 1-Tube Sine-Wave Audio Oscillator
- Antenna & Transmission Line Measurements
- Constr. of a Coaxial S-W-R Indicator
- Silicon Crystal Noise Generator

\$7.50 in U.S.A. (plus sales tax)



**BUY FROM YOUR FAVORITE DISTRIBUTOR**

at above price or odd 10% on direct mail orders to:

**EDITORS and ENGINEERS, Ltd.**

SUMMERLAND 3 CALIFORNIA

BOOKSTORES: ORDER FROM BAKER & TAYLOR CO., HILLSIDE, N.J.

**Important Notice to SUBSCRIBERS**

If you're moving, please don't forget to send us your address including the numbers shown beside your name, as well as your new address. If possible, send us your address label from the lower right-hand corner of the front cover.

If we receive this information before the 20th of the month, you will continue getting the magazine without interruption.

Your cooperation will be most helpful and greatly appreciated. Please send your new address to:

Subscription Department, RADIO-ELECTRONICS, 25 W. Broadway, New York 7, N.Y.

**NOW IN STOCK at ALMO RADIO CO.**

1122 French St. Wilmington, Del.  
317 Park Heights Ave. Salisbury, Md.



**COLOR & BLACK & WHITE**  
5" — 5 MC SCOPE

**KIT \$79.95** Wired \$129.50



**INVENTORS**

Send for  
**PATENT INFORMATION**  
Book and  
**INVENTORS RECORD**  
without obligation

**GUSTAVE MILLER**  
RE-125 WARNER BUILDING  
WASHINGTON 4, D. C.

**REGISTERED PATENT**  
**ATTORNEY**

ASSOCIATE EXAMINER  
U.S. PAT. OFF. 1922-1929

Patent Attorney & Advisor  
U.S. Navy Dept. 1930-1947

**PATENT LAWYER**

LABORATORY DESIGNED for  
UHF and VHF! ... It's NEW!

# MOSLEY

## 2-WAY TV ANTENNA SWITCH

- Extremely low Standing Wave Ratio — by actual test!
- Positive rotary action!
- Silver-to-silver contacts!
- Compact size!
- Solderless — easy to install!
- Low cost!

Cat. No. F-40  
List Price  
\$1.95



**Mosley**  
Electronics, Inc.  
8622 ST. CHARLES ROCK ROAD  
ST. LOUIS 14, MISSOURI

Another PREMIUM QUALITY MOSLEY Accessory  
for BETTER TV INSTALLATIONS!

# Technotes



## G-E 825

Excessive brightness on the left-hand side of the screen in this model has been traced to a defective 5V4 damper tube. Replacement will clear up the trouble.—*John Flint*

## GAROD TELE-ZOOM

A defect in the Tele-Zoom circuit has been found to be caused by dirty switch contacts. Clean the contacts with carbon tetrachloride. To eliminate possible future trouble, also clean the relay in the receiver.—*Lyle Briggs*


## PIE CRUST

On a Motorola 71M I found that pie-crust oscillation covering the entire screen was due to the picture-tube mount touching the shield cover of the high-voltage power supply. Cardboard insulation cleared the trouble.—*Monty Britt*
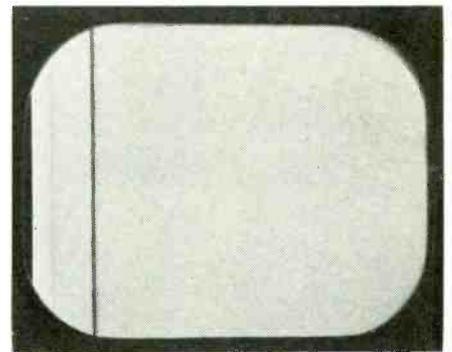
## BLACK VERTICAL LINES

These appear on the left side of the raster and are usually due to Barkhausen oscillation (see photo) in the horizontal output tube.

Remedy: Replace horizontal output tube. Check adjustment of horizontal drive and linearity controls. Bond power



supply and receiver chassis (if separate) together with copper strip or plate. Dress antenna lead-in away from power supply. Install and adjust small permanent magnet on horizontal output tube. Install coaxial transmission line (RG/59/U in strong signal areas, lower-loss RG/11/U in fringe areas). Ground coax shield to antenna connector shield.—*B. J. de Lentore*

## TVI ON AM RECEIVERS

This appears in the form of heterodyning, "birdies" hash, buzz or squeals.

Possible causes: Defective damping tube. Defective horizontal output tube. Incorrect adjustment of horizontal

## NOW!

Step ahead faster  
as an

## INDUSTRIAL ELECTRONICS TECHNICIAN



Turn your experience into a  
big, new better-paying career!

Day by day industrial plants are adding more electronic devices—for sorting, counting, checking almost any control job you can name. Cash in on industry's great need for men who can keep these devices in top working order. Make more money, feel more secure, doing work that is second nature to you. With what you already know about electronics you have a long head start in a field just beginning to boom. GET INTO IT RIGHT NOW with the help of

## PRACTICAL INDUSTRIAL ELECTRONICS LIBRARY

No long sessions on math or theory! These 4 practical volumes show you how to keep the plant's electronic equipment working . . . how to locate and correct tube and circuit troubles . . . how to install, service, and maintain even brand new equipment without being stumped by new circuits.

FREE TRIAL—EASY TERMS!

4 volumes (1390  
pp., 1050 illus.)  
Chute's Electronics  
in Industry

Miller's Maintenance Manual of Electronic Control

Markus & Zetoff's Handbook of Industrial Electronics Circuits

Henney & Fahnestock's Electron Tubes in Industry

McGraw-Hill Book Co., Att: H. W. Buhrow  
Industrial and Business Book Dept. RE-1,  
321 W. 41st St., N.Y.C. 36

Send me the Practical Industrial Electronics Library for 10 days' examination on approval. In 10 days I will send \$2.50, then \$4.00 a month until \$22.50 is paid. (A saving of \$3.50 under the regular price of \$26.00.) Otherwise I will return books PostPaid. (Print)

Name .....  
Address .....  
City ..... Zone ..... State .....  
Company .....  
Position ..... RE-1

For price and terms outside U.S. write  
McGraw-Hill Int'l., N.Y.C.

## ADAPTER



Write for Bull. 3548

TYPE 7B \$2.25

TYPE 8B \$2.50

TYPE 9B \$2.75

(ILLUSTRATED)

plus shipping chgs.

- Min. size for use in crowded spaces
- RETMA color coded terminals
- Uses (All above chassis)

1. Modify circuits for max. performance and testing without soldering or unsoldering.
2. Break into any circuit for trouble shooting.
3. Measure voltage, resistance and current in conjunction with standard instruments.

A. L. PRODUCTS CO., INC.

—311 Hickory St., Kearny, N.J.—

## Give to the MARCH OF DIMES

DON'T JUST SAY CAPACITORS

DON'T JUST SAY CAPACITORS

**Ask For Sprague By  
Catalog Number**

Know what you're getting  
... get exactly what you  
want. Don't be vague...  
insist on Sprague. Use  
complete radio-TV service  
catalog C-610. Write  
Sprague Products Company,  
81 Marshall Street,  
North Adams, Mass.

SPRAGUE®

WORLD'S LARGEST  
CAPACITOR MANUFACTURER

linearity control. Improper shielding of high-voltage power supply. Antenna lead-in unshielded or too close to deflection yoke or high-voltage leads. Unshielded yoke or improper dressing of yoke leads. Direct radiation from grid or anode of picture tube (this is especially prevalent in late-model large-screen sets and in metal-cone picture tubes). Radiation through a.c. power line. Remedies: Replace damper tube (in some early sets the 6W4 damper used a separate heater transformer which had no electrostatic shield. Check this possibility). Replace parasitic or oscillating horizontal output tube. Adjust set for good horizontal linearity with test pattern or bar-dot generator. Reduce horizontal drive if possible without affecting size or quality of picture. Shield the high-voltage power supply with copper screen; ground screen to receiver chassis. Re-dress lead-in away from deflection yoke leads and high-voltage circuits. Shield yoke leads with tinfoil and ground. Re-dress high-voltage leads. Install high-pass filter in TV antenna leads (as close as possible to tuner) to prevent radiation through antenna. Bypass each side of the a.c. line to ground with a .02  $\mu$ f capacitor (or in some cases, .05  $\mu$ f).—John B. Ledbetter

**WHITE VERTICAL LINE**

Trouble is a line that may change or shift when horizontal hold is adjusted. (Same trouble may appear as "veneer" effect on side of screen.)

Possible Cause: Misadjustment of horizontal a.f.c. transformer.

Remedy: Readjust transformer; see that horizontal hold control covers its normal range. If circuit is unstable, check or replace horizontal a.f.c. control tube and realign transformer if necessary. If trouble remains, check horizontal discriminator transformer or coupling capacitor in this circuit. This trouble can also be due to sync generator misadjustment or a defect at the TV station. Check on two or more stations.—L. B. Johnson

**SLOW "AIRPLANE TYPE" FLICKER**

This is so called because it resembles the effect produced by an airplane flying overhead. It may be due to fluctuating line voltage, faulty receiver installation or a defective tube.

To check, measure the line voltage with an undamped 0-150-volt a.c. voltmeter. If variations are excessive, call the service department of local electric utility company for proper action. (In rural or remote areas, a suitable constant-voltage transformer at the set may be necessary.) Check the installation, and correct obvious faults (loose or swaying lead-in, antenna, etc.). Replace defective video i.f. tube. Low line voltage will also result in poor definition in some receivers due to video stages operating at improper bias and plate voltages. Remedies are same as above.—Johti Lehte END

# FREE! BA's NEW 1956 CATALOG



**YESSIR-IT'S THE KING-SIZE CATALOG—**  
**164 "KING-SIZED" (8 1/4 x 10 1/2) PAGES**  
**OFFERS MORE ITEMS PER PAGE--IT'S EASIER TO USE...IT'S EASIER FOR YOU TO ORDER**

**COMPLETE GUIDE TO EVERYTHING IN RADIO, TV, ELECTRONICS**

**100'S OF BRAND NEW ITEMS LISTED HERE FOR THE VERY FIRST TIME**

**INCLUDES 21 BIG PAGES OF BARGAINS NOT FOUND IN ANY OTHER CATALOG**




*A Complete Buying Guide for Everything in-*  
**RADIO TELEVISION ELECTRONICS**

**BURSTEIN-APPLEBEE CO.**  
 1012-14 McGEE ST., KANSAS CITY 6, MISSOURI

**RUSH COUPON FOR THIS BIG CATALOG NOW!**

Send Free B-A Catalog No. 561.

NAME \_\_\_\_\_  
 ADDRESS \_\_\_\_\_  
 CITY \_\_\_\_\_ STATE \_\_\_\_\_

**LMB BOX CHASSIS**

Flangelocking Precision Engineered Interlocking

65 sizes and shapes for the laboratory, manufacturer, industrial, experimenter, builder, and general applications where metal boxes are required. Stocked by all electronic and geophysical distributors. Send for free catalog.

**LMB** 1011 Venice Blvd. Los Angeles 15, Calif.

**"QUIET T. V. LISTENING"**

with the original Portable FLORITONE—quality Extension Speaker. "For Late Evening Programs—"For hard of Hearing"—in spun aluminum base—revolves any position—5" P.M. Speaker—20 ft. cord—4 way switch control, in colorful acoustic fiber glass cone—in white—blue—coral—gold yellow and gray. Model # 100—\$14.95 list—Sample \$8.00—Model # 200 with volume control—List \$19.95—Sample \$10.

Sootlin's—321 N.W. 3rd Ave., Miami 36, Fla.

**NOW IN STOCK at NIDISCO**

**TEICO** NEW

**COLOR & MONOCHROME Laboratory & TV SERVICE 5-MC SCOPE**

713 Newark Av., Jersey City, N.J.  
 55 State St., Hackensack, N.J.  
 294 Passaic St., Passaic, N.J.  
 658 Anterson Av., Cliffside, N.J.  
 128 S. Warren St., Trenton, N.J.




**KIT \$79.95**  
 Factory Wired \$129.50
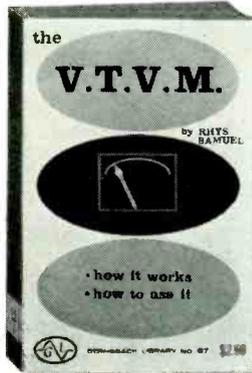
# Do you really know how to use your **V. T. V. M.?**

The vacuum-tube voltmeter is the one instrument you *must* understand and know how to use for servicing or industrial or laboratory test work. Here at last is a brand new book which gives you *all* the facts on this essential instrument. It takes you inside the V.T.V.M. and analyzes each V.T.V.M. circuit carefully so that you can fully understand *why* and *how* the V.T.V.M. works. It shows you how to use it in many new and different ways. This book will give you inside tips on how to use the V.T.V.M. for TV trouble shooting, AM and FM alignment and repair, show

you how to check components, take voltage measurements, find the causes of hum, a.g.c. circuit troubles, and intermittents, and how to use the V.T.V.M. for signal tracing. In short, how to get the most out of the V.T.V.M. in every possible servicing and testing situation, as well as for audio, ham, and miscellaneous applications. This book can be your right hand man when it comes to using the V.T.V.M. Keep it right on your work bench when you tackle tough jobs. Look over this partial list of contents and see all it can do for you.



## THE V.T.V.M.

By Rhys Samuel

224 Pages. Approx. 175 Illustrations. Gernsback Library Book No. 57. Paper-cover edition... \$2.50  
Deluxe hard-cover edition ..... \$4.00

## Some things you can learn from this book

### Instrument characteristics—

Low circuit loading in voltage measurements • High sensitivity • Burn-out-resistant meter circuit.

### How the V.T.V.M. works—

The bridge circuit • D.C. voltage divider network • Resistance-measurement network • A.C. voltage measurements • Frequency response • Power supply.

### Meter scales—

Scale divisions • Linear, nonlinear, and zero center scales.

### Probes and cables —

Direct, isolating, rectifying, peak-to-peak, and multiplier probes • Grounding the probe • Limitations of the V.T.V.M.

### Using the V.T.V.M.—

Front panel controls • How to take measurements • TV trouble shooting—Trouble shooting components, tuners, picture and sound i.f. amplifiers • Trap alignment • Defective picture tubes.

### AM-FM alignment and repair—

Tube failures • Component failures • Signal tracing • Checking power supplies • Hum • Intermittents • R.f. and i.f. alignment • FM receivers.

### Servicing audio amplifiers—


Trouble shooting and signal tracing • Eliminating hum • Frequency response measurements • Checking phonograph equalizers.

### The V.T.V.M. in the ham shack—

Testing the transmitter • Checking oscillator, amplifier and multiplier stages • Adjustment of high-power amplifiers • The V.T.V.M. as a field strength meter.

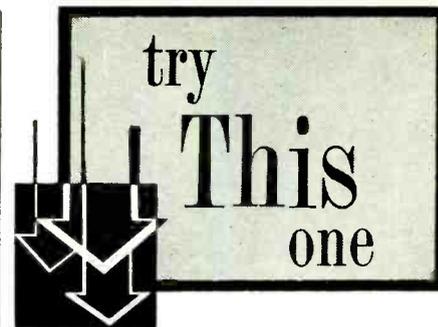
### Miscellaneous applications—

Calibrating voltage output of generators and oscillators • Checking battery voltages, transformers, gassy tubes • Calibrating a scope • Hints and kinks.


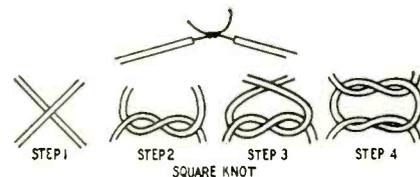
## SPlicing STRANDED WIRE

When splicing two stranded wires, some technicians simply wrap the severed ends around each other before taping. A slight tug on such a splice pulls it apart, often causing blown fuses and service callbacks.




A better method is first to tie the bared ends with a tight square knot (see drawing) and then wrap the ends around each other before taping. This splice will resist all efforts to pull it apart—even to the breaking point of the wire.—*Harry J. Miller*

## IMPROVING CAPACITOR BRIDGES

My capacitor bridge, like many instruments of this type, uses an electron-ray indicator tube as a null or balance indicator. The shadow is not sharp enough and the tube is not sufficiently sensitive to permit matching capacitors as closely as required in some applications. I find that capacitors can be matched much more accurately by connecting a v.t.v.m. between the grid and cathode of the indicator and using the voltage swing to indicate balance.—*George R. Anglado*
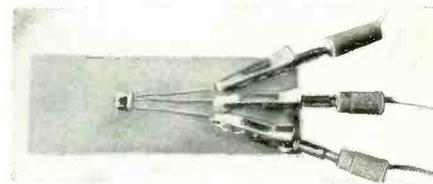
## TRANSISTOR SOCKET

Many experimenters use clip leads in wiring temporary and experimental hookups. If the circuit contains a transistor, there are some difficulties.



If the leads are clipped to the soldering leads of the transistor, the mechanical strain is far too great. If a standard transistor socket is mounted on a little terminal board, it will soon have to be discarded because it is not built for frequent changing of the transistor. I use the gadget shown in the photograph.

Three crocodile clips designed to fit banana plugs are screwed to a piece of plastic sheet as shown. Contact is

## Get the complete Gernsback Library

SEE THE ENTIRE GERNSBACK LIBRARY AT YOUR DISTRIBUTOR



Look for this colorful new revolving book rack at your distributors. See the entire low cost, paper covered library on all the important phases of TV, radio and audio-high fidelity. Examine all the books and see for yourself how much they give you for such low prices!

Basic Audio Course — No. 66. 224 pages. Paper cover ..... \$2.75

Sweep and Marker Generators — No. 55. 224 Pages. Paper cover ..... \$2.50  
Hard cover ..... \$4.00

Probes — No. 54. 224 Pages. Paper cover \$2.50. Hard cover \$4.00

Radio-Control Handbook — No. 53. 192 Pages. \$2.25

The Oscilloscope — No. 52. 192 Pages. Paper cover \$2.25. Hard cover \$4.00

Transistors—Theory and Practice — 144 Pages, No. 51, \$2.00

TV Repair Techniques— No. 50. 128 Pages. \$1.50

Radio & TV Test Instruments, No. 49. 128 Pages. \$1.50

High-Fidelity — Design, Construction, Measurements, No. 48. 128 Pages. \$1.50

Radio & TV Hints—No. 47. 112 Pages. \$1.00

Television Technotes — No. 46. 128 Pages. \$1.50

Radio Tube Fundamentals—No. 45. 96 Pages. \$1.00

Basic Radio Course — No. 44. 176 Pages. Hard cover. \$2.25

Model Control By Radio—No. 43. 112 Pages. \$1.00

High-Fidelity Techniques — No. 42. 112 Pages. \$1.00

Practical Disc Recording—No. 39. 96 Pages. 75c.

See your distributor—or mail this coupon

GERNSBACK LIBRARY, INC. Dept. 16  
25 West Broadway  
New York 7, N.Y.

Enclosed is my remittance of \$.....

Please send me the following books postpaid.

39  42  43  44  45  46  47  
 48  49  50  51  52  53  54  
 55  57  66  
Hard cover editions \$4.00 ea., by mail only.  
 52H  54H  55H  57H

Name .....

(Please print clearly)


Street .....

City ..... State.....


perfect because the transistor leads are held firmly by the jaws of the clips. Little differences in the lead lengths and spacings of different transistors are irrelevant for this socket. For example, you may exchange a 2N36 with a 0C71 in a few seconds.—Joseph Braunbeck

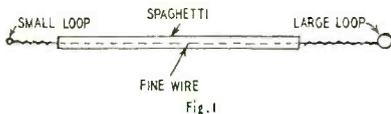**HANDY TEST ADAPTER**

Here is an easy way to measure voltages at the tube sockets from the top of the chassis. Run a length of bare copper wire through a piece of spaghetti tubing and twist a loop in one end to fit pins on miniature sockets



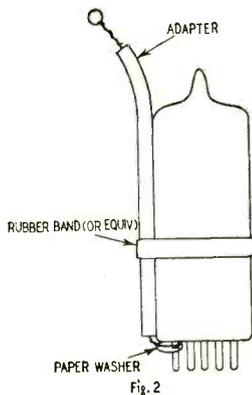and a loop on the other end to fit pins on octal or other tube types. See Fig. 1. Remove the tube from the socket. Scratch the pins with a knife to remove film and corrosion, place the loop over the correct pin and then follow it




with a paper washer (see Fig. 2) to hold the loop in place and insulate it from accidental contact with the chassis.

A miniature test clip or a test prod measures the voltage at the other end of the adapter. A rubber band clamps the adapter to the tube and prevents it from shorting to the chassis.—Arthur Trauffer

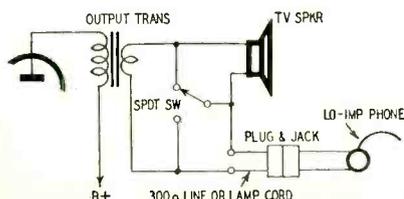**LOW-Z PHONES FOR TV**

There is a demand for extension phones for TV viewers who do not wish to disturb others. A simple and inexpensive installation is shown in the diagram. Using a low-impedance phone for this purpose eliminates the need for blocking capacitors and underchassis wiring.

The headphone is connected in series with the TV speaker voice coil and a s.p.d.t. switch is used to short out the one not being used. The switch is preferably mounted out of sight on the back





**This year it's**

**KINGSBRIDGE 3**

March 19-22  
New York City

for the  
**Radio Engineering Show**

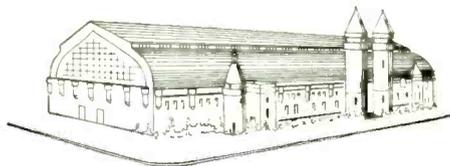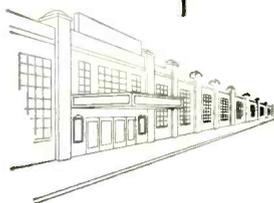

For the third year in succession, the great annual IRE Radio Engineering Show will open its doors to the industry for four spectacular days at the Kingsbridge Armory and Kingsbridge Palace in New York City. As in the preceding years, the Show will be filled to capacity with 704 exhibits and displays of the latest and newest developments in radio-electronics.


Is it too big? Not as a true representative of this giant industry. More than 200 papers presented by 22 Professional Groups at the Convention's 55 technical sessions are an accurate index to new research and development... and the 704 exhibitors represent about 80% of the productive capacity of the industry, ... not one whit larger than necessary to keep pace with electronic America today!

Plan now to attend the industry's most vitally important Show where

**Over 42,000\* meet!**

\*At the 1955 Show, 42,133 men and women from coast to coast and every field of radio-electronics attended the Radio Show. This year, attendance is expected to go even higher. Don't miss it!

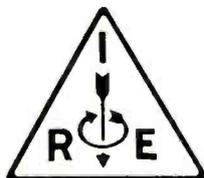**Over 700 Exhibitors will show all that is NEW in radio-electronic engineering!**



**THE INSTITUTE OF RADIO ENGINEERS**  
1 East 79 Street, New York

**COLORDAPTOR PARTS KITS**

- K-5 Universal Delay Line ..... \$5.75
  - K-6 Reference phase shift network ..... 3.65
  - K-9 3.579545 mc Crystal ..... 3.25
  - K-10A Tricolor filter material (sets to 17") ..... 2.35
  - K-11A Complete small parts kit—includes K5, 6, 9, 10A and all other coils ..... 19.75
  - K-1 Complete kit (less color wheel, drive) ..... 79.95
- All other Colordaptor parts & wired chassis available. Write for information, prices.

COLORDAPTOR, 3471 Ramona, Palo Alto, Calif.

**NOW IN STOCK at ALMO RADIO CO.**

1133-37 Haddon Ave. Camden, N. J.  
4401 Ventnor Ave. Atlantic City, N. J.



**COLOR & BLACK & WHITE**  
**5" — 5 MC SCOPE**

**KIT \$79.95 Wired \$129.50**



**EASY TO LEARN CODE**

It is easy to learn or increase speed with an Instructograph Code Teacher. Affords the quickest and most practical method yet developed. For beginners or advanced students. Available tapes from beginner's alphabet to typical messages on all subjects. Speed range 5 to 40 WPM. Always ready—no QRM.



**ENDORSED BY THOUSANDS!**

The Instructograph Code Teacher literally takes the place of an operator-instructor and enables anyone to learn and master code without further assistance. Thousands of successful operators have "acquired the code" with the Instructograph System. Write today for convenient rental and purchase plans.

**INSTRUCTOGRAPH COMPANY**

4701 Sheridan Rd., Dept. RC, Chicago 40, Ill.

# House Current Anywhere



with **TERADO**  
**Trav-Electric**  
**CONVERTERS**

JUST PLUG INTO  
CIGAR LIGHTER  
ON DASH




AND YOU  
CAN USE

**"TOT" USES**—No need to leave appliances for work or pleasure behind. Take them along. Use them on business trips, camping, at the cabin, hunting, etc. Just plug Trav-Electric into cigar lighter on dash. Plug appliances into Trav-Electric. That is all!

**6 MODELS**—for both 6 and 12 volt batteries. All models change battery current to 110 volt A.C. 60 cycle, same as at home. Sizes 2" x 2" x 3 1/2" to 4" x 5" x 6". Capacities: 10 to 125 watts. Fully guaranteed. List prices: from only \$11.95 to \$54.95.

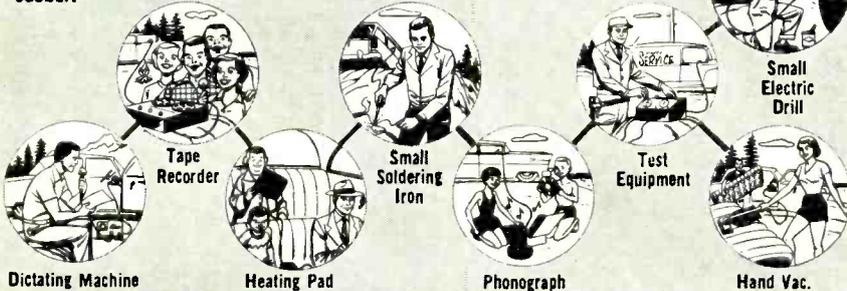See your Jobber Salesman, or write for name of nearest Jobber.



**TERADO COMPANY**  
Mfrs. of Electronic Equipment Since 1927

1057 Raymond Ave., St. Paul 14, Minn.

In Canada write: Atlas Radio Corp., Ltd.  
560 King St. West, Toronto 28, Ont.  
Export Sales Division: Scheel International,  
Inc., 4237 N. Lincoln Ave., Chicago 18,  
Ill., U. S. A. —Cable Address—Harscheel

## LEARN ELECTRONICS & COLOR TV in K.C.

UNIVERSAL TV . . . Famous for 25 Years



Thousands of Successful Grads

**ELECTRONICS**—the world's GREAT-EST new industry is years ahead of its manpower supply. **ELECTRONICS JOBS ARE SEEKING TRAINED TECHNICIANS**, an acute shortage of which exists today. Big companies are actually pirating men from one another because there aren't enough trained electronics experts to go around to fill the many jobs.

**Wide Scope Electronics Course at UNIVERSAL:**

Embraces Radio, Monochrome-Television, Color TV, Industrial Electronics, Industrial Television, Atom-electronics and Automation. Automation, a terrific new field, embraced at UTS.

**25 Years EXCLUSIVELY in Electronics:**

For a quarter of a century UNIVERSAL TV has been training and placing grad technicians in fascinating big-pay jobs from coast to coast. You can start earning as much as \$150 per week; no limit as time goes on, or you can open your own business.

**UNIVERSAL not a Johnny-come lately school:**

Not a home study or correspondence training, but a "genuine" old established resident school staffed by expert instructors and headed by America's first TV broadcasters. Costs so little to prepare yourself for life. Many middle age trainees attend; go into successful business. No previous experience needed. Approved for vets and non-vets.

Send coupon for **FREE BOOK** on TV & electronic opportunities.

WRITE FOR  
**FREE  
CATALOG**

— FILL OUT COUPON —

**UNIVERSAL TV SCHOOL**  
1222R Admiral Boulevard, Kansas City, Missouri  
PLEASE SEND ME INFORMATION FREE. Age \_\_\_\_\_  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_  
 Check here if Korean Veteran

WANT POWER & VERSATILITY?

FOLLOW THE  
LEADER . . .



**KIT**  
**\$29.95**

**Wired**  
**\$38.95**

**6V & 12V BATTERY  
ELIMINATOR & CHARGER #1050**

- operates 6V and 12V auto radios for servicing and sales demonstration.
- charges 6V and 12V storage and Edison Batteries.
- operates mobile and marine receivers, transmitters, boat lights, electric trains, projection and other equipment.

#### SPECIFICATIONS

- 6-Volt range: 0-8V (up to 20 Amp.)
- 12-Volt range: 0-16V (up to 10 Amp.)
- variac-type transformer for continuously variable voltage adjustment.
- reads volts and amperes at same time on 2 separate meters.
- Transformer primary and secondary fully protected.

In stock at local jobbers throughout the world. Write for free Catalog CB-1.

Prices 5% higher on West Coast

**EICO**

84 Withers Street  
Brooklyn 11, N. Y.

TRY THIS ONE

(Continued)

of the cabinet but located so it can be reached easily.

Connection from the TV set to the phone jack may be with lamp cord or 300-ohm lead-in (which can be run under the rug to the viewing location).

Good low-impedance phones of 8 to 15 ohms can be bought for less than \$2. We have used receivers from old apartment-house installations in several cases and even sound-powered toy telephone sets.—*Paul Falk*


(The C. F. Cannon Co. supplies headsets with 11 ohms d.c. resistance at the same price as its equivalent 1,000-ohm single and 2,000-ohm double units.—*Editor*)

## RECTIFIER TESTS

Like the tubes they replace, selenium rectifiers gradually grow weak. In TV sets a common symptom of a weak selenium rectifier is insufficient width (sometimes also height). Portable or a.c.-d.c. radios with weak rectifiers often cut off when an appliance such as a refrigerator or an oil burner goes on.

Selenium rectifiers can be checked by ohmmeters and selenium rectifier testers, but there is no check as positive as direct substitution. The rectifier need not be removed or unsoldered to check it. All that is needed is to parallel an equal-size (or larger) unit across its terminals, observing polarity, of course. If it is inconvenient (as in some TV sets) to get across both terminals, the first and last heat dissipating plates will do equally well. A pair of test leads with color-coded alligator clips on one end and corresponding color-coded test prods on the other makes a handy and useful test unit. A good selenium rectifier is inserted in the clips. If the original unit is O.K., little or no improvement will be noticed. In TV sets with two selenium rectifiers replace both units if improvement is noted as each is bridged. When checking portable radios, reduce the line voltage with a Variac or similar control until the set cuts off. When a defective rectifier is shunted with the test unit, the set will come to life, then go off again when the test unit is removed.

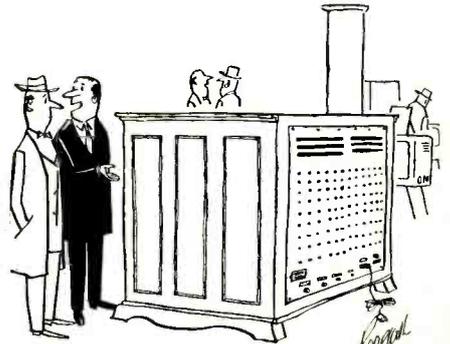With selenium rectifiers that are shorted or have developed a high reverse current, the nose will be the best test. The sickening odor of spoiled eggs common to this type of failures is easily detected.—*Charles Garrett* END




"This is a real honey, sir, 27-inch TV, AM, FM, 5-band shortwave, etc."

RADIO-ELECTRONICS

PERMO  
PERMO  
PERMO  
PERMO  
PERMO  
PERMO  
PERMO  
PERMO  
PERMO  
PERMO



**PERMO, INC.**  
Chicago 26, Illinois

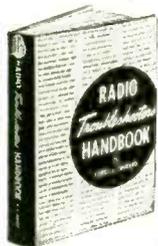

**DON'T  
THROW  
OLD  
RADIOS  
AWAY!**

Here's the data you need  
to fix old sets **FAST**—good as new

Just look up the how-to-do-it data on that old radio you want to fix!

Four times out of 5, this giant, 3 1/2-pound, 744-page Ghirardi **RADIO TROUBLESHOOTER'S HANDBOOK** gives exactly the information you need to fix it in a jiffy. Tells what is likely to be causing the trouble . . . shows how to fix it. No useless testing. No wasted time. Handbook covers common troubles and their remedies in practically every radio receiver model made by 202 manufacturers between 1925 and 1942. Using it, even beginners can easily fix old sets which might otherwise be thrown away because service information is lacking. With simple repairs, most of these old sets can be made to operate perfectly for years to come.

**THE ONLY GUIDE OF ITS KIND!**  
Cuts service time in half!

Included are common trouble symptoms and their remedies for over 4,800 models of old home, auto radios and record changers. Airline, Adpx, Arvid, Atwater Kent, Belmont, Bosch, Brunswick, Clarion, Crosley, Emerson, Fada, G-E, Kolster, Majestic, Motorola, Philco, Pilot, RCA, Silverstone, Sparton, Stromberg and dozens more. Gives how-to-do-it data on 51 "REPAIR" jobs—NOT general theory. Includes hundreds of pages of tube and component data, service short cuts, etc., no longer available from any other source still in print.

**TRY IT 10 DAYS . . . at our risk!**

Dept. RE-16, RINEHART & CO., Inc.  
232 Madison Ave., New York 16, N. Y.  
Send Ghirardi's **RADIO TROUBLESHOOTER'S HANDBOOK** for 10-day free examination. If I decide to keep book, I will then remit the full price of only \$6.50 plus a few cents postage. Otherwise, I will return book postpaid and owe you nothing.

NAME.....

ADDRESS.....

CITY, ZONE, STATE.....

Outside U. S. A.—Price \$7.00, cash only. Same return privilege

Rinehart Books are sold by leading book stores



Merchandising and Promotion

CBS-Hytron, Danvers, Mass., is sponsoring 15 minutes of the Garry Moore TV show on alternate Friday mornings over CBS. The program is aimed at




selling the woman of the house because of a recent survey which showed that it is the woman who usually requests TV service and is at home when the service technician calls.

Raytheon Manufacturing Co., Waltham, Mass., produced a 20-minute motion picture "Safe Passage," which shows why ship collisions occur in spite of radar equipment. Invariably it is because of improper use of equipment or human failure.

Brach Manufacturing Co., Newark, N. J., a division of General Bronze Corp., launched the biggest promotional campaign in its history on its *Magne-Tenna* indoor TV antenna.

Oxford Electric Corp., Chicago, de-

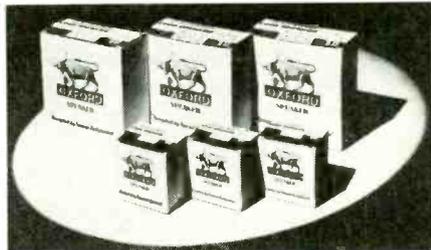

veloped a new line of colorful display packages for its replacement speakers.

Atlas Sound Corp., Brooklyn, N. Y., designed a promotion package for deal-



**a Volt-Ohmmeter  
you can carry in  
your shirt pocket!**



**Simpson  
MIDGETESTER**  
MODEL 355

**SELF  
SHIELDED!**


The world's first practical shirt-pocket volt-ohmmeter. Rugged and accurate. Not affected by any outside magnetic influences. 10,000 Ohms per volt AC and DC! Fourteen ranges: 5 for AC voltages, 5 for DC voltages, and 4 for DC resistances.

**\$29.95**  
including probe leads

See Your Parts Distributor  
**Simpson**  
**ELECTRIC COMPANY**  
WORLD'S LARGEST MANUFACTURER  
OF ELECTRONIC TEST EQUIPMENT

5200 W. Kinzie St., Chicago 44, Ill.  
ESTbrook 9-1121

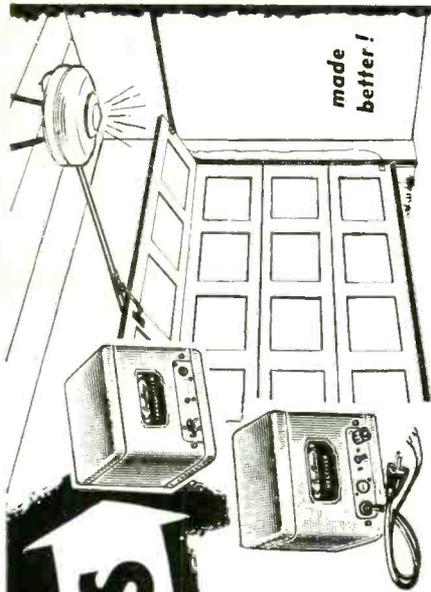IN CANADA: Bach-Simpson, Ltd., London, Ontario



made better!

# NEW DESIGN means NEW SALES

Now, the newest, finest Radio-Control Garage Door Opener styled in a modern spun-aluminum fixture that beautifies garage interiors. Convenience and safety features galore — New automatic shut-off, positive locking of door, FCC authorized radio frequency . . . and many more plus qualities! Write today for descriptive literature.



4727 N. Damen Ave., Chicago 25, Ill.  
Manufacturers of electronic equipment since 1928  
EXPORT: Scheel International, Chicago, Ill.

mfd by **Perma-Power COMPANY**

**NO FREE GIFTS! NO COUPONS! EXCEPT THE**

# LOWEST TUBE PRICES

**BRAND NEW famous make PICTURE TUBES DUMONT and RCA licensed One Year Guarantee In original factory sealed carton**

**NO REPLACEMENT DUD REQUIRED!**

Type	List Price	T. M. Price
10BP4A	19.25	11.95
12LP4A	24.25	14.99
16AP4A	44.75	19.99
16WP4A	41.50	18.00
17BP4A	32.00	19.00
19AP4	39.75	23.00
20CP4	39.00	24.00
21ALP4A	46.00	24.00
21AUP4A	46.00	24.00
21EP4A	39.00	24.00
21FP4	39.75	24.00
24AP4	120.00	42.00

F.O.B. Passaic, N.J. . . . Subject to prior sale. Write for complete tube listing.

## TUBE MART

DISCOUNT HOUSE

The Lokpet Bldg. Passaic, N. J.

**DON'T JUST SAY CAPACITORS**

Ask For Sprague By Catalog Number

Know what you're getting . . . get exactly what you want. Don't be vague . . . insist on Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 81 Marshall Street, North Adams, Massachusetts.

# SPRAGUE

WORLD'S LARGEST CAPACITOR MANUFACTURER

Ready Now! Two Timely Low Cost Books

## "Printed Circuits and Printed Wiring"

Printed circuits are now standard in virtually all new television, radio and hi-fi amplifier production. Completely new service techniques are required to repair these circuits. This new Sprayberry book covers types of printed circuits with service instructions for each. Shows how to replace defective components and repair foil. Covers tools and equipment needed; profusely illustrated. Just off the press — send for yours today.

### "RADIATION DETECTORS, GEIGER and SCINTILLATION COUNTERS"

The most up-to-date book available covering operation and servicing of uranium and other radiation ore prospecting equipment. Thoroughly explains operation and theory of geiger and scintillation counters; covers types of tubes used and methods for obtaining high operating voltages from low voltage source. Covers proper servicing procedure and calibration. Enables any electronic technician to earn top money servicing these units. Illustrated with pictures, diagrams and service charts.

Each Book Only **50¢** POSTPAID

Send 50c coin (no stamps) for one or \$1.00 for both

**SPRAYBERRY ACADEMY OF RADIO**  
Dept. 20-GA, 111 N. Canal St., Chicago 6, Illinois.

**NEW! For the First Time!**

## CHECK CAPACITORS UNDER WORKING CONDITIONS!

# CAPACITEST

Quickly, Accurately checks:

- PAPER, MICA, CERAMIC CAPACITORS
- ELECTROLYTICS
- CONTINUITY
- AC/DC VOLTAGES
- FLASHBULBS

SATISFACTION GUARANTEED OR RETURN WITHIN TEN DAYS FOR REFUND

**9.95** postpaid Dir. Net complete. ready for operation

**NOT A KIT**

**FREE** Special Introductory Offer for limited time only: Set of test leads Free with each CAPACITEST.

Order direct from manufacturer — include \$3 deposit with C.O.D.'s. Save PP & COD fees, send \$9.95 & we'll pay postage.

ment is a new, compact checker that does a giant job to save you time and money. It will check condensers at 150 Volts, which is approximately the working voltage in a radio or TV set. Meters will not give this type of check since the applied voltage is 20 Volts or less. Avoid call-backs by using CAPACITEST. Accurately, quickly, it shows open, shorted, or intermittent capacitors and leaky electrolytics. Compact: 4"x4"x2"—lightweight, for bench or tool kit.

**BARJAY The Barjay Co.** 145 West 40 Street New York 18, N.Y.

ers handling its PA loudspeakers, microphone stands and accessories. It includes mailing pieces and a satin banner for window or wall display.

United Catalog Publishers, New York, issued its distributors a four-color counter and window display with shipments of the 1956 edition of its *Radio-Electronic Master*.

Supreme Publications, Highland Park,



Ill., designed a new display stand for its manuals.

Altec Lansing, Beverly Hills, Calif., is offering high-fidelity establishments a new store display for its products.

Jensen Industries, Forest Park, Ill., needle manufacturer, now features a



chrome-plated wire frame display for distributors and dealers of its needles and accessories.

Pentron Corp., Chicago, is marketing its new prerecorded tapes in a counter merchandiser supplied free with each order of 12 or more *Moods in Music* tapes.

Almo Radio Co., Philadelphia, is sponsoring its Third Annual Industrial Show at the Penn Sherwood Hotel, Philadelphia, Jan. 25-26. Over 90 manufacturers are expected to participate.

Talley Electronic Development Co., Cincinnati, Ohio, is displaying its new *Genuprobe* variable-frequency audio



# NOW! TEST TUBES IN SECONDS! MAKE NEW PROFITS *in MINUTES!*



on every  
service call



**B&K** NEW PORTABLE  
**DYNA-QUIK** MODEL 500  
DYNAMIC MUTUAL CONDUCTANCE TUBE TESTER  
ONLY \$109<sup>95</sup> NET

Now you can easily cut servicing time—make more on-the-spot tube sales—prevent costly call-backs—and give a better service guarantee! DYNA-QUIK—the new top quality, low cost, portable tester quickly locates all weak and in-operative tubes—and easily does the complete job with laboratory accuracy right in the home! You create greater customer confidence because your customer sees for himself the true tube condition. Easy to operate—in just a few minutes you can quickly check all the tubes in a TV set. You can depend upon DYNA-QUIK because it tests under the dynamic heavily loaded conditions that are the actual operating conditions of the set. At such low cost DYNA-QUIK quickly pays for itself—and continues to make money for you every day!

### DYNA-QUIK DOES IT FASTER, EASIER, MORE ACCURATELY

- Makes complete tube test in as little as 12 seconds per tube—faster than any other tester!
- One switch tests everything! No multiple switching—no roll chart.
- Laboratory accuracy right in the home! Large 4½" plastic meter has two scales calibrated 0-6,000 and 0-18,000 micromhos.
- Shows customer true tube condition and life expectancy on "Good-Bad" scale!
- Automatic line compensation! Special bridge continuously monitors line voltage.
- 7-pin and 9-pin straighteners mounted on panel!
- Always up to date! Test procedure instructions for new tubes supplied by factory at regular intervals.

TESTS OVER 95%

OF ALL POPULAR  
TV TUBES\* FOR:

- DYNAMIC MUTUAL CONDUCTANCE SHORTS
- GRID EMISSION
- GAS CONTENT
- LEAKAGE
- LIFE EXPECTANCY

\*Including new 600 mil series tubes,

### PORTABLE—CAN BE USED ANYWHERE

Handsome, rugged, luggage style carrying case, covered in durable, black leatherette. Removable slip-hinged cover. Size: 15½ x 14½ x 5¾ in. For 105-125 volts, 60 cycle, A.C. Net wt. 12 lbs.


SEND FOR BULLETIN 500-E

Made by the makers of  
the famous CRT 350



**B & K MANUFACTURING CO.**  
3726 N. SOUTHPORT, CHICAGO 13

# Examine FREE

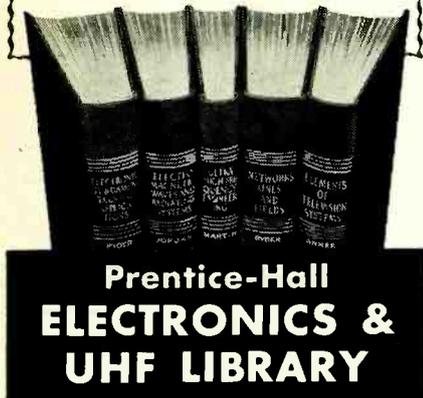

## Prentice-Hall ELECTRONICS & UHF LIBRARY

Edited by  
**W. L. EVERITT**

**5 VOLUMES 1662 ILLUSTRATIONS**

Pay Easy Installments If You Keep the Set

Turn to this new, up-to-date Library with complete confidence, for dependable facts on any phase of modern electronic theory and practice. These volumes, by outstanding authorities, give you thorough guidance—clearly written, logically arranged, profusely illustrated.

### Electronic Fundamentals and Applications

By Prof. John D. Ryder,

Dean, College of Engineering, Michigan State College

Complete, logical, easy-to-follow treatment of (a) physical principles underlying electron tubes, (b) characteristics of vacuum tubes, (c) all basic tube circuits. Includes: Electron Ballistics, Cathode-Ray Tubes, Emission of Electrons, Space Charge in Vacuum Tubes, Diode Rectifiers, Triodes, Multi-Element Tubes, Small-Signal Amplifier Circuits, Audio-Frequency Amplifiers, Radio-Frequency Amplifiers, Oscillator Circuits, Modulation Systems, Wave-Shaping Circuits, Gaseous Conduction, Gas Diodes, Gas Control Tubes and Circuits, Photoelectric Cells, Solid-State Electrodes.

### Electromagnetic Waves and Radiating Systems

By Prof. Edward C. Jordan,

Head, Dept. Electrical Engineering, Univ. of Illinois

Covers entire field of electromagnetic engineering. Includes propagation as well as radiation and transmission. Full treatment of UHF transmission lines, wave guides, antennas, slot antennas, radiation and diffraction, ground-wave and sky-wave propagation.

### Ultra High Frequency Engineering

By Thomas L. Martin

Head, Dept. of Electrical Engineering, Univ. of Mexico  
Theory and technique of ALL the new fields of electronic engineering: Radar, Telemetry, Electronic computing, Facsimile, Television, Blind landing systems, Pulse-time modulation, Ionosphere measurements . . . and the others.

### Networks, Lines and Fields

By Prof. John D. Ryder,

Dean, College of Engineering, Michigan State College

Network transformation and theorems, Resonance, Impedance transformation and coupled circuits, Filters, General transmission line, High-frequency line, Equations of the electromagnetic field, Radiation, Transmission and reflection of plane waves at boundaries, Guided waves between parallel planes, Wave guides.

### Elements of Television Systems

By George E. Anner, University of Illinois

Complete basic theory, plus current practice, covering: Closed TV systems, Commercial Teletexting Systems, Color TV Systems. Gives clear exposition of all phases of picture transmission, including the new technique of dot interlace.

## SEND NO MONEY—EXAMINE FREE

Just mail coupon below to get complete 5-Volume Set on 10 DAYS' FREE TRIAL. If not completely satisfactory, return in ten days and owe nothing. Or keep the set and pay only \$7.50 down and \$8 a month for five months until full price of \$47.50 is paid. Decide for yourself—without risk or obligation—just mail coupon to examine Library ten days free.

Prentice-Hall, Inc., Dept. 5744-A1  
Englewood Cliff, N.J.

Send me the Prentice-Hall ELECTRONICS & UHF LIBRARY (5 Volumes) for ten days' free examination. If fully satisfied in ten days I will send you \$7.50 plus five cents postage and then \$8 a month for five months until full price of \$47.50 is paid. Or I will return the Library in ten days and owe nothing.

Name .....

Address .....

City and State .....

## BUSINESS

(Continued)

generator and voltage indicators in a counter display which holds 12 of the packaged units.

Walsco Electronic Sales Co., Los Angeles, Calif., recently installed its 1,000th Phono Drive display counter unit in the newest branch of Peninsula



Radio & Supply Co., San Jose, Calif. Photo shows William Bundie (left), owner of Peninsula, being congratulated by Walsco representatives Ken E. Ross (center) and Charles N. Meyer.

### Production and Sales

RETMA reported the production of more than 5,760,506 TV sets and 10,027,362 radios for the first nine months of 1955 compared with 4,733,315 TV sets and 7,042,442 radios turned out during the same period during 1954. The association also reported the retail sale of 5,149,977 TV sets and 3,942,676 radios—exclusive of automobile sets—for the first nine months of 1955. During 1954, 4,645,063 TV sets and 4,032,704 radios were sold.

RETMA reported manufacturers' sales of 347,668,000 receiving tubes and 7,680,781 TV picture tubes for the first nine months of 1955. This compares with 266,050,000 receiving tubes and 6,476,566 picture tubes for the 1954 period.

### New Plants and Expansion

Sylvania Electric Products is building a new multimillion dollar plant at Altoona, Pa., for the production of receiving tubes.

CBS-Hytron, Danvers, Mass., is planning a complete new 55,000-square-foot tube and transistor warehouse in Chicago to service its midwestern distributors and dealers better.

Raytheon Manufacturing Co., Waltham, Mass., leased plant space in Maynard, Mass., which will be devoted to the development and engineering of radar equipment for its Missile and Radar Division.

Allen B. Du Mont Labs., Clifton, N. J., has begun operations in its new West Coast headquarters in Los Angeles.

Krylon, Inc., is now located in its new plant in Norristown, Pa.

Westinghouse Electric established a new department in Baltimore for the manufacture of a line of industrial electronic products. Robert C. Cheek, assistant manager of the Baltimore Electronics Division, was named manager of the new department.

James Vibrapower Co. is now located in its new manufacturing facilities in



WRITE FOR OUR BARGAIN "TABOGRAM"  
A Free Bonus with Every Order

SNOOPERSCOPE, Infra Red Tube ..... \$3.90; 2/57.50  
Photoflash Cond. 525MFD/450V/53Wacet. new low  
leakage. Famous mfr..... \$8; 2/515  
PRECISION RESISTORS—1% Accuracy GTD  
10 of one value..... @ \$8.00  
100 of one value..... @ \$1.50  
10 assorted values..... @ \$1.50  
Oil Cond.-AMFD/1200VDC or 10MFD/600VDC \$1.79 ea.  
Special Lots of 12 (any assortment)..... \$1.25 ea.

NEWLY IMPORTED "TAB" POCKET  
AC-DC Multimeter  
1000 Ohms Per Volt  
Only \$7.85 ea.  
(Not A Kit)  
Model 27c Hi-accuracy precision VOM.  
Reads AC & DC Volts: 0, 5, 25, 250,  
1000 V. DCMA: 0, 1, 10, 100 M.A.  
OHMS: 0, 10, 100 K. Size 1 1/4" D.  
4 5/8" L. 3 1/4" W. With test leads.  
Sold with "TAB" Money Back Guarantee.  
(plus 40c ship in U.S.A.)

## NEW, Unused • Individually Boxed TUBES FULL RETMA WARRANTY

None Rewashed or Rebranded  
No Electrical or Mechanical Rejects  
12 Years—Never A Dissatisfied Customer

0Z4	.45 6AV5	.80 6K6	.45 12AX7	.55
1AX2	.95 6AV6	.45 6S4	.45 12BA6	.50
1B3	.65 6AX4	.80 6S7	.65 12BE6	.65
1T4	.50 6BA6	.75 6S17	.65 12BH7	.65
1U5	.45 6BC5	.45 6S7	.50 12BY7	.67
1X2	.85 6BE6	.60 6S17	.55 12CA7	.45
3VP4	.75 6BG6	1.24 6G07	.55 12SN7	.56
5U4	.45 6BK7A	1.11 6T4	1.15 12SQ7	.50
5V4	1.28 6BL7	.90 6T8	.45 12SL6	.42
6X3	.65 6BE6	1.19 6V6	.65 50C5	.52
6AC7	.65 6BQ6	.90 6W4	.35 25W4	1.03
6AG5	.45 6BQ7A	1.30 6X4	.40 35W4	.50
6AK5	.60 6C4	.35 6X5	.45 35W4	.50
6AL5	.40 6CB6	.50 6X8	.85 3Z5	.45
6AQ5	.45 6CD6	1.08 12AT6	.40 50B5	.70
6AT6	.40 6CF6	1.25 12AV6	.41 50L6	.55
6AU4	.95 6CL6	1.65 12AU7	.50 75	.85
6AU5	1.10 6J5	.40 12AU7	.50 75	.85
6AU6	.45 6J6	.45 12AX4	1.29 83V	1.22

1000's of other Tubes in stock, write

## NEW "TABTRON" SELENIUM BRIDGE

RECTIFIERS  
Dated & One Year Gtd  
We manufacture Power Rectifiers to your specifications from 1 Amp up to and above 1000 Amperes. Following List, Full Wave Bridge.

Curr.	18/14	36/28	52/42	130/100
Cont.	Volts	Volts	Volts	Volts
10AMP	2.40	3.40	6.15	11.50
3AMP	3.45	4.75	6.70	14.65
4AMP	6.45	6.45	13.40	28.45
6AMP	5.10	10.05	14.75	36.80
10AMP	7.50	14.35	22.40	47.55
12AMP	* 9.20	18.10	24.40	50.85
20AMP	15.00	28.00	42.80	90.25
24AMP	18.40	36.74	51.15	97.75
30AMP	22.70	38.50	64.95	125.35
40AMP	28.45	54.80	81.10	154.10
50AMP	33.90	62.50	115.95	200.10

Write For Our New Rectifier Catalog PR155

## "TABTRON" HI CURRENT PWR SUPPLY

ONE YEAR GUARANTEE  
Variable 0-28VDC. Completely Built. Incls: Full Wave Selenium Rectifier, Transformer, 1000 Ohm 1/2 W & Amp Meters, Switch, Terminals & Fuse. In Hvy duty Steel Cabinet, Standard 115V/60cy Input or 220V and 3 phase to order. SPECIFY.

Slt. No.	Cont.	Rating	W-Meters
T28V5A	0-28 VDC at 5 Amp		\$125
T28V12A	0-28 VDC at 12 Amp		\$155
T28V30A†	0-28 VDC at 24 Amp		\$155
T28V50A†	0-28 VDC at 50 Amp		\$285

## NEW GE PHONO CARTRIDGES

\*GE Original Boxed, \$ \$ \$ Back Gtd

RPX050A	* Golden Treasure (SS)	\$6.98
RPX052A	* Golden Treasure (DS)	\$19.98
RPX053A	* Golden Treasure (DD)	\$28.98
RPX040A*	* 003 Single (SS)	\$5.25
RPX041A*	* 001 Single (SS)	\$5.25

Replace mt Needles "TETRAD" Diamond†

RPJ010A	Dual (S), .001 & .003 GE	\$1.98
RPJ012A	Dual (D), .001 & .003 "TETRAD"†	\$18.99
RPJ013A	Dual (DS), .001 & .003 "TETRAD"†	\$10.99

Replc mts for New A Cartridge Only

RPJ01D	or RPJ03D Sing (D) "TETRAD"†	\$9.99
RPJ01S	or RPJ03S Single (S)	\$1.35
RPJ01A*	Replc mnt Styl for RPX040 & 041 Only	\$1.35
RPJ001	or RPJ005 Single (S) GE	\$1.35
RPJ003	or RPJ004 Single (D) "TETRAD"†	\$9.99

## FINEST HI-FI RECORDING TAPE

7 1/2" Reel—1200 Ft. Per Reel  
\$ \$ \$ Back Guarantee  
Precision Coated & Slit, Gtd Splice  
Free Quality Controlled, Plastic Base,  
Gtd Constant Output, Fro. 7 1/2 IFS  
40-15KC. Oxide Wnd In. Twelve Lot  
Sold Singly. \$1.80 Special ..... ea. \$1.58

## WRITE FOR NEW BONUS HI FI GRAM

"TAB" HI FI SPEAKERS  
Inhibit network 2 wire neutral for HF & LF Response Famous HI FI mfgs.  
Model P25C 15" Coaxial PM & 5" Tweeter  
25 Watt/20-17500 cycles ..... \$19.50  
Model P12C 12" Coaxial PM & 3 1/2" Tweeter  
12W/45-15KC Cy \$12.75, 3 \$35  
Model PBCO 8" Coaxial PM & 2 1/4" Tweeter  
8 Watt/70-15KC ..... \$7.98; 2/515

TERMS: Money Back Gtd (cost of mds only) \$5 min order  
F.O.B. N.Y.C. Add ship charges  
or for C.O.D. 25% Dep. Tubes  
gtd. via R-Exp Only. Prices  
shown subject to change.

"TAB" 111 LIBERTY ST. N.Y. 6 N.Y. RECY 2-6245  
DEPT. IRE6—CABLE "TABPARTS"

Chicago, adjacent to its former quarters.

Allied Radio Corp., Chicago, opened its third high-fidelity studio in the Chicago area.

**Mergers**

Van Norman Co., Springfield, Mass. machine tool manufacturer, acquired Insuline Corp. of America, Manchester, N. H., which it will operate as a subsidiary. There will be no change in personnel. Samuel J. Spector continues as Insuline president and chief executive officer; Bernard L. Cahn, vice president for sales; and Myles Spector, vice president for manufacturing.

Clevite Corp., Cleveland, acquired full ownership of Transistor Products, Inc., Waltham, Mass., in which it formerly held a majority interest. The company's name has been changed to Clevite Transistor Products and will operate as a division of the parent company.

New York Transformer Co., Alpha, N. J., acquired Tartak Electronics, Burbank, Calif., as a West Coast subsidiary which will now be known as NYT Electronics.

**Business Briefs**

... Ohmite Manufacturing Co., Skokie, Ill., will now manufacture Amrecon relays previously made by its subsidiary, American Relay & Controls, Inc. Formerly available for manufacturers only, they will now be sold to distributors as well.

... The 1956 Los Angeles High-Fidelity Music Show will be held Feb. 8-11 in the Alexandria Hotel in Los Angeles.

... RETMA issued a new booklet outlining its services and activities.

... Electronic Instrument Co., Brooklyn, N. Y., manufacturer of Eico kits, recently celebrated its 10th anniversary.

... Cornell-Dubilier Electric Co., South Plainfield N. J. has modernized and expanded its Powercon line of vibrator-powered converters to include the marine, aircraft, business office,

**Calendar of Events**

1956 Electronic Parts Distributors Show management announced registration for the show—a closed exhibition for distributors, representatives and manufacturers' personnel—would be made by mail only before the show opened.

Polytechnic Institute of Brooklyn international symposium on nonlinear circuit analysis April 25-27.

1956 High-Fidelity Show in Chicago Nov. 2-5.

NEDA and Radio Parts and Electronic Equipment Shows, Inc. are planning a series of five regional distributor seminars to be held in key cities throughout the U. S. during 1956.

ham, appliance, mobile and industrial fields.

... Magnavox, Ft. Wayne, Ind., held the second of its color TV training program courses in New York City recently.

... JFD Manufacturing Co., Brooklyn, N. Y., recently made a shipment of three trailer loads of TV receiving antennas to the U. S. Government which it states is the first shipment of its type in the industry to be made. END



**No. 99 Junior Kit**



**NOW!**

**OFF-THE-SHELF DELIVERY ON THIS POPULAR KIT!**

Here's good news for those of you who haven't been able to get this new 99 Junior kit. Our new plant addition is turning it out full tilt and it's on distributors' shelves. ASK YOUR SUPPLIER to show you this pocket-size roll plastic kit with all its tools (3/16, 7/32, 1/4, 9/32, 5/16, 11/32 and 3/8" nut driver bits—Nos. 1 and 2 Phillips screwdrivers—3/16 and 9/32 slotted screwdrivers). Also ask about the new chrome-plated SUPERREAMER.

**XCELITE, INCORPORATED**  
Dept. J  
ORCHARD PARK, N. Y.



**GARAGE DOOR REMOTE CONTROL**

Actuator Mechanism \$24.50

Write for information

P. E. HAWKINS CO.

631 PROSPECT KANSAS CITY 24, MO.

NOW IN STOCK at R.P.D. arthur nagel, inc.  
NEW EICO 918 E. 55 St.  
Chicago 15, Illinois

COLOR & MONOCHROME Laboratory & TV SERVICE 5-MC SCOPE  
KIT \$79.95  
Factory Wired \$129.50



#460

**SAVE TIME...**

**on EVERY TELEVISION SERVICE CALL with the NEW Senco UNIVERSAL TV Jumper Cord**

Carry only one Jumper Cord for all TV Sets

- Extends Power from back of TV Set—no more moving of furniture to get to the wall plug
  - Turn set off from rear
  - No more winding and un-winding cords
  - Two handy power outlets for soldering iron and test equipment.
  - Fits many speakers, focus coils, etc.
- Write for illustrated Literature. . . .

COMPLETE \$1.95 DEALER NET Available at leading jobbers

**SERVICE INSTRUMENTS COMPANY**  
ADDISON, ILL., (Chicago Industrial Suburb)  
In Canada: Emerald Television Corp., Montreal

**"I will not dance—not until you get a JENSEN NEEDLE for that machine!"**



# BEST FOR COLOR TEST!



**MODEL 617  
3" OSCILLOSCOPE**

The most for your scope dollar. Flat-face CRT gives edge-to-edge accuracy... laboratory precision *plus* field ruggedness. And at your electronic jobber, it's just... \$269.50.

There's just one way to test the new color TV sets... WITH NTSC COLOR PATTERN. That's what Hycon's Model 616 Color Bar/Dot Generator offers... *all* standard colors, sequences and patterns easily selected and graphically shown *in actual color* right on the control panel. For color TV, get ready... **GET HYCON!**

*"Where Accuracy Counts"*  
**Hycon ELECTRONICS, INC.**

A Subsidiary of Hycon Mfg. Company  
321 SOUTH ARROYO PARKWAY  
PASADENA, CALIFORNIA

**MAIL,  
please,  
for Catalogs  
616 and 617**

HYCON ELECTRONICS, INC. Dept. R  
P.O. Box 749 Pasadena, California  
Please send me the new model 616 and 617 catalogs.


Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_



Les A. Thayer, sales manager of the Merchandise Division of Belden Manufacturing Co., Chicago, celebrated his 25th anniversary with the company. He will be presented with a commemorative gold watch and will be admitted to the Belden 25-year Club at its next meeting in February.



**Les A. Thayer**

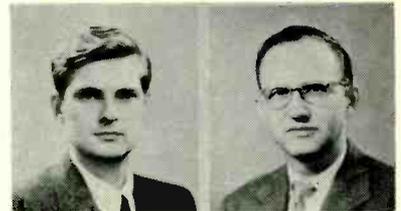

Howard T. Souther (upper right of photo), manager of the Reproducing Components Division of Electro-Voice, Inc., Buchanan, Mich., was named marketing director in a realignment of Sales Division executives. Webster F. Soules, (upper left), manager of the Distributor Sales Division, was named administrative assistant. George Riley (lower right), former assistant manager of the Distributor Sales Division, was appointed manager of the Distributor Sales Division and Cullen H. Macpherson (lower left), assistant manager of the Reproducing Components Division, was promoted to manager of high-fidelity products.

Ray R. Simpson, founder of Simpson Electric Co., Chicago, was honored at the company's recent sales conference at Lac du Flambeau for his 50 years in



W. E. Carroll (left) presents portrait to Ray R. Simpson (right).

PEOPLE

(Continued)

the electrical instruments industry. Simpson was presented with an oil portrait of himself, a gift from the company and its sales representatives, by Wallace E. Carroll, president of the company.

Raymond E. Carlson, vice president in charge of sales and a director of Tung-Sol Electric, Newark, N. J., relinquished his sales responsibilities but



Raymond E. Carlson George W. Keown remains with the company as vice president and a member of the board. George W. Keown, general sales manager of the company, was elected a vice president and assumes the sales responsibilities.

Sam Schlusel, chief field and sales engineer of Channel Master Corp., Ellenville, N. Y., was appointed to the new post of sales manager, antennas and accessories.



Sam Schlusel

John J. Kaul was named sales manager of Terado Co., St. Paul, Minn. Since joining the firm in 1949 he has worked with new product promotion and distribution through jobber and dealer outlets.



John J. Kaul

Robert G. Dailey was appointed vice president of Vokar Corp., Dexter, Mich. He was formerly general sales manager and will continue to direct all sales activities.



Robert G. Dailey

Obituaries

Otto Paschkes, founder and president of Astron Manufacturing Corp., East Newark, N. J., recently at his home in Scarsdale, N. Y., after a long illness.

Irving Golin, president and founder of University Loudspeakers, Inc., White Plains, N. Y., in a New York hospital at the age of 46.

Charles C. Leininger, Jr., advertising manager of National Carbon Co., at his home in New Canaan, Conn.

John B. Merrill, vice president, operations, of Sylvania Electric Products' Tungsten and Chemical, Atomic Energy, Electronics, and Parts Divisions and his wife in the United Air Lines plane

## opportunities

AT  
**BELL TELEPHONE LABORATORIES**

A career for you with one of the nation's leaders in research and development in communications and military electronics.

**ELECTRONIC TECHNICIANS      DRAFTSMEN**  
**ELECTROMECHANICAL TECHNICIANS**

Openings require previous training at high school, armed service school, or technical institute level and in general 2 or more years of applicable industrial or military experience.

Send your name and address for application, telephone collect within 100 miles for information, or visit us Monday through Friday. Evening interviews arranged.


**BELL TELEPHONE LABORATORIES**  
WHIPPANY, N. J. (Near Morristown)  
WHIPPANY 8-1000      EXTS. 2786, 300  
MURRAY HILL, N. J. (Near Summit)  
CRESTVIEW 3-6000      EXTS. 3078, 3204  
463 WEST STREET, NEW YORK CITY  
CHELSEA 3-1000      EXTS. 2871, 2873

## ARKAY KITS

WORLD'S FINEST  
**RADIOS   PHONOGRAPHS   TV**  
**TEST EQUIPMENT   HI-FI**  
Write for FREE Brochure  
RADIO KITS, INC. • 120 Cedar St., N. Y. 6

**EXPERIMENTERS—HOBBYISTS**  
BUILD PROJECTS IN  
THIS MAGAZINE  
Parts available for most articles.  
Free Part-Pak Price List.  
Write  
PART-PAKS    BOX 481    CAMDEN, N. J.
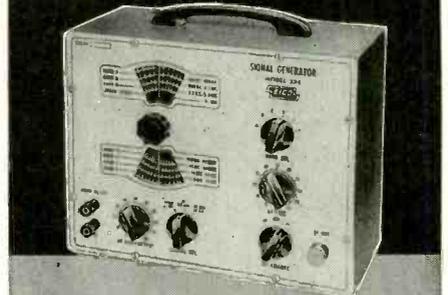
### ONE Generator covers 150 kc—435 mc! WORLD'S BEST GENERATOR BUY!



New! EICO SIGNAL GENERATOR #324  
KIT \$26.95      Wired \$39.95

- 6 fundamental bands: 150-400 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc, 1 harmonic band 111-435 mc. Covers AM, FM, TV, & Amateur freqs.
- ±1.5% frequency accuracy; 6:1 vernier tuning knob & excellent spread at most important alignment frequencies.
- Etched tuning dial, plexiglass windows, edge-lit hairlines.
- Variable depth of int. mod. 0-50% by 400 cps Colpitts osc.
- Variable gain ext. mod. ampl.; only 3.0 v for 30% mod.
- Colpitts RF oscillator plate-modulated by cathode follower.
- Turret-mounted, slug-tuned coils.
- Fine & Coarse (3-step) RF attenuators; 50-ohm output Z.
- RF output 100,000 uv; AF output to 10 v.

In stock at local parts distributors coast to coast.  
Write for free Catalog CG-1

**EICO**® Prices 5% higher on West Coast  
84 Withers Street • Brooklyn 11, N. Y.      © 55

## LEARN TV

the practical way..

17", 21" and 27"  
Designed so that COLOR can be added

### BUILD the New TRANSVISION TV KIT

\*THIS MODEST INVESTMENT gets you started on a most fascinating project— assembling the new "E" type Transvision TV Kit in easy stages. For \$15 you get PACKAGE #1 (standard first package for all new "E" kits). This package gives you the BASIC CHASSIS and required first-stage TV COMPONENTS, with complete instructions. When ready, you order the next stage (pkg. #2), etc.

ONLY \$15.00 gets you started\*

**FREE CATALOG** Shows 8 Great TV Kits:

EXCLUSIVE: Only Transvision TV Kits are adaptable to UHF. Ideal for FRINGE AREAS. No Previous Technical Knowledge required. Write now!

## TRANSVISION

THE OLDEST NAME IN TV KITS  
NEW ROCHELLE, N. Y.

--- MAIL THIS COUPON TODAY ---

TRANSVISION, INC., NEW ROCHELLE, N. Y. Dept. RE-1


I'm enclosing \$ \_\_\_\_\_ deposit. Send standard kit PACKAGE #1, with all Instruction Material. Balance C.O.D.

Send FREE copy of your new TV Kit Catalog.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ State \_\_\_\_\_
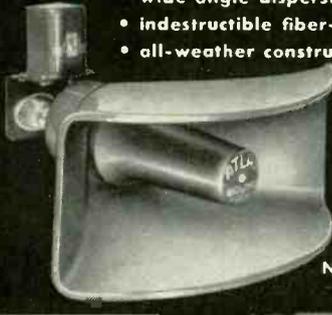
## ATLAS Cobra-Jectors

- wide angle dispersion
- indestructible fiber-glass
- all-weather construction



CJ-30  
Net \$24.00

Weatherproof universal line transformer, \$5.10 Net.



CJ-14  
Net \$16.80

Designed for wide angle coverage, paging, high efficiency intercom, sensitive talk-back. Tops in articulation. Convenient omni-directional mounting bracket. In appearance, they're "beauts".


SPECIFICATIONS	CJ-30	CJ-14
Input pwr (cont.)	15 w	5 w
Input imp.	4 or 8 Ω	4, 8 or 45 Ω
Response (cps)	250-9,000	400-10,000
Dispersion	120° x 60°	120° x 60°
Bell Size	14" x 6"	9½" x 5½"
Over-all length	14"	8½"

Amazing "power packages"—use the Cobra-Jectors for the "tough" jobs.



WRITE FOR COMPLETE CATALOG  
**ATLAS SOUND CORP.**  
1443—39 St., Bklyn. 18, N. Y.  
In Canada:  
Atlas Radio Corp., Ltd., Toronto, Ont.

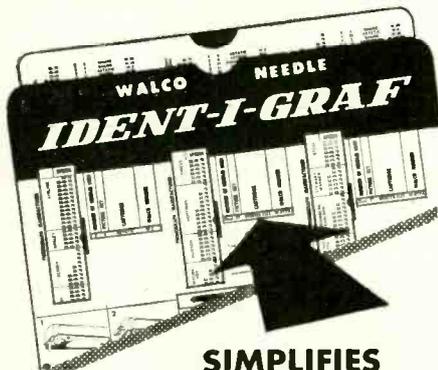**NOW!**  
**Identify ANY Needle**  
**By Phono Manufacturer!**




### SIMPLIFIES NEEDLE SELLING

All you need is the name of the phonograph manufacturer and the Walco Ident-I-Graf gives you positive needle identification in 3 seconds! Saves time and sales. Builds big needle profits. Throw away your complicated wall charts, Rube Goldberg selectors and other gimmicks. Learn how easy it is to sell needles with the Walco Ident-I-Graf. Available FREE to Walco dealers.

**Walco** E. ORANGE, N. J.

# Polio Vaccine

## CAN'T HELP HER...

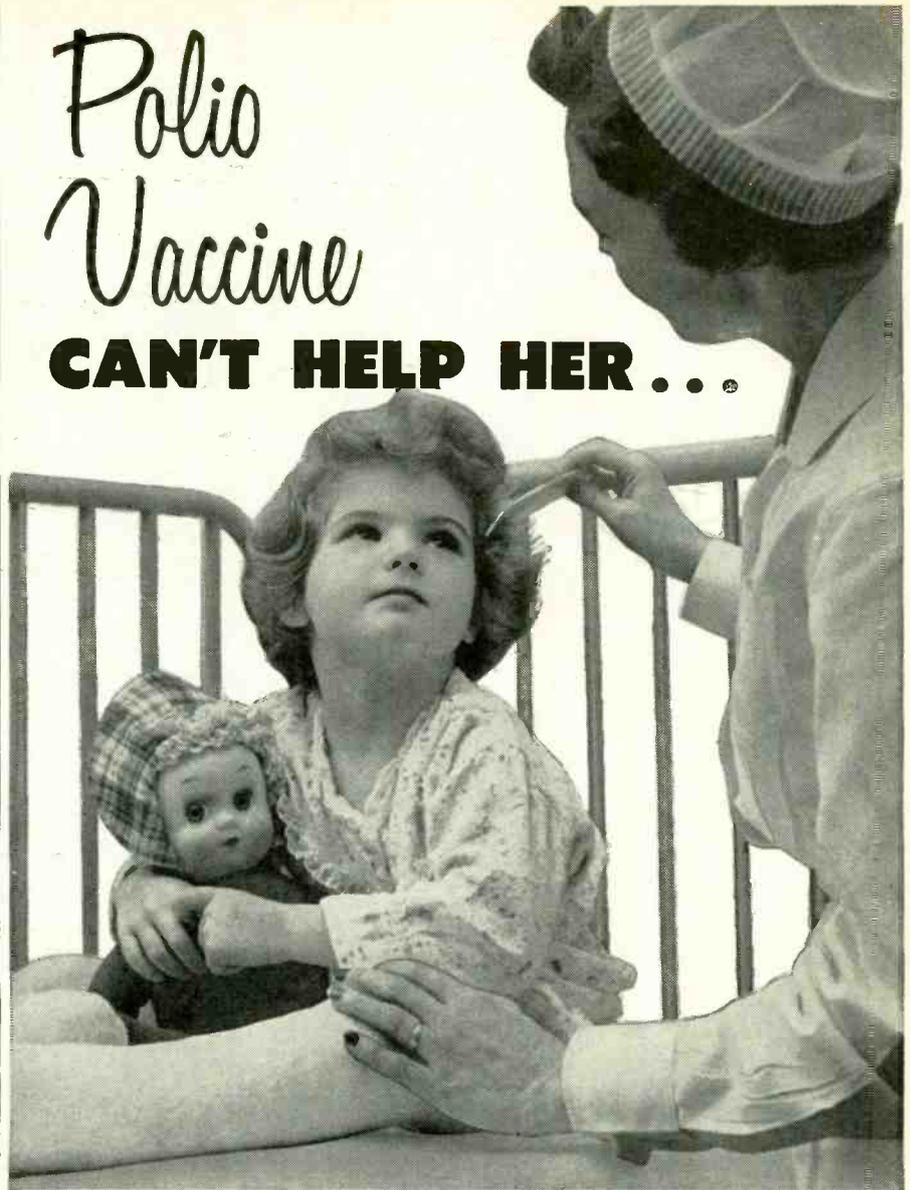

only **YOU** can

Your March of Dimes funds are providing the care she needs. For she is one of the tens of thousands of polio victims "born too soon"—before the epic polio vaccine. Today, March of Dimes funds which developed and tested the vaccine are financing research to improve it. But there still are polio victims who need help. And there will be tens of thousands more stricken before the nation has its blanket of protection. March of Dimes plus the hearts and hands of polio fighters everywhere must continue to provide our main bulwark against polio.

Polio isn't licked yet

Join the **MARCH OF DIMES**  
January 3 to 31

crash near Laramie, Wyo., early last fall.

Alfred H. Corwin, pioneer designer and manufacturer of radio parts and equipment, at his dairy farm near Long Valley, N. J., after a long illness. He was formerly president of Radio Distributing Co., Newark, and Garod Corp., Nutley, N. J.

**Personnel Notes**

... Dr. Elmer W. Engstrom, executive vice president, research and engineering, of RCA, was elevated to the new post of senior executive vice president in a realignment of top level positions at RCA. Ewen C. Anderson was named executive vice president, public relations; Charles M. Odorizzi, executive vice president, sales and services, and W. W. Watts, executive vice president electronic components. Robert A. Seidel continues as executive vice president, consumer products. Dr. Douglas H. Ewing was elected vice president, RCA Laboratories; Charles P. Baxter, vice president and general manager, RCA Victor Television Division; James M. Toney, vice president and general manager, RCA Victor Radio and Victrola Division.

... Frederick D. Ogilby, vice president of the Philco Television Division, was appointed vice president, marketing, and James M. Skinner, Jr., also a former vice president of the Television Division, was named vice president and general manager of the Television Division. Philco also established a new Automotive Division for the manufacture and sale of radios and other products headed by William H. Chaffee, former vice president and general manager of the Radio Division. Henry E. Bowes, advertising and promotion manager of the Television Division, was made general manager of the Home Radio Division.

... A. C. Elles, industrial and contract sales manager of I.D.E.A., Inc., Indianapolis, was appointed general sales manager of the company. He will coordinate sales activities of three divisions—Regency, Monitoradio and Electronic Equipment.

... J. Homer (Robby) Robinson, veteran sales and merchandising executive, was appointed advertising and sales manager of the Brach Manufacturing Division of General Bronze Co., Newark, N. J., manufacturer of TV antennas.


... Arthur V. Loughren, vice president in charge of research for Hazeltine Corp., was elected president of the IRE for 1956. Frank J. Bingley, Philco Corp., was named to receive the Institute of Radio Engineers' Vladimir K. Zworykin Television Prize Award for 1956.

... Seymour D. Gurian, assistant sales manager in charge of the New York office of Radio Receptor Co., Brooklyn, N. Y., and senior engineer of the Engineering Department's components and standards section, was named sales manager of the Engineering Products Division. END


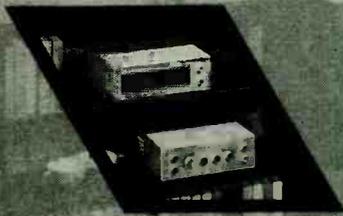
## MUSCLES DON'T MAKE MUSIC

Great music, superbly rendered, draws life and warm beauty from the teamwork of the true artist's heart and hands. Precise coordination of mind and body — not muscular power — is the secret of artistic accomplishment.



Great performance is faithfully recreated in the full brilliance of original rendition by electronic teamwork in high fidelity sound systems.

components are tailored to true balance, to inter-relationship and interaction as precise and coordinated as the fingers and feelings of the musical artist. Only through such thorough integration can you be assured the utmost in listening pleasure.

*for the best in home hi-fi, look to Newcomb*

**NEWCOMB, Dept. RE-1**  
6824 Lexington Ave., Hollywood 38, Calif.

Enclosed is 25c for booklet "Hi-Fi Is for Everybody."

Send name nearest Newcomb dealer and details on Newcomb Compact.

name \_\_\_\_\_

address \_\_\_\_\_

city \_\_\_\_\_ state \_\_\_\_\_

Ask your dealer to demonstrate the new Compact Series of amplifiers and tuners

# NEWCOMB

*the Sound of Quality Since 1937*



## AMPLIFIERS

### for Public Address

*Backed by the world's greatest performance record for power at low cost!*



**3 Popular Sizes**

10, 15 and 30-watt power output. Available with phonograph top or as a complete portable ready-to-use system including microphone, speaker and case. Engineered for top performance and easy operation. A model for every need.



Send for **FREE** New Catalog!

**PRECISION ELECTRONICS, INC.**  
9101-RE King Ave., Franklin Park, Ill.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

106-55

## AUDEL TV TELLS HOW TO ANSWER RADIO T.V. QUESTIONS

### SERVICE LIBRARY

HERE IS LATE INFORMATION IN A HANDY FORM FOR TELEVISION AND RADIO REPAIRMEN, SERVICEMEN AND STUDENTS




**AUDEL'S TELEVISION SERVICE LIBRARY**—Highly Endorsed—Over 1500 Pages—1048 Illustrations & Diagrams. 1001 Important Facts & Figures on Modern Television, Radio, Electronic Devices at your finger ends.

**INCLUDES TRANSISTORS** & Transistor Circuits, Record Changers, Rectifiers, P.A. Systems, Tape Recorders, Phonograph Pick-ups, F.M., Auto Radio, Radio Compass, Short Wave, Radar, etc.

**ASK TO SEE IT!**  
**IT WILL PAY TO KNOW—**  
The Basic Principles—Construction—Installation—Operation—Repairs—Trouble Shooting. Shows How to get Sharp, Clear T.V. Pictures. Install Aerials—How to Test. Explains Color Systems, Methods of Conversion, Terms, etc. Includes Ultra High Frequency—Valuable for Quick Ready Reference and Home Study.

**\$6 COMPLETE 2 VOLUMES**

Get this Information for Yourself.

**7 DAY TEST—PAY ONLY \$1 A Month**

**MAIL ORDER**

**AUDEL Publishers, 49 W. 23 St., N.Y. 10, N.Y.**  
Mail AUDEL'S T.V. RADIO SERVICE LIBRARY (2 Volumes) \$6 on 7 days free trial. If O. K. I will remit \$1 in 7 days and \$1 monthly until \$6 is paid. Otherwise I will return them.

Name \_\_\_\_\_


Address \_\_\_\_\_

Occupation \_\_\_\_\_

Employed by \_\_\_\_\_ RE

THE VERY BEST IN CUSTOM TELEVISION


BY **TECH-MASTER**

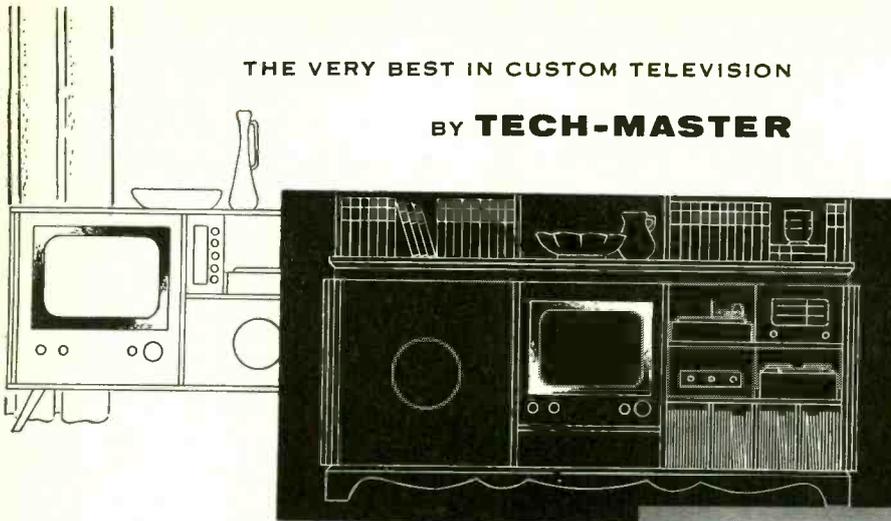

FOUND IN THE FINEST OF INTERIORS

As the custom installation signifies the ultimate in well-chosen decor . . . so the name Tech-Master stands for the utmost in Custom television. The reputation established with the manufacture of the renowned Model 630 chassis is further enhanced by the outstanding Tech-Master Audiophile and Sound Theatre.

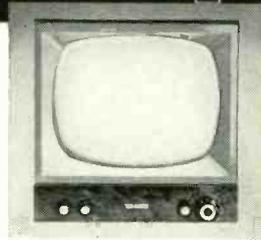
See your Custom hi-fi dealer today . . . or write  
**TECH-MASTER CORPORATION**  
75 FRONT STREET, BROOKLYN, NEW YORK



**ONLY TECH-MASTER HAS THESE OUTSTANDING PLUS FEATURES:**

- World-famous 3 tube synchrolok picture circuit for constant picture stability. • 30 tubes fully used. • "Full Frame Mounting" . . . just a simple cutout is required for installation.
- High fidelity picture as well as exceptional audio reproduction.

for faultless playback and recording!

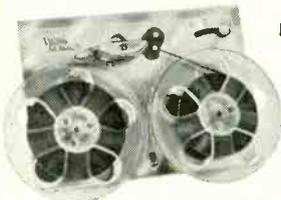

**FULL FIDELITY PERFORMANCE**  
40-14,000 CPS  
at 7.5 IPS  
(±3db)

from  
**\$59<sup>95</sup>**  
USER NET



- Meets broadcast requirements for minimum distortion, flutter and wow.

**GENTLE as a LAMB!**

Now equipped with a fast forward that will not string or break thin-base tape.



- Available in models equipped with monaural, stereophonic (stacked or staggered) and record-playback heads.

At your Dealers. Write for information.

**VIKING OF MINNEAPOLIS**

Dept. RE-1

3520 E. 43rd St., Minneapolis, Minn.



Distributed in Canada by  
Musimart of Canada, 901 Bloor St., Montreal

TV Antennas  
**20% below Dealer Cost!**

Save . . . Buy Direct

from exclusive sales agency of a famous antenna manufacturer.

This is not a closeout but a new "Direct to You" Sales Policy. You pay less and get the very best in VHF and UHF antennas.

featuring


1. Heavy Wall Seamless Aluminum Crossarms. Doweled at points of stress.
2. Heavy Aluminum Elements. Doweled for added strength.
3. Exclusive Reinforced U-Bolt Bracket. Will not spread. Heavy Gauge. Zinc Plated.

Send today for descriptive folder and price lists.

**WILCO PRODUCTS**

5850 N. Whipple Street  
Chicago 45, Illinois

technical  
**Literature**

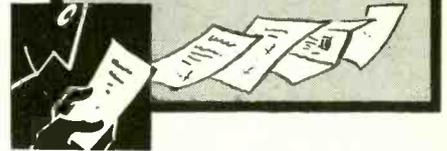

**TV AND BROADCAST MIKES**

Catalog No. 120 contains detailed application information, features and specifications on professional microphones for telecasting and broadcasting. It shows how they work and includes polar patterns, frequency response curves and wiring diagrams. Information on the relation of the particular microphone to the overall station operation is included. Accessories are also illustrated and described.

*Electro-Voice, Inc., Buchanan, Mich.*

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

**OSCILLOGRAPHIC RECORDING**

A 16-page catalog describes the 150 Series of oscillographic recording systems. Included are 11 plug-in preamplifiers and 1-, 2-, 4-, 6- and 8-channel models. Performance data for these interchangeable front ends, as well as frequency response characteristics of galvanometer with driver amplifier, are also provided. Technical details are given on the model 150-1900 master oscillator power amplifier and model 150-300/700 wide-band driver amplifier and power supply. A price list covers basic assemblies, complete systems, preamplifiers, amplifiers, recorders, cabinets, cases and accessories.

*Sanborn Co., Industrial Div., 195 Massachusetts Ave., Cambridge 39, Mass.*

**SINGLE SIDEBAND**

A 24-page bulletin, *Single Sideband, No. 9*, gives ratings for Eimac tubes and discusses other technical topics in this field.

*Technical Services Dept., Eitel-McCullough, Inc., San Bruno, Calif.*

**TEST EQUIPMENT**

Catalog R36A illustrates and describes instruments for servicing TV, radio and other communications equipment as well as industrial electronic and electrical equipment. It also describes the Weston simplified method of visual alignment for TV receivers.

*Weston Electrical Instrument Corp., 614 Frelinghuysen Ave., Newark 5, N. J.*

**POWER AND GAS TUBES**

RCA's 24-page booklet *Power and Gas Tubes, Form No. PG-101B* con-

## TECHNICAL LITERATURE

(Continued)

tains characteristics data on 178 vacuum power tubes, including forced-air- and water-cooled types with output capabilities up to 500 kw. Information on gas, mercury-vapor and vacuum rectifier tubes, gas and mercury-vapor thyratrons, ignitrons, magnetrons and vacuum-gauge tubes is also included. Photographs of representative types and diagrams of either the tube base or envelope connections are included.

Commercial Engineering Dept., RCA Tube Div., Harrison, N. J., 20c.

### TAPE LISTING

Livingston's catalog contains a listing of prerecorded tapes. It includes a large variety of two-channel stereophonic selections and material ranging from Latin-American music, Dixieland and popular to full symphonic works. All releases are at a tape speed of 7.5 i.p.s.

Livingston Electronic Corp., Livingston, N. J.

### REPLACEMENT NEEDLE GUIDE

Recoton's fifth edition of the *Simplified Replacement Needle Reference Guide* lists all popular cartridges and phonographs and their needle replacements, cartridges, recording tape, recording blanks and phonograph accessories.

Recoton Corp., 52-35 Barnett Ave., Long Island City, N. Y., \$2.50.

### HIGH FIDELITY

High-Fidelity Home Music Systems

contains data on Altec's AM-FM broadcast tuner, AM broadcast tuner, control preamplifier, power amplifier, Melodist record reproducer, Iconic speaker system, Biflex speakers, duplex speakers, etc.

Altec Lansing Corp., 9356 Santa Monica Blvd., Beverly Hills, Calif., and 161 6th Ave., New York 13, N. Y.

### TV TROUBLESHOOTING

*Servicing Television Receivers by Signal Tracing* is a 68-page book on TV troubleshooting. It gives data on the Hickok model 650C video-r.f. generator.

Free to interested manufacturers, distributors, etc. Hickok Electrical Instrument Co., 10531 Dupont Ave., Cleveland, Ohio.

### POTTING CONNECTORS

A 12-page two-color *Manual PM-1, Methods of Potting Cannon Plugs*, contains numerous illustrations and instructions on potting connectors for sealing against moisture. Ways to mix the sealant, potting forms, types of guns and various required time intervals are discussed in detail. Also included are both resilient and plastic-insert potting connector types with complete dimensional data.

Cannon Electric Co., 422 W. Avenue 33, Los Angeles 31, Calif.

### CERAMIC MAGNETS

Catalog No. 15 gives in 4 pages the characteristics, design and application

of the *Indox I* ceramic permanent magnet. It describes the manufacturing processes involved and lists the types of *Indox* magnets available for experimental purposes.

Indiana Steel Products Co., Valparaiso, Ind.

### DIELECTRIC CAPACITORS

*Bulletin XC-201-4* illustrates and gives complete technical information on the high-temperature 165°C XC plastic-film dielectric hermetically sealed tubular capacitors. Included are capacitance listings, dimensions and voltages, dimensional drawings and engineering data and typical curves.

Gudeman Co., 340 W. Huron St., Chicago 10, Ill.

### RESISTORS

A bulletin on new glass-sealed carbon-film resistors (*PT 1000*), contains information on their stability characteristics, resistance values, matched networks, tolerances, temperature and voltage limits.

Pyrofilm Resistor Co., 8 Whippany St., Morristown, N. J.

### SHEET METAL

*Forming Sheet Metal for Fun and Profit* by Louis E. Garner describes in detail methods of fabricating boxes, brackets and chassis from sheet metal.

Television Accessories Co., Dept. L, 1412 Great Northern Bldg., Chicago 4, Ill. END

**FREE COUPON** for exciting gifts for every dollar you spend. Electrical appliances, etc. for use in home, sale over counter. Send for **FREE PREMIUM CATALOG** order now. Start collecting these valuable coupons!

**FREE GIFT COUPONS**

Send for **STANLEY'S** Free Complete **TUBE & PART LISTING**

**TUBE SPECIALS**

Till Feb. 1st

Brand New DuMont Licensed **PICTURE TUBE**

178P4 3 for \$50

Single, each, **\$19**

Reg. \$27.50 each

All brand new packed in factory cartons!

**SAVE MONEY ON PARTS & TUBES**

**CATHODE RAY TUBE SPECIALS!**

All brand new! DuMont Licensed! One Year Guarantee!

Discounts on Quantity Purchases

Type	List	Price
10BP4	\$14.95	\$11.99
10RP4	\$14.95	\$10.00
12JP4	\$18.75	\$13.99
12LP4	\$18.75	\$14.99
14BP4	\$22.50	\$15.99
15AP4	\$26.75	\$18.99
16AP4	\$34.25	\$19.99
16EP4	\$34.25	\$21.75
16FP4	\$33.25	\$18.75
16GP4	\$33.25	\$20.99
16HP4	\$28.35	\$18.99
16JP4	\$27.95	\$19.00
16KP4	\$28.35	\$17.99
16LP4	\$28.50	\$17.99
16RP4	\$24.20	\$17.00
17BP4	\$27.50	\$19.00
17HP4	\$27.50	\$19.00
17LP4	\$26.50	\$18.00
19AP4	\$39.75	\$23.00
19DP4	\$39.75	\$23.00
20CP4	\$30.00	\$24.00
21AP4	\$39.75	\$22.00
21EP4	\$36.35	\$24.00
21FP4	\$36.35	\$24.00
24AP4	\$89.75	\$42.00



**FREE** with each \$25 or more order! 5-pc. Sylvania Repair Kit. Value \$4.95. Includes: flashlight head, Philips screwdriver, flat head screwdriver, alignment tool and polystyrene case.

**TERMS** - 25% deposit required on all orders, balance COD. Save COD charges, send full remittance plus postage with order. All unused money refunded with order. **NO MINIMUM ORDER.**

**FREE** with \$3 Order or More!

**Practical, All Purpose ELECTRIC TESTER**

Equipped with genuine GE neon glow lamp. Tests loads from 90 volts to 500 volts. AC or DC. Use it in the home, factory, shop, garage, etc.

Distributors of **SCOTCH MAGNETIC TAPE** made by Minnesota Mining Company

Dept. RE-1

**WELLER DUAL-LITE SOLDER GUN KIT**  
100 watt gun provides the proper heat for most applications. Dual spotlight illuminates work. Kit includes gun, wire solder, dering brush, soldering aid, Kester solder. **\$5.83**

**Packet AC-DC MULTITESTER**  
Hi-accuracy precision VOM-1000 Ohms per V. Reads AC & DC volts 0.5, 25, 250, 1000 V. D.C.M.A. 0.1, 10, 100M. Ohms 1, 10, 100K. Size 1 1/4 D. 4 3/8 L. 3 3/4 W. Test leads. Sold singly, \$9.95. Lots of 3 each \$9.45

**SHELDON PICTURE TUBE BRIGHTENER** \$1.09  
\$1.19 ea. Lots of 3

**TV & RADIO CONTROLS** 5K-50K-100K-200K-500K. 1 meg. less switch. Your choice ea. 19c  
With switch, long shaft, 1/2 meg. -1 meg. ea. 39c  
70° COSINE KEYS TV deflection yoke. New type for anti-magnetic focusing. With leads. List \$10.30 ea. \$2.99

**STANDARD COIL CASCADE TV TUNERS** Long shaft. 41 MC. complete with 6-16, BQ7. 12-channel (2 to 13). ea. \$13.95  
Long shaft can be cut

**UNIVERSAL 4-PRONG AUTO RADIO VIBRATOR** For 90% of 6 volt auto sets. \$1.39 ea. Lots of 10 ea. \$1.29

**KNOB KIT** 25 assorted knobs for radio. TV. ea. kit 89c

**GE TYPE FLYBACK TRANSFORMER** 14.5 KV Flyback. use with 6BP4 or 6CD6. 12 to 14.5 KV ea. \$2.49

**VISULITE TV TUBE CHECKER AND CONTINUITY TESTER** Automatically checks all tubes, tests electrical devices such as fuses, lamps, resistors, etc. ea. \$3.85

**6-FOOT EXTENSION CORD** UL approved. Double outlet. Molded rubber plugs. 22c ea. Lots of 5 ea. 19c

**TUBE SOCKET KIT** 25 asst. octal, loctal, 7 pin, 9 pin miniature in bakelite and wafer type. Complete ea. kit 89c

**TERMINAL STRIP KIT** Assortment of most wanted type for radio. TV. Complete ea. kit 59c

**INSULATED RESISTOR KIT** Assortment of 100 1/2 watt, 1 watt, 2 watt resistors. RIMA color coded. Handy plastic utility kit. List \$15.80 ea. kit \$1.95

**SPEAKERS - Terrific Savings!**

4" PM Matching output transformer ea. \$1.59  
5" FM AC-DC sets, intercons. ea. \$2.00  
\$1.79 ea. Lots of 10 ea. \$2.00  
6" PM ea. \$2.29 ea. Lots of 10 ea. \$3.29  
8" PM For radios, small PA systems. ea. \$3.49 ea. Lots of 10 ea. \$3.75  
10" PM ea. \$3.95 ea. Lots of 10 ea. \$4.50  
12" PM Jumbo Alnico, 5 magnet. ea. \$5.50 ea. Lots of 8

**LEKTRON**  
**KIT KING**  
**SPECIALTIES**

**NEW FOR '56!**  
**CREDIT BONUS PLAN!**  
First Time Ever  
In Electronics!

**EVERY PURCHASE GOOD FOR "CREDITS" TOWARD YOUR FREE BONUS KIT!**

As always...  
**YOUR CHOICE OF ANY KIT FREE WITH EACH \$10 ORDER!**  
(Amounts over \$10 will be credited to your account.)

**Here's How It Works:**  
\* With your first purchase under the plan, you are issued a Credit-Bonus Card, showing 1 credit for each dollar of your purchase.  
\* You send your Credit-Bonus Card with each subsequent order, to have your credits entered.  
\* When your Credit-Bonus Card shows 10 credits, you automatically get the kit you choose, FREE!

**Start Earning Your Free Bonus Kit TODAY!**

- 60 MICA CONDENSERS.** Rare buy! Postage stamp type. 25 values. .00001 to .01 mf. Many silver. 5¢ too! Wt. 1/2 lb. Reg. \$17 **\$1**
- 50 CERAMIC CONDENSERS.** A Kit King first! 25 values in disc, button & tubular ceramics; 5 mmf. to .01 mf. to 1000 V. Duals too! Wt. 1/2 lb. Reg. \$15 **\$1**
- 25 TUBE SOCKETS.** USA first! Subminiatures, 7 & 9-pin miniatures, 4, 7, 8-pins. Radio, TV. Hub must! Wt. 1 lb. Reg. \$9 **\$1**
- 15 VOLUME CONTROLS.** More-for-less! 10 values, concentric & WW. too! Some w/switch. Wt. 1 lb. Reg. \$13 **\$1**
- 15 ROTARY SWITCHES.** Scoop! Single & dual w/keys. Experimenters, note! Wt. 2 lbs. Reg. \$14 **\$1**
- 10 TOGGLE MICRO. PUSH SWITCHES.** Builders' special! Wide variety, with 10 "on-off" plates. Wt. 1 lb. Reg. \$8 **\$1**
- 10 CHASSIS.** Never before! 1, 2, 3, 4 & 6 tube chassis for amplifiers, pre-amps, power supplies, etc. Shop must! Wt. 3 lbs. Reg. \$9 **\$1**
- 30 BATHTUB & TUBULAR OILS.** Wide variety of values. .005 to 2 mf., up to 600 V. Wt. 2 lbs. Reg. \$25 **\$1**
- 60 TUBULAR CONDENSERS.** 25 values. .00035 to 1 mf. to 1800 V. Moulded. too! Wt. 2 lbs. Reg. \$10 **\$1**
- 60 CARBON RESISTORS.** Insulated. 35 values: 15 ohms to 10 megs; 1/2, 1 & 2 w. Many 1 & 5¢ famous Allen Bradley, too! Wt. 1/2 lb. Reg. \$18 **\$1**
- 125 CARBON RESISTORS.** 40 values; 100 ohms to 1 meg; 1/2, 1 & 2 w. Many 5¢. Uninsulated. Wt. 1 lb. Reg. \$21 **\$1**
- 2000 PCS. HARDWARE.** Screws, washers, lugs, grommets, etc. Wt. 3 lbs. Reg. \$11 **\$1**
- 1000 PCS. SPAGHETTI.** Precut for shop use. Lengths to 4", 8 sizes; 2 1/8 thru 3/8". Ass'd. colors. Insulation. Wt. 1/2 lb. Reg. \$7 **\$1**
- 8 PC. NUTDRIVER KIT.** Plastic handle; 3/16, 7/32, 1/4, 5/16, 11/32, 3/8, 7/16" steel socket wrenches in Plastic case. Wt. 1/2 lb. \$3.50 value **\$1**
- TEN 25-FT. ROLLS WIRE.** Plastic & cloth insulated. Solid and stranded. #18 to #24. Ass'd. colors. Wt. 1 lb. Reg. \$3 **\$1**
- 10 TWIST LOCK ELECTROLYTICS.** 5 to 100 mf., up to 450 V. Each can different values. All multiple sections. Wt. 3 lbs. Reg. \$18 **\$1**
- CHECK THESE NEW YEAR'S BELLRINGERS!**
- SAVE \$7 ON FAMOUS CLOCK-TIMER!** REG. \$21... only **\$3.33**
- WESTON 0-100 MICRO-AMP METER** REG. \$21... only **\$3.33**
- CLEAR PLASTIC CASE** WEIGHS ONLY 2 OZ.
- ONLY 1 3/4" x 2"**
- RED HAIRLINE POINTER**
- WELL DAMPED**
- SCALE READS 0 to 25**
- ALL BRAND NEW!** TWO FOR \$6.00

**WRITE FOR NEW 1956 BARGAIN BULLETIN!**  
HOW TO ORDER: Check items wanted. Return entire ad with check or MO. Incl. sufficient postage, excess returned. C.O.D. orders 25% down. Rated, Net 30 days. RE-1

- CONTROLS APPLIANCES, LIGHTS
- HUNDREDS OF USES!
- HANDSOME CHROME FINISH!
- TURNS DEVICES "ON OR OFF" WITHIN 12-HOUR PERIOD
- 110 OR 220 V AC. 25 or 50 Amps.
- With instructions. Wt. 2 lbs.

Name \_\_\_\_\_ (Please PRINT)  
Street \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_  
Enclosed \$\_\_\_\_\_ for kits, \$\_\_\_\_\_ for postage.

**LEKTRON SPECIALTIES**  
28 Garden Street Chelsea 50, Mass.

**Books**

**COLOR TELEVISION FOR THE SERVICE TECHNICIAN**, by Albert C. W. Saunders. Howard W. Sams & Co., Inc., Indianapolis, Indiana. 8 1/2 x 11 inches, 110 pages. \$2.50.

A fine text on color television, this book is beautifully balanced with the development of the color TV signal, and picture tubes, discussed in the first half and the color receiver covered in the second. A notable point is the constant technical level of presentation. While being very complete, it never is too technical, never oversimplified.

The opening half of the book covers colorimetry, color television, the color carrier, color signal analysis and the tricolor picture tube. The text is heavily supported by illustrations.

The section on the color receiver is well done with numerous block diagrams showing the general principles of the receiver, followed by representative schematics from current color TV receivers. In one respect this section falls short: The manufacturer's installation adjustments for several receivers are given. This makes for tiresome reading for those technicians—and there are many—who have never worked on a color TV set. This type information will not be retained by the reader as will, for example, that on theory and circuitry of color television that is supported with photographs and schematics.

This book will surely benefit those who study it. The general circuitry described is unlikely to be changed for some time to come.—JK

**COLOR TV SERVICING**, by Walter H. Buchsbaum. Prentice-Hall, Inc., 70 5th Ave., New York, N. Y. 6 x 9 inches, 257 pages. \$6.35.

The title is somewhat misleading in that a comparatively small part is devoted to color TV servicing. The author does a good job of describing the overall operation of the color TV receiver, using numerous schematic diagrams of current-model color TV sets and many illustrations. This makes for instructive reading but does not add a great deal to the technician's ability to service color receivers.

Buchsbaum opens his book by following the beaten path through an introduction to color television. He follows this with principles of colorimetry and the composition of the color TV signal. Unfortunately, the text at several places becomes much too complex for easy reading. From this point on the book covers the various sections of the

**Ask For Sprague By Catalog Number**

Know what you're getting... get exactly what you want. Don't be vague... insist on

Sprague. Use complete radio-TV service catalog C-610. Write Sprague Products Company, 81 Marshall Street, No. Adams, Mass.

**DON'T JUST SAY CAPACITORS**

**SPRAGUE**  
WORLD'S LARGEST CAPACITOR MANUFACTURER

**NOW IN STOCK at ALMO RADIO CO.**

509 Arch St., Phila. 6205 Market St.  
7540 Frankford Ave.



**EICO**  
**COLOR & BLACK & WHITE**  
**5" - 5 MC SCOPE**  
KIT \$79.95 Wired \$129.50 #460

**Joe Serviceman says:**



**"You can't get somethin' for nothin', especially Quality and Reliability"**

**QUIETROLE**

TRADE MARK REG. U.S. PAT. OFF.



the original lubricant and cleaner for quieting noisy controls and switches, costs little more than the cheapest imitations, but the name assures you are getting the best.

**INSIST ON QUIETROLE**  
THE CHOICE OF BETTER SERVICE DEALERS "EVERYWHERE"



manufactured by **QUIETROLE COMPANY**  
Spartanburg, South Carolina

(Continued)

color TV system including chapters on color picture tubes and circuits, a typical color TV receiver, the color decoder and color synchronization.

The final chapters follow the intent of the title, including installation, r.f.-i.f. alignment, color decoder adjustment, troubleshooting monochrome operation, wrong-color defects and miscellaneous troubleshooting. Included are some excellent color photos.—JK

**SWEEP AND MARKER GENERATORS FOR TELEVISION AND RADIO** by Robert G. Middleton. (Gernsback Library No. 55.) Gernsback Publications, Inc., 25 W. Broadway, New York 7, N. Y. 5 1/2 x 8 1/2 inches, 224 pages. \$2.50.

As its name implies, this volume is concerned mainly with equipment, not technique. Most service books assume that the technician is using perfect test equipment. Here the author points out possible faults and errors in the generator signal, how to test for them, how to correct them.

Of all service shop equipment, the sweep generator is probably the most critical. If it does not put out the signal expected of it, it may cause serious errors in alignment and adjustment of the receiver. Among the requirements and characteristics clearly discussed here are: flatness, calibration, shielding, attenuation, termination, stray effects. Many photos illustrate the effects caused by poor design or equipment failure.

The last two chapters cover alignment procedure. One is for AM and FM radios (shortwave and broadcast), the other describes visual-alignment methods. Diagrams show typical setups and response curves.

**EXPLAINING THE ATOM**, by Selig Hecht. Revised and expanded by Dr. Eugene Rabinowitch. Viking Press, New York, N. Y. 5 1/2 x 8 1/2 inches. 237 pages. \$3.75.

The atomic bomb *can* be described in everyday language. It is done effectively with the aid of simple illustrations in this revised edition that brings the subject right up to date.

The prologue emphasizes that the atomic bomb didn't happen overnight but is the result of more than 50 years of scientific thinking and discoveries. Chapter 1 describes early theories, and later it turns out that the atom is not nearly as simple as first supposed. The nucleus, various particles, charges and isotopes are clearly discussed. Then the relationship between mass and energy prepares the reader to understand the bomb itself. Later chapters discuss peacetime applications of atomic energy and the H-bomb.

One chapter reveals efforts in 1939 by top scientists to interest officials in the military possibilities of atomic energy and how an appeal was finally made direct to President Roosevelt. Also described are postwar efforts to outlaw the bomb and how they failed.



# 460

**KIT**  
**\$79.95**

**Factory Wired \$129.50**

- V amplifier direct-coupled and push-pull thruout; gradual roll-off beyond 4.5 mc; useful at 10 mc.
- High V sensitivity: 25 mv/in.
- Choice of direct coupling (DC) or capacitive coupling (AC).



Write for **FREE** New 1956 Catalog CS-1 and Name of Distributor

84 Withers Street • Brooklyn 11, N. Y.

©56 Prices 5% Higher on West Coast

**NOW IN STOCK AT YOUR NEIGHBORHOOD DISTRIBUTOR . . . ORDER NOW!**

**free!** **ALLIED'S**  
**SPECIAL 100-PAGE**  
**HI-FI CATALOG**



Your guide to an easy understanding of Hi-Fi—plus the world's largest selection of Hi-Fi systems and components

**Send for It**

This leading 100-page book shows you how to select a Hi-Fi music system at lowest cost. Tells you what to look for in each unit; shows many handsome, practical installation ideas. Offers you the world's largest selection of complete systems and individual units from which to make your money-saving choice. To understand Hi-Fi, to own the best for less, you'll want this invaluable catalog. It's **FREE**—write for your copy today.

**ALLIED RADIO**

*America's Hi-Fi Center*

**ALLIED RADIO CORP., Dept. C-16**  
100 N. Western Ave., Chicago 80, Ill.

Send **FREE** High Fidelity Catalog

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**Every Contribution Counts!**

Give to . . .  
**the MARCH of DIMES**

**HI-FI and LP BUYERS**  
**CHOOSE AUDIO UNLIMITED**

- ✓ We ship **PREPAID** and **INSURED**
- ✓ **FAST, PROMPT, COURTEOUS** service
- ✓ **BRAND NEW STOCK—FACTORY SEALED**
- ✓ **FREE LP CATALOG** with **ORDER** only
- ✓ **FREE**—on orders of \$50.00 or **MORE**—A Genuine Diamond Stylus of Your Choice—List \$27.50

**SPECIAL**

**COLUMBIA FAMOUS DUAL SPEAKER; PUSH-PULL MODEL 360**, in Blond or Mahogany Veneers. **RONETTE FLIP CARTRIDGE** with **DIAMOND LP STYLUS**. List \$147.50  
**YOUR COST \$99.50 PREPAID IN U.S.A.**

H. H. Scott, Fisher, Pilot, Pentron, Harman, Karlon, Bozak, Rek-O-Kut, Telefunken, etc. RCA, Columbia, Angel, Capitol, Decca, Mercury, Cook, etc.  
Dept. E-1

**AUDIO UNLIMITED Inc.**  
169 W. 57 St., N. Y. 19, N. Y.  
**DIRECTLY OPPOSITE CARNEGIE HALL**



# DIRECTORY

## LEARN TV

*'At the most practical school in the west'*

Work on late model sets—using modern equipment and service techniques; under qualified technician instructors. Short resident and correspondence courses—no unnecessary math or theory—also UHF and Color TV.

APPROVED FOR VETERANS . . . day and nite classes.

Write for free literature, Dept. IA for residence—Dept. IAC for correspondence.

**V.S.I. TELEVISION SCHOOL**

4570 Firestone Blvd.  
South Gate, California

## RADIO-TV ELECTRONICS



CREI graduates in big demand. ECPD-Accredited Technical Institute Curricula. New classes start monthly. Free placement service for grads. Courses: Radio Engineering, Broadcast or TV Engineering; TV, FM, AM Servicing; resident studies leading to "Associate in Applied Science" degree. Write for free catalog. Approved for vets.

**CAPITOL RADIO ENGINEERING INSTITUTE**

Dept. RE, 3224—16th St., N.W., Washington 10, D.C.

## Get Your F. C. C. LICENSE Quickly!

Correspondence or residence preparation for F.C.C. examination. Results guaranteed.

An FCC commercial operator license means greater opportunities and higher pay. We are specialists in preparing you, in a **MINIMUM OF TIME**, to pass FCC examinations for all classes of licenses. Beginners get 2nd class license in 8 weeks and 1st class in 4 additional weeks.

Regularly scheduled resident classes are held in Washington, D. C., and Hollywood, California. Correspondence courses are conducted from Washington. Write for our free booklet which contains complete details.

**GRANTHAM School of Electronics**

Dept. 40-A 5910 Sunset Blvd. Hollywood 28, Calif. **OR** Dept. 40-A 821 19th St. N.W. Washington, D.C.

**CODE SENDING RECEIVING SPEED**

Be a "key" man. Learn how to send and receive messages in code by telegraph and radio. Commerce needs thousands of men for jobs. Good pay, adventure, interesting work. Learn at home quickly through famous Candler System. Qualify for Amateur or Commercial License. Write for FREE BOOK.

**CANDLER SYSTEM CO.**  
Dept. 3-A, Box 928, Denver 1, Colo., U.S.A.

**wanted career men**

Train for a career instead of a job. Demand for our graduates exceeds supply. Effective placement. Modest costs. Small classes. Well-equipped labs. Beautiful campus. Approved for Vets. Enter March, June, Sept., Jan.

**BACH. SCI. DEGREE IN 27 MONTHS**  
Complete Radio Eng. courses . . . TV, UHF, FM, Electronics. Also Mech., Civil, Elec., Chem., Aero. Eng. 36-month B.S. in Bus. Adm. (Gen. Bus., Acctg., Motor Transport Mgt.) . . . capable students faster. Prep courses. Write Jean McCarthy, Div. Adm., for catalog and "Your Career in Engineering & Commerce."

**TRI-STATE COLLEGE**  
2416 College Avenue, Angola, Indiana

**GET INTO ELECTRONICS**

You can enter this uncrowded, interesting field. Defense expansion. New developments demand trained specialists. Study all phases radio & electronics theory and practice: TV; FM; broadcasting; servicing; aviation, marine, police radio. 18-month course. Graduates in demand by major companies. H.S. or equivalent required. Begin January, March, June, September. Campus life. Write for catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
Dept. C Valparaiso, Indiana



## TV REPAIRMEN EARN TOP MONEY!

IN JUST 12 MONTHS, COMPLETE TV SERVICE TRAINING, INCLUDING COLOR TV. Streamlined course gives you all essentials for a good job as service technician. Graduates in great demand; jobs are plentiful in this growing field. Other electronic courses in radio operation and maintenance. Day or evening classes. Opportunity for employment in local industry. Approved for Korean veterans.

Write for Catalog 111 Today

**INDIANAPOLIS ELECTRONIC SCHOOL**  
312 E. Washington, Indianapolis 4, Ind.

## ELECTRONICS

Prepare for un-engineering degree in 27 months

Limited opportunities in electronics! B.S. degree in 27 months. Intensive, specialized courses. Math, electrical engineering, TV, advanced radio theory & design. Mod. labs. Low tuition. Self-help. Also Aeronautical, Chemical, Civil, Electrical, Mechanical Engineering. G.I. approved. Enter Dec., Mar., June, Sept. Catalog.

**INDIANA TECHNICAL COLLEGE**  
1516 E. Washington Blvd., Fort Wayne 2, Ind.

**EARN MORE MONEY— BE A PROFESSIONAL TELEVISION SERVICE TECHNICIAN**

GET DOWN-TO-EARTH PRACTICAL TV TRAINING WITH WTI EXPERTS FOR THE TOP PAYING \$5,000-\$10,000 PER YEAR JOBS.

**UHF—COLOR—VHF**  
Master the latest, up-to-the-minute TV and Color TV developments QUICKLY.

SEND FOR FREE BOOK TODAY!

WESTERN TV offers real experience on live equipment in our BIG SHOPS AND LABORATORIES in the shortest practical time under expert instructors. Graduates are in big demand because they have the "field experience" necessary for immediate "bench" or supervisory positions. You learn every phase of Radio and TV servicing (AM, FM, VHF, UHF). WTI men win fast promotion . . . can demand better pay . . . develop highly profitable businesses of their own with the latest and most PRACTICAL PERSONALIZED TRAINING BEHIND THEM. You concentrate all your time on being a PROFESSIONAL TV SERVICE TECHNICIAN—non-essential math and engineering theory omitted. YOU CAN EARN WHILE YOU LEARN. Special Finance Plan.

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP—Send for this fact-packed book NOW!

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP—Send for this fact-packed book NOW!

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP—Send for this fact-packed book NOW!

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP—Send for this fact-packed book NOW!

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP—Send for this fact-packed book NOW!

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP—Send for this fact-packed book NOW!

APPROVED FOR VETERANS. Find out how you can get into the TOP PAY GROUP—Send for this fact-packed book NOW!

Western Television Institute Dept. E-156  
341 W. 18th St., Los Angeles 15, Calif.  
Without obligation, please send FREE fully illustrated booklet. (No salesman will call.)

NAME \_\_\_\_\_ AGE \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

Your choice of school is highly important to your career in



INDUSTRIAL ELECTRONICS



RADIO



TELEVISION

Become an ELECTRICAL ENGINEER

or an ENGINEERING TECHNICIAN

at MSOE in Milwaukee

Choose from courses in: ELECTRICAL ENGINEERING Bachelor of Science degree in 36 to 42 months with a major in electronics or electrical power.

ELECTRICAL TECHNOLOGY Engineering Technician certificate in 12 months in electronics, radio, or electrical power;

Associate in Applied Science degree in 18 months in radio and television.

TECHNICAL SERVICE

Service certificate in 6 months in electricity; in 12 months in radio and television.

MSOE—located in Milwaukee, one of America's largest industrial centers—is a national leader in electronics instruction—with complete facilities, including the latest laboratory equipment, visual aid theater, amateur radio transmitter—offers 93 subjects in electrical engineering, electronics, radio, television, electrical power, and electricity.

Advisory committee of leading industrialists. Courses approved for veterans. Over 50,000 former students.

Excellent placement record.



TERMS OPEN JANUARY, APRIL, JULY, SEPTEMBER

Choose wisely—your future depends on it. Write for more information today!

**MILWAUKEE SCHOOL OF ENGINEERING**  
Dept. RE-156, 1025 N. Milwaukee St. Milwaukee 1, Wisconsin

Send FREE career booklets on:  
 Electrical Engineering  Radio-Television

I am interested in \_\_\_\_\_ (Name of course)

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

If veteran, give discharge date \_\_\_\_\_ MS-31

Only the 5 TOP QUALITY brands of

# STANDARD BRAND TUBES

AT SENSIBLE PRICES!

All tubes are BRAND-NEW, factory-fresh TV stock. Each tube carries a dual guarantee. Standard factory RTMA guarantee and Barry's own guarantee of positive customer satisfaction. Be SAFE! Buy BARRY!

- Individually boxed • First quality only
- Latest dating • Standard RTMA guarantee
- No private brands • No rejects
- No rebrands or rewashed bargains

**FREE!** Newest handy air-mail order form printed in carbon snap-out sets for your ordering convenience. Lists over 400 popular replacement types.

**WRITE FOR YOUR FREE COPY TODAY!**

- Lists ALL popular TV & radio types.
- Makes mail-ordering a real pleasure.
- All tube orders over \$25.00 (with remittance) postpaid.

## SPECIAL-PURPOSE TUBES

Write for our complete listing on Transmitting, Industrial, Special-Purpose Tubes, and Crystal Diodes. We STOCK over 2000 types at excellent prices.

### SNOOPERSCOPIES, TUBES, PARTS

Type CRI-143 or 147.....EACH \$3.95

#### INFRA-RED FILTER

Snap-on type, for sharper image.....EACH \$1.05

#### HI-VOLTAGE CONVERTER

7MVT—delivers 6000 v. (low current)..... \$12.50

Write for free plans on "How to build a homemade SNOOPERSCOPE". The device that lets you see in the dark!

### DID YOU GET YOUR FREE TUBE CADDY YET?

Write for details!

## 2 COLOR TUBE CARTONS

Keeps your tube stock neat. New safety partition prevents tube breakage. Distinctively lithographed in glossy red and black. The most distinctive tube carton available today. Minimum quantity: 100 of any one size. Write for case lot prices.

SIZE	FOR TUBE	PER 100
Miniature.....	6AU6, etc.....	\$1.00
GT.....	6SN7, etc.....	1.25
Large GT.....	1B3, etc.....	1.50
Large G.....	5U5G, etc.....	2.00

WHITE GLOSSY BOXES  
Completely blank. No printing or color. Otherwise same as above. Same high quality, same low prices. Specify "white" when ordering.

TUBE STACKERS  
White glossy only. Ministacker holds 10 Mini. tube cartons; "GT" stacker holds 10 "GT" cartons.  
SIZE PER 100  
Ministacker.....\$1.50  
GT.....2.00



### KAY MEGA-MARKER

13 crystal frequency TV marker channels. A laboratory precise piece of test equipment. Accurate and dependable. Used, but in exceptionally good condition. While they last.....NET EACH \$80.00

## DIRECTRON SELENIUM RECTIFIERS

### Full Wave Bridge Type

Max. Amps.	18VAC 14VDC	36VAC 28VDC	54VAC 42VDC	72VAC 56VDC	130VAC 100VDC
1	\$1.35	\$2.35	\$3.75	\$4.50	\$7.45
2	2.00	2.75	5.35	5.90	9.15
2 1/2	2.95	4.15	5.85	7.85	12.75
4	3.50	6.45	11.35	14.35	21.75
6	4.00	7.75	12.85	17.30	29.75
10	5.90	11.45	19.50	24.80	41.35
12	7.25	14.35	22.10	29.75	44.25
20	13.05	25.05	37.25	48.75	78.50
24	14.25	28.75	44.50	57.65	81.00
30	17.95	34.35	56.50	71.00	109.00
36	22.45	42.35	65.00	86.95	134.00
50	29.50	54.35	105.45	115.75	174.00
100	59.50	119.00			

We build other Selenium Rectifiers.

Transformers and Chokes to your specifications. Buy from the Direct Source for Quick Delivery.

## NEW RECTIFIER TRANSFORMERS

Pri: 115V, 60 cycles input	1 Amp.....\$ 5.75
SEC: 9, 12, 18, 24, and 36 volts. Continuous	2 Amps.....6.75
	3 Amps.....8.65
	12 Amps.....16.65
	24 Amps.....35.65
	50 Amps.....59.00
	100 Amps.....108.00

## NEW RECTIFIER CHOKES

Continuous Ratings	1 Amp	2 Amps	4 Amps	12 Amps	24 Amps	50 Amps	100 Amps
1 Amp.....	.1 Hy.....	1.5 ohm.....	\$ 4.95				
2 Amps.....	.04 Hy.....	.9 ohm.....	5.95				
4 Amps.....	.07 Hy.....	.8 ohm.....	6.95				
12 Amps.....	.01 Hy.....	.1 ohm.....	14.95				
24 Amps.....	.004 Hy.....	.025 ohm.....	29.95				
50 Amps.....	.005 Hy.....	.01 ohm.....	54.00				

## FILTER CAPACITORS

Capacity	W. Voltage	Each
500 MFD.....	50 V.....	85
1000 MFD.....	15 V.....	35

TERMS: 25% deposit with order, balance C.O.D. All merchandise guaranteed. F.O.B. N.Y.C.

**BARRY ELECTRONICS CORP.**  
Dept. RE  
512 Broadway - N.Y. 12, N.Y.  
Phone: WALKER 5-7000

## ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the index below.

A. L. Products Co.....	178	National Schools.....	5
Alliance Manufacturing Co.....	129	Newcomb Audio Products Co.....	191
Allied Radio Corp.....	9, 119-123, 195	Nidisco.....	179
Almo Radio Co.....	144, 177, 181, 194	Opportunity Adlets.....	174
American Buyers Service.....	144	Oxford Electric.....	172
American Microphone Co.....	171	Part-Paks.....	189
American Phenolic Corp.....	116	Perma-Power Co.....	184
Arkay Radio Kits, Inc.....	189	Permo, Inc.....	183
Astron Corp.....	33	Phostron Co.....	154
Atlas Sound Corp.....	190	Pickering & Co.....	6
Audel Publishers.....	191	Precise Development Corp.....	140-141
Audio Unlimited, Inc.....	190	Precision Apparatus Co.....	162
B & K Manufacturing Co.....	185	Precision Electronics.....	191
Barjay Co.....	184	Prentice-Hall, Inc.....	186
Barry Electronics.....	198	Progressive Edu-Kits, Inc.....	157
Bellford-Matic.....	144	Pyramid Electric Co.....	111
Bell Telephone Labs.....	32, 189	Quietrole Co.....	195
Blonder-Tongue Labs.....	16	Radiart.....	12
Book-of-the-Month Club, Inc.....	13	Radio & Television Training Association.....	17
Brooks Radio & Television Corp.....	150	Radio Corp. of America.....	Back Cover
Burstein-Applebee Co.....	179	Rad-Tel Tube Co.....	156
Capitol Radio Engineering Institute.....	125-126	Rauland-Borg Corp.....	169
CBS-Hytron.....	30	Raytheon Manufacturing Co.....	23
Century Electronics.....	162	RCA Institutes.....	11
Channel Master Corp.....	20-21	Rek-O-Kut Co.....	170
Chicago Standard Transformer Co.....	144	Rider (John F.), Inc.....	24-25
Cisin (H. G.).....	153	Rinehart Books, Inc.....	142, 167, 183
Claroat Manufacturing Co.....	107	Rockbar.....	130
Cleveland Institute of Radio Electronics.....	159-160	Rohn Manufacturing Co.....	131
Colman Tool & Machine Co.....	172	Ross (Karl F.).....	168
Colordapter Co.....	181	R.P.D. Arthur Nagel, Inc.....	187
Columbia Wire & Supply Co.....	138	Sams (Howard W.) & Co.....	147
Concord Radio.....	161	Sangamo Electric Co.....	151
Cornell-Dubilier Electric Corp.....	12, 156	Seco Manufacturing Co.....	170
Coyne Electrical & Television School.....	31, 155, 176	Service Instruments Co.....	187
Delehanty Institute.....	200		
DeVry Technical Institute.....	7		
Dressner.....	168		
Du Mont (Allen B.) Labs.....	Inside Front Cover		
Dyna Co.....	18		
Editors & Engineers.....	177		
Ekeradio Electronic Developments.....	173		
Electro-Voice, Inc.....	Inside Back Cover		
Electronic Instruments Co. (EICO).....	34, 174, 176, 182, 189, 195		
Electronic Measurements Corp.....	164		
Erie Resistor Corp.....	162		
E-Z Way Towers, Inc.....	146		
General Cement Manufacturing Co.....	158		
General Industries Co.....	18		
Gernsback Publications, Inc.....	156, 180		
Hallcrafters Co.....	168		
Hamilton (Alexander) Institute.....	15		
Hawkins (P. E.) Co.....	187		
Heath Co.....	93-104		
Hershel Radio.....	168		
Hughes Research & Development Labs.....	117		
Hycan Manufacturing Co.....	188		
Indiana Technical College.....	146		
Institute of Radio Engineers.....	181		
Instructograph Co.....	181		
International Business Machines Corp.....	199		
International Radio & Electronics Corp.....	176		
Jensen Industries.....	187		
Jerrold Electronics.....	152		
JFD Manufacturing Co.....	26		
Lafayette Radio.....	166		
Lektron Specialties.....	194		
Leotone Radio Corp.....	146		
L. M. B.....	179		
Macmillan Co.....	174		
Mallory (P. R.) & Co.....	148, 149		
McGraw-Hill Book Co.....	178		
Merit Coil & Transformer Co.....	10		
Metropolitan Electronics & Instrument Co.....	145		
Miller (Gustave).....	177		
Mosley Electronics.....	178		
Moss Electronics Distributing.....	132-133		
Musical Masterpiece Society.....	173		
National Radio Institute.....	3, 27-28		
		Baltimore Technical Institute.....	14
		Candler System Co.....	175, 183
		Capitol Radio Engineering Institute.....	179
		Grantham School.....	182
		Indiana Technical College.....	184, 194
		Indianapolis Electronic School.....	19, 184
		Milwaukee School of Engineering.....	196
		RCA Institutes, Inc.....	193
		Tri-State College.....	173
		Valparaiso Technical Institute.....	163
		V.S.I. Television School.....	186
		Wayne School, Inc.....	192
		Western Electronic Institute.....	22
		Western Television Institute.....	158
		Shure Brothers, Inc.....	135
		Simpson Electric Co.....	165
		Sootin's, Inc.....	182
		Sorenson & Co., Inc.....	113
		Sprague Products Co.....	189
		Sprayberry Academy of Radio.....	115
		Stan-Burn Radio & Electronics.....	184
		Stanley Electronics Corp.....	192
		Superior Instruments Co.....	192
		Supreme Publications.....	29
		Tab.....	137
		Tech-Master Corp.....	143
		Technical Appliance Co.....	165
		Television Hardware Manufacturing Co.....	182
		Telrex, Inc.....	113
		Tenna Manufacturing Co.....	189
		Terado Co.....	115
		Thompson Products Co.....	184
		Transvision, Inc.....	8
		Trio Manufacturing Co.....	182
		Tube Mart.....	192
		Tung-Sol Electric Co.....	137
		Universal Television School.....	29
		Viking of Minneapolis.....	192
		Walco Products, Inc.....	137
		Walsco Electronic Sales.....	192
		Wayco, Inc.....	143
		Wilco Products.....	187
		Winegard Co.....	
		Xcelite.....	

## SCHOOL DIRECTORY PAGES 196-197

# IN RETURN FOR CHARACTER ... A CAREER

Because the finest single attribute anyone can offer is character, this, basically, is what IBM asks of its people, whatever their special aptitudes or abilities. IBM offers them in return—not just a job—but a career.

IBM electronic field technicians, for instance, receive more than training and early responsibility; they have a chance to work with the world's largest computer, use the latest testing equipment, employ

the finest computer testing techniques yet devised. Above all, they have the satisfaction of joining the electronics industry's most advanced program, destined for long-range national importance.

You could ask for no finer future.

*If you are between 19 and 32 and have at least a 2-year technical school background, with emphasis on electronics, you can do important work on COMPUTER INPUT-OUTPUT functions. Write: Nelson O. Heyer, IBM, Room 3101, Neighborhood Rd., Kingston, N. Y.*



*The 702 Electronic Data Processing Machine, typical of advances that have made engineering work at IBM one of the most provocative experiences in electronics.*

INTERNATIONAL BUSINESS MACHINES CORPORATION

**IBM**  
®

Producer of electronic data processing machines, electric typewriters, and electronic time equipment.

# DELEHANTY starts PRACTICAL SHOP WORK with your FIRST LESSON!

**Only DELEHANTY gives YOU a MONEY-BACK GUARANTEE! No Risk! No Obligation!**

**NO PREVIOUS TRAINING OR EXPERIENCE NEEDED!**

YOU GET FULL-SIZE  
**21"**  
TV SET & TUBE  
at No Extra Charge!

**First Kit of Tools and Parts sent Immediately with First Training Unit!**

## Learn At HOME **TELEVISION RADIO & ELECTRONICS**

**...We Furnish ALL Your EQUIPMENT at No Extra Cost!**

**Now YOU Too May Qualify for the HIGHER PAY and JOB SECURITY Enjoyed by More Than 12,000 DELEHANTY TV GRADUATES!**

These men are now "cashing in" on the tremendous opportunities in the TELEVISION-RADIO-ELECTRONICS industry. They are working at BIG PAY for leading concerns all over the country, or are operating their own successful business. YOU CAN DO THE SAME! Mail coupon TODAY for full details of UNIQUE MONEY-BACK OFFER.

**ENTIRELY NEW, FRESH, UP-TO-THE-MINUTE TRAINING THAT INCLUDES NEARLY 400 PRACTICAL SHOP PROJECTS!**

Perfected by a large staff of electronic experts, engineers, technicians and teachers with extensive practical field experience. Entirely new and up-to-date. Includes Ultra High Frequency, Color TV, Printed Circuits, Transistors, Geiger Counters, High Fidelity, and other last-minute electronic developments. You enjoy over 400 interesting and practical experiments in applied electronics during your training with 15 Big Kits of Tools, Tubes, Parts and Equipment that we furnish at NO EXTRA COST!

**YOU EARN EXTRA MONEY SOONER!**

Because you get right down to business with practical work from the very beginning you are able to earn money quickly in spare time. By repairing radios and electrical appliances for friends and neighbors you can actually earn the money to pay for this unique Delehanty training!


In a Matter of Months You Can Be Ready for FULL-TIME JOBS at GOOD PAY or a PROFITABLE BUSINESS OF YOUR OWN!

**SET YOUR OWN PACE OF STUDY PAY AS YOU GO—AVOID DEBT!**

Order each Training Unit only when YOU want it . . . ALL UNITS ARE AT SAME LOW PRICE . . . no time payments to worry about . . . NO EXTRA PAYMENTS —NOT EVEN FOR A POSTAGE STAMP! We pay ALL postage BOTH ways, anywhere in the U.S.

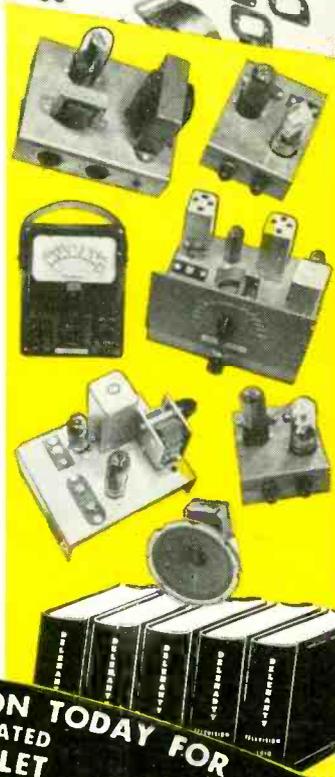**WE SEND YOU 15 BIG KITS . . . YOU BUILD AND KEEP YOUR OWN:**

21-Inch TV Set with 21" Picture Tube—Superheterodyne Radio with All Tubes—Multimeter—Ammeter—Ohmmeter—Voltmeter—Radio Telephone Transmitter—RF Amplifier—And Many Other Useful Electronic Devices—A Valuable Permanent Reference Library of 5 volumes in handsome 3-ring binders.



**MAIL COUPON TODAY FOR FREE ILLUSTRATED BOOKLET**

# DELEHANTY INSTITUTE OF TELEVISION

APPROVED BY STATE OF NEW YORK  
115 EAST 15 ST., NEW YORK 3, N. Y.

NO OBLIGATION • NO SALESMAN WILL CALL

DELEHANTY INSTITUTE OF TELEVISION RE-156  
115 East 15th Street, New York 3, N. Y.

Please send me by return mail your Free Booklet "How to Achieve Success in Television, Radio and Electronics." This does not obligate me in any way.

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

— (PLEASE PRINT — Paste on Post Card or Mail in Envelope) —

# ...STOP UNWANTED SOUNDS

with the NEW **664** VARIABLE D\*



## CARDIOID

### for P.A.



### Now... Broadcast Performance Designed for Public Address

**COMPLETELY NEW ALL-PURPOSE CARDIOID DYNAMIC MICROPHONE BRINGS NEW EFFICIENCY OVER WIDE FREQUENCY RANGE**


All the advantages of the E-V Variable D\* are now available in the new high-fidelity "664"... for public address, recording, communications and similar applications. Uniform cardioid polar pattern provides high front-to-back discrimination against unwanted sounds, without close-talking boominess. Easily solves sound pick-up and reproduction problems under a great variety of conditions. Gives distinct, natural reproduction of voice and music. Increases working distance from microphone. Gives greater protection against feedback. Especially useful where ambient noise and severe reverberation exist. Pop-proof filter minimizes wind and breath blasts. E-V Acoustalloy diaphragm guarantees smooth wide-range reproduction. Can be used on a floor or desk stand or carried in the hand. No other microphone for performance and value! *Write for Technical Specification Sheet.*



\*EV Pat. Pend.

**Model 664.** Variable D\* Super-Cardioid Dynamic Microphone. Uniform response at all frequencies from 60 to 13,000 cps. Output level —5 db, 150 ohm and High impedance. Impedance changed by moving one connection in connector. Line balanced to ground and phased. Acoustalloy diaphragm, shielded from dust and magnetic particles. Alnico V and Armco magnetic iron in non-welded circuit. Swivel permits aiming directly at sound source for most effective pick-up. Pressure cast case. 5/8" —27 thread. Satin chrome finish. 18 ft. cable with MC4M connector. On-Off switch. Size: 1 1/4 in. diam. 7 3/4 in. long not including stud. Net wt.: 1 lb. 10 oz. List Price \$79.50

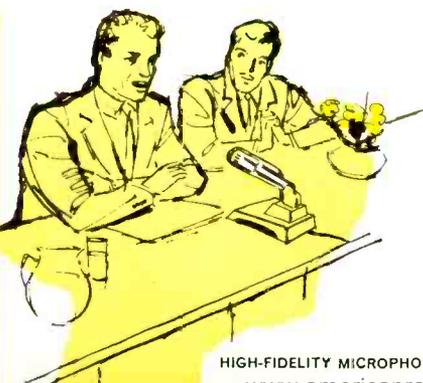Model 419 Desk Stand available for use with the "664" (extra).




# Electro-Voice®

ELECTRO-VOICE, INC. • BUCHANAN, MICH.

Export: 13 East 40th Street, New York 16, N. Y. U. S. A. Cables: Arlab

HANDLE YOUR REPLACEMENTS FOR OVER 110 TYPES OF PICTURE TUBES WITH JUST 25 TYPES...TYPES IN THE GREAT NEW LINE OF
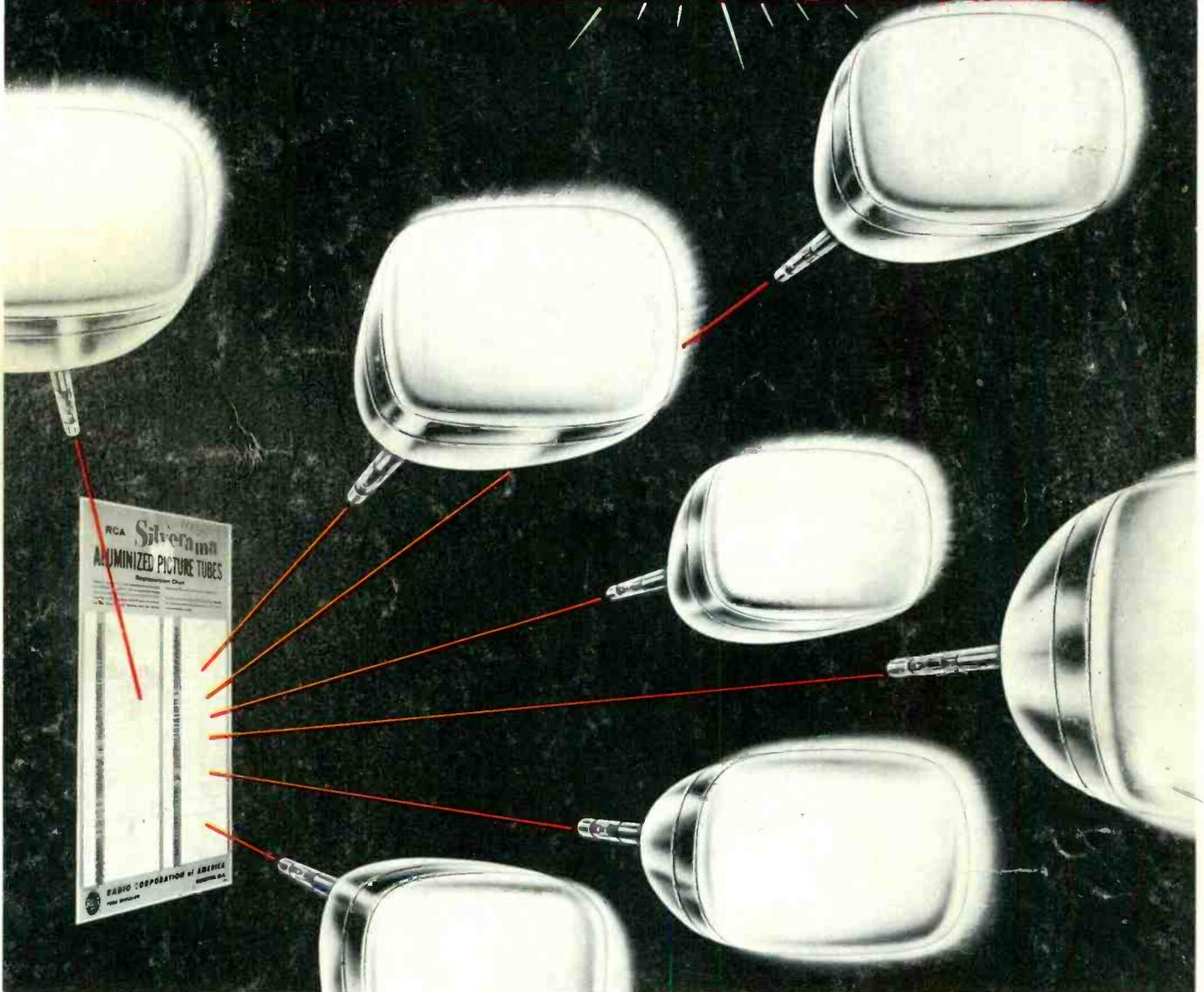
# **RCA** Silverama **SUPER-ALUMINIZED PICTURE TUBES**



**25 types—8 sizes—10" to 27"**

RCA's new Silverama Replacement Chart—yours, for the asking—tells you at a glance what RCA Silverama Picture Tubes to use when making replacements, no matter what model or make set you're servicing. And every Silverama insures a brighter, clearer, sharper picture with greater contrast. Just wait 'til your customers view the new life you've given to their sets with Silverama Aluminized Picture Tubes! See your local RCA Distributor for full details, or write to Commercial Engineering, RCA Tube Division, Harrison, N. J., for form 4F909.

*You profit while you please—with RCA Silverama.*



## **PICTURE TUBES**

RADIO CORPORATION OF AMERICA • HARRISON, N. J.