

How to Build an Audio Ear

January, 1959

IND

# Radio-Electronics

HUGO GERNSBACH, Editor

Signal-Level Comparator for Audio Amplifier Checking

Use Portable Equipment In Color TV Servicing

Simple Super Time Base



**Computers Speed  
Aircraft Design**

See page 4

**35c**  
U.S. and  
Canada

# Jensen's LITTLE \*BEAUTY . . . WITH THE MIGHTY HI-FI VOICE!


NEW "TRI-ette\*" 3-WAY HIGH FIDELITY SPEAKER SYSTEM



Burton Browne Advertising
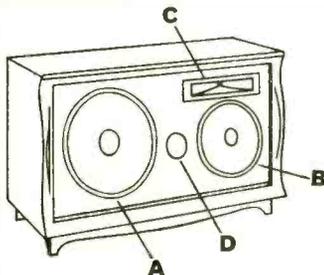
## PERFORMANCE FAR BEYOND COST AND SIZE

If space is a problem, but only true hi-fi sound is for *you* . . . if you want to delight the eye (as well as the ear) . . . if you listen to organ music on occasion, and want the pedal notes to be *there* . . . if you thrill to the full, clean, smooth separated sounds of the orchestra in all their wonderful detail . . . then Jensen's new TR-10 TRI-ette 3-way speaker system is for you! Use one for your compact hi-fi system, a pair for space-saving high quality stereo . . . or add one to your present speaker for stereo conversion. Drives with good 10-watt or larger amplifier. Choice of Walnut, Tawny Ash or Mahogany. Net Price \$114.50. Table Base (illustrated) extra \$5.45. Floor Stand \$12.95. Send for Bulletin JH-1.



## ADVANCE DESIGN 3-WAY SYSTEM COMPONENTS

- A. New 12" Flexair\* high compliance superlow resonance woofer for useful response down to 25 cycles with a new low in distortion for such a small reproducer.
- B. Special 8" mid-channel unit handles the range from 600 to 4,000 cycles, through L-C crossover network.
- C. Compression-driver horn-loaded tweeter carries the response to 15,000 cycles (H-F control for balance adjustment).
- D. Tube-loaded port for amazing bass response in Jensen's new Bass-Superflex\* cabinet.


\*\*13 $\frac{7}{8}$ " H., 25" W., 11 $\frac{3}{8}$ " D (not including base)

\*Trademark Jensen Mfg. Co.

**Jensen**  
DIVISION OF THE MUTER COMPANY

**MANUFACTURING COMPANY**  
6601 S. Laramie Avenue • Chicago 38, Illinois  
In Canada: J. R. Longstaffe Co., Ltd., Toronto  
In Mexico: Radios Y Television, S. A., Mexico, D. F.
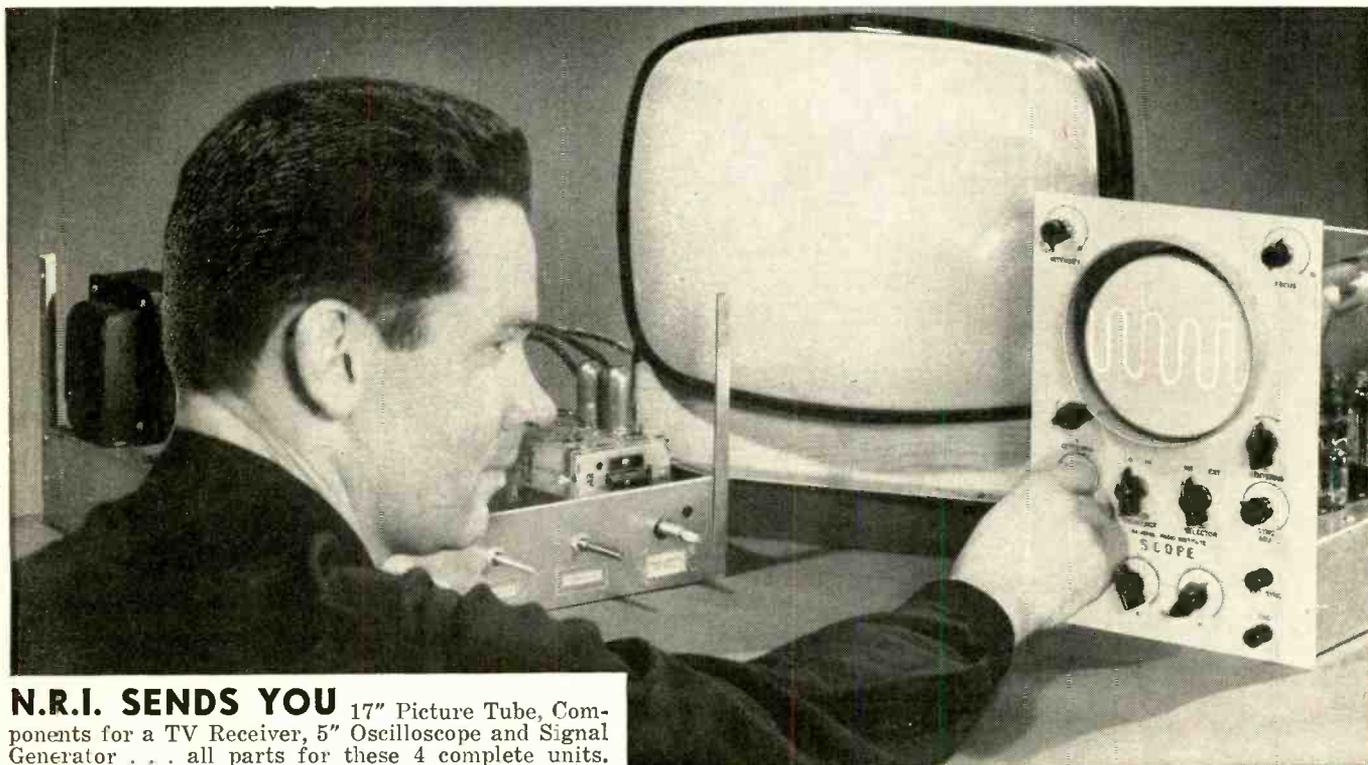
# NOW—A Faster Way to Reach the Top in TV SERVICING



**N.R.I. SENDS YOU** 17" Picture Tube, Components for a TV Receiver, 5" Oscilloscope and Signal Generator . . . all parts for these 4 complete units.

## N. R. I. All-Practice Method Trains You at Home in Spare Time to Fix TV Sets Quickly, with Confidence

The man who knows the answers—the Professional TV Technician enjoys the prestige, gets the better jobs, the higher pay. Here is the learn-by-practice training to be a Professional TV Technician. It shows you the way to be the boss, to earn top pay. Television Servicing needs more well trained men. If you have a basic knowledge of radio and electronics you can make some Television repairs simply by trial and error. But sooner or later you will face TV Service problems you can not solve. And you can't get the training you need while customers wait.

### NRI Is Oldest and Largest Home Study Radio-TV School

Over forty years' experience and the record and reputation of NRI back up this learn-by-doing Professional TV Servicing Course. Instead of just reading about TV problems, you build and conduct experiments on circuits in a TV receiver. You learn methods, "Tricks of the trade" proved by top TV Servicemen. You learn to fix any set, any model with confidence.

### You Get COLOR TV Textbooks Early

The day you enroll, NRI sends you special Color-TV books to speed your knowledge and understanding of this vast, growing phase of Television.

Many full color pictures and diagrams help you recognize defects and help you learn how to correct them quickly and properly. To cash in on the coming Color TV boom, you'll need the kind of knowledge and experience this NRI training gives.

This is 100% learn-by-doing, practical training. Here is a course for men who know basic theory, either from Radio or TV Servicing experience or planned training but realize the need for more knowledge to forge ahead. Here is what one graduate, G. G. Stethem of Belpre, Ohio, says, "I can not praise NRI's Professional TV Course highly enough. I have my own

spare time shop and all the Radio-TV work I can handle."

Another graduate, Edward Ravitsky of Northumberland, Pa., says, "I have taken your course in Professional TV Servicing. It takes the kind of experience you offer to really learn." If you want to go places faster in TV Servicing, make your future more secure as the industry develops, we invite you to find out what you get, what you practice, what you learn from NRI's Course in Professional TV Servicing. Mail the coupon now. There is no obligation. NATIONAL RADIO INSTITUTE, Dept. 9AFT, Washington 16, D. C.



**Send for FREE BOOK** ➔

### NATIONAL RADIO INSTITUTE

Dept. 9AFT, Washington 16, D. C.

Please send FREE copy of "How to Reach the Top in TV Servicing." I understand no salesman will call.

Name.....Age.....

Address.....

City.....Zone.....State.....

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL



JANUARY, 1959

# Radio-Electronics

Formerly RADIO-CRAFT ■ Incorporating SHORT WAVE CRAFT ■ TELEVISION NEWS ■ RADIO & TELEVISION

## EDITORIAL

- 33 Stored Television Reception—Hugo Gernsback

## ELECTRONICS

- 34 Highway Safety . . . Challenge to Electronics—David Lachenbruch
- 37 Computers Speed Aircraft Design (Cover Feature)—Forrest H. Frantz, Sr.
- 39 Electronic Crossword—Wm. R. Shippee
- 40 Improved Solar Flare Indicator—David Warshaw

## AUDIO—HIGH FIDELITY

- 42 Audio Ear in Your Shirt Pocket—Edwin Bohr and Gordon Peters
- 44 How Much Power for a Stadium?—Herman Burstein
- 45 Stabilizing Feedback Amplifiers, Part I—Herbert I. Keroes
- 48 A Box for Your Speaker—P. G. A. H. Voigt
- 51 Stereo Disc Standards
- 51 New Discs and Tapes, Stereo and Mono—Reviewed by Chester Santon

## RADIO

- 53 ABC's of Mobile Radio, Part I—Leo G. Sands
- 57 FM Tuner for Your Car—Henry O. Maxwell

## TEST INSTRUMENTS

- 58 New Kind of Audio Oscillator—Robert F. Scott
- 61 Simple Super Time Base—Tom Jaski
- 76 Audiophile's Signal-Level Comparator—J. E. Pugh, Jr.
- 81 Low-Capacitance Probe—Robert G. Middleton

## WHAT'S NEW?

- 84 Pictorial Reports of New Developments

## TELEVISION

- 85 Portable Test Instruments in Color TV—Robert G. Middleton
- 98 TV Dx in '58—Robert B. Cooper, Jr.
- 106 Television Station List—Compiled by Muriel I. Schiller
- 108 TV Remote Volume Control—Harold Reed
- 110 TV Service Clinic—Conducted by Robert G. Middleton

- 143 Books
- 138 Business and People
- 142 Correction
- 16 Correspondence
- 141 Literature
- 118 New Tubes and Semiconductors
- 6 News Briefs
- 123 Noteworthy Circuits
- 126 On the Market
- 132 Patents
- 114 Technicians' News
- 134 Technotes
- 136 Try This One
- 125 50 Years Ago

## ON THE COVER

(Story on page 37)

Experimental test pilot Robert Rostine "flies" an as-yet-unbuilt aircraft as Greta Beckler changes a connection on a Heathkit analog computer used to simulate an aircraft control, in a cockpit test at Chance Vought Aircraft, Dallas.

Color original by Art Schoeni

- Hugo Gernsback .....Editor and Publisher
- M. Harvey Gernsback .....Editorial Director
- Fred Shunaman .....Managing Editor
- Robert F. Scott .....W2PWG, Technical Editor
- Larry Steckler .....Associate Editor
- David Lachenbruch .....Associate Editor
- I. Queen .....Editorial Associate
- Robert G. Middleton .....Television Consultant
- Elizabeth Stalcup .....Production Manager
- Cathy Coccozza .....Advertising Production
- Wm. Lyon McLaughlin .....Tech. Illustration Director
- Sol Ehrlich .....Art Director
- Fred Neinast .....Staff Artist
- Lee Robinson .....General Manager
- John J. Lamson .....Sales Manager
- G. Aliquo .....Circulation Manager
- Adam J. Smith .....Director, Newsstand Sales
- Robert Fallath .....Promotion Manager



Average Paid Circulation Over 199,000



RADIO-ELECTRONICS is indexed in *Applied Science & Technology Index (Formerly Industrial Arts Index)*

RADIO-ELECTRONICS, January, 1959, Vol. XXX, No. 1. Published monthly at Mt. Morris, Ill., by Gernsback Publications, Inc. Second-Class mail privileges authorized at Mt. Morris, Ill. Copyright 1959 by Gernsback Publications, Inc. All rights reserved under Universal, International and Pan-American Copyright Conventions. SUBSCRIPTION RATES: U.S., U.S. possessions and Canada, \$4.00 for one year; \$7.00 for two years; \$10.00 for three years; single copies 35c, Pan-American countries \$5.00 for one year; \$9.00 for two years; \$13.00 for three years. All other countries \$5.50 a year; \$10.00 for two years; \$14.50 for three years. SUBSCRIPTIONS: Address correspondence to Radio-Electronics, Subscription Dept., 154 West 14th St., New York 11, N.Y. When requesting a change of address, please furnish an address label from a recent issue. Allow one month for change of address. GERNSBACK PUBLICATIONS, INC., Executive, Editorial and Advertising Offices, 154 West 14th St., New York 11, N.Y. Telephone ALgonquin 5-7755. Hugo Gernsback, Chairman of the Board; M. Harvey Gernsback, President; G. Aliquo, Secretary. BRANCH ADVERTISING OFFICES and FOREIGN AGENTS listed on page 149. POSTMASTER: If undeliverable, send Form 3579 to: RADIO-ELECTRONICS, 154 West 14th St., New York 11, N.Y.

\*Trademark registered U. S. Pat. Office.

RADIO-ELECTRONICS


**GREATEST  
ADVANCE IN  
SHOP-METHOD  
HOME TRAINING**

# EARN MORE MONEY... GET INTO TELEVISION ELECTRONICS - RADIO

**Learn ALL 8 PHASES in ONE MODERN HOME-STUDY COURSE**  
At Home - In Spare Time
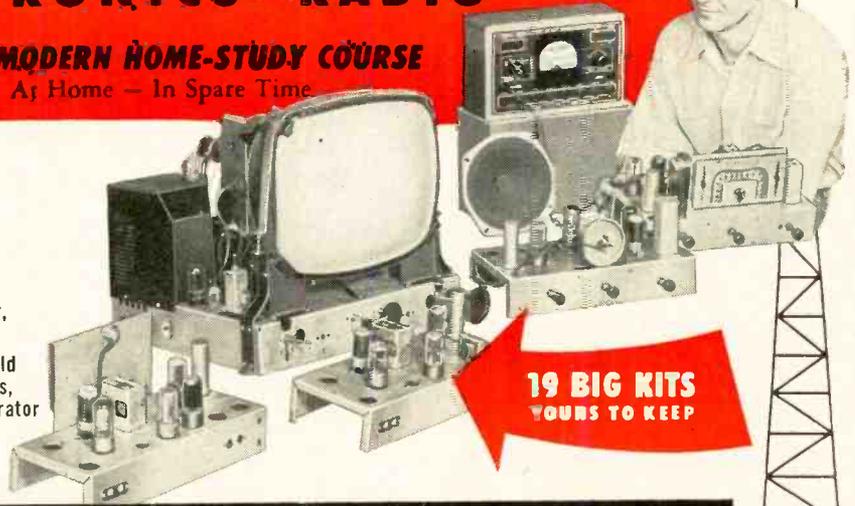
## YOU GET ALL THIS NEWEST PRACTICAL EQUIPMENT

- Parts to build a modern TV set, including all tubes plus a large screen Picture Tube
- Parts to build a powerful Superhet Receiver, standard broadcast and short wave
- Parts to conduct many experiments and build Continuity Checker, RF Oscillator, TV Circuits, Audio Oscillator, TRF Receiver, Signal Generator
- A Valuable Professional Multitester



**19 BIG KITS  
YOUNGS TO KEEP**

## YOUR NATIONAL SCHOOLS TELERAMA COURSE COVERS ALL 8 PHASES

- |                                    |                                |
|------------------------------------|--------------------------------|
| 1. TELEVISION, INCLUDING COLOR TV  | 5. PREPARATION FOR FCC LICENSE |
| 2. RADIO, FM AND AM                | 6. AUTOMATION                  |
| 3. INDUSTRIAL ELECTRONICS          | 7. RADAR AND MICRO WAVES       |
| 4. SOUND RECORDING AND HI FIDELITY | 8. COMMUNICATIONS              |

**YOU ARE NEEDED IN THE TELEVISION-ELECTRONICS-RADIO INDUSTRY!**  
You can build a secure future for yourself if you get into Electronics NOW! Today's shortage of trained technicians creates tremendous opportunities. National Schools Shop-Method trained technicians are in constant and growing demand for high-pay jobs in Broadcasting and Communications, Electronic Research, Servicing and Repair, and many other branches.

Let National Schools, a Resident Technical School for over 50 years train you for today's unlimited opportunities in electronics! Our Shop Method trains you to be a MASTER-TECHNICIAN. Completely up to date, developed by experienced instructors and engineers, your Telerama Course will teach you all phases of the industry quickly, clearly and correctly. You can master the most modern projects, such as Color TV, printed circuits - even prepare for FCC License without taking a special

course. You can handle sales, servicing, manufacturing, or make good money in your own business. SEND FOR FACTS TODAY!

**EARN AS YOU LEARN.** Many of our students earn their entire tuition and more in Spare Time jobs we show them how to do while learning.

**YOU GET EVERYTHING YOU NEED** - Clear, profusely illustrated lessons, shop-tested manuals, modern circuit diagrams, practical job projects - all the valuable equipment shown above

- many other materials and services  
- consultation privilege with our qualified staff, and Graduate Employment Service. EVERYTHING YOU NEED for outstanding success in Electronics

### RESIDENT TRAINING AT LOS ANGELES

If you wish to take your training in our Resident School at Los Angeles, the world's TV capital, start NOW in our big, modern Shops, Labs and Radio-TV Studios. Here you work with latest Electronic equipment - professionally installed - finest, most complete facilities offered by any school. Expert, friendly instructors. Personal attention. Graduate Employment Service. Help in finding home near school - and part time job while you learn. Check box in coupon for full information.



**FREE!** Fully illustrated "Career" Book in TV-Radio-Electronics. PLUS actual sample lesson - yours at no cost, no obligation. CLIP COUPON NOW... MAIL IT TODAY!

APPROVED FOR G. I. TRAINING

# NATIONAL SCHOOLS

4000 S. FIGUEROA ST., LOS ANGELES 37, CALIF.



MEMBER



## NATIONAL SCHOOLS

TECHNICAL TRADE TRAINING SINCE 1905  
LOS ANGELES 37, CALIFORNIA

GET FAST SERVICE - MAIL NOW TO

NATIONAL SCHOOLS, DEPT. RG-19

4000 S. FIGUEROA ST.  
LOS ANGELES 37, CALIF.

Rush free TV-Radio "Opportunity" Book and sample lesson. No salesman will call.


NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

Check if interested ONLY in Resident School training at Los Angeles.  
VETERANS: Give date of Discharge \_\_\_\_\_

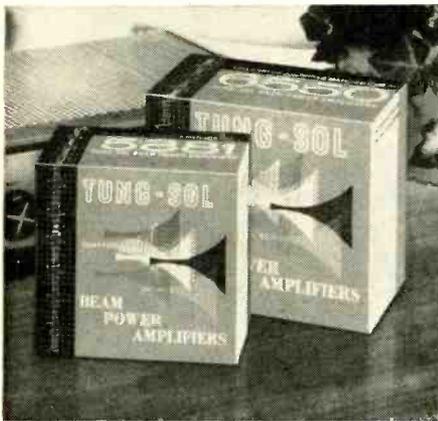**Tung-Sol audio tubes**  
**now twin-packed**  
**in matched pairs**  
**by the manufacturer**



**5881** For service in amplifiers of up to 50 watts.



**6550** For service in amplifiers and commercial audio equipment of up to 100 watts.

**N**ow you can come as close to faultless sound reproduction as the design and circuitry of your hi-fi equipment will permit. Tung-Sol 5881 and 6550 beam-power amplifier tubes are factory-matched to very tight performance limits and twin-packed to help you achieve lowest distortion levels at all volume levels.

Use of Tung-Sol 5881 and 6550 tubes has long been associated with amplifiers of the very finest design. These tubes have always been produced to closest possible tolerances with cathode current ranges held to an absolute minimum.

Now, in twin-packed pairs, they assure the hi-fi enthusiast and the commercial sound engineer of replacement tubes that will provide new standards of performance—a feature of special importance with the newest amplifiers and loudspeakers, particularly binaural sound equipment. See your parts supplier.

Tung-Sol Electric Inc., Newark 4, New Jersey.



**STEREO RADIO STANDARDS** will be proposed by an all-industry group similar to the one which selected the current systems of black-and-white and color television.

A National Stereo Radio Standards Committee, to test all stereo broadcasting systems and make recommendations to the FCC, is being established by the Electronic Industries Association (EIA). Heading the NSRSC's administrative committee will be Dr. W. R. G. Baker, who was chairman of the pioneering National Television System Committee (NTSC). Dr. Baker, former president of EIA and vice president of General Electric, now is EIA engineering director and head of the Syracuse University Research Corp.

The entire electronic industry will be invited to serve on NSRSC. Its goal will be the formulation of standards for a single stereo broadcasting system which is both compatible and inexpensive to the public.

FCC officials indicated they welcome the formation of the industry committee. The commission is now studying the various stereo radio systems, and no decision on standards is expected for a considerable time—probably not for a year or more.

More stereo radio systems undoubtedly will be proposed, but these are the compatible ones which already have been developed and demonstrated:

1. The Crosby sum-and-difference FM system. The main channel carries the sum of the two signals, the multiplexed subcarrier the difference. A converter matrixes these channels into the proper left and right signals.

2. A system somewhat similar to the Crosby proposal, but which permits the use of a second multiplexed channel for a "second program" of specialized music or information beamed to stores and offices while the stereocasting is carried by the first two channels.

3. The RCA compatible AM stereo system, demonstrated recently at RCA Laboratories in Princeton, N. J. Each of the stereo channels is carried by one sideband of the AM carrier. The stereo receiver uses a conventional rf amplifier, converter and if amplifier. Sideband selectors then pick up the upper and lower sidebands separately, detect the signal and amplify it to be fed into the left and right speakers.

4. The Percival system, developed by EMI Ltd. of England and tested by the British Broadcasting Corp. Adaptable to either FM or AM, it transmits a conventional broad-band signal (monophonic) plus a narrow band of direc-

tional information for use by stereo receivers.

**TRANSATLANTIC HI FI** is in sight—in fact, it was approached in the recent United Nations Day international concert featuring orchestras in Geneva, Paris and New York, marking the first use of the new transoceanic cable to carry music.

As a result of more than 6 months of painstaking tests directed by UN Radio operations manager Joe Nichols, East Coast FM listeners were able to hear the Paris concert with a frequency response up to 6,500 cycles, and British listeners received the New York concert with the same fidelity. Conventional network transmission lines in the US often do not pass frequencies higher than 4,000 cycles, and rarely more than 5,000.

The feat was accomplished after many frequency runs conducted experimentally by dividing various bands of frequencies among different lines within the cable. In this country, the program was carried in its full fidelity by the New York and New England FM Concert Network, the New York State WQXR Network (FM) and by FM stations in Philadelphia and Washington.

**AMERICANS VIEWED** a Eurovision telecast for the first time Nov. 4 when Videotape extended the 12-nation European TV network to the US for televising the coronation of Pope John XXIII from the Vatican.

The taping was done in the studios of Granada Television in Manchester, England, with an Ampex Videotape recorder on the 525-line US television standards—but the signal underwent considerable metamorphosis between the camera pickup and the recording.

The TV pickup at the Vatican was made with cameras of Radiotelevisione Italiana (RAI), the Italian broadcasting company, using the European 625-line standard. Fed through 23 microwave hops, the 625-line picture was received from France at Dover, England, across the Channel, where it was converted to the 405-line British standards. The conversion device uses an image orthicon camera to take a 405-line picture directly from a 625-line monitor.


The 405-line picture was microwaved to Manchester, where it was converted—again by optical means—to the 525-line standard used by American TV stations. Then it was fed into the Videotape recorder and a running commentary interpolated.

The 55-minute tape was put aboard an airliner for New York and rushed  
*(Continued on page 10)*

For A Real OPPORTUNITY, Look Into
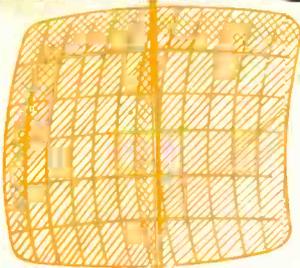
# ELECTRONICS

**DeVry** Tech can prepare you for a profitable future in many branches of Electronics from



**RADAR to GUIDED MISSILES, etc.**  
*No Previous Technical Experience Required!*



Now that Electronics is so important in our daily lives...now that industry is moving so rapidly into Automation and Industrial Electronics, good job opportunities for the trained man never appeared brighter than they do today.

To prepare to enter the field of Electronics, one of the modern

marvels of the 20th Century, you need no advanced education. Believe it or not, you don't need previous technical experience either.

Men 17 to 55, send coupon below for FREE facts! Learn how you may get ready to enter this fascinating, profitable field in your spare time at home or in day or evening classes in our well-equipped Chicago or Toronto laboratories.

**CAN YOU DO IT?**

Labarers, clerks, farmers, salesmen, men of nearly every calling have taken the DeVry Tech program and today have better jobs or Electronic service shops of their own — REAL PROOF of the effective training offered by DeVry Tech.



**FREE EMPLOYMENT SERVICE**

DeVry Tech's effective employment service is available to all graduates at no additional cost.



**Send for FREE BOOKLET!**

"Electronics and YOU" shows how you may take advantage of the opportunities in this fast-growing field.

Check These Opportunities In Electronics:

**INDUSTRIAL ELECTRONICS**



**COMMUNICATIONS**



**AUTOMATION ELECTRONICS**



**COMPUTERS**



**TELEVISION**



**YOUR OWN SERVICE SHOP**



## DeVry TECHNICAL INSTITUTE

CHICAGO 41, ILL.


Formerly DeFOREST'S TRAINING, INC.

Accredited Member of National Home Study Council

"One of North America's

Foremost Electronics

Training Centers"

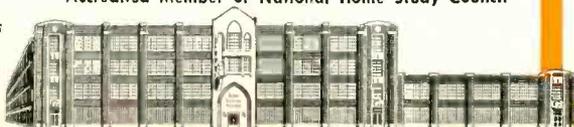

**MAIL TODAY FOR FREE FACTS**

DeVry Technical Institute  
 4141 Belmont Ave., Chicago 41, Ill., Dept. RE-1-P  
 Please give me your FREE booklet, "Electronics and YOU," and tell me how I may prepare to enter one or more branches of Electronics as listed above.

Name \_\_\_\_\_ Age \_\_\_\_\_

PLEASE PRINT

Street \_\_\_\_\_ Apt. \_\_\_\_\_


City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Check here if subject to Military Training.

DeVry Tech's Canadian Training Center is located at  
 2043 626 Roselawn Avenue, Toronto 12, Ontario
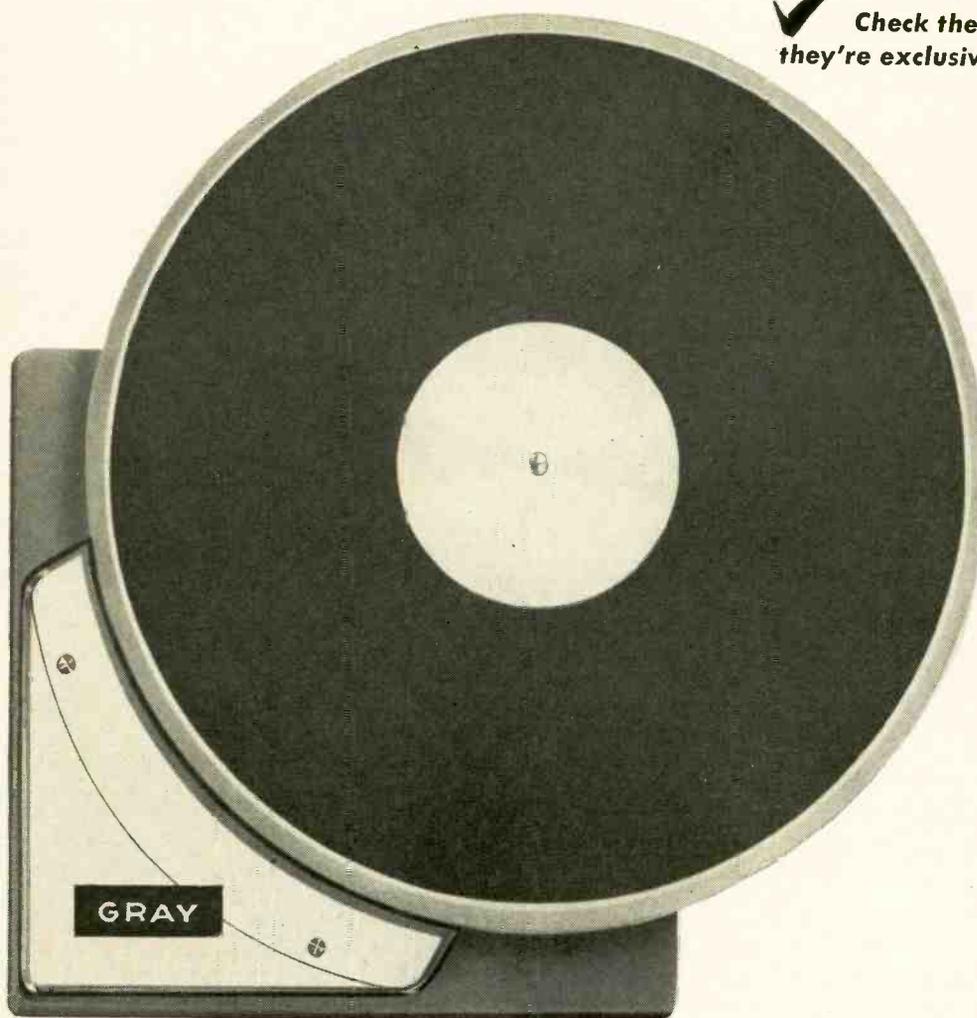
# A HYSTERISIS SYNCHRONOUS TURNTABLE KIT FOR 49<sup>50</sup>

✓ Check these outstanding features,  
they're exclusive with Gray at this LOW price




- Special hysteresis synchronous motor provides constant speed and lowest wow, flutter and rumble content.
- Heavy machine ground 12½" turntable platter with micro polished 7/8" shaft rotates in a super oilite bearing with noiseless nylon underfacing thereby guaranteeing freedom from vertical movement...a stereo prerequisite.
- Customized slip-proof, stretch-limited composite belt offers vibrationless link between motor and platter edge.
- Shock-proof motor mount is adjustable in 3 planes to compensate for lifetime movement and wear.
- Sturdy mounting plate offers maximum shielding. Easy to level and center because it extends past the platter and motor structure.
- Micro precision parts pretested for accuracy in sub assemblies.
- Assembly time 25 minutes or less with simple tools.

## GRAY 33½ RPM SINGLE SPEED HSK-33 TURNTABLE KIT

Here's an exciting project for anybody who wants professional performance at a low kit cost. Gray engineering and custom mass production techniques now make this wonderful value possible. You'll be pleasantly surprised at how easy it is to fully assemble—and have ready for monaural or stereo operation—this studio designed turntable.

*Also available at low cost . . . turntable bases in finished and kit form.*

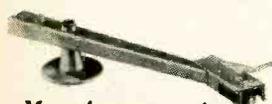*See and hear Gray high fidelity products at your favorite quality dealer.*



Manufacturers of  
the world famous  
Gray tone arm.

**GRAY** our 67th year in communications . . .  
**High Fidelity Division**

DEPT. H • 16 ARBOR STREET, HARTFORD 1, CONN.

RADIO-ELECTRONICS

# Every Essential Term in Physics and Electronics – 12,000 of Them – now in one giant dictionary!

Send today for a free-examination copy of this 1000-page reference work. Used in homes, offices, schools and laboratories.

THE INTERNATIONAL DICTIONARY OF PHYSICS AND ELECTRONICS is the only book available today that gives you – right at your fingertips – definitions, equations, principles and thorough explanations of every important term in physics and electronics.

More than 12,000 laws, relationships, equations, basic principles, instruments, apparatus and techniques are described in half a million words. You'll find everything from alphanopic, band and cybotaxis to Wronksian, ylem and Zwitterion.

#### 16 Reference Books in One

You've never seen so much useful information in one volume. It takes the place of a whole library of reference books on:

- |             |                            |
|-------------|----------------------------|
| Electronics | Units and Dimensions       |
| Meteorology | General Principles         |
| Mechanics   | Heat and Thermodynamics    |
| Gases       | Atomic and Nuclear Physics |
| Liquids     | Mathematical Physics       |
| Solids      | Quantum Mechanics          |
| Acoustics   | Electricity                |
| Optics      | Relativity                 |

No more hunting around from book to book for the information you need. No more wading through long texts to get a simple definition. Everything you need can be found simply and quickly in this one handy volume.

#### Answers Your Questions in Seconds

A unique system of cross-referencing helps you locate information instantly. Each article is arranged progressively, beginning with a concise definition and adding additional details in later paragraphs. Boldface "word signals" refer you to other articles relating to the one you are reading. You get the answers you want in a hurry!

#### Save Time – Avoid Costly Errors

You'll turn to this giant, 1000-page reference work dozens of times a day – to recheck your work, to clarify technical articles or engineering data, to increase your own understanding of the complex world of physics and electronics. Where you might otherwise trust your memory, you'll now turn to the International Dictionary of Physics and Electronics to get an answer you can be sure of. This helpful volume can pay for itself many times over in just one avoided error!

#### Examine it For 10 Days FREE

To fully appreciate the usefulness of this big 2¼" thick book, we invite you to use it for ten days. If you do not find it to be one of the most valuable books you have ever owned, you may simply return it and owe nothing. Otherwise, remit payment on the easy terms indicated in coupon. You take no risk. Send coupon today to **D. Van Nostrand Co., Inc., Dept 181, 120 Alexander St., Princeton, N. J. (Established 1848).**

#### Acclaimed by Major Journals in Every Field of Science

"Unique. Useful. Presents a wide variety of terms"

– SCIENTIFIC AMERICAN

"Remarkably complete. Highly useful. Provides definite and concise answers to a myriad of questions."

– PHYSICS TODAY

"Will undoubtedly make a

well-deserved place for itself." – SCIENCE

"There has been a real need for such a work."

– ELECTRONICS

"Recommended for all that do any reference work in physics."


– LIBRARY JOURNAL

"Unique in its field and exceptionally clear in its typography. It should prove a most useful reference."

– NUCLEONICS

"The best book of definitions available on the market today. Highly recommended."

– TELE-TECH

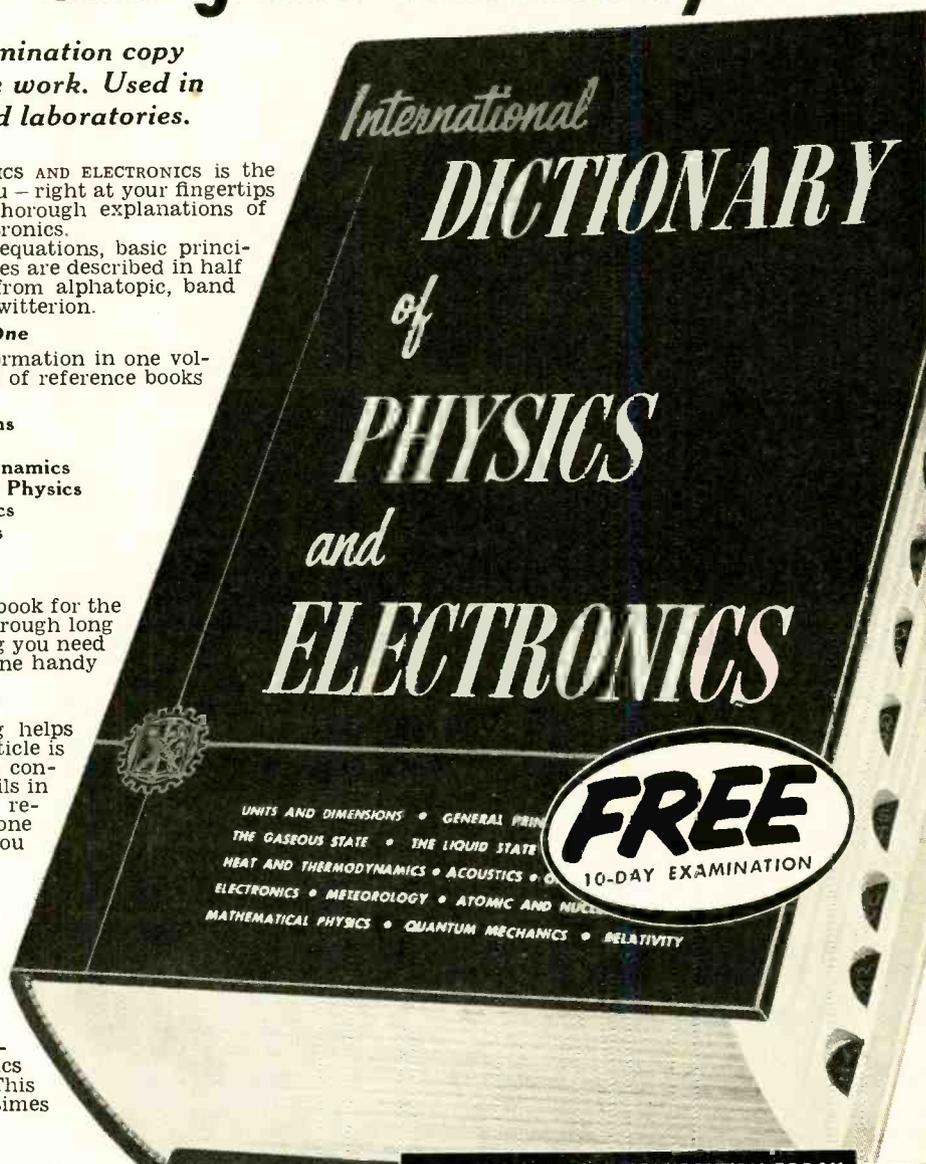

#### MAIL FREE-EXAMINATION COUPON TODAY

**D. Van Nostrand Company, Inc., Dept. 181  
120 Alexander Street, Princeton, N. J.**

Please send me – for 10 days' FREE examination – the "International Dictionary of Physics and Electronics" thumb-indexed edition. If not completely satisfied, I may return it and owe nothing. Otherwise I will remit \$7.50 plus small shipping cost, and \$5 a month for 3 months.

Name.....

Address.....

City..... Zone..... State.....

Save! Enclose full payment (\$22.50) and shipping costs will be prepaid. Money back if not delighted.

In Canada: Order from D. Van Nostrand Co., Ltd., 25 Hollinger Road, Toronto 16, Canada (Price slightly higher)

to the Columbia Broadcasting System studios for a nationwide telecast. The quality of the picture was surprisingly good.

The 525-line Videotape recorder in Manchester, England, was purchased by Granada TV for showing taped American TV programs. An electronic system to convert 525-line TV pictures to 405 lines is being developed by Granada.

**SELF-THREADING CARTRIDGE** is being tested by tape recorder manufacturers and may be on the market in 1959. The new single-reel tape magazine differs in many respects from the two-reel tape cartridges now in use.

Developed by Armour Research Foundation of the University of Illinois, the cartridge consists of a single flanged reel of tape and a graded leader tape with a catch on it. The catch engages with a pre-threaded leader which is a part of the recorder mechanism. When forward recording is completed, an end leader automatically reverses the drive for rewind or operation in the reverse direction.

The self-threading device can be installed on conventional tape recorders, or the tape cartridge can be used on nonequipped recorders by removing the leader tape.

**TWO HAM RECORDS** for long-distance transmission using all-transistor equipment were made during last September by West Coast amateurs. Donald L. Stoner, W6TNS, Ontario, Calif., established contact with ZS6KD, Johannesburg, South Africa, over a 16,000-mile transmission path, on the 20-meter phone band using single-sideband equipment.

ZS6KD described the signals as weak but 100% readable. Stoner's rig operates from a 15-volt battery, supplying 90-mw power input to the final amplifier. The circuit consists of a 2N371 crystal-controlled oscillator which drives a 2N370 as a class-C rf amplifier.

Major Gilbert, K6LMW, an engineer at Hoffman Laboratories, Los Angeles, conversed with two other hams 2,000 miles away, using a transmitter and receiver powered entirely by a bank of silicon solar cells. His "loud and clear" voice signal was received by Henry A. Kusek, W9KZX, Chicago, and W. Leonard Gregory, Jr., W9RLY, Mt. Prospect, Ill., on the 10-meter band. He used 72 solar cells, providing a transmitter power output of 60-75 mw.

**ULTRASONICS** will soon be helping farmers decide which of their livestock to send to market and will be providing housewives with more uniform, leaner meat. In both the US and Britain, ultrasonic devices designed to measure the depth of flaws or impurities in metals are being used experimentally to measure the thickness of the fat and lean on meat-producing animals.

The meat testers emit ultrasonic waves and measure the time required for them to pass through an animal's

# How to Pass

## An FCC License can be

## Get Your FCC License

**We Guarantee**  
to train you until you receive  
**Your FCC License**

Completion of the Master Course (both Sections) will prepare you for a First Class Commercial FCC License with a radar endorsement. Completion of Section I only of the Master Course will prepare you for a Second Class Commercial FCC License. We guarantee to train and coach you, without any additional cost, until you receive the FCC License as indicated above. This guarantee is valid for the entire period of your enrollment agreement.

**Cleveland Institute Training Results in success with commercial FCC examinations . . . easily . . . and quickly.**

**every month our trainees get jobs like these:**



**Boyd Daugherty:**

"I recently secured a position as Test Engineer with Melpar, Inc. A substantial salary increase was involved. My Cleveland Institute training played a major role in qualifying me for this position."

*Boyd Daugherty  
105 Goodwin Ct., Apt. C  
Falls Church, Va.*

### Top Grade Employers Like These Look

**Bendix Radio:**

"We shall look forward to receiving completed applications from your students."

**Philco:**

"We have employed a great number of well qualified electronics personnel who were graduates of Cleveland Institute."

**Westinghouse:**

"We would appreciate your listing our current openings in your monthly Job Opportunities."

(Commercial)

# FCC License Exams

## your Guarantee of Success in Electronics

## in a Minimum of Time

mail  
coupon  
**NOW!**

### here's proof of good jobs

**Irving Laing:**

"Your lessons are helping me a lot in my Navy work. You cover topics that were not presented by the Navy at the E.T. School. . . . Your course has helped greatly to get my 2nd class FCC ticket. I am now a radio and T.V. engineer at WTVS and WDTR in Detroit, Michigan."

*Irving L. Laing,  
15887 Robson,  
Detroit 27, Michigan*


**James Glen:**

When Jim enrolled, he was a temporary employee of the City of Tacoma, Washington. In the space of 14 months, he completed the Master Course and received his first class license. He is now installing and maintaining mobile and microwave equipment.

*James S. Glen, Jr.  
2920 Knob Hill Road  
Tacoma, Washington*




## Get all 3 FREE

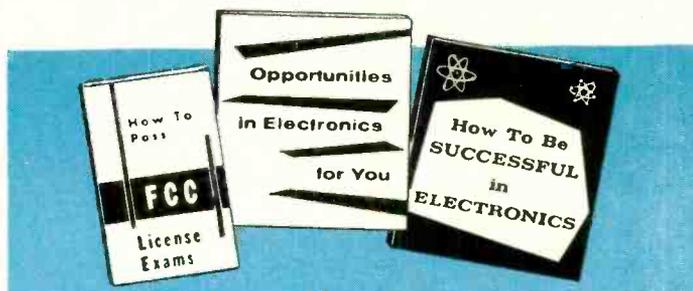

Accredited by The National Home Study Council

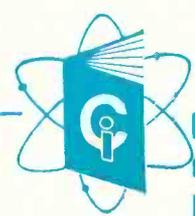**Cleveland Institute of Radio Electronics**

Desk RE-25, 4900 Euclid Ave., Cleveland 3, Ohio



Please send FREE Booklets prepared to help me get ahead in Electronics. I have had training or experience in Electronics as indicated below:

- |   |   |
|---|---|
| <input type="checkbox"/> Military           | <input type="checkbox"/> Broadcasting       |
| <input type="checkbox"/> Radio-TV Servicing | <input type="checkbox"/> Home Experimenting |
| <input type="checkbox"/> Manufacturing      | <input type="checkbox"/> Telephone Company  |
| <input type="checkbox"/> Amateur Radio      | <input type="checkbox"/> Other.....         |

In what kind of work are you now engaged?.....

In what branch of Electronics are you interested?.....

Name..... Age.....

Address.....

City..... Zone..... State.....

Special Tuition Rates to Members of Armed Forces RE-25

### To Cleveland Institute

Aerojet-General  
American Airlines  
American Telephone &  
Telegraph Co.  
Bendix Radio  
Braniff Airways  
Burroughs Corp.  
Capital Airlines  
Continental  
Air Lines, Inc.  
Convair  
General Electric  
Glenn L. Martin Co.

Goodyear Atomic Corp.  
IBM  
International Telephone  
& Telegraph Co.  
Mohawk Airlines  
Motorola  
North American  
Aviation, Inc.  
Northwest Airlines  
Philco  
RCA  
Ryan Aeronautical Co.  
\*Plus many others

**Announcing . . . A BRAND-NEW Home Study Program**  
 — Equips you to enter the exciting, new and booming field of

**A U T O M A T I O N**

**and Industrial  
 ELECTRONICS  
 Engineering Technology**

Automation: "Second industrial revolution" . . . latest and most exciting development in our amazing world of electronics. Current needs: 3,000 specialists per year, well-trained in automation and industrial electronics . . . to fill new jobs and draw top pay.

CREI's new complete home study course covers all phases of automation and industrial electronics, including fundamentals of electronic engineering technology and a specialization in: Machine control systems . . . Data processing systems . . . Instrumentation techniques . . . Digital and Analogue Computers . . . Servomechanism systems . . . Telemetry systems . . . Industrial processes.

Leads to jobs like these:

**NOW A TELEMETRY TECHNICIAN AT RCA MISSILE TEST PROJECT** . . . "On December 31 I will be working for RCA at the Missile Test Project in Florida as a Telemetry Technician. I don't mind telling you that CREI

and your encouragement helped a lot in getting this job."—John S. Trefl, Box 133, Beulah, Mississippi

**NOW ASSISTANT CHIEF ENGINEER OF RADAR INSTRUMENTATION STATION** . . .

"Five years ago I started to work for my present employer as a Radio Repairer and Installer. I also started my CREI course at this time. Three years later I was a supervisory electronic engineer and a year later I was promoted to the position I now hold as assistant chief engineer of a large radar instrumentation station at White Sands Proving Grounds."—Ralph Leo Gagnon, 1255 Gardner Ave., Las Cruces, N. M.

If you have had a high school education, and experience in electronics—and realize the need of high-level technical knowledge to make good in the better electronic jobs — you can qualify for this brand-new CREI Home Study course. Write to Capitol Radio Engineering Institute, Dept. 141X, 3224-16th St., N.W., Wash. 10, D. C.

NEWS BRIEFS (Continued)

outer hide and bounce back from the borders between fat and lean meat and bone. The time differences are read on a cathode-ray indicator and translated to inches of fat and lean. A US Agriculture Department official predicts that within 2 years a simplified ultrasonic meat meter will be available to farmers and ranchers for pretesting the meat on cattle and pigs.

**BATTERY-OPERATED** FM receivers will be possible very soon using a new series of drift transistors, RCA's Semiconductor and Materials Div. has announced. The transistor types, now ready for pilot production, are designed for use as rf amplifier, mixer, oscillator and if amplifier.

**Calendar of Events**

- Hi-Fi Music Show**, Jan. 9-11, Dyckman Hotel, Minneapolis, Minn.
- Symposium on Reliability and Quality Control**, Jan. 12-14, Bellevue Stratford Hotel, Philadelphia, Pa.
- Minneapolis Hi-Fi Music Show**, Jan. 16-18, Hotel Leamington.
- Indianapolis Hi-Fi Music Show**, Jan. 30-Feb. 1, Hotel Antlers.
- San Francisco High Fidelity Show**, Feb. 7-10, Cow Palace.
- Solid State Circuits Conference**, Feb. 12-13, University of Pennsylvania, Philadelphia, Pa.
- Los Angeles High Fidelity Show**, Feb. 18-22, Biltmore Hotel. RADIO-ELECTRONICS will exhibit.

**MAIL THIS COUPON FOR FREE BOOKLET!**

**CAPITOL RADIO ENGINEERING INSTITUTE**

ECPD Accredited Technical Institute Curricula • Founded 1927  
 Dept. 141X, 3224 - 16th Street, N.W., Washington 10, D. C.

Please send me without cost or obligation your brochure describing your brand-new home study course in Automation and Industrial Electronics Engineering Technology.


Name..... Age.....  
 Street.....  
 City..... Zone..... State.....

To obtain fast, immediate service and to avoid delay, it is necessary that the following information be filled in:

Employed By.....  
 Type of Present Work.....  
 Education:  
 Yrs. High School.....  
 Other.....  
 Electronics Experience.....

IF . . . you are interested in other CREI courses in Electronics please refer to CREI's 2-page ad on pages 101 and 102 of this magazine.

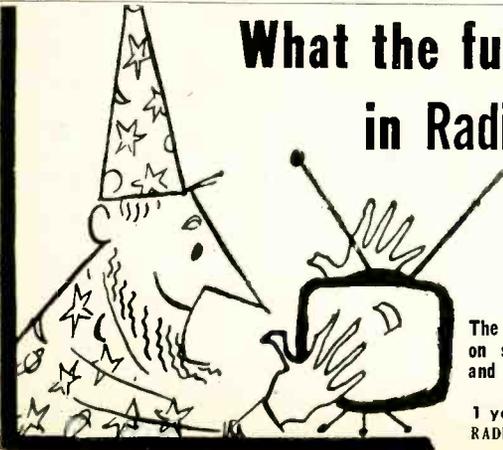**What the future holds for you  
 in Radio-Electronics**



- Single-Sideband Transmission
- Servicing Chroma Demodulators
- Stereo Control Box
- Electronic Control of Motor Vehicles
- Church Chime Projection Systems
- Compatible FM Multiplex

The FEBRUARY issue of RADIO-ELECTRONICS goes on sale January 29 at all better parts distributors and newsstands.

**SUBSCRIPTION RATES**  
 1 year \$4.00 2 years \$7.00 3 years \$10.00  
 RADIO-ELECTRONICS, 154 West 14th Street, New York 11, N. Y.


**RADIOACTIVE CLOUDS** have been spotted and tracked by radar. The Army Signal Corps, using advanced weather radar equipment, was able to measure the size and plot the course of "hot" clouds which formed after a nuclear test. The Army said such information on the height and drift of nuclear clouds would be valuable for providing fallout warning to civilians and troops.

**LONGEST SINGLE-HOP** tropospheric scatter system ever developed has been installed by General Electric between Boston, Mass., and Winston-Salem, N. C. It spans a 640-mile distance and is the prototype of a system to be used by the Air Force as the main communication line between advanced Arctic bases.

Two 50-kw single-sideband transmitters at each site feed into two antennas with 120-foot parabolic reflectors, transmitting 1,000,000,000 watts of effective radiated power. The two-way system has 24 voice and teletype channels and is expected to be "99.9% reliable."

**MAGAZINE THAT TALKS** and plays music is on the newsstands in Paris. *Sonorama*, a news and entertainment publication, contains six thin plastic "sound pages" which alternate with printed pages. A center hole through the entire magazine permits readers (or listeners) to play the sound pages on their phonographs and hear latest song hits, excerpts from theatrical productions, on-the-spot recordings of current events and voices of leading personalities. END



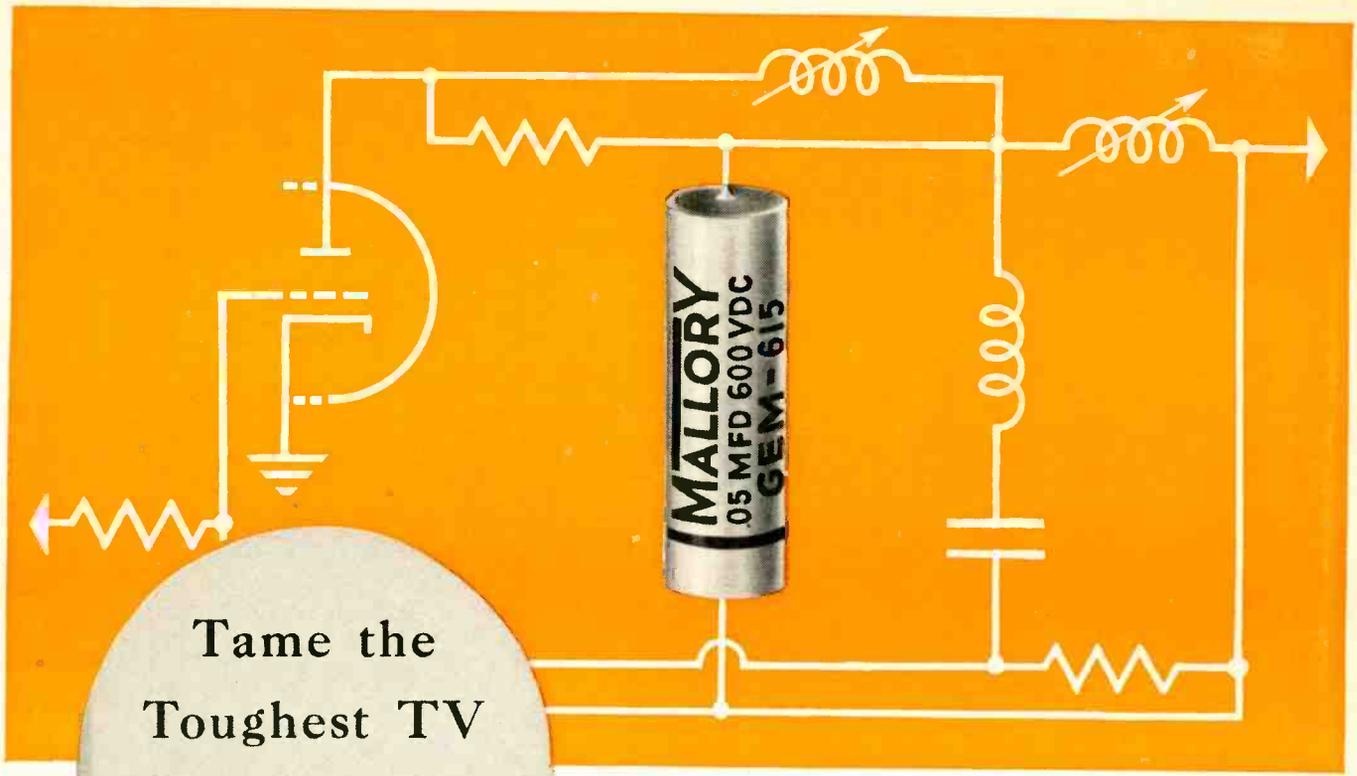

Tame the  
Toughest TV  
Replacement  
Spot with a . . . . .


# Mallory Gem Capacitor

This circuit should be familiar—half of a 6SN7 serving as the horizontal oscillator in a typical TV receiver circuit. The marked spot in the diagram is a tough assignment for a capacitor. If it opens, you lose raster. If it changes capacity, or if the replacement is beyond tolerances, the horizontal sweep will not sync in.

When replacing this capacitor, always use a Mallory Gem. It's moisture-proof—won't drift in capacity or internal resistance. Conservative voltage ratings guarantee reliability—in this, or any circuit. Get Gems today from your Mallory Distributor in the handy 5-pack.



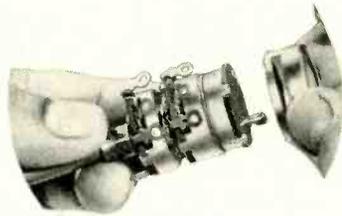
**FP Capacitors**—the original 85°C filter



**Sta-Loc Dual Controls**—tailor-made in 30 seconds



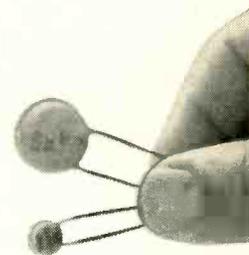**Gold Label Vibrators**—unequalled performance and life



**RMC Discaps**—world's leading ceramic capacitors

**Depend on Mallory components for service**

P. R. MALLORY & CO. Inc.  
**MALLORY**  
 P. R. MALLORY & CO. Inc., INDIANAPOLIS 6, INDIANA

# BIG REWARDS

for the most-wanted men in Radio-TV-Electronics



General Electronics Technician

Radio-TV Engineer

Radio-TV Service Manager

Industrial Electronics Technician

Electrical Engineering Technician

Electrical Draftsman

That's right! There *are* big rewards for the most-wanted men in Radio-TV-Electronics.

You can be one of these men. With the right training you can qualify for a big-pay job in a vital industry. You can start yourself on an exciting, rewarding career in a field that offers unlimited opportunities.

But you must be thoroughly trained. You must know more than wires and tubes. You must *think* in electronic terms.

There's no short-cut to success in Radio-TV-Electronics. But there is a simple, sure way . . . the I.C.S. way.

I.C.S. is the world's oldest and largest technical training school. Sixty-seven years of experience in training 6½ million students have made the I.C.S. system a success-proven method

of home study. Today, there are more trained men from I.C.S. in supervisory and management jobs than from any other school.

Up-to-the-minute I.C.S. Courses make electronic fundamentals clear, easy-to-follow. *Personalized* guidance helps you through each step.

You study at home — in your spare time — at your own pace. Everything you learn is practical, usable. Courses are prepared by experts who know what *you* need to know to go places.

Join the ranks of the most-wanted men in Radio-TV-Electronics. Your first step is to send for your free I.C.S. Career Kit. You have nothing to lose. You can gain an exciting career in the fastest-growing industry of all time.

## HOW WILL YOUR I.C.S. SUCCESS STORY SOUND ?

"I took my diploma from your school in Radio Operating in 1947. In 3 years I became chief engineer of WKOK in Sunbury, Pa. Then I came to California as Audio Engineer for ABC in Hollywood. I still hold this position. I will always be grateful for your help in getting me in the type of profession that has so much to look forward to."  
*William R. Dreese*


"I had been in the radio-repair business for 30 years, when I enrolled in the I.C.S. Television Servicing Course.

"Now I am able to approach a television job in a systematic manner, while others are still operating on the hit-or-miss level."  
*Kelsey G. Cobb*

"Up to the time I enrolled, my interest in electronics was purely a hobby, but before completing my course I was able to do a considerable amount of radio work. Now I have a good part-time business."  
*George A. Chase*

Send the coupon below for your free I.C.S. Career Kit!

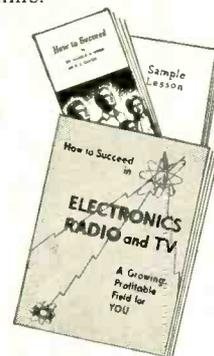- 1 "How to Succeed," 36-page guide to advancement.
- 2 Opportunity handbook for the field of your choice.
- 3 Sample lesson (Math) to demonstrate I.C.S. method.



For Real Job Security—Get an I.C.S. Diploma!

I.C.S., Scranton 15, Penna.

Accredited Member,  
National Home Study Council

## INTERNATIONAL CORRESPONDENCE SCHOOLS



BOX 02225M, SCRANTON 15, PENNA.

(Partial list of 257 courses)

Without cost or obligation, send me "How to Succeed" and the opportunity booklet about the field BEFORE which I have marked X (plus sample lesson):

### RADIO TELEVISION ELECTRONICS

- General Electronics Tech.
- Industrial Electronics
- Practical Radio-TV Eng'r'g
- Practical Telephony
- Radio-TV Servicing

### BUSINESS

- Cost Accounting
- Managing a Small Business
- Purchasing Agent

### DRAFTING

- Electrical Drafting

### HIGH SCHOOL

- High School Diploma
- Good English
- High School Mathematics

### ELECTRICAL


- Electrical Engineering
- Elec. Engr. Technician
- Elec. Light and Power
- Practical Electrician
- Professional Engineer (Elec.)

### LEADERSHIP

- Industrial Foremanship
- Industrial Supervision
- Personnel-Labor Relations
- Supervision

Name \_\_\_\_\_ Age \_\_\_\_\_ Home Address \_\_\_\_\_  
 City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_ Working Hours \_\_\_\_\_ A.M. to \_\_\_\_\_ P.M. \_\_\_\_\_  
 Occupation \_\_\_\_\_

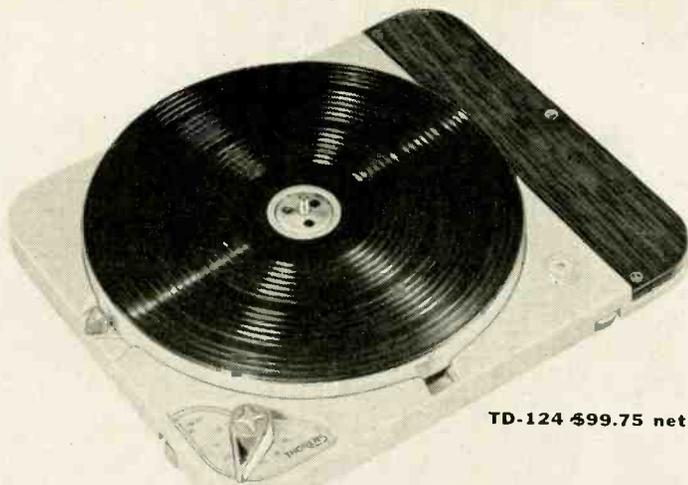Canadian residents send coupon to International Correspondence Schools, Canadian, Ltd., Montreal, Canada. . . . Special tuition rates to members of the U. S. Armed Forces.



TD-124 \$99.75 net

# WHAT MAKES THE TD'S TOPS?

...finer for stereo...finer for mono

If you move in circles where component hi-fi is a by-word, you've no doubt heard about the Thorens TD-124 transcription turntable and its fabulous performance. But for late-comers we'd like to point up just a few of the really big features (non-technical readers may skip remarks in parentheses): • **Extra heavy table for constant speed** (10 lb rim-concentrated table insures low wow and flutter; higher moment of inertia than any similar table). • **Exact speed** ( $\pm 3\%$  adjustment on all speeds— $16\frac{2}{3}$ ,  $33\frac{1}{3}$ , 45, 78—with built-in illuminated strobe for setting after stylus is on record). • **Easy on records** (unique two-table design permits starts

after you've placed stylus, permits  $2\frac{1}{2}$  rev. starts, makes cueing easy). • **Extremely low rumble** (mirror-finish main-bearing, nylon-seated ball-thrust-bearing reduce both vertical and horizontal rumble to a new low, so important for stereo). • **2-way motor rumble reduction** (both an extra-large idler and an ultra-compliant belt-drive keep motor vibration and speed variations from table). Driving parts electronically balanced. No costly base necessary (only \$9.00). 50/60 cycles, 100/250 volt operation.

These are just a few of the TD-124's features. Ask your dealer to tell you the whole story on the fabulous TD-124.

## Now two budget-priced TD turntables

These 4-speed turntables have same basic adjustable-speed precision-drive as famous TD-124 but you save two ways: (1) they come already equipped with stereo-wired professional arm without overhang making them ideal changer replacements. (2) Some TD features have been eliminated to save you money. But they still top the performance of every similar turntable and player on the market. TD-184 has semi-automatic operation. TD-134 is manually operated. Precision metal stroboscope (50/60 cycles) furnished with each unit. 100/250 volt operation. Wooden base only \$6.00.



TD-134  
\$60.00 net

TD-184  
\$75.00 net



Thorens celebrates 75 years of progress in music reproduction

# THORENS

SWISS MADE PRODUCTS  
HI-FI COMPONENTS • LIGHTERS  
SPRING-POWERED SHAVERS  
MUSIC BOXES  
NEW HYDE PARK, NEW YORK



## TV MAN RIDES GRAVY TRAIN?

This article in our November issue was clearly marked as directed at a racket harmful to the TV repair technician—certainly not aimed at TV service as a whole. These letters indicate that the article was not clearly enough flagged. Our apologies to any technicians who may have been offended by the story, and may we suggest they read it again in the light of this correspondence?

Dear Fred:

After hearing numerous complaints about an article, "The TV Man Rides the Gravy Train," by E. H. Leftwich, in your November issue (page 98), I just had to read it despite an almost continuous series of trips that have kept me on the run. Frankly, Fred, had this article appeared in the April issue I would think it was an April Fool gag.

Just who this author is, I don't know, but quite obviously he is *not* a professional home electronics technician and certainly not a businessman or an accountant. His explanation of why he doesn't do TV work, how he went about picking a TV servicer for himself, and his manner of diagnosing trouble are *not* those of a professional servicer; in fact, they are typical of a set owner who "knows it all." This is borne out further in his accounting procedure. Who ever heard of 15 calls per day, especially day in and day out, even assuming a 12-hour day? Further, I would like to see the shop, especially a schlock operator such as he implies, getting 540 calls per week.

We would be most anxious to learn the author's address and business name. We are certain that he is not a professional servicer, even though he describes himself as an electronics engineering writer (what school did he get his degree from?), but also is *not* an author except of purely fictional twaddle, unworthy of publication in any magazine. FRANK J. MOCH  
*Executive Director, National Alliance of Television & Electronic Service Associations*  
Chicago, Ill.


## REPLY TO MR. MOCH

Dear Frank:

I was rather surprised to get your letter. Of course, we had expected some objections to the "Gravy Train" story, chiefly from two types of readers. The first is the literal-minded type who does not expect to find humor or hyperbole in a technical magazine and asks us if the April Fool stories are really just jokes. Even the vastly exaggerated and burlesqued attack on the aggressive do-it-yourselfer, "Beware the Serviceman" which ran in our September,
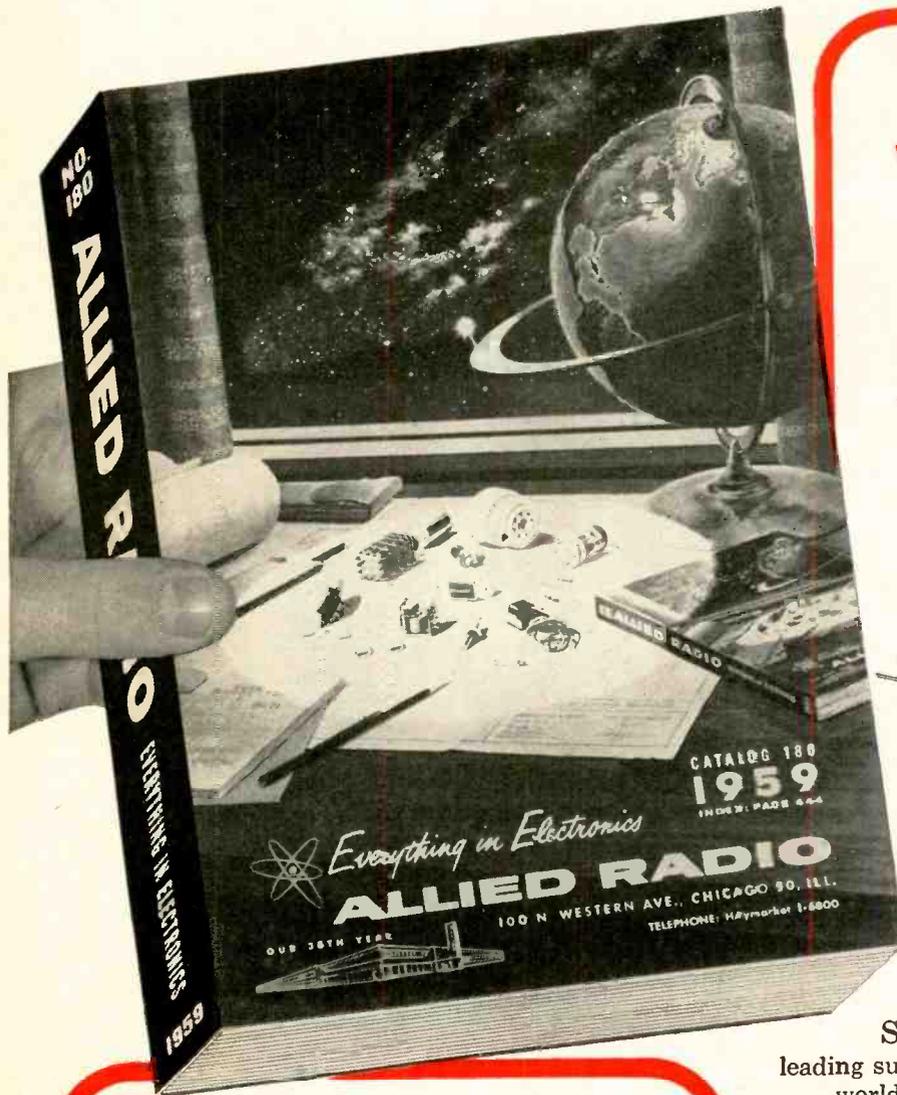
# free! ALLIED'S 1959

value-packed 452-page  
**ELECTRONIC SUPPLY CATALOG**



the only COMPLETE guide  
to everything in electronics

### WORLD'S LARGEST STOCKS

- Latest Stereo Hi-Fi Systems—  
Everything in Hi-Fi Components
- Money-Saving, Build-Your-Own  
KNIGHT-KITS—Latest Models
- Values in Recorders and Supplies
- Latest Public Address Systems,  
Paging and Intercom Equipment
- Amateur Receivers, Transmitters  
and Station Gear
- Test & Laboratory Instruments
- Specialized Electronic Equipment  
for Industrial Application
- TV Tubes, Antennas, Accessories
- Huge Listings of Parts, Tubes,  
Transistors, Tools, Books



### featuring:

**MONEY-SAVING knight-kits:** Finest electronic equipment in money-saving kit form. Complete selection of latest Hi-Fi amplifier, tuner and speaker kits (new Stereo units); Hobbyist kits; Test Instruments and Amateur kits. KNIGHT-KITS are an exclusive ALLIED product.

**HI-FI! STEREO!** See the world's largest selection of quality Hi-Fi music systems and famous name components. First with the latest in STEREO! Save on ALLIED-recommended complete systems. Own the best in Hi-Fi for less!

**EASY PAY TERMS:** Only 10% down; available on orders of \$20 or more. Fast handling—no red tape.

## ALLIED RADIO

 our 38th year  
World's Largest Electronic Supply House

Send for ALLIED'S 1959 Catalog—it's the leading supply guide—452 pages packed with the world's largest selection of quality electronic equipment at lowest, money-saving prices. Get every buying advantage at ALLIED: fastest shipment, expert personal help, lowest prices, guaranteed satisfaction...

send for the leading  
electronic supply guide

**FREE!**

ALLIED RADIO CORP., Dept. 2-A9  
100 N. Western Ave., Chicago 80, Ill.

Send FREE 452-Page 1959 ALLIED Catalog

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

## Auto Radio Control Replacement is Child's Play

with new **Centralab**®

## Exact Replacement Controls



Now one source can fill all your needs for auto radio replacement controls. CENTRALAB has a new line of exact replacements for every popular radio in use today. This is the first time in history that you have been able to get the auto radio control you need—from a control manufacturer.

It's easy to handle more auto radio repair business—and handle it profitably—when you install exact replacement controls bought from your *regular* supplier. No need to run all around town looking for the right unit—you can now be sure that your CENTRALAB distributor has it!

A complete and thorough guide listing all auto radio controls in use today, and their CENTRALAB equivalents, is now available. Pick up your free copy from your distributor—or write direct to CENTRALAB.

# Centralab

® B-5902

A DIVISION OF GLOBE-UNION INC.  
922A E. KEEFE AVE. • MILWAUKEE 1, WIS.  
IN CANADA: 804 Mt. Pleasant Rd. • Toronto 12, Ont.

CONTROLS • ROTARY SWITCHES • CERAMIC CAPACITORS  
PACKAGED ELECTRONIC CIRCUITS • ENGINEERED CERAMICS

### CORRESPONDENCE (Continued)

1945, issue, drew some protests from that group. Second, individuals in the "Trustworthy TV" class would no doubt react vigorously. We believe that they form a very small part of our readership, since not only are they few in numbers, but are usually composed of persons not interested in the technical side of the business, and therefore unlikely to read a technical magazine.

We did not expect to get protests from the bulk of the TV service business, since the racket to which we are calling attention may be as harmful to the legitimate technician as the \$1-per-call and other fly-by-nights we have attacked in the past. In some ways, it may be more harmful, since the "Trustworthy" type of operation clothes itself in bigness, puts up a legitimate-looking front, advertises widely and very actively competes for business. The little outfit working from a telephone number with no address is handicapped from the beginning, and it is easy to expose this type of operator to the customer. If stung by such an outfit, he resolves to deal with the legitimate field from then on. But if he is left with bad will by an outfit like "Trustworthy," he is likely to feel aggrieved at the whole service industry, since he is not as able to spot such organizations as racketeers. In fact, it is very hard for anyone to recognize them (till they are indicted).

Our mail on this has been smaller than I expected—only four letters to date, two of which were highly critical and two critical in a modified way. Yet two service associations have condemned the story, and you have received other complaints. Now, the "Trustworthy" type of company is just the one that does not join service associations—they prefer to go it alone—so I cannot feel that the members of these associations recognize themselves in Leftwich's picture. Is it possible that in each of those meetings that the majority had not seen the magazine and had it described to them by the more emotional of those who had read it?

Obviously, we had no intention of attacking the TV service technician as such—our butter just isn't on that side of the bread, for one thing. What we *thought* we were doing was trying to point out a racket which we felt was doing harm to the legitimate service technician. Leftwich, I was sure, had the same idea. He does happen to be a legitimate electronics author, as you can see from page 39 of the same issue, and wrote the reply to the *Readers Digest* "expose" of infamous memory.

The 15 calls a day you mention are one short of what was required by a get-them-out-of-the-house outfit prosecuted here some years ago. It required that the field men make a call per half-hour for an 8-hour day. And even some legitimate businesses in this town

(Continued on page 22)

# Learn TELEVISION-RADIO

*Servicing or Communications*  
by Practicing at Home in Spare Time



NRI gives you kits to build these and other equipment

## Electronic Technicians Have High Pay, Prestige Jobs

People look up to and depend on the Technician, more than ever before. His opportunities are great, and are increasing. Become a Radio-Television-Electronic Technician. At home, and in your spare time, you can learn to do this interesting, satisfying work—qualify for important pay. A stream of new Electronics products is increasing the job and promotion opportunities for Television-Radio-Electronic Technicians. Right now, a solid, proven field of opportunity for good pay is servicing the millions of Television and Radio sets now in use. The hundreds of Television and Radio stations on the air offer interesting jobs for Operators and Technicians. The military services reward qualified Technicians with higher rank and pay. Police, Aviation, Mobile Two-Way Radio are expanding. To ambitious men everywhere: here is rich promise of fascinating jobs, satisfaction and prestige increasing personal prosperity.

## Make Extra Money Soon, \$10 to \$15 a Week in Your Spare Time

NRI students find it practical and profitable to start fixing sets for friends and neighbors a few months after enrolling. Picking up \$10, \$15 and more a week gives substantial extra spending money. Use the Tester built with parts NRI furnishes, to locate and correct Radio-TV receiver troubles. Many who start in spare time, soon build full time Television-Radio sales and service businesses; others enjoy profitable spare time businesses and the security of a source of income to fall back on in case of layoffs, hard times or other changes in regular job. Postage free card will bring you complete facts about the NRI tested way to better pay.

## NRI Has Trained Thousands for Successful Careers in TV-Radio



**Studio Engr., Station KATV**  
"I am now Studio Engineer at Television Station KATV. Before enrolling for the NRI Course, I was held back by limitation of a sixth grade education." **BILLY SANCHEZ**, Pine Bluff, Ark.



**Has All the Work He Can Do**  
"Since finishing NRI Course I have repaired more than 2,000 TV and Radio sets a year. NRI training certainly proved to be a good foundation." **H. R. GORDON**, Milledgeville, Ga.



**Has Good Part Time Business**  
"Quite early in my training I started servicing sets. Now I have completely equipped shop. My NRI training is the backbone of my progress." **E. A. BREDÁ**, Tacoma, Wash.

**Cut Out and Mail Postage-Free Card NOW**

## Sample Lesson and Catalog Both FREE

SEE OTHER SIDE 

OLDEST & LARGEST HOME STUDY RADIO-TV SCHOOL  
**National Radio Institute**  
Dept. C, Washington 16, D.C.

Please send me sample lesson of your Radio-Television Training and Catalog FREE. (No salesman will call.)

Name..... Age.....

Address.....

City..... Zone..... State.....

ACCREDITED MEMBER NATIONAL HOME STUDY COUNCIL

How Electricity is Produced for Electronics

Job and Career Opportunities for RADIO-TV TECHNICIANS

**ACT NOW FIND OUT WHAT NRI OFFERS YOU** 

**NRI SUPPLIES LEARN-BY-DOING KITS WITHOUT EXTRA CHARGE**  
**Technical Know-How Pays Off in Interesting, Important Work**



**YOU BUILD AC-DC Superhet Receiver**

NRI Servicing Course includes all needed parts. By introducing defects you get actual servicing experience practicing with this modern receiver. Learn-by-doing.



**YOU BUILD This 17 Inch Television Receiver**

As part of your NRI course you can get all components, tubes, including 17" picture tube, to build this latest style Television receiver; get actual practice on TV circuits.

**YOU BUILD Broadcasting Transmitter**

As part of NRI Communications Course you build this low power Transmitter, learn commercial broadcasting operators' methods, procedures. Train for your FCC Commercial Operator's License.




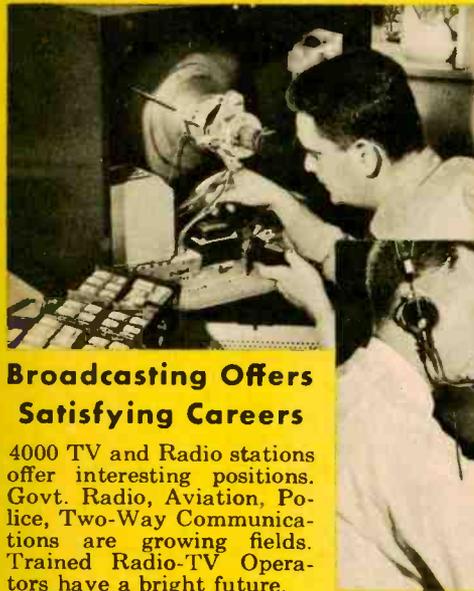**YOU BUILD Vacuum Tube Voltmeter**

Use it to earn extra cash fixing neighbors' sets; bring to life theory you learn from NRI's easy-to-understand texts.



**For Higher Pay, Better Jobs**  
**Be a TV-Radio-Electronic Technician**



**Servicing Needs More Trained Men**

Portable TV, Hi-Fi, Transistor Radios, Color TV are making new demands for trained Technicians. Good opportunities for spare time earnings or a business of your own.



J. E. Smith, Founder


**Train at Home the NRI Way Famous for Over 40 Years**

NRI is America's oldest and largest home study Television-Radio school. The more than 40 years' experience training men for success, the outstanding record and reputation of this school—benefits you in many ways. NRI methods are tested, proven. Successful graduates are everywhere, from coast to coast, in small towns and big cities. You train in your own home, keep your present job while learning. Many successful NRI men did not finish high school. Let us send you an actual lesson, judge for yourself how easy it is to learn.

**No Experience Necessary—NRI Sends Many Kits for Practical Experience**

You don't have to know anything about electricity or Radio to understand and succeed with NRI Course. Clearly written, well-illustrated NRI lessons teach TV-Radio-Electronic principles. You get NRI kits for actual experience. All equipment is yours to keep. You learn-by-doing. Mailing the postage-free card may be one of the most important acts of your life. Do it now. Reasonable tuition. Low monthly payments available. Address: NATIONAL RADIO INSTITUTE, Washington 16, D. C.

**NRI Graduates Do Important Work**

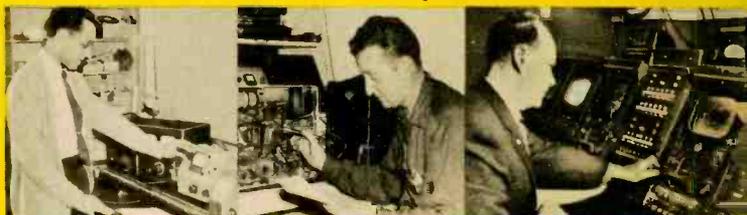

**Now Quality Control Chief**  
 "Had no other training in Radio before enrolling, obtained job working on TV amplifiers before finishing course. Now Quality Control Chief." T. R. FAVAROLO, Norwich, N. Y.

**NRI Course Easy to Understand**  
 "I opened my own shop before receiving my diploma. I have had to hire extra help. I am independent in my own business." D. P. CRESSEY, Stockton, Cal.

**Works on Color-TV**  
 "NRI changed my whole life. If I had not taken the course, probably would still be a fireman, struggling along. Now Control Supervisor at WRCA - TV." J. F. MELINE, New York, N. Y.

FIRST CLASS  
 Permit No. 20-R  
 (Sec. 34.9, P. L. & R.)  
 Washington, D.C.

**BUSINESS REPLY CARD**

No Postage Stamp Necessary if Mailed in the United States

POSTAGE WILL BE PAID BY

**NATIONAL RADIO INSTITUTE**  
 3939 Wisconsin Avenue  
 Washington 16, D.C.

**SAMPLE LESSON**  
**64-page CATALOG**  
**both FREE**

**SEE**  
**OTHER**  
**SIDE**

ownership of a complete and currently maintained  
**PHOTOFACT SERVICE DATA LIBRARY**  
**SPELLS SUCCESS FOR SERVICE TECHNICIANS**  
*here's actual proof from the men who know!*



"We believe it is almost impossible to give fast and efficient service without PHOTOFACT. Sams PHOTOFACTS are a great help in trouble-shooting and replacement parts. They save time and money for us."

—Gerald L. Jellis, Watertown, So. Dak.  
 (Operator of "Radio TV Center")

**HERE'S MORE PROOF... FROM COAST-TO-COAST**

**OHIO**

"I find SAMS PHOTOFACT an absolute necessity in doing a job quickly and accurately... extremely helpful..."  
 —Dan M. Heinrich, Westlake, Ohio

**PENNSYLVANIA**

"PHOTOFACT is an invaluable 'piece of equipment' in our repair shop and it speeds our shop repairs 100%."  
 —Luther W. Wilkes, Houtzdale, Pa.

**NEW JERSEY**

"PHOTOFACT is used here every day, like an extra brain."  
 —Joseph M. Decker Jr., Newton, N. J.

**MASSACHUSETTS**

"I would be lost without PHOTOFACT."  
 —Emilio Conzo, Newton, Mass.

**MAINE**

"Having data on sets plus parts listings, etc., means the difference between getting sets fixed and out in a reasonable length of time or having them tied up while securing such information, as I am located in a small town and have to depend on mail service for parts and information."  
 —Samuel S. Sawyer, Kezar Falls, Maine

**VIRGINIA**

"I don't know how we would get along without PHOTOFACT, as we work on all makes and models."  
 —Kenneth E. Jenkins, Big Stone Gap, Va.

**CALIFORNIA**

"With PHOTOFACT, the information I need is always at hand. I don't have to worry about a repair job because I know I will have a schematic that gives me correct information in the simplest possible form."  
 —J. R. Stukes, Norwalk, Calif.

**WISCONSIN**

"In my business, I service all makes of TV sets. Without good service literature such as PHOTOFACT, this would be an impossible task—especially to do a quick, intelligent job. In my estimation, Sams PHOTOFACTS is unequalled. I would hate to conduct a business without them. Keep up the good work!"  
 —Willard F. Dumke, Menasha, Wis.

**ILLINOIS**

"PHOTOFACT makes it possible to identify any part in any model TV... It is possible to locate trouble in almost any set through the use of Sams."  
 —Sam Rogondino, Lake Forest, Ill.

(These are just a few of the hundreds of "Success with PHOTOFACT" letters in our files)

**SEE YOUR SAMS DISTRIBUTOR TODAY,  
 OR WRITE TO HOWARD W. SAMS FOR FULL DETAILS**



**HOWARD W. SAMS & CO., INC.**  
 2205 E. 46th St., Indianapolis 6, Ind.

- Send me Free booklet "Your Guide To Maximum Profits"  
 I'm a Service Technician:  full-time;  part time

My Distributor is: \_\_\_\_\_

Shop name \_\_\_\_\_

Attn. \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**NEW! EASY-BUY PLAN**

—the money-saving way to build your complete profit-making PHOTOFACT Library!  
 NO INTEREST—NO CARRYING CHARGE—AS LITTLE AS \$10 DOWN

**FREE!** VALUABLE STEEL FILE CABINETS FOR REGULAR PHOTOFACT SUBSCRIBERS AND PHOTOFACT LIBRARY PURCHASERS

**GET THE FULL DETAILS**



**ADDS INCOME 2 WAYS**

**1. Tests and Repairs Picture Tubes**  
(110° Tubes and Color Tubes too, with new C40 Adapter)

**2. Makes New Tube Sales Easier**



**CATHODE REJUVENATOR TESTER**

**CRT 400 PROVES REAL MONEY-MAKER**  
Thousands of servicemen today make money and keep customer good-will by checking and correcting b&w picture tube troubles with the famous B&K CRT 400, right in the home without removing tube from set. Restores emission and brightness. Repairs inter-element shorts and open circuits. Checks leakage. Indicates picture quality customer can expect. Life Test checks gas content and predicts remaining useful life of picture tube. Makes new picture tube replacement sales easier!  
**Model 400 (without adapter) . . . . . Net, \$59<sup>95</sup>**

**NEW MODEL C40 ADAPTER DOUBLES VALUE OF B&K CRT**  
Designed for use with all B&K Models 400 and 350 CRT's. Makes it easy to test and rejuvenate TV color picture tubes and 110° picture tubes. Isolates and detects difficult color troubles. Tests and rejuvenates each gun of the color picture tube separately the same way as a black & white tube.  
**Model C40 Adapter . . . . . Net, \$9<sup>95</sup>**  
See your B&K distributor, or write for Bulletin AP12-E

New C40 Adapter for 110° Tubes and Color Tubes



Makers of CRT, DYNA-QUIK, DYNA-SCAN and CALIBRATOR

**B & K MANUFACTURING CO.**  
3726 N. Southport Ave. • Chicago 13, Illinois



**Wanna' Sell? . . . Buy? . . . Trade?**



For best results use

**Radio-Electronics**

Opportunity Adlets

Rates as low as \$5.

50¢ a word—10 word minimum

**Radio-Electronics** 154 West 14th Street • New York 11, N. Y.

get over 500 calls a week—the figure is not extraordinary, though they presumably do considerable servicing in the home and their calls would take more time. (A large legitimate concern in this city has a norm of 8 standard service calls per day, and pays a bonus of a dollar a call for all over the norm.)

Thank you for writing me immediately about this. You may make any use of this letter you desire.

FRED SHUNAMAN

Managing Editor,  
RADIO-ELECTRONICS

### MORE GRIEF THAN GRAVY

Dear Editor:

When I started reading "The TV Man Rides the Gravy Train" (RADIO-ELECTRONICS, November, 1958, page 98), I assumed that it was intended as pure fiction. But as I read on I realized that we were actually supposed to believe this trash. I have read Gernsback publications for more than the 16 years I have been in electronics service and I am surprised that you would print anything so stupid.

If these conditions exist anywhere in the US, it would be a good location for the many honest TV servicemen I know who aren't making a decent living. Many of the best former TV servicemen in Memphis are now working as truck drivers, policemen and factory workers because they couldn't make enough to get by at television service.

ALEX T. YATES

Memphis, Tenn.

(The unfortunate facts are that outfits like these mentioned by Mr. Leftwich make life harder—not easier—for the legitimate service technician, and that more than one of the "best former TV servicemen" are out of business because of the unfair competition of just such organizations.—Editor)

### SUGGESTIONS TO LEFTWICH

Dear Editor:

Mr. Leftwich left out a few points:

1. He could have reported to the Better Business Bureau anyway—even though the repair shop was a member. Wouldn't they kick out an unsatisfactory member?

2. In his estimated budget for Trustworthy TV, he should have entered about \$30,000 for bad debts. I, for one, wouldn't have paid, and would have sued if they had sold my set to cover repairs without *all* the legal formalities. So would many other people.


3. He should have gotten a loan set to use while his was in the shop. No charge, of course.

I sympathize, but I still think most technicians are good guys caught in the middle of an expensive operation. So, although I pal around with them, I do my own repair work on the three sets in use in my own household—but *no others*.

(Name withheld by request)

END

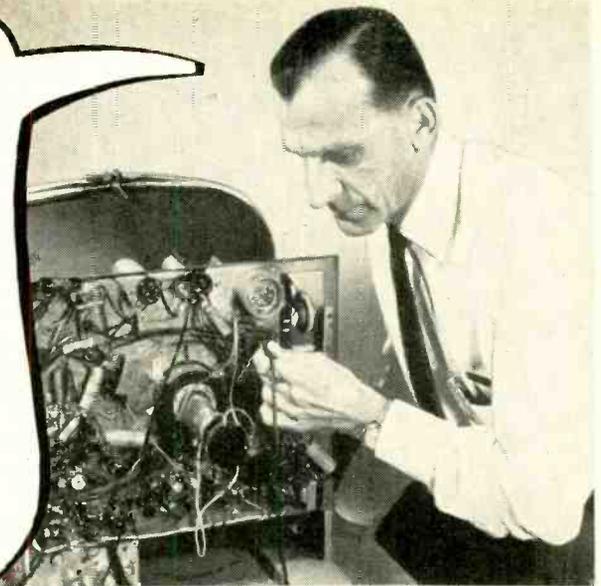I chose **COYNE TELEVISION**  
**RADIO-COLOR TV**  
 home training because  
 Coyne has been training  
 men for good jobs OR  
 their **OWN BUSINESS** for  
**NEARLY 60 YEARS**



Giant opportunity field! Join the thousands Coyne Home Training is preparing for a successful future in TV—open the door to better pay jobs, or your own business! COYNE—a leading residential, practical school—oldest of its kind—established 1899—is the institution behind this training.


Here is **MODERN—QUALITY TELEVISION** Home Training designed to meet the rigid standards that have made Coyne famous. You get personal supervision of Coyne Staff who know TV and know how to teach. **Learn quickly and easily in spare time.** No previous experience or advanced education necessary.

I chose **COYNE** because  
 their new method costs less  
 than half what most others do!



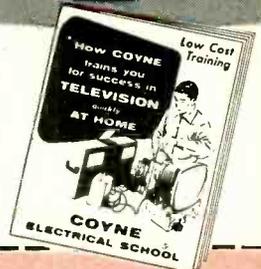**SEND COUPON FOR FREE BOOK**

Send coupon below for all-new fully-illustrated book and full details including **EASY PAYMENT PLAN. NO COST OR OBLIGATION—NO SALESMAN WILL CALL**



Modern, up-to-the-minute. Easy to follow, step-by-step instructions—fully illustrated with 2150 photos and diagrams. **UHF and COLOR-TV included.** So practical you can quickly earn extra money in TV-Radio Sales and Service. Not only Coyne Quality training, but costs *half* what you'd expect to pay because you pay only for training—no costly extras. Free life-time employment service.

B. W. Cooke, Jr.  
 President

**COYNE**  
**ELECTRICAL SCHOOL**

Founded 1899


CHARTERED AS AN EDUCATIONAL INSTITUTION NOT FOR PROFIT  
 1501 W. Congress Parkway Dept. 19-H5 Chicago 7, Illinois

**COYNE TELEVISION**  
**HOME TRAINING DIVISION**  
 Dept. 19-H5 New Coyne Building  
 1501 W. Congress Pkwy., Chicago 7, Ill.

Send **FREE** Book and details of your Television - Radio - Color TV Home Training offer.

Name \_\_\_\_\_  
 Address \_\_\_\_\_  
 City \_\_\_\_\_ State \_\_\_\_\_

# How to save 77 years

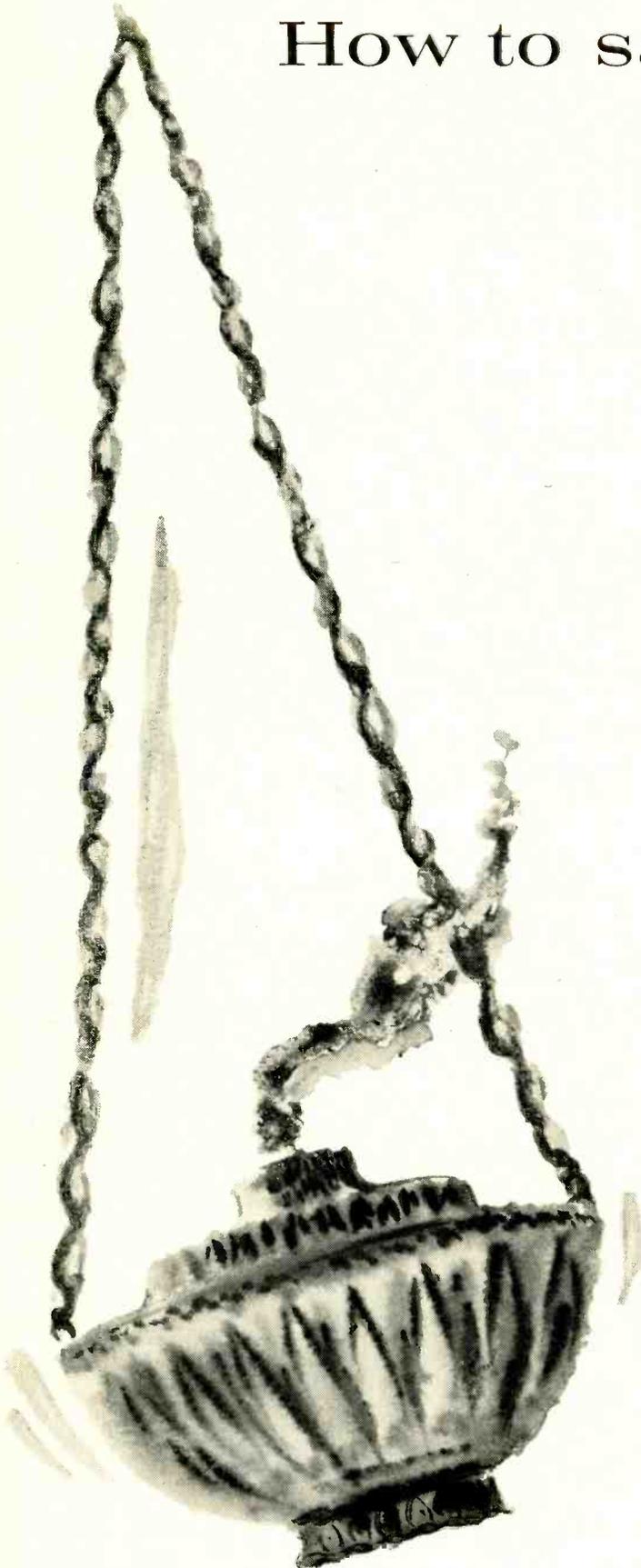

The boy Galileo sat in the sanctuary of Pisa's great cathedral, observing the movement of a lamp which had been set swinging by a sudden gusty draft. The chain by which it was suspended from the high ceiling was of such a length that the arcs decreased but slowly. Strange thing, though. No matter how far the pendulum swung, its movement consumed the same time. Galileo made a note of that. The year was 1581.

The old man sat at his writing desk, sixty years and a thousand disputes later, writing down a new theory. The regularity of a swinging pendulum might be combined with a spring mechanism to improve the unreliable clocks of that day. So Galileo scribbled on, and did nothing more about it. A number of years after his death Huygens took the notes and invented the pendulum clock. *Seventy-seven years had elapsed since the boy made the observation upon which it was based!*

The creative thinker today still need not have a specific use in mind when, by equation or formula, he branches off from the accepted to the hitherto unknown. The classic invention of this decade, the transistor, evolved in the Bell Telephone Laboratories as scientists sought a deeper understanding of semiconductors. On the other hand, another great invention, the feedback amplifier, came from the acutely creative mind of one Bell engineer faced with a specific problem.

Current Bell Laboratories activities—in such areas as data transmission, radar and submarine cable development—call for the coordinated efforts of all types of thinkers and all types of approaches. One type complements another.

Today, seventy-seven years would not have elapsed between the swinging lamp and the swinging clock pendulum—certainly not at Bell Labs, where ideas, though not rushed, are carefully advanced toward fruitful application in national defense, industry and communications. An important part of this harvest is the efficiency of America's telephone service, unequalled anywhere else in the world.

**BELL TELEPHONE LABORATORIES**

WORLD CENTER OF COMMUNICATIONS RESEARCH AND DEVELOPMENT




**WE'RE MAKING IT EASIER THAN EVER TO BECOME A WELL PAID RADIO-TELEVISION SERVICE TECHNICIAN**

**NOW - Just \$6 Starts You Training in**  
**RADIO-TELEVISION**  
**the SPRAYBERRY "Learn-by-Doing" Way . . .**

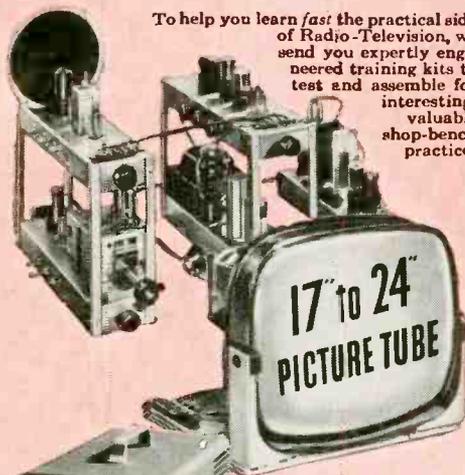**25 BIG, COMPLETE KITS of PARTS & EQUIPMENT**

To help you learn *fast* the practical side of Radio-Television, we send you expertly engineered training kits to test and assemble for interesting, valuable shop-bench practice!





• The new Sprayberry Training Television Receiver, built and tested in 5 sections.

• Now offered . . . this fine modern oscilloscope.

• You build this powerful two-band superheterodyne radio receiver.

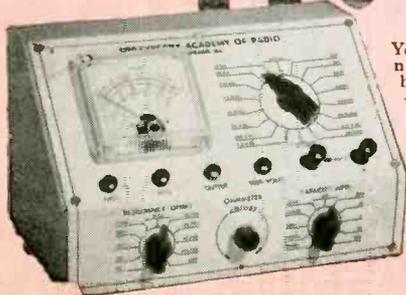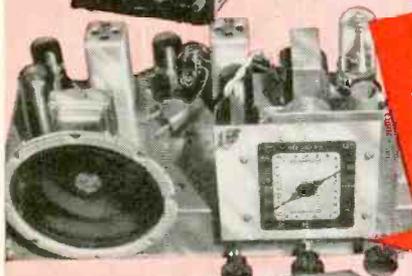**Big New CATALOG AND Sample Lesson FREE!**



You build the new Sprayberry tester—a complete 18-range Volt-Ohm-Milliammeter test meter.

★ ★ ★ This great industry is begging for trained men . . . to step into good paying jobs or a profitable business of their own! Our new plan opens the doors of Radio-Television wide to every ambitious man who is ready to act at once!

Men by the thousands . . . trained Radio-Television Service Technicians . . . are needed at once! Perhaps you've thought about entering this interesting, top paying field, but lack of ready money held you back. Now—just \$6 enrolls you for America's finest, most up to date home study training in Radio-Television! Unbelievable? No, the explanation is simple! We believe Radio-Television *must* have the additional men it needs as quickly as possible. We are willing to do our part by making Sprayberry Training available for less money down and on easier terms than ever before. This is your big opportunity to get the training you need . . . to step into a fine job or your own Radio-Television Service Business.

**Complete Facts Free—Act Now; Offer Limited**

Only a limited number of students may be accepted on this liberal and unusual basis. We urge you to act at once . . . mail the coupon below and get complete details plus our big new catalog and an actual sample lesson—all free. No obligation . . . no salesman will bother you.

**HOME STUDY TRAINING IN SPARE TIME**

Under world-famous 27-year old Sprayberry Plan, you learn entirely at home in spare time. You keep on with your present job and income. You train as fast or as slowly as you wish. You get valuable kits of parts and equipment for priceless shop-bench practice. And everything you receive, lessons and equipment alike, is all yours to keep.

**LET US PROVE HOW EASILY YOU CAN LEARN!**

Radio-Television needs YOU! And Sprayberry is ready to train you on better, easier terms, that any ambitious man can afford. *Just \$6 starts you!* Mail coupon today . . . let the facts speak for themselves. You have everything to gain. Let us prove the kind of opportunity that's in store for you!

**SPRAYBERRY Academy of Radio-Television**  
 1512 Jarvis Avenue, Dept. 20-Q, Chicago 26, Illinois

**Mail This Coupon Now—No Salesman Will Call**


**Sprayberry Academy of Radio-Television**  
 Dept. 20-Q, 1512 W. Jarvis Ave., Chicago 26, Ill.


Please rush all information on your ALL-NEW Radio-Television Training Plan. I understand this does not obligate me and that no salesman will call upon me. Include New Catalog and Sample Lesson FREE.

NAME . . . . . Age . . . . .

ADDRESS . . . . .

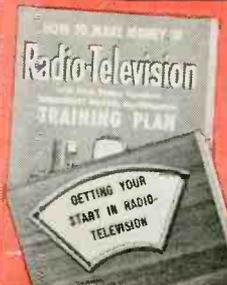CITY . . . . . ZONE . . . . . STATE . . . . .



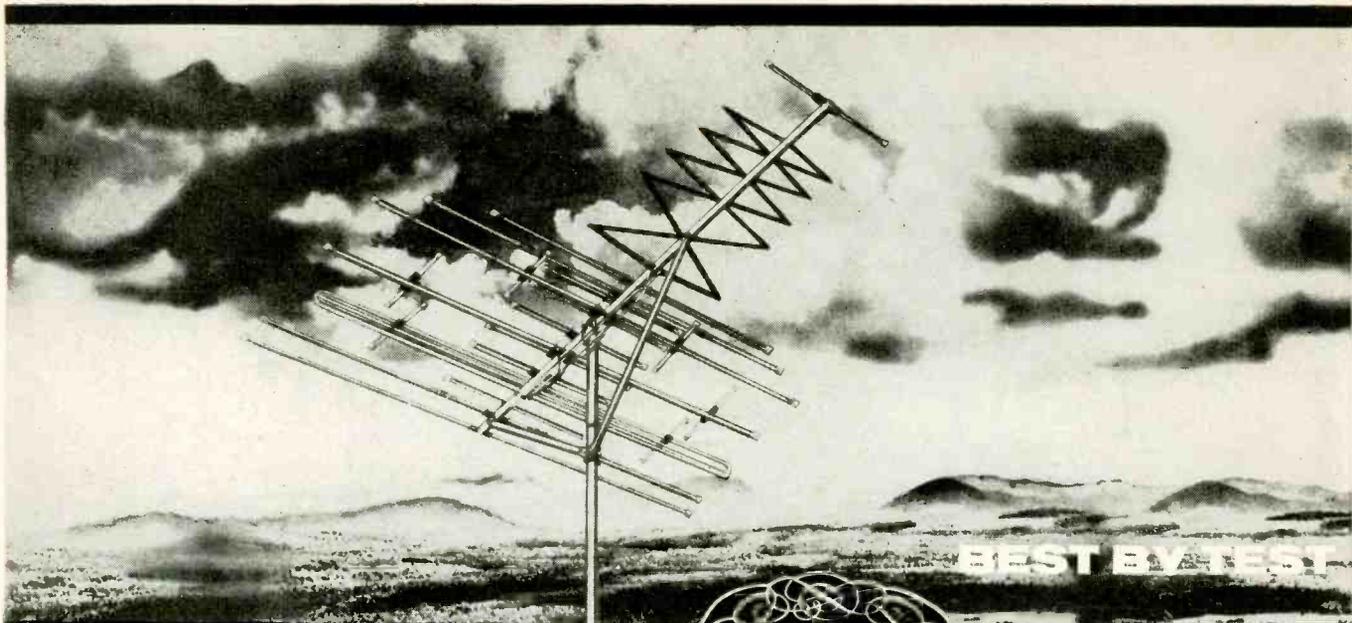

**WHAT EVERY SERVICEMAN SHOULD KNOW ABOUT THE**




**SATELLITE-HELIX**




**1. BALANCED SLEEVE DIPOLE DESIGN!** Shrinks the miles and flattens the mountains. Boosts gain up to 37% over larger fringe antennas. Provides 15 to 1 front-to-back voltage ratio on channels 2 to 6, and 18 to 1 on channels 7 to 13.



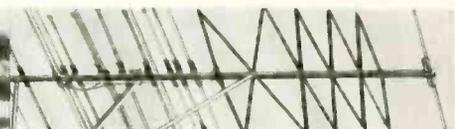**2. 28-ELEMENT "SEARCH LIGHT" DIRECTIVITY!** Multiple driven dipoles pile up needle-sharp directivity that pinpoints distant stations, sidesteps ghosts and interference for flawless picture definition.



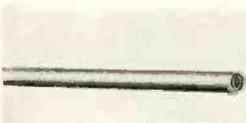**3. FLAT MICROWAVE HELICAL SECTION!** Each individual non-linear additive collector is tuned separately for highest gain and sharpest directivity on each of the 7 high band channels.



**4. 15 INCH ALUMINUM DOWELS!** Reinforce all elements over 30 inches in length. Rigidize elements against sag or sway. Keep antenna working and looking like new.



**5. DOUBLE U-BOLT FOR DOUBLE-STRENGTH!** Grips crossarm powerfully to mast. No shift or slip. Keeps antenna on station beam even in gale-force winds.



**6. ONE INCH TUBULAR BOOM BRACE!** Full size, full length construction. Rigidizes crossarm, prevents twist or droop. Heavy gauge one inch o.d. aluminum tubing.



**7. SEAMLESS ELEMENTS!** Six 1/2 inch diameter seamless elements impart extra strength as well as improve electrical conductivity.



**8. ALCOA ALUMINUM!** Made of 100% aircraft aluminum by ALCOA—world's top-quality producer—for permanent corrosion-resistance.



**9. NATIONALLY ADVERTISED!** Dramatic ads all season long in Progressive Farmer, and other national and local TV, radio and newspaper media send ready-to-buy prospects into your store. Plus big co-op advertising allowances.



**10. SPECTACULAR INCENTIVES!** Yours free! Costly card table and chair sets, hand-painted portraits, aluminum chaise lounge and chair patio sets. No coupon collecting. No contests. Every dealer wins.



**11. YOUR HARVEST OF PROFIT!** The most dynamic merchandising package ever put to work to nail down bigger and better TV antenna sales for service dealers.

**NOW MORE THAN EVER**—It pays to specify a JFD area-engineered Helix Color-tenna (with new Balanced Sleeve Dipole design) for every market. **Call or visit your JFD distributor now.**

**JFD Electronics Corp**  
 6101 Sixteenth Ave Brooklyn 4, New York

JFD International  
 15 Moore Street  
 New York, New York

JFD Canada Ltd.  
 51 McCormack Street  
 Toronto, Ontario, Canada

- SATELLITE HELIX**  
Deep fringe
- POWER HELIX**  
Fringe
- STAR HELIX**  
Near Fringe
- SUPER HELIX**  
Secondary
- JUNIOR HELIX**  
Primary

# UPGRADE YOUR INCOME

through Grantham Training and an F.C.C. License!

## What's in Your Future?

Are you *planning* your future or just drifting into it? Now is the time to get ahead in electronics—the world's fastest growing major industry. Now is the time to add technical knowledge and an F.C.C. license to your practical experience. Now is the time to prepare for higher pay—time to make your future secure.

## Grantham Training Prepares You

Grantham School of Electronics specializes in quality training in communications electronics, preparing students to pass F.C.C. operator license examinations. This training is available either by correspondence or in resident classes.

The Grantham Communications Course does not include actual work with practical kits or other equipment. That is, for example, it does not teach you how to solder or how to remove a TV chassis from the cabinet, etc. It is not a repair course but, instead, is bona fide technical training which teaches you to understand electronic theory—which teaches you the "why" of electronics.

If you are a beginner in this field, the Grantham course will give you the kind of detailed training in radio-electronics theory and operating practices that will enable you to obtain your first class F.C.C. license quickly. Then, this license plus your knowledge of theory will qualify you for certain types of employment, and you can improve your practical ability while on the job earning a salary.

If you already have practical experience in radio-electronics, the Grantham course can add a knowledge of theory and an F.C.C. license to that practical experience. This should qualify you for higher pay and greater job security.

## Train by Correspondence or in Resident Classes

**RESIDENT CLASSES**—The Grantham Communications Electronics Course is offered in both **DAY** and **EVENING** classes in Washington, Hollywood, and Seattle. The **DAY** course meets five days a week, from 9 a.m. until 1 p.m., and prepares you for a *first class* F.C.C. license in 12 weeks. The **EVENING** course meets two nights a week, from 6:30 p.m. until 10:30 p.m., and prepares you for a first class F.C.C. license in 30 weeks. All courses "begin at the beginning"—NO previous electronics training required or assumed.

**CORRESPONDENCE TRAINING**—The Grantham Communications Electronics Course is offered by correspondence from all Divisions of the School—Washington, Hollywood, and Seattle. The course has two major objectives—(1) to *teach* you a great deal of electronics, and (2) to prepare you to pass all F.C.C. examinations required for a *first class* license.

This course can prepare you *quickly* to pass F.C.C. examinations because it presents the necessary principles of electronics in a simple "easy-to-grasp" manner. Each new idea is tied in with familiar ideas. Each new principle is presented first in simple, everyday language. Then after you understand the "what and why" of a certain principle, you are taught the technical language associated with that principle. You learn more electronics in less time, because we make the subject easy and interesting.

## Which License for Which Job?

The **THIRD CLASS** radiotelephone license is of value primarily in that it qualifies you to take the second class

examination. The scope of authority covered by a third class license is extremely limited.

The **SECOND CLASS** radiotelephone license qualifies you to install, maintain and operate most all radiotelephone equipment except commercial broadcast station equipment.

The **FIRST CLASS** radiotelephone license qualifies you to install, maintain and operate every type of radiotelephone equipment (except amateur) including all radio and television stations in the United States, its territories and possessions. This is the highest class of radiotelephone license available.

## Here's Proof . . .

that Grantham students prepare for F.C.C. examinations in a minimum of time. Here is a list of a few of our recent graduates, the class of license they got, and how long it took them:

	License	Weeks
Walter Mengel, Jr., 423 James St., Crystal Lake, Ill.	1st	8
Serge G. Miller, 1315 W. 15th St., San Pedro, Calif.	1st	12
John A. Hayes, 1519 Madison Ave., Memphis, Tenn.	1st	14
Robert A. Morgan, 25 Barrow St., New York, N.Y.	1st	9
Hal Moon, Cook Hotel, 1334 Central, Kansas City, Mo.	2nd	5
W. R. Smith, 1335 E. 8th St., Long Beach, Calif.	1st	12
Erskin D. Davis, 4220 Clay St., NW, Washington, D.C.	1st	12
John R. Bahrs, 72 Hazelton St., Ridgefield Park, N. J.	1st	12
Earl A. Stewart, 3918 Modesto Dr., San Bernardino, Calif.	1st	14
Robert H. Moore, 807 Grace St., Baldwin, L.I., N.Y.	1st	12
Otis A. Towns, 3638 Bates St., St. Louis, Mo.	1st	12

**THREE COMPLETE SCHOOLS:** To better serve our many students throughout the entire country, Grantham School of Electronics maintains three complete schools—one in Washington, D.C., one in Hollywood, Calif., and one in Seattle, Wash. All schools offer the same rapid courses in F.C.C. license preparation, either home study or resident classes.

**MAIL COUPON FOR FREE BOOKLET:** Our free booklet, *Careers in Electronics*, gives details of how you can prepare quickly for your F.C.C. license. For your free copy of this booklet, clip the coupon below and mail it to the Grantham School nearest you.

## GRANTHAM

### SCHOOL OF ELECTRONICS

821-19th Street, N.W.  
Washington 6, D. C.  
(Phone: ST 3-3614)

408 Marion Street  
Seattle 4, Wash.  
(Phone: MA 2-7227)

1505 N. Western Ave.  
Hollywood 27, Calif.  
(Phone: HO 7-7727)

(Mail in envelope or paste on postal card)

TO: **GRANTHAM SCHOOL OF ELECTRONICS**

821-19th, NW • 408 Marion • 1505 N. Western  
Washington • Seattle • Hollywood

Please mail me your free booklet telling how Grantham training can prepare me quickly for my commercial F.C.C. license. I understand there is no obligation and no salesman will call.

Name \_\_\_\_\_ Age \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_

I am interested in:  Home Study,  Resident Classes **94 A**

# Here's the SPECIALIZED



A. A. GHIRARDI

These 2 great Ghirardi books bring you **COMPLETE TRAINING FOR MODERN RADIO-TV SERVICING!**

**SAVE \$1.25**

Make your service library complete! Get both these famous Ghirardi books of a saving of \$1.25 under the regular price. See **MONEY-SAVING COMBINATION OFFER** in coupon.

①

## RADIO & TV CIRCUITRY and OPERATION

Learn about circuits . . . and watch service headaches disappear

You can repair ANY radio, TV or other electronic equipment lots easier, faster and better when you're fully familiar with its circuits and know just why and how each one works . . . and that's exactly the kind of specialized training you get in Ghirardi's 669-page Radio & TV CIRCUITRY AND OPERATION training guide. First it gives a complete understanding of

shortest time. Each book is co-authored by A. A. Ghirardi whose radio-electronics training guides have, for more than 25 years, been more widely used for military, school and home study training than any other books of their types. Books are sold separately at prices indicated—or you save \$1.25 by buying them both. Use coupon or order from Rinehart & Co., Inc., Dept. RE-19, 232 Madison Ave., New York 16, N. Y.

Sold separately for \$6.75—or see **MONEY-SAVING COMBINATION OFFER**.

②

## RADIO & TV TROUBLESHOOTING and REPAIR

Complete training in modern service methods


Radio & TV TROUBLESHOOTING AND REPAIR is a complete 822-page guide to professional service methods . . . the kind that help you handle jobs faster, more profitably. For beginners, this giant book with its 417 clear illustrations is an easily understood course in locating troubles fast and fixing them right. For experienced servicemen, it is an ideal way to develop better

basic modern circuits and their variations. Finally it shows what troubles to look for and how to eliminate useless service testing and guesswork. Throughout, it gives you the above-average training that takes the "headaches" out of trouble-shooting—the kind that fits you for the best-paid servicing jobs. Contains 417 clear illustrations.

Sold separately for \$7.50 or save \$1.25 on **MONEY-SAVING COMBINATION OFFER**.

methods and shortcuts; or to find fast answers to problems. You learn troubleshooting of all types from "static" tests to dynamic signal tracing methods. Step-by-step charts demonstrate exactly what to look for and how to look. A big television section is a down-to-earth guide to all types of TV service procedures. Read it 10 days at our risk!
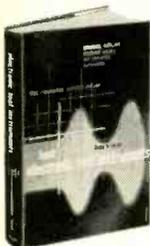
## Get More Work Out of Fewer Instruments!



**BASIC ELECTRONIC TEST INSTRUMENTS**  
254 pages,  
171 illus.  
Price \$4.95

Save time . . . Save money . . . Avoid buying instruments you don't really need!

It pays to think twice before you buy new instruments—without first determining whether you really need them—or just how and where you'll actually use them!


**BASIC ELECTRONIC TEST INSTRUMENTS** is an instrument guide especially for servicemen, amateurs and experimenters. It explains modern instrument types and the advantages and limitations of each. It shows how to choose the instruments you really need; how to understand instrument readings and put them to practical use;

how to work with fewer instruments, and how to put old instruments to new uses.

Over 60 instrument types discussed include everything from simple current and voltage meters to ohmmeters and V-O-M's; V-T volt-meters; power meters; impedance meters; capacitor checkers; inductance checkers; special-purpose bridges; oscilloscopes; R-F test oscillators; signal generators; audio test oscillators; R-F and A-F measuring devices; signal tracers; tube testers; grid-dip oscillators; TV sweep and marker generators; square wave generators; distortion meters and many others. It helps you work better—and saves you money.

Check **BASIC ELECTRONIC TEST INSTRUMENTS** in coupon for 10-day FREE examination

## Now! FIX ANY ELECTRIC MOTOR!

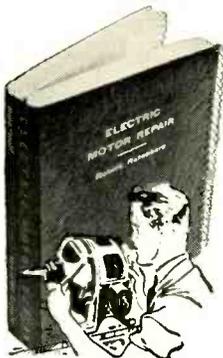

**TRAIN FOR BETTER PAY IN A FIELD THAT ISN'T CROWDED!**

so that you learn fast, easily and right. Every job is explained so clearly you can hardly fail to understand it. Over 125,000 copies in use in motor repair shops, schools, and for home study. Fully approved by repair specialists, unions and instructors.


It's the ideal book whether you want to train for a good-pay motor repair job or simply want to fix motors as a sideline or hobby!  
Order **ELECTRIC MOTOR REPAIR** in coupon.  
Price only \$6.95.

Handle ANY job from minor repairs to complete rewinding

560 pages—  
Over 900  
how-to-do-it pictures

It pays to train for something different! **ELECTRIC MOTOR REPAIR** is a complete guide that helps you cash in on this vast, rapidly growing field. Shows step by step how to handle all repair jobs (including complete rewinding) on practically ANY AC or DC motor or generator in common use—from fractional horsepower to giant industrial motors. Special duo-spiral binding brings text and related how-to-do-it diagrams side by side

## SHORT CUT TO TELEVISION REPAIRS

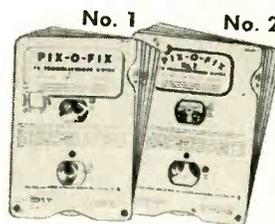

**Pix-O-Fix TV Trouble-Finder Guides**  
Only \$2 for the two

Eliminate useless testing . . . Fix sets twice as fast

Just turn the dial of the handy, pocket-size Ghirardi & Middleton **PIX-O-FIX TV Trouble-Finder Guide**. When the picture in the **PIX-O-FIX** window matches the screen image on the television set you're repairing . . . presto! . . . you've got your clue.

**PIX-O-FIX** then shows the causes of the trouble. Next it indicates the exact receiver section in which the trouble has probably happened. Then it gives step by step repair instructions.


The two **PIX-O-FIX** units No. 1 and No. 2 cover 48 different television troubles . . . just about anything you're likely to be called on to fix. No. 1 identifies 24 of the most common troubles and gives 192 causes and 253 remedies for them. No. 2 covers 24 more advanced troubles not included in No. 1. Together, they are a comprehensive guide to quick "picture analysis" servicing of any TV set . . . **AND THE PRICE IS ONLY \$2.00 for the two.** Money-back guarantee. Specify **PIX-O-FIX** in coupon.

USE COUPON FOR **10-day Free Trial!**

# TRAINING YOU NEED

in its most complete  
economical and  
easily understood form
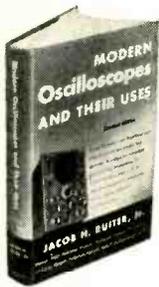
## Here's everything you need to know ABOUT OSCILLOSCOPES!



Complete data  
on getting the  
most out of  
the handiest,  
most versatile  
instrument  
of all!

Oscilloscopes are "gold mines" if you learn to use them fully on every job.  
**THIS BIG BOOK TEACHES YOU HOW!**

Here, in a big, revised 2nd edition, is THE book that really shows you how to get more work out of your oscilloscope. Clearly as A-B-C MODERN OSCILLOSCOPES AND THEIR USES gets right down to "brass tacks" in telling you exactly when, where and how. You learn to locate either AM or FM radio or television troubles in a jiffy. Even tough realignment jobs are made easy. No involved mathematics! Every detail is clearly explained—from making connections to adjusting circuit compo-

nents and setting the oscilloscope controls. And you learn to analyze patterns fast and RIGHT!

Includes latest data on quantitative measurements (the slickest method of diagnosing many color TV troubles and aligning sets properly); using 'scopes in industrial electronics, teaching... even in atomic energy work. Over 400 helpful pictures including dozens of pattern photos make things doubly clear. Price \$6.50.



Oscilloscope experts  
get the  
**BIG PAY jobs!**

Practice 10 days free. Order MODERN OSCILLOSCOPES in coupon.

## Cash in on HIGH-FI SERVICE and BUILDING



**HIGH FIDELITY TECHNIQUES**  
By  
John H. Newitt  
494 pages,  
203 illus.  
Price \$7.50


A complete guide to better High Fidelity methods and results

Get better results from "Hi-Fi" by having all the facts and latest ideas at your fingertips!

This big book brings you complete data on modern sound reproduction methods and equipment. It shows how to get better results at lower cost: how to build your own; how to service hi-fi equipment; discusses all details of components; compares different methods—AND IS CRAMMED FULL OF HOW-TO-DO-IT TIPS AND IDEAS.

Here are just a few of the many subjects! How to get the right hi-fi equipment for your needs: Hi-fi versus P.A. type speaker; Loudspeaker construction and performance; Adjusting bass-reflex cabinets; Controlling distortion; Getting rid of "hangover"; Selecting a woofer-tweeter; Sound-proofing materials; All about output transformers; Special hi-fi circuits; Ways to suppress noise; Negative feedback and how to use it; Amplifier construction hints; Minimizing tuner distortion; Avoiding chatter; Limiter-discriminator vs. ratio detector FM circuits; Avoiding record wear; Tips for custom builders; Bass-reflex charts; Acoustical horn design data; special installation problems; preamps and equalizers; pickup resonance; a novel horn system... and dozens of other subjects. Order High Fidelity Techniques in coupon today for 10-day FREE trial!

## HOW TO GET YOUR TICKET in a jiffy!

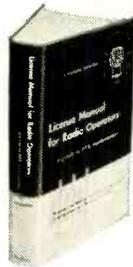

**LICENSE MANUAL for Radio Operators**

by  
J. R. Johnson  
(W2BDL)

A complete, practical study guide for getting your "ticket" as a well paid commercial operator.

Cash in on radio where the pay is best!


Get one of radio's best paying jobs—as a commercial operator aboard ship, in aviation, in broadcasting or telecasting and the many other places where an FCC license is a "must"!

LICENSE MANUAL FOR RADIO OPERATORS by J. R. Johnson is a quick, low-cost guide to help you breeze through FCC exams. Written so you can easily understand and remember it. Covers ALL EIGHT exam elements not just some of them. Reviews almost 2200 typical questions. Gives straight-to-the-point answers. Includes the changes in exam elements 1 and 2. Covers all data from electrical and radio fundamentals to navigation and related subjects.

**JOB OPPORTUNITY NEWS!** Under a new ruling, only holders of 1st or 2nd class radio-telephone licenses can do any work that affects the broadcasting of a transmitter. This is just one of many good job opportunities open to license holders!

Check LICENSE MANUAL FOR RADIO OPERATORS in coupon. Price only \$5.00

## DON'T THROW OLD RADIOS AWAY!

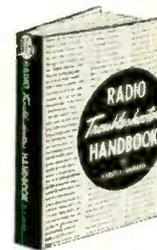

Covers every model made by 202 mfrs. from 1925 to 1942

Here's the data you need to fix old sets in a jiffy!

Just look up the how-to-do-it data on that troublesome old radio you want to fix.

Four times out of 5, this giant, 3 1/2-pound, 744-page Ghirardi RADIO TROUBLESHOOTER'S HANDBOOK tells what is likely to be causing the trouble... shows how to fix it. No useless testing. No wasted time. Using it, even beginners can easily fix old sets which might otherwise be thrown away because service information is lacking. With a few simple repairs,


most of these old sets can be made to operate perfectly for years to come.

### THE ONLY GUIDE OF ITS KIND!

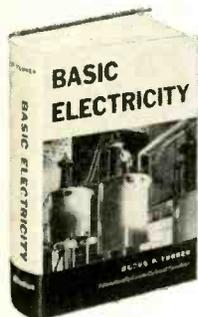**Cuts service time in half!**

Included are common trouble symptoms and their remedies for over 4,800 models of old home, auto radios and record changers. Airline, Apex, Arvin, Atwater Kent, Belmont, Bosch, Brunswick, Clarion, Crosley, Emerson, Fada, G.E. Kolster, Majestic, Motorola, Philco, Pilot, RCA, Silvertone, Sparton, Stromberg and dozens more. Includes hundreds of pages of invaluable tube and component data, service short cuts, etc.

Specify RADIO TROUBLESHOOTER'S HANDBOOK in coupon. Price only \$6.95. 10-day trial.



**BASIC ELECTRICITY**  
The most important training of all!

## HERE'S HOW TO GET AHEAD IN RADIO-ELECTRONICS

No matter what you want to do in radio-electronics, this brand new 396-page BASIC ELECTRICITY manual represents the most important training of all. Learn your basic electricity, learn it fully—then everything else in electronics, radio, TV, communications, hi-fi and all the rest comes 10 times as easy—because they're all based on the same fundamental electrical principles.

BASIC ELECTRICITY covers the entire field... from circuits and currents to electromagnetism... from polyphase to phone principles... from tubes to transistors... from batteries, instruments and measurements to motors, generators, transformers, and dozens of related subjects. More than 300 pictures make everything doubly clear. Set-up diagrams explain procedures. Basic electrical problems and their solutions are included. Then, to top your basic training off, the book includes a complete, easy-to-understand 61-page INTRODUCTION TO ELECTRONICS. Backed with this great training you'll read technical articles with new meaning. You'll know what's what about circuits and their components. Every detail of electrical-electronic operation will be far clearer to you than ever before! Price only \$6.50.

Check BASIC ELECTRICITY in coupon for 10-day Examination. See for yourself!

## TRY ANY BOOK 10 DAYS FREE!

Dept. RE-19, Rinehart & Company, Inc.  
232 Madison Ave., New York 16, N. Y.

Check here for MONEY-SAVING COMBINATION OFFER

...on Ghirardi's Radio & TV Receiver CIRCUITRY AND OPERATION, and Radio & TV Receiver TROUBLESHOOTING AND REPAIR. Price only \$13.00 for the two books plus postage. (Regular price \$14.25... you save \$1.25.) Payable at rate of \$4 (plus postage) after 10 days and \$3 a month for three months until \$13.00 has been paid. If not satisfactory, return books in 10 days and owe nothing.


Check here to order INDIVIDUAL BOOKS

Sent on 10 day free examination. For cash with order we pay postage—money-back guarantee. Otherwise postage extra.

- |   |  |
|---|--|
| <input type="checkbox"/> Radio & TV Receiver CIRCUITRY & OPERATION ...\$6.75      | <input type="checkbox"/> HIGH FIDELITY TECHNIQUES \$7.50               |
| <input type="checkbox"/> Radio & TV Receiver TROUBLESHOOTING & REPAIR \$7.50      | <input type="checkbox"/> MODERN OSCILLOSCOPES AND THEIR USES ...\$6.50 |
| <input type="checkbox"/> BASIC ELECTRONIC TEST INSTRUMENTS ...\$4.95              | <input type="checkbox"/> RADIO TROUBLESHOOTER'S HANDBOOK ...\$6.95     |
| <input type="checkbox"/> ELECTRIC MOTOR REPAIR ...\$6.95                          | <input type="checkbox"/> BASIC ELECTRICITY ...\$6.50                   |
| <input type="checkbox"/> PIX-O-FIX TROUBLE FINDER GUIDES (Nos. 1 and 2) ...\$2.00 | <input type="checkbox"/> LICENSE MANUAL for Radio Operators ...\$5.00  |

To order OUTSIDE U.S.A.—\$14.00 for money-saving combination offer. For all other books, add 50¢ each to above prices for handling through customs, etc. Sold for cash only. Any book may be returned in 10 days and money will be refunded.

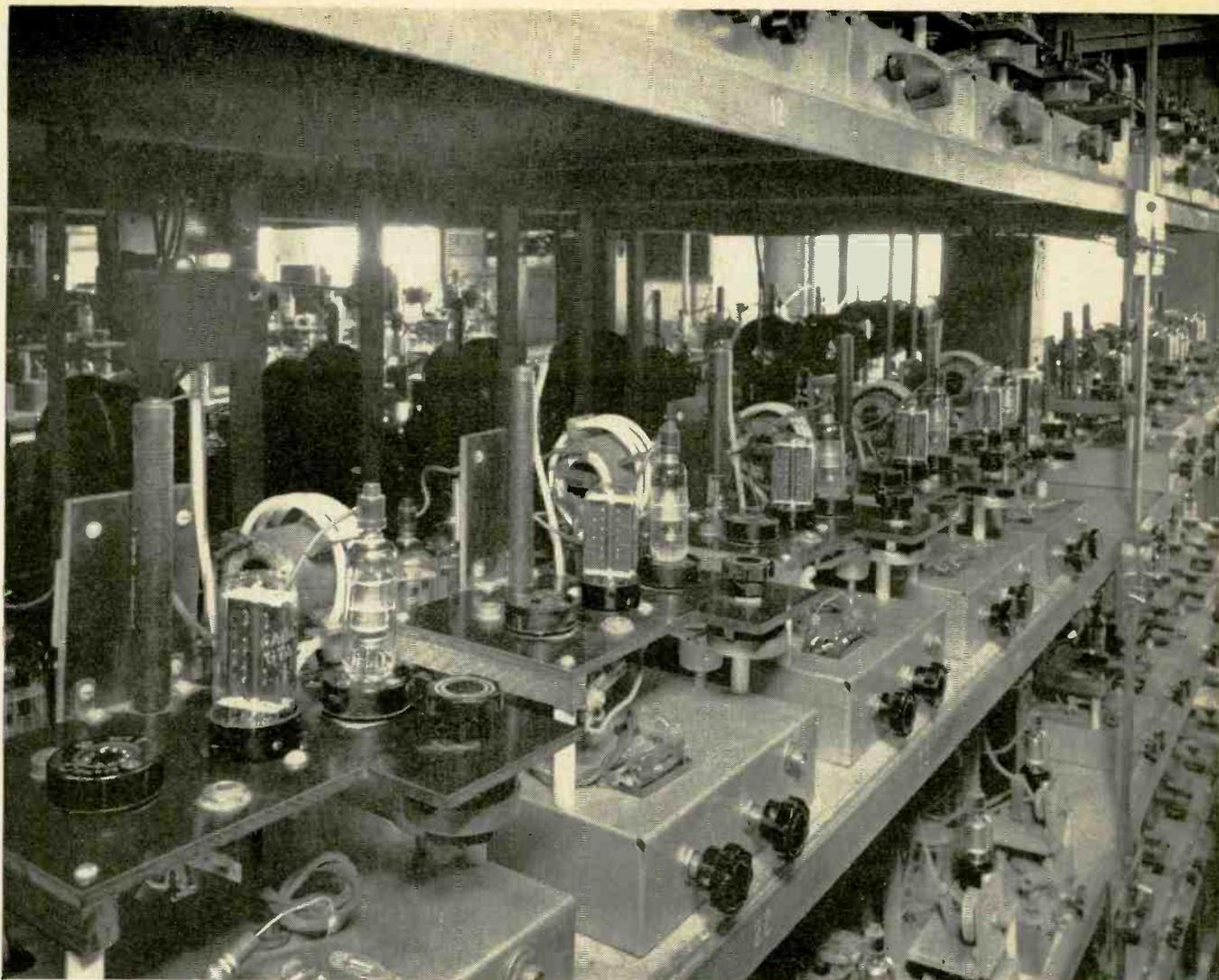Name \_\_\_\_\_  
Address \_\_\_\_\_  
City, Zone, State \_\_\_\_\_



## NEW CONTROLLED

# Dynamic Life Tests...

### ...ASSURE UNIVERSAL TUBE REPLACEMENTS

Testing tubes in sets is good . . . but not the best way. We life-check tubes dynamically in TV sets . . . in addition to many other extensive tests for materials, production, design and static life. But there are interaction problems in set testing which obscure the causes of tube failure. And some models of TV sets operate tubes conservatively. CBS-Hytron has, therefore, developed controlled dynamic life tests to examine all important characteristics under the most stringent TV set conditions.

### ...HELP PINPOINT AND CORRECT FAULTS

Day in, day out, tubes are cycled and checked under accelerated conditions at low (105 v) and high (140 v) line voltages. Components and dynamic operating conditions are controlled to point the finger unrelentingly at the exact nature of tube failures. They may be opens, shorts, gas, gradual deterioration of electrical characteristics, etc. Once the tests locate the fault, the correction is

invariably the same: improvement of tube design or manufacturing techniques.

**...CUT YOUR CALL-BACKS.** This new controlled dynamic life testing is your answer for dependable, universal replacement tubes for all TV sets. It is a big reason why CBS-Hytron tubes can cut your call-backs. Be sure to ask for CBS-Hytron tubes.



*More reliable products through  
Advanced-Engineering*



**CBS-HYTRON**, Danvers, Massachusetts  
A Division of Columbia Broadcasting System, Inc.

**STEREO  
STEREO  
AND  
MONAURAL**

the  
experts  
say...  
in HI-FI  
the best buys are



World-famous  
EICO advantages  
guarantee your complete satisfaction:


- Advanced engineering • Finest quality components
- "Beginner-Tested," easy step-by-step instructions
- LIFETIME service & calibration guarantee
- IN STOCK — Compare, then take home any EICO equipment—right "off the shelf"—from 1900 neighborhood EICO dealers.



Stereo Preamplifier HF85



FM Tuner HFT90

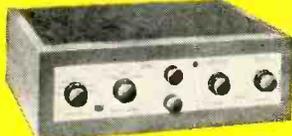

Stereo  
Amplifier-Preamp  
HF81



Monaural Integrated Amplifiers:  
50, 30, 20, and 12-Watt  
(use 2 for Stereo)



Bookshelf  
Speaker System  
HFS1



Speaker System HFS2  
36" H x 15 1/4" W x 11 1/2" D



Monaural Power Amplifiers:  
60, 50, 35, 30, 22 and 14-Watt  
(use 2 for Stereo)

Monaural Preamplifiers:  
HF65, HF61  
(stack 2 for Stereo)



Over 1 MILLION EICO Instruments in use throughout the world.

**NEW STEREOPHONIC EQUIPMENT**

**HF85: Stereo Dual Preamplifier** is a complete stereo control system in "low silhouette" design adaptable to any type of installation. Selects, preamplifies, controls any stereo source—tape, discs, broadcasts. Superb variable crossover, feedback tone controls driven by feedback amplifier pairs in each channel. Distortion borders on unmeasurable even at high output levels. Separate lo-level input in each channel for mag. phono, tape head, mike. Separate hi-level inputs for AM & FM tuners & FM Multiplex. One each auxiliary A & B input in each channel. Independent level, bass & treble controls in each channel may be operated together with built-in clutch. Switched-in loudness compensator. Function Selector permits hearing each stereo channel individually, and reversing them; also use of unit for stereo or monophonic play. Full-wave rectifier tube power supply. 5-12AX7/ECC83, 1-6X4. Works with any 2 high-quality power amplifiers such as EICO, HF14, HF22, HF30, HF35, HF50, HF60. Kit \$39.95. Wired \$64.95. Includes cover.

**HF81: Stereo Dual Amplifier-Preamplifier** selects, amplifies & controls any stereo source—tape, discs, broadcasts—& feeds it thru self-contained dual 14W amplifiers to a pair of speakers. Monophonically: 28 watts for your speakers; complete stereo preamp. Ganged level controls, separate focus (balance) control, independent full-range bass & treble controls for each channel. Identical Williamson-type, push-pull EL84 power amplifiers, excellent output transformers. "Service Selector" switch permits one preamp-control section to drive the internal power amplifiers while other preamp-control section is left free to drive your existing external amplifier. Kit \$69.95. Wired \$109.95. Incl. cover.

**MONAURAL PREAMPLIFIERS (stack 2 for Stereo)**  
**NEW HF65:** superb new design. Inputs for tape head, microphone, mag-phono cartridge & hi-level sources. 1M distortion 0.04% @ 2V out. Attractive "low silhouette" design. **HF65A** Kit \$29.95, Wired \$44.95. **HF65** (with power supply) Kit \$33.95. Wired \$49.95.

**HF61:** "Rivals the most expensive preamps" — Marshall, AUDIOCRAFT. **HF61A** Kit \$24.95, Wired \$37.95, **HF61** (with power supply) Kit \$29.95. Wired \$44.95.

**MONAURAL POWER AMPLIFIERS**  
(use 2 for STEREO)

**HF60:** 60-Watt Ultra Linear Power Amplifier with Acro TO-330 Output Xfmr.; "One of the best-performing amplifiers extant; an excellent buy." AUDIOCRAFT Kit Report. Kit \$72.95. Wired \$99.95. Cover E-2 \$4.50.

**HF50:** 50-Watt Ultra Linear Power Amplifier with extremely high quality Chicago Standard Output Transformer. Identical in every other respect to HF60, same specs at 50W. Kit \$57.95. Wired \$87.95. Cover E-2 \$4.50.

**NEW HF35:** 35-Watt Ultra-Linear Power Amplifier. Kit \$47.95. Wired \$72.95. Cover E-2 \$4.50.

**HF30:** 30-Watt Power Amplifier. Kit \$39.95. Wired \$62.95. Cover E-3 \$3.95.

**NEW HF22:** 22-Watt Power Amplifier. Kit \$38.95. Wired \$61.95. Cover E-2 \$4.50.

**NEW HF14:** 14-Watt Power Amplifier. Kit \$23.50. Wired \$41.50. Cover E-6 \$4.50.

**MONAURAL INTEGRATED AMPLIFIERS**  
(use 2 for STEREO)

**HF52:** 50-Watt Integrated Amplifier with complete "front end" facilities & Chicago Standard Output Transformer. "Excellent value"—Hirsch-Houck Labs. Kit \$69.95. Wired \$109.95. Cover E-1 \$4.50.

**HF32:** 30-Watt Integrated Amplifier. Kit \$57.95. Wired \$89.95. Both include cover.

**HF20:** 20-Watt Integrated Amplifier. "Well-engineered" — Stocklin, RADIO TV NEWS. Kit \$49.95. Wired \$79.95. Cover E-1 \$4.50.

**HF12:** 12-Watt Integrated Amplifier. "Packs a wallop"—POP. ELECTRONICS. Kit \$34.95. Wired \$57.95.

**SPEAKER SYSTEMS (use 2 for STEREO)**

**HFS2:** Natural bass 30-200 cps via slot-loaded 12-ft. split conical bass horn. Middles & lower highs: front radiation from 8 1/2" edge-damped cone. Distortionless spike-shaped super-tweeter radiates omni-directionally. Flat 45-20,000 cps, useful 30-40,000 cps. 16 ohms. HWD 36", 15 1/4", 11 1/2". "Eminently musical; would suggest unusual suitability for stereo."—Holt, HIGH FIDELITY. Completely factory-built: Walnut or Mahogany. \$139.95; Blonde, \$144.95.

**HFS1:** Bookshelf Speaker System, complete with factory-built cabinet. Jensen 8" woofer, matching Jensen compression-driver exponential horn tweeter. Smooth clean bass; crisp extended highs. 70-12,000 cps range. Capacity 25 w. 8 ohms. HWD: 11" x 23" x 9". Wiring time 15 min. Price \$39.95.

**FM TUNER**

**HFT90:** surpasses wired tuners up to 3X its cost. Pre-wired, pre-aligned, temperature-compensated "front end" — drift-free. Precision "eye-tronic" tuning. Sensitivity 1.5 uv for 20 db quieting — 6X that of other kit tuners. Response 20-20,000 cps ±1 db. K-follower & multiplex outputs. "One of the best buys you can get in high fidelity kits." — AUDIOCRAFT KIT REPORT. Kit \$39.95\*. Wired \$65.95\*. Cover \$3.95.

**BEFORE YOU BUY, COMPARE:**

You may examine the complete EICO line at any of 1900 neighborhood EICO distributors coast to coast. Compare critically with equipment several times the EICO cost — then you judge. You'll see why the experts recommend EICO, kit or wired, as your best buy.

EICO, 33-00 NORTHERN BLVD., L. I. C. 1, N. Y.  
Fill out coupon on other side for FREE CATALOG

Copyright 1958 by Electronic Instr. Co., Inc. 33-00 N. Blvd., L. I. C. 1, N. Y.

Add 5% in the West.

\* LESS COVER, F. C. T. INCL.

the specs prove it . . .  
your BEST BUY is

**EICO**®

for COLOR & Monochrome TV servicing

**FREE CATALOG**

shows you HOW TO SAVE 50%  
on 50 models of top quality  
professional test equipment.  
**MAIL COUPON NOW!**




**NEW!**  
TV-FM SWEEP  
GENERATOR &  
MARKER #368  
KIT \$69<sup>95</sup> WIRED \$119<sup>95</sup>

Entirely electronic sweep circuit (no mechanical devices) with accurately-biased inductor for excellent linearity. Extremely flat RF output: new AGC circuit automatically adjusts osc. for max. output on each band with min. ampl. variations. Exceptional tuning accuracy: edge-lit hairlines eliminate parallax. Swept Osc. Range 3-216 mc in 5 fund. bands. Variable Marker Range 2-75 mc in 3 fund. bands; 60-225 mc on harmonic band. 4.5 mc Xtal Marker Osc., xtal supplied. Ext. Marker provision. Sweep Width 0-3 mc lowest max. deviation to 0-30 mc highest max. dev. 2-way blanking. Narrow range phasing. Attenuators: Marker Size, RF Fine, RF Coarse (4-step decade). Cables: output, 'scope horiz., 'scope vertical. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

**NEW! RF  
SIGNAL GENERATOR  
#324**  
KIT \$26<sup>95</sup> WIRED \$39<sup>95</sup>



150 kc to 435 mc with ONE generator! Better value than generators selling at 2 or 3 times its cost! Ideal for IF-RF alignment, signal tracing & trouble-shooting of TV, FM, AM sets; marker gen.; 400 cps audio testing; lab. work. 6 fund. ranges: 150-400 kc, 400-1200 kc, 1.2-3.5 mc, 3.5-11 mc, 11-37 mc, 37-145 mc; 1 harmonic band 111-435 mc. Freq. accurate to ±1.5%; 6:1 vernier tuning & excellent spread at most important alignment freqs. Etched tuning dial, plexi-glass windows, edge-lit hairlines. Colpitts RF osc. directly plate-modulated by K-follower for improved mod. Variable depth of int. mod. 0-50% by 400 cps Colpitts osc. Variable gain ext. amplifier: only 3.0 v needed for 30% mod. Turret-mounted coils slug-tuned for max. accuracy. Fine & Coarse (3-step) RF attenuators. RF output 100,000 uv; AF sine wave output to 10 v. 50-ohm output Z. 5-way jack-top binding posts for AF in/out; coaxial connector & shielded cable for RF out. 12AU7, 12AV7, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet.

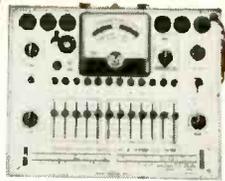

**NEW! DYNAMIC  
CONDUCTANCE  
TUBE & TRANSISTOR  
TESTER #666**  
KIT \$69<sup>95</sup> WIRED \$109<sup>95</sup>

**COMPLETE with steel cover and handle.**  
SPEED, ease, unexcelled accuracy & thoroughness. Tests all receiving tubes (and picture tubes with adapter). Composite indication of Gm, Gp & peak emission. Simultaneous sel of any 1 of 4 combinations of 3 plate voltages, 3 screen voltages, 3 ranges of continuously variable grid voltage (with 5% accurate pot). New series-string voltages: for 600, 450, 300 ma types. Sensitive 200 ua meter. 5 ranges meter sensitivity (1% shunts & 5% pot). 10 SIX-position lever switches: freepoint connection of each tube pin. 10 pushbuttons: rapid insert of any tube element in leakage test circuit & speedy sel. of individual sections of multi-section tubes in merit tests. Direct-reading of inter-element leakage in ohms. New gear-driven rollechart. Checks n-p-n & p-n-p transistors: separate meter readings of collector leakage current & Beta using internal dc power supply. Deep-etched satin aluminum panel; rugged grey wrinkle steel cabinet. CRA Adapter \$4.50




**COLOR  
and Monochrome  
DC to 5 MC LAB & TV  
5" OSCILLOSCOPE  
#460**  
KIT \$79<sup>95</sup> WIRED \$129<sup>50</sup>  
• Features DC Amplifiers!

Flat from DC-4.5 mc, usable to 10 mc. VERT. AMPL.: sens. 25 rms mv/in; input Z 3 megs; direct-coupled & push-pull thruout; K-follower coupling bet. stages; 4-step freq-compensated attenuator up to 1000:1. SWEEP: perfectly linear 10 cps-100 kc (ext. cap. for range to 1 cps); pre-set TV V & H positions; auto. sync. ampl. & lim. PLUS: direct or cap. coupling; bal. or unbal. inputs; edge-lit engraved lucite screen; dimmer; filter; bezel fits sid photo equipmt. High intensity trace CRT. 0.06 usec rise time. Push-pull hor. ampl., flat to 400 kc, sens. 0.6 rms mv/in. Built-in volt. calib. Z-axis mod. Sawtooth & 60 cps outputs. Astig. control. Retrace blanking. Phasing control. 5" PUSH-PULL Oscilloscope = 425: Kit \$44.95, Wired \$79.95. 7" PUSH-PULL Oscilloscope = 470: Kit \$79.95, Wired \$129.50.



**NEW! PEAK-to-PEAK  
VTVM #232 & UNI-  
PROBE (pat. pend.)**  
KIT \$29<sup>95</sup> WIRED \$49<sup>95</sup>

Half-turn of probe tip selects DC or AC-Ohms. Uni-Probe - exclusive with EICO - only 1 probe performs all functions! Latest circuitry, high sensitivity & precision, wide ranges & versatility. Calibration without removing from cabinet. New balanced bridge circuit. High Z input for negligible loading. 4 1/2" meter, can't burn-out circuit. 7 non-skip ranges on every function. 4 functions: +DC Volts, -DC Volts, AC Volts, Ohms. Uniform 3 to 1 scale ratio for extreme wide-range accuracy. Zero center. One zero-adj. for all functions & ranges. 1% precision ceramic multiplier resistors. Measure directly peak-to-peak voltage of complex & sine waves: 0-4, 14, 42, 140, 420, 1400, 4200. DC/RMS sine volts: 0-1.5, 5, 15, 50, 150, 500, 1500 (up to 30,000 v with HVP probe & 250 mc with PRF probe). Ohms: 0.2 ohms to 1000 megs. 12AU7, 6AL5, selenium rectifier; xmfr-operated. Deep-etched satin aluminum panel, rugged grey wrinkle steel cabinet.

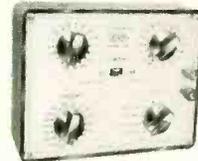


**New!**  
Series/Parallel  
R-C COMBINATION  
BOX #1140  
KIT \$13.95  
WIRED \$19.95



**TUBE TESTER  
#625**  
KIT \$34.95  
WIRED \$49.95  
• tests 600  
mil series  
string type  
tubes  
• illuminated  
roll-chart


Pix Tube Test Adapter .....\$4.50

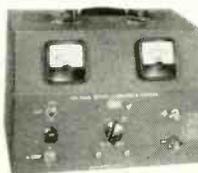

**6V & 12V BATTERY  
ELIMINATOR  
& CHARGER #1050**  
KIT \$29.95  
WIRED \$38.95  
Extra-filtered for  
transistor equipmt.  
#1060 KIT \$38.95  
WIRED \$47.95



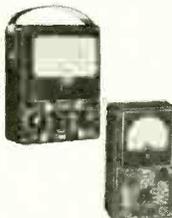**New!**  
Miniaturized  
MULTI-SIGNAL  
TRACER #145A  
KIT \$19.95  
WIRED \$28.95



**20,000 Ohms/Volt  
V-O-M #666**  
KIT \$24.95  
WIRED \$29.95



**1000 Ohms/Volt  
V-O-M  
#536**  
KIT \$12.90  
WIRED \$14.90



Reads 0.5 ohms  
-500 megs, 10  
mmd-5000 mfd,  
power factor.

**R-C BRIDGE & R-C-L COMPARATOR  
#950B**

**VTVM PROBES** KIT WIRED  
Peak-to-Peak .....\$4.95 \$6.95  
RF .....\$3.75 \$4.95  
High Voltage Probe-1 .....\$6.95  
High Voltage Probe-2 .....\$4.95  
**SCOPE PROBES**  
Demodulator .....\$3.75 \$5.75  
Direct .....\$2.75 \$3.95  
Low Capacity .....\$3.75 \$5.75

EICO, 33-00 Northern Blvd.,  
Long Island City 1, N. Y. **C-1**  
Show me HOW TO SAVE 50% on  Test Instru-  
ments  Hi-Fi  Ham Gear. Send me FREE  
Catalog and name of neighborhood dealer.

Name.....  
Address.....  
City..... Zone..... State.....

TURN PAGE  
FOR MORE  
EICO VALUES

**EICO**®

Send for  
**FREE CATALOG**  
now

Prices 5% higher on West Coast.

33-00 Northern Blvd., Long Island City 1, N.Y.

# STORED TELEVISION RECEPTION

... *Television Receivers' Next Great Advance—Home Recorders...*

THE next great advance in home television receivers will no doubt be *stored or recordtelevision*. The year 1958 has seen an important breakthrough in magnetically taped-recorded programs. Now used by many of our television broadcast stations, tape recording enables them to record any program for later rebroadcasting. It took many years to develop this important new advance, but the cost of recording such television broadcasts on magnetic tape is fantastically high. The necessary equipment costs over \$45,000. Obviously, only well financed stations can afford it. The tape on which the program is recorded is expensive, too, because an hour's recording runs into no less than 4,500 feet of 2-inch-wide tape. In addition, the video track is recorded on the tape *laterally*—from side to side—by four recording heads which revolve at the unusually high speed of 14,400 revolutions per minute. In a single second they make a recorded track of 320 feet. In 1 hour the 10-mil-wide track would be 207 miles long! For these reasons, home-television recording at the moment, for economic reasons, is only a dream.

Yet all engineers, as well as the public, agree that home-recorded television reception is a *must* for the future, for many reasons. We are not always home to view an important program. Or we may be otherwise occupied, or it is not convenient to view it. Or there may be two or more other important programs on, which we cannot possibly view at the same time. Or one person wishes to see one program while another desires a different one.

What is the answer? It is plain that present-day recording technique is out of the question for home television. We can neither use rotating disks, which would have to be 10 or 12 feet in diameter to record a single TV program, nor expensive magnetic tape by the mile. And these—outside of the even more costly photographic film—are about all the technical means at our disposal today when it comes to recording.

It will be noted further that in ALL present-day recording, we always use mechanical means—*something speeds past a given recording point*. It also must move mechanically at a certain speed *in time*.

Yet there are other means which have been in use for hundreds of millions of years. We may call them electronic, although in reality they are electro-chemical-biologic. Nevertheless, they work perfectly; neither are they mechanical, nor does anything "move" in the strict definition of that term. Let us take an example: you have a long vivid dream. You wake up and for half an hour you tell your wife all about that dream and all the hundreds of various experiences that you had, what you saw, what was said, etc. Or you see a good movie. Weeks or months later you can at will recall all the visual impressions, practically every scene; you can also recall the faces of the actors, as well as their talk.

All this—and millions of other impressions, ever since you were a few years old—is recorded almost indelibly in the memory part of your brain, ready to be "played back" at an instant. No cumbersome machinery here, nothing that "moves" mechanically. The microscopic nerve ends and the *neurons* of your brain do the recording. Scientists believe that all such recording is effected by electrochemical means and that the recall—the "playback"—is by similar means. While we stand in awe of these, to us, miraculous biological wonders, it is certain that scientists sooner or later will hit on the counterpart of our memory mechanics.

Indeed, we have made an excellent beginning in this direction. Electronic engineers have already designed the very intricate magnetic memories now in use in electronic computers—the so-called electronic brains. Certain of these magnetic memories are fashioned of thin wire screening. Wherever wires cross, there is a tiny magnet—a small ferrite ring locked around the intersection. Such an assembly a few inches square can store myriads of bits of information which the computer scans electronically, when it wishes to recall certain information. In this respect it works amazingly like its counterpart: the human brain.

From such a beginning we may be certain that in the not-too-distant future it will be possible to evolve purely electronic means of storing television home programs.

Can we *store* electrical impulses electronically, *non-mechanically*, without moving tapes or revolving disks? I think so. You can, for instance, charge a large-capacitance capacitor with a weak continuous electrical current, then discharge it slowly. You can also store electricity electrochemically in a storage battery, and much later withdraw its electrical energy over a certain length of time. Here, too, nothing moves mechanically.

Better yet—as an analogy—you can send television impulses to the planet Mars at its nearest opposition, 35 million miles. They take 3 minutes 10 seconds to reach Mars. The signals now bounce back in another 3 minutes 10 seconds. Hence, you "stored" the signals for over 3 minutes. Nothing moved mechanically. (Memories that work on the same principle are used in some computers.)

I can imagine a future, very sophisticated electronic memory, perhaps a combination magnetic memory integrated with an *electret*. (The latter is a permanently polarized piece of dielectric material and is a direct counterpart or analog of a magnet.)\*

With such a combination (or a similar one), I believe a simplified method of home television recording can be produced in due time.

As the impulses of the television picture come in, *they must be recorded and stored successively in time*. If this were not done, all impulses would be piled on top of each other; remember, *nothing moves in this future electronic memory*. (Present-day computer memories record on moving drums.) Thus, in our future electronic-delayer memory, it is possible to *record in time*. When we wish to play back the television recording, we have only to flip a switch which turns on the electric current. The electronic-delayer memory—EDM for short—will then faithfully reproduce the program.


As with all present recorders, the EDM will play back the recording as often as desired. If a new recording is wanted, the old one will be electronically erased, as magnetic tapes now are.

Undoubtedly, the first EDM's will be expensive. But when mass-produced, the price should be within reason. If the device is finally perfected, I am certain that every television set will have an electronic-delayer memory built into it as a necessary accessory.

Obviously, too, all receivers will have to be equipped with special clocks that can be set to record a number of programs as much as a week ahead. These programs can then be released at a desired later date.

—H.G.

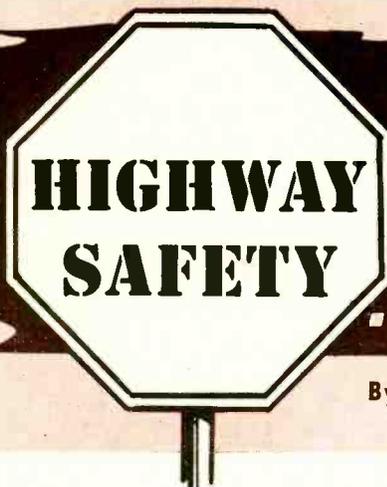\* See RADIO-ELECTRONICS for electret information. "Frozen Electricity, the Electret," *Radio-Craft*, November, 1945; "Electret Construction," *Radio-Craft*, May, 1948; "Improved Electrets," RADIO-ELECTRONICS, April, 1949; "Electret Behavior," RADIO-ELECTRONICS, May, 1949.



*Spurred by rising slaughter on highways, the electronic and automotive industries have been given the green light to eliminate the factor of human error through electronics—and to proceed full speed toward automatic highways and self-driving cars*

## ..Challenge to Electronics

By **DAVID LACHENBRUCH**

ASSOCIATE EDITOR

**T**HE sign at the roadside has one word on it: "Automatic." You relax your grip on the steering wheel, and as you feel the automatic control take over, you release it entirely.

You swivel the driver's seat until you're facing the TV set, and you lean back and prepare to be entertained—while your car neatly maneuvers the cloverleaf approach to the expressway.

By the time you've found a program worth watching, your car has slowed to about 10 miles an hour to pass through the unmanned scanning booth, which makes a quick remote check of the electronic and mechanical equipment of your vehicle and jots down your license number for your toll-highway bill at the end of the month. (Of course, if your credit's no good, they'll put the bite on you at the exit.)

While you watch TV, eat lunch or doze, you traverse the automatic highway at a steady speed, passing the few slower vehicles and slowing down at trouble spots. It's a safe, sunny day, so the autodrive sticks to the 80-mile-an-hour speed limit.

Suddenly you're startled out of your reverie by an insistent beeping tone. You swivel your seat to manual-drive position and prepare to take over.

After the exit scanning booth, you grip the wheel, although you know the autodrive will be on until you have reached the end of the cloverleaf interchange. You pass the parking plaza where a score of cars have been neatly and automatically beached until their drivers regain sufficient alertness for the chore of manual driving.

### How far-fetched is it?

This science-fictionesque version of a Sunday drive is based on research and development already well under way by some of the top electronic and automotive companies. Their engineers won't even speculate when you might be able to take such a drive—but they agree that the day must come, and the sooner the better.

Now let's take another hypothetical Sunday drive—one which uses electronic controls to a more limited extent.

Heeding the call of the open road, you load the family into the car and head for the countryside. But first, there's Main Street to be crossed—and, of course, the traffic light is red. As your car passes under an overhead radar sampler, a pulse is sent to a central computer which is continually measuring traffic flow and controlling light-

change cycles at major intersections.


The green light flashes on and you release the brake. But without warning you get the red light again. Then you hear a siren and a fire engine roars past the intersection—its radio signals changing each traffic light to red for a distance of a block ahead.

Finally you head for open country. To get information on road conditions, you turn on the electronic congestion warning system. A few twists of the knob and you hear the traffic bulletin: "Route 78 is overcrowded, traffic moving slowly." You revise your plans and head for the toll superhighway.


You enter the "correct change lane" at the toll booth, dropping your coins into a receptacle. Your money is electronically counted and the signal changes from red to green.

Once on the superhighway, your car is surveyed by closed-circuit TV cameras mounted on overpasses while a traffic specialist in a distant control room watches a bank of TV monitors for possible tie-ups. You pass a sign which says "Highway Patrolled by Radar" and subconsciously you let up a little on the accelerator.

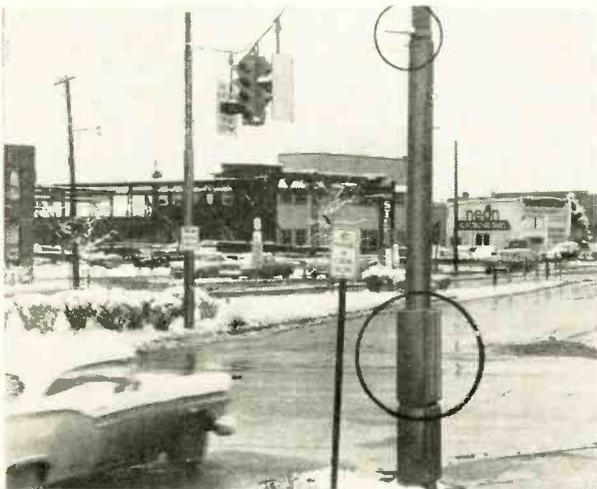Soon it's early evening and you're heading home. The photocell-activated



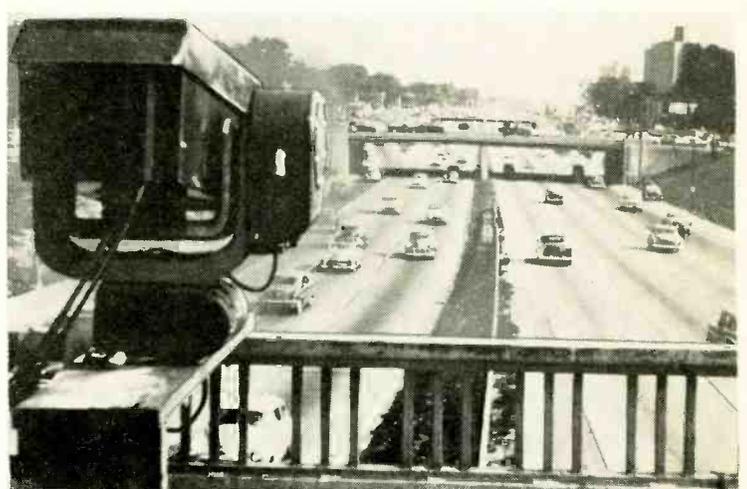Radio replaces cable in traffic-light system. Receiving antenna (upper circle) is cut to 450-mc carrier frequency. Tone translator (lower circle) responds to combinations of audio tones, keying signal-change cycles.



Closed-circuit TV scans a Detroit expressway in recent test. A more extensive experiment is planned, using 33 cameras to patrol an eight-mile stretch. Roadside warning and detour signs will be activated from a central control room.

highway lights flick on and you turn on your headlights, kicking the foot-switch to be sure the electronic headlight dimmer is in action.

Finally home, you wait wearily while the garage-door opener responds to the transmitter in your car.

A Sunday drive of the future? Not at all. All of the electronic devices mentioned are in use now on the streets and highways of America. (For the sake of giving this little excursion a happy ending, one of them—two-way police radio—was left unmentioned.)

#### Preview of coming attractions

Simple as today's highway electronic devices may be, they are the forerunners of systems which eventually will lead to auto automation.

The radar-actuated traffic light system will lead to a whole array of electronic intersection controls which will stop and start your car automatically at busy corners. The fire engine's radio transmitter some day will control the actions of nearby automobiles.

The only piece of electronic equipment currently in most automobiles—the radio—will become an important part of the electronic safety system. Special transmitters along the roadway or carried by traffic policemen will relay warnings and verbal instructions directly to the driver, through his radio, whether it's turned off or on.

The electronic coin counter is an early step toward the automatic toll booth and safety inspection station. Closed-circuit TV installations on superhighways will lead to full-scale traffic surveillance systems which adjust the speed and routing of traffic to road and congestion conditions.

The police radar is a precursor of a whole complex of remotely controlled traffic violation detectors. The electronic headlight dimmer actually is the first detection-warning-control mechanism inside the car itself.

#### The "compatible" approach

Compared to many other fields, today's use of electronics in auto safety is crude and elementary. Yet the very factor which makes electronic safety measures so necessary is also the biggest barrier to their development and use—the tremendous number of cars on the road and the astronomical amount of highway miles in the United States. Since an automated traffic system will require equipment both in the car and on the road, it obviously isn't an overnight proposition.

Most traffic engineers agree on the three-step "compatible" approach to electronic driving devices. The first step is the installation of electronic warning devices in the highway, with roadside "indicators," which may be used to warn and inform drivers of cars which have no electronic control equipment in them.

The second step is to move the "indicators" into the car—in other words, new audible and visual warning and in-

formation instruments within the car would be activated from electronic equipment in the road.

The third stage would be automatic control—cars equipped with small computers and servos would be driven automatically in response to the same signals which activate the roadside and within-the-car indicators. In this way, the nonequipped, partially equipped and the completely equipped cars could be "instructed" by the same highway electronic system.

Don't get the idea that the automatic highway is only a dream. Under a grant from the AAA Foundation for Traffic Safety, the nation's top traffic and highway officials were brought together with engineers from leading electronics companies in a recent meeting. The purpose: to get automatic electronic devices off the drawing board and onto the road.

The traffic officials told the electronics industry, in effect: "We want foolproof electronic safety equipment and we want it in a hurry." A permanent organization was established to get automatic and semi-automatic highway systems into full-scale testing as soon as possible.

#### Highway tests conducted

One automatic system has already had some practical testing under highway conditions. This is the much publicized RCA system, under development for many years by a laboratory team working under famed RCA honorary vice president Dr. Vladimir Zworykin in cooperation with the General Motors Research Lab.

All three stages of this compatible system have been demonstrated by RCA and GM. It requires the installation of rf-carrying cables and loops under the road.

An installation was made in a 400-foot curved strip of new public highway near Lincoln, Neb., last year. A car equipped with special indicators was driven over the strip with its windshield covered; at the same time, conventional nonequipped cars were warned by lights along the road.

Using either the instruments within

the special car or the lights along the highway, the drivers of cars on this stretch were informed electronically whether they were following another vehicle too closely, whether there was an obstacle on the road ahead, and at the same time were accurately guided along the traffic lane.

A modified version of this system is permanently installed in the entrance roadway of RCA's Princeton, N. J., laboratories. This one is strictly a speed analyzer which activates an electric warning sign when drivers exceed the speed limit.

While RCA works on equipment for electronic highways, General Motors is developing gizmos for automatic operation of the car itself. A mile-long test road at GM's Technical Center in Warren, Mich., is equipped with a buried guidance cable similar to the one installed in Nebraska, and a 1958 Chevrolet has been rigged up with a relatively simple glove-compartment computer and servo mechanism which completely takes over the steering function. GM hasn't yet demonstrated other features of the RCA system, such as automatic braking and maintenance of distance between cars.

Much more imminent than the automatic highway are anti-collision proximity devices installed in the car itself—"vehicular radar." Lots of progress has been made in this field in the last few years, and you may be able to select radar as an "option" with your next car. It should be available within the next five years.

At least two such systems have been extensively field-tested. General Motors, which has installed a "prox" system on one of its "cars of the future", is understood to be making production plans for it. Bendix Aviation Corp. has a production-ready radar system which it is now trying to sell to auto manufacturers.

Both systems will be described in a subsequent article in this series.

The idea of self-steering and radar-equipped cars isn't new, of course. A patent was issued in 1937 to A. W. Braun for an electronically controlled highway system in which cars would straddle a white line painted on the

**Semi-automatic control system is demonstrated near Lincoln, Neb. Buried cables and loops detect and respond to passage of vehicles. Roadside lamps light as each car passes over detector loops. Special receiver in the test car (left) picks up warning signals generated by car ahead. Unequipped cars use roadside lights as guide to obstacles ahead or around curves.**





As the driver lights a cigarette, a specially equipped test car is steered around a 1-mile General Motors test track by a magnetic path produced by a buried cable. Tuned pickup coils on the car's front bumper (left) feed voltage variations to a computer in the glove compartment which commands servos to activate the power steering unit and keeps the car on the center of the magnetic path.

highway (instead of a radiating cable) and keep on course with bumper mounted photocells which would actuate an automatic steering system similar to that used by RCA and GM. In 1947, Hugo Gernsback wrote in his annual Christmas booklet of an "electronic robot-steered car," elaborating on this white-line guidance system and incorporating radar to apply the brakes automatically when approaching within 50 feet of the car ahead.

What is new is the exhaustive research and testing now underway by large electronic and automotive firms to transform the idea of the automatic highway into a reality. Field-testing of new and as yet unpublicized electronic auto safety devices is in progress.

#### Wanted: more information

What will these devices do? The best bet is that they'll be designed to keep drivers better informed of what's going on in and around the car.

When you're at the wheel of your V8, you simply don't have enough information to be a safe driver. So says Minnesota state traffic engineer J. E. Darrell. One reason for the fantastically high accident toll, he says, is that we're driving our cars by guess and by gosh. To be a safe driver, you ought to know the answers to these questions at all times, without taking your eyes from the road:

- Is your car operating speed safe for the highway, traffic and weather conditions?
- Are you within the speed limit?
- Do you have enough gas to reach the next filling station?
- Are there any cars approaching you from the rear or at an angle?
- Can you safely pass that car ahead?
- If you pass the bunched-up group of cars ahead of you, will you find open road ahead?
- What's over that hill or around that curve?

- Are you falling asleep?
- How often is this highway patrolled in case of a breakdown?
- Are there excessive carbon monoxide fumes in the car?

How to give you this dashboard encyclopedia is only part of the challenge the highway engineers have flung at the electronics industry—the first part, the "nonautomatic" part.

Or, as another expert—Houston, Tex., traffic director Eugene Maier—put it, your car should be equipped with these lifesaving gadgets the sooner the better, long before you get to take that ride on the automatic highway:

- A device which moves the traffic lights into your car, telling you that you're coming to an intersection and you'll have to stop—or else that you'll be able to clear it without stopping.
- Another one which will tell you when a car is approaching from a cross street.

• A gadget that will warn you that you're in the wrong lane or too close to the edge of the road.

He also wants to equip traffic cops with short-range radio transmitters to relay instructions directly to you via your car radio.

And pedestrians would carry or wear devices which transmit some kind of warning signal to tell you they're crossing the street.

Any one of these systems lends itself to the compatible approach—an information system first and later an automatic car-driving system.

#### Outside the car

Long before automatic cars travel automatic highways, we can begin automating our superhighways to make them safe. A New Jersey Turnpike traffic engineer wants his heavily traveled superhighway to have these automatic devices soon:

- Warning signs which can be changed from a remote control point to indicate speed limits, detours,

weather or congestion conditions. Such a system, coupled with closed-circuit TV traffic monitors, is now being installed on a Detroit expressway.

- A remote "congestion detector," which would spot traffic tie-ups and automatically report them to the control room.

- A remote speed and traffic recorder.

- An automatic "unsafe car detector" which would inspect tires, lights and brakes as cars pass through the toll gate, and automatically bar unsafe ones from the turnpike.

#### What the police want

And then there are the police. They want the long arm of the law to reach right into your car-of-the-future.

They've proposed some gadgets which smack of "Big Brother" snooping. Though they're all within the realm of electronic possibility, it's doubtful whether the public would stand for some of them.

Most involve some type of recorder locked into the car to keep a record of the driver's transgressions. Bus and truck lines now use speed recorders which keep permanent records, and the proposed devices would elaborate on this technique and extend it to the passenger car.

One proposal is a "speed monitor." Here's how it might be used:

You hear the ominous sound of a police siren and pull over to the curb. "Okay, buddy," says the cop. "Let's see your speed monitor."

You sheepishly remove a continuous loop of magnetic tape from a dash compartment. The officer takes it to his car and plays it back, reading your exact speeds of the last five minutes on his own speedometer.

Another version of this device incorporates a mother-in-law effect which "initiates a persistent raucous sound" to warn you that it's recording a speed violation.

A third proposed monitor would be encased in a sealed cartridge and keep a permanent record of traffic violations—such as crossing a "no-passing" line. This would be inspected yearly by the police.

While it's unlikely that you will ever have one of these electronic stool-pigeons in your own car, there's little doubt that devices planted along the roadway will some day be able to detect law violations just as efficiently.

Electronic safety systems in use today and some of them being engineered for tomorrow will be examined in detail in subsequent articles.

In the meantime, New York City Traffic Commissioner T. T. Wiley throws out this challenge to America's electronic inventors, professional and amateur:

"The one device that would probably eliminate more fatal accidents than all other devices combined would be one to prevent the engine from running whenever a person under the influence of alcohol is at the wheel."

Got any ideas?

END

# Computers Speed Aircraft Design



*It's a long way between the drawing board and the flight test. Both analog and digital computers save steps along the way*



By **FORREST H. FRANTZ, SR.**

**B**OTH modern aircraft and guided missiles are highly complex. The aircraft's shape must allow best aerodynamic performance and at the same time the utmost in structural strength. Controls must be designed so the aircraft can be handled easily and safely. Fire control must make the best use of the plane's armament. The pilot's environmental needs must be met, as must those of the equipment. The guidance and control requirements of guided missiles make their design problems even more complex.

These are a few of the general design problems—there are many more. And within each of these general problems are many specific ones. Many of them are solved on paper before the first model is built. But design problems are complicated by many interacting facets, and all cannot be solved so simply. Some of those that can be solved on paper are not always com-

pletely solved because unpredictable factors or human error may lead to incomplete solutions. So in every phase of the paper design, computers are put to work.


The problems which do not lend themselves to complete solution are fair prey for computers, too. Instead of building the first aircraft from a paper design and then modifying it as necessary, there has been an increasing trend to precheck concepts by simulating parts of the aircraft system with a computer. This approach saves time, manpower and dollars. When the aircraft is built, the designers are surer that it will perform properly.

## Computers play two parts

There are two basic approaches to using computers in aircraft design. They may be used to compute or to simulate. If a number of the parameters in a problem are known, the

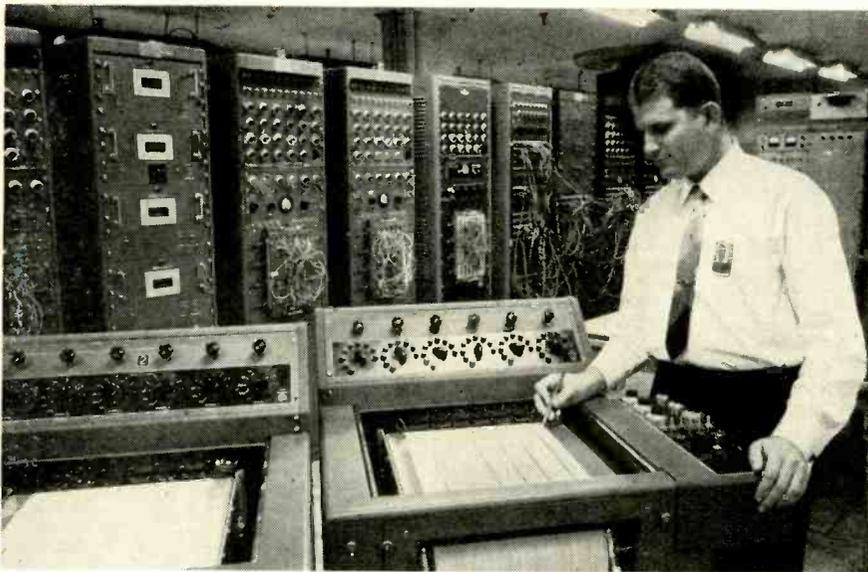problem may be solved by computing the value of the unknown. Unfortunately, the problems in aircraft design are not this simple. Too many unknown intimately related quantities rear their ugly heads. To cope with these problems, aircraft designers usually resort to complicated mathematics. Sometimes, computations are repeated with the quantities in a problem varied slightly each time to determine the best values. Large-scale digital computers handle these jobs readily.

Simulation calls for imitating a system. The imitation may be an exact part-for-part duplicate of the anticipated system. But it's much less expensive and quicker to use a computer to imitate all or part of the system. A capacitor, coil and resistor can simulate a spring-mass-friction mechanical combination (see Fig. 1). It's even easier to simulate the mechanical combination with an analog computer



Many problems associated with aircraft design and performance evaluation are solved by the analog computer division of Chance Vought Aircraft.

because the values of spring, mass and friction constants are easier to select. If the equations which describe the motion of an aircraft and the aircraft's response to pilot control motion are set up on a computer, the designers can "fly" their aircraft before it is built!

As the design progresses, the design problem breaks down into many specific problems that simulating helps solve. As an example of how simulation is used at this design level, consider the aircraft control surfaces actuated from the cockpit. The block diagram of such an electrical hydraulic-control system is shown in Fig. 2.

The stick in the cockpit is attached to an electrical transducer which changes mechanical motion to an electrical signal. This signal is transmitted to hydraulic control valves which actuate control surfaces. The system must provide the right ratio of control to each surface. It must also keep the rate of control and the total range of control within safe limits. Servomechanism, electronic and hydraulic techniques are involved. But all are intimately related with the control-valve characteristics.

A cockpit simulator with actual electrical controls and an analog computer which duplicates the performance of the hydraulic control surface actuators can represent the system. Valve characteristics may be changed readily with analog computer potentiometers. The results of the simulation are used to design the control valves.

Cockpit instruments must tell the pilot everything he needs to know and the cockpit controls must allow the pilot to tell the aircraft exactly what he wants it to do. If the placement of controls in a crowded combat cockpit is such that one control is in the way of another, or that one of the controls hits his knee before it's moved through its full range, the pilot has incomplete

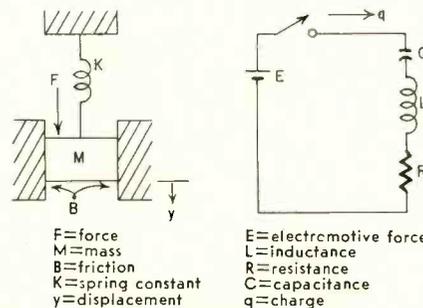


Fig. 1—The simple mechanical system on the left can be simulated with the electrical system on the right.

control. This limits the aircraft's capability and might spell disaster. Cockpit simulators which include analog computers are important tools for eliminating these possibilities.

### Computers along the design road

Computers play an important role at every stage of aircraft development. Aircraft companies submit proposals to the military services to obtain contracts. A considerable amount of preliminary design goes into such a proposal. Even at this earliest stage of the operation, before a company knows it will manufacture the aircraft, computers enter the picture.

After the contract is awarded, additional design of a big-picture nature begins. At this stage, the specific design departments— aerodynamics, structures, propulsion, electronics—and the host of groups in these departments which participated in preparing the proposal have to pin down design details. The details worked out at this point are preliminary to problems like the control-valve and cockpit design. Again, the computer is an important tool.

And, there's a lot more to producing an aircraft than engineering. Plans are laid for production. Methods for the most effective use of manpower and machines are studied. Schedules are

expanded and detailed so tooling and materials will be available when they're needed. Again, computers can help to cut that undertaking down to size. Even routine aspects of running an aircraft business, such as preparing payrolls and bookkeeping records, are simplified with computers. At Chance Vought Aircraft an IBM 704 digital computer aids the business offices as well as the engineering department.

But, again considering the details of aircraft development, the computer still has a host of jobs to do. After the best paper design is completed (and sometimes concurrently with paper design), aircraft and aircraft-system simulators are constructed and studied.

Aerodynamics, propulsion and surface-throttle controls are basic in the airframe design. But many other systems are essential in a modern piloted aircraft or in a missile. Electronics plays a vital role in most of these systems. The pilot needs a cockpit display of information pertaining to navigation and the status of the aircraft's numerous systems. Communications, guidance or navigation, and air-data systems are required. The armament and associated fire control fills the aircraft's basic weapon requirement. Air conditioning, pressurization, and cockpit design for pilot comfort under varying flight conditions are important. Autopilots to ease the strain on the pilot in high-performance aircraft or to control the entire mission flight of a missile are also essential. Weight distribution in the aircraft may be sufficiently critical to require complicated programmed control of fuel consumption. Some aircraft systems

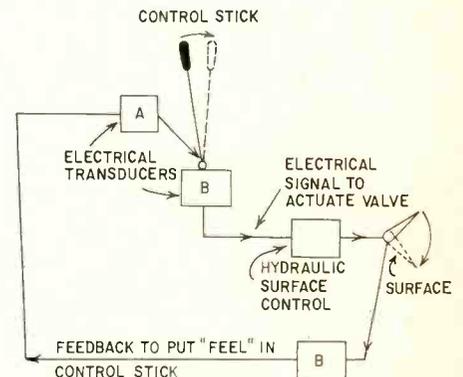


Fig. 2—Simplified diagram of one type of control system. Transducer A converts electrical signals to mechanical energy. Transducer B converts mechanical energy to electrical signal.

contain computers as part of the actual equipment.

Analog or general-purpose digital computers may be substituted in a simulation to arrive at specific airborne computer design. Special computer-circuit tools, such as the Heathkit Analog Computer and Computer Control Co.'s 3C digital-computer building blocks, are sometimes used to finalize computer design. They are also used to check electronic circuits that are not basically computers.

# ELECTRONIC CROSSWORD

By WM. R. SHIPPEE

Problems are simplified by treating the various aircraft systems separately. But, eventually they must be integrated, and the first aircraft must be built. Then there's a period of checking on the ground. Finally, the aircraft is flight-tested. During the flight test, many measurements are made and a considerable amount of data recorded.

This data is reduced with computing equipment, and efforts are made to improve the aircraft and systems designs further.

## Analog vs digital

There's no basis for arguments about whether analog or digital computers are best. For a specific problem one is usually better than the other. Quite often, though, it's a good idea to use both. General arguments of analog vs digital computers advanced in the earlier days of the computing art are no longer heard. Everyone associated with computers admits that the type used is determined by the problem.


If extremely accurate results are needed, a digital computer is best. It can handle discrete pulses which represent numbers, and its accuracy is limited only by the number of binary bits or decimal places designed into it. Large-scale digital computers such as the IBM 704 and the Remington Rand Uni-vac are mathematical machines and their operations are inherently arithmetic. Before an engineer's problem can be run on this type of computer, a rather extensive program must be prepared by a programmer from the engineer's statement of the problem.

The engineer usually states his problem as a differential equation. This usually fits the analog computer directly and the analog computer is simpler to use in most simulations, too. In such a computer, an electronic amplifier with capacitor feedback forms an integrator. Integration with a digital machine is not as simple. Most engineers prefer analog computers for this reason.

At Chance Vought Aircraft, an extensive analog computing facility is kept continuously busy. But sometimes the accuracy of the analog computing equipment (0.1% to about 2% for most problems) is not good enough. Then, the engineer must seek a general-purpose digital computer to solve his problem. Or, he may resort to a digital differential analyzer (DDA). The digital differential analyzer operates with discrete numbers, but it integrates by incremental techniques. A problem is entered into a DDA in much the same way that it would be presented to an analog computer. This feature makes the DDA an important engineering tool which seems destined to grow in popularity in the aircraft industry.

Aircraft companies have sizable analog and digital computing facilities. They have proved valuable and are constantly expanded to increase their utility.

END

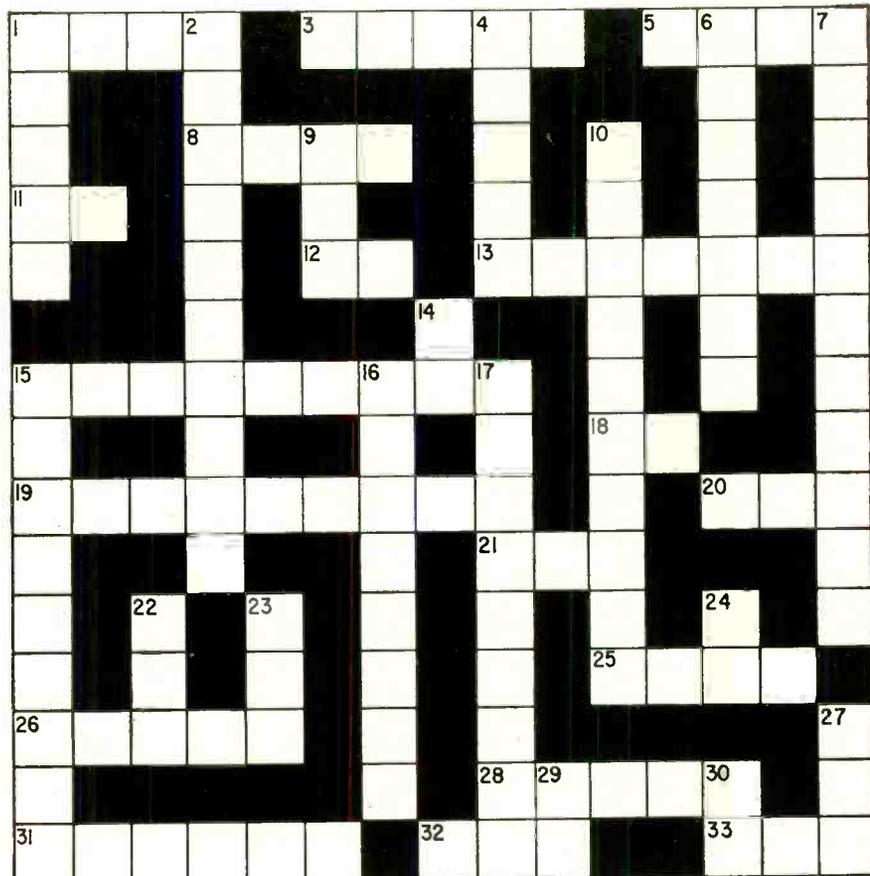

## HORIZONTAL

1. Equipment used to produce high-quality sound.
3. Instrument for checking wave-forms.
5. Unit of power.
8. Every TV set uses electrostatic or magnetic ..... (abbr)
11. Remote control. (abbr)
12. Inductance-Capacitance. (abbr)
13. Tape recorders use these to remove sound from tape.
15. Used in most amplifiers to link one stage to the next.
18. Intermediate frequency. (abbr)
19. The imaginary part of impedance.
20. Transformer used at audio frequencies. (abbr)
21. Output stage. (abbr)
25. Used to convert ac to dc. (abbr)
26. Front-end of a TV set.
28. Transmission of code. (abbr)
31. Three-element vacuum tube.
32. Circuit used to generate alternating voltages. (abbr)
33. Input of most transformers.

## VERTICAL

1. A unit of inductance.
2. A coil has this.
4. Used as a signal pickup for test instruments.
6. A person who operates a noncommercial transmitter.
7. Every ham should have one of these
9. Element of a vacuum tube. (abbr)
10. Semiconductor that is replacing vacuum tubes.
14. Barkhausen oscillation. (abbr)
15. Chemical solvent used in service work
16. Used in the output stage of most transmitters.
17. Used to vary the amount of current flow in a circuit.
22. Type of transistor.
23. Part of a vacuum tube. (abbr)
24. Symbol for collector current.
27. Interference on TV band.
29. Electron-coupled. (abbr)
30. Ground potential. (abbr)

(Answer on page 135)


improved

Solar Flare

indicator

New circuit boosts sensitivity of 3-transistor SEA detector

By DAVID WARSHAW \*

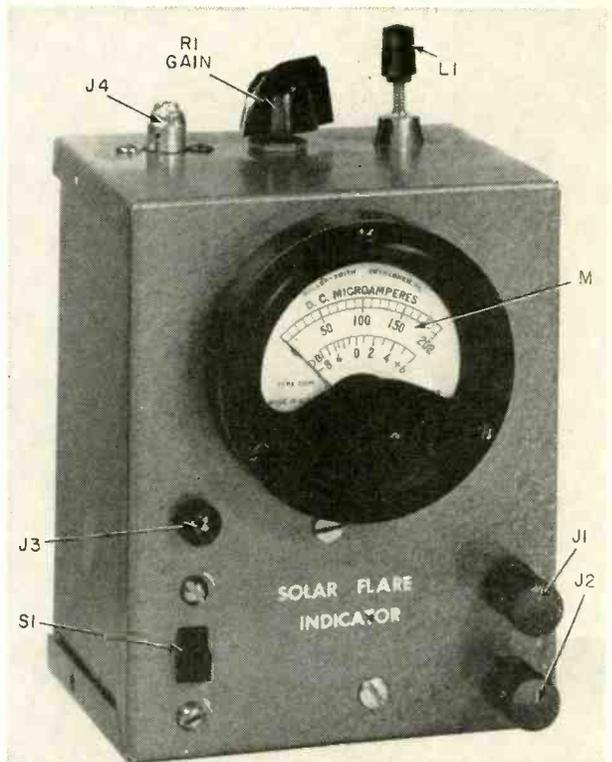

THE all-transistor solar-flare indicator described in the August, 1956, issue of RADIO-ELECTRONICS, has been contributing to basic research during the International Geophysical Year. This receiver, which detects solar flares by the SEA method (Sudden Enhancement of Atmospherics), uses the first all-transistor circuit ever devised for this purpose. At present, the results obtained with these units are being carefully studied and coordinated by the American Association of Variable Star Observers (AAVSO†) and the National Bureau of Standards.

Shortly after the article appeared, letters expressing interest in the instrument arrived from all over the US and even from distant parts of the world. As a result, more than 20 of these instruments are aiding basic research and making valuable contributions to the fund of data being accumulated during the IGY. These instruments were built by readers who used the original circuit, supplemented by information supplied by the author.

Less than 2 months after the solar-flare indicators were in operation, the results shown in Fig. 1 arrived.

The SEA's on 27 kc (11,000 meters), which are caused by solar flares, are quite distinct in their shape on the recorder and are easily identified and separated from sudden increases caused by local interference (see Fig. 2).

Upper-atmospheric studies, through the use of rockets, have confirmed the belief that shortwave fadeouts are due

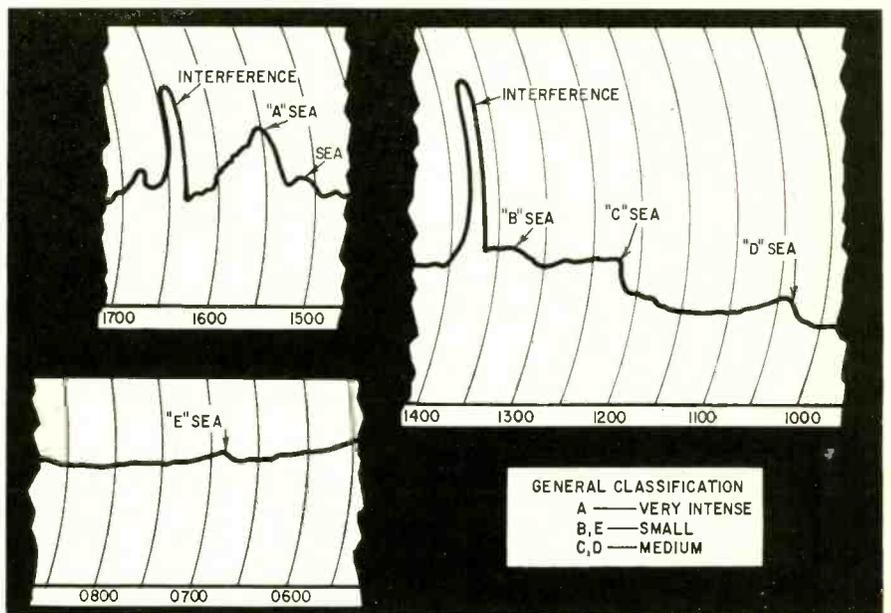


Fig. 1—First results using the 1956 circuit. Top left, Oct. 5, 1956 DST; top right, Oct. 6, 1956 DST; lower left, Nov. 1, 1956 EST.

to an extra layer of ionized air caused by X-rays emitted by the sun during solar flares. This extra layer extends down to about 12 miles below the normal lowest (D) layer. The D layer, 30 to 54 miles high, appears to remain undisturbed during the fadeout. It is this extra ionosphere, present during solar flares, that makes a better reflector for atmospheric pulses on 27 kc, thus causing a sudden enhancement of atmospherics. The atmospheric pulses originate in tropical thunderstorm centers, giving us a useful steady source of very-low-frequency radio energy.

Like other forms of basic research, recording SEA's is not without prob-

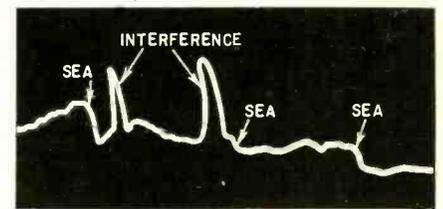


Fig. 2—SEA's and interference are easy to differentiate.

lems. One of the greatest is faced when a certain location is troubled with interference from sparking electrical appliances and TV receiver yoke leads radiating broadly near 31.5 kc—twice 15,750 cycles, the horizontal-sweep frequency. Sometimes, by moving

\*Technical supervisor, American Cable & Radio Co. (ITT).

†The AAVSO is a scientific and educational organization which has been serving astronomy for more than 40 years. Headquarters are at 4 Brattle Street, Cambridge 38, Mass.

antenna and lead-in about 50 feet away from the source of interference, the trouble can be eliminated. Downtown Brooklyn is far from an ideal location, yet I have recorded hundreds of clear SEA's there during the past 2 years.

**Circuit improvements**


After 2 years of use, a number of improvements have been made in the transistor solar-flare indicator's circuit, and the recording system used with it. Any dc recording instrument with 100- $\mu$ a full-scale sensitivity is suitable. In the original circuit, the second class-A stage was direct-coupled to the class-B stage, which used a separate battery. This lowered the unit's sensitivity as it put a slight reverse bias on the diode. Sensitivity was also dependent on the transistor's beta, which varies with temperature. Then too, the transistor's collector current was limited to 150  $\mu$ a. In the new circuit (see Fig. 3), the last stage is ac-coupled, putting a slight forward bias on the detector diode. This increases the circuit's sensitivity and still requires only two batteries—one for emitter current bias and the other for collector supply voltage. Emitter current bias stabilizes the operating point. It is adjusted for about 500- $\mu$ a collector current so the receiver now operates with a higher beta and is dependent only upon the transistor's alpha, which remains essentially constant with temperature variations.

This new circuit stabilizes the transistor's collector current against temperature variations. Collector current, without stabilization, increases with temperature and, in turn, boosts the power dissipated in the transistor, raising its temperature. This is evident from recorded traces showing objectionable oscillatory increases in the trace. Circuit stability depends on negative feedback (similar to cathode bias in electron-tube circuits). Emitter current is stabilized by the degeneration produced by the emitter resistor. At the amplified frequency, a shunt capacitor bypasses the rf around the emitter resistor. Current drain is less than 500  $\mu$ a on each battery, which is about shelf life. L4 is a toroidal 50-mh inductor for even greater output and less stray magnetic field. L1 and L2 should be placed about 1/2 inch apart.

The transistor solar-flare indicator is small and inexpensive, putting it within reach of all who are interested in studying solar flares or wish to participate in basic research. This research will continue after the IGY has ended.

An unexplained phenomenon, first noticed by Harry L. Bondy, chairman of the Solar Division of the AAVSO, has turned up in SEA recordings—even though they were made in widely separated locations. There is a slight, but noticeable, dip in the tracings 35 minutes before sunrise. This is followed by the

ANT APPROX 30 FT HIGH, 100 FT LONG INCLUDING LEAD-IN

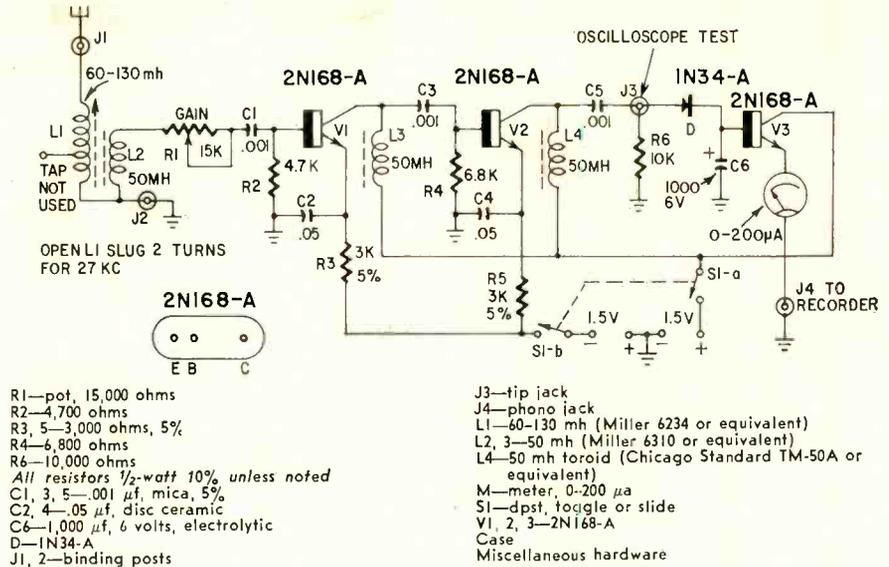

**Fig. 3—Circuit of the improved instrument.**

normal sunrise drop.

The sunrise drop is caused by atmospheric pulses reflected from the D layer, which does not exist at night, instead of the F layer. Since the D layer is lower, the signal is reflected with more hops from its source to the receiver and consequently there is more absorption. The cause of the slight dip and hump just before sunrise is unknown. Perhaps an explanation will come from some perceptive observer in the near future.

The AAVSO Solar Division's radio-astronomy program of recording SEA's is their contribution to the IGY. The National Bureau of Standards has supplied the AAVSO with four recorders to help in the project. The Solar Division started to make records of SEA's caused by solar flares immediately after several of its members built all-transistor receivers.

Mr. Bondy receives the recordings periodically and sends the tabulated results to the High-Altitude Observatory for the US-IGY Solar Panel, for publication in the National Bureau of Standards (NBS) monthly issues of Central Radio Propagation Laboratories (CRPL), *Series F, Part B, Solar Geophysical Data*.

Solar flares are classified by intensities. A class-3-plus flare causes the greatest disturbance to shortwave radio communications between 5 and 30 mc. In most cases, the duration, rather than the amplitude, of an SEA seems to be related to the associated solar flare's classification. A single location cannot produce the useful information that can be garnered by coordinating information from many locations. By doing this job, the AAVSO Solar Division performs an important and necessary service for the IGY. **END**

**N M**  
**E O**  
**X N**  
**T T**  
**H**

**■ FUZZBALL AND RED**

are with us again in Bob Middleton's **Standing Waves and No Color**. Practical servicing and installation hints in the language of the younger TV servicing set. Don't miss it!

**■ AMPLIFIER FOR YOUR TWEETER**


Simple, easily put together 3-tube handles the audio spectrum above 2,000 cycles, gives you a high-quality 2-channel system.

**■ FOR 10 METERS.**


There is practically "no limit to the distance possible" with this 10-meter receiver, built with 5 low-cost transistors by Don Hall, W5OBS. Bench-tested by RADIO-ELECTRONICS.
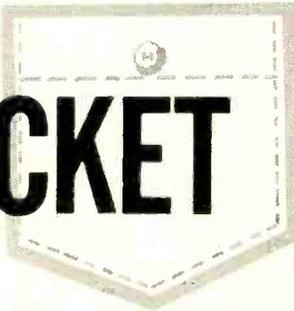
# AUDIO EAR IN YOUR SHIRT POCKET

Miniature electronic package makes wireless paging or silent TV listening possible



By EDWIN BOHR and GORDON PETERS

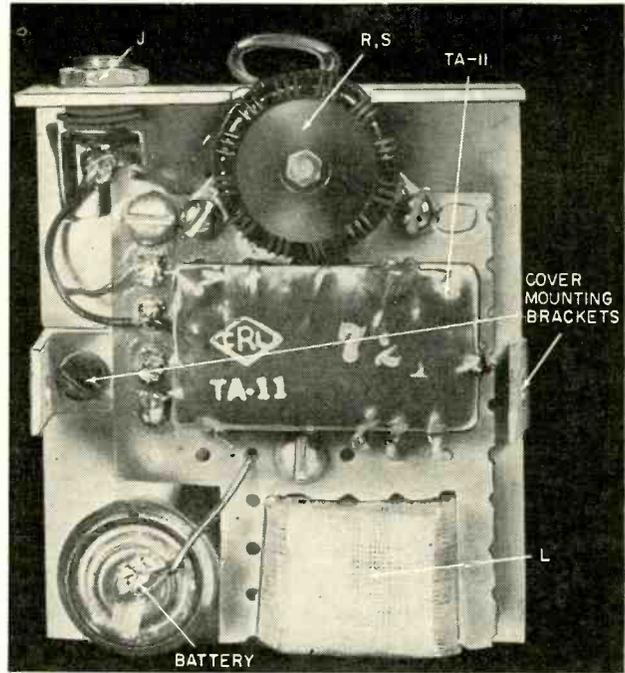

Tiny size of parts makes this pocket-sized receiver practical.

**I**NDUCTIVE coupling makes a simple and effective wireless paging system for personnel walking about in TV studios, department stores, factories, offices and hospitals. Each person carries a small case containing a pickup coil, audio amplifier and mercury cell. The entire assembly is not much larger than a pocket package of matches.

An ordinary audio power amplifier feeds the audio signal to a wire loop surrounding the paging area. About 1 watt of audio for each 1,000 square feet of floor is sufficient. The resulting audio-frequency field is picked up by the induction coil, amplified and fed to a miniature earpiece.

You can rig one of these units so the kids can listen to the TV westerns or a

hard-of-hearing member of the family can listen to a program as loud as he wishes without disturbing others. (And all this without entangling wires.) A TV set's output will saturate any but the largest living rooms with a strong inductive signal.

Many readers, experienced with electronics, are now asking, "And what about the terrific 60-cycle hum that it's going to pick up?" A natural question, considering the usual headaches caused by 60-cycle fields!

Nevertheless, 60-cycle hum problems are almost nonexistent, because 60-cycle magnetic lines of force are normally tightly concentrated around the offending transformers, motors and other equipment. So the signal-to-noise ratio

is usually excellent. Reception is crystal clear and completely free of noise. Infrequently, a poor transistor will generate a quiet frying sound.

### Pickup unit

The pickup unit (see Fig. 1) is built around the Centralab TA-11 amplifier.

### Wire Size and Resistance


AWG	Resistance per 1,000 feet (ohms)
20	10
18	6.5
16	4.0
14	2.57
12	1.6
10	1.0
8	0.64

This four-stage transistor amplifier is completely wired, assembled and potted with epoxy resin in a ceramic "chassis." The constructor may, of course, wish to construct his own transistor amplifier, or use one already available. This can readily be done with some slight sacrifice in compactness.

A single mercury cell with an expected cell life of 250 hours powers the unit. Other components are a 1,000-ohm earphone (these usually have an impedance of about 3,000 ohms), a 25,000-ohm volume control and the induction pickup loop.

This pickup loop is home-made (see Fig. 2). We built ours around the center leg of a miniature transistor transformer core. Individual laminations are clipped with diagonal cutters.

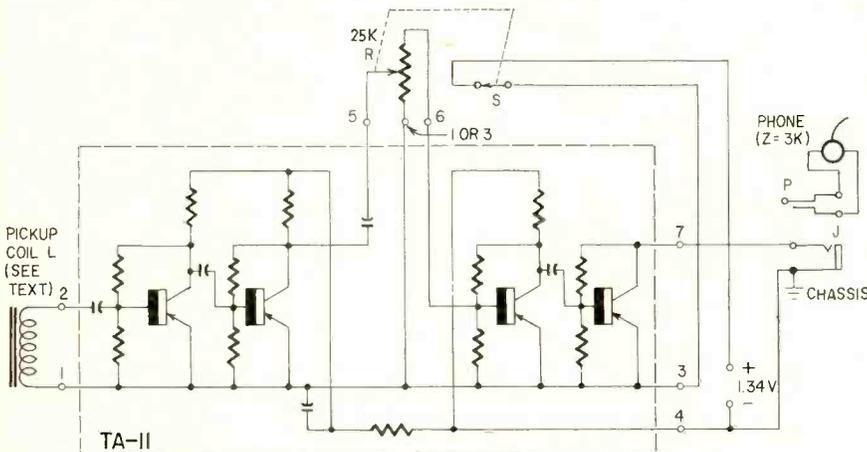Core size is not too critical, but the cross-sectional area should be at least



R—miniature pot, 25,000 ohms, with spst switch S  
J—phone jack  
P—phone plug  
L—pickup coil (see text)  
S—spst on R  
TA-II, 4-stage amplifier (Centralab)

Chassis, aluminum, 1-15/16 x 3-1/16 inches  
Cover, lucite, 3-9/16 x 2-1/4 inches  
End, lucite, 13/16 x 1-15/16 inches  
Battery, 1.34 volts, mercury (Mallory RM-IR or equivalent)  
Miscellaneous hardware

Fig. 1—Circuit of the portable pickup unit.



The finished unit isn't much larger than a box of matches.

photographs but not the drawing) should be placed conveniently to hold the plastic cover in place.

Now the case can be finished with a coat of paint. Red Krylon spray for the cover and white for the chassis make an attractive combination.

Where to use it

From the photographs, it is pretty obvious that this particular unit has been used for TV studio work. This is an application with a very real demand for "pedestrian communications."

The inductive system enables direct communication with people on the studio set who could not normally be entangled with trailing wires. In fact, the unit can be used by persons actually in view of the TV cameras, if the earpiece is artfully concealed.

In this instance, an inductive loop around the studio, fed by an 8-watt monitoring amplifier, delivers an excellent signal to any part of the two-story building and even across an adjacent six-lane boulevard.

However, too strong an inductive signal can be a real headache in a TV studio if it couples into tape recorders, microphones, low-level transformers and amplifiers. If this happens, try the following remedies: Reduce the audio drive to the inductive loop to a minimum, relocate the loop and provide better shielding for the low-level circuits.

Home installations are easy. Place the inductive transmitting loop under a rug, in the attic or basement tacked to either the floor or ceiling joists. In large buildings, the same methods can be used with more flexibility, since the loops can be placed around a picture molding or cornice or in false ceilings.

The loop should be matched approximately to the amplifier's output impedance. Essentially, the loop's impedance is the resistance of the wire. The table gives the resistance per thousand feet of common wire.

For living-room or home installation. (Continued at bottom of next page)

1/16 square inch. The laminations should come from an interstage type transformer, since these use high-permeability core materials.

Signal pickup increases with larger core area and higher permeability. Core materials are annealed to increase their permeability. Therefore, keep cutting strain and mutilation to a minimum.

Wind about 2,000 turns of No. 32 enameled wire on the core. Either tape the core and wind the wire directly on it or make a small bobbin and wind the wire on that. Our coil was wound on a bobbin. The bobbin was then removed, the coil covered with tape and the core pushed into the center of the coil.

The core is mounted vertically to intercept the lines of force generated by a horizontal inductive loop surrounding the room or building.

As the photos show, we used a small piece of perforated phenolic board to facilitate mounting the amplifier and volume control. The control's metal mounting ears must be insulated from ground. So we simply bolted the control directly to the insulating board.

The board is fastened to the chassis with 4-36 screws and spacers. The holes in the chassis are tapped for the screws. These screws are cut to exact length so they fit flush with the chassis back.

The earphone jack grounds the negative side of the mercury cell. Since the jacket of the cell is positive, it too must be insulated from the chassis. Even though it does not show up in the photograph, I cemented a piece of cardboard under the battery to insulate it from the aluminum chassis. Use a rubber-to-metal type cement.

The case is made of aluminum and plastic (see Fig. 3). Its top and back form the aluminum chassis. A plastic cover for the chassis encloses the front, two sides and bottom areas.

Bending the aluminum is easy. Simply score the metal where the bend will be, clamp it along this line between

two square-edge pieces of wood in a vise, and bend.

A similar procedure works with the plastic cover. Warm the plastic in an oven at very low heat, then quickly place it in a vise (as above) and bend it to shape. You can handle the warm plastic with cotton gloves. Now, cut out a bottom piece of plastic and cement it to the piece just bent. The best cement we have found is the type sold with Fiberglas kits in both automobile-accessory and boat stores. Follow the mixing directions exactly.

The average constructor will do a much better job cementing the plastic, rather than welding it with ethylenedichloride. Mix some Fiberglas with the cement and spread the mixture inside the case at the bent corners and junction with the bottom. This will reinforce the box tremendously.

When the cement and Fiberglas have hardened, you can sand them smooth, if necessary. Any pockmarks can be filled with a drop of additional cement.

Two angle brackets (shown in the

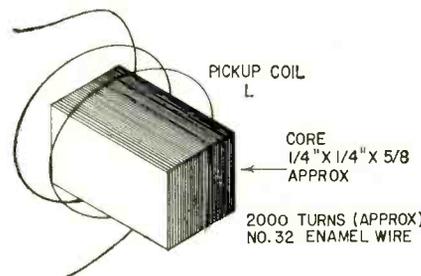


Fig. 2—Details of the pickup coil.


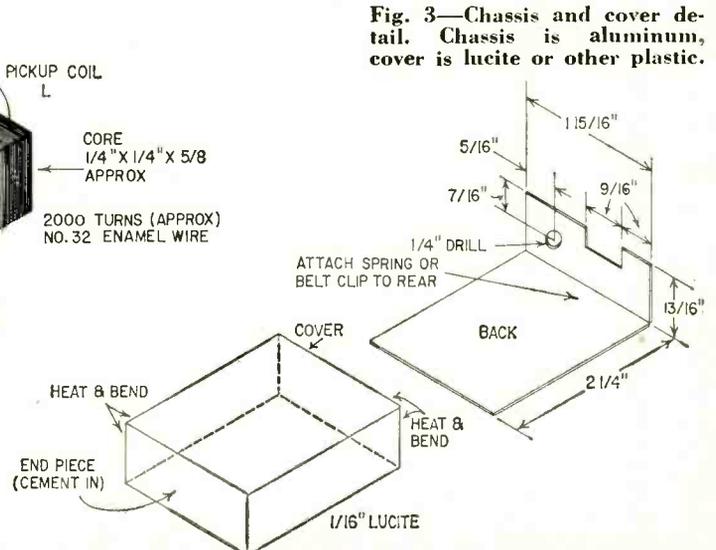


Fig. 3—Chassis and cover detail. Chassis is aluminum, cover is lucite or other plastic.

# HOW MUCH POWER for a STADIUM?

By HERMAN BURSTEIN

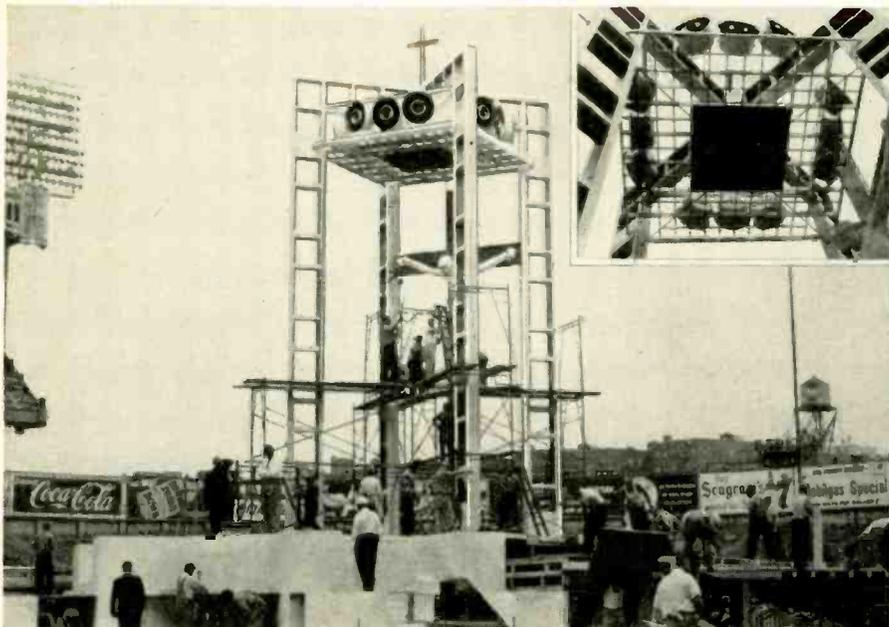

POWER amplifiers of 50 watts and more, and sometimes in excess of 100 watts, are being put into home use in ever greater numbers. Even though differences in speaker efficiency can account for as much as a 20-to-1 ratio between power requirements, there is still room to wonder whether all this power is truly needed for reproduction at, but not above, realistic levels. Cause for wonder increases when one learns that approximately 80 watts was re-

cently found sufficient for a high-fidelity public-address installation in so vast a structure as Yankee Stadium in New York City, which seats 67,000 persons and encloses about 3 acres of field.

A typical living room has a floor area between 200 and 400 square feet and is 8 to 10 feet high. Yankee Stadium contains approximately 130,000 square feet, about 430 times as great an area. Moreover, it is an outdoor site, and the height of the stands is several times that of a

living room. If 50 watts or more is needed for the home, it would seem that many times as much power would be required for the stadium. Yet 80 watts was all that was needed for high-quality reproduction at realistic levels on both music and speech.

This was demonstrated in the fall of 1957 when Francis Cardinal Spellman offered an outdoor mass at the stadium, using a specially engineered public-address system which was temporarily installed behind second base on the ball-field. As organ and vocal music figured prominently, the sound system had to meet high-fidelity standards. Instead of attempting to blast sound into every part of the place with tremendous power fed into a few speakers at one end of the stadium, 12 speakers were centrally located and arranged in a square for 360° coverage. With the aid of sound meters and walkie-talkies (for communication between technicians) the level of each speaker was adjusted to insure penetration of sound into every part of the stadium without noticeable echo effect or blasting.

The photo shows the installation, a 48-foot-high platform holding 12 University WLC speakers having a frequency rating of 50-15,000 cycles. They are of moderately high efficiency—some-where in the 10-20% range—yet not appreciably more efficient than many speakers—particularly horn-loaded ones—found in the home. The system was installed by Edward P. Casey Sound Systems of the Bronx, N. Y.

## AUDIO EAR in your shirt pocket (continued)

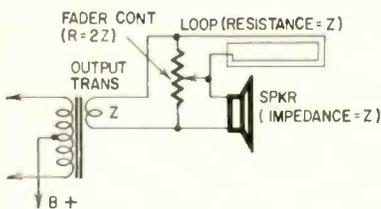


Fig. 4—Hook up the inductive transmitting loop so it and the TV set's speaker can be used at the same time.

tions, small wire is satisfactory and is economically optimum. However, for larger installations, the longer lengths of wire involved and the high cost of additional audio power make bigger wire necessary.

The inductive-loop signal is proportional to the number of turns in the loop multiplied by the loop current. Using wire with half the resistance per foot lets you double the number of loop turns, while maintaining the same resistance and current.

In smaller installations, rather than run a single conductor several times around a given area, string a single multiconductor cable around the area and connect the individual conductor

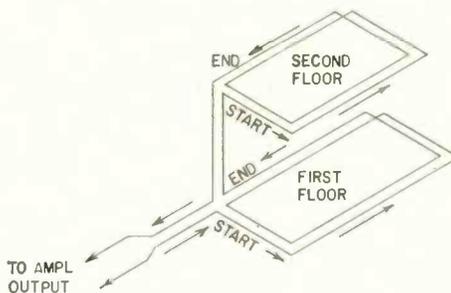


Fig. 5—How to set up transmitting loops for a two-story building.

ends together to form a continuous loop.

Hookup to the amplifier

Fig. 4 shows how to connect an inductive transmitting loop, together with

the existing speaker, to a TV set or amplifier.

For example, if the speaker impedance is 4 ohms, wind 4 ohms of wire around the pickup area and connect it as shown with an 8-ohm wirewound control. The control should be able to dissipate half the maximum audio power output.


The control acts as a fader and feeds all the signal to either the loop or speaker, or divides it between them.

Fig. 5 shows a typical installation for a two-loop arrangement with the loops in series. The same idea is extended to multi-story buildings. This arrangement gives a more than adequately uniform inductive signal. The current must be flowing in the same direction in both coils at any instant. To connect the coils in parallel, be sure both start ends of the wire are connected together. END

### Reference

Ray Zuck. "Audio Induction Picking System," *Electronics*, page 178, February, 1957.

# STABILIZING FEEDBACK AMPLIFIERS

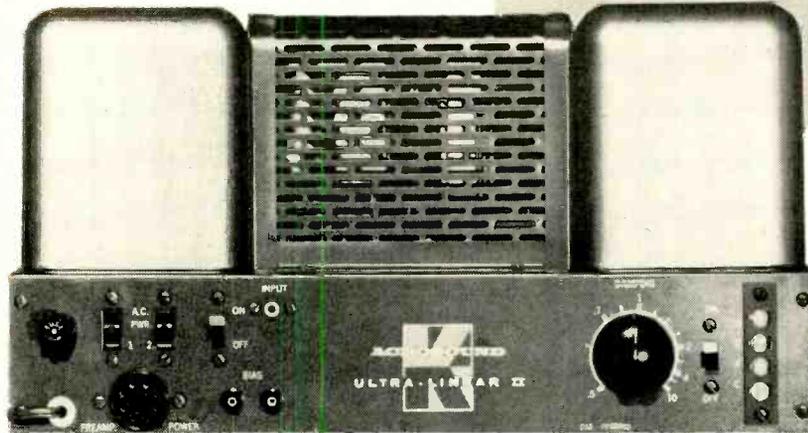

*Part I—A good feedback amplifier must be stable. . . Here are some ways of reaching this goal*

By HERBERT I. KEROES \*

**A**UDIO enthusiasts generally agree that the power amplifier largely determines the audio quality of an audio system. Of course, other components can also limit quality. But a good amplifier can make a mediocre speaker sound quite tolerable, while the best speaker will lose its virtues when connected to a deficient amplifier. Among "good" amplifiers there is a world of difference. Some sound smoother than others; some display muffled or muddy highs, and some break up in bass passages where an extra burst of reserve power is needed. This is true even of amplifiers with more or less identical specifications, including the power rating.

For several reasons, specifications alone do not disclose an amplifier's actual audio qualities. Amplifier specifications are not standardized and therefore do not permit an accurate comparison of quality. Often an amplifier will excel in some particular category, and this is featured in large type as a spellbinder. Consider harmonic distortion, for example. A figure of, say, 1% total harmonic distortion will be quoted, without stating whether the principal harmonic is third, fifth or seventh. It is well known that the seventh harmonic forms an unpleasant discord, while third and fifth harmonics produce only a coloration of the original sound.

The quantities that enter into measured specifications are all taken by steady-state sine- or square-wave excitation. But sound is not a steady-state phenomena. It is ever-changing in waveform, periodicity and intensity—it is transient in nature. The power amplifier must be able to handle the more difficult requirement of providing a burst of power, as in a kettle-drum passage, without noticeably disturbing

the quality of a higher-pitched instrument, such as a flute, played in the same passage.

Finally, specifications are determined by laboratory measurements which do not realistically represent the conditions of actual use. One example is in the presentation of data taken using a rated resistive output load. Speakers are usually resistive over only a relatively narrow band of frequencies within their range, and at all other frequencies produce a reactive impedance several times nominal value. This causes an impedance mismatch which may increase distortion considerably. The amount of increase depends upon the output stage circuit, and it is well known that triode and Ultra-Linear<sup>1</sup> output stages produce less mismatch distortion than pentodes and tetrodes.<sup>2</sup>

So the specifications of an amplifier do not necessarily disclose its audio qualities and should be used only as a guide. An amplifier of good quality usually has excellent specifications. However, another amplifier having the same excellent specifications may produce inferior sound.

## Feedback and stability

If an amplifier has reasonably good frequency response, low IM and harmonic distortion, and good square-wave response at 30 and 10,000 cycles, it is appropriate to look into how well these specifications are maintained under transient operating conditions. This is perhaps the crux of the problem.

We can then attribute any departure from steady-state performance, provoked by transient input signals, to instability in the amplifier circuit, and the general condition may be termed transient instability. Sometimes, the

term syllabic distortion or instability has also been applied to the condition and is particularly appropriate since it gives an apt description of the here-and-gone quality of transients.

Both feedback and nonfeedback amplifiers can be unstable, each for different reasons, and the two types of instability can occur simultaneously in the same amplifier. One type of instability not caused by feedback is due to shifts of plate and grid potentials within the various amplifier stages. Amplifiers using class-AB output stages are particularly susceptible to this condition, since the large change in plate current causes a variation in power supply voltage due to the regulation of the supply. The plate voltages feeding the early stages are progressively decoupled, and in each voltage feed line there is a certain storage capacity in the electrolytic capacitors which tends to maintain the plate potentials for a limited time.

If the voltage suddenly drops in a plate feed line which, for example, is decoupled by 33,000 ohms and 20  $\mu$ f, the voltage at the base of the plate resistor will drop by 63% of the total in 0.66 second. Cathode bias voltages are also bypassed by electrolytics, but generally have a different storage factor than the lines feeding the plates. Plate and grid voltages can therefore drift away from the optimum operating point, producing distortion. The condition is particularly troublesome in direct-coupled stages, since a small percentage change in plate voltage can produce a large-percentage change in grid bias of the following stage.

The remedy for instability of this type lies in using power supplies with good voltage regulation, decoupling networks with similar time constants, and voltage amplifier tubes operated at a mean optimum operating point. It is interesting to note that some of the partiality shown to high-power

<sup>1</sup> US Pat. No. 2,710,312, assigned to Keroes Enterprises

<sup>2</sup> F. Langford-Smith and A. R. Chesterman, "Ultra-Linear Amplifiers," *Radiotronics*, May, June, July, 1955.

\* Acro Products Co., Philadelphia, Pa.

## AUDIO—HIGH FIDELITY

amplifiers may be due to sensitivity of the listener to the type of distortion described, since a high-power amplifier may just loaf along at listening levels that would set up large voltage variations in one of moderate power. Transient distortion is most likely to occur on overload, which presents the same problem in reverse—designing the decoupling networks for fast overload recovery.

Instability caused by feedback is a much more complex situation. Oscillation within the amplifier circuit is the general condition and may range from continuous oscillation, with the amplifier circuit completely disabled, to a less serious condition of excessive square-wave ringing. The oscillation may be ultrasonic or subsonic, and, therefore inaudible but representing a useless expenditure of power and detracting from the amount converted into useful sound. The fidelity of square-wave response may be affected in other ways, thus introducing factors which influence transient response.

### Less distortion through feedback

All modern audio amplifiers use inverse feedback to minimize IM and harmonic distortion. Feedback has often been looked upon as the panacea for correcting all amplifier ills. When indiscriminately applied, it often fails to provide the expected results. For example, it will not correct distortion produced by an output transformer deficient in iron. However, it will linearize a nonlinear element such as tube transconductance, when the deviation from linearity is not too great or abrupt.

Inverse feedback is most intelligently applied when it is used to improve the characteristics of a good amplifier. In fact, the better the circuit is without feedback, the greater seems to be the reward. An additional benefit is obtained when inherent defects can be corrected within the circuit. One good example of this is the Ultra-Linear output stage. At equal output levels, the popular EL-34 in Ultra-Linear operation produces one-third as much distortion as when pentode-connected. At a fixed amount of feedback, say 15 db, total amplifier distortion is reduced by 15 db. However, to get the same maximum distortion figure, the amount of feedback for an Ultra-Linear amplifier can be 10 db less than required for a circuit with a pentode output stage.

There are many ways to apply negative feedback to a power amplifier. Early in feedback-amplifier evolution, negative feedback was fed from plate to grid of the output stage. Since the voltage gain of the power stage was small, the amount of feedback was limited. More grid drive had to be used and, consequently, more distortion was produced by the driver stage. These disadvantages soon outweighed the advantages, and only a small improvement was effected by this scheme.

It was soon recognized that feedback

could be carried over both output and driver stages, thus relieving the driver of the burden of supplying excessive voltage, making possible an increased amount of feedback. This was later brought to the ultimate stage of development by taking feedback over the complete amplifier circuit encompassing all stages, including the output transformer. However, this is not without an important disadvantage. As the number of stages is increased, circuit stability becomes more of a problem, and in multistage amplifiers design must be carried out with extreme care to prevent the circuit from breaking into oscillation.

Practically all modern amplifiers follow the design in which feedback is taken in a single loop from the output winding of the output transformer to the input stage. The number of stages used is usually either two or three—the Williamson arrangement using four being an exception. The amount of feedback may be 12 or 14 db for the two-stage arrangements, and 20 to 26 db for three-stage amplifiers. The amount of feedback used is a compromise between maximum distortion, desired sensitivity and the circuit's basic stability. As the amount of feedback over an amplifier circuit is increased, at a certain value the circuit will break into continuous oscillation. The db difference between this value and the actual value of feedback used is often referred to as the amplifier's stability margin.

The instability point of an amplifier is not as abrupt as the condition of oscillation or no oscillation would lead one to believe, since other effects occur at feedback values between the nominal and absolute amounts. As feedback is increased, the amount of square-wave ringing also increases. Just before the circuit spills over, the amount of ringing may exceed the height of the square wave. Also, it is common practice to conduct amplifier tests on resistive loads equal to the nominal rated speaker impedance. Speakers do not represent a pure resistive load, and an amplifier that is completely stable on a resistive load may spill over on a speaker load. This is particularly likely with the capacitive load reflected by an electrostatic speaker or a two-wire speaker distribution system, and few feedback amplifiers remain really stable under such conditions. There are other aspects of performance which have a direct relationship to feedback stability which we will discuss presently but, at this point, it is sufficient to observe that *an amplifier of inferior stability will manifest itself by the way it sounds.*

### Feedback design

Methods available to the feedback-amplifier designer allow a specific design to be carried out in a straightforward manner with accurate results. These are based on the fundamental feedback relationship which expresses

the gain of a feedback amplifier as:

$$A = \frac{A_0}{1 + A_0 B}$$
 where  $A$  is the gain

with feedback,  $A_0$  the gain without feedback, and  $B$  the fraction of output voltage returned to the amplifier's input.  $A_0 B$  is the voltage gain looking into the amplifier's feedback loop and is called the loop gain. All quantities are vectors and have a phase angle. Therefore, it is possible for the denom-

inator of the fraction  $\frac{A_0}{1 + A_0 B}$  to be-

come zero (when  $A_0 B$  is equal to  $-1$ ). When this occurs, the amplifier oscillates, since the gain with feedback becomes infinite. Hence, a feedback amplifier is stable if loop gain  $A_0 B$  never becomes  $-1$  or less at any real frequency. Note however, that this places no restriction on the loop gain becoming  $-1$  at a frequency other than real. Such frequencies exist mathematically as an imaginary or a conjugate complex frequency—the real part being a real frequency, and the imaginary part a damped exponential wave. This describes a typical transient wave which may be made up of the sum of many such quantities. A single square wave may be expressed in this form and is certain to contain a quantity close to an imaginary frequency at which  $A_0 B$  becomes  $-1$ .

If the imaginary component predominates, it is a damped exponential wave imposed on top of the square wave and, if small, the wave retains a smooth appearance. If large, the leading edge will show a spike. If the real quantity is dominant, an exponentially damped oscillation occurs, and the square wave exhibits ringing. At a particular mixture of real and imaginary frequencies, oscillation disappears and the top of the wave takes on an appearance of a small rise followed by a gradual exponential decay. This is called critical damping and represents a desirable compromise. However, the closer  $A_0 B$  is to  $-1$  at real frequencies, the greater the amount of ringing. Hence, an amplifier circuit may be analyzed for stability at real frequencies and an amount of feedback may be used below the maximum allowable at which oscillation occurs. The feedback range over which the amplifier rings falls within the area of the stability margin which was defined as the decibel difference between the actual amount of feedback used and that which produces continuous oscillation.

No standard value of stability margin that will assure critical damping of a square wave has thus far been determined. Some authorities feel that 6–12 db is sufficient. With this much feedback, the square wave may exhibit a small amount of ringing, say 5% or less. This analysis is usually conducted on a resistive load, and performance on a speaker load can be very much different. This leads us to point 2:

*Perfection in performance depends upon achieving a maximum amount of*

stability margin by design methods which rely on analysis at real frequencies.

### Nyquist diagrams

The stability of a feedback amplifier may be analytically determined with a Nyquist diagram.<sup>3</sup> This is nothing more than a polar plot of loop gain  $A\beta$  taken over all frequencies from zero to infinity. A typical Nyquist diagram is shown in Fig. 1-a, and it is seen that it is the locus of the loop gain  $OA$  expressed as a vector. It was first demonstrated by Nyquist that, if the plot encloses the point located at  $-1$ , the amplifier will oscillate. Several types of Nyquist diagrams are interesting and of practical interest. They describe certain anomalies in the performance of feedback amplifiers which have not been fully explained.

Fig. 1 shows five possible Nyquist diagrams. In the interest of clarity, only half diagrams are shown, and are typical for the frequency range from the midband of the amplifier to either zero or infinite frequency. The diagram from mid-band to zero frequency is usually not similar in appearance to that taken to infinite frequency, and each half of the diagram must be considered separately. Fig. 1-a encloses  $-1$  and the amplifier oscillates. Oscillation could be stopped by reducing the amount of feedback. This would, in effect, shrink the diagram and place  $-1$  outside of it.

Fig. 1-b is of significant interest, since it describes a type of conditional stability called Nyquist stability. Note that  $-1$  is not enclosed and the circuit is, in fact, stable. However, if the circuit loses gain or if the amount of feedback is reduced, the amplifier will break into continuous oscillation. Many feedback amplifiers exhibit this condition. For example, there is the amplifier that "tweaks" when it is turned on. In this case, circuit gain slowly increases as the tubes' heaters warm up. The diagram for a small amount of time goes through  $-1$  and an audible "tweak" is heard. An amplifier with this condition is also certain to break up on peaks since, at maximum output, the output tubes clip, reducing the circuit's gain.

A similar situation occurs in a circuit that is Nyquist-stable if the output transformer is deficient in iron. Pockets of oscillation will be generated on the sides of a low-frequency sine wave when the amplifier is delivering nearly full output. In this instance, the iron in the output transformer saturates, which again reduces circuit gain, causing oscillation. Since the magnetic flux in the transformer core is  $90^\circ$  out of phase with the output voltage, the oscillation appears on the sides of the voltage wave. This gives rise to point 3:

*The Nyquist diagram for a well*

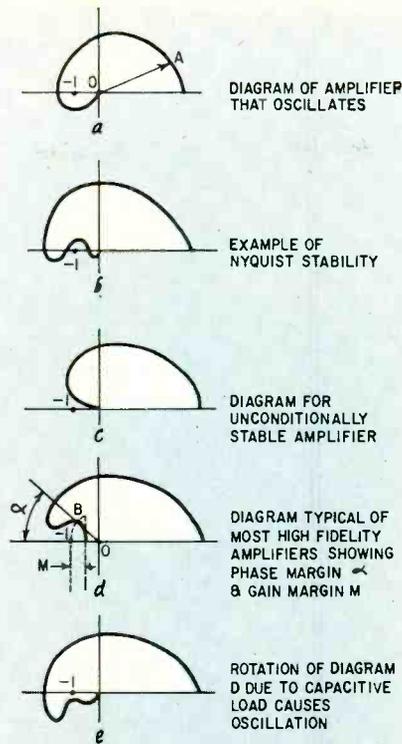


Fig. 1—Typical Nyquist diagrams for feedback amplifiers.

*designed feedback amplifier will not be of the conditionally stable type.*

At this stage, it is wise to inquire what means are available to avoid Nyquist stability, what is the best shape of Nyquist diagram, and how may it be achieved. In Fig. 1-c oscillation is impossible, since no matter how large the diagram becomes,  $-1$  will never be enclosed. This is a most desirable diagram, since it describes an amplifier of infinite stability margin. However, it may be achieved only for relatively simple circuits. The shape of a Nyquist diagram is determined by the total phase shift in the amplifier circuit caused by the sum of the individual phase shifts of interstage networks and output transformer.

Fig. 1-c is typical of a circuit containing two R-C-coupled stages. Since a modern amplifier must contain at least two stages, plus an output transformer, it is impossible to obtain a diagram of this type. Each additional stage adds phase shift, causing the Nyquist diagram to depart more and more from the optimum shape. Hence, we may make point 4. *A well designed feedback amplifier will contain a minimum number of phase shift networks, therefore a minimum number of stages.* This is carried into practice in the design of such amplifiers as the Mullard circuit which contains three high-gain low-phase-shift stages with direct coupling between two stages. The low-frequency Nyquist diagram has the appearance of Fig. 1-c, since only two phase shift networks which have an ultimate phase shift of  $90^\circ$  are present, the R-C network between driver and output stage, and the phase shift caused by the primary inductance of the output transformer.

Note that it may be possible to achieve a Nyquist diagram that approximates Fig. 1-c by staggering time constants of interstage networks. Hence, if one stage of a three-stage configuration can be given a greatly extended response, during which interval the gain of the other two stages is gradually attenuated, the amplifier behaves as a two-stage unit, and Fig. 1-c is approximated. In practice, a limited amount of improvement can be obtained in this manner. Design may call for staggering the time constants of interstage networks, extending the gain of one stage by video techniques or trading the gain of one stage for increased bandwidth. Also, at low frequencies, direct coupling or partial direct coupling may be used.

Fig. 1-d shows a Nyquist diagram for a stable amplifier. Note that the curve cuts away from  $-1$  at a fairly constant distance. This distance is related to the circuit's stability margin. Hence, if it crosses the negative real axis at  $-0.5$ , the amplifier has a stability margin of 6 db. There is a definite design method to achieve this type of Nyquist diagram, desirable because it produces results which predict amplifier performance quite well.

The best known method is that of Bode.<sup>3</sup> This depends on the interrelationship between phase shift and the normal response curve of an amplifier without feedback. The response curve is shaped to fit the requirements imposed by the preferred Nyquist diagram. The response curve may be shaped by a variety of methods which include those mentioned—extending response, staggering interstages, etc.

One additional method is given. The practice of introducing shunt equalization networks between stages reduces maximum bandwidth but makes it possible to maintain more uniform feedback over the useful band and shape the Nyquist diagram to obtain maximum stability margin. The shunt networks introduce a plateau in the response curve outside the useful band, causing a phase reversal. These networks, also called step networks, are used in both the Williamson and Mullard circuits to obtain additional stability. We may then observe point 5:

*It is desirable to obtain maximum feedback stability by making use of the methods of Bode to achieve an idealized Nyquist diagram of the type shown in Fig. 1-d.*

All too often step networks are introduced on a hit-or-miss basis, and best results are not achieved. The introduction of these networks should be carried out to obtain a Nyquist diagram of ideal form.<sup>4</sup>

Now that we've covered the theory, next month we can go further and show just how the steps described in this article are actually used in a quality hi-fi power amplifier on the market today.

TO BE CONTINUED

<sup>3</sup> H. W. Bode, *Network Analysis and Feedback Amplifier Design*, D. Van Nostrand Co. Norman H. Crowhurst and George Fletcher Cooper, *High Fidelity Circuit Design*, Gernsback Library, No. 56.

<sup>4</sup> C. G. Mayo and J. W. Head, "The Impedance Concept," *Wireless Engineer* (London, England), April, May, 1956.

# a **BOX** for your speaker

By P. G. A. H. VOIGT

**T**ODAY, many hi-fi enthusiasts are designing their own speaker cabinets. Can this be done successfully by rule-of-thumb methods at home?

This is one of those questions a straight "yes" or "no" does not answer. Just what do you really mean when you say "successfully"? From the idealist's point of view "successfully" might mean that the cabinet design should make the speaker, even if a poor quality, inexpensive unit, sound 100% perfect, with a level response curve and perfect transient performance. If that is your criterion I would say the answer is definitely "no". But if your criterion of success is that the sound should be considerably better than that from your neighbor's so-called hi fi, I think you will be reasonably successful, if you avoid major acoustic blunders.

If an ordinary moving-coil speaker is used without any baffle or cabinet, the lower frequencies are not radiated properly because the air particles simply flow around the edge of the cone from front to back and vice versa, and do not drive the air in the way necessary to set up a sound wave efficiently. This kind of short circuiting must be stopped or "baffled" in some way. The baffle, cabinet or enclosure (to use the present fashionable term) is used specifically to prevent such air flow around the edge of the cone. If a *small* flat baffle is used, flow still takes place around its edge. With a small baffle such flow is less than that around the edge of the cone when no baffle is present, but it takes a very large flat baffle to be really effective and prevent losses at the lowest frequencies. Such large baffles are cumbersome and difficult to disguise.

The so-called infinite baffle with the speaker mounted in a hole in the wall is the extreme case in which flow around the edge of the baffle is prevented completely (see Fig. 1). However, some people do not like making holes in the walls of their houses and besides, if someone slams the door, a delicate speaker may be injured!

The obvious way to prevent flow of

air from the front of the cone to the back and vice versa is of course to enclose the back completely, leading to the box baffle, forerunner of most present-day cabinets or enclosures.

While the box baffle succeeds in preventing the flow and might therefore be expected to be the ideal answer, enclosing the back of the speaker introduces a new complication. *There is air in the box which encloses the back of the speaker.* Therefore, if the speaker cone moves backward, that air is compressed; when the cone moves forward, the air expands a little. The compression and expansion produce tiny changes of temperature which we need not worry about at present, but we do have to worry about the changes of *pressure*. The air in the box acts as a cushion which stiffens the whole system. This raises the cone's effective resonant frequency and diminishes its excursion at the lowest audio frequencies.

If the pressure changes caused by this cushion are negligible, relative to other pressures involved, we do not have to worry about their effect. That, however, usually requires a large-volume cabinet. The pressure change produced by a given cone excursion depends on the amount of the excursion, the projected area of the cone and the volume of the air cushion. The greater this volume, the smaller the pressure change due to a given cone excursion.


### Cabinet size

When considering dimensions for a

**P. G. A. H. Voigt** is known as the dean of speaker and speaker-enclosure design engineers. A pioneer in the field of electrical recording, he turned his attention to speakers in the early '30's and is credited with the invention of the "whizzer" cone (Hartley, *RADIO-ELECTRONICS*, March 1954). His "fabulous PM-2 driver" (Augsburger, *RADIO-ELECTRONICS*, May, 1955) and back-loaded horn, marketed by Lowther, established a standard when first introduced in Britain. Mr. Voigt, now in semi-retirement in Canada, has consented to write us a series of articles on speaker enclosures.

cabinet, remember that the area of the cone is involved in the relationship. If you have a 12-inch speaker, the 12

*The best speaker enclosure is the one built around the particular speaker you intend to use. Follow the hints to good speaker design and end up with a better speaker system*

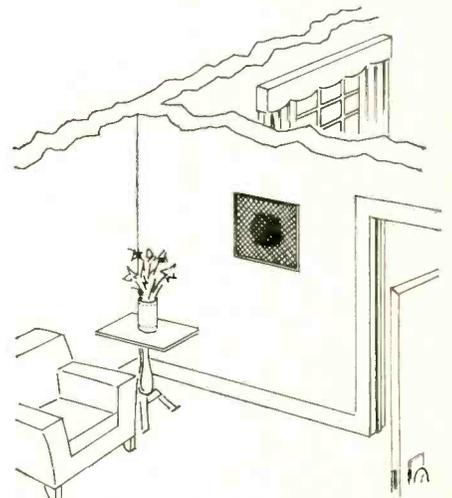

**Fig. 1—Mounting the speaker in one wall of a room puts it in an infinite baffle.**

inches really relates to the "basket" holding the cone. The cone's base may have only a 10-inch diameter, so allowing for the fact that part of the surround is moving as well and ignoring minor corrections, the project area is about 75 to 80 square inches.

On the other hand, if you have a 6-inch speaker, with a cone perhaps 5 inches in diameter, the projected area is much less, possibly only 20 square inches. Therefore, the little cone has to move four times as far as the big one to produce the same compression in the air cushion. That air-cushion pressure then reacts on the cone (of only one-quarter the area) so the actual force exerted on the smaller cone by the cushion compression is only about one quarter that which would have occurred with the 12-inch speaker. Since the small cone is probably stiffer to start with, and has to be displaced four times as far, the cushion pressure is relatively negligible compared with the other forces. Therefore, with a small cone, a smaller cabinet can be used. So the first thing to bear in mind when designing is simple. *Do not restrict the speaker cone's freedom of motion by making the box too small in comparison with the actual speaker with which the*

box is going to be used.

### Building materials

That is not the only rule. In practice, things are rarely as simple as they seem at the beginning. For example, when you speak of a box, just what do you mean? Groceries are delivered in a cardboard box which might be big enough to put over the back of the speaker. But if you do that and play a record and put your hand on the side of the box you will find that at certain frequencies the side vibrates violently. Now, when the box side is vibrating, it acts as a supplementary speaker. Additionally, since the inner surface of that side is vibrating too, the air cushion is affected and reacts to some extent on the speaker itself.

Laboratory measurements show that under certain conditions the vibrating side of the box may be vibrating in just such a way that the sound which the box is supposed to be baffling is actually being helped to take short cuts at a particular frequency. So it is desirable to make the box of good healthy stuff, which, if it vibrates at all, will vibrate very little.

Rigid construction and internal bracing help to minimize vibration. Different materials also vary in their liveness. This concept of liveness in enclosure materials is most easily understood if we regard the enclosure as some kind of system that might vibrate if tapped. A church bell which is tapped vibrates on its specific resonant note for a second or more, but a piece of soft putty of the same shape will not ring at all. The deader the material, the less likely it is to ring and thus build up vibration at any frequency.

For practical reasons, plywood is generally used. Alternatives are devised from time to time for the building industry. By tapping these with your knuckles and listening you can soon learn how to judge their relative deadness or liveness. A dead-sounding material could be a very useful alternative to plywood. The tapping test serves another purpose too. If the note produced is high up the scale, it shows that the material is fairly rigid, while another material of the same dimensions which makes a low-toned note is probably less stiff. Since a good cabinet should be stiff and nonresonant, the higher-toned, deader material is preferable.

If these considerations covered the whole subject, cabinet design would be easy. It would just be a matter of learning how much space the lady of the house is prepared to allocate to the enclosure, and then making a box to those dimensions out of a fairly nonresonant material. Unfortunately things are not that simple. The trouble is that the air in the cabinet is not just a simple cushion behaving in a very dead manner and allowing itself to be compressed or extended by the cone's motion.

The velocity of sound in air is about 1,130 feet per second, so if the cone

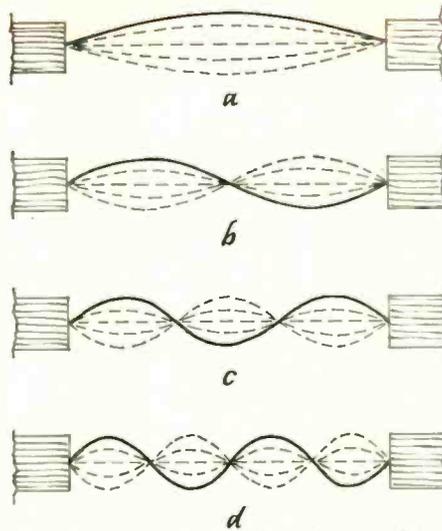


Fig. 2 — Stretched string shows vibration nodes.

moves, any air in the box which is 2 feet 3 inches away from the nearest part of the cone does not "know" anything about that movement until 1/500 second or so later. To make things clear, let us think in terms of a pressure wave; that is, assume the cone is moving inward during the 1/500 second in which the pressure wave is traveling to the part of the cabinet which is 2 feet 3 inches away. The pressure immediately behind the cone during that time is greater than it would have been if the compression had spread instantly to all parts of the cabinet and been distributed evenly.

### Sound reflections

Suppose there is a boundary surface in the cabinet at this 2-foot 3-inch distance. The pressure wave, after meeting that surface, is reflected and so, another 1/500 second later, the reflected wave gets back to the back of the cone. A pressure wave from the back of the cone is thus partly returned, from the surface 2 feet 3 inches away, 1/250 second later. Any cabinet naturally has internal surfaces, and these, each at their various distances, contribute to the reflections inside. So inside the cabinet, a complicated pattern of primary reflections can be built up. These affect cone motion to some extent and in so far as they affect it, they are putting into the sound something which the amplifier is not supplying to the speaker. Unfortunately that is not all, for the reflections do not stop when they reach the back of the cone. The part of the reflected energy which is not absorbed at the speaker goes on bouncing about inside the box and, though some of the energy is absorbed at each reflection, quite a complicated condition is usually set up.

The cone, on any kind of sustained note, is moving alternately in and out. Since the rarefactions reflect in the same way as the compressions, the complications inside the box involve a mixture of compressions and rarefactions. If things can be so arranged that

at any one moment the rarefactions meeting the back of the cone are equivalent to the compressions, the two cancel out and the cone is not affected. That would be a happy state indeed!

If we have an ordinary box, however—a rectangular one—at certain frequencies waves tend to build up between any pair of parallel surfaces. It is then very unlikely that the conditions for such cancellation would occur. More probably, air resonance inside the box will cause a wave buildup in one or more directions. Such a buildup, by acting on the back of the cone, affects its vibration much more than the primary reflection alone, and this affects the sound radiated from the cone face. Bad conditions occur if the sound buildup between one pair of surfaces is at the same frequency as the buildup between another pair of surfaces. The worst case occurs when buildup between all three pairs of parallel surfaces happens at the same frequency. Damping and other internal complications help diminish the trouble, but it is difficult to avoid all buildup between parallel surfaces.

If it is not possible to catch a trouble and strangle it at birth, the next best thing is to prevent it from becoming serious. Here, the trouble can be kept down by making sure, when designing, to arrange matters in such a way that the buildup frequency between one pair of surfaces does not coincide with that between other pairs.

### The stretched string

To see how this can be done, let us take a moment to examine the standard textbook diagrams which show the vibration modes of a stretched string. Fig. 2 shows a string vibrating between fixed points in modes which include 1, 2, 3 and 4 half-wavelengths.

The wavelength is different in each case. Fig. 2-a with its two nodes (points where there is no motion) has the longest wavelength. In Fig. 2-b with its three nodes, the wavelength corresponds exactly to the distance between the fixed ends. In Fig. 2-d with its five nodes, two wavelengths fit into that distance. As the wavelengths become shorter and the number of nodes increases, each individual half-wavelength becomes less important.

In a stretched string the vibration corresponds to a *lateral* displacement. The stationary wave set up in an air column between two reflecting surfaces produces a *longitudinal* vibration of the air particles. At the nodes, however, there is no motion. When there are only two nodes, each situated at one of the two boundary surfaces, it is easy to see why there is no motion. When there are more, however, this is not as clear.

A stationary wave occurs when a wave traveling in one direction is reversed by reflection and the reflected wave interferes with the incident wave. Two equal waves in opposite directions are the exact equivalent. At the reflection points and also at intervals of

## AUDIO—HIGH FIDELITY

half a wavelength the motions of the two waves cancel exactly and produce the nodes. In the case of the air column, it is at these motion nodes that the maximum pressure builds up. Midway between them, where the particle motion builds up to a maximum, it is the pressures which cancel.

With the air column, just as with the stretched string, the lowest buildup frequency is such that the distance between the two parallel surfaces where the nodes form corresponds to a half-wavelength. If, in a rectangular cabinet, the height, width and depth are suitably related, it is possible to ensure that the several buildup frequencies do not coincide.

### Nodes and cabinet dimensions

When working out suitable trial dimensions, remember if the speaker is located on the vertical center line, its position is midway between the two sides. It may also be midway between the top and bottom, but it is *not* midway between the front and back.

Before going into the details of the difference between the front-to-back wave and the others, it should already be obvious that making a speaker cabinet as wide as it is high, and mounting the speaker right in the center, would be a mistake, because buildup due to lateral reflections then occur at the same frequency as buildup due to the vertical reflections. Such combined buildup is far more objectionable than if buildup frequencies are staggered to occur at two distinct frequencies. The trouble from each is then less marked.

If we consider a cabinet 20 inches wide, the lowest-frequency standing wave which can be set up in the lateral direction has a half-wavelength of 20 inches. That half-wavelength standing wave has only two velocity nodes, and they occur at the two side surfaces. At those nodes, the pressure due to the standing wave builds up to maximum, but the air particle velocity is zero. Midway between them, on the cabinet's vertical center plane, is the region of minimum pressure and maximum air velocity due to that standing wave. Since it is *pressure* which affects the back of the diaphragm, that particular standing wave is not troublesome (see Fig. 3-a). The lateral standing wave likely to cause the most trouble is the one in which the 20 inches between the two sides corresponds to a full wavelength. That standing wave has a node on the cabinet's center plane, and that velocity node with its pressure peak is directly behind the cone. So, the trouble frequency due to the lateral standing wave is the one which corresponds to a half-wavelength of 10 inches.

If the cabinet is 32 inches high, we can use the same argument to show that it is the frequency which corresponds to a half-wavelength of 16 inches which excites the vertical standing wave with a node at the mid-level as well as at the top and bottom (see Fig. 3-b). The two frequencies corresponding to half-wavelengths of 10 and

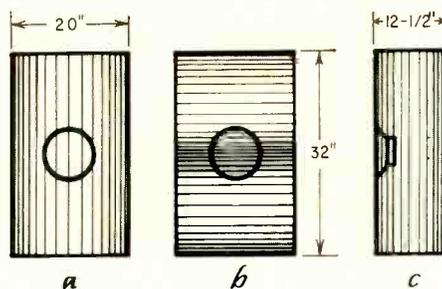


Fig. 3 — Pressure peaks (velocity nodes) inside the cabinet: a—20-inch full wavelength produces peaks at both sides of this enclosure; b—a half-wavelength of 16 inches gives you pressure peaks at top, bottom and middle; c—12½-inch half-wavelength produces an undesirable pressure peak at rear of speaker and back of cabinet.


16 inches certainly do not coincide, so we would have two small and separate packets of trouble at different frequencies rather than one concentrated one.

With the back-to-front standing wave, we run into trouble when a pressure maximum (velocity node) is at the back of the diaphragm (see Fig. 3-c). The danger frequency is that at which one half-wavelength corresponds to the distance between back and front. If we make this 12½ inches, we will have staggered the three main trouble half-wavelengths to 10, 12½ and 16 inches. Since we are dealing with the air inside the cabinet, the dimensions discussed so far should, strictly speaking, be the inside dimensions, but the point to get home at this stage is the relationship between the several dimensions.

A cabinet whose external dimensions are 32 inches high, 20 inches wide and 12½ inches front to back looks well balanced and would have an internal volume of about 3 to 4 cubic feet. If the center of the speaker opening is above the mid-height, appearance is improved. Unfortunately, the best height for appearance of a simple box baffle such as we are discussing is undesirable acoustically.

It is possible to set up a vertical standing wave with three half-wavelengths in the vertical 32-inch dimension. In this mode of vibration there are four nodes spaced about 10½ inches apart. If the speaker is mounted 12 inches down from the top, this particular vertical standing wave could be excited, for the center of the speaker would then be close to the node, which occurs about 10½ inches down from the top. Therefore, it would be better to have the speaker mounted lower and only about 2 inches above the mid-height. Then it is reasonably clear of that particular node and that particular vertical standing wave, which is especially objectionable because its half-wavelength almost coincides with the 10-inch transverse one, would not be set up. If the front of the cabinet is covered with sound-transmitting material, the position of the speaker open-

Fig. 4 — One way of bracing cabinet sides to lower resonant frequency.

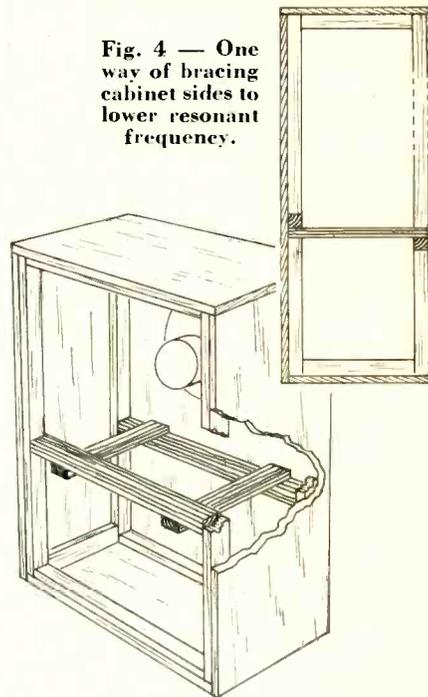

ing will not show.

Such a cabinet should be suitable for use with an 8- or 10-inch speaker and, if it is decorated to match the rest of the furniture in the room, it would probably be accepted by the lady in charge of domestic affairs. Speakers, 12- and 15-inch, unless very stiff, deserve a bigger volume. This also holds true for some 10-inch speakers with very free cones. A cabinet whose top, bottom and sides are only 12½ inches wide has considerable inherent rigidity if ¾-inch or thicker wood is used. However, unsupported front and back surfaces can be expected to vibrate violently at some frequency in the lower part of the scale. Such vibration can be diminished by cross-bracing and other reinforcement.

### Bracing to lower cabinet resonance

A simple method is shown in Fig. 4. It consists of fastening a piece of 2 x 2-inch wood firmly to the inside of the front face just below the speaker opening. To the upper side of that piece attach two cross-struts whose length corresponds to the cabinet's internal front-to-back dimension. Above the back ends of those cross-struts attach another 2 x 2-inch reinforcement. The rear surface of this reinforcing strut should be flush with the rear of the sides. When the back panel is fixed, it is fixed around its edge, and *also* to the second reinforcement. These two reinforcing pieces together with the cross-struts stiffen up front and rear surfaces considerably. Of course, additional stiffening can be added.

Do not paint or varnish the inside of the cabinet as this prevents sound absorption by the pores of the wood. Ideally, internal sound should be effectively absorbed or damped out so unwanted stationary waves inside the cabinet cannot build up and the possibility of their affecting the external

sound becomes negligible. For this reason, a layer of sound-absorbing material on the inside walls is usually recommended. It is at about speaker height that such material on the rear and sides will be most effective.

The air cushion elasticity is in parallel with the cone support elasticity. If there is air damping inside, this also damps the air-cushion elasticity, and the cone resonance, modified by the air cushion, becomes less marked. Internal damping can thus have a direct effect on the external sound.

When fixing the back in place, do not glue it permanently into position. One day, access to the speaker will be necessary, so fix the back with screws. It is not necessary for the joint to be completely airtight, but it is necessary that, when tapped, the whole sounds solid and not buzzy or cracked. A buzz indicates that two parts are in contact but not firmly together. Test for this before fitting the back on. A poor joint which produces a buzz must be traced and put right. Being too economical with glue or screws can give plenty of trouble later. Test again after fitting the back. Soft packing between the back and the cabinet and the reinforcement should prevent a buzz caused by vibration between the back and the rest.

The final test is the ear test. Some people are concerned with organ pedal tones, some with the clarity or edginess of cymbals and triangles. But the real test of a speaker system is male speech. If that sounds boxy, boomy or unnatural in any way, something is wrong somewhere. It may be in the studio or the mike, but if the same kind of unnaturalness persists on all program sources the trouble is usually in the speaker or enclosure. **END**

## STEREO DISC STANDARDS

\* In stereo discs the two channels shall be right-angle modulations of a single groove.

\* In the 45/45 system of stereo disc recording, the two axes of displacement modulation are inclined 45° to the disc surface.

\* In 45/45 stereo discs, the right-hand information, as viewed by the listener, shall appear as modulation of the outer sidewall of the groove.

\* In 45/45 stereo discs, equal in-phase signals in the two channels shall result in lateral modulation of the groove.

\* Lateral modulation of the stereo disc shall produce equal in-phase acoustical signals at the speakers.

\* The 45/45 system is recommended as a standard for stereo discs.


*It is further recommended that:*

\* The desirable tip radius for reproducing stereo discs be 0.5 mil.

\* Included angle of groove be 90°.

\* The bottom radius of the groove of the finished record be 0.2 mil maximum.

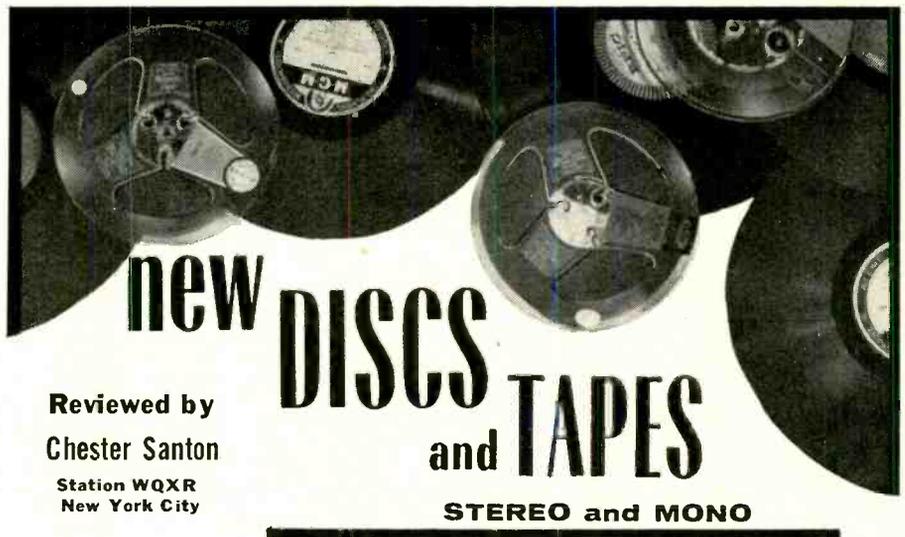*These are the findings of the Engineering Committee of the RIAA as reported in their Bulletin E3.* **END**



Reviewed by  
**Chester Santon**

Station WQXR  
New York City

**STEREO and MONO**

TO do justice to today's stereo discs, the stereo pickup cartridge must be selected very carefully. A poor cartridge may result in an outlook as warped as the appearance of a few early stereo records. The performance of my latest magnetic stereo cartridge is superior to that of the two previous models used in reviewing discs. Consequently, stereo records evaluated in past columns sound better now than they did when first reviewed. Separation is improved. Bass response is firm and clean on records once considered deficient in that respect. Highs are sweeter. The absence of peaks in the latest cartridge solves previous surface-noise problems. One of the better stereo cartridges, tone arms and turntables playing today's best stereo discs can give stereo tape a run for its money on any system.

**VERDI: Il Trovatore**  
Alberto Erede conducting Chorus of the Maggio Musicale Fiorentino and L'Orchestra de la Suisse Romande

London FFSS stereo records (3) OSA-1304  
London's opera releases in stereo carry the new medium to heights undreamed of a year ago. Stereo really transports us to the opera house. The orchestra, spread out in an imaginary pit, stands apart from the singers, yet works with them to better effect. The stars, Renata Tebaldi and Mario del Monaco, shine in a new light. Now Manrico's voice in his Act I serenade preceding his encounter with the Count di Luna can be located several yards upstage. The famous *Anvil Chorus* is particularly effective on a wide-range system. In every way, this album is superior to the earlier monophonic version of the same performance.

**GIORDANO: Andrea Chénier**  
Gianandrea Gavazzeni conducting Chorus and Orchestra of L'Accademia Di Santa Cecilia, Rome

London FFSS stereo records (3) OSA-1303  
This companion operatic stereo release offers Tebaldi and Del Monaco in an equally clean-sounding recording. The story takes place at the time of the French Revolution. A stereo highlight is the courtroom scene in Act 3. For the first time on records, it is possible to separate the shouts of the crowd from the rest of the action as Chénier is sentenced to death by the tribunal. Exciting days lie ahead for opera fans. Angel's first release of opera on stereo tape will be reviewed next month.

**Two for the Show**  
Tom and Jerry Vincent, Piano and Hammond Organ

Livingston stereo tape 1101 CX (7 inch; playing time, 31 min. \$6.95)

Livingston is releasing tapes at 3.75 ips. Supplementing their regular catalog of 7.5-ips tapes, this new CX series offers two tracks on open reels. Switching to the slower speed of my two-track machine, I played this low-priced tape on the system normally used in reviewing stereo tapes. Also on hand was the 7.5 version of these same show tunes (Livingston 1101 F, \$11.95). On a good unit, both reels exhibited

identical steadiness of speed. The CX had tubby bass. The highs, of course, were restricted at the 3.75 speed when using the present-day two-track playback head. This resulted in severe loss of stereo effect. Signal-to-noise ratio, however, was surprisingly close to that of the 7.5 tape. Under these conditions, the new slow-speed tapes are adequate for background music.

**Bob and Ray Throw a Stereo Spectacular**  
RCA Victor stereo record LSP-1773

Robert Bollard, formerly with Cook Laboratories, has joined RCA Victor as producer of stereo discs aimed at the 1959 audiophile. One of his first assignments rewards us with an amazing stereo record. Here are the most fabulous sound effects ever captured in a two-channel groove. The stereo rifle shots alone are worth the price of admission. Also heard are 10 samples of current RCA pop stereo releases. Top equipment will reveal the care and know-how lavished on this album. A more spectacular stereo record did not appear on the scene in all of 1958.

**BEETHOVEN: Symphony No. 3 (Eroica)**  
Charles Munch conducting Boston Symphony Orchestra  
RCA Victor stereo record LSC-2233

Problems still besetting some domestic stereo labels are to be found in RCA symphonic items released in October. This reording of the *Eroica Symphony* offers a ray of hope with fairly clean sound and passable highs and lows. But the Boston Pops *Marches in Hi-Fi* (LSC-2229) released at the same time sounds no better than the first RCA stereo record released last spring (*Hi-Fi Fiedler* LSC-2100). The stereo Dvorak *Fifth Symphony* with Fritz Reiner and the Chicago Symphony Orchestra is equally disappointing due to distortion. On the other hand, the Fiedler *Boston Tea Party* (LSC-2213) ranks with the industry's top items. Very puzzling.

**HANDEL: Organ Concertos Nos. 1-6**  
E. Power Biggs, Organist  
Sir Adrian Boult conducting London Philharmonic Orchestra  
Columbia stereo record K2S-602

With this release of six Handel concertos for organ and orchestra, issued for the 1959 Handel Bicentennial, Columbia takes a good stride forward in its stereo process. Rarely have I heard such sweet, easy, undistorted projection of stereo sound. It closely rivals the best Columbia monophonic work being done today. The organ used was designed and played by Handel. Original scores and an orchestra of the size specified by Handel are employed. The English church currently housing the organ possesses unusually live and forthright acoustics. A wonderful stereo album.

**Percussion in Hi-Fi**  
Ensemble conducted by David Carroll  
Mercury stereo record SR-60003

This recording of a percussion orchestra advances the theoretical perfection date of the stereo disc. Distortion is held to the average found on the better mono records featuring per-

## AUDIO—HIGH FIDELITY

cussion. Exciting highs and lows now identify more easily the individual instrument heard within a group. The stereo-disc medium passes a severe test in this battle of wave-fronts.

**GABRIELI: Processional and Ceremonial Music**  
Edmund Appia conducting Choirs and Orchestra  
of Gabrieli Festival

Vanguard stereo record BGS-5004

In this unusual release, the vocal pomp and splendor of 17th-century Italian music is heard in closeup. More than 300 years ago, Giovanni Gabrieli anticipated our current interest in stereo when he composed these works for four organs and separated choirs. His experiments in the placement of double and triple choruses while organist at St. Mark's in Venice provide fascinating two-channel listening today. Monophonic recordings of this music failed to bring out Gabrieli's daring interweaving of sound. Unfortunately, no attempt was made to capture cathedral acoustics. Surface noise, a shade above normal, may cause trouble if your cartridge peaks in that region.

**LISZT: Four Hungarian Rhapsodies**  
Anatol Fistulari conducting Vienna Opera  
Orchestra

Vanguard stereo record SRV-108-5D

Vanguard submits records for review in these columns in both monophonic and stereo versions. The latest disc in their stereo demonstration series tops its mono counterpart. In each case, distortion is low. This gypsy music thrives in stereo. In the third Rhapsody, woodwind solos are centered while the harp and cimbalom—easily confused in monophonic days—are heard from the left and right, respectively.

**Sounds of the Great Bands**  
Glen Gray and Casa Loma Orchestra

Capitol stereo record SW-1022

Stereo helps enormously in turning a trick seldom accomplished in the past. Famous arrangements long identified with 12 band leaders are revived in an amazing takeoff on the leading orchestras of the swing era. Middle-aged fans of Dorsey, Miller, Krupa, Thornhill, Herman, etc. will have difficulty believing their ears.

**La Belle France**  
Carmen Dragon conducting Capitol Symphony  
Orchestra

Capitol stereo record SP-8427

Natural stereo breathes fresh life into Carmen Dragon's arrangements of favorites representing all forms of French musical life. This well-balanced record foreshadows the importance of good arrangers in the stereo age.

**Die Engelkinder from Tyrol**  
The Engel Family

Vox stereo record ST-VX 25.650

The parents and seven children of the Engel Family are heard in an unusual program of Austrian folksongs and music for the Christmas season. Recorders and Renaissance string instruments supply a fresh, innocent background. Excellent stereo stems from the exceptional clarity of the sound.

**PUCCINI: Madame Butterfly**  
Erich Leinsdorf conducting Rome Opera House  
Chorus and Orchestra

RCA Victor stereo records (3) LSC-6135

One of the three latest RCA opera sets is available on stereo discs. Coupled with the normal advantages of stereophony is a fresh, restudied concept of the opera as a whole. The young-sounding voices of Anna Moffo and Cesare Valetti are an integral part of this restoration. Frequency response more than meets the task of conveying the score's atmosphere of fragile beauty.

**Favorite Songs of College Days**  
Marty Gold Chorus and Orchestra

Kapp stereo record K-1102-S

Exceptionally quiet surfaces set apart the first stereo releases from Kapp Records. Smoothly spread stereo and slight addition of echo rejuvenate these already hearty college songs.

**VIVALDI: Four Oboe Concertos**  
Alberto Caroli, Oboe  
Piero Santi conducting Gli Accademici di Milano

Stereo VOX ST-PL 10.720

One of the early Vox stereo records (Vivaldi Bassoon Concertos) featured the same orchestra heard on this record. Comparing these two releases, issued some five months apart, it is easy to trace stereo disc progress achieved by Vox. The more recent disc displays the most noticeable improvement in the overall sound of the orchestra which in all probability was recorded in the same

hall. Cleaner bass, robust upper middles and more transparent highs are to be found in the orchestral sound that supports oboist Alberto Caroli.

**LISZT: Totentanz**  
**LISZT: Malediction**  
Alfred Brendel, Piano  
Michael Gielen conducting Vienna Symphony  
Orchestra

Stereo VOX ST-PL 11.030

Now we're getting somewhere in recordings of the piano on stereo discs. Franz Liszt's chilling *Dance of Death* makes quite an entrance upon the stereo scene. With two channels sharing the burden, crashing piano chords can be properly handled on today's best equipment.

**BEETHOVEN: Piano Concerto No. 1**

**BACH: Piano Concerto No. 5**  
Glenn Gould, Pianist  
Vladimir Golschmann conducting Columbia  
Symphony Orchestra

Columbia stereo record MS-6017

The bubbling good spirits of the Beethoven concerto come to the surface more easily in stereo. In every way a top item.

### Monophonic discs

Note: Records below are 12-inch LP and play back with RIAA curve unless otherwise indicated.

**Drums on Fire**

World Pacific WP-1247

Four drummers take turns challenging your monophonic equipment in this crisp, meticulously engineered disc. The highlight of the album is a set of Tabla variations played on the traditional two-piece drum of India by Chatur Lal. Different and dazzling.

**Swingin' at the Cinema**

Jonah Jones Quartet

Capitol T-1083

Perk up your tweeters with today's happiest trumpet on records as Jonah Jones bowls over a collection of movie tunes with devastatingly fresh sound.

**En Avant—Marche**  
Band of La Garde Républicaine

Angel 35507

French military marches played in the crisp, distinctive style of France's leading band. Wide-range sound with a different tang.

**BACH: Art of the Fugue**  
Arthur Winograd String Orchestra

M-G-M 2-E3

Bach's final work now heard in a new edition for string orchestra by Mr. Winograd. Four editions of the music preceded the present one. Because Bach did not indicate tempo, dynamics or instruments to be used, this two-record album will interest scholars and musical mathematicians. The close, intense pickup of strings is logical in this case.

**Railroad—A Farewell to Steam**

Hi-Fi Record R 901

Having heard the monophonic disc, I now want to sample the stereo version of this final trip of a Sante Fe steam locomotive. The journey, although a sad one for steam buffs, will continue

to offer a wonderful excursion for your woofers for years to come. Specially designed Altec 21-C microphones fed the sound to an Ampex portable tape recorder with added preamp. Each potent transient during the trip from Los Angeles to Barstow stands ready to rock your system, especially on the heavy grades.

**Debussy by Firkusny**  
Rudolf Firkusny, Pianist

Capitol P-8451

Several years ago Firkusny's first solo piano recording for Capitol typified the new "natural look" in technical specifications. The ideal balance and completely free response of the earlier discs has been brought up to date. Better detail is available in the hushed passages as well as the full-voiced ones.

**The Marvelous Miller Medleys**  
Glenn Miller and His Orchestra

RCA Victor LOP-1005

Miller fans will enjoy this latest pressing of eight medleys from Victor's vaults. The sound cannot meet today's standards yet quality is far superior to the original Bluebird 78's. Particularly interesting is the opportunity to A-B the styles of Glenn's civilian and Army Air Force bands. In fact, one selection, *Stompin' at the Savoy*, occurs in a medley by the civilian band and is later heard in a performance by the AAF band.

**Only the Lonely**  
Frank Sinatra

Capitol W-1053

Sinatra's best mood album to date. Technically, this release is tops in its field. Scrupulously flat response permits full utilization of a wide-range system. Very highly recommended.

**MOZART: Symphony No. 40 in G Minor**  
*Eine Kleine Nachtmusik*

William Steinberg conducting Pittsburgh Symphony Orchestra

Capitol PAO-8432

The two works most popular among Mozart's orchestral writings set forth with care and genuine modesty. The sound, being the latest, is very low in distortion.

**ENESCO: Roumanian Rhapsody No. 1 and 2**  
**TSCHAIKOVSKY: Francesca da Rimini**  
**DYORAK: Carnival Overture**  
Eugene Ormandy conducting Philadelphia Orchestra

Columbia ML-5242

A particularly vivid example of sound quality sacrificed to crowd in an extra selection on one side of an LP. The eight other disc versions devote one side to Tchaikovsky's *Francesca*. Here Columbia jams in a Dvorak overture. The result: on good equipment, both selections on the side are deprived of today's normal bass response. There isn't room on the side to permit normal groove excursion. The Columbia LP of 1948, mentioned earlier, had bass to equal this at the same control setting. The usual Columbia tonal range may be found on the other side of the disc where it enhances splendid readings of the two *Roumanian Rhapsodies*.

**Music of the African Arab**  
Mohammed El-Bakkar and Oriental Ensemble

Audio Fidelity AFLP-1858

More Oriental harum-scarum directed at those who like to judge an album by its cover. Sultry sound.

**Jo Basile and His Accordeon di Roma**

Audio Fidelity AFLP-1871

Light background music for the live-it-up set. Jo Basile's agile accordeon skims through Italian favorites. One of the few instruments on this label that doesn't appear crowded by their ultra-close pickup techniques. No need of stereo here.

**DEBUSSY: La Mer**  
**RAVEL: Mother Goose**  
Ernest Ansermet conducting L'Orchestre de la Suisse Romande

Richmond B-19007

London FFRR is making available some of its early monophonic LP's at the new price of \$1.98 under the Richmond label. This Ansermet performance is one of 18 well-known items in the first release. Although the sound is not a duplicate of the original pressings, it still surpasses reissues generally found on other labels in this price range. END

Name and address of any manufacturer of records mentioned in this column may be obtained by writing Records, RADIO-ELECTRONICS, 154 West 14 St., New York 11, N.Y.




"I got it all on tape! What's it worth?"

Mobile unit designed for under-the-dash mounting in a car or truck.

Photo Courtesy Communications Co. Inc.

Transmitter, receiver and power supply at base station are in rack cabinet in corner. Control unit is on desk.

Photo courtesy RCA

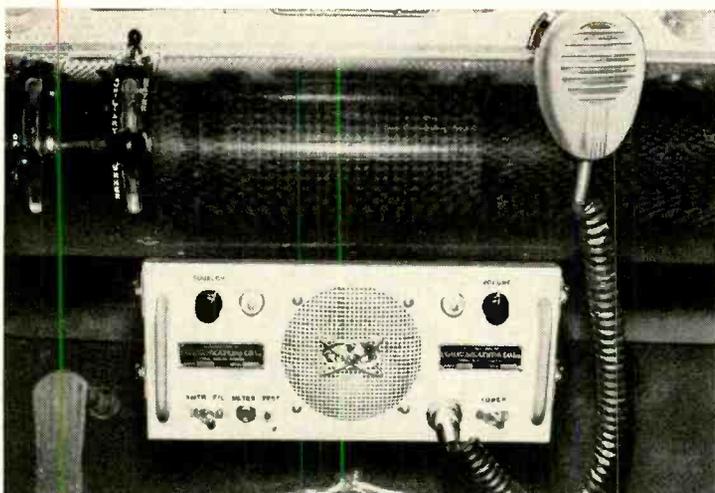

# ABC's of MOBILE RADIO

By LEO G. SANDS\*

*Part I—You can get into mobile radio even if you know nothing of that branch of servicing, but a little knowledge of the special problems of that field is a big help*

**T**ODAY, any citizen of the United States over 18 years of age is eligible for a license for a private two-way mobile radiotelephone system, which can be used for business or for personal pleasure and convenience. No technical knowledge is needed.

Sales of mobile radio equipment are running at the rate of more than \$89,000,000 per year. According to the latest FCC annual report, 1,200,000 transmitters have been licensed in all radio services combined. Each of the 390,000 radio-station authorizations covers one or more fixed or mobile transmitters. The 96,000 station licenses in the mobile radio services (land transportation, industrial and public safety) cover more than 875,000 transmitters, mostly mobile units. At the present rate of growth it won't be long before more than a million vehicles are equipped with two-way radio.

Mobile radio is used by almost every kind of commercial enterprise that uses vehicles. In addition, law-enforcement agencies in almost every community in the United States use two-way mobile radio. Factories, warehouses and wharfs use mobile radio to expedite material and merchandise handling. Power utilities, pipelines and railroads use mobile radio to communicate with vehicles traversing their rights-of-way. Motor trucks, railroad switch engines, taxicabs and tow trucks are regularly

dispatched by radio.

While such enterprises have been permitted to use mobile radio for several years, radio and TV service shops, delivery services and just plain Mr. Citizen were not eligible until the Citizens radio service was established. The FCC opened the air lanes to the butcher, the baker, the candlestick maker and the housewife.

But the Citizens radio service took off slowly because suitable equipment was not available at first. When it became available, it was considerably more expensive than mobile radio equipment for the other radio services. It is only now that Citizens band mobile radio equipment, competitive in price with other mobile equipment, is starting to appear on the market. Notwithstanding the \$200 to \$300 price differential, more than 28,000 Citizens radio authorizations have already been granted, covering more than 100,000 mobile units. But the market has just been tapped. Its growth is expected to be phenomenal.

While hams can communicate with other hams anywhere, users of mobile radio systems must restrict communications to their own systems except in emergencies. For example, a taxicab dispatcher can communicate only with the cabs operated by his company. Special arrangements must be made with the FCC to permit joint use of a base station by two or more firms. In the Citizens band, however, a licensee

may communicate with any other station with a Citizens radio license.

## History

Mobile radio is not new. Before the turn of the century, Thomas A. Edison demonstrated a system which permitted telegraphic communication between a moving train and a way station, without requiring physical connections between the mobile and fixed stations. While Edison's system was really not radio, it was the great-grandfather of the mobile radio art.

About two decades later, mobile radio was used by the Lackawanna Railroad for communicating from a fixed point with moving trains. It was not until after World War I that one-way radio systems were adopted for transmitting messages from fixed points to moving vehicles. Police departments were among the first to use radio. Messages were transmitted by radio on frequencies just above the AM broadcast band. These were picked up by receivers in the cars. Since the vehicles were not equipped with transmitters, patrol-car crews had to reply by land telephone.

Radio amateurs contributed greatly to the development of mobile radio. Hams had already gained considerable experience operating on the 5- and 10-meter bands when mobile transmitters for use on 30-40 mc were introduced. In some early police radio systems, the base station transmitted to vehicles on

\*Author of *Guide to Mobile Radio*. Gernsback Library No. 77.



In the Citizens band, service organizations are eligible for station licenses.

Photo by Cyril Glunk

A remote-control point for a base station equipped with a dial type selective calling.

Photo by Lars Speyer

the hf band and mobile units used AM transmitters operating in the 30-40-mc vhf band. Later, mobile vhf transmitters were developed. Some early sets used superregenerative receivers, but these were soon outmoded by crystal-controlled superheterodyne units.

Early mobile radio systems were AM. Shortly before World War II, the public was exposed to FM and, when the mobile radio business really got going at the close of the war, most manufacturers had started turning out FM mobile radio equipment. Some held out for AM but were forced to switch to FM because of popular demand, but not because of technical considerations.

The AM-vs-FM controversy is still with us. Most equipment now in use is FM. However, AM has been reintroduced in some current models. For example, the Kaar IMP (Industrial Mobile Phone), a low-power industrial radiotelephone for the 25-50-, 118-132- and 152-174-mc bands, is an AM unit. Amplitude modulation was chosen because it permitted the design of a more compact product and is compatible with aviation radio systems, which use AM exclusively. Another manufacturer, Bennett Laboratories, is introducing an AM 450-470-mc mobile radio.

While it would seem that there is plenty of air space for all who want to use mobile radio, extreme congestion is already a problem in highly populated areas. To make more channels available, industry is exploring the radio spectrum above 890 mc as well as AM, single-sideband AM and narrow-band FM, all of which require less band space than existing FM systems and permit narrowing the space made available to individual licensees.

Until recently, nearly all FM mobile radio systems used a 5-to-1 deviation ratio, the frequency being shifted as much as 15 kc above and below the center frequency by a modulating signal with a top frequency of 3,000 cycles. To conserve spectrum space, some mobile radio systems use narrow-band FM where deviation is limited to 8 kc above and below the center frequency.



Philco, for example, produced 30-40-mc equipment in 1949 in both narrow-band and standard deviation types.

Now, the FCC is splitting mobile radio channels so that many additional frequencies will be available. In the 152-162-mc band, where individual channels were spaced 60 kc apart, 30-kc separation is being adopted. Channel splitting, which makes more channels available, requires narrow-band transmission and equipment with greater transmitter frequency stability and receiver selectivity.

Communication at higher frequencies has been tried experimentally and in the not-too-distant future commercial equipment will be available for frequencies above 890 mc. More than 10 years ago, the Rock Island Lines and Sperry Gyroscope Co. experimented with train radio equipment for 2600 mc. These tests conducted under the supervision of Ernest A. Dahl, now a consulting engineer and then electronics engineer for the Rock Island, showed that useful results could be obtained. However, at that time, suitable equipment for this purpose could not be produced at reasonable cost. Nevertheless, these early tests proved

that microwave mobile radio is feasible.

#### Kinds of systems

A mobile radio system generally consists of a base station and one or more mobile units. It can have two or more mobile units and no base station. Or it may have two or more base stations and a number of mobile units.

A base station may be a compact, single-package transmitter-receiver assembly set on a desk and operated locally. Or it may be an elaborate rack-and-panel assembly installed in a shelter on a mountaintop and controlled from a point many miles away.

When there is more than one base station, they may be controlled at their respective locations or from a central point, selectively or simultaneously.

Right-of-way radio systems (see Fig. 1) may use wire lines or microwave circuits for remote control of two or more base stations. A pipeline or railroad may install unattended base stations every few miles along its right-of-way for communications with mobile units anywhere along its route. The base-station operator at a central point hears signals from mobile units that are picked up by any of the base sta-

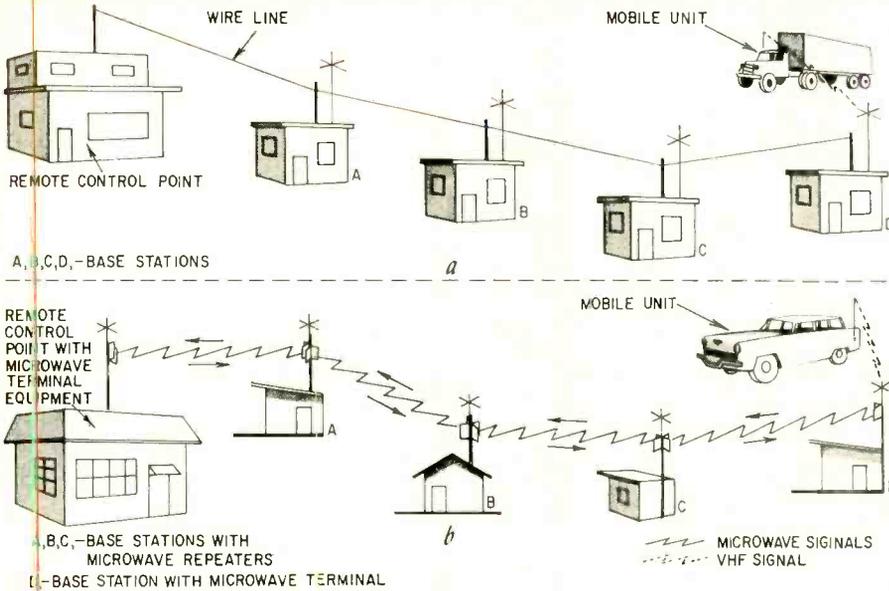


Fig. 1—Right-of-way mobile radio systems: a—all base stations may be connected to the remote-control point by wire; b—a microwave relay system may be the connecting medium.

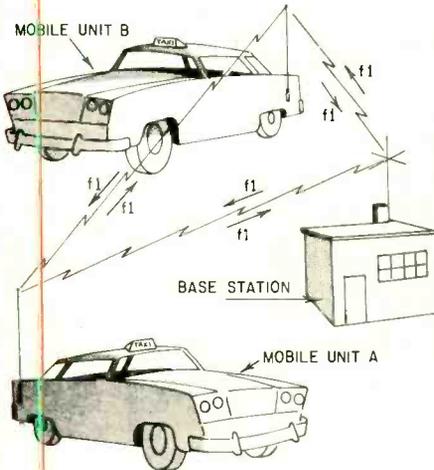


Fig. 2—Single-channel simplex operation. Base and mobile stations use the same frequency.

tions. With a telephone dial or push-buttons he can turn on any of the base-station transmitters along the right-of-way when required. In some systems he can mute all receivers except one when communicating with a specific station. Other systems may use more complex controls.

A mobile unit generally defines a radio station installed on a vehicle. A typical mobile unit includes a transmitter and receiver housed in a single enclosure mounted under the dash or in the trunk of the vehicle. A mobile unit may also be a hand- or pack-carried portable unit.

Most mobile systems are two-way. However, there are one-way systems such as those used for paging. Subscribers to a radio paging service listen with a pocket-size radio receiver or a mobile receiver in a vehicle, replying by land telephone. In some railroad yards, one-way portable transmitters are used for talking to yardmasters and other supervisors, who reply over

a loudspeaker paging system.

Generally, mobile units and base stations operated under a single licensee transmit and receive on the same frequency. Thus, all stations, both mobile and base, overhear all conversations from other associated stations within range. Operation is *push-to-talk*—the transmitter is normally turned off and is energized only when working. When transmitting, the receiver is disabled. A push-to-talk switch or pushbutton, generally located on the handle of the microphone or handset, disables the receiver and energizes the transmitter. To listen, the operator releases the push-to-talk button, reactivating the receiver and shutting off the transmitter. Two-way communication is maintained, but in only one direction at a time. This is called a *simplex* system (see Fig. 2).

Some mobile radio systems are two channels (see Fig. 3). In taxicab radio systems, for example, the base station transmits on one frequency and the

mobile units on another. The base station receiver is tuned to the mobile units' transmit frequency and the mobile receivers are tuned to the base station's transmit frequency. The base-station operator hears only the mobile units and the mobile units can intercept signals from the base station only. Communication between mobile units is not intended.

Common-carrier mobile telephone systems also operate on a two-channel basis. The base station transmits on one frequency and the mobile phones on another. The mobile units use the push-to-talk technique, activating the transmitter only when talking and disabling it when listening. However, the base station transmits and receives simultaneously. This is a form of *duplex* system.

All radio stations, except those operated by hams and those licensed in the Citizens band, are authorized to transmit only on frequencies specified on the license. Sometimes a radio station is licensed to operate on two or more frequencies. In the 460-470-mc Citizens band, specific frequencies are not assigned and licensees may operate on

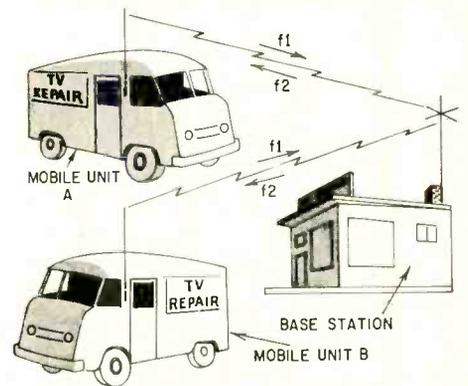


Fig. 3—Two-channel operation. Base station transmits on one frequency, mobile units on another.

any frequency they choose within the band.

Next month we will continue, discussion of range, frequency and licensing of mobile radio. END



"Can you see it all right, Al?"



The FM88BH tuner shown with the required mount-brackets.

The installed tuner mounts on the transmission tunnel and fits right in with the auto decor.



# FM TUNER

## for your CAR

FM tuners for automobiles now come as factory installed equipment

By HENRY O. MAXWELL

SINCE the early 1930's American motorists have listened to their favorite sportscasts, news, music and drama on AM auto radios while driving over the nation's streets, highways and byways. All too often, reception is marred by atmospheric static, interference from leaky power lines and neon signs, radiation from electric and electronic industrial apparatus and other forms of interference common to AM radio. Now, some lucky drivers can enjoy noise-free FM reception comparable to that available from their hi-fi tuners at home.

Until recently, only a few custom FM tuners and German FM-AM receivers for cars have been on the market. However, the set described here is available as a factory-installed unit.

The Bendix model FM88BH (Lincoln model FFC-15491-B) FM tuner is available for owners of 1958 Lincolns equipped with the 1958 Bendix-Lincoln Travel-Tuner AM radio (Bendix model R85BH, Lincoln part No. FFC-18805-C, -D). A similar model is available for 1959 cars.

The FM tuner (diagram p. 56) is an eight-tube superhet type powered by the car's 12-14-volt storage battery and a transistor B-supply. Its power input is 2 amps at 14.4 volts dc. Sensitivity is 10  $\mu$ v for 30-db quieting and audio output is 1.5 volts rms for full limiting. The tuner receives its primary voltage through plug P9 and a matching jack on the AM radio and feeds its audio output through plug P11 into the radio's first af amplifier.

Switch S1 selects the mode of operation. In the AM position, the audio output of the radio's AM detector enters the tuner on pin 1 of P11, passes through S1 and on to the radio's first af amplifier through pin 3 of P11. The output of the tuner's af amplifier (V8-b) is grounded to prevent feed-through. In the FM position of S1, the AM output is grounded, V8-b's output is fed to the radio's af amplifier and

the tuner's dial lights are turned on.

### The circuit

Rf amplifier V1 uses a 12AT7 in a low-noise cascode circuit. The antenna coil (L1) has two taps. One is wired through a length of shielded cable to antenna connector J12-P13. This connector is inserted in series between the antenna lead-in and the antenna terminal on the AM radio. The tap near the grounded end of L1 provides the proper match between the antenna and the grid circuit. The input grid of V1 is connected to the upper tap on L1. This minimizes circuit loading and insures good front-end selectivity and sensitivity.

The plate of the output (grounded-grid) section of the cascode rf amplifier is coupled to the grid of mixer V2-a. This grid is tapped down on rf coil L3 to increase further the selectivity of the front end. Oscillator V2-b is connected in a modified Colpitts circuit with feedback voltage developed across an rf choke (L4) in the cathode circuit (see *Radiatron Designer's Handbook*, 4th Edition, page 952).

The two-stage if amplifier uses sharp-cutoff 12AU6's. The if amplifier is followed by 12AU6's connected as cascade limiters operating with low plate and screen voltages and grid-leak bias. Bias is adjusted so the limiters saturate at low levels to provide good AM rejection.

The FM detector is a 12AL5 in a Foster-Seeley discriminator circuit. Its af output is applied to the grid of audio amplifier V8-b through a de-emphasis network. The dc output of the detector is fed directly to the grid of V8-a, the afc (automatic frequency control) tube.

The plate of V8-a is connected through a 12- $\mu$ f capacitor to the hot end of the oscillator coil (L5). V8-a's plate circuit appears as a variable reactance across the oscillator tank coil. This reactance is controlled by the dc

voltage developed by the discriminator and fed to the afc grid. If the oscillator drifts off frequency, the intermediate frequency changes and a positive or negative voltage is developed at the discriminator output. This error voltage is of the proper polarity and magnitude to cause the afc tube to swing the oscillator back to the correct frequency.

The B-plus power supply is transistorized with a 2N419 transistor oscillator in place of the more conventional vibrator. The oscillator operates at approximately 400 cycles. Potentiometer R32 controls the transistor current. The voltage developed across the secondary of the power transformer (T6) is rectified by a selenium rectifier and filtered to deliver 75 volts to the tuner's B-plus line. A varistor is used as a bleeder and voltage regulator to maintain the plate and screen voltages at the optimum level and to minimize changes in the oscillator frequency with changes in the battery voltage.


### Installation precautions

Before installing the tuner or connecting it to a primary power source, turn R32 fully counterclockwise. Connect the positive side of a 14.4-volt dc source to the A-plus lead (P9) and the negative side to the chassis. Set S1 to AM and let the tuner warm up for several minutes. Adjust the supply voltage to exactly 14.4.

Set a vtvm to its 100-volt dc range and connect the positive test lead to the lug on the top of varistor R34 (the B-plus line) and the negative test lead to the chassis. Carefully turn R32 clockwise until the meter reads exactly 75 volts. *Do not overshoot 75 volts or the transistor may be damaged by excessive current. Be careful when adjusting R32. Its case is above chassis potential and any short from case to chassis, even momentary, will damage the transistor.* END
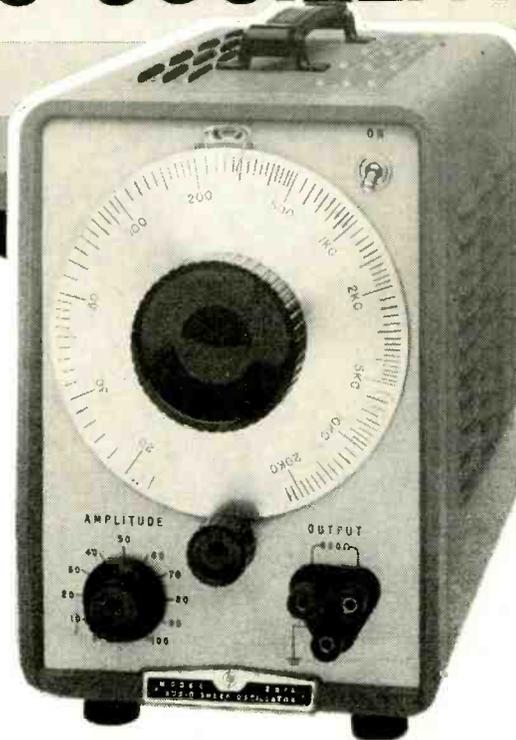
# New kind of AUDIO OSCILLATOR

*A push-pull audio sweep generator — Hewlett-Packard model 207A — derived from the familiar Wien-bridge circuit covers 20-20,000 cycles in a single band*



By **ROBERT F. SCOTT**  
TECHNICAL EDITOR

**N**EARLY all sine-wave audio signal generators are R-C types and most use the time-tested Wien bridge as the frequency-determining element. This article discusses the Hewlett-Packard model 207A audio sweep generator covering 20 to 20,000 cycles in one sweep of the tuning dial and shows how it evolved from the basic Wien-bridge oscillator.

The 207A is a balanced R-C type oscillator with a 1,000-to-1 tuning ratio covering the audio spectrum from 20 to 20,000 cycles in a single band. (This is quite an innovation when compared to the average R-C type generator with its 10-to-1 tuning ratio requiring three bands for the same coverage.) It is especially useful for measuring response of amplifiers, speakers, transformers and other audio components. The tuning-dial shaft extends through the rear of the cabinet and may be fitted with a reversing type motor for scanning the audio spectrum automatically. Also, an accessory potentiometer (type 207A-15) may be ganged to the shaft and connected to an external dc source to supply a voltage proportional to the logarithm of the frequency. This voltage may be used to drive a recorder or to supply horizontal deflection voltage to an oscilloscope to trace the response of the unit under test. The oscillogram shows the type of response pattern that may be made on an amplifier or similar device.

The circuit of the 207A is shown in Fig. 1.

### Basic Wien-bridge oscillator


The basic circuit of the garden-variety Wien-bridge oscillator is shown in Fig. 2. Fundamentally, the circuit consists of an amplifier providing 360° phase shift with positive feedback from its output to the input through a frequency-selective Wien bridge. The selective network, R1-C1 and R2-C2, acts as a voltage divider supplying one-third the total output voltage to the grid of the first stage of the amplifier. The circuit oscillates at a frequency  $F_o$  where phase shift through the network is zero and  $E_{feedback}/E_{output}$  equals  $\frac{1}{3}$  (see Fig. 2).

The frequency  $F_o$  of oscillation is determined from the equation:

$$F_o = \frac{1,000,000}{2\pi RC}$$

where  $F_o$  is in cycles, R in megohms and C in micromicrofarads. The frequency-determining networks are generally tuned by a dual-section variable capacitor substituted for C1 and C2 with the various ranges selected by switching in matched resistors for R1 and R2.

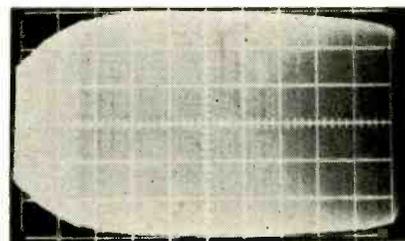The tuning capacitor generally has a capacitance ratio of 10 to 1. Fig. 3 shows that as C is tuned through its range, its reactance  $X_c$  varies through a 10-to-1 ratio—as indicated by the



Oscillogram produced by the model 207A.

shaded area—and frequency variation for each range is also 10 to 1.

Resistive network R<sub>r</sub>-R<sub>L</sub> (Fig. 2) is connected as a voltage divider supplying a negative feedback voltage to the cathode of the amplifier's input stage. R<sub>L</sub> is generally a tungsten filament lamp whose resistance increases with current through it. When network R<sub>r</sub>-R<sub>L</sub> is properly proportioned, R<sub>L</sub> varies the amount of negative feedback, keeping the amplifier's output constant and minimizing distortion.

The thermal time constant of R<sub>L</sub> is one of the principal factors that determine the lowest frequency at which the circuit will oscillate satisfactorily. The total current through the lamp (R<sub>L</sub>) consists of the direct cathode current, the ac component of the cathode current and the ac signal fed back through R<sub>r</sub>. The two ac components are equal in frequency and phase and may be combined. When the frequency of oscillation is low and approaches the thermal time constant of the lamp, R<sub>L</sub>'s resistance tends to vary at the

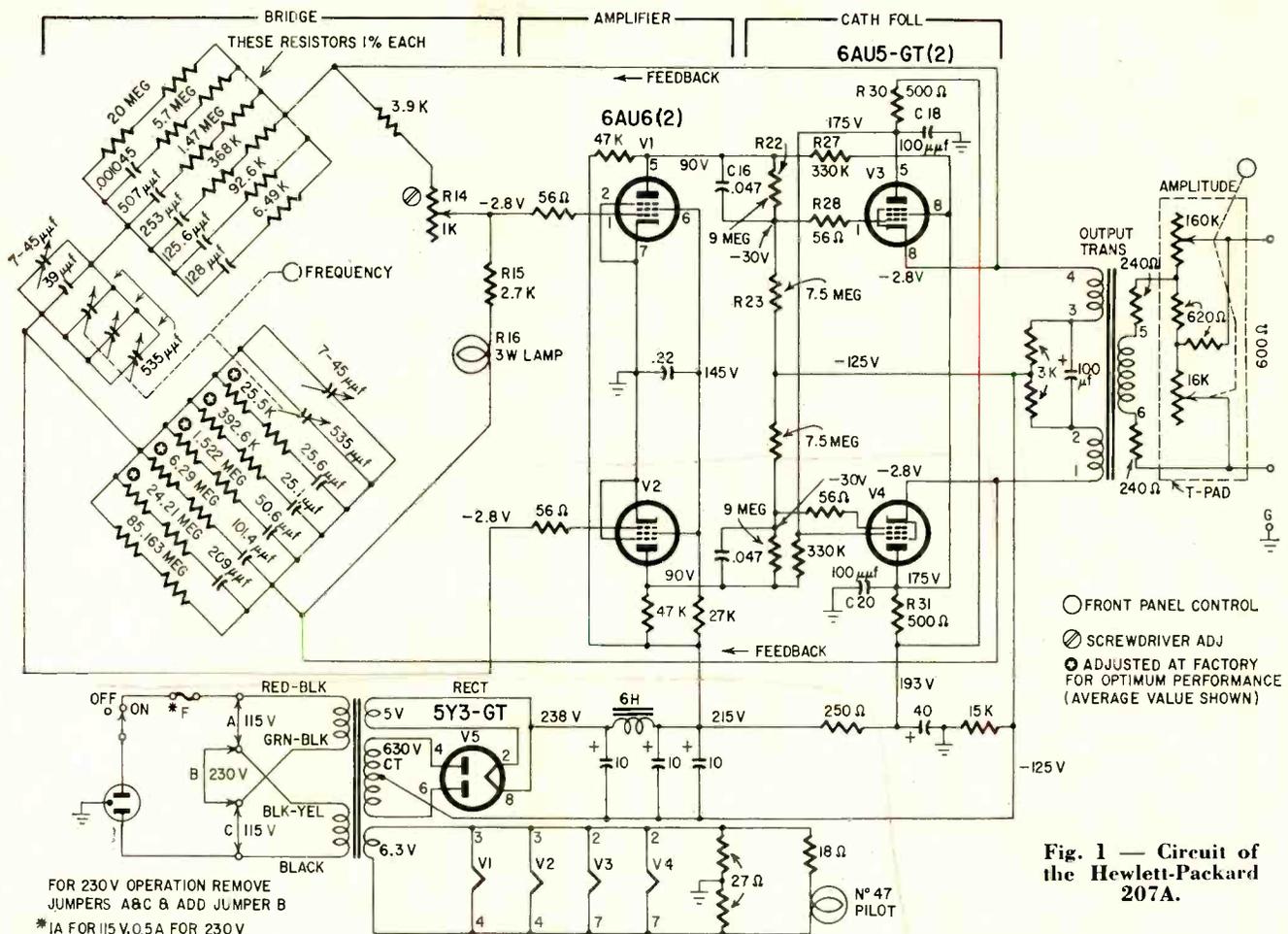


Fig. 1 — Circuit of the Hewlett-Packard 207A.

fundamental frequency. This periodic variation in amplifier gain produces unwanted harmonics in the output.

As the frequency decreases, the impedances in the frequency-determining networks increase. On the lower ranges C2's insulation resistance must be much higher than R2's resistance.

**Balanced R-C oscillator**

Fig. 4 is the basic circuit of the balanced R-C oscillator used in the Hewlett-Packard 200J, 202C and similar models. Here we have two balanced amplifiers fed from a floating bridge and each supplying 180° phase shift. The outputs of amplifiers A and B are 180° out of phase. Note that in this case, C1 and C2 are not equal—C1 equals 2C2 and R2 equals 2R1—and network impedances Z1 and Z2 are equal.

R<sub>r</sub> and R<sub>l</sub> are selected so R<sub>r</sub> is slightly greater than R<sub>l</sub> when the circuit is oscillating and delivering normal output. The input grid of amplifier A will be driven by a small fraction of amplifier B's output. The output of amplifier B is in phase with the normal signal on A's grid so A's output tends to increase. The increase in A's output increases the positive feedback voltage applied to amplifier B. Thus, both amplifiers are excited by positive feedback voltages, and oscillations are sustained.

In this balanced circuit, there is no

dc flow through lamp R<sub>l</sub> and the circuit oscillates satisfactorily at half the frequency that can be obtained with the same thermal time constant with dc in the circuit.

Another advantage of the balanced oscillator is that it does not place such stringent requirements on C2's insulation resistance. In the single-ended circuit (Fig. 2) the voltage across C2 is one-third the output voltage. In the balanced circuit (Fig. 4) the voltage across C2 is no higher than E<sub>out</sub>/2μ, where μ is amplifier gain. In this application μ is around 50. Thus the voltage across C2 is reduced by a factor 3/2μ and the leakage current in C2's insulation resistance is only about 3% of that in a similar single-ended circuit, greatly improving operation.

**Hewlett-Packard 207A**

The circuit of the 207A in Fig. 1 is basically the same as the balanced Wien-bridge oscillator in Fig. 4. However, resistive elements R1 and R2 have been replaced by complex impedances composed of parallel networks of resistors and capacitors in series. The frequency-determining impedance elements in the variable arms of the bridge each have an impedance slope of minus 2/3. As the tuning capacitor is rotated through its range, the reactance varies from X<sub>c</sub> to 10X<sub>c</sub> and the oscillator covers a tuning range of 1,000 to 1 as shown in Fig. 5.

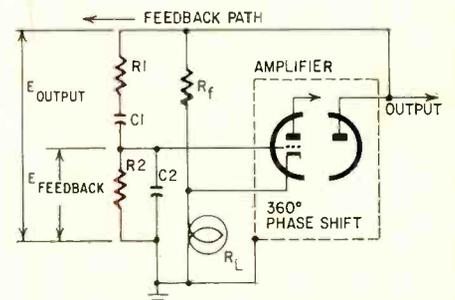


Fig. 2—Basic Wien-bridge oscillator circuit.

In Fig. 1, the oscillator consists of push-pull amplifiers V1 and V2 and cathode followers V3 and V4. V1's grid is fed from the junction of R14 and R15 on the resistive voltage-divider arms of the bridge and V2's grid is coupled to the junction of the frequency-determining arms.

The circuit is push-pull throughout

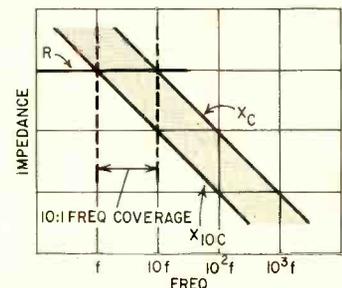


Fig. 3—Reactance plot of one R-C pair in a basic R-C oscillator.

## TEST INSTRUMENTS

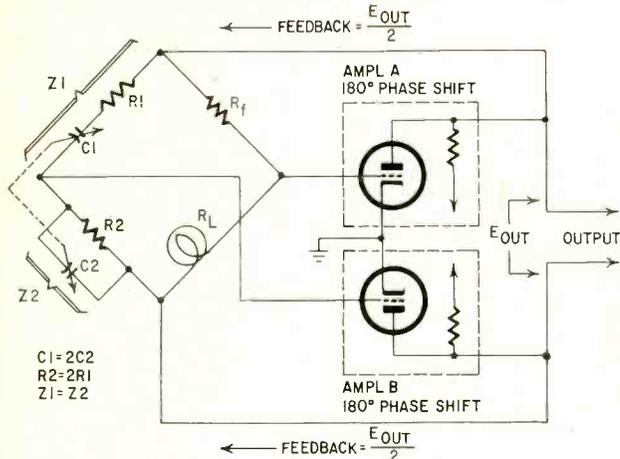


Fig. 4—Basic circuit of the balanced R-C oscillator used in the Hewlett-Packard 200J, 202C and similar models.

so the signals at the output cathodes are 180° out of phase. Assume that a minor disturbance causes V1's grid to swing in a positive direction. This produces a negative-going signal on V1's plate and V3's cathode. If the initial disturbance contains a signal for which the phase shift in the frequency-

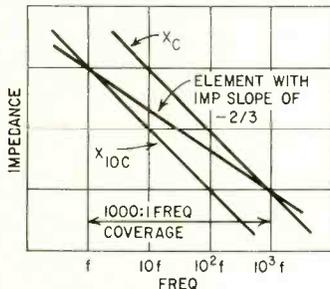


Fig. 5—Reactance plot of the variable arms in the bridge.

determining network is zero, the output of V3's cathode is fed to V2's grid. This signal is shifted 180° in passing through V2 and is passed through V4 and the bridge to reinforce the original signal on V1's grid. Since the outputs of the cathode followers are 180° out of phase and each amplifier excites the input of the other, the circuit oscillates at the frequency determined by the tuned network in the bridge.

The amplitude of the output signal is stabilized against variations in operating voltages and tube characteristics by negative feedback voltages developed across the resistive arms of the bridge. Any unbalance in the output of the cathode followers increases or decreases the amount of feedback on V1's grid, varying the tube's output in the direction of balance.

The output stage (V3 and V4) is transformer-coupled to the external load and is designed for zero cathode-to-cathode impedance. This is done by providing positive feedback from each output plate to the control and screen grids of the opposite member. Each screen grid is direct coupled to the plate of the opposite tube. The positive feedback is developed across the 500-ohm resistor in series with the plate lead (R30 and R31).

Feedback voltage for the control grids is applied across voltage dividers

that are insensitive to frequency. These are R-C types similar to compensated attenuators used in many oscilloscopes.

Fig. 6 shows the basic voltage divider at V3's control grid. The resistive elements consist of 9-meg and 330,000-ohm resistors in series between the control and screen grids and the resistance between control grid and ground. The capacitive elements across the upper arm of the divider are C16 and inter-electrode capacitance  $C_{gs}$  between the control and screen grids. The lower arm is shunted by capacitance  $C_p$  between grid and ground. Series resistor R28 helps to flatten the frequency response of the signal applied to V3's grid. It does not affect the positive feedback.

In addition to providing a very low output impedance, this positive feedback network also helps hold the out-

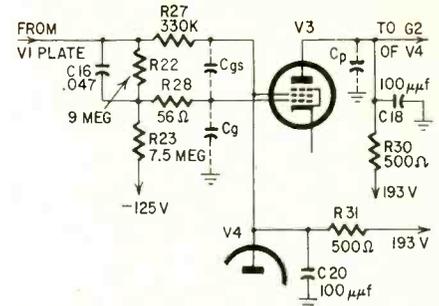


Fig. 6—Details of the voltage divider at V3's control grid.

put voltage constant regardless of variations in load impedance. The amount of positive feedback applied to each cathode follower increases as the load impedance decreases.

At high frequencies, the capacitance between the output cathodes and ground may be high enough to short the cathodes to ground for ac signals. This makes the output stage very unstable and it tends to break into oscillation. However, at frequencies where the output stage would become unstable C18's reactance is low enough to reduce the available feedback voltage and insure stability.

The output transformer's secondary works into a balanced output circuit with a bridged-T attenuator (AMPLITUDE control) in one leg. The output impedance is 600 ohms. Output is 10 volts into a 600-ohm load either balanced or unbalanced. For unbalanced operation the output terminal connected to terminal 6 on the output transformer is grounded. END



Sweet  
Sounding  
Words . . .

are all right in their place. But when it comes to buying tubes by mail make sure the words are clear and to the point! When you buy from RADIO-ELECTRONICS mail order tube advertisers you don't have to worry. Since the January 1956 issue we have insisted that advertisers tell you that their tubes are new and unused—or that they are seconds, rejects or imperfect if that's the case. You need not be afraid of being taken in by sweet sounding words.

# SIMPLE SUPER TIME BASE

By TOM JASKI

*An external triggered-sweep generator you can use with any oscilloscope*

A SIMPLE inexpensive way to extend the usefulness of your oscilloscope is to add a triggered sweep. If you have a medium-price scope, particularly a late-model kit, modifying the scope itself is not an easy job, even after you figure out what must be done. Most of them now use printed circuits, and monkeying with the printed boards is inviting trouble.

A more sensible approach is to build an external sweep generator which can be triggered. Some of these have appeared before (see "Delay and Timing Generator," RADIO-ELECTRONICS, September, 1956, page 50). Although adequate, a lot of them are complicated instruments which you might hesitate to build unless you expected to use them a lot.


Here is a simple version of a sweep generator which has all the important characteristics of the more complicated ones, uses only two tubes and is easy to build. The generator will sweep repetitively or by trigger, with sweep speeds of about 0.2 second up to 0.2  $\mu$ sec per inch, with repetition rates ranging from 1 every 5 seconds to 1,000,000 per second. The sweep is almost perfectly linear over this tremendous range. The generator also provides blanking pulses and can be triggered by as little as 15 volts peak.

The sweep generator is useful wherever you need a single sweep. For example, in ignition analysis with your scope (RADIO-ELECTRONICS, September, 1957, page 46), you want to trigger the generator for each ignition pulse on one spark plug. To do this use the hookup shown in Fig. 1. The input from the breaker points is fed to the oscilloscope through a 100,000-ohm resistor, and with a 100- $\mu$ f capacitor across the scope's input. This setup provides the same patterns as the ignition analyzer if you are careful to set the generator sweep time to a value approximately four times as fast as the trigger pulses come in, or six or eight times, depending on the number of cylinders you want to observe.



Another use is in photographing transients. The trigger which starts the generator should come the same instant the transient starts and the entire transient will be swept, if the sweep speed is the same length as the duration of the transient or a little longer.

Even for normal repetitive sweep the little generator is convenient. Its range is greater than that of sweep generators in most scopes, its linearity is a little better, it synchronizes quite well, has no jitter, has a good blanking pulse and

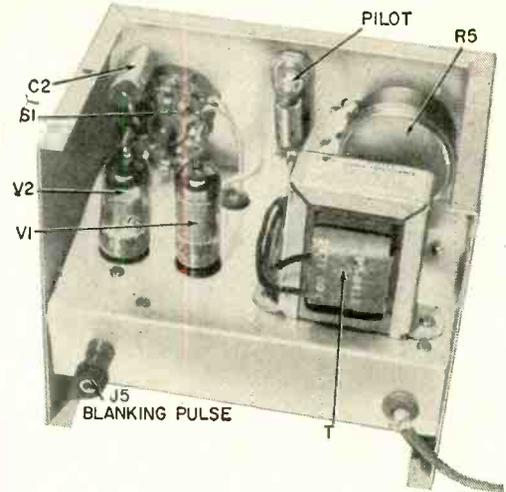
Top-chassis view. Note the blanking-pulse output on the rear apron.



Closeup of the sweep generator.

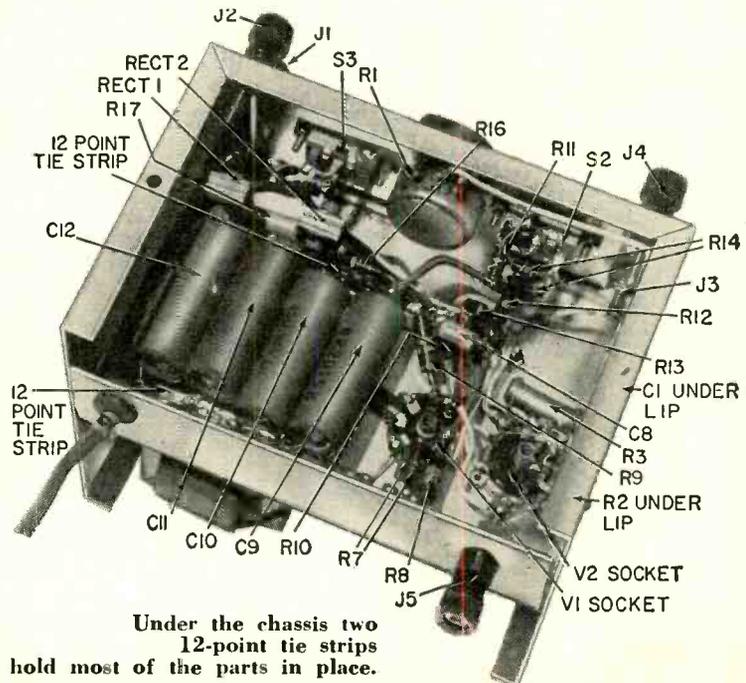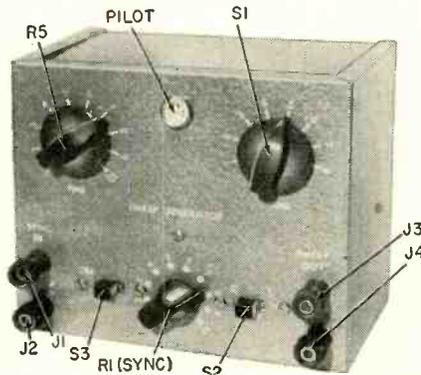



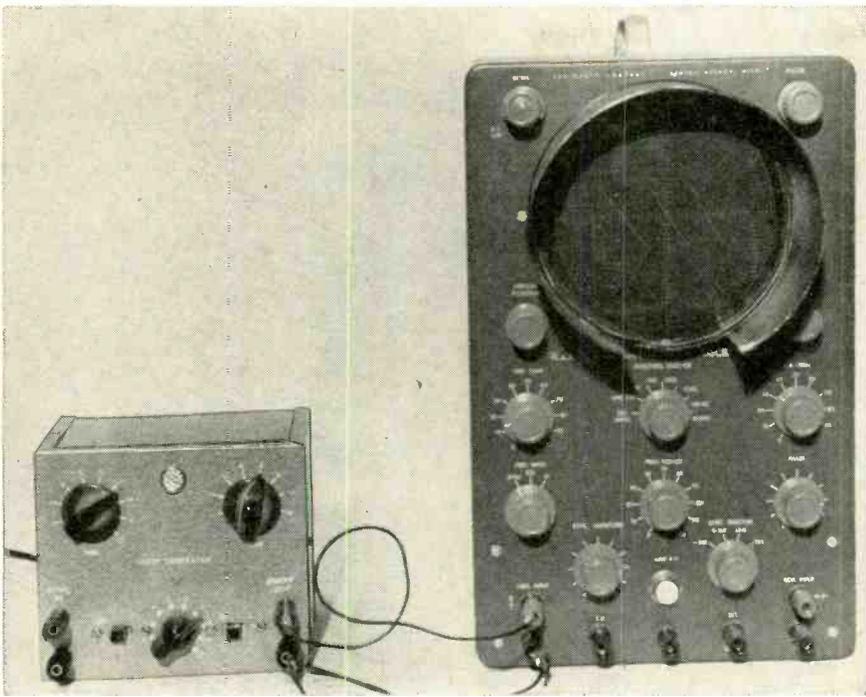

Simple Super Time Base hooked up to scope and ready to use.

use a potentiometer for R12.

However, this adds another control, and the design was worked out to allow continuous repetitive operation at one point, selected by switch S2. This, in the trigger (T) position holds the tube just below the point where it can act spontaneously. You will note that I had to parallel two resistors to make R14. This is the resistor which provides the difference in bias between triggered and repetitive operation. It may be best to adjust this value to exactly what is required for the tube you use. There may be a slight difference in tubes. If the tube refuses to be cut off at approximately these values however, you may have a gassy one. Try another.

From this discussion you can also see that the voltages at the ends of R5 determine the sweep rate to the extent that they affect the voltage of the slider on R5. Thus, by adjusting R4, you can adjust exactly the lowest speed for potentiometer R5, and with R6 the highest speed. These two pots (if included) should be 10,000 ohms each.

Again for the sake of simplicity, I left them out of my generator, because the 25,000-ohm pot provides well over a 10-to-1 sweep ratio, and calibration was not too important to me.

The "kick" given by capacitor C8 to the suppressor is, of course, a negative pulse and it comes exactly at the end of the rundown. Thus it is just right for a blanking pulse and we use it for that purpose. Again we must specify that this connection does not allow us to load the circuit—the blanking pulse must be isolated or fed into a very-high-impedance circuit. On my scope I can connect it directly to the blanking terminal, and it does a fine job without affecting the sweep speed materially.

The results of the circuit are obvious

from the oscillograms. Figs. 3-a and 3-b show the sweep and the blanking pulse, respectively, at 650 kc. This is a very acceptable linearity at that frequency. Fig. 3-c shows the sweep and blanking pulse superimposed at 20 cycles, and again you will notice the linearity of the trace.

Fig. 3-d appears to be nonlinear. There the generator was used to sweep the beam across the C-R tube face for 1 second, with a 60-cycle voltage on the vertical input. The nonlinearity is due to the scope's horizontal amplifier which was not designed to handle such a low frequency. With a dc horizontal amplifier this trace would remain linear.

#### Construction hints

Construction is entirely conventional. Two 12-point terminal strips were used to hold the parts rigidly and neatly. Switch S1 was prewired. All the capacitors are soldered into place and leads attached to the contacts. No unusual or special parts were used. The photos show the top and bottom of the chassis. The tie points provide a rigid mounting for the selenium rectifiers, the resistors and capacitors of the power supply and others as well. The blanking-pulse output was brought out to the rear to keep the front panel symmetrical and because it is the most convenient place. The lead from there to the scope rear is then out of the way.

#### Using the super time base

There are no difficulties in putting the unit into operation. The only juggling which may have to be done was mentioned: the exact value of R14 may vary a little. Leave this resistor out, and turn on the generator. Then with a potentiometer temporarily clipped in place of R14 determine the point where

S2 just changes the sweep from repetitive to nonrepetitive. Disconnect your potentiometer, measure the resistance and put that same value in its place. An excellent trigger source for the generator is the Differentiating Amplifier described in the September, 1958, issue of RADIO-ELECTRONICS, page 100.

If you have included R4 and R6, remember that when you adjust one, the voltages on the other will be affected somewhat. The best procedure is to adjust one, either the upper or the lower limit, to approximately the desired range of sweep speeds. Then adjust the other one. If the first one adjusted is R6, as R4 is made smaller, R6 will also have to have a little less resistance, and vice versa. The exact amount cannot be stated here, it depends on the original setting of the first one to be adjusted.

As mentioned, if you do not insist on accurate calibration, leave R4 and R6 out. The generator works well enough without them.

The whole assembly shouldn't cost over \$15, and most of us have a good many of the parts in our junkboxes and need to buy only a few items.

Whatever you spend on it, if you need a triggered sweep, this generator is about the most inexpensive and reliable way to obtain it. **END**


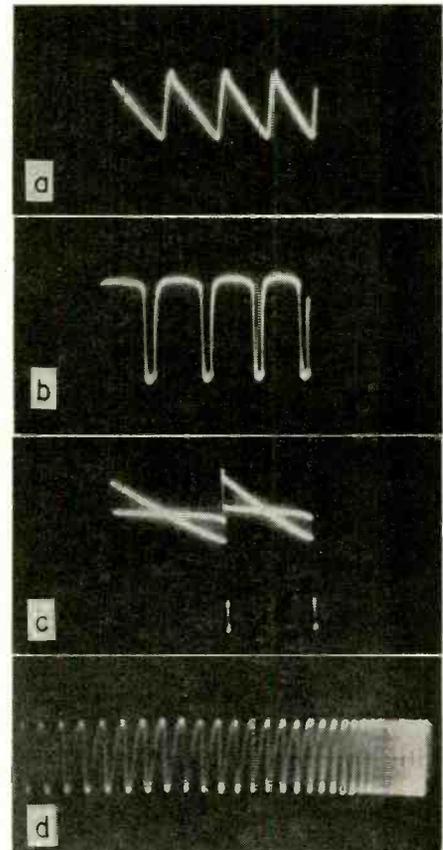


Fig. 3—Some scope patterns obtained from the triggered sweep generator; a—650-kc sweep voltage; b—650-kc blanking pulse; c—20-cycle sweep and blanking pulse (double exposure); d—slow sweep (1 second across scope face), nonlinearity due to scope's horizontal amplifier.

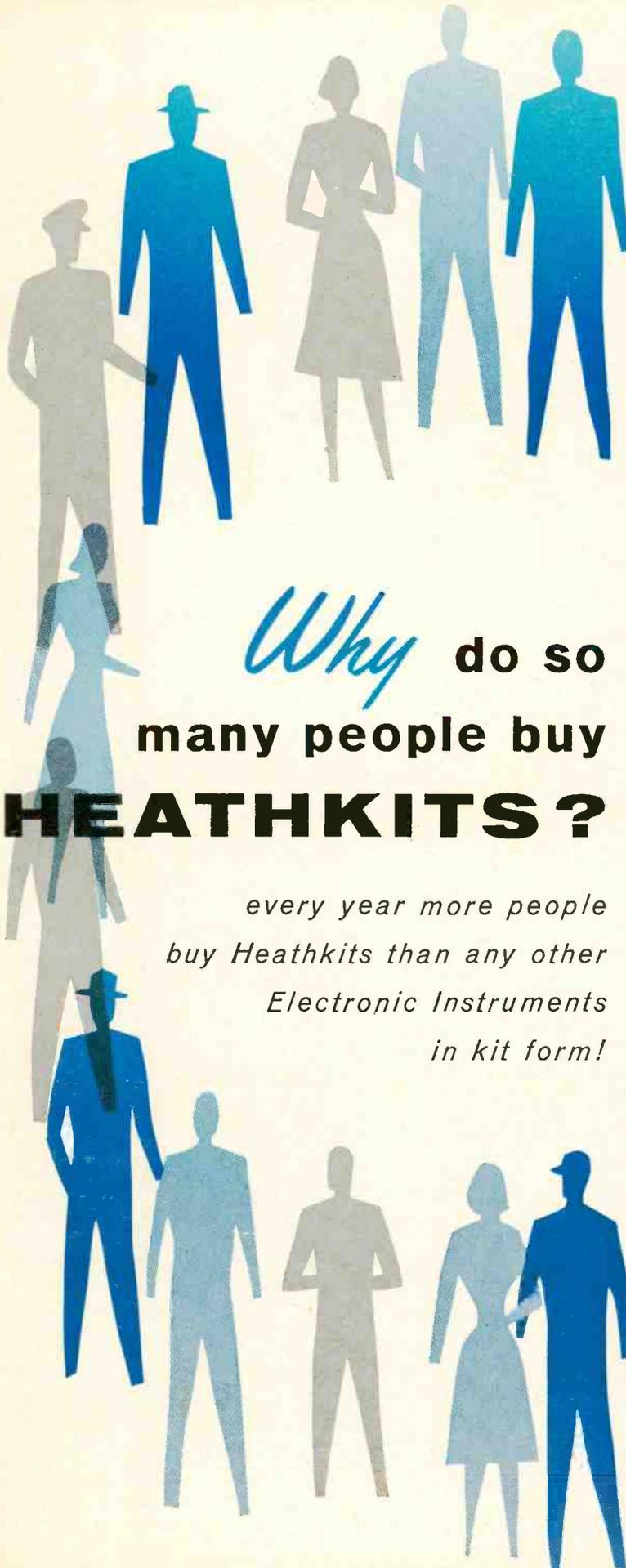

*Why* do so many people buy **HEATHKITS?**

*every year more people buy Heathkits than any other Electronic Instruments in kit form!*

## **Here are a few reasons why...**

### **EASY TO BUILD**

Heathkits are engineered for easy kit construction. You need no electronic or kit building experience whatsoever to successfully complete your own kit. Use of printed circuit boards and pre-wired, pre-aligned assemblies cut construction time. Manuals are carefully prepared, employing step-by-step instructions written in simple, non-technical language. Large pictorial diagrams and photographs show you exactly where each part goes.

### **LASTING QUALITY**

Only top quality components go into Heathkits, assuring you of a finished product that is unsurpassed in performance, dependability and endurance. Rigid quality control standards are maintained at the Heath factory to see that each component lives up to its advertised specifications. Heathkits are conservatively rated. No performance claims are made that are not thoroughly proven and tested under the most stringent laboratory conditions.

### **ADVANCED ENGINEERING**

Progress in electronics engineering never stands still at Heath. The latest developments in circuit design and components are exploited by Heath engineers, offering you superior performance at lower costs. New advances in all fields of electronics are carefully watched by Heath engineers to keep abreast of the rapidly growing industry. The modern, up-to-date styling of Heathkits make them a handsome addition to your home or workshop.

### **WORLD-WIDE REPUTATION**

A pioneer in do-it-yourself electronics, Heath Company, over more than a decade, has established public confidence in its products both in the United States and abroad. Today, as the world's largest manufacturer of electronic kits, Heath stands as the leader in its field.

### **GREATER SAVINGS**

Do-it-yourself Heathkits save you up to 1/2 the cost of equivalent ready-made equipment. Direct factory-to-you selling, eliminating middle-man profit, plus the tremendous Heath purchasing power mean even further savings to you. And the convenient Heath Time Payment Plan allows you to use and enjoy your Heathkit NOW, while you pay for it in easy installments.



**HEATH COMPANY**  
Benton Harbor 20, Michigan

 a subsidiary of Daystrom, Inc.

## TRANSISTOR PORTABLE RADIO KIT

Fun for the whole family, this easy-to-build 6-transistor portable radio is ready to go wherever you go. The modern molded plastic case with pull-out carrying handle and fully enclosed back add beauty and convenience to this splendid kit. Six name-brand (Texas Instrument) transistors are used for good sensitivity and selectivity. The 4" x 6" PM speaker with heavy magnet provides "big set" tone quality. Use of this large speaker and roomy chassis make it unnecessary to crowd components adding greatly to the ease of construction. Transformers are prealigned making the radio ready for use as soon as kit is assembled. A built-in rod-type antenna assures good reception in all locations. Six standard flashlight batteries are used for power, providing extremely long battery life (between 500 and 1,000 hours) and they can be purchased anywhere. Stylish cabinet is two-tone blue molded plastic with gold inlay and measures 9" L. x 7" H. x 3 3/4" D. Shpg. Wt. 6 lbs.

**MODEL XR-1L:** Identical to XR-1P except in handsome leather case instead of plastic case. Leather carrying strap included. Shpg. Wt. 7 lbs.

**LEATHER CASE:** Can be purchased separately if desired. Fits all XR-1P and earlier XR-1 chassis. No. 93-1. Shpg. Wt. 3 lbs. **\$6.95.**

HEATHKIT  
MODEL XR-1P  
**\$29<sup>95</sup>**



MODEL XR-1L **\$34<sup>95</sup>**

## NAVIGATE BY PORTABLE RADIO



HEATHKIT  
MODEL DF-2  
**\$69<sup>95</sup>**

### 2-BAND TRANSISTOR PORTABLE RADIO DIRECTION FINDER KIT

Enjoy the safety, convenience and entertainment of this self-contained, self-powered, six-transistor superheterodyne radio direction finder. It receives aeronautical and marine beacons as well as standard band broadcasts with startlingly clear tone reproduction over a long range. Covering the beacon band from 200 to 400 kc and broadcast band from 540 to 1620 kc, the DF-2 is designed to take directional "fixes" on both aircraft and marine beacons as well as standard broadcast stations, while providing the entertainment of a high quality transistor portable radio. You are able to receive aircraft weather reports every thirty minutes and constant Coast Guard beacons on the 200 to 400 kc band. A dial light is provided for night operation. Power is supplied by six standard flashlight batteries which will last you up to one year under normal operation. Shpg. Wt. 9 lbs.



## POWER CONVERTER KIT

Now you can operate your TV set, radio, razor, and other AC electrical equipment directly from your 12-volt boat or car battery. With the Heathkit Power Converter you can enjoy the convenience of home electricity whether boat cruising or on automobile trips. Two power transistors are employed for years of trouble-free, dependable service. No moving parts to wear out, no tubes to replace. Shpg. Wt. 8 lbs.




MODEL PC-1  
**\$24<sup>95</sup>**

## ELECTRONIC IGNITION ANALYZER KIT

Ideal for use on automobiles, boats, aircraft engines, etc., the IA-1 checks ignition systems with the engine in operation (400 to 5,000 RPM). Shows the condition of coil, condenser, points, plugs and ignition wiring. Shows complete engine cycle or just one cylinder at a time. Two test leads are supplied, each 10' long, which will enable you to reach either the breaker points or the spark plug wires. Shpg. Wt. 20 lbs.



MODEL IA-1  
**\$59<sup>95</sup>**

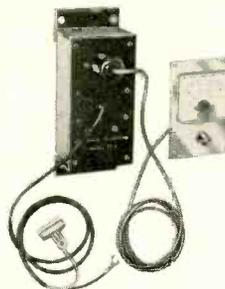

MODEL TI-1  
**\$25<sup>95</sup>**

## ELECTRONIC TACHOMETER KIT

Useful on inboard and outboard boats, as well as in automobiles, the TI-1 operates directly from the spark impulse of the engine. Use on any spark ignited 2 or 4 cycle engine of any number of cylinders. Completely transistorized, it works with 6, 8, 12, 24 or 32 volt DC systems. Indicates revolutions-per-minute from 0 to 6,000. Calibration control provided for adjusting to engine type. Easy-to-build and easy-to-install. Shpg. Wt. 4 lbs.

## PROFESSIONAL OSCILLOSCOPE KIT

Everything you could possibly want in an oscilloscope is found in the new Heathkit model OP-1. Featured are DC coupled amplifiers and also DC coupled CR tube un-blanking. The triggered sweep circuit will operate on either internal or external signals and may be either AC or DC coupled. The polarity of the triggering signal may also be selected, and any point on the waveform may be selected for the start of the sweep by using the "triggering level" control. An automatic position is also provided, in which the sweep recurs at 50 cycle rate, but can be driven over a wide range of frequencies with no additional adjustment. Prewired terminal boards are used for rapid, easy assembly of all critical circuits. Power supply is transformer operated utilizing silicon diode rectifiers and is fused for protection. Handsome cabinet features silver anodized front panel with red and black lettering and matching knobs. Shpg. Wt. 34 lbs.

HEATHKIT  
MODEL OP-1

**\$179<sup>95</sup>**



## VARIABLE VOLTAGE REGULATED POWER SUPPLY KIT

Invaluable in experimental and design work, the PS-4 eliminates the need for building up a separate power supply for each new circuit tried. It provides a convenient source of variable regulated B+, variable bias voltage and filament voltage for labs and work shops. The PS-4 supplies regulated B+ output continuously variable from 0 to 400 volts DC at up to 100 ma, bias voltage variable from 0 to -100 volts DC at 1 ma, and filament voltage of 6.3 volts AC at 4 amps. Separate panel meters continuously monitors voltage and current output. Rugged, top-rated components used throughout for long, reliable service. Shpg. Wt. 16 lbs.



HEATHKIT  
MODEL PS-4

**\$54<sup>95</sup>**

Your best  
dollar value...



**HEATH COMPANY** • Benton Harbor 20,  
Michigan  
A subsidiary of Daystrom, Inc.

## "EXTRA DUTY" 5" OSCILLOSCOPE KIT

Laboratory quality at utility scope price makes this instrument an unusual value. The Heath patented sweep circuit functions from 10 CPS to better than 500 kc in five steps, giving you five times the usual sweep obtained in other scopes. Vertical frequency response extends from 3 CPS to 5 mc +1.5 db -5 db without extra switching. An automatic sync circuit with self-limiting cathode follower provides excellent linearity and lock-in characteristics. Extremely short retrace time and efficient blanking action are characteristic of this scope. Frequency response of the horizontal amplifier is within  $\pm 1$  db from 1 CPS to 200 kc. Horizontal sensitivity is 0.3 volts RMS-per-inch. Construction is simplified through the use of two etched metal circuit boards and precut, cabled wiring harness. Complete step-by-step instructions and large pictorial diagrams are supplied for easy assembly. An ideal scope for all service applications as well as in standard or color TV servicing. Shpg. Wt. 22 lbs.



HEATHKIT  
MODEL O-12

**\$65<sup>95</sup>**



HEATHKIT  
MODEL TO-1

**\$16<sup>95</sup>**

## TEST OSCILLATOR KIT

Provides the test frequencies most often used by servicemen in repairing and aligning modern broadcast receivers. Five fixed-tuned frequencies (262 kc, 455 kc, 465 kc, 600 kc and 1400 kc) are quickly selected for troubleshooting or alignment of the IF frequency and high and low end of the broadcast band for proper tracking. Shpg. Wt. 4 lbs.



MODEL SG-8 **\$19<sup>50</sup>**

## RF SIGNAL GENERATOR KIT

A "must" for any beginning serviceman, this indispensable instrument is used for aligning tuned circuits quickly and tracing signals in faulty RF, IF and audio circuits. Covers 160 kc to 110 mc on fundamentals in five bands and from 110 mc to 220 mc on calibrated harmonics. Coils are pre-wound and calibrated. Complete with output cable and instructions. Shpg. Wt. 8 lbs.



MODEL AG-9A **\$34<sup>50</sup>**

## AUDIO SIGNAL GENERATOR KIT

This unique generator uses three rotary switches to select two significant figures and a multiplier to determine audio frequency, allowing return to the exact frequency previously measured when making multiple frequency measurements. Covers 10 CPS to 120 kc with less than .1 of 1% distortion between 20 and 20,000 CPS. Shpg. Wt. 10 lbs.



MODEL TS-4A **\$49<sup>50</sup>**

## TV ALIGNMENT GENERATOR KIT

TV service technicians will appreciate the outstanding features found in this sweep generator. Provides essential facilities for aligning FM, monochrome TV or color TV sets. The all-electronic sweep circuit employs a trouble-free controllable inductor which varies frequency by magnetic means. An unusual buy at this low price. Shpg. Wt. 16 lbs.



MODEL CD-1 **\$59<sup>95</sup>**

## COLOR BAR AND DOT GENERATOR

The CD-1 combines the two basic color servicing instruments, a color bar and white dot generator in one versatile and portable unit, which has crystal controlled accuracy and stability for steady lock-in patterns. (Requires no external sync leads.) Easy-to-build and easy-to-use. No other generator on the market offers so many features at such a great price saving. Shpg. Wt. 13 lbs.

## ETCHED CIRCUIT VTVM KIT

Time proven for dependability, accuracy and overall quality, the V7-A is one of the wisest investments you can make for your electronic workshop or lab. Its multitude of uses will make it one of the most often used instruments in your possession. Use it to measure all operating voltages and potentials such as B+ and AC-DC, or straight AC power supplies, filament voltage, bias voltage, AVC voltage, line voltage, etc. Ideal for measurements in all types of AM, FM and TV circuits. Checks discriminator or detector operation, AVC or AGC performance, while the ohmmeter may be used to measure circuit continuity, circuit resistance, to test out individual components with resistance measurement, or to trace circuit wiring through cables or chassis openings. Front panel controls consist of rotary function switch and a rotary range selector switch, zero-adjust and ohms-adjust controls. Precision 1% resistors are used in the voltage divider circuit for high accuracy and an etched circuit board is employed for most of the circuitry. The circuit board not only simplifies assembly but permits levels of circuit stability not possible with ordinary conventional wiring methods. Shpg. Wt. 7 lbs.



HEATHKIT  
MODEL V7-A

**\$25<sup>95</sup>**



HEATHKIT  
MODEL M-1

**\$17<sup>95</sup>**

## HANDITESTER KIT

Ideal for use in portable applications when making tests away from the work bench or as an "extra" meter in the service shop. The combination function range switch simplifies operation. Measures AC or DC voltage from 0 to 10, 30, 300, 1,000 and 5,000 volts. Direct current ranges are 0 to 10 ma and 0 to 100 ma. Ohmmeter ranges are 0 to 3,000 and 0 to 300,000. Top quality, precision components used throughout. Small and compact, take it with you wherever you go. Very popular with home experimenters and electricians. Test leads and 1½ volt size C battery are included with the kit. Shpg. Wt. 3 lbs.



HEATHKIT  
MODEL MM-1

**\$29<sup>95</sup>**

## 20,000 OHMS/VOLT VOM KIT

Portable and accurate, this kit features a 50 ua 4½" meter and 1% precision multiplier resistors for high accuracy. No external power required. Provides a total of 25 meter ranges on a two-color scale. Sensitivity is 20,000 ohms-per-volt DC and 5,000 ohms-per-volt AC. Measuring ranges are 0-1.5, 5, 50, 150, 500, 1,500 and 5,000 volts AC and DC. Measures direct current in ranges of 0-150 ua, 15 ma, 150 ma, 500 ma and 15 a. Resistance multipliers are X 1, X 100 and X 10,000. Covers -10 db to +65 db. Housed in an attractive bakelite case with plastic carrying handle. Batteries and test leads included. Shpg. Wt. 6 lbs.

## TUBE CHECKER KIT

Brand new in every respect, the TC-3 features outstanding performance and ease of operation. Sockets are provided for 4-pin, 5-pin, 6-pin, 7-pin, large, 7-pin miniature, 7-pin sub-miniature, octal, loctal, and 9-pin miniature tubes. Protection against obsolescence is provided by a blank socket to facilitate modification for checking newly added tube types. A 10-lever switch makes it possible to connect any element to any other element regardless of the pin numbers involved. A neon bulb indicator shows filament circuit continuity and leakage or shorts between elements. A specially designed spring loaded roll chart mechanism permits the roll chart to run freely throughout its entire length without binding. Thumb wheel drive knobs are provided on both sides of the panel to accommodate the left handed operator. Compact and small in size, the TC-3 is ideally suited for portable applications. Both the roll chart and the meter are illuminated to facilitate use in darkened areas. Shpg. Wt. 12 lbs.



HEATHKIT  
MODEL TC-3

**\$39<sup>95</sup>**

## AUDIO VTVM KIT

This vacuum tube volt meter emphasizes stability, broad frequency response and sensitivity for accurate measurement of critical AC voltages. Features a large 4½" 200 ua meter with increased damping in the meter circuit for stability in low frequency tests. Measures AC from a low value of 1 millivolt to a maximum of 300 volts AC (RMS). Voltage ranges are: 0-.01, .03, .1, .3, 1, 3, 10, 30, 100 and 300 volts. Db ranges cover -52 to +52 db. 1% precision multiplier resistors used for maximum accuracy. Frequency response is essentially flat from 10 CPS to 200 kc. Shpg. Wt. 6 lbs.




MODEL AV-3  
**\$29<sup>95</sup>**



MODEL CT-1 **\$7<sup>95</sup>**
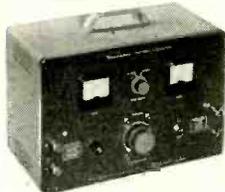
## IN-CIRCUIT CAPACI-TESTER KIT

This handy kit checks capacitors for "open" or "short" right in the circuit. Detects open capacitors from about 50 mmf, not shunted by an excessive low resistance value. Checks shorted capacitors up to 20 mfd (not shunted by less than 10 ohms). Checks all bypass, blocking and coupling capacitors of the paper, mica or ceramic types. (Does not detect leakage nor check electrolytic condensers.) Electron beam "eye" tube is used for quick indication. A 5-position function switch is featured which controls the power to the instrument and selects the test being made. Easy to build and easy to use. Test leads included. Shpg. Wt. 5 lbs.



MODEL BE-5 **\$39<sup>95</sup>**

## LOW RIPPLE BATTERY ELIMINATOR KIT

Completely up to date the BE-5 will power all the newest transistor circuits requiring 0 to 12 volts DC, and the new hybrid automobile radios using both transistors and vacuum tubes. An extra low-ripple filter circuit is employed holding AC ripple down to less than .3%. Doubles as a battery charger or marine converter. Shpg. Wt. 21 lbs.



MODEL T-4  
**\$19<sup>95</sup>**

## VISUAL-AURAL SIGNAL TRACER KIT

New in every respect the T-4 features a built-in speaker and electron beam "eye" tube for signal indication, and a unique noise locator circuit. Ideal for use in AM, FM and TV circuit investigation. Transformer operated for safety and high efficiency. Complete with test leads and informative construction manual. Shpg. Wt. 5 lbs.



MODEL C-3 **\$19<sup>50</sup>**

## CONDENSER CHECKER KIT

Check unknown condenser and resistor values quickly and accurately as well as their operating characteristics with this fine instrument. All values are read directly on a calibrated scale. An electron beam "eye" tube indicates balance and leakage. A valuable addition to any service shop or lab. Shpg. Wt. 7 lbs.



HEATHKIT  
MODEL TX-1  
**\$22950**

- Modern Styling
- Rotating Slide Rule Dial
- Compact, Stable, VFO
- Provision for SSB Adapter

\$50.00 required on C.O.D. orders. Shipped motor freight unless otherwise specified.

## "APACHE" HAM TRANSMITTER KIT

This beautifully styled transmitter has just about everything you could ask for in transmitting facilities. The "Apache" is a high quality transmitter operating with a 150 watt phone input and 180 watt CW input. In addition to CW and phone operation, built-in switch selected circuitry provides for single-sideband transmission through the use of a plug-in external adapter. A completely redesigned, compact and stable VFO provides low drift frequency control necessary for SSB transmission. A slide rule type illuminated rotating VFO dial with full gear drive vernier tuning provides ample bandspread and precise frequency settings. The bandswitch allows quick selection of the amateur bands on 80, 40, 20, 15 and 10 meters (11 m with crystal control). This unit also has adjustable low-level speech clipping and a low distortion modulator stage employing two of the new 6CA7/EL34 tubes in push-pull class AB operation. Time sequence keying is provided for "chirpless" break-in CW operation. The final amplifier is completely shielded for greater TVI protection and transmitter stability. A formed one-piece cabinet with convenient access hatch provides accessibility to tubes and crystal socket. Die-cast aluminum knobs and front panel escutcheons add to the attractive styling of the transmitter. Pi network output coupling matches antenna impedances between 50 and 72 ohms. A "spotting" push button is provided to allow tuning of the transmitter before switching on the final amplifier. This feature also enables the operator to "zero-beat" an incoming frequency without placing the transmitter on the air. Equip your ham shack now for top transmitting enjoyment with this outstanding unit. Shpg. Wt. 110 lbs.

New Styling...  
New Features



**HEATH COMPANY**  
Benton Harbor 20, Michigan


**D** subsidiary of Daystrom, Inc.



HEATHKIT  
MODEL SB-10  
**\$8995**
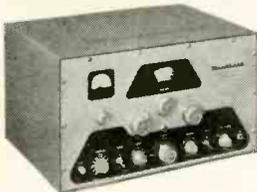
## SINGLE SIDEBAND ADAPTER KIT

Designed as a compatible plug-in adapter for the model TX-1 it can also be used with transmitters similar to the DX-100 or DX-100-B by making a few simple circuit modifications and still retain the normal AM and CW functions. Easy to operate and tune, the adapter employs the phasing method for generating a single sideband signal, allowing operation entirely on fundamental frequencies. The critical audio phase shift network is supplied, completely pre-assembled and wired in a sealed plug-in unit. Features include single-knob band-switching for operation on 80, 40, 20, 15 and 10 meters, an easy-to-read panel meter, built-in electronic voice control with anti-trip circuit. Enjoy the advantages of SSB operation by adding this fine kit to your ham shack now. Shpg. Wt. 14 lbs.



MODEL  
DX-100-B  
**\$18950**

\$50.00 deposit required on C.O.D. orders. Shipped motor freight unless otherwise specified.

### DX-100-B PHONE & CW TRANSMITTER KIT


The same fine performance of the time proven DX-100 is retained in the DX-100-B with improvements in the crystal and loading circuits. The one-piece formed cabinet has convenient access hatch for changing crystals, etc. and the chassis is punched to accept sideband adapter modifications. Features a built-in VFO, modulator and power supply, complete shielding to minimize TVI, and a pi network output coupling to match impedances from 50 to 72 ohms. RF output is in excess of 100 watts on phone and 120 watts on CW. Covers 160 through 10 meters. Single-knob bandswitching and illuminated VFO dial and meter face. RF output stage uses a pair of 6146 tubes in parallel, modulated by a pair of 1625's. Designed for easy assembly. Measures 11 3/8" H. x 19 1/4" W. x 16" D. Shpg. Wt. 107 lbs.



MODEL DX-40 **\$6495**
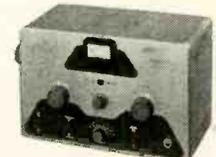
### DX-40 PHONE & CW TRANSMITTER KIT

Operates on 80, 40, 20, 15, 11 and 10 meters, using a single 6146 tube in the final for 75 watt plate power input CW, or 60 watts phone. Single-knob band-switching, pi network output, complete shielding, provision for three crystals and VFO. D'Arsonval movement panel meter. Shpg. Wt. 25 lbs.



MODEL DX-20 **\$3595**

### DX-20 CW TRANSMITTER KIT

This fine unit covers 80, 40, 20, 15, 11 and 10 meters with single-knob bandswitching. Features a 6DQ6A tube in the final for 50 watt plate power input, pi network output, complete shielding to minimize TVI. Easy to build with complete instructions supplied. Shpg. Wt. 19 lbs.

## "MOHAWK" HAM RECEIVER KIT

Designed for ham band operation and for maximum stability and accuracy, the Heathkit "Mohawk" receiver will let you enjoy ham activities to the utmost. This 15-tube receiver features double conversion with IF's at 1682 kc and 50 kc and covers all the amateur frequencies from 160 through 10 meters on seven bands. An extra band is calibrated to cover 6 and 2 meters using a converter. The "Mohawk" is specially designed for single-sideband reception with crystal controlled oscillators for upper and lower sideband selection. A completely pre-assembled, wired and aligned front end coil/bandswitch assembly assures ease of construction and top performance. Many more important features are provided in this outstanding receiver for dependable and effective amateur communications. Ruggedly constructed with well rated components throughout. Shpg. Wt. 66 lbs. Matching accessory speaker kit; optional extra. Model AK-5. \$9.95. Shpg. Wt. 8 lbs.

- Prewired and Aligned Coil/Bandswitch Assembly
- Crystal Controlled Oscillators for Drift-Free Reception

HEATHKIT  
MODEL RX-1

**\$274<sup>95</sup>**



HEATHKIT  
MODEL AR-3


**\$29<sup>95</sup>**

(LESS CABINET)


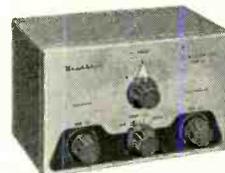
## ALL-BAND RECEIVER KIT

A fine receiver for the beginning ham or short wave listener. Frequency coverage is from 550 kc to 30 mc in four bands. Features include bandswitch, bandspread tuning, phone-standby-CW switch, antenna trimmer, noise limiter, RF and AF gain controls and head-phone jack. Easy to build. Shpg. Wt. 12 lbs.




MODEL  
QF-1

**\$9<sup>95</sup>**
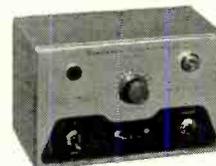
## "Q" MULTIPLIER KIT

Use with any receiver with IF frequency between 450 and 460 kc to add additional selectivity for separating two signals or to reject one signal and eliminate heterodyne. A great help on crowded phone and CW bands. Not for use with AC-DC type receivers. Simple to connect with cable and plugs supplied. Shpg. Wt. 3 lbs.



MODEL  
CA-1

**\$13<sup>95</sup>**

## "SENECA" VHF TRANSMITTER KIT

Brand new in every respect, the model VHF-1 "Seneca" is the latest addition to our line of ham transmitters. This self-contained 6 and 2 meter transmitter features built-in VFO, modulator, and dual power supply. A pair of 6146 tubes are employed in the push-pull final amplifier stage and features up to 120 watts input on phone and 140 watts input on CW in the 6 meter band. Slightly less in the 2 meter band to prolong amplifier tube life. Panel controls allow VFO or crystal control, phone or CW operation on both amateur bands. Four switch-selected crystal positions. Complete RF shielding to minimize TVI. Spotting push-button provided. The VFO slide rule type dial features edge-lighting and vernier tuning. An ideal transmitter for the ham who wants to extend operation into the VHF region. Shpg. Wt. 56 lbs.



HEATHKIT  
MODEL VHF-1

**\$159<sup>95</sup>**

## "AUTOMATIC" CONELRAD ALARM KIT

This easy-to-build device gives instant warning and cuts AC power to your transmitter when a monitored station goes "off-the-air". Use with any radio receiver having an AVC circuit. A sensitivity control adjusts to various AVC levels. Incorporates a heavy duty six-ampere relay and manual "reset" button to reactivate the transmitter. Complete instructions provided for connection to receiver. Shpg. Wt. 4 lbs.



MODEL VF-1

**\$19<sup>50</sup>**

## VARIABLE FREQUENCY OSCILLATOR KIT

Far below the cost of crystals to obtain the same frequency coverage this VFO covers 160, 80, 40, 20, 15, 11 and 10 meters with three basic oscillator frequencies. Better than 10 volts RF output on fundamentals. Requires only 250 volts DC at 15 to 20 ma, and 6.3 VAC at 0.45 a. Illuminated dial reads direct. Shpg. Wt. 7 lbs.



MODEL AM-2 **\$15<sup>95</sup>**

## REFLECTED POWER METER KIT

Check the match of your antenna transmission system by measuring the forward and reflected power or standing wave ratio from 1:1 to 6:1. Handles a peak power of well over 1 kilowatt and may be left in antenna feed line. No external power required. 160 through 6 meters. For 50 or 75 ohm lines. Shpg. Wt. 3 lbs.



MODEL B-1 **\$8<sup>95</sup>**

## BALUN COIL KIT

Unbalanced coax lines can be matched to balance lines of either 75 or 300 ohms by using this balun coil kit. Use without adjustment from 80 through 10 meters at power up to 200 watts. May be located any distance from transmitter or antenna. Protective cover included. Shpg. Wt. 4 lbs.



MODEL VX-1 **\$23<sup>95</sup>**

## ELECTRONIC VOICE CONTROL KIT

This unique device lets you switch from receiver to transmitter merely by talking into your microphone. Provision is made for receiver and speaker connections and also for a 117 volt antenna relay. Adjustable to all conditions by sensitivity and variable time delay controls provided. Shpg. Wt. 5 lbs.

Beautifully Styled With Plenty of  
Room For The Most Complete  
Stereo System




MODEL SE-1 (center unit) **\$149<sup>95</sup>** Shpg. Wt. 162 lbs.


MODEL SC-1 (speaker enclosure) **\$39<sup>95</sup>** each Shpg. Wt. 42 lbs.

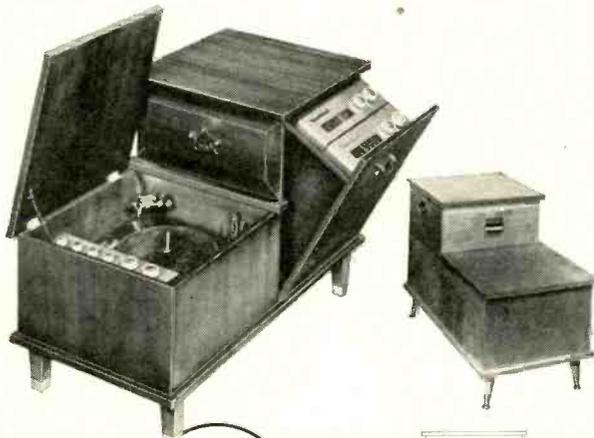**STEREO EQUIPMENT CABINET KIT**

This superbly styled cabinet ensemble is designed to hold your complete home stereo hi-fi system, consisting of a "stereo equipment center" flanked by two individual "stereo wing speaker enclosures". The unit has room for all the components required for stereo sound. Although designed to hold Heathkit stereo components, it is not frozen to this arrangement. The kit is supplied with mounting panels precut to accommodate Heathkits, but interchangeable blank panels are also furnished so you can mount any equipment you may already have. The precut panels accommodate the Heathkit AM-FM tuner (PT-1), stereo preamplifier (SP-1 & 2), and record changer (RP-3). Record changer chassis pulls out easily for convenient loading and unloading. Adequate space is provided for record storage and a pair of matching Heathkit power amplifiers (from 12 to 70 watts). The stereo wing speaker enclosures are open backed, cloth grilled cabinets designed to hold the Heathkit SS-2 or similar speaker systems. The cabinets are available in beautifully grained 3/4" solid core Phillipine mahogany or select birch plywood suitable for the finish of your choice. The matched grain sliding tape deck access door on top pops-up flush when closed. Entire top features a shaped edge. Hardware and trim of brushed-brass and gold finish. Rich toned grille cloth is flecked in gold and black. No woodworking experience required. All parts precut and predrilled for easy assembly. Maximum overall dimensions (all 3 pieces): 82 3/4" W. x 36 1/2" H. x 20" D. Center Cabinet: 47 1/2" W. x 36 1/2" H. x 20" D.



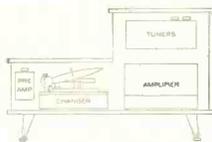HEATHKIT  
MODEL CE-1  
**\$43<sup>95</sup>**  
each



**CHAIRSIDE ENCLOSURE KIT**

Combine all of your hi-fi equipment into one compact control center and, at the same time add a beautiful piece of furniture to your home. The CE-1 is designed to house AM and FM tuners (BC-1A and FM-3A) and the WA-P2 preamplifier along with the majority of record changers which will fit in the space provided. Changer compartment measures 17 3/4" L. x 16" W. x 9 5/8" D. Adequate space is provided in the rear of the unit to house any of the Heathkit amplifiers designed to operate with the WA-P2. Good ventilation is achieved through properly placed slots in the bottom and back of the enclosure. Overall dimensions are 18" W. x 24" H. x 35 1/2" D. All parts are precut and predrilled for easy assembly. The Contemporary cabinet is available in either mahogany or birch, and the Traditional cabinet is available in mahogany suitable for the finish of your choice. Beautiful hardware supplied. Shpg. Wt. 46 lbs.

Plan your own  
Hi-Fi System...



**HEATH COMPANY** • Benton Harbor 20,  
Michigan  
a subsidiary of Daystrom, Inc.

HEATHKIT  
MODEL RP-3  
**\$64<sup>95</sup>**



**HIGH FIDELITY  
RECORD CHANGER KIT**

Every outstanding feature you could ask for in a record changer is provided in the Heathkit RP-3, the most advanced changer on the market today. The unique turntable pause during the change cycle saves wear and tear on your records by eliminating the grinding action caused by records dropping on a moving turntable or disk. Record groove and stylus wear are practically eliminated through proper weight distribution and low pivot point friction of the tone arm. Clean mechanical simplicity and precision parts give you turntable performance with the automatic convenience of a record changer. Flutter and wow, a major problem with automatic changers, is held to less than 0.18% RMS. An automatic speed selector position allows intermixing 33 1/3 and 45 RPM records regardless of their sequence. Four speeds provided: 16, 33 1/3, 45 and 78 RPM. Changer is supplied complete with GE VR II cartridge with diamond LP and sapphire 78 stylus, changer base, stylus pressure gauge and 45 RPM spindle. Shpg. Wt. 19 lbs.

RADIO-ELECTRONICS

## "BASIC RANGE" HI-FI SPEAKER SYSTEM KIT

The popularity of this modestly priced speaker system attests to its high fidelity performance. The SS-2 provides an ideal basic speaker for your home hi-fi system. Flexibility of design allows it to be used as a table top model or as an attractive consolette with optional legs. May also be used as a supplementary speaker in more advanced systems or as replacement speaker for TV sets, etc. The specially designed tweeter horn rotates 90 degrees allowing you to use the speaker in an upright position if desired, as in the Heathkit stereo wing speaker enclosures. Total frequency range is from 50 to 12,000 cycles-per-second. An 8" mid-range woofer covers from 50 to 1,600 CPS while a compression-type tweeter with flared horn covers 1,600 to 12,000 CPS. Both speakers are by Jensen. A variable balance control allows level adjustment of the high frequency speaker. Power rating is 25 watts. Constructed of 1/2" veneer-surfaced plywood suitable for light or dark finish. All wood parts are precut and predrilled for simple, quick assembly. An added feature of the SS-2 is that, although an outstanding performer in its own right, it may be combined with the SS-1B "range extending" speaker system later to extend the frequency range at the high and low ends of the audio range. Build in just one evening for many years of listening enjoyment. Shpg. Wt. 26 lbs.

**ATTRACTIVE BRASS TIP ACCESSORY LEGS** convert SS-2 into handsome consolette. 14" legs screw into brackets provided. All hardware included. Shpg. Wt. 3 lbs. No. 91-26. **\$4.95.**

Assemble it in  
Just One Evening




HEATHKIT  
MODEL SS-2  
**\$39<sup>95</sup>**

OPTIONAL LEGS  
NO. 91-26 \$4.95
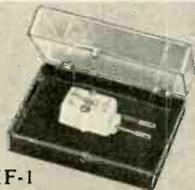
### DIAMOND STYLUS HI-FI PICKUP CARTRIDGE


MODEL MF-1 **\$26<sup>95</sup>**

Replace your present pickup with the MF-1 and enjoy the fullest fidelity your library of LP's has to offer. Designed to Heath specifications to offer you one of the finest cartridges available today. Nominally flat response from 20 to 20,000 CPS. Shpg. Wt. 1 lb.


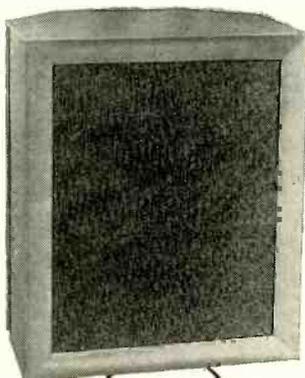
### "RANGE EXTENDING" HI-FI SPEAKER SYSTEM KIT

Designed exclusively for use with the SS-2, the SS-1B employs a 15" woofer and a super tweeter horn to extend the range of the SS-2 to an overall response of  $\pm 5$  db from 35 to 16,000 CPS. When used together the two units form an integrated four-speaker system and are designed to combine into a single piece of attractive furniture. Impedance of the SS-1B is 16 ohms and power rating 35 watts. A control is provided to limit the output of the super tweeter. Constructed of beautiful 3/4" veneer-surfaced plywood suitable for light or dark finish of your choice. All parts are precut and predrilled for simple assembly. No woodworking experience required. All hardware included. Shpg. Wt. 80 lbs.



HEATHKIT  
MODEL SS-1B  
**\$99<sup>95</sup>**

Extended  
Frequency Range  
for Your SS-2



HEATHKIT  
MODEL HH-1  
**\$299<sup>95</sup>**

### "LEGATO" HI-FI SPEAKER SYSTEM KIT

It is difficult to describe in words the performance of this magnificent speaker system. You may never find absolute perfection in reproduced sound, but the Legato comes as close to achieving it as anything yet devised. Perfect balance, precise phasing, and adequate driver design combine to produce the superb quality of reproduction inherent in this instrument. The crisp, clear high frequencies and rich full bass engulf you in a sea of life-like tone. Two 15" Altec Lansing low frequency drivers cover frequencies from 25 to 500 CPS while a specially designed exponential horn with high frequency driver covers 500 to 20,000 CPS. The unique crossover network is built-in making electronic crossovers unnecessary. The Legato emphasizes simplicity of line and form to blend with modern or traditional furnishings. Constructed of 3/4" veneer-surfaced plywood in either African mahogany or white birch suitable for light or dark finishes of your choice. All parts are precut and predrilled for easy assembly. Shpg. Wt. 195 lbs.

Easy to buy...

Easy to build

Easy to use...



**HEATH  
COMPANY**

Benton Harbor 20,  
Michigan

High Fidelity AM  
and FM reception  
in a Single Set

HEATHKIT  
MODEL PT-1  
**\$89<sup>95</sup>**



### Professional Stereo-Monaural AM-FM Tuner Kit


Enjoy stereophonic broadcasts as well as outstanding individual AM and FM radio reception with this deluxe 16-tube AM-FM-stereophonic tuner combination. Features include three etched circuit boards for high stability and ease of construction, prewired and prealigned FM front end, built-in AM rod antenna, tuning meter, FM-AFC (automatic frequency control) with on-off switch, and flywheel tuning. A multiplex jack is also provided. AM and FM circuits are tuned individually making it ideal for stereo applications since both AM and FM can be used at the same time. A switch selected tuning meter functions on either AM or FM. Cathode follower outputs with individual level controls are provided for both AM and FM. Other features include variable AM bandwidth, 10 kc whistle filter, tuned-cascade FM front end, FM AGC and amplified AVC for AM. Anywhere from 1 to 4 limiters or IF's assure smooth, non-flutter reception on weak or strong stations alike. The silicon diode power supply is conservatively rated and is fuse-protected assuring long service life. Flywheel tuning combined with new edge-lighted slide-rule dial provide effortless tuning. Use of three printed circuit boards greatly simplifies construction. Vinyl-clad steel cover is black with inlaid gold design. Shpg. Wt. 20 lbs.



MODEL FM-3A  
**\$26<sup>95</sup>**
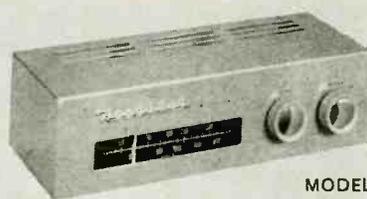
### HIGH FIDELITY FM TUNER KIT

The Heathkit FM-3A Tuner will provide you with years of inexpensive hi-fi enjoyment. Features broad-banded circuits for full fidelity and better than 10 uv sensitivity for 20 db of quieting. Covers the complete FM band from 88 to 108 mc. Stabilized, temperature-compensated oscillator assures negligible drift after initial warmup. Employs a high gain cascode IF amplifier and has AGC. Power supply is built-in. IF and ratio transformers are prealigned as is the front end tuning unit. Two outputs provided, one fixed, one variable, with extra stage of amplification. Shpg. Wt. 8 lbs.



MODEL BC-1A  
**\$26<sup>95</sup>**

### HIGH FIDELITY AM TUNER KIT

The BC-1A incorporates many features not usually expected in an AM circuit particularly in this low price range. It features a special detector using crystal diodes and broad band-width IF circuits for low signal distortion. Audio response is  $\pm 1$  db from 20 CPS to 9 kc with 5 db of pre-emphasis at 10 kc to compensate for station rolloff. Covers the complete broadcast band from 550 to 1600 kc. Prealigned RF and IF coils eliminate the need for special alignment equipment. Incorporates AVC, two outputs, two antenna inputs and built-in power supply. Shpg. Wt. 9 lbs.



MODEL W-6 **\$109<sup>95</sup>**

### "HEAVY DUTY" 70 WATT HI FI AMPLIFIER KIT

Designed for "rugged duty" called for by advanced hi-fi systems and P.A. networks. Silicon diode rectifiers assure long life and heavy duty transformer provides excellent power supply regulation. Variable damping control provides optimum performance with any speaker system. Quick change plug selects 4, 8 and 16 ohm or 70 volt output and the correct feedback resistance. Shpg. Wt. 52 lbs.



MODEL W-5 **\$59<sup>75</sup>**

### 25 WATT HI FI AMPLIFIER KIT


Enjoy the distortion-free high fidelity sound from one of the most outstanding hi-fi amplifiers available today. Features include a specially designed Peerless output transformer and KT66 tubes. Frequency response is  $\pm 1$  db from 5 to 160,000 CPS at 1 watt and within 2 db 20 to 20,000 CPS at full 25 watts output. Hum and noise are 99 db below 25 watts. Shpg. Wt. 31 lbs.



MODEL W-4AM **\$39<sup>75</sup>**
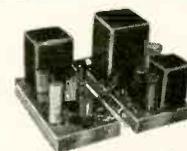
### SINGLE CHASSIS 20 WATT HI FI AMPLIFIER KIT

A true Williamson-type high fidelity circuit, the W-4AM features 5881 push-pull output tubes and a special Chicago-Standard output transformer to guarantee you full fidelity at minimum cost. Harmonic distortion is 1.5% and IM distortion is below 2.7% at full 20 watt output. Hum and noise are 95 db below full output. Taps for 4, 8 or 16 ohm speakers. Shpg. Wt. 28 lbs.



MODEL W-3AM **\$49<sup>75</sup>**

### DUAL CHASSIS 20 WATT HI FI AMPLIFIER KIT

Another famous Williamson-type high fidelity circuit, the W-3AM features the famous Acrosound TO-300 "ultralinear" output transformer and 5881 tubes. The power supply and main amplifier are on separate chassis for installation flexibility. Harmonic distortion is less than 1% and IM distortion is less than 1.2% at 20 watts. Shpg. Wt. 29 lbs.



HEATHKIT  
MODEL SP-2  
(STEREO)  
**\$56<sup>95</sup>**


**Monaural-Stereo Preamplifier Kit  
(2-Channel Mixer)**

This unique kit allows you to purchase it in the monaural model if desired and then add the second or stereo channel later. The SP-2 features 12 separate inputs, six on each channel, with input level controls. Six dual concentric controls consist of: two 8-position selector switches, two bass, two treble, two volume level and two loudness controls, a scratch filter switch and a 4-position function switch. A separate on-off switch is provided. The function switch provides settings for stereo, 2-channel mix, channel A or B for monaural use. Inputs consist of tape, mike, mag phono and three high-level inputs. NARTB equalization and RIAA, LP, 78 record compensation are provided. A remote balance control is included. Printed circuit boards for easy assembly. Built-in power supply. Shpg. Wt. 15 lbs.



MODEL SP-1 (MONAURAL)  
**\$37<sup>95</sup>** Shpg. Wt. 13 lbs.

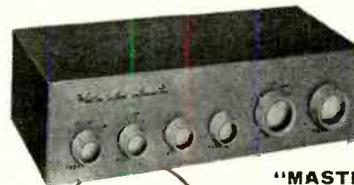MODEL C-SP-1 (CONVERTS SP-1 TO SP-2)  
**\$21<sup>95</sup>** Shpg. Wt. 5 lbs.



HEATHKIT  
MODEL WA-P2  
**\$19<sup>75</sup>**

**"MASTER CONTROL"  
PREAMPLIFIER KIT**

Control your hi-fi system with this compact unit. Features 5 switch-selected inputs to accommodate a record changer, tape recorder, AM tuner, FM tuner, TV receiver, microphone, etc., each with level control. Provision also for a tape recorder output. Equalization for records through separate turnover and rolloff switches for LP, RIAA, AES and early 78's. Shpg. Wt. 7 lbs.



MODEL W-7M  
**\$54<sup>95</sup>**

**"EXTRA PERFORMANCE" 55 WATT  
HI FI AMPLIFIER KIT**

Enjoy this high fidelity power amplifier at less than a dollar per watt. Full audio output and maximum damping is conservatively rated at 55 watts from 20 CPS to 20 kc with less than 2% total harmonic distortion throughout the entire range. Features famous "bas-bal" circuit, EL-34 output tubes and special 70 volt output. Shpg. Wt. 28 lbs.



MODEL  
XO-1  
**\$18<sup>95</sup>**

**ELECTRONIC  
CROSSOVER KIT**


This unique instrument separates high and low frequencies and feeds them through 2 amplifiers into separate speakers. Located ahead of the main amplifier, it virtually eliminates 1M distortion and matching problems. Note: Not for use with Heathkit Legato speaker system. Shpg. Wt. 6 lbs.



MODEL UA-1  
**\$21<sup>95</sup>**

**"UNIVERSAL" 12 WATT HI FI  
AMPLIFIER KIT**

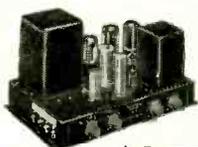The versatility and economy of this fine kit make it a truly "universal" hi-fi amplifier. An ideal basic amplifier for any hi-fi system or a perfect addition to gear your present hi-fi system to stereo sound. Uses 6BQ5/EL84 push-pull output tubes for less than 2% harmonic distortion throughout the entire audio range. Shpg. Wt. 13 lbs.



MODEL A-9C **\$35<sup>50</sup>**

**GENERAL-PURPOSE  
20 WATT AMPLIFIER KIT**

Designed for home installation as well as for PA requirements, the A9-C combines a preamplifier, main amplifier and power supply all on one chassis. Four switch-selected inputs are provided as well as separate bass and treble tone controls offering 15 db boost and cut. Detachable front plate allows for custom installation. Shpg. Wt. 23 lbs.



MODEL SW-1 **\$24<sup>95</sup>**

**SPEEDWINDER KIT**

A real timesaver, the SW-1 leaves your tape recorder free for operation while rewinding tape at the rate of 1200 feet in 40 seconds. Prevents unnecessary wear to the tape and recorder. Handles up to 10 1/2" tape reels. Handles 800' reels of 8 and 16 millimeter film as well. Automatic shutoff prevents whipping at end of rewind. Shpg. Wt. 12 lbs.



NO. 401-6  
**\$7<sup>50</sup>**

**12" UTILITY SPEAKER KIT**

Replace inferior speakers in radio or TV sets to obtain better tone quality or set up an auxiliary speaker for testing purposes with this convenient, high quality speaker. The speaker will handle up to 12 watts with a frequency response of ±5 db from 50 to 9,000 CPS. Speaker impedance is 8 ohms and has a 6.8 oz. magnet. An outstanding dollar value. Shpg. Wt. 7 lbs.



MODEL TK-1 **\$9<sup>95</sup>**

**COMPLETE TOOL SET**


These basic tools are all you need to build any Heathkit. The pliers, diagonal side cutters, 2 screwdrivers, and soldering iron are all of top quality case hardened steel for hard duty and long life. Pliers and side cutters are equipped with insulated rubber handles for safety. A good example of just how easy Heathkit building really is. Shpg. Wt. 3 lbs.
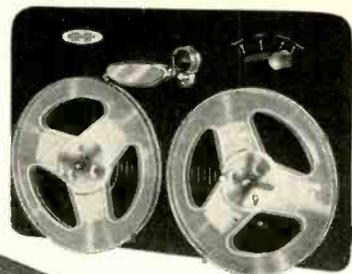
## HIGH FIDELITY TAPE RECORDER KIT

The model TR-1A tape deck and preamplifier combination provides all the facilities you need for top quality monaural recording/playback with fast forward and rewind functions.  $7\frac{1}{2}$  and  $3\frac{3}{4}$  IPS tape speeds are selected by changing belt drive. Flutter and wow are held to less than 0.35%. Frequency response at  $7\frac{1}{2}$  IPS  $\pm 2.0$  db 50-10,000 CPS, at  $3\frac{3}{4}$  IPS  $\pm 2.0$  db 50-6,500 CPS. Both units may be mounted together or separately affording high flexibility in every application. Features include NARTB playback equalization—separate recording and playback gain controls—cathode follower output and provision for mike or line input. Signal-to-noise ratio is better than 45 db below normal recording level with less than 1% total harmonic distortion. A filament balance control allows adjustment for minimum hum level. Complete instructions provided for easy assembly. Overall dimensions of tape deck and preamp is  $15\frac{1}{2}$ " W. x  $13\frac{1}{2}$ " H. x 8" D. Shpg. Wt. 24 lbs.



Includes tape deck assembly, preamplifier and roll of tape.



HEATHKIT  
TE-1  
**\$39<sup>95</sup>**



Tape preamplifier sold separately if desired. Shpg. Wt. 10 lbs.

## Many more Heathkits to choose from

**hi-fi:** Amplifiers—Preamplifiers—Speaker Systems—AM/FM Tuners—Equipment Cabinets—Record Player—Tape Recorder—Electronic Crossover—Stereo Equipment.

**test:** Oscilloscopes—Voltmeters—RF Signal Generators—AF Generators—Analyzers—Battery Eliminators—Tube Checkers—Condenser Checkers—Computer—Color Bar & Dot Generator—Sweep Generator—Impedance Bridge—Power Supplies—Probe Kits—R/C Decade & Substitution Kits.

**ham radio:** Transmitters—Receivers—Antenna Accessories—Voice Control—Conelrad Alarm—Variable Frequency Oscillator—SSB Adapter—"Q" Multiplier.

**marine:** Direction Finders—Marine Converter—Rudder Position Indicator—Fuel Vapor Detector—Charge Indicator—Power Meter.

**general:** Tool Set—6-Transistor Portable Radio—Radiation Counter—Electronic Timer—Crystal Receiver—Superheterodyne Receiver.

*Send for Catalog* describing over 100 easy-to-build electronic instruments in kit form. Complete specifications and detailed information on Hi-Fi—Test—Ham and Marine kits.

**Save with Heathkits... the quality name in kit form electronics.**




**"BOOKSHELF" 12 WATT  
AMPLIFIER KIT**

Here are a few of the reasons why this attractive amplifier is such a tremendous dollar value. You get rich, full range, high fidelity sound reproduction with low distortion and noise . . . plus "modern styling". The many features include full range frequency response 20 to 20,000 CPS  $\pm 1$  db with less than 2% distortion over this range at full 12 watt output—its own built-in preamplifier with provision for three separate inputs: mag phono, crystal phono, and tuner—RIAA equalization—separate bass and treble tone controls—special hum control—and it's easy-to-build. Complete instructions and pictorial diagrams show where ever part goes. Cabinet shell has smooth leather texture in black with inlaid gold design. Cabinet measures 12½" W. x 8¾" D. x 4¾" H. Output transformer has taps at 4, 8 and 16 ohms to match the speaker of your choice. An ideal unit to convert your present hi-fi system to stereo sound. Shpg. Wt. 15 lbs.

An Amplifier, Preamplifier  
all in one!



HEATHKIT  
EA-2  
**\$28<sup>95</sup>**

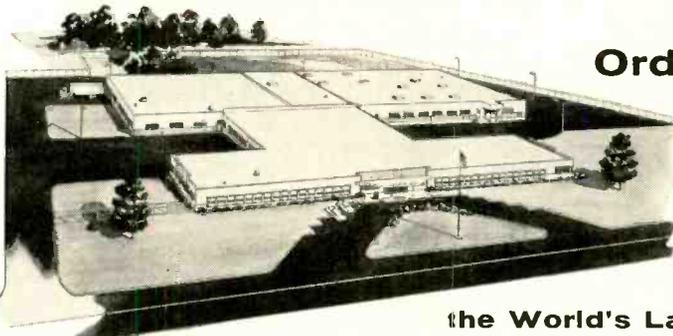

**Order direct by mail...**

Save ½ or more over equivalent ready-made products by buying direct and assembling them yourself. Heathkit Style, Performance and Quality are unsurpassed!

**the World's Largest Manufacturer  
of Electronic Instruments in Kit Form**



**HEATH COMPANY BENTON HARBOR 20, MICH.**

**HE** a subsidiary of Daystrom, Inc.

*NOTE: all prices and specifications subject to change without notice.*

Enclosed find ( ) check ( ) money order. Please ship C.O.D. ( )

On Express orders do not include transportation charges—they will be collected by the express agency at time of delivery.

On Parcel Post Orders include postage for weight shown. All prices are NET F.O.B. Benton Harbor, Michigan, and apply to Continental U.S. and Possessions only. 20% Deposit required on all C.O.D. orders.

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City & Zone \_\_\_\_\_ State \_\_\_\_\_  
(PLEASE PRINT)

SHIP VIA

- Parcel Post
- Express
- Freight
- Best Way

QUANTITY	ITEM	MODEL NO.	PRICE
<input type="checkbox"/> SEND FREE HEATHKIT CATALOG		POSTAGE	
		TOTAL	


**HEATHKITS are also available at your Dealer**

see listing on next page



The ideal instrument for frequency-response tests, audio amplifier gain measurements, meter and scope calibration

# AUDIOPHILE'S SIGNAL-LEVEL COMPARATOR

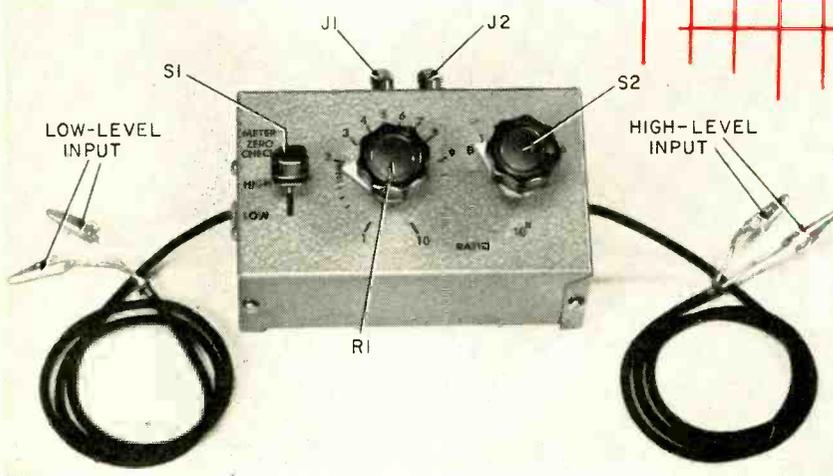

All controls are mounted on comparator's front panel.

By J. E. PUGH, JR.


A SIGNAL-LEVEL comparator is used to make fast frequency-response tests and gain measurements on audio amplifiers, to check meter and oscilloscope calibration, and as a general-purpose ac or dc voltage divider.

Although it is very useful, a comparator is extremely simple. It consists of a low-level input that can be switched directly to the output, and a high-level input that is fed through a calibrated attenuator before being connected to the output terminals for comparison with the low-level signal. The basic circuit is in Fig. 1.

When comparing signal levels the amplitude of the low-level signal is first noted on a meter or oscilloscope for a reference. Then the high-level signal is connected to the same indicator and the attenuator is set to reduce it to the same level as the low-level signal. Then, by simply noting the attenuator setting, the ratio of these two signals is obtained.

The attenuator is calibrated in terms of input to output voltage ratio at various settings. For example, with the variable contact set at the top of the attenuator, the input voltage is equal to the output voltage and the ratio is 1 to 1. With the arm at the half resistance point, the input voltage is two times as great as the output voltage. The attenuator can thus be calibrated at various points over its range.

For some uses the comparator can be as simple as the one in Fig. 1. However, for many uses a wider range of attenuation is needed. Fig. 2 is the complete circuit of such a unit. It includes a step attenuator that works in 10-to-1 steps from 1 to 1 up to  $10^6$  to 1 and a potentiometer to give ratios from 1 to 1 to 10 to 1. This combination provides variable attenuation from 1 to 1 up to  $10^7$  to 1. The higher ratios are not needed for most purposes and the last two can be eliminated if you wish. They were included in this model to permit direct connection to higher voltage cir-

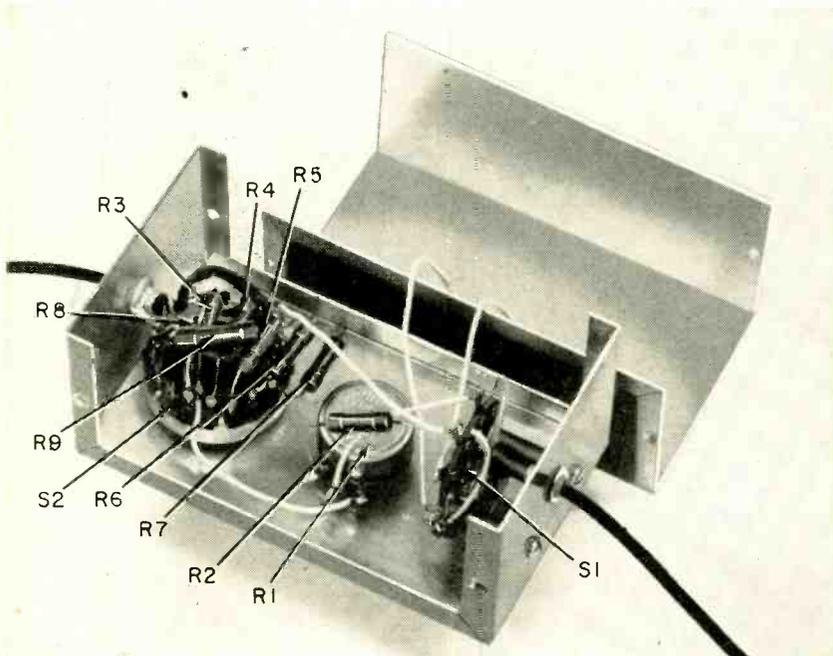

There's plenty of room if you want to try a different layout.

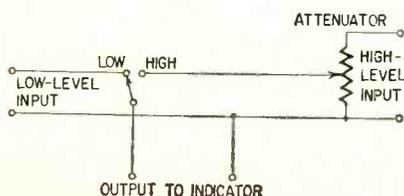


Fig. 1—Basic comparator circuit.

## TEST INSTRUMENTS

R1—pot, 10,000 ohms, 2 watts, counterclockwise log taper (Ohmite CB1031 or equivalent)  
 R2—1,100 ohms  
 R3—91,000 ohms, 2 watts  
 R4—110,000 ohms  
 R5—1,000 ohms  
 R6—91 ohms  
 R7—91 ohms  
 R8—910,000 ohms, 2 watts  
 R9—91 megohms, 1 watt  
 All fixed resistors 1/2-watt 1% unless noted  
 J1, 2—binding posts  
 S1—1-pole 3-position lever switch (Centralab 1475 or equivalent)  
 S2—1-deck 2-pole 9-position rotary switch (Mallory 3229J or equivalent)  
 Case, 5/4 x 3 x 2 1/8 inches  
 Alligator clips (4)  
 Microphone cable or RG-58/U (5 feet)  
 Miscellaneous hardware

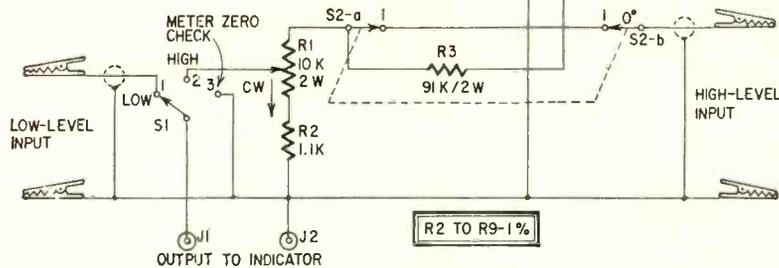


Fig. 2—Seven-range unit covers signal ratios from 1 to 1 to 10<sup>6</sup> to 1.

circuits without exceeding dissipation limits of the resistors as well as to obtain the higher ratios.

For some purposes it may be handier to design the comparator for less than a decade variation over the range of the potentiometer—especially good for measuring small changes accurately. To do this determine the ratio ( $N$  to 1) needed and make  $R2 = R1 / (N - 1)$ .  $R1$  is selected to have a low resistance compared with the reactance of the indicator input capacitance at the highest frequency used so the comparator will have a flat response over the desired range. For example, using the values shown in Fig. 2 and an oscilloscope with a 50- $\mu$ f input capacitance for an indicator, the capacitive reactance is equal to  $R1 + R2$  at approximately 300 kc. Actual tests show no measurable drop in response up to 100 kc, which is more than adequate for all normal audio work.

If you change the variable attenuator's range, modify the step attenuator so it changes by the same ratio ( $N$  to 1) to avoid overlap or gaps in the coverage.

If you want to measure only small variations in the high level (as when making frequency response runs), the comparator can be simplified by using the circuit shown in Fig. 3. The LEVEL ADJUST control is set to reduce the high-level signal to equal the low-level signal with the calibrated attenuator at the 1-to-1 ratio. Level variations at different frequencies are then measured by adjusting the calibrated attenuator for equal signal levels at each frequency and noting its settings.

### Construction steps

The comparator is built into a small aluminum box. The parts layout was selected to make the controls easy to use, but there is plenty of room for variations.

There is nothing critical about the wiring. Simply keep the leads short and away from each other and the chassis. Switch S1 is held from the case by two 1-inch metal sleeves. All grounds are connected to the case via a solder lug under one of the mounting screws.

The potentiometer is a good quality 2-watt type with a counterclockwise log taper. This provides a more even distribution of calibration points than would any other taper, and the 2-watt dissipation permits direct connection to 150 volts on the lowest range. On all other ranges except the last two the maximum input voltage is limited by R3's dissipation factor. On ranges 6 and 7, the cable and switch S2 are the limiting components.

The maximum permissible voltages for the various ranges are listed in Table I. For convenience this table can be cemented to the instrument's side.


Many of the less expensive potentiometers do not have a true logarithmic taper, but combine two or more linear tapers to provide an approximation. Such controls give satisfactory results but not as good a spread of calibration points as the one recommended.

Switch (S2) is a two-pole nine-position type that has been stopped down to seven positions. The two extra positions on the S2-b section are used as tie points for the grounded ends of R4, R5, R6, R7 and the shield of the high-level input cable.

All fixed resistors are 1% tolerance types. If you have an accurate bridge, you can use selected 5% units. When soldering them, hold their leads with long-nose pliers to prevent damage due to overheating.
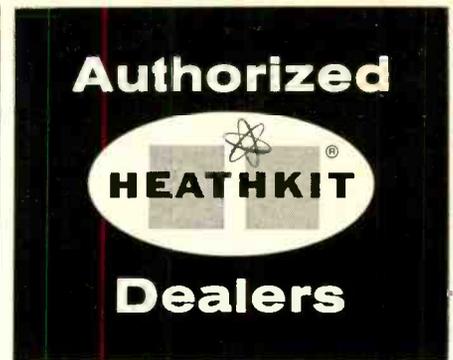
### Calibrate before using

If a resistance bridge is available, use  
 (Continued on page 80)



Although you will find local prices for Heathkits higher than those listed in Heath Company advertising... we're sure you will agree that this increase is justified. Your dealer pays all transportation charges, makes your kit immediately available, provides demonstration facilities, offers you a reliable source for parts and fast service... and stands ready to counsel or advise you on any problems that might arise.

Naturally, you have the continued privilege of dealing directly with the Heath Company if you wish. Now however, you have the added convenience of buying locally.

The following dealers have been carefully selected and are now ready to serve you.

- |   |   |
|---|---|
| <b>CALIFORNIA</b>   | <b>NEW JERSEY</b>   |
| DUNLAP RADIO & TV<br>928 Main Street<br>Chico, California                 | FEDERATED PURCHASER<br>1021 US Route 22<br>Mountainside, New Jersey       |
| DUNLAP RADIO & TV<br>2617 Tulare Street<br>Fresno, California             | FEDERATED PURCHASER<br>114 Hudson Street<br>Newark, New Jersey            |
| BUSHNELL SOUND CORP.<br>12026 Wilshire Blvd.<br>Los Angeles, California   | <b>NEW YORK</b>   |
| KIERULFF SOUND CORP.<br>820 West Olympic Blvd.<br>Los Angeles, California | CROSS ISLAND ELEC. INC.<br>247-40 Jericho Turnpike<br>Bellerose, New York |
| DUNLAP RADIO & TV<br>5th & "J" Street<br>Marysville, California           | ACME ELECTRONICS<br>59 Willoughby Street<br>Brooklyn, New York            |
| DUNLAP RADIO & TV<br>234 West 17th Street<br>Merced, California           | GEM ELECTRONICS<br>34 Hempstead Turnpike<br>Farmlandale, New York         |
| DUNLAP RADIO & TV<br>419 10th Street<br>Modesto, California               | BEAM ELECTRONICS<br>101-10 Queens Blvd.<br>Forest Hills, New York         |
| TEL-RAD ELECTRONICS<br>639 National<br>National City, California          | GEM ELECTRONICS<br>236 Broadway, Hlcksville, N.Y.                         |
| ZACK RADIO SUPPLY CO.<br>654 High Street<br>Palo Alto, California         | ARROW ELECTRONICS<br>525 Jericho Tpk., Mineola, N.Y.                      |
| DUNLAP RADIO & TV<br>18th & "R" Street<br>Sacramento, California          | DAVIS RADIO DISTR.<br>70 East 3rd Street<br>Mount Vernon, New York        |
| TEL-RAD ELECTRONICS<br>3453 University Avenue<br>San Diego, California    | ARROW ELECTRONICS<br>65 Cortlandt Street<br>New York City, New York       |
| ZACK RADIO SUPPLY CO.<br>1422 Market Street<br>San Francisco, California  | HARVEY RADIO CO.<br>103 West 43rd Street<br>New York City, New York       |
| DUNLAP RADIO & TV<br>27 North Grant Street<br>Stockton, California        | <b>OREGON</b>   |
| VALLEY SOUND CORP.<br>18841 Ventura Blvd.<br>Tarzana, California          | ECCLES ELECTRIC CO.<br>237 N.E. Broadway<br>Portland, Oregon              |
| DUNLAP RADIO & TV<br>1725 Mooney Avenue<br>Visalia, California            | CECIL FARNES CO.<br>440 Church Street, N.E.<br>Salem, Oregon              |
| <b>MASSACHUSETTS</b>  | <b>PENNSYLVANIA</b>   |
| AUDIONICS, INC.<br>1348 Boylston Street<br>Boston 15, Massachusetts       | FEDERATED PURCHASER<br>1115 Hamilton Street<br>Allentown, Pennsylvania    |
| <b>MICHIGAN</b>   | FEDERATED PURCHASER<br>925 Northampton Street<br>Easton, Pennsylvania     |
| VOLTA ELECTRONICS<br>6716 Park Avenue<br>Allen Park, Michigan             | AUSTIN ELECTRONICS<br>1421 Walnut Street<br>Philadelphia, Pennsylvania    |
| HI-FI WORKSHOP<br>16400 W. Seven Mile Road<br>Detroit 35, Michigan        | <b>RHODE ISLAND</b>   |
|   | AUDIONICS, INC.<br>790 North Main Street<br>Providence, Rhode Island      |
|   | <b>VIRGINIA</b>   |
|   | KEY ELECTRONICS, INC.<br>126 South Wayne Street<br>Arlington, Virginia    |
|   | <b>WASHINGTON</b>   |
|   | SEATTLE RADIO SUPPLY<br>2117 Second Avenue<br>Seattle 1, Washington       |

Obviously, this is a limited number of dealers. Careful selection of reliable, qualified dealers is a slow process... so please bear with us if your area has not yet been covered. Thank You.


**HEATH COMPANY**

Berton Harbor, Mich.

A Subsidiary of Daystrom, Inc.




# Precision

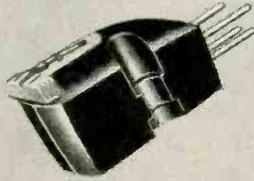

...precisely  
for music!

A pickup precisely  
designed for music!  
A stereo pickup with  
all the compliance,  
frequency response  
and distortion-free  
performance required  
for the highest quality  
music reproduction.

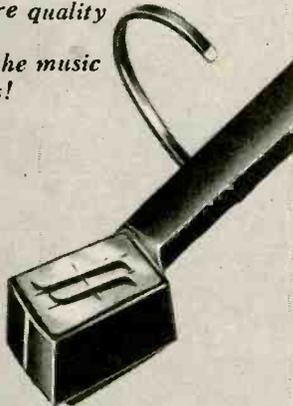This...is the  
**STANTON Stereo-  
FLUXVALVE...**  
where quality  
starts  
and the music  
begins!



The STANTON Model 196  
UNIPOISE Arm with inte-  
grated Stereo-FLUXVALVE  
Pickup—\$59.85 with replace-  
able 0.7 mil diamond  
T-GUARD Stylus.

The STANTON Model 371  
Stereo-FLUXVALVE Car-  
tridge—\$29.85 with replace-  
able 0.7 mil diamond  
T-GUARD Stylus.

Hermetically sealed for a lifetime of trou-  
ble-free use, the STANTON Stereo-FLUX-  
VALVE performs in a way no other pickup  
can equal. Use it in automatic or manual  
record playing systems.

PHOTOGRAPHED BY MORT WELDON



For those who can hear the difference

FINE QUALITY HIGH FIDELITY PRODUCTS BY

**PICKERING & COMPANY, INC.,**

Plainview, N. Y.

FLUXVALVE, T-GUARD, UNIPOISE are registered trademarks

Address Dept. G-19 for a free copy of  
IT TAKES TWO TO STEREO by Walter O. Stanton.

## TEST INSTRUMENTS

(Continued from page 77)

it to calibrate the unit. Otherwise, a high-impedance voltmeter will do. A meter's dc calibration is usually more accurate than the ac calibration, so use dc when calibrating the comparator with a meter.

To use a resistance bridge, connect it to the comparator's output terminals, set switch S1 to HIGH, S2 to 1, and R1 completely counterclockwise. Make a calibration line at this point and label it 1 with decals or India ink. Now measure the resistance with R1 at this point and then rotate the control completely clockwise to measure R2's resistance. If satisfactory, label this point 10 and return R1 to the counterclockwise position. Now adjust R1 to present the various resistance levels listed in Table II. The resistance being measured is R2 plus enough of R1 to give the value listed. Label all of the points needed, and calibration is completed.

If a voltmeter is used for calibrating, connect it to the output terminals and a convenient voltage to the high-level input terminals. Set the controls as before with R1 in the counterclockwise position. Note the voltmeter reading and then rotate R1 clockwise to give voltmeter readings to equal: original reading/1.1, o.r./1.2, o.r./1.3, etc. until all desired calibration points are determined.

The calibration of my model is in terms of voltage ratio but for some uses db may be better. Either way, keep in

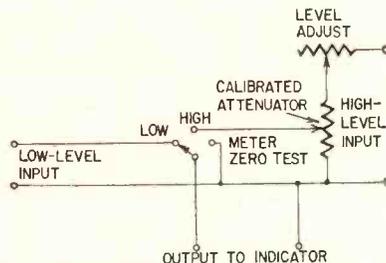


Fig. 3—Simplified circuit for measuring only small variations in high-level signals.

TABLE I

S2 Position	Attenuation Ratio	Maximum High-Level Input (volts)
1	1:1	150
2	10:1	420
3	100:1	420
4	1,000:1	420
5	10,000:1	420
6	100,000:1	1,000
7	1,000,000:1	1,000

TABLE II

R1 Dial Reading	Resistance at Output Terminals (ohms)	R1 Dial Reading	Resistance at Output Terminals (ohms)
1	11,100	2	5,550
1.1	10,100	3	3,700
1.2	9,250	4	2,775
1.3	8,540	5	2,220
1.4	7,930	6	1,850
1.5	7,400	7	1,586
1.6	6,940	8	1,388
1.7	6,530	9	1,233
1.8	6,170	9.5	1,168
1.9	5,840	10	1,100

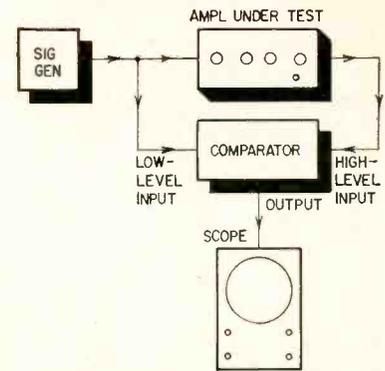


Fig. 4—Setup for measuring frequency response.

mind that the final accuracy can be no better than the calibration.

### How to use it

To make frequency response measurements connect the signal generator, amplifier, comparator and indicator as in Fig. 4. Try reversing each ac power-line plug to keep ac ripple on the indicator at a minimum.

Starting at one end of the frequency range, where the amplifier's response is minimum, adjust the generator to produce a suitable output from the amplifier—without overdriving the amplifier. Throw S1 to LOW and note the signal level. Now throw S1 to HIGH, set R1 to 1 and S2 to give a signal near the level of the LOW signal. Then adjust the amplifier gain control to make the HIGH output exactly equal to LOW output. Now move on to the next frequency, note the level of the LOW signal and adjust R1 until the HIGH signal again equals the LOW signal. The attenuator setting now indicates the signal level at the new frequency as compared with the original frequency. Now go on to the next frequency, checking it and all other necessary frequencies in the same way.

If you use a vtm as the indicator, its zero adjustment can be checked periodically by throwing S1 to METER ZERO TEST.

To make amplifier gain tests connect everything as shown in Fig. 4, set the amplifier's gain control at maximum, note the signal level at LOW and then with the attenuators reduce the signal at HIGH to equal that at LOW. The attenuator settings now show the amplifier's voltage gain.

Meters and oscilloscopes can be accurately calibrated over a wide range, using the comparator. To do so, connect an accurately known voltage, big enough to use on the highest indicator scale, to the HIGH input terminals. Connect the meter or oscilloscope to the output terminals. Then set the attenuator to various points in the desired range and note the indicator readings.

If a suitable high-level voltage is not available, connect a known low voltage to the LOW input and a variable voltage large enough to use on the highest indicator scale, to the comparator's HIGH input. With R1 set at 1 and S2 at a suitable point, adjust the high voltage until

## TEST INSTRUMENTS

the HIGH and LOW outputs are equal. Now the high voltage is of known level, since the low voltage and attenuator ratio are known, and can be used as the calibration standard.

To illustrate this with a practical example, the low-voltage source can be a 1.34-volt mercury cell. Connect it to the LOW input terminals. Connect a variable 0-150-volt dc supply to the HIGH terminals. Set R1 to 1 and S2 to 10<sup>2</sup>. Throw S1 to the LOW position and read the meter. It should be 1.34. Throw S1 to HIGH and adjust the variable voltage until the meter reads the same as in the LOW position. Now the variable voltage will be 100 times greater than the mercury cell or 134 volts. By adjusting R1 and S2, any voltage between 1.34 and 134 can be obtained at the comparator's output terminals.


By connecting any high-voltage source to the HIGH input terminals and taking the output from the output terminals the comparator can be used as a general-purpose voltage divider. However, be sure you don't exceed the voltage limits in Table I unless higher-wattage resistors are used. END

## LOW-CAPACITANCE PROBE

By **ROBERT G. MIDDLETON**

We usually think of a low-capacitance probe as a device to step up a scope's input impedance. By adding a damped peaking coil to the probe circuit, you also improve the scope's high-frequency response, important when checking video circuitry.

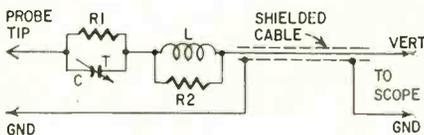R1 and C are the usual components used in a low-capacitance probe. Peaking coil L and damping resistor R2 are added. The required value for L is between 150 and 250  $\mu$ h. The best value for this inductor must be determined



by experiment. R2, about 10,000 ohms, is not critical.

This probe gives the greatest advantage on old-model scopes which do not have peaking coils in the vertical amplifier. To select L and to adjust the probe for best response, apply the output of a video sweep generator to the probe's input. Then view the probe's frequency response curve on the oscilloscope screen.

Try different values for L, and each time it is changed adjust C for the flattest possible frequency response. Use as small a value for L as possible, consistent with a flat response. Correct probe adjustment will give two to three times greater bandwidth than was previously available in old-model scopes.

# TOBE

## America's Fastest-Growing Service Capacitor Line...



# NEW!

## TOBE MYLAR\* MOLDED TUBULAR CAPACITORS

- *Molded of DuPont Mylar*, one of the finest insulation materials ever developed.
- *Thermoset Case Construction* secures leads and sections firmly to withstand extremes of handling, vibration, shock and soldering temperatures.
- *High Insulation Resistance*: Average megohm values per unit 10,000 at 25°C. Small capacitance variation with thermal change.
- *Temperature Operating Range*: -55° to +130°C.
- *Moisture Resistant*: Exceeds JAN-C-91 requirements.
- *Non-Inductive*: Extended foil construction insures low resistance connections and low RF impedance.

DESIGNED FOR SERVICE DEALERS

NEW TOBE MYLAR\* CAPACITOR KIT

FREE KIT CONTAINS  
80 CAPACITORS

ONLY

**\$15.84**



Today, order  
your Tobe Mylar  
Kit from your  
Tobe Distributor

Compact, clear-plastic dispenser contains an assortment of 80 Tobe Mylar capacitors in the most popular sizes, ratings and quantities for quick, efficient servicing. Covers over 60 different ratings at 200, 400 and 600 working volts and from .0001 to 1.00 mfd. Dealer pays only for the Tobe Mylar capacitors, kit is free.



# TOBE

RADIART

## CAPACITORS

**World Famous Philco Quality and  
Exclusive New Chassis Construction**

**make**

**PHILCO<sup>®</sup> TV**

**EASIEST**

**TO SERVICE**

**in the history of the TV industry!**

Philco brings an entirely new concept to the serviceability of television receivers by conveniently placing tubes and components right at your finger-tips. Philco chassis are designed, engineered and manufactured to make your job an easier and more profitable one.

**1**

**What Philco means by  
QUALITY**

At Philco it has been quality first in electronic products for *over 30 years!* "Guard Philco Quality" is a watchword and a creed! The first consideration in every phase of production is the maintenance of the highest standards of quality. In all plants an independent team of Product Performance Specialists is directly responsible to Philco management for the performance and dependability of all Philco products.

**2**

**What Philco means by  
DEPENDABILITY**

The proven and outstanding dependability of all Philco products is acclaimed by the millions of satisfied customers who have bought and used Philco products over the years. Philco goes to the greatest lengths to build in durability and quality that guarantee superior performance, dependable operation and long life in the consumer's home. It is this built-in dependability that pays off in satisfied customers for you.

**PHILCO**

*Famous for*

# Good Bye Mirrors!

Picture tube turns around for viewing while servicing!

**FILE DRAWER CHASSIS**  
Slides out on runners for ease of service

**ALL TUBES RIGHT ON TOP**  
Conveniently located for easy replacement

**ALL TEST POINTS ON TOP** No more awkward maneuvering to test components

**ALL COMPONENTS ACCESSIBLE FOR CHECKING**

**DESIGNED WITH THE SERVICE MAN IN MIND**

The new Philco Predicta chassis pictured above was designed with the service man in mind. It was designed to enable you to take the greatest advantage of your professional skills. It was designed to pay

off by enabling you to do your job quicker . . . make more calls and, thus, increase your profits. All Philco chassis are manufactured with the most modern automated methods in the industry insuring uniformity and dependability in your customers' homes.

IN THE PAST 30 YEARS PHILCO HAS TRAINED OVER ¼ MILLION INDEPENDENT SERVICE MEN.  
GET FAST, EASY "1-2-3" SERVICE TIPS FROM YOUR PHILCO DISTRIBUTOR TODAY!




## Cover Feature in December "Radio-Electronics"

Here is what they say about Philco Predicta TV.

“In the story of design for '59, it can hardly be disputed that one of the most unusual and extraordinary is that of the Philco Predicta line which includes the slide-out 'easy service' chassis and its separately and remotely mounted picture tubes.”

PHILCO ACCESSORY DIVISION • PHILADELPHIA 34, PENNSYLVANIA

**QUALITY** *the World Over*

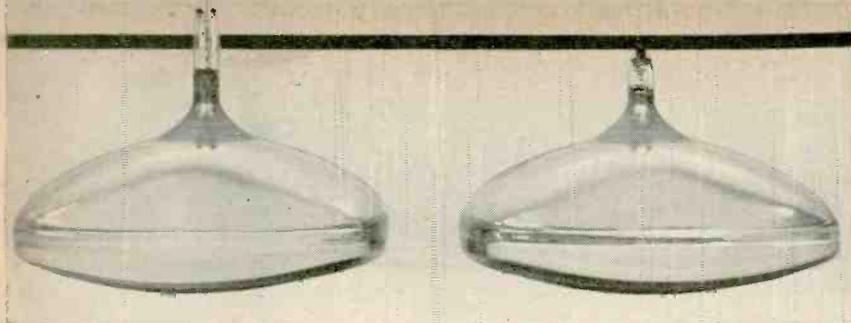

**WORLD'S STUBBIEST** picture tube is new 110° model developed by Sylvania, up to 2½ inches shorter than previous 110° tubes (left). The 17-inch tube shown here measures 10¼ inches from front to back. The new slim shape is the result of the development of a short electron gun which is located closer to the deflection yoke than previous types and may be operated at standard voltage with equal resolution at all beam currents. Philco is making a 17-inch tube of comparable dimensions and a 21-inch tube only 12-1/16 inches long.

**what's**

**new**

**?**



**SUN'S RADIO WAVES** are being studied with this new type radio telescope at Stanford University, Palo Alto, Calif., although it is only half completed. Its resolution will equal that of a single 365-foot dish antenna. At present it consists of 16 aluminum parabolic reflector antennas, each 10 feet in diameter and interconnected electronically and mechanically to move in unison, scanning the sun all day. Later a matching row will bisect the present one, making a huge cross of 32 dishes.

**RADAR ANTENNA** for Signal Corp's new "3-D" Frescanar (frequency scanning radar) system is shown in a plastic bubble with two of its developers, Hughes Aircraft engineers E. W. Templin and Dr. Nicholas A. Begovich. Designed for missile monitoring, Frescanar uses single antenna to detect distance, bearing and altitude, requires but one operator and has greater range, speed and resolution than conventional radar.



**PERSONAL PORTABLE TV**, a developmental lab model demonstrated by General Electric, uses 22 transistors and an 8-inch picture tube. Weighing 10 pounds and about the size of a toaster, it will operate 3-4 hours on a rechargeable silver-cadmium battery and may be operated on house current while the battery is being recharged. Power consumption is 7½ watts. There is no immediate prospect of the set being made commercially. A spokesman for G-E's TV Receiver Dept. points out that present transistor prices prohibits marketing it at an acceptable consumer price.





## PORTABLE Test Instruments

Over a couple of cups of coffee, Red and Fuzzball discuss types of equipment used in outside color TV servicing

By ROBERT G. MIDDLETON

TELEVISION CONSULTANT

THERE was a real gentleman come in about an hour ago," Bess advised Fuzzball.

"There ain't no gentlemen around here," Fuzz replied skeptically.

"This old goat was," Bess maintained. "Left me a dollar tip."

"I notice you been making some corny remarks lately," Fuzzball warned her. "You better be good or I'll turn you over my knee and give you a spanking." "I'd like to see you try," Bess replied bridling.

"Tell me, Fuzz," Red interrupted, "how are you making out with your new Philco hootnanny?"

"Oh, you mean the switch box for the base of the picture tube." (See Fig. 1.) "Aiyuh."

"I'm making out," Fuzzball replied. "There's only one angle I can't figure." "So?"

"Them two binding posts on the box," explained Fuzzball. "What are you supposed to do with them?"

"Come back, come back, Fuzz," Red replied, snapping his fingers. "I told you about them last time. Remember?"

"I must of forgot somehow," Fuzzball admitted.

"I'll tell you once more," Red advised him, "and try to remember this time."

"OK, OK," Fuzzball agreed humbly.

"Like I said before," Red continued, "you connect a scope to those posts."

"Now it rings a bell," Fuzz recalled. "You can switch the scope to the red, blue or green grid, or to the cathodes of the picture tube."

"And . . ." Red encouraged him.

"Well, of course we know that you can switch on the red, green or blue

fields by themselves. Or all three together," Fuzzball added.

"Do you reckon you can mind what we just said?" Red asked.

"I'll remember to my dying day," Fuzz promised.

"When he gets off on that kick, I pass," Bess announced, walking out of the room.

"I'll also remember about the trigger cheater for the high voltage on the Sylvania," Fuzzball offered.

"That's mighty big of you," Red replied.

"But just one thing . . ." Fuzzball hesitated.

"Like what?"

"If there ain't no tubular cheater, how am I going to measure the high voltage on the Sylvania?"

"Look," said Red, pulling a tear sheet from his pocket. "You take off the high-voltage cage. Stick the probe here at the corona cup on the high-voltage rectifier tube." (See Fig. 2.)

"I rang the bell the second time," Fuzzball said ruefully. "I recollect now you told me that last time."

"Is that something I ain't supposed to know?" Red asked good-naturedly.

"How about the fuses?" Fuzzball asked. "Where would I find them on the Sylvania?"

"Right down by the selenium rectifiers," Red explained, "look here." (See Fig. 3.)

"I dig you," Fuzz replied. "Even the size of the fuse is marked."

"Sure saves aggravation when you got to put in a new one," Red replied.

"One thing I sure go for on the Sylvania," Fuzzball announced.

"What's that?"

"That convergence box on the extension cables," Fuzz explained. (See Fig. 4.) "I can stand right in front of the screen while I'm going through convergence."

"I stand corrected," Red grinned. "I figured convergence went through you. But you're right. In fact, quite a few of the new color receivers use this kind of a convergence box."

Fuzzball and Red both looked toward the kitchen. A cracked voice was working over "Casey Was Waltzing With the Strawberry Blonde." Bess came out of the kitchen shaking her head.

"Who put the nickel in him?" Red asked.

"We got a new shipment of vanilla extract in," Bess explained, "and the cook figured he ought to see if it was up to snuff."

"Tell him to stick to snuff," Fuzzball suggested. "It's less revolting."

"But not much," Bess pointed out. "You know what?" Fuzzball asked.

"No, what?" Red returned. "I'm doing the convergence with the dots separated."

"Some guys figure it's easier that way," Red agreed.

"Seems a little easier," Fuzzball observed. "When I get the dot separations all the same, then they slide in easy with beam magnets." (See Fig. 5.)

"Same thing with crosshatch," Red added. "Lots of guys like to keep the color lines about  $\frac{1}{8}$  inch apart. Then when they get even  $\frac{1}{8}$ -inch spacings all over the screen, all they got to do is turn the beam magnets and the entire

(Continued on page 90)



Fig. 1—Fuzzball's new Philco hootnanny.

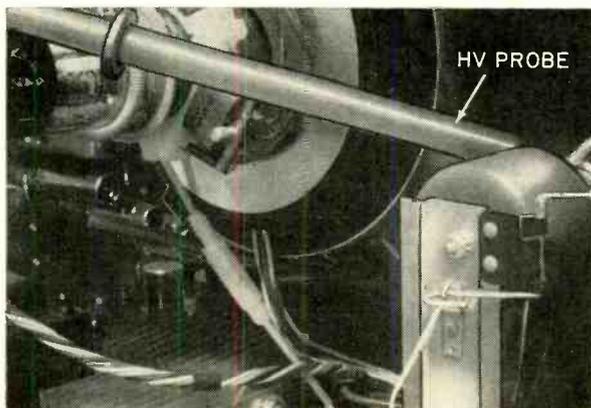


Fig. 2—Red told Fuzz to take off high-voltage cage.

**SUPERIOR'S NEW MODEL TW-11**

# STANDARD PROFESSIONAL TUBE TESTER



- ★ Tests all tubes, including 4, 5, 6, 7, Octal, Lock-in, Hearing Aid, Thyatron, Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity fuse types, etc.
- ★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.
- ★ The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.
- ★ Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.
- ★ NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

### EXTRAORDINARY FEATURE

SEPARATE SCALE FOR LOW-CURRENT TUBES. Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

The Model TW-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover.

**\$47<sup>50</sup>**  
NET

**Model TW-11 — TUBE TESTER . . . Total Price \$47.50 — Terms: \$11.50 after 10 day trial, then \$6.00 per month for 6 months.**

**SUPERIOR'S NEW MODEL 82**



# Multi-Socket Type TUBE TESTER

**TEST ANY TUBE IN 10 SECONDS FLAT!**

- 1 Turn the filament selector switch to position specified.
- 2 Insert tube into a numbered socket as designated on our chart (over 600 types included).
- 3 Press down the quality button —

**THAT'S ALL! Read emission quality direct on bad-good meter scale.**

**Model 82 — TUBE TESTER . . . Total Price \$36.50 — Terms: \$6.50 after 10 day trial, then \$6.00 monthly for 5 months.**

Primarily, the difference between the conventional tube tester and the multi-socket type is that in the latter, the use of an added number of specific sockets (for example, in Model 82 the noval is duplicated eight times) permits elimination of element switches thus reducing testing time and possibility of incorrect switch readings.

To test any tube, you simply insert it into a numbered socket as designated, turn the filament switch and press down the quality switch—THAT'S ALL! Read quality on meter. Inter-element leakage, if any indicates automatically.

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82 will outperform similar looking units which sell for much more — and as proof, we offer to ship it on our examine before you buy policy.

- Tests over 600 tube types.
- Tests OZ4 and other gas-filled tubes.
- Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings.
- Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence.
- Dual Scale meter permits testing of low current tubes.
- 7 and 9 pin straighteners mounted on panel.
- All sections of multi-element tubes tested simultaneously.
- Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms.

Model 82 comes complete, housed in portable, hand-rubbed oak cabinet with removable cover. Only

**\$36<sup>50</sup>**  
NET

**SHIPPED ON APPROVAL  
NO MONEY WITH ORDER — NO C.O.D.**

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — NO INTEREST OR FINANCE CHARGES ADDED. If not completely satisfied, return to us, no explanation necessary.

SEE PAGE 97 FOR COMPLETE DETAILS

**MOSS ELECTRONIC, INC.**

**3849 TENTH AVE., NEW YORK 34, N. Y.**

# PORTABLE Test Instruments



Over a couple of cups of coffee, Red and Fuzzball discuss types of equipment used in outside color TV servicing

By **ROBERT G. MIDDLETON**

TELEVISION CONSULTANT

**T**HERE was a real gentleman come in about an hour ago," Bess advised Fuzzball.

"There ain't no gentlemen around here," Fuzz replied skeptically.

"This old goat was," Bess maintained. "Left me a dollar tip."

"I notice you been making some corny remarks lately," Fuzzball warned her. "You better be good or I'll turn you over my knee and give you a spanking."

"I'd like to see you try," Bess replied bridling.

"Tell me, Fuzz," Red interrupted, "how are you making out with your new Philco hootnanny?"

"Oh, you mean the switch box for the base of the picture tube." (See Fig. 1.) "Aiyuh."

"I'm making out," Fuzzball replied. "There's only one angle I can't figure." "So?"

"Them two binding posts on the box," explained Fuzzball. "What are you supposed to do with them?"

"Come back, come back, Fuzz," Red replied, snapping his fingers. "I told you about them last time. Remember?"

"I must of forgot somehow," Fuzzball admitted.

"I'll tell you once more," Red advised him, "and try to remember this time."

"OK, OK," Fuzzball agreed humbly.

"Like I said before," Red continued, "you connect a scope to those posts."

"Now it rings a bell," Fuzz recalled. "You can switch the scope to the red, blue or green grid, or to the cathodes of the picture tube."

"And . . ." Red encouraged him.

"Well, of course we know that you can switch on the red, green or blue

fields by themselves. Or all three together," Fuzzball added.

"Do you reckon you can mind what we just said?" Red asked.

"I'll remember to my dying day," Fuzz promised.

"When he gets off on that kick, I pass," Bess announced, walking out of the room.

"I'll also remember about the trigger cheater for the high voltage on the Sylvania," Fuzzball offered.

"That's mighty big of you," Red replied.

"But just one thing . . ." Fuzzball hesitated.

"Like what?"

"If there ain't no tubular cheater, how am I going to measure the high voltage on the Sylvania?"

"Look," said Red, pulling a tear sheet from his pocket. "You take off the high-voltage cage. Stick the probe here at the corona cup on the high-voltage rectifier tube." (See Fig. 2.)

"I rang the bell the second time," Fuzzball said ruefully. "I recollect now you told me that last time."

"Is that something I ain't supposed to know?" Red asked good-naturedly.

"How about the fuses?" Fuzzball asked. "Where would I find them on the Sylvania?"

"Right down by the selenium rectifiers," Red explained, "look here." (See Fig. 3.)

"I dig you," Fuzz replied. "Even the size of the fuse is marked."

"Sure saves aggravation when you got to put in a new one," Red replied.

"One thing I sure go for on the Sylvania," Fuzzball announced.

"What's that?"

"That convergence box on the extension cables," Fuzz explained. (See Fig. 4.) "I can stand right in front of the screen while I'm going through convergence."

"I stand corrected," Red grinned. "I figured convergence went through *you*. But you're right. In fact, quite a few of the new color receivers use this kind of a convergence box."

Fuzzball and Red both looked toward the kitchen. A cracked voice was working over "Casey Was Waltzing With the Strawberry Blonde." Bess came out of the kitchen shaking her head.

"Who put the nickel in *him*?" Red asked.

"We got a new shipment of vanilla extract in," Bess explained, "and the cook figured he ought to see if it was up to snuff."

"Tell him to stick to snuff," Fuzzball suggested. "It's less revolting."

"But not much," Bess pointed out.

"You know what?" Fuzzball asked.

"No, what?" Red returned.

"I'm doing the convergence with the dots separated."

"Some guys figure it's easier that way," Red agreed.

"Seems a little easier," Fuzzball observed. "When I get the dot separations all the same, then they slide in easy with beam magnets." (See Fig. 5.)

"Same thing with crosshatch," Red added. "Lots of guys like to keep the color lines about  $\frac{1}{8}$  inch apart. Then when they get even  $\frac{1}{16}$ -inch spacings all over the screen, all they got to do is turn the beam magnets and the entire

(Continued on page 90)

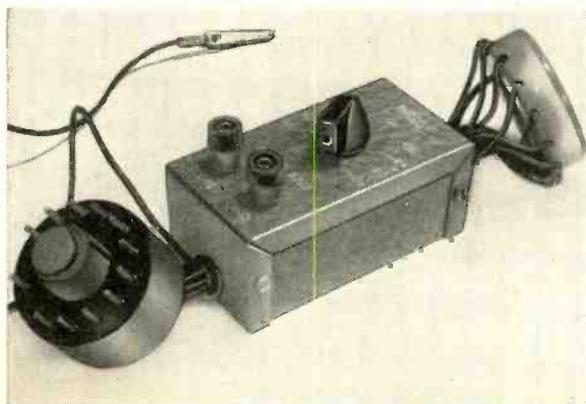


Fig. 1—Fuzzball's new Philco hootnanny.

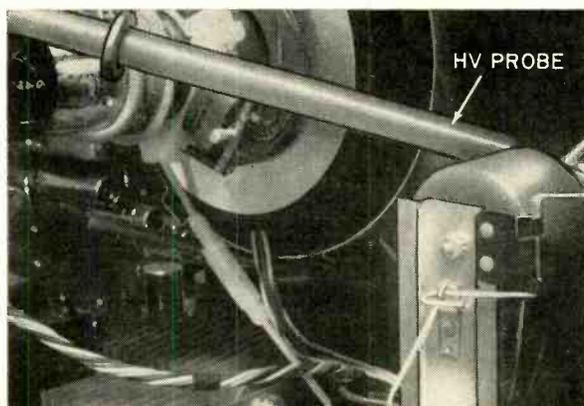


Fig. 2—Red told Fuzz to take off high-voltage cage.

# Build the Best... build **knight®-kits**

A PRODUCT OF ALLIED RADIO

with exclusive "CONVENIENCE ENGINEERING" for easiest building

SAVE UP TO

**50%**

KNIGHT-KIT design goes beyond handsome styling, advanced circuitry and guaranteed specifications. KNIGHT-KIT "convenience engineering" means just that...it goes deep-down, with special attention to those small but vital details that count...details such as carded and identified resistors, plastic-bagged hardware, pre-cut and stripped wire—details that make assembly far easier, that assure absolute accuracy, and finally reward you with proud enjoyment of the superior performance designed into your KNIGHT-KIT.



*America's Low-Cost HI-FI*  
*anyone can afford*  
**THERE'S NOTHING FINER**



### Deluxe FM-AM Hi-Fi Tuner Kit

The best-looking, best-performing FM-AM tuner kit for the money. You'll enjoy building it; you'll be proud of its performance and beauty. FM sensitivity is a remarkable 2.5 microvolts for 20 db of quieting. AM is 3 microvolts for 10 db signal-to-noise ratio. Outstanding features include: single large printed-circuit board with most critical wiring already done; AFC (with disabling feature); flywheel tuning; precisely pre-aligned RF and IF coils—no further alignment needed; tuned RF stage on FM; drift-compensated oscillator; neon glow tuning pointer; cathode follower output; rotatable built-in AM antenna. Beautiful French-gray case, 4 1/4 x 13 1/4 x 8". Ready for interesting easy assembly. Shpg. wt., 12 lbs.

Model Y-787. Net only

**\$49.95**

Easy Terms: Only \$5.00 Down



### STEREO High Fidelity...build your own at great savings

#### Stereo Preamp Control Center Kit

In a class by itself—a control center that will do anything and everything you want. Features complete input flexibility—5 Stereo inputs (including tape heads), additional 4 inputs for monaural; all can be permanently connected and controlled from single switch. Six record equalizations for monaural; RIAA for Stereo. Volume, bass and treble controls on concentric shafts with special clutch for both individual channel and overall control. Single switch selects straight Stereo; Stereo Reverse, either channel separately, or either channel into monaural output. Continuously variable loudness control; cathode follower output and special recorder outputs; hum-free (DC on all tube filaments). Exclusive printed-circuit switches and boards. Custom styled case, 4 1/4 x 13 x 8". Shpg. wt., 17 1/2 lbs.

Model Y-776. Net only

**\$62.50**

Easy Terms: Only \$6.25 Down

#### 60-Watt Stereo Basic Amplifier Kit

Absolutely the finest dual amplifier you can build—equal to highest-priced factory-built units. Ideal for use with the KNIGHT-KIT preamp, either as two 30-watt stereo amplifiers or 60-watt monaural amplifier. Exceptional response from 10 cps to 42,000 cps. Phenomenal 0.08% distortion at full 60 watts. Includes static plate current balancing adjustments for each channel; absolute stability under all operating conditions; custom-quality transformers. Also has special built-in circuitry, with easy external adjustment, for precise balance of gain on each channel to achieve perfect monaural performance. Two printed-circuit boards for easy assembly. Beautiful black and chrome; 9 x 14 x 8 1/4". (Less cover.) 36 lbs.

Model Y-777. Net only

**\$84.50**

Easy Terms: Only \$8.45 Down

Y-779. Gray metal cover. 4 lbs. Net...\$6.50

#### EXCLUSIVE PRINTED CIRCUITRY

KNIGHT-KITS incorporate the latest technical advances; many include exclusive printed-circuit switches, as well as printed circuitry. You save time and you can't go wrong.

#### EXCLUSIVE CUSTOM STYLING

KNIGHT-KIT hi-fi components, as easy to look at as they are to assemble, are professionally designed to take their place alongside the finest of home furnishings. You'll be proud of your finished work.

### Top-Value 12-Watt Complete Amplifier Kit... Best Buy in Hi-Fi



*True Hi-Fi for only*

**\$19.95**

(less cover)

Only \$2.00 Down

Never before has there been so much solid hi-fi value and quality performance at such low cost. Features smooth, clean output for truly rich reproduction. Guaranteed specifications: frequency response, 30-15,000 cps ± 1 1/2 db at half power; less than 1% distortion at full power. Has 15 db of inverse feedback. Has preamp stage equalized for magnetic cartridges; inputs for phono and tuner; separate bass and treble controls with both boost and attenuation, push-pull EL84 output tubes; virtually hum-free performance. Handsomely styled to look well anywhere; size with cover, 5 x 9 1/4 x 7". 7 1/2 lbs.



Model Y-784. 12-Watt Amplifier Kit, less cover. Net only

**\$19.95**

Y-783. Attractive French-gray cover for above. 3 lbs. Net only...\$3.95

**EASY TERMS ON knight-kit ORDERS AS LOW AS \$20**
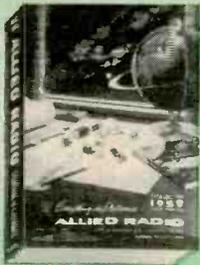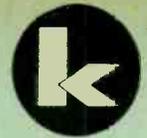
# the kits with the **GUARANTEED\*** specifications



## SEE ALLIED'S 1959 CATALOG FOR COMPLETE DETAILS

For full descriptions of the KNIGHT-KITS below, see the 452-page 1959 ALLIED Catalog. If you haven't a copy, send for it today—use coupon on following page.


there's a money-saving knight-kit for every quality Hi-Fi need




**Universal Stereo Control Kit**  
Provides full centralized stereo control (volume, balance and channel selection) for use with any two amplifiers. Handles up to 20 watts program material. Unit simply connects between speakers and output terminals of amplifiers (no amplifier rewiring needed). Lets you balance speaker system volume; provides master gain control for overall volume (can be used remotely); lets you play either channel monaurally through one or both speakers; provides channel reversal; phase reversal switch for best overall performance. 4½ x 7¼ x 4" 3/8 lbs.  
Model Y-778. Net only... \$9.95
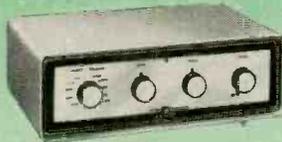
### \*MONEY-BACK GUARANTEE


Every KNIGHT-KIT meets or exceeds published specifications, or we refund your money in full.



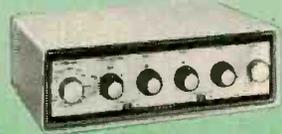**18-Watt Hi-Fi Amplifier Kit**  
Superb hi-fi specifications; deluxe custom styling. Includes 8 inputs for every desired signal source; full equalization; printed-circuit switches and boards for easy assembly. Shpg. wt., 15 lbs.  
Model Y-797. Net only... \$39.95



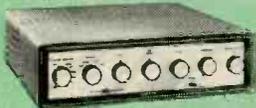**30-Watt Hi-Fi Amplifier Kit**  
Linear-deluxe Williamson-type circuit. Clear, rich 30 watts output; full equalization; 8 inputs; level and loudness controls; DC on filaments or preamp tubes; rumble filter; variable damping. Exclusive printed-circuit switches and boards. Custom-styled. 32 lbs.  
Model Y-762. Net only... \$76.95



**Deluxe Hi-Fi Preamplifier Kit**  
Quality audio control center. 16 combinations of equalization; 8 inputs including tape head; DC on all tube filaments; printed-circuit switches and boards. Custom-styled. 12½ lbs.  
Model Y-754. Net only... \$39.95




**25-Watt Hi-Fi Basic Amplifier Kit**  
Williamson-type circuit. Response, ±0.5 db, 9-70,000 cps at half power. Includes balance control; calibrated damping control; potted output transformer. Shpg. wt., 25 lbs.  
Model Y-793. Net only... \$44.50



**Hi-Fi Basic FM Tuner Kit**  
Authentic Hi-Fi FM response. Includes AFC; flywheel tuning; pre-aligned RF and IF coils. 4 microvolt sensitivity guaranteed. Printed-circuit board for easy assembly. Custom-styled case. Shpg. wt., 12 lbs.  
Model Y-751. Net only... \$38.95



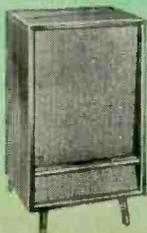**2-Way "Ducted Port" Hi-Fi Speaker System Kit**  
Pre-finished enclosure; easy to assemble. Hi-fi response, 45-14,000 cps. Includes 12" woofer and horn-type tweeter. Available in mahogany, blonde or walnut (specify finish). 26 x 29 x 14". Shpg. wt., 33 lbs.  
Model Y-789. Net only... \$49.95



**Deluxe "Ducted Port" 3-Way Speaker System Kit**  
Pre-finished enclosure, ready for quick assembly. Includes famous KNIGHT 3-way, 12" speaker. Response, 35-15,000 cps. Features "ducted port" for excellent bass response. Available in mahogany, blonde or walnut finish (specify). Shpg. wt., 47 lbs.  
Model DZ-262. Net only... \$73.45

## knight-kits for the Radio Amateur with designed-in value *Ham* appreciate



### Amateur Communications Receiver Kit

IT'S THE BEST • BUILD IT YOURSELF AND SAVE!

Has all the selectivity, sensitivity and features of high-priced commercial units. Covers 540 kc to 31 mc in 4 ranges; calibrated, electrical bandspread on 80-10 meter Ham bands; slug-tuned Hi-Q coils; continuous, VR tube-regulated B+ applied to HF oscillator; built-in Q-multiplier; delayed AVC; provision for Y-256 crystal calibrator (below). Sensitivity, 1.5 microvolts for 10 db signal-to-noise ratio. Selectivity: variable from 300 cps to 4.5 kc at 6 db down. Exalted BFO injection for SSB. Controls: Main tuning, bandspread, band selector, BFO pitch, RF gain, AF gain, BFO-MVC-AVC-AML, off-stby-rec-cal, ant. trim.—plus Q mult. controls: null-off-peak, selectivity, tune. Phone jack on front panel. Exclusive printed-circuit bandswitch; printed-circuit boards. Handsome metal cabinet, 10 x 10 x 16½". (Less speaker and S-meter.) 23 lbs.

Model Y-726. Net only... **\$104.50**

Easy Terms: Only \$10.45 Down

Y-727. S-Meter Kit for above. 1 lb. Net... \$10.75  
Y-728. 4" speaker in matching cabinet. 3½ lbs. Net... \$7.50

### POPULAR AMATEUR knight-kit VALUES!

#### 50-Watt CW Transmitter Kit

Ideal for the novice. Convenient band-switching, 80 through 10 meters. Efficient pi-network antenna coupler; effective TVI suppression. Uses 807 in final. Shpg. wt. 18 lbs.  
Model Y-255. Net only... \$38.95



#### Self-Powered VFO Kit

With built-in power supply. High stability; excellent keying; full TVI suppression. Planetary vernier drive. Calibrated for 80, 40, 20, 15 and 10 meters; output on 80 and 40 meters. Shpg. wt., 11 lbs.  
Model Y-725. Net only... \$29.50



#### Z-Bridge Kit

Accurately measures SWR from 1 mc to 150 mc. Also measures antenna impedance. Has coax input and output. Invaluable for attaining peak antenna efficiency. Shpg. wt., 1½ lbs.  
Model Y-253. Net only... \$5.85



#### 100-kc Crystal Calibrator Kit

Crystal frequency standard for any receiver, at very low cost. Gives marker every 100 kc up to 32 mc. Trimmer for zero-beating with WWV. With crystal. Shpg. wt. 1 lb.  
Model Y-256. Net only... \$10.95



# Fascinating knight®-kits for Hobbyists



Fun to build... with performance you'll proudly demonstrate  
 KNIGHT-KITS are the first choice of hobbyists, experimenters and students because they're truly "convenience-engineered" for easiest assembly, absolute dependability and finest performance. You'll have more building fun, you'll have more enjoyable performance, you'll save more with KNIGHT-KITS.


with exclusive  
*"Convenience Engineering"*  
 for assured build-your-own success...



## "Span-Master" 4-Band World-Wide Receiver Kit

Imagine the thrill of hearing overseas broadcasts on a precision receiver you've built yourself! At the flip of the bandswitch, you tune in the world—continuous 4-band coverage from Broadcast to 30 mc—fascinating foreign broadcasts, ships-at-sea, aircraft, police and marine radio, amateur reception on 80, 40, 20, 15 and 10 meters—all this wonderful short-wave, plus enjoyable local broadcast reception. Features sensitive regenerative circuit; easy bandspread tuning; built-in 4" Alnico V speaker; head-phone terminals; speaker cutout switch. Controls: Main Tuning, Bandspread, Bandswitch, Volume, Coarse and Fine Regeneration. Easy to build from marvelous instruction manual. Handsome cabinet; 6 1/4" x 13 3/4" x 6 1/4". For 110-125 v. AC. Shpg. wt., 7 lbs. **\$24.95**  
 Model Y-258. Net only.....

Easy Terms: Only \$2.50 Down

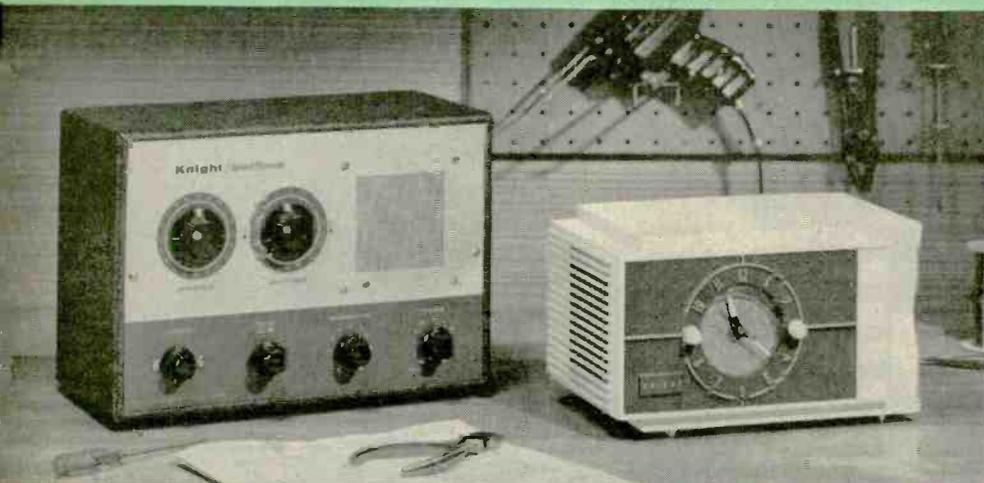

## "Space Spanner" Receiver Kit

Thrilling 2-band receiver, easy to build, fun to operate—a terrific value. Bandswitch selects exciting short-wave, including foreign broadcasts, amateur, aircraft, police and marine radio (6.5 to 17 mc), and standard broadcast. Highly sensitive regenerative circuit. Built-in 4" PM speaker and beam-power output for strong volume. Has head-phone jacks and switch to cut out speaker. Easy to assemble from step-by-step instructions. Handsome cabinet, 7 x 10 1/2 x 6". AC or DC operation. Shpg. wt., 7 1/2 lbs. **\$18.95**  
 Model Y-259. Net only.....

## "Ranger" Clock-Radio Kit

You'll be proud of the performance of this easy-to-build clock-radio. Provides wonderful broadcast band reception. Includes Telechron clock with sleep-switch timer plus automatic radio wake-up/alarm switch. Radio automatically shuts off at night and wakes you in morning; also turns on appliances automatically. Module plug-in circuits and printed-circuit board for quick, easy assembly. Beautiful blue and white plastic cabinet. 6 x 9 1/2 x 5 1/4". For 60 cycle AC only. Shpg. wt., 5 lbs. **\$24.95**  
 Model Y-737. Net only.....  
 Easy Terms: Only \$2.50 Down

## Widest choice of quality Hobbyist Kits

### "Ranger III" AC-DC Radio Kit




Superhet broadcast band receiver. Built-in antenna; AVC; Alnico V speaker. Black plastic cabinet. AC or DC. Shpg. wt., 4 1/2 lbs.  
 Model Y-736. Net only... \$16.95

### "Ocean Hopper" Receiver Kit



Regenerative receiver for broadcast, long wave and short wave reception from 155 kc to 35 mc. With coil for broadcast band. For AC or DC. Shpg. wt., 7 lbs.  
 Model Y-749. Net only... \$15.95  
 Y-748. Set of plug-in long wave and short wave coils. Net... \$2.95

### "Ranger III-PC" AC-DC Radio Kit

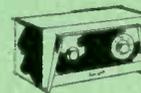

Printed-circuit broadcast band superhet. Easy to assemble. Has AVC, built-in loop antenna, Alnico V speaker. Ivory plastic cabinet. AC or DC. Shpg. wt., 4 lbs.  
 Model Y-738. Net only... \$18.95

### "Ranger" Radio-Intercom Kit



It's a broadcast band radio—it's an efficient 2-way Intercom—both in one! Ivory plastic case for Master station/Radio; smartly styled Remote station. With 50-ft. cable. AC or DC. Shpg. wt., 8 lbs.  
 Model Y-739. Net only... \$27.50

### "Trans-Midge" Radio Kit




Tiny 1-transistor radio for local broadcast reception. Works for months from single penlight cell supplied. Handsome plastic case. Fascinating to build. (Requires headphones and antenna.) 8 oz.  
 Model Y-767. Net only... \$2.45

### 10-Circuit Transistor Lab Kit



Builds any of 10 favorite projects. Entire kit on a printed circuit board. Just plug in leads to change from project to project. 3 lbs.  
 Model Y-299. Net only... \$15.75


### 1-Transistor Radio Kit

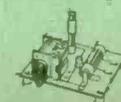

Offers fine local broadcast head-phone reception. Printed circuit board for easy assembly. Works for months from penlight cell supplied. (Antenna and headphones required.) Shpg. wt., 1 lb.  
 Model Y-765. Net only... \$3.95
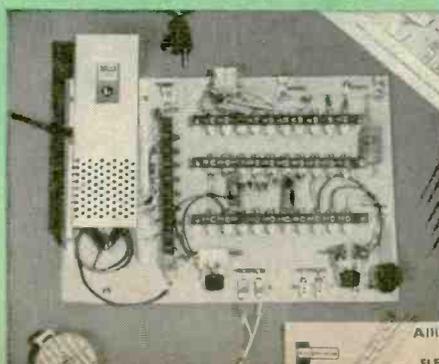
## 12-In-1 Electronic Lab Kit

Fascinating way to learn electronics—build any one of 12 practical circuits! Change circuits just by relocating a few wires. Safety-designed; no voltage exceeds 25v. Makes any one of the following: AM radio, amplifier, code oscillator; home "broadcaster"; electronic timer, switch or flasher; voice-operated, capacity-operated or photoelectric relay; CW "transmitter"; light control oscillator. With all parts, mike, phototube, instructions for each project. For 110-125v. AC. Shpg. wt., 3 1/2 lbs. **\$14.95**  
 Model Y-272. Net only.....



and Experimenters



**knight-kit** Quality Test Instruments

BETTER BY FAR...ADVANCED DESIGN...GUARANTEED SPECS


DO THE EASY ASSEMBLY...SAVE OVER **50%**

**MONEY-BACK GUARANTEE**

Every KNIGHT-KIT meets or exceeds published specifications—or we refund your money in full.

EASY TERMS on orders as low as \$20

**5-Transistor Superhet Radio Kit**

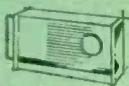


Quality personal portable. Printed circuit for easy assembly. Built-in antenna; 3/4" speaker; prealigned IF's; phono jack; 200-hour battery playing life. Handsome Ivory and gold styling. Less battery (\$1.43). 2 lbs. Model Y-771. Net only. . . . . \$25.95

**2-Transistor Pocket Radio Kit**



Excellent for local broadcast reception. Newest printed-circuit board for easy assembly. Built-in antenna; miniature dynamic earphone; plays for months from single battery. In handsome carrying case; only 4 x 3 1/2 x 1 1/2". Less battery (\$1.25). 1 1/2 lbs. Model Y-263. Net only. . . . . \$11.50

**2-Way Intercom System Kit**

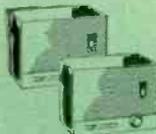

Complete 2-station system; low-cost, easy to assemble. High gain, clear toned, sensitive. Has 2-stage amplifier and 4" PM speakers. Handsome metal cabinets. Includes master, remote and 50-ft. cable. AC or DC. 8 lbs. Model Y-297. Net only. . . . . \$14.95

**Electronic Photoflash Kit**



Fast 1/700th-of-a-second flash; 50 watt/second output. Synchronizes with any camera with X or O shutter. Less battery. Shpg. wt., 4 lbs. Model Y-244. Net only. . . . . \$29.50

**Wireless Broadcaster—Amplifier Kit**



Play music or make announcements through your radio set, using mike or phono—no connection to set needed. Use also as audio amplifier. Has built-in preamp. AC or DC. Shpg. wt., 3 lbs. Model Y-706. Net only. . . . . \$11.95

**Transistor Code Practice Kit**




Ideal for beginners learning code. 500 cps tone. Single penlight cell supplied operates unit for months. Jacks for headphones; screw terminals for key. Shpg. wt., 1 lb. Model Y-239. Net only. . . . . \$3.95

**Crystal Set Kit**



Gives clear headphone reception of local broadcast stations. Sensitive crystal diode; efficient "Hi-Q" coll. (Antenna and headphone required.) Shpg. wt., 1 lb. Model Y-261. Net only. . . . . \$2.35

**Photoelectronic Relay Kit**

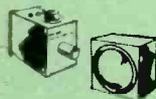

Ultra-sensitive relay at very low cost. Fine for automatic control of lights, door openers, as a burglar alarm, etc. Shpg. wt., 3 1/2 lbs. Model Y-702. Net only. . . . . \$13.50  
Y-703. Light Source only. . . . . \$ 6.75



**Vacuum Tube Voltmeter Kit**

Top buy in a quality VTVM. Entire chassis is printed-circuit board—easy to assemble. Balanced-bridge, push-pull circuit; 1% film-type resistors; 200  $\mu$ a movement; 4 1/2" meter; includes zero center scale and direct-reading db scale. Polarity reversing switch. Input Res.: 11 megs. DC and AC rms, 0-1.5-5-15-50-150-500-1500; AC Peak-to-Peak, 0-4-14-40-140-400-1400-4000; Response, 30 cycles to 3 mc; Ohms, 0-1000-10K-100K and 0-10-100-1000 megs; db, -10 to +5. Includes battery and test leads. For 110-125v., 50-60 cycles. Shpg. wt., 6 lbs. Model Y-125. Net only. . . . . **\$25.75**


Easy Terms: Only \$2.58 Down



**Lowest Cost Tube Checker Kit**

A really tremendous value in a quality tube checker. Checks over 400 tubes. Features "Flip-Card" charts with tube settings in loss-proof pull-out storage drawer. Has sockets for 7-pin miniature, 9-pin miniature, octal and loctal base tubes. Checks for cathode emission, filament continuity, shorted elements. Meter has "Replace-Good" scale and special scale for checking diodes. With quick-setting, universal-type selector slide switches. Includes "Hi-Lo" line-voltage regulator switch. Compact and light—use anywhere. With tube charts. 6 1/2 lbs. Model Y-707. Net only. . . . . **\$19.95**

Easy Terms: Only \$2.00 Down

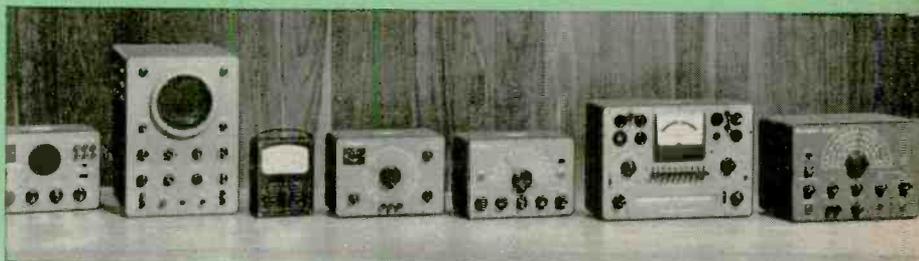

there is a knight-kit to fill every test equipment need

For detailed descriptions, see the 1959 Allied Catalog.

5" Wide-Band 'Scope Kit . . . . .	\$65.75	High-Gain Signal Tracer Kit . . . . .	\$26.50
5" General Purpose 'Scope Kit . . . . .	42.00	Audio Generator Kit . . . . .	32.95
20,000 Ohms/Volt VOM Kit . . . . .	29.50	Resistor-Capacitor Tester . . . . .	19.50
1,000 Ohms/Volt VOM Kit . . . . .	16.95	"In-Circuit" Capacitor Checker Kit . . . . .	12.50
'Scope Voltage Calibrator Kit . . . . .	12.75	Flyback Checker Kit . . . . .	19.50
Counter Tube Checker Kit . . . . .	29.75	Transistor & Diode Checker Kit . . . . .	8.50
Portable Tube Checker Kit . . . . .	34.75	Resistance Substitution Box Kit . . . . .	5.95
TV-FM Linear Sweep Generator . . . . .	44.95	Capacitance Substitution Box Kit . . . . .	5.95
RF Signal Generator Kit . . . . .	19.75	6V-12V Battery Eliminator Kit . . . . .	32.95

ORDER BLANK

**ALLIED RADIO** Dept. 132-A-9

100 N. Western Ave., Chicago 80, Ill.

Ship me the following KNIGHT-KITS:

Quantity	Description	Model No.	Price

\$ . . . . . enclosed. (For parcel post include postage; express is shipped collect.) All prices Net F.O.B. Chicago


My Down Payment in the amount of \$ . . . . . is enclosed. Send Time Payment form

Send FREE 452-Page 1959 Allied Catalog


Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

*Free!* 1959 452-PAGE ALLIED CATALOG

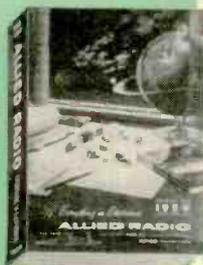See pages 241-273 for detailed descriptions of all KNIGHT-KITS: Hi-Fi, Hobby, Test Instrument, Amateur. The 1959 Allied Catalog is your complete Buying Guide to the world's largest stocks of everything in Electronics.



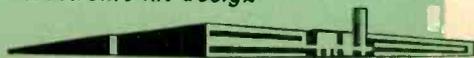38 years of experience in electronic kit design



DON'T SAY "BRIGHTENER"  
SAY

Perma-Power

**UNIVERSAL**

TV TUBE BRITENER

Engineered for quality . . .  
and fully guaranteed!

Model C-301

For use in Series  
or Parallel Wired Sets

List Price \$4.45



Unique design allows operation as constant voltage or constant current transformer. Gives 6.3 or 7.8 volts output with Isolation on Series or Parallel sets. Works on electrostatic or electro-magnetic focus picture tubes. Relieves Cathode-Filament shorts, gives no Boost output.

DON'T SAY "BRIGHTENER"  
SAY

Perma-Power

**VU-BRITE**

Engineered for quality . . .  
and fully guaranteed!

Model C-401

For use in Series Sets

Model C-402

For use in Parallel Sets

List Price \$1.49

The price leader for brightening most sets! Auto-former type transformer increases filament voltage to 7.8 V. Works on electrostatic or electro-magnetic picture tubes.



Don't say "brightener"  
Say PERMA-POWER

The Standard of All Comparison  
Available from your parts distributor

**PERMA-POWER COMPANY**  
3106N. ELSTON AVE., CHICAGO 18, ILL.

**TELEVISION**

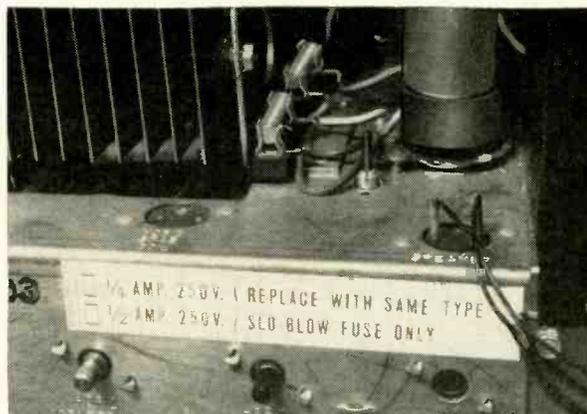


Fig. 3—Fuzzball digs the fuses on the Sylvania.

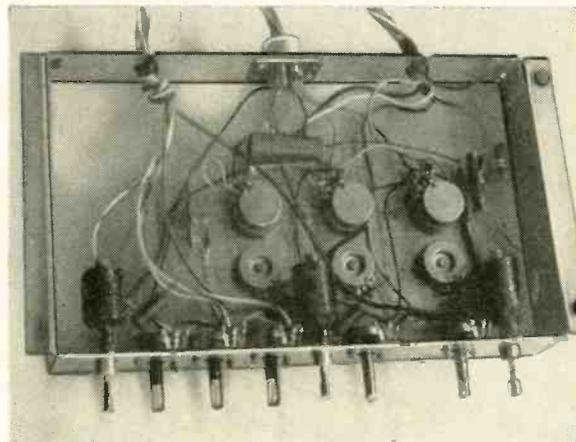


Fig. 4—Portable convergence boxes—Fuzz likes 'em.

(Continued from page 85)  
screen comes into convergence."

"And another thing . . ." Fuzzball ventured.

"What's eating you now?"

**Three kinds of generators**

"These color signal generators we're using. We got three kinds now, and I'm foxed up worse than Hogan's goat."

"We do have different kinds," Red agreed, "and for different reasons."

"I dig the rainbow the most," Fuzz told him. "I been taking that little rainbow along on all my calls."

"A rainbow, if it's crystal-controlled, is it for installation work," Red explained. "It's light, compact, and accurate. And it gives you all the data you need to install a set."

"Just what is the difference between a rainbow and an NTSC generator?" Fuzz asked with a puzzled look.

"Well," Red explained, "the NTSC system of color TV transmits true colors that vary in accordance with the program material."

"Is that what NTSC means?"

"Not exactly," Red replied patiently. "In the NTSC system, the color picture is broken into two parts."

"Two parts?"

"One plus one equals two," Red emphasized. "The color picture is broken up into the black-and-white portion and the color portion."

"That would be the Y signal and the chroma signal," Fuzzball ventured.

"You're cooking with gas, boy," Red complimented him. "The Y signal is just the same video signal that we have

known for years in black-and-white."

"And the chroma signal," Fuzzball continued uncertainly, "is the 3.58-mc color subcarrier?"

"Right," Red replied. "Do you know what the basic properties of color are?"

"Seems I recall that all colors have brightness, hue and saturation," Fuzzball said slowly.

"You recall right," Red assured him. "And what is the Y signal?"

"That's the brightness signal—I know that much, anyhow," Fuzzball said proudly.

"Yep. And so the chroma signal is the hue and saturation signal."

"Then an NTSC color bar generator has both a Y signal and a chroma signal?" Fuzzball asked.

"Exactly," Red replied. "And a rainbow generator . . ."

"I reckon it has the chroma signal but no Y signal."

"You're right on the beam," Red said with a grin. "Let's have another cup of Bess' dishwasher."

"I heard that last remark," Bess said. "A little more of your lip and I'll crown you king for a day," she promised, raising a pot of hot soup to emphasize her words.

"These little things are sent to try us," Red replied soothingly.

"This color TV work is the curse of man," Fuzzball said reflectively.

"Work is the curse of the drinking class. Any kind of work," Red assured him. "Shake a leg there, Bessie."

"To go a little farther into the difference," Fuzzball suggested, "you could say that a rainbow generator is

## TELEVISION

an incomplete NTSC generator."

"Yes and no," Red pointed out. "A rainbow generator does not operate at the color subcarrier frequency, but on an offset subcarrier frequency."

"This halfway rings a bell," Fuzzball said. "A rainbow generator runs at the subcarrier frequency minus the horizontal scanning frequency, I heard somewhere."

"Right you are," Red corroborated, "and if you want to get technical about it, a rainbow is a color simulator—period."

"But it works out OK for us on installation," Fuzzball observed.

"You ain't just a-woofin'," Red replied. "It's a real good deal for field work."

"How about bench work?"

"That depends on whether the rainbow output is keyed, for one thing," Red informed him. "An unkeyed output has very definite limitations."

"But suppose the rainbow is keyed up into bars?"

"In that case, you can get by on bench work, if you use your head."

"What are you driving at?"

"Well, No. 1, you have no white bar on a simulator."

"What do you do about that?" Fuzzball asked.

"You have to check white reproduction on a station signal," Red explained.

"What else?"

"You can't check reproduction of light colors such as yellow," Red continued.

"But you could get a pretty good check on darker colors like green and red, that make yellow when they're

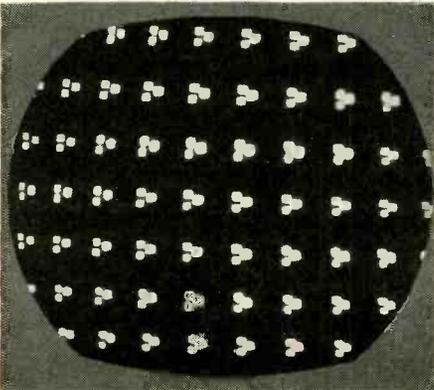
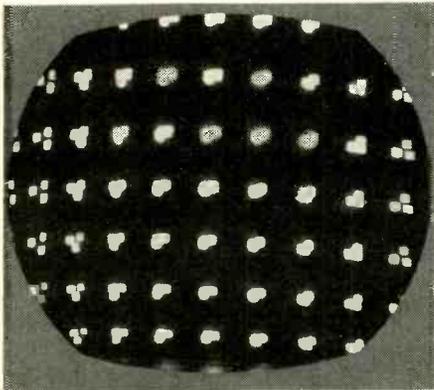


Fig. 5—(top) Misconverged white dots; (bottom) dots ready to be converged with beam magnets.

"FELLAS—THERE'S GOLD IN THESE

# C-D TWIN TREASURE CHESTS"

- **FILLED WITH C-D CAPACITORS**

the finest you can use to establish customer confidence.

- **FASTER CAPACITOR TURNOVER**

because you'll always have the fast movers on hand.

- **SPEEDS UP YOUR WORK**

because replacements are easy to identify, always handy.

- **HANDSOME METAL CABINETS**

make shop neater, prevent misplaced pieces.



See C-D's "Treasure Chests" at your Cornell-Dubilier distributor or write to Cornell-Dubilier Electric Corporation, South Plainfield, N. J., Department RE-1.



### SUGGESTED CONTENTS:

**TWIST-PRONG SECTION CONTAINS** 12 popular C-D "Preferred Type" Twist-Prongs (and room for 6 more)

**TUBULAR SECTION CONTAINS** 16 popular C-D "Blue Beaver" Tubular Electrolytics

73 PM Mylar Tubulars

**BOTH CABINETS ARE FREE. YOU PAY ONLY FOR THE PREFERRED C-D CAPACITORS.**

**YOUR COST: \$49.95**



Consistently **CORNELL-DUBILIER** Dependable

**SERVICE CAPACITORS**

# You learn more from SAMS BOOKS

OVER 1,200,000 IN USE

## JUST OUT!



### "Know Your Oscilloscope"

Paul C. Smith's important new book helps you understand and get the most from your oscilloscope

This know-how, show-how book, packed with new ideas and methods really helps you master the use of this important instrument. Covers oscilloscope circuitry, adjustment, operation, application and servicing. Chapters include: General Information; Power Supplies; Sweep Systems; Synchronization; Amplifiers; Special Features; Accessories; Adjusting and Servicing; Frequency and Phase Measurements; Amplifier Testing with Square Waves and Sweep Signals; Radio and TV Alignment; Practical Applications; Service Procedures. A vital book for anyone who uses an oscilloscope. 160 pages, 5½ x 8½". Only **\$2.00**

## CURRENT BEST-SELLERS



### "101 Ways to Use Your Sweep Generator"

A complete and practical guide to the fullest use of your sweep generator. Each application is covered concisely with full data on connections required, additional equipment needed, proper test procedure and

evaluation of results. Specific sections cover use of the sweep generator for checking and calibrating test equipment, antenna measurements, RF and IF alignment and measurements, special uses in color receiver tests, etc. Over 250 illustrations, waveforms and diagrams. Invaluable for technicians, engineers and students. 148 p., 5½ x 8½". Only **\$2.00**



### "Servicing Transistor Radios"... Vol. 2

You'll save time, you'll earn more on Transistor Radio repairs with this complete data on 60 late models. Based on actual lab analysis of each set. You get the famous Sams Standard Notation schematics;

full photo views of each chassis; complete alignment data; full parts replacement information—everything you need to be successful in fast-growing transistorized radio servicing. Includes valuable section on transistor circuits in general, along with useful troubleshooting chart. 160 p., 8½ x 11". Only **\$2.95**

## HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. A-29 2201 E. 46th St., Indianapolis 6, Ind.

Send me the following books:

- "Know Your Oscilloscope" (KOS-1).
- "101 Ways to Use Your Sweep Generator" (TEM-1).
- "Servicing Transistor Radios," Vol. 2 (TSM-2).

\$.....enclosed.  Send Free Book List

Name.....

Address.....

City.....Zone.....State.....  
(outside U.S.A. priced slightly higher)

## TELEVISION

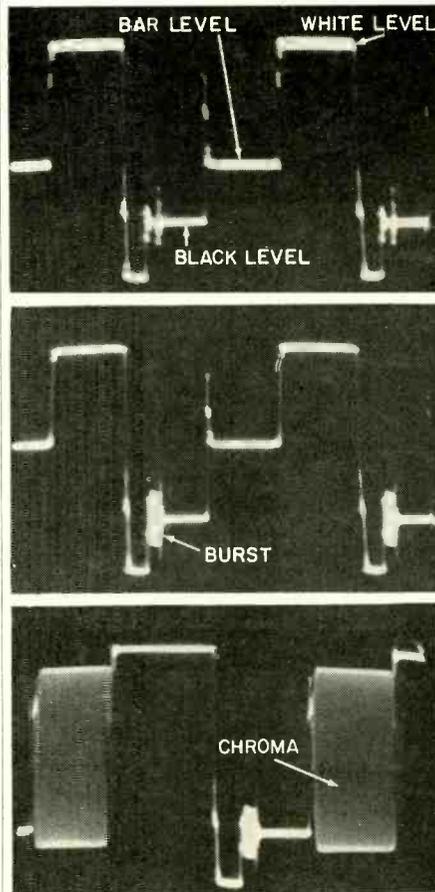


Fig. 6—(top) Y signal only; (center) Y signal with burst; (bottom) Y signal with chroma bar and burst.

mixed," Fuzzball suggested.

"You're really using your bean," Red acknowledged. "What you say is absolutely right."

"What else?"

"This is something you wouldn't get to for a while," Red explained, "but there are certain kinds of trouble in a color chassis where the Y signal gets into the chroma section and causes trouble."

"So if a generator doesn't have a Y signal, you could beat the devil around the stump quite a while."

"Yep. There is one point here, though, that you should keep in mind." "Name it?"

"A few of the higher-priced simulators have the rainbow on a pedestal. That way, you can make the basic Y checks, at any rate."

Bess interrupted. "Say, you guys know so much about electricity, maybe you can tell me something."

"Shoot," Red invited.

"I'm fixing to hit the sack last night after the snowstorm," she explained. "I jerk off one of these silk stockings quick-like, and a blue spark jumps from the stocking to my toe."

Red and Fuzzball both looked at her quizzically.

"What causes that?" Bess asked.

"You must be wearing shocking stockings," Fuzzball observed.

"Don't talk silly," Bess snapped, "I'm asking you a serious question."

"Science probably knows the answer," Red advised her, "but I couldn't tell you. I never wore silk stockings."

"Maybe you ought to wear a ground wire and let it drag behind you," Fuzzball suggested helpfully.

"What's a ground wire?" Bess asked.

"It's pretty technical," Red informed her. "Let's not go into that. You probably wouldn't like it, anyhow."

How about the color test pattern?

"Say, Red," Fuzzball spoke up, "is the color test pattern the same as the output from an NTSC color bar generator?"

"Always breaking out in fresh places," Red observed. "A test pattern from a color TV station has the same type of signal as an NTSC generator. But there is just one thing."

"What's that?"

"The color test pattern is transmitted at 75% saturation. Most color bar generators supply a signal at 100% or 50% saturation. Up-to-date generators have a switch for going from 100% to 50%."

"But I suppose you could adjust the generator to put out a 75% saturated signal?"

"That's right," Red replied. "With a good wide-band scope, it's no bind."

"Why is a color test pattern 75% saturated?"

"Because that is the highest saturation used in normal programming," Red explained.

"I sometimes wonder if I'll ever know my way around this color TV racket," Fuzzball muttered.

"Don't forget that success is as easy as failure—sometimes easier," Red said firmly.

"Does a color TV station ever transmit 100% saturated colors?" Fuzzball asked.

"Once in a great while, you will have a colored object in a scene that is 100% saturated," Red told him. "But when that happens, the picture carrier is temporarily overmodulated."

"What does that mean?"

"Well, the color is not reproduced quite correctly. It is distorted."

"Then why can we use 100% saturated color bars from a generator?" Fuzzball persisted.

"Simply because in a generator, a little more leeway is allowed between

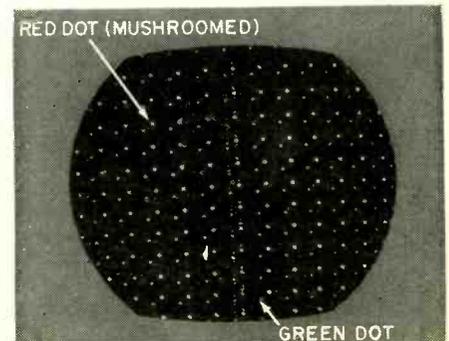


Fig. 7—Red and green dots on screen; red dots mushroomed.

## TELEVISION

white level and zero carrier."

"Is it good to have the 100% saturated output?"

"Definitely," Red replied, "just as it's good to have a 50% saturated output. Depends upon the test that you are making."

"Can you give me a f'rinstance?" Fuzzball asked.

"I could, but that would get us a little off the beam into bench work," Red observed. "Let's take a raincheck on it there."

"OK by me," Fuzzball replied.

"Say, Red."

"What?"

"Does an NTSC generator give you the Y signal with burst only?"

"Most of them do," Red informed him.

"Look at these pictures in my notebook." (See Fig. 6.)

"I see what you mean," Fuzzball agreed. "Why do we have the Y signal and also Y with burst?"

"That gets us into circuit testing again," Red replied. "I doubt if we ought to go into the details now."

"Suits me," Fuzzball agreed. "I'm getting a little punchy as it is."

"Anything else you want to cover before we get on our horse?" Red asked.

"Yes, there is," said Fuzzball. "When you have a white dot pattern on some sets, the red dot seems to spread out more than the blue and green dots. Why is that?"

Red flipped several pages in his notebook. "You mean like this?" he inquired. (See Fig. 7.)

"That's the deal," Fuzzball exclaimed. "What causes it?"

"There's two possibilities," Red replied. "A mushrooming on the red can be caused by setting the red screen too high. You can't do this on all sets, but on some you can."

"What's the other reason?" Fuzzball asked.

"Low emission," Red stated. "When a color picture tube gets near the end of its useful life, you will often see the red beam begin to mushroom."

"It really had me stopped," Fuzz said. "It's one of those deals that I just couldn't figure."

"Well, it's not a simple matter. Something like that will stop about anybody the first time."

"I suppose if the emission is low, you can't do anything about it," Fuzzball suggested.

"I wouldn't say that," Red corrected him. "Just like in a black-and-white picture tube, you can sometimes get a little more service by using a booster."

"If I was old Fatpants, I'd tie a can on your tails," Bess advised them.

"Why would you do a thing like that?" Fuzzball asked.


"Do you guys take a coffee-break or a vacation?" she demanded.

"Bess is right," Red agreed. "We better get on our horse and shovel off."


Fuzzball slipped a dime under his saucer, with a guilty look.

"Are you sure you can spare it?" Bess snapped after him. END

JANUARY, 1959

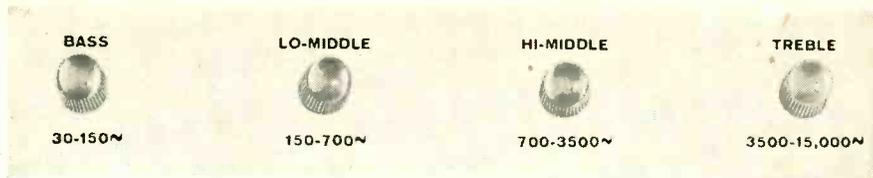
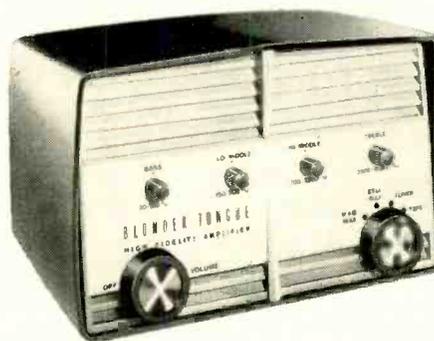
# these 4 knobs provide unlimited control of frequency response




## NEW BLONDER-TONGUE MODEL A-1 HIGH FIDELITY AMPLIFIER

**A unique B-T Development!** The Model A-1 Audio Amplifier divides the audible spectrum into its *four* significant segments (BASS, LO-MIDDLE, HI-MIDDLE and TREBLE.) *Four* separate tone controls permit you to boost or attenuate any frequency range or combination of ranges. The result—a degree of tonal selectivity unobtainable *anywhere* in the amplifier field. Solo instrumentalists or vocalists may be drawn out of the orchestral background to take their places in front of the orchestra. Correction for poor room acoustics, or for deficiencies in associated equipment, is


instant and exact. Power output is 12 watts (music wave forms).

The Model A-1 gives you high fidelity performance you'd expect to find only in amplifiers costing considerably more! Frequency response is uniform within ½ db from 30 to 15,000 cycles; harmonic distortion, below 1% at 10 watts output. Inputs are provided for magnetic and crystal phono cartridges, with *automatic* RIAA equalization on both. Tape and tuner inputs add to its versatility. Complete function selection on front panel. Housed in a handsome, two-tone cabinet, the A-1 lists at 77.50.

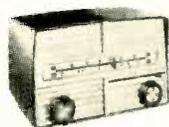
**MATCH THE A-1 WITH THESE BLONDER-TONGUE COMPONENTS FOR  
A COMPLETE, VERSATILE HI-FI SYSTEM COSTING LESS THAN \$160**



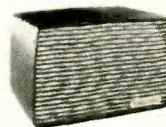**Model T-88 FM-AM Tuner** — Amazing sensitivity on FM and AM. Frequency response, 20-20,000 cycles. Built-in FM antenna, with provision for external antenna. Built-in ferrite AM antenna. Simple, plug-in connection with A-1 amplifier for existing phonograph or TV receiver. Accurate and stable slide-rule tuning. 64.50



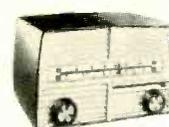**Model SS-2 Twin Speaker System**—Housed in an acoustically correct enclosure, the SS-2 Twin Speaker System includes two carefully matched 4" speakers with overlapping frequency ranges. Ideal for use as a multiple speaker system in a monaural installation or, as a second system for conversion to stereo. 16-ohm impedance. 15.95



**Model R-98 FM-AM Radio** — For those who prefer the convenience of a complete FM-AM radio, with *no sacrifice in quality*, the R-98 provides superb reception, free from interference of every kind—even in critical areas. Amazing sensitivity on FM and AM. Accurate and stable slide-rule tuning. 64.50



## BLONDER-TONGUE LABORATORIES

For complete details, write to Dept. RE-1

9 Alling Street, Newark 2, New Jersey

SUPERIOR'S NEW MODEL TW-11

STANDARD  
PROFESSIONAL

# TUBE TESTER



Model TW-11 — TUBE TESTER . . . Total Price \$47.50 — Terms: \$11.50 after 10 day trial, then \$6.00 per month for 6 months.

★ Tests all tubes, including 4, 5, 6, 7, Octal, Lock-in, Hearing Aid, Thyratron, Miniatures, Sub-miniatures, Novals, Sub-minars, Proximity fuse types, etc.

★ Uses the new self-cleaning Lever Action Switches for individual element testing. Because all elements are numbered according to pin-number in the RMA base numbering system, the user can instantly identify which element is under test. Tubes having tapped filaments and tubes with filaments terminating in more than one pin are truly tested with the Model TW-11 as any of the pins may be placed in the neutral position when necessary.

★ The Model TW-11 does not use any combination type sockets. Instead individual sockets are used for each type of tube. Thus it is impossible to damage a tube by inserting it in the wrong socket.

★ Free-moving built-in roll chart provides complete data for all tubes. All tube listings printed in large easy-to-read type.

★ NOISE TEST: Phono-jack on front panel for plugging in either phones or external amplifier will detect microphonic tubes or noise due to faulty elements and loose internal connections.

### EXTRAORDINARY FEATURE

SEPARATE SCALE FOR LOW-CURRENT TUBES. Previously, on emission-type tube testers, it has been standard practice to use one scale for all tubes. As a result, the calibration for low-current types has been restricted to a small portion of the scale. The extra scale used here greatly simplifies testing of low-current types.

The Model TW-11 operates on 105-130 Volt 60 Cycles A.C. Comes housed in a beautiful hand-rubbed oak cabinet complete with portable cover.

**\$47<sup>50</sup>**  
NET

SUPERIOR'S NEW MODEL 82



Model 82 — TUBE TESTER . . . Total Price \$36.50 — Terms: \$6.50 after 10 day trial, then \$6.00 monthly for 5 months.

Multi-Socket Type

# TUBE TESTER

**TEST ANY TUBE IN 10 SECONDS FLAT!**

- 1 Turn the filament selector switch to position specified.
- 2 Insert tube into a numbered socket as designated on our chart (over 600 types included).
- 3 Press down the quality button —

**THAT'S ALL!** Read emission quality direct on bad-good meter scale.

Primarily, the difference between the conventional tube tester and the multi-socket type is that in the latter, the use of an added number of specific sockets (for example, in Model 82 the noval is duplicated eight times) permits elimination of element switches thus reducing testing time and possibility of incorrect switch readings.

To test any tube, you simply insert it into a numbered socket as designated, turn the filament switch and press down the quality switch—THAT'S ALL! Read quality on meter. Inter-element leakage, if any indicates automatically.

Production of this Model was delayed a full year pending careful study by Superior's engineering staff of this new method of testing tubes. Don't let the low price mislead you! We claim Model 82 will outperform similar looking units which sell for much more — and as proof, we offer to ship it on our examine before you buy policy.

- Tests over 600 tube types.
- Tests OZ4 and other gas-filled tubes.
- Employs new 4" meter with sealed air-damping chamber resulting in accurate vibrationless readings.
- Use of 22 sockets permits testing all popular tube types and prevents possible obsolescence.
- Dual Scale meter permits testing of low current tubes.
- 7 and 9 pin straighteners mounted on panel.
- All sections of multi-element tubes tested simultaneously.
- Ultra-sensitive leakage test circuit will indicate leakage up to 5 megohms.

Model 82 comes complete, housed in portable, hand-rubbed oak cabinet with removable cover. Only

**\$36<sup>50</sup>**  
NET

**SHIPPED ON APPROVAL**  
**NO MONEY WITH ORDER — NO C.O.D.**

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — **NO INTEREST OR FINANCE CHARGES ADDED.** If not completely satisfied, return to us, no explanation necessary.

SEE PAGE 97 FOR COMPLETE DETAILS

MOSS ELECTRONIC, INC.

3849 TENTH AVE., NEW YORK 34, N. Y.

SUPERIOR'S  
NEW MODEL 83

# C.R.T. TESTER

**Tests and Rejuvenates ALL PICTURE TUBES**

**ALL BLACK AND WHITE TUBES**

From 50 degree to 110 degree types—from 8" to 30" types.

**ALL COLOR TUBES**



**Model 83 — C.R.T. TUBE TESTER . . .**  
Total Price \$38.50 — Terms: \$8.50  
after 10 day trial, then \$6.00 monthly  
for 5 months.

Model 83 comes housed in handsome portable Saddle Stitched Texon case—complete with sockets for all black and white tubes and all color tubes. Only

**\$38.50**

Test ALL picture tubes—in the carton—out of the carton—in the set!

- ✓ Model 83 is not simply a rehashed black and white C.R.T. Tester with a color adapter added. Model 83 employs a new improved circuit designed specifically to test the older type black and white tubes, the newer type black and white tubes and all color picture tubes.
- ✓ Model 83 provides separate filament operating voltages for the older 6.3 types and the newer 8.4 types.
- ✓ Model 83 employs a 4" air-damped meter with quality and calibrated scales.
- ✓ Model 83 properly tests the red, green and blue sections of color tubes individually—for each section of a color tube contains its own filament, plate, grid and cathode.
- ✓ Model 83 will detect tubes which are apparently good but require rejuvenation. Such tubes will provide a picture seemingly good but lacking in proper definition, contrast and focus. To test for such malfunction, you simply press the rej. switch of Model 83. If the tube is weakening, the meter reading will indicate the condition.

Rejuvenation of picture tubes is not simply a matter of applying a high voltage to the filament. Such voltages improperly applied can strip the cathode of the oxide coating essential for proper emission. The Model 83 applies a selective low voltage uniformly to assure increased life with no danger of cathode damage.

SUPERIOR'S NEW  
MODEL TV-12

# TRANS-CONDUCTANCE TUBE TESTER



**Model TV-12—TUBE TESTER . . . Total**  
Price \$72.50 — Terms: \$22.50 after 10  
day trial, then \$10.00 monthly for 5  
months.

**ALSO TESTS  
TRANSISTORS!**

## TESTING TUBES

- ★ Employs improved TRANS-CONDUCTANCE circuit. An in-phase signal is impressed on the input section of a tube and the resultant plate current change is measured. This provides the most suitable method of simulating the manner in which tubes actually operate in Radio & TV receivers, amplifiers and other circuits. Amplification factor, plate resistance and cathode emission are all correlated in one meter reading.
- ★ NEW LINE VOLTAGE ADJUSTING SYSTEM. A tapped transformer makes it possible to compensate for line voltage variations to a tolerance of better than 2%.
- ★ SAFETY BUTTON — protects both the tube under test and the instrument meter against damage due to overload or other form of improper switching.
- ★ NEWLY DESIGNED FIVE POSITION LEVER SWITCH ASSEMBLY. Permits application of separate voltages as required for both plate and grid of tube under test, resulting in improved Trans-Conductance circuit.

## TESTING TRANSISTORS

A transistor can be safely and adequately tested only under dynamic conditions. The Model TV-12 will test all transistors in that approved manner, and quality is read directly on a special "transistor only" meter scale.

The Model TV-12 will accommodate all transistors including NPN's, PNP's, Photo and Tetrodes, whether made of Germanium or Silicon, either point contact or junction contact types.

Model TV-12 housed in handsome rugged portable cabinet sells for only

**\$72.50**  
NET

**SHIPPED ON APPROVAL**  
**NO MONEY WITH ORDER — NO C.O.D.**

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — **NO INTEREST OR FINANCE CHARGES ADDED.** If not completely satisfied, return to us, no explanation necessary.

SEE PAGE 97 FOR COMPLETE DETAILS

MOSS ELECTRONIC, INC.

3849 TENTH AVE., NEW YORK 34, N. Y.

SUPERIOR'S NEW MODEL 77

# VACUUM TUBE VOLTMETER

WITH NEW 6" FULL-VIEW METER



Model 77 — VACUUM TUBE VOLT-METER... Total Price \$42.50 — Terms: \$12.50 after 10 day trial, then \$6.00 monthly for 5 months.

Compare it to any peak-to-peak V. T. V. M. made by any other manufacturer at any price!

- ✓ Model 77 completely wired and calibrated with accessories (including probe, test leads and portable carrying case) sells for only \$42.50.
- ✓ Model 77 employs a sensitive six inch meter. Extra large meter scale enables us to print all calibrations in large easy-to-read type.
- ✓ Model 77 uses new improved SICO printed circuitry.
- ✓ Model 77 employs a 12AU7 as D.C. amplifier and two 9006's as peak-to-peak voltage rectifiers to assure maximum stability.
- ✓ Model 77 uses a selenium-rectified power supply resulting in less heat and thus reducing possibil-

ity of damage or value changes of delicate components.

- ✓ Model 77 meter is virtually burn-out proof. The sensitive 400 microampere meter is isolated from the measuring circuit by a balanced push-pull amplifier.
- ✓ Model 77 uses selected 1% zero temperature coefficient resistors as multipliers. This assures unchanging accurate readings on all ranges.

**SPECIFICATIONS**

• DC VOLTS — 0 to 3/15/75/150/300/750/1,500 volts at 11 megohms input resistance. • AC VOLTS (RMS) — 0 to 3/15/75/150/300/750/1,500 volts. • AC VOLTS (Peak to Peak) — 0 to 8/40/200/400/800/2,000 volts. • ELECTRONIC OHMMETER — 0 to 1,000 ohms/10,000 ohms/100,000 ohms/1 megohm/10 megohms/100 megohms/1,000 megohms. • DECIBELS — 10 db to +18 db, +10 db to +38 db, +30 db to +58 db. All based on 0 db = .006 watts (6 mw) into a 500 ohm line (1.73v). • ZERO CENTER METER — For discriminator alignment with full scale range of 0 to 1.5/7.5/37.5/75/150/375/750 volts at 11 megohms input resistance.

AS A DC VOLTMETER: The Model 77 is indispensable in Hi-Fi Amplifier servicing and a must for Black and White and color TV Receiver servicing where circuit loading cannot be tolerated.

AS AN AC VOLTMETER: Measures RMS values of sine wave, and peak-to-peak value of complex wave. Pedestal voltages that determine the "black" level in TV receivers are easily read.

AS AN ELECTRONIC OHMMETER: Because of its wide range of measurement leaky capacitors show up glaringly. Because of its sensitivity and low loading, intermittents are easily found, isolated and repaired.

Model 77 comes complete with operating instructions, probe and test leads. Use it on the bench—use it on calls. A streamlined carrying case, included at no extra charge, accommodates the tester, instruction book, probe and leads. Operates on 110-120 volt 60 cycle. Only

**\$42<sup>50</sup>**  
**NET**


SUPERIOR'S NEW MODEL 79

# SUPER-METER — WITH NEW 6" FULL-VIEW METER

A Combination VOLT-OHM MILLIAMMETER.

Plus CAPACITY, REACTANCE, INDUCTANCE AND DECIBEL MEASUREMENTS.

Also Tests SELENIUM AND SILICON RECTIFIERS, SILICON AND GERMANIUM DIODES.

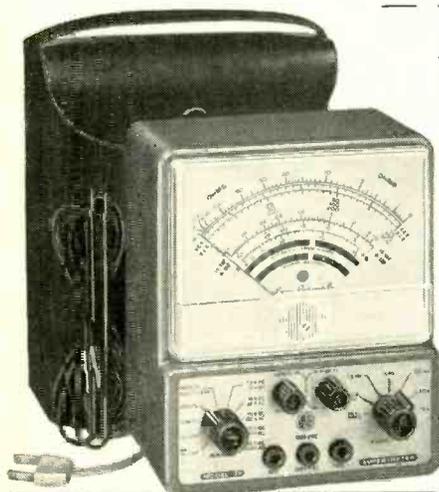

Model 79 — SUPER-METER... Total Price \$38.50 — Terms: \$8.50 after 10 day trial, then \$6.00 per month for 5 months.

The Model 79 represents 20 years of continuous experience in the design and production of SUPER-METERS, an exclusive SICO development.

In 1938 Superior Instruments Co. designed its first SUPER-METER, Model 1150. In 1940 it followed with Model 1250 and in succeeding years with others including Models 670 and 670-A. All were basically V.O.M.'s with extra services provided to meet changing requirements.

Now, Model 79, the latest SUPER-METER includes not only every circuit improvement perfected in 20 years of specialization, but in addition includes those services which are "musts" for properly servicing the ever increasing number of new components used in all phases of today's electronic production. For example with the Model 79 SUPER-METER you can measure the quality of selenium and silicon rectifiers and all types of diodes—components which have come into common use only within the past five years, and because this latest SUPER-METER necessarily required extra meter scale, SICO used its new full-view 6-inch meter.

Model 79 comes complete with operating instructions and test leads. Use it on the bench—use it on calls. A streamlined carrying case included at no extra charge accommodates the tester, instruction book and test leads.....Only

*Specifications*

D.C. VOLTS: 0 to 7.5/15/75/150/750/1,500.  
A.C. VOLTS: 0 to 15/30/150/300/1,500/3,000.  
D.C. CURRENT: 0 to 1.5/15/150 Ma. 0 to 1.5/15 Amperes.  
RESISTANCE: 0 to 1,000/100,000 Ohms. 0 to 10 Megohms.  
CAPACITY: 001 to 1 Mfd. 1 to 50 Mfd.  
REACTANCE: 50 to 2,500 Ohms, 2,500 Ohms to 2.5 Megohms.  
INDUCTANCE: .15 to 7 Henries, 7 to 7,000 Henries.  
DECIBELS: -6 to +18, +14 to +38, +34 to +58.

The following components are all tested for QUALITY at appropriate test potentials. Two separate BAD-GOOD scales on the meter are used for direct readings.

All Electrolytic Condensers from 1 MFD to 1000 MFD.  
All Selenium Rectifiers. All Germanium Diodes.  
All Silicon Rectifiers. All Silicon Diodes.

**\$38<sup>50</sup>**  
**NET**

**SHIPPED ON APPROVAL**  
**NO MONEY WITH ORDER — NO C.O.D.**

Try for 10 days before you buy! If completely satisfied, send down payment after trial and pay balance at indicated monthly rate — **NO INTEREST OR FINANCE CHARGES ADDED.** If not completely satisfied, return to us, no explanation necessary.

See following page for complete details

**MOSS ELECTRONIC, INC.**

**3849 TENTH AVE., NEW YORK 34, N. Y.**

**SUPERIOR'S NEW MODEL TV-50A GENOMETER**



**Model TV-50A GENOMETER . . . Total Price \$47.50 — Terms: \$11.50 after 10 day trial, then \$6.00 monthly for 6 months.**

**7 Signal Generators in One!**

- ✓ R.F. Signal Generator for A.M.
- ✓ R.F. Signal Generator for F.M.
- ✓ Audio Frequency Generator
- ✓ Bar Generator
- ✓ Cross Hatch Generator
- ✓ Color Dot Pattern Generator
- ✓ Marker Generator

**A versatile all-inclusive GENERATOR which provides ALL the outputs for servicing: A.M. Radio • F.M. Radio • Amplifiers • Black and White TV • Color TV**

*Specifications*

**R. F. SIGNAL GENERATOR:** The Model TV-50A Genometer provides complete coverage for A.M. and F.M. alignment. Generates Radio Frequencies from 100 Kilocycles to 60 Megacycles on fundamentals and from 60 Megacycles to 180 Megacycles on powerful harmonics.

**VARIABLE AUDIO FREQUENCY GENERATOR:** In addition to a fixed 400 cycle sine-wave audio, the Model TV-50A Genometer provides a variable 300 cycle to 20,000 cycle peaked wave audio signal.

The Model TV-50A comes complete with shielded leads and operating instructions. Only

**BAR GENERATOR:** The Model TV-50A projects an actual Bar Pattern on any TV Receiver Screen. Pattern will consist of 4 to 16 horizontal bars or 7 to 20 vertical bars.

**CROSS HATCH GENERATOR:** The Model TV-50A Genometer will project a cross-hatch pattern on any TV picture tube. The pattern will consist of non-shifting, horizontal and vertical lines interlaced to provide a stable cross-hatch effect.

**DOT PATTERN GENERATOR (FOR COLOR TV):** Although you will be able to use most of your regular standard equipment for servicing Color TV, the one addition which is a "must" is a Dot Pattern Generator. The Dot Pattern projected on any color TV Receiver tube by the Model TV-50A will enable you to adjust for proper color convergence.

**MARKER GENERATOR:** The Model TV-50A includes all the most frequently needed marker points. The following markers are provided: 189 Kc., 262.5 Kc., 456 Kc., 600 Kc., 1000 Kc., 1400 Kc., 1600 Kc., 2000 Kc., 2500 Kc., 3579 Kc., 4.5 Mc., 5 Mc., 10.7 Mc., (3579 Kc. is the color burst frequency).

**\$47.50 NET**

**For the first time ever: ONE TESTER PROVIDES ALL THE SERVICES LISTED BELOW!**

**SUPERIOR'S NEW MODEL 76**

**ALL PURPOSE BRIDGE**



**Model 76 . . . Total Price \$26.95 — Terms: \$6.95 after 10 day trial, then \$5.00 monthly for 4 months.**

**IT'S A CONDENSER BRIDGE**

with a range of .00001 Microfarad to 1000 Microfarads (Measures power factor and leakage too.)

**IT'S A SIGNAL TRACER**

which will enable you to trace the signal from antenna to speaker of all receivers and to finally pinpoint the exact cause of trouble whether it be a part or circuit defect.

**CAPACITY BRIDGE SECTION**

4 Ranges: .00001 Microfarad to 1000 Microfarads. Will also locate shorts and leakages up to 20 megohms. Measures the power factor of all condensers from .1 to 1000 Microfarads. (Power factor is the ability of a condenser to retain a charge and thereby filter efficiently.)

**SIGNAL TRACER SECTION**

With the use of the R.F. and A.F. Probes included with the Model 76, you can make stage gain measurements, locate signal loss in R.F. and Audio stages, localize faulty stages, locate distortion and hum, etc. Provision has been made for use of phones and meter if desired.

Model 76 comes complete with all accessories including R.F. and A.F. Probes; Test Leads and operating instructions. Nothing else to buy. Only

**IT'S A RESISTANCE BRIDGE**

with a range of 100 ohms to 5 megohms

**IT'S A TV ANTENNA TESTER**

The TV Antenna Tester section is used first to determine if a "break" exists in the TV antenna and if a break does exist the specific point (in feet from set) where it is.

**RESISTANCE BRIDGE SECTION**

2 Ranges: 100 ohms to 5 megohms. Resistance can be measured without disconnecting capacitor connected across it. (Except, of course, when the R C combination is part of an R C bank.)

**TV ANTENNA TESTER SECTION**

Loss of sync, snow and instability are only a few of the faults which may be due to a break in the antenna, so why not check the TV antenna first? 2 Ranges: 2' to 200' for 72 ohm coax and 2' to 250' for 300 ohm ribbon.

**\$26.95 NET**

**SHIPPED ON APPROVAL NO MONEY WITH ORDER — NO C. O. D.**


MOSS ELECTRONIC, INC.  
Dept. D-556 3849 Tenth Ave., New York 34, N. Y.

Please send me the units checked on approval. If completely satisfied I will pay on the terms specified with no interest or finance charges added. Otherwise, I will return after a 10 day trial positively cancelling all further obligation.


Name .....  
Address .....  
City ..... Zone ..... State.....  
All prices net. F.O.B., N. Y. C.

- Model TW-11 ..... Total Price \$47.50  
\$11.50 within 10 days. Balance \$6.00 monthly for 6 months.
- Model 82 ..... Total Price \$36.50  
\$6.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Model 83 ..... Total Price \$38.50  
\$8.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Model TV-12 ..... Total Price \$72.50  
\$22.50 within 10 days. Balance \$10.00 monthly for 5 months.
- Model 77 ..... Total Price \$42.50  
\$12.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Model 79 ..... Total Price \$38.50  
\$8.50 within 10 days. Balance \$6.00 monthly for 5 months.
- Model TV-50A ..... Total Price \$47.50  
\$11.50 within 10 days. Balance \$6.00 monthly for 6 months.
- Model 76 ..... Total Price \$26.95  
\$6.95 within 10 days. Balance \$5.00 monthly for 4 months.

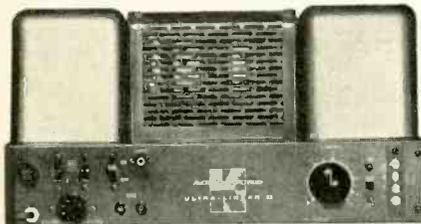
From  
any Point of View,  
more Experts choose  
**ACROSOUND**  
ULTRA-LINEAR II  
60 watt amplifier



**DESIGN** The combination of patented ULTRA-LINEAR circuitry—plus new HYBRID FEEDBACK principle—VARIABLE DAMPING control, and ULTRA STABILITY, represents a new high in the art of amplifier design... an example of ACROSOUND'S latest achievement in AMERICAN Know-How. This superiority of design now enables anyone with or without any previous knowledge of electronics to assemble for himself or herself... (yes! it's that easy!)... the finest of amplifiers and at a most reasonable cost, in only two hours!

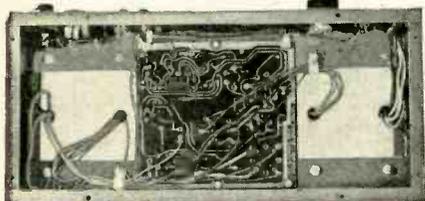

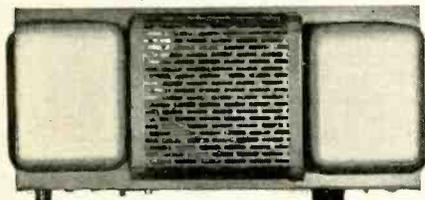**PERFORMANCE** By listening test, or by Instruments... second to none in clarity and frequency response. Normal level distortion is virtually unmeasurable—IM 1% or less at 60 watts, 120 watts peak. Completely stable... unaffected by loads, perfect square waves.



**QUALITY** Every part going into the assembly of critical and even non-critical circuitry is tested and checked to allow no more than  $\pm 1/2\%$  variation from ACROSOUND'S standards. Specialized test equipment unavailable commercially was designed in ACROSOUND'S laboratories to achieve this result. Every printed circuit board is placed in trial operation on a laboratory amplifier. Output tubes are matched by trial and double checked.



**COMPONENTS** ACRO'S newest TO-600 output transformer with special hybrid winding—separates functions of output circuit and feedback circuit. Heavy duty, completely assembled, and thoroughly tested, printed circuit board assures uniformity of performance. Low distortion EL34 output tubes are operated well within their ratings ensuring long tube life and optimum performance.

**PRICE** In preassembled kit form so that you may save money, learn while doing, and have the proud satisfaction you built the best for only \$79.50 net... or if you feel you would prefer it laboratory assembled it still represents a bargain at \$109.50 net.

**HEAR IT AT YOUR DEALER NOW!**

**BE READY FOR ACROSOUND DISTORTIONLESS PRE-AMP DESIGNED FOR THE STEREO-PHILE**

*Experts know why ACRO is best!  
Others... Learn why! Write to*

**ACRO PRODUCTS**  
369 SHURS LANE  
PHILA. 28. PA.

TELEVISION

tv dx in '58

By ROBERT B. COOPER, JR.

**T**HIS year, more than 900 completed TV dx report forms were returned to RADIO-ELECTRONICS.

On these reports are more than 15,500 dx loggings, including 507 television stations in 48 states and 13 countries. Reports arriving on unofficial report forms accounted for an additional 4,000-plus loggings which still have to be tabulated. The number of individual reports reached an all-time high.

From the preliminary accounting of the dx reports, several definite patterns appear for 1958. Sporadic E-skip openings were fewer in number, shorter in duration and smaller in scope than in the preceding 4 years. E skip bunched for the most part in the last 2 weeks of the two big skip months, June and July. No single area seemed to benefit more than others from E-skip openings, although the East and Midwest saw their greatest concentration of Es work during late July and early August, while the Western states got theirs in late June and early July.

One major point stands out in the reports. Percentage-wise, a much greater portion than in past years of the openings noted affected only channel 2 or 3. Skip was just not reaching as high in the TV channels as in 1956 or '57. This is important to FM dxers, who must bide their time until the TV band opens into channel 6 before they can begin to "hear" any E skip. Supporting our observations, Bruce Elving, reporting from Duluth, Minn., heard just one case of E skip on the FM band all summer, and this was noted on the late date of Aug. 30.

Tropospheric conditions conducive to "super dx" (ground wave beyond 500 miles) formed only occasionally during the entire year. The usual good months of June, July and August did provide a few good openings but tropospheric loggings in excess of 500 miles number

less than 75 for the entire season.

Tropospheric openings also fell into well-defined patterns during the year. Dx which traveled along an east-west path between transmitter and receiver was strictly a June-July phenomenon, as the warm air masses followed hot dry zones eastward from the western plains of Canada.


During August and September, the moist warm-air masses moved from the Gulf of Mexico into the eastern half of the country. This south-to-northeast air movement produced good tropospheric conditions along the Atlantic Coast and, often as not, well inland to the Mississippi River. As these humid masses of air moved into our populous Northeast, tropospheric conditions over north-south paths improved markedly.

One of the better periods for north-south tropospheric dx reported by many observers was the early morning hours of Aug. 31. John Cody of Middletown, Conn., found conditions from the Eastern seaboard very good as the local stations leaft the air. Digging into the snow barrier, he found WRAL-TV channel 5, Raleigh, N. C., 517 miles; WITN, channel 7, Washington, N. C., 480 miles; WNCT, channel 9, Greenville, N. C., 490 miles; WTVB, channel 11, Durham, N. C., 520 miles, and WLVA, channel 13, Lynchburg, Va., 450 miles, among a dozen more in the 250-400-mile range. Melvyn Sulzburgh of Philadelphia found the same period interesting when he intercepted WECT, channel 6, Wilmington, N. C., 420 miles, following the local channel 6 signoff.

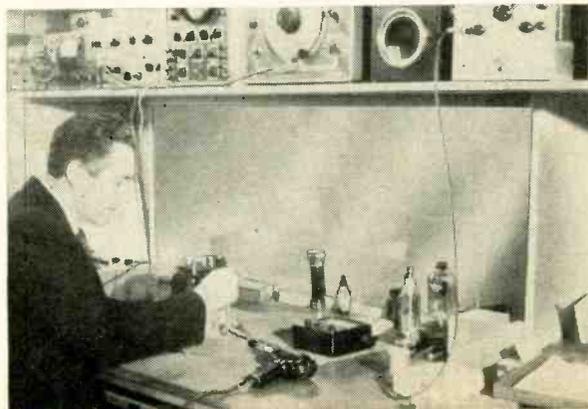
**Auroral tropics?**

For some time I have believed that there is a definite relationship between auroral displays (and the resulting aurora-E reflections of TV signals) and improved ground-wave conditions in the Great Lakes region. Time and time again, we have witnessed an apparent

In his workshop, Stan Hosken adjusts the noise figure of a push-pull cascade booster used with his antenna array.



## TELEVISION

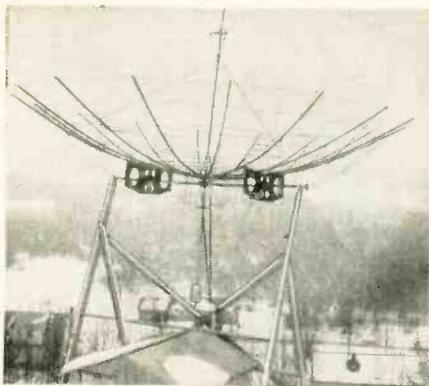

One enterprising dxer, Stan Hosken of North Bay, Ontario, uses this 30-foot parabolic antenna. Changing the resonant dipoles lets him use the dish for any frequency from 40 to 1,000 mc.

correlation between these two decidedly different forms of signal propagation. Past reports hinting at a connection between the two were quite local in nature, usually involving one or two observers reporting dx suddenly picking up in a single direction and ending just as abruptly following a 2 to 3-hour auroral session.

This fall's big aurora came on Sept. 4, with visual displays seen into central Florida. Carl Boecher of Milwaukee, Wis., found the TV channels fairly jumping with hazy sliding lines, indicative of Northern Lights activity, at 2310 hours. From 2330 to 0005 hours on the 5th he discovered excellent quality signals from CFPL-TV, channel 10, London, Ont., 375 miles; CHCH-TV, channel 11, Hamilton, Ont., 450 miles; WWJ-TV, channel 4, WJBK-TV, channel 2, 300 miles, and WXYZ-TV, channel 7, all from Detroit, Mich. These tropospheric signals had not been present prior to the auroral-TV display.

### No South Americans

This year was the first in several that we haven't received at least one report of reception of our Latin American neighbors south of Mexico City. Stations in El Salvador, Guatemala, Venezuela, Brazil and other South American countries did not appear a single time in the 15,500 tabulated dx loggings. One rare one did show up, however, when James Abercrombie of Columbia, S. C., caught HIT-TV, channel 2 from the Dominican Republic, on Aug. 12.


Cuban stations continued to forge toward the top of the list, with eastern dxers in the Middle Atlantic states seeing them most often. However, there are still some dxers who fail to recognize them for what they are. Cuban stations usually belong to one of two networks, and the networks use as their station break insignia the call letters assigned to the network origination station. Thus the CMQ network with its headquarters station in Havana (on channel 6) may show the call CMQ on many other channels. On the other hand, Telemundo (Cuba's second network) alternates its call slide with the

*whether your plans are modest  
or unlimited...*


you can  
build  
your ideal  
stereo system  
with the  
finest  
loudspeakers...



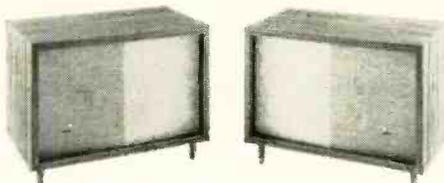Compact, proportioned for bookshelf or table top, JBL Bel-Aires—a pair with components in mirror-image arrangement—will give you the clean, exquisitely detailed stereo reproduction that can only be achieved with transducers of the highest precision.



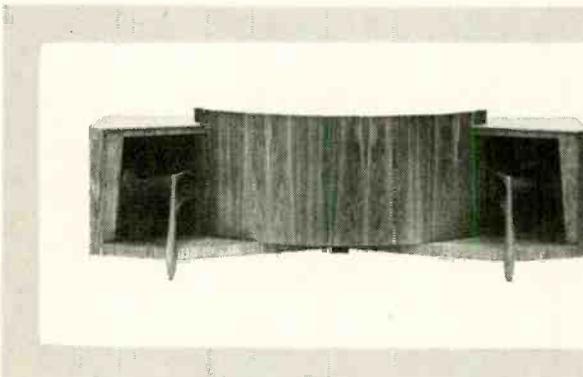Now JBL enclosures are matched for stereo. If you own a JBL C34, C35, C37, C39, or C40, you can add a matching enclosure with speaker units arranged in a pattern that is a mirror image of your present system.



The JBL Ranger-Paragon is the ultimate stereo speaker system. Developed as a master monitor for use in perfecting stereo recording techniques, the Paragon adds to twin folded horns and professional driver units a radial refraction panel which integrates the two sound sources and disperses true stereo throughout the room.



The JBL Ranger-Metregon incorporates the virtues of radial refraction in an enclosure of acceptable size for the average living room. No hole in the middle, no split soloists, but sound reproduction spatially proportional to its original source. The Metregon accepts seven different speaker system combinations; can be upgraded progressively.

Write for free catalog and data sheets.

**JAMES B. LANSING SOUND, INC.**

3249 casitas avenue, los angeles 39, california





It's smart to get the BEST and keep the rest of your PROFITS! . . . with EMC TEST EQUIPMENT . . . the finest quality line of precision instruments at the lowest possible prices.



**Model 102 Volometer**  
Features a 3½", 2% accurate—800 microamperes O'arsonval-type plastic front meter with 3 AC current ranges; and the same zero adjustment for both resistance ranges. Specifications . . . AC Voltage—5 Ranges: 0 to 12-120-600-1200-3000 volts. DC Voltage—5 Ranges: 0 to 6-50-300-600-3000 volts. AC Current—3 Ranges: 0 to 30-150-600 ma. DC Current—4 Ranges: 0 to 6-30-130 ma. 0 to 1.2 amps. Two Resistance Ranges: 0 to 1000 ohms, 0 to 1 megohms. Model 102, Wt. 1 lb. 5 oz. Size: 3¼" x 6¼" x 2". \$14.90; Kit, \$12.50.

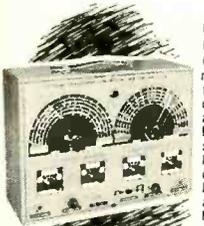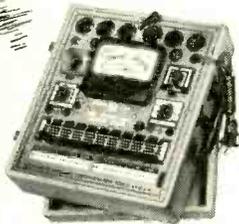**Model 204 Tube-Battery-Ohm Capacity Tester**


Emission tube tester. Completely flexible switching arrangement. Checks batteries under rated load on "reject-good" scale. Checks condenser leakage to 1 meg. Checks resistance up to 4 megs. Checks capacity from .01 to 1 mfd. Model 204P, illustrated, \$55.90. Model DRA, Cathode ray tube adaptor, \$4.50.



**Model 700 RF-AF Crystal Marker TV Bar-Generator**  
Complete coverage from 18 cycles to 108 megacycles on fundamentals. Bar generator for TV adjustment with a variable number of bars available for horizontal or vertical alignment. Square wave generator to 20 kilocycles. Wien Bridge AF oscillator with sine wave output from 18 cycles to 300 kilocycles. Crystal marker and amplitude control. Individually tuned coils. Constant RF output impedance. Stepped RF attenuator. Variable percentage of modulation. Model 700 . . . \$55.90.

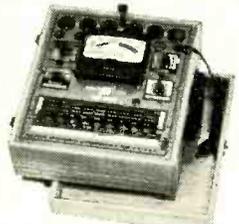**Model 205 Tube Tester**

Uses standard emission test. Tests all tubes including Novel and sub-miniatures. Completely flexible switching arrangement. Checks for shorts, leakages and opens. Model 205P, Hand rubbed oak carrying case, \$47.50 (illustrated); Kit, \$36.20. Model DRA, Cathode ray tube adaptor, \$4.50.



**Model 104 Volometer**  
Features a 4½", 50 microampere meter, with 3 AC current ranges and 3 resistance ranges to 20 megohms. Specifications . . . DC Voltage: 5 ranges (20-200 ohms per volt); 0 to 6-50-300-600-3000 volts. AC Voltage: 5 ranges (1,000 ohms per volt); 0 to 6-50-300-600-3000 volts. DC Current—3 Ranges: 0 to 6-60-600 ma. AC Current—3 Ranges: 0 to 30-300 ma. 0 to 3 amps. 3 Resistance Ranges: 0 to 20K, 0 to 200K, 0 to 20 megs. 5 DB Ranges: —4 to —67 DB. Model 104, with carrying strap, Wt. 2 lbs. 5 oz. Size: 5¼" x 6¾" x 2¼". \$26.95; Kit, \$19.95. Model HVT, 30,000 volt probe for Model 104, \$7.95.

**TELEVISION**

individual station call letters. So there is only one rule of thumb to follow: Call letters which begin with CM are definitely from Cuba.

While we are out of the United States and in Southern waters, two more reports of special interest come to light. Enrique Veazey reports from Ciudad del Carmen, a small island in the southwestern corner of the Gulf of Mexico. Using a 17-inch Herald receiver and a 32-element stacked array, he views with absolute regularity reception from sta-



State hunters all over the US regard this one essential to their totals. KID-TV, channel 3, Idaho Falls, Idaho, as seen by B. J. Bingham, Festus, Mo.

tions all along the Gulf coast of Texas. Nothing unusual about all of this, except . . . these stations are 700 to 800 miles away! Oh yes, can anyone help him get rid of the snow which appears in the picture each evening between 1600 and 1900 hours?

Although Arnaloo Coro, Jr. of Havana doesn't have as regular results with dx across the Gulf as Enrique Veazey, he does note with some pride signals from KTRK-TV, channel 13, Houston, Tex., some 950 miles to the west, during the month of April. Many other high- and low-band stations in Louisiana, Alabama and Florida were also logged with great frequency during the spring months.

Still outside the country, but now to the north, Ross Harvey of Goose Bay, Labrador, found that TV dx holds thrills for isolated fans as well as those surrounded by TV stations. Ross even goes so far as to state, "I am not ashamed to say it's more fun to TV dx than to ham!" Ross' broad-banded low-band Yagi brought him some 30 dx stations by mid-July, including KTWO-TV, channel 2, Casper, Wyo., a nice haul in any log.


**Uhf dx**

Uhfers (TV dxers with more than the average interest in uhf dx) increased during the year, possibly due to the poor Es season, allowing more time to keep an eye on the uhf band. John T. Sowders, Jr. of Richmond, Ky., has 24 uhf stations to his credit with 21 of these more than 175 miles distant. Two (WXIX, channel 19, Milwaukee; WTVO, channel 13, Rockford, Ill.) are beyond the 400-mile mark.

Roderick Luoma of Detroit finds that three very strong locals can crimp your style on the vhf spectrum, so he concentrates his efforts on the uhf chan-

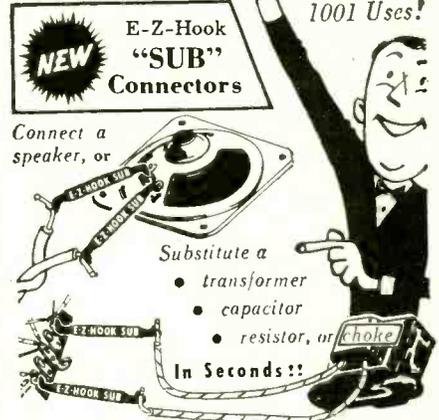**SUBSTITUTE PARTS WITH-OUT SOLDERING**

Quickly with E-Z-Hook "SUB" Connectors Easily Has 1001 Uses!



- ★ Makes connections instantly!
  - ★ Won't pull off!
  - ★ Insures positive contact!
- Saves time, money and parts in servicing, experimenting, instructing and production.

**E-Z-HOOK SUB**  
No. 71-1...SUB... Only 69¢ ea.  
Six Colors! - for Easy Lead Identification  
ORDER THROUGH YOUR PARTS DISTRIBUTOR  
**E-Z-HOOK TEST PRODUCTS**  
Dept. G-1, 1536 Woodburn Ave. Covington, Ky.

*Pure Riee's*  
**OFFICIAL ORDER BOOK**  
for every TV-Radio service call

Triplicate forms serve as order form, invoice and office record with spaces for complete information on every job. Separate listings for receiving tubes, pix tube, parts, serial numbers, labor and tax charges, signatures, etc. 75c a book, \$6.50 for dust-proof box of 10.



. . . and for customer's prices on every replacement part, plus flat rate and hourly service charge data, regional and national, Dave Riee's

**OFFICIAL PRICING DIGEST**  
listing over 63,000 items. \$2.50  
In stock at your distributor, or write  
**ELECTRONIC PUBLISHING CO. INC.**  
180 North Wacker Drive Chicago 6, Illinois


Yes, tell me more, send me FREE—a detailed catalog of the complete EMC line.

NAME \_\_\_\_\_  
STREET \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_

**EMC** Electronic Measurements Corp.  
625 B'way, New York 12, N. Y.  
Ex. Dept. RE-19, 431 Greenwich St., New York 13, N. Y.

*It's packed with career facts!*

**SEND FOR THIS  
FREE  
BOOKLET TODAY**

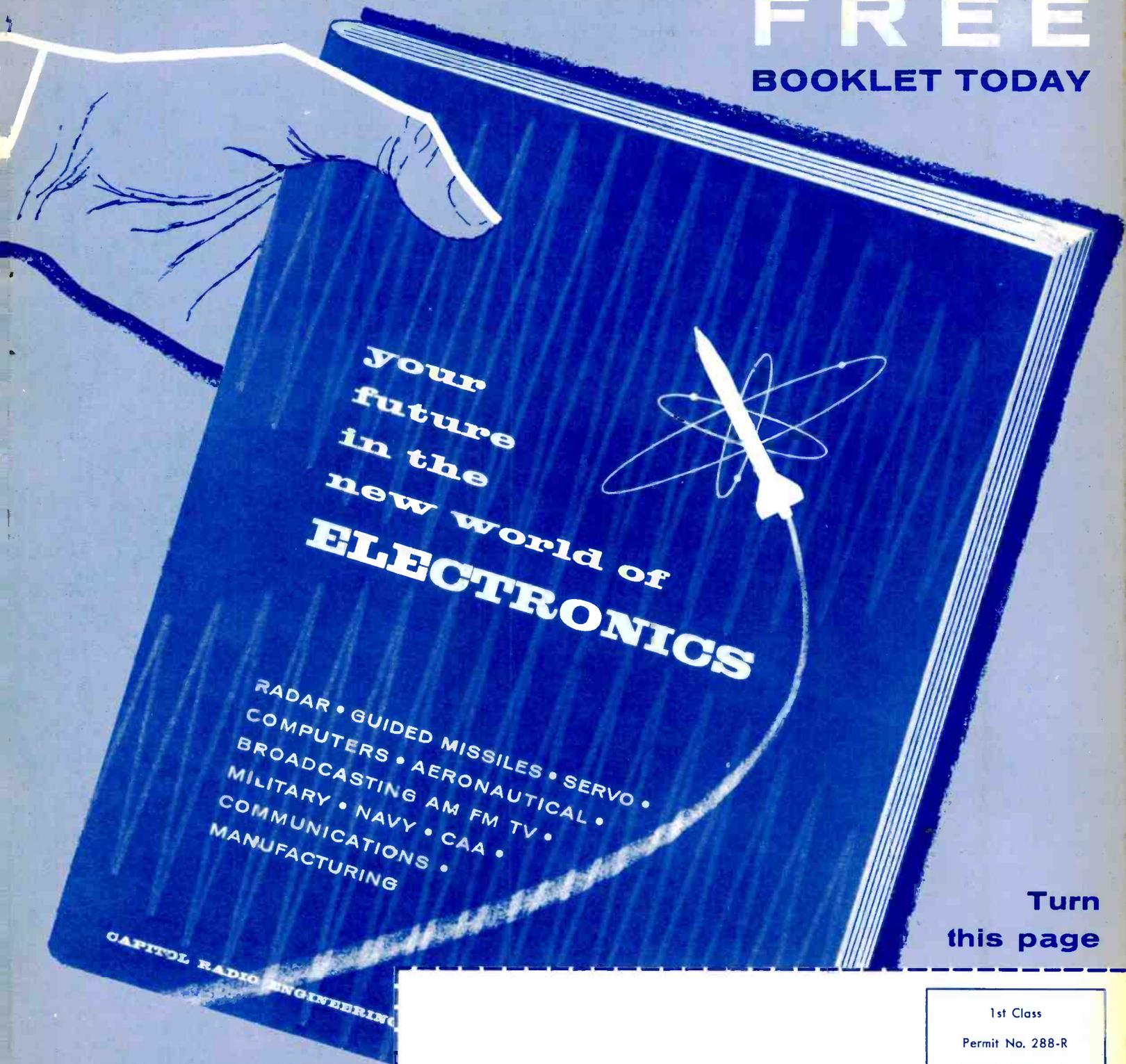

**Turn  
this page**

**See what  
the rapidly  
expanding  
field of  
ELECTRONICS  
offers you**

1st Class  
Permit No. 288-R  
Washington, D. C.

**BUSINESS REPLY CARD**  
*No Postage Stamp Necessary If Mailed in United States*

4¢ Postage Will Be Paid By



3224 SIXTEENTH STREET, N.W.  
WASHINGTON 10, D. C.




# IF JOBS LIKE THESE ARE "ON YOUR MIND"...

... but you can't qualify because you lack  
ADVANCED TECHNICAL KNOWLEDGE...
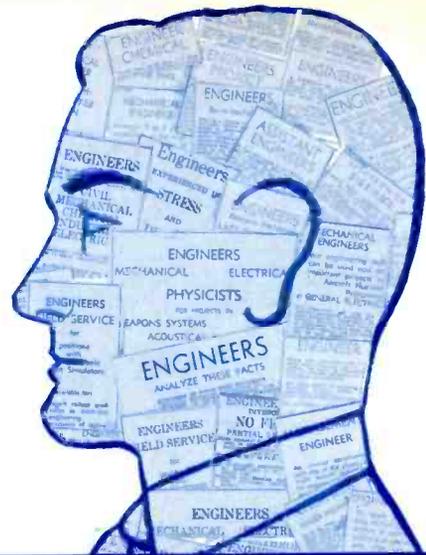
## SEND NOW FOR CREI'S NEW FREE BOOKLET

It's crammed with facts and data—containing a time-proved plan to make you ready for the big jobs and a high-salaried career now being offered in



### ELECTRONICS — TELEVISION — BROADCASTING — GUIDED MISSILES — INSTRUMENTATION RADAR — COMPUTERS — AUTOMATION — ASTRONAUTICS — SERVOMECHANISMS AERONAUTICAL ELECTRONICS — TELEMETERING — COMMUNICATIONS — MANUFACTURING

The want ads above are real ones... they appear almost daily in magazines and newspapers—all over the country. They show how desperately the electronics industry needs trained men. On the other hand, they give you a good idea of what opportunities await you—if you get advanced technical training now. And no wonder trained men are needed! Look what's happening in "astronautics," of which the earth satellite is just the most recent, but by no means ultimate example. Computers, Radar, Aeronautical electronics—all are booming—all need trained electronics men. Top manufacturers sold upwards of 13.5 billions of dollars worth of electronic equipment in 1957. By 1965 it's expected the radio-electronics industry will do about 22 billion dollars of business per year.

What do these figures mean to you? They mean that thousands of new electronic jobs have been added to the great, expanding field of electronics.

#### LITERALLY THOUSANDS ARE NEEDED!

You are needed—for development, research, design, production, testing, inspection, manufacture, broadcasting, telecasting, servicing. But you can qualify only if you take time to advance your knowledge... if you take 2 minutes right

now to write for the free CREI booklet, with no obligation.

#### SHORTEST DISTANCE TO A GOOD CAREER IS CREI TRAINING

If you follow the plan outlined in our free booklet, you will be in line for promotion and pay increases in short order. Read what these typical CREI graduates have to say:

"In this time of less than two years, I have almost doubled my salary and have gone from wire-man to engineering assistant and now to junior engineer. I have CREI to thank."—Frank A. Eckert, 22 Clover Lane, Levittown, Pa.

"I chose CREI training upon recommendation of two top engineers. Before I completed the course, I became transmitter chief of a 5 kw station. I am now employed as a technician at a 100 kw TV station and in spare time have a good TV sales and service business."—Arlie D. Patton, 203 Burke Ave., San Antonio, Tex.

By method, experience, and personnel—CREI is equipped to teach you what you will need when you translate your study into work. As proof that CREI knows what industry wants, many leading companies recommend CREI training for their own personnel. Among them: All American Cables and Radio, Inc.; Canadian Broadcasting Corporation; Columbia Broadcasting System; Gates Radio Company; Federal Electric Corp.; The Martin Company; Douglas Aircraft Co.; U. S. Information

Agency (Voice of America); Canadair Limited; Trans-Canada Air Lines; United Air Lines. Their choice of training for their own personnel is a good cue for your choice of a school.

#### TOP FIRMS LOOK FOR CREI MEN

A CREI diploma itself is ample proof to many leading companies that a man is worth hiring. Moreover, employers contact us regularly for graduates to fill good jobs. Our placement bureau maintains contact with industry, and cooperates with employers and graduates in making satisfactory placements. This free service is available to students, as well as graduates.

What do you want? To pass FCC exams? Start your own business? CREI has helped others reach these goals, and can help you. Or, do you want to go after good-paying electronics jobs, secure, permanent careers like those advertised above? *Whatever* your choice, CREI can help you as it has helped thousands of men—provided you have the ambition to follow the plan.

#### CREI ALSO OFFERS RESIDENCE TRAINING

CREI Residence School in Washington, D. C. offers training at same high technical level. Classes start at regular intervals. Qualified residence school graduates earn degree: "Associate in Applied Science." Check coupon if you prefer residence study, or Write: Capitol Radio Engineering Institute, 3224 16th St., N. W., Washington 10, D. C. You can qualify for CREI home study training if you have had electronic education, or experience in electronics—and realize the need of a high level technical knowledge to make good in the better electronic jobs. (Electronics experience is not required for admission to CREI Residence School.)

#### WAR VETERANS

If you are eligible for training under the new G.I. Bill of Rights, check the coupon for full information.

**BRAND NEW COURSE: AUTOMATION AND INDUSTRIAL ELECTRONICS ENGINEERING TECHNOLOGY.** Complete course, covers all phases of automation. Special emphasis on theory, functioning and applications of servomechanisms and computers. Also noteworthy: Lessons on machine control, instrumentation, data-processing and telemetry.

## FREE BOOKLET! MAIL THIS POSTAGE-FREE POST CARD TODAY

### CAPITOL RADIO ENGINEERING INSTITUTE

ECPD Accredited Technical Institute Curricula • Founded 1927

3224 16th St., N.W., Washington 10, D. C.

RG<sub>2</sub>

(R. E. Jan. 59)

Please send me your course outline and FREE illustrated Booklet "Your Future in the New World of Electronics"... describing opportunities and CREI home study courses in Electronic Engineering Technology.

- CHECK FIELD OF GREATEST INTEREST
- Radar, Servo and Computer Engineering Technology
  - Electronic Engineering Technology
  - Broadcast (AM, FM, TV) Engineering Technology
  - Television Engineering Technology
  - Aeronautical Electronic Engineering Technology
  - Automation and Industrial Electronics Engineering Technology

Name..... Age.....

Street.....

City..... Zone..... State.....

Check:  Home Study  Residence School  Korean Veteran

To help us answer your request intelligently, please give the following information:

EMPLOYED

BY.....

TYPE OF

PRESENT WORK.....

EDUCATION:

YEARS HIGH SCHOOL.....

OTHER.....

ELECTRONICS EXPERIENCE.....

## TELEVISION

nels. He finds that the uhf band is alive with dx much more often than most would think, especially during the summer months. Frequent reception in the 200 to 350-mile range is possible, if the observer is aware of the potentials.

### FM totals

Although a goodly number of dxers are reporting FM dx as part of their regular dxing activities, we do not feel that sufficient totals are in for a summary at this time. Therefore, will FM dxers with more than 50 FM stations to their credit please submit totals to this column for an early tabulation. Included in the summary will be: farthest dx received (with date and time), number of states received, number of stations received daily, total number of stations and a rundown on the equipment being used.

### Dxer extraordinaire

In the past years we have devoted this portion of the Annual TV dx review to the dxer who leads the pack with the greatest total number of stations. This year we will not.

As so much of the TV dxing group is interested in amassing huge station totals and extending dxing records, I wonder why we haven't had more "do-it-yourselfness" in the hobby. Erecting large antenna arrays, souping up receivers, installing ultra-low-loss feed lines are all readymade activities for the TV dx enthusiast. Unfortunately, few dxers seem to have any desire for anything more than a three-stage if 17-inch receiver of production-line design, and a single-bay all-channel Yagi.

One of the first exceptions to this rule that I encountered in 8 years of TV dxing is the subject for this year's review. Stan Hosken of North Bay, Ontario, has been experimenting with huge antenna arrays and souped-up receivers for 5 years. Prior to the installation of a local station in North Bay, Stan was developing a community antenna system, using sixteen 18-element Yagis, stacking 8 Yagis over 8, some 60 feet above ground. This 288-element array provided snow-free reception from Buffalo stations better than 95% of the time, over a 300-mile path.

When a local TV outlet spoiled his community distribution plans, Stan began work on a huge 30-foot parabola which rotates 360° horizontally, 180° vertically and is adjustable for operation at any point from 40 to 1,000 mc.

The array is mounted on an 8 x 8-foot building which rotates with the antenna. This building houses a portion of the receiving and testing equipment. The building is on a hill 400 feet above general terrain, in a very quiet residential location. All this makes for an excellent receiving setup, especially when used with the 288-element channel 4 array.

With the parabola, Stan is primarily interested in consistent reception from the nearest American stations, 300 to 400 miles away. At present, he is work-

# *dynakit*

*For the audio perfectionist!*

- **PRODUCTS WHICH EXCEL in DESIGN, in COMPONENT QUALITY, and in SOUND**
- **SUPERIOR for MONOPHONIC USE and FULLY COMPATIBLE With STEREOHONIC REQUIREMENTS**

## DYNAKIT MARK III



Mark III  
Mark III also available with added 70 volt output.  
Mark III-70 \$84.95\* net

- \* Ease of assembly due to uniquely simple circuitry and printed circuit construction with factory-mounted parts.
- \* Highest stability suitable for all loudspeaker systems including electrostatic.
- \* Dyna Biaset (patent pending) for simplified adjustment and complete freedom from effects of unbalanced components.
- \* Dynaco Super-Fidelity output transformer. This is the finest available transformer of its type for the most critical audio uses.
- \* 60 watts \$79.95\* net

MARK II 50 watts  
\$69.75\* net

## DYNAKIT PREAMPLIFIER

- \* Finest Quality Available of Circuitry and Components.
- \* Lowest Distortion and Noise.
- \* Easiest Assembly Using Pre-Assembled Printed Circuit.
- \* Handsome Styling — Selected for Display at Brussels World's Fair.
- \* Only \$34.95\* net.



Power supply available for 2 pre-amplifiers PS-1 Kit \$8.95\* net

## DYNAKIT STEREO CONTROL




Stereo control with two preamps

- \* Adds Complete Stereo Control To Two Preamps Without Noise or Distortion.
- \* Unique Blend Control Fills In "Hole in Middle."
- \* Level, Balance, Loudness, Channel Reverse, and Dual Tape Monitor Controls.
- \* Only \$12.95\* net
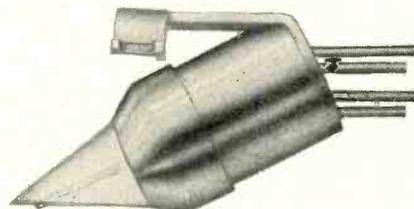
## DYNACO—B & O STEREO PICKUP

- \* New completely symmetrical push pull magnetic pickup for either monophonic or stereo recordings.
- \* High compliance in all directions permits tracking at 2 grams.
- \* Smooth, peak-free response beyond 15kc with ideal channel separation and complete freedom from hum pick up.
- \* With .7 mil replaceable diamond stylus for only \$29.95.



Available from leading Hi-Fi dealers everywhere. Descriptive brochure available on request.  
\*Slightly higher in West

DYNACO INC. 64 J. FORTY-FIRST STREET PHILADELPHIA 4, PA., U.S.A.  
EXPORT DIVISION 25 WARREN STREET NEW YORK 7, N. Y.

# 2X NORMAL OPERATING VOLTAGE +1000

## STANCOR TRANSFORMERS STAND UP!

Every STANCOR iron core transformer gets this breakdown test as a production line operation. To assure you of reliability and safety, each unit is tested for breakdown between windings and to ground—at twice its operating voltage *plus* 1000 volts! STANCOR's thorough testing procedures protect you against failures and call-backs . . . one more reason why experienced technicians everywhere always specify STANCOR.



**CHICAGO STANDARD TRANSFORMER CORPORATION**

3509 ADDISON STREET • CHICAGO 18, ILLINOIS

SAVE TIME with **SENCORE**

See other SENCORE ads in this issue.

**SENCORE Handy "36" R C-Substitution Unit**  
 "36"—Most Often Needed Components at YOUR Fingertips!  
 3 Pole, 12 position switch individually selects one of the "36" components for direct substitution.

- Contains:
- ★ 12—1 watt 10% resistors from 10 ohms to 5600 ohms
  - ★ 12—½ watt 10% resistors from 10K ohms to 5.6 megohms
  - ★ 10—600 volt capacitors from 100-mmf. to .5 mfd.
  - ★ 1—10 mfd., 450V Electrolytic ★ 1—40 mfd., 450V Electrolytic
- ★ For Shop, Lab, or outside service

SENCORE CORP. 121 Official Rd., Addison, Ill.



ONLY \$1295  
 Model H-36 DEALER NET

Completely Isolated Available at all Parts Distributors

## TELEVISION

ing with a 350-mile uhf path, trying to develop it into some form of consistent reception.


Our hat is off to a real pioneer in a field that is all too often overrun with fellows obsessed with quantity and not the more important *quality*.

### Over 50 TV Dx Club:

As TV dxers come and go, so do their ratings in the Over 50 club. Any reporters listed in last year's listing who do not appear in this year's totals may be assumed to be inactive. To maintain one's position in the over-50 listing, it is necessary to transmit no less than two reports per year to this column. It is with a great deal of sadness that we note many of the top dxers of 1954-57 are no longer active. On the bright side, however, this allows more new blood to push closer to the top of the Over 50 TV Dx Club.

Name	Town	Stations	Best Ox Mileage	Uhf Total
Barney Rauch	Peoria, Ill.	263		
Frank Hill	Gallipolis, Ohio	246		
Kingdon P. Schafer	Kenmore, N.Y.	244	2,176	32
David Janowiak	Independence, Mo.	216	1,730	34
B. J. Bingham	Milwaukee, Wis.	200	2,000	20
Ed Rugel	Festus, Mo.	197		
Richard V. Nieman	Kan.	180	1,920	28
Bob Cooper*	Buffalo, N.Y.	168	6,600	8
John Corly	Fresno, Calif.	168		
Bill Eckberg	Midletown, Conn.	165		11
Jim E. Himes	Walnut, Ill.	161		
Ray F. Boyd	Joes, Colo.	159	4,075	
Francis DeGroat	Zirconia, N.C.	150	2,300†	
R. H. Gordon	Salmanca, N.Y.	148		
Ferdinand Ombrowski	Harrisburg, Pa.	141	1,550	7
John T. Sowders	Okauchee, Wis.	132	1,460	17
Milton C. Bay	Richmond, Ky.	129	1,377	24
Dibrell Ingram, Jr.	Brooksville, Ky.	125	810†	34
Stanley Pene	Conway, Ark.	125		
M. W. DeGoer	Utica, N.Y.	124	4,400	
Edwin Prund	Tulsa, Okla.	108		
Kenn Cooper	Ooltun, Ill.	108		24
Jim Hines	Fresno, Calif.	107	2,100	4
Frank Wheeler	Joes, Colo.	106		
Wayne Baer	Erie, Pa.	106	2,117	9
Wesley H. White	Meyersdale, Pa.	105	1,400	4
Alexander H. Ladd, Jr.	New Albany, Ind.	100	1,250	5
Roger Brown	Clearfield, Fla.	98	750†	1
Gary Olson	East Lansing, Mich.	98		9
Ed Hepp	Barrington, Ill.	96		
Oonald Ruland	Portland, Ore.	95	2,900	
Dick Mason	Holly Hill, Fla.	95		
Gary Rahm	Menasha, Wis.	97	1,350	
Ron Pugh	Owen Sound, Ont.	94		
Joseph Valetti	Fort Bragg, Calif.	91		
Mr. & Mrs. W. L. Bush	Monterrey, Mexico	88	5,100	
David Beal	Mexico, Mo.	87		
H. E. Apiey	Tucson, Ariz.	85	1,145	25
Wayne Plunkett	Akron, Ohio	84		22
Morris Foote	Toronto, Ont.	81		
Eddie Albright	Midletown, Ind.	80		
Ronald A. Boyd	Medford, Ore.	80	2,650	
Rod Luoma	Truro, Nova Scotia	78	3,000	
John Black	Detroit, Mich.	78		
David Hanson	Moffat, Ont.	77		
Palmer Ewing	Washburn, Wis.	77	1,300	
Oan Jones	Lindsay, Calif.	76		
Joseph Tibiletti	Chester, Va.	75		
Roger A. Greer	Victoria, Tex.	75		
John Kalb	Auburn, Ill.	72		
Merwyn Dowden	Boonville, Mo.	70		
Ed Davis	Chester, Va.	70		
Bryan Rawlings	Champaign, Ill.	70	730†	23
James Buchmann	Montreal, Que.	68		
David S. Roberts	La Crosse, Wis.	67		
DW Parsons	Royal Oak, Mich.	67	1,125	14
Carl Boehcher	Florence, Ala.	66		
Norris Doyle	Milwaukee, Wis.	63		
Bert Nuber	Pittsburg, Calif.	62	2,350	2
George E. Oldham, 3rd	FT. Lauderdale, Fla.	60		
Russell F. Schafer, 3rd	Johnson City, Tenn.	60	1,680	
David Novick	Junction City, Kan.	59		
J. P. Boyle	Shorewood, Wis.	58		
Julius Bossi	Stratford, N.Y.	58		
Richard J. Maguire	South Bend, Ind.	57		
Tom Rathke	Haddon Heights, N.J.	57	1,130	9
Richard Bergen, 3rd	Clintonville, Wis.	56	1,210	
Robert G. Brasseur	La Grange, Ky.	54		
Harley Hurlburt	Saginaw, Mich.	53	1,657	
Clark F. Conway	Bennington, Vt.	51	1,300	
Barton Cronin	Knightsdown, Ind.	51	1,200	
Amaloo Coro, Jr.	Ontario, Ore.	50		
James Abercrombie	Havana, Cuba	50	950†	
J. P. Boyle	Columbia, S.C.	50		
	Stratford, N.Y.	50		

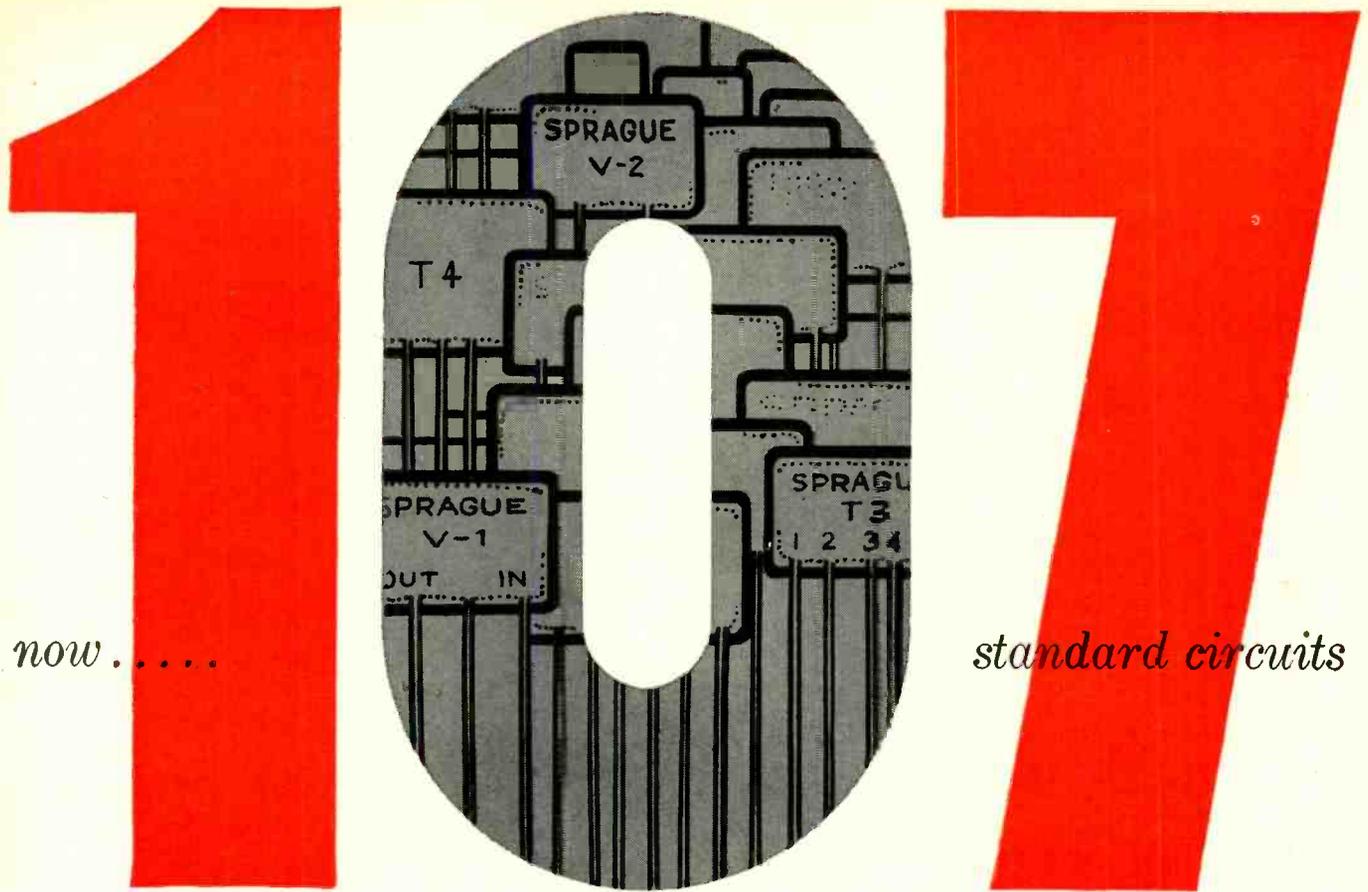\* Uhf editor, Western Radio Amateur  
 † High band  
 ‡ Uhf



now . . . . .

standard circuits

## **BULPLATE® Printed Circuits**

**for all your printed circuit replacements**

Sprague's new BULPLATE Printed Circuit line now includes *the most comprehensive listing of printed circuits available anywhere*. By standardizing on the Sprague BULPLATE line, you'll be able to replace practically every printed circuit found in original equipment, including . . .

antenna-chassis isolation networks  
 detector-triode coupling networks  
 retrace-suppression networks  
 vertical feedback networks  
 triode coupling networks  
 detector-pentode coupling networks  
 automatic gain control networks  
 horizontal deflection networks  
 sound i-f networks

vertical integrators  
 decoupling filters  
 audio output networks  
 phase comparators  
 parallel resistor-capacitor networks  
 tone compensation networks  
 diode filters  
 pentode coupling networks  
 sync take-off networks

Get your copy of Sprague's new BULPLATE Replacement Manual K-351 now. Original set manufacturers' part numbers are cross-referenced to



Sprague replacement part numbers . . . making Sprague BULPLATES extra-easy-to-use. Ask your distributor for a free copy, or send 10c (to cover handling and mailing costs) to Sprague Products Co., 81 Marshall St., North Adams, Massachusetts.

**don't be vague . . . insist on**

# **SPRAGUE®**

*the mark of reliability*

**SPRAGUE RESEARCH IS CONSTANTLY PRODUCING NEW AND BETTER COMPONENTS FOR YOU**







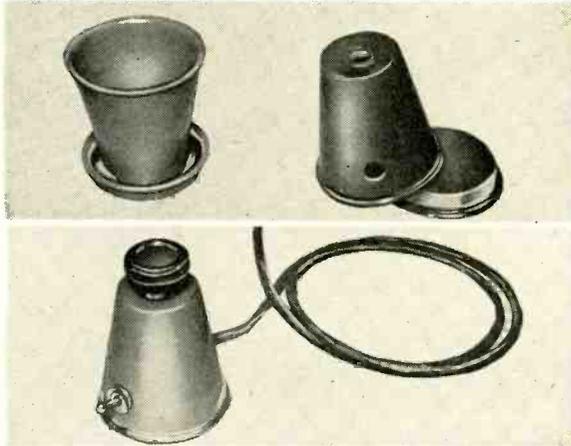
# REMOTE . . . . . VOLUME CONTROL

Flower pot is modified by drilling a hole in its side and bottom.



The completed remote volume control.

*Extremely simple device makes for comfortable listening*

By HAROLD REED

NOT so long ago *Reader's Digest* published a story about an advertising executive who placed on the market a gadget, appropriately called Blab-off, to cut off objectionable television commercial advertising. This little gadget is nothing more than a switch mounted in a suitable container, a two-pair flexible cable with a simple arrangement for connecting into the television set and instructions explaining how anyone may attach the device to the set. (The ad man even pointed out that anyone with a little knowledge of electronic circuitry could buy the few parts himself and make up and attach such a gadget.) All it does is open the loudspeaker voice-coil circuit when the offensive commercial begins and close it again when the blabbing ceases.

For a number of years I have tried various devices to eliminate obnoxious listening of any sort from a television program—a simple switch working like Blab-off and more complicated devices, some using photoelectric cells. All were useful and worth the time and effort put forth in their construction. However, they were all strictly of the on-off type.


Television stations at times seem to regard the audio portion of their transmission of secondary importance. On variety shows the viewer may have the sound level adjusted for comfortable listening volume on skits and other speaking portions of the show, only to have, a little later in the program, musical selections and vocal offerings blaring forth from the loudspeaker. Also, some commercial advertising is not offensive in itself but is shouted at the viewer at an annoyingly high level

not in conformity with the sound level of the rest of the program. Therefore, I felt the need for more than just an on-off device.

A simple gadget for this purpose is shown in the diagrams. It not only cuts the sound on and off but provides volume control from the viewing position.

A constant-impedance variable-L or T attenuator is used. These pads are available in impedances of 6, 8 and 15 ohms. Most loudspeaker voice coils have an impedance somewhere between 6 and 15 ohms; wiring diagrams of the pad are supplied with each of these controls.

An ordinary rheostat or potentiometer is not satisfactory for this purpose. As the resistance of a common control of this type is increased the mismatch between the output transformer and the voice coil also increases, resulting in severe sound distortion. The L or T pad holds the impedance match approximately constant between the output transformer and voice coil, regardless of the attenuation inserted in the circuit.

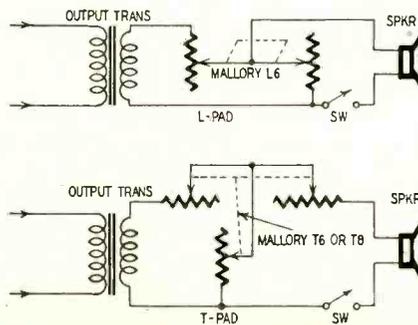

Hookup for the L- and T-pad circuit.

The control and switch of this device can be mounted in any suitable small container. The one shown (see photos) is a small, attractive, plastic flower pot, used in an inverted position. After the parts and cable are attached, the pot's water tray (saucer) is also turned upside down and cemented on what was originally the top of the pot. A piece of felt may be cemented to this new bottom to prevent scratching the furniture. This provides a handy mounting which can be set on a table or placed in the lap of the viewer. It does not upset easily because of its wide bottom.

A very light, flexible cable, 10 feet or more in length, connects the unit to the television receiver. When not in use it is coiled and hung on a hook screwed into the back of the TV cabinet. The gadget itself may be left hanging on the back of the TV receiver or set on top of the cabinet.

When the television set is turned on, the remote volume control is placed in the extreme clockwise position. With the knob in this position attenuation is minimum. The TV set volume control is adjusted so the sound is somewhat louder than desired. Further adjustments of sound level are then made from the viewing position. If desired, the sound may be cut off completely—without disturbing the volume level setting—with the on-off switch.

This little gadget could not be installed easily by persons unfamiliar with radio and TV circuits, but is simple for the experimenter to build and connect. It will provide great satisfaction to the constructor when distasteful babblings start pouring from his television loudspeaker. END

Simply by checking  
all the tubes in the TV set with

**B&K** **DYNA-QUIK**

**YOU CAN INCREASE YOUR INCOME**

**FAST AND ACCURATE**

- Tests complete set in minutes
- Wins customer's confidence
- Saves costly call-backs
- Sells more tubes on-the-spot
- Avoids substitution testing
- Makes more money every day

**\$50\***  
**PER WEEK**

\*ACTUAL EXPERIENCE SHOWS  
TV SERVICEMEN AVERAGE

**2 extra tube sales  
PER CALL**


**5 calls per day in  
5 days equal \$50**

**MEASURE TRUE DYNAMIC MUTUAL CONDUCTANCE**

Thousands of technicians are doing a better servicing job and are making more money today with the famous B&K DYNA-QUIK. Completely tests each tube in seconds, with laboratory accuracy, in home or shop. Measures true dynamic mutual conductance. Shows tube condition on "Good-Bad" scale and in micromhos. No multiple switching or roll chart. Quickly detects weak, short-life, or inoperative tubes. Shows customer the true condition and life-expectancy of tubes in the set; sells more tube replacements per call. Assures customer satisfaction and protects the service guarantee.



MODEL 675

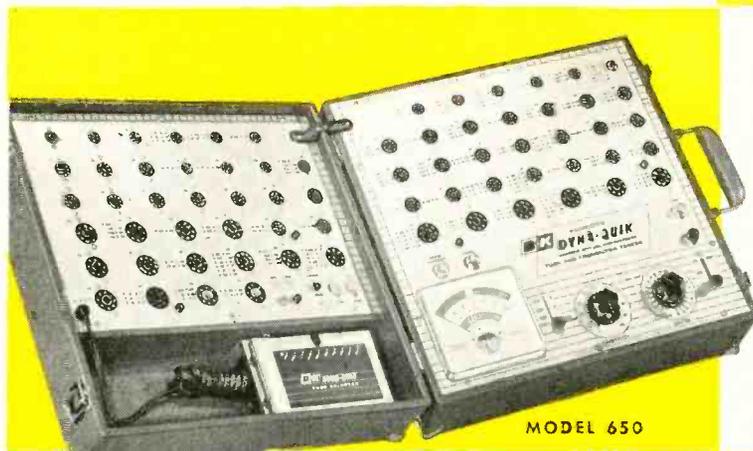

MODEL 650

**Model 650 DYNA-QUIK**

**Fastest, Most Complete, Portable  
TUBE AND TRANSISTOR TESTER**

Checks over 99% of the tubes most widely used in television receivers, plus popular home and portable radio tubes. Tests over 500 tube types. Lists over 125 most commonly used tube types, with settings, on socket panels for maximum operating speed. Complete listing in fast telephone-index type selector. Tests each section of multiple tubes separately for Gm, Shorts, Grid Emission, and Life. Tests each tube for Gas Content. Provides instantaneous Heater Continuity check. Includes 16 spare sockets and sufficient filament voltages for future new tube types. Transistor Section checks junction, point contact and barrier transistors, germanium and silicon diodes, selenium and silicon rectifiers.

Net, **\$169<sup>95</sup>**

**Model 675 AUTOMATIC**

**Simplified, Portable, DYNA-QUIK  
TUBE AND TRANSISTOR TESTER**

With only 60 indexed phenolic Dyna-Cards, you can test over 500 tube types. Dyna-Card automatically sets socket connections for quick, accurate tube test. Checks over 99% of the tubes most widely used in television receivers, plus popular home and portable radio tubes. Easily kept up-to-date by adding new Dyna-Cards. Tests each section of multiple tubes separately for Gm, Shorts, Grid Emission, and Life. Tests each tube for Gas Content and Grid Emission simultaneously with Short Check. Provides instantaneous Heater Continuity test. Transistor Section checks junction, point contact, and barrier transistors, germanium and silicon diodes, selenium and silicon rectifiers.

Net, **\$169<sup>95</sup>**

Manufacturers of Tube Testers, Cathode Rejuvenator Tester,  
Television Analyst, Dyna-Scan, Transistor Tester,  
and other specialized instruments.



See your B&K Distributor or  
Send now for Bulletin AP12-E

**B & K MANUFACTURING CO.**

3726 N. Southport Ave. • Chicago 13, Illinois


Canada: Atlas Radio Corp., 50 Wingold, Toronto 10, Ont.  
Export: Empire Exporters, 458 Broadway, New York 13, U.S.A.

# TV Service CLINIC

conducted by  
**ROBERT G. MIDDLETON**  
TELEVISION CONSULTANT

**C**OLOR TV receiver waveforms have frequency components ranging from 30 cycles to 3.58 mc or sometimes to 4.5 mc. For example, the chroma waveform shown in Fig. 1 has fundamental frequencies of 15,750 cycles and 3.58 mc.

To avoid distorting chroma waveforms, the scope attenuator must pass all waveform frequencies equally, at

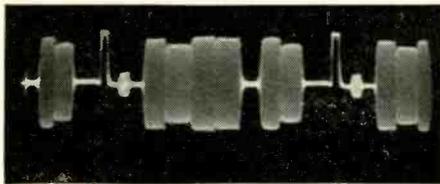


**Fig. 1.—Typical chroma waveform has frequencies from 15,750 cycles to 3.58 mc.**

any attenuator setting. This does not occur in old-style scopes nor in some of the low-priced modern ones.

Using a simple high-resistance potentiometer as an attenuator, as illustrated in Fig. 2, causes distortion. Stray capacitances  $C_{s1}$  and  $C_{s2}$  vary the high-frequency response as the attenuator arm is moved. This distorts a chroma waveform differently at each setting of the potentiometer.

To avoid frequency distortion in a simple potentiometer type attenuator, a low-resistance pot must be used—2,000 or 3,000 ohms. However, such a low input impedance loads down many receiver circuits and is undesirable.

For this reason a high-impedance attenuator which does not cause frequency distortion is used. It is arranged as in Fig. 3. A step configuration is used. When output is taken between  $R1$  and  $R2$ , trimmer  $C$  is used to balance the effect of stray capacitance  $C_s$ . Accordingly, all frequencies in the

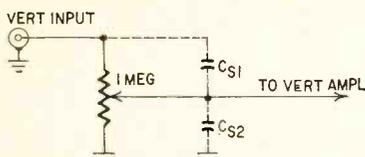


**Fig. 2—A 1-megohm pot is a poor attenuator for a scope used in color-TV service. High-frequency response varies greatly at different attenuator settings.**

waveform are passed equally to the vertical amplifier.

If  $C_s$  is very small,  $R2$  must be shunted by a fixed capacitor (50 or 100  $\mu\text{f}$ ) to bring trimmer  $C$  within range. This is a frequency-balanced system when the time constants  $R1C$  and  $R2C_s$  are made equal.

Most scopes provide several steps of input attenuation so a wide range of operating voltages can be tested without overloading the scope amplifier. For example, a simple step attenuator used in a typical wide-band scope is shown in Fig. 4. It has three decimal steps. Adjusting trimmer  $C1$  balances the divider on the  $\times 10$  step. Trimmer  $C2$  balances the divider on the  $\times 100$  step.

Trimmer capacitors in step attenuators are conveniently adjusted on the basis of high- and low-frequency square-wave patterns. They are adjusted for equal screen deflection at high and low frequencies, without ap-

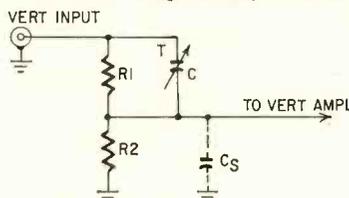

**Fig. 3—A step divider can use high resistance, and causes no frequency distortion when trimmer  $C$  is correctly adjusted.**

preciable tilt or curvature in a reproduced square wave.

### Video puzzler

*I have just repaired an Admiral 21Z1 with no sound or video. I found the tubes OK from the tuner to the picture detector. Then I suspected that there was a bad tube in the video circuit and also one in the sound circuit. The 6AC7 video amplifier was dead. Upon replacing it, both sound and video came in. Since sound takeoff is ahead of the picture detector, how could a dead video amplifier kill the sound? I find the same grid voltage on the sound if, with or without the 6AC7 in its socket. Can you figure this one out?—S. G., Elm Grove, W. Va.*

This is a direct-coupled receiver, with no dc restorer. The age keyer tube re-

ceives its supply voltages from a branch of the direct-coupled video amplifier circuit. Pulling the video amplifier tube changes the dc distribution. This changes the operating point of the keyer tube, and doubtlessly the change in age bias makes the if amplifier inoperative. This accounts for the stoppage of sound when the 6AC7 is pulled.

### Hot chassis

*A Raytheon 2403A has a hot chassis, with frequent failure of the 25CD6 and 12AX4. What do you recommend?—O. B., Flint, Mich.*

A Surgistor will limit the starting current of the series heater string and lengthen the tube life. The hot chassis can be "cooled" only by converting to a transformer power supply.

### Color conversion

*I would like to convert a Westinghouse model H840CK15 to use a newer picture tube, such as the 21AXP22. The 15GP22 in the set has gone gassy. Please advise me if this change is practical.—G. S., Waverly, Pa.*

The 21AXP22 requires 5,000 volts more than the 15GP22 at the ultor. It also requires an electromagnetic convergence system. The electrical and mechanical changes required are so extensive that we cannot recommend this conversion. Perhaps you can convince your customer to trade this receiver in on a large-screen color set.


### Decrease screen size

*What 24-inch tube could be used instead of the 27-inch picture tube in a CBS Columbia receiver? Are any changes required?—A. L. R., Worcester, Mass.*

It is always helpful to have the model number of the receiver. However, this is a conversion which appears practical, requiring mechanical changes only. If you are using a 27AP4, this is an electrostatic-focus tube, of the round metal type. It could be replaced with a 24DP4, which is also a 90° tube, but of glass construction. Both operate OK at 18 to 20 kv. The other 27-inch tubes are magnetically focused, and a suitable replacement would be a 24EP4, having an aluminized screen. Avoid the L type, which would require electrical changes.

### 70° to 90° conversion

*A Fada 21C2 has a bad 21AP4 picture tube. I wish to replace it with a 21-inch 90° tube or a 24-inch tube. What circuit changes would be required*

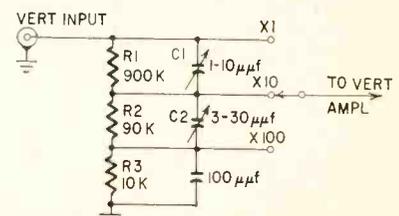

**Fig. 4—A 3-step vertical attenuator as used in a typical wide-band scope for color-TV service.**



**\* NEW TOWERS**

ROHN engineering presents new, dramatic tower lines for your consideration. Be sure to get complete catalog details on this as they are proving to be *tremendous* profit-makers!

**\* MORE DESIGNS**

Outstanding, well-engineered designs of various types are available to suit your *every* requirement.

**\* COMPLETE SELECTION**

The ROHN tower line is now one of the *largest* (and growing larger daily) tower lines of its kind in the nation! By selling and servicing the ROHN line you capitalize on *many* fields and markets that others *cannot* possibly fulfill.

**\* MORE SALES FEATURES**

ROHN towers and its full line of accessories offer *more* sales features and *sooner* than anyone else! Careful inspection always proves the superiority of ROHN towers. Why settle for less than the best? All ROHN products have the *finest* of finishes too... completely hot-dipped galvanized *after* fabrication!

**\* BIGGER PROFITS**

It all adds up to the indisputable fact that ROHN towers make jobber, dealer, serviceman and user *more* money. ROHN has the proof... ask to be shown!

**FABULOUS ROHN "SS" TOWER**

A Completely Self-Supporting Tower to 130' in a Completely Different Design!

This special self-supporting tower is constructed by using 13 different tower sections of varying weight, size, structural strength and taper. Using all 13 sections gives a heavy-duty self-supporting 130 foot tower. However, the individual sections of this tower can be used in various combinations to build a tower to practically any height from 130' on down, and of *specific* strength in order to handle the *particular* antenna that is to be placed on the tower. This means that you can have a ROHN tower *exactly* to meet *your* requirements. Shipping this tower is convenient and installation is simple.

**NO. 50 TOWER**

This tower is a special one utilizing sections of the "SS" tower and is suitable for installations of guyed heights up to 450 feet.

**NO. 60 TOWER**

Special tower using above "SS" tower sections and is suitable in guyed heights up to 600 feet!

**ROHN LINE ALSO INCLUDES:**


**NO. 40 TOWERS**—the communications tower having a structural strength so as to be installed in guyed heights up to 300'. . . thousands are in use today for all types of communication and industrial uses.

**NO. 30 TOWER**—similar to the above No. 40 tower but utilizing different design.

**NO. 6 TOWER**—the widely used tower with the "magic triangle" especially suitable for home television reception.

**P. T. TOWERS**—package towers for easy shipping and storage.

**NO. 25 FOLD-OVER TOWER**

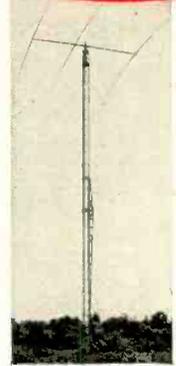

This general purpose communication tower with the zig-zag cross-bracing design is now available as a "fold-over" tower. Amateurs and others requiring a "fold-over" tower are invited to inspect this tower to see its superiority and its many advantages that it has to offer you.

**ROOF TOWERS**—especially designed short height roof installations.

**TUBING**—complete line.


**BASES**—for practically every use.

Also, guying and installation accessories of all types to give **complete** television, amateur or communication towers.

See your ROHN representative in your area, your distributor or contact:

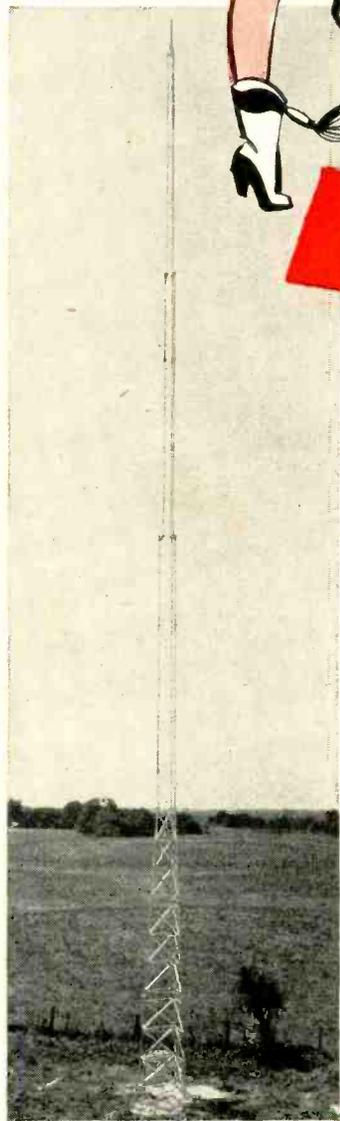**ROHN Manufacturing Company**

116 Limestone, Bellevue Peoria, Ill. Phone 4-9156



**ROHN MANUFACTURING COMPANY**

116 Limestone, Bellevue Peoria, Illinois

GENTLEMEN: Please send me the catalog and information on the following:

- TV Towers
- Amateur Towers
- Communication Towers
- Full line of Rohn products

NAME \_\_\_\_\_

FIRM \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

**MAIL THIS COUPON NOW!**

## TELEVISION

for this replacement?—C. J. D., Brooklyn, N. Y.

We suggest that either a 21ACP4-A or a 21MP4 would be suitable. Both are 90° tubes. It cannot be definitely stated whether your present sweep circuit will fully scan these tubes. A little more sweep power may be required. If so, a 90° yoke and matching flyback must also be installed. However, it is worth trying the present sweep circuit before increasing the sweep power.

### Unstable horizontal sweep

Since replacing the flyback in a Crosley S11-459 with a Ram X117, the horizontal sweep is unstable. The age keying circuit is also inoperative. The video amplifier's plate voltage is 30% low, as is the 105-volt B-line. Removing the 6V6 audio output tube kills the picture. Any suggestions will be greatly appreciated.—G. W., Niagara Falls, Ont.

The keyer difficulty is probably due to incorrect polarity or voltage of the keying pulse, or possibly both. The

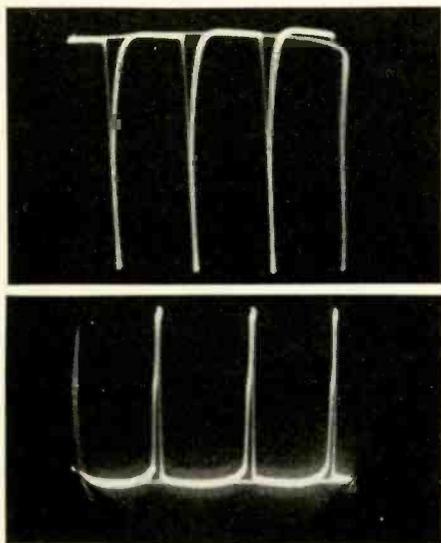


Fig. 5—Keyer pulses must have correct polarity and correct voltage: top—negative-going pulses; bottom—positive-going pulses.

pulses can be obtained in either positive or negative polarity, as shown in Fig. 5. This is best checked with a scope. Since the required keyer voltage is not stated in the service data, it would be helpful to check this against another receiver of the same type. Otherwise, it will be necessary to experiment with various keyer coils to obtain a pulse voltage in a suitable operating range.

To determine whether the horizontal sweep is unstable because of poor age action, you can use override bias for a test. Removing the audio output tube kills the picture because the tube operates as a voltage divider in the B-supply system. Low plate voltage at the video amplifier is probably caused by operating the contrast control at its extreme position to compensate for the incorrect age action.

### Unavailable picture tube

I am working on a Van Aire 14S1 TV

receiver which supposedly uses a 19BP4 picture tube. This type is unavailable, and I would like to determine some other usable tube type.—E. J. S., St. Louis, Mo.

You can use a 19AP4 in place of a 19BP4. Both are 60° tubes. No changes should be necessary.

### 27- to 21-inch screen

I am interested in converting a Muntz 2763A from a 27-inch to a 21-inch tube. Is this a practical change?—W. A. S., Dearborn, Mich.

We assume the problem is the cost of a replacement 27-inch tube. It is quite practical to go from the 27-inch tube to a 21. You could use either a 21AMP4 or a 21ALP4. A 21ALP4-B is somewhat more expensive, but has an aluminized screen which gives a higher contrast picture.

### Needs flyback replacement

A Mirrortone A24C, chassis 9051, has a burned-out flyback transformer THC-10021. My local parts distributors are not able to supply a replacement. I will appreciate any help.—J. G., Racine, Wis.

The flyback originally used in this set was manufactured by Todd. No manufacturer to my knowledge makes a suitable replacement unit. The only alternative is to select some standard sweep circuit for the picture tube and rebuild the flyback section. We regret that no simple repair is possible.

### AM on TV channels

An RCA 21-S-511N receiver is giving some trouble. It is in a home located three blocks from a local AM broadcast station. The AM signal is picked up on all channels. How can I remedy this situation?—E. A. S., Decorah, Iowa

First disconnect the lead-in. If the AM interference is still present, an rf filter must be installed at the receiver's power supply terminals. If this is insufficient, you may have to screen the interior of the cabinet and ground the screening. After any possible pickup

by the line and chassis have been eliminated, reconnect the lead-in. If the interference is now evident, insert a high-pass filter at the tuner's antenna input.

In severe cases, two or three filters can be hooked in series for greater AM rejection. If the tuner input is substantially unbalanced, the lead-in will have a strong antenna effect. This can be eliminated by using shielded 300-ohm line from the antenna to the receiver. Finally, some antenna types are highly directive and can be beamed to minimize the field strength of the broadcast station.

### Fuse-resistor blows


Recently I repaired a Zenith Z1817Z, chassis 15Z1, using a 6-ohm 5-watt fusible resistor. The fuse opens every few days. I have checked the filter, and B-plus voltages are OK. Can you suggest a cause and remedy for this trouble?—M. G. L., Greensboro, N. C.

The most usual cause of this trouble is a starting surge of current (caused by lower heater resistances when cold), inrush of current to the filters and decouplers, as well as the forming current required by the electrolytics when the set has been standing idle. Of course, there may be an elusive intermittent short in the power supply system, but the first thing to try is a Surgistor in the line. It is now being used by RCA (in another form) on their late production. A Surgistor is a relay type protector which prevents more than rated current being drawn until the receiver has warmed up. This requires about 10 seconds.
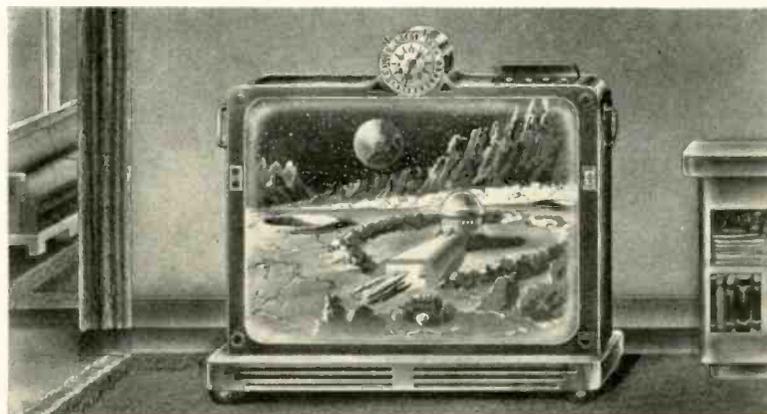
### Tap the TV sound

I want to change the sound portion of an RCA 730TV1 from split sound to intercarrier. It will drive a high-fidelity amplifier. Where is the best place to tap the sound and the best circuit to use for least buzz and distortion? Thank you for this information.—L. B., New York, N. Y.

Intercarrier sound takeoff should be made from the picture detector output



How TV recorder-player described in editorial (page 33) might look while playing back a program. Clock in center top could be set to pick up a number of programs on desired channels, at specified times.

## TELEVISION

lead (input lead to the video amplifier). This avoids the possibility of inter-carrier buzz if the video amplifier should tend to overload. We would advise the use of an intercarrier sound circuit similar to those found in color TV receivers. This will give you top performance. An example is the sound channel used in the Sentinel 816C.

### Sound fades and blasts

*We are having trouble with the audio in a DuMont Travis. It is all right for a few minutes or sometimes long periods, but then fades or gets very loud. We have checked the tubes and parts, but have not been able to locate the trouble.—W. L. McB., Wild-rose, N. D.*

This is a type of trouble best handled by either signal tracing or signal injection. You can use a scope to check stage by stage back from the speaker, to find out where the trouble first appears. In the higher-frequency circuits, a demodulator probe must be used instead of a low-capacitance probe.

### Ion trap and brightness

*In a Zenith 20J23, the ion-trap magnet has to be readjusted as the brightness control is turned up. Any help on this problem will be appreciated.—H. L. DeW., Tiffin, Ohio.*

A 21-inch picture tube operates at high second-anode voltage and the first anode is easily eroded by misadjustment of the ion trap. Erosion causes distortion of the electron lens action in the picture tube. A new picture tube should clear up the difficulty. Be sure the ion trap is correctly adjusted as soon as the new picture tube is installed so the trouble does not recur.

### Poor contrast

*An Airline 05WG-3039B has very poor contrast. However, when the plate of the third if tube is touched, contrast improves to almost normal and remains good until the set is turned off and on again. I would appreciate any suggestions you can offer.—T. W. E. K., Hampton, Va.*

This is very evidently a case of regeneration and border, line oscillation in the third if stage. Use a good sweep and marker generator and align the if strip carefully. However, if this trouble is caused by component failure alignment will not help and you should check the bypass and decoupling capacitors in the third if and detector stages for opens.

### Needs if transformers

*A Craftsman RC-200 with separate sound if's has come into the shop. The sound operates at 21.6 mc. I need replacement sound-if transformers. Can you suggest a source?—A. P., Portland, Ore.*


We suggest the use of Miller 6190 and 6191 if transformers. Miller discriminator transformer 6192 matches these. You can obtain the units from any large parts jobber. END



BY *Grommes*

You turn a dial . . . and something wonderful happens!

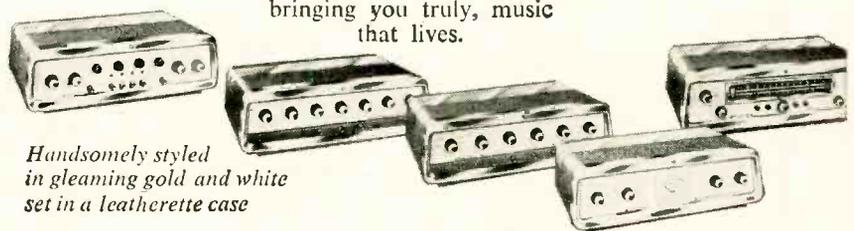You're there . . . reliving the original performance, hearing the songs you love with a new brilliant clarity . . . hearing the depth of life in each musical passage. Grommes Stereo is stereophonic reproduction at its finest . . . superb fidelity with a new realistic depth . . . bringing you truly, music that lives.



*Handsomely styled in gleaming gold and white set in a leatherette case*

You be the judge . . . Your Grommes High Fidelity Dealer will be happy to demonstrate this exciting new line of Grommes Stereo Amplifiers.



Send me full details on the new Grommes Stereo Line

*Grommes* — Division of Precision Electronics Inc.  
Dept. RE-1 9101 King Street, Franklin Park, Illinois


Name \_\_\_\_\_  
Street \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**OUT FRONT all the way...**

**in engineering • styling  
• performance • price!**

# ARKAY STEREO

**Hi-Fi KITS and PRE-WIRED**

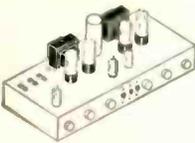

**Arkay CS-12  
12 Watt  
Stereo Pre-Amp  
and Amp**

**Easy-to-build Kit \$35.95**

Enjoy the latest in High Fidelity listening—Stereophonic reproduction through the new ARKAY low-cost Stereo Pre-amp and Amp, Model CS-12. 12 watt Stereophonic and Monaural Integrated power amplifier and pre-amp of advanced design. Selects and controls all Stereo or Monaural program material. Operates from any ceramic or crystal cartridge, high output tape decks, tuners and other auxiliary equipment. All inputs are of the dual variety for the rendering of full Stereo reproduction.

**SPECIFICATIONS**  
Power output, 12 watts, peak power, 20 watts, frequency response, ±1 db, 20-20,000 cps. 1M distortion, 4 to 1; 60-7,000 cps 1.2% impedance 4, 8, 16 ohms. Input levels .3 V. for full output.

## ARKAY SPA-55 STEREO AMP

Priced for everyone's budget, here at last is a STEREO amp which is almost a must for every STEREO fan! Housing two identical 27½ watt distortion-free amplifiers the SPA-55 is unsurpassed in quality and performance. The SPA-55 may be used as a STEREO amp, a bi-amp, and as a 55 watt monaural unit.

Wired and tested \$79.95 Easy-to-build kit **\$64.95**

SPA-35 35 watt \$62.95 Easy-to-build kit \$49.95

## ARKAY SP-6 STEREO CONTROL CENTER



The SP-6 is a completely self powered sensitive dual pre-amp with dual inputs and outputs. Engineered to fit your requirements today, as well as tomorrow, the SP-6 provides unparalleled flexibility. Output of both amps is individually adjusted by one control, reverse position, hi to filters, etc.

Wired and tested \$62.95

**SAVE!** Easy-to-build kit **\$39.95**

Prices less cover—for panel mounting

## ARKAY ST-11 AM-FM STEREO TUNER




Here, for the first time, is an AM-FM STEREO Tuner within the reach of every audiophile. Unmatched by units costing twice the price, the ST-11 is two distinct receivers in one featuring 4 µV, for 20 db quieting. Variable AFC. Single front panel switch controls AM, FM or STEREO selection.

Wired and tested \$74.50

**SAVE!** Easy-to-build kit **\$49.95**
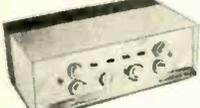
## ARKAY SA-25 STEREO PRE-AMP PLUS ONE 25 WATT AMP



Here is the finest dual channel pre-amp and amp on one precisely engineered and designed chassis... an economical, practical way to convert to STEREO. When the SA-25 is attached to your present power amplifier it reproduces two separate channels of sound for STEREO from tape, records, and AM-FM. One easy, inexpensive step brings you the realistic, breathtaking magic of STEREO—with Arkay's SA-25.

Wired and tested \$89.95

**SAVE!** Easy-to-build kit **\$59.95**

All prices 5% higher west of Mississippi.

**NOW AT YOUR LOCAL DEALER!**

**FREE!** Illustrated catalog with detailed specifications of Arkay Hi-Fi Stereo, Radio and Test Equipment. Write today for your free copy.

**arkay** Dept RE-1  
120 CEDAR STREET NEW YORK 6

**TECHNICIANS'**

# NEWS



## INDUSTRY LEADERS MEET IN ANTI-FRAUD DRIVE

More heat than light was generated at an industry-wide meeting of 100 representatives of technicians' associations, TV manufacturers and distributors in New York City with State Attorney General Louis J. Lefkowitz to map measures to "eliminate fraudulent practices" in TV servicing.

Delegates at the stormy 2½-hour session agreed to nominate members for a seven-man committee to make recommendations for legislation and other state action to curb dishonest repairmen and tube counterfeiting. Several hot disputes developed over the quality of today's TV sets. Technicians' complaints centered around the use of printed circuits and the inaccessibility of chassis of some modern receivers.

The Attorney General said that complaints about TV repair and defective tubes constituted the second largest category of complaints sent to his office. Technicians told of their unsuccessful campaign for a state licensing bill. Lefkowitz called for a "bold solution" from the industry itself, perhaps in the form of a code of ethics or technicians' licensing law. The industry committee had not yet been appointed by press time.

Among those attending the meeting were representatives of the Empire State Federation of Electronic Technicians Associations (ESFETA), Association of Radio & Television Servicemen of New York (ARTSNY), Metropolitan Electrical Appliance Dealers Association, Electronic Industries Association (EIA), Tube Testers Association, Sylvania Electric Products Inc., RCA, New York City Better Business Bureau and several New York TV distributors.

The meeting was called shortly after the Attorney General obtained a court order against a Brooklyn TV repair shop accused of defrauding customers of more than \$500,000 a year. A spokesman for the Attorney General said the shop, Benzack Stores Inc., advertised TV repairs at low prices as a come-on. When customers allowed their sets to be taken to the shop for an estimate, the shop would demand payment before returning the set. He said the company succeeded in appropriating about 1,000 sets from customers who couldn't pay the bill.

## "CROOKS IN EVERY TRADE"

A Culver City, Calif., TV and service dealer won praise from his competitors and favorable comment from his customers with a newspaper ad designed to counteract "sensational newspaper

stories regarding the crooked antics of a few racketeering service companies."

This was the caption of the quarter-page run by Milt Aller's Tops TV in Culver City, Venice and Mar Vista newspapers:

## Newspaper Headlines!

'Banker Absconds With \$500,000'  
'Doctor Accused of Illegalities'  
'Lawyer Swindles Elderly Couple'  
TV Serviceman Bilks Public'

Yes, there are crooks in every trade and profession. That goodness, however, that these vipers represent only a tiny fraction of the millions of folks serving their fellow man and country with the highest ethics.

The ad went on to say that "there are crooks in every trade and profession" but they "represent only a tiny fraction of the millions of folks serving their fellowmen and country with the highest ethics." It warned against bait advertising, "ridiculously low prices" and "night riders."

The response to the ad led Aller to conclude that it may have served its purpose—as he put it—"to help clear the smog in the air and let John Q. Public know that he can get honest service if he calls a reliable company and is willing to pay a fair labor charge."

## TRANSISTOR LECTURES

A series of eight lectures on transistors is being sponsored by Associated Radio and Television Servicemen (ARTS) of Chicago for members and guests. The twice-a-month sessions are conducted by speakers from CBS-Hytron, Zenith, Sylvania, RCA Service Co. and Motorola-Chicago.

## NEW COMMITTEE FIGHTS CAPTIVE SERVICE

A national effort to battle the expansion of set manufacturers in the servicing field has been launched by a group of technicians' organizations under the banner of "Independent Dealers' Electronic Activities committee."

The new committee's initials—IDEA—represent its approach to the problem, declared Karl W. Heinzman, president of Television Service Association (TSA) of Michigan and a prime mover in the new group. He said IDEA intends to seek better communications between manufacturers and independent service dealers and to function as a spokesman in presenting the technicians' side of the picture "to the manufacturer, the public and the legislatures, both state and federal."

Heinzman said 22 state and local associations in 13 states have pledged their support to IDEA, which he

# SENCORE FS-3 FUSE-SAFE METER

Cut down on costly call backs caused by blowing fuse resistors

Nearly all TV Manufacturers now produce TV receivers with fuse resistors in the power supply section. Technicians have learned that this component can be a real source of trouble unless the circuit is serviced properly. Many times, the fuse resistor is replaced and, apparently, the receiver is functioning normally. In a few days, the service technician makes an expensive call back, only to find the fuse resistor open again. The Sencore FS 3 Fuse-Safe meter is designed to test the power supply circuit to determine whether or not it is safe to replace the fuse resistor. It can also be used in much the same manner to test circuits using fuses. It has a third function of serving as a wattmeter at 115 volts.

## WHY A FUSE RESISTOR IS USED

Let us see why a fuse resistor is used. The circuit shown in Fig 1 is a typical TV power supply as used in an Admiral 16AG1 portable. Fuse resistor R501 serves a dual purpose. It protects the selenium rectifiers from inrushing currents when the set is first turned on and at the same time, acts as a B-plus fuse. This lowers production cost, and, therefore, it is usually found in portable TV receivers and radios only.

## HOW A FUSE RESISTOR IS DIFFERENT

The fuse resistor is unlike a fuse or conventional resistor to service. It is neither as stable as a heavy wire-wound resistor nor does it fuse like an ordinary fuse. For example, the AC current being drawn through the fuse re-

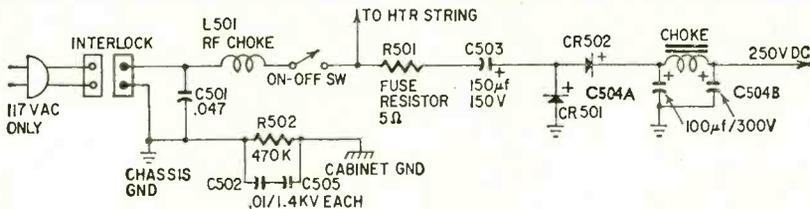


Fig. 1—Power supply of Admiral 16AG1 is typical of TV power supplies using fuse resistors.

sistor in figure 1 is approximately one ampere. This fuse resistor should not draw over 1.2 amperes and is usually operated below this level. If 1.5 amperes were drawn through the fuse resistor, it would open but perhaps not for days. If three amperes of current were drawn through the fuse resistor (which is approximately three times the rated amount), it would still take 60 seconds to open. Of course, the problem with the long delay when you have only a ten percent overload is that you are safely back at your service shop when the fuse resistor opens. This means another trip . . . no charge. The \$8.95 cost of the FS 3 will soon pay for itself as these costly call-backs are prevented.

## WHAT CAUSES THE FUSE RESISTOR TO OPEN

A number of faults in the circuit shown in figure 1 will cause the fuse resistor to open. Here are some.

1. Filter capacitors C503, C504A or C504B becoming leaky. The picture may appear normal but the fuse resistor will blow after several hours of continuous use.
2. Capacitors C504A or C504B increasing in capacitance. Current drawn through the fuse resistor is proportionate to the capacity value.
3. High AC line voltage.
4. Any B plus short in the receiver. This is one condition that may show up in the picture or sound before the fuse resistor blows.
5. A defective fuse resistor. Fuse resistors have been known to give a great deal of trouble under normal operating conditions, often when the circuit is operating properly. However, you can't be sure that it is only the fuse resistor unless the circuit is checked first.

# Time-Saver of the MONTH!

by Herb Bowden\*



Fig. 3—Model FS 3 is designed to aid in checking fuse-resistor circuits.

## HOW TO TEST THE FUSE RESISTOR CIRCUIT WITH THE FS-3 CHECKER

The FS 3 Fuse Safe tester is especially designed to simplify the checking of fuse resistor circuits. Note that the FS 3 checks the

current scale for either AC or DC should be used for circuits that are normally used throughout the receiver, except for line fuses. If the meter indicates above the rating of the fuse, the circuits should be repaired or a higher value fuse used. This is especially handy in horizontal output circuits where the change of a damper tube, or the drive voltage on the output tube will lower the current and stop call backs on these intermittent fuse blowing sets.

To check line fuses or to use the FS 3 as a wattmeter, switch to PWR CORD and to the 10 ampere range. Plug in the line cord and then plug the unit into the AC receptacle. Read either amperes or wattage directly from the two top scales.

## WHY IT IS NECESSARY TO HAVE A SPECIAL METER TO CHECK THESE CIRCUITS

The FS 3 checker is the only service type tester available that will check the fuse resistor circuits accurately. This is because it is necessary to have a meter that will check AC, DC and pulsating DC at the same time. More than this, most service type meters do not read AC current at all. A DC Ammeter will read near zero in this circuit. The most important reason for the use of the FS 3 is that it is the only meter that interprets the current rating of a fuse resistor for you. The TV schematics do not list the optimum ratings of the

Fuse Resistor (ohms)	Maximum Operating AC (amps)
4.7	1.3
5	1.2
5.6	1.2
6	1.2
7.5	1.0
9	0.85
10	0.85
22	0.6
47	0.85
100	0.2

fuse resistors. They are not rated in power dissipation so that one can derive the operating current. More than this, there is little coordination between the physical size of the fuse resistor and the maximum current point. Here is a table of the maximum operating currents as determined by an investigation throughout the industry. The FS 3 red and green scales were determined from these values.

## HOW TO DETERMINE VALUE OF FUSE RESISTOR TO USE IN THE RECEIVER

Most fuse resistors are marked with part numbers only. The schematic will generally show the value of the fuse resistor but is time consuming to look up and often is not available. If a fuse resistor burns out, merely connect the Fuse Safe checker in place of it and note the scale where the reading is about 10 per cent off the red area into the green. Install this value fuse resistor and it will protect the circuit and will not burn out due to overload. Naturally, the TV circuit should be operating properly before using the FS 3 for this check.

## WHERE TO BUY THE FS-3

The FS 3 can be purchased from nearly every parts distributor in America and Canada. Just ask for the Sencore Fuse Safe that sells for \$8.95 dealer net.

\*President SENCORE  
121 Official Road

Addison, Ill.

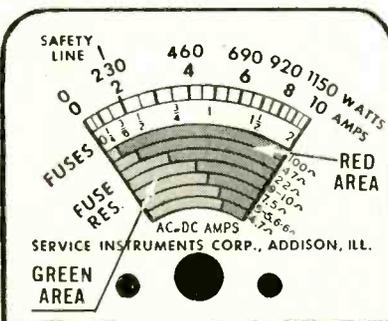


Fig. 2—FS 3 Meter Scale

## OTHER FUSE SAFE CHECKS

The Fuse Safe meter can be used in the same manner as above for checking circuits with fuses to see whether or not it is safe to replace the fuse. A 2 ampere

stressed is "a committee, not an association." He pictured the committee as a spokesman for the independent service dealer to gain him recognition as "an important small businessman," and provide him "a voice in the very things that affect his destiny."

Among the state technicians' associations represented by IDEA are TSA of Michigan, Texas Electronic Association (TEA), Television Electronic Service Association (TELSA) of Connecticut, Associated Radio & Television Servicemen (ARTS) of Illinois, Minnesota Television Service Engineers (TSE), the Electronic Association of Missouri (TEAM).

### GE NAMES ALL-AMERICANS

Wayne E. Lemons, of A-1 TV & Radio, Buffalo, Mo., was one of 10 service technicians winning General Electric's 1958 All-American Awards for public service. He was selected for



his activities in conducting extracurricular electronics courses, youth work and other civic causes. A frequent contributor to RADIO-ELECTRONICS, Lemons' most recent article, "TV Design for '59," appeared in these pages last month.

Other technicians receiving the \$500 All-American Award and honored at a special ceremony in Washington, were: Stanley Everett, Everett's Television & Radio Sales, Alhambra, Calif.; A. George Catavolo, Elm Radio & TV Service, Somerville, Mass.; Albert P. Kazukonis, Brockton Television, Brockton, Mass.; Edwin B. Haines, Oxboro Radio & TV, Bloomington, Minn.; Vernon E. Brooks, Brooks Electric Co., Norristown, Pa.; Theodore W. Fickert, Hoover's Radio-TV, Lansdale, Pa.; T. E. (Buck) Adams, Adams Appliance & Hardware, Channing, Tex.; Bryce R. McNeely, McNeely's Ace TV, Longview, Wash.; Vernon Townsend, Townsend's Radio & Lock Service, Menomonie, Wis.

### HARMON HEADS TESA-OHIO

Russ Harmon of Cincinnati was elected president of the Television & Electronic Service Association (TESA) of Ohio at the convention in Springfield. Don Sisk, Columbus, was chosen first vice president; V. H. Bailey, Dayton, second vice president; John P. Graham, Columbus, secretary, and Marvin Miller, Springfield, treasurer.

Jack Barton of TSA-Detroit spoke on the effectiveness of that city's Technician licensing ordinance. John Graham and Don Wilson reported on a

## —what is the DIFFERENCE?

At a glance, all twin leads look alike. Why then should they sell at such widely different prices? What is the difference between Quality and "Price" twin leads?

To answer this question, AMPHENOL has prepared an informative slide film. It compares "Price" versus Quality twin lead in nine important ways:

- | Quality Twin Lead           | vs | "Price" Twin Lead                          |
|-----------------------------|----|--|
| 1. Virgin Polyethylene      |    | 1. Reclaimed, reground Polyethylene        |
| 2. Pure Polyethylene        |    | 2. Wax extenders                           |
| 3. Exact mil thickness      |    | 3. Up to 10% less than marked              |
| 4. Strong copper conductors |    | 4. Small strands, less copper              |
| 5. Properly annealed wire   |    | 5. Brittle, rejected wire                  |
| 6. 3/4" "lay" of wire       |    | 6. 1 1/2" "lay"—less copper, less strength |
| 7. Proper conductor spacing |    | 7. Conductors close—wrong impedance        |
| 8. Full lengths on spools   |    | 8. Undership as much as 50 ft.             |
| 9. Quality manufacturing    |    | 9. Extrusion speedup, no inspection        |

Because of these differences, it's a gamble every time "Price" twin lead is used—a gamble that "saves" about 26¢ on a 50 foot installation! It's a gamble that the installer always loses.

USE QUALITY—USE AMPHENOL TWIN LEAD!



Arrange with your Authorized AMPHENOL Distributor to see "What is the Difference?"—get the facts on "Price" twin lead.

Write for a copy of "What is the Difference?"—a useful booklet which summarizes the main points of the slide film.



AMPHENOL ELECTRONICS CORPORATION

chicago 50, illinois

www.americanradiohistory.com

proposed license law for Columbus. Other problems discussed were captive service and elimination of unethical practices in servicing. Toledo was selected for the spring convention.

**PART-TIMERS SURVEYED**

The increasing activity of part-time service technicians is under close scrutiny by the Television & Electronic Service Association (TESA-MARTS) of Milwaukee. A recent survey of members revealed that they considered "the wrong kind of part-timers" their biggest problem.

The TESA-MARTS part-timer campaign is aimed at spotlighting those who compete unfairly with law-abiding technicians. Using names of part-timers supplied by members, the association plans to determine through city, state and federal governments whether part-timers are paying their income taxes, keeping adequate books, complying with zoning ordinances, paying commercial telephone rates and making proper declaration on their city personal property tax forms. All discrepancies will be reported to the Better Business Bureau.

**FREE SERVICE DROPPED**

Independent service technicians won a partial victory when a large California radio and television manufacturer agreed to drop a program of servicing all brands of radios and advertising "free service" on its own-make sets.

Following protests by technicians' associations, president Robert S. Bell of Packard-Bell Electronics announced that the plan was a 2-week "experiment" and that "we will no longer advertise or service radios free of charge—nor will we service other brands of radios."

**TV SHOW PLUGS SERVICE**

Organized TV technicians in particular, and the independent service industry in general, is receiving a big boost on a filmed TV show now in national release.

The *Paul Coates Show*, which originates at KTTV, Los Angeles, and is syndicated to other stations in filmed form, devoted one episode to TV service. A reformed "crooked TV technician," was interviewed on the tricks dishonest shops employ. Then Lee Neal, of the Burbank Chapter of Society of Radio & Television Technicians (SRTT), answered questions, urging that set owners choose a technician who is a member of an association and warning against supermarket tube checkers.

The idea was suggested to Coates by SRTT member Ralph Johannut of Tri Color TV, Burbank, while servicing Coates' set. Coates liked it, and the show was arranged, unrehearsed. It had one immediate result in the Los Angeles area: The Better Business Bureau opened an investigation of supermarket tube checkers. **END**



**IMPORTANT NEW BOOKS**

**FUNDAMENTALS OF TRANSISTORS** (2nd edition) by Leonard M. Krugman, P.E. This, the second edition, (revised and expanded) modernizes the highly successful and popular first edition, so as to embrace the latest developments in the transistor art. #160, \$3.50.

**A-C CIRCUIT ANALYSIS** (Electronic Technology Series) edited by Alexander Schure, Ph.D. Fundamental concepts of alternating current made completely understandable. Comprehensive mathematical treatment. #166-19, \$1.80.

**CONDUCTANCE DESIGN OF ACTIVE CIRCUITS** by Keats A. Pullen, Jr., Eng.D. The non-linearity of electron tubes and transistors has for many years greatly complicated the design of active circuits associated with these devices. This book presents a proven method of overcoming these complications. It presents the conductance technique as applied to the design of a wide variety of vacuum tube and transistor amplifier, mixer and oscillator circuitry, in the broadest sense. #207, Cloth Bound, \$9.95.

**BASIC PULSES** by Irving Gottlieb, P.E. Pulses are vital in every area of electronics—computer, radar, industrial, television. This "picture-book" course covers the nature, measurement and application of pulses—what they are and how they are used. #216, \$3.50.

**VACUUM TUBE CHARACTERISTICS** (Electronic Technology Series) edited by Alexander Schure, Ph.D. Provides an extremely comprehensive discussion on vacuum tubes, their constants and characteristics making the fundamentals of vacuum tubes fully understandable. #166-22, \$1.80.

**HOW TO TROUBLESHOOT A TV RECEIVER** (2nd edition) by J. Richard Johnson. The second edition of this highly popular book has been expanded and brought up-to-date. Shows how to pinpoint troubles in all types of TV receivers and how to repair them quickly. #152, \$2.50.

**METALLIC RECTIFIERS & CRYSTAL DIODES** by Theodore Conti. Covers background, construction, characteristics and applications of crystal diodes and metallic rectifiers. #213, \$2.95.

**FAMOUS 'PICTURE-BOOK' COURSES**

Easy, Low Cost Way to the Most Modern Electronic Know-How

**BASICS OF DIGITAL COMPUTERS** by John S. Murphy. #196, 3 vols. soft covers, \$7.50; #196H, Cloth Bound, \$8.50.

**BASIC TELEVISION** by Alexander Schure, Ph.D. #198, 5 vols., soft covers, \$10.00; #198H, Cloth Bound, \$11.50.

**BASIC ELECTRICITY** by Van Valkenburgh, Nooger & Neville, Inc. #169, 5 vols., soft covers, \$10.00; #169H, Cloth Bound, \$11.50.

**BASIC ELECTRONICS** by Van Valkenburgh, Nooger & Neville, Inc. #170, 5 vols., soft covers, \$10.00; #170H, Cloth Bound, \$11.50.

**BASIC SYNCHROS & SERVOMECHANISMS** by Van Valkenburgh, Nooger & Neville, Inc. #180, 2 vols., soft covers, \$5.50; #180H, Cloth, \$6.95.

**BASIC ELECTRICAL POWER DISTRIBUTION** by Anthony J. Pansini, P.E. #187, 2 vols., soft cover, \$4.80 per set.

**WHICH OF THESE RIDER TITLES WILL HELP YOU KNOW MORE .. EARN MORE IN 1959?**

**FOR MORE HOBBY FUN, CAREER ADVANCEMENT**

**TELEVISION—HOW IT WORKS** (2nd edition) by J. Richard Johnson. #101, Marco, \$4.60; #101H, Cloth Bound, \$5.50.

**BASIC VACUUM TUBES AND THEIR USES** by Rider & Jacobowitz. #171, soft cover, \$3.00; #171H, Cloth Bound, \$4.50.

**REPAIRING TELEVISION RECEIVERS** by Cyrus Glickstein. #191, \$4.40.

**BASICS OF PHOTOTUBES & PHOTOCELLS** by David Mark. #184, \$2.90.

**INTRODUCTION TO PRINTED CIRCUITS** by Robt. L. Swiggett. #185, \$2.70.

**INDUSTRIAL CONTROL CIRCUITS** by Sidney Platt. #202, \$3.90.

**RADIO OPERATOR'S LICENSE Q & A MANUAL** (6th edition) by Milton Kaufman. #130, Cloth Bound, \$6.60.

**OBTAINING & INTERPRETING TEST SCOPE TRACES** by John F. Rider. #146, \$2.40.

**GETTING STARTED IN AMATEUR RADIO** by Julius Berens, W2PIK. #199, \$2.40.

**HOW TO READ SCHEMATIC DIAGRAMS** by David Mark. #208, \$3.50.

**MARINE RADIOTELEPHONE PERMIT Q & A MANUAL—Third Class Operator** by Milton Kaufman. #206, \$1.35.

**ELECTRONICS TECHNOLOGY SERIES**  
 #166—RC & RL Time Constant, \$9.00. #166-2—FM Limiters & Detectors, \$9.00. #166-3—Frequency Modulation, \$9.00. #166-4—Crystal Oscillators, \$1.25. #166-5—A-M Detectors, \$1.25. #166-6—Limiters & Clippers, \$1.25. #166-7—Multivibrators, \$9.00. #166-8—R-F Transmission Lines, \$1.25. #166-9—Amplitude Modulation, \$1.25. #166-10—Blocking Oscillators, \$1.25. #166-11—Wave Propagation, \$1.25. #166-12—Superheterodyne Converters & I-F Amplifiers, \$9.00. #166-13—L-C Oscillators, \$1.25. #166-14—Antennas, \$1.50. #166-15—Inverse Feedback, \$9.00. #166-16—Resonant Circuits, \$1.25. #166-17—Electrostatics, \$1.35. #166-18—D-C Circuit Analysis, \$1.35. #166-21—Vacuum Tube Rectifiers, \$1.50. #166-23—Impedance Matching, \$2.90. #166-24—Gas Tubes, \$1.50.

**GET THE MOST OUT OF YOUR HI-FI EQUIPMENT**

**STEREOPHONIC SOUND** by Norman H. Crowhurst. #209, \$2.25.

**HIGH FIDELITY SIMPLIFIED** (3rd edition) by Harold D. Weiler. #142, \$2.50.

**HI-FI LOUDSPEAKERS & ENCLOSURES** by Abraham B. Cohen. #176, Marco, \$4.60; #176H, Cloth Bound, \$5.50.

**REPAIRING HI-FI SYSTEMS** by David Fidelman. #205, \$3.90.

**GUIDE TO AUDIO REPRODUCTION** by David Fidelman, #148, \$3.50.

**HOW TO SELECT & USE YOUR TAPE RECORDER** by David Mark. #179, \$2.95.

**FOR BETTER AND MORE PROFITABLE SERVICING**

**REPAIRING PORTABLE & CLOCK RADIOS** by Ben Crisses & David Gnessin. #224, \$2.75.

**HOME AIR CONDITIONING—Installation & Repair** by J. Derman, F. Makstein, H. Seaman. #211, \$3.50.

**ADVANCED TV SERVICING TECHNIQUES** by Zbar & Schildkraut. #161, \$3.60. **LABORATORY WORK-BOOK.** #161-2, \$9.50.

**HOW TO INSTALL & SERVICE INTERCOMMUNICATION SYSTEMS** by Jack Darr. #189, \$3.00.

**HOW TO SERVICE TAPE RECORDERS** by C. A. Tutthill. #167, \$2.90.

**TV PICTURE TUBE-CHASSIS GUIDE** by Rider Lab Staff. #204, \$1.35.

**TV TUBE LOCATION & TROUBLE GUIDE (RCA)** by Rider Lab Staff. #194, \$1.25.

**SERVICING TV AFC SYSTEMS** by John Russell Jr. #192, \$2.70.

**SERVICING TV VERTICAL & HORIZONTAL OUTPUT SYSTEMS** by Harry Thomas. #150, \$2.40.

**VALUABLE AIDS FOR ENGINEERS, ADVANCED TECHNICIANS**

**TRANSISTOR ENGINEERING REFERENCE HANDBOOK** by H. E. Marrows. #193, Cloth Bound, \$9.95.

**PHYSICS & MATHEMATICS IN ELECTRICAL COMMUNICATION** by James Owen Perrine, Ph.D. #219, Cloth Bound, \$7.50.

**CONDUCTANCE CURVE DESIGN MANUAL** by Keats A. Pullen Jr., Eng.D. #210, Stiff Cover Spiral Bound, \$4.25.

Look for these books at your jobber or bookstore. If not available order direct. REI.


CANADIAN PRICES 5% HIGHER

**JOHN F. RIDER PUBLISHER, INC.** 116 W. 14th St., N. Y. 11, N. Y.

Canada: CHARLES W. POINTON, LTD., 6 Alcina Avenue, Toronto, Ontario

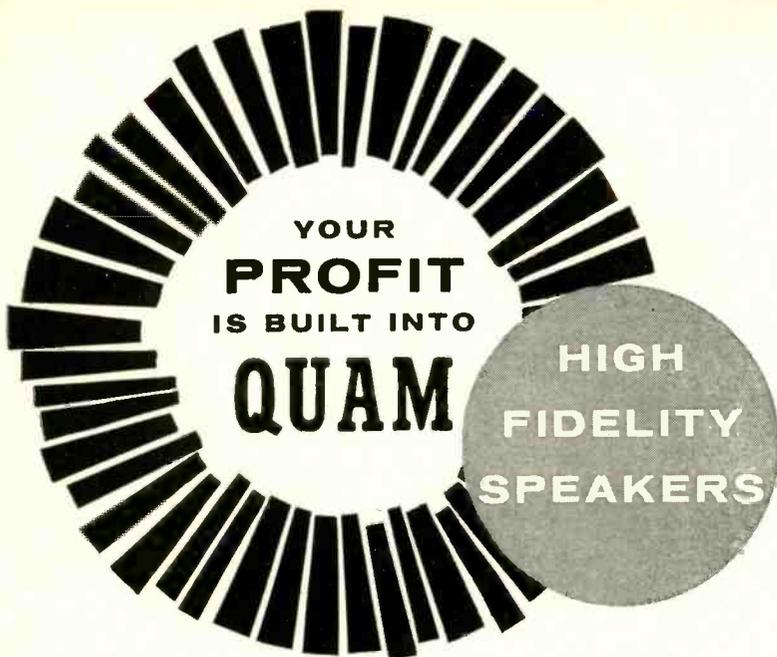Note: All books soft cover except where noted.





Quam Hi-Fi Speakers are the List Price line. They are never promoted to the public at "audiophile net," or some similar phrase which deprives you of the opportunity to make your legitimate profit. When you sell and install Quam High Fidelity speakers, you come out way ahead on the deal.

So does your customer. The speaker he buys from you at *list* compares favorably with any other hi-fi speaker at the same dollar cost *net*. **That's because**

1. The design of Quam speakers emphasizes *performance* rather than non-functional decorative features.
2. Quam Hi-Fi Speakers represent the accumulated skill and experience of thirty years of fine speaker manufacturing.
3. Quam's position as the world's largest exclusive speaker manufacturer permits many production economies to be passed along to you and to your customer.

See your Quam distributor for complete information about the full line of Quam Hi-Fi Speakers—extended range, tweeters, woofers, coaxials. *Quality* is built into every one of them—and so is your profit!

## QUAM-NICHOLS COMPANY

236 East Marquette Road • Chicago 37, Illinois

CANADA:

A.T.R. Armstrong, Ltd., 700 Western Road, Toronto 9, Ontario

D. Eldon McLennan, Ltd., 1624 W. Third Avenue, Vancouver 9, B.C.



A VARIETY of types appear this month. Highlights are a 110° extra short picture tube, a power transistor for TV deflection circuits, an ultra-high-speed switching transistor, and a duo-diode-tetrode for auto radios.

### 2N1046


A p-n-p diffused junction high-frequency power transistor designed for horizontal and vertical CRT deflection circuits. It has a hermetically sealed, welded metal case with glass-to-metal seals between the mounting base and the leads.

Maximum tentative ratings of this Texas Instruments transistor at 25°C are:

V <sub>CB0</sub>	80	(I <sub>c</sub> =2 ma)
V <sub>CE</sub>	80	(V <sub>BE</sub> =0.2, I <sub>c</sub> =2 ma)
V <sub>EB0</sub>	1	(I <sub>E</sub> =2 ma)
I <sub>c</sub> (amps)	3	
P <sub>total</sub> (watts)	15	

Design characteristics at 25°C are:

f <sub>r</sub> (mc)	10	(I <sub>c</sub> =0.2 A, V <sub>c</sub> =20)
h <sub>FE</sub>	70	(I <sub>c</sub> =0.5 A, V <sub>c</sub> =2)
C <sub>ob</sub> (μf)	140	(I <sub>E</sub> =0, V <sub>CB</sub> =40)

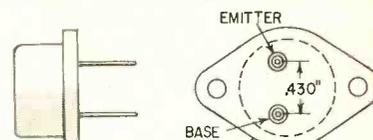

COLLECTOR CONNECTED TO CASE

2N1021 & 2N1022  
& 2N1046

### 2N1021, 2N1022

Germanium p-n-p alloy-junction power transistors designed for high-voltage power converters, amplifiers and switching circuits. They feature low distortion, linear transconductance, low saturation resistance and fast switching times.

Maximum ratings of these Texas Instruments units at 25°C are:

	2N1021	2N1022
V <sub>CE</sub> (I <sub>c</sub> = 2 ma)	100	120
V <sub>BE</sub> (V <sub>BE</sub> = 0.2, I <sub>c</sub> = 2 ma)	100	120
V <sub>EB</sub> (I <sub>E</sub> = 2 ma)	30	30
P <sub>total</sub> (mw)	50	50
I <sub>c</sub> (amps)	5	5
I <sub>B</sub> (amps)	3	3

### 2N307-A

This p-n-p power transistor is intended for general-purpose applications, particularly for audio-frequency circuits.

**YOU GET SOMETHING EXTRA WITH**

JUST REMOVE KNOB AND SPRAY!

**FREE!**

"SPRAY AID" AND "WALL MOUNT" WITH EVERY 8 OZ. CAN

**TROL AID** VOLUME CONTROL & CONTACT CLEANER

**TUN O LUBE** TUNER CLEANER

Non-inflammable • Non-Toxic  
Does NOT contain Carbon-Tet

- CLEANS AND LUBRICATES
- PROVIDES LONGER LASTING PROTECTIVE FILM
- DOES NOT AFFECT ELECTRICAL PROPERTIES NOR HARM INSULATORS

NON-INFLAMMABLE TUNER CLEANER

**TUN O LUBE**

with this uniquely articulated cleaner

DESIGNED FOR ALL TUNERS

**NEW 8 OZ. ECONOMY SIZE ... \$1.98** DEALER NET

**SPECIAL 3 OZ. "CADDY SIZE" ... 98¢** DEALER NET

Write for Brochure and Guide

**CHEMTRONICS inc.**  
122 MONTGOMERY STREET • BROOKLYN 25, N. Y.

**SPRAY AID**  
Remove spray tip by pulling straight up in rotating motion. Replace with Spray Aid.

**WALL MOUNT**  
Screw mount to wall. Slip can edge into position.

Designed to meet the requirements of every specific space, budget, or decor problem—and every listening preference...



FAMOUS MEN OF MUSIC CHOOSE UNIVERSITY



**University**  
offers  
four  
ways  
to  
stereo



**1** Leading Metropolitan Opera Star Leonard Warren converted to stereo quickly, easily and inexpensively... using a compact Stereoflex-2\* "add-on" speaker with his University "Troubadour"

This approach solves many problems for those already possessing a full-range monophonic system, as well as those planning to buy one now with an eye to stereo later. Thanks to the exclusive dual voice coil woofer used in all University stereo-adapted systems, only one such woofer is needed to reproduce the combined bass below 150 cycles† of both stereo channels. Thus all three models of University "add-on" speakers provide a perfect match by direct connection to the original speaker system. Stereoflex-1\* is well suited for bookshelf installations. Stereoflex-2, with its narrow silhouette, makes a fine end table. Model SLC\* can be affixed to a wall or "lite-pole," its decorative fibreglas housing blending smartly with modern furnishings. Each can also be used with any brand monophonic system not having a dual voice coil woofer, by using a University Stereo Adapter Network Model A-1.

**2** Discriminating music lovers may also enjoy magnificent stereo by simply connecting two University "add-on" stereo speakers to a single dual voice coil woofer\* in a suitable enclosure

This approach offers great versatility. Since the woofer's position in the room is uncritical for stereo†, it may be installed wherever most convenient... in a small suitable enclosure, or in a wall, closet, etc. The two "add-on" speakers can then be placed to provide optimum stereo reproduction, without upsetting existing room decor.

**3** Noted maestro Fred Waring chose a pair of University RRL\* Ultra Linear Response speakers for his stereo system

When planning his recent cross country concert tour, *Hi Fi Holiday*, Fred Waring turned to University engineers for a compact, quality high fidelity speaker system that could overcome the acoustical deficiencies of the theatres and auditoriums in which The Pennsylvanians would be playing. The performance of the S-11 Ultra Linear Response speakers, mainstays for the system, proved so outstanding that Mr. Waring chose two of them for his own home. Two such identical speakers are an excellent stereo solution in rooms where they can be placed in reasonably symmetrical positions. All University systems are ideally suited for this purpose, because they are stereo-matched in production to within 1 db.

**4** Internationally famed violinist Mischa Elman prefers his stereo all-in-one... he selected the fabulous TMS-2\*, 'Trimensional' stereo speaker that in his words... "approaches the authenticity of concert hall performance."

A totally integrated single-cabinet system, the TMS-2 literally adds a third dimension to stereophonic sound... the perception of *depth*. Designed to utilize the acoustical properties of the surrounding walls of the room, the TMS-2 performs far beyond the scope of other single-cabinet stereo speakers. Its ingenious combination of electrical and acoustical principles permits placement in a corner or *anywhere* along a wall... lets you and any number of friends enjoy exciting stereophonic sound from almost any position in the room.




**WHICH WAY TO STEREO IS IDEAL FOR YOU?**

You'll find all the answers in University's FREE Informative guide to high fidelity stereo and monophonic speaker systems and components. Here, you'll find complete information on: how to select and place the four major types of stereo speaker systems... how to adapt your present monophonic system to stereo... how to choose a monophonic system *now* for most efficient conversion to stereo *later*... how to plan economical "do-it-yourself" monophonic/stereo speaker systems. See your dealer today or write Desk J7, University Loudspeakers, Inc., 80 So. Kensico Ave., White Plains, N. Y.

\*Trademark and Patent Pending.

†Bass frequencies below 150 cycles do not contribute to the stereo effect.
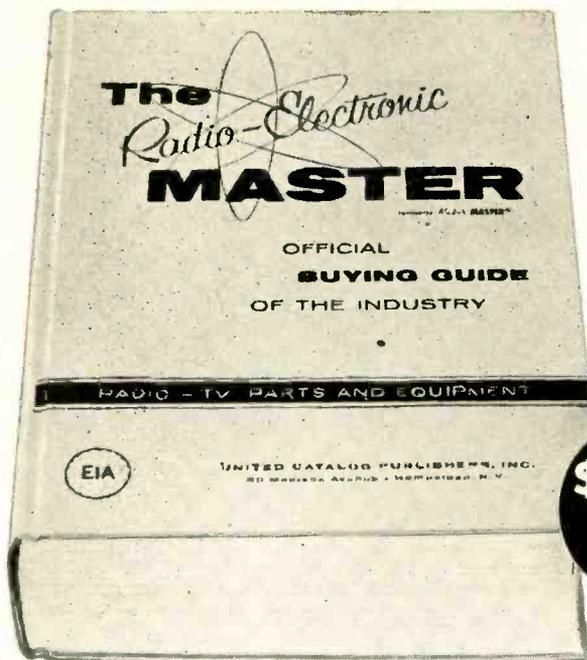
# NOW AVAILABLE at your local distributor



**1,536  
pages**

**\$3.50**  
At parts  
distributors  
\$4.50 in Canada

# 1959 RADIO-ELECTRONIC MASTER

World's largest buying guide  
of TV-Radio - Electronic - Audio Products

**1536**

pages of complete descriptions, specs, illustrations, prices

**150,000**

items including all latest products of

**350**

manufacturers systematically arranged in

**18**

product sections for easy reference

No matter what your interest is in electronics—  
The MASTER saves you time and money

### Ham or experimenter

When you buy, repair or assemble, you get the right product to do the job best because you are shopping in the electronic supermarket—The MASTER. Features descriptions and prices of receivers, transmitters, hi-fi gear, cabinets and hard-to-locate items not found in smaller catalogs.

### Serviceman

The MASTER means more profitable operation. It covers 150,000 items necessary to radio-TV-audio servicing. It offers thousands of other products that can lead to extra income in hi-fi, sound and industrial servicing. You can buy, sell and bill direct from the MASTER... it shows list prices!

### Engineer

The MASTER saves you engineering time. It is the quickest way to get current factory-accurate data on all the products needed for research, design and production. Systematically organized in 18 product sections for rapid product comparison. Minute details so necessary for specifying are included.

No matter what product or component you require...

**YOU'LL FIND IT FASTER IN THE '59 MASTER**


At your local parts distributor, or write for list



**FREE**... Valuable 24-page panel lamp chart at your MASTER distributor, or write direct enclosing 10¢ for handling.

THE RADIO-ELECTRONIC MASTER 58 Madison Avenue, Hempstead, N. Y.

### NEW TUBES & SEMICONDUCTORS (Cont'd)

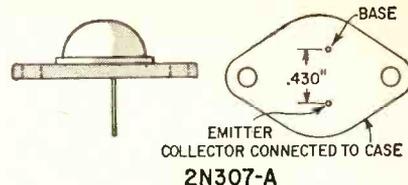

**2N307-A**

Maximum ratings for the Sylvania 2N307-A at 25°C are:


$V_{CB}$	35	
$V_{CE}$	35	( $R_{BE} = 30$ ohms or less)
$I_C$ (amps)	2	

Characteristics at 25°C are:

$h_{FE}$ (min)	20	( $V_{CE} = 1.5, I_C = 0.2$ A)
$f_{\alpha}$ (min) (kc)	3.5	( $V_{CC} = 14, I_C = 0.5$ A)
$P_g$ (typ) (db)	27	
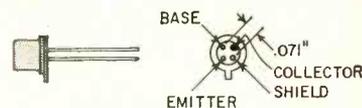
### 2N695

This Mesa type germanium p-n-p diffused-junction transistor is designed primarily for reliable operation in ultra-high-speed switching applications. The small size of junctions and internal



APPROX ACTUAL SIZE

**2N695**


leads required for uhf operation results in a serious limitation on allowable surge currents. These transistors will be damaged by voltage and current surges when plugged into live circuits.

Maximum ratings of this Motorola unit are:

$V_{CB}$	15
$V_{CE}$	12
$V_{EB}$	3
$I_C$ (ma)	20
$P_c$ (mw)	50
(derate 1 mw/°C above 50°)	
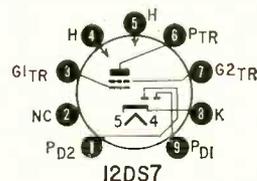
### 12DS7

The 12DS7 is a multi-unit tube of the nine-pin miniature type. It has two diodes and a high-perveance power tetrode in its envelope. It is intended



**12DS7**

for use in hybrid auto radio receivers where tube and transistor electrode voltages are taken directly from the 12-volt storage battery. In such receivers, the diodes are used for AM signal detection and the tetrode serves as a driver for the transistor af power output stage. The unit is made by RCA.

Typical operating characteristics of the tetrode unit in audio driver service are:

$V_p$ supply	12.6	
$V_p$	12.6	(obtained from plate supply through series 100-henry choke with 150-ohm dc resistance)


$V_{g1}$ supply	12.6
$V_{G2}$ supply	12.6
$R_{G2}$ (megohms)	1.8
$R_k$ (ohms)	18
$I_p$ (ma) (0 sig)	23
(Max sig)	13

NEW TUBES & SEMICONDUCTORS (Cont'd)

$I_{G1}$ (ma)	77	
$R_L$ (k ohms)		1.25
Total harmonic distortion (%)		8
Max sig out power (mw)		10
Maximum ratings of the diode sections are:		
$I_p$ (ma)	5	
$V_{intr-cath}$ (peak)	16	

21EAP4/SF21A

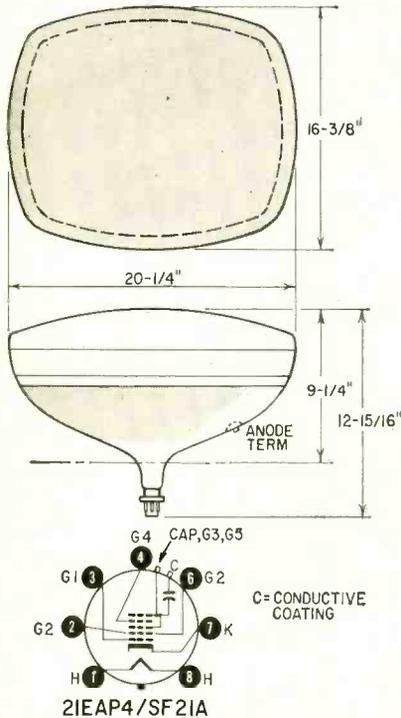An extremely short electrostatic focus and magnetic deflection, direct-view rectangular picture tube for television receivers. Overall length is only 12 15/16 inches. The heater is rated at 600 ma, 2.34 volts with controlled warmup for



series-string circuits. Metal-backed screen, straight gun requiring no ion-trap magnet, external conductive coating and glass button base are featured.

Maximum ratings of this Philco Semi-Flat picture tube in grid-drive service are (voltages positive with respect to cathode unless indicated otherwise):

$V_{anode}$	20,000
$V_{G4}$	-700 to 950
$V_{G2}$	550
$V_{G1}$ (neg bias value)	155
(neg peak value)	250
(pos bias value)	0
(pos peak value)	2
$V_{heater-cathode}$	
(htr neg respect to cath)	
(during 15 sec warmup)	450
(after warmup)	200
(htr pos respect to cath)	200

Miscellaneous

Four alloy-junction transistors for airborne, missile and other military applications have been announced by Sperry. They are the 2N1024, 2N1025, 2N1026 and 2N1027.

A group of 10-watt diffused silicon power regulators have been introduced by Texas Instruments. They come in 5% and 10% tolerances and in ratings from 22-91 volts. **END**

# NO OTHER TUBE TESTER MADE- AT ANY PRICE—can MATCH the VALUE of the CENTURY FAST-CHECK



SIZE:  
 H: 11 1/4"  
 W: 14 5/8"  
 D: 4 3/8"

Guaranteed for  
 One Full Year  
**\$6950**  
 Net

Model FC-2—housed in sturdy wood carrying case complete with CRT adapter . . . only

## 20,000 SERVICEMEN CAN'T BE WRONG!

See for yourself—AT NO RISK—why over 20,000 servicemen selected the FAST-CHECK above all other tube testers—regardless of price. With the FAST-CHECK you will make every call pay extra dividends by merely showing your customer the actual condition and life expectancy of the tube. The extra tubes you will sell each day will pay for the FAST-CHECK in a very short time.

Special compartment accommodates line cord and Picture Tube Test Adapter

### PICTURE TUBE TEST ADAPTER INCLUDED WITH FAST-CHECK

Enables you to check all picture tubes (including the new short-neck 110 degree type) for cathode emission, shorts and life expectancy . . . also to rejuvenate weak picture tubes. This feature eliminates the need of carrying extra instruments and makes the FC-2 truly an all-around tube tester.

FAST-CHECK'S low price is made possible because you are buying direct from the manufacturer.

### Just 2 settings on the FAST-CHECK TUBE TESTER tests over 650 tube types completely, accurately — AND IN SECONDS!

- **POSITIVELY CANNOT BECOME OBSOLETE**  
Circuitry is engineered to accommodate all future tube types as they come out. New tube listings are furnished periodically at no cost.
- **NO TIME CONSUMING MULTIPLE SWITCHING**  
Only two settings are required instead of banks of switches on conventional testers.
- **NO ANNOYING ROLL CHART CHECKING**  
Tube chart listing over 650 tube types is conveniently located inside FAST-CHECK cover. New tube listings are easily added without costly roll chart replacement.

### COMPARE FAST-CHECK WITH OTHER TESTERS RANGING FROM \$40 TO \$200

#### RANGE OF OPERATION

- ✓ Checks quality of over 650 tube types, which cover more than 99% of all tubes in use today, including the newest series-string TV tubes, auto 12 plate-volt tubes, OZ4s, magic eye tubes, gas regulators, special purpose hi-fi tubes and even foreign tubes.
- ✓ Checks for inter-element shorts and leakage.
- ✓ Checks for gas content.
- ✓ Checks for life-expectancy.

#### IMPORTANT FEATURES

- Checks each section of multi-section tubes and if only one section is defective the tube will read "Bad" on the meter scale
- Less than 10 seconds required to test any tube
- 41 long lasting phosphor-bronze tube sockets accommodate all present and future tube types . . . cannot become obsolete
- 7-pin and 9-pin straighteners mounted on panel
- Large D'Arsonval type meter is extremely sensitive yet rugged — fully protected against accidental burn-out
- Special scale on meter for low current tubes
- New tube listings furnished periodically at no cost
- Compensation for line voltage variation.

Other testers may have some of the above features . . . but only the FAST-CHECK has them all!

## SHIPPED ON APPROVAL FOR 10 DAY FREE TRIAL

Try the FC-2 before you buy it! No obligation to buy.

### PAY IN SMALL MONTHLY PAYMENTS

Easy to buy if you're satisfied. Pay at net cash price . . . no financing charges.

**NO MONEY REQUIRED  
WITH ORDER . . .**

### CENTURY ELECTRONICS CO., INC.

Dept. 101, 111 Roosevelt Ave., Mineola, N. Y.

Rush the FAST-CHECK for a 10 day trial period. If not completely satisfied I will return the instrument within 10 days without further obligation. If fully satisfied I agree to pay the down payment within 10 days and the monthly installments as shown. No financing charges are to be added.

Model FC-2 . . . \$69.50 — Pay \$14.50 within 10 days. Balance \$11.00 monthly for 5 months.

Name .....

Address .....

City ..... State .....


F.O.B., Mineola, N.Y.

Of All TWEETERS Tested...

RADIO SHACK'S

**\$27.50**

REALISTIC ELECTROSTAT-3

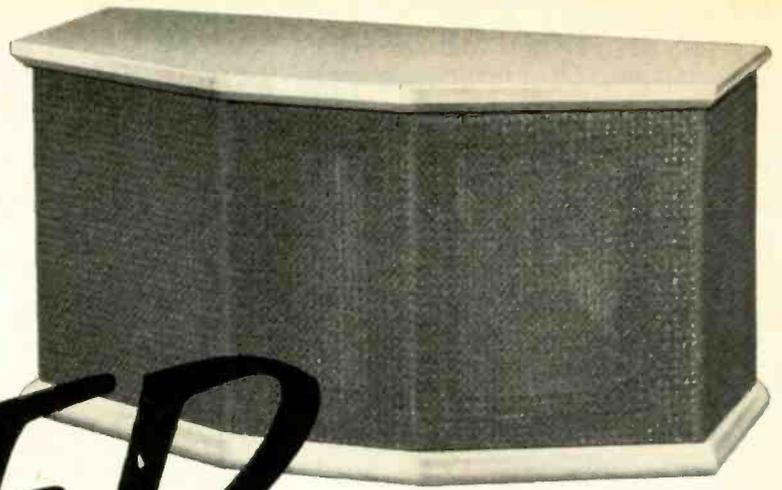

11 7/8" w 5 7/8" h 4 1/2" d  
Order No. 36CX017Y

# RATED BEST!

by national consumers' publication!  
Rated "SUPERIOR" To Tweeters  
COSTING \$150.00 and MORE!

**3 ELECTROSTATIC ELEMENTS!**




Wide 120° sound dispersion angle is attained by the exclusive Realistic three-off-set element design.

**BUILT-IN AC POWER SUPPLY!**



Provides all of the voltage necessary for true electrostatic speaker operation. Double fused for absolute safety!

**COMPATIBLE TO ANY SPEAKER!**

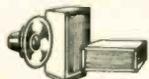

Regardless of size, shape or cost, the ELECTROSTAT-3 will measurably improve any speaker system!

**RECOMMENDED INSTALLATION ACCESSORIES FOR THE REALISTIC "ELECTROSTAT-3"**

**Crossover Network Kit**  
Includes coils, condensers and L pad. Complete with simplified assembly instructions. Ship. Wt. 2 lbs. Available for either 8 or 16 ohms. Ship. Wt. 2 lbs.  
Order No. R-4850 8 ohms .....\$4.95  
Order No. R-4851 16 ohms .....\$4.95

**University N2B Crossover Network**  
Order No. 31CX494 Wt. 2 1/4 lbs. ....\$13.72

**Mallory "L" Pad Attenuators**  
Order No. 09B803 8 ohms, 1/2 lb. ....\$2.67  
Order No. 09B882 16 ohms, 1/2 lb. ....\$2.67

REALISTIC in brand name, REALISTIC in price, REALISTIC in its smooth performance up to and *beyond* the range of human hearing, the fabulous Electrostat-3 is nationally recognized as "tops" among tweeters. Like all Realistic components—speakers, tuners, amplifiers, turntables—the Electrostat-3 is designed by Radio Shack audio engineers and *sold only by Radio Shack* by mail-order or through its three stores. Realistic products bring music lovers "wired hi-fi" at or below "kit prices" and without sacrifice of any *essential* physical or electrical functions!

**IMPROVES EVEN THE FINEST SPEAKER SYSTEMS!**

Designed to fill a void in the reproduction of high fidelity sound, the Realistic ELECTROSTAT-3 will extend the range of any speaker or speaker system to beyond 25,000 cycles. Its unbelievably wide sound dispersion angle opens a new world of acoustic brilliance!

When used with any of the finer high compliance speaker systems such as the KLH, Acoustic Research or the Realistic "Delta-7", the ELECTROSTAT-3 adds a smooth and silky high frequency response from 5000 cycles to the upper limit of audibility . . . and beyond!

**EASY TO CONNECT AND USE!**

The ELECTROSTAT-3 comes complete with simplified installation instructions for any speaker or system. All that is necessary is to plug in the AC power cord, connect an 8 or 16Ω crossover network, (see Realistic Crossover Kit at left) and enjoy the finest high frequency response ever heard! An 8Ω, 5000 cycle crossover network is recommended for the AR-1, AR-2 and KLH-6, and a 16Ω, 5000 cycle network for the KLH-4 and the Realistic "Delta-7".



**NO DELAY!**  
We Ship the Same Day  
We Receive Your Order!



**FREE!**

NEW 1959 CATALOG

- 232 brand new pages!
- 84 Hi-Fi-Stereo systems!
- 30,000 electronic items!

## RADIO SHACK CORPORATION

730 Commonwealth Ave., Boston 17, Mass.

167 Washington St., Boston 8, Mass.

230-240 Crown St., New Haven 10, Conn.

# OTHER RADIO SHACK EXCLUSIVE

## BEST BUYS!

### REALISTIC DELTA-7 SPEAKER



Ideally suited for use with the highly recommended Realistic Electrostat 3 for full range coverage 30-25,000 cycles. Hand rubbed mahogany or oak cabinet 24 1/2 x 13 1/4 x 11" deep. 16Ω.

\$8 Down  
\$7 Monthly **\$79.95**


### REALISTIC 15-WATT AMPLIFIER



Full 15 watts — 18-30,000 cps ±1 db @ 1 watt, 20-20,000 cps ±1 db @ full output. Wired for stereo. Gold metal case 9 5/8 x 4 3/8 x 6 1/8". Reg. \$66.95.

\$5 Down, \$5 Monthly **\$39.95**

### REALISTIC FM-AM TUNER

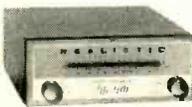

Loise noise cascode FM front end; sensitivity 2 uv for 30 db quieting. Ultra quiet AM. Freq. resp. 20-20,000 cps ±1 db. List \$95.

\$6 Down, \$6 Monthly **\$57.00**

### REALISTIC FM-II TUNER



Sensitivity: 3 uv for 30 db quieting. Freq. resp. 20-20,000 ±1 db. Gold cabinet: 9 5/8 x 4 3/8 x 6 1/8". List \$67.50.

\$5 Down, \$5 Monthly **\$39.50**

### REALISTIC "SOLO" SPEAKER



Genuine mahogany finish on 4 sides make it ideal for stereo twins. Dual-cone, 50-14,000 cps, in solid, tuned enclosure with duct-type vent. Matches 4-8 ohms. 14 1/2 x 11 x 10 1/2".

**\$15.95**

**RADIO SHACK CORPORATION, Dept. C**  
730 Commonwealth Avenue, Boston 17, Mass.

Please send me

Quan.	Realistic Desc.	Wt.	Order No.	Sale
	Electrostat 3	7 lbs.	36CX017Y	\$27.50
	Delta-7 Speaker	45 lbs.	RX-7065Y	79.95
	Solo Speaker	12 lbs.	RX-9036	15.95
	15-watt Amplifier	15 lbs.	33CX005Y	39.95
	FM-AM TUNER	15 lbs.	36CX023Y	57.00
	FM TUNER FM-II	9 1/2 lbs.	36CX888-2Y	39.50

Radio Shack 1959 Hi-Fi Buying Guide

Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# NOTEWORTHY CIRCUITS

## HEATER-B-PLUS SWITCHING

On certain types of equipment, amateur transmitters and other units using mercury-vapor rectifiers, filaments should be switched on before the B plus and off after the B plus. With the circuits shown here you

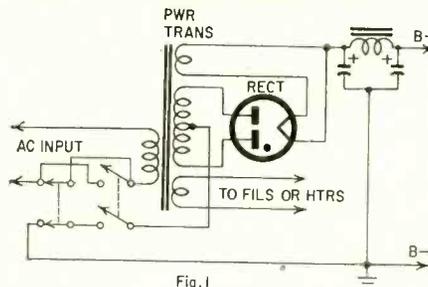


Fig. 1

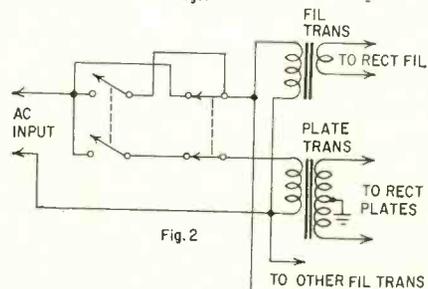


Fig. 2

can't do it any other way. No matter which switch you turn on first, the filaments go on. And no matter which switch is turned off first, it turns off the B plus. Fig. 1 is for supplies with a single power transformer and Fig. 2 for separate plate and filament supplies. You can stop worrying about hitting the wrong switch first and losing an 83 or a couple of 866's.—Leslie Davis

## THE DOT MAKER


Recently, while checking a transmitter "on the air" it became apparent that an automatic dot maker would be an invaluable instrument to have around. On phone it is a violation of FCC rules to leave an unmodulated carrier on for more than about 1 minute. The same ruling probably holds for CW transmitters, not to mention the annoyance and interference to other stations.

As a result the Dot Maker was developed. It is extremely simple to construct and all parts are readily available. Two G-E 2N107 p-n-p transistors are used. The first (V1) is a blocking oscillator having a repetition rate of from 1 to about 40 pulses per second. Referring to the diagram, the combination of R1, R2 and C1 establishes the pulsing frequency. Potentiom-
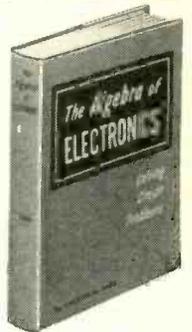
# Now! SOLVE CIRCUIT PROBLEMS FAST!

Goodbye to trial-and-error methods.

Every circuit calculation you need can now be done accurately with  
**THE ALGEBRA OF ELECTRONICS**



YOU'LL BE AMAZED

at how easy it is to figure resistances, load inductances, impedances, etc. for ANY part of ANY electronic circuit. With this new book, THE ALGEBRA OF ELECTRONICS, you will quickly gain the tools, techniques and shortcuts needed.

## Three Great Books in One!

First, it's a textbook. All practical mathematical techniques explained clearly step-by-step; easy to follow by those with no more math training than high-school algebra and simple differential calculus.

Second, it's a handbook. Graphs and tables answer common electronic problems for those not wishing to work out complex derivations themselves.

Third, it's a review. Every equation is discussed, along with its practical on-the-job applications. 100 problems are shown with methods and answers provided.

**THE ALGEBRA OF ELECTRONICS** was written by Chester H. Page, Consultant to the Director of the National Bureau of Standards. Dr. Page discusses basic laws and fundamental principles, practical methods of solving simultaneous equations. He develops elementary Fourier waveform analysis, shows effects of frequency selectivity, modulation, and analyzes tubes, transistors and power supplies.

## Try It FREE for 10 Days

Whether you're a repairman, technician, or engineer, you'll find **THE ALGEBRA OF ELECTRONICS** both profitable and interesting. Send coupon for a FREE 10-DAY EXAMINATION. No obligation — unless you want to keep the book. Mail coupon today to

**D. VAN NOSTRAND CO., INC.**

Dept. 181A,  
Princeton, N.J.

(Established 1848)

## 127 TOPICS

340 Pages  
252 Illustrations

NonLinear Resistance  
Network Topology  
Mesh Currents  
Kirchoff's Law  
Voltage Variables  
Triangularization  
Simultaneous Equations  
Kramer's Rule  
Thevenin's Theorem  
Wheatstone Bridge  
Conjugacy  
Black-Box Variables  
Image Impedances  
Attenuators  
Capacitance  
Dielectrics  
Sinusoidal Voltage  
Energy Storage  
Series-Tuned Circuits  
Series Resonance  
Complex Phasors  
Mutual Inductance  
Transformers  
Critical Coupling  
F-M Discriminator  
Impedance Matching  
Hyperbolic Functions  
Diodes  
Amplifiers  
Transistors  
Thermal Noise  
Demodulation  
—many more

**D. VAN NOSTRAND CO., Dept. 181-A  
PRINCETON, N.J.**

(In Canada: 25 Hollinger Rd., Toronto 161)

Send for free examination—**THE ALGEBRA OF ELECTRONICS**. If I don't feel it can make electronic calculations clearer, easier, and faster, I may return it within 10 days, owe nothing. Otherwise, I will pay \$2.75 down, plus small delivery cost, and \$3 per month for 2 months.

Name \_\_\_\_\_ (Please Print Plainly)

Address \_\_\_\_\_


City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

**SAVE!** Enclose \$8.75 WITH coupon and we will pay all shipping costs. Same ten-day money-back privilege.

# The Most Advanced TV ANTENNAS in the World!

## TRIO®

### ZEPHYR AND COLOR SERIES ANTENNAS

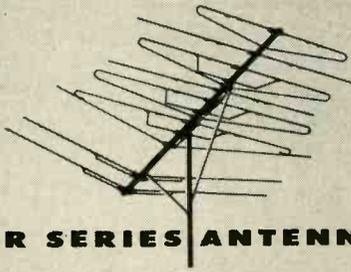

## Look for these 4 Great Features in 1959

### Wing Dipole

Today's most powerful dipole! Contains three active elements on the high-forward Vee to the low band section—plus integrated director.

### Wing Director

Today's most powerful director! A composite director designed to obtain results from the powerful Wing Dipole.

### no-strip load-in connector

Requires no stripping, no soldering, or wire holders—holds the complete insulated wire.

### dyna-coil phasing

Increased performance from uniform transmission of signal strength of each active dipole in a multi-dipole system—AND MAKES POSSIBLE COMPLETE FACTORY ASSEMBLY.

## Choose from... TRIO'S COMPLETE LINE

- COLOR ROYAL—The ultimate in color television reception—or black and white.
- ZEPHYR ROYAL—Extraordinary power and sensitivity.
- ZEPHYR PIONEER—For extreme distance.
- COLORITE—For color and black and white in areas formerly using conicals.

Sharpshooters, Conicals and Yagis

Patents: U.S. 2772413—Canada 541670

Copyright 1958, Trio Mfg. Co.

**TRIO®** Manufacturing Company GRIGGSVILLE, ILL.

SAVE  
TIME  
with

**SENCORE®**

NOW —  
Check Vibrators  
in ANY  
Tube Checker

## 2 Adaptors in 1 SENCORE "VIBRA-DAPTOR"

Checks Both Three and Four Prong Vibrators

- Merely plug into any tube checker. Set for 6AX4 (or 6SN7) for 6 Volt Vibrators and 12AX4 (or 12SN7) for 12 Volt Vibrators. • Two lamps viewed through top of adaptor indicate whether or not Vibrator needs replacing. Rugged—Made of steel. • Replaceable but unbreakable #51 indicating Lamps. Operates easily with Sencore LC-3 Leakage Checker. Complete instructions screened on front.

In stock at your local parts distributor.

SENCORE CORP. 121 Official Rd., Addison, Ill.




MODEL VB-2  
\$275  
DEALER NET

See other SENCORE ads in this issue.
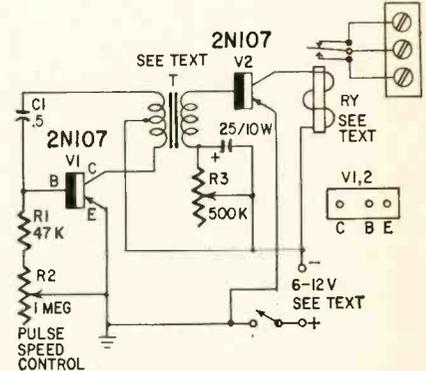
## NOTEWORTHY CIRCUITS (Continued)

eter R2 is the actual speed control and this is mounted on the front panel along with the on-off switch.

Transformer T can be almost any audio transformer designed for plate-to-push-pull grids. In the original model a Stancor A-53-C was used, although specially designed transistor transformers such as the Argonne AR-102 work equally as well. The second stage



using a 2N107 transistor is an amplifier and is used to increase the pulsating current to a value suitable for relay operation. Resistor R3 in the base circuit of the amplifier controls the actual current flowing through the relay. As the 2N107 can operate with 5-ma collector current, any radio-control or plate-circuit type relay having a coil resistance of up to 10,000 ohms and operating on a current of less than 5 ma could be used. The relay in actual use is a surplus unit which came out of a Beacon receiver. It has a coil resistance of 10,000 ohms and operates on only 0.4 ma! Another relay that has been used in this unit is an Advance plate-circuit type having a coil resistance of 2,500 ohms and an operating current of 2 ma. As the 2N107 collector current kicks downward on each pulse, use a spdt relay so that each pulse can either make or break an external circuit. For powering the Dot Maker any battery voltage between 6 and 12 volts may be used, depending upon the relay.


To operate the Dot Maker set potentiometer R2, the speed control, to approximately mid-range. Turn on the power switch and adjust potentiometer R3 until the relay starts operating with each pulse. A 5-ma meter can be connected between the bottom of the relay and the battery's negative terminal to check relay or collector current. Always use the amount of relay current needed for reliable relay operation, but don't exceed 5 ma. There is nothing critical about wiring and, as long as the circuit is wired correctly, it should work. Sometimes, reversing the relay leads will give smoother operation. It may also be necessary to reverse the transformer's secondary leads for improved operation.

Since building the Dot Maker, several other applications have come to mind. As mentioned before, it could be used to key a transmitter carrier, or the clicking of the relay may be used to modulate a phone transmitter. The relay could also key an audio oscillator

which, in turn, may be used for modulation purposes. It might also be used to flash lights in a display or it may serve as a metronome. More uses will soon become apparent to the builder.  
—Mitchel Katz, W2KPE
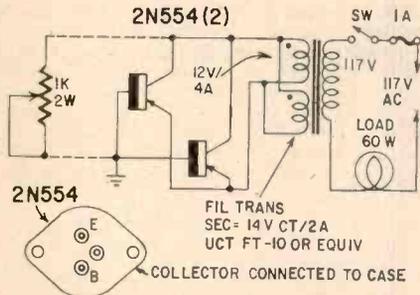
### TRANSISTOR POWER CONTROL

This circuit controls power loads over a wide range from an input resistor rated at 2 watts or less. In effect, the input resistance is amplified by the transistor's current gain, nominally 50,



so that 2 watts dissipation in the input results in 100 watts on the load.

Small motors—sewing machine, mixers, small tools, appliances—are smoothly controlled. The system is applicable to remote control since very light connecting wires may be used. In some cases a single wire with ground return is effective.

In designing for higher powers, more 2N554's may be paralleled and heavier transformers used. Estimate transistor current at about 3 amps per unit on the 12-volt side. Transistors should be mounted on an aluminum chassis or other heat sink.—*Motorola Semiconductors* END

### 50 Years Ago

In Gernsback Publications


#### HUGO GERNSBACK, Founder

Modern Electrics	1908
Wireless Association of America	1908
Electrical Experimenter	1913
Radio News	1919
Science & Invention	1920
Television	1927
Radio-Craft	1929
Short-Wave Craft	1930
Television News	1931

Some larger libraries still have copies of Modern Electrics on file for interested readers.
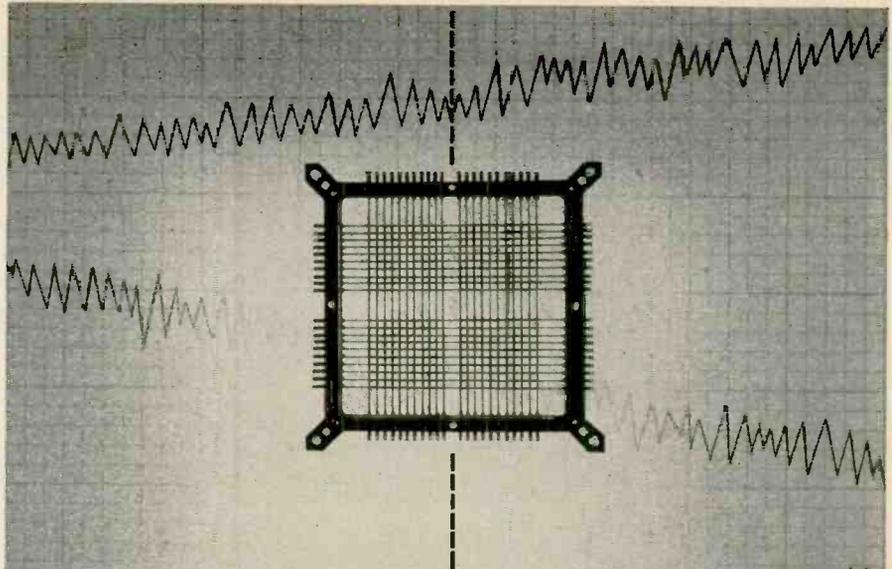
#### In January, 1909, Modern Electrics

- Wireless "Round the World," by Earle William Gage.
- Wireless Association of America.
- New Selenium Cell, by the Paris correspondent.
- Enameled Wire.
- High Speed Phototelegraphy.
- Telescopic Detector.
- The Carborundum Detector, by S. W. Newsom.
- Wireless Troubles. Part II: Testing and Operation of Transmitting Instruments, by L. Spangenberg.
- New Detector.
- Wireless Hints, by Percy E. Palmer.
- Aerophone Tests Before British Admiralty, by Dr. Lee de Forest.
- Carborundum, by Lewis W. Klopper.
- Modern Wireless Instruments.
- Thermoelectric Detectors.
- Walking Wireless Station.



## COMMUNICATED DATA

Modern military weapons systems require instantaneous computation of data... Burroughs, consistent with its recognized leadership in equipment skills and manpower, is providing the answers for complex military weapons systems through automatic suprahuman computation.

The qualified electronics technician who seeks in his work a sense of gratification for a challenge imaginatively met... will find that challenge and its reward in a career in digital computation with Burroughs Military Field Service Division.

#### Add up these facts

1. Formal 22 week training program in Data Processing Systems, PLUS
2. Starting salaries commensurate with ability and experience, PLUS
3. Full salary during entire training program, PLUS
4. Advancement opportunities based on individual performance, AND
5. Fine fringe benefits including educational assistance (in addition to above training), PLUS
6. Nationwide field assignments after completion of training program.

If you are a graduate of an accredited Technical School and/or have military training in radar or communications equipment, plus at least 2 years' experience in electronics, you are invited to address your inquiries to Personnel Department, MILITARY FIELD SERVICE DIVISION, 511 North Broad Street, Philadelphia 23, Pa.



## Burroughs Corporation

"NEW DIMENSIONS" / in electronics and data processing systems

**RADIO and ELECTRONICS TRAINING AT HOME**

**BUILD 16 RADIO**

**CIRCUITS with DELUXE  
1959 Progressive  
RADIO "EDU-KIT"®**

Reg. U.S.  
Pat. Off.

**PRACTICAL only  
HOME RADIO COURSE**  
**\$22.95**



**NOW INCLUDES**

- ★ 12 RECEIVERS
- ★ TRANSMITTER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packed

**FREE EXTRAS**

- SET OF TOOLS • RADIO & ELECTRONICS TESTER • ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • MEMBERSHIP IN RADIO-TV CLUB; CONSULTATION SERVICE • HI-FI GUIDE • QUIZZES • TV BOOK • FCC AMATEUR LICENSE TRAINING • RADIO BOOK • PRINTED CIRCUITRY • PLIERS-CUTTERS • ALIGNMENT TOOL • WRENCH SET • CERTIFICATE OF MERIT • VALUABLE DISCOUNT CARD

**WHAT THE "EDU-KIT" OFFERS YOU**

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs. Code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and layout radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. Today it is no longer necessary to spend hundreds of dollars for a radio course. You will receive a basic education in radio, worth many times the small price you pay, only \$22.95 complete.

**THE KIT FOR EVERYONE**

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world. Many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. Every step is carefully explained. You cannot make a mistake.

**PROGRESSIVE TEACHING METHOD**

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first section you will enjoy listening to regular broadcast stations, learn theory, practice testing and troubleshooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are sixteen Receiver, Transmitter, Code Oscillator, Signal Tracer and Signal Injector circuits. These are not unprofessional "breadboard" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily-learned radio course, the "Edu-Kit" includes practical work as well as theory, troubleshooting in addition to construction; training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material, ranging from simple circuits to well-advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

**THE "EDU-KIT" IS COMPLETE**

You will receive all parts and instructions necessary to build 16 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hookup wire, solder, etc.

In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional soldering iron and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to the F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, and a High Fidelity Guide and Quiz Book. Everything is yours to keep.

J. Statistis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The 'Edu-Kit' paid for itself. I was ready to spend \$240 for a course, but I found your ad and sent for your Kit."

**UNCONDITIONAL MONEY-BACK GUARANTEE**

The Progressive Radio "Edu-Kit" has been sold to many thousands of individuals, schools and organizations, public and private, throughout the world. It is recognized internationally as the ideal radio course.

By popular demand the Progressive Radio "Edu-Kit" is now available in Spanish as well as English.

It is understood and agreed that should the Progressive Radio "Edu-Kit" be returned to Progressive "Edu-Kit" Inc. for any reason whatever, the purchase price will be refunded in full, without quibble or question, and without delay.

The high recognition which Progressive "Edu-Kits" Inc. has earned through its many years of service to the public is due to its unconditional insistence upon the maintenance of perfect engineering, the highest instructional standards, and 100% adherence to its Unconditional Money-Back Guarantee. As a result, we do not have a single dissatisfied customer throughout the entire world.


**ORDER FROM AD—RECEIVE FREE BONUS RESISTOR AND CONDENSER KITS WORTH \$7.00**

- Send "Edu-Kit" Postpaid. I enclose full payment of \$22.95.
- Send "Edu-Kit" C.O.D. I will pay \$22.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."


Name \_\_\_\_\_  
Address \_\_\_\_\_

**Progressive "EDU-KITS" Inc.** 1186 Broadway, Dept. 148G  
Hewlett, N. Y.

**On  
the  
Market**

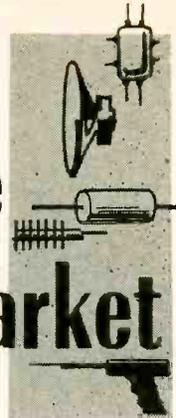

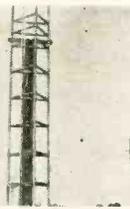**CRANK-UP TOWERS, H series.** Available in 3 sections. No guy wires needed. 14-gauge tubular aircraft steel, 4,200-lb-




test aircraft cable. To 400 feet. Hot-dipped galvanized finish or enamel. 12- and 18-inch triangular construction. 1-inch tubing. —Tele-Vue Towers Inc., 701 49 St. S., St. Petersburg, Fla.

**TAPE RECORDER, model 250.** 3-speed (1 7/8, 3 3/4 and 7 1/2 ips). Pushbutton controls. Solenoid-actuated automatic shut-off stops machine at end of reel and returns controls to neutral position. Dual-cone 6-




inch speaker with 3 1/2-inch tweeter. Distortion less than 2%. Frequency response 50-15,000 cycles. Output jacks for external speakers and amplifiers. High- and low-level inputs. Digital counter. Record-level indicator. —Telectrosonic Corp., 35-18 37 St., Long Island City 1, N. Y.

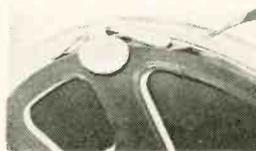**TAPE CLIP, Reel-Neat.** Ends tape spilling. Polished stainless




steel clip snaps onto tape reel, keeping it neatly wound. —Toycro Products, Audio Div., 1712 W. Florence Ave., Los Angeles 47, Calif.

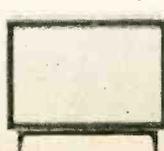**SPEAKER ENCLOSURES, Urban B-305 (shown) and B-302A.** Modern design. Infinite



baffle. B-305 is 2-woofer 3-way system for 30 watts or more, measures 36 x 20 x 30 inches. B-302A accommodates 1-woofer 3-way system for minimum of 20 watts and is 24 x 20 x 30 inches. Walnut, mahogany, ebony or unfinished. —R. T. Bozak Sales Co., Box 1166, Darien, Conn.

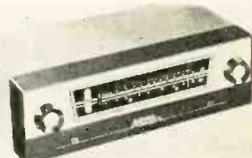**AM-FM TUNER, Model 561.** Flywheel tuning. Feather-ray indicator. Tuned rf stage. Fos-



ter-Seely discriminator. Multiplex jack. Built-in antenna. Sensitivity 2 μv for 20-db quieting on FM. 30 μv for 20-db signal-to-noise ratio on AM. Frequency response 20-20,000 cycles on FM, 20-7,500 on AM. —J. W. Miller Co., 5917 S. Main St., Los Angeles 3, Calif.

**PHONO OSCILLATOR, Stereo Bug model SB-201** adds second channel to any record player for stereo discs. Wireless system uses any broadcast-band radio




as second-channel amplifier-speaker. Battery-operated. Ceramic stereo cartridge required. —Stereo-Ette Co., 4908 N. Lincoln Ave., Chicago 25, Ill.

**STEREO REMOTE CONTROL, model RG-1000.** Sets channel balance and volume from as far as 30 feet from amplifier. Dual plugs fit in amplifier's tape output jacks. May also be used as volume control



with monophonic amplifier and as volume-balance control with pair of monophonic amplifiers. —General Electric Co., Specialty Electronic Components Dept., W. Genessee St., Auburn, N. Y.

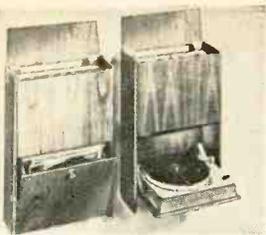**WALL-MOUNTED STEREO.** Music Wall cabinets, available separately or as matching complete stereo system, house DB 212 stereo dual 12-watt preamp-amplifier and stereo phono in



basic unit, **ST 662 AM-FM** stereo tuner and record storage space in companion unit.—**David Bogen Co.**, Paramus, N. J.

**STEREO PICKUP**, London-Scott type 1000 matched stereo arm and magnetic cartridge. Tip



mass less than 1 mg. Compliance  $3.5 \times 10^{-6}$  cm/dyne. Frequency response 20-20,000 cycles  $\pm 2$  db. Output 4 mv. Length of arm 12.5 inches from pivot to stylus. Height adjustable from 1 $\frac{1}{2}$  to 2 $\frac{1}{2}$  inches above mounting board.—**H. H. Scott Inc.**, 111 Powdermill Rd., Maynard, Mass.

**STEREO AMPLIFIER**, Knight KN-720 Bantam. Output 10 watts per channel. Full control facilities for stereo and monophonic. Dc preamp filaments. Hum-balance control. 2 ac out-



lets. Harmonic distortion 1% at 1,000 cycles at full output. Hum 70 db below full output, each channel. Response 20-20,000 cycles  $\pm 1$  db. 6-position selector knob. Slide switches for input balance, stereo reverse, rumble and scratch filters.—**Allied Radio Corp.**, 100 N. Western Ave., Chicago 80, Ill.

**STEREO AMPLIFIER**, Stereo-hi-phonics LA-90. Complete control center has inputs for



dual tuner, all phono cartridges, tape head and outputs for dual speakers and tape monitor. Stereo-monaural switch. Separate level and balance controls for each channel. Channel-reversing and speaker-phasing switches. 14 watts output per channel at 2-mv sensitivity on tape or phono inputs. Frequency response 20-20,000 cycles.—**Lafayette Radio**, 165-08 Liberty Ave., Jamaica 33, N. Y.


**STEREO AMPLIFIER**, model SM-245. Complete stereo con-



trol system. Dual 20-watt. Automatic shutoff position on power

switch turns off entire system after last record has played. Balance control, reverse switch, dual microphone inputs for stereo recording plus low-impedance and dual tape outputs for tape recording. Stereo or mono operation through both speaker systems. Fletcher-Munson compensation. 6 inputs. Cathode-follower tape output. Frequency response  $\pm 1$  db 20 to 20,000 cycles. Harmonic distortion less than 1%, IM less than 1.5% at full output. 11 tubes plus rectifier.—**Pilot Radio Corp.**, 37-50 36 St., Long Island City 1, N. Y.

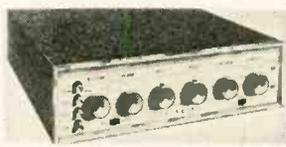**STEREO AMPLIFIER**, model S-5000. Dual 20-watt amplifier and preamp with complete control facilities. Reverse and phase-inversion switches. Monaural operation uses both chan-



nels. Response 20-20,000 cycles  $\pm \frac{1}{2}$  db at 20 watts. IM distortion 1 $\frac{1}{2}$ % at full power. Cathode-follower recording outputs. 11 tubes plus selenium rectifier.—**Sherwood Electronic Labs Inc.**, 4300 N. California Ave., Chicago 18, Ill.

**STEREO PHONO**, Trixtereo portable, manufactured by Trix Electrical Co. of London. Record player with 2 matched full-




range speakers in separate detachable enclosures. Double-channel 8-watt amplifier. Garrard stereo cartridge.—**Ercona Corp.**, Electronic Div., 16 W. 46 St., New York 36, N. Y.

**REMOTE VOLUME CONTROL** easily attached to TV or radio receiver for devotees of



late night listening and for the hard of hearing. Earphone, 2 phone jacks, volume control, 20 feet of cable.—**Argonne Electronics Mfg. Co.**, 165-11 South Rd., Jamaica 11, N. Y.

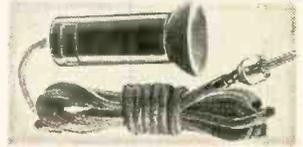**TELEPHONE PICKUP**, model M-133. Detects both sides of telephone conversation for use in



## Get This Valuable Book

# FREE



Just For Examining **COYNE'S** New Set

## "Applied Practical Radio-Television"

on **7 DAY FREE TRIAL!**

**NOW!**

### 7 BIG BOOKS

IN ONE GREAT SET!



FREE!

5 Years Of Valuable Supplements



With your set you also get Coyne's annual Supplement Service FREE for 5 years. Keeps your set up-to-date on everything that will be new in radio, television, electronics and electricity.

**SEND NO MONEY!** Just mail coupon for 7-volume set on 7 days free trial. We'll include book of 150 TV-Radio Patterns & Diagrams. If you keep the set, pay \$3 in 7 days and \$3 per month until \$27.25 plus postage is paid. (Cash price, only \$24.95). Or you can return the library at our expense in 7 days and owe nothing. **YOU BE THE JUDGE.** Either way, the book of TV-Radio Patterns is yours **FREE** to keep! Offer is limited. Act **NOW!**

**FREE BOOK—FREE TRIAL COUPON!**

**Educational Book Publishing Division**  
**COYNE ELECTRICAL SCHOOL, Dept. 19-T1**  
 1501 W. Congress Pkwy., Chicago 7, Ill.

YES! Send 7-Volume "Applied Practical Radio-Television" for 7 days FREE TRIAL per your offer. Include TV-Radio Patterns & Diagram Book FREE.

Name ..... Age .....

Address .....


City ..... Zone..... State.....

Where Employed .....

Check here if you want library sent C.O.D. You pay postman \$24.95 plus C.O.D. postage on delivery. 7-day money-back guarantee.


tape recording or for amplification (by any amplifier with magnetic input). Suction cup holds pickup firmly to receiver. 6-foot shielded lead with phono plug. 5/8 inch in diameter, 2 inches long.—**Olson Radio Warehouse**, 260 S. Forge St., Akron, Ohio.

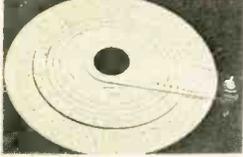**CIRCULAR SLIDE RULE**, *Dial-O-Matic*. Adds and subtracts scale lengths automatically. Log scales read from 10<sup>10</sup>



to 10<sup>-10</sup> with adjacent reciprocal scales. Face of rule carries L, K, A, DI, D, C, I.L., LL<sub>2</sub>, LL<sub>3</sub> and LL<sub>4</sub>; back carries T, ST, S, D, SH and TH scales. Cursor-rotor-stator cooperation simplifies calculation.—**Eckel Co.**, 31 St. Joseph St., Arcadia, Calif.

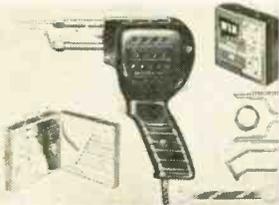**SOLDERING-GUN KIT**, model 250K. Heavy-duty model 250 packed in metal carrying case. Heats in 5 seconds, has rigid tip, trigger switch, built-in spot-



light. Kit contains 25-X-20 ferrous alloy soldering tip, 25-C-1 cutting tip for plastic and vinyl tile, 25-F-33 flat iron tip for removing dents and scratches from furniture, 5-foot roll of rosin-core solder, double-end wrench.—**Wen Products Inc.**, 5806 Northwest Hwy., Chicago 31, Ill.

**SOLDERING IRON**, industrial type, controlled heat, with *Magnastat* temperature controls inside soldering tip. Continuous precise temperature. Model TC-40 is 40-watt iron; TC-60, 60 watts; TC-120 for heavy-duty



jobs. Lightweight, scientifically balanced.—**Weller Electric Corp.**, 601 Stone's Crossing Rd., Easton, Pa.


**CARTRIDGE TOOL**, G-C *Mini-Hold*. Specially designed screwdriver for replacing phono cartridges has device to grip



screw and hold it in place while shaft turns it out. No. 9346 (3 3/4 inches long) in use reduces in size to 2 7/8 inches. No. 9347 reduces from 7 to 6 3/4

inches.—**General Cement Mfg. Co.**, 400 S. Wyman St., Rockford, Ill.

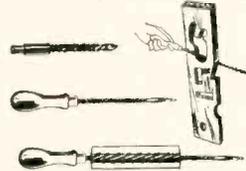**"STICKLEBACK" TOOLS**. Can be used to saw, drill or rout. Cut any size or shape hole




in wood, plaster, plywood, plastic or masonite. Available as hand tools—*Drillsaws* and *File Rasps*—and as *Drill Routers* to fit 1/4-inch chuck for hand drills and drill presses.—**Walsco Electronics Mfg. Co.**, 100 W. Green St., Rockford, Ill.

**DISPLAY PANEL LIGHT**, *Transelec Echo-Lite*. Combines



pushbutton switch and neon lamp. Bifurcated contacts and NE-2E bulb which maintains fixed position relative to lens. Available in 6 models, miniature unit offers independent or common lamp and switch connections with series resistors in either or both lamp and switch circuits.—**Transistor Electronics Corp.**, 3357 Republic Ave., Minneapolis 26, Minn.

**GRID-DIP METER**, *Eico model 710*. Kit or factory-wired. Vfo with microammeter in grid circuit. Sensitivity control and phone jack to facilitate zero-beat listening. 7 ranges with precalibrated coils supplied. Frequency range 450 kc-250 mc. Meter movement 500 μa. Plug-in coils color-coded, accurate with-

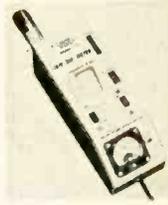

in 0.5%. Tuning capacitor planetary drive with 1:7 ratio. Drum rotates 340°. 117 volts ac.—**Electronic Instrument Co.**, 33-00 Northern Blvd., Long Island City 1, N. Y.

**TRANSISTOR TESTER**, model 690-A. Positive leakage and gain tests for p-n-p and n-p-n types. Measures dc beta from 5 to infinity. Exact test for shorts and leakage, forward and reverse leakage of diodes. Separate "calibrate" and "gain" buttons. Single-switch selection



Cut Down Call Backs ...

INSTALL A **G-C WUERTH**

**SURGISTOR**

ON EVERY SERVICE CALL

Stops harmful voltage surges to picture and radio tubes. Sell your customers tripled tube life and you'll profit on each installation.

Simply connect directly into power line. Functions like a combination resistor-relay to preserve electrolytic capacitors, dry disc rectifiers, transformers, pilot bulbs and other components as well as tubes.

G-C Wuerth No. 5301 ... For Black & White TV ..... List \$1.65

G-C Wuerth No. 5302 ... For Color TV Sets ..... List \$1.95

Available right now from your local electronics parts distributor or write direct to:

**G-C ELECTRONICS MFG. CO.**

division of G-C TEXTRON INC.  
Western Plant: Los Angeles 18, Calif.  
Main Plant: ROCKFORD, ILLINOIS, U.S.A.

"Eureka! I've at last developed one that grows JENSEN NEEDLES!"

**EASIER, QUICKER**

**BIG PROFIT TV REPAIR**

with **TEL-A-TURN**

**TV SERVICE CRADLE**

**PAYS FOR ITSELF IN A VERY SHORT TIME**

TEL-A-TURN simplifies handling of TV chassis and speeds the output of repair jobs. It eliminates struggling with heavy sets, prevents breakage and damage. May be used as portable bench for "in-the-home" repairs. Holds chassis up to 200 lbs. and 9" to 25" wide. Built in speaker, electric outlets, cheater cord, adjustable lamp, pilot light and switch.


**SEE IT AT YOUR JOBBER OR WRITE TODAY FOR DETAILS!**

Fully descriptive, illustrated folder tells how you can make more profit for only pennies a day with low cost TEL-A-TURN. Learn how much faster and easier you can do the job and how this practical service cradle pays for itself in bigger repair profits. Don't delay. Act now. If your jobber cannot supply you, write Department RE-19.

**ROGERS** MANUFACTURING CO.  
LINDSEY, OHIO, U.S.A.
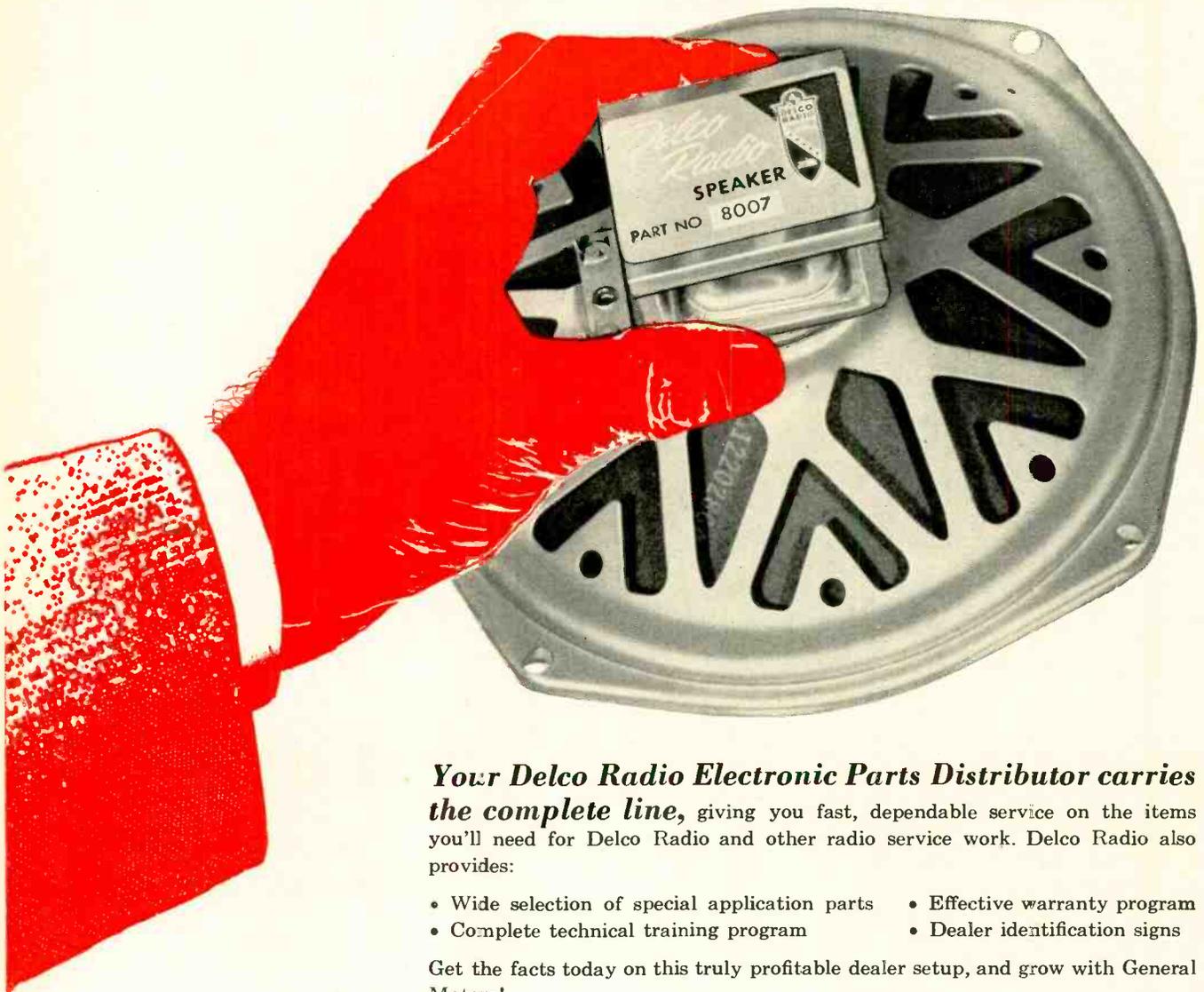
# Use Delco Radio Service Parts!

8-inch "Hi-Fi" speaker, No. 8007 offers the most highs, the most lows, the most watts in a medium-price speaker. Designed for replacement use and high fidelity audio systems.



*Your Delco Radio Electronic Parts Distributor carries the complete line, giving you fast, dependable service on the items you'll need for Delco Radio and other radio service work. Delco Radio also provides:*

- Wide selection of special application parts
- Complete technical training program
- Effective warranty program
- Dealer identification signs





Get the facts today on this truly profitable dealer setup, and grow with General Motors!

Available everywhere through Electronic Distributors associated with ...




## DELCO RADIO

DIVISION OF GENERAL MOTORS, KOKOMO, INDIANA

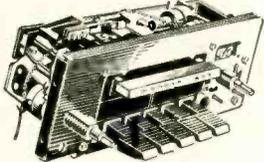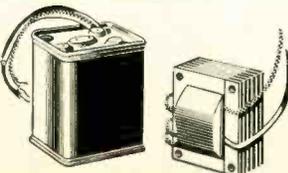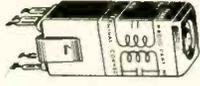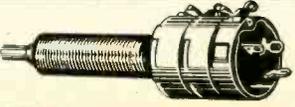 <p><b>TRANSISTORS</b></p>	 <p><b>TUNER PARTS</b></p>	 <p><b>TUBES</b></p>	 <p><b>IRON CORES</b></p>
	 <p><b>TRANSFORMERS</b></p>	 <p><b>COILS</b></p>	 <p><b>RESISTORS</b></p>
		 <p><b>VIBRATORS</b></p>	 <p><b>CAPACITORS</b></p>
			 <p><b>CONTROLS</b></p>

of transistor types.—Triplett Electrical Instrument Co., Bluffton, Ohio.

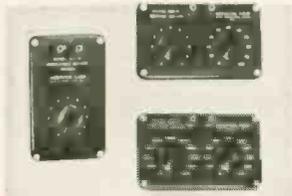**DECADE BOXES.** Complete line of 10 models: 3 capacitance, 3 resistance, 4 inductance. Heavy-duty construction. Multi-




ple-dial units have highest value multiplier on left-hand side so that readings are in order when read.—Aerovox Corp., Distributor Div., New Bedford, Mass.

**GARAGE-DOOR OPERATOR,** model G-500. Quieter operation and greater efficiency than previous models. Radio-controlled. Gear type speed reducer uses double helix gear. ¼-hp 117-volt



capacitor-start motor. Automatic shutoff. Crystal-controlled transmitter uses plug-in coded channel modulation to prevent interference. Perma-Power Co., 3100 N. Elston Ave., Chicago 18, Ill.

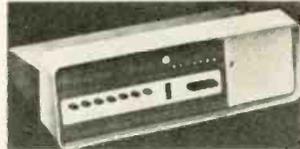**INTERCOM SYSTEMS,** Ektacom E and W 601 series. Pre-



mium quality. No printed circuits. More than 5 watts audio output when driven with 2-mv input.—Fisher Berkeley Corp., 4224 Holden St., Emeryville, Calif.

**HAM TRANSMITTER KIT,** Heathkit Apache. 150-watt phone and 180-watt CW inputs.




Built-in switch-selected circuitry provides for single-sideband transmission with plug-in external adapter. Vfo provides low-drift frequency control. Rotating slide-rule vfo dial. Band-switch gives quick selection of amateur bands on 80, 40, 20, 15 and 10 meters. Adjustable low-level speech clipping and low-distortion modulator stage with 6CA7 tubes in push-pull class-AB operation. Time-sequence keying. Pi-network output coupling matches impedances between 50 and 72 ohms.—Heath Co., Benton Harbor, Mich.

**TRANSISTOR RADIO KIT,** Sextette. 6 transistors, 3 if transformers, push-pull audio output, loopstick antenna, full-action avc. Prepunched printed-



circuit board. Unbreakable case.—Suporex Electronics Corp., 4-6 Radford Pl., Yonkers, N. Y.

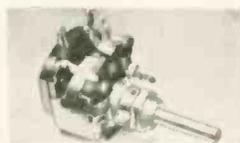**MINIATURE POTENTIOMETER,** series 44. Rated at 0.2 watt. Body diameter 21/32 inch, depth 23/64 inch, shaft



½ inch. Standard ohmages of 25K and 500 K with W taper.—Clarostat Mfg. Co., Dover, N. H.

**FILM CAPACITORS,** Isofarad line. Plastic-film dielectric paper tubular units have capacitance stability of ±0.5% over oper-




ating temperature of 25-80°C. Premolded phenolic housing and plastic resin and seals protect against moisture and mechanical damage. For TV-radio replacements and lab instruments.—Sprague Products Co., North Adams, Mass.

**GERMANIUM RECTIFIERS,** 1N008 and 1N016. Replace entire line of direct replacement



TV set rectifiers. Snap-in type. 1N008 is 400-ma half-wave unit; 1N016, 400-ma doubler.—General Electric Co., Semiconductor Products Dept., Syracuse, N. Y.

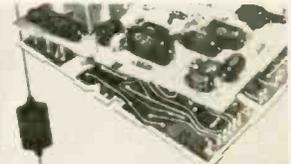**MOLDED CAPACITORS,** Wima Tropicdur. For printed and conventional circuits. Hot-dip fusing process seals element to terminal wires. Tropicalized. Air




inclusion prevented by applying coating in vacuum.—Rhombic Associates, 60 W. 45 St., New York 36, N. Y. END

All specifications on these pages are from manufacturers' data.

# PENTRON STEREO

HIGH FIDELITY  
TAPE RECORDERS

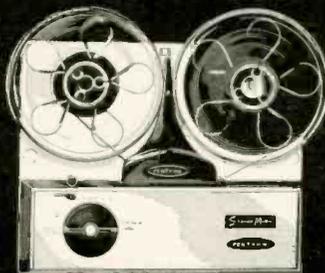

professional performance at popular prices  
NOW YOU CAN RECORD STEREO, TOO!

Pentron's totally new TM-4 Stereo Tape Deck is the ideal addition to your custom high fidelity system: records and plays stereo... 4-track as well as 2-track tape, records and plays monaural and has all the exclusive Pentron stereo features which assure you matchless performance of a professional quality never before possible at popular prices.

Pentron tape mechanisms are precision engineered with full-range frequency response, Azmur-X head azimuth adjustment, single Finger-Flite rotary control, easy dual-speed control lever, four outputs plus two AC convenience outlets, self-energized braking, stereo or monaural erase, designed to operate at any mounting angle.

The Pentron TM-4 is priced at \$109.95 net and is available at professional high fidelity showrooms. For detailed information on Pentron high fidelity tape recorders, amplifiers, pre-amps, mike mixers, tape decks, and stereo conversion kits, write Dept. R-1 or see your yellow pages.

**PENTRON CORPORATION** 777 South Tripp Avenue, Chicago 24, Illinois

CANADA: Atlas Radio Ltd., Toronto EXPORT SALES; Raytheon International Division Waltham, Massachusetts

SEE THE NEW PENTRON EMPEROR II...



THE ONLY COMPLETE POPULAR-PRICED STEREO RECORDING SYSTEM

IF YOU  
MUST SPEND  
YOUR MONEY

Why not get  
Something for it?  
get

**QUIETROLE**



IN BOTTLES  
2, 4 & 8 oz.  
Dropper with  
2 oz.  
SPRAY-PACK  
"CAN"



**QUIETROLE**

Costs little more than the poorest substitutes. Why take less than the BEST...

No Product can match its merit...  
None can equal its quality...  
It's the answer to noisy controls and switches

QUIETROLE is the original product of its kind

MFG BY **QUIETROLE Company**

SPARTANBURG, South Carolina  
IN CANADA: ACTIVE RADIO and TV DISTRIBUTORS  
58 Spadina Ave., Toronto 28, Ontario

**GUIDE**

# **AUTRONIC-EYE<sup>®</sup>**

**TRAINING COURSES**

**MEAN MORE**

**BUSINESS FOR YOU!**




**Courses for experienced service technicians provide latest repair information—enable you to do the job faster and more efficiently.**

Quick, accurate circuit diagnosis and repair to factory specifications boosts your profits. That's why so many qualified auto technicians attend these Guide training courses at no cost other than transportation and living expenses.

The Guide Lamp diploma, awarded only to those who successfully complete the course, is proof that you're equipped to give more and better service to more people—and that means business.

If you're an auto radio service dealer, come yourself, or send your technicians. There's one of 30 GM Training Centers near you. Apply through your local United Motors Service Division Distributor or write

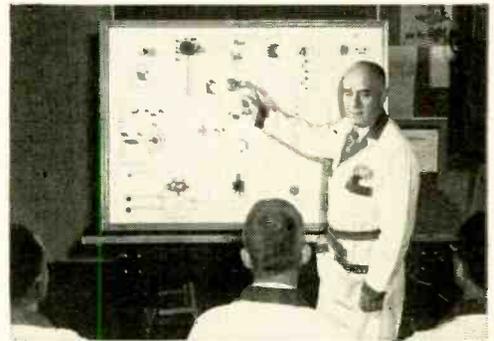GUIDE LAMP DIVISION • GENERAL MOTORS CORP. • ANDERSON, INDIANA




Jumbo-size operational panel of Guide's Autronic-Eye Circuit puts all parts out front for better, more efficient instruction.



Thirty modern GM Training Centers offer newest equipment and latest service techniques. There's one nearby . . . no matter where you live.



**BLINKY MEANS BUSINESS!**

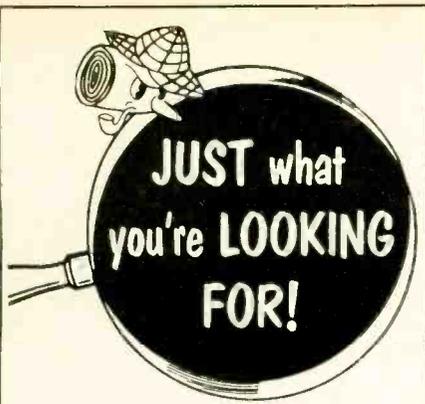

## HOW & WHY of HI-FI & STEREO



### NEWEST HI-FI STEREO book

Has all the answers. Explains complicated subjects in simple easy-to-understand language.

Tells HOW to select amplifiers, pre-amps, record players, tape recorders, microphones, speakers, baffles & enclosures. Explains basic principles of high fidelity and stereophonic sound. Tells how to read and understand manufacturers' specifications of Hi-Fi equipment.

Shows the easy way to understand and use decibels. Also explains distortion and means of eliminating it, feedback, Williamson & Ultra-Linear circuits, impedance matching, audio power requirements, cross-over networks, equalization, volume compression and expansion, bass & treble boost, types of phono pickups & styli & many other subjects.

Includes the latest stereo developments in record players, tuners and tape recorders. Shows how to adapt monaural Hi-Fi systems to stereo.

A STROBOSCOPE DISC in each book.

**Price Only \$1—Biggest HI-FI STEREO Dollar's Worth**


Off the press Jan. 15, 1959. All who send advance order and remittance before that date will also receive absolutely FREE OF CHARGE, a copy of H. G. Cisin's GUIDE TO BASIC ELECTRICITY, Vol. 1.

## TV & RADIO TUBE SUBSTITUTION GUIDE
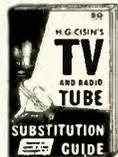
### TUBE SUBSTITUTION WITHOUT REWIRING

1959 EDITION


- \* Includes newest type tubes
- \* No socket changes necessary
- \* U.S.A. Substitutes for foreign tubes
- \* Transistor substitutes
- \* Hi-Fi Substitutes
- \* Special section on TV Picture Tube Substitutions



On sale at over 500 leading Radio-TV jobbers in U. S. and Canada. If jobber cannot supply send his name with your order.

Price.....Only 50¢

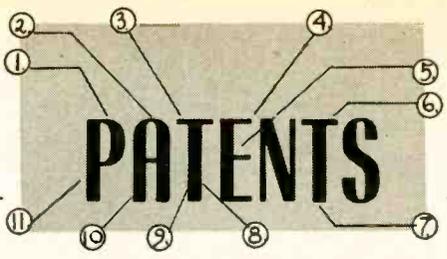**H. G. Cisin, Consulting Engineer**  
 Dept. E-50, Amagansett, N.Y.  
 Enclosed find \$..... RUSH FOLLOWING:  
 HOW & WHY OF HI-FI & STEREO .....\$1  
 TV RADIO TUBE SUBST. GUIDE .....50¢  
 Vol. 1 Basic Elec.  Vol. 2  Vol. 3—50¢ ea.  
 Name.....  
 Address.....  
 City..... Zone..... State.....




## PARKING ALONG THE BEAM

Patent No. 2,818,553

David Lawrence Jaffe, Great Neck, N. Y.  
 (Assigned to Polarad Electronics Corp., Brooklyn, N. Y.)

Here is a solution to the problem of the big car and little garage. A radio beam guides the driver as he moves in or out, the signal being received on the car radio.

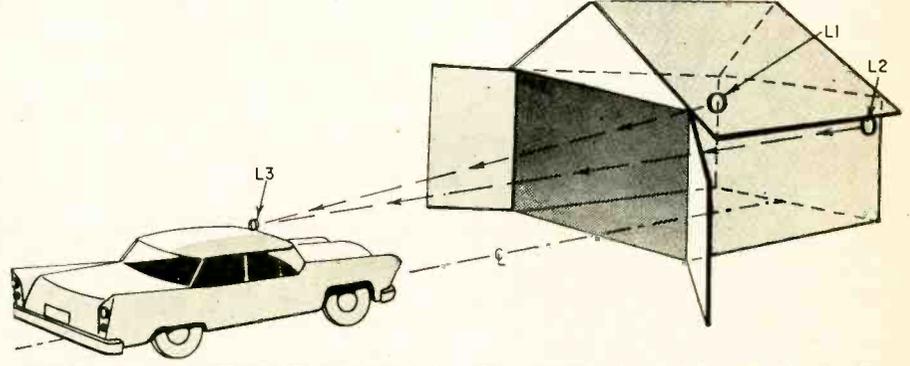the fields cancel. If the car is off center, its radio antenna (loop L3) will receive one carrier more strongly than the other, and the corresponding tone is heard. To park the car correctly,



Two directional loops (L1 and L2) are mounted symmetrically at the rear of the garage. They are energized by rf, each out of phase with the other. Each is modulated with a different audio tone. At any point midway between the loops

the driver merely steers so that he is always along the null line.

The inventor suggests shorting out the radio's avc for maximum sensitivity while using this parking guide.


## PORTABLE TAPE-RECORDER CIRCUIT

Patent No. 2,810,791

Ralph West, Oceanside, and Kalju Meri, Astoria, N. Y. (Assigned to Mohawk Business Machines Corp., New York, N. Y.)

A single tube can combine the functions of signal amplifier and bias voltage generator. The dual-function tube (V) is shown as a filament type for battery operation. Other tubes (not shown) are in the main amplifier.

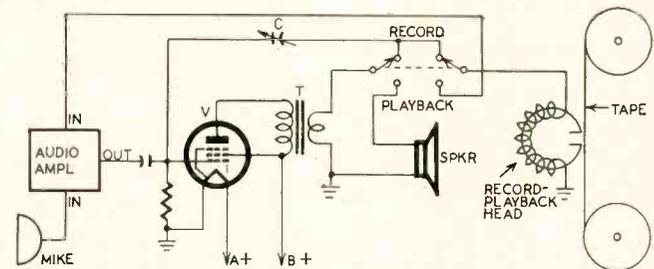tude is adjusted by C. At the same time, the tube adds its gain to the output from the amplifier. The mixed bias-audio voltage is delivered to the recording head.



When switched to RECORD, the tube's output is fed back through T and C for oscillation at some predetermined ultrasonic frequency. Bias ampli-

Switching to PLAYBACK connects the magnetic head to the amplifier input. Output from V appears across the speaker for tape reproduction.


## HEADLIGHT DIMMER

Patent No. 2,827,594

Jacob Rabinow, Takoma Park, Md.

Your headlights should be dimmed when you travel behind another car moving in the same

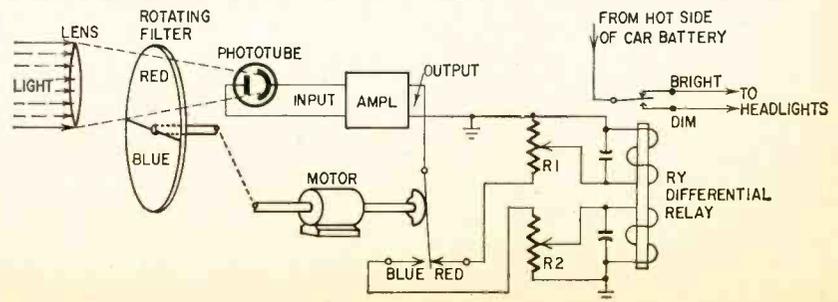direction or when a second car approaches in the opposite direction. This avoids confusing the



driver up ahead or blinding an approaching driver. This automatic device responds automatically both to a strong (white) headlight or to a weak (red) taillight.

The received light beam passes through a lens and a motor-driven filter to the phototube. The same motor drives a synchronous vibrator which closes the "red" contacts while the red filter is in position, and so on. Separate outputs from the vibrator are adjusted by R1 and R2, which feed the coils of relay RY. As long as these outputs are equal (but opposite) the relay is not energized.

Light from a taillight is nearly all red, so the output of the red contact is high and that of the blue contact of the vibrator is practically zero. Therefore the relay closes, dimming the headlights.

Light from the headlights of an approaching vehicle contain quantities of both red and blue light so R1 and R2 are adjusted to provide enough of a difference in red and blue outputs to close the relay.


Now, either approaching headlights or creeping up on the taillights of the car ahead will dim your lights. Of course, after the approaching car has passed or you have passed the car ahead, the bright lights go on again—with no light in front of you there is no output from the red or blue contacts and the relay opens.

**BLINKER**

Patent No. 2,829,257

Elihu Root, 3d, Clinton, N. Y. (Assigned to R. E. Dietz Co., Syracuse, N. Y.)

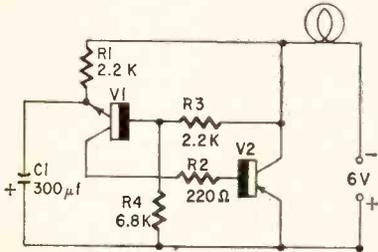This blinker controls a low-voltage lamp. It can be used as a safety flasher—for example, near a stalled car. The car battery could be the power source. One transistor (V1) is a control unit, while the other (V2) must be a power



unit capable of passing the high lamp current. Initially, V1 and V2 are cut off and current flows through R1 to charge C1. V1's emitter goes progressively more negative and soon the transistor conducts. Current flowing through R2 drives V2 to conduction also, permitting lamp current to flow through this transistor. As the lamp voltage rises, V1's base goes still more positive until both transistors are saturated and the lamp is fully lit.


C1 begins to discharge through the transistors, continuing until its voltage becomes too low to support further flow through them. At this point, the transistors block and the cycle repeats.

**DUAL-IMAGE TV SET**

Patent No. 2,832,821

Allen B. DuMont, Cedar Grove, N. J. (Assigned to Allen B. DuMont Labs, Inc.)

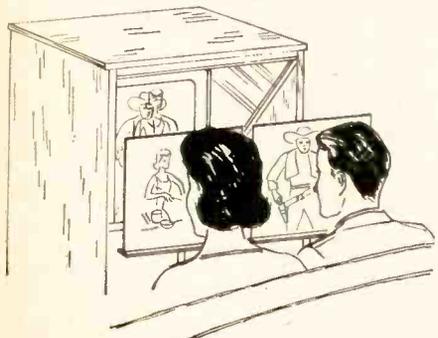This TV receiver has two picture tubes and can reproduce two different images at once. Both pictures are superimposed on a single screen. A polarized sheet is used to filter out



one image, so that a viewer sees only the desired show.

The image from one kinescope is viewed directly, while that of the other is reflected. This polarizes them oppositely and makes it possible to separate them by oppositely polarized glasses or panels. The diagram shows how two viewers may watch different programs at once.

To avoid conflict of sound, each viewer wears an earpiece. **END**

# FREE

## GIANT ALL NEW 1959

# B-A CATALOG

WITH THE BIGGEST SAVINGS ANYWHERE

A COMPLETE BUYING GUIDE FOR EVERYTHING IN

## RADIO TV

# ELECTRONICS

# BA 1959

ANNUAL CATALOG 591

SINCE 1927

**180**  
KING-SIZED  
PAGES

EVERYTHING  
IN RADIO  
TV AND  
ELECTRONICS

100'S OF  
NEW ITEMS  
LISTED HERE  
FOR 1st TIME

21 PAGES  
OF BARGAINS  
NOT IN ANY  
OTHER CATALOG

**RUSH COUPON TODAY!**

**BURSTEIN-APPLEBEE CO. Dept. S**  
1012-14 McGee St., Kansas City 6, Mo.

Send Free 1959 B-A Catalog No. 591.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

**SAVE TIME with**

**SENCORE**

**New! Improved!**

**TRANSISTOR CHECKER**

America's newest, most popular test instrument

Simple to Operate. Controls are accurately set for each transistor by referring to replaceable set-up chart on rear. Test leads or socket provides for fast hook-up.

**NOW CHECKS:**

- ★ Transistors for opens, shorts, leakage and current gain. Only tester that tests power transistors as used in car radio outputs.
- ★ Crystal Diodes checks forward to reverse current ratio on all diodes.
- ★ Selenium Rectifiers checks forward and reverse currents.

**MODEL TRC4**

**\$17.95**

DEALER NET

Cannot become obsolete. Approved by leading manufacturers.

**SENCORE CORP. 121 Official Rd. • Addison, Ill.**

See other SENCORE ads in this issue.

# "So Smooth & Clean-

is the response of the Atlas WT-6 that we demonstrate it in our high-fidelity Audio Torium," says Anton J. Schmitt, Harvey Radio Co., Inc., New York, N. Y.



**New ATLAS**  
COAX-PROJECTOR WT-6


WT-6 NET \$34.50  
support stand only,  
SS-4 NET \$12.60

**ALL-WEATHER**— install it, forget it! —  
**HIGH-EFFICIENCY . . . COMPACT . . .**

True **HIGH FIDELITY TWO-WAY** system — not just a "compromise" of two horns coupled to a single diaphragm. The WT-6 comprises a weather-proof cone type driver (with 6-inch throat) coupled to its individual woofer horn; a separate pressure-type driver loaded to its separate tweeter horn. The built-in crossover electronic filter supplements the electro-mechanical frequency-limiting characteristics of the 2 individual reproducers — providing for smooth frequency division as each speaker functions within its engineered range of frequencies. Universally adjustable "U"-type rugged steel mounting . . . finished in high temperature baked modern beige enamel.


<b>Power Rating</b>	15 watts continuous.
<b>Freq. Resp.</b>	140-15,000 cps
<b>Impedance</b>	8 ohms
<b>Dispersion</b>	120°
<b>Dimensions</b>	Bell opening 15", overall depth 12"

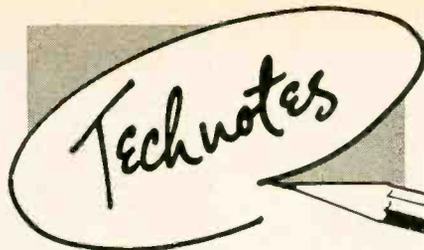See the WT-6 at your local distributor.  
Send for complete catalog. RE-1.



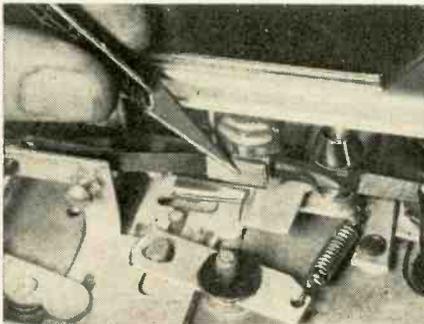
## TAPE RECORDER SERVICING

Loss of volume or high-frequency response in a tape recorder can often be traced to the pressure pad (Fig. 1) not holding the tape firmly against the head. After the recorder has been used



for quite some time without the spring-tension screw being adjusted, the spring tends to loosen up.

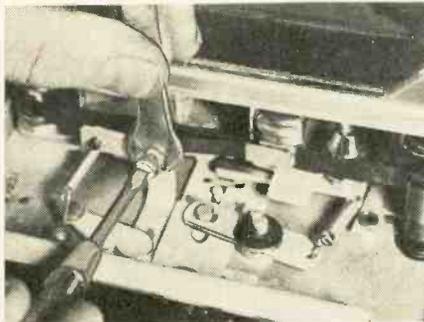To tighten the spring tension, start a tape running through the machine on playback, loosen the small nut which holds the screw tight and tighten the screw for more tension (Fig. 2). (Adjust the screw for firm tension but




not so firm that tape passing through the head tends to slow down.) The increased pad pressure will hold the tape firmly against the head and insure that none of the intelligence on the tape will pass by unreproduced.—*Scott Mock*
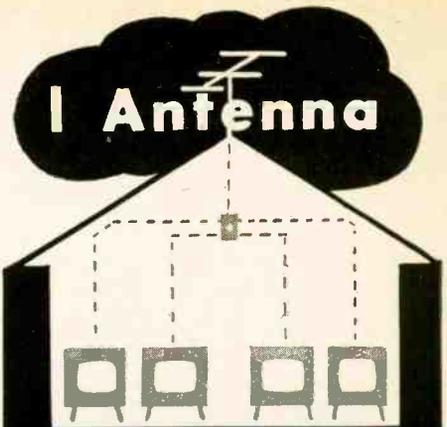
## SWAPPED 3.58-MC CRYSTALS


Recently, I was called into a service shop to take a look at a color TV receiver which would not lock color. The color signal was present but appeared in the form of several rainbows across the screen, drifting back and forth. No adjustment of the color discriminator balance control would help, although it would reduce the number of rainbows and almost bring the color sync into lock.

Tubes had been replaced, the reactance tube tank and the color oscillator slug were varied through their entire ranges with no results. All operating voltages were within tolerance.



## 4 Sets

### MOSLEY 4-Set Coupler

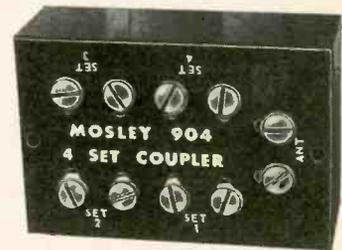

**LOW LOSS**  
**EFFECTIVE ISOLATION**  
**EFFICIENT SIGNAL DISTRIBUTION**

Owners of Duplex or 4-unit Apartment Buildings will want you to install Mosley 4-Set Couplers!

Here's a Big profit-maker in a Big market!

Mosley 904, 4-Set Coupler

\$6.25 List

Another Mosley Premium Quality TV Accessory!

**Mosley**  
*Electronics, Inc.*  
8622 ST. CHARLES ROCK ROAD  
ST. LOUIS 14, MISSOURI

## RADIO-ELECTRONICS

February issue  
on Sale Jan. 29th  
Reserve your copy  
now

We Specialize in REPAIR

of **RCA TUNERS**

All Model Tuners Repaired

\$8 plus parts costs

Television Tuner Service Co.

2534 Rusty Drive  
133 N. Overhill Dr.


Des Plaines, Ill.  
Bloomington, Ind.

Finally I suspected that the color oscillator crystal might have become defective, although this seemed remote. Discussion brought up the possibility that the technician might have mixed up the crystals for the color bar generator and the receiver—both were stamped 3.579545 mc.

The possibility was checked by swapping the crystals. Sure enough, a little touchup of the color sync controls restored perfect reception. Apparently, the color bar generator signal was thrown off frequency by the receiver crystal, just as the receiver was thrown off frequency by the generator crystal. Both were stamped with the same frequency but each operated properly only in the circuit for which it had been intended.—Robert G. Middleton

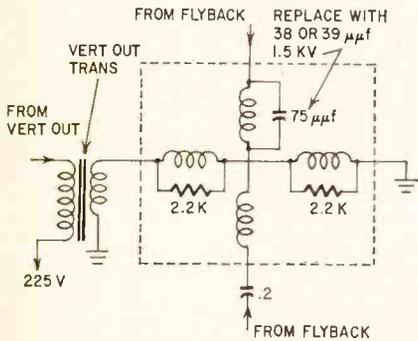**MAJESTIC MODELS 99 TO 105**

Ringling due to insufficient damping in the horizontal deflection circuit has been traced to the 75- $\mu\mu\text{f}$  capacitor




across half of the horizontal yoke winding. Replace this unit with a 38- or 39- $\mu\mu\text{f}$  1,500-volt capacitor to eliminate the trouble.—John A. Comstock

**PACKARD-BELL MODEL 2101**

Trouble: nonlinear retrace lines top half of raster.

Check for slightly leaky capacitor across primary of vertical output transformer. If, with new capacitor installed, trouble returns in a short time, try a new transformer—the one in the set may have shorted turns.—William Porter

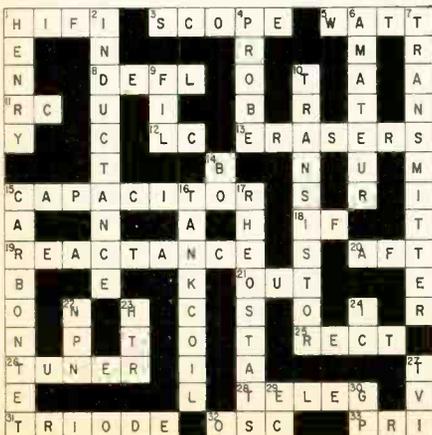Answer to Electronic Crossword on page 39



# UNDER THIS COVER!

## A NEW AND GREATER EDITION OF THE

# RADIO Handbook

### Fifteenth Edition

AC & DC CIRCUITS — VT PRINCIPLES — TRANSISTORS & SEMI-CONDUCTORS — VT AMPLS. — HIGH FIDELITY — Hi-Fi Ampl.; Baby Hi-Fi; High Quality 25-W Ampl. — RF VT AMPL. — OSCILLOSCOPE — SPECIAL VT CIRCUITS — ELECTRONIC COMPUTERS — RECEIVER FUNDAMENTALS — RF ENERGY TRANSMISSION — TRANSMITTER DESIGN — TV & BC INTERFERENCE — FM & RADIO TELETYPE TRANSMISSION — SIDE-BAND TRANSMISSION — TRANSMISSION LINES — ANTENNAS — End-fed and Center-fed Half-Wave Horizontal, Half-Wave, Ground Plane, Marconi, Space-Conserving, Multi-Band Ant.; Matching Non-Resonant Lines to Ant.; Ant. Construction; Coupling to Ant. System; Single-Wire Ant. Tuner — HF ANTENNA ARRAYS — VHF & UHF ANTENNAS — ROTARY BEAMS — MOBILE EQUIPMENT — RECEIVERS & TRANSMITTERS — Simple Transistorized Portable BC Recvr.; 455 Kc. Mechanical Filter Adapter; High Performance Amateur Band Recvr.; Transistorized 144 Mc.; 6 Meter Transcv. for Home or Car; "Hot" Transcv. for 28 Mc. — LOW POWER TRANSMITTERS & EXCITERS — SSB Exciter for Fixed or Mobile Use; Mobile Transistorized SSB Exciter; VHF Transcv. of Advanced Design; Miniaturized SSB Transmitter for 14 Mc.; Duplex Transmitter; Tetra-Driven Kw. Ampl.; Low Distortion DX Operator — HF POWER AMPLS. — Push-pull Triode & Tetra-Modulator; 2 Kw. P.E.P. All-band Ampl.; 10-W Ampl.-Driver; Sideband Linear Ampl.; Kw. Ampl. for Linear or Class C Operation; General Purpose Triode Modulator; Zero Bias Tetra-Driven Mobile Ampl. — SPEECH & AM EQUIPMENT — 200-W 811-A Deluxe Transmitter for 50/114 Mc.; Deluxe Transmitter for the 3.5-29.7 Mc. Range — POWER SUPPLIES — 100-W Mobile Power Supplies; Power Supply Design; 300 V., 50 Ma. Power Supplies; 500 V., 200 Ma. Power Supply; 1500 V., 425 Ma. Power Supply; Dual Voltage Transmitter Supply; Kw. Power Supply with Bridge; Freq. Measurements Ant. and Transmission Line Measurements; Simple Coaxial Reflector; Measurements on Balanced Transmission Lines; "Balanced" SWR Bridge; Antennascope; Silicon Crystal Noise Generator — RADIO MATHEMATICS & CALCULATIONS

\$7.50 at your dealer in U.S.A. (plus any tax)

**BUY FROM YOUR FAVORITE DISTRIBUTOR**

at above price or add 10% or direct mail orders to:

**EDITORS and ENGINEERS, Ltd.**

Summer and 3, California

BOOKSTORES ORDER FROM BAKER & TAYLOR CO., HILLSIDE, N.J.

## SENCORE "Fuse Safe" CIRCUIT TESTER

### Save Time with SENCORE

Save costly call backs by testing the circuit before replacing fuse, fuse resistor or circuit breaker.

Individual scale for each value fuse resistor—no interpretation, just read in red or green area.

- ★ Measures line current and up to 1100 watts of power at 115 volts using line cord and socket.
- ★ Two convenient current ranges—0 to 2 amps and 0 to 10 amps. Test leads clip in place of fuse or fuse resistor.
- ★ 5 ohm, 10 watt resistor prevents TV circuit damage, simulates operating conditions.



MODEL FS-3

**\$8.95** DEALER NET


AC-DC or both as needed for Fuse Resistor Circuits

**SENCORE** As Recommended by Leading Manufacturers

**SENCORE CORP. 121 Official Rd. Addison, Ill.**

See other SENCORE ads in this issue

VHF  
or  
UHF

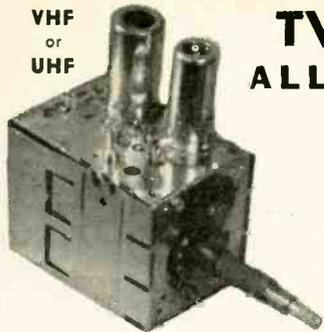

## TV TUNERS REBUILT ALL MAKES & MODELS

THOUSANDS OF TUNERS IN STOCK

EXCHANGED OR OVERHAULED

**\$9.95**  
NET

Price includes WORN parts only. Replacement tubes and smashed or missing parts are charged extra.

COMBINATION UHF/VHF UNITS \$19.90  
90 DAYS WARRANTY

ALIGNED TO ORIGINAL STANDARDS USING THE FINEST EQUIPMENT. ALL WORK PERFORMED BY TUNER EXPERTS WITH YEARS OF EXPERIENCE IN THE TUNER FIELD.

**FAST SERVICE** EXCHANGE OR OVERHAULED TUNER SHIPPED WITHIN 48 HOURS, IN MOST CASES.

Forward Tuner with All Smashed Parts: Quote Make and Model F.O.B. Chicago or Toronto We will ship C.O.D.

*Castle Television Tuner Service*

1723 W. LUNT AVE.,  
CHICAGO 26, ILL.

U.S.A.

152 MAIN ST.,  
TORONTO 13, ONT.

CANADA

Suppliers of rebuilt TV Tuners to leading manufacturers, technicians & service dealers, coast to coast. Original and Only Complete TV Tuner Service covering the North American Continent.



# TRY THIS ONE

### TELEPHONE ANTENNA


Many a technician has encountered the landlord who would not stand for an outdoor antenna. A simple solution to this problem is to take a 10-foot length of insulated indoor antenna wire and wrap one end into a 4-inch coil of about 6 turns. Place this coil under the base of a desk telephone and fasten the other end to the antenna terminals of the AM receiver.

The electrostatic or capacitive coupling between the coil of wire and the phone base transfers rf signals picked up by the external telephone lines to the lead-in and on to the AM receiver.—

*John A. Comstock*
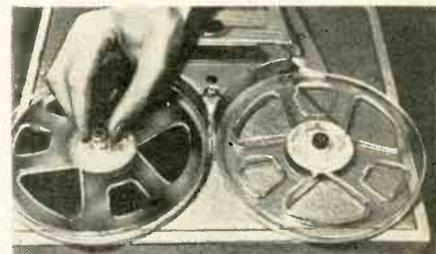
### TAPE RECORDER KINK

If you have ever picked up a tape recorder by its carrying handle while reels of recording tape were still on the spindles, you'll remember how the reels of tape slipped off and fell crash-



ing to the floor in a tangled mess. After this little incident happened to me recently, I decided to take measures to keep it from happening again. Before I pick up the recorder when there are reels of tape on the spindles, I slip a tight-fitting rubber grommet over each spindle. This keeps the reels of tape from slipping off.—*Scott Mack*

### SIMPLE FEEDBACK CONNECTION

You can add inverse feedback to an audio amplifier, radio, TV set or small phonograph in a very simple manner. Just disconnect the plate load resistor of the first audio tube from B-plus and connect it to the plate of the output tube. Thus, that resistor now serves as both a plate load and a feedback resistor. The degree of feedback can be changed by changing the value of this resistor—lower values for more feedback.—*Charles Erwin Cohn*

### FRAYING POWER CORDS

Many radio-TV-electrical-appliance technicians are familiar with the age-

RADIO-ELECTRONICS

## NOW!

Step ahead faster  
as an

## INDUSTRIAL ELECTRONICS TECHNICIAN



Turn your experience into a big, new better-paying career!

Day by day industrial plants are adding more electronic devices — for sorting, counting, checking almost any control job you can name. Cash in on industry's great need for men who can keep these devices in top working order. Make more money, feel more secure, doing work that is second nature to you. With what you already know about electronics you have a long head start in a field just beginning to boom. GET INTO IT RIGHT NOW with the help of

### PRACTICAL INDUSTRIAL ELECTRONICS LIBRARY

No long sessions on math or theory! These 4 practical volumes show you how to keep the plant's electronic equipment working . . . how to locate and correct tube and circuit troubles . . . how to install, service, and maintain even brand new equipment without being stumped by new circuits!

FREE TRIAL—EASY TERMS

4 volumes (1369 pp., 102 illus.)  
Chute's Electronics in Industry

Miller's Maintenance Manual of Electronic Control

Markus & Zeluff's Handbook of Industrial Electronics Circuits

Henney & Fahnestock's Electron Tubes in Industry

McGraw-Hill Book Co., Dept. RE-1,  
321 W. 41st St., N.Y.C. 36

Send me the Practical Industrial Electronics Library for 10 days' examination on approval. In 10 days I will send \$3.50, then \$5.00 a month until \$23.50 is paid. (A saving of \$6.00 under the regular price of \$29.50.) Otherwise I will return books postpaid. (Print)

Name.....  
Address.....  
City..... Zone..... State.....  
Company.....  
Position.....

RE-1  
For price and terms outside U.S., write  
McGraw-Hill Int'l., N.Y.C.

## LOOK

no further . . . if you're searching for hi-fi savings. Write us your requirements now.

Key Electronics Company  
120-A Liberty St., N.Y. 6, N.Y.  
EV 4-6071



### SUITS NEED PRESSING— MERIT DEFLECTION YOKES DO NOT!

Merit deflection yokes are cosine wound TO FORM, not pressed. Pressing can lead to distortion and poor focusing. Pressing after winding frequently causes breakdown.

MERIT COILS AND TRANSFORMERS HAVE "BUILT-IN" ADVANTAGES.



Each Merit yoke is  
100% LIVE TESTED

COMPARE IT WITH  
**MERIT**  
MERIT COIL AND TRANSFORMER CORP.  
MERIT PLAZA • HOLLYWOOD, FLORIDA

# "ONE DOLLAR" buys

As much as \$15 worth—Everything Brand New and sold to you with a money back guarantee.  
**DEDUCT 10% ON ANY ORDER OF \$10 OR OVER**  
**Plus a FREE SURPRISE PACKAGE**


- 15 - ASST. ROTARY SWITCHES \$15 worth ... \$1
- S15 - "JACKPOT" TELEVISION PARTS ... \$1
- 2 - ELECTRIC MOTORS 1 1/2 volt, 1001 uses ... \$1
- 4 - RCA #1U4 TUBES also serves as a 1T4 ... \$1
- 40 - ASST. PRECISION RESISTORS best sizes ... \$1
- 10 - TV CARTWHEEL CONDENSERS 10KV ... \$1
- 1 - 5" PM SPEAKER alnico #3 magnet ... \$1
- 20 - TUBULAR CONDENSERS .05-600v ... \$1
- 20 - TUBULAR CONDENSERS .001-1000v ... \$1
- 100 - ASSORTED FUSES popular sizes ... \$1
- 100 - ASST. 1/2 WATT RESISTORS some 5% ... \$1
- 70 - ASSORTED 1 WATT RESISTORS some 5% ... \$1
- 35 - ASSORTED 2 WATT RESISTORS some 5% ... \$1
- 50 - ASST. TUBULAR CONDENSERS ... \$1
- 10 - 6' ELECTRIC LINE CORDS with plugs ... \$1
- 5 - TV CHEATER CORDS with both plugs ... \$1
- 4 - 50' SPOOLS HOOK-UP WIRE 4 colors ... \$1
- 50 - STRIPS ASST. SPAGHETTI best sizes ... \$1
- 100 - ASST. RUBBER GROMMETS best sizes ... \$1
- 100' - TWIN LEAD-IN WIRE 300Ω heavy duty ... \$1
- 50' - FLAT 4-CONDUCT. WIRE many purposes ... \$1
- 25' - INSULATED SHIELDED WIRE ... \$1
- 1 - S7 INDOOR TV ANTENNA hi-gain 3 section ... \$1
- 50' - ANT. ROTOR 4-CONDUCTOR WIRE ... \$1
- 4 - RATCHET GUY WIRE FASTENERS ... \$1
- 20 - ASST. TV KNOBS, ESCUTCHEONS, Etc. ... \$1
- 3 - ASST. TOGGLE SWITCHES spst, dpdt, etc. ... \$1
- 6 - ASST. SLIDE SWITCHES spst, dpdt, etc. ... \$1
- 4 - BAKELITE KNIFE SWITCHES dpdt, etc. ... \$1
- 100' - FINEST NYLON DIAL CORD best size ... \$1
- 200 - SELF TAPPING SCREWS #8 x 1/2" ... \$1
- 35 - ASST. RADIO KNOBS screw and push-on ... \$1
- 100 - KNOB SPRINGS standard size 9/16" x 1/2" ... \$1
- 100 - ASSORTED KNOB SET-SCREWS ... \$1
- 25 - ASSORTED CLOCK RADIO KNOBS ... \$1
- 400 - ASST. H'DWARE screws, nuts, rivets, etc. ... \$1
- 50 - ASST. SOCKETS octal, noval and miniature ... \$1
- 20 - ASSORTED TUBE SHIELDS best sizes ... \$1
- 50 - ASST. MICA CONDENSERS some in 5% ... \$1
- 50 - ASST. CERAMIC CONDENSERS ... \$1
- 10 - ASST. VOLUME CONTROLS less switch ... \$1
- 5 - ASST. VOLUME CONTROLS with switch ... \$1
- 100 - VOLUME CONTROL HEX NUTS ... \$1
- 20 - ASST. PILOT LIGHTS popular types ... \$1
- 10 - PILOT LIGHT SKTS. bayonet type, wired ... \$1
- 50 - ASST. TERMINAL STRIPS 1, 2, 3, 4 lug ... \$1
- 10 - ASST. RADIO ELECTRO. CONDENSERS ... \$1
- 5 - ASST. TV ELECTROLYTIC CONDENSERS ... \$1
- 25 - ASST. MICA TRIMMER CONDENSERS ... \$1
- 2 - ELECTROLYTIC COND. 40/40-450v ... \$1
- 30 - FP CONDENSER MOUNTING WAFERS ... \$1
- 3 - ELECTROLYTIC COND. 80-450v ... \$1
- 3 - ELECTROLYTIC COND. 50/30-150v ... \$1
- 10 - HV TUBULAR CONDENSERS 006-1600v ... \$1
- 10 - HV TUBULAR CONDENSERS .001-6000v ... \$1
- 10 - HV TUBULAR CONDENSERS .005-6000v ... \$1
- 35 - MICA COND. 20-100 mmf & 15-270 mmf ... \$1
- 35 - MICA COND. 20-470 mmf & 15-680 mmf ... \$1
- 35 - MICA COND. 20-820 mmf & 15-1000 mmf ... \$1
- 35 - CERAMIC COND. 20-5 mmf & 15-10 mmf ... \$1
- 35 - CERAMIC COND. 20-25 mmf & 15-47 mmf ... \$1
- 35 - CERAMIC COND. 20-56 mmf & 15-82 mmf ... \$1
- 35 - CERAMIC COND. 20-100 mmf & 15-150 mmf ... \$1
- 35 - CERAMIC COND. 20-270 mmf & 15-470 mmf ... \$1
- 35 - CERAMIC COND. 20-1000 mmf & 15-1500 mmf ... \$1
- 35 - CERAMIC COND. 20-2000 mmf & 15-5000 mmf ... \$1
- 50 - 100Ω 1/2 WATT RESISTORS 5% ... \$1
- 75 - 470KΩ 1/2 WATT RESISTORS 10% ... \$1
- 35 - 100KΩ 2 WATT RESISTORS 10% ... \$1
- 10 - ASST. WIREW'ND RES. 5, 10, 20 watt ... \$1
- 3 - AUDIO OUTPUT TRANS. 50L6 type ... \$1
- 3 - AUDIO OUTPUT TRANS. 6K6 or 6V6 type ... \$1
- 3 - I.F. COIL TRANSFORMERS 456 kc ... \$1
- 3 - I.F. COIL TRANSFORMERS 10.7 mc FM ... \$1
- 4 - OVAL LOOP ANTENNAS asst' hi-gain types ... \$1
- 3 - LOOPSTICK ANT. new ferrite adjustable ... \$1
- 12 - RADIO OSCILLATOR COILS 456 kc ... \$1
- 3 - 1/2 MEG VOLUME CONTROLS with switch ... \$1
- 5 - 50K VOLUME CONTROLS less switch ... \$1
- 10 - SURE GRIP ALLIGATOR CLIPS ... \$1
- 1 - GOLD GRILLE CLOTH 14"x14" or 12"x18" ... \$1
- 5 - SETS SPEAKER PLUGS wired ... \$1
- 10 - SETS PHONO PLUGS and PIN JACKS ... \$1
- 2 - S2.50 SAPPHIRE NEEDLES 4000 playings ... \$1
- 5 - DIODE CRYSTALS 2-IN21 2-IN22 1-IN84 ... \$1
- 3 - DIODE CRYSTALS 1-IN80, 1-IN84, 1-IN89 ... \$1
- 1 - S11 TODD 60° DEFLECTION YOKE ... \$1
- 2 - SELENIUM RECTIFIERS 1-65 ma & 1-150 ma ... \$1
- 15 - ASST. TV COILS sync. peaking, width, etc. ... \$1
- 1 - TV VERT. OUTPUT TRANS. 10 to 1 ratio ... \$1
- 5 - TV CRT. SOCKETS with 18" leads ... \$1
- 5 - HI-VOLT. ANODE LEADS with 18" leads ... \$1
- 1 - TV RATIO DETECTOR TRANS. 4.5 mc ... \$1
- 1 - SET TV KNOBS standard type incl. decals ... \$1
- 1 - LB ROSIN CORE SOLDER 40/60 ... \$1
- 6 - SPIN TIGHT SOCKET SET 3/16" to 7/16" ... \$1
- 1 - LB - SPOOL ROSIN CORE SOLDER ... \$1
- 3 - TV ALIGNMENT TOOLS 5", 7", 12" ... \$1

HANDY WAY TO ORDER—Simply tear out advertisement and pencil mark items wanted (X in square is sufficient); enclose with money order or check. You will receive a new copy of this ad for re-orders.  
 ON SMALL ORDERS—Include stamps for postage, excess will be refunded. Larger orders shipped express collect.

**BROOKS RADIO & TV CORP.**  
 84 Vesey St. Dept. A, New York 7, N.Y.

TRY THIS ONE (Continued)

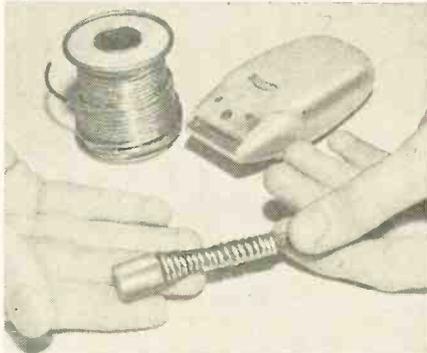old electrical problem. How do you keep a power cord from wearing out near its connector? Flexing of the cord during normal use eventually results in complete breakdown of the wires and insulation. Although there probably is no completely foolproof way to keep




this from happening, try wrapping the cord with solder near the connector, as shown in the photograph. The solder provides additional support for the wires and insulation, and won't eventually wear out as will a wrapping of waxed lacing twine or tape.—J. A. Compton

## STORING RECORDED TAPES

After purchasing a tape recorder I went out and recorded reels full of almost anything that made noise. I shortly discovered I had reels and reels of tape, but no safe place to keep them. A look around the kitchen solved the problem—empty potato-chip cans. They are about 7 1/4 inches in diameter and about 10 inches high—good for holding twenty 7-inch reels. Smaller cans for smaller reels can also be obtained and are very convenient.—Gerald Samkofsky, W2YSF
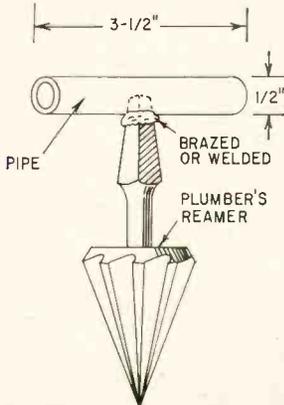
## HANDY REAMER

For enlarging holes drilled in a chassis, the technician and radio builder will both find that a plumber's burring reamer with a T-handle like the one shown can't be beat. It's a cinch to use in close quarters and its large




diameter makes it more versatile than the usual T-handle reamer. Drill a hole in the pipe large enough to accept part of the reamer's shank, then braze it in place. You are sure to find this modified reamer a handy addition to your bench tools.—John A. Comstock END

These men are getting practical training in...

# Electronics

## ELECTRICITY ELECTRONICS

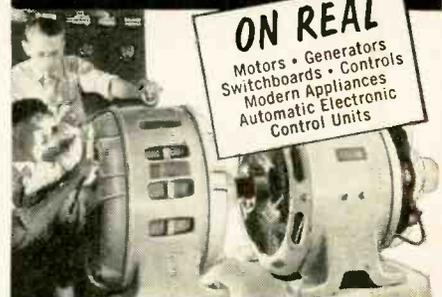

**ON REAL**  
 Motors • Generators  
 Switchboards • Controls  
 Modern Appliances  
 Automatic Electronic  
 Control Units

## TELEVISION RADIO ELECTRONICS



**ON REAL**  
 TV Receivers  
 Black & White and Color  
 AM-FM and Auto Radios  
 Transistors • Printed  
 Circuits • Test Equipment

Train in NEW Shop-Labs of

# COYNE

in Chicago — Electronic Center of the World. Prepare for a better job and a successful future in TOP OPPORTUNITY FIELD. Train on real full size equipment at COYNE where thousands of successful men have trained for 60 years—largest, oldest, best equipped school of its kind. Professional and experienced instructors show you how, then do practical jobs yourself on more than a quarter of a million dollars worth of equipment. No previous experience or advanced education needed. Employment Service to Graduates.

**Start Now—Pay Later—** Liberal Finance and Payment Plans. Pay most of tuition after graduation. Part-time employment help for students. Choose from nine yearly Starting Dates.

**Mail Coupon For Free Book—** "Guide to Careers." Whether you prefer ELECTRICITY-ELECTRONICS, TELEVISION-RADIO ELECTRONICS or COMBINED ELECTRONICS TRAINING, this book describes all training offered and gives all the facts to Vets and Non-Vets.

**Information comes by mail. No obligation and NO SALESMAN WILL CALL.**

B. W. Cooke, Jr., Pres. Founded 1899  
**COYNE ELECTRICAL SCHOOL**  
 Chartered Not For Profit  
 1501 W. Congress Pkwy., Chicago 7, Ill., Dept. 19-5A

### MAIL COUPON FOR BOOK

Coyne Electrical School, Dept. 19-5A  
 1501 W. Congress Pkwy.  
 Chicago 7, Ill.

Send FREE book, "Guide to Careers" and details of all training you offer.

Name .....

Address .....

City ..... State .....

(I understand no Salesman will call)




Popular and Fast Moving . . .

"ILLINI

# ELECTROMITE

## CONDENSERS"

Time Tested  
Quality

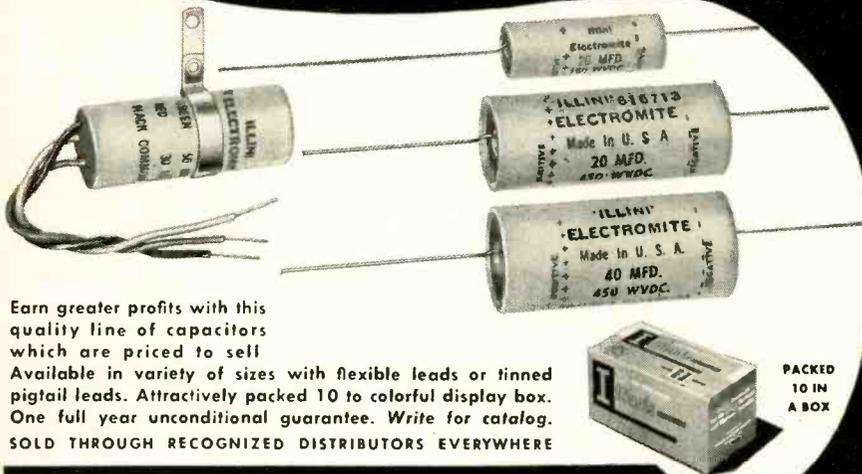

Earn greater profits with this quality line of capacitors which are priced to sell Available in variety of sizes with flexible leads or tinned pigtail leads. Attractively packed 10 to colorful display box. One full year unconditional guarantee. Write for catalog. SOLD THROUGH RECOGNIZED DISTRIBUTORS EVERYWHERE

Telephone: EVergade 4-1300

**ILLINOIS CONDENSER COMPANY**  
1616 N. Throop Street • Chicago 22, Illinois

## ENGINEERING

Prepare for unlimited opportunities of the Electronic Age! Earn your B.S. DEGREE IN 27 MONTHS in Aeronautical, Chemical, Civil, Electrical or Mechanical Engineering; in 36 MONTHS in Mathematics, Chemistry, Physics. Intensive, specialized courses. Comprehensive training in electronics, television, advanced radio theory and design, math, nuclear physics and elec. eng. Engineering Science preparatory courses. Low rate. Graduates in demand. Spacious campus; 20 bldgs., dorms, gym, playing field. Earn part of your expenses in Fort Wayne. G.I. approved. Enter March, June, Sept., Dec. Catalog. **INDIANA TECHNICAL COLLEGE**  
1719 E. Washington Blvd., Fort Wayne 2, Indiana  
Please send me free information on B.S. ENGINEERING DEGREE IN 27 MONTHS as checked.  
 Electronics  Chemical  Aeronautical  
 Civil  Mechanical  Electrical  
B.S. DEGREE IN 36 MO. in: Math  Chem.  Physics   
Name.....  
Address.....




## CONVERT TO COLOR TV

**COLORDAPTOR**—A simple 10-tube circuit and rotating color wheel converts any-size black-and-white TV, direct view or projection, to receive compatible color TV. **COLORDAPTOR** is simply attached to TV set, does not affect normal operation and can be built from parts experimenters have on hand.  
Complete specifications including theory of operation, complete simplified construction plans, schematic and sample color filters \$1.95  
Essential parts kit containing all special parts—coils, delay line, crystal, color filters—  
Up to 16" \$19.95 17" and \$20.95  
sets— larger—  
All other COLORDAPTOR parts, kits, motors, etc. available.  
**COLORDAPTOR**, 1798 Santa Cruz, Menlo Park, Calif.
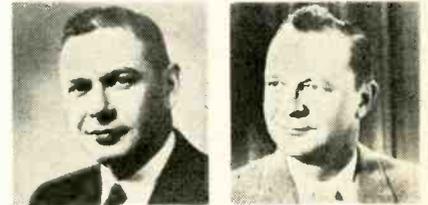
# BUSINESS and PEOPLE

Joseph N. Benjamin (left), former executive vice president of Pilot Radio Corp. has been appointed president of the Bogen-Presto Div. of the Siegler Corp., Paramus, N. J., where he will direct all activities of the high-fidelity



and recorder manufacturer. John G. Brooks, president of the Siegler Corp., has been named to the board of directors of the Electronic Industries Assn. (EIA).

Robert C. Sprague (right), board chairman of the Sprague Electric Co., North Adams, Mass., congratulates president Harry Kalker, of Sprague



Products Co., who has headed the subsidiary for the 25 years of its existence. Founded in 1933, it followed the establishment of the parent company by 7 years.

Philip M. Pritchard has been named marketing manager for entertainment electronic components by General Instrument Corp., with headquarters in Newark, N. J. He will be responsible for the marketing of the company's TV and radio components. He was formerly general sales manager, Parts Div., Sylvania.



C. R. (Russ) Robertson, sales manager, was elected vice president-sales by Weller Electric Corp., Easton, Pa., manufacturer of soldering guns and other tools.



H. D. Johnson, vice president and director of the Hickok Electrical Instrument Co., Cleveland, has been ap-

servicemen everywhere insist on the GENUINE

# "NO NOISE"


# big 3

Beware Of Cheap Substitutes!


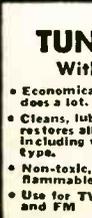
## NO-NOISE NEW RUBBER COAT SPRAY

• Insulates where applied  
• Protects indelibly  
• Prevents arcing, shorting, corrosion  
• Waterproofs thoroughly  
• Non-inflammable  
• Contains no plastic  
6 Oz. Spray Can  
**\$3.25**  
Not To Servicemen



## NO-NOISE TUNER-TONIC With PERMA-FILM

• Economical—a little does a lot.  
• Cleans, lubricates, restores all tuners, including water type.  
• Non-toxic, non-inflammable  
• Use for TV, radio and FM  
6 Oz. Aerosol Can  
**\$3.25**  
NET to Servicemen

## NO-NOISE VOLUME CONTROL and CONTACT RESTORER



• Cleans • Protects • Lubricates  
NOT A CARBON TET SOLUTION  
2 Oz. Bottle 6 Oz. Spray Can  
**\$1.00 \$2.25**  
Not To Servicemen Not To Servicemen

**ELECTRONIC CHEMICAL CORP.** 813 Communipaw Avenue Jersey City 4, N. J.

pointed director of marketing as part of the company's expansion.

Myron S. Friedman (left) has been promoted to manager of branch operations of all stores owned by the Radio Shack Corp., Boston—two in Boston



and one in New Haven. Alfred E. Coe joins the company as manager of the Amateur Sales Div.

Dr. Philip N. Hambleton became supervisor of research and development—tubes for CBS-Hytron, Danvers, Mass. He was previously senior physicist in the Tube Research and Development Laboratory.



Gordon R. Vance was elevated to manager, sales coordination, distributor sales, RCA Electron Tube Div. He has been manager product controls—industrial tubes, in the Distributor Products Dept.



Harold J. Adler was appointed vice president in charge of operations for Shure Brothers Inc., Evanston, Ill., manufacturer of microphones and electronic components. He has been vice president of the Edwin I. Guthman Co., engineering director of Hallcrafters and chief electrical engineer of the Sentinel Radio Co.



Walter L. Brough has been named to the new post of manager, Manufacturing Div., OR-Radio Industries Inc., Opelika, Ala. He was formerly executive vice president of Hercules Motors Corp., Canton, Ohio.



Unit production and sales		First 9 months	
	1958	1957	
TV Set Production	3,572,189	4,589,164	
Radio Set Production	8,178,821	10,376,354	
FM Radio Production	176,061	not given	
TV Retail Sales	3,468,090	4,452,081	
Radio Retail Sales	*4,903,676	5,840,372	
TV Picture Tube Sales	5,844,665	7,308,552	
Receiving Tube Sales	291,718,000	341,663,000	
Transistor Sales	30,387,277	17,842,300	

\* Excluding auto receivers  
Source—EIA

# GIANT NEW YEAR'S SALE OF LEKTRON POLY-PAKS®

## OVER 500,000 SOLD AT \$1 EACH!

# 88¢

### FREE! Buy 10 Poly-Paks, PICK ELEVENTH FREE!

### FREE! Surprise Gift With Every Order

- 70 ONE-WATTERS**  
Asstd. value carbon resistors. 5% Reg. \$12. **88¢**
- 100 HALF-WATTERS**  
Asstd. value carbon resistors, incl. 5% Reg. \$12. **88¢**
- 70 HI-Q RESISTORS**  
Carbon, 1% Ohmite, 1% tool 1/2, 1 & 2 W; 10 ohms to 10 megs. 2 lbs. Reg. \$13. **88¢**
- 20 CAMEL HAIR BRUSHES**  
100% pure bristle, sizes 1-6. Reg. \$2.50. **88¢**
- 1500 PCS. HARDWARE**  
Nuts, screws, washers, etc. 1 1/2 lbs. Reg. \$6. **88¢**
- 5-IN-1 DRILL BIT**  
Reams, saws, shapes, drills, copes, Flts **88¢**
- 8 GERMANIUM DIODES**  
w/long leads. Glass sealed. Reg. \$5. **88¢**
- 60 SUB-MINI RESISTORS**  
3/4" long, 20 values; 1/4 W, to 10 megs. Reg. \$6. **88¢**
- 70 TUBULAR CONDENSERS**  
Paper, molded, oil, porc., .0002 to .5mf. to 1000 V. 2 lbs. Reg. \$14. **88¢**
- 300 FT. HOOKUP WIRE**  
Tinned, asstd colors, sizes. 2 lbs. Reg. \$5. **88¢**
- POSTAGE STAMP MIKE**  
Crystal; 100 to 8,000 cycles-per-sec. 1 lb. Reg. \$7. **88¢**
- 70 TERMINAL STRIPS**  
Solder lug & binding; to 20 terminals. 2 lbs. **88¢**
- 75 MICA CONDENSERS**  
00025 to 0 to 200 V. Silver, too. 25 values. Reg. \$28. **88¢**
- SYLVANIA TV MIRROR**  
10x12" stainless steel. Many uses! 2 lbs. Reg. \$4. **88¢**
- 40 TUBE SOCKETS**  
4 to 9-pin; ceramic, mica, shield-based incl. 2 lbs. Reg. \$10. **88¢**
- NEW FOR '59! Do-It-Yourself-N-Save SIX TRANSISTOR RADIO KIT**  
All parts. Includes carrying case, batteries, instructions. (Less transistors, diodes, tube, etc.) Wt. 2 lbs. **\$15.99**
- 525 SURPRISE PACK!**  
Large & varied asst. radio & TV parts. 3 lbs. **88¢**
- 75-PC. RESISTOR SPECIAL!**  
WW precision, carbon, variable, mini types. 3 lbs. Worth \$15. **88¢**
- 60-PC. CONDENSER SPECIAL!**  
Molded, paper, ceramic, oil, mica, discs. 2 lbs. variables. **88¢**
- 10 ELECTROLYTICS**  
Radio, TV, 10-500 mf to 450 VDC. 3 lbs. Reg. \$12. **88¢**
- 12 POLY BOXES**  
Clear plastic, hinged. Asstd. sizes. 1 lb. **88¢**
- 125 CERAMIC CONDENSERS**  
Hi-Q discs, tubulars. To .01 mf. 2 lbs. Reg. \$12.50. **88¢**
- 10 PANEL SWITCHES**  
Asstd. 115 VAC, power, multiple circuit & SPST, DPST, DPDT. 2 lbs. Reg. \$5. **88¢**
- 70 COILS, CHOKES**  
IF, RF, ant., slug-tuned, too. 3 lbs. Reg. \$15. **88¢**
- 400-FT. HOOKUP WIRE**  
Factory-cut for hobby use. Tinned, w/asstd. insulation, colors. 3 lbs. **88¢**
- 40 PRECISION RESISTORS**  
1% 1/2 & 1W; carbon; 1/2 & WW. 100 ohms to 1 meg. Reg. \$17. **88¢**
- 60 KNOBS, RADIO & TV**  
Asstd. colors, insulation. Some worth \$1 ea. 2 lbs. Reg. \$17. **88¢**
- 35 POWER RESISTORS**  
WW 5 to 50W, to 10,000 ohms; incl. vitreous. 3 lbs. Reg. \$15. **88¢**
- 20 PRINTED CIRCUITS**  
Built-in R/C circuits, incl. integrals. **88¢**
- 40 HI-Q CONDENSERS**  
Finest porcelain. NPO a top! 1 lb. Reg. \$6. **88¢**
- 15 VOLUME CONTROLS**  
Incl. duals; some w/switch. To 1 meg. 2 lbs. Reg. \$12. **88¢**
- 8 TRANSISTOR SOCKETS**  
Mica-filled. For sub-mini tubes. **88¢**
- SUN BATTERY**  
Similar to famed B2M. 1" long. Reg. \$2.50. **88¢**
- 15 ROTARY SWITCHES**  
Asstd. gangs. 3 lbs. Reg. \$12. **88¢**
- 15-PC. TWIST DRILL SET**  
1/16" thru 1/4" by .04ths, w/call. brated case. Reg. \$3. **88¢**
- 40 DISC CONDENSERS**  
Water-thin, .01 mf. Reg. \$5. **88¢**
- 4 OUTPUT TRANSFORMERS**  
50L8, etc. 3 lbs. Reg. \$8. **88¢**
- 8-PC. NUTDRIVER KIT**  
\$3 value. Plastic handle, 3/16, 7/32, 1/4, 5/16, 11/32, 3/8, 7/16" steel socket wrenches in plastic case. 1 lb. **88¢**
- WORLD'S SMALLEST RADIO**  
2x1x1". Kit includes loopstick, jacks, diode, etc. w/instructions. 1 lb. Reg. \$3. **88¢**
- 2 P-N-P TRANSISTORS**  
Popular make. For hundreds of projects. \$5 value. **88¢**
- 4 POWER WOOD BITS**  
Hi-Q steel. 5/8, 1, 3/4, 1" For drills, presses. 5" long. **88¢**
- WIRE STRIPPER**  
Strips & cuts hook-up wire, sizes #18 thru #22. Wt. 1 lb. **88¢**
- 2 MIKE TRANSFORMERS**  
Carbon, imp. 100 to 100K ohms. Leads enclosed. 2 lbs. Reg. \$10. **88¢**
- 2 VARI-LOOPSTICKS**  
Adj. 540-1500 Kcs. Transistor radios, etc. 1 lb. **88¢**
- 30 MOLDED CONDENSERS**  
Assorted. Finest made! Wt. 2 lbs. **88¢**
- 2 TRANSISTOR IF'S**  
Double-tuned. Only 1/2" square. 450 Kcs. **88¢**
- 60 PLUGS, RECEPTACLES**  
Audio, powerspeaker etc. 2 lbs. **88¢**
- 150 CARBON RESISTORS**  
1/2 to 2 W; 15 ohms to 1 meg. incl. insulated types. 2 lbs. **88¢**
- TV PIC BOOSTERS**  
Parallel, 6-wire, extends pic tube life. Wt. 1 lb. **88¢**
- 3 AC-DC CHOKES**  
for power supplies 50 to 200 ma. Open frame. 3 lbs. Reg. \$8. **88¢**
- TEN 3-SECOND TIMER**  
geared. 2 lbs. Precision Reg. \$30. **88¢**
- 40-RECORD CADDY**  
Wrought Iron. Holds 40 records & albums. 3 lbs. Reg. \$2.99. **88¢**
- 7 SCREWDRIVERS/RACK**  
Asstd. screwdrivers w/ plastic handles, incl. Phillips. Wall rack. List \$3.50. 1 lb. **88¢**
- HOBBY BENCH VISE**  
Clamp type, fits tables, too. Many home, shop, hobby uses. Steel. 1 lb. **88¢**
- FILAMENT TRANSFORMER**  
115/1/60 cycles to 6.3 VCT @ 1.5A. 2 lbs. Reg. \$4. **88¢**
- 6 SILICON DIODES**  
Sylvania 1N22. 88¢
- 4 TRANSISTOR OSC. COILS**  
for printed circuit & transistor portable radios. Reg. \$5. **88¢**
- 5 ROLLS "MICRO" WIRE**  
Sizes #4 thru #32, for transistor & sub-mini circuits. 1 lb. **88¢**
- 6 FERRITE CORES**  
Asstd. to 6" flat & round. Hi-Q ferrite. 2 lbs. Reg. \$5. **88¢**
- JEWELERS' PLIERS**  
Chrome plated, drop-forged steel. Side or diagonal cutters. For fine precision work. 1 lb. Reg. \$3. **88¢**
- 40 SUB-MINI CONDENSERS**  
For transistor, printed circuit work. 1 lb. Reg. \$7. **88¢**
- MINI-METER**  
1 3/4" diameter. 0-6 amps. AC. 1 lb. **88¢**

WRITE FOR FREE 16-PAGE FLYER OF BARGAINS!

# LEKTRON

131 Everett Ave.  
CHELSEA 50, MASS.

**HOW TO ORDER** Check items wanted. Return entire ad w/check or M.O. including sufficient funds. C.O.D. orders 25% down; rated, net 30 days. Print name, address WITH POSTAL ZONE NO., amount money enclosed, in margin. (Canada Postage, 46¢ 1st lb., 26¢ ea. add'l. lb.) EXPORT ORDERS INVITED.

SAVE TIME with



**Model ES-102**  
ONLY \$15.95 DEALER NET

Less than you pay for the old rigid capacitors.  
Carry it anywhere—measures only 4 1/4" H x 4 3/4" W x 2 1/4" D

**NEW!**

## SENCORE Electro-Sub

Check all ELECTROLYTIC CAPACITORS in Seconds!

Merely select the electrolytic and substitute it. 10 big electrolytics from 4 to 350 Mfd. to safely substitute in any circuit from 2 to 450 volts.

... COMPLETELY SAFE—no arc or spark when connecting or disconnecting.

... AUTOMATIC CAPACITOR DISCHARGE—within seconds after releasing test switch by unique surge protector circuit.


... NO CAPACITOR HEALING—surge protector circuit prevents accidental healing of capacitor being "bridged" in service work.

See other SENCORE ads in this issue.

**SENCORE CORP.** 121 Official Rd., Addison, Ill.
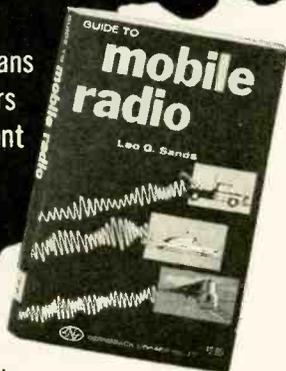
# AT LAST... the first complete new book on MOBILE RADIO

for  
 • service technicians  
 • engineers  
 • equipment buyers



## Guide to Mobile Radio

By Leo G. Sands  
 Gernsback Library Book No. 77  
 Paper cover edition. \$2.85

Mobile radio use in industry, government and civil defense has increased faster than prices and taxes since 1945. Yet good technical literature on it has lagged way behind. Just what is mobile radio? Where is it used? What are the circuits like? Can I service it? How do you judge one system against another? What are the limitations of different receivers and transmitters? This new book answers all your questions. Twelve big chapters cover everything you want to know about systems, unit and base stations, receivers, transmitters, power supplies, antennas, remote control, portable equipment, selective calling, maintenance, licensing, and the field survey.

This is an ideal book for the sales engineer, the purchasing agent and the service technician who wants to maintain and repair mobile equipment. If you want to know more about this vigorous new radio field, get your copy of **GUIDE TO MOBILE RADIO** today.

### OTHER HELPFUL G/L BOOKS

- ELECTRONIC PUZZLES AND GAMES—No. 70—\$1.95
- ELECTRONIC HOBBYIST'S HANDBOOK—No. 69—\$2.50
- BASIC AUDIO COURSE—No. 66—\$2.75
- TV—IT'S A CINCH—No. 62—\$2.90
- RAPID TV REPAIR—No. 60—\$2.90
- SERVICING RECORD CHANGERS—No. 59—\$2.90
- RADIO-CONTROL HANDBOOK—No. 53—\$2.25
- TELEVISION TECHNOTES—No. 46—\$1.50
- BASIC RADIO COURSE—No. 44 (Hard cover) \$2.25

See your distributor or use this coupon

Gernsback Library, Inc. 19A  
 154 West 14th St., New York 11, N. Y.

My remittance of \$..... is enclosed.  
 Please send me postpaid the books checked below.

- |   |   |
|---|---|
| <input type="checkbox"/> No. 77 Guide to Mobile Radio | <input type="checkbox"/> 70   |
| <input type="checkbox"/> 69                           | <input type="checkbox"/> 66 <input type="checkbox"/> 62 <input type="checkbox"/> 60 |
| <input type="checkbox"/> 59                           | <input type="checkbox"/> 53 <input type="checkbox"/> 46 <input type="checkbox"/> 44 |

name \_\_\_\_\_ please print

street \_\_\_\_\_

city \_\_\_\_\_ zone \_\_\_\_\_ state \_\_\_\_\_

## BUSINESS AND PEOPLE (Continued)

Electro-Voice Inc., Buchanan, Mich., has launched the largest promotion in its history for its high-fidelity speakers and enclosures, keyed to the theme, "Step Up to Stereo." Heavy national




and local advertising will feature a free stereo demonstration and a free 12-inch record recorded stereophonically on one side and monophonically on the other.

Service Instruments Corp., Addison, Ill., is offering a \$2.75 Sencore filament



checker free with each purchase of the Sencore TV bias supply and the Sencore Vibradaptor.

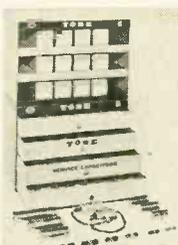Tobe Deutschmann Corp., Indianapolis, has announced the Tobe Twins, enameled metal merchandising cabinets



containing 12 twist-prong capacitors, 16 Jet tubular electrolytics and 73 TPM mylar tubulars.


Tung-Sol Electric Inc., Newark, N. J., is merchandising its performance-matched 6550 and 5881 beam power amplifier tubes twin-packed in pairs for optimum hi-fi performance.

Jensen Industries, Forest Park, Ill., calls its new phono needle display the dangling dozen. It holds 12 needle packages in clear plastic bags. As each is sold, an automatic "sold" signal reminds the dealer to replace the needle.

Michigan Magnetics' new Distributor Div., Chicago, is shipping tape recorder



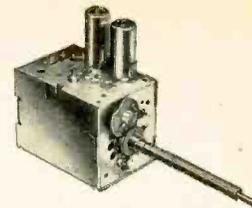heads to jobbers in a new package. The clear plastic box contains a die-cut urethane pad into which the head fits precisely. Every package contains 20 feet of recorder tape bearing a 10,000 cycle note for proper head installation. **END**



## Now YOU can get TUNERS repaired, or replaced, in a hurry!

### Send them to TARZIAN!

• Sarkes Tarzian, Inc., announces a new tuner repair service and factory replacement program for Tarzian-manufactured tuners. Distributors, dealers and servicemen will welcome this direct factory service program which is designed to take delay and confusion out of the tuner repair business.

We're set up to offer a 48 hour service from the date of receipt to shipment to you.

Cost is reasonable, too. Only \$7.50 per unit (\$15 for UV combinations) and that includes ALL replacement parts! Both repaired—or exchange units if available from stock—carry a 90 day warranty against defective workmanship and part failure.

Replacements will be offered at these current prices\* on units not repairable:

- VHF 12 position tuner... \$17.50
- VHF 13 or 16 position tuner... 19.50
- VHF/UHF combination... 25.00
- UHF only... 15.50

\*Subject to change

When inquiring about tuner service, always refer to tuner by part number. When inquiring about direct replacements for tuners other than Sarkes Tarzian-manufactured, please indicate tube complement, shaft length, filament voltage, series or shunt heater. Use this address for quickest service:

## SARKES TARZIAN, Inc.

Attn: Service Mgr., Tuner Division  
 East Hillside Drive  
 Bloomington, Indiana



TARZIAN Electronic Product and Services include TELEVISION TUNERS . . . SELENIUM AND SILICON RECTIFIERS . . . BROADCAST EQUIPMENT . . . AIR TRIMMERS . . . TV STATIONS WTTV and WPTA, and RADIO STATION WTTs.

# LITERATURE

Any or all of these catalogs, bulletins, or periodicals are available to you on request direct to the manufacturers, whose addresses are listed at the end of each item. Use your letterhead—do not use postcards. To facilitate identification, mention the issue and page of RADIO-ELECTRONICS on which the item appears. UNLESS OTHERWISE STATED, ALL ITEMS ARE GRATIS. ALL LITERATURE OFFERS ARE VOID AFTER SIX MONTHS.

**ELECTRONIC EQUIPMENT Catalog No. 69** covers thousands of industrial electronic, amateur, radio, TV and hi-fi items in its 388 pages. It's fully illustrated and contains a product and manufacturer index.—Newark Electric Co., 223 W. Madison St., Chicago 6, Ill.

**RECORDING TAPE Cross Reference Chart**, available to dealers, gives catalog number and trade name for each type of tape made by 4 leading manufacturers. Reverse side contains playing-time chart. — ORRadio Industries Inc., Shamrock Circle, Opelika, Ala.

**WINDOW POSTER** boosting the independent TV technician, with legend, "Your TV Technician Guarantees You the Best Seat in the House."—Sprague Products Co., North Adams, Mass. 10c.

**SILICON CONTROLLED RECTIFIER**, newly developed semiconductor, is described in a 17-page booklet, *Application Notes for ZJ-39A Silicon Controlled Rectifier*, publication No. ECG-327. General circuit design considerations, firing circuit design and typical applications are covered.—General Electric Co., Semiconductor Products Dept., Syracuse, N. Y.

**PHONO AND RECORDER Drive Replacement Chart** is offered to qualified electronic technicians. The 21 x 34-inch chart has actual-size illustrations of each unit, with price, conversion and cross-reference information. — Walsco Electronic Mfg. Co., 100 W. Green St., Rockford, Ill.


**STEREO RECORDS AND TAPES** of most major manufacturers are listed in a new catalog, *Stock No. 68 R 566*. More than 200 discs and nearly 500 tapes are included.—Allied Radio Corp., 100 N. Western Ave., Chicago 80, Ill.

**SPEAKERS AND ENCLOSURES** and dividing networks in the complete JBL line are illustrated and described in *catalog SC504*. A table gives prices at a glance for every combination of speakers and enclosures.—James B. Lansing Sound Inc., 3249 Casitas Ave., Los Angeles 39, Calif.

**KIT CATALOG**. Complete indexed 1959

JANUARY, 1959

# TELEVISION

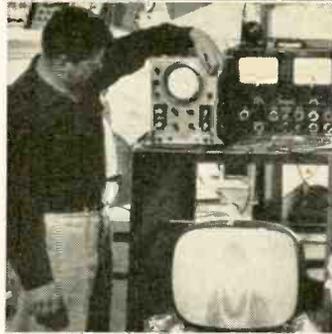

**AT HEADS YOU LEARN BY DOING IN MODERN ELECTRONICS LABORATORIES**

## HEALD ENGINEERING COLLEGE

Established 1863  
Van Ness at Post, RE  
San Francisco, Calif.

Never before in American history has the need been so great for Trained Engineers and Technicians. No other type of training can compare with actual shop practice you get at Healds under expert instructors.

### Bachelor of Science Degree, 27 Months

- Radio-TV Technician including Color TV (12 Months)
- Electronics Technician (12 Months)
- Industrial Electronics Technician (12 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)

Heald College ranks FIRST West of the Mississippi in "Who's Who in America"

Approved for Veterans  
DAY AND EVENING CLASSES

Write for Catalog and Registration Application.  
New Term Starting Soon.

Your Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_


## TAPE RECORDERS



### HI-FI COMPONENTS Sleep Learn Kits

**MERITAPE** | **UNUSUAL VALUES**  
Low cost, high quality recording | **FREE**  
tape, in boxes or cans. | 1959 CATALOG  
**DRESSNER, 69-02RE 174 St., Flushing 65, N.Y.**

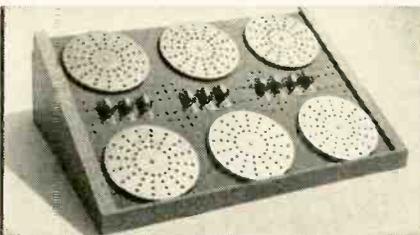Can you think . . .  
faster than this Machine?



Control Panel of GENIAC set up to do a problem in check valve research.

Be careful before you answer. GENIAC® the first electrical brain construction kit is equipped to play tic-tac-toe, cipher and enigma codes, convert from binary to decimal, reason (in syllogisms) as well as add, subtract, multiply and divide. Specific problems in a variety of fields—actuarial, policy claim settlement, physics, etc., can be set up and solved with the components. Connections are solderless and are completely explained with templates in the manual. This covers 125 circuits and shows how new ones can be designed.

You will find building and using GENIAC® a wonderful experience; one kit user wrote us: "This kit has opened up a new world of thinking for me." You actually see how computing, problem solving, and game play (Tic-tac-toe, nim, etc.) can be analyzed with Boolean Algebra and the algebraic solutions transformed directly into circuit diagrams. You create from over 400 specially designed and manufactured components a machine that solves problems faster than you can express them.

Schools and colleges, teachers of science or math, engineering, philosophy or psychology will find these excellent demonstrators of circuitry, solutions in symbolic logic, theory of numbers, cybernetics, and automation.

Note: Teachers take advantage of our 10% discount to educational institutions and for group purchases. SEND for your GENIAC® kit now. Only \$19.95 with over four hundred components and parts, fully illustrated manual and wiring diagrams. We guarantee that if you do not want to keep GENIAC® after one week you can return it for full refund.

### MAIL THIS COUPON

Oliver Garfield Co., Dept. RE-19  
108 East 16th Street, New York 3, N.Y.

Please send me:  
1 GENIAC Electric Brain Construction Kit and Manual.

- \$19.95 (East of Mississippi) \_\_\_\_\_
- \$20.95 (Elsewhere in United States) \_\_\_\_\_
- \$21.95 (Outside the United States) \_\_\_\_\_

Returnable in seven days for full refund if not satisfied.

I enclose \$\_\_\_\_\_ in full payment.  
My name and address are attached.

## MAIL ORDER HI-FI

You can now purchase all your HI-FI from one reliable source and be assured of perfect delivery. Carston makes delivery from NY stock on most HI-FI Records and Tapes within 24 hours. SEND US A LIST OF YOUR HI-FI REQUIREMENTS FOR OUR WHOLESALE QUOTATION and our FREE wholesale catalogue.

**CARSTON STUDIOS** 215-RD E. 88 St.  
New York 28, N. Y.

## Grommes Little Genie HIGH FIDELITY KITS

• LAYER BUILT • COLOR GUIDE

Before you build another kit, see this new method of kit assembly. Each kit complete with all parts and instructions.

"So simple . . . it's like magic"



**20PG8-K 20 Watt Amplifier** with built-in pre-amplifier and all controls. Net 59.50  
**LJ-6K 10 Watt Amplifier** (Little Jewel). Has built-in preamplifier and record compensator on phono channel. Net 24.95  
**207A-K Hi-Fi Preamplifier** (Self-Powered). Feedback circuit with 10 controls. Net 44.50  
**250-K 60 Watt Basic Hi-Fi Amplifier**. For use with a preamplifier (such as 207A-K). Net 79.50

Grommes—Div. of Precision Electronics, Inc.  
Dept. RE-1, 9101 King St., Franklin Park, Ill.

Name of Dealer \_\_\_\_\_  
 Send complete Kit details.  
Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

# NOW 2 ASSEMBLE-IT-YOURSELF

## Schober ELECTRONIC ORGANS


SAVE HALF  
NO SPECIAL SKILLS  
PAY KIT-BY-KIT

Now you can afford an electronic organ. Whether you choose the full Concert model or the smaller Console, you have an organ equal to any made by the foremost manufacturers. In addition, you save over 1/2 the cost because you assemble it yourself...and you enjoy the thrill of achievement. Too, you purchase each kit only when you are ready for it.



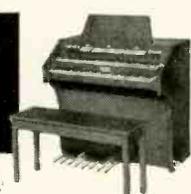**CONCERT MODEL**

- ☆ TWO FULL SIZE PIPE-ORGAN MANUALS, 122 KEYS
- ☆ OCCUPIES 3'5" x 4'7" FLOOR SPACE
- ☆ 26 STOPS AND COUPLERS
- ☆ 32 BASS PEDALS
- ☆ ASSEMBLED CONSOLE
- ☆ CONFORMS TO AMERICAN GUILD OF ORGANISTS SPECIFICATIONS FOR PIPE ORGANS
- ☆ COMPLETE STEP-BY-STEP INSTRUCTIONS



**CONSOLE MODEL**

- ☆ OCCUPIES ONLY 2' x 3'2" FLOOR SPACE
- ☆ TWO FULL SIZE PIPE-ORGAN MANUALS, 122 KEYS
- ☆ 22 STOPS — ABOVE-KEYBOARD TABS
- ☆ 13 HEEL-AND-TOE BASS PEDALS
- ☆ 7 FULL OCTAVES OF TONE (DOWN TO 32 CPS)
- ☆ BUILT-IN SPEAKERS OPTIONAL
- ☆ ASSEMBLED CONSOLE
- ☆ COMPLETE STEP-BY-STEP INSTRUCTIONS

**2 different MODELS  
2 different SIZES  
2 different PRICES**

10" LP RECORD DEMONSTRATING BOTH MODELS  
AVAILABLE FOR \$2, REFUNDABLE UPON PURCHASE

FREE NEW 1959 EDITION OF 16 PAGE ILLUSTRATED BOOKLET ON REQUEST

Write Now — See What Fine Instruments You Get At Such Great Savings

The **SCHOBER ORGAN Corporation** • 2248-B BROADWAY • NEW YORK 24, N.Y.

SCHOBER KITS ALL OVER THE WORLD

☆ Designed by Richard H. Dorf.

### OPPORTUNITY ADLETS

Rates—50¢ per word (including name, address and initials). Minimum ad 10 words. Cash must accompany all ads except those placed by accredited agencies. Discount, 10% for 12 consecutive issues. Misleading or objectionable ads not accepted. Copy for March issue must reach us before January 15, 1959.

**RADIO-ELECTRONICS,**  
154 West 14 St., New York 11, N. Y.

HIGH-FIDELITY SPEAKERS REPAIRED. AMPRITE Speaker Service, 70 Vesey St., New York 7, N.Y. BA 7-2580.

CASH PAID! Sell your surplus electronic tubes. Want unused, clean transmitting, special purpose, receiving, TV types, magnetrons, klystrons, broadcast, etc. Also want military & commercial lab test and communications gear. We swap 100. for tubes or choice equipment. Send specific details in first letter. For a fair deal write, wire or telephone: BARRY, 512 Broadway, New York 12, N.Y. Walker 5-7000.

RECORDERS. Hi-Fi. Tapes. Free Wholesale Catalogue. CARSTON, 215-T East 88th St., New York 28, N.Y.

STEREO TAPE RENTALS. For the very best at lowest prices. Write CALIFORNIA TAPED MUSIC ASSN., 765 El Camino Real, Redwood City, Calif.

DISCOUNTS UP TO 50% on Hi-Fi amplifiers, tuners, speakers, tape recorders, individual quotations only, no catalogs. CLASSIFIED HI-FI EXCHANGE, 2375 East 65th Street Brooklyn 34, N.Y.

LABORATORY QUALITY equipment and Military Surplus Electronics bought, sold. ENGINEERING ASSOCIATES, 434 Patterson Road, Dayton 9, Ohio.

DIAGRAMS FOR REPAIRING RADIOS \$1. Television \$2. Give make, Model. DIAGRAM SERVICE, Box 672-RE, Hartford 1, Conn.

HAVE AMPEX—Will Duplicate. BOB'S TAPE SERVICE, 7909 Lazy Lane, Ft. Worth 18, Texas.

ALL MAKES OF ELECTRICAL INSTRUMENTS AND TESTING equipment repaired. HAZELTON INSTRUMENT Co., 128 Liberty Street, New York 9, N.Y.

TELEVISION Tuner Repairs. DAN'S TELEVISION LABORATORY, 619A Sunrise Highway, Babylon, N.Y.

DIAGRAMS FOR REPAIRING RADIOS \$1. Television \$1. Give make, Model. DALE CO. 319 West 14th St., New York.

NEW BOOKS: GUIDED MISSILES, 575 pages by USAF, \$3.50; BASIC ELECTRONICS, 728 pages by USN, \$2.25; RADIO REPAIR, 177 pages by USA, \$2. Post paid. No C.O.D.'s FOSTER'S, Box 703, Silver Spring, Maryland.

ELECTRONIC SUPPLIES Wholesale—Canadian Mailing Lists—Write MASTER KIT COMPANY—Box 206—Belleville, Ont., Canada.

CAMERA Repairsmen greatly needed! You can learn manufacturers' service methods at home, in your spare time! Free, big illustrated book tells how! Write today. NATIONAL CAMERA REPAIR SCHOOL, Dept. RE-12, Englewood, Colorado.

JOBS—HIGH PAY: USA, So. America, The Islands. All trades. Many companies pay fare. Write Dept. 717, NATIONAL EMPLOYMENT INFORMATION, 1020 Broad, Newark, N.J.

PROFESSIONAL Electronic Projects—Organs, Timers, Intercoms, Counters, etc. \$1 each. List Free. PARKS, Box 1665, Lake City Station, Seattle 55, Wash.

FM TUNERS, 88-108 megacycles, 4 tubes complete, \$12.95. GRUTMAN, 1 E. 167 St., Bx. 52, N. Y.

TRADE-IN TV \$6 up, also color. Write JUSTIS, Newport, Wilmington, Delaware.

MOTOR GENERATOR SETS—200,000 volt, 2 micro-ampere Van de Graaf type. Shipped knock down, assemble in 20 min. \$19.50 postpaid. MORRIS AND LEE, 439 Elm, Buffalo 3, N. Y.

DISCOUNTS to 50%. recorders, tapes, hi-fi components, consoles, photograph equipment. Request specific prices only. Free Stereo Catalog. LONG ISLAND AUDIO & CAMERA EXCHANGE, 3 Bay 26th St., Brooklyn 14-R, N. Y.

LEARN WHILE ASLEEP! Exciting details free. RESEARCH ASSOCIATION, Box 24-HH, Olympia, Washington.

TEEVIE Shop Forms. PRINTED your name. Service, Repair Orders, Invoices, Statements. Letterheads 5 1/2 x 8 1/2 1,000 \$5.95. ROYAL Box 821, Chicago 90, Ill.

PHONOGRAPH RECORDS cheap, postpaid. Catalogue. PARAMOUNT, Box 242-T, Williamsport, Penna.

NEW TUBES: not mechanical or electrical rejects; not washed and/or rebranded. 80% famous brands. SONORET, 36 Woodbury, Wilkes-Barre, Penna.

UNUSUAL VALUES. Hi-Fi components, tapes and tape recorders. Free catalog RE. STEREO CENTER, 51 W. 35 St., New York 1, N. Y.

MATHEMATICS. Home study. Elementary through university levels. UCSM, Philadelphia 26, Penna.

SONGPOEMS and LYRICS WANTED! Mail to: TIN PAN ALLEY, INC. 1650 Broadway, New York 19, N. Y.

RECORDING TAPE—Nationally advertised. Below wholesale. WOLFE ELECTRONICS, 2506 Hoffman, Baltimore 13, Md.

### LITERATURE (Continued)

catalog has 57 pages of make-it-yourself projects covering a wide variety of test instruments, amateur, hi-fi and marine equipment.—Heath Co., Benton Harbor 20, Mich.

**STEREO INFORMATION.** *Bulletin E-305, "An Introduction to Stereophonic Sound,"* describes how a stereo disc is produced and tells what is needed for stereo playback. *E-306, "Hints on Using the Columbia CD Stereo Cartridge,"* describes the mechanics of the cartridge and recommends how to install and equalize it.—CBS-Hytron Advertising Service, Parker St., Newburyport, Mass.

**TRANSFORMERS** for all uses are listed in two 32-page catalogs. *No. S-104* has data on Stancor transformers, chokes and coils for TV, radio, industrial and communications applications. *CT8-58* lists the Chicago line of heavier-duty transformers and reactors and a series of special transformers.—Chicago Standard Transformer Corp., 3501 W. Addison St., Chicago 18, Ill.

**SLIDE-RULE** catalog and buying guide entitled *Slide Rule—May I Help?* is an attractive 24-page 2-color booklet.—Keuffel & Esser Co., Adams and 3d Sts., Hoboken, N. J.

**RELAY CATALOG C-9** has 66 pages listing thousands of types of relays of many manufacturers.—Relay Sales Inc., Box 186, West Chicago, Ill.

**FM TUNERS** with crystal-oscillator circuits for home use are described and illustrated in a new catalog.—Karg Laboratories Inc., 30 Meadow St., South Norwalk, Conn.


**MINIATURIZED VTVM'S** are described in a 4-page short-form catalog *No. 10-A*. Included are panel-mounted models, single- and multi-range, dc and ac, half-relay rack styles, militarized and commercial models.—Metronix Inc., Chesterland, Ohio.

**SILICON SOLAR CELLS** now commercially available are described in 4-page *Technical Information Bulletin 32-58*, which gives complete design parameters and application notes on 9 types of cells with spectral response curves and other data.—Hoffman Electronics Corp., Semiconductor Div., 930 Pitner Ave., Evanston, Ill.

**1958 MASTER INDEX** lists diagrams and service information in the "Most-Often-Needed" series of service manuals covering radio sets from 1926 through 1958 and TV sets from 1948 to date.—Supreme Publications, 1760 Balsam Rd., Highland Park, Ill. 5¢ for RADIO-ELECTRONICS readers. END
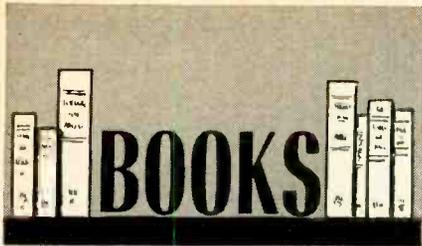
### CORRECTION

A reader called attention to an error in the Heathkit Mohawk communications receiver circuit in December's issue. In the power supply diagram, bottom left corner, page 100, the line switch's right hand terminal should go to the lower end of the power transformer primary. The ac outlet connects directly across the primary.



**MOST-OFTEN-NEEDED 1958 RADIO DIAGRAMS AND SERVICING INFORMATION.** Compiled by M. N. Beitman. Supreme Publications, 1760 Balsam Road, Highland Park, Ill. 8 1/2 x 10 1/2 in., 192 pp. \$2.50

A comprehensive selection of original manufacturers' service information covering 25 brands of phonographs and home, portable and auto radios.

**SINGLE SIDEBAND FOR THE RADIO AMATEUR (2nd Edition—1958).** American Radio Relay League, West Hartford 7, Conn. 6 1/2 x 9 1/2 in., 262 pp., including a 52-page catalog. \$1.50 in US proper, \$1.75 elsewhere.

A digest of over 50 articles on single-sideband reception and transmission compiled from *QST* magazine. Fully illustrated with photographs, diagrams, charts and tables. Ideal as a reference or training text for class or home study.—RFS

**STEREOPHONIC SOUND,** by Norman H. Crowhurst. John F. Rider Publisher, Inc., 116 W. 14 St., N. Y. 11, N. Y. 5 1/2 x 8 1/2 in. 118 pp. \$2.25. (Published 1957)

This well-known author begins with a clear discussion of binaural listening and stereo sound. Then he tells the reader how to obtain maximum pleasure on a minimum budget. Key points are: suitable systems for the home; choice and placement of speakers; radio, disc and tape methods; how to record. All are clearly described and illustrated. Stereo disc recording is, however, given limited treatment, since it was then in the experimental stage.

A chapter on stereo for theatres and auditoriums is also included.—IQ

**TV AND OUR SCHOOL CRISIS,** by Charles A. Siepmann. Dodd, Mead & Co., 432 Fourth Ave., N. Y., N. Y. 5 1/4 x 8 in., 198 pp. \$3.50.

Written by the chairman of New York University's Department of Communications, this nontechnical work reviews the experiences of schools with closed- and open-circuit TV and concludes that television offers promise of helping to solve many problems faced by education today and in the future.

**ELECTRONICS MADE SIMPLE,** by Henry Jacobowitz. Made Simple Books, Inc., 220 Fifth Ave., New York, N.Y., 8 x 10 1/2 in. 192 pp. \$1.

The title sounds like that of a "10 easy lessons" quickie, but this book is definitely not that. It is a serious text that can cover its wide range of topics only through concise wording, careful grading of subjects and omission of unimportant details.

The 18 chapters (plus appendix) cover such basic subjects as atomic  
(Continued on page 146)

# NOTICE!

Transistor users—2 new  Books for you.

## TRANSISTORS—Theory & Practice

Second Edition  
By Rufus P. Turner.  
Gernsback Book No. 75, Paper cover \$2.95

The first edition of this classic on transistor theory and use for the practical man sold over 30,000 copies! Now in answer to thousands of requests, here's a brand new revised and enlarged edition. Covers everything you want to know about transistors. Valuable chapters on theory, characteristics, circuits, design, construction, and care and handling. Ready now—get your copy while the first printing lasts.

### Other G/L Transistor Books

**Transistor Circuits—No. 63. \$2.75**

Another Turner triumph! A selection of scores of debugged transistor circuits for amplifiers, oscillators, power supplies, test instruments, etc.

**Transistor Techniques—No. 61. \$1.50**

A practical transistor handbook. Covers testing, performance, construction, measurements.

See your distributor

or use this coupon. ▶

## SERVICING TRANSISTOR RADIOS

By Leonard D'Airo.  
Gernsback Book No. 76,  
Paper cover edition \$2.90  
Hard cover edition \$4.60

Turn the challenge of servicing transistor radios into an opportunity to make more money. This veteran service and transistor technician shows you how. He gives you bench-tested techniques for finding and fixing transistor set troubles fast. Covers circuits, measurements, terms, fundamentals, techniques, hints and tips. Includes a chapter on auto radios. Keep this handy manual on your workbench for fast and profitable transistor radio servicing.

GERNSBACK LIBRARY, INC. 19  
154 West 14th St., New York 11, N. Y.

My remittance of \$..... is enclosed. Please send me the books checked. Postpaid.

No. 76—Servicing Transistor Radios  
 Paper cover ed. \$2.90     Hard cover ed. \$4.60  
 75     63     61

Name..... please print  
 Street.....  
 City..... Zone..... State.....

## ORDER by MAIL and SAVE! TV PICTURE TUBES

10BP4 ...\$ 7.95	17BP4 ...\$10.95	21AMP4 \$19.95
12LP4 ... 8.95	17CP4 ... 17.00	21ATP4 ... 20.95
14B/CP4. 9.95	17GP4 ... 17.60	21AUP4 ... 20.95
16DP4 ... 14.95	17HP4 ... 13.60	21EP4 ... 14.95
16EP4 ... 15.90	17LP4 ... 13.60	21FP4 ... 15.95
16GP4 ... 15.90	17QP4 ... 11.95	21WP4 ... 17.30
16KP4 ... 10.95	17TP4 ... 19.30	21YP4 ... 15.95
16LP4 ... 10.95	19AP4 ... 19.30	21ZP4 ... 14.95
16RP4 ... 10.95	20CP4 ... 13.90	24CP4 ... 23.95
16WP4 ... 15.20	20HP4 ... 17.95	24DP4 ... 26.95
16TP4 ... 10.95	21AP4 ... 22.10	27EP4 ... 39.95
17AVP4 ... 15.20	21ALP4 ... 20.95	27RP4 ... 39.95

27"—6 month guarantee—all others 1 year. Aluminized Tubes \$5.00 more than above prices. These prices are determined to include the return of an acceptable similar tube under vacuum.

ALL PRICES FOR CHICAGO, ILLINOIS. Deposit required, when old tube is not returned, refundable at time of return. 25% required on COD shipments. Old tubes must be returned prepaid. We ship anywhere.


WRITE FOR COMPLETE LIST.

—PICTURE TUBE OUTLET—  
3032 Milwaukee Ave., Chicago 18, Ill.  
Dickens 2-2048
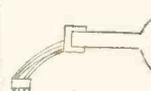
## FREE Biggest News Yet! FABULOUS ALL THIS FREE

- High Voltage Tester
- 3 Tubes (5y1) 1U4s
- 10 .006 Mica Cond 900V
- 2 1/2 Meg Controls w/switch
- 1 65 ma. Sel Rectifier (Federal)

with each purchase of new  
5" TV Test Tube & Adaptor



Replaces 8xP4  
No Ion Trap Needed  
OK for 110° Yoke  
Up 20,000 Volts

This Is The Day You've Been Waiting For...  
sale \$5.95

Write:  
**ZAMCO**  
88-43 77th Street Woodhaven, N.Y.  
Sorry No C.O.D.  
Include 50¢ For Postage. Check—Cash—Money Order.

## WANT TO SELL?—buy? trade? find out?

RADIO-ELECTRONICS Opportunity Adlets bring results—at low cost. Only 50c per word—minimum 10 words.

154 West 14th St. RADIO-ELECTRONICS New York 11, N.Y.

# NEW! "Do-It-Yourself" LAFAYETTE Kits



**LAFAYETTE'S**  
**1959 CATALOG**  
**260 GIANT-SIZE**  
**PAGES**  
**FREE!**

Complete listings of the NEWEST in Stereo and Monaural Hi-Fi, Short Wave, Audio, Transistor, and many other Lafayette electronics kits as well as thousands upon thousands of standard brand nationally advertised kits and electronic parts and components are described in LAFAYETTE'S GIANT NEW 260-PAGE CATALOG. SEND FOR IT—IT'S FREE! Just fill in coupon below and present it at any Lafayette store, or paste it on a postcard and send it to us. THAT'S ALL YOU HAVE TO DO to get your FREE 1959 LAFAYETTE CATALOG!

## LAFAYETTE RADIO ELECTRONIC KITS

- Include the very latest electronic advances.
- Are constantly being modernized by Lafayette's own Engineering Department, by a leading consulting engineering firm, and by your own recommendations.
- Are a product of Lafayette's 38 years of Electronic Leadership.



**SUPER-SENSITIVE PHOTOCCELL ELECTRONIC RELAY ... KT-133 12.95**

**"EXPLOR-AIR" 4-BAND RECEIVER ... KT-135 18.50**

**5-WATT PUSH-PULL AC-DC HI-FI AMPLIFIER KIT ... KT-92 10.95**


**4 TRANSISTOR TELEPHONE PICKUP AMPLIFIER ... KT-131 17.95**

**6 TRANSISTOR SUPERHET RECEIVER ... KT-119A 27.50**

**3 TRANSISTOR SUPERHET POCKET RADIO ... KT-116 14.95**

**3 TRANSISTOR HI-FI PREAMPLIFIER ... KT-117 16.95**

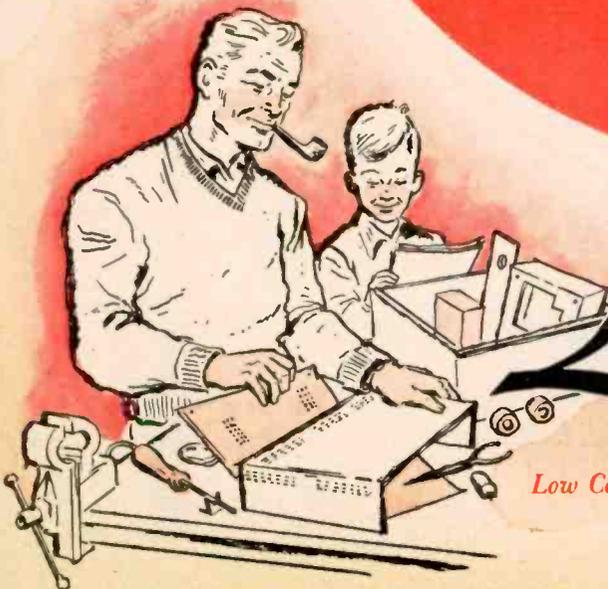**15-IN-1 TRANSISTOR EXPERIMENTER'S KIT ... KT-134 14.95**



*Low Cost Kits For Everyone!*

# Lafayette Radio

# Educational, Practical, FUN To Build!

**LEARN ELECTRONICS BY BUILDING A LOW COST LAFAYETTE KIT**  
**KITS FOR BEGINNERS** • 10-In-1 Lab Kit • Transistor Code Practice Oscillator • AC-DC Broadcast Receiver • 3-Way Broadcast Receiver • 5-Watt Push-Full AC-DC Amplifier • 7-In-1 Radio Lab Kit • 2-In-1 Kit • Germanium Diode Radio • 1-Transistor Pocket Radio • 2-Transistor Pocket Radio  
**HI-FI KITS** • Stereo Master Audio Control Center & Preamplifier • Stereo Remote Control Center—Electronic Stereo Adapter • 36-Watt Basic Stereo Amplifier • AM-FM Stereo Tuner • Preamp-Audio Control Center • 70-Watt Power Amplifier • 4-Watt Stereo Amplifier • Speaker Enclosure Kits  
**ADVANCED KITS** • Broadcast-Shortwave Receiver • Electric Brain Kit • 10-Watt Push-Pull Hi-Fi Amplifier • 15-n-1 Transistor Experimenter's Kit • 4-Band Broadcast-Shortwave Receiver • Photocell Electronic Relay • 6-Transistor Superhet Receiver • 3-Transistor Pocket Radio • 3-Transistor Hi-Fi Preamplifier • 2-Transistor Reflex Radio With Sun Battery • Transistor Code Practice Oscillator • Radio Control Transmitter • Transistor-Diode Checker • Multitester Semi-Kit • 4-Transistor Telephone Pickup Amplifier

## EASY-TO-BUILD LAFAYETTE KITS

**Enjoy and Save**

**LAFAYETTE KITS SAVE YOU REAL MONEY.** You save up to 50% or more when you build a low-cost Lafayette kit as against factory-wired units of equal or even lesser quality. You save also because Lafayette manufactures these kits and sells them *direct to you*, eliminating the usual dealer's markup.

**LAFAYETTE KITS ARE YEARS AHEAD.** Every latest advance in electronics finds its way into educational and practical Lafayette Kits. Lafayette was **FIRST** in **TRANSISTORS**, and Lafayette is now **FIRST** in **STEREO HI-FI!**


**LAFAYETTE KITS ARE EASY TO BUILD.** Whether you are a beginner or an engineer, a novice or advanced amateur, there are Lafayette kits you can build, learn from, and use. Detailed instructions with clear, large blow-ups and dozens of illustrations describe minutely every step of the kit assembly so that there are seldom any questions.

LAFAYETTE KITS ARE AVAILABLE ON OUR EASY PAY PLAN. SEE OUR FREE GIANT-SIZED 260-PAGE 1959 CATALOG FOR DETAILS.


ASK FOR THE FREE 260-PAGE GIANT NEW 1959 LAFAYETTE CATALOG. Fill in and present the coupon below at any Lafayette store for your FREE Catalog, or simply paste the coupon on a postcard and mail it to the address on the coupon. Our catalog is FREE for the asking!



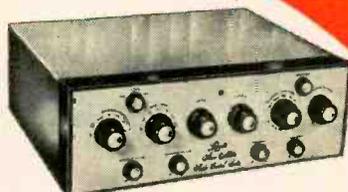
36-WATT STEREO BASIC POWER AMPLIFIER .... KT-310 47.50



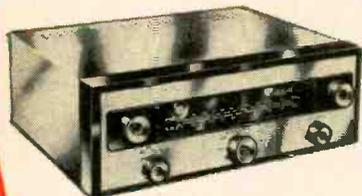STEREO MASTER AUDIO CONTROL CENTER-PREAMP .... KT-600 79.50



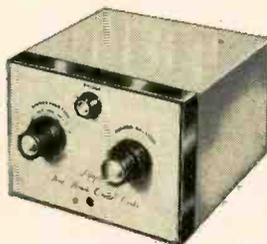
STEREO AM-FM HIGH FIDELITY TUNER .... KT-500 74.50



STEREO REMOTE CONTROL CENTER ELECTRONIC STEREO ADAPTER .... KT-315 27.50



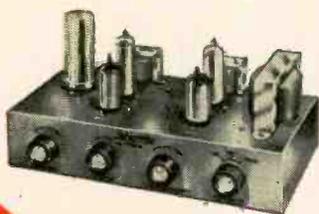70-WATT DELUXE BASIC AMPLIFIER .... KT-400 69.50



4-WATT STEREO PHONO AMPLIFIER .... KT-126 18.95



DELUXE MASTER AUDIO CONTROL CENTER-PREAMPLIFIER .... KT-300 39.50

### LAFAYETTE RADIO STORE LOCATIONS

**JAMAICA 33, N. Y.**  
 165-08 Liberty Ave.  
 AXtel 1-7000  
 Open FRIDAY  
 'till 8:45 P.M.

**NEW YORK 13, N. Y.**  
 100 8th Ave.  
 WOrth 6-5300  
 Open THURSDAY  
 'till 8:45 P.M.

**BRONX 58, N. Y.**  
 542 E. Fordham Rd.  
 FOrdham 7-8813  
 Open THURSDAY  
 'till 8:45 P.M.

**NEWARK 2, N. J.**  
 24 Central Ave.  
 MArket 2-1661  
 Open WEDNESDAY  
 'till 8:45 P.M.

**PLAINFIELD, N. J.**  
 139 W. 2nd St.  
 PLainfield 6-4718  
 Open THURSDAY  
 'till 8:45 P.M.

**BOSTON 10, Mass.**  
 110 Federal St.  
 HUBbard 2-7850  
 Open MON.-WED.  
 'till 8:45 P.M.

**FREE**



CUT  
 OUT  
 AND  
 PASTE  
 ON  
 POST  
 CARD

LAFAYETTE RADIO, Dept. RA  
 P.O. Box 511, Jamaica 31, N. Y.

SEND FOR THE WORLD'S LEADING ELECTRONICS, RADIO, T.V., INDUSTRIAL, AND HI-FI GUIDE

Send FREE LAFAYETTE Catalog 500

Name .....

Address .....

City..... Zone..... State.....

**"TAB" Tubes Tested, Inspected, Boxed**

Six Months Guarantee! No Rejects!  
NEW & Used Gov't & Mfrs. Surplus!

Orders \$10 up. Receiving types only ppd. 48 states

0A2	.80	6B16	.72	12AT6	.59	11Z23	.89
0B2	.72	12BK7	.68	12AU6	.63	4-65A	1.10
0C3	.84	6BL7	1.05	12AU6	.63	4-65A	1.10
0D3	.80	6BN6	1.08	12AU7	.69	2D21	.68
0Z4	.68	6BE6	.59	12BQ6	.70	4-250	3.00
1A7	1.00	6BZ7	1.25	12BA6	.65	717A	5/81
1B3	.78	6C4	.49	12BR7	.90	4-125	29.00
1R5	.78	6C5	.49	12C6	.59	4-250	3.00
1S4	.78	6CB6	.80	12BE6	.59	4E27	7.00
1T4	.78	6CD6	1.49	12BF6	.59	4PR60	29.50

Send for Catalog!

1U4	4/81	6H6	.59	12BY7	1.00	4X150	7.50
1U5	.89	6J5	.59	12BY7	1.00	4X250	33.00
1X2A	.68	6J6	.59	12BZ7	.69	4X500	38.00
3Q4	.68	6K6	.59	12CU6	1.00	5P21	3.98
3Q5	.86	6K7	.70	12SA7	1.29	5BP4	4.98
3S4	.68	6L6	1.19	12SG7	.80	35T	4.00
3V4	.99	6S4	.59	12SH7	.89	100T	7.00
5R4	1.25	6S8	.69	12SJ7	.75	250T	20.00
5U4	.59	6SA7	.69	12SK7	.94	388A	1.00
5V4	.89	6SB7	1.19	12SQ7	.96	418A	14.00

Wanted Surplus Electronics from schools & U.S. Armed Forces

5Y3	.59	6SC7	.89	19BG6	2.15	450T	48.00
6B8A	.59	6SG7	.79	19T8	1.16	807	1.29
6AC7	.79	6X5	.69	200G	1.79	808	1.59
6AG7	.89	6SJ7	.60	25L6	.72	809	3.00
6AH6	.99	6SK7	.72	25W4	.77	4-400A	42.00
6AK5	.69	6SL7	.69	25Z4	.77	811	3.00
6AL5	.59	6SN7	2/81	25Z6	.78	812	3.00
6AQ5	.69	6SQ7	.74	EL34	3.49	813	9.00
6AS7	3.00	6SR7	.70	EL37	2.49	814	2.45
6AT6	.49	6T8	.49	6T8	.59	815	3.95

Wanted 504 U tubes! Top \$ & Paid

6AU4	1.29	6U8	.08	35W4	.52	829B	8.00
6AU5	1.19	6V6	1.39	50A5	.89	866A	7.00
6AU6	.69	6W4	.79	50A5	.89	866A	7.00
6AX4	.79	6W6	.80	50A5	.89	6146	4.00
6BA6	.59	6X4	.39	50B5	.69	5879	1.20
6BA7	1.09	6X5	.59	50B5	.69	5879	1.20
6BD6	.69	6Y6	.89	50L6	.89	6550	3.90
6BE6	.59	7H7	.89	58P1	5.00	5842	11.00
6BG6	1.39	12AL5	.59	58P4	1.99	5854	1.00
6BH6	.79	12AQ5	.75	58P1	3.95	5894	12.00

**TUBES WANTED! WE BUY! SELL & TRADE!**

**NEW "TEKSEL" SELENIUM RECTIFIERS**

FULL WAVE BRIDGE RECTIFIERS. ONE YEAR GTD!

AMP.	18VAC	36VAC	72VAC	144VAC
CONT.	14VDC	28VDC	56VDC	118VDC
1AMP	\$ 1.30	\$ 2.00	\$ 4.90	\$ 9.45
2AMP	2.40	3.50	8.50	16.50
3AMP	2.90	4.00	8.60	16.75
6AMP	4.15	5.80	18.75	36.15
10AMP	4.80	6.45	21.00	41.40
15AMP	9.90	19.00	40.00	66.60
24AMP	15.00	29.45	57.50	108.45

**NEW SILICON 500MA/100°C/280VAC**

400 p.p.v. Rectifier Htmt Sealed. \$1.50  
@ 4 for \$5.60. 40 for \$46. 100 \$105.  
TSF 1.5amp @ 35VAC/30VDC \$2 @ .4/57.00.

**SELENIUM RADIO & TV RECTIFIERS! GTD.**

65ma 45c. @ 10/7. 100ma 59c. @ 10/55.  
100/545. 250ma 75c. @ 10/75. 350ma 85c. @ 10/85.  
100/58. 100/570. 400ma \$1.10 @ 10/510.  
100/585. 500ma. 10/511 100/590.

**NEW DC POWER for TRANSISTORS!!**

New low-cost 25 volt one amp filtered 1% Ripple Power Supply. Same as specified in Transistor Circuits G.E., RCA. Ideal for powering transistor circuits, rugged & small in size! Preassembled kit U-Build B25VIACK \$10, or assembled B25VIAC \$12.

Transistors! Filtered Power Supply Kit used to power transistor circuits, amplifiers, etc. Delivers 12VDC at 2AMPs filtered less than 0.5% ripple on 28VDC at 18VDC. Kit \$18. TRP52W assembled & wired \$24.  
115VAC Inpt Transformer & Full Wave Bridge Rectifier for 12VDC @ 2AMPs, or RECTRAN KIT RT1K.....\$4.58  
RT1W Assembled & Wired.....\$7.50

**BATTERY CHARGER KIT 2 to 4 Amps. Charges 3-1.0 & 12 Volt Batteries. Kit BCK-1 \$11. Bullt \$12.75.**

**HAMS TRANSISTORIZED "TABPAK"**

DC to DC "TABSTAT" Supply.  
12 VDC to HI-VDC POWER SUPPLY!!!  
Kit or Assembled. Filtered, small in size! Quiet! Light Wgt.! Input 12 to 14VDC (Low Idle Current). Output 450Ktap @ 250VDC up to 150ma.  
65 watts. Int. Bullt. TR39CB \$35; in kit form, pre-assembled U-Built, TR39CK \$30.

**"ERIN" FINEST HI-FI RECORDING TAPE**

So fine! We Cannot Use the Manufacturer's True Name!  
1200 Ft.—7" Reel \$1.45 ea. Lots of 3 Money Back Gtd.

**DIAMOND PHONO-NEEDLES! Super Finish**

REGISTERED ONE YR. GUARANTEED BY THE MFR!  
ALL MAKES LP&78-ONE DIAMOND.....\$4.80  
TWO DIAMONDS \$9.45; DIAMOND & SAPPHIRE \$5.70  
PLEASE SEND CATHODE NAME & NUMBER

**KITS! "TAB" THE BEST KITS!**

- All Kits Contain Most Popular Valve & Sizes
- Kit 5 Mylex Glass Strips
- Kit 35 Precision Resistors
- Kit 10 Switches
- Kit 75 Resistors 1/2 1/2W
- Kit 150 Carbon Resistors
- Kit 25 Panel Lamps
- Kit 12 Electrolytic Cond's
- Kit 15 Volume Controls
- Kit 56 Tube Sockets
- Kit 65 Tubular Condensers
- Kit 500 Lugs & Eyelets
- Kit 10 Bathub Oil Cond's
- Kit 5 lbs. Surprise Pkg.
- Kit 10 KMTTR Mica Cond.
- Kit Glyptal & Cement
- Kit 3 Phone/Patch Xfms
- Kit 4 AN Reflector Lamps
- Kit 6 Insult Tuning Tools
- Kit 6 AN plugs & cncnctrs
- Kit 3 Searchlights
- Kit Circular Slide Rule
- Kit 12 Algrt Clip Ass'td.
- Kit 2 Brite Pkts 6x12"
- Kit 5 Pcs. Wrench Set
- Kit 3 Variable Cond's
- Kit 5 Sub-Min Tubes
- Kit 40 Standoff Insulators
- Kit 35 Power Resistors
- Kit 75 Mica Condensers
- Kit 5 Crystal Diodes
- Kit 100 Fuses, Assorted
- Kit 100 Ceramic Cond'sr.
- Kit 50 Coil Forms
- Kit 5 FT243 Xtal Holders
- Kit 95 Inductors & Coils
- Kit 5 Microswitches
- Kit 10 Wheat Lamps
- Kit 5 Translator Xfms
- Kit 8 Xtal Osc-Blanks
- Kit 4 Asstd Rectifiers
- Kit 5-UG/Connectors
- Kit 100 Set Tap Screws
- Kit 8x25 Ft Hookup Wire
- Kit 2 Veeder Counters
- Kit 2 Computer Toroids
- Kit 8 Pc. Nut Driver Set
- Kit High Gain XTAL Mike
- Kit 6 ea. Phono Plgs. Jaks

**"TAB" TERMS: Money Back Guarantee!**

Order 14th year. min. order F.O.B. N.Y.C. Add shipping charges or for C.O.D. 25% Dep. Prices shown subject to change.

111-RA LIBERTY ST. N. Y. 6 N.Y. PHONE: RECTOR 2-6245 for Catalog

**BOOKS (Continued from page 143)**

structure, tubes, transistors, amplifiers, oscillators, hi fi, TV, radar, etc., etc. One finds four separate chapters on tubes: diodes, triodes, multielectrode and special types. Likewise, under power supplies, the author discusses full-wave, half-wave, C and L input, filters, etc.

Self-study readers will appreciate the summary at the end of each chapter. —IQ

**RADIOISOTOPES, A NEW TOOL FOR INDUSTRY, by Sidney Jefferson. Philosophical Library Inc., 15 E. 40 St., N. Y. 16, N. Y. 5 x 7 1/2 in., pp. \$4.75.**

Designed to give the businessman and layman a look at the many ways industry can use radioisotopes, when coupled with electronic detection devices, this book also has a section explaining the fundamentals of radioactivity, including atomic structure, atomic energy and atomic piles.

**DC CIRCUIT ANALYSIS, by Alexander Schure. John F. Rider Publisher, Inc., 116 W. 14 St., N. Y. 11, N. Y. 5 1/2 x 8 1/2 in., 80 pp. \$1.35.**

A part of the Electronics Technology Series, this text covers a fundamental aspect of electricity. After a brief review of electrostatic principles, it introduces the reader to Ohm's and Kirchhoff's laws. This is done through the solving of various circuit problems. More advanced techniques are introduced in later chapters. —LS

**TRANSISTOR MANUAL, 3d edition. General Electric Co., Semiconductor Products, 1224 W. Genesee St., Syracuse, N.Y. 5 1/2 x 8 1/2 in. 168 pp. \$1.**

New and useful data appear in this edition. Unijunction circuits, transistor switches, logic applications, silicon-controlled rectifiers are among the topics. Design data for class-A and -B amplifiers, transistor symbols and how to read specifications are included.

Practical circuits are shown for power supplies, radio receivers and amplifiers. Complete characteristics are given for G-E transistors. An interchangeability list gives JETEC types and the nearest G-E equivalent. —IQ

**GRAPHIC SCIENCE, by Thomas E. French and Charles J. Vierck. McGraw-Hill Book Co., Inc., 330 W. 42 St., N.Y. 36, N.Y. 7 1/2 x 10 in., 758 pp. \$8.50.**

One picture is worth ten thousand words. That's why graphic science is so useful and important. It can describe complex mechanisms, solve certain types of problems and provide extensive information at a glance. This comprehensive volume is written especially for engineers, who don't ordinarily have to prepare their own finished drawings but must know how to evaluate and interpret them.

The book is divided into three parts: engineering drawing, descriptive geometry, graphical solutions. The reader is instructed and trained in free-hand as well as instrument drawing, lettering, and perspective. Nomographs, slide

# SCHOOL DIRECTORY

## GET INTO ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic and advanced courses in theory and laboratory. Assoc. degree in electronics in 28 mos. B.S. in electronic engineering obtainable. ECOP accredited. G.I. approved. Graduates in all branches of electronics with major companies. Start February, September. Dorms, campus. High School Graduate or equivalent. Catalog.



## ELECTRONICS

**PREPARE FOR A GOOD JOB! BROADCAST ENGINEER RADIO SERVICING AUTOMATION**

**TELEVISION SERVICING BLACK & WHITE—COLOR**  
APPROVED FOR VETERANS AND SURVIVORS OF VETERANS  
BUILDING AIR CONDITIONED SEND FOR FREE LITERATURE  
**BALTIMORE TECHNICAL INSTITUTE**  
1425 EUTAW PLACE, BALTIMORE 17, MD.

## ENGINEERING Home Study Courses

COURSES written by world authorities in all branches of engineering. Step-by-step instructions using methods proved successful by thousands of our graduates. One hour each day in your spare time will start you off to higher pay, security, prestige. Check the course you are interested in and we will send you a complete outline of the course with a booklet describing the Institute and our advanced methods of teaching. Send to: Canadian Institute of Science and Technology Ltd., 713 Century Bldg., 412, 5th St. N.W., Wash., D.C.

- Civil Eng.
- Surveying
- Architecture
- Forestry
- Mining
- Structural
- Mechanical Eng.
- Industrial Eng. & Management
- Refrigeration
- Heating
- Drafting
- Plastics
- Electrical Eng.
- Radio
- Electronics
- Television
- Aeronautical Eng.
- Aircraft Engineer
- Navigation
- General Education
- Chemical
- Mathematics
- Journalism
- Accounting

NAME.....  
ADDRESS.....  
CITY..... STATE.....  
Course Interested In.....  
Canadians: Send to Canadian Institute of Science & Technology Limited, 713 Garden Bldg., 263 Adelaide St. West, Toronto, Ont.

# SCHOOL DIRECTORY

## ELECTRONICS ENGINEERING DEGREE IN 27 MONTHS



Prepare for unlimited opportunities in electronics!  
**B.S. Engineering degree (27 mo.):** Mathematics, Electrical Engineering, TV, advanced Radio Theory and Design.  
**B.E. (36 mo.):** Aeronautical, Chemical, Civil, Electrical, Mechanical, Metallurgical Eng. **B.S. (36 mo.):** Math., Chem., Physics. Also preparatory courses. Earn board. G.I. approved. 20 bids.; dorms. Gym. Enter March, June, Sept., Dec. Catalog. Keeping pace with progress.  
**INDIANA TECHNICAL COLLEGE**  
 1519 E. Washington Boulevard, Fort Wayne 2, Indiana

**CODE SENDING RECEIVING SPEED**

Be a "key" man. Learn how to send and receive messages in International Morse code. Communicate with operators around the globe. Learn at home quickly through famous Candler System. Used by best operators. Qualify for Amateur or Commercial License. Write for **FREE BOOK**.

**CANDLER SYSTEM CO.**  
 Dpt. 3-A, Box 9228, Denver 20, Colo. USA

**ENGINEERING DEGREES**

E.E. Option Electronics or Power  
**Earned through HOME STUDY**  
 Resident Classes Also Available if Desired  
**PACIFIC INTERNATIONAL COLLEGE OF ARTS & SCIENCES**  
 Primarily a Correspondence School  
 5719-M, Santa Monica Blvd., Hollywood 38, Calif.

**YOUR CAREER IN AVIONICS!**

**AVIATION - ELECTRONICS JETS - ROCKETS - MISSILES SPACE TECHNOLOGY**

*Jet Airliners; Guidance Systems; Space Studies; Moon Landings - All this means just one thing to a Northrop educated man - OPPORTUNITY!*

**Graduate in two short years**

Thousands of successful Northrop Institute graduates are now employed by leading companies in the fields named above. They hold important, responsible, highly-paid positions, and their Engineering Technology training at Northrop required only 24 months to complete.

**EARN A BACHELOR OF SCIENCE DEGREE**  
 If you elect, you may continue your study an additional year and earn a B.S. degree in the fields of Aeronautical Engineering, Electronics Engineering, or Aircraft Maintenance Engineering.

**GET COMPLETE FREE INFORMATION**  
 Fill out this coupon and mail today. Check the training which most interests you.  
**APPROVED FOR VETERANS**

**NORTHROP AERONAUTICAL INSTITUTE**  
 1181 W. Arbor Vitae Street, Inglewood 1, Calif.

Please send me immediately the Northrop catalog, employment data, and schedule of class starting dates. I am interested in:

Electronic Engineering Technology  
 Aeronautical Engineering Technology  
 Aircraft Maintenance Engineering Technology  
 Master Aircraft and Engine Mechanic  
 Jet Engine Overhaul and Maintenance

Name..... Age.....  
 Address.....  
 City..... Zone..... State.....  
 Veterans: Check here  for Special Veteran Training Information.

## MATHEMATICS

Home study courses. Elementary, high school, and university levels. Very reasonable fees. Consult our catalog in your public library or write us directly.

**UNIVERSAL CORRESPONDENCE SCHOOL OF MATHEMATICS, P.O.B. 5225**  
 Oak Lane Station, Philadelphia 26, Pa.

## REALIZE YOUR DREAM

Become a graduate Electronics Engineer. Share rewards awaiting college men... higher income, rapid advancement. Important firms interview seniors here regularly.

**Electrical Engineer in 27 months**

B. S. degree in Electrical (Electronics or Power major), Mechanical, Civil, Chemical, Aeronautical Engineering. In 36 Months a B. S. in Business Administration (General Business, Accounting, Motor Transport Management majors). For earnest, capable students. Small classes. More professional class hours. Mature students. Well-equipped labs. Modest costs. Veteran approved. Year-round operation. Enter Mar., June, Sept., Jan. Write J. G. McCarthy, Director Admissions, for Catalog and "Your Career" Book.

**TRI-STATE COLLEGE**  
 2419 College Ave. G Angola, Ind.

**EARN MORE MONEY - BE A PROFESSIONAL TELEVISION SERVICE TECHNICIAN**

**UHF-COLOR-VHF**

Master the latest up-to-the-minute TV, Radio & Hi-Fi practices

**WESTERN** offers real experience on live equipment in our **BIG SHOPS AND LABORATORIES** in the shortest practical time under expert instructors. Graduates are in big demand because they have the "field experience" necessary for immediate "bench" or supervisory positions. You learn every phase of Radio and TV servicing (AM, FM, VHF, UHF). WEI men win fast promotion... can demand better pay... develop highly profitable businesses of their own with the latest and most **PRACTICAL PERSONALIZED TRAINING BEHIND THEM**. You concentrate all your time on being a **PROFESSIONAL TV SERVICE TECHNICIAN**—non-essential math and engineering theory omitted. **YOU CAN EARN WHILE YOU LEARN**. Special Finance Plan. **APPROVED FOR VETERANS**. Find out how you can get into the **TOP PAY GROUP**—Send for this **FREE FACT-PACKED book NOW!**

**WESTERN** offers real experience on live equipment in our **BIG SHOPS AND LABORATORIES** in the shortest practical time under expert instructors. Graduates are in big demand because they have the "field experience" necessary for immediate "bench" or supervisory positions. You learn every phase of Radio and TV servicing (AM, FM, VHF, UHF). WEI men win fast promotion... can demand better pay... develop highly profitable businesses of their own with the latest and most **PRACTICAL PERSONALIZED TRAINING BEHIND THEM**. You concentrate all your time on being a **PROFESSIONAL TV SERVICE TECHNICIAN**—non-essential math and engineering theory omitted. **YOU CAN EARN WHILE YOU LEARN**. Special Finance Plan. **APPROVED FOR VETERANS**. Find out how you can get into the **TOP PAY GROUP**—Send for this **FREE FACT-PACKED book NOW!**


**ELECTRONICS**

Train at an industry-recognized school—approved by Los Angeles Electronics Industry Advisory Committee—for better job opportunities & higher income.

Intensive one-year Electronic Technician Course prepares for employment in research, development & design in computer, radar, radio, transistor, industrial electronics, guided missile, broadcasting & other related fields. No experience needed. Easy pay-as-you-go plan for non-veterans. Vets financed until VA checks received. Send for free Booklet.

**WESTERN ELECTRONICS INSTITUTE**  
 5119 Sunset Blvd., Dep't 1-ET  
 Los Angeles 27, Calif.

## Interesting, Pictorial FREE BOOKLET

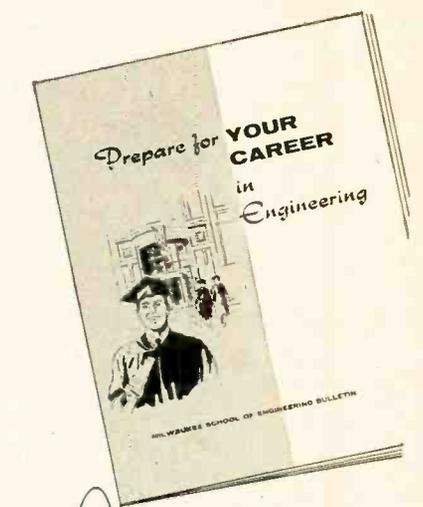

to help you decide on your career in

## ELECTRONICS RADIO-TV COMPUTERS

Here is a graphic story about dynamic careers for engineers and engineering technicians. Booklet covers such subjects as:

- Wide variety of job opportunities.
  - The courses offered, degrees you can earn, and what you are qualified to do.
  - Pictures of the Milwaukee School of Engineering, its facilities, plus Milwaukee scenes.
  - Recreation, student organizations, fraternities.
  - Scholarships, part-time work, admission requirements.
- and many other important and interesting facts to help you understand and decide on your career in engineering. Send for your *free* copy today — no obligation whatsoever.

**Milwaukee School of Engineering**  
 —dedicated to serving young men and industry

**SEND COUPON TODAY**

**Milwaukee School of Engineering**  
 Dept. RE-159, 1025 N. Milwaukee St.  
 Milwaukee, Wisconsin

Please send me free the new booklet "Prepare for Your Career in Engineering"  
 I'm interested in  Electronics  Radio-TV  Computers

Name..... Age.....  
 Address.....  
 City..... Zone..... State.....  
 I'm eligible for veteran's education benefits  
 Yes  No Discharge date.....

**NOW** you can get Crowhurst's great new hi-fi book


at  **Book Club savings!**

# AUDIO MEASUREMENTS

BY NORMAN H. CROWHURST

A book that just had to be written! Hi-Fi ace Norman H. Crowhurst covers audio measurements from the service shop to laboratory level. Shows you how to make tests, what instruments to use, and how to interpret results to get better hi-fi performance. He did the research for you—years and years of it—then selected the useful and practical. Nowhere else can you find so much audio measurement data presented so helpfully and clearly.

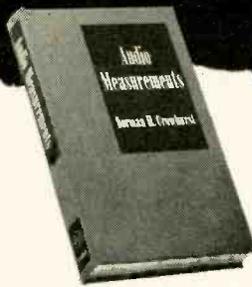BUY THIS \$5.00 BOOK (and others like it) FOR ONLY \$3.75—join the G/L Hi-Fi Book Club. Save \$1.25 on this deluxe book. NO-RISK—return any book you don't like. Get a complete hi-fi library this easy way. Join today.



### HOW TO JOIN

- Select one book on coupon
- SEND NO MONEY. Look the book over first. If you like it send \$3.75—the special club price.
- You receive a new book every 4 months.
- You may cancel after accepting four books—no time limit.

**ORDER**  
AUDIO MEASUREMENTS  
or any of the  
books listed  
in handy  
coupon

### MAIL COUPON NOW!

**Gernsback Library, Inc.**  
154 West 14th St.  
New York 11, N. Y.

19C


Enroll me in the G/L Audio Hi-Fi Book Club. Send me the book checked.

- |  |   |   |
|--|---|---|
| <input type="checkbox"/> Audio Measurements    | <input type="checkbox"/> Elements of Tape Recorder Circuits | <input type="checkbox"/> Understanding Hi-Fi Circuits |
| <input type="checkbox"/> Audio Design Handbook | <input type="checkbox"/> Maintaining Hi-Fi Equipment        | <input type="checkbox"/> Basic Audio Course           |

Name.....  
Street.....  
City..... Zone..... State.....  
please print
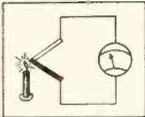
### THERMO-ELECTRONICS

Successor to Thermo-Electricity  
Change heat to electricity DIRECTLY—no acids, liquids, chemicals moving parts or sunlight! Build or buy a thermo-electronic battery. Mail quarter today for information and sample thermo-electronic alloy.



**HERMON E. COTTER**

Dept. O  
15766 Blackstone Detroit 23, Mich.

## RADIO-ELECTRONICS

FOR LIBRARIES

Current yearly volume to be available on microfilm. Write for information.

### UNIVERSITY MICROFILMS

ANN ARBOR, MICHIGAN

## RADIO-ELECTRONICS

February Issue  
on Sale January 29th

Save Time with

## SENCORE LEAKAGE CHECKER

Check these outstanding New Features

The LC3 provides all these new improved features in addition to those employed in earlier leakage or "grid circuit" testers. A must for any TV service technician.

- ★ Checks 156 different tube types—more than any other "grid circuit" type checker. Includes UHF and latest type tubes.
- ★ Checks picture tubes without removing tube from cabinet or chassis.
- ★ New Roll Chart prevents obsolescence—just dial the tube type and save time. Chart is easily replaced at no extra cost.
- ★ Provides instant filament checks on "Fil-Check" position—no need to carry a second filament checker.
- ★ Capacitor checks simplified.
- ★ Two spare preheating sockets to cut down testing time.

In stock at your local parts distributor.

SENCORE CORP. 121 Official Rd. • Addison, Ill.



Model LC-3  
\$28<sup>95</sup>

DEALER NET  
Really Whips  
Tough Dogs

SENCORE

See other SENCORE ads in this issue

### BOOKS (Continued)

rules and conversion charts are discussed in the final chapters. Each chapter ends with problems. A fine book for study or reference.—IQ

**1958 OFFICIAL REGISTRY OF RADIO SYSTEMS IN THE TRANSPORTATION SERVICES.** Communications Engineering Book Co., Radio Hill, Monterey, Mass. 8½ x 11 in., 84 pp. \$4.

This registry, compiled from FCC records, gives details on every mobile radio system in the US operated by railroads, taxicabs, auto emergency services, buses and trucks. It lists the name and address of each company, the number and location of its fixed transmitters, the number of mobile transmitters authorized, operating frequencies, call letters and make of equipment used. Part 1 is a listing by companies. Part 2 by frequencies.—RFS

**ELECTRICAL APPLIED PHYSICS,** by N. F. Astbury. Philosophical Library, 15 E. 40 St., New York 16, N.Y. 5½ x 8¾ in. 241 pp. \$10.

This text is suitable for senior students in physics or engineering. It derives the general laws of magnetic and electric fields and circuits, then applies them. Vectors are explained and used where necessary. Filters, bridges, networks, tubes, transistors and antennas are among the topics studied. Electromechanical and electro-acoustic systems are also discussed.—IQ

**VACUUM TUBE RECTIFIERS,** edited by A. Schure. John F. Rider Publisher, Inc., 116 W. 14 St., New York 11, N.Y. 5½ x 8½ in., 78 pp. \$1.50.

This book covers the subjects of rectifiers and filters as used in single- and polyphase power supplies. It compares and analyzes half-wave and full-wave rectifiers, bridges and voltage multipliers. Equations for filter design are given and typical examples are worked out. Attention is given both to theory and practice. END



"There's just one component we can't sell him—and that's the good sense to put it together properly."

# ADVERTISING INDEX

Radio-Electronics does not assume responsibility for any errors appearing in the Index below.

Acro Products Co. ....	98	Jensen Manufacturing Co. ....	Inside Front Cover
Aerovox Corp. ....	107	Key Electronics .....	136
Allied Radio Corp. ....	17, 86-89	Lafayette Radio .....	144-145
Amphenol Electronics Corp. ....	116	Lansing (James B.) Sound Inc. ....	99
Arkay Radio Kits Inc. ....	114	Lektron Inc. ....	139
Atlas Sound Corp. ....	134	Mallory (P. R.) Inc. ....	14
B & K Manufacturing Co. ....	22, 109	McGraw-Hill Book Co. Inc. ....	136
Barry Electronics Corp. ....	149	Merit Coil & Transformer Corp. ....	136
Bell Telephone Labs .....	24	Mosley Electronics Inc. ....	134
Blonder-Tongue Labs .....	93	Moss Electronic Distributing Co. Inc. ....	94-97
Brooks Radio & Television Corp. ....	137	National Radio Institute .....	3, 19-20
Burroughs Corp. ....	125	National Schools .....	5
Burstein-Applebee Co. ....	133	Opportunity Adlets .....	142-143
CBS-Hytron .....	30	Pentron Corp. ....	130
Capitol Radio Engineering Institute .....	12, 101-102	Perma-Power Co. ....	90
Carston Studios .....	141	Philco Accessory Div. ....	82-83
Castle Television Tuner Service .....	136	Philco Techrep Div. ....	150
Centralab Division of Globe Union .....	18	Pickering & Co. Inc. ....	80
Century Electronics Co. Inc. ....	121	Picture Tube Outlet .....	143
Chemtronics Inc. ....	118	Precision Electronics Inc. ....	113, 141
Chicago Standard Transformer Corp. ....	104	Progressive Edu-Kits Inc. ....	126
Cisin (H. G.) .....	132	Quam-Nichols Co. ....	118
Cleveland Institute of Radio Electronics .....	10-11	Quietrole Co. Inc. ....	130
Colordaptor .....	138	RCA Electron Tube Div. ....	Back Cover
Columbia Record Club .....	13	RCA Institutes .....	78-79
Cornell-Dubilier Electric Corp. ....	91	Radio-Electronic Master .....	120
Cotter (Hermon E.) .....	148	Radio Shack Corp. ....	122-123
Coyne Electrical School .....	23, 127, 137	Rider (John F.) Publisher Inc. ....	117
Delco Radio Div. of General Motors Corp. ....	129	Rinehart & Co. Inc. ....	28-29
Deutschmann (Tobe) .....	81	Rogers Manufacturing Co. ....	128
DeVry Technical Institute .....	7	Rohn Manufacturing Co. ....	111
Dressner .....	141	Sams (Howard W.) & Co. Inc. ....	21, 92
Dynaco Inc. ....	103	Schober Organ Co. ....	142
Editors and Engineers Electro-Voice, Inc. ....	135	Service Instruments Corp. ....	104, 115, 124, 133, 135, 139, 148
Electronic Chemical Corp. ....	138	Sprague Products Co. ....	105
Electronic Instrument Co. (Eico) .....	31-32	Sprayberry Academy of Radio-Television .....	25
Electronic Measurements Corp. ....	100	TAB .....	146
Electronic Publishing Co. Inc. ....	100	Tarzian (Sarkes) Inc. ....	140
E-Z Hook Test Products Inc. ....	100	Television Tuner Service Co. ....	134
Garfield (Oliver) Co. ....	141	Thorens Co. ....	16
General Cement Manufacturing Co. ....	128	Trio Manufacturing Co. ....	124
Gernsback Library Inc. ....	140, 143, 148	Tung-Sol Electric Co. ....	6
Graham School of Electronics .....	27	University Loudspeakers, Inc. ....	119
Gray Manufacturing Co. ....	8	University Microfilms .....	148
Grommes .....	141	Van Nostrand (D.) Co. Inc. ....	9, 123
Guide Lamp Div. of General Motors Corp. ....	131	Zamco .....	143
Heald Engineering College .....	141		
Heath Co. ....	64-75, 77		
Illinois Condenser Co. ....	138		
Indiana Technical College .....	138		
International Correspondence Schools .....	15		
JFD Electronics .....	26		
Jensen Industries .....	128		

BRANCH ADVERTISING OFFICES: Chicago: 1025 Harlem Ave., Glenview, Ill. Glenview 4-6900. Los Angeles: Ralph W. Harker and Associates, 600 South New Hampshire, Tel. DUnkirk 7-2328. San Francisco: Ralph W. Harker and Associates, 44 Market St. Tel. GARfield 1-2481.

FOREIGN AGENTS: Great Britain: Atlas Publishing and Distributing Co., Ltd., 18 Bride Lane, London E.C. 4. Printed in the United States of America

## EQUIPMENT & COMPONENT SPECIALS

- SPRAGUE 50,000 Ohms KOOLOHM BLEEDER RESISTOR @ 120 WATTS... 75c each
  - EASTMAN KODAK INFRA-RED RECEIVER TYPE B 7" long with 5" Schmidt high speed f 0.5 objective lens. Optical system contains coated lenses and operates from 2 penlight batteries. Units are unused, @.....\$15.00
  - Waterproof carrying case for above @ \$2.50
- AUTO-TRANSFORMERS, STEP-DOWN TRANSFORMERS:**
- 150 Watts Autotransformer. 94 Volts in 8 steps, 50/60 CPS. Mfd by Acme. With line cord and plug and built-in AC receptacle. @.....\$4.00
  - 250 Watts Autotransformer. 95 Volts to 260 Volts in 8 steps. 50/60 CPS. With line cord and receptacle.....\$7.00
  - 500 Watts Isolation Transformer for outdoor use or indoor use. 240 Volts input to 240 Volts or 120 Volts output. 50/60 CPS. Mfd. by American Xfmr, @.....\$10.00
  - TRIPLETT 0-100 MICROAMPS DC 3" ROUND METER. Hermetically sealed. In original carton w/hardware. Triplett Model 321-HR. @.....\$4.95
  - MODULATION TRANSFORMER. Conservatively rated 250 watts of audio. Handles up to 600 Watts RF. Prim: 21K. Secon: 8K. Turns Ratio: 1.6 to 1. In original cartons: New. Only \$6.50 each.
  - HAMMARLUND SUPER-PRO FILTER CHOKE Brand New. Exact replacement for Super-Pro Pwr supply—25-Hy. @ 160 Ma. @.....\$2.50
  - DUMONT 10 Mc. LAB SCOPE—(Orig. cost over \$900.00)—only.....\$295.00 Write for further details.
  - DUMONT 274A—Gen'l Purpose Scope.....\$60.00
  - BC-221 FREQ. METERS—Orig. Book & Xtal Lab Tested O.K. only.....\$75.00


### Write For Latest Tube Catalog Free!

Receiving, transmitting, special purpose tubes, diodes, transistors, etc. We have a large diversified stock at sensible prices.

### 2-COLOR TUBE CARTONS

Keeps your tube stock neat. New safety partition prevents tube breakage. Distinctively lithographed in glossy red and black. The most distinctive tube carton available today. Minimum quantity: 100 of any one size. Write for case lot prices. Packed 1000 to case. F.O.B. N.Y.C. No C.O.D.'s on cartons—Send full remittance including postage—Excess refunded.

SIZE	For Tube	Per 100
Miniature 6AU6, etc.		\$1.00
GT.....6SN7GT, etc.		1.25
Large GT.....1B3GT, etc.		1.50
Large G.....5U4G, etc.		2.00

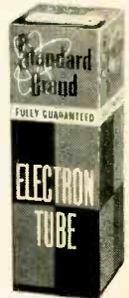

### WHITE GLOSSY BOXES

Completely blank. No printing or color. Otherwise same as above. Same high quality, same low prices. Specify "WHITE" when ordering. When color is not stated, 2 color cartons will be shipped.

We are factory distributors for Vocaline, Gonset, E. F. Johnson, Eimac, B&W, Hexacon, Adjust-A-Volt, CBS, Hammarlund, etc.

### Special Trade-ins on E. F. Johnson and Hammarlund Ham Gear!

TERMS: 25% deposit with order, balance C.O.D. All merchandise guaranteed for cost of merchandise only, F.O.B. N.Y.C.

We are near Prince St./BMT Station, Spring St./IRT Station. Open Monday thru Saturday. Thousands of unadvertised specials. Come in and browse around.


# BARRY ELECTRONICS CORP.

512 Broadway, Dept. RE-1, N.Y. 12, N.Y.  
Phone: Walker 5-7000

# NOW! LEARN COMPUTER TECHNOLOGY AT HOME!
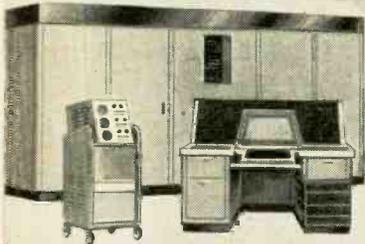
## ELECTRONICS TECHNICIANS:

In this era of space-age electronics you either advance and prosper or you fall behind . . . there is no such thing as standing still.



### THE "NERVE CENTER" OF MODERN INDUSTRY IS IN THE HANDS OF THE ELECTRONICS SPECIALISTS WHO BUILD AND MAINTAIN THE COMPUTERS

Today, top management can't afford to guess. Big decisions are made with up-to-the-minute facts and figures. Only the automatic computer can supply these . . . that's why top management relies on the specialist who can keep the computers running.

*Mail Coupon Today for Complete Information*

(NO OBLIGATION)

THE PHILCO TECHNOLOGICAL CENTER  
22ND AND LEHIGH AVENUE, PHILADELPHIA 32, PA.

1DC-2

Please send free booklet and course information on your Automatic Digital Computer Correspondence Course and other subjects checked below:

- SEMICONDUCTORS—Transistor Principles and Practices
- BASIC RADAR
- ADVANCED RADAR
- BASIC ANALOG COMPUTERS
- ADVANCED ANALOG COMPUTERS

NAME \_\_\_\_\_

COMPANY \_\_\_\_\_ POSITION \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

### PREPARE NOW FOR ADVANCEMENT IN THIS GROWING FIELD WITH A FUTURE . . . WITH COMPLETE, UP-TO-DATE CORRESPONDENCE COURSE FROM THE PHILCO TECHNOLOGICAL CENTER

Learn automatic digital computer technology now with this practical correspondence course from Philco. Learn computer maintenance, installation, manufacturing, programming and you'll be set for a profitable career in an important, fast-growing field that is revolutionizing business methods, manufacturing and defense systems.

#### COMPUTER FIELD IS A FIELD OF OPPORTUNITY

Every major industry . . . nearly every company is now or will soon be using computers to "automate" every phase of business from accounting to production . . . from research to sales. The Military uses them in such operations as missile tracking, telemetering, aircraft flight and fire control. Here is truly a field of opportunity for the electronics technician who wants to get ahead and enjoy the prestige and benefits of an important position in a vital phase of business or defense.

#### COMPUTER SPECIALISTS ARE URGENTLY NEEDED . . . AND THE PAY IS GOOD

It takes a specialist to build, install or maintain a computer. Even during the peak of unemployment during the recent recession, the newspapers were full of help-wanted ads for computer specialists and field engineers. The computer field demands specialists . . . and the computer specialists command good pay.

#### THE PHILCO TECHNOLOGICAL CENTER IS A DEPARTMENT OF PHILCO TECHREP DIVISION, WORLD'S LEADING FIELD ENGINEERING ORGANIZATION


You benefit from Philco's 17 years of experience in electronics training and technical assistance to the Armed Forces and industry. You learn from a proven course specially developed by electronics specialists to give you practical knowledge of the digital computer field.


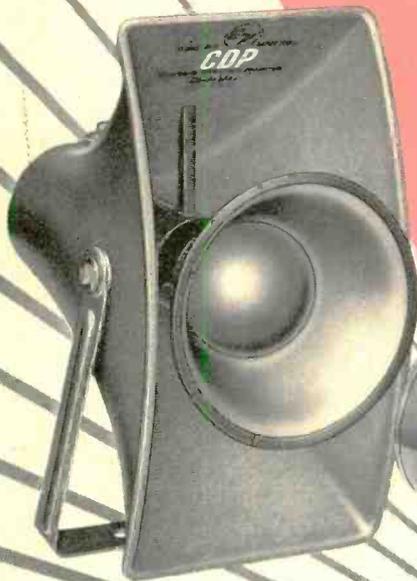
# NOW... AN *Electro-Voice*<sup>®</sup> PUBLIC ADDRESS SPEAKER FOR ANY APPLICATION


For SUPERIOR SOUND . . . CONTROLLED COVERAGE

See Electro-Voice public address projectors. They offer perfect voice penetration and full-range "musicasting." They're weatherproof, splashproof and blastproof.



Model 844 30-Watt Paging Unit. Compact, economical unit for quality, high-efficiency voice reproduction.

**\$34.50**  
LIST

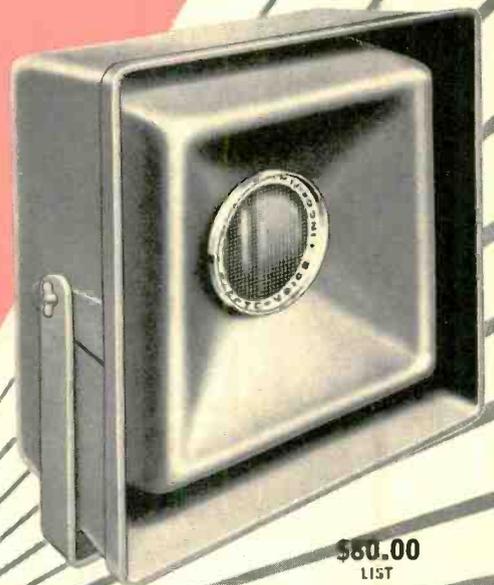

The New Electro-Voice Musicaster. Rugged, weatherproof high-fidelity speaker system for high-quality music reproduction.

**\$80.00**  
LIST



**\$75.00**  
LIST

Model 848LT Long Throw CDP\* (With 1000-cycle concentrating horn). For projecting intelligible, extended-range sound over great distances.

\*CDP (Compound Diffraction Projection) Design Patent 169,904. Additional Patent Pending.



Model 848 30-Watt CDP. For wide-angle coverage and extended range. Standard of the industry.

**\$75.00**  
LIST



Model 847 25-Watt CDP. Smaller version of Model 848.

**\$46.33**  
LIST



Model LS-12. For interior installations requiring full-range response.


**\$32.50**  
LIST



Model LS-8. Smaller version of Model LS-12.

**\$30.00**  
LIST

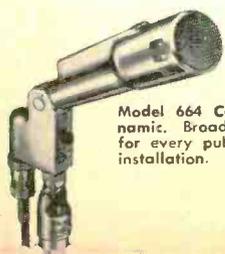THESE ELECTRO-VOICE MICROPHONES ARE  
ESPECIALLY OUTSTANDING FOR PUBLIC ADDRESS



**\$85.00**  
LIST

Model 664 Cardioid Dynamic. Broadcast-quality for every public address installation.



**\$49.50**  
LIST

Model 951 Cardioid Crystal. Excellent, wide-range, all-purpose microphone.

The Sound of Electro-Voice... Assures Superior Installations, Customer Satisfaction, Your Reputation!

*Electro-Voice*<sup>®</sup>

ELECTRO-VOICE, INC.  
BUCHANAN, MICH.

In Canada: E-V of Canada Ltd., 73 Crockford Blvd., Scarborough, Ontario  
Cables: ARLAB



The familiar  
RCA carton  
is the hallmark of  
a quality repair job.

You know, yourself, how comforting it is to see a familiar face among strangers. Well, to the majority of your customers, TV is strange, too. They don't understand it. They count on you to "keep 'em going". And, the "familiar face" is the famous RCA monogram. When they see it on that famous red/black carton, *they know you know your business...* and use the best replacement tubes and parts money can buy.

You can cash in on the built-in prestige of RCA. Make this best-known name your stock-in-trade. Your Authorized RCA Tube Distributor handles a complete line of RCA Tubes to meet your service needs.



**RADIO CORPORATION OF AMERICA**

Electron Tube Division

Harrison, N. J.