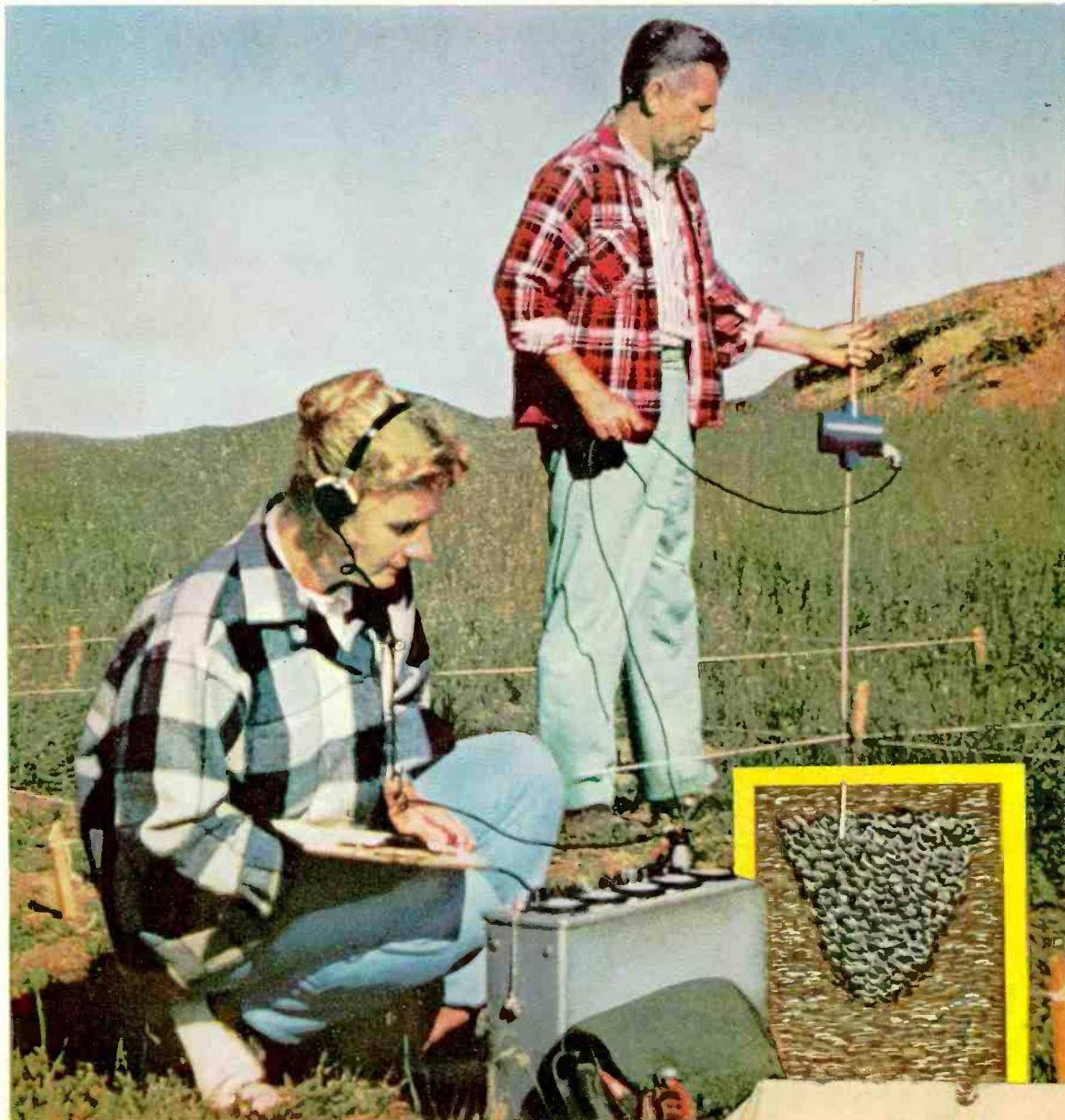


Radio-Electronics

TELEVISION • SERVICING • HIGH FIDELITY

A GERNSTOCK PUBLICATION

BUILD THE SEMI-SWEEPER GENERATOR
 ACCURATE TRANSISTOR TACHOMETER
 TAPE PLAYERS FOR YOUR CAR
 WHAT'S A DELAY LINE?



**MAGNETOMETER — NEW
 ARCHEOLOGIST AND TRE**

ARTHUR L. FRIENDLY 1-67
 BOX 133 BRANDY RD
 RT 1
 ALEXIE WEST VA 25015

PICK ANY NUMBER FROM 1G3GT TO 19AU4 AND YOU'RE A WINNER!

Circle 1 on reader's service card


1G3GT/1B3GT	4HA5	6BZ6	6GW8	8CW5
1X2B	5H08	6CB6A	6HA5	9A8
3BZ6	5U8	6C07	6HG8	10CW5
3CB6	6AL5	6DT6	6S4A	12AT7
3GK5	6AU4GTA	6EH7	6SN7GTB	12AD7A
3HA5	6AU6A	6EJ7	6U8A	12AX4GTB
4BL8	6AV6	6GB5	6U9	12AX7A
4EH7	6AX4GTB	6GJ7	6X9	15CW5
4EJ7	6BA6	6GK5	6Y9	16A2
4GK5	6BL8	6GK6	8BQ5	19AU4

...AND ON AND ON. FOR THE COMPLETE LIST, WRITE
AMPEREX ELECTRONIC CORPORATION, HICKSVILLE, L.I., NEW YORK 11802.



LOOK!

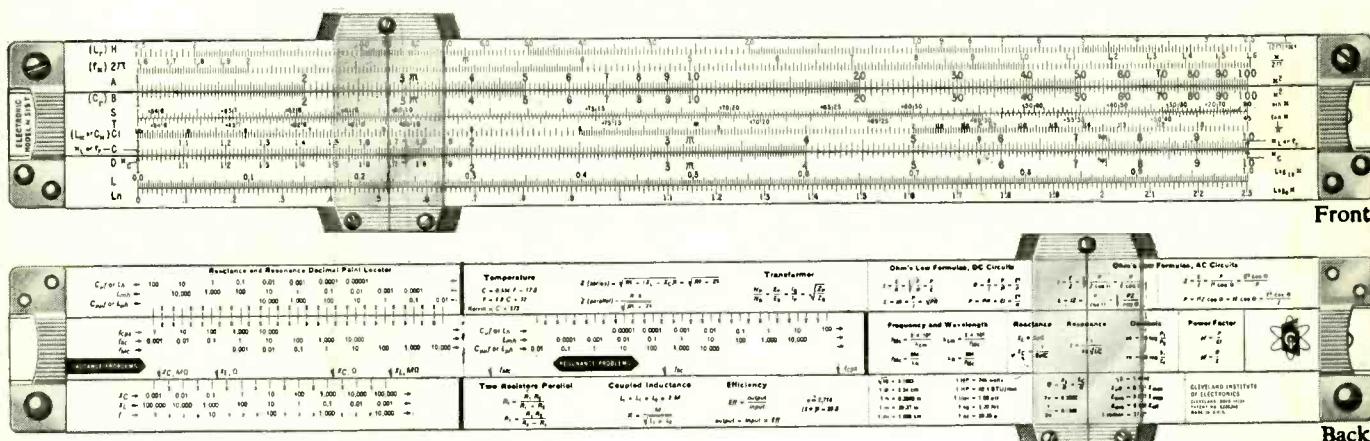A New Electronics Slide Rule with Instruction Course




This amazing new "computer in a case" will save you time the very first day. CIE's patented, all-metal 10" electronics slide rule was designed specifically for electronic engineers, technicians, students, radio-TV servicemen and hobbyists. It features special scales for solving reactance, resonance, inductance and AC-DC circuitry problems . . . an exclusive "fast-finder" decimal point locator . . . widely-used formulas and conversion factors for instant reference. And there's all the standard scales you need to do multiplication, division, square roots, logs, etc.

Best of all, the CIE Slide Rule comes complete with an Instruction Course of four **AUTO-PROGRAMMED*** lessons. It includes hundreds of illustrations, diagrams and practice problems. You'll learn ingenious short cuts...whip through exacting electronics problems quickly and accurately. This course alone is worth far more than the price of the entire package!

Electronics Slide Rule, Instruction Course, and handsome, top-grain leather carrying case . . . a \$50 value for less than \$20. Send coupon for FREE illustrated booklet and FREE heavy vinyl Pocket Electronics Data Guide. Cleveland Institute of Electronics, 1776 E. 17th St., Dept. RE-114, Cleveland, Ohio 44114.


*TRADEMARK

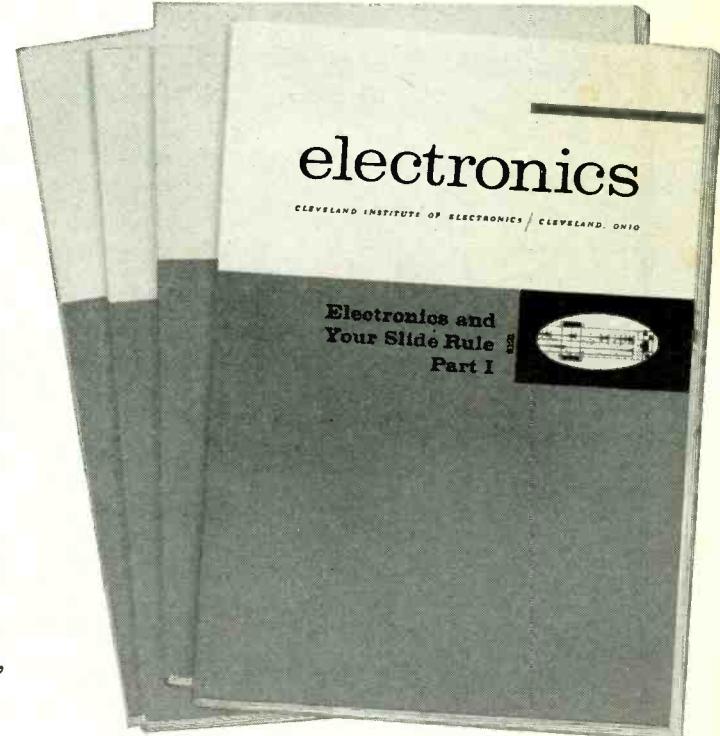

GET BOTH FREE!

ELECTRONICS
SLIDE RULE

Send coupon today →

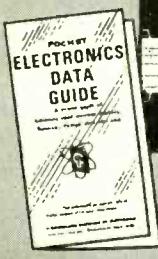

Cleveland Institute of Electronics

1776 E. 17th St., Dept. RE-114, Cleveland, Ohio 44114

Please send FREE Illustrated Booklet describing your Electronics Slide Rule and Instruction Course.

SPECIAL BONUS! Mail coupon promptly . . . get FREE Pocket Electronics Data Guide too!

Name _____ (PLEASE PRINT)

Address _____ County _____

City _____ State _____ Zip _____

A leader in Electronics Training . . . since 1934.

Circle 2 on reader's service card

Radio-Electronics

SEPTEMBER 1965 VOL. XXXVI No. 9

Over 55 Years of Electronic Publishing

EDITORIAL

- 33 The End of the Service Technician? *Fred Shunaman*

TELEVISION

- 45 TV Tuner Troubles *Jack Darr*
Don't automatically send a tuner out for repairs. See what you can do

RADIO

- 40 Diode RF Switches *Irving Math*
They can eliminate contact problems and long rf leads
- 41 What's Your Modulation %? *Fred Blechman*
CB'er or ham—you ought to know. Simple scope check may solve some puzzles

TEST INSTRUMENTS

- 37 Easy Alignment with the Semi-Sweeper *Donald L. Stoner*
Ultra-simple sweep generator makes perfect rf/i.f. curves a cinch
- 59 New Concept in Color Bar Generators *Walter Cerveny*
Amphenol "Color Commander" features several unique patterns to simplify color setup
- 61 Equipment Report: Mercury Model 1400 In-Circuit Capacitor Tester

AUDIO-HIGH FIDELITY-STEREO

- 34 Tape Players For Your Car *Fred Blechman*
Roundup of the latest auto electronics fad: stereo tape players
- 48 40 Watts in 40 Ounces—Building the Two-State Amplifier *Norman Crowhurst*
Concluding article covers construction and testing
- 61 Equipment Report: Euphonics "Miniconic" Semiconductor Stereo Pickup

GENERAL

- 22 Service Clinic *Jack Darr*
"Do Not Measure!" (Why Not?)

- COVER STORY 42 The Proton Magnetometer: New Tool for Archeologists and Treasure-Hunters *E. H. Marriner*
Finds gold, oil and ancient garbage with equal ease

- 44 Who Invented It? *Robert G. Middleton*
Credit may not always go where it ought to

- CAREER SERIES 53 The Engineers' Right-Hand Men *Eric Leslie*
The technician at work in industry

- 54 A Reliable Transistor Tachometer *Stephen Gross*
3-transistor device works on any engine—any number of cylinders, 2- or 4-stroke

- 61 What's Your EQ?

ELECTRONICS

- 39 Foolproofing the Transistor Duo *Rufus P. Turner*
- 56 What's A Delay Line? *Arthur S. Kramer*
And what's more, why would you want to delay a signal?

THE DEPARTMENTS

- 12 Correspondence
106 New Books
81 New Literature

- 75 New Products
71 New Semiconductors & Tubes
4 News Briefs

- 95 Noteworthy Circuits
86 Technotes
90 Try This One
101 50 Years Ago

- 72 Reader's Service Page

ON THE COVER: Color original courtesy Scripps Institute of Oceanography.
Section in yellow rectangle is artist's conception of underground area with magnetic anomaly (ashes of old firepit).



Member,
Institute of High Fidelity
Radio-Electronics
is Indexed in
Applied Science
& Technology Index
(Formerly
Industrial Arts Index).

Choose Your Tailor-Made Course in N.T.S. "PROJECT METHOD" ELECTRONICS!

Now! N.T.S. — one of America's oldest leading home-study and resident technical schools — offers you GREATER CAREER OPPORTUNITIES IN ELECTRONICS. N.T.S. "Project Method" home training lessons are shop-tested in the Resident School in Los Angeles. You work on practical job projects, learn to use shop manuals and schematics. Your N.T.S. training is individual. You proceed at your own pace. The Schools' practical methods, plus more than 60 years of experience, have helped thousands of students all over the world to successful careers. Prepare now for a secure future in one of 8 N.T.S. Electronics Courses designed to fit your own particular needs.



Work on the electronic "brains" of industry — computers, data processing and other automation equipment. Become a TV-Radio Technician, an electronics field engineer, or succeed in your own business.

CHOOSE YOUR FIELD—INSURE YOUR FUTURE!

1 ELECTRONICS-TV-RADIO-SERVICING & COMMUNICATIONS A basic course thoroughly covering fundamentals of electronics, radio, TV servicing and communications.

2 MASTER COURSE IN ELECTRONICS-TV-RADIO, PLUS ADVANCED TV & INDUSTRIAL ELECTRONICS This course covers everything included in Course No. 1 plus Automation and every phase of the Electronics industry.

3 FCC LICENSE Preparation for this government license essential for interesting jobs in radar, radio, television, communications, guided missiles, many others. Upon completion of this course, if you do not pass the FCC exam for a 1st Class Commercial Radiotelephone License your tuition will be refunded.

4 RADIO SERVICING (AM-FM-Transistors) Train for radio sales and service with dealer or distributor.

5 TELEVISION SERVICING (Including Color) Covers installation, adjustment, repair and servicing of black and white and color television . . . prepares you for your own sales and service business.

6 STEREO, HI-FI AND SOUND SYSTEMS A growing field. Prepares you to build, install and service modern sound equipment for home or industry.

7 BASIC ELECTRONICS Gives you the fundamentals you must know to build on for a future Electronics career. Also offers an excellent background for Salesmen, Purchasing Agents, and others in Electronics.

8 ELECTRONICS MATH Simple, easy-to-follow instructions in the specialized math you need in many electronics jobs.

Most courses include Equipment Kits. THERE ARE NO KIT DEPOSITS. Everything included in your low tuition.



CLASSROOM TRAINING AT LOS ANGELES

You can take classroom training in our famous Resident School at Los Angeles in Sunny Southern California. N.T.S. is the oldest and largest school of its kind. Associate in Science Degree also offered in our Resident Program. Check Resident School box in coupon for full details.

MAIL COUPON TODAY FOR FREE BOOK AND SAMPLE LESSON

In Field of Your Choice. You enroll by Mail — and Save Money. No Salesmen: This means lower tuition for you. Accredited Member N.H.S.C.

HIGH SCHOOL AT HOME

Learn easily. New modern method. National also offers accredited high school programs for men and women. Take only subjects you need. Study at your own pace. Latest approved textbooks yours to keep—everything included at one low tuition. Check High School box in coupon for information.



NATIONAL TECHNICAL SCHOOLS

4000 S. Figueroa St., Los Angeles, California 90037

Please Rush FREE Electronics "Opportunity Book" and actual sample lesson on course checked below:

- Electronics-TV-Radio Servicing & Communications
- Master Course in Electronics-TV-RADIO Advanced TV & Industrial Electronics
- FCC License
- Radio Servicing (AM-FM-Transistors)
- Television Servicing (Including Color)
- Stereo, Hi-Fi and Sound Systems
- Basic Electronics Electronics Math

Dept.
206-95

Name _____ Age _____

Address _____

City _____ State _____ Zip _____

Check here if interested ONLY in Classroom Training at L.A.

Check here for High School Department Catalog only.



NATIONAL TECHNICAL SCHOOLS

WORLD-WIDE TRAINING SINCE 1905

4000 S. Figueroa St., Los Angeles, California 90037

Circle 3 on reader's service card

NEWS BRIEFS

TV PRODUCTION TO DOUBLE IN TWO YEARS, SAYS RCA

The Radio Corporation of America announced an expansion program that will double its color TV set production capacity within 2 years, and will double color tube output within 3 years. This expansion is "in response to the explosive increase in consumer demand, which has made color television the fastest-growing industry in the world," according to W. Walter Watts, RCA group executive vice president. A total of \$36.4 million will be spent to expand color tube production, and \$13.3 million to increase color receiver facilities. More than 2.3 million color sets will be sold in 1965, Mr. Watts believes, and this number, he predicted, will increase to well over 5 million sets by 1970. At least 25% of all TV sets sold this year will be color units.

ASTRONAUTS PLAN COMMUNICATION TO EARTH WITH LASER BEAM

Maj. Frank Borman and Lieut. Commdr. James A. Lovell, Jr. will try to talk to earth over a laser beam during their planned orbit next year, they report. The laser experiment was originally set for much later in the Gemini project. It will be one of about 20 experiments that the astronauts will carry out, Commander Lovell stated. The laser transmitter is expected to be able to put out 10 watts.

SOLID-STATE HORN TWEETER ANNOUNCED BY MOTOROLA

A new solid-state exponential horn tweeter, with a response from 4,000 to 15,000 cycles, has been announced by Motorola. It operates by

the expansion and contraction of semiconductor material, according to *Television Digest*. A zirconate titanate tube is partially surrounded with metal, but insulated from it. The tube and the surrounding metal are connected to opposite ends of the secondary of an output transformer (a stepup transformer for this type of circuitry). A diaphragm, attached to the end of the zirconate tube, vibrates in accordance with the signal across the secondary of the transformer.

BOYCOTT CAMPAIGN ENCOURAGES GOOD TASTE IN COMMERCIALS

A campaign, started by O. A. Kemper of East Orange, N. J., is rapidly gaining supporters in "chain-letter fashion," claims its founder. It asks viewers to abstain for one month from buying the product advertised in any commercial which is too loud, contains singing, exceeds 30 seconds, or is used for over one month. Kemper claims that 409,900 households were participating as of the middle of June.

RADIO-FREQUENCY INTERFERENCE INJURES SPACE VEHICLES

Radio-frequency interference at altitudes where it could affect orbiting satellites and other space vehicles is increasing at an alarming rate, according to Larue A. Hoffman of Aerospace Corp. (California).

"There is already suspicion that a number of missiles and payloads may have been prematurely activated by RFI," Mr. Hoffman said.

The most dangerous sources of RFI at orbital altitudes are high-power radars operating from 200 to 3,000 mc. Less important, but still significant, are radar transmitters in the 3,000- to 10,000-mc range. Mr. Hoffman stated

that Aerospace Corp. has launched a program which includes both analytical studies and experimental and exploratory effort to obtain data on the more significant suspected sources of RFI. The program would probably include a low-cost spaceborne monitoring system.

J. E. SMITH, NRI FOUNDER RECEIVES GODDARD AWARD

Mr. J. E. Smith, founder of the National Radio Institute, America's largest and oldest radio-TV-electronics home-study school, has been given the Robert H. Goddard Award for outstanding professional achievement.

The award was made under the joint sponsorship of the Worcester (Mass.) Polytechnic Institute Alumni Association and College Board of Trustees. It is presented annually to one of the alumni, in memory of Professor Goddard, the "father of modern rocketry," one of the most outstanding graduates of Worcester Polytechnic.

Mr. Smith graduated from Worcester Polytechnic Institute in 1906 as an electrical engineer. In 1914 he founded the National Radio Institute, which has since enrolled over three-quarters of a million men throughout the world in its home-study programs.


NEW VIDEO TAPE RECORDER FOR BLACK-AND-WHITE OR COLOR

Ampex has demonstrated a line of video tape recorders operating at two speeds—9.6 and 4.8 inches per second. At the 9.6 ips speed it will record an hour of television, both picture and sound, on a single 2,900-foot reel of 1-inch video tape. At 4.8 ips, 2 hours of TV can be recorded. The tape is a high-quality video type especially designed by Ampex for the new unit. Cost per reel is \$64.95. Smaller reels will also be marketed at \$39.95.

"Tape costs at the higher standard are approximately half that of an equivalent amount of processed 8-mm color-sound movie film," William A. Roberts, Ampex president, pointed out. "At the lower speed, the cost advantage is even more dramatic."

Frequency response extends to 3.2 megacycles at 9.6 ips, and to more than 2 mc at 4.8 ips.

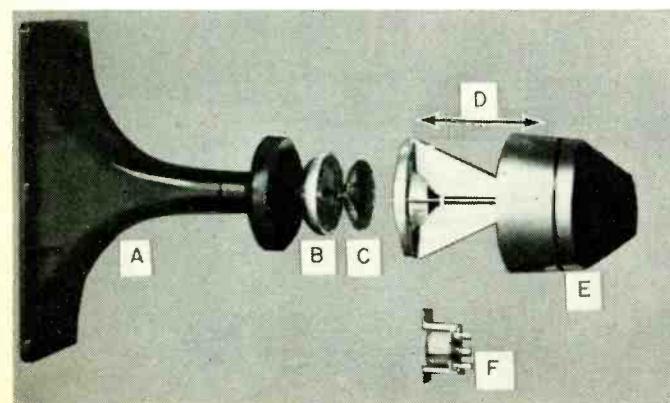The recorder will play back black-and-white television programs through nearly any home television re-



The new Motorola solid-state tweeter. A rod of lead zirconate and lead titanate changes its length according to the applied voltage and thus vibrates the diaphragm.



Something new!

LEARN AUTOMOTIVE and Maintenance ELECTRICITY AT HOME!

Here's another great opportunity for the man who wants his own business or a bigger pay check with a brighter future. It is a NEW DeVry program that gives you the advantage of earning while you learn.

Prepare in spare time at home for profitable jobs which can take you all the way from trouble-shooting on the electrical systems of automobiles, marine engines, trucks, tractors and other gasoline engines, to the general maintenance of electrical equipment in the home or in light industry.

DeVry's new program "brings the classroom to your home" through the magic of AUDIO-VISUAL AIDS: Lectures recorded by DeVry instructors combined with colorful 8 x 10" transparencies to make learning easier. You get the advantages of "programmed" learning through modern texts which are also handy for future



reference. To develop practical skill, you get and keep valuable shop equipment and manuals. This includes building the brand-new DeVry Transistorized Automotive Analyzer and the DeVry Silicon Battery Charger — ideal "tools" for earning extra money as you go.

This new program covers the entire electrical systems in automobiles and other vehicles, including transistorized ignition systems, alternators and regulators and other applications. In the maintenance field, it covers lighting, electric motors, controls, wiring — even transistors. The graduate from this program can be either a specialist as a troubleshooter on the electrical system of an automobile, or handle electrical lighting, heating, alarm and control systems. It is ideal for "one man" maintenance departments.

Check coupon at right and mail it today for FREE facts.

ACCREDITED MEMBER OF NATIONAL HOME STUDY COUNCIL

DeVry Technical Institute
Chicago • Toronto

5,000 FIRMS HAVE EMPLOYED DeVRY TECH ELECTRONICS GRADUATES...

There Must be a Reason!

*Let Us Prepare You at Home or In
One of Our Two Big Resident Schools
for a Profitable Career in*

ELECTRONICS

Across the continent, leading employers of personnel trained in electronics tell us that DeVry training is "Tops." Get the full story of DeVry Tech and the advantages it offers, by filling in the coupon below. The two free booklets pictured below tell of many fine opportunities for trained men in electronics: the great variety of jobs, from research, production, operation, maintenance and servicing of electronic equipment — to a neighborhood TV-radio sales and service business of your own. They'll tell you too, how DeVry has prepared men for good jobs with outstanding firms: on practical, "brass-tacks" problems with actual electronic equipment.

Here's good news: you don't need advanced education or previous technical experience to get started. If you can follow simple directions, you should be able to prepare with DeVry's help for real money in a field that may offer the opportunity of your lifetime.

Employment Service: With many employers so enthusiastic about employment Service can help our graduates get started in electronics, or can assist them toward promotions later.

FREE!

SEND COUPON
FOR BOOKLETS
ON ELECTRONICS
AS A CAREER



DeVRY TECHNICAL INSTITUTE

4141 Belmont Ave., Chicago, Ill. 60641, Dept. RE-9-V

I AM INTERESTED IN ELECTRONICS. Please give me your two free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel"; also include details on how to prepare for a career in this field. The following opportunity fields (check one or more) interest me:

- Space & Missile Electronics
- Television & Radio
- Microwaves
- Automation Electronics
- Radar

- Communications
- Computers
- Industrial Electronics
- Broadcasting
- Electronic Control

I AM INTERESTED IN AUTOMOTIVE AND MAINTENANCE ELECTRICITY. Please supply further information.

NAME _____ AGE _____

ADDRESS _____ APT. _____

CITY _____ STATE _____ ZIP _____


Check here if you are under 16 years of age.

Canadian residents: Write DeVry Tech of Canada, Ltd.,
2095A 970 Lawrence Avenue West, Toronto 19, Ontario

Circle 4 on reader's service card


COMPLETE TUNER OVERHAUL

ALL MAKES—ONE PRICE

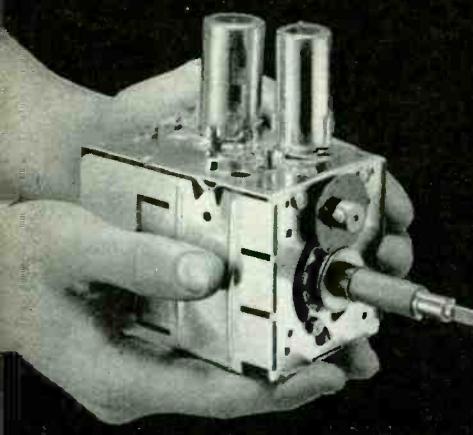

ALL LABOR
AND PARTS
(EXCEPT TUBES
& TRANSISTORS)*

995

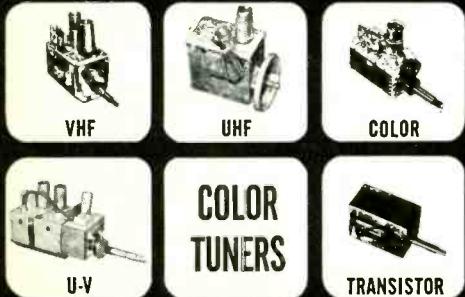

Guaranteed Color Alignment—No Addit. Charge

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.

Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

Pioneers in TV Tuner Overhauling

CASTLE
TV TUNER SERVICE, INC.

MAIN PLANT: 5715 N. Western Ave., Chicago 45, Illinois
EAST: 41-96 Vernon Blvd., Long Island City 1, N.Y.
CANADA: 136 Main Street, Toronto 13, Ontario.

*Major Parts are additional in Canada

NEWS BRIEFS continued



The new Ampex home video tape recorder.

ceiver, either color or black-and-white, by adding special extension components at an estimated cost of about \$25. No internal modification of the receiver circuitry is necessary. Home recorders are interchangeable. The tapes made on one machine may be played back on any other.

Price of a one-speed machine is listed \$1,095. For the two-speed type, \$1,295. Four furniture console systems run from \$1,795 to \$2,495, depending on choice of one- or two-speed recorders and color or black-and-white receivers. A line of television cameras and other accessories will be offered with the equipment.

TOM JASKI DEAD

Thomas Jaski, prolific RADIO-ELECTRONICS author, died suddenly July 4, some weeks after an automobile accident, from which he was making an excellent recovery.

RADIO-ELECTRONICS is published by Gernsback Publications, Inc., Chairman of the Board: Hugo Gernsback, President: M. Harvey Gernsback, Vice President-Secretary: G. Aliquo, Vice President-Treasurer: Charles A. Raible.

Editorial, Advertising, Subscription and Executive offices: 154 West 14th Street, New York 10011.

Subscribers: When requesting change of address please furnish an address label from a recent issue. Allow one month for change of address.

ADVERTISING REPRESENTATIVES: East: John J. Lamson, Eastern Sales Manager, RADIO-ELECTRONICS, 154 West 14th Street, New York 10011, 212 AL 5-7755; Midwest: P. H. Dempers Co., 740 North Rush Street, Chicago, Illinois 60611, 312 MI 2-4245; Southeast: Neff Assoc., 15 Castle Harbor Isle, Ft. Lauderdale, Fla. 33308, 305 LO 6-5656; J. Sidney Crane, Assoc., 22 8 St., N.E., Atlanta, Ga. 30309, 404 TR 2-6720; Texas/Arkansas: Media Representatives, Inc., 2600 Douglas Avenue, Irving Texas 75060, 214 BL 5-6573; West Coast/Oklahoma: Husted-Coughlin, Inc., 1830 W. 8th Street, Los Angeles, Calif. 90057, 213 389-3132; Husted-Coughlin, Inc., 444 Market Street, San Francisco, Calif. 94111, 415 GA 1-0151; United Kingdom: Publishing & Distributing Co., Ltd., Mitre House, 177 Regent St., London W.1, England.

Between September 1955 and August 1965, Mr. Jaski contributed 60 articles to this magazine. He was also the author of two books published by the Gernsback Library, *Industrial Electronics Made Easy*, and *How to Get the Most out of Your VOM*.

Besides being a licensed professional engineer in the State of California, he had recently acquired the degree of Master of Science in psychology, and was working in the field of programmed instruction. It was on this subject that he wrote the editorial in last month's issue.

MARTIAN IONOSPHERE WEAK, MARINER OBSERVATIONS FIND

The ionosphere on Mars is very much less dense than had been expected before Mariner sent back information last July, scientists report. This might make it impossible to communicate from one point on the planet to another on the opposite side as is possible on Earth. In addition, the layer is only half as high as had been supposed.

WASTELAND IN MONTE CARLO

UNESCO reports that the tiny country of Monaco has the highest concentration of TV receivers in the world, more than 52 sets per hundred persons, compared to 33 sets per person in the USA. (But the United States has 100 radio sets per 100 people.) Japan is number two, after the U.S., in numbers of TV sets (US 60 million, Japan 13 million).

MARINER-EARTH TRANSMISSIONS USE DIGITAL TELEVISION

Television pictures of Mars sent to Earth by Mariner IV were made possible by a digital system of television, in which the varying intensities of light and darkness along a scanned line were represented by a series of numbers, rather than by continuously varying signal strength as in ordinary television. (Ordinary television transmission would be known as an *analog* system in the language of computers.)

The principal purpose of the digital technique was to allow exact reconstruction of the image even when the signal was almost drowned in noise.

Each picture was broken down into 200 lines. Each of these lines was separated into 200 components, or dots. A signal value was given to each dot, ranging from zero for pure white to 63 for pure black. These digits were transmitted in a six-bit code—six impulses or spaces (no impulse) per number. Thus, the receiver on earth could allot the right light intensity to any element of the picture, as long as the signal was good enough to make it possible to distinguish between a sig-

◀ Circle 6 on reader's service card

nal and the absence of a signal. Variations in propagation conditions, or noises other than those strong enough to blot out the signal entirely, would have no effect—the original signal could be amplified, or *reconstructed*, to give exactly the signal that started from Mars.

The pictures were taken with a single exposure on a 1-inch vidicon tube and exposed to the light of Mars for .08 to 0.2 second, depending on the variable light. The light was then shut off while the picture was read out onto the tape in 24 seconds. Then another 24-second period elapsed to prepare the vidicon for the next picture. The playback was very much longer. It required 1,284 seconds to play back 1 second of recorded data.

CALENDAR OF EVENTS

6th International Conference on Medical Electronics & Biological Engineering, Aug. 23-27; Tokyo, Japan

20th National Meeting, Association for Computing Machinery, Aug. 24-26; Sheraton-Cleveland Hotel, Cleveland, Ohio

Wescon (Western Electronics Show & Convention), Aug. 24-27; Cow Palace, San Francisco, Calif.

1965 International Antenna & Propagation Symposium, Aug. 30-Sept. 1; Sheraton Park Hotel, Washington, D. C.

Salon International de Radio et de la Television, Sept. 9-19; Hall Monumental du Parc des Expositions a la Porte de Versailles, Paris, France

International Conference on Thermionic Electrical Power Generation, Sept. 20-24; IEE, Savoy Place, London, England

New York High Fidelity Music Show, Sept. 29-Oct. 3; New York Trade Show Building, New York, N. Y.

Second International Exhibition of Industrial Electronics, Sept. 7-11; Swiss Industries Fair, Basel, Switzerland

1965 Fall URSI Meeting (US National Committee of the International Scientific Radio Union, URSI), Oct. 4-6; Dartmouth College, Hanover, N. H.

1965 Canadian Electronics Conference, Oct. 4-6; Automotive Bldg., Toronto, Ont.

17 Annual Audio Engineering Society Convention, Oct. 11-15; Barbizon Plaza Hotel, New York, N. Y.

FCC RAPS LOUD COMMERCIALS

Objectionably loud commercials are contrary to the public interest, the FCC declared in a statement of policy issued July 12. The FCC also singled out commercials that, in addition to being loud, are delivered in a "rapid and strident manner," as well as commercials well above the volume level of the programs they interrupt.

Answering the objection of many broadcasters and TV advertisers that subjective factors play a great part and that what sounds loud to one may not to another, the FCC points out that matters have reached a point where "the complaints obviously cannot be dismissed on the ground that 'commercials aren't really loud—they just sound loud'."

Broadcasters have been instructed to take appropriate measures to eliminate the nuisance.

END

IF THE RCA MARK VIII C-B TRANSCEIVER IS SO GREAT AT \$114.95*



- 9 crystal-controlled transmit and receive channels
- Tunable receiver for reception of 23 C-B channels; dial marked in both channel numbers and frequency
- Exceptionally good voice reproduction
- Highly selective superheterodyne receiver with one rf and two if amplifier stages
- Electronic switching—no relay noise or chatter
- Illuminated "working channel" feature
- Light and compact—only 3½ inches high, weighs only 8 pounds with mike; fits easily under the dashboard of even a compact car
- Improved Automatic Noise Limiter to reduce effects of ignition and similar interference

...HOW COME THE NEW MARK NINE IS WORTH \$20.00* MORE?



It has all the Mark VIII features— PLUS these additional features...

- Combination "S" Meter and Relative RF Output Meter. "S" Meter indicates the relative strength of incoming signal in "S" units. RF Output Meter (EO) indicates relative strength of the signal being transmitted.
- Spotting Switch. Permits precise manual tuning of receiver without use of receiver crystals. Receiver can be tuned (or "spotted") quickly to any incoming channel for which you have a transmit crystal. This means, when you buy crystals for extra channels,

*Optional distributor resale price.

you can (if you wish) omit the RECEIVE crystals and buy only TRANSMIT crystals. This feature alone pays the price difference if you use a number of channels.

- External Speaker Jack. Lets you connect an external speaker to the set, so incoming calls can be heard in remote locations.

GET THE FACTS. Write for free descriptive folder on either the Mark VIII or Mark Nine to: Commercial Engineering, Department I39R, RCA Electronic Components and Devices, Harrison, N.J.

AVAILABLE THROUGH YOUR AUTHORIZED RCA C-B RADIO DISTRIBUTOR



The Most Trusted Name in Electronics

Circle 7 on reader's service card

You get more for your money from NRI-

America's oldest and largest Electronic, Radio-TV home-study school

Compare if you like. You'll find—as have so many thousands of others—that NRI training can't be beat. From the delivery of your first lessons in the remarkable, new Achievement Kit we send you, to "bite size," easily-read texts and carefully designed training equipment . . . NRI gives you more value.

Shown below is a dramatic, pictorial example of all of the training materials included in just one NRI Course. *Everything* you see pictured below is included in low-cost NRI training. Other major NRI courses are equally complete. Text for text, kit for kit, dollar for dollar—your best home-study buy is NRI.




GET A FASTER START WITH NRI'S NEW EXCLUSIVE ACHIEVEMENT KIT

The day we receive your enrollment application we mail out your Achievement Kit. It contains everything you need to make an easy, fast start in the Electronics training of your choice. This attractive, new starter kit is an outstanding, logical way to introduce you to home-study as NRI teaches it . . . an unparalleled example of the value of NRI training . . . training that is backed up by a dedicated staff and the personal attention you should expect of a home-study school. It is your first of a number of special training aids carefully developed by the NRI laboratories to make your adventure into Electronics absorbing, meaningful. What's in the Achievement Kit? Your first group of lesson texts; a rich vinyl desk folder to hold your study material; the industry's most complete Radio-TV Electronics Dictionary; valuable reference texts; lesson answer sheets; pre-addressed envelopes; pencils; pen; engineer's ruler—even postage. No other school has anything like the NRI Achievement Kit.

LEARNING BECOMES AN ABSORBING ADVENTURE WITH NRI TRAINING KITS


Electronics comes alive with NRI training kits. What better way to learn than by doing it? That's why NRI pioneered and perfected the "home lab" technique of learning at home in your spare time. You get your hands on actual parts and use them to build, experiment, explore, discover. NRI invites comparison with training equipment offered by any other school. Begin NOW this exciting program of practical learning. It's the best way to understand the skills of the finest technicians—and make their techniques your own. Whatever your reason for wanting to increase your knowledge of Electronics . . . whatever your field of interest . . . whatever your education . . . there's an NRI instruction plan to fit your needs, at low tuition rates to fit your budget. Get all the facts about NRI training plans, NRI training equipment. Fill in and mail the attached postage-free card today. No salesman will call. NATIONAL RADIO INSTITUTE, Washington, D.C. 20016.

OUR 50th YEAR OF LEADERSHIP

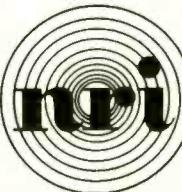

IN ELECTRONICS TRAINING

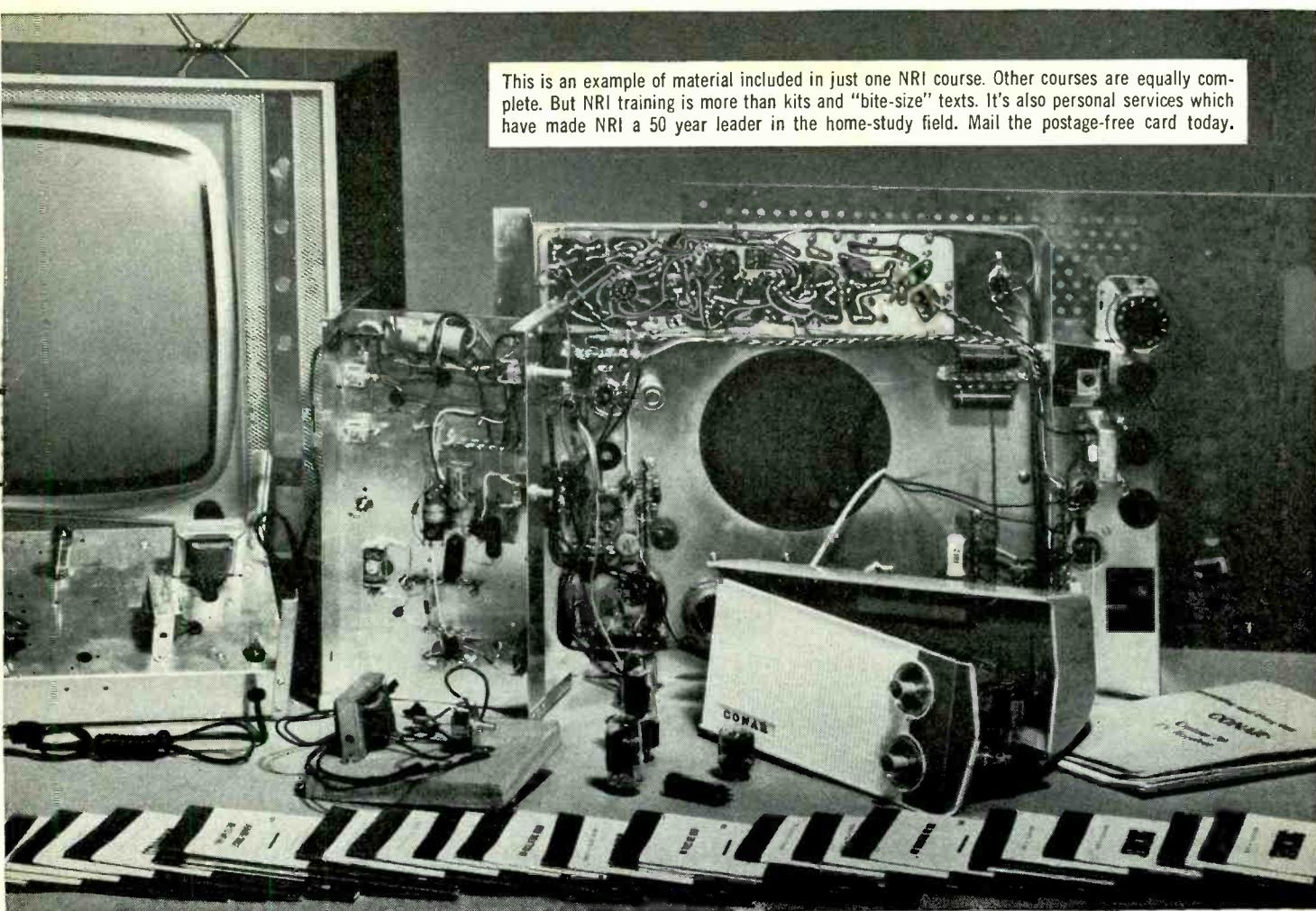
This is an example of material included in just one NRI course. Other courses are equally complete. But NRI training is more than kits and "bite-size" texts. It's also personal services which have made NRI a 50 year leader in the home-study field. Mail the postage-free card today.



great profits

SONOTONE 14T MONO CRYSTAL REPLACEMENT CARTRIDGE

(small inventory)

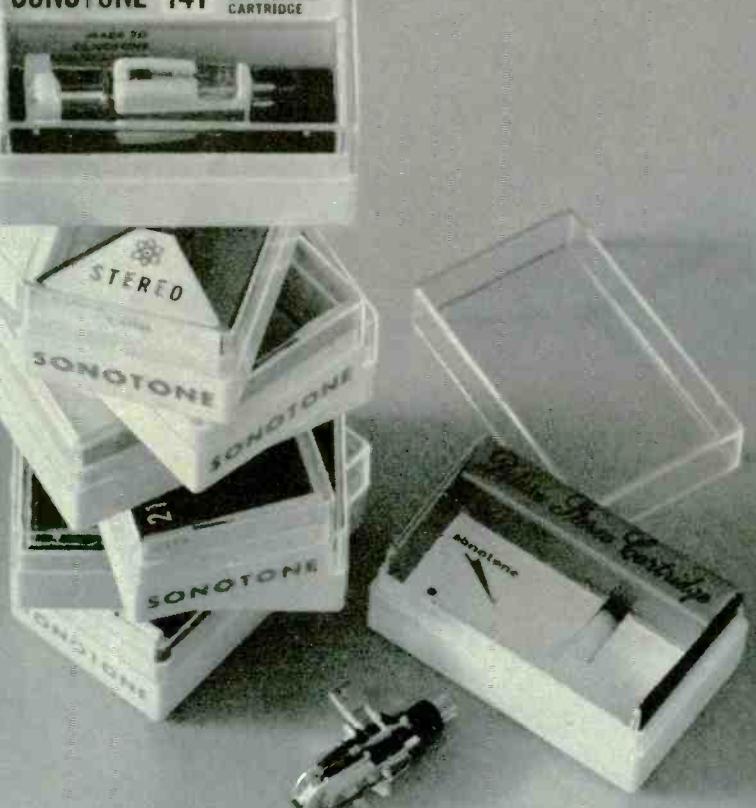

Imagine—just 6 Sonotone® crystal cartridges replace 146 models. In microminiatures, the Sono-tone Micro-Ceramic® series updates to 1965 performance almost any phonograph using a ceramic cartridge produced within the past 20 years.

Replacements in transistor phonographs? The "24T", "27T" and "35T" Micro-Ceramics are the answer. For the world's "safest cartridge," try the "21TR" with its fully retractable, hinged mounting bracket, bottoming button and Sono-Flex® stylus. Replacements in the top-end hi-fi models? The audiophile-accepted Sonotone "9T" series is your best bet. And from the standpoint of customer satisfaction, only Sonotone cartridges are equipped with the virtually indestructible Sono-Flex stylus. Now the clincher: Sonotone cartridges are direct replacements in more than 15 million phonographs in which they are original equipment.

These are just a few of the reasons you need stock fewer Sonotone cartridges than other brands—and still have the right replacement for just about every phonograph that comes into your shop. For comprehensive cartridge replacement guide, write:

SONOTONE

audio products
Sonotone Corp., Electronic Applications Div., Elmsford, N.Y.
Export: Singer Prods. Co., Inc., N.Y.C. Cable: EXREGNIS, N.Y.

Circle 9 on reader's service card



TAKES MORE THAN A GIMMICK
TO GET ALL THE TV CHANNELS

Dear Editor:

Without in any way depreciating the very interesting article by L. W. Reinken, "Get All the TV Channels" (May R-E), I believe he missed one important "gimmick."

The most crucial gimmick for adjustment on production tuners is "spiking": precise-tuning coils by moving a turn, or part of a turn. A "spiking slack" is usually allowed for in production of these coils.

The tool used is a Bakelite or polystyrene rod shaped for the job—hence the name "spike" and "spiking".

I believe Mr. Reinken will agree that neither gimmick nor spiking alone is a panacea. Both together, judiciously applied, make an unbeatable combination.

Using a gimmick means adding something—a twisted pair of wires and sometimes a capacitor—and soldering and twist-and-cut. Spiking requires only low-loss cement to seal the winding after adjustment.

One last point: with either approach, the coil never looks quite neat, and there is always the temptation, for a novice, to clean it up. A young friend, an engineering junior working with me, very proudly showed me two tuners that he had "de-messed" after I had painstakingly spiked them the previous evening. So, I counted ten, and

Meyer evaluates . . . TRANSISTOR OUTPUT CIRCUITS

Daniel E. Meyer, well known to RADIO-ELECTRONICS readers as the designer of several outstanding transistor amplifier and preamp construction projects, describes a variety of transistor output circuits, exploring their merits and drawbacks. Now that things have settled a bit, most manufacturers stick with two or three tried-and-true circuits.

Coming in . . . October
RADIO-ELECTRONICS

p-a-t-i-e-n-t-l-y explained to him the facts of life about spiking.

The moral: no matter how messy a coil looks, if its windings are sealed, don't touch unless you know what you are doing.

A. D. EMURIAN

Westwood, N. J.

SERVICERS GET LOUSY DEAL ON LONG WARRANTIES

Dear Editor:

A letter appeared in the correspondence column of your June, 1965 issue, by Mr. Kenneth Conley, opposing Frank Moch's critical appraisal of TV manufacturers' extended warranties.

I feel that Mr. Conley has misunderstood Mr. Moch's motives and does not understand the problems in retail TV sales and service.

If manufacturers want to place 5-year warranties on their products, then they should up-grade the quality of those products to make such a warranty practical.

A dealer cannot service a TV set over a long period of time, free of charge, without some help from the factory. Some manufacturers seem to want the authority to extend long warranties, without shouldering the responsibility of executing these warranties. Instead, this task is assigned to the dealer, who has to carry on with very little help from the factory.

This is the point that Mr. Moch is trying to get across. He is not disturbed because members of his profession will lose opportunities to "gouge" customers. (You will find customer gougers and incompetent men in all professions. They receive much publicity, although they are few in number.)

As Mr. Conley is an electrical engineer, I am sure he understands the complexity of a TV set and has a nodding acquaintance with its service problems. I sincerely hope he will come to a better understanding of the men who use their knowledge and skill to perform this work.

ORIGEN DANIELS
Radio & Television Service
Niantic, Conn.

SOME COMMON MISUNDERSTANDINGS ABOUT TRANSISTOR IGNITION

Dear Editor:

About Mr. James K. Hall Jr.'s disenchantment with transistor ignition systems (Correspondence, May): he notes the performance of the transistor ignition system as being nothing more than "satisfactory". This points out a common problem, the Madison Avenue

continued on page 16

Otto Werk sent in this Coupon

LTV UNIVERSITY

Desk J-59

9500 West Reno, Oklahoma City, Okla.

- Send me the UNIVERSITY Hi-Fi Guide
 Send me the MUSTANG STORY

Name _____

Address _____

City _____ State _____ Zip Code _____

Look what he got!

Lots of help... right from the horse's mouth, 'cause now University's got a Mustang! Plus a corral full of other speakers. University speaker guides showed him how to choose a speaker system, how to build a custom system with separate speakers—and much more! Send for these guides right away. You'll be an expert too. Just like a smart Dane named Otto.



LTV UNIVERSITY
SPEAKERS / MICROPHONES

9500 W. Reno, P. O. Box 1056, Oklahoma City, Oklahoma

Circle 10 on reader's service card



Your new copy is waiting

FREE! For fun and pride in assembly, for long years of pleasure and performance, for new adventures in creative electronics mail the coupon below and get Conar's brand new catalog of quality do-it-yourself and assembled kits and equipment. Read about items from TV set kits to transistor radios... from VTVMs to scopes... from tube testers to tools. And every item in the Conar catalog is backed by a no-nonsense, no-loopholes, money-back guarantee! See for yourself why Conar, a division of National Radio Institute, is just about the fastest growing entry in the quality kit and equipment business.

CONAR

MAIL THIS COUPON NOW

CONAR 3939 Wisconsin Ave., Washington 16, D.C.
Please send me your new catalog.


JC5C

Name _____

Address _____

City _____ State _____ Z-Code _____

Circle 11 on reader's service card

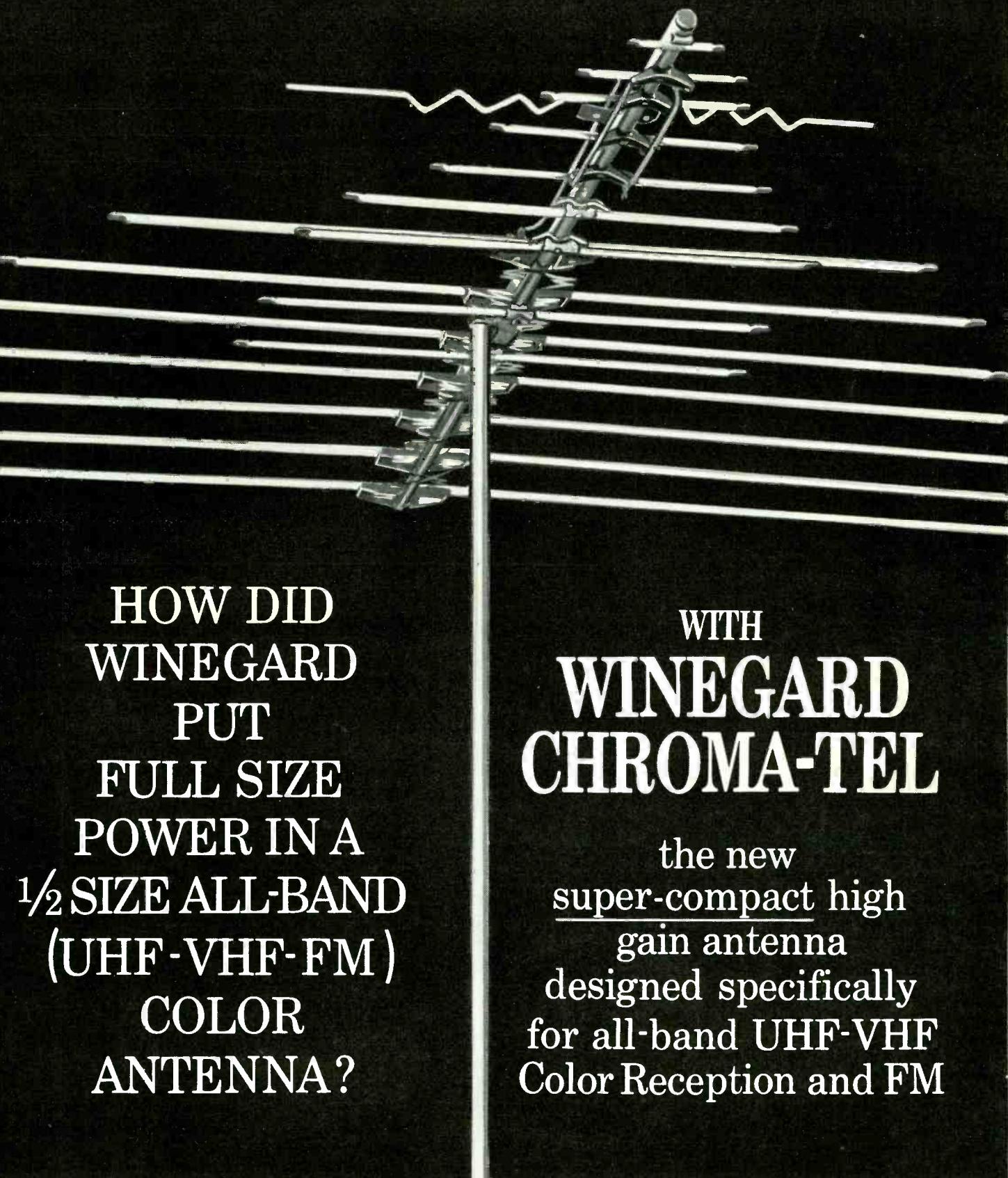

HOW DID
WINEGARD
PUT
FULL SIZE
POWER IN A
1½ SIZE ALL-BAND
(UHF-VHF-FM)
COLOR
ANTENNA?

WITH
WINEGARD
CHROMA-TEL

the new
super-compact high
gain antenna
designed specifically
for all-band UHF-VHF
Color Reception and FM

A big disadvantage of most all-band (UHF, VHF, FM) antennas is that they are larger and heavier than necessary. This is because they are really VHF antennas with UHF antennas tacked on the front end. *Chroma-Tel* isn't. It's super-compact and the

first integrated antenna designed specifically for all-band UHF-VHF color operation.

How did we reduce the size so drastically without sacrificing performance?

Two ways. First with our new *Chroma-Lens*

Director System. With this unique system, we are, for the first time, able to intermix both VHF and UHF directors on the same linear plane without any sacrifice of performance.

Second, with *Impedance Correlators*. These are the special phasing wires that automatically step up the impedance of Chroma-Tel's 72 ohm driven elements to 300 ohms. The correlators make sure each element has an accurate 300 ohm impedance at its given frequency. No other antennas with multiple driven elements have this! They also allow us to place the elements *only 5 3/4"* apart instead of 10" to 14" apart as on other all-band antennas, reducing antenna length by one-half.

With the new Winegard Chroma-Tel antenna, we have eliminated *half* the bulk, *half* the wind loading, *half* the storage space, *half* the truck space, and *half* the weight . . . yet still have the best working, easiest installing UHF-VHF-FM antenna ever developed!

You give your customers a neater installation that performs as well or better than any other all-band antenna on the market . . . and at a much lower price.

Compare Performance. You can't find an all-channel UHF-VHF-FM antenna that will give you better results than Chroma-Tel. Look at the polar patterns. There are no side lobes with Chroma-Tel because the elements are straight . . . unlike V'd elements that offer an element surface sideways to the signal, Chroma-Tel's straight ele-



Exclusive Winegard Impedance Correlators insure 300 ohm impedance on each element


ments will not pick up ghosts from sides or back. Chroma-Tel's front-to-side ratio is practically infinite—Chroma-Tel's exceptional front-to-back ratio is up to 30 db.

Compare Construction. The Chroma-Tel is Winegard quality throughout . . . from its sales-making compact 4-color box, to its weather resistant Gold Vinylized Finish, to its first quality snap-lock hardware.


For complete information on the exciting new Winegard Chroma-Tel All-Band Antenna, ask your distributor or write for Fact-Finder #242 today.



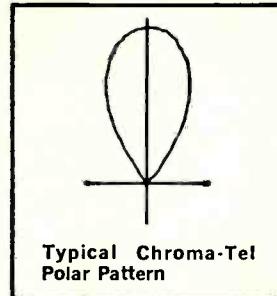So compact it fits in the back seat of a car



Typical Chroma-Tel Polar Pattern

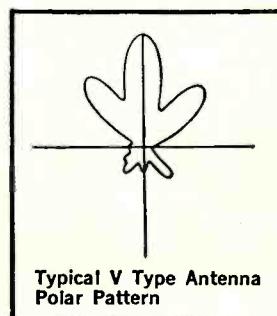


Typical V Type Antenna Polar Pattern




All Chroma-Tels include Winegard's model CS-283 UHF-VHF signal splitter. Splitter hangs conveniently behind TV set. Separates UHF and VHF signals coming from antenna to the two sets of terminals on your set. It's yours FREE when you buy Chroma-Tel.

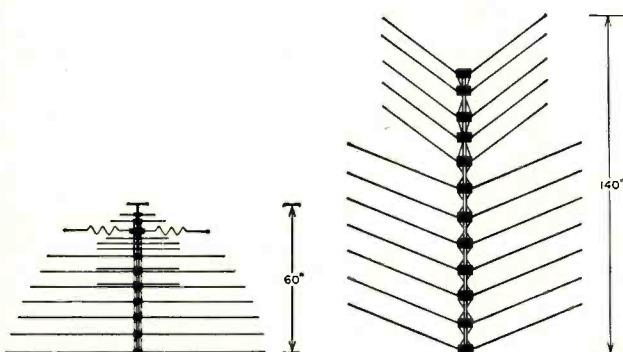Compare Size and Price. We've illustrated the super-compact Chroma-Tel CT-80 and a comparable V type antenna. Note the difference in size, price and weight for equal or better performance. Because it's even much smaller than ordinary VHF antennas of comparable performance, it is perfect for attic installations, too!




Winegard Chroma-Tel V type (Approximate Figures)

Boom Length:	60"	140"
Total Weight:	5 lb., 1 oz.	10 lb., 3 oz.
Carton Size:	.97 cu. ft. (less than 1)	5.8 cu. ft.
Number of Elements:	17	12
List Price:	\$27.50	\$50.00

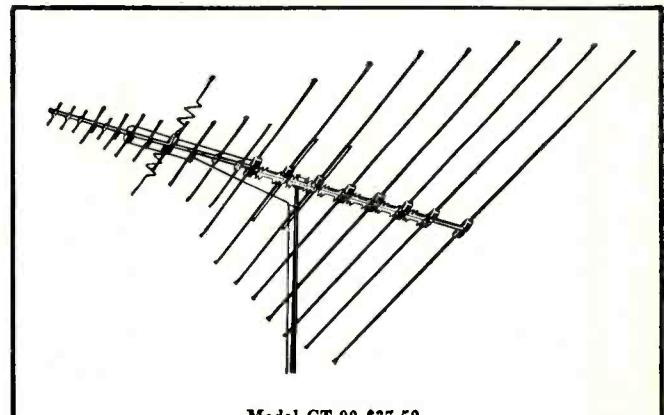

Model CT-90 \$37.50

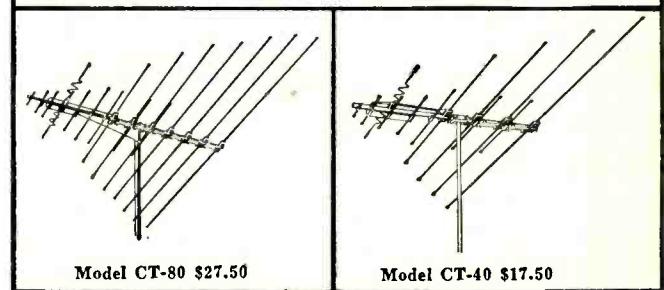

Model CT-80 \$27.50

Model CT-40 \$17.50

Winegard Co.
Antenna Systems

3000 Kirkwood • Burlington, Iowa

Circle 12 on reader's service card

TUNER REPAIRS

Includes ALL parts (except tubes)...
ALL labor on ALL makes for complete overhaul.

\$950.



FAST, 24-HOUR SERVICE with FULL YEAR WARRANTY

Sarkes Tarzian, Inc., largest manufacturer of TV and FM tuners, maintains two completely equipped Service Centers, offering fast, dependable tuner repair service. Tarzian-made tuners received one day will be repaired and shipped out the next. More time may be required on other makes. Every channel checked and realigned per manufacturer's specs. Tarzian offers full, 12-month guarantee against defective workmanship and parts failure due to normal usage. Cost, including all labor and parts (except tubes), is only \$9.50 and \$15 for UV combinations. No additional costs. No hidden charges. You pay shipping. Replacements at low cost are available on tuners beyond practical repair.

Always send TV make, chassis and Model number with faulty tuner. Check with your local distributor for Sarkes Tarzian replacement tuners, parts, or repair service. Or, use the address nearest you for fast factory repair service.

SARKES TARZIAN, INC.
TUNER SERVICE DIVISION

Dept. 200
537 South Walnut St.,
Bloomington, Indiana
Tel: 332-6055

Dept. 200
10654 Magnolia Blvd.,
North Hollywood, Calif.
Tel: 769-2720

MANUFACTURERS OF TUNERS, SEMICONDUCTORS,
AIR TRIMMERS, FM RADIOS, AM-FM RADIOS,
AUDIO TAPE and BROADCAST EQUIPMENT

CORRESPONDENCE continued

selling approach, in which all is promised but little is delivered.

The main advantages of transistor ignition are neither an increase in gas mileage nor an increase in acceleration. The major advantages may be stated in brief as: Transistor ignition extends the time required between tuneups; it maintains correct tuneup for a much longer time; it simplifies tuneup to a check of point gap spacing, sparkplug gap spacing, and timing; it extends greatly the life of breaker points; and it extends (less) the life of the sparkplugs. Adding these advantages, we find that the improved performance of a tuned-up engine over an extended time is the major advantage. Coupled with this improved performance is the reduction in the need for replacement parts. Both advantages will then provide a long-time savings in costs.

As to the difficulty with a defective system, as I have noted in my book on transistor ignition systems (scheduled to be published by John F. Rider Publisher, Inc.), it would be prudent to keep the original system intact and have it wired as a standby so that it may quickly be substituted for the transistor system. This permits a quick check of the transistor system to determine if it is defective. It also permits the use of test instruments that will not work with transistor ignition systems. And most important, it permits operating the engine with the conventional ignition system should the transistor system become defective.

MARVIN TEPPER

Milton, Mass.

BUT IF YOU WANT TO WORK AT BEING A FOOL . . .

Dear Editor:

In Peter Sutheim's interesting article on "Output Protection for Transistor Amplifiers" (page 45, June issue), our simple protection system is described as "foolproof," a word that has a delightful ring to it in our ears. Foolproof, he says, however, except when the transistors are already near maximum temperature. Mr. Sutheim is quite right. If the junctions happen to be as hot as a three-dollar pistol (prices have gone up), a transistor or two will join its ancestors if you short the output.

We'd like to complete the picture, however, for those few undiscriminating souls who don't subscribe to R-E and may have missed Pete's full report on the TR-2 in the May issue. The fact is that neither we nor Mr. Sutheim have found any way to get the transistors even perceptibly warm in actual service —so the user can actually short the output or overload the input (or both) all

he likes, if that's how he gets his kicks, without even popping the circuit breaker.

Both we and Mr. Sutheim (we learned by phone) have found a way to burn up transistors in the TR-2, if this happens to be your project for the month. First you run a steady tone from an audio generator through the amplifier for several minutes (you can't do this with program material), with the output set at 40 to 50 watts into a dummy load. This is the only way to heat up the transistors. Short the output continuously for at least 15 seconds, then give the one or two dead transistors a decent burial.

RICHARD H. DORF
President
Schober Organ Corp.
New York, N. Y.

IN HARMONY ON ELECTRONIC MUSIC

Dear Editor:

Congratulations on your cover and article in the June 1965 issue. It is going to help the cause of electronic music a great deal, because it proves that the field has reached a certain maturity, and that it is quite literally "in tune with our times."

The only point I would like to see more thoroughly emphasized is that it is not absolutely necessary to have a million-dollar studio to enter the field of electronic music and begin composing. My compositions are beginning to get attention even though they are composed on homemade instruments and quite ordinary tape recorders. The field is so vast that anyone caring to explore it will have plenty of room.

And this is a good opportunity to commend RADIO-ELECTRONICS for the enthusiastic backing you have given the cause of electronic music, in many phases, down through the years.

IVOR DARREG
Los Angeles, Calif.

END

37

You can obtain, free of charge, more information or literature about products and services advertised or editorially featured in RADIO-ELECTRONICS. Circle the appropriate numbers on the card facing Page 72—and mail the card to us today.

free

with your purchase of a **PHOTOFACT® Library**—
the supreme gift for your family...

the famous 14-volume **NEW STANDARD ENCYCLOPEDIA!**

**AN INVALUABLE
TREASURY OF
KNOWLEDGE FOR
ALL THE FAMILY**

sells at retail for

\$149.50

now yours

FREE with the purchase
of a *Photofact*
Library consisting of
225 Sets or more—

Offer for limited time only—ACT NOW!



A HANsome, PRACTICAL
HOME REFERENCE
LIBRARY

**Get this wonderful bonus for your family—give
your earning power a big boost with PHOTOFACT
—the world's finest TV-radio service data**


Now, more than ever, it pays to own a PHOTOFACT Library—the time-saving, troubleshooting partner guaranteed to help you earn more daily. Now, you can start or complete your PHOTOFACT Library the special Easy-Buy way, and get absolutely FREE with your purchase, the famous 14-volume NEW STANDARD ENCYCLOPEDIA. It's a great reference library for all the family—complete, authoritative, indispensable. Retails for \$149.50—yours absolutely FREE with the purchase of a PHOTOFACT Library consisting of 225 Sets or more!

OWN A PHOTOFACT LIBRARY THE EASY-BUY WAY:

- Only \$10 down • 30 months to pay
- No interest or carrying charges • Prepaid transportation
- Add-on privilege of a year's advance subscription to current Photofact data, on the same Easy-Buy contract
- Save 30¢ per Set—special \$1.95 price applies on Easy-Buy (instead of regular \$2.25 price)

THERE'S NEVER BEEN A DEAL TO EQUAL THIS!

**GET THE
DETAILS
NOW**

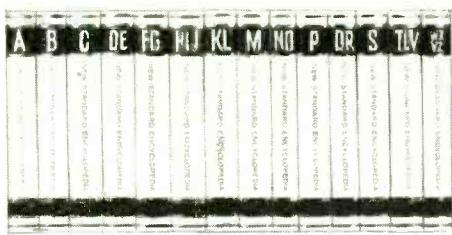

**ORDER YOUR PHOTOFACT LIBRARY NOW—
AND GET YOUR FREE STANDARD ENCYCLOPEDIA**

See your Distributor for the full details of the PHOTOFACT-Encyclopedia Deal, or send coupon at right! Also ask about a Standing Order Subscription to current PHOTOFACT and Specialized Service Series (FREE File Cabinets available with Subscriptions). ACT NOW!

SEE YOUR DISTRIBUTOR OR SEND COUPON TODAY

Circle 14 on reader's service card

HOWARD W. SAMS & CO., INC.

Howard W. Sams & Co., Inc., Dept. REF-9
4300 W. 62nd St., Indianapolis, Ind. 46206

Send full information on the PHOTOFACT Library-Encyclopedia Deal, and details of the Easy-Buy Plan

My Distributor is:

Shop Name _____

Attn. _____


Address _____


City _____ State _____ Zip _____



**“Get more
education
or
*get out of
electronics***

...that's my advice.”

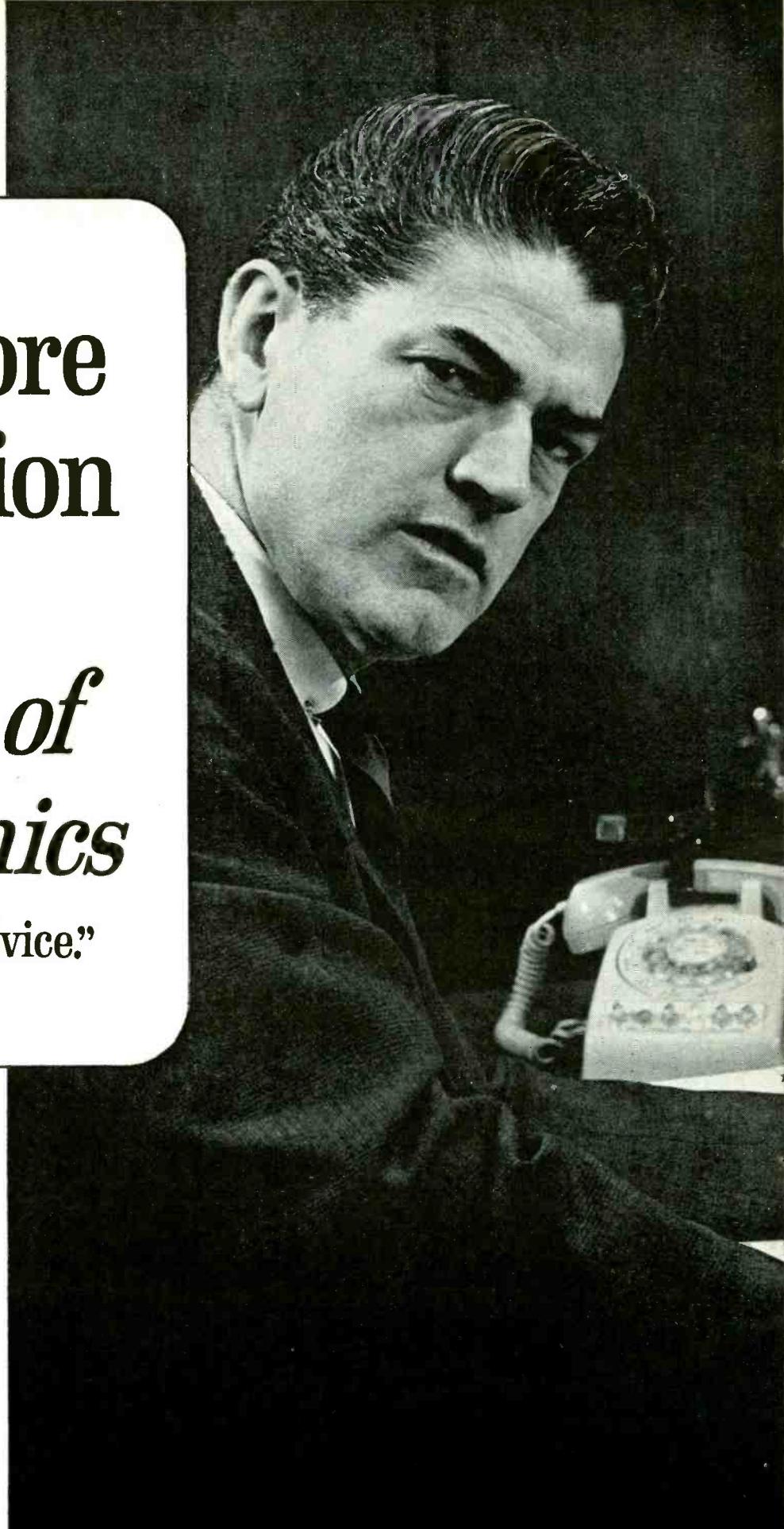

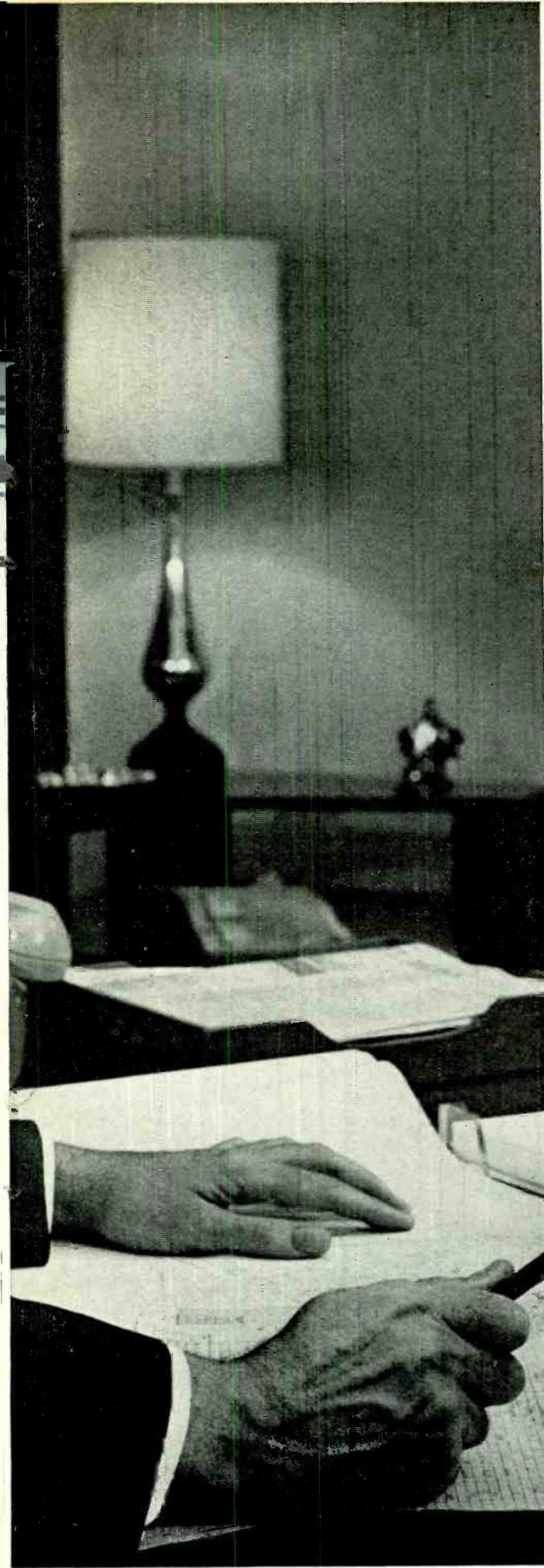

Ask any man who really knows the electronics industry.

Opportunities are few for men without advanced technical education. If you stay on that level, you'll never make much money. And you'll be among the first to go in a layoff,

But, if you supplement your experience with more education in electronics, you can become a specialist. You'll enjoy good income and excellent security. You won't have to worry about automation or advances in technology putting you out of a job.

How can you get the additional education you must have to protect your future—and the future of those who depend on you? Going back to school isn't easy for a man with a job and family obligations.

CREI Home Study Programs offer you a practical way to get more education without going back to school. You study at home, at your own pace, on your own schedule. And you study with the assurance that what you learn can be applied on the job immediately to make you worth more money to your employer.

You're eligible for a CREI Program if you work in electronics and have a high school education. Our FREE book gives complete information. For your copy, airmail postpaid card or write: CREI, Dept. 1409C 3224 Sixteenth Street, N.W., Washington, D.C. 20010



Circle 15 on reader's service card

SEPTEMBER, 1965

SERVICE CLINIC

By JACK DARR Service Editor

"Do Not Measure!" (Why Not?)

FOR TOO MANY TV TECHNICIANS, THE points marked DO NOT MEASURE on a TV chassis are just like a wet-paint sign! We don't get off easy, though, if we disobey. It's easier to wipe paint off an inquiring fingertip than to send off a meter to be repaired. Cheaper, too.


"But," someone says plaintively, "why not?" Here's why not. The warn-

ings are placed on these points because they carry not only high dc voltages, but *very high pulse voltages!* These can play whacky with the input circuits of our test equipment—the voltage dividers of vtm's, vom's and the input blocking capacitors of scopes.

It's not so much the breaking down of the resistors themselves, but the flashing over of selector-switch contacts, wafers, etc. You might have a

large resistor in the circuit, enough to block the voltage, but mounted on a pair of switch contacts that are only about 50–75 thousandths of an inch apart! This is close enough to let an arc start, if you get a pulse of thousands of volts.

Every so often, we get letters: "I measured the boost voltage like you said. Now my meter don't read right no more!" You know where he measured it—on the damper *cathode!* Pulse voltages there can go to 15,000 volts or more! Fig. 1 shows what they look like. This pattern was made by holding the direct probe of a scope *near* the insulated damper cathode lead. The scope attenuator was set at about 100 volts p-p per inch! This pattern reads about 300 volts p-p!

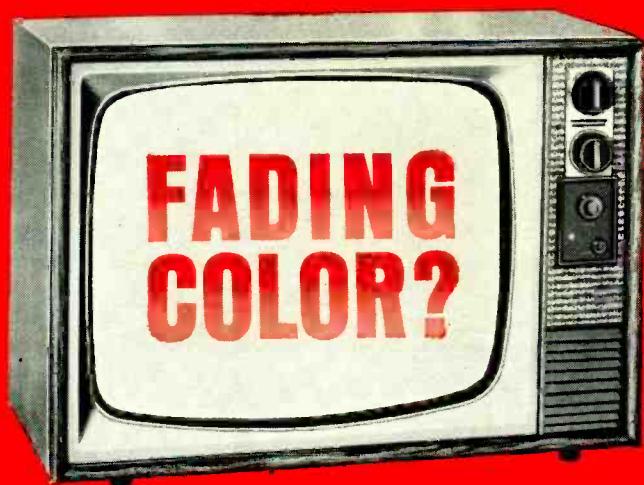

Perk it up with Perma-Power COLOR-BRITE

Perma-Power does for color TV sets what we've done for millions of black and white CRT's: adds an extra year of useful picture tube life.

When a color tube begins to fade, COLOR-BRITE instantly brings back the lost sharpness and detail. It provides increased filament voltage to boost the electron emission and return full contrast and color quality to the 3 gun color picture tube.

COLOR-BRITE is automatic . . . no switching or wiring. Just plug it in. Your delighted customers will brighten up as fast as their color sets!

Model C-501, for round color tubes.

List Price \$9.75

Model C-511, for rectangular color tubes.

List Price \$9.75



COLOR-BRITE is a Hue-Brite product from Perma-Power, famous in TV service for b & w Vu-Brites and Tu-Brites.

Perma-Power COMPANY
5740 N. TRIPP AVE., CHICAGO, ILLINOIS 60646
PHONE (312) 539-7171

Circle 16 on reader's service card

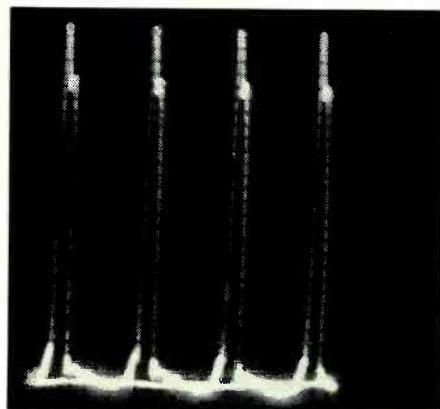


Fig. 1—Spikes this big, from holding probe near damper cathode! Think what would happen if you touched it!

Horizontal pulses like these are found on the damper cathode, on the plate of the horizontal output tube, and on the hv rectifier plate. Most of us know that, and stay away from them. But it's hard to remember that the innocent-looking plate of the vertical output tube can have pulses almost as high—high enough to cause meter damage too.

So stay away from these places. Actually, you don't have to take readings here anyway. You can get the same

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 154 West 14th Street, New York 10011.

The new Amphenol 860 Color Commander cuts alignment time in half!

Ever finish a convergence job to find the raster off center. Lose convergence when you recentered? Can't happen with the Amphenol Color Commander, battery-powered, solid-state color generator. A special, single-crossbar pattern consists of one horizontal and one vertical line, crossing just where the center of the raster should be. No need to guess when centering the raster with this new pattern.

See dots before your eyes when you want only one to start static convergence? The 860 gives you that single dot, right at center screen. You'll be switching back to this important dot during dynamic adjustment to make sure you haven't gone off the track.

Even the old patterns offer something new. Line spacing in the cross-hatch pattern is rigidly maintained for the 4:3 aspect ratio. You can rely on it for linearity, height, and width adjustments. The pattern gives you finely etched line width at normal brightness levels. What good is perfect convergence at reduced brightness if you lose it when the set's readjusted for normal viewing? This special crosshatch also eliminates receiver fine-tuning error. Among the 860's nine (most generators have only 5 or 6) are: multiple-dot, single vertical line, single horizontal line, vertical lines only, and horizontal lines only.

Finally, the Color Commander's unique color bar pattern (just three bars: R-Y, B-Y and -R-Y) simplify color adjustments. You can get a rapid, overall check of color circuits. Then adjust color demodulator phase or pre-set the hue control and check its operating range. In each step, you know precisely how the color bars should look and how they should change during adjustment.



A new timing circuit eliminates instability and loss-of-sync problems. Silicon transistors maintain built-in precision and stability indefinitely. RF output is on channel 3 or 4, switch selected. An attenuator simulates weak-signal conditions. It has gun killer circuit. Uses 9 penlight cells. Weighs 3½ lbs. in compact leatherette carrying case. \$149.95. Optional AC power supply, \$19.95.

AMPHENOL CRT COMMANDER, MODEL 855.


Solid-state. Checks all black-and-white or color CRT's with the same techniques used by tube manufacturers. Rejuvenates where others fail. Versatile 5-socket cable accommodates 7 different sockets. With CRT chart, \$89.95.

See the new Color Commander test instruments at your Amphenol distributor.

Amphenol
DISTRIBUTOR DIVISION
amphenol corporation
2875 S. 25th Ave., Broadview, Ill. 60155



Circle 17 on reader's service card

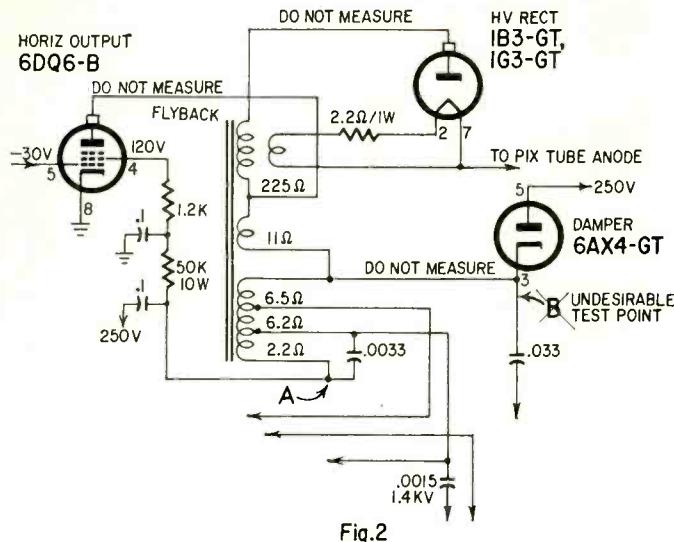

information in safer places. For example, read the boost voltage after it's been filtered a little. By the time it gets to the bottom terminal of the flyback, it's passed through some inductance, and there's a bypass capacitor, too; so the pulses are gone and we can check the voltage safely (Fig. 2).


This voltage measurement plus one resistance measurement (of the flyback primary) will tell you if there is plate

voltage on the horizontal output tube. Vertical output, too: read the voltage at the supply point on the primary winding, then check the dc resistance of the primary (Fig. 3).

Incidentally, while checking around these circuits with substitute electrolytic capacitors, stay off those high-pulse points. While the apparent dc voltage may be well within the rating of the capacitors, those pulses aren't. Someone

Measure at A, after spikes have been filtered out by inductance of part of flyback, and by bypass capacitor—not at B where they're still hot and heavy!

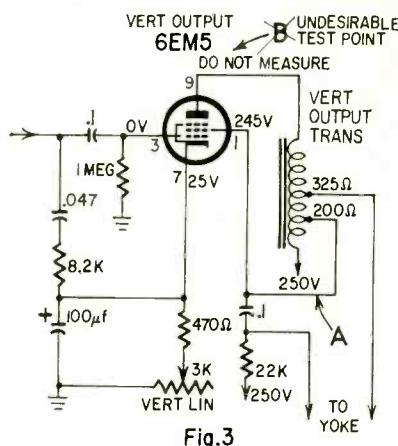borrowed my pet electrolytic "sub-box", and it hasn't been the same since. Three of the big capacitors were just slightly shorted! Upon threats of violence, the borrower admitted that he'd been trying to "find out if the set needed a boost



Same with vertical circuits: check voltage at A, where it's filtered, not at B.

filter!" And that he "just might" have touched the damper cathode with the sub-box lead. He said the set needed a new filter, all right. Now, so do I (in my sub-box)!

"Diamonds" in vertical blanking bar

In a Curtis-Mathes 425-21 color TV receiver, I can see a series of "diamonds" that get smaller from left to right, in the vertical blanking bar between pictures. These show on the screen. What are they, and should they be visible—G.B., Oakland, Calif.

These are "cueing" signals, transmitted on color TV network shows. On the TV station's monitor scopes, they tell the operator how to set up the controls for the best picture.


They shouldn't show on the TV screen. From your description of the trouble, it looks as if you are under-scanning just a little bit. Set up the vertical linearity and height until these "diamonds" or the blanking bar are not visible.

Vertical creep in G-E 21C1548

The picture creeps up from the bottom, after a short while, in a G-E 21C1548. Takes about a half hour, on the bench. This chassis uses a 6BL7 vertical oscillator/output tube. — J. S., Rome, N.Y.

First, change the tube; then change it again. I have found this necessary in quite a few sets like this. Some tubes are OK, but you may find one that still creeps, even though it checks good.

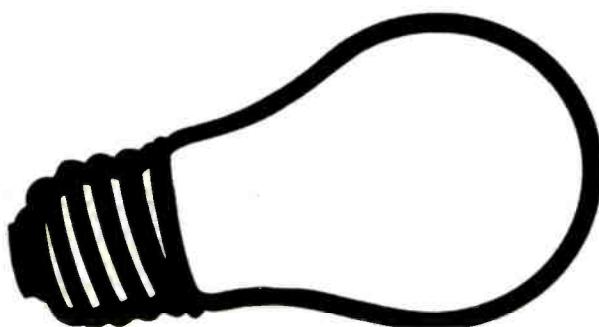Check the temperature-compensating resistor in the plate circuit. This is supposed to be 1 megohm cold and go to about 600,000 ohms hot. I've



Scott's new solid state amplifier kit is completely protected against transistor blow-out. An ingenious "Fail-Safe" circuit using an ordinary light bulb takes the load off expensive silicon transistors when you first plug in your LK-60 . . . so, if you've made a wiring error (almost impossible with this kit), no harm done! Other bright new ideas from Scott: preassembled, factory-tested modular circuit boards; full-color instruction book; amazingly low price: \$189.95

Write for complete spec sheet: H. H. Scott, Inc., 111 Powdermill Road, Maynard, Mass. Export: Scott International, Maynard, Mass. Cable HIFI. Prices slightly higher west of Rockies.


SCOTT

Circle 18 on reader's service card

FINCO

FOR UHF, VHF, FM RECEPTION


ALL-BAND UHF-VHF-FM ANTENNA

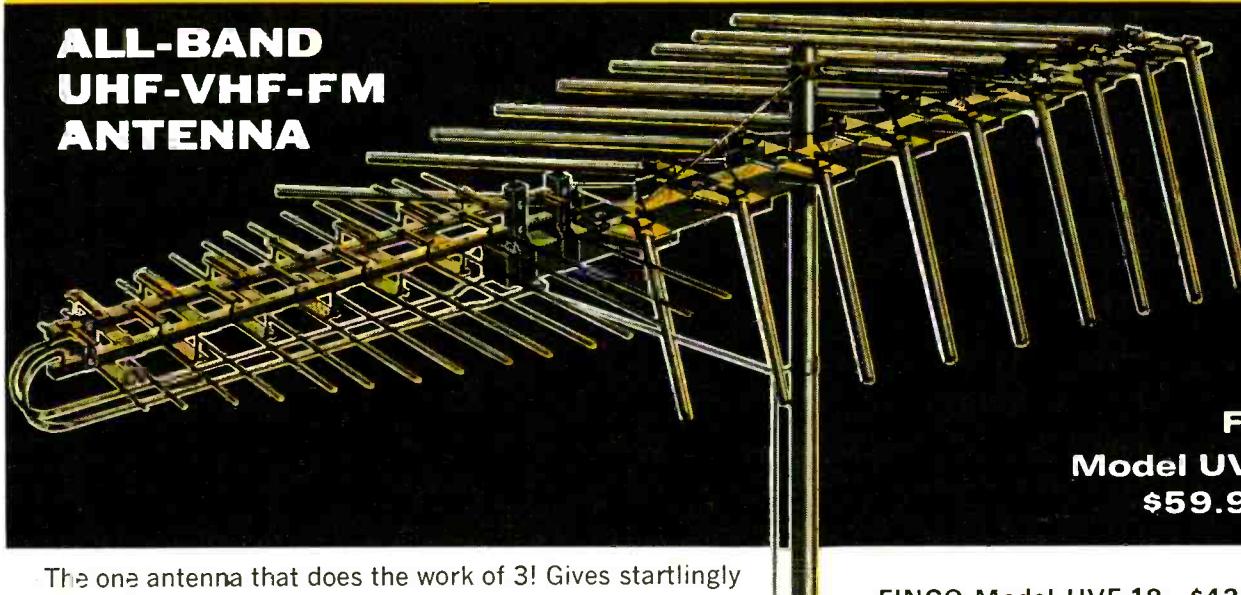**FINCO****Model UVF-24
\$59.95 list**

The one antenna that does the work of 3! Gives startlingly clear black and white pictures and beautiful color on both UHF and VHF television channels — plus the finest in stereophonic and monophonic sound reproduction.

FINCO Model UVF-18—\$42.50 list
FINCO Model UVF-16—\$30.50 list
FINCO Model UVF-10—\$18.50 list

SWEPT-ELEMENT VHF-FM ANTENNA

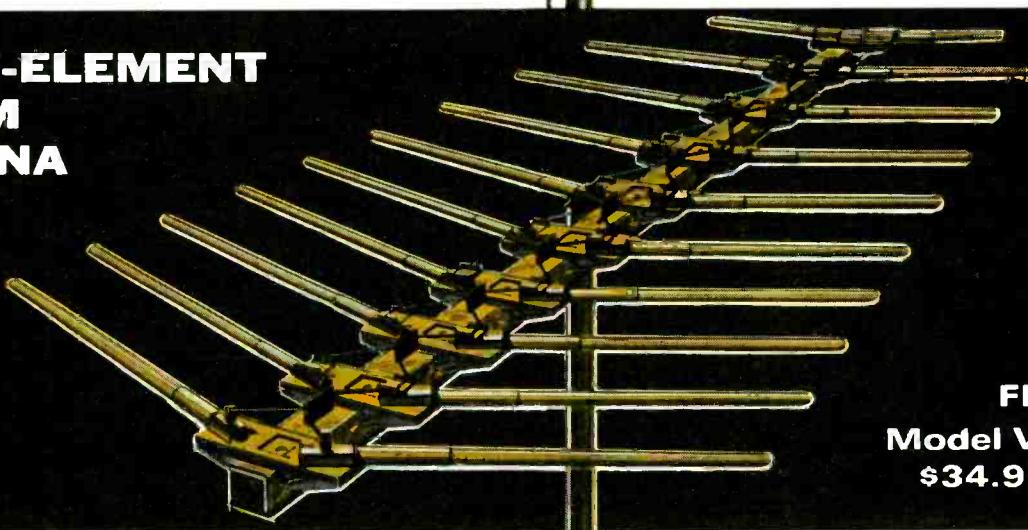**FINCO****Model VL-10
\$34.95 list**

FINCO's Color-Ve-Log challenges all competition! Its swept-element design assures the finest in brilliant color and sharply defined black and white television reception — as well as superb FM monaural and stereo quality.

FINCO Model VL-18—\$54.50 list
FINCO Model VL-15—\$46.95 list
FINCO Model VL-7—\$23.95 list
FINCO Model VL-5—\$16.95 list

Featuring FINCO's exclusive Gold Corodizing

FINCO COLOR-VE-LOG

Prices and specifications subject to change without notice

THE FINNEY COMPANY • 34 W. Interstate Street • Bedford, Ohio
Write for beautiful color brochures Number 20-322, and 20-307, Dept. RE

Circle 19 on reader's service card

SERVICE CLINIC continued

found some go too far and get down to about 300,000 or so hot; this, of course, drops the plate load impedance so far that the tube can't give the right amount of sweep amplitude.

Changing rf coils in Westinghouse radio

Can I change the rf coil in a Westinghouse Y2102? Now covers 5-8 mc, and I want to cover 20-30 mc.—D. K., Rochester, N. Y.

You should be able to, with the right coil. (Can I smell a CB rig coming up?) Try a Miller D-5495 rf coil; this is an unshielded type with an iron core for


tuning. Use your present trimmers to adjust the high-frequency end, and set the core at the low-frequency end. You'll probably have to repeat this several times to get the right adjustment.

You may be able to throw the oscillator up to cover this range. If not, there is an oscillator coil, D-5495-C, in the same series that will do it.

Poor sound in Tele-King K21 TV

I've got a Tele-King TV in my shop with very bad sound. All dc voltages, etc., in the sound i.f. seem to be OK, and the audio stages are clear.

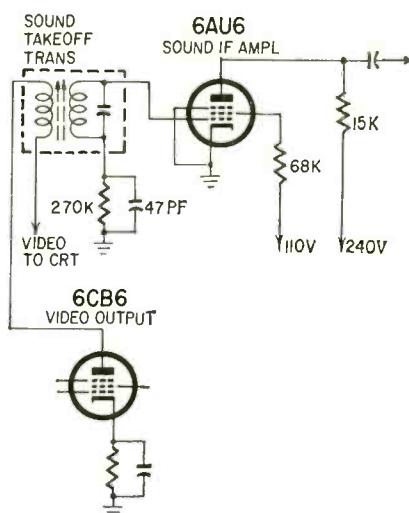Picture OK. 6BN6 detector OK. Where is it?—L.K., New York, N.Y.



Check the sound takeoff transformer. You may have a short in the secondary winding, or an open circuit. This wouldn't affect the video amplifier. Try feeding a 4.5-mc signal in at the video amplifier grid. If this comes through, the transformer is OK; if not, then check the transformer.

Audio feedback in "MC'S P.A."

I built the "MC's P.A." system (p. 26, Feb. 1964 issue). It works fine when I feed the output of a transistor radio into the mike input. If I hook a mike to it, it howls when the volume is advanced. What causes this?—B. L., Denver, Colo.

Plain old audio feedback! Sound from the speaker is getting into the microphone. The only way to get away from this is reduce the volume, reduce the "bounces" in the room, or get the speaker farther away from the mike. In some cases, using a very directional mike will help.


The "feedback" control in this system reduces the treble: treble (high-frequency) sounds bounce around more than lows; so, cutting down the treble sometimes helps cut feedback. A close-talking mike helps.

END

MYSTERY RADIATION FROM 42-MC-I.F. TV SETS

A Nebraska sheriff kept getting TV sound (from various channels) on his 39.9-mc public-service receiver, in spite of months of experiments with filters, traps, suppressors. Finally someone realized that dozens of TV sets were reradiating programs on that frequency. It could be happening in your town! Read what was done about it.

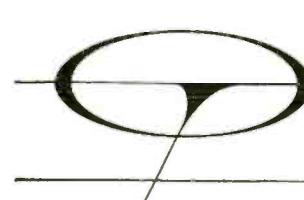COMING IN . . . OCTOBER
RADIO-ELECTRONICS



NOT JUST HORNS NOT JUST CONES OXFORD HAS THE FULL LINE

Model
OP-6



to Supply Commercial
Sound Needs...

Model
DVC-8J4



Model
OH-10




From the OP-6 & OP-8 paging and talkback horns and the OH-10 outdoor high fidelity system, which changed the outdoor speaker market in 1964, to the startling new DVC-8H4 and DVC-8J4 units with two separate voice coil winding, providing immediate access to the speaker, Oxford is the one source best qualified to supply all your speaker needs.

Our line also includes intercom speakers, public address speakers, all-weather cones, shallow ceramic magnet units, and the "Specialist Series." The Specialists (which includes models DVC-8H4 and DVC-8J4) are a series of popular 8-inch speakers that have been prepared for "instant use" by the commercial sound installer, with factory installed transformers and bulk packaging.

It makes good sense to use the line that is orientated toward the commercial sound installer by both design and marketing. For more information on the OXFORD line, write for complete catalog.


**OXFORD
TRANSDUCER
COMPANY**

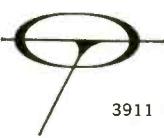


A Division of Oxford Electric Corporation

3911 South Michigan Avenue • Chicago, Illinois 60653

Circle 20 on reader's service card

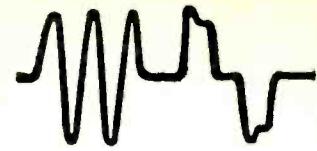

Tips on replacing circuit breakers

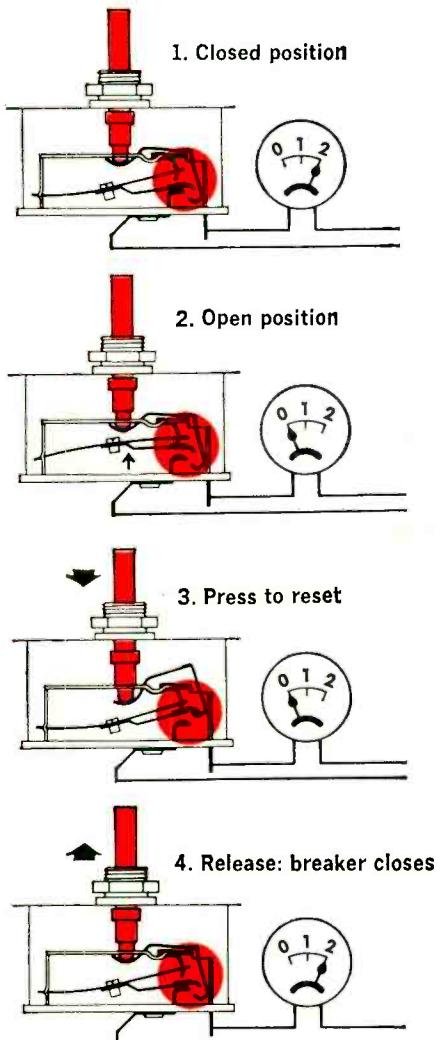

That little red "breaker reset" button that sticks out of the back of nearly every television chassis can be a time-saver or a trouble-maker, depending on what's wrong inside the set, and who's pushing the button. As you well know, when a transient fault has popped the breaker, you can get the set back in business just by pressing the reset. But if there has been a short-circuit failure and some uninformed tinkerer presses the button and *keeps* it pressed, there's a good chance that more power keeps flowing into the fault. Result: a minor trouble becomes a calamity.

This is why Underwriters' Laboratories require that breakers should be "cheat-proof"—that is, they should not allow current to pass when the reset button is held depressed. Some of the replacement breakers you'll find on the market *aren't* cheat-proof. We have one that *is*. It has features that you'll find valuable any time you need to install a new breaker, or when you're working on a breadboard circuit that needs over-current protection.

Take a look at how this breaker works, and you'll see what we mean.


At top (Picture 1) is the way the breaker mechanism looks when it's in the "on" position.

Along comes an overload (Picture 2). The bi-metal strip heats, snaps into the "break" position, opening the current carrying contacts.

Now you press the button to reset (Picture 3). As long as you hold the button down, the contacts at the right remain open.


Release the button and the contacts go back to closed (Picture 4). If the overload is still there, the breaker will open again. You can't keep it closed on a short circuit!

No wonder this particular breaker is used as original equipment on the majority of all television sets. They're made for Mallory by Mel-Rain Corp. to the same specifications as for original equipment, and they're available from a Mallory distributor near you. Off-the-shelf ratings go all the way from 0.5 to 7 amperes break current, and include all the values you'll need for service replacement or for industrial equipment maintenance. And as an extra convenience, you can get them with either a twist-tab or bushing mount. See your Mallory distributor, or write to Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., P. O. Box 1558, Indianapolis, Indiana 46206.

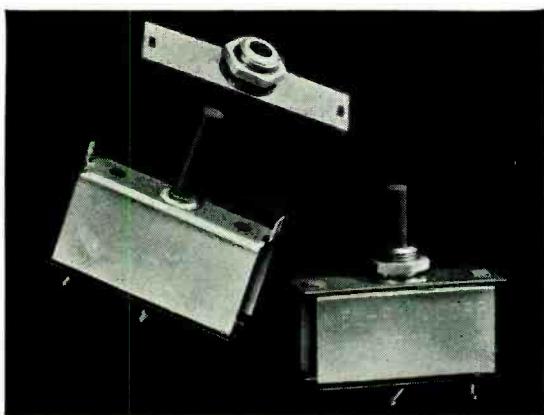

Circle 21 on reader's service card

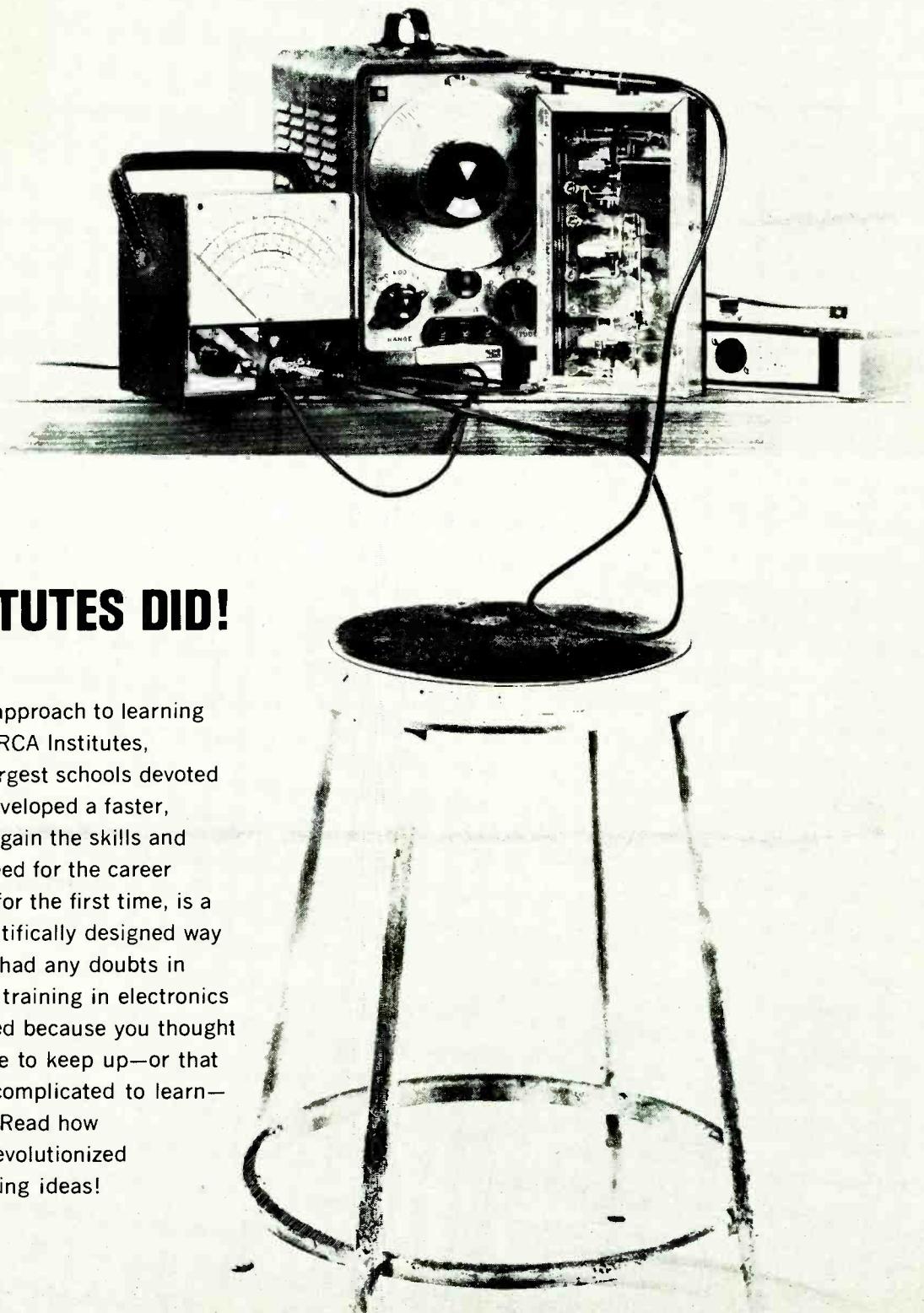SOMEONE SHOULD DEVELOP AN EASY WAY TO LEARN ELECTRONICS AT HOME



RCA INSTITUTES DID!

Here is a whole new approach to learning electronics at home! RCA Institutes, one of the nations' largest schools devoted to electronics, has developed a faster, easier way for you to gain the skills and the knowledge you need for the career of your choice. Here for the first time, is a student-proved, scientifically designed way to learn. If you have had any doubts in the past about home training in electronics—if you have hesitated because you thought you might not be able to keep up—or that electronics was too complicated to learn—here is your answer! Read how RCA Institutes has revolutionized its entire home training ideas!

NEW CAREER PROGRAMS

BEGIN WITH "AUTOTEXT" INSTRUCTION METHOD!

Start to learn the field of your choice immediately!

No previous training or experience in electronics needed!

With this new revolutionized method of home training you pick the career of your choice—and RCA Institutes trains you for it. RCA's Career Programs assure you that everything you learn will help you go directly to the field that you have chosen! No wasted time learning things you'll never use on the job! The Career Program you choose is especially designed to get you into that career in the fastest, easiest possible way!

And each Career Program starts with the amazing "AUTOTEXT" Programmed Instruction Method—the new, faster way to learn that's almost automatic! "AUTOTEXT" helps even those who have had trouble with conventional home training methods in the past. This is the "Space Age" way to learn everything you need to know with the least amount of time and effort.

CHOOSE A CAREER PROGRAM NOW
Your next stop may be the job of your choice. Each one of these RCA Institutes Career Programs is a complete unit. It contains the know-how you need to step into a profitable career. Here are the names of the programs and the kinds of jobs they train you for. Which one is for you?

Television Servicing. Prepares you for a career as a TV Technician/Serviceman; Master Antenna Systems Technician; TV Laboratory Technician; Educational TV Technician.

FCC License Preparation. For those who want to become TV Station Engineers, Communications Laboratory Technicians, or Field Engineers.

Automation Electronics. Gets you ready to be an Automation Electronics Technician; Manufacturer's Representative; Industrial Electronics Technician.

Automatic Controls. Prepares you to be an Automatic Controls Electronics Technician; Industrial Laboratory Technician; Maintenance Technician; Field Engineer.

Digital Techniques. For a career as a Digital Techniques Electronics Technician; Industrial Electronics Technician; Industrial Laboratory Technician.

Telecommunications. For a job as TV Station Engineer, Mobile Communications Technician, Marine Radio Technician.

Industrial Electronics. For jobs as Industrial Electronics Technicians; Field Engineers; Maintenance Technicians; Industrial Laboratory Technicians.

Nuclear Instrumentation. For those who want careers as Nuclear Instrumentation Electronics Technicians; Industrial Laboratory Technicians; Industrial Electronics Technicians.

Solid State Electronics. Become a specialist in the Semiconductor Field.

Electronics Drafting. Junior Draftsman, Junior Technical Illustrator; Parts Inspector; Design Draftsman Trainee Chartist.

SEPARATE COURSES

In addition, in order to meet specific needs, RCA Institutes offers a wide variety of separate courses which may be taken independently of the Career Programs, on all subjects from Electronics Fundamentals to Computer Programming. Complete information will be sent with your other materials.

LIBERAL TUITION PLAN

RCA offers you a unique Liberal Tuition Plan—your most economical way to learn. You pay for lessons only as you order them. No long term contracts. If you wish to stop your training for any reason, you may do so and not owe one cent until you resume the course.

VALUABLE EQUIPMENT

You receive valuable equipment to keep and use on the job—and you never have to take apart one piece to build another. **New—Programmed Electronics Breadboard.** You now will receive a scientifically programmed electronic bread-

board with your study material. This breadboard provides limitless experimentation with basic electrical and electronic circuits involving vacuum tubes and transistors and includes the construction of a working signal generator and superheterodyne AM Receiver.

Bonus From RCA—Multimeter and Oscilloscope Kits. At no additional cost, you will receive with every RCA Institutes Career Program the instruments and kit material you need to build a multimeter and oscilloscope. The inclusion of both these kits is an RCA extra.

CLASSROOM TRAINING ALSO AVAILABLE

RCA Institutes maintains one of the largest schools of its kind in New York City where classroom and laboratory training is available in day or evening sessions. You may be admitted without any previous technical training; preparatory courses are available if you haven't completed high school. Coeducational classes start four times a year.

FREE PLACEMENT SERVICE

In recent years, 9 out of 10 Resident School students who used the Free Placement Service had their jobs waiting for them when they graduated. And many of these jobs were with top companies in the field—such as IBM, Bell Telephone Labs, General Electric, RCA, and radio and TV stations and other communications systems throughout the world.

**SEND ATTACHED POSTAGE PAID CARD
FOR COMPLETE INFORMATION, NO OBLIGATION.
NO SALESMAN WILL CALL.
FREE BOOK INCLUDED. CHECK HOME
STUDY OR CLASSROOM TRAINING.**

RCA INSTITUTES, Inc., Dept. RE-95
A Service of Radio Corporation of America
350 West 4th St., New York, N.Y. 10014



The Most Trusted Name in Electronics

Circle 22 on reader's service card

careers for technicians at IBM

To technicians who seek important roles in today's technology, IBM offers careers in the world of computers. Modern computer systems and new solid state technologies have created rewarding jobs for technicians in Research, Development, Manufacturing, and Systems Test. IBM is an Equal Opportunity Employer.

Owego, New York

Chemical Technicians: Experience in chemical technology, engineering physics or in any of the following: electrochemistry, lamination, adhesives, electroplating, etching, oxide coating, photo-resist, evaporation techniques.

Electromechanical Technicians: Experience in assembly and maintenance of automatic production equipment. A thorough understanding of mechanical and electrical technologies is essential.

Electronic Technicians: Experience in maintenance, calibration and repair of complex electronic test equipment, and development of high-speed circuitry.

Welder: Mag-lithium experience with toolmaking capability.

Qualifications: A.A.S. degree or its equivalent in education or experience.

Please write, outlining your education and experience, to:

D. J. Carlson, Dept. 649J
IBM Corporation
Space Guidance Center
Owego, New York 13827

IBM

Fishkill, New York

Electromechanical Technicians: Experienced in assembly and maintenance of automated production equipment. A thorough understanding of mechanical and electrical technologies is essential.

Designers: Electromechanical packaging mechanism design of automated production equipment.

Electronic Technicians: Experienced in maintenance, calibration and repair of complex electronic test equipment, and development of high-speed circuitry.

Semiconductor Technicians: Experienced in semiconductor process development and manufacturing.

Qualifications: A.A.S. degree or its equivalent in education or experience.

Please write, outlining your education and experience, to:

T. R. Edmonds, Dept. 649J
IBM Corporation
East Fishkill Facility
Route 52
Hopewell Junction, New York 12533

IBM

Endicott, New York

Computer Systems Test: To give final systems tests to newly manufactured computers. A.A.S. degree or equivalent in Electrical Technology, with experience and/or courses in mechanical technology and devices. Should understand solid state switching circuits and computer technology.

Chemical Technicians: A.A.S. degree in Chemical Technology, with experience in any of the following: electrochemistry, lamination, adhesives, electroplating, etching, oxide coatings, photo-resist.

Toolmakers: Must have completed formalized tool and model maker apprentice program; 2 years' experience working to close tolerances on dies, fixtures, gauges, and special machine tools.

This manufacturing and manufacturing research facility is in Endicott, New York, in the Triple-Cities community of the Finger Lakes region.

Please write, outlining your education and experience, to:

J. C. Lloyd, Dept. 649J
IBM Corporation
1701 North Street
Endicott, New York 13760

IBM

Other Technician Assignments

IBM offers a variety of career assignments for technicians in Electronics, Chemistry, Physics, Mechanical Technology, Electrical and Mechanical Design, Systems Test and Customer Engineering. A degree from a two-year technical school, or the equivalent in military or other experience, is required.

In addition to the specific assignments listed here, there are also openings for technicians in:
Huntsville, Alabama
San Jose, California
Cape Kennedy, Florida
Rochester, Minnesota
Kingston, Poughkeepsie, Yorktown Heights, N. Y.
Burlington, Vermont

To inquire about these opportunities, please write, outlining your education and experience, to:

C. Mandelblit, Dept. 649J
IBM Corporate Headquarters
Armonk, New York 10504

IBM

End of the Service Technician?

... He is a long way from being finished...

FRED SHUNAMAN, Managing Editor

The twilight of the service technician is fast approaching, according to "well informed sources." What are the causes? The increased reliability of transistor circuits is said to be one. The expected takeover of integrated circuitry—practically impossible to service—is another. In spite of the tremendous expansion—almost explosion—of electronics in industry and domestic use, the service man is seen as doomed.

No one has stopped to ask who is going to discover and replace the defective integrated circuit modules, nor has anyone pointed out that the supposed reliability of transistors is by no means absolute, and if there is less servicing of transistor equipment it may be because it is cheaper to throw away a \$9 radio than to try to repair it. This will not be the case with transistor TV's, nor will it be the case with solid-state industrial equipment.

While talking about the spread of automation, which usually means electronic control of industrial processes, the "well informed source" has also overlooked the fact that controls need maintenance, and that in many factories the electronic maintenance technician will have a full-time job.

Nor has anyone, apparently, realized that the spread of electronics into household appliances will mean that repair of kitchen devices may become a job for the electronic technician. Already it has been suggested that electrical watches are more likely to get understanding service in the electronic service shop than at the watchmaker's.

Such a change of repairmen will be a good thing for the homeowner and the housewife. The electronic repair man has been derided by many of his critics, accused of lack of technical knowledge and held up to scorn as a screwdriver artist. But even a good screwdriver mechanic is often sought after in some other types of household service.

Not long ago I needed a new fuel pump in my oil burner. It was installed by a presumably competent repairman, an employee of the company that installed the burner and which does not service any but its own fuel customers. I asked him timidly about the supposed pressure of 100 pounds at which the oil was to be injected into the furnace. He snarled: "The fuel pump is set up at the factory—you can't touch it."

A few weeks later I noticed a large black cone of carbon had built up at one side of the nozzle, and had to adjust the needle valve myself for best performance. This reminded me that of all the three repairmen who had serviced my

furnace, none had any instruments whatever. Yet any oil-burner guide will tell you not only about fuel pressure but of the partial vacuum supposed to exist—and be measured—in the combustion chamber, not to mention stack temperatures.

This indifference is not peculiar to oil-burner men. My gas drier goes out periodically at certain periods of the day, and at some times of the year will work only between midnight and 8 o'clock in the morning. These working periods, interestingly enough, coincide with periods of low gas use and of an accumulation of gas in the company's gasometers—in other words, of highest gas pressure. Obviously, the pressure valve on the drier is not properly adjusted.


I will not touch adjustments on illuminating-gas equipment—it can be too dangerous. But, when I explain my problem to the various service technicians, they simply shake their heads and go about replacing heating coils that supposedly ignite the gas which is not supplied to them. Apparently not one man so far—and we have had at least one from the company that supplied the washing machine and one from the gas company—has any notion of what the pressure control valve is about, nor has any of them any instrument for measuring gas pressure or any other quantity in their work.

The coming of the electronic service technician—who at least tries to understand what he is doing—will be a boon to people who have been up against that kind of service. Possibly one reason why the television technician is berated so is that he is expected to turn out good work, whereas with the automobile mechanic or household-appliance technician, we simply hope for the best and trust to luck. Those people will not be able to service electronic equipment, whether it is in automobile ignition systems or washing-machine timers.

The electronics technician may find himself with a different kind of work, but as long as electronics continues to expand at its present rate, he is extremely unlikely to be out of a job. As he developed from a radio to a TV technician and got a foothold in industrial electronics, so will he continue to go with electronics into the other fields it will conquer in the future. That expansion will far more than make up for the results of increased reliability, both in the equipment he is now servicing and in the newer equipment he is already beginning to be called on to service, and which may well make up the bulk of his work in the future.



Orr AutoMate

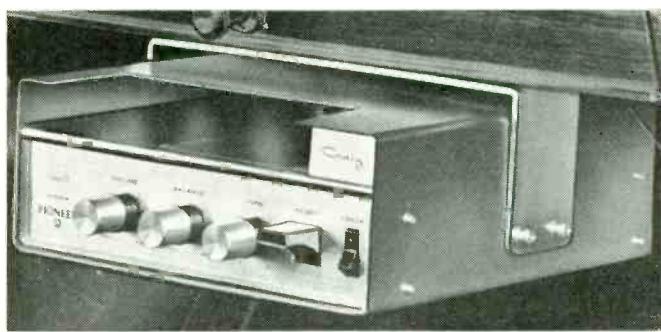

Craig Pioneer

TAPE PLAYERS FOR YOUR CAR

Noise-free, fade-free stereo (or mono) while you drive. See chart on page 35.

By FRED BLECHMAN

THE LATEST ELECTRONIC WIZARDRY TO hit the country by storm is tape players for your car. Most of them feature four-track stereo playback through door-mounted speakers. Traveling along, fixed between the speakers, you'll find driving sheer pleasure.

The stereo separation is especially good since the speakers are mounted on each side of you. The acoustic characteristics of the car add to the stereo effect with a "full" sound that is startling to hear. There are no commercials, no FM reflection, fading or multipath distortion. Neither are you limited to being within a certain distance from a broadcasting station. Also, the static and incessant chatter on AM are completely eliminated.

Most of the designs use four-track stereo tapes playing two $\frac{1}{4}$ -track stereo programs endlessly in prerecorded cartridges that need neither rewinding nor turning over.

These tape players are unique in several ways besides their low cost and fine performance. A typical unit is enclosed in an attractive 4-inch high, 10-inch wide, 9-inch deep black case (bright metallic finish usually optional at higher price), and is installed under the dashboard, although above-the-dashboard, glove-compartment and between-the-seat installations are not uncommon. Installation, including four door-mounted 5-inch speakers, takes only an hour or two and is often included in the quoted price.

Except for the AutoMate, all units contain built-in transistor hi-fi amplifiers, using either 10 or 12 transistors and providing from 2 to 5 watts output per channel; this is more than enough

volume even at high speed with the windows open. Quarter-track playback heads are used, except in AutoMate, which is a two-track unit.

On most units the head is mechanically coupled to a lever that positions it for the desired track pair. This eliminates the bother of turning over the tape cartridge to change tracks. On some units, a switch is used for track selection and the head is stationary.

Except for the Riverside unit, all tracks run in the same direction, which makes these tapes incompatible with Bell or RCA cartridge machines. So don't plan on recording your own tapes. Most manufacturers have an adequate library of prerecorded cartridges at reasonable prices, and the tapes are interchangeable in most cases.

The Conley Electronics Fidelipac automatic tape cartridge, used on all the units described except as indicated in the text and chart, uses an endless-loop principle. Specially lubricated 1-mil Mylar tape is pulled from the center


of the reel, drawn across the playback head and fed back to the outside of the wound tape. Therefore, no rewinding is necessary, and the tape plays over and over without attention. The entire cartridge is constructed of plastic (don't leave it in the sun or it'll melt!). The tape is enclosed under a transparent cover, protecting it from dust, tearing, marring and other mishandling. Pinch-roller engagement holds the cartridge in position without jarring, vibration or flutter from road bumps.

The tape speed is $3\frac{3}{4}$ inches per second, and the cartridges come in three sizes, providing from $\frac{1}{2}$ to over $2\frac{1}{2}$ hours of stereo per cartridge.

Claiming to be the originator and developer of this new listening pleasure is Earl "Mad-Man" Muntz. No longer affiliated with Muntz TV, he began developing the Muntz Music System in 1958, producing the first units and prerecorded cartridges in 1962. The name was later changed to Muntz Autostereo. Desiring to produce units for the popular market (they were priced for the Cadillac crowd at that time), Muntz set about re-engineering and improving the tape player for mass production, and succeeded in reducing the price drastically. Other manufacturers have entered the field, and competition has tended to lower all prices.

The proper dubbing of the tapes, according to Earl Muntz, was the biggest headache he had in developing this system, and he now claims to be the first to record four-track stereo in a Fidelipac tape cartridge.

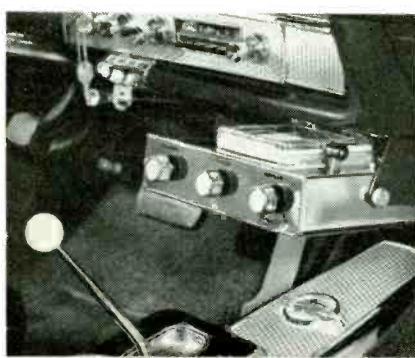Prerecorded tape prices vary with the manufacturer. Muntz tapes, for example, sell for a price determined by



Muntz Stereo-Pak

UNIT NAME & SOURCE	POWER OUTPUT (WATTS PER CHANNEL)	NUMBER OF HEADS	FREQUENCY RESPONSE (CPS)	DISTORTION	FLUTTER & WOW (% RMS)	SIGNAL-TO-NOISE RATIO (db)	TEMP. RANGE (EXCEPT CARTRIDGE) (° F.)	POWER REQUIRED	POSITIVE GROUND UNIT AVAIL?	PRICE			
										UNIT	BLACK	METALLIC	
AUDIO SPECTRUM	(1) (10)	2	70-9,000 ±3 db	2%	0.2	NF	-5 to +150	10-12V 1A	YES	\$69.50	(1)	(7)	
Audio Spectrum 10 Columbus Circle New York, N.Y. 10019													
AUTOMATE P-600RF	(1) (10)	1	50-10,000	2% @ 1 kc	0.25	35	-10 to +170	9-15V 350 MA (9)	YES \$7.50 Extra	\$89.95 (3)	—	(1) \$5.00	
J. Herbert Orr Enterprises, Inc. 309 Williamson Ave. Opelika, Ala.													
AUTOMATIC RADIO	5	(11)	100-15,000	NF	0.3	50	+15 to +165	10.5 to 14.4 1.7A	YES	—	\$125.00	Incl.	
Automatic Radio 2 Main St. Melrose, Mass.													
AUTOPHONIC	3	2	40-10,000 ±3 db	2% @ 1 kc	0.2	35	NF	10.7-14.5V 1 A	NF	—	\$119.95	\$17.00 (4)	\$15.00 (4)
Quality Audionics, Inc. 39 West 55 St. New York, N.Y. 10019													
AUTO-SONIC ST-400*	3	1	40-10,000 ±3 db	2% @ 1 kc	0.2	35	+20 to +130	9-16V 500 MA	YES	—	\$129.95 (5)	Incl. (6)	(7)
SIB, Inc. (Mfd. by Martel) 2356 So. Cotner Ave. Los Angeles, Calif. 90064													
AUTOSTEREO	4	1	50-12,000 ±2 db	1.2% @ 10 kc	0.2	46-52	-20 to +156	9-20V Less than 1 amp (9)	YES \$5.00 Extra	\$139.50	\$159.50	Incl.	\$15.00
Autostereo, Inc. 14617 Keswick St. Van Nuys, Calif.													
CRAIG C502	3	2	100-6,000 ±3 db	3%	0.3	40	0 to +120	12 V 1 A	NO	\$119.00	—	—	(7)
Craig Panorama, Inc. 3412 So. La Cienega Blvd. Los Angeles, Calif. 90016													
FORD	3	1	50-8,000	NF	0.3	40	NF	12 V 2 A	NO	NF	NF	NF	NF
Ford Motor Co. PO Box 608 Dearborn, Mich.													
LEAR													
Lear Jet Corp. Wichita, Kan.													
METRA	4	1	60-10,000 ±3 db	2%	0.3	50	NF	11-14.5V 1 A	YES	\$149.95 (Grey)	\$169.95	(4) (8)	(7)
Metra Electronics Corp. 660 McDonald Ave. Brooklyn, N.Y. 11218 (Also: Lafayette Radio, Cat. 650, P.381)													
MUNTZ STEREO-PAK	5	1	50-10,000	1.2% @ 10 kc	0.2	50	+20 to +140	9.5-18V 500 ma	YES	\$99.50	\$119.50	Incl.	Incl.
Muntz Stereo-Pak 16032 Armita St. Van Nuys, Calif.										\$79.50	—	\$10	\$10
OLSON													
Olson Electronics, Inc. 260 S. Forge St. Akron, Ohio 44308													
POR TAPE													
Telepro Industries, Inc. Cherry Hill, N.J. 08034	(1) (10)	1	80-5,000 ±2 db	2%	0.4	NF	+20 to +140	12 V 300 ma	NO	\$69.95 (Sim. Leather)	—	(1)	(7)
RIVERSIDE													
Montgomery Ward Oakland, Calif. 94616 (1965 Spring/Summer Catalog, P.631)													
TRANS WORLD	5	1	40-10,000	2% @ 1 kc	0.25	40	+25 to +130	9.5-16 V 250 ma	YES	\$119.50		Incl.	
Transworld, Inc. PO Box 482 Metairie, La.													
VIKING AUTO-TAPE 500	2	1	60-10,000 ±3 db	2%	0.3	50	NF	11-14.5 V 1 A	NF	\$149.35	\$169.95	Incl.	Incl.
Viking of Minneapolis, Inc. 9600 Aldrich Ave. South, Minneapolis, Minn. 55420													
WHITNEY	NF	NF											
J. C. Whitney & Co. 1917 Archer Ave. Chicago, Ill. 60616													
APPEARS TO BE IDENTICAL TO AUTOSTEREO UNIT IN LISTED FEATURES, ILLUSTRATION & SPECIFICATIONS. DO-IT-YOURSELF INSTAL.										\$99.50	\$114.50	Incl.	(7)

NOTES: EXCEPT AS NOTED, all units are 4-track stereo, capstan drive, run at 3 1/4 IPS, playback only, and use interchangeable Fidelipac endless-loop tape cartridges. NF = INFORMATION NOT FURNISHED BY MANUFACTURER. All data in table are manufacturers' specs.

* WEST COAST DISTRIBUTION ONLY

- (1) Uses car AM radio for amplifier & speaker.
- (2) Consists of preamp & rf oscillator only.
- (3) Unit price includes 1-hr recorded tape.
- (4) Can be connected through special switch to use car radio speakers.

- (5) Unit price includes 1/2-hr. recorded tape.
- (6) Choice of either four custom 5-inch round speakers & grilles or two do-it-yourself speakers in chrome enclosures.

- (7) Installation is do-it-yourself.
- (8) Insta-Mount speakers available separately.
- (9) Electronically regulated speed.
- (10) Monoaural.
- (11) Uses 8-track Lear cartridge.

tape length and recording artist, running from as low as \$3.98 for 30 minutes to \$24.98 for 2½ hours.

[Muntz cartridges and players will be sold by Montgomery Ward under its Riverside label this fall.—Editor]

All the units described are capstan drive and use a tape speed of 3½ inches per second, and are playback units only. Most are stereo, and most use Fidelipac cartridges except as noted in the chart. Two use the new 8-track Lear cartridges. They are all 12-volt units, so they can be used on 6-volt cars only with an additional battery in series with the car battery. All are designed for a negative-ground system, but some offer positive-ground units (usually at extra cost). In most units the motor is governor-controlled to maintain a constant speed from about 9 to 16 volts.

Total power requirements vary from one brand to another, mostly due to the motors used, but the typical unit draws only ½ to 1 ampere—not much more than a 7-watt night light! Service warranties vary from 90 days to one year, and one manufacturer (Muntz) boasts "never a charge for service."


Since some of the features of individual brands are not self-explanatory in the chart, we'll look at each unit in a little more detail.

The Orr AutoMate is one of a small class of unusual units. It is a two-track monaural unit, and uses special Cousino endless-loop cartridges available from Orr Enterprises. A U-Tape-It Kit K-6 can be used with most reel-to-reel recorders to make your own tapes for the AutoMate. The AutoMate output is a modulated 800–1000-kc rf signal, tunable on the AM broadcast band. Installation consists simply of mounting the unit, connecting it to the battery, plugging the car antenna into the AutoMate and plugging the output of the AutoMate into the automobile radio antenna jack. [The Telepro Porta-Tape uses a similar arrangement.—Ed.]


A simple switch on the AutoMate disconnects the vehicle's antenna when the tape is being played, or reconnects the car antenna to the radio when the player is turned off. Of course, the sound comes through the car radio speakers, so adding a rear-speaker reverberation unit can provide a stereo-like sound.

The Autophonic unit is fairly typical of the stereo Fidelipac-cartridge units, but is the only one listed that has two heads. A special switch is available that allows you to use the car's existing front and rear speakers for the stereo separation, thus saving the cost and installation of Insta-Mount door speakers, which are also available. This unit is available only in a bright metallic finish, and has a pilot light.

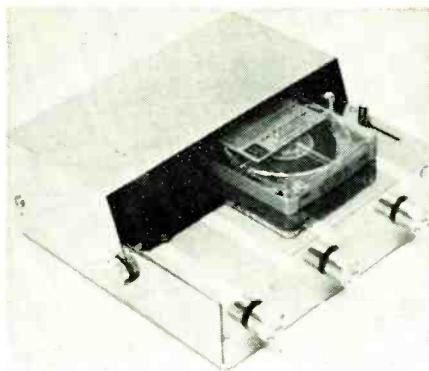The Audio Spectrum player is cartridge-activated (no lever to push) and



Autostereo MC-5

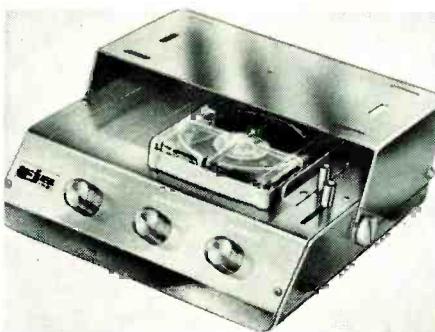

Auto-Sonic ST-400

has a solenoid-actuated mechanism that disengages the pinch roller and cartridge when the car's ignition switch is turned off, to prevent flat spots.

The Auto-Sonic unit is somewhat different in style from the others and is also available only in the bright metallic finish. This unit features optional do-it-yourself speakers in chrome enclosures that don't require large mounting holes.

Autostereo is one of the pioneers in this field and one of the few made with American parts and labor. The chassis is hand-wired (printed circuits are used on other units). The 5-inch speakers are manufactured by Oaktron, and are not subject to rupturing when the volume is turned all the way up—a potential problem with lower quality speakers. A special adapter ring allows for simple speaker installation. The amplifier uses driver transformers with a special core material for flat response.

Particular attention has been paid to motor life in the design of these units, with speed electronically regulated, and regulator contact current reduced by using a principle similar to that used in transistor ignition systems. The result is motor life exceeding 1,000 hours, speed regulation from 9 to 20 volts, and operation down to -20°F.

Autostereo also makes a special fungus- and moisture-proofed unit with waterproof speakers for boats.

The Metra units, available in either baked gray enamel finish or high-luster stainless steel, appear to be identical to the Viking units, which were probably the first on the market. Metra Electronics features the Insta-Mount speakers

for do-it-yourself installation. Metra units and Insta-Mount speakers are also available from one of the country's largest mail-order houses, Lafayette Radio Electronics Corp., which also offers a switch and wiring harness allowing use of the existing car radio speakers.

The most highly promoted unit is the Muntz Stereo-Pak, which is also the least expensive. However, the low price seems to be a result of high production rather than corner-cutting. Also, Muntz will install your unit in another car, complete with four new speakers, for only \$20, so there's no big loss when changing cars.

The Riverside, marketed by Montgomery Ward, uses the common RCA-Bell type of cartridge which must be turned over when the selection is completed. With this system you can record your own tapes if you have an RCA or Bell cartridge tape recorder. The Riverside unit has only recently come out, and information is sketchy.

Viking appears to be the first company to have offered automotive tape players for sale (the history of the development of these machines is clouded by conflicting claims), but it appears to have lost ground to the newer, more aggressively promoted units, and detailed information on Viking units has not been available to me. (Two letters asking for specific information were never acknowledged, let alone answered!)

J. C. Whitney & Co., a large auto parts and accessories mail-order house, is selling a unit that in appearance, description and listed specifications is identical to the Autostereo unit. Even the tape series designations are the same as Autostereo. This is sold strictly for do-it-yourself installation, so the price is considerably lower than the Autostereo price.

The market potential for these units is so vast that you can be sure you'll be running into one of these units soon if you haven't already. Many listeners comment that these car units sound better than anything they have at home, and they must be heard to be appreciated.

And If That Isn't Enough . . .

An auto adapter for the Norelco Carry-Corder portable tape recorder is about to make its entry. The Adapter will sell for about \$30; the recorder costs about \$120. The adapter consists of a Cyclocac tray in a metal frame that mounts under the dashboard. A 1-mc amplitude-modulated oscillator takes its power from the recorder (not from the car) and the signal is picked up on the car's AM radio, tuned to about 1000 kc. Norelco expects to make available recordings from Mercury, Deutsche Grammophon and Philips masters, all in its nonstandard two-reel miniature cartridges.

END

Easy Alignment with the Semi-Sweeper


By DONALD L. STONER

Three-Semiconductor Sweep
generator covers range from
below 100 kc to 60 mc

THE SEMI-SWEEPER ISN'T A PART-TIME janitor. It is an all-solid-state sweep generator that will save considerable alignment time compared to the few hours required to construct it. You can use it to align all radio and TV i.f.'s, filters, plot response curves, check bandwidth. The unit has been stripped of all superfluous controls and is designed to operate between 100 kc and 60 mc without a complicated bandswitching mechanism (lower frequencies are practical). It can be used on higher frequencies by utilizing harmonics or by modifying the circuit slightly.

Basically the Semi-Sweeper consists of a sawtooth generator, a variable-capacitance diode and a transistor oscillator. The rf output of the generator is a constantly sweeping frequency which is fed into the input of a receiver or i.f. strip. A scope is connected to the receiver detector, and dc changes cause the spot to deflect. Thus the amplitude waveform on the scope is a direct indica-

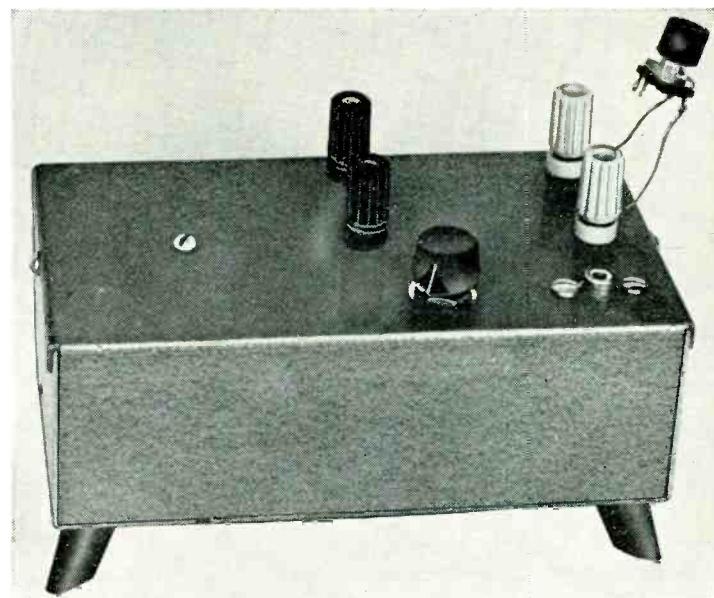Here, *Semi-Sweeper* uses 455-ke transistor i.f. transformer as rf oscillator inductance. Many other coils are suitable, depending on center frequency you want.



cation of signal strength and therefore of the amplifier gain. By using the saw-tooth output of the Semi-Sweeper as a time base, the pattern displayed is a near-perfect replica of the receiver alignment curve. Each time a tuned circuit is adjusted, the effect will be in-

stantly apparent on the screen. Thus broad-band alignment and tuning of discriminators or crystal filters is made infinitely easier.

Circuitry

The sawtooth waveform is generated by a unijunction transistor. The sawtooth drives a variable-capacitance diode, another interesting semiconductor. Reversed-biased, the diode has a capacitance between the two terminals. As the reverse voltage is decreased, the junction capacitance increases. The Pacific Semiconductors V-56 Varicap, used in the Semi-Sweeper, has a junction capacitance of 56 pf at -4 volts. The sawtooth applied to the V-56 causes the capacitance to vary in proportion to the amplitude of the sawtooth. The sawtooth waveform is also brought out to terminals on the Semi-Sweeper to provide a time base for the oscilloscope.

Fig. 1 is the schematic. Power is supplied by two 9-volt transistor batteries. R2 and R3 determine the charge time of C2. R3 adjusts sweep frequency between 5 and 30 cycles per second. Capacitor C1 is an rf bypass. The sawtooth appears across J1 and J2, which connect to the external horizontal input on the oscilloscope. The appropriate

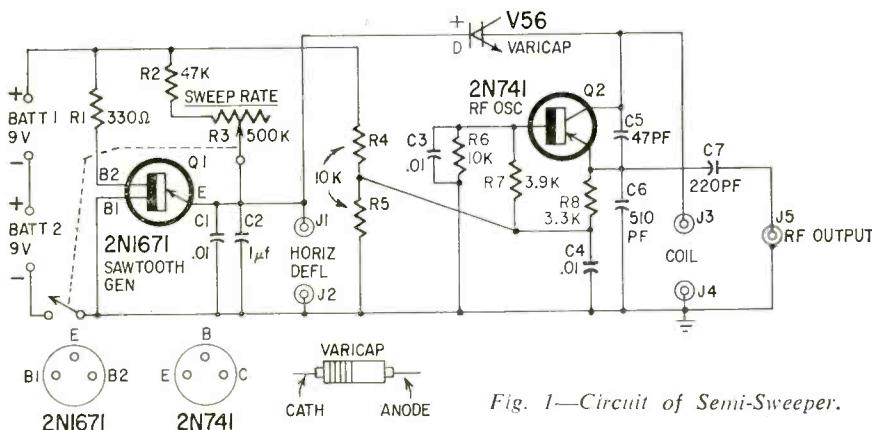


Fig. 1—Circuit of Semi-Sweeper.

BATT 1, BATT 2—9-volt batteries (RCA WS-322 or equivalent)
 C1, C3, C4—0.01 μ f, disc ceramic
 C2— μ f, 100 vdc
 C5—47 pf, silver mica
 C6—510 pf, silver mica
 C7—220 pf, silver mica
 D—V-56 Varicap (Pacific Semiconductor)
 J1, J2, J3, J4—binding posts (E. F. Johnson Co. 111-series or equivalent)
 J5—RCA style phono jack
 Q1—2N1671 (G-E)
 Q2—2N741 (Motorola, Sylvania)

RT—330 ohms
 R2—47,000 ohms
 R3—500,000-ohm pot, with switch (Centralab B-60 or equivalent)
 R4, R5, R6—10,000 ohms
 R7—3,900 ohms
 R8—3,300 ohms
 All resistors $\frac{1}{2}$ watt, 10%
 Cabinet (LMB 138 or equivalent), vector board.
 To aid experimenters in duplicating this project, a circuit board is available from the W. H. Paulin Co., Box 122, Upland, Calif. for \$1.00 postage paid

ate inductance for the desired sweep frequency is connected across terminals J3 and J4 to complete the oscillator circuit.


The oscillator consists of a Motorola 2N741 (Q2) in a Colpitts configuration. A capacitive voltage divider (C5 and C6) is connected across the external inductance, and feedback occurs between collector and emitter through this network. The variable-capacitance diode is connected in parallel with the tuned circuit and causes its frequency to sweep back and forth at a rate determined by the sawtooth frequency. Rf output is coupled from the low-impedance emitter of Q2 to jack J5 through a 220-pf capacitor. Oscillator B-plus comes from a voltage divider connected across the battery (R4 and R5). The oscillator is operated at a reduced voltage to prevent the rf cycles from exceeding the 2N741's collector breakdown rating.

Construction

The Semi-Sweeper is constructed in an LMB chassis box 2 x 3½ x 6 inches. The circuitry is mounted on a piece of Vector board 2 x 3 inches. Vector pins are used to make connections and junctions as required. The board is supported on binding posts J1-J4. The method of mounting the batteries is crude but seems effective: a bolt through the front panel pulls down on an aluminum plate which bridges the two batteries. A phono connector is used for the rf output jack.

Using the Semi-Sweeper

The method of connecting the Semi-Sweeper is shown in the block diagram (Fig. 2). The scope is usually connected across the detector load, as shown. The output of the generator is coupled to the input of the circuit being aligned through a shielded cable and potentiometer. The length of the cable or the impedance it feeds is not critical but simply changes the tuning slightly. The only precaution in using the sweep generator is to avoid overloading the

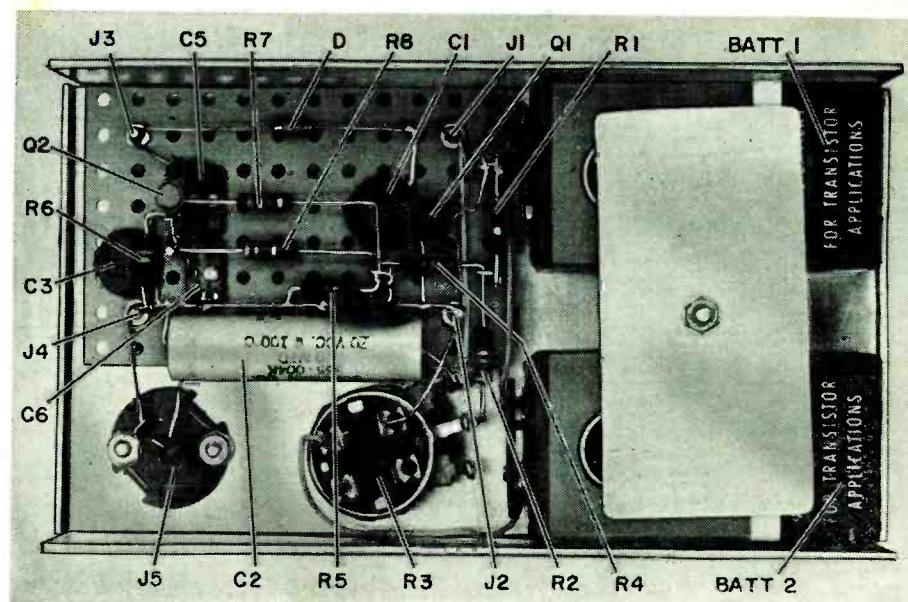

Simple wiring takes little space and looks neat on perforated board. Circuit lends itself nicely to printed-circuit design. A circuit board is available—see the parts list.

circuit under test. Overload is usually evidenced by a perfectly flat top on the alignment curve. It is seldom possible to get such an ideal curve, so you'll recognize it as overload. Always keep scope

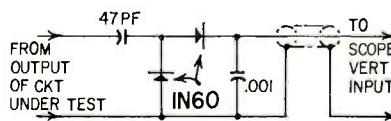


Fig. 3—Rf "probe" (demodulator network) you can make for amplifier without detector. Regular rf probe designed for vvtm or scope will work fine.

gain as high and generator signal as low as possible.

If you need more generator output, increase the value of the potentiometer. For sweeping single stages, when maximum gain is required, the potentiometer can be eliminated altogether. A suitable detector probe for single-stage alignment (where there is no detector) is shown in Fig. 3.

Virtually any inductance can be used externally to determine the sweep

(center) frequency. For 455-kc alignment, one winding of a discarded i.f. transformer makes an excellent tuned circuit. There is no need to remove the internal capacitor unless the sweep frequency is too low to hit 455 kc. I.f. and rf transformers can also be used at other common alignment frequencies. Above 4.5 mc it is more convenient to use slug-tuned coils. At 27 mc and above, a few air-wound turns make an excellent coil. The turns may be spread or compressed to vary the frequency.

If you are not sure of the sweeping frequency, tune it in on a general-coverage receiver. You'll recognize the signal immediately by its distinctive sound. The external inductance can also be checked with a grid-dipper. Turn the sweeper on when you dip the coil.

Sweep linearity is intentionally rather poor. As the frequency is varied, and the alignment curve moves across the scope trace, the pattern width will change. Thus, when you align selective circuits, change the frequency until you get the broadest curve. If you're working with broad-tuned circuits, change the frequency to move the curve to the opposite end of the scope trace to narrow the alignment curve. Sweep width can be decreased by adding capacitance across the external inductance to reduce the effect of the diode capacitance change.

Always use the slowest possible sweep speed to obtain the most faithful reproduction of the alignment curve. Crystal filter alignment is particularly critical. If the speed is increased beyond 20 cycles or so, crystal ringing will distort the curve.

For best results, use the oscilloscope on the dc-coupled position. At slow sweep speeds, the coupling capaci-

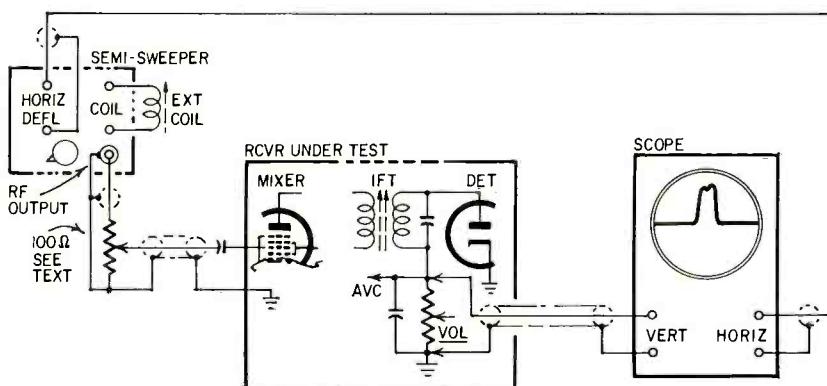


Fig. 2—How to connect Semi-Sweeper to scope and receiver or amplifier to be aligned.

tors in an ac-coupled scope cannot pass the low-frequency components of the waveform and distortion occurs. If a dc scope is not available, increase the generator sweep speed to a compromise setting.

Although 100 kc is an arbitrary minimum, the sweeper will work at lower frequencies. Below 100 kc, comparatively large capacitances are required to resonate a coil to a given frequency. This shunt capacitance across the Varicap reduces the effective sweep width. When you use the sweeper below 100 kc, always use a large inductor so that only a small amount of external parallel capacitance is required. The J. W. Miller multiplex adapter coils (such as No. 1351) are excellent inductors down to 50 kc or so.

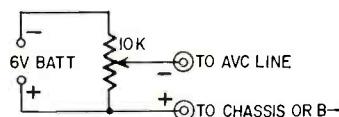


Fig. 4—"Bias box" for replacing *avc/age* voltage with fixed voltage for alignment.

For an accurate alignment curve, disable the *avc*. Otherwise, the rectified sweep signal from the detector will be fed back via the *avc* circuit as a correcting voltage. When the sweep curve changes direction or amplitude, the *avc* tries to counteract the change. Obviously this results in a distorted curve. Use a "bias box," as shown in Fig. 4. By connecting it across the *avc* line you have complete control over the gain of the i.f. simply by adjusting the potentiometer.

The oscillator is so strong that just about any external coil is satisfactory. If you don't have a junkbox full of old coils, you can make suitable inductors out of old slug-tuned coil forms. They can be scramble-, solenoid- or layer-wound with equal success. The more turns you use, the lower the resonant frequency. If you own a grid-dip meter, you can check the tuning range of the coils by tacking a 50-pf capacitor across each. This represents the approximate capacitance inside the sweeper.

As you go higher in frequency, you may find the sweep range excessive. This is because the capacitance of the Varicap has a greater effect on the frequency of the tuned circuit as the inductance is made smaller. Sweep width can be reduced by paralleling the external inductance with additional capacitance and withdrawing the slug or removing turns to maintain the same resonant frequency.

My Semi-Sweeper has been used almost daily since it was constructed. Cost of construction should be about \$20, far less than the cost of a comparable ready-made or kit instrument.

END



FOOLPROOFING THE TRANSISTOR DUO

By RUFUS P. TURNER

A two-terminal p-n-p-n semiconductor device, such as the four-layer diode, has many interesting and useful applications in simple circuits: low-voltage relaxation oscillator, flip-flop, static switch, power inverter, negative resistor, among others. But this is an expensive component.

Many articles have stated that the four-layer diode corresponds to a p-n-p and n-p-n transistor connected in series in a regenerative loop, as in Fig. 1-a. And people have asked immediately, "Why can't I hook up two inexpensive transistors to get the same operation?" Most who have tried such a *transistor duo* have gotten nothing but straight dc conduction, no bistable operation. The secret to foolproofing the arrangement is to connect a small resistance (*R*) between the base and emitter of the n-p-n

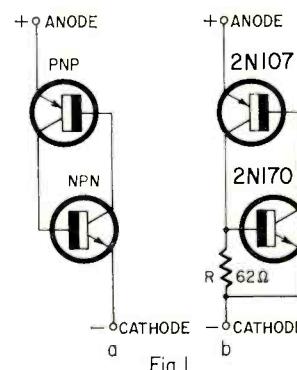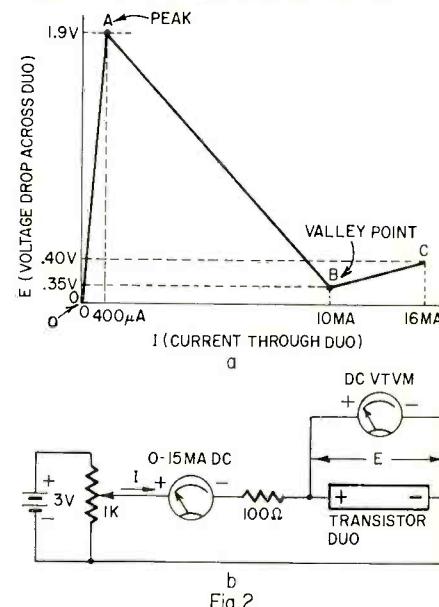μ a. Then as the current is further increased, the voltage drops rapidly to 0.35 at 10 ma. And as the current is increased still further, the voltage again rises to 0.40 at 16 ma, as shown.



transistor, as in Fig. 1-b. This allows the p-n-p collector current to develop a signal voltage drop across *R*, which is high enough to drive the n-p-n vigorously.

Without the resistor, the current flowing into the n-p-n base is not always high enough to trigger the circuit. I found a 62-ohm $\frac{1}{2}$ -watt resistor just right, but some adjustment in one direction or the other may be needed with individual transistors.

Fig. 2-a shows response of the duo. When dc is supplied from a current source (variable voltage source in series with a 100-ohm resistor, Fig. 2-b), the voltage drop from anode to cathode first increases rapidly from zero to 1.9 as the current is raised from zero to 400

μ a. Then as the current is further increased, the voltage drops rapidly to 0.35 at 10 ma. And as the current is increased still further, the voltage again rises to 0.40 at 16 ma, as shown. Region AB indicates negative resistance, whereas OA and BC represent positive resistance. When the duo is driven from a dc voltage source, the current increases slowly to 400 μ a (off state of the duo) as the voltage is increased from zero. When the voltage reaches 1.9, however, the current suddenly jumps to 10 ma (on state of the duo).

In many circuits, the duo is used simply as a neon lamp might be used at higher voltages; in other circuits, as a 10-ma tunnel diode. This combination is cheap when compared with higher-priced p-n-p-n units; at current prices, the 2N107, 2N170 and $\frac{1}{2}$ -watt resistor total \$1.54. Larger transistors may be used, of course, if heavier-current operation is desired. To make a simple, compact unit for wiring into circuits and for experimentation, the wired transistors and resistor may be enclosed in a small plastic tube, encapsulated with wax or other potting material, and a single pigtail brought out at each end.

DIODE RF SWITCHES

Practical circuits—like a transmit/receive switch—demonstrate possibilities for reliable remote rf switching

By IRWIN MATH

ORDINARY COMPUTER DIODES MAKE excellent rf switches. Because switching is completely electrical, there are no moving relays or closing contacts. This results in sure and noiseless contact each time.

It is well known that a forward-biased diode presents a very low impedance—a couple of ohms or less. A reverse-biased diode offers a high impedance, into the megohm region. Thus,

by placing a diode in series with a signal source and properly biasing it, one can produce a very satisfactory “electronic” switch.

Fig. 1 shows a typical diode switch. When a positive control voltage is applied, the diode is reverse-biased and will cause as much as a 10,000:1 reduction in signal (40 db). With a negative voltage, however, the diode is forward-biased. Now, the rf sees a low imped-

ance path, and passes through the circuit quite easily. Using this idea, we can come up with a very useful rf switch for coaxial lines. Fig. 2 shows a single-pole triple-throw switch. The dc bias voltages are the only ones switched mechanically.


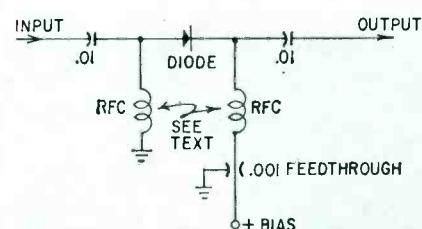


Fig. 1—Basic diode spst switch. The .01- μ f capacitors block dc.

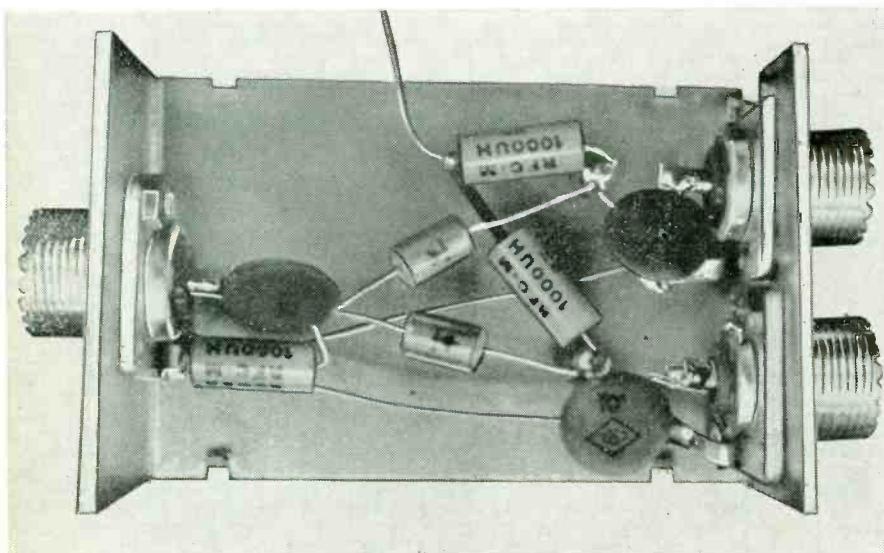Diodes used for these applications should be chosen for very high front-to-back ratios and small forward resistances. For low-power work, computer diodes such as the 1N118 and 1N100 do well. At higher powers, the typical germanium or silicon “top-hat” type, such as the 1N91 series, will be useful. In the uhf region, the 1N21 series would probably prove a good choice for an rf switch.



Author built his antenna-changeover switch into a tightly shielded aluminum box. Free wire in bottom photo is bias connection, brought through feedthrough capacitor in box cover.

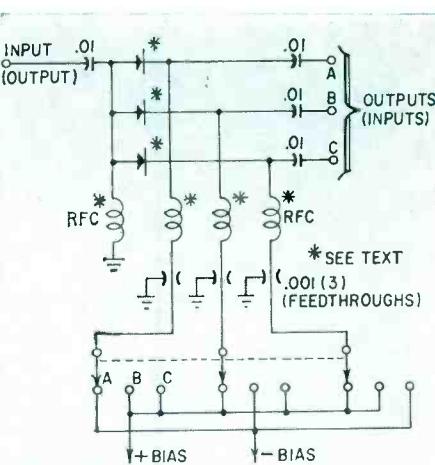


Fig. 2—An sp3t diode rf switch.

Again—the most important characteristic of the diode chosen for rf switching is the front-to-back ratio. This should be as high as possible. The forward resistance, on the other hand, should be as low as possible. At vhf, the capacitance of the diode structure becomes important.

The unit in Fig. 1 was used specifically for test purposes. The diode is

What's Your Modulation % ?

It's easy to find out with a scope

By FRED BLECHMAN, K6UGT

You've often heard "How's my modulation?" on the air. You know it's important—that the receiver responds to the modulation rather than to the carrier strength. But do you know how to measure your own modulation percentage? It's easy if you own (or can borrow) an oscilloscope.

an RCA type 1N1764. The 1-mh chokes should be all right from 3 or 4 mc to about 50. Above that, use 100- μ h chokes; below that, 2.5-mh or larger ones. With this circuit, a positive bias closes the switch. This bias may be anything from about 3 to 6 volts. A convenient source of bias voltage is the 6.3-volt heater supply. Fig. 3 shows a simple method of obtaining either positive or negative voltage from this supply. The 100-ohm resistors limit the current.

After experimenting for some time with diodes, I decided to build a diode-operated antenna changeover relay.

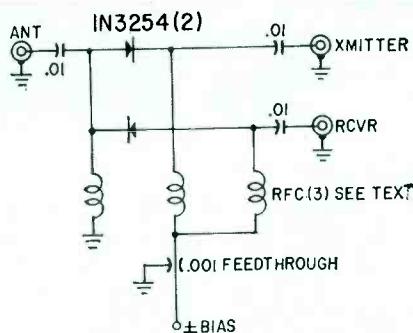


Fig. 4—Practical diode antenna-changeover (transmit/receive) switch. This amounts to an spdt switch.

The final device is shown in Fig. 4 and the photos. Switching is accomplished with the 6-volt supply described. The unit has been tested with 10 watts of rf in the 6-meter band (50–54 mc) and has up to 40 db of isolation between transmitter and receiver. As far as the rf from the transmitter to the antenna is concerned, there is only about $\frac{1}{4}$ to $\frac{1}{2}$ db loss through this path. I did not try the switch at frequencies much higher than 50 mc, but with the proper lead dress and component layout, it seems quite practical. For higher power, use some of the newer stud-mounted diodes on the market.

END

REFERENCES

- Bloom, M. "Microwave Switching with Computer Diodes," *Electronics*, January 1960.
- Hendershot, J. "Design of a Broad Band UHF Diode Switch," *Electronic Design*, November 1961.
- "Simplifying Switching Circuitry with Silicon P-N Junctions," *Solid State Design*, March 1962.

coil with respect to the transmitter coil. Adjust the pickup coil so you get about an inch-high scope pattern if you can. Be careful of exposed high voltages in the transmitter. The scope's vertical gain control, being bypassed, will have no effect on the height of the trace.

Now talk into the transmitter mike. The pattern on the scope should jump wildly. Adjust the scope horizontal width and sweep frequency for a comfortable display. Whistling (hold the mike farther away than when you talk) can give a remarkably clean wave-envelope pattern if you adjust the sweep frequency properly. The best arrangement is to use an audio signal generator as a modulating source; either feed it direct to the modulator input, or hook the generator up to a speaker and hold your mike near the speaker.

Here's how to measure the modulation percentage:

1. Speak as you normally do. Don't shout!
2. Measure the maximum pattern height in any convenient units. Call this height "A".
3. Measure the minimum height of the modulated pattern. Call this "B".
4. Now use this simple formula:

$$\text{Modulation \%} = \frac{A - B}{A + B} \times 100$$

You may find that you can drive your microphone harder without exceeding 100% (bright dots on the trace center line), but your distortion will probably increase. If you use an audio generator to feed the modulator, your display can be a stationary trace (see the photos) and you can pretty well tell where you begin trading clean modulation for distortion.

What do you do if the modulation of your rig is hitting 100%? Back away from your mike or you'll splatter all over the band. If your modulation is too low, speak closer to the mike, speak louder, try a mike with higher output or check the modulator tubes.

The sad fact is that many transceivers are design-limited to a low modulation percentage, since modulator power costs the manufacturer more dollars. If your modulation seems to be limited, you will probably find it worth your while to use one of the several speech-compression amplifiers on the market; these will make the most of the modulation percentage you do have.

The Proton Magnetometer: New Tool for Archeologists and Treasure-Hunters

This exciting electronic prospecting instrument has opened new paths to the past

By E. H. MARRINER

ARCHEOLOGISTS CAN SAVE PRECIOUS TIME with a new instrument: the *proton magnetometer*. Just recently, it has found stone-age civilization sites in England and probed Etruscan tombs in Italy. Now investigators are using it in the USA. No longer must archeologists drill holes and dig trenches just to learn whether there might be anything down there worth looking for. With the proton magnetometer, the center of a site can be plotted on a map long before anyone brings out the shovels.

An electrical method of probing has been used for some time. It works by passing a current into the ground through two outer electrodes in a line of four. The resistivity can then be calculated from a simple formula involving the measured resistance between the inner pair of electrodes and their distances apart. The success of a site survey depends on having a measurable contrast in resistivity between the structures sought and the surrounding ground. The contrast depends on the moisture content of the ground; this, being a variable, can be compensated for on the chart. Information is gathered by making a measurement spread through a right angle. Then the data are processed. A pattern 25 feet wide and 55 feet long can be plotted in 1 hour, against days of digging by the old method.

This method of locating sites has



Elsec Proton Magnetometer—a commercial unit.

been used in Europe for several years but has only recently been tried in this country. The University of California found a new San Dieguito Indian complex in San Diego County, California, on the first field trial. But the resistivity method is being supplanted by a new method, using the *proton magnetometer*.

Any instrument that measures a magnetic field is called a magnetometer.

Such instruments have been used in geophysical studies for many years.

The original magnetometer was called the Swedish mining compass. It was developed about 100 years ago and used only to detect ore bodies. About the turn of the century the Hotchkiss dip needle and super-dip were developed. During World War II, aircraft detection of submarines came out of this principle, although these devices were actually a type of variometer (instrument used to measure variations in magnetic fields).

In 1956 a group of research geophysicists developed the proton magnetometer. This instrument measures the magnitude of the earth's magnetic field. The operator of the device can detect a *magnetic anomaly* spatially on a chart (Fig. 1).

Systematic variations in the physical properties of the earth are what enable the magnetometer to find the structures that cause them. These variations are called *anomalies*. Anomalies due to magnetic material can be detected by the proton magnetometer. Two distinct types sought by the archeologist are those produced by soil of high susceptibility in comparison with its surround-

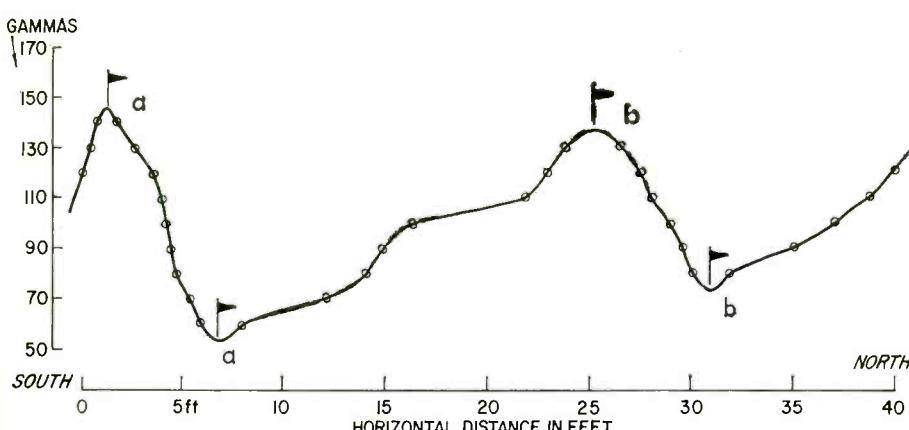


Fig. 1—Magnetometer readings are plotted along a straight line. Points between which magnetic susceptibility changes rapidly (as between the little flags *a-a* and *b-b*) define the areas where the searcher looks for objects of interest.

ing material, and those caused by the ferrimagnetic properties of heated material, which is termed *thermoremanent magnetism*.

The magnetometer is one of the few devices that have been adapted in the past few years to archeological surveying.

The first use of the proton magnetometer for archeological surveying was in the winter of 1957 at Huntingdonshire, England, by a group of Oxford University scientists. They detected a number of Roman and medieval walls and house outlines made of clay.¹

A few years later a group from the Indiana Historical Society used the device to find a pre-Columbian village in southern Indiana and produced enough evidence to map in detail the entire fortified village.²

A proton magnetometer of different design was used in the German Rhineland. This instrument produced readings unaffected by diurnal variations or magnetic storms. It proved of real value in this area since there is a great variety of subsoils in the pits and ditches. The Roman city of Xanten was explored with the proton magnetometer, and the survey data produced detailed maps of the city's foundations and defenses.³

Physical description

The proton magnetometer is composed of a control box and the *bottle* (Fig. 2). In the bottle is a plastic container called the sensing head, 1.85 inches in diameter. The bottle holds about a pint of distilled water. (Alcohol is used in arctic climates.) The bottle

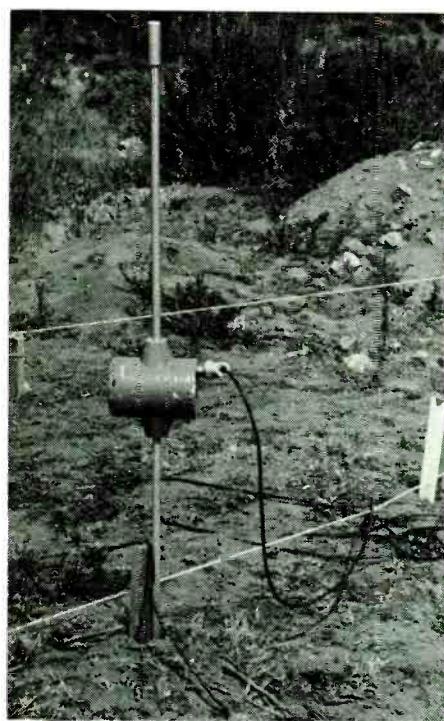


Fig. 2—The "bottle" section of a proton magnetometer.

is surrounded by a coil of wire (1.250 turns of No. 22 SWG) which serves the dual purpose of polarizing the protons and receiving the signal produced by the precession of the protons. In the receive position, the weak signal is amplified by an amplifier connected to the bottle unit by a cable. Digital indicators read this amplified signal and record the measurements.

A magnetometer is a rather simple device, though it depends on nuclear

reactions. It can best be described in the words of an article by Dolan Mansir in the April 1960 issue of **RADIO-ELECTRONICS**, which also showed some of the electronic circuitry used to amplify and detect the magnetometer output. Part of the article is reprinted here.

How a magnetometer works

"Protons are simply the nuclei of hydrogen atoms, and there are two reasons why they can be used to measure magnetic fields: Protons have magnetic moments, like very small bar magnets, and they spin on an axis through their magnetic poles—or at least their behavior indicates they do.

The magnetic moment and spin determine a property known as a gyro-magnetic ratio. This merely means that the tiny bar magnets, spinning on their axes will *precess* at a given frequency (like a spinning gyro, which will wobble but not fall if tipped) if they are placed in a given magnetic field—and if you follow the right sequence of steps to cause the precession to occur.

Causing and detecting precession


What does it take to cause a free precession and how do you detect it? If a bottle of water or other substance containing many hydrogen atoms is placed in a strong nonoscillating magnetic field, the nuclei of a majority of the atoms will align themselves with the applied magnetic field. Now, if the magnetic field is suddenly removed, the spinning atomic gyroscopes are given a "push" by the earth's magnetic field, and they start to precess in phase. After a few seconds, the phase relationship is lost as the nuclei align with the earth's field and it is necessary to start over with the aligning process.

If the aligning field is exactly in the same direction as the earth's field, the protons do not get a push and no precession occurs. For best signal amplitude, the aligning field should be at right angles to the earth's field. Alignment affects only the signal amplitude, not the signal frequency.

In practice, the protons are actually placed in a bottle which is put in the center of a simple coil of wire. The coil does double duty—it furnishes the strong magnetic field to align (polarize) the protons, and the precessing magnetic moments of the protons induce the signal voltage in it. This is exactly analogous to an ac generator."

Magnetic susceptibility

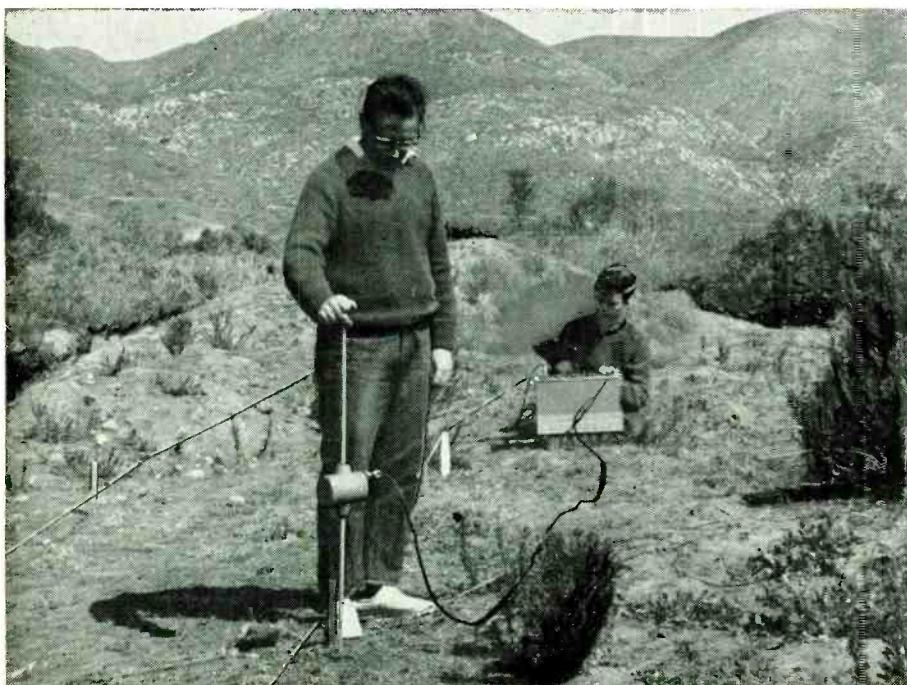Magnetic susceptibility determines the magnetic moment induced in a sample when it has been placed in a magnetic field. By the susceptibility method the proton magnetometer can detect pits, ditches, walls and tombs. The




Two archeologists make a field survey with the proton magnetometer.

amount of susceptibility in a pit is related to the amount of organic matter in the soil from food, waste material, burials or charcoal. Many tombs have air pockets which cause a change in susceptibility from the surrounding material, as was discovered by Dr. Lerici at a few sites in Italy.⁴

Iron oxides in pottery shards, kilns and furnaces produce the second type of variation, thermoremanent magnetism. The overall content of iron oxides on the earth's surface ranges from 0-1%. The oxide is normally magnetite, hematite, or maghemite, a structural combination of the first two. As pottery is fired, its temperature is raised, resulting in the alignment of the ceramic magnetic properties with the earth's field; on cooling, the domains are fixed in one direction, forming a weak permanent magnet.

Anomalies produced in these ways vary in range from 0-100 gammas,⁵ which is equal to about 1/500 of the earth's magnetic field. Iron artifacts or deposits can produce even larger anomalies depending on their size and the depth at which they are buried.

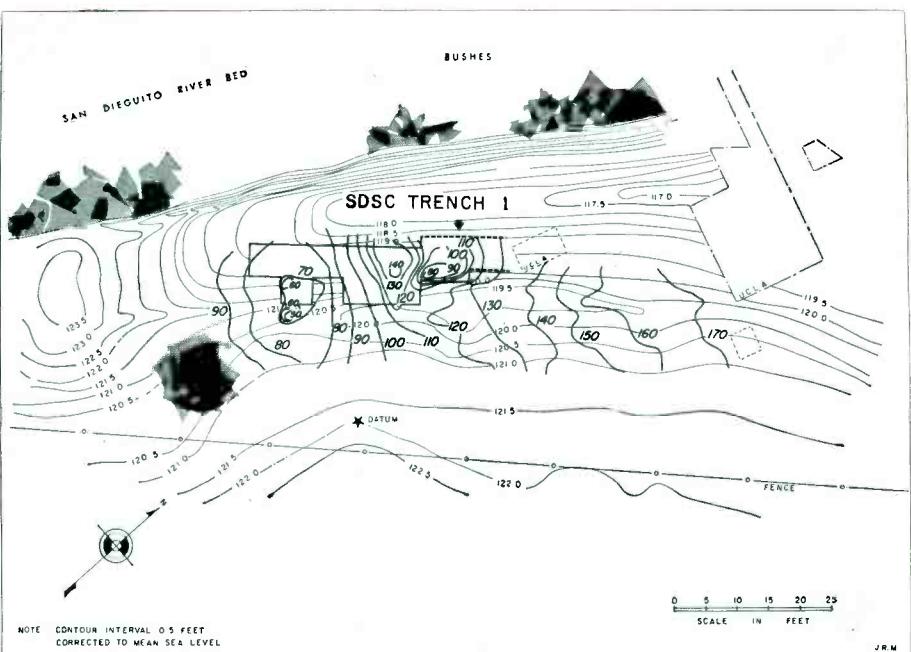The primary reasons for the success of the proton magnetometer are simplicity of operation, fast surveying, reduction of manual labor and relatively low cost compared with prices of other geophysical instruments.



Magnetic contour map. Light lines and numbers are ordinary topographical contour lines; heavy lines and numbers are contours of magnetic susceptibility. Bunched contours represent sharp gradations in magnetic susceptibility and are the areas that interest researchers.

The future of the device looks very promising. Many more discoveries, made with its help, will enlighten our record of man.

END

References

- 1 M. J. Aitken, *Magnetic Prospecting*. *Archaeometry*, 1958, Vol. 1, pp 24-26.

2 R. B. Johnston, *Archaeological Applications of the Proton Magnetometer in Indiana*. *Archaeometry*, 1961, Vol. 4, pp 71, 72.

3 Irwin Schollar, *Magnetic Prospecting in the Rhine-land*. *Archaeometry*, 1961, Vol. 4, pp 74, 75.

4 R. E. Linington, *Quaderni di Geofisica Applicata*, 1960, Vol. XXII, pp 13-28.


5 M. J. Aitken, *Physics and Archaeology*. Interscience Publishers, New York, 1961.

WHO INVENTED IT?

By Robert G. Middleton

The Wheatstone Bridge

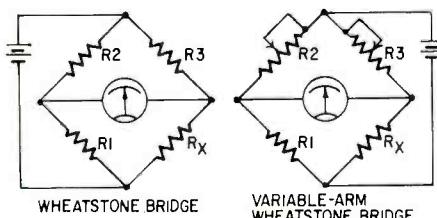Who invented the Wheatstone bridge? Who invented the variable-arm Wheatstone bridge?



R-C checkers, is also called a Wheatstone bridge, used on most service benches in Simeons. The Simeons invented by S. H. Christie of the Royal Military Academy at Woolwich, England, and was described by him in the *Philosophical Transactions of the Royal Society* in 1833. Christie's name was unknown, and his invention was invented by James Clark Maxwell published the science.

Three stupid questions? Not all all! The upside-down answers may surprise you.

The Wheatstone bridge was invented by S. H. Christie of the Royal Military Academy at Woolwich, England, and was described by him in the *Philosophical Transactions of the Royal Society* in 1833. Christie's name was unknown, and his invention was invented by James Clark Maxwell published the science.

Who Discovered Coulomb's Law?

Coulomb's law states that the force exerted between two electric charges is equal to the product of the charges and is inversely proportional to the distance between them: $F = k \frac{q_1 q_2}{r^2}$. Who discovered this law?

Coulomb's name was firmly associated with the law. It has been claimed that Coulomb was the true discoverer because he made the law known to other scientists promptly. However, about 100 years had passed, and is called the Wheatstone bridge to this day. No one has yet had the courage to identify the bridge as a Christie bridge. The variable-arm Wheatstone bridge was invented by Werner Siemens. The Siemens bridge, used on most service benches in Germany, is also called a Wheatstone bridge.

Henry Cavendish, a wealthy scientist and philosopher, discovered the law independently.

Irving Schollar, who made several years before

$F = q_1 q_2 / r^2$. He did not publish this discovery.

And Coulomb discovered the law independently.

James Clark Maxwell published the science.

Charles Pouldier in 1837. However, the in-

vention fell into obscurity. Later, his inven-

tion was named the galvanometer after

Galvani, whose name was well known. One

of Galvani's students discovered that a

frog's leg twiched when it was touched by

metal, with a static machine operating

nearby. Galvani followed up this observa-

tion, and discovered that a frog's leg was

twiched when it was touched by another

frog's leg together at one end, and the other

placed together at the opposite end. He sup-

posed that electricity from the nerves was

passed through the frog's leg. He sup-

posed that electricity from the dissected leg,

which was responsible for attaching his

hand to the frog's leg reacted with the

other frog's leg, and the two different metals were

twiched when a frog's leg was observed.

Galvani followed up this observation

and discovered that a frog's leg was

twiched when it was touched by

the frog's leg.

The current meter was invented by

Claude Pouillet in 1837. However, the in-

vention fell into obscurity. Later, his inven-

tion was named the galvanometer after

Galvani, whose name was well known. One

of Galvani's students discovered that a

frog's leg twiched when it was touched by

metal, with a static machine operating

nearby. Galvani followed up this observa-

tion, and discovered that a frog's leg was

twiched when it was touched by another

frog's leg together at one end, and the other

placed together at the opposite end. He sup-

posed that electricity from the nerves was

passed through the frog's leg. He sup-

posed that electricity from the dissected leg,

which was responsible for attaching his

hand to the frog's leg reacted with the

other frog's leg, and the two different metals were

twiched when a frog's leg was observed.

Galvani followed up this observation

and discovered that a frog's leg was

twiched when it was touched by

the frog's leg.

The current meter was invented by

James Clark Maxwell published the science.

TV TUNER TROUBLES

TV front-ends need be no more frightening than any other part of a set

By JACK DARR

SERVICE EDITOR

LOTS OF US HAVE TROUBLE WITH THESE little tin boxes, and too many of us won't even try to repair them. Worst of all, now and then we have a tuner overhauled, get it back and install it, and still have the same trouble. (Because we weren't *sure* it was tuner trouble.) So, let's see if we can't find some tests that'll tell us definitely that we have a bad tuner. While we're at it, let's see if we can't fix more of them "at home." Tuner repair services are invaluable, but we do ship a lot that could be fixed on our own benches.

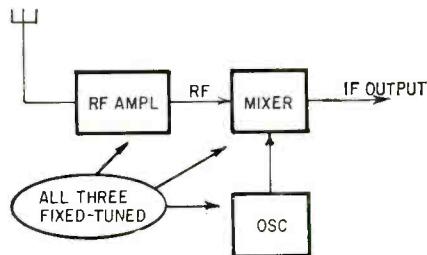


Fig. 1—Three fixed-tuned stages, that's all.

Electrically, a tuner is about as simple as you can get. Three stages: rf, mixer and oscillator (Fig. 1). All fixed-tuned—the only adjustment is a wee capacitor in the oscillator circuit. All the rest are fixed, and we select the right coils with some kind of switch (Fig. 2). It's only the physical construction of a tuner that's complicated.

A tuner tunes by amplifying the rf signal, beating an oscillator signal with it, and selecting the right beat frequency for the i.f. Heavy wire coils are used, with only a few turns, since we're working in vhf. These are tuned mostly by their own, plus some stray, self-capacitance. So, they're not going to give you much trouble, if you let them alone. (Just like a rattlesnake!)

Most tuner troubles turn out to be things like dirty switch contacts, bad tubes and burned resistors. More trouble is caused by unskilled attempts to repair than by actual part failures! So, here's Axiom No. 1, in all tuner work: "Let it alone until you're sure where the trouble is!" We'll show you how to make all necessary tests on any tuner, without ever taking the cover off.

What's the simplest test for any electronic circuit? Performance. See if it's doing what it's supposed to. The tuner's supposed to deliver an i.f. signal to the i.f. amplifier input, so let's see if it does. Here are the symptoms of tuner troubles:

1. Picture flashes on and off, and you see streaks and flashes on the screen when the channel selector knob is turned, or the tuner is jarred.
2. Heavy snow, weak pictures.
3. High channels gone, lows fair or good.
4. Low channels gone, highs OK.
5. White-out: no sound, no pix.


Now, this is where we have to watch out! A couple of these symptoms, most especially No. 5, can be due to other things: age, weak i.f. tube and so on. Too quick a diagnosis can get us into trouble deep. So let's test carefully and eliminate the other causes before we go digging into the tuner, huh?

Quick-check: Override the age with a bias box. If this brings the picture back, then we fix the age trouble and let the tuner alone. *Best test:* feed a test i.f. signal into the i.f. input. If this produces a good picture, but we can't get anything through the set's tuner, then we know that the trouble must be there. Incidentally, we don't have to get a perfect picture on this test; as long as we get a very decided improvement, this is the answer we want. Practice tells you what kind of picture to expect.

Common tuner troubles

There are a lot of switch contacts

Fig. 2—Same basic circuitry appears in most tuners. Some may have neutralized triode rf's, some cascodes, some old ones even pentodes—but they all have rf's!

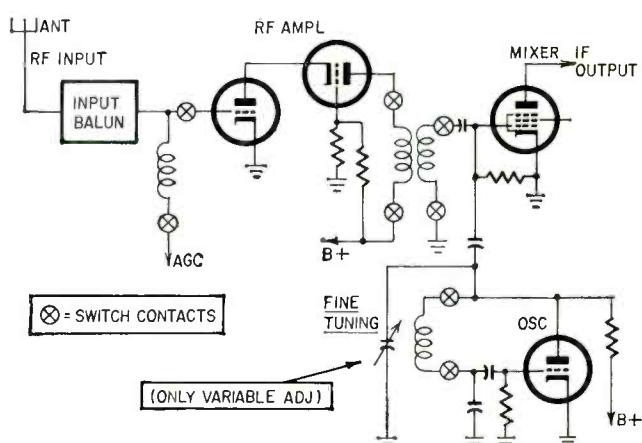

in a tuner: 96 in even the smallest! If any one of these is dirty or intermittent, you've got trouble. Just to be sure, I asked a lot of technicians what the most common tuner trouble was, and got the same answer from all of them. "Dirty switch contacts!"

Test: Turn the channel-selector knob. If you have to wiggle it to make the picture come on, and if there are flashes and streaks on the screen when the knob is moved, that's it. Step 1, spray the tuner thoroughly with tuner cleaner compound. There are several on the market, all good. Use a long thin plastic tube on the nozzle, and push it through the holes in the tuner housing to get closer to the switches. Turn the knob continuously while spraying, to work the dirt loose and flush it out.

In about 8 out of 10 tuners, this will fix the trouble. If it won't, then you're going to have to go inside. This is a shop job. Don't try to do it with the tuner balanced on your knee!

Tuner cleaning, in the shop

Because of the way a tuner works, the best way to test it is in actual operation. Coil resistances are so small you can't measure them. So we need a method that will let us get to the tuner, and at the same time leave it working normally.

Many of the late tuners are mounted separately, on a cable long enough to let you take them loose and examine them, leaving the rest of the chassis in the cabinet. Any tuner can be handled that way! Make up a test cable of insulated wires, about 5 of them. (Handiest: fasten one end to a terminal strip, then screw the wires to that.) Take the wires off the tuner, being sure to mark the color of each on the top near the connection. Tack your extension wires to the tuner; make the cable long enough to let you get the tuner on the bench. The length isn't critical at all, with these.

The i.f. output lead is usually a short piece of coaxial cable. If you want to, make up a plug and socket for extending it, but you'll get about as good results

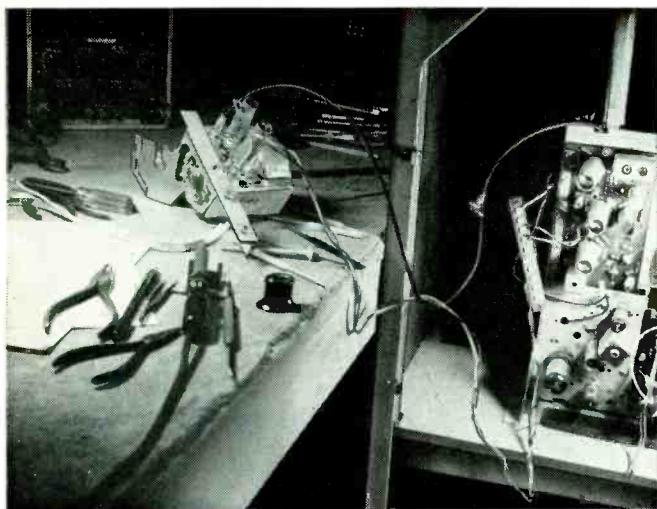


Fig. 3—Extension cables make work easier.

with a piece of insulated wire. Fig. 3 shows this setup in use. You'll be surprised at the good picture you get. Only one thing: don't try to align a tuner out in space like this; wait till you get it back on the chassis.

You'll need one more wire for a ground: if you forget that, the tubes may not light! Also, put a piece of spaghetti or tape on the B+ connections; otherwise, they bite! Now you're all ready to go.

Set up so you can see the screen. Sometimes your cables will let you turn the cabinet far enough. Other times, you'll have to use the mirror. Hook up the antenna, and try the set.

You need the right tools. Right now, before we take the cover off that tuner, let's get that straight! *Suggestions:* a couple of nylon tuning tools, preferably with a screwdriver tip; small long-noses and cutters, or a pair of locking tweezers; a couple of metal "soldering-aid" tools, with a slotted tip; and a long, thin soldering iron of some kind, and we're ready to go. A magnifying glass is a big help, too.

Check to see which channels are giving trouble. Usually, only one or two are really bad. Look at the switch contacts: you'll usually see the dirt on them. If this is a turret tuner, take the drum out by unhooking the spring clips at each end. Clean the contacts on the turret by rubbing them with a clean, dry paper towel (Fig. 4). [Better yet, use a special switch and tuner kit such as Standard Kollsman's Conta Care that contains a special cleaning cloth and sulphur-free contact oil.—Editor] Leave them dry; no lubrication. Now look at the fixed contacts. Fig. 5 shows a set, before cleaning. Give these the paper-towel treatment, too.

In a few cases, these contacts will lose their spring. Using a soldering-aid tool, you can bend them to make contact firmly again. If they've lost tension, slip a short piece of plastic spaghetti through the "loop" to build up the tension. **While cleaning these, or any other tuner, contacts, be sure you don't move any parts or wires; this will throw the unit out of tune!**

Wafer-switch tuners are more dif-

ficult, but not impossible to get into. A strong magnifying glass is a big help, preferably something like the one shown in Fig. 6. Prop the tuner up on a small cardboard box, to keep it still while you're working on it.

In these tuners, caution is even more important. While working "inside," be **VERY** sure that you don't move any of the coils, wiring, etc. Spray cleaners on the switches. If necessary, give them a brushing at the same time. Get a kid's water-color brush at the dime store, and clip the bristles off about $\frac{1}{4}$ inch long. Pipe cleaners leave bits of fuzz on the switch, which could cause trouble.

To find the channel switch that's giving the trouble, look on the switches for the "junction" between the low-band coils, made up of several turns of wire, and the high-band coils, which will be just a half-turn of wire. The last low-band coil will be channel 6, and the first tiny coil, next to it, is channel 7.

With the tuner set on a bad channel, carefully touch the slider on each deck with one of the nylon tools. When

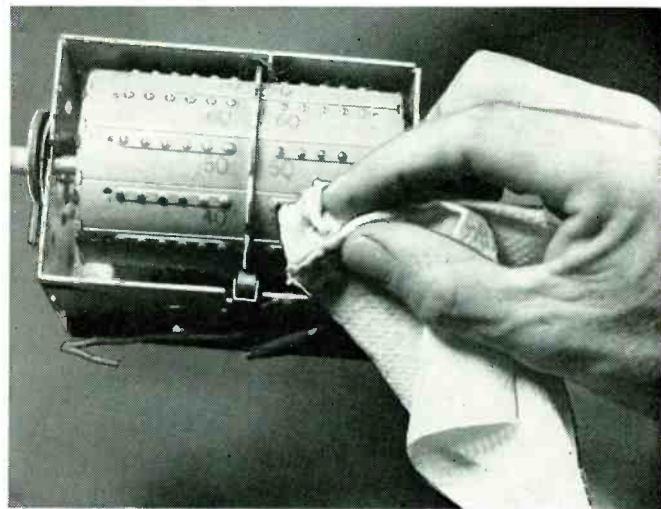


Fig. 4—Shine contacts with a paper towel.

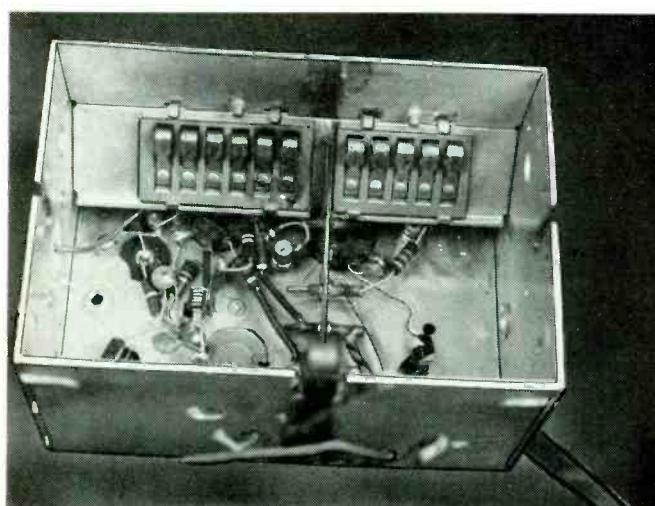


Fig. 5—Shine turret-drum fixed contacts, too.

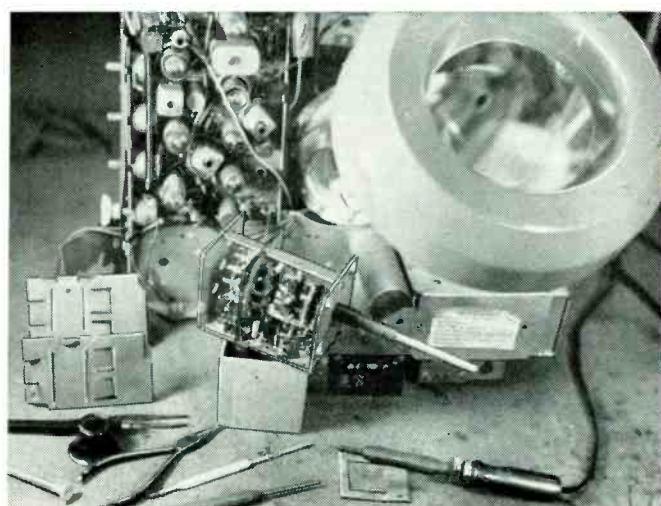


Fig. 6—A big magnifier (upper right) is a big help.

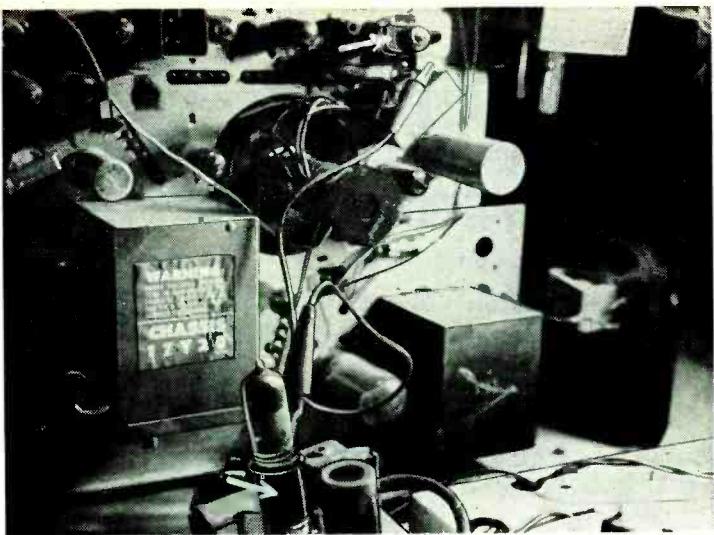


Fig. 7—Injecting an i.f. signal from a working tuner (bottom left) usually establishes definitely whether set's tuner is bad. Use adapter sockets and a clip lead.

you hit the bad contact, the picture will come on. To cure this, turn the tuner to another channel (to get the slider out from between the fixed contacts), and very carefully bend the contacts, just a wee bit! Now, try it again.

On some tuners, watch out for bad contact between the slider itself, on one side of the wafer, and rivets on the other. If you find this kind of trouble, touch the rivet with a very fine-pointed soldering-iron tip, and put just a tiny gob of solder on it. Don't do this on the slider side, as you may get solder on the metal slider which would be hard to get off. If you use soldering paste or flux, use it very sparingly.

Along this line, watch out for bad solder joints, on coils or anything else, especially tube sockets. You can find these by very gently touching the suspected coil with an insulated tool.

Tuner tests without teardown

To sum up: what we need is full information about this tuner without having to go inside to get it. Fortunately, we have gadgets that'll let us do that easily.

First, make a signal substitution test. Feed a test signal at the i.f. from a pattern generator into the i.f. input.

If this brings the picture back, and we have already checked out all the other possibilities, like agc, etc., then we can be fairly sure the trouble's in the tuner. You can get a good test signal from another TV set with the same i.f. Simply connect a test lead, with a clip on each end, from tuner output of the good set to i.f. input of the bad one. This can be done easily with two tube adapters (Fig. 7). Here, we connected from the mixer plate to the i.f. grid.

Now where do we go? To detailed tests of the bad tuner, to find out just why it won't work. Always remember this: this tuner was working, and suddenly quit. So, what's the most likely reason? Some part has failed! We checked the tubes by replacement, before we left the house with the set, so that takes care of them. Now, we must find out what part has failed and replace it.

Set the tubes up on the test adapters, in Fig. 7, and measure the operating voltages. The most common trouble here will be burned resistors in the plate circuit of the rf amplifier. This is caused by a short in the old tube. If the resistor is burned badly enough, it'll change value and upset the rf plate voltage. If the voltage is off (and, remember, the only

way you can get the correct B+ voltage distribution in a cascode rf amplifier is with the tube in the socket!), the chances are that it's this resistor. Confirming check: turn the set off and measure the resistor by connecting your ohmmeter between plate of the tube and the B+ terminal on the tuner (Fig. 8). You can measure all other resistors in a tuner with this method: measure between the correct terminal on the tube socket, and the supply connection (agc, heater or whatever).

Part replacement

OK, the resistor's bad. Its usual location is between two decks of the wafer switch, in a pretty tight place. Don't try to unsolder it. Take the small diagonals and clip it out, leaving as much lead as you can. Now clip the leads on the new resistor to a bit longer than what's left on the bad resistor, tin them nicely, and hold one end on one of the connections. Solder quickly, to keep from overheating the resistor. Now, bend the other end into place, and tack it too. (No strain on these joints, since the resistor is small.) Don't hold the iron on too long, "hit it and git", but be sure to make a good solder joint!

You won't have trouble with oscillators very often. They're so simple that they usually work pretty well, given good tubes and correct voltages. The worst trouble with oscillators is misalignment. This is usually the result of "screwdriver drift," and not of a fault in the oscillator itself. Watch out for dirty tube-socket contacts; they cause a lot of trouble in oscillator circuits, including drift!

Finally, always check the balun coils at the input for continuity. If lightning has paid a visit to the neighborhood lately, there is always the chance that one of the coils is open. Symptoms: snowy pictures, or the same "high channels OK, low channels out" (and vice versa) symptom that you can get from a bad rf amplifier tube, and, in some cases, no pictures at all.

Replace with exact duplicates, to hold your front-end impedance match to the antenna. Quick-check: touch one side of the antenna lead-in to ground (tuner chassis) and touch the other end, with a very small capacitor in series to prevent shorting out the agc, to the input grid of the rf amplifier. To get at the grid, set the tube up on the test adapter. If the picture gets a lot better, then you've probably got an open balun coil. Be sure to check the agc first, though, for you can get some very peculiar results from this test if you don't!

Suggestion: try all the tests outlined here on sets you know are in good shape. That way, you'll know more about what kind of results to expect when you try them on bad ones.

END

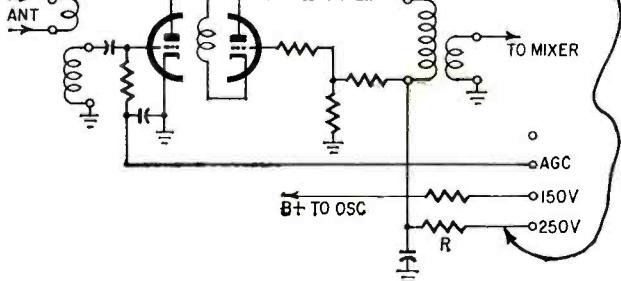


Fig. 8—Plate dropping resistor or agc isolating resistor can be checked between terminal on tuner chassis and correct tube-socket pin.

40 Watts in 40 Ounces— Building the Two-State Amplifier

Full construction and testing details on 40-watt switching-mode PA amplifier introduced last month

By NORMAN CROWHURST

Last month we printed the schematic, parts list and description of a unique 40-watt public-address amplifier that used the output transistors as two-state (on or off) switches rather than as linear amplifiers, producing a tremendously efficient amplifier with very little dissipation in the output transistors. The schematic is reprinted here for convenience. (A full discussion of the theory of the Two-State amplifier was printed in the July issue on page 54.)

This month we build the amplifier, test it and put it to work.

ONCE YOU HAVE THE SUBCHASSIS AND main chassis (case) drilled, clean off burrs and rough spots from around all the holes, but especially from around all holes in the case that will pass the pins or mounting screws of power transistors Q13 and Q14. Sharp metal bits there may puncture the mica insulators between the chassis and the transistor cases (common to the collectors). That could blow a fuse, or, worse, burn out the output transformer.

Lay the outer chassis (case) aside. All the work will be done at first on the subchassis.

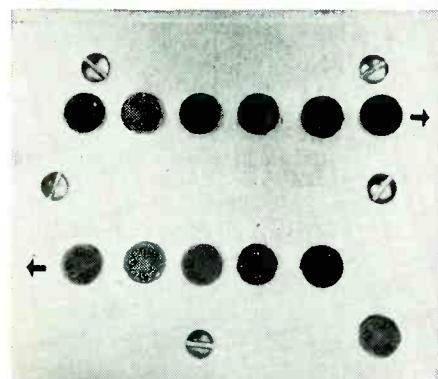


Fig. 1-Line up transistor sockets exactly this way.

Mount the twelve transistor sockets with their snap-on rings as shown in Fig. 1. Align the sockets exactly as shown—note that the base (center) holes “point” one way in one row and the opposite way in the other. Mount terminal strips

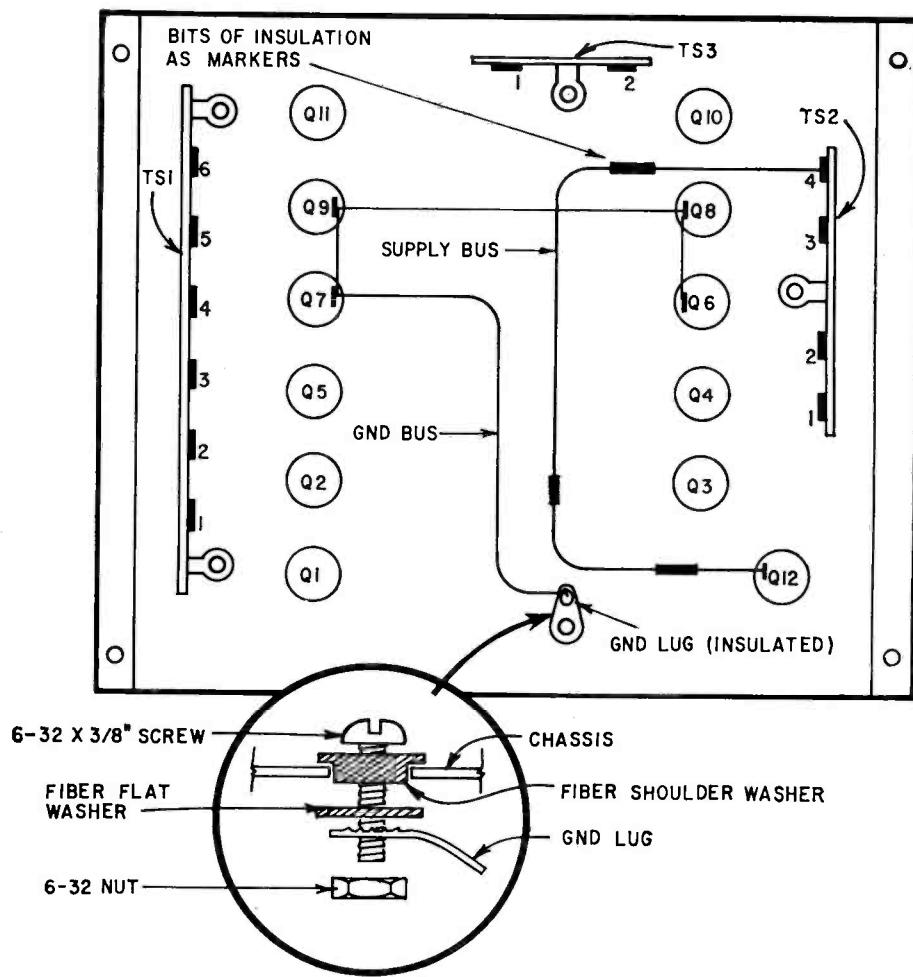


Fig. 2—Terminal-strip positions, ground and supply bus paths, and details of insulated mounting for ground lug. Flat and shoulder fiber washers are available in small plastic-box assortments at almost any electronic parts store.

TS1, TS2 and TS3 as shown in Fig. 2. Opposite TS3, mount a ground lug with one flat and one shoulder fiber washer to insulate it from the chassis; the only connection to chassis should be via the microphone jack on the case (this comes later).

Use lockwashers under all nuts! The vibration of a moving vehicle will loosen nuts in an amazingly short time if you don’t.

Form the ground bus by connecting together the emitter pins of Q6, Q7, Q8 and Q9 with a piece of bare tinned No.

20 solid wire, then run the wire down the center of the chassis to the ground lug (Fig. 2). Solder all connections as you make them, with a small, hot iron and a minimum of solder. The ground bus should be clear of the chassis (by about 1/4 inch) everywhere. You can trace its path approximately in Fig. 3; the insulated ground lug is at the bottom of the photo.

Make up a supply bus (which will carry the negative side of the 12-volt supply) by running a piece of bare tinned No. 20 solid wire from TS2-4 to

the emitter terminal of Q12 socket (Fig. 2). Run it down along the chassis slightly above and to the right of the ground bus. You'll find it helpful to slip a few scraps of colored insulation over it before you wire it in, so that you can distinguish it at a glance from the ground bus during wiring and testing.

Try to lay parts parallel or at right angles where possible, at least at the beginning—not for beauty, but because leads will be far easier to follow after you get the first few dozen parts in, than if you haywire the chassis.

Now begin wiring resistors and capacitors, beginning with emitter resistors R3, R8, R13, etc., and the large 2-watt resistors R36 and R40. Parts that the photo shows you are close to the chassis should go in first, of course—don't wire yourself into a hole. (Keep in mind the picture of the man painting a floor, finishing in a corner opposite the only door to the room.)

All pigtail-wired parts are called out in Fig. 3, and in most cases you can see exactly where the leads go. Use spaghetti tubing wherever it seems desirable; better an extra minute now than an hour later tracking down shorts.

Occasionally you will have to make a floating junction—several leads soldered together without the support of a lug. (R20, R35 and C22, for example.) In such spots, join the floating leads first, while the parts are still loose. Grab, say, the two resistors between thumb and forefinger, crossing the leads at one end of each. With long-nose pliers, grip the leads just beyond the point where they cross and twist tightly three or four times. Then solder—hot, and with as little solder as possible. Clip off the excess lead, and you have a junction almost as rigid as one supported by a tie point.

The wiring is easy if you proceed systematically. Wire with foresight!

Main-chassis wiring

Mount all parts on the case, including the sockets for Q13 and Q14, but not the transistors themselves. Wire the ground connection (Fig. 4) between the mike jack J and the volume control. (The volume control used in this version of the amplifier is somewhat unusual—a surplus item; in the more common type of control the ground connection is the right-hand terminal as you look along the shaft.)

Connect R31 and C16 (if used—see text and table in last month's article) in parallel across the terminal strip (Fig. 4). Connect the speaker terminals to the outermost lugs of the output transformer with No. 18 or heavier wire (ordinary plastic-insulated "zip-cord" is OK). Use equally heavy wire for the connections between Q13 collector and output transformer lug (ditto

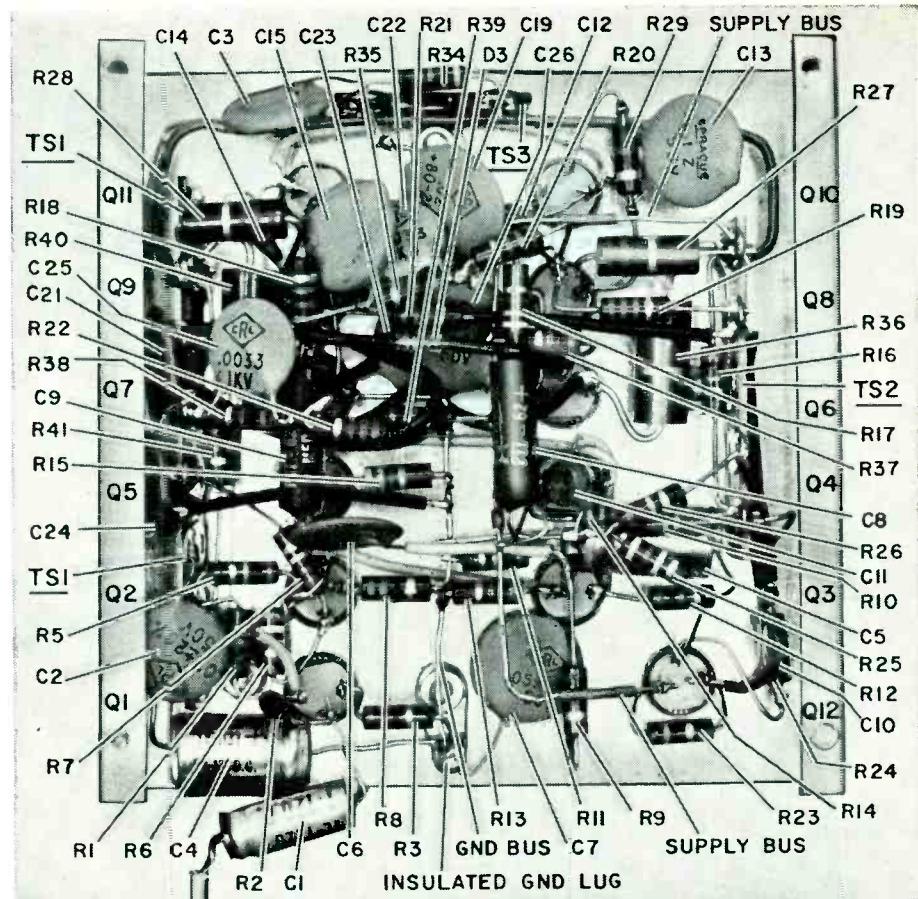


Fig. 3—Completely wired subchassis. D4 and R30 are hidden from sight; C16, C17, C18, C20, D1, D2, R4, R31, R32 and R33 are all part of the main-chassis wiring and do not appear here.

Q14). Connect 18-ohm resistors R32, R33 between base and emitter of Q13 and Q14, respectively. Wire in, according to schematic and photos, C17, C18, C20, D1 and D2. The cathodes—striped ends—of D1 and D2 must be joined. The anodes go to the second and fourth transformer lugs (collectors of Q13 and Q14).

Install the battery cable. Be sure polarity is correct. Determine the polar-

ity of the car electrical system with which this amplifier will be used, and be sure that the negative side goes to the transformer center terminal. The positive side will be connected to the subchassis ground bus and ultimately to chassis via the mike jack.

Now lay the subchassis inside the main chassis approximately as shown in Fig. 5. Set it on a small box or block of wood to raise it so that you can get at

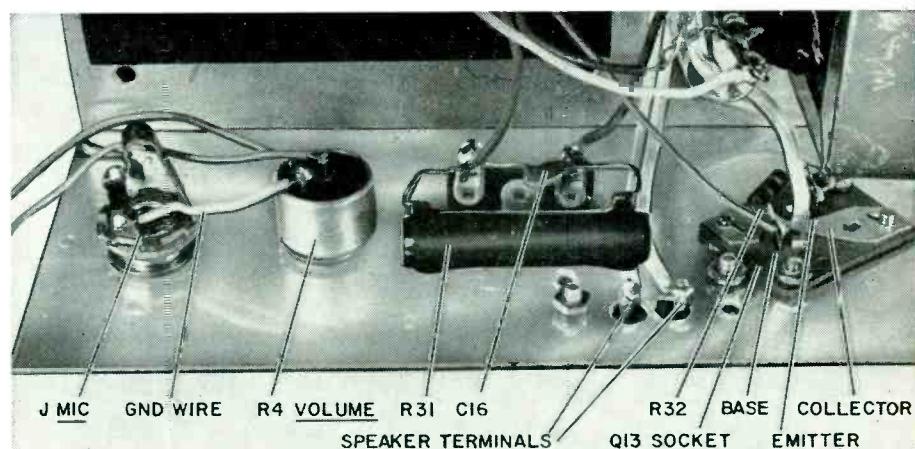


Fig. 4—Parts and wiring along the front of the main chassis.

all connections easily.

Finish all wiring by interconnecting parts on the main chassis to parts on the subchassis according to the schematic and photos. Leave enough slack in the wires to allow maneuvering the subchassis into its final place, but don't overdo the excess length. Stranded wire will be easiest for this job. Figs. 5 and 6 will help you.

Line the main chassis with plastic electrical tape under the area of the subchassis, just in case. Now you're ready to check the circuit stage by stage.

Checking out

For checking out, you need either a 12-volt battery or a supply that will give you a controlled 12 volts. If loading the supply causes the voltage to drop, you'll have to adjust accordingly, as current changes. Be very careful not to put excessive voltage onto the transistors when you take the load off (such as by turning off input signal). Don't forget that when you run the amplifier with signal on, it takes heavy current and when you remove the signal, current drops. Then voltage could rise and cause damage. To play it safe, cut off supply voltage *before* you reduce the input

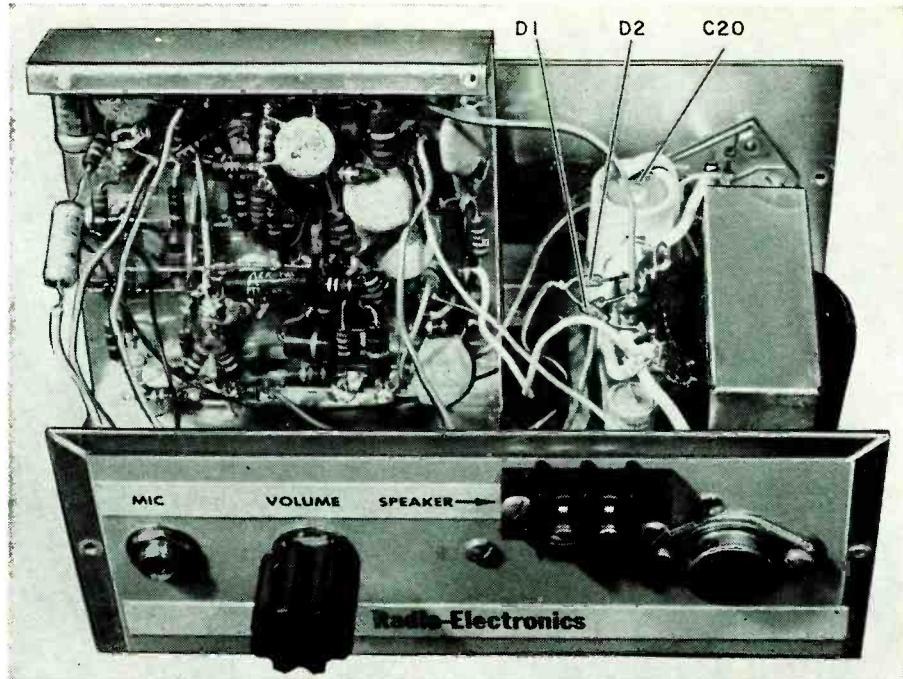



Fig. 5—Interconnecting sub- and main chassis takes only a few minutes.

signal.

Checking the amplifier with an oscilloscope and audio oscillator is more

fun, but it can be done without the oscillator and even without the scope. You do need a good vom. See that every-

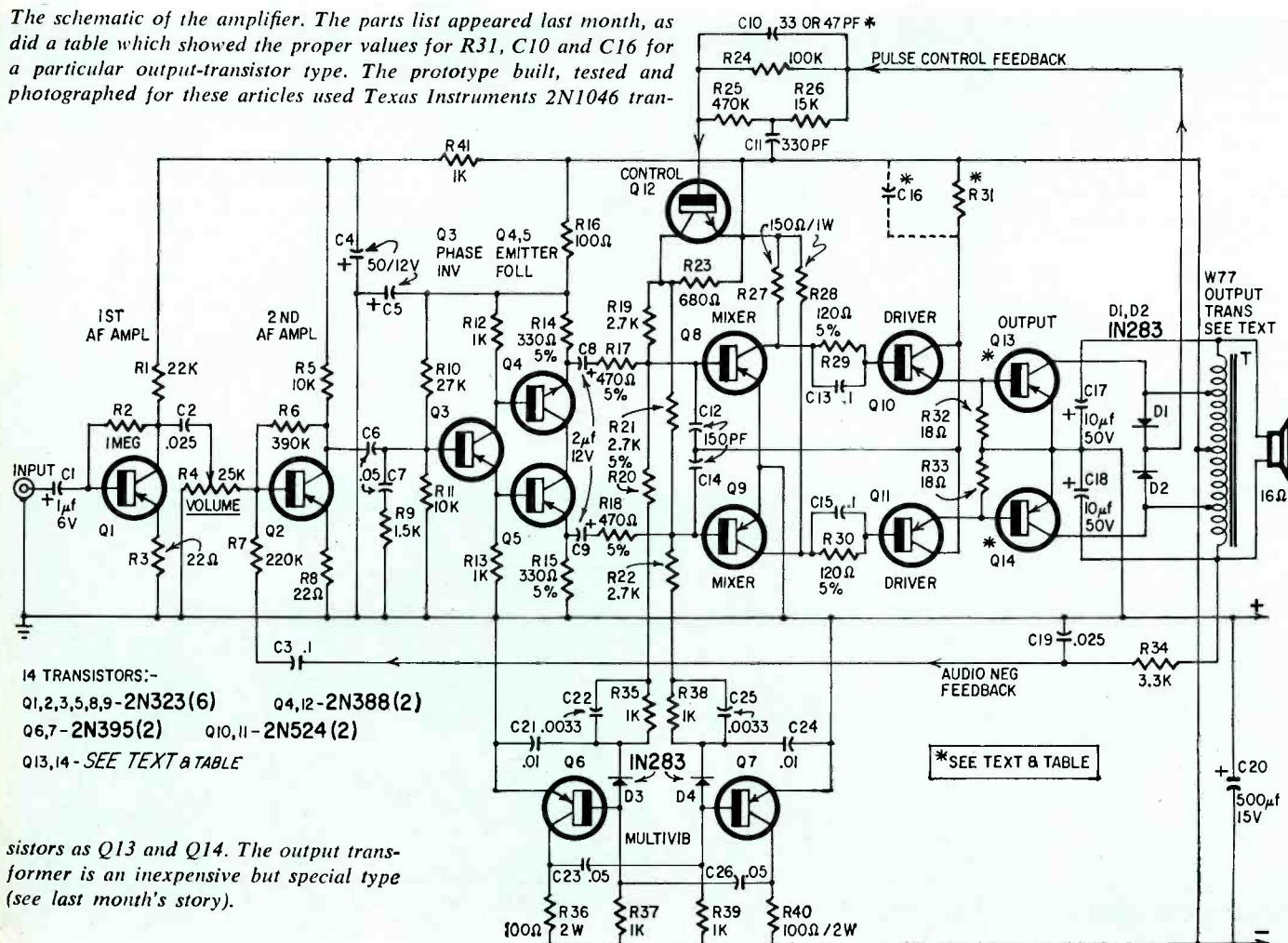The schematic of the amplifier. The parts list appeared last month, as did a table which showed the proper values for R31, C10 and C16 for a particular output-transistor type. The prototype built, tested and photographed for these articles used Texas Instruments 2N1046 trans-



sistors as Q13 and Q14. The output transformer is an inexpensive but special type (see last month's story).

thing is what it should be at each step, before proceeding. If it is not, look to see what has been done wrong, or if a component is faulty or off value, and correct it before proceeding.

First connect the two chassis together with a clip lead, and put a piece of paper or cardboard over the edge of the main chassis where the subchassis may touch it. The cases of the small transistors are "hot" (common to the collectors) and can cause shorts if they touch chassis. Connect your supply (*watch polarity!*) and, if you use a scope and oscillator, connect their grounds to the ground lug of the subchassis. Connect the oscillator through a voltage divider as shown in Fig. 7-a.

First get the multivibrator working. Insert Q6 and Q7 (2N395's). Adjust the supply to 12 volts. If the multivibrator is working, you should see waveforms as in Fig. 8-a at the collectors, and as in Fig. 8-b at their bases. At lugs 4 and 5 of TS1, waveforms should be as in Fig. 8-c. At the junction of C22, R20 and R35, it should be as in Fig. 8-d. (Ditto for junction of C25, R22 and R38.) If you don't have a scope, check the collector voltages. (See the voltage chart.)

Next check the pulse generating system. Insert Q8 and Q9 (2N323's) and check waveforms at their collectors, which should be as in Fig. 8-e. If you don't have a scope, remove one 2N395 (to stop the multivibrator) and the voltage at Q8 and Q9 collectors should be close to zero (measured to ground). Re-insert the 2N395, and the voltage should rise just a little (go more negative), showing that pulses are being formed.

Now check the phase splitter, Q3 (2N323). Check voltages: emitter should be about 2.5, collector 8, or thereabouts. Voltage at junction of R16 and C5 should be about 11.5. Now insert emitter followers Q4 (2N388) and Q5 (2N323). Voltage at the junction just mentioned should now be about 11, and the emitters of Q4 and Q5 should have voltages almost identical with the voltages on the collector and emitter, respectively, of Q3.

If you have scope and oscillator, check the whole audio section next. Insert Q1 and Q2 (2N323's) and check waveform at successive collectors. Check the action of the volume control and that waveforms at the collector of Q2, the emitter and collector of Q3 and the emitters of Q4 and Q5, are all of very nearly the same magnitude. They should also show overload at the same point as audio level is raised. If you don't have an oscillator or scope, check voltages: collector of Q1 should be around 5 volts, and collector of Q2 in same region. Neither is highly critical.

Now revert to pulse-system checking and for the time being remove Q1

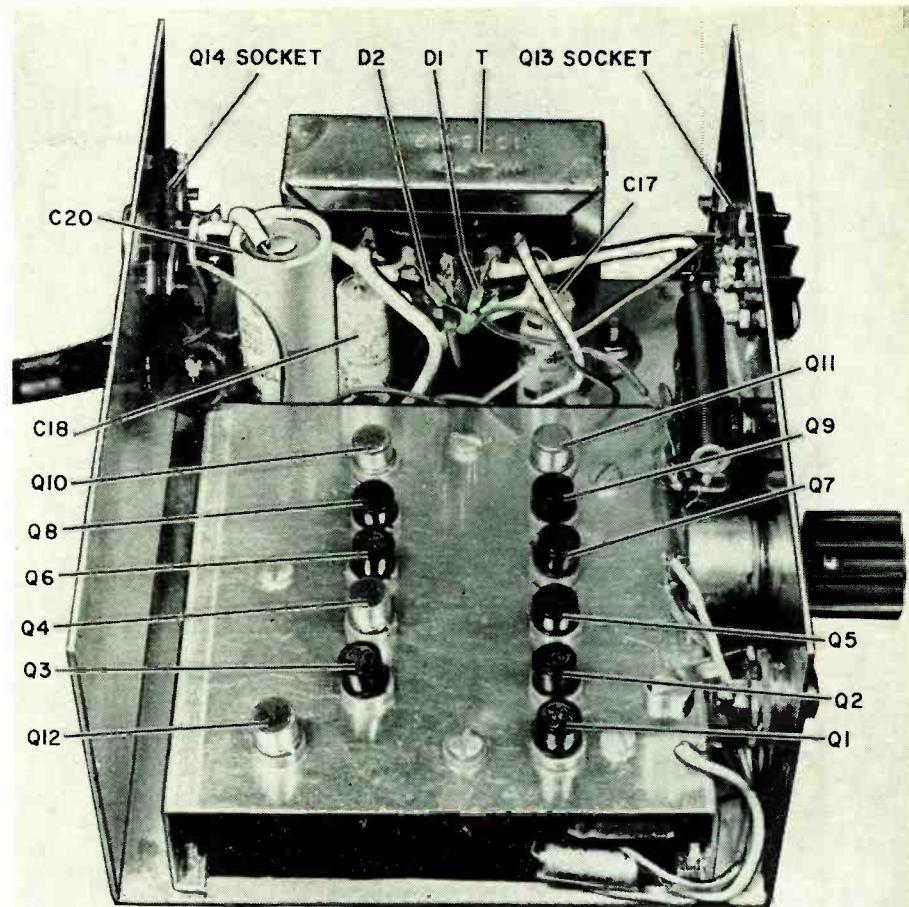


Fig. 6—This is how the amplifier looks with the subchassis wired and fastened down.

and Q2. Connect shorting wires between base and emitter of the output transistors (Q13 and Q14) and insert the drive transistors Q10 and Q11 (2N524's). If you look at the voltage at the collectors of Q10 and Q11 (which are paralleled and therefore the same), it should show both pulses, inverted as compared with those at the collectors of Q8 and Q9.

check pulses in closer detail. By going back to collectors of Q8 and Q9, you will be able to identify which pulse is which, because they will hold the same places, due to the way sync is locked.

If you don't have a scope, check voltage across R31 (this returns to the supply bus instead of to ground). With one 2N395 (Q6 or Q7) withdrawn it should be zero, and rise to a small value when the 2N395 is replaced.

If everything is OK so far, reinsert Q1 and Q2 and turn on some audio (the level at the input jack should be around 1 mv). On the scope, you should see the pulse modulated now, with multiple traces (Figs. 8-g and -h). You can look at this another way, by using the audio as the horizontal scope input (Fig. 9). Then the corresponding traces will look like Figs. 10-a and -b. If you want to check what each pulse modulator is doing separately, take your scope input from the collector of Q8 or Q9. One of the traces should look like Fig. 10-c and -d, and the other should be the same thing, but reversed left to right.

Phase of these scope traces can be improved by inserting some phase shift at the input (Fig. 7-b) and adjusting frequency to eliminate the loops. Then traces of Figs. 10-a through -d become those of Figs. 10-e through -h.

If everything checks OK this far, you can put in the output transistors

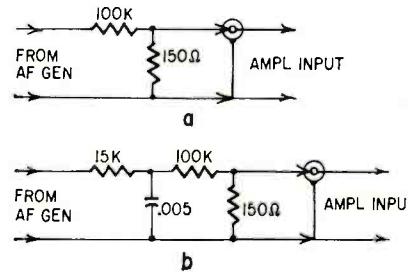


Fig. 7—Two input networks for testing.

From here, it is useful to use the scope's external sync connection. Connect it to lug 4 or 5 of terminal strip TS1. This will enable you to identify which pulse is which and to watch what happens when modulation is added (audio input) without having the trace jump all over the screen. If the pulses are uneven—in alternate pairs—but otherwise steady (Fig. 8-f), everything is fine. But if there is any jittering,

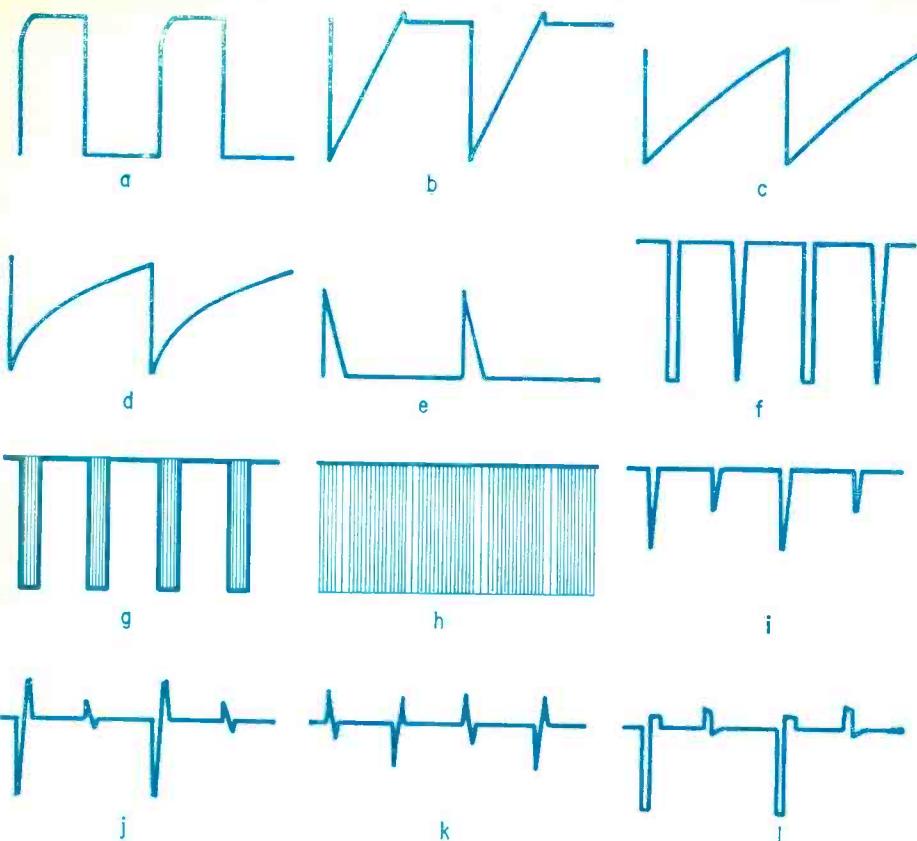


Fig. 8—Waveforms you should find at various circuit points. (See text.)

	VOLTAGE CHART													
	Q1	Q2	Q3	Q4	Q5	Q6	Q7	Q8	Q9	Q10	Q11	Q12	Q13	Q14
Emitter	<0.1	0.1	2.6	8.6	2.5	0	0	0	0	0.2	0.2	*	0	0
Base	0.1	0.2	2.8	8.4	2.7	-1.9	-1.5	0.3	0.3	*	*	*	0.2	0.2
Collector	4.6	4.0	8.4	2.6	2.6	5.8	4.8	0.6	0.6	*	*	*	12	12

All voltages are negative to ground bus except as indicated by minus signs, and rounded to nearest tenth. Variations of 10% either way are unimportant.

Voltages were measured with 20,000 Ω/v meter, no signal input, multivibrator oscillating, supply maintained at 12 volts.

*Depends on choice of output transistors and associated parts.

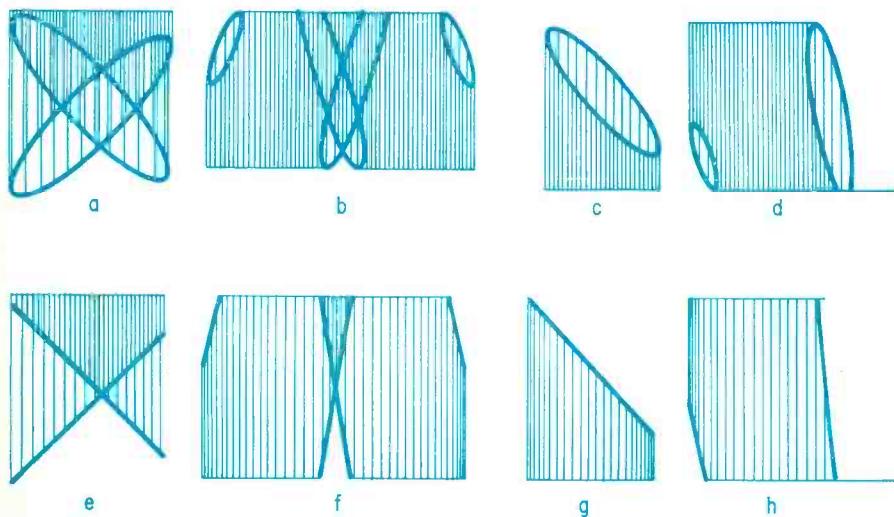


Fig. 10—Lissajous patterns, made with the setup of Fig. 9. (See text.)


and Q12 (2N388). But for the time being remove Q1 and Q2, before reconnecting voltage, and check pulse operation again. The pulse should be shortened and sharper at quiescent (Fig. 8-i). The waveform at the collectors of Q13 and Q14 should be as at Figs. 8-j and 8-k. Ideally, they should be identical, but inevitably there is a little difference. We show a typical pair of traces, using either 2N2832 or 2N1046 outputs. If you use 2N1905, the traces will be more like Fig. 8-l.

If you don't have a scope, the voltage across R31 should be lower than without the output transistors.

Now finish the job by putting in Q1 and Q2 again, and applying audio. The waveform on the collectors of Q13 and Q14 will be quite similar to that at the common collector of Q10 and Q11, except that there will be reflections.

A final check puts input against output and verifies loop gain characteristic. Take the scope vertical input from TS3-1 and the horizontal from the audio oscillator. This takes advantage of the feedback filtering to eliminate most of the pulses from the trace. You can also take the vertical from one side of the

Fig. 9—Connecting the amplifier for Lissajous patterns.

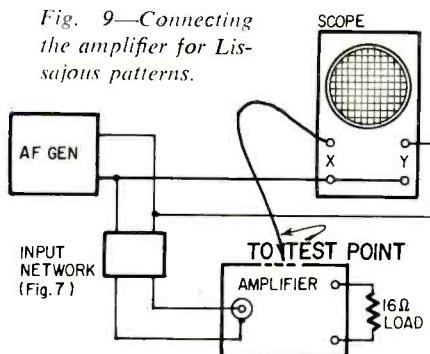

output load (16 ohms, for which use three 50-ohm 20-watt resistors in parallel, unless you have a 16-ohm 50-watt load handy).

Check gain reduction with feedback by lifting 0.1- μf capacitor C3 from lug 1 of TS3. This should raise gain by about 4 times. With feedback connected again, run frequency down to about 100 cycles and up to about 3 kc, having first set a 45° line on your scope at a middle frequency (somewhere between 500 and 1,000 cycles). The trace should go into an ellipse, without peaking (going higher than at mid-band) as it does so.

Finally, button the subchassis down. Lower it into place gently, taking care not to pinch wires or cause shorts. Insert and tighten the four No. 6 sheet-metal screws.

When you've checked the amplifier out with mike and speaker, you can mount the main chassis cover on the speaker frame and fasten the main chassis in its cover, and you're ready to go.

END

The Engineers' Right-Hand Men

By ERIC LESLIE

THOMAS LESKOSKI IS A QUALITY-CONTROL specialist at the Westinghouse TV-Radio Division in Metuchen, N.J. He built crystal sets as a schoolboy. On entering military service at 17, he went to electronics school and got a full year's training in the operation and repair of naval electronic equipment. He was a radio and radar repairman on navigational aids, ground-control-approach and similar equipment for 3 years. Upon discharge from the service, he studied electronics for two years at Newark Technical Institute, with the main accent on TV.

Tom put his schooling to use in local TV service shops, but soon decided that his future would be brighter if he went back to school. He enrolled in Seton Hall University and studied engineering for 2½ years, until he was forced to drop out for personal reasons. At about the same time, Westinghouse opened its assembly plant at Metuchen. Tom got a job as a quality-control inspector on electronic apparatus that Westinghouse was making for the Navy. Moving to TV when production started in the plant, he worked for a couple of years as an electronic troubleshooter on the assembly line.

Now, as a quality-control man, his work is varied, but essentially his job is to be certain that the products of the plant meet the established reliability standards. This sometimes calls for checking components or complete equipment under unusual environments. Products are taken off the line by ran-

Tester Thomas Leskoski puts a production sample of a clock radio through its paces in an rf-field-free "cage", to make sure it meets original specifications.



dom sampling and then compared carefully with engineering specifications to make sure they meet those specs, or, if they don't, to find out why and recommend corrections.

His responsibilities growing as the company grew, Tom has had several promotions, but he'd like to advance to more complex electronics. He feels that electronics offers "a great future to the young men coming out of school who can't get a college education," but points out that a good 2-year technical school—for a person with a strong interest in electronics—is an undeniable help.

Like most electronics men, Tom lives electronics even after hours; he spends much of his spare time with remote-control planes. He's married and lives in nearby North Brunswick (N.J.) but spends as much free time as possible at his vacation cottage in Maine.

Fred Hoffman, another employee at the Westinghouse Metuchen plant, is called a *lab specialist*. Like many other radio technicians, Fred's interest in radio started while he was still in his pre-teens, working over old tuned-radio-frequency receivers. His father worked for a transformer manufacturer and there were always a number of sets and parts of sets around the house. During high school he had a cellar workbench shop, complete with a signal generator, and repaired neighbors' sets for spending money.

While still in school he started with Acme Electric Co., a transformer manufacturer in Cuba, N.Y., working in the engineering department after school and during summers. On gradu-

ating from high school, he took a steady job with Acme for about 2 years. Entering the Navy in 1948, he went through a 42-week accelerated course in the Navy electronics school, afterward spending 3 years aboard the repair ship Yosemite, working on radar, loran and other complex electronic equipment.

Fred was discharged from the Navy in 1952 and worked about a year at Bell Aircraft, Buffalo, N.Y., in the components group. Most of the work was designing test equipment for missile checkouts. On the recommendation of a friend from Acme, during a vacation he came to Metuchen to investigate the possibilities of working at Westinghouse. Starting that same year (1953) as a lab technician, he worked about 5 years with Westinghouse, then took a position in neighboring New Brunswick with a communications maintenance company (Mobile Radio Dispatch) which service police, fire, marine and industrial communications equipment. The company closed out its New Brunswick branch, however, and Fred soon returned to Westinghouse.

Fred's present position is halfway between that of engineer and technician. He works chiefly on new designs and prototypes. He checks out and improves circuit designs, and tests and measures new materials and components. He has done basic color TV research and worked with "transistors when they were new." He is taking a mathematics course at Rutgers, hoping at last to become an engineer. At home, he relaxes with photography and amateur radio (Technician class). Fred is married and lives in East Brunswick, N.J. END



Another of Tom's jobs: watch over dozens of TV sets in a life test and check each set regularly; failures are recorded, analyzed to see whether a pattern appears.

A Reliable Transistor Tachometer

This 3-transistor instrument is inexpensive and yet surmounts most of other units' disadvantages—temperature and voltage sensitivity, excessive dependence on pulse characteristics

By STEPHEN GROSS

HERE AT LAST IS A TACHOMETER CIRCUIT insensitive to variations in input, pulse width, amplitude, rise time and noise content. A voltage-regulating circuit minimizes the circuit's sensitivity to variations in battery voltage, and a temperature-sensing device (theristor) corrects for circuit drift due to temperature change.

An ignition pulse contains much noise and ringing due to point bounce and the inductive reactance of the spark coil. It also varies in amplitude, rise time and width as engine speed changes. The voltage available to operate the tachometer will also vary as the engine speed and electrical load changes. Changes in the ambient temperature will also produce an error. If the tachometer is to be a reliable working instrument, it should maintain an accuracy of at least 5% under all operating conditions.


The schematic of the transistorized tachometer is Fig. 1. Low-voltage ignition pulses, from the points, are applied to the filter (R1, R2, R3, C1 and C2), which eliminates much of the noise due to contact bounce and inductance. The filtered signal goes to the amplifier and wave shaper (Q1, Q2), where the power level of the signal is increased, and a signal is generated which is independent of input pulse rise time, amplitude and width. The output of the amplifier and wave shaper goes to the power amplifier (Q3), where the power level of the signal is further increased. The output of Q3 is displayed on the meter. Capacitor C4 helps integrate the pulses.

A calibrating potentiometer (R7) is included in the power amplifier stage. Its use is discussed in the calibration section.

Circuit operation

With no pulse present, the base of Q1 is at ground potential. The emitter-to-collector impedance of Q1 is then large. Thus, current flows into the base of Q2 through diode D1, since D1 is forward-biased. R4 is chosen so that under these conditions Q2 is saturated. The voltage on the collector of Q2 will be about 0.5. D4 clamps the input pulse.

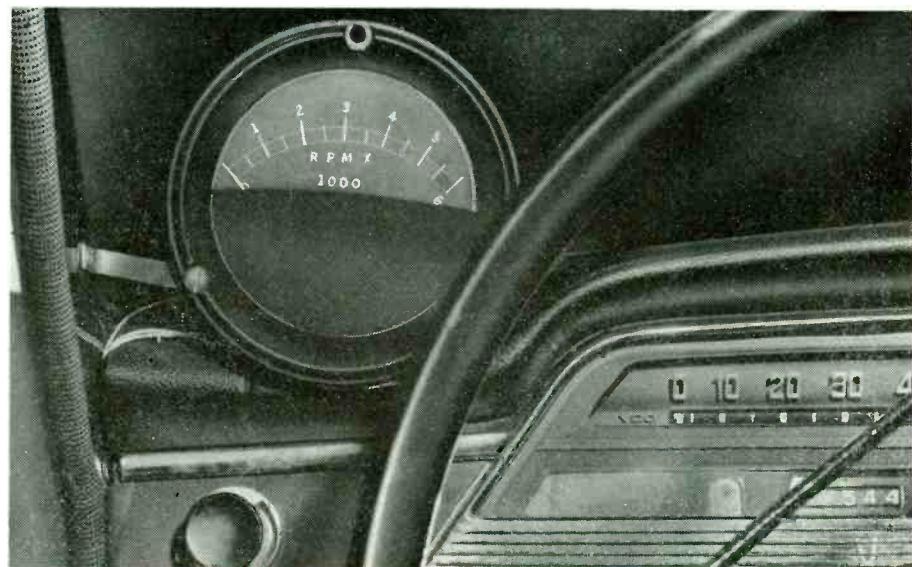The Q1 stage is so designed that an input of 4 volts or more will completely saturate the transistor. When a



Tach indicator mounted in corner of windshield in author's Volvo.

positive pulse arrives at the base of Q1, current flows into the base, causing its emitter-to-collector impedance to decrease. Thus, the current allowed to flow into the base of Q2 can no longer keep D1 forward-biased. At this point, the impedance of D1 becomes high and reduces the current flowing into the base of Q2. The alpha of Q2 falls, its emitter-to-collector impedance becomes large and collector voltage rises to V_{cc} .

Because of the nonlinear diode characteristics, a small change in the impedance of Q1 causes a large change in the impedance of D1. Thus, the time required for D1 to switch is relatively independent of the rise time of the input ignition pulse. The time Q_2 takes to switch from its low-impedance to its high-impedance state depends primarily on how fast diode D1 switches from low impedance to high. Thus the out-

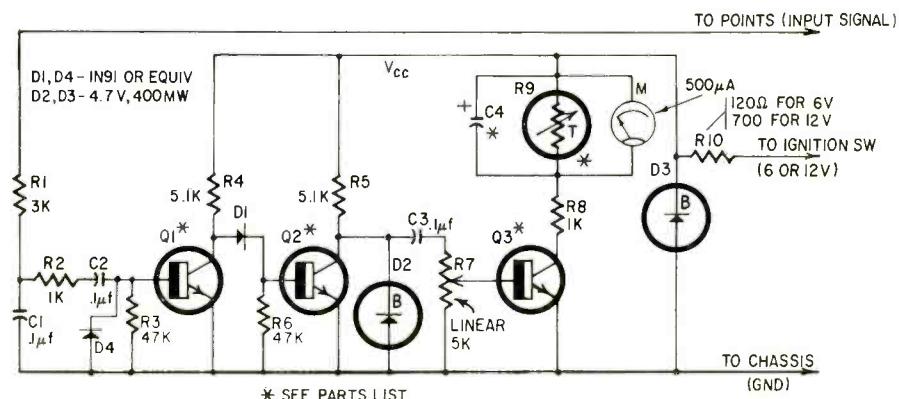


Fig. 1—Circuit of the reliable tach. Note well that C_3 is $0.025 \mu\text{f}$, not $0.1 \mu\text{f}$.

C1, C2— $0.1 \mu\text{f}$
C3— $0.025 \mu\text{f}$
C4—20 to $200 \mu\text{f}$, 15 volts, electrolytic
D1, D4—50-volt germanium rectifier (G-E 1N91 or equivalent)
D2, D3—4.7-volt, 400-mw Zener diode (Int. Rect., TI or Hughes 1N750 or equivalent)
M—500- μA meter
Q1, Q2, Q3—general-purpose n-p-n transistors, minimum $\beta = 20$, minimum $V_{CE(sat)} = 15$ volts (2N339, 2N1302, 2N696). For positive-ground electrical systems, use equivalent p-n-p transistors

R1—3,300 ohms
R2—1,000 ohms
R3, R6—47,000 ohms
R4, R5—5,100 ohms, 5%
R7—5,000 ohms, pot, linear taper
R8—1,100 ohms
R9—Thermistor: 3,000 ohms @ 25°C , temp. coeff. .04 (Fenwal JA33J1 or equivalent)
R10—120 ohms for 6-volt battery, 700 ohms for 12-volt battery
All resistors $1/2$ watt, 10% unless specified
Perforated boards, aluminum box, miscellaneous hardware

put-pulse rise time is relatively independent of the input-pulse rise time.

The pulse appearing at the collector of Q2 is limited by Zener diode D2 and differentiated by C3 and R7. By differentiating the collector waveshape, we generate a drive for Q3 that is independent of the width of the ignition pulse, and further isolate any effects of input variation. The base of Q3 is driven by the waveform at the wiper arm of calibrating pot R7. Q3 acts as a current amplifier and drives meter M, which acts as an integrator. Capacitor C4 maintains the integrating properties of the meter at low pulse-repetition rates.

As the ambient temperature of the circuit increases, the gain of Q3 increases, causing a reading on the meter greater than the true rpm. Thermistor R9 is a temperature-sensitive resistor with a negative thermal coefficient of resistance. As it heats, its resistance decreases, loading the meter and effectively canceling the effects of temperature change.

Zener diode D3 and resistor R10 form a voltage-regulating circuit which maintains a constant supply voltage to the rest of the tachometer circuit.


Construction

The circuit was built on two phenolic boards (Vector type), each $1\frac{3}{4}$ x $2\frac{3}{4}$ inches. The boards were then mounted in a small $1 \times 2 \times 3$ -inch aluminum box for protection. Instead of using a connector as I did, you can pass the leads through a hole in the box.

The external electrical connections are simple. The 6-volt lead is connected to the battery through the ignition switch; the ground is connected to the chassis of the vehicle, and the signal lead is connected to the side of the points tied to the coil. Two unshielded leads, as long as needed, are connected to the meter.

The circuit is designed so that variations in the characteristics of the semiconductors have little effect on operation. Any general-purpose n-p-n audio transistors, any germanium diodes and

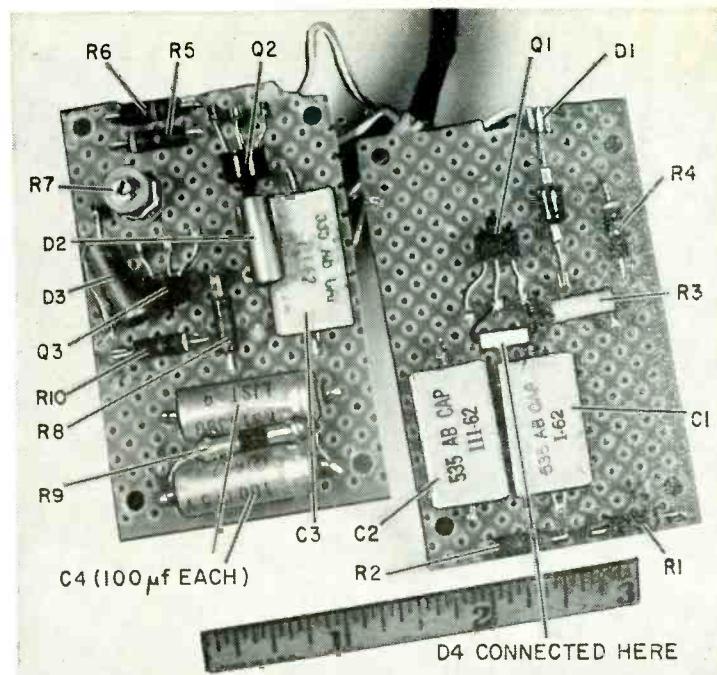Two small perforated phenolic boards carry all parts except the meter. Layout is optional; leads can be practically any length. D4 was added, as shown, to improve performance.



4.7-v Zener diodes may be used. However, if the circuit is to be installed in a vehicle with a positive ground (circuit shown is for a negative ground), p-n-p transistors will be needed. In addition, for positive ground, the connections to D1, D2, D3, D4, M and C4 must be reversed. For a 12-volt ignition system, R10 must be changed to 700 ohms. The rest of the circuit remains the same. Component placement is not critical.

Calibration

The unit may be calibrated by using a sine-wave, square-wave or pulse generator. In any case, the input amplitude to the filter section must be set so that further increase in amplitude has no effect on the meter reading. The pulse-repetition frequency of the input is then set to correspond to the rpm at which full-scale deflection is desired. This frequency (f) may be calculated by using the formula $2N \times \text{rpm} / 60C$, where rpm is desired full-scale reading in rpm, N is number of cylinders, and

C is 2 for a two-cycle engine and 4 for a four-cycle engine.

With this signal supplied to the input of the filter, scaling potentiometer R7 is adjusted for full-scale deflection of the meter.

Stability

Much effort was expended to minimize meter variation with changing temperature, ignition pulse and bias voltage. A known pulse-repetition frequency was supplied to the circuit and, with the formula, converted to an rpm reading. The supply voltage was varied and the error* between the true rpm reading (from the formula) and that observed on the meter recorded. The supply voltage was then fixed and the unit subjected to changes in temperature. Again the error between true rpm and observed rpm was recorded. The results of these tests are shown in Fig. 2-a and 2-b. Over the voltage range from 5.7 to 7.0 and temperature range of 38°F to 120°F, the meter indicator has a stability of better than 5%. Varying the input pulse width, rise time or amplitude produces no variation in the meter deflection.

In operation, the entire unit draws 100 ma when using the Zener voltage-regulating stage. This is only 0.6 watt out of the 300 the average auto system is capable of supplying. It is recommended that the circuit be mounted under the dashboard near the heater, since the temperature variation there is usually less throughout the year than in other locations during operation of the vehicle.

END

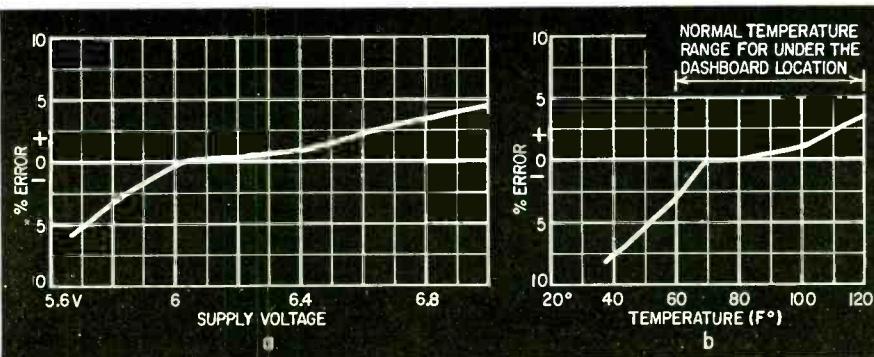


Fig. 2—a—Percent error between indicated and true rpm versus supply voltage.
b—Percent error between indicated and true rpm versus temperature.

$$* \text{Error} = \frac{\text{rpm}_T - \text{rpm}_I}{\text{rpm}_T} \times 100$$

rpm_T = true rpm (computed from formula)
rpm_I = rpm indicated on meter

WHAT'S A DELAY LINE?

Delay lines crop up in color TV, hi-fi audio, computers, radar and hundreds of other applications. Read what they are and how they're used

By ARTHUR S. KRAMER

YOU MAY BE ASTONISHED TO LEARN that many of our most sophisticated electronic devices could never have been perfected without delay lines. Color TV, radar target simulators, radar moving-target indicators (MTI), several types of digital computers, and many others would be unbelievably crude or completely impractical if delay lines didn't exist. What is a delay line?

A delay line is basically a transmission line compressed into a small volume. Its function is to delay information for a specific length of time, usually in the microsecond range.

You might well ask, "Why slow down an electronic signal?" The reason is that it enables you to compare the delayed signal with a later one, or to make another check on the delayed signal, using proper instrumentation. Or it may be used—as in color TV—to keep two signals in step, though one has to travel a longer circuit path than the other.

The whole field of delay lines can be broken down into three broad categories: *high-frequency ultrasonic*, *ultrasonic wire* and *electromagnetic*. These broad categories can be further subdivided.

In Fig. 1 is shown a distributed-constant electromechanical delay line

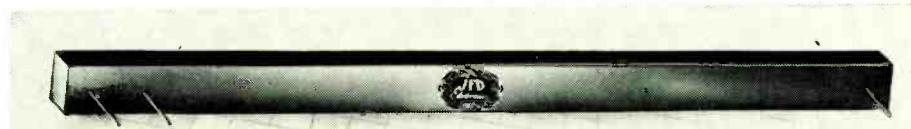


Fig. 1—A distributed-constant electromechanical delay line.

JFD

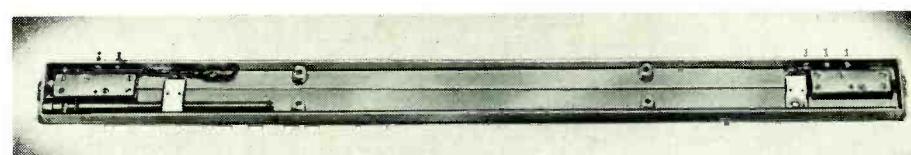


Fig. 2—Long-wire magnetostrictive delay line.

ESC Electronics

suitable for printed-circuit mounting. It comes in sizes from 2 in. long to 6½ in. long, and from .05 to 1.1 μ sec in delay. A long-wire magnetostrictive (ultrasonic wire) type is pictured in Fig. 2. Delay of this model is 80 μ sec, working in the longitudinal mode. A third type, a high-frequency ultrasonic type, is shown in Fig. 3. Two piezoelectric transducers are shown attached to the glass block. These serve as the input and output circuits.

You can specify resistors in ohms and watts, capacitors in farads and volts. How do you specify delay lines?

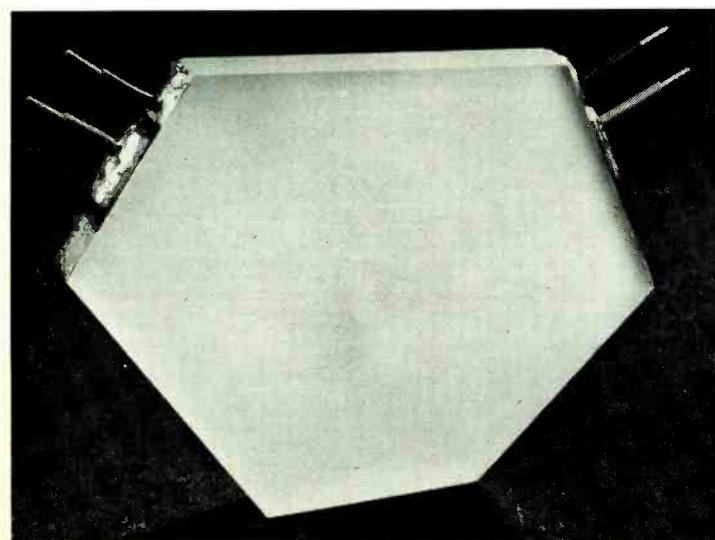


Fig. 3—Glass ultrasonic delay line. Connections are made to pairs of pins on opposite faces.

Corning Glass Works

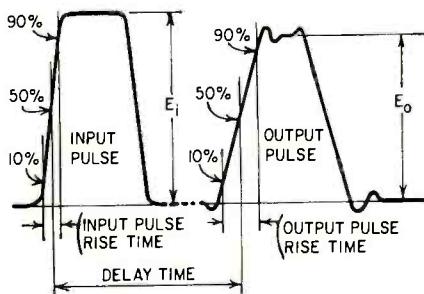


Fig. 4—Pulse waveforms help define some delay-line terms.

Some of the terms used are:

Delay time. The elapsed time between the 50% amplitude points of the input-pulse leading edge and the output-pulse leading edge. (See Fig. 4.)

Rise time. The elapsed time between the 10% and 90% amplitude levels of the leading edge of the output pulse.

Characteristic impedance. Just as in other transmission lines, this is equal to the value of terminating impedance that results in minimum power reflected to the input of the delay line.

Attenuation. The difference in amplitude between the input and output pulses when the delay line is terminated in its characteristic impedance. It can be expressed in db as

$$\text{atten} = 20 \log_{10} \frac{E_i}{E_o}$$

E_i , E_o are input and output amplitudes,



Fig. 5—Simplest magnetostriuctive delay line.

respectively, and must be expressed in the same units.

Longitudinal mode. This is a mode of operation in a magnetostriuctive line in which sound waves are propagated along a wire from one end to the other by the sonic expansion and contraction of waves in the wire. It is similar to the way sound waves travel along a pipe hit on the end with a hammer.

Torsional mode. A mode of operation in a magnetostriuctive line in which sound waves are propagated along a wire by a twisting or torsional stress on the wire. The mechanical stress waves are transferred along the wire in a helical or spiral mode to the other end of the wire. This is similar to turning a length of pipe with a wrench at one end and noting that the pipe tends to revolve about its long axis.

Storage capacity. The number of binary digits (bits) that can be stored on a line is called its "storage capacity."

Center frequency. The mid-frequency of the delay-line frequency range or response is called "center frequency."

Now just how do these different delay lines work?

Magnetostriuctive type

The simplest possible magnetostriuctive delay line that could be built is diagrammed in Fig. 5. It consists of an input transducer coil with a magnetostriuctive core attached to a wire sonic waveguide. A similar transducer is attached to the output end. Sound waves travel at a much lower velocity than do electrical waves. The incoming electrical wave is converted to a sound wave, and travels down the line in the "longitudinal mode." This sound wave is reconverted to an electrical wave at the output end. The delay is proportional to the length of the line.

Glass type

Here, the input transducer transmits a mechanical vibration through a glass block when energized by an electrical signal. At the output, the vibration is reconverted to electricity. Again, delay is proportional to the length of the path taken by the mechanical signal as it travels through the glass.

Photoelastic type

This type is becoming increasingly important. Optical properties of certain kinds of glass vary with mechanical stress. The input to this delay line is through a conventional piezoelectric (crystal or ceramic) transducer, but the output is fed into an optical arrangement. Because the refractive index (light-bending property) of the glass block varies with electrical input signals, optical signals (modulated or chopped beams) passed through the glass will be delayed in accordance with the electrical input signal. Advantages of this type are that the output circuit requires no direct mechanical connection and the line can be "tapped" for intermediate values of delay without affecting the acoustical signal.

How delay lines are used

Anyone who lives in an area over which aircraft fly has experienced the annoyance of "aircraft Doppler" on his TV screen. In my own case, before I can even hear the aircraft, my picture goes slowly in and out of focus. This is followed by severe ghosts and, at times, the vertical sync is lost and the picture shifts rapidly up or down. Occasionally, the picture is badly torn for a short period.

Some work has been done in England to improve TV receivers so that this annoyance will be eliminated. Since Doppler signals from aircraft are

not always available, a device to generate these signals has been developed. It uses sonic delay lines as shown in the partial block diagram of Fig. 6, and is capable of generating a picture like that shown in Fig. 7-a.

To simulate the Doppler effect realistically, the delay line is made variable and its delay control is motor-driven so that the delayed signal slides in and out of phase with the direct signal. Fig. 7-b shows a test pattern with a delay of 120 μ sec, having equal amplitudes of direct and delayed signal.

Delay lines in color TV sets

Delay lines are essential to the proper operation of a color receiver. The rectified video signal is separated into its brightness and color components at some point after the video detector. These brightness and color components are amplified separately and then fed to a


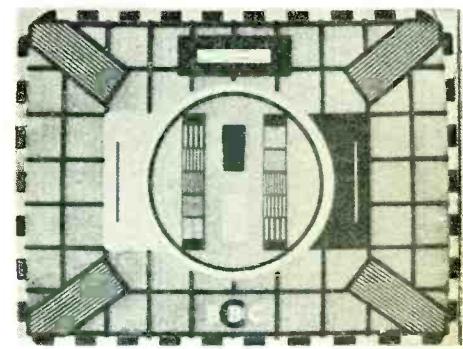


Fig. 7-a (above)—Original signal. (b, below) Signal with shift of 120 μ sec.

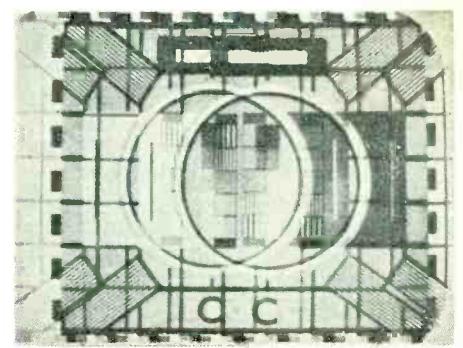

Electronic Engineering

matrix network where they recombine with each other to produce the red, green and blue signal voltages that modulate the color CRT. For good color reproduction, the brightness and color signals must arrive at the matrix within about .05 μ sec of each other.

The amplifiers used for the color and brightness signals have different inherent time delays—the narrower the bandpass of the circuit, the longer it takes a signal to pass through. A delay line is inserted in the brightness (video) amplifier chain so these signals arrive at the color matrix

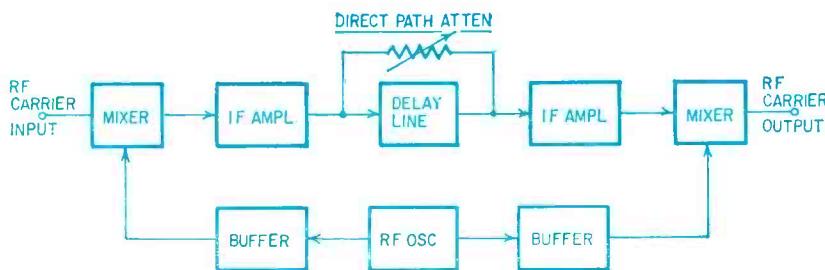


Fig. 6—Aircraft simulator uses delay line to cause doppler-like shift to help study effects on TV reception.

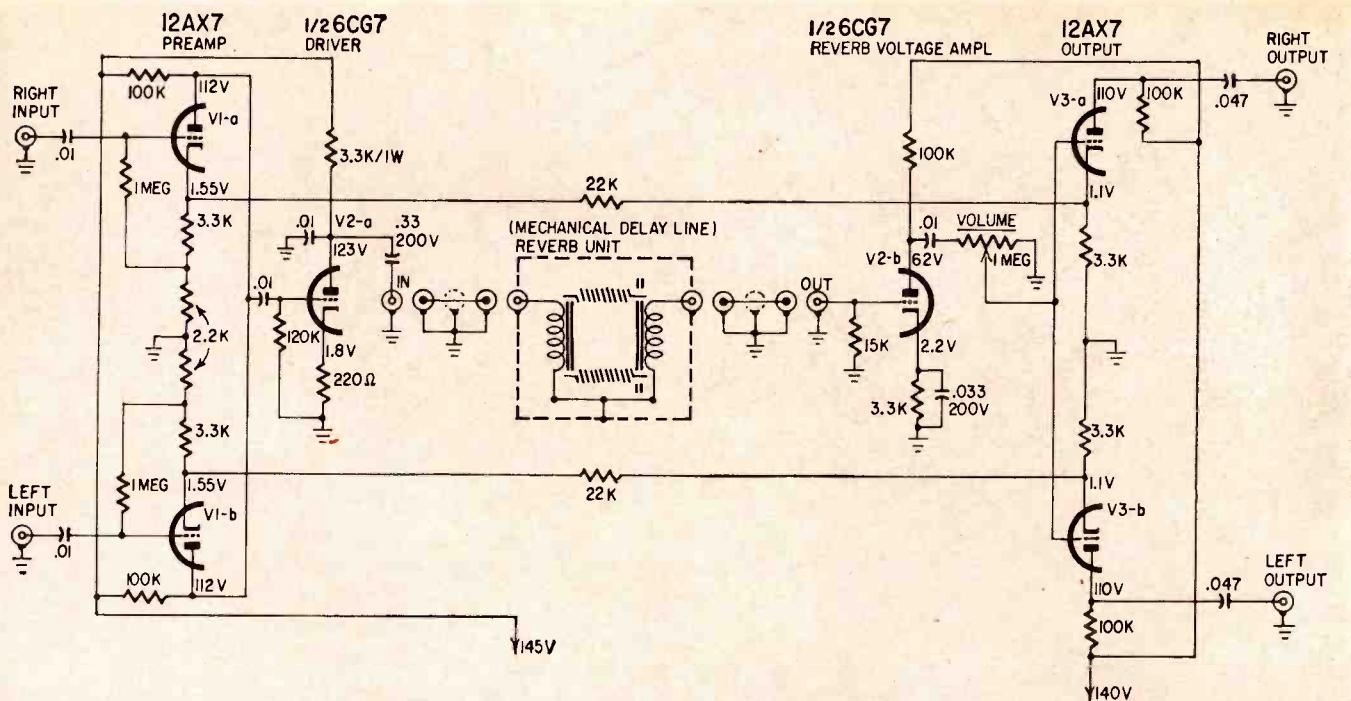


Fig. 8—Artificial reverb portion of Philco hi-fi system uses mechanical delay. Sum of left and right channels is fed through amp-

ifier and electromechanical delay line. Delayed signal is mixed with left and right channels to simulate acoustic reverberation.

at the same time as the slower color signal.

The delay line may be a lumped-constant network, a coil of wire with specific inductance and capacitance values or a length of special type of coax.

Home sound reverberation system

Fig. 8 is a schematic of a special audio amplifier for simulating reverberation effects. The direct path for audio signals is from cathode to cathode of the two sections of each 12AX7, and out to the 12AX7 plate outputs and the output terminals. The right and left signals are mixed in V2-a, amplified and fed through the delay line, through V2-b, and then into the grids of V3-a and V3-b. By varying the pot in V3's grids, the amount of reverberation can be closely controlled for greatest realism.

In a computer application, a delay line adds 50 μ sec delay to the amplifier chain, and is a hermetically sealed ultrasonic type.

Radar applications

One of the earliest, and still one of the most important, applications for delay lines is in MTI (moving-target indicators). This technique is based on two discrete radar scans, one delayed so that it arrives at the indicator at the same time as a second scan. If the indicator is equipped to cancel out information which has not changed between scans, only moving targets will be seen.

This technique is very valuable for tracking aircraft and ships.

For ranging markers, a line of precisely measured delay is used to calibrate a radar sweep. A part of the transmitted pulse is fed into the radar receiver through the delay line. This will cause marker blips to appear on the display at a distance exactly equivalent to the delay of the line.

Often it is desirable to have available a group of pulses that can be used to simulate radar targets that are moving, fixed or moving superimposed on fixed. This can be done with a radar test set by using delay lines to generate simulated echo pulses. The rf signal from the system under test is heterodyned to an i.f. signal which can drive the delay line. The delay line drives another amplifier, which in turn feeds back a portion of the delayed signal to the i.f. amplifier which drives the delay line. The output is the desired group of pulses.

My thanks to the following companies, without whose assistance this article could not have been written: Arenberg Ultrasonic Laboratory; Laboratory for Electronics; Corning Glass Works; Deltime, Inc.; JFD Electronics Corp.; Gray and Kuhn Div., Burnell and Co.; Columbia Technical Corp.; Philco Corp.; Tempo Instrument, Inc.; Control Electronics, Inc.; ESC Electronics Corp.; Consolidated Avionics, and the editors of *Electronic Engineering* of London, England.

COMPANY SUPPLIES

PACKAGE TV STATIONS

FOR INEXPERIENCED OWNERS

Electronics Leasing Corp. has joined with Kamen Associates, a design-marketing consulting group, to make a new proposal to assist "the little guy who wants to get into TV but is frightened and bewildered." It would supply him with a complete TV station ready to go on the air, would provide and train the staff and even obtain programming (which would be supplied to a group of stations).

According to Ira Kamen, president of Kamen Associates, the problem of obtaining legal and engineering services, dealing with contractors, etc., scares off many small community groups and others who might need a station but lack experience. By telling a would-be broadcaster beforehand exactly what costs would be and supplying him with a going station, Kamen believes many who now would not attempt to enter the field will no longer be afraid of the numerous unknowns facing the novice going into television. A further attraction is that the stations would be supplied on monthly payments (\$2,000-\$5,000 monthly). Arrangements would be made by the individual communities to continue on a leasing basis or eventually to purchase the station.



New Concept in Color Bar Generators

Tiny, versatile, battery-powered color test generator is small enough to be carried anywhere and offers a number of new, extra-useful signals

By WALTER CERVENY*

THIS NEW GENERATOR IS SO SMALL AND light that it can be carried in a conventional tube caddy. It is completely transistorized and is battery- or ac-operated. The power required for operation is approximately $\frac{3}{10}$ watt—less power than a flashlight lamp takes.

One major problem in color bar generators has been loss of timer synchronization. This problem, among others, has been overcome in the Amphenol Color Commander.

Patterns and how they're used

The centering pattern. It consists of single horizontal and vertical lines, as seen in the first switch position (lower left pattern in the photograph). The horizontal and vertical crossbars are generated in proper time placement to appear in the electrical center of the pattern when the raster is properly centered. The slight differences in blanking time between the generator blanking and standard broadcast blanking, which

might cause an error, have been compensated with delaying networks.

The prime purpose of this pattern is to enable the service technician to center the raster accurately before starting convergence. Centering after convergence can cause misconvergence.

The second most important function of the single cross-bars is in dynamic convergence. Most TV manufacturers' alignment instructions call for a crosshatch pattern for initial dynamic convergence alignment. The instructions call for picking a vertical line in the center of the screen when starting the dynamic vertical convergence adjustment. With the single cross-bar pattern, this adjustment is easier since only one vertical line is present in the center of the screen.

The single dot. This vitally important pattern (second switch position in photo) is entirely new and not found in any other generator. The accuracy of convergence alignment depends on the initial setting of static convergence in the center of the raster. Normally, this is set with a multiple-dot pattern. The operator selects dots near the center of

the screen and makes his adjustments there. This is a very broad and inaccurate adjustment, since it's difficult to concentrate on a single dot when other dots are present. With only a single dot, in the exact center of the screen, the adjustment can be made very simply and accurately.

The single vertical and horizontal bars (positions 3 and 4) are used in connection with the standard vertical and horizontal bar patterns in dynamic convergence. Where the technician is asked to concentrate on a single vertical or horizontal bar at the center of the screen, he switches in these patterns and is not distracted by the other bars.

The crosshatch pattern. Although this kind of pattern is not new, the one generated by the Color Commander contains many desirable features: a 4 to 3 aspect ratio, finer lines and closer-spaced lines. The pattern contains 20 vertical and 15 horizontal lines. With an aspect ratio of 4 to 3, the height and width or proportioning adjustments are made easily; the operator merely adjusts the controls for perfect squares over the entire screen.

The lines are extremely fine—approximately one scanning line wide. The pulses that produce the lines have short rise and fall times, yet are not steep enough to ring the receiver circuits. The horizontal lines start and end in the blanking region, so there is no discontinuity in the lines. In some other generators, the horizontal lines start and end on the screen, making convergence adjustments difficult.

Some generators produce lines from pulses that have long rise and fall times. Then the brightness control must be set to minimum to produce fine lines and the convergence adjustments must be made in practically total darkness. When the set is tuned to a station with the controls set to normal, convergence adjustments are off slightly. This is due to small differences in beam deflection at various beam current levels.

Another unique feature of this generator is that it enables the service technician to set the fine tuning properly and accurately. In the crosshatch position, the vertical line pulses are adjusted to a lower amplitude than the horizontal line pulses. This is done at the factory during calibration.

The vertical line frequency is 315 kc and contains high-frequency components up to 3 mc. The horizontal line frequency is 450 cycles. Thus the vertical line frequency when modulated on a picture carrier frequency will generate high-frequency sidebands, approximately 315 kc to 3 mc either side of the carrier. The horizontal line frequency, being much lower, will generate lower frequency sidebands immediately adjacent the carrier. The Color Commander

*Vice president, Engineering, Cadre Division, Amphenol Corp.

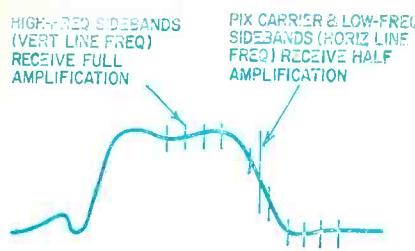



Fig. 1—Automatic fine-tuning adjustment is based on correct amplitude relationship of vertical and horizontal pulses. When vertical and horizontal lines are equally bright on screen, fine tuning is correct.

rf output contains double sidebands along with the picture carrier. Thus, when the fine tuning is adjusted so that the vertical and horizontal lines are the same brightness or intensity on the face of the picture tube, the picture carrier will be set halfway down on the i.f. response curve. The reason for this is immediately evident in Fig. 1.

This shows that the lower-frequency sidebands (horizontal line frequency) are amplified less than the high-frequency sidebands (vertical line frequency). Therefore, when the horizontal- and vertical-line pulse amplitudes are in the proper ratio, the receiver can be fine-tuned simply and accurately without a sound carrier. Once the fine tuning is set with the crosshatch pattern, it will not have to be reset for the color pattern.

The multiple-dot pattern also has an aspect ratio of 4 to 3 and contains 300 dots, less those lost in the blanking region. The chief use of this pattern is for critical inspection of convergence alignment when the job is done. The dot pattern can be used for convergence alignment, though the vertical and horizontal line patterns are somewhat easier to work with.

The horizontal and vertical line patterns are standard and are used in-

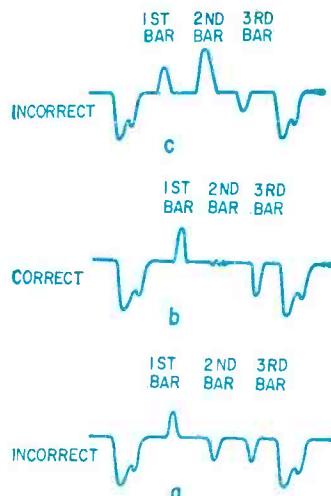

Figs. 2-a and 2-c are incorrect waveforms; second bar should be suppressed as in 2-b.

dividually in convergence alignment where the service technician prefers to view only the vertical lines during vertical convergence and only the horizontal lines for horizontal convergence. However, some technicians prefer to use the crosshatch pattern, so that, if interaction does occur, it is immediately evident.

The color bar pattern generated by the Color Commander is new and not found in any other color bar generator. It was designed to make color adjustments very simple. The generator produces three color bars on the screen: R-Y, B-Y and -R-Y or, in color phase, respectively, 90°, 180° and 270°.


The first two bars (R-Y and B-Y) are used for demodulation alignment. The third bar is used to check the range of the hue control and to preset the hue control accurately to the proper phase before a broadcast color transmission.

The color adjustments can be made with or without an oscilloscope. The scope method is usually used in the shop. This is how it's used:

First, the fine tuning has to be set properly. This is done by switching the Color Commander to the crosshatch position and adjusting the fine-tuning control so that the vertical and horizontal lines have the same intensity. This insures that the picture carrier is tuned halfway down on the i.f. response. It also places the color subcarrier in its proper location on the i.f. response curve. The conditions are now correct for color alignment. The generator is then switched to the color bar position. The hue and color saturation controls are adjusted to midposition.

Three color bars should be seen. (If color locking circuits are not operating properly—lack of color or movement of color through the bars—readjust the locking circuits according to the TV manufacturer's alignment instructions.) Connect the vertical input of the scope to the red grid terminal of the color picture tube. The scope sweep and triggering controls are adjusted to stop one 15,750-cycle waveform. Typical waveforms are shown in Figs. 2-a, -b and -c. With the hue controls in the center of its range, the coarse R-Y adjustments are made so the middle bar as shown in Fig. 2-b is at base line level. The scope input is then switched to the blue grid. The B-Y or quadrature adjustment is then made so that the first and last bars are at base line levels (Fig. 3-b).

Some TV receivers do not have provisions for adjusting B-Y demodulator phase—the adjustment is fixed. However, this method can be used to verify that the fixed phase-shift network is proper. The alignment is now complete since the G-Y output is matrixed from R-Y and B-Y and does not re-

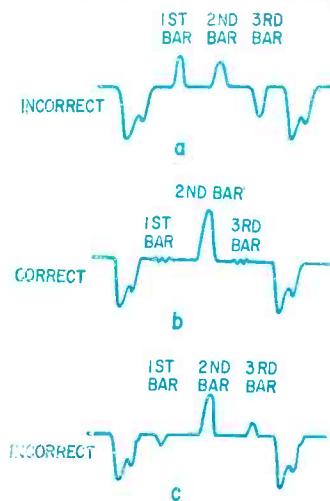

Figs. 3-a and 3-c are incorrect waveforms; first and third bars should be suppressed as in Fig. 3-b.

quire adjustment. However, if the oscilloscope is connected to the green grid, the waveform of Fig. 4 should be seen if the G-Y channel is operating properly.

The other method of alignment does not require a scope and therefore can be made in the customer's home:

The fine-tuning control is adjusted as in the scope method. The hue and saturation controls are set to midposition. Screen controls on the blue and green guns are turned to minimum to cut off the guns. The screen should have a dark red background. With the hue control at mid-range, the coarse R-Y adjustment is made so that the middle bar blends into the red background.

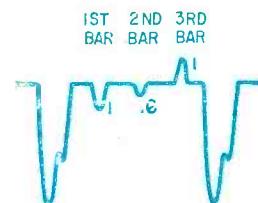


Fig. 4—Just as a double check, waveform at green CRT grid should look like this.

Next, the red and green guns are cut off and the blue gun is turned back on, using the same method as before. The screen should have a dark blue background. While viewing the screen, the B-Y adjustment is made so that the first and last bars blend into the blue background. Alignment is now complete. The guns are then restored for normal operation.

In many cases, the color circuits may not need alignment. However, they should be checked to make certain that alignment is not necessary. To make this check, connect the Color Commander to the antenna. Adjust the fine tuning properly as described earlier. On a well-adjusted set the first bar will be red, an

R-Y red, which has a very slight touch of blue. The second bar will be blue. The third bar will be cyan, a blue-green color. Vary the hue control to check its range. At one end of its range, the last bar should be blue. At the other, it should be green and at approximately mid-rotation, it should be blue-green. This is a very critical setting for correct fact tones when the receiver is tuned to a color broadcast.

The circuit

The heart of this generator is the crystal-controlled timer. The silicon unijunction transistors it uses are stable devices ideally suited for count-down circuits. A unijunction oscillator's frequency stability depends largely on the external R-C timing circuits and, if high-quality resistors and capacitors are used, the circuit will be stable.

The timer starts with a 315-kc crystal oscillator. The output is fed through a buffer to trigger a divide-by-5 stage with a 63-kc output, then through another buffer to trigger a divide-by-2

stage to 31,500 cycles. A sync buffer then provides triggering pulses to the 15,750 stage ($\div 2$) and to the 4,500 stage ($\div 7$). The output of the 15,750 oscillator then triggers the 2,250 oscillator ($\div 7$). That oscillator output triggers the 450 oscillator ($\div 5$). The output of the 4,500-cycle oscillator also triggers the 900 stage ($\div 5$), and it triggers a 300-cycle divider, which in turn synchronizes a 60-cycle stage.

Outputs from the 15,750- and 60-cycle oscillators are fed through pulse-forming networks to the sync gate where the composite sync is formed. The outputs of the 315-kc and 450-cycle oscillators are fed to shaping networks and then through the function selector switch to the video gates to form the video composite for the dot-crosshatch vertical and horizontal line patterns. The outputs of the 31,500-cycle and 60-cycle oscillators are fed through delay networks and then through the function selector switch to the video gates to form the video composites for the single cross-bars, single dot, single horizontal and vertical lines.

The output of the chroma crystal oscillator is fed through an attenuator to the chroma gate. Also fed to the gate is a 63-kc pulse after a suitable delay. The output of the chroma gate consists of chroma bursts which will form the color bar video composite.

All the video composite signals are then fed to the sync gate and adder stage. Here the composite video signals are added to the composite sync signals to form the complete composite signal. Only one composite video signal is on at any one time, depending on where the function selector is set. The complete composite signal is fed to the video output jack, where it can be used for signal injection or monitoring. The complete composite is also fed to a modulator, where it is used to modulate a carrier from the channel oscillator. The channel oscillator carrier is adjustable to channel 3 or 4 by a channel switch on the front panel. The output of the modulator is fed through an attenuator to the panel jack. A cable is supplied to connect the panel jack to the antenna of the TV receiver.

END


WHAT'S YOUR EQ?

Conducted by
E. D. CLARK

Will It Work?

As a conventional inverting amplifier, 6 volts is applied to the emitter and -6 volts to the collector of the transistor shown in the diagram.

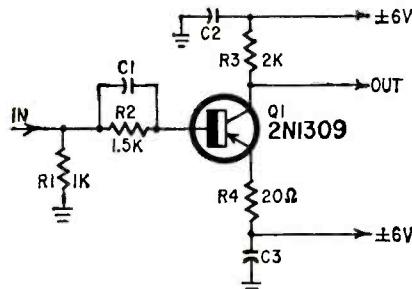A second operating condition reverse-biases Q1 by placing -6 volts on the emitter and +6 volts on the collector.




With Q1 biased this way and an input of positive and negative pulses,

will there be an output from Q1, and if so, what will a positive and negative input pulse produce, and how? The transistor is operating well within its design limits.—David Kaplan

Power-Supply Problem

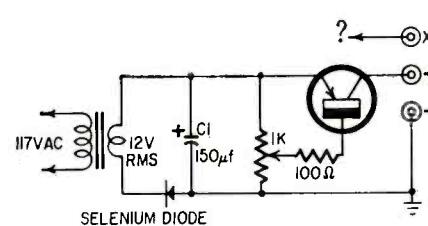You have a black box containing the power-supply circuit shown in the diagram. The transformer primary is connected to an ac line, and there are three terminals—common ground, positive output and one called X, unknown. When a capacitor is connected between terminal X and ground, the ripple in the output increases.




Where is terminal X connected in the circuit, and what capacitance (connected between X and ground) will produce an 8.4-volt peak-to-peak half-wave output?—Randolph B. Gold

Two-Way Meter

A dc shunt generator driven by an experimental gasoline engine serves as a


dynamometer to load the engine during testing by feeding current through a variable resistance. A knife switch is provided so that the generator may be used as a motor to start the engine, taking power from a 250-volt dc line and using the load resistor to limit the starting current. Unfortunately dc ammeter A, intended to measure the load current during testing, is useless during starting since the current through it is reversed.

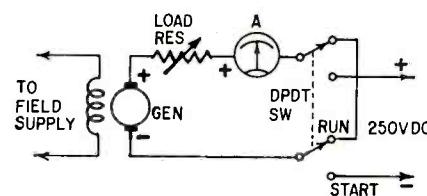

How may the meter be arranged to read both starting and load currents without the need for any additional equipment?—Robert L. Nelson Jr.

**Radio-Electronics
Is Your Magazine!**

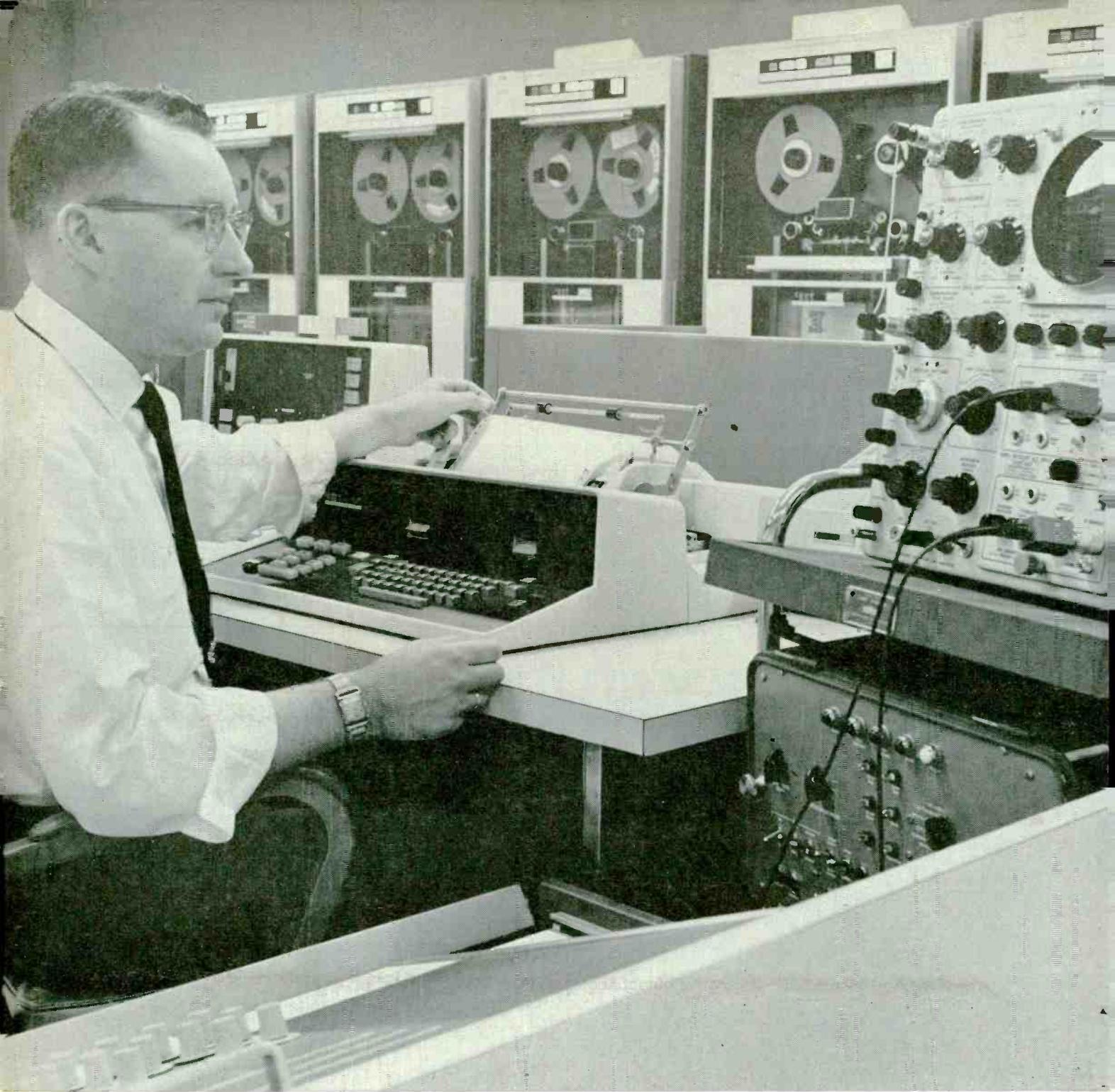Tell us what you want to see in it. Your suggestions may make it a better magazine for the rest of the readers as well as yourself. Write to the Editor, RADIO-ELECTRONICS, 154 West 14th St., New York, N. Y. 10011.



Why Fred got a better job . . .

I laughed when Fred Williams, my old high school buddy and fellow worker, told me he was taking a Cleveland Institute Home Study course in electronics. But when our boss made him Senior Electronic Technician, it made me stop and think. Sure I'm glad Fred got the break . . . but why him . . . and not me? What's he got that I don't. There was only one answer . . . his Cleveland Institute Diploma and his First Class FCC License!

After congratulating Fred on his promotion, I asked him what gives. "I'm going to turn \$15 into \$15,000," he said. "My tuition at Cleveland Institute was only \$15 a month. But, my new job pays me \$15 a week more . . . that's \$780 more a year! In

twenty years . . . even if I don't get another penny increase . . . I will have earned \$15,600 more! It's that simple. I have a plan . . . and it works!"

What a return on his investment! Fred should have been elected most likely to succeed . . . he's on the right track. So am I now. I sent for my three *free* books a couple of months ago, and I'm well on my way to Fred's level. How about you? Will you be ready like Fred was when opportunity knocks? Take my advice and carefully read the important information on the opposite page. Then check your area of most interest on the postage-free reply card and drop it in the mail today. Find out how you can move up in electronics too.

How You Can Succeed In Electronics

. . . Select Your Future From Five Career Programs

The "right" course for your career

Cleveland Institute offers not one, but five different and up-to-date Electronics Home Study Programs. Look them over. Pick the one that is "right" for you. Then mark your selection on the reply card and send it to us. In a few days you will have complete details . . . without obligation.

1. Electronics Technology

A comprehensive program covering Automation, Communications, Computers, Industrial Controls, Television, Transistors, and preparation for a 1st Class FCC License.



2. First Class FCC License

If you want a 1st Class FCC ticket quickly, this streamlined program will do the trick and enable you to maintain and service all types of transmitting equipment.




3. Broadcast Engineering

Here's an excellent studio engineering program which will get you a 1st Class FCC License and teach you all about Program Transmission and Broadcast Transmitters.



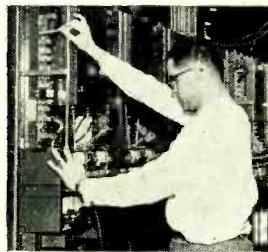
4. Electronic Communications

Mobile Radio, Microwave, and 2nd Class FCC preparation are just a few of the topics covered in this "compact" program . . . Carrier Telephony too, if you so desire.



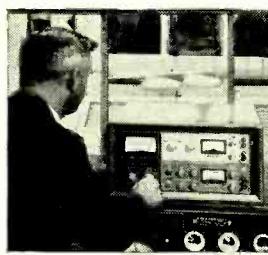5. Industrial Electronics & Automation

This exciting program includes many important subjects such as Computers, Electronic Heating and Welding, Industrial Controls, Servomechanisms, and Solid State Devices.



An FCC License . . . or your money back!

In addition to providing you with comprehensive training in the area indicated, programs 1, 2, 3, and 4 will prepare you for a Commercial FCC License. In fact, we're so certain of their effectiveness, we make this exclusive offer:

The training programs described will prepare you for the FCC License specified. Should you fail to pass the FCC examination after completing the course, we will refund *all* tuition payments. You get an FCC License . . . or your money back!

CIE's **AUTO-PROGRAMMED** lessons help you learn faster and easier

Cleveland Institute uses the new programmed learning approach. Our **AUTO-PROGRAMMED*** lessons present facts and concepts in small, easy-to-understand bits . . . reinforce them with clear explanations and examples. Students learn more thoroughly and faster through this modern, simplified method. You, too, will absorb . . . retain . . . advance *at your own pace*.

*TRADEMARK

Free nationwide job placement service . . . for life, for every CIE graduate

Once enrolled with CIE, you will get a bi-monthly listing of the many high-paying interesting jobs available with top companies throughout the country. Many Cleveland Institute students and graduates hold such jobs with leading companies like these: American Airlines, American Telephone and Telegraph, General Electric, General Telephone and Electronics, IBM, Motorola, North American Aviation, New York Central Railroad, Raytheon, RCA and Westinghouse.

Electronics is a fast moving, dynamic industry . . . Cleveland Institute keeps you current

The Electron Bulletin is CIE's bi-monthly digest of new developments in the world's fastest growing industry. As a CIE student, you will get a free copy throughout your training to keep you up-to-date on Masers, Lasers, Solid State Devices, and other new inventions.



Full accreditation . . . your assurance of competence and integrity

Cleveland Institute of Electronics is accredited by the Accrediting Commission of the National Home Study Council. You can be assured of competent electronics training by a staff of skilled electronics instructors.

**Your Future In Electronics Is
Up To You. Make It A Brighter One.
Mail Reply Card Today.**

CIE

Cleveland Institute of Electronics

1776 East 17th Street, Dept. RE-8, Cleveland, Ohio 44114

EQUIPMENT REPORT

Mercury Model 1400 In-Circuit Capacitor Tester

For manufacturer's literature, circle No. 24 on Reader's Service Card

The Mercury Electronics Corp. model 1400 In-Circuit Capacitor Tester will find ever-increasing use on the modern service bench because printed circuitry requires new testing techniques. You can't keep unsoldering and lifting out components to check them because you'll often loosen the foil from copper-clad boards. Desoldering and resoldering is time-consuming and expensive especially when you ruin a good component.




A technique called *in-circuit testing* has become necessary.

Capacitors can be particularly troublesome. Electrolytics dry out and their capacitance decreases as they get old. Substitution is one method of finding such aged units, but the decrease in capacitance in borderline units is not apparent and does not show up when using test equipment and techniques that are quite suitable for wired chassis.

The proper way to find a changed capacitance value is to measure for it. With electrolytics, this measurement does not have to be very exact since their tolerances are very broad. Some units listed in the current catalogs are -10% to +100%—others have tolerances so broad they are not mentioned.

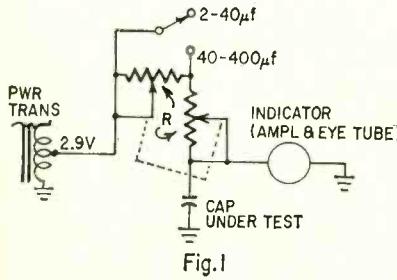Values between 2 and 40 μf are measured using the basic circuit given



in Fig. 1. Values from 40 to 450 μf use the same circuit except that part of dual potentiometer R is shorted out of the circuit by the range switch.

A tap on the heater winding of the transformer supplies 2.9 volts which is applied across the series-parallel resistance network in series with the capacitor under test.

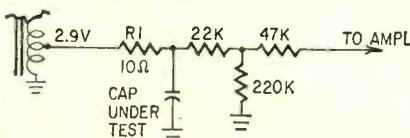


Fig.2

The dial of the dual potentiometer is calibrated in μf . The knob rotates the wiper arms which change the voltage drop across the capacitor in the test circuit. The effective resistance (reactance) of the capacitor under test decreases as the capacitance increases, and a different series resistance is needed to make the electron-ray (eye) tube just close.

Changing the resistance or the capacitance increases or decreases the voltage that goes to the grid of the 6C4 triode amplifier. The triode is direct-coupled to the grid of the EM84 electron-ray tube.

The shorted-capacitor check uses a similar circuit (Fig. 2). The 2.9-volt tap on the power transformer is applied to the capacitor under test through a current-limiting resistor (R1). A capacitor with more than 10 ohms of leakage resistance will not show as shorted—but there will be some “eye” closing. Leakage resistances higher than 30 ohms will have practically no “eye” movement.

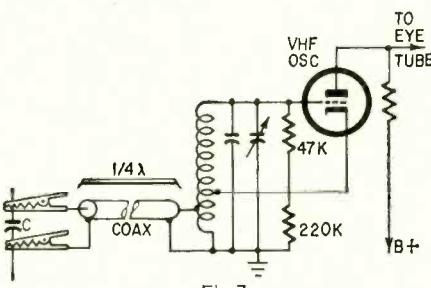


Fig.3

To find an open capacitor, an entirely different principle is used (Fig. 3). A vhf oscillator develops the test frequency. Its plate is direct-coupled to the grid of the “eye” tube. The coaxial test lead, one-quarter wavelength long at the test frequency, is connected across a few turns at the ground end of the oscillator coil. (A quarter-wave line acts as an impedance-reversing transformer. If we connect a high impedance across one end, it appears as a low im-

pedance or a short circuit at the other.)

If the capacitor being tested is *open*, it represents a near-infinity impedance and appears as a short circuit across a section of the oscillator coil. This loads the oscillator and increases the drop across the plate resistor. This increases the bias on the indicator tube and the “eye” closes.


When a good capacitor, or a shorted one, is connected between the clips, the quarter-wave line transforms its relatively low impedance into a high impedance that does not affect oscillator loading. The “eye” remains open. Both OPEN and SHORT tests must be used to determine the condition of a capacitor.

Warning: The 3-volts ac (rms) is nearly 9 volts peak-to-peak, and may damage capacitors with a lower voltage rating.—Elmer C. Carlson

Euphonics “Miniconic” Semiconductor Stereo Pickup

For manufacturer's literature, circle No. 25 on Reader's Service Card

ON PAGE 6 OF THE JANUARY 1965 issue, RADIO-ELECTRONICS published the first news of a remarkable new pickup cartridge that is actually a silicon semiconductor diode. It modulates a dc bias to produce a signal. The Euphonics “Miniconic” is a tiny stereophonic pickup with a frequency response from dc to about 30 kc. Its compliance is among the highest in pickups today, and its dynamic mass among the lowest.

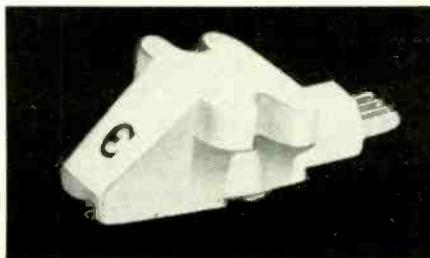

Other salient features of the cartridge are its low output impedance (about 1,000 ohms), its high output level and its complete insensitivity to interference fields, either electromagnetic or electrostatic.

The cartridge comes ready for mounting in any standard tone arm. With it comes a power supply—a neat little box with a line cord, a special plug-in cable and a pair of permanently attached cables with phono plugs at their ends. The power supply provides the operating bias and optional equalization.

On the box is a slide switch marked H—L. In the H (high) position, the

Continued on page 70

Congress DIDN'T GO FAR ENOUGH!

PUBLIC LAW 87-529; 76 STAT. 150

[H. R. 8031]

An Act to amend the Communications Act of 1934 in order to give the Federal Communications Commission certain regulatory authority over television receiving apparatus.

Be it enacted by the Senate and House of Representatives of the United States of America in Congress assembled, That:

Section 303 of the Communications Act of 1934 (47 U.S.C. 303)³⁴ is amended by inserting at the end thereof the following:

"(s) Having authority to require that apparatus designed to receive television pictures broadcast simultaneously with sound be capable of adequately receiving all frequencies allocated by the Commission to television broadcasting when such apparatus is shipped in interstate commerce, or is imported from any foreign country into the United States, for sale or resale to the public."

See. 2. Part I of title III of the Communications Act of 1934 is amended by inserting at the end thereof a new section as follows:



THEY SHOULD HAVE ALSO REQUIRED...

"—that all 82-channel television receivers* must use an 82-channel television antenna."

Of course, you can't take the law into your own hands—but you *can* take advantage of today's ready-made opportunities to sell an 82-channel antenna with each 82-channel TV set.

Our Antenna Research Laboratories in Champaign, Illinois knew what they were doing when they teamed the acclaimed Log Periodic concept of the University of Illinois Antenna Research Laboratories with our new antenna design advance—the capacitor-coupled electronic dipole. Proof is the fact that the JFD LPV-VU is America's No. 1 82-channel TV/FM antenna!

Who says you can't have everything

you want in a TV antenna—VHF?... UHF?... FM Stereo?—with a single down-lead to boot!

MOST EFFICIENT PERFORMANCE EVER ON VHF, UHF, FM/STEREO FROM ONE ANTENNA USING ONE DOWN-LEAD!

- *Cap-electronic* dipole design makes more elements resonate on channels 7 to 13 with a corresponding increase in gain.
- *Higher mode* operation in UHF band achieves higher gain on channels 14 to 83—and FM stereo.
- *Narrower beamwidths* . . . higher front-to-back ratios step up ghost rejection . . . intensify color.
- *Patented frequency independent* design maintains peak perform-

ance characteristics regardless of channel or band tuned.


- Includes 3-way splitter so single down-lead can be tied into individual VHF, UHF and FM system inputs.

REMEMBER — AN 82-CHANNEL TV SET IS NOT AN 82-CHANNEL TV RECEIVER UNLESS IT HAS AN 82-CHANNEL TV ANTENNA!

*Lest we forget—every *color* set is also an *82-channel* set requiring a color-perfect antenna. In fact, many color TV shows are broadcast on UHF channels.

JFD

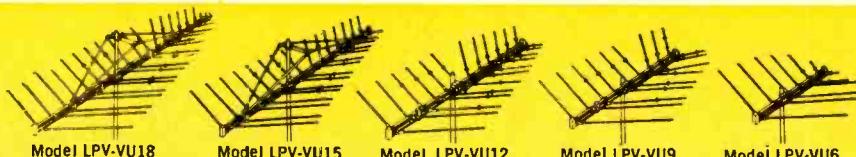SEE YOUR DISTRIBUTOR OR
WRITE FOR BROCHURE 806



JFD LPV-VU LOG PERIODICS for channels 2 to 83 and FM/Stereo.

Licensed Under One or More of U.S. Patents 2,958,081; 2,985,879; 3,011,168; 3,108,280; 3,150,376 and Additional Patents Pending in U.S.A. and Canada. Produced by JFD Electronics Corporation under exclusive license from The University of Illinois Foundation.

Circle 26 on reader's service card

www.americanradiohistory.com

JFD ELECTRONICS CORPORATION

15th Ave. at 62nd Street, Brooklyn, N.Y. 11219

JFD Electronics-Southern Inc.

Oxford, North Carolina

JFD International


64-14 Woodside Ave., Woodside 77, N.Y.

JFD Canada, Ltd.

51 McCormack Street, Toronto, Ontario, Canada

Look What's

NEW LOW PRICES

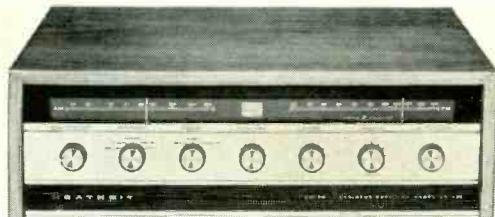


ALL-TRANSISTOR STEREO RECEIVER

Just add 2 speakers for a complete stereo system. AM/FM/FM stereo tuning; 46-transistor, 17-diode circuit for cool, instant operation & natural transistor sound; 66 watts music power @ ± 1 db from 15 to 30,000 cps; walnut cabinet. 35 lbs.

Kit AR-13A
Now Only

\$184⁰⁰

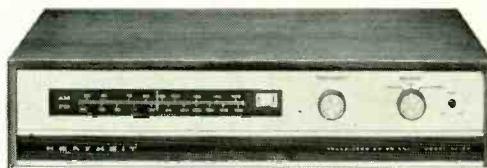

Kit AJ-33A
Now Only

\$94⁵⁰


TRANSISTOR AM/FM/FM STEREO TUNER

Features 23-transistor, 8-diode circuit; built-in stereo demodulator; automatic switching to stereo; stereo indicator light; stereo phase control; filtered outputs for beat-free recording; walnut cabinet. 17 lbs.

OTHER NEW LOW-PRICE COMPONENTS

- ★ Kit AJ-41 (tube), AM/FM/FM Stereo Tuner... Now Only \$112.50
- ★ Kit AJ-12 (tube), FM/FM Stereo Tuner... Now Only \$65.95
- ★ Kit AJ-13 (tube), FM/FM Stereo Tuner... Now Only \$47.00
- ★ Kit AJ-63 (tube), Mono FM Tuner... Now Only \$37.50

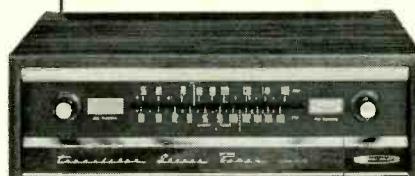Now Install Any Of 3 Ways . . .
Wall, Custom Or Heath Cabinets!



Kit AJ-43D
Now Only

\$109⁰⁰

(less cabinet)

Deluxe Transistor AM/FM/FM Stereo Tuner

25-transistor, 9-diode circuit; automatic switching to stereo; stereo indicator light, stereo phase control; filtered outputs. 15 lbs. Optional cabinets, (walnut \$12.95), (metal \$6.95).



Kit AA-21D
Now Only


\$137⁰⁰

(less cabinet)

Matching 100-Watt Transistor Stereo Amplifier

70 watts RMS power at ± 1 db from 13 to 25,000 cps; 26-transistor, 10-diode circuit; inputs & outputs for any source; 4, 8 & 16 ohm speaker impedances. Opt. cabinets, (walnut \$12.95), (metal \$6.95). 23 lbs.

New Low Price On Deluxe 21" Color TV

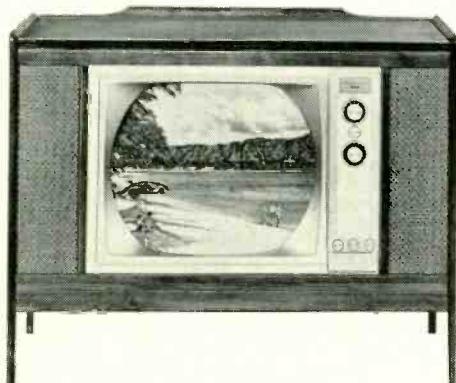


Kit GR-53A
Now Only

\$375⁰⁰

(less cabinet)

Ends costly color TV servicing . . . only set you adjust and maintain yourself. Only Color TV you can install 3 ways . . . wall, custom or Heathkit cabinets. Tunes all channels for 21" of the best color pictures in TV plus true hi-fi sound. Assembles in just 25 hours . . . no special skills needed . . . all critical circuits preassembled and aligned. 1-year warranty on picture tube, 90 days on all other parts. 127 lbs. Also new low prices on preassambled Heathkit cabinets: GRA-53-7, walnut cab. (illus.) 85 lbs... \$108; GRA-53-6, walnut-finish hardboard cab., 52 lbs... \$46.50

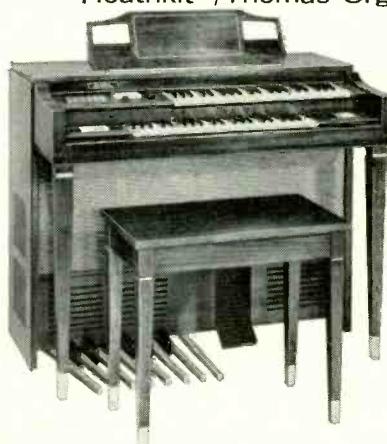New Low Prices On Heathkit®/Thomas Organs



Kit GD-983
Now Only

\$799⁰⁰

The Heathkit/Thomas "Coronado" Transistor Organ, (illus.) boasts 17 organ voices, two 44-note keyboards, Leslie plus 2-unit main speaker system, 28 notes of chimes, 13-note heel & toe pedalboard, color-tone attack & repeat percussion, matching bench, plus many more professional features. 242 lbs. Also the Heathkit/Thomas "Artiste" Transistor Organ with 10 voices, two 37-note keyboards, repeat percussion, etc. now at only \$332. 154 lbs. Both organs have all genuine Thomas factory fabricated components.

Circle 27 on reader's service card

NEW At Heath!

NEW KITS


New Transistor FM Stereo Tuner . . .
Build In 6 Hours!



World's easiest to build stereo/hi-fi kit . . . takes 6 hours or less! 14-transistor, 4-diode circuit for cool instant operation, natural transistor sound. Phase control assures best stereo performance. 4-stage IF for high sensitivity. Filtered outputs for direct stereo recording. Automatic stereo indicator light, preassembled & aligned "front-end." Install in a wall or either Heath cabinet; walnut (\$7.95), metal (\$3.50). 6 lbs.

Kit AJ-14
\$49.95
(less cabinet)

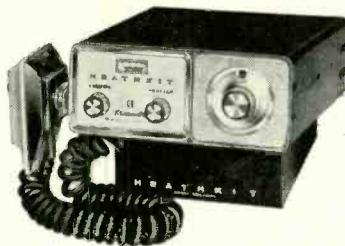
New 23-Channel, 5-Watt Transistor CB Transceiver



23-channel transmit & receive capability. All-transistor circuit for instant operation, low battery drain . . . only .75 A transmit, .12 A receive. Only 2½" H x 7" W x 10½" D . . . ideal for car, boat, etc. ½ uv sensitivity for 10 db signal plus noise to noise ratio. Front-panel "S" meter, adjustable squelch, automatic noise limiter, built-in speaker, ceramic PTT mike, charcoal gray aluminum cabinet. 8 lbs.

Kit GW-14
\$89.95
(Assembled
GWW-14,
\$124.95)

NEW!
1966 CATALOG

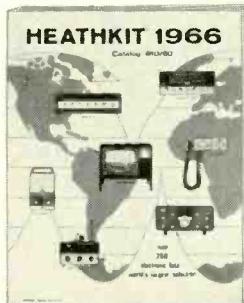

Free! 108 pages . . . many in full color . . . describe these and over 250 easy-to-build Heathkits. Save up to 50%. Mail coupon for your free copy.

Compare it to sets costing \$150 and more! 5 bands cover 200-400 kc, AM, and 2-30 mc. Tuned RF stage, crystal filter for greater selectivity, 2 detectors for AM and SSB, tuning meter, bandspread tuning, code practice monitor, automatic noise limiter, automatic volume control, antenna trimmer, built-in 4" x 6" speaker, headphone jack, gray metal cabinet, and free SWL antenna. Assemble in 15 hours. 25 lbs.

Kit GR-54
\$84.95

New 6-Meter SSB Ham Transceiver



Full SSB-CW transceive operation on 6 meters. 180 watts PEP SSB—150 watts CW. Operates fixed or mobile; PTT and VOX. Switch-selection of upper sideband, lower sideband, and CW. Covers 50-52 mc with crystals supplied, total coverage 49.5-54 mc. Famous Heath SB series Linear Master Oscillator for true linear tuning. Built-in 100 kc calibrator and antenna switching. Accessory mobile mount SBA-100-1 . . . \$14.95. 23 lbs.

Kit SB-110
\$320.00

HEATHKIT®

... Buy Now—Use This Order Blank . . .

HEATH COMPANY, Dept. 20-9, Benton Harbor, Michigan 49023
In Canada: Daystrom, Ltd., Cooksville, Ontario

Please send FREE 1966 Heathkit Catalog.

Model	Description	Weight	Price

Name _____ (Please Print)

Address _____

City _____ State _____ Zip _____

SHIP VIA: Parcel Post Express Collect Freight 20% Included, C.O.D.

Best Way

All prices & specifications subject to change without notice.

CL-216

**WE DON'T CLAIM
OUR ELECTRONIC
IGNITION SYSTEM
IS BEST . . .**



**OUR
CUSTOMERS DO!**

WRITE TODAY FOR FREE LITERATURE

JUDSON

RESEARCH AND MFG. CO.
CONSHOHOCKEN, PA., U.S.A.



Circle 28 on reader's service card

EQUIPMENT REPORT continued

pickup system produces a high-level, flat-response signal, of about the same amplitude as that from a tuner, suitable for feeding directly to an auxiliary input of a stereo amplifier without equalization. The playback curve of the system follows the RIAA standard.

In the L (low) position, the output of the pickup is attenuated and "de-equalized" so that it can be fed into the equalized phono input of an amplifier. Assuming that the amplifier's equalization is accurate, either mode of operation should give equally pleasing results, except that the signal-to-noise ratio will inevitably be better when the Euphonics system is used with a high-level, auxiliary input.

How does the Miniconic system stack up against other pickups? As far as performance goes, very well. Specified tracking-force limits for the CK-15-LS professional model (the one I checked) are $\frac{3}{4}$ to 2 grams; I found it tracked well down to 1 gram on all music even with an inferior arm. (On test-record cuts with extremely high modulation levels, there was some skipping, but much of this was undoubtedly due to the tone arm.) The cartridge tracked a square wave (CBS test record STR 111) very neatly; there was some rounding of the tops (viewed

on an oscilloscope), but not a trace of ringing or overshoot.

The sound was clean and crisp, equal to that from the best magnetics I have heard. Stereo separation is adequate (given as 25 db at 1 kc). Few if any stereo records exceed that. The Miniconic delivers unobtrusive sound, and keeps its head during loud orchestral passages with percussion.

As far as the mechanics of the unit are concerned—well, that's up to you. I am always suspicious of gadgetry, and of any unjustifiable complications. The Miniconic system is more complex than a magnetic or ceramic cartridge. But it's a *simple* complexity. The only extra is a small box, hardly bigger than two packs of cigarettes. And there's always room for another ac plug. Second, it is an installation complexity only; once the cartridge and power supply are installed, they require no further attention. There are no controls or switches except that single slide switch, which is set once and then ignored forever after.

Third, the results seem to justify the complication. Whether the Miniconic system really sounds better than any other cartridge is a personal matter. But it can certainly solve some hum and magnetic-attraction problems. Its already-equalized high-level output can make it useful in some installations where a ceramic or crystal cartridge might otherwise be necessary. For practical purposes, then, you might compare the system to an ordinary pickup with an outboard preamplifier. (But remember that it is nothing like that in its operation.)

The pickup is a *modulating* device, like a carbon or condenser microphone or a strain gage, rather than a generating device, like most other mikes and pickups. Fuller details, including a schematic diagram of a suggested input circuit for the cartridge, were given in the *News Briefs* of our January 1965 issue.

If you're in the market for a new cartridge, don't overlook this one because it's new or offbeat. It's a fine piece of design, sounds good and may solve a hum problem you didn't even realize you had.—Peter E. Sutheim

MANUFACTURER'S SPECIFICATIONS

Frequency response: dc to beyond 30 kc

Separation: more than 25 db at 1 kc

Compliance: 20×10^{-6} cm/dyne

Weight: 2 grams

Output: 0.4 volt, high level; 8 mv, low level

Mounting: standard $\frac{1}{2}$ - and 7/16-in. centers

Effective vertical tracking angle: 15°

Stylus: model U-15-LS, biradial low-mass, .0009 by .0002 in.; model U-15-P, circular low-mass, .0005 in.

Tracking force: model U-15-LS, $\frac{3}{4}$ to 2 grams; model U-15-P, 1 to 3 grams

Price: CK-15-LS conversion kit for existing tone arms (reviewed here), \$55; conversion kit for changers, \$39; complete with special arm, \$71.50 and \$87.50

ATTENTION! CB OPERATORS save on citizens radio equipment

Discontinued Models From International Radio Exchange

Select that extra transceiver for mobile or base installation, or equip a new station. Our stock includes International types as well as other makes.

*Write Today for A
Complete List of
Equipment in Stock*



RADIO EXCHANGE
18 NO. LEE, OKLA. CITY, OKLA. 73102
Division Of International Crystal Mfg. Co.
Dealing In Used Citizens
Radio Equipment




Circle 29 on reader's service card

NEW SEMI- CONDUCTORS AND TUBES

ECONOMICAL SUBMINIATURE 1-WATT ZENER DIODES

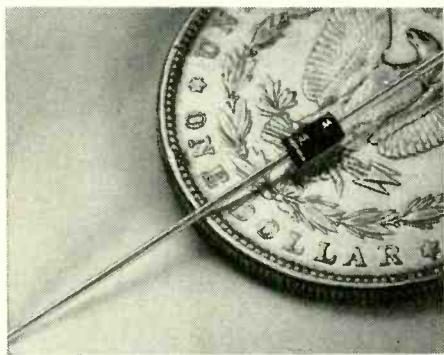
A new series of Zener diodes with breakdown voltages from 3.3 to 100 has been introduced by Motorola. The diodes, about the size of the ordinary 1/4-watt diode or resistor, are rated at 1 watt at 50°C ambient, and up to 3 watts with proper heat-sinking. Voltage ratings are available in 5% or 10% tolerances. The diodes are numbered 1N4728 through 1N4764.




Oxide-passivated silicon "dice" for stable operation, and silver leads for effective heat dissipation are among the features of the new line. All the diodes are encapsulated in Motorola's *Surmetic* process, with a flameproof, void-free silicon polymer plastic. Prices of most of the units fall between \$1 and \$2.

1 WATT, DC TO 100 KC— IN A LITTLE PILL

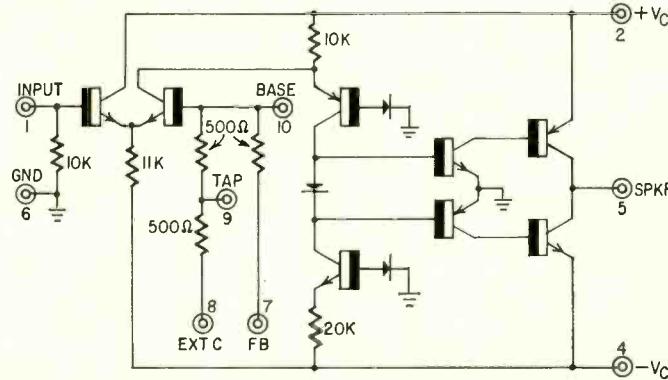This 1-watt integrated-circuit power amplifier is more or less flat between dc and 100 kc, and is packaged in a single TO-5 can (about 3/8 inch in diameter by about 3/8 inch high). Harmonic distortion is claimed to be "as low as 0.5%."



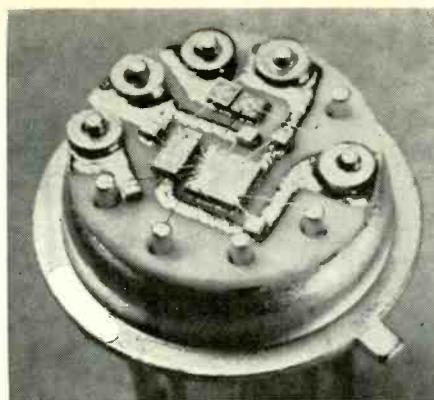Circuit of Moto-
rola MC1524
integrated-cir-
cuit amplifier.



Designated the MC1524, this Motorola IC has three external taps to offer a choice of three internal negative feedback loops. The purpose of that is to insure low distortion and high gain stability under all sorts of conditions from -55 to 125°C.

A glance at the circuit diagram shows that the unit uses a class-B complementary output circuit, which permits coupling it direct to low-resistance loads, like a speaker or a servomotor. Its output (source) impedance is typically 0.5 ohm, which provides high damping for the load.

The MC1524 can be used for servomechanisms, low-power audio, telemetry or as an operational amplifier. Zero-signal current drain is less than 4 ma. It needs no heat sink even at 1-watt output.

Only trouble is, for low-power people like us, it costs \$70.

19-INCH COLOR PIX

The Electronic Tube Div. of Sylvania announced "limited availability" of a rectangular 19-inch, 90°-deflection-angle color picture tube. It is claimed to be even brighter than the Sylvania 21-inch Color Bright 85 tube introduced in June 1964.


The new tube uses a europium-activated yttrium vanadate phosphor for the red parts of the picture, and improved blue and green phosphors. Its viewing area is 180 square inches. Face-to-socket length is about 18 inches, and the tube weighs 20 pounds (24 with bonded faceplate.)

END


brand new
...and very important...

QUAM COLOR TV REPLACEMENT SPEAKERS PREVENT COLOR PICTURE DISTORTION

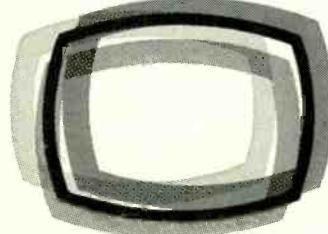OFTEN CAUSED BY STRAY
MAGNETIC FIELDS FROM
ORDINARY LOUDSPEAKERS



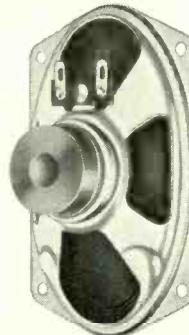When you use an ordinary loudspeaker in a color TV set, you're looking for trouble... picture trouble. The external magnetic fields from standard loudspeakers will deflect the primary color beams, causing poor registration and distorted pictures.



QUAM RESEARCH SOLVES THIS PROBLEM

An entirely new construction technique, developed in the Quam laboratories, encases the magnet in steel, eliminating the possibility of stray magnetic fields and the problems they cause! These new Quam speakers have been eagerly adopted by leading color TV set manufacturers. Quam now takes pride in making them available for your replacement use. Five sizes (3" x 5", 4", 4" x 6", 5 1/4", 8")... in stock at your distributor.

QUAM

QUAM-NICHOLS COMPANY

234 E. Marquette Rd. • Chicago, Ill. 60637

Circle 30 on reader's service card

The following free advertiser material is available through

RADIO-ELECTRONICS READER'S SERVICE

ALLIED RADIO CORP. (Pg. 82-85)	Circle 115
508-page 1966 catalog	
AMPEREX ELECTRONICS CORP. (Second Cover)	Circle 1
Complete list of tubes	
AMPHENOL (Pg. 23)	Circle 17
Descriptive literature on new Color Commander test instruments	
BLODNER-TONGUE (Pg. 79)	Circle 112
Booklet on how and when to use 75 ohm or 300 ohm TV lead in VHF only or VHF-UHF	
BRACH MANUFACTURING CO. (Pg. 95)	Circle 127
Catalog of indoor TV antennas	
BROOKS RADIO & TV CORP. (Pg. 97)	Circle 128
Catalog sheets and price lists of tubes and parts	
CAPITOL RADIO ENGINEERING INSTITUTE (Pg. 18-21)	Circle 15
Book describing CREI programs in electronics and nuclear engineering technology	
CASTLE TV TUNER SERVICE (Pg. 6)	Circle 6
Information on complete tuner overhaul by mail	
CLEVELAND INSTITUTE OF ELECTRONICS (Pg. 1)	Circle 2
Free pocket electronics data guide and booklet describing electronics slide rule and instruction course	
CONAR (Pg. 13)	Circle 11
Catalog on Conar Electronic Kits	
CORNELL ELECTRONICS (Pg. 106)	Circle 135
Catalog and price list of tubes and parts	
COYNE ELECTRONICS INSTITUTE (Pg. 107)	Circle 136
Book on "Your Opportunities in Electronics"	
DATAK CORP. (Pg. 100)	Circle 130
Folder and sample of "Instant Lettering" marking kit	
DE VRY TECHNICAL INSTITUTE (Pg. 5)	Circle 4
Booklets—"Pocket Guide to Real Earnings" and "Electronics in Space Travel"	
ELECTRONIC CHEMICAL CORP. (Pg. 101)	Circle 132
Information on "No Noise" aerosol products	
EUPHONICS MARKETING (Pg. 76)	Circle 109
Booklet on "The Story of Euphonics Miniconic"	
FINNEY COMPANY (Pg. 25)	Circle 19
Booklets on Fincos' Color Ve-Log Antennas	
GERNSBACK LIBRARY (Pg. 98-99)	Circle 129
Information on special membership offer for Electronics Book Club	
HALLMARK INSTRUMENTS (Pg. 81)	Circle 114
Information on Banner 85 CB and AM broadcast radio	
HEATH COMPANY (Pg. 68-69)	Circle 27
1965 Heathkit catalog	
INTERNATIONAL CRYSTAL MFG. CO. (Pg. 70, 112)	Circle 29 & 148
Catalog on citizens radio transceiver and name of your nearest International dealer	
JFD ELECTRONICS CORP. (Pg. 67)	Circle 26
Brochure on 82-channel TV antenna	
JENSEN MANUFACTURING DIV. (Third Cover)	Circle 149
Information on Jensen Model HS-2 stereo headphones	
JERRIOLD ELECTRONICS CORP. (Pg. 89)	Circle 120
Information on new Jerrifold coloraxial TV reception system	
JUDSON RESEARCH & MFG. CO. (Pg. 70)	Circle 28
Descriptive literature and technical data folder on electronic magneto ignition system	
LAFAYETTE RADIO ELECTRONICS (Pg. 93-94)	Circle 125
1965 Lafayette catalog	
MALLORY DISTRIBUTOR PRODUCTS CO. (Pg. 27)	
Information on Mallory circuit breakers	Circle 21
MERCURY ELECTRONICS CORP. (Pg. 91)	Circle 123
Complete catalog on test equipment	
NATIONAL TECHNICAL SCHOOLS (Pg. 3)	Circle 3
Electronics "Opportunity Book" and sample lesson	
OXFORD TRANSDUCER CORP. (Pg. 26)	Circle 20
Complete catalog on commercial sound speakers	
PERMA-POWER COMPANY (Pg. 22)	Circle 16
Folder on Ampli-Vox sound systems	
POLY PAKS (Pg. 111)	Circle 138
Catalog of semi-conductors	
PROGRESSIVE "EDU-KITS" (Pg. 92)	Circle 124
Information describing "Edu-Kit"	
QUAN-NICHOLS COMPANY (Pg. 71)	Circle 30
Folder on Quan line of loudspeakers	
QUIETROLE CO. (Pg. 100)	Circle 131
Information on Quietrole's aerosols for servicing	
RCA CITIZENS' BAND (Pg. 7)	Circle 7
Folder on Mark VIII and Mark Nine CB Transceivers	
RCA INSTITUTES (Pg. 28-31)	Circle 22
Brochure on home study and classroom training	
RADIO SHACK (Pg. 102-105)	Circle 133
Radio Shack catalog	
RYE SOUND CORP. (Pg. 90)	Circle 121
12-page general catalog of sound accessories	
HOWARD W. SAMS CO. (Pg. 17)	Circle 14
Information on Photofact Library-Encyclopedia deal	
HOWARD W. SAMS CO. (Pg. 78)	Circle 111
Sams booklet	
H. H. SCOTT (Pg. 24)	Circle 18
Spec sheet on solid-state stereo amplifier kit	
SENCore (Pg. 87)	Circle 117
Descriptive literature on Sencore's MX129 FM stereo multiplex generator and analyzer	
SONOTONE CORP. (Pg. 12)	Circle 9
Comprehensive cartridge replacement guide	
STANCOR ELECTRONICS (Pg. 90)	Circle 122
TV coil and transformer replacement guide	
UNITED RADIO (Pg. 109)	Circle 137
Complete parts catalog	
UNIVERSITY, LTV (Pg. 13)	Circle 10
Brochure on high-fidelity speakers and systems	
VIKING OF MINNEAPOLIS (Pg. 80)	Circle 113
Complete catalog on Auto-Tape 500 and accessories	
WEBSTER (Pg. 88)	Circle 118
Information on the "565" C-B radio	
WELLER (Pg. 86)	Circle 116
Descriptive literature on Weller soldering guns	
WINEGARD (Pg. 14-15)	Circle 12
Fact-Finder #242, on the Chroma-Tel All-Band Antenna	

Radio-Electronics

READER'S SERVICE

Here's how you can get additional information from the manufacturer, promptly and at no charge, concerning products and services advertised or mentioned editorially in this issue.

Circle the number on the postcard facing this page that corresponds to the number at the bottom of each advertisement or editorial mention that interests you.

Cut out the postcard. Clearly print or type your name and address where indicated — and mail. (Canadian and foreign affix postage.)

If the postcard has already been detached from your copy of RADIO-ELECTRONICS, use the coupon on this page instead. Enclose the coupon in an envelope and address it to: RADIO-ELECTRONICS, P.O. Box 7365, Philadelphia, Pa. 19101. (Use this address only for Reader's Service requests.)

VOID AFTER OCTOBER 31, 1965

RADIO-ELECTRONICS READER'S SERVICE

The numbers I have circled below indicate the material I would like to receive:

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105
106	107	108	109	110	111	112	113	114	115	116	117	118	119	120
121	122	123	124	125	126	127	128	129	130	131	132	133	134	135
136	137	138	139	140	141	142	143	144	145	146	147	148	149	150

Name _____

Address _____

City _____ State _____

9-65 Zip Code _____

NEW PRODUCTS

More information on these new products is available free from the manufacturers. Each item is identified by a Reader's Service number. Turn to the Reader's Service Card facing this page and circle the numbers of the new products on which you would like further information. Detach and mail the postage-paid card.


SOLDERING GUN KIT. Wen Hot Rod model 222-K5, includes gun, single-post medium/heavy-duty tip (heat range—100 to 200 watts), fine line tip (heat range—25 to 100 watts), a plastic cutting attachment, flat iron attachment, roll of



solder, red plastic carrying case, 6-ft line cord. Gun uses on-off trigger switch, has built-in spotlight, operates on 120 volts ac. Kit case: 2 1/2 x 7 1/2 x 10 in.; weight complete 2 lbs, 12 oz.

Circle 46 on reader's service card

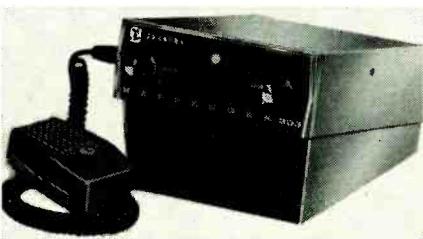BUSINESS/INDUSTRIAL TRANS-CEIVER. E. F. Johnson Co.'s Messenger 303, is adaptable for base station, mobile or portable field pack use; accessory



speaker converts it to PA system. Designed for use on business/industrial frequencies between 25 and 50 megacycles AM, FCC type-accepted. Precision crystal filter.

Circle 47 on reader's service card

SPEAKER SYSTEM. Sonomaster RM-2, from Sonotone. 8 ohms; power rating, 50 watts average program material, 100 watts peak program material; response 40-20,000 cycles; crossover frequency 4,500 cycles. One 8-in. linear high-com-



pliance woofer; one 3 1/2-in. cone tweeter, 19 x 11 1/2 x 8 1/2, 1/4-in. panels, oiled walnut veneer, 22 lb.

Circle 48 on reader's service card

BOOKSHELF SPEAKER SYSTEMS. Lafayette Criterion 50, 100 and 200. Model 50 2-way system has 8-in. woofer, and 4-inch cone-type tweeter, 30-18,000 cycles. 100: 10-in. woofer, and 4-in. tweeter, 25-19,000 cycles. 200: 12-in. woofer, 8-in. mid-range and 3-in. dome-type super tweeter, 25-25,000 cy-



cles. Handle 20, 30 and 40 watts respectively. Impedance 8 ohms, 1/4-in. wood enclosures. Models 50 and 100 are 19 x 10 1/2 x 8 1/2 in., 200 is 24 x 14 x 12 in. 100 shown.—Lafayette Radio Electronics Corp., 111 Jericho Turnpike, Syosset, N. Y. 11791.

Circle 49 on reader's service card

15-WATT AM/FM STEREO RECEIV-ER. Lafayette LR-300. 3-uv in gives 20-db quieting. Switchable afc. Tuner has multiplex separation of 25 db at 400 cycles. Amplifier produces 7.5 watts per




channel with harmonic distortion at 1%. Response: 20-20,000 cycles ±2 db. Hum and noise —55 db at low level and —75 db

at high-level inputs. Output impedances switch-selected at 8 and 16 ohms, input selector controls AM, FM stereo search, FM-MPX, phono and auxiliary music sources. 15 tubes, 7 diodes, EM-84 tuning eye. 16 1/4 x 5 1/4 x 12 1/4. Stock No. 99-0003WX.

Circle 50 on reader's service card

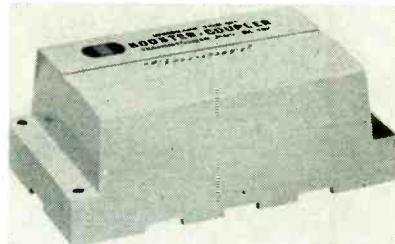BOOSTER/COUPLER. Winegard BC-107, has 7 db minimum gain to TV or FM. Has extra set of terminals to use as booster only with single TV or FM, 12 db gain; can also be used to extend rabbit-ear range. Linear frequency response across



TV and FM bands and an exact match into 300 ohms. Polystyrene housing. 117 vac, 1 watt.

Circle 51 on reader's service card

PORTABLE AM RADIO KIT. the Heathkit GR-224, has 6 silicon transistors and 2 silicon diodes—performance equal to 8-transistor portables. Powered by 6 size-D flashlight batteries; 4 x 6 in. oval speaker; rf stage and double-tuned i.f. stage; diode-biased audio output stage.



Batteries enclosed in plastic holder. Slide-rule dial, built-in 1/2-in. diameter rod antenna.

Circle 52 on reader's service card

TRIMMING POTENTIOMETERS. Series 63 line, from Clarostat Mfg. Available with wire leads for printed circuit mountings, standard solder lugs, molded or metal shafts, molded or metal bearing



Special hinge on cover so it can be left on or removed and held in steel handle. New plastic holder in cover to hold pages of setup booklet open. Setup chart covers more than 3,000 tubes.

Circle 54 on reader's service card

caps. Basic pot dimensions: $\frac{1}{2}$ -in. diameter by $\frac{3}{4}$ -in. maximum height. Power rating: $\frac{1}{4}$ watt, maximum rated voltage of 350 volts. Resistance: 100 ohms to 1 megohm.

Circle 53 on reader's service card

NEW MIGHTY MITE TUBE CHECKER, model TC136 (Mighty Mite IV), from Sencore, has new socket to



test the Amperex and Mullard 10-pin tubes used in many '65 color receivers.



Circle 55 on reader's service card


COLOR CRT CHECKER-REJUVENATOR, the Amphenol *CRT Commander*, tests each electron gun for relative life, cutoff, contrast range, gun balance in multi-gun tubes, has voltmeter measuring up to 50,000 volts. With adapter probe, meter can be used as 0-1,000 and 0-50,000 volt, 20,000-ohm-per-volt meter. As rejuvenator, Commander revitalizes cathode by exposing



new electron-emissive material and enlarging grid apertures. 9 x 12 x 5 in., 7 $\frac{1}{2}$ lb. Uses 117-volt/50-60 cycle ac power.

Circle 56 on reader's service card

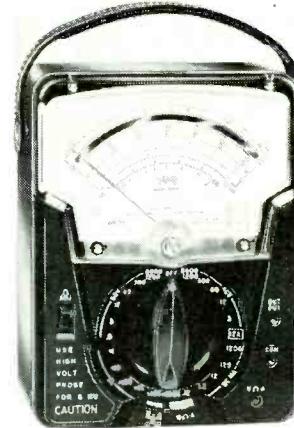ONE MILLION OHM PER VOLT VOM, Triplett 630-M. No amplifiers, no zero drift, no warmup, no power requirements. Has basic 1μ a-dec suspension movement which includes Triplett's bar-ring magnet. Makes current measurements



from 20 nanoamperes, voltage measurements from 5 millivolts, 20,000 ohm-per-volt ac sensitivity, $\pm 1\frac{1}{2}\%$ dc accuracy, $\pm 3\%$ ac accuracy.

Circle 57 on reader's service card

revolutionary new semiconductor transducer breaks all barriers that limit existing phono cartridges

TA-15 Low-mass Tone Arm

U-15 Semiconductor Cartridge


Euphonics MINICONIC®

Easily installed

- **Phenomenal 13 Octave Range.** DC to 50 kcps.
- **Silicon Semiconductor Elements.** 10,000 times the power of magnetics. World's most efficient, hum-free cartridge.
- **Lowest Effective Tip Mass.** Tracks 40 kcps 2nd harmonic pinch effects of 20 kcps fundamental—stylus tip stays in groove at all frequencies.
- **Elliptical Biradial Diamond Stylus.** No playback loss from outside to inside grooves.
- **Energy Derived from External Power Source.** Saves record grooves.



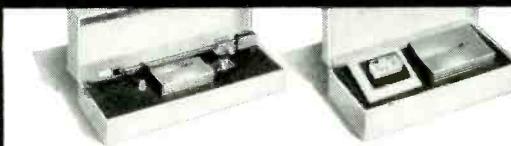See your distributor or write for "The Story of Euphonics Miniconic"



TK-15-LS Lab Standard Phono System. TA-15 low-mass arm, with U-15-LS plug-in cartridge (biradial diamond) and PS-15 power source. For magnetic or auxiliary inputs. **USER NET** **87.50**

TK-15-P Professional Phono System. As above, but with U-15-P cartridge and .5 mil tip conical diamond stylus. **USER NET** **71.50**

CK-15-LS Lab Standard Phono Conversion Kit. U-15-LS cartridge (biradial diamond) for standard heads, and PS-15 power source. For magnetic or auxiliary inputs. **USER NET** **55.00**

CK-15-P Professional Phono Conversion Kit. As above, but U-15-P cartridge with .5 mil tip conical diamond stylus. **USER NET** **39.00**

MADE IN U.S.A. © EUPHONICS CORP. 1965



AUTO SPEAKER REAR-SEAT KITS, 11 models from Oxford Transducer, designed for solderless installation. Feature heavy-gage plastic-coated wire, chrome-plated hardware, moisture-resistant switches and controls. *Custom Series* has impedance of 10-20-40 ohms, 5 models. *Deluxe Series*, 4 models, impedance of 8 ohms, 3-position switches (*Custom* and *Deluxe* have special model for Impalas and convertibles). *Standard series*, 2 models, 6 x 9 speaker and 5 x 7-in. size, 8-ohm impedance.

Circle 58 on reader's service card

AMPLIFIER AND TRANSDUCER SET (from Edmund Scientific) designed for variety of electronic, vibratory, light and sound tests and measurements, includes amplifier in pen-like housing and 8 basic probes: crystal diode, 3 attenu-

Euphonics MARKETING 173 W. Madison St., Chicago, Ill. 60602
FACTORY: GUAYNABO, PUERTO RICO, U.S.A.

Circle 109 on reader's service card


ators, vibration pickup, tape head, inductive and photovoltaic pickups, also earphone and miniature dynamic microphone. Amplifier may be used alone, or



output can be fed to earpiece, or voltmeter. Amplifier powered by 1.5-v Penlite battery. Case measures 10 $\frac{3}{4}$ x 7 $\frac{1}{2}$ x 1 $\frac{1}{2}$ in.

Circle 59 on reader's service card

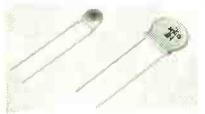
FLAT-BOTTOM DISC CAPACITORS for circuit-board mounting (applications up to 500 volts), from the Hi-Q Div. of Aerovox Corp., prevent rock 'n



roll on printed circuit boards, eliminate electrode exposure encountered with bare-bottom discs, permit lower circuit-board height without kinked leads. Long or short lead lengths.

Circle 60 on reader's service card

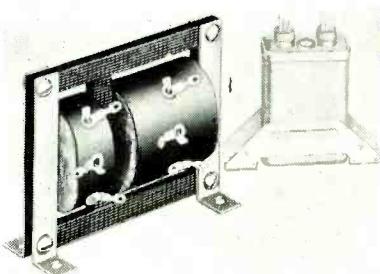CONSTANT-VOLTAGE TRANSFORMER for 2.5-7.5-volt-ampere requirements has been added to the O.E.M. line by Neshaminy Transformer Corp. 3 $\frac{1}{4}$ x 2 $\frac{1}{2}$ x 1 $\frac{1}{4}$ in.; can provide from



6.3 to 118 volts. Normal input voltage: 118 volts ac, 60 cycles. Output constant within $\pm 1\%$ rms with input-voltage fluctuations from 95 to 130 volts.

Circle 61 on reader's service card

TAPE HEADS AND ADAPTER MOUNTS, Nortronics QK 76 Quik-Kit, replacements for heads on Ampex pro-



fessional recorders. Adaptable to shield cups of Ampex head nests with one-time use of Quik-Kit. Rapid changeover of



Look what's happened to the RCA WR-51A FM Stereo Signal Simulator

...it got to be the WR-52A... NEW, REDESIGNED AND IMPROVED

Last year we decided to make a few improvements in our WR-51A Stereo FM Signal Simulator...for two years THE established test instrument for multiplex stereo servicing. We intended to call it the WR-51B. But one thing led to another and we made so many extensive improvements that we virtually had a new instrument on our hands. You're looking at it: the NEW RCA WR-52A STEREO FM SIGNAL SIMULATOR. We've added an RF Deviation Meter to measure the modulation level of both stereo and monaural FM signals. The meter is also used to accurately establish the level of the 19 Kc subcarrier.

We've included provisions for modulating left or right stereo signals with an external monaural source.

We've added a switch to disable the 19 Kc oscillator to provide a low-distortion monaural FM output.

We've added a new frequency (72 Kc)...required, along with the 67 Kc frequency, for trap alignment in some sets.

These features, together with numerous internal circuit design changes have resulted in a vastly improved, almost completely new instrument. And, the RCA WR-52A includes all those features that made its predecessor such a valuable servicing tool.

■ **COMPOSITE STEREO OUTPUT**—for direct connection to multiplex circuit

Choice of left stereo and right stereo signals

■ **RF OUTPUT**—for connection to receiver antenna terminals

100 Mc carrier, tuneable
Choice of FM signals—left stereo, right stereo, monaural FM, internal test and 60 cycle FM sweep
FM stereo deviation adjustable from 0-100%
100 Mc sweep signal adjustable from 0 to more than 750 Kc at a 60 cps rate
RF output attenuator

■ **CRYSTAL-CONTROLLED 19 Kc SUBCARRIER ($\pm .01\%$)**

■ **SINE WAVE FREQUENCIES**
Three low-distortion frequencies—400 cps, 1 Kc, 5 Kc
Two crystal-controlled frequencies—19 and 38 Kc
Additional frequencies—67 and 72 Kc for trap alignment

■ **READY PORTABLE**—weighs only 12 $\frac{3}{4}$ pounds, measures 13 $\frac{1}{2}$ " by 10" by 8"

■ **COMPLETE WITH WIRED-IN CONNECTING CABLES**

We also raised the price... just 50 cents. The WR-52A is now \$250.00.* Ask to see it at your Authorized RCA Test Equipment Distributor.

*Optional distributor resale price, subject to change without notice. May be slightly higher in Hawaii and the West.

RCA ELECTRONIC COMPONENTS & DEVICES, HARRISON, N.J.



The Most Trusted Name in Electronics

for successful

COLOR TV servicing

own these SAMS BOOKS



Color TV Training Manual, New Second Edition.

by C. P. Oliphant & Verne M. Ray. This newly revised comprehensive manual is the most up-to-date guide available for technicians preparing to service color TV receivers. Full information on: Colorimetry; Requirements of the Composite Color Signal; Make-up of the Color Picture Signal; RF and IF Circuits; Video, Sync & Voltage-Supply Circuits; Bandpass Amplifier, Color-Sync and Color-Killer Circuits; Color Demodulation; Matrix Section; Color Picture Tube & Associated Circuits; Setup Procedure; Aligning the Color Receiver; Troubleshooting. Includes full-color illustrations invaluable for setup, alignment, and troubleshooting. 224 pages; 8½ x 11". \$5.95 Order TVC-2, only.

Color TV Servicing Made Easy

by Wayne Lemons. Written in "made easy" style. Takes the mystery out of color TV servicing. Familiarizes you with color principles and setup adjustments; thoroughly covers color circuitry, adjustments, and servicing of all color TV sets produced to date. This book will help to put you into this fast-growing, profitable service work. 128 pages; 5½ x 8½". Order CSL-1, only. \$2.50

Know Your Color-TV Test Equipment

by Robert G. Middleton. Explains clearly and easily the function and circuit action of each color TV test instrument. Covers: White-Dot and Cross-Hatch Generators, Color-Pattern and Color-Bar Generators, Rainbow and NTSC Generators, Principles of Video-Frequency Sweep Generators and Testing, Lab-type equipment, and valuable setup information. Profusely illustrated. 160 pages; 5½ x 8½". Order KOC-1, only. \$2.50

Color TV Trouble Clues

Invaluable field-tested guide to trouble clues and procedures for color TV receiver repair. Describes types of troubles encountered, troubleshooting techniques, alignment and sync problems, convergence, etc. Includes data on use of test equipment to speed color TV servicing. Fully illustrated with photographs and schematics. A "must" for color TV service technicians. 96 pages; 5½ x 8½". Order COL-1, only. \$1.95

101 Ways to Use Your Color TV Test Equipment

by Robert G. Middleton. Written in the time-tested formula acclaimed by thousands of TV technicians. Shows you practical uses for your test equipment to diagnose color TV circuit troubles quickly and easily. Describes proper equipment hookups, how to evaluate test results, how to check instruments; includes time-saving techniques. 144 pages; 5½ x 8½". Order TEM-9, only. \$2.50

Color TV Guidebook

A special Howard W. Sams publication about color TV servicing techniques, equipment required, and related subjects. General information includes outlook for color TV manufacturers, broadcasting networks, and technicians. Specific sections deal with starting a color TV service business, troubleshooting and repair techniques, antennas, color tube stocking, transistorized color TV, small-town color TV problems, new circuits and developments. 8½ x 11". Order PFR-1, only. \$1.00

HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. RE-9, 4300 W. 62nd Street, Indianapolis, Ind. 46206

Send me the following books:

- TVC-2 KOC-1 TEM-9
 CSL-1 COL-1 PFR-1

Send FREE Sams Booklist. \$_____ enclosed

Name _____

Address _____

City _____ State _____ Zip _____

My Distributor is _____

IN CANADA: A. C. Simmonds & Sons, Ltd., Toronto 7

Circle 111 on reader's service card

track styles on Ampex 300, 350, 351, 400, 3,000 and 3,200 series tape recorders.

Circle 62 on reader's service card

LINEAR-ADMITTANCE CARDIODE MIKE, the Neumann U-64, distributed by Gotham Audio Corp. Frequency response from angles of sound-pickup great as $\pm 135^\circ$ from on-axis incidence.



This condenser mike includes amplifier using 7586 nuvistor; built-in switchable 10-db overload protection; foam-rubber anti-pop screen. Interconnect cable between U-64 mike and power supply uses 5-pin Cannon XLR connectors. Audio output is 3-pin XLR; mating connector and swivel microphone stand mount. Matte-satin chrome finish.

Circle 63 on reader's service card

TEMPERATURE AND ELECTRICAL TESTER, model 255 includes vom functions of Simpson's 260 plus addition of temperature range package of



+ 100° to + 1050°F. With ac clamp-on adapter, currents through 250 amps can be checked without disconnecting leads. With test leads and prods, 5-ft thermocouple lead and operator's manual.

Circle 64 on reader's service card


GHOST-KILLING ANTENNA, the Channel Master Coloray for metropolitan



TV, FM and FM stereo, has transposed phasing harness with impedance-balancing power equalizer circuit which kills ghost images and provides higher front-to-back ratios than 10-element Yagis cut to each specific channel. FM gain higher than turnstile type units. 23-in. crossarm; no external power required; matched for direct connection to standard 300-ohm receiver input; EPC gold coating.

Circle 65 on reader's service card

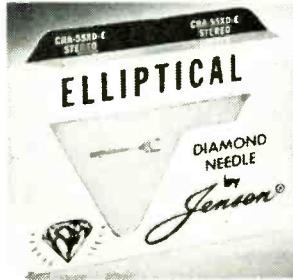JENSEN INDUSTRIES has introduced 36 types of elliptical diamond needles to equip most hi-fi sets, particu-




larly recent models of phonographs with lightweight force of less than 6 grams on record grooves.

Circle 66 on reader's service card

WIDE-BAND SCOPE KIT, KG-635, from Allied Radio. Vertical sensitivity: 17 mv rms per in. Response: ± 1.5 db, dc to 5.2 mc. Over-shoot less than 6%. Rise time 70 nanoseconds. Input impedance: 3 megohms shunted by 35 pf. Attenuator: frequency-compensated and calibrated .05, .5, 5 and 50 volts peak-to-peak per in. Horizontal sensitivity: 0.6 volt rms per in. Response: ± 1.5 db, 1 cycle to 400 kc. Expansion 2 times. Inputs: internal time base, 60 cycles phase-controlled, and external. Input impedance 7 megohms shunted by 25 pf. Linear time-base ranges: (5) 10-100 cycles; 100-1,000; 1-10 kc; 10-90 kc; 90-400 kc. Synchronization: "+" internal, "-" internal, 60 cycles and external. Locks from waveform fundamentals up to 5 mc, will sync on display amplitudes as low as 0.1 in. Line synchronization: phase-variable. Calibration voltage available at front panel jack. Accelerating potential: 1,650 volts. Z axis input impedance: 1 megohm. 10 tubes plus CRT and 2 rectifiers. 11½ x 7½ x 15½ in., 25 lb. Power: 110-130 volts, 50-60 cycle ac.

Circle 67 on reader's service card

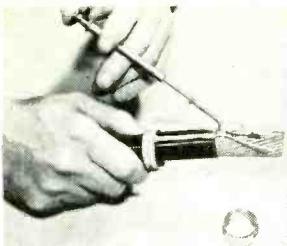EXTRACTOR TOOL FOR SHIELDED CABLE from Thomas & Betts Co., Plunger type device extracts center conductor. Available in 5 sizes which accommodate shield diameters of .055 in. through 0.248 in. Color-coded. After stripping insulation and flaring



braid, conductor tube slips over insulated wire until desired breakout point. With braid held firmly, wire is bent down and plunger is pushed, extracting lead from braid.

Circle 68 on reader's service card

UHF-VHF INDOOR ANTENNA, series 66 from Brach Mfg. for black-and-white and color TV reception. Model 6651 in chrome finish; model 6652




in chrome finish. Has elements with individually spring-loaded ball sockets for complete pivoting in critical signal areas.

Circle 69 on reader's service card


TRANSISTOR WALKIE-TALKIE, model RA-731 from Olson Electronics. Battery meter built into front panel. 45-in. telescoping antenna. Push-to-talk button and on-off volume switch on side of black wrinkle enamel case. Operates on 8 standard penlight batteries. Includes carrying strap and batteries.

Circle 70 on reader's service card

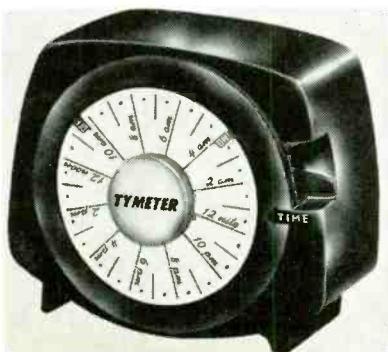ALL-PURPOSE TYMETER, APT-65 from Pennwood Numechron turns



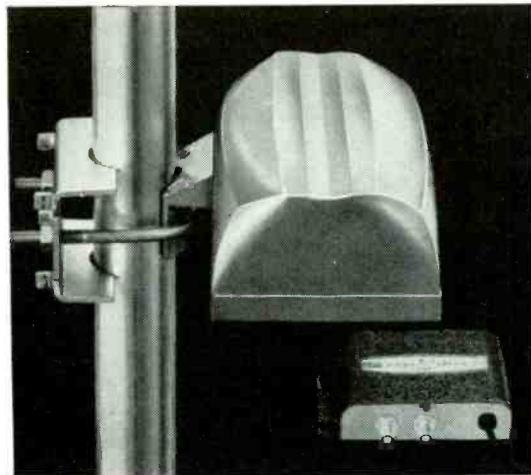"A professional quality TV system priced for the home?"



"Try this!"

"I understand that professional TV systems use 75 ohm coax."

"That's right. Because coax minimizes interference and ghosting."

"How's that?"

"It's shielded—doesn't pick up noise. Also, it's unaffected by changing weather conditions. With 300 ohm twinlead, moisture can play havoc with the signal."

"So, that's it."

"What's more, you can feed coax thru all types of surfaces, even near metal, without interfering with performance."

"I'd like to have a system with TV outlets all over the house—bedrooms, kitchen and patio."

"The new two-transistor Blonder-Tongue Vamp 2-75 is easy to install and it can deliver sharp, clear pictures to as many as 8 TV outlets."

"Sounds real professional. What about the cost?"

"The rugged, weatherproof amplifier with remote power supply lists for only \$44.95."

"I'm on my way to my dealer."

(This message was paid for out of the gross profits of BLONDER-TONGUE, 9 Alling St., Newark 2, N.J.)



Circle 112 on reader's service card

travel in style with stereo . . .



Auto-tape 500

Magnificent music of your choice surrounds you wherever you go in full dimensional stereo. No static noises, no fading, no commercials — just pure undistorted sound you never thought possible in a car.

Occupies minimum space under dash in most cars. Two speakers mount in doors or under dash for full stereo effect. Operates off 12 volt car battery.

Wide variety of music tapes in cartridges — never fuss with threading tape or turning reels — superb recordings by outstanding artists.

Charcoal black or stainless steel satin finish complements car decor. 2 speakers, sample stereo cartridge, hardware included.

From \$149.95



Ask your dealer for the Auto-Tape 500 or write to factory

**MADE BY SKILLED
AMERICAN CRAFTSMEN**
Viking OF MINNEAPOLIS


9600 Aldrich Avenue So. Minneapolis, Minn. 55420

Circle 113 on reader's service card

lights and appliances on and off. Time range: minimum ON time, 15 mins; minimum OFF, 1 hr; maximum ON time, 23 hr; maximum OFF, 23 hr and 45 min. 5 x 4 x 2½ in., 2 lb, 6-ft cord.

Circle 71 on reader's service card

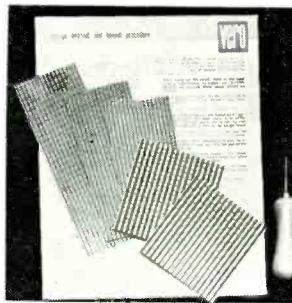BREADBOARD KIT model BK-6 from Vero Electronics, has 6 assorted Veroboard universal wiring boards, Vero



spot face cutter and complete instructions on designing component layout directly on wiring board.

Circle 72 on reader's service card

SUPPRESSKITS, types SK-10, -20 and -30, from Sprague Electric, each specifically designed for installation in Chrysler, Ford and General Motors vehicles having alternator electrical supply systems. Include L-C networks and heavy-duty Thru-pass capacitors to han-



dle the hash and eliminate whine caused by alternator output. Effective interference suppression through 400 mc.

Circle 73 on reader's service card


TAPE RECORDER, Sony Super-scope model 135, dual-track, monophonic. Power 117 volts, 60 cycles. Speeds 3½ and 1½ ips. Response: 90–9,500 cycles at 3½.



Signal-to-noise better than 40 db. Flutter and wow less than 0.3%. No level indication required. One mike, one auxiliary input. Monitor headset output. 9½ x 11 x 5½ in., 7½ lb. 5-in. reel capacity, tube amplifier.

Circle 74 on reader's service card

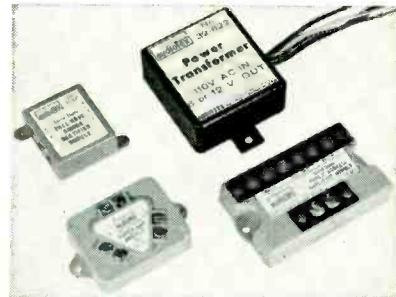SOLID-STATE MODULES, Home Electronics, (Audiotex), consist of 12 com-



patible modules including several amplifiers, a preamp, code oscillator, flasher, power supply, etc.

Circle 75 on reader's service card

UNDER-DASH REVERBERATION UNIT, Stereo Magic, from the Tenna Corp., is 1½ x 9 x 4 in. 3 models: RR-13-R has 6 x 9 in. speaker; RR-14-R



with special 6-in. round speaker for convertibles and RR-15-R without a speaker for cars already equipped with speaker. Chrome with brushed aluminum and wood grain finish.

Circle 76 on reader's service card

COMPACT BRISTOL MULTIPLE-SPLINE SCREWDRIVER SET 99PS-60, from Xcelite, consists of regular-size 4½-in. screwdriver handle, 9 inter-



changeable 4-in. Bristol multiple-spline blades with major diameters from .048 to 0.183 in. and 4-in. extension shaft. Handle and extension feature new positive locking device.

END

Circle 77 on reader's service card

NEW LITERATURE

All booklets, catalogs, charts, data sheets and other literature listed here are free for the asking (except where a price is given). Each item is identified by a Reader's Service number. Turn to the Reader's Service Card facing page 72 and circle the number of items you want. Then detach and mail the card. No postage required!

NEW COMMERCIAL COMPONENTS CATALOG, Amphenol Connector Div. No. CC-1. 68 pages, looseleaf-punched; photos, diagrams and specs on relay plugs and sockets, microphone connectors, 110- and 125-volt plugs and receptacles, rack and panel units, printed-circuit connectors, miniature power connectors and hermetic seal units.

Circle 78 on reader's service card

BROCHURE, The Open Door to TV Profits, describes Windsor Electronics' television picture-tube rebuilding equipment, which will rebuild black-and-white, bonded-face and color cathode-ray tubes. 16 pages, photos.

Circle 79 on reader's service card

COMMERCIAL TV ANTENNAS, TACO Catalog No. 610. 6-page foldout, drawings and callouts, specs on 5-, 8- and 10-element ruggedized Yagi antennas, and cylindrical parabola antennas.

Circle 80 on reader's service card

PAMPHLET, Some Plain Talk from Kodak About Sound Recording Tape, 24 pages, many photos, explains: difference between low-print, general-purpose and high-output tapes; how bias settings affect overall performance; how tape-surface smoothness relates to high-frequency response; what torture tests tell about break strength.

Circle 81 on reader's service card

COMPACTRON FOLDER, ETG-3980. 4-page folder gives information on General Electric's space-saving compactrons for small TV units, including operation, mounting versatility and other application details, plus comparison with typical complement of conventional tubes, transistors or diodes needed for "tiny vision" sets.

Circle 82 on reader's service card

SOLDERING BULLETIN, TR 1014, illustrated, 5 pages, from Alpha Metals, discusses four major considerations: properties of joints, selection of materials, geometric design of the soldered connections, determination of production methods.

Circle 83 on reader's service card

DESIGN AID BROCHURE, RF and Microwave Dielectric Heating System Design Parameters, from the Industrial Applications Lab of Eitel-McCullough, contains: means of generating rf power at microwave and lower frequencies; means of coupling rf fields to material to be processed; detailed information on parameters of materials such as dielectric constants, loss constants.

Circle 84 on reader's service card

BOOKLET, What's This Stuff?, describes the Photo/Phonic School (audio-visual courses on how to use a still or movie camera to tell a story) of National Camera. An adjunct to their camera-repair correspondence course.

Circle 85 on reader's service card

FERROXCUBE ENGINEER, Vol. 7, No. 2, has features on designing linear transformers, digital recording heads and light-dependent resistors. 8 pages, looseleaf-punched.

Circle 86 on reader's service card

DATA SHEET TM-103 gives specs and block diagram of Philco's model 351A Solid-State Tracking Signal Generator, which covers 10 kc to 15 mc.

Circle 87 on reader's service card

FASTENER CATALOG, No. 65. 100 pages, punched, illustrated of Active Screw & Mfg. Co.'s line of: hexagon-head cap, lag, machine, metallic drive, set, tapping, thread-cutting and wood screws; carriage and machine bolts, inserts, lock nuts, nylon fasteners, retaining rings, sems, spring pins, thread-cutting sems, flat washers.

Circle 88 on reader's service card

ELECTRIC APPLIANCES \$3 TO \$5 AN HOUR

fix FREE BOOK tells about it. Our complete, easy profitable spare-time or full-time business starts right now! \$3.25 a week, right at home! 400 MILLION Appliances now in use. People need them fixed. YOU make good money doing now.

NATIONAL RADIO INSTITUTE, Appliance Div. Dept. 503-085, Washington 16, D. C. Send Free Book, Free Appliance Repair Course Lesson. Name..... Address..... City..... Zone..... State.....

New! 8 Channel top-performance CB and AM broadcast radio for only \$99.50



BANNER 85 combines two radios with top performance in both CB and AM broadcast operation!

Hallmark technology has done it again! The sensational new BANNER 85 is an 8 channel, crystal-controlled CB with a built-in AM broadcast band to give you two radios for one low price!

And, you'll get unexcelled Hallmark performance from both. With rugged, hand-wired construction, the CB operation features 0.3μv for 6db S+N/N ratio; 45db selectivity; 4 watts power output and high level modulation. The full fidelity broadcast operation outperforms most AM car radios.

Join the HELP program now with the reliable, low-cost BANNER 85. Write today for complete information.


FCC rules, part 95, applicable to Banner 85 operation.

HALLMARK INSTRUMENTS

P. O. BOX 10941 • 2620 FREEWOOD • DALLAS, TEX. 75220 • (214) FL 7-0184

Circle 114 on reader's service card

FREE

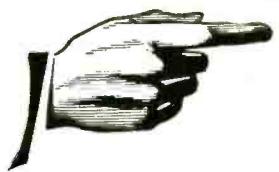

508 VALUE-PACKED PAGES
including exclusive products and
special values available only

from **ALLIED**

send today for your
ALLIED
1966 CATALOG
world's largest selection

SAVE MOST ON:

Stereo Hi-Fi
Tape Recording
CB 2-Way Radio
FM-AM & AM Radios
Short Wave Radios
Portable TV • Phonographs
Amateur Gear
Intercoms & P.A.
Automotive Electronics
Test Instruments
TV Tubes & Antennas
Power Tools, Hardware
Parts, Tubes, Transistors

MORE OF THE BEST IN ELECTRONICS FOR EVERYONE

EASY TERMS
Use the convenient
Allied Credit Fund Plan
—over 24 months to pay

82

ALLIED RADIO
The World's Largest Electronic Supply House

*satisfaction
guaranteed or
your money back*


RADIO-ELECTRONICS

SPECIAL in your **FREE** 1966 ALLIED CATALOG


see what's new in the wonderful world of **knight-kits®**



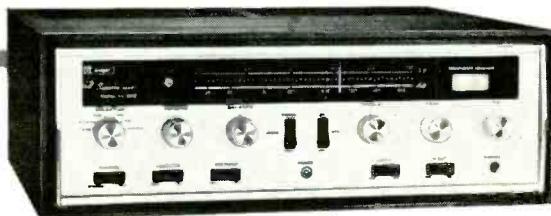KG-895 Superba Series
120-Watt Solid-State
Stereo Amplifier Kit. \$149.95



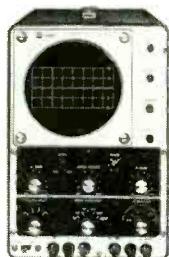
KG-964 Superba
Series 64-Watt Solid-
State FM-AM Stereo
Receiver Kit.
\$189.95



KG-635 5-Inch DC
to 5.2 Mc Wide-
band Oscilloscope
Kit. \$99.95



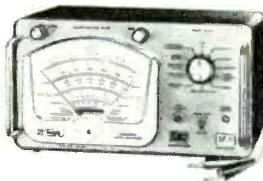KG-371 Solid-State
Auto DC Power
Timing Light Kit.
\$19.95




KG-375 Solid-State
Universal Auto Ana-
lyzer Kit. \$49.95



Safari-I Deluxe
23-Channel Citizens
Band Transceiver Kit. \$129.95



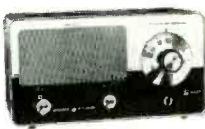C-540 Low-Cost
5-Watt Citizens
Band Transceiver
Kit. \$49.95



KG-221 FM Moni-
tor Receiver Kit
(police, fire, ma-
rine, weather
bands, etc.) \$39.95



KG-201 Solid-State
Motor-Speed/Light
Control Kit. \$9.95



KG-415 Superba
Series Professional
Solid-State Stereo
Tape Deck Kit.
\$249.95

Knight-Kit GUARANTEE: Buy any Knight-Kit. Build it. Operate it. You must be satisfied or we refund your money.

THERE IS A knight-kit FOR EVERY NEED!
easiest to build—enjoy big savings

- Stereo Hi-Fi
- CB 2-Way Radio
- Short-Wave
- Hobby Kits
- Test Equipment
- Automotive
- Intercom
- Amateur Gear

FREE

Send today for your
508-page Allied 1966
value-packed catalog



send for your 508-page 1966 Allied Catalog

FREE!

ALLIED RADIO, Dept. 2-J

100 N. Western Ave., Chicago, Ill. 60680

Send FREE 1966 Allied Catalog

Name _____
PLEASE PRINT

Address _____

City _____ State _____ Zip _____


ALLIED RADIO

Circle 115 on reader's service card

TECHNOTES

HEATH GD-973 SCR SPEED CONTROL

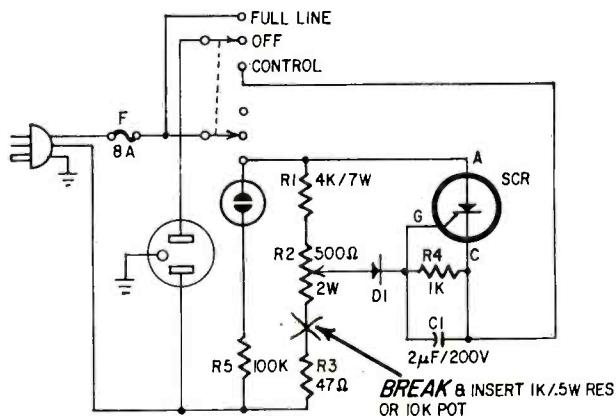This unit was found to have a very limited speed-control range. The speed control functioned only over about 10° of rotation and speed was unaffected over the remaining 350°. The trouble seemed to be a silicon controlled rectifier with very low gate sensitivity. To overcome this defect, I increased



the value of resistor R3 from 47 to 1,000 ohms. This increased the gate voltage, thereby increasing the speed control range.


If the unit is to be used with several devices having different power requirements or in areas where the line voltage varies, I would recommend that a 10,000-ohm potentiometer be inserted in series with R3 to vary the control range more easily.—Sol Libes

GRUNDIG MONO RECORDER TK14

Symptom: Record and playback OK, level-indicator tube does not show record level.


Fault: Bare jumper between pins 9 and 7 on level-indicator socket shorting to pin 8.

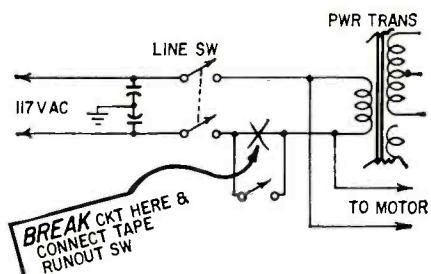Cure: Insulate jumper. Be careful not to alter the position of the level-indicator while doing this—adjustment is difficult. The tube must line up correctly with the slot in the cover panel. To remove the cover panel, hold all the function keys down on both sides about halfway. This will allow the plate to slip off easily.—Steve P. Dow



KORTING 158 AND 158S STEREO RECORDER

The Korting 158 and 158S recorders are equipped with an automatic limit switch which stops the motor on play or record when the tape runs out. It opens the common lead in the synchronous-motor feed circuit from the secondary of the power transformer. Rewiring the switch as shown in the diagram will allow the automatic limit switch to turn the entire machine off when the tape runs out. The leads going to the switch should be dressed away from all audio circuits. Follow the same wiring path that the original leads took to

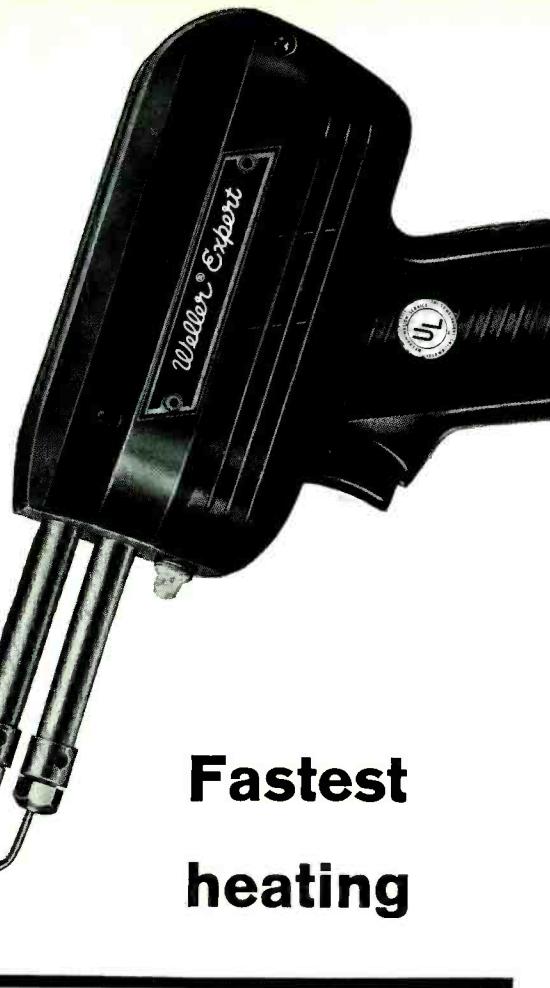

gun in the world

A Weller gun reaches full soldering temperature up to 40% faster than other guns. This is just one of the reasons why Weller is the choice of nearly all professional electronic service technicians.

Weller guns also have trigger-controlled dual heat that permits instant switching to high or low heat to suit the job. They deliver the most heat per rated watt, resulting in the greatest soldering efficiency.

When you buy a soldering gun, be sure to insist on Weller.

Weller Dual Heat Guns and Kits come in wattage ranges from 100 to 325, priced from \$6.95 to \$12.95 list.

Weller®

WELLER ELECTRIC CORP., EASTON, PA.

In Canada: Kingston, Ontario • In England: Horsham, Sussex

World Leader in Soldering Technology

Circle 116 on reader's service card

the switch from the power transformer. Don't forget to connect the original leads together after removing them from the limit switch.

The mechanism bypasses the automatic shutoff if the tape is being wound fast in either direction. When the stop button is pressed, that bypass interlock switch is reset, allowing the unit to warm up while tape is being loaded.—Steve P. Dow

SAFE WAY TO KILL HORIZONTAL "HASH" DURING TV ALIGNMENT


It is usually necessary to disable the horizontal sweep when aligning TV tuners or i.f. strips, to eliminate "hash" from the response curve trace. Pulling the horizontal output tube or fuse reduces B-plus loading enough to affect the alignment, and pulling the horizontal oscillator overheats the output tube.

Try pulling the horizontal oscillator tube after applying a negative bias to the horizontal output tube grid. You can make up a bias box in minutes with a 45-volt battery and a potentiometer.—Glen H. Bryant

OLD G-E 250 RADIO GETS A NEW POWER SUPPLY

This three-way set had been dead and forgotten for years when the owner decided to have it looked at. I found it needed a new 2-volt wet battery, synchronous vibrator and buffer capacitor. The owner said he didn't want the portable feature any more—just ac operation. That still required the vibrator, because B-plus came from the vibrator transformer and was rectified by the synchronous vibrator.

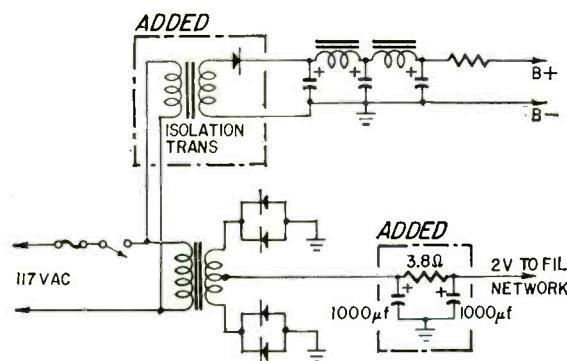I decided to eliminate the vibrator supply, and installed



a new isolation transformer with a selenium rectifier for B-plus. The filament supply was retained, but I added some filtering as shown in the diagram.

The modified set worked very well, and the owner was especially pleased that the hum he remembered was gone. Cost of the new parts was less than that of replacing the old ones, and the new supply will need almost no maintenance.—Paul B. Lavallee

THE TV UPSTAIRS

Seems like the reason I stick to this business is I never know what I'm going to run into on a service call.

I get a call from this fellow and it's not his set he wants fixed, it's his neighbor's upstairs. We go upstairs and the neighbor lets us in. He's got a RCA KCS-68-C chassis. The set plays just fine, sometimes an hour, sometimes 2 hours, sometimes all night. When it goes off, the raster disappears, the fellow gets up, does a little Indian rain dance on the floor, and the raster reappears. Well, the downstairs neighbor has lost a lot of sleep over this and has agreed to have the set fixed if the fellow will stop stamping on his ceiling.

I took the back off and, when the raster was off, I found

**add an fm-stereo service center
with this one new
sencore unit!**



THE SENCORE MX129 FM STEREO MULTIPLEX GENERATOR & ANALYZER

FM-Stereo growth continues to mount and is fast becoming as big a field as Color TV. This means more FM-Stereo service business for you, now and in the future. Is your shop equipped? It can be—completely and economically—with the MX129, the FM-Stereo "Service Center in a Case." The instantly stable, 19-Transistor, crystal controlled MX129 is the most versatile, most portable (only 7½ pounds), most trouble free and efficient multiplex unit on the market—just like having your own FM-Stereo transmitter on your bench or in your truck. Powered by 115 volts AC, it produces all signals for trouble shooting and aligning the stereo section of the FM receiver . . . can be used to demonstrate stereo FM when no programs are being broadcast. Self-contained meter, calibrated in peak to peak volts and DB, is used to accurately set all MX129 controls and as an external meter to measure channel separator at the FM-Stereo speakers. NO OTHER EQUIPMENT IS REQUIRED.

\$169.50
only

SIGNALS AVAILABLE FOR ALIGNMENT, TROUBLE SHOOTING AND ANALYZING:

FM-RF carrier with composite multiplex audio signal with 38kc suppressed carrier, 19kc pilot and 67kc SCA signals • Multiplex signal formed by 60 or 1000 cycle internal tones or any external signal • Full control over left and right channel amplitude (modulation) • External 67kc SCA signal available for trap adjustment • Composite signals available for signal injection FM detector •

professional quality—that's the difference!

SENCORE

426 SOUTH WESTGATE DRIVE • ADDISON, ILLINOIS

Circle 117 on reader's service card

new Webster band-spanner. "565"



CITIZENS BAND 2-WAY RADIO

Low in price... ultra-compact... high in performance... ideal for business and personal use. Both a 2-way radio and a p.a. system.

Fully transistorized... uses effective planar silicon transistors • Extremely low standby drain on battery—no tube filaments • 5-channels • 5-watts power input • "Tiny-lamp" gives positive indication of amplifier operation and modulation • Two-stage noise limiter • Adjustable squelch • 1½" H, 6¼" W, 7½" D.

\$129.95

Suggested price

Please send information on "565" C-B radio

Name _____
Number _____ Street _____
City _____ State _____ Zip Code _____

WEBSTER 317 Roebling Rd. So., San Francisco, Calif.

Circle 118 on reader's service card

Designed and manufactured in U.S.A.

**NEVER
A BURNOUT**
IN 6 EMC DIODE-PROTECTED VOMS

NOBODY ELSE BUT EMC DESIGNS IN SO MUCH VALUE!
• Professional quality and versatility • Lifetime protection against electrical abuse • No meter burnout, needle damage, or fuse replacement

VOLOMETER

Model 109A Factory Wired & Tested \$27.95

Model 109AK Easy-to-Assemble Kit \$20.25

20,000 Ω/V DC sens. 10,000 Ω/V AC sens. 4½" 40μa meter. High impact bakelite case. 5 DC voltage ranges: 0-6-60-300-600-3000v. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 3 DC current ranges: 0-6-60-600ma. 3 AC current ranges: 0-30-300ma; 0-3A. 3 resistance ranges: 0-20K, -20K, -20 megs. 5 db ranges: -4 to +67db. With carrying strap. 5½" W x 6¾" H x 2⅜" D.

VOLOMETER

Model 103A Factory Wired & Tested \$19.75

Model 103AK Easy-to-Assemble Kit \$15.90

4½", 2% accurate, 800μa D'Arsonval type meter. One zero adjustment for both resistance ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 DC voltage ranges: 0-6-60-300-600-3000v. 5 db ranges: -4 to +64db. 5 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-120ma; 0-1.2A. 2 resistance ranges: 0-1K, 0-1 megs. 5½" W x 6¾" H x 2⅜" D.

POCKET SIZE VOLOMETER

Model 102A

Factory Wired & Tested \$15.90

Model 102AK Easy-to-Assemble Kit \$14.10

3½", 2% accurate 800μa D'Arsonval type meter. One zero adj. for both res. ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 DC voltage ranges: 0-6-60-300-600-3000v. 3 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-130ma; 0-1.2A. Resistance: 0-1K, 0-1 megs. 3¾" W x 6¾" H x 2" D.



plenty of high voltage on the top cap of the 1B3 but no rectified high voltage. With the lights in the room off I looked for the filament glow in the 1B3. There was none. But just then I saw some arcing underneath the socket. I shut the set off and examined the socket. There was a fracture in the solder joint that connects the rectifier winding to the 1B3 socket. I resoldered the joint and went away, leaving everyone smiling.—*Sid Elliot*

REVERSED-POLARITY ELECTROLYTICS IN FORD RADIOS

Two 1962 and 1963 Ford Radios (models 2TBO and 3TBO) were in the shop with the same complaint: oscillations and motorboating. The same repair cured both.

In the rf amplifier (Fig. 1) and the first audio stage (Fig. 2), sections A and B of C2 are both connected the

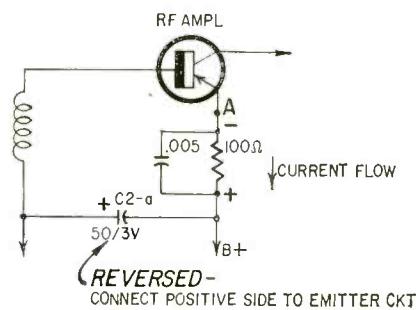


Fig.1

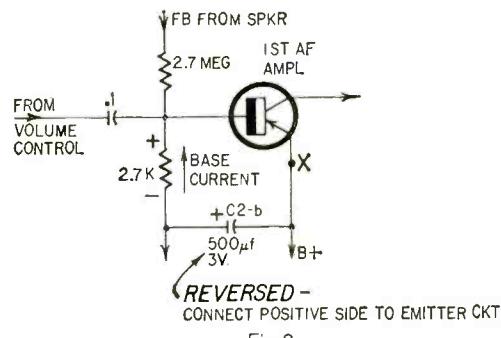


Fig.2

wrong way. I found this in both receivers and I assume it is so in all because Bendix service literature shows the capacitor hooked up with the wrong polarity.

Because the dual capacitor has the negative lead common to both sections, one at least has to be replaced. I replaced the 50-μf section. I re-formed the 500-μf, 3-volt unit and it checked OK. The lead from C2-A should be clipped.

The problem does not arise immediately because the low reverse voltages do not ruin the electrolytics for quite some time.—*James R. Giles*

LESSON WITH RELUCTANCE

I whipped the little foreign car around another tight corner. No use: the siren came closer. Another block and a red light glared as a gruff voice yelled "Pull it over!" I did, dreading what I knew would come. "Follow us!" and I did. They ran away from me. After all, a Volkswagen can't beat a police cruiser. But I was pretty close when we got to the police station. Grabbing my kit, I rushed inside. A burly cop shoved me into an inner room.

On the desk sat the remote control unit for the police radio. "Fix it!" said the cop.

"What's the matter?"

"It won't talk!"


Picking up the mike, I spoke the magic words: "City PD testing, 1, 2, 3, 4." The db meter barely moved. Cranked up the mike gain control. No soap.

On the way to the shop, I thought, "This is a variable-reluctance mike. I've got a replacement cartridge for it. Or have I? The one on the shelf's not in a box! Golly, maybe it's an old one! Have to test it and see."

In the shop—ee-gad! All benches full! Audio signal tracer out of order! Now you remember it! What to do? Hey! TV set on bench, disassembled; sound still good, even if nothing else works. Ah-ha. Connect mike to sound input, use audio amplifier stage for audio signal tracer. Smart idea, there, boy. Good thinking.

Take out cartridge of mike. Clip it to top of volume control and chassis. Now blow in it. Hm. No blow. Bad. Try new (?) one. Oops. No blow there either! Now you're up the creek, smart alec! Think. Turn the volume down on TV, so the sound won't bother you. There. Hey! Where's that sound coming from? The mike? Oh, yes, the mike's still hooked across the volume control, and any mike will act as a speaker. Hey, wait a minute. This is the "new" cartridge, and it sounds clear, and pretty loud. Try the old one. Hmm. Very weak, distorted; try new one again. Loud and clear. Hooray.

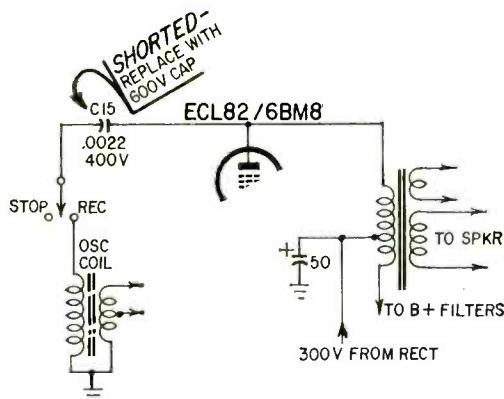Back in the shop, after putting the police back on the air. Remember, knucklehead, from now on, that you can test about any kind of microphone except a carbon or a ribbon (velocity) type, by feeding a low-level audio signal into it and listening, just as well as hooking it to an amplifier and talking into it.—Jack Darr



NORELCO/PHILIPS 300 (EL 3542A)

Symptom: No recording. Playback OK. When recording button is depressed, level-indicator tube extinguishes. Hum in speaker.

Trouble: C15, a .0022- μ f bias coupling capacitor, is shorted, grounding plate 6BM8 through oscillator coil. This shorts the B-plus feeder through the output transformer and kills the voltage to indicator tube, causing hum in speaker. Replace with 600-volt capacitor.—Steve P. Dow

G-E M3 AND OTHER SETS WITH HORIZONTAL MULTIVIBRATOR

Symptoms: Off channel, the set had a normal bright raster with the usual noise. When the tuner was turned to an active channel, the horizontal sweep would collapse with loss of brightness and then complete loss of high voltage at the CRT anode. The audio remained normal at all times. When the tuner was turned off channel, the raster would return with good brightness.

The trouble turned out to be a shorted diode in one section of the germanium phase detector. Due to the biasing in this circuit, the oscillator ran near to normal frequency when no sync pulses were present; but when a video signal was applied, the sync pulses biased the oscillator so that the frequency was out of range of the horizontal output transformer.—Fred W. Rodey



NEW JERROLD **COLORAXIAL™** Reception System

The old familiar twinlead, that worked pretty well for black-and-white TV, is hopelessly inadequate for color reception. When your customers complain about changes in color, ghosting, and smearing of pictures, chances are the fault lies squarely with the twinlead connecting the set to the antenna.

What's the answer? Jerrold announces the exciting Coloraxial TV Reception System—an absolute necessity for color, and also best for black-and-white and FM stereo. With Coloraxial, you can quickly convert any outdoor antenna to shielded coax operation. Installs anywhere in minutes, without need for standoff insulators or the fear of running near metal objects.

Your customers will welcome the predictable, perfect reception that's assured with a Coloraxial system. And you'll welcome the simplicity and profitability of a Coloraxial installation. Jerrold Coloraxial Kits give you everything you need for a quick, perfect job: 50 or 75 feet of sweep-tested, shielded RG-59/U cable with fittings already on; matching transformers for both ends of the cable—even Coloraxial (75-ohm) antennas and preamplifiers where the job calls for them.

Talk with your Jerrold distributor today about Coloraxial, or send coupon for complete information.

JERROLD

Jerrold Electronics Corporation
Distributor Sales Division
15th & Lehigh Ave., Philadelphia, Pa. 19132

Send me complete information on the new Jerrold Coloraxial TV Reception System.


Name _____

Company _____

Address _____

City _____ State _____ Zip _____

Circle 120 on reader's service card

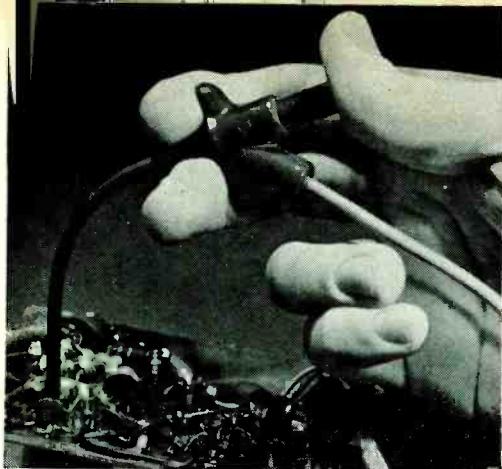


TRY THIS ONE

MODERN TUBES FOR ANTIQUE RADIOS

Briefly, the antiquer the radio, the unavailability of the tube. If you want to restore antique sets to working order, you will have to use modern tubes, but if you modify the sockets or wiring you destroy the radio's value as an antique.

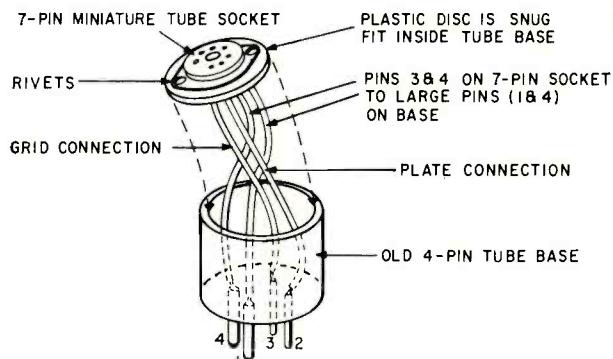Here is a way to make adapters that fit seven-pin miniature tubes to old four-pin sockets.



Get a base from an old four-pin tube, remove it and clean out the old wires and glue. Cut a disc of Micarta to a snug fit inside the old base. Then cut a $\frac{5}{8}$ -inch hole in the center of the Micarta disc to take a seven-pin miniature-tube socket (which can be a ring-mount type, or fastened with rivets). Now solder short wires from the seven-pin tube's plate, grid, heater and cathode terminals to the corresponding pins of the four-pin base. Consult a tube manual for base connections.

Clever Kleps 30

Push the plunger. A spring-steel forked tongue spreads out. Like this  Hang it onto a wire or terminal, let go the plunger, and Kleps 30 holds tight. Bend it, pull it, let it carry dc, sine waves, pulses to 5,000 volts peak. Not a chance of a short. The other end takes a banana plug or a bare wire test lead. Slip on a bit of shield braid to make a shielded probe. What more could you want in a test probe?



Available through your local distributor, or write to:

\$147

RYE SOUND CORPORATION
127 Spencer Place, Mamaroneck, N.Y.

Circle 121 on reader's service card

MR. SERVICEMAN

STANCOR

THE COMPLETE LINE

**FLYBACKS • YOKES • VERTICAL OUTPUTS
AUDIO OUTPUTS • RF AND IF COILS
POWER • WIDTH AND LINEARITY COILS**
• EXACT TUBE-IN-SOCKET REPLACEMENTS
• NO EXTRA HARDWARE
• NO CIRCUIT MODIFICATIONS
• COLOR--BLACK & WHITE

FOR 11 MAJOR MANUFACTURERS*
LAST 7 MODEL YEARS
* AND MOST OTHERS



Ask your Distributor for a copy of the new TV Replacement Guide

Stocked by over 1000 Service Parts Distributors — Back up Stock • Chicago • Dallas • Los Angeles • New York

ELECTRONIC MARKETING DIVISION
ESSEX WIRE CORPORATION
3501 W. Addison Street
Chicago, Illinois 60618

In products, performance, purpose . . . Essex measures up!



Circle 122 on reader's service card

RADIO-ELECTRONICS

For example, to replace a 201-A with a 6AB4, wire pins 3 and 4 of the 6AB4 socket (the heater) to pins 1 and 4 (the large ones) of the four-prong base. Run a jumper at the seven-pin socket from the 6AB4 cathode terminal (pin 7) to whichever heater (filament) terminal is negative in the antique set. The 6AB4 grid (pin 6) goes to pin 3 on the four-pronger, and the plate (pin 1) to pin 2.

In many old sets, regeneration was controlled by the filament rheostat. If a converted antique is to be operated on ac, it is best to use a pot to control the plate voltage instead.—*Robert E. Flanagan*


USE YOUR VOLT-OHM-MILLIAMMETER TO SET IGNITION DWELL ANGLE

Many readers of RADIO-ELECTRONICS tune up their own cars. Those of you who don't own a dwell-angle meter may wish you did. It so happens that you already have a pretty fair dwell-angle indicator but never realized it—your vomm.

Here's how to use it to indicate point dwell:

1. Disconnect the low-tension lead from distributor breaker points to the coil primary.
2. Zero your vomm on any of its ohm ranges.
3. Connect the ohmmeter leads between ground and the disconnected breaker-point lead. Use the starter to crank the engine and read the meter.
4. The meter will read, as a percentage of full scale, the percentage of time the breaker points are closed. Read a dc voltage (not ohms) scale to determine this percentage. For example, a 6.66-volt reading on a 10-volt scale (or an 8-volt reading on a 12-volt scale) means the points are closed two-thirds of the time. This means that the dwell angle would be 30° for an 8-cylinder car or 40° for a 6-cylinder car. The relationship between meter reading and dwell angle is expressed by the formula $D = \frac{360R}{N \times S}$ where R = meter reading in volts, D = dwell angle in degrees. N = number of cylinders, S = meter range you're using (dc volts).—*James G. Barr*

FUSE YOUR CHEATER BOX

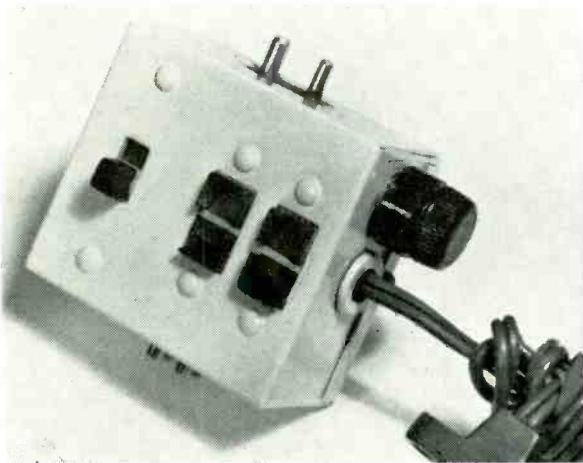

After blowing fuses in a customer's home, I decided it would be less embarrassing to blow my own. So I installed a bayonet type cartridge-fuse holder in my Sencore cheater box (photo). A 3-amp fuse serves me well.—*William Cotton*

MAKE YOUR OWN CLOSE-TOLERANCE RESISTORS

When you need a 1% resistor, you can make one to the exact value you need with an ordinary 5% or 10% carbon resistor, a hot soldering iron and a Wheatstone bridge.

eliminates the time consuming method of unsoldering and resoldering when checking capacitors

The new Model 1400 is the only capacitor to do the whole job. It will quickly find whatever defects exist in a capacitor, no matter how elusive. It will also check electrolytics, bypass, coupling, blocking and filter capacitors, all without disconnecting them from the circuit.

SPECIFICATIONS	Tests In-Circuit	Tests Out-of-Circuit
SHORTS TEST —Detects shorted capacitors of all types incircuit with shunt resistance as low as 6 ohms.	✓	✓
OPENS TEST —Detects open capacitors for all values in-circuit down to 7 mfd., with shunt resistance as low as 15 ohms.	✓	✓
VALUE TEST —Indicates value of electrolytics in-circuit from 2 mfd. to 450 mfd.	✓	✓
HI-LEAK TEST —Detects those hard-to-find leaky capacitors out-of-circuit; Sensitive to 150 megohms... Tests made at 300V D.C.		✓

See your parts distributor... or write for complete catalog

MERCURY ELECTRONICS CORP., 111 Roosevelt Ave., Mineola, New York 11501
IN CANADA: William Cohen Corp., 8900 Park Ave., Montreal

Circle 123 on reader's service card



\$2950
Net

Model 1400 IN-CIRCUIT CAPACITOR TESTER... Saves valuable servicing time

EXCLUSIVE — HI-LEAK TEST

Detects those hard-to-find leaky capacitors (out-of-circuit)... leakage sensitivity to 150 megohms.

EXCLUSIVE — Special low test voltage of 2.9 volts provided to prevent damage to the new low voltage electrolytics used in transistorized equipment.

BUILD2ORADIO

CIRCUITS AT HOME

with the New Progressive

RADIO "EDU-KIT"®

All Guaranteed to Work!

PRACTICAL
HOME
RADIO
COURSE only
\$26.95

NOW INCLUDES

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ AMPLIFIER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR



Reg. U.S.
Pat. Off.

TRAINING ELECTRONICS
TECHNICIANS SINCE 1936

- * No Knowledge of Radio Necessary
- * No Additional Parts or Tools needed
- * Excellent Background for TV
- * School Inquiries Invited
- * Attractively Gift Packed

FREE EXTRAS

- SET OF TOOLS • RADIO & ELECTRONICS TESTER • ELECTRIC SOLDERING IRON • TESTER INSTRUCTION MANUAL • MEMBER-SHIP IN RADIO-TV CLUB: CONSULTATION SERVICE • HI-FI GUIDE
- QUIZZES • TV BOOK • FCC AMATEUR LICENSE TRAINING
- RADIO BOOK • PRINTED CIRCUITRY • PLIERS-CUTTERS
- ALIGNMENT TOOL • WRENCH SET • CERTIFICATE OF MERIT
- VALUABLE DISCOUNT CARD

YOU DON'T HAVE TO SPEND
HUNDREDS OF DOLLARS FOR A RADIO COURSE

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a rock-bottom price. Our Kit is designed to train Radio Electronics Technicians, making it the easiest method of home training. You will learn radio theory, construction and servicing. This is a COMPLETE COURSE IN EVERY DETAIL.

You will learn how to build radios, using regular schematics; how to wire and solder in a professional manner; how to service radios. You will work with the standard type of punched metal chassis, as well as the latest development of Printed Circuit chassis.

You will learn the basic principles of radio. You will construct, study and work with Receivers, Amplifiers and oscillators, detectors, rectifiers, test equipment. You will learn and practice code, using the Progressive Code Oscillator. You will learn and practice trouble shooting, using the Progressive Signal Tracer, Progressive Signal Injector, Progressive Dynamic Radio & Electronics Tester, Square Wave Generator, and the accompanying instructional materials.

You will receive training for the Novice, Technician and General Classes of F.C.C. Radio Amateur Licenses. You will build Receiver, Transmitter, Square Wave Generator, Code Oscillator, Signal Tracer and Signal Injector circuits, and learn how to operate them. You will receive an excellent background for television, Hi-Fi and Electronics.

Absolutely no previous knowledge of radio or science is required. The "Edu-Kit" is the product of many years of teaching and engineering experience. The "Edu-Kit" will provide you with the basic education in a practical Radio, worth many times the low price you pay. The Signal Tracer alone is worth more than the price of the Kit.

THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has desire to learn radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad; it is used for training and rehabilitation of Armed Forces Personnel and Veterans throughout the world.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. Every step is carefully explained. You cannot make a mistake.

PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate what you have learned.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, live music, records, and tapes. Then you learn more about radio, in a progressive manner, and at your own rate, you will find yourself constructing more advanced, multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are 20 Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector, Square Wave Generator and Amplified circuits. These are not unprofessional "bread board" experiments, but genuine radio circuits constructed by the use of professional wiring and soldering on metal chassis plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

In order to provide a thorough, well-integrated and easily learned radio course, the "Edu-Kit" provides you with a complete troubleshooting manual, in addition to construction training for all, whether your purpose in learning radio be for hobby, business or job; progressively-arranged material, ranging from simple circuits to well-advanced topics in Hi-Fi and TV. Your studies will be further aided by Quiz materials and our well-known FREE Consultation Service.

THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, house-wire solder, insulation, etc. In addition you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes a Code Oscillator, a High Fidelity Guide, and a book on "How to Repair" a Radio. Frank Salerno, owner of 28 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a Course, but I found your ad and sent for your Kit."

UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER FROM AD - RECEIVE FREE BONUS
RADIO & TV PARTS JACKPOT WORTH \$15

- Send "Edu-Kit" Postpaid. I enclose full payment of \$26.95.
- Send "Edu-Kit" C.O.O. I will pay \$26.95 plus postage.
- Send me FREE additional information describing "Edu-Kit."

Name
Address

Progressive "EDU-KITS" Inc.
(ATT: S. GOODMAN, M.S. in ED., PRES.)

1185 Broadway, Dept. 246-G
Hewlett, N.Y. 11557

Since resistance of a carbon resistor increases when it is heated, choose a resistor lower in value than the one desired. Connect it to the bridge. Heat it by applying the soldering iron directly to the body, then allow it to cool. Check it on the bridge. By repeating this heating and cooling cycle a few times, you will push the resistance to the desired value.

I have made close-tolerance resistors this way whose accuracy is near the accuracy of the bridge.

This method is far superior to filing the resistor, since dirt and moisture cannot get to the carbon. Contamination will change the value of filed resistors quickly.

After you hit the right resistance, slip a piece of spaghetti over the body of the resistor and ink the new value on it so that others aren't led astray by the color bands.—R. C. Apperson, Jr.

END

NEWS FROM THE SWINDE DEPT.

Our bid for a little criminal thinking ("A Tube with a Sense of Time?", July, p. 64) was received with enthusiasm by our readers. We had asked for suggestions on ways to make a tube in a television set fail predictably about 48 hours after being installed, as some sharpie swindlers had apparently managed to do. A few readers suggested conventional timing devices (even washing-machine timers), but these are all obviously impractical, since any large, conspicuous (and quite probably ticking) device would arouse the set-owner's suspicion.

Reader James Morall of Brooklyn, N.Y., wrote us that, from his experience, the most likely prospect for such a gimmick is a tube with an octal base, since such a base is usually prone to poor solder connections between base pins and element leads.

He experimented with a set that used a 6K6-GT as vertical output stage. "I removed all solder from pin 3 [the plate] so that the wire did not make contact, placed the tube back in the set and made sure vertical sweep was out.

"A mothflake [paradichlorobenzene] was pulverized and tediously packed into the pin-3 sleeve. The pressure forced the wire to make good contact with the sleeve. Warm air . . . causes a very slow evaporation of the powdered crystal, reducing the pressure on the inner wire forced against the sleeve.

"With this system, vertical sweep was lost after 57 hours; the set was on for 15. It seems that with precise powder measurements, packing, and varied chemical mixtures, a break may be controlled from . . . 48 hours to 30 days."

Frank Salerno, known to many RADIO-ELECTRONICS readers for his TV-service cartoons, wrote us this:


"Getting electronic equipment to fail by rearrangement is really very simple if we remember certain electromedical theories. In the case of the TV sets that were rigged to conk out after 48 hours, I'm sure the perpetrators utilized the 24-hour virus principle. After stacking two virus germs in series, one can use a sensing device to detect the demise of the germs and then use the detected signal (after amplification) to disable any given tube. (Of course, it is most expedient to disable a relatively inexpensive tube to keep the cost of the operation down.)

"The possibilities of such a system are almost limitless. Any number of 24-hour periods can be arranged by stacking the appropriate number of virus germs—the main difficulty lying in getting large numbers of germs to cooperate. Experiments have shown that when the number exceeds five the germs tend to break rank and wander about, sometimes forming parallel combinations and upsetting the timing system. Scientists are now working with a foreign strain of virus (discovered quite by accident on a banana stalk) that promises greater predictability in such timing circuits."

END

FREE!

LAFAYETTE 1966 Catalog 660

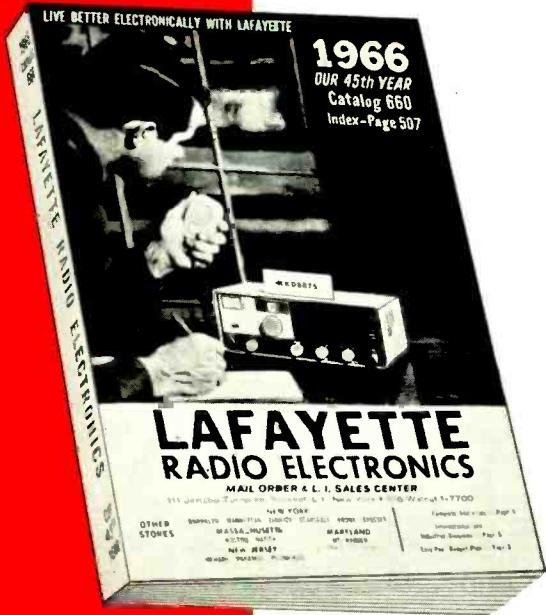


**Now
BETTER
THAN
EVER**

**Over
500
Pages**

*Featuring Everything
in Electronics for*

- HOME
 - INDUSTRY
 - LABORATORY
- from the*

"World's Hi-Fi & Electronics Center"

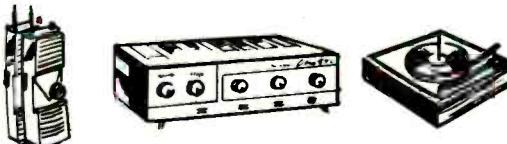

**Use Lafayette's Easy-Pay Budget Plan
No Money Down... Up to 24 Months to Pay
Satisfaction Guaranteed or Money Refunded**

LAFAYETTE Radio ELECTRONICS

Dept. JI-5 P.O. Box 10
Syosset, L.I., N.Y. 11791
Send me the Free 1966 Lafayette Catalog 660

Name

Address

City State

Zip (Please Give Your Zip Code No.)

STORE LOCATIONS

NEW YORK

Brooklyn

Syosset

Manhattan

Jamaica

Scarsdale

Bronx

NEW JERSEY

Newark

Paramus

Plainfield

MASSACHUSETTS

Boston

Natick

MARYLAND

Mt. Rainier

(Wash. D.C. Area)

**Mail the Coupon
Today for Your
FREE 1966
Lafayette
Catalog 660**

Mail This Card Today For Your

FREE!

1966 Lafayette Catalog 660



.....

Name

.....

Address

.....

City

.....

State

.....

Zip

(Please Give Your Zip Code No.)

Dept. JI-5

Mail This Card Today for Your Friend's

FREE!

1966 Lafayette Catalog 660



.....

Name

.....

Address

.....

City

.....

State

(Please Give His Zip Code No.)

Dept. JI-5

LAFAYETTE RADIO ELECTRONICS
P.O. BOX 10
SYOSSET, L.I., N.Y. 11791

PLACE
STAMP
HERE



LAFAYETTE RADIO ELECTRONICS
P.O. BOX 10
SYOSSET, L.I., N.Y. 11791

PLACE
STAMP
HERE



Live Better Electronically With

LAFAYETTE RADIO ELECTRONICS

Mail The Card Today for Your

FREE!

1966 Catalog 660



**Shop At The
"World's Hi-Fi &
Electronics Center"**

**For Widest Selection,
Low Prices**

Stereo Hi-Fi • Citizens Band •
Ham Gear • Tape Recorders
• Test Equipment • TV and Radio
Tubes and Parts • Cameras •
Auto Accessories • Musical In-
struments • Tools • Books

Everything In Electronics for Home • Industry • Laboratory

Exclusively Yours at Lafayette


A Complete Assortment
of Musical Instruments



New! 25-Channel, Solid-
State C.B. Transceiver
Model HB-600



New! Criterion Hi-Fi
Bookshelf Speakers

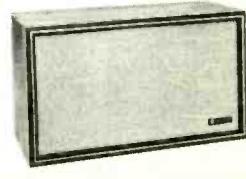

No Money Down • Up to 24 Months to Pay

70-Watt AM-FM Stereo
Receiver, Model LR-800



New! Lafayette U. S.
Army-Look-a-Like
2-Way Radio,
Model GT-3




New! Criterion 1000B
Pushbutton 4-Track
Stereo Tape Recorder in
Teak Case




Satisfaction Guaranteed or Money Refunded

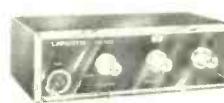New! Lafayette
Mobil-Ade™
12-Channel Solid-State
CB Transceiver,
Model HB-555



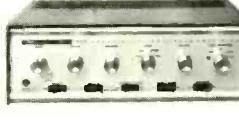50-Watt Solid-State
Stereo Amplifier, Model
LA-248



New! Complete Line of
Lafayette TV Antennas



Do A Friend A Favor...

Have a friend interested in hi-fi or electronics? Send us his name and address and we will send him his own personal copy of the 1966 Lafayette Catalog 660.


FREE

Mail The Card Today

NOTEWORTHY CIRCUITS


CONTINUOUS TUNING FOR HEATH IG-72

The Heathkit IG-72 audio signal generator is a most attractive instrument because of its low distortion, metered output, eight-position output attenuator and low cost. The switch type frequency selectors provide accurate settings with rapid resetability, but they have a serious drawback when the generator must be adjusted exactly to the resonant frequency of a circuit or when it must be tuned to an exact multiple or submultiple of an unknown for comparison by Lissajous figures.

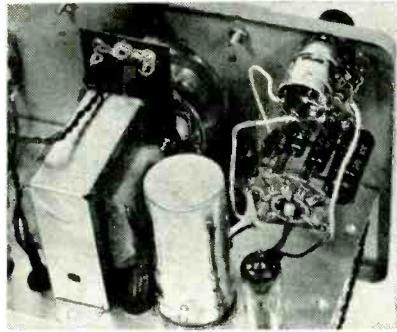

A simple modification, costing about \$3, permits adjusting the IG-72 to any frequency within its basic range of 10 cycles to 100 kc. The frequency selector switch for "10's of cycles" varies each of the two resistors of a bridged-T circuit from 100,000 to 10,000 ohms as the frequency is increased over a 10-to-1 range in 10 steps. In effect, the CYCLES switch shunts each of these with one of 10 resistances which range from approximately 100,000 ohms to 1 megohm.

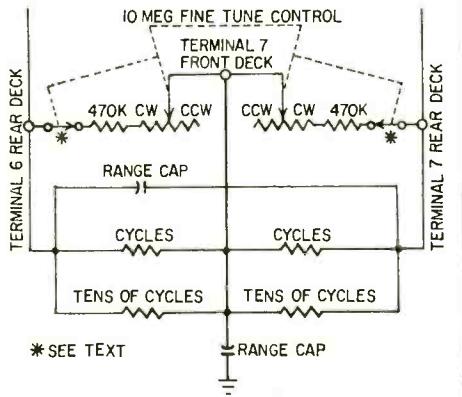The modification to the generator (see diagram) simply consists of a dual 10-megohm variable resistor shunting these resistors to adjust the generator to those frequencies which are skipped over



Circle 125 on reader's service card

SEPTEMBER, 1965

by the CYCLES switch. A dpst switch (optional) isolates this fine-tuning control from the circuit when not in use. If the switch is not incorporated, the control may be turned fully counter-clockwise (10-megohm position) to minimize its effect on calibration. The switch is not really necessary, since it removes only a very small error (1% maximum) remaining after the control has been turned fully counter-clockwise. Each section of the dual control is in series with a 470,000-ohm resistor which is the lower limit of shunting resistance. The ratio from maximum to minimum is thus greater than 10 to 1, which provides a needed overlap between positions of the CYCLES switch.

The control was assembled from IRC PQ11-143 and M11-143 sections and a type 76-2 switch. I mounted it just above the multiplier switch (see photo). The two wipers are connected to terminal 7 on the front deck of the multiplier switch. The clockwise control terminals

SILICON RECTIFIER SALE

IMMEDIATE DELIVERY
FULLY G.T.D.
AMERICAN MADE



NEWEST TYPE
FULLY TESTED

750 MA-SILICON "TOPHAT" DIODES LOW LEAKAGE FULL LEAD LENGTH

PIV/RMS 50/.35	PIV/RMS .05 ea.	PIV/RMS 200/.140	PIV/RMS 300/.210
.400/.250	.07 ea.	.10 ea.	.12 ea.
.400/.250	.14 ea.	.19 ea.	.27 ea.
.800/.560	.35 ea.	.630	.770

ALL TESTS AC & DC & FWD & LOAD SILICON POWER DIODE STUDS

D.C. AMPS	50 PIV 35 RMS	100 PIV 70 RMS	150 PIV 105 RMS	200 PIV 140 RMS
3	.08 ea	.12 ea	.16 ea	.22 ea
12	.25 ea	.35 ea	.50 ea	.75 ea
35	.65	.90	1.25	1.40
50	1.50	1.75	2.20	2.60
100	1.60	2.00	2.40	3.00

D.C. AMPS	300 PIV 210 RMS	400 PIV 280 RMS	500 PIV 350 RMS	600 PIV 450 RMS
3	.27 ea	.29 ea	.37 ea	.45 ea
12	.80 ea	1.30	1.40	1.65
35	2.00	2.35	2.60	3.00
50	3.25	4.00	4.75	6.00
100	3.60	4.50	5.25	7.00

"SCR" SILICON CONTROLLED RECTIFIERS "SCR"

PRV AMP	7 AMP	16 AMP	25 AMP	PRV AMP	7 AMP	16 AMP	25 AMP
25	.30	.50	.85	250	1.75	2.15	2.50
50	.45	.75	1.00	300	2.00	2.40	2.75
100	.80	1.50	2.00	400	2.20	2.75	3.25
150	1.20	2.00	2.50	500	3.20	3.40	3.80
200	1.25	1.80	2.25	600	4.00	4.50	5.00

SPECIALS! SPECIALS!

100 Different Precision Resistors
1/2-1-2 watt 1/2%-1% TOL \$1.50
2 amp 1000 Piv Silicon Power Rect. .70 ea.
10 for \$6.50

R.C.A. P.N.P. TRANSISTOR
Type 2N406 4 for \$1.00, 100 for \$18.
FACTORY NEW

Computer Grade Condenser 15,500 MFD
15 VDC American Mfg. .75 ea.


Type IN34 DIODE GLASS .07 ea 100 for \$5

Money Back guarantee. \$2.00 min. order. Orders
F.O.B. NYC. Include check or money order. Shpg.
charges plus C.O.D. orders 25% down.

Warren Electronic Components
230 Mercer St., N.Y., N.Y. 10012 • OR 3-2620

LATEST and GREATEST!

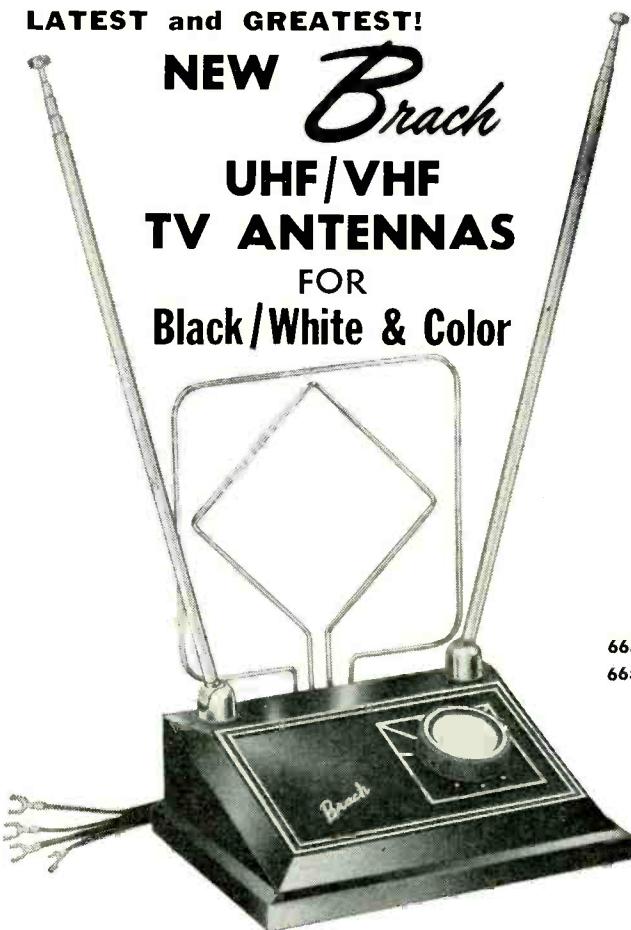NEW *Brach* UHF/VHF TV ANTENNAS FOR Black/White & Color



6651 Gold Finish
6652 Chrome Finish

SEND FOR our latest
catalog with our com-
plete line of antennas

• • •

BRACH MFG. CORP. DIV. of General Bronze Corp.

899 Main Street, Sayreville, N.J. 08872

Circle 127 on reader's service card

Fascination

Relationships between colors and music have fascinated people for years. Until now, most *color organs*—which display colored lights to music from a radio or phonograph—have been complex, cumbersome things. This one, though, is easy to build. It uses silicon controlled rectifiers for simplicity, efficiency and low cost. Input impedance is high enough not to bother the sound source. You'll want to build the Colorgan.

Evaluation

Daniel Meyer, known to RADIO-ELECTRONICS readers as the designer of several outstanding transistor amplifier and preamp construction projects, describes a variety of *transistor output circuits*, exploring their merits and drawbacks. Now that things have settled a bit, most manufacturers stick with two or three tried-and-true circuits.

Radiation

A Nebraska sheriff kept getting *mysterious TV sound* radiation (from various channels) on his 39.9-mc public-service receiver, in spite of months of experiments with filters, traps, suppressors. Finally someone realized that dozens of TV sets were reradiating programs on that frequency. It could be happening in your town! Read what was done about it.

Three big reasons you'll enjoy October

RADIO-ELECTRONICS


are connected to 470,000-ohm resistors which are connected through the dual switch to terminals 6 and 7 on the rear deck of the multiplier switch.

This modification allows the generator to be adjusted for zero beat or stationary Lissajous figures at higher frequencies, and has greatly increased versatility without detracting from the original excellent performance.—*Glen-don C. Smith*

LEAKAGE DETECTOR

Transformerless radios and phonographs, electric tools and many household electric appliances may develop leakage currents that can lead to a fatal shock. The simple leakage detector shown here was developed by Peter Lefferts of Carter-Princeton, and described in *Signalite Application News*.

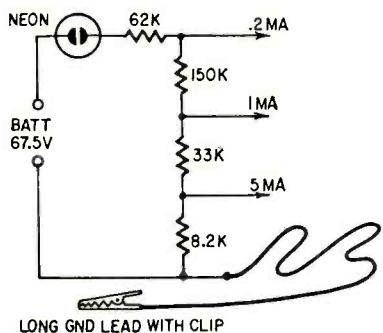The original model was assembled and cast in an epoxy block, with the three probes and the ground lead coming out one end. The glow lamp (Signalite type LT2-27-1) was recessed into the top of the block.




To use, clip the ground lead to a good ground or cold-water pipe and then touch the probes, one at a time, to the equipment being tested while watching to see if the indicator lights. Currents greater than 5 ma (rms) are dangerous and may prove fatal. Less than 0.1 ma is acceptable and less than 1 ma produces a slight shock. Currents from 1 to around 4 ma are borderline but every effort should be made to greatly reduce or completely eliminate them.

LOW-INDUCTANCE HIGH-CURRENT CHOKES

Low-voltage power supplies and ac power-source filters often use chokes with inductance measured in fractions of a henry, together with current ratings measured in amperes.

Such chokes are manufactured, but cost (as compared to more common varieties) is rather high. Fortunately, a simple method exists by which the common 8-henry 50-ma ac-dc choke may be made to serve the purpose.

The schematic shows the hookup. An inexpensive filament transformer is used in reverse, with its secondary connected as the low-inductance choke and its primary connected to the 8-henry unit. With a 6.3-volt transformer, resulting inductance will be approximately equal to .0029 times the choke inductance, or a little more than 23 millihenries. Alternating-current rating will be 18.6 times the rating of the choke, or 930 ma. The direct-current rating will be that of the filament-transformer secondary.

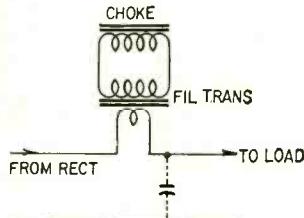

This hookup is now being used to provide the inductance for a 400-cycle low-pass filter in a bench power supply for testing aircraft instruments. The choke and transformer together cost less than a tenth as much as the low-inductance choke listed in the catalogs.

Inductance stepdown is equal to the secondary rated voltage, squared, divided by the primary rated voltage, also squared. Current stepup equals primary voltage divided by secondary voltage (neglecting transformer losses). For transformers other than the 6.3-volt unit, these ratios are:

SECONDARY VOLTS	INDUCTANCE RATIO	CURRENT RATIO
2.5	.00046	47
5	.0018	23.5
7.5	.0041	15.6
10	.0073	11.7
12.6	.0126	9.3
24	.0420	4.9

Why not try this circuit as a substitute for the high-current choke in your next battery charger or eliminator?—Jim Kyle

END



"You mean \$1.50 just for a piece of string?"


MOVING DATE EXTENDED—SALE CONTINUES

"VALUES" THAT DEFY ALL COMPETITION

FREE \$1 BUY WITH EVERY 10 YOU ORDER Only applies to (\$1) Buys FREE GIFT WITH EVERY ORDER

HOTTEST VALUE EVER

IBM COMPUTER SECTIONS

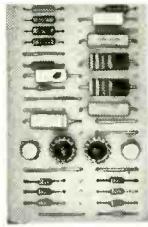


Each Unit "cost IBM over \$5.00"

6 assorted Units we sell for \$1 are loaded with over 100 valuable parts.

6 for \$1
70 for \$10

STANDARD TV TUNER 41mc

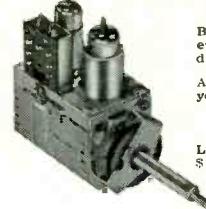Latest "GUIDED GRID" Compact Model — good for all 41mc TV's. All set for parallel — for series change the 6GK5 to a 3GK5.



Best TUNER "Standard Kollman, Inc." ever made — last word for stability, definition & smoothness of operation.

An opportunity — to improve and bring your old TV Receiver up-to-date.

L-3", H-4", W-2"

List price \$35 — former reduced price \$15.97 — now cut in 1/2 to \$7.95.

COMPLETE with Tubes & Schematic \$7.95

<input type="checkbox"/> UNIVERSAL 5" PM SPEAKER \$1	<input type="checkbox"/> 100—ASST 1/4 WATT RESISTORS \$1	<input type="checkbox"/> 50 ASSORTED MYLAR CONDEN- \$1
<input type="checkbox"/> UNIVERSAL 4" PM SPEAKER \$1	<input type="checkbox"/> 100—ASST 1/2 WATT RESISTORS \$1	<input type="checkbox"/> 20 — EXPERIMENTER'S COIL \$1
<input type="checkbox"/> ELECTROSTATIC 3" TWEETER SPEAKER for FM, HI-FI, etc ... \$1	<input type="checkbox"/> 70—ASST 1 WATT RESISTORS \$1	<input type="checkbox"/> 10—ASSORTED DIODE CRYSTALS \$1
<input type="checkbox"/> 2 — UNIVERSAL 2 1/4" PM SPEAKERS for Radios, Intercom, as multiple Speakers, etc. \$1	<input type="checkbox"/> 35—ASST 2 WATT RESISTORS \$1	<input type="checkbox"/> 10—TOP BRAND TRANSISTORS \$1
<input type="checkbox"/> 3 — AUDIO OUTPUT TRANS- FORMERS 506L type \$1	<input type="checkbox"/> 50—PRECISION RESISTORS \$1	<input type="checkbox"/> 2—LINE FILTER COILS 110v, to \$1
<input type="checkbox"/> 10—SPEAKER PLUG SETS \$1	<input type="checkbox"/> 20 — ASST WIREWOUND RESISTORS, 5, 10, 20 watt \$1	<input type="checkbox"/> 20—ITT SELENIUM RECTIFIERS \$1
<input type="checkbox"/> 3 — I.F. COIL TRANSFORMERS 458k, most popular type \$1	<input type="checkbox"/> 100—ASST. CERAMIC CONDEN- SERS some in 5% \$1	<input type="checkbox"/> 65ma for Radios, Meters, Chargers, Transistors, Experiments, etc.
<input type="checkbox"/> 5—I.F. COIL TRANSFORMERS sub-min for Transistor Radios \$1	<input type="checkbox"/> 100—ASST. TERMINAL STRIPS all types, 1-lug to 6-lug \$1	<input type="checkbox"/> \$15.00 RADIO PARTS "JACK- \$1
<input type="checkbox"/> 5 — AUDIO OUTPUT TRANS- FORM sub-min for Trans Radios \$1	<input type="checkbox"/> 50—RADIO & TV SOCKETS all type, pin, 8 pin, 6 pin, etc. \$1	<input type="checkbox"/> POT" handy assortment \$1
<input type="checkbox"/> 4—TOGGLE SWITCHES \$1	<input type="checkbox"/> 25 — INSTRUMENT POINTER KNOBS selected popular types \$1	<input type="checkbox"/> 2—G.E. PIECES OF EQUIPMENT \$1
<input type="checkbox"/> 15—ASST. ROTARY SWITCHES \$1	<input type="checkbox"/> 50—ASST. RADIO KNOBS all selected popular types \$1	<input type="checkbox"/> stacked with over 200 useful parts
<input type="checkbox"/> CLEAN UP THE KITCHEN "JACK- \$1	<input type="checkbox"/> 50—ASSORTED PRINTED CIR- CUIT SOCKETS best types \$1	<input type="checkbox"/> 50—G.E. FLASHLIGHT BULBS \$1
<input type="checkbox"/> POT" big deal only one to a customer \$1	<input type="checkbox"/> 50 — ASST. TUBULAR CON- DENSERS .001 to .47 to 600v .. \$1	<input type="checkbox"/> #PH-9, 2.7 volts \$1
<input type="checkbox"/> 1000—ASST. HARDWARE KIT \$1	<input type="checkbox"/> 25 — SYLVANIA HEAT SINKS \$1	<input type="checkbox"/> CHART ZU DI MITZIA "JACK- \$1
<input type="checkbox"/> screws, nuts, washers, rivets, etc.	<input type="checkbox"/> for Transistors, etc. \$1	POT" double your money back if not completely satisfied \$1
<input type="checkbox"/> 250—ASST. SOLDERING LUGS \$1	<input type="checkbox"/> 100—BRASS FAHNSTOCK CLIPS \$1	<input type="checkbox"/> 10—SYLVANIA 1U4 TUBES \$1
<input type="checkbox"/> best types and sizes	<input type="checkbox"/> popular type size, plated	<input type="checkbox"/> brand new Jant., individual cartons also serves as IT4 \$1
<input type="checkbox"/> 1000—ASSORTED RIVETS \$1	<input type="checkbox"/> 10 — SETS PHONO PLUGS & \$1	<input type="checkbox"/> ALL AMERICAN TUBE KIT \$2
<input type="checkbox"/> most useful selected sizes	<input type="checkbox"/> PIN JACKS RCA type \$1	<input type="checkbox"/> CRYSTAL LAPEL MICROPHONE \$1
<input type="checkbox"/> 1000—ASSORTED WASHERS \$1	<input type="checkbox"/> \$15.00 TELEVISION PARTS \$1	<input type="checkbox"/> high impedance, 200,000 ohms ..
<input type="checkbox"/> most useful selected sizes	<input type="checkbox"/> "JACKPOT" best buy ever	<input type="checkbox"/> 15—DELUXE SLIDE SWITCHES \$1
<input type="checkbox"/> 250—ASST. WOOD SCREWS \$1	<input type="checkbox"/> 4 — TV ALIGNMENT TOOLS \$1	<input type="checkbox"/> useful as SPST, DPST or DTST ..
<input type="checkbox"/> finest popular selection	<input type="checkbox"/> most useful assortment	<input type="checkbox"/> 300—ASST. 1/2 W RESISTORS \$1
<input type="checkbox"/> 250 — ASST. SELF TAPPING \$1	<input type="checkbox"/> 110° FLYBACK TRANSFORMER \$2	<input type="checkbox"/> Top Brand, Short leads, excellent
<input type="checkbox"/> SCREWS #6, #8, etc.	<input type="checkbox"/> for all type TV's incl schematic	<input type="checkbox"/> 100—MOLDED TUBULAR COND. \$1
<input type="checkbox"/> 150—ASST. 6/32 SCREWS \$1	<input type="checkbox"/> 110° TV DEFLECTION YOKE \$2	<input type="checkbox"/> Top brand, short leads, excellent
<input type="checkbox"/> and 150—6/32 HEX NUTS	<input type="checkbox"/> for all type TV's incl schematic	<input type="checkbox"/> 50—ASSORTED #3AG FUSES \$1
<input type="checkbox"/> 150—ASST. 8/32 SCREWS \$1	<input type="checkbox"/> 90° FLYBACK TRANSFORMER \$1	<input type="checkbox"/> Popular assort'd amper ratings ..
<input type="checkbox"/> and 150—8/32 HEX NUTS	<input type="checkbox"/> for all type TV's incl schematic	<input type="checkbox"/> 20—STANDARD TUBULAR \$1
<input type="checkbox"/> 150—6/32 HEX NUTS \$1	<input type="checkbox"/> 90° TV DEFLECTION YOKE \$1	<input type="checkbox"/> CONDENSERS .047-600 ..
<input type="checkbox"/> and 150—8/32 HEX NUTS	<input type="checkbox"/> for all type TV's incl schematic	<input type="checkbox"/> 20—BENDIX CONDENSERS \$1
<input type="checkbox"/> 150—ASST. 2/56 SCREWS \$1	<input type="checkbox"/> 70° FLYBACK TRANSFORMER \$1	<input type="checkbox"/> .007-2000v \$15 value
<input type="checkbox"/> and 150—2/56 HEX NUTS	<input type="checkbox"/> for all type TV's incl schematic	<input type="checkbox"/> 50—BALL POINT PENS \$1
<input type="checkbox"/> 150—ASST. 4/40 SCREWS \$1	<input type="checkbox"/> 70° TV DEFLECTION YOKE \$1	<input type="checkbox"/> retractable, assort'd colors ..
<input type="checkbox"/> and 150—4/40 HEX NUTS	<input type="checkbox"/> 4—DUMONT VERT. OSC. TRANS \$1	<input type="checkbox"/> HEARING AID AMPLIFIER \$2
<input type="checkbox"/> 150—ASST. 5/40 SCREWS \$1	<input type="checkbox"/> incl schematic for many TV user	<input type="checkbox"/> 10—ASST. DUAL CONTROLS for \$1
<input type="checkbox"/> and 150—5/40 HEX NUTS	<input type="checkbox"/> 20—ASSORTED TV COILS \$1	Radio, TV, Hi-Fi, Stereo, etc. ..
<input type="checkbox"/> TRANSISTOR RADIO asst types \$1	<input type="checkbox"/> I.F., video, sound, ratio, etc.	<input type="checkbox"/> 1—SQ. YARD GRILLE CLOTH \$1
<input type="checkbox"/> good, bad, broken, as-is, potluck	<input type="checkbox"/> 20—ASSORTED TV KNOBS \$1	most popular brown & gold design
<input type="checkbox"/> TAPE RECORDER assort'd types \$4	<input type="checkbox"/> all standard types, \$20 value ..	<input type="checkbox"/> BONANZA "JACKPOT" not gold, \$5
	<input type="checkbox"/> 6 — TV ELECTROLYTIC CON- \$1	not oil, but a wealth of Electronic Items—Money-Back-Guarantee ..
	<input type="checkbox"/> DENSERS Sprague 80-175v ..	100 for 10% off
	<input type="checkbox"/> 7 — ASST. TV ELECTROLYTIC \$1	slashed to 20¢ ea.
	<input type="checkbox"/> CONDENSERS popular selection ..	
	<input type="checkbox"/> STANDARD 1/4W RESISTORS 10% \$1	
	<input type="checkbox"/> 470, 1500, 3000, 6800, 15k, 100k, 2.2meg. \$1	
	<input type="checkbox"/> 3meg. Your choice or assort'd ..	
	<input type="checkbox"/> 12AE6, 12AL8, 12FM17, 12FK6, 12U7, 17LG ..	
	<input type="checkbox"/> 20¢ ea.	



HANDY WAY TO ORDER: Pencil mark or write amounts wanted in each box. Enclose with check or M.O. add extra for shipping. Tearsheets will be returned as packing slips in your order, plus new offers.

Name _____ Cost of goods _____
Address _____ Shipping estimated _____
TOTAL _____

CHECK POSTAGE STAMPS MERCANDISE (our choice) with advantage to customer

BROOKS RADIO & TV CORP., 84 Vesey St., New York 7, N.Y.
Circle 128 on reader's service card

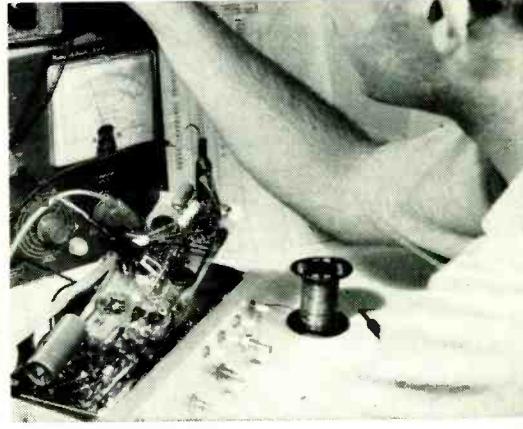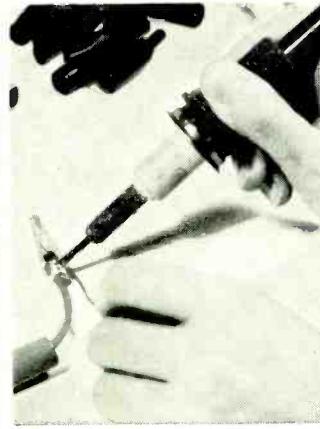AT LAST, A REALLY PRACTICAL WAY TO build your electronics know-how . . . boost your income and prestige and make substantial savings on the most valuable handbooks you can own!



**Accept your risk-free membership in the famous
Electronics Book Club and enjoy these advantages now!**

Everyone talks about the great future of Electronics—but how many people are really doing something about it? If you are the one man in seven who is determined to get ahead in electronics—who wants to cash in on the steadily increasing demand for trained technicians—the Electronics Book Club has astonishing benefits for you.

Your membership in this unique book Club will help you to protect your future . . . increase your knowledge and earning power . . . keep you up-to-date on all the latest electronic developments . . . and bring you greater enjoyment from leisure hours if electronics is your hobby.

SPECIAL INVITATION

Judge for yourself, without risk, what the Electronics Book Club can do for you. Examine the special introductory offer on the opposite page. See how you can receive your choice of \$25 electronics self-training programs for only \$2, with membership.

TAKE YOUR CHOICE of either of these outstanding electronics self-training programs for only \$2—with membership in the Electronics Book Club. Perhaps you want the course on HOW TO FIX TRANSISTOR RADIOS AND PRINTED CIRCUITS; or maybe you'll choose RADIO SERVICING MADE EASY. Whichever you take, remember this: both originally sold for \$25 each as home-learning courses; Now they're available in two-volume book-format. Take your pick at once as your introduction to membership.

RISK-FREE GUARANTEE: You enjoy this *air-tight, no questions-asked* guarantee. If you are not pleased when you receive these books, you may return them in good condition in 10 days and cancel your membership, and that will end the matter.

7 EXCLUSIVE MEMBERSHIP BENEFITS: (1) The Club saves you up to 30% off retail prices on electronics books that interest you most; (2) Club books are *practical, working tools* written to give you clear answers, help you solve problems, increase your know-how and electronics enjoyment; (3) You receive only the books you want because Club News Bulletin tells you about them every other month so you can accept or reject them *in advance*. You need accept *only four additional books within a year*; (4) Members are offered the widest possible range of books covering everything from repair, troubleshooting and building . . . to experimental and hobby projects; (5) Special charts and reports are now given FREE with many Club selections to expand and illuminate the text; (6) *You need send no money in advance*; you pay for your books *after* you receive and examine them and decide to keep them; (7) Permanent Risk-Free Guarantee: if you are ever dissatisfied with a book, you may return it in good condition in 10 days for a full credit.

Mail valuable coupon on opposite page→

DO YOU KNOW HOW
A paper clip can be used for
adjustment of the trimmer?


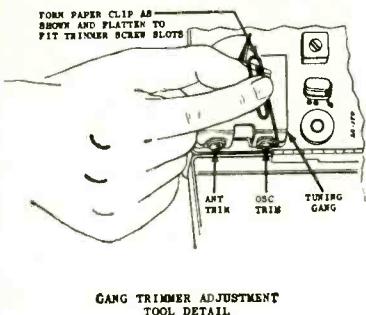


Fig. 1012. A paper clip can be used for adjustment of the trimmer.

For more information, see page 91
in volume 2 of **HOW TO FIX TRANSISTOR
RADIOS AND PRINTED CIRCUITS**

Here is a complete course on fixing transistor radios and printed circuits in **TWO DELUXE, HARD BOUND VOLUMES**. Written by expert, Leonard C. Lane, it was originally developed as a \$25 home study program. It's yours for only \$2 with membership. It treats every aspect of transistors, much of it new, original, unavailable anywhere else in book form. Hundreds of illustrations aid understanding. Completely covers semiconductor fundamentals, how transistors work, transistor types, amplifiers, RF and IF stages, printed circuits, specific servicing methods and techniques. Gives answers to hundreds of questions including those on trouble in the audio section, working with printed-circuit boards, signal generators, the vtv, defects and repairs, soldering techniques and useful tools, speaker defects, volume control, surface-barrier transistor, silicon transistors, transistors at work, servicing chart, antennas on auto radios, dc to dc converter, and many many other subjects.

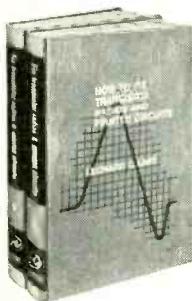

MAIL THIS VALUABLE COUPON TODAY!
It will bring you either of these **TWO-VOLUME TRAINING COURSES** for only \$2—when you join the Electronics Book Club . . . and agree to take only 4 additional books within a year—out of a wide selection that will be offered—all at low Club prices. Thousands of others have already profited from membership. Discover now how you can profit too!

ENJOY THIS RISK-FREE GUARANTEE!

Select your **TWO-VOLUME**, deluxe, hardbound SET of books right now. Clip and mail coupon today, while supplies last. You will be protected by this **RISK-FREE GUARANTEE**: if you are not pleased when you receive the books, you may return them in good condition in 10 days and forget the matter. Mail coupon right away.

Which of these \$25 electronics self-training programs do you want for only \$2—with

your risk-free membership in

the Electronics Book Club:

**simply take 4 additional books
within a year at low Club prices!**

DO YOU KNOW HOW
to draw the circuit for
a manual noise limiter?

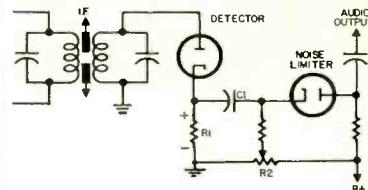


Fig. 918. This noise-limiting circuit has to be adjusted for noise conditions. It is called a manual noise limiter (mln).

For more information—see page 117
in Volume 2 of **RADIO SERVICING
MADE EASY**

This important two-volume set was originally prepared as a \$25 home-study course by famed technician and writer Leonard C. Lane. Now you receive both deluxe hard bound volumes for only \$2 with membership. Tells you everything you want

and need to know about radio servicing in clear, down-to-earth language. Just a few of the many answers you will receive: Working with transistors. Getting started with transistors. Approaching the transistor. Testing transistors and printed circuits. Things to remember. Checking transistors. Servicing transistor radios. Servicing the transistor receiver. Stage-by-stage analysis. Servicing auto radios. Installation and removal. AM receivers. Frequency range. Ac-dc power supplies. Troubleshooting. FM receivers. AM-FM tuners. Why should we have tuners? Communications receivers. Frequency range. Voltage stabilization. Noise limiters. Checking the gain control. Single-sideband reception. Marine receivers. Marine frequencies. The beacon band. The marine band. Mobile radio.



Gernsback Library ELECTRONICS BOOK CLUB c/o Dept. RE-965

154 West 14th Street, New York, N.Y. 10011

Please enroll me as a member of the Electronics Book Club and send me the TWO VOLUME SET checked below:

How to Fix Transistor Radios and printed Circuits

Radio Servicing Made Easy

Bill me only \$2 plus shipping. If not pleased, I may return both books in 10 days and this membership will be cancelled.

I need only accept as few as four additional books a year—and may resign any time after purchasing these four additional books. All selections will be described to me in advance, every other month, in the Club Bulletin, and a convenient form will always be provided for my use if I do not wish to receive a forthcoming selection. You will bill me the special Club price for each book I take. This will often be as much as 30% off retail prices, plus a few cents postage.

Name (please print)

Address

City State Zip Code No.

SAVE POSTAGE COSTS—enclose your payment of \$2 now and we will pay postage. Same return guarantee privilege.

Circle 129 on reader's service card

Because you've got to SEE it to BELIEVE it....we will send you a FREE sample!



A REVOLUTIONARY NEW METHOD FOR MARKING ELECTRONIC EQUIPMENT

Try this sample and you'll agree "Instant Lettering" is the easiest, quickest way to get professional lettering you've ever seen. Self-adhesive letters printed on a special plastic sheet are just pressed down into position on any equipment, drawing, schematic, etc. Transfers to practically any surface. Looks like printing.

AVAILABLE IN THE FOLLOWING SETS AT \$4.95 EACH

- TITLES FOR ELECTRONIC EQUIPMENT
- TERMINAL & CHASSIS MARKING KIT
- METER & DIAL MARKING KIT


With these three kits you can completely mark prototype electronic equipment from component parts to finished control panel and meters—and make them look like finished production equipment. In stock at leading electronics distributors or direct.

SEND FOR FREE SAMPLE AND FOLDER:

THE DATAK CORPORATION

63 71ST STREET • DEPT. 613 • GUTTENBERG, NEW JERSEY

Circle 130 on reader's service card

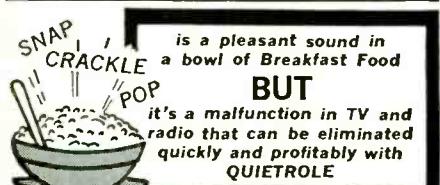

NOW! QUIETROLE
Offers 3 New Aerosols
To save time... make added income

1 QUIETROLE MARK-II
For Tuners

2 QUIETROLE SPRAY-PACK
For Controls & Switches

3 QUIETROLE SILITRON
For General Use

All with extenders
HARMLESS TO PLASTICS
... non-conductive, non-inflammable and non-corrosive. Zero effect on capacity and resistance.
Harmless to metal
YES! Quietrol is still available in bottles with an eye dropper!

manufactured by

QUIETROLE Company
Spartanburg, South Carolina

Circle 131 on reader's service card

Coax Isn't All That Great

Dear Editor:

After withstanding the test of time for two decades of television reception, 300-ohm ribbon lead, the venerable standby for antenna installations, is now being attacked as unsuitable for color reception. It is too easily affected by environment, reads the indictment. When wet, for example, it attenuates signal drastically compared to when it is dry. Worse than mere attenuation is the fact that impedance of the line is altered. The results are standing waves on the line and phase shift, which play havoc with color signals. Still worse, these effects are exaggerated by nearby metal, including the very iron-ring standoffs that support the flat lead-in. The only solution, the argument concludes, is to substitute coaxial cable.

Widespread acceptance of this position, which is based on a rather exaggerated presentation of what can happen when one particular type of ribbon lead is improperly installed, could lead to serious consequences. The fact that many people will be put to unnecessary trouble and expense is just one of these. Worse yet, coax has its own drawbacks. One of these could have a damaging effect on an important area of television growth.

Ribbon lead of high quality, still inexpensive compared to coax, overcomes most of the problems cited. Signal fields surrounding the conductors of an encapsulated 300-ohm line, for example, remain confined within the line, as is the case with coax. This avoids the "drastic changes" wrought by water, ice and metals. Using the wrong type of standoff or staple, or using them improperly, can impair the function of any transmission line. Those who condemn ribbon line and recommend coax are themselves careful to specify certain precautions in the handling and stapling of coax. Why they consider vulnerability to abuse reasonable in one type of line but unforgivable in another is never explained. As to standoffs (a good idea for any downlead), inexpensive ones are available with all-polyethylene heads that do not surround the line with metal rings.

Even so, one may question how harmful nearby metals, including standoff rings, actually are with good ribbon lead. A recent series of tests by Belden Manufacturing Co., which makes both coax and 300-ohm lead, is interesting. Identical signals were fed to identical lengths of RG59/U coax, 8285 encapsulated 300-ohm line in air and 8285 run through a metal pipe. Signal in the pipe-enclosed line was attenuated somewhat compared to the same lead in air, but output was nevertheless higher than at the end of the coax cable. Line im-

pedance was not drastically changed.

The matter of attenuation brings us to the serious but entirely unmentioned flaw in coax. Even in the low vhf band, half the signal sent down by the antenna can be consumed by coax before reaching the set, in a typical run. On uhf, of course, coax is impossible. In fact, few wire manufacturers even bother specifying losses above 400 mc. Toward the low end of the uhf band, signal loss will run about 9 db or more per 100 feet. Toward the high end of the band, with considerably shorter runs, attenuation can be great enough to negate the gain of the most sensitive uhf antennas now available. In other words, an elaborate outdoor array feeding through coax may deliver less signal to a TV set than a simple indoor bowtie or uhf loop at the receiver itself!

We have still to assess the matching transformers needed with coax, which involve more expense and more trouble. These, too, can introduce attenuation and mismatch at certain frequencies. When two are used—and most antennas will require one at each end of the coaxial line—the problem is multiplied. Again we return to the very color-degrading deviations we are trying to avoid.

The only remaining justification for choosing coax is the rare case of severe interference picked up primarily on the downlead. Coax is immune to that.

The outlook for shielded 300-ohm ribbon is good. Manufacturers are working on the problem today. Until it comes along, high-quality ribbon remains the obvious choice except for the rare interference problem. This is recommended by wire manufacturers who make both coax and 300-ohm lead.

JFD is in a similar position. We are proud of our matching transformers, antenna amplifiers, couplers and other accessories, and are pleased to sell them when they are needed. We see no point, however, in saddling a customer with a signal amplification and distribution system for his home that one would expect to find in a hotel, just to make up for deficiencies introduced by an artificial problem.

It does little good to condemn a time-tested type of antenna line categorically by an exaggerated presentation of problems that occur only with the least expensive, flat-ribbon members of its family. It does even less good to promote another type of line that may have more serious drawbacks.

EDWARD FINKEL

Vice President, Sales
JFD Electronics Corp.
Brooklyn, N.Y.

WHAT'S YOUR EQ?


These are the answers. Puzzles are on page 61.

Will It Work?

Reverse-biasing Q1 makes emitter act like collector, and collector like emitter. Effectively, we now have an emitter follower, and an incoming positive or negative pulse produces an output positive or negative pulse respectively.

Note: This circuit is used as a digital inverter in an electrostatic printer capable of 15,625 characters per second.

Power-Supply Problem

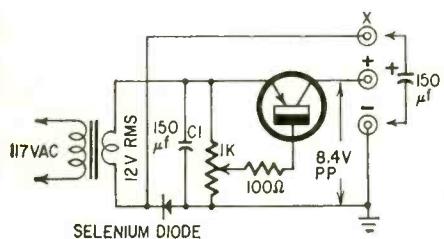

The capacitor is connected across the diode, permitting current flow in both directions. A sine wave will be

50 Years Ago

In Gernsback Publications
In September, 1915
Electrical Experimenter

Combatting Submarines Electrically
Long-Distance Submarine Telegraphy
and Telephony
Selenium Cells and Radio Torpedoes
Radio Time Signals for the Public

BUILD THIS FASCINATING COLORGAN

Relationships between colors and music have fascinated people for years. Until now, most color organs—which display colored lights to music from a radio or phonograph—have been complex, cumbersome things. This one, though, is easy to build. It uses silicon controlled rectifiers for simplicity, efficiency and low cost. Input impedance is high enough not to bother the sound source. You'll want to build the Colorgan.


COMING IN . . . OCTOBER
RADIO-ELECTRONICS

present across C1 as long as the impedance of the external capacitor is as low as the forward resistance of the diode, which is comparatively high in a selenium diode.

When the external capacitor is 150 μ F, the two capacitors form an ac voltage divider with equal legs. Consequently, 6 volts rms (16.9 p-p) is developed across each capacitor. The transistor is used as a nonlinear amplifier, and will cut off on alternate half-cycles, producing a half-wave output of about 8.4 volts p-p.

Two-Way Meter

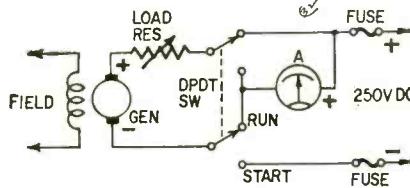The ammeter is connected as shown in the diagram.



Note: Overcurrent protection (fuses) should be provided in the 250-volt line. The neutral of such a system is ordinarily at ground potential. As the generator is still connected to one side of the dc line with switch in "run" position, an accidental ground on the negative lead of the generator would probably destroy the meter. END

Every No-Noise Aerosol Product

Guaranteed

**Non-Flammable
Non-Toxic and
Won't Affect Plastics**

"NO NOISE"

**PROVED BEST
FOR COLOR TV**

**VOLUME CONTROL
and CONTACT RESTORER**

"TUNER-TONIC" WITH PERMA-FILEM

EC-44 for all electrical contacts

FREE 5" plastic extender push-button assembly for pin-point application with all No-Noise products.

ELECTRONIC CHEMICAL CORP.
813 Communipaw Avenue, Jersey City 4, N. J.

Circle 132 on reader's service card

Turn Back

If you missed RADIO-ELECTRONICS Reader's Service Page, turn back to Page 72—and take advantage of this free new service.

ELECTRONICS



Engineering-Technicians

**Bachelor of Science Degree, 30 Months
Save Two Years' Time**

- Radio-Television Plus Color Technician (12 Months)
- Electronics Engineering Technology (15 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree)
(36 Months)

Approved for Veterans

DAY AND EVENING CLASSES

Write for Catalog and Registration Application.
New Term Starting Soon.

Your Name

Address

City

State

HEALD'S ENGINEERING COLLEGE

Est. 1863-102 Years
Van Ness at Post, RE
San Francisco, Calif.

RADIO SHACK IS NOW SELLING REALISTIC "Lifetime" TUBES TO DEALERS AND SERVICEMEN!

(And They're Buying Them Like Crazy — Crazy Like A Fox, That Is)

- You get the world's ONLY lifetime-guaranteed tube: a FREE replacement whenever it fails in the set!
- You get a premium tube at a popular price: beautifully boxed, 24K gold-clad contacts, nationally advertised!

YOU SAVE! BUY AT UP TO 70% OFF!

24K
GOLD CLAD
CONTACTS

YOU ASKED FOR IT!

Hundreds of dealer-service men have requested a deal on our Realistic Lifetime Tubes because of the obvious PROFIT potential for them. If you are now buying at 50-60% off list CHECK THESE PRICES and see how much you save by switching now to Lifetime tubes. Frankly, the savings are staggering. This IS the deal you wanted.

100% GUARANTEE!

Radio Shack's 42-year reputation stands squarely behind our Lifetime guarantee. We WILL REPLACE FREE any of our tubes that fail in use . . . now, later, forever. This unique quality assurance, plus our gold-plated tube contacts give you consumer acceptance beyond our wildest dreams.

65 WAREHOUSES!

Delivery is fast and cheap because each of our 65 stores (see coast-to-coast list next page) is prepared to sell you TODAY at these LOW WHOLESALE prices. Our stores do not compete with you because they sell at "each" prices far above your cost. Get to know the Radio Shack manager near you—he can be trusted to supply you better tubes at prices well below what you are now paying, and you won't have to argue about costs, rebates or terms.

ORDER TUBES NOW!

Radio Shack can look you squarely in the eyes and say: these are the prices, and nobody's buying better than you are. They're the lowest prices in the industry for the only absolutely guaranteed tube. You pay no shipping costs when you pick up your tubes at a Radio Shack store. You pay cash. You can order by mail. Why wait? Nobody but nobody has a deal like Lifetime!

NOW 92
TYPES!



BUY BIG —
SAVE BIG!



Type	Sugg. List	3 of Type Or 10 Asst. Each	5 of Type Or 25 Asst.	10 of Type Or 50 Asst. Each	Type	Sugg. List	3 of Type Or 10 Asst. Each	5 of Type Or 25 Asst.	10 of Type Or 50 Asst. Each
OZ4	2.55	.92	.77	.69	6CG7	.245	.89	.74	.67
IB3/IG3GT	2.90	1.04	.87	.79	6CG8A	3.30	1.19	.99	.90
IK3	2.90	1.04	.87	.79	6CM7	2.90	1.04	.87	.78
IR5	3.05	1.10	.92	.83	6CX8	4.20	1.51	1.26	1.14
IU4	2.90	1.04	.87	.79	6DQ6B	4.15	1.49	1.25	1.13
IU5	2.65	.95	.80	.72	6EA8	3.20	1.15	.96	.86
IX2B	3.05	1.10	.92	.83	6EB8	4.20	1.51	1.26	1.14
2CY5	3.05	1.10	.92	.83	6GH8	3.15	1.13	.95	.85
3BZ6	2.30	.83	.69	.62	6J6A	2.85	1.03	.86	.77
3CB6	2.25	.81	.68	.61	6K6GT	2.65	.95	.80	.72
3V4	2.50	.90	.75	.68	6L6GC	4.35	1.57	1.31	1.18
5AM8	3.95	1.42	1.19	1.07	6S4A	2.50	.90	.75	.67
5AQ5	2.35	.85	.71	.64	6SN7GTB	2.60	.94	.78	.69
5AR4	4.50	1.62	1.35	1.21	6T8A	3.40	1.22	1.02	.92
5U4GB	2.10	.76	.63	.57	6U8A	3.30	1.19	.99	.89
5U8	3.30	1.19	.99	.90	6V6GT	2.20	.79	.66	.59
5Y3GT	1.75	.63	.53	.48	6W4GT	2.40	.86	.72	.65
6AG5	2.75	1.00	.83	.75	6W6GT	2.85	1.03	.86	.77
6AL5	1.85	.67	.56	.50	6X4	1.65	.59	.50	.45
6AM8A	3.45	1.25	1.04	.94	6X8A	3.15	1.13	.95	.85
6AN8A	4.00	1.44	1.20	1.08	12AD6/I2GA6	2.40	.86	.72	.65
6AQ5	2.15	.77	.65	.58	12AT6	1.85	.67	.56	.50
6AS5	2.90	1.04	.87	.79	12AT7	3.05	1.10	.92	.83
6AU4GTA	3.60	1.30	1.08	.97	12AU6	2.15	.77	.65	.58
6AU6A	2.10	.76	.63	.57	12AU7A	2.45	.88	.74	.67
6AU8A	4.20	1.51	1.26	1.13	12AV6	1.65	.59	.50	.45
6AV6	1.65	.60	.50	.45	12AX4GTB	2.70	.97	.81	.73
6AW8	3.70	1.33	1.11	1.00	12AX7A	2.55	.92	.77	.69
6AX4GTB	2.65	.95	.80	.72	12BA6	1.65	.59	.50	.45
6BA6	2.00	.72	.60	.54	12BE6	1.75	.63	.53	.48
6BC5/6CE5	2.35	.85	.71	.64	12BH7A	3.05	1.10	.92	.83
6BE6	2.20	.79	.66	.59	12BL6	2.65	.95	.80	.72
6BG6GA	6.50	2.34	1.95	1.75	12BQ6GTB/I2CU6	4.45	1.60	1.34	1.21
6BK7B	3.40	1.22	1.02	.92	12BY7A	3.20	1.15	.96	.86
6BM8	3.05	1.10	.92	.93	12DQ6B	4.20	1.51	1.26	1.14
6BN6	3.20	1.15	.96	.86	12SQ7GT	3.75	1.35	1.13	1.02
6BQ5	2.40	.86	.72	.65	17DQ6B	4.20	1.51	1.26	1.14
6BQ6GTB	4.35	1.57	1.31	1.18	25L6GT	2.65	.95	.80	.72
6BQ7A	3.95	1.42	1.19	1.07	35C5	2.15	.77	.65	.58
6BU8	3.35	1.21	1.01	.91	35W4	1.10	.40	.33	.30
6BZ6	2.25	.81	.68	.61	35Z5GT	1.85	.67	.56	.50
6BZ7	4.00	1.44	1.20	1.08	50C5	2.15	.77	.65	.58
6C4	1.85	.67	.56	.50	50EH5	2.30	.83	.69	.62
6CB6A	2.25	.81	.68	.61	50L6GT	2.55	.92	.77	.69
6CD6GA	5.80	2.09	1.74	1.57	7199	4.70	1.69	1.41	1.27
6CF6	2.55	.92	.77	.70	7591	3.00	1.08	.90	.81

SEE LIST
(NEXT PAGE)

SEND OR TAKE TUBE ORDERS TO THE NEAREST RADIO SHACK STORE



FREE


THE ONE CATALOG THAT REALLY SAVES YOU MONEY

FILL OUT AND MAIL
THIS CARD TODAY —

Page after page of Exclusive Bargains
from the World's Largest Chain of
Electronics Stores. It's FREE!

Citizens' Band Radio Values

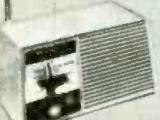. . . and only Radio Shack has 'em! Instant 2-way communications at ranges up to 30 miles. Desk-top, mobile or hand-held models, priced \$\$\$ below what you'd pay for comparable name-brand units. Each can "talk" to any other unit shown!



New
INTRaCOM CB
Transceiver/
Intercom

New solid-state crystal-controlled transceiver/intercom. Wireless 2-way radio! No license! Desk-top styling. 117 VAC. #21-903. Only \$34.95 ea.

16-Transistor TRC-12 Mobile CB Radio



6 crystal-controlled channels; adjustable squelch; no tubes; instant operation! 2x6x7½". #21-909. Only \$119.95.

2-Channel TRC-22 CB Walkie-Talkie



Sends, receives up to 2 miles on TWO channels: 5 & 11! 100 mw no-license operation. Ceramic filter module cuts CB interference! Batteries, case included. #21-904. Only \$39.95 ea.

65 RADIO SHACKS

NOW THERE ARE OVER 65 RADIO SHACKS COAST-TO-COAST

CALIFORNIA

BAKERSFIELD — 1308 19th St.
LOS ANGELES (West L.A.) — Pico Blvd. at Overland
LOS ANGELES (Anaheim) — 504 Katella Ave.
LOS ANGELES (Downey) — Stonewood Shop. Ctr.
LOS ANGELES (Mission Hills) — 10119 Sepulveda Blvd.
LOS ANGELES (Santa Ana) — Bristol Plaza Shop. Ctr.
SAN DIEGO (La Jolla) — Crossroad Shop. Ctr.
LONG BEACH — 3976 Atlantic Ave.
OAKLAND (San Leandro) — Bay Fair Shop. Ctr.
SACRAMENTO — 600 Fulton Ave.

COLORADO

DENVER — 798 South Santa Fe

CONNECTICUT

HAMDEN — Hamden Mart. Shop. Ctr.
MANCHESTER — Manchester Shop. Parkade
NEW HAVEN — 92 York St.
NEW LONDON — New London Shop. Ctr.
STAMFORD — 29 High Ridge Rd.
WEST HARTFORD — 39 So. Main St.

ILLINOIS

CHICAGO — Evergreen Plaza at 95th St.

MAINE

PORTLAND — Pine Tree Shop. Ctr.

MASSACHUSETTS

BOSTON — 167 Washington St.
BOSTON — 594 Washington St.
BOSTON — 110 Federal St.
BRAINTREE — South Shore Plaza
BROOKLINE — 730 Commonwealth Ave.
CAMBRIDGE — Fresh Pond Shop. Ctr.
FRAMINGHAM — Shoppers' World
LOWELL — Central Shop. Plaza
SAUGUS — N. E. Shop. Ctr.
SPRINGFIELD — 1182 Main St.
WEST SPRINGFIELD — Century Shopping Center
WORCESTER — Lincoln Plaza

MINNESOTA

ST. PAUL — 473 North Snelling
NEW HAMPSHIRE
MANCHESTER — 1247 Elm St.

NEW MEXICO
ALBUQUERQUE — 6315 Lomas, N. E.

NEW YORK
BINGHAMTON (Vesta) — Vestal Shop. Plaza
BUFFALO (Clarence) — Transitown Shop. Ctr.
NEW YORK — 1128 Ave. of the Americas
SCHENECTADY (Rotterdam) — Shoporama Shop. Ctr.
SYRACUSE — 3057 Erie Blvd. East

OHIO

CINCINNATI — 852 Swifton Ctr.

OKLAHOMA
OKLAHOMA CITY — Mayfair Shop. Ctr.
TULSA — 2730 South Harvard

OREGON

PORTLAND — 1928 N.E. 42nd St.

PENNSYLVANIA
PHILADELPHIA — 2327 G Cottman Ave., Roosevelt Mall
PHILADELPHIA — 1128 Walnut St.

RHODE ISLAND
CRANSTON — 1301 Reservoir Ave.
EAST PROVIDENCE — Shoppers' Town

TEXAS

ABILENE — 2910 North First St.
ARLINGTON — Collins at Park Row
DALLAS — 1601 Main St.
DALLAS — Medallion Center
DALLAS — 125 Wynnewood Village
FORT WORTH — 1515 So. Univ. Dr.
FORT WORTH — 900 East Berry St.
FORT WORTH — 3524 East Denton Highway
HOUSTON — 8458 Gulf Freeway
HOUSTON — 2315 Travis St.
HOUSTON — 322 Northline Mall
HOUSTON (Bellaire) — 4759 Bissonnet
SAN ANTONIO — 150 Wonderland Shop. Ctr.
SHERMAN — 1620 Highway 75 North
WACO — 1016 Austin Ave.

VIRGINIA
ARLINGTON — Washington-Lee Shop. Ctr.
WASHINGTON
SEATTLE — 2028 Third Ave.
SEATTLE — 837 N.E. 110th St.

Circle 133 on reader's service card

New from
TECHPRESS



RADAR--PRINCIPLES & PRACTICES is a basic study of land, marine, and airborne radar. Includes fundamentals of transmitters, receivers, antennas, synchros, and servos. Also discussed: radar systems; test equipment; all types of oscillators, amplifiers, waveguides, and antennas used in radar. Not only an ideal introduction to small and large craft radar, but a must for broadening your horizons.

6" x 9" 300 pgs. OI-RP only \$4.95

RECEIVING TUBE SPECIFICATIONS & SUBSTITUTIONS

Contains over 2,000 American and foreign tubes listed in two ways: according to type and characteristic. Lists entertainment, industrial, and military types. Specs comprise all cathode and plate voltages and currents, type of cathode, gain, capacitances, etc. Includes substitutes listing, basing info., tec.

6" x 9" 140 pgs. OI-VT only \$1.95

TRANSISTOR SPECIFICATIONS & SUBSTITUTION HANDBOOK lists over 5,000 American and foreign types, and over 16,000 substitutes. Specs listed: PC, IC, Vce, Vcb, Veb, hfe, Icn, Fr, type and use. Base diagrams and other valuable information included.

6" x 9" 128 pgs. TSSH-2 only \$1.95

DIODE SELECT - A - SPEC is a compilation of the specifications and substitutes for both signal and power diodes. Specs include: Vw, PRV, Ir, Vz, and Ir. Over 20,000 American and foreign substitutes listed.

6" x 9" 138 pgs. OI-DS only \$2.95

SELECTED SEMICONDUCTOR CIRCUITS contains simple, easy-to-build circuits on power supplies, converters, RF and AF oscillators and amplifiers, etc.

6" x 9" 80 pgs. OI-SC only \$1.25

TRANSISTOR SELECT - A - SPEC containing the maximum electrical and design parameters for over 5,000 American and foreign transistors. There are seven listings: type, PC at TA and TC, IC, Vce, Vcb, and Veb.

6" x 9" 140 pgs. OI-TS only \$3.95

TechPress Publications
Brownsburg, Indiana, 46112

NEW BOOKS

SERVICING GARAGE-DOOR OPENERS, by Jack Darr. Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis 6, Ind. 5½ x 8½ in., 128 pp. Paper \$2.95

You can install and maintain your own opener with the help of this book. Contains schematics, diagrams and procedures.

COLOR TV REPAIR, by Martin Clifford. Gernsback Library, Inc., 154 W. 14 St., New York, N.Y. 10011. 5½ x 8½ in., 160 pp. Paper \$2.95

This book proves that "color TV is no harder to service than B & W." It discusses speedy troubleshooting of all circuits, replacing a pix tube, servicing chroma stages, using a color bar generator, etc.

A LIVING LEGACY, written and published by Lester C. Worden, 10455 Ashton Ave., W. Los Angeles 24, Calif. 8½ x 11 in., 36 pages. Paper, looseleaf, \$3

Interesting little work telling people how to organize and put down their life stories on tape, with a few hints about the use of tape recorders and tape, and the preservation of the recordings.

INTRODUCTION TO ELECTRIC CIRCUITS (2nd edition), by Herbert W. Jackson. Prentice-Hall, Englewood Cliffs, N.J. 6 x 9 in., 554 pp. Cloth, \$14.

Covers power and electronic circuits, and relies on little more than high school math. Includes numerical examples (some with answers) and math tables.

PRINCIPLES OF TELEVISION ENGINEERING (2 Vols.), by Roy C. Whitehead. Iliffe Books, Ltd., London, S.E.1, England. 5½ x 8½ in; Vol. 1, 178 pp, 25s net; Vol. 2, 270 pp, 35s net

For students in broadcasting, industrial TV and servicing. Vol. 1 discusses basic principles. Vol. 2 continues with studio techniques, transmitters and receivers. No mention of color television or of transistors.

PLANNING THE LOCAL UHF-TV STATION, by Patrick S. Finnegan. Hayden Book Co., Inc., 850 Third Ave., New York 22, N.Y. 6 x 9 in., 296 pp. Cloth, \$10

Based on extensive experience and know-how, this book tells all about the station. It discusses planning, layout, equipment operation and maintenance, FCC regulations.

THE ELECTRONICS OF MATERIALS, by Samuel Ruben. Howard W. Sams Co. Inc., 4300 W. 62 St., Indianapolis 6, Ind. 5½ x 8½ in., 109 pp. Cloth, \$4.25

The book is written to explain and display a periodic table of elements in terms of their valence electron potentials in electron volts. This type of chart is often more useful to the research worker in identifying materials for electronic and electrical applications than the conventional periodic table of the elements.

END

NEON AC/DC ELECTRIC TESTER
FOR HOME AUTO SHOP
SPECIAL!
59¢
Special!
With every \$10 Order
25¢
per tube
(No Limit) from this list.
6A5 6A5 6SN7
6A6 6J6 6S4
6A9 6K6 6W4

Prestige & Success are yours
as an ELECTRONIC EXPERT
FOR CORNELL CUSTOMERS ONLY by
special arrangement with the publisher, these
amazing bargains are available.

Both above courses \$6.00

COMPLETE RADIO SERVICING AND
BASIC ELECTRONICS COURSE ONLY \$3.00!
1230 - 50 per course - \$3.00

NEW PRACTICAL TRAINING COURSE
ONLY \$3.50
(\$3.00 + 50 processing charge)

NEW! EASY TO USE!
RADIO-TV TUBE TESTER
TEST and REPAIR
ONE SET APPLIANCES
\$2.99
plus 30c shipping
1200 ft 100 ft
GIANT REPAIR GUIDE INCLUDED

CORNELL ELECTRONICS CO.
Dept. RE 9 4217 University Ave., San Diego, Calif. 92105

CORNELL TUBES 1 YR. GUARANTEED

Mutual Conductance Lab-tested, Individually Boxed, Branded and Code Dated

33¢
PER TUBE
100 TUBES OR MORE:
30¢ PER TUBE

TUBE CARTONS

HIGH GLOSS CLAY COATED
BEDA BACK WITH BUILT IN
DIAGONAL PARTITIONS

SIZE FOR TUBE	PRICE PER 10 CARTONS	PRICE PER 100 CARTONS
MM. 6A9	.20	2.50
GT. 6SN7	.30	3.40
LG. GT. 6U406	.50	5.20
G. 6U4	.80	7.90

Other tubes at low prices - send for free list
NO SUBSTITUTIONS WITHOUT YOUR PERMISSION

11,000 TUBE SUBSTITUTES
\$1.25

BIG PROFITS ARE HERE IN COLOR TV REPAIR
ABC TV \$100

PICTURE EXPANDER
110 VOLTS
115 VOLTS
120 VOLTS
4930 VOLTS
4935

SCHOOL DIRECTORY

Get Your First Class Commercial F. C. C. LICENSE QUICKLY!

Career opportunities in communications electronics are almost unlimited. Prepare now. Let Grantham train you—by correspondence, or by classroom and laboratory instruction. Get your first class commercial F.C.C. license in as little as 4 months, or at a slower pace if you prefer. Then, continue in more-advanced electronics training if you wish. Diploma awarded. Our catalog gives full details.

Learn how our training can prepare you for your F.C.C. license; write or telephone the School at any one of the teaching divisions listed below, and ask for "Catalog 57."

Grantham School of Electronics

1505 N. Western Av., LOS Angeles, Cal. 90027
(Phone: HO 9-7878)

408 Marion Street, Seattle, Wash. 98104
(Phone: MA 2-7227)

3123 Gillham Road, Kansas City, Mo. 64109
(Phone: JE 1-6320)

818-18th St., NW, Washington, D.C. 20006
(Phone: 298-7460)

B.S. degree in 36 months

Small professionally-oriented college. Four-quarter year permits degree completion in three years. Summer attendance optional. *Engineering*: Electrical (electronics or power option), Mechanical, Civil, Chemical, Aeronautical. *Business Administration*: Accounting, General Business, Motor Transport Administration. One-year Drafting and Design Certificate program. Graduate placement outstanding. Founded 1884. Rich heritage. Excellent faculty. Small classes. Well-equipped labs. New library. New residence halls. Attractive 300-acre campus. Modest costs. Enter Jan., March, June, Sept. For Catalog and View Book, write Director of Admissions.

TRI-STATE COLLEGE
2495 College Avenue, Angola, Indiana

Learn Electronics for your SPACE-AGE EDUCATION at the center of America's aerospace industry

No matter what your aerospace goal, you can get your training at Northrop Tech, in sunny Southern California.

COLLEGE OF ENGINEERING

Get your B.S. degree in engineering in just 36 months by attending classes year round. Most Northrop Tech graduates have a job waiting for them the day they're graduated!

A & P SCHOOL. Practical experience on real aircraft. One-year course prepares you for F.A.A. A & P certificate. WRITE TODAY FOR CATALOG.

NORTHROP INSTITUTE OF TECHNOLOGY
1199 W. Arbor Vitae, Inglewood, Calif.



EARN Electronics Engineering DEGREE


You can earn an A.S.E.E. degree at home. College level HOME STUDY courses taught so you can understand them. Continue your education, earn more in the highly paid electronics industry. Missiles, computers, transistors, automation, complete electronics. Over 27,000 graduates now employed. Resident school available at our Chicago campus—Founded 1934. Send for free catalog.

American Institute of Engineering & Technology
1139 West Fullerton Parkway, Chicago 14, Ill.

GET INTO ELECTRONICS


V.T.I. training leads to success as technician, field engineer, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. One year Electronic Engineering Technician or one year Electronic Technology curriculum both available. Associate degree in 29 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Part time, part day, dormitory campus. High school graduate or equivalent. Catalog.

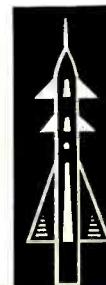VALPARAISO TECHNICAL
INSTITUTE
Department C. Valparaiso, Indiana



LEARN

ELECTRONICS

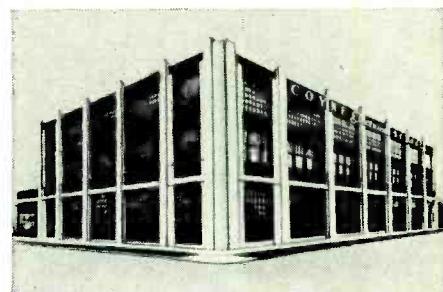

FOUNDED 1899

NOT-FOR-PROFIT

COYNE ELECTRONICS INSTITUTE

Electronics Engineering Technology	—	Degree (2 Yrs.)
Electrical-Electronics Technician	—	Diploma (40 Wks.)
TV-Radio-Electronics Technician	—	Diploma (40 Wks.)
Combined Electronics Technician	—	Diploma (80 Wks.)
Practical Electrical Maintenance	—	Diploma (32 Wks.)
Practical Refrigeration Air Conditioning and Appliance Repair	—	Diploma (24 Wks.)
Specialized Industrial Electronics	—	Diploma (16 Wks.)
Introduction to Electricity-Electronics	—	Certificate (8 Wks.)
FCC First Class Radiotelephone	—	Certificate (100 Hrs.)

Special finance plans. Part time employment service while in school. Also Free graduate employment service.



Use this coupon to get our FREE BOOK
"YOUR OPPORTUNITIES IN ELECTRONICS"
COYNE ELECTRONICS INSTITUTE, Dept. of Electronics 65-N
1501 W. Congress Parkway, Chicago, Illinois 60607

Name..... Age.....

Address..... Phone.....

City..... Zone..... State.....

Unlike most other schools, we do not employ salesmen

Circle 136 on reader's service card

A JOB or a POSITION?

The difference is ELECTRONIC MATHEMATICS

NOW! A NEW WAY TO LEARN—I. H. S. I. WAY. A complete home study course in electronic math to help you get the position you want—MORE MONEY—MORE RESPECT.

COURSE PREPARED BY
COLLEGE PROFESSORS
who have lectured to thousands of men on math and engineering. You learn at home quickly, easily
—AS FAST as you want.

YOU SIGN NO CONTRACTS
Pay only if satisfied—you owe it to yourself to examine the INDIANA HOME STUDY INSTITUTE COURSE IN ELECTRONIC MATH.
FREE BONUS—if you join now, a refresher course in basic arithmetic.

Write for Brochure—No Obligation
THE INDIANA HOME STUDY INSTITUTE
Dept. RE-9, P.O. Box 1189
Panama City, Fla. 32402

MARKET CENTER

MINIATURE CAPACITOR PACKAGE

4000 mfd for \$1.00

High quality, metal cased completely sealed electrolytic capacitors made in USA for use in transistor auto radios, power supplies, communications equipment, "ham" gear and many other applications.

SEND TODAY for this package of 3 units; totaling 4000 mfd rated 16 volts DC; each unit 1 1/2" max dia by 2 1/4" max hgt.

SEND \$1.00 CHECK OR MONEY ORDER for each package, postage prepaid to:

LINDA SALES CORPORATION
PO Box 68, Harrison, N.J.

DIRECT FROM FACTORY

G - LINE FOR UHF RECEPTION

costs no more than coax, but almost no loss (1 db/100 ft 400 to 1200 mc). Needs no booster.

150' kit \$16.85, additional wire \$3.00/100' mail orders accepted prepaid or c.o.d.

SURFACE CONDUCTION, INC.
1501 Broadway, New York, N.Y. 10036

TUCO SPECIALS

2N2613 RCA, PNP low noise preamp 120 hFE	50¢
2N3711/TI 419-NPN 300 MC. Epoxy. New type	50¢
FET. TI SF2887. Field Effect Transistor	4.50
2N703. Motorola. 350 MC. PNP	1.25
2N1100. Tungsol. 100 volt. 15 amp. 90 watts	2.50
1N1692. Rectifier. 1 amp. 100 PIV	.40
25H10. Rectifier. Int'l. Rect. 25 amp. 100v with hardware and insulated	1.25
Transistor Power Transformer. Harman-Kardon. from Citation A. 115 vac. Gacy. min. Sec. 60 vac. C.T. Gvac. @ 1 amp	2.50
1 watt Zeners, any voltage from 4 v. to 80 v.	.75
150 ma., Zeners, 6 volt to 200 volt. T.I. D150	.75

TRANSISTORS UNLIMITED COMPANY
462 Jericho Tpk., Mineola, L.I., N.Y. 11501
WRITE FOR FREE CATALOG



CLIP AND MAIL COUPON TODAY

EDMUND SCIENTIFIC CO., Barrington, N.J.
PLEASE SEND ME FREE CATALOG "EH"
Name _____
Address _____
City _____ State _____

GENERAL

TV SERVICE ORDER BOOKS for use with your rubber stamp. Duplicate or triplicate. Low cost. Write for FREE 32 PAGE CATALOG and Special Rubber Stamp Offer. **OELRICH PUBLICATIONS**, 6556 W. Higgins, Chicago, Ill. 60656.

72 page Illustrated Government Surplus Radio, Gadgeteers Catalog 20¢. **MESHNA**, Nahant, Mass.

McGEE RADIO COMPANY. Big 1965 176-page catalog sent free. America's best values hi-fi amplifiers-speakers-electronic parts. 1901 McGee Street, Dept. RE, Kansas City, Mo. 64108.

BIG CATALOG

World's "BEST BUYS" in GOVT. SURPLUS Electronic Equipment

FULL OF TOP QUALITY ITEMS—
Transmitters, Receivers, Power Supplies, Inverters, Microphones, Filters, Meters, Cable, Keyers, Phones, Antennas, Chokes, Dynamotors, Blowers, Switches, Test Equipment, Headsets, Amplifiers, etc., etc. **SEND 25¢ (stamps or coin) for CATALOG and receive 50¢ CREDIT on your order. Address Dept. RE.**

FAIR RADIO SALES
P.O. Box 1105 • LIMA, OHIO • 45802

→ SUB CARRIER DETECTOR ←



Add programs of commercial-free music thru your FM tuner. Detector, self-powered, plugs into multiplex output of tuner or easily wired into discriminator and permits reception of famous background music programs now transmitted as hidden programs on the FM broadcast band from coast to coast. Use with ANY FM tuner.

WIRED UNIT \$75.00
KIT, with pretuned coils,
no alignment necessary \$49.50
crystal-controlled receivers available

MUSIC ASSOCIATED
65 Glenwood Road
Upper Montclair, New Jersey
phone 744-3387 area code 201

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services): 60¢ per word . . . minimum 10 words.

NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items): 30¢ per word . . . no minimum.

Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for November issue must reach us before September 10th.

WORD COUNT: Include name and address. Name of city (Des Moines) or of state (New York) counts as one word each. Zone or Zip Code numbers not counted. (We reserve the right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols or groups such as 8x10, COD, AC, etc., count as one word. Hyphenated words count as two words. Minor over-wordage will be edited to match advance payment.

Convert any television to sensitive Big-Screen Oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. **RELCO-A25**, Box 10563, Houston 18, Texas.

KIT OF THE MONTH CLUB, Novel, new projects each month. Low Cost. Free information. **LEADER ENTERPRISES**, Box 44718-KC, Los Angeles, California 90044

SAFEGUARD PRIVACY! New instrument detects electronic "bugs", wire-tapping and snooping devices. Free information. **DEE EQUIPMENT**, Box 7263-E8, Houston 8, Texas.

NEW—"The Third Science: Monotonics"; \$1.00. **MONOTRON PRESS**, Box 3332, Laramie, Wyoming.

Canadians

GIANT SURPLUS BARGAIN PACKED CATALOGS. Electronics, Hi-Fi, Shortwave, Amateur, Citizens Radio, Rush \$1.00 (Refunded). **ETCO**, Box 741, Dept. R. Montreal, Canada.

TRANSISTOR AND SEMICONDUCTOR SPECIALISTS. Free catalogue contains reference data on over 300 types. **J. & J. ELECTRONICS**, Dept. RE, Box 1437, Winnipeg, Manitoba.

WANTED

QUICK CASH . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! **BARRY**, 512 Broadway, New York, N.Y. 10012, 212 WALKER 5-7000.

CASH, SONY TRANSISTOR TV's etc. swapped for G-R, H-P, L&N etc. equipment, special tubes, manuals, military electronics. **ENGINEERING ASSOCIATES**, 428 Patterson Road, Dayton, Ohio 45419.

Military surplus radios ARC-27 ARC-34 ARC-38 ARC-39 ARC-44 ARC-52 ARC-55 ARC-73 ARC-84 R-220C/ARM-21 51X-2/17L-7 RT-68/GRC. Test sets with ARM, URM, UPM, SG prefixes. Top cash dollar paid. **SLEP ELECTRONICS**, Drawer 178 Ellenton, Florida. 33532

I NEED 16 thru 28 gauge steel wire very thin plastic or enamel cover. H. G. ZUK, 1431-6th, Madison, Illinois.

SERVICES

METERS—MULTIMETERS REPAIRED and calibrated. **BIGELOW ELECTRONICS**, Box 71-B, Bluffton, Ohio.

TRANSISTORIZED products dealers catalog, \$1. **INTERMARKET**, CPO 1717, Tokyo, Japan.

PROFESSIONAL BUSINESS CARDS Embossed. \$4.00 per M Postpaid. Samples free. **LUMAR**, Box 473, West Hartford, Conn. 06107.

NAMEPLATES, Decals, Signs, Plaques, Trophies, Badges. Write **R. E. SETON**, New Haven 15, Conn.

METERS REPAIRED, VTVM, VOM. 90 Day Warranty. **TV TUNER SERVICE**, Box 793 E, Twin Falls, Idaho.

NEED MONEY? Borrow \$100-\$1000 by mail. Confidential, repay in 24 months. Free loan application. **BUDGET FINANCE CO.**, DEPT. OB-295, 317 So. 20th, Omaha, Nebraska. 68102

AUDIO - HI-FI

Component quotations-tapes Mylar 1800' post-paid \$1.59 each. BAYLA, Box 131RE Wantagh, N.Y.

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. CARSTON, 1686-R Second Ave. N.Y.C. 10028

RENT STEREO TAPES—over 2,500 different—all major labels—free brochure. STEREO-PARTI, 1616 Terrace Way, Santa Rosa, Calif.

STEREO TAPES. Save up to 60% (no membership fees). We discount recorders, batteries, accessories, and mail pre-recorded tape prepaid anywhere that United States rates prevail. Free 60 page catalog. SAXITONE, 1776 Columbia Road N.W., Washington, D.C. 20009

TAPE recorders, Hi-Fi components, Sleep-learning equipment, Tapes, Unusual values. Free catalog. DRESSNER, 1523 Jericho Turnpike, New Hyde Park 5, N.Y.

HI-FI COMPONENTS, Tape Recorders, at guaranteed "WE will not be undersold" prices. 15-day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. HI-FIDELITY CENTER, 1797 (R) 1st Ave., New York, N.Y. 10028

TAPE RECORDER SALE. Brand new, latest models, \$10.00 above cost. ARKAY SALES, 1028-E Commonwealth Ave., Boston, Mass. 02215.

LOW LOW QUOTES, DYNA. A.R. GARRARD E.V. HI-FI, Roslyn, Pa. 19001

GUARANTEED RADIO TUBES one-fourth list. GOODWIN RADIO, Rankin, Ill. 60960

HI-FIDELITY COMPONENTS, Ham Marine and Communication equipment at considerable savings. If you want to save money write us for our low prices on all your needs. AIREX RADIO CORP., 85 (RE) Cortlandt St., N.Y., N.Y. 10007

Compare these prices with all other prices for Brand New Tubes.

The largest stock of obsolete tubes in the USA at the lowest prices—COMPARE

BRAND NEW UNITED'S FIRST QUALITY TUBES DISCOUNTS up to

80% OFF

GUARANTEED ONE FULL YEAR! NOT USED! NO PULLS!

WHY PAY MORE?

Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price	Type	Price
004-UV	.200	3D6	.1.25	6AJ8	.1.95	6CY7	1.22	6J6	.72	8C58	.98	12F8X	1.27	19T8	1.25
3D6	.250	3D7G	.92	59A6K	.94	6C25	1.59	6J7	1.70	8C58	1.60	12G6	.91	21EX6	1.95
0A2	.90	3D24	.1.59	59A6K	.94	6C25	1.59	6J7	1.70	8E8	1.50	12GC6	1.15	21EX6	1.95
0A3	.90	3E17	1.42	5AL5	.73	6D4	1.75	6J7	1.25	8E8	1.50	12GE5	1.46	21GY5	1.49
0A4	1.15	3E17	1.42	5AL5	.73	6D4	1.75	6J7	1.82	8ET7	1.60	12GE5	1.46	21GY5	1.49
0B2	.80	3E15	1.35	5AL11	1.95	6D10	1.59	6JH6	.99	8FQ7	.95	12H6	1.40	22BH3	1.65
0B3	1.20	3F5H	.95	5AM8	1.25	6D45	1.08	6JK8	1.69	8GJ7	1.31	12J5	1.21	22BW3	1.21
0C3	.85	3F5H	1.18	5AN4	2.45	6D85	1.99	6JS6	2.95	8JV8	1.27	12JB	1.21	22DE4	1.15
0D3	.75	3D5X	1.55	5AN5	1.95	6D86	1.01	6JT8	1.69	8K8	1.55	12JB	1.20	22JG6	1.95
0E3	1.00	3D5X	1.55	5AN5	1.95	6D86	1.29	6JV8	1.49	8AB	1.40	12JN6	1.43	22AC5	2.20
0Y4	1.20	3GW5	.98	5AN8	1.50	6D86	1.29	6JV8	1.49	8AB	1.40	12K5	1.19	23AK4	1.19
0Z4	.95	3H45	.79	5AQ5	.79	6D84	1.03	6K6GT	1.95	8DR	1.05	12K5	1.19	23AK4	1.19
1A3	1.95	3H45	1.23	5AQ5	.99	6D86	.93	6K6GT	1.70	8DR	1.10	12K5	1.19	23AK4	1.19
1A4	1.45	3H45	1.23	5AQ5	.99	6D86	1.29	6K7GT	1.49	9EAB	1.49	12K5	1.19	23AK4	1.19
1A6	.99	3Q4	1.35	5AQ5	.99	6D86	1.29	6K7GT	1.49	9EAB	1.49	12L6	.99	23BK5	1.05
1A7	1.95	3Q5	2.00	5AR5	.99	6D86	1.85	6K8GT	2.25	9U8	.99	12L8	.50	23BQ6	1.45
1AB5	.75	354	.99	5AR6	1.50	6D86	.89	6K8GT	1.69	10BQ8	1.39	12M	1.58	23CS5	.66
1AB6	1.75	354	.99	5AR6	1.50	6D86	1.35	6K8GT	1.39	10BQ8	1.39	12M	1.58	23CS5	.66
1AE4	1.45	4AV6	.98	5AS1	1.65	6D87	1.35	6K8GT	1.39	10BQ8	1.39	12M	1.58	23CS5	.66
1AF4	1.45	4AV6	.98	5AS1	1.65	6D87	1.35	6K8GT	1.39	10BQ8	1.39	12M	1.58	23CS5	.66
1AG4	2.20	4B46	.85	5AS6	1.00	6D86	1.50	6LS8	1.49	10E7	1.37	12SA7GT	1.65	23CU6	1.70
1AH4	1.75	4BC5	.90	5AS7	2.85	6D87	1.29	6LS5	1.50	10E7	1.75	12SC7M	1.65	23DN6	2.10
1AU3	1.05	4C6	.90	5AS1	1.45	6D84	1.69	6LG6	.90	10EW7	1.45	12SE5	1.95	23EH5	1.95
1AV2	4.88	4B8L	1.00	5AS1	1.45	6D84	1.21	6LG6	1.50	10GN8	1.30	12SF5GT	1.39	23F5GT	1.39
1AX2	2.10	4BN6	1.48	5AT6	.49	6D75	1.35	6LG6	.75	12HT8	1.19	12L6	.95	23W4	.95
1AY2	.98	4BQ7	1.40	5AT6	1.40	6D76	1.35	6LG6	1.61	12HT8	1.19	12L6	.95	23W4	.95
1B3	.98	4B88	1.35	5AU4	.95	6D78	1.35	6LG6	1.30	10JAB	1.35	12SF7M	1.59	23Z5	1.70
1B4	2.00	4B88	1.35	5AU4	.95	6D78	1.29	6LG6	1.25	10JY8	1.49	12SF7M	1.59	23Z5	1.70
1C5	1.10	4BZ6	.85	5AU6	.52	6D74	1.29	6LG6	1.75	10JY8	1.49	12SJ7GT	1.35	23G8	.95
1C6	1.25	4BZ7	.85	5AU7	.54	6D75	1.55	6M1	1.69	10JY8	1.49	12SJ7GT	1.35	23G8	.95
1D5G	1.25	4CB6	.87	5AU8	1.40	6D88	1.19	6N5	3.10	11CY7	1.10	12SG7M	.85	23L7	.85
1D6S	1.25	4CB6	.87	5AU8	1.40	6D88	1.50	6N5	1.50	10E7	1.75	12SC7M	1.65	23DN6	2.10
1D7S	1.25	4CB8	.89	5AV6	1.40	6D84	1.53	6N7G	1.49	11JE8	1.49	12SH7	1.55	23E5	1.95
1E5G	1.49	4CS6	.59	5AV11	1.52	6EAS	1.35	6N7GT	1.49	11KVB	2.35	12SJ7M	1.35	23G9D5	.95
1E7	1.50	4CY5	1.10	5AW8	1.35	6EAT	1.47	6P5	2.50	12SF5GT	1.39	12AS5	1.20	23SB5	2.30
1F4	1.50	4D6E	1.01	5AX3	1.05	6EA8	1.19	6Q7GT	1.95	12A26	.89	12AS5	1.20	23SB5	.80
1F5	1.20	4DT6	.87	5AX5	1.15	6EBS	1.75	6Q7M	2.00	12A26	.95	12AS5	1.20	23SB5	.80
1G3	.97	4EH7	1.47	5AX7	1.25	6EHS	1.10	6HE5	1.75	12A11	1.69	12AS5	1.20	23SB5	.80
1G4	1.75	4EJ7	1.47	5AX8	1.34	6EH7	.79	6S4	.85	12AS5	.85	12SL7GT	1.45	23W4	.42
1G6	1.50	4EJ6	1.19	5AX8	1.05	6EH8	1.21	6S5	1.95	12ADG	.79	12SN7	1.39	23Y4	1.80
1G7	1.50	4EJ6	1.19	5AX8	1.05	6EH8	1.21	6S5	1.95	12ADG	.79	12SQ7GT	1.49	23Z2	.95
1H5	1.25	4EW6	1.01	5B1	1.45	6D84	1.50	6S6	1.95	12AE6	.79	12SF5GT	1.40	50AS	2.35
1H6	1.25	4EK5	1.59	6B8	4.00	6EM7	1.93	6S7M	1.49	12AE7	1.25	12SF5GT	1.40	50B5	.95
1I1	1.25	4F6	1.10	6B8	1.45	6EAT	1.35	6S7GT	1.49	12AF6	.98	12UT7	1.95	50C5	.95
1J3	.97	4GM6	1.25	6B8	1.00	6EQ7	1.10	6S87	2.35	12AF6	.98	12UT7	1.95	50E5	.95
1J4	1.25	4GM6	1.25	6B8	1.00	6EQ7	1.10	6S87	1.49	12AU6	.69	12UT7	1.95	50F5	.95
1J6	.97	4GM6	1.25	6B8	1.00	6EQ7	1.10	6S87	1.49	12AU6	.69	13110	.90	50H6	.86
1K3	.97	4GZ6	1.19	6B10	1.35	6ES8	2.19	6SFS	1.10	12AZ1	1.44	12W6	.85	50F5	.86
1L4	.85	4H45	1.85	6B10	1.05	6GET	1.60	6SFS	1.25	12AZ1	1.25	12W6	.85	50F5	.86
1L6	2.60	4HC7	1.39	6B10	1.49	6GU7	1.03	6SFT	1.95	12AL1	1.62	12DP7	1.20	50H6	.86
1L7	1.25	4HS6	1.19	6B10	1.49	6GU8	1.25	6SFT	1.95	12AL1	1.62	12DP7	1.20	50H6	.86
1L8	1.95	4HS8	1.18	6B10	1.49	6GU8	1.48	6SFT	1.65	12AT6	.55	13EM7	1.83	50L6	.95
1L9	2.49	4HT6	1.24	6B11	1.45	6GEW	1.92	6SFT	1.21	12AT6	.55	13EM7	1.83	50L6	.95
1LC1	1.95	4JC6	1.35	6B12	2.10	6GEW	1.52	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC2	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC3	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC4	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC5	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC6	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC7	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC8	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC9	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC10	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC11	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC12	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC13	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC14	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC15	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC16	1.95	4JC6	1.35	6B12	2.10	6GEW	1.95	6SFT	1.49	12AZ1	1.25	12AT6	.55	13EM7	1.83
1LC17	1.95	4JC6	1.35	6B12	2.10										

ADVERTISING INDEX

MARKET CENTER

Rectifiers & Transistors

750 Ma-Silicon Diodes "Epoxy" or "Top Hat"					
	PIV	PIV	PIV	PIV	PIV
50	5¢	300	12¢	600	21¢
100	7¢	400	14¢	700	25¢
200	10¢	500	18¢	800	32¢

Full Leads, All tests, Guaranteed, American made

Silicon Power Diode Studs

Amps	50 PIV	100 PIV	150 PIV	200 PIV
3	8¢	14¢	16¢	22¢
15	25¢	50¢	65¢	75¢
18*	18¢	40¢	60¢	70¢
35	60	80	1.15	1.30

*Press Fit Package for Alternators

10 Watt Sil. Zener Stud 6v-150v. 95¢ ea.

1 Watt Zener diode, axial leads 6v-200v 50¢ ea.

Sil. diode Stud, 1500 PIV, 300ma 50¢ ea.

Sil. diode, 1500 PIV, 50ma, axial leads 35¢ ea.

Hi-Voltage-Silicon epoxy diode, 2 1/2" x 3/8" x 1/2"

Hoffman—3000 PIV-200ma \$1.49 ea.

Hoffman—6000 PIV-200ma \$3.49 ea.

Thermistor, bead, 900 or 1200 ohms, 600°F, 2/\$1.00

20 Watt Germanium

(internal & external heat sink)

2N1038	28¢	2N1042	35¢
2N1039	35¢	2N1043	45¢
2N1040	45¢	2N1044	60¢
2N1041	60¢	2N1045	80¢

Silicon Power Transistors, 85 w, 2N1724 \$1.50

Philco Sil., NPN, 2N2479, new 3 for \$1.00

HF Silicon, 2N702, 100 mc 40¢; 2N703-150 mc 60¢

Light Sensitive Resistor

75 ohms—10 meg, 100 volts, 150mow \$1.75 ea.

Sil. diodes, 1N200 series, asst'd., new 15 for \$1.00

Ger. diodes, glass, new, exceeds 1N34 15 for \$1.00

Nickel-Cadmium Battery, 9 1/2 oz., 8 amp-hr. \$1.95

Varicap-Voltage Variable Capacitor

47 pf at 4v., 4:1, new \$1.25 ea.

Silicon Controlled Rectifiers

PRV	7 amp.	16 amp.	PRV	7 amp.	16 amp.
25	28	48	200	1.05	1.70
50	48	70	300	1.60	2.20
100	70	1.20	400	2.10	2.70
150	80	1.50	500	2.80	3.30

All Tests Stud Type 600 3.00 3.90

Money back guarantee. \$2.00 min. order. include postage.

Catalog 25¢.

Electronic Components Co.
Box 29026 Baton Rouge, La. 70821

DIRECT FROM FACTORY

VHF G - LINE FOR CATV

costs no more than coax, but almost no loss (2/10 db/100 ft 50 to 250 mc). Needs no amplifier up to 2-4 miles.

5000' kit \$820.00, additional wire \$8.20/100' mail orders accepted prepaid or c.o.d.

SURFACE CONDUCTION, INC.
1501 Broadway, New York, N.Y. 10036

BUSINESS OPPORTUNITIES

PIANO Tuning learned quickly at home. Tremendous field! Musical knowledge unnecessary. Information free. EMPIRE SCHOOL OF PIANO TUNING, Dept. RE Box 327, Shenandoah Station, Miami, Florida 33145. (Founded 1935.)

New scientific transistor instrument detects buried coins, treasures. Will detect gold, silver, copper, iron, etc. \$19.95 up. Free catalog. RELOCO-A-25, Box 10563, Houston 18, Texas.

CAPE KENNEDY, Spaceport, Down-range, Information, Employment, Housing etc. \$1.00 REA, Box 334, Cape Canaveral, Florida 32920

BUSINESS AIDS

JUST STARTING IN TV SERVICE? Write for FREE 32 PAGE CATALOG of Service Order books, invoices, job tickets, phone message books, statements and file systems. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656.

1,000 Business Cards, "Raised Letters" \$3.95 postpaid. Samples. ROUTH RE12, 2633 Randleman, Greensboro, N.C. 27406.


ELECTRONICS

METERS-Surplus, new, used, panel and portable. Send for list. HANCHETT, Box 1898 Riverside, Calif.

TV CAMERAS, transmitters, converters, etc. Lowest factory prices. Catalog 10¢. VANGUARD, 190-48-99th Ave., Hollis, N.Y. 11423.

PROFESSIONAL ELECTRONICS PROJECTS — Organs, Timers, Computers, etc.—\$1 up. Catalog 25¢, refundable. PARKS, Box 25565, Seattle, Wash. 98125.

CONVERT TO COLOR TV

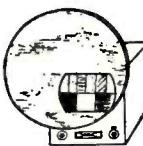

COLORDAPTOR—A simple 10-tube circuit and rotating color wheel converts any size B & W TV to receive compatible color.

COLORDAPTOR — Easily attached to any TV set, does not affect normal operation, often built from parts experimenters have on hand. BRILLIANT COLOR!

Complete booklet—gives theory of operation, all construction details, schematic, and sample color filters. \$1.95

Essential Parts Kit—Includes all special parts—coils, delay line, crystal, color filters. Add \$1.00 for sets over 16". \$19.95

1798 Santa Cruz,
Menlo Park, Calif.

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

Allied Radio Corp. 82-85

Amperex Electronic Corp. Second Cover

Amphenol Distributor Division (Borg Electronics Corporation) 23

Blonder-Tongue 79

Brach Manufacturing Corp. (Div. of General Bronze Corp.) 95

Brooks Radio & TV Corp. 97

Capitol Radio Engineering Institute, The ... 18-21

Castle TV Tuner Service, Inc. 6

CLASSIFIED 108-111

Cleveland Institute of Electronics 1, 62-65

Conair (Div. of National Radio Institute) 13

Cornell Electronics Co. 106

Datak Corporation, The 100

DeVry Technical Institute 5

Electronic Chemical Corp. 101

Electronic Measurement Corp. (EMC) 88

Euphonics Marketing 76

Finney Co. 25

Gernsback Library, Inc. 98-99

Hallmark Instruments 81

Heald's Engineering College 101

Heath Company 68-69

IBM Corporation 32

International Crystal Mfg. Co., Inc. 70, 112

Jensen Manufacturing Division (The Muter Company) Third Cover

Jerrold Electronics Corporation (Distributor Sales Division) 89

JFD Electronics Corp. 67

Judson Research and Mfg. Co. 70

Lafayette Radio Electronics 93-94

Mallory Distributor Products Company (Div. of P. R. Mallory & Co., Inc.) 27

Mercury Electronics Corporation 91

National Radio Institute 8-11, 81

National Technical Schools 3

Oxford Transducer Corporation 26

Perma-Power Company 22

Poly Pak 111

Progressive "Edu-Kits" Inc. 92

Quam-Nichols Co. 71

Quietrole Co. 100

RCA Electronic Components & Devices

Citizens' Band 7

Test Equipment 77

Tubes Fourth Cover

RCA Institutes, Inc. 28-31

Radio Shack 102-105

Rye Sound Corporation 90

Sams & Co., Inc., Howard W. 17, 78

Sarkes Tarzian, Inc. (Tuner Service Div.) 16

Scott, Inc., H. H. 24

Sencore 87

Sonotone Corp. (Electronic Applications Div.) 12

Stancor Electronics (Essex Wire Corporation) 90

Tarzian, Inc., Sarkes (Tuner Service Div.) 16

Tech Press Publications 106

United Radio Co. 109

University, LTV (Div. of Ling-Temco-Vought, Inc.) 13

Viking of Minneapolis, Inc. 80

Warren Electronic Components 95

Webster 88

Weller Electric Co. 86

Winegard Co. 14-15

MARKET CENTER 108-111

Colordaptor

Edmund Scientific Corp.

Electronic Components Co.

Fair Radio Sales

Linda Sales Corporation

Music Associated

Surface Conduction, Inc.

Transistors Unlimited Company

SCHOOL DIRECTORY 107

American Institute of Engineering & Technology

Coyne Electronics Institute

Grantham School of Electronics

Indiana Home Study Institute, The

Milwaukee School of Engineering

Northrop Institute of Technology

Tri-State College

Valparaiso Technical Institute

BEFORE You Buy Receiving Tubes, Transistors, Diodes, Electronic Components & Accessories send for Giant Free Zalytron Current Catalog, featuring all STANDARD BRAND TUBES all Brand New Premium Individually Boxed, One Year Guarantee—all at BIGGEST DISCOUNTS in America! We serve professional servicemen, hobbyists, experimenters, engineers, technicians. WHY PAY MORE? ZALYTRON TUBE CORP., 469R Jericho Turnpike, Mineola, N.Y. 11502

TRANSISTOR IGNITION! Coil, ballast 7.95 Free parts lists. TRANSFIRE Carlisle 20, Mass. 01741

ANY TV BONDED TUBE \$23.00. One year warr. (you keep the dud). Immediate delivery send check or money order. SAMSON KINESCOPES INC., 250 N. Goodman St., Roch. N.Y. 14607

NEED RESISTORS? Factory fresh, NAME BRAND, $\frac{1}{2}$ watt, 10% standard carbon resistors. Any regular value from 10 ohms to 22 megohms, \$0.05 each! Postpaid. Any quantity assorted. Minimum order \$1.00. TEPCO, Box 508, Tullahoma, Tenn.

SCHEMATICS—\$1. Radio, Television. Prompt. BROWN's, 605 Naomi, Philadelphia, Penna. 19144.

TUBES. "Oldies", latest. Lists free. STEINMETZ, 7519 Maplewood, Hammond, Indiana, 46324.

RADIO & TV TUBES 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, California 92105

BUILD DIGITAL CIRCUITS that add, subtract, multiply, and divide using switches and diodes. Instructions. Any two functions \$1. FERWALT, Box 27, Lewiston, Idaho 83501.

COIN-COMBER metal detector. Sensitive silicon transistor circuit. \$39.95 assembled. RACOM, Box 13469-B, Orlando, Fla.

TRANSFORMER BARGAINS! Free catalog. Write CALEMCO, Box 585, San Fernando, Calif.

FREE Catalog. Electronic parts, tubes. Wholesale. Thousands of items. Unbeatable prices. ARCTURUS ELECTRONICS RE, 502-22 St., Union City, N.J. 07087

FREE CATALOGUE transistorized wireless and wired modules, semiconductor kits, electronic components. JONATHAN NEIL ELECTRONIC SALES, 5 West Sunrise Highway, Freeport, N.Y.

DIAGRAMS, servicing information: Radio, \$1.00; Television, \$2.00. SUPREME, 1760 Balsam, Highland Park, Illinois 60035

CUSTOM DESIGN and Built Electronics Equipment BROWN-DAVIS ENTERPRISES RFD-4, Abilene, Kansas 67410

EDUCATION/INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING. New home study course covering all makes electronic organ including transistors. Experimental kits—schematics—trouble-shooting. Accredited NHSC-GI Approved. Write for free booklet. NILES BRYANT SCHOOL, 3631 Stockton Blvd., Dept. F, Sacramento 20, Calif.

HIGHLY—effective home study review for FCC commercial phone exams. Free literature! COOK'S SCHOOL OF ELECTRONICS, Craigmont, Idaho 83523.

FCC LICENSE in 6 weeks. First Class Radio Telephone. Results Guaranteed. ELKINS RADIO SCHOOL, 2603E Inwood, Dallas, Tex.

SLEEP LEARNING. Hypnotism! Tapes, records, books, equipment. Details, strange catalog FREE. RESEARCH ASSOCIATION, Box 24-RD, Olympia, Wash.

BROADCASTING, Communications Electronics taught quickly—resident classes; correspondence. Free details. Write: Dept. 4, GRANTHAM SCHOOLS, 1505 N. Western, Hollywood, Calif. 90027

FCC LICENSE training through tape recorded instruction. Bob Johnson AUDIO-VISUAL LICENSE PREPARATION, 1201 Ninth, Manhattan Beach, Calif.

ZIP

stands for the Post Office Department's new Zoning Improvement Plan. When renewing your RADIO-ELECTRONICS subscription, or sending us a change of address, please let us know what your ZIP Code is. We'll add it to your address mailing plate ... and you'll get speedier delivery

service from the Post Office.
By the way, when writing to us, address:



RADIO-ELECTRONICS,
154 West 14 St.,
New York, N.Y.
10011

CLASSIFIED ADVERTISING ORDER FORM

For complete data concerning classified advertising please refer to box elsewhere in Market Center section.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

{@ .30 Non-Commercial Rate} = \$
No. of Words {@ .60 Commercial Rate}

Total Enclosed \$

Insert time(s) Payment must accompany order unless placed through accredited advertising agency 95
Starting with issue

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

SIGNATURE _____


MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 154 WEST 14TH ST., NEW YORK, N.Y. 10011

DOUBLE BONUS SALE

FREE
\$25 WORTH OF
Transistors
Diodes
Rectifiers
Knobs
Condensers
Coils, etc.
Include 25¢ for handling

FREE
\$1 POLY PAK OF YOUR CHOICE

BOTH FREE WITH ANY \$10 ORDER

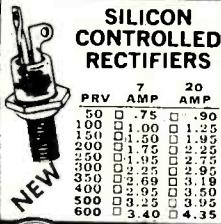

500 MC Silicon Planar
POWER TRANSISTOR
\$149 (ACTUAL SIZE)
Fairchild

NEW FACTORY TESTED DOLLAR POLY PAKS

- 30 SWITCHING TRANSISTORS, TO5 cases/staytheen \$1
- 10-WATT ZENER STUD ANY VOLTAGE to 100V \$1
- 1 CONTROLLED SCR SWITCH. Transistor. TO18. \$1
- 3 40-WATT TRANSISTORS N80BVols pnp, stud. \$1
- "MICRO-T" TRANSISTOR, like TMT-1613. npp, \$1
- 4 -2N155 TRANSISTORS, or equals, TO3 cases \$1
- 2-800 MC, 2N709 NPN Silicon planar TO46 . . \$1
- 3 2N711 300MW. 300 MC, PNP MESA, TO18 . . \$1
- 1 40W, 2N1648 TRANSITR NPN MESA, \$1
- 2 25-AMP SILICON RECTIFIERS, \$1
- 4 ZENER REFERENCES, 1N429, 6-volt, silicon . \$1
- 2 "TINY" 2N1613 2W, 100MC, TO46 case, npn \$1
- 2 500MC TRANSITRS, 2N984, mesas, pnp, TO18 \$1
- 10 "PIN HEAD" TRANSISTORS, rf, if, pnp . . \$1
- 4 2N43 OUTPUT TRANSISTORS, by GE, pnp, TO5 \$1
- 4 2N33 NPN SILICON transistors, by GE, TO5 \$1
- 8 2-6Amp RECT's, studs, silicon, 50 to 400V \$1
- 10 MICRO DIODE ZENER gold axial by Transistor \$1
- 4 -WATT PLANAR TRANSITRS, 2N497, 2N498 \$1
- 4 2N35 TRANSISTORS, npn, by Sylvania; TO22 . \$1
- 6 "MICRO" TRANSISTORS, 2N131's, 1/16", rf . \$1
- 4 CK721 TRANSISTORS, pnp, aluminum case . \$1
- 10 1000 MC-1N251 GERMANIUM DIODES . . \$1
- 30 MC TRANSISTORS, like 2N247, Sylvania . . \$1
- 85 W. TRANSISTOR, silicon npn mesa, 2N424 . \$1
- 5 SUN BATTERIES TO 1 1/2" sizes, lite sensitive \$1
- 15 PNP SWITCHING TRANSISTORS, asstd., TO5 \$1
- 10 NPN SWITCHING TRANSISTORS, 2N338, 440 \$1
- 15 PNP TRANSISTORS, CK722, 2N35, 107 . . . \$1
- 15 NPN TRANSISTORS, 2N35, 170, 440, . . . \$1
- 30 TRANSISTORS, rf, if, audio, no test, TO5 . . . \$1
- 4 35-W. TRANSITRS, 2N1434, CBS, TO10, stud \$1
- 2 2N708 SILICON 400MC NPN PLANAR, TO46 . \$1
- 10 POPULAR CK772 TRANSISTORS, pnp, no test \$1
- 5 2N107 TRANSITRS, by GE, npn, pop, audio pak \$1

PARTS BY THE POUND
500-1000 pcs

ONE POUND DISCS 488

TRANSISTORS

100 for \$298

Power, Audio, RF, untested

- 4 2N170 TRANSISTORS, by GE, npn for gen'l rf \$1
- 25 TOP HAT RECTIFIERS 750 Ma silicon, 50-400V \$1
- 25 GERMANIUM & SILICON DIODES, no test . . \$1
- 1 85W SILICON PWR TRANSITR, npn, like 2N121 \$1
- 6 "TEXAS" 750 MA 400V RECTIFIERS, leads \$1
- 3 TRANSITON TRANSITRS, 2N341, 42, 1W, npn \$1
- \$25 RELAY SURPRISE, sealed, tiny types . . . \$1
- 3 INFRA-RED DETECTORS, with leads \$1
- \$25 SURPRISE PAK: transistors, rect, diodes, etc. \$1
- 40 PRECISION RESISTORS, $\frac{1}{2}$, 1, 2W, 1% values \$1
- 30 CORNING "LOW NOISE" resistors, asstd. . \$1
- 60 TUBULAR CONDENSERS, to .5mf, to 1KV, asstd \$1
- 40 DISC CONDENSERS, 27mmf to .05mf to 1KV \$1
- 60 TUBE SOCKETS, receptacles, plugs, audio, etc. \$1
- 30 POWER RESISTORS, 5 to 50W, to 24 Kiloms. \$1
- 50 MICA CONDENSERS, to 1mf, silvers too! . \$1
- 10 VOLUME CONTROLS, to 1 meg, switch too! . \$1
- 10 ELECTROLYTICS, to 500mf, asstd FP & tubulars \$1
- 50 RADIO & TV KNOBS, asstd. colors & styles \$1
- 10 TRANSISTOR ELECTROLYTICS: 10mf to 600m(\$1)
- 50 COILS & CHOKES, rf, rf, ant, osc, & more . . \$1
- 35 TWO WATERS, asstd incl: A.B., 5% too! . . \$1
- 75 HALF WATERS, asstd incl: A.B., 5% too! . . \$1
- 60 HI-Q RESISTORS, $\frac{1}{2}$, 1, 2W, 1% & 5% values \$1
- 10 PHONO PLUG & JACK SETS, tuners,amps . \$1
- 50 TERMINAL STRIPS, 1 to 8 solder lug types . . \$1
- 30 "YELLOW" MYLAR CONDENSERS, asstd val \$1
- 60 CERAMIC CONDENSERS, discs, npo's, to .05 \$1
- 3 TRANSISTOR SUBMINIATURE AMPLIFIER \$1
- 4 TRANSISTOR TRANSFORMERS, asstd worth \$25 \$1
- 1 FILAMENT TRANSFORMER, 117 to 6.3vct, 3A \$1
- 3 GEIGER COUNTER DETECTOR, tubes, assorted \$1

10 XMAS BARGAIN CATALOG ON: PARTS RECTIFIERS TRANSISTORS SCRS ZENERS


TERMS: Send check, money order, Add postage—av. wt. per pak \$1. Rataed net 30 days. COD 25%.

P.O. BOX 942R
SO. LYNNFIELD, MASS.
"PAK-KING" of the world

Circle 138 on reader's service card

NEW

FROM INTERNATIONAL

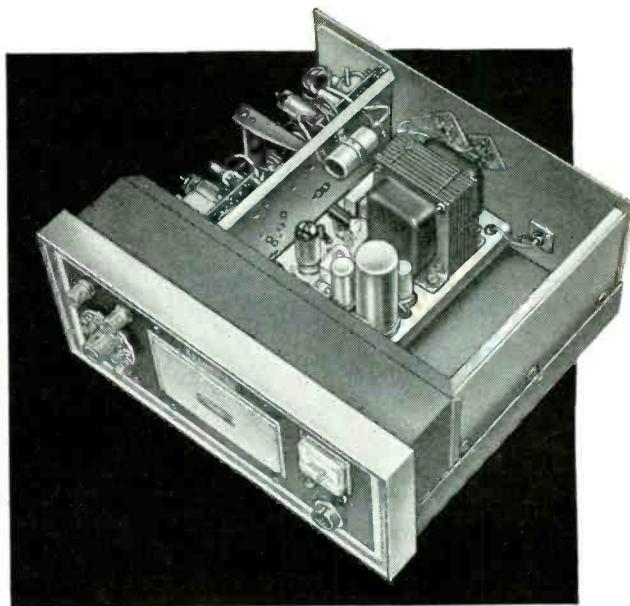

MODEL 660

CITIZENS RADIO TRANSCEIVER

The International Model 660 . . . new in styling . . . new in advanced technical features, combines space-age colors and decor with greater operating convenience.

Designed for base and mobile installations, the Model 660 provides instant push-to-talk operation on all 23 channels. Silicon transistors and tubes are combined in a new hybrid circuit for the highest degree of reliability.

A transistor power supply operates from 6/12 or 115 vac power sources.

See the International Model 660 at your dealer today. It comes complete with crystals, dynamic microphone with coil cord.

- Distinctive New Panel Design
- New Hybrid Circuits
- New Zener Speech Limiter
- Frequency Synthesized Crystal Controlled 23 Channel Operation
- Dual Conversion Receiver
- Illuminated Channel Selector Dial
- Ten Tubes
- Five Silicon Transistors
- Two Power Transistors
- Eleven Silicon Diodes

Write Today For The Name Of Your Nearest International Dealer.

FCC Citizens Radio license required. All use must conform with Part 95, FCC Rules and Regulations.

INTERNATIONAL

CRYSTAL MFG. CO. INC.

18 NORTH LEE — OKLA. CITY, OKLA.

Circle 148 on reader's service card



Jensen Model HS-2 Stereo Headphones bring an exciting new dimension to your favorite recordings. Unusually smooth full range undistorted output set these headphones apart. Soft foam cushions provide feather weight comfort and preserve the undistorted bass response without pressure. Response is true, com-

HAVE YOU HEARD

?

plete, distortion-free from below 20 to 17,000 cycles!

HS-2 Stereo Headphones may be connected to any stereo or mono system. A full 8-foot input cable is conveniently located to the rear of the left phone. Of course, it carries the Jensen 5 year hi-fi guarantee. Suggested resale price \$24.95. See your Jensen hi-fi dealer.



JENSEN MANUFACTURING DIVISION/THE MUTER COMPANY 6601 SOUTH LARAMIE AVENUE, CHICAGO, ILLINOIS 60638
Canada: Radio Speakers of Canada, Ltd., Toronto • Argentina: Ucoa Radio, S.A., Buenos Aires • Mexico: Fapartel, S.A., Naucalpan, Mex.
Circle 149 on reader's service card

RCA announces a zero defects program



through...

personal
quality
performance

RCA's effort to apply some of the concepts of missile-type reliability to the production of commercial receiving tubes

You lose time and money whenever a tube fails.

To minimize such losses, RCA has initiated *still another quality control measure* to guard against tube failure and *keep profits in your pocket*.

It's our ZERO DEFECTS program, an attempt to eliminate as far as possible the factor of human error from commercial receiving tube production.

RCA personnel engaged in the production of RCA receiving tubes have voluntarily signed a pledge of PERSONAL QUALITY PERFORMANCE...a pledge to strive for error-free performance in every task they undertake in the making of RCA receiving tubes.

Their pledge is one more assurance to you of tube reliability and greatest possible reduction in callbacks when you sell and install RCA receiving tubes.

RCA Electronic Components and Devices, Harrison, N.J.



The Most Trusted Name in Electronics