

**SERVICE COLOR TV  
TRAPS AND PITFALLS**

■ DEC. 50c

# Radio-<sup>IND</sup>Electronics

TELEVISION • SERVICING • HIGH FIDELITY

A  
GERNSBACK  
PUBLICATION

HUGO GERNSBACK, Editor in-chief

135

**REPAIR**  
Record Changers

**BUILD**  
The Busy Box:  
A THINKING TOT'S TOY

**TRACK**  
Radio and  
TV Interference

**BUILT FROM A KIT:**  
All-transistor  
Electronic Organ



# STEP UP

TO WIDER RANGES  
GREATER ACCURACY




## Model 630-NA

VOLT-OHM-MILLIAMMETER  
PRICE \$79<sup>50</sup>


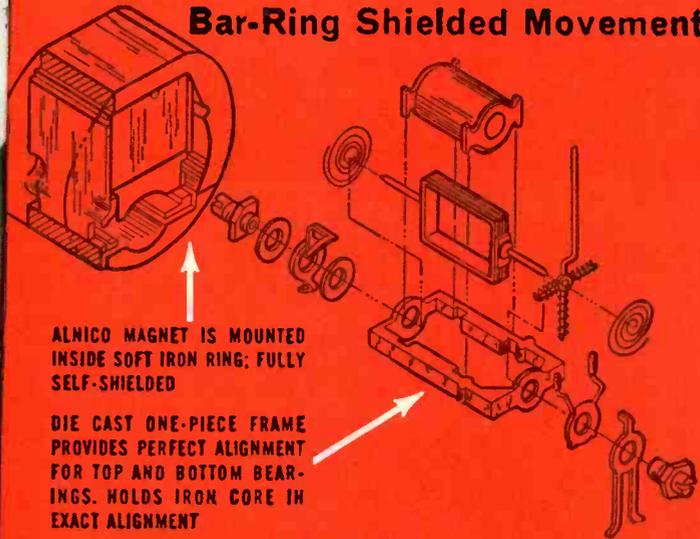
### EXCLUSIVE PATENTED Bar-Ring Shielded Movements




## FACTS MAKE FEATURES:

- 1** 70 RANGES—nearly double those of conventional testers. Un-breakable window. Mirror Scale.
- 2** HIGHEST ACCURACY—1½% DC to 1200 volts, 3% AC to 1200 volts; mirror scale and knife-edge pointer to eliminate parallax.
- 3** FREQUENCY COMPENSATED—Flat from 20 CPS to 100,000 CPS; varies from ¼ to 1¼ DB at 500,000 CPS. Temperature compensated. Meter protection against overloads.

THE TRIPLET ELECTRICAL INSTRUMENT COMPANY, BLUFFTON, OHIO  
*Circle 1 on reader's service card*

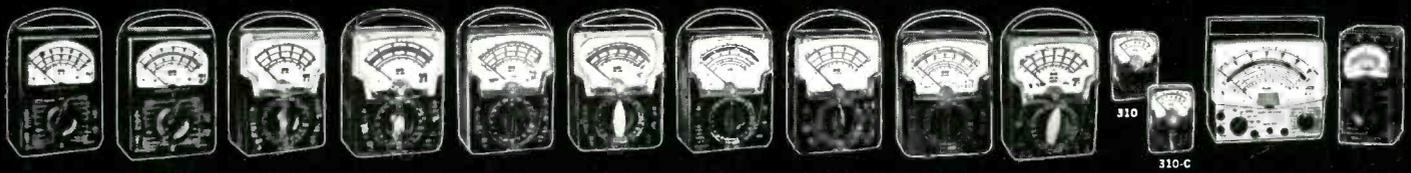
### Uses Unlimited:

- FIELD ENGINEERS ■ APPLICATION ENGINEERS ■ ELECTRICAL, RADIO, TV, AND APPLIANCE SERVICEMEN
- ELECTRICAL CONTRACTORS ■ FACTORY MAINTENANCE MEN ■ INDUSTRIAL ELECTRONIC MAINTENANCE TECHNICIANS ■ HOME OWNERS, HOBBYISTS



THE WORLD'S MOST COMPLETE LINE OF V-O-M'S. AVAILABLE FROM YOUR TRIPLET DISTRIBUTOR'S STOCK

# Crime does pay!

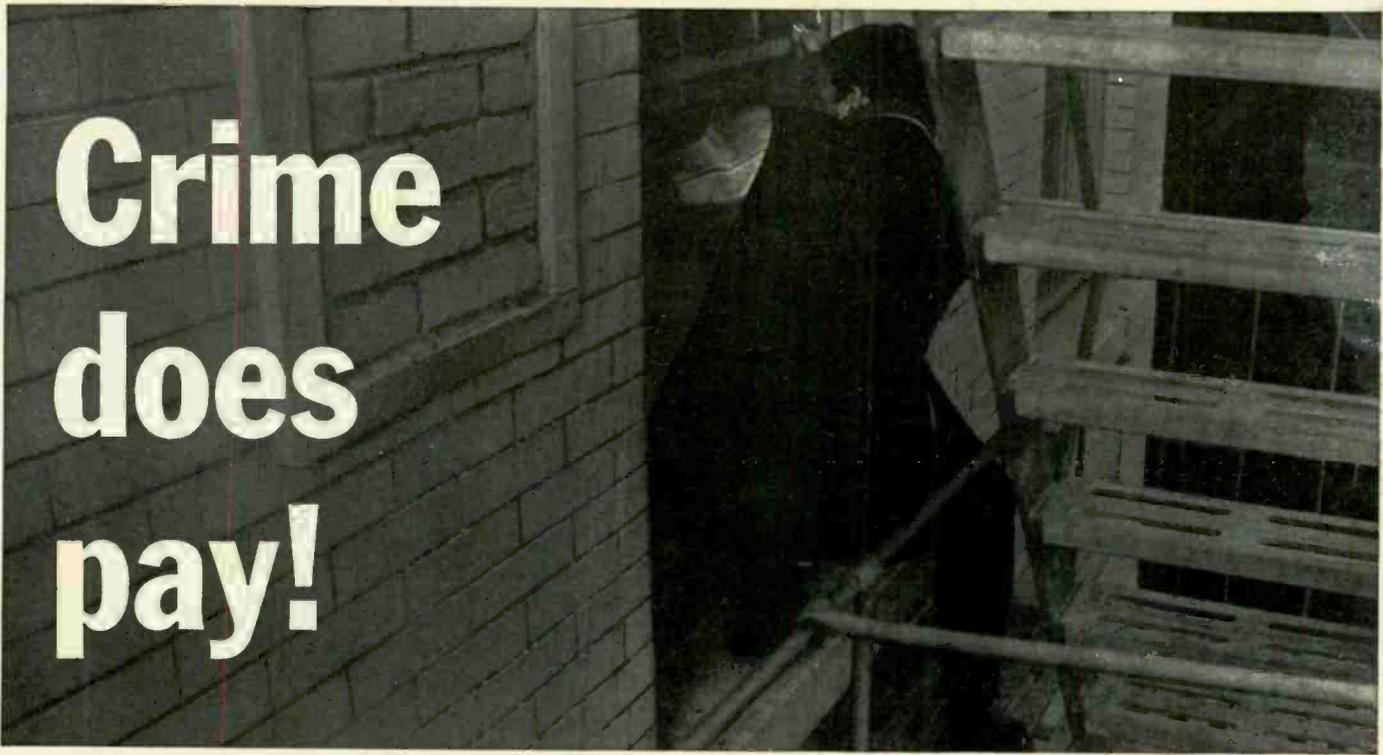

**Every 40 seconds a burglary takes place in the United States.**

#### TECHNICAL INFORMATION

The RADAR SENTRY ALARM is a complete U.H.F. Doppler Radar System which saturates the entire protected area with invisible r.f. microwaves. It provides complete wall to wall—floor to ceiling protection for an area of up to 5,000 square feet. Without human movement in the protected area, the microwave signal remains stable. Any human movement (operation is unaffected by rodents and small animals) in the area causes the doppler signal to change frequency approximately 2 to 4 cps. An ultra-stable low frequency detector senses this small frequency change, amplifies it and triggers the police type siren—which is heard up to a half mile away.

In addition, the RADAR SENTRY ALARM's protection can be extended to other areas with the use of the following optional accessories:

- remote detectors for extending coverage to over 10,000 sq. ft.
- rate of rise fire detector U.L. approved for 2,500 sq. ft. of coverage each (no limit on the number of remote detectors that can be used)
- hold-up alarm
- central station or police station transmitter and receiver (used with a leased telephone line)
- relay unit for activating house lights
- battery operated horn or bell which sounds in the event of: powerline failure; equipment malfunction or tampering

At that rate, it's a multi-million dollar a year business...for burglars.

And an even better business opportunity for you.

Why? Because burglary can be stopped...with an effective alarm system.

In fact, police and insurance officials have proved that an alarm system reduces, and in many cases, eliminates losses—even helps police apprehend the criminal.

Here's where you come in.

Only a small percentage of the more than 100 million buildings—stores, offices, factories, schools, churches and homes are protected by an effective alarm system.

That means virtually every home, every business is a prospect.

You can sell them!

And you don't have to be a super-salesman to sell the best protection available—a Radar Sentry Alarm unit. All you have to do is demonstrate it...it sells itself.

A glance at the technical information shows why.

It's the most unique and effective alarm system ever invented.

And here's the proof.

In the past six years, thousands of RADAR SENTRY ALARM units have been sold in the Detroit, Michigan area alone—sold by men like yourself on a part-time and full-time basis.

Here are just a few customers who are protected by RADAR SENTRY ALARMS:

U.S. Government  
U.S. Air Force  
Detroit Board of Education  
Hundreds of Churches,  
Banks, Businesses and  
Homes.

Everyone is a prospect.

So take advantage of your profession. Put your technical knowledge and experience to work for you in a totally new area—an area that will make money for you!

Don't wait!

Let us prove that crime does pay.

Become a distributor.

Write now for free details.

#### RADAR SENTRY ALARM



Circle 2 on reader's service card

Mail to: RADAR DEVICES MANUFACTURING CORP.  
22003 Harper Ave., St. Clair Shores, Michigan 48080



Please tell me how I can have a business of my own distributing Radar Sentry Alarm Systems. I understand there is no obligation.

Name \_\_\_\_\_ RE-12

Address \_\_\_\_\_

City \_\_\_\_\_ State & Code \_\_\_\_\_

# Get on the green.



Get with the new PRECISE Green line for truly new design and decor in test instruments. These unique units have color dynamic front panels featuring easy-on-the-eyes Green to aid readability and accuracy. New functional design and layout make operation fast and foolproof. Inside, they're on line with sophisticated circuitry checked out for reliability. So when it comes to test instruments, take the best course. Swing with PRECISE scopes, VTVMs, power supplies, signal generators, tube testers, decade boxes and probes.

#### MODEL 636

**AF SINE SQUARE GENERATOR** — 20 cps to 200 kc in four ranges. Less than 0.25% sine wave distortion at 10 vrms into 600 ohms load.

Kit: \$45.95 Net    Wired: \$61.95 Net

#### MODEL 780

**CONTINUOUSLY VARIABLE REGULATED VOLTAGE SUPPLY** — Regulated dc output from 0 to +400 v at 150 ma, and 0 to -150 v bias. Also provides unregulated ac. Meters for voltage and current.

Wired: \$99.95 Net

#### MODEL 905

**VACUUM TUBE VOLTMETER** — Comes with assembled dc/ac-ohms probe. Direct reading of p-p voltages. Separate ac low voltage scale. Low 0.5 vdc range for transistor circuit measurements.

Kit: \$32.95 Net    Wired: \$49.95 Net



**PRECISE ELECTRONICS** / Division of Designatronics, Inc. / Mineola, L. I., N.Y.

Circle 3 on reader's service card

# Radio-Electronics

Over 55 Years of Electronic Publishing

## SEMI-ANNUAL INDEX

84 Index for July–December 1965, inclusive

## EDITORIAL

31 Fuel Cells.....Hugo Gernsback

## AUDIO

### COVER STORY

40 We Built An Electronic Organ.....Fred Shunaman  
*Formidable-sounding project is easy with new Heathkit*

42 Home "Message Center" Features Electronic Stop.....Robert F. Scott  
*Miniature tape recorder signals when message has been left*

46 Repair Record Changers.....Homer L. Davidson  
*All at sea with mechanical things? This article should help*

56 Feedback, Phase & Instability.....Norman Crowhurst  
*A peek into what makes modern amplifiers sound so good—or so bad*

64 Equipment Report: Sonotone RM-2 Speaker System; Electro-Voice Sentry II Studio Monitor Loudspeaker (p. 68)

77 RIAA Issues Tape Standard

80 The Search for Sound.....Elbert Robberson  
*Restrain yourself, buddy*

## ELECTRONICS

48 De Luxe Printing Timer.....Ronald L. Ives  
*Build-your-own darkroom accessory works with contact printers or enlargers*

58 The Ion Gage—A Tube Looking for a Vacuum.....T. F. Sinclair  
*It has a large, deliberate hole in it*

## TEST INSTRUMENTS

53 Scope Plug-In Unit Seeks Range, Shows Waveform

54 Scope Improvers.....Elmer C. Carlson  
*Four quick, inexpensive alterations for low-priced scopes*

64 Equipment Report: EICO Model 342 FM Multiplex Generator

69 Add a Zero-Setter to Your AC VTVM.....Lyman E. Greenlee  
*Mercury cell bucks out zero offset due to internal hum and noise*

## GENERAL

14 Service Clinic.....Jack Darr  
*Replacing Weak High-Current Seleniums*

43 What's New

44 Busy-Box: A Thinking Tot's Toy.....John A. Tiso  
*Build one for the Junior Engineer*

### CAREER SERIES

51 The Factory Analyzer.....Charles R. Wheeler  
*Could you make the grade in this exciting field?*

55 What's Your EQ?

## TELEVISION

32 How to Track Interference.....Thomas R. Haskett  
*Systematic procedure for finding the source of radio-TV interference*

38 Service Color TV—Traps and Pitfalls.....Matthew Mandl  
*Some familiar black-and-white circuits are a little different in color sets*

## RADIO

34 Are We Really Making Progress?.....Harold Davis

▶ 35 Transistorize Your Tube Portable.....James E. Pugh, Jr.  
*Emitter-coupled stages use old antenna, i.f. and oscillator transformers*

50 Check That Antenna Pigtail

## THE DEPARTMENTS

10 Correspondence  
97 New Books  
77 New Literature

71 New Products  
87 New Semiconductors & Tubes  
4 News Briefs

94 Noteworthy Circuits  
88 Technotes  
92 Try This One  
55 50 Years Ago

70 Reader's Service Page

Cover photograph by Harry Schlack

HUGO GERNSBACK, editor-in chief and publisher. M. HARVEY GERNSBACK, editor. Fred Shunaman, managing editor. Robert F. Scott, W2PWG, technical editor. Peter E. Suthem, associate editor. Jack Darr, service editor. I. Queen, editorial associate. John J. Larson, eastern sales manager. Wm. Lyon McLaughlin, technical illustration director.

RADIO-ELECTRONICS, December 1965, Volume XXXVI, No. 12. Published monthly by Gernsback Publications, Inc. at Ferry Street, Concord, N. H. 03302. Second-class postage paid at Concord, N. H. Printed in U.S.A. One-year subscription rate: U. S. and possessions, Canada, \$5. Pan-American countries, \$6. Other countries, \$6.50. Single copies: 50¢. © 1965, by Gernsback Publications, Inc. All rights reserved. POSTMASTERS: Send Form 3579 to 154 W. 14th St., New York 10011.



Member,  
Institute of High Fidelity  
Radio-Electronics  
is indexed in  
Applied Science  
& Technology Index  
(Formerly  
Industrial Arts Index).

# NEWS BRIEFS

## AUTOMATED NEWSPAPER ESTABLISHED IN ENGLAND

The Evening Post of Reading, England is going to press with computer control, photographic typesetting and offset color printing. The owner of the new Post, Lord Thomson of Fleet, states that computer operations may be extended to more of his 128 newspapers. He said, "I can envisage one big computer that would be capable of setting type for the whole of England."

The copy is first typed manually onto punched tape. This tape is fed into a computer, which divides the typed material up into lines and justifies the lines—makes a uniform right margin—like a newspaper column. It also hyphenates words properly when they have to be divided at the end of a line.

The tape produced by the computer is fed into a photographic typesetting device that turns out readable newspaper columns. These are assembled on pages and reproduced on photosensitive plates from which the newspaper is printed by the offset method.

## ANALYZING HEARTBEATS ULTRASONICALLY


A device which uses the Doppler shifts of frequency in the ultrasonic echoes returned by moving surfaces is being used in cardiovascular research at the National Naval Medical Center in Bethesda, Md. The invention of J. R. Richards, it can detect the respiratory activity of a goldfish, monitor different parts of the heart, or keep check on a baby's heart during delivery. Cost is estimated at about one-seventh the price of a complete electrocardiograph.

## NEW LASER LIGHT DETECTOR HAS HIGH SENSITIVITY, SPEED

A new supersensitive light detector for practical laser communications has been announced by the Radio Corporation of America. Developed by Drs. Henry S. Sommers, Jr. and Edward K. Gatchell, the new light sensor is said to be the first detector developed with a sensitivity, speed and frequency range that could make laser communications practical across the optical spectrum. It can sense up to 100 million intensity changes a second in a beam of light. Thus it could dis-

tinguish as many as 25 separate TV programs carried simultaneously.

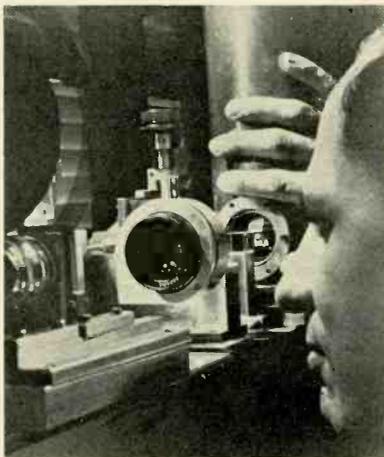The new light sensor is a freckle-size speck of photoconductive material mounted in a small cavity, con-



*Herbert Ogawa of RCA's Princeton Laboratories checks the high-frequency laser detector.*

tinuously bathed in microwaves at a frequency of 10 gigacycles. When amplitude-modulated light enters the cavity and strikes the photoconductor, it frees electrons, which begin to oscillate rapidly up and down within the material in response to the alternating electric field of the microwaves. The amplitude of these oscillations controls the amount of microwave power permitted to leave the cavity. Thus intensity variations in the incoming light are converted to intensity variations in the outgoing microwaves. The modulated microwave signal can then be detected and processed by conventional techniques.

## MICROWAVE FREQUENCY MULTIPLIER SHOWS 4-DB POWER GAIN

The first single transistor to offer watts of microwave power was announced recently by RCA Electronic Components & Devices. The new device is an "overlay" transistor, RCA 2N4012. It extends transistor performance into the gigacycle frequency region with 2.5 watts output and 4 db conversion gain when operated as a tripler with output at 1 gc. One 2N4012 can replace both the transistor power-amplifier and varactor-diode stages formerly required, making it possible to simplify circuit design greatly and to reduce cost in new telemetry and microwave equipment.

Frequency multiplication with power amplification is possible with the overlay structure because the variable collector-to-base capacitance becomes the nonlinear element of a harmonic generator. The collector-to-base capacitance acts like a variable-capacitance diode, or varactor, in parallel with the amplifier section of the transistor.

In the overlay structure, which has been used before for uhf-microwave work, are a number of individual emitter sites, all connected in parallel and used with a single base and collector region. This arrangement provides a substantial increase over other transistor structures in emitter periphery, increasing current or power; and a corresponding decrease in emitter and collector areas, reducing input and output capacitances. The overlay structure thus offers greater power output, gain, efficiency and frequency capability.


## SWEDISH STAMP COMMEMORATES ONE HUNDRED YEARS OF ITU

The Swedish government has issued a stamp with a short-wave antenna motif, commemorating the centenary of the International Telecommunications Union. The stamp is mod-



eled after an actual log-periodic antenna belonging to a remote-controlled short-wave transmitting station of the Swedish Post Office. The antenna is installed at Grimeton. It is rotatable, and both its direction and frequency are automatically controlled from Stockholm, 300 miles away.

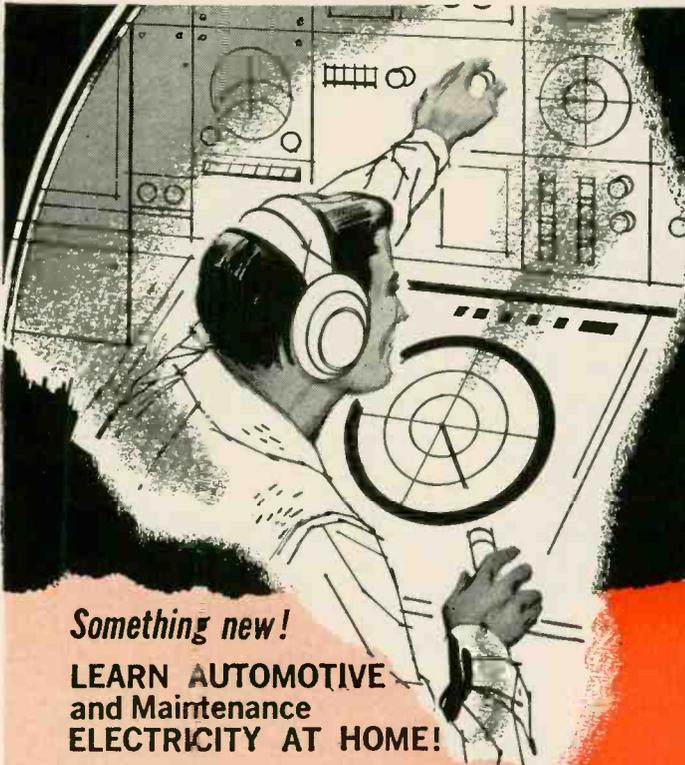The 43-meter antenna and its single-sideband short-wave transmitter



# 5,000 FIRMS HAVE EMPLOYED DeVRY TECH ELECTRONICS GRADUATES...

There Must be a Reason!

*Something new!*

## LEARN AUTOMOTIVE and Maintenance ELECTRICITY AT HOME!

Here's another great opportunity for the man who wants his own business or a bigger pay check with a brighter future. It is a NEW DeVry program that gives you the advantage of earning while you learn.

Prepare in spare time at home for profitable jobs which can take you all the way from trouble-shooting on the electrical systems of automobiles, marine engines, trucks, tractors and other gasoline engines, to the general maintenance of electrical equipment in the home or in light industry.

DeVry's new program "brings the classroom to your home" through the magic of AUDIO-VISUAL AIDS: Lectures recorded by DeVry instructors combined with colorful 8 x 10" transparencies to make learning easier. You get the advantages of "programmed" learning through modern texts which are also handy for future



reference. To develop practical skill, you get and keep valuable shop equipment and manuals. This includes building the brand-new DeVry Transistorized Automotive Analyzer and the DeVry Silicon Battery Charger — ideal "tools" for earning extra money as you go.

This new program covers the entire electrical systems in automobiles and other vehicles, including transistorized ignition systems, alternators and regulators, and other applications. In the maintenance field, it covers lighting, electric motors, controls, wiring — even transistors. The graduate from this program can be either a specialist as a troubleshooter on the electrical system of an automobile, or handle electrical lighting, heating, alarm and control systems. It is ideal for "one man" maintenance departments.

Check coupon at right and mail it today for FREE facts.

ACCREDITED MEMBER OF NATIONAL HOME STUDY COUNCIL

## DeVry Technical Institute

Chicago

*Let Us Prepare You at Home or In  
One of Our Two Big Resident Schools  
for a Profitable Career in*

# ELECTRONICS

Across the continent, leading employers of personnel trained in electronics tell us that DeVry training is "Tops." Get the full story of DeVry Tech and the advantages it offers, by filling in the coupon below. The two free booklets pictured below tell of many fine opportunities for trained men in electronics: the great variety of jobs, from research, production, operation, maintenance and servicing of electronic equipment — to a neighborhood TV-radio sales and service business of your own. They'll tell you too, how DeVry has prepared men for good jobs with outstanding firms: on practical, "brass-tacks" problems with actual electronic equipment.

Here's good news: you don't need advanced education or previous technical experience to get started. If you can follow simple directions, you should be able to prepare with DeVry's help for real money in a field that may offer the opportunity of your lifetime.

**Employment Service:** With many employers so enthusiastic about DeVry Tech graduates, it's no wonder our Employment Service can help our graduates get started in electronics, or can assist them toward promotions later.

**FREE!**

SEND COUPON  
FOR BOOKLETS  
ON ELECTRONICS  
AS A CAREER



### DeVRY TECHNICAL INSTITUTE

4141 Belmont Ave., Chicago, ILL 60641, Dept. RE-12-V

I AM INTERESTED IN ELECTRONICS. Please give me your two free booklets, "Pocket Guide to Real Earnings" and "Electronics in Space Travel"; also include details on how to prepare for a career in this field. The following opportunity fields (check one or more) interest me:

- |  |   |
|--|---|
| <input type="checkbox"/> Space & Missile Electronics | <input type="checkbox"/> Communications         |
| <input type="checkbox"/> Television & Radio          | <input type="checkbox"/> Computers              |
| <input type="checkbox"/> Microwaves                  | <input type="checkbox"/> Industrial Electronics |
| <input type="checkbox"/> Automation Electronics      | <input type="checkbox"/> Broadcasting           |
| <input type="checkbox"/> Radar                       | <input type="checkbox"/> Electronic Control     |

I AM INTERESTED IN AUTOMOTIVE AND MAINTENANCE ELECTRICITY. Please supply further information.

NAME \_\_\_\_\_ AGE \_\_\_\_\_

ADDRESS \_\_\_\_\_ APT. \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_


Check here if you are under 16 years of age.

2095A

Available in Canada


# COMPLETE TUNER OVERHAUL

ALL MAKES—ONE PRICE

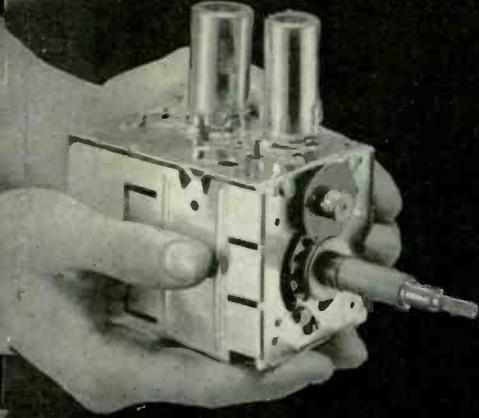
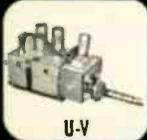
# 995

ALL LABOR AND PARTS (EXCEPT TUBES & TRANSISTORS)\*



Guaranteed Color Alignment—No Addit. Charge

Simply send us the defective tuner complete; include tubes, shield cover and any damaged parts with model number and complaint. Your tuner will be expertly overhauled and returned promptly, performance restored, aligned to original standards and warranted for 90 days.

UV combination tuner must be single chassis type; dismantle tandem UHF and VHF tuners and send in the defective unit only.

Exact Replacements are available for tuners unfit for overhaul. As low as \$12.95 exchange. (Replacements are new or rebuilt.)

Pioneers in TV Tuner Overhauling

# CASTLE

TV TUNER SERVICE, INC.

MAIN PLANT: 5715 N. Western Ave., Chicago 45, Illinois  
 EAST: 41-96 Vernon Blvd., Long Island City 1, N.Y.  
 IN CANADA: Castle Television Services, Ltd. . . .  
 Nation-wide service

\*Major Parts are additional in Canada

were designed and built by the German firm of Rohde & Schwarz. Sweden, one of the 20 nations that 100 years ago signed the International Telegraphic Convention that led to today's ITU, has issued the stamp in two denominations, 60 and 140 öre (about 12 and 24 cents).

## ULTRASONIC PROBES— NEW TEST INSTRUMENTS

An ultrasonic detector is being used to locate breakdowns in a series of 80 capacitors in 12-foot long, 2-million-volt flash X-ray pulser assemblies.

The equipment was designed by Lyman Davidson of the Field Emission Corp. in Oregon. According to its developer, it gives immediate indication of the breakdown's nature and locates it to a module of four capacitors among the 80.



Engineer checks for point of greatest noise in 2-mev flash X-ray system.

The device, known as the Delcon Ultrasonic Translator, is the size of a small camera, and consists of two interchangeable probes that respond to signals between 36 and 44 kc, plus equipment that translates the ultrasonic signal into the audible range and amplifies it for headphones.

The internal arcing caused by discontinuities in the encapsulating resin of a capacitor releases 40-kc energy which, when translated and amplified, is recognized by technicians as the sputtering, frying sound of corona.

## NEW YORK HI-FI SHOW BUCKS NEWSPAPER STRIKE

The 1965 New York High Fidelity Music Show, held Sept. 29 through Oct. 3, drew sizable crowds in spite of the fact that only two of New York's six major daily papers were being published, and therefore publicity was limited.

The extensive display of home

high-fidelity equipment, which covered four floors of the New York Trade Show Building, was sponsored by the Institute of High Fidelity.

With the 1965 show, transistors have finally gained the upper hand over tubes. While many manufacturers are still using tubes primarily, all are now producing transistor equipment. Marantz, one of the most steadfastly conservative manufacturers in the matter of transistor design, presented an all-solid-state stereo control center which its president, Saul Marantz, described as "a transistor version of the model 7." Dyna, another holdout, announced its first transistor stereo power amplifier, which was to become available some time early in 1966.

Shure displayed a transistor headphone-only amplifier, the first of its kind, and McIntosh introduced a tube-and-transistor receiver—the first such beast from that company.

Newer manufacturers, children of the solid-state era—Acoustech, C/M Labs and Hadley—also showed new transistor units.

The show also featured seminars for the public, designed to acquaint them with component high fidelity and its advantages over "package" or "furniture" systems.

## "MONGOLISM" LINKED TO RADAR

Mongolism, a form of mental retardation in children in which a fanciful resemblance to Mongol facial characteristics is noted, may be caused by radar exposure, according to a report presented to the annual meeting of the American Public Health Association held recently in Chicago.

A four-year study by Johns Hopkins University researchers shows that a significant number of mothers of mongoloid children had been exposed to larger than usual doses of radiation and that some of the fathers had a history of working around radar equipment.

German measles during the early part of the mother's pregnancy is considered the chief factor inducing mongolism.

## H. A. HARTLEY DEAD

H. A. Hartley, loudspeaker designer and audio-high-fidelity author, died late in August. He had a sudden heart attack while vacationing.

Mr. Hartley's name is associated with Hartley speakers and with the "Baffle" (box/baffle) enclosure. He was the author of the Gernsback Library book *Audio Design* and of other books on a variety of subjects, as well as numerous articles in RADIO-ELECTRONICS and other magazines.

← Circle 5 on reader's service card

# america's no. 1

LICENSED UNDER ONE OR MORE OF U.S. PATENTS 2,953,081; 2,995,879; 3,011,168; 3,108,280; 3,150,376 AND ADDITIONAL PATENTS PENDING IN U.S.A. AND CANADA. PRODUCED BY JFD ELECTRONICS CORPORATION UNDER EXCLUSIVE LICENSE FROM THE UNIVERSITY OF ILLINOIS FOUNDATION.



model LPV-VU12 Near-Fringe \$49.95



## VHF/UHF/FM ANTENNA!

Because it delivers best 82-channel TV performance—COLOR or black/white—plus FM/Stereo—using only a single downlead!

No other antenna works like the 82-channel JFD LPV-VU Color Log Periodic...

- Only the JFD LPV-VU is designed according to the patented **log periodic** design of the **University of Illinois Antenna Research Laboratories**.
- Only the JFD LPV-VU utilizes **capacitor-coupled Cap-Electronic** dipoles for **higher** mode operation that achieves **higher** gain, **narrower** beamwidths on VHF channels 7 to 13 and UHF channels 14 to 83. (Our competition's copies of the JFD LPV-VU use only **fundamental** mode which resonate as simple dipoles with consequently limited gain.
- Only the JFD LPV-VU offers true **frequency-independent** performance that insures brilliant **color** on any channel.

# JFD®

# LPV-VU®

# Color®


## LOG PERIODIC

You bet you can have everything you want in **one** antenna—VHF, UHF, FM—with a **single** down-lead, too! Start teaming up JFD 82-channel **LPV-VU** Color Log Periodics with all the 82-channel TV sets in your area—see the difference in profits and performance. Call your distributor or write for brochure 806.


32 million readers of LIFE will be seeing spectacular JFD LPV Color Log Periodic advertisements all season long. This unprecedented LIFE campaign will be pre-selling JFD LPV antennas for **you!**

Full-color television commercials will show millions more why the LPV's patented space-log periodic design works best on **any** channel—**color & black/white**.

5 GREAT MODELS TO CHOOSE FROM

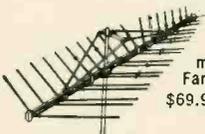


model LPV-VU18 Far-Fringe \$69.95

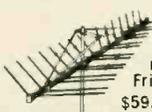


model LPV-VU15 Fringe \$59.95



model LPV-VU12 Near-Fringe \$49.95

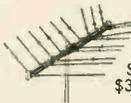

model LPV-VU9 Suburban-Fringe \$39.50

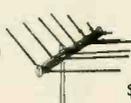

model LPV-VU6 Metro-Suburban \$27.50

JFD ELECTRONICS CORPORATION 15th Avenue at 62nd Street, Brooklyn, N. Y. 11219

Circle 6 on reader's service card

# ATTENTION! CB OPERATORS

save on citizens radio equipment

## Discontinued Models From International Radio Exchange

Select that extra transceiver for mobile or base installation, or equip a new station. Our stock includes International types as well as other makes.

*Write Today for A Complete List of Equipment in Stock*



**RADIO EXCHANGE**  
18 NO. LEE, OKLA. CITY, OKLA. 73102  
Division Of International Crystal Mfg. Co.  
Dealing In Used Citizens Radio Equipment



Circle 7 on reader's service card

## NOW! Solve Electronics Problems fast with New Patented Slide Rule.



That's right! This amazing new Electronics Slide Rule will save you time the very first day you use it. It's a patented, all-metal 10" rule that features special scales for solving reactance, resonance, inductance and circuitry problems . . . an exclusive "fast-finder" decimal point locator . . . widely-used formulas and conversion factors for instant reference. And there's all the standard scales you need to do multiplication, division, square roots, logs, etc.

Best of all, the CIE Electronics Slide Rule comes complete with an Instruction Course

of four **AUTO-PROGRAMMED** lessons. You'll quickly learn how to whip through tough problems in a jiffy while others plod along the old-fashioned "pad and pencil" way.

Electronics Slide Rule, Instruction Course, and handsome, top-grain leather carrying case . . . a \$50 value for less than \$20. Send coupon for **FREE** illustrated booklet describing this Electronics Slide Rule and Instruction Course and **FREE** Pocket Electronics Data Guide. Cleveland Institute of Electronics, 1776 E. 17th St., Dept. RE-117, Cleveland, Ohio 44114.

\*TRADEMARK

**GET BOTH FREE!**

**ELECTRONICS SLIDE RULE**



Send coupon today →

### Cleveland Institute of Electronics

1776 E. 17th St., Dept. RE-117, Cleveland, Ohio 44114

Send **FREE** Electronics Slide Rule Booklet. Special Bonus: Mail promptly and get **FREE** Pocket Electronics Data Guide too!

NAME \_\_\_\_\_ (Please Print)  
ADDRESS \_\_\_\_\_ COUNTY \_\_\_\_\_  
CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

A leader in Electronics Training... since 1934

Circle 8 on reader's service card

#### CALENDAR OF EVENTS

International Conference on UHF Television, Nov. 22-23; London, England  
Fall Joint Computer Conference, Nov. 30-Dec. 2; Convention Center, Las Vegas, Nev.  
Philco Service Training Meetings: Montgomery, Ala., Nov. 23, South Ala. Distrib. Co.; Andalusia, Ala., Nov. 24, J. B. Restaurant; Columbia, S. C., Nov. 29, Brown-Rogers-Dixon Co.; Winston-Salem, N. C., Dec. 1, Brown-Rogers-Dixon Co.; Raleigh, N. C., Dec. 2, Brown-Rogers-Dixon Co.; Chattanooga, Tenn., Dec. 13, Philco Distributors, Inc.; Knoxville, Tenn., Dec. 15, Philco Distributors, Inc. For more detailed information, exact times and places, contact the local Philco distributor.

#### BRIEF BRIEFS

Exact locations of piston-ring blow-by and cylinder scoring in operating engines and compressors are detected with an ultrasonic microphone by a new electronic analytical procedure.

Using an engine analyzer and an ultrasonic detection unit that translates sounds in the 36-44-kc range to audible signals, the electronic inspection gives the maintenance engineer an instantaneous scope presentation of each cylinder's complete stroke.

William Shockley, one of the Bell Lab team that invented the transistor, will join Bell Telephone Laboratories again after an absence of over 9 years. His new title is Executive Consultant on Applied Research and Development of Electronic Components.

A new type of magnetohydrodynamic generator, recently tested successfully by North American Aviation, uses a liquid metal rather than the superhot gas used in previous MHD generators.

US servicemen, according to a poll conducted by the USO in Vietnam, want voice tape recordings from their families for Christmas more than any other one thing. **END**

RADIO-ELECTRONICS is published by Gernsback Publications, Inc. Chairman of the Board: Hugo Gernsback President: M. Harvey Gernsback Vice President-Secretary: G. Aliquo Vice President-Treasurer: Charles A. Raible Editorial, Advertising, Subscription and Executive offices: 154 West 14th Street, New York 10011.

Subscribers: When requesting change of address please furnish an address label from a recent issue. Allow one month for change of address.

**ADVERTISING REPRESENTATIVES:** East: John J. Lamson, Eastern Sales Manager, RADIO-ELECTRONICS, 154 West 14th Street, New York 10011, 212 AL 5-7755; Midwest: P. H. Dempers Co., 740 North Rush Street, Chicago, Illinois 60611, 312 MI 2-4245; South Central: Media Representatives, Inc., 2600 Douglas Avenue, Irving, Texas 57060, 214 BL 5-6573; West Coast: J. E. Publishers' Representative Co., 8380 Melrose Avenue, Los Angeles, California, 213-653-5841; United Kingdom: Publishing & Distributing Co., Ltd., Mitre House, 177 Regent St., London W.1, England.

## RECENT PROFESSIONAL INSTALLATIONS OF AR SPEAKERS

### AR-2<sup>x</sup>

(\$89-\$102, depending on finish)

Aelian-Skinner reverberation system corrects excessively dead acoustics in the chapel of Choate School, Wallingford, Connecticut. Duncan Phye, musical director of the school, describes the effect on live pipe organ and chorus as "so natural one is not aware of an electronic reverberation system."

Similar Aelian-Skinner installations are operating in Christ Church, Cambridge, Massachusetts, and in St. John's Episcopal Church, Washington, D. C. AR speakers were chosen because of their lack of coloration, their undistorted, full-range bass, and their reliability.



### AR-2ax

(\$109-\$128)

Sound reinforcement system for the summer jazz concerts in the sculpture garden of New York's Museum of Modern Art. Live music had to be amplified without giving the sound an unnatural, "electronic" quality; AR speakers were chosen after testing many brands.



© 1965, LINCOLN CENTER FOR THE PERFORMING ARTS

### AR-3

(\$203-\$225)



One of the listening rooms in the Library & Museum of the Performing Arts at Lincoln Center in New York City. AR-3's were chosen for these rooms to achieve an absolute minimum of artificial coloration.




Experimental Music Studio of the University of Illinois. Dr. Hiller (seated) writes about the AR-3's, used as monitor speakers: "I wish all our equipment were as trouble free."

AR speakers and turntables are often used professionally, but they are primarily designed for natural reproduction of music in the home. Literature is available for the asking.

**ACOUSTIC RESEARCH, INC., 24 Thorndike Street, Cambridge, Massachusetts 02141**  
Circle 9 on reader's service card

DECEMBER, 1965

# 3 WAYS TO BIGGER

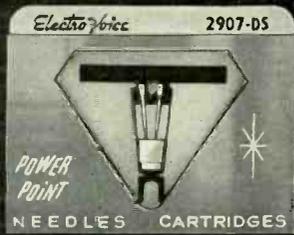

## NEEDLE




## CARTRIDGE PROFITS!

1. More "look-alike" exact replacement models than any other brand. Over 350 needles, 225 cartridges.
2. Easy-to-use reference material. E-V computer-printed catalogs make proper needle/cartridge selection easy, fast and accurate.
3. Highest standards. Rigid quality control and inspection cuts call-backs, gives full value to every customer.

Stock and sell E-V needles and cartridges for more profits. Pick up your FREE replacement guide at your nearby Electro-Voice distributor today!

**ELECTRO-VOICE, INC.**  
Dept. 1257E, Buchanan, Michigan 49107

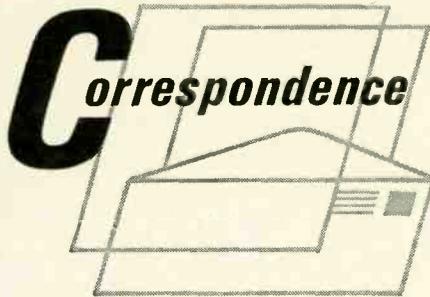**Electro-Voice®**  
SETTING NEW STANDARDS IN SOUND



### WRONG-WAY DIODE

Dear Editor:

I believe that in the Motorola MC1524 circuit (New Semiconductors and Tubes, Sept. 1965), the diode connected to ground from the base of the transistor with the 20,000-ohm emitter load is in backward. As it is, the diode is reverse-biased and thus isolates the transistor from the rest of the circuit. Hence there can be no transistor action.

GARY LORENZ

Compton, Calif.

[He's right.—Editor]

### ECHOES EDITORIAL SENTIMENTS

Dear Editor:

The editorial by Fred Shunaman in the September 1965 issue ("End of the Service Technician?") was of very special interest to me, the subject of the editorial fitting my own situation: a "dropout" from the radio-TV field. I am now in industrial electronics. After 9 years in that, I would welcome the company of more electronic technicians of the sort that (to quote Mr. Shunaman) "at least tries to understand what he is doing." I have encountered innumerable responsible people who erroneously blame faulty operation of systems on equipment (namely electronic) that they do not understand. They, pretending to understand, would make adjustments to such equipment, including combustion controls, without considering the possible drastic consequences. In agreement with Mr. Shunaman's statement "I will not touch adjustments on illuminating-

### BUILD THIS VIDEO MODULATOR

It takes the signal from any TV camera and puts it on your TV set—on any channel! Use it for closed-circuit, educational TV, for home fun, amateur TV, and experiments. Crystal oscillator keeps it tuned perfectly.

Coming in January  
**RADIO-ELECTRONICS,**  
the 3rd Annual Color-TV issue

gas equipment . . .", I would add: ". . . until I understand fully the operation of the complete system."

MYRLE DEPPE

Selinsgrove, Pa.

### RESEARCH ON SHOCK DANGER

Dear Editor:

I agree wholeheartedly with reader Piette's statement ("Watch Where You Stimulate!", Correspondence, August 1965) that the probes [of my Muscle Stimulator described in June R-E] should not be used in the chest area or in any way that might cause current to flow through the heart. I also would not advocate placing the probes at one's temples in an effort to induce sleep or electronarcosis. This is dangerous ground for the uninitiated.

I have conducted a brief literature search on the topic of shock. Here is a table from an article in the January 1960 *Electrical Manufacturing* by Edwin Schechter:

#### The Effects of 60-cycle Alternating Current on the Human Body

1 ma	No sensation
More than 5 ma	Painful shock
More than 10 ma	Local muscle contraction sufficient to cause freezing to the circuit in 2.5% of population
More than 15 ma	Ditto, 50% of population
More than 30 ma	Breathing difficult; can cause unconsciousness
50 to 100 ma	Possible ventricular fibrillation
.01 to 2 or 3 ampere	Certain ventricular fibrillation

Another source, *Electrical Safety* by H. W. Swan, states that an adult male can let go of a 60-cycle circuit as long as the current is 9 ma or less. Women have a lower limit: 6 ma. The "danger zone" given is 20 to 24 ma.

So Mr. Piette's figure of 5 ma for "complete muscle control" seems small; but my unit's 150 volts across 2,000 ohms is 75 ma, and that's enough to warn everyone to be very careful.

SAM BRESKEND


Washington, D. C.

### HONEYCOMB COILS

Dear Editor:

I thought you might be interested to know that recently I dug up some old De Forest honeycomb inductances, and, using one tube, I managed to breadboard a set and pick up a lot of stations around 10 to 20 kc (NAA, NSB and many

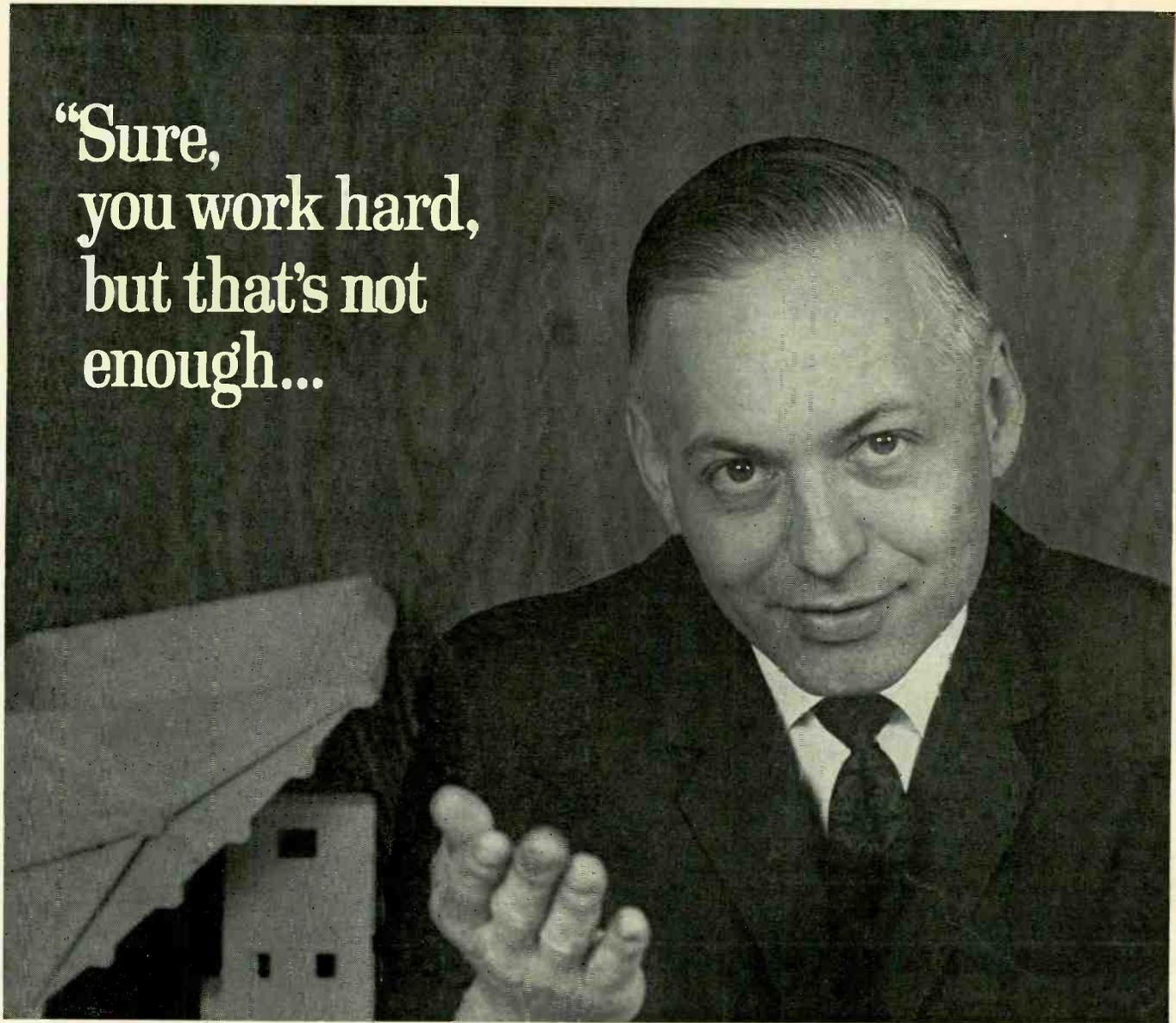“Sure,  
you work hard,  
but that’s not  
enough...”



...you need more education to get ahead in electronics”

No matter how hard you work, you can't really succeed in electronics without advanced, specialized technical knowledge.

Going back to school isn't easy for a man with a full-time job and family obligations. But CREI Home Study Programs make it possible for you to get the additional education you need without attending classes. You study at home, at your own pace, on your own schedule.

CREI Programs cover all important areas of electronics including communications, servomechanisms, even spacecraft tracking and control. You're sure to find a program that fits your career objectives.

You're eligible for a CREI Program if you have a high school education and work in electronics. Our FREE book gives all the facts. Mail coupon or write: CREI, Dept. 1412C 3224 Sixteenth Street, N.W., Washington, D. C. 20010

**SEND FOR FREE BOOK**



**The Capitol Radio Engineering Institute**  
Dept. 1412C 3224 Sixteenth Street, N.W.  
Washington, D.C. 20010

Please send me FREE book describing CREI Programs in Electronics and Nuclear Engineering Technology. I am employed in electronics and have a high school education.

Name \_\_\_\_\_ Year Born \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

Employed by \_\_\_\_\_

Type of Present Work \_\_\_\_\_

Accredited Member of the National Home Study Council



others). The reception was fine and the news reports being sent were the best. The code sending was very good and in a few minutes I was doing pretty good, after a lapse of many years.

LEROY H. SMELTZER

Greensburg, Pa.

#### UNIUNCTION TO DRIVE DEMO CIRCUITS

Dear Editor:

R. E. Baird's "Look Inside an Amplifier" (August 1965) can be a real asset in helping "see" dynamic circuit variations. There is no question that the

person who can visualize several complex circuit variations at one instant will be more confident and successful in electronics than one who cannot. Practical demonstrations, as suggested by Mr. Baird, can certainly be helpful during course work.

A simple and economical method to drive such an active demonstration is with the basic unijunction relaxation oscillator. This oscillator is unusually simple, requires few components and will perform at low supply voltages. Sweep rates to a fraction of a second are easily obtained. The unijunction is presented

in Chapter 13 of the seventh edition of General Electric's Transistor Manual.

JOHN F. CLEARY

General Electric Co.  
Syracuse, N.Y.

#### TACHOMETERS MAKE HARD STARTING

Dear Editor:

I have found after constructing and installing several kinds of electronic tachometers that they cause hard starting when the engine is cold.

I went through a long round of troubleshooting and replacement (coil, condenser, carburetor, points) before I decided that the hard starting is due to the fact that a vital but little known function of the capacitor (condenser) across the points is hindered by the low input resistance of the tachometer circuits.

It is common knowledge that one purpose of the capacitor is to prevent arcing across the breaker points when the coil primary circuit is suddenly opened. But another function of the capacitor is often overlooked.

The coil primary is energized by the battery when the breaker points close. When the points break the circuit, the current tends to continue in the same direction, and the stored magnetic energy in the core starts to collapse. The flux cuts primary and secondary windings. The faster the flux can be brought to zero (i.e., the greater its rate of change), the higher will be the voltage induced in the secondary.

With the points now open, the capacitor, which had been shorted (directly across the closed points), now acts itself as a short circuit for an instant as it becomes charged by the current created in the primary by the collapsing field. It thus aids in bringing the induced current rapidly to zero. If the capacitance is correct, it will discharge through the battery and the coil before the points close again.

The reverse flow of energy stored in the capacitor "purges" the coil of flux so there will be no counter-emf to oppose the flow of current from the battery when the points close again. This cycle repeats itself as long as the engine runs.

**Any resistance across the breaker points (and hence across the capacitor) reduces the effectiveness of the capacitor and impairs the function of the whole ignition system.**

I am eager to hear other views on this subject.

L. E. MUELLER

Philadelphia, Pa.

END


RECEIVE FREE literature and catalogs by mailing Readers' Service Card, page 70.



...IT'S THE FINEST

## Color Keyed

# Model 825 Picture Tube Tester/Booster

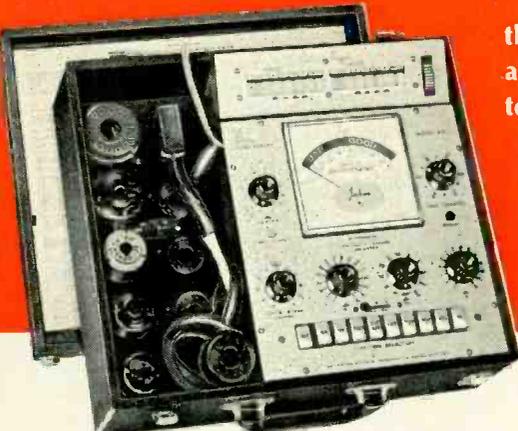

the most versatile and accurate of all CRT testers...for all

### BLACK/WHITE and COLOR PICTURE TUBES...

**look** at all the valuable and profitable functions

- Tests for continuity, leakage, emission, picture tube cut-off and life-expectancy
- Removes shorts
- Welds cathode
- Boosts picture tube back to life

---

**look** at these brilliantly engineered Jackson features

- 12 separate heater voltages including color
- Line indicator control for accurate voltages
- Grid guard limits peak current for protection of picture tube
- Checks each color gun separately
- Plug-in socket cable for easy replacement or repair
- Separate variable voltages applied to G1-G2 of picture tube

---

**look** at all these convenient operational features

- Color keyed—push buttons for ease and speed in testing
- FM tuning eye...no separate lights to interpolate
- Angled view roll chart on panel...tube set-up information at your fingertips
- Easy to keep up-dated

Size: 14<sup>3</sup>/<sub>4</sub>" W x 13<sup>1</sup>/<sub>2</sub>" D x 5<sup>3</sup>/<sub>4</sub>" H.  
Wt.: 13 lbs. 3 oz. Dealer Net **\$11995**

See your Jackson distributor, or write for catalog

## JACKSON ELECTRICAL INSTRUMENT COMPANY

124 McDonough Street, Dayton 2, Ohio

In Canada: William Cohen Corp. Export: Morhan Exporting Corporation.  
458 Broadway, New York 13, N.Y.

IF IT'S A JACKSON...IT'S THE FINEST

Circle 12 on reader's service card

# Use this check list before you install a home TV distribution system

	COAXIAL VHF	TWINLEAD* VHF	COAXIAL UHF/VHF	TWINLEAD* UHF/VHF AND UHF ONLY
Channels received	2-13	2-13	2-83	2-83 (14-83 for UHF only)
Color reception when properly installed	Excellent	Excellent	Excellent	Excellent
Cable loss: @ channel 13 for VHF only @ channel 83 for UHF/VHF	4 db (foam filled) 6 db (solid)	1.8 db/100 ft. @ Channel 13	9 db (foam filled) 13 db (solid)	5.6 db/100 ft. @ Channel 83
Loss increase when wet	Nil	Negligible	Nil	Negligible
Reception when run near or through small metal areas	Excellent	Excellent when properly installed	Excellent	Excellent when properly installed
Reception when run near or through considerable amounts of metal	Excellent	Not recommended	Excellent	Not recommended
Ease of installation	More difficult	Easy	More difficult	Easy
Extra parts required	Connectors, matching transformers	None	Connectors, matching transformers	None
Performance in strong-signal areas	Excellent	Excellent—fair**	Excellent	Excellent—fair**
Performance in weak-signal areas	Excellent	Excellent	Excellent	Excellent
Cable pickup of interference (ignition, appliances, etc.)	None***	None—slight**	None***	None—slight**

\*A high quality, low-loss foam encapsulated cable type \*\*Depends upon local conditions \*\*\*Poorly designed accessories will pickup interference.

Once you know the facts—there is one best choice for your home system—Blonder-Tongue. Whether you prefer 300 ohm or a 75 ohm coax system, Blonder-Tongue has the products you'll need. There is only one way you can protect your home TV system against obsolescence when new UHF stations come on the air—that's with a Blonder-Tongue all-channel UHF/VHF system.

Blonder-Tongue products designed for all-channel home systems include: All-channel signal amplifiers (V/U-All-2 indoor and U/Vamp-2 mast mounted); all-channel couplers (A-102-U/V two-set and A-104-UV four-set). Rounding out the all-channel concept are UHF/VHF matching transformers (Cablematch U/V set mounted; MT-283 mast-mounted) and the TF-331-U/V flush-mounted feed-thru.

Take your pick. Blonder-Tongue makes them all—and all are "Color Approved". Buy the line with 15 years of quality leadership. Write for free booklet "How to Plan a Color-Approved Home TV System".

## BLONDER-TONGUE


9 Alling Street, Newark, New Jersey 07102

home TV accessories • closed circuit TV •  
community TV • UHF converters • master TV

Circle 13 on reader's service card

# Complete TUNER REPAIR

## \$9.50

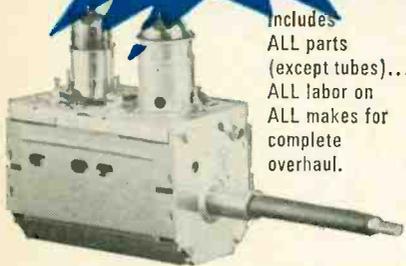

Includes  
ALL parts  
(except tubes)...  
ALL labor on  
ALL makes for  
complete  
overhaul.

**FAST, 24-HOUR SERVICE  
with FULL YEAR WARRANTY**

Sarkes Tarzian, Inc., largest manufacturer of TV and FM tuners, offers unexcelled tuner overhaul and factory-supervised repair service.

Tarzian-made tuners received one day will be repaired and shipped out the next. More time may be required on other makes. Every channel checked and realigned per original specs. And, you get a full, 12-month guarantee against defective workmanship and parts failure due to normal usage. Cost, including labor and parts (except tubes) is only \$9.50 and \$15 for UV combinations. Replacements at low cost are available on tuners beyond practical repair.

Always send TV make, chassis and Model number with faulty tuner. Check with your local distributor for Sarkes Tarzian replacement tuners, parts or repair service. Or, use the address nearest you for fast, factory-supervised repair service.

**SARKES  TARZIAN**

TUNER SERVICE DIVISION

537 S. Walnut St., Bloomington, Ind.

Tel: 812-332-6055

10654 Magnolia Blvd., N. Hollywood, Calif.

Tel: 213-769-2720

TUNER SERVICE  CORPORATION

(Factory-supervised tuner service  
authorized by Sarkes Tarzian, Inc.)

547 Tonnele Avenue, Jersey City, N.J.

Tel: 201-792-3730


**Manufacturers of Tuners, Semiconductors,  
Air Trimmers, FM Radios, AM-FM Radios,  
Audio Tape and Broadcast Equipment**

# SERVICE CLINIC

By **JACK DARR** Service Editor
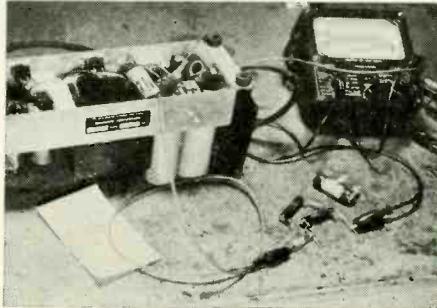
## Replacing Weak High-Current Seleniums

The Gulbransen Transistor Organ (and that's all it says on the label—no model number) uses transistor tone generators, and tubes for power amplifiers. The amplifier tubes and the power supply are on a small chassis in the upper right side of the cabinet, from the front. To get at it, and the "works", lift the upper manual, or take out the three big screws along the top of the back panel, and take the top off.



Checking load capability of a supply is merely a matter of hanging on various load resistors and watching what happens to current and voltage.

The trouble in this organ was in the stops. Any one would work, but when more than one was pushed, nothing. The stops (which select the different "voices" of the organ) are relay-operated, in an unusual way. Normal-looking relays are used, but instead of closing spring-blade contacts, each one pulls a string! The string causes a long, thin rod to turn 180°. Resting against the rod are very fine wire contacts. Half of the circumference of the rod is insulated; when it turns, the wires make contact with the bare half. There is a total of 14 such assemblies in this instrument.


This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge, and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. Don't forget to enclose a stamped, self-addressed envelope. Write: Service Editor, Radio-Electronics, 154 West 14th Street, New York 10011.

The relays weren't closing when more than one was used. The voltage fell badly when more than one was switched in. I bridged the big filter capacitors, just in case, but that wasn't it, so it had to be one of the big selenium rectifiers in the power supply.


I broke the circuit and inserted a dc milliammeter. Each relay drew 500 ma. So, the rectifier had to supply 7.0 amperes. Bench tests with various load resistors and an ammeter showed that the voltage dropped badly at about 2-3

Continued on page 20

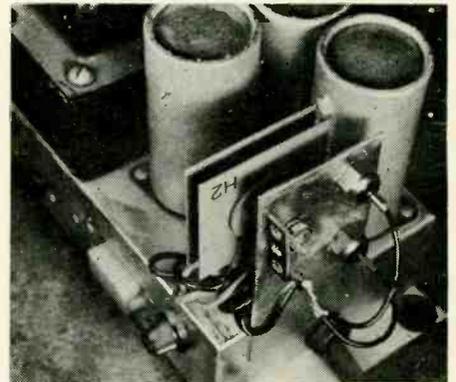

The new silicon rectifiers, mounted with insulating mica washers on a small aluminum plate as a heat sink.

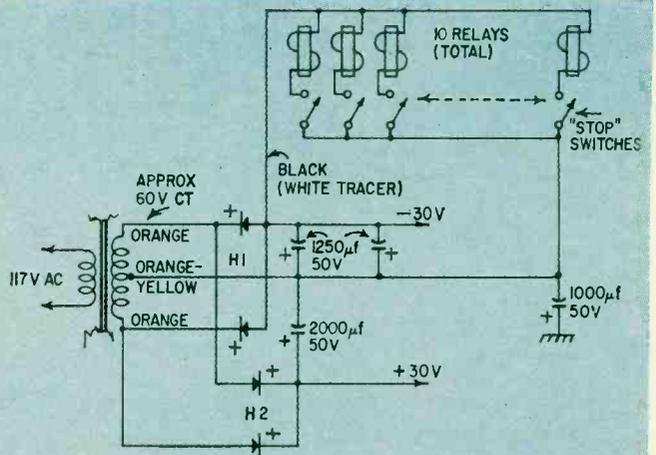Control power supply of Gulbransen electronic organ. Other electronic organs, especially large ones, have similar supplies.





# Hy-Gain's DX Roof Topper for Citizens Band

How many times every day, week or month do you find yourself back-tracking or heading for some distant hill so that you can get your mobile unit within range of your base station? Certainly a lot more times than would be necessary if your mobile unit was equipped with a Hy-Gain "DX Roof Topper". Hy-Gain "DX Roof Toppers" are a breed all their own. In fringe areas where signals are weak using other mobile antennas, signals on both transmit and receive are loud and clear with a "DX Roof Topper". As a matter of fact, with a "DX Roof Topper", you can maintain rock-solid communications with remote areas you never dreamed possible. For less back-tracking or heading for some distant hill to get within range of your base station...to save time, save gas...to get a whole new dimension in 2-way communications, get a Hy-Gain "DX Roof Topper". Guaranteed to out-perform any other mobile antenna for Citizens Band, or your money back. Comes complete with antenna, stainless steel shock spring, "can't leak" roof mount, 16' of coaxial cable with PL-259 connector and a special adapter plate for replacing any existing roof mount antenna. Model TQRDX . . . . . \$16.95 Net

**OTHER TOPPER MODELS**— Each one unconditionally guaranteed to out-perform any other CB mobile antenna of comparable length and mounting position:

- AM-CB Combination ■ Jiffy Trunk Mount
- Fender Mount ■ Shorty Roof Topper
- Cowl Mount ■ Marine Topper

**free** Mobile Antenna Comparison Report No. 15  
Available today from your Hy-Gain  
Distributor or Dealer or write...

**HY-GAIN ELECTRONICS CORPORATION**  
8560 N.E. Highway 6 • Lincoln, Nebraska 68501

# You get more for your money from NRI-

## America's oldest and largest Electronic, Radio-TV home-study school

Compare if you like. You'll find—as have so many thousands of others—that NRI training can't be beat. From the delivery of your first lessons in the remarkable, new Achievement Kit we send you, to "bite size," easily-read texts and carefully designed training equipment . . . NRI gives you more value.

Shown below is a dramatic, pictorial example of all of the training materials included in just one NRI Course. *Everything* you see pictured below is included in low-cost NRI training. Other major NRI courses are equally complete. Text for text, kit for kit, dollar for dollar—your best home-study buy is NRI.



## GET A FASTER START WITH NRI'S NEW EXCLUSIVE ACHIEVEMENT KIT

The day we receive your enrollment application we mail out your Achievement Kit. It contains everything you need to make an easy, fast start in the Electronics training of your choice. This attractive, new starter kit is an outstanding, logical way to introduce you to home-study as NRI teaches it . . . an unparalleled example of the value of NRI training . . . training that is backed up by a dedicated staff and the personal attention you should expect of a home-study school. It is your first of a number of special training aids carefully developed by the NRI laboratories to make your adventure into Electronics absorbing, meaningful. What's in the Achievement Kit? Your first group of lesson texts; a rich vinyl desk folder to hold your study material; the industry's most complete Radio-TV Electronics Dictionary; valuable reference texts; lesson answer sheets; pre-addressed envelopes; pencils; pen; engineer's ruler—even postage. No other school has anything like the NRI Achievement Kit.


## LEARNING BECOMES AN ABSORBING ADVENTURE WITH NRI TRAINING KITS

Electronics comes alive with NRI training kits. What better way to learn than by doing it? That's why NRI pioneered and perfected the "home lab" technique of learning at home in your spare time. You get your hands on actual parts and use them to build, experiment, explore, discover. NRI invites comparison with training equipment offered by any other school. Begin NOW this exciting program of practical learning. It's the best way to understand the skills of the finest technicians—and make their techniques your own. Whatever your reason for wanting to increase your knowledge of Electronics . . . whatever your field of interest . . . whatever your education . . . there's an NRI instruction plan to fit your needs, at low tuition rates to fit your budget. Get all the facts about NRI training plans, NRI training equipment. Fill in and mail the attached postage-free card today. No salesman will call. NATIONAL RADIO INSTITUTE, Washington, D.C. 20016.

OUR 50th YEAR OF LEADERSHIP




IN ELECTRONICS TRAINING

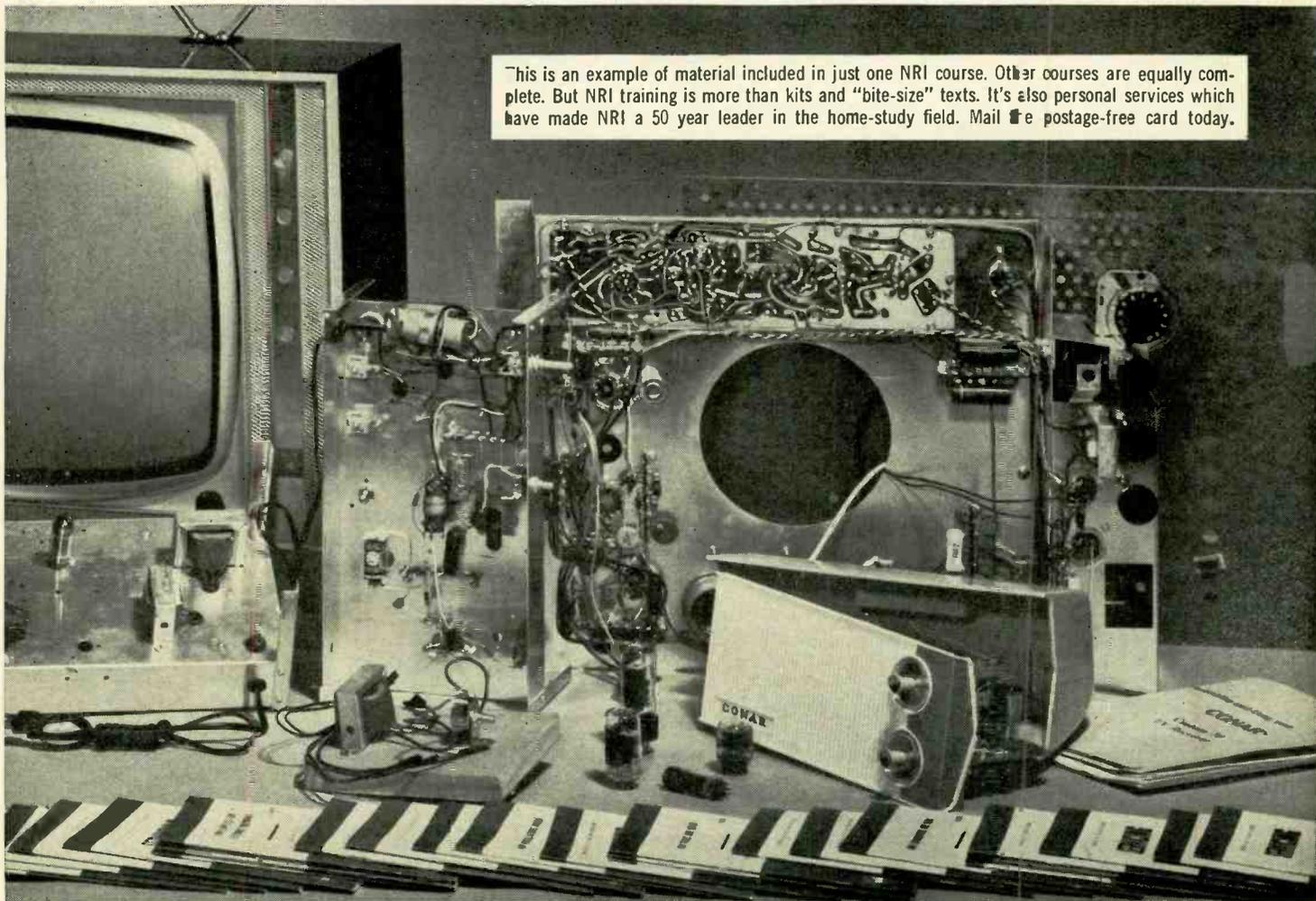

This is an example of material included in just one NRI course. Other courses are equally complete. But NRI training is more than kits and "bite-size" texts. It's also personal services which have made NRI a 50 year leader in the home-study field. Mail the postage-free card today.
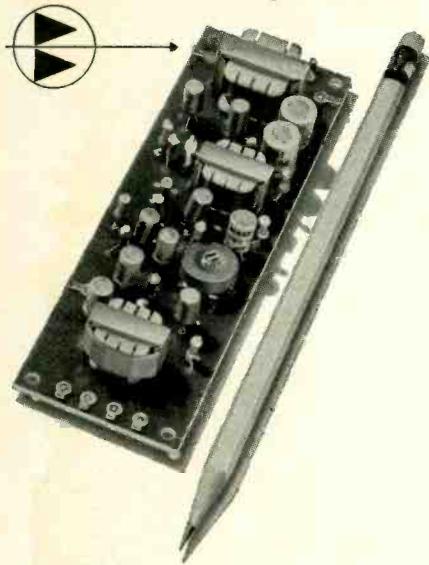
# Birnbach's Compact Transistor Audio Amplifier



Look at these amazing features . . .

- ★ 5 Transistors and 1 Thermistor
- ★ Shielded Input Transformer with 2 PRIMARY WINDINGS . . . 50 ohms and High Impedance
- ★ Output Transformer with 2 SECONDARY WINDINGS . . . 8 ohms (for speakers), 500 ohms (for modulation and high impedance loads)
- ★ Volume Control included and mounted on Circuit Board
- ★ Low Distortion . . . 400 Milliwatt Push-Pull Output
- ★ Extremely high gain . . . 80 db! Handles low level mikes, phono pickups, telephone pickups, etc.
- ★ Sturdy Printed Circuit Board is 5½" long by 1¾" wide
- ★ Weighs only 3½ ounces
- ★ Power Supply: Any 9-volt DC source
- ★ Standard 90 day warranty

## USE IT FOR:

PA System  
Hi-Fi System (use 2 for stereo)  
Guitar Amplifier  
Surveillance Listening System  
Electronic Stethoscope  
Intercom Amplifier  
Modulation for Transmitter  
Phono Amplifier  
Utility Amplifier  
Science Projects

**COMPLETE AMPLIFIER \$7.95** each

INCLUDING SCHEMATIC DIAGRAM We Pay Postage!

**BIRNBACH** Radio Co., Inc.  
Dept. R, 435 Hudson St., New York, N.Y. 10014

Please rush me \_\_\_\_\_ (qty) of your Compact Transistor Audio Amplifiers Model A-300 at \$7.95 each, postpaid. My check or money order for \$\_\_\_\_\_ is enclosed. Sorry, no COD's.

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

## SERVICE CLINIC continued

amps. So, new rectifier needed. Big seleniums are hard to find. I used a pair of stud-mounted silicons, rated at 10 amps each.


One of the photos shows the mounting of the replacements. The original mounting hole was enlarged and another one drilled; the studs of the silicons (the cathodes) had to be insulated; mica washers come with them. One terminal strip was added, to hold the common negative connection securely.

One final word: if you make load tests with resistors on a new high-current hookup, *don't* pick up the resistors with your bare hands! They get HOT!
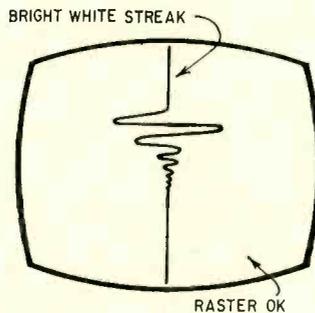
## A very short Christmas tree

*I've got one I don't understand. It's a Motorola TS-579B. It gets a flashing white streak down the middle of the picture (Fig. 1) and there are flashes and pops. Tuner seems to affect this on channels 2 and 6, which are unused. With a strong signal, it flashes only once in a while. Everything else is OK—brightness, contrast, etc. This has been going on for some time.—D. D., Glendive, Mont.*

This is actually a "very short Christmas tree" (one that was picked too young?). In other words, your horizontal output (oscillator-damper-output tube-HV-rectifier-yoke)—something in there—is cutting in and out very rapidly! If you had a few more streaks, you'd see the regular Christmas-tree pattern.



This could be in any one of the major parts of the horizontal output stage, as listed above. About the fastest way to run it down is to substitute for various sections.

Lift the plate cap from the 6DQ6 horizontal output tube and feed in a "plate-drive" signal from a horizontal sweep tester or from another TV set in good working order. Connect the plate of its horizontal output tube to the plate lead on the Motorola flyback. (*Don't* use an ac/dc TV for this!) Now, turn 'em both on, and see if this cures the flashing. If so, the trouble is *before* this point, in the horizontal oscillator, afc, etc.

If the flashing is still there, then it's in the flyback, yoke or damper circuits of the Motorola. Go over these very carefully, looking for a loose solder joint or small arcover point. You've probably done this already, but replace the damper tube; it's a common cause of such troubles, via internal arcing between plate and cathode or heater and cathode. Take an insulated tool and work over the various connections around this circuit. Poke, pry and jar things, looking for one that'll cause the streak to show up. Don't overlook the socket connections on the damper tube, etc. Be sure they're clean and tight.

The high-voltage rectifier doesn't cause too much of this particular kind of trouble (you're losing horizontal sweep: note the pattern!) but check it in the same way. Shouldn't take too long to find the cause, especially if you use a logical process of elimination and substitute various drive signals from another set. Good luck!

## Another mystery set

*The owner says this is an RCA TV set. The only numbers I can see are 'K66132' Uses two 5U4's; the power transformer has "ET101B" on it. Can you tell me anything about this set?—E. H., Winchester, Va.*

I can tell you one thing: it isn't an RCA! From the numbers, it is most apt to be a "Mattison" (Macy's, Mirror-tone, Artone, etc.) Many of these were made by Hallicrafters for different mail-order houses.

Get a catalogue from one of the transformer makers: Triad, Merit, Stancor, etc., and go through the set, looking up part numbers on the major parts like power transformer, vertical output transformer, and so on. In this way, you can often match up numbers and find out what the set is.

## "Open" meter in vom?

*My vom suddenly quit working. I opened the case and checked the meter movement itself. It seems all right. It's one of the printed-circuit-board types. Do you think this is a PC board break, or what?—F. D., Yuma, Ariz.*

Suggestion, from an experience I had once: loosen the mounting nuts on the meter terminals, which hold the PC board in this instrument. Clean these connections and retighten, and see if the vom doesn't work fine again. These instruments are moistureproofed by varnishing, and once in a while this varnish gets between the terminals.

If this doesn't work, disconnect the meter movement and, with another vom, check back from the meter terminals to the ohmmeter jacks. This will give you an idea of where a possible open circuit could be: bad switch contacts, etc. END

**FREE**

with your purchase of a **PHOTOFACT**® Library...


★  
sells at retail for  
**\$149.50**

now yours

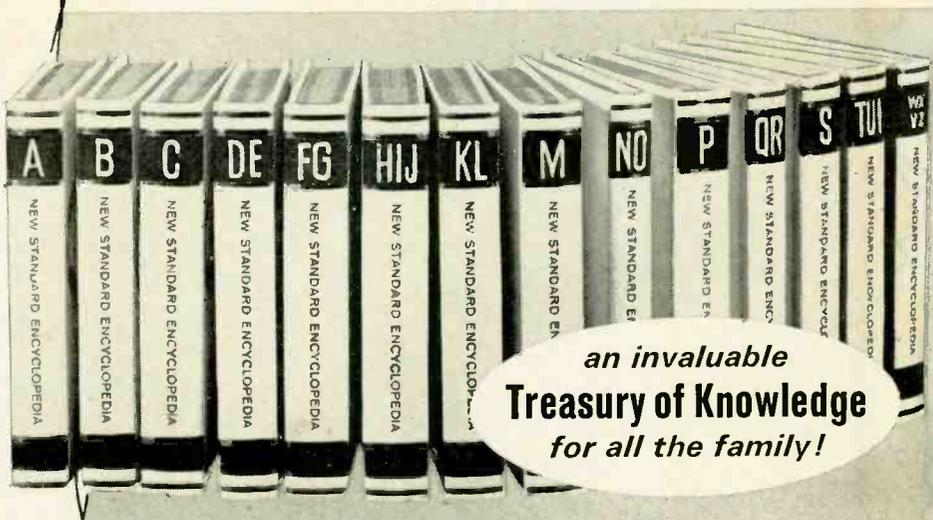**FREE**

with the purchase of a Photofact Library consisting of 225 Sets or more... **ACT NOW**—get the Encyclopedia in time for your family Christmas!

the supreme *Christmas Gift* for your family...the famous 14-volume **NEW STANDARD ENCYCLOPEDIA!**



an invaluable **Treasury of Knowledge** for all the family!

give your family this wonderful gift—  
give your earning power a big boost with **PHOTOFACT**—world's finest TV-radio service data

Now, more than ever, it pays to own a PHOTOFACT Library—the time-saving, troubleshooting partner guaranteed to help you earn more daily. Now, you can start or complete your PHOTOFACT Library the special Easy-Buy way, and get absolutely FREE with your purchase, the famous 14-volume NEW STANDARD ENCYCLOPEDIA. It's a great reference library for all the family—complete, authoritative, indispensable. Retail for \$149.50—yours absolutely FREE with the purchase of a PHOTOFACT Library consisting of 225 Sets or more!

**THERE ARE 4 CONVENIENT WAYS TO SELECT YOUR PHOTOFACT LIBRARY**

1. Complete your present PHOTOFACT Library.
2. Order a PHOTOFACT "Starter" Library—225 Sets (Sets 451-675—coverage from 1959 to 1964—only \$14.29 per month).
3. Order by brand name and year—see the handy selection chart at your distributor.
4. Order a complete PHOTOFACT Library—and the famous 14-Volume New Standard Encyclopedia is yours FREE!



**ORDER YOUR PHOTOFACT LIBRARY NOW—AND GET YOUR FREE STANDARD ENCYCLOPEDIA**

See your Distributor for the full details of the PHOTOFACT-Encyclopedia Deal, or send coupon at right! Also ask about a Standing Order Subscription to current PHOTOFACT and Specialized Service Series (FREE File Cabinets available with Subscriptions). **ACT NOW!**

**SEE YOUR DISTRIBUTOR OR SEND COUPON TODAY**

Circle 18 on reader's service card

**OWN A PHOTOFACT LIBRARY THE EASY-BUY WAY:**

- Only \$10 down • 30 months to pay
- No interest or carrying charges • Prepaid transportation
- Add-on privilege of a year's advance subscription to current Photofact data, on the same Easy-Buy contract
- Save 30¢ per Set—special \$1.95 price applies on Easy-Buy (instead of regular \$2.25 price)

**THERE'S NEVER BEEN A DEAL TO EQUAL THIS!**

**GET THE DETAILS NOW**

**HOWARD W. SAMS & CO., INC.**

Howard W. Sams & Co., Inc., Dept. REF-12  
4300 W. 62nd St., Indianapolis, Ind. 46206

Send full information on the PHOTOFACT Library-Encyclopedia Deal, and details of the Easy-Buy Plan

My Distributor is: \_\_\_\_\_

Shop Name \_\_\_\_\_

Attn. \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_





with  
rear  
seat
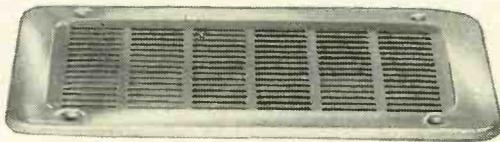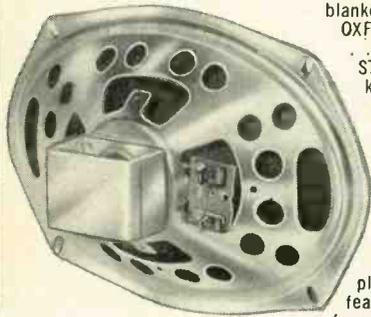
## OXFORD Transducer AUTO SPEAKER KITS

Now, one great line . . . OXFORD TRANSDUCER . . . gives you blanket coverage of the auto rear seat speaker kit field. OXFORD gives you three separate price and value levels . . . the CUSTOM line . . . the DELUXE line and the STANDARD line. In all, there are 11 different speaker kits to choose from.

All kits are designed and engineered to the highest performance standards, to give top satisfaction to you and your customer. Alnico V magnets, and oversize gap clearances, compatible to original automotive equipment used throughout the entire line. Easy to install, no soldering; solderless connectors used on all speakers. Top quality switches and faders throughout the entire line. Wiring harnesses are completely assembled and heavy gauge plastic coated wire are but two of the extra quality features of the entire line. Switches and controls are both fungus and moisture resistant for longer life and trouble-free operation. Complete with all necessary hardware.



Get the complete story on the OXFORD TRANSDUCER line of 11 different auto rear seat speaker kits . . . and "BLANKET THE MARKET". Write for Catalog A-105:



### OXFORD TRANSDUCER COMPANY

Division of OXFORD ELECTRIC CORPORATION

3911 South Michigan Avenue  
Chicago, Ill. 60653

Circle 19 on reader's service card

## NEW...POSITIVELY NEW

**Positively—**

- CONTAINS NO CARBON TETRACHLORIDE
- HARMLESS TO ANY PLASTICS KNOWN TO KRYLON
- CLEANS AS IT LUBRICATES
- NON-FLAMMABLE
- NON-CORROSIVE . . . NON-TOXIC

Contact your local jobber for Tuner Cleaner and other everyday Krylon aerosol products—Crystal Clear, Let-Go (oil penetrant), Red Insulating Varnish, Silicone Lubricant, Cleaner and Degreaser

If you prize it...KRYLON-ize it!®




## OUR STANDARD ABBREVIATIONS


RADIO-ELECTRONICS has always tried to maintain a consistent style in the abbreviations used in text and artwork (diagrams and photo "callouts"). New abbreviations are developed as new terms are added to our electronic vocabulary. We are printing this revised list of abbreviations to bring our old readers up to date and to help readers who have not been with us long enough to recognize the forms consistently used in our magazine.

The abbreviations are indexed by symbol with Greek letters treated like English phonetic equivalents. Many of those listed are always spelled out in the text and are abbreviated in our artwork. Terms used only in artwork—and those capitalized in text—appear in capitals. Abbreviations in lower-case letters are so used in text and are capitalized in artwork. Periods are used in abbreviations only where the abbreviation might be confused with a word. For example, rf and i.f. are our abbreviations for radio frequency and intermediate frequency, respectively.

ABBREVIATION	ELECTRONIC TERM
A	ampere(s)
ac	alternating current
acc	automatic chroma control
ADJ	adjacent, adjustment
af	audio frequency
afc	automatic frequency control
AFT	audio-frequency transformer
agc	automatic gain control
AM	amplitude modulation
amp	ampere(s)
AMPL	amplifier
ANT	antenna
apc	automatic phase control
ATTEN	attenuator
AUTOTRANS	autotransformer
avc	automatic volume control
AWG	American wire gage
b or base	base (of transistors)
BAL MOD	balanced modulator
BALUN	balanced-to-unbalanced transformer
BATT	battery
BCI	broadcast interference
bfo	beat frequency oscillator
BO	Barkhausen oscillation
BTO	blocking-tube oscillator
c	collector (of transistors)
C, CAP	capacitor (capacitance)
CALIB	calibrate
cath (K on tube diagrams)	cathode
CATH FOLL	cathode follower
CATV	community-antenna television
CB	Citizens band
CCTV	closed-circuit TV
CENT	centering
CH	choke
CHAN	channel
CHG	charge
CKT	circuit
CKT BKR	circuit breaker
coax	coaxial
COM	common
COND	conductor
CONN	connector, connection
CONT	control
CONV	convergence, converter
counter emf	counter electromotive force
C-R	cathode-ray (tube, etc.)
CRO	cathode-ray oscilloscope
CRT	cathode-ray tube
CT	center tap

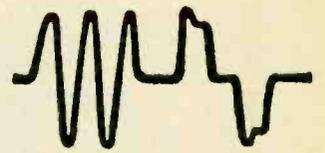

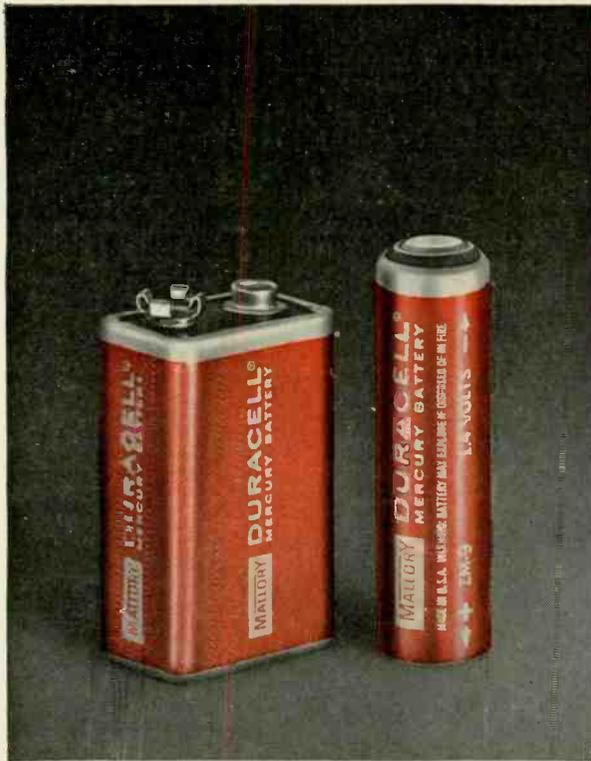
## Why New Duracell® Mercury Batteries last even longer in transistor radios



The best way to explain why mercury batteries are *better* is to compare a typical transistor radio with a standard 2 cell flashlight. The vast majority of flashlights use zinc-carbon batteries. The bulb draws about  $\frac{1}{2}$  ampere. And the flashlight is used only a minute or two at a time. Therefore the zinc-carbon battery does a reasonably adequate job.


But a typical transistor radio draws only 10 *milliamperes* . . . (the flashlight draws *50 times* as much current). And the radio is used for hours on end. What's needed here is a battery which supplies power in small doses over a very long period of time. There *is* such a battery and it was invented by Mallory. Over the years, it has been improved so much we've given it a new name . . . the DURACELL Mercury Battery. The DURACELL crams *more useable power* into *less volume* than *any other battery system* available. Strangely enough, you'd expect to pay more, but it is actually more economical.

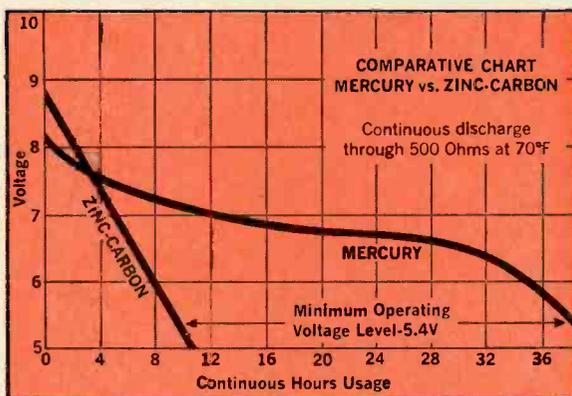Want proof? Okay, the new TR146X is the 9 volt size that fits most transistor radios. It will run a typical transistor radio at *least* 37 hours. The zinc-carbon equivalent goes for only 9 hours, or less than  $\frac{1}{4}$  as long. (We're talking about top-quality domestic zinc-carbon's here . . . not cheap imports with *very* short life.)



What does this mean to the pocketbook? The zinc-carbon costs 69c while the TR146X \$1.95 . . . but don't let that fool you. Divide 69c by 9 and you'll see that it costs you 7.67c per hour to use the zinc-carbon. Now divide \$1.95 by 37 and you'll see that it comes to only 5.27c! That's a bargain! In the penlight size, the ZM9 DURACELL gives 4.8 times more *life* for only 3.8 times more money . . . another bargain.

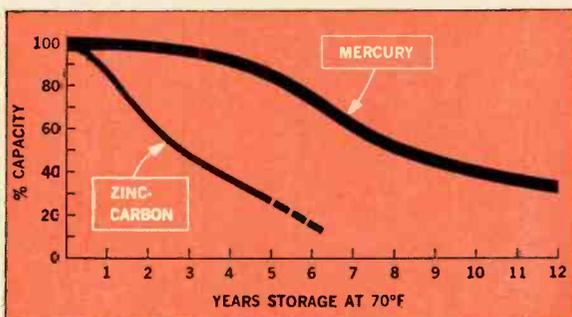Forget the money! Think of performance. Mercury battery voltage stays *constant* while the zinc-carbon fades fast. This means that B+ voltage stays where it belongs for *days longer* rather than dropping into the distortion range.



Forget the money! Forget the performance! Think of storage life. Zinc-carbon batteries die in a few months *whether they are used* or not. Mercury batteries can sit around for 2 or 3 *years* and still provide instant power.

There's more, too . . . *dependability*. The same dependability and safety that makes the heart pacer possible.

If you need *more proof*, try a new DURACELL Mercury Battery in *your* radio or any electronic gadget . . . you can get 'em at your Mallory Distributor. Mallory Distributor Products Company, a division of P. R. Mallory & Co. Inc., Indianapolis, Indiana 46206.

Circle 21 on reader's service card

# ASSEMBLE YOUR OWN ALL-TRANSISTOR *Schober* ELECTRONIC ORGAN



3 NEW MODELS  
Recital \$1500  
Console II \$850  
Spinet \$550

This is the all-new, all-transistor Schober

Recital Model...the most versatile electronic organ available today. Its 32 voices (plus amazing "Library of Stops"), 6 couplers and 5 pitch registers delight professional musicians...make learning easy for beginners. Comparable to ready-built organs selling from \$5000 to \$6000.

The pride and satisfaction of building one of these most pipe-like of electronic organs can now be yours...starting for as low as \$550. The Schober Spinet, only 39 1/4 inches wide, fits into the smallest living room. The new, all-transistor Schober Console II is the aristocrat of "home-size" organs...with two full 61-note manuals, 17 pedals, 22 stops and coupler, 3 pitch registers and authentic theatre voicing.

AND YOU SAVE 50% OR MORE BECAUSE YOU'RE BUYING DIRECTLY FROM THE MANUFACTURER AND PAYING ONLY FOR THE PARTS, NOT COSTLY LABOR.

It's easy to assemble a Schober Organ. No special skills or experience needed. No technical or musical knowledge either. Everything you need is furnished, including the know-how. You supply only simple hand tools and the time.

You can buy the organ section by section...so you needn't spend the whole amount at once.

You can begin playing in an hour, even if you've never played before—with the ingenious Pointer System, available from Schober.

Thousands of men and women—teenagers, too—have already assembled Schober Organs. We're proud to say that many who could afford to buy any organ have chosen Schober because they preferred it musically.

Send for our free Schober Booklet, describing in detail the exciting Schober Organs and optional accessories; it includes a free 7-inch "sampler" record so you can hear before you buy.

## THE Schober Organ CORPORATION

43 West 61st Street, New York, N.Y. 10023

Also available in Canada, Australia, Hong Kong, Mexico, Puerto Rico, and the United Kingdom

THE SCHOBER ORGAN CORP., DEPT. RE-40  
43 West 61st Street, New York, N.Y. 10023

Please send me FREE Schober Booklet and free 7-inch "sampler" record.

Enclosed find \$2.00 for 10-inch quality LP record of Schober Organ music. (\$2.00 refunded with purchase of first kit.)

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip No. \_\_\_\_\_

Circle 22 on reader's service card

CW	continuous wave	NE	neon
D	diode	NEG	negative
db	decibel	NET	network
dc	direct current	N.O.	normally open (switch or relay)
dcc	double cotton covered (wire)	NP	nonpolarized (electrolytic capacitor)
DC REST	direct current restorer	n-p-n	negative-positive-negative (transistors)
DEFL	deflection	OF	oil-filled (capacitor)
DEM0D	demodulator	OSC	oscillator
DET	detector	P	plate, plug
df	direction finder	PA	public address
DIELEC	dielectric	PC	photocell
DIFF	differentiator	PERM	permanent
DISCH	discharge	pf	picofarad ( $\mu\mu\text{f}$ )
DISCRIM	discriminator	phone(s)	telephone, headphones
dpdt	double pole double throw	PHOTO MULT	photomultiplier
dpst	double pole single throw	pix	picture (TV)
dsc	double silk covered (wire)	PL	pilot lamp
DYN	dynamic	PM	permanent magnet (speaker)
dx	distance	PM	phase modulation
e	emitter (of transistors)	p-n-p	positive-negative-positive (transistors)
E	potential	POS	positive
E (sometimes V in transistor diagrams)	voltage	POT	potentiometer
ECO	electron-coupled oscillator	PP	peak-to-peak
ELEC	electric; electrolytic	PPI	plan-position indicator (radar)
ELECT	electrode	pps	pulses per second
emf	electromotive force	preamp	preamplifier
ENAM	enameled (wire)	prf	pulse repetition frequency
EQUIV	equivalent	PRI	primary
ERASE HD	erase head	PT	phototube
ERP	effective radiated power	Q	reactance-resistance ratio
EXT	external or extension	Q	transistor
F (f as suffix)	farad(s)	QUAD	quadrature
f, FREQ	frequency	R	resistance (resistor)
FET	field-effect transistor	RCDG	recording
FIL (F in tube diagrams)	filament	RCDR	recorder
FM	frequency modulation	RECT	rectifier
FOLL	follower (-ing)	REG	regulator
g	giga- (one billion)	regen	regeneration
G (in tube diagrams)	grid	rf	radio frequency
GCA	ground controlled approach	RFC	radio-frequency choke
GDO	grid dip oscillator	RFI	radio-frequency interference
GEN	generator	RFT	radio-frequency transformer
GND	ground	rms	root mean square
h	henry (-ies)	RY	relay
HD	head	S	switch
hf	high frequency	SCA	subsidiary communications authorization
HORIZ	horizontal	sec	single cotton covered (wire)
HTR (H)	heater	SCR	silicon controlled rectifier
I	current	sec	second
IC	internal connection (on tubes)	SEL (RECT)	selenium (rectifier)
i.f.	intermediate frequency	SEP	separator
IFT	intermediate frequency transformer	SG	screen grid
ILS	instrument landing system	SIG	signal
IM	intermodulation	SIL or Si (RECT)	silicon (rectifier)
INT	integrator	SLD	solenoid
INV	inverter	spdt	single pole double throw (switch, etc.)
ips	inches per second	SPKR	speaker
J	jack	spst	single pole single throw (switch, etc.)
K	thousand	SSB	single sideband
K	cathode (on tubes)	ssc	single silk covered (wire)
kc	kilocycle	SW	shortwave, switch
kw	kilowatt	SWR	standing wave ratio
$\lambda$ (lambda)	wavelength	sync	synchronization
L	inductor (inductance)	T	transformer, trimmer
L	coil	TELEG	telegraph
LDR	light-dependent resistor	TERM	terminal
lf	low frequency	tptg	tuned plate tuned grid transformer
LIM	limiter	TRANS	tuned radio frequency transformer
LIN	linearity	trf	television interference
$\mu$ (mu)	micro- (one-millionth)	TVI	television interference
$\mu\text{f}$	microfarads	uhf	ultra-high frequency
$\mu\text{h}$	microhenry(ies)	v	volt(s)
$\mu\mu\text{f}$	see pf	V	tube
$\mu\text{sec}$	microseconds	va	volt-ampere
M	meter	vac, vdc	volts ac, dc
M	million	VAR	variable
ma	milliampere(s)	VC	voice coil
MATV	master-antenna television	VDR	voltage-dependent resistor
MAX	maximum	VERT	vertical
mc	megacycle(s)	VFO	variable frequency oscillator
meg	megohm	vhf	very high frequency
mh	millihenry(ies)	vibrator	vibrator
mike	microphone	VIB	volume
MIN	minimum	VOL	volt-ohm-milliammeter
MOD	modulation (modulator)	VOM	voltage regulator (tube)
MPX	multiplex	VR	vacuum-tube voltmeter
MULT	multiplier	vtvm	volume unit(s)
MVB	multivibrator	VU	watt(s)
n	nano- (one-billionth)	W	reactance
NBFM	narrow-band FM	X	crystal
NC	neutralizing capacitor	xtal	impedance
N.C.	normally closed (switch or relay)	Z	

—END—



B&K MODEL 970 RADIO ANALYST

# SERVICE AM & FM AUTO AND TRANSISTOR RADIOS AT A PROFIT!

**NEW!**

Jobs that used to be unprofitable now go so quickly that you can make good money handling them! There are millions of auto radios and transistor radios in the field—portables, auto and table models, plus hi-fi and communications equipment. Instead of turning them away, you can turn them into money-makers with the B&K Model 970 Radio Analyst.

The 970 is effective because it's *accurate* and *complete*. Using the famous B&K signal injection technique, this all-in-one instrument provides the required dc power, lets you test power and signal transistors in and out of circuit; generates RF and audio signals, and includes a rugged, accurate VOM. Four functions in one compact package—with solid state reliability, B&K professional quality.

### LOW INVESTMENT—QUICK RETURN

See your B&K Distributor or write for Catalog AP22-R

Net \$199<sup>95</sup>



**B & K MANUFACTURING CO.**  
DIVISION OF **DYNASCAN CORPORATION**  
1801 W. BELLE PLAINE AVE. • CHICAGO, ILL. 60613

Export: Empire Exporters, 123 Grand St., New York 13, U.S.A.  
Circle 23 on reader's service card

### FEATURES:

#### BUILT-IN POWER SUPPLY

**Auto Radios**—High current, low-ripple, for transistor, hybrid, and vibrator types.

**Transistor Portables**—1½ to 12 volts for battery substitution—plus separately variable voltage tap for bias.

#### QUICK AND ACCURATE TESTING OF POWER AND SIGNAL TRANSISTORS

**In-Circuit**—stage by stage DC signal injection and sensitive metering of power supply current.

**Out-of-Circuit**—Direct Beta and Leakage meter scale readings. Easy balancing or matching.

#### VERSATILE SIGNAL GENERATORS

**RF Generators**—provide broadcast and IF frequencies for both AM and FM bands.

**Audio Generator**—for AM or FM modulation of the RF signals, and for troubleshooting audio circuits.

#### RUGGED VOM

**Volt-OHM-Milliammeter**—with rugged, taut band meter—provides correct ranges for easy, fast servicing of all home and auto radios, as well as transistor portables.


# 696,000 TECHNICIANS NEEDED BY 1970!

## Government Report\* Points Out Rapidly Growing Job Opportunities: Need for Trained Electronics Technicians An Important Factor

By Bill Gordon, RCA Institutes, Inc.

**President Johnson Emphasizes Need.** In his 1964 annual manpower report, President Johnson indicated that the demands for manpower are expanding most in, among other fields, service and technical (including technician) occupations. This expansion is the result of a handful of causes underlying today's big changes in the occupational picture: (1) increasing complexity of modern technology, (2) trend toward automation of industrial processes, (3) growth of new areas of work, such as in the field of atomic energy, earth satellites and other space programs, and (4) data systems analysis and data processing. Indicative also of the growing importance of the use of technicians is a recent revision of the "List of Critical Occupations" published by the U.S. Department of Labor in which technicians are listed for the first time by the U.S. Government.

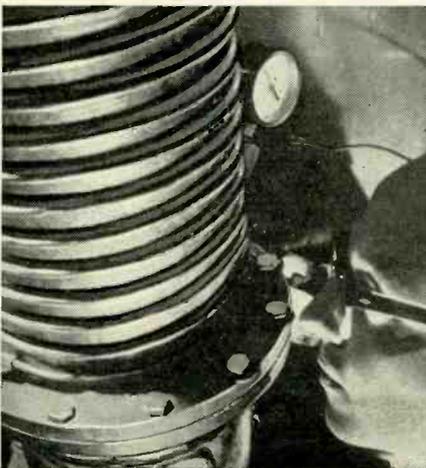
**Salary Levels for Trained Technicians Rising Fast.** Beginning salaries for graduates of top level technician education programs have continued to go up during the past five years, at a faster rate than salaries of similar types of jobs. In fact, a U.S. Labor Department projection based on the figures shows that by 1970, technician salaries will average an all-time high.



Nuclear Instrumentation

**Technical Education is One of Today's Best Investments.** Today, a person interested in becoming a technician can choose Home Training or Classroom Training to begin building his career. One of the nation's largest schools devoted to training electronics technicians, RCA Institutes, offers a wide variety of courses in both categories. In addition, the RCA "AUTOTEXT" Programmed Instruction Method is helping people learn faster and easier so they can get started on their careers in the shortest possible time. Dramatic proof comes from the success stories of countless graduates who find profitable positions in government, industry, or in their own businesses. Of the total 696,000 technicians needed by 1970, it can be estimated that electronics technicians at all levels will form a vital core in today's major job picture.

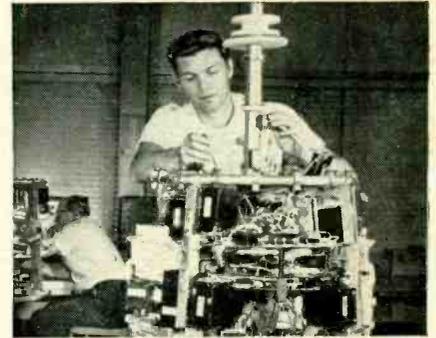\*"Scientists, Engineers, and Technicians in the 1960's" U.S. Department of Labor, Bureau of Labor Statistics.



Space Electronics

# RCA DEVELOPS AN EASY WAY TO LEARN ELECTRONICS AT HOME

New "Career Programs" Help Train You For Expanding Job Opportunities.  
RCA "AUTOTEXT" Instruction Method Speeds Learning

Choose an RCA "Career Program" that will train you for the job you want in Electronics! No time wasted learning things you'll never get to use. "Career Programs" answer the need for today's growing job opportunities for trained Electronics Technicians. They can help you get the job you want faster and easier than you ever dreamed possible!

And each "Career Program" starts with the amazing "AUTOTEXT" Programmed Instruction Method—the scientific way to learn that's almost automatic! "AUTOTEXT" helps even those who have had trouble with ordinary methods of home training in the past. This is the "Space Age" way to learn everything you need to know with the least amount of time and effort!

Choose a "Career Program" now. Each one is designed to train you for a specific, rewarding career in one of the following exciting fields:

- TELEVISION SERVICING
- FCC LICENSE PREPARATION
- AUTOMATION ELECTRONICS
- AUTOMATIC CONTROLS
- DIGITAL TECHNIQUES
- TELECOMMUNICATIONS
- INDUSTRIAL ELECTRONICS
- NUCLEAR INSTRUMENTATION
- SOLID STATE ELECTRONICS
- ELECTRONICS DRAFTING

In addition to these "Career Programs" RCA Institutes offers a wide variety of separate



Radar Microwave

courses on many subjects—from Electronics Fundamentals to Computer Programming.

#### VALUABLE EQUIPMENT INCLUDED

And, with your RCA Training, you receive top-quality equipment to keep and use on the job. When you train with RCA Institutes, you never have to take apart one piece to build another. You'll get the new Programmed Electronics Breadboard which provides limitless experimentation...and, with which you construct a working signal generator and a superheterodyne AM Receiver.

#### SPECIAL BONUS— OSCILLOSCOPE and METER KITS

Valuable Oscilloscope and Multimeter Kits are yours at no additional cost when you enroll in any one of the RCA Career Programs... "must" equipment for electronics technicians in almost all jobs.

#### LIBERAL TUITION PLAN

Only RCA offers you this most economical way to learn. You pay for lessons only as you order them. No long term contracts. You may stop your training at any time without owing a cent.

#### CLASSROOM TRAINING ALSO AVAILABLE

If you prefer to learn in a classroom, RCA Institutes maintains one of the largest schools of its kind where the latest classroom and laboratory training is available in day or evening sessions. You may be admitted without any previous technical training.

Preparatory courses are available if you haven't completed high school. Coeducational classes start four times a year.


#### FREE PLACEMENT SERVICE

RCA Institutes records prove that in a recent class 9 out of 10 Resident School students who used the Free Placement Service had their jobs waiting for them when they graduated. And, many of these jobs were with top companies in the field—IBM, Bell Telephone Labs, General Electric, RCA, and radio and TV stations, and other communications systems throughout the world.

**SEND THE ATTACHED POSTAGE PAID CARD FOR COMPLETE INFORMATION WITHOUT OBLIGATION. NO SALESMAN WILL CALL. VALUABLE FREE BOOK INCLUDED. CHECK HOME STUDY OR CLASSROOM TRAINING.**



Computer Programming

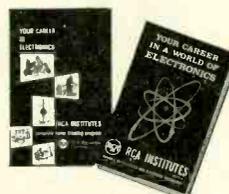

THE MOST TRUSTED NAME IN ELECTRONICS

Circle 24 on reader's service card

**RCA INSTITUTES, Inc.,** Dept. ZRE-D5  
A Service of Radio Corporation of America  
350 West 4th St., New York, N. Y. 10014

"AUTOTEXT"—An RCA Trademark

# Be super-critical.

Whether you're looking for the fun and economy of building quality kits or you want ready-to-use factory-wired equipment — before you buy, examine carefully. Compare

EICO with anybody else — feature for feature, chassis for chassis, part for part. The more critical you are, the more you'll see for yourself that your best buy is EICO.



Over 3,000,000 EICO instruments now in use! Preferred by engineers, scientists, technicians and students. EICO equipment is available nation-wide through 2500 EICO dealers.



**New Model 435** — DC Wideband Scope. Top-quality DC 4.5mc scope with 3" flat-face CRT. Zener calibrator. Outperforms 5" scopes three times its size, facilitates on-location color TV and other servicing. \$99.95 kit, \$149.95 wired.



**New Model 342** — FM Multiplex Signal Generator. Design lab quality. Both composite audio and FM RF outputs. Inputs for stereo audio source for store demonstrations, critical A/B listening tests. \$149.95 wired.




**New Model 965** — FaradOhm Bridge/Analyzer. 9-range, low-voltage capacitance-resistance bridge safely measures even 1-volt electrolytics. Metered bridge balance, leakage test voltage (6 DC VTVM ranges 1.5-500V), leakage current (11 DC VTAM ranges 0.15ua-15ma). DC VTVM & VTAM externally usable. \$129.95 wired.



**New Model 1030** — Regulated Power Supply. Speeds troubleshooting, design work, production line testing, electronics teaching. Variable bias and plate sources regulated to 1/3 of 1%: 0-150V @ 2ma; 0-400V @ up to 150ma. Ripple less than 3mv rms. Unregulated fil. volts of 6.3V & 12.6V, @ 3A. Switchable, monitoring milliammeter and voltmeter. \$59.95 kit, \$99.95 wired.



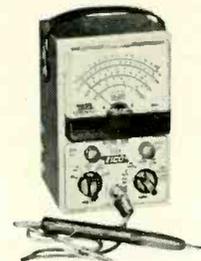**New Model 378** Audio Generator. Near-distortionless sine wave generator (< 0.1% 20-20,000c) providing fast, convenient, switch-selection of frequencies from 1c to 110kc (1c steps 1c-100c, 10c steps 100c-1kc, 100c steps 1kc-10kc, 1kc steps 10kc-110kc). 8-pos. 10db/step output attenuator & fine attenuator. Output meter (4 1/2" 200ua) with 8 voltage ranges & db scale. \$49.95 kit, \$69.95 wired.



**Model 232** Peak-to-Peak VTVM. A must for color or B & W TV and industrial use. 7 non-skip ranges on all 4 functions. With Uni-Probe® \$29.95 kit, \$49.95 wired.



**New Model 779** — Sentinel 23 CB Transceiver. 23-channel frequency synthesizer provides crystal-controlled transmit and receive on all 23 channels. No additional crystals to buy ever! Features include dual conversion, illuminated S/R/F meter, adjustable squelch and noise limiter, TVI filter, 117VAC and 12VDC transistorized dual power supply. Also serves as 3.5 watt P.A. system. \$169.95 wired.



**New Model 712** — Sentinel 12 Dual Conversion 5-watt CB Transceiver. Permits 12-channel crystal-controlled transmit and receive, plus 23-channel tunable receive. Incorporates adjustable squelch & noise limiter, & switches for 3.5 watt P.A. use, spotting, & Part 15 operation. Transistorized 12VDC & 117VAC dual power supply. \$99.95 wired only.



**New Model 753** — The one and only SSB/AM/CW Tri-Band Transceiver Kit. 200 watts PEP on 80, 40 and 20 meters. Receiver offset tuning, built-in VOX, high level dynamic ALC. Unequalled performance, features and appearance. Sentionally priced at \$179.95 kit, \$299.95 wired.



**New Model 3566** — All Solid-State Automatic FM MPX Stereo Tuner/Amplifier. No tubes, not even novistors. Delivers 112 watts IHF total to 4 ohms, 75 watts to 8 ohms. Completely pre-wired and pre-aligned RF, IF and MPX circuitry, plus plug-in transistor sockets. \$219.95 kit (optional walnut cabinet \$14.95), \$325.00 wired including walnut cabinet. UL approved.



**Model ST70** 70-Watt Integrated Stereo Amplifier. Best buy of highest ranked stereo amplifiers according to independent testing. \$99.95 kit, \$149.95 wired. ST40 40-Watt Integrated Stereo Amplifier, \$79.95 kit, \$129.95 wired. ST97 Matching FM MPX Stereo Tuner, \$89.95 kit, \$139.95 wired.

**EICO Electronic Instrument Co., Inc.**  
131-01 39th Ave., Flushing, N. Y. 11352

Send for **FREE** catalog describing the full EICO line of 200 best buys and name of nearest dealer. I'm interested in:

- test equipment
- hi-fi
- ham radio
- CB

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Zip \_\_\_\_\_

RE-12

**1945-1965: TWENTY YEARS OF LEADERSHIP IN CREATIVE ELECTRONICS**

Circle 25 on reader's service card

## FUEL CELLS

*... The fuel cell was discovered in 1839, but its use has only begun ...*

The fuel cell was discovered by Sir William Grove in 1839. Fifty years later, Ludwig Mond and Carl Langer experimented with a similar device and coined the name "fuel cell." But the dynamo was then becoming a cheap and convenient means of generating electricity, and fuel-cell development was pushed into the background. It did not receive any serious attention until F. T. Bacon started work with his hydrogen-oxygen cell in the early 1930's. The present-day fuel cell had its first important use in the Gemini spacecraft this year.

Fuel cells produce power from a continuous supply of fuel. They weigh far less than other batteries of comparable power output. Modern tests on fuel cells have shown no sign of wearout in more than 7 months of continuous operation.

The General Electric fuel cells which have been used in spacecraft contain an anode and a cathode which are in contact with a solid electrolyte that permits the exchange of hydrogen ions between the electrodes. The key to the modern long-life cell lies in the new solid polymer electrolyte which is extremely resistant to chemical oxidation at high temperature.

The fuels commonly used are hydrogen and oxygen. The hydrogen fuel is introduced on one electrode and the oxygen on the other. By the aid of a catalyst the hydrogen atoms give out one electron each, forming ions which migrate through the solid electrolyte to the cathode. There they combine with oxygen to produce electricity and, as a byproduct, potable water, which is carried off by capillary action in wicks to a collection point.

The unusual feature of fuel cells is their high efficiency: they convert between 50% and 70% of their energy to electric power. A fuel cell produces uninterrupted electrical power directly from a continuous chemical reaction, as long as the fuel and oxidant are supplied. Normally, fuel cells have no moving parts and therefore need little or no maintenance. They are silent and give off no fumes.

The principal components of a typical fuel-cell power system are: the fuel supply system, the battery of fuel cells, water and heat removal, setup electrical control. Fuel consumption is approximately 0.9 lb per kilowatt hour.

The fuel cells used in the Gemini craft operate at a voltage of 0.73 to 0.9, delivering up to 73 watts per square foot of cell.

Fuel cells are, of course, never recharged as are storage batteries, but work by the use of fuel only.

One of the latest developments of the G-E fuel cell is centered in the solid polymer electrolyte already mentioned. This design is characterized by the use of a tough, thin sheet of polymer plastic. An ion exchange membrane forms the electrolyte. By binding a simple catalytic electrical structure to

each side of the sheet, it becomes possible to construct a fuel cell of unique simplicity and light weight. As the membrane rejects water above a fixed amount, that byproduct of operation can be easily removed by condensing the vapor on cool wicks, which carry it off by capillary action.

G-E scientists have also announced development of a fuel cell that operates from hydrogen and air, and also one that operates from hydrocarbon fuel and air. Furthermore, the 8-day Gemini project proved that fuel cells can provide spacecraft power under almost all space conditions, irrespective of the space-gravity conditions.

Fuel cells are connected in series and parallel to obtain the necessary power output. In the Gemini unit, 32 cells are connected into modules, with three modules electrically in parallel in each fuel-cell battery. The complete Gemini fuel-cell battery system is composed of two batteries, each in a container about 2 feet long and 1 foot in diameter.

When operated together, these two fuel-cell batteries produce up to 2 kilowatts peak power, and give 1 pint of water per kilowatt hour of operation. The complete system weighs 135 lb, exclusive of fuel.

On preliminary tests, one fuel-cell battery completed a 6-week test run of 1,100 hours, equal to more than 750 orbits; in other words, five times to the moon and back.

These are only the bare facts about the fuel cell, which is still in the early stages of its development. What may we expect from it in the future? It would seem that in most cases where storage batteries are used the fuel cell will be able to do the job much better. First, we have replacement for ignition batteries. Wherever weight is of not much consequence, the fuel cell can do the work better and often cheaper. It is true that the usual storage battery gives 2 volts per cell whereas the fuel cell gives only slightly less than half of this. Yet, if all factors are weighed, the fuel cell will come out on top.

Where power is concerned, the fuel cell will often prove much cheaper and much lighter than storage batteries. It may in many instances replace the gasoline engine.


The fuel cell may often prove more advantageous than an isolated electric plant which requires an internal combustion engine to furnish power. Wherever it is impossible or impractical to employ an electric line, the fuel cell will find an opportunity.

Delivery trucks, some of which still use storage-battery propulsion, will find fuel cells very useful. The Allis Chalmers Co. has developed an experimental fuel-cell-powered tractor.


Because fuel-cell power units can be stored for long periods, they promise many other industrial applications, including power supplies for remotely located commercial equipment, TV repeater stations, beacons, etc. —H.G.

*Merry Christmas—Happy New Year*


The Staff of RADIO-ELECTRONICS

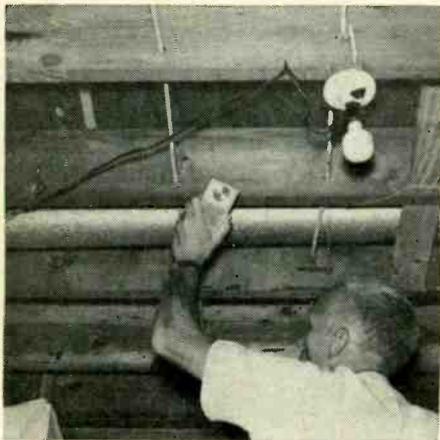

*Chase it along the cord . . .*

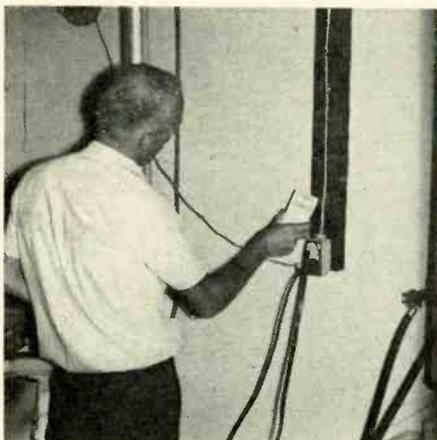

*to the outlet box . . .*

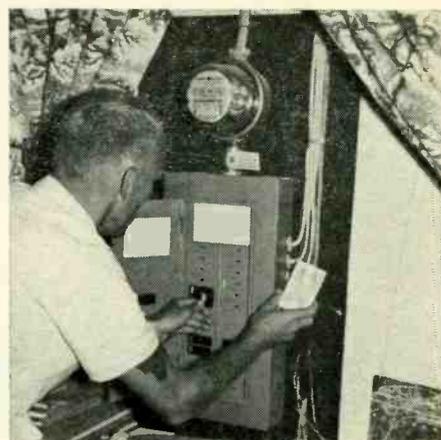

*through the breakers . . .*

# HOW TO TRACK INTERFERENCE

**A small transistor portable, moved along suspected wiring, can guide you to the source of the noise or snow**

**By THOMAS R. HASKETT**


INTERFERENCE IS ANY SIGNAL THAT interferes with a radio listener's or a TV viewer's enjoyment of his desired program. This includes reception of CB, amateur and two-way radio, as well as all entertainment sources. Before you can eliminate interference, you have to identify the source, localize the source and track it down.

While it won't *always* help, if you can identify the source, you can often go straight to it and remedy the trouble. For example, if you hear CB or a ham operator coming in on your TV or broadcast receiver, write down the call letters. Amateur radio call signs consist of K or W followed by a numeral from 0 to 9 and two or three letters. The letters A, B or N may be inserted between the first letter and the digit. Examples

of amateur call signs are W2PWG, KAØXKC, WN2HTW and WB7XAZ. Older Citizens band licensees have call signs consisting of one or two digits, one or two letters, followed by four digits. All other two-way radio stations such as fire, police, ambulance and taxi cabs and CB stations licensed since January 1962 use call signs consisting of the letter K followed by two letters and three or four numerals. Examples of these are 2W3056 and KEC863. If it is an amateur or CB station you may be able to contact the operator through the local amateur or CB club. If you can't identify the station, send the call letters to the FCC or call the FCC field office in your area. Once you contact the operator, you can take it from there. While he may not be at fault, he can (and usu-


ally will) tell you what frequency he's operating on, and thereby enable you to try trapping out his signal. If you know what you're looking for, it's usually easier to search. Except for atmospheric static, which we won't consider here, interference sources fall into three categories.

**1. Nonradio, manmade sources:** Electric motors, fluorescent lights, oil burners, blinker or traffic lights, old long-filament light bulbs, neon signs, arc welders, thermostats and the power line itself. The point to remember here is that these sources make clicks, pops, buzzes and other peak noises, that identify them as nonradio in origin. They are actually rf, but they don't originate from what's usually considered radio equip-

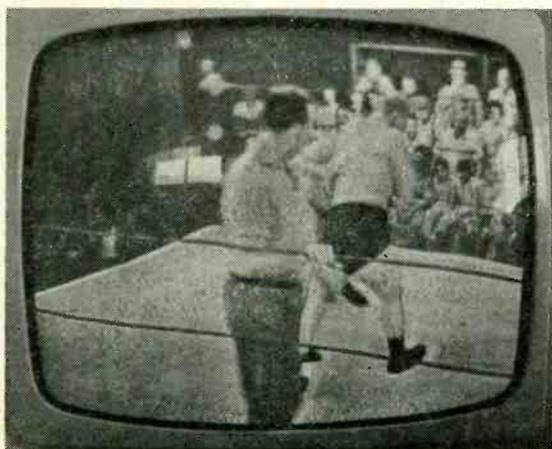


*Fig. 1 — Irregular white flecks are usually motor noise—caused by sparking brushes.*

*Fig. 2 — Heavy oblique bars often result from beat between video carrier and some other unmodulated carrier near it in frequency.*

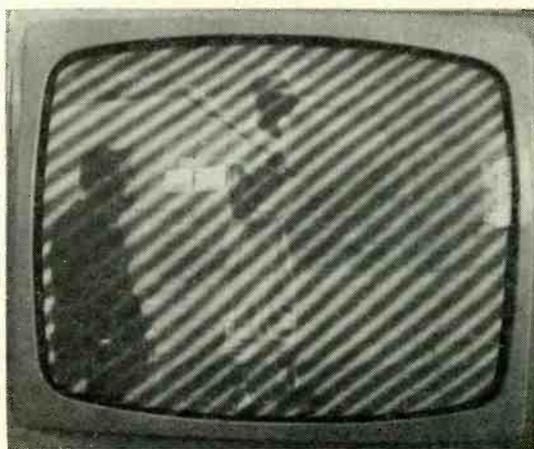



up the service drop . . .

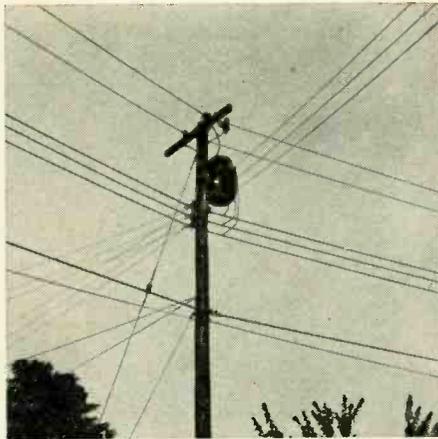

along the power lines!

ment. Sometimes they radiate through free space; most of the time such interference enters a receiver via the power line. An example of the video pattern produced by one of these noises is shown in Fig. 1—the source is dirty brushes in an electric drill motor, brought into the TV set through the power line.

**2. Transmitters:** Broadcast, amateur, police, CB and other transmitters can cause interference, but often **not** at their fundamental frequency. Every transmitter is a harmonic generator. Although FCC rules require harmonics to be suppressed, rigs sometimes become defective. At times the fundamental of one transmitter cross-modulates the fundamental of another; the resultant sum or difference frequency can pop up in the middle of a TV channel. When an FM station is heard through a TV set on one channel only, cross-modulation is often the cause.

Sometimes a transmitter puts such an intense signal into an area that it causes rectification and spurious signal generation in such things as conduits, air ducts, drain pipes, metal laths and stove pipes. Seldom a problem in new houses, this trouble is usually found in older construction.

Strong fundamental frequencies from nearby transmitters also get into battery chargers, electronic control devices, and even audio amplifiers, where some nonlinear element produces beats and reradiates this interference. Since this type of interference consists of a radio wave, it appears as a steady carrier, sometimes with identifying modulation, but often without.

Figs. 2 and 3 show what happens when a strong rf carrier gets into a TV, producing the familiar herringbone pattern characteristic of a steady carrier. In this case, it was the third harmonic of a CB transmitter interfering with channel 6. In Fig. 2, the presence of few bars tells you the interference is located *close* to the video carrier on

83.25 mc. In Fig. 3, the presence of a fine-mesh pattern of many bars indicates the interference is located well *away* from the video carrier. Of course, similar results would be produced by interference getting into the video i.f. in either the 20- or 40-mc range.

An oft-reported type of interference produces “strange voices” from the electronic organ in a church or funeral parlor, from the PA system at the stadium or the sound system at the movie house. This occurs when a strong rf signal—usually from a hf or vhf transmitter—gets into audio circuitry and is rectified. The interfering signal can come from a TV, FM, CB, ham or any two-way radio transmitter. This problem is generally caused by direct pick-up of a fundamental signal and is solved by installing rf filters and shields in the audio circuits. If the signal is intermittent ask the station operator to help when testing or adjusting the rf filter.

Remember that some transmitters carry no modulation or only raw ac—such as diathermy equipment, some radio-controlled garage-door openers, mercury-vapor germicidal lamps, and rf heating equipment. Remember also that cross-modulation often occurs in the

receiver's rf or mixer stage. The rf amplifier may be overdriven by strong interference, and thereby operate on the nonlinear portion of its plate-characteristic curve, producing heterodynes; the mixer is already nonlinear and will readily produce other beats.

**3. Receivers:** They can interfere with each other and with themselves. Nearly all contain a local oscillator. TV's also contain horizontal and vertical oscillators, and their respective output-amplifier stages. These are usually operated class-C and have high harmonic content. The vertical is seldom troublesome, but the horizontal output is a buzz-saw that can mar reception across the broadcast band and well into the 80-meter ham band. Local-oscillator interference usually consists of an unmodulated carrier that rides in over a desired station (in radio) or produces a herringbone (in TV). Occasionally a receiver interferes with itself. An example is Barkhausen oscillations, consisting of vertical stripes down the left side of the raster, produced by a harmonic of the horizontal scanning output, picked up by the TV's own tuner.

#### Localize

If you cannot go directly to the source, eliminate the negatives and concentrate your attention on the most likely path for interference.

1. Substitute another receiver, known to be in good condition, at the same location, to prove the interference is not self-generated. If an outdoor antenna is used, as in TV, be sure to attach it to the substitute receiver. It's usually easier to combine this step with the next one.

2. Use a battery-powered receiver at the location of the problem receiver, eliminating the ac line. Open the breaker or fuse box and disconnect the particular branch circuit feeding the receiver location. If the interference disappears, it's being carried via the power line and you can trace it accordingly. If not, try grounding the *load* side of the ac

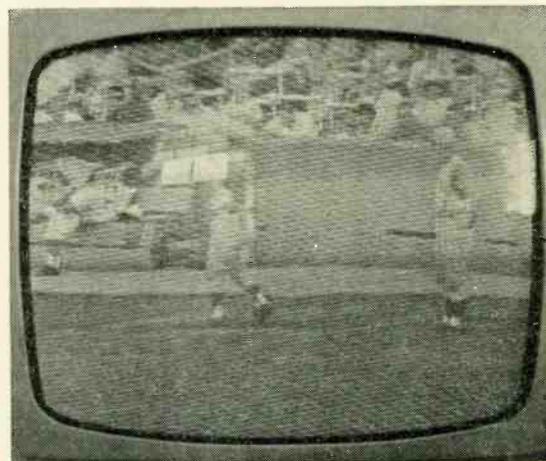


Fig. 3—Light “tweed” pattern is higher-frequency beat, from carrier comparatively far in frequency from video carrier.

line at the breaker box, to see if *this* gets rid of the interference. *Caution: be very careful with that jumper.* Kill the main circuit breaker first. Then attach the jumper to the electrical ground bus, which will have white wires connected to it. Finally, touch the jumper to each branch circuit in turn (Fig. 4) and see if the interference disappears. When finished, remove the jumper, replace the protective panel, and restore the main breaker. If you can't kill the interference by grounding the power line, chances are it's coming in through space.

### Track

1. If the interference is coming via the power line, it won't be too difficult to run it down. First determine if it's inside or outside the building. Pull the main breaker at the breaker box, follow the power line up the service drop, and out to the street, with a portable receiver. If the interference is gone, it must be generated within the house. Put the main breaker back in and throw off all branch circuit breakers but one, listening on the receiver to see if the interference reappears. After you find the offending circuit, trace wiring to outlets, unplug appliances, until the trouble disappears. You may have to crawl into an attic or basement fruit cupboard to dig out an all-but-forgotten outlet. Sometimes old radios, TV boosters or heating pads are ignored and left on for years. They can radiate over a wide area.

If the interference enters the building via the power company's service cable, it may be due to the power line itself. In many cases it won't go much beyond a pole transformer, and it's a good idea to take the portable receiver as close to the pole as possible. Check service drops to other houses. If in doubt, call the power company and have them send out an interference-tracing crew. They are usually quite cooperative and will take any reasonable steps to get rid of interference caused by their own equipment. Cracked or open insulators on lines will generate buzz and crackling noises. Sometimes lines sag and intermittently touch grounded objects.

2. If interference is not being received through the power line, it must be traveling by free-space radiation. The only way to track it is by using a portable receiver with a directional antenna. The usual portable AM radio has a bi-directional loop, and the signal nulls (points of minimum reception) are at right angles to the plane of the loop. Some portable FM and TV receivers have monopole antennas, which are useless for direction finding. Get rabbit-ears and connect them in place of the monopole. You will then have a simple

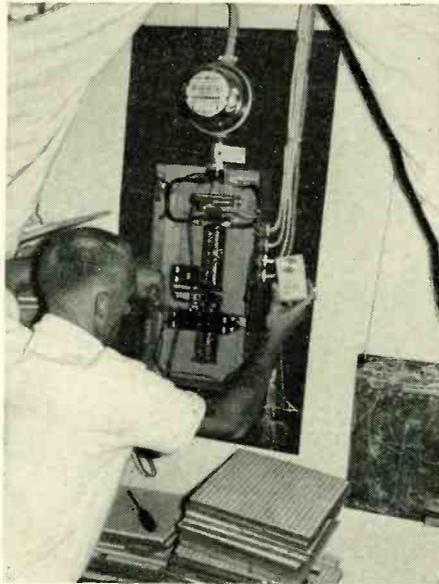


Fig. 4—Transistor portable traces interference on power lines. Be very careful! Pull main breaker or fuses before beginning this test.

dipole antenna, which has its nulls along its length. The reason for using nulls is that they offer sharper indication than lobes (points of maximum reception).

Nulls pinpoint direction, but to determine whether the interference is getting better or worse, it's necessary to use lobes. It might be supposed that receiver *ave* or *age* defeats the attempt at direction finding, but this isn't true. You aren't concerned with the *absolute* field strength of the radiated interference—you're interested only in the *ratio* of undesired to desired signal, and *ave* won't alter that, provided you are still getting a clear pickup of signal from the desired transmitting station. Each time you take a bearing, note which way the nulls point, and move one way or the other along this line. If the interference gets worse, you're going in the right direction.

It is sometimes possible to speed up the tracking process by using an automobile. Whatever the method, you can usually determine the interference source. The owner can be politely asked to remedy the situation. If it's not his fault, you can at least determine the frequency or frequencies the radiation is emitted at, which will then allow you to use traps or filters to keep it out of the receiver. It is usually more desirable to correct the problem at the source, for then you clean up many receivers. Besides, once the interference gets into the vicinity of a receiver it's difficult to eliminate it entirely. Remember that where the interference source is clearly at fault, and a polite request to investigate the problem doesn't produce any action, you can always report the matter to the FCC, either in Washington, D.C., or their nearest district office. END

## ARE WE REALLY MAKING PROGRESS?

I WAS CLOSING MY CADDY WHEN SHE said, "Wait a minute. I have something else for you to look at."

She came back a minute later with an old radio in a wood cabinet. I could spot the vintage by the bay window that housed the speaker. I also knew the tubes with top caps were not 6BQ6's.


"This old set has the best tone I ever heard, and I would like to get it fixed. It also has a sentimental attachment. My first boy friend gave it to me."

It was the light in her eye as she said this that made me tuck it under my arm and promise to try.

The next day I dug it out and plugged it in. There was not a sound.

I slipped the chassis out of the cabinet. The voltmeter revealed no B-plus. Touching a screwdriver from the plates of the 80 to chassis indicated no ac on them. The ohmmeter showed the secondary of the power transformer wide open both sides of center tap.

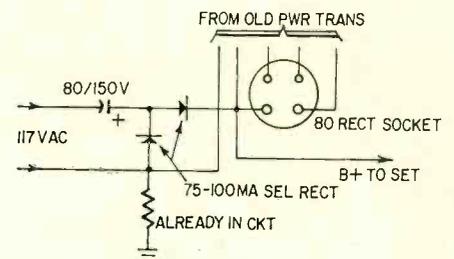I was thinking in terms of forgetting it right then, but I remembered the twinkle in the eye and decided to go a step further.




I rigged up a voltage-doubling circuit with two seleniums and an 80-uf 150-volt capacitor, just lying on the bench. When I touched the positive to the 80 filament connection, the volume seemed up to normal and the tone was good. (It sounded almost like a hi-fi.)

I flipped the bandswitch to the short-wave position just to see, and was really surprised to pick up a Britisher and a bunch of Spaniards, even though the antenna was only a few feet of wire lying on the floor.

I installed the voltage-doubling circuits permanently (no trouble finding space) and slid the chassis back into the cabinet. The solid wood case rounded out the tone to a point that left nothing to be desired.

A check of tubes revealed that all were at least 15 years old. None needed replacing.

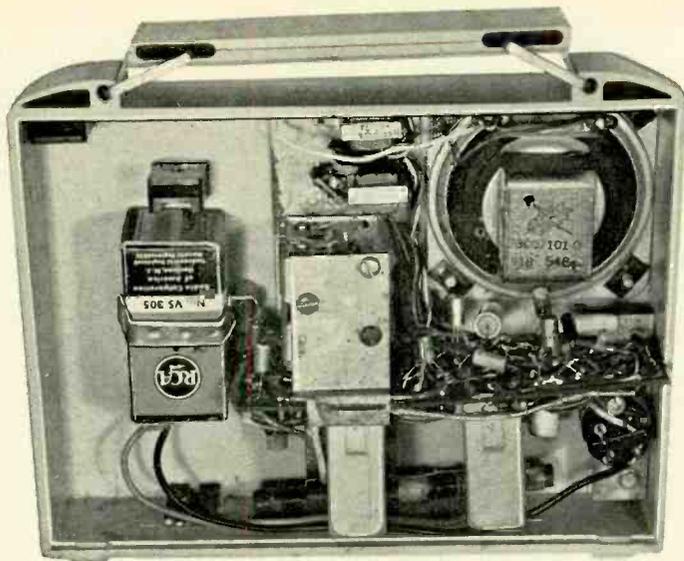As I fastened the back on I couldn't help but wonder—Are we *really* making progress?—Harold Davis



*Wide-open space around battery is where bulky A- and B- batteries of tube set used to be. When you do your conversion, you might want to shuffle the parts around and install a bigger speaker—or twin speakers.*

# TRANSISTORIZE Your Tube Portable

**We don't normally like the word "transistorize", but we really mean it here! You can rebuild your old tube portables to use transistors, and save a lot in tube and battery replacement!**

By JAMES E. PUGH, JR.

Practically every experimenter has wondered whether it might be practical to convert old portable tube radios—now universally discarded as uneconomic—to transistors. Until now the low input impedance and medium output impedance of transistors would have required replacing or drastically altering all rf, i.f. and oscillator transformers.

But now you can do it—with only the simplest rewiring. A flexible way to get high input and output impedances makes it possible to connect transistors directly to unmodified tube-type rf, i.f. and oscillator transformers. All you add are suitable transistor biasing networks and a few turns to the oscillator transformer.

This circuitry can, of course, be used to convert any tube-type broadcast set—table, console or auto, as well as portables.

The basic circuit is an *emitter-coupled amplifier*. It uses two transistors per stage, coupled together across a common-emitter resistor—R in Fig. 1. Q1 is a common-collector amplifier (high input impedance and very low output impedance). Q2 is a common-base amplifier (very low input impedance and high output impedance). Considered together as one stage, this emitter-coupled pair has an input and output


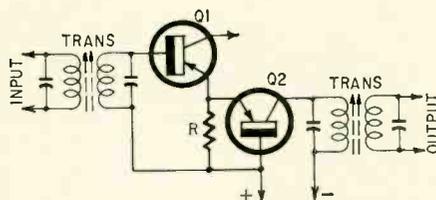


Fig. 1—Basic emitter-coupled amplifier has tubelike input and output impedances.

impedance much higher than normal in a transistor stage.

The input impedance is slightly lower than optimum, but the output impedance is high enough to give no perceptible deterioration in performance. Input capacitance is slightly higher, and output capacitance slightly lower, than that of the tube which the transistor pair replaces. Overall power gain is slightly greater (theoretically) than from a well matched common-emitter

Fig. 2—Basic complementary (p-n-p/n-p-n or vice versa) emitter-coupled amplifier.

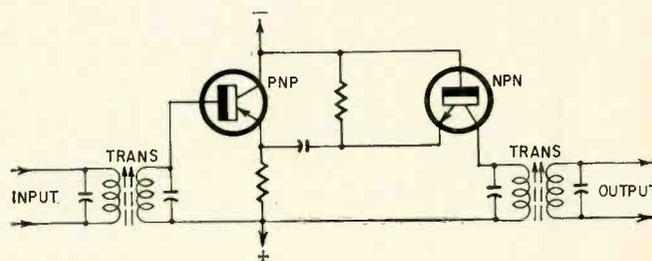

stage. Voltage and current gains are about the same.

Fig. 2 shows a complementary p-n-p/n-p-n pair in the same kind of circuit.

Fig. 3 is the complete circuit diagram of a converted radio. The basic emitter-coupled circuit is used in the rf section, but with one high-impedance input section (the rf amplifier) and two high-impedance output sections (the oscillator and mixer). In this stage Q1 is direct-coupled to Q3 across R1 to form a pair like that in Fig. 1.

Since the oscillator is a common-base section with low input and high output impedance, it too can be coupled into the mixer at the low-impedance point (R1) through capacitor C3, putting a negligible load on transformer T1. This section has its own emitter resistor, and the signal injection into the mixer is determined by the size of C3.

This circuit not only gives conventional oscillator and mixer action, but also an rf amplifier with about 15 db gain.

The i.f. amplifier is essentially the same as the basic circuit in Fig. 1. It uses double-tuned transformers for very good selectivity (four tuned circuits) in just one stage. Avc voltage from the detector (D1) is applied to both sections of this stage as well as to the rf and mixer sections.

Although all these transistors obtain their base and collector voltages from a common source, separate decoupling filters are not used in the i.f. afc lead or in the collector return of any transistor. Where possible, all such parts were eliminated to keep conversion costs to a minimum. But if your set has two i.f. stages, you will have to add decoupling and possibly neutralize both stages to prevent oscillation.

The audio amplifier is conventional except that it uses an inexpensive germanium diode (instead of a thermistor) that not only compensates for temperature, but also extends battery life by automatically regulating the base-bias voltage for Q7 and Q8 to minimize crossover distortion as the battery voltage drops off with age.

Since this particular case is roomy, I used a large 9-volt battery for economy. It should last about 200 hours with a 9-ma drain, while the conventional 2U4 would last only about 35 hours. Of course, I could have reduced cost by

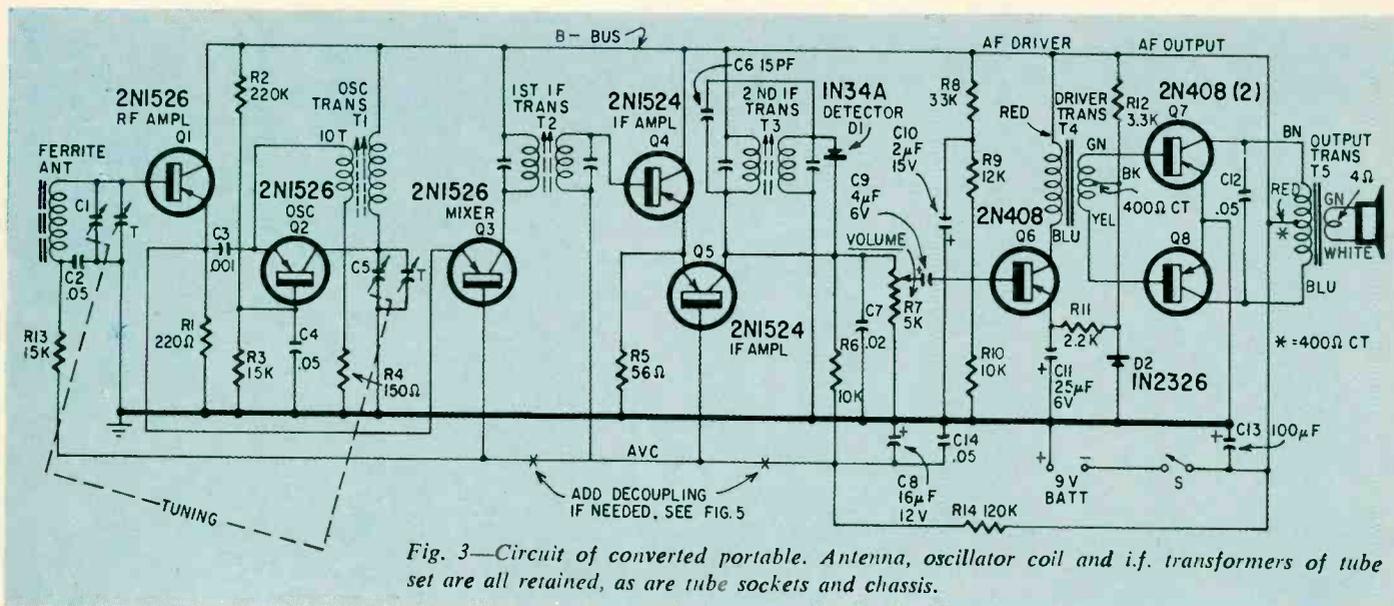


Fig. 3—Circuit of converted portable. Antenna, oscillator coil and i.f. transformers of tube set are all retained, as are tube sockets and chassis.

- C1, C5—tuning capacitor\*
- C2, C4, C12, C14—.05- $\mu$ f, 100-volt paper or Mylar
- C3—.001- $\mu$ f ceramic
- C6—15-pf ceramic
- C7—.02- $\mu$ f, 100-volt, paper or Mylar
- C8—16  $\mu$ f, 12 volts
- C9—4  $\mu$ f, 6 volts
- C10—2  $\mu$ f, 15 volts
- C11—25  $\mu$ f, 6 volts
- C13—100  $\mu$ f, 15 volts
- C8, C9, C10, C11, C13 are electrolytic
- D1—1N34A or equivalent
- D2—1N2326 (RCA)

- Q1, Q2, Q3—2N1526 (RCA)
- Q4, Q5—2N1524 (RCA)
- Q6, Q7, Q8—2N408 (RCA)
- R1—220 ohms
- R2—220,000 ohms
- R3, R13—15,000 ohms
- R4—150 ohms
- R5—56 ohms
- R6, R10—10,000 ohms
- R7—volume control, 5,000 ohms, audio taper
- R8—33,000 ohms
- R9—12,000 ohms
- R11—2,200 ohms
- R12—3,300 ohms

- R14—120,000 ohms
- S—spst switch\*
- T1—oscillator transformer\*
- T2—i.f. transformer, input\*
- T3—i.f. transformer, output\*
- T4—audio transformer, 10,000 to 2,000 ohms ct (Stancor TA-35 or equivalent)
- T5—audio transformer, 500 ohms ct to 4/8/16 ohms (Stancor TA-21 or equivalent)
- SPKR—3.2 ohm speaker\*
- \* parts retained from tube circuit
- BATT—9-volt battery (RCA VS-305 or equivalent)

using 6 type-C flashlight cells.

### The conversion

The first step in making your conversion is to determine what changes, if any, will be necessary in the circuit shown in Fig. 3. If you use two i.f. stages, add the second one to the diagram. Make it identical with the one shown, but add decoupling filters to the first stage.

Next, remove all parts that will not be used, leaving only the rf, i.f. and oscillator transformers, the tuning capaci-

**REPORT ON TRANSISTORIZED PORTABLE**  
 R-E checked the converted set 25 miles from New York City. 18 stations were received with fair volume, and more could be received with careful tuning. One exceptional night, Bonaire in the Netherlands West Indies was received. Tone quality and selectivity were about the same as those of a similar tube portable. A tendency to drop off at the high-frequency end was noticed—all stations were received at 1400 kc or below.


tor, and the tube sockets if you want to use them for tie points. Also, remove all wiring. If it is an etched-circuit board, existing conductors can, by careful plan-

ning, be used with only minor changes. Although the original volume control can be used, the value shown gives better results.

The next step is to plan the layout of all parts. Unused portions of foil conductors can be cut out with a sharp knife, and any necessary bridges between sections made with short pieces of insulated hookup wire.

Solder all parts in place (transistors last, of course), and then wind 10 turns of enameled wire (about No. 32) adjacent to the present oscillator coil. Fasten it in place with coil dope or melted wax. Connect the battery and momentarily bridge a milliammeter across the switch (with switch off). The current drain should be about 8 to 10 ma if everything is satisfactory.

If current is normal, remove the meter, turn the switch on, and set the tuning capacitor to the high end of the band. Now peak the i.f. transformers at 455 kc. Start with the last and work toward the mixer. If double-tuned transformers are used, the primaries and the secondary connected to the detector should not need much adjustment. Any secondary connected to the base of a transistor will need to be retuned more. Back out the slug or loosen the capacitor to peak the transformer at 455 kc. If the i.f. amplifier oscillates, try grounding the transistor cases. A very fine wire can be soldered quickly to the case and then to ground without damaging the transistors. If this doesn't stop oscillation, try

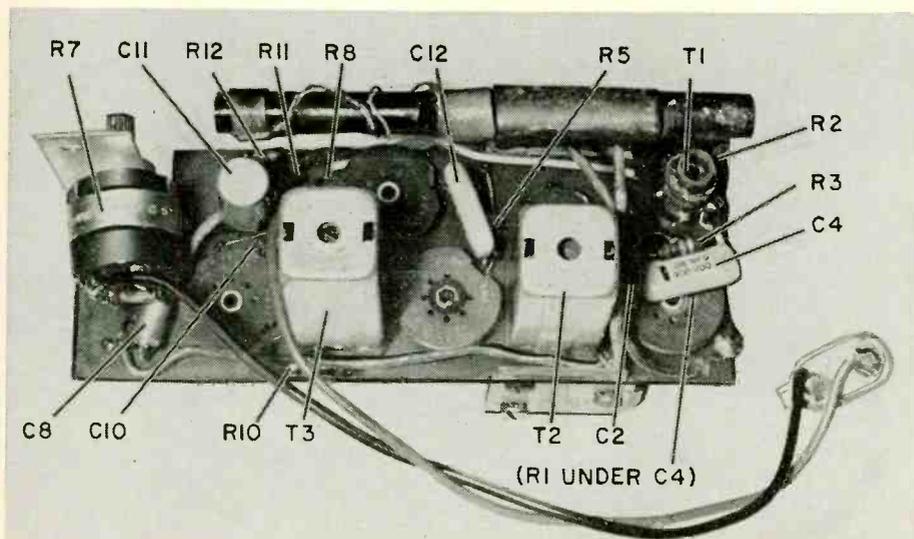

Top of converted chassis. Several turns of the antenna winding have been pulled toward end to lower total inductance.


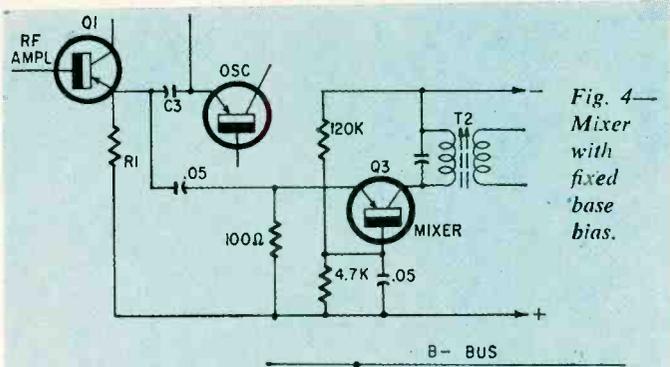
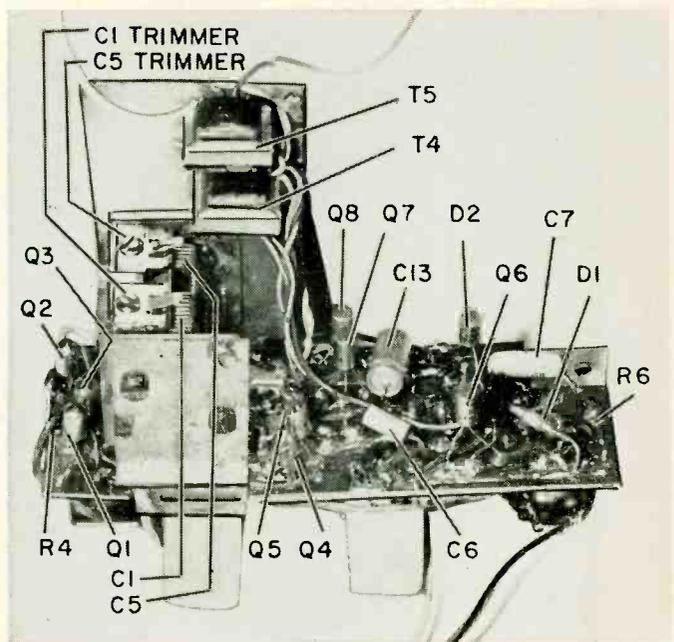


Fig. 4—Mixer with fixed base bias.

Fig. 5—Optional decoupling filters for supply and avc leads.

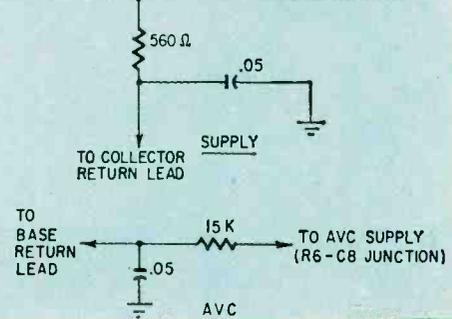

Underside of chassis displays most of the small parts.

neutralizing each stage.

Next, see if you can hear any stations. If not, reverse the two leads from the added oscillator winding. Then adjust the oscillator tuned circuit to cover the broadcast band. If a slug-tuned oscillator transformer is used, adjust the slug to give correct tracking at the low end of the band, and use the trimmer on the tuning-capacitor oscillator section to adjust the top end of the range. The trimmer adjustment should be adequate in most sets that do not use a slug-tuned coil. If not, the coil inductance can be changed by removing turns from the secondary to shift the low-end coverage

these adjustments two or three times to get the best alignment. There is always some interaction between oscillator and antenna circuits.

Possibly you will want to use some of the parts that were removed in this economy program, so you can be sure of top performance under all conditions. Fig. 4 shows what's needed for a separate bias network to the mixer. The separate emitter resistors and a coupling capacitor are necessary for maximum isolation of the mixer from the avc circuit. Otherwise the avc voltage will pull the mixer circuit.

Decoupling filters for avc and

this circuit the i.f. transformer supplies the 180° phase shift when the feedback is taken from the correct end of the secondary. If oscillation increases, simply reverse the connections to either primary or secondary.

Fig. 7 shows how the oscillator transformer can be used without changes. Connect the windings as shown, and reverse the leads of either (if necessary) to get oscillation. This circuit is good, but adds slightly more capacitance across the oscillator's tuned circuit than is desirable for full coverage of the broadcast band. It can be used if you want the utmost simplicity at the cost


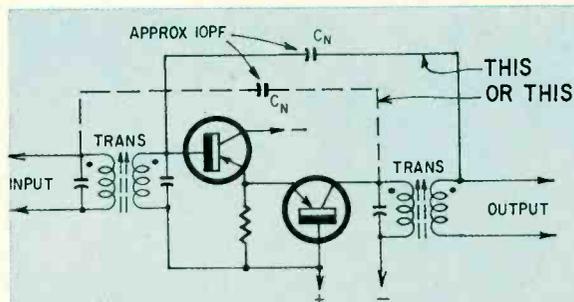


Fig. 6—Two ways to neutralize emitter-coupled amplifier.

Fig. 7—Common-collector oscillator circuit avoids need to modify coil.

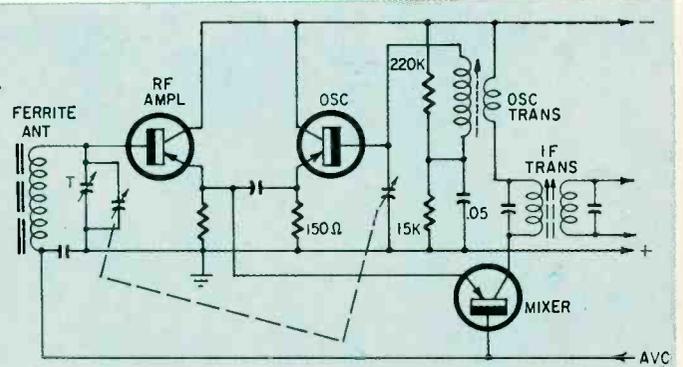

up, or by adding turns to shift it down.

When you get the oscillator perking, tune up the antenna circuit by sliding a few turns of the antenna winding toward the end of the ferrite core for maximum response at 600 kc. Next, adjust the antenna trimmer for maximum response at 1400 kc, and check to see if any touchup is required on the low-frequency end. Sets with antennas that can't be adjusted may require a slight readjustment of the oscillator frequency to peak the response at 600 kc. Go over


battery supply leads are shown in Fig. 5. Simply add them as needed for the required stability.

If your set needs to be neutralized, keep in mind that both the common-collector and the common-base amplifier have no phase inversion between input and output; thus there will be no phase inversion in the emitter-coupled stages used in this set. Since the feedback voltage must be 180° out of phase with the input voltage to neutralize any amplifier, a method like Fig. 6 must be used. In

of a slight reduction in coverage at the high-frequency end of the band.

If your set uses the older loop antenna without a ferrite core, you may want to replace it with a ferrite type for increased performance. Make sure the inductance of the new antenna is right for your tuning capacitor. Mount it at least 2½ to 3 inches from the chassis and not too close to an unshielded oscillator coil. If necessary, put a shield between oscillator coil and antenna.

END

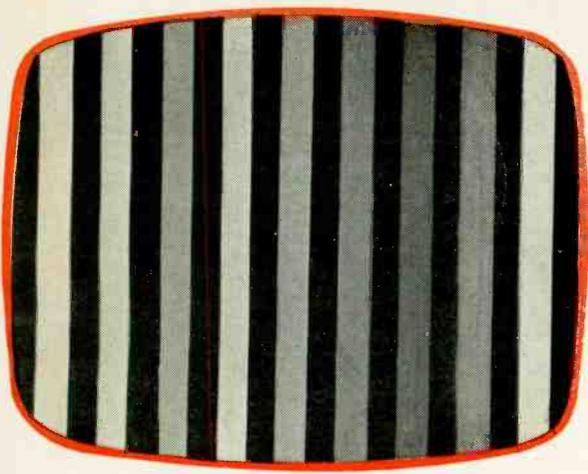

# Service Color TV Traps and Pitfalls

Three sections of a color receiver worth special attention

By MATTHEW MANDL

THE SPECIAL CIRCUITS IN COLOR RECEIVERS need special care in service. Even then, some results may be highly unexpected to the man who is used to black-and-white. The best way to localize any fault in any electronic equipment is to understand the circuit and apply logical checks to pinpoint a defective component. The really tricky circuits are those that have a dual purpose, and can affect several others.

The sound trapping in color sets is more elaborate than in black-and-white, so there often isn't enough sound signal at the output of the video detector to use the conventional sound takeoff found in black-and-white sets. An additional detector circuit is used.

A typical dual detection system is shown in Fig. 1. It is used in the Admiral color chassis D11, 1D11, 2D11, etc. Here the 6JC6 third pix i.f. feeds two diodes as shown. The sound detector mixes the sound i.f. and video carriers, and heterodyning produces the 4.5-mc sound i.f. signal. The video detector demodulates the picture signal but at the same time does what it does in a black-and-white receiver—that is, produce a 4.5-mc signal. The sound signal is then trapped out completely before

it can reach the first video amplifier stage.

Because we have two diode detector circuits here instead of the single one used in black-and-white, possibility of trouble is doubled. Note that the sound detector also supplies the signals for the sync-separator and agc systems. Hence, defects in the sound detector circuit will also affect sync and gain control.

With no sound (but with picture) the usual continuity and component checks used for black-and-white receivers are a good start. The 10,000-ohm resistor shunting the diode detector is its load resistor and you can connect a scope there to check for a signal. (Don't expect to find audio here—only the 4.5-mc i.f. signal, which must still be amplified and detected later.) Check for a leaky coupling capacitor between the plate of the 6JC6 and the crystal diode. A voltage leak can affect detector operation and kill the sound.

Note the adjustable traps in the video detector circuit. The coupling transformer from the 6JC6 to the video detector is also a 43.8-mc resonant circuit—part of the overall i.f. tuning system. Above this is the 41.25-mc sound i.f. trap, and an additional sound-rejection potentiometer is used in this

input circuit. A 4.5-mc sound i.f. trap is also included.

Thus, when interference bars show up on the screen (and vary with the audio), the sound traps should be adjusted slightly. If the traps haven't been tampered with, and were correctly adjusted originally, not much retuning should be necessary. Try adjusting the 41.25-mc trap first. If there are still some faint interference lines, adjust the 4.5-mc trap.

If drastic readjustments are necessary (or if tuning doesn't eliminate the interference), check components. Substitute a new video crystal diode when troubles occur. Lack of video (but sound OK) localizes the trouble to the video detector circuit, or the stages after it. (Presumably, if there is sound, all stages before the dual detection system are OK.)

An oscilloscope check for signals at the grids of the two video amplifier stages will help pinpoint the stage that's giving trouble. If the fault seems to be in the dual detector system, remember how the third pix i.f. feeds both detector systems. Trouble in one circuit can influence the other.

Shorted or defective parts in one detector system will often reduce effi-

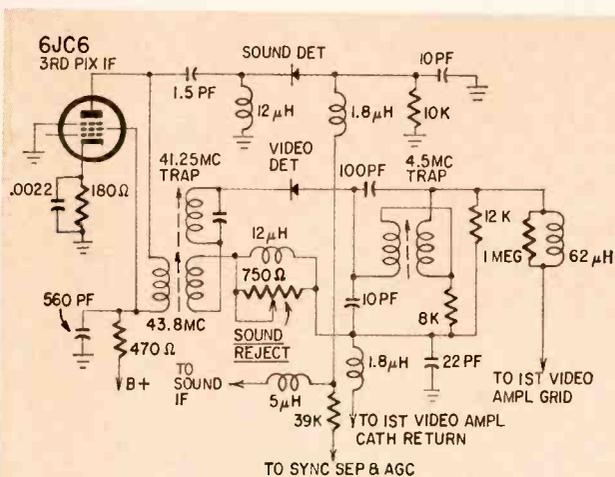


Fig. 1—Dual detectors in Admiral chassis—one for video, one for sound.

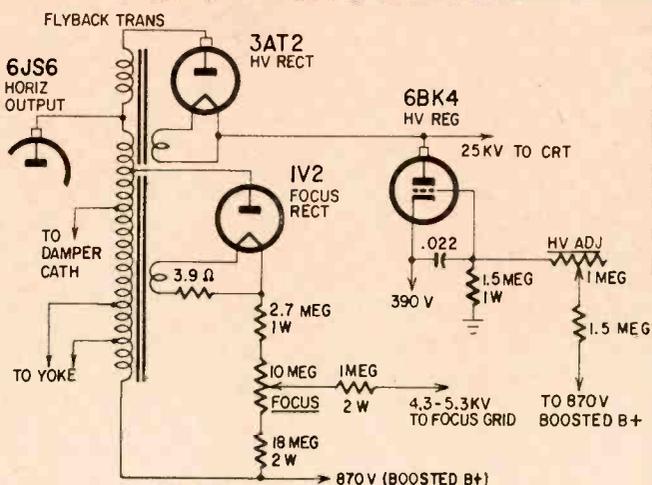


Fig. 2—Focus and high-voltage rectifiers in Zenith 25MC30 chassis.

ciency in the other. Thus, a leaky coupling capacitor in the sound detector circuit could reduce sound output (or produce distorted sound) and also reduce picture contrast. Also, a weak third pix i.f. tube will affect both picture and sound. Because the third pix i.f. feeds two detector systems, both low impedance, its gain is not as high as that of the first and second video i.f. stages, and any decline in performance shows up immediately at the detectors.

### Focus rectifier and HV regulator

Another circuit in color receivers with a dual function compared to black-and-white sets is the high-voltage system, which most cases includes a focus rectifier to generate a separate 5,000 volts for the focus electrode of the picture tube. There is usually also a shunt regulator for more precise control of the high voltage for the pix tube.

A typical high-voltage system used in the Zenith 25MC30 is shown in Fig. 2. The focus rectifier does the same thing as the high-voltage rectifier, except that its anode is tapped off at a lower-potential point on the horizontal output transformer as shown. A 10-megohm focus control adjusts picture-tube focus.


The shunt regulator is a variable load on the high voltage and tends to keep the output voltage constant, once it has been set by the 1-meg high-voltage-adjust pot. The circuit is designed so that the grid bias for the shunt regulator changes with changes in high voltage. If the high voltage increases, the grid bias decreases and the shunt regulator conducts more heavily. Then it imposes a greater load on the high voltage and reduces it. If the high-voltage decreases, the bias on the regulator increases (goes more negative) and the tube conducts less; thus the load is decreased and high voltage goes up.

Special high-voltage probes must be used here to set voltages to the levels recommended by the manufacturer. If you don't get the right voltages, check tubes by substitution before doing anything else. Next, check resistor values around the adjusting pots. Occasionally a resistor will increase considerably in value. As in all high-voltage compartments, check for arcing. Clean the terminals, avoid sharp bends in the wiring, and cut away pointed pieces of solder. Make sure the damper tube is functioning properly, because it can affect both the focus voltage and the high voltage.

### Scope patterns

When you use a scope for signal observation and testing, be careful not to assume that the same signal waveform exists at all points fed from a common point. This is another tricky aspect of

Fig. 3—Sync feed in RCA CTC16. Waveforms at the three test-points are not the same.

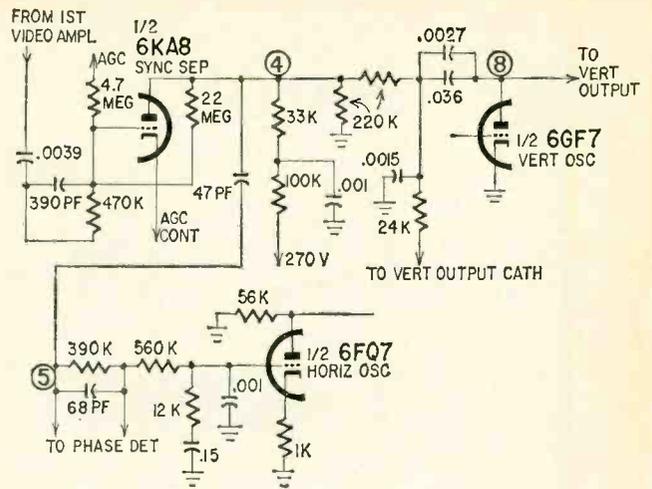

trouble shooting often overlooked. Take, for instance, the sync separator and oscillator sections shown in Fig. 3. It would appear that a scope signal at test point 4 on the schematic would look about the same as that at 5, since this is the same feed line with only a 47-pf coupling capacitor between. Similarly, it would seem that the same signal should appear at test-point 8, since it too is fed from test point 4.

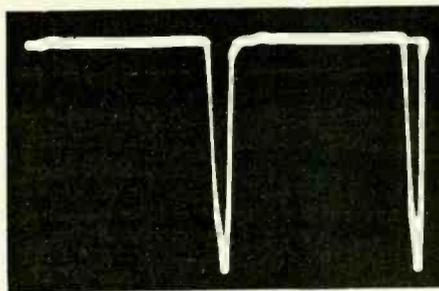


Fig. 4—Waveform at test-point 4 in Fig. 3 (60 volts peak-to-peak).

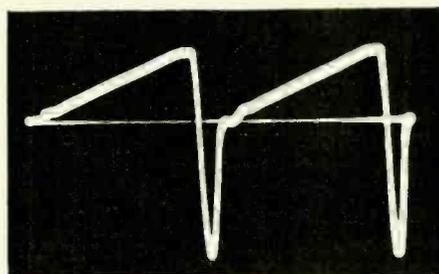


Fig. 5—Waveform at test-point 5 in Fig. 3 (20 volts peak-to-peak).

Actually, however, the waveform at point 4 consists of inverted sync pulses as shown in Fig. 4, but at test point 5 the waveform is a typical relaxation-oscillator type (Fig. 5). At point 4 the peak-to-peak voltage is 60, while at point 5 it is 20. At point 8 the same waveform shown in Fig. 5 will be observed, except that the peak-to-peak voltage is 185, as indicated in the service

schematic for this RCA CTC16. Incorrect waveshapes and voltages localize a defective stage immediately. Once the defective stage has been found, the same procedures apply to color receiver circuits as to black-and-white. First test tubes, then components and voltages.

The same basic principles apply to other sections of color receivers. And for circuits virtually identical to black-and-white designs, the same testing procedures apply. For circuits exclusive to color receivers, additional equipment may be necessary (color dot-bar generators, etc.). Signal tracing, scope-pattern observation, and voltage and component testing all follow familiar lines. Take a little extra care, and you'll have no trouble. END

### SOLDER SUCKER FOR PC BOARDS

Unsoldering components from printed-circuit boards is a beastly nuisance. For occasions when you have a lot of unsoldering to do, get set with this efficient vacuum-cleaner method.

Take an empty plastic squeeze bottle, such as the kind glue comes in (the 1½-oz size), cut off the bottom and about ⅜ inch of the nozzle. Wash the bottle out, peeling any hardened glue off the inside surfaces. Slip the open bottom end over the vacuum-cleaner hose.

The best way to handle the job is to melt the solder with a clean, hot iron until it flows freely, then quickly cover the terminal with the suction nozzle. The air current will draw the solder up into the bottle. If you don't get all the solder the first time, go back again. When the nozzle gets clogged, poke out the solder—it doesn't stick to the plastic. Any solder that gets into the vacuum cleaner will have hardened, and won't do any more harm than the metal filings you normally pick up with it.—*John H. Hughes*

# WE BUILT AN ELECTRONIC ORGAN!

Heath introduces kit version of Thomas all-transistor electronic organ

By **FRED SHUNAMAN**  
MANAGING EDITOR



BUILD AN ORGAN? THE IDEA SOUNDED tempting, but would it even be possible? With the literally thousands of connections, the hundreds of chances for error, could a person ever get it straightened out and debugged? Many years of experience as constructor and repairman had taught me a great deal about bugs and debugging, and it seemed incredible that such a complex thing would start immediately after being hooked up and turned on. And the *time!* I remembered spending all my spare evenings during a whole summer on an automatic audio voltmeter, and this looked several times as complex.

I would have given up the idea—

actually I would never have reached it—had I not made the mistake of mentioning it at the dinner table. My 14-year-old daughter was delighted. "Let's build an organ! I'll do the work."

That made it quite a bit easier. I knew that if she would stick to it she could do the soldering. (She had been following kit-assembly instructions on simple pieces of equipment from age 6.) So, after eliciting solemn affirmations of perseverance, we sent away for the kit.


Experience was with me. At least I can boast of having made a lot of the mistakes before. Maybe it wouldn't be necessary to repeat them. When the equipment came—a Heathkit GD-983

—every bit of packing was gone over carefully, then religiously saved in the basement against the day we should put the organ into operation. Evelyn and Margery—ages 9 and 6—claimed the big box. It was dedicated as a summer playhouse.

The precautions paid off. A few items were missing, but were turned up as soon as they could be identified properly. But the biggest single unit, the distribution circuit board, was not to be found. Before writing to complain, however, we took one last careful look through all the packing, and sure enough, between two sheets of cardboard which together made a piece just the same size and shape as several other padding strips, we found the slim board. Three keys were also missing, but they had dropped behind some of the equipment and were wedged against a bookcase in the living room. The precaution of not sweeping the livingroom during the assembly period had also paid off!

Wiring went on in a strangely uneventful way. A few things puzzled us for a time, but further progress straightened them out. Every time we guessed, we guessed right. I found no errors in the instruction book. (This is a bit strange, because Heath assured me there were a few. However, it is sometimes as easy to pass over a mistake when the right way is obvious as it is to make an error when the instructions are correct and explicit.)

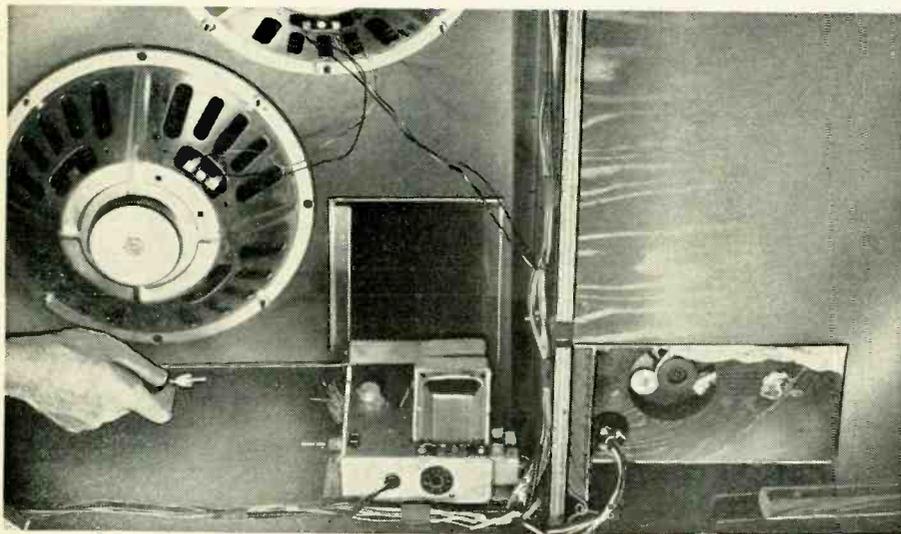A little slip of paper mentioned a 220-ohm resistor that wasn't on the parts list and urged us not to be puzzled about it, but there was no mention of a missing 10,000-ohm resistor—maybe it



Almost ready to go . . . connecting audio signal lead to power amplifier. Heath organ, a kit version of Thomas Coronado BL-3, has two 12-inch main speakers and a two-speed Leslie rotating speaker system, for chorus, celeste and vibrato effects.


was something else that went out in the packing. And we were terribly startled to have a transistor left over. However, well along in the book we discovered that an extra transistor had been packed, so that straightened itself out.

One other slight difficulty was home-made. We were working 1 hour every evening during the week, and put in as much time as possible over weekends. To make more efficient use of our time, we split our efforts—and consequently the book. After a while it became rather difficult to get the pages in sequence and to find out exactly what we had to do next.

But we triumphed over all these things. Just a little more than a month from the time the equipment arrived, we came to the instruction "Turn the organ on." We did—and got a beautiful sync buzz from the amplifier. Turning it off quickly for fear that overload might blow the output transistors, we checked wiring and joints. Two joints that were not soldered at all, and three that looked dubious, were resoldered.

We put the amplifier back again, but the buzz continued. Tried the expression pedal (volume control). It had no effect. In desperation I used the old radioman's remedy—a sharp blow to the transformer with the flat of the hand. It worked—temporarily—but there was still no sound. We went through circuitry until we were interrupted by smoke rising from the 15-ohm resistor in the circuit to the swell keyboard. It had 15 volts on one side of it, and was supposed to have about the same on the other. Unfortunately, the voltage on the other side was zero.

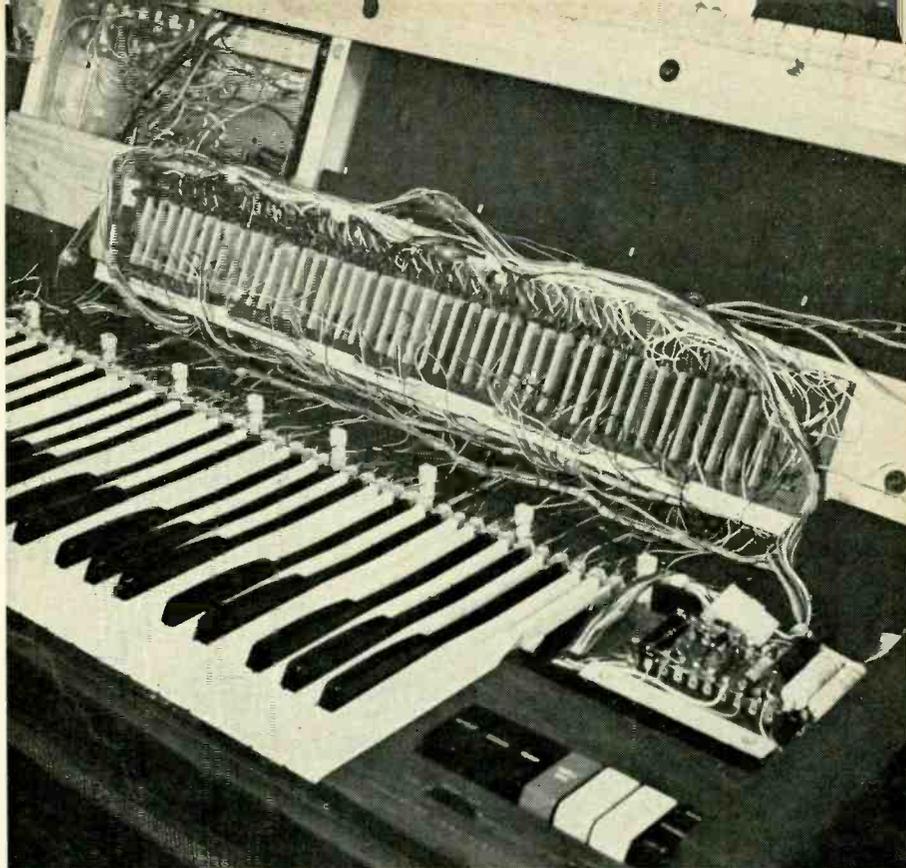I was a bit afraid of using ohmmeters on circuits containing transistors, but I dug up an ancient volt-ohm-milliammeter with a shunt type low-volts range made by shorting the ordinary ohmmeter terminals, and connecting the probes directly across the meter.



*Keying filters on long factory-assembled printed-circuit board occupy space between manuals. (Upper manual is shown tilted back.) Wiring is orderly and systematic.*

With the zero adjustment set for full scale, the greatest current that could possibly flow was 1.5 ma.


The multimeter showed a solid ground on the swell keyboard. Tracing the leads down, I found a washer-head bolt screwed down firmly on top of the bare 15-volt lead that ran along the back of the swell-manual frame. Releasing it made everything normal, and we went ahead, up to the point where the instruction "Press any key near the middle of the great keyboard" started us playing the organ. It worked. We couldn't resist pressing all the other keys, in spite of the fact that this test was not

supposed to come for another page or two, and found that everything produced good sound.

Following through with a series of tests as instructed, we found that the SUSTAIN tab killed everything. Ohmmeter checks showed a 15-volt circuit grounded. We carefully traced the ground down to the big swell-circuit distribution board. I had a vision of a shorted diode among the 160 or so on that board.

It was Friday evening, so we decided to leave that job until the next morning. Unscrewing the board and turning it over, we started with the input strip, which ran along the lower edge of the board. Following it down about two-thirds of the way, and looking at each point in turn, we discovered a small solder bridge—a thin thread that was actually above the board rather than on it. A touch of the soldering tip and everything checked normal. It sounded normal, too, when we put the board back again and tried it out. Meantime, the buzz had started up again in the amplifier, and we had to quit everything to attend to it.

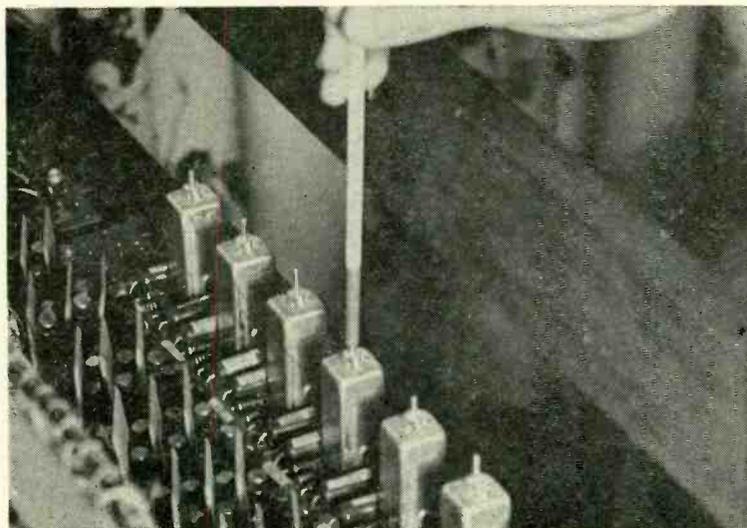
The amplifier trouble showed us something about soldering transistor circuits. Old radio and TV technicians have run into many instances of sets that have developed intermittents or absolute opens after years of use, and have cured the trouble with a soldering iron on a dry or rosin-insulated joint. The marvel has always been that the set would work so long without giving trouble. No tech-



*After check-out comes tuning. Step-by-step instructions according to an ingenious method make it easy for anyone. No musical or electronic skill is required.*




# WHAT'S NEW

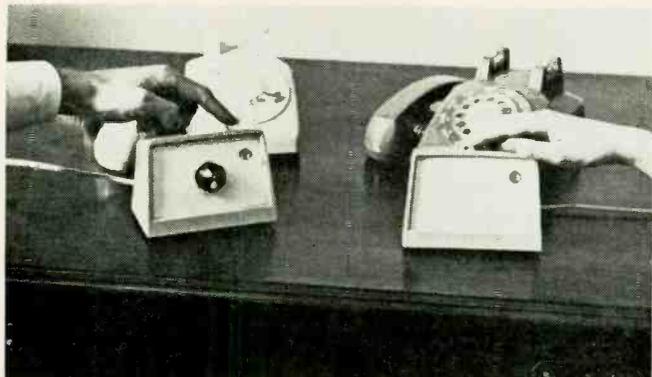

**SENSICALL** permits deaf people to use telephone by sight or touch. Deaf people who can see can use one kind of Sensicall—the kind that has a light that blinks in time with impulses on the line. Deaf-blind persons can use a kind with a vibrating button, which they must touch. Person at other end of line “talks” by humming, tapping or whistling to make Morse or other code symbols. Users of either kind can easily learn to distinguish between dial, ringing and busy tones. Device was developed by New York Telephone Co.

**STREAMERS OF LIGHT** graced opening of 1966 Shipstads & Johnson Ice Follies. They're made of Sylvania Tape-Lite flexible electroluminescent ribbon. Excited with ac, tape glows with light ranging from green to blue, depending on frequency. Performers carry self-contained battery-powered inverter, making them independent of external power and free to move any distance. Changes in color and intensity are possible via elaborate radio remote control.

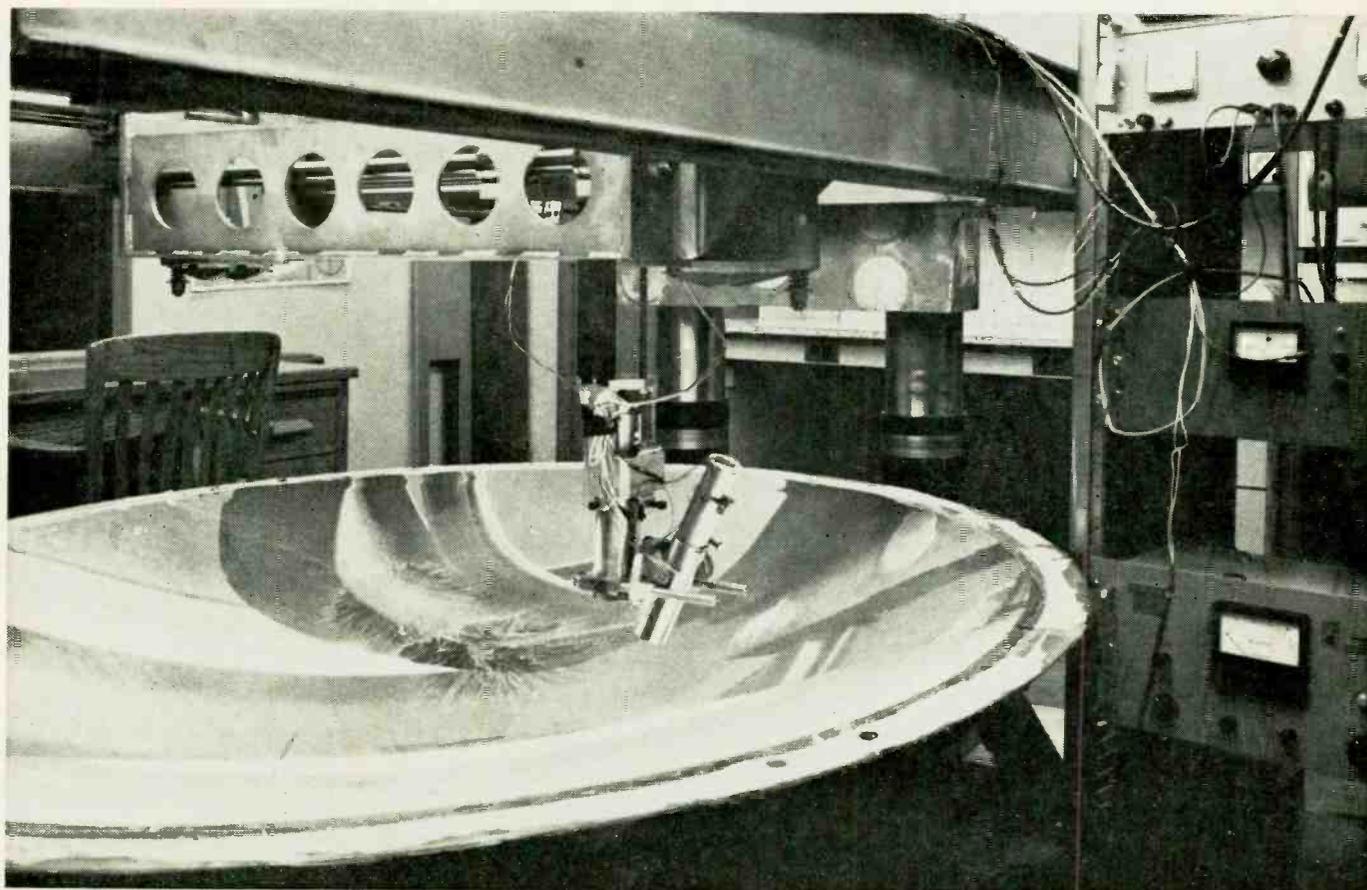

**PRECISE MEASURING WITHOUT TOUCHING** is the specialty of this device developed by the Boeing Co. for gaging accuracy of extremely fine-finished parabolic mirrors that would be scratched by ordinary instruments. Electro-optical scanner moves above mirror. One of its units projects pinpoint of light, which is reflected into second unit. Servomotors work to keep reflected light centered in prism, and their motions are recorded as variations in surface contour.



# THE BUSY-BOX:

## A Thinking Tot's Toy

Build your kids a Christmas toy that does things

By JOHN A. TISO

HOW MANY TIMES HAVE YOU BOUGHT a new toy for the baby or some young friend, only to have it join a host of dust-covered predecessors in the closet after a few hours of use? "Too many times!" you say? Don't despair, you've plenty of company. Young children have a very short span of interest, and, with added competition these days from TV, a new toy just doesn't have the kick it used to have.


and 16 No. 112 miniature lamps, connected in parallel from each pole of S1 to the common side of the 1½-volt battery supply. Note that only 16 of S1's 17 poles are used. Switch S2 is included so the circuit can be turned off, conserving batteries and bulbs.

Circuit B includes the telephone dial, paralleled by pushbutton switch S3 (clown's nose), the buzzer, and the miniature No. 136 lamps (PL17, PL18)

Circuit C is simply the music-box movement wired in series with pushbutton switch S4 and a 1½-volt battery. Use the right polarity here, since the motor must turn in the correct direction.
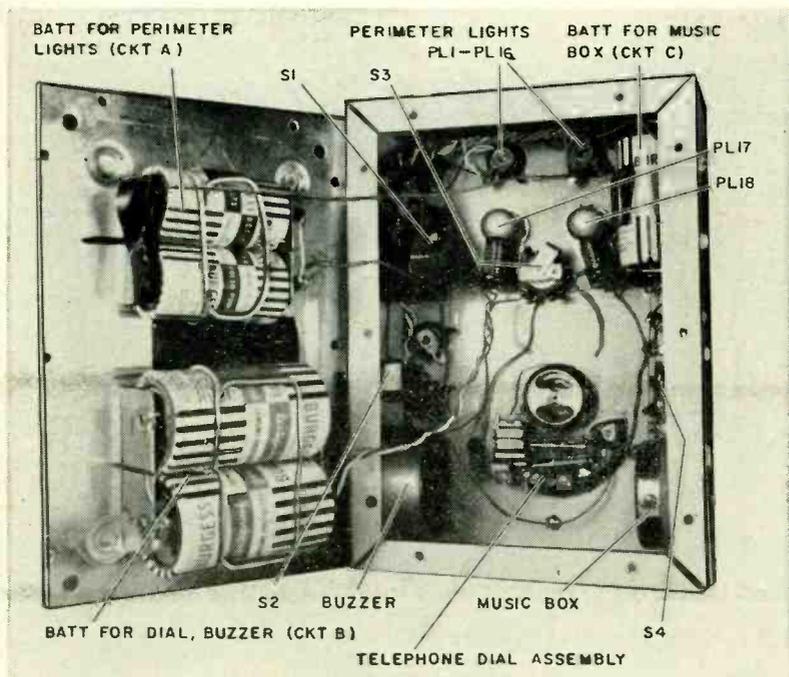
### Construction

It's smart to acquire all the parts before starting. Begin by laying out and drilling all the holes in the aluminum chassis box. Follow the drawing in Fig. 2 as closely as possible—some clearances are tight. Notice that the drawing does not show the exact hole sizes and locations for all the components; because of possible slight variations. The cutout for the telephone dial is an irregular shape,



Inside, the box is crowded, but a little care in planning will insure success.

The Busy Box is different. It's rugged, has lots of variety and, while primarily intended for 2- or 3-year-old, will also attract the attention of older youngsters. You'll see this toy used and enjoyed long after the other trinkets have bit the dust.

The Busy Box consists of three separate, simple switching circuits, each with its own power supply for maximum battery life.

Circuit A (Fig. 1) is made up of rotary switch S1 in series with toggle S2,

for the clown's eyes. Use the 3-volt buzzer specified in the parts list, since imported types were found to be unreliable.

You may have to spend a couple of minutes to determine which terminals to use on the telephone dial. With the dial at rest, the circuit should be open. When a number is dialed, the circuit should close, and, as the dial is released and spins back to rest, the contacts will open and close intermittently. This will make the eyes "blink" accompanied by a series of short "beeps" from the buzzer.

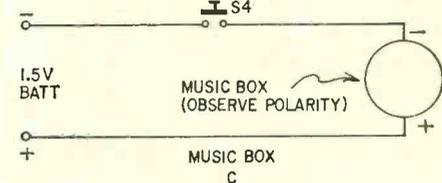
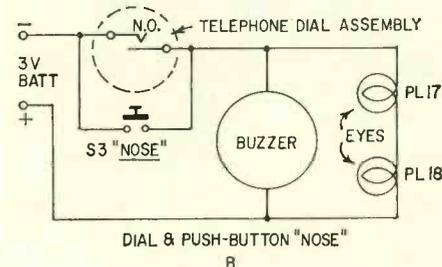
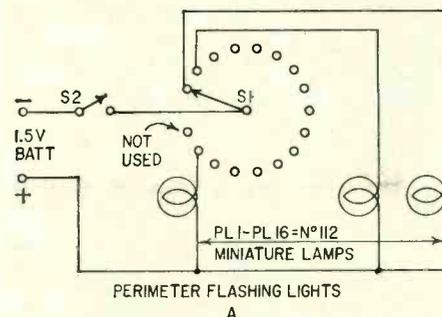


Fig. 1—Busy-Box is made of three separate, simple circuits. Complete details are given in the text.

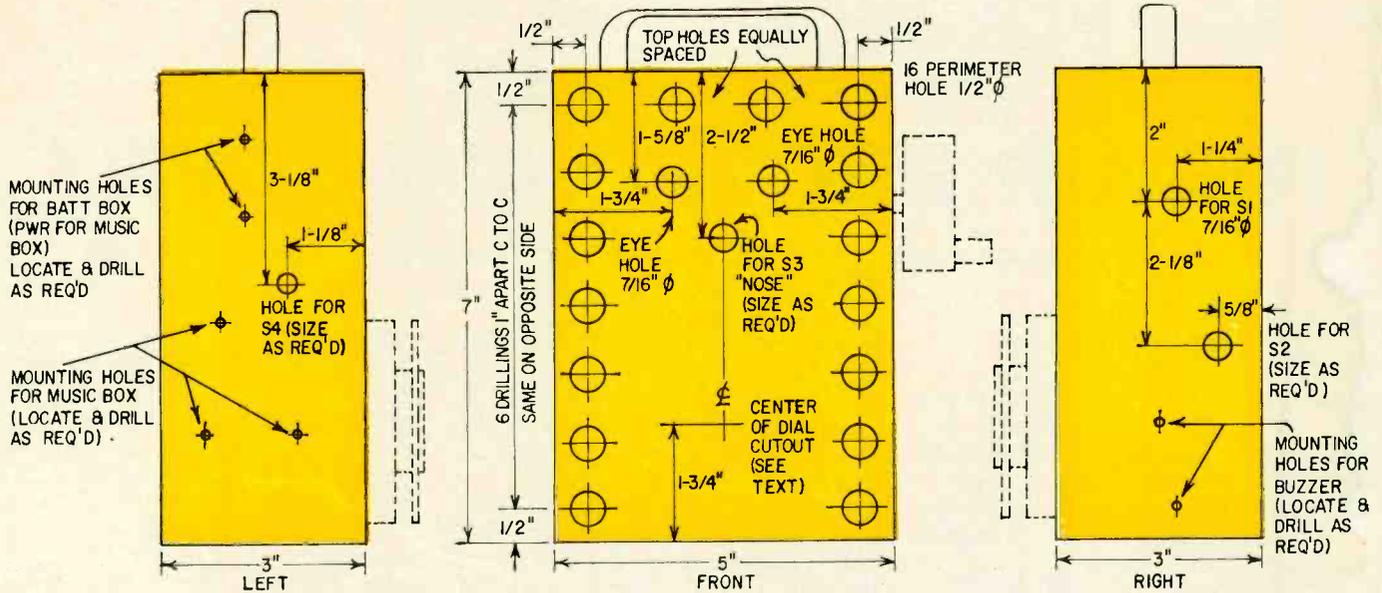


Fig. 2—How to lay out the chassis box. Exact hole sizes and positions depend on particular parts used. Better have them on hand before you pick up the drill!

and will depend on the particular unit you buy. The best way to cut it is to make a trial-and-error template from thin cardboard. Make sure the cutout clears all moving parts of the dial, and locate the mounting holes accurately. Transfer this layout to the aluminum box, then drill and cut.

The miniature lamp sockets around the perimeter of the box are mounted by force-fit in the rubber grommets. Therefore, make the holes for these grommets carefully, to insure a tight fit. As shown in the photograph, two of the battery boxes are mounted on the inside of the rear cover. Be especially careful when locating these boxes so they will not interfere with other parts when the cover is put on.

Smooth all rough edges, and make a trial assembly of the components. With any kind of luck, they will all fit perfectly. OK? Now, remove everything

from the chassis box, and you're ready for finishing.

Spray on a couple of coats of enamel or lacquer (don't forget the screw heads which will show), and let dry thoroughly. Next, paint the clown's face. You don't need much talent to do this; a clown's face is supposed to be funny. But, if you're chicken, you can probably find a suitable decal transfer at the local hardware store.



18-month-old Marilyn Tiso, busy discovering the secrets of the Busy-Box.

When the paint is completely dry, you can start final assembly. Put the handle on first, then mount all the parts on the face of the box. The miniature sockets for the perimeter lamps PL1-PL16 are forced into the rubber grommets after the grommets have been installed. A little rubber cement will make this operation easier, and hold the sockets firm. Now wire the "common" lugs for these lamps together, and bring out a lead to be connected later to the batteries on the rear cover.

Rotary switch S1 comes next. It must be wired before being installed. Multiple-conductor telephone cable is good for this, since the wires are very

thin and color-coded. The switch on the unit shown here was wired for consecutive operation, so that the lights create a rotating effect, but a random pattern might be even better. However you decide, cut each lead to approximate length, and twist the resulting bundle of wires tightly together. Bring a lead out from the fixed or "hot" pole, to be connected later to switch S2. Now mount S1 where shown, and wire the leads from each of the 16 poles to the "hot" lugs of PL1 to PL16. At this stage, push all wiring out of the way into the corners of the chassis, and see that S1 rotates freely.

All the remaining parts on the sides of the box, as well as the battery boxes on the rear cover, can now be installed and wired, following the schematics and photographs. When all wiring is completed, install the batteries, bulbs and spinner knob, and carefully secure the back cover, checking for shorts. Bare No. 16 wire wrapped tightly around the ears of the battery boxes, as shown in the photograph, will keep the batteries from falling out when jarred. The No. 112 miniature lamps are fairly strong but, as an extra precaution, paint each bulb with clear model cement to prevent shattering if broken.

Finally, test the operation. The telephone dial and pushbutton nose should beep the buzzer and blink the eyes; S4 will activate the music box; and, with S2 on, the rotary knob will light the perimeter lamps, one at a time.

After you've had your fun with the Busy Box, offer it to the nearest 2-year-old. You'll be surprised how eagerly it's accepted, and how rapidly its functions are figured out. Your only problem now is how to deal with requests for copies of the Busy Box from relatives and friends. Maybe this wasn't such a good idea after all? END

- PL1-PL16—Sixteen No. 112 miniature lamps with miniature screw-base sockets (Dialco No. 507)
- PL17, PL18—Two No. 136 miniature lamps with panel jewel assemblies (Dialco No. 510-121)
- S1—Daven SP, 17-point rotary switch (Burstein-Applebee 18C503)
- S2—spst toggle switch
- S3, S4—Momentary-contact, normally-open, pushbutton switches
- 3-volt buzzer (E. F. Johnson type 114-400 or equiv.)
- Telephone-dial assembly (available from Radio Shack Corp., Fair Radio Sales, or Olson Electronics)
- Aluminum chassis box 5 x 7 x 3 in., with back cover (bottom)
- Spinner knob for 1/4-in. shaft, 2 3/8 in. dia
- Battery-operated music box movement (Burstein-Applebee 18B166. Not in catalogs but available through 1966)
- 3 C-cell battery boxes
- 6 C-cells
- 16 rubber grommets, 1/2-inch mounting hole
- Handle, wire, hardware
- Burstein-Applebee Co., 1012 McGee St., Kansas City, Mo. 64106
- Radio Shack Corp., 730 Commonwealth Ave., Boston 17, Mass.
- Olson Electronics, Inc., 260 So. Forge St., Akron, Ohio 44308
- Fair Radio Sales Co., 2133 Elida Rd., Lima, Ohio 45802

# REPAIR RECORD CHANGERS

First of two parts—What the mechanism does, and how; what goes wrong, and how to fix it

By HOMER L. DAVIDSON

IT IS NOT EASY — NOR PROFITABLE — TO turn down record changer business. More record changers on the market means more record changer repair. Since hi-fi and stereo have come into their own, we've never seen record changer business so good.

The technician will find most of his work organized into three main divisions—cycling, speed and adjustment. Fig. 1 is a top view of a typical record

changer, and Fig. 2 shows its underside. When the function control is set at automatic (AUT), speed control at 33 $\frac{1}{3}$  rpm and the reject arm triggered, the changer starts to go through its cycle.

Let's load the changer. Lift the stabilizer arm and place a stack of 12-inch records on the spindle. Pull the arm over on the records and let it rest on them. (Do not pull the stabilizer arm up by its free end, but lift near the back post.) If the arm is hard to pull up or moves jerkily, rub some light oil on its shaft

with a cloth.

With the control knob in automatic position, trip the reject button. Underneath, the linkage (Fig. 2) moves the on-off switch, and the motor starts. The opposite end of the control lever actuates the automatic neutral link detent lever, and this engages the drive wheel. The turntable starts to turn. The flanged end of the control lever strikes the tab end of the trip pawl lever. The lever comes out into the path of a flange that rotates with the turntable hub, starting the cycling gear in motion.

## When it doesn't work

If the changer does not cycle, check for a bent control lever tab, bent trip pawl lever or a dry trip pawl bearing. Sometimes the small trip pawl lever is dry and will not be pushed out far enough to engage the protrusion on the turntable hub. Lubricate with a light machine oil. If the motor does not turn, check the on-off switch with an ohmmeter to see if the contacts are open. One of the small tips or tabs on the switch assembly might also be broken off. Repair of the phono motor itself will be discussed in the next instalment.

As the cycling gear rotates, the cycling slide (Figs. 3 and 4) moves forward. The cycling gear goes through one complete revolution. A lift pin on the pickup arm rises along the lance of the moving cycling slide, causing the pickup arm to lift. When the flat portion of the lance on the cycling slide is past, the arm has finished rising and has also unlatched the shutoff activator and landing lever (Fig. 5). The pickup arm moves toward the record and contacts the pickup arm lever. The feeler (or cycling slide) reaches its full position and now starts the arm for the correct setdown point, according to the record diameter. At this time the pickup arm is free and can go downward. The arm should never be touched when the changer is cycling. When the cycling slide has reached its outermost position, it causes the actuator spring to latch the pickup arm momentarily, until the push-off lever drops another record on the turntable.

The push-off lever activates the push-off finger on the thin spindle and one record falls. The cycling gear is now halfway through its rotation. If the pickup arm moves erratically, check the lift

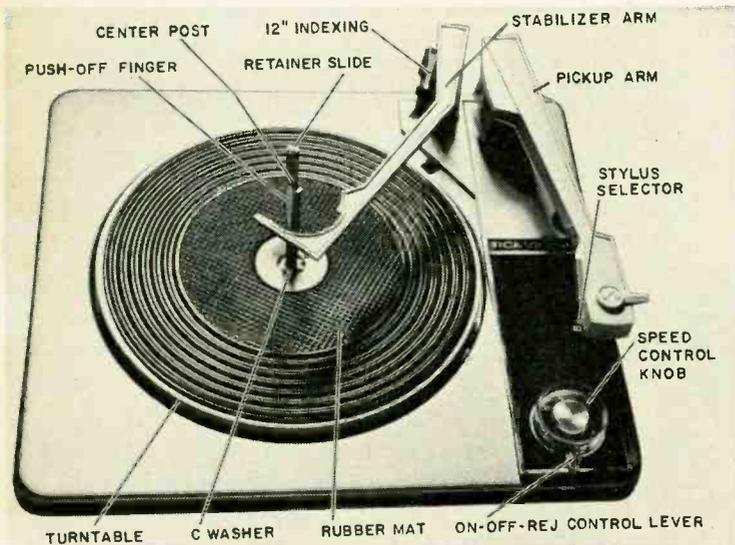


Fig. 1—Principal parts of a record changer above deck.

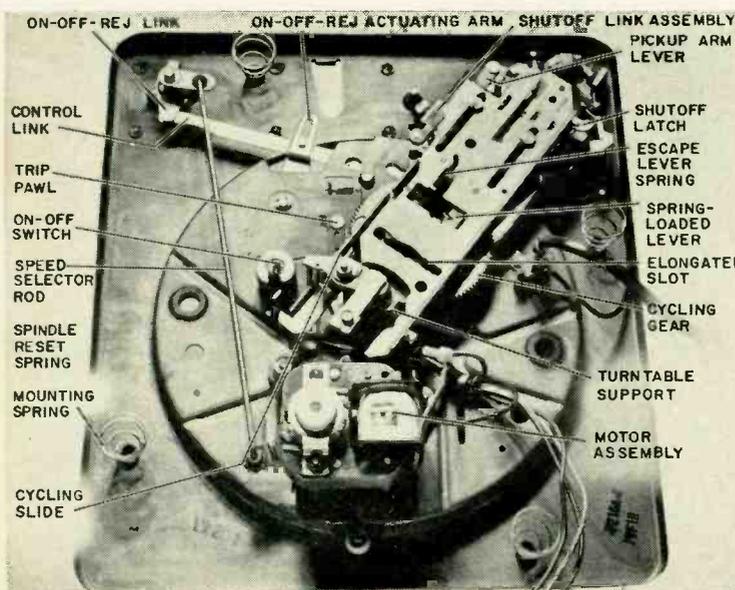


Fig. 2—Proper names for the doodads, thingamajigs and whosises under the base.

pin for dryness and sharp edges.

One of the biggest changer complaints is "all the records fall down on the turntable at once." This is caused by either a pulled-up retainer slide or too-large holes in the records. If the retainer slide is in its correct position, only one record can fall at a time. Sometimes, when the user plays a load of records, he pulls them up along the spindle to load them again for a repeat performance. If they are not pulled clear off the spindle, the retainer slide will be caught and stay up with them. When the reject button is tripped, all the records will be pushed off and down. Demonstrate this when you sell a unit.

The cycling slide starts the rest of the rotation, and the pickup arm follows the landing lever. Spring force moves the landing lever at this time. When the cycling gear has finished one complete revolution, the pickup arm lands at the starting diameter of the chosen record. The lift pin has gone down the small incline and the engagement pawl is reset by striking the casting on the hub of the turntable assembly. Oil on the landing lever and improper height adjustment will cause erratic landing.

The record has now started to play. If the changer keeps tripping and does not play the record, check the clutch lever and trip pawl. On some changers, this trip pawl may stay stuck out if it is bone-dry, causing continuous tripping. The pickup arm may skate across the record grooves and toward the center. Check for a worn needle and improper leveling of the changer. A defective record will do the same thing.

When the last record has been played, most new changers shut themselves off. The cycle starts to repeat and the shut-off latch is forced inward, missing the shut-off lever. The pickup arm lever and the landing lever remain in position. The stabilizer arm shaft drops to the shut-off lever and triggers the on-off switch.

If the changer is loaded with several records and shuts off automatically before playing the last record when the reject button is tripped, check the stabilizer arm shaft. It may be bent, letting the shaft extend down in front of the shut-off lever.

Another complaint is "The arm of my record changer starts over in the middle of the record." You'll always find this condition (perfectly normal) when only one record is on the turntable, the stabilizer arm is not in position, and there is no 12-inch record on the spindle to fall and trip the 12-inch index lever.

In the next installment, we'll talk about speed troubles, drive slippage and motor overhauling, and cover a few simple adjustments you can make quickly.

TO BE CONTINUED

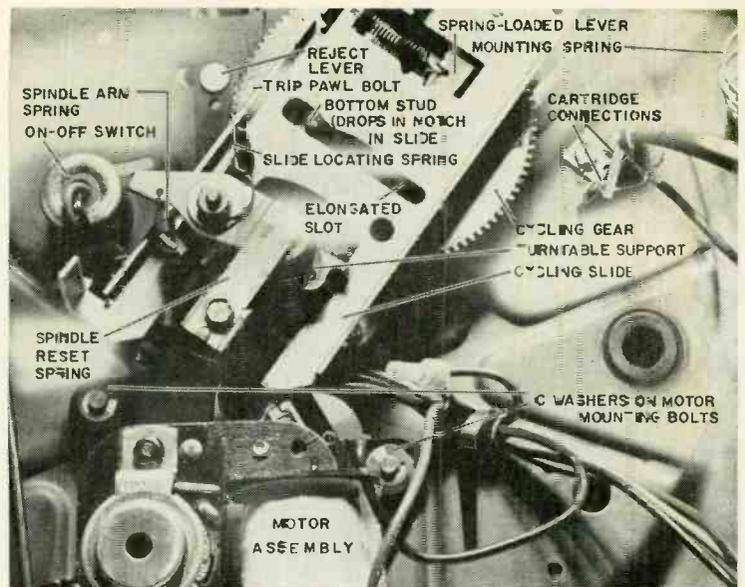


Fig. 3—End of cycling slide near motor.

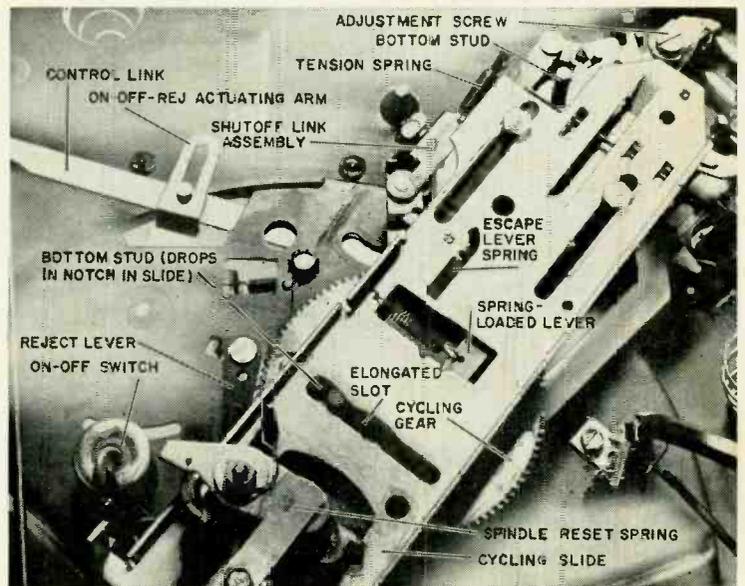


Fig. 4—The cycling slide's other end.



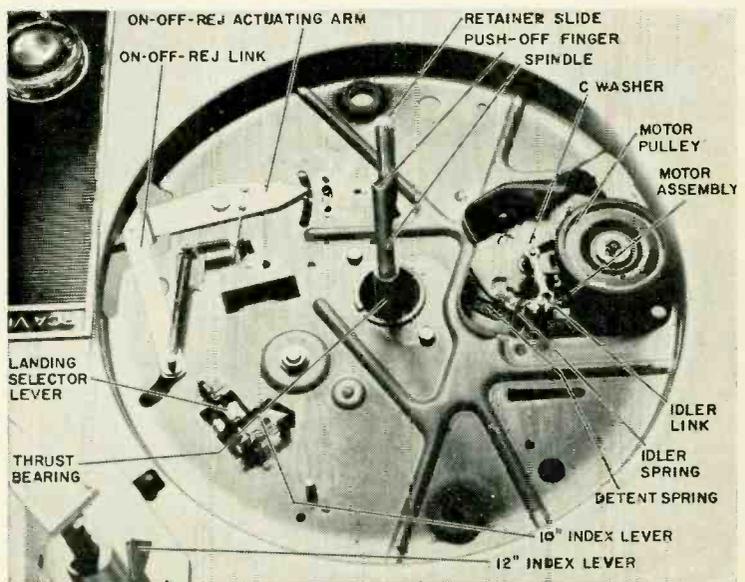


Fig. 5—There are parts even under the turntable.

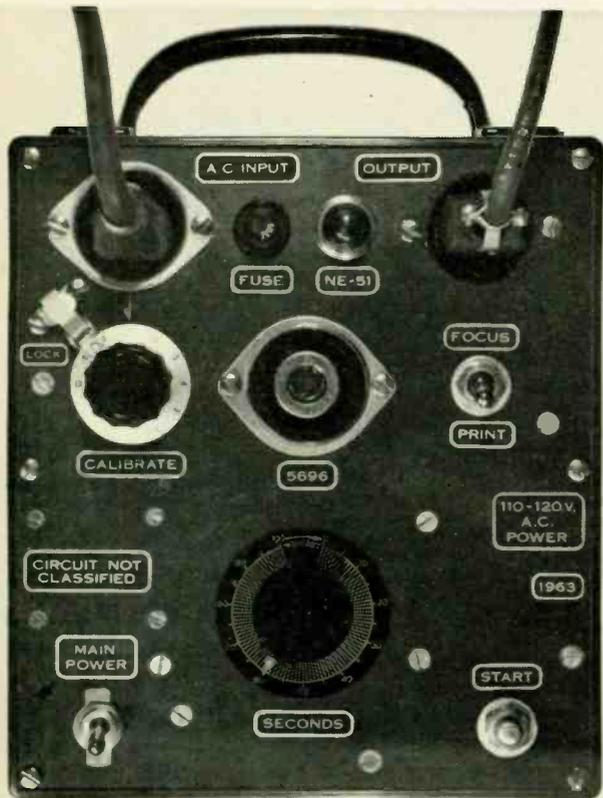

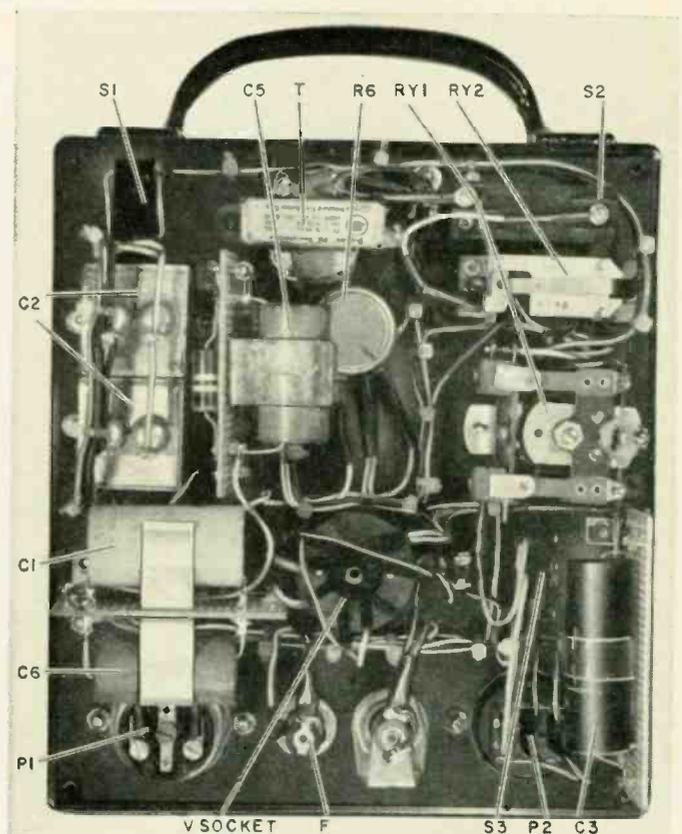In use, timer lies flat with handle toward rear. This keeps controls handy, cords out of the way.



Inside the timer. Layout is compact but not crowded. Major components are called out here.

# De Luxe Printing Timer

Simple, accurate, versatile darkroom timer assures painless prints

By RONALD L. IVES

THE PROBLEM OF TIMING PHOTOGRAPHIC printing processes accurately and consistently has been with us since the days of wet plates and albumen paper. Until recently most printing processes were timed by guess, even though a variety of mechanical and electromechanical printing timers have been marketed. Although some were most ingenious in design, few were widely adopted. In unhappy consequence, few photographers can produce 100 prints all exactly alike without an enormous waste of paper and time.

Two general types of printing timers are commercially available—the kind incorporating an electric clock movement, as does the Gra-Lab; and the type employing a thyatron tube and an electronic delay circuit, such as the popular Heathkit darkroom timer. Recent improvements of the electronic timer have made it most suitable for photographic work<sup>1</sup>, and some changes in the conventional format add to versatility.

It is now possible to build a printing timer, using standard over-the-counter parts, that will time either contact prints or enlargements for intervals from 5 to 85 seconds, with a maximum error of 1 second and with repeatability to within one-fifth second at any setting.

In normal operation there are only two controls—the time setting (SECONDS), and the actuating pushbutton (START). A panel switch is provided to give continuous illumination (FOCUS).

The circuit is shown in Fig. 1. A 5696 computer thyatron is used here, in place of the slightly less expensive and more popular 2D21, because of its lower grid and heater currents.

General formula for the operation of the circuit is—

$$T = 2.303RC \log_{10} (E_n/E_d)$$

Here, T is the time in seconds, R the control resistance in megohms, C the storage capacitance in microfarads,  $E_n$  the calibration voltage, and  $E_d$  the extinction voltage of the thyatron. T/R is a constant, so that time intervals measured are exactly proportional to the set-

ting of R, which is the time setting control SECONDS.

## How it works

When the timer is connected to the line and the power is turned on, the thyatron tube draws current on each positive half cycle, no holdoff voltage being applied at this time. Plate relay buzzing is prevented by shunt capacitor C3. The armature of the plate relay is held down, so that there is no voltage on contact 5 of the output plug. At the same time, storage capacitor C2 is charged from the line through rectifier D1 and calibration potentiometer R2 to a voltage determined by the calibration setting.

When the START pushbutton is depressed, opening the cathode circuit of the thyatron, conduction stops and the armature of the plate relay is released. This puts voltage on contact 5 of the output plug, disconnects the storage capacitor from the calibration voltage supply and connects it into the grid circuit of the thyatron, providing holdoff voltage, so that the tube does not immedi-

<sup>1</sup>R. L. Ives, "Linearizing the Thyatron Timer," *Electronics World*, Vol. 67, No. 5, May 1962, pp. 92-95.



tom. All other parts are entirely standard, and equivalent components of the same grade can be substituted for those specified.

Most of the minor components are mounted on small sections of punched epoxy board (Vector 85G24WE) with push-in terminals (Vector T-28). To prevent strain on the terminals, all capacitors are also held with clips or clamps bolted to the boards. Wiring is cabled at strategic points.

Although most photographers, used to working in total darkness, operate their equipment "Braille", function labels are most desirable. Those used here are Metalphoto, made and applied by the Kohler techniques<sup>2</sup>. Decals can also be used here, if they are protected against wear and dampness by a coating of clear lacquer.

Connection to printer or enlarger will be easier if the external device is equipped with a plug (Cinch-Jones P-306-RP), wired as in Fig. 2, to take care of the specific needs of the device. Such a connector, mounted on a small contact printer, is shown in a photo here.

Connecting cable between timer and printer or enlarger is a good grade six-wire cable with a male connector (Cinch-Jones P-306-CCT) on one end and a female connector (S-306-CCT) on the other. Pin connections are 1—1, 2—2, 3—3, etc. With this method of connection, the same cable will connect printer or enlarger, and transfer of the plug from one to the other automatically also changes the switching functions of the timer.

### Adjustment

When all wiring is completed and checked, insert a fuse in the socket and connect power. Allow the timer to warm up for 15 minutes. Then, with the SECONDS control set at any convenient low value (such as 15), check the operation of the plate relay by pressing the START button and noting if the relay armature releases immediately and pulls in again after a short time (not necessarily 15 seconds). Next check the remote start control by shorting terminals 1 and 2 of the output plug. This should also cause the plate relay to release immediately, and to pull in again after a short time.

Now connect any sort of an indicator, preferably a self-starting electric clock, between terminals 3 and 5 of the output plug. Set the SECONDS control at 30, press the START button and note the time at which the indicator starts. Repeat this process, adjusting the CALIBRATE dial, until the *on* cycle of terminals 3 and 5 is exactly 30 seconds, then lock the calibration dial. Check several times as a safety measure—they will be



*Airequipt "Junior" contact printer, adapted for use with timer by addition of six-contact recessed plug, mounted in aluminum box.*

right on within about 1 second unless you have either a bad misconnection or a defective timing potentiometer (rare trouble).

This completes the routine adjustment of the timer.

Maintaining a timer of this general type is quite simple, as most of the parts are rugged and pretty much immortal. Timing should be checked about every 100 hours of operation, and the tube changed when either the timing drifts badly or the tube is 5,000 hours old, whichever occurs soonest.

Relay contacts should be cleaned (not filed) about every three months, and the relay hinges very sparingly lubricated with a good grade of clock oil at the same time.

With the exception of the thyatron (5696), which has a life somewhat over 5,000 hours in this type of service, all components have an operating life of 5,000,000 or more cycles.

### Performance

This time is one of several built for use in darkrooms where sensitized metal plates are processed. The principal requirement is that plates printed in one production run will exactly match in tone those printed in another production run several months previously. This type of processing calls for rigorous standardization of chemical solutions, uniformity of temperatures, regulation of line voltages for the printing lamps—and standardization of development and printing times.

When used with processes of this type, which are more "particular" than ordinary print processing, this timer is entirely satisfactory in both accuracy and consistency. In ordinary printing and enlarging, it is equally satisfactory, and usually gives good results even with unregulated line voltages. Its timing varies roughly with the logarithm of the supply voltage, making it quite insensitive to ordinary line-voltage fluctuations. END


### CHECK THAT ANTENNA PIGTAIL

*Mobile whip connection can cause erratic transmission or none at all*

If the mobile ham rig or CB transceiver works fine when receiving, but the transmitter won't get out or works erratically, check the little braided pigtail inside the base spring of the antenna (photo). Grab the antenna and bend it over to spread the turns of the spring.

That bit of braid is absolutely necessary in these antennas. Without it, the turns of the spring act as a coil, and the movement of the car changes the inductance continuously! This helps the tuning no end, as you can imagine!

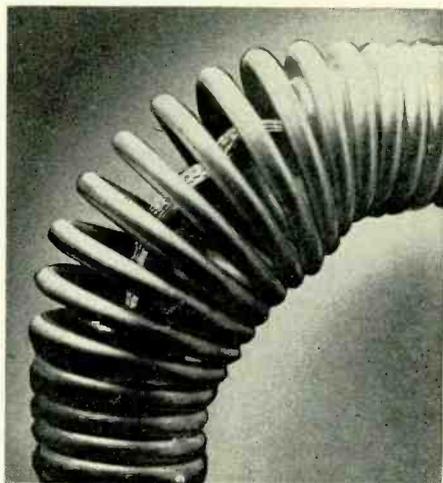To replace a broken pigtail, take the spring off and remove the antenna rod. Clamp one end in a vise and bend the spring over. Some springs have small



Allen (recessed hex-head) setscrews on the side of the end pieces; others have Allen setscrews inside the holes where the antenna rod and base screw into the spring. Remove the setscrews and pull out the old pigtail.

Replace it with a piece of 1/4-inch shielding braid squeezed flat except at the ends. Run just a bit of solder into the ends. Now, thread the ends through the holes from inside the spring. Hold the turns open by inserting a small wooden block in them. Push the end of the braid through the hole, and then run the setscrew down on it; this will flatten it out and hold it tightly.

Make a habit of checking this pigtail every time you get near the antenna, and your transmission will be more reliable. END

### Radio-Electronics Is Your Magazine!

Tell us what you want to see in it. Your suggestions may make it a better magazine for the rest of the readers as well as yourself. Write to the Editor, RADIO-ELECTRONICS, 154 West 14th St., New York 10011.

<sup>2</sup>G. M. Kohler, "Photography Makes Custom Labels" *Electronics*, Vol. 33, No. 1, Jan. 1, 1960, p. 100 et seq.

# The Factory Analyzer

Technical men with this specialty are in critically short supply—the field demands high, pays high

MATHEMATICS CAN PROVE IT IS IMPOSSIBLE to mass-produce TV sets. What's more, with ordinary methods of statistical analysis, the mathematics would be correct! Yet sets are mass-produced every day. There must be an X factor at work that defeats the mathematics. This article is about the X factor.

What is it? Skilled electronics technicians with special training: factory *electronics analyzers*. Except possibly for service technicians, they constitute the largest group of skilled technicians in the country.

Factory analyzers are usually the best paid technicians in every factory, and their take-home pay is increased by considerable overtime. Their work must be done at high speed; they are respected and essential. Depending on the plant and products, top analyzers make from \$6,800 to \$9,000 a year.

Why analyzers? Television and similar devices are by long odds the most complex electronic devices mass-produced. The average unit consists of 300 to 500 parts whose characteristics must be precisely controlled. Failure of one part in 500 results in a reject chassis. One human error results in a reject chassis. Uncontrolled, this would result in such a high percentage of rejects that no manufacturer could afford to build anything.

With careful inspection and quality control, the reject level drops to 0.2%. In any other industry, that would be fabulous. For electronics it is not good enough. It would soon choke a plant with rejects, and halt production.

Let's examine a specific case: a printed-circuit-board line running 100 units per hour. Each board carries 300 parts including jumper wires.

This means that, besides the boards, an average of 30,000 parts per hour must be installed. If the combination of faulty parts and workmanship is 0.2%, it is possible for 60 boards out of 100 to be defective, or 60%! (This figure is high for a number of reasons; the final figure will usually come to 15% to 25%.) Imagine: out of a run of 10,000 TV sets, 2,500 would be sitting around needing repairs!

Which part among the 300 on that board is missing? Which capacitor is open? Which resistor is off value? Which

By CHARLES R. WHEELER

i.f. coil has reversed windings? What combination of parts in a network has tolerance runoff that throws the unit out of engineering limits and results in a poor i.f. curve?

An inspector is helpless with problems like these. Someone must tell the repair department speedily and accurately what part must be changed so production can move.

Without good analyzers an electronics company is faced with these alternatives: price itself out of the market, or go broke.

## An analyzer demonstrates his job

Motorola's enormous new building is on the outskirts of Chicago and is guarded like Fort Knox. I was taken in hand by Bill Mahoney of Public Relations and brought into the factory. The production department is a huge cavern jammed with production lines, conveyors and electrical test equipment. The odor of hot bakelite and resin flux is everywhere.

Thousands of men and women are busily engaged in turning more than a million parts a day into finished TV sets. We pass a TV chassis line. One set a minute rolls off the line for electrical test. And this is only one line—

one operation.

Bill introduces me to John Waycullis, a tall chap with an engaging grin, whose official title is assistant plant manager. He seems to be the focus of an endless number of analyzers and supervisors with problems that won't wait. Finally he settles down for a few minutes and explains the plant analyzing setup.

I asked him if analyzing is a function of inspection or of quality control.

"Neither," he answered. "The system that works best for us seems to be an independent analyzing and electrical test department under one head. But this doesn't mean we don't work closely with the other groups.


"Workmanship is the direct responsibility of the inspection department here, and one function of analyzing is to feed back immediately to inspection any deviations from workmanship standards. Inspection takes it from there and has the problems corrected.


"While parts quality runs high, we always have problems. When you realize the large number of parts per day, supplied by hundreds of outside manufacturers. . . ." I nodded.

"When problems run less than 2% on a given part we handle it as an analyzing function on units in process.

*Motorola analyzer Willard Spivey checks reject TV i.f. board on alignment jig. All connections to board are made automatically through pneumatically actuated contact fingers.*

*Photos by the author*

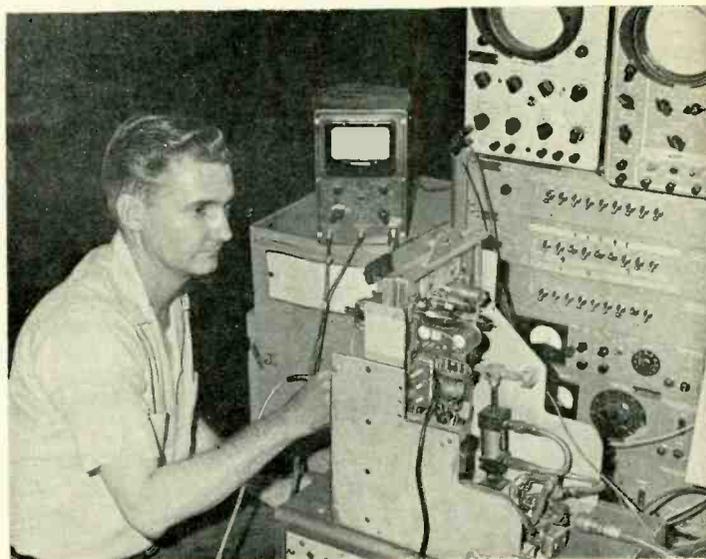

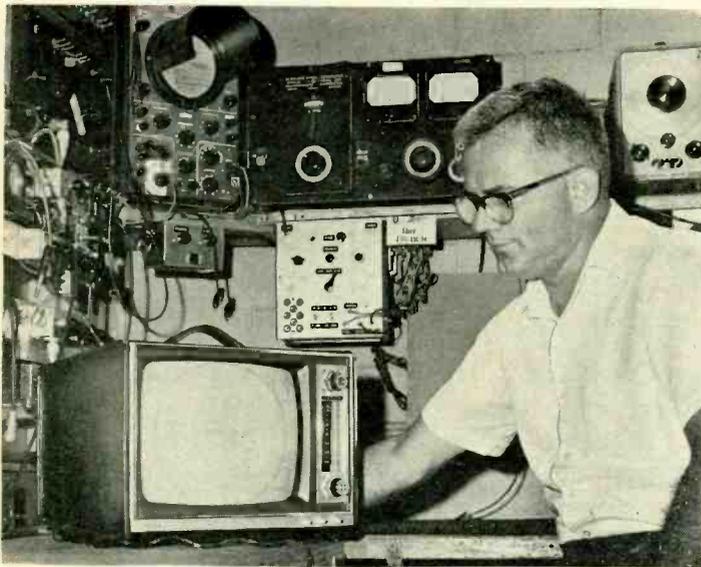

Zenith quality-control analyzer Ray Paluch touches up vertical linearity on model 1290 transistor portable.

This is the cheapest way, because the trouble is usually random or confined to small batches of parts, and tends to correct itself.

"At 2% or up our analyzers will alert us and we get Quality Control on the job immediately. They will 100%-inspect the lots affected or do whatever else they consider necessary.

"Let me take you over to Willard Spivey, one of our ace analyzers. He can show you directly how we operate and let you see some of the operations."

Willard was apparently very busy on the firing line. He was analyzing phasing rejects on an i.f. board fixture. We watched him for a few minutes.

He read the reject tag, glanced briefly at the foil side of the board and slapped it into the fixture to warm up. Meanwhile he checked the top-side parts visually. Then he moved into the affected circuit with a scope and signal-traced to the defective area. After pinpointing, he moved in with the vtvm as a final check. Within 3 to 5 minutes after starting he wrote out the repair tag and bounced the job to Repair.

He picked up another reject. Glancing at the tag, he frowned, then inspected the top of the board. "This is the third board in the last half hour with the wrong capacitor for C104."

Suddenly there was flurry of activity. A supervisor warned the inspector, then went into a huddle with the production supervisor. The production supervisor checked the production operator while the inspection supervisor checked the line from the operator down to the end. Four more bad boards were found and sent to Repair; finally a few wrong capacitors were found mixed in the production operator's bin and cleaned out. A minor crisis was over.

Over coffee in the cafeteria I asked him how he ever got into the analyzing

field.

"I came to Motorola 17 years ago and got a job on auto radios. I saw pretty soon that analyzing was the field for me, but I found it very hard to get in. I studied basic electronics on my own, but it wasn't enough. The analyzing information I needed wasn't in books.

"So I took steps to knock out my daily quota early, then went over to the analyzers and rubber-necked. I gradually caught on, and 3 years later I made analyzer. If what I needed had been in books, I could have made it in one year."

"That's hard for me to understand, Willard. I thought everything could be found in books."

"Many articles written for service techs are invaluable. But the greatest flaw in books and articles from the would-be analyzer's point of view is that they always discuss electronics according to how a circuit *should operate*. What the analyzer needs to know is how a circuit works when it is *defective*."

"It doesn't work."

Willard laughed. "I don't mean that. Let me give you an illustration. You saw the little incident this afternoon involving the wrong-value C104. The first one I saw was on the bench of another analyzer. The video amp was cut off. He was a new man. He said he had a 'sneaker'; would I please take a look at it?"

"Normally V5-a runs 65 volts on the plate, 30 on the screen and -5 on the control grid. The cutoff stage ran plate 145, screen 145 and grid -25 volts. Plate and screen voltages showed that the tube was not conducting. The high negative grid voltage was clearly the reason. A few simple checks then showed that the stage ahead of the detector was oscillating and generating a high negative voltage through the de-

tor, cutting off V5-a. Oscillation was caused by the wrong value of C104.

"This problem was *not* a sneaker. It was a perfectly simple problem we expect an analyzer to solve as fast as any other. In our work speed is essential if we are to meet production schedules.

"Now, here's the point: this man was not dumb. He passed a very stiff test for basic electronic knowledge before he was hired. Yet he had never been taught tube conduction theory thoroughly. Except for men who have worked in other factories, we always have to teach tube theory to new men on the factory floor. This is one major reason why it costs so much to train new men. It also explains why so many fail to make the grade.

"Regardless of how much a new man knows, even where he has had actual servicing experience, he always seems to be weak on tube conduction theory. The same thing goes for transistors. Another weakness is a lack of thorough practical knowledge of Ohm's law. It isn't just three formulas to manipulate arithmetic with on paper. It is an extremely practical tool for the analyzer to obtain rapid answers to problems in defective circuits."

"OK, Willard. What advice can you give to a man interested in analyzing for a living?"

"First, learn the basic electronics taught in schools and books. Then train yourself to be a good visual inspector, sharp at catching wrong parts and hair-line shorts. Get thorough training in using a scope for signal-tracing and pinpointing trouble. Learn to interpret Ohm's law and tube conduction with a thorough mastery of the vtvm. Sprinkle all this with a liberal dose of horse sense and you'll make the grade as an analyzer in any plant in the country."

John Waycuilis had told me that Willard Spivey was always used as lead-off analyzer on major new products. The many projects he had started off at Motorola included the analyzing used for color and transistor TV.

Later that evening I met Willard at his home in Wood Dale near Chicago. He and his wife Jo were planning their vacation trip to Colorado and oiling up their fishing gear. They spanked the kids and sent them off to bed and we settled down for a short visit. I needed a little more personal information about Willard.

While his seniority with Motorola is 17 years, more than 2 of these years were spent as a radio instructor in the Army, at Fort Knox, Camp Pickett and Camp McCoy. He also spent some time in Colorado.

His wife volunteered something Willard hadn't mentioned. In 1955 he started an electronics course at DeVry

Technical Institute in Chicago and achieved the highest grade average the school ever gave: 96.8%.

### Another man's view

Zenith Radio Corp. is another Chicago electronics giant on the far west side. Deep beneath the hurly-burly of production runs the same undercurrent—the need for highly trained technical production personnel.

I met Ray Paluch in the office of Ted Krueger, chief of Zenith quality control. Ray is an analyzer with special duties who works directly for Quality Control. He is specifically charged with liaison between QC and design engineering. In his lab, I asked him in what way liaison between factory and engineering benefited Zenith.

He thought for a moment. "Let's take a hypothetical case," he said. "Assume that a new job is running and production complains that the set breaks into oscillation at a certain stage of alignment. Is the test equipment at fault? Is set design at fault? Is it the man doing the testing? It's my job to find out *what* and *why* in a hurry!

"Remember, engineering specifications are our bible and the set was thoroughly checked before engineering released it. In addition, I myself checked out the first sets as routine before releasing them to Production. So it's my baby!

"The solution to the problem may be changes in alignment procedures or in test equipment. If so, I must see that the changes are made.

"Occasionally, on new models, the design of the set may be involved; some little thing that didn't show up before the production run. First I must prove the cause on my bench to eliminate factory problems. Then I get together with Engineering on the best solution and make up and test samples of the new changes. These are then released to Production."

"Sounds like a good way to work it, Ray," I said. "But you don't have problems like this every day, do you? What is your normal routine?"

"I run electrical checks on five sets a day of every model that runs through Installation. That's enough to catch any tendency in Production or Phasing before it drifts too far from engineering design centers. To save trouble in installation we try to stay well within engineering limits. Steady sampling makes any drift easy to correct.

"Based on what I learn from steady sampling, I also supply production with realistic standards of electrical performance. For instance, Engineering sets the specifications on a job based on a history of past average parts runs. This spec we must meet or we cannot ship to distributors.

"But often it's possible to better

these specs considerably if parts averages permit. We can take advantage of this by setting factory standards higher. However, such decisions take nice judgment. The other face of the coin might involve production stalled at costs of hundreds of dollars an hour.

"In my lab there's a duplicate production alignment setup. No set can run in production if it does not align and meet engineering specs on this equipment. If it is necessary to change factory equipment for a specific model, it will be done."

I nodded. "Ray, how did you get into this line of work?"

He grinned and his eyes twinkled. "My godfather gave me a cat's whisker, a Quaker Oats box and a coil of wire!"

"Are you joking?"

"No, sir. Building my first crystal set started me off and interested me in radio. Later I took a 2-year course in radio at Crane Technical High School in Chicago.

"In 1945 I went to work for Zenith as an engineering stock chaser. Of course, I was a greenie, but was in a good spot to see how engineers tackled design problems. You might say I got to be a very nosy stock chaser. The men taught me a lot.

"During lunch hour we practiced code in the engineering lab, and in 1947 I got my ham license—K9IZZ.

"Shortly afterward I was transferred to Zenith Consumer Products as an electrical repairman. There I got my first chance to practice applied electron-

ics and get analyzing experience.

"My taste of the engineering and analyzing approach made me want more of the same. Ham radio gave me the opportunity to upgrade my knowledge. I became a 'home-brew' artist. Using Q meters, impedance bridges, generators and such in my own design gave me a tremendous advantage over analyzers with only basic theory.

"Many of the projects I designed and built took firsts in ham radio contests, and that gave me an incentive to continue. I directly attribute my first real break at Zenith to my ham radio experience. Forty books couldn't have taught me as much.


"When Zenith Space Command (TV remote control) was under development, I was put in charge of a group of analyzers assigned to that project only. Management felt that my ham radio design background made me the logical choice. This group was in on Space Command from the pilot-run stage all the way to production. The project was a hush-hush first and was quite an experience for all of us."

"Ray, aside from technical knowledge, what one thing will most help a man who tries to become an analyzer?"

"Know the product you are working on. Don't *think* you know it—*know* it! Engrave the schematic and parts layout on your brain! My experience has been that this is the greatest failing of analyzers and would-be analyzers. They do not really take the trouble to know the product." END
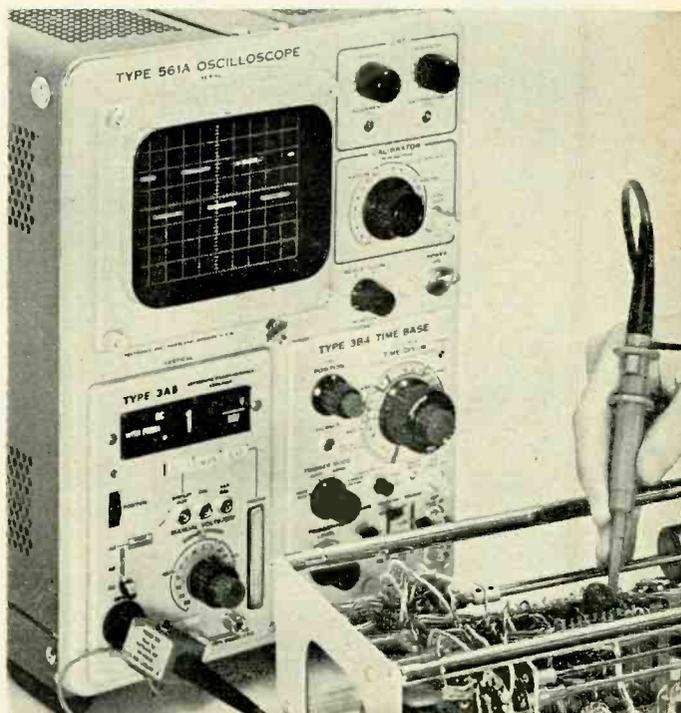
## Scope Plug-In Unit Seeks Range Automatically

**New Tektronix plug-in amplifier** for production-line scopes uses transistor logic circuits to eliminate need for resetting vertical sensitivity where signal voltages vary. Range (volts per division of scope graticule) is read out in window at top of plug-in, while the waveform is shown on the screen. In 100 msec, circuits compare signal amplitude with preset reference. If it exceeds reference, pulse from logic circuits fires ring counter, which trips reed-switch attenuator to next higher range. This continues until display is within preset limit on screen.



# SCOPE IMPROVERS

Make your scope more useful and convenient. Couple of hours and a few parts are all you need

By ELMER C. CARLSON

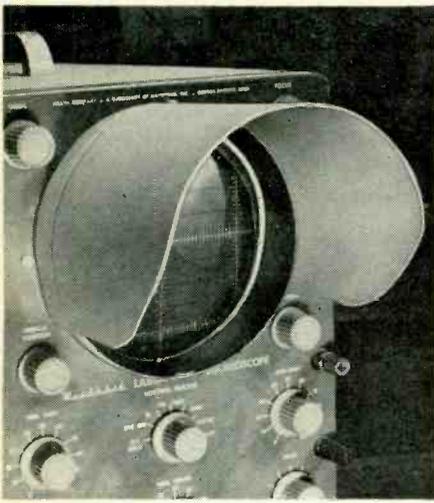


Fig. 1—Light shield over CRT face cuts down glare and confusing reflections.

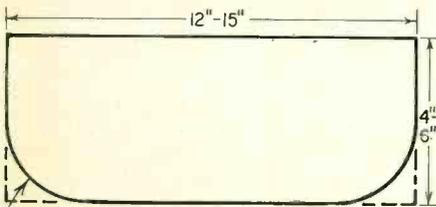


Fig. 2—Sheet metal for light shield of Fig. 1 can be cut quickly with tinsnips.

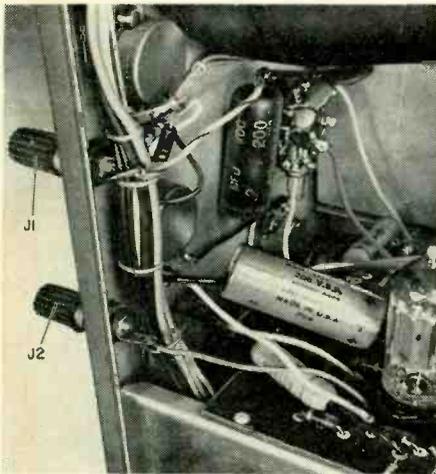


Fig. 3—Two extra binding posts are sawtooth-voltage takeoff point and external capacitance terminal for low sweep frequencies.

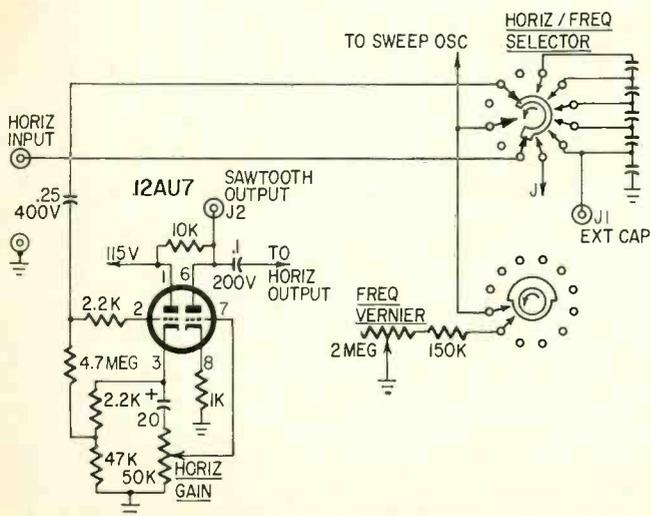


Fig. 4—Partial schematic of horizontal amplifier and sweep frequency selector show where to add binding posts.

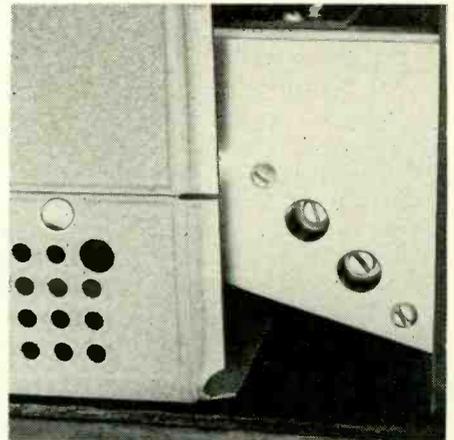


Fig. 5—Holes in cabinet match vertical attenuator compensating trimmers.

too short persistence with sweep speeds near 1 cycle per second.

Some scopes have a terminal available for taking a signal to allow the vertical input step-attenuator trimmers to be checked. Others just indicate a wiring point or tube-socket pin where such a signal can be found. This often means removing the scope from the case.

If the trimmers are not adjustable from the outside of the scope, it might be convenient to drill two small holes (Fig. 5) through the side of the cabinet. Double-check to make sure the holes will line up with the trimmer adjusting screws before you use the drill.

Follow the scope service-manual procedure for adjusting the attenuator trimmers before attempting to adjust the low-capacitance probe trimmer. Proper and improper traces are given in Fig. 6.

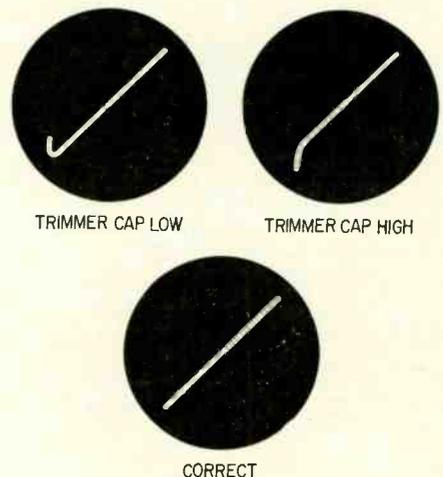


Fig. 6—Sawtooth-against-sawtooth trace checks compensating trimmer adjustment. Follow procedure in scope manual.



# Feedback, Phase & Instability

FEEDING PART OF AN AMPLIFIER'S OUTPUT back to its input out of phase does wonders in reducing distortion and noise and extending frequency response. But it also opens a Pandora's Box of subtleties, which are worth knowing about in some detail if you enjoy designing, modifying, or just understanding high-quality amplifiers.

A feedback loop connected in the most conventional way (Fig. 1) usually contains a phase-compensating capacitor. This is a convenient point at which to make small adjustments in the amplifier's overall response. If the response from input to output is level, then because of the phase-compensating capacitor, the response from the output back to the cathode will have a high-frequency boost (Fig. 2). This means that the loop gain from the grid as input point back to the cathode as feedback insertion point must be given a corresponding high-frequency boost, if the overall response measured externally is to be flat.

In measuring amplifier phase and feedback performance, a very important factor is how the input and output circuits, particularly the latter, are loaded. Change in output loading, from nominal resistance load to open circuit, or to loudspeaker load, either dynamic or electrostatic, can make a tremendous difference to these phase measurements, as well as to the response, as normally measured.

## Loudspeakers

Another realm where we hear quite a bit about phase concerns loudspeakers. Measurements can help here too, and may dispel some of the misstatements one hears.

To check the phasing of different units in a multiway system or of complete loudspeaker systems either on single-channel or stereo, apply a suitable frequency to the input of the system, and use it as a phase reference. For multiway systems, use the crossover frequency, so the two units give out the same relative level. For separate channels use a fairly low frequency to avoid

ambiguity and, in a stereo system, parallel the inputs to give in-phase operation.

Now place the microphone so it is a short distance, and the same distance, from the units being phased (Fig. 3). Switch off each unit in turn to see what the phase angle of the other unit is and thus check that the phase angle of both are in the same region. It may vary by a few degrees between the two units, but the important thing is to see that the phase difference between them is within a few degrees of  $0^\circ$  and not a few degrees of  $180^\circ$ . More about this in a minute.

We sometimes get statements about the phase response of a speaker. This cannot be checked with a microphone because the sound has to travel from the loudspeaker to the microphone, which takes time—an interval which corresponds with a phase angle that is proportional to frequency, and at the high-frequency end is probably many wavelengths (or  $n \times 360^\circ$ ).

The only way to measure the phase performance of the speaker is to use a motion-sensing coil on the diaphragm. A simple way to do this is to cement lightly a turn or two of fine wire out in front of the voice coil, where there will be enough leakage field to indicate direction and phasing of movement by the voltage developed (measured on a scope screen), if not to show the linearity (because the field itself will be nonlinear). With this setup, the phase relation between drive current, or voltage, and voice-coil motion can be measured. Also, a rough indication of the response of the speaker drive mechanism, as distinct from its external acoustic response as measured with a microphone in an anechoic chamber, can be obtained (Fig. 4).

The impedance characteristic of a speaker can be measured, in both magnitude and phase, by a similar technique, by comparing voice-coil current with its terminal voltage. None of these measurements will get beyond a range of  $\pm 90^\circ$ , but phase and magnitude measurements can help in determining

the effectiveness of an enclosure in conforming to theory—for example, how a bass reflex achieves its phase reversal.

## Equipment and method

So much for the phase measurements that can be made and are useful in audio and high-fidelity work. Now for how to make them. A very simple method uses the comparator ellipse on an oscilloscope (Fig. 5). The "reference" voltage is fed into the "horizontal" terminals of the scope, with the switch in the "external" position. The output, or whatever voltage whose phase relation to the reference is required, is connected to the usual "vertical" input.

A line sloping one way represents in-phase condition, while one the other way represents  $180^\circ$ . In between come ellipses, which can best be interpreted for phase by adjusting the deflection so the height is equal to the width (center group of patterns in Fig. 6). The phase can be recognized by identifying it in the family shown in Fig. 6. If the slope is nearer the in-phase line, the reading gives phase angle direct. If the slope is the opposite way, subtract the reading from  $180^\circ$ .

If the oscilloscope method is used for phasing speakers, adjust the distance of the microphone from the speakers to get a line, or approximately a line trace, rather than something near to a circle. Phase reversal from a circle gives another circle. Phase reversal from a sloping line reverses the slope. So the latter readily permits distinguishing  $0^\circ$  from  $180^\circ$ , which the circle does not.

If the device whose phase is measured produces some harmonic distortion, the comparator method also indicates the phase of the harmonics, as well as the fundamental, although precise evaluation of fundamental phase is a little more difficult. To aid in interpreting "odd shapes," Fig. 7 tabulates possibilities with the simpler harmonics.

Another method is to use an electronic switch with a scope so both wave-

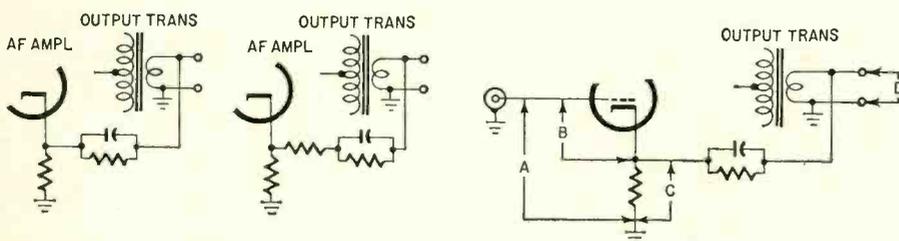


Fig. 1—Different ways in which phase compensating capacitor can be connected in feedback.

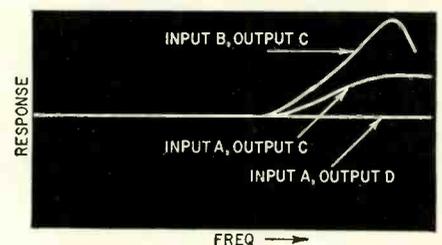


Fig. 2—Why use of a capacitor in feedback means loop gain response must show peaking.

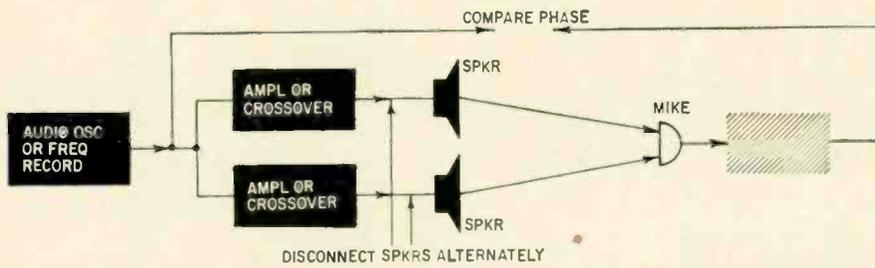


Fig. 3—Using a microphone to check phase of speakers, whether multiway or separate system.

forms can be displayed on the same screen (Fig. 8). Then phase is simply measured as a fraction of the complete wave. If both waves are not pure sine waves, it may be difficult to assess precisely the lateral distance representing phase difference on the scope.

Finally, an even more elaborate device has the advantage of being able to measure phase and give a direct indication. This is done by first converting both waves into square waves by clipping, using a circuit known as an automatic mark-space control to make the top of the square wave equal to the bottom. This works on an ave principle. Finally, the square waves are used to control the current in a "gating" circuit. Current flows only for the part of a cycle during which the square waves are opposite. Thus in-phase square waves give no current—zero phase. Out-of-phase square waves give current for a complete half-cycle—180°. Intermediate readings are proportionate, and a simple integrating meter that reads average current will give a direct read-

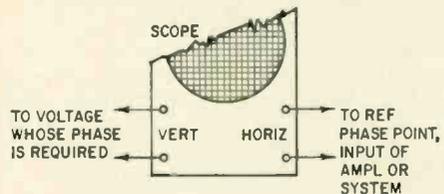


Fig. 5—The oscilloscope comparator method is simple to set up.

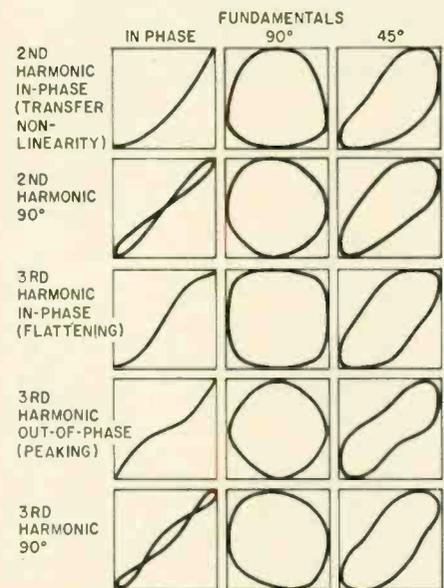


Fig. 6—How phase is indicated using the comparator method.


ing of phase in degrees, independent of frequency (Fig. 9).

One thing should be apparent from this article: phase reading is always relative. You always have to compare the phase of one waveform with that of another of the same frequency related to it. There is no such thing as a 1,000-cycle note coming out of a loudspeaker "out of phase." It has to be out-of-phase with something else. This seems obvious enough, but it is surprising how often one reads or hears a statement about phase without any mention of the reference point. **END**

**References**

H. Nyquist, "Regeneration Theory," *B.S.T.J.*, January 1932.

Fig. 4—Using motion sensing coil on dynamic speaker can provide more detailed information about speaker's performance.

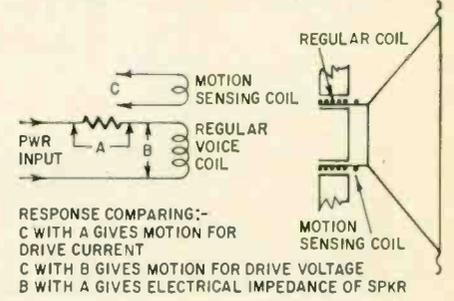

H. W. Bode, *Network Analysis and Feedback Amplifier Design*, D. Van Nostrand, 1945.  
 Norman H. Crowhurst, "Speaker Phasing and Dissociation Effect," *Radio-Electronics*, February 1953.  
 Norman H. Crowhurst, "Oscilloscope Patterns Aid Diagnosis," *Radio-Electronics*, October 1953.  
 Norman H. Crowhurst, "A New Approach to Negative Feedback," *Audio Engineering*, May 1953.  
 F. P. Moss, "An Audio-Frequency Phase Meter," *Electronic Engineering*, August 1954.  
 Norman H. Crowhurst, "Feedback from the Voice Coil," *Radio-Electronics*, October 1956.  
 Norman H. Crowhurst and George Fletcher Cooper, *High-Fidelity Circuit Design*, Gernsback Library, 1956.  
 Joseph Marshall, *Maintaining Hi-Fi Equipment*, Gernsback Library, 1956.  
 Norman H. Crowhurst, "Phase, Feedback and Instability," *Radio-Electronics*, December 1964.

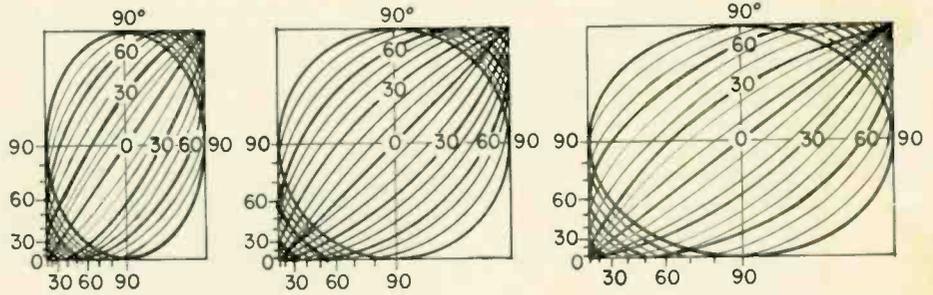


Fig. 7—How presence of harmonics in different phase relationships in output waveform alters trace.

Fig. 8—Method of measuring phase using an electronic switch with a scope.


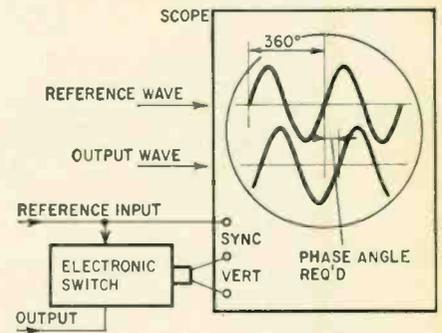


Fig. 9—Operating principle used in direct-reading phase meters.

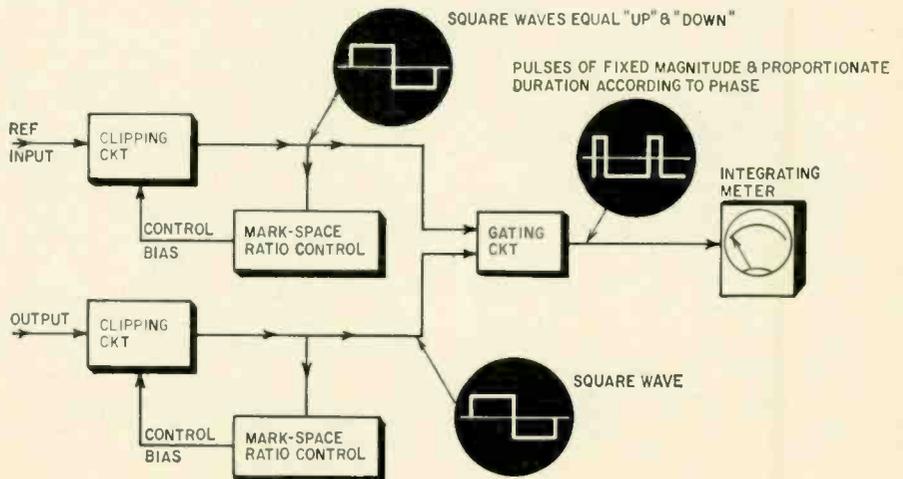

Used in industry and in laboratories all over the world, this vacuum-monitoring tube is much like an ordinary triode

# THE ION GAGE — A Tube Looking for a Vacuum

By T. F. SINCLAIR

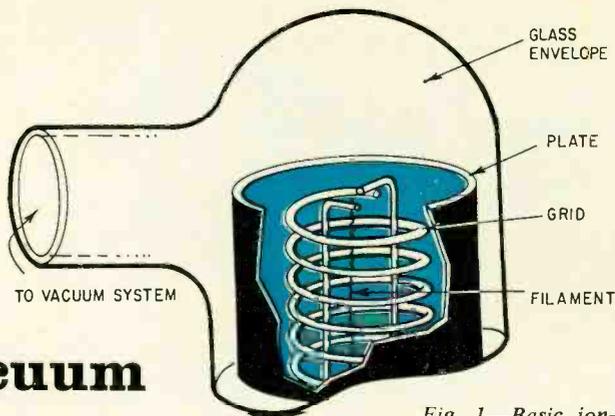


Fig. 1—Basic ion-gage structure.

EVERY SERVICE TECHNICIAN KNOWS the “gassy” electron tube. When a receiving tube partially loses its vacuum, it acquires drastically different operating characteristics and can no longer work properly in its circuit. Substituting a well evacuated replacement cures the trouble.

A not-too-distant cousin of the common electron tube is *designed* to operate in partial vacuums. The resulting changes in its operating characteristics measure very low gas pressures (vacuums). The *hot-filament ionization tube*, more commonly known as the *ion gage*, is an electronic vacuum gage that has been used by vacuum technologists for several decades.

Measuring vacuum has become particularly important in recent years with the growth of industrial vacuum processes. The preparation of ultra-

pure materials for semiconductors and the deposition of thin-film circuits are two important processes carried out in a vacuum. Of course, our tremendous program in space exploration requires producing and measuring extreme vacuums to simulate the conditions of outer space. The ion gage serves as the workhorse of the vacuum industry. Measuring pressures from a millionth of an atmosphere to ones a million times lower again, the ion gage operates over the range most useful to modern technology.

by the grid toward the plate. These fast-moving electrons have a good chance of hitting a gas molecule between the grid and the plate. If an electron and a gas molecule collide, the energy of the impact may cause the molecule to release one of its own electrons. This process is called *ionization* and a molecule stripped of an electron is a positive *ion*.

The number of positive ions formed is directly proportional to the gas pressure in the gage tube. If the plate is maintained at a negative potential, it will collect the positive ions


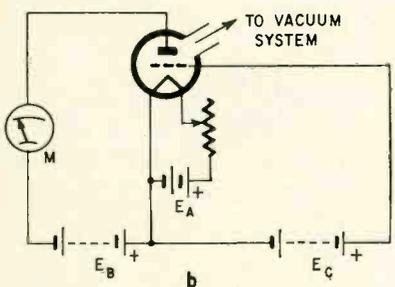


Fig. 2—Simple circuits for measuring vacuum with an ion gage. a—Grid maintained negative. b—Plate maintained negative for greater stability and sensitivity.

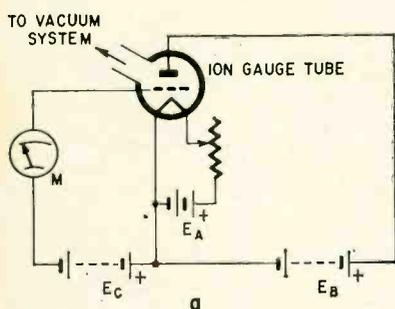

Varian Associates

Ion-gage control unit. Meter is calibrated in pressure and in altitude.

## How it works

The ion gage has much in common with the familiar electron tube. The arrangement of electrodes in the basic gage is very similar to that in a triode electron tube. In fact, early vacuum workers used ordinary triodes as vacuum gages. The ion-gage structure (Fig. 1) consists of a tungsten filament, centrally placed inside a spiral-wound wire grid. The plate is a metal cylinder which surrounds both the filament and the grid. The electrodes are then enclosed in a glass envelope which connects to the system under vacuum.

When the filament is heated, it emits electrons which are accelerated

formed. The ion current which then flows in the circuit is a direct measure of pressure in the gage tube.

## Ion-gage circuits


Two simple circuits which may be used to measure the ion current are shown in Fig. 2. The schematic in Fig. 2-a should be familiar to electronic technicians—it is very similar to a typical triode amplifier. In this arrangement the *grid* is negatively charged and collects the positive ions. Meter M indicates the ion current flowing in the grid circuit and may be calibrated directly in pressure units. Although this hookup is not particularly stable or sensitive,

grid current has been used by electron-tube makers to indicate the pressure in sealed-off vacuum tubes.

A more sensitive gage can be obtained if the *plate* is used as the negative electrode, as in Fig. 2-b. Sensitivities are greater by at least a factor of 2 with this circuit. Ion current flowing in the plate circuit is indicated by meter M. The variable resistor in the filament lead is an emission control. This control is adjusted to maintain a constant current between filament and grid for stable operation. Typical operating potentials would be 150 volts on the grid and -45 on the plate.

These simple circuits bring up several problems. The heater current has to be maintained constant manually in a system where the composition and pressure of gas are changing. Also, the ion currents are very small and the sensitivity of the meter limits the range of the instrument. Electronic control circuits and high-gain amplifiers have been developed to overcome these difficulties.

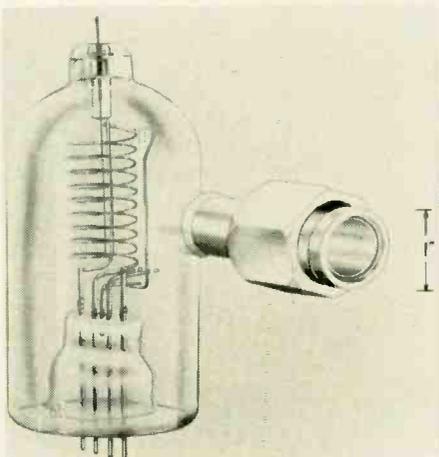Commercial ion-gage control circuits have automatic emission regulators. In some, saturable reactors hold the emission from the filament constant with changes in line voltage or pressure.




RCA

Fig. 3—Inverted-structure ion gage

The ion current amplifier is usually a multistage, electrometer type circuit with 100% negative feedback. In addition, a safety shutoff feature is often provided that will automatically turn off the power to the filament when the pressure inside the gage becomes too high. Special modifications are also available. The control unit shown in the photo has a readout meter calibrated in altitude as well as pressure.
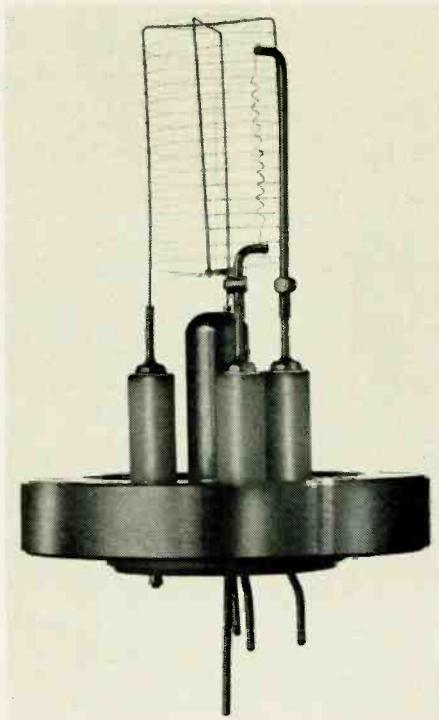
#### Limits of operation

The basic ion gage has limits of operation at both the high and low pressure ends of its range. At gas pressures greater than a millionth of an atmosphere,



Varian Associates

Fig. 4—"Nude" ion gage with inverted structure, for direct insertion into vacuum system. Such a unit can cost \$150.

the ion current tends to saturate and levels off at a constant value which is independent of pressure. High concentrations of reactive gases inside the gage cause rapid failure or burnout of the filament. Fortunately, other vacuum gages operating on the thermal-conduction principle perform satisfactorily in this range of pressures.

At the other end of the scale, the measurement of very low pressures is limited by the emission of X-rays, which are formed when the ionizing electrons

strike the grid wire. The X-rays fall on the plate and release photoelectrons which cause a current to be produced at the plate. This current is of the same sign as the ion current but it is independent of pressure. At very low pressures the ion current becomes less than the current caused by the X-rays, and the gage has reached its useful limit.

#### Modifications for lower pressure


The development of an inverted-structure ion gage has extended the lower limit of the hot-filament ion gage by a factor of at least 200. The inverted gage (Fig. 3) has the filament *outside* the spiral-wound grid. The plate is reduced to a single, fine wire suspended inside the grid. The plate is several hundred times smaller than the usual metal cylinder and receives only a fraction of the X-rays produced at the grid. Because of its lower operating limit, the inverted-structure gage has become the standard measuring instrument for workers in the ultra-high vacuum field.

#### UNITS OF VACUUM

Any pressure less than atmospheric pressure is considered to be a vacuum. While early workers in the field measured vacuum in inches or centimeters of mercury, modern vacuum technologists express low pressures in terms of the absolute unit: *torr*. One *torr*, named after Torricelli who discovered the principle of the barometer, is equal to 1/760 of a standard atmosphere. Therefore, normal atmospheric pressure may be considered to be 760 *torr*. The pressure in a typical vacuum tube is about  $1 \times 10^{-6}$  or .000001 *torr*. The basic ion gage, described in this article, has a useful range from  $1 \times 10^{-3}$  *torr* to about  $1 \times 10^{-8}$  *torr*.

Vacuum technology is closely associated with space exploration. The table here shows the degree of vacuum that would be encountered at various heights above the earth's surface.

Height in miles	Pressure in torr
Sea level	760 or $7.6 \times 10^2$
10	$1 \times 10^2$
100	$1 \times 10^{-5}$
1,000	$1 \times 10^{-11}$
Interplanetary space	$1 \times 10^{-16}$

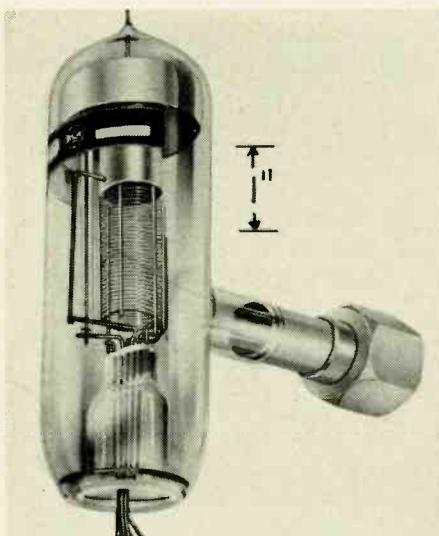

RCA

Fig. 5—Suppressor type ion gage with inverted structure, for ultra-high-vacuum measurements.

The walls of the glass envelope and the tube connecting the gage to the vacuum system sometimes interfere with accurate measurements. To overcome these problems, the ion gage is available in an unenclosed or "nude" form (Fig. 4). The electrodes are sealed directly into the vacuum system.

Several other design modifications have been employed to extend the useful range of the hot-filament ion gage. As an example, the gage tube in Fig. 5 has added elements in the form of a suppressor ring and a collector shield, which aid in extending the limits of vacuum measurements.

The common electron tube and the highly specialized ion gage have much in common. The service technician who pulls a "gassy" tube and the scientist who measures high vacuums with an ion gage are dealing with the same problem. They both have a vacuum tube that needs a vacuum. END

# You can earn more money if you have an FCC License

FCC FORM 750 A

*The United States of America*

NUMBER  
P1-20-6490

**FEDERAL COMMUNICATIONS COMMISSION**

**RADIO TELEPHONE OPERATOR LICENSE**

**FIRST CLASS**  
(General Radiotelephone Certificate)

*This certifies that* \_\_\_\_\_ TOMMY WILLIS DUFFY \_\_\_\_\_

IS A LICENSED RADIO OPERATOR, AUTHORIZED, SUBJECT TO ANY SPECIAL ENDORSEMENT PLACED HEREON, TO OPERATE THE CLASSES OF LICENSED RADIO STATIONS FOR WHICH THIS CLASS OF LICENSE IS VALID UNDER THE ORDERS, RULES AND REGULATIONS OF THE FEDERAL COMMUNICATIONS COMMISSION, ANY STATUTE OF THE UNITED STATES AND ANY TREATY TO WHICH THE UNITED STATES IS A PARTY.

THIS LICENSE IS GRANTED UNDER THE AUTHORITY OF THE COMMUNICATIONS ACT OF 1934 AS AMENDED, AND THE TERMS AND CONDITIONS THEREOF AND OF ALL LEGISLATIVE ACTS, EXECUTIVE ORDERS AND TREATIES TO WHICH THE UNITED STATES IS SIGNATORY, AND ALL ORDERS, RULES AND REGULATIONS OF THE FEDERAL COMMUNICATIONS COMMISSION, WHICH ARE BINDING UPON RADIO OPERATORS, ARE MADE A PART HEREOF AS THOUGH SPECIFICALLY SET OUT IN FULL HEREIN.

NEITHER THIS LICENSE NOR THE RIGHTS CERTIFIED TO HEREIN SHALL BE ASSIGNED OR OTHERWISE TRANSFERRED TO ANY OTHER PERSON.

PLACE AND DATE OF ISSUANCE: BUFFALO, NEW YORK - SEPTEMBER 11, 1963

DATE AND TIME OF EXPIRATION: SEPTEMBER 11, 1968 AT THREE O'CLOCK A. M., EASTERN STANDARD TIME.

SPECIAL ENDORSEMENT: SHIP RADAR ENDORSEMENT - SEPTEMBER 11, 1963 - BUFFALO, NEW YORK

*[Signature]*  
ISSUING OFFICER

*Federal Communications Commission*

*[Signature]* (Licensee)      *[Signature]* (Issuing Officer)      *[Signature]* (Secretary)

NOT VALID UNTIL SIGNED

## Employers are paying good money for men holding FCC tickets. Read how to get yours:

When you hold a Commercial License issued by the FCC (Federal Communications Commission) you have written proof that you know and understand basic electronic theory and fundamentals. It's worth plenty . . . particularly to companies on the lookout for qualified electronics technicians. Here's how one of the country's leading office machine manufacturers rates men with FCC Licenses:

"An FCC License is an asset to any man looking to enhance his career in the field of electronics. At our Company, a licensed man is well-rewarded because an FCC License attests to his knowledge of electronics theory . . ."

Thousands of employers will tell you the same thing. Licensed men get the good jobs. They make more money

. . . move ahead faster . . . enjoy exciting, challenging work. What's more, they're needed badly in every field of electronics. Industrial electronics. Radio-TV Broadcasting. Aerospace. Electronics Servicing . . . including mobile and marine radio *plus* CB.

Yes . . . your opportunities are unlimited once you're carrying that FCC Commercial Ticket. AND CLEVELAND INSTITUTE OF ELECTRONICS CAN GET ONE FOR YOU! On the facing page, read how four ambitious men just like you have cashed in on CIE's sure-fire FCC Licensing Program. Read about CIE's exclusive money-back offer. And then send in the postage paid reply card. CIE will quickly send you complete FREE information. You will soon be on *your* way to a Commercial FCC License and the many rewards that go with it!

# These CIE men have good jobs

(they have Commercial FCC Licenses)



**Matt Stuczynski, Senior Transmitter Operator, Radio Station WBOE.** "I give Cleveland Institute credit for my First Class Commercial FCC License. Even though I had only 6 weeks of high school algebra, CIE's AUTO-PROGRAMMING teaching method makes electronics theory and fundamentals easy. After completing the CIE course, I took and passed the 1st Class Exam. I now have a good job in studio operation, transmitting, proof of performance, equipment servicing. Believe me, CIE lives up to its promises!"



**Ted Barger, Electronic Technician, Smith Electronics Co.** "I've been interested in electronics ever since I started operating my own Ham rig (K8ANF). But now I've turned a hobby into a real interesting career. Cleveland Institute of Electronics prepared me for my Commercial FCC License exam . . . and I passed it on the first try. I'm now designing, building and testing all kinds of electronic equipment . . . do a lot of traveling, too. It's a great job . . . and thanks to CIE and my FCC License, I'm on my way up."



**Chuck Hawkins, Chief Radio Technician, Division 12, Ohio Dept./Highways.** "Cleveland Institute Training enabled me to pass both the 2nd and 1st Class License Exams on my first attempt . . . even though I'd had no other electronics training. (Many of the others who took the exam with me were trying to pass for the eighth or ninth time!) I'm now in charge of Division Communications and we service 119 mobile units and six base stations. It's an interesting, challenging and extremely rewarding job. And incidentally, I got it through CIE's Job Placement Service . . . a free lifetime service for CIE graduates."



**Glenn Horning, Local Equipment Supervisor, Western Reserve Telephone Company (subsidiary of Mid-Continent Telephone Company).** "There's no doubt about it. I owe my 2nd Class FCC License to Cleveland Institute. Their FCC License Program really teaches you theory and fundamentals and is particularly strong on transistors, mobile radio, troubleshooting and math. Do I use this knowledge? You bet. We're installing more sophisticated electronic gear all the time and what I learned from CIE sure helps. Our Company has 10 other men enrolled with CIE and take my word for it, it's going to help every one of them just like it helped me."

## FCC LICENSE WARRANTY

A CIE FCC License Course will quickly prepare you for a Commercial FCC License. If you don't pass the FCC exam . . . on the first try . . . after completing your course, CIE will refund all your tuition. You get an FCC License . . . or your money back!

Two out of three men who took the 1st Class Commercial FCC License exam in 1964, failed.

Nine out of ten CIE-TRAINED men who take this exam, pass . . . the very first try!

And that's why CIE can back their courses with the warranty you see at the left. CIE-trained men know their stuff . . . because CIE AUTO-PROGRAMMED Home Study works!

Get started now. Send postage-paid reply card for free information about a plan that gets you an FCC License or costs you nothing!

**CIE** **Cleveland Institute of Electronics**  
1776 East 17th Street, Dept. RE-11, Cleveland, Ohio 44114

# new SAMS BOOKS

## Color-TV Servicing Guide



by Robert G. Middleton. This great new book on color-TV troubleshooting follows the same picture-tube-and-trouble-symptom format made famous in the best-selling *TV Servicing Guide*, now used by more than 100,000 servicemen. Shows how to apply fast troubleshooting procedures, based on an analysis of trouble symptoms. Includes many full-color picture tube photos illustrating various operating troubles, accompanied by clear, concise explanations of probable causes and diagnosing procedures. Takes you through each section of the color-TV receiver, describing the symptoms for various types of troubles. A final chapter explains in detail how to test and service color-bar generators. If you service color-TV, this book is a gold-mine of help. **\$3.95** 112 pages, 8½ x 11". Order **SGC-1**, only.....

**OTHER SAMS COLOR-TV SERVICING BOOKS**  
**Color TV Training Manual** (new 2nd Edition), by Oliphant & Ray. Order **TVC-2**, only..... **\$5.95**  
**Color TV Servicing Made Easy**, by Wayne Lemons and Carl Babcoke. Order **CSL-1**, only..... **\$2.95**  
**Know Your Color-TV Test Equipment**, by Robert G. Middleton. Order **KOC-1**, only..... **\$2.50**

## Inventors Idea Book

by L. George Lawrence. Have you ever thought of inventing a laser defense against nuclear warheads, or a thawing device for water hydrants? These are just two of hundreds of ideas awaiting the attention of an inspired inventor. If you are an experimenter, technician, engineer, or student with imagination and initiative, this new book is for you. Contains more than 175 suggestions about specific needs of industry and technology; provides possible approaches toward their solution. Encompasses such varied areas as safety appliances for the home, devices for communications, meteorology, aeronautics, transportation, medicine, and the conquest of space. This challenging book not only points up the vital need for original invention, but also stimulates creative thinking. 128 pages; 5½ x 8½". **\$1.95** Order **IBL-1**, only.....

## Know Your Square-Wave and Pulse Generators

by Robert G. Middleton. Square-wave and pulse generators are very useful in component testing, and for making amplifier performance checks with an oscilloscope. This book, another in the practical "know your test equipment" series, offers comprehensive information on the operating principles and applications of square-wave and pulse generators and tells how to determine their performance quality in terms of their rise (and fall) time. Begins with basic principles and proceeds to a step-by-step analysis of both service and laboratory-type generators. Mathematics is used only when absolutely necessary. This book provides technicians and technical institute and engineering students with a sound foundation for further study. 144 pages, 5½ x 8½". **\$2.50** Order **KOP-1**, only.....

## Transistor Etched-Circuit Projects



by James Kyle. The only complete book available on etched-circuit construction for experimenters, hobbyists, and students. Unique, easy-to-use negatives are included right in the book; just clip them out and follow the simple instructions. You can build 30 fascinating projects; each is explained so that you gain a fuller understanding of the principles involved. One chapter also tells you how to design and photo-etch your own projects; a list of suppliers of materials required for photo-etching is included. The only book of its kind, packed with building fun and valuable instruction. 144 pages; 5½ x 8½". **\$2.95** Order **TCK-1**, only.....

## HOWARD W. SAMS & CO., INC.

Order from your Sams Distributor today, or mail to Howard W. Sams & Co., Inc., Dept. RE-12, 4300 W. 62nd Street, Indianapolis, Ind. 46206

Send me the following books:  
 SGC-1  CSL-1  IBL-1  TCK-1  
 TVC-2  KOC-1  KOP-1

Send FREE Sams Booklist. \$\_\_\_\_\_ enclosed

Name \_\_\_\_\_

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

My Distributor is \_\_\_\_\_

Circle 32 on reader's service card

# EQUIPMENT REPORT

## Sonotone RM-2 Speaker System

Circle 37 on reader's service card



SONOTONE'S RM-2 IS A RECENT ADDITION to what is now a family of three speakers. It all began about a year ago with the RM-1, a midget system with a 6-inch woofer. Now redesigned, the RM-1 is flanked by two newer designs: the baby, whimsically named the RM-0.5, and a big brother, the RM-2, which has an 8-inch woofer and a 3-inch cone tweeter.

Measuring 19 x 12 x 8 inches, the RM-2 cabinet is sturdily built of walnut-veneered chip-and-resin board (great stuff for nonresonant boxes—even better than plywood), with lots of corner bracing. The back is fastened with a generous number of screws (12), spaced an average of about 6 inches around the edges. No rattles here.

This rugged box is completely filled by two thick blocks of glass wool; there is virtually no "empty" air space in the enclosure. The somewhat paradoxical result, as any acoustician will be happy to puzzle you with, is an enclosure effectively quite a bit larger than its actual structural size. This technique, related to that of the acoustic suspension speaker systems, is being used in a large number of bookshelf-size speakers.

The woofer is brought out to the terminals through a coil, to keep high frequencies out of it, and the tweeter is connected through a capacitor (to block lower frequencies) and a potentiometer, which allows its output to be varied between nothing at all and full volume. The nominal crossover frequency is 4,500 cycles; the nominal impedance, 8 ohms.

The RM-2 sounds pleasant and listenable. At the manufacturer-recommended tweeter control setting of 8, the highs are rather steamy, which isn't irritating, because it's smooth, but just a

bit unnatural. In any case, the control permits adjustment to suit individual taste. High-frequencies are beamed somewhat, as is typical of most simple cone tweeters.

At low frequencies, there is some doubling below about 80 cycles. This is not a serious flaw. All speakers—even big ones—begin producing more second-harmonic than fundamental eventually, as you go down the scale. Second-harmonic distortion is mild, inoffensive stuff; the ear can tolerate large amounts of it without being disturbed—sometimes without even noticing it, and it gives a satisfying illusion of real bass.

(A popular radio design of the 30's and 40's used an audio amplifier that, with the help of a simple R-C feedback network, generated controlled amounts of second- and third-harmonic distortion, while suppressing the fundamental below about 150 cycles. This predistorted audio, fed to a 5-inch speaker, produced amazingly full sound. It was called *synthetic bass*.)

The RM-2 isn't guilty of a tubby or boxy sound, characteristic of many small systems. What is missing is really only the gut-rumbling bass around 50 cycles that only two or three of the small bookshelf speaker systems can produce. (And they cost more than the RM-2.)—Peter E. Sutheim

## EICO Model 342

### FM Multiplex Generator


Circle 38 on reader's service card

JOINING THE LIST OF LOW-COST, EFFICIENT instruments for testing and aligning FM stereo multiplex circuits as well as complete stereo FM receivers, the model 342 just introduced by Eico proves to be design-lab quality at service-bench cost. The model 342 has extraordinary circuit refinements to insure excellent separation in the composite stereo signal. The measured separation capability of this instrument actually exceeded the 40 db claimed in the specifications. When you recall that the FCC requires only 30-db separation from *broadcasters*, the significance of this outstanding figure can be fully appreciated.

It is perhaps this refinement in design which prompted Eico to offer the model 342 in wired form only. The average kit builder might well find it difficult to calibrate this instrument to the precision that can be achieved in the factory. After subjecting the unit to several hours of continuous use, I noticed absolutely no drift in the alignment of the circuits that produce the composite stereo waveform. The rf signal (available as a convenience in aligning tuners or receivers) did drift during

warmup, but this is not serious. Simply tune the receiver under test to around 100 mc until the test signal is found.

The model 342 has both a controlled amplitude composite audio output for direct injection into multiplex circuits (beyond the detector), and the same signal—modulating an FM rf carrier at about 100 mc with controlled deviation ( $\pm 75$  kc)—for connection to the antenna terminals. Either a built-in 1-kc audio oscillator or an external oscillator may be used for left-only, right-only, difference (L - R) or sum (L + R) signals. The 19-kc pilot signal is crystal-controlled and may be switched on and off independently of the composite signal. A signal can also be set up without audio information and only the 19-kc pilot.

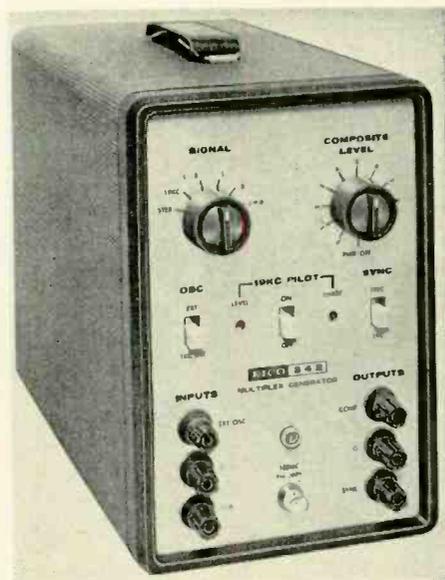

A scope sync output offers a choice of either 19-kc sync or 1-kc sync. The 342 also has an input for connecting an external audio oscillator to provide an SCA (background music subcarrier) signal when required.

Another important feature of the model 342 (and one not found on most competitive units) is a pair of inputs and isolation amplifiers for a stereo program source to permit FM stereo demonstrations to customers when there are no stereo programs being broadcast. The amplifiers even pre-emphasize the program material properly (75  $\mu$ sec), just like an FM broadcast transmitter, so that tone controls do not have to be radically altered from flat when the program is heard on a receiver with normal de-emphasis.

While an rf signal is very handy in evaluating the performance of a complete tuner or stereo receiver, I felt that the signal strength of the 100-mc carrier in the model 342 is so great that it pre-

vents judging a receiver's stereo performance under "weak signal" conditions. Of course, the rf cable can be removed from the antenna terminals of the receiver being tested to approximate a weak signal, but then there is no way of knowing *how* weak the signal is. In other words, some form of calibrated attenuator would have been desirable to allow the unit to double as a general FM rf generator. But in view of its superior performance for aligning multiplex sections of receivers, this minor omission certainly does not detract from the very fine qualities of this compact, well de-

signed instrument.—Leonard Feldman

**MANUFACTURER'S SPECIFICATIONS**

- Separation: 40 db minimum from 200 cycles to 10 kc; 30 db minimum from 50 cycles to 15 kc.
- Composite signal output: 0-5 v p-p, continuously variable; output impedance 1,500 ohms
- Rf output: 200 millivolts; output impedance 50 ohms
- Pilot frequency: 19 kc  $\pm 2$  cycles, crystal controlled
- Signal selection: L + R, L - R, L only, R only, 19 kc only, external stereo source
- Power requirement: 117 vac, 50-60 cycles
- Size: 8 1/2 x 5 3/4 x 12 1/2 inches
- Weight: 10 lb
- Price: \$149.95 (wired only)

*Continued on page 68*

# FREE

## NEW 1966 GIANT CATALOG

TUBES PARTS  
ETC. AT  
LOWEST  
PRICES

SAVE UP TO  
50% ON  
CHOICE  
KITS

Satisfaction  
GUARANTEED  
or your money  
back!

SAVE  
ON CAMERAS  
FILM &  
PHOTO  
EQUIPMENT

100's  
OF BARGAINS  
NOT IN  
ANY OTHER  
CATALOG

100's of  
new items  
listed for  
first time.

EVERYTHING  
IN HI-FI  
AND  
STEREO

TOP  
VALUES IN  
POWER  
& HAND  
TOOLS

**NO MONEY DOWN  
PLUS REVOLVING  
CHARGE ACCOUNT**

100's of pages packed with savings

**BURSTEIN-APPLEBEE CO. Dept. RE,  
1012-14 McGee St., Kansas City, Mo. 64106**

Rush me the FREE 1966 B-A Catalog.

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_

Please be sure to show your Zip No. \_\_\_\_\_


**BUYING GUIDE FOR:**

- Stereo & Hi-Fi Systems and Components
- Tape Recorders
- Electronic Parts, Tubes, Books
- Phonos & Records
- Ham Gear
- Test Instruments and Kits
- Cameras and Film
- Public Address
- Citizens Band
- Transistor & FM-AM Radios.

RUSH COUPON TODAY
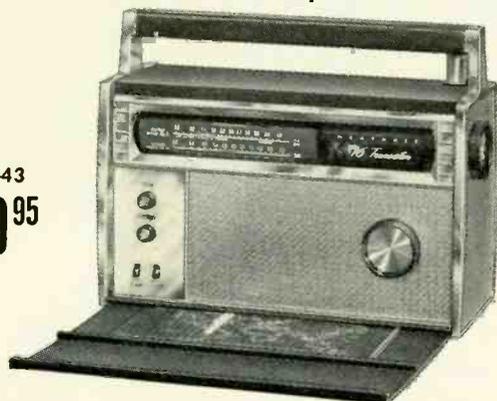
# New Ideas For Christmas Giving . . .


A Gift For Everyone . . . In This Vast Heathkit® Selection!



Kit GR-43  
**\$159<sup>95</sup>**
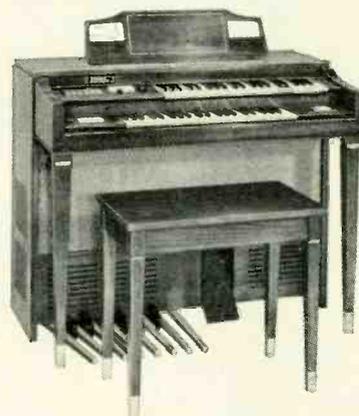
## New Heathkit 10-Band Transistor Portable!


10 bands tune Longwave, Standard Broadcast, FM and 2-22.5 mc Shortwave. 16 transistors, 6 diodes, and 44 factory assembled and pretuned circuits. Two separate AM & FM tuners and IF strips. FM tuner & IF strip are same components used in deluxe Heathkit FM stereo gear. 2 built-in antennas. Battery saver switch cuts current drain up to 35%. Rotating tuning dial. Dial light. 4 simple controls for tuning, volume, tone, AFC and band switching. 4" x 6" PM speaker. Earphone & built-in jack. Optional 117 v. AC converter/battery charger available @ \$6.95. Time zone map & "listener's guide." Man size: 13½" W x 5½" D x 10¼" H. 17 lbs.



Kit GD-983  
Now Only  
**\$799<sup>00</sup>**
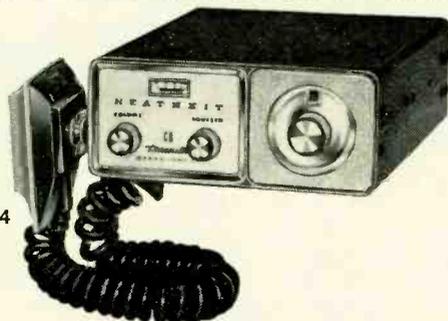
## Ideal Gift For The Whole Family . . . Heathkit®/Thomas Organs!

The Heathkit/Thomas "Coronado" Transistor Organ, (illust.) boasts 17 organ voices, two 44-note keyboards, Leslie plus 2-unit main speaker system, 28 notes of chimes, 13-note heel & toe pedalboard, color-tone attack & repeat percussion, matching bench, plus many more professional features. 242 lbs. Also the Heathkit/Thomas "Artiste" Transistor Organ with 10 voices, two 37-note keyboards, repeat percussion, etc. now at only \$332. 154 lbs. . . . Both organs have all genuine Thomas factory fabricated components.



Kit GW-14  
**\$89<sup>95</sup>**

Assembled GWW-14  
**\$124<sup>95</sup>**

## New 23-Channel, 5-Watt Transistor CB Transceiver!


23 crystal-controlled transmit & receive channels for the utmost reliability . . . at competitive prices! All-transistor circuit for instant operation, low battery drain . . . only .75 A transmit, .12 A receive. Only 2⅞" H x 7" W x 10½" D . . . ideal for car, boat, any 12 v. neg. gnd. mobile use. "S" meter, adjustable squelch, ANL, built-in speaker, ceramic PTT mike, aluminum cabinet. 8 lbs. Kit GWA-14-1, optional AC power supply, 5 lbs., \$14.95.



Kit SB-100  
**\$360<sup>00</sup>**
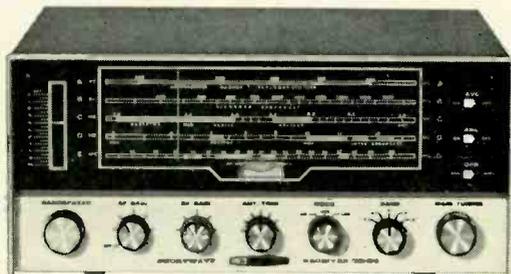
## New DeLuxe 5-Band SSB Ham Transceiver

Full SSB-CW transceive operation on 80-10 meters. 180 watts PEP SSB—170 watts CW. Switch select for USB/LSB/CW operation. Operates PTT and VOX; VOX operated CW with built-in sidetone. Triple Action Level Control™ allows greater variation in speech level. Heath SB series Linear Master Oscillator (LMO) for true linear tuning. Mobile or fixed operation with appropriate power supply. 23 lbs. Accessory mobile mount, SBA-100-1 \$14.95.



## New Deluxe Shortwave Radio

Compare it to sets costing \$150 and more! 5 bands cover 200-400 kc, AM, and 2-30 mc. Tuned RF stage, crystal filter for greater selectivity, 2 detectors for AM and SSB, tuning meter, bandspread tuning, code practice monitor, automatic noise limiter, automatic volume control, antenna trimmer, built-in 4" x 6" speaker, headphone jack, gray metal cabinet, and free SWL antenna. 25 lbs.

Kit GR-54  
**\$84<sup>95</sup>**



Kit HD-10  
**\$39<sup>95</sup>**


## New Heathkit Solid-State Electronic Keyer

All solid-state circuitry. Speed range—15 to 60 words per minute. Solid-state switching—no relays to stick or clatter. Adaptable to either right or left handed operators. Convertible to semi-automatic operation. Variable dot-space ratio. Self-completing dashes. Sealed switches on paddle—no exposed contacts to clean or adjust. Built-in paddle—"feel" is adjustable to your fist during assembly. "Hold" switch for transmitter tuning. Transformer-operated power supply isolates keyer from line power. Fused for protection. 6 lbs.

Circle 34 on reader's service card

# ... "Do-It-Yourself" Heathgifts!


Now Choose From 2 Heathkit® Transistor Stereo Receivers!

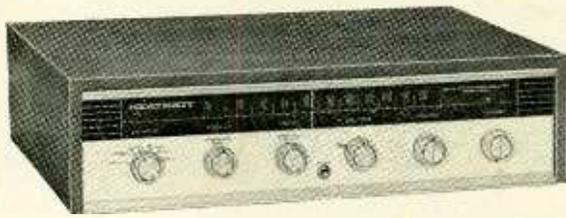

**New 30-Watt Transistor FM Stereo Receiver . . .  
Less Than \$100!**

Features 31 transistors, 11 diodes for cool, natural transistor sound; 20 watts RMS, 30 watts IHF music power @ ±1 db, 15 to 60,000 cps; wideband FM/FM stereo tuner plus two preamplifiers & two power amplifiers; front panel stereo headphone jack; compact 3 3/4" H x 15 1/4" W x 12" D size. Assembles in 20 hours or less. Custom mount it in a wall, or optional Heath cabinets (walnut \$9.95, beige metal \$3.95) 16 lbs.

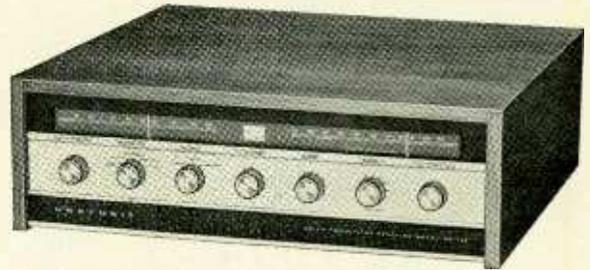Kit AR-14  
**\$99<sup>95</sup>**  
(less cabinet)




**66-Watt Transistor AM/FM Stereo Receiver**

Just add 2 speakers for a complete stereo system. Boasts AM/FM/FM Stereo tuning; 46-transistor, 17-diode circuit for cool, instant operation and natural transistor sound; 66 watts IHF music power (40 watts RMS) at ±1 db from 15 to 30,000 cps; automatic switching to stereo; preassembled & aligned "front-end" & AM-FM IF strip; walnut cab. 35 lbs.

Kit AR-13A  
Now Only  
**\$184<sup>00</sup>**

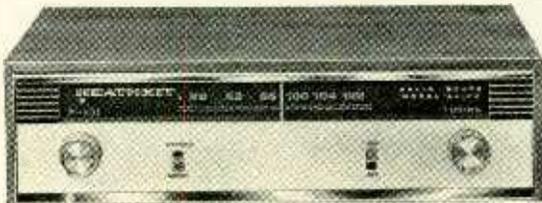
## Best Hi-Fi News Of '65 . . . New Low-Cost Transistor Stereo Twins!



**New Transistor FM/FM Stereo Tuner**

Heath's easiest to build stereo/hi-fi kit . . . takes only 4 to 6 hours! 14 transistor, 5 diode circuit for cool instant operation, transparent transistor sound. Phase control assures best stereo performance. 3 transistor "front-end" plus 4-stage IF section. Filtered outputs for direct stereo recording. Automatic stereo indicator light. Preassembled & aligned "front-end." Install in a wall or either Heath cabinet (walnut \$7.95, beige metal \$3.50). 6 lbs.

Kit AJ-14  
**\$49<sup>95</sup>**  
(less cabinet)

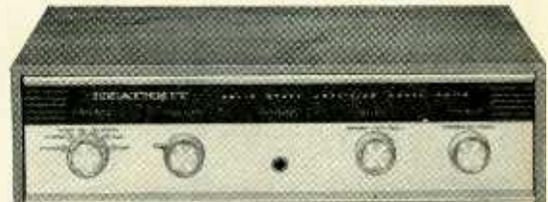

**Matching 30-Watt Transistor Stereo Amplifier**

Assembles in 10 hours or less! 17 transistors, 6 diodes. 20 watts RMS, 30 watts IHF music power @ ±1 db, 15 to 60,000 cps. No audio transformers . . . assures minimum phase shift, extended response, lower distortion. Solid-state power supply plus electronic filter for regulation within 10%. Accommodates phono, tuner, auxiliary . . . 4, 8, 16 ohm speaker impedances. Lighted panel. Installs in wall, or Heath cabinets (walnut \$7.95, metal \$3.50). 10 lbs.

Kit AA-14  
**\$59<sup>95</sup>**  
(less cabinet)

Buy Now—Use This Order Blank

## NEW 1966 CATALOG!



Free! 108 pages . . . many in full color . . . describe these and over 250 easy-to-build Heathkits. Save up to 50%. Mail coupon for your free copy.

Heath Company, Dept. 20-12  
Benton Harbor, Michigan 49023



Please send FREE Heathkit Catalog

Model	Description	Weight	Price


Name \_\_\_\_\_ (Please Print)

Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

SHIP VIA:  
 Parcel Post  Express Collect  Freight  20% Included, C.O.D.  Best Way  
All prices & specifications subject to change without notice.

CL-227

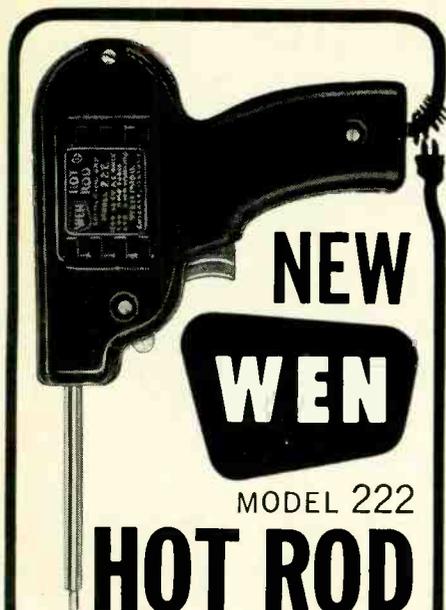

## NEW WEN MODEL 222 HOT ROD SOLDERING GUN

The perfect answer to all Radio, TV and electronic soldering jobs.

222, with Wen's exclusive ATR (Automatic Thermal Regulation), is a power packed, lightweight precision instrument that gives you more than just dual heat. It gives you an effective and efficient range of heat up to 200 watts. The Wen Hot Rod Soldering Gun can deliver the heat-power found in a 200-watt soldering device on a current draw of only 110 watts surge and 55 watts working. Feature for feature, there's not a better soldering gun to be found anywhere. Check 'em off.

- Exclusive ATR (Automatic Thermal Regulation) permits heat-power to be automatically adjusted to the correct level for the job being done.
- Tip automatically adjusts heat-power up to 200 watts.
- New CS 1200 heat element in the tip puts heat-power on the work.
- Economy performance—more heat-power, less current draw.
- Lighter weight, more compact—beautifully balanced.
- ONLY \$7.95

Model 222 K-5 Kit, with rugged custom fitted case, contains flat iron and plastic cutting attachments which seal plastic bags, remove wood dents and perform dozens of accessory jobs. Kit also contains fine soldering tip for delicate soldering jobs. Only \$11.95.

**WEN PRODUCTS, INC.**  
5810 Northwest Highway  
Chicago, Illinois 60631


Circle 35 on reader's service card

### EQUIPMENT REPORT continued
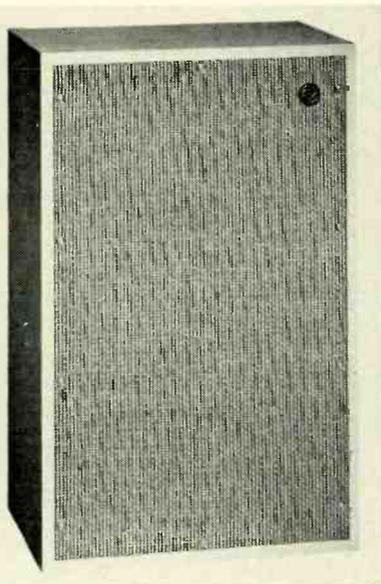
## Electro-Voice Sentry II Studio Monitor Loudspeaker

Circle 39 on reader's service card

DURING A RECENT TRIP THROUGH THE Midwest, I stopped, among other places, at Electro-Voice. There I was introduced (among other things) to a special kind of speaker I hadn't come upon before. It was Electro-Voice's Sentry II studio monitor loudspeaker. It is, the manufacturer claims, designed for extremely smooth, flat response and lack of coloration, and intended for use as a broadcast or recording studio monitor, rather than to satisfy someone's conception of "what the public wants."



The Sentry II is a big box. It measures 32 by 20 by 13 inches outside, which amounts to an internal volume of about 7,000 cubic inches, or about 4 cubic feet. It contains a 12-inch Electro-Voice SP-12B woofer and a small horn tweeter, with, I would guess, a pretty high crossover point, judging by the size of the tweeter horn. E-V does not specify the crossover frequency. The enclosure, built of ¾-inch stock, is a bass-reflex type with a 6½-inch duct behind the port. About an inch of acoustic padding lines about half the inside surface of the enclosure.

Extensive listening on all kinds of music and on speech showed that the Sentry II is indeed free of a particular "color", and in general has an easy, effortless quality of reproduction that usually comes only from the biggest speaker systems. The high end is bright, and there is a suggestion of either a peak or some harmonic distortion somewhere in the lower treble. (However, I listened to it in a hard, bright room. Broadcast studios and control rooms are usually heavi-

ly padded with acoustic tile.) The overall sound is smooth and extremely pleasant.

Bass goes quite low; there is plenty of power at 50 cycles and still some audible output at 30, though much of what comes out at 30 cycles input is really 60 and 90 cycles. About 35 cycles is the "true bass" limit of this speaker. Absolutely no effort has been made, apparently, to firm up the bass end to please a bass-happy public. And the bass is flat, praise 'em—no boom, no heavy one-note emphasis.

The Sentry II is at least about four times more efficient than acoustic-suspension and other sealed-enclosure designs. (Studio monitoring amplifiers generally produce between 10 and 25 watts output; the 50-, 60-, 100-watt monsters that have become so common in the hi-fi field are almost unknown in broadcast studios.) Such a high efficiency makes it practical to fill a room with sound from a 5-watt amplifier, or, to look at it another way, almost every high-quality amplifier on the market today would simply loaf along even at high-power orchestral passages. About ¾ (electrical) watt at 100 cycles fed to this speaker makes a loud noise in a 10 x 15 room.

This is definitely not everyman's speaker. (Electro-Voice obviously knows this, for it has not promoted the Sentry II among audiophiles.) But if you think you might be happy with an "austere" speaker—one that doesn't have any "warmth," "color," "sweetness," as such, built into it, and you have room for it, you might want to listen to the Sentry II. Its sound, speaking subjectively, is one of great naturalness on speech as well as on music.

Electro-Voice also manufactures a Sentry I, whose electrical and acoustic specifications are the same as those of the Sentry II, but which has a sloping-front cabinet design for mounting between wall and ceiling or halfway up a corner, between two walls. It measures 17 by 37 by 21¾ inches and its profile is just like that of the popular wooden baffles for wall-mounting intercom or paging speakers.

Both Sentry I and Sentry II come with a built-in transformer that can match the system's impedance (nominally 16 ohms) to 150- or 600-ohm lines. Both come in sanded, grain-sealed, light-colored wood cabinets, ready for painting.—Peter E. Sutherland END

### MANUFACTURER'S SPECIFICATIONS

Frequency response: 30–20,000 cycles  
EIA sensitivity rating: 49 db  
Impedance: 16, 150 or 600 ohms  
Power-handling capacity: 20 watts  
Size: 32 x 20 x 13 inches  
Weight: 68 lb.  
Price: \$159.  
Electro-Voice, Inc.



The following free advertising material is available through

## RADIO-ELECTRONICS READER'S SERVICE

- ACOUSTIC RESEARCH INC.** (Pg. 9) Circle 9  
Literature on AR speakers and turntables.
- ALLIED RADIO CORP.** (Pg. 75) Circle 110  
Free 1966 catalog.
- B & K MANUFACTURING CO.** (Pg. 25) Circle 23  
Complete catalog.
- BLONDER-TONGUE** (Pg. 13) Circle 13  
Free booklet "How to Plan a Color-Approved Home TV System".
- BROOKS RADIO & TV CORP.** (Pg. 92-93) Circle 125  
Catalog sheets and price lists of tubes and parts.
- BURSTEIN-APPLEBEE CO.** (Pg. 65) Circle 33  
New 1966 Giant catalog.
- CASTLE TV TUNER SERVICE, INC.** (Pg. 6) Circle 5  
Information on complete tuner overhaul by mail.
- CLEVELAND INSTITUTE OF ELECTRONICS** (Pg. 8) Circle 8  
Free electronics slide rule booklet and pocket electronics data guide.
- CORNELL ELECTRONICS CO.** (Pg. 97) Circle 131  
Catalog and price list of tubes and parts.
- CONAR INSTRUMENTS** (Pg. 73) Circle 108  
Catalog on Conar electronic kits.
- COYNE ELECTRONICS INSTITUTE** (Pg. 96) Circle 129  
Book on "Your Opportunities in Electronics."
- DE VRY TECHNICAL INSTITUTE** (Pg. 5) Circle 4  
Free booklets "Pocket Guide to Real Earnings" and "Electronics in Space Travel."
- EDLIE ELECTRONICS, INC.** (Pg. 94) Circle 126  
Latest catalog of electronic components, tubes and equipment.
- EICO ELECTRONIC INSTRUMENT CO.** (Pg. 30) Circle 25  
Free catalog on full EICO line of 200 best buys and names of nearest dealers.
- ELECTRONIC COMPONENTS CO.** (Pg. 98) Circle 133  
Information on rectifiers and transistors.
- GRANTHAM SCHOOL OF ELECTRONICS** (Pg. 96) Circle 130  
Free 48-page booklet, "Careers in Electronics."
- HEALD'S ENGINEERING COLLEGE** (Pg. 95) Circle 128  
Catalog and registration application.
- HEATH COMPANY** (Pg. 66-67) Circle 34  
New 1966 108-page catalog of easy-to-build kits.
- HY-GAIN ELECTRONICS CORP.** (Pg. 15) Circle 15  
Free Mobile Antenna Comparison report No. 15.
- INTERNATIONAL CRYSTAL MFG. CO. INC.** (Third Cover) Circle 149  
Information on International Model MO Transceiver for Citizens Radio Service.
- INTERNATIONAL RADIO EXCHANGE** (Pg. 8) Circle 7  
Complete list of equipment in stock.
- JFD ELECTRONICS CORPORATION** (Pg. 7) Circle 6  
Information on JFD LPV Color Log Periodic Antennas.
- JACKSON ELECTRICAL INSTRUMENT COMPANY** (Pg. 12) Circle 12  
Complete catalog on test instruments.
- JERROLD ELECTRONICS CORP.** (Pg. 81) Circle 115  
Information on the Tele-Mate cordless UHF converter.
- LAFAYETTE RADIO ELECTRONICS** (Pg. 83) Circle 118  
Free 1966 Lafayette catalog 660.
- MALLORY DISTRIBUTOR PRODUCTS CO.** (Pg. 23) Circle 21  
Information on Solid State Circuits
- MULTICORE SALES CORP.** (Pg. 75) Circle 111  
Information on Ersin Multicore 5-core solder.
- OLSON ELECTRONICS, INC.** (Pg. 72) Circle 107  
Free one year's subscription to Olson Electronics catalog.
- OXFORD TRANSDUCER CO.** (Pg. 22) Circle 19  
Complete catalog on the Oxford Transducer line of 11 different auto rear seat speaker kits . . . and "Blanket the Market."
- POLY PAKS** (Pg. 101) Circle 135  
Catalog of Semi-conductors.
- PRECISE ELECTRONICS & DEVELOPMENT** (Pg. 2) Circle 3  
Information on the new line of test instruments.
- PROGRESSIVE "EDU-KITS" INC.** (Pg. 89) Circle 122  
Information describing Edu-Kits.
- RADAR DEVICES MANUFACTURING CORP.** (Pg. 1) Circle 2  
Information on how to have a business of your own distributing Radar Sentry Alarm Systems.
- RADIO SHACK** (Pg. 102) Circle 136  
Radio Shack Catalog.
- RAY-TEL CB PRODUCTS** (Pg. 91) Circle 124  
Complete details on Ray-Tel TWR-5 and TWR-7.
- RCA INSTITUTES INC.** (Pg. 26-29) Circle 24  
Brochure on home study and classroom study.
- RYE SOUND CORPORATION** (Pg. 82) Circle 117  
Information on the Kleps 30 test prober.
- HOWARD W. SAMS & CO. INC.** (Pg. 64) Circle 32  
Free Sams booklet.

- HOWARD W. SAMS & CO. INC.** (Pg. 21) Circle 18  
Information on Photofact Library Encyclopedia deal.
- SCHOBER ORGAN CORP.** (Pg. 24) Circle 22  
Booklet and 7" sampler record.
- SENCORE** (Pg. 90) Circle 123  
Information on CG135 Transistorized color generator.
- TRIPLETT ELECTRICAL INSTRUMENT** (Second Cover) Circle 1  
Information on the world's most complete line of V-O-M's.
- TURNER MICROPHONE COMPANY** (Pg. 80) Circle 114  
Complete Turner Microphone catalog.
- UNITED RADIO CO.** (Pg. 99) Circle 134  
Complete parts catalog.
- UNIVERSITY SOUND** (Pg. 72) Circle 106  
Free book, "Microphones '66" for tape recording.
- WARREN ELECTRONIC COMPONENTS** (Pg. 95) Circle 127  
Information on Silicon rectifiers.
- WELLER ELECTRIC CORP.** (Pg. 88) Circle 120  
Information on New Marksman Pencil soldering iron.
- WEN PRODUCTS** (Pg. 68) Circle 35  
Information on Wen hot rod soldering gun.
- WINDSOR ELECTRONICS, INC.** (Pg. 82) Circle 116  
Booklet entitled "The Open Door to TV Profits."
- WINEGARD CO.** (Pg. 74) Circle 109  
Fact-finder #242 with information on Chroma-Tel antenna.

Here's how you can get manufacturers' literature fast:

1. Tear out the post card on the facing page. Clearly print or type your name and address.
2. Circle the number on the card that corresponds to the number appearing at the bottom of the New Products, New Literature or Equipment Report listing in which you are interested. For literature on products advertised in this issue circle the number on the card that corresponds to the number appearing at the bottom of the advertisement in which you are interested, or use the convenient checking list in the column at the left.
3. Mail the card to us (no postage required in U. S. A.)

Note: If the postcard has already been detached from your copy of RADIO-ELECTRONICS, use the coupon on this page instead. Enclose the coupon in an envelope and address it to: RADIO-ELECTRONICS READER'S SERVICE, P. O. Box 7365, Philadelphia, Pa. 19101. (Use this address only for Reader's Service requests.)

## RADIO-ELECTRONICS READER'S SERVICE

P.O. Box 7365, Philadelphia, Pa. 19101

The numbers I have circled below indicate the material I would like to receive:

1	2	3	4	5	6	7	8	9	10	11	12	13	14	15
16	17	18	19	20	21	22	23	24	25	26	27	28	29	30
31	32	33	34	35	36	37	38	39	40	41	42	43	44	45
46	47	48	49	50	51	52	53	54	55	56	57	58	59	60
61	62	63	64	65	66	67	68	69	70	71	72	73	74	75
76	77	78	79	80	81	82	83	84	85	86	87	88	89	90
91	92	93	94	95	96	97	98	99	100	101	102	103	104	105
106	107	108	109	110	111	112	113	114	115	116	117	118	119	120
121	122	123	124	125	126	127	128	129	130	131	132	133	134	135
136	137	138	139	140	141	142	143	144	145	146	147	148	149	150

VOID AFTER JANUARY 31, 1966

Name \_\_\_\_\_

Address \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_

12-65 Zip Code \_\_\_\_\_
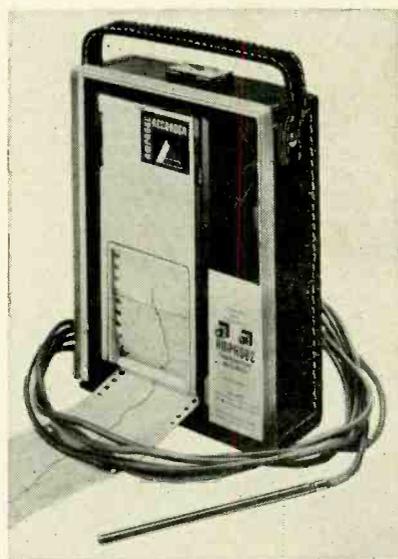
# NEW PRODUCTS

More information on these new products is available free from the manufacturers. Each item is identified by a Reader's Service number. Turn to the Reader's Service Card facing page 70 and circle the numbers of the new products on which you would like further information. Detach and mail the postage-paid card.

**MINIATURE STRIP-CHART RECORDER**, model LT8100, will record temperature in 2 ranges;  $-50^{\circ}$  to  $+100^{\circ}$ F;  $+50^{\circ}$  to  $+250^{\circ}$ F. Monitors temperature conditions on pressure-sensi-




tive strip chart 30 ft long by 2½-in. wide. Leather case; available with 1-, 6-, or 12-in. per hour feed speed.—Amprobe Instrument

Circle 46 on reader's service card

**AUTO RADIO ANTENNA**, the A-85 CB/AM combination, uses encapsulated top-loading coil to get one-quarter-wavelength resonance. VSWR 1.1 to 1. No degradation when used for entertainment radio. Signal divider prevents 27-mc signals from entering AM radio. 47 in. extended, telescopes to 30 in.—Webster Mfg.

Circle 47 on reader's service card

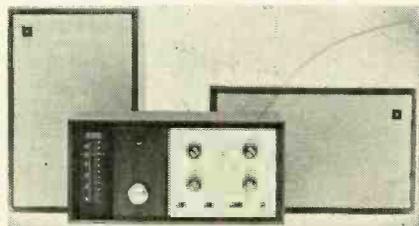


**FM STEREO RECEIVER SYSTEM**, the Stereomaster 2400. Frequency re-

sponse 20–20,000 cycles; sensitivity 2.8  $\mu$ v; distortion at normal listening level less than 0.5%. Walnut cabinet. Tuner/amplifier 12½ x 7 x 7 in. Speakers (each) 14 x 8½ x 5 in. Shipping weight with speakers, 34 lb.—H. H. Scott, Inc.

Circle 48 on reader's service card

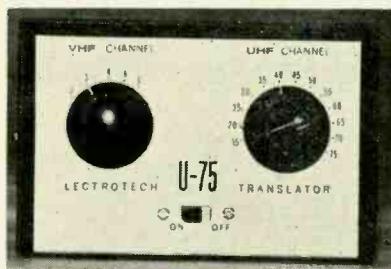**UHF TRANSLATOR**, model U-75, converts any rf signal between 55 and 85 mc to any ulf channel between 15 and 75. Requires minimum signal of 2,500  $\mu$ v.



Input for either 300 ohms balanced or 50–75 unbalanced. Uhf dial calibration exact for 69 mc; maximum error  $\pm 5$  channels. Uses standard 9-volt battery. 6 x 6 x 4 in., 3 lb. For color and black-and-white.—Lectrotech, Inc.


Circle 49 on reader's service card



**SOUND RECORDING TAPE** now available in brown-and-beige library-box packaging. Space on back of box for listing taped selections. Identifying sleeve is removed after purchase of tape; sizes from 625 feet on 5-in. reel to 3,600 feet on 7-in. reel.—Eastman Kodak Co.


Circle 50 on reader's service card

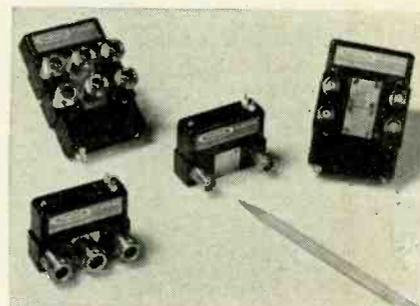**COAXIAL SWITCHES**. New *Dynafom* switch line uses standard modules to produce hundreds of combinations.



Special-purpose switches available in a few days in prototype quantities for bread-boarding. Spdt and transfer switches weigh about 4 oz; dpdt types about 8 oz. Gold-plated beryllium copper bifurcated moving-contact blades; area of contact and pressure satisfactory for 500 watts. Mechanical life rating minimum 1 million cycles.—Amphenol RF Div.


Circle 51 on reader's service card

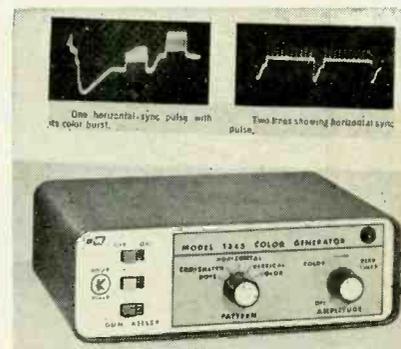

**SOLID-STATE COLOR GENERATOR**, model 1245, permits accurate setting of color-killer threshold control without waiting for color telecast. Produces all necessary waveforms to station quality standards. Complete blanking of all video information during sync periods. Crystal-controlled keyed rainbow color bar display; dot/crosshatch/horizontal line/vertical line patterns, gun killer controls. Dots are one line high, 0.2  $\mu$ sec wide. 2½ x 8½ x 8½ in., 3 lb.—B & K Mfg. Co.

Circle 52 on reader's service card

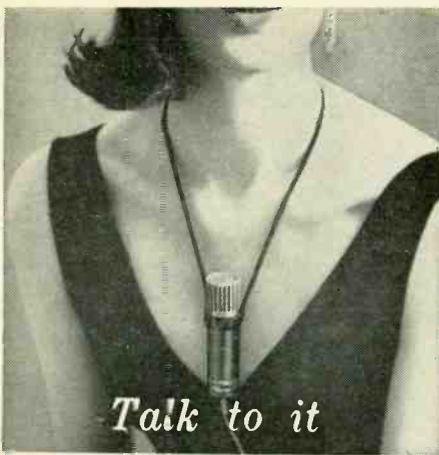**MINIATURE SEALED ELECTROLYTIC CAPACITORS**. Operating temperature rating from  $-20^{\circ}$  to  $+85^{\circ}$  C and close tolerance on capacity of  $-0$ ,  $+100\%$ . Available capacitances range from 2 to 1,000  $\mu$ f; voltage ratings from 6 to 50



*Talk to it*

... right into your tape recorder — then play it back and listen to the lively sound of your own voice — so natural, no one can tell the difference. University's new revolutionary Attaché is the smallest cardioid dynamic microphone ever made. Priced right too! Free! "Microphones '66" — a book every owner of a tape recorder should have.



**UNIVERSITY SOUND**  
A DIVISION OF THE LIND ALTEC, INC.  
Dept. M59, Box 1056  
Oklahoma City, Okla. 73101



Name \_\_\_\_\_  
Address \_\_\_\_\_  
City \_\_\_\_\_  
State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 105 on reader's service card

**Olson**

**FREE**

Fill in coupon for a FREE One Year Subscription to **OLSON ELECTRONICS'** Fantastic Value Packed Catalog — Unheard of **LOW, LOW PRICES** on Brand Name Speakers, Changers, Tubes, Tools, Stereo Amps, Tuners, CB, Hi-Fi's, and thousands of other Electronic Values. Credit plan available.


NAME \_\_\_\_\_  
ADDRESS \_\_\_\_\_  
CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

If you have a friend interested in electronics send his name and address for a FREE subscription also.

**OLSON ELECTRONICS, INC.**

432 S. Forge Street Akron, Ohio 48430

Circle 107 on reader's service card

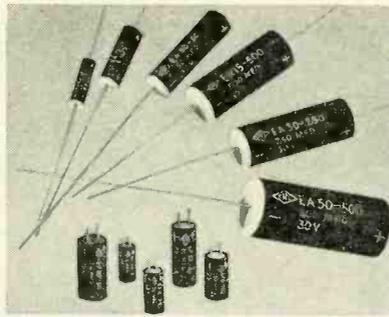

dc working volts. Molded phenolic plastic case, epoxy-sealed ends. Axial and printed-circuit lead types. Case dimensions small as 1/8-in. long by 1/8-in. diameter for 25- $\mu$ f 6-volt unit.—Centralab

Circle 53 on reader's service card


**FM STEREO RECEIVER**, the 440-T. 70 watts of music power at 4 ohms; 50 watts at 8-ohm impedance. 2.0- $\mu$ v sensitivity (IHF). Wide-band ratio detector;



wide-band solid-state i.f. strip; 4 i.f. stages; 3 limiters; d'Arsonval tuning meter; time-division multiplex system; tape and phono facilities; gold-plated front panel. 16% x 5 1/2 x 12 1/2 in., 21 lb.—Fisher Radio Corp.

Circle 54 on reader's service card

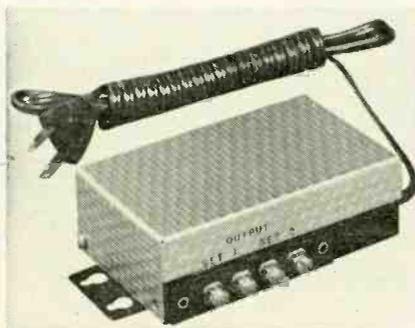**LINE OF COLOR AMPLIFIERS**, Tele-Amp. *HVU-3*; up to 18 db gain; noise 4.2 db; 3 transistors. *HV-2*; up to 13 db gain for 2 sets, up to 8 db for 4 sets; noise figure to 4 db; 2 transistors. *HV-1*; for vhf fringe reception with high-pass filter: up to 12 db gain for 2 sets, up to 8 db with all outputs used;




noise 4.5 db; 1 transistor. *HV-1* amplifies FM/FM stereo up to 15 db gain; noise 5.1 db; 1 transistor. *EV-1* for vhf fringe, 2 vhf/FM outputs: up to 17 db gain for 1 set, to 14 db with both outputs; noise to 5.1 db; 1 transistor. *EF-1*: economy amplification; 15 db gain; noise 5.6 db; 1 transistor.—JFD Electronics Corp.

Circle 55 on reader's service card

**2- AND 6-METER CONVERTER KITS**. Heathkit model SBA-300-3, the

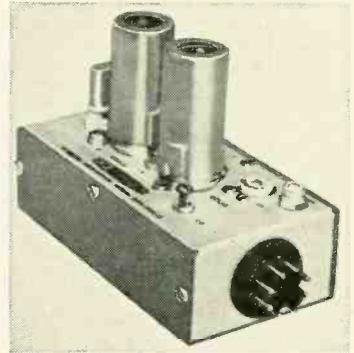
6-meter model (shown), extends coverage of SB-300 receiver from 48 to 54 mc (50 to 52 mc with crystal supplied), and the 2-meter converter, kit SBA-300-4, ex-



tends coverage from 142 to 150 mc (144 to 146 mc using crystal supplied). Each converter uses 6DJ8 cascode amplifier for low noise factor and high sensitivity. Age provision.—Heath Co.

Circle 56 on reader's service card

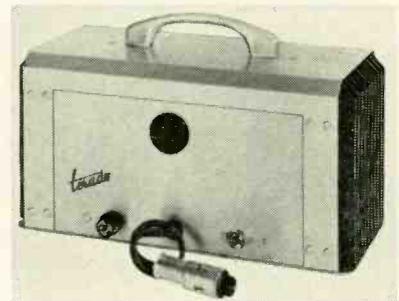**SOLID-STATE POWER INVERTER**, the *Tempest* model 50-170. Changes battery current of car or boat to



117 vac. Capacity 125 to 150 watts. Copper-clad case, carrying handle.—Terado Corp.

Circle 57 on reader's service card


**MINIATURIZED AUDIO TRANSFORMER**, the *PIL-50*. 5/16-in. diameter, 3/16-in. high, 1/20 oz. Primary impedance 500 ohms et; unbalanced dc in primary 3 ma; primary dc response 40 ohms;



maximum level 100 mw;  $\pm$ 3-db frequency range at 1 mw 800 cycles–250 kc.—United Transformer Corp.

Circle 58 on reader's service card

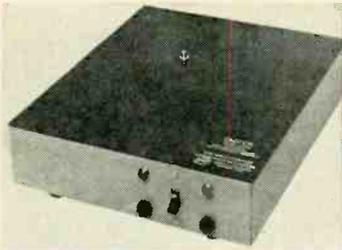**BULK TAPE ERASER**, *Cinema* type 9205A for erasing program and residual noise from magnetic tape on 17-in. reel or



films with magnetic sound tracks. Active field area can erase recorded signal to more than 50 db below saturation. Double-pole switches, double-fused with pilot lights; 3-conductor cord with 2-prong plug and ground connector with 6-ft rubber-covered cord.—Aerovox Corp., Hi-Q Div.


Circle 59 on reader's service card

**TRANSISTOR REGULATED POWER SUPPLY KIT**, model PZ-107, will deliver output continuously variable from 7 to 25 volts at 200 ma dc (30 v at 100 ma dc). Input 105-125 v 50-60 cycles ac.



Load regulation  $\pm 0.2\%$ . Line regulation  $\pm 0.4\%$ . Ac ripple less than 1 mv.  $3\frac{3}{4} \times 4\frac{1}{4} \times 5\frac{1}{2}$  in.—Viking Engineering

Circle 60 on reader's service card

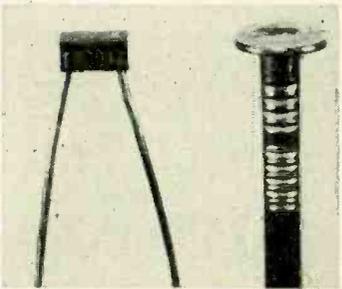

**CERAMIC CAPACITOR, EPCO4 Nailhead**. Capacitance range of 10 pf through .027  $\mu\text{f}$ ; case measures 0.2 x 0.1 x 0.1 in. Modified barium titanate dielectric. Available in axial-lead tubular style as well as rectangular case shown.—Marshall Industries, Electron Products Div.


Circle 61 on reader's service card

**AUDIOMATIC GENERATOR**, model 610-A. Manual frequency range 25-46,000 cycles in one continuous range. Automatic range by separate control from 0 to 20 kc, markings at 1,000-cycle increments. Accuracy of-calibration  $\pm (1\% + 5 \text{ cycles})$ . Output impedance: 4,000 ohms single-ended and 600 ohms

balanced to ground. Output power 100 mw at 4,000 ohms, + 19 db at 600 ohms. Output essentially flat from 50-10,000 cycles. Waveform distortion less than 0.5% over most of range. Ac hum less than 0.1%.  $19\frac{1}{2} \times 11 \times 15$  in., 48 lb.—The Clough-Brengle Co.


Circle 62 on reader's service card

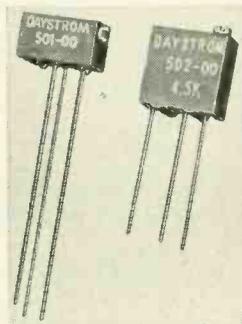**POTENTIOMETERS**, models 501 (back pins) and 502 (side pins) Square-trims, require only .07 cubic inch space. Range 10 to 30,000 ohms. Precision tolerance is  $\pm 5\%$ ; resolution better than 0.124%. Adjustability 15 turns with slip-




clutch. High power 0.5 watt at 70°C; low noise 100 ohms maximum. Temperature range -55° to +150°C; low-temperature coefficient  $\pm 70$  ppm maximum.—Weston Instruments, Inc.

Circle 63 on reader's service card

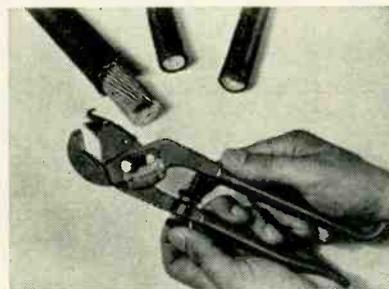


**CABLE INSULATION STRIPPING TOOL**, model 369, cuts, slits, strips insulation from cables ranging from No. 1 to 1,000 MCM (Million Circular Mils). Designed to remove insulation without cutting or nicking conductor strands. Guide markings for each cable size. Tool can be used at end of conductor or anywhere along its length.—Thomas & Betts Co.

Circle 64 on reader's service card

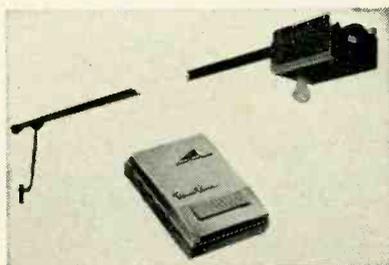

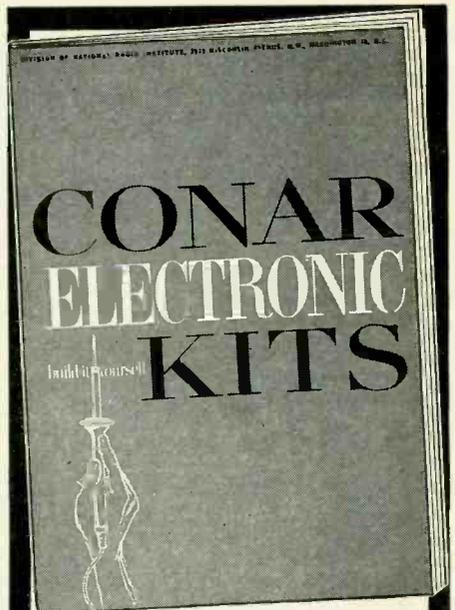**GARAGE-DOOR OPENER**, model G-670, which claims to be free from



Your copy is waiting...

The do-it-yourselfer's newest catalog

Here's your new catalog of quality electronic kits and assembled equipment . . . your shopping guide for TV set kits, transistor radios, voltmeters, scopes, tube testers, ham gear, PA systems, and a host of other carefully engineered products. Every item in the Conar catalog is backed by a no-loopholes, money-back guarantee. It's not the biggest catalog, but once you shop its pages you'll agree it's among the best. For years of pleasurable performance, for fun and pride in assembly, mail the coupon. Discover why Conar, a division of National Radio Institute, is just about the fastest growing name in the kit and equipment business.

CONAR

MAIL NOW!

CONAR NC 5C  
3939 Wisconsin Avenue, Washington, D.C. 20016  
Please send me your new catalog.

Name \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_ Z-Code \_\_\_\_\_

Circle 108 on reader's service card

# Meet Winegard Chroma-Tel

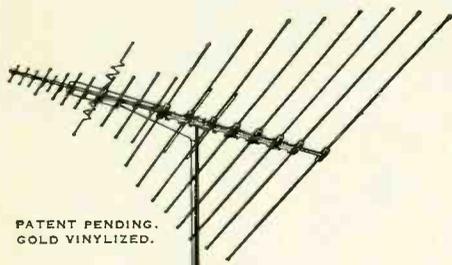

PATENT PENDING.  
GOLD VINYLIZED.

First 1/2 size all-band (UHF, VHF, FM) antenna with full size power

- Delivers Brilliant Color, Beautiful Black and White, Full-Tone FM Sound
- Brings in All the UHF, VHF and FM Stations in Your Area

Now there's an All-Band (UHF, VHF, FM) antenna that is actually half the size of most other all-band antennas. It eliminates half the bulk, half the wind loading, half the storage space, half the truck space and half the weight of ordinary all-band antennas... without sacrificing one bit of performance! Features Winegard's new Chroma-Lens Director System and impedance correlators.

Compare size, cost and performance... you'll choose Winegard Chroma-Tel every time. Ask your distributor or write for Fact-Finder #242 today.

3 Models from \$17.50 list.

**Winegard Co.** ANTENNA SYSTEMS

3000 Kirkwood • Burlington, Iowa

Circle 109 on reader's service card

for your convenience

over  
**600**  
electronic  
parts  
distributors

now sell  
**Radio-Electronics**  
in the United States  
and Canada

phantom operation by stray radio signals, employs new radio coding system. This unit works via pulse tone modulation, a patent-applied-for technique that makes each radio signal personal, and complies with FCC rules. Transmitter and receiver are all-transistor; motor is controlled by computer logic circuit. Handles metal, fiberglass or wood doors up to 20 feet wide and 8 feet high; works from 117 v, 60 cycles.—Perma-Power Co.

Circle 65 on reader's service card


**REGULATED POWER SUPPLY**, model 1030, has two continuously variable sources: one bias output from 0-150 volts at 2 ma; the other from 0-400 volts at up to 150 ma. The latter output is regulated to .03% for loads up to 100 ma. Change of line voltage of  $\pm 10$  volts will cause less than 0.5-v maximum change in output. Ripple less than 3 mv rms.



Front-panel connections provide unregulated filament voltages of 6.3 v, with or without centertap, and 12.6 v, all at 3 amperes. 13 x 8 1/2 x 7 in., operates from 117-volt 50-60 cycle line. Power consumption 160 watts. Wired or kit.—EICO

Circle 66 on reader's service card

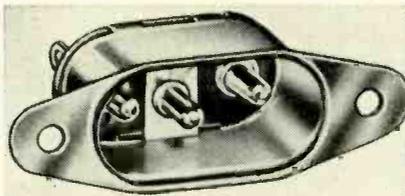**3-PIN AC RECEPTACLES**, part No. AC3 (ungrounded), AC3G (grounded), have self-aligning feature which allows movement of pins 1 and 3 in shell to take up off-centering of plug contact locations.



Stationary center pin 2 acts as guide. AC3G has metal strap to ground pin 2. Each mates with Belden type PH-243 plugs or equivalent. Both are rated at 115 volts, 7 amperes.—Switchcraft Inc.

Circle 67 on reader's service card

**DIELECTRIC STRENGTH CHECKER**, the *Insta Test*, gives audio and visual response at breakdown point of windings used in coils, motors, transformers, etc. Selection scale graduated in ranges of 750, 1,000, 1,250, 2,000, 3,000 ac volts. Operates on 117 volts at 50 or 60 cycles. Two high-voltage probes permit quick check across any winding; buz-




zer sounds at potential breakdown point; red lamp lights if part is defective.—Grand Transformers, Inc.

Circle 68 on reader's service card



**STEREO DYNAMIC HEADPHONE** for use in school language labs announced by Koss/Rek-O-Kut. Model K/R 2+2 has boom-mounted microphone, hi-fi sound and special foam-filled ear cushions to prevent outside room noise from disturbing study. Shatterproof plastic is basic material; cord is reinforced.—Koss Electronics Inc.

Circle 69 on reader's service card

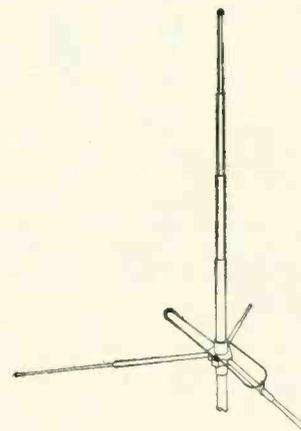


**ANTENNA FOR BUSINESS BAND**, the *Dispatcher DP-275*, for 27.23 to 50 mc. 1/2 wave vertical; radial radius of 9 feet and height of 20 feet at 27 mc. Radi-

RADIO-ELECTRONICS

ation pattern 360°. Coax female connector in radial support assembly. VSWR 1.5/1 or better. Gain 3.4 db over  $\frac{1}{4}$ -wave ground plane; 5.9 db compared to isotropic source. Maximum power input 1,000 watts.—Mosley Electronics Inc.

Circle 70 on reader's service card

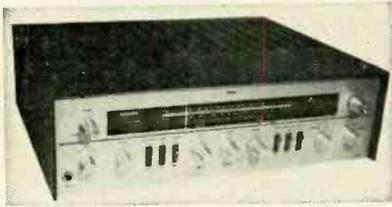
**SOLID-STATE STEREO RECEIVER**, model RA-727. Tuner sensitivity 1  $\mu$ v. Image ratio over 30 db. MPX separation 30 db. Amplifier output 44 watts music power. Response: 30 to 30,-



000 cycles. Crosstalk more than -32 db. Distortion 0.5% at 1,000 cycles. Input sensitivity: phono 8 mv. Auxiliary: 300 mv. Brushed-gold panel, 9 $\frac{1}{2}$  x 5 $\frac{1}{4}$  x 12 $\frac{1}{2}$  in., oiled walnut cabinet.—Olson Electronics, Inc.

Circle 71 on reader's service card

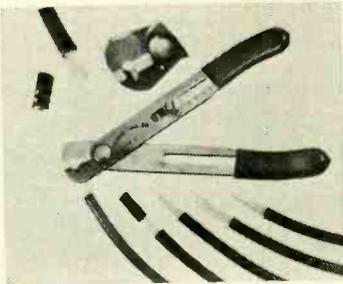**COAX CUTTER AND STRIPPER**, stock No. X55F, is designed to cut and strip RG-59/U coax. Two stripping holes:



larger for removing outer insulation and braid; smaller removes inner insulation. Spring steel, honed and heat-treated cutting edges.—Hunter Tools

Circle 72 on reader's service card


**FM STEREO TUNER**, model 532. Range 87.5-108.5 mc with 2- $\mu$ v sensitivity. 800-kc bandwidth; channel separation of 30 db. Afc circuit, stereo beacon light, antenna inputs for 75 and 300 ohms. 12 $\frac{1}{2}$  x 7 x 2 $\frac{1}{2}$  in. Power consumption 30 watts.—Trutone Electronics, Inc.



Circle 73 on reader's service card

**SOLID-STATE WIRELESS INTER-COM**, stock No. 99-4573M. No wiring required; plug each unit into ac outlet. Each unit is master with volume/on-off control, push-to-talk bar with lock-bar feature for


DECEMBER, 1965

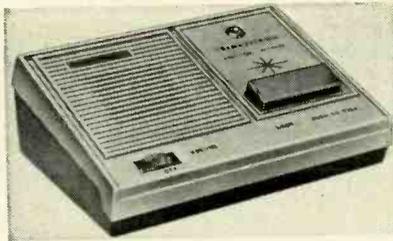

continuous operation. Plastic case with rubber-tipped base. 6 $\frac{1}{2}$  x 5 x 2 $\frac{1}{2}$  in., 2 lb. For 110-120 volts 60 cycles ac.—Lafayette Radio Electronics Corp.

Circle 74 on reader's service card

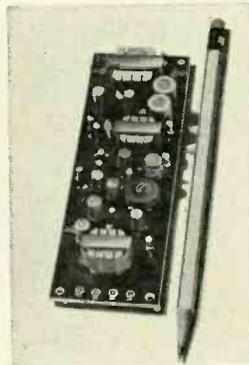
**COMPACT TRANSISTOR AUDIO AMPLIFIER**, to handle low-level mikes, phono pickups, etc., features: volume control; 5 transistors; 1 thermistor; shielded input transformer with 2 primary



windings for 50 ohms and high impedance; output transformer with 2 secondary windings, 8 ohms (for speakers), 500 ohms (for modulation and high impedance loads). 400 mw push-pull output; 80 db gain; 9-volt dc source. Mounted on printed circuit board 5 $\frac{1}{2}$  x 1 $\frac{1}{4}$  in., 3 $\frac{1}{2}$  oz.—Birnbach Radio


Circle 75 on reader's service card

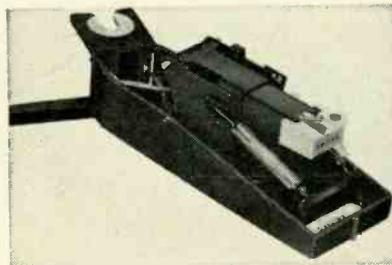**ELLIPTICAL STYLUS CARTRIDGE ASSEMBLY**, the Gard-A-Matic model M80E, features retractile safety suspension system and elliptic diamond stylus, plugs into tone arm of Garrard Lab 80 and Type A70 changers. Response: 20-20,000 cycles. Output volt-



age 6.6 mv per channel at 1,000 cycles at 5 cm/sec. Channel separation over 25 db at 1,000 cycles. Recommended load impedance 47,000 ohms. Compliance 25 x 10<sup>-6</sup> cm/dyne. Tracking force: 1-1 $\frac{1}{2}$  grams maximum. Inductance 720 mh. Dc resistance 630 ohms.—Shure Brothers, Inc.

Circle 76 on reader's service card

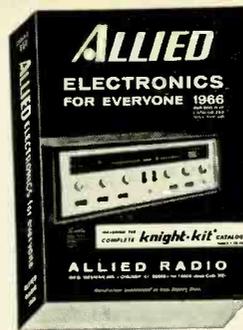

**FREE**

send for your **MONEY-SAVING** 508-page

1966 **ALLIED** CATALOG

**SAVE MOST ON:**

Stereo Hi-Fi  
Tape Recording  
CB 2-Way Radio  
Shortwave & Ham Gear  
Automotive Electronics  
FM-AM & AM Radios  
Portable TV & Phonos  
Test Instruments  
TV Tubes & Antennas  
Power Tools, Hardware  
Parts, Tubes, Transistors

See the world's largest selection of top money-saving buys, including exclusive Knight-Kits and products available only from ALLIED. Get fastest service, easy-pay terms, satisfaction guaranteed or your money back. Send coupon today for your FREE 1966 ALLIED Catalog.

**EASY TERMS:** Use the Allied Credit Fund Plan.

**ALLIED RADIO**

free catalog

ALLIED RADIO, Dept. 2-M  
100 N. Western Ave., Chicago, Ill. 60680

Send FREE 1966 ALLIED Catalog.

Name \_\_\_\_\_

PLEASE PRINT

Address \_\_\_\_\_

City \_\_\_\_\_

State \_\_\_\_\_

Zip \_\_\_\_\_

Circle 110 on reader's service card

**WORLD'S FINEST**  
**5-CORE SOLDER**

**ERSIN MULTICORE**  
**NEW EASY DISPENSER PAK ONLY 69¢**

**BUY IT AT RADIO-TV PARTS STORES**  
MULTICORE SALES CORP. WESTBURY, N.Y. 11591  
Circle 111 on reader's service card

**TRANSISTORIZED MICROPHONE**, model +2, has adjustable out-



put level, will increase range and signal strength of any transceiver. Operator can dial output level best for his set; changes output for big or little voice, close or far work. Touch-to-talk or lock on-off switching. Screwdriver adjustment connects

terminal wire in base for electronic switching or relay switching. SSB response limited to 300-3,000 cycles. One-piece diecast case.—Turner Microphone Co.

Circle 77 on reader's service card



**CAPACITORS**, type P8292ZN, use plastic-cased metallized paper. Rated dc voltages of 200, 400, 600 based on life test of 1½ times working voltage at 100°C for 1,000 hours. Capacitance values available from .01 to 10 µf.—Aerovox Corp.


Circle 78 on reader's service card



**TAPE SOUND SYSTEM FOR CARS**, the Norelco Car-Mount, can play

back through car radio as well as record and be removed from car for use as portable, separate recorder. Comprises a universal mounting attached below dashboard, plus the Carry-Corder 150, a cordless, cartridge-loaded, portable tape recorder.—North American Philips Co., Inc.

Circle 79 on reader's service card

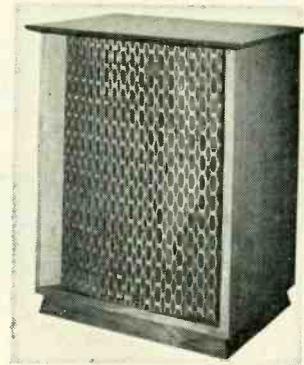

**PLAYBACK SPEAKER SYSTEM**, the 847A Seville. Contemporary upright walnut cabinet with Spanish wood fretwork grille, uses less than 2 sq. ft. of floor space. Inside are type 414 12-in. bass speaker, exponential horn, compression high-frequency driver, 2-section 3,000-cycle crossover network. Operates from 8 or 16 ohms; rated at 20 watts; response 40 to 22,000 cycles. 26 x 19 x 14 in.—Altec Lansing.

Circle 80 on reader's service card

**BIG CATALOG**  
World's "BEST BUYS" in GOV'T. SURPLUS Electronic Equipment

FULL OF TOP QUALITY ITEMS—Transmitters, Receivers, Power Supplies, Inverters, Microphones, Filters, Meters, Cable, Keys, Phones, Antennas, Chokes, Dynamotors, Blowers, Switches, Test Equipment, Headsets, Amplifiers, etc. SEND 25¢ (stamps or coin) for CATALOG and receive 50¢ CREDIT on your order. Address Dept. RE.

**FAIR RADIO SALES**  
P.O. Box 1105 • LIMA, OHIO • 45802

## 3 New GERNSBACK LIBRARY Paperback books...


### TV SWEEP OSCILLATORS

By Harry E. Thomas

TV SWEEP OSCILLATORS is a practical working tool and handy reference book for everyone who fixes TV sets. Written in

clear, easy-to-understand language, it gives you all the practical facts you will ever need on the subject. Includes:

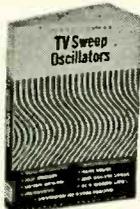TV Sweep Systems—The Relaxation Oscillator... Capacitor Charge and Discharge-Pulse Techniques... Multivibrators and Blocking Oscillators... Sawtooth Generation in Sweep Systems... Variations in Sweep Oscillators... Failure Analysis in the General Operation and Servicing of Sweep Oscillators... and much more!  
No. 119 Paperback—252 pages .....\$3.95



### THE HANDBOOK OF ELECTRONIC TABLES

is fast... easy... accurate... unique... and provides a wide variety of solutions to electronic problems!

The HANDBOOK is the first book to be totally devoted to electronic tables. The advantages of these tables are multiple: they're easy to use, they give you a high degree of accuracy and offer a wide variety of solutions. The tables are carried out to several decimals. You don't have to memorize any formulas, carry a slide rule or work out your problems: the answers have already been worked out for you.

No. 125 Paperback—160 p. ....\$2.95



### ADVANCED RADIO CONTROL

by Edward L. Safford, Jr.

A revolutionary challenge for the hobbyist interested in expanding his knowledge of radio control.

NEW IDEAS and concepts stimulating the imagination of the radio control hobbyist.

EXPLAINS how to use advanced radio control techniques for model planes, boats, trains, trucks, tractors, autos, and robots. This latest book brings you ideas which have never appeared in print before. And... it's a practical introduction to rockets and robots at the hobby level. Contains clear and concise diagrams.

No. 122 Paperback—192 pages .....\$3.50



Get your copies of these new **GERNSBACK LIBRARY** Handy Paperback books at Your local Radio-Electronics Parts Distributor ... or use the handy coupon to order

GIVE THIS COUPON to your local Parts Distributor or mail to:  
**GERNSBACK LIBRARY**  
154 West 14th Street,  
New York, N.Y. 10011

Please send me:

- No. 119  TV SWEEP OSCILLATORS \$3.95  
No. 125  THE HANDBOOK OF ELECTRONIC TABLES \$2.95  
No. 122  ADVANCED RADIO CONTROL \$3.50

I enclose \$ \_\_\_\_\_

NAME \_\_\_\_\_

STREET ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_

STATE \_\_\_\_\_

ZIP \_\_\_\_\_  
RE-1265

# NEW LITERATURE

All booklets, catalogs, charts, data sheets and other literature listed here are free for the asking (except where a price is given). Each item is identified by a Reader's Service number. Turn to the Reader's Service Card facing page 70 and circle the number of items you want. Then detach and mail the card. No postage required!

**SOLDERING-GUN BROCHURE, No. 15.** 8 pages of pictures and text on applications of Markel's soldering guns and accessories.—**Markel**  
Circle 81 on reader's service card

**CINEMA PRECISION AUDIO EQUIPMENT, Catalog 32-EF.** 8 pages of specs, photos, curves on equalizers, dip filters, transmission measuring sets, power supplies.—**Hi-Q Div. of Aerovox**  
Circle 82 on reader's service card

**ISO-CURVE THERMISTORS, Bulletin L-2,** 6-page foldout with 3 data sheets, curves, photos, configurations, resistance vs temperature characteristics table on Iso-Curve line of curve-matched, interchangeable thermistors.—**Fenwal Electronics**  
Circle 83 on reader's service card

**CAPSULE THERMISTOR COURSES 1** through 10, now collected in one 5½ x 11 in. booklet. Plus glossary.—**Fenwal Electronics Inc.**  
Circle 84 on reader's service card

**CATALOG, No. S-323,** of Littell Multi-Switches, series 35000, 36000, 37000, 38000. 10 pages, photos, drawings, specs of illuminated and nonilluminated switches, ganged assemblies, accessories, special functions.—**Switchcraft Inc.**  
Circle 85 on reader's service card

**CONTROL KNOBS BROCHURE,** 4 pages, illustrated, with military specs of the KMS series of knobs.—**National Radio Co., Inc.**  
Circle 86 on reader's service card

**POWER SUPPLY CATALOG,** 48 pages, photos, diagrams, application notes, nomogram of voltage drop, glossary. Supplies indexed by output voltage.—**Kepeco, Inc.**  
Circle 87 on reader's service card

**QUICK-REFERENCE METER CATALOG, M865,** 12 pages, cross-section of complete line of custom-built panel and switchboard meters.—**Hickok Electrical Instrument Co.**  
Circle 88 on reader's service card

**CANADIAN MAIL-ORDER CATALOG,** introductory No. 1, features hi-fi, test equipment, tools, tape recorders, transceivers, etc.—**Gladstone Electronic Supply Co.**  
Circle 89 on reader's service card

**CB AND HAM EQUIPMENT CATALOG.** 12 pages of CB, commercial, amateur antennas; fixed-station, portable, mobile, tone-signaling CB equipment; mobile mounts and springs; accessories (shielding systems).—**Webster Band Spanner**  
Circle 90 on reader's service card

**SPECTRUM ANALYZER BOOKLET,** 8 pages, titled "Getting Acquainted with Spectrum Analyzers." General discussion of the electromagnetic spectrum, nature of signals in various radio-frequency bands, heterodyning, related problems of analysis.—**Tektronix, Inc.**  
Circle 91 on reader's service card

**DESIGNER DATA BOOK,** 45 pages. "Piezoelectric Technology—Data for Designers." Principles of piezoelectricity, characteristics of materials, applications.—**Piezoelectric Div. of Clevite Corp.**  
Circle 92 on reader's service card

**CATALOG 65/66,** 65 pages, photos. Wire, cable, tubing, hardware, switches, radio-TV accessories, components, government and commercial specifications.—**Birnbach Radio Co. Inc.**  
Circle 93 on reader's service card

**FACTORY PRICE LIST,** quantities 1 to 999, of Texas Instruments' semiconductor products. 24 pages, looseleaf-punched, from their distributor in New York, Delaware Valley and Washington.—**Milgray**  
Circle 94 on reader's service card

**APPLICATION NEWS, Vol. 3, No. 2,** 15 pages. Contains an illustrated paper called "A New Method for Precise Voltage Regulation for Use with Photomultipliers." Also other gas-tube applications, most contributed by readers.—**Signalite, Inc.**  
Circle 95 on reader's service card

**TERMINAL-BLOCK/BARRIER-STRIP CATALOG, No. XLX-7A.** Items formerly manufactured by Excellex Electronics Inc.—**Eby Sales Co. Inc.**  
Circle 96 on reader's service card

**CATALOG, No. 252,** "1965 Gift Season Specials". 82 pages, color photographs. Bargains in hi-fi, tape recorders, cabinetry, mikes, test equipment, many other gift ideas.—**Allied Radio**  
Circle 97 on reader's service card

**SWITCH CATALOG,** 4 pages, looseleaf punched, lists **ECCoSWITCH Series 700/800** sealed and lighted subminiature thumb-wheel switches. Includes specs, output code tables, and covers related mounting hardware.—**ECCoSWITCH, Div. of Engineered Electronics Co.**  
Circle 98 on reader's service card

**TEST AND REPAIR INSTRUMENT CATALOG,** 8 pages; photos, specs, of tube testers, component substitutor, capacitor tester, signal generator, CRT tester-reactivator, color TV analyzer, multi-head pix-tube adapter, voltmeter, vom.—**Mercury Electronics Corp.**  
Circle 99 on reader's service card

Write direct to the manufacturers for information on the items listed below:

**TV CHASSIS SERVICE MANUAL, Singlpak.** At 79 cents each, all the TV service manuals of top line TV set manufacturers for the years 1955 through 1965.—**Singlpak, Inc.,** 58 Stewart Ave., New Hyde Park, N. Y.

**APPLICATION NOTE, No. 69,** 40 pages, titled "Which DC Voltmeter?" explains available types of multirange analog and digital meters and the reasons for their existence, tells how to minimize the effect of unwanted signals. Analyzed from point of view of applications.—**Hewlett-Packard,** PO Box 301, Loveland, Colo. 80537  
END

## HOW YOU SEE COLOR —

in color TV. Read how the three-gun, shadow-mask picture tube really works. (It's used in every US-made color set.) Also, get astonishing details on an entirely different kind of color tube—that has only one beam, no convergence or degaussing nuisance.

Coming in January  
**RADIO-ELECTRONICS —**  
the 3rd Annual Color-TV Issue


## RIAA ISSUES TAPE STANDARD

The curves below show the new RIAA playback response standard for magnetic tape at 3¾ and 7½ inches per second. The 7½-ips curve is the same as the long-time NAB 15-ips standard; the 3¾-ips curve is new, but differs from the higher-speed characteristic only in having less high-frequency rolloff, to compensate for the poorer high-frequency response at the slower speed.



In terms of time constants, the new curves are described by the same low-frequency constant: 3,180 μsec. The

high-frequency constant of the 7½-ips curve is 50 μsec; that of the 3¾-ips curve, 90 μsec.

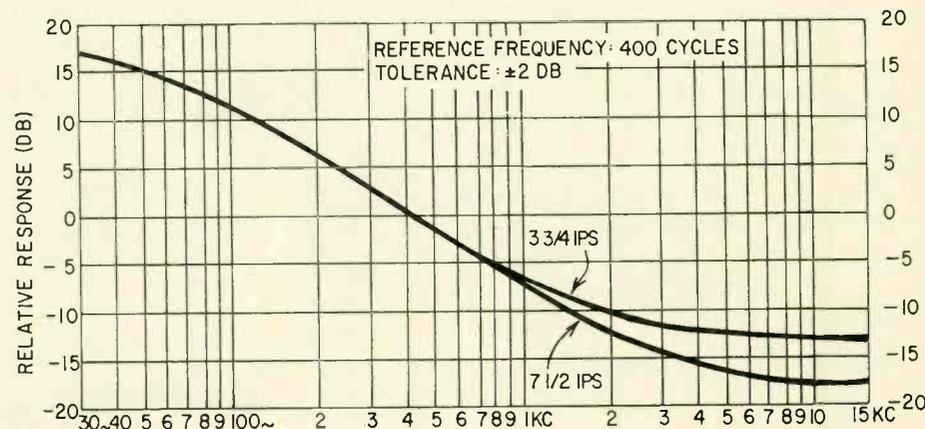The curve is drawn and described in the RIAA's Bulletin No. E5, issued July 15, 1965. The leaflet, titled "Standards for Magnetic Tape Records", also covers speed, dimensions, direction of tape wind, and sequence of tracks in two, four and eight-track recordings. Copies are available from the Record Industry Association of America, 1 E. 57th St., New York, N.Y. 10022


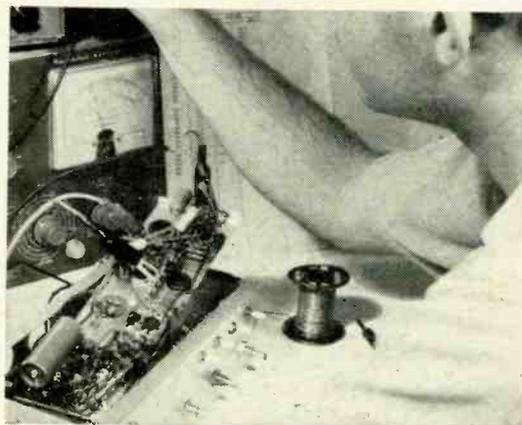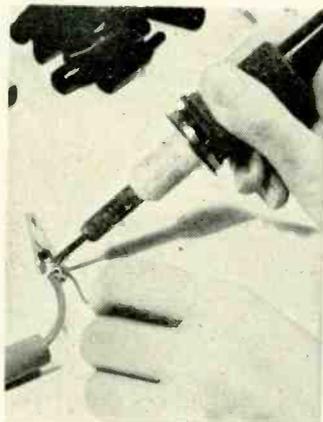
# AT LAST, A REALLY PRACTICAL WAY TO build your electronics know-how . . . boost your income and prestige and make substantial savings on the most valuable handbooks you can own!



## Accept your risk-free membership in the famous Electronics Book Club and enjoy these advantages now!

Everyone talks about the great future of Electronics—but how many people are really doing something about it? If you are the one man in seven who is determined to get ahead in electronics—who wants to cash in on the steadily increasing demand for trained technicians—the Electronics Book Club has astonishing benefits for you.

Your membership in this unique book Club will help you to protect your future . . . increase your knowledge and earning power . . . keep you up-to-date on all the latest electronic developments . . . and bring you greater enjoyment from leisure hours if electronics is your hobby.

### SPECIAL INVITATION

Judge for yourself, without risk, what the Electronics Book Club can do for you. Examine the special introductory offer on the opposite page. See how you can receive your choice of \$25 electronics self-training programs for only \$2, with membership.


**TAKE YOUR CHOICE** of either of these outstanding electronics self-training programs for only \$2—with membership in the Electronics Book Club. Perhaps you want the course on **HOW TO FIX TRANSISTOR RADIOS AND PRINTED CIRCUITS**; or maybe you'll choose **RADIO SERVICING MADE EASY**. Whichever you take, remember this: both originally sold for \$25 each as home-learning courses; Now they're available in two-volume book-format. Take your pick at once as your introduction to membership.

**RISK-FREE GUARANTEE:** You enjoy this *air-tight, no questions-asked guarantee*: If you are not pleased when you receive these books, you may return them in good condition in 10 days and cancel your membership, and that will end the matter.

**7 EXCLUSIVE MEMBERSHIP BENEFITS:** (1) Members are offered the widest possible range of books covering everything in electronics from repair, troubleshooting and building . . . to experimental and hobby projects . . . to self-teaching handbooks on important areas of electronics; (2) The Club saves you up to 30% off the regular retail prices on electronics books that interest you most; (3) Club books are *practical working tools* written to give you clear answers, help you solve problems, increase your know-how and electronics enjoyment; (4) You receive only the books you want because the Club News-bulletin tells you about the books every other month so you can accept or reject them *in advance*; (5) Special charts and reports are now given **FREE** with many Club selections to expand and illuminate the text; (6) *You need send no money in advance*; you pay for your books after you receive and examine them and decide to keep them; (7) Permanent Risk-FREE Guarantee: if you are ever dissatisfied with a book, you may return it in 10 days for full credit.

**Mail valuable coupon on opposite page** ➤

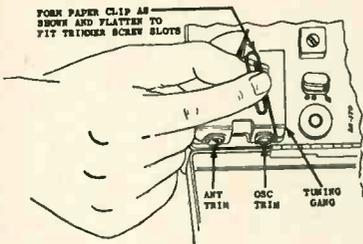**DO YOU KNOW HOW**  
A paper clip can be used for  
adjustment of the trimmer?



**GANG TRIMMER ADJUSTMENT  
TOOL DETAIL**

Fig. 1012. A paper clip can be used for adjustment of the trimmer.

For more information, see page 91  
in volume 2 of **HOW TO FIX TRANSISTOR  
RADIOS AND PRINTED CIRCUITS**

# Which of these \$25 electronics self-training programs do you want for ONLY \$2—

with risk-free membership in  
**the Electronics Book Club:**

simply take 4 additional books  
within a year at low Club prices!

**DO YOU KNOW HOW**  
to draw the circuit for  
a manual noise limiter?


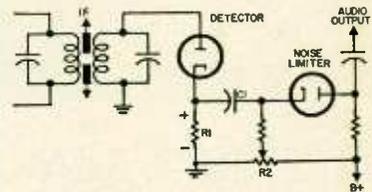


Fig. 918. This noise-limiting circuit has to be adjusted for noise conditions. It is called a manual noise limiter (mnl).


For more information — see page 117  
in Volume 2 of **RADIO SERVICING  
MADE EASY**

Here is a complete course on fixing transistor radios and printed circuits in **TWO DELUXE, HARD BOUND VOLUMES**. Written by expert, Leonard C. Lane, it was originally developed as a \$25 home study program. It's yours for only \$2 with membership. It treats every aspect of transistors, much of it new, original, unavailable anywhere else in book form. Hundreds of illustrations aid understanding. Completely covers semiconductor fundamentals, how transistors work, transistor types, amplifiers, RF and IF stages, printed circuits, specific servicing methods and techniques. Gives answers to hundreds of questions including those on trouble in the audio section, working with printed-circuit boards, signal generators, the vtm, defects and repairs, soldering techniques and useful tools, speaker defects, volume control, surface-barrier transistor, silicon transistors, transistors at work, servicing chart, antennas on auto radios, dc to dc converter, and many many other subjects.

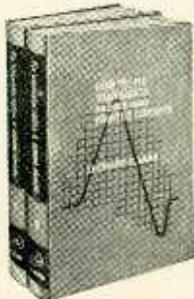

This important two-volume set was originally prepared as a \$25 home-study course by famed technician and writer Leonard C. Lane. Now you receive *both* deluxe hard bound volumes for only \$2 with membership. Tells you everything you want

and need to know about radio servicing in clear, down-to-earth language. Just a few of the many answers you will receive: Working with transistors. Getting started with transistors. Approaching the transistor. Testing transistors and printed circuits. Things to remember. Checking transistors. Servicing transistor radios. Servicing the transistor receiver. Stage-by-stage analysis. Servicing auto radios. Installation and removal. AM receivers. Frequency range. Ac-dc power supplies. Troubleshooting. FM receivers. AM-FM tuners. Why should we have tuners? Communications receivers. Frequency range. Voltage stabilization. Noise limiters. Checking the gain control. Single-sideband reception. Marine receivers. Marine frequencies. The beacon band. The marine band. Mobile radio.

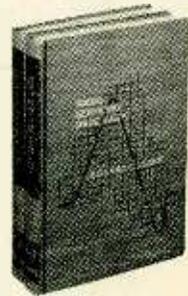

## MAIL THIS VALUABLE COUPON TODAY!

It will bring you *either* of these **TWO-VOLUME TRAINING COURSES** for only \$2—when you join the Electronics Book Club . . . and agree to take only 4 additional books within a year—out of a wide selection that will be offered—all at *low Club prices*. Thousands of others have already profited from membership. Discover now how you can profit too!

## ENJOY THIS RISK-FREE GUARANTEE!

Select your **TWO-VOLUME**, deluxe, hardbound **SET** of books right now. Clip and mail coupon today, while supplies last. You will be protected by this **RISK-FREE GUARANTEE**: if you are not pleased when you receive the books, you may return them in 10 days and forget the matter. Mail coupon right away.

### Gernsback Library **ELECTRONICS BOOK CLUB**

c/o Dept. RE-1265

154 West 14th Street, New York, N.Y. 10011

Please enroll me as a member of the Electronics Book Club and send me one of the **TWO VOLUME SETS** checked below:

How to Fix Transistor Radios and Printed Circuits    **OR**     Radio Servicing Made Easy

Bill me only \$2 plus shipping. If not pleased, I may return both books in 10 days and this membership will be cancelled.

I need only accept as few as four additional books a year—and may resign any time after purchasing these four additional books. All selections will be described to me in advance, every other month, in the Club Bulletin, and a convenient form will always be provided for my use if I do not wish to receive a forthcoming selection. You will bill me the special Club price for each book I take. This will often be as much as 30% off retail prices, plus a few cents postage.

Name ..... (please print)

Address .....


City ..... State ..... Zip Code No. ....

**SAVE POSTAGE COSTS**—enclose your payment of \$2 now and we will pay postage. Same return guarantee privilege.

# Recommend the TURNER 500 Cardioid


**DON'T GO WRONG  
... GO TURNER**

In your business, your reputation depends on your recommendation. Don't risk either — always recommend the high-performing, trouble-free Turner 500 Cardioid. Most problems in PA or sound applications — extraneous noises, poor acoustics, etc. — can be successfully solved by incorporating Turner 500's into the system. So before you make your next installation, write for the complete Turner catalog. Get details on the Model 500 — list price \$84.00 — and the rest of the Turner line, including the popular and versatile microphones shown below.

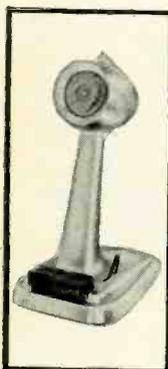

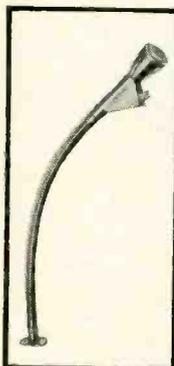
**MODEL 251**

Low cost, high performance paging microphone with Turner's unique lift-to-talk feature. List price \$49.50




**MODEL SR5850**

Fixed mounted microphone conveniently mounted on a flexible 16" gooseneck. List price \$40.

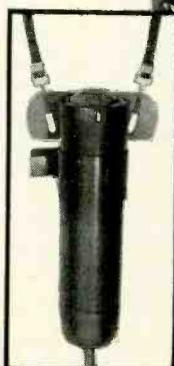

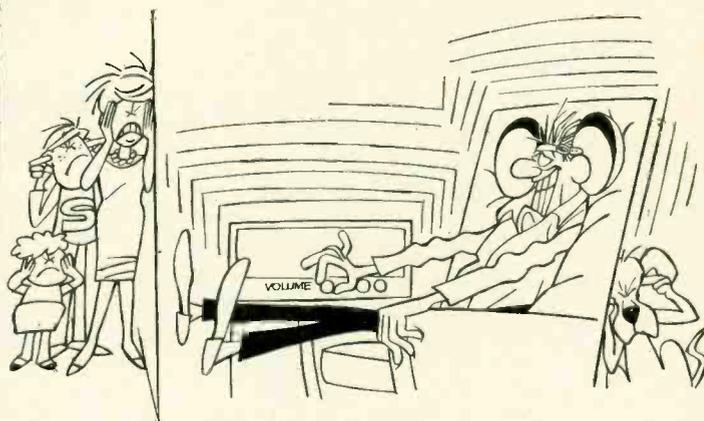**MODEL 58**

A natural for any application requiring freedom and mobility ... does double-duty on desk stand. List price \$57.



## THE SEARCH FOR SOUND

By **ELBERT ROBERSON**

I DON'T SEE LARRY ANY MORE. NOBODY SEES HIM. NOT EVEN his wife, Ellen. She left, taking their kids and everything in the house but the sound.

I know the mover. "The guy acted nuts," he told me. "He kept yelling, 'Don't touch this room!' I told him to cool it—I wasn't after that stuff. Another thing—why would a guy wear a hat in the house in August?"

I remember when it started. Larry came into the shop, quietly browsing around, spinning the turntables, hefting the tone arms. Then he turned to the speakers lined up open on the shelf. Lightly he tapped his fingertips on the cones. "Tump, tump," he would go, then move to the next speaker, cocking his head first one way and then the other as he tumped.

"There shouldn't be any coloration," he said. He tumped on a cone. "This one rings."

He carried out a box of Bozaks—a woofer, a squawker and a tweeter. The second load was a McIntosh preamp and 50-watter, and his third a professional turntable. He didn't raise his voice over the price, just asked me to help hook up the system.

That evening, I did. He had a nice wall-to-wall house, some fair paintings, well behaved kids, and a pleasant blonde wife. When we were finished, she offered me a drink, as Larry put a record on the turntable, set the knobs to "flat" and settled back in the deep chair with his eyes closed.

"Listen to that dynamic range," he breathed during a lull.

"But why so loud?" Ellen asked. She made a flat-handed motion toward her ears, crinkling her nose.

"Has to be, so you can get the quiet passages. Listen—did you hear that? He hums while he plays!"

Ellen winked me out the door. "He'll get over it."

"Yeah, the novelty wears off. And thanks for the drink."

The second time I visited was to bring a tape deck. There were some strays in Ellen's coif, and the kids were commandos.

**THE TURNER MICROPHONE COMPANY**  
933 17th Street N.E.  
Cedar Rapids, Iowa

In Canada: Tri-Tel Associates, Ltd.

Export: Ad Auriema Inc., 85 Broad Street, New York 4, N.Y.

Circle 114 on reader's service card

"He's in there," Ellen said, jerking her head. "It's the Sound Room, now."

In the other room a steam locomotive was whistling for a grade crossing, its connecting rods clanking and the wheels clicking on the rail ends. One of the boxcar wheels thumped from a flat—they get that way when the brakes lock on a downgrade. Ellen shook her head and sighed. "I ask him why doesn't he just go down to the freight yard, if that's what he wants to hear. But that's too far from the gold-mine stamp mill on the next band."

Larry was hunched in his chair, hands cupped behind his ears. "This does things for the sound," he said to me. "Try it. You get it all—nothing goes by."

I did. "I see what you mean," I said.

"What did you say?"

"It . . ."

"It fills in the whole sound," he shouted. "Puts you right there."

I connected up the tape deck and left. Ellen waved a wet hand from the kitchen. "See you," she said.

What comes after a professional turntable, tape deck, a monaural amplifier and speakers? Stereo, naturally. This was a whole new setup: double amplifiers, new matched speakers. And Larry wanted more power.

When I came to make the hookup, Ellen was rushing out, makeup dabbed. She yelled at one of the kids. "Tie that shoelace, idiot, before you trip and break your little neck! We're off to the drive-in," she explained, then slammed the door.

Larry was in his chair, head centered between two curved reflectors that reached out like metal clam shells growing from his ears.

"Had these especially cast from my own patterns," he yelled. "Quarter-inch-thick aluminum, no resonance. Sound gathering is tremendous. Leave the stuff—I'll hook it up later."

"Why don't you get earphones," I asked. "We've got some that go from below 50 cycles to above 15,000."

"You'll have to talk louder," he yelled.

"Earphones . . ." I started.

"Can't wear 'em. Besides, you lose the depth, and the room."

As I left, I wondered what sound ¼-inch reflectors could bring out of a bank of fiddles that wasn't already present.

There was a long lapse, with no Larry. Then I got a note, asking me to drop by.

At the door, Larry yelled, "Pardon the delay—had to put a flasher on the doorbell; don't always notice it. Ellen's out, come on in."

Larry looked like the villain in a late-late movie. His head was shaved, and he had a couple of suction cups stuck to his skull.


"Bone conduction was all right for a while, but the reproducers just didn't have it. Now I'm trying electrical stimu-

### Coming next month Radio-Electronics 3rd Annual Color TV Issue

Information-packed issue, designed to bring you up-to-the-minute on everything that's happening in the field. Front-to-back, every word, picture and page will bring you facts you want to know . . . about how the color tube works, the latest sets and circuits, trends in tubes, parts, antennas, test equipment, progress and problems of color TV, how to rejuvenate old color sets, plus a valuable chart to help you spot TV color troubles in a hurry.

January Issue is on sale December 21st at your favorite newsstands and electronic parts distributors.

**A MUST  
FOR  
COLOR  
TV!**

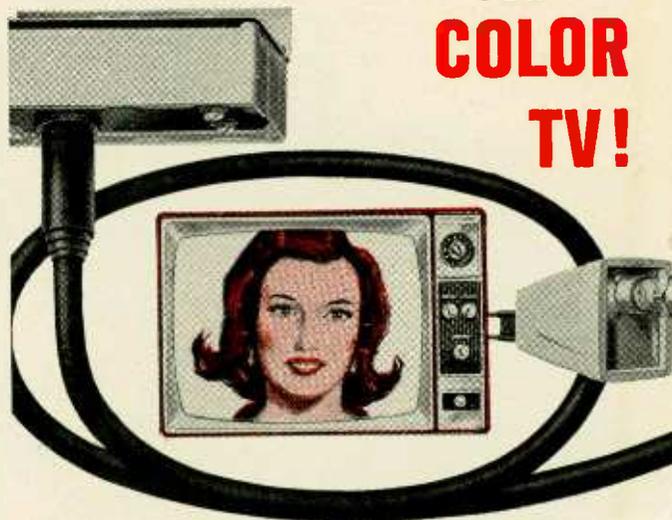

## NEW JERROLD COLORAXIAL™ Reception System

The old familiar twinlead, that worked pretty well for black-and-white TV, is hopelessly inadequate for color reception. When your customers complain about changes in color, ghosting, and smearing of pictures, chances are the fault lies squarely with the twinlead connecting the set to the antenna.

*What's the answer?* Jerrold announces the exciting Coloraxial TV Reception System—an absolute necessity for color, and also best for black-and-white and FM stereo. With Coloraxial, you can quickly convert any outdoor antenna to shielded coax operation. Installs anywhere in minutes, without need for standoff insulators or the fear of running near metal objects.

Your customers will welcome the predictable, perfect reception that's assured with a Coloraxial system. And you'll welcome the simplicity and profitability of a Coloraxial installation. Jerrold Coloraxial Kits give you everything you need for a quick, perfect job: 50 or 75 feet of sweep-tested, shielded RG-59/U cable with fittings already on; matching transformers for both ends of the cable—even Coloraxial (75-ohm) antennas and preamplifiers where the job calls for them.

Talk with your Jerrold distributor today about Coloraxial, or send coupon for complete information.

**JERROLD**

Jerrold Electronics Corporation  
Distributor Sales Division  
15th & Lehigh Ave., Philadelphia, Pa. 19132

Send me complete information on the new  
Jerrold Coloraxial TV Reception System.

Name \_\_\_\_\_

Company \_\_\_\_\_


Address \_\_\_\_\_

City \_\_\_\_\_ State \_\_\_\_\_ Zip \_\_\_\_\_

Circle 115 on reader's service card

# Me...? Rebuild Color Tubes???

*Why Not!*

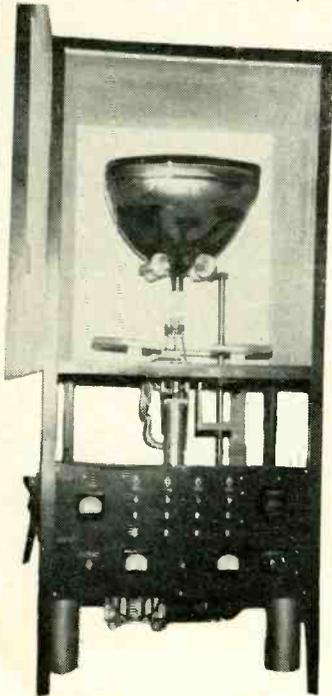

Windsor Equipment  
Handles Color & Bond-  
ed-Face As Well As  
Black-and-White Tubes.

## So What?

Rebuilding with Wind-  
sor is a **QUALITY  
PROCESS . . . and  
PROFITABLE !!!**

Rebuild Color Tubes for  
a Cost of \$11.75 each  
. . . You sell them for???

Windsor Equipment  
pays for itself in a few  
months.



Financing Available  
Free Training at our  
Plant

Write for our Booklet "The Open Door to TV Profits"

### WINDSOR ELECTRONICS, INC.

Equipment Division  
999 N. Main St., Glen Ellyn, Illinois

Circle 116 on reader's service card

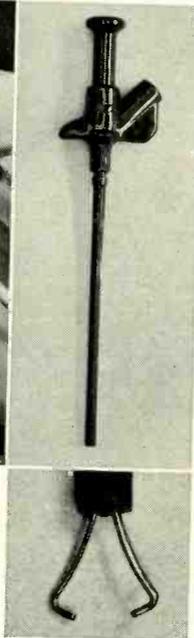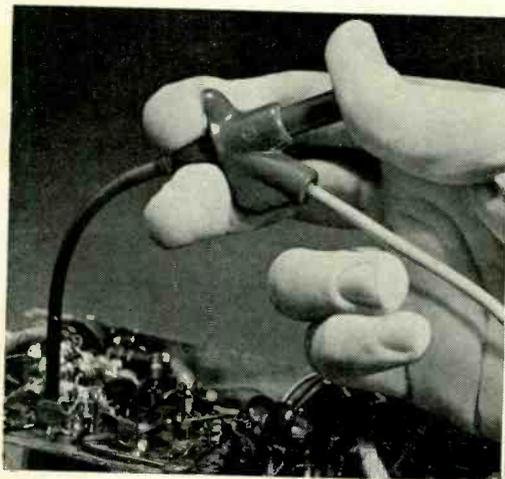

## Clever Kleps 30

Push the plunger. A spring-steel forked tongue spreads out. Like this  Hang it onto a wire or terminal, let go the plunger, and Kleps 30 holds tight. Bend it, pull it, let it carry dc, sine waves, pulses to 5,000 volts peak. Not a chance of a short. The other end takes a banana plug or a bare wire test lead. Slip on a bit of shield braid to make a shielded probe. What more could you want in a test probe?

**rye**  
SOUND

Available through your local distributor, or write to:

**\$147**

**RYE SOUND CORPORATION**  
123 Spencer Place, Mamaroneck, N.Y.

Circle 117 on reader's service card

lation, but the output impedance of these amplifiers doesn't match, and I wondered if you could fix me up with a couple of transformers. Wish you could hear this" he beamed. "It's the greatest! Gets the juice right to the auditory nerve without any distortion at all."

"If you step up the amplifier output impedance, the output voltage will go up, too," I told him.

"Speak into my ear," he said.

"You'll get a shock—a loud passage might knock you out."

"Oh, I know. I get some tingles now. Puts real body into it—you can really feel it!"

"The damn fool," I thought. But I connected him up to the 70-volt taps on his amplifiers.

His smile was beatific. I got out as quickly as I could.

Time passed. Then I got a note from Larry. It started: "To get the proper stimulus, the voltage had to be too high, and it knocked me out a couple of times. I've read that doctors have been able to implant needle electrodes directly into the nerves or brain to give full stimulus at lower voltages. I thought you might know a doctor who has worked in medical electricity. . . ."

I quit reading. Isn't there some agency, some law against driving yourself crazy? Electro-shock could make a nice quiet moron out of him. I called a doctor friend.

"As long as he's not my patient, I can't stop him," he said. "Is he hurting anybody?"

"Just himself and his family."


"Can you prove it? If they don't complain, you could find yourself in trouble, making accusations you can't back up."

"But the guy's nuts—he ought to be taken care of!"

"Aren't all of us, a little?"

I hung up. But the question still churned: there must be something that can be done before it's too late! Too late? Then I remembered the rest of what the mover had said: ". . . a hat in the house in August—with wires coming out from under!"

END

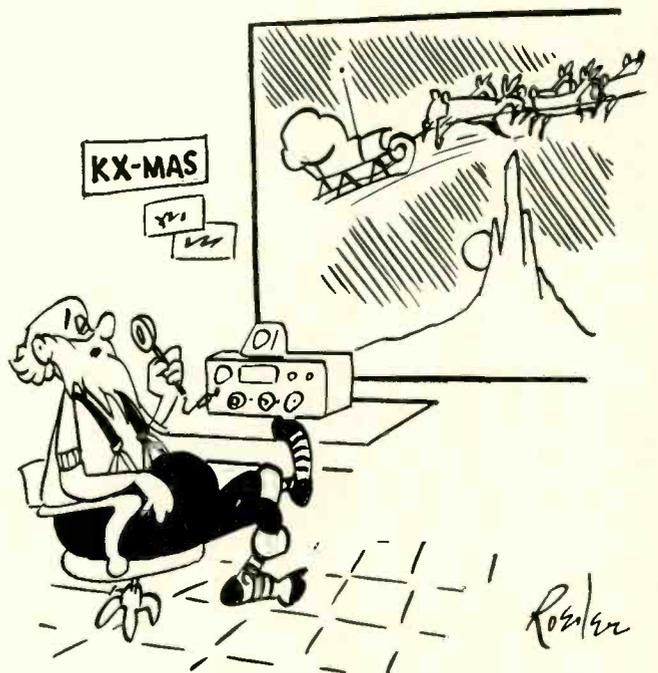

"On Dancer, on Prancer, on Donder and Blitzen"

RADIO-ELECTRONICS

Coming Next Month

# Radio-Electronics



Here are a few of the exciting features you'll be reading:

- How you see color—an analysis of how the color tube works.
- Roundup of 1966 color sets. A complete directory that gives you the lowdown on features and circuits in new color TV receivers. It's a valuable reference for set owner and service technician alike.
- A rundown on the latest color test equipment for service technicians and experimenters.
- Color TV trends in tubes, parts, antennas.
- A report on the progress and problems of Color TV.
- Special chart to spot TV color troubles.
- Convergence in basic English: why it's needed, how it's done.
- Rejuvenating old color TV sets.

Plus many other articles of vital interest to you!

**JANUARY ISSUE on sale December 21  
AT YOUR FAVORITE NEWSSTANDS  
AND ELECTRONIC PARTS DISTRIBUTORS**

Live Better Electronically With

# LAFAYETTE RADIO ELECTRONICS FREE!



**512  
Pages**

**1966  
Catalog  
660**

## Now BETTER THAN EVER

*Featuring Everything in Electronics for*  
**• HOME • INDUSTRY • LABORATORY**  
*from the*  
**"World's Hi-Fi & Electronics Center"**


Stereo Hi-Fi • Citizens Band • Ham Gear • Tape Recorders • Test Equipment • TV and Radio Tubes and Parts • Cameras • Auto Accessories • Musical Instruments • Tools • Books



**CRITERION 1000B  
4-TRACK STEREO  
RECORDER IN  
TEAK CABINET**



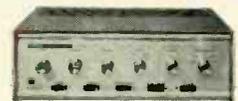**"PRO-50" COMPACT SOLID  
STATE COMPONENT STEREO  
MUSIC SYSTEM**



**50-WATT SOLID STATE  
STEREO AMPLIFIER  
MODEL LA-248**

**Mail the Coupon Today for Your  
FREE 1966 Lafayette Catalog 660**

**LAFAYETTE Radio ELECTRONICS**

Dept. JL-5, P.O. Box 10

Syosset, L.I., N.Y. 11791

Send me the Free 1966 Lafayette Catalog 660

Name .....

Address .....

City .....

State ..... Zip .....

(Please Give Your Zip Code No.)

Circle 118 on reader's service card

# 1965 SEMI-ANNUAL INDEX

RADIO-ELECTRONICS July-December 1965 of Vol XXXVI

## A

Abbreviations, our standard	Dec 22
Add Zero-Setter to Ac Vtvm (Greenlee)	Dec 69
Alarm	
Pluto Tells Where It Is (Brown)*	Aug 50
Antenna	
Longest in world built in Antarctic (NB)	Jul 8
Pigtail, Check That	Dec 50
Rotator Remote Control for TV, CB and Hams (Bintliff)*	Jul 46
Are We Really Making Progress? (Davis)	Dec 34
<b>AUDIO—HIGH FIDELITY—STEREO—see also Servicing, Audio</b>	
<b>Amplifiers</b>	
Complementary Amplifier/Loudspeakers, New Designs in (Augsburger)	Nov 48
Latest Transistor Power Designs (Meyer)	Oct 38
Output stages, matching transistors in (NC)	Jul 80
Transistor, Output Circuit Protection for (Sutheim) (Corres)	Sep 16
Two-State (Crowhurst)*§	
Part I—Principles	Jul 54
Part II—40 Watts in 40 Ounces!	Aug 35
Part III—Construction	Oct 34
Colorgan (Lancaster)*	Aug 44
Concert Hall Gets New Sound (Moir)	Aug 44
Delay Line, What's A (Kramer)	Sep 56
Feedback, Phase and Instability (Crowhurst)	Dec 56
40 Watts in 40 Ounces!—Two-State Amplifier (Crowhurst)*§ Aug 35;	Sep 48
Filters for Recording FM Stereo (Blechman)	Jul 48
"Message Center," Home, Features Electronic Stop (Scott)	Dec 42
Microphones, Magneto-resistive Mike adapter, miniature, to standard phono jack (TTO)	Aug 86
Organ, We Built an Electronic (Shunaman)	Dec 40
Public Address	
Concert Hall Gets New Sound (Moir)	Aug 44
Old-Timer Builds the Intercombo (Darr)	Oct 46
Receiver, Harman-Kardon SR-900†	Jul 65
Recording, electrical, 40 years old (NB)	Jul 4
Search for Sound (Robberson)	Dec 80
Speaker balancing record (KCS)†	Oct 67
Speaker System (Sonotone RM2)†	Dec 54
Squelch, fail-safe (NC)	Aug 82
Stereo	
Amplifiers	
Headset Hi-fi (Shure Solo-phone) (Sutheim)	Oct 66
T-40/40: 80-Watt All-Transistor (Meyer)*§ (Corr)	Aug 62
Center channel for (NC)	Dec 94
Filters for Recording FM Stereo (Blechman)	Jul 48
FM tuner/amplifier, solid-state (Eico 3566)†	Aug 64
Pickup (Euphonics Miniconic semi-conductor)†	Sep 66
Tape Players for Your Car (Blechman)	Sep 34
Tape Recorders	
How They Work (Smith) (Corres)	Aug 12
VOX for (Corres)	Aug 14
Tape Standard, RIAA Issues	Dec 77
Turntable Wow and Flutter, Measuring (Villchur)	Jul 32
Wow and Flutter, Measuring Turntable (Villchur)	Jul 32
<b>AUTOMOBILE</b>	
Analyzer, Service Your Car with Electronic Auto (Dezettel)	Jul 38
Ignition	
Dwell angle, setting (TTO)	Sept 91
System, electronic, uses photocell breaker (NB)	Aug 4
Transistor (Corres)	Aug 15, Sep 13, Nov 16
Piston-ring blowby located by electronic analytical procedure (NB)	Dec 8
Radio	
New Life for Old (Burr) (Corres)	Jul 12, 13
Servicing—see Servicing, Radio	
Tachometer makes hard starting (Corres)	Dec 12
Tachometer, Reliable (Gross)*§	Sep 54
Tape Players (Blechman) Sep 34; (Corres)	Nov 14

## KEY TO SYMBOLS AND ABBREVIATIONS

* Construction Articles	
† Section of full-length article	
§ Transistorized	
Cl	Service Clinic
Corr	Correction
Corres	Correspondence
NB	News Briefs
NC	Noteworthy Circuits
Tech	Techniques
TTO	Try This One
WN	What's New
	Regular departments not itemized are New Books, New Literature, New Products, What's Your EQ?

## B

Boat's Electronics, Launching (Robberson) (Corres)	Jul 13
Broadcast Engineering: Radio (Career Series) (Darr)	Jul 50
Burnout-proof Your Volt for Less Than Dollar (Dezettel)	Nov 39
Busy-Box—Thinking Tot's Toy (Tiso)*	Dec 44

## C

Calibrate Your Scope (Middleton) (Career Series)	Nov 36
Broadcast Engineering: Radio (Darr)	Jul 50
Engineers' Right-hand Men (Leslie)	Sep 53
Factory Analyzer (Wheeler)	Dec 51
CB i.f.'s on the Nose (Conhaim)	Aug 52
Change Plus-Ground to Minus-Ground	Aug 34
Check That Antenna Pigtail	Dec 50
Chokes, low-inductance, high-current (NC)	Sep 96
Coax Isn't All That Great (Finkel)	Sep 100
Code-Practice Oscillator—on a Key (Chesson)*§	Jul 53
Colorgan (Lancaster)*	Oct 34
Come Along on CB Service Call (Mivec) (Corres)	Nov 16
Component Curve Tracer (Blechman)*	Nov 52
Concert Hall Gets New Sound (Moir)	Aug 44
Convergence by ABC's (Middleton)	Aug 39
Cycloids for Frequency Measurement (Jaski)*	Jul 60

## D

De Luxe Printing Timer (Ives)*	Dec 48
Diode RF Switches (Math)	Sep 40
Do You Understand What You Read on Meter? (Margolis)	Nov 46

## E

Easy Alignment with Semi-Sweeper (Stoner)*§	Sep 37
<b>EDITORIAL</b>	
Electromedicine: End of Wonder-Drug Era? (Hixson)	Jul 27
Electronics and Programmer Instruction (Jaski) Aug 31; (Corres) (Allen)	Oct 53
End of Service Technician? (Shunaman) (Corres)	Sep 33;
Fuel Cells (Gernsback)	Dec 10
High Fidelity, What Is (Goldmark) (Corres)	Dec 31
Past and Future of Test Equipment (Meagher)	Aug 15
Television in Space (Gernsback)	Nov 33
Educational Television	Oct 33
Delaware initiates state-wide system (NE)	Oct 4
Done with mirrors in French classroom (NB)	Jul 6
Electronic writing unit competitor to (NB)	Jul 4
Phonograph records, pictures on (NB)	Jul 9
Writing unit competitor (NB)	Jul 4

## ELECTRONICS

Chokes, low inductance, high-current (NC)	Sep 96
Coaxial cable handles 32,400 channels (NB)	Nov 6
Coils, massive final (WN)	Nov 45
Computer rounds up scaffolds (NB)	Nov 4
Electrolytic, Make Variable (Jaski)	Oct 52
Electro-optical scanner (WN)	Dec 43
Fence Charger, SCR (Hansen)*§	Jul 35
Fuel-cell system, experimental (WN)	Nov 45
Ion Gage—Tube Looking for Vacuum (Sinclair)	Dec 58

Pressure Cells Aid Civil Engineers (Essex)	Aug 54
Landing system in a suitcase, automatic (NB)	Oct 4
LCR bridge, 10-turn pot is heart of (NC)	Oct 104
Streamers of light (WN)	Dec 43
Microwave Motors—Space-Age Power? (Stockman)*	Oct 42
Microwave frequency multiplier shows 4-db power gain	Dec 4
Music, What Is (Seawright) (Corres)	Sep 16
Newspaper, automated, established in England (NB)	Dec 4
Nomogram, do-it-yourself (Corres)	Jul 14
Oscillator, optical-frequency, can now be tuned (NB)	Oct 4
Q, Measuring with Scope (Cohn)	Oct 61
Solar Cells: Space Power (Stoner)	Aug 32
TCS's, Make Own (Lavender)*§	Oct 58
Transformers, Using surplus (TTO)	Dec 92
Typesetting and TV trends (NB)	Jul 4
Voltage Doubler Doesn't Really (Patrick)	Aug 56
Engineers' Right-hand Men (Career Series) (Leslie)	Sep 53
Exposure Meter (Knight-Kit KG-275)†	Oct 45

## F

Factory Analyzer (Career Series) (Wheeler)	Dec 51
Feedback, Phase and Instability (Crowhurst)	Dec 56
Fence Charger, SCR Electronic (Hansen)*§	Jul 35
Filters for Recording FM Stereo (Blechman)	Jul 48

## FM

Antenna, master, on Empire State (NB)	Jul 4
Stereo, Filters for Recording (Blechman)* Tuner/amplifier, solid-state (Eico 3566)†	Jul 48
	Aug 64
Foolproofing the Transistor Duo (Turner)	Sep 39
40 Watts in 40 Ounces!—Two-State Amplifier (Crowhurst)*	Aug 35; Sep 48

## G

Garage-door openers jam air navigation (NB)	Aug 4
Get All TV Channels (Reinken) (Corres)	Sep 12

## H

Headset Hi-fi: Shure Solo-phone Stereo Amplifier (Sutheim)	Oct 66
Home "Message Center" Features Electronic Stop (Scott)	Dec 42
How to Set Up Color Bar Generator Wrong (Darr)	Nov 94
How Tape Recorders Work (Smith) (Corres)	Aug 12
How to Track Interference (Haskett)	Dec 32
How to Wide-Band Scope (Turner)*	Aug 58

## I

Inductance Checker and Tone Generator (Poskelsky)*§ (Corres)	Aug 14
Industrial Electronics	
Long Arm of Remote Control (Dietrich)	Aug 60
Servo Amplifier Has Heavy Feedback	Jul 39
Intercombo, Old-Timer Build the (Darr)	Oct 46
Intercom-radio circuit, novel (NC)	Aug 83
Ion Gage—Tube Looking for Vacuum (Sinclair)	Dec 58

## K

Keyed Circuit, What's a (Darr)	Jul 37
--------------------------------	--------

## L

<b>Laser(s)</b>	
Astronauts plan communication to earth with (NB)	Sep 4
Beam, 2-mile, generated by multiple reflections (NB)	Jul 8
Flowing gas, has 16 watts output (NB)	Oct 4
Fog detector (NB)	Jul 6
Light detector has high sensitivity, speed (NB)	Dec 4
Transmitter (WN)	Nov 45
Latest Transistor Power Amplifier Designs (Meyer)	Oct 38
Long Arm of Remote Control (Dietrich)	Aug 60
Launching the Boat's Electronics (Robberson) (Corres)	Jul 13
Look Inside Amplifier (Baird) (Corres)	Aug 43; Dec 12

## M

Magneto-resistive Microphones	Aug 38
Make a Variable Electrolytic (Jaski)	Oct 52
Make Your Own TCS's (Lavender)*§	Oct 58
MATV, Plug In to (Cantor)	Jul 28
Measuring Q with a Scope (Cohn)	Oct 61
Measuring Turntable Wow and Flutter (Villchur)	Jul 32
Medicine	
Heartbeats analyzed ultrasonically (NB)	Dec 4
"Mongolism" linked to radar (NB)	Dec 6
Muscle Stimulator (Breskend)*§ (Corres)	Aug 14; Dec 10
Television tranquilizes caged gorillas (NB)	Aug 4



Signal-Makers, Complete Directory	Nov 60
Solar Cells: Space Power (Stoner)	Aug 32
Solid-State Muscle Stimulator (Breskind)*§ (Corres)	Aug 14
Space	
Digital TV, Mariner-earth transmissions use (NB)	Sep 6
Laser beam, astronauts plan communication to earth with (NB)	Sep 4
Martian ionosphere weak (NB)	Sep 6
Rf interference injures space vehicles (NB)	Sep 4
Spurious Radiation from 42-Mc. 1.f. TV Sets (Austin)	Oct 54
Switches, Diode Rf (Math)	Sep 40

**T**

T40/40: 80-Watt All Transistor Stereo Amplifier (Meyer)*§ (Corr)	Aug 62
Tachometer, Reliable (Gross)*†	Sep 54
Tape Players for Your Car (Blechman) Sep 34; (Corres)	Nov 14
TCS's, Make Your Own (Lavender)*§	Oct 58
Telephone	
Bandwidth, new trick squeezes	Nov 96
Sensicall for deaf (WN)	Dec 43
Subway system, for New York, leaky-coax (NB)	Aug 6
Writing unit competitor to CCTV (NB)	Jul 4
TELEVISION—see also Servicing, Television	
Antenna(s)	
Ears so good, maybe foot is better? (NB)	Aug 8
Master, setting up (CI)	Oct 22
MATV, Plug Into (Cantor)	Jul 28
Rotator Remote Control for TV, CB and Hams (Bintliff)*	Jul 46
Coax Isn't All That Great (Finkel)	Sep 100
Closed-circuit	
Competitor (NB)	Jul 4
Done with mirrors in French classroom (NB)	Jul 6
Prevents subway crime (NB)	Jul 4
Color	
Delay Line, What's (Kramer)	Sep 56
New G-E 11-inch (NB)	Jul 10

Tube, RCA 15-inch rectangular (NB)	Nov 4
Tubes, G-E will manufacture (NB)	Jul 10
Commercials	
Boycott campaign encourages good taste (NB)	Sep 4
FCC raps loud (NB)	Sep 7
Digital, Mariner-earth transmissions use (NB)	Sep 6
Keyed Circuit, What's (Darr)	Jul 37
Pay-TV	
California ban ruled unconstitutional (NB)	Aug 6
Destined to fail? (NB)	Oct 4
Phonograph records, pictures on (NB)	Jul 9
Portables	
Can be carried off (NB)	Jul 9
Pocket-size (WN)	Nov 45
Transistor (Scott)	Jul 40
Production to double in 2 years (NB)	Sep 4
Stations Packaged for Inexperienced Owner	Sep 58
Tape recorder	
Color or black-and-white (NB)	Sep 4
Home, to sell for less than \$1,000 (NB)	Aug 4
Ingenious pickoff (NB)	Aug 4
Variable-speed (NB)	Aug 8
30-kc bandwidth uses velocity scanning (NB)	Nov 12
Trends (NB)	Jul 4
Uhf	
Converting Vhf to, for Tests and Demonstrations	Jul 47
Philadelphia service techs promote (NB)	Oct 6
Stations, compact planned (NB)	Aug 4
Wasteland in Monte Carlo (NB)	Sep 6
Ten Transistor and Hybrid Auto Radio Troubles (Held)	Oct 49
TEST INSTRUMENTS—see also Servicing; Servicing, Test Instruments	
Amplifier, Look Inside (Baird)	Aug 43
Audio signal generator, continuous tuning for (Heath IG-72) (NC)	Sep 95
Auto Analyzer, Service Your Car with Electronic (Dezettel)*	Jul 38
Capacitor tester (B&K 801)*† Nov 72; (Mercury 1400 in-circuit)*†	Sep 66

Cheater box, fuse your (TTO)	Sep 91
Color Bar Generators	
How to Set Up Wrong (Darr)	Nov 94
New Concept in (Cervený)	Sep 59
Curve Tracer, Component (Blechman)*	Nov 52
Cyoloids for Frequency Measurements (Jaski)*	Jul 60
Dip Meter, Versatile (Turner)	Nov 42
Frequency Standard (Viking VFS)*†	Jul 65
Horizontal deflection circuit meter (Lectrotech T-100)*†	Oct 68
Inductance Checker and Tone Generator (Posklesky)*§ (Corres)	Aug 14
LCR bridge, 10-turn pot is heart of (NC)	Oct 104
Leakage detector (NC)	Sep 96
Meter, Do You Understand What You Read on (Margolis)	Nov 46
Meters, borrowing saves expense (Corres)	Jul 12
Multiplex Generator (Eico 342 FM)*†	Dec 64
Probes, ultrasonic (NB)	Dec 6
Scope	
Calibrate Your (Middleton)	Nov 36
Dc/wide-band (Eico 435)*†	Nov 73
Grid, easy-to-make (TTO)	Nov 100
Improvers (Carlson)	Dec 54
Measuring Q (Cohn)	Oct 61
Plug-In Unit Seeks Range, Shows Waveform	Dec 53
× 100 (Jaski)	Nov 56
Wide-Band Your (Turner)*	Aug 58
Semi-Sweeper, Easy Alignment with (Stoner)*§	Sep 37
Signal injector (NC)	Dec 94
Signal-Makers, Complete Directory	Nov 60
Square-wave adapter, simple signal-powered (NC)	Oct 105
Test record, speaker balancing (KCS)*†	Oct 66
Tone Generator and Inductance Checker (Posklesky)*§ (Corres)	Aug 14
Voltmeter	
Meterless Dc (Stasior)*	Nov 51
Volt-ohm-microammeter (Triplet 630-M)*†	Aug 64
Vom	
Scale Expander Measures Low Resistances (Roetger)*	Oct 44
Burnout-proof, for less than Dollar (Dezettel)	Nov 39
Vtvm (EMC 107A)*†	Nov 75
Zero-Setter for Ac (Greenlee)	Dec 69
Toilet Trainer, 20th Century	Oct 51
Tone Generator and Inductance Checker (Posklesky)*§ (Corres)	Aug 14
TRANSISTOR(S) (IZED)	
Coding, European (Corres)	Oct 14
Matching in audio output stages (NC)	Jul 80
Tube Portables (Pugh)	Dec 35
TV Portables (Scott)	Jul 40
Vacuum tube's day not yet over? (NB)	Jul 4
Tunnel Diodes detect sound (NB)	Aug 6
TV Picture on Oscilloscope Screen (Huneault)	Oct 92
TV Technician's Dictionary (Salerno)	Oct 41
TV Tuner Troubles (Darr)	Sep 45
Two-State Amplifier (Crowhurst)*§	
Part I—Principles	Jul 54
Part II—40 Watts in 40 Ounces!	Aug 35
Part III—Construction	Sep 48

**U**

Uhf	
Converting Vhf to, for Tests and Demonstrations	Jul 47
Philadelphia service techs promote (NB)	Oct 6
Station, compact planned (NB)	Aug 4

**V**

Variable Electrolytic, Make a (Jaski)	Oct 52
Versatile Dip Meter (Turner)	Nov 42
Voltage Doubler Doesn't Really (Patrick)	Aug 56
Vom Scale Expander Measures Low Resistances (Roetger)*	Oct 44

**W**

We Built An Electronic Organ! (Shunaman)	Dec 40
What, No Color? (Davidson)	Jul 57
What's a Delay Line (Kramer)	Sep 56
What's a Keyed Circuit (Darr)	Jul 37
What's Your Modulation % (Blechman)	Sep 41
Who Invented It? (Middleton)	Sep 44

**X Y Z**

Yoke Troubles (Darr)	Aug 47
Your Shop—Service Tool (Darr)	Nov 34

**Now save hours of design time  
with GERNSBACK LIBRARY'S new**

# ELECTRONIC DESIGN CHARTS

By Norman H. Crowhurst

- 59 CHARTS
- 128 PAGES
- FULL EXPLANATION
- EASY-TO-READ TEXT

An invaluable, convenient working tool for engineers and technicians with useful charts like these: Frequency and Wave-length • Reactance and Frequency • Time Constants • Input Chokes • Vector Addition of Complex Quantities • Parallel Resistors and Series Capacitors • AND 53 OTHER CHARTS.

**A comprehensive collection of nomographs in one convenient book.**

Simplifies design procedures. Saves hours of time and effort on computations. Helps solve virtually every electronic design problem quickly. Eliminates uncertainty and mistakes. Large, accurate, clear charts on 8½ x 11 page size. Lies flat or stands up.

**Permanently cloth-bound \$5.95**

Money-back guarantee within 10 days if not completely satisfied with book

**GERNSBACK LIBRARY, Inc., Dept. 1265**  
154 West 14th Street, New York, N. Y. 10011

Enclosed is \$\_\_\_\_\_ Please send \_\_\_\_\_ copy(ies)  
of **Electronic Design Charts** @ \$5.95.

Name \_\_\_\_\_

Street \_\_\_\_\_


City \_\_\_\_\_ State \_\_\_\_\_ Zip Code \_\_\_\_\_

**BOOKS PURCHASED FOR PROFESSIONAL PURPOSES ARE TAX DEDUCTIBLE**

# NEW SEMI- CONDUCTORS AND TUBES
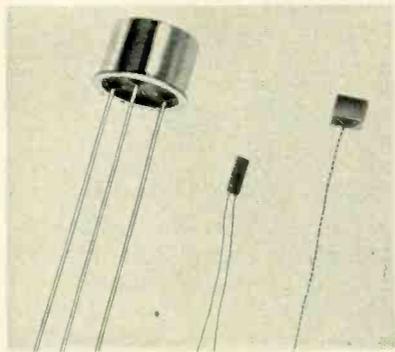
## WIDE-SWING MAGNETORESISTORS

A new line of magnetoresistors with an unusually large resistance change when placed in a magnetic field has been announced by Instrument Systems Corp.



The new sensors' resistance increases from 8 to 20 times the zero-field value under the influence of a 10,000-gauss magnetic field. Previous types changed by a factor of only 2 to 3 times. The new magnetoresistors are made of combined indium antimonide/nickel antimonide. They can supplant photoconductors and magnetic reed switches in many applications. Above 3,000 gauss, the ratio of resistance under flux to zero-field resistance is directly proportional to magnetic-flux density.


The photo compares the sizes of two ISC magnetoresistors to a TO-18 transistor case.

## LOW CROSS-MODULATION TUBES

One of the most serious problems in designing sensitive, wide-band front ends is *cross-modulation*, created when an undesired signal is strong enough—even after tuning and preselection—to swing an amplifier stage into a nonlinear part of its characteristic. The nonlinearity causes the signals to intermodulate, or cross-modulate, rather than simply mix. They can then no longer be separated by tuned circuits, and the result is a whopping case of incurable interference.

The usual approach to preventing this has been to use elaborate tuned preselector circuits, which are expensive to design and manufacture, and difficult to make track. Recently, Westinghouse Electronic Tube Division announced two miniature tetrodes designed so that

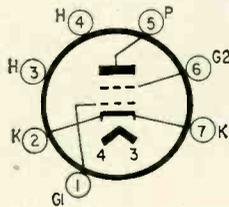an undesired signal of 5 volts peak-to-peak amplitude will produce only 1% cross-modulation. One of the tubes, the WX-4733A, is intended as an rf amplifier up to 100 mc; the other, the WX-4733D, is good to 300 mc. Both were designed expressly to permit using simple, conventional circuitry.



WX-4733A  
WX-4733D

Both tubes have comparatively low transconductance: 2,000  $\mu$ mhos for one and 2,700 for the other. This appears to be the price paid for the low cross-modulation factor.

Cross-modulation factor, by the way, is defined as the percentage of modulation transferred from an undesired carrier modulated 30% to an unmodulated, desired carrier.


## LOW-NOISE GERMANIUM AUDIO TRANSISTORS

Texas Instruments sends word of a new line of p-n-p alloy-junction germanium transistors for low-noise audio-amplifier applications. They are inexpensive (around 50 cents in small quantities) and have a high breakdown voltage—50 volts between collector and base. They are named TIXA01 and -02.

Their low noise (noise figure of 4 db maximum at 1 kc) makes them attractive for low-level audio preamp service, while the high breakdown voltage makes them useful as higher-level driver stages, or even possibly as output stages for low-power amplifiers of the switching, or pulse-width-modulated, design.

Common-base alpha cutoff is 4 mc; typical beta is 180 at 6 volts between collector and emitter with 1 ma flowing. Dissipation is 150 mw; maximum collector current, 150 ma.

## LOW-HEATER-POWER CRT

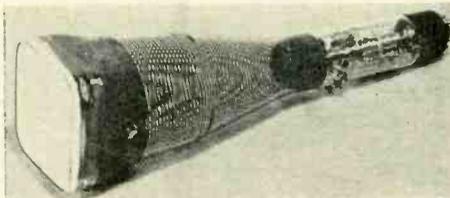

Powder metallurgy and other recent technologies have made possible a family of low-heater-power cathode-ray tubes, which, according to the manufacturer,

will run for 400 hours off a 1½-volt No. 6 dry cell.

Developed primarily for portable transistor oscilloscopes and similar equipment, tubes in the new line of Sylvania CRT's consume less than 6% of the heater power of conventional CRT's. Their heaters are rated at 1.5 volts 140 ma, compared to the usual 6.3 volts 600 ma. A further benefit of the reduced power is less heat to be dissipated in the equipment. END

## LOWDOWN ON THE LATEST COLOR-TV SETS

Color TV is bigger and better—but it's also smaller and better in 1966. New, smaller screens are appearing alongside 21 and 23 inch tubes. See valuable directory of 1966 sets and learn what's new in features and circuits.

## Coming in January RADIO-ELECTRONICS,

the 3rd Annual Color TV Issue

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION. Required by the Act of October 23, 1962, Section 4369, Title 39 United States Code. Radio-Electronics, published monthly at 10 Ferry Street, Concord, Merrimack County, New Hampshire 03302. The General Business offices of the Publisher are located at 154 West 14 St., New York City.

1. The names and addresses of the publisher, editor and managing editor are: Publisher, Hugo Gernsback, 154 West 14 St., New York City; Editor, M. Harvey Gernsback, 154 West 14 St., New York City; Managing Editor, Fred Shunaman, 154 West 14 St., New York City.

2. The owner is: Gernsback Publications, Inc., 154 West 14 St., New York City; Hugo Gernsback, 154 West 14 St., New York City; M. Harvey Gernsback, 154 West 14 St., New York City.

3. Known bondholders, mortgagees, and other security holders owning or holding 1 percent or more of total amount of bonds, mortgages or other securities: None.

4. The above paragraphs include, in cases where the stockholder or security holder appears upon the books of the company as trustee or in any other fiduciary relation, the name of the person or corporation for whom such trustee is acting, also the statements in the two paragraphs show the affiant's full knowledge and belief as to the circumstances and conditions under which stockholders and security holders who do not appear upon the books of the company as trustees, hold stock and securities in a capacity other than that of a bona fide owner. Names and addresses of individuals who are stockholders of a corporation which itself is a stockholder or holder of bonds, mortgages or other securities of the publishing corporation have been included in the above paragraphs when the interests of such individuals are equivalent to 1 percent or more of the total amount of the stock or securities of the publishing corporation.

5. The average number of copies each issue during the preceding 12 months are: (A) Total number copies printed (net press run): 222,345; (B) Paid circulation: (1) To term subscribers by mail, carrier delivery or by other means: 97,275; (2) Sales through agents, news dealers, or otherwise: 60,091; (C) Total paid circulation: 157,366; (D) Free distribution: 2,013; (E) Total number of copies distributed: 159,379; (F) Office use, leftover, unaccounted, spoiled after printing: 62,966. The number of copies single issue nearest to filing date are: (A) Total number copies printed (net press run): 216,681; (B) Paid circulation: (1) To term subscribers by mail, carrier delivery or by other means: 96,503; (2) Sales through agents, news dealers, or otherwise: 58,671; (C) Total paid circulation: 155,174; (D) Free distribution: 2,034; (E) Total number of copies distributed: 157,208; (F) Office use, leftover, unaccounted, spoiled after printing: 59,473.

I certify that the statements made by me above are correct and complete.

(Signed) M. Harvey Gernsback  
Editor

Now you can solder tuners, planes, pre-amps and trains with the finesse of a production-line pro



*New*  
**MARKSMAN**  
**PENCIL**  
**Soldering Iron**

Featherweight precision tool has stainless steel long-reach barrel with replaceable tip. Handle remains cool. Tip runs up to 750°F. Complete with cord. Model SP-23. **\$2<sup>98</sup>** list

Also available in kit with two extra soldering tips, handy soldering aid and supply of solder. Model SP-23K. **\$4<sup>44</sup>** list

**WELLER ELECTRIC CORP., Easton, Pa.**  
WORLD LEADER IN SOLDERING TECHNOLOGY  
Circle 120 on reader's service card

Designed and manufactured in U.S.A.

**NEVER**  
**A BURNOUT**  
IN 6 EMC DIODE-PROTECTED VOMS

NOBODY ELSE BUT EMC DESIGNS IN SO MUCH VALUE!  
Professional quality and versatility  
Lifetime protection against electrical abuse  
No meter burn-out, needle damage, or fuse replacement

**VOLOMETER**

Model 109A Factory Wired & Tested \$27.95  
Model 109AK Easy-to-Assemble Kit \$20.25  
20,000 Ω/v DC sens. 10,000 Ω/v AC sens. 4 1/2", 40μa meter. High impact bakelite case. 5 DC voltage ranges: 0-6-60-300-600-3000v. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 3 DC current ranges: 0-6-60-600ma. 3 AC current ranges: 0-30-300ma; 0-3A. 3 resistance ranges: 0-20K, -200K, -20 megs. 5 db ranges: -4 to +67db. With carrying strap. 5 1/4" W x 6 3/4" H x 2 7/8" D.

**VOLOMETER**

Model 103A Factory Wired & Tested \$19.75  
Model 103AK Easy-to-Assemble Kit \$15.90  
4 1/2", 2% accurate, 800μa D'Arsonval type meter. One zero adjustment for both resistance ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 DC voltage ranges: 0-6-60-300-600-3000v. 5 db ranges: -4 to +64db. 5 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-120ma; 0-1.2A. 2 resistance ranges: 0-1K, 0-1 meg. 5 1/4" W x 6 3/4" H x 2 7/8" D.

**POCKET SIZE VOLOMETER**

Model 102A  
Factory Wired & Tested \$15.90  
Model 102AK Easy-to-Assemble Kit \$14.10  
3 1/2", 2% accurate 800μa D'Arsonval type meter. One zero adj. for both res. ranges. High impact bakelite case. 5 AC voltage ranges: 0-12-120-600-1200-3000v. 5 DC voltage ranges: 0-6-60-300-600-3000v. 3 AC current ranges: 0-30-150-600ma. 4 DC current ranges: 0-6-30-130ma; 0-1.2A. Resistance: 0-1K, 0-1 meg. 3 3/4" W x 6 1/4" H x 2" D.

EMC, 625 Broadway, New York 12, N.Y.

Send me FREE catalog of the complete value-packed EMC line, and name of local distributor.

RE-12

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ ZONE \_\_\_\_\_ STATE \_\_\_\_\_

**EMC**

ELECTRONIC MEASUREMENTS CORP.  
625 Broadway, New York 12, New York  
Export: Pan-Mar Corp., 1270 B'way, N.Y. 1

# TECHNOTES

## TEKTRONIX 561-A SHOWS FLICKERING OR INTERMITTENT TRACE

A particularly baffling trouble on a Tektronix 561-A oscilloscope appeared regularly in the shop but was never to be seen when the instrument was sent out for service. As soon as the scope came back, the trouble reappeared. The trace would flicker erratically.

The cause was finally traced to an intermittent insulation failure in the high-voltage oscillator coil. The leakage or arcing depended on the humidity of the air—and apparently the air in our shop was wetter than the air in the efficiently air-conditioned service shop center.


The same scope once showed a horizontal trace only half the width of the screen. After replacing many tubes and checking many voltages, someone discovered that one of the leads to the deflection-plate pins on the CRT envelope was loose enough to interrupt the circuit to that plate.—*Frederick W. Chesson*

## MOTOROLA T51GGV TWO-WAY-RADIO

A Motorola two-way model T51GGV radio had no squelch or audio, intermittently. Flicking the switch off and on could make the set work. The unit worked more than 50% of the time; when it didn't work the vibrator for the receiver B-plus did not function. Tapping it would cause it to start up; however, a new vibrator did not cure the difficulty. Neither did a new buffer capacitor or anything else I replaced.

Half of the heaters were not lit, and some were too bright. Hitting the vibrator, or switching the set off and on, would start the vibrator and light the rest of the heaters.

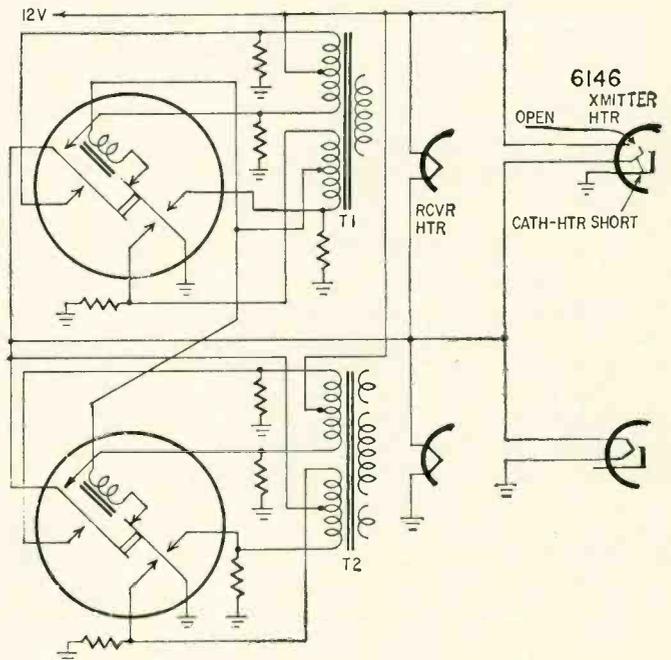The 1701 vibrator needs a 6-volt source, which is derived from the heater string. The heaters are wired in series-parallel and the 6 volts obtained by the drop across them. A




tube check showed the 6146 had an open heater with a short to cathode. However, when the vibrator was working, the heater in the 6146 would light, and the tube had normal power output. How about that! Just what was happening, I

don't know, but when the vibrator worked, it appeared to supply 6 volts to the other heater. Possibly the vibration made the filament ends weld together temporarily?—Don Dudley
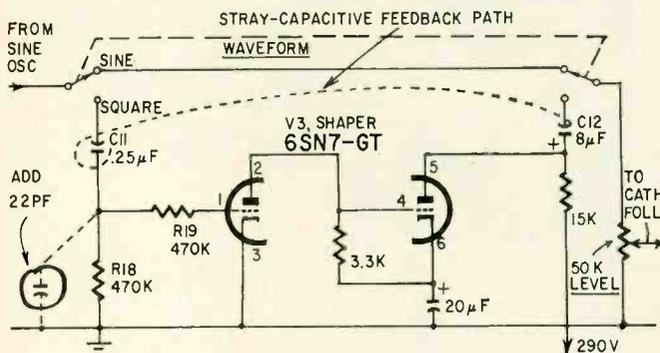
### SPURIOUS OSCILLATIONS IN EICO 377

An Eico model 377 Sine-Square Audio Generator, wired from a kit, began to show a parasitic oscillation riding on sine waves only, regardless of their amplitude or frequency. The generator worked perfectly in every way, except for this "fuzz" on the waves or parts of them, that hampered fine measurements.

A little investigation showed that oscillations appeared



in the output even when the WAVEFORM slide switch was halfway between SINE and SQUARE. The cathode-follower output stage, right after the switch, couldn't possibly oscillate. The sine-wave oscillator portion was producing sine waves with no fuzz, so that left only the square-wave shaper, V3.


A scope at the switch terminal connected to C12 (switch set halfway between positions) showed approximately square "blobs" of high-frequency oscillation, recurring at about a 10-kc rate. Much the same waveform appeared at the junction of R18 and R19. Apparently the shaper was acting as a free-running multivibrator, all by itself! Moving C11 or C12, both physically large and close together, affected the oscillation. Separating them a little removed the capacitive feedback path from V3 pin 5 to V3 pin 1. A ceramic capacitor of 22 pf connected with short leads from the junction of R18 and R19 to ground stabilized the circuit completely without affecting square-wave quality.—P. E. Sutheim

### VISCOUS-DAMPED TONE ARMS

Viscous-damped tone arms need very little attention as a rule except when the unwary audiophile attempts to move his player, spilling the oil. When you refill the ball chamber, screw the container tube right into the refill plug thread. The hard machine threads will tap the soft metal tube of the container and hold it firmly while the contents are squeezed out. This prevents a loss of fluid from spilling caused by air bubbles in the chamber.—Steve P. Dow
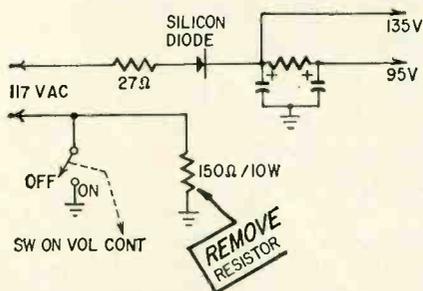
### THE RADIO THAT WOULDN'T SHUT UP

We installed a phono jack in a Sylvania FT24BK table radio. An spst switch was added to switch in the radio or the



phono attachment. Everything worked perfectly in the shop. But in the customer's home the local radio station would

# BUILD 20 RADIO

## CIRCUITS AT HOME

with the New Progressive  
**RADIO "EDU-KIT"®**

Reg. U.S.  
Pat. Off.

All Guaranteed to Work!

**PRACTICAL** only  
**HOME RADIO COURSE** \$26.95



### NOW INCLUDES

- ★ 12 RECEIVERS
- ★ 3 TRANSMITTERS
- ★ SQ. WAVE GENERATOR
- ★ AMPLIFIER
- ★ SIGNAL TRACER
- ★ SIGNAL INJECTOR
- ★ CODE OSCILLATOR

TRAINING ELECTRONICS  
TECHNICIANS SINCE 1946

- ★ No Knowledge of Radio Necessary
- ★ No Additional Parts or Tools needed
- ★ Excellent Background for TV
- ★ School Inquiries Invited
- ★ Attractively Gift Packaged

### FREE EXTRAS

- SET OF TOOLS
- RADIO & ELECTRONICS TESTER
- ELECTRIC SOLDERING IRON
- TESTER INSTRUCTION MANUAL
- MEMBER-SHIP IN RADIO-TV CLUB: CONSULTATION SERVICE
- HI-FI GUIDE
- QUIZZES
- TV BOOK
- FCC AMATEUR LICENSE TRAINING
- RADIO BOOK
- PRINTED CIRCUITRY
- PLIERS-CUTTERS
- ALIGNMENT TOOL
- WRENCH SET
- CERTIFICATE OF MERIT
- VALUABLE DISCOUNT CARD

### WHAT THE "EDU-KIT" OFFERS YOU

The "Edu-Kit" offers you an outstanding PRACTICAL HOME RADIO COURSE at a top-bottom price. Our kit is designed to train Radio & Electronics Technicians, making use of the most modern methods of home training. You will learn radio theory, construction, servicing, basic Hi-Fi and TV repairs, code, FCC amateur license requirements.

You will learn how to identify radio symbols, how to read and interpret schematics, how to mount and lay out radio parts, how to wire and solder, how to operate electronic equipment, how to build radios. Today it is no longer necessary to spend hundreds of dollars for a radio course. You will receive a basic education in radio, worth many times the small price you pay, only \$26.95 complete.

### THE KIT FOR EVERYONE

The Progressive Radio "Edu-Kit" was specifically prepared for any person who has a desire to learn Radio. The "Edu-Kit" has been used successfully by young and old in all parts of the world, by many Radio Schools and Clubs in this country and abroad. It is used for training and rehabilitation of Armed Forces Personnel and veterans, and for the non-profit work of the Y.M.C.A.

The Progressive Radio "Edu-Kit" requires no instructor. All instructions are included. Every step is carefully explained. You cannot make a mistake.

### PROGRESSIVE TEACHING METHOD

The Progressive Radio "Edu-Kit" is the foremost educational radio kit in the world, and is universally accepted as the standard in the field of electronics training. The "Edu-Kit" uses the modern educational principle of "Learn by Doing." Therefore, you will construct radio circuits, perform jobs and conduct experiments to illustrate the principles which you learn.

You begin by examining the various radio parts included in the "Edu-Kit." You then learn the function, theory and wiring of these parts. Then you build a simple radio. With this first set, you will enjoy listening to regular broadcast stations, learn theory, practice testing and troubleshooting. Then you build a more advanced radio, learn more advanced theory and techniques. Gradually, in a progressive manner, and at your own rate, you will find yourself constructing more advanced multi-tube radio circuits, and doing work like a professional Radio Technician.

Included in the "Edu-Kit" course are 20 Receiver, Transmitter, Code Oscillator, Signal Tracer, Signal Injector, Square Wave Generator and Amplifier circuits. These are not unprofessional "bread board" experiments, but genuine radio circuits, constructed by means of professional wiring and soldering on metal chassis, plus the new method of radio construction known as "Printed Circuitry." These circuits operate on your regular AC or DC house current.

### THE "EDU-KIT" IS COMPLETE

You will receive all parts and instructions necessary to build 20 different radio and electronics circuits, each guaranteed to operate. Our Kits contain tubes, tube sockets, variable, electrolytic, mica, ceramic and paper dielectric condensers, resistors, tie strips, coils, hardware, tubing, punched metal chassis, Instruction Manuals, hookup wire, solder, selenium rectifiers, volume controls, switches, knobs, etc. In addition, you receive Printed Circuit materials, including Printed Circuit chassis, special tube sockets, hardware and instructions. You also receive a useful set of tools, a professional electric soldering iron, and a self-powered Dynamic Radio & Electronics Tester. The "Edu-Kit" also includes Code Instructions and the Progressive Code Oscillator, in addition to the F.C.C.-type Questions and Answers for Radio Amateur License training. You will also receive lessons for servicing with the Progressive Signal Tracer and the Progressive Signal Injector, and a High Fidelity Guide and Quiz Book. Everything is yours to keep.

J. Statkis, of 25 Poplar Pl., Waterbury, Conn., writes: "I have repaired several sets for my friends, and made money. The "Edu-Kit" paid for itself. I was ready to spend \$240 for a course, but I found your ad and sent for Your Kit."

### PRINTED CIRCUITRY

At no increase in price, the "Edu-Kit" now includes Printed Circuitry. You build a Printed Circuit Signal Injector, a unique servicing instrument that can detect many Radio and TV troubles. This revolutionary new technique of radio construction is now becoming popular in commercial radio and TV sets.

A Printed Circuit is a special insulated chassis on which has been deposited a conducting material which takes the place of wiring. The various parts are merely plugged in and soldered to terminals.

Printed Circuitry is the basis of modern Automation Electronics. A knowledge of this subject is a necessity today for anyone interested in Electronics.

### UNCONDITIONAL MONEY-BACK GUARANTEE

ORDER FROM AD — RECEIVE FREE BONUS  
RADIO & TV PARTS JACKPOT WORTH \$15

Please rush my Progressive Radio "Edu-Kit" to me, as indicated below:

- Check one box to indicate choice of model
- Regular model \$26.95.
- Deluxe model \$29.95 (same as regular model, except with superior parts and tools).
- Check one box to indicate manner of payment
- I enclose full payment. Ship "Edu-Kit" post paid.
- Ship "Edu-Kit" C.O.D. I will pay postage.
- Send me FREE additional information describing "Edu-Kit."

Name \_\_\_\_\_  
Address \_\_\_\_\_

Progressive "EDU-KITS" Inc. 1185 Broadway, Dept. 249G  
Hewlett, N. Y. 11557  
(ATT: S. GOODMAN, M.S. in ED., PRES.)

Circle 122 on reader's service card

at last...  
instant color patterns  
at your finger tips...  
zero warm-up time



## THE ALL NEW SENCORE CG135 DELUXE TRANSISTORIZED COLOR GENERATOR

The big push is on in Color TV. Equip yourself now with the new, solid state Sencore CG135 and cash in on the zooming volume of new service business as Color-TV booms! Instant, service-ready RCA standard color bars, cross-hatch, white dots and individual vertical and horizontal bars enable you to set up or trouble-shoot more Color TV sets per day; earn top money in this fast growing service field. It's an analyzer too: Color gun interruptors, unmodulated video for chroma circuit trouble isolation and unmodulated sync pulses to keep Zenith receivers in sync for this test, make color trouble shooting a snap. Sturdy all-steel construction for rugged, heavy duty in the field or shop. Another Best Buy in profit-building service instruments from Sencore at

**\$149<sup>95</sup>**


COMPARE THESE FEATURES: SEE WHY THE CG135 IS IN A CLASS BY ITSELF

- Solid state construction employs high priced GE "Unijunctions" to develop six "jump out proof counters" that guarantee stable patterns at all times with no warm-up
- Standard RCA licensed patterns as shown on schematics throughout the industry
- Handy universal color gun interruptors on front panel
- Lead piercing clips insure non-obsolence
- CRT adaptors optional
- Crystal-Controlled 4.5mc Sound Carrier Analyzing Signal to insure correct setting of fine tuning control
- RF output on Channel 4 adjustable to Channel 3 or 5 from front of generator when Channel 4 is being used
- No batteries to run down; uses 115 V AC
- Less than one foot square, weighs only 8 lbs.

professional quality — that's the difference!

**SENCORE**  
426 SOUTH WESTGATE DRIVE • ADDISON, ILLINOIS

Circle 123 on reader's service card

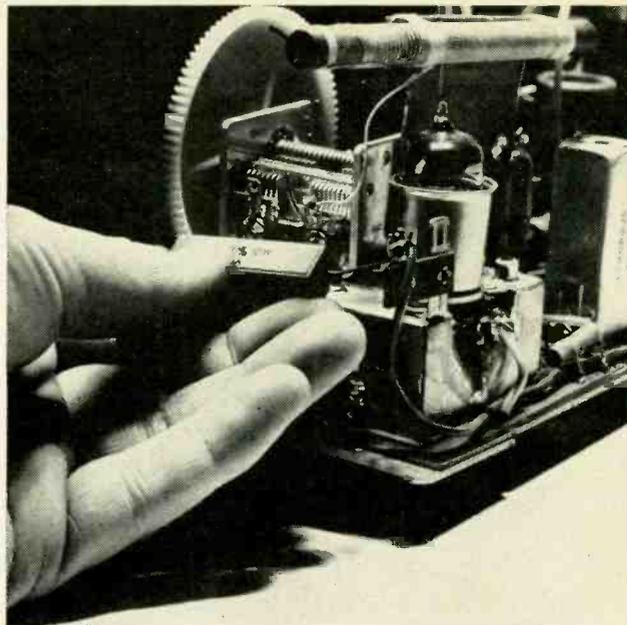


come in when the radio switch was turned off. The tubes went out when the switch was off, as far as the eye could see. It didn't seem possible that music could still come from the radio.

In the shop, it was found that the heaters *seemed* out, but there was voltage on the tubes. We found that a 510-ohm 10-watt resistor was wired across the ac switch to keep the tubes warm for a quick warmup when the radio is switched on. With the tubes partly warmed up, a local station was able to get through via the new audio wiring. Since the shop is shielded, this did not occur while the radio was there. We cut out the resistor.—Homer L. Davidson
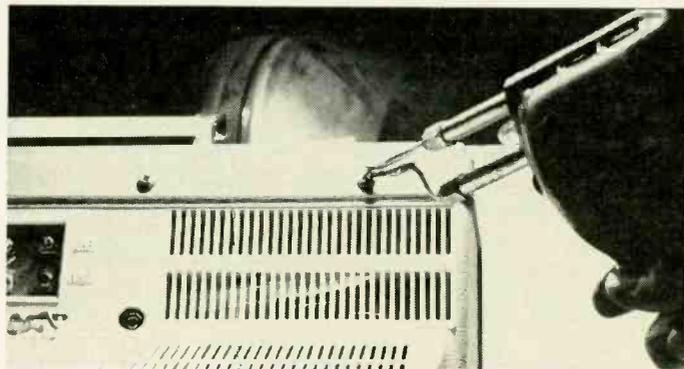
### HEAT LOOSENS PHILLIPS SCREWS

To remove machine-tightened Phillips head screws from plastic TV-set backs or other assemblies, try holding a



hot soldering iron against the head for a few seconds. Then use the correct size Phillips driver to loosen the screw. Don't hold the iron on too long: the plastic will melt around the screw.—Homer L. Davidson


### HUM AND RIPPLES IN CCTV

In a closed-circuit TV system, ripples and hum bars will sometimes drift up or down the screen. This occurs in better-grade systems where a master oscillator is divided down to provide vertical sync. The master oscillator drifts out of the range of the automatic frequency control circuit, so that the vertical sync is no longer in phase with the ac line.

The remedy, in most cases, is simple—open the camera control unit, find the master oscillator frequency control, and

adjust it until the ripples and bars disappear. Find the range of adjustment over which the afc will hold the oscillator locked to the correct frequency, and set the frequency control to the middle of this range.—*Charles Erwin Cohn*

#### A BUTTERFLY STORY

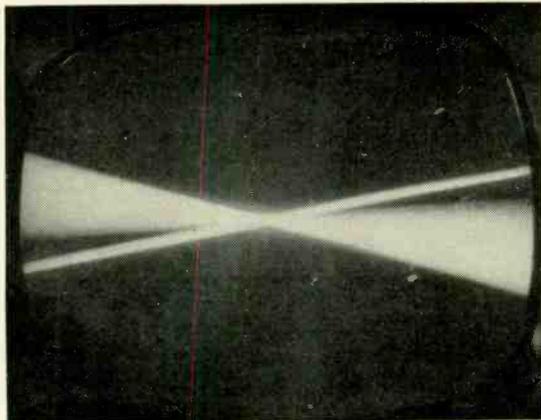


A few days ago I came upon a service case which apparently called for an entomologist rather than a TV service tech. The customer had a Zenith model D 2315 receiver, and the defect, when I saw the set, was a trapezoidal picture such as you often find with a shorted deflection yoke coil. I had no replacement yoke with me, so I decided to take the defective yoke to the workshop, hoping to be able to repair it. The customer agreed very quickly to this; the repair would cost him less than a new yoke. (Original service parts are rather expensive here in Argentina.)

In the workshop I changed the defective vertical coil and made a quick resistance check. Everything seemed all right. I went back to the customer's home and put the repaired yoke into the set. Much to our surprise we saw a picture like the one in the photograph. We had a perfect television butterfly. The cause of this defect was a reversed vertical deflection coil. Transposing its connections fixed everything very quickly.—*Egon Strauss*
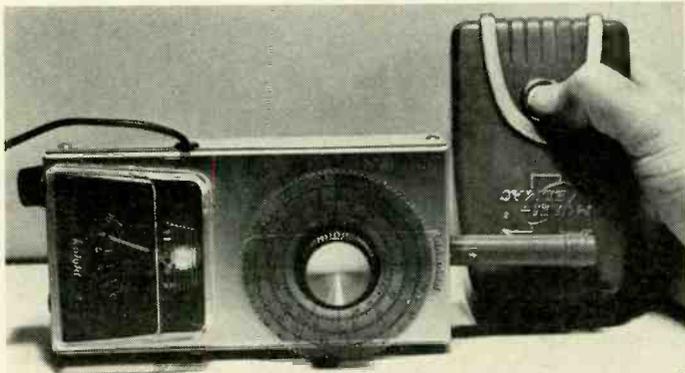
#### CHECKING PORTABLE DOOR-OPENER TRANSMITTER


You can check your portable door-opener transmitter with a grid-dip oscillator, if one is handy. Set the grid-dip oscillator around 27 mc and set the meter to full scale. Place



the portable door transmitter unit next to the grid-dipper's coil. Point the transmitting coil in the door opener toward the grid-dip coil.

Press the button on the door opener; the meter pointer should fall back. Adjust the grid-dip oscillator for deepest null, then let up on the button. This will show you that the transmitter is operating, and also the transmitter's operating frequency.—*Homer L. Davidson*

END

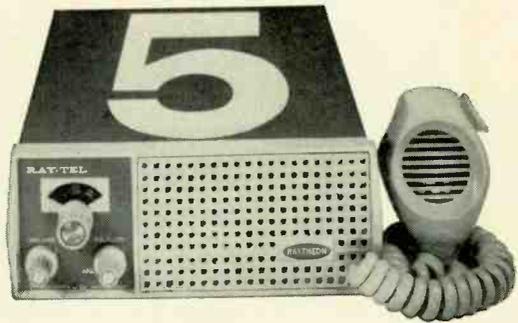

AND



PERFECT  
PAIR...

SOLID  
STATE...

SOLID  
STATEMENT

QUOTE:

Ray-tel, all-transistor C-B radio line, broadest of any in scope, priced to reflect full value at all equipment levels.

This fine line ranges from the sophisticated, full-feature 11-channel TWR-5 intended for personal and business communication systems, to the diminutive 5-channel TWR-7, price and performance peer of all the solid-state mobile radios.

We will be pleased indeed to send you complete details.

Please send details on Ray-tel TWR-5 and TWR-7.

Name

Number

Street

City

State

Zip Code

**RAY-TEL**


213 E. Grand Ave., So. San Francisco, Calif. 94080

Circle 124 on reader's service card

# TRY THIS ONE
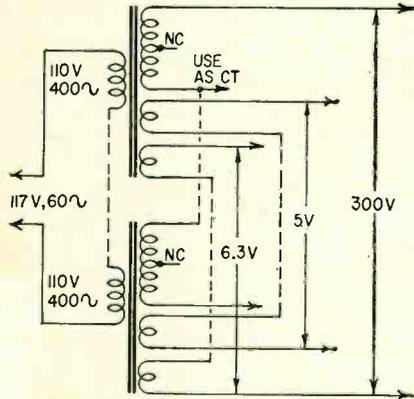
## USING SURPLUS 400-CYCLE TRANSFORMERS

Most experimenters discard 400-cycle transformers when they remove them from surplus equipment. But, by connecting their primaries in series with a 120-volt 100-watt bulb, you can use them on 117-volt 60-cycle ac. You will get half the rated secondary voltage of the transformer.




Another trick is to connect two identical transformers with their primaries in series across 117 volts 60 cycles, and all corresponding secondaries in series (see diagram). The output voltage

is approximately equal to the rated output of one of the transformers. Current capacity remains at the rated value in all cases.—Milton Lenheim
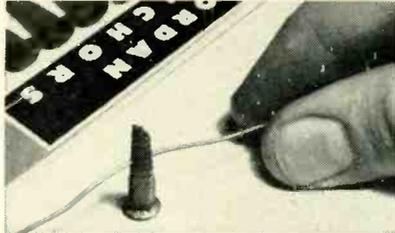
## SMALL WIRE STANDOFFS

To avoid undesirable coupling, it is often wise to prevent certain leads from getting too close to each other, or too close to the chassis. Jordan plastic screw



anchors cemented to the chassis make good wire standoff. Simply wedge the wire in the anchor slot as shown.—John A. Comstock

## MODIFYING THE HEATH CT-1

This capacitor tester is a unique and helpful instrument. With a few simple modifications, it can be made even handier around the shop.

To keep the 1629 "eye" tube from being pushed back, wire it to its mount-

ing clamp through the upper hole in its socket.

The spring-return switch is not very handy for testing a large number of capacitors. The shaft and bearing assembly may be replaced with a positive-action mechanism from an old rotary switch. Be sure not to disturb the wafer.

One side of the ac line is connected through a .02- $\mu$ f capacitor, making the chassis slightly "hot." Cure this by putting the grounded side of the capacitor either to the other side of the transformer or the other side of the switch.

On occasion, in two separate instruments, the "eye" tube has "overlapped". This has been due, in both cases, to excessive leakage in 0.1- $\mu$ f capacitor across the pins 3 and 4 of the 1629 tube. Replace it with a good-quality paper or plastic capacitor.


Other modifications include adding a neon pilot lamp and wiring in the test leads permanently.—Allan Glaser

## SLIP-ON TV SIGNAL INJECTION

If a TV set is dead or intermittent somewhere in the rf, i.f. or video section, connect the ground lead of your signal generator to the TV chassis. Tune the TV to an unused channel. Connect the generator output lead to a spare tube shield. Tune the signal generator to the operating frequency of the stage, with the modulation on. Place the shield over each of the i.f. and rf stages in
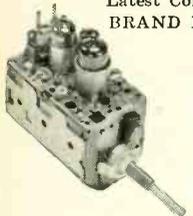
## SARKES TARZIAN TV TUNER 41mc

Latest Compact Model—good for all 41 mc TV's. BRAND NEW—MONEY BACK GUARANTEE




Best TUNER "SARKES TARZIAN" ever made—last word for stability, definition & smoothness of operation. An opportunity—to improve and bring your TV Receiver up-to-date. List price \$35—former reduced price \$15.97—now cut in 1/2 to \$7.95

L-3", H-4", W-2"

COMPLETE with Tubes & Schematic ... \$7.95

## HOTTEST VALUE EVER

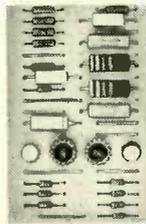


## IBM COMPUTER SECTIONS

Each Unit "cost IBM over \$5.00"  
8 assorted Units we sell for \$1 are loaded with over 100 valuable parts.

8 for \$1  
100 for \$10

## RCA 110° FLYBACK TRANSFORMER

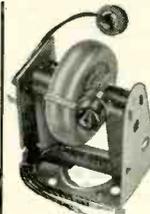

We scooped the Market on 10000

Latest type RCA—standard for all 110° TV's—also good for 90° TV's

RCA's design of extra large Coil Produces upwards of 18KV—assuring adequate width and height.

Included—Schematic Diagram showing easy application for any TV

List price \$13.90  
Dealer price 8.35

your price ... \$3

100% off in lots of 3 or over


- |  |   |   |   |
|--|---|---|---|
| <input type="checkbox"/> 300—ASST. 1/2 W RESISTORS \$1<br>Top Brand, Short leads, excellent                      | <input type="checkbox"/> 100—ASST. CERAMIC CONDENSERS some in 5% ... \$1                      | <input type="checkbox"/> 550 STARLITE AM-FM RADIO \$12<br>complete needs slight adjustment                          | <input type="checkbox"/> WESTINGHOUSE TV TUNER \$2<br>41mc, brand new (less tubes) ...          |
| <input type="checkbox"/> 100—MOLDED TUBULAR COND. \$1<br>Top brand, short leads, excellent                       | <input type="checkbox"/> 100—ASST. MICA CONDENSERS some in 5% ... \$1                         | <input type="checkbox"/> 20—ASSORTED TUBES \$1<br>Radio, Television and Industrial ...                              | <input type="checkbox"/> 10—ASST. 4 WATT WIRE WOUND CONTROLS ... \$1                            |
| <input type="checkbox"/> 50—ASSORTED #3AG FUSES \$1<br>Popular assorted ampere ratings ...                       | <input type="checkbox"/> 100—ASST 1/4 WATT RESISTORS \$1<br>stand. choice ohmages, some in 5% | <input type="checkbox"/> ALL AMERICAN TUBE KIT \$2<br>Top Standard Brand — 12BA6, 12BE6, 12AV6, 50C5, 35W4 ...      | <input type="checkbox"/> 4—TRANSISTOR RADIO EARPIECES wired complete with plug ... \$1          |
| <input type="checkbox"/> 5—I.F. COIL TRANSFORMERS \$1<br>sub-min for Transistor Radios ...                       | <input type="checkbox"/> 100—ASST 1/2 WATT RESISTORS \$1<br>stand. choice ohmages, some in 5% | <input type="checkbox"/> 3—TOP BRAND 35W4 TUBES \$1   | <input type="checkbox"/> 2—G.E. PIECES OF EQUIPMENT \$1<br>stacked with over 200 useful parts   |
| <input type="checkbox"/> 5—AUDIO OUTPUT TRANSFORMER \$1<br>sub-min for Trans Radios                              | <input type="checkbox"/> 70—ASST 1 WATT RESISTORS \$1<br>stand. choice ohmages, some in 5%    | <input type="checkbox"/> 10—SYLVANIA 1U4 TUBES \$1<br>brand new Jan., individual cartons also serves as 1T4 ...     | <input type="checkbox"/> G.E. TV POWER TRANSFORMER \$4<br>250ma, 360/360v, 6.3-9A, 5v-3A        |
| <input type="checkbox"/> 4—TOGGLE SWITCHES \$1<br>SPST, SPDT, DPST, DPDT ...                                     | <input type="checkbox"/> 35—ASST 2 WATT RESISTORS \$1<br>stand. choice ohmages, some in 5%    | <input type="checkbox"/> 25—SYLVANIA HEAT SINKS \$1<br>for Transistors, etc.  | <input type="checkbox"/> 50—G.E. FLASHLIGHT BULBS \$1<br>#PR-9, 2.7 volts ...                   |
| <input type="checkbox"/> 15—ASST. ROTARY SWITCHES \$1<br>all popular types \$20 value ...                        | <input type="checkbox"/> 50—PRECISION RESISTORS \$1<br>asst. list-price \$50 less 98% ...     | <input type="checkbox"/> 100—MIXED DEAL "JACKPOT" \$1<br>Condensers, Resistors, Surprises ...                       | <input type="checkbox"/> 4—G.E. SAPPHIRE NEEDLES \$1<br>4G, VR-11, etc. (\$10.50 value) ...     |
| <input type="checkbox"/> CLEAN UP THE KITCHEN "JACKPOT" \$1<br>Big Deal only one to a customer ...               | <input type="checkbox"/> 20—ASST WIREWOUND RESISTORS, 5, 10, 20 watt ... \$1                  | <input type="checkbox"/> 100—BRASS FAHNSTOCK CLIPS \$1<br>popular type & size, plated ...                           | <input type="checkbox"/> FATHOM DEPTH PIECE OF EQUIPMENT loaded with fine parts ... \$1         |
| <input type="checkbox"/> 50—RADIO & TV SOCKETS \$1<br>all type 7 pin, 8 pin, 9 pin, etc.                         | <input type="checkbox"/> 50—ASST. TERMINAL STRIPS \$1<br>all types, 1-lug to 6-lug ...        | <input type="checkbox"/> \$15.00 RADIO PARTS "JACKPOT" \$1<br>handy assortment ...                                  | <input type="checkbox"/> RONETTE SAPPHIRE CARTRIDGE \$1<br>dual flipover type—value \$5 ...     |
| <input type="checkbox"/> 2—UNIVERSAL 2 1/4" PM SPEAKERS for Radios, Intercom, as multiple Speakers, etc. ... \$1 | <input type="checkbox"/> 25—INSTRUMENT POINTER KNOBS selected popular types ... \$1           | <input type="checkbox"/> 3—ELECTROLYTIC CONDENSERS 50/30-150v ... \$1   | <input type="checkbox"/> RONETTE STEREO CARTRIDGE \$2<br>latest dual sapphire flipover type ... |
| <input type="checkbox"/> UNIVERSAL 4" PM TWEETER SPEAKER for FM, HI-FI, etc. ... \$1                             | <input type="checkbox"/> 50—ASST. RADIO KNOBS all selected popular types ... \$1              | <input type="checkbox"/> 50—RMC DISC CERAMIC COND \$1<br>Your choice 25, 50, 100, 1K, 5K, 10K mfs (or assorted) ... | <input type="checkbox"/> 3—SAPPHIRE STYLUS NEEDLES \$1<br>Ronette type for most cartridges ...  |
| <input type="checkbox"/> 10—SPEAKER PLUG SETS deluxe type, 2 conductor, wired ... \$1                            | <input type="checkbox"/> 50—RCA LUCITE RADIO KNOBS popular type w. indicator pointer ... \$1  | <input type="checkbox"/> 2—POWER TRANSISTORS No. 1 Replace 2N155, 2N176, 2N301, etc. ... \$1                        | <input type="checkbox"/> 3—STANDARD SAPPHIRE NEEDLES for all thumb screw cartridges ... \$1     |
| <input type="checkbox"/> UNIVERSAL 4" PM SPEAKER Alnico 5 magnet, Quality tone ... \$69¢                         | <input type="checkbox"/> 5—PNP TRANSISTORS general purpose, TO-5 case ... \$1                 | <input type="checkbox"/> ELECTROSTATIC 3" TWEETER SPEAKER for FM, HI-FI, etc. ... \$1                               | <input type="checkbox"/> 4—SHOCKPROOF SCREWDRIVERS best sizes incl Phillips ... \$1             |

BROOKS RADIO & TV CORP., 84 Vesey St., Dept. A, New York 7, N.Y. TELEPHONE CORtlandt 7-2359

turn, not letting it touch chassis. The capacitance between the shield and the tube electrodes will inject the generator signal into the stage. If the stage and all following are OK, the usual bar pattern will appear on the screen. This technique is faster than pulling tubes.—Charles Erwin Cohn

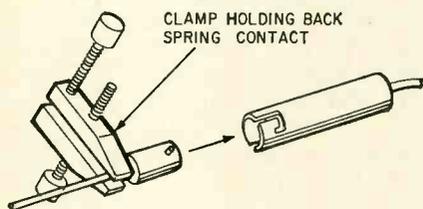**HANDLING IN-LINE FUSE RETAINERS**

Fuse retainers of the in-line type can be difficult to put together if they are in a tight spot that can be reached only with one hand. To simplify cou-




pling, first pull back the wire with the spring contact and hold it with a small clamp. The two sections may then be easily put together, and the clamp removed.—Hugh Lineback

**TOOLBOX SOLDER BOTTLE**

Dropping small bits of solder into your toolbox for field jobs is wasteful, but not having any solder is worse. A plastic solder container slips into a pocket, drops into a toolbox or stays handy on the bench and contains enough solder for any dozen jobs you're likely to encounter.

To make it, get a small pill or throat lozenge vial from your druggist and drill a 1/8-inch hole centered in the bottom. Now wind 2 or 3 inches of solder neatly around a pencil and leave a 2- or 3-inch "tail". Push the tail back through the coil so it sticks out about an inch at the other end. Drop the coil into the pill bottle, making the end come out through the hole, put the cap back on the bottle, and your solder bottle is finished.

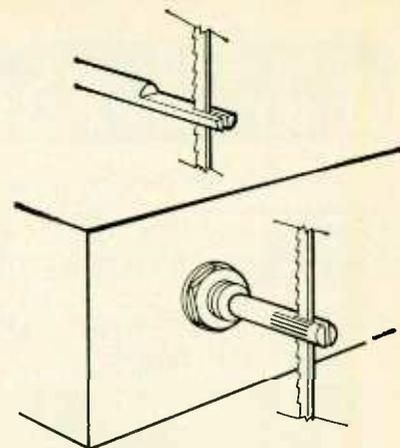Pick a vial that's sturdy enough to withstand banging around with heavy tools in your toolbox. I used one that contained Tracinets sore-throat tablets.—Charles A. Brunjes



again and again if necessary. Be careful not to mar the cabinet with the saw.—Tom Jaski

**TIGHTEN KNURLED OR FLATTED KNOBS**

When radio or TV push-on knobs on knurled or flattened shafts get too loose, slot the shaft for 1/4 inch with a jeweler's saw and spread the slot. Knobs will now fit tight and can be tightened

**Turn Back TO PAGE 70** for Radio-Electronics FREE Reader's Service Page. Special postpaid card will bring you helpful information.

**MOVING DATE EXTENDED—SALE CONTINUES**

**FREE \$1 BUY WITH EVERY 10 YOU ORDER**

Only applies to "\$1" Buys

**FREE GIFT WITH EVERY ORDER**

- 1000—ASST. HARDWARE KIT \$1  
screws, nuts, washers, rivets, etc.
- 250—ASST. SOLDERING LUGS \$1  
best types and sizes
- 250—ASST. WOOD SCREWS \$1  
finest popular selection
- 250 — ASST. SELF TAPPING SCREWS #6, #8, etc. \$1
- 150—ASST. 6/32 SCREWS and 150 6/32 HEX NUTS \$1
- 150—ASST. 8/32 SCREWS and 150-8/32 HEX NUTS \$1
- 150-6/32 HEX NUTS and 150-8/32 HEX NUTS \$1
- 150—ASST. 2/56 SCREWS and 150-2/56 HEX NUTS \$1
- 150—ASST. 4/40 SCREWS and 150-4/40 HEX NUTS \$1
- 150—ASST. 5/40 SCREWS and 150-5/40 HEX NUTS \$1
- 500—ASSORTED RIVETS \$1  
most useful selected sizes
- 500—ASSORTED WASHERS \$1  
most useful selected sizes
- 100 — ASST. RUBBER & FELT FEET FOR CABINETS \$1  
best sizes
- 10—ASSORTED SLIDE SWITCHES \$1  
SPST, SPDT, DPDT, etc.
- CHAPT ZU DI MITZIA "JACKPOT" \$1  
double your money back if not completely satisfied

- 100—MINIATURE ZIP CORD \$1  
2 conductor, serves 101 uses
- 50 ASSORTED MYLAR CONDENSERS \$1  
Popular types .001 to .47
- 10 SETS — DELUXE PLUGS & JACKS \$1  
asst. for many purposes
- 10 — SETS PHONO PLUGS & PIN JACKS RCA type \$1
- 10 — SURE-GRIP ALLIGATOR CLIPS 2" plated \$1
- 4-50' SPOOLS HOOK-UP WIRE \$1  
4 different colors
- 200—BUSS WIRE #20 tinned for hookups, special circuits, etc. \$1
- 50 — STRIPS ASSORTED SPAGHETTI handy sizes \$1
- 100—ASSORTED RUBBER GROMMETS best sizes \$1
- 50—ASSORTED PRINTED CIRCUIT SOCKETS best types \$1
- 3-1/2 MEG VOLUME CONTROLS \$1  
with switch, 3" shaft
- 20—ASSORTED VOLUME CONTROLS less switch \$1
- 7—ASSORTED VOLUME CONTROLS with switch \$1
- 15—RADIO OSCILLATOR COILS \$1  
standard 456kc
- 20—ASST. PILOT LIGHTS \$1  
#44, 46, 47, 51, etc.
- BONANZA "JACKPOT" not gold, not oil, but a wealth of Electronic Items—Money-Back-guarantee \$5

**TV BARGAIN COLUMN**

- \$139 STARLITE TV PORTABLE \$47  
16" complete, needs adjustment
- 110° TV DEFLECTION YOKE \$2  
for all type TV's incl schematic
- 90° FLYBACK TRANSFORMER \$1  
for all type TV's incl schematic
- 90° TV DEFLECTION YOKE \$1  
for all type TV's incl schematic
- 70° FLYBACK TRANSFORMER \$1  
for all type TV's incl schematic
- 70° TV DEFLECTION YOKE \$1  
for all type TV's incl schematic
- STANDARD COLOR TV TUNER \$8  
Complete with Tubes
- 10—ASST UHF TUNER STRIPS \$1  
standard 16 to 67 \$50 value
- \$15.00 TELEVISION PARTS \$1  
"JACKPOT" best buy ever
- 4 — TV ALIGNMENT TOOLS \$1  
most useful assortment
- 4—DUMONT VERT OSC TRANS \$1  
incl schematic for many TV uses
- 20—ASSORTED TV COILS \$1  
I.F. video, sound, ratio, etc.
- 40—ASSORTED TV KNOBS \$1  
all standard types, \$20 value
- 20—ASSORTED GRID CAPS \$1  
for 1B3, 1X2, 6BG6, 6BQ6, etc.
- 50—ASSORTED TV PEAKING COILS \$1  
all popular types

**MARKET SCOOP COLUMN**

- TRANSISTOR RADIO *asst type* \$1.50  
good, bad, broken, as-is, potluck
- TAPE RECORDER—assorted types \$4  
good, bad, broken, as-is, potluck
- 10—ASSORTED DIODE CRYSTALS \$1  
1N34, 1N48, 1N60, 1N64, 1N82
- 10—TOP BRAND TRANSISTORS \$1  
NPN & PNP 2N404, 2N414, etc.
- 1 — SQ. YARD GRILLE CLOTH \$1  
most popular brown & gold design
- STANDARD TELEPHONE JACK or PLUG \$1  
make telephone portable
- TELEPHONE RECORDING DE-VICE \$1  
place it under telephone
- CRYSTAL LAPEL MICROPHONE \$1  
high impedance, 200-6000 cps
- 10 — ASST. RADIO ELECTROLYTIC CONDENSERS \$1
- 7 — ASST. TV ELECTROLYTIC CONDENSERS popular selection \$1
- 50 — ASST. TUBULAR CONDENSERS .001 to .47 to 600v \$1
- 20—STANDARD TUBULAR CONDENSERS .047-600v \$1
- 10—ASST DUAL CONTROLS \$1  
for Radio, TV, Hi-Fi, Stereo, etc.

**IMMEDIATE DELIVERY . . .** Scientific light packing for safe delivery at minimum cost.  
**HANDY WAY TO ORDER:** Pencil mark or write amounts wanted in each box, place letter F in box for Free \$1 BUY. Enclose with check or money order, add extra for shipping. Tearsheets will be returned as packing slips in your order, plus lists of new offers.

Name ..... Cost of goods .....  
Address ..... Shipping estimated .....  
..... TOTAL

Please specify refund on shipping overpayment desired:  CHECK  POSTAGE STAMPS  MERCHANDISE (our choice) with advantage to customer

Circle 125 on reader's service card

# CAN YOU SAVE MONEY ON PARTS?

Now You Can. Just Write for Edlie's

## FREE MONEY-SAVING CATALOGUE

Listed below are just a few of the many

### BARGAINS

#### 4 TUBE STEREO AMPLIFIER

A new and completely working 2 channel unit, suitable for use with a record changer, tape recorder, etc. Operates from a 115 volt AC or DC source. Contains 3 output transformers, 3-35EH5 and 1 - ECC83 tubes, and 1 top hat silicon rectifier. 2 single and 1 dual control, and all related components. Housed on a chassis 5 1/4"x6 3/4"x1" high. Weight 2 1/2 lbs.



Price \$6.95

#### EPOXY SILICON RECTIFIER

rated at 750 ma, 500PIV  
RE 101



Price 22¢ each; 6 for \$1.25.

#### STUD MOUNTED SILICON RECTIFIER


rated at 20 amperes, 300 PIV  
RE 102



Price 79¢ each; 6 for \$4.50
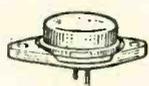
#### 25 WATT POWER TRANSISTOR T25


PNP type, audio usage, suitable for use in place of 2N158, 2N235, 2N251, etc. (Over 25 other types).  
RE 103



Price 59¢ each; 6 for \$3.25.
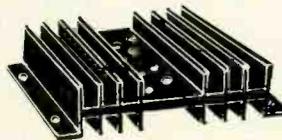
#### DUAL HEAT SINK

Black anodized aluminum with 4 fins on either side. Will house 2 power transistors size 3" x 4 1/2".  
RE 104




Price 95¢ each.

#### HI-FI DYNAMIC MICROPHONE

Omni-Directional, moving coil type for both high and low impedance, built in desk type stand; base threaded for floor stand, suitable for tape recorder or amateur use.

RE-105

Price \$2.95.

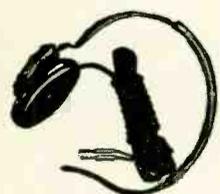

#### ACME SINGLE HEADSET

1000 ohms complete with headband and cord.

RE 106 Price 95¢

#### Weston DC Milliammeter, Model 801-58

4 1/2" Rectangular  
Basic 0-5 Ma, DC  
Scale 0-1 in 50 divisions  
and 0-3 in 30 divisions

Price \$4.95



#### EDLIE ELECTRONICS, INC.

Dept. RE-5  
(The Electronic Bargain House)  
154 Greenwich St.,  
New York 6, N.Y.

Circle 126 on reader's service card

# NOTEWORTHY CIRCUITS

## CENTER CHANNEL FOR STEREO

A number of methods have been developed for adding a third- or center-channel speaker to a stereo system. Several were described in "Add a Third Speaker the Easy Way" in the October 1960 issue. The Merit A-4110 and Microtran HM-90 mix/match audio transformers were developed to simplify connecting a third speaker while maintaining correct impedances, signal polarities and power levels.

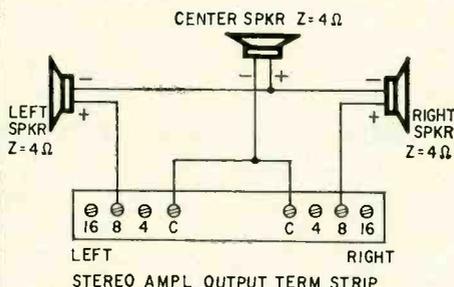


Fig. 1

Fig. 1 shows a recent patent-pending development by David Hafler of Dynaco. The three speakers should have the same impedance and efficiency. The outside ones are connected in series-opposing across the two output terminals for speakers of twice their impedance. The third speaker is bridged between the common or ground terminal on the amplifier and the common return lead from the outside speakers.

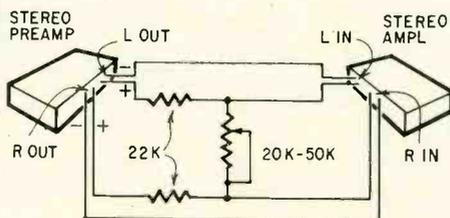


Fig. 2

Mr. Hafler notes that this system may degrade separation and cause some crosstalk. This can be eliminated by a resistive bridge network—also covered in the patent application—connected between the preamps and power amplifiers or between two identical high-impedance points in the circuit. The resistive network is shown in Fig. 2.


To adjust the bridge, connect only one channel of a stereo pickup to one

amplifier channel, the left one for example. Play a mono record and adjust the pot for minimum output from the right speaker. Switch the phono plug to the right channel. The control setting should be correct for minimum output from the left speaker. If not, then correct it with the amplifier's balance and tone controls.

Plug both phono channels into the amplifier and carry on from there. Incidentally, the center output can be used to feed a mono (L+R) signal to the patio, basement or any other remote point.
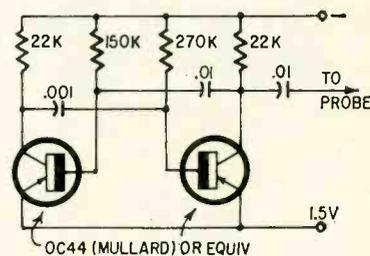
## TRANSISTOR SIGNAL INJECTOR

A simple untuned af-rf signal generator is handy for tracking down inoperative or defective audio and low-frequency rf circuits. You can use it on the bench, in the field and even in a well equipped lab. The diagram shows a simple multivibrator that Pye Telecommunications engineers use for rapid troubleshooting in radiotelephone transceivers. It was described in *Industrial Electronics* (London, England).



The circuit develops a 1-kc square-wave signal of about 0.5 volt peak to peak and rich in harmonics to about 500 kc. The tester was built on a tiny circuit board and installed in a penlight case along with the 1.5-volt battery. END

## HOW TO SPOT TV COLOR TROUBLES INSTANTLY

Having trouble pinning down color-tv defects to a particular spot? Jack Darr's simple *Chroma Trouble Chart* provides quick and easy assistance. Step-by-step, it leads you from one critical check point to the next. Guaranteed to save you time and effort in locating the fault.


Coming in January  
**RADIO-ELECTRONICS** —  
the big Color-TV Issue

# WHAT'S YOUR EQ?

These are the answers. Puzzles are on page 55.
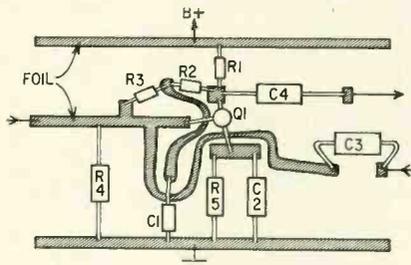
## Printed Circuit

The trick to the solution is that the components are on one side of the board while the foil permits running a lead



This method permits running a lead "through" any component. Therefore it is not necessary to redraw the circuit to avoid crossovers.

## How Many Ohms?


This one has a built-in joker. The center tie between the bridges can be disregarded; it connects corresponding points. Probably the easiest solution is to simplify by means of the Delta-Wye transformation. By opening the circuit at X—Y, we can find the resistance first of one bridge and then the other.

$$R1 = \frac{RA \cdot RB}{RA + RB + RC} = 1 \text{ ohm}$$

$$R2 = \frac{RA \cdot RC}{RA + RB + RC} = 1 \text{ ohm}$$

$$R3 = \frac{RB \cdot RC}{RA + RB + RC} = 1 \text{ ohm}$$

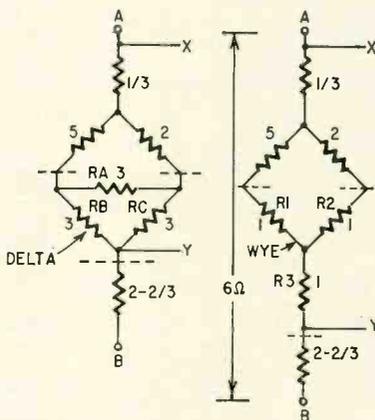The total resistance for this bridge is 6 ohms. In the same manner, the other bridge is found to be 3 ohms and the two paralleled equal 2 ohms.




With the center tie open, connect a voltage source (say 6 volts) to A—B. Determine voltage at center tie points. In this case, they are both 2 2/3 volts. So, any connection between these points has no effect on terminal resistance.
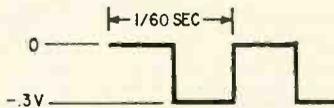
## Wave-Shaping Circuit

Here's how it operates: The self-potential (Edison effect) between the

right-hand diode plate and the common cathode causes direct current to flow through the 220,000- and 1,000-ohm resistors. This dc causes a drop of 0.3 volt across the 220,000-ohm resistor, thus a potential difference of 0.3 volt between A and B. The direction of current makes terminal A negative to terminal B.



The left-hand section of the tube operates as a half-wave rectifier. It is, in effect, an ac electronic switch that controls the flow of dc through the right-hand diode circuit. During positive half-cycles of the input voltage, a rectified voltage pulse is developed across the 1,000-ohm resistor. When this voltage exceeds + 0.3 volt, the 1,000-ohm resistor does not conduct dc from the right-hand circuit and, as a result, the voltage between A and B is zero. During negative half-cycles of the input voltage, no rectified voltage opposes the dc through the 1,000-ohm resistor; therefore, dc flows through the right-hand circuit and the voltage between A and B is 0.3 volt.

By using half-wave rectified voltage pulses to switch the right-hand circuit on and off, a near square-wave output is developed between A and B. The pulse repetition rate equals the frequency of the ac input voltage. END

## SILICON RECTIFIER SALE

IMMEDIATE

DELIVERY

FULLY GTD  
AMERICAN MADE



NEWEST TYPE  
FULLY TESTED

### 750 MA-SILICON "TOPHAT" DIODES

LOW LEAKAGE FULL LEAD LENGTH

PIV/RMS 50/35 .25 ea.	PIV/RMS 100/70 .07 ea.	PIV/RMS 200/140 .10 ea.	PIV/RMS 300/210 .12 ea.
PIV/RMS 400/280 .14 ea.	PIV/RMS 500/350 .19 ea.	PIV/RMS 600/420 .23 ea.	PIV/RMS 700/490 .27 ea.
PIV/RMS 800/560 .35 ea.	PIV/RMS 900/630 .45 ea.	PIV/RMS 1000/700 .60 ea.	PIV/RMS 1100/770 .75 ea.

### ALL TESTS AC & DC & FWD & LOAD

SILICON POWER DIODE STUDS

D.C. AMPS	50 PIV 35 RMS	100 PIV 70 RMS	150 PIV 105 RMS	200 PIV 140 RMS
3	.08 ea.	.12 ea.	.16 ea.	.22 ea.
12	.25	.35	.45	.75
35	.65	.90	1.25	1.40
50	1.50	1.75	2.20	2.60
100	1.60	2.00	2.40	3.00

D.C. AMPS	300 PIV 210 RMS	400 PIV 280 RMS	500 PIV 350 RMS	600 PIV 450 RMS
3	.27 ea.	.39 ea.	.37 ea.	.45 ea.
12	.90	1.30	1.40	1.65
35	2.00	2.35	2.60	3.00
50	3.25	4.00	4.75	6.00
100	3.60	4.50	5.25	9.00

### "SCR" SILICON CONTROLLED RECTIFIERS "SCR"

PRV AMP	AMP	AMP	AMP	PRV AMP	AMP	AMP
25	.30	.50	.85	250	1.75	2.15
50	.45	.75	1.00	300	2.00	2.40
100	.80	1.25	1.50	400	2.40	2.75
150	.90	1.50	2.00	500	3.20	3.40
200	1.25	1.80	2.25	600	3.40	4.00

### SPECIALS! SPECIALS!

100 Different Precision Resistors  
1/2-1-2 watt 1/2%-1% TOL \$1.50  
2 amp 1000 Piv Silicon Power Rect. .70 ea. 10 for \$6.50

### R.C.A. P.N.P. TRANSISTOR

Type 2N406 4 for \$1.00, 100 for \$18. FACTORY NEW

Computer Grade Condenser 15,500 MFD 15 VDC American Mfg. .75 ea.

Type IN34 DIODE GLASS .07 ea. 100 for \$5

Money Back guarantee. \$2.00 min. order. Orders F.O.B. NYC. Include check or money order. Shpg. charges plus. C.O.D. orders 25% down.

### Warren Electronic Components

230 Mercer St., N. Y., N. Y. 10012 • OR 3-2620

Circle 127 on reader's service card

## DID YOU MISS

the valuable Reader's Service Page?  
Turn back to page 70 for free info.

# ELECTRONICS

## Engineering-Technicians

Bachelor of Science Degree, 30 Months  
Save Two Years' Time

- Radio-Television Plus Color Technician (12 Months)
- Electronics Engineering Technology (15 Months)
- Electronics Engineering (B.S. Degree)
- Electrical Engineering (B.S. Degree)
- Mechanical Engineering (B.S. Degree)
- Civil Engineering (B.S. Degree)
- Architecture (B.S. Degree) (36 Months)

Approved for Veterans

DAY AND EVENING CLASSES

Write for Catalog and Registration Application.  
New Term Starting Soon.

Your Name .....

Address .....

City .....

State .....

## HEALD'S

ENGINEERING COLLEGE

Est. 1863-102 Years  
Van Ness at Post, RE  
San Francisco, Calif.


Electronic Technicians, Radio TV Technicians is at an all time high. Heald Graduates are in demand for Preferred High Paying Salaries. Train now for a lucrative satisfying lifetime career.

Circle 128 on reader's service card

# SCHOOL DIRECTORY

LEARN

## ELECTRONICS

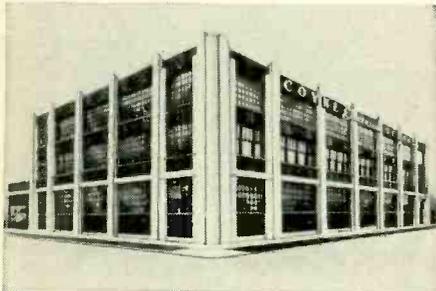

FOUNDED 1899

NOT-FOR-PROFIT

### COYNE ELECTRONICS INSTITUTE

Electronics Engineering Technology	—	Degree (2 Yrs.)
Electrical-Electronics Technician	—	Diploma (40 Wks.)
TV-Radio-Electronics Technician	—	Diploma (40 Wks.)
Combined Electronics Technician	—	Diploma (80 Wks.)
Practical Electrical Maintenance	—	Diploma (32 Wks.)
Practical Refrigeration Air Conditioning and Appliance Repair	—	Diploma (24 Wks.)
Specialized Industrial Electronics	—	Diploma (16 Wks.)
Introduction to Electricity-Electronics	—	Certificate (8 Wks.)
FCC First Class Radiotelephone	—	Certificate (100 Hrs.)

Special finance plans. Part time employment service while in school. Also Free graduate employment service.



Use this coupon to get our FREE BOOK "YOUR OPPORTUNITIES IN ELECTRONICS" COYNE ELECTRONICS INSTITUTE, Dept. of Electronics 95-N 1501 W. Congress Parkway, Chicago, Illinois 60607

Name \_\_\_\_\_ Age \_\_\_\_\_  
Address \_\_\_\_\_ Phone \_\_\_\_\_  
City \_\_\_\_\_ Zone \_\_\_\_\_ State \_\_\_\_\_

Unlike most other schools, we do not employ salesmen  
Circle 129 on reader's service card

## B.S. degree in 36 months

Small professionally-oriented college. Four-quarter year permits degree completion in three years. Summer attendance optional. **Engineering:** Electrical (electronics or power option), Mechanical, Civil, Chemical, Aeronautical. **Business Administration:** Accounting, General Business, Motor Transport Administration. One-year Drafting and Design Certificate program. Graduate placement outstanding. Founded 1884. Rich heritage. Excellent faculty. Small classes. Well-equipped labs. New library. New residence halls. Attractive 300-acre campus. Modest costs. Enter Jan., March, June, Sept. For Catalog and View Book, write Director of Admissions.



**TRI-STATE COLLEGE**

24125 College Avenue, Angola, Indiana

### ENGINEERING DEGREES



Associate—Bachelor  
Also Associate in LIBERAL ARTS earned by

#### HOME STUDY

Resident Classes Also Available if Desired  
Specify course preferred

**PACIFIC INTERNATIONAL COLLEGE OF ARTS & SCIENCES**

Primarily a correspondence school  
Chartered 1935  
5507 M Santa Monica Blvd. Hollywood, Calif., 90038

### EARN Electronics ENGINEERING DEGREE

You can earn an A.S.E.E. degree at home. College level HOME STUDY courses taught so you can understand them. Continue your education, earn more in the highly paid electronics industry. Missiles, computers, transistors, automation, complete electronics. Over 27,000 graduates now employed. Resident school available at our Chicago campus—Founded 1934. Send for free catalog.  
**American Institute of Engineering & Technology**  
1139 West Fullerton Parkway, Chicago 14, Ill.

#### GET INTO

### ELECTRONICS

V.T.I. training leads to success as technicians, field engineers, specialists in communications, guided missiles, computers, radar and automation. Basic & advanced courses in theory & laboratory. Electronic Engineering Technology and Electronic Technology curricula both available. Assoc. degree in 29 mos. B.S. also obtainable. G.I. approved. Graduates in all branches of electronics with major companies. Start Feb., Sept. Dorms, campus, High school graduate or equivalent. Catalog.

**VALPARAISO TECHNICAL INSTITUTE**  
Department C, Valparaiso, Indiana




#### Learn Electronics for your SPACE-AGE EDUCATION at the center of America's aerospace industry

No matter what your aerospace goal, you can get your training at Northrop Tech. in sunny Southern California.

**COLLEGE OF ENGINEERING.** Get your B.S. degree in engineering in just 36 months by attending classes year round. Most Northrop Tech graduates have a job waiting for them the day they're graduated!

**A & P SCHOOL.** Practical experience on real aircraft. One-year course prepares you for F.A.A. A & P certificate.

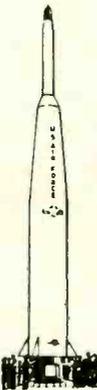**WRITE TODAY FOR CATALOG.**  
**NORTHROP INSTITUTE OF TECHNOLOGY**  
1199 W. Arbor Vitae, Inglewood, Calif.



### A JOB or a POSITION?

The difference is **ELECTRONIC MATHEMATICS**

**NOW! A NEW WAY TO LEARN—I. H. S. I. WAY.** A complete home study course in electronic math to help you get the position you want—**MORE MONEY—MORE RESPECT.**

**COURSE PREPARED BY COLLEGE PROFESSORS** who have lectured to thousands of men on math and engineering. You learn at home quickly, easily—**AS FAST** as you want.

**YOU SIGN NO CONTRACTS** Pay only if satisfied—you owe it to yourself to examine the **INDIANA HOME STUDY INSTITUTE COURSE IN ELECTRONIC MATH.**  
**FREE BONUS**—if you join now, a refresher course in basic arithmetic.

Write for Brochure—No Obligation  
**THE INDIANA HOME STUDY INSTITUTE**  
Dept. RE-12, P.O. Box 1189  
Panama City, Fla. 32402

## Earn Your A.S.E.E. DEGREE and More Money

Move up. Increase your salary and prestige. How? By acquiring the knowledge and skill that industry needs and pays for!

The unique A.S.E.E. degree program available at Grantham School of Electronics teaches you what industry wants you to know for *advanced* employment. And you can complete three-fourths of this program while at home on your present job. Only one semester must be completed in residence.

You are eligible to enroll if you are (1) a high school graduate, and (2) now employed in electronics. Even the first few lessons should help you understand your job better—perhaps enable you to earn a promotion. Upon completion of the second semester's work, you should have already passed the F.C.C. examinations for your first class radiotelephone license and radar endorsement. Upon completion of four semesters of technical work, one English course, one history course, and one year of technical employment in electronics, you are awarded the A.S.E.E. (Associate in Science in Electrical Engineering) degree. The year of technical employment may be completed either during your enrollment or within two years after you complete the educational program.

Get the facts from our free catalog. Then, with our assistance, get the knowledge. Your F.C.C. license, your A.S.E.E. degree, and higher-paid employment follow naturally. Ask for CATALOG 57-T.

#### Grantham School of Electronics

1505 N. Western Av., Hollywood, Cal. 90027  
(Phone: HO 9-7878)

OR

818 18th St., NW, Washington, D.C. 20006  
(Phone: 298-7460)

Circle 130 on reader's service card

RADIO-ELECTRONICS

# NEW BOOKS

**BASIC ELECTRONICS**, by Bernard Grob. McGraw-Hill Book Co., 330 W. 42 St., New York, N. Y. 10036. 6½ x 9½ in., 588 pp. Cloth, \$7.50

A true basic book. Every effort has been made to keep the language simple, and the mathematics within the bounds of ordinary arithmetic, even when explaining such things as complex numbers, Kirchhoff's laws and Thevenin's theorems. The second edition is thoroughly revised with two chapters added.

**ELECTROMAGNETIC THEORY AND GEOMETRICAL OPTICS**, by Morris Kline and Irvin W. Kay. John Wiley & Sons Inc., 605 Third Ave., New York, N.Y. 10016. 6 x 9 in., 525 pp. Cloth, \$15

Electromagnetic-theory approach to classical geometrical optics. Written for physicists and mathematicians.

**ELECTRIC GUITAR AMPLIFIER HANDBOOK**, by Jack Darr. Howard W. Sams & Co., Inc., 4300 W. 62 St., Indianapolis 6, Ind. 5½ x 8½ in., 144 pp. Paper, \$2.95

Typical circuits, service methods and testing techniques plus all the information available on commercial instruments. Many schematics and a few parts layout diagrams.

**ELECTRONIC SYSTEMS FOR CONVENIENCE, SAFETY AND ENJOYMENT**, by Edward A. Alshuler. Howard Sams & Co., Inc., 4300 W. 62 St., Indianapolis 6, Ind. 5½ x 8½ in., 255 pp. Paper, \$4.95

A review of the present and future of electronics, from a commercial rather than technical viewpoint. Covers entertainment, communication systems, controls, office systems, education, government and medicine. Part III is entitled "The ABC's of Selling Electronic Systems."

**WAVEFORMS**. Dover Publications, Inc., 180 Varick St., New York, N.Y. 10014. 5½ x 8½ in., 785 pp. Paper, \$3.25

Originally authored and edited by many specialists for MIT Radiation Labs. A comprehensive survey of generators, shapers, timers, counters and modulators. Includes many schematics with parts values and wave patterns. Tubes are those of 15 and 20 years ago, but circuits are still very useful.

**GENERAL ELECTRIC ELECTRONIC COMPONENTS HOBBY MANUAL**, (2nd edition). Electronic Components Div., General Electric, Owensboro, Ky. 5½ x 8½ in., 199 pp. Paper, \$1.50

Includes 5 automobile projects, 10 entertainment projects, 9 for home or camp, and 11 for the electronic experimenter's workshop, with an excellent introduction about the structure and operation of various semiconductor components.

**BEST WAYS TO USE YOUR VOM AND VTVM**, written under direction of Publications Div., Allied

when it's time to think of college you should read this

**FREE CAREER BOOKLET** about electronics at

## MSOE



**MILWAUKEE MS-237**  
**SCHOOL OF ENGINEERING**  
 Dept. RE-1265, 1025 N. Milwaukee Street  
 Milwaukee, Wisconsin 53201  
 Tell me about an engineering career through residence study in:

Electrical fields     Mechanical fields

Name.....Age.....  
 Address.....  
 City, State.....

Radio Corp., edited by Fred Shunaman. Allied Radio Corp., 100 N. Western Ave., Chicago, Ill. 60680. 5½ x 8½ in., 96 pages. Paper, 50 cents

Complete coverage for the beginning user; describes fundamentals, testing components, checking hi-fi equipment, receivers, CB and ham gear, and continues with miscellaneous applications (measuring light intensity, soil resistance, etc.) and care of the instruments. **END**

**NEON AC/DC ELECTRIC TESTER**  
FOR HOME AUTO SHOP  
**Special! 59¢**

**Special!**  
With every \$10 Order  
**25¢**  
per tube  
(No Limit) from this list.

6AG5	6SN7
6AU6	6J6
6AQ5	6K6
6W4	

# CORNELL TUBES

## 1 YR. GUARANTEED

Mutual Conductance Lab-tested, Individually Boxed, Branded and Code Dated Tubes are new, or used and is marked

33¢

PER TUBE

100 TUBES OR MORE:  
**30¢ PER TUBE**

**21 PICTURE TUBES**  
1395 1 1/2" Size  
Minimized Pay Dad Deposit  
COD or Send Dues with Order

11A9A	20PP4	21DP4
11B2A	21AP4	21EP4
11B4A	21AK4	21EK4
11B6A	21AL4	21EL4
11C4	21AR4	21ER4
11D4	21AW4	21EW4
20C4	21AX4	21EX4
20D4	21AY4	21EY4
	21C4	

0Z4	6AS5	6CD6	6K6	6X4	12BF6
1B3	6AT6	6CF6	6K7	6X8	12BH7
1J3 1K3	6AT8	6CG7	6Q7	7A7	12BL6
1H5	6AU4	6CG8	6S4	7AB	12BY7
1L4	6AU5	6CM7	6SA7	7B6	12C5
1L4	6AU6				12C5
1T4	6AV6				12CA5
1U4	6AW8				12SN7
1X2	6AX4				12SQ7
3BZ6	6BA6				25L6
3DG4	6BC5				25Z6
5U4	6BD6	6CZ5	6SH7	7C5	35W4
5U8	6BG6	6D6	6SJ7	7N7	35Z3
5V4	6BG6	6DA4	6SK7	7Y4	50L6
5Y3	6BJ6	6DE6	6SL7	12AD6	24
6A6	6BL7	6DQ6	6SN7	12AE6	27
6A8	6BN4	6EA7	6SQ7	12AF6	77
6AB4	6BQ6	6EM5	6SR7	12AT7	78
6AC7	6BR7	6F6	6U8	12AU7	84/6Z4
6AG5	6BZ6	6GH8	6V6	12BA6	56B7
6AK5	6C4	6H6	6W4	12BD6	6350
6AL5	6C6	6J5	6W4	12BE6	6463
6AN8	6CB6	6J6	6W6	12BF6	7044
6AQ5					

Other tubes at low prices... send for free list

**NO SUBSTITUTIONS WITHOUT YOUR PERMISSION**

**all purpose ELECTRONIC CLEANER**  
89¢ plus shipping

**SILICON RECTIFIERS**  
750 MA 400 P.I.V. **69¢** PAIR

**DIODES / RECTIFIERS**  
39¢ per pack sensational **KIT VALUE!**

**21 PICTURE TUBES**  
1395 1 1/2" Size  
Minimized Pay Dad Deposit  
COD or Send Dues with Order

**CHEATER CORDS**  
29¢ plus shipping

**NOISE FILTER STOP TV & RADIO NOISE INSTANTLY!**  
89¢ plus shipping

**SOLDERING GUN**  
EASY TO HANDLE **HOT SHOT**  
THE ALL PURPOSE ELECTRIC SOLDERING GUN  
2.99 plus shipping

**Electronic SOLDER**  
SOLDER  
sensational **VALUE! 29¢**

# CORNELL ELECTRONICS CO.

Dept. RE 12 4217 University Ave., San Diego, Calif. 92105

# MARKET CENTER

## FREE CATALOG!



148 PAGES • NEARLY 4,000 BARGAINS  
OPTICS • SCIENCE • MATH

Completely new 1986 edition. New items, categories, illustrations, 148 easy-to-read pages packed with nearly 4000 unusual items. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes, Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Many war surplus items: for hobbyists, experimenters, workshop, factory. Write for catalog "EH".

### CLIP AND MAIL COUPON TODAY

EDMUND SCIENTIFIC CO., Barrington, N. J.  
PLEASE SEND ME FREE CATALOG "EH"

Name .....  
Address .....  
City ..... State .....

### CONVERTER SALE

New series 300 with 3 VHF-UHF transistors, crystal-controlled oscillator, tuned R.F. stage and low noise mixer. One microvolt sensitivity. More than 30 high quality parts carefully assembled and tested. Measures only 3" x 2 1/4" x 2". Operates at 12 volts DC 4-5 ma. Available in the following models:

	Model	Input mc.	Output mc.	Price
2M	300-D	144-148	50-54	\$12.95 ppd.
	300-E	144-145	6-1.6	\$12.95 ppd.
	300-F	144-146	28-30	\$12.95 ppd.
	300-Q	144-148	14-18	\$12.95 ppd.
6M	300-B	50-51	6-1.6	\$12.95 ppd.
	300-C	50-54	14-18	\$12.95 ppd.
	300-J	50-52	28-30	\$12.95 ppd.
20M	300-G	14.0-14.35	1.0-1.35	\$11.95 ppd.
	300-A	26.965-27.255	1.0-1.29	\$11.95 ppd.
CB	300-H	5.0	1.0	\$11.95 ppd.
WWV	300-I	9.0-10.0	6-1.6	\$11.95 ppd.
CHU	300-K	7.3	1.0	\$11.95 ppd.
	300-L	3.35	1.0	\$11.95 ppd.
Marine	300-M	2-3	6-1.6	\$11.95 ppd.
Aircraft	300-N4	121-122	6-1.6	\$13.95 ppd.
	300-N5	122-123	6-1.6	\$13.95 ppd.
Fire, Police, etc.	300-P	155-156	6-1.6	\$13.95 ppd.

All above converters are supplied with Motorola type connectors. For two SO-239 connectors instead, add 75¢

For prompt shipment of stock models include postal money order or cashier's check. Special models shipped within six weeks. Personal checks must clear before shipment. For C.O.D.'s include 20% deposit. New York City residents add 5% sales tax. New York State residents add 2% Sales tax.

VANGUARD ELECTRONIC LABS Dept. R-12  
190-48-99th Ave. Hollis 23, N. Y.

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services): 60¢ per word . . . minimum 10 words.

NON-COMMERCIAL RATE (for individuals who want to buy or sell personal items): 30¢ per word . . . no minimum.

Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. Misleading or objectionable ads not accepted. Copy for February issue must reach us before December 10th.

WORD COUNT: Include name and address. Name of city (Des Moines) or of state (New York) counts as one word each. Zone or Zip Code numbers not counted. (We reserve the right to omit Zip Code if space does not permit.) Count each abbreviation, initial, single figure or group of figures or letters as a word. Symbols or groups such as 8x10, COD, AC, etc., count as one word. Hyphenated words count as two words. Minor over-wordage will be edited to match advance payment.

## GENERAL

TV SERVICE ORDER BOOKS for use with your rubber stamp. Duplicate or triplicate. Low cost. Write for FREE 32 PAGE CATALOG and Special Rubber Stamp Offer. OELRICH PUBLICATIONS, 6556 W. Higgins, Chicago, Ill. 60656.

CONVERT ANY TELEVISION to sensitive Big-Screen Oscilloscope. Only minor changes required. No electronic experience necessary. Illustrated plans \$2.00. RELCO-A25, Box 10563, Houston 18, Texas.

FREE Wine Recipes and Home Brewing Supplies Catalog COUNTRY WINEMAKER, Box 243RE, Lexington, Massachusetts

ALNICO-CERAMIC-FLEXIBLE-ASSEMBLIES. What you need, we have. MARYLAND MAGNET, 5412G Gist, Baltimore, Maryland 21215.

AUTOMATIC WASHER Repair Manuals for: Frigidaire, General Electric, Hamilton, Hotpoint, Kelvinator, Kenmore, Norge, RCA Whirlpool, Speed Queen, Westinghouse. \$2.50 EA. PPD. Refrigeration Parts Catalog 50¢. Sunbeam Appliance parts list 25¢. MAJOR APPLIANCE, 13106 Caine Avenue, Cleveland, Ohio 44105.

PICTORIAL STUDY in Amateur radio. Free details. D. CROSS, 1212 Lynch, St. Louis, Mo. 63118.

ADD, SUBTRACT, MULTIPLY, DIVIDE with switches and diodes. Instructions and theory \$1.95. FERWALT, Box 27, Lewiston, Idaho 83501.

MELODY ORGAN, easy to build. Demonstration record \$1. Construction Manual \$3. Free folder. SOLOTRON COMPANY, 29641 Gilchrist, Farmington, Mich.

## WANTED

QUICK CASH . . . for Electronic EQUIPMENT, COMPONENTS, unused TUBES. Send list now! BARRY, 512 Broadway, New York, N. Y. 10012, 212 WALKER 5-7000.

CASH, SONY TRANSISTOR TV's etc. swapped for G-R, H-P, L&N etc. equipment, special tubes, manuals, military electronics. ENGINEERING ASSOCIATES, 428 Patterson Road, Dayton, Ohio 45419.

ELECTRICAL EXPERIMENTER, most issues 1913-1920 for cash, optical or electronic equipment or will swap Science and Invention. E. KAPRELIAN, 811 Phila. Rd., Joppa, Md. 21085

LABORATORY test equipment. ELECTRONIC-CRAFT, P. O. Box 13, Binghamton, N.Y. 13902

## SERVICES

METERS—MULTIMETERS REPAIRED and calibrated. BIGELOW ELECTRONICS, Box 71-B, Bluffton, Ohio.

TRANSISTORIZED products dealers catalog, \$1. INTERMARKET, CPO 1717, Tokyo, Japan.

## AUDIO - HI-FI

COMPONENT QUOTATIONS—tapes Mylar 1800' postpaid \$1.59 each. BAYLA, Box 131RE Wantagh, N.Y.

WRITE for highest discounts on components, recorders, tapes, from franchised distributors. Send for FREE monthly specials. CARSTON, 1686-R Second Ave. N.Y.C. 10028

RENT STEREO TAPES—over 2,500 different—all major labels—free brochure. STEREO-PARTI, 1616 Terrace Way, Santa Rosa, Calif.

HI-FI COMPONENTS, Tape Recorders, at guaranteed "WE will not be undersold" prices. 15-day moneyback guarantee. Two-year warranty. NO Catalog. Quotations Free. HI-FIDELITY CENTER, 1797 (R) 1st Ave., New York, N.Y. 10028

TAPE RECORDER SALE. Brand new, latest models, \$10.00 above cost. ARKAY SALES, 1028-E Commonwealth Ave., Boston, Mass. 02215.

LOW LOW QUOTES, DYNA. A.R. GARRARD E.V. HI-FI, Roslyn, Pa. 19001

### Rectifiers & Transistors

#### 750 Ma-Silicon Diodes "Epoxy" or "Top Hat"

PIV	PIV	PIV	PIV
50	5¢	300	12¢
100	7¢	400	14¢
200	10¢	500	18¢
		600	21¢
		700	25¢
		800	32¢
		900	40¢
		1000	55¢
		1100	70¢

Full Leads, All tests, Guaranteed, American made

#### Silicon Power Diode Studs

Amps	50 PIV	100 PIV	150 PIV	200 PIV
3	8¢	14¢	16¢	22¢
15	25¢	50¢	65¢	75¢
18*	18¢	40¢	60¢	70¢
35	60	80	1.15	1.30

Amps	300 PIV	400 PIV	500 PIV	600 PIV
3	25¢	28¢	35¢	40¢
15	90	1.30	1.40	1.65
18*	85	1.25	1.35	1.60
35	1.90	2.25	2.50	2.90

\*Press Fit Package for Alternators  
 10 Watt Sil. Zener Stud 12-200 v, 20% . . . 95¢ ea.  
 1 Watt Zener diode, axial leads 8-200v, 20% . . . 50¢ ea.  
 Sil. diode Stud, 1500 PIV, 300ma . . . 50¢ ea.  
 Sil. diode, 1500 PIV, 50ma, axial leads . . . 35¢ ea.  
 Hi-Voltage-Silicon epoxy diode, 2 1/2" x 3/8" x 1/2" . . . \$1.49 ea.  
 Hoffman—6000 PIV-200ma . . . \$3.49 ea.  
 Hoffman—6000 PIV-200ma . . . \$3.49 ea.  
 Thermistor, bead, 900 or 1200 ohms, 600°F, 2/\$1.00

#### 20 Watt Ger. (Int & Ext heat sink)

#### 150 w Ger Power TD-3

2N1044	60¢	2N1045	80¢
2N457A	80¢	2N1022	1.25
2N458A	90¢	2N511B	1.50
2N1021	1.00	(25 amp)	

Silicon Power Transistors, 85 w, 2N1724 . . . \$1.50  
 Philco Sil., NPN, 2N2479, new . . . 3 for \$1.00  
 HF Silicon, 2N702, 100 mc 40¢; 2N703-150 mc 60¢

#### Light Sensitive Resistor

75 ohms—10 meg, 100 volts, 150mw . . . \$1.75 ea.

Sil. diodes, 1N200 series, ass't'd., new . . . 15 for \$1.00  
 Ger. diodes, glass, new, exceeds 1N34 . . . 15 for \$1.00  
 Nickel-Cadmium Battery, 9 1/2 oz., 8 amp-hr. . . \$1.95

#### Varicap-Voltage Variable Capacitor

27, 47, or 100 pf, 4v, 4:1, new . . . \$1.25 ea.

#### Silicon Controlled Rectifiers

PRV	.75A	1A	7A	16A	PRV	.75A	1A	7A	16A
25	—	.20	.28	.48	200	.80	.90	1.05	1.70
50	—	.40	.48	.70	300	1.20	1.30	1.60	2.20
100	—	.55	.70	1.20	400	1.70	1.85	2.10	2.70
150	.60	.70	.80	1.50	500	1.95	2.05	3.80	3.30
75A Tophat	—	1A T0.5	—	7A	600	2.30	2.50	3.00	3.90

& 16A Stud  
 Money back guaranteed. \$2.00 min. order, include postage.  
 Catalog 25¢.

Electronic Components Co.  
 Box 2902B Baton Rouge, La. 70821

Circle 133 on reader's service card  
RADIO-ELECTRONICS



# MARKET CENTER

## DISTRIBUTOR WANTED

No competition. To service and set up new accounts in exclusive territory. Investment secured by fast moving inventory of amazing plastic coating used on all types of surfaces interior or exterior. Eliminates waxing when applied to any type of floor. Eliminates all painting when applied to wood, metal or concrete surfaces.

Minimum Investment—\$500  
Maximum Investment—\$12,000

For details write or call:  
Phone: 314 AX-1-1500  
MERCHANDISING DIVISION  
P. O. BOX 66  
ST. ANN, MISSOURI 63074

## SUB CARRIER DETECTOR



Add programs of commercial-free music thru your FM tuner. Detector, self-powered, plugs into multiplex output of tuner or easily wired into discriminator and permits reception of famous background music programs now transmitted as hidden programs on the FM broadcast band from coast to coast. Use with ANY FM tuner.

WIRED UNIT \$75.00  
KIT, with pretuned coils,  
no alignment necessary \$49.50  
crystal-controlled receivers available

MUSIC ASSOCIATED  
65 Glenwood Road  
Upper Montclair, New Jersey  
phone 744-3387 area code 201

## EMPLOYMENT OPPORTUNITIES

FLORIDA EMPLOYMENT. List of Florida Electronic-Aerospace Firms \$3.00. J. ROTHFUSS, P.O. Box 966, Lake Worth, Florida 33460.

## ELECTRONICS

FREE CATALOG of 200 special slide rules and calculating aids. DYNA-SLIDE, 600 South Michigan, Chicago, Illinois 60605

TV CAMERAS, transmitters, converters, etc. Lowest factory prices. Catalog 10¢. VANGUARD, 190-48-99th Ave., Hollis, N.Y. 11423.

BARGAINS in Canadian Electronic equipment and surplus. Send \$1.00 for giant catalogs. ETCO, Dept. R, 520 Fifth Avenue, New York 36, N.Y.

SEMI-SWEEPER sweep generator circuit boards. Refer September issue RADIO-ELECTRONICS, \$1.00. PAULIN SALES, Box 122, Upland, California.

PROFESSIONAL ELECTRONICS PROJECTS — Organs, Timers, Computers, etc.—\$1 up. Catalog 25¢, refundable. PARKS, Box 25565, Seattle, Wash. 98125.

BEFORE You Buy Receiving Tubes, Transistors, Diodes, Electronic Components & Accessories ... send for Giant Free Zalytron Current Catalog, featuring all STANDARD BRAND TUBES all Brand New Premium Individually Boxed. One Year Guarantee—all at BIGGEST DISCOUNTS in America! We serve professional servicemen, hobbyists, experimenters, engineers, technicians. WHY PAY MORE? ZALYTRON TUBE CORP., 469R Jericho Turnpike, Mineola, N.Y. 11502

## CLASSIFIED ADVERTISING ORDER FORM

For complete data concerning classified advertising please refer to box elsewhere in Market Center section.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35

No. of Words { @ .30 Non-Commercial Rate } = \$  
{ @ .60 Commercial Rate }

Total Enclosed \$

Insert \_\_\_\_\_ time(s)

Starting with \_\_\_\_\_ issue

Payment must accompany order unless placed through accredited advertising agency 125

NAME \_\_\_\_\_

ADDRESS \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_

SIGNATURE \_\_\_\_\_

MAIL TO: RADIO-ELECTRONICS, CLASSIFIED AD DEPT., 154 WEST 14TH ST., NEW YORK, N.Y. 10011

# ADVERTISING INDEX

RADIO-ELECTRONICS does not assume responsibility for any errors which may appear in the index below.

Acoustic Research, Inc. ....	9
Allied Radio Corp. ....	75
Birnbach Radio Co., Inc. ....	20
B & K Manufacturing Co., (Div. of Dynascan Corp.) .....	25
Blonder-Tongue .....	13
Brooks Radio & TV Corp. ....	92-93
Burstein-Applebee Co. ....	65
Capitol Radio Engineering Institute, The ....	11
Castle TV Tuner Service, Inc. ....	6
<b>Classified</b> .....	<b>98-101</b>
Cleveland Institute of Electronics .....	8, 60-63
Conar (Div. of National Radio Institute) ....	73
Cornell Electronics Co. ....	97
DeVry Technical Institute .....	5
Edlie Electronics, Inc. ....	94
EICO Electronic Instrument Co., Inc. ....	30
Electro-Voice, Inc. ....	10
Electronic Measurement Corp. (EMC) .....	88
Fair Radio Sales .....	76
Gernsback Library, Inc. ....	76, 78-79, 86
Heald's Engineering College .....	95
Heath Company .....	66-67
Hy-Gain Electronics Corporation .....	15
International Crystal Mfg. Co., Inc. ....	8, Third Cover
Jackson Electrical Instrument Company ....	12
Jerrold Electronics Corporation (Distributor Sales Division) .....	81
JFD Electronics Corp. ....	7
Krylon .....	22
Lafayette Radio Electronics .....	83
Mallory Distributor Products Company (Div. of P.R. Mallory & Co., Inc.) .....	23
Milwaukee School of Science & Engineering	97
Multicore Sales Corp. ....	75
National Radio Institute .....	16-19
Olson Electronics, Inc. ....	72
Oxford Transducer Company (A Division of Oxford Electric Corporation) .....	22
Poly Paks .....	101
Precise Electronics & Development (Div. of Designatronics, Inc.) .....	2
Progressive "Edu-Kits" Inc. ....	89
Radar Devices Manufacturing Corp. ....	1
Radio Shack .....	102
Ray Tel (Raytheon) .....	91
RCA Components & Devices Tube Division .....	Fourth Cover
RCA Institutes, Inc. ....	26-29
Rye Sound Corporation .....	82
Sams & Co., Inc., Howard W. ....	21, 64
Sarkes Tarzian, Inc. (Tuner Service Div.) ...	14
Schober Organ Corp., The .....	24
Score .....	90
Tarzian, Inc. Sarkes (Tuner Service Div.) ...	14
Triplett Electrical Instrument Company, The .....	Second Cover
Turner Microphone Company, The .....	80
United Radio Co. ....	99
University Sound (Div. of LTV Ling Altec, Inc.) .....	72
Warren Electronic Components .....	95
Weller Electric Co. ....	88
Wen Products, Inc. ....	68
Windsor Electronics, Inc. ....	82
Winegard Co. ....	74
<b>MARKET CENTER</b> .....	<b>98-101</b>
Edmund Scientific Corp.	
Electronic Components Co.	
Music Associated	
Penguin Plastics & Paint Corp.	
Vanguard Electronic Labs	
<b>SCHOOL DIRECTORY</b> .....	<b>96-97</b>
American Institute of Engineering & Technology	
Coyne Electronics Institute	
Grantham School of Electronics	
Indiana Home Study Institute	
Milwaukee School of Engineering	
Northrop College of Science & Engineering	
Pacific International College	
Tri-State College	
Valparaiso Technical Institute	

TRANSISTOR IGNITION! Coil, ballast 7.95 Free parts lists. TRANSFIRE Carlisle 20, Mass. 01741

TRANSISTOR ignition kits, components. Free diagrams. ANDERSON ENGINEERING, Epsom, N.H. 03239

RADIO & TV TUBES 33¢ each. One year guaranteed. Plus many unusual electronic bargains. Free catalog. CORNELL, 4217-E University, San Diego, California 92105

36 PAGE CITIZENS BAND CATALOG. All major brands and accessories. 10¢ Dealer inquiries invited. KNOX ELECTRONIC, Dept. RE-2, Galesburg, Ill. 61401

TUBES. "Oldies", latest. Lists free. STEINMETZ, 7519 Maplewood, Hammond, Indiana, 46324.

FREE Catalog. Electronic parts, tubes. Wholesale. Thousands of items. Unbeatable prices. ARCTURUS ELECTRONICS RE, 502-22 St., Union City, N. J. 07087

McGEE RADIO COMPANY. Big 1966 catalog sent free. America's best values. Hi-Fi-amplifiers-speakers-electronic parts. Send name, address and zip code number to McGEE RADIO COMPANY, 1901 McGee Street, Dept. RE, Kansas City, Missouri 64108

TELEVISION CAMERAS transistorized also monitors. SPERA ELECTRONICS, 37-10 33 Street Long Island City, N. Y.

GOVERNMENT SURPLUS Jeeps from—\$52.50, Voltmeters from—\$1.05, Transmitters from—\$6.18, Oscilloscopes, Walkie-Talkies, Multimeters. Typical "As Is" Bid Bargains from Uncle Sam. Tremendous variety. Exciting free list. Write: ENTERPRISES, Box 402-F4, Jamaica, New York 11430.

METAL DETECTORS and kits, powerful, sensitive, light-weight, rugged. High-quality circuits, low cost. ELECTRONIC DEVELOPMENT, INC.; 2538-R Colorado, Sarasota, Florida.



**Christmas Seals protect all homes.**  
Help protect your home against tuberculosis and other respiratory diseases. Answer your Christmas Seal letter today!



GIANT 20th Anniversary Catalog. TV Cameras and Electronic Equipment. FREE copy. DENSON ELECTRONICS, Rockville, Conn.

T.V. Servicemen. Write for free list of good buys on parts. M & S ELECTRONICS, Box 3971, Wichita, Kansas 67216.

EXPERIMENTERS, BUILDERS giant catalog—25¢, refundable. LABORATORIES, 993-B, Redwood City, California 94064.

## EDUCATION/ INSTRUCTION

LEARN ELECTRONIC ORGAN SERVICING. New home study course covering all makes electronic organ including transistors. Experimental kits—schematics—trouble-shooting. Accredited NHSC-GI Approved. Write for free booklet. NILES BRYANT SCHOOL, 3631 Stockton Blvd., Dept. F, Sacramento 20, Calif.

HIGHLY—effective home study review for FCC commercial phone exams. Free literature! COOK'S SCHOOL OF ELECTRONICS, Craigmont, Idaho 83523.

FCC LICENSE in 6 weeks. First Class Radio Telephone. Results Guaranteed. ELKINS RADIO SCHOOL, 2603E Inwood, Dallas, Tex.

SLEEP LEARNING. Hypnotism! Tapes, records, books, equipment. Details, strange catalog FREE. RESEARCH ASSOCIATION, Box 24-RD, Olympia, Wash.

BROADCASTING, Communications Electronics taught quickly—resident classes; correspondence. Free details. Write: Dept. 4, GRANTHAM SCHOOLS, 1505 N. Western, Hollywood, Calif. 90027

RADIO/TELEVISION SERVICING. Train at home in your spare time. Keep your job and still earn while you learn. No contract to sign. Write for particulars on Coordinated Training Units. SPRAY-BERRY, Dept. CS-468-MW, 1512 Jarvis Avenue, Chicago, Illinois 60626.

**DOUBLE BONUS**

\$25

WORTH OF  
TRANSISTORS  
RECTIFIERS  
RESISTORS  
CONDENSERS  
DIODES & ETC

Add 25¢ for handling

**BOTH FREE WITH ANY \$10 ORDER**

**WORLD'S MOST POPULAR \$1 PARTS PAKS**

**1.00**

3-TRANSISTOR AUDIO AMPLIFIER  
 Printed Circuit       Subminiature  
 With Transistors       Wired

40 WORLD'S SMALLEST COND., to .05mf ... \$1  
 4 TRANSISTOR TRANSFORMERS, asst. worth \$25 \$1  
 \$25 RELAY SURPRISE, sealed, tiny types ... \$1  
 3 INFRA-RED DETECTORS, with leads ... \$1  
 \$25 SURPRISE PAK: transistors, rect, diodes, etc. \$1  
 40 CORNING "LOW NOISE" resistors, asst. ... \$1  
 60 TUBULAR CONDENSERS, to .5mf, to 1Kv, asst \$1

**85 WATT**

NPN SILICON MESA



2N1212 Drift. 10 mc \$1.00 EA  
 2N424 \$1.99

**HIGH VOLTAGE RECTIFIERS**



-6000 piv 200 ma.  
**\$1.99**

- 60 TUBE SOCKETS, receptacles, plugs, audio, etc. \$1
- 30 POWER RESISTORS, 5 to 50W, to 24 Kohms. \$1
- 50 MICA CONDENSERS, to .1mf, silvers too! . \$1
- 10 VOLUME CONTROLS, to 1 meg, switch too! . \$1
- 10<sup>6</sup> ELECTROLYTICS, to 500mf, asst FP & tubulars \$1
- 50 RADIO & TV KNOBS, asstd, colors & styles . \$1
- 10 TRANSISTOR ELECTROLYTICS: 10mf to 500mf \$1
- 50 COILS & CHOKES, if, rf, ant, osc, & more . \$1
- 3<sup>1</sup>/<sub>2</sub> TWO WATERS, asst incl: A.B., 5% too! . \$1
- 75 HALF WATERS, asst incl: A.B., 5% too! . \$1
- 60 HI-Ω RESISTORS, 1/2, 1, 2W, 1% & 5% values \$1
- 10 PHONO PLUG & JACK SETS, tuners, amps . \$1
- 30 "YELLOW" MYLAR CONDENSERS, asstd, val \$1
- 60 CERAMIC CONDENSERS. discs. npo's: to .05 \$1
- 40 "TINY" RESISTORS, 1/10W, 5% too! . . . \$1
- 5 SUN BATTERIES TO 1 1/2" sizes, lite sensitive \$1
- 10 TRANSISTOR SOCKETS for pnp-npn transistors \$1
- 40 PRECISION RESISTORS. 1/2, 1, 2W: 1% values \$1
- 60 DISC CONDENSERS. 27mmf to .05mf to 1KV \$1

**ZENER VOLTAGE REGULATORS 1 watt**

**3 for \$1**

| Volts |
|-------|-------|-------|-------|-------|-------|-------|-------|
| 6.8   | 10    | 15    | 22    | 33    | 47    | 68    | 100   |
| 7.5   | 11    | 16    | 24    | 36    | 51    | 75    | 110   |
| 8.2   | 12    | 18    | 27    | 39    | 56    | 82    | 120   |
| 9.1   | 13    | 20    | 30    | 43    | 62    | 91    | 130   |

**TRANSITRON**

TESTED SILICON CONTROLLED RECTIFIERS

PRV	7A AMP	16A AMP	25A AMP	PRV	7 AMP	16 AMP	25 AMP
25	.30	.50	.85	250	1.75	2.15	2.50
50	.45	.75	1.00	300	2.00	2.40	2.75
100	.80	1.25	1.50	400	2.40	2.75	3.25
150	.90	1.60	2.00	500	3.20	3.40	3.80
200	1.25	1.85	2.25	600	3.40	4.00	4.50

# sale

**DELCO HIGH POWER \$1**

PNP 100Watt/15 Amp HiPower  
T036 Case1 2N441, 442, 277,  
278. DS501 up to 50<sup>2</sup> Volts



**FACTORY TESTED SEMI-KON-DUCTORS**

- 40 FAMOUS "EPOXY" DIODES, asst. untested. \$1
- 3 500MC TRANS'TRS, 2N964, messas. nnp. TO18 \$1
- 4 2N35 TRANSISTORS, nnp, by Sylvania. TO22 \$1
- 4 2N43 OUTPUT TRANSISTORS, by GE, pnp, TO5 \$1
- 4 2N333 NPN SILICON transistors, by GE, TO5 \$1
- 8, 2-6 Amp RECT's, studs, silicon, 50 to 400V . \$1
- 4-2N170 TRANSISTORS, by GE, rf, npns . . . \$1
- 2-35 AMP SILICON STUD RECTIFIERS . . . \$1
- 4 2N35 TRANSISTORS, nnp, by Sylvania, TO22 . \$1
- 2-800 MC, 2N709 NPN Silicon planar TO46 . \$1
- 3 2N711 300MW. 300 MC, PNP MESA, TO18 . \$1
- 2-20 WATT NPN SILICON MESA 2N1648 . . . \$1

**750MA TOP HAT RECTIFIERS**

Full Leads  
**1000 PRV 3 for \$1**  
Factory Tested



- 4-20 WATERS, 2N1038/42, w/sink by Sylvania. \$1
- 3 SILICON NPN 'PLANAR' RHEEM 2N697, 100mc \$1
- 3 40-WATT TRANSISTORS PNP, stud, b80HVolts \$1
- 25 GERMANIUM & SILICON DIODES, no test . \$1
- 4 2N213 TRANSISTORS, mixer-conv, TO22 . . . \$1
- 30 PRINTED CIRCUIT SWITCHING TRANSISTORS, \$1
- 3 2N706 500MW, 300MC NPN PLANAR, TO46 . \$1
- 6 FAMOUS CK722 TRANSISTORS, aluminum. \$1
- 5 2N107 TRANS'TRS, by GE, pnp, pop, audio pak \$1
- 10 PNP SWITCHING TRANSISTORS, osc-ifs-driver, \$1
- 10 NPN SWITCHING TRANSISTORS 2N440 equals \$1
- 15 PNP TRANSISTORS. CK722, 2N35, 107 no test \$1
- 15 NPN TRANSISTORS. 2N35, 170, 440, no test \$1

100's SOLD AT 4:05

**TRANSISTORS**

**100 for 2<sup>98</sup>**

POWER, RF, IF, AUDIO, SWITCHING no test

**SPECIAL SALE**

**500 MC Silicon Planar TRANSISTOR \$1.49**

(ACTUAL SIZE)

Fairchild

Watts	V	hFE	ma
3	25	35-140	1100

Space Saver, 3 Amp Switching

**POWER TRANSISTORS**

2N1755 3 for \$1  
2N1760 20 WATTS

**10¢ FOR OUR "SPRING" BARGAIN CATALOG ON:**

Semiconductors     Poly Paks     Parts

**POLY PAKS**

TERMS: send check, money order, include postage—avg. wt. per pak 1 lb. Rated, net 30 days. CODs 25% down.

P.O. BOX 942R  
SO. LYNNFIELD, MASS.

Circle 135 on reader's service card

# RADIO SHACK Citizens' Band Transceiver

# sale!

OVER 75 STORES  
COAST-TO-COAST

- ARIZONA**  
Phoenix: 3905 East Thomas Rd.
- CALIFORNIA**  
Anahelm: 507 East Karalla Ave.  
Bakersfield: 1308 19th St.  
La Habra: 1511 West Whittier Blvd.  
Long Beach: 3976 Atlantic Ave.  
Los Angeles:  
Downey: Stonewood Shop. Ctr.  
Ladera Shopping Center:  
5305 Centinela Ave.  
Mission Hills: 10919 Sepulveda Blvd.  
Redwood: 19389 Victory at Tampa  
Torrance: 22519 Hawthorne Blvd.  
West Covina: 2516 East Workman Ave.  
West L. A.: Pico Blvd. at Overland  
Oakland (San Leandro): Bay Fair Shop. Ctr.  
Sacramento: 600 Fulton Ave.  
San Diego (La Mesa): Grossmont Shop. Ctr.  
Santa Ana: Bristol Plaza Shop. Ctr.,  
1212 South Bristol
- COLORADO**  
Denver: 798 South Santa Fe
- CONNECTICUT**  
Hamden: Hamden Mall Shop. Ctr.  
Manchester: Manchester Shop. Parkade  
New Haven: 92 York St.  
New London: New London Shop. Ctr.  
Stamford: 29 High Ridge Rd.  
West Hartford: 39 So. Main St.
- ILLINOIS**  
Chicago: Evergreen Plaza at 95th St.
- MAINE**  
Portland: Pine Tree Shop. Ctr.
- MARYLAND**  
Langley Park: Hampshire-Langley Shop. Ctr.
- MASSACHUSETTS**  
Boston:  
167 Washington St.  
594 Washington St.  
110 Federal St.  
Braintree: South Shore Plaza  
Brookline: Westgate Mall  
Brookline: 730 Commonwealth Ave.  
Cambridge: Fresh Pond Shop. Ctr.  
Framingham: Shoppers' World  
Lowell: Central Shop. Plaza  
Saugus: N. E. Shop. Ctr.  
Springfield: 1182 Main St.  
West Springfield: Century Shop. Ctr.  
Worcester: Lincoln Plaza
- MINNESOTA**  
St. Paul: 473 North Snelling
- MISSOURI**  
St. Louis: 1125 Pine St. Walker Ashe Div.
- NEW HAMPSHIRE**  
Manchester: 1247 Elm St.
- NEW MEXICO**  
Albuquerque: 6315 Lomas, N. E.
- NEW YORK**  
Binghamton (Vestal): Vestal Shop. Plaza  
Buffalo (Clarence): TransTown Shop. Ctr.  
New York: 1128 Ave. of the Americas  
Schenectady (Rotterdam): Shoporama Ctr.  
Syracuse: 3057 Erie Blvd. East
- OHIO**  
Cincinnati: 852 Swifton Ctr.
- OKLAHOMA**  
Oklahoma City: Mayfair Shop. Ctr.  
Tulsa: 2730 South Harvard
- OREGON**  
Portland: 1928 N. E. 42nd St.
- PENNSYLVANIA**  
Philadelphia:  
2327 G. Cottman Ave., Roosevelt Mall  
1128 Walnut St.
- RHODE ISLAND**  
Cranston: 1301 Reservoir Ave.  
East Providence: Shoppers' Town
- TEXAS**  
Abilene: 2910 North First St.  
Arlington: Collins at Park Row  
Brownsville: 847 S. E. Elizabeth St.  
Dallas:  
1601 Main St.  
Medallion Center  
125 Wynwood Village  
Fort Worth:  
1515 So. University Dr.  
900 East Berry St.  
3524 East Denton Highway  
2615 West 7th St.
- Houston:**  
8458 Gulf Freeway  
322 Northline Mall  
Bellevue: 4759 Bissonnet  
San Antonio: 150 WandaLand Shop. Ctr.  
Sherman: 1620 Highway 75 North  
Waco: 1016 Austin Ave.
- VIRGINIA**  
Arlington: Washington-Lee Shop. Ctr.
- WASHINGTON**  
Seattle:  
2028 Third Ave.  
837 N. E. 110th St.

## LOWEST PRICE IN THE COUNTRY FOR A 3-WATT CB TRANSCEIVER

# 3995

2 FOR \$78.00

- Built-in Mike/Speaker
- Push-to-Talk Lever
- Range up to 8 Miles
- Send and Receive Ch. 5 Crystals Supplied
- Operates on 117 VAC


RADIO SHACK stuns the CB world with the most powerful and ONLY 3-watt transceiver on the market under \$60! Operates on 117 VAC. "Intercom-type" mike/speaker: depress lever to talk . . . or raise to talk continuously . . . release to listen. Arm's length communication with exceptionally clear modulation! Range up to 8 miles. No tangle of wires, no separate microphone, no batteries. Built-in 34" telescoping antenna, separate external antenna input; special low-power switch for optional "no license" power. Built-in squelch control! Both send and receive are crystal-controlled with plug-in Ch. 5 crystals supplied. Crystals for other channels only \$2.49 each. Handsome 8½" x 5½" x 5" beige molded case. If CB is for you, our price is irresistible! Mail order today or shop in person at your nearest Radio Shack. 21-1160. Ship. wt. 4 lbs.
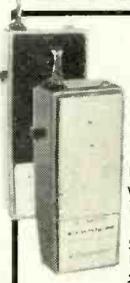
## RADIO SHACK'S BEST SELLING WALKIE TALKIES



Walkie-Talkie  
**3995** Each  
Singly

Dual-Channel. Use with SELECTaCOM. 100 mw. output. #21-904. Same as above with 12 trans., battery #21-906. \$49.95



6-Transistor  
Walkie Talkie  
**2195** Each  
Singly

Up to 1 Mile. Tunes with SELECTaCOM. 100 mw. output. #21-1139. Same with 9 trans. Up to 2 miles. #21-1001. \$29.95.



"Space Patrol"  
Walkie-Talkie  
**950** Each in  
Pairs

America's favorite wired hand radio. Ready to use; not a kit! Talk up to ¼ mile! #60-3030.



**795**

### AC/DC POWER SUPPLY CONVERTER

Operate any of the 100 mw. Walkie-Talkies above on 117 VAC house current. Conserve battery power. Sturdy tabletop stand for base station operation. 2x3½x4½". #21-1002.

### MAIL TO YOUR NEAREST RADIO SHACK STORE

Please send items I have checked at right.  
ADD 50¢ PER ORDER FOR PACKING AND SHIPPING

NAME (print) \_\_\_\_\_

STREET \_\_\_\_\_

CITY \_\_\_\_\_ STATE \_\_\_\_\_ ZIP \_\_\_\_\_


- 21-1160, SELECTaCOM
- 60-3030, Space Patrol
- 21-906, TRC-33
- 21-904, TRC-22
- 21-1139, TRC-1
- 21-1001, TRC-2
- 21-1002, Converter

RE-1265




Send me a  
FREE 1966  
Catalog.

Circle 136 on reader's service card

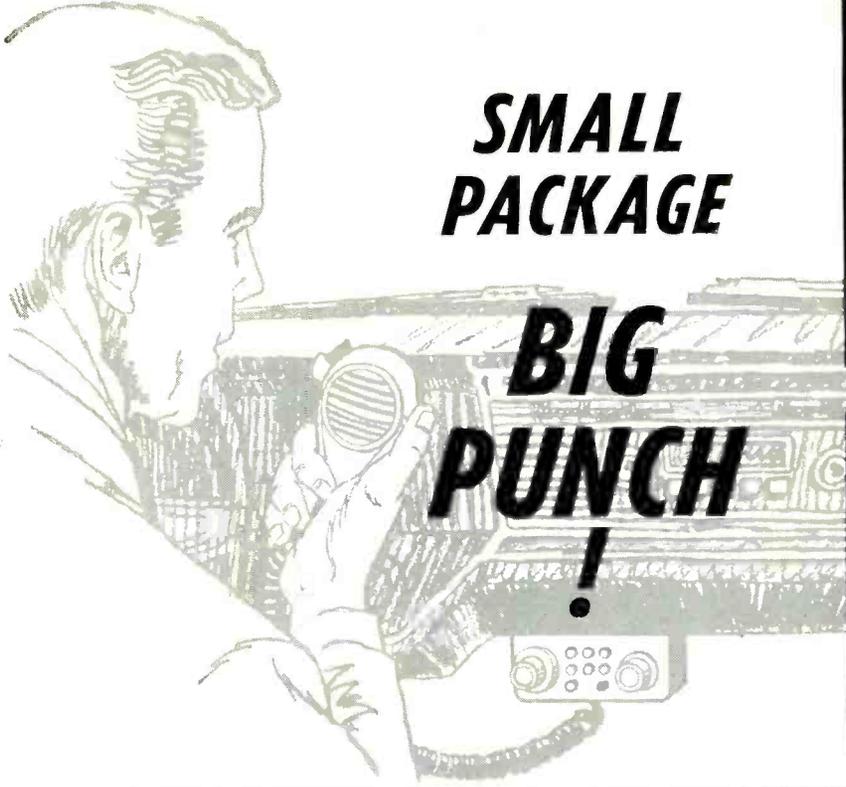

**SMALL  
PACKAGE**

**BIG  
PUNCH  
!**

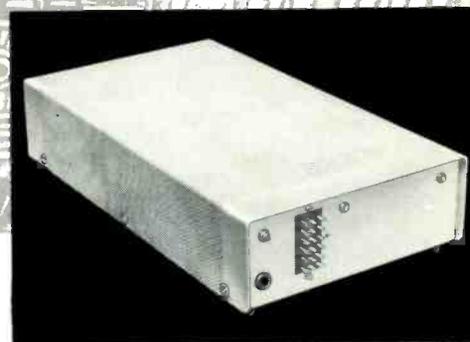

### INTERNATIONAL Model MO TRANSCEIVER For CITIZENS RADIO SERVICE

- New Compact Size
- New Solid-State Crystal Switching Circuit
- New Photo-Control Volume Circuit
- New Remote Control With Matching Microphone



The International Model MO Citizens Radio transceiver, custom designed for mobile installation, provides instant push-to-talk crystal controlled operation on any 6 channels with full 5 watts power input. The new compact control head provides complete remote controlled operation. All circuits are dc using solid-state crystal switching. The operating channel is indicated by an illuminated button on the control head. Tubes and silicon transistors are combined to provide a rugged trouble-free circuit.

The complete transceiver includes: a remote control head (about the size of a cigarette package), matching white microphone, new compact transmitting/receiving unit which may be conveniently installed in the trunk, and a matching white speaker which mounts under the dash. Operates from 12 vdc negative ground power source. Other power input units are available on special order.

*See the "all new" International Model MO at your dealer today.*

FCC Citizens Radio license required. All use must conform with Part 95, FCC Rules and Regulations.



**INTERNATIONAL**

**CRYSTAL MFG. CO., INC.**

18 NO. LEE · OKLA. CITY, OKLA. 73102


Circle 149 on reader's service card

# RCA rare-earth

## Hi-Lite
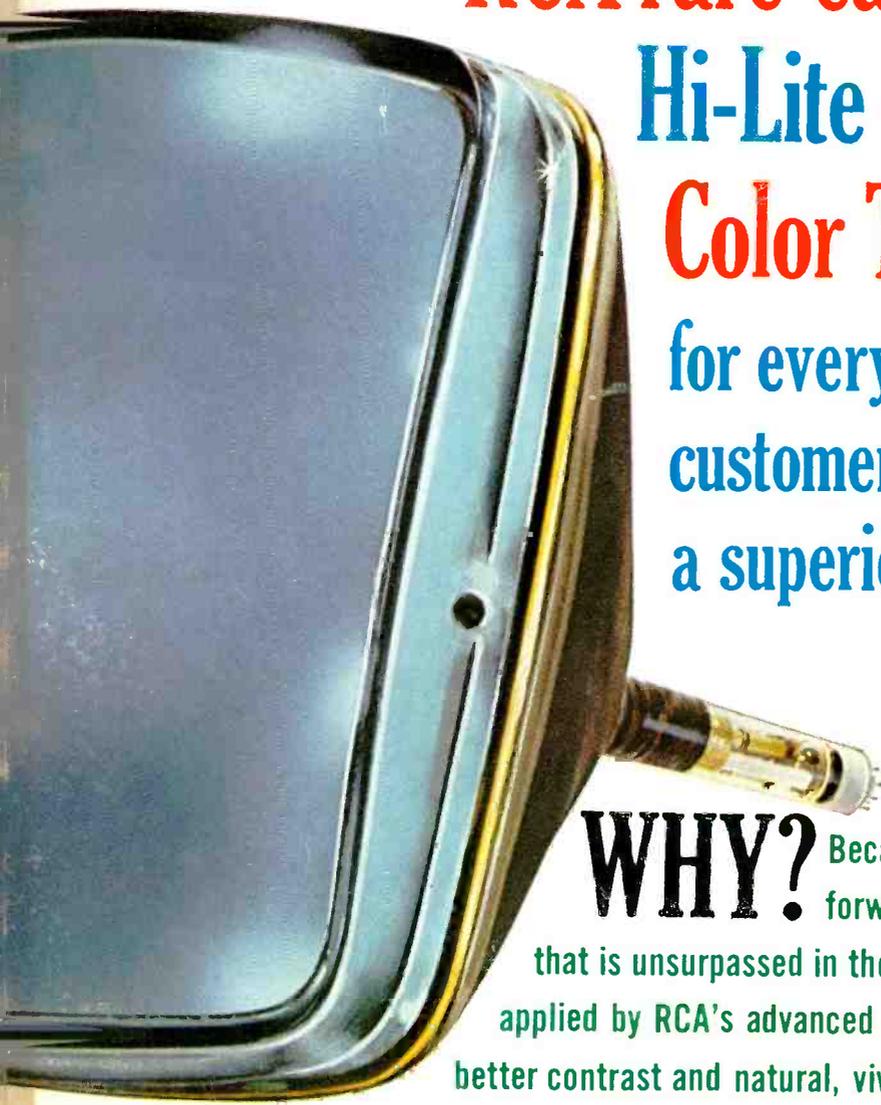
# Color TV Picture Tubes

for every smart  
customer who wants  
a superior color picture



## WHY?

Because RCA's Hi-Lite line represents a big step forward in color picture brightness—brightness that is unsurpassed in the color TV industry. Rare-earth phosphors applied by RCA's advanced screening methods create brighter reds, better contrast and natural, vivid colors . . . Everything the smart customer wants. Are you ready to service your smart customers? Keep posted. See your RCA Distributor today.

RCA ELECTRONIC COMPONENTS AND DEVICES, HARRISON, N.J.



The Most Trusted Name in Electronics

