

CB REPORT—CIRCUITS TO BUILD—HI-FI TESTS

\$1.00 ■ NOV. 1976

Radio-Electronics

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS

rare and unusual
CB ACCESSORIES
dress up your rig

build for your car
ANTI-THEFT
circuits using IC's



expand dynamic range
CASSETTE TAPE
for higher fi

easy to build
DIGITAL IC CLOCK
with automatic brightness

make your calculator a
TELEPHONE DIALER
with a few IC's

PLUS

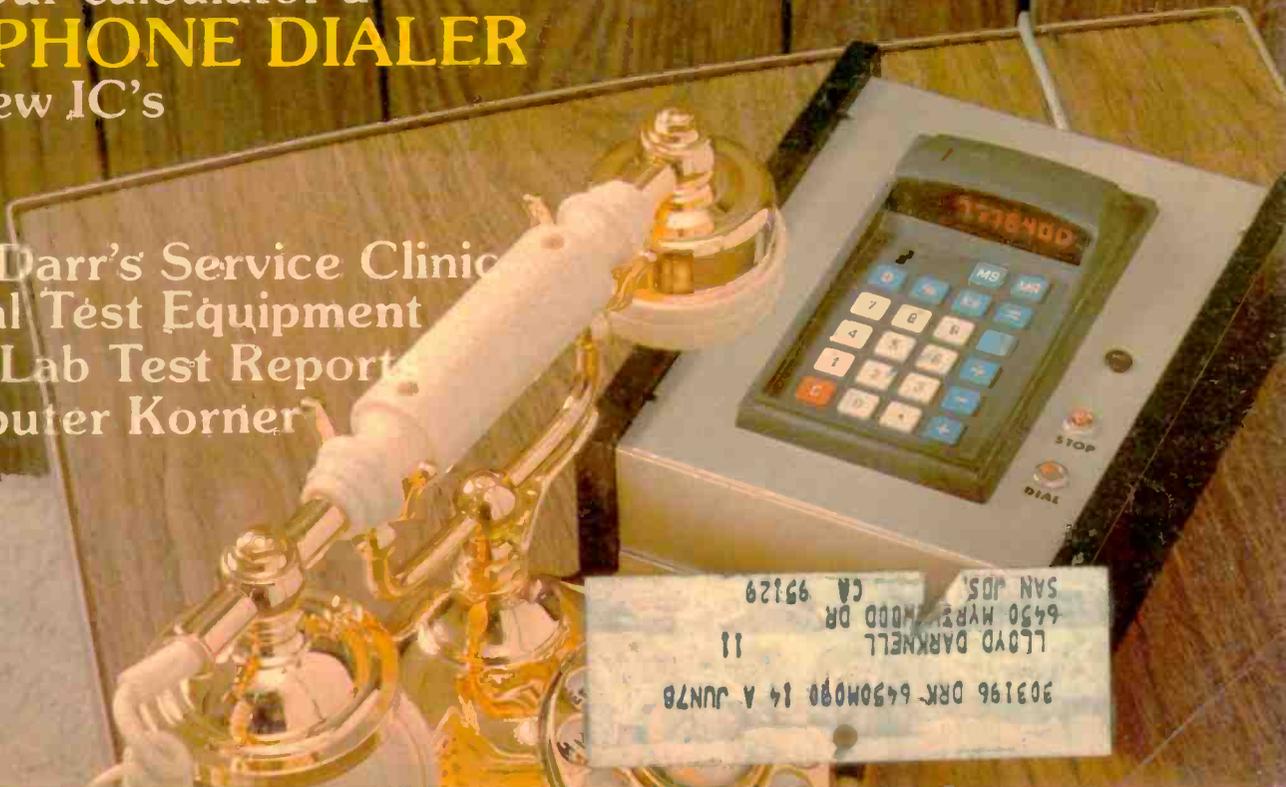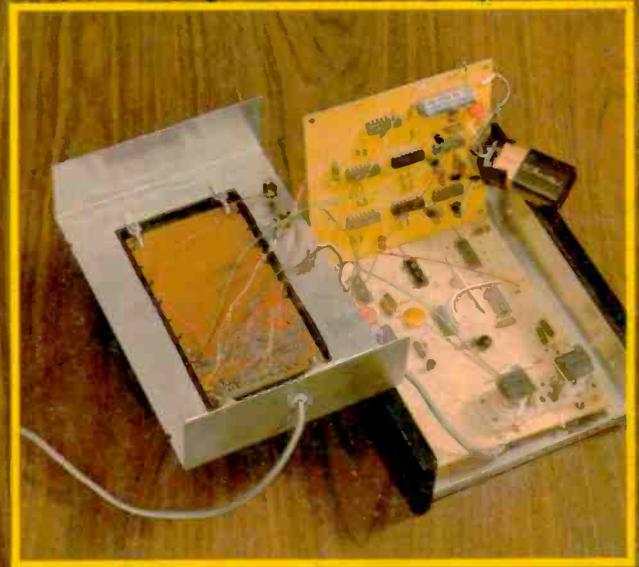- ★ Jack Darr's Service Clinic
- ★ Digital Test Equipment
- ★ Hi-Fi Lab Test Reports
- ★ Komputer Korner



GERNSBACK
PUBLICATION

303196 DRK-6490898 14 A JUN78
 11
 LLOYD DANKNELL
 6450 WAREWOOD DR
 SAN JOSE, CA 95128

The Big Stick[®] Antenna.

High, wide- ranging and handsome.

ENGINEERED
FOR
PRESENT
23 CHANNELS
AND ADDITIONAL
17 CHANNELS
AUTHORIZED
FOR USE
AFTER 1-1-77

This half-wave, omni-directional fiberglass beauty punches out the big signal from 60 feet up to outperform all other base station antennas.

The Big Stick Antenna illuminates 12 times more capture area at 60 feet, sending the energy towards the horizon in a unique low angle radiation pattern.

Distributed dielectric loading, achieved by Shakespeare's exclusive fiberglass construction, enables the Big Stick to outrange taller, heavier metal antennas under all conditions.

Move up to the Big Stick. Pretuned. No ground radials. Works anywhere with any length cable. Also available in a lower cost model, Big Stick II. Shakespeare Antenna Group, P. O. Box 246, Columbia, South Carolina 29202.

Style 176

Shakespeare

THE ROYAL LINE OF FIBERGLASS ANTENNA

In Canada/Len Finkler, Ltd.,
25 Toro Road, Downsview, Ontario
CIRCLE 84 ON FREE INFORMATION CARD

altair^{T.M.}

Number One in low-cost computing.

Altair, from MITS, is the number one name in microcomputers for home, business, personal and industrial applications. Because the Altair was first, it has set the standard in the industry. More Altair 8800's are now operational than all other microcomputers combined.

Whether you buy a \$395 complete computer kit* or a multi-disk system for under \$10,000; MITS will provide you with thorough and lasting support. Satisfied Altair users include schools, corporations, small businesses, students, engineers, and hobbyists.

Altair hardware includes three microcomputers; the Altair 8800a, 8800b, and 680b. MITS has a complete selection of Altair plug-compatible memory and interface options, including the new Altair 16K Static board and Altair multi-port serial and parallel I/O boards. Also available is a complete line of Altair peripherals including line printers, CRT's, and multiple disk systems.

Altair software is by far the most complete and best for any microcomputer. Our Extended BASIC and Disk BASIC have received industry wide acclaim for programming power and efficiency. Application packages are available at many Altair Computer Centers:**

The Altair computer is a revolution in low cost computing. Shouldn't you write for more information including our free, color catalogue.

*The Altair 680b turnkey model.

**Retail Altair computer outlets now opened in many large cities.



mits

MITS, Inc. 2450 Alamo S.E. / Albuquerque, New Mexico 87106

Announcing an . . .

Exclusive New Broadband MATV Amplifier

with Automatic Overload Control



Model 3662

Just set it... and forget it.

- Automatic control for input variations of up to 20 dB
- Eliminates nuisance service calls
- 45 dB Gain, VHF High Band
- +52 dBmV Output Capability
- Separate Lo and Hi VHF band controls
- Operates at full output rating
- Switch selectable AOC or MAN operation
- Lightning protected
- Universal rack or surface mounting bracket
- UL listed

Jerrold Model 3662 is the only broadband MATV amplifier with output signal levels automatically controlled. This exclusive feature permits use of the full output capability of a broadband amplifier without fear of overload due to input signal fluctuations. AOC operates to:

1. Prevent overloading the amplifier when input levels increase.
2. Increase amplifier gain to compensate for signal fades.
3. Prevent system cross-modulation even if only one channel level increases or fades.

TRY THE 3662 FOR YOUR NEXT MATV INSTALLATION



JERROLD ELECTRONICS

GENERAL INSTRUMENT CORPORATION

Horsham, Pa. 19044 • (215) 674-4800

CIRCLE 52 ON FREE INFORMATION CARD

Radio-Electronics[®]

THE MAGAZINE FOR NEW IDEAS IN ELECTRONICS


Electronics publishers since 1908

NOVEMBER 1976 Vol. 47 No. 11


CB RADIO	40	Accessories For Your Rig A look at the little "extras" that make living with your CB a lot easier. by Robert F. Scott		
BUILD ONE OF THESE	48	Automatic Telephone Dialer Convert a calculator into a telephone dialer—it's not difficult. by Larry Wilson and Tim Funderbunk		
	56	Anti-Theft Alarm Circuits Thirteen circuits to help keep your car from being stolen. There are ignition immobilizers, fuel pump cutoffs, alarms and combinations of these devices. by R. M. Marston		
	67	Digital Alarm Clock Bright gas-discharge display; automatic variable display intensity, AM-PM indication. What else could you want? by Paul Emerald		
HI-FI SOUND AUDIO STEREO	76	Improved Noise Reduction for Cassette Tape Yes! It can be done. A look at the JVC Super-ANRS System. by Len Feldman		
	78	R-E Lab Test Report Crown IC-150A Preamp. by Len Feldman		
	81	R-E Lab Test Report AKG P8E Cartridge. by Len Feldman		
TEST EQUIPMENT	32	Equipment Report Helectronix L-15 pulse-sweep frequency generator.		
	34	Equipment Report Non-Linear Systems frequency meter		
	45	Digital Test Equipment <i>Part I:</i> All about digital multimeters. by Charles Gilmore		
COMPUTERS	24	Komputer Korner <i>Part II:</i> 8080 instruction set. by Tim Barry		
	30	Equipment Report Jolt 4K RAM module		
GENERAL ELECTRONICS	4	Looking Ahead Tomorrow in electronics—Today. by David Lachenbruch		
	59	Making Sinewaves Digitally Six circuits for experimenters. Learn how you can generate perfect sinewaves from digital signals. by Don Lancaster		
TELEVISION	83	VIR & Better TV Pictures A special signal called "Vertical Interval Reference" makes for perfect color pictures even when you change channels. by Roger Kenfield		
	86	Service Clinic More bits and pieces. by Jack Darr		
	88	Reader Questions R-E's Service Editor solves reader problems		
DEPARTMENTS	106	Advertising Index	100	New Literature
	12	Advertising Sales Offices	94	New Products
	16	Letters	102	Next Month
	105	Market Center	107	Reader Service Card
	6	New & Timely		

ON THE COVER

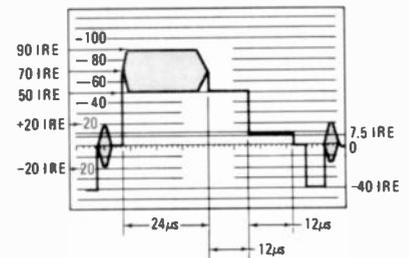It only looks like a calculator, but it's more. . . . It's an automatic telephone dialer. Punch in the number you want; then push the button. If the line is busy; hang up and punch the button again. Learn how to build your own. The story starts on page 48.



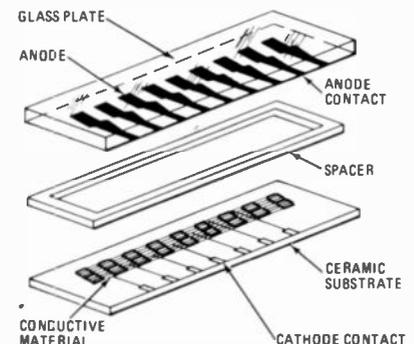THE VIR SIGNAL makes color TV pictures perfect. It's tucked away on line 19 between two horizontal sync pulses. See how it works on page 83.



THIS GAS-DISCHARGE DISPLAY is a part of a digital clock you'll want to build. For details turn to page 67.

Radio-Electronics, Published monthly by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Phone: 212-777-6400. Second-class postage paid at New York, NY and additional mailing offices. One-year subscription rate: U.S.A., U.S. possessions and Canada, \$8.75. Pan-American countries, \$10.25. Other countries, \$10.75. Single copies \$1.00. © 1976 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

Subscription Service: Mail all subscription orders, changes, correspondence and Postmaster Notices of undelivered copies (Form 3579) to Radio-Electronics Subscription Service, Box 2520, Boulder, CO 80302.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

looking ahead

TVI problem

The FCC says it's receiving complaints about RF interference at the rate of some 100,000 a year, and that 87% of these are attributable to CB. By far the majority involve interference to TV sets. In the FCC's channel-expansion decision, it specified that CB equipment must have harmonic suppression of 60 dB—far lower than the limit proposed by broadcasters and television set manufacturers. The Commission also said that any CB operator causing harmonic interference to TV Channels 2, 5 or 6 would be required to install a low-pass filter.

But CB can also cause interference across the entire TV band. A very small amount of this is the result of illegal CB equipment, such as linear amplifiers. But FCC officials say the vast majority of interference cases are the result of inadequate filtering and shielding of the TV receiver. Most TV set manufacturers have always followed a policy of providing a filter free of charge at the request of the set owner—but until the CB boom they haven't had many requests. Even now, the TV set owner is likely to blame the CB operator for interference, rather than his own set.

Why not include filters as standard equipment in all television sets? The set manufacturers say this would push prices up and force TV buyers to pay for filters whether they need them or not. But the rapid growth of CB and other devices that emit RF radiation may force a change. The FCC currently has no power to make television manufacturers include filters in all of their production, although there have been several bills introduced in Congress to give it that authority.

More 1977 TV's

The last of the 1977-model TV sets have now been intro-

duced by Zenith. As expected, they included some 19-inch sets with Zenith's all-new color tube designed for precision automatic manufacture, using a new glass design, a new tri-potential gun, 100-degree deflection and a new shadow-mask (*Radio-Electronics*, June 1976). In addition, Zenith introduced a new series of slim 17-inch color sets using conventional-type tubes but with 100-degree deflection, as opposed to the standard 90 degrees.

All of Zenith's 25-inch sets and its newly-introduced 19-inch sets feature a new automatic color adjustment system, Zenith's answer to RCA's ColorTrak, Sylvania's GT-Matic and G-E's VIR. Zenith's Color Sentry combines five automatic circuits; a light sensor that adjusts color and contrast to room lighting, a color signal monitor that prevents oversaturation, a tint stabilizer to correct flesh tones, a contrast regulator that eliminates separate contrast control and keeps contrast, brightness and color at a constant ratio, and a color-level lock that balances color and tint.

Video game boom

At least 32 video-game attachments made by 22 different manufacturers have received FCC approval as we went to press. The simple tennis-type games are now beginning to yield to far more sophisticated home variations of coin-operated arcade games, involving races, battles, space travel and so forth with programmable microprocessor games on the verge of commercial introduction. Many major electronics names are getting into the video game business, which was pioneered by Magnavox. RCA plans a microprocessor game, as does Fairchild. National Semiconductor is already in the business, as is Radio Shack. Channel Master is also preparing an entry. Of course, prices of simple video games are rapidly dropping, the lowest mentioned so far being a

two-player black-and-white tennis game entered in the toy market at \$39.95 by First Dimension.

40 CB channels

The FCC's expansion of the Citizens band from the current 23 to 40 channels was, in effect, a compromise. The demands for more channels were almost overwhelming. At one time, the Commission had considered going to as many as 58 channels, but the potential for intermodulation interference and the fact that the remote-control hobbyist frequencies (Class C) would be wiped out if FCC went above 40 channels dictated the final choice.

Even these expanded frequencies in the 27-MHz band (26.965-27.405 MHz) are considered temporary, and the Commission stressed it was seeking a permanent home for personal communications "upstairs"—perhaps the 220- or 900-MHz range. But this is still fairly far in the future.

New transceivers operating on the full 40-channel band will be available starting January 1, 1977. The FCC decision prohibits the use of converters to extend 23-channel transceivers to 40, but it will permit the "remanufacture" of 23-channel sets to 40-channel specifications so long as they meet the Commission's type-acceptance requirements.

The FCC has also tightened specifications for type-acceptance of new CB units in an attempt to minimize interference with TV and other services—although it seems likely that TVI will increase with the enlargement of the band. The 23-channel units are capable of causing harmonic interference to TV Channels 2 and 5; with the extension of the band, Channel 6 will also be affected.

The Commission and CB equipment manufacturers stress that 23-channel transceivers will in no way be obsolete. The major special-purpose channels—highway Channel-19 and emergency

Channel-9—are located within the original 23-channel band. And it's certainly a good bet that from now through the end of the year there'll be some great bargains in 23-channel units in preparation for the start of marketing of the new, more costly, extended-band transceivers.

Home VTR chaos


The videocassette recorder is now well launched as a consumer product, with Sony making and selling about 10,000 a month, 2,500 of these in the United States. As reported here, two other incompatible systems are on the market in Japan (all home units so far use half-inch tape)—Matsushita's Home Video, to be sold here by Quasar and Sanyo's V-Cord II, to be sold here under the Sanyo name.

A fourth—and also incompatible—system has been developed in Japan by Japan Victor (JVC). At presstime, it had not been demonstrated, but it is said to be an extremely compact machine with two hours recording or playing time for a cartridge of half-inch tape. Some observers feel the JVC machine will be the subject of an all-out attempt to "standardize" by winning over uncommitted (or even some already committed) Japanese manufacturers.

Meanwhile, Betamax continues to roll, with a production schedule of 200,000 set for 1977 and a two-hour cassette said to be in the works (current playing time is only 60 minutes). And in the U.S., Sony and Paramount Pictures have formed a joint venture to explore distribution of pre-recorded tapes as well as recorders. Thus Betamax is now being put forward as a competitor to the video disc systems that are tentatively scheduled for introduction in late 1977 by Magnavox and RCA.

DAVID LACHENBRUCH
CONTRIBUTING EDITOR

Tuner Service Corporation

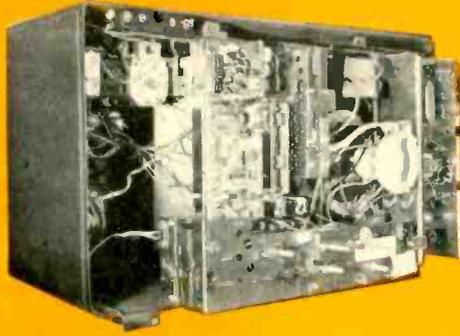

STILL ONLY
\$995
U.S.A. ONLY

Major Parts and Shipping Charged at Cost

One Year Guarantee

MODULE REPAIRS



TSC has been repairing private brand TV modules for over 2 years.

Expanded facilities now include modules for

- RCA
- GE
- ZENITH
- W. T. GRANT
- J. C. PENNEY
- WESTERN AUTO
- GAMBLES

as well as Zenith IF subchassis.

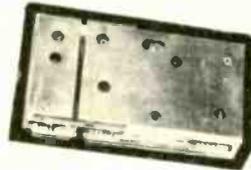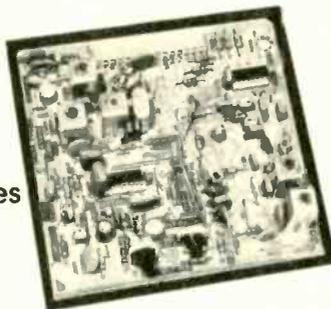For free Price List and complete information write or phone; TSC HEADQUARTERS, BLOOMINGTON, IND. or any of the TSC locations listed below.



PROVIDES YOU WITH A COMPLETE SERVICE FOR ALL YOUR TELEVISION TUNER REQUIREMENTS.

REPAIR

VHF OR UHF ANY TYPE (U.S.A. ONLY) \$ 9.95
UHF/VHF COMBINATION (U.S.A. ONLY) \$15.00

MAJOR PARTS AND SHIPPING CHARGED AT COST.

- Fast, efficient service at our conveniently located Service Centers.
- All tuners are ultrasonically cleaned, repaired, realigned, and air tested.

REPLACE

UNIVERSAL REPLACEMENT TUNER \$12.95 (U.S.A. ONLY)

- This price buys you a complete new tuner built specifically by Sarkes Tarzian Inc. for this purpose.
- All shafts have a maximum length of 10½" which can be cut to 1½".
- Specify heater type parallel and series 450 mA. or 600 mA.

CUSTOMIZE

- Customized tuners are available at a cost of only \$15.95. With trade-in \$13.95. (U.S.A. ONLY)
- Send in your original tuner for comparison purposes to any of the Centers listed below.

SAME DAY SERVICE — ONLY ORIGINAL FACTORY PARTS USED



HEADQUARTERS	BLOOMINGTON, INDIANA 47401	537 South Walnut Street	Tel. 812/834-0411
ARIZONA	TUCSON, ARIZONA 85713	1528 South 6th Avenue	Tel. 602/791-9243
CALIFORNIA	NORTH HOLLYWOOD, CALIF. 91601	10654 Magnolia Boulevard	Tel. 213/769-2720
	SAN MATEO, CALIF. 94402	600 S. Amphlett Boulevard	Tel. 415/348-3292
MODERNO, CALIF. 95351	123 Phoenix Avenue		Tel. 209/527-8051
	TAMPA, FLORIDA 33606	1505 Cypress Street	Tel. 813/253-0324
FLORIDA	FT. LAUDERDALE, FLORIDA 33318	104 S.W. 23rd Street, Bay 10	Tel. 305/524-0914
GEORGIA	ATLANTA, GEORGIA 30310	848 Evans Street S.W.	Tel. 404/758-2232
ILLINOIS	CHAMPAIGN, ILLINOIS 61820	405 East University Street	Tel. 217/356-6400
	DOLTON, ILLINOIS 60419	1507-09 East 142nd Street	Tel. 312/841-4444
INDIANA	SKOKIE, ILLINOIS 60076	5110 West Brown Street	Tel. 312/675-0230
	INDIANA POLIS, INDIANA 46204	112 West St. Clair Street	Tel. 317/632-3493
KENTUCKY	LOUISVILLE, KENTUCKY 40205	2244 Taylorsville Road	Tel. 502/452-1191
LOUISIANA	SHREVEPORT, LOUISIANA 71104	3025 Highland Avenue	Tel. 318/221-3027
MARYLAND	BALTIMORE, MARYLAND 21215	5505 Reisterstown Road, Box 2624	Tel. 301/358-1186
MASSACHUSETTS	SPRINGFIELD, MASSACHUSETTS 01108	405 Dickinson Street	Tel. 413/788-8206
MISSOURI	ST. LOUIS, MISSOURI 63132	9577 Page Avenue	Tel. 314/429-0633
NEVADA	LAS VEGAS, NEVADA 89102	1412 Western Avenue	Tel. 702/384-4235
NEW JERSEY	TRENTON, NEW JERSEY 08638	1139 Pennsylvania Avenue	Tel. 609/393-0999
NEW YORK	JERSEY CITY, NEW JERSEY 07307	547-49 Tonnole Avenue, Hwy 1 & 6	Tel. 201/792-3730
	ROCHESTER, NEW YORK 14615	37 Bullman Avenue	Tel. 716/647-9180
NORTH CAROLINA	GREENSBORO, NORTH CAROLINA 27405	2914 East Market	Tel. 919/273-6276
OHIO	CINCINNATI, OHIO 45216	7450 Vine Street	Tel. 513/821-5080
	CLEVELAND, OHIO 44109	4525 Pearl Road	Tel. 216/741-2314
OREGON	PORTLAND, OREGON 97210	1732 N.W. 25th Ave., P.O. Box 10141	Tel. 503/222-9059
PENNSYLVANIA	PITTSBURGH, PENNSYLVANIA 15200	515 Grant Avenue	Tel. 412/821-4004
TENNESSEE	MEMPHIS, TENNESSEE 38111	3158 Barron Avenue	Tel. 901/458-2355
TEXAS	DALLAS, TEXAS 75218	11540 Garland Road	Tel. 214/327-8413
VIRGINIA	NORFOLK, VIRGINIA 23513	3295 Santos Street	Tel. 804/855-2518
CANADA	ST. LAURENT, QUEBEC H4N-2L7	308 Decarie Boulevard	Tel. 514/748-8803
	CALGARY, ALBERTA T2H-1Y3	P.O. Box 5823, Stn. "A"	Tel. 403/243-0971

WATCH US GROW

If you want to branch out into the TV Tuner Repair Business write to the Bloomington Headquarters about a franchise.

new & timely

CB'ers see mixed prospects in future of Citizens band

The announcement that the Citizens band will go to 40 channels January 1 was unquestionably the good news that CB'ers have been awaiting for months. The first 23 channels extended from 26.965 to 27.255 MHz, with channels spaced 10-kHz apart except for a few gaps. The new channels begin with the addition of two channels at 27.235 MHz and 27.245 MHz (filling the gap between Channel 22 at 27.225 and Channel 23 at 27.255 MHz) and will continue 10 kHz apart—with only one gap—and end at 27.405 MHz for a total of 40 channels.

Not only will the new channels reduce interference, but the new 40-channel sets will be constructed to tighter standards and will not be as likely to create interference on other channels or to outside services.

The unhappy side of the picture is that many sets now in the field do not even measure up to present standards. Manufacturers, first rushing to supply sets for the CB explosion; later to get the 23-channel sets now in production off the lines to prepare for the 40-channel line, have tended to cut corners and relax quality control. The result has been sets with splatter that creates adjacent-channel interference and other weakness that cause interference to TV and other services. To add to the problems, FCC enforcement has actually been reduced instead of increased, due to the tremendous workload on the Commission because of the CB application jam during the rapid increase in CB use during the past year, and to the work on new standards and regulations for the 40-channel service.

A second cloud on the CB horizon is the coming sunspot peak. CB'ers who lived through the last sunspot peak remember (many with delight!) how signals took off into the wild blue yonder and permitted long-distance communications. They also remember that they were able to handle local traffic in spite of the occasional sporadic reception of stations hundreds of miles away, and are looking forward with little fear to a similar situation in 1979 or thereabouts.

Digital watches may have battery-life problems

The dealer who has been doing a good business in LED digital watches may be in for some surprises, thinks Henry Goldsmith, J.C. Penney merchandising manager. Many dealers, relying on their experience with older types of electronic watches, have sold the newer watches on the basis that the batteries will last a year.

The average life for a man's LED digital watch is six to nine months, says Mr. Goldsmith, and of a woman's watch three to six months. The customer, of course, will expect and demand free replacement of batteries that give out sooner, regardless of whether the watch cost \$20 or \$200.

The situation can create real trouble for the dealer, who will not only be expected to replace the batteries free of charge, but will also have the expense of the labor required for their replacement—often a job that requires time and occasionally special instruments.

There are two bright spots in the picture. Some dealers have been alert to the situation and have explained to the LED watch customer that battery life depends on how much use is made of it. And experience has shown that the second battery lasts longer than the first. Apparently, once the novelty has worn off, the user does not need to know the time so often!

Manufacturers team to create vehicle hi-fi stereo system

An automobile (or other vehicle) hi-fi system presented jointly by Nakamichi Research (USA) of Carle Place, NY, and Analog Digital Systems, Wilmington, MA, introduces a number of unique features in mobile stereo systems. The cooperative project is an effort to "upset the popularly held notion that true hi-fi is wasted in automobiles."

The cassette player is a Nakamichi model 250, with a frequency response of

± 3 dB from 85 to 20,000 Hz and a signal-to-noise ratio of 62 dB. It features selectable playback equalization, Dolby noise reduction circuitry and a built-in preamplifier with volume, balance and tone controls. Maximum output is 500 millivolts.

The model 250 feeds into a pair of ADS model 2002 loudspeakers. Secret of the 2002's effectiveness is in their amplifier system. Three power amplifiers are built into each system. Two of them are bridged to power the 4-inch miniature woofer; the third drives a 1-inch diameter soft dome tweeter. The 2002 measures 6.85 x 4.5 x 4.9 inches. Output is 40 watts. Price of the system is listed as \$696.

Television now 30 years old

In the Fall of 1946, as American industry turned from war to peace production, RCA introduced black-and-white television on a commercial basis. Through July of 1976, more than 76,000,000 color sets alone had been sold in this country. (Color came along in 1954.)

According to experts, the curves indicate that progress is just beginning. David E. Daley of RCA Consumer Electronics states that all indications are that nearly 40 million sets will be sold between now and 1980.

Among the factors responsible for this acceleration, Mr. Daley notes: the fact that more than half the nation's population is 30 years old or younger—people who think of television as a natural adjunct to

continued on page 12



THE HI-FI CAR STEREO SYSTEM combines the Nakamichi model 250 tape player and ADS model 2002 speaker system to make up a high fidelity system for cars, boats and similar vehicles. Rated at an undistorted acoustical output of 104 dB SPL, these units claim to be the world's smallest truly high-fidelity speakers.

SBE. The single best name for single sideband.

If you take the professional approach to CB you'll end up with SBE Single Sideband—be it mobile or be it base. SIDEBANDER II and CONSOLE II are two outstanding reasons why.

SIDEBANDER II is noted for having the biggest "talk power punch" in mobile CB. It reaches those 46 SSB channels crisply and clearly with a full power of 25 watts in. And because it's synthesized, it achieves more precise frequency and better stability. Exceptional features include: noise blanker, RF and AF gain controls, clarifier, and squelch.

CONSOLE II brings frequency synthesization to home base. It's a true no-nonsense professional with performance that gets your message through and brings in signals loud and clear. Superb features include "on the air" indicator, triple-function meter, automatic load and gain controls.

Two classic examples why SBE has the answers SSB users like.



SIDEBANDER II (SBE-12CB)
SSB/AM Mobile



CONSOLE II (SBE-16CB)
SSB/AM Base

SBE Better Communications through Creative Technology

For information write: SBE, Inc., 220 Airport Blvd. Watsonville, CA 95076

INTERNATIONAL OFFICES: E. S. Gould Marketing Co. Ltd., Quebec, Canada / Linear Systems, S.A. Geneva 1, Switzerland

CIRCLE 25 ON FREE INFORMATION CARD

new & timely continued from page 6

Radio-Electronics®

Hugo Gernsback (1884-1967) founder
M. Harvey Gernsback, KOD-6694
 editor-in-chief and publisher
Larry Steckler, KTX-3644, CET, editor
Robert F. Scott, CET, W2PWG,
 KXK-8533, technical editor
Arthur Kleiman, KTZ-3288, associate
 editor

Jack Darr, CET service editor
Leonard Feldman
 contributing high-fidelity editor
Karl Savon, semiconductor editor
David Lachenbruch, contributing editor
Rudolph F. Graf, contributing editor
George Whalen, contributing editor
Vincent P. Cicenia, production manager
Dale Allinson, production assistant
Harriet I. Matysko, circulation director
Sheila Werling, circulation assistant
Arline R. Bailey, advertising coordinator

Cover design by Louis G. Rubsamen
 Cover photo by Walter Herstatt

Radio Electronics is a member of the *Institute of High Fidelity* and is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.



Radio-Electronics magazine is published by Gernsback Publications, Inc., 200 Park Ave. S., New York, NY 10003 (212) 777-6400

President: M. Harvey Gernsback
 Vice President: Larry Steckler
 Treasurer: Carol A. Gernsback
 Secretary: Bertina Baer

ADVERTISING SALES

EAST

Stanley Levitan, KZA-5580, Sales Manager
 Radio-Electronics
 200 Park Ave. South
 New York, NY 10003
 (212) 777-6400

MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen, KXD-8396
 Jim Reilly
 The Ralph Bergen Co.
 6319 N. Central Ave.
 Chicago, IL 60646
 (312) 792-3646

PACIFIC COAST Mountain States

Jay Eisenberg, KYF-3277
 J.E. Publishers Representative Co.,
 8732 Sunset Blvd.,
 4th Floor,
 Los Angeles, CA 90069
 (213) 659-3810
 Sales Mart Building
 1485 Bayshore Blvd., Box 140
 San Francisco, CA 94124
 (415) 467-0125


SOUTHEAST

J.E. Publishers Representative Co.,
 214-387-2424

their lifestyles, the growth of cable TV and the new features being introduced into that facility, the growing demand for video games that connect to the antenna terminals, the video tape-recorder-player and the video disc player.

Quernemoen, Fablet and Piazza win Hugo Gernsback Award

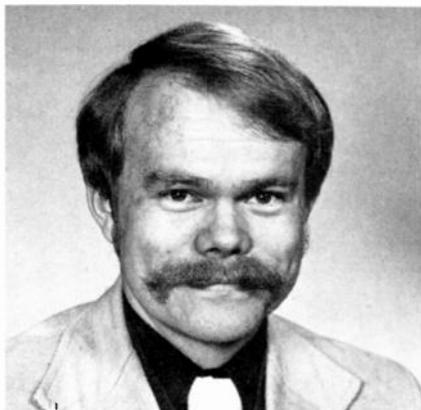Wayne Quernemoen of Alexandria, MN, is this month's winner of the Hugo Gernsback Memorial Award, a \$150 check presented annually to an outstanding student in each of eight leading electronics home study schools. Through the generosity of two test instrument manufacturers, students who place second and third in the contests held by the schools to determine the award winners also receive prizes.




WAYNE QUERNEMOEN

Wayne Quernemoen was and is a radio amateur. He had worked in a TV repair shop and at TV station KCMT—where he is now studio engineer, before enrolling with Grantham School of Engineering. Enrolled in the Electronics Engineering Technology course, he has completed the first four phases and is nearing completion of the fifth (engineering calculus, electrical networks and solid-state design). After completion and a seminar at the school, he will have earned the degree of Associate in Science in Electronics Engineering (ASEE).

Mr. Quernemoen intends to continue in his field of TV broadcast engineering, with possibly some attention to biomedical electronics, and to do some technical writing in those two fields. Eventually he hopes to continue his education to include an MSEE degree.

Runner-up Jose Luis Fablet, who receives a B&K Model 280 Digital Voltmeter, was born in Buenos Aires, Argentina, and now lives in Montevideo, Uruguay. He owns a factory making TV

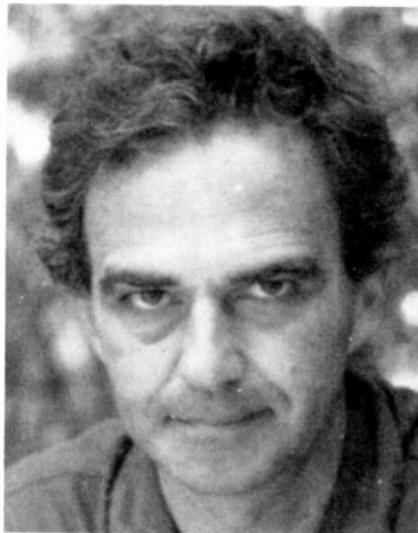tuners, handles TV repairs on all brands, and deals in TV replacement parts, having a staff of 20 employees in all. He is



JOSE LUIS FABLET

enrolled in the Electronics Engineering Course and, having completed three of its four phases, has received the degree of Associate in Electronics Engineering Technology (ASET). He expects to enroll in Part 4 to earn a higher degree.



NICHOLAS A. PIAZZA

Third-place Nicholas Piazza, Newport Beach, CA, is the winner of a VIZ WV-529A service VOM. He was introduced to electronics in the Navy, receiving 94 weeks of formal training. He is at present assigned to the Defense Communications Support Detachment at Marine Corps Air Station, El Toro, CA. Like Mr. Fablet, he has completed three phases of the Electronics Engineering course, receiving the ASET degree on May 6, 1975. He is now continuing in the course to earn an ASEE degree.

Mura, now we hear you above all the others; better than ever before. Your voice sounds amazingly crisp and clear. Without garble and without audio breakup. We copy your beautiful voice coming through the revolutionary new Model PRX-100 technologically advanced PRM[™] microphone, designed to carry your voice further than the others.

Here is what the PRM offers: Unlike other power microphones which just amplify your voice, PRM (peak redistribution modulation) tailors your voice signal to give the highest

average modulation without clipping and over-modulation. PRM circuitry, patented* and exclusive to Mura, reshapes unsymmetric voice peaks to assure high modulation density without peak overload.

For full information on the exciting PRM[™] line of microphones and other outstanding Mura products, visit your nearest CB outlet today. Ask him for Mura — to be sure that you are getting the finest accessories available. Or write to us directly.

*U.S. Patent No. 3,060,389 and Foreign Patents

Mura, we read you. Loud and clear.



M MURA
CORPORATION
177 Cantiague Rock Road,
Westbury, N.Y. 11590

CIRCLE 78 ON FREE INFORMATION CARD

Imagine a microcomputer

Imagine a microcomputer with all the design savvy, ruggedness, and sophistication of the best minicomputers.

Imagine a microcomputer supported by dozens of interface, memory, and processor option boards. One that can be interfaced to an indefinite number of peripheral devices including dual floppy discs, CRT's, line printers, cassette recorders, video displays, paper tape readers, teleprinters, plotters, and custom devices.

Imagine a microcomputer supported by extensive software including Extended BASIC, Disk BASIC, DOS and a complete library of business, developmental, and industrial programs.

Imagine a microcomputer that will do everything a mini will do, only at a fraction of the cost.

You are imagining the Altair™ 8800b. The Altair 8800b is here today, and it may very well be the mainframe of the 70's.

The Altair 8800b is a second generation design of the most popular microcomputer in the field, the Altair 8800. Built around the 8800A microprocessor, the Altair 8800b is an open ended machine that is compatible with all Altair 8800 hardware and software. It can be configured to match most any system need.


MITS' plug-in compatible boards for the Altair 8800b now include: 4K static memory, 4K dynamic memory, 16K static memory, multi-port serial interface, multi-port parallel interface, audio cassette record interface, vectored interrupt, real time clock, PROM board, multiplexer, A/D converter, extender card, disc controller, and line printer interface.


MITS' peripherals for the Altair 8800b include the Altair Floppy Disc, Altair Line Printer, teletypewriters, and the soon-to-be-announced Altair CRT terminal.

Introductory prices for the Altair 8800b are \$840 for a kit with complete assembly instructions, and \$1100 for an assembled unit. Complete documentation, membership into the Altair Users Club, subscription to "Computer Notes," access to the Altair Software Library, and a copy of Charles J. Sippl's Microcomputer Dictionary are included. BankAmericard or Master Charge accepted for mail order sales. Include \$8 for postage and handling.

Shouldn't you know more about the Altair 8800b? Send for our free Altair Information Package, or contact one of our many retail Altair Computer Centers.

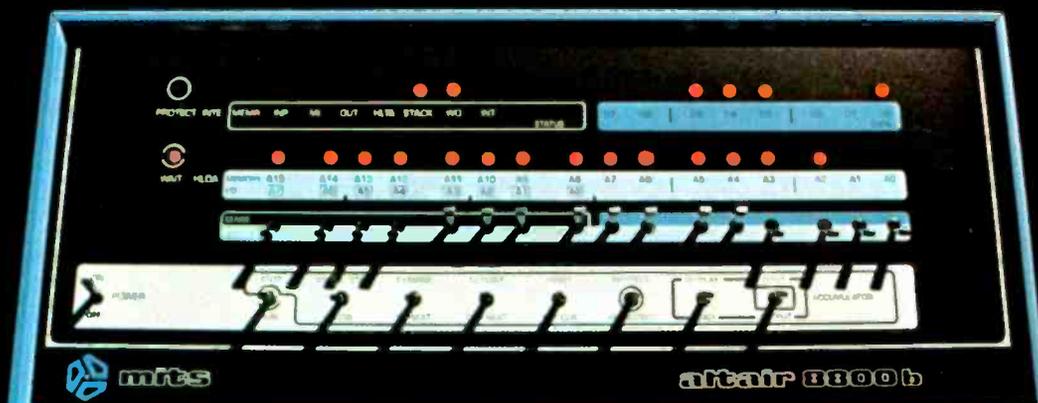mits 2450 ALAMO S.E. ALBUQUERQUE, NEW MEXICO 87106 (505) 243-7821



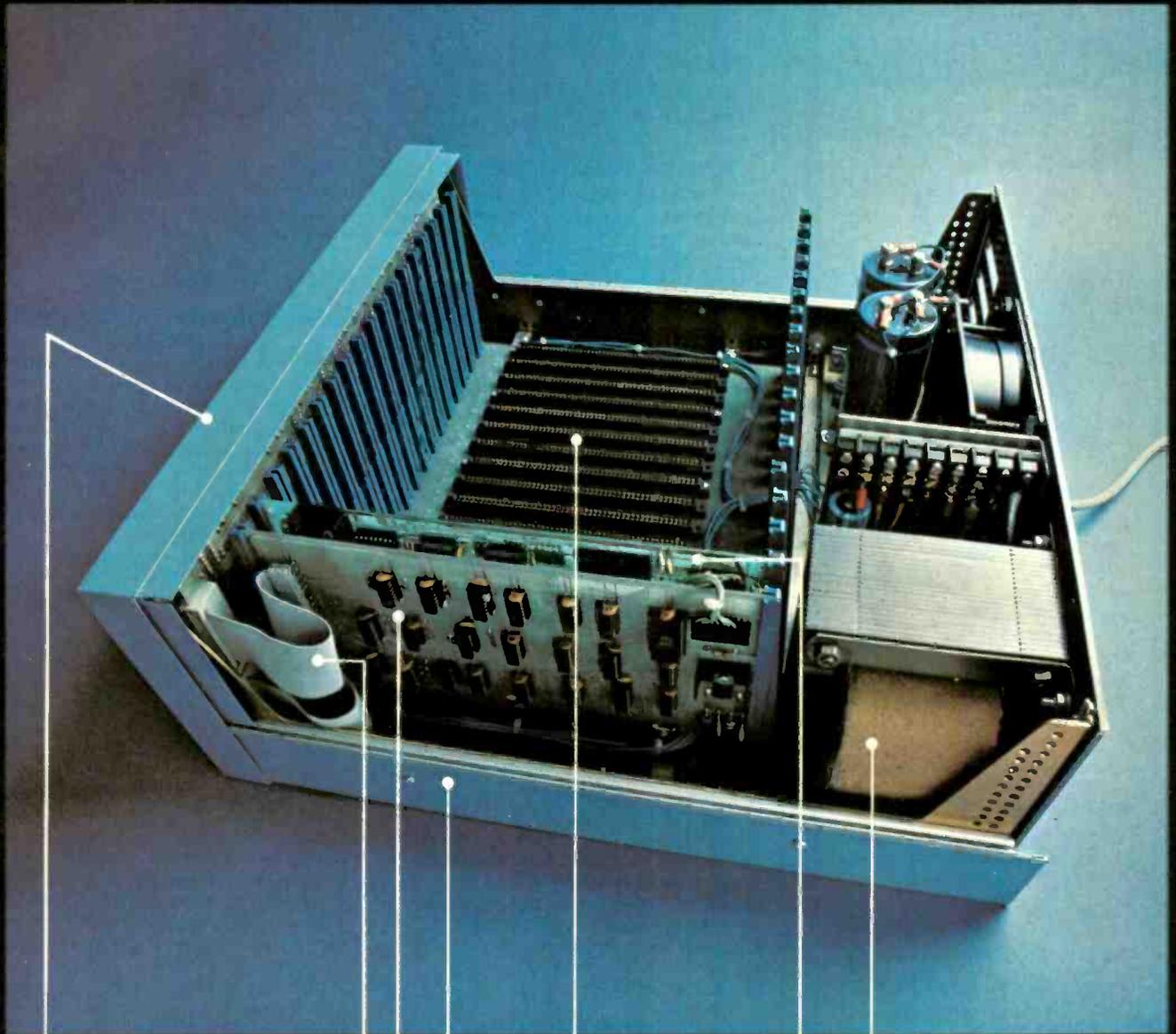

Redesigned front panel. Totally synchronous logic design. Same switch and LED arrangement as original Altair 8800. New back-lit Duralith (laminated plastic and mylar, bonded to aluminum) dress panel with multi-color graphics. New longer, flat toggle switches. Five new functions stored on front panel PROM including: DISPLAY ACCUMULATOR (displays contents of accumulator), LOAD ACCUMULATOR (loads contents of the 8 data switches (A7-A0) into accumulator), OUTPUT ACCUMULATOR (Outputs contents of accumulator to I/O device addressed by the upper 8 address switches), INPUT ACCUMULATOR (inputs to the accumulator from the I/O device), and SLOW (causes program execution at a rate of about 5 cycles per second - for program debugging).

Full 18 slot motherboard.

Rugged, commercial grade Optima cabinet.

New front panel interface board buffers all lines to and from 8800t bus.

Two, 34 conductor ribbon cable assemblies. Connects front panel board to front panel interface board. Eliminates need for complicated front panel bus wiring.

New, heavy duty power supply: +8 volts at 13 amps, +18 volts at 2 amps, -18 volts at 2 amps. 110 volt or 220 volt operation (50/60 Hz). Primary tapped for either high or low line operation.

New CPU board with 8080A microprocessor and Intel 8224 clock generator and 8216 bus drivers. Clock pulse widths and phasing as well as frequency are crystal controlled. Compatible with all current Altair 8800 software and hardware.

altair 8800-b



2450 Alamo SE/Albuquerque, NM 87106/505-243-7821

Prices, delivery and specifications subject to change.

NOTE: Altair is a trademark of MITS, Inc.

CIRCLE 70 ON FREE INFORMATION CARD

how often
could you use
an Xcelite®
"99"?



it's every
tool you
need 99%
of the time...
an Xcelite original!

it's a screwdriver



...for slotted, Phillips, Frearson, Bristol, clutch head, Scrulox® screws; in inch and metric size Allen hex and Allen hex ballpoint socket types; and Pozidriv® style.

it's a nutdriver

...in inch and metric sizes, regular, stubby, and magnetic, for hex nuts, screws, and bolts.



it's a reamer



it's extendable



...for greater reach and torque.

5 DIFFERENT HANDLE STYLES

...regular and Tee, with and without reversible ratchet; junior, and stubby; all with Xcelite's unique spring device for quick blade insertion and removal. All shockproof, breakproof (UL).

85 INTERCHANGEABLE BLADES

...all the popular types and sizes. All precision-made, genuine Xcelite quality. Fit all five handles.

IN SETS, KITS,
OR PIECEMEAL

...roll-up service kits, compact, stand-up, plastic-cased sets; or individually as needed.



in stock at leading
electronic distributors... nationwide

Weller-Xcelite
Electronics Division



The Cooper Group

P. O. BOX 728,
APEX, NORTH CAROLINA 27502

CIRCLE 22 ON FREE INFORMATION CARD

letters

MCS6501 MICROPROCESSOR

In the June, 1976 issue of *Radio-Electronics* there are two mistakes in the *State-of-Solid-State* article. These mistakes concern the MCS6501.

MOS Technology's announcement of April, 1976 states they have "agreed to withdraw the MCS6501 from the marketplace . . ." This microprocessor IC was introduced about September, 1975, as was a second chip, the MCS6502.

The MCS6501 IC did not have an on-the-chip clock. It required an input from an external two-phase clock. The MCS6502, which is still produced by MOS Technology, is similar to the MCS6501 except that it does have an on-the-chip clock.

WILLIAM J. HARTWEG
Staten Island, NY

SR-52 CALCULATOR MEMORY

There is a rebuttal to a previous letter I had written concerning the availability of memory registers on Texas Instruments calculators printed in the September issue of *Radio-Electronics*.

Mr. Lemmon is absolutely correct in his statements concerning the SR-51. However, reader Lemmon infers that there are no extra memory registers available on other T.I. calculators. This is incorrect. The memory registers 98 and 99 are definitely accessible on the SR-52. Program registers 70 through 97 are addressable from the keyboard, as are the operational stack registers 60 through 69.

THOMAS S. COX
Greenville, SC

DYNA-MICRO

I am a third-year computer systems engineering student at Oregon Institute of Technology, with my major interest in microcomputers. I have been searching for a good basic microcomputer to use as the core of my system. The Dyna-Micro, as described in the May, June, and July issues of *Radio-Electronics*, fit my plans beautifully.

After modifying the logic diagrams to fit my requirements, I began wire-wrapping my system. When I checked out the keyboard logic diagram in preparation to wire-wrapping it, I noticed a mistake. The keyswitches are encoded by two 74148 8-to-3 line priority-encoder IC's. One handles the numeric values and the other handles the alphanumeric values. For these IC's to operate, a wire must be connected from pin 5 (ENABLE IN) to ground or a low signal.

I checked out the logic diagram and the foil patterns to see if these connections were included. The foil pattern is complete and ready to go. I imagine the connections on the logic diagram were overlooked in the process of printing the

article. Perhaps this letter can save others some trouble-shooting time if they decide to build the Dyna-Micro and employ wire-wrapping in the construction.

DARREL WRIGHT
Klamath Falls, OR

MICROCOMPUTER APPLICATIONS PROGRAMS

On page 14 of the June 1976 issue of *Radio-Electronics*, Jonathan Titus states: "The PDP-8, PDP-11 and NOVA families have thousands of applications programs that just aren't available for microcomputers."

The facts are:

1. The IM6100 microprocessor emulates the PDP-8.
2. The LSI-11 microprocessor emulates the PDP-11.
3. The mN601 microprocessor emulates the NOVA.

Virtually all of the existing applications programs for the above machines will run on the emulating microcomputers with no change whatever.

J. GORDON
Los Angeles, CA

The Intersil IM6100 is compatible with PDP-8 software. This is an exception. It is, however, difficult to use the system with subroutines in PROM or ROM. This is because of the method used in the PDP-8 to recover a return address when it is finished with a subroutine. Front-panel controls aren't easy to add to an IM6100. I'd rather buy a PDP-8.

The LSI-11 from Digital Equipment Corporation is compatible with the PDP-11 software at the source level. This means that the software must all be converted before you can transfer it. The LSI-11 is not compatible with PDP-11 peripherals without a converter unit, available at additional cost. If you're not an OEM, I'd suggest you buy a PDP-11 and forget the LSI-11 for now.

The Data General mN601 (Micro Nova) is supposed to be a nice machine. They can't deliver before December according to the Data General people at the National Computer Conference. You can't run software on a machine you don't have.

I stand by my statement, but I expect the situation to change in a couple of years.

JON TITUS

IT ISN'T! OR IS IT?

I read, with interest, the letter sent to you by Continental Specialties and Sharp Advertising. Their contention that their product is a direct replacement for the SK-10/IF-18 solderless interface socket included in the parts list for the Dyna Micro (*Radio-Electronics*, May 1976 is-

continued on page 22

Find semiconductors fast.



With the new, updated Mallory PTC Semiconductor Product Guide.

Instead of looking all over for replacement semiconductors, just open the guide.

There's new indexing and cataloging for fast, easy access to the electrical and physical parameters of each PTC product. Plus, a listing of thousands of semiconductors, each cross-referenced to Mallory PTCs.

It's the authoritative source-book and cross-reference for transistors, zener diodes, diodes, high-voltage rectifiers, color crystals, integrated circuits, field-effect transistors.

Now it's easier than ever to get Mallory performance and reliability in your semiconductor replacement parts.

See your Mallory distributor or give him a call, today.

MALLORY

MALLORY DISTRIBUTOR PRODUCTS COMPANY

a division of P. R. MALLORY & CO. INC.

Box 1284, Indianapolis, Indiana 46208; Telephone: 317-856-3731

Batteries • Capacitors • Controls • Security Products • DURATAPE® • Resistors • Semiconductors • SONALERT® • Switches • Fastening Devices

DURATAPE® and SONALERT® are registered trademarks of P. R. Mallory & Co. Inc.

CIRCLE 69 ON FREE INFORMATION CARD

The "giftbook" of is in the

and if you aren't already on our customer mailing list,

The Heathkit Christmas Catalog is off the press, and that's good news for gift-givers, kitbuilders and everyone else, too. It's brim-full of the latest electronic products in easy-to-build kit form. Everything from lamp dimmers to color TV's, nearly 400 great gift ideas. Gifts for homeowners, businessmen and people interested in electronics, sports, fishing,



electronics mail

now's the time to send for your copy

amateur radio—gifts for anyone you can think of. And giving a Heathkit product is the way to make someone really happy this Christmas. They're interesting and fun-to-build. They give pride and satisfaction along with great performance. So send the coupon today and get your FREE copy of the Heathkit "giftbook". It will help you have a happier holiday, too.



THE NEW HEATHKIT CHRISTMAS CATALOG

World's largest selection of easy-to-build electronic kits—stereo components, color TV, test equipment, Amateur Radio, digital clocks and weather instruments; marine, aircraft and auto accessories, nearly 400 kits in all. Plus special buys on CB radios and antennas, and many special sale and bonus offers just in time for the holidays. Send coupon for your copy today. It's



FREE

MAIL COUPON TODAY!

FREE

Send for your FREE "Heathkit Giftbook" today — in time for early-bird Christmas shopping!

Heath Company, Dept. 20-23
Benton Harbor, Michigan 49022

HEATH
Schlumberger

Heath Company,
Benton Harbor, Michigan 49022

Please send me my FREE Catalog.
I am not on your mailing list.

Dept. 20-23

Name _____

Address _____

City _____

State _____

CL-619

Zip _____

I'd like to do a favor for a
friend — send another catalog to:

Dept. 20-233

Name _____

Address _____

City _____

State _____

Zip _____

LETTERS

continued from page 16

sue) is not correct. This socket is not a standard breadboarding socket, but one designed especially for direct connection at the rear plane of the socket.

Your readers should be aware that until Continental and AP manufacture an interfacing/type of socket, E&L is the only vendor. The correct part number for the Dyna Micro interface/breadboarding socket is SK-10/IF-18. It sells for \$18.75 in single quantity.

RICHARD J. VUILLEQUEZ

Vice President, Sales
E&L Instruments, Incorporated
Derby, CT

PRO SOUND SYSTEMS

Your article "Microphones in Pro Sound Systems" was notable for the things not included rather than what was said. Though you got off to a good start and provided some interesting basics, it is beyond me that the writer of the article should actually believe that condenser microphones should be omitted entirely from the body of the article. We are informed that there are five major types of microphones used in Pro Sound systems, but the thought that ceramic and crystal-type microphones are frequently used could only be sustained by someone looking into the state-of-the-art fifteen years ago! Or perhaps twenty-five! Hurrah for getting some good basics (albeit skim-

py), but the selection of information on specific microphones could perhaps have been better by mentioning fewer types and going into just a little bit more detail on some of the weaknesses and strengths of each.

Finally, I think it's ironic that in an article having information supplied solely by Shure Brothers, Incorporated of Evanston, Illinois, the microphone picture on the front page is an *obsolete* Electro-Voice microphone.

WILLIAM A. RAVENTOS
Buchanan, MI

MICROCOMPUTER/TV INTERFACE

In reference to Mr. Paul Hyde Jr.'s letter (July 1976 issue) concerning microcomputer/TV interface: I purchased a kit from a company in Dallas to interface my Intel 8080 with my TV. It was very reasonably priced. I believe that this kit will meet Mr. Hyde's needs, as it did mine. The company name is IOR, Box 28823, Dallas, TX 75228.

WAYNE FOX
Garland, TX

R-E

General Motors, dealers competing on car radios

General Motors is finding itself in a dispute with some of its dealers over what radios are to go into GM cars. Delco, GM's radio division, reports that it has been losing orders because dealers have been purchasing and installing foreign radios instead of Delco. The parent company has been bothered enough about the situation

to start an ad campaign, urging buyers to "Tell your dealer 'Delco.' Don't settle for a look-alike radio in your new GM car."

The matter is apparently not one that will threaten the survival of either GM or the dealers, since radios come already factory-installed in nearly 90 percent of the company's cars.

R-E



PILOT PRODUCTION LINE for making optical waveguides, now operating in Atlanta, GA. To make the lightguides, high-silica-content glass rods are prepared on a glass lathe (glowing area, upper right), then softened (upper left) and pulled into hair-thin fiber lightguides through equipment in lower left.


Hi! We're PAIA

A lot of you already know us. We're the ones who keep getting better!

Most of our kits are musically related; but that doesn't mean that you have to be a pro-musician - or a musician at all to enjoy them. For instance:

Surf Synthesizer

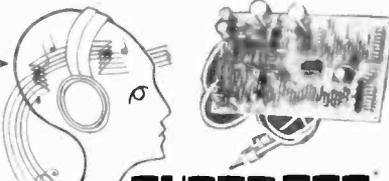Imagine the roar of the surf electronically synthesized and played through your hi-fi.
#3711K \$12.95 + \$1.00 shipping chg.



CHORD EGG

The EGG* plugs into any stereo amp to create soothing, flowing environmental sound textures - and through headphones it's incredible. The chords and notes EXIST in your mind. They pan and swell and phase their way through your psyche in unpredictable patterns never repeating.

The combination of LSI organ technology with synthesizer-type processing and digital randomizing/control elements make the EGG an altogether intriguing package from either technological or metaphysical viewpoints.

#3790 \$24.95 + \$1.00 shipping

*EGG - Encephalo-Gratification Generator

OZ & GNOME



THE GNOME MICRO-SYNTHESIZER kit

The Gnome can make outer space sounds for rock musicians, demonstrate principles of music and acoustics for educators, provide rhythmic pulses and tones for modern dance groups, create sound effects for theatre companies and is one of the neatest toys in the world for an audiophile.

#3740 - \$48.95 - + shipping for 4 lbs.

OZ - MINI-ORGAN

OZ is polytonic with over 6-1/2 octaves total range from its 1-1/2 octave keyboard. Large scale integration & CMOS technology allow battery powered portability. Output jack and switch selectable step or multiple pulse trigger provides simple synthesizer interface. OZ has a unique pressure-sensitive pitch bender that chromatically transposes single notes or whole chords, and a built in speaker and amplifier.

#3760 - \$84.95 - + shipping for 12 lbs.

And don't forget... these two were designed to operate together in one of the most synergistic relationships imaginable. Just think, a completely portable polytonic synthesizer-like instrument for less than you'd expect to pay for a guitar. Terrific!

Now, if it happens that you are a Pro musician, you really owe it to yourself to check out our electronic music synthesizer packages. Like our 4700/S for example. It costs about 50% of what "mini" packages from other manufacturers do - and you can judge for yourself whether it's a mini or not.

4700/S



Synthesizer

When you combine all of the modules that are part of this package including keyboard, 12-event sequencer and a four input stereo mixer, it's almost like having 2 synthesizers in a single package. Wrap them all in sturdy road cases and you have an instrument that goes anywhere and does any job.

#4700/S Kit - \$499.00
shipped air freight col.

Send TODAY for your FREE catalog with details on these and dozens of other fascinating PAIA kits.

PAIA ELECTRONICS DEPT. 11-R
1020 WEST WILSHIRE BLVD.
OKLAHOMA CITY, OK 73116

Solder is for sissies.


Are you still designing circuits the old fashioned way? Soldering and unsoldering? Burning up valuable IC's? If so, it's time you made a switch to solderless breadboarding. E&L Instruments offers a complete line of breadboarding products from sockets to the most complete systems for professional use. Here are five ways you can go solderless . . .

SK-10 Socket



This precision solderless breadboarding socket will pay for itself in one afternoon. Integrated circuits and discrete components insert directly, without adapters. All interconnections are made with 20 to 26 gage solid conductor wire. \$17.75.

Breadbox III

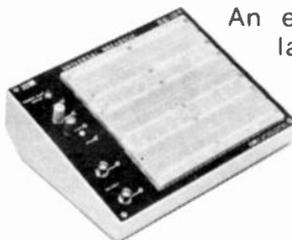

An economical approach to a large breadboarding area. Three SK-10 sockets, four 5-way binding posts, two BNC connectors, six BP-22 solderless breadboarding pins. \$65.00.

Op-Amp Designer #OA-2K




Powerful design tool for linear work and CMOS digital circuitry. SK-10 socket. Heavy current capacities on all three power supplies [+/- 15V & +5V DC]. Sensitive null detector and a full function generator with external frequency adjustment. All interconnections are solderless. \$95.00 in kit form.

Op-Amp Designer #OA-3K



SK-10 socket. Plus and minus variable supplies (1 to 15V). This adjustable feature makes the unit exceptionally flexible, allowing it to be more useful for odd voltage requirements. The fixed 5 volt supply allows interfacing with TTL circuitry. \$80.00 in kit form.

Digi-Designer #DD-1K

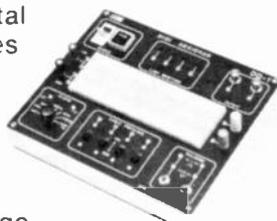

A must for every student, engineer or technician doing digital circuit design. Handles both IC and discrete components without soldering. Connections to the SK-10 socket are made using any solid 22 gage insulated wire. The DD-1K includes a clock, power supply, logic lights, pulsers, logic level switches and much more. All circuitry is now in one circuit board. \$70.00 in kit form.

CIRCUIT DESIGN, INC.

Division of E & L Instruments, P.O. Box 24, Shelton, Conn 06484

It's time you went solderless! Order any one of the five products above by completing and sending in this coupon. Please don't forget to sign coupon and include check, money order or charge card information.

Please send me your model # _____
_____ pictured above for \$ _____.
Enclosed find my Check _____ Money
Order _____ or Charge information for
BankAmericard _____ or Master Charge
_____. (Make sure you sign the order
blank.)

NAME: _____

ADDRESS: _____


CITY: _____ STATE: _____ ZIP: _____

SIGNATURE: _____

Circuit Design will prepay shipping anywhere in the U.S.

The IMSAI 8080.

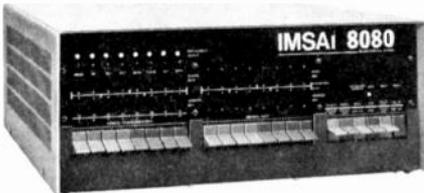A commercial yet personally affordable computer.



If you thought you could never afford a computer at home, think again. The IMSAI 8080 is built for rugged industrial performance. Yet its prices are competitive with Altair's hobbyist kit. Fully assembled, the 8080 is \$931. Unassembled, it's \$599.

The IMSAI 8080 is made for commercial users, and it looks it. Inside and out. The cabinet is attractive, heavy gauge aluminum. The heavy duty lucite front panel has an extra 8 program controlled LED's. It plugs directly into the Mother Board without a wire harness. And rugged commercial grade paddle switches are backed up by reliable debouncing circuits.

The system is optionally expandable to a substantial system with 22 slots in a single printed circuit board. And the durable card cage is made of commercial-grade anodized aluminum.

The IMSAI 8080 power supply produces a true 28 amp current, enough to power a full system. You can expand to a powerful system with 64K of software protectable memory plus an intelligent floppy disk controller. You can add an audio tape cassette input device, a printer plus a video terminal and a teletype. And these peripherals will function with an 8-level priority interrupt system. BASIC software is available in 4K, 8K and 12K.

Get a complete illustrated brochure describing the IMSAI 8080, options, peripherals, software, prices and specifications. Send one dollar to cover handling to IMS. The IMSAI 8080. From the same technology that developed the HYPERCUBE Computer architecture and Intelligent Disk systems.

Dealer inquiries invited.

IMS

IMS Associates, Inc.
14860 Wicks Boulevard
San Leandro, CA 94577
(415) 483-2093

Dept. RE-11

KOMPUTER KORNER

A look at the arithmetic/logic instructions and processor flags of the 8080 microprocessor

TIM BARRY

WE PREVIOUSLY DISCUSSED THE DATA-TTRANSFER instructions that can be performed by the 8080. This month we will continue on with this presentation by examining the arithmetic/logic instructions that the 8080 uses to operate upon the data located in its registers and the system memory. (You may wish to refer to the previous column for an explanation of some of the notations used to represent various register groups, data types, and data transfers.)

Arithmetic/logic instructions

Any computer instruction that modifies the contents of a register, memory location or flag by any arithmetic or logic operation is considered to be a member of this group. As with data-transfer instructions, we can consider arithmetic/logic instructions in the context of data sources and data destinations. The execution of an arithmetic/logic operation causes the contents of one or more data sources to be operated upon by the computer's arithmetic/logic unit. The result of the operation is then placed into the data destination. The contents of the data sources used in the operation are called *operands*. Most computer arithmetic/logic operations use one, two or occasionally three operands. The 8080 uses arithmetic/logic operations that require either one or two operands.

Processor flags

Intimately related to the concept of arithmetic/logic instructions is the concept of *processor flags*, or simply *flags*. A flag is an internal logic element (usually a flip-flop) that indicates the state of the processor. Some of these flags are set and reset based upon the result of the various arithmetic/logic operations. These flags can then be tested and their state used to determine whether or not some operation is to be executed. For example, the operation to take place after an addition operation has been performed may depend on whether or not the result of the operation was zero. If the processor has a flag that is set if the result of an operation is zero, it could be tested and the next step based on whether or not it was set or clear. Without flags to set and test, the ability of the computer to modify its operation based upon the results of operations performed would be lost, and with it the flexibility of programmed control.

The 8080 provides four flags that are affected by arithmetic/logic operations and they are tested under program control. These are the carry flag, the zero flag, the sign flag and the parity flag. The conditions that are indicated by these flags are described below:

Carry flag: The carry flag is set or reset under the following conditions:

1. Set if the result of an addition is greater than 256
2. Set if the result of a subtraction is less than 0

3. Cleared by all logic operations (AND, XRA, ORA)
4. Set or cleared by the rotate instructions

In addition, there are two 8080 instructions that can be used to directly modify the state of the carry flag. Each instruction is listed below (in bold) followed by the data-transfer notation and the meaning.

STC (1)

Operation performed: $1 \rightarrow C$
The carry flag is set to 1.

CMC (1)

Operation performed: $\bar{C} \rightarrow C$
The state of the carry flag is complemented.

Zero flag: The zero flag is set to a logic-one anytime an arithmetic or logic operation results in a zero in the accumulator.

Sign flag: The sign flag corresponds to the sign of the two's complement number in the accumulator after an arithmetic or logic operation has been performed. If bit-7 of the accumulator is a zero (the number is positive), the sign flag will be set to a logic-0. If bit-7 of the accumulator is a logic-1 (the number is negative), the sign flag will be set to a logic-1.

Parity flag: The parity flag is set or reset based upon the number of logic-1's left in the accumulator as the result of an arithmetic or logic operation. If the number of bits set to logic-1 in the accumulator is even (even parity), then the parity flag will be set to logic-1. If the number of bits set to logic-1 in the accumulator is odd (odd parity), then the parity flag will be set to logic-0.

It is important to remember that the flags are only set or cleared as the result of arithmetic and logic operations. With one exception, data-transfer instructions do not alter the state of the flags. This means that to test a value from memory or an input device, you must perform an arithmetic or logic operation with that value to set the flags. The act of transferring data, by itself, does not set flags to correspond to the data transferred.

When using the 8080, the contents of the accumulator and all flags can be treated as a program status word (PSW). PSW can be saved in the stack by using the PUSH PSW instruction. This saves the status of the flags when the push instruction is executed. This status can then be restored later by using a POP PSW instruction. (POP PSW is the data transfer-instruction that violates the general statement that data transfers don't alter flags.)


continued on page 26

you don't
listen to the
Realistic
Mach One...

you
experience
it!



Realistic® and Radio Shack lower the cost of thrilling theatre-like sound. 22 years of design know-how and sales of a million speakers annually have shown us how. Powerful 15" woofer. Multi-cell midrange horn. High-compliance tweeter horn. Removable grille for easily balancing midrange and treble response. And genuine walnut veneer cabinetry. It's a real experience to hear the Mach One at live-performance listening levels. Bring in your favorite LP and we'll give you a thundering demonstration that will change your notions about who's really pioneering in hi-fi. Buy the amazing Mach One and we'll also give you a 5-year limited warranty. Ask for 40-4024 at your nearby Radio Shack store or participating dealer. **199^{50*}**

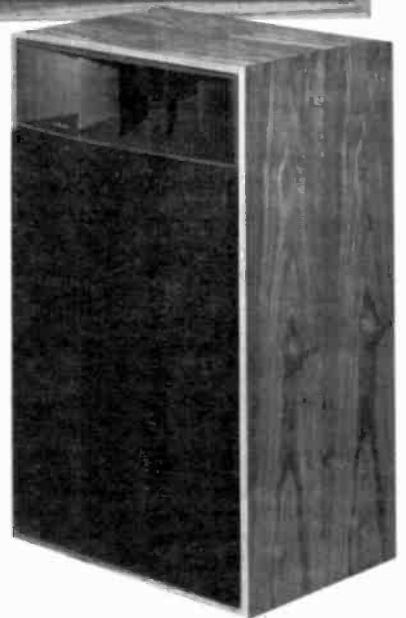

Use your credit card
at most stores

SOLD ONLY WHERE YOU SEE THIS SIGN:

Radio Shack®

A TANDY COMPANY • FORT WORTH, TEXAS 76107
5000 LOCATIONS IN NINE COUNTRIES

*Price may vary at individual stores and dealers.

CIRCLE 79 ON FREE INFORMATION CARD

NOVEMBER 1976

25

KOMPUTER KORNER

continued from page 24

Two-operand instructions

The 8080 provides nine basic two-operand arithmetic/logic operations. Eight of these are 8-bit operations and one is a 16-bit operation. For the 8-bit operations, the two data-sources are the A register and one of the following: A single register (A, B, C, D, E, H, or L), the contents of memory as addressed by the HL register pair (M), or an 8-bit immediate data value (D8). The data destination is always the A register. For the 16-bit operation, the two data-sources are the HL register pair and one of the 16-bit register pairs (BD, DE, HL) or the stack pointer (SP). The data destination is always the HL register pair.

ADD S (A) + (S) → A (1)
ADD M (A) + ([HL]) → A (1)
ADI D8 (A) + D8 → A (2)

The above program adds the contents of the specified data source to the contents of A and the result is placed in A. All flags are affected.

ADC S (A) + (S) + C → A (1)
ADC M (A) + ([HL]) + C → A (1)
ACI D8 (A) + D8 + C → A (2)

The above program adds together the contents of the specified data source, the contents of A and the carry flag, and the result is placed in A. All flags are affected.

SUB S (A) - (S) → A (1)

SUB M (A) - ([HL]) → A (1)
SUI D8 (A) - D8 → A (2)

Here, the contents of the selected data source are subtracted from the contents of A and the result is placed in A. All flags are affected by this operation.

SBB S (A) - (S) - C → A (1)
SBB M (A) - ([HL]) - C → A (1)
SBI D8 (A) - D8 - C → A (2)

The contents of the selected data source and the carry flag are subtracted from the contents of A and the result is placed in A. All flags are affected.

ANA S (A) ∧ (S) → A (1)
ANA M (A) ∧ ([HL]) → A (1)
ANI D8 (A) ∧ D8 → A (2)

The logic and operation is performed using the contents of A and the selected data source. The result is placed in A. All flags are affected.

XRA S (A) ⊕ (S) → A (1)
XRA M (A) ⊕ ([HL]) → A (1)
XRI D8 (A) ⊕ D8 → A (2)

The exclusive-or operation is performed using the contents of A and the selected data source. The result is placed in A. All flags are affected.

ORA S (A) ∨ (S) → A (1)
ORA M (A) ∨ ([HL]) → A (1)
ORI D8 (A) ∨ D8 → A (2)

The logic-or operation is performed using the contents of A and the selected data source. The result is placed in A. All flags are affected.

CMP S (A) - (S) (1)
CMP M (A) - ([HL]) (1)
CPI D8 (A) - D8 (2)

The contents of the selected data-source are compared to the contents of A. The comparison is made by subtracting the contents of the data source from A, with the flags set based on what the result would have been. *Neither A nor the data source is modified by the operation.* All flags are affected.

DAD RP (HL) + (RP) → HL (1)

The contents of the selected register pair are added to the contents of the HL register pair. The result is placed in HL. Only the carry flag is affected.

Single-operand instructions

Single operand arithmetic/logic instructions use the same data resource as both data source and data destination. These operations are used to modify the individual registers, register pairs, and memory locations in the 8080 system.

RLC (A₇) → C, (A₇) → A₀, (A_n) → A_{n-1} (1)

RRC (A₀) → C, (A₀) → A₇, (A_n) → A_{n+1} (1)

RAL (A₇) → C, C → A₀, (A_n) → A_{n+1} (1)

RAR (A₀) → C, C → A₇, (A_n) → A_{n-1} (1)

These four instructions treat the A register and carry flag as a serial rotation register. The graphical representation of these rotations is shown in Fig. 1. Note how RAL and

continued on page 28

a revolutionary concept in kit building...

THE PROGRAMMABLE CLOCK KIT! \$27.95

SYSTEM 5000 is the first full-feature timepiece available in programmable form. After the circuit has been assembled and tested, all that is necessary is to add the appropriate switches and jumpers to easily program the system for the desired functions. The system may be expanded or reprogrammed at any time.

This represents a revolutionary concept in adaptability and flexibility. Build an Alarm/Clock/Calendar or a full feature Desk or Radio Station clock. Use the DUPLICATE TIME REGISTER to monitor GMT, another time zone, or as an elapsed timer. Add the optional relay to control AC or DC accessories. The possibilities are limited only by your imagination.

features

TIME OF DAY REGISTER • DUPLICATE TIME REGISTER • FOUR YEAR CALENDAR - month/day or day/month format • ALARM WITH SPEAKER TONE OUTPUT • ADDITIONAL ALARM - use for "his and hers" alarm or activate an accessory at a preset time • 10 MINUTE SNOOZE & "D" REMINDER • 3 FUNCTION ALARM OUTPUT SELECT - tone, relay, or relay then tone • ONE HOUR DOWN COUNTER • BRIGHT FLUORESCENT DISPLAY - .5" blue or green digits with AM/PM • AUTOMATIC DISPLAY DIMMING • POWER FAILURE INDICATION • 12 & 24 HOUR DISPLAY • BLINKING OR STEADY COLOR • SIMPLE FORWARD AND REVERSE TIME SETTING •

DIRECT DRIVE ELIMINATES RFI • SINGLE 9 VOLT BATTERY BACKUP • DISPLAY SECONDS CONTROL • HOLD AND RESET CONTROLS • 50/60 HZ OPERATION • 700 WATT RELAY OUTPUT OPTIONAL

SYSTEM 5000 includes all components, 2 time setting switches, and complete assembly and programming manuals. Switches for additional functions and relay are not included but are available as options. Case not included. Specify blue or green display.

RELAY OPTION - \$4.00

Includes 700 watt relay and all interface components. Will control AC or DC accessories such as appliances, stereos, etc.

SWITCH OPTION - \$3.75

Contains 4 black SPST pushbuttons, 2 black DPDT pushbuttons, and 2 black SPST slide switches. Programs all major features.

Send your check or money order today for fast delivery. Add \$1.00 per clock to cover shipping and insurance. Money back guarantee on all products if not fully satisfied. N.J. residents add 5% sales tax. Use your Master Charge or BankAmericard. Phone orders accepted.

add a new dimension to time itself...
SERIES 2000 Decorator Clocks



A bright Fluorescent display provides easy to read numbers that brighten and dim automatically according to the light. The clear Acrylic tube with Acrylic or Hardwood end blocks gives these clocks a unique look of simple elegance. AM/PM & power failure indication. Seconds display button. 3 1/2" x 5 1/2" x 5 1/2". 50/60 HZ. Specify blue or green display, 12 or 24 hour time, and choice of Hardwood - Walnut, Zebra wood, or Rosewood.

FACTORY ASSEMBLED - 1 YEAR WARRANTY
 EC-2001 Solid Acrylic "Time Capsule" \$69.95
 EC-2002 Acrylic & Hardwood \$49.95

COMPLETE KITS - 90 DAY WARRANTY
 EC-2001-K Solid Acrylic NEW! \$34.95
 EC-2002-K Acrylic & Hardwood SPECIAL! \$29.95

 digital concepts

DIGITAL CONCEPTS CORPORATION
 249 Route 46, Saddle Brook, N.J. 07662
 201/845-7101

CIRCLE 77 ON FREE INFORMATION CARD

ONE RIG DOES IT ALL!

Tube and Solid State

THE UNIVERSAL
PJS-298

33KV LEADED GLASS 19" CRT

EIA recommended to protect against
dangerous X-radiation

BUILT-IN SPEAKERS

Easy audio checking

40 KV METER

50aU sensitivity monitoring

FRONT CONNECTORS

Convenient cable plug-in

~~\$298.98~~ VALUE

SPECIAL INTRODUCTORY OFFER

\$229.95

COMPLETE WITH CRT



OBSOLETE PROOF

Plug in modules for up-dating

**A MUST FOR
TODAY'S
SERVICING**

ACCESSORIES INCLUDE:

- CRT 90° Extension
- Yoke Extension
- Transverter
- Convergence Load
- Universal Yoke
- Convergence Assembly
- Blue Lateral Assembly
- Anode Extension

SOLD THROUGH DISTRIBUTORS ONLY

PLEASE SEND ME MORE INFORMATION

N-6

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

Telematic

2849 FULTON ST., BROOKLYN, NY 11207
PHONE: (212) 827-1500

KOMPUTER KORNER

continued from page 26

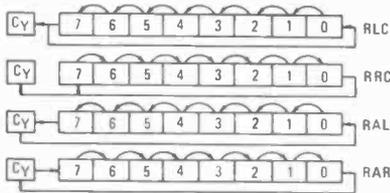


FIG. 1

RAR actually include the contents of the carry flag in the rotation. RLC and RRC modify the carry flag but do not include it in the rotation. No flags other than carry are affected by these instructions.

INR S (S) + 1 → S (1)

INR M ([HL]) + 1 → [HL] (1)

The contents of the selected data source are incremented by one. All flags *except* carry are affected.

DCR S (S) - 1 → S (1)

DCR M ([HL]) - 1 → [HL] (1)

The contents of the selected data source are decremented by one. All flags *except* carry are affected.

INX RP (RP) + 1 → RP (1)

The contents of the selected register pair are incremented by 1. No flags are affected.

DCX RP (RP) - 1 → RP (1)

The contents of the selected register pair are decremented by 1. No flags are affected.

DAA IF (A₀ - A₃) > 9, (1)

then (A) + 6 → A

If (A₄ - A₇) > 9,

then (A) + 60H → A

The DAA instruction is used to adjust the hexadecimal contents of A into two BCD digits. If the four least-significant bits of A (commonly called the least significant nibble, since a nibble is about half a byte) is a value greater than nine, six is added to A. This forces the least significant nibble into the range zero to nine. The most significant nibble is then tested. If it is now greater than nine, 60H is added to A to force the value into the range zero to nine. If the result of adjusting the value in A results in a value greater than 99 decimal, the carry flag is set. All flags are affected by the operation.

CMA $\bar{A} \rightarrow A$ (1)

The contents of the accumulator are complemented. No flags are affected.

This column has presented a look at the arithmetic/logic instructions offered by the 8080. In this short space it is practically impossible to provide all the details of a complex computer instruction set. We have attempted instead to give a good overview into the operation of these instructions. In future articles we will use these instructions as the building blocks of more complex operations. If we need a more detailed analysis of the operation of a particular instruction, it will be presented at that time.

This article was the second in our series on

the 8080 instruction set. In a future column we will conclude the presentation by examining the transfer of control and processor control instructions. **R-E**

Optoelectronics now used in auto ignition systems

As a new type of "breaker points" for the transistor auto ignition system, Siemens is experimenting with what they call a "light barrier", or light switch, as being simpler and longer lasting than systems now in use. The first electronic ignition systems simply used the breaker points already on the car, on the basis that the points might last indefinitely with the negligible current drawn by a transistor circuit. Later, magnetic pick-up systems that require no physical contact of the "breaker points" have been used, and the Siemens report also speaks of magnetoresistor sensors and Hall generators being used to trigger the transistor ignition.

In the Siemens device, an LED transmits the trigger signal for the ignition and a phototransistor picks it up. Between the light-emitting diode and the phototransistor is a slotted disc that rotates on the distributor shaft, allowing a narrow beam of light to pass at the firing point. The duration, or dwell, depends on the slot width.

Before full-scale production can be started, there are temperature and economic problems to be ironed out. Metal cases would be satisfactory at the temperatures to be withstood, but cost considerations indicate the use of plastic. **R-E**

Build your own Digital Clock!

It's easy with the Calectro Digital Clock Kit! The complete kit with everything necessary for fast, easy assembly, including illustrated step-by-step instructions. See the Digital Clock, TTL Power Supply, Motor Speed Control, DC Regulated Power Supply and Burglar Alarm kits at Calectro dealers everywhere!


CAT. NO.
G2-108

- Bright LED readout
- AM-PM indicator
- 110 V operation
- Step-by-step instruction booklet

*Calectro Kits - Ready to Assemble
Fun - Practical - Educational*



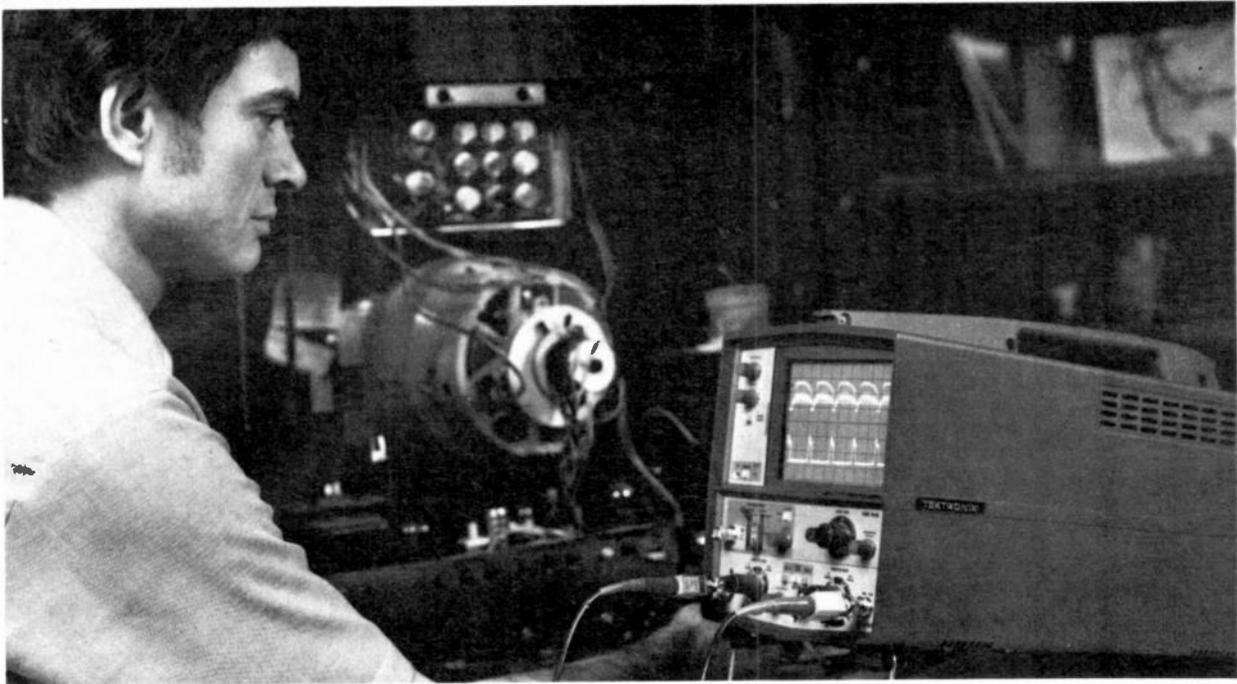GC ELECTRONICS
DIVISION OF HYDROMETALS, INC.
ROCKFORD, ILLINOIS 61101 U.S.A.



Now you can service with a TEKTRONIX Oscilloscope for as little as \$695*

Cost of service instruments is an important factor in any purchase. But so is reliability. Now T900 Oscilloscopes give you both Tektronix quality *and* reliability at prices *designed* for cost sensitive applications.

- T921—Ds to 15 Mhz; single trace,
single time base \$695*
- T922—Dc to 15 MHz; dual trace,
single time base \$850*
- T932—Dc to 35 MHz; dual trace,
single time base \$1195*
- T935—Dc to 35 MHz; dual trace,
delayed sweep time base \$1395*
- T912—Dc to 10 MHz; bistable stor-
age; writing speed to 250
cm/ms; dual trace, single time
base \$1300*


Performance to Spare

All T900 scopes feature large (8x10 cm), bright crt's; sensitivity of 2 mV/div to 10 V/div in twelve calibrated steps; regulated power supplies; and 3% accuracy. T900 Oscilloscopes are also equipped

with important convenience features; beam finder, single knob triggering, automatic selection of chopped or alternate mode, and automatic selection of tv line or frame display (except T912 Storage model). T900 scopes are compact (7x9x19 in.) and lightweight (only 16 lb.). They are available with a full selection of accessories.

For a demonstration of any T900 Oscilloscope or a free copy of the new T900 brochure, write to Tektronix, Inc., P.O. Box 500, Beaverton, OR 97077. For immediate assistance, call (503) 644-0161, extension T900.

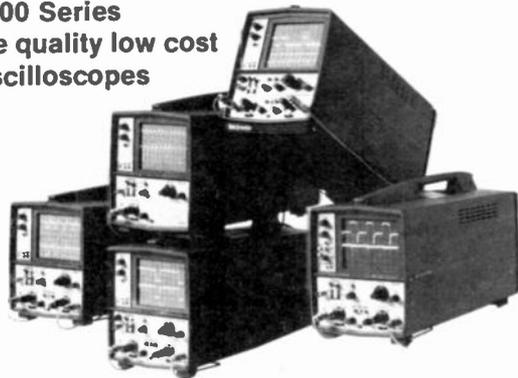T900 Series the quality low cost Oscilloscopes



*All prices include 10X probes. U.S. sales price FOB Beaverton, Oregon.




TEKTRONIX®

committed to
technical excellence

CIRCLE 32 ON FREE INFORMATION CARD

equipment reports

Jolt 4K RAM Module

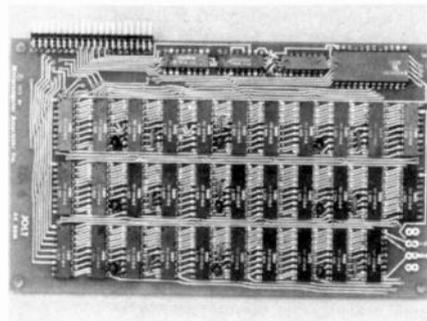

CIRCLE 87 ON FREE INFORMATION CARD

I WAS INTRODUCED TO THE EXCITING REALM OF microcomputers and machine language programming through the JOLT CPU board, and I continue to have great respect for the system. For some time, I have been eager to expand the system's memory and get on to bigger and better things. And that is what the 4K RAM board is all about—a nice large chunk of additional programming space.

Packaged onto the 4.25 × 7-inch JOLT board are a total of 36 integrated circuits, of which 32 are the memory devices. The only other components are 18 bypass-capacitors and three jumper wires. Each memory IC is organized as 256 4-bit words. Multiplying 256 by the 32 IC's gives 8192 4-bit words. Converting to the 8-bit word length of the 6502 μ P, the number of words is halved to 4096, or 4K for short.

There are 8 input-address leads to each memory IC to address the 2^8 (256) words, and 4 output lines. The eight least-significant address lines (A0-A8) originating from the CPU card, feed the eight memory-address terminals of all the memory IC's in parallel. CPU address lines A8 through A11 are the inputs for a 74154 4-line to 16-line decoder. Each output from this IC connects to the enable pins on a pair of memory IC's. The four input/output data leads on one of the pair connects to the RAM board data lines D0 through D3, and the other circuit to D4 through D7.

This leaves the upper four address lines A12 through A15. In the JOLT scheme of


things, one-half the total memory space has been reserved for user RAM and the other half for inputs, outputs and other peripheral functions such as the interval timer on the MOS Technology 6530 IC. The A14 input is permanently wired to the chip-enable pins of all the 32 memory circuits, which blocks off two 16K blocks from 4000₁₆ to 7FFF₁₆ and C000₁₆ to FFFF₁₆.

Address lines A12, A13, and A15 or their complements are connected to assign the 4K board to a segment of the remaining 32K memory space. Two gates of a 7400 quad 2-input NAND gate are wired as a three-input gate that connects to the two enable pins of the 4-to-16 line decoder. As an example, when A12, A13 and A15 are all complemented, and since A14 is permanently complemented, the most significant hex address digit of 0 would enable the decoder and the memory will respond to addressing from 0000 to 0FFF.

The basic CPU board comes with 512 words of RAM assigned to 0000 to 01FF. If the 4K board is assigned 0000 to 0FFF, the

continued on page 32

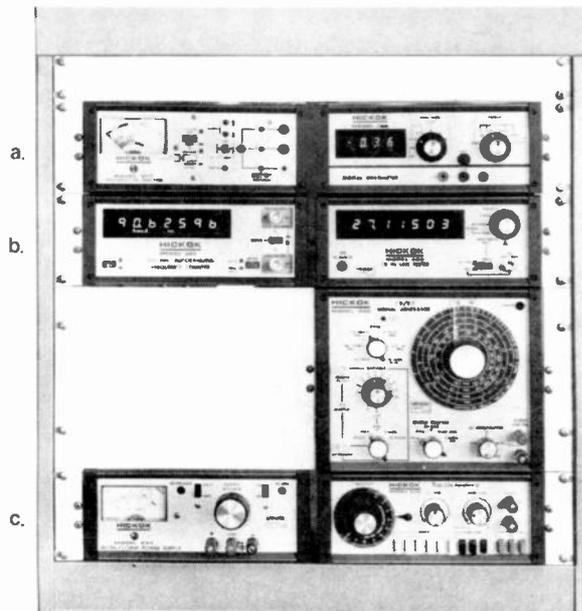Make working on CB's easier with the CommLine from Hickok.



- a) Model 217 Semiconductor Analyzer. \$169
- b) Model 385 Autoranging 500 MHz Frequency Counter. \$499
- c) Model 244 Mobil/Comm Power Supply \$125
- d) Model 334 Digital Multimeter \$234
- e) Model 388X Pro CB In-Line Tester. \$475
- f) Model 256 CB / RF Signal Generator. \$199
- g) Model 270 Function Generator. \$189
- h) Model CL-1 CommLine Rack Cabinet. \$35

f. **HICKOK** CommLine
To put together exactly the CommLine CB Service Center you need, see your Hickok distributor.

HICKOK

h. **the value innovator**

INSTRUMENTATION & CONTROLS DIVISION
THE HICKOK ELECTRICAL INSTRUMENT CO
10514 Dupont Avenue • Cleveland Ohio 44108
(216) 541-8060 • TWX 810-421-8286

CIRCLE 7 ON FREE INFORMATION CARD



6800-SOFTWARE

WARNING – It has been determined that reading this ad may be hazardous to your health, if you own another type computer system. We will not be responsible for ulcers, heartburn, or other complications if you persist in reading this material.

4 K BASIC^o — 8 K BASIC^o

- * Full floating point math
- * 1.0E-99 to 9.99999999E+99 number range
- * User programs may be saved and loaded
- * Direct mode provided for most statements
- * Will run most programs in 8K bytes of memory (4K Version) or 12K bytes of memory (8K Version)
- * USER function provided to call machine language programs
- * String variables and trig functions—8K BASIC only

COMMANDS

LIST
 RUN
 NEW
 SAVE
 LOAD
 PATCH

REM
 DIM
 DATA
 READ
 RESTORE
 LET*
 FOR

STATEMENTS

END
 GOTO*
 ON...GOTO*
 ON...GOSUB*
 IF...THEN*
 INPUT † DES
 PRINT* † PEEK
 NEXT † POKE

FUNCTIONS

ABS † VAL † SIN
 INT † EXTS † COS
 RND † LENS † TAN
 SGN † LEFTS † EXP
 CHR † MIDS † LOG
 USER † RIGHTS † SQR
 TAB

* Direct mode statements
 † 8K Version only

MATH OPERATORS

- (unary) Negate
- * Multiplication
- / Division
- + Addition
- Subtraction
- † Exponent

RELATIONAL OPERATORS

- = Equal
- < > Not Equal
- < Less Than
- > Greater Than
- <= Less Than or Equal
- >= Greater Than or Equal



© Copyright 1976 by Southwest Technical Products Corp. 4K and 8K BASIC Version 1.0 program material and manual may be copied for personal use only. No duplication or modification for commercial use of any kind is authorized.



You guys are out of your minds, but who am I to complain. Send —

- 4K BASIC CASSETTE \$4.95 MP-68 Computer
 8K BASIC CASSETTE \$9.95 Kit \$395.00

NAME _____

ADDRESS _____

CITY _____

STATE _____

ZIP _____

Southwest Technical Products Corp.
 Box 32040, San Antonio, Texas 78284

EQUIPMENT REPORTS

continued from page 30

first 512 words would overlap the CPU memory space and the memory on the CPU board would have to be removed. Microcomputer Associates recommends that additional memory space be filled starting at 1000. That makes good sense and that is precisely where I wired it by inverting A15 and A13, while using the noninverted A12 lead. Two CMOS circuits (a 4050 non-inverting hex-buffer and a 4049 inverting hex-buffer) buffer these high-order address lines as well as A8 through A11.

Don't get worried by all this; the documentation is excellent and there is a simple chart

telling where to connect the three jumpers for all possible memory space allocations.

Also interconnecting the CPU and RAM boards are the eight D0 through D7 data leads and the \overline{RW} (read-write) and \overline{WRITE} signals. The data lines are bi-directional for both reading and writing data. \overline{RW} is wired to the 32 output-disable pins in parallel. When the signal is at a logical 1—a read condition—the data lines become high-impedance inputs. The R/W memory IC pins connect to the CPU \overline{WRITE} lead; when it is low the memory is in its write state. Only the pair of memory IC's selected to write at any time will present a low drive impedance to the data lines.

Construction of this board calls for the same care as all computer boards. The right

tools are a must and should include a first-class soldering iron and a magnifying glass.

The 4K memory board can be stacked with the CPU, PIA, power supply, and future options using connectors for the address, data, and control lines, or with simple wire loops.

Typical current drain is 1-amp from a single 5-volt power supply. And typical boards do exist since our sample took just about 1 amp. The maximum current drain is 1.9 amps. You must evaluate your power-supply situation and may have to beef up its capacity. The standard JOLT supply will support a CPU, 4K RAM, and an I/O card.

Just what does 4K of memory do for you? A mathematical operating system easily fits. I have just finished writing a floating point package that uses a little more than 1K of memory.

The JOLT 4K RAM card sells for \$199 in kit form and \$249 assembled. It is available from Microcomputer Associates, 2589 Scott Boulevard, Santa Clara, CA 95050. Also available are cards for the Intel 8080A and the Motorola 6800. The Signetics 2650 system is on the drawing board. **R-E**

Here's The REAL THING

No imitators here. These are the original, genuine CHANNELLOCK tongue-'n-groove pliers. The ones with the smooth-working, machined, undercut mating parts that can't slip out. The ones with the reinforcing flange that practically eliminates stress breakage. The first of their kind and still best of their kind. Be sure you get the real thing. CHANNELLOCK. Look for the trademark on the handle.

CHANNELLOCK, INC., • Meadville, Pa. 16335


CHAN NEL LOCK

The ORIGINAL Tongue-'N-Groove Plier

Models shown: No. 424 • 4½", No. 426 • 6½", No. 410 • 9½", No. 420 • 9½", No. 422 • 9½", No. 415 • 10", No. 430 • 10", No. 440 • 12", No. 442 • 12", No. 460G • 15"

CIRCLE 28 ON FREE INFORMATION CARD

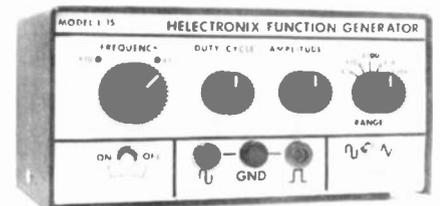Helectronix L-15 Pulse-Sweep Function Generator



CIRCLE 88 ON FREE INFORMATION CARD

THE FUNCTION GENERATOR IS RAPIDLY REPLACING the audio-signal generator on the service bench. It is actually an audio-signal generator, but much more versatile and covers a wider range of frequencies and waveforms. With modern IC's, it can do many tricks not before possible. A good example of this is the model L-15 Pulse-Sweep Function Generator made by Helectronix, 8100 St. Clair Av., North Hollywood, CA 91605.

This is an extremely compact little instrument, only 6 × 2 × 4 inches (16 × 8 × 10 cm.) It has all of the standard function generator outputs—sine, square and triangle waveforms. We've used squarewaves for audio testing for quite a while and they're still good. You'd be surprised, though, at how handy a triangle wave really is! It will show up any tendency of the equipment to clip (when the wave form peaks flatten). Any other kind of distortion will show up as a curvature of the straight (sloping) sections of the waveform.

The frequency coverage of the L-15 is wide—from 1 Hz to 100 kHz in 5 switched ranges. A variable control calibrated from ×1 to ×10 is also provided for fine-tuning the frequency, if needed. An AMPLITUDE control sets the output level of the sine and triangle waveforms. The waveforms can be selected by a switch. The squarewave has its own output jack on the front panel. All outputs have an impedance of 600-ohms and are short-circuit proof.


continued on page 34

EVERY PROJECT IN THIS BOOK IS ANOTHER REASON TO OWN CSC'S QT SOCKETS AND BUS STRIPS.

With QT solderless breadboarding sockets and bus strips, you can build twice the projects in half the time. Because making connections or circuit changes is as fast as pushing in — or pulling out — component leads. No special clips or jumpers required, either.

When you're building circuits just for the fun of it, you can take them apart in minutes — not hours. So you save money by re-using parts, while eliminating heat damage to expensive components. Interlocking QT Sockets and Bus Strips are infinitely expandable, too: start small and "grow" breadboards as large as you wish.

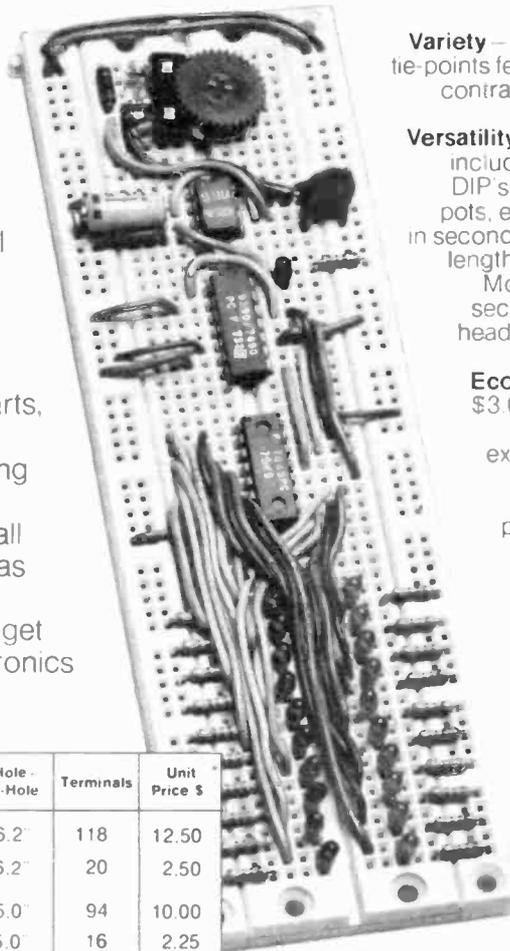For as little as \$3.00, you can get a lot more out of your time in electronics — so why not treat yourself to a QT Socket today?



Variety — 10 models from 70 to 590 solderless tie-points feature snap/lock design to expand or contract your breadboard to fit every circuit and budget requirement.

Versatility — Use with virtually all types of parts, including resistors, capacitors, transistors, DIP's, TO-5's, LED's, transformers, relays, pots, etc. Most plug-in directly and instantly, in seconds. No special jumpers required — just lengths of #22-30 AWG solid hookup wire.

Molded-in holes let you mount QT units securely on any flat surface with 4-40 flat head screws, or 6-32 self-tapping screws, from behind panel.

Economy — Sockets are priced as low as \$3.00*. Save more money by eliminating heat and mechanical damage to expensive parts, re-using components.

Speed — For fast circuit layouts, QT Sockets have 5 interconnecting tie-points per terminal. Bus Strips feature 2 separate rows of interconnecting terminals. Both connect and disconnect easily, without damage to socket or parts.

Visibility — All parts are instantly and easily visible and accessible, for quick signal tracing, circuit analysis and diagramming.

Durability — Higher-temperature sockets with abrasion-resistant, glass-filled plastic, rated better than 100°C. Screw-down-and-interlocked design provides high mechanical strength.

Reliability — Ruggedly designed to professional engineering standards for heavy day-in, day-out use. Non-corrosive prestressed nickel-silver contacts insure more secure mechanical and electrical connections. Vinyl backing prevents shorting when mounted on conductive surfaces.

Length Hole-to-Hole		Length	Hole-to-Hole	Terminals	Unit Price \$
	QT-59S	6.5"	6.2"	118	12.50
	QT-59B	6.5"	6.2"	20	2.50
	QT-47S	5.3"	5.0"	94	10.00
	QT-47B	5.3"	5.0"	16	2.25
	QT-35S	4.1"	3.8"	70	8.50
	QT-35B	4.1"	3.8"	12	2.00
	QT-18S	2.4"	2.1"	36	4.75
	QT-12S	1.8"	1.5"	24	3.75
	QT-8S	1.4"	1.1"	16	3.25
	QT-7S	1.3"	1.0"	14	3.00

All QT units are .33" thick

See your CSC dealer or call 203-624-3103 (East Coast) or 415-421-8872 (West Coast) major credit cards accepted.

*Manufacturer's suggested list • Prices and specifications subject to change without notice
© 1976 Continental Specialties Corporation

CONTINENTAL SPECIALTIES CORPORATION



44 Kendall Street, Box 1942
New Haven, CT 06509 • 203-624-3103 TWX 710-465-1227
West Coast office: Box 7809, San Francisco, CA 94119 • 415-421-8872
TWX 910-372-7992

CIRCLE 29 ON FREE INFORMATION CARD

Incredible counter!

Incomparable price!

A 500mHz (6-Digit) FREQUENCY COUNTER for under 40 cents per mHz! Figure it out. It adds up to unheard-of savings! With guaranteed quality to match and exceed overpriced brands. Let us prove it to you now!

169⁹⁵

\$199.95 assembled

Perfect for: CBers, Hams, Service Techs, & Experimenters!

- HAM, CB, & COMMERCIAL BANDS • WIRED & TESTED AVAILABLE • 100HZ READOUT • 6 DIGITS
- CRYSTAL TIME-BASE • 1Hz OPTIONAL • MASTER CHG. / B. AMERICARD OK • ADD \$2 SHIPPING

Hufco

Incredible counters starting at \$45.95 are also available!
All counters can be factory wired and tested. Write or call today!
Box 357, Dept. 62, Provo, UT 84601 (801) 375-8566

(6-DIGIT/500mHz KIT)
FREQUENCY COUNTER



CIRCLE 56 ON FREE INFORMATION CARD

PTS TV TUNER
TEST INSTRUMENTS...
GIVE YOUR CUSTOMERS
SERVICE, NOT EXCUSES.



With a PTS analyst you know immediately if a set's tuner is malfunctioning. And if it is, the analyst can replace the defective tuner while it is sent to PTS for repair. No delay, no leaving customers without the use of their set, no excuses. All you have left to give is service.

PTS TUNER ANALYSTS

Available preassembled or in money saving Do-It-Yourself kits.
Specify Color: Walnut, Blue or Black. Handles available at no extra cost.

VHF Part-A-Analyst (1010)	\$49.95
Kit (1010K)	\$43.95
UHF Conversion Kit (UKT-10)	\$16.95
All Channel TV Tuner Analyst (2002)	\$44.95
Kit (2002K)	\$39.95
All Channel Part-A-Tuner (3001)	\$49.95
Kit (3001K)	\$43.95
All Channel Part-A-Analyst (4001)	\$59.95
Kit (4001K)	\$49.95
All Channel Field Strength Analyst	\$94.50
Not Available in Kit Form	

For more information or to order PTS TV tuner test instruments, contact:



PTS ELECTRONICS, INC.

P.O. Box 272 Bloomington, IN 47401 812-824-9331

OR, check the white pages for the location of the PTS branch nearest you.

CIRCLE 42 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 32

The squarewave output of the L-15 is fixed-amplitude (4.5-volts minimum) and TTL compatible. The risetime and falltime are 1.0 microsecond. Beside this, a DUTY CYCLE control can be used to give pulses of either polarity, from a 5% to 98% duty-cycle. (This controls the pulse-width. In tests on a scope, we found that we could make stable pulses that were very close to only 1.0 microsecond wide!)

You can also use one of my pet quick-check tests, an audio-frequency sweep with the L-15. All you have to do is apply a variable voltage to a jack that is provided on the back panel. The voltage-controlled oscillator will give sweep ranges from 100:1 to 1000:1. Sweep width depends on the amplitude of the applied voltage, which can be from 0.5 volt to 10 volts maximum. Excessive sweep voltage will make the output clip, so watch it!

The design looks simple. It is built around the Intersil 8038 VCO IC. Its sinewave and triangle wave outputs are fed into a high slew-rate op-amp for buffering. This op-amp also provides a short-proof output with a low impedance. The TTL squarewave is derived from the triangle wave and fed into another op-amp. The other input of this op-amp is pulse-width modulated between the + and - voltage supplies. This lets you get either a logic "1" or "0" by adjusting the duty-cycle control either fully clockwise or counter clockwise. Because all signals have a common source, the VCO, all of them can be swept if the need arises.

The sinewave output can be varied from 0 to 20 volts P-P, at a distortion of 0.5% typical. The triangle wave's amplitude varies over the same range, and its nonlinearity is 2% maximum.

The L-15 sells for \$75.00 fully assembled and tested. You can also get it in kit form for \$55.00 plus \$2.00 for postage and insurance. The PC board, a complete schematic and parts list can be had for \$10.00. A wide range of choices!

This is a versatile little instrument and one that you'll be seeing on more and more service benches pretty soon. It can be used for a great many tests on all kinds of home entertainment electronics and for testing digital circuitry, which is going to be showing up in our shops pretty soon. R-E

Non-Linear Systems FM-7 Frequency Meter




CIRCLE 89 ON FREE INFORMATION CARD
REMEMBER THIS OLD CLICHE: "GOOD THINGS come in small packages"? The cause of this
continued on page 36

ELECTRONICS BOOK CLUB

invites you to take this
1624-page electronics library
for only

\$ **1.99**

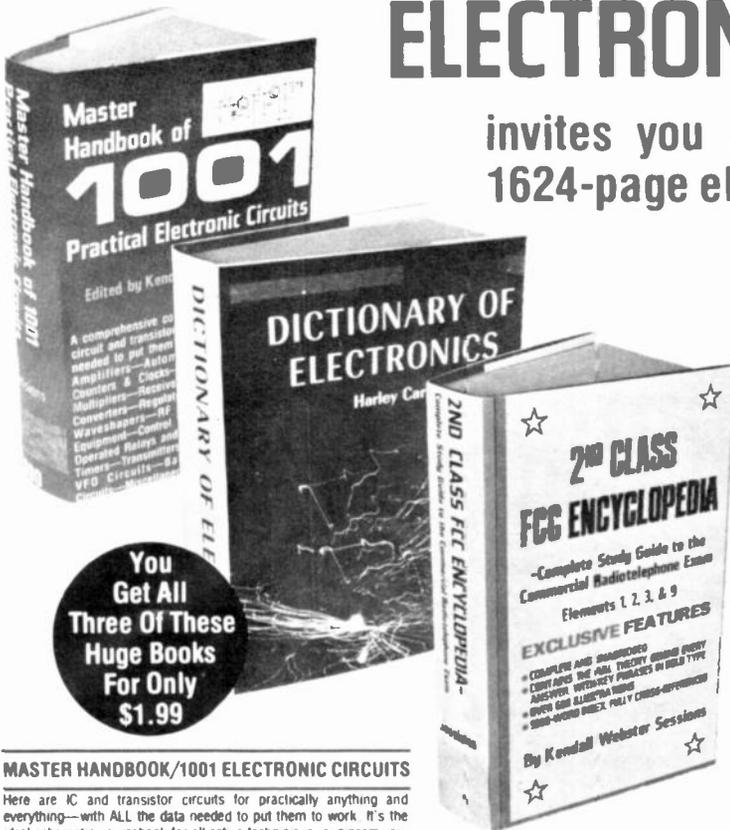

You Get All Three Of These Huge Books For Only \$1.99

- ✓ Only \$1.99 for all three!
- ✓ Regular List Price \$33.85.
- ✓ Top-Quality Hardbinding
- ✓ Features huge quick-find index
- ✓ Over 2300 illustrations
- ✓ Contains over 800,000 words
- ✓ 1624 data-packed pages

with a Trial Membership in the Book Club that Saves you 25% to 75% on a wide selection of electronics books

MASTER HANDBOOK/1001 ELECTRONIC CIRCUITS

Here are IC and transistor circuits for practically anything and everything—with ALL the data needed to put them to work. It's the ideal schematic sourcebook for all active technicians, engineers, experimenters, amateurs—for anyone who must occasionally or regularly construct or adapt electronic circuits for any purpose whatsoever. Each circuit diagram has every component carefully labeled, and every schematic is accompanied by all the info you need to construct the circuit for use in your own individual application. If there are coils to be wound, you'll find full and complete coil-winding details right there on the spot. If special parts are required, you won't have to invest a lot of time and effort before the fact, for it's all there before you in condensed captions. The circuits included are completely up-to-date, and have been designed, built, tested, reworked as necessary, and perfected. You'll find any circuit you're ever likely to need in the pages of this rich volume. Includes an ultracomplete 22-page cross-reference index so you can quickly find the circuit you need. The schematics are classified according to general application. If you're in the business of servicing/repairing commercially built electronic equipment, you're going to especially appreciate the comprehensive Appendix of IC substitutions, which includes base diagrams for most popular ICs, and gives you all the info you need to adapt the IC packages of one manufacturer to the circuit applications of another. 602 pgs., over 1250 illus.

2ND CLASS FCC ENCYCLOPEDIA

Truly a one-volume electronics library all by itself, a 602-page supercourse in electronics that belongs on the bookshelf of everyone in electronics. It's as sweeping and all-encompassing as the FCC exam itself. It's a quick-guide to learning the answers to the 2nd and 3rd Class FCC exams (plus Element 9, for the broadcast endorsement), as well as an intensive, non-nonsense series of courses that can make you the master of any field related to radio communication. A special feature of this unique guide is the short-form, long-form answer format to hundreds of FCC-posed questions. Whenever possible the answer to a question is divided into the shortest answer needed to satisfy the FCC requirements, a longer answer then shows how any similar question may be answered, and is included for reference or for more complete understanding. Questions appear in italicized type. A boldface type section in most answers enables you to immediately extract from the detailed discussion that portion which directly answers the specific question. These theory packets amount to an extremely comprehensive educational approach to the FCC exam, and are just one of the many ways in which this book is one of the easiest-to-use of all radio courses. An extremely complete 5000-word index, fully cross-referenced, provides instant access to any rule, formula, circuit diagram, or technical explanation. 602 pgs., over 600 illus.

DICTIONARY OF ELECTRONICS

This huge quality dictionary is a handy reference that will serve most of your needs—extremely useful in whatever connection you have with electronics. Defines most all of the electronic terms you will run across in your everyday reading—from alpha particles through zoom lens including those found in radio, TV, communications, radar, electronic instrumentation, broadcasting, industrial electronics, etc. The concise but clearly written definitions from all the various branches of electronics are of value to technicians, engineers, hobbyists, experimenters, and students. It provides full, complete and easily understandable explanations of thousands of specific electronic terms. A unique feature is the cross-indexing whereby key words contained in the definitions (words that are defined more fully elsewhere in the book) are printed in small capitals so the user is not left in the dark by any definition. Appendices provide you with still more data—an extensive list of units and abbreviations, graphic symbols used in schematics, component color codes, dB conversion tables, data on the electromagnetic spectrum, tube base diagrams, etc. 420 pgs., 487 illus.

Let us send you these three practical, time-and-money-saving books as part of an unusual offer of a Trial Membership in Electronics Book Club.

Here are quality hardbound volumes, each especially designed to help you increase your know-how, earning power, and enjoyment of electronics.

These handsome, hardbound books are indicative of the many other fine offerings made to Members important books to read and keep volumes with your specialized interest in mind.

Whatever your interest in electronics—radio and TV servicing, audio and hi-fi, industrial electronics, communications, broadcasting, electronics as a hobby—you will find Electronics Book Club will help you get the job you want, keep it, improve it or make your leisure hours more enjoyable. With the Club providing you with top quality books, you may broaden your knowledge and skills to build your income and increase your enjoyment of electronics, too.

This Special Offer is just a sample of the help and generous savings the Club offers you. For here is a Club devoted exclusively to seeking out only those titles of direct interest to you. Members are annually offered over 50 authoritative books on all phases of electronics.

This extraordinary offer is intended to prove to you, through your own experience, that these very real advantages can be yours—that it is possible to keep up

with the literature published in your areas of interest and to save substantially while so doing. As part of your Trial Membership, you need purchase as few as four books during the coming 12 months. You would probably buy at least this many anyway without the savings offered through Club Membership.

To start your Membership on these attractive terms, simply fill out and mail the coupon today. You will receive the 3-volume Electronics Library for 10-day inspection. YOU NEED SEND NO MONEY! If you are not delighted, return them within 10 days and your Trial Membership will be cancelled without cost or obligation.

ELECTRONICS BOOK CLUB, P.O. Box 10, Blue Ridge Summit, Pa. 17214

TYPICAL CLUB SELECTIONS (and List/Club prices):
Microprocessor Microprogramming Handbook \$9.95/\$5.95—VHF/UHF Fire, Police, Ham Scanners Service Manual \$9.95/\$5.95—Modern Guide To Digital Logic \$9.95/\$5.95—CB Radio Schematic Servicing Manuals—3 Volumes \$26.85 \$9.95—Color TV Trouble Factbook \$9.95/\$4.95—C-ber's Handbook Of Simple Hobby Projects \$6.95/\$3.95—Modern Electronics Math \$12.95/\$8.95—Electronic Music Circuit Guidebook \$9.95/\$5.95—Build Your Own Working Robot \$8.95 \$5.95—Intro To Medical Electronics \$9.95/\$6.95—21 Simple Transistor Radios You Can Build \$6.96/\$3.95—Ham Radio Advance Class License Study Guide \$8.95/\$4.95—Aviation Electronics Handbook \$11.95/\$7.95—Practical CB Radio Repair \$8.95/\$5.95—Radio Astronomy for the Amateur \$8.95/\$5.95

Facts About Club Membership

- The 3 introductory books carry a publishers retail price of \$33.85. They are yours for only \$1.99 (plus postage and handling) with your Trial Membership.
- You will receive the Club News describing the current Selection, Alternates and other offerings, every 4 weeks (13 times a year).
- If you want the Selection, do nothing, it will be sent to you automatically. If you do not wish to receive the Selection, or if you want to order one of the many Alternates offered, you simply give instructions on the reply form (and in the envelope) provided, and return it to us by the date specified. This date allows you at least 10 days in which to return the form. If, because of late mail delivery, you do not have 10 days to make a decision and so receive an unwanted Selection, you may return it at Club expense.
- Personal service for your account—no computers used!
- To complete your Trial Membership, you need buy only four additional monthly selections or alternates during the next 12 months. You may cancel your Membership any time after you purchase these four books.
- All books—including the Introductory Offer—are fully returnable after 10 days if you're not completely satisfied.
- All books are offered at low Member prices plus a small postage and handling charge. Prepaid orders shipped postpaid.
- Continuing Bonus: If you continue after this Trial Membership, you will earn a Dividend Certificate for every book you purchase. Three Certificates, plus payment of the nominal sum of \$1.99 will entitle you to a valuable Book Dividend of your choice which you may choose from a list provided Members.

ELECTRONICS BOOK CLUB

P.O. Box 10
Blue Ridge Summit, Pa., 17214

Please open my Trial Membership in ELECTRONICS BOOK CLUB and send my 3-volume Electronics Library, invoicing me for only \$1.99 plus shipping. If not delighted, I may return the books within 10 days and owe nothing, and have my Trial Membership cancelled. I agree to purchase at least four additional books during the next 12 months, after which I may cancel my Membership at any time.

Name _____ Phone _____

Address _____

City _____

State _____ Zip _____

(This offer valid for new Members only. Foreign and Canada add 10%.) RE-116

CIRCLE 16 ON FREE INFORMATION CARD

the gift everybody loves...
new wireless remote control car



Here is a gift that will always please, exciting sports car action for all ages, the BCM-100. From up to 300 feet away you can race this car in any room, on sidewalks or driveways... steering it left or right... stop it, send it in reverse and forward again. The BCM-100 is more than a toy... both car and remote control have rugged, sophisticated circuits that rival highly developed commercial devices. Battery-powered safe for everyone to operate. Control circuitry includes 37 transistors 8 diodes and 1 crystal. Suggested retail per set \$59.95... Now for Christmas only \$49.95PPD. (Less batteries)

eic EASTERN INDUSTRIAL CORP. INC.

1380 Jarvis Ave., Elk Grove Village, Ill. 60007 (312) 640-8737

- Send details and literature
 Send _____ BCM-100 sets at \$49.95
 Ck. or MO enclosed. Send C.O.D. Ill. residents add 5%.

30 day guarantee on all parts and labor.

Name _____
 Address _____
 City _____
 State _____ Zip _____

(Dealer Inquiries Invited)

CIRCLE 72 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 34

is a complex, accurate instrument in an unbelievably small box. It is the FM-7 Frequency Meter manufactured by Non-Linear Systems, Inc. (Just when I was getting used to saying "frequency counter" they call this one a frequency meter.)

The whole instrument measures only 1.9 x 2.7 inches, and 4 inches deep. The panel has one BNC connector and a two-position switch; that's all. The top half of the panel is a nice-sized LED readout with seven digits. This small size includes the self-contained batteries that are rechargeable.

They've taken full advantage of the space saving possibilities of integrated circuits, of course. The model FM-7 is a direct counter. The preamp circuitry conditions the input signal, amplifies it and then counts the input pulses for 1 second and displays the result for 1 second. This results in a display that is updated every two seconds. The display is multiplexed (each digit is scanned) which reduces power drain. The scan rate is fast enough so that there is no perceptible flicker. A highly accurate 2.097152 MHz crystal oscillator is used as the timebase; this controls the counting and gating circuitry, even the 1-second gate.

The switch selects one of two ranges: 0-10 MHz that gives a 1-hertz resolution on the 7-digit display, and a full-scale range of 100 MHz that is usable to 60 MHz with a resolution of 10 Hz. This is well within the FCC standards for frequency measurement. Because of the use of the 7-digit display, the instrument can be calibrated to 0.00001% for a given temperature and battery voltage.

The instrument comes complete with a coaxial cable terminated in alligator clips, the NiCad batteries and the battery charger. Fully charged batteries will give continuous operation for two hours; it can be recharged completely in 14 hours. It can be operated from the AC line while the batteries are being charged. Overcharge protection is built in, so there is no chance of over-charging. In emergencies, the NiCad cells may be taken out and the unit operated from four standard AA cells. These cannot be "charged" of course. Battery replacement is very simple; the back cover of the case snaps off and the works slide out so that you can get to the batteries.

For calibration testing, the display can be checked against a frequency standard. If the readout is not accurate to one part in 10⁷, it can be adjusted: There is a trimmer capacitor that is accessible by taking off the back cover. Calibration should always be made with the batteries fully charged. Temperature stability is given as ± 10 PPM (parts-per-million) from 0°C to 40°C. The accuracy is ± 1 count ± timebase accuracy.

The sensitivity of the model FM-7 is good. In fact, you can make frequency readings—for example, on CB radios—by simply wrapping the red lead of the input cable around the coax where it comes out of the CB case. There's enough RF leakage in a typical coax so that you get plenty of signal. To read the RF from the antenna, clip a short piece of wire in the red clip, about 8 inches long, and hold it up parallel with the antenna rod. I tried this both ways and they're right—it works!

continued on page 38

TEST SEMICONDUCTORS ANYWHERE

Portable, in-circuit tester for all bipolar transistors, Darlingtons, FETs, SCRs



B&K-PRECISION MODEL 510 \$90

- Combines Dynapeak™ testing method with HI/LO power drive
- Tests semiconductors and identifies all leads; base, emitter, collector in LO drive
- Provides GOOD/BAD indicator in circuits with shunt resistance as low as 10Ω; shunt capacitance up to 25 μF, in HI drive
- Test performed as quickly as one can turn the switch
- Measures 6 5/8" x 3 3/4" x 1 3/4"
- Weighs 1/2 pound, less four "AA" batteries
- Price includes test clips and carrying case
- Available from local B&K-PRECISION distributors

B&K PRECISION

PRODUCTS OF DYNASCAN

6460 West Cortland Avenue Chicago, Illinois 60635 • 312/889-9087

In Canada: Atlas Electronics, Toronto

CIRCLE 85 ON FREE INFORMATION CARD

LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

A BETTER LIFE STARTS HERE

SAVE 50%!

8 X 20 MONOCULAR


Fantastic bargain! Top quality Spy Scope, a \$30 value, now offered at \$14.95! Our special purchase saves you 50% and you get 100% coated optics: 393 ft. field of view. Only 2 oz.—stores in pocket, purse, glove compartment. Fits in your palm—peer into hard-to-see places without letting subject know you're spying. Great for birders and race fans; incl. neck strap, leatherette 3½x1½x2" case. Beautiful brushed metal finish. Buy two—one for a gift!



Stock No. 1568EH \$14.95 Ppd.

SEE MUSIC IN PULSATING COLOR

New 3-Channel Color Organ adds to music listening pleasure. Lets you modulate 3 independent strings of colored lamps with intensity of your music to create an audio "light show." They flash, vary in brightness related to music's rhythm, pitch, volume—pulsating lighting performance to music! Fully assembled & priced half that of others, the Edmund Sound To Light Control is a terrific value. Plug in, turn on!

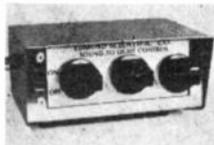

No. 42,309 EH (ASSEMBLED) \$17.95 Ppd.
No. 42,336 EH (UNASSEMBLED) \$13.95 Ppd.

AN ALPHA MONITOR FOR \$34.95?

Yes, because you built it! Use your ability to tune in your brainwaves, an aid to relaxation, concentration. Kit incl. everything you need (except 9v trans. batt.) to own a portable self-cont. BIOFEEDBACK unit for a pittance: steth. earphones, electrode headband, solid-state circuitry; 5 microvolt sensitivity, more! Compl. assembly instructions & op. manual. With basic electronics knowledge, you can do it!



No. 61,069 EH (KIT) \$34.95 Ppd.
No. 71,809 EH (FULLY ASSEMBLED) \$55.00 Ppd.

¼" ASTRONOMICAL TELESCOPE

See moon craters, rings of Saturn, double stars. New equatorial mount. f/10, ¼ wave mirror (Pyrex®). Gives theoretical limit of resolution. Rack & pinion focusing. Aluminum tube, 6X finder. 1" F.L. 45X Kellner achromatic eyepiece and Barlow lens to double & triple power up to 135X. Free Star Chart plus 2 Books. Stock No. 85,105EH... (Shipping Wt. 42 lbs.) \$159.50 FOB
4¼" WITH CLOCK DRIVE #85,107EH \$199.50 FOB
6" REFLECTOR TELESCOPE (48X to 360X) #85,187EH \$249.50 FOB
6" WITH CLOCK DRIVE #85,086EH \$285.00 FOB
3" DELUXE REFLECTOR (30 to 90X) #80,162EH \$ 89.95 Ppd.
STANDARD 3" REFLECTOR #85,240EH \$ 59.95 Ppd.



GREAT FOR CHRISTMAS GIFTS! A UNIQUE SELECTION OF MEMORABLE, LONG-LASTING GIFTS FOR ALL AGES.


LOW COST PORTABLE INFRA-RED EYE



For infra-red crime detection surveillance, security system alignment, I.R. detection, laser checking, nite wildlife study, any work req. I.R. detection & conversion to visible spectrum. Self-cont. scope incl. I.R. light

source (90' nite vision!), 6032 I.R. converter tube, f/3.5 obj. lens, adjust. triplet eyepiece, auto lighter adapter. 1.6X, focuses 10' to inf.; 6, 12v DC. Not avail. to CA res. exc. authd. pers./sci., educ.
No. 1683EH (11x14¼ x 3") \$299.95 Ppd.
BINOCULAR STYLE: AS ABOVE, BUT 2.5X
No. 1685EH (SUPER BRIGHT I.R. EYE) \$329.95 Ppd.

CAN'T SLEEP, RELAX? TRY THIS!

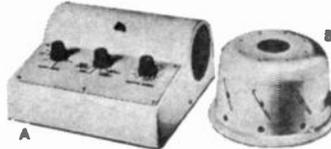

Electronic sound conditioner simulates 4 kinds of soothing sounds of ocean surf and rain. "White sound" helps mask unwanted noise, adds restful, intriguing background sound. Program the solid state unit to your own need: 2 surf, 2 rain; or "white sound". Proven by medical tests to have analgesic effects. Great for meditation, restlessness, sleeplessness psychology.
(A)-No. 71,997EH (7¼x7x3½") 110V AC \$79.95 Ppd.
(B)-AS ABOVE, BUT "WHITE SOUND" ONLY
No. 71,980EH (6" Rd.x3½" H) \$28.00 Ppd.

PRO ELECTRONIC SOUND CATCHER



Parabolic mike w/18¼" transparent reflecting shield & 2 I.C.'s in amplifier magnifies signals 100x that of omni-direction mikes. Catch sounds never before heard! Highest signal to noise ratio poss. Earphones, tape recorder output, trans. batt. (not incl.).

tripod socket; req. two 9V
No. 1649EH (5½ LB.) \$299.00 Ppd.
LOW COST MODEL: NO EARPHONES, ELECTR. CIRC.
No. 1665EH \$149.95 Ppd.
LOWER SENSITIVITY ECON. MOD. W/O ELECTR.
No. 80,242EH \$89.50 Ppd.

LEARN HOW TO RELAX BETTER!



New inexpensive biofeedback monitoring device helps you learn tension reduction techniques w/o electrode headbands, messy creams. Designed by clinical psychologists working in the stress reduction field, this handsome Executive Galvanic Skin Response

Meter features solid-state electronics for great sensitivity, compactness, dependability Walnut & gold-plated brass case. Uses 9v batt. (incl). Learn to take a 10-minute "vacation" at your desk!
No. 42,393EH (2½ x 4 x 1½") \$55.00 Ppd.

KNCW YOUR ALPHA FROM THETA!



For greater relaxation, concentration, monitor your Alpha/Theta brainwaves w/ audible or visible signal on Biosone II. Has 3 feedback modes, outputs to monitor logic signal, filter sel. feedback, broad sensitivity control; other professional feats. of \$200-up units. Easily operated 4-lb. portable has total brainwave monitoring capability! Req. 2 9v tr. batteries.

No. 1668EH (9½x5½x4¼") \$149.95 Ppd.
LOW COST STARTERS' UNIT (PORTABLE)
No. 71,809EH (4½x2¼x4¼") \$ 55.00 Ppd.

MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN 4500 UNUSUAL BARGAINS

Completely new 1977 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.
300 Edscorp Building, Barrington, N.J. 08007
Please rush Free Giant Catalog "EH".

Name _____
Address _____
City _____ State _____ Zip _____



COMPLETE AND MAIL WITH CHECK, M. O. OR CHARGE NO. EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

PLEASE SEND GIANT FREE CATALOG "EH"

Charge my American Exp BankAmericard Master Chg

Interbank No. _____

My Card No. Is _____

Card Expiration Date _____

30-DAY MONEY-BACK GUARANTEE.
You must be satisfied or return any purchase in 30 days for full refund.

How Many Stock No. _____

Description	Price Each	Total

Add Handling Charge \$1.00

I enclose check money order for TOTAL \$ _____

Signature _____

Name _____

Address _____

City _____ State _____ Zip _____

CIRCLE 21 ON FREE INFORMATION CARD

We checked the model FM-7 against a couple of other frequency counters that were much larger and more expensive, and it was right on the button. For mobile two-way radio (up to the high bands), CB radio and low-frequency aircraft radio, this compact little instrument can be very handy. The small size makes it very easy to use when working on mobile units, and in tight places.

They send along an instruction manual with full data for calibrating, checking batteries and so on. They also have Application Note No. 1 that gives a good deal of

plain-language data on frequency testing.

For frequency testing in the 25-50-MHz band, the FCC requires that the transmitter be held to a tolerance of 0.002%. The frequency-measuring instrument must be capable of ten-times better accuracy, or reading within 0.0002%. This means 30-Hz resolution at 60 MHz where the tolerance is 0.00005%. The FM-7 can be calibrated and certified to have accuracy of ± 10 Hz at 60 MHz. The stability with changing battery voltages is 0.0002% from 4.5 volts to 6.5 volts, which is 120 Hz—better than FCC standards. Below 50 MHz, it is quite a bit better than the required accuracy.

The price of the model FM-7 is as \$195.00, complete with cable and battery charging unit. **R-E**

Manufacturers feeling effect of in-warranty rates suit

At least one manufacturer has complained publicly about the side-effects of the current industry-supported struggle spearheaded by Electro-TV of California, in a lawsuit brought against 10 major TV manufacturers (Radio-Electronics, May 1976, page 12). The suit attempts to force them to cease violating California law by soliciting service repair work below cost. In an answer to the suit, Sylvania incorporated the statement:

"Sylvania has been compelled to pay higher rates to television and repair agencies than it otherwise would have paid." The statement went on to admit that the plaintiff (Electro-TV) had disrupted economic relationships between Sylvania and repair service agencies, and that this damaged Sylvania by denying it "the future economic benefits expected to flow therefrom." (Presumably some of the benefits have been diverted to the "service agencies.")

The Scanner, official publication of the Arizona State Electronics Association (ASEA), from whom we got this news, points out that: "Although Sylvania has not had all the profits it 'expected,' it should be noted that the service industry has not been seeking warranty profits. Rather, it has been the effort of the trade associations to save their members from losing money and losing their businesses," through servicing below cost.

The Scanner goes on: "Sylvania is still holding out a threat of countersuit, so keep the SIS contributions coming. Mail them to M. L. Finneburgh, The Finney Co., 34 W. Interstate St., Bedford, OH 44146, attention Electro-TV SIS Fund."

A contribution to this cause might be a worthwhile investment; the knowledge that an industry group has resources can be a deterrent to any contemplated counter-suit.

Satellites permit savings on business communications

RCA has instituted a new service that offers businesses the advantages of 24-hour-a-day private-line service but will be charged principally on a usage basis. The rate structure of the "Instant Private Network" is made possible by using Satcom I and II synchronous orbiting satellites. Each satellite has 24 communication channels, each channel is designed for 1,000 voice-grade circuits.

Normally a company's private line—permanently connected between two specific points—is charged for on a 24-hour basis, though generally used only during the regular daytime business hours. The Instant Private Line is a pool of trunk lines, one of which is brought into service at any time by the user, who cannot distinguish any difference between it and a conventional private line.

Each subscriber pays a \$100 installation charge and a fixed monthly switch termination charge of \$50, a local channel charge and a charge of three cents for each six-second period of satellite usage. The usage charge drops to 2.7 cents per six-second increment for the next 30 minutes, and to 2.5 cents after the first 90 minutes. Weekend rates are lower. **R-E**

SPECIAL OFFER!

Buy 23-channel CB now. Get new 40-channel later at 1/2 price!

UPON FCC TYPE ACCEPTANCE

"Don't be without CB while waitin' for the FCC"

NO MODIFICATION FEES—NO MODIFICATION DELAYS—OWN AND KEEP TWO UNITS




handic®

handic USA, Inc., 14560 NW 60th Ave., Miami Lakes, FL 33014

THE ORANGE EQUIPMENT KNOWN FOR PROFESSIONAL QUALITY THE WORLD OVER

CIRCLE 34 ON FREE INFORMATION CARD

The Black Watch Kit \$19.95

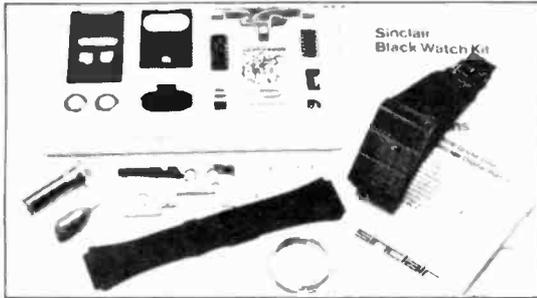

THE KIT CONTAINS

1. printed circuit boards
2. integrated circuits
3. encapsulated quartz crystals
4. trimmers
5. capacitors
6. LED displays
7. 2-part case with window in positions
8. batteries
9. battery-clip
10. black strap (black stainless-steel bracelet optional extra — see order form.)
11. full instructions for building and use.

All you provide is a fine soldering iron and a pair of cutters.


The Black Watch Kit by Sinclair is unique. Controlled by a quartz crystal... powered by two hearing aid batteries. Styled in understated elegance the Sinclair way. No knobs no buttons. To see the exact time or date just touch the face of the case. A re-set control is on the back.

Dimensions: 1-1/2" X 1" X 3/10"
 Weight: 1/2 ounce
 Strap: 3/4" wide
 Case: Specially designed unbreakable black matte plastic. Water resistant.
 Batteries: Mallory RM41H
 Accuracy: On a built watch we guarantee accuracy within a second a day. In building it yourself you may be able to adjust the trimmer to achieve an accuracy within a second a week.



sinclair (Actual Size)

Scientific Calculator Kit \$14.95

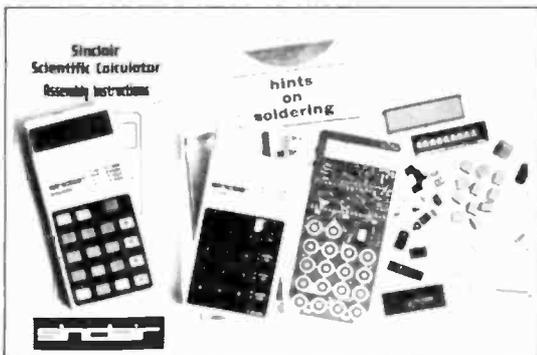

KIT COMPONENTS

1. Coil
2. LSI chip
3. Interface chips
4. Printed circuit board
5. Keyboard panel
6. Electronic components pack
7. Battery assembly and on/off switch
8. Case moldings, with buttons windows and light-up/display in position. Soft carrying case
9. Comprehensive instructions
10. Assemble time is approximately 3 hours.

Designing the Sinclair Scientific was no small feat of engineering, but you don't have to be an engineer to assemble it with our kit.

You can put together the world's most remarkable scientific calculator from eight groups of components, using only a soldering iron and a pair of cutters. (Complete instructions are included.) Less than 3/4-inch thin and 3-3/4 ounces light. British-made Sinclair Scientific isn't just portable, it's pocketable.

All parts are tested before shipment — and we guarantee any correctly assembled calculator for one year.

1. **FREE TRIAL OFFER** If you decide not to keep and assemble your kit, you may return it undamaged within 10 days for a refund of its purchase price.

2. **SERVICE** If a problem arises in building your kit, Sinclair Service Department will fix it for you at a nominal charge.

Features of the Sinclair Scientific

FUNCTIONS SUMMARY —

Algebraic logic
 Five function memory
 Sine, cosine, tangent, arcsine, arccosine, arctangent
 Degrees/radians switch
 Ln and e^x
 Square root, pi and reciprocal
 8 digit mantissa, plus 2 digit exponent
 Automatic constant
 Pocket-sized. 4-1/3" X 2" X 11/16".
 Weight: 4 ounces.
 Battery life. Low-cost, disposable AAA batteries (not included) operate for around 25 hours of continuous use.

3. **WARRANTY** Your correctly assembled kit will be repaired or replaced by Sinclair if it fails to operate within one year of purchase free of charge (except in the case of misuse).

4. To order your kit, just use the coupon and mail it with your check or money order to: GFN Industries, Inc., 6 Commercial Street, Hicksville, New York 11801.

To: GFN INDUSTRIES, INC., 6 Commercial Street, Hicksville, New York 11801

Black Watch Kit(s) at \$19.95 \$ _____
 Black Watch Kit(s) with stainless steel band at \$24.95 \$ _____
 Scientific Calculator Kit(s) at \$14.95 \$ _____
 Assembled Black Watch(es) with stainless steel band at \$39.95 \$ _____
 Assembled Scientific Calculator(s) at \$19.95 \$ _____
 Sales Tax (N.Y. Residents) \$ _____
 Shipping and handling (\$2.00 PER UNIT) \$ _____
 Enclosed is check/MO (payable to GFN Industries Inc.)
 TOTAL \$ _____

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

Quantity discount: For 6 or more units, the total shipping and handling charge is \$6.00.

RE-10W

CB Roundup

New and Unusual Accessories


NO MATTER WHAT OUR FIELDS OF EMPLOYMENT OR OUR HOBBIES may be, there will always be accessories available to simplify and expand the scope of our activities and to enable us to obtain more pleasure from them. Presently, this applies more to CB radio than to any other activity. There are a huge number of different types of devices and accessories available to the CB operator. To list all types and models of all devices and accessories that are possible additions to the basic transceiver/antenna combination would be impossible.

Security

Any means that can be used to protect a CB radio and antenna against malicious damage and theft are prime considerations for the CB operator. This includes alarms and locks, various quick-release devices for rapid removal of the transceiver and antenna from the car and also various devices that help conceal the fact that your car is CB equipped.

A standard CB antenna is a sure tip to the rip-off artist that your car has a CB radio. Disguise or remove your antenna and you lessen the chance that your car will be a target for a thief. You can do this with one of the following devices:


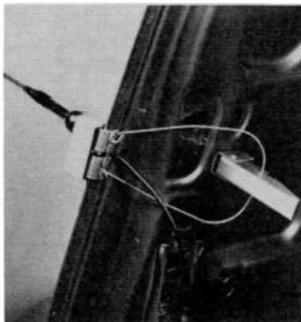
The **Foiler** converts your existing antenna and trunk-lip mount so the antenna can be removed and stowed in the trunk in a



matter of seconds. Mounts the antenna on the front edge or side lip of the trunk lid. \$4.95.—SouthCom, Inc.

Stowit is a unique antenna mount providing a quick and

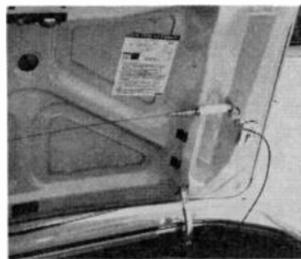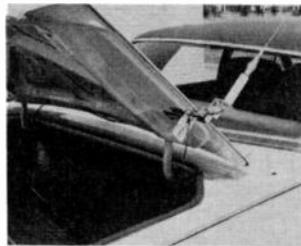easy method of concealing a CB antenna in the trunk of a car. Applicable to either a trunk-mount or roof-mount antenna. One photo shows the antenna in




its normal position on the trunk lid and the other shows it folded to the underside of the trunk lid.—Holly Enterprises.

Quick-release mounts, models M-450 and M-460, are two quick-release accessories that allow fast, temporary removal of mobile CB antennas to prevent theft or damage. The *model M-460* uses a combination lock on the antenna collar to discourage theft. The locking collar and base insert between the antenna's coil and mount; permitting only the user to remove the loading coil and whip. The quick-release allows temporary disassembly to prevent damage

from automatic car washes.

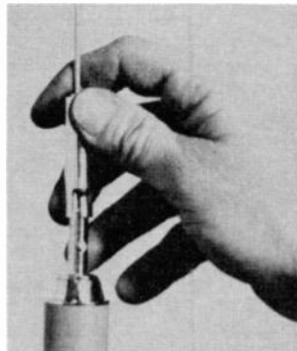
The *model M-450* is a quick-release kit that allows the whip to be removed from a base-loaded antenna for protection in car washes. A downward push and twist on the new knurled adapter releases the antenna's



whip from the base. Kit includes adapter, Allen wrench and whip trimming instructions. *Model M-460*, \$16.95; *model M-450*, \$4.25.—Antenna Specialists Co.

Electric antenna, model CBE-10, is designed for fender mounting. With a flick of a switch, the antenna extends to its full length and turns on the radio automati-

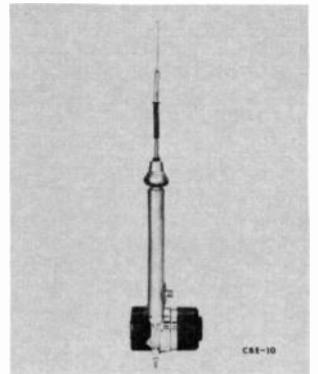cally. Another flick of the switch and it disappears into the fender, turning off the radio. The *CBE-10* (shown in the photograph) consists of approximately 31-



inches of chrome-plated stainless-steel telescoping mast with 18 feet of coaxial cable. Retracts into the fender well to within 3 inches of the mounting surface. The preferred location is in the left rear fender. Center loaded. SWR 1.3:1. \$64.95.—Tenna Corp.

Pro-Elec-Tele-Tenna, model VE-027-FR (not shown), at the flick of a switch extends to a 5-section stainless-steel 48-inch antenna in 5 seconds. Impedance 50 ohms. SWR 2.0:1. Supplied with RG-58/U and PL-259 connector and extension cables for either front or rear mounting. \$89.50.—Valor Enterprises, Inc.

Electric AM/FM/CB antenna, model EMA-100 (not shown), that disappears into the fender of a passenger car or light truck when not in use. It replaces the existing AM or AM/FM radio antenna or can be mounted inde-

A look at a few of the new and unusual CB accessories that you can add to the basic transceiver and antenna

ROBERT F. SCOTT
TECHNICAL EDITOR

pendently in the front or rear fender of virtually any car or truck. The coil of this top-loaded antenna is connected directly to the output of the radio at all times; even when the coil is retracted into the fender. This precludes the possibility of damage to the transceiver if the mike is keyed into an open circuit of an antenna not fully extended or coupled. The SWR is 1.5:1 or better when fully extended and 3.0:1 when fully retracted into the fender. Depth of space required in fender well is 19 inches. Bandwidth is 26.5 to 27.5 MHz. The *EMA-100* incorporates a relay that can be connected to any convenient circuit such as the CB radio to allow automatic extension when the radio is turned on and automatic retraction when the set is turned off. \$69.95.—CPD Industries, Inc.

Low-Profile Anti-Rip-Off, model *GPL-69*, is an antenna tuner that permits the standard AM or AM/FM radio antenna to be used for CB as well. It mounts under the dash in a convenient location and has a directional coupler to facilitate tuning. Just key the mike and adjust the tuning controls for




maximum brightness in the green indicator and minimum intensity in the red indicator. If someone changes the height of your broadcast antenna, the red indicator lights so you'll know to check the antenna height. Or, if it is more convenient, to readjust the tuning controls for the new antenna height.

The *GPL-69* includes a TVI-suppression filter and a circuit that protects your radio and isolates it from the full CB power output if a critical component fails. With the *GPL-69*, the

average car radio antenna gives performance roughly equivalent to a gutter-mount antenna.—Glatzer Industries Corp.

Antenna converter, model *210* (not shown), matches a CB transceiver to a car's broadcast radio antenna. A tuning set-screw enables you to adjust the matching network for the lowest SWR. An indicator light provides assurance of correct tuning. Measures $3\frac{1}{2} \times 2\frac{3}{4} \times 1\frac{1}{2}$ inches.—Lake Electronics, Inc.

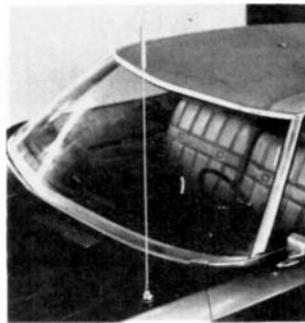AM/FM/CB Antennas, models *M-267* and *M-264*. The *M-267* installs easily in the space that AM or AM/FM antennas occupy on the cowl of a car. Center-loaded 46-inch stainless-steel whip fits any existing $\frac{7}{16}$ -inch to $\frac{15}{16}$ -inch mounting hole.



Coax phasing harness comes with all connectors attached. It permits an exact match to both radio systems.

The model *M-264* AM/FM/CB *Disguise Antenna* (not shown) hides the fact that you have a CB radio in your car. Detachable 40-inch stainless-steel whip looks like normal cowl-mounted AM/FM antenna. Fits $\frac{15}{16}$ -inch mounting hole and includes adapter for mounting in holes up to $1\frac{1}{4}$ inches. Includes coupler that permits you to operate AM or AM/FM radio along with CB rig.—The Antenna Specialists

If you plan a permanent or semi-permanent installation in your vehicle, protect it with the most secure and substantial mounting hardware you can

find. If you decide on a slide mount, select one with a cylinder-type lock. If you opt for the standard hanger brackets, consider the security offered by some models that come with a pair of cylinder locks instead of the two knurled thumb screws that fasten the bracket to the sides of the radio.

Another means of providing maximum security along with ease of portability is the use of the new *Brammall Barrels* as part of the installation hardware. Mounting screws pass through the barrels or lock bodies—cylinders with a hole just large enough to pass the shank of the mounting screw at one end and threads to engage a cylinder lock at the other—into the dashboard or the sides of the CB radio case. Figures 1 and 2 show how

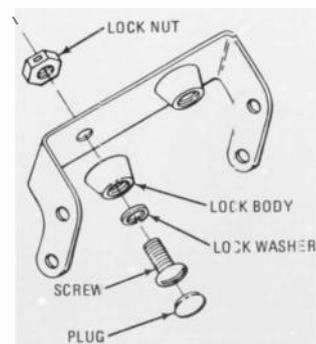


Fig. 1

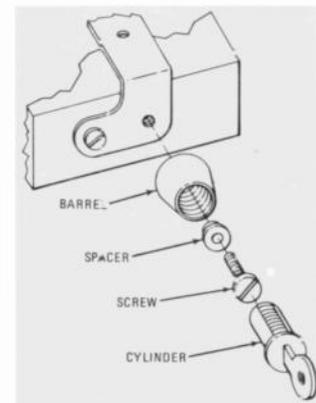


Fig. 2

Brammall Barrels are used.

When fastening mounting brackets to the dash, the screw heads are made inaccessible to plugs hammered into the threaded ends of the barrels as shown in Fig. 1. The CB set—or tape player or radio—is fastened to the hanger bracket with ordinary mounting screws whose heads are protected by lock-in plugs as in Fig. 2. The plugs can be removed with keys to provide easy access to the mounting screws. The radio can then be removed from the vehicle for maximum security.



The *Brammall Barrel* kit comes with all necessary hardware and a warning sticker to paste on the inside of one of the car's windows. The kit is \$9.95.

If you must leave your car for long periods in unattended parking lots, you are advised to protect your radio with a good alarm system or remove the set and take it with you. In any event, here are several items to consider:

CB-Saver is a storage and travel case for CB radios. It is a



tough, attractive, molded case with a foam cushion interior that can be custom fitted for most CB radios measuring up to 3 x 9 x 12 inches.—Falcon Enterprises, Inc.

CB-Porta-Protector is made in three sizes: the basic 12 x 7 x 4-inch model being the most popular. Body material, includ-



ing the carrying strap, are 39-ounce expanded vinyl with cotton lining.—Andor Corp.

The Nailer is a protective device for CB radios and CB antennas that is hooked up to the car's horn or an auxiliary alarm system. If a thief tries to remove



either the radio or antenna and breaks a ground wire or removes the PL-259 connector from the set, the alarm will automatically sound. The Nailer works off the car's 12-volt battery and can be installed in a matter of minutes. \$29.95.—Valor Enterprises

Radio-Sentry CB Theft Alarm can guard two units such as the CB radio and a tape player. Tampering with or removing either device activates a solid-state sensor that sets off the



alarm. Options include a siren and an expanded sensor that will operate as a vehicle burglar alarm in addition to providing CB protection. Basic Radio Sentry is \$13.95, siren \$14.50, expanded anti-theft alarm \$19.95.—Electronic Specialists

Self-contained alarm system, model CR10-33, for installations



where no alarm is presently in operation. It emits a 100-dB signal the instant that an unattended CB radio is touched. The unit operates on a 9-volt transistor battery and can be concealed under the dash. Installation does not require a connection to the car's electrical system. Comes with sensor tape and interconnecting wire. \$29.95.—The Magitran Co.

Convenience

Any device that increases the versatility, efficiency and operating ease is a worthwhile addition to any CB installation. There are a number of new "convenience" accessories that you welcome as adjuncts to your station. Dollars to doughnuts; you'll select a few of these for your Christmas shopping list.

Channel Monitor, model CM-2, operates in conjunction with the automobile radio and your CB transceiver. When a CB call is received, the car radio cuts out so the call can be heard. After a short delay, following the call, the car radio returns to normal



operation. The CM-2 is sensitive to both audio and RF so it will also silence when you transmit.

It operates with any car radio that has an external speaker, and any CB, ham or marine radio that is equipped with an external speaker jack. Equipped with all necessary mounting hardware, installation instructions and details on modifying equipment that does not have the necessary "plug-in-and-play" connections. \$29.95.—FICO Electronic Instrument Co.

Solid-state Killer switching system permits hands-free operation of both the broadcast radio and CB transceiver in a car. When a CB call is received, the



Killer immediately switches the car's speakers from the broadcast radio to the CB rig. The device is also actuated whenever the mike is keyed. A short time-delay on drop-out prevents switching back and forth between words and sentences.

The Killer operates with almost all types of two-way radio systems, monitor receivers, scanners, etc., and will control most audio sources such as AM/FM radios, tape players, etc. Works on both mono and stereo audio systems. Installation does not require opening either radio. \$39.95.—Rogers Electro-Matics, Inc.

CB Boom Mike Headset, model CB-88, features a noise-cancelling power microphone that delivers clear, crisp speech even in a moving vehicle where wind, traffic and engine noises normally interfere with the transmission. The mike has a variable-gain amplifier and is mounted on a pivoting boom so



that it can be close to the lips and moved aside when not in use. The push-to-talk switch has a clip for convenient attachment to a shirt or blouse.

Can be used with either the right or left ear and, if desired, can be worn without the headset. An adapter is furnished which allows the ear-piece to be clipped to the user's eyeglasses. Less than \$70.00.—Telex Communications, Inc.

Mobile headphone, model CR10-2SMD, has a noise-cancelling boom mike with a remote push-to-talk button that mounts quickly on the turn-signal or gear-shift levers. The unit includes a 500-ohm microphone with an adjustable noise-cancelling feature. The headphone has



a built-in automatic gain control that prevents ear "blasting" or overload from nearby transceivers. \$45.00.

The model CB10-2SVX

(not shown) is similar to the CB10-2SMD except that it includes a VOX circuit that automatically keys the mike at the sound of the operator's voice—allowing completely hands-free operation. \$100.00.—Suprex Electronics Corp.

CB Caddy is both an anti-theft device and a convenient mounting complete with a built-in 4-inch 8-ohm speaker that rests on the transmission hump, floor or seat of nearly any vehicle. It is adjustable to fit various shapes of mounting surfaces. Made of high-impact molded ABS plastic.



The Caddy adjusts to hold most CB radios up to 3 x 8 1/2 x 8 1/2 inches. Once the radio is clamped in place on the shock-resistant foam, only the 12-volt DC and antenna connections are required for installation. Compact and light weight, the Caddy stores easily in the trunk or can be carried anywhere with the convenient retractable handle.—Falcon Enterprises, Inc.

CB mounts, Ten-Two and Good Buddy, have all the features vital to safe and efficient operation of CB radios. Radios can be quickly and easily detached. There is nothing to unplug—antenna, power and speaker cables are wired through contacts in the mount. Controls and mike are easily reached and visible from the normal driving position. Each mount has a communications-type speaker that improves sound quality and filters out noise. Both mounts are positioned so sound is directed toward the driver and mount securely to the roof or transmission hump.

The Ten Two (shown) is made of textured 1/4-inch ABS plastic with a matte finish that complements the car's interior. It is 5 1/2-inches high, 6 1/4-inches wide and 9 1/2-inches deep. The detachable




mike-mount section is inverted when the Ten-Two is roof mounted. The transceiver is fas-

tened to the mount through a slide connector. \$29.95 with antenna connector and \$24.95 without.

The *Good Buddy* model (not shown) is made of heavy scuff-resistant wood-grain vinyl over 1/8-inch particle board. Measures 5 1/4-inches high, 7 1/4-inches wide and 10-inches deep. \$34.95 with antenna connector, \$29.95 without.—Gamber-Johnson, Inc.

CB mount, Port-A-Mount 302. is a completely portable flat-based mounting unit designed for use in cab-over trucks, vans and recreational vehicles and cars without transmission humps. Mounts without drilling. Velcro fasteners securely adhere to carpeted surfaces. Mating self-adhesive Velcro fasteners furnished for surfaces without carpeting. Tilted surface design permits ready access to controls and limits sound dispersion from the built-in auxiliary speaker.—SMA Products, Inc.

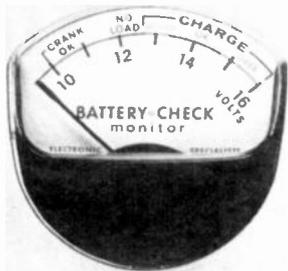Battery Check continuously monitors battery, charging system and electrical loads in vehicles equipped with 12-volt electrical systems. Maximum CB-range and trouble-free operation requires that the car's battery and electrical system be in top-notch condition. The *Battery*



Check, with its expanded-scale meter with its red and green "status bands" provides high accuracy and easy reading. Checks the electrical system when cranking, with no load and when charging. \$39.95 to \$45.95, depending on model and finish.

Flash-Cube CB transmitter monitor has LED's that form a light bar "meter" that glows as transmitter power is applied. The



LED's flash to show modulation. Has a detachable mount and can be used mobile or base. \$25.95—Electronic Specialists.

Regulated power-supply, model VRPS-6. is designed to give maximum performance from mobile CB radios when used at



home or office. It has an output of 6.0 amperes. Comes complete with input power cord, switch, pilot light and operating instructions. Power input 120-VAC 60-Hz; output 13.8 VDC.—Valor Enterprises.

CB power supply, model 138A3. lets you operate a mobile CB transceiver, tape deck and other auto electronic devices from 117-VAC sources. The output is 13.8-volts 3-amps. The



voltage regulation is such that no-load to full-load results in a change of only 0.05 volt. Typical ripple is 2 to 5 mV P-P. Output is short-circuit protected by current limiting. Current is limited to 3.5 to 4 amps. \$49.88—E & G Research and Manufacturing, Inc.

Power supply, model AD-112. is designed to power mobile CB transceivers and other mobile electronic devices. Equipped



with lever-type on-off switch and LED power indicator. 5 1/2-inches wide, 3-inches high, 6 1/2-inches deep.—Sharp Electronics Corp.

Antenna Matcher, model CBM-4. is an antenna matching device designed for the Citizens



band. Most transceivers operate into 50-ohm loads, delivering maximum power with minimum distortion and harmonic radiation. A mismatch between antenna and transceiver occurs because the antenna impedance varies widely with frequency and physical location. The *Antenna Matcher* assures that the transceiver will be matched to the antenna at any time and on any channel with minimum harmonic radiation. Matches radio to antenna impedances of 35 to 150 ohms. Fitted with SO-239 connectors.

The *LP-7* low-pass filter is inserted between the output of the CB transceiver and the transmission line to attenuate the



TVI-producing harmonics that are produced by many radios. The cutoff frequency is 30 MHz. Impedance is 50 ohms. Maximum SWR is less than 1.2:1 at 27 MHz.—Siltronix

CB Receive Signal Preamp, model VRSC-115. is designed to provide a gain on weak received signals and attenuate loud received signals to a desired level. It lets you receive weak signals with an additional gain of +15 dB and lets you attenuate loud



signals as much as -20 dB on all CB channels. Has bracket for under-dash mounting. Front panel includes GAIN/ATTENUATE control, power indicator light and transmit indicator light. \$39.95—Valor Enterprises, Inc.

CB Range Controller, model CRC-11. is designed as the answer to crowded CB channels in metropolitan areas and the need for close-range private communications on CB. It independently controls the receive range and the transmit range of your CB set. It is essentially an adjustable linear RF attenuator with a solid-state transmit receive relay that insures full power output



when you transmit. In the receive mode, signals can be attenuated by as much as 50 dB, eliminating much of the cross-modulation and bleed-over and reducing the effective noise level.

The *GRC-11* has a privacy feature. When the mode switch is switched from NORMAL to PRIVATE, both transmit and receive signals are attenuated approximately 36 dB. This results in an effective range of approximately one-quarter mile. In this mode, you can have private, uninterrupted conversations with a friend traveling along with your convoy.—Glazer Industries Corp.

Mobile CB receive preamp, model LR-3. is a valuable adjunct to any CB communications system. It provides 20-dB voltage gain into 50 ohms. Connected in series between the antenna and



the receiver input, the LR-3 boosts received signals without in any way degrading the transmitted signal. A "sniffer" circuit senses the presence of transmitted RF signals and automatically causes the transmitted signal to bypass the receive preamplifier and be fed directly to the antenna.

Intended for negative-ground systems, the LR-3 operates from 12-volts DC so it is easily integrated into any mobile CB installation.—EICO Electronic Instrument Co.

RF preamplifier, model 3000. is a small "put it anywhere" device that brings in those weak signals.



Typical gain is 25-dB with only 1.5-dB noise gain. Bandwidth is 2 MHz. Features dual MOSFET design, polarity protection and measures only 1 1/4 x 3 1/4 x 2 inches.—Digital Sports Systems

Signal Hunter, model 1043. is a direction-finding antenna that tracks any signal without triangulation. Mounts on car in seconds for simple, fool-proof operation. In emergencies, find

lost or stranded motorists or boats in distress, day or night. Also useful in tracking down the source of interference from neon signs, leaky power-line insulators



and electrical machinery. Also useful to CB self-policing groups who want to locate illegal CB operators.

The 1094 portable CB antenna is a center-loaded antenna you can use at a base or other indoor installation where it is inconve-



nient to mount a regular outdoor antenna. This compact antenna simplifies carrying your mobile indoors to operate as a base.

Co-Phase Antenna Matcher, model 1098, tunes dual CB-antennas for lowest SWR without special harness. Length of cable from antennas to matcher is not critical. Correct co-phase



matching and low SWR contribute to more uniform coverage and increased antenna gain.

Twin-rig Transceiver Coupler, model 1075, is a line-splitter and



coupler that lets you hook up your main transceiver and a spare rig or receiver and work both off the same antenna. Impedance 50 ohms, frequency 11 to 65 MHz; insertion loss less than 0.5 dB.—**Gold Line**

Tools and test instruments


Installation aids and the proper tools are essential to a simple, attractive and efficient CB installation. Test instruments are vital when adjusting the transmitter and antenna for most efficient operation.

A field-strength meter is useful when tuning the antenna/transmitter combination for maximum signal output during the initial installation. Subsequently, it can be used to keep a constant check on transmitter performance.

Similarly, a SWR bridge or SWR meter is used to measure the degree of match between the transceiver and antenna and is a useful guide when positioning the antenna on the car and tuning it for best performance on the favorite channels.

The power-output meter or wattmeter is connected to the transmitter output as it feeds an antenna or dummy load. It reads the power leaving the transmitter but does not indicate possible losses due to transmission-line attenuation to a high SWR.

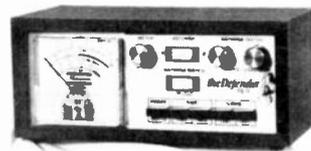Precision test console, Defender TS-1, provides for a constant control of SWR and a constant



check on power output and modulation. Includes an antenna tuner or matcher, and a switch to select either one of two antennas.—**Shakespeare Co.**

Long terminal stud, type 98-500, fits all standard side-terminal auto batteries and replacement cables. The extended length provides for easier

DIRECTORY OF MANUFACTURERS

Antenna Specialists Co.
12435 Euclid Ave.
Cleveland, OH 44106

Audnor Corp.
245 Old Meramac Station Road
Manchester, MO 63011

Brammall, Inc.
PO Box 208
Angola, IN 46703

CPD Industries, Inc.
2100 E. Wilshire Ave.
Santa Ana, CA 92705

Digital Sports Systems
PO Box 337
West Liberty, IA 52776

EICO Electronic Instrument Co.
283 Malta St.
Brooklyn, NY 11207

Electronic Specialists, Inc.
PO Box 122
Natick, MA 01760

Falcon Enterprises, Inc.
3960 S. Marginal Road
Cleveland, OH 44114

Gamber-Johnson Inc.
801 Francis St.
Stevens Point, WI 54481

Glazier Industries Corp.
268 Huguenot St.
New Rochelle, NY 10801

Gold Line
25 Van Zant St.
E. Norwalk, CT 06855

Holly Enterprises
PO Box 486
Addison, TX 75001

Kris Inc.
Pioneer Road
Cedarburg, WI 53012

Lake Electronics Inc.
1135 Greenridge Road
Buffalo Grove, IL 60090

The Magitran Co.
311 E. Park St.
Moonachie, NJ 07074

Rogers Electro-Matics, Inc.
PO Box 186
Syracuse, IN 46567

Shakespeare Co.
PO Box 246
Columbia, SC 29202

Sharp Electronics Corp.
PO Box 588
Paramus, NJ 07652

Silltronix—Cubic Corp.
269 Airport Road
Oceanside, CA 92054

SMA Products, Inc.
PO Box 152
Springfield, IL 62705

SouthCom, Inc.
PO Box 11212
Ft. Worth, TX 76109

Superex Electronics Corp.
151 Ludlow St.
Yonkers, NY 10705

Telex Communications, Inc.
9600 Aldrich Ave. South
Minneapolis, MN 55420

Tenna Corp.
19201 Cranwood Parkway
Cleveland, OH 44128


Valor Enterprises, Inc.
185 W. Hamilton St.
West Milton, OH 45383

booster-cable hook-ups and simplifies auxiliary power take-offs for accessories and tune-up ac-



cessories. Fits all GM cars from 1969 to date.—**Falcon Enterprises, Inc.**

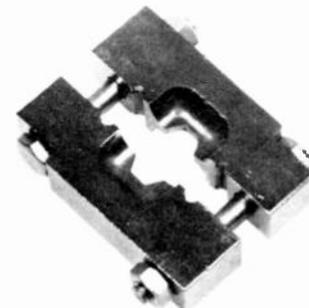Crimper, model 1100, for PL-259 connectors makes a no-solder connection that can withstand a 40-lb pull on the connector. With it, you can avoid taking a soldering iron to unusual



places such as to the top of a tower or on a rooftop.

Ground-strap kit, model 1095 (not shown), helps eliminate static caused by poor ground connections between engine and frame, body and frame, hood or deck and frame and other areas where a good metal-to-metal contact must be maintained.—**Gold Line.**

Coax switch, model 418-502, is an accessory for the operator using multiple antennas of multiple transceivers. The switch has three switch positions plus a 10-watt dummy load in the fourth



position. All input and output connectors are on the rear panel to facilitate a neat base or mobile installation. 3 1/2 x 8 1/4 x 4-inches. \$12.95.—**Kris Inc. R-E**

PART I. An in-depth look at digital multimeters—how they work, their specifications and applications



all about digital multimeters

CHARLES M. GILMORE*

THE CONCEPT OF THE DIGITAL VOLTMETER HAS been around for some time. Nonlinear Systems introduced the first digital voltmeter in the early 1950's. This unit would measure only DC voltages, used a combination of vacuum tubes and relays, was not exactly portable, and cost thousands of dollars. But it was a start. From that point to the mid 60's the instrument remained the laboratory digital voltmeter. Major changes were made in the accuracy, type of conversion (analog to digital) and resolution. Circuit components changed from vacuum tubes to discrete solid-state and then to integrated circuits.

The first units barely classified as portable and cost nearly one thousand dollars. But the advances were rapid. The DMM as we know it today was brought to the market in the early 70's. To date there has been a great race to see who could build the lowest-cost, most accurate, highest-volume instrument. The result is hundreds of thousands of these instruments for many applications—for the user, a real dream come true.

Theory of digital instruments

The vast majority of DMM's are of one type of analog-to-digital conversion: dual-slope. Other types have been used to construct digital voltmeters. The single-slope converter is used in very-low-cost instruments. Although not too common today, it does have some special characteristics that make it interesting, and numerous instruments in the field employ this technique.

The single-slope converter

The fundamental concept of the single-

* Manager Design Engineering, Heath Co., Benton Harbor, MI

slope converter is simple. It is to convert an unknown voltage to time. Time is chosen because simple digital counting circuits and an oscillator of known frequency may be used to display this time in a digital format. To make the single-slope converter work, it is necessary not only to convert the unknown voltage into time, but to do it linearly.

To convert voltage to time is relatively easy. If a voltage is used to charge a capacitor through a resistor, the voltage across the capacitor increases in time and approaches the charging voltage. The time required for the voltage across the capacitor to reach a particular value depends on the value of the voltage source, the capacitance and the resistance. Unfortunately, this charging rate is not linear but exponential.

A capacitor may be charged linearly, however, if a constant-current source is used instead of the more common constant voltage with a series resistance. Figure 1 shows three curves of voltage across a capacitor versus time. Figure 1-a shows the familiar exponential charge obtained from a constant-voltage source with a series resistance. Figure 1-b shows the linear charge obtained from a constant-current source. Figure 1-c shows a capacitor being discharged from some initial voltage by a constant-current source (source of negative current as the current flows out).

Figure 2 is a block diagram of a simple single-slope converter. The voltage (E_x) across the capacitor generated by charging the capacitor from the constant-current source, and the unknown voltage (E_u) are applied to separate inputs of a voltage comparator. The voltage comparator converts analog information on its input to a

digital signal on its output. If the voltage at the + input of the comparator is greater than the voltage at the - input, the output will be a logic 1. But if the voltage on the + input is less than the voltage on the - input, the output will be a logic 0. The output of the comparator is connected to one input of a gate, the other input is connected to an oscillator of known frequency. When the output of the comparator is a logic 1 and switch S2 is at a logic 1, the oscillator signal passes from the gate to the counting circuits; if the output of the comparator is logic 0 or switch S2 is logic 0, no signal is passed to the counters.

Initial conditions of operation require the counters to be reset to zero, S1 closed, S2 at logic 0 (keeping the charge on the capacitor at zero and blocking any oscillator signal from passing through the gate), and that an unknown voltage be placed on the - input of the comparator.

The measurement cycle is initiated by simultaneously opening S1 and switching S2 to logic 1. When S2 is switched to logic 1, both control inputs of the gate become logic 1, as the unknown voltage at the + input of the comparator is greater than the initial voltage across the capacitor. With both the control inputs at logic 1, the oscillator signal passes to the counters, which begin to accumulate counts. Simultaneously, the voltage across the capacitor begins to rise as there is no longer a short across it. After some length of time has passed, the linearly rising voltage across the capacitor becomes equal to the unknown voltage at the + input of the comparator. An instant after these voltages become equal, the voltage at the + input is less than the voltage at the - input. The

...through time has passed, the output voltage of the integrator passes through zero

...sequence of the counters would be 000 at T_1 , 1000 at T_2 , and 1500 at T_3 . As the first


...voltage between the two comparators
continued on page 92

output voltage of the comparator therefore switches from a logic 1 to a logic 0. This change on the output of the comparator

unknown voltage, especially as the voltage on the capacitor approaches the unknown voltage. Like any charge-type converter, the

cially long-term accuracy, forced development of an improved converter. It uses the linear charge concept of the single-slope type.

Build an Automatic Telephone Dialer

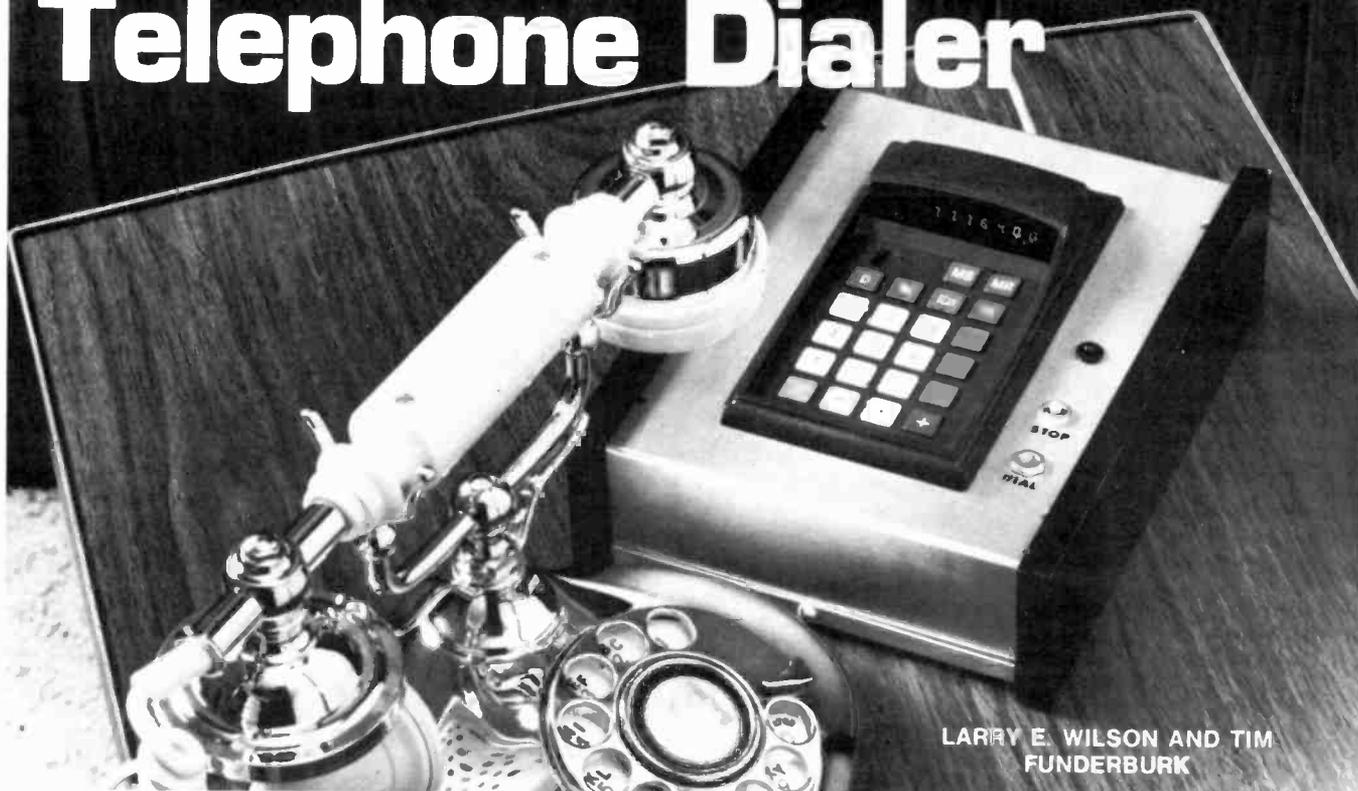

LARRY E. WILSON AND TIM FUNDERBURK

Convert an ordinary calculator into an automatic telephone dialer. If the calculator has a memory, you can store a telephone number as well. And when not dialing, the unit can be used as an ordinary calculator

TOUCH-TONE® DIALING IS GREAT! DIAL A zero just as quickly as dialing a one—and you don't have to watch all those holes go by! What's that—your telephone office doesn't offer Touch Tone®? Well, cheer up—build this dial converter and go Touch Tone® two better: the number you are dialing is displayed by an LED read-out, and you can use the converter as a calculator when it isn't dialing.

The dial converter accepts and displays a keyboard-entered telephone number (up to 8 digits). On command, this number is converted digit by digit (most significant digit first) into corresponding dial pulses, thus dialing a number. Dialing can be repeated by retaining the number in memory and pressing the DIAL switch again. The system is based on an IC that can be used as a calculator when not dialing. All telephone interfacing is with high-isolation relays to avoid any telephone network damage from stray voltages due to failures.

Operation

The converter is based on a calculator

using the National Semiconductor MM5738 calculator IC and DM8864 digit driver. Twenty-two connections are made to the calculator; one for each of the 8 digits and two for each of the segments. Calculator operation is not affected.

A telephone number is entered as it appears in the book—most significant digit first. The number is displayed on the 8-digit LED read-out. The telephone receiver is taken "off hook" and the DIAL button is pressed.

The DIAL button loads a one into the first position of digit register IC12 (Fig. 1) at the same time overflow register IC11-a is cleared. Dial pulse oscillator IC7-c and IC9-d is enabled and begins to output 10–12-Hz pulses. Dial relay RY1 opens and closes the telephone circuit at this rate and commences "dialing" a digit. Counter IC10 accepts these pulses and synchronously decodes them to 7-segment format. The segment outputs from the calculator chip and from IC12 are compared in exclusive-OR gates IC3 and IC4 for coincidence. When all segment outputs agree, all exclusive-OR outputs are "zeros" and

are inverted and applied to the input of IC13-c. Gates IC1 and IC2 serve to demultiplex the read-out information.

In the calculator, the read-out is multiplexed by having common segment-lines for all digits and presenting segment information for each digit in turn as the digits are sequentially enabled by the digit drivers. This is done very rapidly so the human eye cannot register the change and the eye sees a continuous display. Gates IC1 and IC2 serve to select a single digit regardless of the scanning. The output of the exclusive-OR gates may register coincidence several times as the digits are scanned; however, AND'ing the outputs of the digit gates and the exclusive-OR gates insures that only the digit selected by the shift register is detected. When the output of both the segment coincidence gates and the selected digit gate are at a logical-1 level, the dial pulser is stopped, IC10 is reset, and an interdigit pause is activated. The interdigit pause serves to identify the end of a digit to the telephone central office.

Since the number of pulses dialed corresponds to the number displayed on

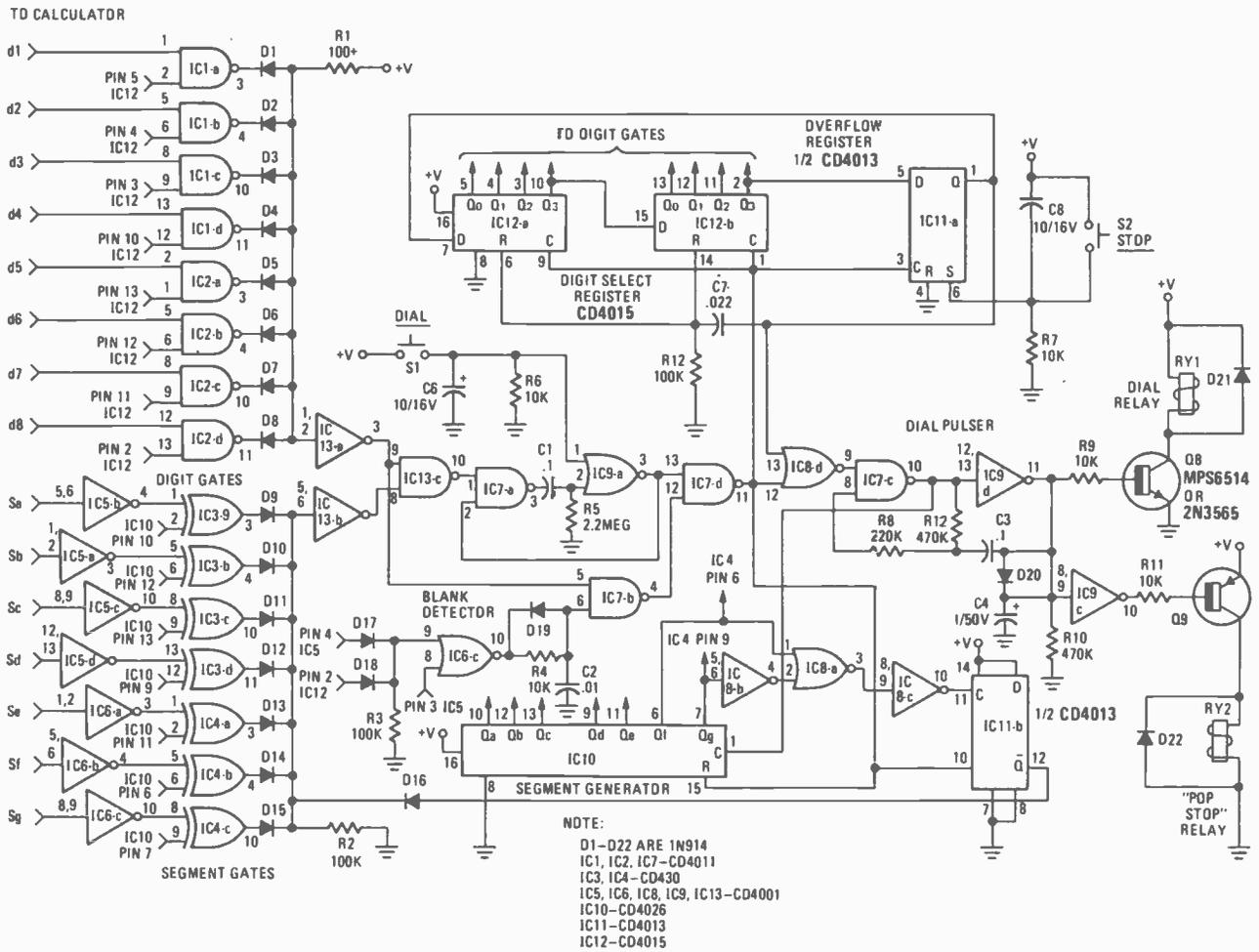


FIG. 1—THE TELEPHONE DIAL CONVERTER. Connections marked d1, #1, etc., are connections to the calculator (see Fig. 2).

the readout, we have just "dialed" the first number. At the end of the interdigit pause, the digit register is advanced, the next most significant digit is selected, and the dial pulser is again enabled.

This process continues until the least significant digit has been dialed. The "one" that was shifted across the digit register falls into the overflow register, disabling the dial pulser and hence the entire system. The telephone number you selected has now been dialed.

Special considerations

Dialing a zero: When the number to be dialed is a zero we have complications, since in seven-segment language a zero is 0, and in dial language a zero is 10. Thus we have to inhibit the coincidence gates on the initial zero. Initially, IC11-b is reset and the Q output (at a logic-1 level) prevents the coincidence gates from switching. As soon as IC10 goes from zero to one, IC11-b is clocked to a one via gates IC8-a and IC8-b (which detect the presence of a zero in the segment output of IC10) removing the inhibit from coincidence gates. The next time IC10 reaches zero, the normal

end-of-digit is signalled and since IC10 has only stepped 10 times, a ten was "dialed."

Skipping blank digits. Whenever less than 8 digits are entered in the calculator display (which will be most of the time), we must somehow tell the digit register to advance until a valid digit is present. Otherwise the counter and calculator segments would never agree and the dial pulser would dial forever.

Blank detector gates IC6-c and IC7-b sample segments that are always lighted as long as a number is displayed. The absence of both segments is interpreted as a blank. This output is AND'ed with the digit gates and clocks IC12 to the next digit position. This process repeats very rapidly until a non-blank digit position is found and dialing proceeds normally. This skip effect occurs so rapidly that the dial relay never has a chance to operate!

Resistor R4 and capacitor C2 filter out the very narrow pulses that occur in the calculator during the blanking period between each digit. Diode D18

PARTS LIST

- All resistors 1/2-watt, 10%, unless noted
 R1, R2, R3—100,000 ohms
 R4, R6, R7, R9, R11—10,000 ohms
 R5—2.2 megohms
 R8—220,000 ohms
 R10, R12—470,000 ohms
 R13, R14—560 ohms
 R15 to R21—22,000 ohms
 C1, C3—0.1 μF, 25 volt, ceramic
 C2—.01 μF, 25 volt ceramic
 C4—1 μF, 35 volt electrolytic
 C5—470 μF, 16 volt electrolytic
 C6, C8—10 μF, 16 volt electrolytic
 C7—.022 μF, 25 volt ceramic
 D1-D22—1N914
 IC1, IC2, IC7—CD4011 Quad 2-input NAND gate
 IC3, IC4—CD4030 Quad exclusive-OR gate
 IC5, IC6, IC8, IC9, IC13—CD4001 Quad 2-input NOR gate
 IC10—CD4026 decade counter with decoded 7-segment outputs
 IC11—CD4013 Dual type-D flip-flop
 IC12—CD4015 Dual 4-bit shift register
 Q1 to Q8—MPS6514, 2N3565
 Q9—2N3638
 RY1, RY2—Sigma 65F, 9 volts DC, PC mount
 S1, S2—SPST Momentary pushbutton switches
 Calculator—Any type using MM5738 calculator IC.
 Misc—Chassis, ribbon cable, spacers, LED indicator.

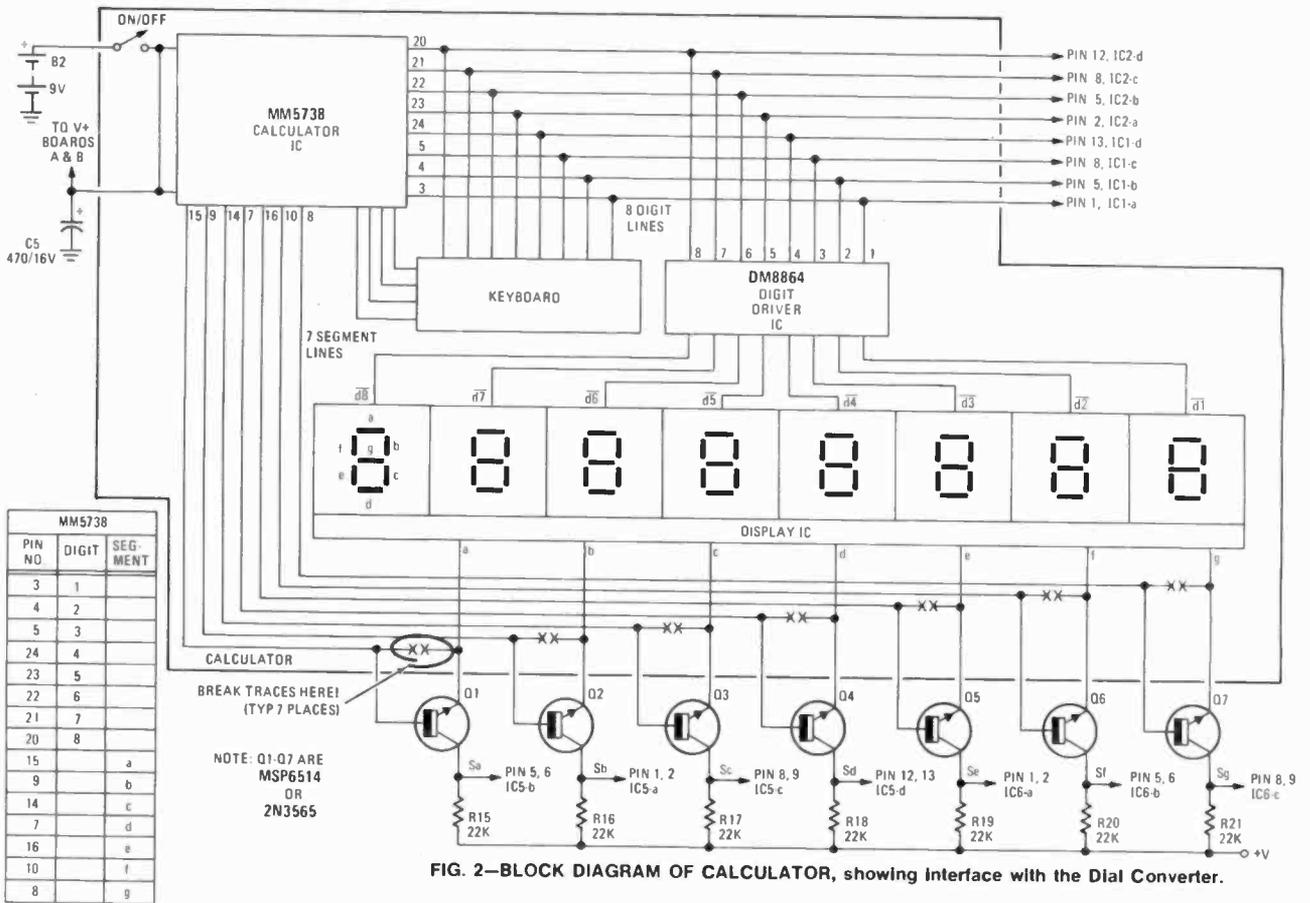


FIG. 2—BLOCK DIAGRAM OF CALCULATOR, showing interface with the Dial Converter.

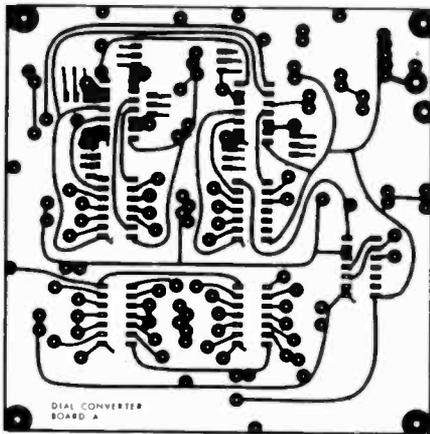


FIG. 3 (left)—PRINTED CIRCUIT pattern for Board-A shown half-size.

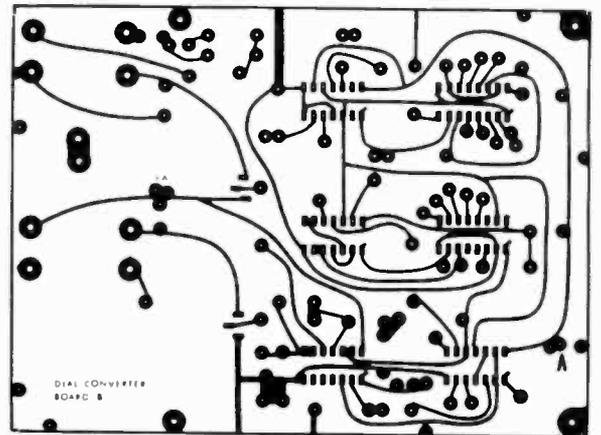


FIG. 4 (right)—PRINTED CIRCUIT pattern for Board-B shown half-size.

inhibits the blank detector when a digit-1 is selected. (The calculator scans digits from right to left but the dial converter reads out from just the opposite direction.) When we get to the last digit—calculator first digit—the end-of-word blanking pulse combines with the selection of digit one and immediately clocks IC12 into overflow. Since there never can be a blank in digit one position—the cleared calculator always displays a zero—it is safe to allow the pulser to always operate in this position.

Calculator converter interface

For the calculator to display a segment, the segment driver in the calculator chip raises the anodes of all

the selected segments toward V_{DD} ; the selected digit driver pulls the cathodes of all of the segments toward ground and current flows through the selected segment, causing it to light.

To interface with the calculator chip we have to obtain both digit and segment information. Digit interfacing is OK; the levels are compatible with CMOS thresholds. The segments, however, show very little usable voltage change from on to off. There is of course plenty of current change. Transistors Q1-Q7 (Fig. 2) translate the current change to a voltage change.




"Pop" elimination

In your telephone, the dial shunts the

handset during pulsing to eliminate an annoying "pop" with each dial pulse. As we have the handset "off the hook" we need to simulate this consideration. The "pop stop" circuit-capacitor C4 is charged rapidly from the dial pulser and discharges only through R10. As long as the voltage on C4 is above IC9-c's threshold, relay RY2 will be operated. RY2's contacts remove the telephone from the line and replace it with approximately 600 ohms of resistance. This makes the central office think there is a phone across the line. It also gives us an indication that the converter is dialing, as part of the 600-ohm load is composed of an LED indicator. The level at IC9-c input will slowly decay after the last dial

The better the training the better you'll

Send for
FREE
illustrated
career
guide

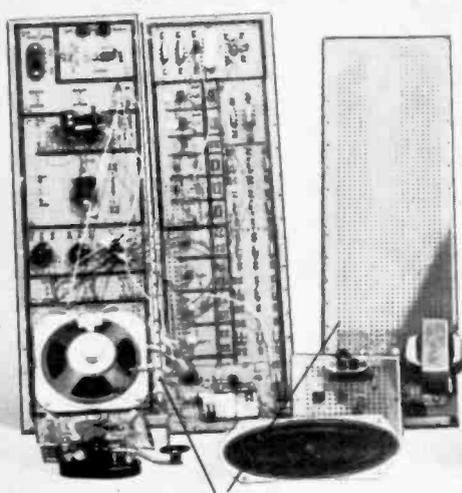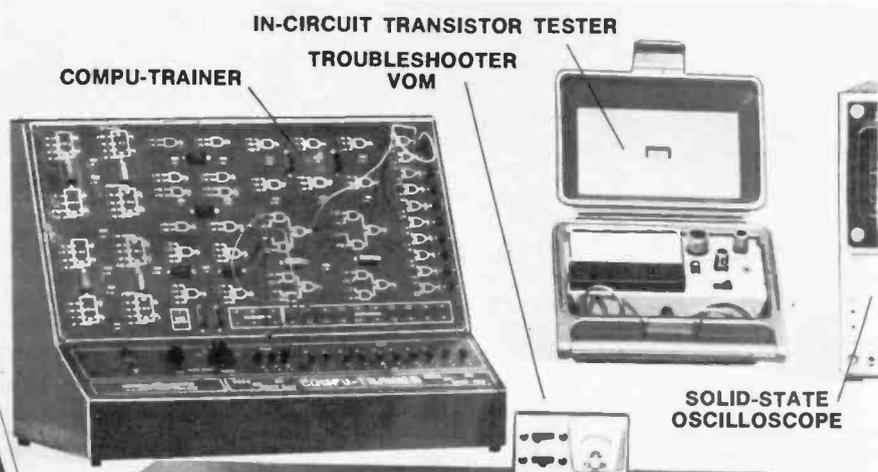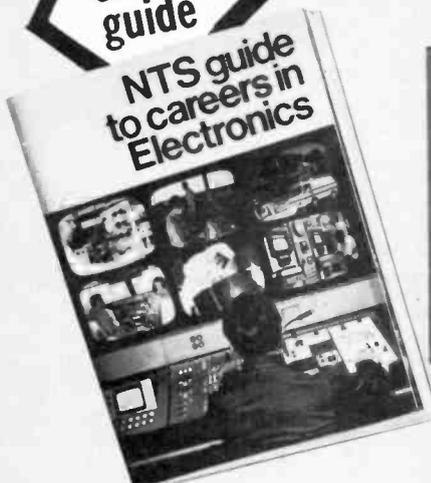

ELECTRO-LAB

(Simulated TV Reception)

As an NTS student you'll acquire the know-how that comes with first-hand training on NTS professional equipment. **Equipment you'll build and keep.** Our courses include equipment like the **NTS/Heath Digital GR-2000 Solid State color TV** with first-ever features like silent varactor diode tuning; digital channel selection, (with optional digital clock), and big 315 sq. in. ultra-rectangular screen.

Also pictured above are other units — 5" solid state oscilloscope, vector monitor scope, solid-state stereo AM-FM receiver with twin speakers, digital multimeter, and more. It's the kind of better equipment that gets you better equipped for the electronics industry.

This electronic gear is not only designed for training; it's field-type — like you'll meet on the job, or when you're making service calls. And with NTS easy-to-read, profusely illustrated lessons you learn the theory behind these tools of the trade.

Choose from 12 NTS courses covering a wide range of fields in electronics, each complete with equipment, lessons, and manuals to make your training more practical and interesting.

Compare our training; compare our lower tuition. We employ no salesmen, pay no commissions. You receive all home-study information by mail only. All Kits, lessons, and experiments are described in full color. Most liberal refund policy and cancella-

and the equipment be equipped.

**COMPARE OUR
KITS AND LESSONS.
COMPARE OUR
TUITION.**



tion privileges spelled out. Make your own comparisons, your own decision. Mail card today, or clip coupon if card is missing.

NO OBLIGATION. NO SALESMAN WILL CALL

APPROVED FOR VETERAN TRAINING

Get facts on new 2-year extension

NATIONAL TECHNICAL SCHOOLS

TECHNICAL-TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 So. Figueroa St., Los Angeles, Calif. 90037

NATIONAL TECHNICAL SCHOOLS
4000 South Figueroa St., Los Angeles, Calif. 90037 Dept. 206-116

Please send **FREE** Color Catalog and Sample Lesson.
NO OBLIGATION. NO SALESMAN WILL CALL.

<input type="checkbox"/> Color TV Servicing	<input type="checkbox"/> Electronics Technology
<input type="checkbox"/> B & W TV and Radio Servicing	<input type="checkbox"/> Computer Electronics
<input type="checkbox"/> Electronic Communications	<input type="checkbox"/> Basic Electronics
<input type="checkbox"/> FCC License Course	<input type="checkbox"/> Audio Electronics Servicing

NAME _____ AGE _____

ADDRESS _____ APT # _____

CITY _____ STATE _____

Please fill in Zip Code for fast service _____

Check if interested in G.I. Bill information.
 Check if interested **ONLY** in classroom training in Los Angeles.

NOVEMBER 1976

**BUILD FOR
YOUR CAR**

Anti-Theft Devices

PART I. Practical circuits you can build and connect to any vehicle with a 6- or 12-volt electrical system for protection against thieves

R. M. MARSTON

ONE OF THE MOST PERSISTENT DANGERS facing the modern automobile owner is that of having his vehicle stolen or burglarized. It is impossible to protect oneself 100% against that kind of danger. But the thoughtful owner can gain up to 99% protection by using a little common sense and by fitting his vehicle with fairly simple electrical or electronic anti-theft devices.

Anti-theft devices.

Vehicle anti-theft devices fit into two basic classes. The first is the "immobilizer" type, designed to simply reduce a thief's chances of starting or driving a target vehicle away. Immobilizers give no protection against the car *burglar*, who simply wishes to steal objects left inside the vehicle.

Most vehicles already have a built-in immobilizer—the ignition switch—but this device is easily bypassed by a skilled thief. Many modern vehicles are fitted with an additional immobilizer, the mechanical steering lock, which gives fairly good protection. Further protection can easily be gained by wiring a simple immobilizer switch into some part of the electrical section of the vehicle's power unit.

The second class of anti-theft device is the true burglar alarm that sounds an alarm (and perhaps also immobilizes the automobile's ignition system) if any unauthorized person tries to enter the vehicle. These alarms may be activated in any one of three basic ways. One of the most popular is via microswitches that operate when the car doors or hood or trunk are opened. Microswitch-activated alarms are relatively inexpensive, highly reliable, and can give excellent anti-theft protection.

Another method of activating an alarm is by detecting the small drop in the vehicle's battery voltage when a door, hood, or trunk courtesy light turns on, or when the ignition is turned on. These so-called "voltage sensing"

alarms give the same degree of anti-theft protection as the microswitch alarm system, but are generally more expensive and far less reliable.

A third way of activating an alarm is by detecting the vibration or swaying that takes place when a vehicle is entered or moved. This type has a number of disadvantages. If its sensitivity is adjusted so that it activates when anyone enters or rocks the vehicle, the system will tend to go off in gusty winds or when a person leans on the automobile. This system, therefore, has a very low reliability rating. If the system is adjusted so that it activates only when the vehicle is actually moved

tive alarm is inferior to that of the micro-switch-activated type.

Practical automobile anti-theft alarm systems may be turned on and off either from within the car, or from outside. Systems that are switched from within the vehicle have a number of disadvantages. To enable the owner to leave the vehicle without activating the alarm, the systems must incorporate a built-in "exit" delay of about 30 seconds, and to enable the owner to enter it again they must have an additional built-in "entry" delay of about 15 seconds.

Consequently, the circuits tend to be fairly complex and expensive, and to have a relatively poor reliability rating.

	SNATCH BURGLAR	CASSETTE THIEF	JOY RIDER	DRIVE-AWAY THIEF	TOW-AWAY THIEF
IMMOBILIZER	NIL	NIL	GOOD	GOOD	NIL
INTERNALLY-SWITCHED MICROSWITCH-ACTIVATED ALARM	NIL	GOOD	GOOD	GOOD	NIL
INTERNALLY-SWITCHED VOLTAGE-SENSING ALARM	NIL	GOOD	GOOD	GOOD	NIL
INTERNALLY-SWITCHED VIBRATION ALARM	NIL	POOR	GOOD	POOR	FAIR
EXTERNALLY-SWITCHED MICROSWITCH-ACTIVATED ALARM	GOOD	GOOD	GOOD	GOOD	NIL
EXTERNALLY-SWITCHED VOLTAGE-SENSING ALARM	GOOD	GOOD	GOOD	GOOD	NIL
EXTERNALLY-SWITCHED VIBRATION ALARM	POOR	POOR	GOOD	POOR	FAIR

TABLE 1—DEGREE OF PROTECTION provided by different types of alarm circuits.

or subjected to substantial "G" forces, it won't be sensitive enough to give effective anti-burglar protection.

Sometimes, thieves may deliberately activate the vibration sensitive alarm on a number of successive occasions, by rocking the vehicle, until the owner eventually disconnects the system in frustration. The thieves are then free to steal the unprotected vehicle. Thus, the protection given by the vibration sensi-

More important, the systems give very poor anti-burglar protection, since the thief is allowed a full 15 seconds of entry time in which to steal any worthwhile goodies before the alarm sounds off.

By contrast, externally-switched alarm systems can be very simple, reliable, inexpensive and (since they can be made to sound off the instant a car door starts to open) can give excellent anti-

burglar protection.

Thus, the best all-round kind of alarm system is the externally-switched micro-switch-activated type. Later we'll show you some practical examples of this type of alarm. In the meantime, let's look at the different types of thieves who may try to steal or burglarize your vehicle.

Car thieves

Car thieves can be described as fitting into five basic classes:

Snatch burglars: These are the most common car thieves. They simply roam around looking to see if any theft-worthy goodies have been left lying around inside parked cars, or if vehicles' luggage compartments have been left unlocked. You can obtain a high degree of protection against this type of thief by fitting your vehicle with an externally-switched microswitch-activated or voltage-sensing alarm system that sounds off the instant a car door starts to open. But your best protection is common sense: Don't leave attractive goodies in sight in the car! Always lock the luggage compartment!

Cassette Thieves: This type of thief specializes in stealing radios or cassette players from vehicles. It takes the average thief several minutes to steal one of these units, so you can easily scare him off by fitting almost any type of burglar-alarm device that is activated

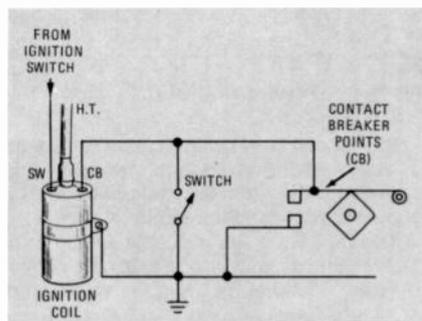


FIG. 1—IMMOBILIZER operates by shorting contact breaker points.

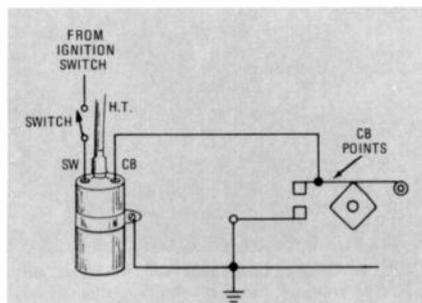


FIG. 2—IGNITION IMMOBILIZER operates by disabling vehicle's ignition circuit.

by opening the car doors.

Joy Riders: These characters usually steal vehicles without premeditation. Most times, they simply look for an unlocked car, then short out its ignition switch and start the vehicle by briefly shorting out the starter switch. You should be able to beat this type of thief

by fitting your vehicle with any type of immobilizer or anti-theft alarm, but the chances are that if you don't lock your car doors, you'll also be thoughtless enough to forget to switch on your anti-theft system. In this case, your best protection is lots of insurance.

Drive-Away Thief: This thief usually has enough skill to open locked car doors and bypass ignition switches, and then steal the vehicle by simply driving it away. You can often beat him by fitting your vehicle with a good immobilizer circuit or an anti-theft alarm.

Tow-Away Thief: This is the least common but most dangerous type of car thief. He specializes in stealing good quality and easily disposable vehicles. He steals them by either towing them away or by hoisting them onto the back of a tow-away vehicle. He selects vehicles very carefully before stealing them and often does his best to find out if a target vehicle is fitted with an anti-theft alarm before trying to steal it. In most cases, if he knows that the target vehicle is fitted with an alarm system, he will simply look for an alternative target. In extreme cases, however, he may go to almost any lengths to steal an exceptionally desirable vehicle.

The best defense against this type of thief is a vibration type alarm, but even it offers only limited protection. In most cases, the thief will try to persuade the owner to disconnect a vibration type alarm by repeatedly making it trigger falsely before finally stealing a target vehicle.

Table 1 shows the degree of protection offered by different types of anti-theft devices against different types of thief. As can be seen, immobilizers give good protection against joy riders and drive-away thieves but provide no protection against burglars or tow-away thieves. Externally-switched micro-switch-activated and voltage-sensing alarms give good protection against all except tow-away thieves.

Having cleared up these points, let's look at some practical anti-theft circuits.

Immobilizer circuits.

These are used to reduce a thief's chances of starting or driving away a target vehicle. Most vehicles already have a built-in immobilizer—the ignition switch, but it is readily visible and can easily be bypassed by a skilled thief. So a simple additional concealed immobilizer circuit can give considerable extra anti-theft protection.

Simple immobilizers consist of a concealed switch wired into some part of the electrical section of the vehicles power unit. Figures 1 and 2 show how immobilizers can be wired into the vehicle's ignition system. In Fig. 1, the switch is wired between the chassis and the vehicle's contact breaker (CB) points.

When this switch is open, the ignition operates normally. When it is closed, the points are shorted out and the engine is unable to operate. This circuit gives excellent protection, particularly if the wiring is carefully hidden at the CB points.

The circuit shown in Fig. 2 has the immobilizer switch wired in series with the vehicle's ignition switch, so that the engine can operate only when the switch is closed. The protection of this circuit is inferior to that of Fig. 1 since the thief can bypass the immobilizer and the ignition switch by simply hooking a wire from the battery to the sw terminal of the coil.

Figure 3 shows how an immobilizer switch can be wired into the vehicle's electric starter system so that the starter

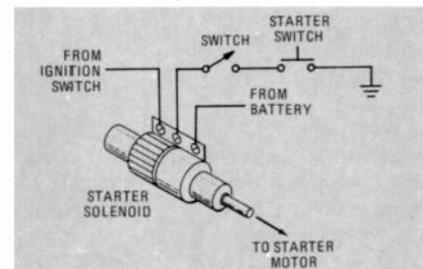


FIG. 3—STARTER IMMOBILIZER operates by opening starter-motor circuit.

operates only when the switch is closed. This system gives better protection than Fig. 2, but is not as good as Fig. 1 since the starter solenoid can be operated manually on many vehicles and also because the starter and immobilizer switches can be bypassed by a single length of wire.

Finally, Fig. 4 shows how an immobilizer switch can be wired in series with the electric fuel pump on suitable vehi-

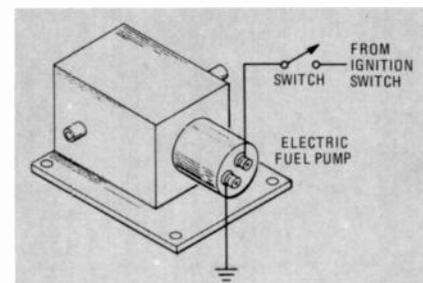


FIG. 4—FUEL-PUMP IMMOBILIZER operates by opening electric fuel-pump circuit.

cles so that the pump operates only when this switch is closed. A feature of this system is that it permits a thief to start the engine and drive for several hundred yards on the fuel remaining in the carburetor before the lack of fuel immobilizes the vehicle.

A major weakness of the circuits shown in Figs. 1 to 4 is that they must all be turned on and off manually so they give protection only if the owner remembers to turn them on each time he leaves his car. Figure 5 shows an immobilizer circuit that turns on auto-

matically each time an attempt is made to start the engine, but which can be turned off by briefly pressing a hidden pushbutton switch. A small "reminder" light turns on when the engine is disabled by the immobilizer. This circuit gives a high degree of protection since it does not depend on the memory of its owner.

How the immobilizer works

The relay coil RY1 is wired in series with 1,000 μ F capacitor C1, and the combination is wired across the vehicle's ignition switch. Capacitor C1 is shunted by the series combination of normally-open relay contacts RY1-1 and normally-closed pushbutton switch S1. Relay contacts RY1-2 are wired across the vehicle's breaker points. An LED (light-emitting diode) is wired in series with current-limiting resistor R1 and the combination is wired across the coil of the relay.

Normally, C1 is fully discharged. When the ignition switch is first closed, a surge of current flows through the relay coil via C1 and the relay turns on. As the relay energizes, contacts RY1-1 close and lock the relay on via S1. Relay contacts RY1-2 close and short out the vehicle's breaker points, thus immobilizing the engine. Under this condition, current flows in the LED via R1.

The relay stays on until S1 is opened briefly, at this point the relay unlatches, C1 charges up rapidly via the relay coil, and the relay and the LED turn off. As the relay turns off, the short is removed from the vehicle's breaker points and the engine is able to operate normally.

The relay used in the Fig. 5 circuit

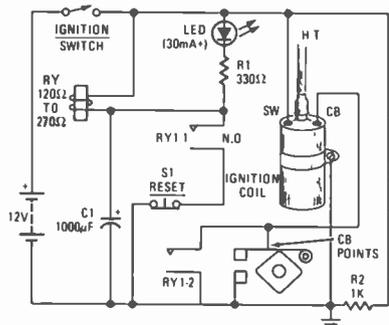


FIG. 5—SELF-ACTIVATING IMMOBILIZER circuit for vehicles with -V ground systems. For vehicles with +V grounded, reverse the polarities of C1 and the LED.

can be any 12-volt type with a coil resistance in the range of 120 to 270 ohms, and with two or more sets of normally-open contacts. The LED can be any type with a mean current rating greater than 30 mA or so. The circuit is shown as for use on vehicles with negative-ground electrical systems. On positive-ground vehicles, reverse the polarities of C1 and the LED.

Practical anti-theft alarms.

The most efficient and useful type of

vehicle anti-theft alarms are externally-switched microswitch-activated or voltage-sensing types. These alarms are turned on and off via a concealed toggle switch or a key switch that is fitted to the outside of the vehicle. Figures 6 to 13 show a few practical examples of alarm systems of these types. All of these circuits also act as immobilizers, and operate the vehicle's horn and lights under the 'alarm' condition.

In the circuits shown in Figs. 7 to 11, microswitches are used to trip a self-latching relay when the car doors, hood or trunk are opened. This relay immobilizes the engine and operates the horn and headlights either directly or via additional circuitry. Two suitable front-door microswitches are built into most vehicles as standard fittings and are used to operate the courtesy or dome lights. Additional switches can easily be fitted to the rear doors. The hood and trunk can be protected by 'auxiliary' microswitches.

Microswitch-activated immobilizer

The operation of the circuit shown in Fig. 6 is very simple. Normally, the key switch is open and no voltage is fed to the relay network, so the alarm is off. Suppose, however, that the key switch is closed. If any of the door switches close, current flows via D1, or if

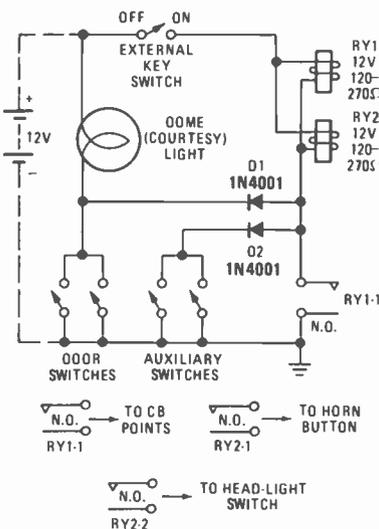


FIG. 6—MICROSWITCH-ACTIVATED alarm/immobilizer operates horn and lights until switched off, or until battery discharges. Circuit is for vehicles with -V ground electrical systems.

any of the auxiliary switches close, current flows via D2. In either case, both relays turn on. As RY1 energizes, contacts RY1-1 close and lock both relays on, and contacts RY1-2 close and short out the vehicle's contact breaker (CB) points, thus immobilizing the vehicle.

Simultaneously, contacts RY2-1 close and switch on the car horn, thus giving an audible indication of the intrusion. Also, contacts RY2-2 close and switch

on the headlights, thus giving a visual identification of the violated vehicle. The horn and lights remain on until the key switch is opened or until the vehicle's battery runs down.

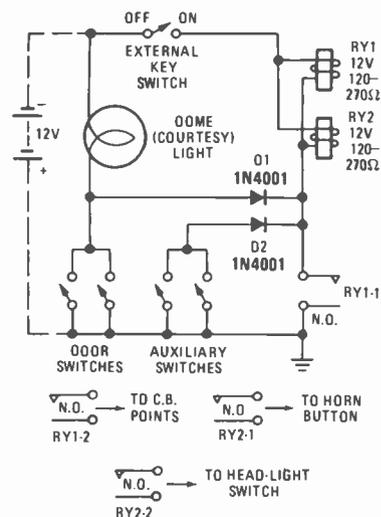


FIG. 7—MICROSWITCH-ACTIVATED alarm/immobilizer designed to operate on vehicles with +V ground electrical systems.


The circuit shown in Fig. 6 is for use on negative-ground vehicles. The circuit can be modified for use on positive ground vehicles by simply reversing the polarities of D1 and D2, as shown in Fig. 7.

to be continued.

Newest small calculator is also a wrist-watch

Hughes Aircraft Co. has just introduced a new electronic watch module that includes a nine-function calculator with a standard four-function digital watch.

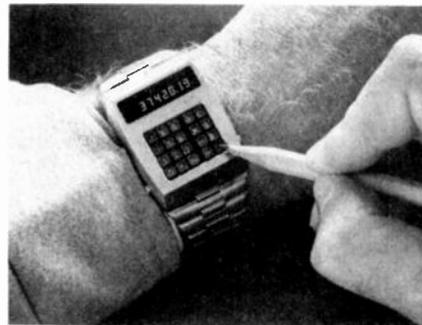The module measures only 1.4 x 1.25 inches and it adds, subtracts, multiplies, divides, calculates percentages and




COMBINATION CALCULATOR-WATCH, supplied in module form by Hughes Aircraft Co. (Hughes does not market watches, but is a leading manufacturer of watch modules.)

squares, and has a memory and multiplication and division constant. The watch displays the standard four functions—hours, minutes, seconds and date.

The memory retains entries even when the unit is in non-display or time-display mode. Thus the user can interrupt a calculation to check the time, then return to his calculation without losing his figures.

R-E

6 NEW CIRCUITS

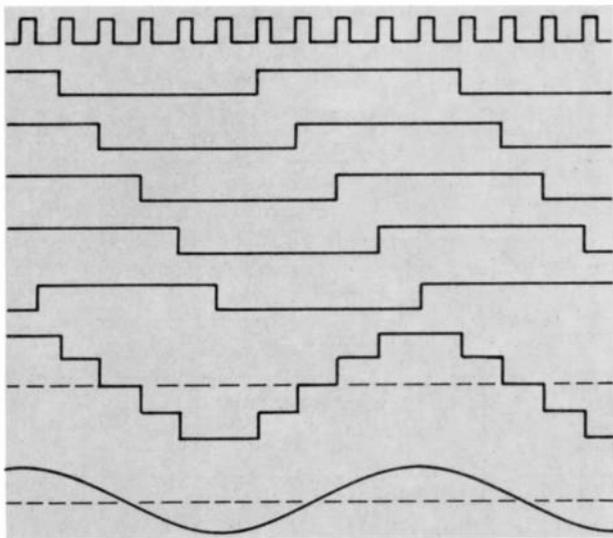

Create Sinewaves Using Digital IC's

Digital techniques can be used to synthesize sinewaves whose amplitude and frequency can be precisely and rapidly controlled and whose distortion is low

DON LANCASTER

EVERY ONCE IN A WHILE A REALLY GREAT IDEA gets buried deep in the technical literature. For instance, back in 1969, a very elegant and ultra-simple way to generate sinewaves digitally appeared. Then, apparently, it was nearly forgotten. Today we can use a \$1.00 CMOS integrated circuit, three or four 5% resistors, and this "lost" method to build ultra-simple digital sinewave sources—sinewave sources whose amplitude and frequency we can precisely and rapidly control, and whose distortion is very low. We can use sinewaves like these in electronic music, lab function generators, sweepers, microprocessor and minicomputer analog I/O, digital cassette recorders and MODEMS. But, you're sure to find lots more places where you can use these simple, quick and sophisticated techniques.

The basic idea

Any method of generating sinewaves digitally is usually a two-step process. First, you generate a convenient waveform that consists of a fundamental and some harmonics. Then you get rid of the harmonics by filtering them out. The trick is to pick a convenient waveform that has as few harmonics as possible to start with. We also want the harmonics to be as small as possible, and we want them to be as high an order as possible. All these requirements simplify our filtering and let us change frequency over a reasonable range

without necessarily changing our filtering.

Our search for a convenient waveform starts with a *symmetrical* one. This automatically gets rid of all the even harmonics. From here, we want to pick some waveform that inherently doesn't have as many of the odd harmonics as is possible. Ideally, we'd like to get rid of all the low-order odd harmonics. Directly using squarewaves doesn't look too promising because of a third harmonic only 10 decibels ($1/3$ amplitude) down from the fundamental that's staring you in the face. Similarly, most any relatively simple system based on binary counters will probably also have lots of strong, low-order odd harmonics.

The secret of digital sinewave generation is shown in Fig. 1. You use a circuit called a *walking-ring* or a *Johnson counter* to ultimately generate your sinewave. You make the counter as long as you have to. The longer the counter, the more parts, but the higher the odd harmonics you end up with and the weaker they are. A second part of the secret is that you combine outputs of the counter with resistors, into either a single small-value summing resistor, or into the summing input on an operational amplifier. *But you skip one counter stage in your summing.* This makes our sinewave waveform take twice as long automatically on the peaks and valleys. As we'll shortly see, the waveforms look rather strange and choppy before

filtering, but *they have no low-order harmonics!*

You can make a walking-ring counter out of type-D flip-flops or out of many different types of shift registers. The CMOS 4018 is ideal for 6, 8, and 10-step sinewave synthesis, as we'll shortly see, and several 4018's can be cascaded for longer sequences. Our ten-step system takes only one 4018 (or five type-D flip-flops). Pick the resistors just right, and the first harmonic after the fundamental is the *n*th, and it's almost 20 dB (one-tenth amplitude) down from the fundamental *before* you do any filtering. The only other low-order harmonics are the 11th, the 19th, 21st, 29th, 31st, and so on. All these are so low in amplitude and so high in frequency that if you get rid of the ninth by low-pass filtering, the rest will utterly disappear.

A type-D flip-flop or a register stage is a clocked logic block. When an input clock arrives, information on the D input is passed onto the Q output and its complement is passed onto the \bar{Q} output. (If D is a "1", clocking puts a "1" on Q and a "0" on \bar{Q} . If D is a "0", clocking puts a "0" on Q and a "1" on \bar{Q} .)

To build a walking-ring counter, connect the Q output of one stage to the D input of the next stage and so on down the line. At the last stage use the complementary \bar{Q} output to feed back to the D input of the first stage. If we use a five-stage register and start with

00000, one clocking gives us 10000 since the \bar{Q} output of the last stage was a "1" and gets passed on to the first stage. More clockings give us 11000, 11100, 11110, and 11111. The Q output is now a 0, so the next clocking gives us 01111, 00111, 00011, 00001, and finally 00000, repeating the ten-step sequence as we close the series. The length of our sequence is ten or twice the number of stages.

The sequence length usually equals twice the number of stages in use. If we look at the five outputs A through E in Fig. 1, we see that we get a group of five phase-shifted squarewaves. We now sum four of these five waveforms with just the right "magic" resistor values, and we get a composite waveform that is a fundamental sinewave along with low-amplitude ninth, eleventh, and a few very small and very high-order remaining odd harmonics. For many uses you can use this sinewave pretty much as is, but it's a simple matter of filtering to get a sinewave of good purity.

Our clock frequency sets the output frequency. With a five-stage, ten-step system, the clock input is ten times the output frequency. As the clock frequency changes, so does the output on a nearly instantaneous basis, since there are no time constants or inductors in the circuit. Note also that a sudden change in clock frequency coherently changes the sinewave without any transients or jumps.

With CMOS and relatively light loading (20K or more) the output logic swing is equal to the supply voltage, so we can change the output amplitude either by changing the supply voltage or by changing the gain (digitally or otherwise) of any op-amp that's summing our phase-shifted squarewaves into the composite sinewave output.

Circuits

Figs. 2 and 3 show us two circuits using a single 4018 CMOS register that you can use for digital sinewave generators.



In Fig. 2, we've built a four-stage counter that gives us an eight-step output using one IC and three resistors. The output is summed across the 4.7K resistor and then actively filtered by the PNP emitter follower and the third-order Bessel active filter. This particular circuit is used in a digital cassette recording system, where a digital "1" is a 2400 hertz and a digital "0" is a 1200 hertz sinewave recorded on the tape. You can shift the cutoff frequency of the active filter by proportionately changing capacitors C1, C2, and C3. Doubling these capacitors reduces the cutoff frequency in half and so on. The input clock of this circuit is eight times the output frequency.

In Fig. 3, we have a five-stage counter and four resistors that sum into a type-741 operational amplifier. The op amp is filtered with a single capacitor. This particular circuit drives the transmitter speaker of a "103" style MODEM, outputting a 1070 hertz sinewave for a digital logic "0" and a 1270 hertz sinewave for a digital logic "1". This time the clock frequency is ten times these output values.

Magic numbers


Figures 4, 5 and 6 show us the magic resistor values, the circuits, and the waveforms for three, four and five-stage registers of length 6, 8, and 10. The value in parenthesis is the resistor ratio we want, while the

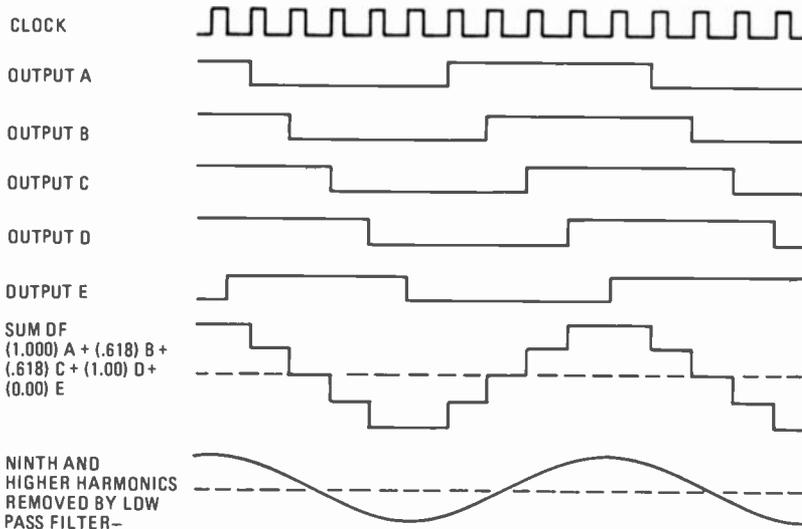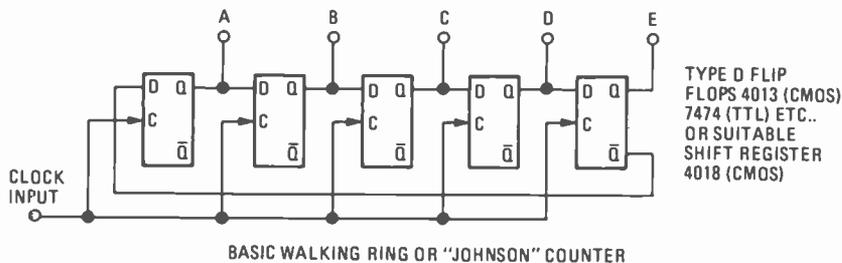1. THE WALKING RING COUNTER and its waveforms, which combine to produce a good sinewave (after filtering).




KEY WAVEFORMS. NOTE THAT OUTPUT "E" IS NOT USED

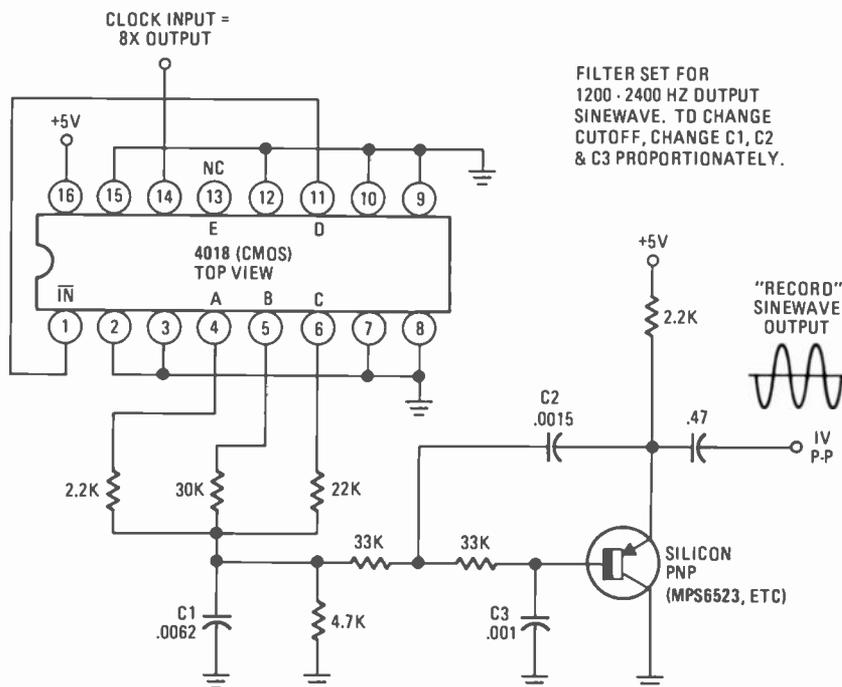2. AN EIGHT-STEP GENERATOR, as used in a digital cassette recording system.



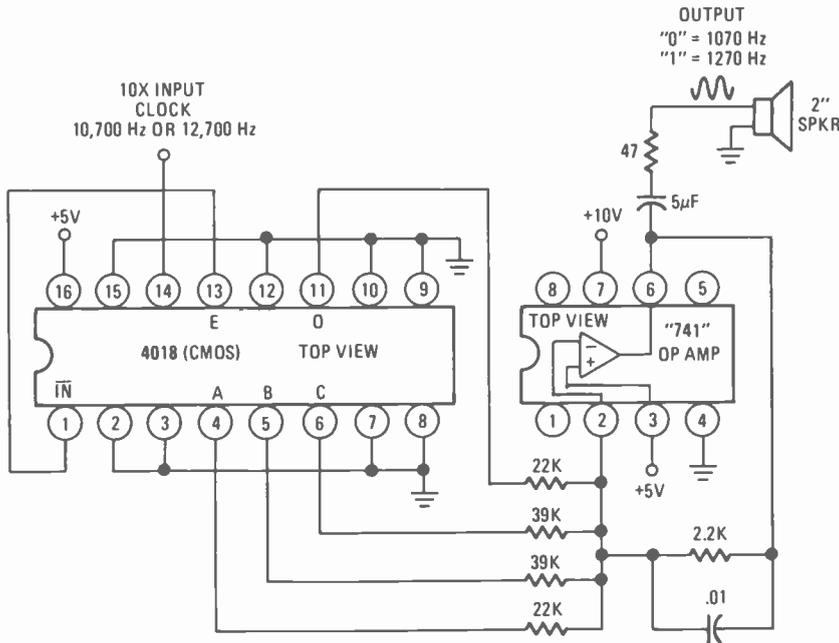3. 10-STEP SINEWAVE GENERATOR drives the transmitter speaker of a MODEM.




resistor value has been rounded off to a stock 1 percent value. Actually, 5 percent resistors are more than adequate for practically all sinewave generators, particularly for those of ten stages or less.

You'll get more performance by lengthening the registers and using more resistors. Values for any length are shown in Table I, along with the harmonics and their strengths that you can expect. Once again, the parenthesis values are exact ratios, while the resistor values are 1 percent based on 22.1 K being the smallest value used.


These longer lengths make filtering more easy since the odd harmonics you do get are higher in frequency and lower in amplitude as you add stages. Note that the input clock frequency goes up as you add stages. Two or more 4018's can be cascaded as needed for these longer lengths. Usually binary lengths of 8 and 16 or decimal lengths of 10 or 20 make for the easiest interface with the system timing in the rest of your circuit.

Note that with a longer register, you can have a fixed filter and still operate over a wide frequency range. For instance, with a 10-stage register and a 10:1 frequency change, the lowest harmonic of the lowest output frequency will still be 1.9 times the frequency of the highest output frequency and reasonably easy to get rid of with a sharp-cutoff filter.

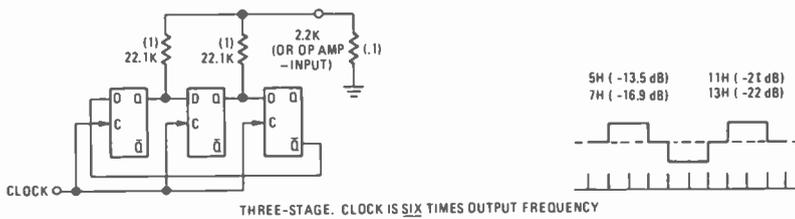
4. THREE-STAGE DIGITAL SINEWAVE GENERATOR. Resistance values are shown in ratios (parentheses) and ohms. The amplitude of the harmonics are also shown.



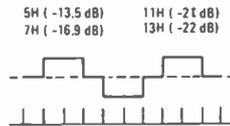
THREE-STAGE. CLOCK IS SIX TIMES OUTPUT FREQUENCY



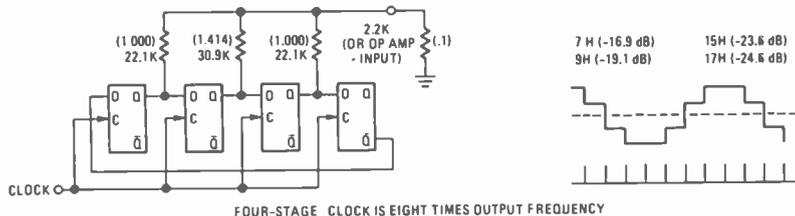
5. FOUR-STAGE DIGITAL SINEWAVE GENERATOR.



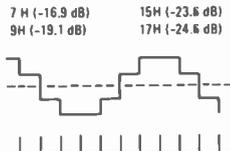
FOUR-STAGE. CLOCK IS EIGHT TIMES OUTPUT FREQUENCY



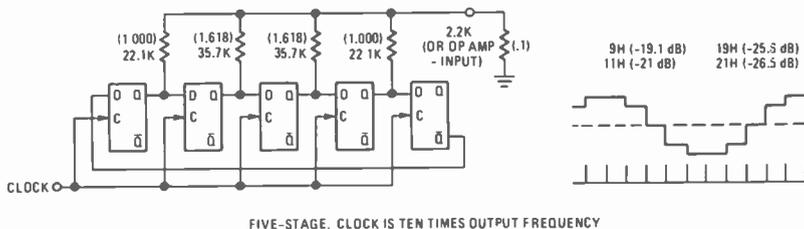6. FIVE-STAGE DIGITAL SINEWAVE GENERATOR.



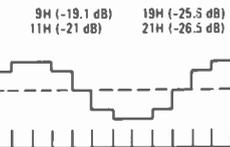FIVE-STAGE. CLOCK IS TEN TIMES OUTPUT FREQUENCY



Some loose ends

You may have to look into several details when generating your own digital sinewaves. These include the counter sequences, resistor tolerances, offsets, and the choice of filtering.


Walking-ring counters longer than two stages have *disallowed sequences* that make up the difference between the total possible counter states and the states you are actually using. For instance, a three-stage counter has the valid 000, 100, 110, 111, 011, 001 and back to 000 six-count state sequence. It also has a disallowed 101, 010, 101, 010 . . . two-count rut it can get into. All walking-ring counters must be set up to eliminate the disallowed states.

This is done internally in the 4018 counters, and cascaded 4018's will probably eliminate most if not all the possible disallowed sequences. You can also use a reset button or signal to get your sequence off on the 000 state before you begin. Or you can add gating to force the internal stages to zero when the end stages are zero; or to all ones when the end stages are ones. (If you have only a common reset line for all stages, be sure to shorten the reset pulse so it doesn't permanently hang up the register.)

How accurate do the resistors have to be? For registers of ten stages or less, a tolerance of 5 percent is good enough, even though we've shown you 1 percent values. Resistors out of tolerance introduce lower-order odd harmonics, but for most 5 percent variations, these should be 40 decibels below the fundamental or lower.

Note that there will be a DC offset in the output sinewave that usually must be eliminated somehow. The simplest way is with a blocking capacitor as we did with the output capacitor in Figs. 2 and 3. With our CMOS outputs, we have a choice of summing to the positive supply voltage, to ground, or to an op amp's inverting input biased halfway between positive supply and ground. In Fig.

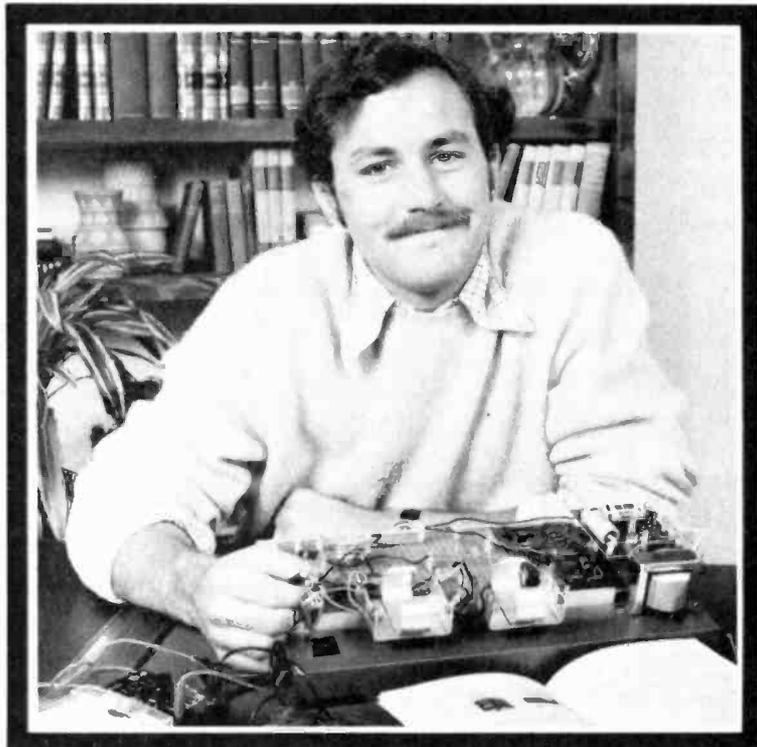**CIE has
a terrific idea
for a few people
who know what
they want.**



If you want success in electronics . . . if you want the skills people are glad to pay for . . . find out about CIE training. It's a terrific idea that can get you on your way to success in electronics troubleshooting.

Let's face it, learning valuable new skills isn't something you just breeze through. Especially in a modern technological field like electronics troubleshooting. You've got to really *want* success if you're going to build your skills properly.

But, oh boy, the rewards when you do! In today's world, the ones who really *know* electronics troubleshooting find that people . . . even industries . . . look for their help.

What about you? How much do you want the thrill of success . . . of being in demand? Enough to roll up your sleeves and work for it?

Why it pays to build troubleshooting skills .

Suppose the automated production controls on an assembly line break down. Imagine how much money the manufacturer can lose when help doesn't come *fast!* And it takes a skilled electronics troubleshooter to move in . . . locate the problem . . . solve it . . . and get the lines moving again.

Or take a TV station. Breakdowns are costly in broadcasting where time is money. Viewers won't sit forever waiting for sound or the picture to come back. Before they change channels, the station needs to get back on the air again — with the help of a skilled troubleshooter.


No question about it. Building new skills in electronics troubleshooting is an investment in your future. It's well worth the effort.

Why you should get CIE to help you do it .

Troubleshooting starts with *ideas* . . . principles. CIE's Auto-Programmed[™] Lessons help you get the idea — at your own most comfortable pace. Step by step at home, you explore each principle — each theory — until you understand it thoroughly and completely. Then you start to use it.

How CIE helps you turn ideas into reality .

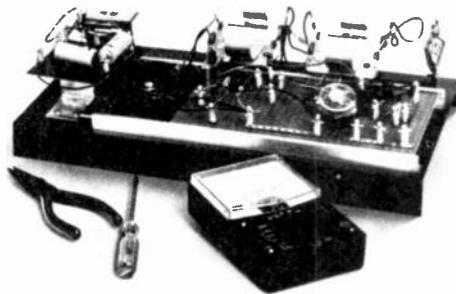If you're a beginner, you start with CIE's Experimental Electronics Laboratory. You actually perform over 200 experiments to help you grasp the basics. Plus you use a 3-in-1 Precision Multimeter to get your first taste of the testing, checking, analyzing steps you take in troubleshooting!



How 3 practical steps help you build troubleshooting skills .

You'll take your first practical step in professional troubleshooting when you build your own 5MHz triggered-sweep, solid-state oscilloscope.

As a trained troubleshooter, you'll use your oscilloscope the way a doctor uses his X-ray machine. As a student, you learn how to "read" waveform patterns on a big, 8cm. x 10cm. screen . . . how to "lock them in" for closer study . . . how to understand and interpret what they tell you.

Your second practical, skill-building step begins when you get your Zenith 19-inch diagonal, solid-state color TV — featuring nine removable modules! Now's your chance to apply the new skills you learned with your oscilloscope!

With CIE's guidance, you perform actual service operations — the kind you'd handle on the job as a trained troubleshooter! Using the TV, you learn to trace signal flow . . . detect and locate malfunctions . . . restore perfect operating standards . . . just as you would with any sophisticated electronics equipment.



Finally, step three rounds out your experience as you work with a completely solid-state color bar generator — actually a TV signal transmitter that produces ten different display patterns on your TV screen!

You study a gated color bar rainbow . . . crosshatch lines . . . dot patterns.

You explore digital logic circuits . . . observe the action of a crystal-controlled oscillator!

This practical, "hands on" training takes concentration and effort. But it's enjoyable and rewarding. And it's a great way to prepare for a troubleshooting career!

Why it's important to get your FCC License .

For some troubleshooting jobs, you *must* have your FCC License. For others, employers often consider it a mark in your favor. It's government-certified proof of specific knowledge and skills!

Almost 4 out of 5 CIE graduates who take the exam get their Licenses. More than half of CIE's courses can prepare you for it . . . and the broadest range of career opportunities!

Free catalog!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name of this magazine. We'll send you a copy of CIE's FREE school catalog — plus a complete package of independent home study information! For your convenience, we'll try to have a representative call to help you with course selection. Mail the card or coupon . . . or write: CIE, 1776 East 17th Street, Cleveland, Ohio 44114.

CIE Cleveland Institute of Electronics, Inc.

1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

YES . . . I want to succeed in electronics. Send me my FREE CIE school catalog — including details about troubleshooting courses — plus my FREE package of home study information!

NAME (please print)

ADDRESS APT.

CITY

STATE ZIP

AGE PHONE (area code)

Check box for G. I. Bill information:
 Veteran Active Duty

Mail today!

RE-90

TABLE I—DESIGN INFORMATION FOR LONGER GENERATORS

STAGES	CLOCK	RESISTORS*	HARMONICS
6	12x	22.1K; 38.3K; 44.2K; 38.3K; 22.1K (1.000) (1.732) (2.000) (1.732) (1.000)	11H (-21 dB) 23H (-27 dB) 13H (-23 dB) 25H (-28 dB)
7	14x	22.1K; 40.2K; 49.9K; 49.9K; 40.2K; 22.1K (1.000) (1.803) (2.248) (2.248) (1.803) (1.000)	13H (-23 dB) 27H (-29 dB) 15H (-24 dB) 29H (-29 dB)
8	16x	22.1K; 41.2K; 53.6K; 57.6K; 53.6K; 41.2K; 22.1K (1.000) (1.849) (2.412) (2.613) (2.413) (1.849) (1.000)	15H (-24 dB) 29H (-29 dB) 17H (-25 dB) 31H (-30 dB)
9	18x	22.1K; 41.2K; 56.2K; 63.4K; 63.4K; 56.2K; 41.2K; 22.1K (1.000) (1.877) (2.532) (2.879) (2.879) (2.532) (1.877) (1.000)	17H (-25 dB) 35H (-31 dB) 19H (-26 dB) 37H (-31 dB)
10	20x	22.1K; 42.2K; 57.6K; 68.1K; 71.5K; 68.1K; 57.6K; 42.2K; 22.1K (1.000) (1.896) (2.618) (3.077) (3.236) (3.077) (2.618) (1.896) (1.000)	19H (-26 dB) 39H (-32 dB) 21H (-27 dB) 41H (-33 dB)
16	32x	22.1K; 43.2K; 63.4K; 80.6K; 93.1K; 105K; 110K; 113K; (1.000) (1.961) (2.847) (3.624) (4.262) (4.736) (5.027) (5.125) 110K; 105K; 93.1K; 80.6K; 63.4K; 43.2K; 22.1K (5.027) (4.736) (4.262) (3.624) (2.847) (1.96) (1.000)	31H (-30 dB) 63H (-36 dB) 33H (-31 dB) 65H (-36 dB)
n	2nx	1; $\frac{\sin \frac{2\pi}{n}}{\frac{\pi}{n}}$; $\frac{\sin \frac{3\pi}{n}}{\frac{\pi}{n}}$; $\frac{\sin \frac{4\pi}{n}}{\frac{\pi}{n}}$; ... $\frac{\sin \frac{(n-1)\pi}{n}}{\frac{\pi}{n}}$	$(2n-1)H (\frac{1}{2}n-1)$ $(4n-1)H (\frac{1}{4}n-1)$ $(2n+1)H (\frac{1}{2}n+1)$ $(4n+1)H (\frac{1}{4}n+1)$

* The resistor values in parentheses are exact ratios; values in ohms are rounded off to stock 1 percent values.

2. we've summed to ground so the emitter follower will have a reasonably constant emitter current and thus not distort the waveform. In Fig. 3 we sum to one-half the supply voltage to minimize the offset at the output even before capacitor coupling.

A final detail is filtering. Complete information on active filters appears in the *Active Filter Cookbook*. For some uses, the harmonics are high enough in frequency that they can simply be ignored. For others, a simple capacitor or two to introduce rolloff is all you need. For more critical uses, a better quality active filter is called for.

Sharp-cutoff low-pass filters using Butterworth or Chebyshev response curves have the

advantages of producing very clean sine-waves with a minimum of circuitry. But these sharp filters have one possible drawback—if the input sinewave is changing or jumping between several frequencies, the filters will introduce *group-delay distortion*, or simple smearing that will generally mess up any sudden input frequency changes. Where you are suddenly or often changing input frequencies, use the higher-order "more gentle" Bessel active filters since Bessel filters are designed to absolutely minimize this form of distortion.

These circuits actually make digital sine-waves easier and simpler and cheaper than analog ones, so there should be all sorts of

things you can do with them. Let us know what uses you come up with. **R-E**

FOR MORE READING:

Generating digital sine-waves—
"Digital Generation of Low Frequency Sinewaves," Anthony C. Davies, *IEEE Transactions on Instrumentation and Measurement*, IM18, No. 2, June 1969 PP 97-105.

Active filters—
The Active Filter Cookbook No. 21168, Howard W Sams, Indianapolis, IN, 46206.



ELECTRONIC LANDMARK GONE

THE "GOLF BALL" 160-FOOT RADOME of the radar system built by RCA in southern New Jersey in 1959, is now a thing of the past. The Air Force reports that it has become unnecessary; its functions are now being performed at other radar sites.

Designed as a prototype for the Air Force's Early Warning system in the North, the 84-foot dome was constructed to withstand the 150-mph winds of the Arctic. It was made with nearly 1,650 interlocking hexagonal pieces, and one pentagonal piece at the top.

The "Golf Ball" was considered the most powerful radar in the world when it was designed. It could track a three-foot object 3,000 miles away. It has been used to track spacecraft, study eclipses, and take precise measurements of objects in space. Among its feats was a more precise determination of the value of the Astronomical Unit, the mean distance between the earth and the sun. This measurement has been valuable to scientists in determining orbital data on satellites and other planets more accurately.

FCC gets petition to permit stereophonic AM broadcasting

Kahn Communications, Inc., of Freeport, NY, has filed a petition asking that the Federal Communications Commission institute rule-making proceedings looking toward regulations that would allow AM broadcasters to operate stereophonically. The petition states that the Kahn AM stereo broadcasting system is completely compatible with standard AM broadcasting and does not degrade present broadcast service; and that it will allow AM broadcast listeners to enjoy stereophonic reception with little or no additional investment in receiving equipment.

The system has been demonstrated several times in on-the-air experiments, notably over WFBR, Baltimore, and was in use by station XETRA, Tijuana, Mexico, for more than three years.

The Kahn system is a type of compatible single-sideband that can be received with two ordinary broadcast receivers, one tuned slightly below and the other slightly above the carrier frequency. A receiver designed to receive this type of AM stereo might have two IF's, one tuned slightly higher in frequency than the other.

An ordinary receiver tuned to the carrier receives both channels with the same results as if the station were using conventional modulation. **R-E**

Gas-Discharge Alarm Clock


A digital clock with a gas-discharge display that uses neon gas to produce a pleasing orange glow. The alarm feature is optional and the clock is powered from a 115-volt AC line

PAUL EMERALD*

THE ELDER STATESMAN AMONG ELECTRONIC displays is the gas-discharge display panel; its ancestry lies in the ubiquitous neon lamp, and later in the Nixie tube pioneered by Burroughs in the 1950's. Newer gas-discharge displays are planar, multi-digit, seven-segment types such as the Burroughs Panaplex series. These displays are evident in a wide variety of display applications, particularly desk-top calculators. Rather than the single formed-wire characters found in the Nixie tubes, the planar displays usually operate in a multiplexed seven-segment format while emitting the same pleasing orange glow.

The gas-discharge panel used in this full-feature clock has six digits and is easily read from 25 feet. The hours and minutes digits are 0.7-in. high while the seconds are 0.5-in. high. This display is coupled with two state-of-the-art IC drivers from Sprague Electric and a Mostek PMOS alarm clock IC to form the many featured electronic clock that is described. The clock can be readily turned into a wall, mantel or bookcase

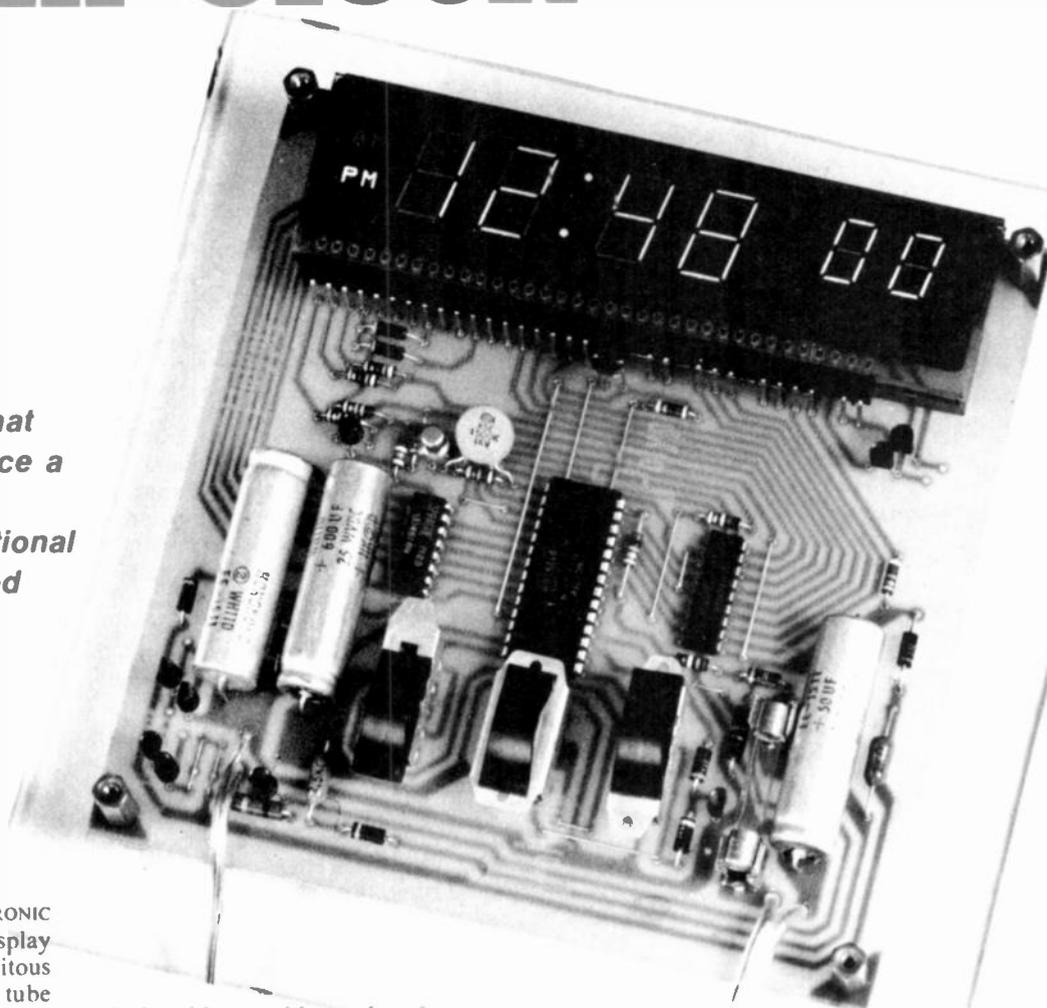* Manager Applications Engineering, Sprague Electric Co., Worcester, MA.



clock—with or without the alarm option.

Display

The Panaplex display requires a minimum ionization voltage of 180 volts for operation, and it's a thin/thick film circuit sandwich with a neon gas mixture between the anode (+) and cathode (-). An orange glow is visible when the neon mixture is ionized by the application of appropriate voltage and current.

The segment (cathode) side of the sandwich is thick-film technology on either a ceramic or, more recently, a glass substrate. All like segments are internally connected (Digit 1a to Digit 2a, D1b to D2b to D3b, etc.) for multiplexed operation. This technique minimizes display connections, MOS IC pins, board wiring, interface electronics, etc. Segments in the display are switched to a negative supply potential, in this case -95 volts. Figure 1 shows

the internal segments and bussed connections between like segments (cathodes) in an exploded view.

The digit (anode) half of the display panel is glass with a thin film conductor such as tin oxide. The anode is switched to a positive potential, in this case +95 volts. The digit (anode) is fundamentally the same as the wire-screen anode of the Nixie tube, or the common terminal (anode or cathode depending upon type) in LED's, etc. Figure 2 shows the connections for the display.

Clock IC

The clock IC is Mostek's MK 50250—a PMOS, multiplexed 28-pin DIP with several available features. The MK 50250 can operate as either a 12-hour 60-Hz clock, or a 24-hour 50-Hz clock. For this clock, the 12-hour 60-Hz option is used. The MK 50250 has several features—alarm (24 hour period), snooze

(10 minute interval), three intensity levels (pulse modulated outputs) and AM/PM capability. Also, with a brown-out or momentary power failure, the clock will alternately flash the AM and PM numerals to indicate that the displayed time is incorrect.

Of the available features, only the AM/PM feature requires any appreciable number of components. Its level of complexity is due to the incompatibility of the MOS chip and the display configuration itself. The schematic diagram (see Fig. 3) shows the interface to the separate AM/PM indicators in the display. This interface consists of transistors Q2 and Q3 and the associated components.

The MK 50250 is actually a 24-hour clock, even though the display never indicates other than a 12-hour cycle. However, the AM/PM is important when incorporating the alarm. The alarm will not go off at 6:30 PM if it is set for 6:30 AM. Hence the need to know if the clock is set to an AM or PM state—a feature not available in electro-

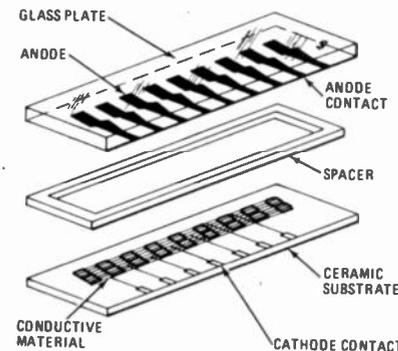


FIG. 1—CONSTRUCTION of the gas-discharge planar display. Like segments of each digit are connected together for multiplexed operation.

mechanical clocks.

Another feature is the three-level display intensity—bright, medium, and dim. The digit and segment outputs are pulse-width modulated to provide three distinct intensity levels to correspond to ambient light conditions. High ambient light gives the brightest display, while low ambient light produces a low duty-cycle strobing of the display and results in a readout that does not glare harshly in a dim or dark room.

The automatic intensity feature is easily accomplished by using only a cadmium-sulphide photocell (R2) and a single resistor (R3). The MK 50250 IC has a three-level intensity control input (pin 11). When this input is pulled toward the V_{SS} potential ($V_{SS} = 16$ volts), the outputs are multiplexed with

the maximum duty cycle (approx. 14.29%) resulting in a bright display. With the intensity input at a level close to the V_{DD} potential (ground) the outputs are pulse modulated to the minimum duty cycle (approx. 2.60%) resulting in a dim display.

The photocell and fixed resistor operate in a manner similar to having a potentiometer connected to the resistor, the resistance of the photocell with the ambient light. Minimum resistance (high ambient light) pulls IC2 pin-11 well toward V_{SS} , while low light levels produce a high resistance and the input voltage is close to V_{DD} . The medium level is when the fixed resistor and photocell are approximately equal. The duty cycle of the intermediate intensity level is approximately 7.20%. The

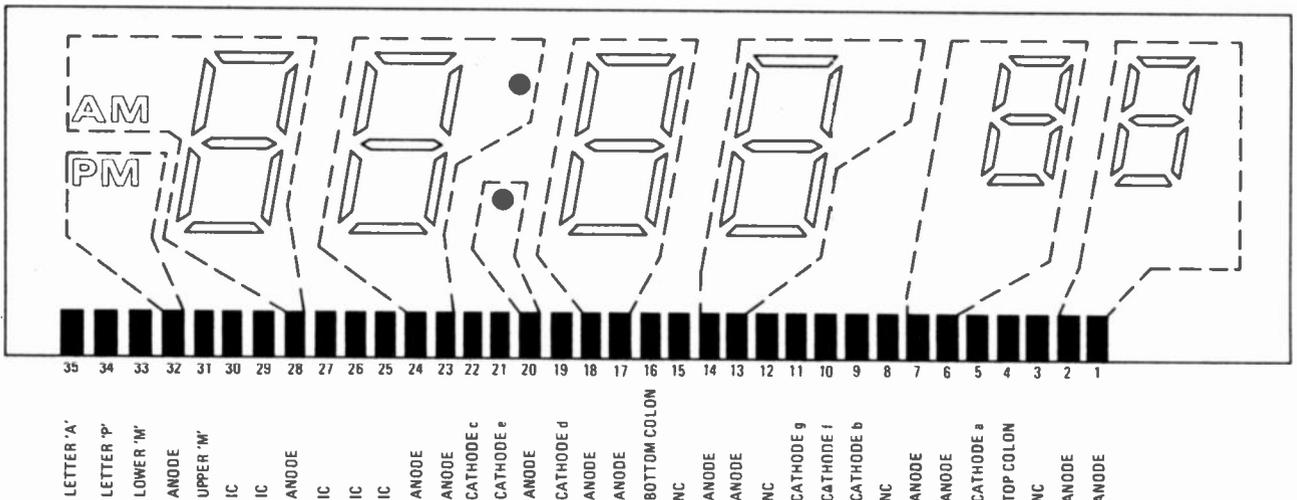
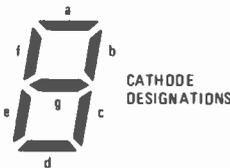


FIG. 2—PIN CONNECTIONS of the gas-discharge planar display.

SETTING CLOCK TIME

- Begin:** TIME SET switch in RUN position, FUNCTION switch in COUNT INHIBIT position.
- Set Minutes:** Push TIME SET switch to SET MINS position. Increment minutes to correct setting.
- Set 10 Minutes:** Quickly slide TIME SET switch to next lowest position when minutes have been set.
- Set Hours:** Quickly slide TIME SET switch to next lowest position where it then will increment to proper hour setting. Note: With AM/PM operation it is a full 24-hour cycle.
- Run:** As proper hour and AM/PM indication is set, push slide switch to bottom position for clock operation.
- Count Inhibit:** Although it is not necessary to start with the FUNCTION switch in this position, it allows the synchronization of the clock with an appropriate time reference.

Note: This clock will operate effectively with a 60-Hz input frequency and an input voltage range from 95 VAC to 115 VAC. Do not exceed 115 VAC since damage to the power supply may result.

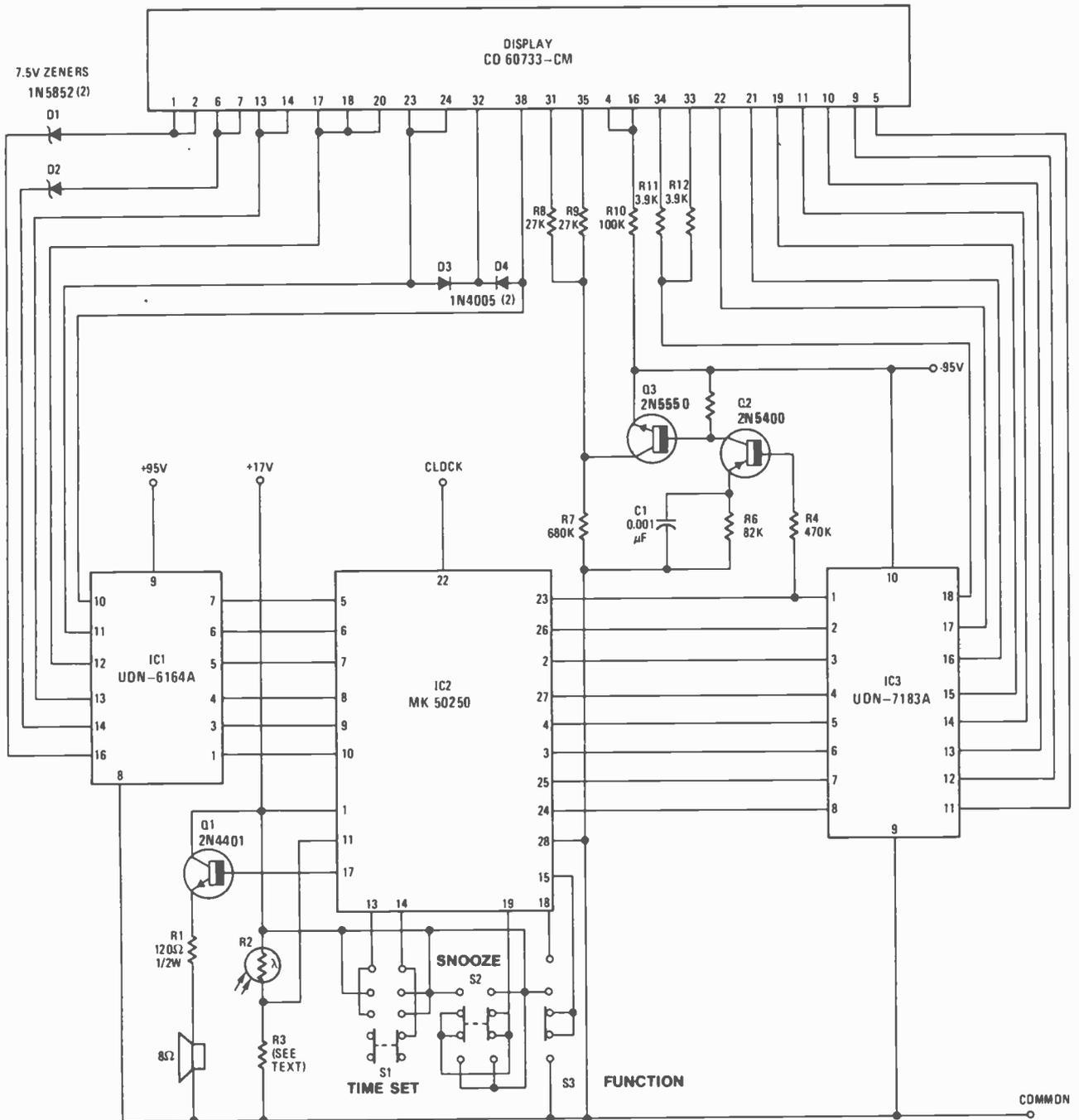


FIG. 3—CLOCK CIRCUIT is built around a MOS IC and has an optional alarm circuit.

All resistors are 1/4-watt, 10%, unless noted.

- R1—120 ohms, 1/2 watt (required for optional alarm)
- R2—CdS photocell, 3.3K at 2 foot-candles, 220K minimum dark resistance, 125 mW at 25°C maximum power (Clairex CL7P5L, Vactec VT801, or equal.)
- R3—See text
- R4—470,000 ohms
- R5, R15—22,000 ohms
- R6—82,000 ohms
- R7—680,000 ohms
- R8, R9—27,000 ohms
- R10—100,000 ohms
- R11, R12—3900 ohms
- R13—180,000 ohms
- R14—2000 ohms, 3 watts (1500 ohms,

- 5 watts with optional alarm)
- R16—2000 ohms, 3 watts
- R17, R18—68,000 ohms, 1/2 watt
- C1—.001 μF, 100V disc
- C2—.01 μF, 125VAC disc (Sprague 125L-S10 or equal.)
- C3—600 μF, 25V electrolytic
- C4, C5—50 μF, 150V electrolytic
- D1, D2—7.5-volt Zener (1N5852 or equal.)
- D3-D7, D9, D14, D15—600-volt, 1A diode (1N4005 or equal.)
- D8—16-volt, 10% Zener (1N5862 or equal.)
- D10-D13—47-volt, 1-watt, 5% Zener (1N4756 or equal.)
- Q1—2N4401 transistor (or equal.)
- Q2—2N5400 transistor (or equal.)
- Q3—2N5550 transistor (or equal.)
- IC1—UDN-6164A (Sprague)

- IC2—MK50250 (Mostek)
- IC3—UDN-7183A (Sprague)
- S1—2 pole, 4-position slide switch
- S2—2p, 3p, spring return
- S3—1 pole, 4-position slide switch
- Misc: PC board, display (Burroughs CD60733-CM or Cherry Electric W06-0001), display connector, 1/4-ampere fuse, fuse clips, wire, solder, etc.

The following parts are available from AVTEK Electronics, P.O. Box 457, Andover, MA 01810: A complete kit of parts that includes a PC board and all other electronic components—\$59.50; and a partial kit that includes a PC board, three IC's, three switches, photocell, display and connector—\$39.50. A case consisting of plastic front and back covers plus hardware is also available for \$7.50.

current in each segment is the same at any intensity level, but the reduced duty cycle results in a reduction of average light emitted. The value of the fixed resistor R3 can vary widely and depends on the type of enclosure used. If the photocell is exposed directly to ambient light, then R3 will be between 4K and 5K ohms. If a colored filter covers the photocell, then R3 will be between 27K and 30K ohms. The correct value should be determined by experimentation.

Another simple feature is the COUNT INHIBIT position of the function switch. Switching to this inhibit position allows "locking up" the clock time and setting the clock in synchronization with a time standard such as WWV. From that point on, the clock is at the mercy of the power company for short-term accuracy, but corrections are made by the power company to provide long-term accuracy.

Another optional feature is the alarm. The alarm provides a 400-600 Hz "beep-off-beep" alternating tone. The clock IC requires only a buffer transistor (2N4401 or equiv.), a 100-ohm 1/2-watt resistor to limit current and the necessary transducer (speaker). Additionally, you may also wish to add the SNOOZE switch while the alarm is operating deactivates the alarm for a period of ten minutes, after which the alarm will go off again.

Interface circuits

The interface circuits to convert low-level logic to the high-voltages necessary to drive gas-discharge displays has been a difficult problem for the IC industry for several years, but a new family of Sprague display drivers has dramatically simplified this situation. Previous schemes of either discrete components or discrete components coupled with IC's have almost always required large numbers of components or were expensive due to the rather exotic process technologies. A joint Sprague/Burroughs effort has resulted in a much simpler, less expensive interface to these high-voltage displays. This new IC series is employed in this clock to minimize components and simplify the clock circuitry.

A detailed explanation of the anode (digit) and cathode (segment) circuit interface is rather lengthy and will not be presented. However, any one interested may easily obtain applications information by requesting MAR75-1 from their Sprague dealer.

Fundamentally, the digit and segment IC's employ high-voltage bipolar processing and the use of thin-film resistor technology on the surface of the IC chip to accommodate all the functions necessary in gas-discharge interface schemes. The level shifting from the low level (low voltage) logic to the display panel

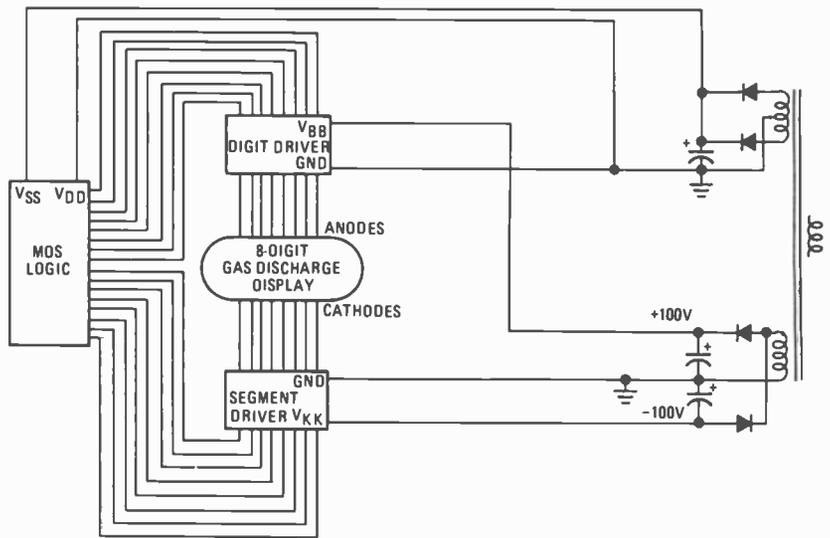


FIG. 4—SIMPLIFIED SCHEMATIC of the split power-supply used to drive the gas-discharge display.

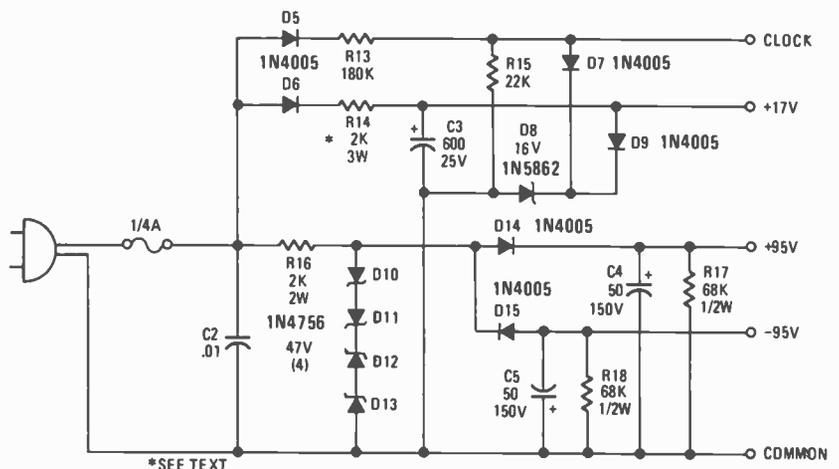


FIG. 5—POWER SUPPLY has split high-voltage supply to drive display and low-voltage source for IC's. Timebase is derived from low-voltage supply.

is done by high-voltage transistors (PNP's in 7100 series segment circuits and NPN's in 6100 series digit circuits). Necessary input current limiting, segment current limiting, pull-up or pull-down resistors are included via chrome silicon resistors added to the IC. Also, the appropriate reference voltages are internally generated.

As the result of this circuit breakthrough, this display may be used with only two IC's—one digit circuit and one segment IC—while previous discrete approaches might have resulted in 50-75 components to perform the same function. Figure 4 shows the basic interface from the clock IC to the display. Level shifting to a positive supply (approx. +100V) is done on the digit side, while the DC level shifting on the segment side to a negative voltage (approx. -100V) provides a total of approximately 200V (+100V and -100V). This split supply technique allows the use of high-voltage bipolar processing using PN diode isolated circuitry rather than more expensive solutions such as dielectric isolation.

Formerly, supplies for gas-discharge panels were single-ended (either +200V or -200V etc.) rather than the use of a split technique to provide the necessary ionization voltage.

Power supply

The schematic diagram of the split power-supply is shown in Fig. 5. The high-voltage split power-supply uses Zener diodes D10-D13 to limit the AC peaks to ± 95 volts. This voltage is then half-wave rectified by diodes D14 and D15 and filtered to provide the +95V and -95V source for the display.

The low-voltage supply for the alarm circuit and clock IC is derived from the AC line voltage. The line voltage is half-wave rectified by diode D6 and filtered by R14 and C3. Zener diode D8 and diode D9 regulates the output of the filter to produce the +17V source. R14 is a 2000-ohm 3-watt resistor. The resistance of R14 should be reduced to 1500-ohms when the alarm option is used. This prevents the alarm circuit from

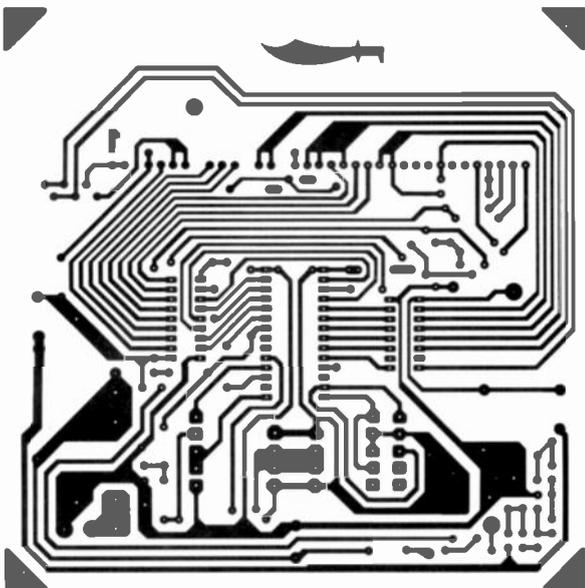


FIG. 6—FOIL PATTERN of PC board shown half-size.

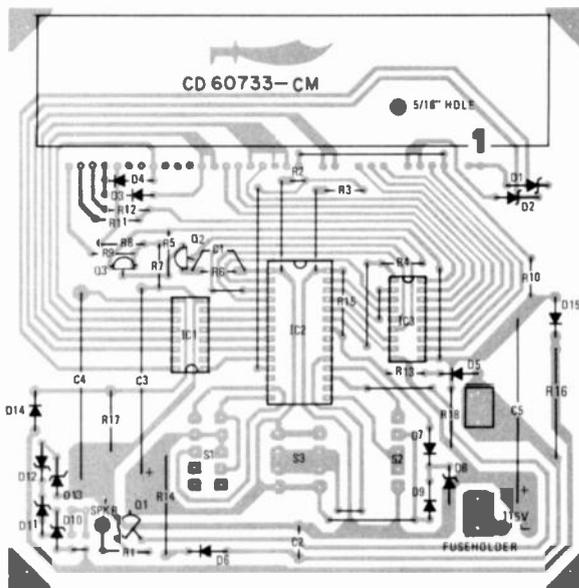


FIG. 7—COMPONENT PLACEMENT diagram shown from component-side of board.

overloading the 17V source and prevents the clock IC from issuing a power-interrupt indication (AM/PM indicators flash) when the alarm sounds.

The 60-Hz timebase for the clock IC is derived from the AC line voltage. Diode D7 clamps this signal to the 16-volt drop developed across Zener diode D8.

Construction

Assembling the clock is rather easy, and begins with installing the eleven jumper wires. The foil pattern for the single-sided PC board is shown in Fig. 6, while the component placement diagram is shown in Fig. 7. A word to those concerned with neatness: use the

employed (board will take these also) as shown.

Slide switches may be mounted toward front or rear. A wall clock would normally omit the SNOOZE switch and have switches soldered on the foil side of PC board. If switches are to be out of sight (rear) they must be spaced off the board to allow soldering. Figure 8 shows the functions of the three slide switches.

Slowly insert the display into connector from one end—proper position is with the small, center contact tab of connector facing upward or against the front (anode) position. These slip-in connectors are rather fragile and care must be taken to prevent bending

anode and cathode plates, bend the leads at the point where they exit the connector. When the leads have been properly bent, remove paper from double-sided tape (or use alternate adhesive) to secure the display unit to the PC board. Solder all leads after checking to be certain that all are properly lined up to appropriate holes. Trim all leads again. Solder in line cord and insert fuse (1/4 A).

Prior to inserting the three IC's, it is desirable to measure three supply-voltages to prevent possible damage to the IC's from faulty or improperly oriented components. Use *caution!* The PC board connects to one side of the 115 VAC line for its ground; use an isolation transformer if available. Use a VOM and be certain to rest the PC board on an insulated surface when measuring voltages.

Connect the meter ground-lead to the junction of C4 and R17 and measure $+95V \pm 1.7V$ across C4; and measure $+17V \pm 0.2V$ at the junction of C3 and R14.

Reverse the meter connections prior to making the measurement at the junction of C5 and R18; this should measure $-95V \pm 1.7V$. If all three voltages are correct, then the IC's may be soldered into the board. If the voltages are not correct, then check diode and capacitor polarities, etc. Be certain that IC1, IC2 and IC3 are oriented correctly as shown in Fig. 7.

Check the operation of the clock. Plug it into a 115-volt 60-Hz AC line and, if available, use an isolation transformer. The display should ionize and indicate "AM 12:00:00." The display will hold in this state until the time is set. For setting to the exact time, use the count inhibit function and lock the clock to a reference standard such as WWV. From that point the accuracy is maintained by the local power company.

R-E

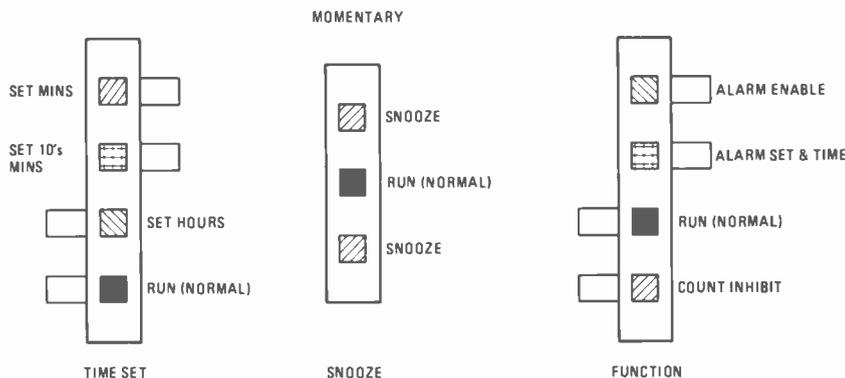


FIG. 8—SWITCH FUNCTIONS of the three slide switches.

trick employed by any fussy technician—stretch the jumper wire to straighten it before cutting to length (stretch 12" to 15" lengths). Push the leads through the board and bend them slightly to retain the jumper until soldering.

Mount the components on the PC board as shown in Fig. 7 and solder. Note: conservative use of 30 and 33V Zeners in the power supply requires 6 Zeners, but two may be omitted (substitute a jumper) if 1-watt 47-volt types are

contacts, etc. After mating display and connector, use either double-sided adhesive tape or other adhesive to mount display to 1/8" spacer for raising display to proper height. Begin at one end of display leads and slip them into proper holes in PC board. Four leads have no holes; bend them away initially—after display is fully mounted and soldered they can be cut off.

Display leads must be bent 90°. With connector fully inserted between display

If you can't go to college for your career in electronics —read this!

CREI brings college-level training to you with eight educational advantages, including special arrangements for engineering degrees

The best way to qualify for top positions and top pay in electronics is obviously with college-level training. The person with such training usually steps more quickly into an engineering level position and is paid considerably more than the average technician who has been on the job several years.

A regular college engineering program, however, means several years of full-time resident training—and it often means waiting several years before *you can even start your career*. This, of course, is difficult if you must work full time to support yourself and your family.

If your career in electronics is limited without college-level training, take a look at the advantages a CREI home study program can offer you.

1. Convenient Training

CREI brings the college to you. Through the convenience of home study, you receive exactly the same level of training you will find in any college or university offering programs in electronic engineering technology. With CREI, however, you can "go to college" whenever you have spare time at home or on the job.

2. Specialized Programs

With CREI, you enjoy the advantage of *specialized* training. That is, your program will include only those courses directly applicable to your career in electronics. We omit such courses as English, social studies and other subjects, which are usually required in resident schools. Therefore, with CREI, you move ahead faster to the more interesting and useful part of your training.

3. Practical Engineering

CREI programs give you a *practical engineering* knowledge of electronics. That is, each part of your training is planned for your "use on the job." By using your training, you reinforce the learning process. And by demonstrating your increased knowledge to your employer, you may qualify for faster career advancement.

4. Engineering Degrees

CREI offers you a number of special arrangements for earning engineering degrees at recognized colleges and universities. You can earn college credit while you are taking your CREI program or apply later, whatever is best for your career plans.

Career Training at Home

5. Unique Laboratory

Only CREI offers you the unique Electronic Design Laboratory Program. This complete college laboratory makes learning advanced electronics easier and it gives you extensive practical experience in many areas of engineering, including design of electronic circuits. No other school offers this unique program. It is a better "Lab" than we have found in many colleges. And the professional equipment included in the program becomes yours to keep and use throughout your professional career.

6. Wide Program Choice

CREI gives you a choice of specialization in 14 areas of electronics. You can select exactly the area of electronics best for your career field. You can specialize in such areas as computer electronics, communications engineering, microwave, CATV, television (broadcast) engineering and many other areas of modern electronics.

7. Prepared by Experts

Experts in industry and technical organizations of government develop CREI programs. Each part of your training is developed by a recognized expert in that area of electronics. That means you get the most up-to-date and practical instruction for your career.

8. Industry Recognition

That CREI training is recognized by industry and government is evident from the fact CREI provides training to advanced technical personnel in over 1,700 technical organizations. Many subsidize the training of their employees with CREI. If there is any question about the advantages of CREI training for you, ask your employer or any engineer to evaluate the outline of a CREI program for you.

Other Advantages

Of course, there are many other advantages to CREI training. For example, throughout your training, CREI's staff gives you personal instruction for each step of your program. And in many industrial areas, both in the U. S. and abroad, CREI Field Service Representatives provide a number of important personal services for your training and your career.

FREE Book

There isn't room here to give you all of the facts about career opportunities in advanced electronics and how CREI prepares you for them. So we invite you to send for our free catalog (if you are qualified). This fully illustrated, 80 page catalog describes in detail the programs, equipment and services of CREI.

Qualifications

You may be eligible to take a CREI college-level program in electronics if you are a high school graduate (or the true equivalent) and have previous training or experience in electronics. Program arrangements are available depending upon whether you have extensive or minimum experience in electronics.

Send for this **FREE Book** describing your opportunities and **CREI college-level programs in electronics**



Mail card or write describing qualifications to

CREI **CAPITOL
RADIO
ENGINEERING
INSTITUTE**

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue Northwest
Washington, D.C. 20016

Accredited Member National Home Study Council

GI Bill

CREI programs are approved for training of veterans and servicemen under the G.I. Bill.



Improved Noise-Reduction for Tapes



Super-ANRS—developed by JVC and incorporated in several of their newly introduced stereo cassette decks—provides improved noise-reduction and increased dynamic-range capability

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

AS JUST ABOUT EVERY CASSETTE DECK OWNER knows by now, noise-reduction systems such as Dolby and ANRS (the Automatic Noise Reduction System developed by Japan Victor Company) increase the dynamic range capability of the cassette recording format by lowering the noise threshold, above which the softest recorded sounds can be heard. Both of these systems increase the recording level of high-frequency sounds when those sounds are part of a soft passage of music. The amount of high-frequency pre-emphasis during the record process is dependent upon the average signal level being recorded and varies continuously. Loud passages, for example, undergo no pre-emphasis whatever, while softest passages undergo the greatest amount of pre-emphasis during the record process.

During playback, voltage-controlled frequency-sensitive amplifiers reverse the process, attenuating high-frequency playback by the amount required to restore flat frequency-response at all loudness levels. Typically, this process improves the signal-to-noise ratio above about 5 kHz (where tape hiss is most audible) by approximately 10 dB. While most people think of this action in terms of noise reduction, the process can also be thought of as increasing the dynamic-range capability. The boundaries of dynamic range in tape recordings consist of the low residual tape noise-level at one extreme and the tape saturation level at the other extreme. If we think of the recorded program as a ship passing under a bridge, taller ships can be accommodated either by "low-

ering the water or raising the bridge." Noise reduction systems, in this analogy, "lower the water."

Upward dynamic expansion

In an attempt to "raise the bridge," JVC has now come up with a modified version of their original ANRS system that they call Super-ANRS. In order to understand how it works, it is necessary to review some of the principles of tape recording. During the recording process, input signals are equalized so that high-frequency signals are boosted by a prescribed amount. This is done so that the playback response will be reasonably flat beyond the point at which the playback-head response begins to fall off. The principle of record equalization is illustrated in the graph of Fig. 1.

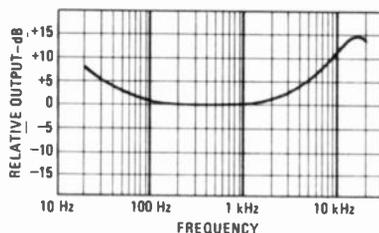


FIG. 1—TYPICAL RECORD EQUALIZATION applied to cassette systems to compensate for head and tape characteristics.

Because cassette recorders operate at the slow speed of 1½ IPS and use a narrow tape, the record equalization used in cassette decks pre-emphasize high frequencies much more than does the equalization applied to faster operating open-reel decks. As a result, tape saturation at high frequencies occurs more

readily. Figure 2 illustrates this effect. At low recording levels, playback output level is linear with respect to record input level for both the 1 kHz and 10 kHz signals. But, at higher recording levels, the 10-kHz signal saturates the tape at a level that is nearly 15 dB lower than the saturation point for the 1 kHz signal. If the music you try to record contains a high percentage of higher frequencies (music dominated by cymbals, piccolo or even guitar sounds that have high-frequency transients), the

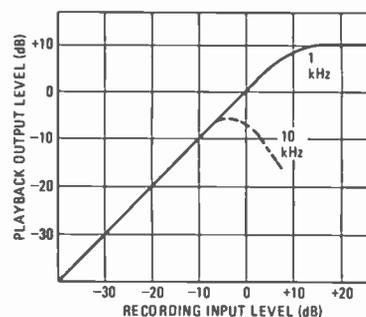


FIG. 2—CASSETTE TAPE saturates more readily at high-frequencies, as this linearity curve shows.

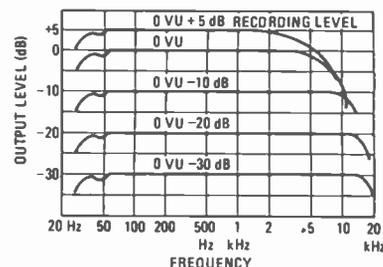


FIG. 3—RECORD/PLAYBACK frequency response of cassette tape.

dynamic range of the tape is exceeded and when the recording is played back, sounds are distorted.

This point is further illustrated in the curves of Fig. 3. If you try to measure the response (record/playback) of a cassette deck using a record level of 0 dB (as indicated on the record level meters) or even +5 dB, high-frequency response rolls-off above about 5 kHz (for 0 dB recording level) or at an even lower frequency for the +5-dB record level. It is for this reason that most manufacturers quote the record/playback frequency response of their products on the basis of a -20 dB or even a -30 dB recording level. At this lower recording level, the overall response is improved because the high frequencies are not saturating the tape, even with record equalization added. But, there are moments in musical recording when high-frequency musical peaks do occur and often they occur too rapidly to be observed on the record-level meters.

How super-ANRS works

Figure 4 is a simplified block diagram of the Super-ANRS principle developed by JVC. Basically, the circuit consists of a variable impedance circuit that determines the amount of high-frequency boost of the regular ANRS (noise reduction) filter circuit at the left plus a second Super-ANRS filter circuit. The super-ANRS filter circuit shares the common variable impedance elements of the regular ANRS circuit. At low signal levels, the variable impedance

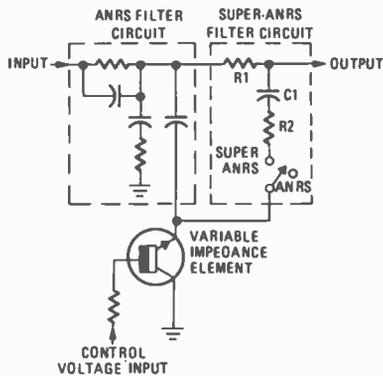


FIG. 4—SUPER-ANRS CIRCUIT is added to basic ANRS circuit and is controlled by a variable impedance.

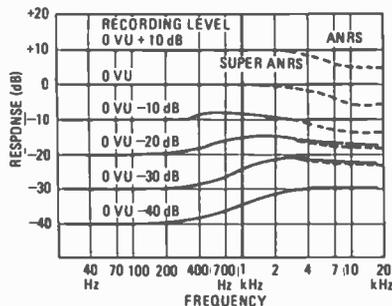


FIG. 5—RECORDING CHARACTERISTICS of the ANRS and Super-ANRS circuits.

risers in value (determined by the control voltage) and the record response at various input levels is made to vary in accordance with the solid lines of Fig. 5. When the selector switch is thrown to Super-ANRS, an additional high-cut filter element formed by R1, C1 and R2 is introduced. This additional high-cut filter compresses or attenuates high-level high-frequency signals in the recording process as indicated by the dotted lines of Fig. 5. Low level operation of the regular ANRS filter remains the same. The extra Super-ANRS circuit selectively compresses the signals with up to 6 dB for a +10 dB (as indicated on the meter) signal at 10 kHz.

During playback, exactly the reverse process takes place, as shown in Fig. 6. Low-level high-frequency signals are

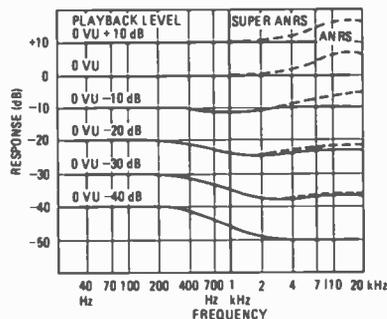


FIG. 6—PLAYBACK CHARACTERISTICS of the ANRS and Super-ANRS circuits.

correspondingly attenuated by the action of the regular ANRS circuit (restoring the flat frequency-response at moments of low-level reproduced music) while high-level high-frequency signals that had been compressed in the Super-ANRS recording process are now expanded during playback (shown by the dotted lines in Fig. 6). The 10-kHz signal that was compressed by 6-dB in recording (at a 10-dB level) is now expanded by precisely the same 6 dB and is therefore reproduced at exactly the input of the tape deck.

The use of ANRS together with Super-ANRS therefore provides a double benefit. ANRS extends the dynamic-range downwards as it reduces tape noise-level, while Super-ANRS also extends the dynamic-range capability upwards. An illustration of the overall effect of both circuits is shown in Fig. 7. The double process reduces high-level sounds and boosts low-level sounds during recording. The sounds are processed in such a way that loud sounds (which might exceed the tape saturation level) and soft sounds (which might be obscured by tape hiss) can now be recorded within the available dynamic-range boundaries of the tape. In playback, the system restores the original levels with tape hiss significantly reduced and the effective saturation level raised.

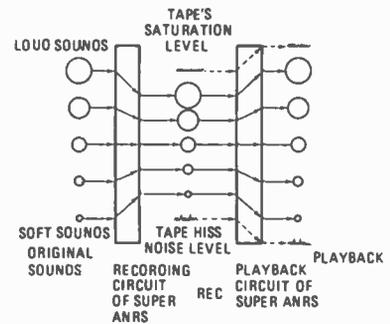


FIG. 7—COMPRESSION/EXPANSION characteristic of Super-ANRS circuit. The size of the circles are proportional to the signal levels.

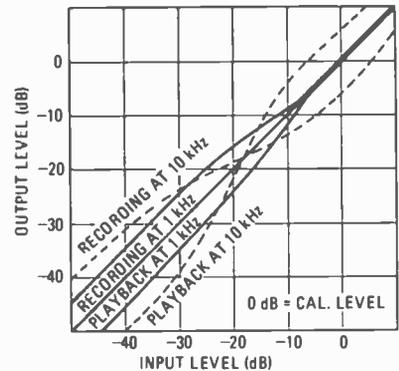


FIG. 8—INPUT/OUTPUT characteristics of the Super-ANRS circuit.

Figure 8 illustrates the action of Super-ANRS in terms of input/output characteristics. Note that for a 10-kHz signal, the system actually switches over from an expand-compress process (below levels of about -20 dB) to a compress-expand system (at levels above -20 dB).

Figure 9 compares the record/playback linearity characteristics of normal tape for a 10-kHz signal with and without the Super-ANRS circuit acti-

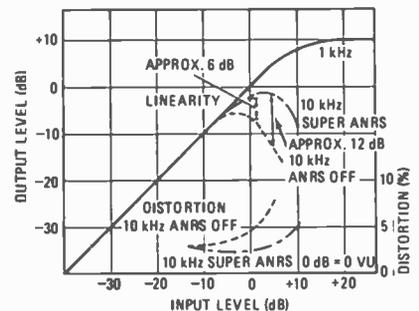


FIG. 9—RECORD/PLAYBACK linearity characteristics of cassette tape with and without Super-ANRS

ated. With the circuit turned off, the 10-kHz curve is the same as that plotted earlier in Fig. 2. With Super-ANRS in the circuit, the linearity for this 10-kHz signal is significantly increased and, while it still does not approach the linearity of a 1-kHz signal, the output level for a +5-dB input level is increased by approximately 12 dB. The lower two curves of Fig. 9 show distortion versus input level. For a 10-kHz signal at 0-dB record level, distortion

continued on page 104

Radio-Electronics

Tests Crown IC-150A Preamplifier

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR


ANYONE FAMILIAR WITH CROWN'S EARLIER model IC-150 will immediately realize that the new IC-150A is a totally redesigned unit, both in terms of front-panel arrangement and internal circuitry. The newer preamplifier-control unit, shown in Fig. 1, is supplied with a vinyl-clad black wrap and can be operated free-standing. Additionally, it can be mounted in an optionally available wood cabinet, custom mounted in a cabinet panel of your choice, or rack-panel mounted by means of angle brackets and hardware supplied with each unit. When rack-mounted, the unit is light enough so that no support shelf is required.

Major controls along the upper section of the panel include a SELECTOR switch (with two PHONO settings, a TUNER position and three AUX positions plus two TAPE positions), BALANCE control, dual-concentric BASS and TREBLE controls, a unique continuously variable PANORAMA control (that makes a smooth transition from stereo, to mono, to reverse stereo) and a precision switch-type VOLUME control calibrated in 2-dB steps from 0 dB to -58 dB. A pushbutton located between the VOLUME and SELECTOR switches activates the loudness control circuitry, while a similar pushbutton between the BASS and TREBLE controls serves to bypass the tone control circuitry completely for absolutely flat response. Five pushbuttons centered along the lower, black section of the panel take care of two tape monitor circuits, low and high filters and the power on/off function. At the lower left are a pair of single-circuit phone jacks for front panel connection to the AUX 3 inputs, while at the extreme lower right is a stereo (two-circuit) phone jack for monitor output.

The rear panel is shown in Fig. 2. No less

than six convenience AC outlets are provided, five of which can handle a combined AC drain of 25 amperes. Input and output jacks are all mounted on a horizontal surface, but descriptive legends corresponding to these jacks are screened on the rear

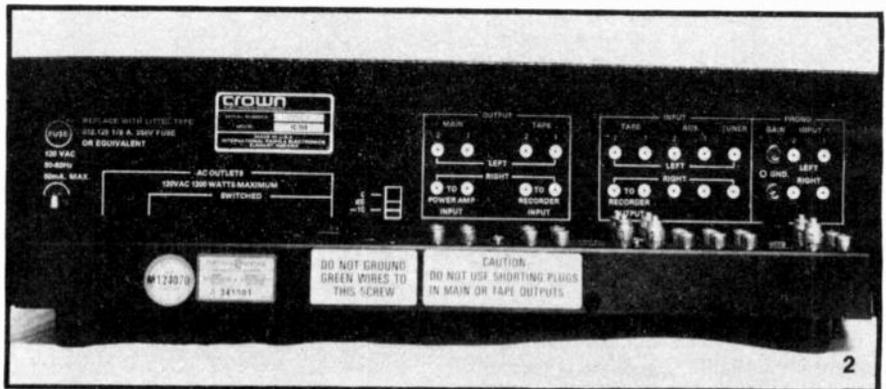too, that since there are two pairs of main output jacks, signals could be fed to two separate stereo power amplifiers, if desired, or to a power amplifier and a headphone amplifier as shown in the connection diagram.



vertical surface for legibility. Near the pairs of PHONO inputs are screwdriver adjustment controls that permit you to vary the gain of the phono preamp section over a 20-dB range, with maximum sensitivity being 0.7 mV for rated output. In all of our subsequent tests, these controls were set to provide rated output (2.5 volts) from the main outputs with a phono input level of 2.5 mV. A slide-switch changes the gain by a fixed 10 dB.

Circuit description

The number and type of equipment that can be connected to the IC-150A is extremely diverse. As illustrated in the connection diagram of Fig. 3, as many as four different tape decks could be used with the system, along with two turntables and a tuner. Only two decks could be monitored however if they are of the three-headed variety. Note,

A signal-flow block diagram of the IC-150A is shown in Fig. 4. The electronics of the IC-150A are built around five integrated circuits that provide the equivalent of 89 transistors, 25 FET's, 3 Zener diodes and 12 diodes. In addition, 7 bipolar transistors, 1 FET, 1 Zener and ten diodes are used in discrete form. The output of the IC-150A is muted for several seconds after turn-on to protect speakers against "pops". The phono-preamplifier section employs a low-noise complementary design, using an LM301AN operational amplifier IC. Tone control and voltage amplifiers are LF356H FET op-amp IC's; one per channel.


Two major circuit boards are used in the construction of the IC-150A: one containing the phono-preamp circuitry, the other for high-level amplification, tone control circuits and power-supply parts. The regulated power-supply delivers plus and minus 18 volts. The master VOLUME control is positioned directly following the high-level input circuits, followed by the BALANCE and PANORAMA controls that precede the tone control amplifier stages. The 10-dB output attenuator is in the form of a precision voltage-divider arrangement just preceding the actual output terminals. Muting relay contacts (that delay audio turn-on) follow all the active signal-handling elements of the circuit.

Laboratory measurements

A summary of our test measurements is shown in Table I and can be readily compared with manufacturer's claims. At

MANUFACTURER'S PUBLISHED SPECIFICATIONS:


Frequency Response: High Level: ± 0.6 dB from 3 Hz to 100 kHz; Phono (RIAA): ± 0.5 dB. **Phase Response:** High Level: $+1^\circ$ to -12° , 20 Hz to 20 kHz; Phono: $\pm 5^\circ$, 20 Hz to 20 kHz. **Hum and Noise:** Phono: 85-dB below 10 mV input; High Level: 95-dB below rated output. **THD:** Less than 0.0005% at rated output with 1-kHz input; 0.05% from 20 Hz to 20 kHz. **IM Distortion:** Less than 0.002%. **Input Gain:** Phono: adjustable from 30 to 50 dB; High Level: 20.8 dB ± 0.2 dB. **Phono Overload:** 33 to 330 mV, depending upon gain setting of input. **Output Level:** 12-volts maximum before overload; 2.5 volts, rated. **Tone Control Range:** ± 15 dB at 30 Hz (bass) and 15 kHz (treble). **Filters:** Rumble: -3 dB @ 24 Hz, 6 dB/octave; Scratch: -3 dB @ 5 kHz, 12 dB/octave. **Power Requirements:** 2 watts @ 120V or 240V, 50-400 Hz. **Dimensions:** 19-inches standard rack mount; $17 \times 5\frac{1}{4} \times 8\frac{1}{8}$ -inches behind panel. **Weight:** 10 lbs (20 lbs in optional walnut-finish cabinet).

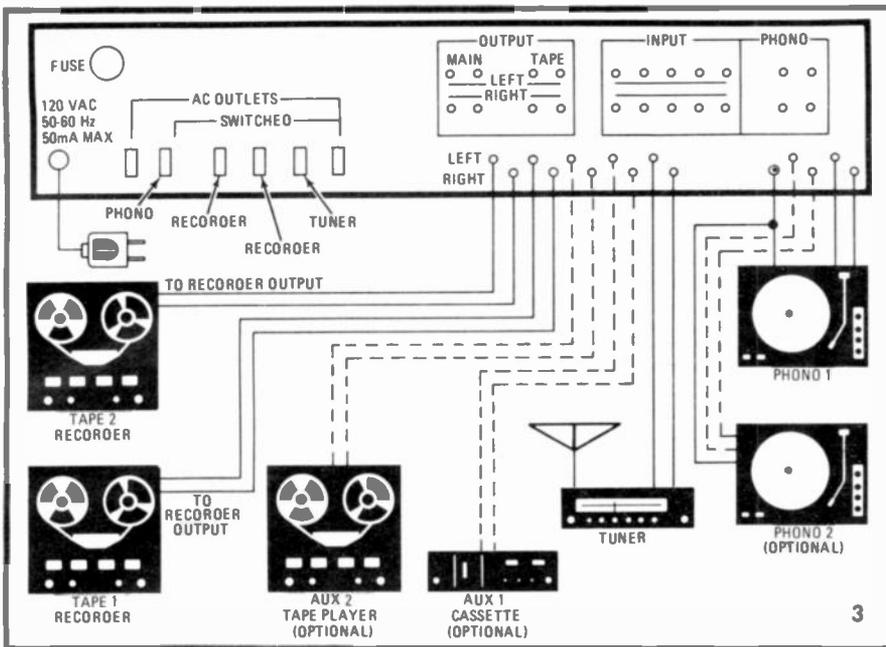

maximum deviation occurring at the extreme low end of the audio spectrum. Our phono hum measurement of 72 dB is referred to an input sensitivity of 2.5 mV. Translated to a 10 mV input (as specified by Crown), the number becomes 84 dB, or within a hair's breath of the 85 dB claimed. Both Crown's claim and our measurements were made without any weighting network applied. Frequency response for the high-level inputs was within 1-dB from 4 Hz to 37 kHz, and hum-and-noise for these inputs was exactly 95-dB below rated output as claimed.


As stated earlier, all of our phono performance measurements were made with respect to a 2.5-mV input for an output of 2.5-volts (a total system gain of 60 dB), but we did check the range of the gain adjustments for phono and determined that overall gain could be varied from 70 dB to 50 dB so that the phono input-signals ranging from 0.79 mV to 8.0 mV could be adjusted to produce the rated output.

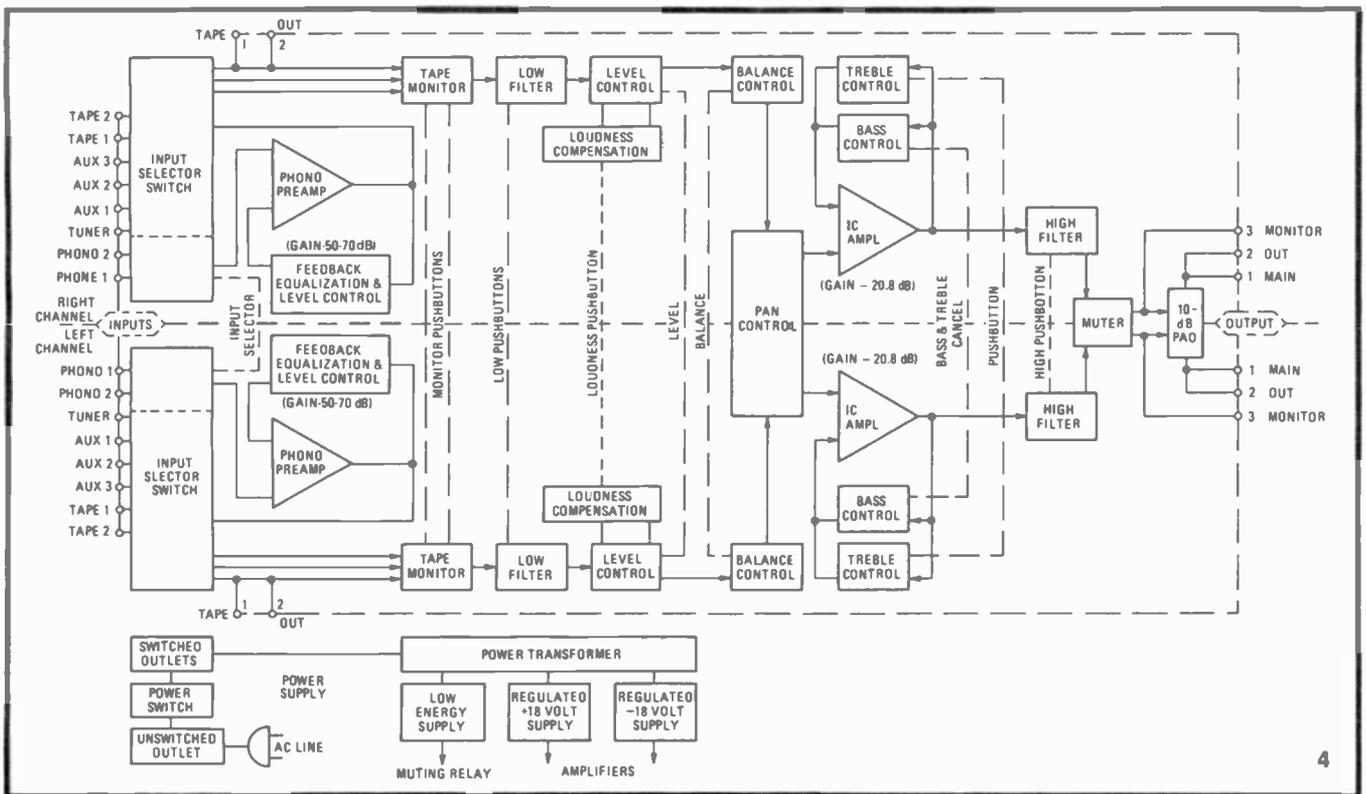The range of the BASS and TREBLE controls are shown in the composite scope photo of Fig. 5, with a flat-response trace superim-



mid-frequencies, the maximum output obtained before overload exactly equaled the 12.0-volts claimed. The harmonic distortion observed for rated output (2.5 volts) is undoubtedly produced by our signal source, which is known to contain around 0.002% THD. Thus, we cannot substantiate Crown's claim of 0.0005% for this specification. Obviously, at these distortion levels, the readings become a bit academic anyway since no one is likely to hear this level of distortion under actual listening conditions. Note, however, that there is a tendency for THD to increase, however slightly, at the high-frequency end of the spectrum where we did measure 0.047% for rated output.

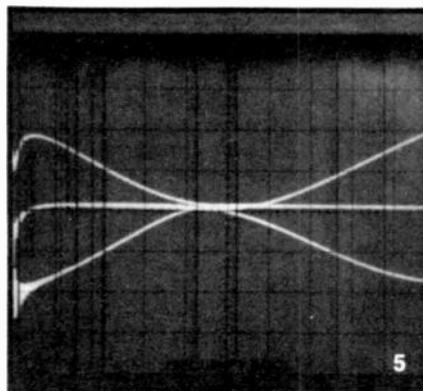
The phono equalization was accurate to within 0.4 dB of the RIAA curve, with



posed for reference. High and low filter response corresponds exactly to manufacturer's claims, with the rumble filter exhibiting a 6 dB-per-octave slope and the high-cut filter attenuating frequencies above about 5 kHz at a rate of 12 dB-per-octave.

Figure 6 serves to illustrate two important features of the IC-150A. First, of course, we see the loudness control compensation at 10 dB intervals. This loudness compensation differs somewhat from the so-called Fletcher-Munson curves that have been traditionally used as a basis for loudness compensation at low listening-levels. These new curves are based upon more recent work by Robinson and Dadson (1956) which has been adopted by the International Standards Organization. Note, in particular, that no high-frequency

emphasis is introduced at low levels, since very little of such emphasis was found to be needed for most listeners in the more recent investigations. In order to use this loudness control most effectively, it is necessary to calibrate your master VOLUME control on the IC-150A so that its maximum clockwise position corresponds to a listening level of around 100 dB SPL. Allowing for the many variables such as power amplifier gain, speaker efficiency and room size, this requires that all input program source levels be normalized in level to deliver that final sound pressure level. This is easily done with respect to phono program sources (thanks to the gain controls included for this circuit), but unless the amplifier used with the IC-150A has input level controls as well and unless your tuner and tape decks are equipped with output level controls, all the effort and precision built into this loudness compensation control may be for naught.

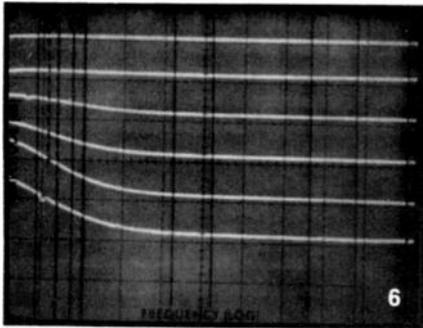

The second purpose served by the scope photo of Fig. 6 is to illustrate the precise calibration of the VOLUME control of the IC-150A. We did not reduce this control by observing successive 10-dB reductions in output, but simply by reading the numbers on the front panel that surround the knob: 0 dB, -10 dB, -20 dB, -30 dB, -40 dB and -50 dB. Since each vertical division on our spectrum analyzer corresponds to an amplitude difference of exactly 10 dB, you can see how extremely precise that master VOLUME control really is.

Using the IC-150A

Our overall comments concerning the performance of Crown's IC-150A will be found along with an overall product analysis in Table II. Control action is smooth and positive, though we did run into a bit of trouble with the tone defeat switch on our sample, which seemed to exhibit an intermittency during its first few pushes. This problem cleared up by itself and may have been caused by a bit of dirt or dust that had gotten into the contacts during shipment and/or packing. While the front panel (and our description of it) seems devoid of any indicator lights, there is, in fact, a camouflaged red spot of light that seems to shine right through the lower section of the panel when power is applied. In general, the IC-150A gives one a feeling of a total control over one's music without imposing redundancy of controls, switches, and what have you. Such front panel simplicity and flexibility denotes a good sense of human engineering on the part of the designers of the IC-150A who are to be commended for improving upon their own earlier IC-150 which was a very fine preamplifier-control unit to begin with.

R-E

TABLE I
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Crown International

Model: IC-150A

PREAMPLIFIER PERFORMANCE MEASUREMENTS

	R-E Measurement	R-E Evaluation
OUTPUT VOLTAGE MEASUREMENTS		
Rated output (volts) (per mfr.)	2.5	
Maximum output before overload (V)	12.0	Excellent
DISTORTION MEASUREMENTS		
Harmonic distortion, rated output, 1 kHz (%)	0.0025	Superb
Harmonic distortion, rated output, 20 Hz (%)	0.0035	Superb
Harmonic distortion, rated output 20 kHz (%)	0.047	Excellent
IM distortion, rated output (%)	0.0025	Superb
IM distortion, 10-volt output (%)	0.001	Superb
Harmonic distortion, 10-volt output (1 kHz)	0.0017	Superb
PHONO PREAMPLIFIER MEASUREMENTS		
Frequency response (RIAA \pm ___ dB)	0.4	Good
Maximum input before overload (mV)	150	Very good
Hum/noise referred to full output (dB) (at rated input sensitivity)	72	Excellent
HIGH LEVEL INPUT MEASUREMENTS		
Frequency response (Hz-kHz, \pm ___ dB)	4-37, 1.0	Excellent
Hum/noise referred to full output (dB)	95	Excellent
Residual hum/noise (minimum volume) (dB)	95	Very good
TONAL COMPENSATION MEASUREMENTS		
Action of bass and treble controls	See Fig. 6	Good
Action of low frequency filter(s)	See Fig. 7	Very Good
Action of high frequency filter(s)	See Fig. 7	Very good
COMPONENT MATCHING MEASUREMENTS		
Input sensitivity, phono 1/phono 2 (mV)	2.5 / 2.5	See Text (Variable)
Input sensitivity, auxiliary input(s) (mV)	230	
Input sensitivity, tape input(s) (mV)	230	
Output level, tape output(s) (mV)	230	
EVALUATION OF CONTROLS, CONSTRUCTION AND DESIGN		
Adequacy of program source and monitor switching		Very good
Adequacy of input facilities		Excellent
Arrangement of controls (panel layout)		Very good
Action of controls and switches		Good
Design and construction		Excellent
Ease of servicing		Good
OVERALL PREAMPLIFIER PERFORMANCE RATING		Excellent

TABLE II
RADIO-ELECTRONICS PRODUCT TEST REPORT

Manufacturer: Crown International

Model: IC-150A

OVERALL PRODUCT ANALYSIS

Retail price	\$399.00
Price category	Medium
Price/performance ratio	Very Good
Styling and appearance	Good
Sound quality	Superb
Mechanical performance	Very good

Comments: In our opinion, this excellent preamplifier-control unit from Crown should probably have been assigned a completely new model number, instead of the "A" which has been added on to the old IC-150 that has been around for several years. The IC-150A is completely redesigned and, in many ways, runs rings around the older unit, which is no small accomplishment since the original IC-150 was a very fine preamp for its time. Hum-and-noise of the IC-150A is a good 5-dB lower than on the earlier unit, and distortion has been reduced by another order of magnitude, so that even our latest lab test equipment limits factual readings. We particularly liked the new step-calibrated master volume control with its 2-dB steps all the way down to -58 dB. The new loudness compensation circuitry is also an improvement, though we would have liked to see a few input level controls on the back panel so that it could be used more effectively. Welcome, too, are the high-current convenience outlets. Many preamps supply enough outlets for other equipment, but they usually cannot handle the power requirements of a basic amplifier that is likely to be used with a preamplifier of this high quality.

While it is difficult to discuss the "sound" of a preamplifier when it is being used with a basic power-amplifier (Who is to determine which of these components is ultimately responsible for what we end up hearing?), in our tests, using a Lux M-4000 to power a pair of Dahlquist DC-10 speakers, sound was exceptionally transparent, devoid of coloration and totally free of audible hum-and-noise. We are familiar with Crown's excellent amplifier, model DC-300A that is similar to their earlier DC-300 but with minor modifications incorporated to increase stability under unusual load conditions. The IC-150A, while representing a more major redesign effort, should make a perfect companion to that amplifier or to any other high-quality top-grade basic amplifier.

AKG Model P8E Cartridge

LEN FELDMAN
CONTRIBUTING HI-FI EDITOR

AKG, BASED IN VIENNA, IS PERHAPS BEST KNOWN for its expertise in microphone technology. Its products are distributed in this country through North American Philips Corporation. Recently, the company announced availability of a new line of phonograph cartridges, five in all, ranging in price from around \$40 to \$135. We tested the next-to-the-top model P8E, packaged as shown in Fig. 1 and carrying a suggested list price of \$100.



The new line features what AKG calls a Transversal Suspension System in which a single "knife-edge" suspension element in the form of a rubber diaphragm provides both the spring (suspension and restoring force) and frictional (damping) functions. Tracking force of the cartridge is transferred to the stylus tip through torque forces created at the suspension element. The design of the pivot point concentrates all forces at essentially one point so that no restrictive tie or support wires are required.


A cross-sectional view of the cartridge construction (basic configuration of all models is essentially the same, with primary differences arising from the differences in stylus assemblies) is shown in Fig. 2. Numbered items are identified as follows: (1) stylus assembly that is user replaceable. (2) transverse suspension system. (3) "nude" diamond tip. (4) aluminum stylus cantilever. (5) thin-wall tubular moving iron. (6) four-pole-pieces. (7) four pickup-coils. (8) crystal oriented permanent magnet. (9) soft-iron housing. (10) soft-iron back plate. (11)

suspension plate. (12) hinged stylus-guard. (13) connecting terminals. (14) mounting bracket. (15) cartridge body.


The replaceable stylus assembly, identified by the model number X8E when purchased separately at a suggested price of \$55.00, has two tiny protrusions in its housing that insure accurate mating with the cartridge body. Basically, the cartridge principle is the "induced magnet" type in which the permanent magnet is not part of the moving stylus assembly and therefore does not contribute to the effective mass of the stylus. Connection terminals are color coded and lettered for

Laboratory measurements

We tested the AKG P8E cartridge by mounting it in the pickup arm of a new Empire model 698 turntable. We were able to align the stylus tip for proper overhang with no difficulty or dimensional interference. Downward tracking force and anti-skating were adjusted for a 1 gram setting—the optimum force recommended by AKG for this particular model. A frequency response check was made for both channels which turned out to be identical within 0.5 dB over the frequency range from 20 Hz to 20 kHz (the limits of our CBS test record. Series

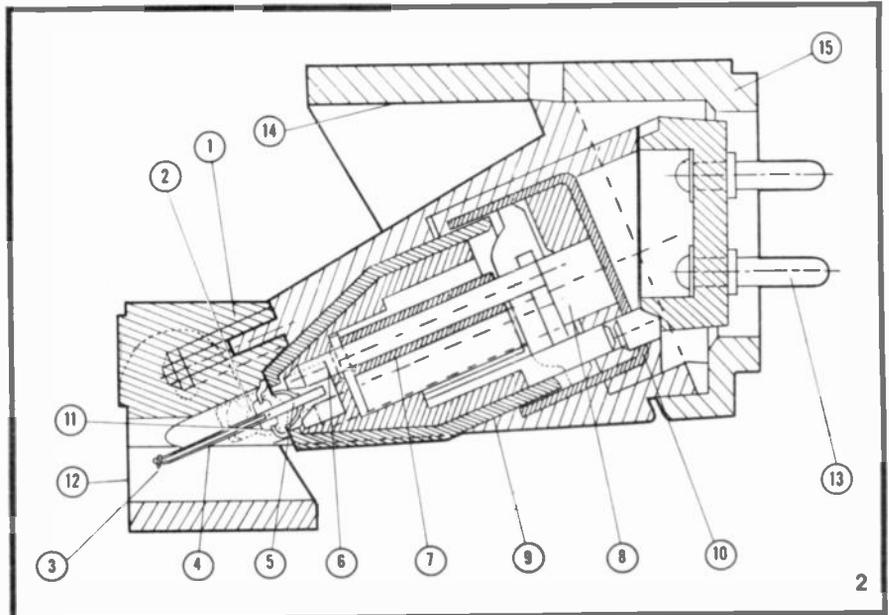

channel and phase identification in accordance with internationally adopted standards. Standard 1/2-inch mounting centers and a variety of mounting screws are provided, together with a spacing wedge that may be required for mounting the cartridge in some pickup-arm shells. Open, semi-circular shapes in the body of the cartridge make installation extremely simple, since mounting screws can be turned part-ways into the shell before the cartridge is tucked under them and tightened in place after correct orientation and positioning of the entire cartridge body. Installation of the cartridge should be done with the stylus assembly dismounted to prevent accidental damage to the stylus itself. Care should be exercised when mounting the stylus.

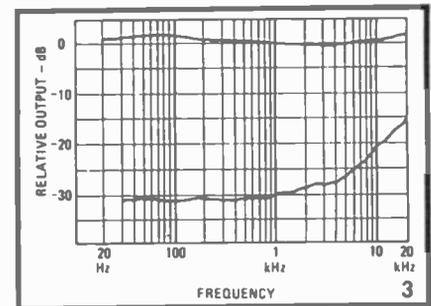

STR-130). Nominal output measured at 1 kHz was 3.0 millivolts for a stylus velocity of 3.54 cm-per-second. This corresponds quite closely to the 4.0 mV claimed by AKG for a velocity of 5.0 cm-per-second.

We measured trackability using a Shure TTR-103 test record after first increasing downward tracking force to the maximum recommended 1.25 grams. For mid frequencies, the stylus was able to track velocities of 31.5 cm-per-second before audible breakup was perceived. At high frequencies, a velocity of 30 cm-per-second was successfully tracked. These figures are quite good compared with those obtained with other competitively

MANUFACTURER'S PUBLISHED SPECIFICATIONS:

Frequency Response: 10 Hz to 23,000 Hz. **Output Voltage:** 4.0 mV at 5 cm-per-s. **Effective Stylus Mass:** 0.45 milligrams. **Tracking Force Range:** 0.75 to 1.25 grams. **Stylus Tip Radius:** 0.0002 × 0.0007-inch elliptical. **Compliance:** 35 × 10⁻⁶ cm-per-dyne. **Channel Separation:** 30 dB at 1 kHz; 20 dB at 10 kHz. **Channel Balance:** within 2 dB. **DC Resistance:** 860 ohms. **Inductance:** 280 mH. **Optimum Load Resistance:** 47,000 ohms. **Optimum Load Capacitance:** 470 pF. **Weight:** 5.86 grams.

priced cartridges we have checked. Table I lists our measurement results.

Frequency response obtained with the 1-gram tracking force setting, as well as channel separation, are shown in Fig. 3. Channel separation at 1 kHz was an impressive 30 dB, exactly as claimed. At 10 kHz, separation decreased to 22 dB, somewhat better than claimed. Results were virtually identical for both channels so only the right channel is shown for frequency response and the left channel was measured for separation. It should be noted that to obtain this extremely smooth response it was necessary to add capacitance to the cartridge loading circuitry so that the total (including internal pick-up wires) added up to the recommended 470 pF. During an earlier trial test, we noted a rising characteristic at the high-frequency end of the spectrum, amounting to around +3 dB. Since this did not correspond with the manufacturer's stated results (an individual response curve and separation curve is supplied with each model of the P8E cartridge), we checked the cables we had been using only to discover that our previous testing with this turntable had involved a discrete 4-channel pickup that required a very low (100 pF) capacitance cable. Our Empire turntable had been fitted with low capacitance cable for the purpose of those earlier tests and once we reconnected the standard cable (that measured 350 pF for its 4-foot length) we were able to obtain the curves shown, which corresponded almost precisely with the manufacturer's included graphs.

Use and listening tests

As with all transducers (speakers, headphones and phono pickups), measurements alone do not tell a complete story. We used the AKG P8E cartridge for several days for both casual and serious musical listening and came to appreciate its accurate tracking capability as well as its ability to pick up and reproduce difficult transients contained in some especially demanding musical test records. Our summary comments will be found together with our overall product analysis in Table II. From tests of this relatively high priced cartridge, we can only conclude that AKG has managed to impart the same high level of technological achievement in the P8E (we cannot, of course, speak for lower priced models in the new line) as they have done in their highly regarded line of professional microphones—and that level is considerable.

R-E

New Sony anti-dubbing device to foil video tape pirates

The Sony Corp. is now marketing in Japan a dub-proof tape recording system, CSX-100, designed for the Betamax cassette video-tape recording system.

The new system is used at copy-producing centers that mass-produce Betamax video-tape cassettes. It produces special electrical signals to make the tape uncopyable by any other Betamax VTR. When an illegal operator tries to reproduce a tape the result is a tape with images so scrambled as to be unsuitable for commercial sale.

Sony spokesmen stated that the new device might solve the pirating problem for computer software producers as well as for the entertainment tape producer.

The system was being marketed in


TABLE I		
RADIO-ELECTRONICS PRODUCT TEST REPORT		
Manufacturer: AKG (Phillips)		Model: P8E
PHONOGRAPH CARTRIDGE MEASUREMENTS		
	R-E Measurements	R-E Evaluation
FREQUENCY RESPONSE (Hz-kHz, ±__dB)	20-20, 2 See Fig. 3	Excellent
STEREO SEPARATION		
Separation, 1 kHz (dB)	28	Very good
Separation, 10 kHz (dB)	22	Excellent
Separation, 30 kHz (dB)	N/A	
CHANNEL BALANCE, 1 kHz (dB)	0.5	Excellent
TRACKABILITY MEASUREMENTS		
Stylus velocity at 1 kHz (cm/s)	31.5	Very good
Stylus velocity at 10 kHz (cm/s)	30.0	Very good
COMPONENT MATCHING CHARACTERISTICS		
Output level, 1 kHz, 3.54 cm/s (mV)	3.0	
Optimum load impedance (ohms)	47,000	
Tracking force range (— to — grams)	0.75 to 1.25	
Cartridge weight (grams)	5.86 grams	
OVERALL PHONO CARTRIDGE RATING		Excellent

TABLE II	
RADIO-ELECTRONICS PRODUCT TEST REPORT	
Manufacturer: AKG (Phillips)	Model: P8E
OVERALL PRODUCT ANALYSIS	
Retail price	\$100.00
Price category	High
Price/performance ratio	Very good
Styling and appearance	Excellent
Sound quality	Excellent
Mechanical performance	Very good
<p>Comments: Aside from the measurement of frequency response, trackability and required tracking force for best tracking results, the evaluation of any phono cartridge becomes a highly subjective matter. Most of the cartridges of the pre-quadruphonic era exhibited a high-end resonance that gave them a characteristic "brightness" that many listeners came to regard as "natural" and desirable. It was only when the demands of the CD-4 disc forced manufacturers to "push" pickup resonance to beyond audibility that listeners began to realize that they had been listening to high-frequency response that was anything but "flat". Properly loaded, the AKG model P8E cartridge has no peak in response to beyond 20 kHz and this gives it a smooth, natural sounding quality that may take some getting used to. In our opinion, it is a highly desirable trait and one which will come to be appreciated the more one listens to this excellent pickup. Orientation of the cartridge seemed to be less critical than with most, and stereo imaging and positioning of instruments is extremely stable and well defined. With tracking forces of only 1 gram, the cartridge was able to reproduce music from our most demanding test discs with no evidence of mis-tracking and very good transient reproduction. The use of this model should be limited to installation in pickup arms that have extremely low pivotal friction such as those found in better single-play manual or semi-automatic turntable systems and a very few multiple-play high quality systems.</p>	

Japan early last summer for about \$3,300. Bernie Mitchell now president of Institute of High Fidelity

The Institute of High Fidelity elected Bernie Mitchell, head of U.S. Pioneer Electronics Corp., president of the Institute at its 1976 general meeting in New York. He succeeds George De Rado, president of TEAC Corp. of America, who was elected vice president at the same meeting. Richard Ekstract, of *Audio Times*, was elected secretary and Walter Stanton, of Stanton Magnetics, treasurer.

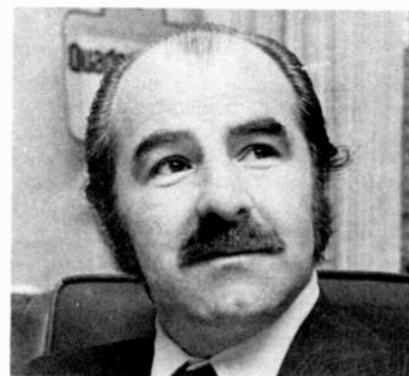
The Board of Directors includes Victor Amador of Audio Dynamics; Arthur Gasman, British Industries; Ed Hopper, Ziff-Davis; Jerry Kalov, Jensen Sound Labs, and Jay Schaub, United Audio, together with the four officers.



BERNIE MITCHELL

Mrs. Gertrude Nelson Murphy continues as Executive Director.

R-E

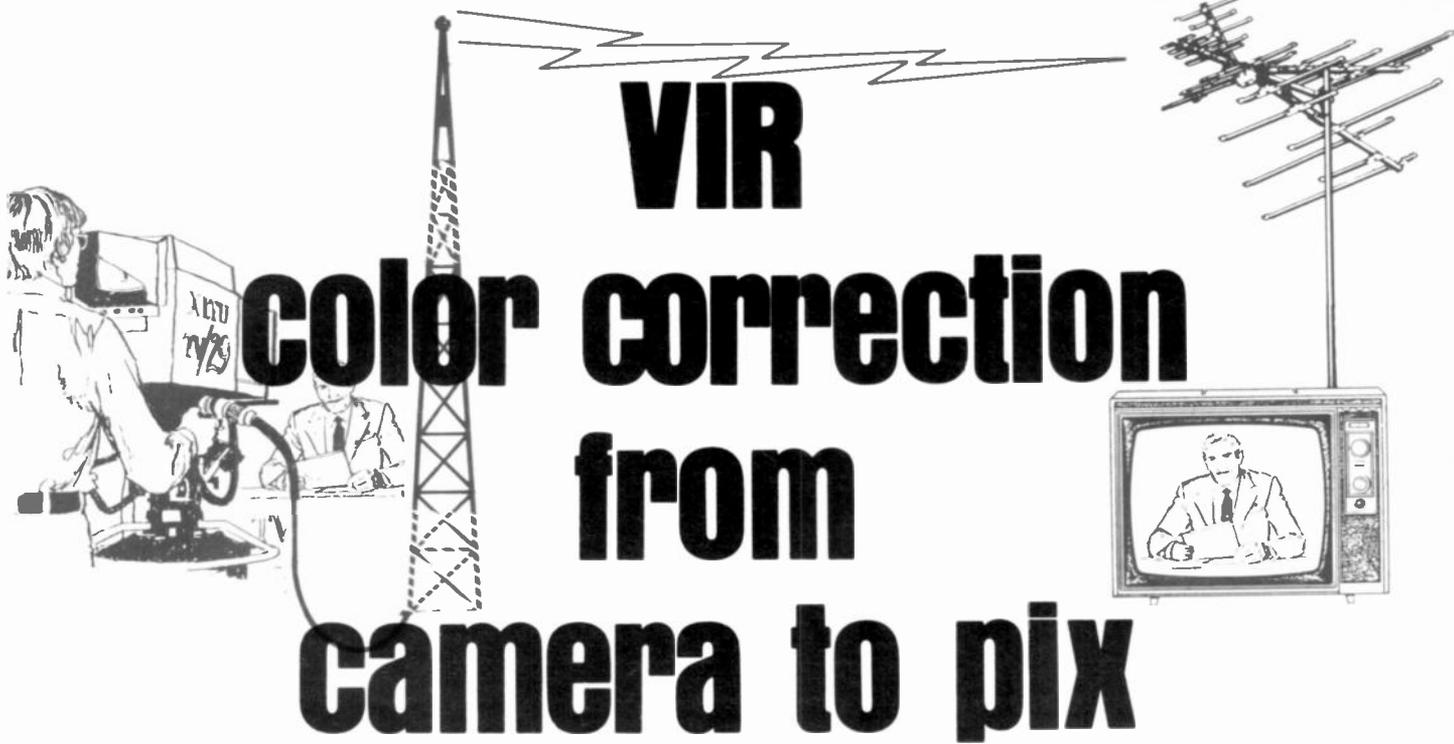

*A new system that automatically adjusts
the color from the camera all the way to the
picture on the TV screen in your home*

TURNING ON YOUR FIRST COLOR SET brought the exhilaration of a jump in TV viewing enjoyment. Unfortunately, after the initial novelty wore off, the system faults rose to the surface somewhat diluting your enthusiasm. High on the list of complaints were the annoying inconsistencies in tint and color level.

Changes in hue, color saturation and brightness levels were not only noticeable from channel to channel but from one program to the next, and especially between entertainment and commercial segments. Hue and saturation levels simply did not stay within reasonable limits. Constant adjustment was necessary, or the viewer gave up and watched a generally poor facsimile of the original studio image.

Much has been done to vastly improve the consistency of color television pictures. The VIR (*Vertical Interval Reference*) concept is capable of helping to produce pictures of excellent consistency by *tying together the total state-of-the-art transmission technology*. It is responsible for most of the improvements you have noticed over the last year or two.

There are many points between the studio where the program originates and your home receiver where color problems crop up. The underlying problem is the place where the color reference burst is inserted. The back porch of the horizontal sync pulse is a very vulnerable position where small amounts of

ROGER KENFIELD

video signal compression affects the burst amplitude and phase. Deviations from the original burst characteristics cause corresponding errors in the reproduced picture since the burst ultimately is used by the receiver demodulators to reproduce the picture color information. These signal imperfections show up at virtually any point in the signal processing chain. Video tape recorders, stabilizing amplifiers and the transmitter itself are typical trouble spots.

VIT signal

In response to these problems, the Broadcast Television System Committee of the Electronic Industries Association did something about the sad situation in 1969. There already existed the VIT (*Vertical Interval Test*) signals that included such things as sine-squared pulses and multiburst signals. These were designed to give diagnostic information of the equipment in the broadcast link. VIT signals may be inserted and measured at any point in the transmit signal chain and in general, do not follow the signal from studio to transmitter. Finding and improving individual equipment characteristics may help, but does not lead to an electrically transparent transmission path. (A transmission system that does not alter the original information.)

VIR signal

It became apparent that a new type of signal was needed and it was decided to experiment with VIR (*Vertical Interval Reference*). The vertical blanking interval is a nice place to put new signals since this is a relatively long period of 21 horizontal lines that is blanked from the viewer's eye. It is the popular place where most facsimile schemes have been known to hide their signals.

As a reference signal, VIR is created and "certified" as close to the camera as possible. Once the technician adjusting the equipment decides that the picture on his monitor is correct, the reference is encoded in such a way that allows readjustment to the video signal further down the line without artistic judgments. The logical point for this readjustment is at the furthest point just before electromagnetic radiation, namely at the transmitter.

In contrast to VIT, VIR is not meant to be a measure of system performance; it is designed so that deviations in signals can be easily corrected for.

The VIR system has been extensively field tested by the television networks and manufacturers to detect any problems unforeseen at its conception. Originally on line 20, the signal has now been assigned exclusive rights to line 19 on both fields of the interlaced picture by the FCC. The relative positions of the VIT and VIR signals in the vertical blanking-interval are shown in Fig. 1.

While line 19 has been reserved for this purpose, the transmission of VIR is not mandatory! So VIR is really still experimental and its full benefits are yet to be realized.

Figure 2 shows the relative amplitudes of the VIR signal segments. The waveform is shown as it appears on a

the bottom swing of the subcarrier reference. An uncalibrated waveform check will quickly show a signal disparity. The 7.5 IRE luminance reference has been chosen above the blanking level so that clipping at the blanking level will not affect the reference. EIA's *Television System Bulletin No. 1* gives suggestions

signal using the VIR as the reference, and the fourth burst phase setup was made only on the color burst.

The Tektronix *model 1441* VIR Signal Deleter/Inserter will remove the signal appearing on the chosen vertical blanking interval line and replace it with an internally generated VIR signal. Another mode of operation inserts the VIR signal only if none is present on the input. Special effects such as fades require manual control. The original VIR may have to be removed during the effect.

All this leads up to the Tektronix *model 1440* Automatic Video Corrector that makes all the necessary video corrections based on the VIR signal. Six parameters are automatically corrected: master gain, setup, chroma gain, burst phase, burst gain, and sync gain.

Master gain, or video amplification, is corrected so that the 50 IRE unit luminance reference is in the right signal proportion. Setup sets the black level using the 7.5 IRE reference. The 40 IRE unit chrominance signal is used by the *model 1440* to adjust chrominance amplitude. Burst gain is set on the basis of the VIR chrominance amplitude. This adjustment is important for those receivers that have color saturation levels proportional to the burst level. Burst phase is aligned with the VIR chrominance phase. The sync gain corrections are important for the sync tip clamping used throughout the transmission link as well as the TV sets that clamp on sync tips.

An additional feature of the *model 1440* is an output voltage that drives a monitoring device such as a strip recorder to give a record of the variations in the incoming signal. The instrument does other useful functions such as clamping to remove 60-Hz hum and field-time tilt on the video. Signal bounce common to microwave links is removed.

Distortion in the transmitter is a source of color problems that cannot be open-loop corrected at any point up to

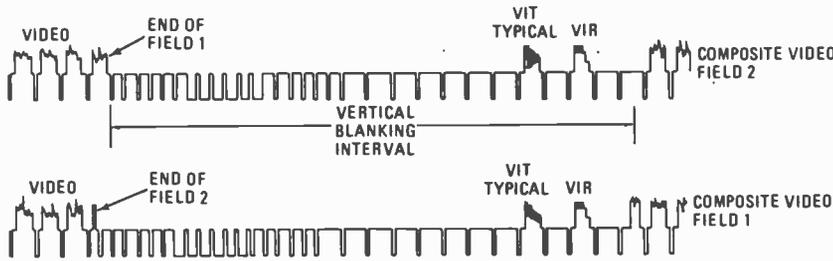


FIG. 1—RELATIVE POSITION OF VIR SIGNAL in the composite video signal.

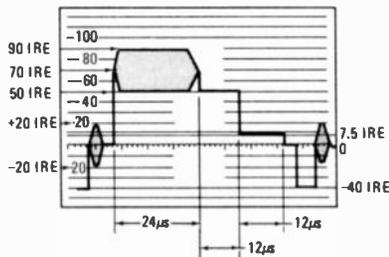


FIG. 2—VIR signal shown between two horizontal sync pulses.

waveform monitor calibrated in IRE units (140 IRE units equals 1 volt peak-to-peak). Zero is the blanking level. The signal starts out with 24 microseconds of color subcarrier reference. Similar to the subcarrier burst on the rear porch of the video sync, the subcarrier VIR reference contains both the phase and amplitude information. The phase of the signal is exactly the same as the burst. The important difference lies in its amplitude and average level. Sitting on a pedestal of 70 IRE units, the signal swings with a peak-to-peak amplitude of 40 IRE units. Sometimes you will see 286 millivolts associated with the 3.58 MHz reference. When the 140-IRE unit video signal is adjusted for its standard 1 volt P-P level, 40 IRE units corresponds to 0.2857 volt. The chroma reference extends to neither the white or black signal extremes. Signal compression common to the sync pulses will not affect this reference. The 70 IRE unit pedestal and the 40 IRE unit amplitude is about the level of flesh tones, so if the chroma reference frequency is shifted in phase differently from the other video frequencies, at least the flesh tones can be corrected close to their right values.

The first of two luminance reference levels follows directly after the subcarrier reference—12 microseconds of a constant 50 IRE unit level. Next is the second luminance reference that is also 12 μ s in duration but at 7.5 IRE units.

The first 50 IRE unit luminance reference has been selected to line up with

for monitoring the VIR signal with a waveform monitor and vectorscope.

Using VIR

The most obvious way of using the VIR signal is an open-loop method in which an operator sits in front of a waveform monitor and vectorscope, observes discrepancies in the waveform and readjusts the signal to correct the VIR. Tektronix has a number of instruments that are ideal for this purpose. One type of waveform monitor can be adjusted to give a two-field display and the sweep magnifier used to examine the VIR waveform in detail. Some other models such as the *model 529* Waveform Monitor include selectors that pick out the individual lines of a TV picture.

Manual adjustment of the video signal at the TV studio proceeds by first setting the luminance gain so that the 50 and 7.5 IRE unit reference levels are correct. Then the blanking level and sync amplitude are set. Chrominance gain is adjusted next so that the reference signal is 40 IRE units in amplitude. Finally the color burst is corrected so that its phase is the same as the VIR reference. Note that the first three adjustments are made on the total video

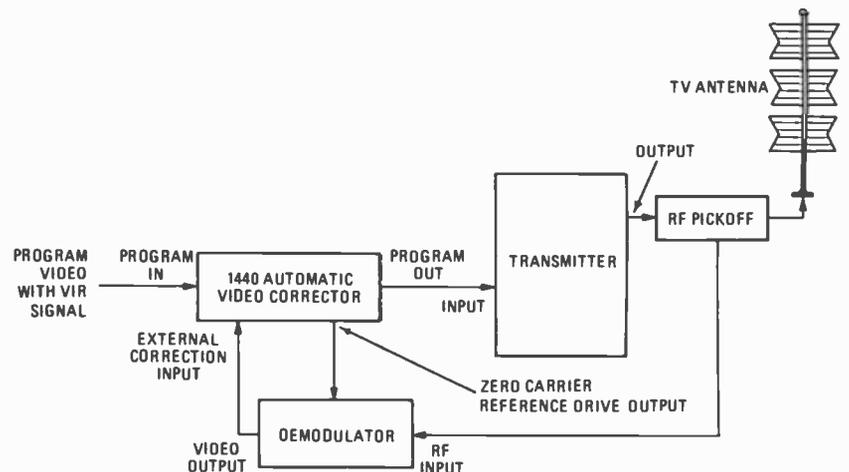


FIG. 3—COLOR SHIFTS due to transmitter distortion are corrected by negative feedback.

the video input to the modulator. Figure 3 shows an innovative solution to this dilemma. A closed loop is formed around the transmitter by detecting the RF output after modulation! Here the *model 1440* is used as a precorrector. The signal at the input to the transmitter is predistorted so that the RF output is distortion-free. The effect is analogous to a feedback amplifier. The sum of the input and feedback signals in the input amplifier stage produces error signal. The negative feedback signal distorts the input in such a way that the output distortion is reduced. Vestigial sideband demodulation must be done with something other than an inaccurate diode detector. The demodulator must be a precision device since its faithful detection is vital to producing the corrected output.

VIR and the consumer

Although the VIR system was originally envisioned to be used by the broadcasters, G-E has gone a step further and actually built a VIR recog-

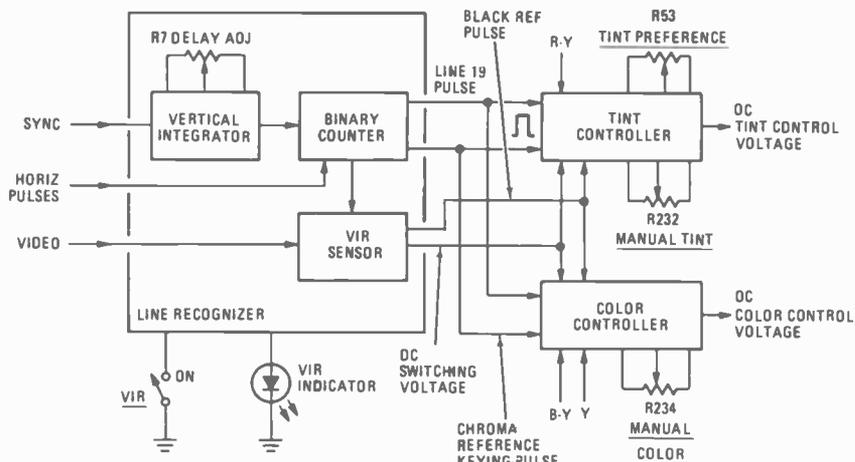



FIG. 4—G-E's BROADCAST CONTROLLED COLOR SYSTEM.

A separate VIR module performs the functions of the block diagram in Fig. 4. The module has 5 IC's and 30 transistors and can be completely removed for servicing. First the module detects the 19th horizontal-line of each video field and determines whether a VIR signal is present. DC voltages are then

generated.

Some algebraic manipulation shows that when the chrominance reference level and black reference level have the same amplitude at the output of the R-Y detector, the chroma-burst phase is the same as the VIR reference.

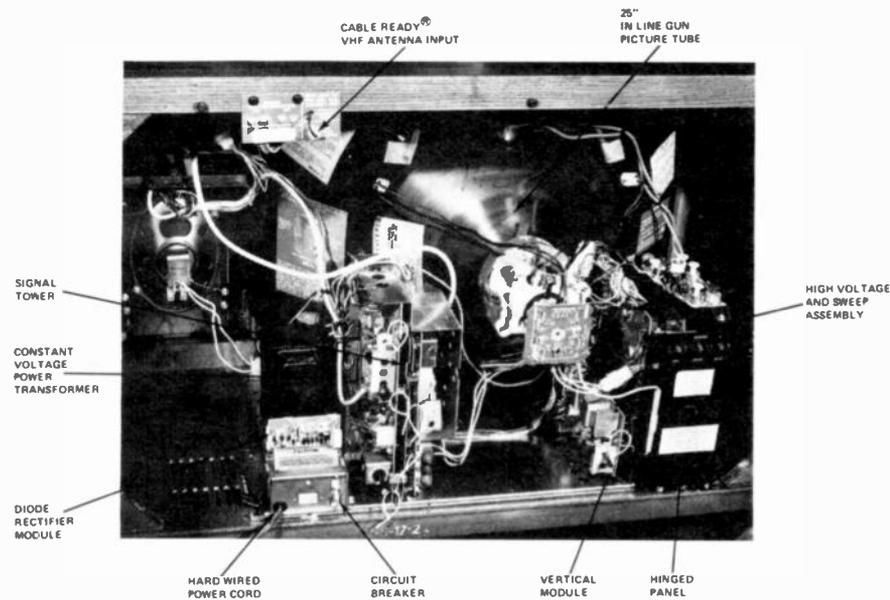Based on this principle, the *tint controller* circuit compares the chroma detector output and the black reference and generates a DC error voltage. As in any closed-loop control system, the voltage is fed back to control one of the signals being compared, in this case the chroma phase. Control R53 gives the set owner a small range of tint control that



REAR VIEW of G-E's new television receiver containing the VIR module.


nition system right into their 1977 TV receiver line. The G-E VIR Broadcast Controlled Color System used in their YM 25-inch and some of their YC-2 19-inch models make the final corrections right in your home. Any problems such as differential phase caused by a non-ideal antenna system are corrected for with this system.

The viewer knows this set is different than the others because of the presence of a VIR switch and an LED indicator. When the switch is flipped to the ON position and a VIR signal is being received, the indicator lights. The automatic circuitry takes over the color functions and the COLOR and TINT controls on the front-panel of the television receiver become inoperative.

developed for color amplitude and phase correction.

Because of the half-line variation in the phase of the two vertical fields, an intermediate point between the 4th and 5th line is located as a timing reference. The trigger point is sensed on an integrated vertical-sync waveform. Factory adjusted potentiometer R7 (DELAY ADJ) sets the exact instant of the timing pulse. Fifteen more horizontal pulses must be counted to get to line 19. A 7493 TTL 4-stage binary counter counts from 0000 to a full count of 1111 (15 counts) that is detected by a decoder.

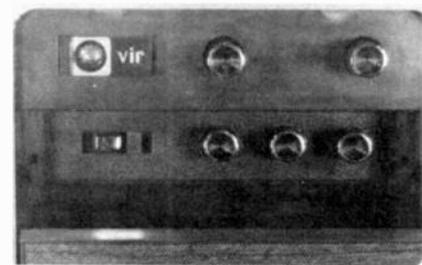The VIR sensor circuitry then examines line 19 to see if the signal is there. The *tint controller* and *color controller* circuits is enabled by the line recognizer



VIR INDICATOR on front-panel of G-E's new television receiver.

he can use for his own preference.

Operation of the *color controller* circuit is very similar. The theory says that when the chrominance reference level and black level reference are equal in amplitude to the blue drive, the chroma level is correct. So a similar closed loop is constructed using a comparator to feed the DC chroma gain control circuits. Blue drive is simulated from the B-Y demodulator output and a signal from the luminance, or Y, video amplifier.

Both the *color controller* and *tint controller* circuits are switched with diodes in response to the output of the VIR sensor. The DC control inputs to the chroma amplitude and tint circuits are switched between the tint control and tint controller, and the color control and color controller.

R-E

R-E's Service Clinic

More bits and pieces

Series strung heaters

JACK DARR
SERVICE EDITOR

THE CLINIC COLUMN ABOUT "BITS AND pieces" (*Radio-Electronics*, Feb. 1976) proved to be quite popular. Some readers asked for more. So, have some more! Let's look at some peculiarities that you can run into in sets using series-heater circuits. There are quite a lot of these around, including a lot of the hybrid color TV's. If one tube goes dead, they all go out. Or, is this always true? Let's see.

For one, there's the set with several tubes in the string, say 8 or 9. Only 5 of these are dead, the remaining 4 are burning far too brightly. The basic series heater circuit uses tubes with a total heater voltage adding up to the applied line voltage. When a short to ground develops somewhere in the string, the full line voltage is applied across only a few tubes. The heaters of these tubes are running at a higher than normal temperature.

We turn the set off and start hunting for the short with an ohmmeter. We don't find one. Now what? A little reasoning will tell you what's going on. The heater string should go to common only at the "far end". How can it get to common in the middle? Through an element in each tube that *does* go to common—the cathode. One of the tubes on either side of the point where they stop lighting has a heater-to-cathode short. Now, which one? See Fig. 1.

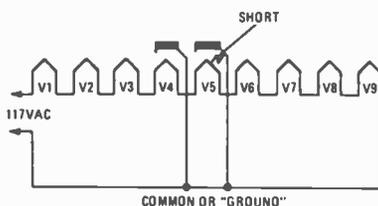


FIG. 1

Let's say that V1 through V4 are lit. We can pin this down to one of two tubes—V4 or V5. One of these has a *hot-short* between the heater and cathode. It doesn't show up until the heater gets warm and expands. The *location* of this short, on the heater, causes the different symptoms. If the output side of the heater is shorted, V4 would be the culprit. If the input side of V5's heater is the villain, that's it. Quick-check: Turn the set on and pull V5. If the others go out, this is the bad one. If they stay lit, then V4 is it. Naturally this kind of

trouble can be intermittent to add to the joy of the occasion.

If this isn't really a dead short, heater-cathode *leakage* can cause some dandy problems, too. This shows up as bending, ripple or a hum-bar in the picture. When you see this, you usually check the filter capacitors. They cause most of this kind of trouble and should be checked first. Also, they're easy to check: just bridge a good one across each one. Alternate test, scope the DC power supply lines and look for excessive ripple or signals. You can also scope the signal path looking for the point where the ripple first shows up. If the signal is clean before this point, all tubes between here and the tuner can be eliminated.

The characteristics of the hum-bar can help in many cases. If the set has a full-wave DC power supply, the hum-bars will be 120 Hz (two bars visible at once.) Heater-cathode leakage produces only one hum-bar or a 60-Hz ripple. If the set has a half-wave rectifier, this will also produce only one hum-bar, of course.

There is one key point to remember. The stage you're looking for *must* have a *cathode resistor*. If the cathode goes directly to common, there will be no resistance for the leakage current to develop a hum-voltage across! Since the cathode circuit is a part of the *plate* circuit, any hum voltage appearing here will modulate the signal at the plate. You'll have hum in the signal from this point all the way to the picture tube. A scope check on the cathodes of all suspected tubes will catch it. On a properly bypassed cathode, there should be no signals of any kind, including hum.

The dropping rectifier.

The original series-heater circuit sometimes used a dropping resistor in series to take care of any excess voltage. Many of them still do. However, there is one peculiar thing that you'll run into now and then and this can cause some weird problems. This is the "dropping diode"—a diode in series with the heater string. This makes the heater current flow in only one direction (pulsating DC instead of a true AC.) This can give you some extremely odd voltage readings along the heater string! More on this in a moment. If this diode develops leakage, or shorts, the full AC line

REPLY COUPON

Expires 12/30/76

This column is for your service problems—TV, radio, audio or general and industrial electronics. We answer all questions individually by mail, free of charge and the more interesting ones will be printed here.

If you're really stuck, write us. We'll do our best to help you. *This coupon must accompany all questions. No reproductions or facsimile will be accepted.* Don't forget to enclose a stamped, self-addressed envelope. If return postage is not included, we cannot process your question. Write: Service Editor, Radio-Electronics, 200 Park Ave. South, N.Y. 10003.


The Right DMM Decision Means Five-Function Autoranging for only \$225*

Introducing HP's 3476 DMM

The price is a big story in itself. But performance and reliability play a large part too. Take a look:

Convenient size—just right to hold in your hand... take with you in a briefcase... or use on your bench. The convenient finger ridge across the top gives you the leverage you need for easy, one-hand operation of any of the function switches. And the rubber feet are so "sticky" they hold the 3476 fast to the bench top so you can press buttons without pushing the meter around. An optional carrying case and probe kit let you hang the instrument from a strap for "no-hands" operation. The "A" version (\$225*) operates from the AC line for lab use. And for portable applications, the "B" version (\$275*) has built-in batteries and recharging circuitry.

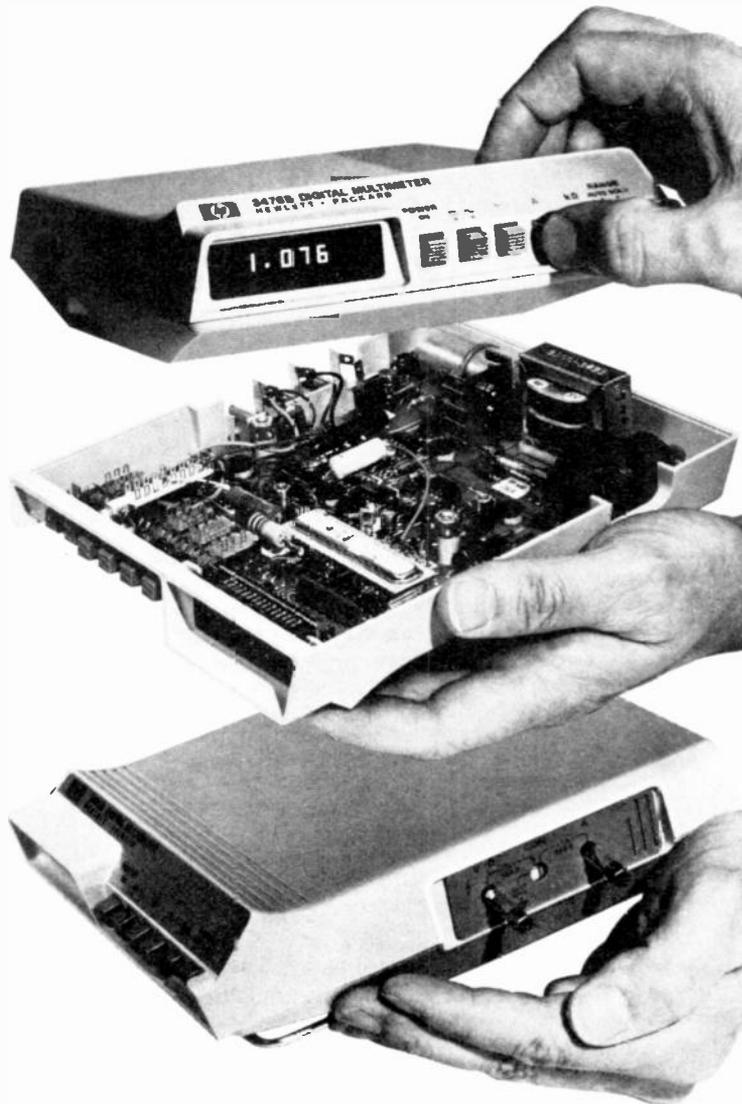Autoranging—a big plus in a low cost DMM. It lets you concentrate on the point of measurement... minimizes reading errors... and speeds readings too. All readings are made directly in volts, kilohms, or amps—on an LED display. And there's a rangehold to speed and simplify repetitive measurements.



Five functions—all the functions you want and need in a low-cost DMM. Simply push the appropriate button to read AC volts, DC volts, AC or DC current, and ohms. There's no worry about polarity or zero... they're both automatic.

Rugged—At HP, we've instituted a new DVM abuse program. We temperature cycle the 3476A/B, discharge 10kV to all exposed metal (static discharge simulation), connect 220-VAC to every terminal with all pushbutton combinations, and apply a 1000V square wave to the input voltage terminals.

We also put front-end precision resistors on one chip for good reliability, and for better temperature and tracking stability.


Easily Serviced—Should a fuse ever blow, replacement is simple because they're accessible from the outside. And since you can change fuses without breaking your calibration seal, recalibration is unnecessary.

The 3476A/B is backed by HP's service organization... another big plus for a low-cost DMM. With these prices and features, why not put your hands on the 3476A/B for your 3½ digit measurements? Your local HP field engineer can tell you how.

*Domestic U.S.A. prices only.

**HP DVM's—
the right
decision**

Actual Size

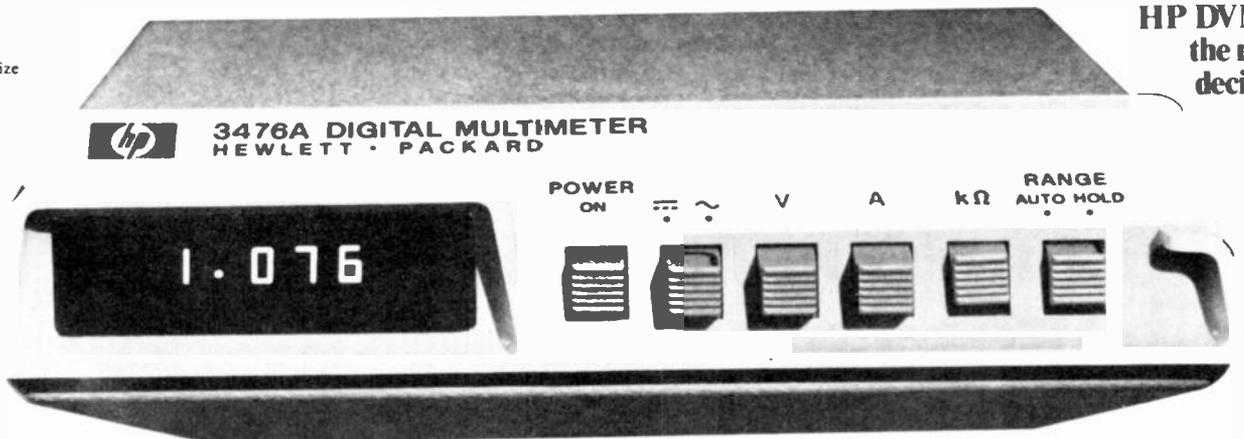

HEWLETT  PACKARD

Sales and service from 172 offices in 65 countries.
1507 Page Mill Road Palo Alto Ca 94304

CIRCLE 86 ON FREE INFORMATION CARD

096/41

NOVEMBER 1976

87

SERVICE CLINIC

continued from page 86

voltage is applied to the heater string. This overloads the tubes and usually blows at least one. Several of the makers who used this circuit now recommend modifying it by using a dropping resistor in place of the diode. However, there are still a few floating around.

One example of a complex circuit like this is the Sears 564.41102100 chassis, Sams 1317-2, shown in Fig. 2. This is an

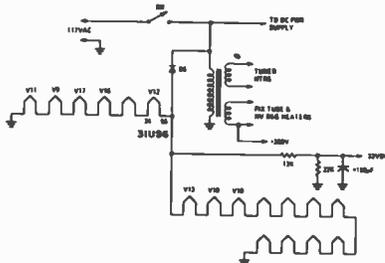


FIG. 2

all-tube set. Note the heater circuits. There are two of them in parallel, both of which are fed through diode D6. The heater voltage is given as -55 volts, so it is evidently read on a DC voltmeter! A standard AC voltmeter would probably give you a very weird reading since it's calibrated for sinewaves.

Now we come to the first curious

thing. If you add up the heater voltages of the tubes in the upper string, (two 8's, a 6, a 21 and a 31) you get 74 volts! The voltage drop across V12 is shown as 55-34 volts or 21 volts. This tube is a 31J56. The two-winding transformer shown there feeds the tubes in the tuner from the top winding and the picture tube and the high-voltage regulator from the lower winding. The DC protective voltage is applied to this one from the +300 volt DC source. All of the other tubes are in the lower string with the same 55 volts shown across it.

A novel circuit is used here. Note that they have added a series resistor, shunt resistor and a filter capacitor to the 55 volt half-wave rectified DC output. This is used to develop a -33 volt DC source that is used in the AGC and AFT circuit and one other place I never did find.

One odd problem reported by Max Zimmerman of Fairborn, OH, in this chassis was that it had a habit of eating 12AZ7 tubes. This was V19, in the R-Y/B-Y amplifier stage. After much checking, he found that the diode X6 showed a normal scope pattern at first (half-wave humps) but that as it warmed up, it began to show a full sinewave output! Neither of us have any idea as to why V19 was the tube that blew, but it did. Replacing diode X6 cleared up the problem.

So, if you run into odd symptoms in

series-heater-string sets, look for any or all of these troubles. Don't be fooled by the AC voltage readings you get on your voltmeter. It will *not* read this voltage correctly. I keep forgetting to check for this, but I suspect that a DC voltmeter won't read it correctly either! However, if the thing works, then the voltages must be nearly right no matter what the instruments say. This can really be confusing. I get a lot of mail about it. If you know it's there and what it does, it won't bother you! Good luck! R-E

reader questions

SUBSTITUTE FOR UNKNOWN TRANSISTOR

I need a replacement transistor for a transistor mike. Can't find any data on it, but the original has the numbers C828(S).—C.C., Centreville, VA.

In quite a few of the import transistors, the first two digits of a JEIA type number are left off. So, this could be a "2SC828(S)". RCA shows a 2SC828S as an SK-3122. This is an NPN audio-transistor in a TO-220 (flat-pack) case. If this should be too large, an SK-3122 is almost the same characteristics and is in a TO-92 case, much smaller.

CORRECTION

The inventor of the famous Darr Portable Full-Floating Decimal Point has struck again! In the June 1976 issue, page 64, the yoke-return capacitor in the Magnavox T979 chassis should have been a 1.0 μ F., not a 0.1 μ F. It should also be a special type, Magnavox Part No. 250653-2. This must be a special RF high-current carrying type, with polycarbonate dielectric.

Thanks to Gene McLin, Magnavox Service Training Manager, and George Crouch CET of Ace TV-Electronics, Concord, CA, for telling me about this. Gene also notes that if this capacitor fails, the horizontal-centering control and resistor R29 may also be damaged; check them. Both suggested replacing the D panel with Part No. 703505-11, which has the new rated parts in it.

NO RASTER

I have plenty of high-voltage and the picture tube bias voltages are OK, but I have no raster. This is a Zenith 20BC50. Resistor R166, 47K 3W, is burning up. I have changed tubes, etc., but no help. 6LB6 cathode current around 275-300 mA I'm missing something, but what?—B.T., Delta, IA.

I think that what you're missing is the *focus voltage*. Without focus voltage the raster will not come on. R166 is the one feeding the drive pulse to the focus rectifier. I would definitely suspect

In any hi-fi system, the one component most likely to wear out is the phono cartridge. Or more specifically, the phono stylus.

While you're relaxing to your favorite music, the stylus is riding miles of groove, withstanding accelerations that would black out an astronaut.

Which is why the Shibata stylus, used on the top models of Audio-Technica



cartridges, is so important. Its shape reduces tracking pressure at any given tracking force. Even with a setting as high as 2 grams it will outlast an elliptical stylus tracking at a *fraction* of a gram. Which means the good sound of Audio-Technica lasts longer. And so do your records.

Audio-Technica with a Shibata stylus: lower cost per record/mile and better sound in the bargain!

audio-technica 
INNOVATION / PRECISION / INTEGRITY

When you shop for better sound ask about good mileage!

AUDIO-TECHNICA U.S., INC., Dept. 116E, 33 Shiawassee Ave., Fairlawn, Ohio 44313
Available in Canada from Superior Electronics, Inc.

something in this area if it is getting hot. Most likely suspect would be a shorted focus rectifier.

HIGH-VOLTAGE PROBLEMS

I have too much cathode current on the 6KD6 in this Admiral 3K16. High voltage is quite low and the focus jumps in and out. When I turn the brightness up, the focus goes completely out and the high voltage drops to about 10 kV.—L.P., Oscola, IA.

From all of these symptoms, plus the reaction of the controls, I'd be inclined to suspect that the focus bleeder resistor is defective. Try this; disconnect the high-voltage lead to this bleeder and see if the high-voltage jumps back up and the current drops to normal. If so, try a new bleeder resistor. This one has probably broken down internally. (Remember that without any focus voltage, you will *not* see a raster! So, don't be alarmed at that.

VOLUME CONTROL PROBLEM

There is an odd problem in this Magnavox 1FM053 radio. I can't turn the volume down enough. In fact, it hardly works at all. I've replaced the control and it does the same thing.—V.S., Dalton, PA.

Simple; the bottom end of the volume control is not grounded. A control like this is just a variable signal-voltage divider. If the bottom (low end) is not grounded, the control will have no effect.

Incidentally, this does not have to be a DC ground. The bottom of the control may be open but grounded for audio signals through a capacitor. Trace the circuit.

(Feedback: Found it. Open electrolytic capacitor!)

WHY USE THE SCOPE?

In response to a question in the June, 1976 issue, you stressed the importance of using an oscilloscope. Can you tell me why?—V.F., Hickory, NC.

You use a scope in TV servicing because it is the ONLY instrument that will SHOW you the signal at a given point in a circuit. Other instruments will tell you only that there is a certain voltage (AC or DC) or resistance there. What you need to know is whether this point has a NORMAL waveform on it. This works both ways. In all DC power supply circuits, the normal "signal" is no signal at all, just a nice straight green line. Any kind of signal means trouble due to feedback.

GATE CONTROL SWITCH

Please recommend a replacement for a gate-turn-off switch used in the horizontal output stage of an Emerson 11P04. I found a couple listed but they were all small ones. This is in a TO-3 case.—E.M., Washington, DC.

I fell over this same thing quite a while back. Ordered one from the factory. They sent me a big TO-3, power transistor! I thought that a clerk had made a mistake, but then it dawned on me that a power transistor was a gate turn-off switch! Put it in and it worked beautifully.

Try SK-3115, HEP-740 or any transistor with similar characteristics.

SUBSTITUTE FOR 7687 TUBE

I need a couple of 7687 tubes for an old Sylvania stereo. I've checked with the maker and these tubes are no longer available. I can't find anything on the characteristics either. Can you give me a

practical substitute? Need help.—R.W., Schenectady, NY.

I thought at first this was going to be one of those screw-ball-base types, but it isn't.

7687 is a triode-pentode with a 6.3-volt 0.5-amp heater and transconductances of 2500/6800 on a 9AE base. Similar tubes with this base would be 6CG8, 6LX8, 6FG7, 6EA8 or 6GH8. All of these are in the ballpark as far as the transconductance is concerned. Plug-in replacements.

HOT ELECTROLYTIC CAPACITORS

There are four big can-type electrolytic capacitors in this Philco TV. I happened

LTS
3 1/2 digit
multimeter
thermometer*
in the palm of your hand.

Only \$198.
Model 12: DMM
w/o temperature

- 0.1% Accuracy for DC Volts
- Autoranging and Autopolarity
- Measures Surface and Ambient Temperature*
- Rechargeable NiCd Batteries Included
- Plug-in Tips for Temperature and Multimeter Functions*

Temperature: -55° to 153.5°C, ±1°C from 0° to 100°C*

DC Voltage: 1 mV to 750 V, input impedance 10 megohms

AC Voltage: 200 mV_{rms} to 750 V_{rms}, input impedance 10 megohms shunted by 14 pF

Resistance: 1 ohm to 19.99 megohms

Both models include ac adaptor/charger, carrying case and operator's manual.

Model 12T: Combined Thermometer/DMM. \$259.*



LOGICAL TECHNICAL SERVICES CORP.

71 West 23rd Street, New York, N.Y. 10010
(212) 741-8340 Telex #12-7698

Representative and dealer inquiries invited.

CIRCLE 23 ON FREE INFORMATION CARD



CB Power Supply

117 VAC/12VDC
2 AMP Continuous
5 AMP Surge

Use your CB Radio, 8-Track Tape or other Car Equipment at home.

Mail \$17.95 plus \$1.50 handling charges to:

CB Division
P.O. Box 486
Sturtevant, Wisconsin 53177

DEALER INQUIRIES INVITED
CIRCLE 43 ON FREE INFORMATION CARD

to discover that three of them are running very warm, almost hot. The other is cold. Could this have anything to do with some of the symptoms I have? That is, bad sync and a wide floating bar up and down the picture. Found a couple of resistors that were running very warm and discolored.—F.K., Chicago, IL.

I'd say so, yes! Any electrolytic capacitor that runs definitely warm or hot to the touch is pretty sure to have excessive leakage. However, make sure that this is definitely due to internally generated heat and not heat radiated from a very hot tube close to the capacitor. (Test by putting a piece of aluminum foil between the tube and the capacitor for a heat shield and running the set for about 20-30 minutes.)

HORIZONTAL LINE WITH WIGGLES?

I replaced a blown fuse on this Magnavox T941 portable. Turned it on and got sound, high voltage, etc. Looked at the screen and all I had was a horizontal line with little pulses on it! Something like a video signal on a scope. Everything in the vertical output section seems to be OK. What the heck?—J.A., Pensacola, FL.

Check the schematic of the vertical output circuit. You'll find a component that looks like a vertical output transformer. It isn't; it's a vertical output coil

or choke. The vertical winding of the deflection yoke is also connected to the collector of the output transistor. The return of this winding is back to the +12-volt source through a 500 μ F electrolytic capacitor. I believe you'll find this capacitor is open. This would leave you with a sawtooth signal on the collector but no vertical deflection. Check the yoke plug and socket too, just for luck!

ONE MORE MARKER


I'd like to have a 44.0-MHz marker on my Heath IG-57A sweep generator for the center of the IF passband. Can you tell me how to get it?—H.M., Bristol, TN.

If you insist! You can take one of the markers you aren't using, for example the 39.75-MHz crystal, out and install a 44.0-MHz crystal in place of it. The tuning coils used for all of the IF marker oscillators are the same, so this one should tune up to 44.0 MHz. Follow the directions in the manual for setting the amplitude of this marker.

WHY THE NARROW EYE?

I've been checking some capacitors scrounged from junk TV's with a Heath IT-28 capacitor checker. I note that on some, the eye-tube won't open all the way. On others, it hardly opens at all. Capacitance always checks close to the rated value. I checked some capacitors

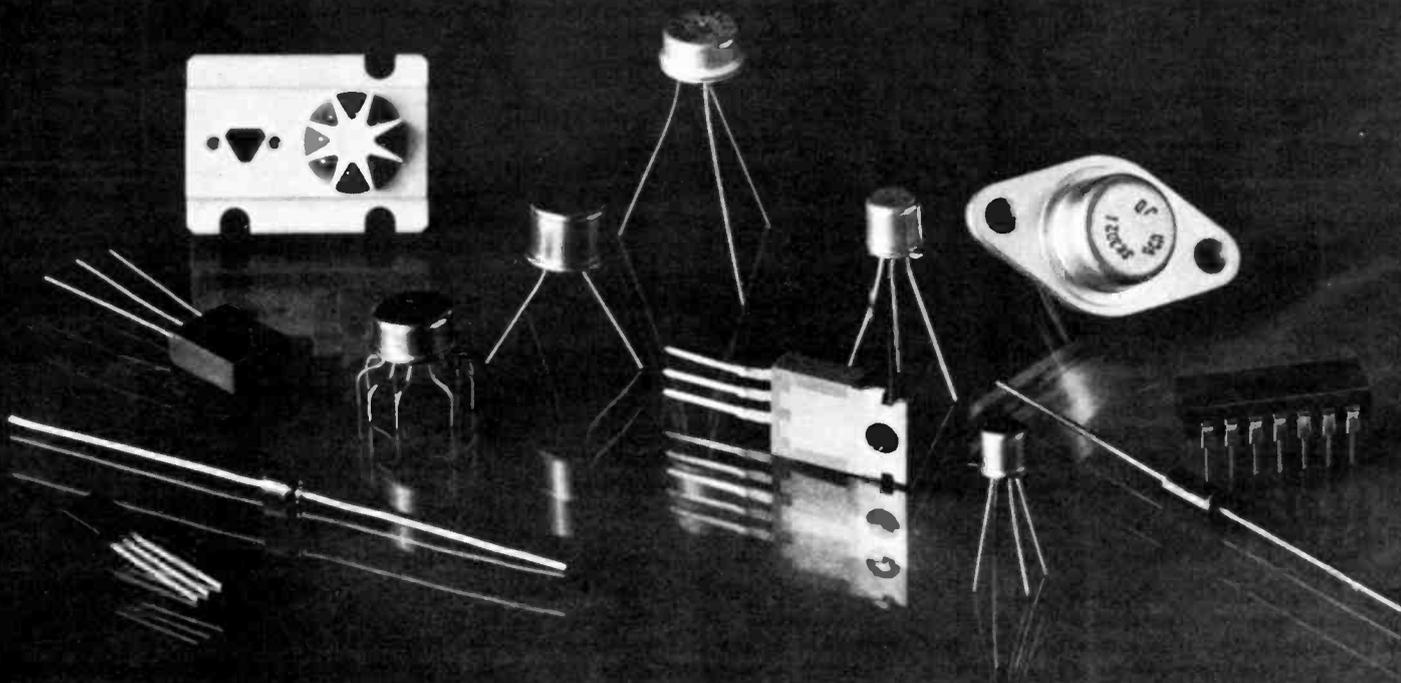Now you can stock only 300 semiconductors instead of 112,000.



from stock which had been around for some years. Same kind of thing. Can you explain this?—A.G., Hyattsville, MD.

From my experience with bridge capacitor testers, a "squint" of the eye-tube usually means that this capacitor has some insulation resistance leakage. The wider the eye opening, the better the insulation resistance. This may be several megohms, or even tens of megohms.

In some uses, such as bypassing, this may not hurt. I wouldn't use a capacitor with a narrow eye for a coupling capacitor in audio stages, though. Possible that just enough DC voltage could leak through to upset the grid bias on the next stage.

ALL DC VOLTAGES LOW

The vertical size and linearity weren't too good on this CTC-25. Had other problems, too. Finally discovered that all of the DC voltages were quite a bit low. Changed the diodes in the bridge, and the input filter capacitor. Voltages came up to normal, stayed there for half an hour and then down again! I'm on the wrong track somewhere!—R.Z., Lincoln, NE.

I wouldn't say that you've been eliminating the most likely causes! You just haven't gone far enough along that track. From an experience with the same kind of thing not long ago, I would suggest checking that thermistor in the

degaussing circuit, and the coil. If this thermistor has gone up in hot-resistance and the coil is unplugged or open, you can get just this kind of problem. Quick-check; just hook a short clip-lead across the thermistor. If the voltages come up, replace thermistor.

BIAS PROBLEM?

The 6CZ5 output tubes in this 1960 Knight amplifier glow red, and burn out. I changed the 250-ohm bias resistor in the cathodes; same problem. Finally had to use a 1000-ohm bias resistor. This works at low volume, but there is bad distortion if I turn it up. What's the problem?—P.G., Charles City, IA.

Well, you were in the right place; in the bias. It sounds a little obvious to say it, but if a tube is red hot, it's drawing too much current. If there are no shorts in the output, the problem has to be incorrect bias. A 6CZ5 tube with +250 volts on plate and screen grid should have a net bias of -14 volts on the grid, and draw about 45 mA per tube.


One other good possibility. This could cause both problems; heat and distortion. Check for leaky coupling capacitors. This will put too much positive voltage on the 6CZ5 control grids. To check quickly, pull the 6CZ5's, turn power on and read voltage on grids with your VTVM: should be zero.

continued on page 103

The quick charge iron with 16 different quick change tips.




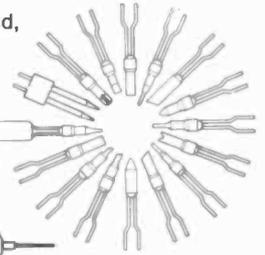ISO-TIP®
QUICK CHARGE
 Cordless Soldering Iron completely recharges in 3½-4 hours. Low voltage, battery powered, ground free isolated tip design.



16 snap-in tips to fit any job plus a PC Drill.

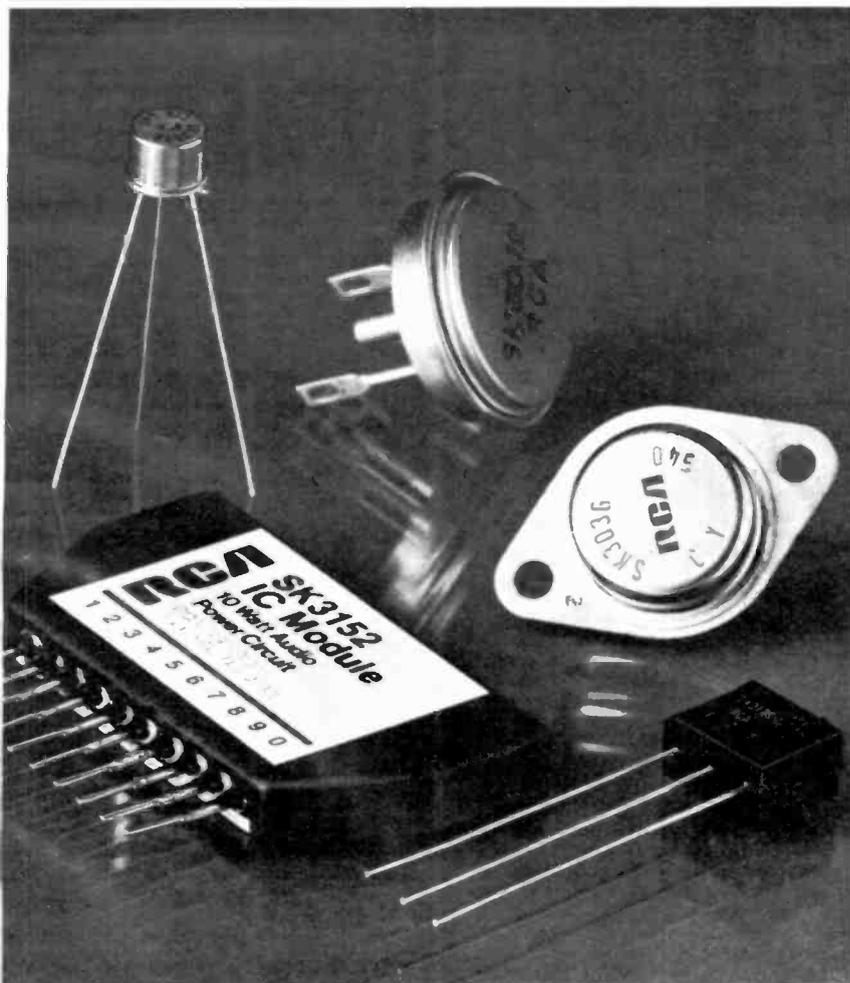WAHL CLIPPER CORPORATION
 ORIGINATORS OF PRACTICAL CORDLESS SOLDERING
 • Sterling, Illinois 61081 • (815) 625-6525
 "Manufacturing Excellence Since 1919"
CIRCLE 1 ON FREE INFORMATION CARD




With RCA's SK Series you need stock fewer different semiconductors than you'd have to with any other major brand. Because our 300 devices can replace 112,000. And they're all immediately available.

OEM Quality. You don't have to be concerned about quality with RCA SK's. They measure up to strict AQL Standards to protect you from time-wasting callbacks. Lets you make more calls. And more profits.

See your **RCA Distributor** for a copy of the new RCA SK Replacement Guide. Or send \$1.00 to RCA Distributor and Special Products Division, P.O. Box 85, Runnemede, N.J. 08078. Phone: (609) 779-5735.

RCA SK Replacement Semiconductors

Gold-ens

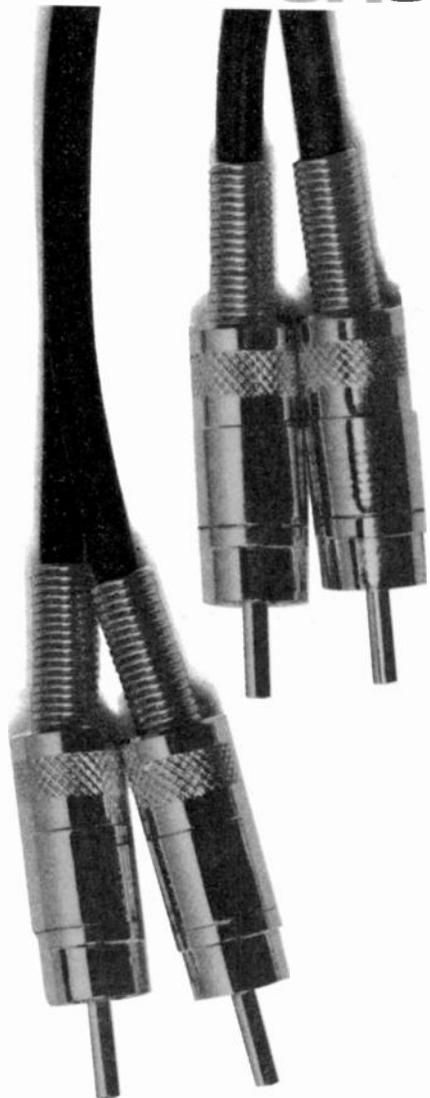

Gold plated connector cables for the perfectionist.

- Highest degree of electron transfer and longevity will never corrode or add resistance with age.
- Spring steel strain reliefs.
- Ultra-low capacitance cables.

\$8.00 per matched pair, 1 meter length.

From the people who brought you Discwasher.

At audio specialists worldwide.

discwasher inc.

Columbia, Mo. 65201

CIRCLE 81 ON FREE INFORMATION CARD

DIGITAL MULTIMETERS

continued from page 47

inputs should drift (commonly this changes with temperature), the voltage measured by the single-slope converter changes. With the dual-slope converter, drift in the comparator trip point does not cause a problem unless it happens between the time of the up ramp and the down ramp of a conversion cycle.

The reference signal for both the single and the dual-slope converters must be stable. To ensure good stability with time and temperature, the voltage (or current) reference source is commonly derived from a temperature-compensated Zener diode that may have been selected for aging characteristics. This Zener diode normally has a constant load impedance, and may be driven by a constant-current source.

The dual-slope converter also has some inherent noise rejection capabilities. The most common noise problem, apparent when making DC measurements, is generated by line-frequency signals riding on the DC voltage to be measured. Considering the single-slope converter, it is possible that noise on the input line causes the comparator to trip on the sum of the noise and the DC input signal or on the difference between them. For example, a 0.5-volt DC signal having 0.25 volt of AC peak noise could cause a measurement as high as 0.75 volt, or one as low as 0.25 volt.

The input to a dual-slope converter is applied to an integrator. The output voltage of the integrator at the end of the ramp-up cycle is the average value of the DC signal plus any noise which might have been present during the integration period. The length of the integration cycle is determined by the number of counts required to fill and overrange the counter and by the frequency of the clock.

The length of this integration is of course constant from conversion to conversion within the stability of the clock. The average value of a sinewave is zero after both the positive and negative halves of a cycle are complete. The oscillator frequency of most dual-slope converters is adjusted to make the unknown integration cycle a whole number of line frequency cycles. Typically, the integration time is chosen to be an even multiple of the period of one cycle of the line frequency (for example, 100 milliseconds which is the time required for six cycles at 60 Hz or five cycles at 50 Hz).

Integrating six cycles of the interfering signal simply improves the technique of averaging sinusoidal noise to zero, even with slight discrepancies in the integration period. This technique, of making the integration time equal to an integral number of line frequency cycles, gives the dual-slope converter a good immunity to line frequency related noise. The rejection of such signals is called "line frequency normal mode rejection".

Obviously this simple converter needs some extra supporting circuitry to create a full-fledged voltmeter. The overrange circuits are usually sophisticated enough so they are not only able to handle the two overranges (indicated in the previous explanations) but also to handle a third overrange, permitting the normal range of the voltmeter to be 0 to 1999.

This means a first overrange when the

★ **FREE!** ★



NEW CATALOG OF HARD-TO-FIND PRECISION TOOLS

Jensen's new 128-page catalog is jam-packed with more than 2800 quality items. Your single source for hard-to-find precision tools used by electronic technicians, scientists, engineers, instrument mechanics, schools, laboratories and government agencies. This wanted catalog also contains Jensen's world-famous line of more than 40 tool kits. Plus 10 pages of useful "Tool Tips" to aid in tool selection. Send for your free copy today!



JENSEN TOOLS AND ALLOYS
4117 N. 44th Street, Phoenix, Arizona 85018

A BLUSS & LAUGHLIN INDUSTRY

CIRCLE 9 ON FREE INFORMATION CARD



**save on gas!
save on tune-ups!
save on maintenance!**

Electronic Ignition is "IN"! So says Detroit.

Update your car with either a TIGER CD or a TIGER I breakerless system.

Enjoy the benefits of better gas mileage, quicker starting, elimination of tune-ups, 50,000 miles on points and plugs, and reduced maintenance expenses.

TIGER MAX CD	\$69.95
TIGER 500 CD	59.95
TIGER SST CD	42.95
SIMPLIKIT CD	31.95
TIGER I	45.95

Postpaid U.S.A. only.

Tri-Star Corporation

Dept. WW, P.O. Box 1727
Grand Junction, Colorado 81501

CIRCLE 18 ON FREE INFORMATION CARD

unknown signal is being measured, a second overrange when the reference voltage cannot reduce the integrator to zero in the same time allowed the unknown voltage, and a third overrange if the reference voltage requires twice as long to reduce the integrator to zero as did the unknown voltage to charge the integrator.

A third overrange with a simultaneous detection of zero output from the integrator would indicate an unknown voltage twice the reference voltage. Some models of voltmeter have provisions permitting even greater overrange capability. Display ranges of 2999 or 3999 are available. Such voltmeters simply make a trade-off between the voltage swing of the integrator for 0 to 1,000 inputs and the overrange voltage swing which must be permitted if the integrator is to have extensive overrange capability.

The previously described dual and single-slope converters have been monopolar—the converter only works with unknown signals of a single polarity. Most digital voltmeters either indicate the necessity for reversing the polarity of the unknown signal to display a proper reading, or they reverse polarity automatically and indicate the proper polarity of the unknown signal with a \pm indicator. Single-slope converters and some dual-slope converters simply employ an additional comparator on the input (or at the output of the integrator) which detects an improper polarity input and indicates it on a display. Automatic polarity selection with the dual-slope converter is usually made by changing the polarity of the reference voltage. Signals directing the polarity reference source of the

converter are generated by comparators at the output of the integrator.

To measure unknown signals at or close to zero volts effectively, an offset voltage is added to the converter. For example, a 1-volt full-scale converter might actually measure signals from 0.1 volts to 1.1 volts at the converter. Thus the dual-slope integrator would never have to integrate an input signal of less than 0.1 volts. Some dual-slope converters have been developed with an additional cycle in the measurement scheme. This additional cycle is completed with zero input. As the input during this cycle is known to be zero, any reading present at the completion of the cycle can be used to correct zero-offset circuits. Such an additional cycle ensures a true zero condition.

There are many other variations on the dual-slope converter. One of the first efforts was to remove the switch from the input signal entirely, as switches in the input line present a design problem. Mechanical ones, such as reed relays, have a definite short life span, and long-life semiconductor switches have serious temperature problems, in addition to causing variations when used in circuits where voltage and impedance levels are not carefully controlled.

to be continued



You can build a better organ than you can buy!

A magnificent Schober Electronic Organ

What a marvelous way to put your special talents to work! With our Schober Electronic Organ Kits and your skill, you can build yourself some very special satisfaction, and a lifetime of great music!

Schober Organs are literally far superior to comparably-priced "ready-made" units. You could actually pay twice as much and get no better organ and miss the fun of assembling it yourself. A PC board at a time, component by component, you'll assemble your own "king of instruments." And when you're done, you'll wish there was more to do. And there is! For then, Schober will help you learn to play, even if you've never played a note before!

Schober Organ Kits range from \$650 to \$2850, and you can purchase in sections to spread costs out or have two-year time payments.

Just send the coupon for the fascinating Schober color catalog (or enclose \$1 for a record that lets you hear as well as see Schober quality.)

The Schober Organ Corp., Dept. RE-156
43 West 61st Street, New York, N.Y. 10023

- Please send me Schober Organ Catalog
 Enclosed please find \$1.00 for 12-inch L.P. record of Schober Organ music

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

CIRCLE 41 ON FREE INFORMATION CARD



"FERRET" TV MINI-ANALYZER

FOR FAST STEP-BY-STEP TROUBLE SHOOTING

SUB TUNER


VHF AND UHF TUNER FOR RAPID TESTING OF ALL CHANNELS. CALIBRATED GAIN ADJUSTMENTS PROVIDE FOR SIGNAL STRENGTH COMPARISON.

DIGITAL GENERATOR

CRYSTAL CONTROLLED FOR GENERATING STABLE PATTERNS WHEN CONVERGING RED, GREEN AND BLUE GUNS. IDEAL FOR LINEARITY, PIN CUSHION, CENTERING, FOCUS AND ALL PICTURE ADJUSTMENTS.

40 MHz OUTPUTS

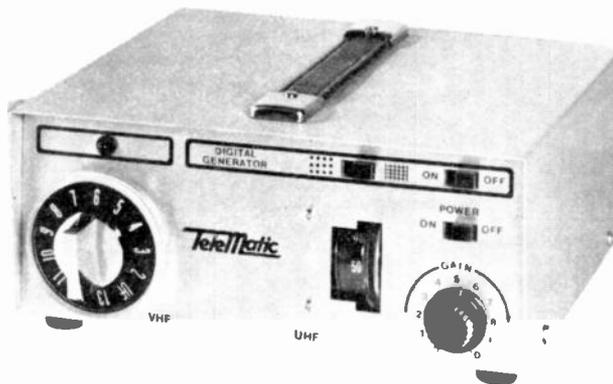
IF SIGNALS FROM DIGITAL GENERATOR AND SUB TUNER FOR STAGE-BY-STAGE ANALYZING AND TROUBLE SHOOTING.



SG 785 \$99.95


GENERATOR SECTION

CROSS-HATCH

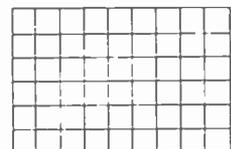

LINEARITY ADJUSTMENT
STANDARD FOR VERTICAL AND HORIZONTAL POSITIONING, PICTURE CONTRAST, IF BANDWIDTH TEST

DOT PATTERN

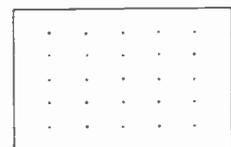

CONVERGENCE ADJUSTMENT
STATIC AND DYNAMIC CONVERGENCE, BEAM ADJUSTMENTS.

The VHF/UHF section of the Ferret allows direct substitution of the TV's tuner for fast, positive localizing of front end trouble.

The crystal controlled digital circuitry assures complete accuracy of both the vertical and horizontal frequencies. Accuracy is better than .005%. Output from the generator may be coupled thru the tuner section or directly to the IF-video stages. Resolution is limited only by the picture quality of the TV receiver. Operates from 105 to 125 volts 50-60Hz.

SOLD THRU DISTRIBUTORS ONLY

Please send me more information. N6
Name _____
Address _____
Code _____



2849 FULTON STREET; BROOKLYN, NY 11207
PHONE: (212) 827-1500

CIRCLE 75 ON FREE INFORMATION CARD

FREE EICO CATALOG

**358 Ways
To Save On
Instruments,
Citizens Band,
Burglar Alarms,
Automotive &
Hobby
Electronics!**

The more you know about electronics, the more you'll appreciate EICO. We have a wide range of products for you to choose from, each designed to provide you with the most pleasure and quality performance for your money. The fact that more than 3 million EICO products are in use attests to their quality and performance.

"Build-it-Yourself" and save up to 50% with our famous electronic kits.

For latest EICO Catalog and name of nearest EICO Distributor, check reader service card or send 50¢ for fast first class mail service.

**EICO—283 Malta Street,
Brooklyn, N.Y. 11207**

*Leadership in creative electronics
since 1945.*




CIRCLE 61 ON FREE INFORMATION CARD

new products

More information on new products is available from the manufacturers of items identified by a Reader Service number. Use the Free Information Card following page 106.

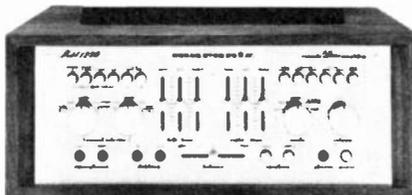INTEGRATED AMPLIFIER, model 1250, delivers 125 watts minimum continuous power per channel with both channels driven, covering a power bandwidth of 20 Hz to 120 kHz. It is rated at no more than 0.1% total harmonic distortion with an 8-ohm load.



The model 1250 features a separate record mode selector for 2 tape recorders. This enables the user to select a different source for each tape recording, even while listening to a third program source. Special circuitry enables the user to monitor the quality of those recordings. In addition, the front panel contains detented slide-graphic controls for bass, mid-range and treble. This provides the user with selectable frequency turnover points.

The model 1250 is equipped with inputs for stereo microphones, two turntables, a tuner, and two auxiliary stereo sources.—Marantz Co., Inc., 8150 Vineland Ave., Sun Valley, CA 91352.

CIRCLE 90 ON FREE INFORMATION CARD

FREQUENCY COUNTER, model FM-7, is a miniature battery-powered test instrument. The unit measures only 1.9 x 2.7 x 4 inches and will monitor frequencies from 10 Hz to 60 MHz and display that frequency to seven digits using 0.25-inch high LED's. Input sensitivity is 30 millivolts RMS from 50 Hz to 30 MHz, and 100 millivolts RMS from 10 Hz to 60 MHz with a 1-megohm input impedance. It has an input signal overload capability of up to 250 volts RMS at 500 kHz.




Resolution is 1-Hz below 10 MHz and 10-Hz from 10 MHz to 60 MHz. The internal timebase has an aging rate of less than 10 PPM from 0°C to +40°C. The unit operates on self-contained

type-AA NiCad rechargeable batteries. The batteries and charger unit are furnished with the frequency meter. The meter can be operated continuously for two hours on a fourteen-hour recharge. Options include a panel-mount flange, a tilt stand and a leather case. Price: \$195.00—Non Linear Systems, Inc., P.O. Box N, Del Mar, CA 92014.

CIRCLE 91 ON FREE INFORMATION CARD

SPEAKER SYSTEMS, model EPI 70 and EPI 120, features 1-inch air-spring tweeters with a crossover frequency of 1800 Hz.

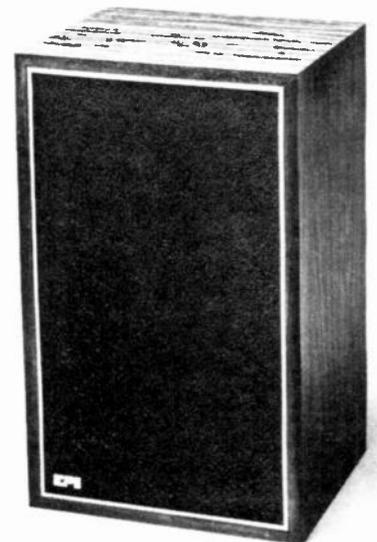The model EPI 70 is a bookshelf model using a long-traverse 6-inch woofer, plus tweeter. The frequency response is 60 to 20,000 Hz with a recommended RMS power range of 10 to 80 watts. Measures 16 x 10 1/2 x 7 1/2 inches and weighs 17 1/2 pounds.




The model EPI 120 is a floor/bookshelf model featuring a 10-inch woofer plus tweeter. Frequency response is 38 to 20,000 Hz, ± 3 dB, with a recommended RMS power range of 25 to 80 watts. Measures 25 x 15 x 12 1/2 inches and weighs 47 pounds.

Both models are finished in wood-grain vinyl with bronze trim, and have acoustically transparent matte-black foam grilles. The model EPI 70 is priced at \$139.90 per matched pair and the EPI 120 sells for \$139.95 each.—Epicure Products, Inc., 1 Charles Street, Newburyport, MA 01950.

CIRCLE 92 ON FREE INFORMATION CARD

POWER AMPLIFIER, model 620, features a radically new circuit referred to as a "Tetra-Linear Differential Amplifier". It is a pure Class-B design that virtually eliminates crossover and switching distortions found in all popular class

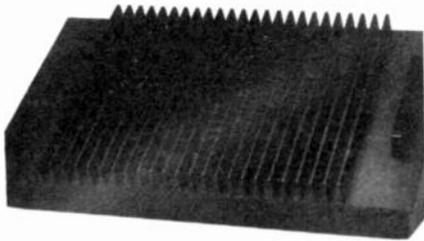A-B power amplifiers. This results in a barely measurable total harmonic and intermodulation distortion figures that are an entire order of magnitude lower than those of most high-quality preamplifiers at all power levels right up to and beyond its rated maximum output of 100-watts-per-channel.



The new circuit design also increases temperature stability and efficiency. The idling current of the model 620 is 1/25 that of other power amplifiers of comparable output ratings. The amplifier is reportedly stable into all types of loads, including reactive loads. Protection of the output transistors and loudspeakers is accomplished without the use of relays or current-limiting devices. Short-circuiting the outputs will not cause any damage.

Specifications include: power output at less than 0.01% THD of 100 watts-per-channel from 5 Hz to 20,000 Hz, both channels driven into 8 ohm loads; damping factor of greater than 100 at 1-kHz into an 8-ohm load, total harmonic distortion is less than 0.002% at any frequency up to 1 kHz and less than 0.005% at any frequency up to 10 kHz; intermodulation distortion is less than 0.002% into an 8-ohm load with a 100-watt output; frequency response is 5 Hz to 100,000-Hz +0-dB, -1-dB; input impedance is 10,000 ohms and input sensitivity is 1 volt. The residual noise ratio is better than 117-dB with A-weighting.


The front-panel features peak-indicating

lamps that are integrated into the heat-sink fins. These lamps may be programmed with rear panel switches to light green at 1, 5, or 25 watts and red at 25, 50 watts or clipping. The lamps indicate the true preset peak value at any frequency.

The model 620, measures 15³/₄ x 6³/₄ x 9³/₈-inches and weighs 27.6 pounds. Price: \$600.00—Nakamichi Research (U.S.A.), Inc., 220 Westbury Ave., Carle Place, NY 11514.

CIRCLE 93 ON FREE INFORMATION CARD

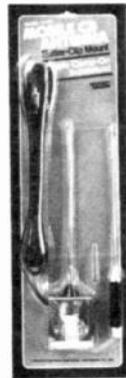MOBILE CB ANTENNAS, model CA-10 and CA-20. The Trunk-Lid model CA-10 is a base-loaded



unit that attaches to the trunk-lid without the need for screws or drilling. It features a neutral-



EVERY DEALER
NEEDS A

Levelite[®]
INSTANT TV SIGNAL INDICATOR

Levelite is not just a new product, it's a great new patented profit maker for distributors. About the size of a pocket calculator, it is invaluable for troubleshooting TV antenna and MATV systems. Every dealer will want to carry one with him on service calls, so he can instantly isolate the trouble either to the set or the antenna.

Jerrold is advertising the new Levelite heavily in dealer magazines. Be sure you stock it and display it.

JERROLD



GENERAL INSTRUMENT CORPORATION

Horsham, Pa. 19044 • (215) 674-4800

CIRCLE 53 ON FREE INFORMATION CARD

Get More from Your Car with a Mark 10 System.

The best-selling CDI system of its kind in the world—now at discount prices!

Would you like more power? Better mileage? And could you stand to eliminate 3 out of 4 of those expensive tune-ups? Well, that's what the MARK 10 capacitive discharge electronic ignition system is all about. Very simply, it boosts the spark to your engine—promoting better combustion, and minimizing combustion contaminants. Spark plug life is extended, all-weather starts are insured, and you can feel an increase in acceleration and overall engine performance—no matter what kind of car you drive. Learn more about a MARK 10 CDI system for your car (and take advantage of year-end discount prices), when you write today for a catalog and price list.



DELTA PRODUCTS, INC.

P.O. Box 1147, Dept. RE
Grand Junction, CO 81501
(303) 242-9000

I want to know more about Mark Ten CDI's. Send me complete no-nonsense information on how they can improve the performance of my car.

Name _____

Address _____

City _____ State _____ Zip _____

CIRCLE 33 ON FREE INFORMATION CARD

CB Secret Antenna

• CONVERTS YOUR CAR RADIO ANTENNA TO A CB MOBILE ANTENNA*
 • EASY-TO DO IT YOURSELF INSTALLATION

\$13.95

Limited **5 yrs** Warranty
 Unit will be replaced for 5 yrs

MONEY BACK GUARANTEE
 If you are not completely Satisfied

"SECRET" BECAUSE NO CB ANTENNA IS VISIBLE

• HELPS STOP THEFT
 • For all antennas, including windshields

ORDER TODAY

Sandia Sales
 235 K Robbins Lane
 Syosset, N.Y. 11791

Please rush me 1 CB Secret Antenna at the purchase price of \$13.95 plus 90¢ for Shipping & Handling

Enclosed is Check or Money Order for \$ _____
Sorry No C.O.D.'s (N.Y. Residents Add Sales Tax)

Please Print Name _____

Address _____

City _____ State _____ Zip _____



CIRCLE 65 ON FREE INFORMATION CARD

For faster service

USE ZIP CODE

on all mail

grey coil housing that will blend with the color of any vehicle and has a chromed base and spring that seats on a rubber base cushion. The overall length is 45 inches and the unit is equipped with 15 feet of coaxial-cable terminated in a standard PL-259 connector.

The Gutter-Clip model CA-20 features a center-loaded whip that attaches directly to the rain gutter of any car, truck or recreational vehicle without the need for drilling or screws. The antenna is only 21-inches high and features a tunable stainless steel whip, a 9-foot coaxial cable terminated with a PL-259 standard coaxial connector.

The model CA-20 is priced at \$19.95 and the model CA-10 at \$24.95.—EICO Electronic Instrument Co., Inc., 283 Malta St., Brooklyn, NY 11207.

CIRCLE 94 ON FREE INFORMATION CARD

CB ANTENNA, Long Gainer, is a tunable base-loaded stainless-steel antenna that can be easily adjusted to cover all channels across the band. A frequency adjustment screw is provided that brings in the desired channel clearly. It also has the capability of tuning in all the new channels as they become available.

Some of the best TV repair tools you can buy come in cans.



Meet the proven, dependable line of electronic spray chemicals from RCA.

At the head is Big Red, the concentrated spray foam that cleans, polishes and lubricates tuner contacts with no drift or detuning after-effects.

Next in line: our Heavy Duty Control Cleaner and Lubricant that's safe for plastics; our Tuner Cleaner Lubricant; our instant-cooling Circuit Chiller; and our non-flammable Relay and Contact Cleaner.

All are necessary tools from RCA, the name electronic technicians rely on for quality and work-saving dependability. To do the best job, you've got to use the best tools: RCA Deluxe Electronic Spray Chemicals. See your RCA Spray Chemical Distributor or, for additional information, contact RCA Distributor and Special Products Division, Sales Promotion Services, Bldg. 206-2, Cherry Hill, N.J. 08101.

RCA Distributor and Special Products Division

BETTER THAN A THIRD HAND!



PANA VISE TILTS, TURNS, AND ROTATES TO ANY POSITION. IT HOLDS YOUR WORK EXACTLY WHERE YOU WANT IT.

PanaVise has great strength yet is gentle enough to firmly hold delicate objects.

Quite possibly the finest new tool you will buy this year, PanaVise is built to exacting professional standards. We guarantee it!

Illustrated is the Electronics Vise Model 396. Three other bases and a wide variety of heads are available. All interchangeable! Buy a basic unit, then add on to create your system.


Available through your dealer. Write for a free catalog.

PANA VISE Dept. 22E
 10107 Adella Ave., South Gate, CA 90280
 In Canada: 25 Toro Rd., Downsview, Ont. M3J 2A6

A Division of Colbert Industries

CIRCLE 15 ON FREE INFORMATION CARD

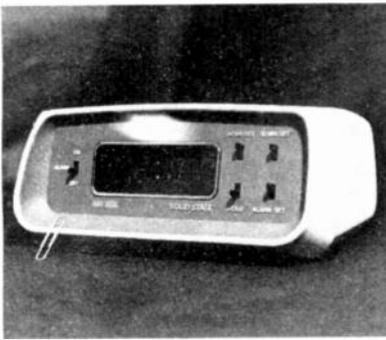EXECUTIVE DIGITAL ALARM CLOCK KIT-ONLY \$29.95



FAMOUS MAKE-LIMITED QUANTITY
AVAILABLE
ALL Parts Included

FEATURES

- Delux Ivory Case
 - 24 Hr. Alarm Set
 - Easy To Read 3/4" LED'S
 - AM/PM Indication
- Send Check Or Money Order To—
(N.J. Residents Add 5% Sales Tax)

J.B. ELECTRONICS INC.
P.O. BOX 104
SHORT HILLS, N.J. 07078

CIRCLE 39 ON FREE INFORMATION CARD

The Long Gainer has a long lasting stainless-steel whip and deluxe mount with high-quality coaxial cable designed for easy snap-on installation. No drilling is required because it mounts easily to the trunk lip. A PL-259 coaxial



connector is also provided. Maximum height of the antenna is 60-inches and the tuning range is 26.9 to 27.5 megahertz.—Anixter Bros., Inc., 4711 Golf Road, One Concourse Plaza, Skokie, IL 60076.

CIRCLE 97 ON FREE INFORMATION CARD

FREE catalog

over 2000

unique tools,
handy kits,
precision
instruments,
technical
supplies.

Over 24 years of service to the world's finest craftsmen and technicians.

A carefully selected and tested assortment of unique, hard-to-find tools, clever gadgets, precision instruments, bargain kits. One-stop shopping for the technician, craftsman, hobbyist, lab specialist, production supervisor. Many tools and measuring instruments available nowhere else. One of the most unusual and complete tool catalogs anywhere. Get your copy of the NC FLASHER today.


National Camera
2000 West Union Ave., Dept. GBA
Englewood, Colorado 80110
(303) 789-1893

CIRCLE 11 ON FREE INFORMATION CARD

A COMPLETE SYSTEM FOR ONLY \$459.00 IN KIT FORM
\$709.00 ASSEMBLED & TESTED

VERSATILITY

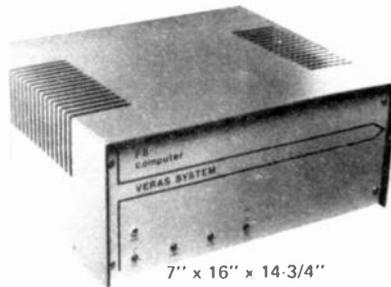With CPU card, buffered mother card, power supply and cabinet. The VERAS System is developed around the popular F-8 Series of chips which in our estimation is the finest and most versatile Micro processor now available.



7" x 16" x 14-3/4"

OUR 4K STATIC RAM BOARD FEATURES: (OPTIONAL)

- Outputs buffered.
- On board decoding for any four of 64 pages.
- Address and data lines are fully buffered
- 32 2102 1 static RAM's, 500 ns. or less, requiring no refreshing
- No onboard regulators to cause heat problems (Chassis mounted)
- 4K memory boards with connector, buffers and static RAM's are available in kit form for \$149.00

The fully buffered mother board will accept (4) 4K RAM boards for a total of 16K bytes of memory. Individual power terminals for each 4K RAM board are provided. Memory expansion beyond 16K bytes can be accomplished by the addition of more mother boards. Extra buffered mother boards with connector are available in kit form for \$45.00

Our modular power supply is designed around a high frequency torroid transformer which affords a large saving in size and weight and keeps filtering to a minimum. It is rated at +5V at 10 amps and -5V and ±12V at 1 amp. This power supply will drive our CPU, four memory boards and some peripherals.

POWER SUPPLY KIT \$139.00

All boards are high quality G-10, double sided, solder plated with gold plated edge connector.

TINY 2K BASIC (AVAILABLE) OCTOBER 15, 1976 \$25.00
5K BASIC (AVAILABLE) DECEMBER 15, 1976 \$50.00

PACKAGING FEATURES ARE:

- All Complete modular plug in construction.
- B) Specifically designed rugged aluminum card rack with provisions for voltage regulators (TO-220 supplied) to keep heat off the boards
- C) Designed for convection or optional forced cooling
- D) All I/O ports brought out to the rear panel connectors for easy accessibility
- E) Auxiliary DC power available at the rear panel to power peripherals

Veras Systems is currently developing the following:

UV PROM board, DMI and DMA board, Cassette, modern, video board and more. All these boards will have innovative design, something you will come to expect from VERAS SYSTEMS.

Computer dealers and hobbyist club inquiries are invited.

Expected delivery time 30 days or less.

CIRCLE 66 ON FREE INFORMATION CARD

THE VERAS F8 COMPUTER

THE BEST DESIGNED COMPUTER
FOR THE LOWEST DOLLAR COST
ON THE MARKET TODAY

THE CPU BOARD FEATURES:

- Two I/O ports each on the CPU and ROM chip make 32 bidirectional TTI lines
- The Fairbug* programmed storage unit provides the programmer with all I/O subroutines, allows the programmer to alter or display memory, and register its contents via teletype
- Programmable internal timer is built into the ROM chip.
- Built in clock generator and power on reset are built into the CPU chip
- There is a local interrupt with automatic address vector
- It is expandable to 65K bytes of memory
- 20 mil loop and/or RS232 interface included
- 1K of on board 2102 RAM
- Serial interface built into PSU chip

The More Flexible and Expandable
Computer at a Comparative Price.

VERAS SYSTEMS

Warranty: 90 days on parts and labor for assembled units. 90 days on parts for kits. Prices, specifications, and delivery subject to change without notice.

* Fairbug is a registered trademark of Fairchild Corp

VERAS SYSTEMS
A Div. of Solid State Sales, Inc.
Box 74D, Somerville, MA 02143
(617) 547-1461

Enclosed is check for \$ _____
or Master Charge # _____


VERAS F 8 Computer Kit Assembled
 4K Ram Board Quantity _____
 Power Supply Kit

Name _____
Address _____
City, State _____ Zip _____

WANT TO HOOK UP A CIRCUIT QUICK?

The PB-100 is only one of our family of solderless Proto-Board breadboarding units, designed to help you assemble, test and modify circuits as fast as you can push in or pull out a lead. *Preassembled* sockets with durable 5-point terminals provide low-resistance interconnections you can arrange and re-arrange at will.

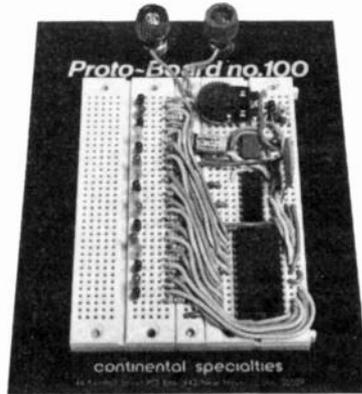Resistors, capacitors, transistors, DIP's, TO-5's, LED's etc. plug in without damage to leads. And jumper connections, where required, are lengths of #22 AWG solid wire. Models from 630 to 3060 tie-point (6 to 32 14-pin DIP) capacity available. For more information, see your CSC dealer, or write for our catalog and distributor list.



Proto-Board® 100. 760 solderless tie-points. Kit, \$19.95*

CONTINENTAL SPECIALTIES CORPORATION



EASY DOES IT
44 Kendall Street, Box 1942
New Haven, CT 06509 • 203-624-3103 TWX 710-465-1227
West Coast office Box 7809, San Francisco, CA
94119 • 415-421-8872 TWX 910-372-7992


© 1976, CSC

*Mfrs. sugg. list

CIRCLE 30 ON FREE INFORMATION CARD

CASSETTE DECK, model CG-362, is front loading and has three motors and full digital IC logic controls. Also featured is a digital tape counter, auto-stop, tape-flow control, remote control possibilities, input mixing and three position replay program selector.

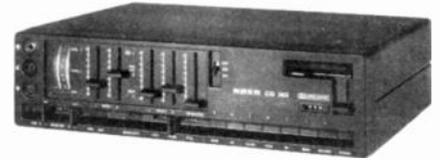The model CG-362 incorporates Dolby noise reduction and DNL. There's a switchable multiplex filter that's important when dubbing from FM Stereo and disconnectable when dubbing from records. Automatic bias and EQ is available and there is a 3-position switch for setting three types of tape—ferric oxide or ferrichrome. RCA-type input and output connectors are included as well as DIN connectors.



Frequency response is 20 Hz to 18,000 Hz, wow-and-flutter is less than 0.15% RMS and the signal-to-noise ratio is better than 68 dB with chrome tape and Dolby.

The output of the model CG-362 is 0.5 watts 4-ohms and is ideal for driving Philips' type motional feedback speakers.—Uher Of America, 621, S. Hindry Ave., Inglewood, CA 90301.

CIRCLE 98 ON FREE INFORMATION CARD

VHF SCANNER, model SBE-11SM, is a super-sensitive, ultra-compact VHF scanner monitor with exceptionally low current-drain. The scanner receiver is called the Pocket Sentinel because it fits neatly inside a shirt pocket.

The unit delivers a full 100-mW audio output with only 0.08-amps power consumption. Sensitivity is 0.7µV for 12-dB SINAB. Adjacent channel rejection is -55 dB.



The model SB-11SM offers both low- and high-band VHF coverage from 30 MHz to 50 MHz and from 148 MHz to 174 MHz. It provides four-channel coverage and features LED channel indicator lights. Also featured are separate volume and squelch controls, switch for channel lockouts, a switch for manual scan of all four

NEWS RELEASE 1976

OFFICIAL TESTING LAB RATES ALLISON #1...

the BEST of ALL Ignition Systems!

★ The ALLISON "Opto" was Officially Rated #1 by a Foreign Government Testing Laboratory as the BEST "Fuel Saving" Ignition of ALL the Ignition Systems Tested, including Systems with C.D. "add-ons!"

NEW ALLISON 'OPTO XR-700'

with the Exclusive... "Built-In" SOLID-STATE VOLTAGE REGULATOR

★ The "XR-700" is a NEW, redesigned, EASIER TO INSTALL version of the Allison "Opto-Electric", with the New addition of the Voltage Regulator, making it the MOST RELIABLE and Fool-Proof Ignition System ever invented.




★ Allison replaced the mechanical Breaker-Points and Condenser with a "Highly Accurate" Optical Control. A Beam of Light, passing through a specially designed ROTOR" precisely triggers a Heavy-Duty "POWER MODULE" that BOTH "Charges and Fires" the Ignition Coil, with the "FASTEST" High Voltage RISE TIME, producing the MAXIMUM "HIGHEST ENERGY" SPARK available.

★ Since there is NO Mechanical Friction, there are NO Parts to ever WEAR or need replacing, and ONCE properly Timed, it should NEVER need any Maintenance! DWELL never needs adjustment, it is PRE-SET to supply the OPTIMUM Performance at BOTH High and Low Speeds. The RPM Capability of the "XR-700" is Factory Tested to 15,000 RPM.

★ The "High-Energy" SPARK INTENSITY and DURATION... permits the Positive FIRING of Spark-Plugs, even under the MOST ADVERSE conditions, results in more COMPLETE COMBUSTION and Eliminates "Engine Misfire", hence fewer exhaust Emissions, IMPROVED Fuel Mileage, a HIGHER Performance Level... and helps keep Plugs FROM FOULING, which greatly extends the Spark-Plug LIFE!

★ Only the Highest Grade (U.S. Made) Solid-State Components are used. UNAFFECTED by Moisture or Vibration! The Allison "XR-700" was engineered to OUTLAST the LIFE OF YOUR CAR!

★ "EASY-TO-FOLLOW" INSTALLATION. (Not Necessary to Dismantle your Distributor.)

★ "XR-700"...Designed for those who want the BEST in Performance, Gas Mileage, Quicker Starting, Eliminate frequent Tune-Ups and Maintenance Costs.

FACTORY-BACKED 10-YEAR WARRANTY.
FREE Unit Repair or Replacement on ANY Defects

★ **ORDER WITH CONFIDENCE...**
Remember, even if you PAY Three Times as much, you cannot get a better Ignition System than the "XR-700"!

★ **SAVE! ORDER FACTORY DIRECT.**
Send Check or M.O., Car Make, Year, No. Cyl. (4, 6, or 8-Cyl.)

★ You may use your MASTER CHARGE or BANKAMERICARD. Send us (1) Your Number, (2) Interbank No., (3) Exp. Date

★ MC or BA Card Holders, ORDER by TOLL FREE PHONE: (800) 423-6525, Ext. 2. (When in Continental U.S.A.)

★ **Before Buying ANY other Type Ignition System... Send Postcard for FREE BROCHURE.**

★ "CB" USERS: The XR-700 completely ELIMINATES the Major Cause of Primary (Ignition Noise) Interference.

★ **Convert Your "C-D" Unit to BREAKERLESS!**
INCREASE ITS EFFICIENCY with "XR-CD"...Only \$34.95

★ America's Oldest and Largest Manufacturer of Opto-Electronic Ignition Systems. ©

ALLISON ★ Our BEST Salesmen...are the USERS of our ALLISON Systems!
AUTOMOTIVE CO. 1267 -E9, East EDNA Pl., COVINA, CAL. 91722

FREE burglar — fire alarm catalog



over 900 systems, detectors, controls, sounders, tools, locks, supplies

TO PROTECT HOMES, BUSINESSES, INDUSTRY

Huge selection of hard-to-find security equipment from stock. 64 fact-filled pages loaded with 100's of highest quality professional alarm products, technical notes, diagrams.

ONE-STOP SUPERMARKET SELECTION INCLUDES:

ultrasonics, radar, infrared, undercarpet mats, magnetic contacts, smoke & heat detectors; Controls; Alarms: bells, sirens, phone dialers, lights, guard panels. Large selection of tools, relays, wire, holdup alarms, books. Fills need for industry, alarm cos., businesses, homes, institutions. Order your copy today. (Outside U.S., send \$1.00.)




mountain west alarm
4215 n. 16th st.
phoenix, az. 85016
(602) 263-8831

CIRCLE 10 ON FREE INFORMATION CARD

channels, an earphone jack and a built-in charger jack for use with an optional SBE-5AC charger for nicad batteries. The unit measures 6.5 high x 2.75 wide x 1.38-inches deep and weighs 12.5 ounces with batteries.—SBE, Inc., Department P. 220 Airport Blvd., Watsonville, CA 95076.

CIRCLE 99 ON FREE INFORMATION CARD

CB MOUNTING BRACKET, model 14T170, provides quick removal and reinstallation of CB transceivers to prevent theft or unauthorized use of such equipment during the operator's absence. The adaptor permits quick-release brackets to be mounted either under-the-dash-board of the automobile or on the vehicle's floor. Connections between the transceiver and the power source are made with spring-loaded brass contacts. The antenna circuit includes a shielded connector for coaxial cable.

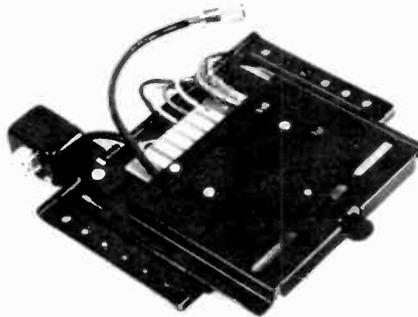

A separate dash-mount section—model 14T171—is also available for installation of a single transceiver unit in a second vehicle, providing a convenient transfer from one operating location to another—RCA, Distributor and Special Products Division, Cherry Hill Offices, Camden, NJ 08101.

CIRCLE 101 ON FREE INFORMATION CARD

SUPER SIGNAL SOURCE!



L-15 PULSE-SWEEP FUNCTION GENERATOR

\$55 KIT \$75 ASSEMBLED (+\$2.00 P&H)

FOR: Designers, Service Techs, anyone working with electronics!

FEATURES: 1Hz to 100KHz in 5 ranges, at constant amplitude • Sine and triangle adjustable to 20vp-p into 600 ohms • Sine distortion is .5% typical • Voltage controlled sweep of sine and triangle waves • TTL square wave has a fully adjustable pulse and drives 600 ohms • Frequencies of lower than 1Hz and greater than 100KHz are obtainable • short proof and guaranteed for 1 full year • Small, only 3" H x 6 1/4" W x 4" D • State-of-the-art design!

DEALER INQUIRIES INVITED



HELECTRONIX
8100 St. Clair Ave.
N. Hollywood, CA 91605
(213) 767-5624

CIRCLE 36 ON FREE INFORMATION CARD

- 6-Top Brand Silicon RECT. 1 amp. 1000 PIV RCA 110 FLYBACK TRANSFORMER For Blk & Wht. sets—18KV For all types TVs, inc. schem. 3 FOR 100.00. 3.95
- 110 TV DEFLECTION YOKE for all types TV's incl schematic 4.95
- "COMBINATION SPECIAL" RCA 110 FLYBACK plus 110 DEFLECTION YOKE 6.95
- 90 FLYBACK TRANSFORMER for all type TV's (Blk & Wht.) 2.95
- 70 FLYBACK TRANSFORMER for all type TV's (Blk & Wht.) 2.00
- 70 TV DEFLECTION YOKE for all type TV's (Blk & Wht.) 2.00
- OLYMPIC & SHARP FLYBACK Part #NPT592 Equip Stancor #HO-408-Thordarson #Fly389 2.00
- 90 COLOR YOKE For all Rectangular 19 to 25" Color CRT's. 7.95
- 70 COLORE YOKE For all round color CRT's 5.95
- DELMONICO NIVICO COLOR FLYBACK Part #A20411-B 7.95
- WESTINGHOUSE FM TUNER #476-V-015D0 1 Transistor 3.99
- WESTINGHOUSE FM TUNER (121978) Tube 1.00
- UHF TUNER—Transistor Type Used in all TV sets 2.95
- G.E. UHF TUNER—TRANSISTOR TYPE Model #83A4 3.95
- ADMIRAL TV TUNER Model #94C393-1 (2HA5-4L8) Model #T91C441-3 (Transistor) 7.95
- WELLS GARDNER TUNER Part #7A 128-1 (6ES7-21AT Tubes) 7.95
- G.E.—TV TUNER (2GR3-4L8) Model #EP 80X11 7.95
- PHILCO UHF/VHF TUNER Transistorized 9.95
- 100 GREY SPEAKER WIRE 2 Cond. min. 2 ft. 101 uses 2.00
- UNIVERSAL TV Antenna Back of set mounting 1 section rods 2.99
- BLUE LATERAL Magnet Assy. Replacement for most color TV's 1.79
- COLOR CONVERGENCE Assy. Universal type—good for most sets 2.49
- 7 TUBE AM-FM STEREO AMPLIFIER CHASSIS. Completely assembled—with tubes AS IS needs slight adjustments 9.95
- 10—MINI ELECTROLYTIC Cond For Transistor & miniature work 1.00
- TUBE SPECIAL—IN LOTS OF 5 2CY5-518-12BD6-12BH7-18FV6 2.50

- ### GE NI-CAD RECHARGEABLE BATTERIES
- CHARGER & ANY 2 BATTERIES \$12.95
- 2-AA BATTERIES..... \$5.95 Pair
 - 2-C BATTERIES..... \$6.25 Pair
 - 2-D BATTERIES..... \$6.50 Pair
- 1000 Recharges guaranteed
- HIGH VOLTAGE POWER TRANSISTOR Equiv. HEP 707 List price \$16.00 2.29
 - TACHOMETER 2 1/4" Sq. Panel Meter 1-VDC, full scale 33 Ohm coil resistance 0-9000 R.P.M. 2.00
 - 1-CASSETTE type dynamic Mike with universal plugs—200 Ohms 2.99
 - 1-VARCO STEREO CARTRIDGE Model TN-4B with holder 2.95
 - 2-ELECTROLYTIC CONDENSERS 100-100 60 MFD—160V 1.00
 - 2-ELECTROLYTIC COND 200/30/4—mfd—350V 1.00
 - 3-ELECTROLYTIC COND 100 mfd.—100V 50 mfd.—75V 1.00
 - 2-ELECTROLYTIC COND 80 mfd.—500V 40 mfd.—300V 1.00
 - 8—MINI PILOT BULBS With 8 Leads—6.3V, 30MA (5000 Hrs.) 1.00
 - 8—MINI PILOT BULBS With 12 Leads—6.3V, 150MA (5000 Hrs.) 1.00
 - 32—TEST PROD WIRE DELUXE QUALITY red & black 1.00
 - 1—COLOR POWER TRANSFORMER RCA 36R150 special 6.95
 - 2—Colorburst Quartz-Crystal For most color TV sets \$579.545 KC 1.89
 - 5 ASST GLOBAL VARISTOR Popular replacements for most COLOR TV. 1.00
 - COLOR-TV RECTIFIER—Used in most color sets—6500 kv 3 for 1.95
 - 4—TV ALIGNMENT TOOLS most useful assortment = 1 1.00
 - 4—TV ALIGNMENT TOOLS For Color TV #2 1.49
 - 6—TV COLOR ALIGNMENT TOOLS Most popular type 2.79
 - TV TWIN LEAD-IN 300 ohm 500'—\$.70 1.00
 - CO AX CABLE RG59U (Black) 250'—\$.10, 100'—\$.40, 50'—\$.70 2.69
 - 5—DUAL DIODE—MOST POPULAR TYPES Common cathode or Series connected 2.50

MARKET SCOOP COLUMN

- ZENITH SILICON STICK RECTIFIER. PART # 103-215—45K PIV, also used in Electrohme, Motorola, E.O.I. 5.95
- 3-ZENITH VIDEO AMPLIFIER PART # 121-743 2.00
- 2-SILICON NPN TRANSISTOR HEP-80015 List \$1.75 1.90
- 1-SILICON NPN TRANSISTOR (SK3534—HEP S6004) 1.00
- 5-ZENIER DIODE 1N4757A Watt—50 V 1.90
- 4—ASSD. PHILCO SWITCHES—PUSH-PUSH TYPE #TV2-3-4, & Sig. Sv. With knobs latest type 2.99
- POWER TRANSFORMER (1T-46)—110V Pri.—12V Sec. Used in many transistor Power supplies 2.29
- COLOR DELAY LINE—Used in most color sets 1.59
- Silicon NPN HV TRANSISTOR RCA—SK-3022—Hep-240 RCA—SK-3026—Hep-241 1.20
- Transistor Specials—Your Choice SK3006, SK3018, SK3020, SK3122, SK3124 1.20
- Transistor Specials—Your Choice SK3006, SK3024, SK3040 1.98
- WAIL-CORDLESS SOLDER IRON Complete with Auto Charger—Fast Heating—Compact 17.95
- 5—Audio Output TRANSFORM Sub-min for Trans Radios 1.00
- 5—L.F. Coil TRANSFORMERS 456-ke for Transistor Radios 1.00
- 6" UNIVERSAL SPEAKER Top quality Special Buy EA 1.59
- 10"—UNIVERSAL SPEAKER Large Magnet—Top quality EA 4.95
- 8" UNIVERSAL SPEAKER—Large Magnet—Special Buy EA 2.99
- 2 1/2"x4" SPEAKER Special Buy 10 for \$5 EA 69¢
- 4"x6" "QUAM" 16 OHM SPK. Large magnet Special BUY (10 for \$15.00) 1.79
- 8"—HEAVY DUTY 10 OZ. SPEAKER Ceramic Type—8 ohm EA 5.95
- 1—6"x9" Heavy Duty 10 oz. Speaker Ceramic Type—8 ohm EA 5.95
- 3-ELECTROLYTIC CONDENSERS 100/30-20 MFD—300 Volts 2.00
- ZENITH TRIPLER PART #212-109 Equivalent to ECG501-33K V Out, 2500pf. 3.95

Test Equip. Special Discount Prices

- ## Leader

SENCORE
- TRANSISTOR RADIO asst type good, bad, broken, as-is, pulltek 1.50
 - TAPE RECORDER assorted types good, bad, broken, as-is, pulltek 4.00
 - 200 ASST. 1/2 W RESISTORS Top Brands, Short Leads, Excellent Selection 1.00
 - 75-ASST 1/4 WATT RESISTORS stand, choice ohmages, some in 5's 1.00
 - 100-ASST 1/2 WATT RESISTORS stand, choice ohmages, some in 5's 1.00
 - 70-ASST 1 WATT RESISTORS stand, choice ohmages, some in 5's 1.00
 - 35-ASST 2 WATT RESISTORS stand, choice ohmages, some in 5's 1.00
 - 50-PRECISION RESISTORS asst. list-price \$50 less 98% 1.00
 - 20-ASSORTED WIREWOUND RESISTORS, 5, 10, 20 watt 1.00
 - 250-ASST SOLDERING LUGS best types and sizes 1.00
 - 250-ASST WOOD SCREWS finest popular selection 1.00
 - 250-Asst Self Tapping SCREWS = 6, = 8, etc. 1.00
 - 100-ASST 6/32 SCREWS and 100-6/32 HEX NUTS 1.00
 - 100-ASST 8/32 SCREWS and 100-8/32 HEX NUTS 1.00
 - 100-ASST 2/56 SCREWS and 100-2/56 HEX NUTS 1.00
 - 100-ASST 4/40 SCREWS and 100-4/40 HEX NUTS 1.00
 - 100-ASST 5/40 SCREWS and 100-5/40 HEX NUTS 1.00
 - 500-ASSORTED RIVETS most useful selected sizes 1.00
 - 100-ASST RUBBER BUMPERS for cabinet bottoms—other uses 1.00
 - 100-Asst RUBBER GROMMETS best sizes 1.00
 - 10-ASST SLIDE SWITCHES SPST, SPDT, DPDT, etc. 1.00
 - 15-ASST. ROTARY SWITCHES All popular types—\$20 value 1.00
- Minimum Order \$5.00

IMMEDIATE DELIVERY . . . Scientific light packing for safe delivery at minimum cost.

HANDY WAY TO ORDER . . . Send check or money order, add extra for shipping. Lists of new offers will be returned in your order.


Please specify refund on shipping overpayment desired: CHECK POSTAGE STAMPS MERCHANDISE (our choice) with advantage to customer

BROOKS RADIO & TV CORP., 529 Columbus Ave., New York, N.Y. 10024

TELEPHONE
212-874 5600

CIRCLE 40 ON FREE INFORMATION CARD

A PRIME STANDARD AT YOUR FINGERTIPS

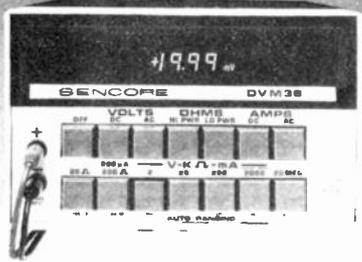

\$348

FOR COMPLETE MEASURING CONFIDENCE

A NEW STANDARD IS BORN
High accuracy you can trust
Versatile measuring capabilities
An efficient, easy to operate meter
All at an affordable price
That's the DVM38 . . . The complete DVM that sets new performance standards in 4 key areas.

A NEW ACCURACY STANDARD
The 3 1/2 digit, .1% accuracy is backed by a 15 meg Ω input impedance, compared to 10 meg Ω input of conventional DVM's, which guarantees up to 50% greater accuracy with 1/3 less circuit loading on every measurement for high accuracy you can trust.

A STANDARD IN CAPABILITIES
The DVM38 is more accurate in MORE circuits with these versatile ranges: 100 μ V to 2000V DC, 1KV AC; .01 Ω to 20 meg Ω ; 0.1 μ A to 2A . . . Plus

HI and LO ohms and a 50KVDC range with accessory Hv probe.

A NEW STANDARD IN SPEED AND EASE OF OPERATION
Large pushbuttons and callouts - no need to hunt and peck. Large .4" L.E.D.'s with direct readout, down to V and mV indicators. SINGLE STEP AUTO-RANGING for maximum resolution and efficiency. 2KV DC protection minimizes downtime.



THE AFFORDABLE STANDARD
There are few .1% DVM's less expensive - there are none as complete in this price range, plus backed by a LIFETIME guarantee against factory workmanship errors.

THE DVM38 A NEW STANDARD IN DVM'S FOR SPEED, VERSATILITY AND ACCURACY.

DVM38 BACKED BY SENCORE'S 100% MADE RIGHT LIFETIME GUARANTEE

SENCORE 3200 Sencore Drive Sioux Falls S.D. 57107 Phone 1 605 339 0100 TWX 910 660 0300

CIRCLE 37 ON FREE INFORMATION CARD

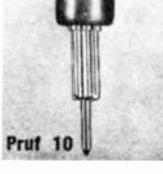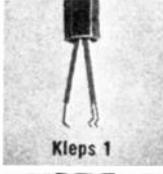

Clever Kleps

Test probes designed by your needs - Push to seize, push to release (all Kleps spring loaded).

- Kleps 10.** Boathook clamp grips wires, lugs, terminals. Accepts banana plug or bare wire lead. 4 3/4" long. \$1.39
 - Kleps 20.** Same, but 7" long. \$1.49
 - Kleps 30.** Completely flexible. Forked-tongue gripper. Accepts banana plug or bare lead. 6" long. \$1.79
 - Kleps 40.** Completely flexible. 3-segment automatic collet firmly grips wire ends, PC-board terminals, connector pins. Accepts banana plug or plain wire. 6 1/4" long. \$2.59
 - Kleps 1.** Economy Kleps for light line work (not lab quality). Meshing claws. 4 1/2" long. \$.99
 - Pruf 10.** Versatile test prod. Solder connection. Molded phenolic. Doubles as scribing tool. "Bunch" pin fits banana jack. Phone tip. 5 1/2" long. \$.89
- All in red or black - specify. (Add 50 \cent postage and handling). Write for complete catalog of - test probes, plugs, sockets, connectors, earphones, headsets, miniature components.

Available through your local distributor, or write to:

RYE INDUSTRIES INC.

133 Spencer Place, Mamaroneck, N.Y. 10543
In Canada: Rye Industries (Canada) Ltd.

CIRCLE 76 ON FREE INFORMATION CARD

1 out of 2 who have it don't know it...



21 million Americans have a high blood pressure. But 50 percent of those who have it don't know it!

When blood pressure goes higher than it should and stays high it sets the stage for heart attack or stroke.

Most cases of high blood pressure can be controlled with drugs and other advances in treatment. That's why you should see your doctor regularly. Only he can tell if you need help.

A public service message from your Heart Association



new lit

More information on new lit is available from the manufacturers of items identified by a Reader Service number. Use the Free Information Card following page 106.

TOOL CATALOG, No. 20. contains a comprehensive selection of hand tools and accessories for production and maintenance work in the electronics and electro-mechanical oriented industries. Product lines range from vapor degreasers to parts-holding boxes.

This edition introduces a self-contained catalog of tool kits for practically every service and installation. The 25 kits shown in the catalog range from security kits for alarm installers to computer installation units. Also included is a Design-A-Kit program to enable you to design, select and price a kit to your own specific requirements. -Techni-Tool, Inc., 5 Apollo Road, Plymouth Meeting, PA 19462.

CIRCLE 102 ON FREE INFORMATION CARD

COMPONENT CATALOG, No. 514. 56 pages of electronic components, test equipment, tools and production aids that are stocked for immediate delivery. Included are cabinets, alligator clips, speakers, battery holders, capacitors, fuses & holders, hardware, knobs, lamps,


CASTLE Timesavers

... for the Professional

SUBBER*

TV signal circuit analysts

* Made in U.S.A.

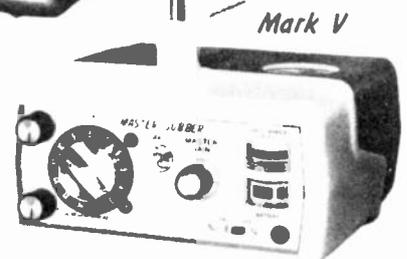

- Castle products
- advanced technology
 - modern styling
 - and they work!

Ask your electronic distributor for them or write for more details

CASTLE ELECTRONICS, INC.

5715 N. Western Ave. Chicago Ill 60645

Ph (312) 728 1800

In Canada Len Finkler Ltd. Ontario

CIRCLE 59 ON FREE INFORMATION CARD

meters, plugs & jacks, potentiometers, relays, resistors, semiconductors, switches, test equipment, soldering equipment, tools, transformers and wire. Prices are included.—Mouser Electronics, 11511 Woodside Ave., Lakeside, CA 92040

CIRCLE 103 ON FREE INFORMATION CARD

SOLDERING EQUIPMENT CATALOG, No. 76, features a full line of soldering and desoldering equipment for electronic service, industrial, craft and military users. Included are soldering irons, desoldering irons, kits and a desoldering head that converts a soldering iron into a desoldering iron. Also shown are tips, desoldering bulbs, and soldering-tool stands.

All irons feature a safety light that tells when it's on; a cool, unbreakable polycarbonate handle; and a flexible, burn-resistant Neoprene cord set. Soldering irons provide two heats—40W and 20W—to handle a wider range of work. Desoldering irons operate at 40W; Idle at 20W for longer tip life. An exclusive bracket insures alignment and prevents damage. Prices are included.—Enterprise Development Corp., 5137 East 65th Street, Indianapolis, IN 46220


CIRCLE 104 ON FREE INFORMATION CARD

IGNITION SYSTEMS. Four-color illustrated booklet describes a full line of electronic Ignition systems. The systems are designed to improve engine performance for the broad variety of people who have yet to purchase 1975-76 model cars.

Among the benefits claimed by the Mark 10 systems are the elimination of 3-out-of-4 regular engine tune-ups, up to 20% improvement in gas mileage, better acceleration and quicker starts. The systems (some of which are available in kit form), install easily in a matter of minutes.—Delta Products, Inc., P.O. Box 1147, Grand Junction, CO 81501.

CIRCLE 105 ON FREE INFORMATION CARD

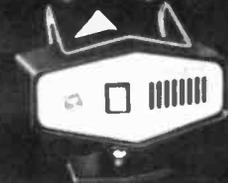Senturion Ultimate Long Range Radar Detector



NEW!

NOW ONLY \$89.95

SENTURION — 12 Volts Powerful

Safe professional drivers require the ultimate in advance notice of radar traffic control zones — computer designed antenna-integrated circuitry — audible and visual warning — operates off your car's electrical system. Send check, C.O.D. or charge to my credit card as indicated.

10 Day Money Back Guarantee
RADATRON CORP.

Dept. 2424-49 P.O. Box 177
N. Tonawanda, N.Y. 14120

- Am. Exp.
 Carte Blanche
 Diners Club
 Master Charge
 C.O.D.

Charge my credit card acct. no. Expir. Date _____

\$89.95 each plus postage & tax where applicable.

Signature _____

Name/Please Print _____

Address _____

City _____ State _____ Zip _____

CIRCLE 82 ON FREE INFORMATION CARD

LEARN QUICKLY—EASILY—AT HOME

Only I.H.S.I. offers these unique correspondence courses

MATHEMATICS ■ ELECTRONICS ■ ENGINEERING MATHEMATICS ■ ADVANCED MATHEMATICS ■ ADVANCED ENGINEERING MATHEMATICS ■

These unusual courses are the result of many years of research and teaching by the President of INDIANA HOME STUDY INSTITUTE, who has *personally* lectured in the classroom to *thousands* from all walks of life on mathematics, electrical and electronic engineering.

- You must see these lessons to appreciate them!
- NOW you can master mathematics and electronics and actually *enjoy* doing it!
- WE ARE THIS SURE:—you order your lessons on a *money-back guarantee*.
- In plain language, *if you aren't satisfied you don't pay a cent.*

There are no strings attached.

WRITE TODAY for more information and your outline of courses. You have everything to gain and nothing to lose!

LICENSED BY THE STATE BOARD OF INDEPENDENT POST-SECONDARY VOCATIONAL, TECHNICAL, TRADE AND BUSINESS SCHOOLS.

THE INDIANA HOME STUDY INSTITUTE


EASTERN DIVISION

P.O. BOX 1189

PANAMA CITY, FLA. 32401

CIRCLE 57 ON FREE INFORMATION CARD

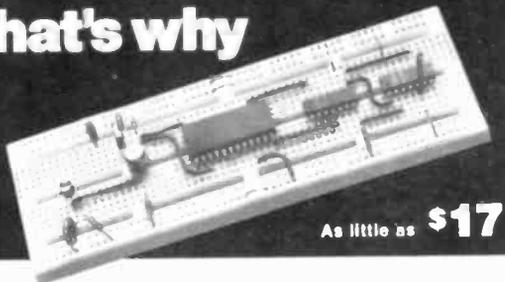It's faster, easier and less expensive. That's why we call it Super-Strip.



As little as **\$17**

This versatile mini breadboard features the same superior contacts, materials and construction we use in our full-scale ACE All Circuit Evaluators. Any solid hookup wire up to #20 plugs right in to connect DIPs, discretes and almost any components you have on hand. Super-Strip gives you 128 separate five-tie-point terminals in the circuit building matrix and 8 power and signal distribution lines — enough capacity to build circuits with as many as nine 14-pin DIPs. And when you're done with your hookup, just pull it apart — everything's as good as new. Super-Strips come with your choice of nickel-silver or gold-plated terminals. Plus an instant-mount backing and quick-removal screws for fast and easy stacking or racking. Heard enough? Then stop looking and start cooking with A P Products Super-Strips.

For quick phone service, call the A P distributor nearest you:

- | | |
|----------------|----------------|
| (201) 224-8032 | (513) 236-9900 |
| (206) 682-5025 | (516) 483-9200 |
| (213) 768-3800 | (516) 883-0999 |
| (213) 875-2862 | (914) 664-0088 |
| (215) 698-4000 | (602) 277-7661 |
| (216) 441-3000 | (612) 488-0201 |
| (218) 587-3600 | (617) 273-1880 |
| (312) 298-8580 | (617) 879-0860 |
| (313) 525-1800 | (713) 350-6771 |
| (314) 863-7800 | (713) 777-1666 |
| (412) 782-2300 | (714) 549-8611 |
| (415) 326-5432 | (714) 580-0515 |
| (415) 969-9240 | (803) 253-5333 |

Part Number	Model Number	Terminal Type	Price Each
923252	SS-2	nickel-silver	\$17.00
923748	SS-1	gold-plated	\$18.90

Orders subject to acceptance at factory.
Company PD's FOB Painesville. No COD Orders.



A P PRODUCTS INCORPORATED

Box 110-R Painesville, OH 44077 (216) 354-2101 TWX: 810-425-2250

Our Distributor List is growing daily.
If none in your area call
toll Free 800-321-9668.

CIRCLE 2 ON FREE INFORMATION CARD

next month

DECEMBER 1976

■ Projection TV Is Here Now

See the systems, the prices, how they work. You may have been looking to buy one, but did you know that there are more than 25 to choose from?

■ TV Games

Bad programming may give way to game boards on the TV screen as a new and growing competitor. Radio-Electronics looks at all the games you can buy and use now.

■ Installing A CB Rig

It isn't difficult if you have a guide. This story shows you how to do the job, in step-by-step detail, to help you do it right.

■ Noise Measurements In Audio

Careful testing is a must in this land of almost unmeasurables. Len Feldman shows how it's done and what to look for.

■ Expand A Calculator

We show how to take a common Novus calculator and add extra buttons and functions to the unit. Upgrade your calculator in December.

PLUS


Jack Darr's Service Clinic

More On Digital Multimeters

Two Hi-Fi Lab Tested Reports

Anti-Theft Circuits

Reader Questions and Solutions

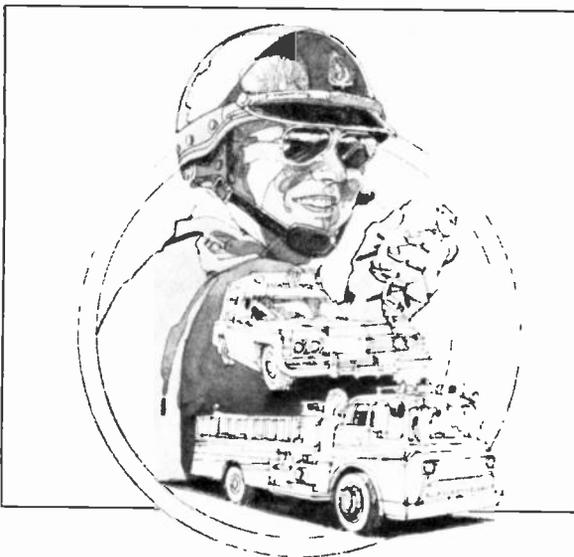

INTERNATIONAL FM 2400CH

FREQUENCY METER for testing mobile transmitters and receivers



- Tests Predetermined Frequencies 25 to 1000 MHz
- Extended Range Covers 950 MHz Band
- Pin Diode Attenuator for Full Range Coverage as Signal Generator
- Measures FM Deviation

The FM-2400CH provides an accurate frequency standard for testing and adjustment of mobile transmitters and receivers at predetermined frequencies.

The FM-2400CH with its extended range covers 25 to 1000 MHz. The frequencies can be those of the radio frequency channels of operation and/or the intermediate frequencies of the receiver between 5 MHz and 40 MHz.

Frequency Stability: $\pm .0005\%$ from $+50^{\circ}$ to $+104^{\circ}$ F.

Frequency stability with built-in thermometer and temperature corrected charts: $\pm .00025\%$ from $+25^{\circ}$ to $+125^{\circ}$ (.000125% special 450 MHz crystals available).

Self-contained in small portable case. Complete solid state circuitry. Rechargeable batteries.

FM-2400CH (meter only)\$595.00
RF crystals (with temperature correction) ... 24.00 ea.
RF crystals (less temperature correction) 18.00 ea.
IF crystalscatalog price



International Crystal Manufacturing Company, Inc.
10 North Lee, Oklahoma City, Oklahoma 73102
CIRCLE 24 ON FREE INFORMATION CARD

SINGLE CHANNEL ATTENUATION

I need a filter that will attenuate a single TV channel without affecting adjacent channels. Channel 3 is a very strong signal in my area and it laps over into Channel 2 and Channel 4. Is there such a filter?—W.M., Janesville, WI.

Yes. Jerrold, Blonder-Tongue, J.W. Miller and others make single-channel traps that tune sharply from 40 to 80 MHz. This would cover Channel 3, which is 60 to 66 MHz.

You might try the little RCA trap which is just a 4.5-inch length of 300 ohm twin-lead. Short one end and tie a ceramic trimmer capacitor (3–15 pF) across the other. Tape this tightly to your lead-in as close to the antenna terminals as possible. Now, tune for least interference on either Channel 2 or 4. If one of these helps but doesn't cure it, make up another one and try it as close to the first as possible.

CRITICAL SYNC

This is a tough dog! This Truetone MIC-4219A-27 has very critical sync, but it's not a sync problem! The video waveform at the detector doesn't have much sync on it. I can inject a video signal here and it works. Run this through the crystal-ball and see what shows up, please!—D.D., Apalachicola, FL.

It's a sync problem but it isn't the sync? (It's going to be one of those days.) OK: crystal-ball says this could be a "feedback cancellation of sync" due to open capacitor somewhere. Scope the DC power supply and the AGC line, etc., looking for any sign of signals.

(Feedback: reader says "Bless you and your crystal ball! I scoped the AGC line first and there it was; a 0.25-volt positive going spike at horizontal rate. Replaced the 1.0-μF non-polarized AGC filter and Bingo. Thanks.") R-E

BOOKS

by Donald J. Grantham

Check (✓) books you are ordering, and see below.

- GRANTHAM'S F.C.C. LICENSE STUDY GUIDE.** Includes 1475 FCC-type multiple-choice practice questions, covering all subjects (technical and non-technical), with answers and discussions, for 3rd, 2nd, and 1st class commercial radiotelephone license exams. Four information sections. 192 illustrations. 7×10½, 377 pages. ©1975. \$9.95
- INTRODUCTORY ELECTRICITY WITH MATHEMATICS.** For beginners (and for technicians who need a better understanding of "the basics"). Includes circuit diagrams, practice problems with answers, multiple-choice examinations. Written for self-study. 169 illustrations. 7×10½, 288 pages. ©1975. \$9.95
- FUNDAMENTAL PROPERTIES OF AC CIRCUITS.** Continues where *Introductory Electricity With Mathematics* (listed above) leaves off. Same format. 215 illustrations. Written for self-study. 7×10½, 267 pages. ©1976. \$9.95
- MATHEMATICS FOR BASIC CIRCUIT ANALYSIS.** Continues where *Fundamental Properties of AC Circuits* (listed above) leaves off. Same format. 104 illustrations. ©1976. \$9.95
- GEOMETRY FOR SCIENCE AND TECHNOLOGY.** Covers basic and analytic geometry, as needed by science and technology students at the community college level. Many illustrations. Practice problems with answers. Multiple-choice examinations. 7×10½, 141 pages. ©1976. \$4.25

■ Check the books you are ordering, complete the form below, clip ad and mail with your payment to:

GSE BOOKS

2000 Stoner Ave., Los Angeles, CA 90025

Please send the book(s) I have checked above. The price of the book(s) is \$____, and I am sending 75¢ extra to cover postage and handling of my complete order. Thus, I am enclosing a total of \$ _____

Name _____

Address _____

City _____ State ____ Zip _____

RE-77

Earn Your College DEGREE in Electronics by Correspondence


The Grantham college-degree program (by home study) begins with basics, leads first to the A.S.E.T. degree, and then continues through the B.S.E.E. degree level. Our free bulletin gives complete details of the program itself, the degrees awarded, the requirements for each degree, and how to enroll. Write for BULLETIN R-77.

Grantham School of Engineering
2000 Stoner Avenue, Los Angeles, CA 90025

CIRCLE 6 ON FREE INFORMATION CARD

EIGHT INSTRUMENTS IN ONE

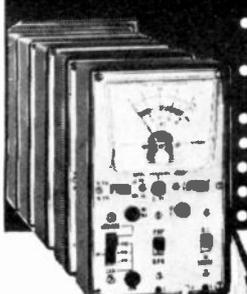- Out-of-Circuit Transistor Analyzer
- Dynamic In-Circuit Transistor & Radio Tester
- Signal Generator
- Signal Tracer • Voltmeter
- Milliammeter
- Battery Tester
- Diode Checker



Transistor Analyzer Model 212
Factory Wired & Tested—\$28.24
Easy-to-Assemble Kit—\$19.21

YOU DON'T NEED A BENCH FULL OF EQUIPMENT TO TEST TRANSISTOR RADIOS! All the facilities you need to check the transistors themselves — and the radios or other circuits in which they are used — have been ingeniously engineered into the compact, 6-inch high case of the Model 212. It's the transistor radio troubleshooter with all the features found only in more expensive units. Find defective transistors and circuit troubles speedily with a single, streamlined instrument instead of an elaborate hook-up.

Features:
Checks all transistor types — high or low power. Checks DC current gain (beta) to 200 in 3 ranges. Checks leakage. Universal test socket accepts different base configurations. Identifies unknown transistors as NPN or PNP.

Dynamic test for all transistors as signal amplifiers (oscillator check), in or out of circuit. Develops test signal for AF, IF, or RF circuits. Signal traces all circuits. Checks condition of diodes. Measures battery or other transistor-circuit power-supply voltages on 12-volt scale. No external power source needed. Measures circuit drain or other DC currents to 80 milliamperes. Supplied with three external leads for in-circuit testing and a pair of test leads for measuring voltage and current. Comes complete with instruction manual and transistor listing.

EMC, 625 Broadway, New York 12, N. Y.

Send me FREE catalog of the complete value-packed EMC line, and name of local distributor.


NAME _____ RE-11

ADDRESS _____

CITY _____ ZONE _____ STATE _____

EMC

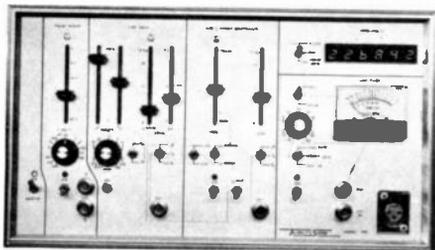ELECTRONIC MEASUREMENTS CORP.
625 Broadway, New York, N. Y. 10012



MODEL 100 AUDIO RESPONSE PLOTTING SYSTEM and general purpose sweep/tone burst/pulse generator consists of two sine/square/triangle function generators, pulse generator, frequency counter and peak amplitude measurement sections. It is primarily intended to generate a frequency response plot on an X-Y recorder or scope.

Time base generator offers symmetrical or independent control of the positive and negative sides of the ramp providing a duty cycle of .7% to 99.3%. Frequency range is .0035Hz to 100kHz. Amplitude is 15Vpp into 500 ohms with ± 5 VDC offset. The time base output drives the X axis of an X-Y recorder.

Audio sweep generator provides manual frequency adjustment or log/linear sweep of 20Hz to 20kHz. Blanking mode produces zero reference line on X-Y recorder or tone burst. Amplitude is 15 Vpp into 500 ohms or 10 Vpp into an 8 ohm speaker.

Pulse generator frequency range is .0035Hz to 525kHz. Pulse width is adjusted independent of frequency from 4 seconds to 40 nanoseconds. Outputs are complementary TTL.

Peak amplitude measurement section measures internal or external signals from mike to power amp level. Amplitude output drives Y axis of X-Y recorder.

Frequency counter is 6 digit, line triggered, and reads either internal or external. Sensitivity is 50 mv peak at 20kHz.

Dimensions: 8 x 14 x 3. Warranty: 1 year. \$525, stock to 30 days.

FIDELITY SOUND

1894 Commercenter W. #105
San Bernardino, Ca 92408
(714) 889-7823

CIRCLE 4 ON FREE INFORMATION CARD

NOISE REDUCTION

continued from page 77

with Super-ANRS is approximately half of what it would be without this circuit addition.

Finally, Fig. 10 illustrates the effect of Super-ANRS on overall record/playback frequency response for a recording made at the 0-dB record level. Without Super-ANRS, the response is down 3 dB

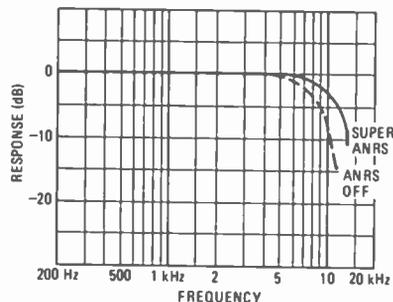



FIG. 10—RECORD/PLAYBACK frequency response with and without Super-ANRS.

at around 8 kHz while with Super-ANRS in the circuit, the 3 dB roll-off point extends to beyond 10 kHz. At lower recording levels, the improvement will, of course, be even more significant.

JVC has incorporated this new dynamic range expanding feature in

several of their newly introduced stereo cassette decks. One of these units, the model CD-1636, can be battery operated for use in live, field recording work.

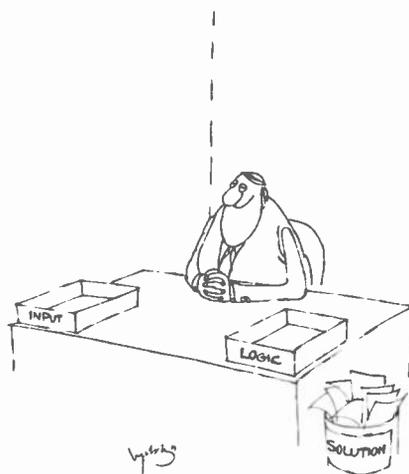The incorporation of Super-ANRS in such a deck is especially useful since in live microphone recording work, sudden transients are more likely to occur than when re-recording FM programs or phono discs in which a fair amount of signal compression has already been "built in" to and is inherent in the program source. **R-E**



GO DIGITAL, GO DANAMETER®

(The New VOM For Today's Needs.)

- 0.25% Accuracy
- Full Overload Protection
- Really Drop-Proof
- Full One Year Battery Life

DANA®

Dana Laboratories, Inc.

2401 Campus Dr, Irvine, Ca 92715, (714) 833-1234

CIRCLE 26 ON FREE INFORMATION CARD

The 5 SECOND TUNER RESTORER

CLEANS! LUBRICATES! POLISHES!

Spray TUN-O-POWER on tuner contacts, rotate the tuner and *within 5 seconds* you get beautiful color pictures on all channels. It's a minor miracle!

TUN-O-POWER is the most powerful polisher and lubricant ever developed. It works so well, you use a lot less. You can spray twice as many tuners with TUN-O-POWER as you can with an ordinary cleaner/lubricant.

What's more, TUN-O-POWER lubricant lasts for months longer than ordinary sprays. Detent action stays smooth as silk so you never have to worry about callbacks.

CHEMTRONICS INCORPORATED
45 HOFFMAN AVE., HAUPPAUGE N.Y. 11787 • (516) 582-3322

Our business is improving yours!

CIRCLE 54 ON FREE INFORMATION CARD

market center

CLASSIFIED COMMERCIAL RATE (for firms or individuals offering commercial products or services). \$1.40 per word... minimum 15 words.

NONCOMMERCIAL RATE (for individuals who want to buy or sell personal items) 85¢ per word... no minimum.

ONLY FIRST WORD AND NAME set in bold caps. Additional bold face (not available as all caps) at 10¢ per word. Payment must accompany all ads except those placed by accredited advertising agencies. 10% discount on 12 consecutive insertions, if paid in advance. All copy subject to publisher's approval. Advertisements using P.O. Box address will not be accepted until advertiser supplies publisher with permanent address and phone number. Copy to be in our hands on the 26th of the third month preceding the date of the issue (i.e. August issue closes May 26). When normal closing date falls on Saturday, Sunday or a holiday, issue closes on preceding working day.

BUSINESS OPPORTUNITIES

INCREASE TV set sales with your own, exclusive newspaper column. For free details, write **TELEVISION TIPS**, P.O. Box 157, Clarkston, GA 30021

HIGHLY PROFITABLE ONE-MAN ELECTRONIC FACTORY

Investment unnecessary, knowledge not required, sales handled by professionals. Ideal home business. Write today for facts! Postcard will do. **Barta-BK**, Box 248, Walnut Creek, CA 94597.

WANTED

QUICK cash... for electronic equipment, components, unused tubes. Send list now! **BARRY**, 512 Broadway, New York, NY 10012. 212 Walker 5-7000

C-MOS PROBE

will convert your voltmeter into a sensitive FET INPUT millivoltmeter. Complete kit \$112 plus shipping. Also: Temp Meters, Power Supplies, Design Consoles.

Send for FREE CATALOG

SCIENTIFIC INSTRUMENTS
BOX 1054R LIVERMORE CA 94550

EDUCATION & INSTRUCTION

DC regulated supplies—\$2.00, operational amplifiers—\$2.00. Design, build, use, and troubleshoot through understanding. An engineer authors. Technical Information Department, **JAKUSH ENTERPRISES**, Box 875, Troy, NY 12181

ELECTRONICS DESIGN NEWSLETTER

Learn Design Techniques!
★ Logic Design Techniques
★ Digital & Linear Design Theory & Procedures
★ Construction Projects
Write for FREE CATALOG of parts & kits
Subscription \$6 Sample Copy \$1
VALLEY WEST Box 2119-L Sunnyvale, CA 94087

TELEPHONE bugged? Don't be Watergated! Countermeasures brochure \$1.00. **NEGEYE LABORATORIES**, Box 547-RE, Pennsboro, WV 26415

FREE educational electronics catalog. Home study courses. Write to: **EDUKITS WORKSHOP**, Dept. 285G, Hewlett, NY 11557

PASS FCC examinations! Proven topical questions-answers cover First, Second, Third licenses. \$6.95, **EGW PUBLICATIONS**, Box 5516-FK, Walnut Creek, CA 94596

UNLOCK your future. Become professional Locksmith with spare time homestudy. \$13.00 in an hour possible. All tools, equipment included. Facts FREE. Send name. **LOCKSMITHING INSTITUTE** (homestudy). Dept. 1339-116, Little Falls, NJ 07424

F.C.C. EXAM MANUAL
PASS FCC EXAMS! Memorize, study—Test-Answers for FCC 1st and 2nd class Radiotelephone licenses. Newly revised multiple choice questions and diagrams cover all areas tested in FCC exams, plus Self-Study Ability Test. \$9.95 postpaid. Money-back guarantee.

Tests-Answers for FCC First and Second Class Commercial Licenses

COMMAND PRODUCTIONS P.O. Box 26348 E
RADIO ENGINEERING DIV. SAN FRANCISCO, CAL. 94126

GRANTHAM's FCC License Study Guide—377 pages. 1465 questions with answers/discussions—covering third, second, first radiotelephone examinations. \$10.70 postpaid. **GSE PUBLICATIONS**, 2000 Stoner, Los Angeles, CA 90025

PLANS & KITS

TREASURE finder kit and manual \$22.95. Five transistor circuitry. Manual only \$3.00. Shipping \$2.00. **TRIANGLE ELECTRONICS**, Box 377, Merrick, NY 11566

ORGAN KITS KEYBOARDS
THE ULTIMATE IN DESIGN AND SOUND
FREE LITERATURE

Wurlitzer reproductions
DEVTRONIX ORGAN PRODUCTS, Dept. 4B
5872 Amapola Dr. • San Jose, CA 95129

FOR SALE

CARBON film resistors—1/4W, 5% 10—4.7 megohms for 3 1/2¢ each. Fifty per value \$0.85. Discounts available. Free samples/specifications. Other quality components. \$1.00 postage. **COMPONENTS CENTER**, Box 134R, New York, NY 10038

NEW
Wafers are meant to be inserted in a .063" maximum thickness board and have .043" diameter pins on .156" centers.

CATALOG NUMBER	DESCRIPTION	PRICES	
		1-10	11-99
13-0001	12 pos. rt. angle connector	60	.50
13-0002	12 position wafer	60	.50
13-0003	9 pos. rt. angle connector	60	.50

SPECIAL!
1000 Molex IC terminals for \$7.50
2000 for \$13.50

SPECIAL!
Motorola 741 Mini Dip 35¢—10 for \$3.00

LINEAR

ELECTROLYTIC CAPACITORS
These orders in multiples of 5 per item

WVDC	WORKING (uF)	VOLTS	PRICE \$
10	16, 35, 50	.16	
20	16, 35, 50	.16	
30	16	.16	
50	16, 35	.22	
100	16, 35, 50	.25	
200	16	.22	
500	16	.34	
1000	16	.52	
2200	16	.80	

NE501A 2.80
NE555A 50
A710CA 60
A741V 40
A747CA 1 10
A748CV 74
A723CA 1 00
MC1468L 3 90

Red Led & Mtg. Hardware
T1-3/4
1-10 11-100
.35 .29

MINIATURE FILM CAPACITORS

VALUE (uF)	PRICE TABLE		
	1-14	15-50	51-100
.001	10	10	.06
.0047	10	10	.06
.01	10	10	.06
.05	19	17	.15
1	20	18	.16
22	25	23	.21

These units are made by International Gem. permits Cap. All units 100 V

FIXED POWER SUPPLY KITS

Specifications	P8518	F1218	F1818
Input Voltage (50 500Hz)	105 125v	105 125v	110 125v
Output Voltage	5v ± 5%	12v ± 5%	15v ± 5%
Output Current (I _a @ 25° C)	1.5A Max	1.5A Max	1.1A Max
PRICE	\$14.00	\$14.00	\$14.00

INDEX NITE SHORT CIRCUIT PROTECTION. Price includes Pre-drilled G 10 Board All Parts and Transformer

DISPLAY BEZELS

CATALOG NUMBER	FILTER COLOR	PRICE 12x	FRAME WIDTH C.
B04-80	Red	\$2.75	1.37
B14-80	Red	2.80	2.00
B14-80	Red	2.90	3.00
B24-80	Red	3.00	4.00
B24-70	Amber	2.95	4.00

These bezels are heat resistant plastic with a black matte finish. Filters are circular polarized type

SOCKETS
LOW PROFILE
These sockets are from TI

NUMBER OF PINS	5-10	10-15
8	21	18
14	25	24
24	48	35
28	50	48

TRANSISTORS

Part number	Package	Quantity	Price
2N3638A	P	5 TO-92	25
2N2222A	N	5 TO-18	20
2N5133	N	05 TO-18	25
2N5494	N	700 TO-220	1 05
2N4401	N	60 TO-92	60
2N4403	P	60 TO-92	30
TIP32	P	300 TO-220	1 05

TRIMMER POTENTIOMETERS

These are 5/16" diameter thru-mount trimmer potentiometers

VALUES OHMS	100 500 1K 5K 10K 20K	25K 250K 50K 100K	500K 1M 5M
1-10	11 99	100	
30	29	37	

80 of 50 MOLEX PIN NESTERS
7 pin style \$2.00
8 pin \$2.25

MOLEX IC TERMINAL
100 for \$1.80 300 for \$2.80 800 for \$4.20
180 for \$1.80 400 for \$3.40 800 for \$5.00
700 for \$5.00 900 for \$7.40
800 for \$5.00 1200 for \$9.20
Real of \$0.800 \$ 270.00

REGULATOR CIRCUITS

IC	5 volt regulator @ 1 SA max	1 99
MC7805CP	5 volt regulator @ 1 SA max	2.00
MC7812CP	12 volt regulator @ 1 SA max	2.00
MC7815CP	15 volt regulator @ 1 SA max	2.00

16 Page Catalog 25¢

DIODES

1N4001	10/\$1.00
1N4002	10/\$1.00
1N4148	10/\$1.00
1N5401	5/\$2.00
(3A 100PIV)	
1N744-739A	5, 3, 200

TRACY DESIGN CORP.
15870 BCHAER F • DETROIT, MI 48227 • (313) 838 2501

TERMS: Add 50¢ to orders under \$10. No CDD orders; place Mastercharge® or BankAmericard® orders by calling 415-562-0636, 24 hours. Cal res add tax.



GODBOUT
BILL GODBOUT ELECTRONICS
BOX 2355, OAKLAND AIRPORT, CA 94614

8PST DIP SWITCH \$1.95

**SPECIALS:
LIMITED QUANTITIES**

9601 Precision one-shot 3/\$1.00
74H40 High speed 7440 7/\$1.00
MM5262 2K dynamic RAM, Good price... \$1.25
FPQ3725 Quad PNP transistor array, type 2N-3725 transistors, in DIP... 4/\$1.95
Excellent core or LED drivers.

**RESISTOR ASSORTMENT
No.1 IS BACK! still \$3.95**
500 ½ watt resistors, good mix of values.


COOL MEMORY
DISCOUNT: Buy 10, take 10¢
Buy 100, take 20¢.

We just got a batch of low power and fast (450 ns maximum--full temp range) 2102L1 static RAMs. Perfect for memory boards--and at our usual reasonable price: \$1.95!

**PLAY WITH WIRE?
REQUEST OUR FLYER**

CIRCLE 31 ON FREE INFORMATION CARD

**DIGITAL ALARM
CLOCK
KIT-\$19.50**

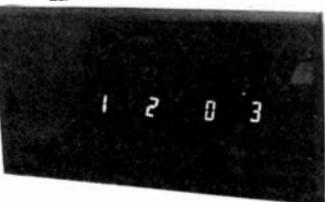

ALL PARTS INCLUDED
Includes Case (Blue or Red)
And Line Cord
Simple Assembly Instructions

FEATURES

- 24 Hr Alarm Setting
- AM/PM Indication
- Seconds Display
- Snooze Alarm
- 12 or 24 Hour Display
- 50/60 Cycle Operation

N.J. Residents Add 5% sales tax.
Send check or Money Order to:

J. B. ELECTRONICS INC.
P.O. Box 104
Short Hills, N.J. 07078

CIRCLE 38 ON FREE INFORMATION CARD

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page
48	Allison Automotive98
81	American Audioport..... 92
2	AP Products101
	Audio-Technica.....88
85	B&K-Div. of Dynascan36
40	Brooks Radio & TV99
59	Castle Electronics100
28	Channellock32
54	Chemtronics104
	CIE, Cleveland Institute of Electronics62-65
3	Cobra-Division of Dynascan... Cover IV
29,30	Continental Specialties 33,98
	CREI-Div. of McGraw-Hill Continuing Education 72-75
26	Dana Labs.....104
33	Delta Products95
77	Digital Concepts.....26
21,20	Edmund Scientific 37,124
61	EICO94
16	Electronics Book Club35
	E&L Instruments23
	EMC-Electronic Measurement103
4	Fidelity Sound104
58	GC Electronics28
72	Gem's Enterprises36
	GFN Industries (Sinclair).....39
6	Grantham School of Electronics103
	GTE Sylvania-Consumer Renewal Cover III
34	Handic of U.S.A.38
100	Heath18-21
36	Helectronix99
86	Hewlett-Packard.....87
7	Hickok Electrical Instruments30
56	Hufco Labs34
	IMS Associates24
43	International Business Systems90
57	Indiana Home Study Institute101
24	International Crystal Mfg.102
39	J.B. Electronics97
9	Jensen Tools.....92
52,53	Jerrold Electronics..... 2,95
23	Logical Technical Services.....89
69	Mallory Distributor Products.....17
71,70	MITS-Micro Instrumentation Telemetry Systems 1,14-15
10	Mountain West Alarm Supply99
78	Mura13
11	National Camera Supply.....97
	National Radio Institute (NRI)-Div. of McGraw-Hill Continuing Education Center8-11
	National Technical Schools52-55
27	PAIA Electronics22
15	Panavise, Division of Colbert Industries96
42	PTS Electronics34
82	Radatron101
79	Radio Shack25
	RCA Distributor & Special Products 90-91,96
76	Rye Industries.....100

Free Information Number Page

165	Sandia Sales96
25	SBE7
41	Schober Organ93
37	Sencore100
84	Shakespeare Cover 11
60	Southwest Technical Products..... 31
32	Tektronix.....29
74,75	Telematic-Div. of UXL 27,93
18	Tri-Star92
17	Tuner Service5
66	Veras Systems, Div. of Solid State Sales97
1	Wahl Clipper.....91
22	Weller-Xcelite, Div. of Cooper Industries.....16
MARKET CENTER	
49	Active Electronics Sales109
	American Used Computer114
51	Babylon Electronics118
	Karel Barta105
	Consumertronics110
	Command Productions105
	Cornell Electronics118
	Dage Scientific Instruments105
68	Delta Electronics120
	Devtronix Organ Products105
80	Digi-Key110
55	Eltron120
62	Fordham Radio Supply122
5,106	Formula International 119,120
	Financial Management Associates118
31	Godbout Electronics106
	Information Unlimited118
8	International Electronics.....121
	Interfab118
47	Jade115
44,45,46	James Electronics111,116,117
38	J.B. Electronics106
	Lab Science118
	Lakeside Industries114
63	Meshna Electronics114
64	New-Tone Electronics114
13	Nexus Trading110
12	Olson Electronics.....112
35,14	Poly Paks 112,123
50	Quest118
73	S.D. Sales113
67	Solid State Sales122
19	Surplus Center110
83	Tracy Design105
	Trintronics Limited114
	Trumbell118
	Valley West105
	Visulex 110,114

RADIO-ELECTRONICS

TTL 7400N

SN7400N	.15	SN74121N	.36
SN7401N	.15	SN74122N	.42
SN7402N	.15	SN74123N	.59
SN7403N	.15	SN74125N	.45
SN7404N	.18	SN74126N	.45
SN7405N	.18	SN74128N	.65
SN7406N	.18	SN74132N	.84
SN7407N	.34	SN74136N	.64
SN7408N	.18	SN74137N	.93
SN7409N	.18	SN74142N	3.70
SN7410N	.15	SN74143N	3.98
SN7411N	.21	SN74144N	3.98
SN7412N	.28	SN74145N	.89
SN7413N	.41	SN74147N	1.68
SN7414N	.79	SN74148N	1.25
SN7416N	.26	SN74150N	.99
SN7417N	.31	SN74151N	.63
SN7420N	.15	SN74153N	.63
SN7421N	.21	SN74154N	.99
SN7422N	.21	SN74155N	.78
SN7423N	.27	SN74156N	.69
SN7425N	.27	SN74157N	.64
SN7426N	.24	SN74159N	2.50
SN7427N	.27	SN74160N	.89
SN7428N	.35	SN74161N	.89
SN7430N	.15	SN74162N	.89
SN7432N	.24	SN74163N	.89
SN7433N	.35	SN74164N	1.10
SN7437N	.23	SN74165N	.99
SN7438N	.23	SN74166N	1.19
SN7440N	.15	SN74167N	2.98
SN7442N	.38	SN74170N	1.75
SN7443N	.85	SN74172N	8.75
SN7444N	.85	SN74173N	1.29
SN7445N	.74	SN74174N	.99
SN7446AN	.78	SN74175N	.89
SN7447AN	.78	SN74176N	.79
SN7448N	.74	SN74177N	.78
SN7450N	.15	SN74178N	1.25
SN7451N	.15	SN74179N	1.60
SN7453N	.15	SN74180N	.69
SN7454N	.15	SN74181N	1.99
SN7460N	.15	SN74182N	.69
SN7470N	.28	SN74184N	1.89
SN7472N	.27	SN74185AN	1.85
SN7473N	.31	SN74186N	6.95
SN7474N	.31	SN74188N	3.50
SN7475N	.48	SN74190N	1.09
SN7476N	.34	SN74191N	1.09
SN7480N	.39	SN74192N	.88
SN7481AN	.99	SN74193N	.88
SN7482N	.59	SN74194N	.94
SN7483AN	.69	SN74195N	.59
SN7484AN	1.65	SN74196N	.93
SN7485N	.88	SN74197N	.83
SN7486N	.32	SN74198N	1.69
SN7489N	1.95	SN74199N	1.69
SN7490AN	.65	SN74221N	1.20
SN7491AN	.65	SN74224N	1.85
SN7492AN	.64	SN74226N	1.85
SN7493AN	.46	SN74248N	1.75
SN7494N	.74	SN74249N	1.75
SN7495AN	.69	SN74251N	1.40
SN7496N	.69	SN74265N	.85
SN7497N	2.85	SN74278N	2.45
SN74100N	.99	SN74279N	.59
SN74104N	.43	SN74283N	1.45
SN74105N	.43	SN74284N	4.50
SN74107N	.29	SN74285N	4.50
SN74109N	.49	SN74290N	.85
SN74110N	.54	SN74293N	.85
SN74111N	.54	SN74296N	1.98
SN74116N	1.75	SN74325N	1.92
SN74120N	1.40	SN74365N	.65
		SN74366N	.65
		SN74367N	.65
		SN74368N	.65
		SN74390N	1.40
		SN74393N	1.40
		SN74490N	1.90

ZENER DIODES

IN4728-IN4752A	19
(1 watt molded)	
IN746A-IN759A	15
(400 MW)	

TTL LOW POWER SCHOTTKY

SN74LS00N	.25	SN74LS138N	1.49
SN74LS01N	.25	SN74LS139N	1.49
SN74LS02N	.25	SN74LS145N	1.25
SN74LS03N	.25	SN74LS151N	1.25
SN74LS04N	.30	SN74LS153N	1.25
SN74LS05N	.30	SN74LS155N	1.45
SN74LS06N	.25	SN74LS156N	1.45
SN74LS09N	.25	SN74LS157N	1.25
SN74LS10N	.25	SN74LS158N	1.20
SN74LS11N	.25	SN74LS160N	1.95
SN74LS12N	.25	SN74LS161N	1.95
SN74LS13N	.69	SN74LS162N	1.95
SN74LS14N	.35	SN74LS163N	1.95
SN74LS15N	.25	SN74LS164N	1.98
SN74LS20N	.25	SN74LS168N	2.25
SN74LS21N	.25	SN74LS169N	2.25
SN74LS22N	.25	SN74LS170N	2.80
SN74LS26N	.40	SN74LS174N	1.40
SN74LS27N	.30	SN74LS175N	1.40
SN74LS28N	.30	SN74LS181N	3.50
SN74LS30N	.25	SN74LS190N	1.95
SN74LS32N	.37	SN74LS191N	1.95
SN74LS33N	.39	SN74LS192N	1.95
SN74LS37N	.39	SN74LS193N	1.95
SN74LS38N	.39	SN74LS194A	1.40
SN74LS40N	.30	SN74LS195A	1.40
SN74LS42N	1.10	SN74LS196N	1.45
SN74LS48N	1.10	SN74LS197N	1.45
SN74LS47N	1.10	SN74LS221N	1.35
SN74LS48N	1.10	SN74LS240N	2.50
SN74LS49N	1.10	SN74LS241N	2.50
SN74LS51N	.25	SN74LS242N	2.40
SN74LS54N	.25	SN74LS243N	2.40
SN74LS55N	.25	SN74LS244N	2.50
SN74LS56N	.75	SN74LS247N	1.30
SN74LS73N	.49	SN74LS248N	1.30
SN74LS74N	.49	SN74LS249N	1.30
SN74LS75N	.69	SN74LS251N	1.55
SN74LS76N	.49	SN74LS253N	1.55
SN74LS78N	.49	SN74LS257N	1.60
SN74LS83AN	1.49	SN74LS258N	1.50
SN74LS85N	1.75	SN74LS261N	2.95
SN74LS86N	.58	SN74LS266N	.59
SN74LS90N	.99	SN74LS279N	.75
SN74LS91N	1.15	SN74LS283N	1.40
SN74LS92N	1.15	SN74LS290N	1.35
SN74LS93BN	.99	SN74LS293N	1.35
SN74LS95AN	1.60	SN74LS295AN	1.75
SN74LS96N	.75	SN74LS298AN	1.75
SN74LS107N	.49	SN74LS324AN	2.25
SN74LS109N	.55	SN74LS352AN	1.45
SN74LS112N	.49	SN74LS353AN	1.40
SN74LS113N	.49	SN74LS365AN	.75
SN74LS114N	.49	SN74LS366AN	.75
SN74LS122N	.89	SN74LS367AN	.75
SN74LS123N	1.09	SN74LS368AN	.75
SN74LS124N	1.95	SN74LS375AN	.80
SN74LS125N	.75	SN74LS386AN	.59
SN74LS126N	.75	SN74LS395AN	1.95
SN74LS132N	1.25	SN74LS670AN	2.95
SN74LS136N	.55		

We offer the largest variety of current production Texas Instruments and Fairchild Semiconductor only 74LS devices from stock. Even through the competition for current production major manufactured 74LS devices is limited, we are dedicated to provide the best prices possible. As our costs decrease, we pass the savings on to you, our customer.

TEXAS INSTRUMENTS DATA BOOKS

STK NO.	DESCRIPTION	PRICE
LCB1011	Understanding Solid State Electronics	2.95
LCB1041	Linear & Interface Applications	6.95
LCC4041	Power Data Book	3.95
LCC4111	TTL Data Book	3.95
LCC4131	Transistor & Diode Data Book	4.95
MCC4151	Linear & Interface I.C. Data Book	3.95
LCC4161	TTL Supplement Data Book	1.95
LCC4191	Optoelectronics Data Book	2.95
LCC4200	Semiconductor Memories Data Book	2.95

FAIRCHILD DATA BOOKS

Linear Integrated Circuits Data Book	2.95
Low Power Schottky & Macrologic TTL	1.75
MOS/CMOS/N-MOS/P-MOS & charge coupled Devices Interface Data Book	2.50
Full Line Condensed Catalogue	1.00
GENERAL INSTRUMENT DATA BOOK	1.95
Microelectronic & MOS Data Book	2.95

STANDARD MICROSYSTEMS

COM2502	8 Bit Uart	7.95
COM2601	Universal Synchronous Receiver Transmitter	23.50
COM2017	8 Bit Uart	8.50

CMOS

CD4000BE	.10
CD4001BE	.19
CD4002BE	14
CD4006BE	1.19
CD4007BE	.18
CD4008BE	.85
CD4009BE	.39
CD4010BE	.39
CD4011BE	.19
CD4012BE	.18
CD4013BE	.39
CD4014BE	.95
CD4015BE	.95
CD4016BE	.39
CD4017BE	.99
CD4018BE	1.09
CD4019BE	.44
CD4020BE	1.09
CD4021BE	1.15
CD4022BE	.95
CD4023BE	.19
CD4024BE	.69
CD4025BE	.18
CD4026BE	1.45
CD4027BE	.44
CD4028BE	.79
CD4029BE	.89
CD4030BE	.39
CD4033BE	1.70
CD4034BE	2.95
CD4035BE	1.05
CD4040BE	1.05
CD4041BE	.69
CD4042BE	.65
CD4043BE	.50
CD4044BE	.50
CD4049BE	.39
CD4050BE	.39
CD4051BE	1.20
CD4052BE	1.20
CD4053BE	1.25
CD4055BE	1.35
CD4056BE	1.50
CD4060BE	1.50
CD4066BE	.65
CD4068BE	.25
CD4069BE	.25
CD4070BE	.25
CD4071BE	.25
CD4072BE	.30
CD4073BE	.30
CD4078BE	1.10
CD4078BE	.25
CD4081BE	.25
CD4082BE	.30
CD4085BE	.75
CD4086BE	.75
CD4502BE	1.20
CD4507BE	.54
CD4510BE	1.50
CD4512BE	1.20
CD4516BE	1.19
CD4519BE	.95
CD4519BE	.89
CD4520BE	.89
CD4528BE	1.25
CD4531BE	1.25
CD4539BE	1.20
CD4555BE	.75
CD4556BE	.75
CD4558BE	1.80
74C85/40085PC	1.20
74C160/40160PC	1.65
74C161/40161PC	1.65
74C162/40162PC	1.65
74C174/40174PC	1.50
74C175/40175PC	1.50
74C192/40192PC	1.65
74C193/40193PC	1.65
74C194/40194PC	1.50
74C195/40195PC	1.50

LED's

IL1	1.05
IL5	1.15
IL12	.69
IL74	.82
AL2	.23
Texas Instruments	
TIL111	.99
TIL112	.95
TIL113	1.25
TIL114	1.15
TIL116	1.20
TIL117	1.30
TIL118	.80
TIL119	.85
TIL138	2.25
TIL139	2.25
TIL209A	.18
TIL211	.39
TIL220	.20
TIL221	.19
TIL222	.35
TIL23	1.98
TIL24	3.95
TIL302	3.98
TIL303	3.98
TIL304	3.98
TIL305	4.95
TIL306	7.95
TIL307	7.95
TIL308	7.95
TIL309	7.95
TIL311	8.95
TIL312	1.60
TIL313	1.60
TIL31	1.50
TIL32	.85
TIL63	.95
TIL66	.75
TIL78	.60
LS601	1.20
LS600	2.10
Fairchild	
FCDB02	.60
FCDB06	.75
FCD810	60
FCD820A	75
FLV117	18
MV5054-1	18
FND357	1.75
FND500	1.75
FND507	1.75
FND807	3.00
FNS700	.60

Plastic Power Transistors

TIP29A	.45	TIP116	.80
TIP30C	.59	TIP117	.90
TIP31A	.52	TIP121	1.25
TIP32A	.55	TIP122	1.50
TIP33C	.90	TIP125	1.35
TIP41A	.65	TIP127	1.60
TIP42A	.75	TIP295S	.89
TIP47	.88	TIP305S	.85
TIP112	.80		

LINEARS

LM301AH	.34
LM301AN-8 (mini dip)	.34
LM304H	.75
LM305H	.78
LM305AH	.90
LM307H	.28
LM307N-8 (mini dip)	.28
LM308H	.84
LM309H	.75
LM309K	1.15
LM311H	.89
LM311N-8 (mini dip)	.99
LM318H	1.50
LM318N-8 (mini dip)	4.95
LM323K	6.95
LM324N	1.10
LM339N	1.20
LM555N-8 (mini dip)	1.20
LM556N-14	.89
LM709CN-14	24
LM711CN-14	.29
LM711CH	.50
LM723CH	.49
LM723CN-14	.49
LM733CN-14	.99
LM739CN-14	1.20
LM740CH	3.50
LM741CH	
LM741CN	
LM741CN-8 (mini dip)	.28
LM741CH-14	.25
LM747CN-14	.64
LM748CN-8 (mini dip)	.29
LM748CH	.45
LM776CH	1.50
LM776CN-8 (mini dip)	1.50
LM1437N-14	.49
LM1458H	.54
LM1458N-8 (mini dip)	.69
LM1488D	1.75
LM1489D	1.75
LM3046N-14	.

U.S. GOV'T ELECTRONIC SURPLUS

* Nationally Known - World Famous SURPLUS CENTER offers finest, most expensive, Government Surplus electronic units and components at a fraction of their original acquisition cost.



300-AMP., 200-VOLT RECTIFIER

* (ITEM #22-1048) - FOUR STAR SPECIAL WEST-INGHOUSE, heavy duty unit. Excellent for use in 12 or 24-volt fast chargers, high current power supply systems, etc. 3-5/8" x 1-3/8" x 1" (1 lb.)

\$6.95 List Over \$20.00

SNAP-AROUND VOLT-AMMETER

* (ITEM #21-1028) - "MINIPROBE" clamp type AC ammeter-voltmeter. Small enough to carry in shirt pocket. Will measure 0 to 50-amperes, 0 to 250-volts. Furnished with test leads. Overall size 4-1/2" x 2-3/4" x 1" (1 lb.)



\$22.95

STANDARD DIAL TELEPHONE

* (ITEM #715) - Same as used on commercial systems in U.S.A. Use as extension to private system. Connect several together for local intercom system. Instructions furnished.

\$8.79

Original Cost \$24.50 (9 lbs.)

RUNNING TIME METER

* (ITEM #2180) - Record number of operating hours of electric lights, electrical devices such as refrigerators, furnaces, etc. Records total hours, tenths and hundredths to 9,999.99 hours. For 115-volts, 60-cycles. 4 1/4" x 3" x 2 1/2" (2 lbs.)



Cost \$29.00

\$4.39

SPECIAL SALE Correspondence Course In ELECTRICAL ENGINEERING

Prepaid in U.S.A. **\$11.79**
Outside U.S.A. **\$12.79**

* (ITEM #9-101) - Technical training at low cost! Lincoln Engineering School suspended Correspondence Course because of rising costs. Limited number of Electrical Engineering Courses are available without exams and grading services. Consists of fifteen lesson books, each with associated exams and standard answers. Book showing how to build prize-winning Home Experimental Laboratory Bench included at no extra cost.

ALL ITEMS SHIPPED F.O.B. LINCOLN, NEBR.
Order Direct From Ad - Send for FREE Catalog

SURPLUS CENTER

DEPT. RE- LINCOLN, NEBR. 68501

CIRCLE 19 ON FREE INFORMATION CARD

CLOCKS

6 digit AUTOMOTIVE CLOCK KIT complete with a CRYSTAL TIMEBASE accurate to .01 percent. 12 volts d.c. operation - built in noise suppression and voltage spike protection. Readouts blank when ignition is off - draws 25 mA in standby mode. Has .3 in. readouts. Use it in your car or for all applications where a battery-operated clock is needed. Approximate size 3" x 3.5" x 1.75"

WITH BLACK PLASTIC CASE \$34.95 ppd.
WITHOUT CASE \$29.95 ppd.
ASSEMBLED AND TESTED \$45.95 ppd.

MM 5320 TV CAMERA SYNC GENERATOR - this LSI chip supplies the basic sync functions for either color or monochrome 525 line/60 Hz. camera and video applications. The price is \$4.95 ppd. and includes the data sheet.

CMOS CRYSTAL TIMEBASE KITS with .01 percent accuracy. 5-15 v.d.c. operation. Draws only 3 mA at 12 volts. Single I.C. - very small size - the P.C. board is 7/8" x 1-5/8". Choose a main output of 50 or 100 Hz., 60 Hz., 500 or 1000 Hz., or 1 Hz. Several related frequencies are also available on each board, in addition to the main ones listed above. Be sure to specify the Frequency you want. All kits are \$10.95 ppd.

Flyer available - write for it or circle the reader service card.

NEXUS TRADING CO.
Box 3357
San Leandro, Ca 94578

CIRCLE 13 ON FREE INFORMATION CARD

BLINK 'N' BOOPER

IS HERE!!!

The Memory Concentration Timing Game.

Send \$1.00 (refundable with order) for illustrative information packet - includes technical description circuit functions, component line up, and game dynamics.

visulex P.O. Box 4204R Mountain View, CA 94040

Low cost digital analog test equipment. Exceptional values. Free catalog. SALEN ELECTRONICS, P.O. Box 82, Skokie, IL 60076

SEMICONDUCTOR and parts literature, J. & J. ELECTRONICS, Box 1437R, Winnipeg, Manitoba, Canada. U.S. Inquiries Invited.

SURPRISE! Build Inexpensively, the most unusual test instruments, futuristic gadgets using numerical readouts! Catalogue free! GBS, Box 100B, Greenbank, WV 24944



Quality Electronic Components

Accelerated Discount Schedule
Saves You Even More!

2102-1 \$1.99	8080A \$24.95	LM3909 69¢
INTEGRATED CIRCUITS - TTL, CMOS, LINEAR & MOS		
7400 .21 7473 .30 74174 .98 4001 .23 4073 .72	7474 .30 74175 .93 4002 .23 4075 .72	4076 .72 4077 .72 4078 .72 4079 .72
7401 .21 7474 .30 74176 .79 4006 1.23 4081 .72	7475 .32 74177 .79 4007 .23 4082 .72	4083 .72 4084 .72 4085 .72 4086 .72
7402 .21 7475 .32 74178 .79 4008 .29 4502 .79	7476 .32 74179 .79 4009 .29 4503 .79	4504 .79 4505 .79 4506 .79 4507 .79
7403 .21 7476 .32 74180 .79 4010 .29 4508 .79	7477 .32 74181 .215 4009 .44 4510 .114	4511 .105 4512 .105 4513 .105 4514 .105
7404 .21 7477 .32 74182 .79 4011 .23 4515 1.28	7478 .32 74183 .215 4012 .23 4516 1.28	4517 1.28 4518 1.28 4519 1.28 4520 1.28
7405 .21 7478 .32 74184 .219 4013 .40 4521 1.80	7479 .32 74185 .219 4014 .40 4522 1.80	4523 1.80 4524 1.80 4525 1.80 4526 1.80
7406 .25 7483 .70 74186 .350 4013 .40 4527 1.80	7480 .25 74187 .350 4014 .40 4528 1.80	4529 1.80 4530 1.80 4531 1.80 4532 1.80
7407 .25 7485 .89 74188 .350 4015 .40 4533 1.80	7481 .25 74189 .350 4016 .40 4534 1.80	4535 1.80 4536 1.80 4537 1.80 4538 1.80
7408 .21 7486 .28 74189 .350 4017 .40 4539 1.80	7482 .21 74190 .123 4018 .40 4540 1.80	4541 1.80 4542 1.80 4543 1.80 4544 1.80
7409 .21 7489 .219 74191 .123 4019 .40 4545 1.80	7483 .21 74192 .88 4018 1.05 4546 1.80	4547 1.80 4548 1.80 4549 1.80 4550 1.80
7410 .21 7490 .44 74193 .88 4019 1.05 4551 1.80	7484 .21 74194 .88 4018 1.05 4552 1.80	4553 1.80 4554 1.80 4555 1.80 4556 1.80
7411 .21 7492 .44 74195 .88 4020 1.14 4557 1.80	7485 .21 74196 .88 4021 1.14 4558 1.80	4559 1.80 4560 1.80 4561 1.80 4562 1.80
7412 .21 7494 .44 74197 .88 4022 .96 4563 1.80	7486 .21 74198 .88 4023 .96 4564 1.80	4565 1.80 4566 1.80 4567 1.80 4568 1.80
7413 .25 7493 .44 74199 .88 4024 .84 4569 1.80	7487 .21 74199 .88 4025 .28 4570 1.80	4571 1.80 4572 1.80 4573 1.80 4574 1.80
7414 .89 7494 .44 74200 .58 4026 .28 4575 1.80	7488 .21 74201 .58 4027 .40 4576 1.80	4577 1.80 4578 1.80 4579 1.80 4580 1.80
7415 .25 7495 .70 74202 .58 4028 .89 4581 1.80	7489 .21 74203 .58 4029 .89 4582 1.80	4583 1.80 4584 1.80 4585 1.80 4586 1.80
7416 .25 7496 .70 74204 .58 4030 1.14 4587 1.80	7490 .21 74205 .58 4031 1.51 4588 1.80	4589 1.80 4590 1.80 4591 1.80 4592 1.80
7417 .25 7497 .70 74206 .40 74366 .67 4028 .89 4589 1.80	7491 .21 74206 .40 74367 .67 4029 1.14 4590 1.80	4591 1.80 4592 1.80 4593 1.80 4594 1.80
7418 .21 74100 1.26 74207 .30 74197 .98 4029 1.14 4595 1.80	7492 .21 74207 .30 74198 .98 4030 1.51 4596 1.80	4597 1.80 4598 1.80 4599 1.80 4600 1.80
7419 .21 74101 1.26 74208 .30 74199 .98 4031 1.51 4597 1.80	7493 .21 74208 .30 74200 .58 4032 1.51 4598 1.80	4601 1.80 4602 1.80 4603 1.80 4604 1.80
7420 .21 74102 1.26 74209 .30 74201 .58 4033 1.51 4599 1.80	7494 .21 74209 .30 74202 .58 4034 3.50 4605 1.80	4606 1.80 4607 1.80 4608 1.80 4609 1.80
7421 .25 74103 1.30 74210 .30 74203 .58 4035 1.26 4610 1.80	7495 .21 74210 .30 74204 .58 4036 1.26 4611 1.80	4612 1.80 4613 1.80 4614 1.80 4615 1.80
7422 .35 74109 .99 74211 .35 74205 .58 4037 1.26 4612 1.80	7496 .21 74211 .35 74206 .58 4038 1.26 4613 1.80	4614 1.80 4615 1.80 4616 1.80 4617 1.80
7423 .35 74109 .99 74212 .35 74207 .58 4039 1.26 4614 1.80	7497 .21 74212 .35 74208 .58 4040 1.26 4615 1.80	4616 1.80 4617 1.80 4618 1.80 4619 1.80
7424 .35 74109 .99 74213 .35 74209 .58 4041 1.26 4616 1.80	7498 .21 74213 .35 74209 .58 4042 1.26 4617 1.80	4618 1.80 4619 1.80 4620 1.80 4621 1.80
7425 .35 74109 .99 74214 .35 74210 .58 4043 1.26 4618 1.80	7499 .21 74214 .35 74210 .58 4044 1.26 4619 1.80	4620 1.80 4621 1.80 4622 1.80 4623 1.80
7426 .35 74109 .99 74215 .35 74211 .58 4045 1.26 4620 1.80	7500 .21 74215 .35 74211 .58 4046 1.26 4621 1.80	4622 1.80 4623 1.80 4624 1.80 4625 1.80
7427 .35 74109 .99 74216 .35 74212 .58 4047 1.26 4622 1.80	7501 .21 74216 .35 74212 .58 4048 1.26 4623 1.80	4624 1.80 4625 1.80 4626 1.80 4627 1.80
7428 .35 74109 .99 74217 .35 74213 .58 4049 1.26 4624 1.80	7502 .21 74217 .35 74213 .58 4050 1.26 4625 1.80	4626 1.80 4627 1.80 4628 1.80 4629 1.80
7429 .35 74109 .99 74218 .35 74214 .58 4050 1.26 4626 1.80	7503 .21 74218 .35 74214 .58 4051 1.26 4627 1.80	4628 1.80 4629 1.80 4630 1.80 4631 1.80
7430 .35 74109 .99 74219 .35 74215 .58 4051 1.26 4628 1.80	7504 .21 74219 .35 74215 .58 4052 1.26 4629 1.80	4630 1.80 4631 1.80 4632 1.80 4633 1.80
7431 .35 74109 .99 74220 .35 74216 .58 4052 1.26 4629 1.80	7505 .21 74220 .35 74216 .58 4053 1.26 4630 1.80	4632 1.80 4633 1.80 4634 1.80 4635 1.80
7432 .35 74109 .99 74221 .35 74217 .58 4053 1.26 4631 1.80	7506 .21 74221 .35 74217 .58 4054 1.26 4632 1.80	4634 1.80 4635 1.80 4636 1.80 4637 1.80
7433 .35 74109 .99 74222 .35 74218 .58 4054 1.26 4632 1.80	7507 .21 74222 .35 74218 .58 4055 1.26 4633 1.80	4636 1.80 4637 1.80 4638 1.80 4639 1.80
7434 .35 74109 .99 74223 .35 74219 .58 4055 1.26 4633 1.80	7508 .21 74223 .35 74219 .58 4056 1.26 4634 1.80	4638 1.80 4639 1.80 4640 1.80 4641 1.80
7435 .35 74109 .99 74224 .35 74220 .58 4056 1.26 4634 1.80	7509 .21 74224 .35 74220 .58 4057 1.26 4635 1.80	4640 1.80 4641 1.80 4642 1.80 4643 1.80
7436 .35 74109 .99 74225 .35 74221 .58 4057 1.26 4635 1.80	7510 .21 74225 .35 74221 .58 4058 1.26 4636 1.80	4642 1.80 4643 1.80 4644 1.80 4645 1.80
7437 .35 74109 .99 74226 .35 74222 .58 4058 1.26 4636 1.80	7511 .21 74226 .35 74222 .58 4059 1.26 4637 1.80	4644 1.80 4645 1.80 4646 1.80 4647 1.80
7438 .35 74109 .99 74227 .35 74223 .58 4059 1.26 4637 1.80	7512 .21 74227 .35 74223 .58 4060 1.26 4638 1.80	4646 1.80 4647 1.80 4648 1.80 4649 1.80
7439 .35 74109 .99 74228 .35 74224 .58 4060 1.26 4638 1.80	7513 .21 74228 .35 74224 .58 4061 1.26 4639 1.80	4648 1.80 4649 1.80 4650 1.80 4651 1.80
7440 .35 74109 .99 74229 .35 74225 .58 4061 1.26 4639 1.80	7514 .21 74229 .35 74225 .58 4062 1.26 4640 1.80	4650 1.80 4651 1.80 4652 1.80 4653 1.80
7441 .35 74109 .99 74230 .35 74226 .58 4062 1.26 4640 1.80	7515 .21 74230 .35 74226 .58 4063 1.26 4641 1.80	4652 1.80 4653 1.80 4654 1.80 4655 1.80
7442 .35 74109 .99 74231 .35 74227 .58 4063 1.26 4641 1.80	7516 .21 74231 .35 74227 .58 4064 1.26 4642 1.80	4654 1.80 4655 1.80 4656 1.80 4657 1.80
7443 .35 74109 .99 74232 .35 74228 .58 4064 1.26 4642 1.80	7517 .21 74232 .35 74228 .58 4065 1.26 4643 1.80	4656 1.80 4657 1.80 4658 1.80 4659 1.80
7444 .35 74109 .99 74233 .35 74229 .58 4065 1.26 4643 1.80	7518 .21 74233 .35 74229 .58 4066 1.26 4644 1.80	4658 1.80 4659 1.80 4660 1.80 4661 1.80
7445 .35 74109 .99 74234 .35 74230 .58 4066 1.26 4644 1.80	7519 .21 74234 .35 74230 .58 4067 1.26 4645 1.80	4660 1.80 4661 1.80 4662 1.80 4663 1.80
7446 .35 74109 .99 74235 .35 74231 .58 4067 1.26 4645 1.80	7520 .21 74235 .35 74231 .58 4068 1.26 4646 1.80	4662 1.80 4663 1.80 4664 1.80 4665 1.80
7447 .35 74109 .99 74236 .35 74232 .58 4068 1.26 4646 1.80	7521 .21 74236 .35 74232 .58 4069 1.26 4647 1.80	4664 1.80 4665 1.80 4666 1.80 4667 1.80
7448 .35 74109 .99 74237 .35 74233 .58 4069 1.26 4647 1.80	7522 .21 74237 .35 74233 .58 4070 1.26 4648 1.80	4666 1.80 4667 1.80 4668 1.80 4669 1.80
7449 .35 74109 .99 74238 .35 74234 .58 4070 1.26 4648 1.80	7523 .21 74238 .35 74234 .58 4071 1.26 4649 1.80	4668 1.80 4669 1.80 4670 1.80 4671 1.80
7450 .35 74109 .99 74239 .35 74235 .58 4071 1.26 4649 1.80	7524 .21 74239 .35 74235 .58 4072 1.26 4650 1.80	4670 1.80 4671 1.80 4672 1.80 4673 1.80
7451 .35 74109 .99 74240 .35 74236 .58 4072 1.26 4650 1.80	7525 .21 74240 .35 74236 .58 4073 1.26 4651 1.80	4672 1.80 4673 1.80 4674 1.80 4675 1.80
7452 .35 74109 .99 74241 .35 74237 .58 4073 1.26 4651 1.80	7526 .21 74241 .35 74237 .58 4074 1.26 4652 1.80	4674 1.80 4675 1.80 4676 1.80 4677 1.80
7453 .35 74109 .99 74242 .35 74238 .58 4074 1.26 4652 1.80	7527 .21 74242 .35 74238 .58 4075 1.26 4653 1.80	4676 1.80 4677 1.80 4678 1.80 4679 1.80
7454 .35 74109 .99 74243 .35 74239 .58 4075 1.26 4653 1.80	7528 .21 74243 .35 74239 .58 4076 1.26 4654 1.80	4678 1.80 4679 1.80 4680 1.80 4681 1.80
7455 .35 74109 .99 74244 .35 74240 .58 4076 1.26 4654 1.80	7529 .21 74244 .35 74240 .58 4077 1.26 4655 1.80	4680 1.80 4681 1.80 4682 1.80 4683 1.80
7456 .35 74109 .99 74245 .35 74241 .58 4077 1.26 4655 1.80	7530 .21 74245 .35 74241 .58 4078 1.26 4656 1.80	4682 1.80 4683 1.80 4684 1.80 4685 1.80
7457 .35 74109 .99 74246 .35 74242 .58 4078 1.26 4656 1.80	7531 .21 74246 .35 74242 .58 4079 1.26 4657 1.80	4684 1.80 4685 1.80 4686 1.80 4687 1.80
7458 .35 74109 .99 74247 .35 74243 .58 4079 1.26 4657 1.80	7532 .21 74247 .35 74243 .58 4080 1.26 4658 1.80	4686 1.80 4687 1.80 4688 1.80 4689 1.80
7459 .35 74109 .99 74248 .35 74244 .58 4080 1.26 4658 1.80	7533 .21 74248 .35 74244 .58 4081 1	

SOLID STATE TECHNOLOGY KIT


- FOR THE EXPERIMENTER WITH TASTE FOR "STATE OF THE ART" PRODUCTS
- COMPLETE SPECIFICATIONS ARE PRINTED ON THE BACK OF EACH TECHNOLOGY KIT

FTK0020



CARD FRONT

FTK0020

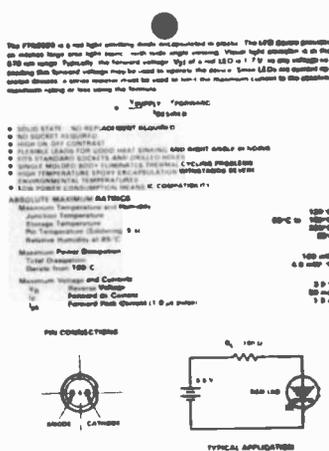

CARD BACK

FTK0106



CARD FRONT

DIGITS

FTK0001	0.5" High Common Cathode Digit	\$1.00
FTK0002	0.5" High Common Anode Digit	1.00
FTK0003	.357" High Common Cathode Digit	.75
FTK0004	0.8" High Common Cathode Digit	2.00
FTK0005	0.8" High Common Anode Digit	2.00

0.8" HIGH DISPLAY ARRAYS

FTK0010	12 Hour, 3½ Digit Clock Display	7.00
FTK0011	24 Hour, 4 Digit Clock Display	8.00

LED LAMPS

FTK0020	10 Red LED Lamps	1.00
FTK0021	5 Mixed Colored LED Lamps	1.00
FTK0022	10 LED Mounting Clips	1.00
FTK0023	5 Three Piece LED Mounting Adapters	1.00

PHOTO TRANSISTORS

FTK0030	5 Flat Lens Photo Transistors	1.00
FTK0031	5 Round Lens Photo Transistors	1.00
FTK0032	3 Flat Lens Photo Darlington	1.00
FTK0033	3 Round Lens Photo Darlington	1.00

PHOTO ARRAYS

FTK0040	9-Element Tape Reader Array	16.00
FTK0041	12-Element Card Reader Array	24.00
FTK0042	Reflective Opto Coupler	4.00

COUPLERS

FTK0050	3 General Purpose Opto Couplers	1.00
FTK0051	Darlington Opto Coupler	1.00

MOS CLOCK CIRCUITS

FTK0400	Digital Clock/Calendar Circuit (FCM7001)	7.00
FTK0401	Digital Clock/Calendar with BCD Outputs (FCM7002)	7.00
FTK0402	Direct Drive Digital Clock Circuit with AC Output (FCM3817A)	5.00
FTK0403	Direct Drive Digital Clock Circuit with DC Output (FCM3817D)	5.00
FTK0405	Direct Drive Digital Clock/Calendar Circuit (FCM7015)	6.00

KITS

FTK0106	Automobile Clock Kit	40.00
---------	----------------------	-------

• THESE PRODUCTS ARE PACKAGED FOR OUT-STANDING WALL DISPLAY APPEARANCE

• FULL **FAIRCHILD** PRODUCT LINE TO FOLLOW

• DEALER'S AND WHOLESALER'S INQUIRIES INVITED - PRICE LIST AVAILABLE.

• BUY WITH PRIDE THE PRODUCTS BUILT BY THE INDUSTRY'S LEADER - **FAIRCHILD**

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds. California Residents - Add 6% Sales Tax. Send a 24c Stamp (postage) for a FREE 1977 Catalog.

JAMES
NOW OPEN SATURDAYS

1021 HOWARD STREET
SAN CARLOS, CA 94070
PHONE ORDERS - (415) 592-8097

Olson[®] Parts and electronics Accessories

SPECIALIZING IN ELECTRONICS FOR 35 YEARS



Under-Dash LOCK MOUNT

AU-344



229
Reg. \$6

Locks player in place. Slides in & out. 6 x 13/16 x 7". 6 or 12 VDC. Shipping weight 2 lbs.

Standard Dial DESK PHONE

PH-117



799
Reg. \$13

Factory reconditioned. Comes with base, dial & coil. Less bell. Styles may vary. Wt. 8 lbs.

Auto Stereo 8-Track Tape Player

AU-428



1999
Reg. \$24

Player mounts easily under dash. Slide controls. 7 1/2 x 5 1/2 x 2 1/2". 12 VDC. neg. grd. Styles may vary. 4 lbs.

Police Converter Kit

KB-380

Model EC-2900. Use AM radio & tune in the 152-174 MHz band for police, etc. 2 lbs.

799
Reg. \$13



Pencil-Tip Soldering Iron

TL-448

Tip reaches temperature to 250°. Is 9/4" long. 117 VAC. 1/4 lb. Reg. \$3.29

PARTS & COMPONENTS

	REG.	SALE
8 Track Tape Deck Chassis	RM-383	17.00 11.99
4 Digit Mechanical Counter	XM-367	1.49 59
5 Digit Mechanical Counter	XM-543	3.00 1.29
2 watt Solid-State Phono Amp	AM-529	16.00 11.00
5 Digit 117 volt AC Counter	XM-533	2.00 99
12 Hour Timer, 117 V. AC	SW-777	4.00 1.79
6 Digit 117 V. AC Counter	XM-481	2.25 1.39
L.E.D. Pkg. of 5 Small Red 2V, 5 MA	PL-234	1.19 60
L.E.D. Pkg. of 5 Large Green 2 V, 5 MA	PL-235	1.19 60
L.E.D. Pkg. of 5 Small Green 2 V, 5 MA	PL-236	1.19 60
L.E.D. Pkg. of 5 Large Yellow 2V, 5 MA	PL-237	1.19 60
L.E.D. Pkg. of 5 Small Yellow 2 V, 5 MA	PL-238	1.19 60
L.E.D. Pkg. of 5 Large Orange 2 V, 5 MA	PL-249	1.19 60
L.E.D. Pkg. of 5 Large Clear 2 V, 5 MA	PL-274	1.19 60
7 Seg. L.E.D. Readout, 3" Com. K Reel	XM-414	2.00 1.29
LM-309K 5 V. IC Regulator 10-3	TR-511	1.60 1.19
3 Amp. 50 PIV Diodes Pkg. of 2	DI-055	70 59
3 Amp. 400 PIV Diodes Pkg. of 2	DI-056	1.20 79
1 Amp. 200 PIV 50 Piece Kit	DI-051	1.69 69
P Channel FET 2N5460	TR-430	1.19 59
18 Amp. 200 PIV Diode IN3493R	DI-054	1.49 59
Medium Power Transistor 25B474	TR-147	3.79 1.29
Cadmium Photo Cells, 500 Ohm. Pkg. 2	TR-512	90 59
N Channel FET 2N3819	TR-429	1.00 49
40 Watt NPN Transistor, Pkg. of 4	TR-440	1.29 59
709 IC Hi-Gain OP-Amp	RE-131	4.49 69
PC Board Kit - Make Your Own	XM-393	6.59 3.99
PC Wire Kit, 150 Ft.	WW-575	1.89 99
Magnet Wire, 28 Ga. 375 Ft.	WR-281	89 69
4POT Plug-In Relay, 117 V. AC Coil	SW-543	2.69 1.79
16 Step Relay, 110 Ohm Coil, 450 Ohm Reset	SW-842	5.79 3.79
SPDT 5A. Plug-In Relay 117 V. AC	SW-417	1.19 79
DPST Power Relay 25A. Cont. 117 V. Coil	SW-646	2.69 1.69
Heavy Duty Solenoid, 117 V. AC	SW-839	1.79 79
Miniature Solenoid, 1/2" Trav. 117 V. AC	SW-840	2.00 89
Reed Switch with Mag. Pkg. 10	SW-632	2.69 79
SPDT Key Switch 3A. Contacts	SW-808	1.20 79

Poly Pak's EXCLUSIVE BARREL KITS

Avg. Ship. Wt. 6 lbs.

100'S OF BARRELS PURCHASED!

For the first time anywhere, Poly Pak merchandisers introduce a new way in buying the economical way. Raw stock from the "barrel". Remember the "good ole days"? They're back again. The same way merchandisers throughout the United States buy from various factories... their overflow in barrels Poly Pak has done the same. Therefore you are getting the same type of material as the RE-TESTERS DO!

TEST 'EM YOURSELF 'N SAVE!

Buy 10 BARREL KITS the 11th Free

\$1.98

YOUR CHOICE OF ANY KIT

KIT	PRICE	KIT	PRICE
21-5N7400 DIP IC'S	75 for \$1.98	288-LITRONICS LED READOUT	10 for \$1.98
Cat.No.11R2415,untested	\$1.98	Cat.No.11R2861,all misc	\$1.98
22-LINEAR OP AMPS	75 for \$1.98	291-SILVER MICAS	100 for \$1.98
Cat.No.11R2416,untested	\$1.98	Cat.No.11R3018,variety	\$1.98
23-1N4148/914 DIODES	100 for \$1.98	292-3 AMP EPOXY RECT	100 for \$1.98
Cat.No.11R2418,untested	\$1.98	Cat.No.11R3204,untested	\$1.98
24-"4000" RECTIFIERS	100 for \$1.98	293-HALF WATTERS	200 for \$1.98
Cat.No.11R2417,untested	\$1.98	Cat.No.11R3046,100% good	\$1.98
27-VOLUME CONTROLS	40 for \$1.98	299-PHOTO ELECTRIC CELLS	10 for \$1.98
Cat.No.11R2421,100% good	\$1.98	Cat.No.11R3052,100% good	\$1.98
28-SUBMINI IF XFMR'S	100 for \$1.98	304-SLIDE VOL CONTROLS	10 for \$1.98
Cat.No.11R2422,100% good	\$1.98	Cat.No.11R3136,wide asst	\$1.98
31-POWER TAB TRANS	40 for \$1.98	310-TERMIAL STRIPS	150 for \$1.98
Cat.No.11R2425,untested,non	\$1.98	Cat.No.11R3137,untested	\$1.98
32-POWER TAB TRANS	40 for \$1.98	311-MICRO MINI LEDS	40 for \$1.98
Cat.No.11R2426,untested,non	\$1.98	Cat.No.11R3139,variety	\$1.98
34-PRECISION RESISTORS	200 for \$1.98	315-MOLEX SOCKETS	200 for \$1.98
Cat.No.11R2428,marked-no mark	\$1.98	Cat.No.11R3144,100% good	\$1.98
35-MOS FET TRANSISTORS	60 for \$1.98	319-PRECISION RESISTORS	100 for \$1.98
Cat.No.11R2429	\$1.98	Cat.No.11R3205,100% good	\$1.98
38-DIPPED MYLARS	60 for \$1.98	321-MINI MAGNETS	100 for \$1.98
Cat.No.11R2597,100% good	\$1.98	Cat.No.11R3168	\$1.98
39-LONG LEAD DISCS	150 for \$1.98	326-UPRIGHT ELECTROS	100 for \$1.98
Cat.No.11R2598,100% good	\$1.98	Cat.No.11R3226,100% good	\$1.98
328-PLASTIC TRANSISTORS	100 for \$1.98	327-AXIAL ELECTROS	40 for \$1.98
Cat.No.11R2604,untested	\$1.98	Cat.No.11R3227,asst	\$1.98
330-PRE-FORMED RESISTORS	250 for \$1.98	328-MINI DIP IC'S	75 for \$1.98
Cat.No.11R2608,100% good	\$1.98	Cat.No.11R3245,untested	\$1.98
332-TRANS WITH HOLE	50 for \$1.98	330-CRYSTALS	12 for \$1.98
Cat.No.11R2610,untested	\$1.98	Cat.No.11R3250,many in Bmc	\$1.98
335-NEON LAMPS	30 for \$1.98	331-TANTALUM ELECTROS	30 for \$1.98
Cat.No.11R2613,100% good	\$1.98	Cat.No.11R3255,mixed	\$1.98
337-1 AMP BULLET REC	100 for \$1.98	333-C-MOS IC'S	60 for \$1.98
Cat.No.11R2617,100% good	\$1.98	Cat.No.11R3289,by Oak	\$1.98
338-2N3055 TRANSISTORS	15 for \$1.98	340-LAMPS, INDICATORS	20 for \$1.98
Cat.No.11R2618,100% good	\$1.98	Cat.No.11R3297,many types	\$1.98
340-HI-POWER PNP TRANS	20 for \$1.98	341-10 WATT ZENERS	15 for \$1.98
Cat.No.11R2619,100% good	\$1.98	Cat.No.11A3298,good yield	\$1.98
343-JUMBO RESISTOR PAK	100 pc. \$1.98	344-ROA PHONO PLUGS	40 for \$1.98
Cat.No.11R2721,100% good	\$1.98	Cat.No.11R3293,100% good	\$1.98
344-8 DIGIT READOUTS	7 for \$1.98	349-ROCKER SWITCHES	25 for \$1.98
Cat.No.11R2722	\$1.98	Cat.No.11R3300	\$1.98
345-SLIDE SWITCHES	30 for \$1.98	358-MAGNIFIED MAN-38	12 for \$1.98
Cat.No.11R2726,100% good	\$1.98	Cat.No.11R3255,38s rejects	\$1.98
351-POLYSTYRENE CAPS	100 for \$1.98	359-MODULAR SWITCHES	25 for \$1.98
Cat.No.11R2729,100% good	\$1.98	Cat.No.11R3150,Controlab	\$1.98
355-MIXED READOUTS	15 for \$1.98	360-LM309K V. REG	15 for \$1.98
Cat.No.11R2733,untested	\$1.98	Cat.No.11R3330,untested	\$1.98
358-2 WATTERS	100 for \$1.98	361-PLASTIC TRANSISTORS	25 for \$1.98
Cat.No.11R2735,100% good	\$1.98	Cat.No.11R3343,100% material	\$1.98
371-CAPACITOR SPECIAL	100 for \$1.98	363-MINI TRIMPOTS	30 for \$1.98
Cat.No.11R2738,100% good	\$1.98	Cat.No.11R3345,for p.c.	\$1.98
373-TRANSISTOR ELECTROS	50 for \$1.98	372-25 AMP ACRS	3-pcs. \$1.98
Cat.No.11R2747	\$1.98	Cat.No.11R3255,100% material	\$1.98
376-1 WATT ZENERS	100 for \$1.98	373-25 AMP TRIACS	3-pcs. \$1.98
Cat.No.11R2741,untested	\$1.98	Cat.No.11R3356,100% material	\$1.98
383-LM340T VOLT REG	15 for \$1.98	384-1/2 WATT METAL FILM	150 for \$1.98
Cat.No.11R2835,untested	\$1.98	Cat.No.11R3413,100% material	\$1.98
386-HOBBY LEDS	40 for \$1.98		
Cat.No.11R2859,untested	\$1.98		
387-NATIONAL IC BONANZA	100 for \$1.98		
Cat.No.11R2860,untested	\$1.98		

DELTRON TUBULAR SOLENOID

Cat. No. 11R3394

\$1.49

It's new! Different! 1st time we've seen these popular tubular solenoids at this price. Designed for maximum FLD, in minimum space. Features: 2VDC, 1/2" x 1/2" x 1/2" coils, continuous duty, only 3/4" x 1/2" with 1/2" threaded bushing for panel mtg. stroke. plunger, with pointed end for precision smooth recut action. With wire connections. Wt. 2 oz.

- Space Saver 1/2" x 1/2"
- Powerful 17-oz. pull
- Unique panel mtg.
- Weights only 2 oz.
- 12 VDC

AA NICAD BATTERY

\$1.49 3 for \$4.

Return of a sellout. Popular standard AA nicads at good price. 1.2 VDC 1 oz. Cat. No. 11R3214

FILAMENT TRANSFORMER PANIC

The Revolutionary **PowerDIP** SOLID STATE 5V DC RELAYS

• ALL 110 VAC INPUT
• STANDARD MOUNTING

Cat.No.	Output	Amps	Wt.	Rate	3 for
11R2768	6.3V	2	6.0oz.	\$2.95	\$8.00
11R2266	12 V	.5	8.0oz.	1.95	5.00
11R2474	12 V	1	1-lb.	2.95	8.00
11R3448	12 V	2	2-lbs.	3.50	9.00
11R2773	48 VCT	2	2-lbs.	2.95	8.00

• Operates directly from C-MOS (no control sensitivity)

• TTL/DTL Compatible (7 ramp control rate)

• Switches up to 4 amps without heat sinking

• Fits standard 16-pin DIP sockets.

\$650 3 FOR \$18

Terms: Add postage. Rated: net 30
Phone: Wakefield, Mass. (617) 245-3829
Retail: 16-18 Lel Carmine St., Wakefield, MA.
MINIMUM ORDER — \$6.00

POLY PAKS
P.O. BOX 942R LYNNFIELD, MASS. 01940

Send for FREE Fall-Winter CATALOG

RADIO-ELECTRONICS

OLSON ELECTRONICS, 250 S. FORGE ST. DEPT LR. AKRON, OHIO 44327

NAME _____
 ADDRESS _____
 CITY _____ STATE _____ ZIP _____

SEND OLSON CATALOG FREE PA CATALOG

SHIP THE FOLLOWING

HOW MANY	STOCK NUMBER	DESCRIPTION	PRICE EACH	TOTAL

ENCLOSE POSTAGE AND SALES TAX

4K LOW POWER RAM BOARD KIT

THE WHOLE WORKS

Imesai and Altair 8080 plug in compatible. Uses low power static 21L02-1 500 ns. RAM's, which are included. Fully buffered, drastically reduced power consumption, on board regulated, all sockets and parts included. Premium quality plated thru PC Board.

\$89.95

8 Digit LED
"METRIC MASTER"
\$19.95
"RAPID MAN - 12"
\$29.95

\$1,000,000 CALCULATOR PURCHASE!
We bought the entire stock of a major manufacturer. New, guaranteed units.
Five functions PLUS complete Metric Conversion functions. Rechargeable batteries. Small, hand held size. With AC charger.
12 Digit - Desk Top Style. Sturdy design. With memory and four complete functions. Big, bright display.

ALARM CLOCK KIT SIX DIGIT LED
Thousands of hobbyists have bought and built our original clock kit and were completely satisfied. But we have received many requests for an alarm clock kit with the same value and quality that you have come to expect from S. D. So, here it is!
THE KIT INCLUDES:
1 Mostek 50252 Alarm Clock Chip
6 Hewlett Packard .30 in. common cathode readouts
15 NPN Driver Transistors
2 Switches for time set
2 Slide Switches for alarm set and enable
1 Filter Cap
4 IN4002 Rectifiers
1 IN914 Diode
1 .01 Disc Cap
15 Resistors
1 Speaker for alarm
1 LED lamp for PM indicator
\$9.95
PCB - \$3.00
XFMR - \$1.50

60 HZ CRYSTAL TIME BASE - FOR DIGITAL CLOCKS
S. D. SALES EXCLUSIVE! **\$5.95**
KIT FEATURES:
A. 60 hz output with accuracy comparable to a digital watch
B. Directly interfaces with all MOS Clock chips
C. Super low power consumption (1.5 Ma typ.)
D. Uses latest MOS 17 stage divider IC
E. Eliminates forever the problem of AC line glitches
F. Perfect for cars, boats, campers, or even for portable clocks at ham field days. **BUY TWO FOR \$10.00!**
G. Small size, can be used in existing enclosures.
KIT INCLUDES CRYSTAL, DIVIDER IC, PC BOARD PLUS ALL OTHER NECESSARY PARTS AND SPECS.

MOTOROLA RTL IC'S
Brand new, factory prime. Hard to find, but still used in a variety of projects. (See the RTL Cookbook by Howard W. Sams.)
MC724P - 59c MC780P - 89c MC791P - 69c
MC725P - 59c MC785P - 49c MC792P - 59c
MC764P - 49c MC787P - 89c MC799P - 59c
MC767P - 69c MC788P - 49c MC970P - 89c
MC771P - 49c MC789P - 59c MC9709P - 69c
MC775P - 89c MC790P - 89c MC9760P - 69c

TTL INTEGRATED CIRCUITS

7400 - 19c	7430 - 19c	7476 - 35c	74153 - 75c
7402 - 19c	7432 - 34c	7480 - 49c	74154 - 1.00
74L04 - 29c	7437 - 39c	7483 - 95c	74157 - 75c
74S04 - 44c	7438 - 39c	7485 - 95c	74161 - 95c
7404 - 19c	7440 - 19c	7586 - 45c	74164 - 1.10
7406 - 29c	7447 - 85c	7490 - 65c	74165 - 1.10
7408 - 19c	7448 - 85c	7492 - 75c	74174 - 95c
7410 - 19c	7451 - 19c	7495 - 75c	74181 - 2.50
7411 - 29c	7453 - 19c	7496 - 89c	74191 - 1.25
7413 - 50c	7473 - 39c	74121 - 38c	74192 - 1.25
7420 - 19c	7474 - 35c	74123 - 65c	74193 - 1.00
	7575 - 35c	74141 - 75c	74195 - 69c



"CUBO" - DIGITAL ALARM CLOCK CUBE
A PERFECT GIFT - NOT A KIT!
The CUBO Alarm Clock mfg. by Corvus, division of MOSTEK CORP. Originally sold for \$49.95. We bought out their entire inventory. All new, individually gift boxed. Mini size (2 1/2" cube) with max performance.
FEATURES:
A. 4 Digit H.P. Bright Display
B. "Second Hand" LED Activity Indicator
C. 24 Hour Alarm; 12 hour real time format
D. 10 Minute Snooze
E. Auto Display Dimming - Adjusts to Ambient Light
F. AM/PM Indicator
G. Power Failure Indicator
Uses Famous Mostek MK50250 MOS LSI IC
\$14.95 EACH
(Add 75c P.&H.)



1000 MFD FILTER CAPS
Rated 35 WVDC. Upright style with P.C. leads. Most popular value for hobbyists. Compare at up to \$1.19 each from franchise type electronic parts stores.
S.D. SPECIAL 4 for \$1.

SLIDE SWITCH ASSORTMENT
Our best seller. Includes miniature and standard sizes, single and multi-position units. All new, first quality, name brand. Try one package and you'll re-order more. **SPECIAL - 12/\$1.**



MOTOROLA POWER DARLINGTON
Back in Stock!
Like MJ3001. NPN 80V, 10A. HFE 6000 TYP. TO-3 case. We include a free 723 C volt reg. with schematic for power supply.
SPECIAL - \$1.99

WESTERN DIGITAL UART
No. TR1602B. 40 pin DIP.
This is a very powerful and popular part.
NEW - \$6.95 with data
LIMITED QUANTITY

FAIRCHILD BIG LED READOUTS
A big .50 inch easy to read character. Now available in either common anode or common cathode. Take your pick. Super low current drain, only 5 MA per segment typical.
YOUR CHOICE: 6 for \$7.50
FND - 510 Common Anode \$1.50 ea.
FND - 503 Common Cathode \$1.50 ea.

MICROPROCESSORS & THINGS
By AMD
8080A Better than Intel **\$24.00**
8008-1 High Speed 8008 **12.50**
8212 I/O Port **3.50**
8224 Clock Generator **4.95**
2513 Character Generator **10.00**

RESISTOR ASSORTMENT
1/4 W 5% and 10%. PC leads.
A good mix of values. **200/\$2.**

74S200
256 Bjt High Speed RAM
Same as 82S16
\$3.95

1K PROM BACK IN STOCK!
82S129. 256X4. Bipolar. 50 NS.
FAST. WITH SPECS.
\$3.95

8T97B
Hex Tri-State Buffer. Back in stock.
\$1.25

UP YOUR COMPUTER!
21L02-1 1K LOW POWER 500 NS STATIC RAM
TIME IS OF THE ESSENCE
And so is power. Not only are our RAM's faster than a speeding bullet but they are now very low power. We are pleased to offer prime new 21L02 - 1 low power and super fast RAM's. Allows you to STRETCH your power supply farther and at the same time keep the wait light off.
8 FOR \$17.50

CALL YOUR BANK AMERICARD OR MASTER CHARGE ORDER IN ON OUR CONTINENTAL UNITED STATES TOLL FREE WATTS:
1-800-527-3460

SALE ON CUT LEAD SEMICONDUCTORS
Leads were cut for PCB insertion. Still very useable. All new, unused. Some House no.
IN914/IN4148 100/\$2.
IN4002 1 Amp 100 PIV 40/\$1.
IN4745A 16V 1W Zener. 20/\$1.
EN2222 NPN Transistor 25/\$1.
EN2907 PNP Transistor 25/\$1.
2N3904 NPN Driver Xstr 25/\$1.
2N3392 GE Pre-amp Xstr 25/\$1.
C103Y SCR, 800MA 60V 10/\$1.


C&K MINI TOGGLE SWITCH
No. 7103 SUB MINI SPDT Center OFF.
SPECIAL - 99c

TERMS:
Money Back Guarantee. No COD. Texas Residents add 5% tax. Add 5% of order for postage and handling. Orders under \$10. add 75c. Foreign orders: US Funds ONLY!

Texas Residents Call Collect
214/271-0022

S. D. SALES
P. O. Box 28810-C
Dallas, Texas 75228

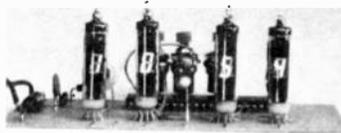ORDERS OVER \$15. CHOOSE \$1. FREE MERCHANDISE



CLOCK KIT \$14.00

Includes all parts with MM5316 chip, transformer, drilled & etched PC board, all except case. #SP-284 \$14 or 2/\$25

ASCII KEYBOARD, brand new w/paperwork \$45.00

AA NICAD CELLS brand new \$1.25 each 9/\$9.00

C-MOS LINEAR all brand new RCA

301	\$.60	747	\$.82	CLOCK CHIPS
307	.52	748	.50	MM5314 \$3.00
324	1.80	1458	.96	MM5316 3.00
339A	1.60	3401	.80	
741	.50	555	.60	7001 8.00

POWER SUPPLY KIT

Puts out 24-12-6 volt DC 2 amps. Includes xfmr, line cord, filter, silicon bridge. #PK-2B \$9.00

B & L HELIUM NEON GAS LASER

Fully assembled, runs on 115 volts AC. Less Laser tube. \$15.00

POWER AMP TRANSFORMER \$9.00
115 volts input, output of 96 VCT 2 amps. \$9.00 each 3/\$25

Please add shipping cost on above.

FREE catalog

Meshna SURPLUS ELECTRONIC MATERIAL
P.O. Box 62
19 ALLERTON STREET
E. LYNN MASS. 01904

CIRCLE 63 ON FREE INFORMATION CARD

**12" ALL PURPOSE
1 VOLT P TO P
GREEN PHOSPHOR
VIDEO DISPLAY**
IDEAL UNIT FOR ANY DIGITAL
OR GRAPHICS APPLICATION
\$150 Add \$10 for packing and
shipping in continental US

COMPUTER WAREHOUSE STORE WRITE FOR OUR CATALOG % Dept R
584 Commonwealth Ave. Boston 02215

CANADIAN discount and factory clearouts catalog. Top brand stereo equipment, calculators, test gear, CB & communications, telephones. Factory dumps—government surplus. Amazing bargains. Unusual items. Rush \$1. ETCO-RE, 521 5th Ave., NYC, 10017

NEW Canadian Magazine, "Electronics Workshop", \$5.00 yearly, sample \$1.00. ETHCO, Box 741 "A", Montreal

TV games kits P/C boards

Send for your information packet today— which also includes circuit functions, component line-up, and accessories. Information Packet \$1.00 (refundable with order)

visulex P O Box 4204R Mountain View, CA 94040

UNSCRAMBLES: We manufacture one of the finest police code unscramblers on the market. Our prices are very competitive and our service is the best. For further information call or write: **DON NOBLES ELECTRONICS, INC.**, Dept. RE, Rt. 7, Box 265B, Hot Springs, AR 71901

NOW! For Canadian Consumers & Hobbyists; **LOW PRICED, QUALITY PARTS** by mail

Featuring TTL, CMOS, LED's, Linears, Transistors, etc. Prices like... For complete catalogue, send 25¢ for handling to: **TRINTECHNICS LTD.** PO Box 181, Station G, Toronto, Ont M4M 3G7

CMOS 4000... \$24 TTL74LS02... \$45
CMOS4049... 86 741 mini-dip... 45
CMOS4011... 29 resistors... 06
TTL7440... 23 switching... 05
TTL7410... 86 diodes... 05

Unitronics Limited

NEW adjustable three output regulated power supply, plus 900 parts worth \$400.00 list. Solid state cartrivision television recorder electronic unit. Schematics, parts cross reference. Heath-kit television transistor substitutions. Power CB radios, microprocessors. \$17.95 plus \$3.50 S&H, USA. Free brochure. Master Charge, BankAmericard. Satisfaction guaranteed. **MADISON ELECTRONICS COMPANY, INCORPORATED**, Box 369, D101, Madison, AL 35758

PICTURE TUBE MACHINE
We buy and sell NEW and USED CRT rebuilding machines. COMPLETE TRAINING. Buy with CONFIDENCE from the ORIGINAL MFR.

For complete details send name address zip code to:
LAKESIDE INDUSTRIES
2520 W. Fullerton Ave
Chicago Ill 60647
Phone 312-342-3399

FOR discriminating builders: quality parts, bits, pieces, military and industrial. U.S., Canada, Mexico. Free catalog. **BRAND X**, Rt. 3, Box 223-11, Ontario, OR 97914

600-MHZ 7-digit portable frequency counter, battery or electric. \$299.95. 600-MHz prescaler +10 or +100. \$59.95. **CBS**, Box 1356, Cocoa Beach, FL 32931

FREE catalog. Calculators \$4.95 each, ultrasonic devices, digital thermometers, strobe light kits, memories, photographic electronic flash units, rechargeable batteries, LED's, transistors, IC's, piezoelectric crystals, toroidal cores, unique components. **CHANEY'S**, Box 27038, Denver, CO 80227

CB SPECIALS—R.F. DRIVERS—R.F. POWER OUTPUTS—FETS

2SC481 1.85	2SC767 15.75	2SC866 5.85	2SC1449-1 1.60	40081 1.50
2SC482 1.75	2SC773 .85	2SC1013 1.50	2SC1475 1.50	40082 3.00
2SC495 1.10	2SC774 1.75	2SC1014 1.50	2SC1678 5.50	2SC608 4.85
2SC502 3.75	2SC775 2.75	2SC1017 1.50	2SC1679 4.75	SK3046 2.15
2SC517 4.75	2SC776 3.00	2SC1018 1.50	2SC1728 2.15	SK3047 3.75
2SC614 3.80	2SC777 4.75	2SC1173 1.25	2SC1760 2.15	SJ2095 3.50
2SC615 3.90	2SC778 3.25	2SC1226A 1.25	2SC1816 5.50	SK3048 3.25
2SC616 4.15	2SC797 2.50	2SC1237 4.50	2SC1908 1.50	SK3054 1.25
2SC617 4.25	2SC798 3.10	2SC1239 3.50	2SC1957 1.50	
2SC699 4.75	2SC781 3.00	2SC1243 1.50	2SF8 3.00	2SK19 1.75
2SC710 .70	2SC789 1.00	2SC1306 4.75	HEP-S 3001 3.25	2SK30 1.00
2SC711 .70	2SC796 3.15	2SC1307-1 4.90	2SD235 1.00	2SK33 1.20
2SC735 .70	2SC799 4.25	2SC1307 5.75	MRF8004 3.00	
2SC756 3.00	2SC802 3.75	2SC1307-1 6.00	4004 3.00	3SK40 2.75
2SC765 9.50	2SC803 4.00	2SC1377 5.50	4005 3.00	3SK45 2.75
2SC766 10.15	2SC839 .85	2SC1449 1.30	40080 1.25	3SK49 2.75

JAPANESE TRANSISTORS

2SA52 .60	2SB187 .60	2SC458 .70	2SC815 .75	2SC1569 1.25
2SA316 .75	2SB235 1.75	2SC460 .70	2SC828 .75	2SC1756 1.25
2SA473 .75	2SB303 .65	2SC478 .80	2SC829 .75	
2SA483 1.95	2SB324 1.00	2SC491 2.50	2SC830 1.60	2SD30 .95
2SA489 .80	2SB337 2.10	2SC497 1.60	2SC839 .85	2SD45 2.00
2SA490 .70	2SB367 1.60	2SC515 .80	2SC945 .65	2SD65 .75
2SA505 .70	2SB370 .65	2SC535 .75	2SC1010 .80	2SD68 .90
2SA564 .50	2SB405 .85	2SC536 .65	2SC1012 .80	2SD72 1.00
2SA628 .65	2SB407 1.65	2SC537 .70	2SC1051 2.50	2SD88 1.50
2SA643 .85	2SB415 .85	2SC563 2.50	2SC1061 1.65	2SD151 2.25
2SA647 2.75	2SB461 1.25	2SC605 1.00	2SC1079 3.75	2SD170 2.00
2SA673 .85	2SB463 1.65	2SC620 1.80	2SC1096 1.20	2SD180 2.75
2SA679 3.75	2SB471 1.75	2SC627 1.75	2SC1098 1.15	2SD201 1.95
2SA682 .85	2SB474 1.50	2SC642 3.50	2SC1115 2.75	2SD218 4.75
2SA699 1.30	2SB476 1.25	2SC643 3.75	2SC1166 7.0	2SD300 2.50
2SA699A 1.75	2SB481 2.10	2SC644 .70	2SC1170 4.00	2SD313 1.10
2SA705 .55	2SB492 1.25	2SC681 2.50	2SC1172B 4.25	2SD315 1.75
2SA815 .85	2SB495 .95	2SC684 2.10	2SC1209 .55	2SD318 .95
2SA816 .85	2SB507 .90	2SC687 2.50	2SC1213 .75	2SD341 .95
	2SB511 .70	2SC696 2.35	2SC1226 1.25	2SD350 3.25
2SB22 .65		2SC712 .70	2SC1243 1.50	2SD352 .80
2SB54 .70	2SC206 1.00	2SC713 .70	2SC1293 .85	2SD380 5.70
2SB56 .70	2SC240 1.10	2SC732 .70	2SC1308 4.75	2SD389 .90
2SB77 .70	2SC261 .65	2SC733 .70	2SC1347 .80	2SD-390 7.5
2SB128 2.25	2SC291 .65	2SC739 .70	2SC1383 .75	2SD437 5.50
2SB135 .95	2SC320 2.00	2SC715 1.75	2SC1409 1.25	
2SB152 4.50	2SC352 .75	2SC762 1.90	2SC1410 1.25	MPS-U31 4.00
2SB173 .55	2SC353 .75	2SC783 1.00	2SC1447 1.25	MPS8000 1.25
2SB175 .55	2SC371 .70	2SC784 .70	2SC1448 1.25	
2SB178 1.00	2SC372 .70	2SC785 1.00	2SC1507 1.25	
2SB186 .60	2SC394 .70	2SC793 2.50	2SC1509 1.25	

POWER-TRANSISTORS HIGH-VOLT. TV. TYPE

BU204 1300V 3.90	BU207 1300V 5.40	2SC1172B 1100V 4.25
BU205 1500V 4.70	BU208 1500V 6.25	2SC1308 1100V 4.95
BU206 1700V 5.90	2SC1170 1100V 4.00	2SC1325 1100V 4.95

OEM SPECIALS

1N270 .10	2N960 .55	2N2219A .30	2N2913 .75	2N3740 1.00	2N4401 .20
1N914 .10	2N962 .40	2N2221 .25	2N2914 1.20	2N3771 1.75	2N4402 .20
	2N967 .50	2N2221A .30	2N2916A 3.65	2N3772 1.90	2N4403 .20
	2N173 1.75	2N2222 .25	2N3019 .50	2N3773 3.00	2N4409 .20
	2N178 .90	2N2222A .30	2N3053 .70	2N3819 .32	2N4410 .25
	2N237A 1.15	2N2270 .40	2N3054 .30	2N3823 .70	2N4416 .75
	2N234 1.20	2N2302 .25	2N2322 1.00	2N3856 .20	2N4441 .85
	2N2336 .90	2N2305 .30	2N2323 1.00	2N3866 .85	2N4442 .90
	2N2338A 1.05	2N2320 .20	2N2324 1.35	2N3902 .20	2N4443 1.20
	2N2398B .90	2N2321 .95	2N2325 2.00	2N3904 .20	2N4452 .55
	2N404 .30	2N2326 2.85	2N2326 2.85	2N3905 .20	2N5061 .30
	2N443 1.75	2N2327 3.80	2N2327 3.80	2N3906 .25	2N5064 .50
	2N456 1.10	2N2328 4.20	2N2328 4.20	2N3925 3.75	2N5130 .20
	2N501A 3.00	2N2329 4.75	2N2329 4.75	2N3954 3.50	2N5133 .15
	2N508A .45	2N2368 2.50	2N2368 2.50	2N3955 2.45	2N5198 3.75
	2N555 .45	2N2369 2.25	2N2369 2.25	2N3957 1.25	2N5294 .50
	2N652A .85	2N2484 .32	2N2484 .32	2N3958 1.20	2N5296 .50
	2N677C 6.00	2N2577 1.18	2N2577 1.18	2N4037 .60	2N5306 .20
	2N706 .25	2N2894 .40	2N2894 .40	2N4093 .85	2N5354 .20
	2N706B .40	2N2903 3.30	2N2903 3.30	2N4124 .20	2N5369 .20
	2N711 .50	2N2904 .25	2N2904 .25	2N4126 .20	2N5400 .40
	2N711B .60	2N2904A .30	2N2904A .30	2N4127 .20	2N5401 .50
	2N718 .25	2N2905 .25	2N2905 .25	2N4128 .20	2N5457 .35
	2N718A .30	2N2905A .30	2N2905A .30	2N4129 .20	2N5458 .30
	2N720A .50	2N2906 .25	2N2906 .25	2N4130 .20	2N5459 .35
	2N718 .35	2N2906A .30	2N2906A .30	2N4131 .20	2N5459 .35
	2N930 .25	2N2907 .25	2N2907 .25	2N4132 .20	2N5459 .35
	2N956 .30	2N2907A .30	2N2907A .30	2N4133 .20	2N5459 .35
		2N2907B .30	2N2907B .30	2N4134 .20	2N5459 .35

SILICON UNIUNCTIONS		INTEGRATED CIRC.		RECTIFIERS	
2N2646 .50	2N4871 .50	UA703C .40		10	100
2N2647 .60	2N4891 .50	709C OP. AMP. .25		IN4001 .60	5.00
2N6027 .55	2N4892 .50	741C OP. AMP. .25		IN4002 .70	6.00
2N6028 .70	2N4893 .50	7400 .15		IN4003 .80	7.00
05E37 .25	2N4894 .50	TA7061P 3.50		IN4004 .90	8.00
2N2160 .65	MU10 .40	TA7205P 8.00		IN4005 1.00	9.00
2N4870 .50		UPC1001h2 6.00		IN4006 1.10	10.00
		Ne555 1.25		IN4007 1.20	11.00

n-te **New-Tone Electronics**
P.O. Box 1738 A
Bloomfield, N.J. 07003
Phone: (201) 748-6171
748-6172
748-6173


ALL PARTS GUARANTEED

N.J. residents add 5% sales tax. Minimum order \$5.00. All orders add \$1.00 postage. Dealers write or phone for discount prices.

CIRCLE 64 ON FREE INFORMATION CARD

RADIO-ELECTRONICS

SPECIAL OF THE MONTH

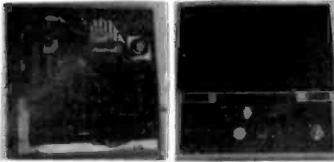

MADE FOR HOTEL ROOM SERVICE WAKE UP SERVICE Here's a parts list- All new not used, just installed in the board. 1-LM309K, heat sink, 2-2N5137, 5-2N3904, 2-7400, 7402, 1-7403, 3-7410, 1-7413, 2-7430, 9-7474, 1-7486, 1-74151, 1-74154, 1-4001, 2-741CT, 5-TIP29 & 30, 1-LM380 AN (14), 3-MDA942-1 Bridges, 1-555 Timer, 1-OnOff 10K Vol Con 1-Fuse Block with 1 A StoBto 1-4" Speaker 3, 2 Ohm 1 Watt, 1-Transformer 16V Pri 5V-12V 1-Thumbwheel Switch 2 Digit 12 Positions, 40 other Misc. Weight 4 lbs
USE FOR: 5V DC Power Supply P. A. or Music Outlet
Price: **\$12.95**

TTL IC'S

7400 .18	7441 .75	7496 .65	74160 .86
7401 .20	7442 .44	7497 2.00	74161 .62
7402 .20	7443 1.20	74100 1.25	74162 1.35
7403 .20	7445 .89	74107 .26	74163 .76
7404 .20	7446 .87	74109 .35	74164 .80
7405 .20	7447 .69	74110 .50	74165 .90
7406 .39	7448 .81	74116 2.00	74166 1.00
7407 .39	7450 .20	74120 1.25	74167 3.00
7408 .20	7451 .20	74121 .34	74170 2.00
7409 .24	7453 .20	74122 .39	74172 9.72
7410 .20	7454 .20	74123 .50	74173 1.25
7411 .20	7460 .20	74125 .45	74174 .85
7412 .24	7470 .20	74126 .45	74175 .75
7413 .35	7472 .23	74128 .65	74176 .85
7414 .70	7473 .26	74132 .95	74177 .85
7416 .33	7474 .29	74136 .50	74180 .75
7417 .33	7475 .39	74141 .80	74181 2.00
7420 .20	7476 .31	74142 4.00	74182 .90
7422 .50	7479 2.40	74143 4.00	74184 1.65
7423 .28	7480 .69	74144 4.00	74185 1.30
7425 .24	7482 .72	74145 .70	74190 1.00
7426 .24	7483 .75	74147 2.50	74191 .65
7427 .24	7485 .90	74148 1.75	74192 .85
7428 .40	7486 .25	74150 1.00	74193 .85
7429 .40	7488 3.50	74151 .70	74194 1.20
7430 .20	7489 1.50	74153 .70	74195 .55
7432 .28	7490 .39	74154 .90	74196 .80
7433 .34	7491 .65	74155 .70	74197 .83
7437 .28	7492 .39	74156 .90	74198 1.50
7438 .28	7493 .39	74157 .70	74199 1.75
7439 .36	7494 .70	74158 1.75	74200 3.50
7440 .20	7495 .50	74159 2.25	74279 1.75

Crowntec L.E.D. watches



6-Function, 1-Button Solid State. Hours, Minutes, Seconds, Day of Week, Month & Day. The Crowntec L.E.D. watch contains the finest custom designed quartz crystal to assure accuracy of 3 min. per year. Guaranteed 1 yr. from date of purchase (battery excepted).

FROM **29.95 up**

Illustrated:
Men's Rhodium with Leather Band \$29.95
Ladies \$39.95

Other styles available in gold tone as well as Rhodium finish.

CLOCK KIT \$12.95

MM5316, pc bd., display tubes switches, etc, instructions.



CLOCK CHIPS

MM5375, CT7001, MM5316
Your choice **\$4.95**

MICROPROCESSOR COMPONENTS





8008-1	8 Bit CPU	18.95
8080	Improved 8008	24.95
8080A	Super 8080	34.95
DYNAMIC RAMS		
31L01	64 Bit low pow	4.45
1103	1024x1	2.50
2107B-4	4096x1	8.00
8225B	16x4	1.50
93407	16x1	4.85
STATIC RAMS		
1101	256x1	1.75
2102	1024x1	2.00
2501B	256x1	1.75
3107	256x1	4.00
7489	64 Bit R/W	2.00
74200	256 Bit R/W	5.75
PROMS		
1702A	256x8 Eras	12.00
1702AL	256x8 low pow	12.00
8223B	32x8	3.50
74S 287N	256x4	6.95
SHIFT REGISTERS		
MM5058	1024x1 Static	4.75
TMS3002LR	Dual 50	4.00
TMS3132NC	Dual 144	3.00
COMPARES TO		
2107B4	TMS4060	
2102	AMD9102, ISL7552-1, TMS4033	
MM5058	AMD2533, FSC3355, TMS3133	
TMS3002	SIG2509	
TMS3132	MM4060, FSC3346	

VIDEO GAME KIT 5IVE Games To Play

A CHALLENGE TO BUILD,
A CHALLENGE TO PLAY.

Features:

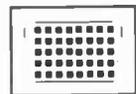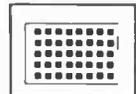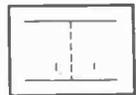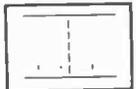1. Basic Tennis games in three variations.
2. Plus 2 variations of Wipe Out the squares. A fascinating game for 1 or 2 players. Not available in most games sold.
3. All 5 games in one kit.
4. Curve Button for added excitement.
5. On screen scoring between plays.
6. Sound.
7. Basic TTL circuitry except for VK-6 proms.
8. Requires 5V DC + at 2 A.



VK-1	PC Board Only Includes parts list & wiring Diagram requires VK-6	25.00
VK-2	PC Board with parts Includes PC Board, 78 IC's (those necessary are pre-programmed) resistors & capacitors to stuff the board.	125.00
VK-3	Hardware Kit Controls, switches, wire Does not include Housing.	17.50
VK-4	RF Module Kit To convert video signal to TV receiver signal. Eliminates internal "wire in" on TV set.	22.50
VK-4-A	Antenna-Game Switch Allows outside antenna to remain connected while game is in use.	9.50
VK-5	Power Supply Kit For VK-1 or VK-2 PC Board ONLY.	12.50
VK-6	PROM Set 3 Programmed DM8574N with 2 DM8130N for VK-1 (If you have plenty of TTL).	50.00

SMOKE DETECTOR

PHOTO ELECTRIC TYPE



NOT A KIT

But a complete unit ready to install. U. L. approved Listed by Cal. Fire Code **\$29.95**

NATIONAL RA1001A DIGITAL ALARM CLOCK MODULE



FEATURES:

- Bright 4 Digit 0.5" LED Display
- Assembled & Tested Module
You only need mount transformer & antenna
- 12 Hour Format with PM Indicator
- 50 or 60 Hz Operation
- Power Failure Indication
- Brightness Control Capability
- Alarm and Snooze Timers
- Compact 3.8" x 1.75"

\$9.95

JADE Co

ELECTRONICS DISTRIBUTION

2007 W. CARSON (213) 320-1250
P.O. BOX 4246 TORRANCE, CA. 90510

TERMS:

Add \$1.00 for shipping plus \$.85 if COD
California Residents add 6% Sales Tax
\$20 minimum on BotA & M.C.

Orders from Foreign countries add appropriate postage

CRYSTALS

THESE FREQUENCIES ONLY

Part #	Frequency	Case/Style	Price
CY1A	1,000 MHz	HC33/U	\$4.95
CY2A	2,000 MHz	HC33/U	\$4.95
CY3A	4,000 MHz	HC18/U	\$4.95
CY7A	5,000 MHz	HC18/U	\$4.95
CY12A	10,000 MHz	HC18/U	\$4.95
CY14A	14,31818 MHz	HC18/U	\$4.95
CY19A	18,000 MHz	HC18/U	\$4.95
CY22A	20,000 MHz	HC18/U	\$4.95
CY30B	32,000 MHz	HC18/U	\$4.95

EDGE CONNECTORS

22 Pin dual Read Out .156 2.25
50 Pin dual Read Out .125 5.00

LED'S

TIL302	0.27 ChHt	1.00
MAN4	0.187 ChHt	2/1.00

CRYSTALS

THESE FREQUENCIES ONLY

Part #	Frequency	Case Style	Price
CY1A	1.000 MHz	HC33/U	\$5.95
CY2A	2.000 MHz	HC33/U	\$5.95
CY3A	4.000 MHz	HC18/U	\$4.95
CY7A	5.000 MHz	HC18/U	\$4.95
CY12A	10.000 MHz	HC18/U	\$4.95
CY14A	14.31818 MHz	HC18/U	\$4.95
CY19A	16.000 MHz	HC18/U	\$4.95
CY22A	20.000 MHz	HC18/U	\$4.95
CY30B	32.000 MHz	HC18/U	\$4.95

CLOCK CHIPS — CALCULATOR CHIPS

MM5309	6 Digit, BCD Outputs, Reset Pin	\$9.95
MM5311	6 Digit, BCD Outputs, 12 or 24 Hour	4.95
MM5312	4 Digit, BCD Outputs, 1 PPS Output	4.95
MM5314	6 Digit, 12 or 24 Hour, 50 or 60 Hz	4.95
MM5316	4 Digit, Alarm, 1 PPS Output	6.95
MM5318	Video Clock Chip, For Use With MM5841	9.95
CT7001	6 Digit, Calendar, Alarm, 12 or 24 Hour	5.95

CALCULATOR CHIPS

MM5725	5 Digit Four Function, Less Decimal	\$2.95
MM5738	8 Digit, 5 Function, %	2.95
MM5739	8 Digit, 4 Function, Floating Decimal	2.95
CT5030	12 Digit, 4 Function and %	7.95

MISC. MOS

MM5320	TV Camera Sync Generator	\$19.95
MM5330	4 1/2 Digit DVM Chip	9.95
MM5359	60 Hz Timebase Circuit From 3.58 MHz	3.95
MM5451	Video Generator for MM5318	18.00
MC1406-L7	7 Bit Digital to Analog Converter	9.95
MC5007	4 Decade Counter with Latches	10.95
LD110 LD111	3 1/2 Digit DVM Chip Set	25.00
85H90	100 MHz — 10 Counter For Prescalars	13.95

IMC 3 1/2 DIGIT DVM KIT



This 0-2 VDC .05 per cent digital voltmeter features the Motorola 3 1/2 digit DVM chip set. It has a 4' LED display and operates from a single -5V power supply. The unit is provided complete with an injection molded black plastic case complete with Bezel. An optional power supply is available which fits into the same case as the 0-2V DVM allowing 117 VAC operation.

A. 0-2V DVM with Case \$49.95
B. 5V Power Supply \$14.95

VECTOR WIRING PENCIL



Vector Wiring Pencil P173 consists of a hand held featherweight (under one ounce) tool which is used to guide and wrap insulated wire. Fed off a self-contained replaceable bobbin onto component leads or terminals installed on pre-punched "P" Pattern "Vectorboards". Connections between the stripped wire and component leads, pins or terminals are made by soldering. Complete with 250 FT. of red wire.

\$7.95

REPLACEMENT WIRE — BOBBINS FOR WIRING PENCIL

W36-3-A-Pkg	3	250 Yd.	36 AWG GREEN	\$1.95
W36-3-B-Pkg	3	250 Yd.	36 AWG RED	\$1.95
W36-3-C-Pkg	3	250 Yd.	36 AWG CLEAR	\$1.95
W36-3-D-Pkg	3	250 Yd.	36 AWG BLUE	\$1.95

1/16 VECTOR BOARD

Material	Part #	Size	Price
PHENOLIC	64H23 DE2 UXP	1.50 x 9.50	1.79
	159P21 D2 UXP	1.50 x 12.00	3.09
EPOXY GLASS	64P11 D62	1.50 x 6.50	2.07
	84P11 D62	1.50 x 8.50	2.56
EPOXY GLASS COPPER CLAD	189P44 D62	1.50 x 17.00	5.01
	189P84 D62	8.50 x 17.00	9.23
	189P44 D62C1	1.50 x 17.00	6.90

HEAT SINKS

205-CB	Beryllium Copper Heat Sink with Black Finish for TO-3	.25
291-36H	Aluminum Heat Sink for TO-220 Transistors & Regulators	.25
680-75A	Black Anodized Aluminum Heat Sink for TO-3	1.60

NIBBLING TOOL



Nibbling Tool Replacement Punch \$3.75 Each

Diagonal Cutter Semi-Flush Cut Fine Diagonal \$4.50 ea.

63 KEY KEYBOARD

This keyboard features 63 unswitched RSPT keys, unattached to any kind of P.C.B. A very solid molded plastic 13 x 4 base suits most applications.

\$19.95

MO0165 16 LINE TO FOUR BIT PARALLEL KEYBOARD ENCODER \$7.95

JOYSTICK

These joysticks feature four potentiometers, that vary resistance proportional to the angle of the stick. Sturdy metal construction with plastic components only at the movable joint. Perfect for electronic games and instrumentation.

***5K Pots \$6.95**
***100K Pots \$7.95**

MICROPROCESSOR COMPONENTS

8080 SUPPORT DEVICES

8080A	8 BIT INPUT/OUTPUT PORT FOR 8080	\$ 5.95	8080	8 2 25
8212	NON INTERRUPT BI-DIRECTIONAL BUS DRIVER	7.95	\$24.95	2 for 1.00
8224	CLOCK GENERATOR AND DRIVER FOR 8080	12.95		
8228	SYSTEM CONTROLLER AND BUS DRIVER FOR 8080	12.95		

Part #	Price	Part #	Price
8008	\$19.95	1101	256 x 1
8080	24.95	1103	1024 x 1
8080A	34.95	2101	256 x 1
		2102	1024 x 1
2504	\$ 9.00	2107	4096 x 1
2518	7.00	2111	256 x 4
2519	4.00	7010	1024 x 1
2524	2.49	7489	16 x 4
2525	6.00	8101	256 x 4
2527	3.95	8111	256 x 4
2529	4.00	8509	16 x 4
2532	3.95	91102	1024 x 1
2533	7.95	74200	256 x 1
3241	6.95	93421	256 x 1
74LS670	3.95	MM5262	2K x 1

BIPOLAR PROM SPECIAL

6300-1 (70 NS)	256 x 4 OPEN COLLECTOR BIPOLAR PROM (EQUIVALENT TO 82S126)	\$2.95
6301-1 (70 NS)	256 x 4 TRI STATE BIPOLAR PROM (EQUIVALENT TO 82S129)	\$2.95

Continental Specialties

Proto Board 100 \$19.95

Proto Board 101 \$29.95

Proto Board 102 \$39.95

Proto Board 103 \$59.95

Proto Board 6 \$15.95

LOGIC MONITOR \$84.95

Part #	Price	Part #	Price
QT-595	\$1.50	QT-165	\$1.50
QT-598	\$1.50	QT-125	\$1.50
QT-475	\$1.50	QT-185	\$1.50
QT-478	\$1.50	QT-75	\$1.50
QT-385	\$1.50		
QT-358	\$1.50		

DIGITAL WATCHES

Ladies Watch	\$69.95	EXELAR Mens Watch	\$29.95
--------------	---------	-------------------	---------

DIGITAL QUARTZ CAR CLOCK

Complete kit from mounting bracket of the injection molded case down to the three conductor power cord and all components including MM5314 clock chip. Features quartz accuracy of .01%, six digit, .35" high LED display, and P.C. boards. Works on any 12 volt system — motorcycles, boats, vans, motorhomes, autos, and trucks.

DIMENSIONS: 4 1/2" x 4" x 2" — 12 OR 24 HOUR MODE.

Kit: \$29.95 Assembled: \$39.95

DIGITAL CLOCK KIT — 3 1/2" INCH DIGITS

This clock features big 3 1/2" high digits for viewing in offices, auditoriums, etc. Each digit is formed by 31 bright 0.2 LED's. The clock operates from 117 VAC, has either 12 or 24 hr. operation. The 6 digit version is 27" x 19" x 1 1/2", and the 4 digit is 18" x 13" x 1 1/2". Kits come complete with all components, case and transformer.

Specify 12 Or 24 Hr. When Ordering

4 DIGIT KIT	\$49.95	4 DIGIT ASSEMBLED	\$59.95
6 DIGIT KIT	\$69.95	6 DIGIT ASSEMBLED	\$79.95

Satisfaction Guaranteed. \$5.00 Min. Order. U.S. Funds. California Residents — Add 6% Sales Tax — Data Sheets 25¢ each. Send a 24¢ Stamp (postage) for a FREE 1977 Catalog.

NOW OPEN SATURDAYS

JAMES

1021 HOWARD AVE., SAN CARLOS, CA. 94070
 PHONE ORDERS WELCOME — (415) 592-8097

CB RADIO



NEW IDI ICB-630

23-Channel Synthesized CB Transceiver

SIZE: 6 1/2" (W) x 2 1/2" (H) x 8 1/4"
 POWER INPUT: 5 Watts/12-Volt Max.
 POWER OUTPUT: 4 Watts RMS

\$99.95

MOBILE CB ANTENNA

BASE LOAD - FIBERGLASS WHIP

Mounts on Hood or Trunk Lid

\$24.95 KA-2401

AMTEX 8 TRACK AM/FM STEREO

FEATURES \$69.95

- 8 Track stereo player
- AM-FM mpx radio
- Advanced IC construction
- Dial on door and side-rod switch type
- Compact — only 1-25/32" (45mm) high, 4-13/16" (122mm) deep, 6-11/16" (170mm) wide and 5 position adjustable shaft distance
- Complete in-cash type design
- Easily adjustable antenna trimmer for best performance

KRACO CAR SPEAKERS

Flush Mount 10 Oz. Mag./8 ohm Model SST-101F

\$14.95

5 FUNCTION ELECTRONIC CALCULATOR

RADOFIN MODEL 8P

FEATURES: \$8.95

- 8 Digit Display
- 5 Functions consists of addition, subtraction, multiplication, division, percentage, with constant on all functions, with full floating decimal point
- Power source is 1 piece 9V DC Battery 009P, rack for AC adapter
- Black surface grain finished plastic cabinet

5 FUNCTION ELECTRONIC CALCULATOR WITH WALLET-NOTEBOOK AND POCKET CHECKBOOK

RADOFIN MODEL 1710

FEATURES: \$19.95

- 8 Digit Display
- 5 Functions consists of addition, subtraction, multiplication, division, percentage, with constant on all functions, with full floating decimal point
- Power source is 6 AAA cells 9 V DC
- Wallet is 2 tone lexan, cabinet is black plastic

DIGITAL ALARM CLOCK

Novus

This 4 digit Novus Alarm Clock is a very reliable and smartly styled unit. It provides such features as an alarm settable to any minute of the day, a 7 minutes snooze alarm, a power failure indicator, and even an A.M., P.M. indicator.

\$17.95 NOT A KIT

JE700 CLOCK

The JE700 is a low cost digital clock, but is a very high quality unit. The unit features a simulated walnut case with dimensions of 6" x 2 1/2" x 1". It utilizes a MAH72 high brightness readout and the MM5314 clock chip.

12 or 24 Hour

115 VAC

\$17.95

12:49:38

KIT - ALL COMPONENTS & CASE \$34.95 WIRED & ASSEMBLED \$39.95

JE803 PROBE

The Logic Probe is a unit which is for the most part independent in trouble shooting logic families TTL, DTL, RTL, CMOS. It derives the power it needs to operate directly off of the circuit under test, drawing a scant 10 mA max. It uses a BAK33 readout to indicate any of the following states by these symbols: (H) - 1 (LOW) - 0 (PULSE) - P. The Probe can detect high frequency pulses to 45 MHz. It can't be used at MOS levels or circuit damage will result.

\$9.95 Per Kit printed circuit board

TTL 5V 1A Supply

This is a standard TTL power supply using the well known LM300K regulator IC to provide a solid 1 AMP of current at 5 Volts. We try to make things easy for you by providing everything you need in one package, including the hardware for only

\$9.95 Per Kit

± 5 VOLT POWER SUPPLY

Completely Assembled

- +5 Volts @ 6 Amps
- Regulated Output
- 5 Volts @ 6 Amps
- Regulated Input
- 6.3 Volts @ 5 Amps
- Unregulated Output

Length 8 1/2" x Width 6 1/2" x Height 4"

Limited Supply

\$39.95

7400N TTL

SN7400N	16	SN7459A	25	SN74154N	1.00
SN7401N	21	SN7460N	22	SN74155N	99
SN7402N	15	SN7470N	45	SN74156N	99
SN7403N	18	SN7472N	39	SN74157N	99
SN7404N	18	SN7473N	37	SN74158N	99
SN7405N	24	SN7474N	32	SN74159N	99
SN7406N	20	SN7475N	50	SN74161N	99
SN7407N	28	SN7476N	32	SN74163N	99
SN7408N	25	SN7479N	5.00	SN74164N	1.10
SN7409N	25	SN7480N	90	SN74165N	1.10
SN7410N	18	SN7482N	98	SN74166N	1.25
SN7411N	30	SN7483N	70	SN74167N	5.10
SN7412N	33	SN7485N	89	SN74170N	2.10
SN7413N	45	SN7486N	39	SN74172N	8.95
SN7414N	69	SN7488N	3.50	SN74173N	1.50
SN7416N	35	SN7489N	2.25	SN74174N	1.25
SN7417N	23	SN7490N	45	SN74175N	99
SN7420N	31	SN7491N	75	SN74176N	90
SN7421N	33	SN7492N	49	SN74177N	90
SN7422N	49	SN7493N	49	SN74180N	99
SN7423N	37	SN7494N	79	SN74181N	2.49
SN7425N	29	SN7495N	79	SN74182N	95
SN7426N	29	SN7496N	89	SN74184N	1.95
SN7427N	43	SN7497N	4.00	SN74185N	2.00
SN7429N	42	SN74100N	1.00	SN74186N	5.00
SN7430N	26	SN74107N	39	SN74187N	6.00
SN7432N	31	SN74121N	39	SN74188N	3.95
SN7437N	27	SN74122N	39	SN74190N	1.19
SN7438N	21	SN74123N	70	SN74191N	1.25
SN7439N	25	SN74125A	60	SN74192N	89
SN7440N	15	SN74126N	80	SN74193N	89
SN7441N	89	SN74132N	1.09	SN74194N	1.25
SN7442N	59	SN74136N	95	SN74195N	75
SN7443N	75	SN74137N	1.15	SN74196N	99
SN7444N	75	SN74142N	4.00	SN74197N	75
SN7445N	75	SN74143N	4.50	SN74198N	1.75
SN7446N	81	SN74144N	4.50	SN74199N	1.75
SN7447N	69	SN74145N	1.15	SN74200N	99
SN7448N	79	SN74147N	2.95	SN74207N	1.25
SN7450N	26	SN74148N	2.00	SN74251N	1.79
SN7451N	27	SN74150N	7.00	SN74284N	6.00
SN7453N	29	SN74151N	79	SN74285N	6.00
SN7454N	29	SN74153N	89	SN74287N	75

MAN Y OTHERS AVAILABLE ON REQUEST
20% Discount for 100 Combined 7400's

CONSUMER ELECTRONICS

PONG SUPER PONG PONG

SINGLE GAME \$55.00
4 GAMES IN ONE \$79.95

FOR YOUR HOME TV

GAMES INCLUDED IN SUPER PONG ARE:

- PONG
- SUPER PONG
- CATCH
- HANDBALL

FEATURES OF PONG AND SUPER PONG

- Incremental speed on volleys increases excitement
- Playing field adapts to any size screen
- Game appears in color or black & white, depending on television set
- Unmistakable "PONG" sound accompanies each volley
- Digital scoring flashes on the screen between each point
- 2 player challenge or Solitaire
- Hooks up simply to any model television set, the screen actually becomes the playing field
- English and other techniques can be used to make any member of the family a Pong champion
- Battery operated by 4 size "D" flashlight batteries included with the Unit

AC Adaptor (Eliminates Batteries) \$9.95



125" dia. DISCRETE LEDS

XC209 Red	10/51	XC111 Red	10/51
XC209 Green	4/51	XC111 Green	4/51
XC209 Yellow	7/51	XC111 Yellow	4/51
XC209 Orange	4/51	XC111 Orange	4/51

200" dia. 185" dia. 200" dia. .085" dia. DISPLAY LEDS

TYPE	POLARITY	HT	TYPE	POLARITY	HT
MAN 1	Common Anode	.270 2.95	MAN 3620	Common Anode-orange	300 1.75
MAN 2	5 + 7 Dot Matrix	300 4.95	MAN 3640	Common Cathode-orange	300 1.75
MAN 3	Common Cathode	30 125 99	MAN 4710	Common Anode Red	400 9.95
MAN 4	Common Cathode	187 1.95	DL 21	Common Anode-red	300 1.95
MAN 7	Common Anode	300 1.25	DL 70	Common Anode	300 1.50
MAN 7G	Common Anode-green	300 1.95	DL 72B	Common Cathode	500 2.95
MAN 7Y	Common Anode-yellow	300 1.95	DL 747	Common Anode	600 2.25
MAN 52	Common Anode-green	300 1.75	DL 760	Common Cathode	600 2.49
MAN 64	Common Anode-red	400 1.75	DL 338	Common Cathode	400 9.95
MAN 72	Common Anode	300 1.25	FND70	Common Cathode	250 75
MAN 74	Common Cathode	300 1.50	FND503	Common Cathode	500 1.29
MAN 82	Common Anode-yellow	300 1.75	FND507	Common Anode	500 1.29
MAN 84	Common Cathode-yellow	300 1.75			

MINIATURE TOGGLE

IPDT - SERIES PB, PBT

Miniature Toggle Switches
Push Button

PB-123 \$1.75
PB-126 \$1.75

THUMBWHEEL SWITCHES

THUMBWHEEL SWITCH ONLY

Ordering: Order correct switch or switches and select accessories for your particular application.

Series PB from Most Mount

DIP SWITCH

These switches feature seven SPST slide switches in a molded cap. They are ideally suited for microprocessor applications.

\$1.95

CLIPLITE !! 4/\$1.00 NEW LED MOUNTING SYSTEM

- CLIPLITE mounts from the front of the Panel in a .250 hole on 3/32" centers. Panel thickness from 1/16" to 1/8".
- CLIPLITE equalizes and increases the brightness of commonly used wide beam LEDs.
- CLIPLITE is to be used with XC556 LEDs.
- Specialty colors—red, green, amber, or yellow when ordering.

ZENERS-DIDDERS-RECTIFIERS

TYPE	VOLTS V	PRICE	TYPE	VOLTS V	PRICE
1N457A	3.3	400M	1N4007S	600 PIV	1 AMP 101.00
1N458A	5.1	400M	1N4007	900 PIV	1 AMP 101.00
1N459A	6.8	400M	1N4007P	1000 PIV	1 AMP 101.00
1N460A	8.2	400M	1N4620	50	200M 61.00
1N461A	10	400M	1N4618	75	10M 151.00
1N462A	15	400M	1N4615	25	10M 121.00
1N463A	20	400M	1N4620S	75	25M 261.00
1N464A	25	400M	1N4734	5.6	1W 28
1N465A	30	400M	1N4735	6.2	1W 28
1N466A	36	400M	1N4736	6.8	1W 28
1N467A	43	400M	1N4737	7.5	1W 28
1N468A	50	400M	1N4742	1.2	1W 28
1N469A	56	400M	1N4744	1.5	1W 28
1N470A	63	400M	1N4745	1.8	1W 28
1N471A	70	400M	1N4746	2.2	1W 28
1N472A	75	400M	1N4747	2.7	1W 28
1N473A	82	400M	1N4748	3.3	1W 28
1N474A	90	400M	1N4749	3.9	1W 28
1N475A	100	400M	1N4750	4.7	1W 28
1N476A	110	400M	1N4751	5.6	1W 28
1N477A	120	400M	1N4752	6.8	1W 28
1N478A	130	400M	1N4753	8.2	1W 28
1N479A	140	400M	1N4754	10	1W 28
1N480A	150	400M	1N4755	12	1W 28
1N481A	160	400M	1N4756	15	1W 28
1N482A	180	400M	1N4757	18	1W 28
1N483A	200	400M	1N4758	22	1W 28
1N484A	220	400M	1N4759	27	1W 28
1N485A	240	400M	1N4760	33	1W 28
1N486A	270	400M	1N4761	39	1W 28
1N487A	300	400M	1N4762	47	1W 28
1N488A	330	400M	1N4763	56	1W 28
1N489A	360	400M	1N4764	68	1W 28
1N490A	400	400M	1N4765	82	1W 28
1N491A	450	400M	1N4766	100	1W 28
1N492A	500	400M	1N4767	120	1W 28
1N493A	560	400M	1N4768	150	1W 28
1N494A	630	400M	1N4769	180	1W 28
1N495A	700	400M	1N4770	220	1W 28
1N496A	780	400M	1N4771	270	1W 28
1N497A	870	400M	1N4772	330	1W 28
1N498A	960	400M	1N4773	390	1W 28
1N499A	1050	400M	1N4774	470	1W 28
1N500A	1150	400M	1N4775	560	1W 28
1N501A	1250	400M	1N4776	680	1W 28
1N502A	1350	400M	1N4777	820	1W 28
1N503A	1450	400M	1N4778	1000	1W 28
1N504A	1550	400M	1N4779	1200	1W 28
1N505A	1650	400M	1N4780	1500	1W 28
1N506A	1800	400M	1N4781	1800	1W 28
1N507A	2000	400M	1N4782	2200	1W 28
1N508A	2200	400M	1N4783	2700	1W 28
1N509A	2400	400M	1N4784	3300	1W 28
1N510A	2700	400M	1N4785	3900	1W 28
1N511A	3000	400M	1N4786	4700	1W 28
1N512A	3300	400M	1N4787	5600	1W 28
1N513A	3600	400M	1N4788	6800	1W 28
1N514A	4000	400M	1N4789	8200	1W 28
1N515A	4500	400M	1N4790	10000	1W 28
1N516A	5000	400M	1N4791	12000	1W 28
1N517A	5600	400M	1N4792	15000	1W 28
1N518A	6300	400M	1N4793	18000	1W 28
1N519A	7000	400M	1N4794	22000	1W 28
1N520A	7800	400M	1N4795	27000	1W 28
1N521A	8700	400M	1N4796	33000	1W 28
1N522A	9600	400M	1N4797	39000	1W 28
1N523A	10500	400M	1N4798	47000	1W 28
1N524A	11500	400M	1N4799	56000	1W 28
1N525A	12500	400M	1N4800	68000	1W 28
1N526A	13500	400M	1N4801	82000	1W 28
1N527A	14500	400M	1N4802	100000	1W 28
1N528A	15500	400M	1N4803	120000	1W 28
1N529A	16500	400M	1N4804	150000	1W 28
1N530A	18000	400M	1N4805	180000	1W 28
1N531A	20000	400M	1N4806	220000	1W 28
1N532A	22000	400M	1N4807	270000	1W 28
1N533A	24000	400M	1N4808	330000	1W 28
1N534A	27000	400M	1N4809	390000	1W 28
1N535A	30000	400M	1N4810	470000	1W 28
1N536A	33000	400M	1N4811	560000	1W 28
1N537A	36000	400M	1N4812	680000	1W 28
1N538A	40000	400M	1N4813	820000	1W 28
1N539A	45000	400M	1N4814	1000000	1W 28
1N540A	50000	400M	1N4815	1200000	1W 28
1N541A	56000	400M	1N4816	1500000	1W 28
1N542A	63000	400M	1N4817	1800000	1W 28
1N543A	70000	400M	1N4818	2200000	1W 28
1N544A	78000	400M	1N4819	2700000	1W 28
1N545A	87000	400M	1N4820	3300000	1W 28
1N546A	96000	400M	1N4821	3900000	1W 28
1N547A	105000	400M	1N4822	4700000	1W 28
1N548A	115000	400M	1N4823	5600000	1W 28
1N549A	125000	400M	1N4824	6800000	1W 28
1N550A	135000	400M	1N4825	8200000	1W 28
1N551A	145000	400M	1N4826	10000000	1W 28
1N552A	155000	400M	1N4827	12000000	1W 28
1N553A	165000	400M	1N4828	15000000	1W 28
1N554A	180000	400M	1N4829	18000000	1W 28
1N555A	200000	400M	1N4830	22000000	1W 28
1N556A	220000	400M	1N4831	27000000	1W 28
1N557A	240000	400M	1N4832	33000000	1W 28
1N558A	270000	400M	1N4833	39000000	1W 28
1N559A	300000	400M	1N4834	47000000	1W 28
1N560A	330000	400M	1N4835	56000000	1W 28
1N561A	360000	400M	1N4836	68000000	1W 28
1N562A	400000	400M	1N4837	82000000	1W 28
1N563A	450000	400M	1N4838	100000000	1W 28
1N564A	500000	400M	1N4839	120000000	1W 28
1N565A					



Same day shipment. First line parts only. Factory tested. Guaranteed money back. Quality IC's and other components at factory prices.

INTEGRATED CIRCUITS

74081TL	SN74175N	.90	LM3201-5	1.60	CMOS	47	CD4529	1.50
SN7400N	SN74191N	1.25	LM3201-8	1.60	CD3401	42	CD4583	4.50
SN7400N	SN74193N	.85	LM3201-12	1.60	CD4001	25	CD4585	2.45
SN7400N	SN74204B	6.00	LM3201-15	1.60	CD4002	25	CD4018	3.00
SN7410N	SN74288A	6.00	LM3201-15	1.60	LM3001	1.90	74000	.78
SN7414N	SN74296A	1.65	LM3201-15	1.60	CD4007	25	74004	.33
SN7415N	74LS00	1.95	LM3201-15	1.60	CD4009	25	74007	.28
SN7417N	SN74LS00N	.34	LM3201-5	1.70	CD4010	53	74C14	2.10
SN7420N	SN74LS00N	.34	LM3201-8	1.70	CD4011	25	74C20	.28
SN7430N	SN74LS02N	.34	LM3201-12	1.70	CD4012	25	74C30	.28
SN7430N	SN74LS02N	.34	LM3201-15	1.70	CD4013	25	74C48	2.95
SN7433N	SN74LS04N	.39	LM3201-15	1.70	CD4017	2.00	74C74	.75
SN7440N	SN74LS04N	.39	LM3201-15	1.70	CD4018	50	74C100	2.10
SN7442N	SN74LS04N	.39	LM3201-15	1.70	CD4020	1.35	74C160	2.00
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4021	2.00	74C221	2.75
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4022	25	74C205	10.40
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4024	1.20	74C277	2.00
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4025	32		
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4026	3.85		
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4027	55	8095	.75
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4028	55	8096	.75
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4029	2.25	8097	.75
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4030	2.25	8098	.75
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4031	2.25	8099	1.25
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4032	2.25	8100	1.25
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4033	2.25	8101	1.25
SN7445N	SN74LS04N	.39	LM3201-15	1.70	CD4123	2.25	8191	1.25

COMPLETE ALARM CLOCK

- * 4 Digits 0.5" LED with brightness control
- * 12 Hour display with AM/PM indication
- * True 24 hour alarm with repeatable snooze
- * Power failure indication for power interrupt



MODEL EC 400

(Not A Kit)

Only \$22.50

ON SALE \$17.50 ea.

NEW CLOCK KITS!



MODEL OC1032

JUMBO DIGITS
ALARM CLOCK
1.2" Bright Yellow
Color Readouts

Features: 12/24 Hour Display, 24 Hour Alarm Set, 10 Min Snooze Switch, AM/PM Indicator

Kit Includes: Woodlike Color Plastic Case, 4 Digit 1.2" Neon Display with AM/PM, TMS 3834 Alarm Chip, 2 pcs. double sided PC Boards, 16 transistors, all other components, Transformer and speaker

SPECIAL \$35.90

MODEL OC1030

4 DIGIT
ALARM CLOCK KIT
0.5" Green Color
Readouts


Features: 12/24 Hour Displays, 24 Hour Alarm Set, 10 Min Snooze Switch, AM/PM Display.

Kit Includes: Orange Color Plastic Case, 0.5" LD8132 Green Color Readouts PC boards with transformer, all electronic parts with speaker.

Only \$28.50

THE MOST POPULAR

MM5314 KIT

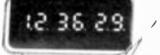

WITH A NEW CASE!!

Features: 12/24 Hour Display

50/60 HZ Input 6 Digits Readout

Kit Includes: Grey Color Plastic Case MM5314 Clock Chip PC Boards and Transformer, 6 Green Color 0.3" Tube Readouts, All other transistor Drivers and other Components.

Special Only \$19.95 ea.

MODEL CT7001



Drive 6

Fairchild FND

0.5" Red LED

with MONTH & DATE

50/60HZ and ALARM

Only \$28.50 ea.

CASE ONLY \$6.00 EACH

COMPUTER KEYBOARDS



Standard Teletype Keyboards with gold plated contact switches. All switches are independent and allow you to connect into any form of output.

Only \$22.50

ASCII KEYBOARD ENCODER CHIP

G1 AY-53600

40 pin DIP package, 4 level, 10 BITS per level, encoding for up to 90 keys. Latched data outputs and control signal output, TTL compatibility for all controls.

WITH DATA ONLY \$18.50 EACH

COMPLETE ASCII DECODED KEYBOARD KIT (Using the above 64 key keyboard and the AY-5 encoder chip.) Kit includes keyboard, PC board, encoder LSI chip, TTLIC, LED, all electronic components and the instructions.

ONLY \$54.50

VOLTAGE REGULATORS

ALL POSITIVE OUTPUT

FAIRCHILD 78 MG

Adjustable Volt Regulators

500MA 5V 30V Output

with data ONLY \$1.60 ea.

LM340T 1 amp Output

5V, 6V, 9V, 12V, 15V, 24V

Positive only \$1.10 ea.

MINI SIZE REGULATOR


in TO-92 package

78L05, 78L012 by Fairchild

Low Power 100MA Output

Only \$0.80 ea.

LM309K 5V 1amp TO-3 \$1.00 ea.

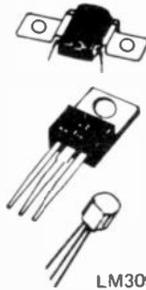

3 AMP POWER SUPPLY

UA723 REGULATED

Output 5V and 12V


input 110AC



only \$19.50

*Postage for this item

\$2.50

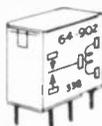

12 VDC Relay

SPDT 4 amp

\$1.25 ea.

MINI SIZE
12V RELAY

DTDT 500

\$1.40 ea.



6V GAMPH YUASA

Wet Rechargeable Battery

\$7.50 ea.

BRAND NEW

*** Add 50c Postage for This Item



AC ADAPTERS

110V AC Input

4.5V 100MA 6V 100MA

9V 100MA 12V 100MA

\$2.85 each

12V 150MA AC Output \$2.00 ea.



TRANSFORMERS

110V input

12-0 12V 1amp \$2.25 ea.

12V CT 500MA

with one group 165V \$1.50 ea.

C 3 12 24V 500MA \$2.75 ea.



NI-Cd FAST CHARGE

Rechargeable AA Size

BATTERIES

BY SANYO

ALL BRAND NEW

\$1.25 each 4 for \$4.50



AUTO ALARM KIT



The Crim-Lighter Auto Alarm is an electronic, self controlled auto protection system originally mounted within the glove box of an automobile.

Two minutes after turning off the ignition the alarm automatically turns itself "on". When the auto is reentered, the horn will sound after a 0.45 second entry delay. The automobile owner, by inserting the ignition key, will activate the alarm. Once activated the alarm will sound for two minutes before automatically turning off. The alarm then resets and is ready to again protect the vehicle from unwanted entry.

FEATURES: Simple installation, 5 wires. Automatically "turns on" when auto is parked. Adjustable entry time. Extended exit time to allow for unruhsh exit from vehicle. Numerous applications include protection of boats, campers, trailers, motorcycles, trucks. Cannot be deactivated by "hot wiring" an auto. Can not be turned off without ignition key. Neg atter ground only.

ONLY \$10.00 per kit Completed Unit \$16.00

LED READOUTS



Fairchild FSC 8000

0.8 Red LED 3, Digits

with AM-PM

Direct Drive by MM 5318 or Fairchild 3817

\$10.50 ea.



JUMBO LED

Fairchild FND 800

0.8 Common Cathode

Red Color

ONLY \$3.50 ea.

MAN 74	Red	\$1.00
MAN 84	Yellow	\$1.50
HP 0.3	Red	\$1.20
DL 747	RZ D	\$2.50
DL 727	Double D q t	\$2.50
DL 707	0.3 Red	\$1.30
FND 70	0.25 Red	\$0.60
FND 503	0.5 Red	\$1.60
FLV 50	Submini Red	\$0.15 ea.
FLV 209	Mini Red	\$0.15 ea.
	Jumbo Red	\$0.15 ea.
	Jumbo Green	\$0.25 ea.
	Jumbo Orange	\$0.25 ea.

50 UA PANEL METER

First designed for metal Finder Scaled from 0 10 but can be erased and your own scale put on too. Brand new in box. Only \$3.80 ea.

150UA METER


only \$1.50 ea.



QUAD VOLUME CONTROL

(JOY STICK) 4 100K Volume pot none unit very resistance pot part com to the angle of the stick. Perfect for electronic games or model remote control.

only \$8.50

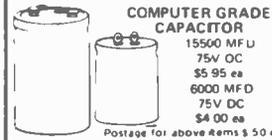

COMPUTER GRADE CAPACITOR

15500 MFD

75V OC

\$5.95 ea.

6000 MFD


75V DC

\$4.00 ea.

Postage for above items \$ 50 ea.

ELECTRONIC SWITCH KIT

CONDENSER TYPE

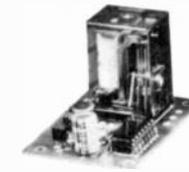

Touch on Touch Off

use 7473 I.C.

and 12V relay

\$5.50 each



FM WIRELESS MIC KIT

Transmit range up to 500ft.

Easy to assemble

\$4.50 each

Sub-Mini Size
Condenser Microphone



\$2.50 each

5W AUDIO AMP KIT



USE 2 LM380

with Volume Control

POWER SUPPLY 6VDC

only \$5.00 ea.

SAE DIP SWITCHES



Part No 1004 692 4XSPST SW

1008 692 8XSPST SW

4 Toggle SPST Switches on a Mini-DIP

(8 pins) Only \$1.50 ea.

8 Toggle SPST Switches on a DIP

(16 pins) Only \$2.60 ea.



SPDT On None On \$1.30 ea.

DPDT On None On \$1.50 ea.



8 positions \$1.25 ea.

10 positions \$2.15 ea.

12 positions \$2.50 ea.




COLORFUL SUB MINI PUSH BUTTON SWITCH

Nor Open Contact

Color: Red, Green, Yellow Black


4 for \$1.00

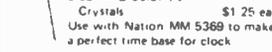

1MHZ Computer Crystals \$4.25 ea.

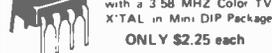3.58 MHz Color TV Crystals \$1.25 ea.

Use with Nation MM 5369 to make a perfect time base for clock.



NATIONAL MM 5369 17-STAGE PROGRAMMABLE OSC/DIVIDER generate A

60 Hz reference Frequency with a 3.58 MHz Color TV

X'TAL in Mini-DIP Package

ONLY \$2.25 each



COMPLETE 60HZ DC TIME BASE KIT

Kit includes MM5369, X'TAL, capacitor, resistor and PC board

SPECIAL PRICE ONLY \$5.25 each



THUMBWHEEL TRIM POTS

VALVE 300R, 2K, 25K, 5K, 10K, 12K, 50K, 1M

Special Offer: 5 for \$1.00



Big Sale On Computer I.C.

INTEL C8008 CPU \$9.95 ea.

INTEL 1702A ERASABLE PROM 9.50 ea.

NATIONAL 2102 1K RAM 1.99 ea.

TI TMS4030 4K RAM 5.50 ea.

Limited Quantity of the Above Parts

MINIMUM ORDER \$10.00 California residents add 6% sales and 1.50 to cover postage and handling

Out of state and overseas countries add \$2.50

SEND CHECK OF MONEY ORDER TO



FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250

For more information please call (213) 679-5162

STORE HOURS 10 7 Monday - Saturday

11/76



DELTA ELECTRONICS CO.

P.O. BOX 2, AMESBURY, MASS. 01913



REVERSIBLE SYNCRO-TAPE DRIVE MOTOR
115v 1.25A 60Hz. This is a capacitor start motor (10 mfd 370 vac 60 Hz oil capacitor supplied) The shaft speed is 3250 rpm and the shaft dia is .315 x 1 inch long. It is equipped with lubricated-for life, sealed ball bearings. The size is 5.125 x 3.25 dia. Front mounting is 2.85x2.85 They are currently selling for \$60.00...our price..

STOCK NO. 6421R \$12.95 2/ 24.00
METER r/hr



This is a 0 - 20 micro amps meter. The meter scale is 0 to .5. This attractive meter is encased in clear plastic. Mounting is a 2.05 dia hole, the face dia is 2.65. The screw locations are 120% of each other.

STOCK NO. 5447R \$2.50 3/ 6.00



SOLAR CELLS

See how the sun's energy can be converted into fun electricity..46v 500ma. This item is usually sold for \$18.00 elsewhere.....

STOCK NO. 1001R \$8.95 3/ 24.00
CRYSTAL



4.000,000 MHz. CR-18A/L. The crystal can is .75x.75. The pins are .05 thk and the mounting spacing is .50. STD. STOCK NO. 1000R \$3.95 2/ 20.00
CRYSTAL HOLDER STD.

STOCK NO. 9169R 5/ 1.00



BATTERIES

AA 1.5v Penlight batteries are great for equipment and alike. Also advantages for the hobbyist. All batteries are guaranteed before shipment. Most all AA batteries are sold competitively for 2/1.59.....

but.....DELTA'S.....

Send for latest free catalog. Minimum order \$5, phone orders welcome: (617) 388-4705. Include sufficient postage; excess will be refunded. BANKAMERICARD & MASTERCARD welcome. ALL numbers needed for processing. Minimum charge \$15.

CIRCLE 68 ON FREE INFORMATION CARD

World's Lowest IC Prices

* SPECIAL PRICES *

MEMORIES					
74152	.90	HIGH SPEED	4007	.16	
74155	.60	74H00	4008	.70	
2102	1.50*	74H01	4011	18**	
Proms		74H04	4012	18**	
82S23 S123	1.95*	74H10	4015	30**	
TTL		74H11	4016	35**	
7400	12*	74H40	4019	.70	
7402	14	74H51	4020	.90	
7403	14**	74H52	4021	.95	
7404	16**	74H74	4023	16**	
7407	20	74H103	4024	.75	
7410	12**	74H106	4025	20**	
7420	12**		4027	.40	
7427	25	74181	4028	.60	
7432	25	74190	4030	.35	
7437	20	74191	4040	.95	
7438	20**	74192	4042	.60	
7440	12**	74193	4043	.75	
7441	65**	74194	4044	.70	
7444	45	74198	4049	35**	
7445	45	9602	4050	35**	
7447	75	9300	4056	.65	
7450	14	9312	4068	.35	
7451	14**		4069	.16	
7473	22	SCHOTTKY	4071	.16	
7474	23	74501	4073	.16	
7475	40**	74502	4075	.16	
7480	40**	74503	4516	.85	
7483	55	74538	4528	.75	
7493	50	74585	4585	.85	
7495	49	745113	74LS175	1.50*	LINEARS
74107	29	745140	74LS221	1.50*	NE536T 2.75
74109	30	745153	74LS251	1.50*	NE555V 43
74116	1.50	745172	74LS253	1.50*	NE556A 90
74123	45**	745174	74LS257	1.50*	1456V 75
74141	80**	745175	74LS258	1.50*	1456V 52
74145	75	745181	CMOS		566V 1.25
74150	60**	745187	4001	16**	567V 1.35
74151	60	745197	4002	16**	540L 2.00
		745257	4006	90	

Order Minimum \$10.00. Add \$1.00 shipping and handling charge per order. California residents add 6% sales tax. All orders shipped First Class within 24 hours.

Order the famous lasix 6 volume Programmed Learning Course "Microcomputer Design is a Snap" for \$99.50 and receive a special \$10.00 credit on any group of IC's.

Satisfaction 100% guaranteed

C.O.D. Orders Phone (day or night) 408-354-1448

ELTRON

PO BOX 2542 D
Sunnyvale, CA 94087

Free monthly catalog—Just send us your name and address

CIRCLE 55 ON FREE INFORMATION CARD

ROCKWELL A4001 I.C.

ELECTRONIC SLIDE RULE SCIENTIFIC CALCULATOR KIT !!

Kit Includes



Rockwell A4001 IC
HP 9 Digit LED Readouts
Complete Keyboard with Case
PC Board with all Electronic Parts
Instructions and Batteries

SPECIFICATION

- 9 digit HP Red Led Displays
- 8 digits capacity for data entry or results (10⁸ ~ 10⁸)
- Full floating point
- Dome keyboard for excellent response and preventing double entry input

BASIC FUNCTION

- Algebraic mode operation
- Constant operations
- Repeat Operations
- Chain operations
- Change sign operation
- Display and Y register exchangeable
- One accumulating memory
- Display and memory exchangeable

SPECIAL FUNCTION

- Trigonometric functions (sin, cos, tan)
- Inverse trigonometric functions (sin⁻¹, cos⁻¹, tan⁻¹)
- Radian or degree selectable
- π constant
- Logarithms (ln, log)
- Anti logarithms (e^x)
- Power functions (y^x)
- Reciprocal (1/x)
- Square root (√x)
- Display recall

AC adapter for the unit
\$4.50 ea.
*postage \$1.50 per unit.

ONLY \$24.⁵⁰

Dimension 32.5mm(H) x 77mm(W) 145mm (L)
1.9 32 in (H) x 3.1 32 in (W) x 5.23 32 in (L)

STEREO PRE AMP I.C. MC 1303L



0.27" 7 segment
LED, Latch and
Driver built in
one chip
ONLY \$4.00 ea.



SPECIAL SALE ON I.C. SOCKETS

14 PIN SOLDER TYPE.
10 for \$1.89
16 PIN SOLDER TYPE
10 for \$2.25

NEW ALARM CLOCK CHIPS

NE555 555 timer, 24 pins, 1.5V, 100KHz, 100KHz, 100KHz, 100KHz
ONLY \$3.50 ea. (311, 24 ea)

FEATURE	OPTION	PROGRAMMABLE OPTIONS				PART
		AA	AB	AC	AD	
Reg. Frequency	88 KHz 98 KHz	x	x	x	x	
Time D. plus	12 H. 24 H.	x	x	x	x	
Digital Repeat	Alarm Counter Date Counter Minute Counter Set and 1 st	x	x	x	x	
Alarm Sine	1 st or DC Level	x	x	x	x	
Alarm Output	Modulated 20KHz Non-Modulated	x	x	x	x	
Alarm of P. over Failure	ON OFF	x	x	x	x	
Strobe out for Alarm	V. 1 D. plus V. 2 D. plus	x	x	x	x	
AM or PM Indication	Off during time display D. display at all time	x	x	x	x	

NUMERIC DISPLAY WITH LOGIC TIL 308



ONLY \$1.00 each


Two Preamplifiers
built in a 14 PIN DIP
Channel Separation=
60dB at 10 KHZ
w/Short-Circuit-
Proof Design



1014 PLASTIC CLOCK CASE

Good for clock
or other
instrument
\$4.00 each

5V REED RELAY

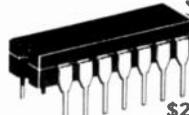

DPST Normal
Open in a DIP
Package

\$2.25 each / 2 for \$4.00

MINIMUM ORDER \$10.00 California residents add 6% sales and 1.50 to cover postage and handling
Out of state and overseas countries add \$2.50

SEND CHECK OR MONEY ORDER TO

FORMULA INTERNATIONAL INC.

12603 CRENSHAW BOULEVARD • HAWTHORNE, CALIFORNIA 90250

For more information please call (213) 679-5162

STORE HOURS 10-7 Monday - Saturday

11/76

UNIVERSAL BREADBOARD
Silver plated copper circuit board
1-1/4" x 5-1/2" x 1/2" rows of 27
holes for DIP IC's - space for
transistors, resistors & capacitors.
Versatile and simple for bread-
boarding IC circuits \$1.50 ea.

FREE CATALOG AVAILABLE ON REQUEST INCLUDES
RESISTORS +1% & +5%, TANTALUM CAPACITORS,
POWER SUPPLY KITS, CLOCK KITS, TOOLS, RESIS-
TOR & CAPACITOR KITS & MISCELLANEOUS DEVI-
CES

NOVEMBER SPECIALS

TTL	LINEAR	MEMORIES	DISPLAYS
7406 \$.17	301 \$.22	1103 \$.95	DL10A \$1.79
7474 .23	309K .99	1702 8.95	MAN5 1.59
7486 .33	311 .79	2102 1.49	MAN8 1.69
7490 .39	340T-5V .99	5203 8.95	LED's
74107 .59	723 .39	5260 .95	JUMBO CLEAR .13
74123 .29	741 .25	5261 .95	JUMBO ORANGE .15
9602 .59	1414 1.69	F93410 1.39	MV50 10/\$1.00

7400	.13	7451	.17	74153	.89
7401	.16	7453	.17	74154	1.20
7402	.15	7454	.17	74155	.97
7403	.15	7460	.35	74156	.97
7404	.16	7464	.35	74157	.99
7405	.19	7465	.30	74158	1.79
7406	.20	7470	.30	74160	1.23
7407	.28	7472	.35	74161	.97
7408	.18	7473	.28	74162	1.39
7409	.19	7474	.28	74163	1.09
7410	.16	7475	.49	74164	.99
7411	.25	7476	.30	74165	.99
7413	.43	7483	.68	74166	1.25
7414	.65	7485	.88	74170	2.10
7416	.35	7486	.40	74173	1.49
7417	.35	7489	2.25	74174	1.23
7420	.16	7490	.43	74175	.97
7422	.30	7491	.75	74176	.89
7423	.29	7492	.48	74177	.84
7425	.27	7493	.48	74180	.90
7426	.26	7494	.78	74181	2.45
7427	.29	7495	.79	74182	.79
7430	.20	7496	.79	74184	1.90
7432	.23	74100	.98	74185	2.20
7437	.25	74105	.44	74187	5.75
7438	.25	74107	.37	74190	1.15
7440	.15	74121	.38	74191	1.25
7441	.89	74122	.38	74192	.95
7442	.59	74123	.65	74193	.85
7443	.73	74125	.54	74194	1.25
7444	.73	74126	.58	74195	.74
7445	.73	74132	.89	74196	1.25
7446	.81	74141	1.04	74197	.73
7447	.79	74145	1.04	74198	1.73
7448	.79	74150	.97	74199	1.69
7450	.17	74151	.79	74200	5.45

IC SOCKETS
Solder Tail - low profile

8 pin	5	17	24 pin	.42
14 pin		.20	28 pin	.59
16 pin		.22	40 pin	.69
18 pin		.29		

WIRE WRAP - gold plate

14 pin	.49
--------	-----

CMOS

4000A	.26	4018A	1.39	4066A	.89
4001A	.25	4020A	1.72	4068A	.44
4002A	.25	4021A	1.18	4069A	.44
4006A	1.35	4022A	.94	4071A	.26
4007A	.26	4023A	.25	4072A	.35
4008A	1.52	4024A	.89	4073A	.39
4009A	.57	4025A	.25	4075A	.39
4010A	.54	4027A	.59	4078A	.39
4011A	.29	4028A	.98	4082A	.35
4012A	.25	4030A	.44	4518A	1.56
4013A	.45	4035A	1.27	4518A	1.56
4014A	1.27	4040A	1.39	4585A	2.10
4015A	1.27	4042A	.49		
4016A	.48	4049A	1.57		
4017A	1.01	4050A	.59		

74C00	.19	74C74	1.04	74C162	2.49
74C02	.26	74C76	1.34	74C163	2.66
74C04	.44	74C107	1.13	74C164	2.66
74C08	.68	74C151	2.62	74C173	2.22
74C10	.35	74C154	3.15	74C195	2.26
74C20	.35	74C157	1.76	80C95	1.15
74C42	1.61	74C160	2.48	80C97	.96
74C73	1.04	74C161	2.49		

RESISTOR KIT

Carbon film - 5%
1/4w - 1/2 watt
455 resistors, 48 values
supplied in a 15 drawer
60 compartment storage
cabinet. Table or wall
mount. Ready to use



14 WATT 0155
12 WATT 0156

\$24.95 ea.

RESISTOR ASSIGNMENT
RIBBONS: - \$2.00 SHIPPING & HANDLING
SHIPPING VIA UPS OR PARCEL POST

R	QTY	R	QTY	R	QTY
15	5	880	10	47K	10
22	5	10K	20	68K	10
6.8	5	15K	10	100K	20
10	10	22K	20	150K	10
15	5	27K	10	200K	10
22	5	33K	10	270K	5
33	5	39K	10	330K	10
47	10	47K	20	470K	10
60	5	68K	10	500K	10
100	10	10K	20	700K	20
150	10	15K	10	1.5M	5
220	10	22K	10	2.2M	5
270	5	27K	10	3.3M	5
330	10	33K	20	4.7M	5
470	20	39K	10		

OTHER AVAILABLE RESISTOR KITS
For additional information write for free catalog.

180 carbon film resistors - 5% 1/4 or 1/2 watt
15 each of 12 values most needed for solid
state electronics. 1st quality resistors
in a styrene utility box with color code chart. **\$9.95**

1395 carbon film resistors - 5% 1/4 watt 03255 or 1/2 watt 03505
105 values with quantities of each determined
by typical usage **\$60.00**
supplied in a 36 drawer, 144 compartment
steel cabinet with plastic drawers.

2200 carbon film resistors - 5% 1/4 watt 04255 or 1/2 watt 04505
50 resistors per value, 44 values
supplied in a 15 drawer, 60 compartment
steel cabinet with plastic drawers **\$74.95**

2610 carbon film resistors - 1/4 watt 05255 or 1/2 watt 05505
150 values with quantities of each determined
by typical usage. **\$107.00**
supplied in a 58 drawer, 158 compartment
steel cabinet with plastic drawers

400 metal film resistors - 1% 1/4 watt 11251
RN 60 temp coeff - 50 PPM/C
10 resistors per value, 40 values
supplied in a 15 drawer, 60 compartment
steel cabinet with plastic drawers **\$54.95**

TANTALUM CAPACITOR KIT \$19.95

1st quality capacitors in a durable styrene
utility box - with color code charts

330	10	22K	10	10	25V
47	10	6.8K	10	10	25V
22	10	33K	10	10	50V
10	10	10K	10	10	50V

LINEAR CIRCUITS

304	Neg V Reg TO-5	.80
305	Pos V Reg TO-5	.71
307	Op AMP (super 741) mDIP TO-5	.26
308	Micro Pow Op Amp mDIP TO-5	.89
309K	5V 1A regulator TO-1	1.35
310	V Follower Op Amp mDIP	1.07
311	Hi-Pre V Comp mDIP TO-5	.95
319	Hi Speed Dual Comp DIP	1.13
320J	Neg Reg 5, 12, TO-220	1.39
320K	Neg Reg 5, 12 TO-3	1.39
322	Precision timer DIP	1.70
324	Quad Op Amp DIP	1.52
339	Quad Comparator DIP	1.58
340K	Pos V Reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-1	1.69
340T	Pos V Reg (5V, 6V, 8V, 12V, 15V, 18V, 24V) TO-220	1.49

LOW POWER

74L00	.29	74L51	.29	74L90	1.40
74L02	.29	74L55	.29	74L91	1.20
74L03	.23	74L71	.29	74L93	1.50
74L04	.29	74L72	.45	74L95	1.50
74L06	.29	74L73	.56	74L98	2.25
74L10	.29	74L74	.56	74L164	2.25
74L20	.29	74L78	.75	74L165	2.30
74L30	.29	74L85	1.09		
74L42	1.39	74L86	.65		

THESE DISCOUNTS APPLY TO TOTAL OF ORDER - SPECIALS INCLUDED

10% OFF ON ORDERS OVER \$25
15% OFF ON ORDERS OVER \$100

LARGE QUANTITY PRICING AVAILABLE ON REQUEST
PLEASE SPECIFY ITEM AND QUANTITY

LOW POWER SCHOTTKY

74LS00	.36	74LS32	.38	74LS95	2.09
74LS02	.36	74LS40	.45	74LS107	.59
74LS04	.36	74LS42	.40	74LS164	2.20
74LS08	.36	74LS54	.59	74LS193	2.20
74LS10	.38	74LS70	1.30	74LS197	2.20
74LS12	.36	74LS93	1.30		

MEMORIES

1101	256 bit RAM MOS 16 pin	1.39
1103	1024 bit RAM MOS dynamic 18 pin	1.95
1702A	2048 bit PROM static electrically programmable UV erasable 24 pin	10.95
2102	1024 bit RAM static 16 pin	1.95
5203	2048 bit PROM static electrically programmable UV erasable 24 pin	10.95
5260	1024 bit RAM MOS dynamic 16 pin	1.95
5261	1024 bit RAM MOS dynamic 16 pin	1.95
7489	64 bit ROM TTL 16 pin	2.25
82523	256 PROM-SCHOTTKY 16 pin	3.69
F93410	256 bit RAM bi-polar 16 pin	1.95
74187	1024 bit ROM TTL 16 pin	5.75
74200	256 bit RAM tri-state 16 pin	5.45

CLOCK KIT \$14.95

6 Digits (NS71L)
MM5314 Clock Circuit
2 PC Boards Clock & Display
All Transistors, Resistors
Capacitors & 3 switches with Schematic
& Instructions

370	ACC/Squelch AMPL DIP	1.20
372	41-IF Strip detector DIP	2.93
373	AM FM/5B Strip TO-5	2.42
176	Prm V Reg mDIP	.68
380	2w Audio Amp DIP	1.30
380-8	bw Audio Amp mDIP	1.25
381	to Noise Dual preamp DIP	1.75
382	to Noise Dual preamp DIP	1.75
531	High Slew rate Op Amp	2.95
540	Power driver TO-5	2.95
550	Pre V Reg DIP	1.02
555	Timer mDIP	.45
556A	Dual 555 Timer DIP	1.19
560	Phase Locked Loop DIP	3.39
562	Phase Locked Loop DIP	3.39
565	Phase Locked Loop DIP TO-5	1.18
566	Function Gen mDIP TO-5	1.95
567	Tone Decoder mDIP	1.95
709	Operational AMP TO-5 or DIP	.26
710	Hi Speed Volt Comp DIP	.35
711	Dual Differential Compar DIP	.26
723	V Reg DIP	.62
733	DHil. video AMPL TO-5	1.02
739	Dual Hi Per Op Amp DIP	1.07
741	Comp Op Amp mDIP TO-5	.32
747	741 Dual Op Amp DIP or TO-5	.71
748	Freq Adj 741 mDIP	.35
1304	FAM Multis Stereo Demod DIP	1.07
1307	FAM Multis Stereo Demod DIP	.74
1456	Op Amp mDIP	1.83
1458	Dual Comp Op Amp mDIP	.62
1800	Stereo multiplexer DIP	2.48
3900	Quad Amplifier DIP	.49
7524	Dual core memory sense Amp	.71
7525	Dual core memory sense Amp	.90
8038	Voltage control osc. DIP	4.16
8864	9 DIC Led Cath Drive DIP	2.25
75150	Dual Line Driver DIP	1.75
75451	Dual Peripheral Driver mDIP	.35
75452	Dual Peripheral Driver mDIP	.35
75453	(151) Dual Periph Driver mDIP	.35
75491	Quad Seq Driver for LED DIP	.71
75492	Hes Digit driver DIP	.80

HIGH SPEED

74H00	.25	74H22	.25	74H61	.25
74H01	.25	74H30	.25	74H62	.25
74H04	.25	74H40	.25	74H74	.39
74H08	.25	74H50	.25	74H101	.58
74H10	.25	74H52	.25	74H102	.58
74H11	.25	74H53	.25	74H103	.60
74H20	.25	74H55	.25	74H106	.72
74H21	.25	74H60	.25	74H108	.72

CLOCK CHIPS

MM5311	6 digit multiplexed BCD, 7 seg, 12-24 Hr, 50-60 Hz - 28 pin	4.45
MM5312	4 digit multiplexed BCD, 7 seg, lpps, 12-24 Hr, 50-60 Hz - 24 pin	3.95
MM5314	6 digit multiplexed 12-24 Hr, 50-60 Hz 24 pin	4.45
MM5316	4 digit, 12-24 Hr, 50-60 Hz. alarm 40 pin	4.95
537AA	4-6 digit, 12 hour, 60 Hz snooze alarm brightness control capability, alarm tone output - 24 pin	4.95
CT7001	6 digit, 12-24 Hr, 50-60 Hz. alarm, timer and date circuits - 28 pin	5.95

DISPLAYS

MAN1	51.95	ME1	5.29
MAN2	3.95	MS10	.12
MAN3A	.19	NS101	.12
MAN5	2.25	NS102	.15
MAN6	2.49		
MAN7	1.49		
MAN8	2.25	RED	.15
MAN6A	2.25	GREEN	.15
DL10A	2.19	AMBER	.15
FND500	1.89	CLEAR	.15
NS71L	1.39		

DISCRETE LED'S

304	Neg V Reg TO-5	.80
305	Pos V Reg TO-5	.71
307	Op AMP (super 741) mDIP TO-5	.26
308	Micro Pow Op Amp mDIP TO-5	.89
309K	5V 1A regulator TO-1	1.35
310	V Follower Op Amp mDIP	1.07
311	Hi-Pre V Comp mDIP TO-5	.95
319	Hi Speed Dual Comp DIP	1.13
320J	Neg Reg 5, 12, TO-220	1.39
320K	Neg Reg 5, 12 TO-3	1.39
322	Precision timer DIP	1.70
324	Quad Op Amp DIP	1.52
339	Quad Comparator DIP	1.58
340K	Pos V Reg (5V, 6V, 8V, 12V, 15V, 18V, 24V)	

CB testing just became a snap.



26.98500 Frequency
 0.142 SWR
 0.39 Power
 0.97 % Modulation

MODEL 388

MODEL 388X

Hickok Model 388X features a precision temperature compensated crystal oscillator with 1 ppm accuracy.

Now one unit does it all.

Hook our versatile Model 388 in line with your transmitter and instant digital readouts of a transmitter's four most important operating parameters are a turn of a switch away.

A front-panel AM Monitor Output makes scope display of modulation easy. A pushbutton selects front panel or in-line frequency input. And changing to 12V operation is easy, too.

Get your hands on the new Hickok Model 388 CB In-Line Tester. We're betting you can't let go.

The Hickok Model 388 CB In-Line Tester is one element of the modular Hickok CommLine.

HICKOK
CommLine

In stock and available from . . .

FORDHAM

RADIO SUPPLY CO., INC.
 855R Conklin St., Farmingdale, N.Y. 11735
 (516) 752-0050

YOUR ONE STOP DISCOUNT CENTER
 CB Radios • Test Equipment • Tubes • Tools • Electronic Supplies

Send for FREE 108 page catalog

CIRCLE 62 ON FREE INFORMATION CARD

INTEL 8080 CPU	\$24.50
2518-HEX 32 BIT SR	\$6.00
2102-1 1024 BT RAM	\$1.80
5200-4K DYNAMIC RAM	\$12.50
5202A UV PROM	\$12.50
MM5203 UV PROM	\$12.50
1702A UV PROM	\$12.50
5204-4K PROM	\$24.95
MINIATURE MULTI-TURN TRIM POTS	
100, 500, 2K, 5K, 10K, 100K, 200K	\$3.92/00
\$.75 each	
MULTI-TURN TRIM POTS Similar to Bourrns	
3010 style 3/16"x5/8"x1-1/4": 50, 100, 1K, 10K, 50K ohms	
\$1.50 ea.	3/\$4.00
LIGHT ACTIVATED SCR's	
TO-18, 200V 1A.	\$1.75

TRANSISTOR SPECIALS

2N3585 NPN Si TO-66	\$.95
2N3772 NPN Si TO-3	\$ 1.60
2N4908 PNP Si TO-3	\$ 1.00
2N6055 NPN Si TO-3 Darlington	\$ 1.30
2N5086 PNP Si TO-92	4/\$ 1.00
2N4898 PNP TO-66	\$.60
2N404 PNP GE TO-5	\$ 3.50
2N3919 NPN Si TO-3 RF	\$ 1.50
MPSA 13 NPN Si TO-92	3/\$ 1.00
2N3767 NPN Si TO-66	\$.70
2N2222 NPN Si TO-18	5/\$ 1.00
2N3055 NPN Si TO-3	\$.80
2N3904 NPN Si TO-92	5/\$ 1.00
2N3906 PNP Si TO-92	5/\$ 1.00
2N5296 NPN Si TO-220	\$.50
2N6109 PNP Si TO-220	\$.55
2N3638 PNP Si TO-5	5/\$ 1.00
2N6517 NPN TO-92 Si	3/\$ 1.00

C/MOS (DIODE CLAMPED)

74C02-.25	4016-.50	4035-1.75
74C10-.25	4017-1.30	4042-1.60
4001-.25	4018-1.40	4047-2.60
4002-.25	4019-.60	4049-.70
4006-1.60	4022-1.20	4050-.70
4007-.25	4023-.25	4055-1.20
4009-.60	4024-1.25	4066-1.20
4010-.60	4025-.25	4071-.30
4011-.25	4027-.65	4077-.70
4012-.25	4028-1.50	4081-.35
4013-.50	4029-1.75	4076-1.20
4015-1.40	4030-.90	

LED READOUTS

FND 500-5" C.C.	\$1.95
HP 7740-3" C.C.	\$1.40
MAN-7-3" C.A.	\$1.25
NS 33-3 dig. array	\$1.35
DL 747	\$2.75

Send 25¢ for our catalog featuring Transistors and Rectifiers
 145 Hampshire St., Cambridge, Mass.

PRINTED CIRCUIT BOARD

4-1/2"x6-1/2" SINGLE SIDED EPDXY BOARD 1/16" thick, unetched
 \$5.00 ea. \$5/2.00
 VECTOR BOARD 1" SPACING
 4.5" x 6" SHEET \$1.25

4-WATT IR LASER DIODE \$7.95

2N 3820 P FET	\$.45
2N 5457 N FET	\$.45
2N 4891 UJT	\$.45
TIS 43 UJT	\$.35
ER 900 TRIGGER DIODES	4/\$1.00
2N6028 PROG. UJT	\$.65

VERIPAX PC BOARD

This board is a 1/8" single sided paper epoxy board, 4 1/2"x6 1/2" DRILLED and ETCHED which will hold up to 21 single 14 pin IC's or 8, 16, or LSI DIP IC's with buses for power supply connector. \$4.00

MV 5691 YELLOW-GREEN	
BIPOLAR LED	\$1.25
MT-2 PHOTO TRANS	\$.60
RED, YELLOW, GREEN OR	
AMBER LARGE LED's	ea \$.20
14 PIN DIP SOCKETS	\$.25
16 PIN DIP SOCKETS	\$.28
MOLEX PINS	100/\$1.00
	1000/\$7.50
8 PIN MINI DIP SOCKETS	\$.25
10 WATT ZENERS 3.9, 4.7, 5.6, 8.2, 12, 15, 18, 22, 100, 150 or 200V	ea. \$.60
1 WATT ZENERS 4.7, 5.6, 10, 12, 15, 18 OR 22V	ea. \$.25

Silicon Power Rectifiers

PRV 1A	3A	12A	50A	125A
100	06	14	30	80
200	07	20	35	115
400	09	25	50	140
600	11	30	70	180
800	15	35	90	230
1000	20	45	110	275

SILICON SOLAR CELLS

2 1/2" diameter
 5V at 500 ma. . . . \$5.00 ea., 6/\$27.50

REGULATED MODULAR POWER SUPPLIES

+15 VDC AT 100ma	\$27.95
115VAC INPUT	
5VDC AT 1A, 115VAC INPUT	\$24.95
12 VDC AT 5 AMP	\$24.95
IN 4148 (IN914)	15/\$1.00

TANTALUM CAPACITORS

.22UF 35V 5/\$1.00	6.8UF 35V 3/\$1.00
.47UF 35V 5/\$1.00	22UF 35V \$.40
68UF 35V 5/\$1.00	33UF 35V \$.40
1UF 35V 5/\$1.00	30UF 6V 5/\$1.00
3.3UF 35V 4/\$1.00	100UF 35V \$.50
4.7UF 35V 4/\$1.00	150UF 15V \$.40
M7001 ALARM CLOCK CHIP	\$6.00

NATIONAL MOS DEVICES

MM1402-1.75	MM5057-2.25
MM1403-1.75	MM5058-2.75
MM1404-1.75	MM5060-2.75
MM5013-2.50	MM5061-2.50
MM5016-2.50	MM5555-4.75
MM5017-2.70	MM5556-4.75
MM5055-2.25	MM5210-1.95
MM5056-2.25	

TTL IC SERIES

74L00-.25	7441-.85	74126-.60
7400-.16	7442-.55	74150-1.00
7401-.18	7445-.75	74151-.80
7402-.18	7446-.80	74153-.79
7403-.22	7447-.69	74154-1.05
7404-.27	7448-.77	74155-1.00
7405-.27	7472-.40	74157-.75
7406-.35	7473-.40	74161-1.00
7407-.33	7474-.40	74164-1.05
7408-.25	7475-.50	74165-1.05
7409-.25	7476-.40	74173-.95
7410-.16	7480-.48	74174-1.20
7411-.25	7483-.80	74175-.95
7412-.40	7485-.88	74177-1.00
7413-.45	7486-.45	74180-1.00
7414-1.00	7489-2.00	74181-2.40
7416-.33	7490-.48	74190-1.15
7417-.33	7491-.75	74191-1.10
7420-.18	7492-.49	74192-.80
7425-.30	7493-.49	74193-.90
7426-.35	7494-.80	74194-1.25
7427-.28	7495-.80	74195-.74
7430-.16	7496-.73	74196-1.10
7432-.30	74107-.40	75324-1.75
7437-.30	74121-.39	75491-.60
7438-.30	74123-.75	75492-.60
7440-.18	74125-.60	

MINIATURE DIP SWITCHES

CTS-206-4 Four SPST switches	
in one midip package.	\$1.50
CTS-206-8 Eight SPST switches in a 16 pin DIP package.	\$2.55

ALCO MINIATURE TOGGLE SWITCHES

AY-5-1013-A30K ser./par./par./ser./universal UART.	\$6.95
MTA 106 SPDT	\$1.20
MTA 206 DPDT	\$1.70

Full Wave Bridges

PRV 2A	6A	75A
200	.95	1.25
400	1.15	1.50
600	1.35	1.75

SANKEN AUDIO POWER AMPS

Si 1010 G 10 WATTS	\$ 6.90
Si 1020 G 20 WATTS	\$13.95
Si 1050 G 50 WATTS	\$24.95

CCD 110 LINEAR 256 XI BIT SELF SCANNING CHARGED COUPLED DEVICE \$99.00

CCD 201 100 x 100 CHARGE COUPLED DEVICE	\$135.00
---	----------

LINEAR CIRCUITS

LM 309K 5V 1A REGULATOR	\$1.16
723 - 40 + 40V/V REGULATOR	\$.50
301/748 Hi Per. Op. Amp.	\$.31
320T 5, 12, 15, OR 24V NEGATIVE REG.	\$1.50
709C - Op. Amp.	\$.31
741A or 741C OP AMP.	\$.31
710 COMPARATOR	\$.35
CA 3047 Hi Per. Op. Amp.	\$1.50
340T 5, 6, 8, 12, 15, 18, 24V POS REG. TO-220	\$.95
101 OPER. AMP. HI PERFORM.	\$.75
LM 308 Oper. Amp., Low Power	\$.95
747 - DUAL 741	\$.65
556 - DUAL TIMER	\$1.00
537 - PRECISION OP. AMP.	\$1.70
LM 3900 - QUAD OP. AMP	\$1.49
LM 324 - QUAD 741	\$.50
560 - PHASE LOCK LOOP	\$2.00
561 - PHASE LOCK LOOP	\$2.00
565 - PHASE LOCK LOOP	\$1.25
566 FUNCTION GEN.	\$1.50
567 - TONE DECODER	\$2.75
LM 1310N FM STEREO DEMOD.	\$2.50
8038 IC VOLTAGE CONT. OSC.	\$3.90
LM 370 - AGC SOUELCH AMP.	\$1.15
555 - 2us - 2 HR. TIMER	\$.45
553 QUAD TIMER	\$2.50
ICD 810 OPTO-ISOLATOR	\$.80
1458 DUAL OP AMP.	\$.60
LM 380 - 2W AUDIO AMP.	\$.95
LM 377 - 2W Stereo Audio Amp.	\$2.50
LM 381 - STEREO PREAMP.	\$1.50
LM 382 - DUAL AUDIO PREAMP	\$1.50
LM 311 - HI PER. COMPARATOR	\$.90
LM 319 - Dual Hi Speed Comp.	\$1.25
LM 339 - QUAD COMPARATOR	\$1.50

TRIACS SCR'S

PRV 1A	10A	25A	1.5A	6A	35A
100	.40	1.30	.40	.50	1.20
200	.70	1.10	.75	.80	1.60
400	1.10	1.60	2.60	1.00	1.20
600	1.70	2.30	3.60	1.50	3.00

Terms: FOB Cambridge, Mass.
 Send Check or Money Order.
 Include Postage. Minimum Order \$5.00, COD'S \$20.00



SOLID STATE SALES

P.O. BOX 74D
 SOMERVILLE, MASS. 02143 TEL. (617) 547-4005

WE SHIP OVER 95%
 OF OUR ORDERS THE
 DAY WE RECEIVE THEM

CIRCLE 67 ON FREE INFORMATION CARD

LIVE IN THE WORLD OF TOMORROW... TODAY!

And our FREE 164 PAGE CATALOG is packed with exciting and unusual values in electronic, hobby and science items — plus 4,500 finds for fun, study or profit... for every member of the family.

A BETTER LIFE STARTS HERE

SUPER POWER FOR ANY AM RADIO

New antenna assist turns a tiny transistor into a tiger, has pulled in stations 1000* miles away! Just set beside radio (no wires, clips, grounding) and fine-tune Select-A-Tenna's dial to same frequency—"gangbusters"! Great for clearing weak signals in radio depressed areas, off-coast islands, crowded frequency stations. Solid state—uses no electricity, batts., tubes.

Stock No. 72,095 EH \$19.95 Ppd.
Ultra Select-A-Tenna No. 72,147 EH (*Over 1000 Mi.) \$24.95 Ppd.



NASA-CHOSEN FOR APOLLO/SOYUZ

157 mi. out in space, the Astronauts used this super 20x60 binocular (modified) to view Earth! Our biggest, most powerful for distance. Far-off objects come in big, clear & sharp to the edge through big 60mm objective lenses; 173-ft. field of view at 1000 yds. Relative brightness, 9.0. Fully coated optics; 20X spcl design eye lenses. Coated BK-7 Porro prism. Extra long All-American style with fold-down rubber eyecups. Includes case & straps.

No. 1556EH . . . (9 1/4 x 8 1/2"; 47.5 oz.) \$99.95 Ppd.
No. 1559EH . . . (4 1/2 x 6 1/4"; 19 oz.) \$29.95 Ppd.



AN ULTRA-MINIATURE AM RADIO!

It's about the size of a small matchbox—and your ear will light up when you hear it. Pulls in stations with amazing volume and clarity (number depends on locale), yet you can wear it on your key chain, conceal it in pocket or purse! Get news, sports, music wherever you go—listen to the game as you watch it at the stadium. Just insert the earplug (incl) and your directional AM mini marvel plays! Runs ab. 100 hrs. on 2 hearing aid batts (incl). A super gift!


No. 1976EH . . . (LESS THAN 1/4 OZ.!) \$14.95 Ppd.



FUEL WISER RECLAIMS HEAT


Save your 40% wasted heat to warm a basement, garage or rec room at no extra cost! Instead of going "up the chimney" it goes where you want it. Remove part of furnace exhaust pipe, slip Heat Exchanger in. At 125° fan automat. forces clean air through unit which heats to over 200°F., can be ducted to 20 ft. from unit. 110v AC. Inst.

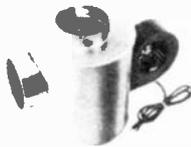No. 19,194EH . . . (5" DIA.) Shpg. 17 lb. \$121.50 FOB
No. 19,195EH . . . (6" DIA.) Shpg. 17 lb. \$121.50 FOB
No. 19,198EH . . . (7" DIA.) Shpg. 17 lb. \$121.50 FOB



GREAT FOR CHRISTMAS GIFTS!
A UNIQUE SELECTION OF MEMORABLE, LONG-LASTING GIFTS FOR ALL AGES

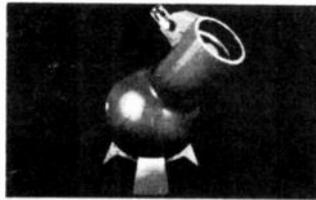
NEW! THE UNIQUE EDMUND 4 1/4" NEWTONIAN RICHEST FIELD REFLECTOR TELESCOPE.



Clearst, brightest, most spectacular wide angle views of moon, stars, comets, galaxies ever—and portable! See heavenly wonders! Sets up in seconds (precollimated, ready to use). Pop the eyepiece in, focus—and zing! 3 1/2" field of view gives you more stars in a single view than any other type 'scope! Bright, crisp, finely resolved images. For sky gazing and earth gazing! Take it anywhere (only 17", 10 lb.), easily use it over your shoulder, (has adjustable carrying strap), in your lap, on a tripod; rotate the spherical base on its own mount for use on a table, car hood. Top quality optical system features 4 1/4", f/4 parabolic primary mirror (1/4 wave, 17" F.L.); std. 28mm Kellner eyepiece (15X). No other telescope like it. Great Christmas gift—it's even brighter red!

No. 2001EH \$129.95 Ppd.
Spcl. Introductory Price! Goes to \$149.95 Dec. 25, 1976

18 HOURS' WEATHER AT A GLANCE

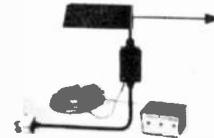

Glance at our Weather Wizard and know what to expect for the next 8-18 hrs. Be up to 80-85% accurate (better than most pro's)! Based on wind—no charts, dials—no computations! Program WW for your location once, then forecasting is automatic. Roofmounted

windvane sends pulses to indoor control unit programmed w/75 yrs. data; interprets on 3 panel lights (Unsettled; Fair; Change). Who needs TV! Incl vane, support, 60 ft. of cable, 5x4x3 1/2" control unit, instruc.

No. 72,200EH . . . (110V, 60 CYCLES) \$99.95 Ppd.


WORLD'S SMALLEST HI-FI (6 1/4 x 4 1/2 x 6")



Now, the gorgeous sound of true hi-fi w/ a receiver & sep. 8-ohm speaker (6 1/4 x 1 x 6") small enough, and priced low enough, to go in your bedroom, den, kitchen, office, shop! Great for doctors, dentists. Its wide-range rich sound compares favorably to any stereo at its price, but it's not—it's a monophonic FM radio into which you can plug a cassette, etc. (record, play back)! Hi-Fi system has Baxandall type controls (ab. 12 dB boost or cut @ 100 Hz & 10 KHz). Beautiful!

No. 72,262EH.....(120V AC) \$127.50 Ppd.

SOLAR ENERGY CUBE!

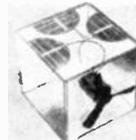

Unique demonstrator dramatically shows how sunlight converts to kinetic energy. Clear plastic Solar Energy Cube placed in the sun with its 3 highly efficient silicon solar cells powers the motor to whirl the propeller! Unit actually produces 1.5v DC,

225ma. Same cells found in our mighty panels. Speed directly related to sunlight available. Nothing to wear out! Great for executives, hobbyists, teachers.

No. 42,287EH . . . (4x4x4") \$19.95 Ppd.



MAIL COUPON FOR GIANT FREE CATALOG!

164 PAGES • MORE THAN 4500 UNUSUAL BARGAINS

Completely new 1977 edition. New items, categories, illustrations. Dozens of electrical and electromagnetic parts, accessories. Enormous selection of Astronomical Telescopes. Unique lighting and ecological items. Microscopes, Binoculars, Magnifiers, Magnets, Lenses, Prisms. Hard-to-get surplus bargains. Ingenious scientific tools. 1000's of components.

EDMUND SCIENTIFIC CO.
300 Edscorp Building, Barrington, N.J. 08007
Please rush Free Giant Catalog "EH".

Name _____
Address _____
City _____ State _____ Zip _____



COMPLETE AND MAIL WITH CHECK, M. O. OR CHARGE NO. EDMUND SCIENTIFIC CO. 300 Edscorp Building, Barrington, N.J. 08007

How Many	Stock No.	Description	Price Each	Total

PLEASE SEND GIANT FREE CATALOG "EH"

Charge my American Exp BankAmericard Master Chg

Interbank No. _____

My Card No. is _____

Card Expiration Date _____

30-DAY MONEY-BACK GUARANTEE.
You must be satisfied or return any purchase in 30 days for full refund.



Add Handling Charge \$1.00
 I enclose check money order for TOTAL \$ _____

Signature _____

Name _____
Address _____
City _____ State _____ Zip _____

Riley really rallied to our "rally 'round the tab!"

Our 1976 "rally 'round the tab" award program is under way, and a lot of dealers and technicians are already collecting awards ranging from coffeemakers to camping gear.

You can start collecting, too. All you have to do is tear off the tab—the end flap of Sylvania receiving tube boxes with the Waltham, Third Ave. or Broadway address on it.


And save color picture-tube serial labels, too. They're worth the equivalent of 20 receiving tube tabs. (You'll find the label on the upper left-hand corner of every carton.)

Then just pick the awards you want from over 300 items in the official catalog and drop your order in the mail. Keep in mind, the program ends at midnight November 30th, 1976.

You can get your catalog, order forms and mailing kit from your local Sylvania Distributor or from Sylvania Award Headquarters, P.O. Box 4000, Fenton, Missouri 63026.

Start your tab collection today. It's our way of helping you to live the life of Riley.

GTE SYLVANIA

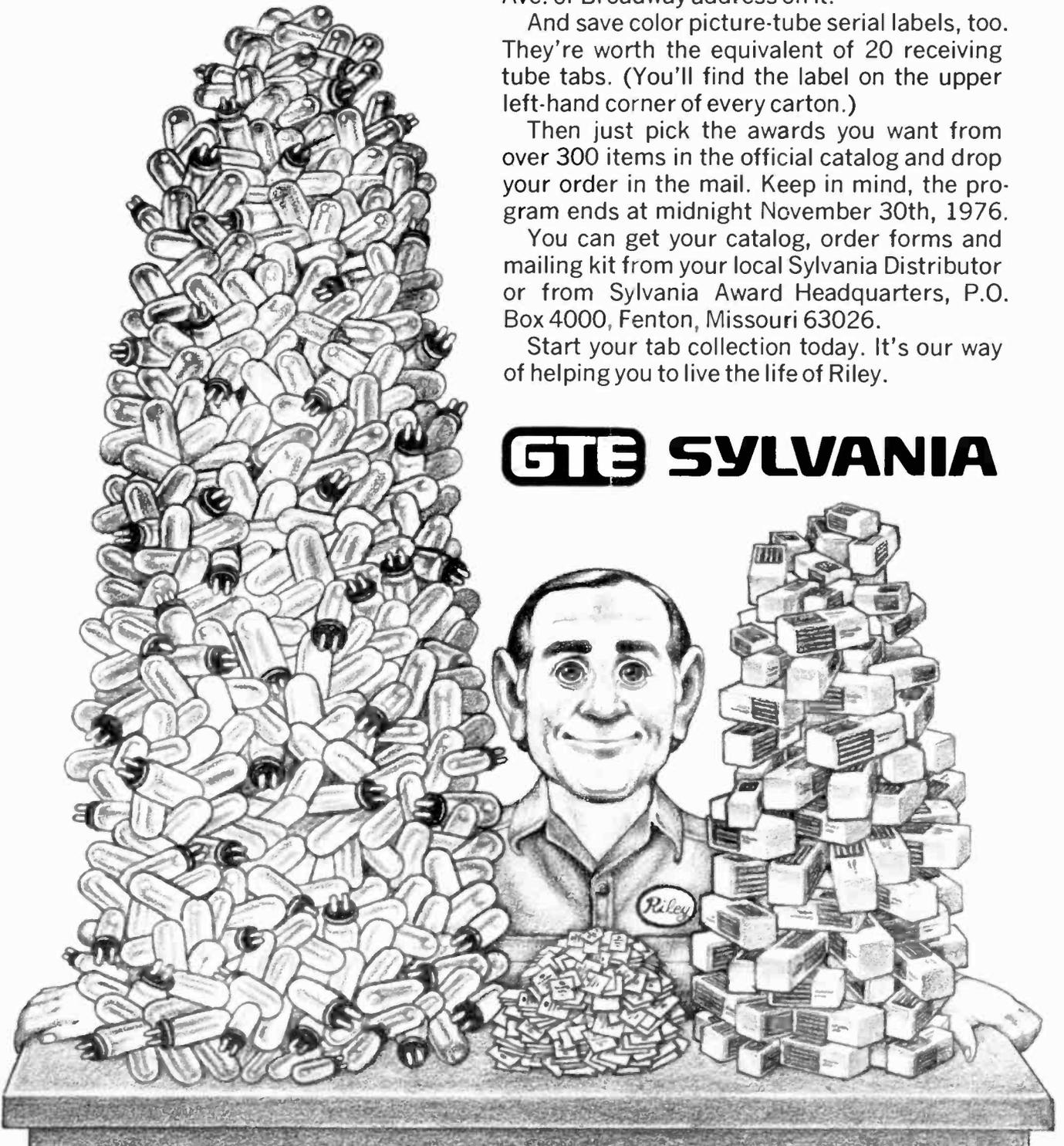

Experience is the best teacher. You might settle for any CB first time around. Understandably. A lot of people think they're all pretty much alike. But you'll soon discover that, like everything else, there are exceptions.

Ask the pros. America's long distance truckers. These guys talk CB day in and day out. And they demand the best. That's why truckers refer to the Cobra 29 as "The Diesel Mobile."

Listen to Cobra. You'll hear a big difference. Because the Cobra 29 gives you features which assure crystal clear reception. Like switchable noise limiting and blanking, to cut out practically all pulse and ignition interference. Add squelch control and RF gain and you've got exceptional — adjustable — receiver clarity. Even in the heaviest CB traffic. You also get Delta Tuning which makes up for the other guy, because even off-frequency transmitters are pulled in. Perfectly.

Talk to Cobra. And you know you're punching through. One glance at the

29's over-sized illuminated meter tells you just how much power you're punching out and pulling in. For voice modulation the DynaMike delivers at 100%. Same way with power: The 29 transmits at maximum power levels.

Sooner or later you'll get a Cobra. And you'll get engineering and craftsmanship second to none. Performance that will make your first CB seem obsolete. Reliability and durability that have set standards for the industry. Above all, you'll get power. The power to punch through loud and clear like nothing else. Because when it comes to CB radio, nothing punches through loud and clear like a Cobra.



Punches through loud and clear.

Cobra Communications Products
DYNASCAN CORPORATION
6460 W. Cortland St., Chicago, Illinois 60635

IF YOUR FIRST CB ISN'T A COBRA YOUR SECOND ONE WILL BE.



CIRCLE 3 ON FREE INFORMATION CARD