### IMPROVE YOUR AUDIO SYSTEM! **BUILD R-E's HIGH-PERFORMANCE 500-WATT AUDIO AMP** \$1.95 JAN. 1985 IN CANADA \$2.25

TECHNOLOGY -- VIDEO - STEREO - COMPUTERS - SERVICE


Build R-E's Video Switcher. Add push-button control to your video entertainment

center >

**Build R-E's Atari duplicator** and transfer your game cartridges to cassette tape

How to service your own **Videodisc** player

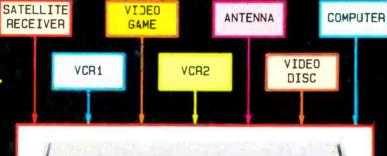What's available in add-on accessories for your satellite-TV system





How to design sinewave. squarewave, and triangular waveform generators

using

op-amps

**GERNSBACK** 

All about

thermistors

and how to

effectively

use them

Special 16-page tear-out section.

COMPUTERDIGEST

**PT056** er on Satellite TV DH#ID

Reports \* Drawing Board 303035 DKK 6420W031 14 8 DEC86 Service Clinic



### 100 MHz scope, counter, timer, multimeter: All one integrated system.

Gated measure-

scope's intensified

marker to measure

frequency, period,

width and to count

specified portions

events within

of the signal.

ments. Use the

#### 100 MHz dual time base scope.

3.5 ns risetime; sweeps from 0.5 s to 5 ns/div; alternate sweep; ±2% vertical/horizontal accuracy; vertical sensitivity to 2 mV/div @ 90 MHz.

#### 9-digit fluorescent display.

Digitally accurate readouts accompany the CRT waveform. Error messages and prompts also appear on the display.

#### Dc volts and ac

coupled true RMS volts. Measured through the Ch 1 scope input.

#### Auto-ranged, auto-averaged counter/timer.

Frequency, period, width, delay time, Δ-time, plus totalize to more than 8 million events —with 7 digits plus exponent displayed.

#### Auto-ranged

DMM. Use floating DMM side inputs with up to 5000-count resolution. Get precise readouts of average dc and true RMS voltage. Measure resistance from milliohms to gigohms.



### Now make measurements faster, easier, with greater accuracy and user confidence.

The Tek 2236 makes gated counter measurements, temperature, time, frequency, resistance and voltage measurements pushbutton easy. You see results concurrently on the 9-digit numeric readout and CRT display.

Its complete trigger system includes pushbutton trigger view, plus peak-to-peak auto, TV line, TV field, single sweep and normal modes.

At just \$2650,\* the 2236 includes the industry's first 3-year warranty on all parts and labor, including the CRT.

Integrated measurement system. 3-year warranty. 15day return policy. And expert advice. One free call gets

it all! You can order, or obtain literature, through the Tek National Marketing Center. Technical personnel, expert in scope applications, can answer your questions and expedite delivery. Direct orders include probes, operating

manual, 15-day return policy, full warranty and worldwide service back-up.

### Order toll-free: 1-800-426-2200 Extension 57

In Oregon call collect: (503) 627-9000 Ext. 57 Or write Tektronix, Inc. P.O. Box 1700 Beaverton, OR 97075





When you need to hear the action from wherever you are, Regency delivers. Our portable scanners keep you in touch with the local news. Whether it's bank hold ups, three alarm fires, weather, business, marine radio, or aircraft calls, Regency portables bring you the on the scene action. While it's happening from where it's happening . . in your neighborhood.

#### PROGRAMMABILITY WITH A CHOICE

Regency offers you two new exciting keyboard programmable hand held scanners. First there's the HX2000 20 channel, no crystal scanner. It offers UHF and VHF ranges with the important addition of 800 MHz and aircraft frequencies. And with features like search and scan, priority, liquid crystal display, and selectable search

increments, the HX2000 is a sure winner.

If you don't need the extended coverage, there's the HX1000. It let's you cover your choice of over 15,000 frequencies on 30 channels at the touch of your finger. No crystals are necessary. Six band coverage, search and scan, priority control, and a liquid crystal display with special programming messages and clock are all part of the package. And with the sealed rubber keyboard and die-cast aluminum chassis, the HX1000 is the most rugged and durable hand held on the market.

#### CRYSTAL-CLEAR

If you don't need all the features of programmables, but you want the convenience of portability, we've got you covered. Our two crystal controlled hand held scanners, the HX650 and HX750, offer

CIRCLE 261 ON FREE INFORMATION CARD

six channels, individual channel lock outs, LED channel indicators, step control, two antennas and an adaptor/charger. Both cover VHF high and low, UHF and "T" public service bands, with the HX750 offering the additional coverage of VHF aircraft band.

#### DECIDE FOR YOURSELF

Your Regency Scanner dealer would be happy to give you a free demonstration of these and other new Regency Scanners. Stop in today. Or, write Regency Electronics, 7707 Records St., Indpls., IN 46226.



7707 Records Street Indianapolis, IN 46226

### NEW! uniden<sup>®</sup> Bearcat **Products**

Communications Electronics." the world's largest distributor of radio scanners, is pleased to announce that Bearcat brand scanner radios have been acquired by Uniden Corporation of America. Because of this acquisition, Communications Electronics will now carry the complete line of Uniden Bearcat scanners, CB radios and Uniden Bandit™ radar detectors. To celebrate this acquisition, we have special pricing on the Uniden line of electronic products.

#### Bearcat® 300-E

List price \$549.95/CE price \$339.00
7-Band, 50 Channel • Service Search • Nocrystal scanner • AM Aircraft and Public Service bands. • Priority Channel • AC/DC Bands: 32-50, 118-136 AM, 144-174, 421-512 MHz. The Bearcat 300 is the most advanced automatic scanning radio that has ever been offered to the public. The Bearcat 300 uses a bright green fluorescent digital display, so it's ideal for mobile applications. The Bearcat 300 now has these added features: Service Search, Display Intensity Control, Hold Search and Resume Search keys, Separate Band keys to permit lock-in/lock-out of any band for more efficient service search.

#### Bearcat® 20/20-E

List price \$449.95/CE price \$269.00
7-Band, 40 Channel • Crystelless • Searches
AM Aircraft and Public Service bands • AC/DC
Priority Channel • Direct Channel Access • Delay
Frequency range 32-50, 118-136 AM, 144-174, 420-512 MHz
Find an easy chair. Turn on your Bearcat 20/20 and you're in an airplane cockpit. Listening to all the air-to-ground conversations. Maybe you'll pick up an exciting search and rescue mission on the Coast Guard channel. In a flash, you're back on the ground listening as news crews report a fast breaking story. Or hearing police and fire calls in your own neighborhood, in plenty of time so you can take precautions. You can even hear ham radio transmission, business phone calls and govern-ment intelligence agencies. Without leaving your easy chair. Because you've got a Bearcat 20/20 right beside it.

The Bearcat 20/20 monitors 40 frequencies from bands, including aircraft. A two-position switch, located on the front panel, allows monitoring of 20 channels at a time.

#### Bearcat® 210XL-E

List price \$349.95/CE price \$209.00
6-Band, 18 Channel • Crystalless • AC/DC
Frequency range 32-50, 144-174, 421-512 MHz.
The Bearcat 210XL scanning radio is the second generation scanner that replaces the popular Bearcat 210 and 211. It has almost twice the scanning capacity of the Bearcat 210 with 18 channels plus dual scanning speeds and a bright green fluorescent display. Automatic search finds new frequencies. Features scan delay, single antenna, patented track tuning and more.

#### Bearcat® 260-E

List price \$399.95/CE price \$249.00
8-Band, 16 Channel • Priority • AC/DC
Frequency range 30-50, 138-174, 406-512 MHz.
Keep up with police and fire calls, ham radio operators and other transmission while you're on the road with a Bearcat 260 scanner. Designed with police and fire department cooperation, its unique, practical shape and special two-position mounting bracket makes hump mounted or under dash installation possible in any vehicle. The *Bearcat* 260 is so ruggedly built for mobile use that it meets military standard 810c, curve y for vibration rating. Incorporated in its rugged, all metal case is a specially positioned speaker delivering 3 watts of crisp, clear audio.

#### NEW! Bearcat® 201-E

List price \$279.95/CE price \$179.00
9-Band, 16 Channel • Crystalless • AC only
Priority • Scan Delay • One Key Weather
Frequency range 30-50, 118-136 AM, 146-174, 420-512 MHz The Bearcat 201 performs any scanning function you could possibly want. With push button ease, you can program up to 16 channels for automatic monitoring. Push another button and search for new frequencies. There are no crystals to limit what you want to hear.

#### NEW! Bearcat® 180-E

List price \$249.95/CE price \$149.00 8-Band, 16 Channel • Priority • AC only Frequency range: 30-50, 138-174, 406-512 MHz. Police and fire calls. Ham radio transmissions. Business and government undercover operations. You can hear it all on a Bearcat 180 scanner radio. Imagine the thrill of hearing a major news event unfold even before the news organizations can report it. And the security of knowing what's happening in your neighborhood by hearing police and fire calls in time to take precautions. There's nothing like scanning to keep you in-the-know, and no better way to get scanner radio performance at a value price than with the Bearcat 180.

#### Bearcat® 100-E

The lirst no-crystal programmable handheld scanner. List price \$449.95/CE price \$234.00/SPECIAL! 8-Band, 16 Channel • Liquid Crystal Display Search • Limit • Hold • Lockout • AC/DC frequency range: 30-50, 138-174, 406-512 MHz. The world's first no-crystal handheld scanner has compressed into a 3" x 7" x 11/4" case more scanning power than is found in many base or mobile scanners. The Bearcat 100 has a full 16 channels with frequency coverage that includes all public service bands (Low. High, UHF and "T' bands), the 2-Meter and 70 cm. Amateur bands, plus Military and Federal Government frequencies. It has chrome-plated keys for functions that are user controlled, such as lockout, manual and automatic scan. Even search is provided, both manual and automatic. Wow...what a scanner!

The Bearcat 100 produces audio power output of 300

milliwatts, is track-tuned and has selectivity of better than 50 dB down and sensitivity of 0.6 microvolts on VHF and 1.0 microvolts on UHF. Power consumption is kept extremely low by using a liquid crystal display and exclusive low power integrated circuits.

Included in our low CE price is a sturdy carrying case,

earphone, battery charger/AC adapter, six AA ni-cad batteries and flexible antenna. The Bearcat 100 is in stock for quick shipment, so order your scanner today

#### Bearcat® DX1000-E

List price \$649.95/CE price \$489.00 Frequency range 10 kHz to 30 MHz.
The Bearcat DX1000 shortwave radio makes tuning in London as easy as dialing a phone. It features PLL synthesized accuracy, two time zone 24-hour digital quartz clock and a built-in timer to wake you to your favorite shortwave station. It can be programmed to activate peripheral equipment like a tape recorder to record up to five different broadcasts, any frequency, any mode, while you are as eep or at work. It will receive AM, LSB, USB, CW and FM broadcasts.


There's never been an easier way to hear what the world has to say. With the Bearcat DX1000 shortwave receiver, you now have direct access to the world.

#### Uniden® PC22-E

List price \$159.95/CE price \$99.00 The Uniden PC22 is a 40 channel AM remote mobile CB radio. It's the answer for today's smaller cars which don't always provide adequate space for mounting. Since all the controls are on the microphone, you can stash the "guts" in the trunk. The microphone has up/down channel selector, digital display, TX/RX indicator and external speaker jack. Dimensions: 5% W x 7% D x 112 H. 13.8 VDC, positive or negative ground.
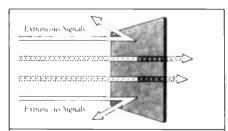
#### QUANTITY DISCOUNTS AVAILABLE

Order two scanners at the same time and deduct 1%, for three scanners deduct 2%, four scanners deduct 3%, five scanners deduct 4% and six or more scanners purchased at the same time earns you a 5% discount off our super low single unit price.



Both Bandit\* radar detectors feature EDIT\* the Electronic Data Interference Terminator that edits out talse alarm signals

#### Uniden® PC33-E

List price \$59.95/CE price \$44.00
The Uniden PC33 boasts a super-compact case and front-panel mike connector to fit comfortably in today's smaller cars. Controls: Power & Volume, Squelch; Switches: ANL, Other features of the PC33 include Graduated LED "S"/RF Meter, Digital channel indicator. Dimensions: 6" W x 6" D x 1%" H, ±13.8 VDC.

Uniden® PC55-E List price \$89.95/CE price \$59.00 The full featured *Uniden* PC55 front-panel mike connector makes installation easier when space is a factor. It has ANL, PA-CB, Channel 9 and RF Gain switches. LED "S"/RF meter, TX lite, PA & external speaker jacks. Dimensions: 6" W x 6" D x 1%" H. ±13.8 VDC.

#### **Bandit™ Radar Detectors**

Now that everyone else has taken their best shot at radar detection, the Uniden Bandit" has done them one better...with E.D.I.T.," the Electronic Data Interference Terminator that actually edits-out false alarm signals.

The Bandit 55, features a convenient brightness/ dimmer control for comfortable day or night driving, plus a handy highway/city control for maximum flexibility wherever you drive. The Bandit 95 Remote, is a two-piece modular unit that lets you mount the long-range radar antenna behind the grill, out of view. The ultra-compact control unit can then be inconspicuously tucked under the dash or clipped to the visor. Order Bandit 55-E for \$119.00 each or the Bandit 95-E Remote for \$139.00 each.

OTHER RADIOS AND ACCESSORIES
FB-E-E Frequency Directory for Eastern U.S.A....\$12.00
FB-W-E Frequency Directory for Western U.S.A...\$12.00
BC-WA-E Bearcat Weather Alert\*...\$35.00 A60-E Magnet mount mobile antenna \$35.00
A70-E Base station antenna \$35.00
Add\$3.00 shipping for all accessories ordered at the same time. Add \$3.00 shipping per scanner antenna.

#### **BUY WITH CONFIDENCE**

To get the fastest delivery from CE of any product in this ad, send or phone your order directly to our Scanner Distribution Center." Michigan residents please add 4% sales tax or supply your tax I.D. number. Written purchase orders are accepted from approved government agencies and most well rated firms at a 10% surcharge for net 10 billing. All sales are subject to availability, acceptance and verification. All sales on accessories are final. Prices, terms and specifications are subject to change without notice. All prices are in U.S. dollars. Out of stock items will be placed on backorder automatically unless CE is instructed differently. A \$5.00 additional handling fee will be charged for all orders with a merchandise total under \$50.00. Shipments are F.O.B. Ann Arbor, Michigan. No COD's. Most products that we sell have a manufacturer's warranty. Free copies of warranties on these products are available prior to purchase by writing to CE. International orders are invited with a \$20.00 surcharge for special handling in addition to shipping charges. Non-certified checks require bank clearance.

Mail orders to: Communications Electronics," Box 1002, Ann Arbor, Michigan 48106 U.S.A. Add \$7.00 per scanner, radar detector or CB or \$12.00 per shortwave receiver for U.P.S. ground shipping and handling in the continental U.S.A. For Canada, Puerto Rico, Hawaii, Alaska, or APO/FPO delivery, shipping charges are three times continental U.S. rates. If you have a Visa or Master Card, you may call and place a credit card order. Order toll-free in the U.S. Dial 800-521-4414. In Canada, order toll-free by calling 800-221-3475. WUI Telex CE anytime, dial 671-0155. If you are outside the U.S. or in Michigan dial 313-973-8888. Order today.

Scanner Distribution Center\* and CE logos are trademarks of Communications Electronics. Ad # 070184-E f Bearcat is a registered trademark of Uniden Corporation. Copyright® 1984 Communications Electronics

#### Order Toll Free . . . call 1-800-521-4414



#### **Consumer Products Division**

818 Phoenix 🗆 Box 1002 🗆 Ann Arbor, Michigan 48106 U.S.A. Call TOLL-FREE 800-521-4414 or outside U.S.A. 313-973-8888

### JANUARY 85



Electronics publishers since 1908

		Vol. 56 No. 1
SPECIAL 63 FEATURE:	Part 2. This month, we turn our attention to the CED system with a look at how a CED player works. John D. Lenk	VIDEO 91 SERVICE CLINIC A look at kit building. Jack Darr
	RF SWITCHER Gets rid of your video-switching woes and that jumble of cables at the back of your set. Bob Grossblatt ATARI GAME RECORDER	RADIO 83 COMMUNICATIONS CORNER "Phantom" power. Herb Friedman
	Part 2. This month we look at the software you need to operate the game recorder.  David A. Chan and Guy Vachon  HIGH-POWER FET AUDIO AMPLIFIER  Part 2. More on this high-performance, high-fidelity FET amplifier. Reinhard Metz	COMPUTERS  Following COMPUTER DIGEST  page 82 A machine-code development system for your ZX-81, expanding the VIC-20, Building the Bio- Box, and lots more!
V20020 01	VIDEO ELECTRONICS Tomorrow's news and technology in this quickly changing industry. David Lachenbruch SATELLITE TV	EQUIPMENT REPORTS 28 Radio-Shack Model 4 Personal Computer 31 Computer Accessories P12 Power Director
	TVRO components. Bob Cooper, Jr.  SATELLITE-TV ACCESSORIES Add-on devices. Marc Stern	DEPARTMENTS 114 Advertising and Sales Offices 114 Advertising Index 115 Free Information Card
COMPONENTS	NEW IDEAS  Multiple-outlet control circuit.  ALL ABOUT THERMISTORS  Learn more about how thermistors work, and how they are used. This month, we'll	22 Letters 94 Market Center 38 New Products 10 What's News
	look at the basics. Harry L. Trietley  DESIGNING WITH LINEAR IC's Part 8. Op-amp based sinewave, square wave, and triangular-wave generators. Joseph J. Carr  HOBBY CORNER A versatile expansion module for your	ANNUAL INDEX JANUARY—DECEMBER 1984  To present the maximum number of articles to our readers, we have not published the Annual Index as part of this issue. A 4-page brochure containing this index is available for those who need one. To get your free copy, send a stamped self-addressed envelope (legal size) to:
85	calculator. Earl "Doc" Savage, K4SDS  STATE OF SOLID STATE  Get rid of some of those house keys with an electronic lock. Robert F. Scott	Radio-Electronics Annual Index 45 East 17th Street New York, NY 10003

Radio-Electronics, (ISSN 0033-7862) Published monthly by Gernsback Publications Inc. 200 Park Avenue South. New York NY 10003. Second-Class Postage paid at New York NY and additional mailing offices. Second-Class mail authorized at Ottawa. Canada One-year subscription rate U.S. A and possessions S15.97. Canada S20.97, all other countries S23.47. subscription orders payable in U.S fundamental money order or check drawn on a U.S. A bank. Single copies S1.95.1. 984. by Gernsback Publications. Inc. All rights reserved. Printed in U.S. A POSTMASTER: Please send address changes to RADIO-ELECTRONICS, Subscription Dept. Box 2520. Boulder. CO. 80322.

A stamped self-addressed envelope must accompany all submitted manuscripts and or artivork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the

Doing division with the 4089, and more!

How to protect audio circuitry from

overloads. Robert Grossblatt

87 DRAWING BOARD

89 DESIGNER'S NOTEBOOK

loss or damage of manuscripts and or artwork or photographs while in our possession or otherwise

Any requests postmarked on or before April

30 are free. After that date there is a 50c fee.

Questions and comments about anything other

than the Index that are included with your request cannot be handled. Send them sepa-

rately to our Editorial Offices.

## Buying our reputat



Introducing a broad, new line of multifeature, cost-competitive instruments from Beckman Industrial Corporation.™

They're in stock now and as close as your local Beckman Industrial Corporation distributor. Just walk in and choose the instruments that provide the features and functions you need. Then buy them and take them home, or to work. No more ordering and waiting.

Whichever instruments you choose, you'll be buying our reputation for high quality and reliability, plus straightforward, easy operation.

And you'll be getting it all for a very afford-

able price. In fact, you'll have a hard time finding comparable instruments that offer as much functionality and quality.

All of which makes this line of instruments an exceptional value.

Choose between our 100MHz or 60MHz advanced design oscilloscopes. Both provide professional grade performance. Both also feature dual time base and three channels.

The UC10 Universal Counter measures unit count, period, time interval and frequency to 100MHz. And the FG2 Function Generator produces sine, triangle and rectangular waves up to 2MHz and at continuously variable duty cycles.

ion just got easier.



Our new circuit-powered LP10 Logic Probe is the ideal, low cost way to check TTL, DTL, HTL and CMOS signals.

The CM20 Capacitance Meter is a low cost, hand-size meter that lets you measure capacitance up to 2000 µF, easily and quickly.

The CT233 AC/DC Current Clamp enables you to use your digital multimeter to measure AC or DC current without breaking the wire.

Plus every instrument is designed, manufactured, and tested to ensure years of troublefree, reliable operation.

And whichever products you buy, service

available close to home from your local Beckman Industrial Corporation distributor.

Now it's easier than ever to buy the name with a reputation for the best quality-and value — in electronic and electrical instruments: Instrumentation Products Division, Beckman Industrial Corporation, A Subsidiary of Emerson Electric Co., 630 Puente Street, Brea, CA 92621, (714) 773-8111.

#### Beckman Industrial

© 1984 Beckman Industrial Corporation

# COVER 1



These days, the home TV has become much more than a device for viewing broadcast TV. Cable-TV, pay-TV, videocassette recorders, videodisc players, videogames, and personal computers all make use of the TV for display. That means a tangle of wires, and a constant hooking up and unhooking of connectors—unless you have a device like our RF switcher. To learn more about the switcher, including how to build it, turn to page 41.

### **NEXT MONTH**

#### **ON SALE JANUARY 17**

#### STEREO-TV

Stereo TV is here at last! Next month, we'll look at the technical standards that have been adopted to make it all possible.

#### OSCILLOSCOPE UPGRADE

Add a video-sync separator to your oscilloscope.

#### UNIVERSAL CASSETTE INTERFACE

Record your programs on cassette tape via your computer's RS-232 port.

#### **RESISTOR AND CAPACITOR SELECTION**

All about the many different types of resistors and capacitors, and when and where each type should be used.

#### **AND LOTS MORE!**

#### Radio-**Electronics**

Hugo Gernsback (1884-1967) founder M. Harvey Gernsback, editor-in-chief Larry Steckler, CET, publisher

#### EDITORIAL DEPARTMENT

Art Kleiman, editor

Brian C. Fenton, technical editor

Carl Laron, WB2SLR, associate editor

Robert A. Young, assistant editor

Julian S. Martin, editorial associate

Byron G. Wels, editorial associate

lack Darr, CET, service editor

Robert F. Scott,

semiconductor editor

Herb Friedman, communications editor

Earl "Doc" Savage, K4SDS, hobby editor

Bob Cooper, Jr. satellite-TV editor

Robert Grossblatt, circuits editor

David Lachenbruch, contributing editor

Lou Frenzel, contributing editor Bess Isaacson, editorial assistant

#### PRODUCTION DEPARTMENT

Ruby M. Yee, production manager

Robert A. W. Lowndes,

editorial production

Dianne Osias, advertising production

Karen Tucker, production traffic

#### CIRCULATION DEPARTMENT

Jacqueline P. Weaver, circulation director

airector

Rita Sabalis, assistant circulation

director

Jacqueline Allen, circulation assistant

Cover photo by Robert Lewis

Radio-Electronics is indexed in Applied Science & Technology Index and Readers Guide to Periodical Literature.

Microfilm & Microfiche editions are available. Contact circulation department for details.

Advertising Sales Offices listed on page 114.







As a service to readers, Radio-Electronics publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers. Radio-Electronics disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

RADIO-ELECTRONICS



**77** • 0.3% Accuracy

 Manual or Autorange

10A + mA RangeBeeper

• "Touch-Hold" Function

\$119<sup>95</sup>

WE CARRY A FULL LINE OF FLUKE MULTI-METERS. IN STOCK NOW

Sale ends Jan. 85

## BECKMAN'S CIRCUITMATE® ALL UNDER \$100

AVAILABLE NOW ....

\$64 95

Circuitmate DM 20— 3½-digit, pocket-size multimeter; 0.8% Vdc accuracy, diode test, hFE test, conductance, 10 amps AC and DC ranges, auto-polarity auto-zero, autodecimal

\$7995



Circuitmate DM-25— 3½ digit, pocket-size multimeter; 0.5% Vac accuracy, dlode test, capacitance, continuity beeper, conductance, 10 amps AC and DC ranges, auto-polarity, auto-zero, autodecimal




\$**69** 95

Circuitmate DM-40 — 3½-digit multimeter; 0.8% Vdc accuracy, diode test, autopolarity, auto-zero, auto-decimal

\$8995

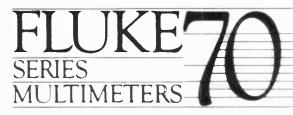Circuitmate DM 45 — 3½-digit multimeter; 0.5% Vdc accuracy, diode test,continuity beeper, 10 amps AC and DC ranges, autozero, auto-polarity, auto-decimal



Analog Display • Rotary Knob • Volts AC & DC • Resistance to • 32 MΩ• 10 Amps • Diode Test • 3200 Counts • Fast Autoranging • Function Annunciators in Display • Power-Up Self Test
 • 2000 + Hour Battery Life w/ Power Down "Sleep Mode" • New Test Leads • VDE & UL Approval



\$9900

**75** 

• 0.5% Accuracy

 Manual or Autorange

• 10A + 300 mA Range

Beeper

\$**79**95

and free C70 holster **73** 



\$6395

- 0.7% Accuracy
- Autorange Only
- 10 Amp Only

NEW!

BECKMAN CIRCUITMATE DM10 \$395

IN STOCK NOW



The DM73 is the smallest digital multimeter on the market. Its probe-style design makes it ideal for taking measurements in hard-to-reach test areas.

Small Size

•"Touch Hold"

CompleteAutoranging

 Audible continuity checking



10LL FREE HOT LINE

212-730-7030

26 WEST 46th STREET, NEW YORK, N.Y. 10036

THE TEST EQUIPMENT SPECIALISTS

ADVANCE\_==

### **VIDEO NEWS**



DAVID LACHENBRUCH CONTRIBUTING EDITOR

• Super VCR. Although some firms are now introducing VCR's in the new 8mm video format, many Japanese video companies have lost their enthusiasm for the new small tape and instead are working to develop ½-inch recorders of vastly improved quality, while retaining compatibility with existing formats. While the original thought behind 8mm was to develop miniaturized units that will provide quality equal to ½-inch, those companies instead are seeking to apply the new 8mm specifications to ½-inch tapes and come up with vastly better quality in the older compatible formats.

Those projects are still closely guarded secrets, but they are aiming at a home machine capable of 400 lines of horizontal resolution, as compared with about 250 on today's VCR's, and a 50–55 dB signal-to-noise ratio, up from 40-45 today. Being explored is the use of high-band color, similar to that used in broadcast VTR's, along with metal tape, new heads, and highly integrated electronics. Both the VHS and Beta groups are working toward these super VCR's, which could be ready in about two years. One of the goals is to make the new system far superior to anything that could be accomplished within the 8mm video format, thereby calming any fears that 8mm will take over as the standard for home decks and keeping it relegated to the status of a system for portable use only.

The key to any improved ½-inch system must be compatibility, according to Shizuo Takano, Managing Director of Video Products for JVC, who is known as the "father of VHS." Takano envisions the current ½-inch formats existing for many years, and being flexible enough to encompass many signal improvements. Takano recently told us: "If a completely new format is ever necessary, it should be when the broadcasting system is changed"—for example, to a widescreen high-definition system.

• Cassettes that communicate. Borrowing a page from 8mm, the Video 2000 VCR system

developed by Philips and Grundig in Europe uses a notched cassette to let the recorder know how much tape it contains, so that the display panel on the VCR can show the time remaining in the cassette. The 8mm videocassette specifications, developed by a 122-company committee in Japan, provides for similar "recognition holes which make an automatic detection of such parameters as kind of tape and tape thickness possible."

The use of notched videocassettes may soon become universal. The VHS group is now exploring whether to add such notches to standard ½-inch cassettes, and undoubtedly the Beta proponents are working on a similar project. Such a notched cassette could tell the VCR of the future whether the tape is of an oxide or metal type and direct it to make automatic adjustments in bias and signal processing, retaining compatibility of any future "super VCR" with current tape types.

A new VHS recorder developed by Grundig for the European market uses a somewhat similar cassette identification system to cue a taperemaining indicator on the VCR. Instead of notches, that system involves stick-on bar-code symbols, which are read by the machine as the tape is loaded. The Grundig VCR also contains a special security system—the user punches in any four-digit code on the keypad. After the cassette is loaded, the machine won't play unless the code is re-entered—as a matter of fact, unless the code is re-entered the cassette can't even be removed from the recorder. A user who forgets his security code can have the machine unlocked only by taking it to an authorized Grundig service station with proof of purchase. A sticker on the recorder notifies prospective burglars that the VCR is totally useless without the four-digit security code.

The Grundig recorder, which is compatible with other VHS machines but uses a "U"-type wrap—around the head drum instead of the standard VHS "M"-wrap—is expected to be available eventually in the U.S.

R-E

























IBM-Compatible Computers



# Heathkit CATALOG



450 kits and products: solar hot water systems, all-in-cne 16-bit computers, test instruments, amateur radio gear, self-study courses in computer literacy and state-of-the-art electronics, energy conservation and home security devices, fine stereo components, color televisions, automotive or marine aids, home conveniences, robots and more - things you've always wanted and needed, right now at low kit prices

For people with imagination, there's nothing to compare with the exclusive thrill of hand-built satisfaction.

Discover the fun of kitbuilding - it's a great way to relax in your spare time and share a rewarding pastime with your whole family. The great kits you build will reflect the pride of your craftsmanship, too. The tamous Heathkit illustrated manuals make it easy for anyone to build reliable, professionalquality kits.

#### SEND FOR FREE CATALOG

Our colorful catalog is Free! If coupon is missing write: Heath Company, Dept. 020-254, Benton Hartor, MI 49022.





I want to "build in" the quality difference.

		ч	١
			•
_	_		ı

A STATE OF THE STA	
Heathkit products are also displayed, so	d and serviced at 64 Heathkit Electronic

ace Phone

Centers' nationwide. Consult telephone directory white pages for location Operated by Veritechnology Electronics Corporation, a wholly wwned subsidiary of Zenith Electronics Corporation.

CL-764B2

Address City Zip.

# RADIO-ELECTRONICS

### WHAT'S NEWS

#### **Library of Congress receives Compact Discs**

The Compact Disc Group—in a special presentation last July 25—presented more than a thousand compact digital-audio discs to the Library of Congress. The presentation included every compact disc released in the United States to that date.

The Compact Disc Group is composed of leading equipment and record manufacturers, united to educate the public and create further awareness of the distortion-free sound of the laser-read Compact Disc.

The discs were officially presented to Deputy Librarian William J. Welsh by Leslie Rosen, Director of the Compact Disc Group. An 1897 Berliner recording of John Philip Sousa's "Stars and Strips Forever," recorded just 13 days after Sousa composed the work, was compared with later renditions, the finale being a Compact Disc recording.



WILLIAM J. WELSH, DEPUTY LIBRARIAN of the Library of Congress, receives a Compact Disc from Leslie Rosen, Director of the Compact Disc Group. Toward the rear, from left to right, are: John L. Broderick, Deputy Librarian for Research Services, Roger Nichols, recording engineer and producer, Robert Saudek, Chief of the Motion Picture, Broadcasting and Recorded Sound Division of the Library, and RCA recording artist Larry Elgart.

#### ARRL wants volunteers as Amateur examiners

With the decision by the FCC to discontinue administering licensing exams to radio amateurs it becomes necessary to develop an organization of Voluntary Examination Coordinators (VEC's) and examiners to administer amateur license exams.

The American Radio Relay League will serve as a VEC in all the

13 FCC call areas of the United States. (More than one VEC may serve in a given call area.) The League is, accordingly, calling for volunteer examiners. Those must hold advanced or extra class licenses. Advanced class license holders may administer only the exam elements required for the technical license; Extra class licensees may administer all written element and international code tests. (Novice licenses will continue to be given by novice examiners under the new novice rules.)

Applicants need not be members of the ARRL. They must be at least 18 years old, hold advanced or extra class licenses, and have no record of license suspension or revocation.

If you qualify and would like to be a volunteer examiner in ARRL's VEC program, you may request an application by writing to Volunteer Examiner Accreditation, American Radio Relay League, 225 Main St., Newington, CT 06111.

#### Semiconductor shortage eases up in 1984

The year-long semiconductor shortage, which peaked in January 1984—when orders overran shipments by more than 50 percent—was reported to be dropping off by early Fall 1984. Some parts, such as microprocessors, were still reported in short supply but the shortage of older products had declined sharply.

Part of the greater availability of many types of semiconductors may have been due to the seasonal summer slowdown in sales, especially of personal and home computers. In June, 1984, orders outstripped shipments by 15 percent—in July the difference was down to 6 percent.

### LITTLE THINGS MEAN A LO

Being the first company to make solderless breadboards isn't necessarily what makes us the best. It's all the little things you don't see, like our spring clip terminals, that make AP' PRODUCTS

ACEBOARDS so big on reliability.

From our largest ACEBOARD with over 5000 tie points, to a single tie point block, our spring clip terminals give you nothing but good, solid contact on every connection. They accommodate a wide variety of leads and have the best electrical properties, because our spring clips are solid alloy, not plated nickel. We've even developed enough normal force to break through any oxides which could flat. No skimping or occur on solder plated leads. You've come to trust our test clips for the same reason.

Since one bad connection can ruin a whole circuit, we pay close attention to how well our spring clip terminals sit within the insulator cell areas. Spring clip edges are never exposed at the insertion window.

For the name of the distributor nearest you. call TOLL FREE (800) 321-9668. (In Ohio, call collect (216) 354-2101)



A P PRODUCTS INCORPORATED

9325 Progress Parkway, Box 540 Mentor, Ohio 44060, (216) 354-2101 TWX: 810-425-2250

In Canada, call Lenbrook Electronics • (416) 477 7722

**CIRCLE 76 ON FREE INFORMATION CARD** 

Leads won't buckle, clips won't oxidize, it all adds up to longer life.

> Even from the outside there's more to an ACEBOARD than meets the eye. Our durable Acetal Copolymer plastic body is a

good insulator with excellent

dielectric properties. And special manufacturingtechniques in the insertion of the contacts into the plastic body insure that your Breadboard will always remain planned obsolescence here. Again, just good solid contact on every connection.

Turn our breadboard body over...and you'll discover another key to it's reliability. The

double-sided adhesive foam you'll doesn't

see there is more than a pressure sensitive mount. It also insulates to prevent shorts and seals the bottom of the individual spring clip cells. If solder shavings from

> resistors or component leads drop into the cell, they can't spread into other cells to

Take a close look at our ACEBOARDS. A P PRODUCTS has the biggest and most complete line of

ACEBOARD sizes. It's also our commitment to you that if your **ACEBOARD** 

work perfectly, bring it back to your A P PRODUCTS distributor. He'll replace it, no hassles.

To help you see for yourself what a big difference the little things make, we're offering you a 10% discount on the entire A P PRODUCTS ACEBOARD/ short them out. Breadboard line.

> Just fill out the coupon and present it to your A P PRODUCTS distributor.







This coupon is worth 10% off the purchase price of any size ACEBOARD or Breadboard product. Offer expires 2/28/85.

Your Name			_
Address			 _
City	State	Zip	 _
Dealer Name			_
ACEBOARD #			

Limit 5 ACEBOARDS or Breadboards per coupon. Offer valid only at participating A P PRODUCTS distributors






INIC







#### PORTABLE OSCILLOSCOPES

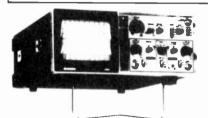


MODEL V-212

\$461.00

DC to 20MHz, 1mV/div, Dual Trace


Feature 6" Rectangular CRT Full 2 year parts and labor warranty.

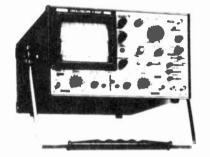

MODEL V-650F

\$956.00

DC to 60MHz, Dual Trace Delayed Sweep

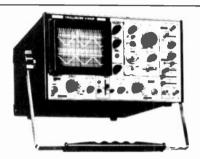

MODEL V-1050F

\$1276.00

DC to 100MHz, Quad Trace, Delayed Sweep.

- All prices include full set of factory probes - up to \$120.00 value.

#### ■Polaroid CR-10 Camera

Now you can get an instant picture in black & white or color from any oscilloscope screen. Includes CRT hood.

\*Large hoods also available to fit computer terminals and CAD/ CAM screens.



\$369.00


#### **GLOBAL SPECIALTIES** DP-1

#### DIGITAL PULSER

\$83.00

- Senses state of node, presets pulse polarity
- Short circuit protected, circuit powered Handheld digital signal injector
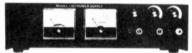
#### **GLOBAL SPECIALTIES** TRIPLE OUTPUT POWER SUPPLY



#### MODEL 1301

\$219.00

DC POWER

SUPPLY

\$125.00

- Fully regulated triple output
- Fixed 5VDC, 1A V1 + 5 VDC to 18 VDC .5A
- V2 5 VDC to 18 VDC .5A
- Fully automatic current limiting

ELECTRO INDUSTRIES, INC



#### **MODEL 1650**

\$319.00

- Functions as three separate supplies
- Exclusive tracking circuit
- Fixed output 5 VDC, 5A
- Two 0 to 25 VDC outputs at 0.5A Fully automatic, current-limited
- overload protection + and - terminals of each output
- are fully isolated, in all modes All three outputs may be connected in series or parallel for higher voltage or current



PROTO-BOARD

- Length = 7.4" Width = 4.5
- 14 pin IC capicity = 12
- Terminals = 248
- Tie points = 1240

\$34.95 MODEL P8-102



#### DIGITAL LOGIC PROBE Use to 50 ns. 10 MHz

\$19.95

Circuit powered, portable Compatible with most logic families

#### DIGITAL CAPACITANCE METER



- Battery operated
- 3½ digit LCD display Range 1 PF to 2,000 UF
- 0.2% basic accuracy

**MODEL 3000** \$139.00

MODEL 3002A/0-30 VDC/0-2A

**CALL US TOLL FREE** 

1-800-732-3457 IN CALIFORNIA TOLL FREE

1-800-272-4225

Master Charge ■ VISA ■ COD

Money Order ■ Check



ADD FOR SHIPPING AND INSURANCE \$251.00 to \$600.00 . . . . . . . . \$6.50 \$501.00 to \$750.00 ...... \$8.50 \$751.00 to \$1000......\$12.50

RAG ELECTRONICS, INC. / 21418 Parthenia Street / Canoga Park, CA 91304 / 1-818-998-6500















**CIRCLE 269 ON FREE INFORMATION CARD** 





#### GIANT 14th ANNIVERSARY SALE!



#### **70 SERIES MULTIMETERS**







 Analog Display ● Rotary Knob ● Volts AC & DC ● Resistance to ● 32 MΩ ● 10 Amps ● Diode Test ● 3200 Counts ● Fast Autoranging • Function Annunciators in Display ● Power-Up Self Test ● 2000+ Hour Battery Life w/Power Down "Sleep Mode" . New Test Leads VDE & UL Approval

\$85.00 73

- 0.7% Accuracy
- **Autorange Only**
- 10 Amp Only

#### \$99.00 75

- 0.5% Accuracy
- Manual or Autorange
- 10 A + 300 mA Range
- Beeper

#### **\$**129.00

- 0.3% Accuracy
- Manual or Autorange
- 10A + mA Range
- Beeper
- "Touch-Hold **Function**



- Distortion from <0.03%
- 10 Hz to i MHz



\$259.95



PRECISION

**FUNCTION GENERATOR** 

**MODEL 3010** 

\$189.00

- Sine, square and triangle output Variable and fixed TTL outputs
- 0.1 Hz to 1 MHz in six ranges
- Typical distortion under 0.5% from 1 Hz to 100
- Variable DC offset
- VCO input for sweep tests

**MULTI-FUNCTION** COUNTER



MODEL WD-755 **\$259.00** 

- 8 Digit LED Display
- Period Measurement 5 Hz to 2 MHz Totalizes to 99,999,999 Plus Overflow
- Frequency Ratio Mode Time Interval Mode
- Switchable Attenuator & Low Pass Filter

RELAY VOM . . 5-way protection



\$49.00

MODEL WV-532A

- Fast relay opens input circuit on overload
- Lamp indicates when relay is open
- Easy-access battery compartment and testlead storage
- High-accuracy: ±2% DCV, ±3% ACV 3-to-1 ranges (like VTVM) Large, 5½" mirror meter

- Front panel and meter scales coded in 3 colors for quick function identification
- Battery-condition indicator for overload
- protection circuit

5 K 4 4 4 VARIABLE TRANSFORMER



\$145.00

MODEL 3PN1010V

**RAG CARRIES THE COMPLETE STACO** VARIABLE TRANSFORMER LINE CALL US WITH YOUR REQUIREMENTS.

#### WE CARRY A FULL LINE OF FLUKE MULTI-METERS. COUNTERS. AND DIGITAL TEMPERATURE METERS

#### 41/2 DIGIT MULTIMETER


- Frequency measurements to 200KHz
- dB measurements
- Basic dc accuracy 0.4%:
- $10 \mu V$ , 10 nA and 10 m  $\Omega$  sensitivity
- True RMS
- High-speed Beeper

\$349.00



#### PORTABLE OSCILLOSCOPES

MODEL 8060A

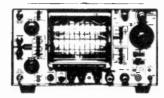

#### MODEL SS-5705

\$899.00

DC to 40MHz

Vertical and horizontal deflection accurate within ±2%. CRT acceleration voltage 12KV. 3 channels, 6 traces. High precision calibrator

Alternate time base

- CH1 signal output
- Beam finder
- Delayed sweep
- (±1%). Fastest sweep rate: 10 ns. High sensitivity 1 mv/div



**MODEL SS-5702** 

6 inch rectangular internal graticule

Includes 2 each x1/x10 probes and full factory warranty; 2 years on parts, labor and CRT.









\$535.00








# RADIO-ELECTRONICS

### **SATELLITE TV**

#### Changes in the TVRO industry

BOB COOPER, JR.\* SATELLITE EDITOR

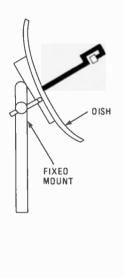

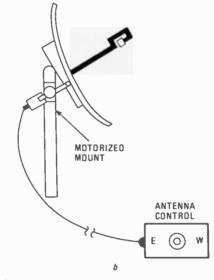


FIG. 1

IN THE LAST INSTALLMENT OF THIS COLumn, we looked at the business opportunities presented by the home-TVRO industry today. We also took a backward look at the basic hardware contained in the system with a sort of "then-andnow" comparison of how hardware developments have paced rapidly expanding equipment sales. This time we'll look at the individual components that make up those systems.

#### **TVRO** components

The first home-TVRO systems, bought by genuine consumers (not "technology buffs" who'd purchase anything new and exciting) were extremely cumbersome to operate. Not only that, one segment of the system was missing from the equipment line-up: the "dish mover" or motor-drive unit.

\* Publisher, CSD magazine

(It had not yet been invented, nor would it be until late in 1980.)

Early enthusiasts who built or assembled their own systems were seldom satisfied to watch programming from a single satellite for long. After all, part of the fun and excitement was being able to "cruise the skies" looking for action. With cable programming concentrated on a single satellite (F1 in 1980), the 20 or so channels emanating from its transponders were entertaining, but were hardly all that was in the sky.

Those early TVRO owners talked glibly about picking up 30 or 40 channels as if they were all easily accessible from an easy chair. Of course, they were not. In fact, to receive programming beyond the first 20 or so channels, somebody had to go out in the yard and "wrestle" with the antenna because the original mount was of

the fixed variety, as shown in Fig. 1-a (not exactly a "consumer friendly" product!).


Motor drives have been troublesome parts of TVRO systems since they first appeared commercially in the fall of 1980. The earliest drives (available as retrofit devices for virtually any polar-mount style dish) were simple devices that had a three-positions switch (OFF, EAST, and WEST).

The switch connected to a motorized jack-screw actuator (see Fig. 1-b) that mounted between the dish and the post portion of the polar mount. The post was stationary (they hoped!), while the dish would pivot when pushed or pulled by the motordriven jack screw. If the dish and mount were capable of tracking the Clarke orbital belt, the motor would provide the remote-controlled push/pull action to drive the dish through the belt. Simple enough, but there were many problems.

The earliest motorized mounts were not designed for frequent use—moving the dish on the mount quickly proved they weren't. Poor calculation of weights and loads resulted in extremely heavy strains on the small motors chosen to rotate the jack-screw actuators. The jack screws, in turn, proved too lightweight and they soon bound-up under the strain.

Needless to say, the first year of motorized dish-mounts was a disaster and those who purchased those units probably junked them within a few months. It took a mul-

continued on page 20

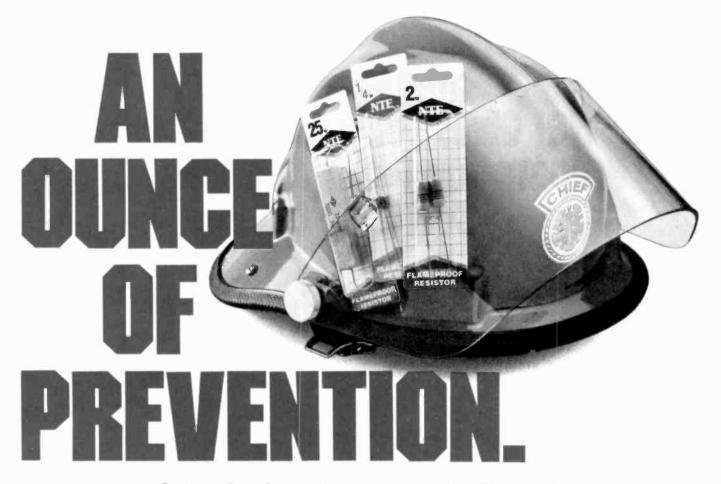

### Introducing the complete line of Flameproof Resistors from New-Tone Electronics.

NTE Flameproof Resistors are the latest addition to NTE's line of quality components. They're designed to provide you with a premium quality replacement device ... that won't flame out or short even under the most severe overloads.

Our resistors range in capability from 1/4 Watts to 25 Watts with resistance values from .10 to 1.5 Megohms.

They're totally noncombustible with a metallic resistance material between a nonresistant core and a special ceramic outer cover.


NTE Flameproof Resistors are the ideal replacement components for electronic

games, telecommunications, medical, data processing, military, broadcast and home entertainment equipment.

Don't take chances with your expensive equipment. Use NTE Flameproof Resistors ... they handle the current.

Look for NTE's full line of quality replacement parts in the bright green

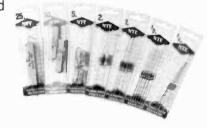polybags and cartons at your nearest distributor.





New-Tone Electronics, inc.

44 FARRAND STREET • BLOOMFIELD, NEW JERSEY 07003

# Only NRI Gives You This Kind of Training and Equipment. Only NRI Gives You So Much Professional Preparation For a TV/Audio/Video Servicing Career.

Build this 25" Heath/Zenith Color TV with 112 channel tuning system, infrared remote control, advanced sound system, and in-set space phone.

Get complete, thorough instruction in the theory, servicing, and repair of TV, VCR, video disc players, audio equipment, AM/FM receivers, an-

tenna systems, home video cameras, projection TV, and more with 65 easy-to-digest, bite-size lessons.

See servicing techniques demonstrated in close-up detail. Graphic presentations make theory and systems come alive on NRI Action Videotapes covering VCRs, disc players, and TVs.

Perform challenging state-ofthe-art electronic experiments and demonstrations using your NRI Discovery Lab®. Learn how to diagnose problems using a professional 3½-digit digital multimeter. Exclusive NRI Action Audio instructions talk you through its complete operation and use.

Learn servicing and adjustment techniques with this 6-hour, remote control videocassette recorder you get as part of your training.

Only NRI gives you so much practical training with equipment you learn on and keep. You learn by doing. That's the way to make it interesting, that's the way to make it enjoyable, that's the way to get the hands-on experience and know-how vou need.

#### **Hands-On Training For Real Bench Experience** and Priceless Confidence

You start with experiments and demonstrations on the unique NRI Discovery Lab. You learn basic circuit wiring and soldering techniques, and then quickly move on to more advanced concepts as you come to understand electronic theory. solid-state devices, digital systems, and microprocessors. You learn by actually building and observing the action of circuitry you'll be working with in real-life situations.

#### Exclusive NRI Training On Videotape

In addition to profusely illustrated lessons, you get NRI's Action Audio cassette to "talk" you through the use and operation of the professional digital multimeter you receive as part of your equipment. Even more exciting are your NRI Action Videocassettes...videotaped lessons that show you graphic presentations of electronic systems, vivid closeups of servicing techniques and profes-

sional "shortcuts" to study and replay as often as you want.

#### You Get TV, VCR, **DMM and More** Equipment To Keep

You also build your own 25" Heath/Zenith color TV. a state-of-the-art unit that includes infrared

remote control, a Time Control Programmer, and the incredible Advanced Space Phone that lets you telephone from your chair. Using the videocassette recorder that's included as part of your training, you learn how to adjust, service and repair these fast-selling units. Your front-loading VCR features up to 6-hour recording capacity, remote control, and programmable touchbutton tuning.

The digital multimeter you receive is a truly professional instrument. You use it in the experiments throughout your course and as a key servicing tool on the job. Using the meter along with the NRI Discovery Lab, you'll learn how to measure voltage, current and resistance and how to diagnose all types of servicing problems.

**Advanced Systems Demand** Advanced **Technicians** for Service and Maintenance

The art of TV/Audio/Video servicing has taken quantum leaps into the future. Now, successful technicians must understand advanced concepts like digital control, electronic tuning, laser video discs, microprocessors, and more. NRI gives you the training you need for success...state-of-the-art concepts and practical, hands-on experience working with the kind of

equipment you'll encounter on the job.

#### 7 Decades of Teaching **Electronics Skills At Home**

NRI is the oldest. largest, and most successful school of its kind in


the world. It has pioneered and refined the teaching techniques that make learning at home the NRI way one of the most economical and effective methods ever conceived. You learn at your convenience as a class of one, backed by skilled NRI instructors and carefully designed lessons that take you a step at a time toward your goal. No time away from your job, no night school grind, no classroom pressures. Yet your training is thorough and complete. with a foundation of hands-on experience unequalled by any other training organization.

#### Send For Free Catalog **Covering 12 Electronics** Courses

Our 104-page catalog gives you all the details. In it, you'll find a summary description of every lesson, and photos and specifications for every item of equipment included in vour course. You'll also learn about other fascinating career opportunities in the world of electronics... Microcomputers, Industrial Electronics including robotics, Communications, and more.

Mail the postage-paid card today for your free copy. See how completely and how thoroughly NRI gets

vou started on your tomorrow

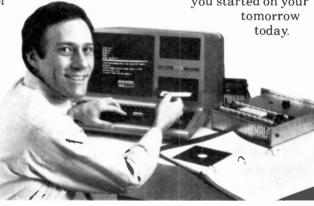



NRI SCHOOL OF **ELECTRONICS** McGraw-Hill Continuing **Education Center** 3939 Wisconsin Avenue Washington, DC 20016

#### **SATELLITE TV**

continued from page 14

titude of field failures to get suppliers thinking about the strains being placed on the system.

To complicate things, just as the mechanics of the system were being ironed out, a firm in Tulsa, Oklahoma introduced a drive system with a built-in programmable memory. The user simply pro-

grammed several satellite locations into the unit using a two- or three-digit code and the control box "remembered" where the satellites were.

As you might expect, that development brought with it an entire new wave of problems. Memories would fail (forget) when there was a power failure or glitch. Dish positioning would be knocked off by a degree or two by a glitch. Power surges would wipe out memory entirely, and the user

#### TVRO dealer "Starter Kit" available

Bob Cooper's CSD Magazine has arranged with a number of TVRO equipment suppliers to provide a single-package of material that will help introduce you to the world of TVRO dealership. A short booklet written by Bob Cooper describes the start-up pitfalls to be avoided by any would-be TVRO dealer, in addition, product data and pricing sheets from prominent suppliers in the field are included. That package of material is free of charge and is supplied to firms or individuals in the electronics service business as an introduction to the 1984/85 world of selling TVRO systems retail.

You may obtain your TVRO Dealer Starter Kit free of charge by writing on company letterhead, or by enclosing a business card with your request. Address your inquiries to: TVRO STARTER KIT, P.O. Box 100858, Fort Lauderdale, FL 33310. That kit not available to individuals not involved in some form of electronics

sales and service.

#### SATELLITE TV/

### The First Five Years!



THE MOST COMPLETE report on the mushrooming home 'TVRO' industry ever compiled, written as only the 'father of TVRO' could have prepared. More than 1000 pages (!) tracing the complete story of home TVRO, lavishly illustrated with equipment photos, schematic diagrams, equipment analysis reports. Bob Cooper, the first private individual to own and operate a TVRO (1976) has collected and polished hundreds of individual reports into a unique 'collector's edition' which clearly explains the TVRO phenominon in North America. From Coop's first 20 foot 'monster' dish to the present day 5 foot 'C-band' TVROs, the fascinating growth of TVRO equipment and its legal status unfolds for you.

THIS TWO VOLUME SET totaling more than 1,000 pages is available for the first time to readers of Radio-Electronics at special discount pricing. Originally sold at \$100 per two-volume set, a limited supply is now available ONLY through this advertisement. PLUS, you will also receive a special extraordinary bonus; the 200 page (+) October 1984 edition of CSD/Coop's Satellite Digest. This very special edition of CSD is a best-seller in the TVRO industry, with the most comprehensive collection of TVRO facts and figures ever compiled. Combined with the 1,000 page 'CSD ANTHOLOGY' report, you have instant reference to everything you will ever need to know about the state of the home TVRO industry. It is MUST reading for every person in, or thinking about 'getting into,' any segment of the home TVRO world.



SEND CSD ANTHOLOGY/2 Vols. + CSD Bonus. SEND CSD October '84 Special Issue ONLY,

NAME	ME COMPANY		
ADDRESS			
CITY	STATE	ZIP	

Payment: \$60 US funds (Anthology + Bonus), \$15 US funds CSD Oct. ONLY; payable "CSD ANTHOLOGY."

Shipping charges prepaid. Enter order to: CSD Anthology, Radio-Electronics Magazine, 200 Park Av. S., New York, NY 10003; or call 305-771-0505 for credit card orders ONLY.

would be forced to re-program the memory. The problems seemed endless.

Fortunately, virtually all those early problems are now behind us. Modern drives have memories that remember, infrared or UHF wireless remote-controls, and "floating" gimbel-type brackets that transfer the load of the dish away from the motor-driven jack screw. They also have the ability to interface to fully remote-controlled receivers, as well.

As recently as 1983, dealers were reporting in annual TVRO-dealer surveys that "dish movers" were their most frequent problem causers. That's not true anymore. However, pricing still continues to be surprisingly high for that portion of the system.

At dealer pricing levels, simple "east-west" systems with a single switch control run in the \$300 and up range. More elaborate systems with memories can cost twice that amount, while those with full remote-control capabilities may cost a dealer.

Perhaps the most significant signs of maturity in the TVRO industry are the warranties now attached to motor-drive and control systems. One year is standard, and some offer even longer full-coverage protection.

Next month, we'll look at more component changes. R-E



## RADIO-ELECTRONICS

### LETTERS

#### WRITE TO:

#### LETTERS

Radio-Electronics 200 Park Ave. South New York, NY 10003

#### CORRECTION

In "All About Power Supply Circuits", Radio-Electronics, July 1984, I believe an error exists in the schematic shown in Fig.4. The caption for that figure states that Figs. 3 and 4 are equivalent. Please note that diodes D1 and D2 are connected "across" the whole secondary of T1, whereas diodes D3 and D4 are "across" only one-half the winding. Therefore, -V out will be one-half that of +V out, supposedly. However the circuit shown in Fig. 4 would not work well because the cathode of D3 is grounded.

Lenjoy your magazine very much, as long as you do not go "computer happy." I was a fan of Popular Electronics, but they went crazy over computers and that turned me right off (I'd rather switch than fight)! Please, minimize your articles on computers. Let's continue to have good material on phone accessories, control circuits, timer circuits, and such, along with explanations of how various circuits function. For example, the "All About Power Supply Circuits" article was great. **EDWARD BALASKI** Torrington, CT

An error certainly does exist in Fig. 4. The caption describes what was supposed to be there. But, as you indicate, diode D3 is shown incorrectly. Its cathode should be connected to the bottom of the transformer.—Editor

#### SERVICE MANUAL NEEDED

I enjoy your magazine very much and I eagerly await the first of the month for the latest issue so that I can see what new projects I can build and find what new information I can use.

Perhaps some of your readers can help me. I have a Sansui AU

#### Versatile Lab Power Supply





MODEL 3002A

• 0-30 VDC at 0-2A • Excellent Regulation • Ripple & Noise - 500 uV RMS • Built-in Short-Circuit and Overload Protection

Model 3002A features continuously adjustable current limiting and precision constant voltage/constant current operation with "automatic crossover." This lab-grade unit can also be used as a current regulated power source. Options: 10-Turn Voltage and Current Controls, \$25.00 ea. (can be ordered individually)

Also available...TRIPLE MIGHTY-MITE LAB POWER SUPPLY: Three Fully Regulated DC Outputs; two 0-25V/0.5A and one fixed 5V/3A, Variable Tracking & Independent Modes, Dual Panel Meters. Other models to 60 VDC, to 12A.

TERMS: Check, Money Order or COD. COD's \$2.00 extra. Add \$3.50 for shipping & insurance in 48 states. Please contact our Sales Department for other shipping rates. Illinois residents add 7% sales tax.



Free Literature On Request ELECTRO INDUSTRIES

4201 W. IRVING PK., CHICAGO, IL 60641 312/736-0999

### CABLE CONVERTER PRICE SLASHERS

- 60 Channel Capacity
- P.L.L. Tuning
- 6 Channel Memory
- TV On-Off Feature
- Infra-Red Wireless Remote Control

ONLY \$5995 FACTORY REFURBISHED



- MasterCard & Visa Add 5%
- . Checks Allow 14 Working Days
- Freight Charges: Sent Collect
- Order 20 or More Freight Prepaid
- Special Price on New Factory Fresh Units \$69.95
- · Warranty Not Valid After 15 Days From Receipt

#### OTHER MODELS ALSO AVAILABLE

Jerrold JRX-3 \$49.95°

Jerrold RSC-3 \$39.95°

Jerrold DRX-3 \$69.95\*


\*Reconditioned Units With 30 Day Warranty

#### Phoenix Electronics

1 Midwood Allendale, NJ 07401 (201)848-8229

# THE MOST WANTED OSCILLOSCOPE...

# THE DUAL Trace

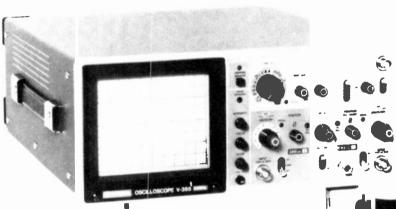

HITACHI Cat. No. V-355 \$599<sup>95</sup> With Probes

#### OFF-THE-SHELF DELIVERY

**DESCRIPTION** Its thin, light, compact design features a large 6 inch rectangular, internal graticule CRT with percent calibrations, autofocus, scale illumination and photographic bezel.

Reward Eliminates distortion and para

Eliminates distortion and parallax. High performance. Most cost effective scope around.

■ MASTER CARD

■VISA

**■** C.O.D.

■ MONEYORDER

■ CHECK

C.O.D.'s extra(required 25% deposit) • Add \$8 50 for shipping and insurance • N.Y. State residents add appropriate sales tax

Fordham 260 Motor Parkway, Hauppauge, New York 11788 (800) 645-9518

1788 In New York State Call 800-832-1446

3900 amplifier that is not operating. I need a schematic or, better yet, a service manual for the unit, but the Sansui distributors are unable to get it for me. In addition, neither Sam's Photofact nor the Radio College of Canada list the appropriate schematic. I am hoping someone can help me. BRIAN COLLINS

3179-138th Ave. Edmonton, Alberta, Canada T5Y 1R1

#### **EXPANDING THE ZX81**

I was working on a project in which an output line is turned alternately high and low under computer control using a Timex/Sinclair 1000. When Neil Bungard's article on interfacing the ZX81 appeared in the July 1984 issue of Radio-Electronics, I felt a modification of his circuit was just what I needed.

I sat down at my computer to test the program I wrote to accom-

plish the task. Immediately I ran into trouble. In spite of using only even-numbered addresses as Neil has advised, my program crashed. Experimentation finally revealed that the program ran fine using odd-numbered addresses. Had Neil mislead his readers? No! The problem arose because he only told half the story.

There exists somewhere in the innards of the ZX81 an NMI (nonmaskable interrupt) generator. That generator must be on in the slow mode, but off in the fast mode. Evidently Sinclair uses the address line AØ to turn that generator on and off. I was operating in the fast mode, so every time the computer executed an OUT instruction to an even address, it turned on the NMI generator, causing a crash. Neil must have been operating in a slow mode, so every time his computer executed an OUT instruction to an odd address, it turned off the NMI generator, causing a crash.

The rule then is: In the fast mode, OUT instructions should use only odd addresses, but in the slow mode, OUT instructions should only use even addresses.

Another caution: The monitor uses hexadecimal output addresses FF, FE, and FD, and hexadecimal input address FE. That means that it will activate output 8 on IC3 and IC4. That could result in undesired outputs and inputs by the normal running of the monitor. Neil has guarded against that by the decoder circuit using IC9 and IC1-c. He also has left open output 8 on IC3 and IC4.

WALTER E. STYLES Richmond Area Timex/Sinclair Users Group Chester, VA

#### **MANUAL NEEDED**

I received some old equipment from friends, but they did not have the operating manual. Perhaps there are some Radio-Electronics readers who know where I can get a manual and hopefully a schematic for an Electronic Measurement Corp. tube and transistor Tester, model 215.

TOM BRACLETT 22258 Gregory Dearborn, MI 48124

### **EXPLORE THE ROBOTICS AGE...**

by reading Robotics Age magazine. Discover industrial, commercial and experimental robotics. Enhance your technical skills. Robotics

Age explores technological applications, research and current events in:

- Microprocessor engineering
- Real-time control software
- Mechanics and kinematics
- Vision...and other senses
- Robot communications
- Mobility
- Artificial intelligence
- Practical techniques

Robotics Age is your monthly journal of intelligent machines.

#### **Subscribe today!**

YES! Sign me up TODAY for my personal subscription to Robotics Age, The Journal of Intelligent Machines.

RE 851





US Subscriptions	
_ 12 Issues	\$24
_ 24 Issues	\$45
36 issues	\$63
Canada & Mexico	\$28

_ 36 Issues	\$7
Foreign	
= 12 Issues (surface)	\$3
= 12 Issues (Air Mail)	\$6
24 Issues (surface)	\$6
24 Issues (Air Mail)	\$13
36 Issues (surface)	\$8
36 Issues (Air Mail)	\$19

#### Non-U.S. Subscription Rate

Payable in US funds, drawn on a US bank. Subscription length will be adjusted downward on a pro-rata basis for any currency conversion charges. Foreign subscription orders may be paid in US dollars via MasterCard or VISA.

Name	
Title	
Company	
Address	
Town	·
State	Zp (Postal Code)
Country	
Bill Me Check or credit card pay	iment enclosed. Payment bonus! Orders accompanied by payment will receive one extra issue
Credit Card Information	Card Number
_ VISA	Expiration Date

RETURN WITH PAYMENT TO: Robotics Age, 174 Concord Street, Peterborough, NH 03458 (USA)

Also available at many local book and magazine dealers.

#### SATELLITE STEREO DEMODULATOR

The correct telephone number of Video Control, who is offering kits of parts for the satellite stereo demodulator described in the October issue of Radio-Electronics, is (206) 693-3834.

#### ANTIQUE RADIO CLASSIFIED

There is now a publication that may interest the growing number of antique-radio collectors. Beginning in September, 1984 Antique Radio Classified will feature free classified ads for buyers, sellers, and traders of old radios and related items.

Antique Radio Classified will be published nationally each month and will also contain coverage of upcoming radio conventions, meetings, and flea markets for the antique-radio collector.

GARY B. SCHNEIDER Publisher Antique Radio Classified 9951 Sunrise Blvd. Cleveland, OH 44133

#### **INFORMATION EXCHANGE**

The Data Processing Amateurs Society of Quebec is the oldest such association in Eastern Canada.

The goal of the association is to have an interesting hobby, and together to increase our knowledge and experience. We do our best to help beginners with meetings, courses, demonstrations, etc.

Our members asked us to try contacting other clubs or associations in Quebec and surrounding areas to exchange experiences, information, and friendship. As over 30% of our members are using modems, we succeeded in organizing our own telecommunication system: TELESAIQ 11. We are learning a lot with this project, and it is not over, because we do not have full services.

We are negotiating with other systems and networks to exchange services.

Since yours is one of the most popular publications in the field, we thought of turning to you for assistance. We would appreciate if you could help us by publishing our address so that other similar organizations could contact us. GERALD BOULET SIAQ

Societe D'Informatique Amateur du Quebec C.P. 9242

Sainte Foy, Quebec, Canada G1V 481


#### **SCHEMATIC NEEDED**

I recently acquired a B&K model 1075 TV Analyst in need of repair. I know it needs a horizontal width/frequency coil, but I have no other

information on the unit itself. I would hope that one of your readers has a schematic and parts list for that older device. I am a student in electronics and would greatly appreciate any and all help other readers could provide. TERRY B. SCHWARTZ 1864 Eleanor Ave. St. Paul. MN 55116
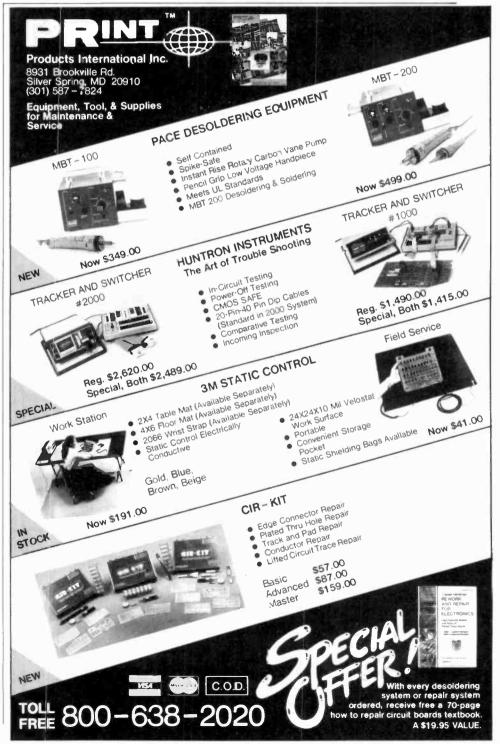
#### **POWER-SUPPLY CORRECTIONS**

The article, "All About Power-Supply Circuits," (Radio-Elec-



tronics, July, 1984) contained several significant errors and omissions:

- 1. The VA rating calculation for a power-supply transformer is not correct for the circuits shown. It should be: Secondary RMS voltage  $\times$  DC current  $\times$  1.2 (CT) or 1.8 (bridge). Also, the transformer regulation factor for the typical small hobbyist transformer is 15-20%, not the 10% stated.
- 2. The PIV rating for the rectifiers is at least twice the second-

ary voltage, allowing for a safety

- 3. 3-terminal regulators can rarely be used for their rated current unless "bolted to an anvil sitting on a block of ice." Without any heat sink, those popular 1-amp "tab" regulators are only good for about 100-200 mA. The heat sink is what really determines the rating of most regulators.
- 4. A good-quality filter capacitor is important. Audio-grade capacitors, identified by their flimsy

leads, are not suited for output currents above ½ amp.

- 5. Allow adequate ventilation, especially around the power transformer. Keep the filter capacitor and regulator away from it.
- 6. To prevent current surges from blowing the rectifiers, put a very small resistor in series with one side of the transformer secondary (or center-tap, if you are using it). The value to use is approximately: (secondary RMS voltage)/ $(20 \times rectifier current rating)$ .
- 7. Safety first! Use a fuse, and locate it before any switch. Ideally, use a grounded power cord, and put the fuse and switch on the "hot" side of the line.

Finally, a construction tip: for low-current supplies, a wall-plug transformer is the safest and usually the cheapest approach. ALVIN H. NICHTER New York, NY

#### ZX81 DESIGN—OKAY!

I've just built the ZX81 Interface, (Radio-Electronics, July, 1984).

It's an excellent design, but there is an error in the schematic. For address inputs through IC8 (74LS373), A2 comes in on pin 7, and should leave via pin 6, not pin 5, as shown.

Thank you for the article on the ZX81. Let's have many more, please!

MERLIN TINKER Casper, CA

#### MORE MEDICAL ELECTRONICS

Since you have started printing articles about medical electronics, I'd appreciate some more about the repair of the instruments used in that field. There seems to be a dearth of information about their repair as I have, to this point, only been able to locate one book on the subject. Any articles that could enlighten me further about the care and repair of electronic medical instruments, or even just a suggested reading list, would be most helpful.

ALBERT SHUGZDIS Arkadelphia, AR

#### **BACKWARD X-RAY**

I have read the article by Dr. Fish, "Electronic Measurement in Medicine," (Radio-Electronics,

#### **VIEW 8 TRACES ON YOUR SINGLE** OR DUAL TRACE SCOPE WITH THIS LOW COST DEVICE!!



Now you no longer have to spend thousands on an expensive multitrace oscilloscope – our single trace Hitachi scope combined with this module will allow you to view up to 8 simultaneously occuring analog or digital (or both) signals in their real time and amplitude relationship. The MPX 101 may be used on any oscilloscope, whether single, dual or multiple traces. Its low cost makes it a particular favorite for designers, testers, hobbyists and repairmen who want to compare and analyze displayed signals in a timing diagram format. The controls on the front panel of the metal case allow you to vary amplitude and spacing of the displayed signals.

**MODEL MPX101** 

REPLACE-MENT WARRANTY

Made In The United States -

SPECIFICATIONS

Inputs: 8 signals plus ground via 9 input leads terminated with alligator clips

Bandwidth: ± 1dB to 5 MHz Impedance: 10.9 K Input Voltage: ± 5V peak (diode clamped to ± 5 Volt supplies) Output: Staircase waveform summed

with input signals, 0-800 mV full scale Step Amplitude: Variable 0 to 150

Signal Voltage: Variable 0 to

150 mV/step @ 5V Input Multiplex Rate: Switch selectable, 40 KHz or 4 KHz

Impedance: 50 Ohms Power: 105-135 VAC @ 1 V a Dimensions: 6.25" x 3.25" x 4.75" (WxHxD)

Operating Temperature: 0-40°C Weight: 1 lb. 10.5 oz.

Warranty: one year full replacement warranty from date of purchase Lighted on/off power switch Wood grain finished metal case

DISTRIBUTOR AND REPRESENTATIVE INQUIRIES INVITED

NOT

KIT



VISA, MASTERCARD, AMEX TELEPHONE ORDERS ACCEPTED! 6 Herman Drive, E. Granby, CT 06026 □ 203/651-0285

**CIRCLE 61 ON FREE INFORMATION CARD** 

September 1984) with interest. On the whole someone outside medicine might not find the article interesting. It is, however very informative. There is one error of note in Fig. 5, page 57. The radiograph (X-ray), is printed backward, making some of the labeling incorrect.

I mention that because I am a Radiographer by profession and things like backward X-rays really stick out.

Keep up the good work. I really enjoy your magazine. RONALD J. BOHLAND, R.T.(R) Toledo, OH

#### **EDITORIAL "AMEN"**

I saw your editorial in Radio-Electronics, September 1984, "When is a Change not a Change?", and I say AMEN! There are plenty of magazines that tell about computers—seems like they all do—and that is the sole reason I changed to Radio-Electronics a few months ago from another similar magazine. I am a circuit guy, not a button pusher. I realize that computers are great for the non-technical, but there are a lot of us who are technical. Anyhow you get the point.

That particular issue really rang the bell on articles. I liked "Sonic Motion Detector," (I have been looking for years for this), "Electronic Measurements in Medicine," "What's New in Batteries," "Squarewave Generator Circuits," and the departments were also of interest.

Congratulations! I think your courage will pay off! CHARLES DEMING Mariposa, CA

#### AMPLIFIER SCHEMATIC NEEDED

A few years ago, I brought a Lafayette *LA-324A* stereo amplifier from a friend. Last week it burned up due to a power overload. I am interested in rebuilding that amplifier, but the schematic diagram is missing from my records. Is there any reader that can help? I need a copy of the service manual or the schematic diagram. I'd appreciate any help from any source. ARTURO OTERO BRACERO *P.O. Box 2821-S*,

San Juan, Puerto Rico, 00903




Each year cancer strikes 120,000 people in our work force, and causes our economy to lose more than \$10 billion in earnings. Earnings that American workers might still be generating if they had known the simple facts on how to protect themselves from cancer.

Protect your employees, your company, and yourself....call your local unit of the American Cancer Society and ask for their free pamphlet, "Helpfing Your Employees to Protect Themselves Against

Cancer." Start
your company on
a policy of good
health today!

American Cancer Society

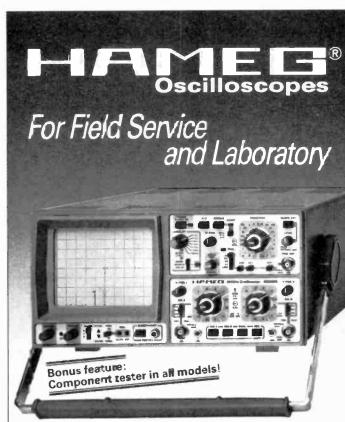

#### HM 605 60 MHz Dual Trace · US\$ 965,-

Sensitivity 5mV-20V/div at 60 MHz, 1mV at 5MHz • Automatic peak-value or normal triggering to 80 MHz • Delay line • Variable sweep delay from 100 ns-1s • Timebase range from 2.5s/div to max. 5ns/div • Unique fast-rise-time 1kHz/1MHz calibrator • Bright high-resolution 14kV CRT.

#### HM204 20 MHz Dual Trace · US\$ 758,-

Sensitivity 5 mV-20 V/div • 1 mV at 5 MHz • Timebase range 1.25 s/div-10 ns/div • Automatic peak-value triggering to 50 MHz Delay line • Variable sweep delay • Single sweep mode • Y-Output • Z-modulation • Overscan indicator • Unique 1 kHz/1 MHz calibrator.

#### HM 203 20 MHz Dual Trace · US\$ 605,-

Western Europe's best selling 29 MHz-Scope! • Sensitivity 2 mV-20 V/div • Triggerbandwidth 40 MHz • Timebase range 0.2 s — max. 20 ns/div

#### HM 103 10 MHz Single Trace US\$ 410,-

Small, compact service scope • Sensitivity 2 mV-20 V/div • Timebase range 0.2 µs-0.2s/div • TV-V and TV-H triggering.



### **EQUIPMENT REPORTS**

#### Radio Shack Model 4 Computer

An 8-bit, Z80-based personal computer




CIRCLE 5 ON FREE INFORMATION CARD

THE RADIO SHACK (ONE TANDY CENTER, Ft. Worth, TX 76102) Model 4 is a personal computer that will run both TRSDOS and CP/M programs without the need to get into the guts of the computer and attempt some rather hairy and complex circuit retrofits. As such, essentially the Model 4 is a merger of the best features of Radio Shack's Model III and Model II computers.

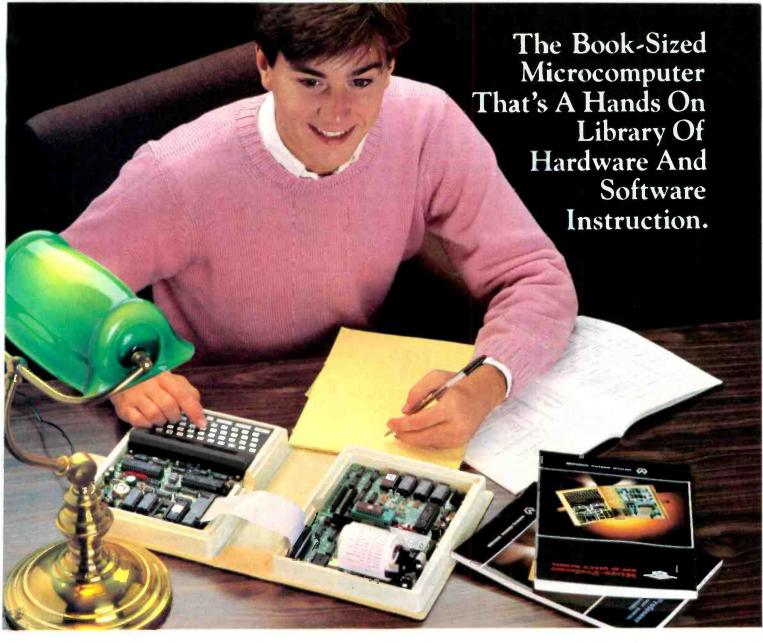The computer is available in three configurations: tape-based at \$799; one disk drive for \$1099; and two disk drives plus the optional RS-232 I/O for \$1299. We will concern ourselves only with the





#### MEET THE MICROPROFESSOR

#### A portable learning center.

Learning shouldn't be limited to the classroom. That's why we made the MicroProfessor lighter and less bulky than the average textbook. Supported by easy-to-understand documentation, the MicroProfessor leads you through dozens of experiments. And with a wealth of accessories to choose from, including a printer, EPROM programming board and sound and speech synthesis, there's virtually no limit to the kinds of applications you can try your hand at.

#### Custom tailored to a variety of educational needs.

Whether you're a computer novice or prodigy, interested in guided instruction or independent learning, the MicroProfessor will meet your educational objectives. A teaching tool without peer, the MicroProfessor puts hundreds of hands on lessons in programming, system architecture and circuit design right at your fingertips. Your computer skills will increase dramatically as the MicroProfessor translates important concepts into practical



#### The most cost-effective instructional microcomputer on the market.

Today, tight budgets are a fact of life and doubly so for educators and students. At under \$200.00 including Instruction Manual and AC Power Supply—less than half the price of any competitive product—the MicroProfessor is a very attractive educational resource.

For more information about putting the MicroProfessor advantage to work in your computer education, please write or call:



Unique Microcomputer Products for Education

CIRCLE 265 ON FREE INFORMATION CARD


195 West El Camino Real, Sunnyvale California 94097 Outside California call (800) 538-1542 In California call (408) 773-8400

two-disk model because that offers the user the best value; the others are but way-stations on the way to two disk drives.

Highlights of the two-disk Model 4 include 64K of RAM that can be user-upgraded to 128K, automatic operation in the *Model III* mode by simply using *Model III* disks, and a Model 4 mode that features an 80-column × 24-line screen with normal and reverse video, a 4-MHz Z80 CPU, and the

ability to run CP/M. Also, the computer will read and write tapes for the Model 100 "briefcase" comput-

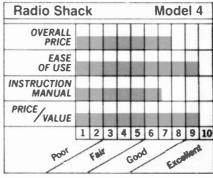The *Model 4* is very similar in appearance to the Alodel III except for color and minor, though important, keyboard improvements. Replacing the "Mercedes gray" color of the previous models—which looks great on a car but awful on a plastic cabinet—is the light beige color common to most



modern "high-tech" equipment. The keyboard, though similar to the earlier computers, now features a real CONTROL key—there is no longer a need to hold down the SHIFT key simultaneously with an UP-ARROW OF DOWN-ARROW key in order to simulate the function of the CONTROL key. Also, there are three software-definable function keys, labeled FL F2, and F3.

The two-disk configuration consists of the basic computer with TRSDOS Version 6.0 and TRSDOS 6.0 BASIC, two double-density 51/4 inch disk drives, 64K of RAM (an additional 64K of RAM can be added), and the ROM set from the Model III.

If you are wondering about the Model III ROM set, it's there to let the Model 4 act like a Model III computer. It works this way: The Model 4 is meant to handle both the new TRSDOS Version 6.0 and the CP/M disk-operating systems, both of which require that the full RAM be available from memory address 0000H. Earlier Radio Shack computers, on the other hand, located their operating (driver) routines and BASIC, in ROM, in the first 16K of memory; thus the useravailable RAM was located only in the upper 48K of memory. When the user inserts a Model III disk, the Model 4 senses the fact and automatically switches out the first 16K of RAM and switches in the Model III ROM's, causing the Model 4 computer to function as a Model III. In that way, Radio Shack has retained complete compatability with the software for their earlier computer. When the computer is run in the Model 4 mode, the full 64K of RAM is avail-

Since the Z80 microprocessor can only address 64K of memory at a time the 64K RAM upgrade (for a total of 128K) is bank-switched in

### A breakthrough Global Data Breakout Breadboards.

ow, reroute data transmission lines in any pattern... faster than ever before!

of these features plus a gigantic patchboard area for building test fixtures, modems, timers and switches

All Data Routers have two

sturdily mounted 25 pin RS-232 standard connectors for simple, fast installation. The solderless breadboarding area has nickel-silver contact

points, which assures sound electrical connections and trouble-free performance indefinitely. EIA signal mnemonics are screened on the face of each Data Router for ready reference.

And, our breakout breadboards are priced so low that you can always have several on hand.

Save time, save energy and save money. Call our Product Availability Line: 1-800-243-6077 for the name of your local distributor.

#### GLOBAL-DATA A DIVISION OF GLOBAL SPECIALTIES

An Interplex Electronics Company 70 Fulton Terrace, New Haven, CT 06512 (203) 624-3103 TWX: 710-465-1227

Choose from three Data Router models: Our basic 125 with the unique Global breadboard interface area, the 225 with 8 LED's for monitoring signals

Data Router Breakout Breadboards

from Global Data represent a significant

breakout box design innovation. With

our solderless breadboard interface

area, rewiring, testing and monitoring

data transmission lines is as quick and

easy as slipping a wire lead into a con-

tact point. To change the routing, simply

pull out the wire and insert it into another

uration, even split signals and multiple

loopback connections. There is a wide

variety of possible interface connections

You can reroute signals in any config-

contact point. That's all there is to it.

for up to 24 lines.



**CIRCLE 62 ON FREE INFORMATION CARD** 

and out by the software. It can be used as straight additional memory, or all or part can be used to function as a simulated disk (RAM disk), or as a printer spooler. If you don't install the optional 64K RAM expansion, the computer's TRSDOS operating system can use part of the basic 64K of memory for both RAM disk and spooling. (Spooling is a way to print and use the computer at the same time; it avoids tying up the computer when printing.)

By itself the Model 4 is a formidable machine, but a complete package consisting of the Model 4, CP/M (from Montezuma Micro, Box 32027, Dallas, TX 75232), and Newdos 80 (for those who use Model III and Model I software) is hard to beat. Newdos 80 is available from Apparat Inc. (4401 South Tamarac Pkwy, Denver, CO 80237). The complete package is ideal for schools, small businesses, or anyone who needs a lot of computing power at a reasonable price. R-E

#### Computer Accessories P12 Power Director

End powerline woes, add powerline conditioning, and centralize control of your computer system with this device.



CIRCLE 6 ON FREE INFORMATION CARD

IE YOUR COMPUTER SYSTEM IS LIKE most, one of its most apparent "features" is a maze of powerlines. Likewise, powering up your system might be a task worthy of a contortionist, what with all of the reaching and stretching required to hit all of the power switches. If so, you may be a candidate for a product like the P12 power director from Computer Accessories (7696 Formula Place, San Diego, CA 92121). In addition to alleviating the above conditions, the unit provides line conditioning to guard against powerline glitches.

#### The power director

The power director provides three functions. First of all, it is a six-outlet power strip. Most computer installations have a common problem—the number of power cords exceeds the number of available power outlets. The power director allows your computer and all of its peripherals to be plugged into one central location, eliminating powerline tangles in the process. A single line leads from the unit and is to be plugged into a grounded outlet.

Each of the outlets is individually controlled by front-panel mounted rocker switches. If you leave the computer's and/or peripherals' power switches permanently on, you can use those rocker switches to turn any device connected to the power director on or off. Each of the rocker switches has a pilot light to help

#### A QUALITY TRIPLE-REGULATED POWER SUPPLY AT A LOW, **LOW PRICE!!** NOT A KIT!



This DC triple regulated variable power supply has all the features you could ask for plus a full 1 year guarantee. Fully adjustable from 11/2 VDC to 35 VDCI Three completely independent supplies that offer many advantages! They can be either a pcs. supply or a neg. supply...they can also be stacked in series so that a 5V and two 15V sup-plies can total a 35 VDC supply or any combination of the three...(after one of the terminals is grounded to give it a reference)...for the first time you can now purchase this American made fully adjustable power supply at a price that is one half of what you'd expect to pay!

MODEL PS101 **FULLY ASSEMBLED & TESTED!** 

– Made In The United States -

#### **SPECIFICATIONS**

3 outputs: Fixed 5 VDC ± 0.2V 2 variable ≤11/2 V to ≥15 VCC Polarity - floating; can be used as pos. or neg.

Ripple less than 10mV at full load, Regulation ≤1% no load to full load, Line Regulation <0.2% 108 VAC to 135 VAC.

Current:

Fixed supply 1.0 amp max. Variable supplies 0.5 amp max. Protection built in, current limiting, with thermal shutdown

Power: 108-135 VAC.

Dimensions: 81/4" x 31/4" x 71/4" (WxHxD) Wood grain finished metal case.

Weight: 4 lbs., 9 ozs.

Lighted on/off power switch, easy-to-read Voltmeter and large binding posts. Warranty: one year full replacement

warranty from date of purchase

DISTRIBUTOR AND REPRESENTATIVE INQUIRIES INVITED



VISA, MASTERCARD, AMEX TELEPHONE ORDERS ACCEPTED! 6 Herman Drive, E. Granby, CT 06026 ☐ 203/651-0285 you quickly identify which switches are on or off. Finally, there is a master switch that can be used to turn on or off the entire system.


Last, and perhaps most important, the power director contains line-conditioning circuitry. The level of protection afforded by the unit exceeds that specified by the 1983 IEEE industry guide for surge voltages in low-voltage AC circuits (IEEE-587). The surge-suppression device used in the power director is General Semiconductor's

TranZorb. That device responds in less than a nanosecond to suppress transients. An RF filter is used to handle RF noise. Each outlet has line-to-line and line-to-ground protection against voltage spikes, surges, RF noise, etc.

Other features of the unit include a digital clock and a media (5½-inch floppy disk) storage slot. An option available is a *Data Director* switch box. That switch box can direct the data from your computer's serial or parallel port to any of

up to 3 peripherals.

The unit is rated for a maximum current of 15 amps and a maximum power capacity of 1800 watts. A circuit breaker is used to protect against problems caused by equipment overloads. The line-conditioning circuitry is rated for a maximum transient peak-current of 4500 amps. The RF filter has a frequency response (stop band) of 0.15 to 30 MHz. The peak-to-peak power dissipation of the the unit is rated at 10,000 watts. Maximum transient voltage is 6000. Clamp voltage is 276 volts, maximum, at 102 amps. Clamping time, as indicated earlier is less than one nanosecond.

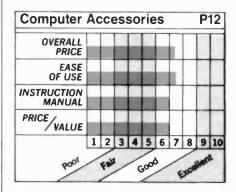


The P12 power director measures  $19\frac{1}{2} \times 2\frac{1}{4} \times 13\frac{1}{2}$ . It is sized to fit atop an IBM PC system. Other models of the power director, sized to be stacked with disk drives, or to serve as a monitor stand, are available. Those units have fewer outlets and differing specifications however. No weight was specified for the unit, but it is heavy, as the beige cabinet is made primarily of steel.

The one major complaint we had about the unit was the stiffness of the switches. Because of that stiffness, they were exceptionally difficult to operate. Perhaps that stiffness will ease with time and use, but we would have liked to have seen better quality switches used.

The "manual" that accompanied the unit was also quite skimpy, offering little besides some basic operating instructions, specifications, and warranty information.

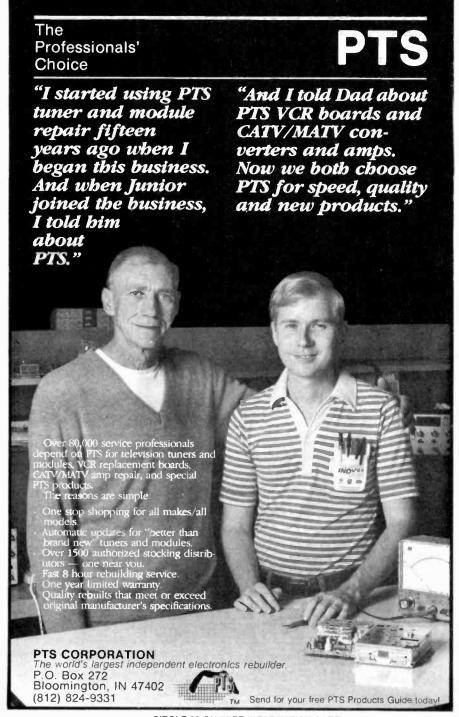The P12 power director certainly does make your computer setup more attractive and easier to use, and it has a suggested retail price of \$199.



### **NEW IDEAS**

#### Multiple-outlet control circuit

ALMOST EVERY ELECTRONIC DEVICE IS used with one or more different accessories. For example, an AM/FM receiver might have a tape deck, equalizer, and turntable connected to it. Or you may have a video system consisting of a TV set, VCR, video enhancer/stabilizer, and so on.

Each of those units has its own power-on switch, which means that if you want use one or more of those components in conjunction with the main unit (receiver or TV set), you'll have to turn on each component individually. That means that there is always the possibility that one or more components will be accidentally left on when you're finished.


There are many ways to get around that problem—for instance, you could use one of several commercially available switched outlet-strips, which can cost \$15 and up. Those products (often containing a surge suppressor) are fine for things like computers; but for other electronic devices, like stereos or TVs, they're simply not needed. There is, however, another way to go about it and save some bucks in the process.

#### Outlet control circuit

Figure 1 shows a circuit that can be use to turn on several components of an audio or video system at the same time. The beauty of that scheme is that it can be built using a handful of easy-to-get parts. But that's not all: With a little imagination and some experimenting, it can be made to do the same things that the commercial products do, making it more than worth the parts cost and time spent building it.

First you should note that the circuit draws no standby current; in other words, when a device plugged into socket SO1 is turned off, no power is supplied to SO2. You may be wondering why no switch is included in the 110-volt AC line. Well, the answer to that question will become clear as we discuss the circuit's operation.

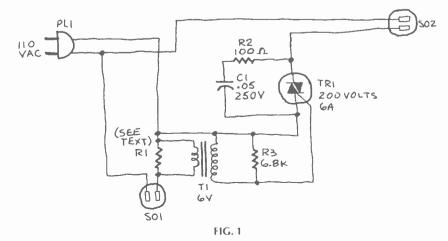One more point: T1 is a 6-volt transformer with its primary and secondary connected in reverse (i.e. the secondary in parallel with R1 and the primary feeding the Triac gate). Resistor R1 is chosen according to the load connected to SO1: If the SO1 load is 125–150 watts, R1 should be a 1-ohm, 10-watt unit. For loads of 250–300



#### **NEW IDEAS**

This column is devoted to new ideas, circuits, device applications, construction techniques, helpful hints, etc.

All published entries, upon publication, will earn \$25. In addition, for U.S. residents only, Panavise will donate their *model 333*—The Rapid Assembly Circuit Board Holder, having a retail price of \$39.95. It features an eight-position rotating adjustment, indexing at 45-degree increments, and six positive lock positions in the vertical plane, giving you a full teninch height adjustment for comfortable working.



I agree to the above terms, and grant Radio-Electronics Magazine the right to publish my idea and to subsequently republish my idea in collections or compilations of reprints of similar articles. I declare that the attached idea is my own original material and that its publication does not violate any other copyright. I also declare that this material has not been previously published.

Title of Idea			
Signature			
Print Name		Date	
Street			
City	State	-	Zıp
to: New Idea 20	a along with this s Radio-Electro 00 Park Ave. So ew York, NY 10	onics, outh,	

watts, use a .5-ohm, 10-watt resistor or you can parallel two 1-ohm, 10-watt units if desired.

When the device connected to SO1 is turned off, no current will flow because that leg of the circuit is open and therefore, there is no voltage developed across R1. (Remember the power switch on any device is used to complete a circuit.) Because there is no voltage drop across resistor R1, no voltage is fed to transformer T1. When the device plugged into SO1 is turned


on, current flows to SO1 through resistor R1 causing a small voltage to be developed across the resistor.

The voltage across R1 is then applied to the secondary of T1 (which is used as a step-up transformer), resulting in a higher output voltage at its primary. The output from T1 is fed to the gate of Triac TR1. When TR1 is turned on, power is supplied to the load at SO2. That means that the on-off function of any device connected to SO2 is

controlled by the power switch of the SO1 load. Therefore, it is not necessary to include one in the AC power line.

Additional sockets may be placed in parallel with SO2 so that any other device that you may want to use in conjunction with the main unit at SO1 may be powered up in the same manner. Just keep the 6-amp limitation of the Triac and the total current requirements of the load in mind when adding extra sockets. Also, the current rating of the Triac assumes proper heat sinking. If the 6-amp limit is a problem, you may want to check into some of the higher rated Triacs, like those listed in the ECG Replacement Guide.

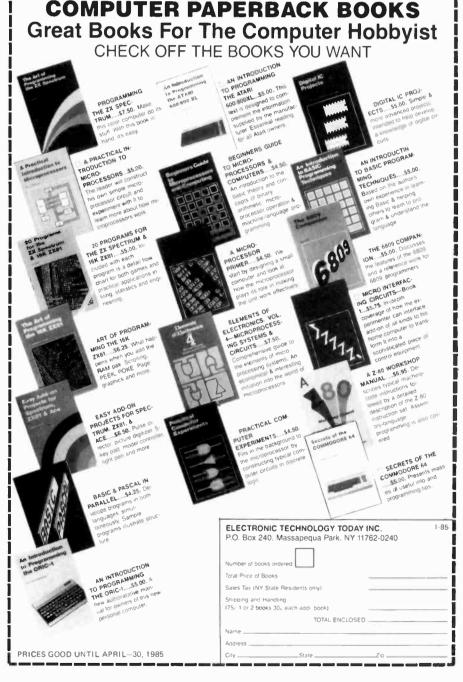Although it is not necessary, you may want to add switches in series with the extra sockets, so that any device connected to those sockets may be turned off from a central location as needed. A final note: The circuit should be mounted in a case for safety's sake. —Theodore Stern





QUALITONE INDUSTRIES INC.

DEPT. C - 696 LOCUST ST. - BOX 214 MT. VERNON. NEW YORK 10552

#### MASTER THE NEW ELECTRONICS WITH McGRAW-HILL'S

The fast, easy and low cost way to meet the challenges of today's electronic innovations. A unique learning series that's as innovative as the circuitry it explains, as fascinating as the experiments you build and explore.

From digital logic to the latest 32-bit microprocessor, the McGraw-Hill Contemporary Electronics Series puts you into the electronic picture one easy step at a time. Fifteen unique Concept Modules, sent to you one every 4-6 weeks, give you a handle on subjects like optoelectronics, robotics, integrated circuits, lasers, fiber optics and more.


Each Concept Module goes right to the heart of the matter. You waste no time on extraneous material or outdated history. It's a fast, efficient, and lively learning experience...a non-traditional approach to the most modern of subject matter.
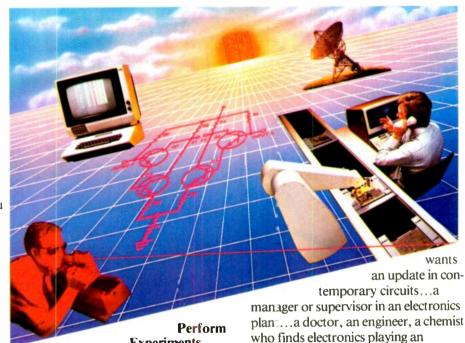
#### **Unique Interactive Instruction**

With each module, you receive a McGraw-Hill Action Audio Cassette. Each tape is a dynamic discussion that drives home the key facts about the subject. Your learning



experience is reinforced through interaction with vividly illustrated text, audio cassettes, and actual electronic experiments. Indexed binders preserve backup material, notes, and tapes for convenient referral.



**Experiments** in Contemporary Electronics

Throughout your series, laboratory experiments reinforce every significant point. This essential experience

...dynamic, hands-on demonstrations of theory in practice... will help you master principles that apply all the way up to tomorrow's latest VLSI (Very Large Scale Integrated) circuitry.

In your very first module, you'll use integrated circuits to build a digital oscillator, verifying its operation with a light emitting diode (LED). You'll learn to identify passive and active components, understand concepts common to all electronic circuits.

#### For Anyone Interested in Electronics

The Contemporary Electronics Series is designed for anyone from hobbyist to professional. It's for you if you're looking for new fields of interest...if you're a teacher who

most convenient, probably least expensive way to do it. And the only one that gives you hands-on experience.

#### 15-Day No-Risk Trial

To order your first module without risk, send the postage-paid card today. Examine it for 15 days under the terms of the order form and see how the Contemporary Electronics Series gets you into today's electronics. If card has been used, write us for ordering information.

increasingly important role in your

or technicians who feel their training

needs freshening up. It's the quickest,

work. It's even for electronics engineers



McGraw-Hill **Continuing Education Center** 3939 Wisconsin Ave. Washington, D.C. 20016

### Measures frequency to 1.2GHz

With period, period average and totalize functions too, for only \$750



The B&K-PRECISION Model 1855 is a high accuracy multifunction counter with ± 1ppm temperature stability (TCXO), with all these features:

- 5 Hz to 1.2GHz range
- 0.5 μS to 200,000 μS period range
- Totalizes to 99,999,999
- Selectable resolution 8 digit LED display
- · Low pass filter · Display hold
- Switchable X1/X10 attenuator
- · Remote start-up
- kHz, MHz, µSEC, Gate and overflow indicators

For measurements to 520MHz, the Model 1851, with the same features as the Model 1855, sells for \$575.

Both Models are available for immediate delivery from B&K-PRECISION distributors.



6460 West Contland Street
Chicago, Illinois 60635 • 312 889-9087
International Salis 6460 W. Contland St. Chicago. It. 60635
Canadian Salis Altis Electronis - Sonatar.
South and Central American Sales

### NEW PRODUCTS



**CIRCLE 11 ON FREE INFORMATION CARD** 

#### AUDIO/VIDEO CONTROL CEN-

TER, NEC model AV-200E, performs its audio functions via a 12-watt-per-channel, built-in stereo amplifier with tone control, headphone jack, and inputs for a tape deck, tuner, and auxiliary sources such as a CD player. A sophisticated synthetic-stereo circuit uses a bucket-brigade device to synthesize a stereo signal from any mono source.

Video signals are processed through a full complement of inputs and outputs, including inputs/outputs for two VCR's (one front-panel set; one rear-panel set), and two AUX inputs—all with stereo audio capabilities. Monitor output and a set of inputs and outputs for an audio tape deck are also provided. A switchable image enhancer improves contrast and sharpness for either playback or dubbing purposes.

The NEC model AV-200E is priced at \$199.00.—NEC Home Electronics (USA) Inc., 1401 Estes Avenue, Elk Grove Village, IL 60007.

**SCANNER**, model *HX750*, is a six-channel hand-held scanner that can monitor activity in six popular bands—including such services as police, fire, public safety, aircraft, business, and amateur 2-meter bands. Channels can be scanned automatically at about 15-per-second, or stepped manually.

Individual channel lock-out switches temporarily skip over unwanted channels. LED's indicate which channel is being monitored. The model *HX750* comes with an AC adapter/charger, a flexible ("rubber ducky") antenna, and a wire antenna. It offers both a built-in speaker and an earphone jack for private listening. It can be operated from a 6-volt external DC power-supply, or four standard or rechargeable AA batteries (not included). Current drain is 16 mA (stand-by, squelch on) to 70 mA at full audio output. The unit is FCC-certified (part 15, subpart C); it measures  $3\frac{1}{4} \times 5\frac{1}{2} \times 1$  inches and


38



CIRCLE 12 ON FREE INFORMATION CARD

weighs approximately nine ounces (without batteries). It is priced at \$159.95.—Regency Electronics, Inc., 7707 Records St., Indianapolis, IN 46226-9989.

MICROCONTROLLER, the model R8E is an enclosed, stand-alone programmable-control system that features real-world inputs and outputs. It is configured as a programmable controller, data logger, or interface device; both transducers and AC devices may be connected directly. Included are high and low level A/D inputs (8 channels), numerous digital-control lines, parallel and serial ports, and solid-state power relays. The

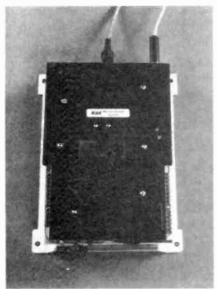

**CIRCLE 13 ON FREE INFORMATION CARD** 

controller is programmed in its resident BASIC interpreter through any terminal or CRT; no "programmer" or host system is needed. Sockets for up to 16K of ROM/EPROM or RAM are provided.

The model R8E runs on 2-volts DC or 24-volts DC and is priced at \$599.00.—HHS Microcontrollers, 5876 Old State Road, Edinboro, PA 16412.

100-MHz OSCILLOSCOPE, model 1580 features dual time-base circuitry and 5 mV/div vertical sensitivity over the 100-MHz bandwidth with 1-mV/div vertical sensitivity to 50 MHz in the  $\times$ 5 mode. The V mode can be used to display two signals unrelated in frequencv. Other features include Z-axis input; Channel-1 output; calibrated delayed sweep; X-Y operation; Channel-2 invert; 20-MHz bandwidth limiter, and a variable trigger hold-off that permits stable observation of complex pulse

The user can select from 23 calibrated sweep-time ranges from 0.5 s/div to 20 ns/div in a 1-2-5 sequence. Sweep time is fully adjustable between calibrated ranges. To allow closer examination of waveforms, a × 10 sweepmagnification feature is provided.



CIRCLE 14 ON FREE INFORMATION CARD

The triggering circuitry offers five trigger sources: CH1, CH2, EXT ernal, LINE, and V MODE. In the V MODE, each waveform displayed becomes its own trigger, thereby allowing steady display of two signals unrelated in frequency. Signals are displayed on an 8×10 div (1 div = 10 mm) rectangular CRTwith internal graticule and 16-kilovolt accelerating potential.

The model 1580 is priced at \$1,595.00.—B&K Precision/Dynascan Corporation, 6460 West Cortland Street, Chicago, IL 60635. R-E



#### **OVER 50 KITS AVAILABLE**



## CATALOG OF ALL KITS

At allable nationwide at your local electronics store.

(Or send \$1 00 shipping & handling to address below.)

#### **EKI ELECTRONIC KITS** INTERNATIONAL, INC.

791 RED ROCK ROAD ST. GEORGE, UTAH 84770

Call TOLL FREE 1-800-453-1708 For store nearest you.

Special Prices for Educators

### Where's Your ELECTRONICS Career Headed?



### The Move You Make Today Can Shape Your Future

Yes it's your move. Whether on a chess board or in your career, you should plan each move carefully. In **electronics**, you can *move ahead* faster and further with a

## B. S. DEGREE

Put professional knowledge and a COLLEGE DEGREE in your electronics career. Earn your degree through independent study at home, with Grantham College of Engineering. No commuting to class. Study at your own pace, while continuing your present job.

The accredited Grantham non-traditional degree program is intended for mature, fully employed workers who want to upgrade their careers . . . and who can successfully study electronics and supporting subjects through

#### INDEPENDENT STUDY, AT HOME

Free Details Available from:

Grantham College of Engineering 10570 Humbolt Street Los Alamitos, California 90720

#### Independent Home Study Can Prepare You

Study materials, carefully written by the Grantham staff for independent study at home, are supplied by the College, and your technical questions related to those materials and the lesson tests are promptly answered by the Grantham teaching staff.

#### **Recognition and Quality Assurance**

Grantham College of Engineering is accredited by the Accrediting Commission of the National Home Study Council.

All lessons and other study materials, as well as communications between the college and students, are in the English language. However, we have students in many foreign countries; about 80% of our students live in the United States of America.

Grantham Col 10570 Humbolt S	lege of Engine treet, Los Alamit	eering R-1-85 os, CA 90720
Please mail me you B.S. Degree indep	ur free catalog wh endent-study prog	nich explains your gram.
Name		Age
Address		
City	State	Zip

RADIO-ELECTRONICS

# BUILD THIS

Get rid of switching woes, and that "pile of spaghetti" in back of your TV set, with the "Select-A-Matic" RF switcher.

# RF SWITCHER

#### ROBERT GROSBLATT

IN THE DIM PRE-HISTORY OF THE ELECtronic age, just after the disappearance of the dinosaurs, the family television set had but one simple job—displaying broadcast TV signals (although many of you probably thought that it was to keep your children from doing their homework).

Not any more.

Today's family television set has a whole new set of functions. And it sometimes seems that not a day goes by without the development of yet another device that uses the tube for a display. Computers, videodiscs, VCR's, and videogames all compete with the simple antenna for access to the back of the set. But since the input on most televisions is limited to the two little screw terminals for the antenna, you can find yourself doing a lot of wire swapping anytime you decide to watch a tape or blast a few aliens.

That is, unless you build the Select-A-Matic. That device can take any one of eight inputs and assign it to any one of four outputs. Not only will that make it much easier to organize things, it will also help eliminate the usual pile of "spaghetti" found at the back of the set. Keyboard entry and a visual display make operation of the Select-A-Matic a snap. And even if you don't have a lot of interest in RF switching, the theory and design can easily be incorporated into audio, appliance control, or just about any area where you need to choose among several devices.

The theory behind the Select-A-Matic is evident when you take a look at Fig. 1,

the block diagram of the circuit. One input and one output are selected from a keyboard, and the control signal that results is stored in a latch at the selected part of the circuit. It's really that simple. There's nothing exotic in the parts list and the basic design of the Select-A-Matic is easy to adapt to a whole host of other uses.

The simplicity of the circuit can be seen further in Fig. 2, the schematic. Since we're dealing with eight inputs and four outputs, there are 32 possible combina-

tions we have to be able to select. Although there are several ways to handle it, the most straightforward approach is to arrange the I/O in a matrix with the inputs on the columns and the outputs on the rows as shown in Fig. 3. Selecting an input turns on the whole column and selecting an output turns on a whole row. That scheme routes the selected input exclusively to the selected output.

The easiest way to see how that theory is translated from ink to electrons is to go

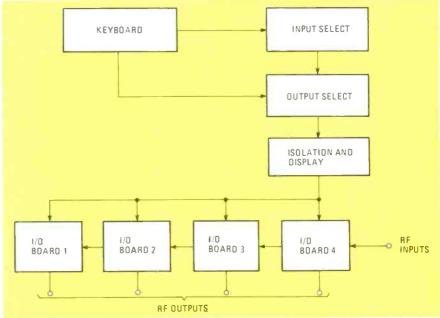


FIG. 1—BLOCK DIAGRAM of the Select-A-Matic. The unit can switch things other than RF signals by modifying the I/O boards to suit the particular application.

2 2 0 2 1 5 E = 5 2 1 R13 27042 R12 270Ω 810 27052 27052 435 48 090 台中 曹华 042 058 990 042-073 5082. 2835 590 84 254 8 本 1(510 等十 ⊕lı ĕ INPUTS 1-8 25 H(C23) 20 岩中 48 24 1/0 80ARD
1/0 80 ¥5 - (A) 心 (文 1034 (A) LEO 25 1/0 BOARD LEO 1/0 BOARD **★ 5** ★ LOGIC -08 23 STB OB \* 0110 × > ---\$ 01F 02 03 2, 14 0.2 03 50 9 90 07 0.4 90 80 0.5 04 02 03 0.5 ٠, O 03 04 0.5 GND GND 112 1C4 GND GND 105 106 1C7 D1 CLEAR DICLEAR 1, 13 D1 CLEAR 1, 13 3, 15 -108 EN 3, 15 3, 15 9 % 90 08 03 D4 90 90 0.5 12 0.7 90 03 D3 14 90 07 0.5 90 90 03 22 9 = 9 22 22 90 20 22 90 20 55 RESET 16 18 20 22 01 02 03 04 05 06 07 08 5 7 9 11 17 19 21 23 D1 D2 D3 D4 D5 D6 D7 D8 1/4 4011 101 1C3 4508 1C2 4017 ~<del>\*</del> CLEAR STB > 1/4 4011 101 2 1,13 ¥ R2 100K R9 10K R8 10 X **₩** NOTE: UNLESS OTHERWISE INDICATED: ALL CAPACITORS ARE 12pF D1-D9 ₩ 2ĕ 04 5 02 60 8 99 07 D8 1 09 **\$**8.5\$\$\$5\$₹ 1/4 4011 SIONO \* SEE TEXT 30 30 80 8 200 80 8 IC1 d 1/4 4011 \$13 SIIS \$12 254 S) 210 \$14 considerations CLEAR IN Sister Convider % § § \$ EE BER SELECT

FIG. 2—SCHEMATIC DIAGRAM of the unit. Note that the unit is built on five PC boards: which components mount on which boards is clearly noted in this illustration. Refer to the text for grounding

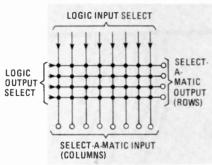


FIG. 3—IN THE SELECT-A-MATIC, switching is handled using a matrix arrangement.

back to the schematic and follow the operation of the circuit. IC1-a and IC1-b are half a 40H quad NAND gate set up as a gated oscillator running at about 8 kHz. That simply means that a high on pin 2 turns the oscillator on, and a low turns it off. The output is connected to the clock input of IC2, a 4017 decade counter. That IC sequentially turns each of its outputs high as long as pin 13, the ENABLE input. is held low. When one of the INPUT SELECT switches, S1 to S9, is closed, nothing happens until that particular output of the 4017 goes high. As soon as it does, one of the corresponding keyboard diodes. D1 to D9, is forward biased; that disables both the clock (through ICI-d) and IC2 (by presenting a high to its ENABLE input).


That same high also stores the selected column information in IC3, a 4508 dual quad latch. Although that IC has two separate quad latches, we've set it up-and shown it in the schematic-as an octal latch by connecting the control pins of each side in parallel. Pins 2 and 14 control the IC's inputs. When they're high, data presented to the inputs will be stored, and when they're low, the inputs are ignored. Closing one of the input switches, therefore, selects one of the inputs and stores it in the "column" latch. You should also notice that we're able to get an input-clear function for free by selecting one of the 4017 outputs that's not connected to IC3. That's taken care of by connecting the CLEAR IN switch to pin 9, an unused output of the 4017. When it's pressed, eight lows are stored in IC3, overwriting any other data that was stored there.

Pins 3 and 15 of the 4508 are the output control pins. Bringing them low will enable the outputs, and making them high will put the IC in its high-impedance mode. Since there's no need for that in the circuit all these pins are connected together and tied low, permanently enabling the outputs of all the 4508's in the circuit. The importance of that can be seen by looking at the row selectors, IC4 to IC7. The inputs of those IC's are all in parallel and are connected to the outputs of IC3. If IC3 was allowed to go to its high-impedance state, the inputs of IC4 to IC7 would be able to float and, since we're dealing with CMOS, that is a definite nono.

The operation of the row selector is much the same as the column selector. Closing one of the OUTPUT SELECT switches, S11 to S14, causes the selected IC to store whatever information is presented at its inputs. Since the outputs are always enabled, they follow the inputs, and the selected control signals are available on the appropriate line of the 32-bitwide output bus. Selecting one input and one output, therefore, will turn on one of the output, control lines. Since the outputs are grouped in four rows of eight lines, selecting an output for IC4, for example, won't change the information stored in 1C5 to 1C7, the other output

Turning off the outputs can be done one of two ways. You can press the CLEAR IN key and then select the output you want to turn off. That will store a low in each cell of the output latch and turn off everything controlled by it. Closing switch \$10 will turn off all the outputs as well as clearing the input latch, IC3. That happens because all the CLEAR pins of the 4508's are tied together and pressing \$10 brings them all high. Ordinarily they're controlled by ICI-c. That gate is set up as a power-on reset to make sure that all the latches are cleared when the Select-A-Matic is first turned on, Resistor R5 and capacitor C2 generate a negative pulse at power up. The pulse is cleaned up and inverted by ICI-c, causing a short positive pulse to be sent through R3 to all the clear pins of all the latches. After that, the clear pin is held low unless \$10 is closed.

Each of the output control lines go through a IN914 diode and an LED. Both of those devices help isolate the digital control circuitry from the things they're controlling. The LED's also serve to show which outputs are turned on, but it's interesting to note that they're also used as old fashioned diodes. The great majority of the circuits that have LED's in them use them only as status indicators of one kind or another and it's easy to forget that they're really diodes, not some kind of long lasting light bulb. One side benefit of

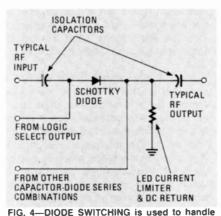

the RF switching in the Select-A-Matic. Because they can handle the frequencies involved, Schottky diodes are used.

using them like this is they don't have to have their own current limiting resistors. You can't forget about that altogether because some other part of the circuit can take care of it.

The RF switching of the Select-A-Matic is a straightforward application of diode switching. Figure 4 makes it a lot easier to see what's going on. The input signal passes through a capacitor to isolate the source of the signal from the DC control voltages generated by the Select-A-Matic. The next thing the signal sees is a Schottky diode that does the actual switching in the circuit. As long as the Select-A-Matic has the output turned off. the diode is turned off. When the output is turned on, the diode is forward biased and starts conducting. The input RF passes through the diode, the output capacitor, and shows up at the output connector of the Select-A-Matic. The resistor not only provides the DC return for the Schottky diode, it also serves as the current limiter for the LED.

#### The layout

As you can see, the basic operation of the Select-A-Matic is easy to understand and, although we're using it to switch RF, the same approach can be used to switch just about anything. The PC layout (the foil patterns for the boards are shown in Figs. 5, 6, and 7) was designed with the aim of making the Select-A-Matic as versatile as possible. All the digital control circuitry is located on the main logic board (see Figs. 5 and 6). The output bus shows up at the far end of that board and is grouped conveniently in four groups of nine solder pads—the ninth connection is system ground. If you want to switch audio signals, for example, you only have to design your analog I/O (to replace the RF LO used by this project) and connect it to the logic I/O on the logic board of the Select-A-Matic.

The I/O boards of the Select-A-Matic (see Fig. 7) have female connectors (see Fig. 8) to mate with right-angle male connectors on the logic board making the assembly of the whole unit a plug-in operation. The connectors used are header strips with 0.1-inch spacing. Of course you can replace the board connectors with wire, but since we're switching RF, vou'll have to be really careful about length, layout, and shielding. The frequencies being switched by the Select-A-Matic can go up as high as 800 MHz., (the top of UHF), and signal behavior can get really strange when you get up in that kind of rarefied atmosphere. Stray capacitance, leakage, and some unplanned-for resonance are only a few of the pitfalls that can completely foul up the operation of the circuit. If you take a look at the foil pattern for the I/O boards, you'll see that component leads are kept as short as possible and several options are provided for handling

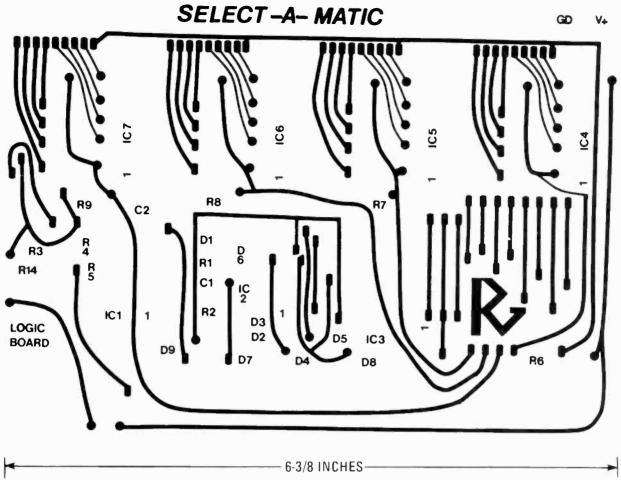


FIG. 5—COMPONENT SIDE of the double-sided logic board. The board is shown full sized.

ground.

A ground plane is provided for both the RF ground, (at the top of the board), and logic ground, (at the bottom of the board). The answer to how you should handle this is a resoundingly unsatisfying "it depends." There are as many theories about grounding as there are about why the dinosaurs disappeared. The best approach is to try various things and decide what works best. It pains us to say this, but as far as this problem is concerned, a logical approach is no help whatsoever. Anyone who uses a simple dipole antenna for FM knows that there is a prescribed way to orient it. They also know that the best orientation is usually found by bunching it up and throwing it on the floor!

Pads are provided on the I/O board to connect RF and logic ground as well as mounting holes if you want to surround all the components on the RF circuit with a metal shield. You should use shielded cable to go from the chassis-mounted F-connectors at the back of the unit to the I/O boards. There are places on the I/O board to connect the cable shield (see Fig. 9). But whether connecting the shield there, elsewhere, or nowhere works best is something you'll have to find out by experiment.

For what it's worth, here's what hap-

pened in our case. We had a lot of trouble with crosstalk when we first assembled the Select-A-Matic. We got rid of it completely by lining the inside of the case with aluminum foil (see Fig. 10). That tied together all the RF grounds at the chassismounted F-connectors. We connected the shield of the cable on the case side but left it unconnected at the I/O boards. Jumpers on the I/O boards were used to connect the RF and logic ground. That eliminated all of our crosstalk problems. If it had not, the next step would have been to build shields for the I/O boards—probably with aluminum foil at first and then with copper foil so we could solder a connection from the shield to the board. Fortunately that nightmare was unnecessary in our

Since signal strength in our location is very good, the slight loss of signal through the Schottky diodes didn't present us with any problem. You may find that to be different—it all depends where you live. In general, signals that come in well won't be degraded much by putting the Select-A-Matic in the signal path. If, however, you're looking at reception that's marginal even on a good day, you've got a problem. You can use the Select-A-Matic to handle home-grown RF from such things such as VCR's, videogames,

and the like, but broadcast signals are probably out of the question unless you add an RF amplifier to the Select-A-Matic output lines. That can be a one-transistor circuit or anything you need to get the job done.

#### Construction

There's nothing especially difficult about constructing the Select-A-Matic if you use PC boards. As previously mentioned, the foil patterns for that board, one of which is double-sided, are shown in Figs. 5. 6. and 7: the parts placement diagrams are shown in Figs. 9 and 11. Wirewrapping or breadboarding are unsuitable because of the frequencies running around the circuit. The breadboarded version we built worked, but the performance of the circuit was terrible. When it was put on PC boards, noise, crosstalk, rejection, and all the other things that had been a problem completely disappeared. Remember, CMOS digital signals are just about noise immune-even if you grind the wires into the ground with your heel. Look cockeyed at RF and the whole circuit can go bananas

The power supply for the Select-A-Matic is designed to be located elsewhere. All you've got is a jack for a small wall unit that puts out more than 5- but less

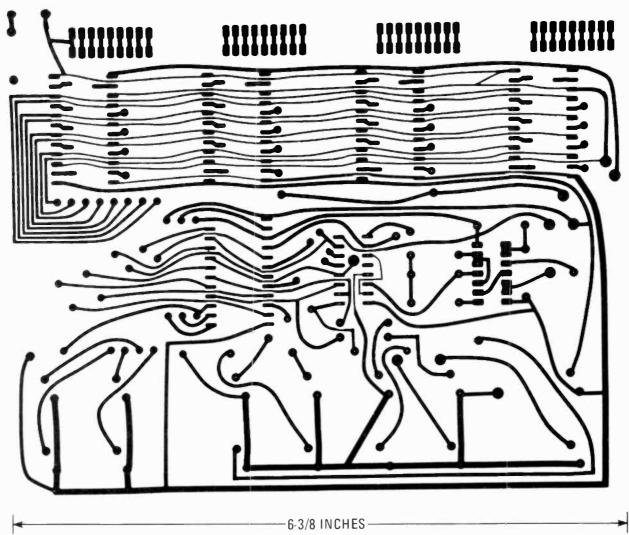


FIG. 6-FOIL SIDE of the logic board. The board is shown here full sized.

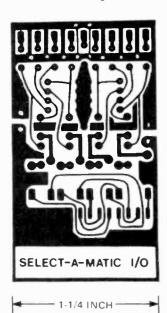


FIG. 7—FOIL SIDE of the I/O board. Four of these single-sided boards are required.

than 7-volts DC with a reasonably small amount of ripple. If you use one that's really noisy, you can put a nice chunky capacitor across the pins of the jack on the

chassis. If it's really a problem isolate the circuit by putting a resistor in series between the power supply and the Select-A-Matic—you can use the power jack for that as well. Since the whole circuit draws less than 20 mA, a value around 200 ohms should be in the ballpark. You can also leave out the protection diode on the  $\pm V$  line, but it's always better to be safe than sorry.

The switches used in the Select-A-Matic are soldered directly to the logic circuit board. They're made by Oak Switches and the pin spacing on the board was designed to accommodate them.



FIG. 8--HEADER STRIPS are used to make the connections between the I/O boards and the logic board.

Those switches are brand new (and a special thank you to Henry Richter. Inc. for providing them to us for use in this project), but should be available from most Oak distributors by the time you read this. If you have a hard time finding them, you can make up a wiring harness and locate the switches off the board. The same is true of LED33, the power pilot-light. Just make sure you keep the leads straight and remember that the current limiter for that LED, R14, is located on the board.

When you're assembling the board, watch the polarity of all the diodes, especially the Schottky diodes. These are a lot more expensive than your garden-variety diodes and it's distressing, to say the least, to break one when you solder it. We used those diodes because they're fast enough and have a low enough turn on voltage to be perfect for UHF mixing. Although we haven't tried it. IN914 or IN34A germanium diodes could be used as well, but we don't know how far up the spectrum you'll be able to go before signal loss gets excessive. All we can tell you is they work for channel three but we don't know if they can even make the frequency jump found around Channel 6. If you want

to try them, go ahead.

Since the logic board is double-sided, you'll have to solder feedthroughs from one side of the board to the other. Thread hookup wire back and forth through the indicated holes (marked with an asterisk in Fig. 11), solder on both sides and then cut it off. We tried to do all the side jumping on component legs, but there aren't a lot of components on the board so there are quite a few stand alone feedthroughs.

Use IC sockets, caution, and common sense to keep potential problems from the board. And make sure you use a low-wattage iron when you're soldering the diodes—glass-cased diodes are really fragile.

One note on the I/O board. While there are four such boards required, only one is shown in the interest of space. All four

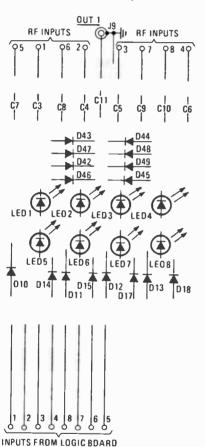


FIG. 9—PARTS PLACEMENT DIAGRAM for the I O boards. Note that only board 1 is shown; four I/ O boards in all are used by the project (see text).

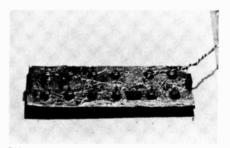


FIG. 10—TO ELIMINATE CROSSTALK, the inside of the case was lined with aluminum foil.

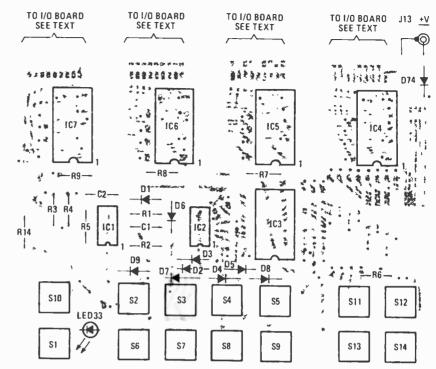


FIG. 11—PARTS PLACEMENT diagram for the main logic board. Note that—although not marked by an asterisk—feed throughs are required at the I'O connections.

#### **PARTS LIST**

All resistors ¼ watt, 5%, unless otherwise noted
R1, R3, R4, R6–R9—10,000 ohms

R1, R3, R4, R6–R9—10,000 ohms R2, R5—100,000 ohms R14—1000 ohms

R10-R13-270 ohms

Capacitors

C1, C2-.01µF, ceramic disc

C3-C38-12pF, ceramic disc

Semiconductors

IC1-4011 quad NAND gate

IC2—4017 decade counter

IC3-IC7-4508 dual guad Latch

D1-D41-1N914 diodes

D42-D73-5082-2835 Schottky diodes

D74-1N4001 diode

LED1-LED34-miniature LED's

S1-S14-SPST switch, momentary

boards are identical. In other words, where board I (shown) uses eight 12-pF capacitors (C3–C10), board 2 (not shown) uses eight 12-pF capacitors (C11–C18) and so on. A quick look at the schematic (Fig. 2) should help remove any confusion; which components go on which board is clearly shown there.

#### **Troubleshooting**

If the unit doesn't work when you get it all assembled, and it probably won't the first time, use all the standard troubleshooting techniques. The most suspect things are mechanical—solder bridges, bad joints, components in backwards, and all of the rest of the usual stuff. If everything seems OK as far as that goes, then start suspecting the components. Is the clock clocking? Are signals showing up

pushbutton (Oak 225) S15—SPST switch, toggle J1-J12—F-type connectors, chassis mount

J13-miniature jack

Miscellaneous: PC boards, aluminum foil for shield, case, wire, solder, male header strips, right angle (AP products 929835 or equivalent), female header strips (AP products 929974 or equivalent), etc.

A set of the five PC boards, etched and drilled, but not plated through, is available from Hal-Tronix, PO Box 1101, Southgate, MI 48195. The price is \$39.95. Please add \$2.00 for shipping and handling. MI residents add 4% tax.

where they should?—but you've heard all of that before. Exercise simple caution and you shouldn't have any major problems (famous last words). Actually, though, the circuit is simple enough to severely limit the number of problems you can have. Save all your energy for figuring out how to take care of the ground.

If you find that nothing you do will solve the kinds of RF problems we talked about before, you always have the option of substituting small relays for the Schottky diodes and capacitors (RF). That kind of last resort solution should work no matter what the problem is. And you'll be able to switch anything—including audio and video. Another benefit you'll get is that the coil resistance of the relay will probably be great enough to work as a current limiter for the LED's.

# ALL ABOUT THERMISTORS

HARRY L. TRIETLEY

Here's an article designed to make you feel at ease with thermistors.

This month, we'll look at thermistor basics.

WE ALL KNOW WHAT THERMISTORS ARE. The name "thermistor" itself gives us a good idea: THERMal resISTOR—a device whose resistance changes with temperature. While you might be familiar with those devices from building one of the projects you've seen in Radio-Electronics that used them, do you really know how to design with them?


Thermistors are highly nonlinear—and often only loosely defined—devices. That's the reason why even many experienced engineers and circuit designers do not feel at ease with them. But once you get familiar with them, you'll find that thermistors are actually quite straightforward. That's what this article is for: to

help you become familiar with thermistors. This month, we'll study the basics of thermistors—how they're made, what types are available, the equations and specifications that describe them, and how they typically behave. After we go through the basics, we'll present design techniques, circuit examples, and applications ideas.
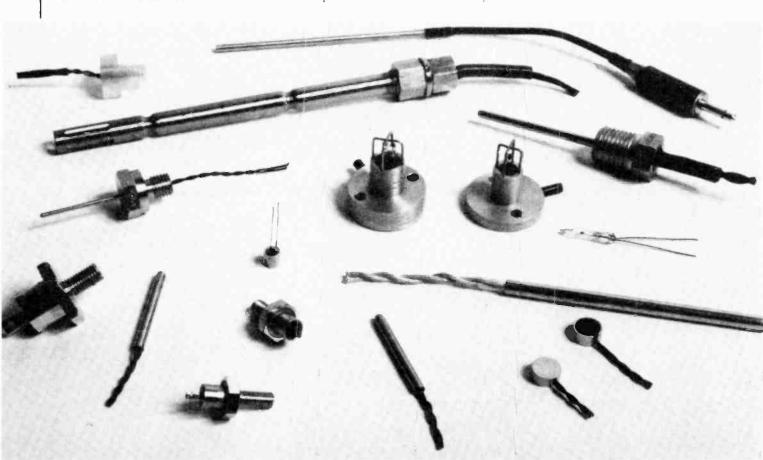
#### Thermistor basics

We should start off by saying that not all devices that change resistance with temperature are called thermistors. For example, resistance thermometers are made from small, wirewound coils or from deposited metal films. While they are temperature dependent, they don't behave like thermistors. The term thermistor is generally reserved for thermally sensitive *semiconducting* devices.

There are two general classes of thermistors: NTC (Negative Temperature Coefficient) and PTC (Positive Temperature Coefficient). There are two distinctly different types of PTC thermistors manufactured. One is produced by means similar to NTC thermistors, the other is made of silicon. We will cover PTC's only briefly, reserving most of the space for the much more common NTC's. In fact, from this point on, unless we specify otherwise, we will be talking about NTC-type thermistors.



NTC thermistors are narrow-range, nighly sensitive, nonlinear devices whose resistances decrease with increasing temperature. Figure 1—a curve relating resistance change to temperature—shows typical resistance-temperature characteristics. The sensitivity is about 4–5%/°C (1°C = 2.5°F). A wide range of resistance is available, and resistance changes may be many ohms or even kilohms per degree.

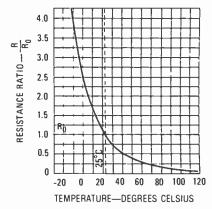


FIG. 1—NEGATIVE TEMPERATURE COEFFI-CIENT thermistors are very sensitive and highly nonlinear. Ro may be ohms, kilohms, or megohms.

Basically, thermistors are semiconducting ceramics. They are formed from powdered metal oxides (usually nickel and manganese oxides), sometimes with small amounts of other oxides added. The powdered oxides are mixed with water

TABLE 1— RESISTANCE-TEMPERATURE CHARACTERISTICS OF TYPICAL NTC THERMISTORS

Temperature	100() @ 25°C	1K @ 25°C	10K @ 25°C	1MEG @ 25°C
−80°C (−1112°F)	14.47K	278.80K	3558K	
−70°C (−94°F)	7475	132.60K	1694K	
– 60°C ( – 76°F)	4066	66.78K	845.9K	
−50°C (−58°F)	2315	35.39K	441.3K	
−40°C (−40°C)	1374	19.64K	239.8K	
−30°C (−22°F)	846.0	11.35K	135.2K	
- 20°C ( - 4°F)	538.9	6815	78.91K	
– 10°C (14°F)	354.1	4232	47.54K	
0°C (32°F)	239.2	2710	29.49K	3966K
10°C (50°F)	165.9	1785	18.79K	2238K
20°C (68°C)	117.7	1206	12.26K	1299K
30°C (86°F)	85.4	834.0	8194	774.5K
40°C (104°F)	63.1	589.5	5592	473.2K
50°F (122°F)	47.5	424.8	3893	295.9K
60°C (140°F)	36.4	311.9	2760	189.1K
70°C (158°F)	28.3	233.0	1990	123.3K
80°C (176°F)	22.3	176.9	1458	81.98K
90°C (194°F)	17.8	136.2	1084	55.48K
100°C (212°F)	14.3	106.4	816.8	38.20K
110°C (230°F)			623.5	26.76K
120°C (248°F)			481.8	19.03K
130°C (266°F)			376.4	13.74K
140°C (284°F)			297.2	10.05K
150°C (302°F)			237.0	7447

and various binders to form a sturry, which is formed into the desired shape and sintered (fired) at temperatures above 1000°C (1832°F). A conductive metal coating (generally silver) is fired on, and leads are added. The finished thermistor is usually coated with epoxy or glass, or otherwise packaged.

MOUNTED BEAD

RODS

BEADS

PROBE ASSEMBLIES

BEADS

BEADS

FIG. 2—A BROAD VARIETY OF thermistor styles and assemblies are available. Shown here are some of the more common.

As you can see from Fig. 2, there is a wide variety of thermistor styles available. Those styles include discs and washers from under 0.1 inch to an inch or so in diameter, and rods of various dimensions. Some thermistors are formed first as large, flat sheets, then diced to form squares. Very small bead thermistors are made by firing a drop of the slurry directly on a pair of high-temperature platinum alloy lead wires, then dipping the thermistor in glass to coat it.

#### Typical specifications

To say "typical specifications" is misleading—there are very few typical specifications for thermistors. The wide variety of thermistor styles, sizes, shapes, resistances, and tolerances that are available creates an equally wide variety of specifications. What's more, thermistors offered by different manufacturers often are not interchangeable with one another.

Table I lists resistance versus temperature for a few commercially available devices. You can buy thermistors with resistances (at 25°C-which is how a thermistor's resistance is normally specified) as low as one ohm and as high as ten megohms or more. A thermistor's size and shape influence its resistance, but for any given style the manufacturer can provide a five- or six-decade range of resistance values simply by changing the oxide mixture. Changing the mixture also changes the shape of the resistance-temperature (R-T) curve and influences the stability at high temperatures. Fortunately, thermistors that have resistances high enough to be useful at high temperatures also tend to be more stable.

Inexpensive thermistors usually have fairly loose specifications. For example, resistance tolerances (again at 25°C) range from  $\pm 20\%$  down to  $\pm 5\%$ . At higher or lower temperatures, those specifications loosen further. For a typical thermistor with a sensitivity of 4% per degree C, the corresponding temperature measurement tolerances are around  $\pm 5$  to  $\pm 1.25$ °C ( $\pm 9$  to  $\pm 2.2$ °F) at 25°C. Much higher precision is available at costs generally ranging from \$2.00 on up, depending on specifications. We will explore high-precision thermistors later in this article.

We stated earlier that thermistors are narrow-range devices. That should be clarified: Most thermistors operate from  $-80^{\circ}$  to  $+150^{\circ}$ C (112 to  $+302^{\circ}$ F), and units are available (generally glass coated) which work to 400°C (752°F) and beyond. For practical purposes, however, the high sensitivity of thermistors limits their useful temperature range. A typical thermistor's resistance may change by 10,000 or 20,000 to one between -80 and +150°C. You can imagine the difficulty of trying to design a circuit that will accurately measure both ends of such a range (unless you use range switching). A thermistor having a useful resistance at zero degrees will be no more than a few ohms at 400°C.

Most thermistors use solder to attach their leads internally. Obviously, you can't use such a thermistor to measure temperatures higher than the melting point of solder. Even without solder, their epoxy coatings are good only to around 200°C (392°F). For higher temperatures it is necessary to use glass-coated thermistors with welded or fired-in lead wires.

Stability considerations also limit hightemperature use. Thermistor structures tend to change when left at high temperatures, and the rate and type of change is greatly affected by the oxide mix and the way that the thermistor is manufactured. Epoxy-coated thermistors begin to drift a bit at temperatures above 100°C (212°F) or so. If such a thermistor is operated continuously near 150°C, it may drift by several degrees in a year. Low-resistance thermistors (below, say, 1000 ohms at 25°C) often are worse—they can drift noticeably when used at about 70°C (158°C) and become unreliable by 100°C.

Inexpensive, loosely specified devices are produced with less attention to detail and can give even worse results. On the other hand, some properly constructed glass-coated thermistors have excellent stability at even higher temperatures. Glass-coated bead thermistors show excellent stability as do the glass-coated disc thermistors that have recently become available. Remember that drift depends on time as well as temperature. So, for example, you can generally use an epoxy-

coated thermistor for brief times at 150°C without significant shifts.

When using thermistors you must be aware of the specification for dissipation constant. A small epoxy-coated thermistor, for example, will have a dissipation constant around one milliwatt per degree C in still air. In other words, one milliwatt of power in the thermistor will raise its internal temperature by one degree C; two milliwatts will raise it by two degrees, etc. If you apply one volt to a 1K thermistor with a dissipation constant of I mW/°C, you will produce a measurement error of 1°C. Thermistors will dissipate more power if they are immersed in liquids. The same small epoxy-coated thermistor we used in our example will dissipate 8 mW/°C in well-stirred oil. Larger thermistors have better dissipation constants than smaller devices. For example, a one-inch disc or washer may dissipate 20 or 30 milliwatts per °C in air. Keep in mind that as the thermistor's resistance changes with temperature, so does its power dissipation.

#### Thermistor equations

There is no such thing as an exact equation to describe a thermistor's behavior: there are only approximations. We will look at two commonly used approximations.

The first approximation, an exponential, is reasonably good over limited temperature ranges, especially when using non-precision thermistors. The second, known as the Steinhart and Hart equation, provides excellent precision over ranges as wide as 100°C.

The resistance of an NTC thermistor decreases *approximately* exponentially with increasing temperature. Over limited temperature ranges its R-T curve is described reasonably well by:

$$R_{T2} = R_{T1}e^{\beta\left(\frac{1}{\tau_2} - \frac{1}{\tau_1}\right)}$$

where Tl and T2 are absolute temperatures in degrees Kelvin (°C + 273);  $R_{T1}$  and  $R_{T2}$  are the thermistor's resistances at Tl and T2, and  $\beta$  is a constant, determined by measuring the thermistor at two known temperatures.

If beta and  $R_{T1}$  are known, this equation can be rearranged and used to calculate temperature by measuring the resistance:

$$\frac{1}{T2} = \frac{1}{T1} + \frac{1}{\beta} \ln \frac{R_{T2}}{R_{T1}}$$

Beta is a large, positive number whose units are degrees Kelvin. Typical values run from 3000 to 5000°K. Manufacturers often include a value for beta in their specifications but, since the exponential equation is only an approximation, the value of beta depends on the two temperatures

used to calculate it. Some manufacturers use 0 and 50°C; others, 25 and 75°C.

Other temperatures may be used: you can compute your own values for beta from the manufacturer's resistance-temperature tables. The equation will typically agree with measured values to within ±1°C over a span of 100°C. The equation should not be trusted very far beyond the temperatures used to find beta.

Before going on to the Steinhart and Hart equation let us look at two other terms often used to specify thermistors: alpha (α) and ratio. Alpha is simply the slope of the R-T curve—the sensitivity, at some particular temperature. Alpha is usually specified as a "percent per degree." Typical values run between 3% and 5%/°C. Like beta, alpha depends on the temperatures at which it is measured. Its value decreases somewhat at higher temperatures.

The ratio term is simply the ratio of the resistance at one temperature (usually 0 to 25°C) to the resistance at a second, higher temperature. For example, the 0°/50°C ratio of the 10-kilohm thermistor shown in Table 1 is 7.58. Beta may be computed from this ratio and vice versa. Typical values of the 0°/50°C ratio are between 5 and 10.

When using precision thermistors, you generally will have a degree-by-degree chart of resistance versus temperature furnished in the manufacturer's data. Sometimes, however, it is handy to have a precise equation when doing design calculations or (especially) when using a computer to convert the thermistor's resistance to temperature. Except for very narrow temperature spans, the single-term exponential is not good enough: more terms are needed.

The best approximation in common use today is known as the Steinhart and Hart equation:

$$\frac{1}{T} = a + b \ln R + C (\ln R)^3$$

where T is the absolute temperature (in degrees Kelvin), R is the thermistor's resistance, and a, b, and c are experimentally determined constants.

Rewriting the equation to show resistance as a function of temperature results in a rather messy-looking equation. However, it is easily handled using a computer or programmable calculator:

$$R = \exp\left[\left[-\frac{\alpha}{2} + \left(\frac{\alpha^2}{4} + \frac{\beta^3}{27}\right)^{12}\right]^{13} + \left[-\frac{\alpha}{2} - \left(\frac{\alpha^2}{4} + \frac{\beta^3}{27}\right)^{12}\right]^{13}\right]$$
where  $\alpha = \frac{a - \frac{1}{T}}{c}$  and  $\beta = \frac{b}{c}$ 

We should point out that these values of alpha and beta are *not* related to the alpha and beta used with the single-term exponential equation.

Although the Steinhart and Hart equation is more complex, it generally agrees with the actual thermistor to within a few thousandths of a degree over spans as wide as 1000°C. Of course, it can be that good only if the experimental thermistor data is equally accurate. Temperatures accurate to thousandths of a degree can be provided only in top-grade laboratories. You will probably want to rely on the manufacturer's tables rather than try to provide your own measurements.


To find a, b, and c it is necessary to know the thermistor's resistance precisely at three temperatures and substitute each set of data (R and T) into the Steinhart and Hart equation, in three unknowns. (The unknowns are a, b and c.) Algebra must then be used to simultaneously solve the three equations to find the three constants. Using the manufacturer's tables, choose R versus T data at each end and at the middle of the temperature range you plan to use. Manufacturer's generally do not provide specified values of a, b and c, since they vary depending on your temperature range.

#### **Precision thermistors**

Ordinary thermistors are specified only to between ±5% and ±20% at 25°C, with looser tolerances at other temperatures. With proper manufacturing control and measurement, however, much better precision is possible. Three types of precision thermistors are available: precision interchangeable discs, precision beads, and matched-curve bead pairs. Precision thermistors allow readout instruments to be electronically calibrated without the need for precise temperature sources. Interchangeable thermistors also allow replacement of the thermistor without recalibrating the electronics.

Precision interchangeable disc thermistors are manufactured with careful control and measurement of the R-T characteristics and stability of the oxide mixture. Mixes that don't conform to precise specifications are discarded. The thermistors are mixed, shaped and fired using normal techniques. Then, in a fluid bath at a carefully controlled temperature, each thermistor is ground to bring its resistance to a specified value. Before shipment, each thermistor is measured at two or three temperatures and discarded if it does not meet specifications.

You can buy stocked, cataloged tolerances between 0 and  $70^{\circ}\text{C}$  of  $\pm 0.2^{\circ}\text{C}$  or  $\pm 0.1^{\circ}\text{C}$ , with accuracies loosening to about  $+1^{\circ}\text{C}$  at -80 and  $+150^{\circ}\text{C}$ . Special high-stability glass-coated disc thermistors are offered with tolerances as tight as  $0.05^{\circ}\text{C}$ . Figure 3 shows the resistance-and temperature-tolerance characteristics

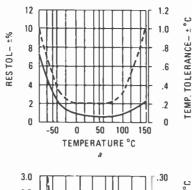

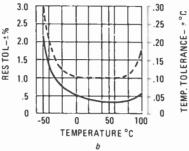


FIG. 3—TEMPERATURE AND RESISTANCE TOLERANCE for precision interchangeable thermistors. The dotted lines show temperature tolerance ( $\pm$ °C) and the solid lines show resistance tolerance ( $\pm$ %). In a, we see the curves for a  $\pm$ 0.2°C thermistor, while in b we see the curves for a  $\pm$ 0.1°C thermistor.

need to make precision measurements with beads (which offer the ultimate in small size and high-temperature operation), you can ask the manufacturer to provide a measurement and printout of each thermistor's R-T curve. Or, you can specify thermistors selected to a specific resistance and tolerance at one temperature.

Another way in which bead manufacturers provide precision and interchangeability is to routinely measure each thermistor, then connect selected matched pairs in series or parallel to match a specific curve.

#### Thermal behavior

Thermistors are resistors. They obey Ohm's law  $(E = I \times R)$ —until you change their temperature. Remember that it takes only a few milliwatts to raise a thermistor's temperature by one degree or more and that the resistance will drop by about 4% per degree C. If you connect a current source to a thermistor, and slowly increase the current, you will see the voltage rise more and more slowly as the thermistor's resistance decreases. Eventually the voltage will stop rising al-

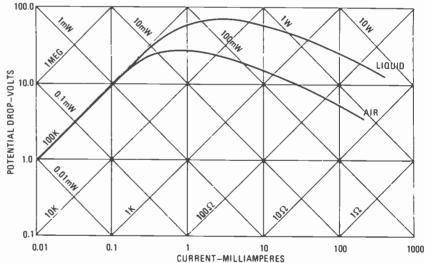


FIG. 4—THE RESISTANCE OF AN NTC thermistor drops as it is heated by high currents until it eventually enters a negative-resistance mode.

for typical interchangeable thermistors.

Those high-precision, interchangeable thermistors are available only as small size discs or squares coated with epoxy or (for higher stability) glass. Several manufacturers offer some or all of the following resistances at 25°C: 100, 300 and 500 ohms, 1.0, 2.252, 3.0, 5.0, 10.0, 30.0, 50.0, 100.0, and 300.0 kilohms and 1.0 megohm. The 2.252, 3.0 and 5.0K thermistors are interchangeable among manufacturers, the other generally are not. A variety of temperature probes that use 2.252K thermistors are available.

Bead thermistors can be very precise and very stable, but their small size and methods of construction make it impossible to grind them to an exact value. If you together, then actually drop as the current is increased further. The graph of Fig. 4 shows typical voltage-versus-current curves. Also on the graph are lines indicating constant resistance and constant power dissipation. At low current and low power, the curve follows a line of constant resistance, showing that the thermistor is not being heated very much. As the power increases, you can see that its resistance begins to drop. At the high-power end of the curve, the thermistor, in a sense, acts as a negative resistance in that its voltage goes down as the current goes up.

That's all we have room for now. Next time, we'll continue with our look at thermistor basics and then turn our attention to some practical applications.

# BUILD THIS

Part 2 LAST MONTH, WE looked at the basic approach we'll follow to store the contents of Atari 2600 game cartridges on audio cassette tape. We also looked at the hardware that's required, and briefly studied how cassette I/O is handled. This time,


discussing cassette I/O. Figure 5 showed a flowchart that described the cassette-read algorithm. Let's look at the software in more detail to see how it's used to detect the data and sync pulses. (Remember that sync pulses are sent out every 2 milliseconds. Data pulses are sent between the

might wonder why we write 2000 zero bits and look for only 50. There's a very practical reason: It allows the automatic gain control (AGC) of most recorders enough time to settle down.

After the recorder finds 50 consecutive zero bits, it keeps on looking until it finds

# ATARI Game Recorder

**GUY VACHON and DAVID A. CHAN** 

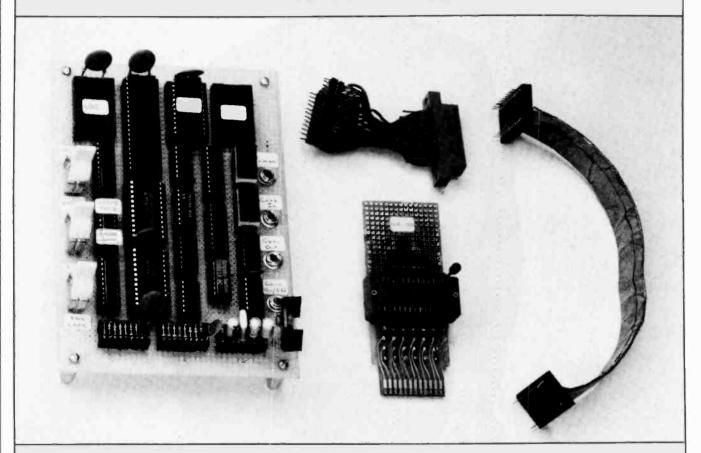

You can record the contents of your Atari 208 videogame cartridges on audio cassette tape! This month, we'll take a look at the software that's needed.

we'll look at the software in more depth. Then we'll see how we can build the game recorder and put it to use.

#### Game-recorder software

The complete software listing for the game recorder's operating system appears in Table 1. Note that it is written in Z80 mnemonics. Although we won't be discussing the software line by line, you might want to study Table 1 to get the details.

When we left off last time, we were

sync pulses—a pulse represents a 1 bit, while the lack of a pulse represents a zero bit.)

When the contents of a game cartridge is written to a cassette tape, a header of 2000 zero bits preceeds the actual beginning of the program bits. After the header, the game recorder also writes a (user-selected) label before each game. When the game recorder reads the contents of a cassette tape, its software looks for fifty consecutive zeros to decide that it has found the beginning of a game program. You

a I bit. It then checks the name tag, which is output to the LAST GAME FOUND display. If the name tag matches the name of the game you selected, it keeps on reading bytes and storing them in the RAM. If the tag doesn't match, the game recorder keeps looking for another start-of-game beader. (We'll give more details on that—and other operation aspects of the computer—a little later on in this article.)

You may recall that a parity bit is added to each instruction so that the game recorder will recognize when something

# At CIE, you get electronics career training from specialists.



If you're interested in learning how to fix air conditioning, service cars or install heating systems— talk to some other school. But if you're serious about electronics... even earning an Associate Degree... come to CIE—The Electronics Specialists.

#### Why trust your education and career future to anything less than a specialist?

You shouldn't. And you certainly don't have to.

If you talked to some of our graduates, chances are you'd find a lot of them shopped around for their training. They pretty much knew what was available. And they picked CIE as number one.

Be sure to shop around. Because, frankly, CIE isn't for evervone.

There are other options for the hobbyist. If you're the ambitious type—with serious career goals in electronics-take a close look at what we've planned for you at CIE.

#### What you should look for first.

Part of what makes electronics so interesting is it's based on scientific discoveries—on ideas! So the first thing to look for is a program that starts with ideas and builds on them!

That's what happens with ClE's Auto-Programmed®Lessons. Each lesson takes one or two principles and helps you master them -before you start using them!

How practical is the training?

This is the next big important question. After all, your career will be built on what you can doand on how well you do it.

Here are ways some of ClE's career courses help you get your "hands-on" training...

With CIE's Personal Training Laboratory...


you learn and review the basicsperform dozens of experiments. Plus, you use a 3-in-1 precision Multimeter to learn testing, checking, analyzing!

When you get your own 5MHz, solid-state **oscilloscope**, you take some real professional steps. You use it as a doctor uses an X-ray nachine-to "read" waveform atterns...lock them in...study, nderstand and interpret them!

Vhen you get your Digital earning Laboratory, you'll be into digital theory—essential training today for anyone who wants to keep pace with the state of the art of electronics. With ClE's Digital Lab, you'll be applying in dozens of fascinating ways the theory you've learned. For example, you'll compare analog and digital devices. You'll learn to make binary to decimal conversions and to work with semiconductor devices and circuits. You'll see how digital equipment is vital to today's exciting, growing fields such as security... where digital theory provides the brains for space-age alarm and protective devices.

You'll build your Microprocessor Training Laboratory, a working microcomputer—from "scratch." You'll also learn how to program and interface it with displays, memories, switches, and more.

Earn An Associate Degree from CIE.

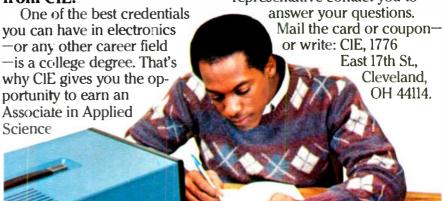

in Electronics Engineering Technology. Any CIE career course can offer you credit toward the degree...more than half of the number needed in some cases.

You can also prepare for the government-administered FCC (Federal Communications Commission) Radiotelephone License, General Class. It can be a real mark in your favor... government-certified proof of your specific knowledge and

#### Shop around...but send for CIE's free school catalog first!

Mail the card. If it's gone, cut out and mail the coupon. If you prefer to write, mention the name and date of this magazine. We'll send you a copy of ClE's FREE school catalog-plus a complete package of independent home study information! For your convenience, we'll try to have a representative contact you to

East 17th St., Cleveland. OH 44114.

### Cleveland Institute of Electronics, Inc.

East 17th Street, Cleveland, Ohio 44114 Accredited Member National Home Study Council

YES... I'm shopping around for the right kind of career training in electronics and CIE sounds well worth looking into. Please send me my FREE CIE school catalog-including details about the Associate Degree program-plus my FREE package of home study information!

Print Name				
Address		Apt		
City	State	Zip		
Age	Area Code/Phone No			
Chack how for	G L Bill information:   Veteran	☐ Active Duty		

MAIL TODAY!

RE-01

# RADIO ELECTRONI

#### IABLE 1-GAME-RECORDER SOFTWARE

```
CURRENT GAME OUT
                                  EQU 8000H
                                                          LOOPD:
                                                                     DEC
GAME_SEL_OUT
                                  EQU ØAØØ0H
                                                                     JP
                                                                          NZ.LOOPD
INPUT
                                  EQU
                                        ØCØØØH
                                                                     LD
                                                                          A,(INPUT)
RAM FIRST BYTE ADD
                                  EQU
                                        4000H
                                                                     AND
                                                                          04H
ROM_FIRST_BYTE_ADD EQU
LAST_PLUS_1_BYTE_RAM_HIGH EQU
LAST_BYTE_ADD_RAM EQU
                                        2000H
                                                                     JP
                                                                          NZ,LAB3
                                        50H
                                                                     EXX
                                                                                            START OF DOWNLOAD
                                        4FFFH
                                                                                            ; PROGRAM
START OF INITIALIZATION
                                                                                            TURN ON DECIMAL
                                                                     LD
                                                                          A,C
           .Z80
                                                                                            ; POINT
                A,00H
           LD
                                  ;CLEAR LEDS
                                                                     EXX
           EXX
                                                                          80H
                                                                     OR
           LD
                B.A
                                                                     LD
                                                                          (GAME SEL OUT), A
                                                                          DE,01F4H
           LD
                (CURRENT GAME OUT), A
                                                          BLOCIN:
                                                                     LD
                A,3FH
           LD
                                                          LOOPE:
                                                                     LD
                                                                          HL,XX2
                                                                                            ;FIND 500 ZEROS
           LD
                C,A
                                                                     JP
                                                                          BITIN
           LD
                (GAME SEL OUT),A
                                                                     JP
                                                          XX2:
                                                                          C.BLOCIN
           EXX
                                                                     DEC
                                                                          DE
START OF MAIN PROGRAM
                                                                     LD
                                                                          A,E
LOOP1:
           LD
                A,(INPUT)
                                  ;SEE IF INC GAME
                                                                     ADD
                                                                          A,D
                                  : PUSHED
                                                                     JP
                                                                          NZ,LOOPE
           AND
                01H
                                                                     JP
                                                                          C.LOOPE
           JP
                NZ, LAB1
                                                          LOOPF:
                                                                     LD
                                                                          LH,XX3
                                                                                            :FIND 1ST BIT OF 1ST
           LD
                A,ØFFH
                                  ;WAIT AND CHECK
                                                                                            : BYTE
                                  : INPUT AGAIN
                                                                     JP
                                                                          BITIN
LOOPA:
           DEC
                                                          XX3;
                                                                     HP
                                                                          NC,LOOPF
                                                                          A,01H
           JP
                NZ,LOOPA
                                                                     LD
                                                                                            ;GET 1ST BYTE
           LD
                A,(INPUT)
                                                                     LD
                                                                          B,07H
           JP
                NZ,LAB1
                                                                     LD
                                                                          IX.XX4
           EXX
                                  START OF INC GAME
                                                                     JP
                                                                          BYTEIN
                                  ; PROGRAM
                                                          XX4;
                                                                     AND
                                                                          0FH
                                                                                            ;CONVERT TO 7 SEG
           LD
                A,B
                                                                                            ; AND DISPLAY
           INC
                                                                     LD
                                                                          IY.XX5
           AND
                ØFH
                                                                     JP
                                                                          CONVERT
           LD
                B,A
                                                          XX5:
                                                                     LD
                                                                          (CURRENT GAME OUT), A
           EXX
                                                                     LD
                                                                                            SEE IF CORRECT
           LD
                IY.XX1
                                                                                            ; GAME
           JP
                CONVERT
                                                                     EXX
XX1:
           EXX
                                                                     LD
           LD
                C,A
                                                                     EXX
           EXX
                                                                     CP
           LD
                (GAME_SEL_OUT)A
                                                                     JP
                                                                          NZ,BLOCIN
           LD
                DE.7FFFH
                                  ;WAIT HALF A SECOND
                                                                     JD
                                                                          DE,RAM_FIRST_BYTE ADD
LOOPB:
           DEC
                Α
                                                                                            :GET REST OF BLOCK
           LD
                A.E
                                                          LOOPG:
                                                                     I D
                                                                          A.00H
           ADD
                A,D
                                                                     LD
                                                                          B.08H
           JP
                NZ,LOOPB
                                                                     LD
                                                                          IX.XX6
           JP
                C.LOOPB
                                                                     JP
                                                                          BYTEIN
                                                          XX6:
                                                                     LD
                                                                          (DE),A
;CONTINUATION OF MAIN PROGRAM
                                                                     INC
                                                                          DE
                A,(INPUT)
LAB1:
          LD
                                  ;SEE IF COPY PUSHED
                                                                     LD
                                                                          A.D
           AND
                02H
                                                                     CP
                                                                          LAST_PLUS_1_BYTE_RAM_HIGH
           JP
                NZ.LAB2
                                                                     JP
                                                                          NZ.LOOPG
           LD
                A,ØFFH
                                  ;WAIT AND CHECK
                                                                     LD
                                                                          CE, ØFFFFH
                                                                                            :WAIT ONE SECOND
                                  : INPUT AGAIN
                                                          LOOPH:
                                                                     DEC CE
LOOPC:
           DEC
                                                                     LD
                                                                          A,E
           JP
                NZ.LOOPC
                                                                     ADD
                                                                          A,D
           LD
                A,(INPUT)
                                                                     JP
                                                                          NZ.LOOPH
                02H
           AND
                                                                     JP
                                                                          C,LOOPH
           JP
                N7.1 AB2
                                                                     EXX
                                                                                            TURN OFF DECIMAL
           LD
                DE, RAM FIRST BYTE ADD
                                                                                            ; POINT
                                  START OF COPY
                                                                    LD
                                                                          A.C
                                  : PROGRAM
                                                                     EXX
                HL, ROM_FIRST BYTE ADD
           LD
                                                                          (GAME SEL OUT), A
                                                                     LD
           LD
                BC.1000H
           LDIR
                                                          CONTINUATION OF MAIN PROGRAM
CONTINUATION OF MAIN PROGRAM
                                                          LAB3:
                                                                          A,(INPUT)
                                                                    LD
                                                                                            ;SEE IF RECORD
LAB2:
          LD
                                  SEE IF DOWNLOAD
                A,(INPUT)
                                                                                           : PUSHED
                                  ; PUSHED
                                                                          08H
                                                                    AND
           AND
                04H
                                                                     JP
                                                                          NZ,LAB4
           JP
                NZ,LAB3
                                                                    LD
                                                                          A, ØFFH
                                                                                            :WAIT AND CHECK
           LD
                A.ØFFH
                                  :WAIT AND CHECK
                                                                                            ; AGAIN
                                  : INPUT AGAIN
                                                         LOOPI:
                                                                    DEC A
```

#### **TABLE 1 (continued)**

TABLE 1 (continued)							
	JP LD AND	NZ,LOOPI A,(INPUT) Ø8H		LAB5:	EX	AF,AF'	;RECALL BYTE & ; FLAGS AND CHECK ; PARITY
	JP EXX	NZ,LAB4	;START OF RECORD ; PROGRAM	PERROR:	JP JP LD	PO,PERROR (IX) A,94H	;ERROR, DISPLAY
	LD EXX	A,C	TURN ON DECIMAL POINT		LD LD	(CURRENT_GAME	
	OR LD LD	80H (GAME_SEL_OUT DE,07D0H		;BITIN SUB	JP ROUTI	(IX)  NE - GETS ONE BIT I	_
LOOPJ:	PJ: AND 0FFH ;OUTPUT 2000 ZEROS ;HL = RETURN ADDRESS LD HL,XX7 ;RESULT: BIT IS CARRY JP BITOUT ;USES: D',E',H'						
XX7:	DEC LD	DE A,E		;CANNOT A	AFFEC	T: DE,B,A	
	ADD JP JP	A,D NZ,LOOPJ C,LOOPJ		BITIN:	EXX LD	D,A	;START OF BITIN ; PROGRAM ;EXCHANGE
	EXX	·	;OUTPUT BLOCK ; ADDRESS	LOOPM:	LD	A,(INPUT)	; REGISTERS AND ; STORE A ;FIND HIGH
	LD EXX OR	A,B ØFØH		LOOPINI.	AND JP	10H Z,LOOPM	
XX8:	LD JP LD	IX,XX8 BYTEOUT DE,RAM FIRST E	RYTE ADD	LOOPN:	LD DEC JP	E,8FH E NZ,LOOPN	;WAIT 1MSEC
LOOPK:	LD	A,(DE)	OUTPUT BLOCK		LD	E,ØCH	;SEE IF 1 OR Ø FOR ; Ø.25MSEC
XX9:	JP INC	IX,XX9 BYTEOUT DE		LOOPO:	AND CCF	A,(INPUT) 1ØH	
7,7,0	CP JP	LAST_PLUS_1_E NZ,LOOPK	<del>-</del> -		JP DEC		
LOOPL:	DEC LD	DE,ØFFFFH DE A,E	;WAIT ONE SECOND	LAB6:	JP CCF LD	NZ,LOOPO E,5DH	;WAIT Ø.65MSEC
	JP	A,D NZ,LOOPL		LOOPP:	DEC JP LD	E NZ,LOOPP A,D	;RECALL A,
	JP EXX	C,LOOPL	;TURN OFF DECIMAL ; POINT				; EXCHANGE REGS & ; RETURN
	EXX				EXX JP	(HL)	
LAB4:	JP	(GAME_SEL_OUT LOOP1	T),A	;BYTEOUT ;IX = RETI		OUTINE - WRITES A	BYTE ONTO TAPE
;IX = RETU	JBROU JRN AI	ITINE - GETS ONE B' DDRESS	YTE FROM TAPE	;GIVEN: A ;USES: B ;CALLS: BI ;CANNOT	IS BYT TOUT	E	
;RESULT: A	S # BI	TS LEFT		BYTEOUT:	LD	B,08H	;START OF BYTEOUT ; PROGRAM ;OUTPUT BYTE
;USES: B ;CALLS: BI ;CANNOT A		: DE		LOOPQ:	RLC LD JP	HL,XX12 BITOUT	,0017018112
BYTEIN:	LD JP	HL,XX10 BITIN	;START OF BYTEIN ; PROGRAM :GET ENTIRE BYTE	XX12:	JP AND	B NZ,LOOPQ OFFH	COMPUTE AND
XX10:	RLA DEC	В			JP CCF	PO,LAB7	OUTPUT PARITY
	JP AND EX	NZ,BYTÉIN ØFFH AF,AF'	COMPUTE PARITY	LAB7:	LD JP	HL,XX13 BITOUT	
	LD JP	HL,XX11 BITIN	GET PARITY BIT	XX13:	JP	(IX)	- 0.170
XX11:	JP	C,LAB5	;SEE IF ERROR BY ; CHECKING 'CARRY' ; THEN	;HL = RET ;GIVEN: C/	TURN A		I ONTO TAPE
	JP JP	AF,AF' PE,PERROR (IX)		;USES: C ;CALLS: PULSE ;CANNOT AFFECT:DE,B,A			

			TABLE 1 (cont	inued)			
BITOUT:	EX	AF,AF	START OF BITOUT		LD	A.06H	
			PROGRAM		JP	(IY)	
	SCF		STORE ORIGINAL	LABB:	CP	02H	
			BYTE AND FLAGS	EADD.	JP	NZ,LABC	
	LD	IY,XX14	OUTPUT 1ST PULSE		LD	A,5BH	
	JP	PULSE			JP	(IY)	
XX14:	LD	C,6BH	:WAIT	LABC:	CP	03H	
LOOPR:	DEC			CADO.	JP	NZ,LABD	
	JP	NZ,LOOPR			LD	A,4FH	
	EX	AF,AF'	GET ORIGINAL FLAGS		JP	(IY)	
			AND BYTE	LABD:	CP	04H	
	LD	C,A	STORE ORIGINAL	2,00.	JP	NZ,LABE	
			BYTE ONLY		LD	A,66H	
	EX	AF,AF'			JP	(IY)	
	LD	A,C		LABE:	CP	05H	
	EX	AF,AF'		CAUL.	JP	NZ,LABF	
	LD	IY.XX15	OUTPUT 2ND PULSE		LD	A,6DH	
	JP	PULSE	,		JP	(IY)	
XX15:	LD	C,6BH	:WAIT	LABF:	CP	06H	
LOOPS:	DEC			LADI.	JP		
	JP	NZ,LOOPS			LD	NZ,LABG A,7DH	
	EX	AF AF	:RECALL ORIGINAL				
	1116		BYTE AND RETURN	LABG:	JP CP	(IY) 07H	
	JP	(HL)	, D. IE AND HEIOIN	LADG.			
					JP	NZ,LABH	
:SUBROUT	NE PU	LSE - WRITE A PULS	SE ONTO TAPE		JP	A,07H	
					JF	(IY)	
:IY = RETL	JRN AD	DRESS		I ARH			
;IY = RETU;GIVEN: PU				LABH:	CP	08H	
;IY = RETU				LABH:	CP JP	08H NZ,LABI	
;IY = RETU ;GIVEN: PU ;USES: C	LSE IF	CARRY		LABH:	JP LD	08H NZ,LABI A,7FH	
;IY = RETU ;GIVEN: PU ;USES: C	LSE IF	CARRY			CP JP LD JP	08H NZ,LABI A,7FH (IY)	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A	LSE IF	CARRY	START OF PULSE	LABH:	CP JP LD JP CP	08H NZ,LABI A,7FH (IY) 09H	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A	LSE IF	CARRY ::DE,B	;START OF PULSE : PROGRAM		CP JP JP CP JP	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A	LSE IF	CARRY :DE,B A,00H	PROGRAM		CP JP LD JP CP JP LD	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A	LSE IF	CARRY ::DE,B	; PROGRAM ;SET OUT IF	LABI:	CP JP DP CP JP LD JP	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY)	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A	LSE IF	CARRY :DE,B A,00H	PROGRAM		CP LD CP LD FC FC FC	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE:	LSE IF AFFECT LD JP	CARRY  CDE,B  A,00H  NC,LAB8  80H	: PROGRAM :SET OUT IF : REQUIRED	LABI:		08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE:	LSE IF  AFFECT  LD  JP  OR	CARRY  DE,B  A,00H  NC,LAB8	: PROGRAM :SET OUT IF : REQUIRED _OUT),A	LABI:	CP	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A.6FH (IY) 0AH NZ,LABK A,77H	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE:	LSE IF  AFFECT  LD  JP  OR	CARRY  DE,B  A,00H  NC,LAB8  80H (CURRENT_GAME	: PROGRAM :SET OUT IF : REQUIRED	LABI: LABJ:	C	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY)	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE:	LSE IF  AFFECT  LD  JP  OR  LD  LD	CARRY  DE,B  A,00H  NC,LAB8  80H (CURRENT_GAME C,24H	: PROGRAM :SET OUT IF : REQUIRED _OUT),A	LABI:	C	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE:	LSE IF AFFECT LD JP OR LD	CARRY  DE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C	: PROGRAM :SET OUT IF : REQUIRED _OUT),A	LABI: LABJ:	6 4 6 4 6 4 6 4 6 4 6 4 6 4 6 4 6 4 6 4	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE:	LSE IF  AFFECT  LD  JP  OR  LD  LD  DEC  JP	CARRY  DE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT	LABI: LABJ:	0-0-0-0-0-0-0-0-0	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE:	LSE IF  AFFECT  LD  JP  OR  LD  DEC  JP  LD  DEC  JP  LD	CARRY  DE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT	LABI: LABJ: LABK:	0,00,00,00,00,00,00,00	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY)	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE:	LSE IF  AFFECT  LD  JP  OR  LD  LD  DEC  JP	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT	LABI: LABJ:	0-11-0-	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE:	LSE IF  AFFECT  LD  JP  OR  LD  DEC  JP  LD  LD  LD  LD  LD  LD  LD  LD  LD	CARRY  DE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT	LABI: LABJ: LABK:	646464646464646464	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8:	LSE IF  LD  JP  OR  LD  DEC  JP  LD  LD  LD  LD  LD  LD  LD  LD  LD  L	CARRY  DE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT TURN OFF OUT),A	LABI: LABJ: LABK:	6+6+6+6+6+6+6+6+6	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT:	LSE IF  IFFECT  LD  JP  OR  LD  DEC  JP  LD  LD  LD  DEC  JP  LD  LD  NE CO	CARRY  DE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT	LABJ: LABK: LABK:	645464546464646464646464646464646464646	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY)	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU	LSE IF  IFFECT  LD  JP  OR  LD  DEC  JP  LD  LD  JP  LD  LD  LD  LD  LD  LD  LD  LD  LD  L	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT TURN OFF OUT),A	LABI: LABJ: LABK:	6+6+6+6+6+6+6+6+6+6	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU ;GIVEN: A IS	LSE IF  FFECT  LD  JP  OR  LD  DEC  JP  LD  LD  DEC  JP  LD  LD  DEC  JP  LD  DEC	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS E CONVERTED	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT TURN OFF OUT),A	LABJ: LABK: LABK:	646464646464646464646464	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH NZ,LABN	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU ;GIVEN: A IS	LSE IF  FFECT  LD  JP  OR  LD  DEC  JP  LD  LD  DEC  JP  LD  LD  DEC  JP  LD  DEC	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT TURN OFF OUT),A	LABJ: LABK: LABK:	6+6+6+6+6+6+6+6+6+6+6	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH NZ,LABN A,5EH	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU ;GIVEN: A IS ;RESULT: A	LD JP OR LD LD JP NE CO IS TO BE IS COM	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H  C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS E CONVERTED NVERTED DATA	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT  TURN OFF OUT),A  DATA TO 7 SEGMENT	LABJ:  LABK:  LABL:  LABM:	64	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH NZ,LABN A,5EH (IY)	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU ;GIVEN: A IS ;RESULT: A	LD JP OR LD LD JP NE CO IS TO BE IS COM	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS E CONVERTED	; PROGRAM ;SET OUT IF ; REQUIRED OUT),A ;OUT AND WAIT ;TURN OFF OUT),A ; DATA TO 7 SEGMENT ;START OF CONVERT	LABJ: LABK: LABK:	6+6+6+6+6+6+6+6+6+6+6+6	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH NZ,LABN A,5EH (IY) 0EH	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU ;GIVEN: A IS ;RESULT: A	LSE IF  IFFECT  LD  JP  OR  LD  DEC  JP  LD  LD  JP  NE CO  IRN AD  STO BE  IS COI  CP	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H  C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS E CONVERTED NVERTED DATA  00H	PROGRAM SET OUT IF REQUIRED OUT),A OUT AND WAIT  TURN OFF OUT),A  DATA TO 7 SEGMENT	LABJ:  LABK:  LABL:  LABM:	84548454845484548454845484	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH NZ,LABN A,5EH (IY) 0EH NZ,LABO	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU ;GIVEN: A IS ;RESULT: A	LSE IF  FFECT  LD  JP  OR  LD  DEC  JP  LD  LD  DEC  JP  NE CO  RN AD  STO BE  IS CO  CP  JP	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS E CONVERTED NVERTED DATA  00H  NZ,LABA	; PROGRAM ;SET OUT IF ; REQUIRED OUT),A ;OUT AND WAIT ;TURN OFF OUT),A ; DATA TO 7 SEGMENT ;START OF CONVERT	LABJ:  LABK:  LABL:  LABM:	6+6+6+6+6+6+6+6+6+6+6+6+6	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH NZ,LABN A,5EH (IY) 0EH NZ,LABO A,79H	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU ;GIVEN: A IS	LSE IF  FFECT  LD  JP  OR  LD  DEC  JP  LD  LD  LD  LD  LD  CO  JP  LD  CO  JP  LD  CO  JP  LD  JP  NE  CO  CP  JP  LD  JP  LD  LD  LD  LD  LD  LD  LD  LD  LD  L	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS E CONVERTED NVERTED DATA  00H  NZ,LABA A,3FH	; PROGRAM ;SET OUT IF ; REQUIRED OUT),A ;OUT AND WAIT ;TURN OFF OUT),A ; DATA TO 7 SEGMENT ;START OF CONVERT	LABJ:  LABK:  LABL:  LABM:  LABN:	64546454646464646464646464646464	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH NZ,LABN A,5EH (IY) 0EH NZ,LABN A,5EH (IY) 0EH NZ,LABO A,79H (IY)	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU ;GIVEN: A IS ;RESULT: A	LSE IF  FFECT  LD  JP  OR  LD  DEC  JP  LD  LD  LD  LD  LD  LD  JP  CO  JP  LD  JP  NEN AD BE  SIS COO  JP  LD  JP  LD  JP  NEN AD BE  JP  LD  JP  NEN AD BE  JP  JP  JP	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS CONVERTED NVERTED DATA  00H  NZ,LABA A,3FH (IY)	; PROGRAM ;SET OUT IF ; REQUIRED OUT),A ;OUT AND WAIT ;TURN OFF OUT),A ; DATA TO 7 SEGMENT ;START OF CONVERT	LABJ:  LABK:  LABL:  LABM:	6+6+6+6+6+6+6+6+6+6+6+6+6+6	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH NZ,LABN A,5EH (IY) 0EH NZ,LABO A,79H (IY) A,71H	
;IY = RETU ;GIVEN: PU ;USES: C ;CANNOT A PULSE: LAB8: LOOPT: ;SUBROUTI ;IY = RETU ;GIVEN: A IS ;RESULT: A	LSE IF  FFECT  LD  JP  OR  LD  DEC  JP  LD  LD  LD  LD  LD  CO  JP  LD  CO  JP  LD  CO  JP  LD  JP  NE  CO  CP  JP  LD  JP  LD  LD  LD  LD  LD  LD  LD  LD  LD  L	CARRY  CDE,B  A,00H  NC,LAB8  80H (CURRENT_GAME  C,24H C NZ,LOOPT A,00H (CURRENT_GAME (IY)  NVERT - CONVERTS DRESS E CONVERTED NVERTED DATA  00H  NZ,LABA A,3FH	; PROGRAM ;SET OUT IF ; REQUIRED OUT),A ;OUT AND WAIT ;TURN OFF OUT),A ; DATA TO 7 SEGMENT ;START OF CONVERT	LABJ:  LABK:  LABL:  LABM:  LABN:	64546454646464646464646464646464	08H NZ,LABI A,7FH (IY) 09H NZ,LABJ A,6FH (IY) 0AH NZ,LABK A,77H (IY) 0BH NZ,LABL A,7CH (IY) 0CH NZ,LABM A,39H (IY) 0DH NZ,LABN A,5EH (IY) 0EH NZ,LABN A,5EH (IY) 0EH NZ,LABO A,79H (IY)	

has been misrecorded. If incorrect parity is detected when the computer is reading from the tape, it will stop reading, and the LAST GAME FOUND display will show a message of three horizontal bars to indicate an error.

Before we go any further, we should talk a little about the memory mapping used in the game recorder. The system ROM resides from 0000H to 1FFFH. (Note that a capital "H" indicates that a number is written in hexadecimal.) The game cartridge occupies the second 8K block—2000H to 3FFFH. The game re-

corder's RAM is located from 4000 to 5FFFH. Cassette I/O and the displays are also memory mapped: The block from 800 0H to 9FFFH is used for the LAST GAME FOUND display and the cassette data output, while the block from A000H to BFFFH is used for the GAME SELECTED display and for the remote cassette control. The cassette data input and the switches are memory mapped from C00 0H to DFFFH. Note that two 8K blocks (6 000H–7FFFH and E000H–FFFFH) are not used.

The easiest job that our computer has to

do is to read the program ROM. As it operates now, the computer can copy all  $2K \times 8$  ROM's and  $4K \times 8$  ROM's. As you might expect, it is possible to modify the recorder to copy  $8K \times 8$  ROM's. Note, for example, that although an 8K block was left available for program-storage RAM, the hardware as presented has provision for only 4K.

We'll talk more about how to expand the unit to record larger programs, and show you how to build and use it, when we continue our look at the Atari game recorder next time.

R-E

# BUILD\_THIS



Part 2 NOW THAT WE KNOW how our FET power amplifier works, let's now turn our attention to building the unit

#### Building the amplifier

It is essential that a printed-circuit board be used for the amplifier. Figures 6 and 7 show foil patterns for the component and solder side respectively. Note that one board is required for each channel. If you don't want to eich your own boards. etched, pre-drilled, and plated-through boards are available; see the Parts List for information. If you do want to etch your own boards from the patterns shown, keep in mind that the board uses plated-through holes. You can, of course, get around that by soldering some of the components. including the output transistors, on both sides of the board. Note that the wiring to the output transistors is incorporated in the PC-board layout. That keeps the wire lengths to the output devices to a minimum. (It also simplifies construction by eliminating 48 wires, reducing the chance of error in that particularly critical area!)

Get high performance and high fidelity from this FET stereo amplifier. It feels equally at home in your living room or in a disco!

Before we begin with the construction details, we should point out that the values shown in the schematic are for 1%-tolerance resistors. For most applications, it is not essential that you use such parts. Thus, the parts list also shows acceptable values for 5%-tolerance resistors. (One source for 1% resistors is Digi-Key Corporation. Highway 32 South, P.O. Box 667. Their River Falls, MN 56701.)

Once you have your boards and components, you can begin construction by referring to the parts-placement diagram in Fig. 8 and by installing the fixed resistors. Check the values with an ohmmeter as you go, and be sure that the leads are sufficiently far from the ground plane!

Next, install capacitors, carefully checking values and ensuring that the polarized electrolytic types are properly oriented. Follow by installing the diodes.

except for D3-D5. (Those three diodes mount on the output-transistor heat sink. and should not be installed yet.) Again, be careful of the polarity—the diode band indicates the cathode. Next, install the transistors (except for the output transistors Q21-Q28). Transistors Q19 and Q20 should be mounted with insulators and heatsink compound. (If you look closely at Fig. 9, you'll see some heatsink compound around those transistors.) Transistors Q12, Q13, Q15, and Q18 use TO-5-type heat sinks.

Adjust potentiometers R8 and R19 to their middle positions and install. (For R19, which is a multiturn potentiometer, you will need to use an ohmmeter.) You will have to make L1: Wind 15 turns of 16gauge magnet wire on R42. Solder to the leads of R42, and install the assembly. The PC boards are now complete

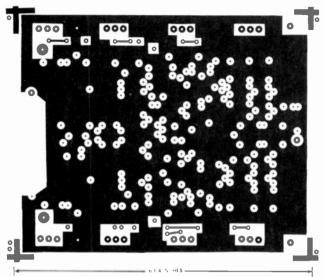


FIG. 6—THE COMPONENT SIDE of the amplifier board is mainly used as a ground plane.

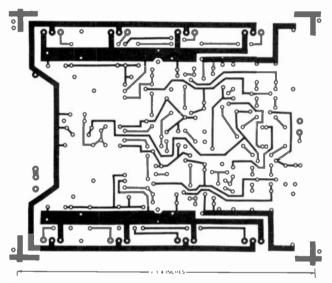


FIG. 7—THE SOLDER SIDE of the amplifier board. Remember that you need one board for each channel.

#### Preparing the heat sink

The Wakefield heat sinks that are used for the output transistors (see Fig. 10) were not chosen arbitrarily. Their design is almost 100% more efficient for natural convection applications than conventional designs of equivalent volume.

You can use other heat sinks but a minimum surface area of 800 square inches per channel is required. A flat-backed heat sink is desirable for the TO-220 package, but is not essential.

The Wakefield type 512 is available in a 14-inch long extrusion, which needs to be cut in half to yield the two 7-inch pieces called for. After you cut it, drill holes for the output transistors according to the layout shown in Fig. 11. To keep the transistor-mounting hardware to a minimum, you might want to drill and tap the heat sink. However, screws with nuts may also be used. The optional over-temperature sensor and thermal-compensating diodes

D3-D5 should also be glued to the heat sink as shown in Fig. 11.

If you have a confined-space application, you can mount the two heat sinks back to back; they will then readily accept a muffin fan for forced convection. For home applications, however, we recommend natural convection—to eliminate the noise, filter, and/or temperature-sensing aspects typically associated with fans. We should make a final note that wiring length should be kept to a minimum, with less than 2 inches from transistor to PC board. Even with that length, a ferrite bead is necessary on each gate lead, and using coaxial cable is recommended.

#### Preparing the chassis

The design and construction of a chassis for the amplifier is not critical. The author's prototype was built with rack mounting in mind. It consists of an 8 × 17 inch bottom plate with 1 inch turned up at

the front and back. The front plate is  $19 \times 17$  inches. As shown in Fig. 10, the two heat sinks mount on the back of the unit, leaving a  $2\frac{1}{2} \times 7$ -inch strip for a small plate where the input and output jacks and fuses are mounted. Finally, an  $8\frac{1}{4} \times 31$ -inch U-shaped piece of perforated metal makes up the cover.

Begin mounting the components with the transformer, bridge rectifier, filter capacitors, and fuse-holders. Then, mount the power switch, pilot lights, and level controls on the front panel.

Next you'll have to make up a suitable mounting plate and install output jacks that are insulated from their mountings. Install the input-fuse holder and the power cord with a strain relief. Then wire the transformer primary and secondary as shown in the schematic. If you plan to use the optional thermal cutouts, leave a pair of wires to go to the heat-sink area. Use 18-gauge (minimum!) wire in the power supply. We recommend that you use some simple color code for the DC wiring—it will help reduce the possibility of errors during subsequent tests.

Locate a suitable single-point ground, such as a screw through the bottom of the chassis near the power supply, and attach the filter capacitors' common power-supply ground to it. If you use a 3-wire power cord, do not ground or terminate the cord's ground lead.

#### Checkout procedures

The amplifier checkout is by far the most important part of building this amplifier, so, shift into low gear and proceed with great care through the following steps!

First we strongly advise you to make a final visual check of all parts placements on the circuit boards and the power-supply wiring. Then, before applying any power, measure each supply terminal with an ohmmeter to ground. An initial low reading should slowly move up to high resistance as the capacitors charge. Install the main power fuse and, with the DC fuses F2-F5 not installed, apply power. Check the two supplies for  $\pm$  75 volts. Remove power, and discharge the filter capacitors through a 1K resistor.

Next, install a pair of 1/4-amp fuses for F2 and F3. Measure the resistance from each power-supply input to ground on both driver boards. The reading should be greater than 100K. If it is, temporarily connect one board to F2, F3 and ground. Connect a clip-lead from the collector of Q1 to the collector of Q3. Connect another clip-lead from the collector of Q7 to the collector of Q8. Temporarily clip-lead D3, D4, and D5 into the circuit, Apply power, and measure the voltage between the bases of Q16 and Q17. It should be near 7 volts. Adjust R19, and observe this voltage changing. Leave it at 6,8 volts. Measure the voltage from the emitter of

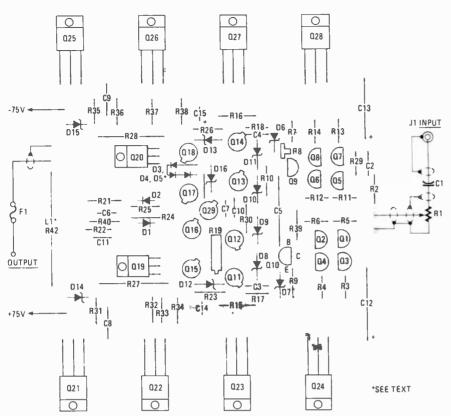


FIG. 8—PARTS-PLACEMENT DIAGRAM for the amplifier board. Refer to the text for information on mounting the output transistors (Q21–Q28) on a heat sink.

each particular type) so that they will share the output current equally. A simple circuit for checking the matching is shown in Fig. 12. They should be matched to be within 100 millivolts of gate voltage at 50 mA of drain current and 200 millivolts of gate voltage at 2 amps of drain current. Make the 2-amp measurement quickly, or with the transistor heat-sinked.

To mount the transistors, first bend the leads up at a 90-degree angle right at the point where their width changes. Spread the leads a bit and insert in board. Solder carefully while aligning the transistors as much as possible in a common plane. (They may temporarily be screwed to the heat sink as a holding fixture for this operation.) Solder short leads from D3–D5 to the bottom of the driver board, carefully observing polarity. Apply heat-sink compound and insulators to the transistors, and screw the driver and output-transistor assembly to the heat sink, using insulating shoulder washers. Tighten carefully.

Measure each transistor's tab (or case, if you are using TO-3's) to the heatsink. The readings should all be infinite, indicating no insulator shorts. (If you are using TO-3 output parts, it will be necessary to run individual leads to each transistor. When doing that, be extremely cautious: Double-check all your connections and

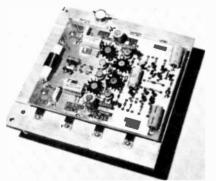


FIG. 9—AMPLIFIER BOARD is shown here mounted on heat sink. Note that Q12, Q13, Q15, and Q18 use TO-5 type heat sinks.

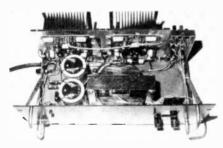


FIG. 10—COMPLETE STEREO AMPLIFIER with cover removed. The chassis configuration is not at all critical.

Q19 to the +75-volt supply, and the voltage from the emitter of Q20 to the -75-volt supply. One should be around 7 volts and the other about .6 volt. Remove

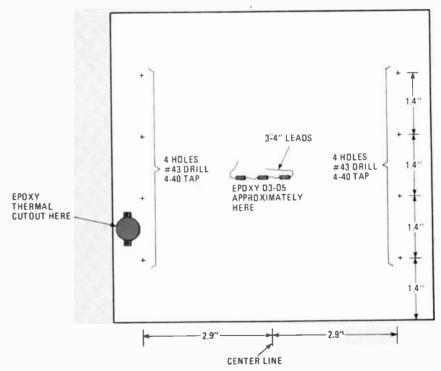


FIG. 11—HEAT-SINK DRILLING GUIDE. Note that some parts are fastened with epoxy to the heat sink.

power, discharge the filter capacitors, remove clip leads, and repeat with the other driver board.

Next, solder the output transistors to the driver board. Note that it is important that the transistors be matched (within keep your leads as short as possible. Don't forget to install a ferrite bead on each gate lead if you are using TO-3's. In no case should the wiring to the transistors be more than 2 inches in length.) Install the heatsink and driver assemblies.

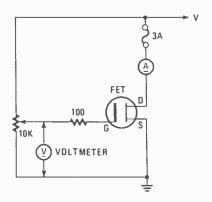


FIG. 12—TO CHECK THE MATCHING OF TRAN-SISTORS, you might want to use this simple circuit. Start by setting the potentiometer's wiper voltage to zero. Then turn it up to the desired drain current and measure the voltage as shown. For N-channel devices (IRF630), V should be 5 volts. For P-channel devices (IRF9630), V should be 5 volts.

Wire one channel to F2 and F3 with 18gauge (minimum) wire. Connect a wire from the circuit board ground, near the output, to the chassis single-point ground. Install a 1/2-amp fuse for F3, and a I-mA fuse for F2. Apply power, and check for a current through F3 of less than 500 mA. Also check that the output voltage at L1 is between ± 1 volt. If either of those tests fail, immediately turn off power, and look for the source of the problem before proceeding. Adjust R19 to set the current through F3 to about 250 mA. corresponding to an output idle current of about 150mA. Next, adjust R8 carefully to bring the output voltage at L1 as close as possible to zero. Turn off the power, and repeat for the second channel, using fuse positions F4 and F5.

#### PARTS LIST-BARGRAPH DISPLAY and CLIPPING INDICATORS All resistors are 1/4 watt, 5%, unless otherwise specified. R43-24,000 ohms R44, R46, R53—12,000 ohms R45, R52, R70—22,000 ohms R47, R54-1000 ohms R48, R55-470,000 ohms R49, R51, R58, R59, R61, R62-10,000 ohms R50, R56-150 ohms R57, R60-53,000 ohms R63, R65-1200 ohms R64, R66-7500 ohms R67-350 ohms, 20 watts R68-15,000 ohms R69-2200 ohms, 5 watts Capacitors C18, C19-1 µF, 10 volts, electrolytic C20-2.2 µF, 10 volts, electrolytic Semiconductors IC1-LM139 Quad op-amp Q30---ECG291 D17, D18-1N4001 D19, D20-1N4741A 11 volts, 1-watt, **Zener** D21—1N4735A 6.2 volts, 1 watt, Zener D22-1N4744A 15 volts, 1 watt Zener

D19, D20—1N4741A 11 volts, 1-watt, Zener
D21—1N4735A 6.2 volts, 1 watt, Zener
D22—1N4744A 15 volts, 1 watt Zener
D23—1N4750A 27 volts, 1 watt, Zener
LED1, LED2—Standard red LED
DISP1, DISP2—NSM39158 logarithmic bargraph display with driver (National)
Other components
S2, S3—SPDT
The following items are available from

The following items are available from A&T Labs, Box 552, Warrenville, Illinois, 60555: Etched, drilled, plated-through PC boards, \$22 each; Power transformer, \$69 each; Set of 8 matched power FET's, \$66; Drilled heatsink (type 512), \$27. Add 5% shipping and handling, 12% for transformer. Illinois residents include 5-1/4% sales tax.

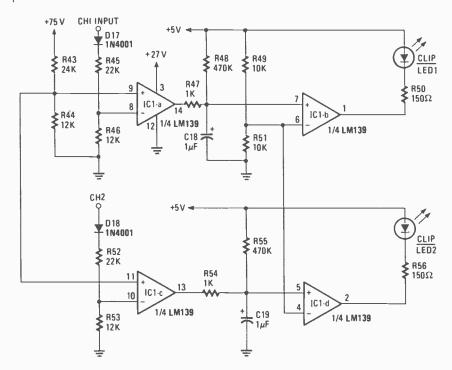


FIG 13—CLIPPING INDICATORS can be added to your amplifier, if desired.

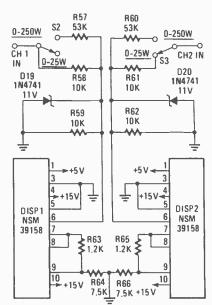


FIG. 14—BAR-GRAPH POWER METERS will certainly make a nice addition to any stereo amplifier.

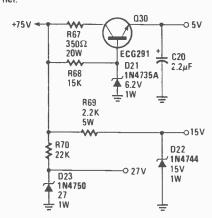



FIG. 15—THIS POWER SUPPLY is needed if the clipping indicators and bar-graph power meters are added. Note that Q30 requires a 10-watt heat sink.

Upon completion of those initial tests, finish wiring the remainder of the chassis. Run at least 18-gauge wire from each driver-board output, along with a ground from the board to the output binding posts. Shielded cable should be used from the level controls to the input jacks. The input-coupling capacitors mount at the level controls.

For continuous full-power applications, it will be necessary to use 5-amp fuses for F2-F5, and 8-amp output fuses for F1. However, for normal, or even loud general listening situations, it is advisable to use much smaller fuses to protect the speakers. It is usually sufficient to use 2amp supply and 1- or 2-amp output fuses, and work up from there if necessary.

You may want to add clipping indicators and or bar-graph power meters to your amplifier. The clipping indicator is shown in Fig. 13, the power meter, in Fig. 14, and the power supply needed for the two additions is shown in Fig. 15.

# Servicing Videodisc Players

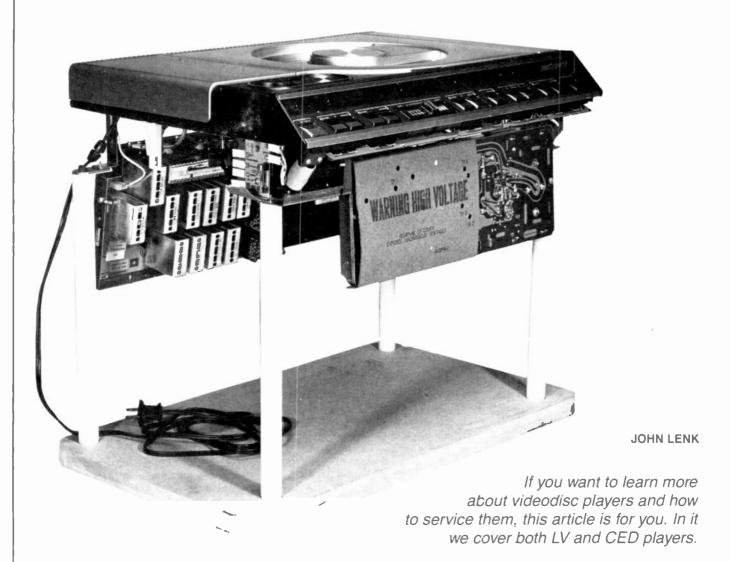

Part 2 LAST TIME, WE BEGAN our look at servicing videodisc players with a discussion of how LV players worked. Let's finish that discussion now and then move on to an overview of the CED system.

Referring to Fig. 6 (see P. 68, December 1984 Radio-Electronies), the prism is designed to deviate the path of the reflected beam so that the beam passes through the cylindrical lens to the photodiodes, which generate (or control) three voltages in response to the three light beams returning from the disc. The center beam generates the FM signal and

the focus error-voltage. As shown in Fig. 7, if the disc is too close or too far from the objective lens, the reflected beam becomes elliptical in shape. If the disc moves too close to the objective lens, diodes x and B receive more light, and conduct more than c and D. The opposite is true if the disc moves too far from the lens. If the light bundle is not perfectly focused on x,B,C, and D, a focus error-voltage is generated to move the objective lens up or down as required to maintain correct focus. (The objective lens is attached to a coil of wire and is surrounded by a permanent magnet, similar to a loudspeaker.

Current through the coil, as determined by the photodiodes, moves the lens up or down as necessary.)

The light beams striking diodes E and Eserve to maintain correct radial tracking. If the beams shift to the left or right, Execeives a different amount of light than E, and a radial error-voltage is generated to move the radial-tracking mirror as necessary to deflect the beam back onto the center of the track. The movable tangential-mirror operates in an identical manner, but receives the error correction-voltage from the video circuits.

We will not go further into the LV op-

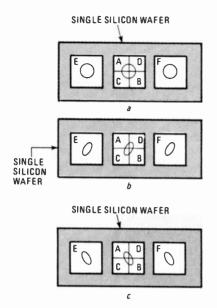


FIG. 7—PHOTODIODES are used to keep the videodisc perfectly in focus. The ones in a show a disc in focus, the ones in b show a disc that is too far away, and the ones in c show a disc that is too close.

tical system here, except to say one thing: The optical system of an LV player (or more properly the optical/mechanical system) is the critical part of the player from a servicing standpoint. You must follow the manufacturer's instructions regarding adjustment and/or replacement. Even a minor misadjustment can result in poor player performance (and possibly no performance).

#### The basic CED videodisc system

Let's begin our look at CED with a review of user controls. Again, remember that the controls described here are "typical" for most CED players.

With CED, the disc is stored in a protective plastic sleeve or caddy, which is inserted into the player as shown in Fig. 8. The CED disc is mounted on a rigid spine (Fig. 9) that holds the disc in place, both in the caddy and in the player.

In some players, a FUNCTION lever (or some similar control) must be in the load position to insert and remove the disc. Many of the more recent CED players have some form of automatic load function, and do not include such a lever.

The caddy ensures that the CED disc is always correctly loaded, as well as protected when not being played. Once the disc is loaded, the FUNCTION lever is set to play (or the automatic mechanism places the player in play). At that time, a system control microprocessor takes control of the player. At the end of the program, the user sets the FUNCTION lever to unload (or the player puts itself into unload) and the user reinserts the caddy into the player to remove the disc. The caddy now serves as a safe, convenient storage container for the CED videodisc mounted on the spine.

In players equipped with a function lever, throwing the FUNCTION lever to load applies power and opens the caddy door. allowing the caddy to be inserted into the player. After the caddy has been removed, leaving the disc and spine inside the player, the FUNCTION lever is placed in the play position. That causes a stylus to be lowered onto the disc, allowing the player to begin detecting signals on the disc and generating a display on the TV screen. Note that the CED stylus is somewhat similar to that of an ordinary phonograph pickup, in that the stylus must be driven across the grooves by means of an arm and drive motor (although not a true tracking servo as in the case of LV).

To operate a player equipped with autoload, you apply power by pressing the ON/ OFF button, which places the player in load (caddy door open). A loaded caddy is then inserted into the player (gently) until the player's automatic loading mechanism takes hold and pulls the caddy into the player. (In any type of CED player, do not force the caddy into the player.) When the caddy spine is latched, the loading mechanism reverses and returns the empty caddy out beyond the door. You then remove the empty caddy and the player places itself in play. In about 10 seconds, a picture appears on the TV screen. In most players, a digital readout displays the elapsed playing time in minutes.

About 10 seconds after play is completed, the player places itself in UNLOAD. The caddy door then opens, and you insert the empty caddy to retrieve the disc and spine.

In a typical CED player, the user controls also include RAPID-ACCESS (to rapidly move in both forward and reverse directions for quick location of a particular program segment) and VISUAL-SEARCH controls (which do the same thing). The difference is that with former, the stylus is lifted and you get no display on the TV (you use the elapsed time indicator to find a program segment), and with the latter, you get a video display in fast motion (but no audio). Most CED players also have a PAUSE feature that raises the stylus (no video display) and cuts the audio at any point during the program.

A special code is recorded at the end of the program on each side of the disc. That code causes the player to go into and "end" mode. When the code is detected, the stylus is lifted and the elapsed-time readout will display a flashing E. The player remains in the end mode until the disc is removed, or until RAPID ACCESS OF VISUAL SEARCH are selected.

#### Capacitance pickup theory

The CED disc is somewhat like a typical phonograph record in that the signal information is placed in grooves. However, there are many differences. One such difference is the density of the

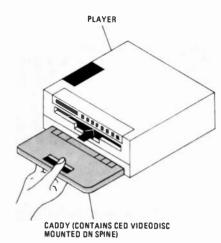


FIG. 8—THE CED DISC is protected by a plastic caddy. The disc is inserted into the player by inserting the caddy as shown.

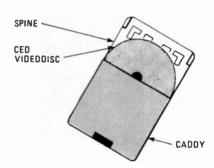


FIG. 9—THE CED DISC rests on a rigid spine. Both the disc and the spine are enclosed by the caddy.

grooves. There are about 10,000 grooves in a 1-inch radius of the CED disc (that density is about 40 times that of a phonograph record).

In CED, the audio and video signals are placed on the disc via FM carriers by varying the groove depth. As the stylus travels over the grooves, the vertical position of the stylus remains constant (unlike that of a phonograph record). A thin metalized electrode is placed on the trailing surface of the stylus. That electrode acts as one plate of a "capacitor." The CED disc, which is made of a conductive plastic with a thin lubricating coating, acts as the other plate. As the disc rotates, the distance between the bottom edge of the stylus electrode and the modulation in the groove varies as a function of the modulation, even though the stylus does not move vertically. That action varies the distance between the plates of the "capacitor" at the modulation frequency, and thus modulates the capacitance of the stylus capaci-

The changing of stylus-to-disc capacity, in turn, modulates a UHF signal in the pickup-arm resonator assembly. The resultant AM UHF signal is peak-detected, generating an output signal that is a voltage replica of the FM audio and video carrier signals recorded on the disc. Those FM carriers are then demodulated to re-

cover the video and audio signals.

Note that the stylus is part of a *cartridge*. Many CED player cartridges are provided with handles, and are easily removable. That makes it possible to replace the stylus/cartridge simply, often from the outside of the player through an access door. (But do not count on such easy access to the stylus/cartridge on all CED players. Also, do not assume that all CED cartridges are interchangeable with all other CED cartridges.)

#### **CED** signals

The CED system uses a vertical field rate of 60 Hz, and is phase-locked to the AC power line. The CED system also uses the conventional black-and-white TV horizontal rate of 15,750 Hz. The color signals from a CED player are at the NTSC standard of 3.579545 MHz. The video signal recorded on the CED disc is an FM 5-MHz video carrier. As shown in Fig. 10, the black level of the video signal causes zero deviation of the carrier, or a frequency of 5 MHz. Sync tips cause the video-carrier frequency to deviate to 4.3 MHz. Peak white in the video signal causes the video-carrier signal to deviate to 6.3 MHz. The sidebands from that frequency modulation extend from 2 to 9.3 MHz.

On monaural CED videodiscs, one channel of audio is placed on a FM carrier at 716 kHz. On stereo or two-channel independent CED discs, the two channels of audio are at 716 and 905 kHz. Audio signals generate a frequency deviation of ±50 kHz.

Prior to modulating the 5-MHz video carrier, the 3.58-MHz chroma subcarrier, and resultant sidebands are down converted to 1.535626 MHz (usually called 1.53 MHz), as shown in Fig. 11. Down-converted chroma is developed by heterodyning the 3.58-MHz chroma with a 5.115170-MHz oscillator signal. The resultant 1.53-MHz chroma subcarrier is then sideband-limited to ±500 kHz. Luminance information is then added to the down-converted chroma to generate a composite video signal.

#### CED player operation

As shown in Fig. 12. The operation of a CED player is controlled entirely by a microprocessor. User functions such as PLAY, RAPID ACCESS, VISUAL SEARCH, etc., are input to the microprocessor through the corresponding user function switches. In turn, the microprocessor decodes the commands and controls the player's electronics to carry out the functions. Note that when the *squelch* line from the microprocessor is low, all electronic circuits are disabled (to provide an automatic shutoff feature).

The microprocessor also controls the pickup arm electronics, including the *stylus lifter* operation (which raises and

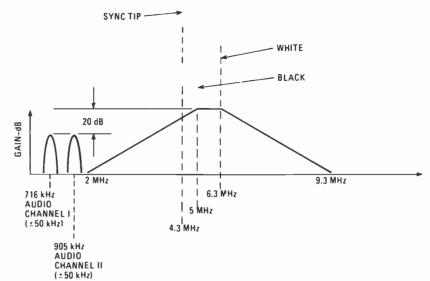


FIG. 10—CED SIGNALS. As shown here, the black level is at 5 MHz, which is the carrier frequency, the peak white is at 6.3 MHz, and the sync tips are at 4.3 MHz.

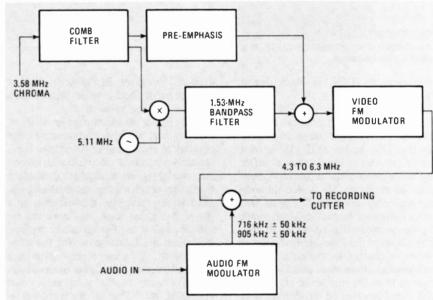


FIG. 11—THIS SIMPLIFIED BLOCK DIAGRAM shows the method used to record CED discs

lowers the stylus as various functions are initiated) and the kicker operation (which enables the system to provide visual. SEARCH, and to prevent the stylus from being stuck in a groove). The microprocessor also decodes the digital auxiliary information (DAXI) code recorded on the disc. The DAXI code contains a field identification number that is decoded to display the elapsed play time of the program (in minutes). Since DAXI is not available during RAPID ACCESS (the stylus is lifted from the disc) a photo interrupter circuit provides the approximate elapsed time by tracking the relative position of the pickup arm with respect to the disc.

The pickup arm assembly contains components that are responsible for detecting video information on the disc. The arm also contains stylus-kicker coils that cause the stylus to skip grooves in the disc (to prevent a locked groove condition and

to provide for VISUAL SEARCH). Also located in the pickup arm is the armstretcher transducer, which corrects for timebase variation in the recovered chroma and luminance signals (the variation may be due to warpage, eccentricity, and/or changes in turntable speed).

The main function of the pickup electronics is to detect the video signals on the disc. That is done by modulating a 910-MHz resonator circuit (a UHF tuned line) with capacitance changes on the disc surface. The variations in capacitance cause the 910-MHz resonator center frequency to be modulated. The video and audio carrier signals from the arm are applied to two FM demodulator stages. The sound demodulator decodes one of the audio carriers and generates an audio signal that then FM-modulates a 4.5-MHz carrier in the RF modulator. The sound demodulator also contains a defect corrector or

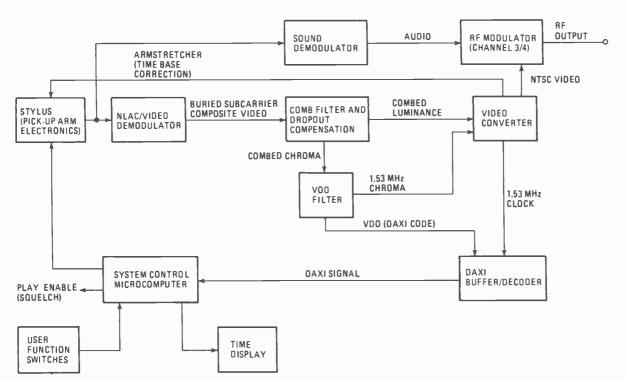


FIG. 12—SIGNAL PROCESSING CIRCUITS. This simplified block diagram shows the circuitry used to playback a CED videodisc.

dropout corrector (DOC) similar to that in a VCR.

Before demodulation, the FM videocarrier is passed through a nonlinear aperture correction (NLAC) circuit that eliminates the 716- and/or 905-kHz sound beats in the video due to sound-carrier phase modulation of the recovered videocarrier information. The video demodulator also contains a DOC circuit that allows a portion of the previous horizontal line to be inserted when a dropout occurs.

The output of the video demodulator is applied to a comb-filter circuit that separates chroma, luminance, and DAXI information from the composite video. The DAXI signal is supplied through a DAXI buffer/decoder to the microprocessor. The chroma luminance information is applied to the video converter, which up converts the 1.53-MHz data to 3.58 MHz, and combines the chroma/luminance signals. The composite-video signal is then supplied to the RF modulator (along with the audio).

The video converter also develops a drive signal for the armstretcher time-base correction circuits. Any phase or frequency difference produces an error signal, which is applied to the armstretcher sole-noid and moves the stylus as necessary to maintain a constant disc-to-stylus velocity. The armstretcher output is also coupled to the video-converter oscillator in order to maintain phase lock between the up-converted 3.58-MHz color signal and the 3.58-MHz reference.

#### Test equipment

The test equipment used in videodisc player service is basically the same as that

used in TV service. In addition, a test, or reference disc, and a video monitor can prove to be most valuable.

Most player manufacturers provide test dises as part of their recommended test equipment and/or tools. A test disc is essentially a standard videodisc with several very useful signals recorded at the factory using very precise test equipment and signal sources. You play the test disc on a player being serviced, and note the response, and/or use the signals to perform alignment and adjustment. With the proper test disc, you can generally eliminate the need for your own signal sources (signal generators, audio generator, color generator, etc.) There is no standardization in test discs. Also, the alignment procedures found in most service literature calls for signals and displays not available on all test discs. The only way around that problem is to use the recommended test disc.

A video monitor has no tuner; it is designed to accept video and audio inputs from some source such as a separate tuner. VCR, or videodisc player. There are also some TV receivers on the market that can accept video and audio inputs. A monitor or receiver with video/audio inputs is very useful in videodisc-player service as they make it possible to examine the audio and video signals from the player before they are applied to the RF modulator so you can check the baseband signals independently from RF. Without such connections, it is difficult to tell if faults are present in the audio/video circuits or in the RF unit. If you use a TV receiver as a monitor, it is helpful to adjust the verticalheight control to underscan the picture (so you can see the video switching point in relation to the start of vertical blanking).

#### Maintenance

Videodisc player manufacturers disagree considerably about routine maintenance. For example, one manufacturer recommends that the laser be replaced at 5000 hours, the motors at 3000 hours, and the turntable components after 9000 plays. Another manufacturer recommends "fix it if it breaks down." Nevertheless, remember the following points.

The picture quality of an LV player can be degraded if too much dust or dirt accumulates on the objective lens. Dust can be removed with an air blower (as used on a camera lens). Never touch the lens surface. Keep the lid closed, except when inserting or removing a disc. If an LV disc becomes very dirty, hold the disc by the edges, and wipe both sides with a clean, soft, dry cloth. Check for warped LV discs since a warped disc can cause skipping, loss of picture, and even hit the lens or lid. Some manufacturers recommend removing scratches on an LV disc with polishing compound (but never use rubbing compound). If LV discs are very cold (frozen), allow about 45 minutes for the disc to return to room temperature before playing. Store LV discs in their jackets on the edge in a standard phonograph record rack. Do not stack LV videodiscs, and avoid storage in hot areas.

Keep CED discs in their caddy. Never remove a CED disc from the caddy (except in the player). Never try to clean a CED disc.

Next time, we'll show you how to service LV and CED players. R-E

# DESIGNING WITH LINEAR IC'S

A look at op-amp based sinewave, squarewave, and triangular wave generators.

JOSEPH J. CARR

Part 8 turn our attention to squarewave, triangular wave, and sinewave generator circuits based on operational amplifiers. The heart of each circuit is a comparator. While there are several different types of IC comparators available, for the purposes of our discussion we will consider only op-amp-based comparators.

#### **Op-amp comparators**

One author once called the comparator "an amplifier with too much gain." The purpose of the comparator is to provide unique outputs to indicate the relative values of two voltages, V1 and V2. The three possible conditions are: V1 = V2, V1 less than V2 and V1 greater than V2.

Figure 1 shows a simple comparator circuit. Note that the operational amplifier has no negative feedback circuit. That fact means the gain is essentially the open-loop gain (A<sub>VOL</sub>) of the op-amp. Depending upon type, A<sub>VOL</sub> might be anything from 20,000 to over 1,000,000. An implication of that is that very small input voltages will saturate the output of the op-amp. Let's assume, for example, an op-amp with 12-volt power supplies that permits  $\pm 10$ -volt output signals. With a gain of 100,000 (moderate for an op-amp), the input voltage that will saturate the output is (10-volts)/100,000, or 0.0001 volt (i.e. 100µV)!

If V1 equals V2, then output V<sub>OO</sub> will be zero. If V1 is greater than V2, we get the same result as applying a positive voltage to an inverting amplifier: the output saturates at a negative voltage. The last situation, V1 less than V2, is the same as applying a negative voltage to an inverting amplifier: the output saturates at a positive voltage.

Diodes D1 and D2 are sometimes used to limit the output voltage  $V_{\rm OO}$  to some value. That limitation might be to protect a following circuit, or to sharpen the output waveform (saturated amplifiers don't always recover quickly). Diode D1 limits the output on positive excursions to  $V_{\rm D1}$  + 0.7 volts, while diode D2 limits negative excursions to  $-(V_{\rm D1}+0.7~{\rm volts})$ . In both cases, one diode is in the reverse-bias Zener region, while the other is forward biased (which accounts for the 0.7-volt term).

If we ground the noninverting input of a comparator, then V2 = 0. By applying a

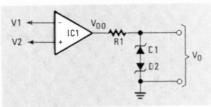


FIG. 1—A SIMPLE COMPARATOR built around an op-amp. Note that the op-amp has no feedback circuit.

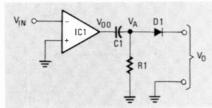


FIG. 2—THIS COMPARATOR CIRCUIT can be used to convert sinewaves to squarewaves and to detect positive to negative (zero crossing) transistions.

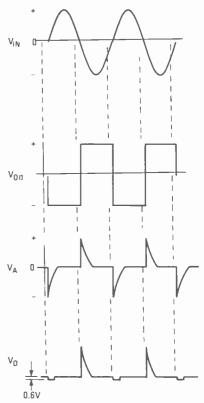


FIG. 3—WAVEFORMS for the circuit shown in Fig. 2.

sinewave to the inverting input we will generate a squarewave ( $V_{\rm OO}$  in Fig. 3) at the comparator output. Because of their ability to convert a sinewave into a squarewave, comparators are used sometimes as the input stage of frequency counters. Modem's and other devices.

A comparator can also be used as a zero-crossing detector by differentiating the comparator output; that is the function of R1 and C1 in Fig. 2. The waveform at  $V_A$  is the differentiator output. The time-constant formed by R1 and C1 should be very, very short (e.g. 0.01) compared with the duration of waveform  $V_{OO}$ . We can select either positive-going (as shown) or negative-going transitions by placing diode D1 in series with the signal line. That diode will clip the spikes of one polarity or the other. (As shown in Fig. 2, it clips the negative spikes (see Fig. 3); reverse it to clip positive spikes).

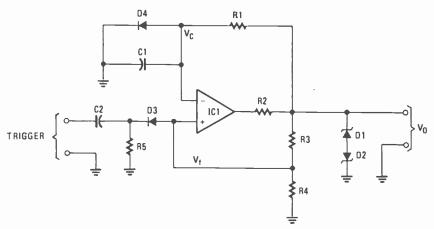


FIG. 4-AN OP-AMP BASED one-shot circuit.

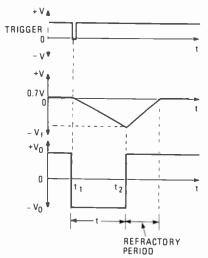


FIG. 5-TIMING WAVEFORMS for the circuit shown in Fig. 4. Note that the one-shot can not be retriggered until both the period t and the refractory period have expired.

#### Monostable multivibrators

A monostable multivibrator, or oneshot, is a circuit that has but one stable state. When triggered by an input pulse, the one-shot switches to the unstable state for a predetermined period of time before reverting to the stable state.

Figure 4 shows a one-shot circuit based on the op-amp, while Fig. 5 shows the timing waveforms for that circuit. There are two feedback paths in the circuit of Fig. 4. The negative feedback path consists of R1 and C1, in which C1 charged by the current in R1 generated by potential V<sub>O</sub>. The positive feedback loop consists of R3 and R4;  $V_f$  is the positive feedback voltage.

When a negative-going trigger pulse is applied to differentiator C2-R5, the opamp output will snap to  $-V_{\rm O}$ , and remain there. The voltage will be negative, so capacitor C1 will begin to charge to a negative voltage. When  $-V_C = -V_{O}$ the op-amp output snaps high again, ending the output pulse period. Capacitor C1 is then discharged because  $V_{\underline{O}}$  is positive. Diode D1 clamps  $V_0$  to  $\pm 0.7$  volts.

The period T of the output pulse is:

$$T = R1C1ln \left[ \frac{1 + (0.7V/V_0)}{1 - R4 (R3 + R4)} \right]$$
 (1

If we put some constraints on values, then Equation 1 can be simplified. If  $V_O$  is much larger than 0.7 volts (it almost always is!), and R3 = R4, then Equation 1 reduces to:

$$T = .69R1C1$$
 (2)

Normally, we know the required period T, and will select C1 from tables of standard values. We will thus want to rearrange Equation 2 to find R1:

$$R1 = \frac{T}{.69C1} \tag{3}$$


When designing the circuit, try several values of C1 in order to find a value for R1 that is close to a standard value.

The circuit of Fig. 4 cannot be retriggered until both period t<sub>m</sub> and the refractory period (i.e. time to discharge C1) expire. Figure 6-a shows the operation of such a circuit. When the first trigger pulse is received at time  $t_1$ , the output  $V_{\rm O}$  drops to  $-V_O$  for period  $t_m$ . The second trigger pulse (at  $t_2$ ) has no effect. The third trigger pulse (at t<sub>3</sub>) effects the output because the period has expired, as has the refractory period. That type of one-shot is sometimes called a nonretriggerable monostable multivibrator.

Figure 6-b shows the timing diagram for a retriggerable monostable multivibrator. The output drops low (i.e. to  $-V_O$ ) at time  $t_1$  when the first trigger pulse is received. If no other pulses are received, the output will snap high (i.e. to  $+V_{O}$ ) after time period  $t_{m1}$  expires. But before t<sub>m1</sub> expires, a second trigger pulse is received. That pulse resets the timing for another period t<sub>m2</sub>. The total period the output remains low is t<sub>m</sub> plus the previously expired portion of the other pulse. In other words,  $t_m(total) = t_m + (t_2 -$ 

Figure 7 shows a method for making the one-shot circuit of Fig. 4 into a retriggera-

ble one-shot. Transistor Q1 is connected across timing capacitor C1. In the dormant state, the positive voltage on the trigger input keeps QI reverse biased. thereby turned off. But when a negative triggering pulse is received, however, Q1 is momentarily forward biased, discharging C1; that restarts the timing period. A subsequent trigger pulse will discharge Cl again, provided the pulse is received prior to the end of t<sub>m</sub> (or after the refractory period).

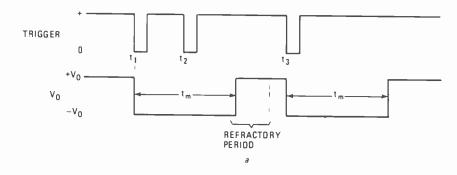

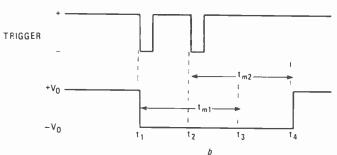


FIG. 6—A NONRETRIGGERABLE ONE-SHOT can not be retriggered until both  $t_{\sf m}$  and the refractory period have expired; the timing diagram for such a circuit is shown in a. In a retriggerable one-shot, each trigger pulse restarts the timing period,  $t_m$ ; the timing diagram for that circuit is shown in b.

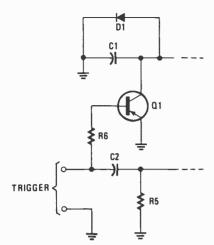


FIG. 7—THE NONRETRIGGERABLE ONE-SHOT of Fig. 4 can be turned into a retriggerable one-shot with the modification shown here.

#### Squarewave generator

A squarewave generator produces a train of equal duration pulses that alternately snap between positive and negative extremes. A perfect squarewave is symmetrical in two ways: amplitude and period. In other words, the positive and negative excursions have equal durations and equal amplitudes. A perfect squarewave will also have extremely fast rise and fall times (which requires high-frequency op-amps). An implication of that latter characteristic is that the squarewave is rich in upper harmonics (which is why squarewave oscillators are used in frequency multipliers and crystal frequencymarkers).

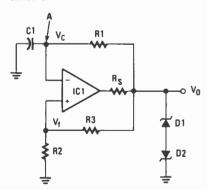


FIG. 8—A SIMPLE op-amp based squarewave generator.

Figure 8 shows a typical squarewave generator based on an IC operational amplifier; Fig. 9 shows the timing diagram for the circuit.

The squarewave-generator circuit bears a certain resemblance to the one-shot circuit shown previously. There are two feedback paths. The negative feedback path consists of timing components R1 and C1. That circuit causes capacitor C1 to be charged by a current in R1, which is generated by output voltage  $V_{\rm O}$ .

The positive feedback path consists of resistor voltage-divider network R2/R3.

Voltage  $V_f$  (see Fig. 8) is the feedback voltage, and is a equal to  $V_O \times R2/(R2+R3)$ .

Looking at Fig. 9, output waveform  $V_O$  is superimposed on capacitor charging voltage  $V_C$ . Let's assume the output  $V_O$  snaps high (i.e. to  $+V_O$ ) at turn-on. Capacitor C1 will start charging in a positive direction at a rate determined by the values of R1, C1, and  $V_O$ . When capacitor voltage  $V_C$  rises to  $+V_f$ , the op-amp essentially sees a zero-voltage differential input, so the output snaps low again. At this point,  $V_O$  is negative so capacitor C1 begins to charge in the negative direction. When  $-V_O = -V_f$ , the output will snap high again.

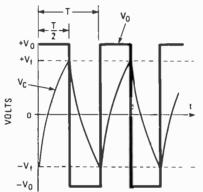


FIG. 9—TIMING DIAGRAM for the circuit shown in Fig. 8.

A generator whose output alternates back and forth, as is the case for the circuit in Fig 8, is called an astable multivibrator; in other words, it has no stable states.

The period of the waveform in Fig. 9 is the sum of high and low times, and can be expressed by:

$$T = 2R1 C1 \ln \left( 1 + \frac{2R3}{R2} \right)$$
 (4)

where T is in seconds. If R2 = R3, we can simplify Equation 4 to the form:

$$T = 3.2 R1C1$$
 (5)

As with many textbook equations, Equations 4 and 5 are not in the most practical format. In most cases, we will know T and will select C1 from a table of standard values. Thus, we need to rearrange Equation 6 to solve for R1. The value of R1 can be calculated from:

$$R1 = \frac{T}{3.2C1} \tag{6}$$

For example, let's find the value of R1 if T is 0.2ms (2x10 4seconds) and C1 is 0.01μF.

R1 = T/3.2C

 $R1 = 0.0002 \text{ sec/} 3.2(1x10^{-8} \text{ farads})$ 

 $R1 = 2 \times 10^{-4} \text{ sec/3.2} \times 10^{-8}$ 

R1 = 6250 ohms

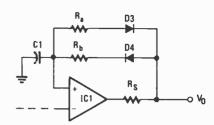


FIG. 10—A SYMMETRICAL WAVEFORM is not always desired. This modification to Fig. 8 produces an asymmetrical waveform.

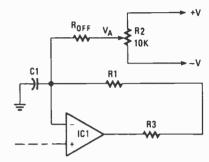


FIG. 11—ANOTHER WAY to generate a squarewave with an asymmetrical waveform is to use a potentiometer. The circuit shown here is another modification of the one shown in Fig. 8.

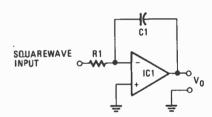


FIG. 12—ONE COMMON METHOD of generating a triangular wave is to input a squarewave into a Miller integrator.

The circuit of Fig. 8 produces the symmetrical waveform of Fig. 9. Both positive and negative excursions occupy equal time durations. That situation occurs because  $1+V_OI=1-V_OI$ , and C1 is charged through R1 on both sides of the waveforms. Unfortunately, however, symmetry is not always desired. The modifications to Fig. 8 shown in Figs. 10 and 11 provide asymmetry in a controlled manner.

The method shown in Fig. 10 uses two feedback resistors and a pair of switching diodes to accomplish the job. The polarities of the diodes are such that D3 is forward biased by negative  $V_{\rm O}$ , while D4 is forward biased by positive  $V_{\rm O}$ . As a result, the capacitor is charged by  $-V_{\rm O}$  via  $R_a$ , and by  $+V_{\rm O}$  through  $R_b$ . If  $R_a$  and  $R_b$  are not equal, then the durations of positive and negative excursions of waveform  $V_{\rm O}$  are not equal.

An alternate to varying the symmetry is shown in Fig. 11. An offset voltage (either positive or negative) is provided by setting potentiometer R2. Since varying R2 will vary the voltage across C1, it can be used to modify the charging time required for  $V_t$  to reach either  $-V_f$  or  $+V_f$  (depend-

# RADIO-ELECTRONICS

# In Computer Electronics...

# NTS INTRONC HOME TRAINING GIVES YOU THE EDGE

The competition for High-Technology careers is strong, and the rewards are great. Give yourself the edge you need by training

NTS INTRODIC home training provides you with a special kind of "Hands-On" experience that prepares you better, develops your skills faster. You advance as quickly as you wish, working with actual circuits, diagrams, schematics, and state-of-the-art hardware. There are a dozen different NTS programs in electronics to help you develop and reach your potential. They range from basics to advanced areas in several fields. And the ALL-NEW NTS course catalog spells it all out. It's free, and does not obligate you in any way. Send for it today.

#### A GROWTH INDUSTRY

with NTS.

High-Technology is a growth industry. The evidence is clear, and most observers predict a steady expansion due to a relatively strong flow of investment capital into computers, electronics and precision instruments. Sales of computers alone will reach an estimated ten million units this year. This means challenges and new



employment opportunities, especially in servicing and maintenance. Computer servicing skills can best be learned by working directly on field-type equipment. NTS electronic hardware is selected and developed especially for the training program with which it is associated. You learn by doing, by assembling, by performing tests and experiments, covering principles of computer electronics, microprocessor trouble-shooting, and circuitry.

#### **MICROCOMPUTERS**

NTS offers three programs in computer electronics. You will receive training covering solid-state devices, digital logic circuitry, and the fundamentals of the computer itself. Instruction includes micro-control technology and detailed operation of microcomputers. These courses will prepare you for entry-level in many facets of the computer industry such as field service and customer engineering as well as programming. In addition to written texts your course includes the NTS/HEATH disc-drive computer which you assemble as part of the training process. The assembly and use of the computer will serve to reinforce practical application of principles.

#### MICROPROCESSOR TECHNOLOGY

The field of industrial and microprocessor technology encompasses the application of electronic microprocessor control principles. Your course takes you from fundamentals of digital electronics and associated circuitry through the application of the microprocessor as a control device. You will learn how to move and manipulate instructions and information. The microprocessor trainer included in your course is a microcomputer system designed as a practical tool for learning the use of software and hardware techniques utilized in the linking of microprocessors to various systems.

#### DIGITAL ELECTRONICS

The NTS Compu-Trainer is a fascinating solid-state device which you will build in order to perform over ninety logic circuit experiments. These experiments serve to emphasize an area of electronics which is essential to the understanding of state-of-the-art control equipment; they are also extremely important to those wanting to pursue a career in computer servicing. Separate courses involving the Compu-Trainer are also available in Microcomputer Servicing and Digital/Analog Electronics.

#### **ROBOTICS & VIDEO TECHNOLOGY**


Other NTS courses cover a wide range of specialization. In Robotics, the NTS/Heath Hero I is included to train you in robotic applications in



NO OBLIGATION



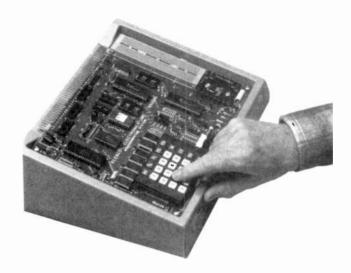TECHNICAL TRADE TRAINING SINCE 1905
Resident and Home-Study Schools
4000 So. Figueroa St., Los Angeles, CA 90037



manufacturing processes. In Video technology, a new course features the advanced NTS/Heath Z Chassis "Smart Set" color TV with computer space command remote control and space phone. This is an excellent program for those interested in a career in video servicing with microcomputer basics.

#### **EARN CEU CREDITS**

America's industrial giants are turning more and more frequently to home study as an effective way to upgrade employee skills. You benefit from the experience NTS has gained in its 79 years as a leader in technical training. The skills and experience gained in the building of kits and test equipment provide you with training that cannot

be duplicated. And, depending on the program you select, you can earn up to 30 CEU credits for successful completion. Complete details included in the catalog.



Use the mail-in card or fill out and mail the coupon, indicate the field of your choice. (One, only please.) FREE full color catalog will be sent to you by return mail.

NATIONAL TECHNICA 4000 South Figueroa Street, Please send FREE color catal	Los Angeles, CA 90037			
☐ Robotics. ☐ Digital Electronics ☐ Auto Mechanics ☐ Air Condition	☐ Computer Electronics ☐ Video Technology ☐ Home Appliances ning / Solar Heating			
Name	Age			
Address	Apt			
City State				
ZipPhone ( )				
☐ Check if interested ONLY in classroom training in Los Angeles ☐ Check if interested in G.I. Bill Information.				

ing upon the polarity of  $V_{\Delta}$ . An advantage of the circuit shown in Fig. 11 is that it includes a potentiometer that allows you to continuously vary the relative duration of the positive and negative excursions of the waveform.

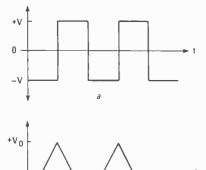


FIG. 13—TIMING DIAGRAM for Fig. 12. The squarewave, shown in a, is input to the Miller integrator; the resulting triangular waveform is shown in b.

#### Triangular waveform generator

There are several ways to generate a triangular waveform. Figure 12 shows one very common method—drive a Miller integrator with a squarewave generator. The timing waveform is shown in Fig. 13.

The triangle, wave circuit is modified in Fig. 14 to include a self-generating squarewave source. The frequency of the output of that circuit is given by:

$$f = \frac{R2}{4R3 R1 C1}$$
 (7)

#### Sinewave oscillators

Sinewaves can be generated either by filtering a square or triangular waveform, or by using a feedback oscillator circuit.

The filtering method uses a very sharp cut-off low-pass filter, or a notch filter, to remove the harmonics from a complex waveform such as a triangular wave or squarewave. Of course, the amplitude is greatly reduced, but that problem is easily overcome through the use of fixed-gain amplifiers.

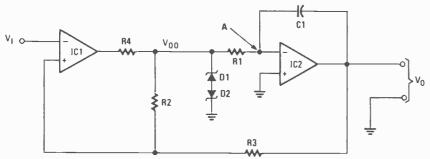


FIG. 14—THIS TRIANGULAR-waveform generator includes an integral squarewave generator.

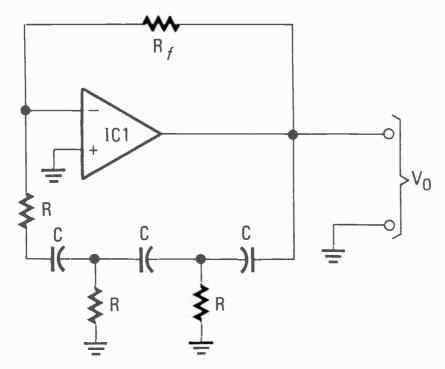


FIG. 15—AN RC phase-shift oscillator, such as the one shown here, can be used to generate a sinewave.

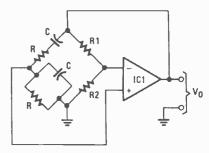


FIG. 16—THIS WIEN-BRIDGE OSCILLATOR can also be used to generate a sinewave output,

An advantage of the filtering method is that it is easy to maintain amplitude stability over a wide range of frequencies. Where fixed frequency operation is used, however, one might want to use a feedback oscillator

There are two criteria that must be met by a feedback oscillator: The loop gain must be one or greater, and the feedback must be in-phase with the input signal only at the desired frequency of oscillation. Two different sinewave oscillator circuits are presented here—the RC phaseshift oscillator and the Wien-bridge oscillator.

The RC phase-shift oscillator is shown in Fig. 15. The inverting amplifier IC1 provides 180 degrees of the required 360 degrees of phase shift. The remaining 180 degrees of phase shift is provided by a three-stage RC network (each stage provides 60 degrees). The frequency of oscillation is given by:

$$f = \frac{1}{2\sqrt{6BC}} \tag{8}$$

The circuit will oscillate provided that the gain, which is set by  $-R_f/R$ , is sufficient too overcome the losses of the RC phase-shift network. Analysis shows that the attenuation factor of the network ( $V_f/V_O$ ) is 1/29, so the gain must be 29 or more.


The Wien-bridge oscillator is shown in Fig. 16. The "bridge" is a frequency-selective AC version of the old-fashioned Wheatstone bridge. If R1 = 2R2, the circuit will oscillate at a frequency of  $f = 1/2\pi$ RC.



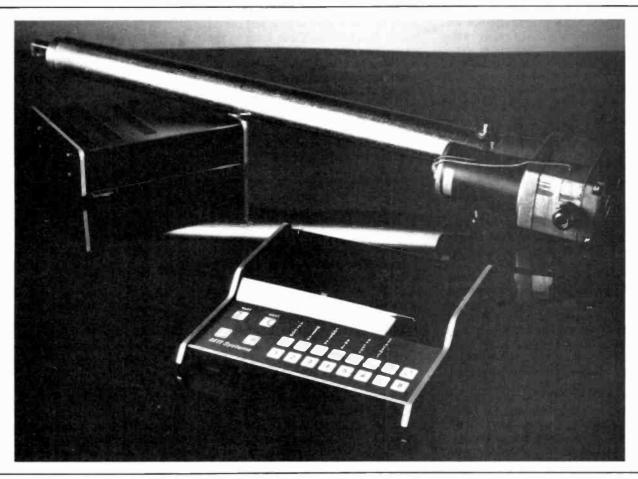"Radio is just like TV—only the picture tube blew,"







## Satellite-TV Accessories

Once you have your basic TVRO system set up, it's time to look for add-on devices to make your viewing more enjoyable, or simply more convenient. Here we'll take a look at some of those accessories.

#### MARC STERN

WHILE A BASIC TVRO SYSTEM—MADE UP of a receiving anienna, LNA, downconverter, and receiver—will certainly bring you much enjoyment, there are many accessories that can make your setup even more pleasant. For example, you can add a stereo synthesizer or stereo processor, a remote antenna actuator, and a host of other devices.

In this article, we'll tell you about some of the many of the satellite add-ons that are available and how to choose them. We'll also describe what they can do for your system. Let's begin our look at these items with the stereo synthesizer and the stereo processor, both of which will add to your listening pleasure.

#### Stereo synthesizers and processors

A stereo synthesizer, as its name implies, creates synthetic stereo sound from the mono signal that may be transmitted by a satellite's transponder. It is pseudo stereo, not true stereo sound. However, when you use such a synthesizer with a good stereo amplifier, you can achieve rather good results.

A stereo processor, on the other hand, is used to decode stereo signals from satellites. The result is true stereo, not pseudo stereo. We recommend stereo processors over stereo synthesizers, especially since the price of decoders has dropped rather dramatically. In fact, stereo synthesizers are becoming in-

creasingly difficult to find, because their price advantage has slipped away.

A stereo processor should have a tuning range from 5.5 to 8 MHz—that will permit you to tune in the whole range of possible audio subcarrier frequencies. If you're a regular Radio-Electronics reader, then there's a good chance that you'll want to build a stereo processor yourself. It'so, check our October 1984 issue for construction details for a stereo decoder.

Many stereo processors feature selectable bandwidths (150 and 500 kHz, for example). Selectable audio bandwidth can be a useful feature to help increase the signal-to-noise ratio of many signals. But remember that as you decrease the band-

width, you lose some of the high-frequency music information. However, in noisy conditions, that is often a worthwhile tradeoff.

#### IF filter

Another useful add-on component for your TVRO setup is an IF filter. There are several kinds. One type is a passband filter—it filters out those frequencies above and below the satellite-TV IF. It also narrows the IF bandwidth. Thus, it can be useful to pull some weak signals out of the snow (but you don't want to use it with stronger signals).

Another type of filter is the notch filter. Its main purpose is to eliminate annoying black and white spots (sparklies), which are usually caused by terrestrial interference. (Transcontinental telephone microwave transmissions have carriers at ±10 MHz from the transponder's center frequency.) When connected between the downconverter and receiver, the filters can eliminate the interference at 60 and/or 80 MHz.

Do you really need a filter? We think that you should put off buying one until you set up your TVRO system. You may find that your reception is adequate without a filter. Anyway, they are easy enough to install (they just connect in-line between the downconverter and receiver) so that you can add them at any time.

#### Antenna positioners

Because of their popularity, it is becoming hard to think of antenna positioners as TVRO add-ons. Since few people are willing to run outside to crank their dishes to a new position, antenna positioners are becoming more like standard equipment! In general, an antenna positioner consists of two parts: a control unit and an antenna actuator. The control unit is mounted indoors at the satellite receiver. It controls the actuator, which is mounted at the dish.

The two units are connected by a cable, and the control voltage is low, usually around 24 volts DC. Many control units feature digital displays that let you return the antenna to a particular satellite. Those displays, typically from 2 to 4 digits, are not true indicators of position. They are guide numbers so that you can return to a particular satellite. In other words, when you locate a satellite (such as SATCOM F3), you make note of the display (say, "247"). Then, whenever you want to return to SATCOM F3, you simply press the direction controls until the display shows "247." Some positioners allow you to store satellite positions in memory so that you can return to them, with a single command. And some units let you store the satellite name in memory as well.

When shopping for an antenna positioner, make sure that the actuator is protected against damage from overtravel. If

it isn't, someone who is not familiar with the system could easily damage the actuator. Most systems do have limit indicators and automatic braking so that the possibility of damage from misoperation is small.

Some positioners offer "extra" features that you might find to be very convenient. Read through our look at the marketplace for more details. The other considerations in buying an antenna positioner are mostly mechanical. Of course, you should look for sturdy construction, and systems with little backlash. Weatherproofing is also desirable. Most important of all, perhaps, is to make sure that your actuator has at least a one-year warranty.

#### Video switching

It is quickly becoming true that the average television set isn't just receiving an input from a VHF or UHF antenna anymore. Instead, it may have inputs from a video cassette recorder, a cable-television system, a home computer, as well as a home satellite-signal receiving system. A video switcher is almost a necessity to eliminate the familiar "rat's nest" of wire and cable, and the confusion that grows as the TV is called upon to handle so many items.

There are two things you want to look for when buying a switcher: High isolation between inputs, and a lot of inputs. (You should get more inputs than you think you have need for—you're sure to need them eventually.) As an added convenience, you might want to buy one with two or more outputs as well.

There are other accessories that you can get for your TVRO. Signal splitters, distribution amplifiers, remote controllers, outboard signal-strength meters and tunable audio (if your receiver is not so equipped), etc. can all be found along with a host of other goods. Let's now take a look at just some of those add-ons you will find in the marketplace:

#### Arunta

Arunta has three IF filters available for \$165. The 47022 threshold extension filter passes 59 to 81 MHz with fairly sharp skirts. It helps to reduce interference on weak transponders. The 47019 notch filter features dual notches at 60 and 80 MHz. It is most useful for eliminating terrestrial (telecommunications) interference. The narrow-bandwidth 47015 enhances reception of INTELSAT feeds. (While most TVRO systems have bandwidths of about 27-30 MHz, INTELSAT signals have bandwidths of about 18 MHz.) Each filter can be simply turned on or off with the touch of a button (especially important with the 47015).

Arunta also offers their SSP-318 satellite-stereo processor, which can be used to listen to mono signals as well as those broadcast in multiplex, adaptive deviation multiplex, matrix, and discrete formats. It features dual tuners, a 5–8 MHz range, automatic deviation, dual tuning meters, noise reduction, dynamic-range expansion, and AFC. Dual IF bandwidths (300 kHz and 130 kHz) are also offered.

#### **Burr Equipment**

Burr's Sat-Trol 1 satellite actuator and positioner control box, is available for \$479.95. The *Mini-Trol* is available for \$399.95.

The Sat-Trol 1 uses membrane-type EAST-WEST control keys; it has dual scan rates and a position indicator. The actuator uses zinc-plated tubes, a die-cast aluminum powerhead, and a special weatherproof boot.



BURR EQUIPMENT Sat-Trol 1 actuator.

The Mini-Trol is designed to eliminate electronic problems. Built without potentiometers or Hall-effect sensors, only the motor and screw are left at the dish. Although that system is very reliable, there is no display of position at the control unit. So returning to a specific satellite is more difficult than it would be with the Sat-Trol 1, which does feature a digital display of position. The Mini-Trol features pushbutton operation and an automatic brake circuit. It is rated at 1,000 pounds thrust and 5,000 pounds static loads.

#### R.L. Drake

Drake offers several add-on TVRO accessories; among them are *APS24* antenna positioner (\$499), their *VS35* video selector (\$165), and their *NF60/80* notch filters.

The APS24 makes it easy to relocate a polar-mount antenna. The console features a two-digit LED display and EAST-WEST actuator buttons. The control motor operates on 36-volts DC, and can be used with most antennas that require a maximum linear travel between 18 and 36 inches.



R.L. DRAKE VS-35 video switch.

The VS35 video selector takes inputs from 5 program sources. It offers pushbutton source-selection and isolation is better than 60 dB. Its frequency response (0 dB to 3.5 dB) is 50–400 MHz. Three outputs are offered: TV, REMOTE, and

The NF60/80 notch filters, available for \$79.95, cut out terrestrial microwave interference. The NF60 is for removing interference at 60 MHz, while the NF80 is for 80 MHz. For each filter, the notch depth is 45 dB, and the 3-dB bandwidth is  $\pm$  1.5 MHz of the center frequency.

#### **Dynasat**

The DT-200 Power Tracker, available for \$289, combines a weather-sealed, maintenance-free actuator and an electronic control unit that features two-speed east and west controls. An LED readout and Polarotor I control are also included. The 24-volt DC system uses Hall-effect sensors. It features an 18-inch stroke, hardened steel gears, stainless steel extension tube, and a rated thrust of 2,000 pounds.

#### **Earth Station Accessories**

A weatherproofing boot for satellite actuators/positioners is available for \$21.50. It can be used to protect many positioning jacks. A two-piece boot protects motor and gear works.

#### **Houston Tracker Systems**

The *Tracker IVplus* is a top-of-the-line antenna positioner with remote control (\$610 with remote, \$439 without). The computer-programmable drive system features UHF wireless remote control (up to 200-feet away). Other features include a 16-character, blue fluorescent display that gives instructions while programming, and parental lockout capability.

The *Tracker IVplus* offers control of the Chaparral *Polarotor 1*, and can interface

directly to many receivers for automatic polarity selection. (Some receivers require an interface board.) The east-west over-travel limits are user programmable. The unit is supplied with an 18-inch, ball-screw actuator and 100 feet of wire.

The *Tracker II* (\$305) is a manual-drive antenna and positioner that features an LCD readout of satellite "location" and user-adjustable over-travel limits. It features a self-contained 6-amp power supply. The suggested system load is 800 pounds or a 10-foot lightweight dish. The *Tracker II* is supplied with an 18-inch actuator and 100 feet of wire.

#### ICM/Video

The VP-300C (\$349) is a completely automatic video processor. It regenerates synchronizing signals, and a clamp circuit removes hum and flicker. It features a copyguard stabilizer, four video and audio outputs, NTSC and PAL compatibility, AGC, and a 6-MHz bandwidth. Its S/N is specified at 50 dB.



ICM VIDEO Signal Purifier

The VE-200C (\$495) is also automatic. It regenerates all sync signals and features a copyguard stabilizer, four audio and video outputs, image enhancement and noise reduction, fade to black, a 5-MHz bandwidth, and its S/N is specified as 60 dB. It has controls for video level, color level,

burst phase, and noise level.

The SA-50 Signal Purifier (\$150) is a filter/amplifier containing a five-pole bandpass filter to reduce out-of-band interference. The SD40 (\$325) stereo matrix decoder is used to decode matrix-stereo transmissions. The TA-30 (\$115) is a tunable-audio device—it allows you to tune all subcarrier frequencies from 5.5 to 8.5 MHz (but not in stereo).

#### **Kent Research**

The SurveyorSeven, available for about \$320, is a programmable (12-memory) antenna positioner that offers an optional remote control. It features an LCD antenna "position" indicator; east-west travel and limit indicators. Up to 12 positions can be set in its non-volatile memory and recalled by turning a 12-position rotary control.

The Surveyor-167, which sells for about \$700, is perhaps the most sophisti-




KENT RESEARCH Surveyor-7 antenna positioner and actuator.

cated controller on the market. It is interfaced directly with your receiver. (That is done by your dealer—or by yourself, if Kent is convinced that you are capable of doing it yourself. One disadvantage is that interfacing the *Surveyor-167* will void your receiver warranty.) Once the *167* is installed, your complete station can be controlled by a handheld unit. That includes channel, scanning, polarity, audiofrequency (and stereo) selection; video inversion, power and volume control, antenna position, fine tuning, bass and treble, AFC, etc. The *167* also features a parental lock-out system.

There are no knobs, dials, or readouts on the unit—all controls are on the handheld remote. Another impressive feature is that you can display in color, on your TV screen, the satellite that you are watching, the channel you are watching, the date and time, the channel lock-out status and total system status.

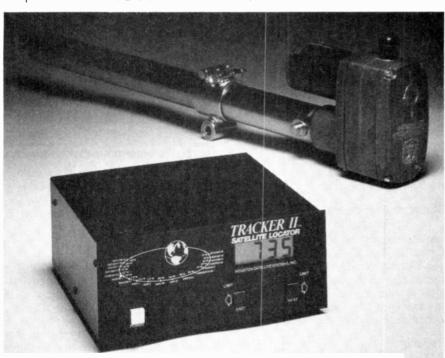The Surveyor-167 features a 36-satellite memory, two-speed drive, up and down scanning, a timer, parental lock-out, a key lock to prevent unauthorized programming, polarity control, non-volatile memory. LED indicators, skew compensation, and a scan function. The actuator has an



HOUSTON TRACKER SYSTEMS Tracker II antenna positioner and actuator.

18-inch stroke and its thrust is rated at 1,500 pounds. Skew, tilt, and format correction are chosen automatically, and audio frequencies are automatically selected. It also features stereo decoding, volume mute, bass-treble adjustment, AFC, and dynamic noise reduction.

#### **KLM**

KLM station-accessory offerings include their *Memory Trak* (\$550) and a stereo processor (\$360). *Memory Trak* is an antenna positioner featuring a 50-satellite-position memory, digital readout of relative position and satellite name, polarity control, full east-west manual dish control, and 80-hour memory retention.

which features a 3.7–4.2 GHz output. It is calibrated in transponder numbers and the output can be modulated with audio and video to test LNA's, LNC's or downconverters. It features an RF-transmitting horn antenna, and selectable signal level at 70 MHz and 3.7–4.2 GHz. Audio (mono, discrete or matrix stereo) and composite video outputs, as well as a color-bar output are available. The unit contains a built-in battery charger.

The GBS 2000 (\$2,995) features a microwave output that is tunable from 3.7–4.2 GHz. Its power level is equivalent to 11 dB CNR. Its LNA feed has a nominal level of -30 dBm. The 70-MHz output, which can be used to align IF and detector



REGENCY electronic video switcher

matic pushbutton switching of four inputs (labeled ANT, SAT, VCR, and GAME) to two outputs (TV and VCR). The inputs are indicated by LED's.

#### Sat-Tec

The \$159 S-5000 stereo demodulator decodes matrix or discrete stereo. It features 5–8 MHz subcarrier tunability. The bandwidth is selectable (150 or 500 kHz)



SAT-TEC S5000 stereo demodulator.

and its frequency response is 15 Hz to 15 kHz. Its harmonic distortion is specified as less than 1 percent. Standard line outputs, for connection to stereo amplifiers, are included.

#### **Satellite Reception Systems**

A variety of devices are available, including the *Speedster* trailer (\$1885),




SATELLITE RECEPTION SYSTEMS Speedster trailer and dish.

which includes an 8-foot dish and feed. The trailer, which weighs 875 pounds, can be taken with you when traveling! It uses a 3-inch pole polar mount.
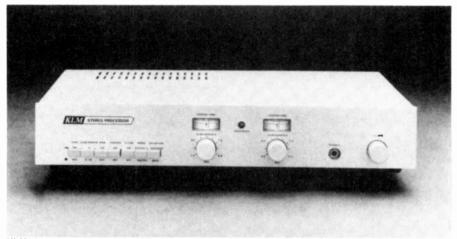
#### Superwinch

Superwinch offers their \$470 Sky-walker II programmable antenna controller and actuator. It features an LED readout, a 16-position satellite memory, illuminated satellite-position display, a limit indicator (which shows antenna is at end of travel), one-week memory protection, overvoltage protection, and full automatic and manual operation.



KLM stereo processor


KLM's stereo processor works with standard receiver video outputs or unfiltered, unclamped video outputs. It features discrete and matrix modes, A and A+B subcarriers, narrow and wide deviation, individual A and B tuning controls, a 5.3–8.3 MHz range, center tuning edgemeters. noise reduction, an interference filter, expansion switch, LED multiplex indicator, video output jack, and mono-audio output jack. The decoder includes an amplifier section (5 watts per channel) with volume control, left and right speaker terminals, headphone jack, and bass boost.

#### Luxor

The model 9534 remote-controlled antenna actuator is available for \$699. It features wireless remote operation, microprocessor control, 30-satellite memory; battery backed-up memory, 175-feet of cable, and automatic polarity switching. The unit can be manually controlled for programming setup and override. An LED satellite readout and position readout is included. The 9536 infrared remote control sensor is available for \$99.
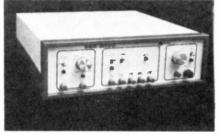
#### **Newton Electronics**

Newton offers satellite-TV test equipment, including the \$995 GBS 2600,



NEWTON ELECTRONICS GBS 2000 satellite-TV test set.

systems, has a power level of  $-10 \, \mathrm{dBm}$ . It contains an internal audio generator, and the four most commonly used subcarrier frequencies (5.8, 6.2, 6.8, and 7.4 MHz) are front-panel selectable.

#### **Quantum Associates**

The \$395 Quanta Q-7 programmable satellite scanner can be programmed for 12 satellites and has a 2-digit LED position readout as well as a liquid-crystal clock display. It features manual and automatic scanning capability. Two drive units are available: The short unit extends 18 inches, the long drive one 52 inches.

#### Regency

The VDS-5000 electronic video switcher, available for \$119.95, features auto-

# RADIO-ELECTRONICS

# HOBBY CORNER



EARL "DOC" SAVAGE, K4SDS, HOBBY EDITOR


## A versatile module

ONE OF THE MORE INTERESTING THINGS in the fast-paced world of electronics is to discover a small company starting up on the basis of a new idea or product. The fascinating part is to watch what happens to the company after it has started up. Many such fledglings last only a short time and then fade away. You can't always predict whether they'll be able to make a go of it, because there are so many factors involved.

Many emerging companies with good products or ideas have gone down the tubes because their service, dependability, and responsiveness to customers has been somewhat less than desirable. Don't get us wrong: We're not saying that an occasional new product or idea doesn't make a difference in the success or failure of the company. What we are saying is that there's more to the creation of a successful business than the product itself.

Ben Johnson's Kaltek is one of those enterprises that seems to be doing the right things and turning out useful new products. You may recall a discussion back in March 1982 in which I told you about their small module—the RC-111—which, along with a calculator and a handful of common components, can be used to build a capacitance meter, ohmmeter, and so on. That original module is still available (\$14.62, postage paid). But now, there is an advanced version of the original device.

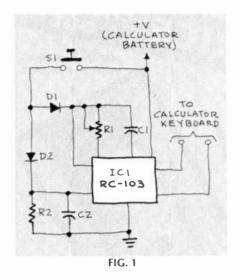The RC-103 (which sells for \$18.00 postage paid) is an RC-111 with Schmitt-trigger inputs for in-



creased precision. Using the RC-103 along with a half-dozen common components and a simple calculator, you can build an instrument to measure resistance, capacitance, temperature, RPM, length, or angles. A stopwatch or a light meter may be constructed just as easily. So that you will know just how simple the whole thing can be, the basic circuit is shown in Fig. 1.

That circuit may be used, too, in a variety of applications depending on the component used at R2. For instance, by replacing R2 with a photodiode, you can build a light-intensity meter. The circuit may also be used to construct a capacitance meter, ohmmeter, and so on. (For more information and/or applications contact Kaltek at the address below).

Another item that should be of special interest to many of you are several circuits, developed by Kaltek, which use the RC-103 along with an inexpensive Timex Sinclair computer. One circuit forms a signal conditioner for reading "difficult" tapes. Others provide onscreen readouts of resistance, capacitance, and frequency. (Though I haven't tried it yet, I see no reason why the same circuits shouldn't work equally well with other computers—Commodore, Radio Shack, etc.—provided appropriate changes are made in the short machine-language and BASIC programs.)

As you would expect, using a computer for the calculations and display opens up all sorts of possibilities. For example, the measurements can be displayed just in numbers, but why not graphs or words, or both for convenience (which would be especially useful to the young student)? And how about a "lie detector" measuring skin resistance and showing a thermometer-like readout rising from "True" through "Are you sure?" to "Why not tell the truth?"

If you have been looking for low-cost test instruments, give some thought to the RC-111 and RC-103 with a calculator or computer. James Pennington (FL) could make a device for tuning his musical instrument. Kaltek will send you the application notes for \$1.00 and an SASE, then give you a buck credit on your subsequent order.

The saga of Kaltek is not yet up to date. They've developed another module, the SL-6. With a couple of components (included with the SL-6 for \$17.46, postage paid), it

RADIO-ELECTRONICS

makes a touch-sensitive switch that holds "on" for about one second. Of course, the hold time can be changed by substituting another capacitor for the one that is supplied.

So what good is a short delay circuit? The SL-6 was developed as an addition to the keyboard of the Timex Sinclair 1000 computer (also known as the Sinclair ZX81). In small inexpensive computers, like the Timex 1000, many keys serve several functions, depending on which mode the computer is in.

For example, a single key might be use to enter a letter, a graphics character, and the cosine function. To enter the function you first press the SHIFT key and then the alphanumeric/function-control key. In the function mode, the alphnumeric keys become function

The short delay allows you to press the shift key and then use

the same hand or finger to hit the control key. That greatly increases the convenience and speed of keyboard operation. It can be especially valuable for certain handicapped individuals.

While the SL-6 application notes refer to the Timex 1000 and its shift key, it should function equally well on other keys and other machines. I am just beginning to experiment with the SL-6 on other computers, and I'll let you know the results of my efforts.

Certainly, use of the SL-6 is not limited to computer keys. Instead of completing a circuit around a computer key, it could complete a circuit to energize a small relay. That could make a dandy compact and portable alarm to sound off when someone touches a doorknob or a car, for example.

Perhaps now you can understand why I find Kaltek an interesting company. I suspect that more and more applications will be found for the RC-111, RC-103, and SL-6 modules. (If you discover one, be sure to let me know about it.) There is also a rumor that Kaltek is on the development trail that will soon lead to another useful module.

Oh yes, please note that I own no stock in Kaltek (wish I did!). And if you wish to contact them, be aware that they are planning to move. The current address is Box 7462, Rochester, NY 14615. After January 1, it will be Box 971, Adjuntas, PR 00601.

A request has come in from Jack Agueros (NY) for information that I have been completely unable to find. He is looking for a means of getting in touch with others interested in old radio receivers. There must be clubs and newsletter publishers for collectors and hobbyists. If you know of one (or more), let me know and I'll pass the word to lack and others who are interested that subject. (Editor's note: You might try these: The Horn Speaker, PO Box 53012, Dallas, TX 75253, Bruce Kelley, Secretary, Antique Wireless Association, Holcomb, NY 14469, and Niagara Frontier Wireless Association, Box 68, Central Park Station, Buffalo, NY 14215.)



Select 5 Books for Only \$295

Save up to \$108.75 when you join

# ELECTRONICS BOOK CLUB

•A wealth of Troubleshooting & Repair tips!

•Hundreds of Projects!

•State of the Art Technology!

•Exceptional Savings!

•The Choice of Hobbvists! and Professionals for over 19 years!




1682 List \$14.95



1765 List \$21.95



1532 List \$11.50 (paper)

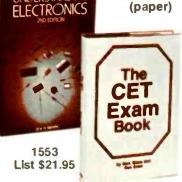

1670 List \$14.95

See other side for more exciting selections!



List \$16.95



List \$16.95







HE BUILD IT BOOK OF ELECTRONIC PROJECTS ELEPHONES

1537 List \$16.95

## **FREE BONUS!**

The Mail Order Guide to **Electronic Parts and Components** 



# ELECTRONICS BOOK CLUB P.O. Box 10, Blue Ridge Summit, PA 17214

Please accept my membership in Electronics Book Club and send the 5 volumes circled below, plus my free copy of the Electronics Buyer's Guide billing me only \$2.95 plus shipping and handling charges. If not satisfied, I may return the books within ten days without obligation and have my membership cancelled. I agree to purchase 4 or more books at reduced Club prices (plus shipping/handling) during the next 12 months, and may resign any time thereafter. Order subject to acceptance by Electronics Book Club. Valid for new members only.

> 800 1183 1199 1211 1218 1409 1431 1449 1474 1487 1498 1532 1536 1537 1542 1553 1561 1575 1577 1605 1616 1670 1673 1679 1682 1719 1765 1820

Name	Phone
Address	
City	
State	Zip

Foreign applicants will receive special ordering instructions. Canada must remit in U.S. Currency

RF-185

## **Build Your Electronics Skills . . . Join Now!**

## No other book source offers so much for such low cost!



List \$18.95

1487 List \$15.95

1449 List \$19.95



List \$19.95

1561 List \$19.50 (paper)

1575 List \$24.95



1605 List \$19.95

1616 List \$19.95

800 List \$19.50 (paper)

## Take 5 Books for Only \$2.95

The Electronics Book Club puts you in the mainstream of today's electronics practice.

- · Access to the latest state of the art developments in lasers, microcomputers, holography, robotics, test instrumentation, and more!
- Step-by-step how-to's for building your own electronic games, gadgets, home control devices. solar energy units, more!
- Expert quidance in every phase of electronics practice!
- Time- and money-saving tips on choosing, installing, maintaining all kinds of electronic equipment!
- · Practical advice on how to turn your electronics knowledge into a profitable full- or part-time career!
- · No other electronics information source offers you so much at such low cost . . . Save now, save every time you order the latest electronics and microcomputer titles from the Electronics Book Club!



1431 List \$17.95





List \$15.95

BUILD A PERSONAL EARTH STATION FOR WORLDWIDE SATELLITE TV




1183 List \$15.95




29 Electronic

1719 List \$18.95

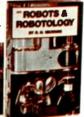

List \$13.95

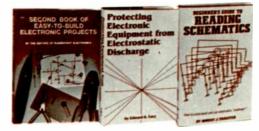

1679 List \$17.95

1820 List \$16.95

1536 List \$14.95

If card is missing, use this address to join: Electronics Book Club, P.O. Box 10, Blue Ridge Summit, PA 17214



## **BUSINESS REPLY CARD**

FIRST CLASS PERMIT NO. 9 BLUE RIDGE SUMMIT, PA 17214

POSTAGE WILL BE PAID BY ADDRESSEE

The Electronics Book Club P.O. Box 10 Blue Ridge Summit, PA 17214

NO POSTAGE **NECESSARY** IF MAILED IN THE UNITED STATES

### 7 very good reasons to join **Electronics Book Club** P.O. Box 10

Blue Ridge Summit, PA 17214 · Big Savings. Save 20% to 70% on books sure to

- Increase your know-how

  No Risk Guarantee, All books returnable within 10
- days without obligation
   Club News Bulletins. All about current selections—
  mains, alternates, extras—plus bonus offers
  Comes 13 limes a year with hundreds of up-to-the-
- comes to times a year with nundreds of up-to-the-minute titles you can pick from "\*Automatic Order." Do nothing, and the Main selec-tion will be shipped automatically! But ... if you want an Alternate selection—or no books at all—we'll follow the instruction you give on the reply form with every News Bulletin

  Bonus Books, Immediately get Dividend Certificates
- with every book purchased and qualify for big dis-
- counts of 60% to 80%.

  Bonus Specials, Take advantage of sales, special
- events, and added-value promotions
   Exceptional Quality. All books are first-rate publisher's editions selected by our Editonal Board, filled with useful, up-to-the-minute information

# COMPUTER OF STATES

NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS

## MACHINE CODE DEVELOPMENT SYSTEM

Build this and put your Sinclair ZX-81 to work as a machine code development system, PROM programmer, and PROM emulator



## **COMPLETING THE BIOBOX**

Build our Biofeedback Monitor and use your computer to keep calm.



# EXPANDING THE COMMODORE VIC-20

Enjoy the convenience of additional expansion ports for more memory or games

## **Electronics Paperback Books**

## Quality Paperbacks at Affordable Prices



HOW TO GET PROJECTS WORK-ING. \$5,00. Helps you troubleshoot and repa

BOARD PROJECTS \$5.00. A variety of prijects that can all be board that has 10 strips and is 24 holes long Wide range of special-ized op-amp circuits in-cluding lo-noise, lo-distortion, ultra-hi input

MULTI-CIRCUIT \$5.00. 21 fairly simple projects that can all be built on a single

lended for the be



GRAMMING THE 16K ZX81, \$6.25. Topics in-

THE 6809 COM-PANION, \$5,00, Writ-ten for the average assembly language programmer. A discus programmer. A discus-sion of 6809 features &

PRACTICAL COM-PUTER EX-PERIMENTS. \$4.50. Fills in background to microprocessor by con-structing typical compu-ter circuits using dis-crete logic components.

GRAMMING THE 1K ZX81. \$5.00, How to use the features of the 2X81 in programs that fit the 1K machine and are still fun to use.

INTRODUCTION
TO BASIC PROGRAMMING TECHNIQUES, \$5.00. Based
on author south

A MICROPROCES-SOR PRIMER, \$4.50.

☐ THE PRE-COMPUTER BOOK, \$5.00. Aimed at the absolute beginner with no knowledge of com-puters. A non-lechnical discussion that helps you enter the computer world painlessly.





AN INTRODUC-TION TO VIDEO. \$5.00. Perfect for the person just about to buy a VCR. Discusses pros & cons of the var ious formats; video discs; videotext, tape copying and more.

FIRST BOOK OF

PRACTICAL COMPUTER EX-PERIMENTS, \$4,50.



TRANSISTOR EQUIV

ELECTRONIC HOUSEHOLD PRO-JECTS, 54,50.



POWER SUPPLY PROJECTS. \$4.50. ply the experimenter is likely to need

REMOTE CON TROL PROJECTS. \$5.00. Radio-control infra-red, visible light, & ultrasonic systems are

ELECTRONIC
TEST EQUIPMENT
CONSTRUCTION,
\$4.50. Construction de nenter can build at PROJECTS USING SOLAR CELLS. \$5.00.

ER PROJECTS. \$5.00 Timing circuits for almost any application the experimenter might need. A most valuable reference.

COUNTER DRIVER & NUMERICAL-DISPLAY PROJECTS. \$4.50. Features ap-plications & projects using various types of ical-display de



TRONICS CALCULA-

INTERNATIONAL
DIODE EQUIVALENTS
GUIDE. \$5.75. Helps
Find substitutes for you find substitutes the many different types of semicondui diodes in use today

INTERNATIONAL TRANSISTOR EQUIV-ALENTS GUIDE. \$7.50. Products of more than 100 man-ufacturers are listed & cross-referenced with possible replacements

FLECTRONIC CALCULATOR UScalculation, conversion factors & more from the view of the calculator

LINEAR IC EQUIV-

PRACTICAL ELEC TRONIC BUILDING BLOCKS-Book 1.



ELECTRONIC

HOUSEHOLD PRO-JECTS. \$4.50.

ELECTRONIC MUSIC PROJECTS. \$4.50.

SPECIAL OFFER Book 1 & Book 2
PRACTICAL ELECTRONIC BUILDING BLOCKS.
\$9.00. Shipping included, Save \$1.75.

FOR BEGINNERS.

ELECTRONIC GAMES \$4.50.

PROJECTS IN OPTO-ELECTRONICS \$5.00,

RADIO STATIONS

ANTENNA PRO-JECTS. \$5.00. Covers

GUIDE. \$4.75. Comprehensive listing of transmitters around tion, frequency, power POPULAR ELEC-TRONIC PROJECTS \$3.75.

\$5.00. A number of useful and interesting designs to CB accessories, Speech

CRYSTAL SET CONSTRUCTION. \$4.50, Packed full of easy to durlicate de-signs for clystal radio receivers

AN INTRODUC-TION TO RADIO DX-ING, \$5.00. Listen, in your home, to broad-casts originating thousands of miles away Tells how you can do it



THE SIMPLE
ELECTRONIC CIRCUIT & COMPONENTS, \$5.75. All
The fundamental theory understanding of the simple electronic circuit

MICROPROCESS-ING SYSTEM & CIR-CUITS. \$7.50, A Iruly comprehensive guide to all of the elements of a microprocessing system.

SEMICONDUCTOR TECHNOLOGY. \$5.75. Everything you always needed to know aboul solid-state devices in one volume.

COMMUNICATIONS. \$7.50. Covers most ellite, digital multiplex, radio & telegraphy.

SOLID STATE NOVELTY CIRCUITS. \$3.50.

28 TESTED TRANSISTOR PROJECTS. \$4,25.

## **ELECTRONIC TECHNOLOGY TODAY INC.**

P.O. Box 240, Massapequa Park, NY 11762

Number of books ordered	Name		
Total Price of Books\$	Address		
Sales Tax (NY State Residents)	Address		
Shipping (75¢ 1st two books, 30¢ ea additional)	City	State	ZIP
TOTAL ENCLOSED			

RE 1/85

# CONTENTS

Vol. 2 No. 1

January 1985

## 7 Machine Code Development System

Turn your Timex Sinclair 1000 into a machine-code development system, EPROM programmer, and EPROM emulator. Mark W. Latham


#### 12 Build The Bio-box

Part 2. This month, we show you the software needed to drive our biofeedback monitor. Jim Barbarello

#### 15 VIC-20 Expander

Add three or more expansion ports to your Commodore VIC-20 computer. Jim Steele


- 4 Editorial
- 5 Letters
- 5 Computer Products

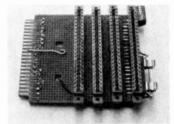

Our VIC-20 Expander is shown here ready to go. To find out more about it, see page 15.
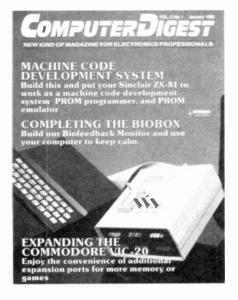
## ON THE COVER

If you own a Sinclair ZX81 or a Timex Sinclair 1000, you already know that programs written in BASIC execute very slowly on those machines. What's more, programming those computers in machinecode can be somewhat less than convenient. This month, we'll show you a project that can make writing and storing machinecode programs a lot easier. What's more, it can double as an EPROM programmer for the ZX81/1000, or an EPROM emulator for another computer system. See page 7.



## **EDITORIAL**

## Here we go again!

It's 1985. You know what that means... For the next few weeks, you're still going to be writing "1984" on your checks and letters. A new year takes a little getting used to. But the number of the year isn't the only thing that

We're going to be seeing some changes—drastic changes—in our business, too. It seems that there will be drastic new developments announced this year. That computer that you bought because it was the latest, the best, the most up-to-the-minute model, is suddenly going to pale by comparison, and you're going to wonder if you shouldn't trade it in on one of those newer units. Suddenly, the features announced on the new machines will seem essential to you, and you'll wonder how you manage to get along without them.

Don't misunderstand—This is called "built-in obsolesence," and we're in favor of it. It helps keep the economy moving, keeps the money circulating (your money) and the challenge to produce the new and unique in order to compete, keeps the manufacturers on their toes. This results in technological advancement that benefits us all.

Timing is usually a critical factor, too. Remember when the Christmas Season began on December 25th? Now it seems to start on Thanksgiving Day. And the people in Detroit introduce their next year's models during the previous Summer. Happily, computers haven't fallen prey to that gambit as yet. The 1985 models will be coming out now—in 1985. That has both its good and bad aspects. On the positive side of the ledger, those who plan to buy new computers will now be ready to spend their bucks, now that they can shop for the new lines. And others who have been looking for a traded-in "bargain" will therefore find the shelves loaded with choices. And many of us, our Christmas-present money burning a hole in our pockets, will be ready to spend.

People who had been planning to change their jobs waited until after the holidays so they could collect their time off and those Christmas bonuses, but since that's behind us, they will be changing jobs now. That's probably going to mean more money for them, a chance to advance for others, and still more openings for those looking for jobs.

Yes, 1985 bodes well for the economy.

And for all of us too.

We, the staff of **ComputerDigest** wish all of our friends a healthy, happy and prosperous 1985

Byron G. Wels

Byron G. Wels

ComputerDigest is published monthly as an insert in Radio-Electronics magazine by Gernsback Publications, Inc., 200 Park Avenue South, New York, NY 10003. Second-Class Postage Paid at New York, NY and additional mailing offices. All rights reserved. Printed in U.S.A.

A stamped self-addressed envelope must accompany all submitted manuscripts and or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and or artwork or photographs while in our possession or otherwise.

# COMPUTER

**Hugo Gernsback** (1884-1967) founder

M. Harvey Gernsback, editor-in-

Larry Steckler, CET, publisher Art Kleiman, editorial director Byron G. Wels, editor Brian C. Fenton, technical editor Carl Laron, associate editor Robert A. Young, assistant editor Ruby M. Yee, production manager Robert A. W. Lowndes, production associate

Dianne Osias, production assistant

Karen Tucker, production assistant Jacqueline P. Weaver, circulation director

Arline R. Fishman, advertising coordinator

Gernsback Publications, Inc. 200 Park Ave. South New York, NY 10003 Chairman of the Board: M. Harvey Gernsback President: Larry Steckler

#### **ADVERTISING SALES 212-777-6400**

Larry Steckler **Publisher** 

#### **EAST/SOUTHEAST**

Stanley Levitan Radio-Electronics 200 Park Ave. South New York, NY 10003 919-777-6400

#### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen Radio-Electronics 540 Frontage Road—Suite 325 Northfield, Illinois 60093 312-446-1444

#### **PACIFIC COAST Mountain States**

Marvin Green Radio-Electronics 15335 Morrison St., Suite 227, Sherman Oaks, CA 91403 818-986-2001

## LETTERS

#### **DESIGN THOSE AUDIO NETWORKS CORRECTLY!**

It was a pleasure to see my article "Computer-Designed Audio Networks" in the November issue of ComputerDigest. It was not as pleasant to see that some errors crept into the program listing. The corrected lines follow:

5 CLS: PRINT

115 ON N GOTO 120,150; PRINT "ERROR - DO OVER": GOTO 110

125 RA = INT(Z ((K-1) (K + 1))): RC = INT(Z ((2 - K))(K[2-1)):A = Z:B = Z

145 GOSUB 2000: GOSUB 2025: GOSUB 2055: GOTO 3000

160 RA = INT((((A - B) KA) +

(A - B)) 2)

220 GOSUB 1000: GOSUB 1030: GOSUB 1050

310 RA = INT((A SQU(A B))(((K~SQR(A B)) - 1) K))

530 DB = CINT(ABS(20 (LOG(SQR (1 (A B)) (1 - SQR(1 - (1 (A B))))) LOG(10)) - 1

2055 X = 60: FOR Y = 16 TO 19: SET(X.Y): NEXT Y

2060 X = 60: FOR Y = 24 TO 28. SET(X,Y): NEXT Y

In line 135, the auotation marks were omitted after the last word, but the program will run without them —Frank Gaides, Murrysville,

Sorry, Frank. Program listings are inherently subject to typesetting transcription errors—even more so than schematics! If anyone has plans to submit a listing with an article, sending it on an 8-inch SSSD (IBM 3740 format) disk is the best way to avoid any problems

#### FLYING ENTHUSIAST

I've become enchanted with the flight simulator on my computer and want to know how valuable this can be toward getting a pilot's license?—Frank Stembo, Dallas, TX.

Frank, as a pilot myse f, I can tell you it's very valuable! Student pilots spend a lot of time in the air (and qual instruction costs p entyl) learning the rudiments of instrument fiight and navigation Your flight simulator is saving you a forture in that way alone But as one of the old great aviators once said, If you want to learn about fying, watch the birds. If you want to learn to fiy, get into an airpiane!"

#### COMPUTER VERSATILITY

Most peop e buy computers to so ve one particular problem in their lives and only rare y do they look for other applications outside their immediate sphere of interest Your magazine has made me aware of some of the other things computers can do, and you've broadened my own computer usage Thanks!—Mort Sabin, Yonkers, NY.◀Φ►

## **COMPUTER PRODUCTS**

## For more details use the free information card inside the back cover

EDUCATIONAL SOFTWARE, The Notable Phantom, teaches children ages 5-10 basic keyboard (musical) and note-reading skills as they compete against a slew of specters, spiders, and the famous phantom nimse f

Haunted-house ghouls lead players through exercises to identify note names and positions on a music sta<sup>44</sup> and keyboard, and to train the ear to



CIRCLE 21 ON FREE INFORMATION CARD

identify different tones, depending on which lesson plan the user selects

Children learn to read music using a sangbook of favorite tunes that is included in every game. Budding composers can save their own song creations and play them back ater

The software comes with a realistic keyboard overlay of black and white notes, more than an obtave and a half The suggested price of The Notable Phantom is \$49.95 — Designware, 185 Berry Street, San Francisco, CA 94107

PRINTER, the ThinPrint 80, is designed for use with portable computers. It is battery-powered, weighs only four pounds, and supports either serial or parallel interfacing to most computers (including Tandy 100 & PC-2, Epsor +X-20, IXO Telecomputer, IBM PC XT, Jr and many others)

The ThinPrint 80 has 80 or 136



columns per line, 40 character-persecond bidirectional printing, 2K buffer memory, and 120 dot-per-inch graphics It holds 80 pages of 8 ~" wide paper, produces silent thermal ornting, and fits into less than half a

briefcase. Its suggested retail price is \$279 00, complete with rechargeable batteries. AC adapter, and one roll of paper.—Axonix Corporation, 417 Wakara Way, Salt Lake City, UT 84108.

FILING SYSTEM, Dial 'N File, is designed for 51/4 diskettes. It is made of high-density, molded plastic and holds up to ten 51/4-inch diskettes and one PerfectData drive-head cleaning

disk. When opened, the plastic cover swings into an easel position and becomes a display stand. A clockwise turn of the dial operating the fanning action, places individual diskettes at the user's fingertips, with all diskette labels clearly visible. The Dial 'N File case closes with a counterclockwise turn of the dial, and locks securely to protect diskettes from damage and contaminants. Its suggested retail price 15 \$6.95— PerfectData Corporation, 9174 Deering Ave., Chatsworth, CA.



CIRCLE 23 ON FREE INFORMATION CARD

SPREADSHEETS, the VisiCalc Package. is a two-in-one product containing both a single and a double disk-drive spreadsheet program—VisiCalc and VisiCalc Advanced Version—for users of the Apple // family of personal computers.

The VisiCalc disk includes models in home management and finance that can be expanded by the user. They are: checkbook balancing, household budget, individual retirement account analysis, future value of an investment.



CIRCLE 24 ON FREE INFORMATION CARD


income averaging, and car-loan payment analysis.

The VisiCalc Advanced Version features full word prompts and variable column-width capabilities, as well as date functions, print commands that produce presentation-quality reports. and both 40- and 80-column displays.

The VisiCalc Package is priced at \$179.00.—Software Arts Inc, 27 Mica Lane, Wellesley, MA 02181
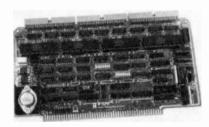
#### **COMMUNICATIONS INTERFACE** is

IEEE-696 (S-100) compatible. It provides a means to connect up to 8 RS232-C devices, regardless of their baud rate, stop bit, and parity configuration. Up to eight of these cards can be used in one system, for a total of 64 channels, with data rates up to 38.4 baud. Also featured are a



CIRCLE 25 ON FREE INFORMATION CARD

calendar/clock, switch register, and an encryption device. The calendar/clock is battery backed-up and the device may be disabled in systems requiring several cards. The encryption device is an MMI PAL, and its use is generally for software protection. The interface is priced at \$695.00.—Inner Access Corporation, PO Box 888, Belmont, CA 94002. **◀①**▶



## **GRAPHIC TERMINAL 4012**

- **Fully Operational**
- Fast RS-232 Serial I/O
- **Bistable Storage Display**
- Full ASCII Char. Set 1024 x 780 Pt. Display
- **Industry Standard**

U.S. built, found in sophisticated CAD/CAM Systems & other applications. 96 Char. ASCII Keyboard, Selectable Baud Rate & other control features.

Originally Sold §6

Unused! Like New!

complete

Removed From Equip't for Upgrade

DEX 4100 FACSIMILE (FAX) MACHINES

Ideal for Experimental Page Scanner or Low Cost Copier Found in offices everywhere, these units can transmit & receive to and from Standard Telecopier Machines over standard phone lines. Transmits documents and photos. Features

auto feed of originals, built-in roll feed, page cutter for automatic sizing & "photo" mode for the grey scale & halftones. Full duplex (Separate Xmit plus Recv. Sections). May be used as a copier.

OPERATIONAL!

Write of Call for Our latest Flyer NOW!!!



NAREHOUSE: 18 Granite St., Haverhill, Mass. 01830 MAIL ORDERS: Box 204, Newton, New Hampshire 03858 17/372-8637







# MACHINE CODE DEVELOPMENT SYSTEM **FOR YOUR TIMEX SINCLAIR 1000**

Turn your Timex Sinclair 1000 or Sinclair ZX81 into a high-speed, machine-code development system.

#### MARK W. LATHAM

■By now you may have seen dozens of Timex Sinclair 1000/Sinclair ZX81 add-on projects in various electronic magazines. It's not surprising considering that at one time, Timex was shipping 100,000 units a morth. While some people are content to fool around with whatever they can hook up to the back of the unit, others have bought real keyboards and extra RAM, hoping to turn their computers into real business or entertainment machines.

If you've ever used a Timex Sinclair 1000 (which we'll simply call a TS 1000 from here on), you know that speed keeps that computer from serving any useful purpose. You could take a short nap while the computer is loading even a 16K program from cassette. Once it's loaded, you run into the other speed problem—execution time. That's because the Z80A CPU spends most of its time updating the video, and, let's face it, the BASIC is too slow, even in the FAST mode. The simplicity of the TS 1000, which is one of its virtues, is also its downfall.

If you own a TS 1000 and want to turn it into a useful device, why not consider the following: 1) run highspeed machine-language level programs and, 2) store those programs in EPROM.

This project, a machine-code-development-system/ EPROM-programmer, will let you do just that. With it, you can use your TS 1000 to load programs from EPROM's, and program EPROM's with data anywhere in the RAM. You will be able to store and recall 4K bytes of battery-backed-up external CMOS RAM. Also, the unit can be disconnected from the TS 1000 and used to emulate an EPROM for a different microprocessor.

You will be able to use the EPROM programmer as a general I/O port, each line of which is monitored by LED's. The LED's are great if you are just learning machine language commands. Of those lines, 20 are available for input/output, while four others are configured as output-only lines capable of sinking 500 mA each. All those lines are available through a socket in the back of the unit and, if you hook them up with a test clip, you will have a five-volt, multi-channel logic monitor with both LED and on-screen viewing. Best of all, the whole EPROM I/O system operates under machine-language level software control, which is, of course, stored in EPROM.

### System architecture

The unit is interfaced to the TS 1000 with an 8255 PPI (parallel peripheral interface) I/O port. We could have treated the program socket as a memory space accessed directly by the Z80A, but then we would have had to insert many wait states during the program pulse. Unfortunately, there is no way the CPU can refresh dynamic RAM during waits so that option is out. What we must do then is create a second bus system as shown in Fig. 1, the schematic diagram.

Gates IC1-c and IC2-c allow the Z80A to access the 8255 when A7 and iorg are low. (A7 is included to ensure that there will be no erroneous writes to the 8255.) If we leave the 8255's AØ and A1 lines set for all I/O operations, the computer's monitor system won't crash during I/O operations regardless of whether the computer is in the fast or slow mode. The A4 and A5 lines of the Z80A are used to control the 8255's AØ and A1 inputs, so, in hexcidecimal, the I/O addresses will be Ø3H, 23H, and 33H.

The 8255 has three eight-bit ports, one of which is bit-addressable. Port C (PB4-PB7) will function as the secondary bus control outputs. Port B (PBØ-PB7) will function as the data I/O port, and ports C (PC3-PCØ) and A (PAØ-7) will function as address outputs Ø-11, respectively: (The reason PC3-PCØ are used in reverse as AØ-A3 is twofold; that both simplifies circuit board layout and arranges the bus and LED's for use as a logic monitor, as you will see later.)

When the 8255 is reset (either by the computer or on power up) all the ports are configured as inputs. Any time those ports are changed from inputs to outputs, or vice-versa, all the port registers are reset. That presents a problem for the control lines in our secondary bus system because those lines must remain high (set) until a memory access is desired. Transistors Q1-Q4 are used to alleviate that problem. If a port's input or output is low, the corresponding transistor output is high, holding the control line secure. If the data in the CMOS RAM is of no importance, then those transistors may be used as high current outputs. capable of sinking up to 500 mA each.

The CMOS RAM, IC9 and IC10, and the CMOS oneof-eight decoder, IC7, provide 4K of data storage for program saving and ROM emulation. The decoder



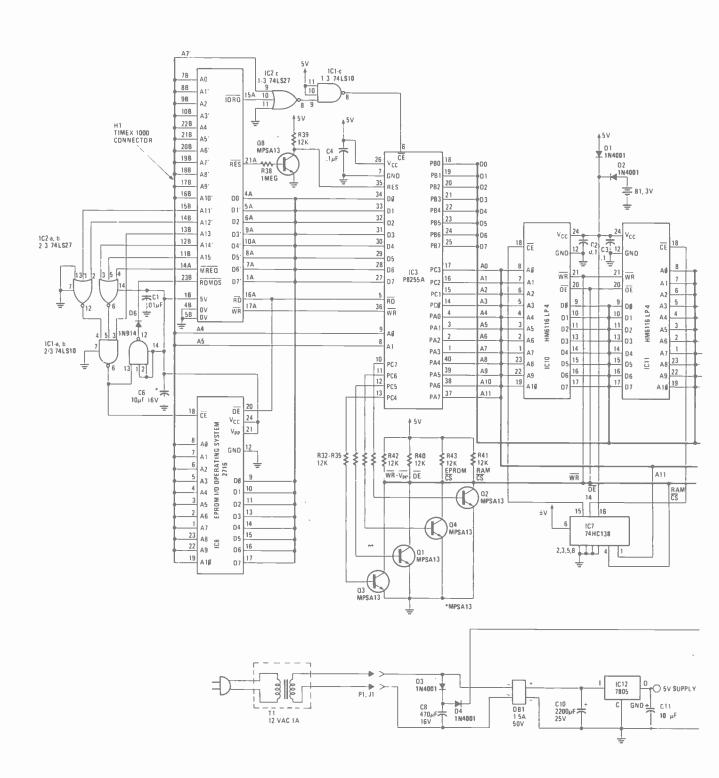


FIG. 1-COMPLETE SCHEMATIC DIAGRAM. Reference the diagram carefully while reading the text, as it helps clarify some of the more-complicated points.

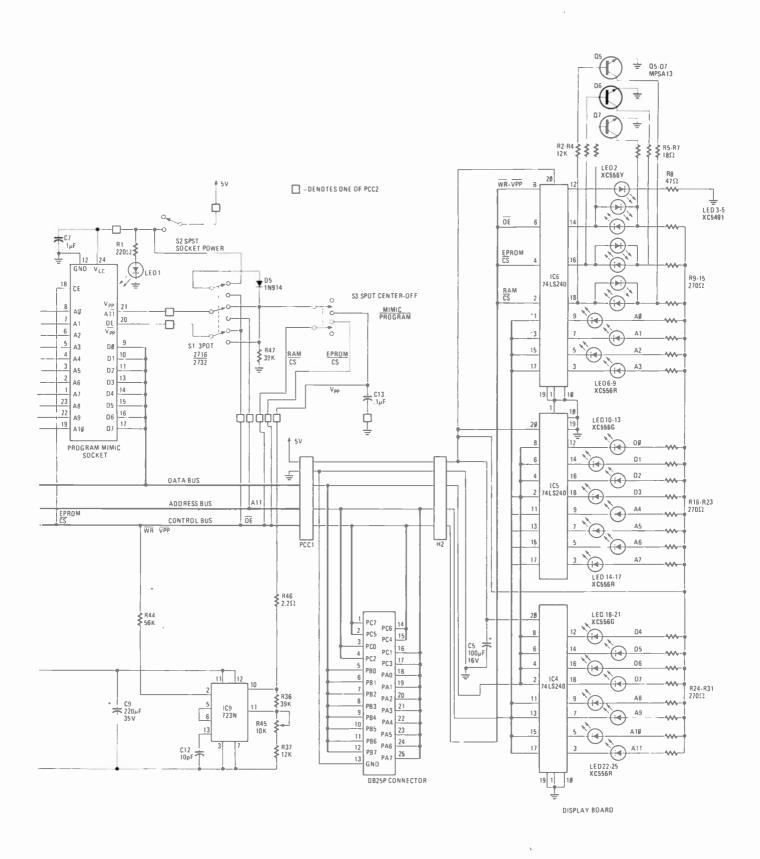

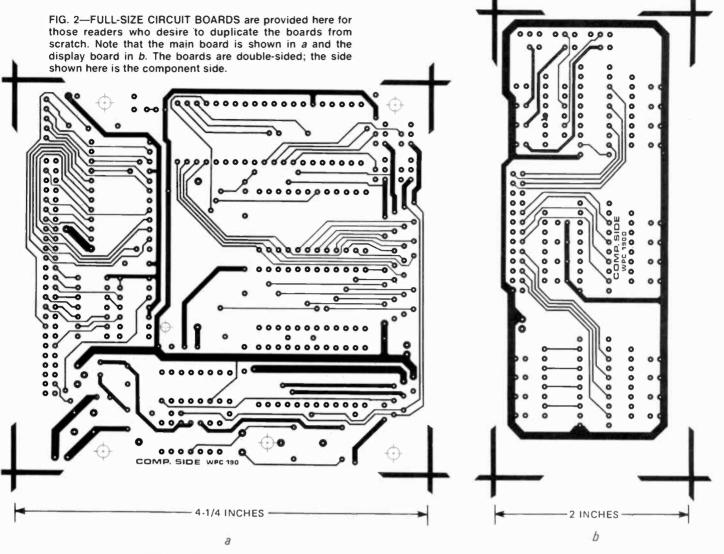

#### PARTS LIST

#### Resistors

#### All resistors are 1/4 watt, 5%

R1-220 ohms

R2-R4, R32-R35, R37, R39-R43-12,000 ohms

R5-R7-18 ohms

R8-47 ohms

R9-R31-270 ohms

R36, R47—39,000

R38-1 megohm

R44-56,000 ohms

R45-10,000 ohms, potentiometer, PC mount

R46-2.2 ohms

#### Capacitors

C1-C4, C7, C13-0.1 µF, ceramic disc

C5—100 µF, 16 volts, miniature radial electrolytic

C6, C11-10µF, 16 volts, miniature radial electrolytic

C8—470μF, 16 volts, miniature radial electrolytic

C9-220 µF, 35 volts, miniature radial electrolytic

C10-2200 µF, 25 volts, miniature axial electrolytic

C12-10pF, ceramic disc

Semiconductors

D1-D4-1N4001

reads RAMCS (PC7) and A11 to select the appropriate memory IC. Those three IC's are powered by either the five-volt supply through D1 or the lithium three-volt

D5, D6-1N914

DB1-RB151 1.5-amp, 50 volt, diode bridge

Q1-Q18-MPSA13

LED1, LED6-LED9, LED14-LED17, LED22-LED25-

red LED, XC556R or equivalent

LED 2—yellow LED, XC556Y or equivalent

LED3-LED5-tricolor LED, XC5491 or equivalent

LED10-13, 18-21-XC556G

IC1-74LS10 triple 3-input NAND gate

IC2-74LS27 triple 3-input NOR gate

IC3—P8255 programmable peripherial interface

IC4-IC6-74LS240 octal buffer

IC7-74HC138 3 to 8 decoder/multiplexer

IC8-2716 EPROM

IC9—723N positive adjustable regulator IC10, IC11—HM6116LP-4 CMOS static RAM

IC12-7805 5-volt regulator

#### Miscellaneous


T1-12VAC, 1-amp, wall-plug transformer

P1—coaxial power plug

J1—coaxial power jack

S1-3PDT switch

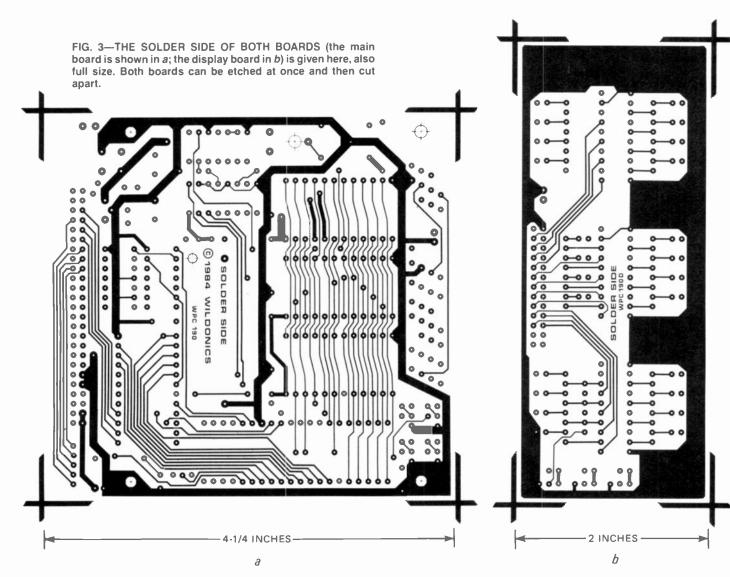battery through D2. Pin 6 of the decoder monitors the five-volt supply and disables the RAM when the power is off



S2-SPST switch

S3-DPDT switch, center-off

H1-50-contact, right-angle header

H2—26-contact header

PROGRAM SOCKET—24-pin ZIF socket with extender pins (or wire wrap socket)

PC boards, IC sockets, enclosure, hardware, ribbon cable, card-edge connector, DB-25 connector, etc.

The following are available from Wildonics Computer Technologies, P.O. Box 1763, Boise, ID, 83701: Complete kit of all parts including power supply, all connectors, lithium battery, PC boards, and case (does NOT include 2716 EPROM with Operating System), \$149.95; 2716 EPROM with Operating System, \$19.95; set of drilled and etched PC boards only \$19.95; Assembled and tested unit with Operating System Software, \$219.95. Shipping, handling and insurance, \$3.00 for EPROM with software or PC boards only. \$6.00 for complete kit or assembled unit.

With S3 set for mimic and the 8255's ports all configured as inputs, a secondary CPU can directly access the CMOS RAM through the program socket.

Setting S3 for mimic simply or-ties the rames and the EPROMCS lines and bypasses Vpp-blocking diode D5. Resistors R38 and R39, and transistor Q8, which normally act as an inverter for the RESET signal, hold the 8255 reset if the EPROM-I/O unit is used apart from the ZX81 during a mimic operation.

When S3 is set to program, the output of the  $V_{pp}$ switching regulator, IC9, is connected to the appropriate EPROM I/O pin. WR (PC7) controls the regulator's output by sourcing the base of the regulator's current limiting transistor. For that application, that transistor's emmitter is connected to ground. Capacitor C12 is connected to the frequency-response pin to slow the  $V_{pp}$  rise and fall times. Diodes D3 and D4 and capacitors C8 and C9 act as a voltage doubler to provide 30 volts at 60 mA to the regulator's input.

All the bus lines can be monitored with the display board. Three 74LS240's, IC4-IC6, power the LED's. Red LED's (LED6-LED9, LED14-LED17, and LED22-LED25) are used for the the address lines and the LED's for the data lines (LED10–LED13 and LED18–LED17) are green. Those LED's will light when the corresponding bus lines are high or high-impedance. The yellow LED (LED2) will light if the WR-VPP line is low.

While we are out of space, we're not our of things to say. We'll finish up next month. ◀••

# **BUILD THE BIO-BOX**

You can build this biofeedback monitor for your TRS Model I or Model III.

#### JIM BARBARELLO

Part 2 Last month, we described the BioBox and told you how to build it. However, while we gave you a brief idea of what software was involved, we still have a lot to say about it. We'll start there. Then we'll tell you how to put the BioBox in action.

#### The BASIC program

The BioBox BASIC program is shown in Program Listing 2. This version is for the *Model I*, cassette or disk based, 16K to 48K memory.

On the *Model I*, addresses 16561 (least significant byte or LSB) and 16562 (Most Significant Byte or MSB) point to the top of BASIC memory. Addresses 16527 (LSB) and 16528 (MSB) point to the single USR entry point in a cassette-based system. Also, address 16561 is always 255, but 16562's contents vary according to the available memory (127 for 16K, 191 for 32K and 255 for 48K). With this understood, we must protect memory for the machine-language subroutine that will be placed there by POKE-ing the individual data values. So our first command is to POKE the number 215 into location 16561. This reserves an ample 40 bytes for our subroutine. Next, we clear 1000 to reserve string storage space and reset BASIC pointers. Line 10 also defines an error handling routine starting at line 550.

Line 20 is valid for a disk system. J is set to two bytes past the protected memory start. The second statement adjusts J if it is greater than 32767, so it can be used in the POKE statements. Finally, we jump over line 30 (which is used only for cassette-based systems) and continue execution at line 40. If we run this program on a cassette-based system, the DEFUSR statement in line 20 will cause an error, branching execution to line 550.

Line 560 checks to see if the error has occurred in line 20 (indicating that this is not a disk system). If so, we resume execution at line 30. In this manner, we can have the program decide which line to use, based on the system configuration.

The first statement in line 30 is for older Model I's. Those units had a software error in the ROM which affected the DATA pointer, making DATA reads impossible. POKE-ing 255 into location 16553 corrects this. Line 30 then sets the USR entry point and calculates the starting location to begin POKE-ing the machine language code. Line 40 prints a heading, while line 50 POKES the subroutine code into memory. Line

50 also performs a checksum and aborts the program if the sum of all placed bytes is incorrect.

Line 60 clears the working area of the screen (GOSUB 900) and prints the vertical graph axis. Lines 90 through 140 complete the screen presentation. Line 150 tests a flag (FLG) to see if this is the initial run of the program (as opposed to a restart). If FLG is not equal to 0, the option to view the instructions is skipped. Otherwise, the user is given the option to view the instructions contained in a subroutine starting at line 600. Line 170 sets the flag and asks for your initial mood. Line 180 allows only numbers between 2 and 9 as a valid input. Line 190 equates the number you enter to CC, which is then used to create string AB. Line 200 uses AB to reprint the graph presentation minus all boxes to the right of the row you specified. It also clears the message line (above the graph).

Initialization takes place in lines 210 through 240. Based on the user's individual skin resistance, the BioBox will produce a count between 1 and 65535. The initialization procedure obtains an average start reading, equating this to the initial mood you selected. It then sets upper (maximum calm) and lower (maximum tenseness) count limits and a change increment (INC). INC is the maximum change in count that will cause one box to be removed or added. The USR call in line 210 is not included in the average count, but simply insures that the BioBox is reset before sampling begins. Line 240 erases the INITIALIZING message before proceeding to the actual biofeedback monitoring of lines 250 through 410.

First we print a box at the present position, and a period (dot) directly above it. Then line 260 samples the BioBox and, if 0 is returned, creates an error to pass execution to the error-trap routine at line 550. Line 270 increments the time (XT) and line 280 polls the keyboard to see if a Restart or End was requested (GOSUB 740). If not, the current square is blanked out (this creates the blinking effect). Line 300 checks to see if the count change is less than one increment. If so, execution branches to line 410 where a delay proportional to the current count is created before returning to line 250 for the next sample.

If the change is greater than one increment, line 310 checks to see if the count is increasing (less tense) or decreasing. For an increasing count, line 330 increases XO by one increment. Then R and C are checked and adjusted if necessary to point to the top of the preceding column (if the last square in the current

#### PROGRAM LISTING 2

- 10 POKE 16561,215:CLEAR 1000:DEFSTR A: DEFINT C.I.R:DIM T(50.3) ON ERROR GOTO 550
- 20 J = 217 + PEEK(16562)\*256:J = J + (J > 32737)\*65535:DEFUSR = J + 1:GOTO 40
- 30 POKE 16553,255:POKE 16526,217:POKE 16527,PEEK (16562):  $J = 216 + PEEK(16527)^256: J = J + (J > 32737)$ 65535
- 40 CLS:PRINTTAB(14):"BIOFEEDBACK MONITOR": PRINTSTRING\$(63,131): PRINTTAB(18);"(c) 1983 by J. J. BARBARELLO"
- 50 FORI = 1TO32:READ N:POKE J + I,N:K = K + N:NEXT:IF K<>3647 THEN PRINT (11 536, "CHECKSUM ERROR.":END
- 60 GOSUB 900; FORI = 1TO10; PRINT" "; CHR\$(157) :NEXT:PRINT" ":CHR\$(141)
- 70 DATA 243,62,1,211,255,6,64,16,254,62,0,211,255,17.1, 0.33
- 80 DATA 0,0,219,255,254,255,40,3,25,48,247,251, 195,154,10
- 90 PRINT((1839,CHR\$(140);:FORI = 1TO10:PRINTSTRING \$(2,140):CHR\$(142):STRING\$(2,140);:NEXT
- 100 AL = " ":A = STRING\$(3, 143) + " ":FORI = 1TO10: AL = AL + A:NEXT
- 110 FORI = 1TO10:PRINT(a 201 + (I-1)\*64,AL;:NEXT
- 120 PRINT@ 905, ::FORI = 1TO10:PRINTUSING"## ';I::NEXT
- 130 PRINT@ 968, "CALM"; TAB(52); "TENSE";
- 140 T\$ = " \TENSE":FORI = 1TO6:PRINT(a 259 + 1\*64. MID\$(T\$.I.1)::NEXT
- 150 IF FLG>0 THEN 170
- 160 PRINT@980, "INSTRUCTIONS? (Y N)...";:GOSUB 80 0:IF AI = "N" THEN PRINT (4) 980.STRING\$(25.32): ELSE GOSUB 600
- 170 FLG = 2:PRINT@ 145, "SELECT INITIAL MOOD (2-9)...
- 180 AR = INKEY\$:IF AR = ""THEN180 ELSE GOSUB 760:IF VAL(AR) <2 OR VAL (AR)>9 THEN 180
- 190 PRINTAR;:CC = VAL (AR) :R = 200:C = CC\*5: AB = STRING\$((10-CC)\*5.32)
- 200 FORI = 0 TO9:PRINT(() R + C + 64\*I,AB;:NEXT: PRINT( $\alpha$  145,STRING\$(50,32); :C = C-5)
- 210 PRINT(a 985, "INITIALIZING...";:Y = 0:FLG = 2:XT = 0: X = USR(0)
- 220 FORI = 1TO5:PRINT((a R-62 + C, ".";:X = USR(0): PRINT((() R-62 + C," ";:IFX<0 THEN X = 65534 + X
- 230 Y = Y + X:NEXT:XO = Y 5:INC = XO (10\*(CC + 5)):XL = XO-CC\*INC\*10
- 240 PRINT@ 985,STRING\$(15,32):
- 250 PRINT((a R + C + 1, A;:PRINT((a R-62 + C, ".";
- 260 X = USR(0):IF X<0 THEN X = X + 65536 ELSE IF X = 0THEN ERROR 1
- 270 XT = XT + X 30000
- 280 GOSUB 740
- 290 PRINT@ R-62 + C. " ":
- 300 IF ABS (XO-X) < INC THEN 410
- 310 IF X<XO THEN 370
- 320 IF X<XO THEN 400
- 330 PRINT(() R + C + 1,STRING\$(50-C,32);:XO = XO + INC:R = R + 64:IF R = 840 THEN R = 200:C = C - 5
- 340 IF C>-1 THEN GOSUB 500:GOTO 320
- 350 PRINT@ 468, "MAXIMUM CALM ATTAINED.";: PRINT (1) 525, "PRESS <R> TO RESTART, OR <E> TO END...
- 360 GOSUB 740:GOTO360
- 370 R = R-64:IF R = <136 THEN R = 776:C = C + 5
- 380 IF C>45 THEN C = 45:R = 200:GOTO 400
- 390 XO = XO-INC:PRINT(a R + C + 1,A):GOSUB500:GOTO 310
- 400 X = XO
- 410 FORI = 1TO(X-XL)\*250/XL:NEXT:XT = XT + I/500:GOTO
- 510 FOR Z = 1 TO 50:NEXT:XT = XT + .25:RETURN
- 530 PRINT@ 980, "PRESS ANY KEY TO CONTINUE";
- 540 AI = INKEY\$:IF AI = "" THEN 540 ELSE RETURN
- 560 IF ERR = 56 THEN PRINT@ 985, "PRINTER

- ERROR"::STOP ELSE IF ERL = 20 THEN RESUME 30 570 PRINT@ 966, "ERROR OCCURRED, PRESS <R> TO RESTART, <E> TO END ..
- 580 AR = INKEY\$:IF AR = "THEN580 ELSE NU = ASC(AR):IF NU>91 THEN AR = CHR\$(NU-32)
- 590 IF AR<> "R" AND AR<> "E" THEN 580 ELSE PRINT@ 966,STRING\$(55,32);:RESUME 760
- 610 GOSUB 890:PRINT@ 260, "The Biofeedback System I measures and displays your changes in mood. Before beginning, check that the hardware interface is attached. and power is applied."
- 620 PRINT" Next, attach one BioProbe to your index finger above the first joint. Then place the remaining BioProbe on your middle finger above its first joint."
- 630 PRINT" When you have finished reading these instructions, you'll be asked the question ";CHR\$(34);" SELECT INITIAL MOOD (2-9)...";CHR\$(34);". Select a number between 2 (CALM) and 9 (TENSE).
- 64C PRINT"If you're in an average mood, select 5. If you're calmer, try a lower number (like 3). Otherwise, select a higher number (like 8).";
- 650 GOSUB 530:GOSUB 890
- 660 PRINT@ 260, "Your mood is represented by the 100 blocks. When you select your initial mood, the higher tension-indicating b ocks will disappear.";
- 67C PRINT"The object is to relax and in the process make all the blocks disappear. If you increase tension the blocks will begin reappearing. A blinking dot will remind you where you currently are.";
- 680 PRINT The more tense you get, the faster it blinks. The calmer you get, the slower it blinks."
- 690 PRINT"If a fault occurs in the BioBox (EX: BioProbes come loose, power not applied), a message will appear and allow you to re-start by pressing <R>. If you wish to restart at any other time, press <R>.";
- 700 PRINT"When you wish to end the session, press <E>."
- 710 GOSUB 530:FLG = 2:GOTO 60
- 750 AR = INKEY\$:IF AR = ""THEN RETURN 760 IF AR = "R" OR AR = "r" THEN PRINT@ 128, TAB(24); "R E S T A R T";TA3(60);:GOSUB 840:GOTO 60
- 770 IF AR = "E" OR AR = "e" THEN GOSUB 840:GOTO 990 **ELSE RETURN**
- 800 AI = INKEY\$:IFAI = ""THEN800 ELSE NU = ASC(AI)
- 810 IFNU>91THEN NU = NU-32
- 820 AI = CHR\$(NU):IFAI <> "Y"ANDAI <> "N"THEN80 **OELSERETURN**
- 840 REM\*\* STORE RESULTS
- 850 PRINT@ 980, "STORE RESULTS? (Y/N)...";:GOSUB 800:PRINTAL:
- 860 IF AI = "Y" THEN  $S = S + 1:T(S,1) = CC:T(S,2) = XO-(Y 5))^{/}$ INC:T(S,3) = XT
- 870 RETURN
- 900 PRINT(a 128," ":FORI = 1TO11:PRINT" ":NEXT: PRINT@ 960 STRING\$(63,32);:PRINT@ 192.;; RETURN
- 1000 ST = 1:TN = 0:GOSUB 9000:IFS = 0 THEN 1050 ELSE ON ERROR GOTO 1050
- 1010 PRINT@ 64, TAB(27);"R E S U L T S"TAB(63): PRINT(a 129, "TRIAL #" TAB(20) "START"TAB(32) "END"TAB(44) "TIME"TAB(56) "FACTOR":PRINTSTRING\$(62."-")
- 1020 FORI = ST TO S:PRINTUSING" ##";I;:PRINTTAB(21); :PRINTUSING"###";T(I,1)\*10::PRINTTAB(32); PRINTUSING":T(I,1)\*10-TI,2);:PRINTTAB(43); :PRINTUSING"####";T(1,3);
- 1030 PRINTTAB (55);:PRINTUSING"######";T(I,3)/ T(1,2)
- 1040 TN = TN + 1:IF TN = 10 THEN GOSUB 530: TN = 0:ST = ST + 10:GOSUB 900:GOTO 1010 **ELSE NEXT**
- 1050 PRINT:PRINT"RESTART? (Y/N)...";:GOSUB 800:IF AI = "Y" THEN PRINT( $\alpha$  64,STRING\$(63,131); STRING\$(65,32):ON ERROR GOTO 550:GOTO 60
- 1060 END

column is being removed). If C has not been decremented past 0, we jump to the subroutine at line 500, where a fixed delay is created and the time is updated. Then we return to line 320. This procedure continues until the difference between X and XO is less than one increment. The same procedure is followed in lines 370 through 390 for a decreasing count.

If at any time, all squares are removed, execution passes to line 350 where the MAXIMUM CALM ATTAINED message is displayed, and we are allowed to (R)estart or (E)nd. Lines 500 through 710 contain various subroutines, including that to display the instructions. The Restart/End subroutine begins at line 740. This subroutine is used throughout the program and allows one to restart or end at almost any time. It also calls another subroutine that gives you the option to save the results of any trial for later presentation. (STORE RESULTS, beginning at line 840).

The END routine begins at line 990. Line 1000 passes execution to Line 1050 (Restart?) if no data are present, or branches to the error trap if any error occurs. Otherwise, line 1010 proceeds to display the results previously stored in the Tarray. Notice that the "Factor" is a relative measure of results, since it reflects number of squares removed per unit time. Since up to 50 trials can be stored, the FOR/NEXT loop starting at line 1020 prints results in groups of 10 maximum, waits for you to press any key, and then continues. Line 1050 allows you to restart or truly end. In this manner, you can select the END function at any time, review your results and then RESTART to continue monitoring.

#### Using the biobox

Select a quiet, comfortable area (around 70 degrees F). Relax by loosening tight clothing, removing your shoes, etc. Sit in a comfortable position that provides arm and elbow support. Make sure your hands are clean and dry.

Type in, save and then RUN the BIO program. After the initial screen has been displayed, place the black cassette cable plug in J2 (out) and the large grey cassette cable plug in J1 (in). The small grey plug is not used. Place S1 (power) in the ON position.

The display consists of a title at the top, an underline, an "option/status" line, the biofeedback graph and a command line. At this point, the status line contains a copyright notice and the command line is asking "Instructions? (Y/N)..." Press "Y." The screen will clear below the title and the first page of instructions will be displayed. When done reading, press any key to continue (as instructed at the bottom of the screen) to read the second page of instructions. When you press any key again, you are returned to the opening screen. But note that the copyright notice is replaced by the question "SELECT INITIAL MOOD (2-9)..." You would have been brought to this point immediately if you responded N (no) to the "INSTRUCTIONS" question.

Now place one bioprobe on your index finger, and the other bioprobe on the middle finger of the same hand. The bioprobe foil should contact the fingerprint. Set the BioBox's ON/OFF switch to the ON position, and press "5." Columns 6 through 10 will disappear. The

message "INITIALIZING" will appear at the bottom, and a dot (period) will appear over the top box on the last row (5th row in this example). If the BioBox is not working properly, (power not on, bioprobe not attached, skin resistance too high, etc.) the message "ERROR OCCURRED. PRESS (R) TO RESTART, (E) TO END..." will appear at the bottom. Correct the problem (power up the BioBox, attach probes, clean fingers, etc.) and press (R) to try again. You will be asked if you want to "STORE RESULTS? Y/N..." If you have completed a valid session, you would select "Y." If you encountered an error (or simply do not want to store results) press "N." The message "R E S T A R T" will appear at the top of the screen and the original display will be provided.

Select an initial mood between 2 and 9. The dot will blink five times, and the "INITIALIZING" message will then disappear. You are now in the biofeedback monitoring mode. Make a fist; boxes will begin to be added. Release the fist; boxes will disappear (in an actual session, you should keep your hand stationary). The object is to remove all boxes. If you do, the message "MAXIMUM CALM ATTAINED. PRESS (R) TO RESTART, OR (E) TO END..." will appear in the middle of the screen. Whichever you choose, the message "STORE RESULTS? (Y/N)..." will appear at the screen bottom. Note that during monitoring you may press (R) to restart or (E) to end at any time, but you may have to hold the key down for a second or so before it is recognized. When you select (E) you will see the RESULTS screen. The RESULTS display contains five columns, labelled TRIAL #, START, END, TIME and FACTOR. For each trial, the START and END columns show the number of squares you started and ended with. For instance, if you selected "6" as your initial mood and acheived maximum calm, the START indication would be 60 (6 columns  $\times$  10 squares/ column = 60) and the END indication would be 0. The next column indicates the elapsed time of the session (not seconds, but relative units of time). The final column gives an indication of how well you did. It is a ratio of the number of squares removed per one unit of time. The object is to get this number as close to zero without going negative (which indicates squares were added, not removed.)

If there are more than 10 results stored, they will be shown in pages of 10. When all results have been displayed, you will be given the option to "RESTART? (Y/N)..." By pressing "Y" you can continue monitoring. (This allows you to periodically check your progress and then return to monitoring.) If you select "N," the program will end. As currently written, the data is not permanently saved. Depending on your individual system and requirements, a short subroutine may be added to save the data to a tape or disk file.

#### Summing it up

The BioBox can turn your Model I or III into a computerized biofeedback monitoring system, and may even help you to reduce everyday stress and tensions. But don't limit it strictly to biofeedback monitoring. Try it as a lie detector at your next party. Just make sure you don't become the subject!

# **VIC-20 EXPANDER**

Build this expansion port for your VIC-20.

#### JIM STEELE

■If you own a Commodore VIC-20, you're probably tired of switching memory-expansion modules and game cartriges in and out of the user port. You might have considered buying one of those port expanders you've seen advertised. They are certainly a possible solution—you can switch between several cartridges at the flip of a switch—but they're expensive. We'll show you a less-expensive alternative—building your own port expander.

#### Additional ports

While the expander module shown here will provide three additional ports with another available for future expansion, there is no reason why this selfsame system could not be further expanded upon almost to an infinite number of ports, limited only by your own requirements and your own pocketbook. There are actually two ways to go.

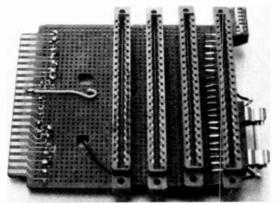


FIG. 1-EXPANSION MODULE READY TO GO. Here, we're looking down at the top of the board.

One way is to make additional expanders, as shown here, and simply plug the second expander unit into the open port on the first one. However, if you anticipate the need for several more ports than would be furnished by this unit, you can readily "expand the expander" by adding additional ports wired in the same configuration as these are.

The result will be even more versatility.

The justification for this expander is simply in its added conveniece to the user. Before the expander, it was necessary (within limiations) to pull a cartridge

and replace it with another when cartridges needed changing. If you rarely if ever change cartridges, the expander will seem a mere nicety that you could probably do as well without. However, if you're constantly changing cartridges, as would be the case when you're using your computer predominatly for game-playing, the expander becomes a vital and important tool, as you leave all the cartridges plugged in, and flip switches to change from one to another. It makes life a great deal simpler.

You can put the expander together for about \$20.00—perhaps less if you have some of the parts around. But it will work just as well as the commercial models that cost up to five times as much. The expander we'll show you was built to accept three cartridges, with a fourth available for future additions. It is fully switchable and it's fused to protect both the VIC and cartridges.

#### Easy to build

Even if you don't have much experience building electronics projects, you shouldn't have too much trouble with the expander. The hardest task is the point-to-point wiring, but you can get around that by designing a printed-circuit board. Whatever method you use, you should be able to finish everything up in a weekend.

To begin with, you will need a general-purpose plug board with a 22/44 eage connector. Such boards are available from many sources, including Radio Shack. Next, you will need three or four wire-wrap 44-pin card-edge connectors. Those, too, are easily available. You'll also need some 30-gauge (or larger) insulated wire. Stranded wire works best, and you should try to use a color-coded arangement. Finally, you will need a 2- or 3-amp line fuse and three or four switches. I used an eight-position PC-board-mounted switch.

With one exception, the card edge and card-edgeconnector sockets are wired in parallel. Example: Contact "A" on the contact board is wired to contact "A" on each card-edge socket. Contact "B" is wired to contact "B" on each socket, etc. (See the diagram, Figure 2.) The only exception to that is contact No. 21, which is the +5 volt supply from the computer to the expander board. This contact is wired through a switch for each socket, and then to contact No. 21 of the socket. Thus, what is plugged into the socket will be powered up only when the switch is closed. Contacts 'Z" and No. 22 are common ground.

Another alternative for those who are of an experimental turn of mind, would be the use of a rotary switch mounted to a small panel. You'd want to use a switch with the same number of contacts as there are switches on the boards, or ports on the boards, and wire to the rotary switch instead of having individual switches at each port. While this might appear to complicate the circuit a bit, it would result I up-front control of the ports. Make sure you use a nonshorting rotary switch for this application, and the rotary switch can then be mounted in a small separate plastic box of its own and placed either atop or alongside the computer. The added convenience that this affords would make it worth looking into.

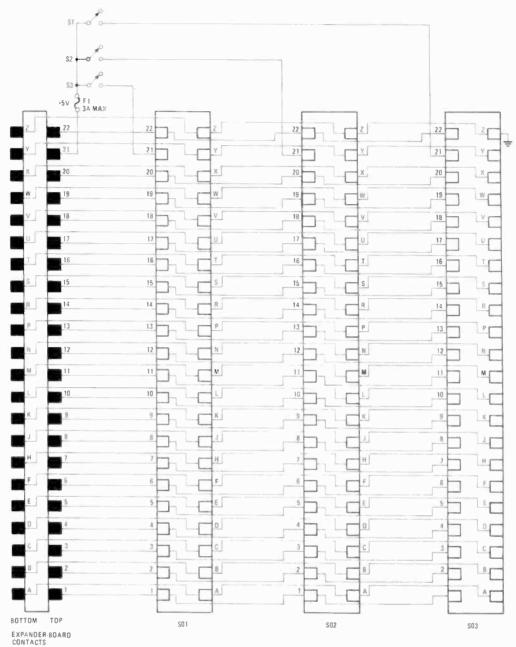


FIG. 2—SCHEMATIC DIAGRAM shows simple point-to-point wir ng. Circuit is straightforward and direct with no hidden traps.

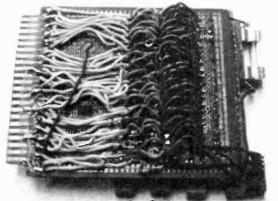


FIG. 3-UNDERSIDE VIEW REVEALS WIRING. The VIC-20 expander makes a good one-weekend project that will reward you with years of added convenience.

#### Check the wiring!

Once the wiring is completed, check the continuity of each circuit. This procedure is a must because any bad connection could cause your VIC to behave radically or crash memory at a most inopportune time. When you are sure that each connection is right, plug your unit into the VIC-20 expansion port, wire-side down, making sure the contacts line up. Plug in your game and/or your memory expansions. Check the operation of each of the expansion ports with a game you are familiar with or a memory expansion. If you turn on your VIC and it does not work properly, turn it off and recheck your wiring and make sure that the contacts from the plug line up with the expansion port contacts.

That's all there is to it! Unless you have more than three expansion modules and games you don't have to worry about plugging in a module every time you need one—just switch it on when you need it! ◆ ◆

# COMMUNICATIONS CORNER

HERB FRIEDMAN. COMMUNICATIONS EDITOR

## Phantom power

ONE OF THESE DAYS, SOMEONE IS going to write a definitive book called Reinventing the Wheel. It will be a book containing all the ideas rediscovered by succeeding generations. If asked for suggestions about what wheels to include, I think phantom power should head the list. Each new generation of students and hobbyists with whom I've been involved has "discovered" phantom power. For those of you who haven't rediscovered it yet, phantom power is a means whereby the supply voltage for a device is carried along on the same line with the signal.

The first time I ever heard of phantom power was as an assistant radio-technician on my first remote broadcast. I was the guy who lugged around heavy cases containing boat anchors (better known as portable mixers). Maybe it was the free lunch that we were served, but my supervisor took ill and I was left hanging on by my fingernails with equipment that I knew next to nothing about. Under such circumstances, everything will go wrong. (And every-

thing did!)

First, the private phone line dropped out; then the headphones wouldn't work. Finally, after locating a public telephone, I called the head honcho at the studio who mumbled something about us being on a solid-wire circuit. He then told me to bypass the resistive pad on my mixer's output, and connect a spare dial lamp from the center tap of the mixer's output transformer to an earth ground. I was told that when the light went on I was "on the air."

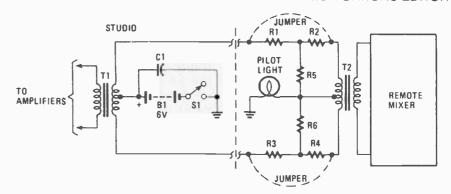


FIG. 1

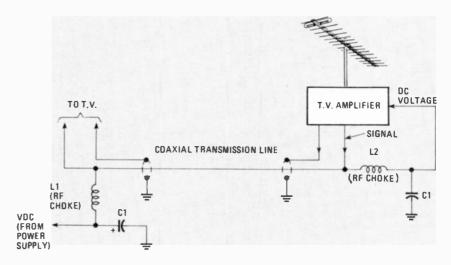


FIG. 2

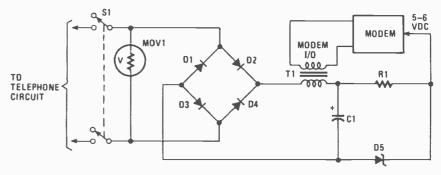


FIG. 3

### Phantom-powered circuits

The phantom-power circuit used to light the signal lamp is shown in Fig. 1. It's almost a textbook circuit. Back then, though, it was "the cutting edge of technology." (Textbooks, however, forget to mention that between the transformer and the output lines, we usually place a resistive padthe one I had to jumper.) Needless to say, the darn thing worked. And even though we had plenty of induced hum in the commonground circuit, someone back at the studio was able to get rid of it with a notch filter.

In the years that followed, I've seen phantom power rediscovered to feed such devices as condenser microphones. If we were to look back and trace the history of phantom power, we would find that it originated with the telephone system (for their line amplifiers). Most of you are probably more familiar with phantom power for TV amplifiers and microwave converters.

Figure 2 shows the most com-

mon phantom-powered circuit that technicians are likely to run across: a mast-mounted TV "antenna amplifier." Of course, in such an application, you do not want to run both a power line and antenna feed to the amplifier. Phantom power lets the amplifier gets its supply voltage from the transmission line. At the receiver end, a DC voltage from the power supply is coupled to the coaxial cable through an RF choke, L1. The choke isolates the RF circuit from the power supply.

At the amplifier/converter end (on the antenna mast), the DC voltage is stripped off the coaxial cable by another RF choke, L2, to power the solid-state devices. As far as the RF signal is concerned, the choke impedance is so high that no RF appears on the DC side.

### Phantom powered modems

One of the inconveniences of a modem is the power supply. It can be internal (which requires a fairly large cabinet) or external (which requires a wall-mounted AC adapt-

er—always an inconvenience.) The modem may have to be plugged into the terminal or computer so it can tap the equipment's power supply; or the supply could be a battery, which is sure to fail when most needed.

The more modern (not really modern) way to get the power is the way it's done in the Universal Data Systems 1003LP answer/originate modem, directly from the telephone system. The no-load voltage on a dial-up telephone line is 48-volts DC, which falls to nominally 6 volts when the handset is taken off hook, or any normal load is connected across the line.

Fortunately, micropowered solid-state devices—like modems—work very well on 5–6 volts, so we can phantom-power a complex active device directly from the telephone circuit. Figure 3 shows a simplified phantom-power source for a manual communications modem, therefore, no ring detector/automatic power circuits are shown.

Switch S1 connects the modem to the telephone line. The full-wave rectifier (consisting of diodes D1–D4) ensures against polarity problems with the telephone lines; regardless of the line connections, the rectifier's output polarity is unchanged. A metal-oxide varistor, MOV1, is inserted on the line side of the bridge rectifier to prevent transients that may be on the line from entering the modem.

The modem's I/O transformer, T1, is in series with the DC output of the rectifier. Capacitor C1 provides DC filtering and the AC return path for T1. (The signal current in T1 induces an input voltage to the modem, while the modem's output varies the DC current, hence the current in the telephone circuit.) Zener diode D5 is used to clamp the DC at 5 or 6 volts; however, it can be replaced by a voltage regulator.

While the circuit in Fig. 3 looks simple enough, it is not seen in general use because it takes a lot of hardware when a high supply-current is required. In such a case, it simply isn't cost effective. But if micropower devices are used, it's possible to sell a modem—such as Universal Data System's 103LP—for a list price of \$150.




# JANUARY 1985

# STATE OF SOLID STATE



ROBERT F. SCOTT, SEMICONDUCTOR EDITOR

Electronic locks

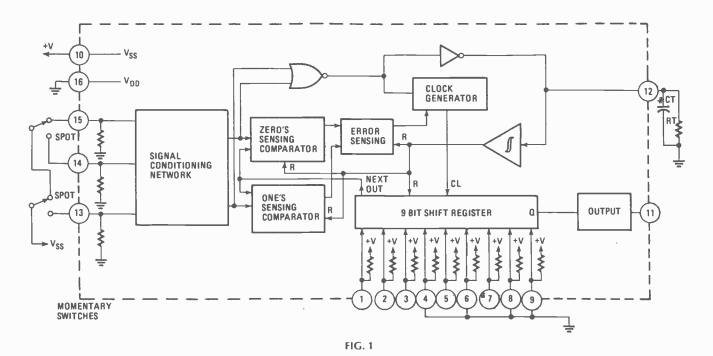

THE RAPIDLY RISING CRIME RATE HAS forced us to go to the extremes to protect our valuables. For instance, it is not uncommon to see two and three locks on a single door.

If you use conventional locks to secure your home or valuables, you could find yourself carrying large numbers of keys. That means everytime you want to open a door or gain access to your property, you'll be saddled with the task of sorting through several keys to find the one you need at that particular moment. However, there is another way to get the needed security—replace some of those conventional locks with coded electronic types.

Two electronic locks worth your consideration are the LS7228 and

LS7229 from LSI. Figure 1 is a block diagram of the innards of the LS7229 (the LS7228 is similar). Both units are ion-implanted, PMOS encoder circuits that include all the necessary logic to interpret the entry code and develop a momentary lock-control output. The LS7228 address decoder is keyed by two pulse trains of logic one's and zero's applied to the correct terminals. The LS7229 is keyed by two double-throw momentary pushbutton switches (which are used to enter one's and zero's).

Both units (housed in 16-pin DIP's) feature stand-alone lock logic, out-of-sequence disabling circuits, current-source lock-control outputs, externally controlled delay to set maximum time between pulses, and a 9-bit entry

code determined by 9 parallel inputs. Each IC is powered from a single-ended 2.5- to 15-volt supply. Maximum standby current is 15 IIA

The locks are controlled by a 9-bit binary code that has 512 possible combinations. The leading or most significant bit is set by pin 1 and the end (least significant) bit is set using pin 9. Code terminals 1 through 9 control a 9-bit shift register. The entry code is programmed into the lock by either jumpering or floating (leaving open) certain pins. Refer to Fig. 2, a practical circuit for the LS7229.

To program any given input to accept a logic 1, the pin corresponding to that input is left open. Jumpering a pin to ground programs a zero into the device at the

corresponding position in the entry code. For example, if pins 3, 4, 5, 6, and 9 are grounded and the others left open, the binary access-code would be 110000110.

The device is unlocked by entering the code (one's and zero's) in the correct sequence through switches \$1 and \$2. The zeros' and ones' entry ports are initially at logic zero (ground). As each key is pressed, its entry port goes to logic one and then returns to zero. When the first correct bit of the

ADER

lektronix

BECKMAN

**■Polaroid** 

DATA PRECISION

AMEE

POWER DESIGNS

SOLTEC

code is keyed in via \$1 and \$2, the external capacitor is discharged and an internal inhibit is removed so the circuit will be receptive to the second bit, and so on.

If all nine bits are in the correct sequence, a logic one passes through the shift register to the lock output at pin 11. An out-ofsequence entry or incorrect bit at any point in the entry code inhibits any further entry. After a delay period (determined by the time constant of an external R/C net-

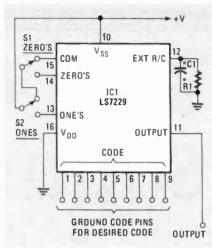


FIG. 2

work) a new sequence of key pulses may be applied. The lock-output (pin 11) switch-

es from zero to logic one as the voltage on pin 9 returns to zero following the last pulse of the entry code. It remains at logic one for a period about 30% longer than the R/C time constant. To hold the output at logic one, apply a tenth entry bit to either pin 13 or pin 14 and hold it high for as long as is necessary.

The output control is a current source so a load must be connected between pin 11 and ground. The source-current range depends on the supply voltage and the voltage across the load. For example, the source current averages 9 mA with a 9-volt supply and 8.5 volts across the load. It sources 26 mA with 7.5 volts across the load.


The time constant of the external R-C network at pin 12 determines the duration of the output pulse and the maximum permissible interval between valid entrycode bits. The time constant in seconds is the product of the resistance of R1 in megohms and the capacitance of C1 in microfarads. When using a 9-volt supply, the minimum suggested value for R1 is 2200 ohms and the maximum value is 3.3 megohms.

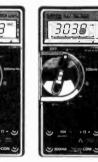The LS7228 and LS7229 binarylock circuits are available from LSI Computer Systems, Inc., 1235 Walt Whitman Road, Melville, NY 11747 at \$2.70 each for 1 to 24 pieces. Include \$5.00 for shipping and handling. New York State residents add sales tax. Data sheets are available on request.









Fluke 73 \$85

Analog, digital display Volts, ohms, 10A, diode

Autorange 0.7% hasic de accuracy 2000 + hour battery life 3-year warranty

Fluke 75

\$99

Analog/digital display Volts, ohms, 10A, mA, diode test Audible continuity

Autorange/range hold 2000 + hour battery life Fluke 77

\$129

Analog/digital display Volts ohms 10A mA diode test Audible continuity Touch Hold function Autorange/range hold 2000 + hour baffery life 3-year warranty Multipurpose holster

FROM THE WORLD LEADER IN DIGITAL MULTIMETERS





## The Professional Test Equipment Source The Instrument Mart

295 Community Drive, Great Neck, New York 11021 [516] 487-7430 Outside N.Y. (800) 645-6535

Sales, Service, Rental/Leasing Programs .. and Pre-Owned Test Equipment also Available







# **DRAWING BOARD**

More on the 4089


LAST MONTH WE LEARNED A THING OR


two about the 4089, but were not

quite finished with that device.

This time, let's start off by seeing

how it can be used to do division.

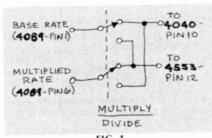

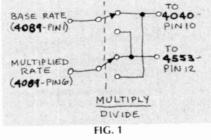

Division with rate multipliers Since we treated multiplication as successive addition, let's think of division as successive subtraction. In simpler terms, how many times can we subtract one number from another before we reach zero? To be practical about it, let's take a look at the circuit from our last discussion.

What we want to do with the circuit this time around is to keep track of the multiplied-rate pulses and count the base-rate pulses (the opposite of what we did previously). In hardware terms, that means we have to switch two wires in the circuit!

Figure 1 can be considered an addendum to the circuit we did last month; it shows the extra hardware needed to switch between the multiplication and division modes. With the display added, all we need do is put a DPDT switch to change the operation of the circuit from multiplication to division.

Doing more complex forms of arithmetic, such as squares and roots, is possible as well. Virtually any arithmetic operation can be written as a series of operations that involve only multiplication and division. A good mathmatics textbook will show you what has to

Once you have that taken care of, arrange your circuit to do the necessary arithmetic and that should be that. Start out with

(ADD MODE) WEIGHTED 015 ICI IC2 12 4089 4089 11 CLOCK INO WEIGHTED 015 TC2 ICI 4089 4094 CLOCKINO (MULTIPLY MODE)

FIG. 2

square roots and continue from there. If any of you do breadboard such a circuit, send me the details and I'll put them in the column for everybody else to see. Remember that the whole point of this col-



ROBERT GROSSBLATT

umn is to share information (you've got to give a little to get a little).

There are two problems left for us to talk about. The first is figuring out a way to make the circuit easier to use and the second is making the circuit more useful. Let's tackle the second one first.

## Cascading the 4089

The 4089, and all the other rate multipliers, are easy to cascade and there are two different ways of doing it. Which way you choose depends on the kind of arithmetic vou want to do.

In Fig. 2-a, the IC's are cascaded in what National Semiconductor calls the "add" mode. IC1 works just the way it did in our demonstrator circuit and if you were to check the output of IC1, you would see the same results we saw earlier. Things aren't terribly straightforward when you're in the "add" mode, however. Since IC2 has its cascade input connected to the output of IC1, its multiplied rate will be 16 times greater than that of IC1.

On the other hand, if you wanted to do division by-let's say, 72you would have to remember that IC1 is working with a base of 16 and IC2 is working with a base of 256 (16 times 16). In order to figure out what numbers to present to the inputs of the 4089, you have to do some additional work to reduce everything to a base of 256. If A is the most significant digit (at IC1) and B is the least significant digit (at IC2), then:

 $(A \times 16) + B = 72$ The trick is to find how large you can make A without exceeding 73.

88



Sales of small computers are running over a billion dollars a year. That's why a whole new business is starting up-devoted entirely to small computer repair. And right now is the time to get in on the ground floor-either working for someone else or in your own computer repair business

Start making money in electronics

No need to gult your job, change your daily routine or take time from family responsibilities. And you don't waste



Experts show you what to do... how to do it! We start you fast with the basics, and everything is explained in easy-to-understand language complete with plenty of dia-GET INTO SMALL grams and COMPUTER drawings

REPAIR

SEND FOR FREE FACTS!

You receive

microprocessor

trainer, digital V.O.M. and much

more included

with course

School of Computer Repair, Dept. DE@C4
Since 1891
Scranton, Pennsylvania 18515
Scranton, Pennsylvania 18515 Send free facts and color brochure telling how I can get into computer repair at home In my spare time. No obligation. No salesman will call.

Name	Age
Address	
City / State / 7in	



## **SAVE BY BUILDING OUR RACK MOUNT** STUDIO EQUIPMENT

QUADRAFUZZ - for separate frequency bands of distortion are mixed for the smoothest fuzz you've ever heard. no. 6720 . . . . . . . . \$ 39.88

HYPERFLANGE/CHORUS - the cleanest, widest range, most versatile flanger anywhere at any price. no. 6750 . . . . . . . . . . . .

VOCODER - unmatched performance in a versatile, low cost rack package. no. 6710 . . . . . . . . \$99.95

HOT SPRINGS - user's agree, short of studio plate systems, you won't find a better reverb at any price. no. 6740. \$59.95

> **ADD \$3 SHIPPING** FOR EACH KIT ORDERED

Innovative, cost effective designs by Craig Anderton in easy to assemble kits from:

## **Phia** Electronics, Inc.

Direct mail orders and inquiries to: Dept. 11R 1020 W. Wilshire , Oklahoma City, OK 73116 - (405)843-9626 Ask for your free catalog.

CHARGE TO VISA OR MC TOLL-FREE 1-800-654-8657 9AM to 5PM CST MON-FRI

CIRCLE 90 ON FREE INFORMATION CARD



Minor brain burning gives us an answer of four for A; therefore, B has to be eight. To sum it up, we put a binary four (0100) and a binary eight (1000) at the weighted inputs of rate multipliers IC1 and IC2, respectively.

A much easier way to take care of that is to use the second method of cascading the 4089, which National Semiconductor refers to as the "multiply" mode. That configuration, shown in Fig. 2-b, is a standard cascading arrangement. It is more common than the "add" mode, but as we'll soon see, it is not as versatile.

The procedure is little different and a lot simpler than the previous method. Here the outputs of the IC's are multiplied together in a normal cascade arrangement, making the arithmetic a lot easier, as can be seen from the equation:

 $A \times B = 72$ 

Our only restriction in choosing values for A and B is the four-bit width of the IC's; 12 and 6 are the only choices.

You've probably noticed that not all numbers can be obtained using that method, which is why the add mode is more versatile. However, if we were doing multiplication, the restriction wouldn't apply and this method would be better, since it would mean fewer traces on the board.

Like almost everything else in digital circuitry, our description makes it sound much more complicated than it really is. If you try working with the rate multiplier, you'll find that it can provide easy solutions to what would otherwise be seemingly impossible circuit problems.

The second problem is designing some sort of circuit that would make it easy for us to select the numbers we want to use. Because the 4089 has binary inputs, the keyboard encoder covered in the February, March, and April 1983 installments of "Drawing Board" would be perfect.

If you're interested in the topic of keyboard data entry, check out those issues of Radio-Electronics (if you don't have them, try your local library). If there is enough interest in the subject, let us know; we'll spend some more time talking about it.

# JANUARY 1985

# DESIGNER'S NOTEBOOK




ROBERT GROSSBLATT

## Audio overload protection

IN ANY CONTEST TO RATE THE MOST popular areas of electronics, audio circuits and projects would undoubtedly be among the top ten. There is probably more home "tinkering" done in the areas of equalization, noise reduction, amplification, and so on than in any other field. And, as we all know, hardly a day goes by without an announcement from one semiconductor manufacturer or another about a new audio IC.

Each successive generation of audio IC has more features packed into it than its predecessor and can handle really mind boggling amounts of power. For instance, it wasn't long ago that an LM386 driver-amp blew everybody away because, with just a handful of external parts, it could output a ½ watt of continuous power into an 8-ohm load. These days, however, IC power-amps need virtually no external components, and one

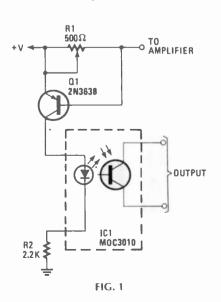


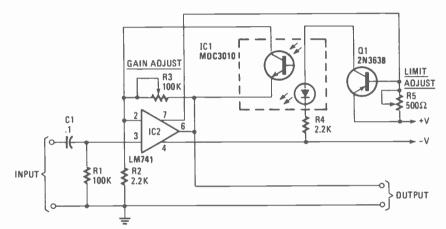


FIG. 2

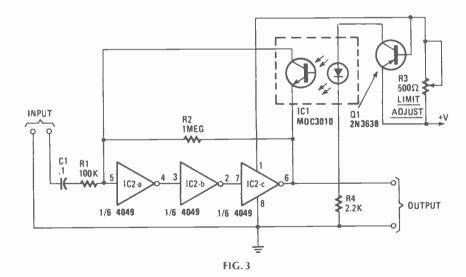

with more than 10 watts of powerhandling capability can be held on the end of your little finger!

Every amplifier (regardless of type) has maximum power ratings. It those limits are exceeded, the amplifier and any associated components may be destroyed, so you must be careful. (Remember overloading can cause lots of trouble.)

Overloading is hard to guard against because a typical audio signal can have a really wide dynamic range—sometimes more than 30dB.

## Overload protection scheme

Protecting audio circuitry against overload (accidental or otherwise) is an important consid-












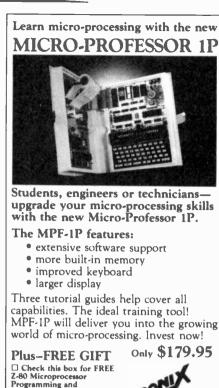

MPF-1P will deliver you into the growing world of micro-processing. Invest now! Only \$179.95

Check this box for FREE Z-80 Microprocessor Programming and Interfacing textbook when you order within 7 days. 12.95 value. (Include \$5.00 postage & Redmond, WA 98052 handling) For immediate action call TOLL FREE:

Dent. RE015 14803 N.E. 40th Redmond, WA 98052

1-800-426-1044

Full money back guarantee.

CIRCLE 111 ON FREE INFORMATION CARD



No costly School. No commuting to class. The Original Home-Study course that prepares you for the FCC Radiotelephone license exam in your spare time! An FCC Government license is your "ticket" to thousands of exciting jobs in Communications, Radio & TV. Mobile two-way, Microwave, Computers, Radar, Aerospace and more. You don't need a college degree to qualify, but you do need an FCC License. No need to quit your job or go to school! You learn how to pass the FCC License exam at home at your own pace with this easy-to-understand, proven course. It's easy, fast and low cost! GUARANTEED PASS You get your FCC I icense or money retunded. Write for free details. Soon you could be on your way to being one of the highest workers in the electronics field. Send for FREE facts now. MAIL COUPON TODAY!

COMMAND FCC LICENSE TRAIL P.O. Box 2223, San F Rush FREE facts on In spare time. No ob	NING, Dept. 90 Francisco, CA 9412 how I can get my	26 FCC License
NAME		
ADDRESS		
CITY	STATE	ZIP



eration, and should be on the mind of any serious audio-circuit designer. The best place to guard against overload is in the early stages where signal levels are low. The further along you are in the audio chain, the "beefier" the signal becomes, and the harder it is to add some type protection scheme. To complicate matters, overloads in the final power stages stand a much greater chance of "smoking" some expensive parts.

The circuit shown in Fig. 1 is the beginning of a protection scheme that can be made from a few common components. It's capable of monitoring circuit gain, and will also make sure that signal levels stay within the pre-set range. (The original circuit used a nonstandard optocoupler or optoisolator constructed from readily available parts, which we'll tell you how to make a little later.)

The best place to put the circuit is either in the feedback loop or shunted across the preamp input. Although the circuit tends to limit the gain of a preamp, keep in mind that it's meant to show you one way to approach the problem, and is by no means the only way to get the job done. Once you try it and become familiar with how it works, there are several "offshoots" of that design, which you can make following the same basic idea.

Figure 1 shows a 500-ohm potentiometer (R1) sitting right on the line feeding power to the preamp. When the audio signal is increased, the preamp draws more power to handle the larger signal. That results in a greater amount of current through R1, which causes a proportionate voltage to develop across the potentimeter.

Transistor Q1 monitors the voltage supplied to the amp through resistor R1. Whenever that voltage reaches the V<sub>CE</sub> threshold, the transistor turns on, causing the LED in the optocoupler to light. That, in turn, causes the phototransistor to conduct. What you do with output of the optocoupler depends on how you design your audio circuit but (as already stated) the best place for it is either in the feedback loop or across the preamp input.

continued on page 112

# JANUAHY 1985

# SERVICE CLINIC

## Kit building made easy

HANDS-ON ELECTRONICS IS A GOOD phrase. Everyone should have some experience in making things. Once you've actually built something, you'll know much more about how it works.

One thing every electronics hobbyist should have is some test equipment. But, as you probably know, the most desirable equipment can be expensive. There is, however, a way to get the test gear you need, and save a good deal of money in the process. Of course, I'm referring to test equipment in kit form.

Saving money isn't the only advantage—you can also gain much knowledge about how the device is made and what it can do. Kits range from the simplest (an analog VOM, for example) to things more complex than a digital frequency counter. I speak from much experience: at least ten instruments among my collection were made from kits, and they're darn good instruments, too!

One of the niceties of kit building is that the most complex instrument can be just as easy to build as the simplest one! Instruction and construction manuals (see Fig. 1) supplied with the kit tell you exactly how the instrument works and how to use it. Be warned, however, you must follow the construction manual to the letter. Don't take short cuts!.

The manuals were written by people who have made and sold thousands of those devices. Therefore, what they tell you to do is always the best way to do that particular job. Follow them closely and you'll find that the job goes much faster, and you'll wind up



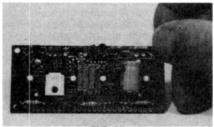


FIG. 2

with an instrument that stands a far greater chance of working the first time it's turned on.

Believe it or not, I've almost never had one work the first time—always because of some stupid mistake I'd made! And that's what this article is about: how to find and correct those mistakes. Not only will the information found here aid you in kit building, but it can help make any construction project or repair job go a bit smoother.

### **Correcting construction errors**

In building any electronic device, you should check your work



**JACK DARR** 

both during and after each phase of construction. For instance, when placing a part in a circuit board, make sure it's in the right place, correctly oriented, and is the value called for in the instructions before soldering. In that way, any mistakes—parts put in backwards, etc.—can easily be corrected.

After soldering, check for solder bridges—splashes of solder caused by sloppy workmanship—especially between closely-spaced, adjacent PC-board conductors (see Fig. 2). Solder bridges can be a real headache to locate, because they are the same color as the conductors of the PC board! A magnifying glass is a handy thing to have around when checking for solder bridges. It can help you locate those hair-line bridges, which often are undetectable to the naked eye.

I once wired up a fairly complex kit, taking extreme care (or so I thought) to avoid solder bridges. But when I powered it up, it did nothing! Checking over my work carefully with a big magnifying glass, I found no less than five bridges. After correcting the problem, my kit worked like a charm. So don't ever be too confident that you haven't made any bridges. Look your work over very closely, and if you find any bridges, take them out.

While you're checking for bridges, look for any unsoldered terminals or cold solder joints. Unsoldered terminals are a common occurrence in kit building. That is, after you've finished putting the kit together, a joint or two is still not soldered. That's usually

caused by not reading the instructions carefully.

A good construction manual (from Heathkit, for example) will tell you to put in a part and then "S," for solder or "NS," for not solder—which should tell that there are more parts to be connected to that joint—so that terminal should not be soldered yet. After completing a section, make sure that each terminal is soldered or not soldered as instructed.

Cold solder joints are another common source of trouble. They can be identified by their frosty appearance. If you find one or more, simply reheat the joint and, if necessary, apply a bit more solder. A good solder joint usually shines like silver. Assuming that all appears well, you can power up the device.

If nothing happens, follow the same routine you would with any other piece of "dead" equipment. Go back and check the wiring, parts placement, and so on. Then if you find no errors, power it up again and check the DC voltage source and the places where DC voltages should be.

Chances are you'll find that the voltage is missing in one or two places. When you find a place that should have voltage but does not, simply trace back through the circuit until you find the place where the trouble is. Fix that point and make sure that there are no more missing voltages. Once you get the DC voltages all straightened out, the device should work. If it doesn't, you'll have to recheck everything. Never be lulled into a false sense of security because you believe you've followed every step. Remember, overconfidence can be disastrous!

Suspect everything until you have double checked it. Go back, recheck the manual, and be sure the part in each position is the type and value called for. If you do that carefully, there's a far greater chance of your project working the first time.

Kits are really very easy to assemble (as you will find out) if you follow the instructions. Take it very slow and easy, and be sure to check off each step as you go (using a red pencil, so the check marks will stand out).



TIMEX/SINCLAIR 1000, 1500, 2068, ZX81, SPECTRUM Hardware & Software for all computers: NEW! Floppy disk interface. Std format. Order FLOPPY: \$200. PRTR I/F—Centronics printer interface. Order PRTIF: \$50. ASM/DSM—Full featured assembler/disassembler. Order ASMDSM: \$40. ALSO, Cables for all products. Write for prices and descriptions. When ordering, specify type of computer. Research Service Laboratories, P.O. Box 19124, OKC, OK 73144.

**CIRCLE 274 ON FREE INFORMATION CARD** 



P-250 AMBIANCE/SURROUND SOUND DECODER. Extracts ambiance from stereo recordings and Surround Sound effects from Dolby™ encoded movies. P-250-DL (kit) \$180, P-250-DLA (assem & tested) \$250. MC/Visa OK. 203-643-4484 Phoenix Systems, Inc., POB 628-RE, Manchester, Ct. 06040.

**CIRCLE 69 ON FREE INFORMATION CARD** 



- 6 × rate \$650 per each insertion.
- Reaches 225,016 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads
- We typeset and layout the ad at not additional charge.

Call 212-777-6400 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS. RADIO-ELECTRONICS. 200 Park Ave. South, New York, NY 10003.



APPLIANCE REPAIR HANDBOOKS—13 volumes by service experts; easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. \$2.65 to \$5.90 each. Free brochure. APPLIANCE SERVICE, PO Box 789, Lombard, IL 60148. 1-(312) 932-9550.

**CIRCLE 84 ON FREE INFORMATION CARD** 




SATELLITE CONTROL CABLE-NEMAL ELECTRONICS has designed a new series of combination cables for TVRO installations. These cables provide all necessary wires for signal, motor and receiver power and sense circuits together in one direct burial jacket. TYPE-1 RG-59 + 9 conductor (2-18gu) \$495/1000', TYPE-2 RG-59 + 11 conductor (2-12gu) \$689/1000', TYPE-3 dual RG-59 + 11 conductor (2-12gu) \$879/1000', all made with milspec RG59, 96% copper shield. tinned drain wires. Over 500 types of cable, connectors, SMATV products in stock, Authorized distributor Kings-Amphenol-Columbia. NEMAL ELECTRONICS Inc., 12240 N.E. 14th Ave., N. Miami, FL 33161 (305) 893-3924.

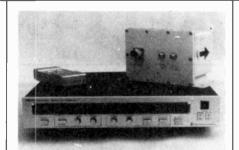**CIRCLE 257 ON FREE INFORMATION CARD** 



SUBSCRIPTION TV MANUAL. This information packed book details the methods used by subscription TV companies to scramble and descramble video signals. Covers the Sinewave, Gated Pulse, SSAVI system, and the methods used by most cable companies. Includes circuit schematics, theory, and trouble shooting hints. Only \$12.95 plus \$2.00 first class P&H. ELEPHANT **ELECTRONICS INC., (formally Random** Access) Box 41770-R, Phoenix, AZ 85080. CIRCLE 120 ON FREE INFORMATION CARD



SATELLITE TELEVISION RECEIVER SEMIKIT with dual conversion downconverter. Features infrared remote control tuning, AFC, SAW filter, RF or video output, stereo output, Polorator controls, LED channel & tuning indicators. Install six factory assembled circuit boards to complete. Semikit \$400.00. Completed downconverter add \$100. Completed receiver and downconverter add \$150. JAMES WALTER SATEL-LITE RECEIVER, 2697 Nickel, San Pablo. CA 94806. Tel 415-724-0587.


**CIRCLE 124 ON FREE INFORMATION CARD** 



ZENITH SSAVI-1, STV -1, STV-2 **COMPLETE DESCRAMBLER MANUAL** Original Zenith schematics. Theory of operation and repair information. Modifications for use on cable and satellite systems. How to bypass addressing system. Replacement parts and power supplies available.

\$19.95 plus S&H C.O.D. Visa or Mastercard. S&L ELECTRONICS, 3800 Enterprise Drive, Allen Park, Michigan, 48101. (313)562-9747.

CIRCLE 272 ON FREE INFORMATION CARD

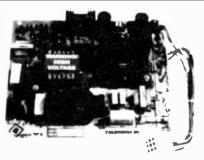


California-DC Regulated Switching Power supply +5v dc @ 5 amp + 12v dc @ 2.8 amp +12v dc @ 2 amp -12v dc @ .5 amp 115-230v ac input, fused. EMI filtered. Removable DC Power Harness and Schematics included. 7.4"  $\times$  6.2"  $\times$  1.7" ht. Visa/MC/ M.O./check; when clears. \$37.50 ea. (Free shipping in U.S.) 1-800-327-7182/305-830-8886. Power Plus, 130 Baywood Ave., Longwood, Fl. 32750. (Call for quantity

CIRCLE 125 ON FREE INFORMATION CARD



FREE 1984 ELECTRONIC TOOL & IN-STRUMENT CATALOG is packed with over 5,000 quality technical products for assembling, testing and repairing electronic equipment. All products fully illustrated with photographs, detailed descriptions and pricing to allow for easy ordering by phone or mail. Most orders are shipped within 24 hours. 100% satisfaction guarantee. CONTACT EAST, 7 Cypress Drive, Burlington, MA 01803. (617)272-5051.

**CIRCLE 55 ON FREE INFORMATION CARD** 

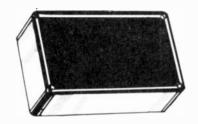

SCIENTIFIC ATLANTA Introducing the CM-04 cable TV descrambler. Compatible with Scientific Atlanta 8500 series cable systems. Total channel capability. Assembled and tested. Simple plug-in installation. Regular Price \$180.00. Special Introductory Offer \$145.00, C.O.D. orders accepted. Quantity discounts available. V.I.P. Electronics, P.O. Bcx 628, Forestdale, R.I. 02824, (617) 755-9778.

**CIRCLE 273 ON FREE INFORMATION CARD** 




**ZORBA 64K PORTABLE COMPUTER 9"** Green or Amber CRT. Two 400 K DSDD Drives, CP/M 2.2 Operating System. \$799.00. Gemini Electronics, Inc., 130 Baywood Ave., Longwood, FL 32750. 1-800-327-7182, 305-830-8886.

**CIRCLE 258 ON FREE INFORMATION CARD** 



FREE CATALOG OF HARD-TO-FIND TOOLS is packed with more than 2000 quality items. Your single source for precision tools used by electronic technicians, engineers, instrument mechanics, schools, laboratories and government agencies. Also contains Jensen's line of more than 40 tool kits. Send for your-free copy today! JENSEN TOOLS INC., 7815 46th St., Phoenix, AZ 85040. (602) 968-6231.

**CIRCLE 115 ON FREE-INFORMATION CARD** 

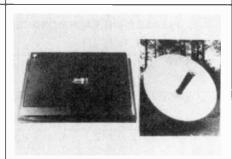

ZENITH SSAVI DESCRAMBLERS only \$159; complete with power adapter ready for UHF channels 22,23,27,31,50,54, and others, or Z-tac cable, chs. 2-13, A-W, with optional block converter. Quantity discounts! GATED PULSE & SINEWAVÉ decoders available. SATELLITE SYSTEMS starting at \$845; Installation and program guide, \$3. Dealers welcomed, Catalog \$1. Visa/Master-Card AIS SATELLITE, P.O. Box 1226-E, Dublin, PA, 18917. (215) 249-9411.

**CIRCLE 255 ON FREE INFORMATION CARD** 

## MARKET CENTER

#### FOR SALE

CABLE-TV Secrets—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Suppliers list included. \$8.95. CABLE FACTS, Box 711-R, Pataskala, OH 43062.

RESISTORS 1/4W&1/2W5% 3 cents. 1%metalfilms, precision custom wirewounds, \$1.00 refundable to: JR INDUSTRIES, 5834-B Swancreek, Toledo, OH

FREE catalog featuring scanner accessories, carrier/subcarrier detectors, voice scramblers, unusual kits. CAPRI ELECTRONICS, Route 1R, Canon, GA 30520.

THE Intelligence Library—Restricted technical information & books on electronic surveillance, surveillance-device schematics, lock-picking, investigation, weapons, identification documents, covert sciences, etc. The best selection available. Free brochures. MENTOR, (Dept. Z), 135-53 No. Blvd., Flushing, NY 11354.

CABLE-TV equipment, tunable notch filters for "beeping" channels. Information \$1.00. DK VIDEO, PO Box 63/6025 RE, Margate. FL 33063.

DIGITALKER Speech Synthesizer has 136 word vocabulary. Interfaces with parallel port of your computer. PCB and plans \$12.00. JIM RHODES, INC., 1025 Ransome Lane, Kingsport, TN 37660.

THE BEST PLACE to BUY, SELL or TRADE NEW and USED EQUIPMENT NUTS & VOLTS MAGAZINE

BOX 1111-E • PLACENTIA, CA 92670 (714) 632-7721 oin Thousands of Readers Nation Every Month ONE YEAR U.S. SUBSCRIPTIONS \$10.00 - 3rd Class \* \$15.00 - 1st Class \$35.00 - Lifetime - 3rd Class HAM GEAR

TUBES, new, unused. Send self-addressed, stamped envelope for list. FALA ELECTRONICS, Box 1376-2, Milwaukee, WI 53201.

FREE Pay-TV reception. "How-To" book. HBO, Showtime, Cinemax. \$5.00. DIPTRONICS, Box 80 (E2), Lake Hiawatha, NJ 07034.

CONVERTERS all types for all systems. Lowest prices anywhere, quantity discounts, dealer inquiries accepted. Send \$1.00 for catalog, PG VIDEO CORP., PO Box 296, Latham, NY 12110. (518) 274-6593

AUTOMOTIVE Security Catalog. 1984, 24-page color catalog, \$2.00. ASE, Dept. 1, PO Box 382, Plainview, NY 11803.

COMPUTER hacking: How it's done and how to stop it! Details: A.T.I.S., 61 Gatchell, Buffalo, NY

WANTED: RCA, Cunningham, Western Electric, Genalex, Telefunken, GE, Sylvania, McIntosh, Marantz, Altec, JBL, Tannoy: Tubes, amplifiers, speakers. (713) 728-4343, MAURY, 11122 Atwell, Houston, TX 77096.

CABLE-television facts and secrets. Now you can get the informative publication that CATV comcan get the informative publication that CATV companies have been unsuccessfully trying to get banned for 15 years. Movie Channel, HBO, and Showtime converters, etc. Send \$8.75 to: CABFAX, P.O. Box 091196, Bexley, OH 43209.

WHOLESALE MATV/CATV equipment, antenna, accessories, cartridges, radios, speakers, wires. (718) 897-0509, D&WR, 68-12 110 Street, Flushing, NY 11375.

BIGGEST TI-99/4A selection. Newest exciting software and hardware bargains. Hard-to-get items. Send for free catalog. Fast service. **DYNA**, Box 690, Hicksville, NY 11801.

GUARANTEED quality surplus for less! Free flyer. ELECTRONIX LTD., 3214 South Norton, Sioux Falls, SD 57105.

CORDLESS- phone owners, Increase distance, reduce static on 1.7/49MHz phones. Details \$1.00 refundable. HP PHONES, Box 273, Mesa, AZ

DELUXE cable/UHF converters. Zenith, SSAVI-1-\$199.95. Zenith Cable—\$229.95. Jerrold, Oak and others available. Dealers wanted. \$2.00 catalog—UNITED ELECTRONIC SUPPLY, Box 1323, Elgin, IL 60121-0119. (312) 697-0600.

COCO owners—Free color computer software and hardware catalogue. SPECTRUM, Box 9866, San Jose, CA 95157-0866.

INDIVIDUAL photofact folders. No. 1 to no. 1400, \$3.00 postpaid. LBT, 414 Chestnut Lane, East Meadow, NY 11554.

This ad is set with a background screen. Notice how it stands out on the page. This ad incurs a 25% premium charge. Perhaps your next ad could have a screen background. For ordering information, see top of Market Center listing.

TRICKS of the burglar alarm trade: Well iliustrated, non-technical. Covers equipment, installation procedures, troubleshooting, "by-pass" methods & countermeasures. Free brochure: MENTOR PUBLICATIONS, (Dept. L), 135-53 No. Blvd., Flushing, NY 11354.

CABLE-TV equipment: Jerrold, Hamlin, Zenithmany others. Factory units/lowest dealer prices. Send large self-addressed-stamped-envelope to: CABLETRONIX, 7325½ Reseda Blvd., Reseda, CA 91335, (818) 346-5071.

AUTOMOTIVE AM/FM stereos \$49.95 up. 40 piece socket set, lifetime warranty \$39.95. Free catalog, NEPTUNES CAVE, Box 8837, Fort Worth, TX

B&K 747B tube tester like new, \$250.00---(702)

#### **CLASSIFIED RATES**

CLASSIFIED RATES

15 word minimum: \$37.50, \$2.50 per word commercial; \$30.00 \$2.00 per word personal. Expanded type ad, \$3.75 per word. Ads set in all bold-face type at 20% premium. Ads set with background screen at 25% premium. Display ads 1" × 2¼" - \$270.00; 2" × 2¼" - \$540.00; 3" × 2½" - \$810.00. General Information: frequency rates and prepayment discounts are available. Payment must accompany order. Copy subject to publishers approval. Must be typewritten or printed. First word set in all capitals and boldface: Advertisers using P.O. Boxes must supply permanent address and telephone numbers. Orders are not acknowledged. They will appear in the next available issue after receipt. Copy to be in our hands on the 20th of the third month preceding the date of the issue (i.e. August issue closed May 20th. When normal closing date falls on Saturday Sunday or a holiday issue closes on issue closed May 20th. When normal closing date falls on Saturday, Sunday or a holiday issue closes on preceding working day. Send order and remittance to Classified Advertising Radio-Electronics, 200 Park Avenue South, New York, New York 10003. For your convenience a simplified order form is provided on this page.

#### **ORDER FORM**

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$20.00. ( ) Business Opportunities truction ( ) Wanted ( Plans/Kits ) For Sale ) Satellite Television **Education/Instruction** (

Special Category: \$20.00

PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15
16	17	18	19	20
21	22	23	24	25
26	27	28	29	30
31	32	33	34	35



Tel.: 1 (816) 842 5092 1901 MCGEE STREET KANSAS CITY, MO. 64108

## TRANSFORMERS RS-232 EXTENSION



5.6 VOLTS @ 750 MA OLTS @ 150 MA \$1.25 12 VCT @ 200 MA \$2.00 18 V. @ 650 MA \$3.50 18 VOLTS @ 1 AMP 24 VOLTS @ 250 MA 24 VCT @ 1 AMP \$2.50 \$4.50

#### TRANSFORMER WALL

ALL ARE 115 VAC PLUG IN



#### SPRING LEVER **TERMINALS**

WO COLOR KELITE PLATE



\$1.00 EACH 10 FOR \$9.00



LINES 1 THROUGH 8 & 20. DB25 MALE TO FEMALE. 10 FEET SHIELDED \$11 00 FACH

## 

5 CONDUCTOR IN-LINE PLUG AND CHASSIS MOUNT JACK TWIST LOCK STYLE 12CL5M \$2.50 PER SET

#### MULTI-**SWITCHES**



3 - 2PDT SWITCHES. EACH OPERATES INDEPENDENTLY 14" BETWEEN MOUNTING CENTERS. \$1.75 EACH

#### **5 STATION** INTERLOCKING

MADE BY ALPS - COOL 3 - 2PDT AND 2 - 6PDT SWITCHES ON FULLY INTERLOCKING ASSEMBLY

34" BETWEEN MOUNTING CENTERS

#### 5 STATION NON-INTERLOCKING

SAME AS ABOVE. EXCEPT EACH SWITCH OPERATES INDEPENDENTLY \$2.50 EACH

## 2 CHANNEL LIGHT ORGAN

EASILY HOOKS INTO STEREO SPEAKERS AND ALLOWS 110 VAC LIGHTS TO DANCE WITH MUSIC, TWO SEPARATE 110 VAC OUTPUTS FOR HIGH AND LOW FREQUENCY AUDIO SIGNALS. USE TWO ORGANS FOR STEREO

\$6.50 PER LINIT

COLOR LIGHT STRING AVAILABLE \$1.75 FA



## MIKE CONNECTOR

#### METER 0 - 15 V.D.C.



THIS 2-1/4 QUARE METER MEASURES 0-15 VDC \$4.50 EACH

#### SUB-MINIATURE D TYPE CONNECTOR

ो रामगामा

CHIMHHIP PO SOLDER TYPE SUB-MINIATURE CONNECTORS USED FOR COMPUTER HOOK UPS.

DB-15 PLUG DB-15 SOCKET DB-15 HOOD \$2.75 \$4.00 \$1.50 DB-25 PLUG DB-25 SOCKET DB-25 HOOD

#### 'PARALLEL" PRINTER CONNECTOR



USED ON "PARALLEL" DATA CABLES

### I.D.C. MALE



#### 7 CONDUCTOR RIBBON CABLE



\$5.00 PER ROLL (100 FT.)

## 1 POLE 6 POSITION

75° EACH





DOUBLE POLE POWER SWITCH PUSH-OFF \$1.00 EACH

#### **SWITCHES** MINI-PUSH BUTTON

SPST MOMENTARY NORMALLY OPEN 1/4" BUSHING

> 35¢ EACH 10 FOR \$3.25 100 FOR \$30.00

SPECIFY COLOR: RED. BLACK, WHITE GREEN, YELLOW

COMPUTER

GRADE

2,000 mfd, 200 VDC

3/4" DIA. + 5" HIGH

3,600 mfd. 40 VDC

6,400 mfd. 60 VDC

22,000 mfd. 40 VDC

31,000 mfd. 15 VDC

13/4" DIA. - 4" HIGH

72,000 mfd. 15 VDC

185,000 mfd, 6 VDC

2" DIA . 4 3/8" HIGH

2" DIA = 6" HIGH

13/8" DIA + 33/4" HIGH

13/8" DIA × 41/4" HIGH

CAPACITORS



SPECTRA STRIP RED MARKER

## **2K 10 TURN**

SPECTROL MOD 534-7161 \$5.00 EACH

## ROTARY SWITCH

1%" DIA x 11/2" HIGH



### EDGE CONNECTORS



#### 10 PIN EDGE CONNECTOR

TRW #50-10-A-20 \$2.00 EACH 18/36 GOLD

SOLDER EYELET \$2.00 EACH 22/44 TIN

C. STYLE: NO MOUNTING EARS \$1.50 EACH 10 FOR \$14.00 22/44 GOLD

\$2.00 EACH 10 FOR \$18.00 PC. STYLE 28/56 GOLD

28/56 GOLD PLATED CONTACTS .156 CONTACT SPACING. \$2.50 EACH 10 FOR \$22.00

48 PAGE CATALOG FREE! FREE! FREE!

1

75¢ EACH

SLIDE & POTS

100K Ilnear tape

500K linear taper

DUAL 100K audio taper

CRYSTALS

CASE STYLE HC33/U

COLORBURST 3579.545 KC

3 1/2" LONG 2 1/2" TRAVEL. \$1,50 EACH

\$3.50 EACH \$1.00 EACH

METAL OXIDE

VARISTOR

50 VOLTS, NOMINAL D.C. VOLTAGE 5/8" DIAMETER

2" LONG 1 5/8" TRAVEL

2 7/8" LONG 1 3/4" TRAVEL

П

2 MH2

G.E. # V82ZA12

### REVERBERATION UNIT



\$7.50 EACH

ACCUTRONICS COIL SPRING TYPE UNITS. USED IN ELECTRONIC ORGANS TO PROVIDE ACOUSTIC DELAY SOUND EFFECTS. INPUT IMPEDANCE 8 OHMS, OUTPUT IMPEDANCE 2250 OHMS. 41/2" x 161/4" x 15/16."

#### SOUND AND VIDEO MODULATOR FOR T.I. COMPUTER



\$10.00 FACH

#### **48 KEY ASSEMBLY FOR** T.I. COMPUTER



**NEW TEXAS INSTRUMENTS** KEYBOARD. UNENCODED 48 S.P.S.T. MECHANICAL SWITCHES. TERMINATES TO 15 PIN CONNECTOR. SOLID METAL FRAME 4" x 9."

\$6.50 EACH 2 FOR \$11.00

## 120V INDICATOR 0

NEON INDICATOR, RATED 120 V 1/3 W. MOUNTS IN 5/16" HOLE ... RED LENS 75¢ EACH

10 FOR \$7.00 100 FOR \$65.00

#### **GEL CELL** BATTERY



12 VDC @ 1.2 AMP HOUR 4" X 1 13/16" X 2 1/8: \$15.00 EACH

L.E.D.'S

STANDARD JUMBO

DIFFUSED

FLASHER LED

5 VOLT OPERATION RED JUMBO SIZE

\$1.00 EACH

**BI POLAR LED** 

2 FOR \$1.70

LED HOLDERS

TWO PIECE HOLDER

CLEAR CLIPLITE
HOLDER
MAKE LED A FANCY

3 1/2"

10 FOR 65¢

200 FOR \$10.00

INDICATOR, CLEAR, 4 FOR \$1.00

SPEAKER

8 OHM IMPEDANCE, FULL RANGE SPEAKER.

8 OZ MAGNET. 4° DIAGONAL

RED 10 FOR \$1.50 GREEN 10 FOR \$2.00 YELLOW 10 FOR \$2.00

## FREE! FREE! FREE! SEND FOR

### LINE CORDS

TWO WIRE 18ga TWO WIR 3 FOR \$1.00

18 INCH 18ga THREE WIRE 2 for \$1.00 8 FOOT 18ga THREE WIRE

## **IRON STAND**



\$5.00 EACH

#### TRANSISTORS

HAR	13 I UK
2N706	4 FOR \$1.00
2N2222A	3 FOR \$1.00
PN2222	4 FOR \$1.00
2N2904	3 FOR \$1.00
2N2905	3 FOR \$1.00
2N2907	3 FOR \$1.00

5 KEY



\$1,00 EACH

NORMALLY OPEN SWITCHES MEASURES 3 3/4" LONG



CONTAINS 6 SINGLE-POLE NORMALLY OPEN SWITCHES MEASURES 4 1/4" LONG.

#### DC-DC CONVERTER



DESIGNED TO PROVIDE STEADY ±5 VDC @ 240 MA FROM A BATTERY SUPPLY OF 3.5 TO 6.25 V.

\$1.50 EACH

## RELAYS SOLID STATE RELAY

HEINEMANN ELECTRIC #101-5A-140-5 AMP CONTROL: 3-32VDC LOAD: 140VAC 5 AMPS #101-5A-140 \$5.00 10 FOR \$45:00

#### MINIATURE **6 VDC RELAY**



SUPER SMALL SPDT RELAY; GOLD COBALT CONTACTS

RATED 1 AMP AT 30 VDC HIGHLY SENSITIVE, TTL HIGHLY SENSITIVE, 112 DIRECT DRIVE POSSIBLE, V. COIL RES. 220 OHM

1 3/16" = 13/32" = 7/16" AROMAT # RSD-6V \$1.50 EACH 10 FOR \$13.50

## 13 VDC RELAY

CONTACT: S.P.N.C. 10 AMP @ 120 VAC ENERGIZE COIL TO

14 pin style 3 amp contacts 24 volt d.c. or 120 volt a.c. coil \$1.70 EACH



COIL: 13 VDC 650 OHMS SPECIAL PRICE \$1.00 EACH

#### 4 PDT RELAY

SOCKETS FOR RELAY SOS each

Used but fully lested



## CLAMPS TO FIT CAPACITORS 504 as

S.P.D.T. (on-on) P.C STYLE. NON-THREADED BUSHING

754 EACH 10 FOR \$7.00 S.P.D.T. (on-off-on)

#### (on-on) SOLDER LUG TERMINALS \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00

\$1.00

\$2.50

\$3.00

\$2.50

\$3.50

\$1.50

S.P.D.T. (on-on) P.C. LUGS. \$1.00 EACH 10 FOR \$9.00 100 FOR \$40.00

#### 2 FOR \$1.50 **MINIATURE TOGGLE SWITCHES** ALL ARE RATED 5 AMPS @ 125 VAC SPDT

(on-off-on) SOLDER LUG TERMINALS. \$1.00 EACH 10 FOR \$9.00 100 FOR \$80.00

DPDT (on-on)



## SOLID STATE

MOUNTING CENTERS



#### \$1.00 EACH 10 FDR \$9.00 QUANTITIES LIMITED VISA

MINIMUM ORDER \$10.00 USA: \$2.50 SHIPPING FOREIGN ORDERS: INCLUDE SUFFICIENT SHIPPING CALIF. RES. ADD 6 1/2% NO C.O.D.!



THREE WIRE

### \$2.00 EACH SOLDERING

## KEY

ASSEMBLY

CONTAINS 5 SINGLE-POLE

6 KEY

\$1,25 EACH





TOLL FREE ORDERS ONLY 1-800-826-5432 (ORDER ONLY)

ALASKA, HAWAII,

OR INFORMATION (213) 380-8000

(IN CALIFORNIA: 1-800-258-6666)

POWER SUPPLY W/ PRE-AMP THIS SUPPLY WAS USED TO POWER AN 8 TRACK/CASSETTE UNIT IT VILL SUPPLY APPROX. 18 VDC AND INCLUDES A SMALL PRE-AMP TO BOOST SIGNAL LEVEL

## RCA PLUGS FOR LINE IN/OUT \$4.50 EACH

LOCATION

P.C. STYLE 75¢ EACH 10 FOR \$7 00 層

> 6228 SEPULVEDA BLVD. VAN NUYS, CA 91411

905 S. VERMONT AVE. P.O. BOX 20406 LOS ANGELES, CA 90006

### 95

WALKMAN style headphones \$7.00. Plezo super tweeter, 40,000 Hz \$8.00. JAMES FIGIELSKI, PO Box 42, Florham Park, NJ 07932. No checks.

DESCAMBLERS for downconverters. High gain. Send \$2.00. RB ELECTRONICS, PO Box 643, Kalamazoo, MI 49005.

CABLE- TV converters, Zenith, Scientific Atlanta, Jerrold, Oak, others available. Fast service, UNITED ELECTRONICS SUPPLY, PO Box 1206, Elgin, IL 60121. (312) 697-0600.

PCB for Satellite Stereo Project in October article is now only \$15.00. JIM RHODES, INC., 1025 Ransome Lane, Kingsport, TN 37660.

"SATELLITE descramblers"—lowest prices anywhere! Dealer inquiries welcome. Send \$3.00 for catalog. We ship C.O.D.s, STARVIEW INC., PO Box 103, Rexford, NY 12148, (518) 785-1288.

AUTOMATIC telephone dialing, programming unit, solid-state, auto-reset, drives cheap recorder, cassette tapes, monitors refrigeration etc. Alarm control module, patch cords, instructions, warranty, \$39.95. HAROLD DAVIS, (601) 366-4112.

CONVERT overseas videotapes PAL/SECAM to American system, viceversa. Optical/digital, lowest rates. 110-220 audlo, video, TV's. Copying machines discounted. APPLE AUDIO, 74-18, 37th Avenue, Queens, NY 11372, (718) 507-5800.

SAMS Photofacts, old radios, television, combos, \$2.00 each, \$10.00 set. SEASAW, 575 East Tremont, Bronx, NY 10457

This ad is set with a background screen. Notice how it stands out on the page: It incurs a 25% premium charge. Perhaps your next ad could have a screen background. For more information, see top of Market Center listing. CABLE-TV products. Jerrold, Hamlin, and Oak converters. Send \$3,00 for information. ADDITIONAL OUTLET CORP., 1041 W. Commercial Blvd., Ft. Lauderdale, FL 33309.

ZENTIH SSAVI Manual. Original manual used by technicians. Theory of scrambling, schematics, parts list, repair. For UHF and cable. For speedy delivery send \$15.00 cash or money order. BAY STATE ELECTRONICS, PO Box 263, Accord, MA 02018.

INTEL model No. MDS225, Intel Dual Disk Drive model No. MDS720, Intel Universal Prom Programmer model No. UPP103. Equipment in excellent condition. Call Ted Belben, (416) 832-2241, EIRICH MACHINES LTD., PO Box 550, Maple, Ontario, Canada LOJ 1E0

TOKO coils and printed circuits. Quantity discounts. JIM RHODES, INC., 1025 Ransome Lane, Kingsport, TN 37660.

ELECTRONIC catalog. Over 4,500 items. Parts & components. Everything needed by the hobbyist or technician. \$2.00 postage & handling (United States only), refundable with first \$15.00 order. **T & M ELECTRONICS**, 472 East Main Street, Patchogue, NY 11772, (516) 289-2520.

OPTICAL character reader input any computer. Construction cost \$75.00. Plans \$29.95. 50 page catalog \$3.00. DBE, Box G, Waikiki, HI 96815, MC/ VISA orders (808) 395-7458.

RECONDITIONED test equipment. \$1.00 for catalog. JAMES WALTER TEST EQUIPMENT, 2697 Nickel, San Pablo, CA 94806.

CABLE-TV converters, police radar detectors and scanners. Send \$1.00 for catalog. GREAT LAKES COMMUNICATIONS, INC., 0-2026 Chicago Dr. Jenison, Mi 49428

IMPORTS—car stereos, boosters, speakers, tools, jewelry. List \$1.00 (refundable). J.R.C. IMPORTS, 329-76th, N. Bergen, NJ 07047.

## CB MODIFICATIONS

Increase channels, range, privacy! We specialize in frequency expanders, speech processors, FM converters, PLL & slider tricks, how-to books, plans, kits. Expert mail-in repairs & conversions. 16-page catalog \$2.

CBC INTERNATIONAL, P.O. BOX 31500RE, PHOENIX, AZ 85046 (602) 996-8700

#### **TIMEX/SINCLAIR 1000**

TS-1000 2K software. Personal finance, educational, robotics, business, \$9.99 each. Postpaid. Guaranteed. Visa/MasterCard. Free information. STURDIVANT LABORATORIES, Box 116RE, Bedford, MI 49020.

This is an expanded type ad. Notice the Increased visibility. Yes, you'll pay a premium for this kind of ad. But it will help your ad stand out from the rest. For ordering information, see top of Market Center listing.

#### APPLE SOFTWARE

ELECTRONICS made easy for Apple II users with Mentor, the proven theoretical circuit design package. Excellent learning aid too. \$174.95, KORSMEYER ELECTRONIC DESIGN, INC., 5701 Prescott, Lincoln, NE 68506, (402) 483-2238.

#### **ENJOY SATELLITE TV**

Save money with easy, guaranteed, do-lt-yourself antenna plans / kits. Electronic knowledge not necessary. Send \$1.00 for catalog or \$8.95 for 1984 "Consumer Guide to Satellite Television."



Box 9108 Missoula, MT 59807



## 

 8020B
 \$170

 8021B
 \$139

 8022B
 \$125

 8024B
 \$217

 8026B
 \$174

4 1/2 DIGIT DMM

8060A \$305 8062A \$244

DIGITAL COUNTERS

1900A (80MHz)......\$345 1911A (250 MHz)......\$501 1910A (125MHz)......\$414 1912A (520MHz)......\$632

ALL ACCESSORIES FOR ABOVE UNITS IN STOCK AND READY FOR SAME-DAY SHIPMENT

**WM. B. ALLEN SUPPLY** 

300 BLOCK NORTH RAMPART, NEW ORLEANS, LA 70112

LOUISIANA TOLL FREE 800 462-9520

COMPLETE INVENTORY OF MULTIMETERS AND SCOPES FROM 18 MANUFACTURERS

800 535-9593

96

# DIGI-KEY

# 1-800-344-4539

QUALITY -Name brand products from nationally recognized manufacturers SERVICE - Computerized order processing and inventory control SAVINGS — Volume Discounts · OEM Quantity Pricing · Toll Free 800 Number Cat. No P6200 K ONLY NEW'KIT \*3595 15495 SOLDER TAIL DIP SOCKETS Vehicle 100 Period 100 MPO TYPE 19 1 15 1,45 1 60 2 10 2 25 2 50 2 50 4 20 #2011 | P2019 8 94 9 90 11 31 14 80 17 12 26 56 12 14 60 15 14 1 (8) 1 15 1 19 1 36 1 70 2 06 2 07 2 19 4 21 7 46 10 01 13 43 d 1 08 1 08 1 15 1 22 1 36 1 70 1 90 1 90 1 42 4 62 7 06 0 7 1 7 , NC3401 , NC3401 , NC3401 , NC3411 , NC3411 , NC3411 , NC3411 18 3 60 4 90 5 60 8 70 7 50 8 20 8 30 10 30 12 30 -13 13 14 19 31 23 24 40 52 66 92 196 57 00 37 0 83 00 97 00 117 00 127 00 137 00 167 00 \$5495 ### 100 | 100 | 100 | 100 | 10 HILLI AAAAAA 101 0 0 1 133 Per No. Bilder Tax CS 10 CS 10 CS 15 CS 17 CS 18 CS 20 CS 22 CS 25 CS 25 CS 30 CS 31 CS 35 CS 40 CS 40 CS 40 CS 40 CS 50 7 95 3 40 3 60 3 56 3 90 4 20 4 50 4 95 5 20 5 80 6 30 6 80 7 80 7 40 Capacity 12

Turning 12

Turni C3-10 C3-10 C3-10 C3-10 C3-20 2 95 3 40 3 70 3 95 4 20 4 95 5 25 8 10 6 10 6 56 7 40 7 90 15 17 57 12 215 00 806 40 15 12 57 12 215 00 806 40 SILICON RECTIFIERS 24 38 24 36 24 36 24 36 24 00 41 00 41 00 41 00 41 00 41 00 41 80 80 80 80 80 80 100 150 80 788 7 00 7 00 7 90 7 90 8 00 8 00 12 00 9 00 60 00 80 88 64 00 88 00 74 88 80 00 100 00 32 00 3 AMP SILICON RECTIFIER MOUNTING HARDWARE AVAILABLE \*3595

## Radio Shaek Parts Place

Over 1000 Items in Stock! The Store for Builders and Fixers Since 1921.

■ Wide Selection

**■ First Quality** 

■ No Waiting

### Save Money, Install Your **Own Phones**

Easy-to-Understand "How-to" Manual

Illustrated 150-page manual gives you step-by-step instructions for installing telephones, automatic dialers, answerers, ringers and wiring. Plus into on single and multi-line business systems. 5.95 62-1390



### 4000-Series **CMOS ICS**

With Pin-Out and Specs

Туре	Cat. No.	Each
4001	276-2401	.99
4011	276-2411	.99
4013	276-2413	1.19
4017	276-2417	1.49
4049	276-2449	1.19
4066	276-2466	1.19

## 1/4-Watt. 5% Resistors

Pkg. of 5 390

Ohms	Cat. No.
10	271-1301
100	°271-1311
150	271-1312
220	271-1313
270	271-1314
330	271-1315
470	271-1317
1k	271-1321
1.8k	271-1324
2.2k	271-1325
3.3k	271-1328
4.7k	271-1330
6.8k	271-1333

Ohms	Cat. No.
10k	271-1335
15k	271-1337
22k	271-1339
27k	271-1340
33k	271-1341
47k	271-1342
68k	271-1345
100k	271-1347
220k	271-1350
470k	271-1354
1 meg	271-1356
10 meg	271-1365

### **Communications ICs**

With Pin-Out **And Data** 



	Туре	Cat. No.	Each
XR 2206	AFSK Generator	276-2336	5.95
XR 2211	AFSK Decoder	276-2337	5.95
ICL8038	Function Generator	276-2334	5.95
LM565	Phase Locked Loop	276-1720	1.99
MC1488	Quad Line Driver	276-2520	1.79
MC1489	Quad Line Receiver	276-2521	1.79

## **TTL Digital ICs**

With Pin-Out and Specs

Type	Cat. No.	Each
7400	276-1801	.89
7404	276-1802	.99
7408	276-1822	1.29
7447	276-1805	1.59
7490	276-1808	1.09

#### Replacement **Transistors**



With Pin-Out and Data

Туре		Cat. No.	Each
2N1305	PNP	276-2007	1.19
MPS2222A	NPN	276-2009	.79
PN2484	NPN	276-2010	.89
MPS3904	NPN	276-2016	.69
TIP31	NPN	276-2017	.99
TIP3055	NPN	276-2020	1.59
MPS2907	PNP	276-2023	.79
MJE34	PNP	276-2027	1.49
2N3053	NPN	276-2030	.99
MPS3638	PNP	276-2032	.79
TIP120 2N3055 MJ2955 2N4401 MPSA06	NPN NPN PNP NPN NPN	276-2068 276-2041 276-2043 276-2058 276-2059	1.29 1.99 2.19 59
MPSA13	NPN	276-2060	.59
MPSA42	NPN	276-2061	.69
2SC945	NPN	276-2051	.79
2N3819	N-FET	276-2035	.99
MPF102	N-FET	276-2062	.99
IRF511	V-FET	276-2072	2.59
IRFD1Z3	V-FET	276-2073	1.49
2SC1308	NPN	276-2055	7.95

## **Computer / Game Connectors**

Type	Positions	Cat. No.	Each
Solder Sub-D Male	9	276-1537	1.99
Solder Sub-D Female	9	276-1538	2.49
Hood for Above	9	276-1539	1.99
Solder Sub-D Male	15	276-1527	2.49
Solder Sub-D Female	15	276-1528	3.49
Hood for Above	15	276-1529	1.99
Solder Sub-D Male	25	276-1547	2.99
Solder Sub-D Female	25	276-1548	3.99
Hood for Above	25	276-1549	1.99
Solderless Sub-D Male	25	276-1559	4.99
Solderless Sub-D Fem.	25	276-1565	4.99
Printer Connector	36	276-1534	6.99
Cable Socket	34	276-1525	3.19
Disk Drive Connector	34	276-1564	4.95

Voice Synthesizer IC

SPO256-AL2. MOS LSI, Uses a program stored in its built-in ROM to synthesize any English word.

Requires low-cost support components and host computer. Easy to interface. Requires 3.12 MHz

## Operational **Amplifiers**

Туре		Cat. No.	Each
741	(Single)	276-007	.89
MC1458	(Dual)	276-038	.99
LM324	(Quad)	276-1711	1.29
TL082	(Dual)	276-1715	1.89
TL084	(Quad)	276-1714	2.99
LM3900	(Quad)	276-1713	1.39
LM339	(Quad)	276-1712	1.49
TLC271	(Single)	276-1748	1.59
TLC272	(Dual)	276-1749	2.19
TLC274	(Quad)	276-1750	2.99

## **Voltage Regulators**



Type	Adjustable	Cat. No.	Each
LM723	0 to 40 VDC	276-1740	.99
LM317T	1.2 to 37 VDC	276-1778	2.79

			_
Type	Fixed Output	Cat. No.	Each
7805	+5 VDC	276-1770	1.59
7812	+ 12 VDC	276-1771	1.59
7815	+ 15 VDC	276-1772	1.59
7905	- 5 VDC	276-1773	1.59
7912	- 12 VDC	276-1774	1.59

### Compact SPST **Reed Relays**

Only 149 Each



Perfect for use when space is limited. Approx. 1 x 5/16". Pins for PC mounting. Contacts rated 1 1.49 12 VDC Coll. 275-233 1.49

#### Fold-Up 25-Range Multitester

- Detented Hinge With 4 "Stops"
- Easy-to-Read 4"



"Big meter" features at a "little meter" price! Fused, surge-absorber protected. Shunt protection of meter movement when shut. With leads, manual. Open: 71/4 x 45/16 x 11/4" Battery extra. 22-211

## **Digital Logic Probe**



#### Simultaneous Tone Output For Faster Testing

The quick way to "peek inside" TTL, LS and CMOS digital circults. Colorcoded LEDs indicate high, low or pulsed logic states. Simultaneous tone output. Overload and polarity protected. 22-302 19.95

## Regulated DC Supply



Breaker **Protected** 

#### Converts 120 VAC to 12 VDC

Ideal test bench power source for autosound, CBs, ham rigs and more. Produces 13.8 VDC at 2.5 amps continuous load. 5 A surge. Rugged metal cabinet, 21/2 x 41/2 x 63/4". U.L. 34.95 listed. 22-124

#### Compact 16-Range Digital Multimeter



Single-IC Design For Low Battery **Drain and High** Accuracy

4995

High-contrast LC display for precise readings at a glance. Fused, overload protected. Diode/semi junction test and many other features. 53/16 × 31/4 × 17/16". With leads, manual. 22-189

#### **PLANS AND KITS**

PRINTED-circuit boards. Quick prototypes, production, design, reflow solder. Send print or description for quote to KIT CIRCUITS, Box 235, Clawson, MI 48017.

FREE catalog, 99 cent kits—audio, video, TV, computer parts. ALLKIT, 434 West 4th Street, West Islip, NY 11795.

HI-FI speaker kits, auto speaker systems and speaker components from the world's finest manufacturers. For beginners and experts. Free literature. A & SPEAKERS, Box 7462R, Denver, CO 80207 (303) 399-8609.

CABLE-TV converters: Jerrold, Hamlin, SB-3, AN-3, Mini-Code, Zenith & more. UHF converters: Deluxe II sinewave kits \$95.00, gated pulse add/on \$70.00. Complete units \$195.00, with gated pulse \$255.00. (Quantity discounts.) Repairs of all converters & cable boxes. Send S.A.S.E. (54 cents postage) or call for info. 1 (312) 637-4408. HIGGINS ELECTRONICS, 6014 W. Nelson, Chicago, IL 60634. No Illinois orders accepted.

PROJECTION TV...Convert your TV to project 7 foot picture...Results comparable to \$2,500.00 projectors...Total cost less than \$30.00...Plans and 8" less \$19.95...Illustrated information free. MAC-ROCOMA-GE, Washington Crossing, PA 18977. Creditcard orders 24 hours, (215) 736-3979.

CATALOG: Hobby, radio broadcasting, CB, lowfers. Transmitters, linears, active antennas, converters, scramblers, bugging devices, more! PANAXIS, Box 130-F1, Paradise, CA 95969.

DESCRAMBLER kits repaired for February's issue \$24.00 parts & labor, \$2.50 S&H, for details send \$1.00 (offer void in Massachusetts.) 6-8 weeks returns, NORTH EASTON ELECTRONICS. PO Box 534, North Easton, MA 02356.

**DIGITAL** Klock Kit plays 1-of-12 melodies each quarter hour. Displays time, date, and other features. Send \$2.50 for assembly plans and pricing to **KERBER KLOCK KO.**, 36117 Hillcrest, Eastlake, OH 44094.

QUALITY printed-circuit boards. 15 cents sq-in. Free drilling. Quantity discounts. INTERNATIONAL ENTERPRISE, 6452 Hazel Circle. Simi Valley, CA 93063.

DESCRAMBLER plans. New design decodes gated sync suppressed signals—newest pilotless method. Circuit boards, most parts from Radio Shack. Detailed theory, drawings, schematics, instructions \$14.95 plus \$2.00 shipping. DIRIJO CORP., Box 212, Lowell, NC 28098.

CHRISTMAS Sale—Improve TV reception! 25dB UHF preamp kit \$22.95. 24dB VHF/UHF/FM assembled amplifier \$29.95. A must for stablizing descrambler units. FV-3, FV-4, FV-5, Super-Z kit repair \$99.95 plus \$5.50 shipping. HOWARD RESEARCH AND DESIGN, Box 204, Ellicott City, MD 21043, (301) 465-8116.





THE ELECTRONIC COMPONENTS PEOPLE

#### QUALITY PARTS, NOT MAIL ORDER SURPLUS

	DIODES	1	DIP
ACTIVE PART NO.	DESCRIPTION	PRICE	ACTIVE PART NO.
01160	1N914B	25/ .50	22071
01165	1N4148	25/ .50	22072
01024	1N4003	10/ .50	22073
01027	1N4004	10/ .50	22074
		101 .30	22075
01156	1N751A	6/ .49	22076
01101	1N4744A	5/ .35	22077

		IP SWITCHES	1	
	ACTIVE PART NO.	POSITION	PRICE	
	22071	4	.99	
	22072	5	1.09	
	22073	6	1.09	
	22074	7	1.09	
	22075	8	1.09	
ľ	22076	9	1.19	
	22077	10	1.29	

Did you r our new catalog?	198	
NAME		,
ADDRESS		
CITY		
STATE	ZIP	CODE

T	RANSISTORS	
ACTIVE PART NO.	DESCRIPTION	PRICE
02165	2N2222A	3/ .96
02193	2N2907A	3/ .96
02224	2N5401	5/ .80
02086	2N5550	5/ .80
44070	MPSA13	3/ .66
44013	MPSA42	3/ .72
44073	MPSA92	4/ .88
44077	PN2222A	3/ .66
44078	PN2907A	3/ .68

MICROPROCESSORS									
	ACTIVE PART NO		PRICE						
	12001	5502	4.75						
	12005	5522	6.95						
	12010	5551	10.85						
	12014	6802	7.50						
	12021	5850	3.20						
	12023	8085APC	9.95						
	12038	8284APC	9.89						
	12053	8088DC	26.80						
ı	41002	Z80A-CPU	2.59						
	41001	Z80-CPU	2.28						

		IC SOCKETS	
	ACTIVE PART NO	DESCRIPTION	PRICE
	23085	8 pins	8/ 1.10
ě	23086	14 pins	7/ 1.10
j	23087	16 pins	6/ 1.10
ì	23084	18 pins	6/ 1.30
	23088	20 pins	5/ 1.19
1	23069	22 pins	5/ 1.42
ı	23090	24 pins	4/ 1.19
A	23091	28 pins	4/ 1.30
	23092	40 pins	3/ 1.42

#### Mail orders shipped within 48 hours STORES OPEN AT 8:00 am

ACTIVE PART NO.	DESCRIPTION							
	PRO	OM's						
71017	32 x 8-TS-1	BPC 16 pin	2.7					
71004	256 x 4-TS-1	256 x 4-TS-16PC 16 pin						
71020	512 x 8-TS-20PC 24 pin							
	EPR	OM's						
48021	C2532-45 (4K x 8)	450ns, T.I. pino	ut 5,9!					
48014	C2516-45 (2K x 8) 4	50ns, Intel pine	out 5.2					
	DYNAMI	C RAM's						
48011	P4164-15 64K	(64Kx1) 150ns	5.65					
48037	P4116-15 16K 150ns							
48010	P4118-20 1	16K 200ns	1.49					
	STATIC	RAM's	'Low Powe					
46002	P2114-20	(1K x 4) 200ns	1,99					
48003	P2114-20L*	(1K x 4) 200ns	2.9					
48005	P2016-15	(2K x 8) 150ns	5.9					
48049	P5101-45L*	(256 x 4) 450ns	4,50					
48008	P6116-15L* (2K x 8) 150ns							
	FA	NS						
52001	115VAC 27CF	M.15MA 12W	22.89					
52003	115VAC 100CFM .24A 18W							
52005	115VAC 110C	FM .28A 18W	27.51					
	ОРТОСО	JPLERS						
13184	4N3		.74					
13067	4N2		2/ 1.25					
13193	MCT	2E	2/ 1.10					

ACTIVE PART NO.	DESCRIPTION	PRICE
	CRYSTALS	
68001	1.0000MHZ-HC33	3.70
60003	1.8432MHZ-HC33	3.10
8008	3.579545MHZ-HC18	2.60
68011	4,000MHZ-HC18	2.15
68020	5.0000MHZ-HC18	2.25
68021	6.0000MHZ-HC18	2.39
68023	8,0000MHZ-HC18	2.19
	LED's	
1 3056 (LED220)	T-1-3/4 Red 5mm	7/ .85
13045 (LED222)	T-1-3/4 Green 5mm	10/ 1.45
13046 (LED224)	T-1-3/4 Yellow 5mm	5/ .75
13269 (LED209A)	T-1 Red 3mm	50/ 6.99
	LED DISPLAYS	
13120	MAN6710 double digit .5" Red	2.45
13272	MAN72A single digit .3" Red	1.10
13103	TIL311 hexadec. logic display	8.25
	UART's	
49001	AY3-1015D 0-25K Baud	4.89
49005	AY5-1013A 0-40K Baud	3.24
	PCB ETCHANTS	
	n Persulphate Crystals nt/1 litre. Active No. 69028	3.59
Ferric Chil     Vields: 1 au	oride art/1 litre, Active No. 69012	3.89

#### ORDERING INFORMATION

Use only Active part no's when ordering, Items must be ordered in exact multiples shown using our Active part no. Sample: Our PIN: 13056 (LED220) 7/8.85 If you require 12 pcs. of LED220 order: 2 pc. of no. 13056 @ \$.85 sa. equals 14 pcs. LED220

MAIL ORDER: (U.S.) P.O. Box 9100 Westborough, Mass. 01581 Toll Free 1-800-343-0874 (outside Mass. only)

(outside Mass. only) MAIL ORDER: (Canada) Toll Free 1-800-361-5884 STORE LOCATIONS

Westborough (617) 366-9684

Seattle (206) 881-8191 NEW!!

AND T-ELEMENT

12 db GAIN

\$8.95 EA. 4 OR MORE 17.95 EA

46 CHANNEL VHF TO UHF CATY/VCR CHANNEL CONVERTER With Built In Amplifier and Fine Tuning

Standard UHF channels

\* Designed to anhance VCR units end cable add one.

\* Convenient line tuning control permits adjushment without special tools or screedivers

\* Built in Amplifier for UHF gain of \* 5 to 8 db.

\* Channel conversion chart on top of unit

\* Easy hookup and excellent performance

GMI Model 3840 Our Price \*32.95 ea. 2 or more \*28.95 ea.

SANYO UHF VARACTOR TUNERS 75 Ohm Input - 45 MHz Output For Channels 14 - 83

Now! 816.95 EACH

> Call for Quantity Price 1000



1

Model 1045 TELEPHONE PRODUCT TESTER

1329.95

Brand New Hitachi NICAD BATTERIES

ISOATIP

WAHL SOLDERING IRONS

ODEL 7470 merature Adjustable Station

139.95 ea.

MODEL 7700
"Quick Charge"
Iso-Tip Cordless
Soldering Iron
Recharges companies

129.95 ₩

\*39.95

MODEL 7800 Iso-Tip "80" Cord-less Soldering Iron Fastest replanging cor-less soldering iron on the market. Same as

\$1,49 1,59 3,50 1,49 1,69 2,29 2,08 1,75 2,60 1,75 3,19 \$1,49 1,10 2,86 90 96 1,59 1,56 1,19 2,09 1,84 2,30 59 1,34 1,95



ON SALE \$24.95

Phone A Tenna EXTENDS CORDLESS TELEPHONE RANGE UP TO 3 TIMES!

& Introductors

\$37.95

SUPER SALE

NEW!

Model SC-34

AB SWITCH ELIMINATOR

SIGNAL COMBINER

with Switchable Chan, 3 or 4 insertion Permits STV, MDS, Satellitie of VCR signal Insertion into existing

Our Price \$14.95 ea.

PREMIUM QUALITY 75 OHM COAXIAL CABLE RG59/U TYPE

ORDER NOW TOLL FREE 800-854-4655 OUTSIDE CALIFORNIA 714-635-5090

By the 1000 ft roll \$64.95 ...

SURPLUS SYLVANIA

WHF VARACTOR TUNERS
45 MHz output, Channels 2
through 13 as well as the mid-band channels. Hookup data
included.

5.335

1N4001 DIODES 15 for \$1.00....100 for \$5.00

GEN. INSTRUMENT LCC58 58 CHAN. CATV CONVERTER

199.95

WHILE THEY LAST! 113.95 an

CLOSED SUN & MO MAJE CALIFORNIA MOST ORDERS SHIPPED WITHIN 24 HOURS — NO MINIMUM ORDER ALL PREPAID ORDERS 2 LBS OR LESS MUST INCLUDE \$2.50 SHIPPING & HAMPLING — SHIPPED SAME DAY RECEIVED

CIRCLE 121 ON FREE INFORMATION CARD

# **DON'T** BLAMETHE

Our Isolators eliminate equipment interaction, clean up interference, curb damaging power line spikes and

lightning bursts.



#### **ISO-1 ISOLATOR**

3 isolated sockets; quality spike suppression; basic protection. . \$81.95

#### **ISO-3 SUPER-ISOLATOR**

3 dual isolated sockets; suppressor; commercial protection. . . . . 8122.95

#### ISO-17 MAGNUM ISOLATOR

4 quad isolated sockets; suppressor, laboratory grade protection. . \$213.95

Electronic Specialists, Inc.

171 S. Main, Natick, MA 01780 (617) 855-1532

Toll Free Order Desk 1-800-225-4878 MasterCard, VISA, American Express

## HIGH QUALITY #75dB GAIN

Varible from 1.9 to 2.5 GHz



The latest advance in microwave technology with a SNOW-FREE PICTURE.

Two Models to choose from.

Both Models Include:

- 20" Parabolic Dish Pre-assembled Probe with Down Converter
- Power Supply and Coax Switch
- 60' of RG-59/U Coax with Connector Transformer for 75 to 300 Ohms
- All Mounting Hardware for Fast and Easy Installation


20" Fiberglass Dish Up to 55dB Gain Special \$9895

20" Aluminum Dish Up to 55dB Gain Low Priced \$9895

Add 10% for Foreign orders or U.S. Parcel Post

High Gain Yagi Antenna with Down Converter and \$8995 Power Supply. Complete System, Ready to Use.

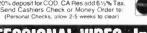Send \$2.00 for Catalog, Refundable with first purchase Available thru Mail and Phone Orders Only 20% deposit for COO. CA Res add 61% Tax. Send Cashiers Check or Money Order to: (Personal Checks, allow 2.5 weeks to clear)



# PROFESSIONAL VIDEO, Inc. 4670 Hollywood Blvd., Hollywood, Calif. 90027

For C.O.D. Orders Call (213) 219-0227

CIRCLE 119 ON FREE INFORMATION CARD

CONTROL your world with your computer! Control up to 48 devices easily. Complete plans, schematics, programs \$9.95. B & W ELECTRONICS, 3621 Lowden, Kalamazoo, MI 49008

FREE: 44 page parts catalog available from HOSFELT ELECTRONICS, 2610 Sunset Blvd., Steubenville, OH 43952.

FUNCTION GENERATOR KIT \$59.9 Auto-Ranging Cap-meter kit \$79.95

Phone 209-772-2076

Write or Phone for FREE CATALOG

EXPERI-MENTER'S EQUIP

DAGE SCIENTIFIC INSTRUMENTS
BOX 144 VALLEY SPRINGS CA 95252

APPLE II + compatible cards: Z80 \$39.95, disk controller \$35.95, EPROM programmer \$49.95, RS-232C \$42.95, 16K-RAM \$34.95, 5 amp power supply \$39.95, R.F. modulator \$5,95. Great prices on I.B.M. items too! Free listing. 3 month warranty. KOMPUTECH, Box 597, Alexandria Bay, NY 13607.

DESCRAMBLE cable/over-the-air programs—kits \$97.95—plans \$9.95—details \$1.00—MINUTE, Box 531, Westchester Station, Bronx, NY 10461

TIMEX SInclair Brother EP20 interface plans and software listing. \$10.00 U.S., Michigan res. 4% tax, \$1.00 S.& H., check or M.O.. OROSZ, 1604 Pagel, Lincoln Park, MI 48146.

GET more spatial realism with these kits. The KIR-1 at \$97.00 expands stereo sound to fill your room. The KVSP-1 at \$95.00 creates full stereo from mono and patches your TV to your audio system. Plans alone \$1.00 each. Prices include UPS to 48 states. Send check, Visa or M.C. to SOUND CONCEPTS, 2014 155. Problem MA 03146. Box 135, Brookline, MA 02146.

PROJECT your TV to wallsize image for \$19.95. "Guaranteed". Details, VIDEOQUEST, Box 231Z, Glenview, IL 60025.

COMMODORE 64 numeric keypad for use with MLX and numeric data entry. Plans and software \$4.00—complete kit of parts \$24.00, ck or M.O. SYNTRONICS, 2324 Dennywood Dr., Nashville, TN 37214

**ELECTRONIC** kits: Polyphonic digital synthesizer, digital sound sampler and accessories. Build a professional system at low cost. The VMS synthesizer system is compatible with most microcomputers, (Apple, Commodore, Sinclair, etc...) Complete soft-ware packages available for the Commodore 64. Imported from West Germany. Send \$5.00 for bro-chure and demo-cassette. Mail to: CEDOS ELEC-TRONICS, PO Box 101, Waukesha, WI 53187

#### SINE WAVE QUESTIONS?

TROUBLE shooting, alignment, antenna hookup, improvements manual, \$6.00. STV authorization control, \$3.00. Both, \$8.00. SIGNAL, Box 2512-R, Culver City, CA 90231.

#### GRAPHIC EQUALIZERS, ETC.

NOISE eliminators, expanders, power meters, others. Twelve-24 bands/channel equalizers from \$89.00 Kit see R-E 5-6/78, 2/80, 3-4/81. Catalog: SSS, 856R Lynnrose, Santa Rosa, CA 95404. (707) 546-3895.

#### CABLE TV

DEALERS wanted: Channel 2, 3, and 4 notch filters. Money back guarantee. Send \$15.00 for sample and quantity price list. Specify channel(s). LEE KURTZ, PO Box 291394, Davie, FL 33329.

#### CABLE CONVERTERS & DESCRAMBLERS HAMLIN OAK JERROLD SCIENTIFIC SYLVANIA ZENITH

ALL TYPES OF CABLE TV EQUIPMENT
MICROWAVE ANTENNAS & ACCESSORIES
— FREE ILLUSTRATED BROCHURE
— CALL OR WRITE
H.M.R. SALES



221 E. CAMELBACK # 1 PHOENIX, AZ 85012 (602) 993-0398



# **ECTRONICS**

E HAVE WHAT YOU NEED AT E PRICES YOU WANT!

1-800-762-4315)



#### TENMAR® 31/2 DIGIT LCD MULTIMETER

- DC input impedance 10M ohm Diode and HFE Transistor tests
- Overload protection Auto polarity 2 year limited Warranty



#### TENMAR® **20MHZ DUAL TRACE** OSCILLOSCOPE

Two High Quality 10:1 probes included. Backed by our 2 year limited warranty. For specifications see MCM Catalog #8 page 108.

#72-320



#### TENMAN® COMBINATION DMM **CAPACITANCE METER**

(With Transistor Gain Tester)

- User can easily read Voltage, AC and DC current, resistance up to 20M ohms, capacitance up to 20 microfarad, and HFE on a clear 1/2 inch, 31/2 digit LCD display
- 2 year limited Warranty

#72-045 \$74.95 each



#### LOGIC **PROBE WITH MEMORY**

- Multi-family compatibil-My-DTL/TTL/HTL/CMOSIC
- Detects pulses as short as 50 nanoseconds

#72-190





- Zinc diecast construction
- Power passive ■ 5-900MHZ
- #33-070

(min 10)

OSCILLOSCOPE PROBE KIT



■ Bandwidth: 10:1 position: 100MHZ at—3dB into 20pF

Rise Time: 10:1 position

less than 3.5<sub>NS</sub> nominal ■ Kit contains: 10" earth lead, retractable hook. Ic test tip, insulator, **BNC** adaptor and trimming tool.

#72-010

\$26.95 (1-4)

(5-up)

#### MATCHING TRANSFORMER



■ 75-300 ohm matching transformer

#33-050

■ UHF/VHF/FM



Quick connect matching transformer

#33-010

#### **PUSH ON BALUN**



#### F-59 CONNECTOR



■ Attached ½ ferrule

#33-410

## #33-200

■ 75 ohm ■ UHF/VHF/FM ■ Comes with F-59 connector

3-WAY SPLITTER



■ Replaces VEHS0011 head used in 2-4-6 hour record/playback machines

#32-180

**BE SURE TO** CALL FOR YOUR FREE 120 PAGE CATALOG! **OVER 4,500** ITEMS!!



# COMBINE Tru Spec.

#### CHANNEL COMBINER

■ The 33-255 enables the user to combine a channel 3 output signal from an STV, MDS, VCR or video game device with an existing MATV system containing adjacent channels 2 and 4.

#33-255 \$11.25 (1-9) (10-UP)

#### **DELUXE CORDLESS CABLE CONVERTER** BY JERROLD



- Approved by the F.C.C., UL and C.S.A.
- Wireless hand controller switches channels, turns TV set on and off and even fine tunes the picture
- Compatible with all cable systems
- Jerrold model #LCC-58-3

#32-380

We Also Have...a full line of: test equipment computer accessories, telephone accessories, speakers, television parts, flybacks, yokes, switches, fuses, lamps, capacitors, resistors, cartridges, styll, wire, CATV equipment, and many more. Over 4,500 Items AT THE LOWEST PRICES AROUND!

#### Terms:

VISA

- +\$10 minimum order. \$1.00 charge for orders under \$10
- \$20 minimum charge-card order
   Orders shipped UPS C.O.D
   Most orders shipped within 24 hours
   Sales office open 8:30am to 6.00pm
- Saturdays 10:00am to 3pm, EST





858 East Congress Park Drive Centerville, Ohio 45459 513-434-0031

SOURCE NO.RE-5







The JE232CM allows connection of standard serial RS232 printers, modems, etc. to your VIC-20 and C-64. A 4-pole switch allows the inversion of the 4 control lines. Complete installation and operation instructions included.

Plugs Into User Port · Provides Standard RS232 signal levels · Uses 6 signals (Transmit, Receive, Clear to Send, Request to Send, Data Terminal Ready, Data Set Ready). JE232CM

#### **VOICE SYNTHESIZER** FOR APPLE AND COMMODORE



JE520CM

 Over 250 word vocabulary-affixes allow the termation of more than 500 words • Built-in amplifier, speaker, volume control, and audio jack • Recreates a clear, natural male voice • Plug-in user. ready with documentation and sample software - Case size:  $74^{\circ}L \times 34^{\circ}W \times 1-3/8^{\circ}H$ 

APPLICATIONS	Security Warning     Teaching     Instrumentation	Telecommun     Handicap Aic     Games
Part No.	Description	

For Commodore 64 & VIC-20 \$114.95 For Apple II, It+, and Ile . \$149.95

#### Computer Memory Expansion Kits

#### IBM PC AND PC XT

Most of the popular Memory Boards (e.g., Quadram" Expansion Boards) allow you to add an add't 64K, 128K, 192K or 256K. The IBM64K Kit will populate these boards in 64K byte increments. The Kits simple to install—just insert the 9 - 64K RAM chips in the provided sockless and set the 2 groups of switches. Complete

#### IBM64K (Nine 200ns 64K RAMs)...... \$43.95 COMPAQ . COLUMBIA . EAGLE

IBM64K (Nine 200ns 64K RAMs). . . . . . \$43.95

APPLE //e Averused 80-Column/64K RAM Card Expands memory by 64K to give 128K when used with programs like VisiCalc\*, Fully assembled and tested. JE864...

TRS-80 MODEL 1, 111

Each Kit comes compilete with eight MM5290 (JPD44 f6/4116) 16K

Dynamic RAMs and documentation for conversion. Model 1: 16K
eaulpped with Expansion Interface can be expanded to 48K with
2 Kits. Model III. Can be expanded from 16K to 48K using 2 Kits.
Each Kit will expand compiler by 16K increments. TRS-16K3 200ns (Model III). \$8,95 TRS-16K4 250ns (Model 1). \$6,95

.... \$6.95 TRS-80 MODEL IV

TRS-80 MODEL IV
Easy to install kit comes complete with 8 ea. 4164N-20 (200ns)
64K Dynamic RAMs 8 conversion documentation
TRS-64K-2 (Converts from 16K to 64K). \$38.95
TRS-64K-2PAL (8 ea. 4164 w/Special PAL Chip
to expand from 64K to 128K). \$59.95

#### TRS-80 COLOR AND COLOR II

Easy to Install Kit comes complete with 8 each 4164N-20 (200ns) 64K Dynamic RAMs and documentation for conversion Converts TRS-80 Color Computers with D. E. ET, F and NC circuit boards to 32K. Also converts TRS-80 Color Computer II to 64K. Flex DOS or OS-9 required to utilize Null 64K RAM on all computers.

#### MDUSTRIES Protect Yourself...



#### **DATASHIELD® Surge Protector**

Eliminates voltage spikes and EMI-RFI noise before it can damage your equipment or cause data loss -6 month warranty - Power dissipa-tion (100 microseconds): 1,000,000 watts -6 sockets -6 foot power cord - Normal fine volt-age indicator light - Brown out/black out reset witch Model 100. . . . .

Protect

#### **DATASHIELD®** Back-Up **Power Source**

Provides up to 30 minutes of continuous 120 VAC 60Hz power to your computer system (load dependent) when you have a black out or voltage sag - Six month warranty - Weight (PC200): 24 lbs —(XT300): 37.5 lbs

..

C200 (Output rating: 200 watts). . . . \$299.95 XT300 (Output rating: 300 watts). . . . \$399.95

## HAPPY HOLIDAYS! 🛠



#### Intelligent 300/1200 Baud Telephone Modem with Real Time Clock/Calendar

The ProModem® is a Relt 212A (300/1200 baud) intelligent stand-alone modem · Full featured expandable modem · Standard features include Auto Answer and Auto Dial, Help Commands, Programmable Intelligent Dialing, Touch Tone™ and Pulse Dialing & More · Hayes command set compatible plus an additional extended

Part No.	Description Price
PM1200	RS-232 Stand Alone Unit
PM1200A	Apple II, II+ and I/e Internal Unit
PM1200B	IBM PC and Compatible Internal Unit \$269.95
PM1200BS	IBM PC & Comp. Int. Unit w/ProCom Software \$319.95
MAC PAC	MacIntosh Package
	(Includes PM1200, Cable, & ProCom Software)

#### OPTIONS FOR ProModem 1200

PM-COM         (ProCom Communication Software).         \$79.           Please specify Operating System.         (Options Processor).         \$79.           PMO-16K         (Options Processor Memory — 16K).         \$10.	
PMO-16K (Options Processor Memory — 16K)	95
	95
PMO-32K (Options Processor Memory — 32K)	
PMO-64K (Options Processor Memory — 64K)\$39.	
PM-ALP         (Alphanumeric Display).         \$79.           PM-CC         (Apple lic to PM1200 Cable).         \$29.	
PM-MC (Macintosh to PM1200 Cable)	

#### KEYBOARDS



## Mitsumi 54-Key Unencoded All-Purpose Keyboard

SPST keyswitches • 20 pin ribbon cable connec-ion • Low profile keys • Features; cursor controls control, caps (lock), function, enter and shift keys Color (keycaps); grey • Wt.: 1 lb. • Pinout include KB54.....\$14.95

## 76-Key Serial ASCII Keyboard

- Simple serial interface - SPST mechanical switching - Operates in upper and lower case - Five user function keys; F1-F5 - Stx flager edge card connection - Color (keys): tan - Weight: 2 lbs: - Data incl KB76. . . . . . . . . . . . . \$29.95



## Apple Keyboard and Case for Apple II and II+

- Keyboard: Direct connection with 16-pin ribbon connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connection with 16-pin ribbon connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connection with 16-pin ribbon connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connection with 16-pin ribbon connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connection with 16-pin ribbon connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connection with 16-pin ribbon connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connection with 16-pin ribbon connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connector • 26 special functions • Size: 14%"L x 5%"W x 1%"H

- Keyboard: Direct connector • 26 special functions • 26 s

Description KB-EA1 68-Key Apple Keyboard only.
Expanded Apple Enclosure Case only. **KB-A68** EAEC-1

## POWER SUPPLIES

## TRANSACTION TECHNOLOGY, INC. 5VDC @ 1 AMP Regulated Power Supply

- Output: +5VDC @ 1.0 amp (also +30VDC regulated) - Input: 115VAC, 60 Hz - Two-lone (black/berge) sell-enclosed case - 6 fool, 3-conductor black power cord - Size: 6½°L x 7°W x 2½°H - Weight 3 lbs.

PS51194



Power/Mate Corp. REGULATED POWER SUPPLY · input: 105-125/210-250 VAC at 47-63 Hz · Line regulation:  $\pm 0.05\%$  · Three mounting surfaces · Overvoltage protection · UL recognized · CSA certified

 Pan No.
 Output
 Size
 Weight
 Price

 EMA5/6B
 5V@3A/6V@2.5A
 4%"Lx 4"W x 2%"H
 2 lbs
 \$2.95

 EMA5/6C
 5V@6A/6V@5A
 5%"L x 4%"W x 2%"H
 4 lbs
 \$39.95

### POWER PAC INC. REGULATED POWER SUPPLY

· Perfect for computer systems · Output. +5VDC @ 11 Amps. -5VDC @ 1 Amp. +12VDC @ 2 Amps. -12VDC @ 0.5 Amp and +24VDC @ 3 Amps · Over-voltage protection · Size: 12%L x 6%W x 4%H · Weight: 17 lbs. · Spec incl.

#### 4-CHANNEL SWITCHING POWER SUPPLY

\*-Microprocessor, mini-computer, terminal, medical equipment and process control applications: Input: 90-130/AC, 47-440Hz; Output: 5VDC 6:5A, 5VDC 6:15A, 12VDC 6:15A, 12VDC 6:15A, Liber equilations: \$20 %\* Rippie: 30mV p-p-Load regulations: \$1% - Overcurrent protection: Adj; 5V main output: \$10% - Size 6%1, x 1% W x 4-15/16%1 - Veight: 1% lbs.

FCS-604A. \$69.95



## Switching Power Supply for APPLE II, II+ & IIe™

 Can drive four floppy disk drives and up to eight expansion cards
 Short circuit and overload protection - Fits inside Apple computer
 Fully regulated +5V @ 5A, +12V @ 1.5A, -5V @ .5A, -12V @ .5A · Direct plug-in power cord included · Size: 9% L x 3½ W x 2% H Weight: 2 lbs

KHP4007 (SPS-109). . . .

\$10,00 Minimum Order — U.S. Funds Only California Residents Add 6½ % Sales Tax Shipping — Add 5% plus \$1.50 Insurance Send S.A.S.E. for Monthly Sales Flyer!

Spec Sheets — 30c each Send \$1.00 Postage for your FREE 1985 JAMECO CATALOG Prices Subject to Change



V/SA'

1355 SHOREWAY ROAD, BELMONT, CA 94002 12/84 PHONE ORDERS WELCOME - (415) 592-8097 Telex: 176043

#### Apple Accessories

#### 514" APPLE" Direct Plug-In Compatible Disk Drive and Controller Card



The ADD-514 Disk Drive uses Shugarl SA390 mechanics—143K formatted storage · 35 tracks · Compatible with Apple Controller & ACC-1 Controller · The drive comes complete with connector and cable — Just plug Into your disk controller card · Size · 6"L x 3½" W x 8-9/16"D · Weight: 4½ lbs.

ADD-51	4 (Disk Dri	ve)					\$ 169.95
ACC-1	Controller	Card).					\$ 49.95

#### More Apple Compatible Add-Ons

More	apple compandle Add-Ons
APF-1	(Cooling Fan) \$39.95
KHP4007	(Switching Power Supply) \$59.95
JE614	(Numeric/Aux. Keypad for He) \$59.95
KB-A68	(Keyboard w/Keypad for II & II+) \$79.95
<b>MON-12G</b>	(12" Green Monitor for II,II+, I/e, IIc) \$99.95
JE864	(80 Col. +64K RAM for He) \$99.95
ADD-12	(5%" Half-Height Disk Drive) \$179.95



FD480	(Remex 54" full-ht,) \$129.95	
A551-2	(Panasonic 5¼" half-ht)\$139.95	
M100-2	(Tandon 54" full-ht.) \$159.95	
D55B	(Teac 5%" half-ht.)\$149.95	
A455	(Shugart 5%" half-ht.) \$159.95	
DD100-8	(Siemens 8" full-ht.) \$139.95	
CK-5	(54" Power Cable Kit) \$2.95	
CK-8	(8" Power Cable Kit) \$3.95	

#### **UV-EPROM Eraser**



1 Chip - 15 Minutes

Erases all EPROMa. Erases up to 8 chlps within 21 minutes {1 chip in 15 minutes}. Martians constant exposure distance of one linch. Special conductive loam lince eliminates static build-up. Built-in salety lock to prevent UV exposure. Compact — only 9 00°L x 3.70°W x 2.60°H. Complete with holding tray for 8 chips.

DE-4	UV-EPROM Eraser \$74.95
UVS-11EL	Replacement Bulb \$16.95



#### JE664 EPROM PROGRAMMER 8K to 64K EPROMS - 24 & 28 Pin Packages

OR to 64R EPHOMS — 24 & 28 PIN PACKAGES Compitely Self-Carlinge — Registers in Additional Systems for General Programs and validates EPHOMs - Checks for proporty exceed EPHOMs - EPHOMS - PE222C Compouter Microbiacy Compilers and PAM by report - Compilers and an IRAM by report - Compilers - Com

5-% tigs.

The £664 FPROM Programmer emulates and programs various 6-86 Word EPROMS from bit to 664 RB memory capacity, titts, can be entered rise the £664's retimal 8's 1-8 BB RAM in three says, (1) from a flow 6 FPROM (2) from an external complex in the program (565 RS220'C BS); (3) from the paine keybourd. The £664's RAM in his accessed for emulation purposes.

BS; (3) from the paine keybourd. The £664's RAM in his be accessed for emulation purposes. The flow of the painer keybourd in the programmer amunitation, the £664's RAM in the program content. The £664's RAM in the painer keybourd outside the series to the tild the series of the program content. The £664's RAM ADDRESS in content in the £664's RAM address the first painer in the £664's Ram and the first painer in the £664's Rogarimer includes one £164's Aurignet Moderate to £864's Rogarimer includes one £164's Aurignet Moderate (as kitsed become £164's RAM and the £664's Rogarimer includes one £164's Aurignet Moderate (as kitsed become £164's RAM and £164's Aurignet Moderate (as kitsed become £164's Aurignet Moderate (as kit

JE664-A EPROM Programmer. \$995.00 Assembled & Tested (Includes JM16A Module)

JEBSS — RSS23C INTERFACE OPTION — The RS22C Interface Option movements computer access to the JESSF SAME. This allows the computer to manyouter, size and instanted PRIFOM fails and from the JESSF A sample program failing is supplied in MEMSIC for OPM computers. Documentation is provided to adapt the software to other computers with an RSC22 point 9000 Bable 5 of well-off, only with 7.5 also believed.

#### **EPROM Programmer w/JE665 Option** JE664-ARS. \$1195.00 Assembled & Tested (Includes JM16A Module)

EPROM JUMPER MODULES — The JE664's JUMPER MODULE (Personality Module) is a plug-in Module that pre-sets the JE664's or the proper programming purses to the EPROM and configures the EPROM socket connections for that particular EPROM.

JESH (PRIN) Augus Dal In	6PMILE	Programming Strings	SPRING MOUNTACTURES	PRICE
3MOBA	2708	29/	AME Motorole, Red, Intel. Ti	314.95
A81ML	2716. TNIS2516 (TI)	25V	Intel Motorcia, fast REC, TL AMC, Heachs, Mosays.	. \$14.95
JM158	1MS2716 (3-V si	54, + 54, + 124	Montros, TL	. \$14.95
.9M32A	TMS2532	25V	Motorola, 71, rysechs, OHI	. \$14.9
M328	2732	25V	AMD, Fuetau, MEG, Heach, seel, Missionis, Pational	. 814 9
3M32C	2732A	SIA	Fugliss, 2000	\$14.9
,8854A	MCM58764 MCM68L764	219	Motorala	\$14.90
.64648.	2764	21V	MM, Farchist (I/C	\$14.9
,M64C	TM52564	259	η	\$14.95

7400	74F00	NEW 74ALS00	85	Digitalker™
Part No.   Pins Price   Part No.   Pins Price   Part No.   Pins Price     Part No.   Pins Price     Part No.   Pins Price     Part No.   Pins Price     Part No.   Pins Price     Part No.   Pins Price     Part No.   Pins Price     Part No.   Pins Price     Part No.   Pins Price   Part No.   Pins Price   Part No.   Pins Price     Part No.   Pins Price   Part No.   Part	Part Nr. Plass Function 74F00 14 Oxand 2-Input MANO Nate. 74F00 14 Oxand 2-Input MOR Gate 74F04 14 Merc Insurerier	Priss   Part Na.   Plant Feacher   Priss   P	DT1050 -	Applications: Teaching aids, clocks, automotive, telecommunica-
\$N7402N 14 29 \$N7476N 16 39 \$N74161N 16 56 \$N7403N 14 29 \$N7476N 14 495 \$N74162N 16 56 \$N7404N 14 25 \$N746N 14 89 \$N74162N 16 56	74F06 14 Quad 2-Input AMD Gate. 74F10 14 Inple 3-Input MAMD Gate. 74F32 14 Quad 2-Input OR Gate.	75 74ALS04 14 Hex Investor. 75 74ALS08 14 Quad 2 Input AND Gate 79 74ALS10 14 Troot 3-Input NAMO Gate	tions, language	ge translations, etc. andard DIGITALKER hit encoded with 137 separate
SN7405N 14 .49 SN7482N 14 1.49 SN74164N 14 66 SN7405N 14 59 SN7433N 18 55 SN74165N 18 .66	74674 14 Daal 0 Fig-Flop 7466 14 Quad Exclusive OR Gate 746109 16 Daal Jil Yoshive Edgi-Flip-Flop 744136 16 Expandate 3/8 Occuder 746157 16 Quad 24-lyou Multiplinian	85 74ALS30 14 8 input NAMC Gate 74ALS32 14 Quad 2-input QR Gate 74ALS32 14 Quad 2-input QR Gate 74ALS74 14 Qual Q Flip-Flop	65 words and lones h 79 possible to output	, 2 tones, and 5 different silence durations. The tave been assigned discrete addresses, making it single words or words concatenated into phreses.
\$17409H 14 29 \$17486H 14 39 \$17417H 16 29* \$17409H 14 35 \$117489H 16 225 \$174170H 16 156	74F157 16 Quad 24-put Multipliner (hv.). 74F158 16 Quad 24-put Multipliner (hv.). 74F193 16 4-Bri Up/Down Brazy: Counter 74F240 19 In-State Octal Line Diner (broading).	169 74ALS109 18 Dual JK Pos. Edge Pap-Pap . 169 74ALS138 18 Expandiable 3/8 Discoder. 529 74ALS340 20 In-State Octat Line Driver (invention).	1.25 telligible male voice	i, The "voice" output of the DT1050 is a highly in- ce. Female and children's voices can be synthesiz- y is chosen so that it is applicable to many pro-
SN7411N 14 29 SN7491N 14 79 SN74178N 16 55 SN7412N 14 49 SN7492N 14 45 SN74174N 18 59	74F257 B In-State 3ctal (see United Auritolexer	3.75 3.79 74ALS244 28 In-State Octal Line Driver 3.79 74ALS245 20 Octal Bus. Transceiver (flori line) 4.89 74ALS373 28 In-State Octal Latch	259 ducts and markets 259 The DT1050 consist	
SN7413M 14 39 SN743M 14 .45 SN74175M 16 59 SN7414M 14 .49 SN7494M 14 .89 SN74176M 14 .79 SN7416M 14 .49 SN7495M 14 .49 SN741777M 14 .79		SOR COMPONENT	along with a Mar diagram on the ap	star Word list and a recommended schematic plication sheet.
\$\text{SN7417N}\$ 14 59 \$\text{SN7496N}\$ 18 .49 \$\text{SN7417N}\$ 18 1.49 \$\text{SN747PN}\$ 18 1.49 \$\text{SN7427N}\$ 18 1.49 \$\text{SN742NN}\$ 14 .59 \$\text{SN747ND}\$ 24 1.95 \$\text{SN74181N}\$ 24 1.95	MICROPROCESSOR CHIPS	Proce Part No. Price Francisco	D11000 D1	igitalker™ \$34.95 ea. rocessor Chip \$14.95 ea.
\$M7422N 14 59 \$M74104N 14 1.19 \$M74182N 18 1.05 \$M7412N 16 69 \$M74105N 14 1.19 \$M74184N 18 2.29 \$M7425N 14 39 \$M74105N 18 29 \$M74186N 14 2.29 \$M7416N 14 39 \$M74100N 18 30	0765AC 40 Floppy Disk Convoller 03242 26 Adok Multiplexer & Ridresh Countil TMS5501 40 Synchronius Data Interface (SIRC)	. 19.95 7.95 14.95 1	DT1057 - Expans words. Includes 2	ds the DT1050 vocabulary from 137 to over 260 PRDMs and specs.
SN7427N 14 25 SN74116N 24 1.49 SN7419N 16 69 SN7428N 14 59 SN74121N 14 .45 SN74132N 18 69	Z80. Z80A. Z808. Z8000 SERIES — Z80	4110N-4 18 16,384x1 (250ns) 89	- 8/6 95	S24.95 ea.
\$\text{SN7430N}\$ 14 35 \$\text{SN74125N}\$ 14 69 \$\text{SN74193N}\$ 18 59 \$\text{SN74125N}\$ 14 39 \$\text{SN74125N}\$ 18 55 \$\text{SN74194N}\$ 18 59 \$\text{SN7433N}\$ 14 ,49 \$\text{SN74195N}\$ 14 ,49 \$\text{SN74195N}\$ 14 ,49	Z80-DART 40 Dual Asynchronous Rec_/Irans . Z80-DMA 40 Direct Memory Access Carcuit . Z80-P10 40 Parallel I/O Interface Controller .	8.95 MMS270 18 1024s1 (300nS) 35 12.49 MMS270 18 4096s1 (250ns) MM45270 18 4096s1 (250ns) MM4096 3.49 MM5270 28 4096s1 (250ns) MM4096	495 Part No. Plas	Function Price
SN7437N   14   20   SN74126N   14   29   SN74196N   14   25   SN74136N   14   25   SN74136N   14   25   SN7439N   14   27   SN74136N   14   69   SN74196N   24   1.19	280-510/0 48 Serval MD (BrCB and RxCB Bonded) 280-510/1 49 Serval MD (Lacks OTRB) 280-510/2 49 Serval MD (Lacks SYNcB) 280-510-9 49 Serval MD (Lacks SYNcB)	11.49 MMS2883 16 819241 (200ms) 41256 16 262,14451 (200ms) 11.49 STATIC RAMS	31.95 7045EV/KR 28 7106CPL 40	CMOS Precision Timer         14.95           Stopwatch Chip, XTL (Evaluation Kit)         19.95           3 to Olgal AZD (LCD Drive)         10.49
\$N7440N 14 19 \$N24141N 18 89 \$N74199N 24 1.19 \$N7441N 15 89 \$N74142N 18 3.95 \$N74221N 18 1.19 \$N7442N 15 .45 \$N74143N 28 3.95 \$N74221N 18 1.19	ZBOA 40 CPU (MPCI880N 4) (780C-1) 4MPU; ZBOA-CTU 28 Counter Timer Circuit ZBOA-DART 40 Dual Asyrichronous Rec./Irans	3.49 2101 22 256x4 (450ms) 8101. 4.49 2102 16 1024x1 (350ms) 995 2102-2L 16 1024x1 (250ms) LP (91L02)	89 7106EV/kgl 40 149 7107CPL 40	3% Digit LCD Display for 7106 & 7116 14.95 IC, Circuit Board, Display (Evaluation Kit) 46.95 3% Digit A/D (LED Drive) 18.95
\$\\ \text{SN7445N}  \text{16}  125  \text{SN74146N}  24  3.95  \text{SN744273N}  \text{29}  \text{195}  \text{SN7445N}  \text{16}  \text{126}  \text{SN7415N}  \text{18}  \text{18}  \text{5874279N}  \text{80}  \text{2979N}  \text{18}  \text{79}  \text{5874279N}  \text{18}  \text{79}  \text{79747N}  \text{7974N}   \text{7974N}  \text{7974N}   \text{7974N}    \text{7974N}	ZBOA-DMA	12.95 3.95 2112 11.95 21140 21140 21	- 8/9 95 7116CPL 40 - 8/13.95 72011US	IC, Circuit Board, Display (friedulation Kit) . 46.95 31b Digit A/D LCD Dis. HLD. 18.95 Low Battery Voll Indicator . 2.25
SN7446N   18   75   SN74146N   18   89   SN74283N   18   1.39   SN7447N   10   .75   SN74150N   24   1.49   SN74283N   18   2.05   SN7445N   10   2.05   SN745N   11   2.05   SN7485N   11   2.05	Z80A-S10/2 40 Serial I/O (Lacks SYNCB) Z80A-S10/9 40 Serial I/O Z80B 40 CPU (MICCARDIN-S) (AMPL)	. 11.95 211.00-25, 14 102.4s4 (200ms) LP, 1.69 - 11.95 214.7MB 14 4096x1 (70ms) . 8.95 2148MB 14 102.4s4 (20ms)	- 8/13.49 7205EV/IGE 24 4.49 7206CJPE 16	CMOS LED Stopwatch / Timer         14.95           Stopwatch Chip, XTE, (Evaluation Kit)         16.95           Tone Generator         4.95
SN7454N 14 19 SN74155N 14 49 SN74365N 18 55 SN7459N 14 35 SN74153N 18 99 SN74366N 18 55 SN7466N 14 39 SN74154N 24 1.49 SN74367N 18 55	2808-CTC   29   County Tener Circuit   2808-DART   40   Dual Asyrichronous Rec / Rans   2808-P10   40   Parathel I/O Interface Controller   280018   45   CPU Segmented (10Metz)	11.95 TMSA045 18 1024s4 (450ns) 19.95 TMSA04,47-45 28 1024s4 (450ns) 10.95 5101 22 256s4 (450ns) CMOS 79.95 MMS257 18 6096s1 (450ns) 4044	195 7207AIPD 14 395 7207AEV/RH 14	Tone Generator Chip, XTL (Evaluation Kill) 7:95 Oscillator Controller 5:95 Freq. Counter Chip, XTL (Evaluation Kill) 8:49
SN7470N 14 39 SN74155N 18 .69 SN74356N 18 .55 SN7472N 14 39 SN74156N 18 .50 SN74350N 16 .149 SN7473N 14 39 SN74157N 16 .49 SN74333N 14 .149	280026 40 CPU Non Segmented (10MHz)	59.95 HM6116P-2 24 2048x8 (120ms) LP CMOS HM6116P-2 24 2048x8 (120ms) LP CMOS HM6116P-3 24 2048x8 (150ms) CMOS HM6116P-3 24 2048x8 (150ms) CMOS	7.95 77215IPG 24 8.95 7215EV/RR 24 4.95 7216ALJI 28	4 Func. CMOS Stopwalch CKT 16.95 4 Func. Stopwalch Chip, XTL /Evaluation Kds 19.49 8 Digit Univ. Counter C. A 31.49
74,500 14 29 74LS 74,5244 78 129 74,501 14 29 74LS 74,5245 26 149	6502 46 MPU with Dlack (1MHz) 6502A 49 MPU with Clack (2MHz) 6502B 40 MPU with Clack (3MHz) 6520 48 Peripheral Inter Adapter	6.49 HM6116P-4 24 2048x8 (200ms) CMOS 8.95 HM6516LP-4 24 2048x8 (200ms) LP CMOS 8.95 HM6516AP-12 PM 8192-8 (200ms) LP CMOS	4.75 7210UP1 28 5.49 7217UI 28 - 37.95 7217AIPI 28	8 Digit Freq. Counter C.C. 21,49 4 Digit LED Up/Down Counter C.A. 10,95 4 Digit LED Up/Down Counter C.C. 9,95
74LS02 14 35 74LS132 14 65 74LS251 16 59 74LS03 14 29 74LS133 16 59 74LS253 16 59 74LS04 14 39 74LS13 16 39 74LS257 18 59 74LS05 14 35 74LS138 16 59 74LS258 16 59	6522 48 Perghara Inter Adapter. 6551 29 Async Curvin interface Adapter. 6800 40 MPU	5.49 HM6264P 15 29 8192x8 150ns) CMOS 10.95 HM6264LP 15 29 8192x8 150ns) LP CMOS 2.95 27LS00 14 256x1 (80ns) LP CMOS	37 95 7228AEV/Kir 40	LCD 41% Digit Up Counter DR: 10.95 5 Function Counter Chip, XTL (Evaluation (61) 99.95 ITERSIL Data Book (1356.p.) \$9.95
74LS08 14 35 74LS139 18 59 74LS260 14 59 74LS09 14 35 74LS145 18 1.19 74LS266 14 69 74LS10 14 35 74LS147 18 1.95 74LS262 14 69	6809CP 46 MPU with Clock and IAM 6809 48 CPU = 8-81 (Dx CPu ) Set (ascrize 5809E 40 CPU = 8-81 (External Doctoring) 68809E 40 CPU = 8-81 (External Doctoring) 2 MPs	8 95 74C921 19 25634 (250%) CMDS (9518) 195 74C930 14 1024x1 (250%) CMDS (8518) 18 1644 (35%) 93405	74HC	High Speed CMOS
74LS14 14 50 74LS151 16 59 74LS280 14 1.95 74LS15 14 35 74LS153 16 59 74LS280 14 1.95	68810 24 128±8 Static RAM (2MPU)	2.95 82510 16 1024z1 (50ns) 0.C. (93415) 2.95 82525 16 16x4 (50ns) 0.C. (74\$289)	2 95 74HC00 14 59 3 95 74HC02 14 59 2.25 74HC03 14 89	74HC139 16 1.06 74HC245 28 2.59 74HC187 16 1.29 74HC251 16 99 74HC151 16 99 74HC253 16 1.09
74LS26 14 35 74LS155 16 69 74LS322 28 395 74LS26 14 29 74LS156 16 69 74LS323 29 395 74LS27 14 35 74LS157 18 69 74LS323 18 29	6845   46   CRT Controller (CRTC)   68845   48   CRT Controller (CRTC)   2409c   6850   24   Asynchrolous Comm. Adapter   6860   24   0-600pp Deptal MODEM	1495	3.95 74HC004 14 59 74HC004 14 69 3.95 74HC00 14 59 3.49 74HC10 14 59 4.95 74HC11 14 69	74HC153 18 109 74HC257 18 99 74HC154 24 265 74HC259 18 1.69 74HC157 18 99 74HC266 14 89 74HC158 16 99 74HC273 28 2.79
74LS30 14 39 74LS160 18 69 74LS353 18 1.09 74LS32 14 39 74LS161 18 69 74LS365 18 49	68000L8 64 MPU 16-Bit (Bliety)	7.95 2708.5 28 1024±8 (550ms) \$4000246 19.95 TMS2516 28 204648 (450ms) 2716 9.96 TMS2532 24 4096±8 (450ms) 140C532 TMS2716 28 2046±8 (450ms) 3 v7tage 14.95. 2716 24 2046±8 (450ms) 3 v7tage	10.95 74HC20 14 59	74HC161 IS 1.39 74HC299 29 5.59 74HC162 IS 1.39 74HC366 IS 2.59
74LS18 14 39 74LS163 16 69 74LS367 16 49 74LS36 18 49 74LS373 20 L49	8031 46 Control Oriented OPE avRAM & V0 8035 40 MPI — N.Bri	74.95 2716 24 2048.8 (250m). 5.95 27C16 24 2048.8 CMOS 5.95 2716-1 24 2048.8 (350ms).	3.95 74HC37 14 59 3.95 74HC30 14 69 14.95 74HC32 14 79	74HC163 15 139 74HC367 15 2.59 74HC164 14 135 74HC373 20 2.59 74HC165 16 2.15 74HC374 20 2.69 74HC166 18 2.49 74HC390 18 1.59
74LS74 14 49 74LS170 16 149 74LS375 16 69 74LS374 14 49 74LS170 16 149 74LS386 14 39	8040N 6 48 CPU (256 bytes RAMB) 8060 40 CPU – 6 Bir NMOS 8070N 48 CPU (64 bytes RAMB)	9.95 2732 24 4096x8 (450ns)	4.95 74HC51 14 89 10.95 74HC58 14 89 11.49 74HC73 14 29	74HC173 16 129 74HC393 14 159 74HC174 16 109 74HC533 20 2.69 74HC175 16 109 74HC534 26 2.69
74L576 18 39 74L5174 16 69 74L5399 18 1.49 74L585 18 89 74L5175 16 69 74L5490 18 1.95 74L586 14 39 74L5181 24 2.49 2.44513 78 104	8073N 46 CPU w/Basic Micro interpreter. 8085A 46 CPU 8085A 46 CPU 16-bit 8Metr	195 2732A-45 24 4095x8 (450rs) 21V.	6.49 74HC75 18 99 .22.95 74HC76 18 79	74HC190 16 159 74HC595 16 3.19 74HC191 16 159 74HC688 20 3.59 74HC192 16 1,49 74HC4024 14 1,75
74L590 14 55 74L5190 16 79 74L534 20 195 74L592 14 55 74L5191 18 89 74L540 20 149 74L596 16 89 74L5193 18 89 74L540 20 149 74L596 16 89 74L5193 18 89 74L540 20 21 219	8087 44 Arithmesii Processor 8088 40 CPU 8/16-Bit. 8155 46 HMIOS RAM 1/O Port-Timer.	189 95 2754-25 <b>78</b> 8192x8 (250ns) 21V. 19,05 2754-45 <b>79</b> 8192x8 (450ns) 21V.	14.95 74HC85 16 1,69 7.19 74HC86 14 75 6.49 74HC107 14 79 27.95 74HC109 16 79 24.95 74HC109 16 79	74HC4060 18 1.19 74HC4060 18 1.49 74HC4075 16 1.19 74HC4075 14 59 74HC221 16 295 74HC4076 14 59
74LS107 14 39 74LS194 16 69 74LS641 20 2.19 74LS109 16 39 74LS195 16 59 74LS645 28 2.19 74LS119 16 35 74LS196 14 89 74LS645 18 1.49	8156 46 RAM with I/O Port amil Tener 8205 16 is Speed 1 out of 8 Binary Decelor. 8212 24 8-Bit Imput/Output (745412). 8224 16 Cack Gastrator/Driver.	3.95 27/26-25 24 16,384:86 (250ns) 1/284 Eprom 211 2.95 27/256-25 28 32/268:8 (250ns) 2/284 Eprom (14/ 2.95 745188 14 3248 PROM D.C. (6230m)	VI 99 95 74HC123 IS 2.29 1.75 74HC125 I4 1.75	7HHC237 16 1.49 74HC4511 16 1.95 7HHC240 26 229 74HC4514 24 4.19 7HHC241 26 229 74HC4530 16 2.59 7HHC242 14 2.15 74HC4543 16 3.75
74.5114 14 39 74.5197 14 89 74.5688 29 2.95 74.5122 14 49 74.5221 18 1.99 81.595 29 1.49 74.5122 16 79 74.5240 29 1.09 81.595 29 1.49 74.5125 14 59 74.5240 29 1.09 81.597 78 1.49 74.5125 14 59 74.5241 29 99 81.597 78 1.49	8298 28 System Cont /Bus Dreer (74S428) 8237-5 40 High Perf Prog DMA Cont (5MPtp 8238 29 System Controller (74S438)	4 95 745288 11 32x8 PROM 15 (6331-1) 19 95 745387 16 256x4 PROM 0.C (6300-1) 4 95 746471 21 256x8 PROM 25 (6309-1)	179 74HC137 18 159 195 74HC138 18 1,19	74HC243 14 2.15 74HCU04 is unbuffered 74HC244 28 2.29 All others are buffered
74LS126 14 59 74LS243 14 109 81LS96 20 149 74S00 14 35 74LS/PROMS* 74S241 20 195	8243 24 I/O Expander for 48 Series 8250W 44 Asym, Cerrim Flement 8251 29 Prog. Cerrim I/O (USART) 8251A 29 Prog. Cerrim, Intercace (USART)	10.95 745473 28 512x8 PROM 0.E. (\$348) 745474 28 512x8 PROM 0.E. (\$348) 4.95 745475 24 512x8 PROM 0.E. (\$340)	4.95 74C00 14 29 4.95 74C02 14 35 4.95 74C04 14 35 4.95 74C08 14 35	74C—C/MOS BC240 20 B95 74C107 14 79 74C373 20 239 74C151 10 2.19 74C374 20 2.29
74507 14 35 74514 14 55 745243 14 219 74503 14 35 74514 14 55 745243 14 219 74504 14 .45 745124 16 275 745244 20 219	8253 24 Prog Interval Times 8255 49 Prog Perisheral I/O (PPs 82554-5) 40 Prog Perisheral I/O (PPs 5MHz	- 0.95	6.95 9.95 74C10 14 35 2.95 74C14 14 59 2.95 74C20 14 35	74C154 84 3.25 74C901 14 59 74C157 16 1.75 74C902 14 .79 74C160 16 1.19 74C903 14 59
74505 14 .45 745132 14 1.89 745251 16 99 74508 14 .45 745133 16 .45 746253 16 99 74509 14 .39 745135 16 .89 745257 16 .39	8259 28 Prog. Interrupt Control	. 19 95   745573   14 1024x4   PROM LS (825137)	. 495 74C30 14 38 495 74C32 14 39 2.95 74C42 16 1,19	74C162 18 1.19 74C907 14 89 74C163 18 1.19 74C911 20 8.95
74510 14 35 745136 14 1.39 745258 18 99 745257 17 74513 14 35 745138 18 89 745260 14 79 74515 14 35 745139 18 89 745273 28 2.39	8279 48 Prog. Reytourd/Ospitay Interface: 8282 20 Octal Latels. 8284 18 Occa Generator/Onver. 8286 28 Octal Bus Transceiver. 8287 29 Octal Bus Transceiver (Invented)	8.95 825123 15 32x8 PROM TS (27519) 6.95 825126 14 25614 PROM TS (27520) 7.86 825129 18 25614 PROM TS (27520) 7.86 825129 18 25614 PROM TS (27521)	295 74C73 14 69 -295 74C74 14 59 -295 74G85 16 1.39	74C165 16 1.29 74C915 16 1.19 74C173 16 89 74C917 21 8.95 74C174 18 1.19 74C922 16 4.49
74520 14 35 745140 14 69 745290 14 169 74522 14 35 745151 16 99 745297 16 179 74530 14 35 745153 18 99 745298 16 179	6286 79 Bus Controller 6303 88 8-Bit In State 8-Directional Trans. 6304 20 8-Bit Bi-Directional Receiver	19.95 825191 2048:4 PROM 25 (TBP24581). 3.49 DARPS181N 24 1024-8 PROM 25 (R25181).	9.95 74086 14 29 14.95 74089 16 5.95 9.95 74090 14 1.09 9.95 74093 14 1.09 9.95 74095 14 5.19	74C175 18 1.19 74C923 20 4.95 74C192 14 1.39 74C925 16 5.95 74C193 14 1.39 74C926 18 5.95 74C195 18 1.29 80C95 18 69
74532 14 .45 745157 16 99 745299 28 5.95 74537 14 99 745150 16 99 745373 28 2.49 74538 14 69 745160 16 2.29 745374 28 2.49	8310 28 Octal Latched Peripheral Dream. 8741 46 8-Bit Unis, Perupheral Interface. 8748 40 HMDS EPROM MPU. 8749 40 MPU 8-Bit /FPROM Metam of 80491	29.95 DM875191N 24 2048x8 PROM ES (825195) 39.95 DM875191N 24 2048x8 PROM ES (825191)	14.95 TL071CP \$ 79	74G21 18 1.75 80097 IB 69
74551 14 35 745169 18 4.29 745367 18 1.95 74554 14 39 745174 18 1.09 745471 28 4.95 74555 14 39 745175 18 1.09 745472 28 4.95	8749 40 MPU 6-Bit (EPROM Marson of 8049) . 8755 41 88 EPRCM with VO . 80186-6 40 High Integration 16-Bit MPU . DESK CONTROLLERS	39 95 DC10 Mostes DC/SC Converter +5V to - 39 95 ADC0801 28 8-Bit AV Converter (1/4(158) ADC0803 28 8-Bit AV Converter (1/4(158) ADC0804 28 8-Bit AV CONVERTER (1/4(15	9V 2.95 TL072CP # 1.09 14.95 TL074CN 14 1.95 4.95 TL081CP # 59	LINEAR LM747N 14 69 LM748N 8 59 LF355N 8 109 UN760HC 8.95
74\$74 14 55 74\$188* 16 175 74\$473* 20 4.95 74\$85 16 1.99 74\$194 16 1.49 74\$570* 16 2.95 74\$66 14 55 74\$195 16 1.49 74\$\$71* 18 2.95	PS1771-1 48 Single Density. FD1791 48 Single/Dual Density (Hrs.) FD1793 40 Single/Double Density (Bruc).	16.95   ADCOBOR   28 8-81 A/D Conventre (15-0)	9 9.95 TL084CN 14 1.95 4.49 LM109N 5.95 og 14.95 LM301CN 8 39	LF356N 8 1.09 LM1456V 8 1.95 LM359N 8 59 LM1456CN 8 59 LM359N 14 1.79 LM1468N 14 69 LM370N 14 4.95 LM146NN 14 60
745112 18 55 745196 14 1.49 745572" 18 4.95 745113 14 55 745240 28 195 745573" 18 4.95 CA3010M 1.09 CA-LINEAR CA3130E 6 1.19	FD1795 40 Dual Density/Side Select (Pre)	26.95 DAC0806 16 8-Bit D/A Conventor (0.70% URL) 29.95 DAC0807 16 8-Bit D/A Conventor (MC1408-7) DAC0808 16 Bit D/A Conventor (MC1408-8)	195 LM302H 249 149 LM304H 1.95 .225 LM305H 99	LM373N 14 4.95 LM1496N 18 99 LM377N 14 1.95 LM1605CK 9.95
CA3039H 125 CA3081N NS 1.15 CA3140E 8 85 CA3046N 14 99 CA3082N 16 1.15 CA3160H 1.79 CA3082N 16 1.15 CA3160H 1.79	DS0026CN 8 Dust MOS Clock Dyner (SMMtz) 9857851 28 Communication Clop MC3470P 18 Floopy Dish Read Arrip System 17 Camera Sync. Generator	. 1.95 DAC0831 20 8-Bit Up D/A Com 10% Lini	. 649 LM308CN 8 69 5461795 LM309K 125	LM380N 14 89 LM1871N 18 2:95 LM381N 14 1:79 LM1872N 18 3:25
CA3080N 16 2.95 CA3080N 16 1.15 CA3161E 16 179 CA3085E 14 1.49 CA3080N 16 1.95 CA3162E 18 6.95 CA3085E 14 1.49 CA3080N 16 1.95 CA3189E 16 2.79	MM54240H 24 Asynchrolous Parsumber Placever   MM58167AN 24 Microprocessor Real Birne Clack   MM5817AN 18 Micro Corpositio Time Clack	9.95 DIC1020 16 10-Bit D/A Come (0.05% Lin.). 5.95 DIC1022 18 10-Bit D/A Come (0.05% Lin.). 5.95 DIC1022 18 12-Bit D/A Come (0.05% Lin.). 6.95 DIC1230 28 12-Bit Up D/A Come (0.05% Lin.). 1.79 DIC1231 28 12-Bit Up D/A Come (1.0% Lin.).	7.95 LM3110N 6 59 59 5.595 LM312N 2.79 1.19 1.495 LM317T 1.19	LM382N 14 1.49 LM1877N-9.14 2.95 LM384N 14 1.95 LM1889N 18 1.95 LM386N-3 6 89 LM1896N 14 1.99 LM387N 8 1.38 LM20027 1.95
CD4001 14 29 CD - CMOS CD4503 16 69 CD4502 14 28 CD4505 18 129	MMS369AA/N Prog Oscillator/Divider (60Hz) MMS369EST Prog Oscillator/Divider (100Hz)	179 DAC1231 29 12-Bit Up D/A Conv (10% Lim). 195 AT-8-1813A 48 381 Bad MAIT (TRYBE).	1.350 LM318CN \$ 1.59 LM319N 14 1.49 LM320N-5 1.35	LM389N 16 1.19 ULN2003A 16 1.69 LM391N-80 16 1.19 XR2206 16 3.95
C04006 l4 89 CD4041 14 69 CD4507 14 1.19 CD4007 14 29 CD4042 18 69 CD4508 24 1.95 CD4008 18 89 CD4043 18 79 CD4510 18 65	Salderthi (Gaid) Stan	Societs  Gold  Level #3   DUVILU-	LMG20K-12 1.35 LMG20K-15 1.35 LMG20K-24 1.35 LMG20T-5 85	LMG92N 6 59 X02207 14 2.49 LMG93N 6 .45 XR2208 16 1.79 LF398N 6 3.95 XR2211 14 2.95 LMG99N 595 LMG97P 1.95
CDM009   18   59   CDM044   18   79   CD4511   18   85   CD4010   16   49   CD4046   18   89   CD4512   16   85   CD4512   16   85   CD4512   14   1.49   CD4514   24   1.49   24   1	Low Profile (Tin) Securits Part to 18 18-90  Part No. 1-8 19-90 180-92 8 pm 5G 39 35	198-09 8 pm WW 55 .49 .45 Header Plugs [Get 29 10 pm WW 69 55 59 Pm 44 14 10.00	LM3207-12 .85 LM3207-15 .65 LM3207-24 .65	LF412OH 8 195 LM2878P 2.95 TL494ON 18 2.79 LM2901N 14 79 TL496CP 8 1.59 LM2902N 14 89
CD4012 14 29 CD4048 18 59 CD6515 24 1,49 CD4014 16 89 CD4050 16 39 CD4516 16 89 CD4049 1 8 39 CD4516 16 89 CD4516 16 89 CD4516 16 89 CD4518 16 89 CD4518 16 89	8 pm LP 16 .14 13 14 pm SG .49 .45 14 pm LP .17 .15 .14 16 pm SG .55 .49 16 pm LP .19 .17 .16 18 pm SG .65 .59	39 14 pm WW 75 69 65 14 pm HP 65 59 16 pm WW 95 85 75 16 pm HP 69 65	55 LM323K 4.95 59 LM324M 14 59 89 LM329DZ 66	NESSIV 6 1.79 LM2907N 14 2.49 NES4NN 14 1.95 LM2917N 6 1.95 NES50A 14 1.95 LM3900N 14 59
CD4015   16   39   CD4051   18   79   CD4519   16   59	20 pm LP 30 27 25 22 pm 3G 79 69 22 pm LP 31 28 26 24 pm 3G 79 69 24 pm LP 33 30 28 28 pm 3G 95 85	65 22 pn WW 1.29 1.79 1.05 Header Covers 65 24 pn WW 1.35 1.79 1.09 Header Covers .75 26 pn WW 1.69 1.55 1.39 14 pn HC 15 .13	UM331N # 3.95 UM3342 1.19 .12 UM335Z 1.29	ME555V 6 35 LM3905CN 8 1,19 1XH1555 6 69 LM3909N 8 89 LM556N 14 .79 LM3914H 18 2,30
C04019 18 49 C04059 18 2.95 C04528 16 1.19 C04020 18 .75 C04060 16 .89 C04531 18 .89	28 pm LP .40 .37 .35 .36 pm 56 .125 .1.5 40 pm LP .49 .46 .43 .40 pm 56 .1.39 .125 \$10.00 Minimum Orcler — U.S. Funds Only	1.15 40 pm WW 2.29 1.95 1.79 24 pm HC 29 25	22 LNC337MP 1.15 LNC337T 1.89 LNC338K 6.95	MESSAN 16 159 (M3915M 16 2.39 MESSAN 16 195 (M3916M 16 2.39 LMSS5N 14 99 RC4136N 14 1.25
CDM021   18 .75   CDM066   14 .45   CDM538   16 1,49   CDM022   18 .75   CDM088   14 .39   CDM541   14 1.49   CDM023   14 .29   CDM069   14 .35   CDM543   16 1.19	California Residents Add 61/m Sales Tax Shipping — Add 5% jlus \$1.50 Insurance Send S.A.S.E. for Monthly sales Flyer!	Send \$1.00 Poetage for you FREE 1985 JAMECO CATA Prices Subject to Change	UF (M339N 14 69	LMS6CN 8 1.49 RC4151MB 6 1.95 LMS67V 8 99 RC4195TK 5.95 ME57ON 18 2.95 LM4250CN 8 1,49
CD4024 14 59 CD4070 14 29 CD4562 14 6.95 CD4025 14 2.99 CD4071 14 29 CD4566 16 2.95 CD4026 16 1.59 CD4072 14 29 CD4563 16 2.49 CD4027 16 4.6 CD4072 14 29 CD4563 16 2.49		Order Electronics - Worldwide	LM340H24 1.35 LM340T-5 75 LM340T-12 75	NE5710 16 2.49 LM4500A 16 2.95 NE592N 14 1.19 NE5532 8 1.69 LM703CN 8 1.49 NE5534 8 1.39
CD4027 18 .45 CD4073 14 29 CD4584 14 59 CD4028 18 69 CD4027 14 35 CD4723 18 1,19 CD4029 18 79 CD4028 14 .49 CD4728 18 1,19	MasterCard 3	meco VISA	LM3407-15 75 LM3407-24 75 LF347N 14 1,49	LM710N 14 69 79M05AH 1.29 LM711N 14 79 KL8038B 14 3.95 LM723N 14 49 LM13080N 8 1.19
CD4030 14 39 CD4061 14 29 MC14410 18 8.95 CD4034 24 1.79 CD4093 14 49 MC14411 24 11.95 CD4035 18 79 CD4094 18 1.95 MC14412 18 7.95		ECTRONICS ROAD, BELMONT, CA 94002	LNI348N 14 89 LNI350N 4 79 LF351N 8 59 LF353N 4 89	LM733N 14 89 LM13600N 16 1.19 LM739N 14 195 78477 20 3.95 LM741CN 6 39
CD4040 18 .75 CD4098 16 195 MC14433 24 17.95 MR 1967 is CD4099 16 1.89 MC14572 18 119	12/84 PHONE ORDERS WELD	OME — (415) 592-8097 Telex: 176	The same of the sa	t. Linear Data Book (1952 pgs.) . \$11.95

SN 60/40 Rosin Core (RA) One fb. Reel 16 swg. 18 swg. 19 swg.

\$7.95 \$8.45 \$8.95 (.040) \$9.45 (.032) \$9.95

1/2 fb. Reels 22 swg. (.028) 24 swg. (.022) \$5.95 \$7.95 SN 62 (2% Silver)

Rosin Core 21 swg. (.031)

FREE Freight On All Orders Over \$25 Under \$25 add \$2.50 per order

Minimum order \$10

FREE Desoldering Wick

Check Money Order VISA

Call TOLL FREE 800-645-4808

#### INVENTORS!

IDEAS have value! Ever think of an idea, forget it, and see it later on the market? Many people don't forget, act quickly, and are rewarded by American industry. Write down your idea! We offer free disclosure registration and initial consultation regarding your idea's potential value. Call or write without delay for your free information package. AMERICAN INVENTORS CORPORATION, 82 Broad Street, Dept. RE, Westfield, MA 01086, (413) 568-3753. A fee based marketing company. Offices coast to coast

#### NEWSLETTERS

ELECTRONIC SYSTEMS NEWSLETTER is a monthly publication written especially for the electronics hobbyist/experimenter. Fascinating new ideas, sources. Free details. AF PUBLISHING. Dept. R2, PO Box 524, So. Hadley, MA 01075.

#### **BUSINESS OPPORTUNITIES**

US \$8.00 including disk thousand name brand programs for Apple IBM-PC details RELIANT, PO Box 33610, Sheungwan, Hong Kong.

MECHANICALLY inclined individuals desiring ownership of small electronics manufacturing business—without investment. Write: **BUSINESSES**, 92-R, Brighton 11th, Brooklyn, NY 11235.

PROJECTION TV...Make \$\$\$'s assembling proj ectors... Easy... Results comparable to \$2,500.00 projectors... Your total cost less than \$20.00... Plans, 8" lens & dealer's information \$17.50... Illustrated information free... MACROCOMA GEX, Washington Crossing, PA 18977. Creditcard orders 24 hours (215) 736-2880.

YOUR own radio station! AM, FM, cable. Home operation possible. **BROADCASTING**, Box 130-F1, Paradise, CA 95969.

BURGLAR alarms—booming business. Get In now. Starting information \$2.00. DYNAMIC SECURITY, PO Box 1456-T, Grand Rapids, MI 49501.

PICTURE tube rebuilding equipment. Buy/sell, new/used machinery. Full training. CHICAGO TELEVI-SION, 633 North Semoran Blvd., Orlando, FL 32807, (305) 281-1260

## PROFITS

#### ELECTRONIC ASSEMBLY BUSINESS

Start home, spare time, Investment knowledge or experience unnecessary, BIG DEMAND assem-bling electronic devices. Sales handled by profes-sionals. Unusual business opportunity.

FREE: Complete Illustrated literature BARTA, RE-O Box 248 Walnut Creek, Calif. 94597

#### DO-IT-YOURSELF TV REPAIR

NEW!...Repair any TV...Easy. Anyone can do it. Write, RESEARCH, Rt. 3, Box 601 BR, Colville, WA

#### **EDUCATION & INSTRUCTION**

FCC General Radiotelephone License correspondence course, \$89.50 for 60 individual lessons. Payment plan, results guaranteed! Details free. AMERICAN TECHNICAL INSTITUTE. Box 201, Cedar Mountain, NC 28718.

## ATTENTION ELECTRONIC TECHNICIANS



Highly Effective Home Study BSEE Degree Pro-gram for Experienced Electronic Technicians Our New Advanced Placement Program grants Credit for previous Schooling & Professional Ex-perience. Advance Rapidlyl. Our 40th Yearl FREE DESCRIPTIVE LITERATURE!

Cook's Institute of Electronics Engineering P.O. BOX 20345 JACKSON MS 39209

#### WANTED

OLD tubes: 2A3, 10's, 45's, 50's, 80's, 81's, 211, 242, 845, VT-52, VT-62. WESTERN ELECTRIC EQUIP-MENTS: (818) 576-2642, David POB 832, M-Park, CA 91754

OLD tubes, unused and boxed. Send your stocklist. TSUTOM YOSHIHARA, C1-105, Deguchicho-34, Suita, Osaka 564, Japan

INVENTIONS, ideas, new products wanted! Industry presentation/national exposition. Call free (1-800) 528-6050. Arizona, (1-800) 352-0458. X831.

#### **REEL-TO-REEL TAPES**

AMPEX professional series open reel tape, 1800-or 2400-feet on 7-inch reels, used once. Case of 40, \$45.00. 101/2 × 3600 feet and cassettes available MasterCard/Visa. VALTECH ELECTRONICS, Box 6-RE, Richboro, PA 18954 (215) 322-4866.

## MICROWAVE TV ANTENNA SYSTEMS

Freg. 2.1 to 2.7 GHz . 34 db Gain +

LIFETIME LIMITED WARRANTY **PARTS & LABOR** 



**COMPLETE SYSTEMS:** (as Pictured)

Commercial 40' \$99.95 **Rod Style** Parabolic 20

Dish Style \$79.95 COMPONENTS **Down Converters** 

(either style) **Power Supplies** \$24.95

(12V to 16V, DC+) Data Info (Plans) \$ 9.95

CALL OR WRITE FOR KITS, PARTS, OR MORE INFORMATION

Shipping & Handling Add \$5.00 We Repair Most Types Down Converters & Power Supplies

Phillips-Tech ectronics P.O. BOX 34772 Phoenbi, AZ <u>8506</u>7

(802) 987-8972 Special Quantity Pricing **Dealers Wanted** 



VISA

COD'S

ALUMINUM EQUIPMENT CABINET

9" X 12" X 3-1/2" ORIG COST \$40. NEW HEAVY GAUGE ALUMINUM (1/8" SIDEWALLS) WITH ATTRACTIVE CAUGE ALUMINUM (176 SIDEWALLS) WITH ATTRACTIVE BLACK FINISH, GREAT FOR ALL SORTS OF TEST AND COMPUTER EQUIP. FRONT PANEL IS PUNCHED FOR COUNTER/DVM USE (EASILY COVERED), REAR PANEL HAS OPENINGS FOR LINE PLUG, SWITCH, ETC.

X-8000 WT 5 LB

\$9.95 10/\$89 100/\$75

END STACKABLE

LED VU METER

M-4275 WT O.I LB



NSM INCLUDES A 10 ELEMENT LED LINEAR ARRAY WITH AN LM3916 DECODER/DRIVER. THRESHHOLDS
ARE SET AT COMMON VU POINTS
THE FIRST 7 LEDS ARE GREEN,
THE LAST 3 ARE RED. 2" X
0.85" OVERALL, OPERATES OVERALL, VDC, 18 FROM ACCURACY. 375 9

10/\$ 34 100/\$300

7-12 VDC ED CLOCK 0000 0000 75 0000

NATIONAL MA-6008 IS A COMPLETE DC POWERED CLOCK WITH KEYBOARD TIME/DATE ENTRY, TIME BASE CONSISTING OF AN MM5369 AND 3.579 MHz CRYSTAL, ALL IN A 2-3/8 X J-1/4 MODULE BRAND NEW, 1008 FUNCTIONAL. DATA- 35'

100/ \$200. 10/\$25 M-6008 WT O.I LB

SOUND EFFECTS



COMPLETE, OPERATING ASSY. HAS FLASHING LIGHTS, HEAVY SPEAKER, ON 9-12 VDC1 MAKES SIREN & CAN RE-PROGRAM THE SN76487 TO MAKE LOTS OF OTHERS!

X-1560 WT 0.2 LB \$ | 95 10/\$17

50

YOU SAY YOU WANT A FREE PLYER AND YOU WANT IT NOW? JUST SEND US A SELF ADDRESSED STAMPED BUSINESS SIZE ENVELOPE.

IAMONDBACK

ELECTRONICS COMPANY PO BOX 12095 SARASOTA, FL. 33578

Phone Orders (813) 953-2829

Continental US add \$1.80 for the first pound and 50¢ for each additional pound. Canada add \$3.50 first lb and \$1 for each additional. Plorida add 5% sales tax. MAIL ORDER \$7 MINIMUM COD, UPS CASE CHLY \$15 MIN. VISA & MASTENCARD \$15 MIN.

# HE FIRST NAME IN LECTRONIC TEST G



#### 20 MHz DUAL TRACE OSCILLOSCOPE


Unsurpassed quality at an unbeatable price, the Ramsey oscilloscope compares to others costing hundreds more. Features Include a component testing circuit for resistor, capacitor, digital circuit and diode testing. • TV video sync filter • wide bandwidth & high sensitivity \* internal graticule • front panel trace rotator • 2 axis • high quality hook on probes included sensitivity \* y mode • regulated power supply • built-in calibrator • rock solid friggering • USA—Add \$10.00 per unit for postage, overseas orders add 15% of total order for insured surface mail.



#### **NEW RAMSEY 1200 VOM MULTITESTER**

Check transistors, dlodes and LEOs with this professional quality meter. Other features include; decibel scale • 20K volt metering system • 3½" mirrored scale • polarity switch • 20 measuring ranges • safety probes • high impact plastic case

\$2495 test leads and battery included

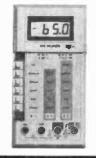

## 45 MHz DUAL SWEEP OSCILLOSCOPE

...

The Ramsey 525 is a dual time base, delayed sweep unit that includes a built-insignal delay fine to permit clear viewing during very short rise times of high frequency waveforms. Other features include variable trigger holdoff < 20 callbraied sweep time ranges from 0.5 x/div to 0.2 x/5/div. \* fully adjustable sweep
time \* X5 sweep magnification • five trigger sources; CPL, CPL, LINE EXTernal
and INTernal (V mode) • front panel i-y operation, 2 axis input • sum difference of CPL, and CPL sweetorms displayed as single trace • sweep gate and
sweep output • auto focus • single sweep

\*Same as runt to loft. Same as unil to left

**\$799**95 high quality hook on probes included

#### RAMSEY D-1100 **VOM MULTITESTER**

Compact and reliable, designed to service a wide variety of equipment. Features include • mirror back scale • double-jeweled precision moving coil • double overload protection • an ideal low cost unit for the beginner or as a spare back-up unit.

\$1995 lest leads and battery included



#### **RAMSEY D-3100** DIGITAL MULTIMETER

Reliable, accurate digital measurements at an amazingly low cost • In-line color coded push buttons, speeds range selection • abs plastic till stand • recessed input lacks • overload protection on all ranges • 3% digit LCD display with auto zero, auto polarity & low BAT. indicator

\$4995 test leads and battery included



•

#### CT-70 7 DIGIT 525 MHz COUNTER

Lab quality at a breakthrough price. Features
• 3 frequency ranges each with pre amp • du
selectable gate times • gate activity Indicator
• 50mV @ 150 MHz typical sensitivity • wide
frequency range • 1 ppm accuracy

\$11995 wired includes AC adapter

-70 kit -4 nicad pack . \$99.95 ....8.95



#### CT-90 9 DIGIT 600 MHz COUNTER

The most versatile for less than \$300, Features 3 selectable gate times • 9 digits • gate Indicator • display hold • 25mV @ 15t MHz typical sensitivity • 10 MHz timebase for WWV calibration • 1 ppm accuracy

\$14995 wired includes AC adapter

CT-90 kit ... OV-1 0.1 PPM oven timebase BP-4 nicad pack ... \$129.95 ...59.95 ....8.95



#### CT-125 9 DIGIT 1.2 GHz COUNTER

A 9 digit counter that will outperform units costing hundreds more. • gate indicator • 24mV @ 150 MHz typical sensitivity • 9 digit display • 1 ppm accuracy • display hold • dual inputs with preamps

\$16995 wired includes AC adapter

BP-4 nicad pack .....



#### CT-50 8 DIGIT 600 MHz COUNTER

A versatile lab bench counter with optional receive frequency adapter, which turns the CT-50 into a digital readout for most any receiver • 25 mV @ 150 MHz typical sensitivity • 8 digit display • 1 ppm accuracy

\$16995 wired



#### **DM-700 DIGITAL MULTIMETER**

Professional quality at a hobbylst price. Fea-tures include 26 different ranges and 5 func-tions • 3½ diglt, ½ Inch LED display • auto-matic decimal placement • automatic polarity

\$11995 wired includes AC adapter



#### **PS-2 AUDIO MULTIPLIER**

The PS-2 is handy for high resolution audio resolution measurements, multiplies UP in frequency • great for PL tone measurements • multiplies by 10 or 100 • 0.01 Hz resolution & built-in signal preamp/conditioner

\$4995

wired



#### **PR-2 COUNTER PREAMP**

The PR-2 is Ideal for measuring weak signals from 10 to 1,000 MHz • flat 25 db gain • BNC connectors • great for shifting RF • ideal receiver/TV preamp

\$4495 wired includes AC adapter



#### **PS-1B 600 MHz PRESCALER**

Extends the range of your present counter to 600 MHz • 2 stage preamp • divide by 10 cir-cultry • sensitivity; 25mV @ 150 MHz • BNC connectors • drives any counter

\$5995 wired includes AC adapter

\$49.95

#### **ACCESSORIES FOR RAMSEY COUNTERS**

Telescopic whip antenna—BNC plug .. \$ 8.95 Direct probe, general purpose use ..... 13.95 Tilt bail. for CT-70, 90, 125 ...... 3.95 VISA

**PHONE ORDERS CALL TELEX 466735 RAMSEY CI** 

TERMS: • satisfaction guaranteed • examine for 10 days; if not pleased, return in original form for retund • add 6% for shipping and insurance to a maximum of \$10.00 • overseas add 15% for surface mail • C000 add \$2.50 (C00 in USA only) • orders under \$15.00 and \$1.50 • NY residents add 7% sales tax • 90 day parts warranty on all kits • 1 year parts & labor warranty on all wired units.



RAMSEY ELECTRONICS, INC. 2575 Baird Rd. Penfield, N.Y. 14626



ORDER TOLL FREE

(800) 538-8800

(CALIFORNIA RESIDENTS)

(800) 848-8008



MasterC**ard** 

#### STATIC RAMS

2101	258 x 4 (450ms)	1.90
5101	256 x 4 (450es) (cmes)	3.90
2102-1	1024 x 1 [450ms]	.88
2102L-4	1024 x 1 (450ms) 1024 x 1 (450ms) (LP)	.98
2102L-2	1024 x 1 [250ms] [LP]	1.45
2111	258 x 4 (450ms)	2.45
	256 x 4 [450es]	2.95
2114	1024 x 4 (450ms)	.99
2114-25	1024 x 4 (250ms)	1.10
21141-4	1024 x 4 (450ms) (LP)	1.20
2114L-3	1024 x 4 (300ms) [LP]	1.30
2114L-2		1.40
2125	1024 x 1	2.49
2147	4096 x 1 (55ms)	4.90
TM84044-4		3.45
TM 84044-3		3.95
TM84044-2	4096 x 1 (200ms)	4.45
MK4118	1024 x 8 (250ms)	9.90
TM M2016-200	2048 x 8 (200ms)	4.10
TMM2018-150		4.90
TMM2018-100	2048 x 8 (100ms)	6.10
HM6116-4	2048 x 8 (200mx) (cmes)	4.70
HM8116-3	2048 x 8 (150as) (cmes)	4.90
HM8116-2	2048 x 8 (120ms) (cmes)	8,90
HM8118LP-4	2048 x 8 (200ms) (cmes)	5.90
HM8118LP-3	2048 x B (150ms) (cmes)(LP)	6,90
HM6116LP-2	2048 x 8 (120ms) (cmes)(LP)	
Z-6132	4096 x 8 (300ma) (Quint)	
HM8264P-15	RIO2 - 0 (150cc) (usus)	38.95
		48.95
HM6264LP-15	8192 x 8 (150ms) (cmes)	40.70

LP = Law Power Quant = Quani-Static

#### **DYNAMIC RAMS**

TM34027	4096 x 1	(250ms)	1.95
UP0411	4096 x 1	[300as]	1.95
MM5280	4096 x 1	(300ms)	1.95
MK4108	8192 x 1	[200ma]	1.90
MM5298	8192 x 1	(250ma)	1.80
4116-200	16384 x 1	(200ma)	.79
4116-150	16384 x 1	(150ms)	1.20
2118	16384 x 1	(150es) (5v)	4.90
4164-250	85536 x 1	(250ms)	4.45
4184-200	65536 x 1	(200ms) (5v)	5.00
4164-150	65538 x 1	(150ms) (5v)	5.00

5V = Single 5 Volt Supply

#### **EPROMS**

1702	256 x 6 (1us) 4.45
2708	1024 x 8 (450ms) 2.49
2758	1024 x 8 (450ms) (5v) 5.90
2716	2048 x 8 [450ms] [5v] 2.95
2716-1	2048 x 8 (350es) (5v) 5.90
TM32516	2048 x 8 [450ms] [5v] 5.45
TM\$2716	2048 x 8 (450mg) 6.95
TM \$2532	4098 x 8 (450mm) (5w) 5.90
2732	4096 x 8 (450ms) (5w) 4.45
2732-250	4096 x 8 (250es) (5v) 8.90
2732-200	4096 x 8 (200ms) (5V) 10.95
2784	8192 x 8 (450ms) (5v) 6.45
2784-250	8192 x 8 (250ms) (5v) 7.45
2764-200	8192 x 1 (200ms) (5v) 16.45
TM \$2564	8192 x 8 (450ms) (5v) 16.95
MC88764	8192 x 8 (450ms) (5v) (24 pin) 38.95
27128	18384 x 8 Call 24.95
MC88764	8192 x 8 (450ms) (5v) (24 pin) 38.95

5v = Single 5 Volt Supply

	74LS00										
74L800	.23	74L\$125 74L\$126	.48	74L8260 74L8266	.58						
74LS01 74LS02	.24	7418132	.58	7418273	1.45						
741803	.24	74L8133	.58	7418275	3.30						
74LS04	.23	74L\$138	.38	74L\$279	.48						
74LS05	.24	74L\$137	.98	74L8260	1.95						
74L808	.27	74L8138	.54	74L8283	.68						
74L309	.28	74L8139	.54	74L8290	.88						
74L810	.24	74L8145	1.15	74L8293	.88						
74L811	.34	74L\$147 74L\$148	2.45 1.30	74L8295 74L8298	.98						
74L812 74L813	.44	74L8151	.54	7418299	1.70						
74L814	.58	74L\$153	.54	74L\$323	3.45						
74L815	.34	74L8154	1.85	74L8324	1.70						
74L820	.24	74L8155	.88	74L8352	1.25						
74L821	.28	74L8156	.68	74L8353	1.25						
74L822	.24	74L8157	.64	74L\$363	1.30						
74L826	.28	74L8158	.58	74L\$364 74L\$365	1.90						
74L827 74L828	.28	74L8160 74L8161	.64	7412366	.46						
741830	24	7418162	.68	7418367	.44						
741832	.28	74L\$163	.64	74L\$368	.44						
74L833	.54	74L\$164	.68	74L8373	1.35						
74L837	.34	74L8165	.94	74L8374	1.35						
74L\$38	.34	74L\$166	1.90	74L\$377	1.35						
74L840	.24	74L8168	1.70	74L8378	1.13						
74L842	.48	74L8169	1.70	74L8378 74L8385	1.30						
74L847 74L848	.74	74L8170 74L8173	1.45	7418385	.44						
741849	.74	7418174	.54	74L8390	1.15						
74L851	24	7418175	.54	7418393	1.15						
74L\$54	.28	74L\$181	2.10	74L8395	1.15						
74L855	.28	74L8189	8.90	74L\$399	1.45						
74L863	1.20	74L\$190	.88	74L8424	2.90						
74L873	.38	74L8191	.88	74L8447	.36						
74L874 74L875	.34	74L8192 74L8193	.78 .78	74L8490 74L8624	1.90 3.95						
741878	.38	7418194	.68	7418640	2.15						
741878	48	74L8195	.68	7418645	2.15						
74L383	.59	74L\$198	.78	74L\$888	1.65						
74L885	.68	74L\$197	.78	74L\$669	1.85						
74L888	.38	74L8221	.88	74L8870	1.45						
74L890	.54	74L8240	.94	74L8674	9.50						
74L891	.88.	7418241	.98	74L\$882	3.15						
74L892 74L893	.54	74L8242 74L8243	.98	74L8683 74L8684	3.15						
741895	.74	7418244	1.25	7418685	3.15						
74L898	.88	7418246	1.45	74L\$888	2.35						
74L8107	.38	74L8247	.74	74L8889	3.15						
74L\$109	.38	74L8248	.98	7418783	23.95						
74L8112	.38	74L8249	.98	811895	1.45						
74L\$113	.38	74L\$251	.58	81LS96	1.45						
74L8114 74L8122	.36	74L8253 74L8257	.58 .58	81L\$97 81L\$98	1.45						
7418123	.78	74L\$258	.58	25182521	2.75						
74L8124	2.85	74L8259	2.70	25L82589	4.20						

#### CRT CONTROLLERS

1771		14.95	2797	 84.65
			6843	
	0.75		8272	 38.95
1795		28.95	UP0765	 38.95
1797		48.95	M88876	 23.95
2791		79.95	M88877	 25.95
2793		79.95	1691	 16.95
			2143	
2100		04.00		 

#### DISC CONTROLLERS

1771						14.95	2797 .					84.95
1791						23.95	6843					33.95
1793						25.95	8272			í		38.95
1795							UP0765					38.95
1797		ì	i			48.95	M88870	5				28.95
2791						79.95	M 88877	1				33.95
2793						79.95	1691				ì	18.95
2795						84 95	2143					17.95

#### QUV-T8/1 EPROM Eraser



#### QUV-T8/1 Economy Model:

Low cost EPROM eraser in plastic enclosure. The UV element is in the lid and you place the EPROMS in the bottom half. No timer or switch option.

- · Erases up to 8 EPROMS in 15 20 minutes.
- 12,000 uWatts at 1" distance.
- 90-Day Warranty

49.95

							65	500				Ī			Ī		
	1	h	A	٠	1	Z			2	P	И	۲	12	Z			
6502							4.90	6502A								6.9	0
6504							6.90	6522A								9.9	0
6505							8.90	6532A							1	0.9	5
6507							9.90	6545A							2	6.9	15
6520							4.30	6551A							-1	0.9	15
6522							6.90		_								
6532							9.90		3	1	ů	ŀ	14	4			
6545							21.50	6502B		×		,				9.9	10
6551							10.85										

68	300
66000, 58.95	6860 9.90
6600 3.90	6862 10.95
6802 7.90	6675 6.90
6808 12.90	6880 2.20
8809E18.95	6883 21.95
6809 10.95	6804723.95
6810 2,90	68488
6820 4.30	
6821 3.20	1 MHZ
6828 13.95	68800 9.95
6840 11.95	6880221.25
6843 33.95	68809E 28.95
6844 24.95	6880928.95
6845 13.95	68810 6.90
6847 10.95	68821 6.90
6850 3.20	68845
6852 15.70	68850

8035			ě						5.90	8089	×	×			i.	88.95
8039									8.90	8155				ì		6.90
M8-80								٠	18.95	8155-2						7.90
INS-80 8080									49.95 3.90	8156						6.90
8085	*	•					٠		5.90	8185						28.95
8085A	-1	2		į					10.95	8185-2					٠	38.95
8088								į.	28.95	8741						38.95
8087								1	99.00	8748	٠					49.95
8008	٠	٠	٠		٠	٠			38.95	8755						23.96

02	.00
820223.95	6255-5 5.20
8203	8257 7.90
8205 3.45	8257-5 8.90
8212 1.75	8259
8214 3.80	8259-5 7.45
8216 1.70	8271
8224 2.20	8272
6226 1.75	8275 28.95
82283.45	8279 8.90
8237 18.95	8279-5 9.00
8237-5 20.95	8282 6.45
8238 4.45	8263 6.45
8243 10.95	8284 14.95
8250 16.95	8286
82514.45	8287 6.45
8253 6.90	828824.00
8253-5 7.90	8289 48.95
82554.45	8292

2.5 MHZ	4.0 MHZ
Z80-CPU 3.90	Z80A-CPU 4.29
Z80-CTC 3.95	Z80A-CTC 4.90
Z80-OART 10.95	Z80A-OART 9.95
Z80-DMA 13.95	ZB0A-0MA 12.95
Z80-P10 3.95	Z80A-P10 4.29
Z80-810/0 11.95	Z80A-810/0 12.95
Z80-810/1 11.95	Z80A-810/1 12.95
Z80-810/2 11.95	Z80A-810/2 12,95
Z80-810/9 11,95	ZBOA-810/9 12.95

6.0 MHZ	
Z808-CPU 9.95	ZILOG
Z608-CTC 12.95	Z8132 33.9
Z80B-P10 12.95 Z80B-OART 12.95	Z8671 38.9

#### **DIP SWITCHES**



	POSITION																
5	POSITION																.8
6	<b>POSITION</b>															4	.1
7	POSITION			ì								į.					.5
	POSITION											į					.5

#### 1984 THE IC MASTER

Your ticket to fast and easy IC selections



\$ 89.95

#### INTERFACE CHIPS

8T26					1.54	8T98		٠			.88
68T28					1.84	OM8131					2.90
8195			į.		.88	DP8304					2.24
					.88	088835					1.94
8T97						D\$8836					.98

#### **CRYSTALS**

1.0000	MHz .	3.69	8.0000	MHZ.	 2.69
1.8432	MHz .	3.69	10.0000	MHz.	 2.69
2.0000	MHz .	2.69	10.7386	MHZ.	 2.89
2.0972	MHz .	2.89	12,0000	MHz.	 2.69
2.4578	MHz .	2.69	14.3182	MHz.	 2.69
3.2788	MHz .	2.69	15.0000		
		2.69	16,0000		-
		2.89	17.4300		-
		2.69	18.0000		
		2.69	18.432D		
5.0000	MHŻ.	2.69	19.6608		-
5.0888	MHz .	2.59			
5 1850	MMz	2.69	20.0000	MHZ.	 2.59
		2.69	22,1184	MHZ.	 2.69
		2.69	32.0000	MHZ .	 2.69
		2.69	38,0000	MHz .	 2.69
			48,0000	MHz.	 2.69
			49,4350	MHz	2 69
		2.89			
0.000					 
		32,768 KHz.	1.0	A	

#### CRYSTAL CLOCK OSCILLATORS

PART NO.	FREQUENCY	PRICE
1.000	1.0000 MHz	9.95
1.843	1.8432 MHz	9.95
2.000	2.0000 M Hz	9.95
4.000	4.0000 M Hz	9.95
8.000	8.0000 MMz	9.95
10.000	10.0000 MMz	9.95
16.000	16.0000 MHz	9.95
18.432	18.4320 MHz	9.95
19.560	19.6608 MHz	9.95
20.000	20.0000 MHz	9.95
32.000	32.0000 MHz	9.95

#### **VOLTAGE REGULATORS**

7805T	7905T
78M05C34	7908T
7808T	7912T 8
7812T	7915T
7815T	7924T 8
7824T	7905K 1.4
7805K 1.34	7912K 1.4
7812K 1.34	7915K 1.4
7815K 1.34	7924K 1.4
7824K 1.34	
78L05	79105
78L12	79L12
78115	79L15
78H05K 9.90	LM323K 4.9
78H12K 9.90	UA78840 1.5
	<u> </u>

C,T = TO-220 K = TO-3 L = TO-92

#### IC SOCKETS (1 to 99)

.12 4 pin ST. 14 nin WW. 68 15 pie WW .68 18 pie ST. 20 pin ST. 28 20 pia WW. 1.04 22 pin 8T. 29 22 pin WW 1.34 24 pin WW 1.44 28 pin ST. 39 28 ple WW

40 min ST. 48 ST = Soldertail

WW = Wirewran

40 nin WW

#### ZIF SOCKETS

																			8.90 rce
																			7.90
15	pin	ZIF	-	٠		٠	-	*	×	٠	ř				×				5.90



## DISKETTES 51/4"

**ATHANA** 

SS/SD..... 15.90 SS/DD..... 16.90 DS/DD..... 22.90

SOFT SECTOR with HUB RING

**BULK 51/4" DISKETTES** (NO LABEL)

SS/DD ... 10 for 14.90 100 up......139.00

(Lifetime Warranty)

#### The FLIP SORT™

The new Flip Sort™ has all the fine qualities of the original with some added benefits: a new design and 50% greater capacity. Holds 75 diskettes and the price is now lower than ever- \$16.95



## The Flip Sort PLUS™

The new Flip Sort PLUS™ adds new dimensions to storage. Its smoked acrylic elegance holds over 100 diskettes with all the features you expect from the Flip Sort Family -\$24.95



## IBM ACCESSORIES

MEMORY EXPANSION KIT



4164 150ns 9 for \$45.00

#### MULTIFUNCTION CARD



- 64K to 384K RAM
- Parallel Port
- Sarial Part
- Clock Calendar
- Software included
- 1-Year Warranty

\$249.95

#### **MEMORY CARD**



- Expandable to 512K
- Fully compatible with IBM software
- Fully compatible w/IBM diagnostic utilities
- · Sarial Pert Available
- 1-Year Warranty

\$199.95

#### -VUTEK-

Color • Parallel • Serial Card



- Full bit-mapped Color Graphics
- Printer Port (LPT1, LPT2, LPT3)
- Sertal Port (Com1, Com2)
- · IBM PC, XT and Portable compatible
- Full softwara compatibility
- · Compatible with Lotus 1-2-3, Multi-Plan and Flight Simulator
- Full 2-Year Warranty Parts and Labor

\$299.00

#### DISK DRIVES

Tandon TM 100-2 DS/DD Teac FD-558 DS/DD

KEYBOARD EXTENSION CABLE \$19.95

## APPLE ACCESSORIES

80 Column Apple II+ 149.95
80 Column Apple IIE 129.95
Z80 Apple II+ 89.00
Z80 Apple IIE 89.00
16K Card 39.95
Cooling Fan
Power Supply 74.95
Joystick 29.95
RF Modulator 13.95
Disk Drive 199.00
Controller Card 59.95
Paddles 7.95

#### APPLE COMPATIBLE JOYSTICK

29.95



### COOLING FAN

38 95



#### APPLE COMPATIBLE POWER SUPPLY

74.95



- Powers Apple type systems
- +5V @ 5A +12V @ 3A -5V @ .5A -12V @ .5A
- Includes Instructions

## 16K RAM Card - Apple II+

• 2-Year Warranty



Assembled & Tested .... 39.95

### APPLE COMPATIBLE DISK DRIVE



199.00

- · Shugart mechanism, made in U.S.A.
- Directly replaces Apple Disk II
- Fully compatible with Apple Controller or other Apple compatible controllers
- One Year Warranty

## micromax

VIEWMAX-80

14995

- 80 Col. card for Apple II+
- Video Soft Switch
- Inverse Video
- 2 Year Warranty



VIEWMAX-80e

- 80 Col. card for Apple IIE
- 64K RAM Expandable to 128K

64K RAM Upgrade 40.00



#### Reg. Power Supply Model 4A/PS (99/4) 3 DC Outputs:

12V @ .4A, +5V @ 1.1A -5V @ .2A Highly Filtered

6.95



TERMS: Minimum order \$10.00 For shipping and handling, include \$2.50 for UPS ground or \$3.50 for UPS Blue (air). For each additional air pound, add \$1 for UPS Blue shipping and handling. California residents must include 6% sales tax: Bay area and LA residents include 61/2% sales tax. Prices are subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturers. All merchandise subject to prior sale

CALL for VOLUME Quotes
HOURS: Mon. - Fri. 7:30 to 5:00
Saturdays 10:00 to 3:00

VISIT OUR RETAIL STORE

2100 De La Cruz Blvd. Santa Clara, CA 95050 (408) 988-0697

ALL MERCHANDISE IS 100% GUARANTEED



199.00

159.00

## DADTIAL LISTING ONLY, PLEASE CALL OR WRITE FOR ERFE CATALOG

PAKIIAL LISTING UNLY-	rleade uall	DR WRITE I OR	TREE UNIALUG.
STATIC RAMS	8000	6500	74LS00
2112 256x4 (450ns) 2.99 2114 1024x4 (450ns) 8/9.95 2114-25 1024x4 (250ns) 8/10.95 2114L-4 1024x4 (450ns)(LP) 8/12.95 2114L-3 1024x4 (300ns)(LP) 8/13.45	8035 5.95 8039 5.95 8080 3.95 8085 4.95 8085A-2 11.95	6502 4.95 6520 4.35 6522 6.95 6532 9.95 6551 11.85	74LS00 .24 74LS157 .65 74LS01 .25 74LS158 .59 74LS02 .25 74LS160 .69 74LS03 .25 74LS161 .65
2114L-3 1024x4 (300ns)(LP) 8/13.45 2114L-2 1024x4 (200ns)(LP) 8/13.95 TMM2016-200 2048x8 (200ns) 4.15 TMM2016-150 2048x8 (150ns) 4.95	8087 175.00 8088 29.95 8155 6.95 8155-2 7.95	6502A 6.95 6522A 9.95 6551A 11.95	74LS04 .24 74LS163 .65 74LS05 .25 74LS164 .69 74LS08 .28 74LS165 .95
TMM2016-100 2048x8 (100ns) 6.15 HM6116-4 2048x8 (200ns)(cmos) 4.75 HM6116-3 2048x8 (150ns)(cmos) 4.95	8155-2 7.95 8156 6.95 8748 24.95 8755 24.95	6800 68000-8 49.95	74LS09 .29 74LS166 1.95 74LS10 .25 74LS169 1.75 74LS11 .35 74LS173 .69 74LS12 .35 74LS174 .55
HM6116LP-4 2048x8 (200ns)(cmos)(LP) 5.95 HM6116LP-3 2048x8 (150ns)(cmos)(LP) 6.95 HM6264P-15 8192x8 (150ns)(cmos)(LP) 34.95	8200 8203 39.95	6800 2.95 6802 7.95 6809E 14.95	74LS13 .45 74LS191 .89 74LS14 .59 74LS192 .79 74LS20 .25 74LS193 .79
DYNAMIC RAMS	8205 3.50 8212 1.80 8216 1.75	6809 11.95 6821 2.95 6845 12.95 6850 3.25	74LS21 .29 74LS194 .69 74LS26 .29 74LS195 .69 74LS27 .29 74LS197 .79 74LS32 .29 74LS221 .89
4116-250 16384x1 (250ns) 8/7.95 4116-200 16384x1 (200ns) 8/12.95 4116-150 16384x1 (150ns) 8/14.95	8228 3.49 8237-5 21.95 8243 4.45 8250 10.95	DISK CONTR	74LS32 .29 74LS221 .89 74LS33 .55 74LS240 .95 74LS37 .35 74LS241 .99 74LS38 .35 74LS242 .99
4164-200 65536x1 (200ns)(5v) 9/44.95 4164-150 65536x1 (150ns)(5v) 9/49.00 TMS4164 65536x1 (150ns)(5v) 8.95	8250 10.95 8251 4.49 8253 6.95 8253-5 7.95	1771 15.95 1791 23.95 1793 23.95	74LS40 .25 74LS243 .99 74LS42 .49 74LS244 1.29 74LS47 .75 74LS245 1.49
5v = Single 5 Volt Supply  EPROMS	8255 4.49 8255-5 5.25 8259 6.90	UPD765 19.95	74LS51 .25 74LS251 .59 74LS73 .39 74LS253 .59 74LS74 .35 74LS257 .59
2708     1024x8 (450ns)     3.95       2716     2048x8 (450ns)(5v)     3.95       2716-1     2048x8 (350ns)(5v)     5.95	8259-5 7.50 8272 39.95 8275 29.95 8279 8.95	8T26 1.59 8T28 1.98 DM8131 2.95	74LS75 .39 74LS258 .59 74LS76 .39 74LS259 2.75 74LS85 .69 74LS260 .59 74LS86 .39 74LS266 .55
TMS2532 4096x8 (450ns)(5v) 5.95 2732 4096x8 (450ns)(5v) 4.95 2732-250 4096x8 (250ns)(5v) 8.95 2732-200 4096x8 (200ns)(5v) 11.95	8282 6.50 8284 5.50 8286 6.50	CLOCK CHIPS	74LS90 .55 74LS279 .49 74LS92 .55 74LS280 1.98 74LS93 .55 74LS283 .69 74LS107 .39 74LS290 .89
2732A 4096x8 (250ns)(5v)(21vPGM) 9.95 2732A-2 4096x8 (200ns)(5v)(21vPGM) 13.95 2764 8192x8 (450ns)(5v) 6.95	Z80	MM5314 4.95 MM5369 3.95 MM58167 8.95	74LS109 .39 74LS293 .89 74LS112 .39 74LS299 1.75 74LS122 .45 74LS323 3.50
2764-250 8192x8 (250ns)(5v) 7.95 2764-200 8192x8 (200ns)(5v) 19.95 27128-30 16384x8 (300ns)(5v) 22.95 5v = Single 5 Volt Supply	2.5 Mhz Z80-CPU 3.95 Z80-CTC 3.95 Z80-PIO 3.95	MSM5832 3.95 DATA ACQ	74LS123 .79 74LS365 .49 74LS124 2.90 74LS367 .45 74LS125 .49 74LS368 .45 74LS126 .49 74LS373 1.39
21vPGM = Program at 21 Volts  SPECTRONICS CORPORATION	z80-SIO/0 11.95 4.0 Mhz	ADC0804 3.49 ADC0809 4.49 ADC0817 9.95 DAC0808 2.95	74LS132 .59 74LS374 1.39 74LS136 .39 74LS377 1.39 74LS138 .55 74LS390 1.19
EPROM ERASERS	Z80A-CPU 4.49 Z80A-CTC 4.95 Z80A-DART 9.95 Z80A-PIO 4.49	MC1408L8 2.95 SOUND CHIPS	74LS139 .55 74LS393 1.19 74LS145 1.20 74LS640 2.20 74LS148 1.35 74LS645 2.20 74LS151 .55 74LS670 1.49
Chip Intensity Timer Capacity (uW/Cm²) PE-14 9 8,000 83.00 PE-14T X 9 8,000 119.00 PE-24T X 9 9,600 175.00	Z80A-PIO 4.49 Z80A-SIO/0 12.95 6.0 Mhz Z80B-CPU 9.95	76477 3.95 76488 5.95 AY3-8910 12.95 SSI263 39.95	74LS151 .55 74LS682 3.20 74LS154 1.90 74LS688 2.40 74LS155 .69 81LS95 1.49 74LS156 .69 25LS2521 2.80
74000	A A A A HICH	Trough	LINEAD

	74	00		745	00			TECH**	$\star\star$		LINE		
7400	.19	7492	.50	74500	.32		C02	\$12.95		TL084	2.19	NE564	2.95
7400	.19	7493	.35	74502	.35			N OF THE 1 MH	z	LM301	.34	LM565	.99
7402	.19	74100	1.75	74504	.35	65	02 MICRO	PROCESSOR		LM307	.45	LM566	1.49
7403	.19	74107	.30	74805	.35	* LOW POWE	R-8ma OPE	RATION, 10 MIC	ROAMP	LM308	.69	NE592	.98
7404	.19	74116	1.55	74508	.35	STANDBY				LM309K	1.25	LM733	.98
7405	25	74121	.29	74510	.35	. SINGLE PO	WER SUPP	LY: 3-6 VOLTS		LM310	1.75	LM741	.35
7406	.29	74122	.45	74511	.35	. 27 NEW IN:	STUCTION	S AND ADDRESS	MODES	LM311	.64	LM747	.69
7407	.29	74123	.49	74520	.35			<b>IBILITY WITH 65</b>		LM317T	1.19	LM1310	1.49
7408	.24	74125	.45	74532	.40			MORY LOCK FEA	TURES	LM317K	3.95	MC1330	1.69
7409	.19	74126	.45	74537	.88	. USED IN A				LM318	1.49	MC1372	6.95
7410	.19	74132	.45	74574	.50	444.	T CDUT	LIGHT★★	441	LM323K	4.95	LM1458 LM1488	.59 .69
7411	.25	74145	.60	74586	.50	XXX	X OF UI	LIUIII X X	A A A	LM324	.59	LM1488 LM1489	.69
7413	.35	74148	1.20	745112	.50	The second second	100	The second second		LM331	3.95 1.19	LM1489	.85
7414	.49	74150	1.35	745124	2.75	CODYOT	410	UART	c V	LM334 LM335	1.19	LM1496	2.37
7416	.25	74151	.55	745132	1.24	CRYST	ALS I	UANI	3	LM335	1.75	LM1812	8.25
7417	.25	74153	.55	745133	.45	00 70044	1.95	AY5-1013	3.95	LM337T	1.95	LM1889	1.95
7420	.19	74154	1.25	745138	.85	32.768Khs	3.95	AY3-1015	6.95	LM3371	3.95	ULN2003	2.49
7421	.35	74155	.75	745139	.85	1.0Mhz	3.95	TR1602	3.95	LM338K	.99	XR2006	3.75
7425	.29	74157	.55	745140	.55 .95	1.8432 2.0	2.95	2651	8.95	LM348	.99	XR2211	5.25
7427	.29	74159	1.65	74S151 74S153	.95	2.4576	2.95	IM6402	7.95	LM350K	4.95	CA3146	1.85
7430	.19	74161	.69	745153	.95	3.579545	2.95			LF351	.60	LM3900	.59
7432	.29	74163	.69	745157	.95	4.0	2.95	BIT-RA	ILE I	LF353	1.00	LM3911	2.25
7437	.29	74164	.85	745156	1.95	5.0	2.95	GENERA'	TORS I	LF356	1.10	LM3914	3.95
7438	.29	74165	.85	745163	1.95	5.0688	2.95	GENERA	ONS	LF357	1.40	MC4024	3.95
7442	.49	74166	1.00	745163	.95	6.0	2.95	BR1941	11.95	LM 358	.69	MC4044	4.50
7445	.69	74173	.75	745174	.95	6.144	2.95	4702	12.95	LM359	1.79	RC4136	1.25
7447	.69	74174	.89	745240	2.20	8.0	2.95	COM8116	10.95	LM377	1.95	75150	1.95
7448	.69	74175	.89	745240	2.20	10.0	2.95	14411	11.95	LM383	1.95	75154	1.95
7473	.34	74185	2.00	745244	2.20	10.738635	2.95			LM386	.89	75188	1.25
7474	.33	74192	.79 .79	745280	1.95	14.31818	2.95	MISC	· .	LM393	1.29	75189	1.25
7475	.45	74193	.79	745287	1.90	15.0	2.95	3242	7.95	LM393	1.29	75451	.39
7476	.35	74194 74259	2.25	745288	1.90	16.0	2.95	MC3470	4.95	TL497	3.25	75453	.39
7483	.50 .59	74259	.65	745373	2.45	17.430	2.95	AY5-3600 PRO	11.95	NE555	.34	75492	.79
7485	2.15	74367	.65	745374	2.45	18.432	2.95	HD46505SP	15.95	NE556	.65		
7489	.35	74368	1.35	745471	4.95	20.0	2.95	CRT5027	19.95	T : TO		K : TO	0.3
7490	.35	74393	1.35										

VISIT OUR NEW, EXPANDED RETAIL STORE AT 1256 SOUTH BASCOM IN SAN JOSE HOURS: M-W-F, 9-5 T-TH., 9-9 SAT., 10-3

JDR Microdevices

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING TERMS: Minimum order \$10. For shipping and handling inclusions.

Copyright 1985 JDR Microdevices FAX (408) 275-8415

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING

TERMS: Manimum order \$10. For shipping and handling include \$2.50 for UPS Ground and \$3.50 for UPS Air. Orders over 1 lb. and torsign orders may require additional shipping charges — please 800-538-5000 • 800-662-6279 (CA)

(408) 995-5430 • Telex 171-110

Payright 1985 JDR Microdrylces FAX (408) 275-8415

## PARTIAL LISTING ONLY- PLEASE CALL OR WRITE FOR FREE CATALOG.

#### CAPACITORS **ELECTROLYTIC**

RADIAL		A	CIAL	
10 47 100	16v .18		16v 50v 15v	.14
5	Ov MON	OLIT	HIC	:
.01uf .047	.14 .15	.1 .47		.05
	50v	DISC		
10pf 22 25 27 33 47 56 68 82 100 220 330	.05 .05 .05 .05 .05 .05 .05 .05	.001s .0015 .0022 .005 .01	if	.05 .05 .05 .05 .05 .05 .05

#### **ACCESORIES & PERIPHERALS FOR IBM**

MAXIMIZER Memory Multifunction	259.95
HAYES SMARTMODEM 1200B	419.95
PC PEACOCK Color Display Adaptor	239.95
130W POWER S JPPLY	175.00
PROTOTYPE CARD	27.95
PROTOTYPE CARD With Decoding	29.95
FOR APPLE	
JDR 16K RAM CARD	39.95
BAL-500 1/2 Ht. Disk Drive, Teac Mechanism	169.95
MITAC AD-1 Ful Height, Shugart Mechanism	179.95
DISK CONTROLLER CARD	49.95
OMNIGRAPH Parallel Graphics Card	79.95
VIEWMAX-80 80 Column For Apple III	159.95
VIEWMAX-80e 30 Column For Apple IIe	129.95
THUNDERCLOCK Official PRODOS Clock	129.95
KRAFT JOYSTICK	39.95
60W POWER SUPPLY	49.95

# **BARGAIN HUNTERS CORNER**

2 LEVEL WIRE WILD SOCKETS
THESE SOCIETS LAVE SO LEE SOUS A LITTLE
SHORTER OF THAN THE STANDA OF LEVEL WIRE
WIND SOCKETS WITH 67

	1-99 100-UP
3 PIN WW-2	.40 .35
14 PIN WW-2	.45 .39
15 PIN WW-2	A5
20 PIN WW-2	.75 .59
22 PIN WW-2	.50 .39
24 PIN WW-2	.89 .75
28 PIN WW 2	.89 .75
40 PfN WW-2	.89
SPECIALS	FND 1/31/85

## .07

SPECIALS	ON RAL	ASS CAPS
.01uf disc	50v	100/6.00
1uf disc	12v	100/8.00
.01uf mono	50v	100/12.00
1uf mono	50v	100/15.00

MISCELLANEOUS	
ZENITH ZVM-123 15 MHz Green Monitor	105.00
NEC JB12C1M 20 MHz Green Monitor	169.00
BMC BM-AU9151U Comp. 13" Color Monitor	279.00
BMC BX-80 PRINTER	249.00
NASHUA DISKETTES SS/SD Box of 10	19.95
VERBATIM DATALIFE DISKETTES DS/DD	34.95
DISKETTE FILE Holds 70 Diskettes	16.99

#### 514" DISK DRIVES

3/4 DISIN	DHIVE	>
TANDON TM100-2	DS/DD	199.00
SHLGART SA400L	SS/DD	199.95
MPI B52	DS/DD	139.95
TEAC FD55B 1/2 Ht.	DS/DD	159.00
TEAC FD55F 1/2 Ht.	DS/Quad	200.00

#### 8" DISK DRIVES

SIEMENS	FD200-8	DS/DD	195.00
SIEMENS	FD100-8	SS/DD	149.95

#### IC SOCKETS/DIP CONNECTORS

	LOW PROFILE SOLDERTAIL		3 LE	VEL	ZERO INSERTION	COMPONENT	IDC PLUG RIBBON CABLE
1	1-99pcs.	100&up	1-99pcs.	100&up	ZIFxx	ICCxx	IDPxx
8	.13	.11	.59	.49	1.00	.65	
14	.15	.12	.69	.52	5.95	.75	1.45
16	.17	.13	.69	.58	5.95	.85	1.65
18	.20	.18	.99	.90		1.00	
20	.29	.27	1.09	.98		1.25	840
22	.30	.27	1.39	1.28		1.25	
24	.30	.27	1.49	1.35	7.95	1.35	2.50
28	.40	.32	1.69	1.49	8.95	1.50	
40	.49	.39	1.99	1.80	10.95	2.10	4.15
64	4.25		***			***	0.00

#### SWITCHING POWER SUPPLIES KEPCO/TDK MODEL MRM174KF MODEL AA11190

ODEL MINISTER	INODEL AATTI.
+5V @ 5A	+5V @ 4A
+12V @ 2A	+12V @ 2.5A
+12V @ 2.8A	-5V @ .25A
- 2V @ .5A	-12V @ .30A
49.95	39.95

#### **IDC CONNECTORS**

	00050 04			CONTACT		
DESCRIPTION	ORDER BY	20	26	34	40	50
RIBBON HEADER SOCKET	IDSxx	1.86	2.43	3.15	3.73	4.65
RIBBON EDGE CARD	IDExx	2.36	2.65	3.25	3.80	4.74

ORDERING INSTRUCTIONS: Insert the number of contacts in the position marked "xx" of the "order by" part number listed. EXMAMPLE: A 20 plr ribbon edge card would be IDE 20.

#### LIGHT EMITTING DIODES JUMBO **DISPLAYS**

	1-99	100-up	MAN-72	CA .3"	.99
RED	.10	.09	MAN-74	CC .3"	.99
GREEN	.18	.15	FND-500	CC .5"	1.49
YELLOW	.18	15	FND-507	CA .5"	1.49

#### **D-SUBMINIATURE**

DESCRIPTION		ORDER BY	CONTACTS			
DESCRIPTION		ONDERBY	9	15	25	37
	MALE	DBxxP	2.08	2.69	2.50	4.80
SOLDER CUPS	FEMALE	DBxxS	2.66	3.63	3.25	7.11
RT. ANGLE	MALE	DBxxPR	1.65	2.20	3.00	4.83
PC SOLDER	FEMALE	DBxxSR	2.18	3.03	4.42	6.19
IDC	MALE	IDBxxP	3.37	4.70	6.23	9.22
RIBBON CABLE	FEMALE	IDBxxS	3.69	5.13	6.84	10.08
HOODS	BLACK	HOOD-B			1.25	***
	GREY	HOOD	1.60	1.60	1.25	2.95

MOUNTING HARDWARE - \$1,00
FOR ORDERING INSTRUCTIONS, SEE IDC CON V. ABOVE

## 9000

9334	2.50
9368	3.95
9602	1.50
INTER	RSIL
CL7107	12.95
CL7660	2.95
CL8038	3.95
DID COLUE	FOLLEC

4 position .85 .90 .95 6 position 7 position 7 position 8 position

#### **TRANSISTORS**

ZNZZZZ	.25 PN2307	.23
PN2222	.10 2N3055	.79
2N2905	.50 2N3904	.10
2N29C7	.25 2N3906	.10
	DISCRETE	
	DISCHLIL	
1N751	5.1v zener	.25
1N755	12.0v zener	.25
1N4148	(1N914) switching	25/1.00
1N40C4	400 PIV rectifier	10/1.00
KBP02	200PIV 1.5a bridge	.45
4N33	OPTO-ISOLATOR	1.75

#### RIBBON CABLE

CONTACTS	SINGLE	COLOR	COLOR CODE	
CONTACTS	11	10'	1'	10"
25	.75	6.60	1.32	11.80
34	.98	8.80	1.65	14.50
50	1.38	12.10	2.50	22.00

#### **36 PIN CENTRONICS**

CEN36 MALE SOLDER CUP	7.95
IDCEN36 MALE RIBBON CABLE	8.95
IDCEN36F FEMALE RIBBON CABLE	8.95

#### **VOLTAGE** DECLII ATORS

NEG	OL	AIUI	13
7£05T	.75	7915T	.85
7EM05C	.35	7805K	1.39
7E 08T	.75	78H05K	9.95
7E 12T	.75	7812K	1.39
7£ 15T	.75	7912K	1.49
7E 24T	.85	78L05	.69
75-05T	.85	79L05	.79
75 12T	.85	79L12	.79
C, T=TO-2	20, K	=TO-3, L=T	0-92

## **CMOS**

4001	.25	4)27	.45	4066	.39	4538	1.95
4002	.25	4 ) 28	.69	4069	.29	4543	1.19
4011	.25	4 ) 29	.79	4070	.35	4553	5.79
4012	.25	4 )40	.75	4071	.29	4584	.75
4013	.38	4)42	.69	4081	.29	74C00	.35
4015	.39	4 346	.85	4082	.29	74C04	.35
4016	.39	4)47	.95	4093	.49	74C14	.59
4017	.69	4 ) 4 9	.35	4503	.65	74C74	.65
4018	.79	4 350	.35	4511	.85	74C906	.95
4020	.75	4 351	.79	4518	.89	74C922	4.49
4023	.29	4 )53	.79	4520	.79	74C923	4.95
4024	.65	4 360	.89	4528	1.19	74C926	7.95



Your friends at 9DR would like to wisk you and your family a pleasant holiday season, and a prosperous New Year.



VISA

Copyrigh: 1985 JDR Microdevices

#### ECG®/GE®/SK® **POPULAR** HORIZONTAL OUTPUT TRIPLERS MIN. 3 PC./TYPE TRANSISTORS **500**/SK3304..... 9.**50** MIN. 5 PC. PER TYPE 523/SK3306..... 9.95 165 . . . . . . . . 2.25 **526A**/GE521......**9.95 528**/SK3906......**11.75** 238.....2.25 283 . . . . . . . . . 2.75 **529**/SK3307.....10.75 2SC1308K .... 2,45 556/sk3905......14.95 557/sk3904......14.95 2SD1341P .... 2.25 POPULAR **AUDIO POWER** DIODES MIN. 100 PC. PER TYPE **TRANSISTORS** 152 ... 30¢ 153 ... 30¢ 196 ... 49¢ 197 ... 59¢ 291 ... 49¢ 1 MIN. 10 PC. PER TYPE 292 ... 49¢

SE5020 35¢ ea. RF/IF OSSCILATOR, MIN. 10 PC. 712/LA1365 75¢ ea.

TV Sound/IF/FM/Det. Min.10 Pc. William

SPECIAL OF THE MONTH 152 ... 25¢ MIN. 10 PC.

SPECTACULAR SAVINGSII
ON REPLACEMENT FOR ECG® TYPES MIN. 10 PC. PER TYPE 85. .21 102A .35 108 .18 121 .1.20 171 184 185 130 ... 59 154 ... 75 157 ... 49 159 ... 16 191 198 199 234 .18 .19 .29 186 187 188 .88 287 288 162 .... 2.25 163A .... 2.35 189 . .55

FOR A COMPLETE LIST CALL OR WRITE - C.O.D. Orders Welcome (Min. Order \$25)

DIGITRON ELECTRONICS

110 HILLSIDE AVENUE, SPRINGFIELD, NEW JERSEY 07081

TOIL Proc 800-526-4928 IN NJ 201-379-8016 Telex 138441

PRICES SUBJECT TO CHANGE WITHOUT NOTICE. OFFER GOOD WHILE SUPPLY LASTS.

ECG Is a Trade Mark of Philips ECG.

Digitron Electronics is not associated in any way with Philips ECG.

CIRCLE 57 ON FREE INFORMATION CARD

508 Central Ave ld. N.J. 07090 (201) 654-6008

UHF-TV PREAMP	
(As featured in Radio Electronics March/ May articles, 1982)	
This inexpensive antenna mounted pre-	
amp can add more than 25 dB of gain to	

amp can add more than 25 dB of gain to your system. Lots of satisfied customers and repeat orders for this high quality kit, which includes all component parts, PC BD, Casa, Power Supply and Balun \$34.50 Assembled Version \$57.50

APPLE Heart Rate Monitor KIT-\$39.95
4164 DYNAMIC RAMINEC B4 DATE CODE, PRIME!
IDEAL FOR 18H PC'S & CLONES 4.50
1. ONH: CRYSTALS
JUMBO RED LED'S-DIFFUSED LENS, PRIME (TI)
NO COSMETIC REJECTS. ALL 1005 15/1.00
100/6.00, 1,000/57.50,
COILS FOR RADIO ELEC'S FEB 84 TV PROJECT,
TOKO 8'S T-1,T-2, L-1(12uH) & L-2(,071uH)
COMPLETE SET OF ALL 3 COILS 8.30
MC1330- PRIME (MOTO)
BF0-05 TRANS
Z-80A 510/0- SERIAL 1/0:ZILOG1 2.95
Z-80A DMA- DIRECT MEM ACCESS(ZILOS), 7.95 555 TIMERS- PRIME, (TI)
# PIN IC SOCKETS
1,000uf 50v RADIAL INICHICONI 4/1.00
47uF 25V RADIAL INICHICONI 10/1.00
SOPHISTICATED SOUND ACTIVATED SWITCH WITH
POT. SENSITIVITY CONTROL "BUG" TYPE.
REACTS TO HIGH RISING SOUNDS W/DATAL 3.50
TEXAS INST/FUTABA KEYBOARD- INC/BAIA FOR
PINS MADE WHEN EACH KEY DEPRESSED 3.00
CLOCK MODULE- CRYSTAL CONTROLLED, GREEN
DISPLAY/12VDC/TIME SET SWITCHES/DATA-5.00
POTS- 1 NEG, LIMEAR TAPER 5/1.00
DIP SWITCH- 3 POSITION 10/1-00
MOTION DETECTOR BOARDS-92 EACH 7/10.00
MOTION DETECTOR IC'S (ULN223213/02, 20/010
BLACK, PLASTIC PROJECT BOX FOR ABOVE-2.50
EXTENSIVE CONSTRUCTION ARTICLE FOR DET. 01
1,000 PC RESISTOR ASS'T(30 VALUES)[/2W-63
78LOS VOLTAGE RESULATORS 10/1.00
.22uF SOV MINI DISCS 20/1.00
3200uF SOV THIST LOCK (IDEAL FOR POWER
BUPPLIES)
.3344 100V DIP MYLAR 10/1.00
4.7u+ 40V RADIAL
TRIM POTS-PIHER PTIOV, HOR, 3/8"-MIX/MATCH,
100 DHM, 1K, 10K, 25K, 50K, 100K, 200K 4/1.00
10uH COIL (FIXED)

LH380(ULH2280)
BERN TO-S HIGH QUALITY HEAT SINKS, 10/1.00
* TO-18 * * * 10/1.00
MOLEX PINS- 7 PIN/STRIP-900/4.00,1,000/84
HEAT SENSITIVE SWITCHES 10/1.00
2N5 308
KEYBOARD PUSH BUTTON TOPS30/1.00
LED HOUNTING CLIPS/RINGS
ZENER DIODES- 20V 1 AMP
IN4002'820/1.00
ZENITH TY REPLACEMENT IC SPECIAL DI EACH
221-42, 221-43, 221-45, 221-48, 221-49,
221-79, 221-87, 221-96, 221-104, 221-105
221-10e
221-132 2.50
221-140 (INDUSTRY REPLACEMENT #845) 4.90
REPLACEMENT #844(CA3217),28 PIN 1C 8.90
25C11728:TOSHIBA- HORIZ, OUTPUT! 1.95
3.579545MHz COLOR BURST CRYSTAL 85
2732 EPROMS 4,95
SIGNALMAN MARK 1 MODER+300 BAUDI 849
GORILLA HIGH RESOLUTION GREEN MONITOR 679
AHBER - 884
7-12UH ADJUSTABLE COIL 2.50
HIGH BUALITY COOLING FAMILPAROTOR:
TRANSFORMERS- 6.3V 1.2AMP
14H FIXED CHOKE, RFC-102 3/1 00 3,3004F 30V ANIAL 2/1 00
3.300uf 30V ANIAL 2/1 00
22AM9 & 27AWG WIRE 50"/1,00
CRYSTAL - 2940.000HC
VOLIGHE-MOIE SWITCHING REGULATOR HIT
THIS PROJECT FEATURES ADJUSTABLE DC/DC.
OUTPUT- 1-124 TO 1+130VBC, STEP UP, BOWN
AND INVERSION HODES
CHIP CAPS- SET OF 4,2 EACH 2.763.384-2.50
ZENER DIODES- 13V IW. OLASS 30/1.00
BNC "T" CONNECTOR (AMPHENOLING-274 . 95
BNC 'T' CONNECTOR (AMPHENDLING-274 95
4-32×1/4,3/8,1/2- 4.50
GRAIN O WHEAT LAMPS, CLEAR 3/1.00
RIBBON CABLE, 26 CONDUCTOR, 28 AWG50/FT
* 50 * * 75/FT
11,000uF 40V COMPUTER GRADEIMALLORY1-Z.00
2N3055'S IPRIME TIL 2/1.00
FREQUENCY COUNTER IC-INTERSIL 7225- 9.00
CRYSIAL-CONTROLLED PULSE GENERATOR KIT
YOU PICK THE FREQUENCY FROM I HE TO ANY
MULTIPLE OF 10 UP TO 1 MHE ISAME KIT AS
FEATURED IN RADIO ELEC'S SPECIAL PROJECTS
MAGAZINEI SPRING- 84 39.95

MICRO-CONTROLLER BOARD (Kit/899.50)

Terms: MICRO-MART accepts Visa, MC and telephone COD's. Minimum order \$10.00. Shipping—U.S. orders, \$2.00. Canada and other countries \$3.50 (includes ins.). Shipping rate adjusted where applicable. NJ residents add. 6% sales tax.

MICRO-MART ● 508 CENTRAL AVE., WESTFIELD, NJ 07090 ● (201) \$54-6008

DISK DRIVE SPECIAL: Shugart #SA 200 51/4 In. 2/3 Height. New In Box. 40 Track, SS-DD. Compare At Up To \$159 Ea. Our Price \$69.95 or Two For \$125. Limited Qty.

THE NEW ZRT-80

CRT TERMINAL BOARD! A LOW COST Z-80 BASED SINGLE BOARD THAT ONLY NEEDS AN ASCII KEYBOARD, POWER SUPPLY, AND VIDEO MONITOR TO MAKE A COMPLETE CRT TERMINAL. USE AS A COMPUTER CONSOLE. OR WITH A MODEM FOR USE WITH ANY OF THE PHONE-LINE COMPUTER

SERVICES.

COPY UPON

WARRANTY.

LIMITED

OUR

OF

TERMS

SUBJECT TO

Uses a Z60A and 6345 CRT Controller for powerful video capabilities

RS232 at 16 BAUD Rates from 75 to 19,200. 24 x 80 standard format (60 Hz).

Optional formats from 24 x 80 (50 Hz) to 64 lines x 96 characters (60 Hz).

Higher density formats require up to 3 additional 2K x 8 6116 RAMS.

 Uses N.S. INS 8250 BAUD Rate
Gen. and USART combo IC.
 3 Terminal Emulation Modes which are Dip Switch selectable. These include the LSI-ADM3A, the Heath H-19, and the Beehive.
Composite or Split Video.

Any polarity of video or sync. Inverse Video Capability.
Small Size: 6.5 x 9 inches.

. Upper & lower case with descenders.

\* 7 x 9 Character Matrix.
\* Requires Par. ASCII keyboard.

SOURCE DISK! (CP/M COMPATIBLE)

**BLANK PCB WITH 2716** CHAR. ROM, 2732 MON. ROM

\$4995

SOURCE DISKETTE - ADD \$10 SET OF 2 CRYSTALS - ADD \$7.50

\$995 (COMPLETE KIT. 2K VIDEO RAM) (COMPLETE KIT.

## **Digital Research Computers**

P.O. BOX 461565R • GARLAND, TEXAS 75046 • (214) 225-2309

Call or write for a free catalog on Z-80 or 6809 Single Board Computers, SS-50 Boards, and other S-100 products.

TERMS: Add \$3.00 postage. We pay balance. Orders under \$15 add 75¢ handling. No C.O.D. We accept Visa and MasterCard. Texas Res. add 5-1/8% Tax, Foreign orders (except Canada) add 20% P & H. Orders over \$50 add 85¢ for insurance.

#### **ELECTRONIC PARTS - KITS - ACCESSORIES** RETAIL/WHOLESALE/SURPLUS HOBBIESTS - EXPERIMENTERS - TECHNICIANS - REPAIRMEN

	CAPACITORS - All types & values
	IC'S - Popular linear & CMOS
	POTS - PC mt., pannel mt., etc
	SWITCHES - Mini-toggle (AMF 5A/120 vac)
	SPDT 1.00 ea.
	DPDT 1.50 ea.
	REGULATORS - 7851 (8.5V), 7812,
	7815, 7818
	CHOKES - 15µh, 33µh, 100µh, 1mh50 ea.
1	OUTDOOR MATCHING
	TRANSFORMER 2.00 ea.
	A-B SWITCH

**UHF ANTENNA 4 BAY BOW-TIE** 

BEST-BUY FOR UNDER \$50.00!

\$14.95 ea./3 FOR \$40.00 (Mounting Hardware Included)



\$1.50 ea./3 for \$4.00

\$1.00 ea./3 for \$2.50

\$4.00 ea./3 for \$10.00

UHF/VHF/FMANTENNA AMPLIFIER (With FM Trap) HIGH GAIN! A D ... 9. (25 DB AVERAGE) for Male or 1

\*\*\* A GREAT BUY! \*\*\* \$22.95 ea./3 FOR \$60.00 SPEAKERS:

3"×5" (8 Ohm, 2W) 3" (Round) TRANSFORMERS:

120/20 vac 120/12 VDC Wallnack STERED AMP HORRY KIT (GREAT FOR TINKERING)

\$4.00 ea./3 for \$10.00

\$7.00 ea MUCH, MUCH, MORE!!!!

NEW DEAL ELECTRONICS 3462 N. PULASKI CHICAGO, IL. 60641 (312) 286-0908

#### **CURRENT SPECIALS**

SEMICONDUCTORS: 1330 Generic (No mrking.) .80 ea. LM386N .50 ea. or \$35.00/100 NF564 2.00 ea. 565 Generic .70 ea 1349 Generic 1.00 ea. 7815(House #).50 ea.or \$35.00/100 **CAPACITORS:** 470 µf Rad. Lytic .50 ea. or \$10/100 2200 uf Axial Litic 1.00 ea. 50 pf Trimcap .65 ea. or \$50/100 RESISTORS/POTS: Resistor assortments (mixed values) \$5,00/100 1 Watt . . \$10.00/100 25K CRL Vert. PC Trimpots .30 ea. 20K Pot (Bourns 3386.type) .50 ea. 5K Pannel Mt. Pot + Knob .75 ea.

**MUCH MORE!!!** SEND FOR FREE FLYER

#### X-TRA SPECIALS

Indoor Matching Transformer .50 ea.

ANY SIZE OROER PUTS YOU ON OUR MAILING LIST. YOU WILL RECEIVE OUR UPDATED CATALOGS FREE OF CHARGE OR OBLIGATION.

#### **TERMS**

Check, Money Order or COD Minimum Order \$10.00 Add \$2.50 S&H/\$4.00 COD IL. add 7% Sales Tax (Allow 2-3 wks. for personal checks) Phone 10 AM - 5 PM Chicago Time

MAIL ORDER PRICING ONLY

6800

\$5,000,000 SALE CELEBRATION SAVE NOW AT NEW LOW PRICES! 9th Year Anniversary SALE!

Corporate Buyers ...

NESSO 24 NESSO 25 NES

VOLTAGE REGULATORS

DISKETTES

\$1.19 -0/1000 \$1.35 -0/250

\$1.5500/25

905T Also 6, 12, 15, 24V SPECIA

'IBM PC®'

Hub Rings Tyvac Cover Major Mfgr.

THEAD CLEANING KIT

S" "HEAD CLEANING KIT

"" "HEAD CLEANING KIT

"" "HEAD CLEANING KIT

"" "HEAD CLEANING KIT

"" "HEAD CLEANING KIT

SH DISKETTE HOLDER EXPANSION MEMORY 64K UPGRADE (Set of 9)\$39.95

256K RAMS (258Kx1) \$24.95 CABLES/ACCESSORIES

SPECIALS OF THE MONTH FARADAY 6400/64K MS-DOS Motherboard PERFECT AB Switch (Parallel)

TELEDATA Modem for VIC20/6~

APPLE IIe Keyboard

69.95

49 95

LM3916
LM3916
IMC4004
IMC4004
IMC4004
IMC4004
IMC4004
IMC4004
IMC4003
CA3003
CA

Call For Volume Quotes!

1985 CATALOG **SINCE 1976** Send \$1.00

A-F-CE COMPANIE
ALS CPAN 3.0 PLUS CARD. SALE \$199.00
COEX 18K RAM CARD SALE 39.95
COEX PAR PRINTER CARD W/CABLE . 49 95
COEK 80 COL EXT 84K CARD. SALE 99.95
IS PKASO (IO (II lie)
KENNSINGTON SYSTEM SAVER
KENNSINGTON PC SAVER
KRAFT JOYSTICK
MCT SPEED DEMON 249.95
MICROSOFT Z-80 SOFTGARD . 247 95
GRAPPLER PLUS 119 95

BLE PERIPHERALS	
BUFFERED GRAPPLER	\$349.95
GRAPPLER SUPER SERIAL . SALE	\$119.95
VIDEO 7 RGB lic I/O	189.95
APPLE IIC SERIAL CABLE	36 95
APPLE III KEYBOARD	.49.95
APPLE MIN POWER SUPPLY	59 95
APPLE II/III DISK CONTROLLER.	49 95
APPLE HITH COOLING FAN SYSTEM	19.95
STREET ECHO II SPEECH SYSTEM	99.95
TITAN ACCELERATOR II CARD	449.95
WIZARD BO COLUMN CARD . SALE	99.00

KENNSINGTON PC SAVER         .39 98           KRAFT JOYSTICK         .38 95           MCT SPEED DEMON         .249 95           MICROSOFT 2-80 SOFTCARO         .247 95           GRAPPLER PLUS         .119 95	APPLE II/III DISK CONTROLLER. 49 95 APPLE II/III COOLING FAN SYSTEM 49 95 ATREET ECHO II SPEECH SYSTEM 90 95 TITAN ACCELERATOR II CARD 449 95 WIZARD 80 COLUMN CARD . SALE 99 00
FARADAY IBM PC® Competible CPU Board w/64K, MS DOS \$349.95	MOST MAJOR LINES IN STOCK CALL TOLL FREE
IBM PC H	ARDWARE
ABT "COMBOPILUS" 6MK \$199.00 SIGMA "BANDEZE" 6MK 249 P5 SIGMA DISK CONTROLLER. 168 96 HARD DISK CONTROLLER. 249 P5 10 MB INTERNAL HARD DISK .706 00 10 MB EXTERNAL HARD DISK .706 00 15 MB INTERNAL ENCORPTUS .706 00 15 MB INTERNAL EN	MOUSE SYSTEMS MOUSE WISW 2 144,95 COLADBOARD WHAT 283,00 TECMAR GRAPHICS MASTER 580,00 TECMAR GRAPHICS MASTER 580,00 TECMAR GRAPHICS MASTER 580,00 TECMAR GRAPHICS MASTER 580,00 TECMAR GRAPHICS TO 580,00 TECMAR GRAPHICS TO 580,00 TECMAR GRAPHICS TO 580,00 TECMAR GRAPHICS TO 580,00 TEMBERS TO 580,00 T
PRINTERS	S-100 SALE ITEMS
BROTHER HR 1978 (120cm)	PLUS MAJOR DEM PURCHASE WHILE SUPPLY LASTS ALL NEW, SOME W/O DOCUMENTATION TUART BOARD SALE 96,95
SPECIAL STAR STX:80 THERMAL 129 00 NEC 8027A PORTABLE PRINTER 369 00 PANASONIC 1091 SALE 359 00	PN2222A 7/81.00   2N3904   11/81.00   PN2386A 5/1.00   2N3906   11/1.00   PN918   3/1.00   11/29A   2/1.00   2N2218A 45   11/20A   2/1.00

0	PN2222A	7/\$1,00	2N3904	11/81 0
٥	PN2389A	5/1 00	2N3906	11/1 0
0	PN918	3/1 00	TIP29A	2/1.0
۱.	2N2218A	45	TIP30A	2/1.0
	2N2219A	.45	TIP31A	2/1 2
1	2N2905	.45	TIP32A	2/1.2
	2N2907	.25	1N414B	25/1.0
ı	2N3055	.89	1N751	5/1.0
ı	2N3565	4/1,00	1N4002	12/10
ı	2N3636	4/1.00	1N4004	10/1 0
ı	2N3772	1,69		
Į	0	PTO IS	DLATOR	S
I	MCT-2	\$ ,59	4N33	3.8

	Ambo Red		8	-99	3	100
		LED L	AM S			ı
١	4N28	89				
П	4N27	65	SPX33			20
1	4N26	.86	TIL117			79
1	MCA-255	1.09	4N36			98
1	MCT-66	.55	4N37		1	26
1	MCT-8	1 39	4N35		- 1	25

No.		1:09		100
16	Ambo Red	\$ 09	s	G8
35	Jumbo Green	.17		18
95	Jumbo Yellow	17		-11
95	Mini Stze Red	.10		00
95	Mini Size Green	19		10
100	Mini Size Yellow	19		16
6	EDGE CON	NECTORS		
٥	2000	1-99		100

S SMARTMODEM 300 (EXT)	229 95	Jumbo Yallow	17	15
IOMODEM APPLE He	249.95	Mini Stze Red	.10	09
METHEUS 1200M (MACINTOSH)	489 95	Mini Size Green	19	16
METHEUS 1200 (PC EXT)	359.95	Mini Size Yellow	19	18
ATION ACCESS 1-2-3	389.95	Annual Control of the		
COMMUNICATIONS SYSTEM	419.96	EDGE CON	NECTORS	
E COMP, LOW COST MODEM (3)	00) 49.96	2 7000	1-90	100
HARD DISKS		3-100 ST	\$3.95	\$3.25
	_	S-100 WW	4.78	4,10
SATE ST508 5Mb	\$299.00	44 Pin ST	2.75	2.60
1 OMb	Cell	44 Pm WW	4.76	4.25
15Mb	Call	72 Pm ST	6.60	8.10
22Mb	Celt	72 Pm WW	7 25	8.95
AME 10Mb	Cell	12 110 1110	, 20	0.00
ME 15Mb	Coll	D-SUBMIN	MATURE	

CAPACITY HARD DRIVES		1-24	25
	0825S (Female	83 10	\$2.90
	DB25P (Mare)	2 40	2,29
SUPER SAVER	Hood \$1.25	Mtg H/W \$ 99	
*****	DE37S (Female)	\$5.95	\$5.75
HARD	DE37P (Male)	5 25	5,10
ERAL DISK	Hood \$1.75	Mtg H/W 8 ,00	
SAMP DISK	DD50S (Female)	\$8.95	\$8.85
U \$199.00 I	DD50P (Male)	8.00	5,75
5Mb \$199.00	Hood \$3.25	Mtp HAV \$ 99	
NO RETURNS AT THIS PRICE	OTHER STYLE	S IN CATALOG)	

DISK DRIVE	S
TEAC 568	\$149.95
MITSUBISHI 4851	149.95
SHUGART 455	159 95
TANDON TM100-2	159.95
B" DISK DRIVES	
SHUGARIT BOTR	\$209.95
SIEMENS FDD100-6	129.95
SIEMENS FDD200-8 DS/DD	196.00
MITS M2894	439 P5
MITS M2896 WHI.	439.95
TANDON 848E VIHIL	369.95
QUME 242 WHL	399.95

MONITORS 300G (GREEN) 300A (AMBER) 310A (IBM AMI

MODEMS IP "PC INTELLIMODEM" (INT SMARTMODEM 1200 (EXT) SMARTMODEM 12008 (INT) SMARTMODEM 300 (EXT)

CALL FOR QUOTE ON HIGHER CAPACITY HARD DRIVES!

NEW FACTORY DIRECT NO RETURNS AT THIS PRICE

CALL FOR COLOR I &

DRIVE CAB NETS		ı
5%" CASE POWER SUPPLY	\$89	9:
5%" DUAL WHR W/POWER SUPPLY	79	91
8" DUAL CASE W/POWER SUPPLY	279	94
6" THINLINE DUAL W/POWER SUPPLY	199	8
5%" HARD DISK W/POWER SUPPLY	199	94
514" W HIGH HARD DISK	199	9
ADDLE DICK DOLVES	_	۰

AFFEE DISK DRIVE	
APPLE KNIN COMPATIBLE	\$174.95
APPLE II/IIII COMPATIBLE IN HIGH	184 95
MICROSCI APPLE III DRIVE	219 95
APPLE II to APPLE IIC ADAPTOR	19.95
APPLE II/III DISK CONTROLLER	49 95

OTICE TO DEALERS - We Will Pay Top Dollar For Your Excess Inventor

Bolder 36 Pin I	Mala		7.49
iolder 36 Ptn i	Female		8 95
(CALL	TOLL FREE FOR	IDC's)	
	C SOCKET	S	
OLDERTAIL		1-00	100
	8 Pm STAP	8 .13	\$ 10
	14 Pin ST/LP	.15	11
	16 Pm ST/LP	.17	12
	18 Pin ST/LP	.20	17
	20 Pm ST/LP	28	26
	22 PM STAP	.29	,27
	24 Pin ST/LP	29	.27
	26 Pm STAP	,39	32
	36 Pm STAP	.45	.36
	40 Pm ST/LP	.48	.42
	64 Pin ST/LP	3 95	3 25
VIREWRAP (GI	DLD)	1-99	100
	8 Pin WW/3L	\$ .40	\$ .40
	14 Pin WW/3L	62	,49
_	18 Pin WW/3L	65	.66
	18 Pin WW/3L	88	.77
THEFT !	20 Ptn WW/3L	.99	.96
19911111	22 Pin WW/3L	1.19	1.13
1111111	24 Fln WW/3L		1,17
	26 Pin WW/3L		1 39
	40 Pin WW/3L	1.89	1.75
20420	DI CITIE SEED INC.		

		68	100			Ł
IJ	68000 \$48.6			6850	\$ 3.25	1
	68000L10 89 6 6800 2 6			6852 6860	8 65 7 90	ħ.
	8802 7.1	5 6828		6875	6.75	ш
ı	6803 18 6			6880	2 20	ш
	6809E 14.8		CALL FOR 6	8008 FAI	UIT.AJ	
	100	65	00	110		ı
	8502 \$4.60	8504	\$6.75	6522	\$6.75	ı
	8502A 8 90 8502B 9 50	8507 8520	9.75	6532	9 50	
	00028 9 90			9001	11 00	ı
1	-6	80	100			ı
1	8035 \$ 5.75	8214	\$ 3.78	8259	\$ 8.75	
1	8039 6.75 8080A 2.95	8216	1.95	8271	69 95 26 95	
-	8085A 4 90	8226	1.95	8279	8.75	
1	80C85A 9.95	8228	3 40	8282	6.25	
	8086 24 50 8087 189 95	6237 8237-5	14.75	8283	6 25	
3	8088 29 50	8238	4 25	8286	8.45	ш
3	8089 38.95	8243	3.95	8287	8.45	ı
1	8156 6,75 8158 6,75	8250	10 50	6288 8289	14.95	ı
1	8185 ::6.95	6251A	8 95	8292	12.95	
1	8202 23.95 8203 37,95	8253	8.75 4.25	8741 8748	27 95 24 80	L
1	8205 37,95	8255 8255A	6.95	8748	24.80	п
1	8212 196	8257	8 75	8755A	34.95	
1	8.52	Z:	80	-		ı
1		2 SMHz	"A" 4 DMH	z *****	6 OMHz	L
Į	ZBO-CPU	3.75	4 35		9 50	
i	ZBO-CTC	3.75	4.75		2 25	ш
1	Z90-DART Z90-DMA	12,95	9 50		7.95 7.95	п
1	Z80-PIO	3,75	4.26		2.50	П
d	280-\$10/0 280-\$10/1	11 25	12.25		-	Ш
1	Z80-SIO/2	11.95	12.75	3	6 95	П
1	Z80-SIO/9	1/1.95	12.75		-	L
4	Z8030 \$34 95	Z8001	\$34.95	Z6132	\$32.95	П
1	Z8530 34.95	Z8002	34,95	Z8071	37,95	L
1	DIS		TROLLE		ı	L
4	uPD765\$24.95	1797	\$29.95 49.95	8272	\$32.95 24.95	ı.
	1791 24.78	2793	49 95	1891	11.95	1
1	1793 26 50	2795	49,95	2143	12.95	
	1795 28 50	2797	49.95	9218	12 95	L
1	_		POLLE		ı.	L
J	5845 \$14.74 58845 17,95			WS9918 360	\$39.50	
	6847 11.50			360 545	39.95	ı
1	46505 14.75		21 95 80	303	19.95	L
1	88047 24 50					П
1	-	JARTS/	USARTS	5	l I	ı
1	16028 \$3.95	2350 \$		16403	\$ 8.76	ь
ı	1013A 3.95 1015A 8.75	B250 PM6402	10 50 TI	W\$5501	14 95 8 95	ы
1	10 September 1	EPR	OMS			
١			_		ļ.,	1
1	1702 (1mG) 2708 (450nS)	\$ 3.90 3.65	2732A-4 (2)		8 95	Li
1	2758 (5V)	5 50	2732A-2	200nS)	12 60	1
1	2716 (450nS) 2716 (360nS)	3.75	2764 (46)		6 50 7.80	L
ı	2518 (38(nS) 2518 (6V)	5.50	2764 (256 2764 (206	uns) OnS)	7.80 17.50	ľ
ı	7MS2718	7.50	TMS2564	(450nS)	12.95	
J	TMS2532 2732 (46(nS)	5 80 4 60	MCM6876 MCM6876			1
J	2732 (26CnS)	8 25	27128-31	300nS)	21 50	
1	2732 (20(n8)	10.96	27128 (2	50nS)	22 96	
ı	CMOS EPROMS 27C18	\$17.95	27C32 27C84		\$22.95 26.95	
I	1000	STATIC	RAMS			
Į	2101 (45CnS)	\$2.29	-		\$4.95	
ł	21L02 (450nS)	19		18-2 (200	nSI4.10	
١	2102-1 (450nS) 21L02-2 (250nS)	1.38	TMM20	16-15 (15 16-1 (100	un) 4 95 nS) 6 10	
ŀ	2111 (45CnS)	2.76	HM6116	3P-4 (200)	n8) 4,75	
1	2112 (45CnS)	2,75	HM6116	SP-3 (150)	ASI) 4 96	

27C18	\$17.95	27C32 27C84	\$22.95 26.95
S	TATIC	RAMS	
2101 (45CnS)	\$2.29	MK411B	\$4.95
21L02 (450nS)	.12	TMM2018-2 (200)	
2102-1 (450nS)	.79	TMM2018-15 (15)	On) 4 95
21L02-2 (250n8)	1.39	TMM2016-1 (100)	15)6 10
2111 (45ChS)	2.76	HM6116P-4 (200)	8) 4,75
2112 (45CnS)	2.75	HM6116P-3 (150r	9) 4 95
2114 (45Cn8) 1.	45 8/9 50	HM6116P 2 (120r	S) 8.85
2114L-4 (450n) 1.8	N B/12 50	HM6116LP-4 (LP)	5.90
2114L-3 (300n) 1.7	9 8/13 30	HM6116LP-3 (LP)	6.75
2114L-2 (200n) 1 8	9 8/13 90	HM6116LPI2 ILPI	9.95
2147 (55nS)	4.50	Z8132 (300nS)	32.95
4044-4 (450nS)	3 25	HM8284P-15 (150	1 32 95
4044-3 (3i)0nS)	3,75	HM8284LP-15 ILF	38.95
4044-2 (200nS)	4 35	745189 (35nS)	1.85
UPD410 (100hS)	3 75	93415 (50nS)	3.95
5101 (CMOS)	3 80	93426 (50nS)	3.95
D	NAMIC	RAMS	
4027 (25CnS)	31.29	TMS4416 (150n8	\$9.75
1103 (300nS)	79	41256-150 (150h	29 95
4116N 2 (150nS) 1			
4116N-3 (200nS) 1	65 8/12 60	TM\$4050 (300n\$	1.85

DYN	AM	IC	RAMS	
4027 (25CnS)	\$1	29		
1103 (300nS)		79	41256-150 (150h)	
4116N 2 (150nS) 1.80			41258-200 (200n)	
4116N-3 (200nS) 1.65			TMS4050 (300nS)	1.85
4116N-4 (250nS) 1,45			TMS4060 (300nS)	1.85
4164N-150 (150n)5.96	9/44	95	MM5280 (300nS)	1.85
4184N 200 (200n)4.96	9/39	50	UPD411 (300nS)	1.65
4164N-120 (120n8)	6	49	MM5298 (250nS)	1.85
TMS4184 [150nS]	7	95		

COEX	80F/T	PRINT
	of dre	Dot Matrix, 80cp ctional Printing Buffared Memory
	80, Gra	96, 132 Columns phics and Block P

\$14995 HI-TECH SPECIALS

SU	PEA	SAI	ÆR.
HE	M	P	20
Comp		Dreat	
8	12	4	5

Л	14"						
٩QÜ	ISITI	DN					
0817	\$9.76	1408L6	81.95				
00800	4,75	1408LB	2.85				
00808	2.85	DAC100	7.95				
1020	7.05	DACOS	7.05				

MAIL ORDER PFICING ONLY

TMS99532NL

ER

	1	TOLL FR	EE		
ADC0816	14.25	DAC1022	5.85	DAC01	8.95
ADC0809		DAC1020	7 95	DAC08	7.95
DAC0805		DAC0808	2.85	DAC100	7,95
ADC0804	3 45	DAC0800	4,75	1408LB	2.85
ADC0800		ADC0817		1408L6	\$1.95

iBM PC Compatible Reyboard 99.95 ISM PC Compatible Reypoard SANYO 555 MS-DOS Computer DEC "Rainbow 1004" (3245 list) DEC "Rainbow 100+" (5475 list) 5Mb Winchester Upgrade DEC NEC8201 Portable Computer 799.00 1699 00 3499.00 775.00 449.00 ZENITH Z151 100% PC Compatible Compute SANYO (Silver Reed 500) LQ Printer DEADLINE" Atari Software (49 95

VISICALC IIe Advanced

KR2207	0.00	Tt.081C	P 59			741	S00		
XR220/					_				1
XR220		7L484	4 10	74L900		74LS113		74LS247	1
LM2871		TL496		74LS01	25	74L5114	.39	74L3248	
LM2871		TL497		74LS02	25	74LS122		74LS249	
LM2900		HC3423		74LS03	26	74LS123	,95	74LS251	
LM2901		NIC3463		74LS04		74LS124	2,75	74LS253	
LM290		MC3456		74LS05	25	74LS125	49	74LS267	
LM2911		MC3456		74LS08	.27	74LS126	,40	74L8258	
LM3900		MC3486		74LS09	28	74LS132	.50	74LS258	
LM3905		MC3470		74LS10	.25	74LS136	39	74LS260	
LM3909		I I I	/ / #5	74LS11	33	74LS138	59	74LS261	
				74LS12	33	74L\$139	59	74L5266	
AGE R	FGUL A	TORS		74LS13	.39	74LS145	1,19	74LS273	
				74LS14	59	74LS148	1 38	74L9275	
00	7905K	Alac	4 00	74LS16	33	74LS181	55	74LS279	
69	12, 1	5, 24V.	1.39	74L\$20	.28	74LS153	.56	74LS283	
.85	79L05,	12, 15V	75	74LS21	29	74LS154	1.49	74LS290	
,89	LM309	K	1.25	74LS22	29	74LS155		74L3293	
1,49	LM317	K	3.86	74LS28		74LS156	.89	74US295	
. 8,75	LM323		4.85	74LS27		74LS157		74LS298	
4 00	LM337		3.75	74LS28		74LS158	69	74L9324	
1.29	LM338		8 75	74LS30		74LS180		74LS347	
70	LM350		4.55	74LS32		74LS181		74LS348	
79	LM360	K	4.75	74LS33		74LS182		74LS352	
AL DRAF	DOCE	CHIPS		74LS37		74LS163		74LS363	
AL PUR	TUSE	CHIES		741.536		74LS184		74LS363	
58174	\$11.25	98490	\$ 8 25	74LS40		74LS166		74LS365	
5832	3,75	76477	3 75	74LS42		74LS188		74L3366	
AY52376		76488	5.75	74LS47	.74	74LS168	1,15	74LS367	
AY53808		76480	8.75	74LS48	.74	74LS189	1.15	741.5388	
2513-001		AY38910	11.96	74LS51	25	74LS170	1,40	74LS373	
2513-002		AY38912	11.95	74LS54	.29	74LS173	67	74LS374	
UPD7201		\$54-263	36.95	74LS56	29	74LS174		7418375	
3341	4.50	Vorrasi	39 95	74LS73		74LS175		74LS377	
11090			34 95	74LS74	,34	74LS181		74LS385	
11000	10.00	- Congression	04.00	741 976		741 9190	85	7-U S386	

74LS37	35	74LS103	- 69	7 4LS363	- 1
741.536	39	74LS184	- 69	74LS363	1
74LS40	25	74LS185	80	74LS365	
74LS42	.44	74LS188	1.90	74LS366	
74LS47	.74	74LS168	1.15	741.5367	
74LS48	.74	74LS189	1.15	741.5388	
74L351	25	74LS170	1,40	741.5373	1
74LS54	.29	74LS173	67	74L8374	7
74LS56	29	74LS174	67	741.8375	
74LS73	39	74LS175	67	74L8377	1
74LS74	.34	74LS181	1.95	74LS385	
741375	.39	74LS190	85	74LS386	
74LS78	.39	74LS191	85	74LS390	,
74L378	.39	74LS192	.78	74LS393	
741.583	59	74LS193	78	741,5396	
741.985	,89	74LS194	.89	74LS399	1
74LS86	39	74LS195	69	7413424	- 2
741.590	.54	74LS196	.79	74L3666	-
74LS92	.84	74LS197	.79	74L8870	- 1
74L993	.84	74LS221	89	81LS95	1
74LS95	.75	74LS240	95	81LS96	- 1
74LS96	89	74LS242	95	81LS97	1
74LS107	.39	74LS243	.95		1
74LS109	39	741.9244	1 25	25LS2521	- 1
74LS112	39	74L8245	1,45	25LS2589	- 5
		CM	os	44.5	
4000 \$ .21	402	8 \$ ,85   40	69 \$7 B	0   4805	6

\$ 06, 74123 66, 74126 68, 74126 69, 74126 19, 74132 19, 74132 19, 74141 19, 74141 19, 74141 19, 74141 19, 74141 19, 74141 20, 74144 33, 74147 33, 74147 34, 74150 34, 74150 35, 74150 36, 74150 36, 74150 37, 74150 37, 74150 38, 74150 39, 74150 30, 74150 31, 74150 32, 74150 33, 74150 34, 74150 35, 74150 36, 74150 37, 74150 37, 74150 37, 74150 38, 74150 39, 74150 30, 74150 31, 74150 31, 74150 32, 74150 33, 74150 34, 74150 35, 74150 36, 74150 37, 74150

74LS00

	. 7			С	MOS	•		
	4000 \$	.29	4028	\$ ,85	4059	\$7.90	4805	6.95
	4001	.24	4029	.75	4060	85	4508	1.10
ı	4002	.24	4030	.39	4086	39	4507	1.10
1	4008	.79	4031	3.25	4089	28	4508	1 90
	4007	26	4032	2.15	4070	36	4510	71
1	4008	95	4034	1 91	4071	28	4511	.71
ı	4009	39	4036	79	4072	28	4512	.71
ı	4010	.39	4037	1,95	4073	.28	4514	1.31
ı	4011	.24	4040	75	4078	.28	4515	1.71
1	4012	24	4041	75	4078	.76	4518	1 11
g	4013	36	4042	65	4077	35	4518	8
1	4014	75	4043	85	407B	36	4820	.71
1	4015	.39	4044	89	4081	29	4555	Bi
1	4018	35	4048	80	4082	29	4556	94
1	4017	65	4047	89	4085	.96	4586	1 3
1	4018	.79	4048	99	4086	95	80C95	1.80
1	4019	39	4049	35	4093	.45	80C97	1.25
1	4020	.89	4050	34	4094	2.95	MC14408	12.95
1	4021	89	4051	75	4098	1 90	MC14409	12 9
1	4022	.89	4052	75	4099	1.85	MC14410	12.9
1	4023	.25	4053	75	4501	.89	MC14411	11.9
1	4024	50	4055	3.95	4502	.95	MC14412	12 9
-1	40.94	24	4055	2.04	4602	47	88714410	4.00

4024	59	4055 3.95		C14412 12.95
4025	.25	4056 2 95 1	4503 ,62 M	C14419 4.95
4027	45			
402	_			
		74500	PROMS.	
	_			
74500	\$ 36	74874 8 55		745260 \$1.19
74802	35	74385 1 89	745180 2.49	745280 1.95
74303	.35	74586 55	745161 1.69	74S287° 1 95
74904	.45	748112 55	748174 1.19	74S288* 1.98
74805	45	745113 58	749175 1.19	748373 2 09
74508	.39	748114 55	745188* 1,49	749374 2 09
74509	.39	7451242 89	745194 1.49	745387* 1 95
74510	.36	7481321.39	745195 1.49	74S471 * 8.95
74511	35	749133 45	745196 1.49	745472" 4 95
74315	35	743134 50	748240 1,99	748473* 4.95
74520	35	74S136 .59	745241 1,99	745474* 4 95
74822	36	7451361.39	745242 1,99	7454751 4 95
74530	35	749138 89	745243 1 99	749570* 2 96
74532	.45	745139 ,89	743244 1 99	74867112.95
74538	.89	745140 55	748251 1.19	745572* 4.95
74540	.39	748181 99	749253 1.19	74\$573* 4.95
74551	35	743153 .99	745257 1.19	745940 249
74564	.39	745157 99	748258 1.19	743941 2 49

- 3		7.	4C00	
74C00	\$ 35	74074 8.85	740181.15	74037382 35
74002	35	74C85 1 89	74C176 1.18	74C374 2.35
			74C240 1.89	
74008	35	74C93 1 15	74C244 1.89	74C922 4 45
74C10	35	MORE 74C IP	STOCK - ALS	O IN CATALOG

Mail Order: P.O. Box 17329 Irvine, CA 92713 Retail: 13108 E. Edinger, Santa Ana, CA 92705 (714) 558-8813 542 W. Trimble, San Jose, CA 95131 (408) 946-7010 910-595-1565

continued from page 90

You can build an optocoupler using a Light Dependant Resistor (LDR), a jumbo red LED, and some heatshrink tubing. To make the optocoupler, simply place the LED and LDR inside the tubing so that the light from the LED can strike the lens of the LDR. Don't forget to allow the leads to extend beyond the tubing.

You can then use your optocoupler as you would any other pre-packaged type. Using that arrangement helps keep the activecomponent count to a minimum. The slow rise and fall times of the LDR actually work out for the best because it gives the action of the limiter a much more natural sound.

As I said, the general approach is more important to understand than the particular example. Figure 2 is an actual preamp using the familiar 741 as a non-inverting amplifier. As you see, the phototransistor (contained in the optocoupler) is connected in parallel with the feedback resistor. When an excessively high signal is pumped into the circuit, the amplifier draws more power to handle the increased input.

When the threshold voltage of the transistor is reached, it turns on and the LED inside the optocoupler lights causing the phototransistor to turn on and lower the gain of the amplifier.

You could just as easily have connected the phototransistor or LDR from the input leg of the preamp to ground. However connecting it in such a manner requires a bit of recalculation of the resistor values in the circuit. Since I don't know what the change in voltage would be across your choice of optoisolator, you'll have to work the values out yourself.

Remember, because our approach to the problem of audio limiting is a general one, you'll have to tailor it to fit the specific needs of your circuit.

In Figure 3, I've put the limiter to work in an amplifier made from a 4049 CMOS hex inverter. Since the gain of the circuit is only a function of R2/R1, connecting the phototransistor in parallel with R2 will reduce amplifier gain whenever signal levels get excessive. The trigger for the circuit comes from the amp's current draw, rather than from the audio itself. That means that the gain is decreased before the amp overloads.

Our approach to limiting has several advantages over more conventional ones. It's has a built-in failsafe because if anything happens to the LED, the phototransistor will not conduct (or the LDR will assume it's in-dark resistance—usually well over 1 megohm).

Since what we've been talking about here is an idea rather than any one particular circuit, drop me a line and let me know how you were able to use this method of signal limiting. More than likely you'll find a use for it that never even occurred to me.

# RECEIVING ANTENNA

Gives excellent reception, 50 KHz to 30 MHz.

> New MFJ-1024 Active Receiving Antenna mounts outdoors away from electrical noise for maximum signal. Gives excellent reception of 50 KHz to 30 MHz signals. Equivalent to wire hundreds of feet long. Use any SWL, MW, BCB, VLF or Ham receiver. High dynamic range RF amplifier. 54

in. whip. 50 foot coax. 20 dB attenuator prevents receiver overload. Switch between two receivers. Select auxiliary or active antenna. Gain control. "ON" LED. Remote unit, 3x2x4 in. Control

6x2x5 in. 12 VDC or 110 VAC with optional adapter,

MFJ-1312, \$9.95 29 95

Order from MFJ and try it. If not delighted return within 30 days for refund (less shipping) One year unconditional guarantee.

Order today. Call TOLL FREE 800-647-1800. Charge VISA, MC. Or mail check, money order Write for free catalog. Over 100 products.

CALL TOLL FREE 800-647-1800
Call 601-323-5869 in Miss., outside continental USA, tech/order/repair info. TELEX 53-4590.

ENTERPRISES, INCORPORATED Box 494, Mississippi State, MS 39762

CIRCLE 105 ON FREE INFORMATION CARD

#### ANAZING w DEALCE? PERSONAL DEFENSE AND PROPERTY PROTECTION **UTILIZE SPACE AGE TECHNOLOGY** CAUTION THESE DEVICES CAN BE HAZARDOUS AND MAY SOON BE ILLEGAL

POCKET PAIN FIELD GENERATOR — IPG50 PHASOR PAIN FIELD CROWD CONTROLLER — PPF10 Assembled \$250.00
PPF1 ... Plans ... \$15.00 PPF1K Kit/Plans \$175.00
BLASTER— Provides a plasma discharge capable of puncturing Assembled \$10.00 BLS1K

BLS<sub>1</sub> SHOCKER/PARALYZING DEVICE — Very intimidating and effective 5 to 10 feet

SHG60 Assembled \$99.50

SHG60 Assembled \$99.50
SHG6 Plans. \$10.00 SHG6K Kit/Plans \$69.50
RUBY LASER RAY GUN — Intense visible red beam burns and welds hardest of metals. MAY BE HAZARDOUS.
RUB3AII Parts Available for Completing Device\$15.00
CARBON DIOXIDE BURNING, CUTTING LASER — Pro-

CARBON DIOXIDE BURNING, CUTTING LASER — Produces acontinuous beam of high energy. MAY BE HAZARDOUS. LCS. All Parts Available for Completing Device. \$15.00 VISIBLE LASER LIGHT GUN — produces intense red beam for

VISIBLE LASEMERGH I GUN – produces intense red beam of sighting, spotting, etc. Hand held complete LGU3. Plans. \$10.00 (Kit. & Assembled Units Available) IR PULSED LASER RIFLE — Produces 15-30 watt infra-red pulses at 200-2000 per sec. LRG3. All Parts & Diodes Available. \$10.00 BEGINNERS LOW POWER VISIBLE LASER — Choice of the pulse of the produce of the pulses.

red, yellow, green — provides an excellent source of monochromatic light. Plans \$5.00 LHC2K.

SNOOPER PHONE - Allows user to call his premises and listen S in without phone ever ringing.
Assembled

in without phone ever ringing

SNP20 Assembled \$89.50

SNP2 Plans \$9.00 SNP2K Plans/Kit \$59.50

LONG RANGE WIRELESS MIKE — Miniature device clearly
transmits well over one mile. Super sensitive, powerful

MFT1 Plans \$7.00 MFT1K Plans/Kit \$49.50

WIRELESS TELEPHONE TRANSMITTER — Transmits both Ċ sides of phone conversation over one mile, shuts off automatically VWPM5 ... Plans ... \$8 00 VWPM5K... Plans/Kit ... \$39.50 TALK & TELL AUTOMATIC TELEPHONE RECORDING

I T Y DEVICE — Great for monitoring telephone use TAT20 Assembled TAT2 Plans... \$5 00 TAT2K ...Pla ..Plans/Kit

Our phone is open for orders anytime. Technicians are available 9-11 a.m., Mon-Thurs for those needing assistance or information. Send for free catalog of hundreds more similar devices. Send check, cash. MO, Visa, MC, COD to: INFORMATION UNLIMITED DEPT R8. P.O. Box 716. Amherst. N. H. 03031Tel: 603-673-4730.

**CIRCLE 72 ON FREE INFORMATION CARD** 

# 24" DEEP DISH MICROWAVE TV ANTENNAS



1.9 to 2.6 GHz Frequency Range 24" Parabolic Dish. Preassembled Probe with Down

Converter, Power Supply and Tuner Switch, 63' of Coax Cable with Connector. Transformer for 75-300 Ohms Mounting Hardware for Fast and Easy Installation.

**ORION ELECTRONICS** P.O. Box 26420 Tempe, Arizona 84282





(602) 897-2321 SPECIAL \$74.95

#### SATELLITE TELEVISION

UNSCRAMBLE secret satellite channels watch all the good stuff. Plans \$19,95—kits \$169,95—complete units \$395.00—Details and order forms \$3.00. SCRAMCO, 8688 Royal Drive, Noblesville, IN

SATELLITE-TV receiver breakthrough! Build your own system and save! Instruction manuals, schematics, circuit boards! Send stamped envelope: XANDI, Box 25647, Dept. 21G, Tempe, AZ 85282.

MULTI channel microwave antennas, highest quality, low prices, dealers welcome. D.T. compact \$38.00, PT-1 \$48.00, SR-1 \$65.00, D.T. grid \$69.00, PTS-33 \$75.00, all units complete. DAISY TENNA, Box 42010, Phoenix, AZ 85080, (1-800) 874-9033.

SATELLITE systems and accessories. Dishes, receivers, LNA's, actuators. Top brands, low prices. \$5.00 catalog. B & T ELECTRONICS, PO Box 3156, Grand Rapids, MI 49501.

# STOP DREAMI

#### HANDY MAKES IT EASY!

Build anything from computers to LED flashers ... any project you want the fast, easy, fun way. Use HANDY solderless breadboards to build, test, modify and expand your ideas.

#### SATISFACTION GUARANTEED OR YOUR MONEY BACK!

#### JUST LOOK AT THESE SOCKET FEATURES...

- Full contact labeling simplifies component layouts
- New durable clip design assures reliable, low resistance, corrosion-free interconnections
- High temp plastic no warping or melting...ever!
- Self-adhesive backing mounts anywhere
- Big 9 14-pin IC capacity per socket
- Expands horizontally and vertically

HB-0100, 1 Buss Strip. 100 tie points. Compares at \$3.00!

\$725

HB-1000. 1 Socket Strip. 640 tie points. 9 14-pin IC capacity. Compares at \$12.50!

**\$Q**95

HB-4714. 4 Socket Strips. 7 Buss Strips. 4 Binding Posts. 3260 tie points. 36 14-pin IC capacity. Compares at \$89.00!

HB-2312. 2 Socket Strips. 3 Buss Strips. 3 Binding Posts. 1580 tie points. 18 14-pin IC capacity. Compares at \$51.50!

HB-2112. 2 Socket Strips. 1 Buss Strip. 2 Binding Posts, 1380 tie points 18 14-pin IC capacity.

\$7495

·HB-1110. 1 Socket Strip. 1 Buss Strip. Ground plate. 740 tie points 9 14-pin IC capacity. Compares at \$15.50!

HB-1210. 1 Socket Strip. 2 Buss Strips. Ground plate. 840 tie points. 9 14-pin IC capacity. Compares at \$18.501

**\$13**95

HB-3514. 3 Socket Strips. 5 Buss Strips. 4 Binding Posts. 2420 tie points. 27 14-pin IC capacity. Compares at \$66.00!

**\$47**95



contact markings simplify layout, wiring and documentation.

SEND FOR FREE Colorful **Brochure!** 

Available at Selected Distributors throughout the USA and Canada

HANDY PRICES ARE UP TO 25% LESS THAN COMPETITORS!







ORDER TOLL FREE 1-800-34-HANDY ...charge with VISA or MasterCard. All items off-the-shelf for Immediate Shipment!



a division of RSP Electronics Corp.

7 Business Park Drive • P.O. Box 699 • Branford, CT 06405 Telephone: (203) 488-6603 CompuServe: 71346, 1070

TWX: (910) 997-0648

Easy Link Mail Box: 62537580

Mail Orders: Please add \$3 (Canada & Int'l add \$5) for shipping/handling. Charge Cards: {Min. \$15}. Please include Acct. No., Exp. Date and your signature. Checks: drawn in U.S. Dollars on U.S. banks only. C.O.D.'s accepted Connecticut Residents: Add 7.5% Sales Tax.



\$139.95

Cable Converter

Micro computer technology ◆ Quartz controlle IC's lock in picture & prevent drift • 60 channel selections • Programmable time on a off • 24 hour LED digital clock • Favorite channel mem-ory & recall pilos scan • Wireless hand held "infra-red" transmitter system • Automatic time time • Magibale to any brand television • One year warranty service.

#### **RS232 TRANSMISSION LINE TESTER**

Features: "Male to Female connector for easy insertion into RS232 Line." Test 7 Lines (TD. RD. RTS. CTS. DSR. CD. DTR) using LEO s to indicate status of each. "Directly powered by RS232 \$23.95





SOUND ACTIVATED SWITCH MODEL R-1 \$29.95 For Home Security. Hears a Noise. Turns On Lights!

When lights turn on, intruders are frightened away, ask any policeman. The new SOUND activated SWITCM automatically turns on lights at any sound, so it looks filely our lend need even when you're not. SOUND activated SWITCH protects your home better than timers. It turns on lights at the sound of an attempted break-in, and automatically turns them off when it's sale.

SOUND activated SWITCH.


It's the lightwatchman you can't afford to be without.

Entry Hall • Nursery • Sick Room • Family Room • Stainways and Halls • Children's Rooms • Attics • Basements • Garage • Closets

#### REFURBISHED MONITORS

9" and 12" Bell & Howells or GBC Commercial Grade as low as \$10.00 off with a purchase

Call for quantity prices.

 

\$169.95

\$39.95

#### **RS232 TRANSMISSION LINE TESTER** Features: "Ali 25 Signal lines accessible: "Dual

Color: Red Green Accessories: 1 Cable 10" male to Female Extension

Jumper Set: 6 Straight 1 T-Jumper



Jerrold 58 Channel Wireless Remote Converter \$109.95 Jerrold 36 Channel Remote





Deluxe Version - Features fine tuning knob, matching X former & 2 cables \$38.95

## BEFORE YOU PAY SS FOR A TELEPHONE SERVICE CALL, TEST IT YOURSELF

- Telephone Line Analyze Model #1042
- Tests telephone time functions that affect
- tests telephone time functions that affect telephone operation. Verifies line and ring vortage fevers. Checks condition of felephone line from central office to user's telephone lank. Verifies felephone time potartly that can affect potartly sensitive telephones.



1.00

#### BK PRECISION PROFESSIONAL TELEPHONE PRODUCT TESTER

Features: MODEL 1045

telephone line cords and tis cords for continuity shorts \$335.95

at voice and DTMF (Dual spie Fraguency) levels are

Dealers Welcom

Volume				All above discount
Discounts	C O D n	ioney o	rder che	ck Add for
Min Order \$25 00 International shippii	Libby ou	to	75.00	.\$2 50
Prices subject to ch	lange	76 00 to		\$4 50 \$6 00
without notice COD 2 00 Extra		01 00 to		\$8 50
Add I shipping		51 00 to		\$12.00
for monitors (516)		ver 1000		\$12 50
499-9500	Mon Th		W F 9-6	Sa 9:30-5

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

in the index below.				
Free Info	rmation Number Pag	je		
255	A.I.S. Satellite	13		
108	AMC Sales	8		
76	A P Products	1		
_	Active Electronics	9		
_	Advance Electronics	7		
106	Advanced Computer Products	1		
107	All Electronics	15		
72	Amazing Devices	2		
84	Appliance Service	2		
77	B&K Precision	18		
98	Beckman Instruments 4.	5		
81	CEI	30		
_	CIE			
56	CPU CE	_		
_	Command Productions			
79	Communications Electronics			
55	Contact East			
	Coop's Satellite Digest			
263	Diamondback			
82				
-	Digi-Key.			
	Digital Research Computers			
57	Digitron			
110	Dokay			
99	EKI			
_	Electro Industries			
60	Electronic Specialists			
-	Electronic Technology Today 34. CI			
61, 260	Electronic Warehouse 26. 3	31		
-	Electronics Book Club	31		
120	Elephant Electronics			
111	Etronix	90		
100	Firestik II	90		
-	Fluke Manufacturing	/4		
-	Fordham Radio	23		
258	Gemini Electronics	93		
62	Global Specialties	30		
_	Grantham College of Engineering	40		
259	Hameg	27		
71	Handy Prods./RSP Elec	13		
86	Heath Company	. 9		
_	ICS Computer Training	88		
63	Instrument Mart	86		
113	JDR Microdevices 108, 1	09		
114	.Jameco	03		
124	James Walter Satellite Rec	93		
115	Jensen Tools	93		
116	KCS	04		
87	MCM Audio	01		
105	MFJ	12		
_	McGraw-Hill Book Club	-		
67	McIntosh Labs			
253	Micro-Mart			
117	Mouser			
265	Multitech			
205	NRI			
_				
257	NTS			
431	ivenial Electronics	72		

268	New Deal Electronics
_	New-Tone Electronics
270	OK Industries
252	Omnitron
89	PTS32
90	Paia 88
	Phoenix Electronics
69	Phoenix Systems
264	Pocket Technology
125	Power Plus
251	Print Products International 25
119	Professional Video
-	Qualitone Industries
269	RAG Electronics
121	RF Electronics
78	Radio Shack98
70	Ramsey
261	Regency
274	Research Service Lab 92
-	Robotics Age 24
272	S & L Electronics
75	Spartan Electronics
_	Tektronix
273	VIP Electronics93
_	Wersi
103	Wm. B. Allen

Gernsback Publications, Inc. 200 Park Ave. South New York, NY 10003 (212) 777-6400 Chairman of the Board: M. Harvey Gernsback President; Larry Steckler

#### ADVERTISING SALES 212-777-6400

publisher Shelli Weinman advertising associate Arline Fishman advertising coordinator Lisa Strassman credit manager Donna Goldstein credit associate Naomi Matten

Sales Offices

Larry Steckler

#### **EAST/SOUTHEAST**

Stanley Levitan Radio-Electronics 200 Park Ave. South New York, NY 10003 212-428-6037, 212-777-6400

advertising assistant

#### MIDWEST/Texas/Arkansas/Okla.

Ralph Bergen Radio-Electronics 540 Frontage Road—Suite 325 Northfield, IL 60093 312-446-1444

#### **PACIFIC COAST/ Mountain States**

Marvin Green Radio-Electronics 15335 Morrison St.—Suite 227 Sherman Oaks, CA 91403 818-986-2001

# **FOR FREE** INFORMATION **USE THESE POST-PAID CARDS**

- Print your name, address and Zip Code on one of the attached postage-paid cards.
- Circle the number (or numbers) on the card that matches the number at the bottom of each ad or editorial item that you want information on. Advertisers' free information numbers also appear in the ad index on the facing page.
- Mail the card. It's Postage-Paid.

The bottom free-information card is a BUSINESS/PRO-FESSIONAL CARD. If you use this card you MUST complete the spaces for Company Name, Title, and Phone Number. If these are not filled in, the card will not be processed.

#### NOTE

Use the postcard address for Free Product Information only. Address all editorial inquiries to Editor, Radio-Electronics, 200 Park Ave South, New York, NY 10003.



Your favorite electronics magazine and still getting better

processing this request POSTAGE-PAID FREE INFORMATION CARD Company Name (if applicable) Name (please print Address

me 4 issues of HANDS-ON Ę.

**ELECTRONICS for** \$12.00-=

274 275 276 277

202 203 204 205 205 201

297 298 300 300 301 302 305 306 306

320 321 322 323 324 327 332 332 333 333 333 333 333 333

# **BUSINESS REPLY**

# Radio-Electronics

271

SUBSCRIPTION SERVICE P.O. Box 2520 **BOULDER, COLORADO 80321** 



CARD

Z

FORMATI

Ż

ш

Ш

止

weeks for delivery of first issue

VOID after March 31, 1985



Company Address

Dept./MS

FREE INFO CARD

business information redues

**BUSINESS/PROFESSIONAL** 

Unclear or incomplete mailing info will prevent our processing this request.

and bill me. 

send me 4 issues of HANDS-ON Please \$15.97

Please s

and bill

FORMATION VOID after March 31, 1985 Ш Ш  $\alpha$ 

6-8 weeks for delivery of first issue

CARD



IN THE UNITED STATES

4SA50

# **BUSINESS REPLY CARD**

POSTAGE WILL BE PAID BY ADDRESSEE

Radio-Electronics

FREE PRODUCT INFORMATION P.O. Box 13775 PHILADELPHIA, PA. 19101

# Radio Electronics

Subscribe today to the magazine that keeps you up-to-date with the newest ideas and innovations in electronics. (If you already are a subscriber, do a friend a favor and pass this subscription card along to him.)

### check offer preferred

- ☐ 1 Year—12 issues ONLY \$15.97 (You save \$7.43 off single copy price) □ Canada—12 issues \$20.97
- ☐ 2 Years (SAVE MORE)—24 issues \$30.97 (You save \$15.83 off single copy price)
- ☐ Canada—24 issues \$40.97

#### ALL SUBSCRIPTIONS PAYABLE IN US FUNDS ONLY

- Payment enclosed
- ☐ Bill Me
- Check here if you are extending or renewing your subscription

Name (Please Print) \_\_ Company Name (If applicable).

Address

City\_

State

Zip

Allow 6-8 weeks for delivery of first issue



POSTAGE WILL BE PAID BY ADDRESSEE

# Radio-Electronics.

FREE PRODUCT INFORMATION P.O. BOX 13775 PHILADELPHIA PA. 19101

IN THE UNITED STATES

# For New Ideas In Electronics read Radio-**Electronics** every month.

## During the next 12 months

Radio-Electronics will carry up to the minute articles on:

- Computers Video
- Solid-state technology
- Outstanding construction projects
- Satellite TV . Telephones
- Radio Stereo Equipment
- reports
- Test equipment VCR's Servicing
   Industrial electronics



**NEW IDEAS AND INNOVATIONS** IN ELECTRONICS APPEAR IN EVERY **ISSUE OF RADIO-ELECTRONICS** 

**KEEP UP TO DATE! DON'T MISS** ANY ISSUES!

SUBSCRIBE TODAY!

**USE THE ORDER CARD ON YOUR LEFT!** 




Delivers construction article after construction article.....Exciting columns including Jensen on DXing, Friedman on computers, Test bench tips, Noll with Calling All Hams, New Products and more.



SUBSCRIBE TODAY!

USE THE REPLY CARDS ON YOUR LEFT!
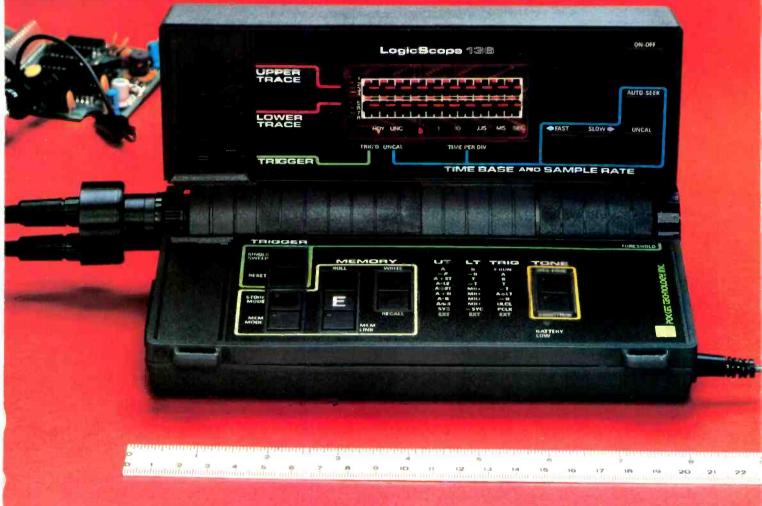
# Meet Our New LogicScope<sup>™</sup>136. ... A True Dual Trace 10 MHz Digital Storage Scope. Only \$495.



True Dual Trace • 10 MHz Real Time Bandwidth • 3 Input Channels • I/O Port Digital Waveform Storage • Boolean Waveform Operations • Audio Functions 8.25 (L) x 4.5 (D) x 1.75 (H) Inches • 1.25 Pounds • 9 Volt Battery/AC Operation

#### Consider the LogicScope TM 136

- The LogicScope 136 is the next logical step in test instrumentation for you. It combines many of the features and capabilities of sophisticated logic analyzers and oscilloscopes . . . and it fits in your hand. Never before has so much technology been available in so small an instrument, at such a low price.
- The pocket-sized LogicScope 136 is made possible by a patented breakthrough in display technology. The conventional cathode ray tube has been replaced by a unique array of 400 LED's that permits simultaneous display of two digital waveforms.
- The 136 can be used for viewing single shot events, or repetitive waveforms. It can be operated in real time mode, or in memory mode which permits acquisition and storage of up to 24 128-bit waveforms. These can be recalled, logically compared (AND, OR, EXCLUSIVE OR) to other stored/input waveforms, or output to an external device via an RS 232 port.
- Its very low cost, convenience and ease-of-use make the LogicScope the ideal instrument, for designing, troubleshooting or repairing digital systems.

#### Consider its Engineering & Field Service Applications:

- On microprocessor-based systems, check the timing relationship of various parameters relative to the system clock and other key events. Its storage capability allows visual and logical comparison of non-repetitive waveforms to known reference signals. Output in the start-up of the digital device can be compared to reference signals to determine the operating state of the device. Questionable waveforms can be stored for analysis.
- Its light weight and small size make the LogicScope convenient to take on every service call. The 136 provides much more information for trouble shooting a digital system or peripheral than a logic probe or digital multimeter, without having to lug an oscilloscope or logic analyzer along.

Contact us for the name of your local distributor
CIRCLE 264 ON FREE INFORMATION CARD





### POCCET TECHNOLOGY, INC.

7320 Parkway Drive, Hanover, MD 21076 301-796-3300

# You touch.

# It holds.

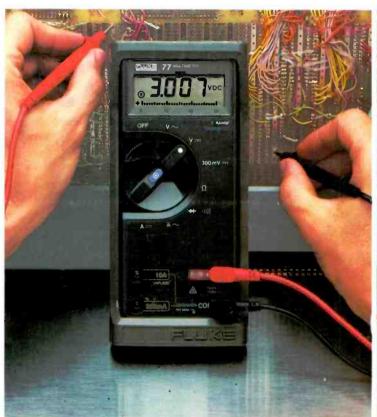

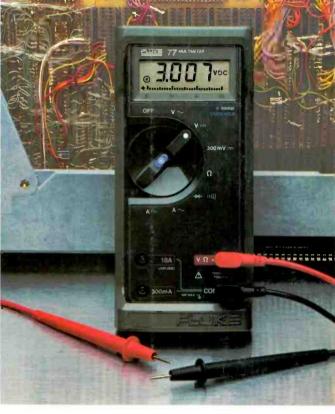

gets you the world's first handheld digital/analog multimeter with "Touch Hold."

#### The Fluke 77

Its unique "Touch Hold" \*\* function automatically senses and holds readings, leaving you free to concentrate on positioning test leads without having to watch the display.

Then, when you have a valid reading, it signals you with an audible beep.

The Fluke 77 is perfect for those test situations where accessibility is a problem. or when extra care is needed for critical measurements.

It's the top model in the world champion Fluke 70 Series line — the first industrial quality autoranging multimeters to combine digital and analog displays. These tough, American-made meters feature a three-year warranty and 2000+ hour battery life.

So call now for the complete story on the Fluke 77 with "Touch Hold." Because if you don't deserve the world's first, who in the world does?

For the name of your distributor or a free brochure, call our toll-free hotline anytime 1-800-227-3800, Ext. 229.

From outside the U.S., call 1-402-496-1350, Ext. 229.

#### FROM THE WORLD LEADER IN DIGITAL MULTIMETERS.





Analog/digital display Volts, ohms, 10A\_giode

7% basic de accuracy 000 - hour battery life



#### **FLUKE 75**

Analog/digital display Volts, ohms, 10A, mA,

Autorange/range hold % basic de accuracy 000 + hour battery life

Suggested U.S. list price, effective July 1, 1984 Patent pending.



