

48783

Radio-

NEW! Don Lancaster's HARDWARE HACKER

\$2.25 JAN. 1988
IN CANADA \$2.75

Electronics

TECHNOLOGY - VIDEO - STEREO - COMPUTERS - SERVICE

UNINTERRUPTABLE POWER SUPPLY

OUR 40-WATT UPS KEEPS GOING
WHEN YOUR POWER COMPANY QUILTS

AUDIO SCRAMBLER/DESCRAMBLER

BUILD A DEVICE TO KEEP
YOUR VOICE MESSAGES PRIVATE

R-E ROBOT

ADD A ROTATING HEAD
TO YOUR ROBOT

BUILD A 60-HZ TIMEBASE

AN ACCURATE, STABLE REFERENCE
WITHOUT CRYSTALS!

COMPUTERDIGEST

MICROSOFT BOOKSHELF
CD ROM REFERENCE LIBRARY

A NATIONWIDE RADIO PAGING SYSTEM



NOW YOU CAN STAY IN TOUCH
ANYWHERE YOU GO



A
GERNSBACK
PUBLICATION

**NOW!
DIGITAL
STORAGE
ANSWERS
STARTING AT
\$2995.**



The new 60 MHz Tek 2221 (above) offers such features as CRT readout and measurement cursors for just \$3995.

Now you have three low-cost choices in Tek digital storage oscilloscopes. All featuring powerful 20 MS/s digitizing along with familiar, full-bandwidth analog operation. It's the best of both worlds in one easy-to-use, portable package.

Discover the potential!

With digital storage you can freeze waveforms. Capture events invisible to non-storage scopes. Find signals buried in noise. And build a library of reference waveforms.

CRT readout and cursors distinguish the new 2221. For even higher performance, there's the 100 MHz, dual time base 2230 with optional battery-backed

Features	2230	NEW! 2221	2220
Analog/Digital Storage BW	100 MHz	60 MHz	60 MHz
Maximum Sampling Speed	20 MS/s	20 MS/s	20 MS/s
Record Length	4K/1K (selectable)	4K	4K
Peak Detect	100 ns	100 ns	100 ns
Save Reference Memory	One, 4K Three, 1K	One, 4K	One, 4K
Vertical Resolution	8 bits 10 bits (AVG mode) 12 bits (AVG mode over the bus)	8 bits 10 bits (AVG mode)	8 bits
CRT Readout/Cursors	Yes	Yes	No
GPIB/RS-232-C Options	Yes (\$750)	Yes (\$500)	Yes (\$500)
Battery-Backed Memory (save 26 waveform sets)	Yes (inc with GPIB/RS-232-C)	No	No
Warranty	3 year on labor and parts, including the CRT		
Price	\$4995	\$3995	\$2995

memory for saving up to 26 waveform sets. And if it's economy you want, choose the 60 MHz 2220 with many of the same features at an even lower cost.

With each scope you can automate measurements with interface options. And output direct to a printer or plotter. Tek software is available for systems.

**Call Tek direct:
1-800-426-2200**
for free video brochure for orders/assistance.



Tektronix
COMMITTED TO EXCELLENCE

BUILD THIS

- 45 UNINTERRUPTABLE POWER SUPPLY**
It keeps going when the power company doesn't.
Duane M. Perkins
- 51 AUDIO SCRAMBLING SYSTEM**
Protect your privacy by scrambling your voice.
Kevin Lindell
- 67 R-E ROBOT**
Part 13. Add a rotating head.
Steven E. Sarns

TECHNOLOGY


- 16 HDTV UPDATE**
HDTV—sooner than you think.
Brian C. Fenton
- 41 NATIONWIDE RADIO PAGING SYSTEM**
Stay in touch anywhere you go.
Herb Friedman

CIRCUITS AND COMPONENTS

- 55 60-Hz TIMEBASE**
Accurate and flexible timebase generator uses a single IC.
J. Daniel Gifford
- 57 CALIBRATING VCR COUNTERS**
Convert those digits to real time.
Fred Blechman
- 63 TESTING SEMICONDUCTORS**
Part 8. Testing TTL devices.
TJ Byers

DEPARTMENTS

- | | |
|---|--|
| <ul style="list-style-type: none">12 VIDEO NEWS
What's new in the field.
David Lachenbruch32 EQUIPMENT REPORTS
Heathkit's GR-9009 9-inch portable color TV kit.71 HARDWARE HACKER
Welcome to a new column!
Don Lancaster78 AUDIO UPDATE
Feedback.
Larry Klein | <ul style="list-style-type: none">80 DESIGNER'S NOTEBOOK
Making sine wave oscillators.
Robert Grossblatt82 COMMUNICATIONS CORNER
How IC's have changed us.
Herb Friedman84 ANTIQUE RADIOS
Ancient components.
Richard D. Fitch |
|---|--|

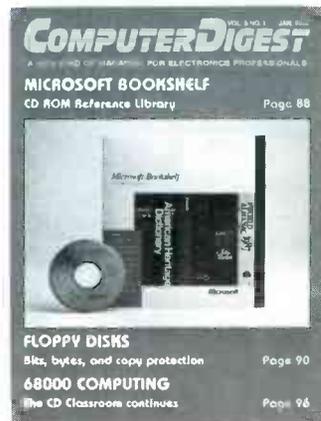

PAGE 87



PAGE 45

AND MORE

- 120 Advertising and Sales Offices**
- 120 Advertising Index**
- 22 Ask R-E**
 - 4 Editorial**
- 121 Free Information Card**
- 24 Letters**
- 103 Market Center**
- 34 New Products**
- 67 PC Service**
- 6 What's News**

ON THE COVER



If you like to stay in touch at all times—while riding a subway in New York, attending a conference in Washington, or relaxing on a beach in California—the nationwide paging system is for you. Cue Paging Corp. has combined satellite communications, SCA FM radio transmissions, *Touch-Tone* dialing, LCD digital displays, and computers to create a paging system that can reach you virtually anywhere in the United States. With six memories, and voice message retrieval you'll never have to worry about missing a message. To learn more about how it works, turn to page 41.

COMING NEXT MONTH

THE FEBRUARY ISSUE IS ON SALE JANUARY 5

REACTS

Build Radio-Electronics' advanced control system.

PROGRAMMABLE LOGIC DEVICES

How to put them to work.

MAKING PC BOARDS

It's easy to do it yourself—we show you how!

BUILD AN AUDIO/VIDEO SWITCHER

Simplify your equipment hookups.

As a service to readers, RADIO-ELECTRONICS publishes available plans or information relating to newsworthy products, techniques and scientific and technological developments. Because of possible variances in the quality and condition of materials and workmanship used by readers, RADIO-ELECTRONICS disclaims any responsibility for the safe and proper functioning of reader-built projects based upon or from plans or information published in this magazine.

Since some of the equipment and circuitry described in RADIO-ELECTRONICS may relate to or be covered by U.S. patents, RADIO-ELECTRONICS disclaims any liability for the infringement of such patents by the making, using, or selling of any such equipment or circuitry, and suggests that anyone interested in such projects consult a patent attorney.

RADIO-ELECTRONICS, (ISSN 0033-7862) January 1988. Published monthly by Gernsback Publications, Inc., 500-B Bi-County Boulevard, Farmingdale, NY 11735 Second-Class Postage paid at Farmingdale, NY and additional mailing offices. Second-Class mail registration No. 9242 authorized at Toronto, Canada. One-year subscription rate U.S.A. and possessions \$16.97. Canada \$22.97, all other countries \$25.97. All subscription orders payable in U.S.A. funds only, via international postal money order or check drawn on a U.S.A. bank. Single copies \$1.95. © 1987 by Gernsback Publications, Inc. All rights reserved. Printed in U.S.A.

POSTMASTER: Please send address changes to RADIO-ELECTRONICS, Subscription Dept., Box 55115, Boulder, CO 80321-5115.

A stamped self-addressed envelope must accompany all submitted manuscripts and/or artwork or photographs if their return is desired should they be rejected. We disclaim any responsibility for the loss or damage of manuscripts and/or artwork or photographs while in our possession or otherwise.

Radio-Electronics®

Hugo Gernsback (1884-1967) founder

M. Harvey Gernsback,
editor-in-chief, emeritus

Larry Steckler, EHF, CET,
editor-in-chief and publisher

EDITORIAL DEPARTMENT

Art Kleiman, editorial director

Brian C. Fenton, managing editor

Carl Laron, WB2SLR, associate editor

Jeffrey K. Holtzman,
computer editor

Marc Spiwak, associate editor

Robert A. Young, assistant editor

Julian S. Martin, editorial associate

Byron G. Wels, editorial associate

M. Harvey Gernsback,
contributing editor

Jack Darr, CET, service editor

Robert F. Scott,
semiconductor editor

Herb Friedman,
communications editor

Bob Cooper, Jr. satellite-TV editor

Robert Grossblatt, circuits editor

Larry Klein, audio editor

David Lachenbruch,
contributing editor

Don Lancaster,
contributing editor

Richard D. Fitch,
contributing editor

Teri Scaduto, editorial assistant

PRODUCTION DEPARTMENT

Ruby M. Yee, production director

Robert A. W. Lowndes,
editorial production

Andre Duzant, technical illustrator

Karen Tucker, advertising production

Marcella Amoroso, production traffic

CIRCULATION DEPARTMENT

Jacqueline P. Cheeseboro,
circulation director

Wendy Alanko,
circulation analyst

Theresa Lombardo,
circulation assistant

Typography by Mates Graphics

Cover photo by Diversified

Radio-Electronics is indexed in *Applied Science & Technology Index* and *Readers Guide to Periodical Literature*.

Microfilm & microfiche editions are available. Contact circulation department for details.

Advertising Sales Offices listed on page 120.




TEST EQUIPMENT THAT MEASURES UP TO YOUR SPECIFICATIONS



DMM-300 \$79.95
3.5 DIGIT DMM / MULTITESTER

Our best model. A highly accurate, full function DMM loaded with many extra features. Audible continuity, capacitance, transistor, temperature and conductance all in one handheld meter. Temperature probe, test leads and battery included.

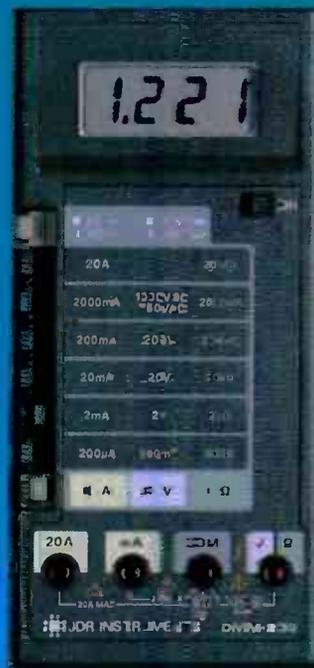- Basic DC accuracy: plus or minus 0.25%
- DC voltage: 200mv — 1000v, 5 ranges
- AC voltage: 200mv — 750v, 5 ranges
- Resistance: 200 ohms — 20M ohms, 5 ranges
- AC/DC current: 200uA — 10A, 6 ranges
- Capacitance: 2000pf — 20uf, 3 ranges
- Transistor tester: hFE test, NPN, PNP
- Temperature tester: 0° — 2000° F
- Conductance: 200ns
- Fully over-load protected
- Input impedance: 10M ohm



DMM-200 \$49.95
3.5 DIGIT FULL FUNCTION DMM

High accuracy, 20 amp current capability and many range settings make it the ideal for serious bench or field work. The starc for hard-to-see operation, 2030 year battery life with standard 9v cell. Probes and battery included.

- Basic DC accuracy: plus or minus 0.25%
- DC voltage: 200mv — 1000v, 5 ranges
- AC voltage: 200mv — 750v, 5 ranges
- Resistance: 200 ohms — 20M ohms, 6 ranges
- AC/DC current: 200uA — 20A, 6 ranges
- Fully over-load protected
- Input impedance: 10M ohm
- 180 x 86 x 37mm, weight: 320 grams



DMM-700 \$49.95
3.5 DIGIT AUTORANGING DMM

Auto-range convenience or fully manual operation. Selectable LO-Ohm mode permits accurate in-circuit resistance measurements involving semi-conductor junctions. MEM mode for measure tests relative to a specific reading. Probes and battery included.

- Basic DC accuracy: plus or minus 0.5%
- DC voltage: 200mv — 1000v, autoranging or 5 manual ranges
- AC voltage: 2v — 750v, autoranging or 4 manual ranges
- Resistance: 200 ohms — 20M ohms, autoranging
- AC/DC current: 20mA — 10A, 2 ranges
- Fully over-load protected
- Audible continuity tester
- Input impedance: 10M ohm
- 150 x 75 x 34mm, weight: 230 grams



DMM-100 \$29.95
3.5 DIGIT POCKET SIZE DMM

Shir-pocket portability with no compromise in features or accuracy. Large, easy to read 5" LCD display, 2000 hour battery life with standard 9v cell provides over two years of average use. Probes and battery included.

- Basic DC accuracy: plus or minus 0.5%
- DC voltage: 2v — 1000v, 4 ranges
- AC voltage: 200v — 750v, 2 ranges
- Resistance: 2k ohms — 2M ohms, 4 ranges
- DC current: 2mA — 2A, 4 ranges
- Fully over-load protected
- Input impedance: 10M ohm
- 130 x 75 x 28mm, weighs 195 grams



MODEL 2000 \$349.95
20 MHz DUAL TRACE OSCILLOSCOPE

Model 2000 combines useful features and exacting quality. Frequency calculation and phase measurement are quick and easy in the X-Y Mode. Service technicians will appreciate the TV Sync circuitry for viewing TV-V and TV-H as well as accurate synchronization of the Video Signal, Blanking Pedestals, VITS and Vertical/Horizontal Sync pulses.

- Lab quality compensated 10X probes included
- Built-in component tester
- 110/220 Volt operation
- X-Y operation • Bright 5" CRT • TV Sync filter



MODEL 3500 \$499.95
35 MHz DUAL TRACE OSCILLOSCOPE

Wide bandwidth and exceptional 1mV/DIV sensitivity make the Model 3500 a powerful diagnostic tool for engineers or technicians. Delayed triggering allows any portion of a waveform to be isolated and expanded for closer inspection. Variable Holdoff makes possible the stable viewing of complex waveforms.


- Lab quality compensated 10X probes included
- Delayed and single sweep modes
- Z Axis intensity modulation
- X-Y operation • Bright 5" CRT • TV Sync filter



DPM-1000 \$54.95
3.5 DIGIT PROBE TYPE DMM

Autorangeing, pen style design for the ultimate in portability and ease of use. Custom 80 pin LSI chip increases reliability. Audible continuity tester and data hold feature for added convenience. Case, test leads and batteries included.

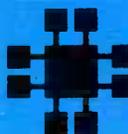- Basic DC accuracy: plus or minus 1%
- DC voltage: 2v — 500v, autoranging
- AC voltage: 2v — 500v, autoranging
- Resistance: 2k ohms — 2M ohms, autoranging
- Fully over-load protected
- Input impedance: 11M ohm
- 162 x 28 x 17mm, weighs 75 grams



JDR INSTRUMENTS

110 Knowles Drive, Los Gatos, CA 95030
(408) 866-6200 • FAX (408) 378-8927 • Telex 171-110

COPYRIGHT 1986 JDR MICRODEVICES
THE JDR INSTRUMENTS LOGO IS A REGISTERED TRADE-MARK OF JDR MICRODEVICES.
JDR INSTRUMENTS IS A TRADEMARK OF JDR MICRODEVICES.

**2 YEAR
WARRANTY
ON ALL
MODELS**



**ORDER TOLL FREE
800-538-5000**

OR VISIT OUR RETAIL STORE
1256 SOUTH BASCOM AVE.
SAN JOSE, CA. (408) 947-8881
CIRCLE 59 ON FREE INFORMATION CARD

EDITORIAL

Some happenings at the FCC



The Federal Communications Commission has proposed opening up the 902 to 928 MHz band to license-free consumer "broadcasting." The band, which would have no bandwidth, use, or modulation restrictions, could be used for everything from wireless speakers to wireless video cameras and VCR's. We think that the proposal (Gen Docket 87-389) is a great idea that will serve both the electronics industry and the electronics consumer.

The electronics industry would benefit tremendously from the new markets opened—just think of all the products that could be developed. We already know that there is a tremendous market for wireless video links for video cameras—even though the FCC has ruled that they are illegal. And although the Commission is doing its best to stop the sale of those devices, they're having trouble keeping up. Based on sales of the *VCR Rabbit* video distribution system, we also know that there would be an even larger market for wireless VCR's.

The license-free band could also open up new horizons in home automation. With an RF link, it becomes simple to monitor your front door or backyard pool with a video camera. It also becomes practical to send control-computer data via RF signals. Your stereo speakers could be installed anywhere, without running cables.

Can you imagine having not only a wireless computer keyboard, but a wireless monitor as well? How about

a wireless printer? I'm sure you get the idea, and can come up with a dozen applications that you could use the new band for. The possibilities are endless.

Needless to say, there will be many problems to overcome before the band can come into use. Interference from the amateur-radio and government agencies that currently use the band is only one of them. Of course without careful planning of the new regulations—including power and restricted use provisions—the new band could end up being a disaster. We're confident that the FCC and the electronics industry can come up with a workable plan.

But perhaps we have too much confidence in the FCC, which has considered making the NTSC TV standard voluntary. The Commission reasons that relaxing the standard might facilitate the development of high-definition advanced television systems. *We feel that a voluntary NTSC standard would be a serious mistake.*

A non-compatible HDTV system is not in the best interests of either broadcasters or consumers. Giving up on NTSC isn't the answer. Before a compatible color system was developed, many industry experts said that it couldn't be done. And many experts said the same of a high-definition NTSC compatible system. But, fortunately, the people at the David Sarnoff Research Center didn't listen, and you might be watching compatible HDTV in your living room as early as 1993! For an update on HDTV, turn to page 16.

BRIAN C. FENTON
Managing Editor

Information radio is on the air.



Before you hear about it on your old radio, hear it live on your new Informant Information Radio. Whether its an all-points-bulletin from the State Police, the dispatcher for the city's Fire Department, an ambulance racing to the hospital or a National Weather Service report, the new Informant from Regency makes you a part of all the action... instantly.

Breakthrough Technology. Instant Information.

Informant Information Radio uses a revolutionary new technology that allows you to constantly monitor your police, fire and



emergency frequencies, as well as NOAA weather information channels in all 50 states. All pre-programmed. This new Information Radio utilizes a principle similar to the seek and scan feature found on expensive AM/FM radios. Your information radio scans the public service channels in the area, locates the active signals, locks in and broadcasts all the information right to you. With revolutionary TURBO-SCAN speed!

Hear Your Hometown Like You've Never Heard it Before.

Just turn it on. As easy to use as your AM/FM radio. Instantly, you're tuned into real life adventures. One touch control lets you select and hold police, fire and emergency broadcasts so you don't miss a single minute of the action.

Hear the amazing Information Radio today. Take it home and be a part of the action tonight!!



Information Radio for Real Life Adventure



CIRCLE 179 ON FREE INFORMATION CARD

WHAT'S NEWS

Manufacturer "Fights Back" against "scientific test"

Last year, consumer reporter David Horowitz, of the syndicated TV show, *Fight Back*, ran a claimed "scientific comparison" of small batteries, using toy singing birds to make the tests. One of the batteries tested was the Kodak *Supralife* alkaline cell, which in the tests did not show up as well as a competitor's. At the end of the tests, Horowitz challenged any manufacturer "to invite us into its labs and show us how scientifically they do their tests."

Kodak's Martin H. Adams immediately accepted the challenge and invited Horowitz to visit the independent Electrical MET Testing Lab in Baltimore, MD, which tests Kodak batteries. As a result of the trip, which was taped and aired on the *Today Show* this past Sept. 14, Horowitz was persuaded that sing-

ing birds can not serve as accurate test instruments.

During the visit, both the independent lab and Kodak's Ultra Technologies division tested battery performance in the toy birds according to international standards, using precision equipment.

"In repeated comparisons, *Supralife* cells performed better overall, though some of the toy birds operated better or worse with continued use," said Adams, "The performance of these toys indeed change, as they are built with inexpensive parts."

"It's a challenge we couldn't pass up. The *Fight Back* supposedly fair test was fraught with inconsistencies. Mr. Horowitz gave us an opportunity to show the public how meaningful battery tests are conducted."



SINGING BIRDS AS TEST INSTRUMENTS have many deficiencies, explains Leonard Frier of Electrical Testing Co. to TV personality David Horowitz (center). Martin H. Adams, marketing VP of Kodak's Ultra Technologies, who initiated the test, is at right.

measurement-equipment company in the world.

Under terms of the agreement, Fluke will sell, support, and service Philips' products in North



GEORGE WINN, President of John Fluke, Inc., and George de Kruiff, Senior Managing Director of N.V. Philips, sign the agreement binding their two companies in a world-wide sales and service alliance.

America, The People's Republic of China, Hong Kong, and Japan. Philips will do the same for Fluke products in the rest of the world. Both companies will continue to develop products independently, but in addition the companies will consider joint ventures to develop product lines in categories in which neither is a significant participant currently.

In commenting on the alliance, Fluke Chairman John Fluke, Jr. said, "Fluke and Philips offer one another non-competing, complementary products which enable each company to greatly expand its product offerings to customers in various test and measurement applications."

According to George de Kruiff, Senior Managing Director of Philips, Philips offers an important and established presence for Fluke products in all of Europe and Fluke offers Philips a strong sales, marketing, and service organization in North America. R-E

Fluke and Philips join forces

The John Fluke Manufacturing Co. (Everett, WA) and N.V. Philips

(Eindhoven, The Netherlands) have joined forces to create the third largest electronics test- and

The Electronic Industries Association/Consumer Electronics Group has recently completed the first in a series of videocassette training tapes.

EIA/CEG ANNOUNCES COMPLETION OF NEW "BASIC CAR AUDIO INSTALLATION" VIDEO TAPE

If you are thinking of "cashing in" on the profits in the ever growing car audio service business, the troubleshooting—service—installation—and removal of car audio products is a large, non-competitive profit center for your service facility. This thirty minute video introduces you to the ever increasing complex world of car stereo installation. It guides the new installer or owner in the correct layout and design of a car stereo installa-

tion facility, covering basic as well as specialized tools needed for the installation business.

This informative videotape is also an excellent aid to the electronics technician in that it gives the correct procedure for removing and replacing "any" car radio from the dashboard of any car and shows the installer's, salesperson's and customer's role in the installation and sale of car audio products.

KEY TOPICS COVERED IN THIS VIDEO

- The design and layout of a car stereo installation center.
- Basic and specialized tools needed for car audio installation work.
- Safety in the shop.
- How to treat the customer's car, from pre-installation checkout to demonstrating to the customer the completed job.
- The proper procedure



for installing car audio equipment.

- The technical resources available for information about specific types of vehicles, dashboard dismantling, speaker sizes and antenna locations.
- Speaker wiring types found in the automobile. Common and floating ground systems—how to differentiate. Proper wiring procedures used in the car.

The cost of the videocassette is \$30.00. Use the order form below to order yours now!

Send to: EIA/CEG, Department PS, P.O. Box 19100, Washington, D.C. 20036

ORDER FORM

Basic Car Audio Installation	Quantity	Amount	Total Enclosed
Videocassette	_____	\$30.00 each	_____
VHS <input type="checkbox"/> BETA <input type="checkbox"/>			

Name																	
Title																	
Firm																	
Address																	
City											State			Zip			

Train for the Fastest Growing Job Skill in America

Only NRI teaches you to service all computers as you build your own fully IBM compatible microcomputer

With computers firmly established in offices—and more and more new applications being developed for every facet of business—the demand for trained computer service technicians surges forward. The Department of Labor estimates that computer service jobs will actually *double* in the next ten years—a faster growth rate than for any other occupation.

Total systems training

No computer stands alone... it's part of a total system. And if you want to learn to service and repair computers, you have to understand computer

systems. Only NRI includes a powerful computer system as part of your training, centered around the new, fully IBM PC compatible Sanyo 880 Series computer.

As part of your training, you'll build this highly-rated, 16-bit IBM compatible computer system. You'll assemble Sanyo's "intelligent" keyboard, install the power supply and disk drive, and interface the high-resolution monitor. The 880 Computer has two operating speeds: standard IBM speed of 4.77 MHz and a remarkable turbo speed of 8 MHz. It's confidence-building,

real-world experience that includes training in programming, circuit design and peripheral maintenance.

***No experience necessary—
NRI builds it in***

Even if you've never had any previous training in electronics, you can succeed with NRI training. You'll start with the basics, then rapidly build on them to master such concepts as digital logic, microprocessor design, and computer memory. You'll build and test advanced electronic circuits using the exclusive NRI Discovery Lab[®], professional digital multimeter,

Learn Computer Servicing Skills with NRI's "Hands-On" Training . . .



Using NRI's unique Action Audio Cassette, you are talked through the operation and practical application of your hand-held digital multimeter—the basic, indispensable tool for the computer specialist.



You'll set up and perform electronics experiments and demonstrations using your NRI Discovery Lab. You'll even interface the lab with your computer to "see" keyboard-generated data.



After you build this digital logic probe, you'll explore the operation of the Sanyo detached "intelligent" keyboard and its dedicated microprocessor.

NEW!

Train with the newest Sanyo 880 Series Computer—it's fully IBM-compatible and runs almost twice as fast as the IBM PC!

Your NRI total systems training includes all of this: NRI Discovery Lab[®] to design and modify circuits • Four-function digital multimeter with walk-you-through instruction on audio tape • Digital logic probe for visual examination of computer circuits • Sanyo 880 Series Computer with "intelligent" keyboard and 360K double-density, double-sided disk drive • High resolution monochrome monitor • 8K ROM, 256K RAM • Bundled software including GW BASIC, MS DOS, WordStar, CalcStar • Reference manuals, schematics, and bite-sized lessons.

and logic probe. Like your computer, they're all yours to keep as part of your training. You even get some of the most popular software, including WordStar, CalcStar, GW Basic and MS DOS.

Send for 100-page free catalog

Send the post-paid reply card today for NRI's 100-page,

full-color catalog, with all the facts about at-home computer training. Read detailed descriptions of each lesson, each experiment you perform. See each piece of hands-on equipment you'll work with and keep. And check out NRI training in other high-tech fields such as Robotics, Data Communications, TV/Audio/Video Servicing, and more.

If the card has been used, write to NRI Schools, 3939 Wisconsin Ave., N.W., Washington, D.C. 20016.

NRI SCHOOLS

McGraw-Hill Continuing Education Center
3939 Wisconsin Avenue, NW
Washington, DC 20016



We'll Give You Tomorrow.

IBM is a Registered Trademark of International Business Machine Corporation.

as You Build Your Own Sanyo 880 Computer System.



The power supply is assembled in the main unit of the computer. You check out keyboard connections and circuits with the digital multimeter included for training and field use.



Next, you install the disk drive. You learn disk drive operation and adjustment, make a copy of MS-DOS operating disk and begin your exploration of the 8088 CPU.



Using the monitor, you focus on machine language programming, an indispensable troubleshooting tool for the technician. You continue by learning BASIC language programming.

VIDEO NEWS



DAVID LACHENBRUCH,
CONTRIBUTING EDITOR

● **Europe going HDTV.** Last year, sparked by the European broadcasting authorities' distaste for any system based on the 60-Hz field rate (Europe uses 50 Hz), an American-backed proposal for a worldwide high-definition TV production standard based on the Japanese-developed 1,025-line, 60-field widescreen system was rejected by the United Nations' broadcasting body, the International Consultative Radio Committee (better-known as the CCIR). At that time, the Europeans promised to come up with their own HDTV system.

The European system, called "Eureka," was formally unveiled at the *Internationale Funkausstellung* (international TV-radio exposition) in West Berlin in a cooperative effort of virtually all European broadcasting authorities and TV-set and component manufacturers. The major points made by the Europeans—who say they are committed to the system—are "graduality" and "compatibility".

The Eureka project will use the forthcoming direct satellite-broadcasting system as a way-station on the route to HDTV. That system is expected to build on the D2-MAC format, scheduled to be broadcast by both German and French satellites this year. The MAC (Multiple Analog Component) format separates luminance and chrominance signals for a better picture. MAC will be a decided improvement over the European broadcast-standard PAL systems, increasing the picture resolution to 180,000 pixels from PAL's 120,000.

The second step in the gradual evolution will be the addition of widescreen transmission (16:9 ratio), and the third step will be an increase to 1,250 horizontal lines, bringing the number of pixels to 480,000. Each of those steps, according to the plan, will maintain compatibility; viewers with older sets will continue to receive the D2-MAC picture, while those with newer-type sets would get the wide-screen and/or high-definition picture.

Although the basic field rate would be 50 Hz, circuitry in deluxe HDTV receivers would double that to 100-fields per second, thereby eliminating

the picture's flicker. The Europeans claim that the transmission bandwidth of the full widescreen HDTV picture would be held to 10 MHz by the use of "...advanced digital-sampling and bandwidth-reduction techniques to eliminate redundant information and compress relevant data for transmission."

An NTSC-compatible HDTV system designed for the United States is expected to be proposed by the Europeans. Because Europe now controls a considerable portion of the TV-receiver market through Thompson (RCA and GE sets) and Philips (Magnavox, Sylvania, and Philco), the gradual approach to HDTV is likely to carry considerable weight here.

● **End of the 3/4-inch road?** The 3/4-inch videotape format, the U-matic system that has been the standby for industrial TV and broadcast electronic newsgathering for well over a decade, may be on the way out. Two professional 1/2-inch formats—Sony's Betacam and Panasonic's MII—threaten it at the broadcast end, and now the Super VHS (SVHS) system may replace it in the industrial arena.

At least, that's Panasonic's view; the company has introduced a completely new line of industrial video equipment using the SVHS system. Panasonic thinks that it will be used for industrial, institutional and educational video, as well as by some cable-TV systems and local TV stations. Although the cost of SVHS equipment is about 30 percent above standard VHS, it's 30 percent below 3/4-inch gear and provides longer recording time, better resolution and a better signal-to-noise ratio than U-matic. Panasonic says it stopped developing 3/4-inch equipment "several years ago (when) it became evident that 1/2-inch could produce much better quality with lighter weight and lower cost." Panasonic expects industrial producers to use SVHS for production, standard VHS for distribution. Sony, which has developed a new version of 3/4-inch recording using non-compatible metal tape (U-matic SP) may not agree—but Sony has its own super-1/2-inch system called ED Beta.

R-E

Your Career in *ELECTRONICS* or *COMPUTERS*

Add *prestige and earning power* to your technical career by earning your Associate or Bachelor's Degree in electronics or computers—through independent home study.


No commuting to class. Study at your own pace, while continuing on your present job. Learn from easy-to-understand lessons, with help from your Grantham instructors when you need it.

Grantham College of Engineering is a specialized institution catering to adults who are employed in electronics and allied fields such as computers. These fields are so enormous that opportunity for advancement is always present. Promotions and natural turn-over make desirable positions available to those who are *prepared to move up!*

An important part of being prepared to *move up* is holding the proper college degree, but the absolutely essential part is *really knowing your field*. In electronics or computers, Grantham can prepare you in both ways. But don't expect to really know your field *or* earn that college degree without hard work. Any degree that's worth your while can't be had without giving effort to the task. Of course it's what you learn in the process, as much or more than the degree itself, that makes you stand out above the crowd — that places you and your career in an enviable position, prestige-wise and financially.

Why not "go for it"? Go for the knowledge, and the degree will follow naturally. Be a "can do" person, with the right credential to put your best "moving-up" foot forward!

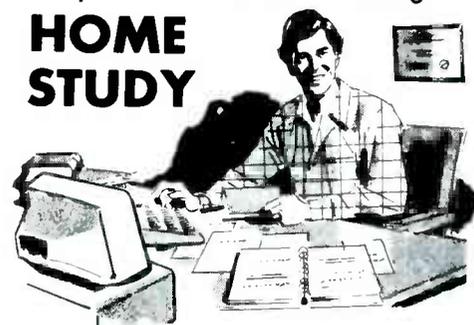Put Professional Knowledge and a
COLLEGE DEGREE
in your Technical Career through
HOME STUDY




NHSC Accredited

Grantham College of Engineering
10570 Humbolt Street
Los Alamitos, California 90720

Write for our free catalog
(see coupon below) or phone
(213) 493-4421 (no collect calls)
and ask for our "degree catalog."

Grantham offers two B.S. degree programs — one with major emphasis in *ELECTRONICS* and the other with major emphasis in *COMPUTERS*. Either program can be completed by correspondence (also known as "distance education.") An A.S. degree is awarded along the way in each B.S. program, but the B.S. program is not complete without the A.S. part. Our catalog gives complete details.

Now in Our 38th Year

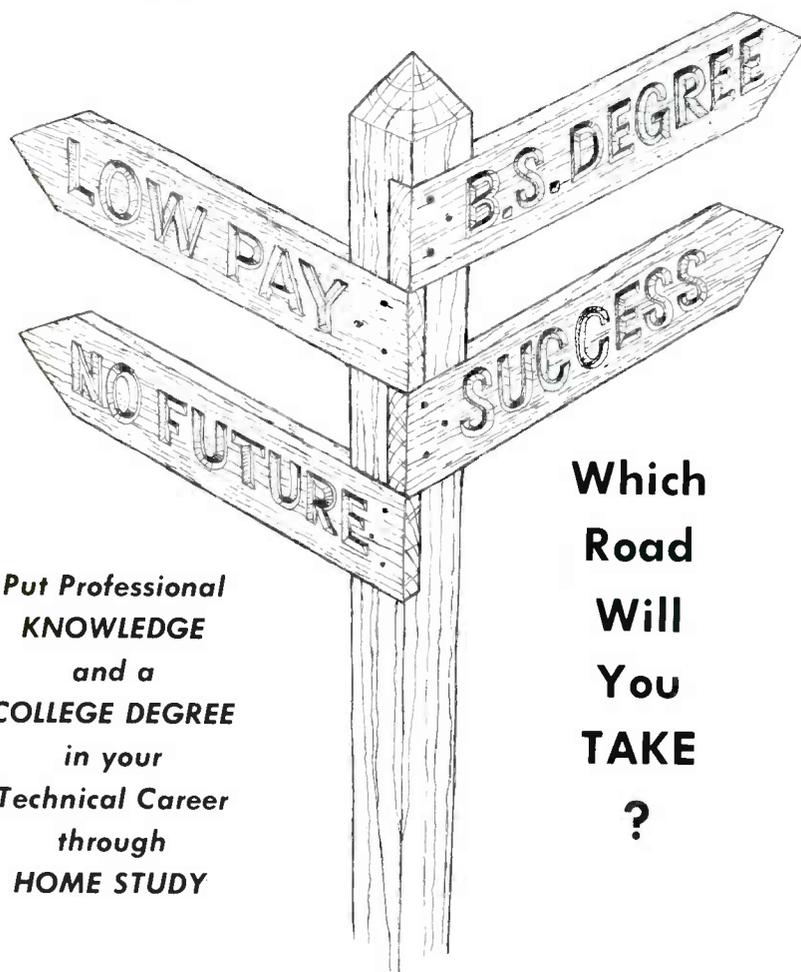

**Put Professional
KNOWLEDGE
and a
COLLEGE DEGREE
in your
Technical Career
through
HOME STUDY**

**Which
Road
Will
You
TAKE
?**

Grantham College of Engineering
P.O. Box 539, Los Alamitos, CA 90720

Please mail me your free catalog which explains your distance-education (home study) degree programs.

NAME _____

ADDRESS _____

CITY _____ STATE _____ ZIP _____

R-01-88

Is Escort Scared or Smart?

Cincinnati Microwave, the maker of Escort and Passport radar detectors, has ignored DAK's third, one-on-one Maxon versus Escort radar challenge. I think they're hiding behind 'independent' magazine reviews and refusing to meet us on the true field of battle. And now, I think I've finally figured out why. I believe they're in a NO WIN SITUATION! Read On.

By Drew Kaplan

It's time to attack. No more Mr. Nice Guy for me. I've done everything I can to get them out for a conflict.

I've offered \$10,000, then \$20,000, if they could beat Maxon's lowest price \$99⁹⁰ detector (now on sale for just \$79⁹⁰) by more than 10 feet. I've even offered to print the results in my next catalog, win, lose or draw.

In a minute, I'm going to introduce Maxon's revolutionary new Micro-Detector that is CORDLESS and built to trounce Escort and Passport, but first let's see what we can do to compare detectors.

IS THIS FAIR? YOU DECIDE

In their recent ads, Cincinnati Microwave quotes what Car and Driver Magazine's April '87 issue says about Passport, "At \$295 direct from the factory, it's the most expensive piece of electronic protection in the group, but it's worth every nickel in roadgoing peace of mind."

Well, wouldn't you think that Passport obliterated every other detector by a country mile? And, don't you think everyone is going to go out and find the magazine and read the **WHOLE** review???

Well, look what else Car and Driver said in the same article (and not quoted in Passport ad), "As it turned out, the top five brands are so close in their "Overall Sensitivity" scores that a minor juggling of the X/K-band weighting formula would upset the apple cart." Wow, imagine that!

So, Passport didn't beat everyone by a mile. In fact, on the X Band tests, it appears that it came in 3rd in a Dead-Ahead Trap, 3rd in an Over-the-Hill Trap, and 3rd in an Around-the-Corner Trap.

But in choosing Passport as best, Car and Driver says, "... an 'excellent' appraisal of support systems (cords, lights, alarms etc.) is well worth several hundred feet of warning distance..."

Which brings me back to the point I've been trying to make since I first challenged Escort. Today, a good detector can often sniff out police radar as much as 60 seconds ahead.

Traveling at 55 mph, you only cover about 80 feet a second. So, whether there's a 10' or even 100' difference in sensitivity, with today's detectors it just doesn't make much difference.

READ THIS

So, if Passport or Escort lose to the

A \$20,000 Challenge To Escort

Let's cut through the Radar Detector Glut. We challenge Escort & Passport to a one-on-one Distance and Falsing 'duel to the death' on the highway of their choice. If they win, the \$20,000 check pictured below is theirs.

By Drew Kaplan

We've put up our \$20,000. We challenge Escort to take on Maxon's Dual Superheterodyne RD-1 \$99⁹⁰ detector (right) (Now just \$79⁹⁰), Maxon's new Mini RD25 \$99⁹⁰ detector (middle) or Maxon's Cordless Micro-Trouncer \$149⁹⁰ radar detector (left) on the road of their choice in a one-on-one conflict.

The real question today is: 1) How many feet of sensing difference, if any, is there between Maxon's Detectors and Escort's or Passport's? And 2) Which is

\$79⁹⁰ Maxon, it would be catastrophic for their advertising. And, even if they beat Maxon by a second or two, are they worth double or even triple the price?

So, that's why I think they're in a **no win situation**. Without the magazine's loving editorial comments, we'd be down to **who won** and by **how many feet?**

And while they may or may not be scared of losing to Maxon, so far, they sure seem to be smart enough to stay out of a footage contest.

MAGAZINE ROUND UP

Popular Mechanics Magazine in November '86, in their Around A Corner Test said, "The low ranked . . . and Passport had to be rounding the bend and pointing at the radar gun before they'd detect it. Too late then!" (Not quoted by Passport.)

Although in July, after Cincinnati Microwave complained, Popular Mechanics said in an Around A Corner Test, "Consistent with the results of our previous test, Passport was easily the best of the minis." (Quoted in Passport Ads.)

Speaking of 'consistent', the magazines aren't consistent even from issue to issue.

By the way, in July's test they hated Maxon, but at least they said, "No detector in this group had to round the corner before sniffing out Smokey."

Road and Track Magazine (September '86) top rated Passport even though Maxon (a recommended buy) appears to have beaten Passport in Uninterrupted Alert, and Passport beat Maxon in initial alert.

So, when you get right down to which detector protects you, an **on-the-road test** without all the loving editorial 'quotable remarks' seems to be the only way to go.

We need to win or at least tie, to prove to the world that our challenge is for real, and not, as Cincinnati Microwave said, "an advertising gambit". But, speaking of advertising gambits, read this!

PROTECTION FROM RASHID \$5? WHOOPEE

Last year, Cincinnati Microwave announced to the world, in virtually every magazine I picked up, that all radar detectors but theirs would be obsolete.

It seemed that a K band collision avoidance system called Rashid VRSS would knock out everyone's detectors.

Well, I said then that the \$558 system that recommends cutting a 6 1/2" hole in your grill for installation, wasn't going to

take over the highways.

But Cincinnati Microwave kept advertising about Rashid. (My opinion of an advertising gambit). It's been a year and nobody I've talked with has run into a Rashid. I challenged Cincinnati Microwave to prove that there were even 500 on the road in the whole U.S., but they've been silent. (I wonder why???)

Anyway, just to prove that we had the technical expertise, Maxon has developed and implemented an Anti-Rashid circuit in the new Micro-Detector.

It's added about \$5 to your cost which **we all think is a waste**, but at least we won't get any more letters saying that the only reason we think it's worthless is because Maxon doesn't have it.

TRUE BREAKTHROUGH NO. FIVE

Unlike the questionable value Anti-Rashid circuit from Cincinnati Microwave, Maxon has now leapt ahead. Now you can have a micro detector that operates from 6 AA rechargeable batteries (included).

Now you can forget plugging your radar detector into your cigarette lighter. A revolutionary circuit design gives you cordless freedom and **improved** protection.

Maxon is using a circuit used in jet fighters and other military applications which replaces the traditional Gunn diode oscillator with a DRO (Di-electrically Resonated Oscillator).

The efficient DRO circuit is much more stable when subjected to temperature extremes and vibration (hence its use in the military, especially aircraft). Its only disadvantage is that it costs more.

The new detector also has incredible "support systems". Its bright LEDs, dim themselves at night. And speaking of dimming, they can be switched off so you can't be spotted from the rear.

And, as for the separate X and K warning tones, not only is the volume adjustable, 'Mute' lets you silence the alarms without adjusting volume. They will automatically reset after the alert passes.

You can plug the Micro into your cigarette lighter, you can run it for about 8 hours on its rechargeable batteries, and it automatically recharges from your cigarette lighter overnight or while you use it plugged in during the day.

OK, now it's time to prove that Maxon is Number One. Cincinnati Microwave, eat our dust!

more accurate at interpreting real radar versus false signals?

So Escort, you pick the road (continental U.S. please). You pick the equipment to create the false signals. And finally, you pick the radar gun.

Maxon and DAK will come to your highway with engineers and equipment to verify the results.

And, we'll have the \$20,000 check (pictured) to hand over if you win!

BOB SAYS MAXON IS BETTER

Here's how it started. Maxon is a mam-

moth electronics prime manufacturer. They actually make all types of sophisticated electronic products for some of the biggest U.S. Electronics Companies. (No, they don't make Escort's.)

Bob Thetford, the president of Maxon Systems Inc. and a friend of mine, was explaining their anti-falsing Dual Superheterodyne Radar detector to me. I said "You know Bob, I think Escort really has the market locked up." He said, "Our new designs can beat theirs".

...Next Page Please

... Challenge Continued

So, since I've never been one to be in second place, I said, "Would you bet \$20,000 that you can beat Escort?" And, as they say, the rest is history.

By the way, Bob is about 6'9" tall, so if we can't beat Escort, we can sure scare the you know what out of them. But, Bob and his engineers are deadly serious about this 'duel'. And you can bet that our \$20,000 is serious.

We only ask the following. 1) The public be invited to watch. 2) Maxon's Engineers as well as Escort's check the radar gun and monitor the test and the results.

3) The same car be used in all tests. 4) We'd like an answer from Escort no later than December 31, 1987, and 60 days

1/4 second gives you protection from signals from other detectors, intrusion systems and garage door openers.

So, when the lights and X or K band sounds explode into action, take care, there's very likely police radar nearby. You'll have full volume control, and a City/Highway button.



Maxon detectors are backed by Maxon's standard limited warranty.

There are many cheap imports that aren't very good. My quarrel with them is that except for themselves, I don't know who they think is any good!

CHECK OUT RADAR YOURSELF RISK FREE

Put a detector on your visor, dash or windshield. When it sounds, look around for the police. There's a good chance you'll be saving money in fines and **higher insurance rates.**

If you aren't 100% satisfied, simply return it in its original box within 30 days for a courteous refund.

(RD-1 Pictured to Right.) To get your Maxon, Dual Superheterodyne, Anti-Falsing Radar Detector risk free with your credit card, call toll free or send your



notice of the time and place of the conflict to alert the public. And, 5) If Escort can prove that there are even 500 Rashid units in operation, we will present them with a check for \$5,000 at the conflict.

HOW'S THIS FOR FAIR?

Cincinnati Microwave will be deemed the winner and given the check if **either** Escort beats Maxon's RD-1 or RD-25 by 10 feet in both uninterrupted and initial alerts or **equals** the Micro-Trouncer, **OR** if Passport beats Maxon's RD-1 or RD-25 by 2 seconds at 55mph in both uninterrupted and initial alerts or **equals** the Micro-Trouncer. So, DAK wins **only** if we beat **both** the \$295 Passport and \$245 Escort Radar Detectors.

SO, WHAT'S DUAL SUPERHETERODYNE?

OK, so far we've set up the conflict. Now let me tell you about the new dual superheterodyne technology that lets Maxon leap ahead of the pack.

It's a technology that tests each suspected radar signal 4 separate times before it notifies you, and yet it explodes into action in just 1/4 of one second. (1/10th second for the Micro-Trouncer.)

Just imagine the sophistication of devices that can test a signal 4 times in less than a 1/4 of one second. Wow!

But, using Maxon is easy. These long range detectors have all the bells and whistles with **separate** audible sounds for X and K radar signals.

LED Bar Graph Meters accurately **show the radar signal's strength.** And, you won't have to look at a needle in a meter.

Keep your eyes on the road, you'll see these meters with your peripheral vision.

You'll have a very high level of protection. Maxon's Dual Conversion Scanning Superheterodyne circuitry combined with **die-cast aluminum** ridge guide wide-band horn internal antennas, really ferret out radar signals.

And the key word is 'radar', not trash. The 4 test check system that operates in

Note from Drew: 1) Use of radar detectors is illegal in some states.

2) Speeding is dangerous. Use your detector to help keep you safe when you forget, not to get away with speeding.

DON'T WASTE MONEY

As I've said, **good** radar detectors today are very similar. The RD-1 is great. It is much smaller than Escort at just 3 1/2" wide, 4 3/4" deep and 1 1/2" tall.



If you want an even smaller detector, the RD-25 at just 2 1/8" wide, 4 1/2" deep and 1" tall, with its included windshield mount and identical specs is for you.



If you want the very best, or if you want to forget cords and be able to slip a



4 1/2" wide, 3 3/4" deep, 3/4" tall (It mounts sideways to the rest) detector into your shirt pocket, choose the Micro-Trouncer.

I'd love to tell you that the Micro-Trouncer is light years ahead in detection, because its circuitry certainly is.

But, I'd be into advertising gambit-land if I claimed that 1 or 2 seconds of improvement over Maxon's other detectors or even over Escort and Passport really make a significant difference.

Caution: Cincinnati Microwave is right.

check for DAK's \$79⁹⁰ sale price (\$4 P&H). Order No. 6168.

Note: An optional suction cup windshield mount and extra coiled power cord (we can't afford to throw them in for free) is just \$5⁹⁰ (\$2 P&H) Or. No. 4800.

(RD-25 Pictured in Middle.) To get your Maxon, Dual Superheterodyne, Anti-Falsing Mini Radar Detector complete with 2 Power Cords, Window Suction Cup, Dash and Visor Mounts risk free with your credit card, call toll free or send your check for just \$99⁹⁰ (\$4 P&H) Order No. 6169. CA res add tax.

(Micro-Trouncer Pictured to Left.) To order Maxon's Top-Of-The-Line, DRO Circuit Radar Detector with Mute, 4 Second LED Meter Hold, Dark Switch, Cordless Battery Operation (6 AA Ni-Cad Batteries Included) with Windshield, Dash, and Visor mounts and 2 power/charging Cords risk free with your credit card, call toll free or send your check for this revolutionary \$249 suggested retail detector at DAK's market breaking price of just \$149⁹⁰ (\$6 P&H) Order No. 6170.

OK Escort, it's up to you. We've got \$20,000 that says you can't beat Maxon on the road. Your answer, please?

Escort and Passport are registered trademarks of Cincinnati Microwave. Rashid VRSS, and Rashid Radar Safety Brake are registered trademarks of Vehicle Radar Safety Systems, Inc.

DAK INDUSTRIES INC.
 Call Toll Free For Credit Card Orders Only
 24 Hours A Day 7 Days A Week
1-800-325-0800
 For Toll Free Information, Call 6AM-5PM Monday-Friday PST
Technical Information . . . 1-800-272-3200
Any Other Inquiries . . . 1-800-423-2866
8200 Remmet Ave., Canoga Park, CA 91304

HDTV UPDATE

BRIAN C. FENTON MANAGING EDITOR

HDTV—sooner than you think


YOU COULD BE WATCHING HIGH-DEFINITION television in your home in as little as five years, thanks to a breakthrough from the David Sarnoff Research Center (formerly RCA Labs). They announced—in collaboration with NBC and GE/RCA Consumer Electronics—the development of a new high-definition television system called ACTV or *Advanced Compatible TeleVision*. It's the most exciting thing to happen to TV since color.

ACTV is a single-channel, NTSC-compatible, widescreen, extended-definition television system. It has features that set it apart from any of the other high-definition systems proposed to date, including NHK's MUSE, Philips' HD-MAC, or the Del Rey Group's HD-NTSC. (For back-

ground information on those HDTV systems, see the August 1987 issue of **Radio-Electronics**.)

The most important feature of ACTV is that the high-definition picture can be delivered within the existing 6-MHz NTSC broadcast channel. And ACTV is completely compatible with today's TV sets. Of course, a standard NTSC receiver can't display a high-definition picture, but it can display an ACTV picture with the same quality as it can display an NTSC one today.

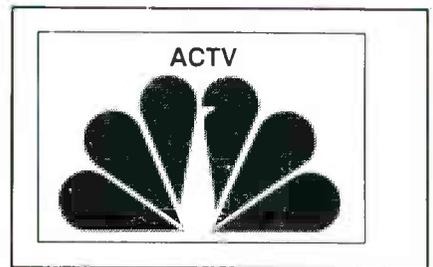On the other hand, a high-definition ACTV receiver would display a picture with 1050 lines per frame (that's double the 525 we get today). Its aspect ratio—the ratio of the picture's width to its height—is 5:3,



which is close to that of motion pictures, and a far cry from NTSC's 4:3 aspect ratio.

How it works

Figure 1 shows how ACTV delivers what no other system has been able to. The process starts with a high-definition signal, which is separated into four components. The four components are processed and recombined into a single NTSC-compatible signal for both standard and ATSC receivers.

The first component of the high-definition signal is the main NTSC signal, which contains the center panel of the widescreen picture. The low-frequency information of the side panels is also contained in the first


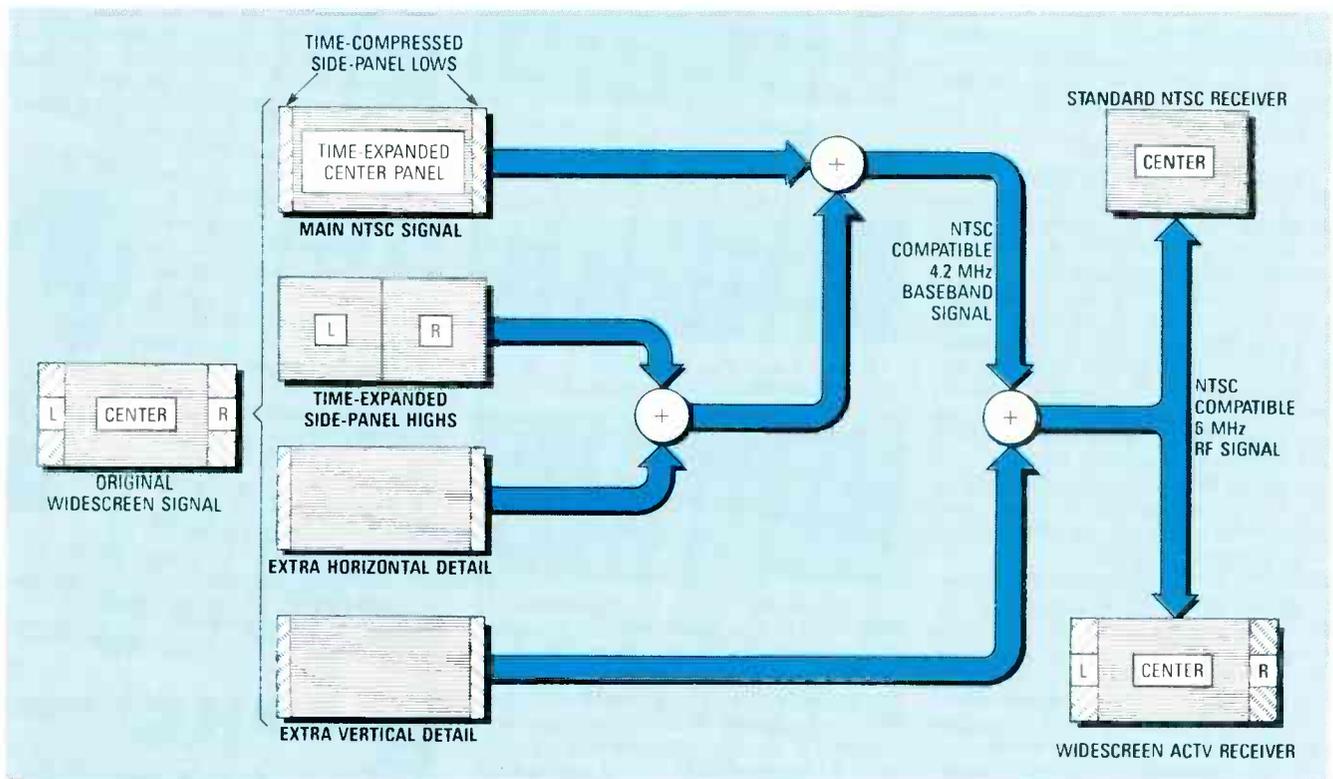


FIG. 1—THE ACTV SIGNAL starts with a widescreen picture that is separated into four components. Those components are digitally processed and combined using quadrature modulation techniques into an NTSC-compatible 6-MHz RF signal.

R-E Engineering Admart

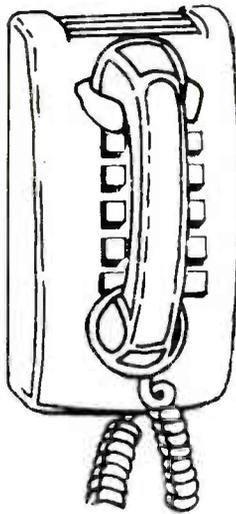Rates: Ads are 2 1/4" x 2 7/8". One insertion \$825. Six insertions \$800 each. Twelve insertions \$775 each. Closing date same as regular rate card. Send order with remittance to Engineering Admart, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. Only 100% Engineering ads are accepted for this Admart.



CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$800.00 per each insertion.
- Reaches 245,824 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Engineering Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

DISK SERVICE MANUAL \$20

Maintain, Repair, Adjust, Align Drives without special equipment or software. 5.25", 8" and 3.5". IBM-PC/AT, Compaq, Apple, Commodore, Kaypro, Epson, Tandy, Atari, TI, HP, DEC, other systems. Dozen Chapters. 100+ Photos, Figures. All drives need servicing. Save \$\$\$!

COMPUTER PHREAKING \$15

Dozens of Computer Crime and Abuse Methods, and Countermeasures. How systems are penetrated. BBS Advice; Password Defeats; Van Eck, TEMPEST Methods; CrossTalk Attack; more. 230 Phreak-Term Glossary.

ABSOLUTE COMPUTER SECURITY \$15

Dozens of Simple, Versatile, Very Secure Computer Security Methods, Tips. Invulnerable Cipher Program. Plus \$1,000 CONTEST rules. Manual + ME/PCDOS Disk (COM, BAS, Source Code, Test Files) - \$25.

HIGH VOLTAGE DEVICES \$15

STUNNER; ZAPPER; BLASTER; JAMMER; FLASHER; STIMULATOR; JACOBS LADDER; OZONE; PLASMA and VAN DE GRAAFF GENERATOR; GEIGER COUNTER; FENCE CHARGER Plans. Stocking!

PHONE COLOR BOXES \$15

Designed by Phreakers! 15 Phone Color Boxes described. Dozens of Circuits. Plus Call Forwarding, Conferencing! From sixties versions to modern, including computer simulations. Use not suggested.

RADIONICS MANUAL \$20

Comprehensive Manual on ElectroMagnetic Therapies, Diagnosis, Preventions. Dozens of Plans, Circuits. Includes FDA-approved.

ELECTROMAGNETIC BRAINBLASTER \$20

Comprehensive Manual on ElectroMagnetic Weapons and Laboratory Devices. Dozens of Plans, Circuits. A Must Have! Mind-Boggling!

By John Williams, former Senior Engineer (Lockheed); CS Professor (NMSU). FREE CATALOG with Order (else \$1), describes 100 manuals. Postage included with price (CODs are \$5 extra). (505-434-0234).

CONSUMERTRONICS

2011 CRESCENT DR. P.O. DRAWER 537
ALAMOGORDO, NM 88310

CIRCLE 198 ON FREE INFORMATION CARD

FCC LICENSE PREPARATION

The FCC has revised and updated the commercial license exam. The NEW EXAM covers updated marine and aviation rules and regulations, transistor and digital circuitry. THE GENERAL RADIOTELEPHONE OPERATOR LICENSE - STUDY GUIDE contains the necessary preparation for ONLY \$25.00.


WPT PUBLICATIONS
979 Young Street, Suite E
Woodburn, Oregon 97071
Phone (503) 981-6122

CIRCLE 185 ON FREE INFORMATION CARD

117 PRACTICAL IC PROJECTS BUILD YOU CAN


2645T-117 PRACTICAL IC PROJECTS YOU CAN BUILD.....

\$10.95. Dozens of fully-tested, ready-to-build circuits you can put together from readily-available, low cost IC's! There are a total of 117 IC circuits ranging from an audio mixer and a signal splitter to a tape-deck amplifier and a top-octave generator organ! From TAB Books. To order your copy send \$10.95 plus \$2.75 shipping to Electronic Technology Today Inc., P.O. Box 240, Massapequa Park, NY 11762-0240

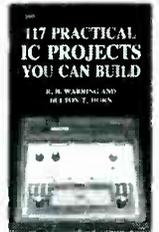

LINEAR IC EQUIVALENTS & PIN CONNECTIONS

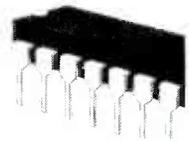Linear IC Equivalents and Pin Connections



BP141—Shows equivalents & pin connections of a popular user-oriented selection of European, American and Japanese linear IC's 320 pages, 8 x 10 inches. \$12.50 Plus \$2.75 shipping. ELECTRONIC TECHNOLOGY TODAY INC., PO Box 240, Massapequa Park, New York 11762-0240.

component, but it is time-compressed and forms a narrow band on each side of the picture (which is hidden by the normal overscan in home receivers.)

The second component of the ACTV signal contains the high-frequency information of the side panels. It is combined with the third component, the extra horizontal detail. Those three are digitally processed and then combined into a single NTSC-compatible baseband signal, which is then combined with the fourth component, the extra vertical detail, on the RF carrier.

NTSC still survives

Today's NTSC standard was developed in the early 1940's by the National Television Standards Com-

mittee. Considering that the standard was developed for black-and-white TV, it is truly amazing that the advances in TV technology we've seen since that time—such as color, stereo sound, and teletext—have been developed within its framework.


With the investment in television transmitting and receiving equipment estimated at \$100-billion, a compatible system is certainly desirable. But until the Sarnoff/NBC announcement, most had considered that goal to be unachievable.

NTSC compatibility is a tremendous benefit to viewers and broadcasters alike. It gives a consumer the option of keeping his current TV set—with no degradation in picture quality—or of buying a new TV set to


receive the improved picture. And each broadcaster can decide when he is ready for the change.

But not all of the players in the HDTV game are concerned with compatibility. The cable-TV industry, for example, does not have the same spectrum-conservation concerns as TV broadcasters. It's possible that they wouldn't mind having an exclusive HDTV system to call their own. In fact, the cable industry is studying a plan to use fiberoptics to distribute programming—perhaps high-definition cable programming. That, in the words of a cable-industry executive, would give cable "enormous advantages over broadcasting."

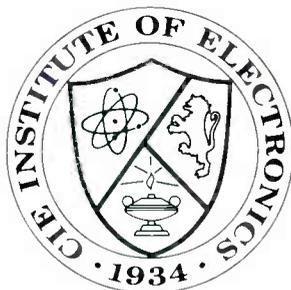The Sarnoff research center has
continued on page 66



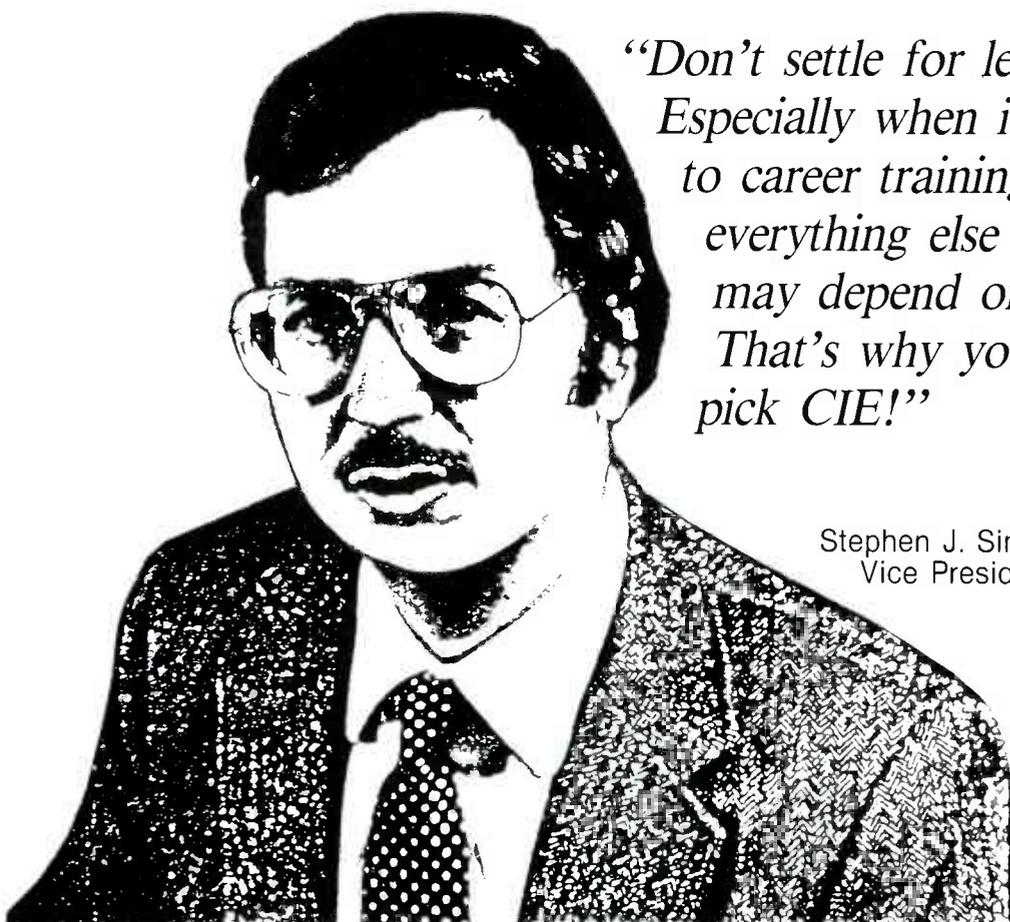“If you’re going to learn electronics, you might as well learn it right!”



*“Don’t settle for less.
Especially when it comes
to career training...because
everything else in your life
may depend on it.
That’s why you ought to
pick CIE!”*

Stephen J. Simcic
Vice President, Academic Affairs

You've probably seen advertisements from other electronic schools. Maybe you think they're all the same. They're not!

CIE is the largest independent home study school in the world that specializes exclusively in electronics.

Meet the Electronics Specialists.

When you pick an electronics school, you're getting ready to invest some time and money. And your whole future depends on the education you get in return.

That's why it makes so much sense to go with number one . . . with the specialists . . . with CIE!

There's no such thing as bargain education.

If you talk with some of our graduates, chances are you'd find a lot of them shopped around for their training. Not for the lowest priced but for the best. They pretty much knew what was available when they picked CIE as number one.

We don't promise you the moon. We do promise you a proven way to build valuable career skills. The CIE faculty and staff are dedicated to that. When you graduate, your diploma shows employers you know what you're about. Today, it's pretty hard to put a price on that.

Because we're specialists we have to stay ahead.

At CIE, we've got a position of leadership to maintain. Here are some of the ways we hang onto it . . .

Programmed Learning

That's exactly what happens with CIE's Auto-Programmed Lessons. Each lesson uses famous "programmed learning" methods to teach you important principles. You explore them, master them completely, before you start to apply them. You thoroughly understand each step before you go on to the next. You learn at your own pace.

And, beyond theory, some courses come fully equipped with electronics gear (the things you see in technical magazines) to actually let you perform hundreds of "hands-on" experiments.

Experienced specialists work closely with you.


Even though you study at home, you are not alone! Each time you return a completed lesson, you can be sure it will be reviewed, graded, and returned with appropriate instructional help. When you need additional individual help, you get it fast and in writing from the faculty technical specialist best qualified to answer your question in terms you can understand.

Pick the pace that's right for you.

CIE understands people need to learn at their own pace. There's no pressure to keep up . . . no slow learners hold you back. If you're a beginner, you start with the basics. If you already know some electronics, you move ahead to your own level.

Enjoy the promptness of CIE's "same day" grading cycle.

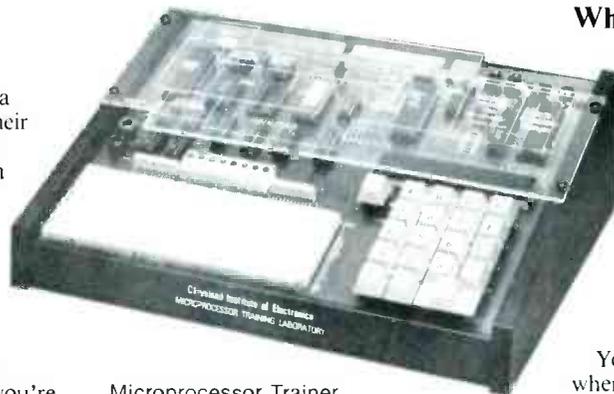When we receive your lesson before noon Monday through Saturday, we grade it and mail it back the same day. You find out quickly how well you're doing!



Microprocessor Trainer

State-of-the-art Laboratory Equipment

Some courses feature the CIE Microprocessor Training Laboratory. An integral part of computers, microprocessor technology is used in many phases of business, including service and manufacturing industries.

The MTL gives you the opportunity to program it and interface it with LED displays, memory devices, and switches. You'll gain all the practical experience needed to work with state-of-the-art equipment of today and tomorrow.

CIE offers you an Associate Degree.

One of the best credentials you can have in electronics — or any other career field — is a college degree. That's why CIE gives you the opportunity to earn an Associate in Applied Science in Electronics Engineering Technology. Any CIE career course can offer you credit toward the degree — more than half of the number needed in some cases.

"Cleveland Institute of Electronics is the only accredited institution of higher learning offering an Associate Degree program with tuition based on actual study time used. The faster you complete your degree assignments, the less your overall tuition."

Steve Simcic
Vice-President Academic Affairs

Which CIE Training fits you?

Beginner? Intermediate? Advanced? CIE home study courses are designed for ambitious people at all entry levels. People who may have:

1. No previous electronics knowledge, but do have an interest in it;
2. Some basic knowledge or experience in electronics;
3. In-depth working experience or prior training in electronics.

You can start where you fit and fit where you start, then go on from there to your Diploma, Associate Degree, and career.

Today is the day. Send now.

Fill in and return the postage-free card attached. If some ambitious person has removed it, cut out and mail the coupon. You'll get a FREE school catalog plus complete information on independent home study. For your convenience, we'll try to have a CIE representative contact you to answer any questions you may have.

Mail in the coupon below or, if you prefer, call toll-free 1-800-321-2155 (in Ohio, 1-800-523-9109).

CIE

ARE-76
Cleveland Institute of Electronics, Inc.
 1776 East 17th Street, Cleveland, Ohio 44114
Accredited Member National Home Study Council

YES...I want to learn from the specialists in electronics — CIE. Send me my FREE CIE school catalog...including details about the Associate Degree program... plus my FREE package of home study information.

Print Name _____

Address _____ Apt. _____

City _____ State _____ Zip _____

Age _____ Area Code/Phone No. _____/_____

Check box for G.I. Bill/bulletin on Educational Benefits: Veteran Active Duty

MAIL TODAY!
CIRCLE 60 ON FREE INFORMATION CARD

ASK R-E

AUTOMOBILE BATTERY MONITOR

In Alaska, where I live, it's important to keep a constant watch on the car's battery voltage. My new car's dashboard has digital instrument displays, but it lacks a voltmeter. Obviously, I would prefer to add a digital device. Any suggestions?—F.R., Juneau, Alaska

Figure 1 shows a simple and inexpensive digital monitor system that was published in the December 1976 issue of *Electronic Engineering*. Three colored LED's keep track of the car's electrical system voltage. The circuit uses four switching transistors, a couple of Zener diodes, and red, yellow, and green LED's to indicate four voltage levels.

When the red LED alone is lit, the battery voltage is below 10. That is a serious condition and indicates an electrical-system malfunction. At 11 volts, both the red and the yellow LED's are lit. At 12 volts, the yellow LED alone is lit. The yellow and green LED's both are lit when the voltage reaches 13. Above 14 volts, only the green LED is on.

WHAT'S A CROWBAR?

I've seen the word "crowbar" used in an electronics context. I don't know what it means and I can't find a definition that sound reasonable. A friend says that it amounts to throwing a short-circuit across the output of a power supply. Is that correct?—T.B., Greensboro, NC

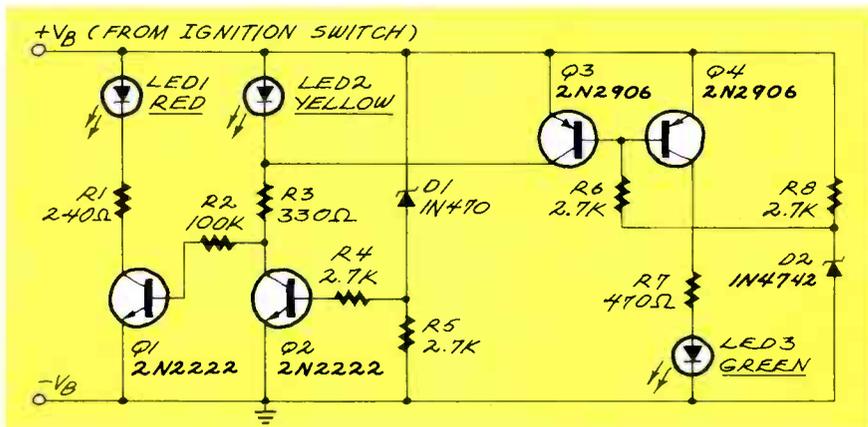


FIG. 1

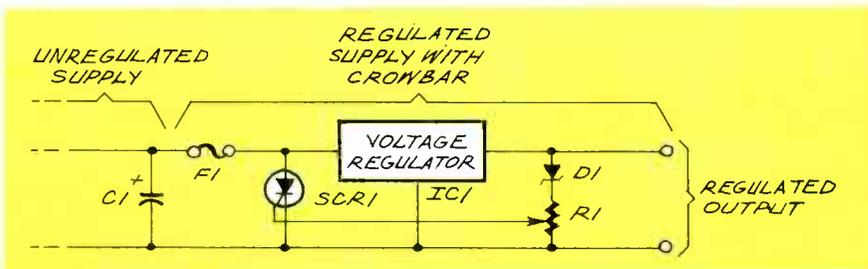


FIG. 2

WRITE TO:

ASK R-E
Radio-Electronics
500-B Bi-County Blvd.
Farmingdale, NY 11735

A "crowbar" is an electronic circuit that monitors the output voltage of a regulated power supply and immediately throws a short circuit or "crowbar" across the output whenever the voltage rises above a preset level.

Many semiconductor devices are designed to operate from supply voltages that are only a few volts lower than an absolute maximum voltage. For example, the nominal supply voltage (V_{CC}) for all TTL devices is +5 volts with a $\pm 5\%$ (250 mV) tolerance, while their absolute maximum rating is 7 volts. Above that level, a TTL device can be destroyed or its serviceability seriously impaired.

A 5-volt regulated supply is often derived from an unregulated 8-volt or higher DC supply. If the series-voltage regulator fails, the full unregulated voltage is applied to the load, destroying any TTL or other voltage-sensitive devices.

Figure 2 shows a series-voltage regulator with crowbar components (fuse F1, SCR1, D1, and adjustable resistor R1) added. The Zener diode is selected for a voltage rating just below the specified V_{CC} . Resistor R1 is adjusted so that the SCR gate voltage remains just below the conduction voltage as long as the regulated output voltage remains below 5.85.

If the output voltage rises above the preset limit, the SCR fires and short-circuits the unregulated supply's output and, almost instantaneously, removes the voltage from the logic load. The fuse blows and protects the components in the unregulated supply from possible damage caused by the short circuit.

The SCR is used because of its
continued on page 33

Eliminate Costly Guesswork And Interpretation Errors In LCR Testing!



- **Completely Analyze Capacitors**
From 1pf to 20F for value, leakage, Dielectric absorption and ESR.
- **Thoroughly Test Inductors**
From .1uH to 20H for value, opens and shorts, even to one shorted turn!
- **Dynamically Test For Resistance**
Measure resistances up to 1,000 Megohms, and leakage down to 1 microamp with 1,000 volts applied potential.
- **Good/Bad Tests Eliminate Guesswork**
Exclusive good/bad readout gives you easy to read, reliable tests to meet EIA and industry standards.
- **100% Portable**
Works all day on one charge for testing in the field or on the bench.

LC77 AUTO-Z™
Capacitor-Inductor Analyzer
\$1895 Patented

SEE A&P
BUS-COMPATIBLE

THE 2 STANDARD

100% American Made

CIRCLE 176 ON FREE INFORMATION CARD

SENCORE

Call **1-800-843-3338** today.

In Canada call **1-800-851-8866** today.

LETTERS



DIGITAL DASHBOARD

I would like to notify builders of the "Digital Tachometer" and "Digital Speedometer" (*Radio-Electronics*, June and July 1987) of a fix for a possible problem that they may have encountered.

After several units were built using IC's from different manufacturers, a problem developed that caused the digital readout to occasionally jump to a reading of "000" during normal operation. That timing problem can be corrected by soldering a .001- μ F capacitor across pins 8 and 10 of IC7 on the tachometer; across pins 11 and 13 of IC5 on the speedometer.

The cause of the problem is that the MC14553 needs a minimum amount of time between the latch and reset pulses. If the CD4001 NOR gate used to build the projects is too fast—has too little propagation delay—the reset pulse will arrive before the internal latches have stabilized and locked in the current reading.


My apologies go out to anyone who has been struggling with that problem.

ROSS ORTMAN
Dakota Digital

CELLULAR PHONES

It was good to see my article, "All About Cellular Telephone," in the September issue of *Radio-Electronics*. You need all the information you can get to keep up with that rapidly expanding sphere of communications.

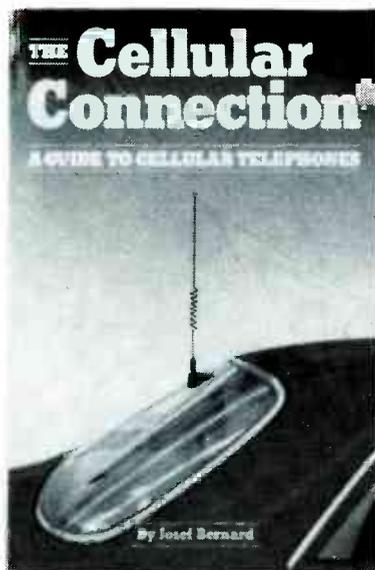Readers interested in learning still more about cellular phones, and the cellular system in general, will find what they're looking for in my book, *A Guide to Cellular Telephones*, available at Radio Shack stores. If you can't find it locally, a



basically similar one, *The Cellular Connection*, can be purchased by mail from Quantum Publishing, Inc., Box 310, Mendocino, CA 95460. The cost is \$9.95, plus \$1.50 for postage and handling.

Keep up the good work in informing the public of what's going on, and what's coming up, in the world of electronics.

JOSEF BERNARD

AUDIO DROPOUTS

Larry Klein's theory as to why there is dropout of audio signal at the beginning of cassette tapes ("Audio Update," *Radio-Electronics*, August 1987) was interesting. Subsonic overload could well be the problem for some—or most—cases. Having suffered that problem myself, I decided to investigate, and I've come up with my own theory about the broken-up audio at the beginning of cassette tapes.

I was using high-quality 90-minute audio-cassette tapes to record source material. When replaying them, the audio would sound un-

even and slightly garbled near the beginning of each tape, and would sometimes blank out very briefly. Invariably, the audio dropouts occurred only at the start of the tape, whether or not that corresponded to the start of the record. At the instant the dropout occurred, I stopped and removed the tape to look at it. What I found each time, on approximately a dozen tapes, was that at the instant of the dropout there were little lines, resembling thin ridges or dents, crossing the recording tape in the middle of the cassette shell (where the tape would be above the tape head).

Take out a cassette and examine the first few inches of tape past the leader and you'll see what I'm referring to. I never had a dropout occur where there was no dent. Those dents apparently make the tape briefly lose contact with the head, causing the dropout.

As far as I can determine, the dents are caused by the overlap of the tape when it is being wound onto the hub in layers. It is apparently due to the non-uniform thickness where the leader attaches to the recording tape, because the lines seem to align with the places of thickness-change in the leader/tape junction area. As more layers are wound on, the effect would, of course, decrease. That would explain why the dents and dropouts do not occur in the middle of the tape. Does that sound reasonable?

MARK S. HAYWORTH
Tuscon, AZ

Mr. Hayworth's specific problem—and its cause—are well explained in his letter. I'm surprised that any better-grade cassettes manifest the problem, as most

manufacturers take special precautions to avoid bumps where the tape is attached to the leader or hub. Subsonic overload is, nevertheless, the major cause of the dropout symptoms that I described in the August issue.—Larry Klein, Audio Editor

BLUE BOXES

Having just read Herb Friedman's article, "The Blue Box and Ma Bell," (Radio-Electronics, November 1987) I am convinced that he knows very little about Automatic Message Accounting (AMA) in particular, and the phone company's use of it in general.

For instance, customer billing through the use of electromechanical meters has been used since the turn of the century. The photographing of the meters started in the early 1920's. AMA came into being in 1948, as a natural adjunct to a new telephone-switching system, namely Number Five Crossbar. (Number One Crossbar used the meters for billing at that time, as did other types of switching systems.) Thus, the introduction of AMA was evolutionary—not a direct result of customer complaints.

The AMA system was not designed to record the details of local calls. It simply recorded the number of message units for message-rate subscribers, exactly as the electromechanical meters did. Flat-rate local calls were by far the most numerous, and they didn't need to be recorded because there was no charge associated with them. (Subscribers served by AMA could have their billing complaints resolved by being connected to a special circuit that forced the AMA to record local-call details.) Knowing that, it seems that Ma Bell was telling the truth when she said there was no detailed record on local calls.

One AMA billing center handled the output of scores of AMA offices on a three-shift basis using electromechanical computers. To imply that sorting through millions of call records to trace criminal or obscene calls was a simple task shows a lack of familiarity with the system. Besides, most obscene calls are of local origin, and no record is generated.

HITACHI SCOPES AT DISCOUNT PRICES!

20MHZ



Model V212 \$475

Model V-212 20MHZ Dual Channel (1mV Sens.) \$475
 Model V-422 40MHZ Dual Channel (1mV Sens.) \$699
 Model V-425 40MHZ Dual Channel (with cursor) \$795
 Model V-660 60MHZ Dual Channel (Delayed Sweep) \$990
 Model V-1060 100MHZ Dual Channel (Delayed Sweep) \$1,375
 All above scopes have a 3 year warranty on parts and labor


100MHZ



Model V1060 \$1,375

15-25%
OFF LIST
PRICE

ELENCO PRODUCTS AT DISCOUNT PRICES!

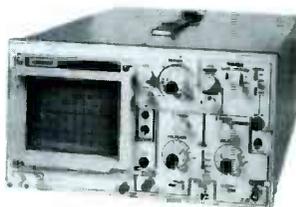

MO-1253
40MHz
Dual Trace
12KV HV
Delayed Sweep
\$550



20MHz DUAL TRACE OSCILLOSCOPE

35MHz DUAL TRACE OSCILLOSCOPE

\$349 MO-1251

\$498 MO-1252

Top quality scopes at a very reasonable price. Contains all the desired features. Elenco's 2 year guarantee assures you of continuous service. Two 1x, 10x probes, diagrams and manual included. Write for specs. 100MHZ test probes, switchable 1x, 10x, Ref. (Complete w/ 5 accessories) Fits most scopes \$22

MULTIMETER with CAPACITANCE AND TRANSISTOR TESTER
 Model CM-1500A \$58
 Reads Volts, Ohms, Current, Capacitors, Transistors & Diodes w/Case

TRUE RMS 4 1/2 DIGIT MULTIMETER
 Model M-7000 \$135
 .05% DC Accuracy
 .1% Resistance with Freq. Counter & Deluxe Case

Auto Ranging plus Manual Ranging
 3 1/2 Digit Meter
 28 Functions
 Fully protected
 M-1180 .7% Acy \$36.95
 M-1182 .25% Acy \$39.95
 M-1181 .1% Acy \$42.95

GF-8016 FUNCTION GENERATOR with Freq. Counter
 \$239
 • Sine, Square, Triangle
 • Pulse, Ramp, 2 to 2MHz
 • Frequency .1 thru 10MHz
 GF-8015 without Freq. Meter \$179

10MHZ OSCILLOSCOPE
 \$239
 Model S-3000
 • 10MHz DC or AC
 • Triggered Sweep
 • Calibrated Vert & Hor
 • Reads Volts & Freq

BREADBOARD
 Model 9436 Shown
 9430 1,100 pins \$15
 9434 2,170 pins \$25
 9436 2,860 pins \$35

DIGITAL TRIPLE POWER SUPPLY
 Model XP-765 \$239
 0-20V @ 1A
 0-20V @ 1A
 5V @ 5A
 Fully Regulated, Short Circuit Protected with 2 Limit Cont. 3 Separate Supplies
 XP-660 with Analog Meters \$169.50

DIGITAL LCR METER
 \$138
 Model LC-1800
 Measures: Inductors, Capacitors, Resistors

50MHz LOGIC PROBE
 20 nsec with memory LP-700
 Logic Pulsar LP-600 \$23

QUAD POWER SUPPLY
 Model XP-580 \$59.95
 Fully regulated and short circuit protected
 2:20V @ 2A
 12V @ 1A
 +5V @ 3A
 -5V @ .4A

MULTI-FUNCTION COUNTERS
 F-1000 1.2GH \$259
 F-100 120MH \$179
 Frequency, Period, Totalize, Self Check with High-Stabilized Crystal Oven Oscillator, 8 Digit LED Display

C&S SALES INC., 1245 Rosewood Dr. Deerfield, IL 60015 800-292-7711 (312) 459-9040 ASK FOR CATALOG
 15 DAY MONEY BACK GUARANTEE
 2 Year Limited Guarantee! Add 5% for Postage (\$10 max), IL Res., 7% Tax
 CIRCLE 109 ON FREE INFORMATION CARD

IF YOU WANT A BETTER COMPUTER BUILD IT YOURSELF.

Heath makes building the powerful 386 computer quick, fun, easy... and a great value.


Now you can own the fastest, most powerful home computer available today - at an affordable cost. Just by building it yourself.

Introducing the Heathkit H-386 Desktop Computer. With its powerful 32-bit processor, 16 MHz computing speed and "zero wait" technology,



the H-386 can breeze through complex calculations in seconds.

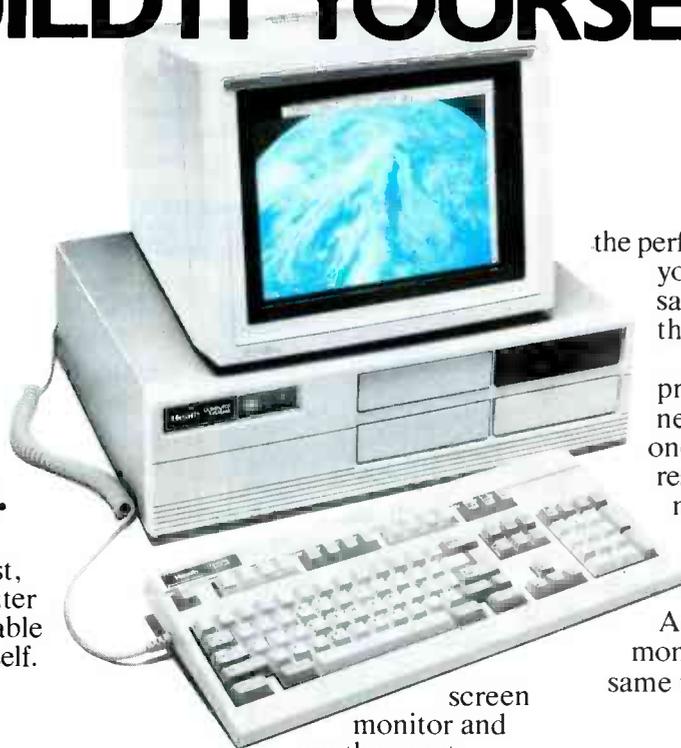Every INTEL 80386 micro-processor used in our H-386 is 100% tested for all functions. And you get superb graphics because one video port provides dazzling 640-by-480 color on Zenith's new flat



screen monitor and another port drives EGA, CGA and TTL monochrome monitors. Both ports automatically emulate common video formats for easy system configuration.

Designed for people using large spreadsheets, CAD/CAM or other computation-intensive applications, or anyone who simply wants to own the newest, most powerful hardware on the market, the Heathkit H-386 can be assembled easily and quickly. One or two evenings is all it takes, and no special tools or equipment are required.

In the bargain, you get the satisfaction of having built a powerful computer system all by yourself, and the confidence that this exciting product will deliver all

the performance and dependability you expect. At a significant savings over comparable off-the-shelf brands.

What's more, all Heathkit products are backed by a newly extended, limited one-year warranty, highly respected manuals and technical consultation service.

So if you want a better computer, build it yourself. Impress your friends.

And save money at the same time.



To order the new Heathkit H-386 Desktop Computer, simply call toll-free **1-800-253-0570**. Ask for operator 301. Use your Visa, MasterCard or Heath Revolving Charge. Or call **616-982-3614** for the Heath/Zenith Computers and Electronics store location nearest you.

For more information on all our quality kits, send now for your free four-color Heathkit catalog. **Write Heath Company, Dept. 020-614, Benton Harbor, MI 49022.**

Prices, product availability and specifications are subject to change without notice.

Heathkit®

Heath
Company

Heathkit is a registered trademark of Heath Company, a subsidiary of Zenith Electronics Corporation.

©1987, Heath Company

CIRCLE 86 ON FREE INFORMATION CARD

www.americanradiohistory.com

Finally, the mention of service observing and the reference to Senator Dodd had nothing to do with the Blue-Box story. It was Senator Long of Missouri who conducted the investigation to which the article referred. Ma Bell had many types of switching equipment and a variety of crossbar switching types. I have never seen detailed instructions or even a so-called manual. (Switching offices were described in documents known as "Bell System Practices.")

RICHARD R. PLUM

*Bell Communications Research
Red Bank, NJ 07701-7020*

The manual shown in Fig. 1 of the article is a Bell manual, and it details the AMA billing procedures—including detailed local calls. The Number Five Crossbar manual had the circuit and recommended monitoring procedure for operators.

In the New York area, at least, the local office had the AMA. It wasn't handled by just one billing center.

Senator Dodd handled the investigation of the Westchester County Fire Department telephone delay, at which subscriber monitoring was first mentioned in the media.—Herb Friedman

FREEDOM OF PRESS

Thank you very much for your October 1987 cover story, "Build This Laser Listener." I strongly disagree with Mr. Mim's criticisms (Letters, November 1987.) The people have a right to know everything. Crooks have access to the information, so nothing is lost—and much is gained—by letting the rest of us know also. We gain the awareness of the existence of those devices, and how they are designed. Design details are critical because they let you know how the device is used, how it looks, and what its capabilities and limitations are.

It's refreshing to know that 200 years after the signing of our Constitution, you can still find freedom of the press alive and well in publications such as **Radio-Electronics**. You also provide an important service by helping to keep electronics a rewarding and fascinating profession and hobby,

and by keeping the public informed about new technologies, products, and techniques. With the ever-increasing technological competition world-wide, and the slippage of our educational system, you do a tremendous service to our country.

I also found "The Blue Box and Ma Bell" (**Radio-Electronics**, November 1987) to be well-written and most informative. However, it has one glaring mistake—the Red Box, also described in the article, is the Black Box. The Red Box was used to generate tones that emulated those made by coins deposited in payphones to place free payphone calls. I would have liked to see a little on Captain Crunch and others who "pioneered" boxing; more explanation on the effects of ESS, automatic tone monitoring and computerized billing on boxing; and at least a tabulation of the many other phone color boxes.

JOHN J. WILLIAMS
Alamogordo, NM

SURFACE-MOUNT TECHNOLOGY

The first article in your November 1987 special section on Surface Mount Technology (SMT) correctly points out the advantages of working with components that have no wire leads to cut, bend, etc. If SMC's do become the standard in the 1990's, then home experimenters, as well as engineers working in R&D labs, will need a method to quickly evaluate circuits—as we do now with breadboard matrixes designed for "standard size" components (100-mil spacing.) The tremendous savings in time and money that breadboarding provides cannot be overstated.

A possible solution might be a series of rugged, close-tolerance, machined sockets made to fit each SOP, combined with a new breadboard matrix with 50-mil centers to match the new SO devices. Any reluctance to familiarize oneself with SMT would be greatly reduced if a system for evaluating those circuits designed with SMC's could be demonstrated as practical.


DANIEL KATZNELSON
*Danielson Electronics
Willingboro, NJ*

R-E

TALK IS CHEAP.

Have you heard? For less than \$90 your AT or XT-compatible computer can talk! All it needs is the HV-2000 Computer Voice Kit from Heathkit.

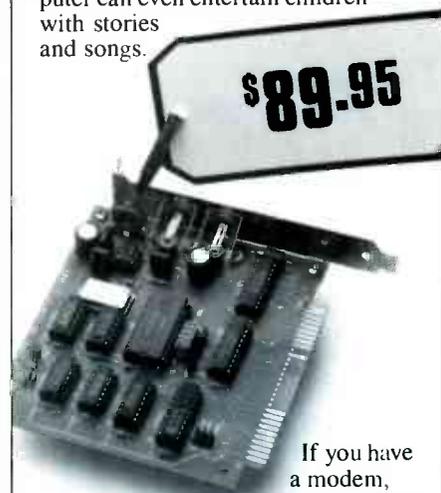Reading letters, transcriptions and computerized instruction can be easier and quicker than you ever thought possible. Computer games gain a new dimension. Your computer can even entertain children with stories and songs.



\$89.95

If you have a modem, the HV-2000

Computer Voice will allow your computer to recite reference and research information from time-sharing services. Or, speak radio transmitted ASCII information.

The HV-2000 Computer Voice Card, containing speech synthesizer and audio amplifier, plugs into any AT or XT-compatible computer's expansion slot. An external speaker is also included. Versatile, Heath-developed software gives you a wide variety of voices and easy interface to high and low level languages.

The HV-2000 Computer Voice. At less than \$90, talk IS cheap. To order, call toll-free 1-800-253-0570. Ask for operator 301. Use your Visa, MasterCard or Heath Revolving Charge card. Or call 616-982-3614 for the nearest store location.

Heathkit®

Heath
Company

Benton Harbor, MI 49022


Prices, product availability and specifications are subject to change without notice.

© 1987, Heath Company

CIRCLE 86 ON FREE INFORMATION CARD

TAKE ANY ONE OF THESE HANDBOOKS — when you join the ELECTRONICS AND

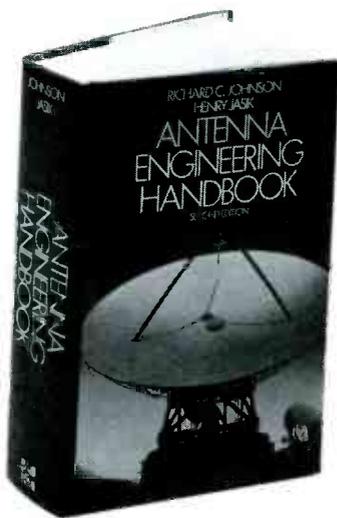- your one source for engineering books from over 100 different publishers
- the latest and best information in your field
- discounts of up to 40% off publishers' list prices



322/910

Publisher's Price \$110.00

ANTENNA ENGINEERING HANDBOOK, Second Edition

Edited by R. C. Johnson and H. Jasik


- 1,408 pages, 946 illustrations
- covers all types of antennas currently in use with a separate chapter devoted to each
- provides detailed data on physical fundamentals, operating principles, design techniques, and performance data
- up-to-the-minute information on antenna applications
- a must for those involved in any phase of antenna engineering

Publisher's Price \$64.50


STANDARD HANDBOOK OF ENGINEERING CALCULATIONS, Second Edition

By T. G. Hicks

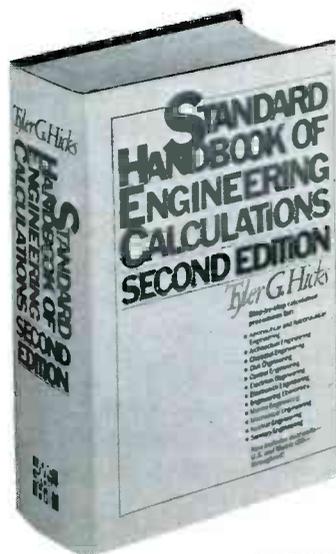- 1,468 pages, 793 illustrations, 499 tables
- puts more than 1,100 specific calculation procedures at your fingertips
- every calculation procedure gives the exact, numbered steps to follow for a quick, accurate solution
- virtually all procedures can be easily programmed on your PC or calculator
- uses USCS and SI units in all calculation procedures



287/35X

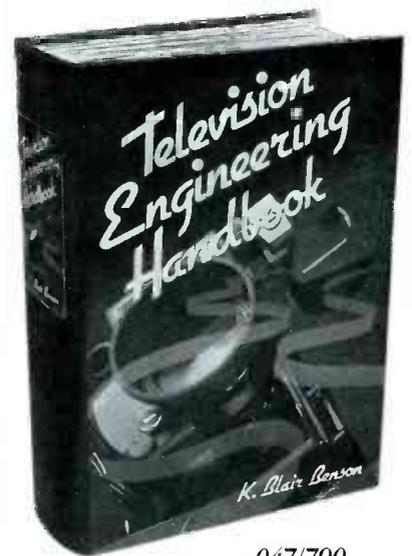

047/790


Publisher's Price \$89.50

TELEVISION ENGINEERING HANDBOOK

Edited by K. B. Benson

- 1,478 pages, 1,091 illustrations
- packed with all the technical information today's engineer needs to design, operate, and maintain every type of television equipment
- extensive coverage of receivers, broadcast equipment, video tape recording, video disc recording, and the latest technological advances
- provides television system and industry standards for the U.S. and other countries
- the most comprehensive book on the subject of television engineering

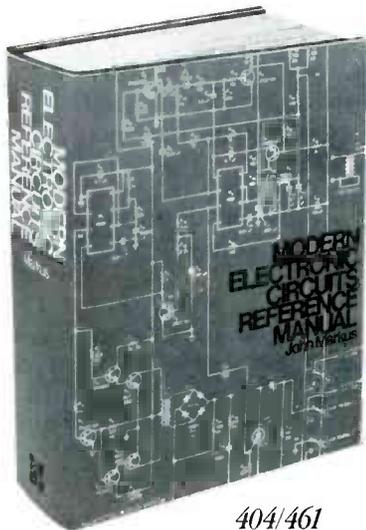FOR ONLY \$14.95 — VALUES UP TO \$110.00 CONTROL ENGINEERS' BOOK CLUB®



404/461

Publisher's Price \$82.50

MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL

By J. T. Markus

- 1,264 pages, 3,666 circuit diagrams
- a handy, desktop reference with 103 chapters organized by "family" grouping
- filled with predesigned and use-tested circuits to save you production time and money
- includes concise summaries of all the recent applications notes, journal articles, and reports on each circuit, efficiently organized and indexed for the practicing engineer



4 reasons to join today!

1. Best and newest books from ALL publishers! Books are selected from a wide range of publishers by expert editors and consultants to give you continuing access to the best and latest books in your field.

2. Big savings! Build your library and save money, too! Savings range up to 40% off publishers' list prices.

3. Bonus books! You will immediately begin to participate in our Bonus Book Plan that allows you savings up to 70% off the publishers' prices of many professional and general interest books!

4. Convenience! 14-16 times a year (about once every 3-4 weeks) you receive the Club Bulletin FREE. It fully describes the Main Selection and alternate selections. A dated Reply Card is included. If you want the Main Selection, you simply do nothing — it will be shipped automatically. If you want an alternate selection — or no book at all — you simply indicate it on the Reply Card and return it by the date specified. You will have at least 10 days to decide. If, because of late delivery of the Bulletin you receive a Main Selection you do not want, you may return it for credit at the Club's expense.

As a Club member you agree only to the purchase of three additional books during your first year of membership. Membership may be discontinued by either you or the Club at any time after you have purchased the three additional books.

Publisher's Price \$89.00

ELECTRONICS ENGINEERS' HANDBOOK, Second Edition

By D. G. Fink and D. Christiansen

- 2,272 pages, 2,189 illustrations
- unrivaled for its completeness, authority, reliability and timeliness
- 80% new or extensively revised
- prepared by a staff of 173 expert contributors
- brings you more than 2,000 formulas and equations
- has over 2,500 bibliographic entries



209/812

FOR FASTER SERVICE IN ENROLLING CALL TOLL FREE 1-800-2-MCGRAW

McGraw-Hill Book Clubs
Electronics and Control Engineers' Book Club®
11 West 19th Street
4th floor
New York, NY 10011

Please enroll me as a member of the Electronics and Control Engineers' Book Club® and send me the book I have chosen for only \$14.95, plus local tax, postage, and handling. I agree to purchase a minimum of three additional books during my first year as outlined under the Club plan described in this ad. Membership in the club is cancellable by me or McGraw-Hill any time after the three book purchase requirement has been fulfilled. A shipping and handling charge is added to all shipments.

I wish to order the following book:

- ANTENNA ENGINEERING HANDBOOK (322/910)
- MODERN ELECTRONIC CIRCUITS REFERENCE MANUAL (404/461)
- ELECTRONICS ENGINEERS' HANDBOOK (209/812)
- TELEVISION ENGINEERING HANDBOOK (047/790)
- STANDARD HANDBOOK OF ENGINEERING CALCULATIONS (287/35X)

Signature: _____

Name: _____

Address/Apt. #: _____

City/State/Zip: _____

This order subject to acceptance by McGraw-Hill. Offer good only to new members. Foreign member acceptance subject to special conditions.

E33920

EQUIPMENT REPORTS

Heath GR-9009 Portable Color TV

A 9-inch set you can build yourself

CIRCLE 20 ON FREE INFORMATION CARD



COLOR TV'S USED TO BE AMONG THE most popular types of electronic kits. While they are not as popular as they once were, there are still a few models available. This month, we take a look at the model GR-9009 9-inch portable color-TV kit from the Heath Company (Benton Harbor, Michigan 49022).

The GR-9009 offers a most of the features that you would expect to find on a modern TV, such as a 178-channel tuning capability, quartz-controlled electronic tuning, programmable up/down channel scanning, and an auto-control color system. We'll say more about those features later. First, let's see what it's like to go and build a TV set.

Putting it together

The kit contains six major circuit boards or modules. Despite the fact that five of the six come pre-assembled and factory aligned, there is still plenty of work for the kit builder to do. We guess that it would take the average kit builder about 10 hours to assemble the GR-9009 from start to finish. We wouldn't recommend the kit to a rank beginner—some of the adjustments require working around high voltages. But if you have some electronics-building experience, a healthy respect for high

voltages, and some patience, you should have no trouble building the GR-9009.

The assembly work begins with the crosshatch generator board—the only circuit module that must be assembled from scratch. Heath couldn't make building that module any easier. Many of the parts are supplied on taped strips, in the order that they are called for in the assembly instructions. The most difficult task is wiring and assembling a pair of connectors that connect the crosshatch generator to the TV set's main module. Connecting the free ends of the wires to the main module is difficult, because that preassembled module has no provision for the connections. The six wires must be crimped and soldered to component leads on the main module.

That situation is not as strange as you might think. The pre-assembled modules are the same as are used in Zenith factory-built TV sets. Therefore, when you're finished building Heath's kit, you end up with what is essentially a Zenith TV, with the addition of a crosshatch generator that you must use for purity and convergence adjustments.

Most of the rest of the assembly work consists of mounting pre-assembled modules—such as the

keyboard/channel-display module, the tuner module, and the power-supply module—to the cabinet chassis. The picture tube must be mounted to the cabinet front, and the video-output module is mounted to the rear of the picture tube.

Once the modules are mounted, they have to be connected to each other. Pre-wired and labeled cable assemblies make what could be a very tedious job pretty easy. More important, pre-wired assemblies greatly reduce the chance of error.

When you complete the inter-module wiring, it's time to turn the TV on and begin the adjustment procedure. Those adjustments call for caution. Many of the heatsinks are electrically hot. And, of course, very high voltages (up to 18,000 volts) are present at several points of the set's circuitry. A respect for high voltages and a knowledge of electrical safety practices are the only essential ingredients that must be supplied by the kit builder.

Once the purity, centering, convergence, and other adjustments are completed, and the final assembly is finished, you're ready to sit back and enjoy some of the features that the GR-9009 has to offer.

Features of the set

The set's 178-channel tuner accepts signals, through a single 75-ohm connector, from VHF, UHF, MATV, standard CATV cable systems, or HRC (*Harmonically Related Carrier*) or IRC (*Incremental Coherent Carrier*) cable systems. The set has a fixed AFC and adds a "search" AFC mode that can be used to electronically tune in frequencies that vary from FCC standards. It's most useful with some video games and cable systems.

All channel, band, and mode se-

continued on page 38

ASK R-E

continued from page 22

ability to carry the short-circuit current and because it can react to the over-voltage condition faster than a fuse.

HUM PROBLEM

I have a Sharp RT-3388A stereo cassette deck and two Carver magnetic field-effect amplifiers that I use in a portable disc-jockey system. The setup has to be very compact so the tape deck is only about six inches from each of the amplifiers. The amplifiers induce a hum in the deck that is easily heard over the speakers. The tape head is not shielded and a shielded replacement doesn't seem to be available. How can I eliminate the hum?—P.S., Belle Plaine, MN


We are not familiar with the physical design and placement of the parts in the three components in question. No doubt you tried temporarily reorienting the amplifiers and also moving them away from the tape deck, so that you can be sure that the hum is caused by 60- or 120-Hz voltages induced in the playback head by magnetic fields around the amplifiers.

If you are sure that the hum is induced, and greater separation between deck and amplifiers is not practical, try magnetic shielding. Take a sheet of thin, soft, sheet iron and shape it so that it can be inserted between the parts of the amplifier and the tape head. Try placing it in the different positions between the amplifier's transformers and the tape deck—each time making sure to ground the shield securely to the amplifier chassis.

You want to be sure that the magnetically induced hum is not masking a hum that can develop when two or more sensitive audio components are connected together and to a common power line. First, connect a good electrical ground between the three chassis. Plug the tape deck and one amplifier into the AC line. While monitoring the hum level, try reversing the AC-line plugs, one at a time. Finally, plug in the remaining amplifier, reversing its plug if necessary for minimum hum.

R-E

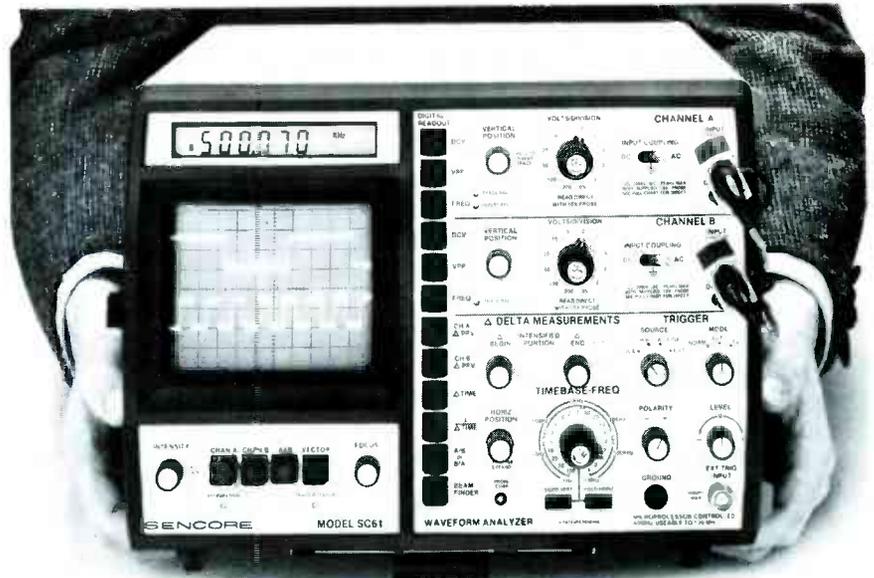Analyze defective waveforms faster, more accurately, and more confidently — every time or your money back



with the SC61 Waveform Analyzer
Patented \$2,995

If you value your precious time, you will really want to check out what the exclusively patented SC61 Waveform Analyzer can do for you. 10 times faster, 10 times more accurate, with zero chance of error.

End frustrating fiddling with confusing controls. Exclusive ultra solid ECL balanced noise cancelling sync amplifiers, simplified controls, and bright blue dual trace CRT help you measure signals to 100 MHz easier than ever.

Accurately and confidently measure waveforms from a tiny 5 mV all the way to a whopping 3,000 V without hesitation with patented 3,000 VPP input protection — eliminates expensive "front end" repairs and costly equipment downtime.

Make only one circuit connection and push one button for each circuit parameter test: You can instantly read out DC volts, peak-to-peak volts and frequency 100% automatically with digital speed and accuracy. It's a real troubleshooting confidence builder.

Confidently analyze complex waveforms fast and easily. Exclusive Delta measurements let you intensify any waveform portion. Analyze glitches, interference signals, rise or fall times or voltage equivalents between levels; direct in frequency or microseconds.

Speed your digital logic circuit testing. Analyzing troublesome divide and multiply stages is quicker and error free — no time-consuming graticule counting or calculations. Simply connect one test lead to any test point, push a button, for test of your choice, for ERROR FREE results.

To see what the SC61 can do for your troubleshooting personal productivity and analyzing confidence, CALL TODAY, WATS FREE, 1-800-843-3338, for a FREE 15 day Self Demo.



Call Today Wats Free 1-800-843-3338

SENCORE
3200 Sencore Drive
Sioux Falls, SD 57107
605-339-0100 In SD Only

*innovatively designed
with your time in mind.*

CIRCLE 178 ON FREE INFORMATION CARD

NEW PRODUCTS



CIRCLE 10 ON FREE INFORMATION CARD

INTEGRATED SECURITY SYSTEM.

The Heath-Zenith model SS-5810 is designed for trouble-free installation and is ready to use "out of the box" as the motion sensor is built into the unit. It uses advanced passive infrared (PIR) technology to monitor movement in a large room or office. If desired, it can be transformed into a complete home-security system by attaching a number of different alarms, which may be hard-wired to the system.

The unit contains features that are usually found in top-line security systems—like the tamper-proof alarm that's activated if the

unit's back cover is removed. By adding magnetic contact switches, smoke alarms, and additional infrared motion sensors in other areas of the home or office, the unit is able to monitor virtually all areas of a home, office, apartment, or condominium.


The model SS-5810 is priced at \$149.00.

Three further PIR products are the model SL-5320 Motion Sensor Light Control; the model SI-5910 Wireless Motion Sensor Light Control, and the model SS-5910 Wireless Security System.—**Heath-Zenith**, Hilltop Road, St. Joseph, MI 49085.

DATA GENERATOR. B&B Electronics' model 232DG outputs ASCII data in various combinations of line length, baud rate, parity, number of stop bits, and word length. The output may be inhibited via Data Terminal Ready (pin 20), or Request to Send (pin 4), or by X-on and X-off. The status of Clear to Send (pin 5), Data Set Ready (pin 6), and Carrier Detect (pin 8) all may be controlled by using the switches.

In the ASCII mode, the model 232DG produces all of the printable ASCII characters including space: A 2716 PROM is used to store those characters and may be reprogrammed for custom test patterns, or used for sending messages. In the U-U-Mode, the model 232DG outputs the letter "U" constantly. That is a square wave at one-half the selected baud rate and represents a good "worst case" test. The Output Switch will

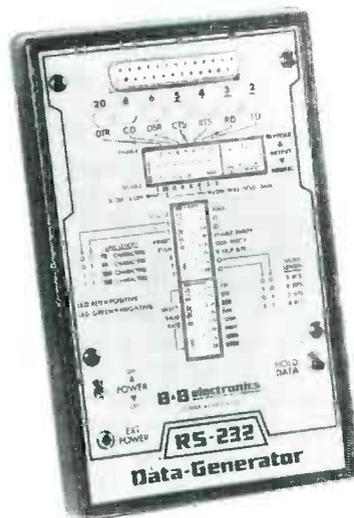allow the user to output data on pin 2 or pin 3. The model 232DG uses a 9-volt battery (not included with the Data Generator). Also, an optional AC power supply is available that can be used to replace the battery.



CIRCLE 11 ON FREE INFORMATION CARD

The model 232DG is priced at \$199.95. The model 232PS Optional AC Power Supply costs \$14.95.—**B & B Electronics Mfg. Co.**, 1500 Boyce Memorial Drive, P.O. Box 1040, Ottawa, IL 61340.

LIGHTNING-SURGE ARRESTOR.

The Spi-Ro model LA-4 is designed specifically for use on TV's, VCR's and satellite-receiver systems. It uses a gas-filled discharge element that is very sensitive to unwanted transients that may appear



CIRCLE 12 ON FREE INFORMATION CARD

on the antenna line, incoming cable, etc. The model LA-4 diverts unwanted surges (such as lightning) away from the equipment and to a safe ground. The unit fits all equipment that uses the standard "F-type" connector. It is priced at \$19.95.—**Spi-Ro Manufacturing, Inc.**, P.O. Box 1538, Hendersonville, NC 28793.

CORDLESS MOTO-TOOL. The Dremel *Freewheeler*, is available in tool-only and kit forms. The model 850 includes the *Freewheeler* cordless moto-tool and charger; the model 8500 includes the tool, charger stand, and 30 accessories. A keyless chuck is included with the model 850 as a special introductory offer—a \$5.00 retail value—and is standard with the model 8500 kit.



CIRCLE 13 ON FREE INFORMATION CARD

The suggested retail price for the model 850 is \$59.99; the suggested price for the model 8500 is \$79.99.—**Dremel**, 4915 Twenty-first Street, Racine, WI 53406.

TACK KIT. Chemtronics' *Micro Bond Tack Kit* includes a 5-ounce no-spill squeeze bottle of Micro Bond #200 cyanoacrylate adhesive, a Teflon applicator needle, and a Micro Bond activator pen. The kit provides fast, reliable wire tacking and component bonding to printed-circuit boards—resulting in a low PCB profile that prevents damage due to sagging wires or loose components.

Each kit contains enough adhesive for approximately 800-1000



CIRCLE 14 ON FREE INFORMATION CARD

drops of "tacks." Other uses for Micro Bond include repairing control knobs, radio and TV parts, cameras and business equipment, as well as bonding other metal, plastic, glass, ceramic, and rubber surfaces. The *Micro Bond Tack Kit* is priced at \$9.40.—**Chemtronics, Inc.**, 681 Old Willets Path, Hauppauge, NY 11788.

HIGH PASS FILTERS. The Ameco *HP-75T* and the Ameco *HP-300T*, are laboratory-type instruments,

Nobody Offers YOU Better Prices on HITACHI SCOPES Now at 1987 Prices...Order Today!



40TH YEAR ANNIVERSARY SALE!

SPECIAL HITACHI SCOPES!

Model V-660 Scope

DC to 60 MHz
Dual channel,
delayed sweep,
CRT readout,
sweep time
autoranging,
trigger lock

REG. \$1095

\$960
40th Year
Special

Model V-665 Scope

DC to 60 MHz
Dual channel,
delayed sweep,
CRT readout,
cursor readout,
sweep time
autoranging,
trigger lock

REG. \$1295

\$1185
40th Year
Special

Model V-1060 Scope

DC to 100 MHz
Dual channel,
delayed sweep,
CRT readout,
sweep time
autoranging,
trigger lock

REG. \$1495

\$1340
40th Year
Special



Model V-1065 Scope

DC to 100 MHz Dual channel delayed sweep, CRT readout, cursor readout, sweep time autoranging, trigger lock

REG. \$1795 **\$1590**

ORDER TODAY and SAVE!

40th Year Special

HITACHI Model V-212

SAVE Up to 40%* Dual Trace-DC to 20 MHz 6" CRT - 1mv Sensitivity - Vert. Deflection, Ch1, CH2, Chop, Add (Diff) - XY Mode.

REG. \$615

***40% Discount \$369**

HITACHI Model V-422

Dual Trace - DC to 40MHz; 1mv Sensitivity - DC Offset for DMM Output - 6" PDA CRT - Vert. Mode Trigger

REG. \$925

40th Year Special \$685

CRT READOUT MODELS

Model V-1100A

DC to 100 MHz,
Quad Channel,
Delayed Sweep,

REG. \$2490

\$1995
40th Year Special

Model V-1150

DC to 150 MHz -
Delayed Sweep,
Quad Channel 8 trace

REG. \$2950

\$2575
40th Year Special

SPECIAL HITACHI Model V-6020



1 MHz sampling Dual Channels Usable as both a conventional oscilloscope and a digital storage scope

REG. \$1950

\$1695
40th Year Special

ALL HITACHI SCOPES INCLUDE FULL 3 YEAR FACTORY WARRANTY

JOSEPH ELECTRONICS, INC. Dept. R
8830 N. Milwaukee Ave. Niles, IL 60648

Rush merchandise per attached order. I understand rated accounts are shipped open account; otherwise send per credit card. Include \$10.00 per Scope for shipping and handling.

Visa Master Card Discover
 Check Money Order Rush Catalog
Card No. _____ Exp. Date _____

Name _____

Company _____

Street Address _____

City _____ State _____ Zip _____

Send for FREE 480 page "Industry Products Catalog". I understand it is FREE with any order or if requested on company letterhead. (Otherwise, \$4.95 to cover catalog and shipping costs.)


ORDER TOLL FREE
1-800-323-5925
IN ILLINOIS
312-297-4200
Our 40th Year

Joseph Electronics



IL Res. 7% Tax

Radio-Electronics mini-ADS

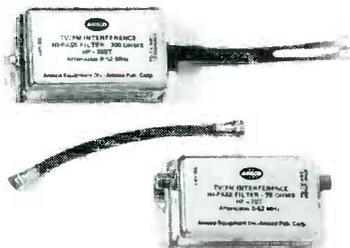

CIRCLE 15 ON FREE INFORMATION CARD

containing nine sections in five shielded compartments, and are designed to eliminate interference from amateur, CB, and short-wave radio; appliances and industrial equipment; electrical storms and auto ignition; diathermy and X-ray equipment, and police radio and paging systems. They are priced at \$12.95 each.—Ameco Equipment Company, 220 E. Jericho Turnpike, Mineola, NY 11501.

CRT READOUT OSCILLOSCOPE. The Leader Instruments' model LBO-2060 allows the user to observe waveforms, setting conditions, and measured values on a single display. It reduces setup time by displaying setting conditions such as CH-1 and CH-2 sensitivity, main and delayed sweep time, and triggering controls.



CIRCLE 16 ON FREE INFORMATION CARD

The on-screen cursors provide the user direct reading of measured values, as well as making the unit extremely user-friendly and simple to operate. They provide direct readout of voltage difference in volts and percentage, time difference in seconds and percentage, frequency in Hz, and phase difference in degrees.

The model LBO-2060 is priced at \$1490.00.—Leader Instruments Corporation, 380 Oser Avenue, Hauppauge, LI, NY 11788. R-E



THE MODEL WTT-20 IS ONLY THE SIZE OF A DIME, yet transmits both sides of a telephone conversation to any FM radio with crystal clarity. Telephone line powered - never needs a battery! Up to 1/4 mile range. Adjustable from 70-130 MHz. Complete kit \$29.95 + \$1.50 S + H. Free Shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD




ZENITH SSAV1 from \$169, UHF INPUT, reconditioned. Level II modules available for SSAV1s. UHF SSAV1 project handbook \$6.50 ppd. Sylvania 4040 \$169. Z-TAC, N-12, MLD-1200s. Converters, amplifiers and accessories. Satellite components. Radar speed guns for car/boat racing, bowling, skiing; baseball, etc, from \$275 used. Professional police models. IBM-compatible computer systems from \$895. Catalog \$1. **AIS SATELLITE, INC., P.O. Box 126-E, Dublin, PA 18917. (215) 249-9411.**

CIRCLE 81 ON FREE INFORMATION CARD



APPLIANCE REPAIR HANDBOOKS—13 volumes by service experts; easy-to-understand diagrams, illustrations. For major appliances (air conditioners, refrigerators, washers, dryers, microwaves, etc.), elec. housewares, personal-care appliances. Basics of solid state, setting up shop, test instruments. \$2.65 to \$5.90 each. Free brochure. **APPLIANCE SERVICE, P.O. Box 789, Lombard, IL 60148. (312) 932-9550.**

CIRCLE 84 ON FREE INFORMATION CARD

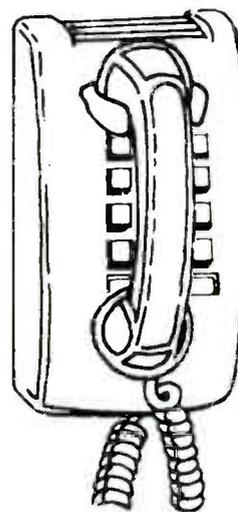

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$745.00 per each insertion.
- Reaches 245,824 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.
- We typeset and layout the ad at no additional charge.


Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: mini-ADS, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.



DECODE NEARLY ANY SINGLE LEVEL GATED PULSE SIGNAL. New circuit works with Hamlin, Jerrold, Sylvania, and Eagle systems. Decodes In-band, Out-band, AM or FM reference. Complete educational kit including P.C. board, parts, case, and 40 page gated pulse theory booklet is only \$47.00 plus \$3.00 shipping. Order no. 1PFD-1K. **ELEPHANT ELECTRONICS INC. P.O. Box 41865-R, Phoenix, AZ 85080. (602) 581-1973**

CIRCLE 187 ON FREE INFORMATION CARD

Radio-Electronics mini-ADS

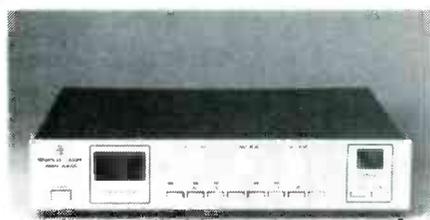

SATELLITE RECEIVER NOW JUST \$35.00. Our loss is your gain! We have an oversupply of the WorldTech model 3401 70MHz home satellite receiver. All mchdse is brand new-retail price was \$399. Great Christmas or hobby gift. Features include digital # readout and stereo. Custom 70MHz down-converter available separately. To order, send check or money order plus \$5/unit for shipping to: **INTEK CO., Box 76417, Los Angeles, CA 90076.**

CIRCLE 67 ON FREE INFORMATION CARD



SIMPLY SNAP THE WAT-50 MINIATURE FM TRANSMITTER on top of a 9v battery and hear every sound in an entire house up to 1 mile away! Adjustable from 70-130 MHz. Use with any FM radio. Complete kit \$29.95 + \$1.50 S + H. Free shipping on 2 or more! COD add \$4. Call or send VISA, MC, MO. **DECO INDUSTRIES, Box 607, Bedford Hills, NY 10507. (914) 232-3878.**

CIRCLE 127 ON FREE INFORMATION CARD



CHRISTMAS SALE on the Line Zapper II. During Nov. and Dec. only, the complete KIT (not recommended for the beginner) is only \$49.95 and the fully assembled unit is only \$89.95 (add \$3.00 ea. postage). Decode the Marco-Mess and start watching recent video tape movie releases without the flashing, jumping, jittering and video noise. **ELEPHANT ELECTRONICS INC., P.O. Box 41865, Phoenix, AZ 85080 (602) 581-1973**

CIRCLE 120 ON FREE INFORMATION CARD



CABLE TV CONVERTERS AND DE-SCRAMBLERS. Large selection of top quality merchandise. Low prices. Quantity discounts. We ship COD. Most orders are shipped within 24 hrs. Send \$2.00 for catalog. **CABLETRONICS UNLIMITED, P.O. Box 266 Dept. R, S. Weymouth, MA 02190 (617) 843-5191**

CIRCLE 194 ON FREE INFORMATION CARD




BUILD STEVE CIARCIA'S NEW SUPER IC TESTER Tests over six hundred 7400-series TTL, L, S, H, C, HC, HCT, F, AS, and ALS devices, 4000-series CMOS and PALs. Identifies unmarked chips and bad IC pins. User definable test sequence and user expandable ROM library. Tester operates standalone with LCD display, or with IBM PC or terminal. Partial kit—\$99. Full board kit—\$179. **CCI, 4 Park St., Suite 12, Vernon, CT 06066. (203) 875-2751.**

CIRCLE 52 ON FREE INFORMATION CARD




FREE CATALOG OF HARD-TO-FIND TOOLS is packed with more than 2000 quality items. Your single source for precision tools used by electronic technicians, engineers, instrument mechanics, schools, laboratories and government agencies. Also contains Jensen's line of more than 40 tool kits. Send for your free copy today! **JENSEN TOOLS INC., 7815 46th St., Phoenix, AZ 85044. (602) 968-6231.**

CIRCLE 115 ON FREE INFORMATION CARD

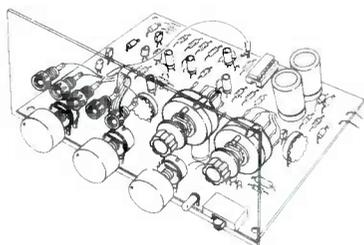


1 MHz FUNCTION GENERATOR KIT. Covers 0.1 Hertz to 1 MHz in 6 ranges. 100:1 frequency ratio. Sine, Triangle & Square waves available. (with DC offset). TTL output. FM & AM modulation inputs. 47 ohm output. Includes all parts, board, power supply and face plate decal. Excellent detailed assembly and theory of operation manual included. Superb classroom project. \$99.95 (Free Shipping). **OCTE ELECTRONICS, Box 276, Alburg, VT 05440. (514) 739-9328**

CIRCLE 80 ON FREE INFORMATION CARD

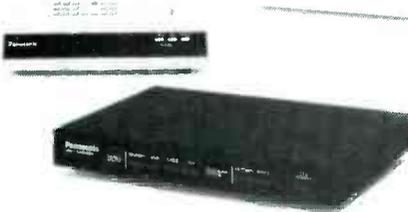

PANASONIC CABLE CONVERTERS, Wholesale and Retail. Scientific Atlanta and Pioneer Cable Converters in stock. Panasonic model 130N 68 channel converter \$79.95, Panasonic Amplified Video Control Switch Model VCS-1 \$59.95. Scientific Atlanta Brand new Model #8528 550MHZ 80 Channels Converter \$89.95. Video Corrector (MACRO, COPYGUARD, DIGITAL) ENHANCER \$89.95. We ship to Puerto Rico, Caribbean countries, & So. Amer. Write or call **BLUE STAR IND., 4712 AVE. N, Dept 105, Brooklyn, NY 11234. Phone (718) 258-9495.**

CIRCLE 85 ON FREE INFORMATION CARD

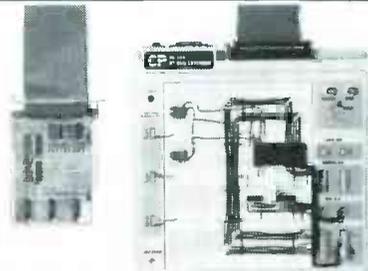

PC-601 XT BUS EXTENDER BREADBOARD LAB connects to any IBM PC compatible computer and extends all PC electrical bus connections out to the PC-601 for easy circuit prototype connection, testing and trouble-shooting. Includes large 3060 tie-point breadboard, ±5V and ±12Vdc AC line powered power supplies. Includes buffer card, 2' ribbon cable & 1-Year warranty. Price: \$369.95 **CHENESKO PRODUCTS, 21 Maple St., Centereach, NY 11720. 516-736-7977, Fax: 516-732-4650**

CIRCLE 193 ON FREE INFORMATION CARD

EQUIPMENT REPORTS

continued from page 32

lection is done from the front-panel keyboard. Direct channel entry is possible, as is up-and-down channel scanning. The channel scan can easily be programmed by the user to pass over unused or unwanted channels.

The portable TV can be powered from either 120 volts AC or 12 volts DC, and two power cords are supplied. (The DC cord terminates in a cigarette-lighter plug.) Other accessories include a removable tinted sunscreen, and an earphone for private listening. The picture tube is a *Chromacolor Contrast* type; that type of tube has a black matrix surrounding each phosphor element. Our picture was sharp with high contrast.

The GR-9009 has a suggested retail price of \$249.95. Why would you build a TV kit that when you could buy a preassembled TV for less? If you've asked yourself that question, then you are not a kit

builder. Assembling a kit can be a lot of fun. And the advantages are not limited to being able to proudly say "I built it myself."

With the Heathkit manual, you really can learn about the TV's circuitry and how it works. If problems arise in the future, you will

feel confident about going in and doing something about it—even if it is just replacing a module with a Zenith equivalent. And if you want to modify your receiver, you'll find the clear schematics and circuit descriptions a great help. But remember that any user modifications will void your warranty, and you will not be able to obtain servicing from Heath.

We know you're all probably wondering if our GR-9009 worked the first time we powered it up. Well, we were very surprised when it didn't—past experience taught us that if we followed the Heathkit instruction manual, everything would work. At least we had a chance to try out the manual's troubleshooting charts. Using them, we found the problem in less than five minutes. If the problem had turned out to be more perplexing, we could have used the telephone help line. That line is available only to purchasers of Heath kits and is manned by a technician who can quickly track down most problems. **R-E**

No previous experience necessary

LEARN PROGRAMMING



Master computers in your own home at your own pace in your spare time. Learn even before you decide on a computer.

BE YOUR OWN COMPUTER EXPERT

Programming is the best way to learn to use computers, and we can show you the best—and most economical—way to learn programming!

Send today for your free information package. No obligation. No salesman will call.

HALIX INSTITUTE
CENTER FOR COMPUTER EDUCATION DEPT. 49
1543 W. OLYMPIC, #226
LOS ANGELES, CA 90015-3894

YES! Send me free information on how I can learn about computers and programming at home!

Name _____
Address _____
City _____ State/Zip _____

HITACHI COMPACT SERIES OSCILLOSCOPES



V-1065 DC to 100MHz With Cursor Readout
\$1595. Save \$200!

- 6" CRT with Internal Graticule
- Dual Channel X-Y Display
- Sweep Time Autoranging
- 400V High Input Voltage Protection
- TV Sync Trigger Circuit
- Delayed Sweep • CRT Readout
- Single Sweep • ±3% Accuracy
- Trigger Lock • Bandwidth Limiter

V-1060 DC to 100MHz
\$1345. Save \$150!

V-665 DC to 60MHz

\$1145. Save \$150!

V-660 DC to 60MHz

\$970. Save \$125!

Instant Hard Copy!!
From Oscilloscopes

POLAROID® DS-34 CAMERA



Save \$135! **\$290.**

- 5", 6" and 7" Hoods (Available separately @ \$51 ea. Please Specify size)
- Pistol Grip For Ease of Operation
- Works on Any Make of Oscilloscope
- Three Full Year Warranty

PROBES INCLUDED WITH ALL HITACHI
SCOPES AT NO EXTRA CHARGE!



**WM. B. ALLEN
SUPPLY COMPANY**

ALLEN SQUARE
300 Block North
Rampart Street
New Orleans
Louisiana 70112

TOLL FREE 800 535-9593 • LA 800 462-9520
NEW ORLEANS 504 525-8222 • FAX 504 525-6361
• American Express • Visa • MasterCard •
928 pg Catalog FREE with your order

Dual Channel 6" CRT Scopes

V-425 DC to 40MHz, CRT Readout

\$845. Save \$150!

V-423 DC to 40MHz, Single Time Base Delayed Sweep

\$745. Save \$250!

V-422 DC to 40MHz, DC Offset

\$795. Save \$130!

V-225 DC to 20MHz, CRT Readout

\$720. Save \$75!

V-223 DC to 20MHz, Delayed Sweep

\$695. Save \$100!

V-222 DC to 20MHz, DC Offset

\$515. Save \$200!

V-212 DC to 20MHz

\$440. Save \$175!

Dual Channel Mini-Portable Scopes

V-509 DC to 50MHz,

Delayed Sweep

\$1195. Save \$250!

V-209 DC to 20MHz

\$822. Save \$175!

Quad Channel Multi-Function Scopes

V-1150 DC to 150MHz,

Delayed Sweep

\$2650. Save \$300!

V-1100AU DC to 100MHz,

Delayed Sweep

\$2240. Save \$250!

Digital Storage Scope

V-6020 1MHz Sampling,

Dual Channels

\$1750. Save \$200!

NTSC Waveform Monitors

V-079 6" CRT

\$1625. Save \$125!

V-099 3.5" CRT

\$950. Save \$300!


NTSC Vector Scopes

V-069 6" CRT

\$1825. Save \$125!

V-089 3.5" CRT

\$1284. Save \$400!

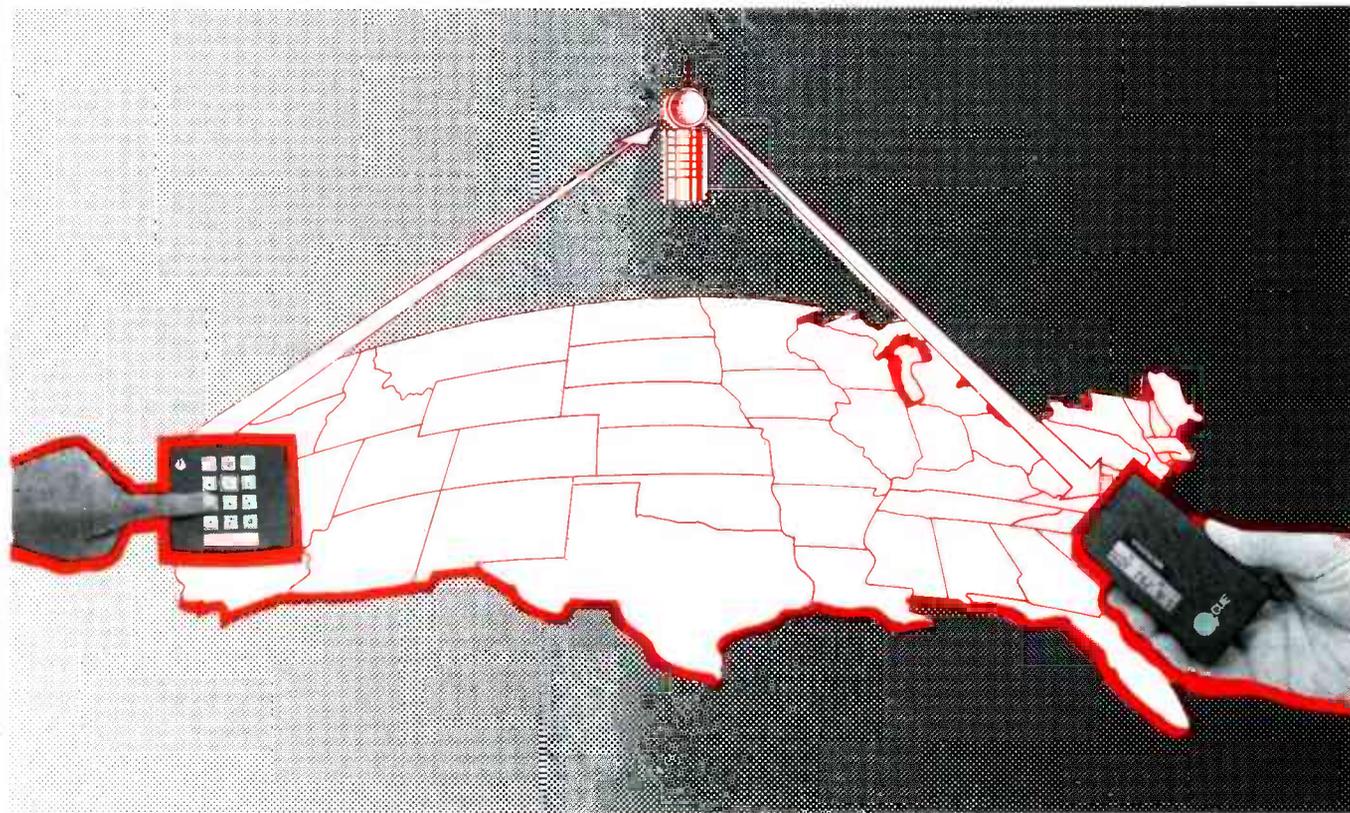

A NATIONAL RADIO PAGING SYSTEM

You can run but you can't hide—from satellite paging

HERB FRIEDMAN, COMMUNICATIONS EDITOR

IT WAS A DARK AND STORMY night...somewhere back down the road Snoopy had fallen out of the family's pickup truck, and Charlie Brown had just discovered he was gone. Faster than Clark Kent changing to Superman, Charlie Brown rushed to a roadside telephone booth, punched in an 800 telephone number plus a few more digits, and out in the night Snoopy heard a small brown box on his belt go *beep...beep...beep...beep*, and when he looked down at the box he saw the telephone number of Charlie's phone booth. A quick call and Snoopy was rescued.

Snoopy's rescue worked like this. The 800 number that Charlie called is the free access for the Cue Paging Corp.'s (Box 7789, Newport Beach, CA 92658.) *national* paging system. Cue Paging uplinked the next set of *Touch-Tones* punched in by Charlie Brown—which represented the access code for Snoopy's "brown box"

pocket-pager and the telephone number of Charlie's phone booth—to the Westar 4 satellite. Across the U.S., satellite downlinks sent the data signals to more than 100 FM stations, which rebroadcast the data on a 57-kHz SCA subcarrier.

Meanwhile, the pocket-pager on Snoopy's belt, which is a scanning FM receiver with a 12-digit LCD display, was searching for an FM station that was broadcasting a 57-kHz SCA subcarrier modulated with Cue Paging's *attention code*. (The attention code is broadcast so the receiver can distinguish between a Cue Paging subcarrier and all others). The receiver's tuning locked onto the FM station having the strongest Cue Paging subcarrier. When the FM station broadcast Snoopy's access code, the receiver beeped and displayed the data, which was the telephone number of Charlie Brown's phone booth. When Snoopy heard the beep,

he simply looked at the receiver's LCD display and saw Charlie's telephone number.

A lot of technology.

As you can gather from our comic-strip scenario, many high-tech disciplines go into nationwide radio-paging. Figure 1, which is a pictorial of the system, gives a better idea of the various technologies used.

Assuming you're the subscriber, the system works this way. Anyone who wants to reach you—even if they have no idea whether you're around the block or on the other side of the continent—uses their *Touch-Tone* phone (1) to dial a toll-free 800 number that accesses Cue Paging's computer (2) in Virginia. Depending on where the telephone is located and the long-distance carrier used by the 800 connection, the telephone signal travels to the computer via ordinary telephone wires, fiber optics, micro-

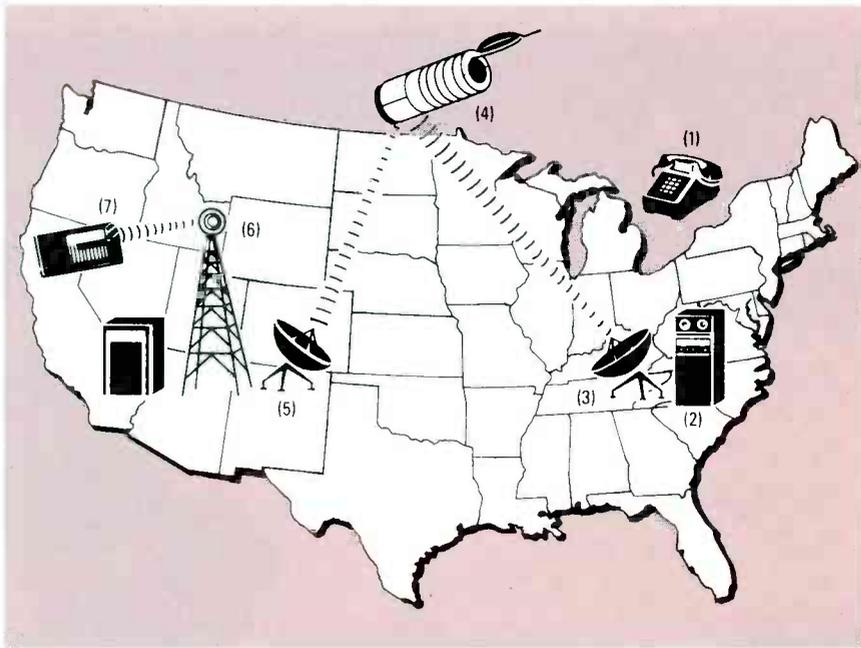


FIG. 1—NATIONAL RADIO PAGING depends on FM stations rebroadcasting the data received from a satellite.

wave, satellite link, or any combination of communication paths. A digitized voice from the computer asks the caller to input the subscriber's access code. A tone beep informs the caller that the computer has recognized the code will accept 12 *Touch-Tone* digits, which can represent a telephone number, or anything else (like a secret code).

The data representing the access

code and up to 12 digits is stored in the computer for possible *Voice Message Retrieval* (we'll explain that later) and sent to a Westar 4 satellite uplink (3). The Westar 4 satellite (4) downlinks the signal to local or regional satellite receiving facilities (5), which send the data to one or more local FM stations (6) via telephone, radio relay, or a microwave link.

For example, because of its un-

usually large metropolitan area and its "canyons" created by many tall buildings, New York City requires several Cue Paging SCA stations for complete coverage (right down into the subway system). The satellite signal is received by WQXR's SRO (Satellite Receive Only), which passes the signal along to WCBS by conventional radio line. Another paging station, WNYE, gets its paging data feed from a special receiver that is tuned to the WCBS SCA.

Each FM station is equipped with automatic Cue Paging failure detection, central monitoring station notification, and a satellite-signal bypass via the telephone switched network (dial-up). We will cover that part of the system later.

Six memories

Your pocket pager (7)—called an FM/SCA Cue Unit—receives the message from a participating FM station and stores it in one of six 12-digit memories.

The Cue Unit can be set to either beep or remain silent when it receives new data. Either way, you can read the data in any of the six memories on an LCD display and save or erase the data as desired. A memory without data cannot be read, therefore no time is wasted stepping through empty memories.

Since every FM station in the sys-

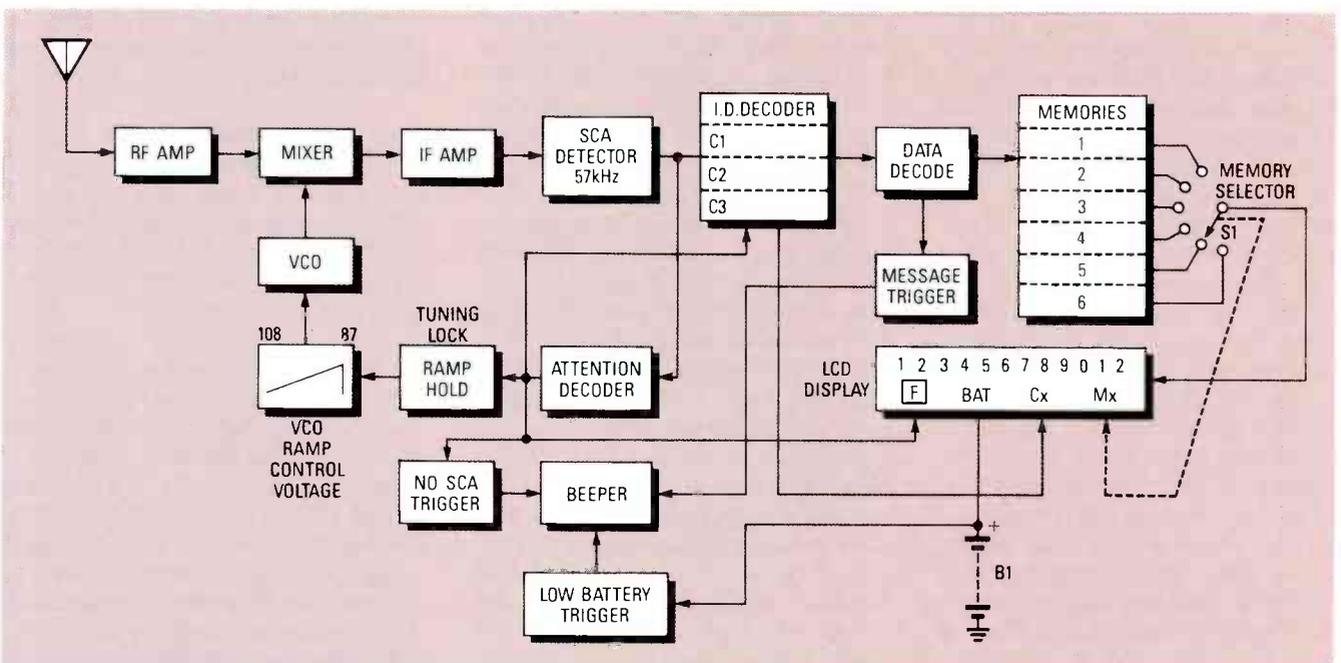


FIG. 2—THE PAGING RECEIVER'S FUNCTIONAL CIRCUIT. The six memories are arranged in a stack so that the most recent message fills the first memory, pushing the other messages down the stack until the one at the bottom, in memory 6, "falls out."

tem receives the data at the same time, you can receive your message anywhere as long as you're within range of an FM station that supplies Cue Paging. Presently, all major metropolitan areas from coast to coast are served by the system, as well as some not-so-major but important industrial areas.

Coverage is not complete, however, and there are some surprising holes in the system. For example, although we can't expect coverage in the wide-open-spaces of Montana, Wyoming, the Dakotas, and Idaho, at the time this article was prepared Cue Paging's service map showed there was no service in Virginia (outside the D.C. area), Oklahoma, and New Mexico. However, Cue Paging plans to expand coverage as FM station access permits.

The individual pieces

The Cue Unit is a special 87-108-MHz scanning receiver that is manufactured in Finland. It is powered by four 100-mAh Ni-Cd batteries that are recharged in 12 to 16 hours by a supplied trickle-charger base. A full battery charge can carry the receiver for about three days. The functional block diagram of the receiver is shown in Fig. 2. (Remember, Fig. 2 is functional for ease of understanding; it does not represent the actual digital/microprocessor circuits.)

An internal antenna feeds the received FM signal into an RF amplifier, then into the mixer and on to the IF amplifier. Tuning is done through a VCO (Voltage Controlled Oscillator) that automatically sweeps the FM band. The output of the IF amplifier feeds through to a 57-kHz SCA detector, a digital identification decoder, a data decoder, the memory stack, and the LCD digital display. A sampling circuit from the SCA detector's output senses the *attention signal* of a Cue Paging SCA and locks the VCO on frequency. Assorted trigger circuits sound an internal beeper when data is received, the battery is low, or the SCA signal fails (due to low or no SCA signal strength).

ID decoder

The digital identification decoder has two functions. The first sends received data to the data decoder if it receives the "go-ahead" from the attention-signal's decoder. The second function opens the receiver's memory

when it senses one of three subscriber access codes. Normally, the receiver responds to a single access code. However, the subscriber user might also want a selected group of receivers to respond to a single code: that would be a second access code. Or, a business might use several receivers having individual access codes but might want a third access code that could simultaneously activate all receivers. Presently, Cue Units can respond to three access codes.

Memory stack

The received data is fed to a 6-memory stack. A user-activated electronic switch selects a memory and feeds its data to an LCD readout. An ERASE switch allows the user to selectively clear a particular memory location.

Since the memories are arranged in a stack, new messages go into the top and push the previous messages down the stack. If all memories are full, a new message will push the message in the No. 6 memory out the bottom of the stack. For example, assume memories 1 to 6 are loaded. If a seventh message is received, it fills the No. 1 memory, causing the message in No. 1 to move into memory No. 2, etc.



FIG. 3—THE LCD DISPLAY LOOKS LIKE THIS when data is received. In addition to the numeric data, the display shows the memory it's in and the access ("C") code being used. The unit is shown in its charger base, which permits simultaneous reception and charging of the NiCd batteries.

The message in No. 6 vanishes. If one or more memories have been cleared by the user, the messages push down until the created space is filled. For example, assume the LCD readout shows all 6 memories are filled, but you clear Nos. 3 and 5. Now you have messages in memories 1, 2, 4, and 6. The next received message fills memory No. 1, which pushes 1 into 2 and 2 into 3. Memory 5 is still empty. If another message is received, everything is bumped down, so No. 4 moves into No. 5 and all the memories become filled. The data in No. 6 is still there because it hasn't been bumped when the two new messages were received. But now that all memories are full, No. 6 gets bumped out of the stack if another new message is received.

Figure 3 shows how a typical readout is displayed. Note that the display shows the memory (1) along with its data—**Radio-Electronics'** phone number—that's when they tried to reach me while I was in Disneyworld—and the letters "C1." C1 indicates it's my first access code, meaning the call originated at **Radio-Electronics** because they are the only ones who know my C1 access code. A C2 would have indicated my children were calling because only they have my C2 access code. A C3 would mean that the central station that is dialed by my home's security system in the event of fire, flood, break-in, or other hazard, is trying to reach me because only they have my C3 access code.

In fact, if the display shows a C3 the data doesn't have to be a call-back telephone number because I know the central monitor's phone number. They would send a special code number that represented the hazard so I would know what happened, and therefore, what person—other than the fire or police—to call for immediate action: a neighbor, a plumber, or a friend who can repair the furnace. (Twelve digits can pack a lot of information if they represent special codes rather than a telephone number.)

F for Fail

In addition to the data, memory number, and access group (C1, C2, or C3), the LCD display will also show the letters BAT when the battery power is low, and an F if the received SCA signal strength is too low to receive a reliable paging signal.

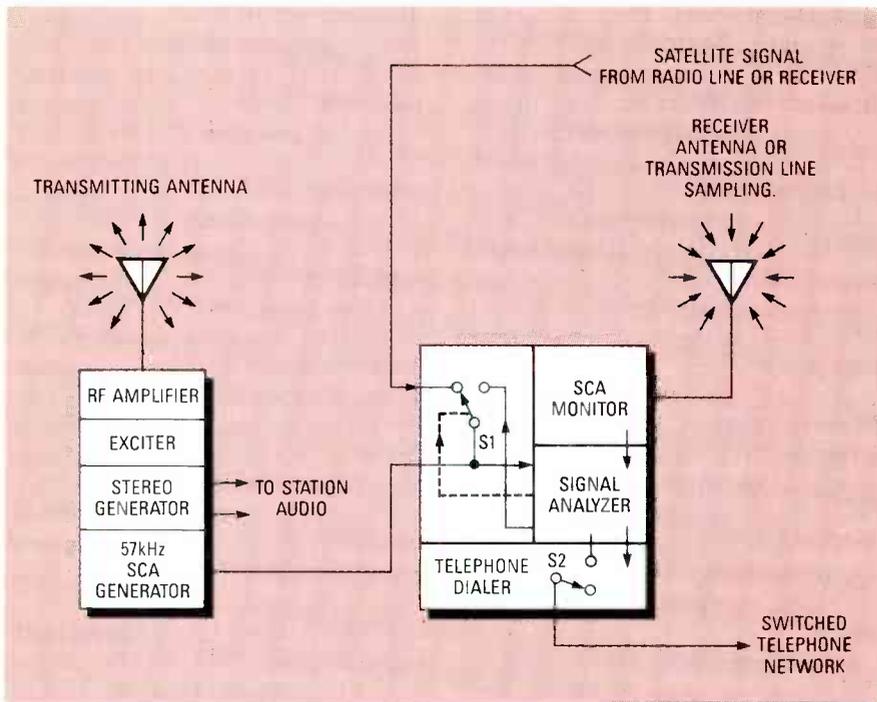


FIG. 4—THE FUNCTIONAL CUE PAGING MONITORING SYSTEM at the FM station. In the event of SCA signal failure, the equipment automatically dials a central monitor, who can instruct the equipment to switch to a dial-up telephone signal feed if necessary.



THE ACTUAL EQUIPMENT installation at WNYE-FM doesn't take up much rack space. Its Cue Page signal originates in a receiver that is tuned to WCBS.

Voice retrieval

Now it's perfectly possible that the user has been paged while his receiver was displaying an **F**. It is also possible that there was a failure at the local FM station, or anywhere else within the system, that would also turn on the **F**. Since Cue Paging transmits data only once, it is conceivable that some data wasn't received, and there is no provision to inform the user via radio that a message has been previously transmitted; so a *Voice Message Retrieval System* is provided to handle all situations where the user cannot receive a radio message.

In plain language, voice retrieval means making a toll-free telephone call to Cue Paging's computer to hear

a digitized voice repeat *all* the numeric messages that had been transmitted during the previous 12 hours. Even if you had received the data on your receiver, you will hear it again if you call up the computerized Voice Message Retrieval System.

If desired, the user can use the telephone's *Touch-Tones* to selectively or completely erase the voice messages, replay a message, get the time a message was received, or store a message for up to 12 hours.

System failure

Nothing in this world is perfect, so it's possible for the FM station, or anything in the system that delivers the signal to the station, to fail. For example, the satellite receiver might fail, the radio line between the satellite receiver and the FM station can fail, etc. To handle those problems, special off-the-air monitors that analyze the Cue Paging equipment and its signal are installed at each FM station. Figure 4 shows the functional circuit of the monitoring system, which consists of an SCA monitor, a signal analyzer, and a modem/auto-dialer for the switched-network (dial-up) telephone system. The 57-kHz SCA generator shown as part of the transmitter in the functional diagram is actually part of the Cue Paging equipment package.

If the SCA monitor's signal shows there is some kind of problem, such as intermittent or complete loss of the SCA subcarrier, loss of the attention code, or loss of signal data, the monitoring equipment causes the autodialer to connect to a dial-up telephone line and automatically dials Cue Paging's central-station operator. The monitor also flips S2, connecting the monitoring equipment to the telephone line, and then uploads digital data from the signal analyzer that represents the various conditions at the FM station.

There are several options available to the control operator. He can try to diagnose the problem, alert the FM station's technicians, or even try to correct the condition using digital signalling. If the condition originates with the satellite signal being fed to Cue Paging's SCA modulator, the central monitoring operator can instruct the monitoring equipment to hang up and then dial into a direct-to-computer telephone link for the data until the satellite-originated data link can be re-established. The direct-dial data from the computer is fed to the SCA generator via S1.

Auto-scan

Meanwhile, back at the receiver, any condition that causes the loss of proper subcarrier reception causes the receiver to display the **F** and to go into the scan mode. If the receiver is in an area where only one FM station is broadcasting Cue Paging, the **F** will continue to display and the receiver will beep intermittently to remind the user that he or she must use Voice Message Retrieval. If the receiver is in a multi-station area, it simply scans to the next station having an SCA signal that is strong enough to provide reliable reception. The receiver remains locked to the station as long as reliable reception exists.

Mars and beyond

Practically, there is almost no limit to where you can be paged. Presently, paging is national because the system uses the Westar 4 satellite. Notwithstanding the required international agreements, there's nothing to prevent paging to be done through one of the international communication satellites. Who knows, on your next trip to Lower Slobbovia the boss might decide to page you by radio—at 3 AM your time.

R-E

BUILD THIS

AN UNINTERRUPTABLE POWER SUPPLY, usually called a UPS, is one that continues to supply power when the powerline fails, and it does so without even a momentary interruption. The switchover is made so quickly that a computer connected to the UPS wouldn't even know that the powerline had failed.

A UPS's backup power is supplied by a storage battery that switches in only during a power outage. Naturally, a backup battery isn't going to provide a full day's operation, but it will power the computer for a few minutes; certainly long enough to save whatever data is in the computer, and if necessary, allow enough time to close down in an orderly, non-destructive manner.

Sinewave output

The UPS described here can supply 40 watts continuously at 115 volts with a frequency of 60 Hz. The output is essentially a sinewave that looks to the load like standard household power. A built-in power supply functions as a battery charger. While the UPS can be used for many different purposes, it was designed specifically to power a small personal computer and a critical peripheral, such as a disk drive, so that a power failure will not result in loss of data or interruption of the program that is running at the moment. What constitutes "a small personal computer?" Something like the Radio Shack Color Computer, or a Commodore VIC-20 or C64, although the C64 when used in conjunction with a disk drive draws about 45 watts. The 40-watt UPS will not carry an IBM PC or XT or a clone, which normally run upwards of 60 watts—the actual power depending on the number and type of floppy and hard-disk drives, expansion boards, and the internal modem.

Another advantage in using our UPS is that it supplies "clean" power: defects such as noise, surges, or low voltage on the powerline will not affect the computer's operation.

The load

Before undertaking construction, be sure that the planned load will not exceed the capacity of the UPS. Current ratings for computer peripherals are maximums that may occur only

UNINTERRUPTABLE



POWER SUPPLY

*Power failures? Don't worry!
This UPS will keep your computer running
when the powerline fails.*

DUANE M. PERKINS

momentarily when a motor starts. The author operates a Radio Shack Color Computer 2 and a disk drive even though the combined current rating is .53 amperes. The momentary overloads do not adversely affect operation. If the load can operate satisfactorily when a 25-ohm, 10-watt resistor is connected in series with one of the leads from the powerline, then it should operate from the UPS.

The power supply

The power supply is unique in that it draws energy from an external 12-volt storage battery as well as from the AC power line because the battery is required for circuit operation. As shown in Fig. 1, when CHARGE-OFF-OPERATE switch S1 is set to either the CHARGE or OPERATE position, relay RY2 is energized and its contacts supply AC power to the primaries of power transformers T1 and T2. The current from the secondaries is rectified by diodes D1, D2, D3, and D4.

Chokes L1 and L2 limit the charging current to the battery and also block most of the ripple. The choke coils are available in Radio Shack's 270-030 automotive filter kit. The 220- μ F capacitors that come in the kits can be used for C6 and C7. Diode D5 provides "crowbar" overload protection; its job is to protect the other components by causing fuse F1 to blow out if the battery is inadvertently connected with its polarity reversed.

Op-amp IC1 is connected as an inverting voltage comparator whose reference potential can be varied through the range of 11 to 14 volts by potentiometer R3. When the battery voltage drops below the reference, opto-coupler IC2 is triggered, which energizes relay RY1. Current flowing through RY1's contacts will charge the battery if the load is light. When the UPS is operating at or near its full capacity, an external battery charger is required to supply enough current to keep the battery from being discharged. A 10-

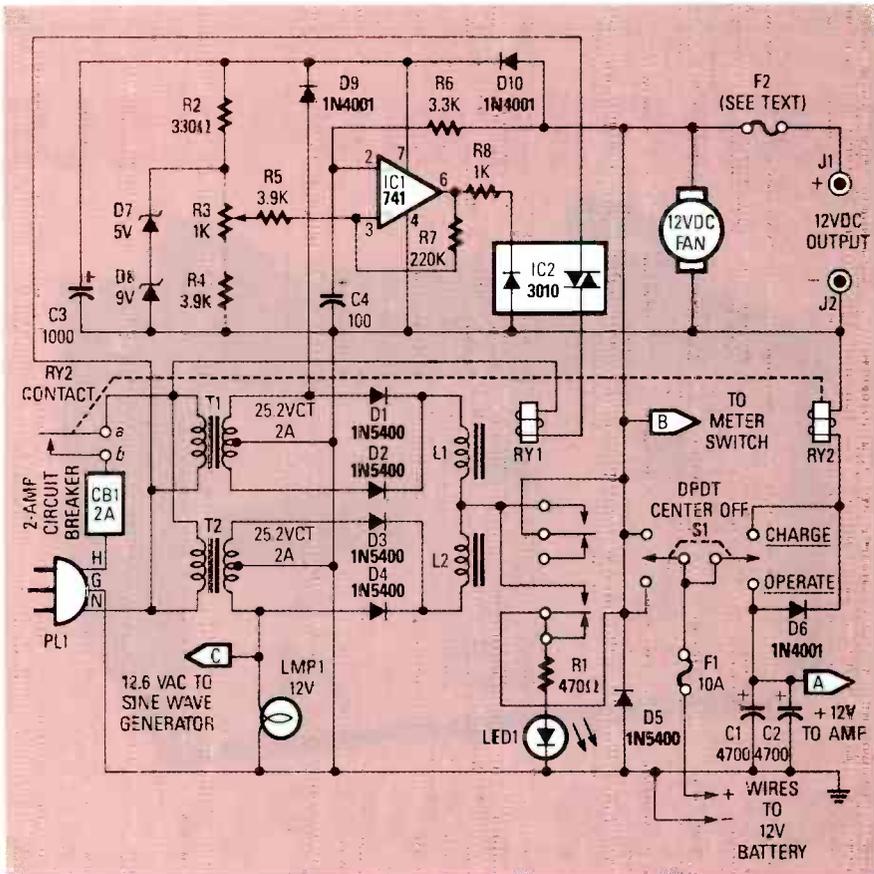


FIG. 1—WHEN THE UPS IS NOT OPERATING, or operating under a light load, this power supply also is used to charge the 12-volt battery. When the UPS is under a heavy load, however, an external 10-amp charger is needed to keep a full charge on the batteries. To prevent overcharging the battery, that charger must be turned off whenever the UPS is not operating.

ampere charger is recommended. Since most battery chargers do not have a filter, a Radio Shack 270-05/10-amp. filter should be connected between the charger and the battery to reduce ripple. So as not to overcharge the battery, the charger should be turned on only when the UPS is operated under full load.

The 12-volt DC output at jacks J1 and J2 can be used to power a small lamp and possibly a small 12-volt TV receiver for use as an emergency monitor. Fuse F2 should be smaller than 10 amps so that the main fuse, F1, will not blow if the 12-volt output is accidentally shorted.

The amplifier

As shown in Fig. 2, the AC output of the UPS is supplied by a transformer-coupled Class-B amplifier. The four pairs of Darlington-connected transistors (Q4-Q8, Q5-Q9, Q6-Q10 and Q7-Q11) function as emitter-followers to supply voltage to the primaries of power transformers T5 and T6, which are standard power transformers connected in reverse—the secondary windings serve as the primaries and vice versa.

Capacitor C8 filters any high-frequency components that result from

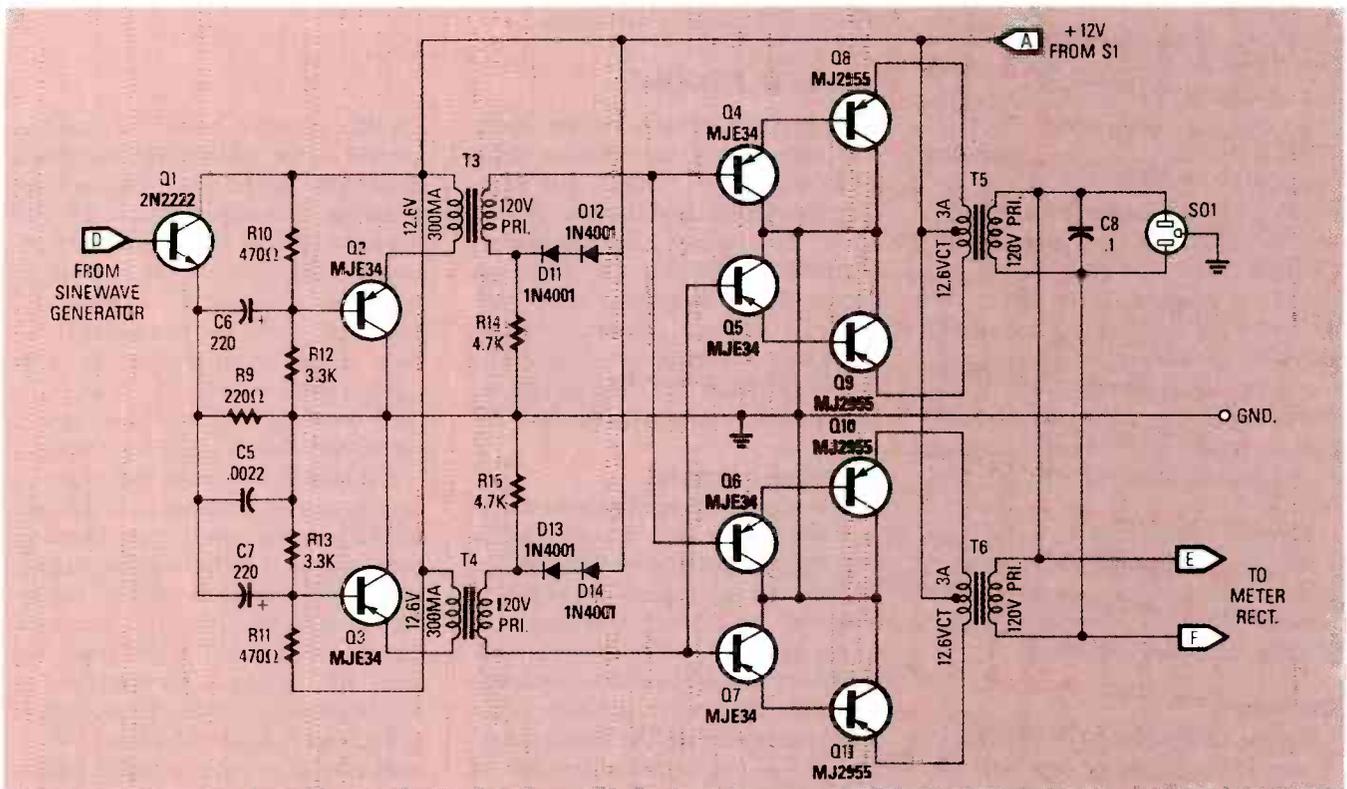


FIG. 2—THE AMPLIFIER STEPS UP the 60-Hz signal from the sine wave generator to nominally 120 volts. To ensure a clean output, C8 is included to remove any high-frequency components caused by crossover distortion or clipping from the output. It also prevents high-frequency self oscillation.

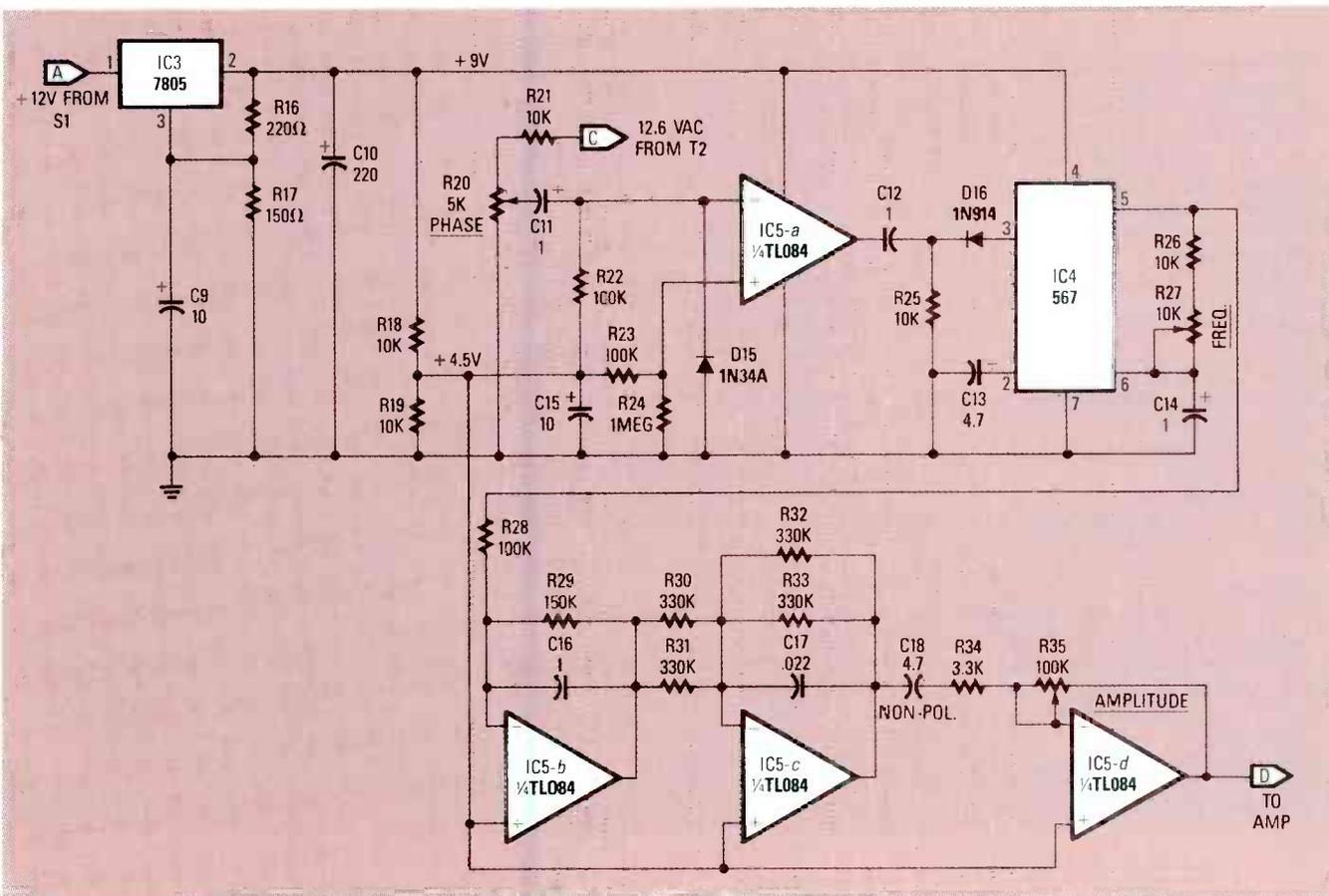


FIG. 3—THE TONE GENERATOR first develops a 60-Hz squarewave. IC5-b and IC5-c then shape the squarewave into a sinewave.

amplifier crossover distortion or clipping, and also prevents high-frequency self-oscillation.

Two of the Darlington pairs are driven in parallel by transformer T3; the other two are driven in parallel by T4. Diodes D11, D12, D13, and D14 provide a fixed DC base voltage that biases the output transistors near cut-off.

The Class-A drivers, transistors Q2 and Q3, also consist entirely of emitter followers. The necessary voltage step-up is provided by T3 and T4, which are also standard power transformers connected in reverse. Transistor Q1 drives Q2 and Q3 in parallel. The base of Q1 is directly coupled to the output of IC5-d (see Fig. 3), which is at 4.5 volts DC. Phase reversal for push-pull drive of the output stage is accomplished with proper connection of the secondaries of T3 and T4.

The sinewave generator

As shown in Fig. 3, the oscillator is built around IC4, a 567 tone detector. The IC's free-running frequency is controlled by resistors R26 and R27, and capacitor C14, and is set as close

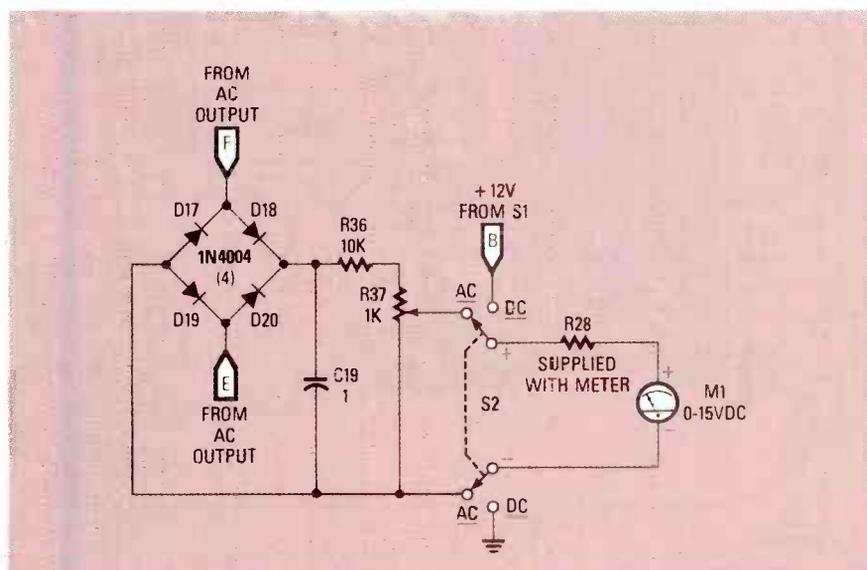


FIG. 4—THE METER CIRCUIT MEASURES both the battery voltage and the UPS output voltage. It is calibrated to the output voltage by potentiometer R37.

to 60 Hz as possible. IC4's square-wave output is converted to a triangle wave by IC5-b, which is in turn converted to a sinewave by IC5-c. Op-amp IC5-d's gain is controlled by potentiometer R35, which is used to set the AC output voltage,

Op-amp IC5-a converts the sine-

wave from the 12.6-volt output of T2 to a 60-Hz pulse train. D15 protects against damage that could occur if the inverting input were to go negative with respect to ground; the diode is normally reverse biased. The 60-Hz pulses, which are coupled to IC4 through C12 and D16, cause the os-

PARTS LIST

All resistors are 1/2-watt, 10% unless otherwise noted.

R1, R10, R11—470 ohms
 R2—330 ohms
 R3, R37—1000 ohm trim pot
 R4, R5—3900 ohms
 R6, R12, R13, R34—3300 ohms
 R7, R9, R16—220 ohms
 R8—1000 ohms
 R14, R15—4700 ohms
 R17—150 ohms
 R18, R19, R21, R25, R26, R36—10,000 ohms
 R20—5000 ohm trim pot
 R22, R23, R28—100,000 ohms
 R24—1 megohm
 R27—10,000 ohms trimmer potentiometer
 R29—150,000 ohms
 R30, R31, R32, R33—330,000 ohms
 R35—100,000 ohm potentiometer

Capacitors

C1, C2—4700 μ F, 35 volts, electrolytic
 C3—1000 μ F, 35 volts, electrolytic
 C4—100 μ F, 35 volts, electrolytic
 C5—.0022 μ F, 250 volts
 C6, C7, C10—220 μ F, 35 volts, electrolytic
 C8—.1 μ F, 250 volts
 C9, C15—10 μ F, 35 volts, electrolytic
 C11, C14—1 μ F, 10 volts, tantalum

C12—.1 μ F, 50-volts
 C13—4.7 μ F, 35 volt, electrolytic
 C16—1 μ F, 10 volts, metal film
 C17—.022 μ F, 10 volts
 C18—4.7 μ F, 10 volts, nonpolarized electrolytic
 C19—1 μ F, 250 volts
Semiconductors
 IC1—741 op-amp
 IC2—MOC3010 opto-triac coupler
 IC3—7805 voltage regulator
 IC4—567 tone detector
 IC5—quad op-amp, TLC274, TL084 or similar
 Q1—2N2222, NPN small-signal transistor
 Q2—Q7—MJE34 transistor
 Q8, Q9, Q10, Q11—MJ2955 transistor
 D1—D5—1N5400 silicon rectifier diode
 D6, D9—D14—1N4001 silicon rectifier diode
 D7—5-volt Zener diode D8—9-volt Zener diode
 D15—1N34A small-signal germanium diode
 D16—1N914 small-signal silicon diode
 D17, D18, D19, D20—1N4004 silicon rectifier diode
 LED1—Light-emitting diode
Other components
 CB1—2-amp, 120-volt pushbutton circuit breaker

F1—10-amp automotive-type fuse
 F2—automotive-type fuse, as required for 12-VDC output
 LMP1—12 volt panel lamp
 J1, J2—5-way binding posts
 L1, L2—choke coil, from Radio-Shack 270-030 filter kit
 M1—0-15-VDC voltmeter
 PL1—3-wire line cord with grounding plug
 RY1—DPDT relay, 120-VAC coil, 10-amp contacts
 RY2—SPST or SPDT relay, 12-VDC coil, 3-amp contacts
 S1—DPDT toggle switch, center off, 20-amp contacts
 S2—DPDT mini toggle switch
 SO1—AC outlet, single or duplex
 T1, T2—Power transformer: 120 volt primary; 25.2-volt, 2-amp secondary
 T3, T4—Power transformer: 120 volt primary; 12.6-volt, 300-Ma secondary
 T5—Power transformer: 120 volt primary; 12.6-volt, 3-amp secondary

Miscellaneous: Two automotive-type fuse holders, chassis mounting 12-VDC cooling fan suitable 12-volt battery cable suitable enclosure hardware

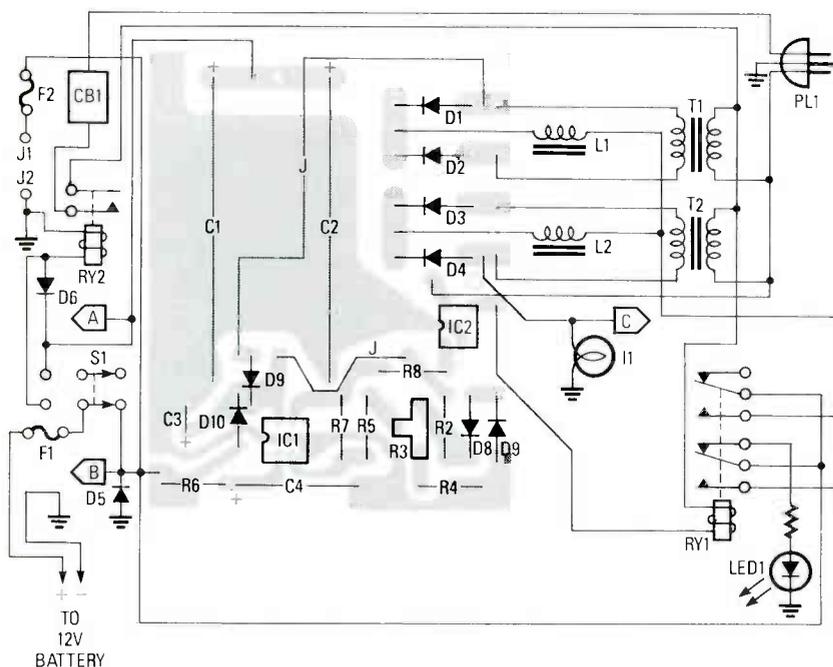


FIG. 5—THE PARTS PLACEMENT diagram for the power supply. Make certain that the parallel-wired connections of T1 and T2 are in-phase. Reversed phase will produce zero output.

The meter circuit

Either the battery voltage or the AC output voltage can be monitored with the meter circuit shown in Fig. 4. A bridge rectifier made up of four silicon rectifier diodes converts the AC to DC, which is filtered by C19. A DPDT switch connects a 15-volt DC voltmeter to the 12-volt supply or the voltage divider consisting of R36 and R37.

Construction

There are two important considerations to bear in mind. A considerable amount of heat is generated, particularly by Q8, Q9, Q10, and Q11. A large heatsink is required for those transistors, and a small fan is essential to keep the heatsink at a reasonable operating temperature. The physical placement of the components should allow for free movement of air through the enclosure, with the intake through the sides and the exhaust through the top. The heat-sink should be located near the fan. The power supply's rectifier diode should also be located near the fan and mounted so that the leads hold them about a half inch above the board. To protect them, Q2 and Q3 should each be fitted with a small heatsink.

collator to lock to the powerline frequency. Some degree of control over the exact phase relationship is possible by adjusting potentiometer R20. When properly adjusted, the AC output will be in-phase with the powerline, and the unlocking and locking that occurs when the power

fails and then returns will be gentle, causing very little disturbance.

The sine wave generator is supplied with clean, ripple-free 9 volt power by IC3, a 7805 5-volt regulator. Pin 3 of the regulator is held at 4 volts above ground by R16 and R17 to obtain 9 volts output.

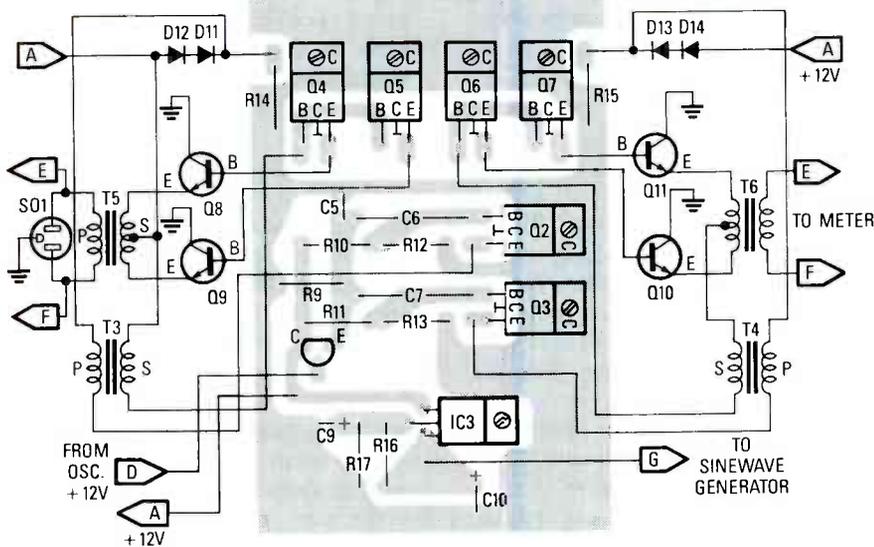


FIG. 6—THE PARTS LAYOUT FOR THE AMPLIFIER. Transistors Q8–Q11 and diodes D11–D14 must be mounted on a heatsink, as indicated by the dashed lines.

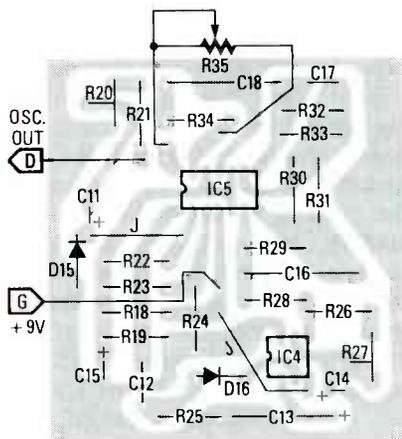


FIG. 7—THE SINEWAVE GENERATOR'S parts layout. Nothing is critical.

The amplifier draws a very high current. A fraction of a volt lost as a result of voltage drop in the power supply leads will result in several volts lost at the output, so use heavy-gauge wire for all leads from the power supply and battery to the center-taps of T5 and T6, and to the chassis ground. (12-gauge wire is recommended.)

A Radio Shack 270-238 aluminum chassis box makes an excellent heat-sink. Mount the cover upside down in the bottom of the enclosure. Mount the power transistors on the other section with the leads protruding inward. The transistors' metal cases, which are connected to the collectors, should be grounded to the heatsink. Drill holes for D11, D12, D13, and D14, sized for a tight fit. Position pairs of diodes between the two transistors they affect electrically; i.e., D11 and D12 between Q8 and Q9; D13 and D14 between Q10 and Q11. Use a

small amount of heat-sink compound when mounting the transistors and diodes. Insert the diodes in their mounting holes so that the leads from the anode of D11 and the cathode of D12 protrude from the top. Bend and solder the leads together to form a bar between the two diodes. Do the same with D13 and D14. Use soldering terminal strips on the underside of the heatsink for all connections.

Position the heatsink in the other half of the chassis box so that the tops of the transistors will be near the fan, then drill holes for self-tapping screws to hold the two halves together. Transformers T3 and T4, and chokes L1 and L2 will fit nicely in the lower half of the chassis box.

The large power transformers can be mounted in the base of the enclosure to either side of the heatsink. The sides of the enclosure should be

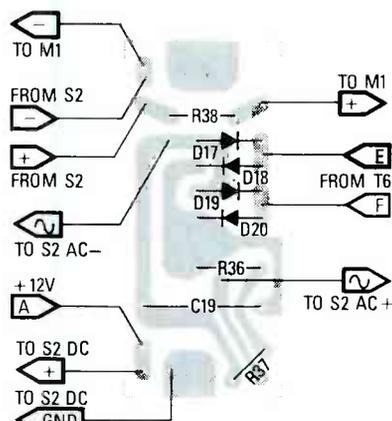


FIG. 8—THE PARTS LAYOUT for the meter board is simple, but there are many connections to other circuits; so take extra care with the interconnections.

vented so that cool air is drawn over them. Depending on the enclosure used, it may be necessary to provide a shelf over each pair of transformers for the associated components.

Although printed-circuit board construction isn't required, it is recommended, and foil patterns are shown in PC Service for those who wish to use them. The corresponding parts-placement diagrams are shown in Figs. 5–8. The foil patterns can be modified to suit your needs, or the circuits can be built in a similar manner on perforated wiring board. Mounting tabs of Q2, Q3, Q4, Q5, Q6, and Q7 are their collector connections; they must be grounded by machine screws if PC board construction is used.


The author used a small section cut from an aluminum chassis box as a heatsink for Q2 and Q3. That heatsink is mounted against the transistor's mounting tabs with machine screws extending through holes drilled in a lip on the heatsink. The heat sink extends down over the edge of the PC board into the flow of air entering the side of the enclosure. The sine wave generator board is piggy-backed over the amplifier board using 6-32 machine screws and spacers.

The fan must operate on 12-volts DC, otherwise cooling would be lost during a power outage. Mount the fan in the top of the enclosure so that it exhausts the air. The vent should be closed except for a circle whose diameter matches that of the fan blades, so that all air must enter the enclosure through the side vents.

Testing the power supply

The power supply should be tested before the amplifier is connected. That can be done before the amplifier is even built. Set R3's wiper at the end that's connected to R4. Do not plug the linecord into an outlet yet. Connect a 12-volt storage battery to the supply and set S1 to either CHARGE or OPERATE. Relay RY2 should energize and LED1 should light. You should measure about 12 volts at pins 2 and 7 of IC1. Pin 6 should be low.

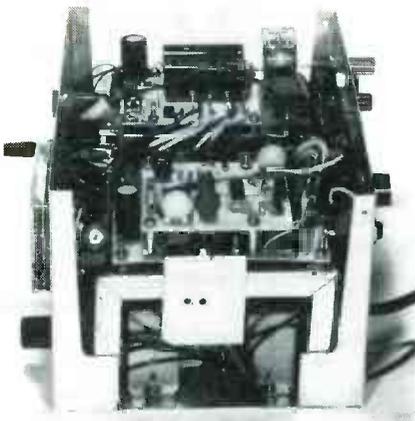Plug the linecord into an outlet. Lamp LMP1 should light. Relay RY1 should remain deenergized and you should measure about 14 volts at its normally-open contacts. Pin 7 of IC1 should measure about 14 volts and pin 3 should measure about 11 volts. Pin 6 should remain low. Rotate R3 to its



THE UPS IS BUILT LAYER ON LAYER upwards from the base of the cabinet. Stacked mounting nuts, or spacers, at the mounting screws can be used to separate the layers.

opposite end to obtain 14 volts at pin 3; RY1 should now energize and LED1 should be dark.

You should measure about 13 volts across the battery. Rotate R3 just to the point where RY1 deenergizes.

The charger should cycle *off* and *on* as the battery voltage rises and falls. The correct setting of R3 is where, with a fully-charged battery, the charger cycles very infrequently and turns off almost as soon as it turns on. The battery potential should measure 12.5 volts with no charging current. At a lower battery voltage, the charger should cycle unless the battery is so badly discharged that the full current of the charger cannot bring the voltage back up to 12.5.

Testing the sinewave generator

The sinewave generator can be tested independently. If you build it on a PC board without the 9-volt regulator, you can use a 9-volt transistor battery or an external power supply for the test. Set R20's wiper to its ground end. A scope should show a square-wave at pin 5 of IC4. With a 60-hertz sinewave driving the scope's horizontal sweep, set R27 for a frequency of 60 Hz—which will produce a rectangular Lissajous pattern. The frequency need not be exact. A slowly changing pattern is acceptable.

With the scope set for a normal 60-Hz sweep, you should observe a triangle wave at the output of IC5-b and a sinewave at the output of IC5-c. A sinewave should also be present at the output of IC5-d, varying in amplitude as R35 is adjusted. If any of those tests are negative, check for 4.5 volts DC at all input and output pins.

With 12.6-volts AC connected to R21, rotate R20 until the scope shows output pulses from IC5-a: The oscillator should be locked to the line frequency. Set up the scope for a Lissajous display as before and observe the output from IC5-d. It should be an oval that is nearly closed. It should be possible to adjust R20 so that the display is very nearly a sloping straight line, indicating that the output signal is in-phase with the powerline. If the AC signal is removed by unplugging the linecord, the pattern should begin a slow change to an oval that opens and closes. Readjust potentiometer R27 in order to minimize the rate of change. When the AC signal is restored, the display should quickly return to the sloping line pattern.

Testing the meter circuit

The meter circuit can be tested and calibrated by connecting the rectifier to the AC powerline. With S2 in the AC position, adjust R37 for a meter reading one-tenth that of the AC line voltage as measured independently with a calibrated meter. If there is no reading, check for about 130 volts DC across C19 to see if the rectifier is properly connected. A scope will show a large ripple component since C19 has a relatively low capacitance.

Testing the amplifier

Connect the amplifier to the 12-volt power source and the sinewave generator. Set the wiper of R35 to the end connected to the output of IC5-d, which is the setting for a zero output signal. Set S1 to the OPERATE



THE AMPLIFIER OUTPUT TRANSISTORS (one is under the function switch) are mounted on the top of a small chassis box that serves as the heatsink. The cooling fan is positioned on the cabinet cover directly over the transistors.

position. Check for 12.5 volts at the emitters of Q2, Q3, Q8, Q9, Q10, and Q11. Those transistors should become slightly warm, but not hot. Check for about 11 volts at the bases of Q4, Q5, Q6, and Q7, and for about 4 volts at the emitter of Q1.

During the following procedures, use the same caution in handling the output as you would with 117-volt household power. Connect one lead of each of the 120-volt windings of T5 and T6 together, leaving the others unconnected. Connect an AC voltmeter across one of the windings and set it to a range higher than 110 volts. Slowly rotate R35 until there is a measurable output voltage. If that fails, make sure that drive to the output stages are opposite in phase. The AC voltage from the base of Q4 or Q6 to the base of Q5 or Q7 should be twice the reading to ground. If it is not, reverse the connections to the windings of either T3 or T4, not both.

Next, check that the 120-volt windings of T5 and T6 are parallel-connected in-phase. Connect the voltmeter to the leads left unconnected. If the voltage is double the previous reading, the windings are connected in series. Reverse the connection of one of the windings. If no voltage is measured, connect the other two leads together. Connect a 15-watt lamp to the output. Adjust R35 for full output. The lamp should reach full brilliance and you should measure about 125 volts.

Using the UPS

In use, S1 should be set to OPERATE before the load is switched *on*. Check the AC output to be sure it is supplying at least 120 volts; the voltage will drop slightly under load. If the voltage is wavering, the oscillator is not locked in synchronization with the power line; readjust R27 and R20 after a short warm-up period. When properly adjusted, lock should occur at turn-on.

Switch the load on and recheck the voltage. It cannot be set high enough to cause harm, but it need not be set to the maximum. Some clipping will occur at the highest setting. A dip to 110 volts during operation of a discontinuous load, such as a disk drive or a printer, is acceptable.

The duration of operation during an outage will depend on the size of the battery. A motorcycle battery should allow 15 minutes of operation. **R-E**

BUILD THIS

AUDIO SCRAMBLING SYSTEM

PERHAPS THE MOST SERIOUS PROBLEM with any kind of radiotelephone transmission is its inherent lack of privacy. Anyone can monitor the signal—using a scanner or a conventional receiver—and eavesdrop on both sides of the conversation.

Although there may be legal considerations either in effect now or under consideration that would limit or prevent the unauthorized reception of some or all radiotelephone signals, the fact remains that there is unauthorized eavesdropping that no amount of laws, rules, or regulations is going to stop.

To thwart both eavesdropping and the unauthorized use of information that might be attained, many communication systems make the signal unintelligible through some kind of scrambling; and only those specially-equipped receivers having matching decoder circuits can unscramble the signal.

One relatively simple but effective technique that's used to scramble voice transmissions is known as "frequency inversion." Briefly, in frequency inversion a fixed-frequency scrambling "carrier" is mixed with the audio signal in such a way that the original audio spectrum is translated into a different spectrum, and the resulting transmitter modulation sounds like duck chatter. As a matter of fact, the scrambled sound is often called "Donald Duck." Even if the scrambled duck chatter is translated back to the vicinity of the original spectrum, *but not necessarily back to the original frequencies*, the audio will still be unintelligible.

Frequency-inversion scrambling is commonly used by the police for radio communications in order to prevent casual listeners from eavesdropping on sensitive messages. Private enterprises also use similar methods to scramble telephonic communications to prevent the interception of proprietary information.



Here's a high-tech version of the old "Captain Midnight" secret decoder ring. Only this time out you scramble and unscramble sound instead of written messages.

KEVIN LINDELL

Your own scrambler

If you have a need to scramble and descramble any kind of radio or telephone voice message, even a cassette tape that is sent through the mail, you'll find you can do the job quickly and cheaply with the combination scrambler/descrambler unit described in this article. The scrambled output, whether by radio, telephone, or tape, sounds similar to the duck chatter that is produced when a single-sideband radio transmission is received by an AM receiver.

The scrambler/descrambler uses a device called a *balanced modulator* to produce frequency-inversion scrambling. A balanced modulator is a special kind of mixer that will produce an output containing sidebands when fed both a carrier frequency and modulation. The upper sideband consists of the *sum* of the carrier frequency and the modulating frequencies while the lower sideband consists of the *difference* frequencies. It is the difference frequencies in the lower sideband that are used for scrambling.

The balanced modulator

The balanced modulator inherently tries to null the two original input frequencies in the process of creating new products at its output.

If the carrier and modulation waves are of the form:

$$A_{PEAK} \sin(\omega t) \quad (1)$$

where, A = Amplitude, $\omega = (2\pi f)$, f = frequency, and t = time, then, multiplying two such waves produces:

$$A_{OUT} = (A_c)(A_m)(\sin \omega_c t)(\sin \omega_m t) \quad (2)$$

where, m = modulation frequency, and c = carrier frequency.

Recalling the trigonometric identity:

$$(\sin A)(\sin B) = \frac{1}{2}[\cos(A-B) - \cos(A+B)] \quad (3)$$

substituting equation (3) into (2) produces the following equation, which clearly shows the sidebands:

$$A_{OUT} = \frac{A_c A_m}{2} \left[\cos 2\pi(f_c - f_m)t - \cos 2\pi(f_c + f_m)t \right] \quad (4)$$

where

$$\cos 2\pi(f_c - f_m)t$$

is the lower sideband and

$$\cos 2\pi(f_c + f_m)t$$

is the upper sideband

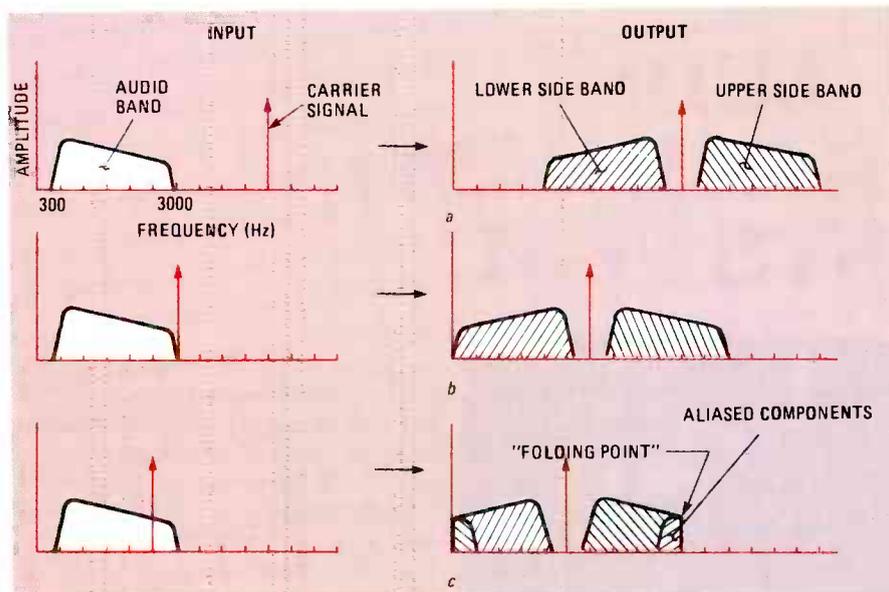


FIG. 1—THE MODULATION WILL FOLD BACK ON ITSELF if the carrier is within the modulation passband. *a* shows how the modulation is inverted and shifted higher in frequency if the carrier signal is displaced from the highest modulating frequency. In *b* the carrier is just above the audio band so the modulation is inverted, but the difference frequencies occupy essentially the original passband. In *c* the carrier is within the audio band, causing some modulating frequencies to fold back within the audio band.

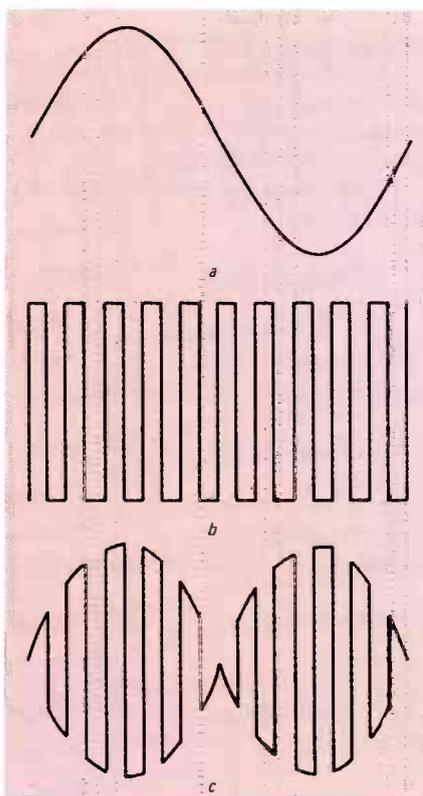


FIG. 2—HOW THE SCRAMBLER'S modulation works. If the audio signal shown in *a* is used to modulate the square-wave carrier in *b*, the resultant output is the signal shown in *c*: the original audio chopped by the carrier.

If the carrier frequency is not higher than the audio range to be inverted, then a distortion that is known as *aliasing* will occur in which the audio frequencies appear to "fold over" on themselves. Figure 1 shows how the

aliasing effect might affect a scrambler/descrambler. Figure 1-*a* might be considered normal modulation/carrier positioning. As the carrier frequency moves closer to the audio band (Fig. 1-*b*), the sideband spectrum is shifted lower. When the carrier is within the audio range (Fig. 1-*c*), it causes the output spectrum to produce false, or aliased, products that are "folded" around the carrier frequency.

There are two basic ways to make a balanced modulator. One method

uses devices that have non-linear characteristics, such as a diode's voltage/current relationship. That method requires a critical matching of the components to achieve good performance. The second method, which is used in the scrambler/descrambler, uses time-variant devices having two states, either *on* or *off*. The two-state characteristic can be used to pass or not pass a signal through a circuit or a circuit path. If the signal can be toggled through a symmetrical pair of switches whose outputs are summed in a balanced manner (i.e., with equal magnitude and opposite sign), the result will be the signal multiplied in time by the switching rate.

The balanced modulator in our scrambler/descrambler uses a quad FET IC having four closely-matched switches in a single package (which reduces the component-matching problem). The circuit also uses an op-amp to provide the balanced summing operation. The switches are controlled by the clock circuit. Toggling the switches rapidly creates a constant amplitude and frequency square-wave carrier for the balanced modulator.

How it works

Figure 2 shows how the scrambler works in the time-domain. Fig. 2-*a* shows a typical sinewave audio-input signal. Figure 2-*b* shows the square-wave carrier. If the input signal is chopped by the carrier into several smaller pieces at the carrier rate and the phase is reversed at each chopped

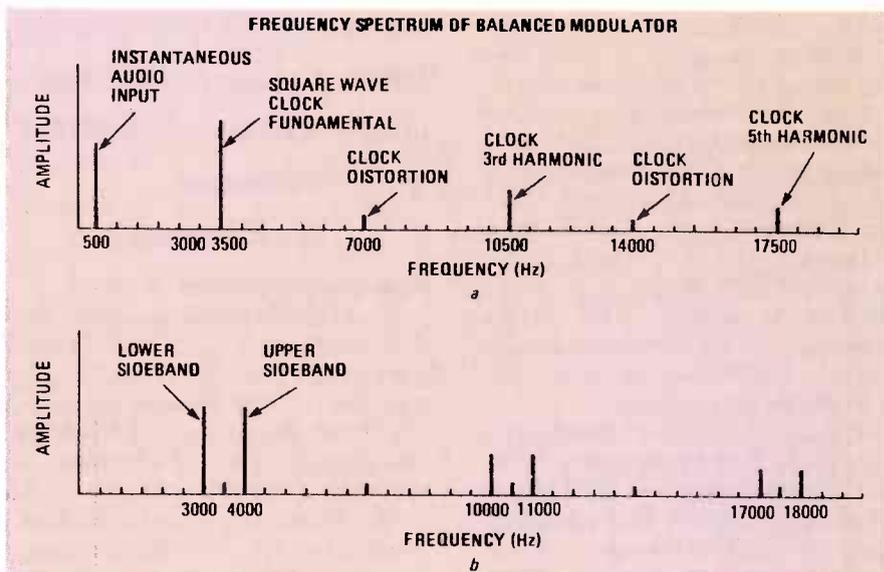


FIG. 3—THE SQUARE-WAVE CARRIER produces unwanted audio products in the form of harmonics and sidebands, shown in *a*. Those products must be filtered out. The resulting frequency spectrum, shown in *b*, has components located at the modulation frequencies both above and below each carrier harmonic.

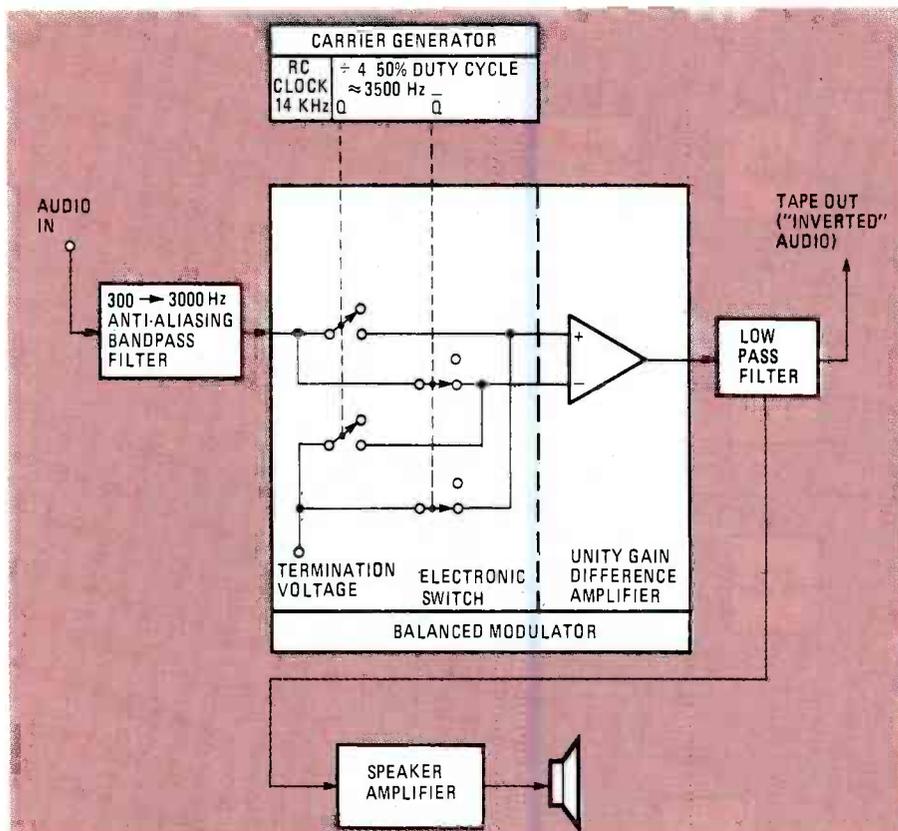


FIG. 4—FUNCTIONAL DIAGRAM OF THE SCRAMBLER. The switching is actually done by a balanced modulator that is driven from the carrier generator.

interval, the resulting output will appear as shown in Figure 3-c when viewed on an oscilloscope.

As shown in Fig. 3-a, the square-wave carrier also produces unwanted audio products in the form of harmonics and sidebands. Those products add to the distortion and must be filtered out in order to return the audio signal to its original form.

Mixing the squarewave with the audio-input signal results in an output that has sideband components centered around each harmonic of the square wave. As shown in Fig. 3-b, the resulting frequency spectrum has components located at the modulation frequencies both above and below each carrier harmonic, but there are no components at the carrier frequency or its harmonics. Filtering out the lower sideband, which is below the fundamental frequency of the squarewave, produces the scrambled audio output.

As long as the carrier switching-rate is maintained slightly above the normal audio range, the scrambled audio will still be audible, but low input tones will produce high output tones, and vice-versa, making the final output sound highly distorted and unintelligible. If an identical method is used to demodulate the dis-

torted speech, the signal will be restored to its original form.

A graphic representation of how the scrambler/descrambler affects the normal audio input is shown in Figure 3-b. The carrier, or switch-toggle rate, is set at 3500 Hz. The audio input at the instant shown in this example equals 500 Hz. Note the sidebands that are produced. The upper sideband, also called the sum frequency, is equal to the carrier frequency plus the audio frequency, which, for this example, is 4000 Hz. (3500 Hz plus 500 Hz.) The lower sideband, or difference frequency, is 3000 Hz. (3500 Hz minus 500 Hz). Having selected the lower sideband as the scrambled audio, the 500 Hz tone, which was put into the scrambler, is changed into a 3000 Hz tone. Similarly, a 3000 Hz audio input tone produces a 500 Hz output tone. Carrying that process on for the entire spectrum of input audio frequencies produces the scrambled result. Reversing the process effectively descrambles the audio. The original carrier tone may still be heard when there is no audio modulation present—although at a volume much below that of the scrambled audio level. Carrier leak-through is due to the fact that the carrier frequency is in the

audible range and that the balanced modulator is not perfectly balanced.

The major components

Figure 4 is a block diagram of the scrambler's five major sections. The CARRIER GENERATOR is an RC clock and divide-by-four counter that produces the switching signals for the balanced modulator.

The ANTI-ALIASING BANDPASS FILTER conditions the audio-input signal by limiting the frequencies fed into the balanced modulator to the nominal range of 300-to 3000 Hz, thereby reducing the high-frequency components that would cause aliasing distortion. Without the filter the balanced modulator would include erroneous information that would appear in the output signal as distortion.

The BALANCED MODULATOR is the heart of the scrambler/descrambler. Its purpose is to feed the conditioned audio input alternately, at the timing-generator rate, to the inverting input and then the non-inverting input of a differential amplifier. That process mixes the conditioned audio with the timing generator's square-wave signal, thereby creating a composite output signal that contains several sideband and harmonic frequencies.

The LOWPASS FILTER removes all but the first lower-sideband frequencies from the balanced modulator's output. The filter's output is "inverted audio," the scrambled signal.

The SPEAKER AMPLIFIER drives an internal speaker. When the device is used as a scrambler the speaker reproduces the scrambled output from the lowpass filter. When the device is used as a descrambler the speaker reproduces the descrambled sound. Alternately, the sound can be fed through the TAPE OUTPUT connection to an external amplifier, speaker, tape recorder, or whatever.

Circuit description

Figure 5 shows the schematic of the scrambler/descrambler. Integrated circuit IC1 is an astable 7555-timer circuit running at approximately 14 kHz. The timer's frequency is determined by R1, R2, and C2. Small changes to the frequency can be made by adjusting R1, which is an externally-accessible multi-turn trimmer.

The output from IC1 is fed to the clock input of IC2, a dual D-type flip-flop that is used to divide the 14-kHz clock output by a factor of 4 ($\div 2 +$

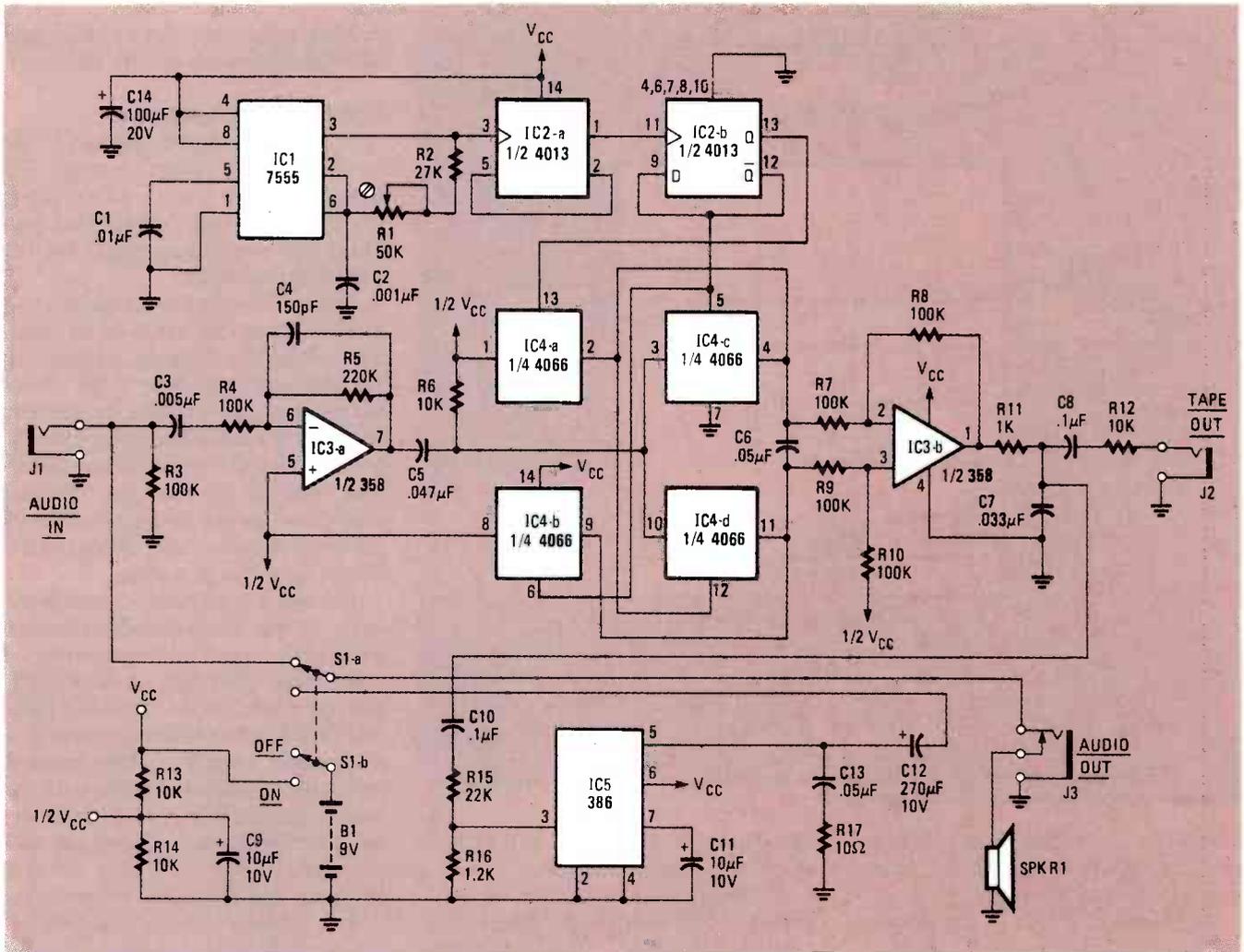


FIG. 5—THE COMBINATION SCRAMBLER/DESCRAMBLER. Switch S1 controls the power through one section and bypasses the scrambler through its other section.

÷ 2). The division creates a 3.5-kHz 50% duty-cycle square wave at IC2 pin 13, and an identical but inverted waveform at pin 12. The two square-wave signals are used as carriers to control IC4, a quad analog switch that functions as the balanced-modulator's switching network.

The other input to the balanced modulator is the audio signal from J1 that is to be scrambled. The input signal should be derived from a low-impedance source such as a tape-player's headphone or speaker-output jack. Using a line-level or AUX signal source is not recommended because the scrambler's speaker is connected directly to the audio input when the scrambler unit is off, and the low impedance of the speaker would load down a high impedance line or AUX signal source. The input signal's frequency range is limited to nominally 300–3000 Hz by bandpass filter IC3-a.

At any given time the squarewave carrier will turn on either switches

IC4-a and IC4-d, or IC4-b and IC4-c at the 3.5-kHz rate. When switches IC4-a and IC4-d are on, IC4-d passes the audio input signal to the non-inverting input of differential amplifier IC3-b, and IC4-a terminates the inverting input. Switches IC4-c and IC4-d work similarly on the other half of the squarewave carrier cycle.

Unity-gain differential-amplifier IC3-b multiplies the audio input by a factor of plus or minus one, depending on the state of the IC4 switches. Resistors R7 and R8 set the gain on the inverting input while resistors R9 and R10 set the gain on the non-inverting input.

The balanced-modulator output, IC3 pin 1, is fed through the R11/C7 low-pass filter, which passes only the scrambled audio to TAPE OUT jack J2. The output level from J2 will depend on the input level to the scrambler. A sample of the signal fed to J2 is also fed to audio power amplifier IC5. The output of that device drives SPKR1.

Switch S1 turns the scrambler circuit on and off. When switch S1 is off, section S1-a connects the audio input directly to the speaker, thereby bypassing the audio scrambler circuit so that normal, unscrambled audio, can be monitored.

Construction

A template for the printed-circuit board is shown in PC Service. A pre-drilled board is available from the source given in the Parts List. Figure 6 shows how the components are installed on the PC board.

Although there is nothing unusual about the assembly, standard CMOS component-handling precautions should be used to avoid damage from static discharges. Whether you choose to use a large or a small cabinet, installation of the switch and the jacks is easier if they are pre-wired to the PC board before being mounted on the case.

If you intend to unscramble mes-

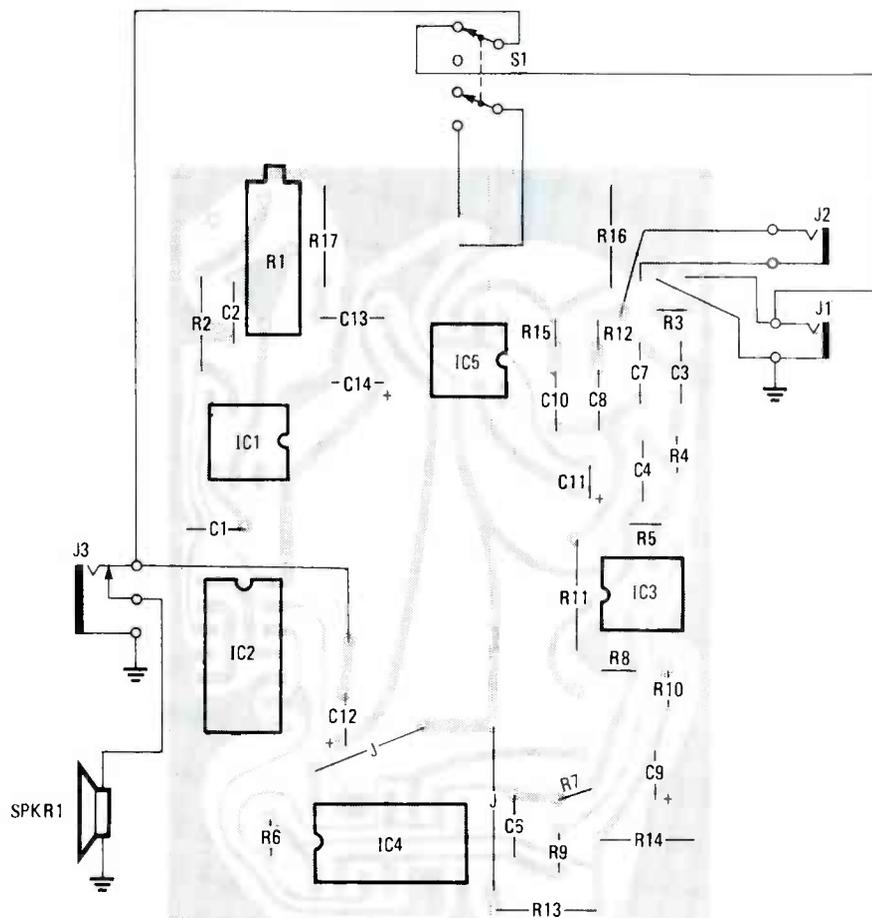


FIG. 6—THE PARTS LAYOUT. Keep the center of the board free so it can fit over the speaker.

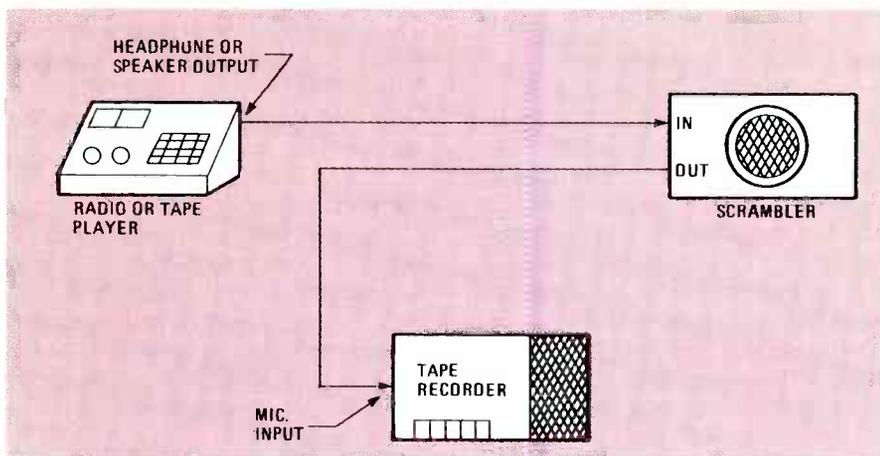


FIG. 7—THIS ARRANGEMENT CAN BE USED for either scrambling or descrambling a signal provided by a radio or tape player.

sages from several sources using different scramblers, it's possible that trimmer potentiometer R1 might have to be re-adjusted for each scrambling source; hence, to minimize headaches later on, R1 should be installed so that it is conveniently accessible from outside the cabinet.

Tuning and adjustment

Trimmer potentiometer R1, which is used to tune the square-wave scram-

bling/descrambling carrier signal, should initially be set to approximately its center position. If the scrambling device that was used to scramble the audio is also used for descrambling, no further adjustment will probably be required. If different scrambler units are used, as is sure to be the case in a typical two-way communication setup, the receiving unit's R1 will have to be tuned manually until the scrambled audio is suc-

PARTS LIST

All resistors are 1/4-watt, 10%, unless otherwise noted.

- R1—50,000 ohm, 10-turn trimmer potentiometer
- R2—27,000 ohms
- R3, R4, R7—R10—100,000 ohms
- R5—220,000 ohms
- R6, R12—R14—10,000 ohms
- R11—1000 ohms
- R15—22,000 ohms
- R16—1200 ohms
- R17—10 ohms

Capacitors

- C1—.01 μ F, 100 volts, ceramic disc
- C2—.001 μ F, 100 volts, mica
- C3—.005 μ F, 100 volts, ceramic disc
- C4—150 pF, 100 volts, ceramic disc
- C5, C6, C13—.05 μ F, 100 volts, ceramic disc
- C7—.033 μ F, 100 volts, ceramic disc
- C8, C10—0.1 μ F, 100 volts, ceramic disc
- C9, C11—10 μ F, 10 volts, electrolytic
- C12—220 μ F, 10 volts, electrolytic
- C14—100 μ F, 20 volts, electrolytic

Semiconductors

- IC1—7555, CMOS timer
- IC2—4013, dual D-type flip-flop
- IC3—LM358, dual op-amp
- IC4—4066, quad analog switch
- IC5—LM386, audio power amplifier

Other components

- B1—9-volt battery
- J1, J2—Miniature phone jack
- J3—Two-circuit miniature phone jack
- S1—DPDT toggle switch
- SPKR1—2 1/8" speaker

Miscellaneous: battery terminals, battery holder, printed-circuit board materials, enclosure, wire, solder, etc.

cessfully descrambled and can be clearly understood.

Applications

The device can be used in many applications, although its use may be restricted by local and/or Federal laws. It should only be connected to the telephone line through an FCC-approved interface, and in conformance with local regulations or procedures of the local telephone company. Be sure to comply with any restrictions before using the device.

Figure 7 shows the scrambler/descrambler connected to a radio, or a tape player. In this application, the device will either scramble the audio coming from the source or descramble an incoming scrambled transmission. The output can be monitored via the built-in speaker and/or passed on to a tape recorder.

The scrambler/descrambler also can be connected between a tape recorder and its source in order to create

continued on page 77

60-Hz TIMEBASE

Here's a one-IC
timebase generator
that's both accurate
and flexible.

J. DANIEL GIFFORD

WHILE A STABLE REFERENCE FREQUENCY is often needed when doing electronics experimentation, generating one can present some problems. Usually, a reference frequency is generated using either a crystal timebase or some form of line-frequency divider. But crystal timebases are fairly expensive and line-frequency dividers usually require two or three IC's to get a usable 1 or 10 Hz frequency from a 60-Hz line. There is, however, a relatively obscure CMOS IC that can do the job inexpensively.

That IC, the Motorola MC14566B (and the equivalent 4566), carries the imposing title of "Industrial Timebase Generator," which is probably a large part of the reason it isn't commonly used. However, the device can be used anywhere an experimenter or hobbyist needs an inexpensive reference frequency: in clocks, frequency meters, period counters, etc.

Being a CMOS device, the MC14566B can operate with any supply between 5 and 15 volts. And, being CMOS, it draws only about 10 mA of supply current across that voltage range.

Inside the MC14566B

As Fig. 1 shows, the MC14566B contains three independent function blocks: a BCD (Binary Coded Decimal)-output divide-by-10 counter, a BCD-output divide-by-5 or -6 counter, and a monostable multivibrator. The two counters share a common reset, which is tied to ground for nor-

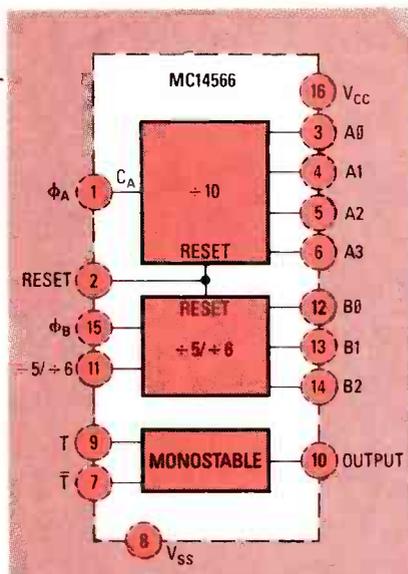


FIG. 1—PINOUT AND BLOCK DIAGRAM of the Motorola MC14566B, or the equivalent 4566, timebase generator.

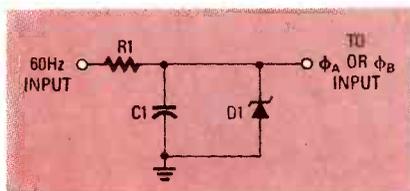


FIG. 2—THIS RESISTOR-CAPACITOR-ZENER network allows the MC14566B to take its clock signal from either end of the transformer that powers the circuit.

mal operation and brought high to reset both counters to zero.

Both counters are clocked by the falling or negative edge of the clock pulse, and both have pulse-shaping networks on their clock inputs (ϕ_A and ϕ_B) that allow them to be directly driven by a low-voltage sinewave signal via a resistor-capacitor-Zener network like the one shown in Fig. 2. The source for the sinewave is the transformer that powers the circuit; the input of the network may be connected to either end of the winding that

powers the MC14566B circuit. The Zener should be a 1/2- or 1-watt unit, and have a voltage rating that's within 10% of the supply voltage. With such a Zener in place, the AC peak-to-peak voltage (V_{PP}) can be from 70–200% of the circuit's DC supply.

Although the counters have standard BCD outputs, we have little need for that format for our application. Therefore, it is more practical to regard them as division-ratio outputs. Table 1 shows the output-division ratios and the accompanying duty cycles for each counter's outputs.

Using the IC

Figure 3 shows the most common set-up for using the MC14566B as a frequency standard. With the 60-Hz signal from the transformer applied to ϕ_B , the B2 output will provide a 10-Hz frequency. If that signal is used to drive ϕ_A , the A3 output will provide a 1-Hz signal.

Many other output frequencies can be obtained from the IC. The actual output depends upon which output of the first counter is used to clock the second, and which of the seven outputs is then used. Through various combinations, some 12 different frequencies should be available, with duty cycles of 20, 40, and 50 percent.

The third section of the MC14566B is a simple monostable multivibrator with a fixed pulse-width output, positive- and negative-edge triggering, and a normally-low output. With

continued on page 77

TABLE 1

OUTPUT	DIVISION RATIO	DUTY CYCLE (%)
A0	2	50
A1	4	40*
A2	10	40
A3	10	20
B0	2(2.5)	50(40*)
B1	6(5)	33(40)
B2	6(5)	33(20)

*PULSES IRREGULARLY SPACED
FIGURES IN () FOR ÷5 MODE

Calibrating VCR Counters



Can't figure tape-timing? Here's an easy way to make a tape counter indicate in hours and minutes.

FRED BLECHMAN

ALL MODERN VIDEOCASSETTE RECORDERS and players, and some tape rewinders, have either mechanical or electronic digital tape counters. With very rare exception—those being the few “pro quality” models with counters that indicate tape timing down to the nearest second—tape counters are “relative reading” devices. That is, they have no correlation to actual timing nor to the length of tape used or remaining. The digits are merely numbers whose rate of change is linked to the design of the mechanism rather than the elapsed time of the recorded program.

The counter is usually powered by a belt that is driven in some way by the take-up reel. Since the tape moves at a constant speed and accumulates to an increasing radius on the takeup reel, as time goes on fewer revolutions of the take-up reel are needed to hold the same length of tape. Therefore, the counter's rate is constantly changing; decreasing because the reel slows down as the tape is wound.

When the rate changes continuously, about the only value that a counter has is to indicate the relative

tape position. A given number of counts from the beginning of a tape should bring you to the same point on the tape each time. Although that is a handy way to locate a section of the tape, the counter would be even more useful if its reading were related to the tape's running time. For example, if you go out for the evening and automatically record four hours of TV shows, on returning you can conveniently and quickly cue the tape to the second, or even the fourth program by fast-winding to a known time reading.

Recalibrating a conventional VCR or rewriter counter to be time-indicating is a rather simple task. We'll show you how easily you can do it using two different methods.

Calibrating VCR counters

There are basically two ways to calibrate a VCR's counter. One method takes only paper and pencil, a watch or clock that indicates in seconds, and two hours of your attention. The other method requires a video camera and a specially prepared tape. Either way, the results can be graphed as shown in Fig. 1 through Fig. 4. Once you cali-

brate your own counter, you'll be able to use the graph and the counter's reading so that you can fast-wind precisely to the desired selection.

The calibration procedures described are for a VHS T-120 (2/4/6) hour tape, which is by far the most popular video-tape size and format. (The procedure would be the same for Beta tapes.) Keep in mind that all tapes do not necessarily have the same takeup-reel hub size, so never assume that a counter reading has the same meaning for various tape lengths. The

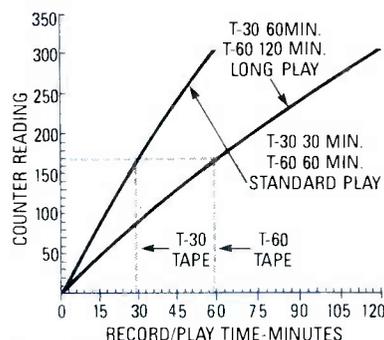


FIG. 1—IT'S ONLY NECESSARY to calibrate the highest speed. The calibrations for a slower speed are simply a linear multiple of the highest speed.

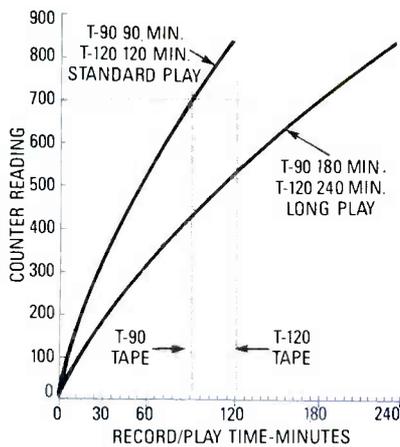


FIG. 2—BECAUSE THE SAME SIZE hubs are used, the curve for a T-90 tape is the same as the first three-fourths of a T-120 tape.

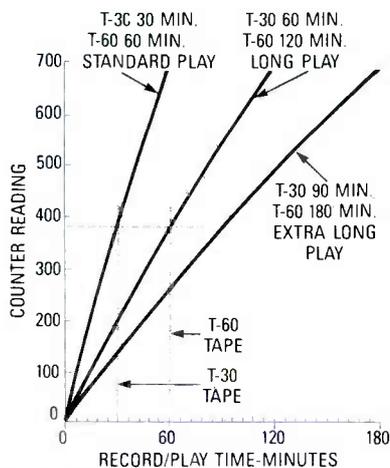


FIG. 3—THIS IS HOW the calibrations for "short" tapes work out for a particular Magnavox 3-speed VCR.

shorter tapes use a larger-diameter hub to create the visual appearance of a "full reel." In the VHF format, the T-90 and T-120 tapes use the same hub, while the T-30 and T-60 tapes use a similar, but larger hub.

Time the tape

Timing a tape is an easy, but time-consuming task. Start by completely rewinding a T-30 or T-60 blank tape. Then set your VCR's counter to zero. Next, set the recorder to the SP (Standard Play) speed, or whatever the *fastest* speed (shortest recording time) is called on your VCR.

Next, using a watch or a clock (a stopwatch is best), wait until the seconds are at zero and then start to record. Every five minutes write down the time and the counter's reading. Do that until the tape ends. That's all there is to it!

Using the data, plot a curve of the kind shown in Fig. 1; which is for a

T-60 tape recorded on an RCA model VBT200. Once you have drawn the standard-speed curve you can plot a curve for the LP mode (Long Play:

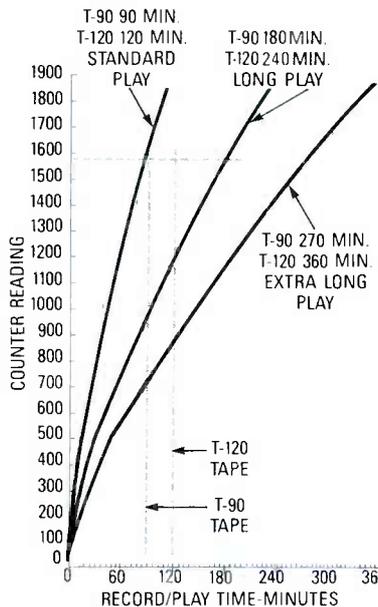


FIG. 4—USING "LONG" TAPES on the Magnavox VCR, we find that the calibrations for the 0-500 reading are exactly the same as those for the shorter tapes.

half-speed, twice-time) by simply doubling the time for each counter setting. Also, since the same hub size is used, the counter readings for a T-30 tape are the first half of each T-60 curve.

Figure 2 shows the the SP and LP curves for a T-120 tape on the same recorder. Notice that the T-90 tape is shown as the first three-fourths of each T-120 curve; that is because the same size hub is being used.

The RCA model VBT200 recorder is a relative antique; it has only two speeds, 2 and 4 hours, so there are only two curves for each tape. Figures 3 and 4 show what the curves would be like for a typical three-speed VCR; in this instance a Magnavox model VR8316BK01.

The curves shown in Figs. 1 through 4 only illustrate the calibration procedure. It is unlikely that your VCR would have the same counter readings.

Using a camera

Although creating a calibration curve is simple, it does take at least two hours of your attention to calibrate a T-120 tape. A faster calibration procedure is possible, but it requires a video camera. However, it is the *only*

good method to use when calibrating the counters used on some rewinders.

The first step is to make a T-120 two-hour tape of a clock face. While any kind of clock having a sweep hand or a digital readout for indicating seconds can be used, you'll find the old-fashioned analog clock (meaning it has hands) easiest to photograph. In a pinch you can use a watch if your camera has a macro-focus (close-up) lens.

Make sure your camera lens is aimed straight at the center of the clock. Since the minute hands on most clocks are placed well above the clock face, parallax may make it difficult to tell the exact minute reading if you are too close to the clock, especially if the camera isn't aimed directly at the center of the clock.

Set the clock to Midnight (all hands straight up). Rewind the tape, set the recorder to the fastest speed, and start the clock when you start recording. You will be, in effect, creating a special tape that has the elapsed time displayed on the entire length of tape.

Rewind the tape. Set the VCR counter to zero and prepare your TV for playback of the tape. Fast-forward the tape until the VCR counter reads, say, 25. Stop the tape. Then play the tape at that point and make a record of the clock reading vs. the tape counter's reading. Stop the tape, fast-forward to another counter setting, and again read the clock face. Do that as many times as you like, advancing the tape a set amount (25, 50 or 100 counts) between readings. Then plot the curves as described earlier. As shown in Figs. 1 through 4, you only need to make T-120 and T-60 "clock" tapes to cover T-30, T-60, T-90 and T-120 calibrations.

Counter-graph accuracy

Whether you're dealing with a VCR's counter or the one on a re-winder, don't be alarmed if the calibration isn't extremely accurate. Counter belt slippage, inaccuracy in your data, and poor curve plotting all take their toll. However, you'll be surprised, if you use reasonable care in gathering your data and plotting the curves, how close your calibration will be to the actual running time. You should be able to get within a couple of minutes of the desired tape location, and that's certainly better than the hunt-and-guess method you've probably been using.

R-E

R-E ROBOT

Adding some "sense" to the robot.


Part 13 LAST TIME, WE looked at an electronic eye for the robot. However, we had no way to connect the eye to the robot. This month, we'll take care of that by showing you a head unit that serves as an interface for the navigational and sensory circuits, including the eye. The head unit also controls the movement of a small rotating platform that it and its associated sensors are mounted on. The advantage of using a rotating platform is that it allows for more accurate angular movements and measurements than trying to step the robot through 1/2-degree angles.

The specific functions that the head unit will support are:

- Stepper-motor drive for horizontal scanning.
- Optional stepper drive for vertical scanning.
- Ultrasonic range finder.
- Interface to the light-sensitive eyes that we discussed last time.

Mechanical design

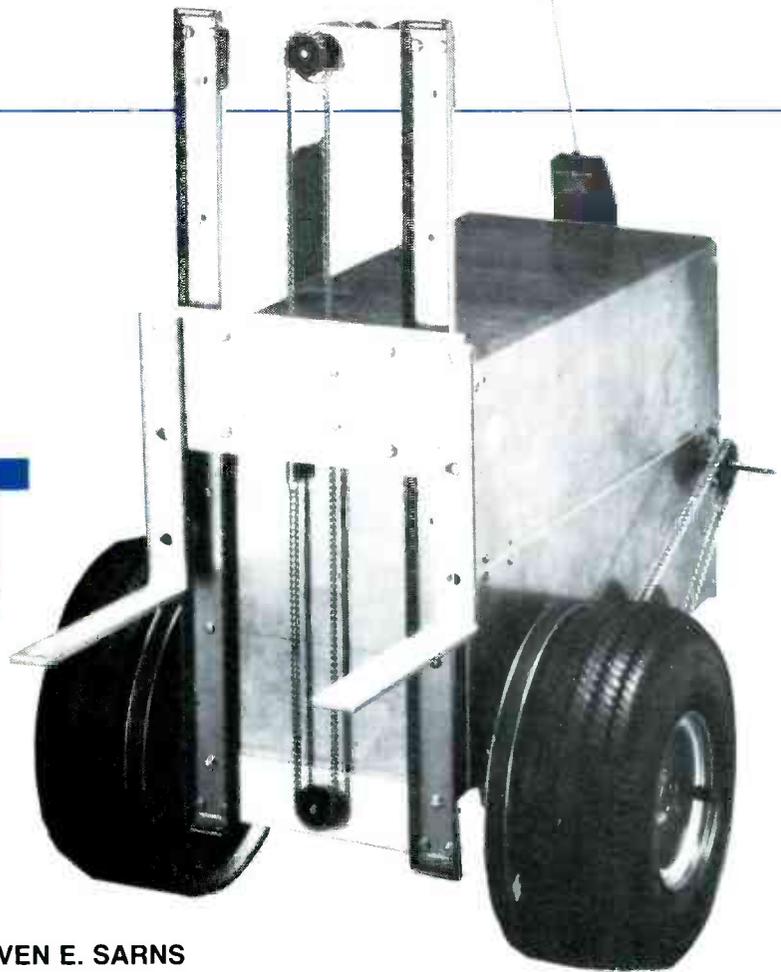We decided to design the head assembly in such a way that the entire unit, including the motors, etc., is detachable. That means that mounting the motors in the base unit and using a pulley system is out. Instead, a rather simple mechanical design has been used, one that relies on two key components for easy solutions to



STEVEN E. SARNS

tough problems. That design is shown in Figs. 1 and 2.

As shown in Fig. 1, a 78-tooth timing-belt pulley serves as a mounting base for the entire head assembly. The timing-belt pulley is secured to the base unit, but the pulley does not rotate. Instead, the head rotates around it, driven by a motor in the head assembly. A "lazy-susan bearing" attaches the head to the pulley, providing a large diameter access hole in the middle through which all of the control wires can pass. Those bearings are used in barstools and are available at most hardware stores.

The driving motor is mounted on the bottom and inside the head, with the drive belt on the bottom. A 12-

tooth timing pulley on the motor results in a 6.5:1 gear-reduction ratio for the assembly. The result is a self-contained, detachable, rotating head. The assembly can be mounted either to the top of the robot's chassis or to the top of the arm unit.

The entire head-drive unit is mounted within a 10 × 6.6 × 4.5-inch aluminum case. (The case is available from the supplier mentioned in the Sources Box that is elsewhere in this article.) One .062-inch removable aluminum side is used as the bottom and all of the drive components are mounted to that flat plate. See Fig. 2. Once the unit has been tested, the remainder of the case is slipped back over the plate and re-

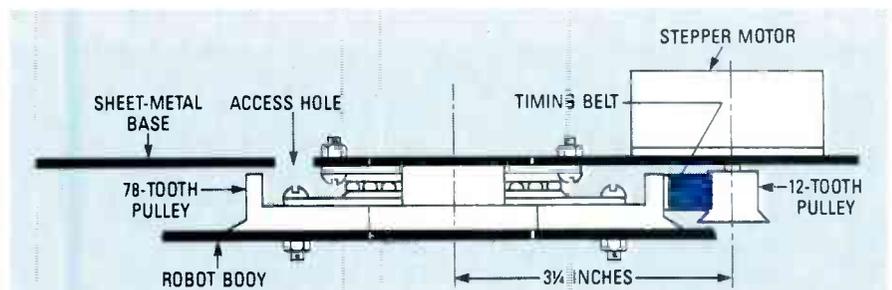


FIG. 1—THE HEAD UNIT mounts on a 78-tooth pulley. The pulley is secured to the base unit and does not rotate; instead the head rotates around it.

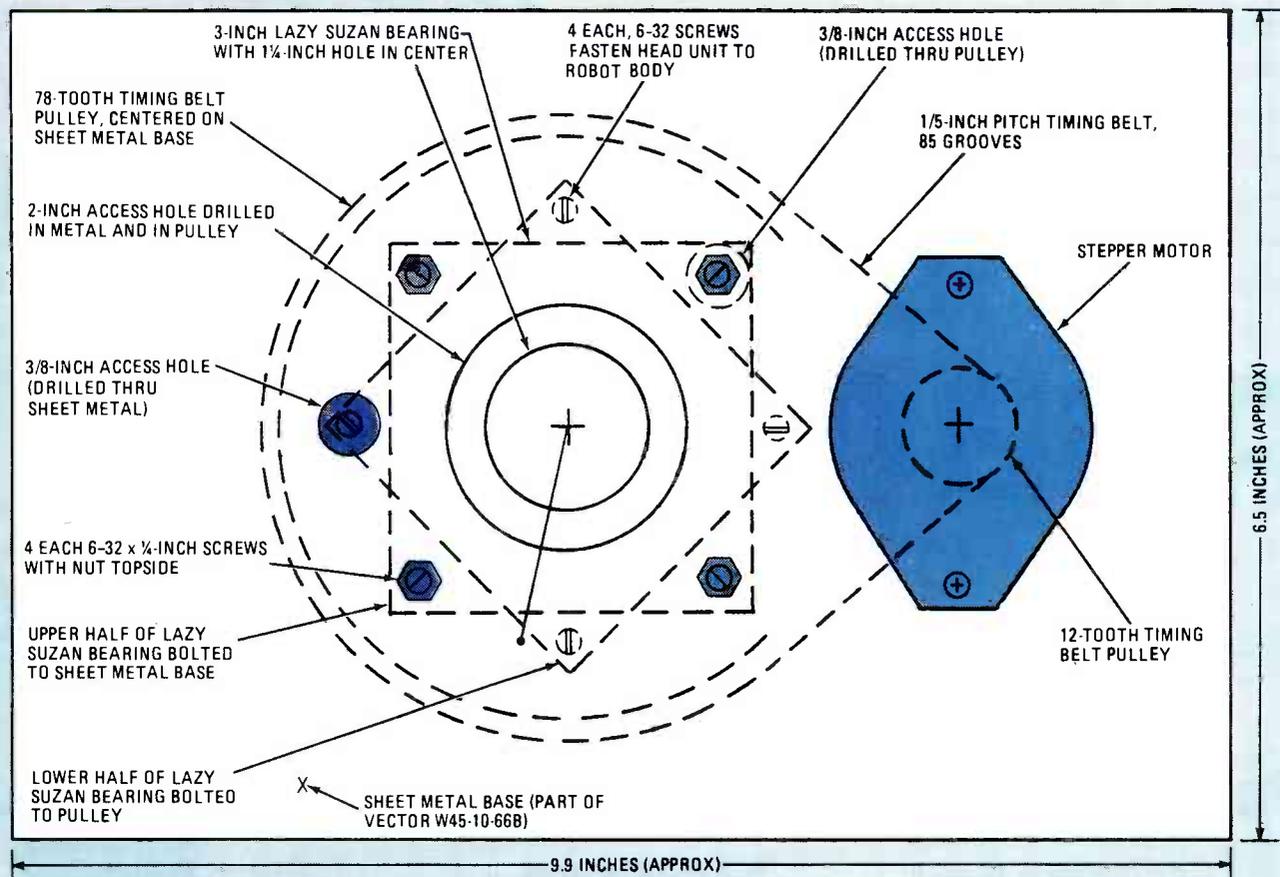


FIG. 2—THE HEAD'S DRIVE-TRAIN is detailed in this top view.

fastened. The case is ample enough to allow a 3.5-inch disk drive to be mounted in the head assembly.

User-bus interface

The schematic of the head-unit electronics is shown in Fig. 3. The head-unit circuit attaches to the bi-directional user bus via PL1. The head unit is mapped at location 0FH and consists of the peripheral functions listed in Table 1.

The peripheral address of 0FH is decoded with a single 74LS138 decoder, IC1. User-bus address lines A0 through A2 are connected to that IC's A0 through A2 inputs (pins 1-3); the

fourth address line, A3, is connected to the active-high ENABLE input (pin 6). The output is taken from pin 7, the 07 output. Thus, all inputs must be high for the output to go low. You can use that decoding scheme to map other peripherals on the user bus.

Upon examination, you will notice that the 74LS138 actually decodes the 8 addresses between 08H and 0FH, each one appearing as an active low on its 8 respective outputs. If you connect address line A3 to an active-low enable, you can decode addresses 00H to 07H.

The active-low output of the address decoder is connected to the en-

able input of a 74LS377 output latch, IC3. The clock input is activated by the WRITE signal on the user bus. Thus we can write a byte of information to the output latch by setting up the data on the 8 data lines, setting up the address on the 4 address lines, and then strobing the WRITE line low to clock the data into the 74LS377 latch.

Inputs are read in a similar fashion. The output of the address decoder is applied to one ENABLE input of a 74LS541 buffer, IC2. The other ENABLE input is activated by the READ signal on the user bus. A byte of data is read from our head peripheral unit by setting the address lines to 0FH, bringing the READ strobe low, reading the byte on the data lines, and then returning the READ strobe high.

Stepper-motor control

Stepper-motor control can be achieved in a number of ways. One is to use a microprocessor-intensive approach by driving each coil of the stepper with a single-bit output of the microprocessor. That means that each step of the stepper is accomplished by

TABLE 1

Input	Function	Ouput	Function
D0	Left eye, high freq	D0	Horz stepper step
D1	Left eye, low freq	D1	Horz stepper enable
D2	Right eye, high freq	D2	Horz stepper direction
D3	Right eye, low freq	D3	Sonar echo initiate
D4	Sonar echo return signal	D4	Vert stepper step
D5	Limit sensor 0	D5	Vert stepper enable
D6	Limit sensor 1	D6	Vert stepper direction
D7	Limit sensor 2	D7	Sonar blank inhibit

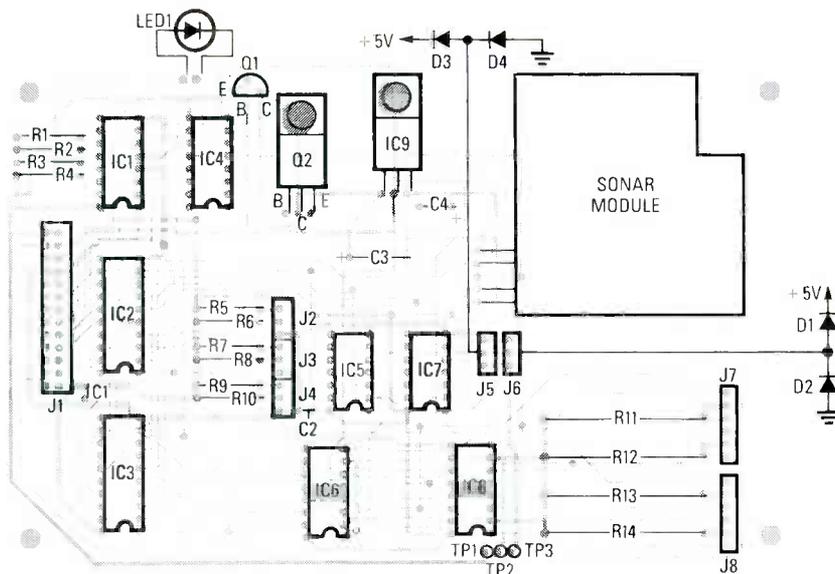


FIG. 4—ALL OF THE HEAD'S ELECTRONICS are mounted on one double-sided PC board.

LISTING 1

(HEAD UNIT—STEPPER MOTOR TEST)

HEX		VARIABLE HEAD-POS	
: M +	9 F PCX!	1 HEAD-POS +!	8 F PCX!
: M -	D F PCX!	- 1 HEAD-POS +!	C F PCX!
: M0	A F PCX!		
: TEST			
BEGIN			
M +	10 DELAY KEY?		
UNTIL MO ;			

is used to control the head's rotation. The other, IC8, is used to control the head's elevation. Since vertical scanning is an optional function, the second controller is optional. In any event, both stepper-motor controllers work in an identical manner. For simplicity, we will only discuss the operation of IC6.

The stepper controller is connected directly to the four coils of its associated stepper motor via PL7. The common wires of the two pairs of coils are returned to the power supply through optional resistors R11 and R12. Direct shorts could be used in place of those resistors in most cases. However, in some cases the use of the resistors will allow you to use a higher coil-drive voltage. That drives the stepper in the current mode, enabling a higher step rate due to the reduced effect of coil inductance. Since both 12- and 24-volt supplies are available, steppers with 12- or 24-volt coils can be used. We suggest using steppers with 24-volt coils if possible since the 12-volt regulator on the robot's main board can only supply about 1 amp total.

Motion-control software

Our software must set the direction of rotation and enable the control bits. It then must apply a pulse to the controller's step input, which causes the device to output each of the four phase-drive sequences to the motor. The top speed of our motor will be limited by the ability of the software to output the step commands, but that will not be a problem because the head must stop every few steps to accumulate data. We will not attempt to accelerate the motors, merely step them at a low speed.

As the code in Listing 1 demonstrates, the software required to rotate and test the head unit is very simple. (It is assumed that you have the PCX! and PCX@ words installed. Those were defined in Part 8 of this series, which appeared in July, 1987.)

The word M + rotates the motor one step clockwise and increments the value in the variable HEAD-POS; the word M - rotates the motor counterclockwise. The word M0 turns off the coils. TEST can be rewritten to rotate in the opposite direction by sub-

- #### PARTS LIST
- all resistors 1/4-watt, 5%, unless otherwise noted
- R1—1 ohm
 - R2, R6, R8, R10—10,000 ohms
 - R3—100 ohms
 - R4, R5, R7, R9—1000 ohms
 - R11—R14—1 ohm, 1 watt
- Capacitors**
- C1, C2—0.1 μF, ceramic disc
 - C3, C4—1000 μF, 25 volts, electrolytic
- Semiconductors**
- IC1—74LS138 1-of-8 decoder
 - IC2—74LS541 octal buffer/line driver
 - IC3—74LS377 octal D flip-flop
 - IC4—ULN2003 seven-inverter IC
 - IC5, IC7—4024 7-stage binary ripple counter
 - IC6, IC8—UCN2005 stepper controller
 - IC9—7805 5-volt regulator
 - Q1—2N3906 PNP transistor
 - Q2—TIP30 NPN transistor
 - D1—D4—1N4148 diode
 - LED1—red LED
- Other components**
- PL1—26-pin, dual-row male header
 - PL2—PL6—3-pin male header
 - PL7, PL8—6-pin male header
- Miscellaneous:** PC board, case (Vector W45-10-66B or equivalent), mechanical components (see text), wire, solder, etc.

stituting M - for M +. In operation, the 10 DELAY would be replaced by the analog-to-digital conversion process of the optical information from the eye or the sonar information from the sonar module (or both) as well as possibly releasing the Forth-83 multitasker to another task. The following word will rotate the head a given number of steps while maintaining the current relative position in HEAD-POS.


```
:CW ( STEPS — ) 0
DO
M + 30 DELAY
LOOP M0 :
```

Sonar interface

Sonar ranging modules are available from Texas Instruments and Polaroid. The TI module is the latest generation and offers improved noise-rejection characteristics. Either module will work in the circuit as will ranging devices that do not use the Polaroid transducer. We have simply designed the circuit board with a mounting area for the module and the control lines ready to wire to the module. See Fig. 4.

That's all for this month. Next time we'll show you how to use the TI module, connect the eye, build the head, and more!

R-E

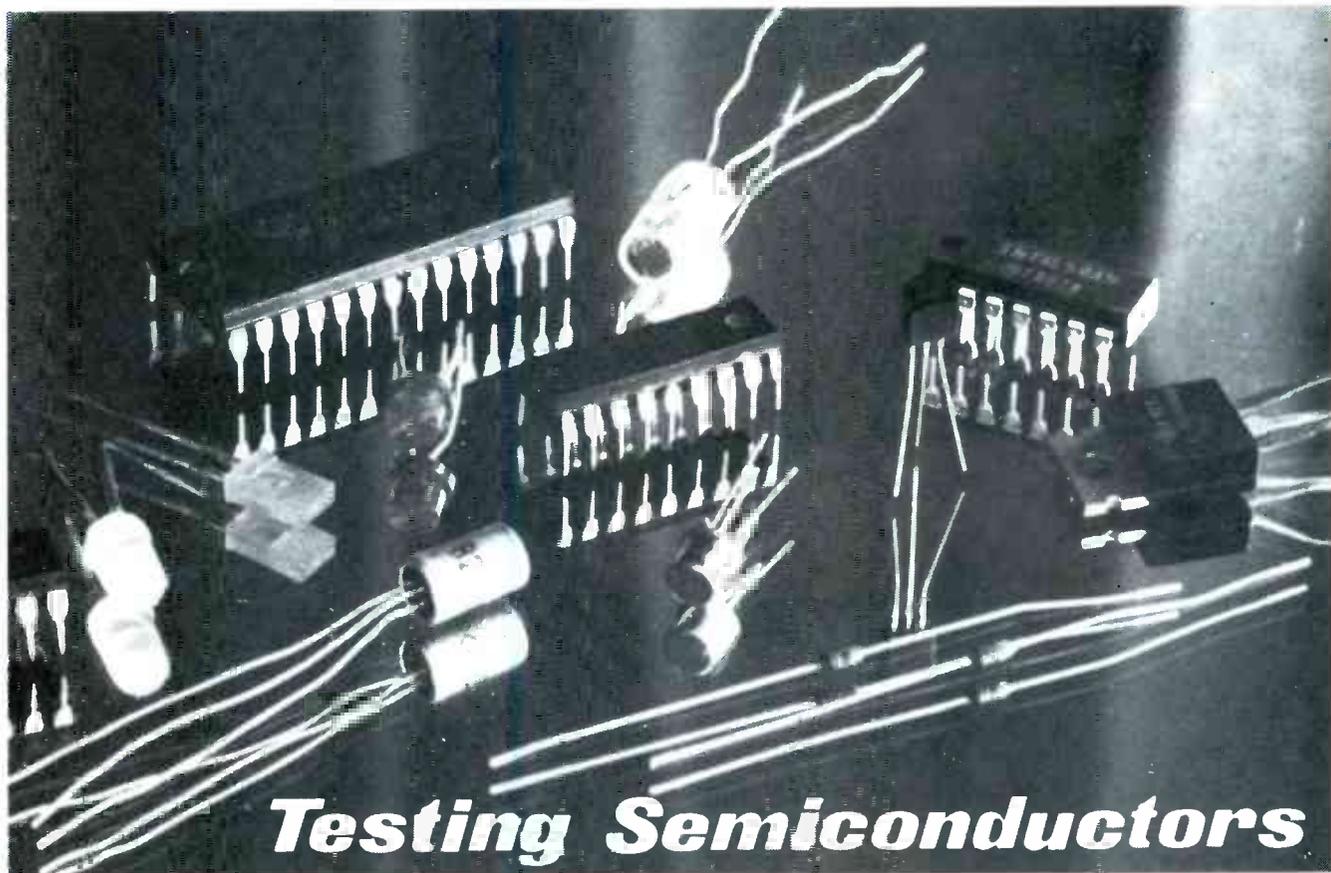

Testing Semiconductors

Our back-to-school series continues this month with a discussion of how to test TTL devices, and what the results mean.

TJ BYERS

Part 8 IN 1964, TEXAS INSTRUMENTS introduced a line of digital-logic devices for the military—which they designated as Semiconductor Network series 54 (SN54)—that forever changed the concept of electronic design. That family of TTL (Transistor-Transistor Logic) military integrated circuits quickly evolved into the popular SN74 and 74LS devices now used in nearly every electronic product. In this installment we will explore the static (DC) testing characteristics of TTL devices, and discover facts about their heritage that you may not be aware of.

TTL operation

The internal parts of a typical TTL four-input NAND gate are shown in Fig. 1-a; its schematic symbol is shown in Fig. 1-b. The device depends on input transistor Q1 having multiple

emitters—four, to be exact, labeled INPUT A, INPUT B, INPUT C, and INPUT D. Each emitter represents a logic-gate input. With all four inputs at a high input voltage (representing a logic 1), transistor Q1 is reverse biased, so Q1's base current is channeled through its collector to Q2, thereby causing Q2 to conduct, which in turn causes Q3 to conduct. Since Q3's base-emitter junction is across Q2's emitter resistance (R3), Q2's total emitter impedance is less than the value of R3, which causes a further increase in the current flow through Q2. That decreases Q2's collector voltage, which results in turning off Q4 and Q3 saturating. In that state the output voltage at Q3's collector is theoretically zero volts, representing a logic 0.

If any of Q1's emitters is returned to ground via a low input voltage (logic 0), transistor Q1 begins to conduct

heavily, thus diverting base current away from transistor Q2 and essentially saturating Q1. With transistor Q1 saturated, transistor Q2 drops out of conduction, forcing Q2's collector voltage high and its emitter voltage low. In that condition, transistor Q4 will conduct while transistor Q3 is cut off, resulting in a high voltage on Q3's collector, representing a logic 1 state.

TTL parameters

In theory, the output levels at Q3's collector should be V_{CC} for logic 1 (Q3 not conducting) and V_{DD} for logic 0 (Q3 saturated). In fact, that is not the case.

Transistors Q3 and Q4 make up what is referred to as a *totem-pole* or *active pull-up* output. Their purpose is to provide a low-impedance current source for capacitive output circuits. Through the use of brute force, subsequent logic gates can be forced to

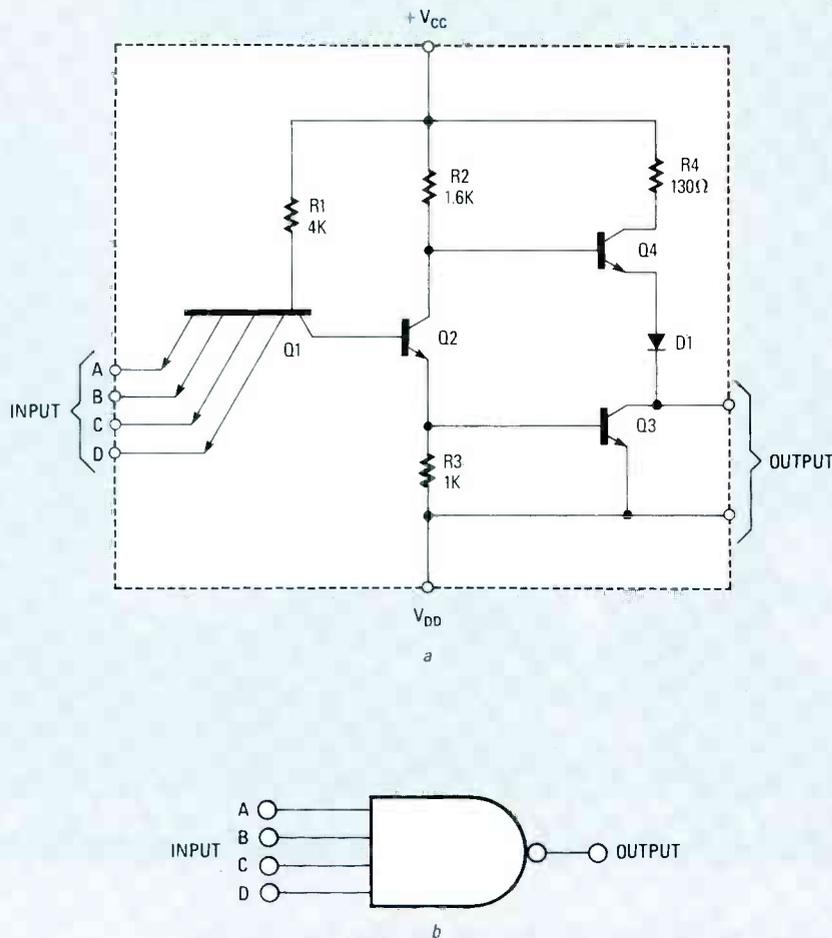


FIG. 1—THE INTERNAL STRUCTURE of a TTL 4-input NAND gate is shown in a. The equivalent logic diagram of a 4-input NAND gate is shown in b.

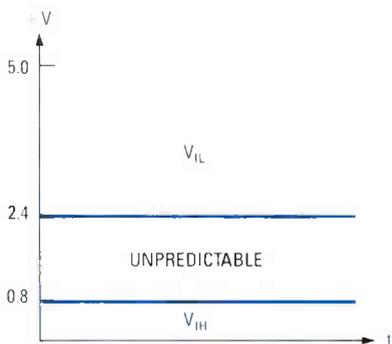


FIG. 2—THE MINIMUM AND MAXIMUM voltage limits of V_{IH} and V_{IL} for TTL negative logic (NAND, NOR). For positive logic (AND, OR) the values are reversed.

switch faster than could be expected from a simple single-transistor driver. With the output in logic 1 state, the output impedance is very low because Q4 appears as an emitter-follower source, driving current into the capacitive load. When in a logic 0 state, Q3 is saturated, resulting in a low shunt impedance to ground that quickly discharges the capacitive load.

Therein lies the problem. Tran-

sistor saturation is a relative state of events, and not a simple on/off toggle of a switch. Real transistors have real resistance, as was explained at the beginning of this series. Because transistor saturation voltage— $V_{CE(sat)}$ —depends on both base and collector currents, Q3 will go out of saturation either by decreasing its base current (I_B) or else by increasing its collector current (I_C).

Consequently, there is a region in which either the base drive current is too small or the collector current too large to sustain the ideal values of V_{CC} and V_{DD} for logic 1 and logic 0, respectively.

Collector current, I_C , is a function of the output load, which is a function of the resistance between Q3's collector and V_{CC} . As the load resistance from V_{CC} to Q3 decreases, collector current increases, which demands a larger base current to sustain saturation.

Base current to Q3, on the other hand, depends on the h_{FE} of Q1 and

V_{CC} . Consequently, limits must be placed on the values of minimum supply voltage (V_{CC}), maximum Q3 collector current (I_{sink}), and maximum Q3-saturation voltage (V_{OL}) before testing of the gate may begin. For reasons that will be discussed later in this installment, TTL-output saturation is defined as 0.4 volt at 16 mA.

The Q1 emitter-input voltage levels at which the output signal at the collector of Q3 switches between logic 0 and logic 1 are referred to as V_{IH} and V_{IL} . V_{IH} is defined as the minimum input voltage required to guarantee a 0-level output, while V_{IL} is the maximum allowed input voltage to guarantee a logic 1 output. See Fig. 2.

Between those two input voltages lies an area that is considered unpredictable. Depending on the transistor's gain and the value of V_{CC} , the output signal may actually come to rest at some voltage midway between logic 0 and logic 1. V_{IH} and V_{IL} are measured to guarantee that it does not happen.

While the following test procedures center around the use of negative logic (the NAND and NOR family of devices), the test parameters are nevertheless valid for all TTL devices. To accommodate positive logic in the described test circuits, such as for AND and OR gates, simply invert the input or output logic voltages to the device (depending on the value to be measured) and proceed accordingly.

Measuring V_{IH}

Before V_{IH} testing can begin, a voltage range must be specified for V_{CC} . Nominal V_{CC} voltage for a TTL device is +5 volts. Fluctuations in power-supply output, however, can

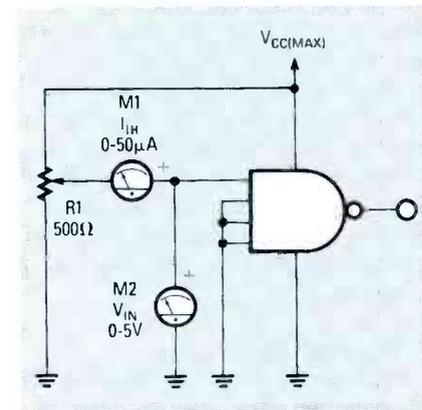


FIG. 3—THE TEST CIRCUIT used for measuring V_{IH} , V_{OL} , and I_{OL} .

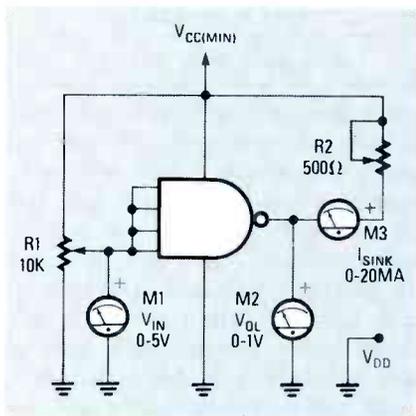


FIG. 4—THE TEST CIRCUIT used for measuring V_{IL} , V_{OH} , and I_{OH} .

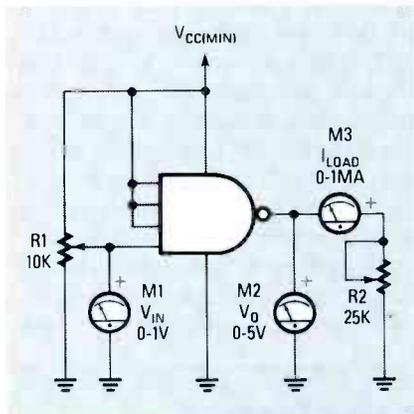


FIG. 5—THIS TEST CIRCUIT is used for measuring I_{IL} .

cause that value to change by as much as 15%. Consequently, a lower limit for V_{CC} must be determined before testing begins.

For 54-series devices, $V_{CC(min)}$ is +4.50 volts; for devices $V_{CC(min)}$ is +4.75 volts. The difference in minimum V_{CC} values between the two families can be explained by the fact that the military part (SN54) must be able to endure more extreme conditions than are normally experienced by commercial equipment.

Now that the test parameters have been defined, V_{IH} can be determined using the test setup shown in Fig. 3. Notice that all four inputs have been tied together and tested as one. That is normal. The test procedure goes as follows.

The value of V_{CC} is first set to the $V_{CC(min)}$ value specified for the device under test. Variable resistor R1 is adjusted so that the input gates (emitters) are essentially connected to V_{CC} . That causes the output to go low (logic 0). Variable resistor R2 is then adjusted so that meter M3 (I_{sink}) measures 16 mA. The test parameters are now set.

V_{IH} is tested by using R1 to decrease the voltage to the input gates while monitoring I_{sink} . As the voltage to the input emitters decrease, V_{OL} increases. When V_{OL} is 0.4 volts, the corresponding V_{in} voltage represents V_{IH} . Typically, V_{IH} is 2.0 volts or greater.

Measuring V_{IL}

V_{IL} is the voltage at which Q3 drops out of saturation and the output signal is at logic. In that state, Q4 is conducting and supplying current to a capacitive or resistive load. Nominal load current is defined as 400 μ A.

The test circuit for V_{IL} is shown in Fig. 4. In that test, only one gate at a time is measured. All unused gate inputs are connected to V_{CC} .

The test begins by adjusting the power supply to $V_{CC(min)}$ for the device under test and adjusting R1 so that meter M1 (V_{in}) shows zero volts. Variable resistor R2 is then adjusted so that meter M3 (I_{load}) is 400 μ A. Potentiometer R1 is then adjusted while monitoring M2 (V_O). As V_{IL} increases, V_O decreases. When V_O reaches a minimum of 2.4 volts with a load current of 400 μ A, the voltage V_{in} is equal to V_{IL} . V_{IL} is typically less than 0.8 volts.

Gate input current

In TTL design, input current is required by the gate emitters before the circuit will function. The maximum input current that flows when the input is at logic 0 is defined as I_{IL} .

Because I_{IL} is a function of V_{CC} , and increases as V_{CC} increases, the worst-case condition exists when the device under test is subjected to $V_{CC(max)}$. Consequently, it is at that voltage that I_{IL} is tested. For the 54 series, $V_{CC(max)}$ is +5.5 volts; for the

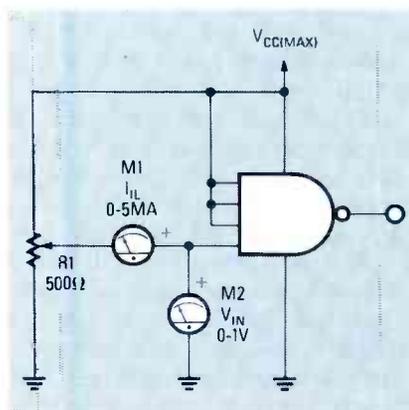


FIG. 6—THIS IS THE TEST CIRCUIT for measuring I_{IH} .

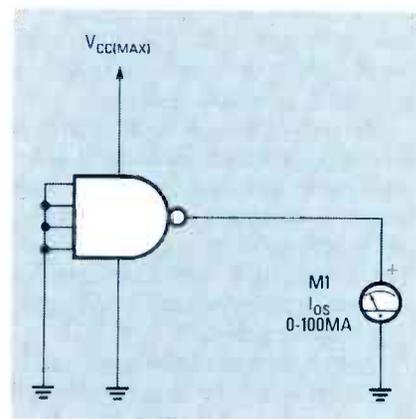


FIG. 7—THE TEST CIRCUIT for measuring I_{OL} .

74 series, $V_{CC(max)}$ is +5.25 volts. Again, the difference in test parameters can be attributed to the more demanding standards imposed by military specifications.

The test setup for I_{IL} is shown in Fig. 5. With the exception of the input under test, all unused inputs are tied to V_{CC} to maximize any contribution the inputs might have on I_{IL} . Should they be grounded instead, one or more of the unused gates could siphon potential leakage current around the input being tested, causing a measurement error. No output loading is required, so the output pin may remain unconnected.

The test is performed by adjusting R1 until meter M2 (V_{in}) indicates 0.4 volt. The current indicated by the series input ammeter, M1, is I_{IH} . Each input is tested and measured separately.

Transistor Q1 (see Fig. 1) is back-biased and a small leakage current flows when the input is logic 1. The input current that flows when the input is at logic 1 is defined as I_{IH} .

The test circuit for I_{IH} is shown in Fig. 6. In that test, the power supply is set to $V_{CC(max)}$, and R1 adjusted until meter M2 (V_{in}) indicates 2.4 volts. The current displayed by series ammeter M1 is I_{IH} . I_{IH} is typically less than 40 μ A.

Gate output parameters

As indicated earlier, transistors Q3 and Q4 (see Fig. 1) form an active pull-up output that provides a low-impedance current source for capacitive output circuits. By brute force, an external load can be made to change logic states faster than RC conditions normally allow.

The brute force, of course, is supplied by current: one for the up swing,

the other for the down swing. The amount of current a TTL gate is capable of sinking or sourcing is defined as I_{OL} and I_{OH} , respectively.

The output voltage is dependent on the output current. Because it is impossible to maintain Q3 in saturation under all conditions, the output voltage is going to vary as the load varies. The values of the output high and low voltages are represented by V_{OH} and V_{OL} , respectively.

Output current and voltage can be measured using the circuits shown in Figs. 3 and 4. All output measurements are made under the worse-case input conditions; that is, the input logic 1s to the gate are adjusted so that they are just within tolerance of TTL specifications for the device under test. In the case of a logic 1 input, the value is 2.4 volts; for a logic 0 input, it is 0.8 volt.

The measurements of I_{OL} and V_{OL} are made using the circuit shown in Fig. 3. Measuring I_{OL} is done by adjusting R1 until meter M1 (V_{in}) indicates 2.4 volts. Variable resistor R2 is then adjusted until meter M2 (V_{OL}) indicates 0.8 volt. Meter M3 (I_{sink}) indicates I_{OL} (16 mA).

V_{OL} is measured by setting R1 for an input of 2.4 volts and adjusting R2 until M3 indicates 16 mA. Meter M2 indicates V_{OL} . Maximum V_{OL} voltage is 0.8 volt.

The measurements of I_{OH} and V_{OH} are done using the circuit shown in Fig. 4. Measuring I_{OH} is done by adjusting R1 until meter M1 (V_{in}) indicates 0.8 volts. Variable resistor R2 is then adjusted until meter M2 (V_O) registers 2.4 volts. Meter M3 (I_{load}) displays the value of I_{OH} . Minimum I_{OH} is 400 μA .

V_{OH} is measured by setting R1 for an input of 0.8 volts and adjusting R2 until M3 indicates 400 μA . The value registered by M2 is equal to V_{OH} . Minimum V_{OH} is 2.4 volts.

Fan out

If you examine the four tests we've gone through, you will notice that a minimum or maximum value is stated for each. The limits are established to guarantee that the output logic levels of a TTL gate are capable of driving 10 other gates.

During the evaluation stage of TTL development, it was determined that the maximum I_{IH} input leakage current of a good TTL gate was never greater than 40 μA ., consequently,

minimum output-current requirements for I_{OH} were set at 400 μA (40 $\mu A \times 10$ gates).

It was further determined that I_{IL} did not exceed 1.6 mA per input. The result of that decision yields a minimum I_{OL} current of 16 mA. The upper and lower limits of V_{OL} and V_{OH} were selected on the basis of noise immunity.

In many instances, the values of I_{OL} , I_{OH} , V_{OL} , and V_{OH} are never actually measured. The gate is simply placed in a test configuration where the operator decides between a go or no-go situation.

Short-circuit output current

A puzzling test parameter that appears on the TTL data sheet is I_{OS} ; meaning, the output current with the output shorted to ground. Essentially, it describes the amount of current the gate is capable of supplying through a short circuit when the output is at logic 1 (high). The test circuit is shown in Fig. 7. In that test, output voltage is not a factor. V_O may assume any value because output current is the measured value.

While the usefulness of the test may seem obscure, its origin is not. Lore (or mythology) has it that during early development of TTL technology at Texas Instruments, an engineering technician accidentally reversed the gate inputs for the outputs during a routine I_{IL} input-current test. Connected to the devices was, obviously, a current meter for monitoring what was supposed to be input current I_{IL} . Instead, the meter indicated short-circuit output current.

The error became apparent when a government inspector questioned the wide variations in the recorded I_{IL} readings.

To save face, the technician calmly stated that the test was done intentionally to reveal the true nature of the device's durability under the most adverse of all conditions. The inspector bought the story, and mandated all government devices be subjected to the same test. To this date I_{OS} appears on all TTL data sheets.

And on that note, we will take our leave till next time, when we will continue our examination of integrated digital components as we review the test techniques for Low-power Schottky (LS) and Complementary Metal Oxide Semiconductor (CMOS) digital devices. R-E

HDTV UPDATE

continued from page 17

spent about \$45 million over the last decade developing ACTV and expects that another \$30 million is needed to complete development. Because everyone involved in the TV industry has so much to gain from a successful, compatible HDTV system, we would expect them to quickly adopt the new system, and to work on solving any of the problems that arise.

Despite the promise of the new system, it's important to realize that no broadcast field tests of ACTV have taken place. However, ACTV signals have been computer-simulated at Sarnoff's Digital Video Facility and stored on videotape. The system was demonstrated publically for the first time at the HDTV Colloquium in Ottawa in early October, and we hope to have a first-hand report and more technical details of the new system in the near future. If the system lives up to its promise, perhaps compatible 3-D TV isn't too far behind! R-E

COMING NEXT MONTH

BUILD REACTS THE ^{Radio}Electronics ADVANCED CONTROL SYSTEM



PC SERVICE

One of the most difficult tasks in building any construction project featured in **Radio-Electronics** is making the PC board using just the foil pattern provided with the article. Well, we're doing something about it.

We've moved all the foil patterns to this new section where they're printed by themselves, full sized, with nothing on the back side of the page. What that means for you is that the printed page can be used directly to produce PC boards!

Note: The patterns provided can be used directly only for *direct positive photoresist methods*.

In order to produce a board directly from the magazine page, remove the page and carefully inspect it under a strong light and/or on a light table. Look for breaks in the traces, bridges between traces, and in

general, all the kinds of things you look for in the final etched board. You can clean up the published artwork the same way you clean up your own artwork. Drafting tape and graphic aids can fix incomplete traces and doughnuts, and you can use a hobby knife to get rid of bridges and dirt.


An optional step, once you're satisfied that the artwork is clean, is to take a little bit of mineral oil and carefully wipe it across the back of the artwork. That helps make the paper translucent. Don't get any on the front side of the paper (the side with the pattern) because you'll contaminate the sensitized surface of the copper blank. After the oil has "dried" a bit—patting with a paper towel will help speed up the process—place the pattern front side down on the sensitized copper blank, and make the exposure. You'll

probably have to use a longer exposure time than you are used to.

We can't tell you exactly how long an exposure time you will need as it depends on many factors but, as a starting point, figure that there's a 50 percent increase in exposure time over lithographic film. But you'll have to experiment to find the best method for you. And once you find it, stick with it.

Finally, we would like to hear how you make out using our method. Write and tell us of your successes, and failures, and what techniques work best for you. Address your letters to:

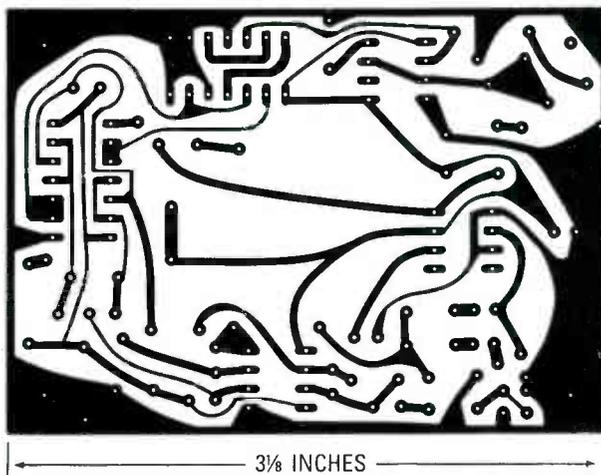
Radio-Electronics
Department PCB
500-B Bi-County Blvd.
Farmingdale, NY 11735




THE AUDIO SCRAMBLER lets you communicate in privacy. The circuit is built on this PC board. The story begins on page 51.

PC SERVICE


PC SERVICE

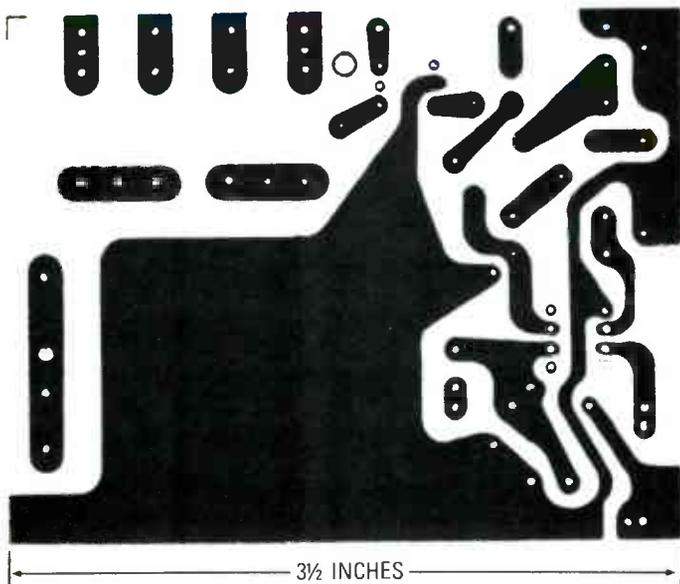

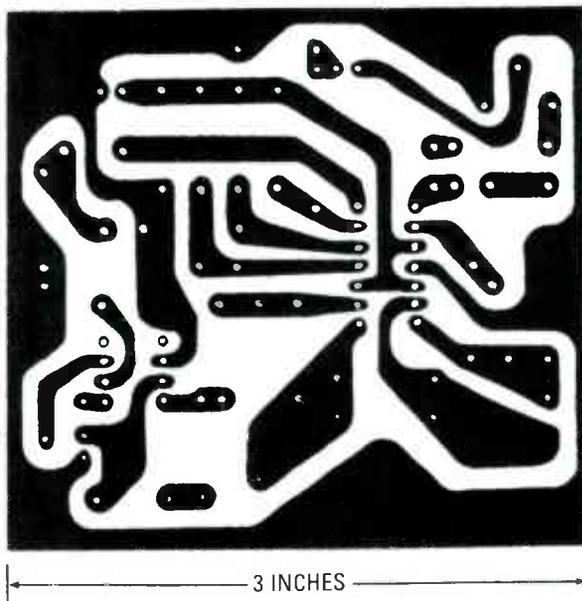
THE FOUR BOARDS on this page are used to build the Uninterruptible Power Supply. The board shown here is the power-supply board.



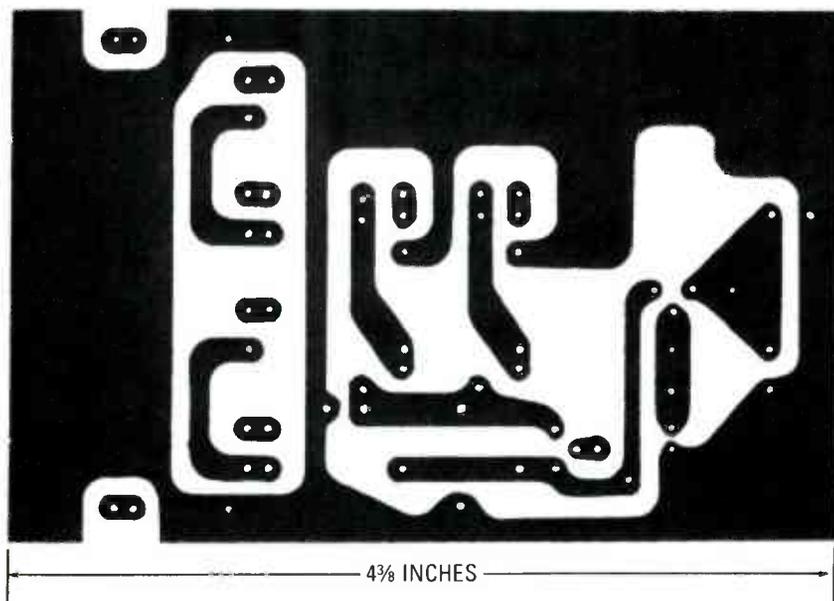USE THIS BOARD to build the sine-wave generator circuit.



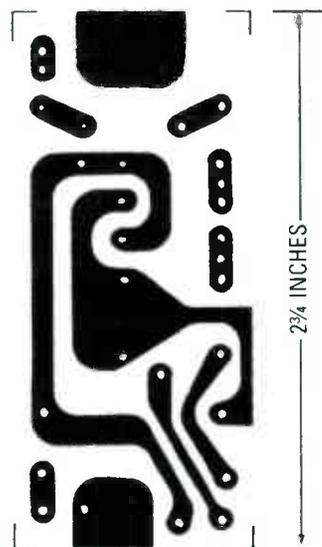BUILD THE AMPLIFIER for the UPS on this board.



THE METER CIRCUIT can be built on this simple board.

PC SERVICE

HARDWARE HACKER

Welcome to a new column

WELCOME TO A NEW RADIO-ELECTRONICS feature column. I'll be doing what I can here to find needed resources, answers, and opportunities for all you readers. While we will center mostly on traditional stand-alone electronics, just about anything at all in the "neat stuff" category can and will come up.

You will find an end box listing a new and no-charge help line that you can call most weekdays 8-5 mountain standard time to talk to the guru himself. A new resource file will also appear at the end of each column, containing all the names and numbers that are very hard to pin down otherwise.

And, from time to time, we will have a contest or two to close the loop and get you involved. Some of them will be technical and some not. The usual prizes will be a book of mine or an all-expense-paid *tinaja* quest (FOB Thatcher, AZ), with occasional extra cash for an outstanding entry. One hint: your odds of winning one of those are very good!

Let's just jump right in...

What's new in automotive electronics?

There's an outfit called the SAE who used to be known as the *Society for Automotive Engineers* that have a very wide variety of books, technical articles, and other publications on most anything vehicular.

While some of their stuff is rather pricey, there's lots of goodies in the \$10 to \$30 range. For a complete listing, ask for their current *Publications Catalog*.

Some of the more interesting titles include *Commercial Vehicle Electronics*, *Some Unusual Engines*, *Automobile Audio Systems*, *Recycling of Automotive Catalysts*, *Understanding Automotive Electronics*, *Sensors*, *Audio Systems: Speakers and Receivers*, and *A History of the Internal Combustion Engine*.

They have hundreds more, so be sure and check them out.

Tell me about EEPOT's.

Suppose you took a 100-position selector switch and 99 resistors of, say, 1000 ohms each. You could connect them up to make a 100-position volume control, as was done in older broadcast-quality audio attenuators. Now, what would really be nice is finding some way to *remote-control* the switch setting. That way, you or a computer could change the switch position at will.

The switch would be able to "remember" its correct setting and would still be correct the next time that you applied power.

Well, the folks at *Xicor* have done you one better. They have come up with an 8-pin mini-dip beastie called an *EEPOT* that can be used as a remotely controlled vol-

A digital potentiometer
Automotive electronics
Accessing trade journals
New technical literature
The Santa Claus machine

DON LANCASTER

ume control. You can also think of it as an unusual digital-to-analog converter or else as a multiplier that can multiply a digital and an analog value together.

Three of the available devices include the X9103 (10K), the X9503 (50K), and the X9104 (100K). *Xicor* has been known to send out free samples on letterhead requests; otherwise, they cost under \$5.

Figure 1 shows you a block diagram of an EEPOT. A pair of leads are used for the +5-volt DC supply and ground. Three leads are used for the two ends and the wiper of the equivalent potentiometer. Finally, three leads, named *CHIP SELECT*, *UP/DOWN*, and *INCREMENT* are used for the digital control.

The position in the resistor string is selected by one of 100 internal field-effect transistors connected as data selectors. The present position is remembered by a seven bit, modulo-100 counter. When the chip is selected, you can raise or lower the position one count at a time, through use of the *UP/DOWN* and *INCREMENT* inputs.

To initially set your volume-control position, you bring the *CHIP SELECT* low. If you want a "louder" output, you make the *UP/DOWN* input high and then pulse the *INCREMENT* line by bringing it low and then back high again exactly once. Repeat for each step as needed.

Now for the neat part. The internal position counter is "backed up" by seven non-volatile memory cells. When you deselect by making the *CHIP SELECT* high, the memory cells "remember" the counter position for you, even after supply

NEED HELP?

Phone or write your **Hardware Hacker** questions directly to:

Don Lancaster
Synergetics
Box 809
Thatcher, Az 85552
(602) 428-4073

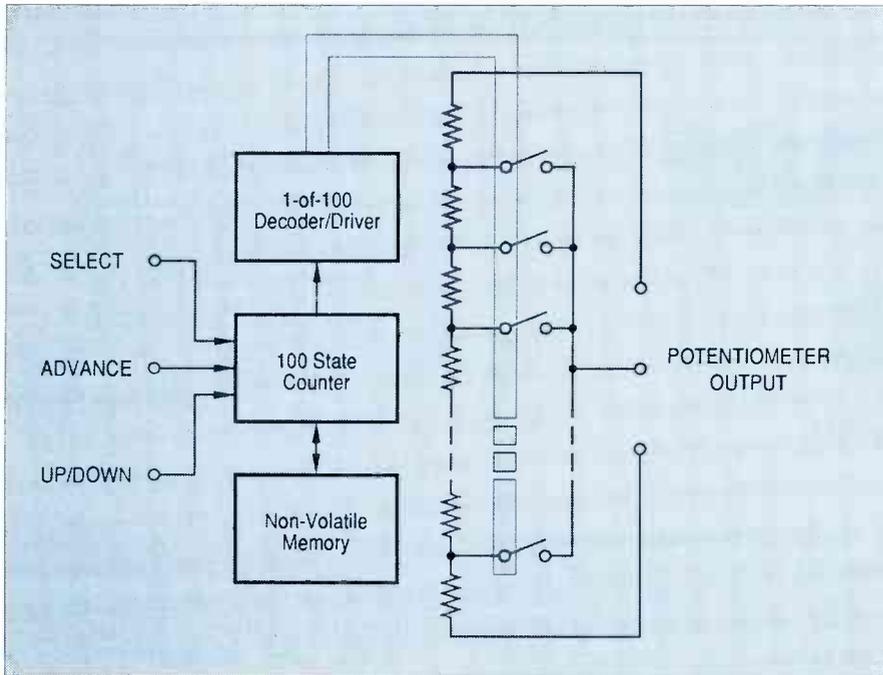


FIG. 1—AN EEPOT CAN SIMULATE an ordinary potentiometer and can be remotely controlled, either manually or by a computer. The wiper position is remembered during any power-down times by an internal non-volatile memory.

power is disconnected. Thus, if you use the beastie to remotely set the volume on your stereo, you will have the same volume setting the next time you apply power.

There are a few "gotchas," though. While a hundred positions are more than enough for most audio uses, it just plain isn't nearly enough resolution for such neat things as remotely setting a floppy-disk drive's speed. While the output distortion is quite low, you are limited to a maximum of + or - 5 volts of analog input signal. And you should not try to source or sink more than half a milliamperes of output current.

There's one very important use rule: *You absolutely must not disconnect the supply power while the chip is selected.* As is typical with most non-volatile memories, powering down while active can lead to incorrect memory values being stored.

You also have to keep the chip's power applied when you are actually using the output. Thus, while we do have a low-power device, it is not suitable for truly micro-power uses.

Figure 2 shows you the pinouts, while Fig. 3 shows you a "bouncelless" pushbutton that will let you experiment with the INCREMENT input on your EEPOT without anything fancy in the way of computers or test gear.

A bounceless switch is also shown for the CHIP-SELECT input. Note that debouncing is abso-

lutely essential for those two inputs when you are working with mechanical contacts.

The UP/DOWN input does not need any mechanical contact debouncing, provided that you wait a few milliseconds each time you change it.

In the real world, you are more likely to use the "already clean" and parallel outputs of a personal computer port or the output commands from a remote controller integrated circuit to drive your EEPOT. In those cases, any extra debouncing circuits are not at all needed.

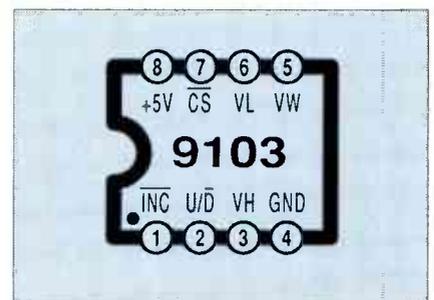


FIG. 2—EEPOT PINOUTS. VL, VW, and VH are the terminals of the output potentiometer. The chip select CS is brought low to change position, but is left at +5 otherwise. Position is changed by bringing INC low and then high again, with direction set by up/down pin u/d. A high u/d advances the position.

Now, I could sit here and tell you all the marvelous things you can do with a volume control whose setting is remotely and digitally controllable and then later remembered during power down times. Things like variable-gain amplifiers, electronic multipliers, self-calibrating instruments, and stuff like that.

Instead, we'll use the EEPOT for our first contest. Just dream up a good use or two for that IC. Be sure to send your entries directly to me via the address in the box, and *not* to the Radio-Electronics editorial offices.

What are trade journals?

Trade journals are far and away the most important resource available to any hardware hacker, yet I still get countless helpline calls from people who have never even heard of them.

Just about any technical field has its own set of special-interest magazines that are intended strictly for "insiders". Those magazines

**NEW FROM
DON LANCASTER**

HANDS-ON BOOKS

Ask the Guru Reprints	24.50
CMOS Cookbook	15.50
TTL Cookbook	15.50
TV Typewriter Cookbook	15.50
Active Filter Cookbook	15.50
Micro Cookbook vol I or II	15.50
Enhancing your Apple vol I	15.50
Enhancing your Apple vol II	15.50
Applewriter Cookbook	19.50
Apple Assembly Cookbook	21.50
Incredible Secret Money Machine	7.50
Postscript Ref. Man. (Adobe)	22.50
Postscript Cookbook (Adobe)	16.50

UNLOCKED SOFTWARE

Absolute Reset IIe & IIc	19.50
Applewriter/Laserwriter Utilities	49.50
Postscript Show & Tell (IIe/Mac/PC)	39.50
Postscript Technical Illustrations	39.50
Intro to Postscript VHS Video	39.50
Apple Ram Card Disassembly Script	24.50
Enhance vol I Companion Disk	19.50
Enhance vol II Companion Disk	19.50
Assembly CB Companion Disk	19.50
Applewriter CB ProDOS C. Disk	24.50

FREE VOICE HELPLINE VISA/MC

SYNERGETICS
Box 809-RE
Thatcher, AZ 85552
(602) 428-4073

Our guaranteed savings plan.



Fluke 70 Series Analog/Digital multi-meters are like money in the bank. Buy one, and you're guaranteed to save both time and money.

Money, because you get longer battery life and longer warranty coverage — 3 years vs. 1 year or less on others.

And time, because 70 Series meters are easier to operate and have more automatic measurement features.

So before buying any meter, look beyond the sticker price. And take a closer look at the new low-priced \$79 Fluke 73, the \$109 Fluke 75, and the deluxe \$145 Fluke 77. In the long run, they'll cost less, and give higher performance, too.

And that, you can bank on.

For a free brochure, and your nearest distributor, call toll-free **1-800-227-3800, ext. 229.**

FROM THE WORLD LEADER
IN DIGITAL MULTIMETERS.

FLUKE

© 1985 Fluke

CIRCLE 121 ON FREE INFORMATION CARD

JANUARY 1988

73

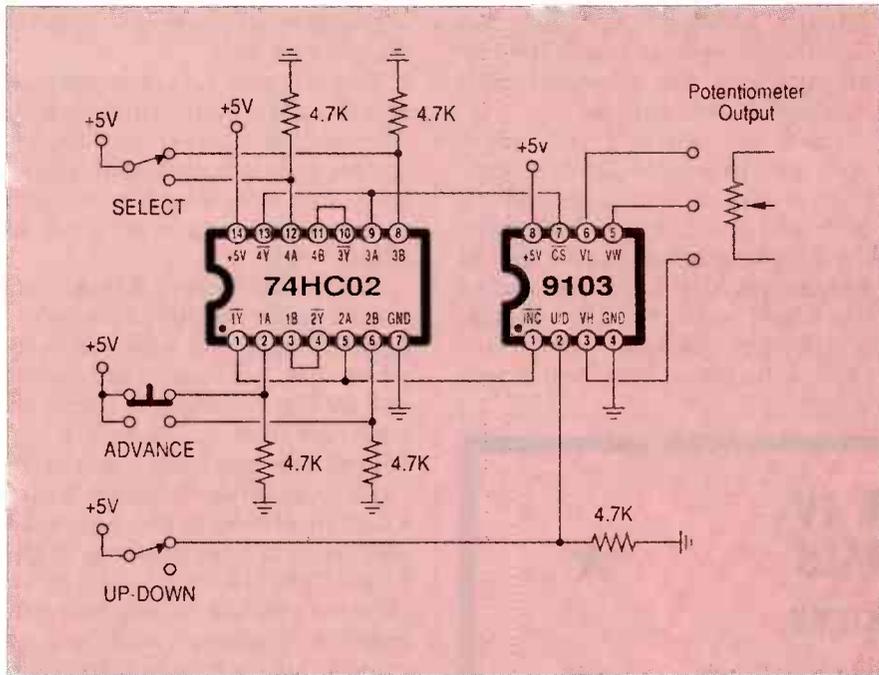


FIG. 3—USE THIS CIRCUIT to test your EEPOT. The debouncing shown is only needed when you are using mechanical contacts.

are often free, but are rarely advertised; they're never seen on newsstands. Inside a trade journal, you will find ads for the latest and the best, technical and survey articles, year-end directories, bingo cards, and various assorted freebies.

There are many thousands of different trade journals being published today. Some important electronic examples include *EDN*, *Electronic Design*, *E. E. Times*, *Electronic News*, *Powerconversion* and *Electronics*. A few of the great journals on robotics include *Machine Design*, *Design News*, and *Motion* magazines.

To emphasize the wide variety of stuff that is available, some other trade journals that I have found personally useful include *Signcraft*, *Textile World*, *Printing Impressions*, *Technical Photography*, *Computer Reselling*, *Electronic Publishing*, and *Fire Engineering*.

So how can you tap those resources that are absolutely essential for serious hacking? First, go to your local library and check into a most useful reference book called *Uhfricts Periodicals Dictionary*. That, and the similar *International Standard Periodicals Dictionary*, will give you a fairly complete list of what is available from whom.

If you already have your own business letterhead (an *absolute*

must for serious hacking, and utterly trivial to do in these days of laser printers), the next step is to write or call the various journals and ask for a reader-qualification card. Chances are you can qualify for a free subscription.

If not, check any large technical library, or see if an engineer at a larger electronics outfit can cop you older issues, or else use the *interlibrary loan service* available at any branch library.

But do not ignore the trade journals. They represent your most valuable resources for serious hardware hacking.

Is there really a Santa-Claus Machine?

Yes, Virginia, there really is a Santa-Claus machine. It exists here and now, and represents enough new hacking opportunities to last you a lifetime.

Most science-fiction authors, including Hugo Gernsback, at one time or another introduced a Santa-Claus machine. This was either a mass teleportation device or an elemental atom smasher and rearranger. All you would have to do is feed it the right set of plans, and out would pop a sports car, an oscilloscope, a roast-beef dinner, or, for that matter, a brand new girlfriend.

As many copies as you like,

even. Might as well print us up some \$20 bills while we're at it.

Believe it or not, such a Santa-Claus machine exists today, albeit a very expensive one with very limited capabilities. While you can't yet duplicate the exact function of any object, you can in fact duplicate its exact form, and do so anywhere in the world, given the right set of plans.

The idea is both very simple and astoundingly profound. You take either a tray (2-D) or a tank (3-D)

full of an ultraviolet-curing plastic called a *photopolymer* liquid resin. This resin is related to the UV-curing resins already widely used by dentists and printers.

Then you create a very small spot of ultraviolet light, either from a laser or from a special UV bulb and some optics. You move the light spot around as needed to *harden* any desired object out of the liquid resin. For 3-D objects, you place an "elevator" on the surface of the liquid and then slowly

lower the elevator so that layers are applied as needed to build up the final object.

You can easily machine the un-machinable with this device. Things like perfect and hollow spheres, blind undercut square holes, or very complex turbine blades with compound curves are utterly trivial.

While the current Santa-Claus machines are limited to a very few plastics, once you have made the prototype, you can easily make any molds, pantagraph copies, or whatever from it, ultimately converting into most any material.

You can also think of Santa-Claus machines as the next giant step beyond laser printing. With a Santa-Claus machine, you could create a replica of any three-dimensional object, while today's printers are pretty much limited to two-dimensional images using very limiting ink or toner.

Think of it. A \$500 box beside your personal computer that can create a 3-D model replica of *any* object.

So what does all that have to do with you? Just this: Here is an incredible new opportunity in a brand new field that you can experiment with in a home lab or even on a kitchen table.

The leader in the new field seems to be an outfit called *3-D Systems*, while I think that one source of the UV-curing photopolymeric resins is *Mobay Chemical*. Their current machines sell for \$70,000 and \$125,000. Those prices, of course, are dirt cheap "must-have" bargains to the automotive people and other large manufacturers who can now make their molds and prototypes in 36 minutes instead of 36 weeks. That is an offer they cannot refuse.

What can we do on a hacker's budget? I don't see any reason why a limited-performance Santa-Claus machine cannot be built up for well under \$300.

Figure 4 shows how I would go about it. First, I would initially stick with two-dimensional objects such as letters, nameplates, bezels, or whatever. That third dimension just adds complications at a time when getting the basic process working any way at all should be your foremost goal.



CABLE TV SPECIALS CONVERTERS



JRX-3 DIC—36 Channel Corded Remote . . . \$139.⁹⁵
 JSX-3 DIC—36 Channel Set Top \$129.⁹⁵
 SB-3 — 'The Real Thing' \$109.⁹⁵
 SB-M-Refurbished \$89.⁹⁵
 DRZ-3D1C—68 Channel Wireless
 with Decoder \$199.⁹⁵

ZENITH: Z-TAC Cable Add-On \$199.⁰⁰

VIEW STAR: EVSC-2010—60 Channel Wireless—
 with Parental Lockout \$ 99.⁰⁰

EVSC-2010 A-B—Same as above with
 A-B Switch \$109.⁰⁰

View Star 2501—60 Channel Wireless
 with Volume \$119.⁰⁰

Unika MR-702—72 Channel Wireless
 with Parental Lockout \$89.⁹⁵

MISCELLANEOUS

OAK: N-12 Mini-Code \$ 89.⁰⁰
 N-12 Mini-Code Vari-Sync \$99.⁹⁵
 N-12 Mini-Code Vari-Sync Plus Auto On-Off . . \$159.⁹⁵

JERROLD: 400 & 450 Handheld Transmitters \$ 29.⁰⁰

HAMLIN: MLD-1200 \$ 99.⁰⁰

NEW ITEMS: Ripco Tape Copy Stabilizer \$109.⁹⁵

Scientific Atlanta SA-3 \$129.⁹⁵

GENERAL INSTRUMENTS: VCU Amplified Video Switch
 Signal Amplifier \$59.⁹⁵

ALL UNITS GUARANTEED. QUANTITY PRICES AVAILABLE.

UNITED ELECTRONIC SUPPLY

P.O. BOX 1206 • ELGIN, ILLINOIS 60121 • 312-697-0600

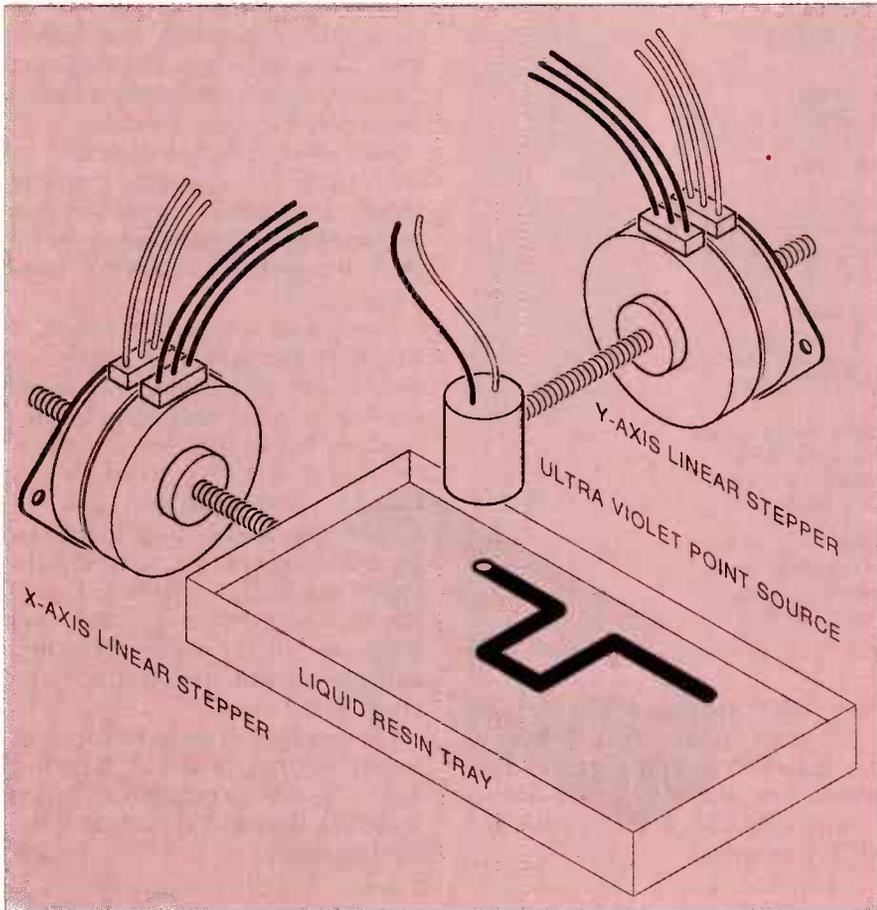


FIG. 4—TWO-DIMENSIONAL SANTA-CLAUS MACHINE can create a replica of virtually any flat object through the selective ultraviolet hardening of a liquid plastic resin.

Second, I would flush the laser and the beam scanning stuff, replacing the laser with a scientific ultraviolet lamp from EG&G or whoever, and replacing the beam scanning with two linear steppers such as the *Hurst* type SLS.

And, third, I would not worry about complexity or speed. If it takes a week to machine a simple part, so what? Particularly if you are now three orders of magnitude cheaper than your competition.

There are some very important safety considerations in all that. The resins must be used in a very well ventilated area, and you should avoid breathing any and all fumes. Touching or handling the uncured resin is also probably a very bad idea.

Even worse, intense ultraviolet light can easily cause blindness. That's why all those elaborate interlocks are present on EPROM erasers. Your Santa-Claus machine should be totally enclosed with opaque shields. Experiments on focusing or whatever should be done on a trial and error basis only.

Do **not**, under any circumstances **ever** look at the ultraviolet spot! I would also suggest wearing heavy sunglasses as an additional precaution against an inadvertent powering of the lamp with your shields down.

Needless to say, the editors here at **Radio-Electronics** will pay very well for construction details on the first Santa-Claus machine that can make non-trivial replica models on a hacker's budget.

What's new in the technical literature?


This seems to be a very good month for technical data books. Data books usually contain very detailed specifications on electronic devices, often with accompanying application notes and use hints. The price of a data book varies from free to optional to nominal, depending on the manufacturer, who you are, and how you ask for the book. Once again, you get the best results with your own laser-printed business letterhead.

Data books are a resource sec-

CRYSTEK

The pulse of dependable communications

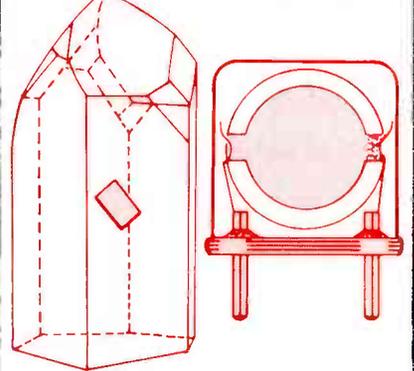Reliability & Quality
From Start To Finished Product



QUARTZ
CRYSTALS/OSCILLATORS
FOR
ELECTRONIC — INDUSTRIAL


- Micro-Processor Control
- Computers/Modems
- Test/Measurement
- Medical

COMMUNICATIONS—REPLACEMENT

- Mobile/2-way/Channel Elements
 - Pagers
 - Marine
 - Aircraft
 - Telemetry
 - Monitors/Scanners
- AMATEURS**

- CB
- Hobbist
- Experimenter

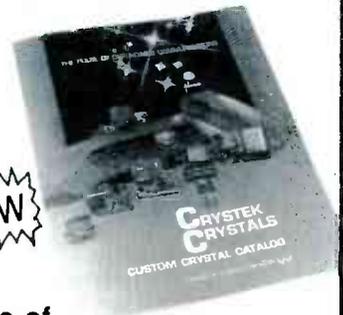- COST EFFECTIVE
- MODERATE PRICING
- FAST DELIVERY



NEW

The Pulse of Dependable Communications.

Crystek Crystals offers their new 16 page **FREE** catalog of crystals and oscillators. Offering state-of-the-art crystal components manufactured by the latest automated technology. Custom designed or "off the shelf," Crystek meets the need, worldwide. *Write or call today!*

CRYSTEK CRYSTALS

2351/2371 Crystal Dr. • Ft. Myers, FL 33907
P.O. Box 06135 • Ft. Myers, FL 33906-6135

TOLL FREE 1-800-237-3061

(813) 936-2109 • TWX 510-951-7448

CIRCLE 191 ON FREE INFORMATION CARD

NAMES AND NUMBERS

AMD
901 Thompson Pl.
Sunnyvale, CA 94088
(800) 538-8450

EG&G
35 Congress St.
Salem, MA 01979
(818) 967-9521

Hewlett-Packard
PO Box 10301
Palo Alto, CA 94303
(408) 988-7000

Hurst Manufacturing
Box 326
Princeton, IN 47670
(812) 385-2564

Mobay Chemical
Mobay Road
Pittsburgh, PA 15205
(412) 777-2000

Motorola
PO Box 20912
Phoenix, AZ 85036
(602) 244-6900

SAE
400 Commonwealth Dr.
Warrendale, PA 15096
(415) 776-4970

Sprague
115 NE Cutoff
Worcester, MA 01606
(617) 853-5000

Texas Instruments
PO Box 225012
Dallas, TX 75265
(214) 995-2011

Xicor
851 Buckeye Court
Milpitas, CA 95035
(408) 946-6920

and only to trade journals in their usefulness to all you hardware hackers. The best rule is—collect them all!

At any rate, there are some real winners this month. Start with the

Texas Instruments Interface Circuits data book, plus the new *Sprague Integrated Circuits* data book, and the *Advanced Micro Devices* data book on Bipolar and MOS memories.

Hewlett-Packard has a pair of new publications out, one called their *Microwave and RF Designers Catalog*, and the other their *Opto-Electronic Designer's catalog*.

And Motorola has checked in with their *Telecommunications Device Data Book*, containing lots of hard-to-find information on all their integrated circuits for telephone use.

Turning to my own products, I do stock autographed copies of most of my own books as a special service to you **Radio-Electronics** readers. For insider secrets on integrated circuits, there's my *CMOS Cookbook* and my *TTL Cookbook*. For the real lowdown on microprocessors, you should check out my pair of *Micro Cookbooks*, Volumes I and II. You may write or call for a complete list, along with some hard-to-find "free stuff" info.

Do feel free to write or call over anything that is worth hacking over. This is your column and your feedback is essential to make it the best possible. **R-E**

MOVIE TIME



V-7200 or V-7500

CABLE CONVERTERS

72 Channel Wireless Remote Cable Converter

Remote Fine Tuning . . . Fine Tune Centering . . . Last Channel Recall
Favorite Channel Memory . . . HRC/Standard Switch . . . 2/3 Switchable
90 Minute Sleep Timer . . . Switchable AC Outlet . . . 12 Mo. Warranty
Compatible with all CABLE DECORDERS **ONLY \$79.95**

For the same unit with **Volume Control** and **Audio/Video Outputs** -
Order V-7500 **\$109.95**

V-430 Video Control Center wireless Remote Switcher, with 4 Inputs and 3 Outputs **\$79.95**

MOVIETIME, V-7800

78 Channel Remote Converter (same features as the V-7200) + Parental Control and built in 10 DB Amplifier. 24 Mo. Warranty **\$89.95**

Replacement Hand Units for the JERROLD 400 or 450 **\$24.95**

Shipping Charge \$5.50 per order. We accept AMERICAN EXPRESS, COD or Personal Checks. Checks must clear prior to shipping.

Dealer Inquiries Welcome
Call 1-305-652-3971

MOVIETIME

1-305-652-1981 20203 NE 15 Ct.
1-800-843-9845 Miami, FL 33179

30 DAY MONEY BACK GUARANTEE

CIRCLE 192 ON FREE INFORMATION CARD

**Technicians,
Get Serious
About Your
Profession**



Being a certified electronics technician lets people know that you are a professional in your field. It tells them that you are serious about your work and can perform up to CET standards.

Now you can order the "Study Guide for the Associate-Level CET Test" from the International Society of Certified Electronics Technicians. It includes material covering the most often missed questions on the Associate CET exam. 8 1/2" x 11", paperback, 60 pages.

For More Information Contact:

IS CET, 2708 W. Berry, Fort Worth, TX 76109; (817) 921-9101

NAME _____
ADDRESS _____
CITY _____ STATE _____
ZIP _____
_____ copies @ \$5 (+ \$1 postage.)
_____ send material about IS CET and becoming certified.

60-Hz TIMEBASE

continued from page 56

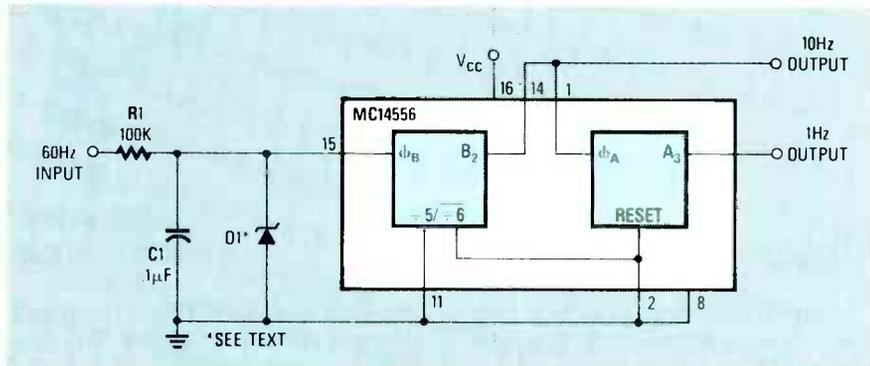


FIG. 3—THIS CONFIGURATION will deliver 1- and 10-Hz signals from either 50- or 60-Hz line frequencies. Note that the outputs do not have 50% duty cycles.

\bar{T} input tied to the power supply, a falling edge at the \bar{T} input will trigger an output pulse. See Fig. 4-a. On the other hand, if the \bar{T} input is tied to ground, a rising edge will generate a pulse. See Fig. 4-b. The output pulse width is short, fixed, and somewhat dependent on the supply voltage.

If desired, any of the counter outputs can be routed to the monostable to get a pulse output with the same frequency and a duty cycle of less

than 1%. With the dual RC network shown in Fig. 5, the monostable becomes a dual-edge detector or frequency doubler, generating a pulse on each incoming edge, thus synthesizing an output frequency that's twice the input. That doubled frequency (with a sub-1% duty cycle) can be used directly or used to clock the sec-

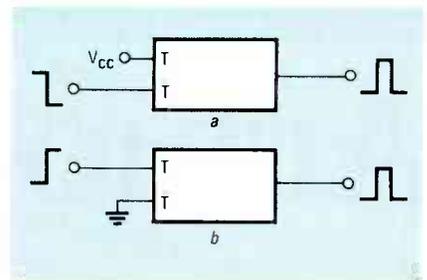


FIG. 4—THE MONOSTABLE can be configured to respond to either a rising or falling edge.

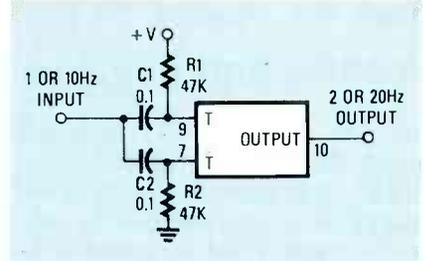


FIG. 5—USING A DUAL RC network, the monostable becomes a frequency doubler with an output duty cycle of less than 1%.

ond counter. Note that any unused inputs must be tied to ground.

Finally, pin 11 ($-5/\bar{6}$) allows use with 60- or 50-Hz line frequencies. Ground the pin for 60-Hz operation; tie it high for 50-Hz. **R-E**

AUDIO SCRAMBLER

continued from page 55

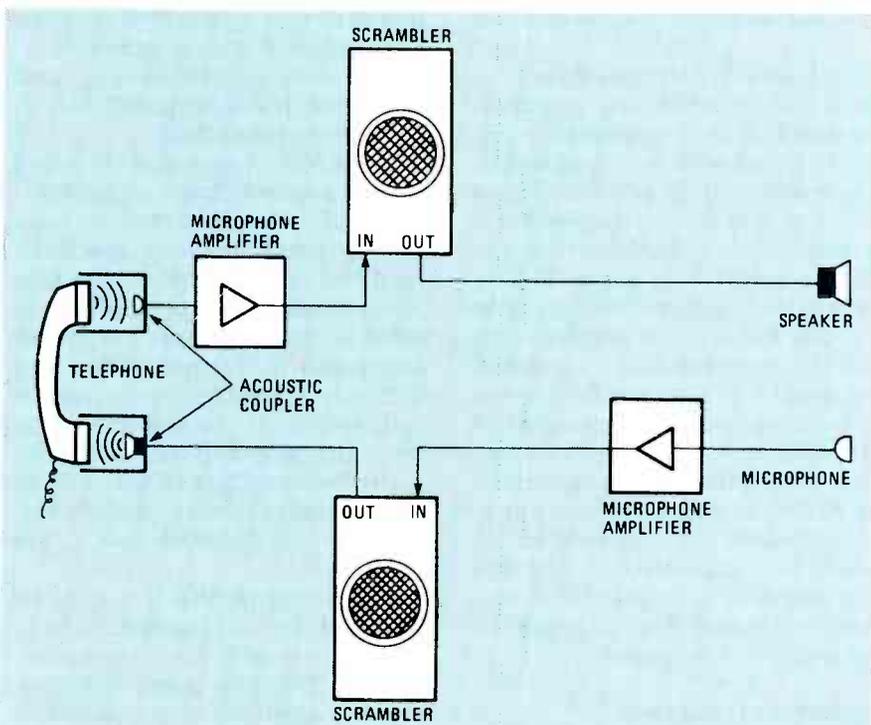


FIG. 8—TWO SEPARATE UNITS are needed in order to provide full-duplex telephone scrambling/descrambling.

scrambled tapes, or between a tape recorder and its output to decode them.

The device can also be used to

scramble and descramble two-way telephone conversations. For instance, a single scrambler/descrambler unit can be used in a half-duplex mode, which means only one person can speak at a time because the unit must be switched between connections. A mechanical TX/RX switch can be used to do the switching. A much better approach is a full-duplex set-up. Figure 9 shows how two scrambler/descrambler units are connected for full-duplex, meaning that no switching is necessary. (The conventional telephone is full-duplex.) Other than merely eliminating the RX/TX PUSH-TO-TALK switch needed in the half-duplex configuration, the full-duplex application offers a more secure environment. A would-be eavesdropper would have to descramble both sides of the conversation, a difficult task because each transmitting scrambler unit would, of course, be tuned to a slightly different frequency by the users.

The device can also be used to provide computer data transmission security. For that you can connect the full-duplex configuration to a 300-baud computer modem. **R-E**

AUDIO UPDATE

Positive and negative feedback

NEGATIVE FEEDBACK WAS INVENTED about 50 years ago by Harold S. Black of Bell Laboratories. Because Black's technique seemed to contradict many of the accepted technical concepts of the day, it took almost 10 years for a patent to be granted for his work. However, his work drew international applause once the electronics community realized what Black had accomplished, and for the next 20 years or so hundreds of articles were published in popular and professional engineering journals exploring and extending the ramifications of feedback technology. For example, the servomechanisms of today's sophisticated robotic devices owe much to Black's invention of feedback control circuitry.

Negative feedback is a technique that taps off a portion (sample) of a signal and reintroduces it—180° out of phase—to a point earlier in the circuit. Negative Feedback—usually identified as NF—can be applied from the output to the input of a single stage, or the NF loop can include everything between an amplifier's speaker output and its input-signal jack. A few speaker manufacturers have even extended the amplifier's NF loop to include the speaker itself, usually using some kind of motion-sensing transducer on the speaker's voice coil or cone to supply the feedback signal.

How feedback works

The basic purpose of negative feedback in amplifiers is to reduce nonlinearities. Feedback can correct both individual waveform aberrations (distortions) and frequency-response fluctuations.

To illustrate frequency-response correction, let's assume that we add 20 dB of NF to an amplifier using the R1 path shown in Fig. 1. That means that the amplifier's overall gain is reduced by 20 dB, except—and here's the key to NF—in those areas where frequency-response loss, waveform distortion, or other aberrations have occurred. If, for example, there's an unwanted 6-dB-per-octave drop above 10 kHz in the amplifier's frequency response, the feedback

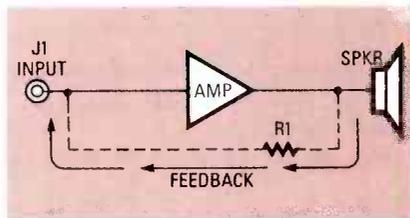


FIG. 1

signal would naturally have the same roll-off. When the rolled-off feedback signal is combined in opposite phase with the input signal, the result is 20 dB of cancellation below 10 kHz (where the feedback is fully in force), that lessens at a 6-dB-per-octave rate above 10 kHz (where the feedback itself starts to roll off). Or to put it another way, the negative feedback modifies the input signal to produce a rise of 6-dB-per-octave starting at 10 kHz relative to the lower frequencies, which have been depressed by 20 dB. In effect, feedback precompensates the input signal for losses (or peaks) that occur later in the amplifier's circuit. If everything works out, the end result is a flat frequency response.

Distortion reduction

The distortion-canceling action of feedback is illustrated in Fig. 2



LARRY KLEIN,
AUDIO EDITOR

(exaggerated for clarity). The input signal is shown in Fig. 2-a. The distorted waveform (Fig. 2-b) is fed back from the output of the amplifier and combined out of phase (Fig. 2-c) with the input waveform (Fig. 2-a). That results in a signal (d) whose distortion "precompensates" for the distortion of the amplifier.

However, if the magnitude of the distortion—or the frequency-response irregularity—exceeds the amount of the feedback available to compensate for it, the amplifier is said to have "run out of feedback," a condition that can cause oscillation, instability, and other unhappy audible effects when clipping occurs. For that reason, it is good engineering practice to design for the best possible performance under "open-loop" (no feedback) conditions, and then apply feedback judiciously as a touch-up procedure.

Is the loss of gain that is caused by negative feedback a problem? Not really—for this reason: Suppose an amplifier before feedback could be driven to full output by a .025-volt input signal. Applying 20 dB of feedback reduces the gain to one-tenth its former value, and 0.25 volt is now required to realize full output. If the feedback has been properly applied, distortion is also reduced by a factor of 10, all at the small expense (these days) of adding 20 dB more gain to the circuit.

Incidentally, the benefits of feedback are not confined just to distortion and frequency response. Properly used, feedback also has a salutary effect on an amplifier's noise and on damping-factor specifications.

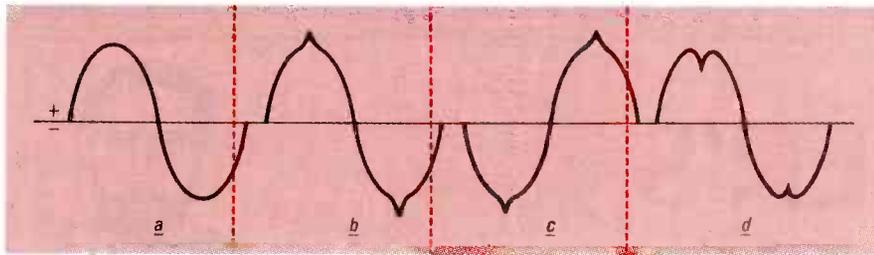


FIG. 2

some audio quarters. Indeed, some manufacturers have made much of the fact that their new equipment uses little or no negative feedback. A few other manufacturers have taken the purely semantic path to feedback elimination and instead substituted what they call *beta* or *servo* control circuits. In any case, the controversy about feedback dates from the time that Matti Ojala, a Finnish researcher/engineer, rediscovered that under certain conditions amplifiers using negative feedback would go into input overload, even though the input signal was theoretically too small to cause such a problem. He dubbed the effect "transient intermodulation distortion" or TIM. I say rediscovered, because several investigators published papers during the early 1950's discussing the TIM effect—although not by that name—and its solution.

In a nutshell, the problem is/was this: A rapidly changing signal—meaning one having high-frequency components—would
continued on page 81

Positive feedback

What about positive feedback, which is defined as feedback that is in-phase with the signal at the point of its reinsertion into the signal path? Whereas negative feedback works to restore the status quo, so to speak, positive feedback tends to introduce instability. Squealing sound-reinforcement systems and howling turntable setups are both examples of uncontrolled and unwanted *acoustic* positive feedback. However, controlled electrical positive feedback is used in the audio and radio-frequency oscillator circuits found in test instruments and tuners.

As far as I know, the only use of positive feedback in an audio-am-

plifier was in an old Dynaco tube preamplifier where a positive-feedback loop (enclosed within a negative-feedback loop to ensure stability) was used for increased gain using fewer stages of amplification. Since gain is both cheap and easy to come by in this age of solid-state, I don't expect to see positive feedback in future amplifier circuits. Feed-forward, Black's earlier invention, which has experienced a slight comeback, is sometimes confused with positive feedback, but it's a completely different approach.

Feedback negatives

In the past several years, feedback has fallen into disrepute in

NEW RUGGEDIZED SCOPE PROBES

Just a phone call away.

\$35 P6103

50 MHz 10x
Compensation Range
15 to 35 pF

\$58 P6109

150 MHz 10x
Compensation Range
18 to 22 pF


These new passive voltage probes can be used with any oscilloscopes having matching compensation ranges.

Screw in tips mean easy repair, no downtime.

To order call toll free **1-800-426-2200**

In Oregon, call collect (503) 627-9000.

VISA and MasterCard accepted.

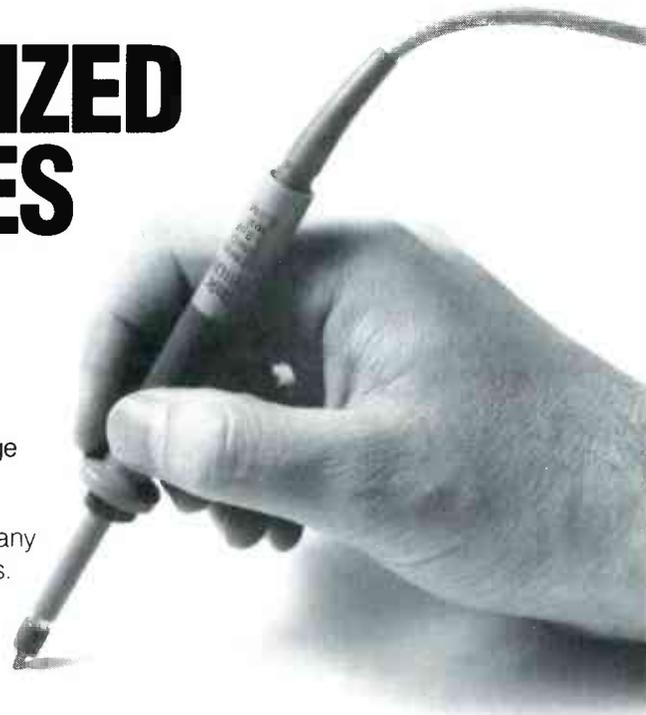

Tektronix
COMMITTED TO EXCELLENCE

DESIGNER'S NOTEBOOK



ROBERT GROSSBLATT,
CIRCUITS EDITOR

Making sinewave oscillators

ALTHOUGH WE'VE EXAMINED MANY kinds of oscillator circuits, there's one we've left out: the sinewave oscillator. Most of the circuits that we've looked at have been digital squarewave generators of one kind or another. Although I've shown you how you can alter them to get a triangular wave, even with a lot of filtering there's no easy way to get a low-distortion sinewave at the output when you start with a squarewave at the input.

Trying to convert squarewaves into sinewaves can lead to some real design nightmares. Calculating the filter values, dealing with the various kinds of distortion, and, in general, guaranteeing the purity of the output waveform is a lot more difficult than designing a sinewave generator from scratch. If you want a circuit that produces clean sinewaves you have to build one specifically for that purpose; and all it takes is a handful of parts that can be used to produce sinewaves that are much better formed than those you would get from a manipulated squarewave.

Sinewave oscillator

How much more difficult is it to convert a squarewave to a sinewave? Figure 1 will give you a good idea of how simple a sinewave generator can be. The circuit is built around the op-amp's feedback loop in a configuration of resistors and capacitors that is often referred to as a twin-T or twin-tee network. It's mostly used when the designer is interested in one particular frequency.

How well the circuit works is a direct function of: 1) how closely the components are matched; 2) using as low a source impedance

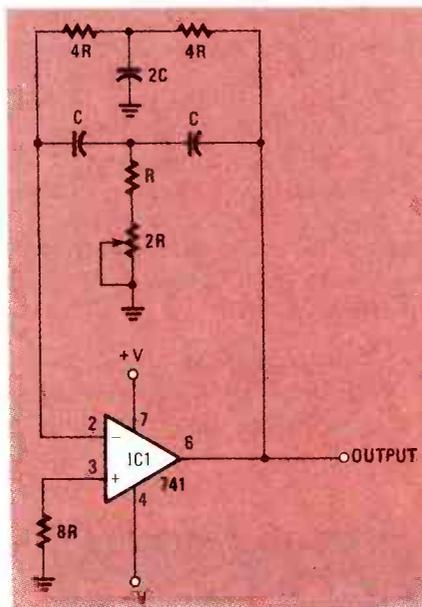


FIG. 1

as is possible for the tee network; 3) making the tee's output load impedance as high as possible.

The center frequency of the network (f) can be easily calculated by plugging numbers into the formula:

$$f = 1/(2\pi RC)$$

and by using components rated 1% or better.

The best way to understand how a twin-T network operates is to look at each half of the tee by itself. The upper half of the circuit is configured as a low-pass filter so it will tend to reject frequencies above a certain value. The lower half is set up as a high-pass filter and tends to reject frequencies below a certain value. Since the twin-T has the two circuits connected in parallel, a frequency-versus-gain plot for the circuit will look like Fig. 2. If both halves of the tee are carefully

matched, the filter will reject a particular frequency.

By using a potentiometer (2R) in one tee, we can detune the tee until the phase of the frequency going to the op-amp's non-inverting input is shifted 180°, which is the same as applying positive feedback. That will cause the op-amp to start oscillating, and the output will be a sinewave whose frequency is equal to the center frequency of the twin-T filter.

The other conditions for optimum operation of a twin-T network are satisfied by the op-amp. The tee is being fed by the op-amp's output (pin 6), which is a low impedance, and the tee's output is connected to the op-amp's input, which is a high impedance.

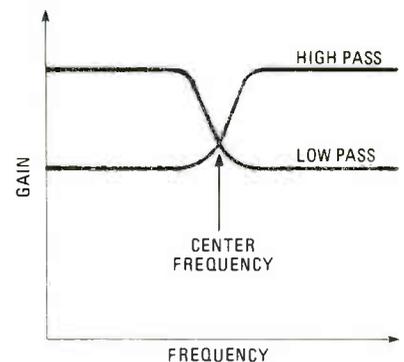


FIG. 2

I haven't given any values for the components because you can use the formula to determine what you need for whatever output frequency you want. Realistic limits are between 1K and 10K for the resistor and .01 μ F to 1 μ F for the capacitor. I used a 741 op-amp when I put the circuit together, but just about any op-amp will do. The best ones to use are those that have an FET in-

put, such as a TL084, since their input impedance is about as high as you can get. It's also a good idea to build the circuit with a dual op-amp and use the second amplifier as a buffer, since that will help improve the performance of the oscillator when it's connected into an actual working circuit.

The twin-T network is one of the basic building blocks for the design of analog filters. You should experiment with this month's circuit and get familiar with how component values can change the operation of the circuit. By combining the tee configuration with op-amps you can design a wide variety of different filter circuits: high pass, low pass, notch, and bandpass. While working out the component values for those circuits will usually involve a considerable amount of math, don't let that put you off. That's what calculators are for.

R-E

AUDIO UPDATE

continued from page 79

overdrive an amplifier's input stages, while a signal of the same amplitude, but without the high-frequency components, would cause no such problem. The overload occurred because the input stages were designed to operate with the gain-reduction of negative feedback; but when very fast high-level transients were involved, the feedback signal did not get back to the input stages quickly enough to prevent overload. The basic solution to TIM is to design-in sufficient bandwidth—before feedback—to ensure that high-frequency signals can *slew* (travel) through the amplifier fast enough to avoid problems.

Fortunately, any competent audio designer can easily achieve adequate *slew rate*—and thereby eliminate the possibility of TIM—without really straining his design talents. In my view, those engineers, sales managers, and audiophiles hyperconcerned with TIM problems are essentially chasing a wild goose carrying a straw man up a blind alley. In today's products, TIM is not likely to be the source of any differences you can hear.

R-E

#1 IN CABLE BOXES

Write for FREE CATALOG 136 page


JERROLD CORDLESS CABLE TV BOX

MODEL DRZ/450

- 66 channels
- On/off switch
- Automatic fine tuning
- A/B switch option
- Compatible with descramblers

\$69⁹⁵ / 10 Lot

\$79.95/1-9

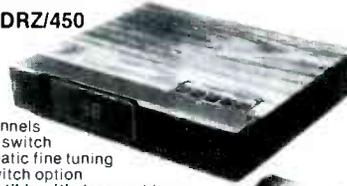

CORDLESS CABLE TV BOX

- 72 channels
- Parental control
- Remote fine tuning
- On/off switch
- Compatible with descramblers

MODEL DRX3-105/400
\$59⁹⁵ / 10 Lot

\$69.95/1-9



JERROLD CORDLESS CABLE TV BOX

MODEL STARCOM-CVS

\$99⁹⁵ / 4 Lot

\$109.95/1-3



- Volume control
- 68 channels
- Automatic fine tuning
- On/off switch
- Compatible with descramblers

SHIPPING CHARGES

For Orders	Add
\$25-100	\$6.50
\$100-500	\$8.50
\$500-750	\$10.50
\$750 and up	\$20.00

Send Check, Money Order, or C.O.D. or Call Toll Free

800-223-0826
in N.Y. State (212) 865-5580

OMNITRON ELECTRONICS

770 Amsterdam Ave., New York, NY 10025



* ADD 5% FOR CREDIT CARDS

CIRCLE 110 ON FREE INFORMATION CARD

SUPER LONG PLAY TAPE RECORDERS

10 Hour Model — \$95.00*
14 Hour Model — \$159.00*

Modified Panasonic Slimline, high quality, AC-DC Recorders provide 5 or 7 continuous hours of quality recording & playback on each side of cassette for a total of 10 or 14 hours depending on model. Built-in features include • Voice level control. • Digital counter. etc. TDK DC 180 Cassette Furnished.



PHONE RECORDING ADAPTER

Records calls automatically. All Solid state connects to your telephone jack and tape recorder. Starts recording when phone is lifted. Stops when you hang up. **\$24.50*** FCC APPROVED



VOX VOICE ACTIVATED CONTROL SWITCH
Solid state. Self contained. Adjustable sensitivity. Voices or other sounds automatically activate and control recorder. Uses either recorder or remote mike. **\$24.95***

*Add for ship & hdlg. Phone Adapter & Vox \$1.50 ea. Recorders \$4.00 ea. Cal. Res. add tax. Mail order, VISA, M/C, COD's OK. Money Back Guarantee. Qty. disc. avail. Dealer Inquiries invited. Free data. ©

AMC SALES, Dept. A 9335 Lubec St., Box 928, Downey, CA (213) 90241 Phone 869-8519

CIRCLE 108 ON FREE INFORMATION CARD

Cash in on the Video-Cassette Boom! START YOUR OWN TV/VCR REPAIR BUSINESS at Home in Spare Time



Now it's easy for you to get into this money-making business. Be the person in demand by the millions of families who own videocassette recorders—the fastest-growing product in the home entertainment field. Train at home in your spare time for an exciting career as a TV/VCR Repair Specialist. Experts show you how to start small at home with low overhead. Later you can go after repair business from hotels, offices, hospitals and other companies who use TVs and VCRs in their daily operations.

Experts show you what to do, how to do it...guide you every step of the way!

Learn how to handle house calls and shop repairs—everything you need to know to get started fast. Tools are included with your course so you get "hands-on" practice as you follow your lessons step by step. Everything is explained in easy-to-understand language, but if there is ever anything in your lessons you don't understand, you can write or phone your instructor and you can count on getting an authoritative answer. Get free facts and color brochure that tell about home business opportunities. No cost. No obligation. No salesman will visit!

MAIL COUPON TODAY!

ICS SCHOOL OF TV/VCR REPAIR, Dept. DEOC7
SINCE 1981 Scranton, Pennsylvania 18515

Please send me free facts on how I can learn TV/VCR Repair at home in my spare time.

Name _____ Age _____

Address _____

City/State/Zip _____

Phone () _____

CIRCLE 188 ON FREE INFORMATION CARD

COMMUNICATIONS CORNER



HERB FRIEDMAN,
COMMUNICATIONS EDITOR

The phantom hand.

ONE OF THE QUESTIONS OFTEN ASKED by hobbyists, technicians, and technical students who got into communications after the development of the transistor is why older equipment didn't use certain high-performance circuits. After all, some of the circuits actually originated back in the stone-age of electronics. The answer to their question is simply one word: *cost*. Using vacuum tubes, or even discreet solid-state devices, just the cost of the extra power-supply capacity and the larger cabinet needed to accommodate certain circuits could easily add \$100 or more to the retail price of a receiver, transmitter, or transceiver; and we have not even started to factor in the labor cost for assembling the circuit. But because integrated circuits and automated assembly of high-density circuits sharply reduces overall manufacturing cost, we can now include even the most sophisticated functions in general-purpose communications equipment.

A good example of an old idea made practical by combining the integrated circuit with automated assembly is the *automatic antenna tuner*, such as the Kenwood AT-250. (Keep in mind as we discuss the AT-250 tuner that a similar circuit is included in certain Kenwood transceivers—the whole assembly can actually fit in the palm of a hand.)

An automatic antenna tuner works this way: You select a transmit frequency, set the transmitter's function switch to *tune*, wait a few seconds for the whirring in the tuner to stop (or wait for the SWR

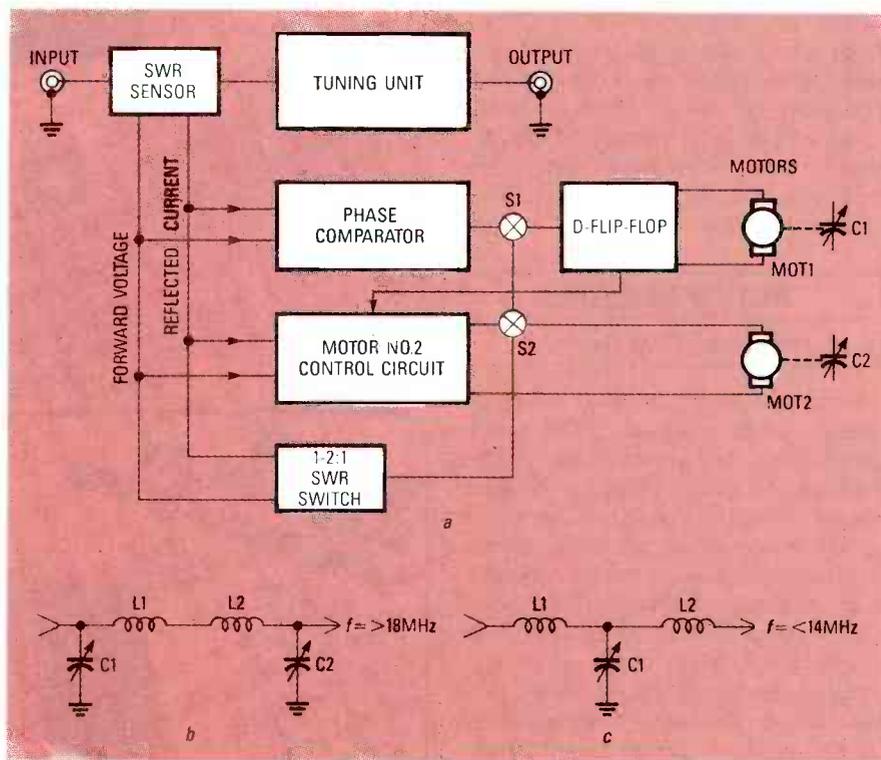


FIG. 1

indicator built into the transmitter or tuner to drop to about 1.2:1), and then switch to full power. In the few seconds it takes for the SWR to reach minimum, the automatic antenna tuner matches the antenna system to the transmitter. It sure is a lot more convenient than manually rocking a couple of tuning capacitors back and forth until your SWR meter indicates an acceptable value.

At first thought, automatic antenna tuning appears to be very simple. All we need are motor-driven capacitors controlled by some kind of SWR indicator. It should even be possible to build

an automatic tuner using vacuum tubes. So how come the "old-time" radio operators didn't use automatic antenna tuning? The answer is the amount of hardware needed, and what the hardware would cost if we built the circuit using discreet components. For example, the circuit used in Kenwood's automatic antenna tuner has 31 transistors, 13 IC's, 2 FET's, and 77 diodes. Want to try doing it with vacuum tubes, or by using all discrete solid-state components?

How it works

Figure 1-a shows a simplified block diagram of Kenwood's auto-

matic antenna tuner. The input jack connects to the transmitter's output; the output jack connects to the antenna system's coaxial transmission line. Within the section labeled TUNING UNIT are two tapped coils and two motor-driven variable capacitors. Above 18 MHz, a switching scheme automatically configures the components as a pi network as shown in Fig. 1-b. Below 14 MHz, the components are configured as a Tee-network as shown in Fig. 1-c. The coil taps are selected by transistor-driven relays. Either a bandswitch on the tuner selects the proper taps, or the taps are automatically selected when the tuner is used with certain transceiver models. Essentially, the coils are set for the band-in-use.

When the transmitter is set to its tune function, a very low RF-output level, about 3 watts, is fed into the antenna tuner. The SWR SENSOR develops an output representing the forward voltage and the reflected current. Keep in mind that when the SWR is low the two are in-phase; the greater the SWR the greater the phase difference between the forward voltage and the reflected current.

From there, the forward voltage and reflected current are fed to a PHASE COMPARATOR. If there is a difference in phase, the comparator develops an output that passes through electronic switch S1 to a D-type flip-flop switch. The switch "flips" and powers motor MOT1, which drives variable-capacitor C1. When C1 can reduce the SWR no further the flip-flop is turned off, which sends a signal through a feedback line to the MOTOR NO. 2 CONTROL CIRCUIT, which causes motor MOT2 to drive C2.

During the adjustment of C1 and C2, the reduction in SWR is tracked by an SWR SWITCH, that derives the SWR value by comparing the phase of the forward voltage with that of the reverse current. When the SWR SWITCH senses that the SWR has been reduced to 1.2:1 it opens electronic-switches S1 and S2, thereby disabling the tuning motors. The user knows the rig is ready for use because he or she can observe the SWR value on a built-in meter, or see a tuning indicator turn off. R-E

DOES YOUR DIGITAL CAPACITANCE METER DO THIS?

FULL 4 DIGIT 0.5 INCH LCD DISPLAY COMPLETELY AUTORANGING WITH 10 RANGE MANUAL CAPABILITY

- AND THIS RANGE OF 0.0 pF to 1 FARAD (999.9 mF) 0.5% BASIC ACCURACY UP TO 100 uF
- AND THIS READS DIELECTRIC ABSORPTION
- AND THIS EXTENDED PSEUDO 5 DIGIT RESOLUTION ON SOME RANGES ONLY
- AND THIS ABILITY TO ZERO LARGE CAPACITANCE VALUES UP TO 99.99 uF
- AND THIS CALCULATES TRUE CAPACITANCE IF CAPACITOR IS LEAKY
- AND THIS DIODE CLAMP AND FUSED PROTECTED INPUT DISCHARGE RESISTOR IN OFF POSITION AT TERMINAL INPUTS. POWERED BY 9V BATTERY
- ONE YEAR PARTS & LABOUR WARRANTY
- FOR ONLY THIS



- AND THIS IDENTIFIES TRANSISTORS (NPN, PNP) AND THEIR LEADS (E, B, C, ETC.)
- AND THIS TESTS ZENER DIODES AND RECTIFIERS. UP TO 20V ZENER WITH AC ADAPTOR, ZENER VOLTAGE WITH 9V BATTERY DEPENDS ON ITS CONDITION
- AND THIS AUTOMATICALLY CALCULATES LENGTHS OF CABLES IN FEET, METRES, MILES, KILOMETRES (THEORETICAL RANGE OF 9,999 MILES)
- AND THIS ABILITY TO SORT CAPACITORS IN MANY DIFFERENT MODES
- AND THIS ABILITY TO READ LEAKY CAPACITANCE (INSULATION RESISTANCE OR CURRENT)
- AND THIS CALCULATES TIME CONSTANTS WITH USER DEFINED RESISTANCE VALUES
- AND THIS HOLD FUNCTION FREEZES DISPLAY

\$169.95

MODEL **MC300** Approx. Size 7" x 4" x 1 1/2"
DAETRON
 a division of Bergeron Technologies Inc.
 935 THE QUEENSWAY, BOX 641
 TORONTO, ONTARIO M8Z 5Y9
 CANADA (416)676-1600

SHIPPING INSTRUCTIONS:

All units shipped out F.O.B. Buffalo NY via United Parcel Service (except Hawaii & Alaska) unless otherwise indicated (in which case shipments will be F.O.B. Canada)

PLEASE SEND ME	U.S. FUNDS
(QUANTITY) MC300(S) @ \$169.95	\$ _____
CARRYING CASE \$ 16.95	\$ _____
AC ADAPTOR \$ 9.95	\$ _____
SHIPPING AND HANDLING @ \$5.00 PER INSTRUMENT	\$ _____
<input type="checkbox"/> CHECK <input type="checkbox"/> MONEY ORDER	\$ _____
<input type="checkbox"/> VISA <input type="checkbox"/> MASTERCARD	TOTAL \$ _____
<input type="checkbox"/> CARD NO. _____	SIGNATURE _____
EXPIRY DATE _____	TELEPHONE _____
NAME _____	ADDRESS _____
CITY _____	STATE _____ ZIP CODE _____

DEALER ENQUIRIES INVITED

CIRCLE 190 ON FREE INFORMATION CARD

Get A Complete Course In

ELECTRONIC ENGINEERING

8 volumes, over 2000 pages, including all necessary math and physics. 29 examinations to help you gauge your personal progress. A truly great learning experience.

Prepare now to take advantage of the growing demand for people able to work at the engineering level.

Ask for our brochure giving complete details of content. Use your free information card number, or write us directly. **\$99.95**, Postage Included. Satisfaction guaranteed or money refunded.



Banner Technical Books, Inc.
 1203 Grant Ave.
 Rockford, IL 61103

CIRCLE 180 ON FREE INFORMATION CARD

ATTENTION! ELECTRONICS TECHNICIANS

EARN YOUR **B.S.E.E. DEGREE**

THROUGH HOME STUDY

Our New and Highly Effective Advanced-Placement Program for experienced Electronic Technicians grants credit for previous Schooling and Professional Experience, and can greatly reduce the time required to complete Program and reach graduation. No residence schooling required for qualified Electronic Technicians. Through this Special Program you can pull all of the loose ends of your electronics background together and earn your B.S.E.E. Degree. Upgrade your status and pay to the Engineering Level. Advance Rapidly! Many finish in 12 months or less. Students and graduates in all 50 States and throughout the World. Established Over 40 Years! Write for free Descriptive Literature.

COOK'S INSTITUTE OF ELECTRONICS ENGINEERING




347 RAYMOND ROAD
 P.O. BOX 20345
 JACKSON, MISSISSIPPI 39209

CIRCLE 58 ON FREE INFORMATION CARD

ANTIQUE RADIOS

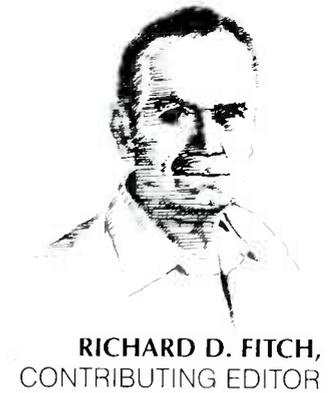Ancient transformers, tubes, and speakers



ALTHOUGH THERE'S BEEN TREMENDOUS developments in electronics technology during the past 100 years, fortunately for those of us into antique radios, we don't have to concern ourselves with either the pioneering days or the high-tech '80s. Our interest is primarily the era of the vacuum tube: from the 1920's through the 1940's.

Tube radios have five basic components: 1) Transformers and coils; 2) Resistors; 3) Capacitors (which used to be called "condensers"); 4) Tubes; 5) Speakers. This time out, we'll discuss the different types of transformers, resistors, and speakers, and how they're used.

Transformers and coils are related because they are essentially inductors. Power, IF, and audio-output transformers are the types most commonly used in radios. Components considered to be coils—even though they might ac-

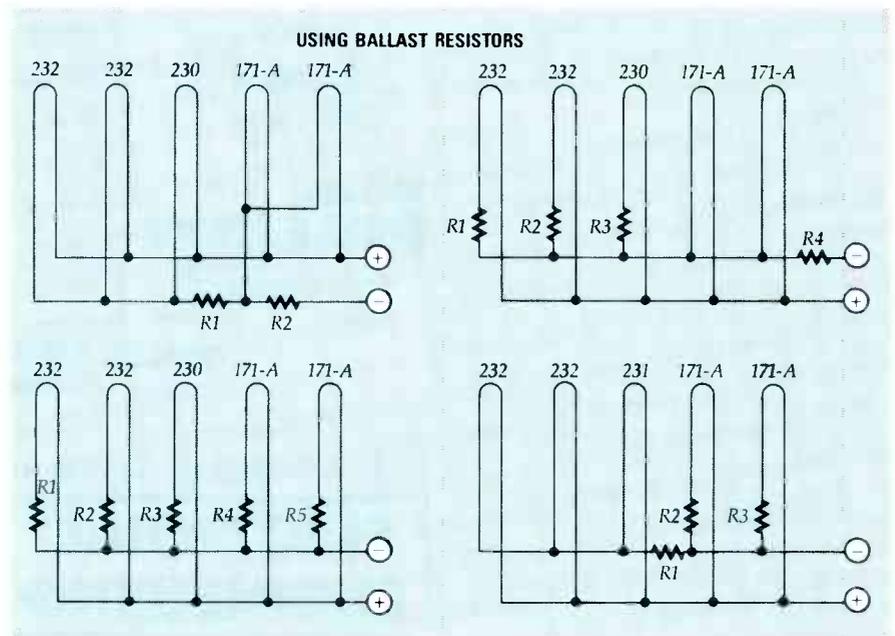


FIG. 2

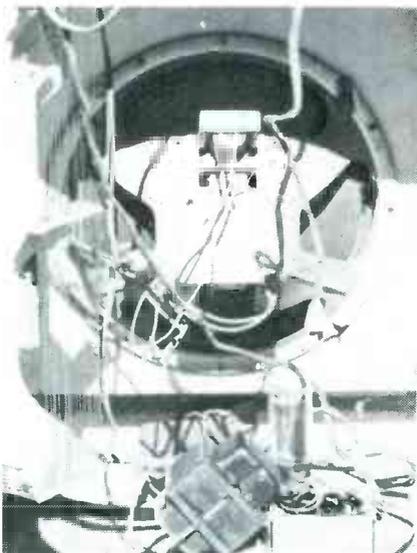


FIG. 1

tually be transformers—are those in the antenna and RF-amplifier circuits, a speaker field, and the speaker's voice-coil.

How is a transformer a coil? Simple! That's what we choose to call it. For example, an antenna input "coil" usually has primary and secondary windings, and that's a transformer in anyone's engineering textbook. Same thing with an RF amplifier's output circuit. While it might use a single inductor (a coil) as a load, more often than not the *plate coil* has primary and secondary windings; and once again, that's a transformer in an engineering textbook. However, in early radio service manuals, and even in modern manuals, both transformer types are usually called coils. It's sort of like calling cycles-

per-second Hertz. Hertz is a term created from what alchemists used to call the *ether*—air. Since we all breathe the same air we know what Hertz really is—it just takes a textbook two pages to explain what used to be obvious.

Although many antique radios had more transformers and coils than tubes, it's the tubes that collectors expect to be burned out; few expect transformers and coils to go bad. Unfortunately, power transformers in antique radios have often burned out many years earlier, and it's something you might not be able to check at the time you're purchasing the radio. But it's been my experience that radios with a defective transformer have been worked on at some time or other, so be wary of a

set where the transformer's mounting screws are missing or disturbed. Whoever worked on the set shown in Fig. 1 left the power transformer a wreck.

Besides total burn-out, open and shorted windings are also common to old radio transformers. While it's easy to use an ohmmeter to determine whether a winding is open, troubleshooting shorted windings with a conventional instrument is usually impossible.

The nose knows

Antique radio collectors soon learn to recognize the odor of an overheated or burning power transformer. If you fire up an antique radio and the transformer smells or overheats, turn the power off *fast* before a handful of other expensive parts go up in smoke. But keep in mind that a hot power transformer doesn't necessarily mean that the transformer is at fault: make certain that you at least check the rectifier and the filter capacitors before deep-sixing the power transformer.

Removing the rectifier tube or the selenium rectifier (if used instead of a rectifier tube) can help determine if the power transformer is shorted, or if a short in the B+ supply is drawing excessive current. That's because removing the rectifier usually disconnects the transformer from the rest of the circuit. (However, take care that there isn't a second rectifier—perhaps used for grid bias—separately connected to the power transformer.) In all likelihood, the transformer is probably OK if it doesn't overheat when the rectifier is removed.

A superheterodyne radio's IF transformer is another troublesome device. While it can have any of the usual transformer troubles such as shorts, opens, and poorly-soldered terminals, more frequently you'll find that the problem is man-made—or more accurately, tinkerer-made. An old radio that has lain around for many years could have been "repaired" by persons trying to make it play by tightening "the loose screws"—the IF transformer's adjustments.

Moving on to the output transformer, the device that matches

the high impedance of the output tubes to the low impedance of the speaker, the most common problem is an open primary winding, which is easily confirmed by using an ohmmeter. Since there are still plenty of universal replacement output transformers available, it shouldn't be too difficult to locate a substitute.

Although it's possible, I don't recall coming across an electrodynamic speaker having an open field coil. As a general rule, a defective antique radio's speaker usually has a damaged or distorted cone that can't be repaired because few technicians have the knowledge, ability, tools, or even the material to re-cone a speaker. So if you must remove what is an otherwise a good speaker from its mounting, be careful not to touch the cone because it's probably so brittle from old-age.

Voice-coil testing

The voice coil is sturdy and rarely opens or shorts; but a problem in early radios known as an *continued on page 108*



**THE MOST POPULAR
WIRE-WOUND CB ANTENNAS
IN THE WORLD**

Because...they perform!

FACT

"When CB was legalized in England, 'Firestik' antennas were barred from sale because the emitted signal was too strong. Fortunately, no other country, including the U.S., limits antenna efficiency."

**YOU CAN HAVE SECOND
BEST OR, 'Firestik'!**

Call or Write for **FREE** Catalog

'Firestik' Antenna Company
2614 East Adams
Phoenix, Arizona 85034
(602) 273-7151

MILLIONS OF SATISFIED OWNERS

CIRCLE 100 ON FREE INFORMATION CARD

87" HI-TECH SALE

Cobra Stun Gun generates 45,000 volts of stopping power, the Cobra also delivers a burst of high intensity light directly into an attacker's eyes. Chances are that his optic nerves will be so overdosed with excess light energy that he will not be able to see you let alone continue the attack. If he does, the Cobra delivers its painful bite, leaving him dazed and confused. \$49.95. With NiCad battery & charging kit \$59.95 + \$3.74 shp.

Centron Security Light

The Centron security light puts unwelcome visitors in the spotlight... instantly! This smart lighting system's infrared sensors guard your yard or driveway when you're away or home alone. It senses the presence of people or cars by changes in temperature patterns and instantly floods the area with bright light. It guides your guest to your door and scares a way would-be prowlers \$55.00 plus \$4.99 shipping.

Remote Control Pen.

Not only is it a hand-some high quality ball point writing pen, but a powerful remote-control device. Effective at distances up to 75 yds., the Remote Control Pen is perfect for turning on or off any 120 volt appliance or alarm system. Think of the possibilities. \$39.00 shipping \$3.74.

The Private Eye Motion Detector.

Alarm warns you to the presence of an intruder but the intruder doesn't know he has been detected. No wires just plug it in and it works. Information travels from the detector to the receiver via the electrical system. \$63.00 shipping \$5.40

World's smallest dialer \$49.95	Alcohol Breath Analyzer \$59.00
Levigator \$79.95	Telemonitor 2000 \$175.00
Pistol Cross Bow \$59.95	Remote Car starter..... \$225.00

****All products ready to use and Guaranteed****
ORDERS CALL TOLL FREE 1-800-624-1150 For information or free catalog call 402-554-0383 or write. Order by December 16th and we guarantee delivery by the 24th
6846 Pacific St. Omaha, Nebraska 68106 M.C. 5784

CIRCLE 53 ON FREE INFORMATION CARD

Be an FCC LICENSED ELECTRONIC TECHNICIAN!



Learn at home in spare time. No previous experience needed. No costly school. No commuting to class. The Original Home-Study course prepares you for the "FCC Commercial Radiotelephone License". This valuable license is your "ticket" to thousands of exciting jobs in Communications, Radio-TV, Microwave, Computers, Radar, Avionics and more! You don't need a college degree to qualify, but you do need an FCC License.

No Need to Quit Your Job or Go To School
This proven course is easy, fast and low cost! **GUARANTEED PASS** - You get your FCC License or money refunded. **Send for FREE facts now. MAIL COUPON TODAY!**

COMMAND PRODUCTIONS

FCC LICENSE TRAINING, Dept. 90
P.O. Box 2223, San Francisco, CA 94126

Please rush **FREE** details immediately!

NAME _____
ADDRESS _____
CITY _____ STATE _____ ZIP _____

R-E Computer Admart

Rates: Ads are 2 1/4" x 2 1/4". One insertion \$825. Six insertions \$800 each. Twelve insertions \$775. each. Closing date same as regular rate card. Send order with remittance to Computer Admart, Radio Electronics Magazine, 500-B Bi-County Blvd., Farmingdale, NY 11735. Direct telephone inquiries to Arline Fishman, area code-516-293-3000. **Only 100% Computer ads are accepted for this Admart.**

ICs PROMPT DELIVERY!!!

SAME DAY SHIPPING (USUALLY)

QUANTITY ONE PRICES SHOWN FOR OCT. 25, 1987

OUTSIDE OKLAHOMA: NO SALES TAX

DYNAMIC RAM		PRICE
1Mbit	1048Kx1 100 ns	
1Mbit	256Kx4 120 ns	32.00
51258	* 256Kx1 100 ns	6.95
4464	64Kx4 150 ns	3.60
41256	256Kx1 80 ns	5.95
41256	256Kx1 100 ns	5.15
41256	256Kx1 120 ns	3.95
41256	256Kx1 150 ns	3.50
41264	+ 64Kx4 120 ns	5.25
EPROM		PRICE
27C1000	128Kx8 150 ns	
27C512	64Kx8 200 ns	15.50
27256	32Kx8 250 ns	5.75
27128	16Kx8 250 ns	5.50
STATIC RAM		PRICE
43256L-12	32Kx8 120 ns	
5565PL-15	8Kx8 150 ns	3.30

OPEN 6 1/2 DAYS, 7:30 AM-10 PM. SHIP VIA FED-EX ON SAT.

SUNDAYS & HOLIDAYS: SHIPMENT OR DELIVERY, VIA U.S. EXPRESS MAIL

SAT DELIVERY INCLUDED ON FED-EX ORDERS RECEIVED BY: **FR. 11 5:00/12 11**

MasterCard VISA or UPS CASH COD
Factory New, Prime Parts μ P
MICROPROCESSORS UNLIMITED, INC.
 24 000 S. Peoria Ave. (918) 267-4961
 BEGGS, OK 74421

No minimum order. Please note that prices are subject to change. Shipping & insurance extra. \$3.50 to \$11 for packing materials. Orders received by 9 PM CST can usually be delivered the next morning, via Federal Express Standard Air - \$4.00, or guaranteed next day Priority One - \$10.50!

CIRCLE 61 ON FREE INFORMATION CARD

THE RAM BACK CHAIR

For Stressless Sitting and Perfect Posture



Features

- Adjustable Height 21"-27"
- Adjustable knee and seat pad
- Solid Wood - Oak Finish
- Thick Velour Cushions
- Folds for Storage

\$54 EA

Credit 1-800-227-2001

Cards 213-839-5974

Add \$9 ea. for UPS Delivery



RAM

8306 Wilshire Blvd., #10
 Beverly Hills, CA 90211

Free Brochure • Money Back Guarantee

CIRCLE 69 ON FREE INFORMATION CARD

CHRISTMAS SPECIAL

12-16-20 MHZ.
 HIGH SPEED

TURBO-286/386



- ▶ CPU-286-12/386-16 MHZ.
- ▶ 287/387 and 16-20 MHZ. opt.
- ▶ 1 MGB. on board. Max. 16 MGB.
- ▶ 2 Teac 1.2, or 360/3.5/720.
- ▶ 60 MGB. 28 MLS. with W.D. Contr.
- ▶ I/O, Serial, Parallel, Game.
- ▶ PGA, EGA, CGA, MGA, HERC. S. Sw.
- ▶ Deluxe Keybrd. 102/12 Funct. Keys.
- ▶ 200 W.P.S. Case. Digital Display.
- ▶ ☆☆ TURBO-XT-W/Monitor...\$899.00

TURBO-286/386-\$2,499.00/\$3,499.00

COMPSTAR, INC.
 (818) 842-4606

239 E. Alameda Ave., Burbank, CA 91502
 TELEX: 797196 FAX: (818) 845-0739

CIRCLE 196 ON FREE INFORMATION CARD

COMPUTER

ASSEMBLY



Eliminate
 Guesswork!
 Build with
 Confidence!

MANUALS

BIG BLUE SEED for IBM™ BUILDERS!

Parts list, placement diagrams, instructions, mods, for assembling over 90 IBM-compatible bare cards. Latest version with guides for 640K, Turbo, AT & Baby AT MthBds. **\$17.95**

APPLE™ BUILDERS NEED APPLE SEED!

Instructions for assembling over 90 Apple-compatible bare cards including II+ & IIe MthBds. For ALL Apple enthusiasts and hobbyists. **\$14.95**

SAVE 10% - ORDER TWO OR MORE MANUALS OVER 40 BARE IBM & APPLE CARDS IN STOCK

(MthBds • Disk • Video • Burner • MultiFn • I/O • Modem • Proto • etc)

Check/Money-order, VISA/MasterCard to:
NuScope Associates™, Dept RE

In U.S.A. In CANADA
 P.O. Box 790 P.O. Box 742, Stn B
 Lewiston, NY 14092 Willowdale, Ont. M2K 2R1

* A Division of Kosmic MicroTech Inc.

CIRCLE 72 ON FREE INFORMATION CARD

LASER PRINTER P.C. COPIER OWNERS



*H.P., Apple, OASYS, QMS, and more.
Recharge Your Used Toner Cartridges.

RECHARGING: PRINTER COPIER

BLACK	\$45	\$40
DK BLUE/BROWN	\$65	\$60
NEW CARTRIDGE	\$89	

(RETURN SHIPPING INCLUDED)

20 Years of Laser Printing and Xerography Experience
-Unconditional Guarantee-

LASER EDGE

800 W. Burlington, Fairfield, IA 52556
 (800)635-8088 (515)472-7850

CIRCLE 195 ON FREE INFORMATION CARD

IF YOU KNEW HOW EASY IT IS TO BUILD AN IBM® XT COMPATIBLE COMPUTER, YOU WOULDN'T PAY IBM® \$1000 TO DO IT FOR YOU!

- Anyone can do it! No special skills required □ Takes less than 2 hours!
- With a screw driver and my video tape you can save up to \$1000 over the price of an assembled IBM® □ Includes a list of suppliers of computer kits. (All kits have 90 day warranty and full compatibility) □ **MONEY BACK GUARANTEE** - If you aren't totally convinced that you can assemble your own computer after viewing my fail-safe, step by step video instructions, you pay nothing!

SEND \$29 FOR VIDEO TAPE TO:
 WOLFER PRODUCTIONS, Dept. R
 10153 1/2 Riverside Dr. #153
 Toluca Lake, CA 91602
 (California residents add 6.5% sales tax)



IBM PC/COMPATIBLES

- TEN PROGRAMS
- 100% BASIC
- EASY TO LEARN
- EASY TO USE
- WRITTEN BY EMERALD DIRECT
- SINCE 1981

NOT COPY PROTECTED

CA RESIDENTS ADD STATE TAX **\$49.95 + \$2** VISA ONLY SHIPPING & HANDLING

BLECHMAN ENTERPRISES
 7217 BERNADINE AVE., #10
 CANOGA PARK, CA 91307

INFO/ORDER: 9AM - 5PM M. - SAT. PACIFIC TIME

818-346-7024

* Amway has not reviewed or endorsed these programs.

CALL NOW AND RESERVE YOUR SPACE

- 6 x rate \$800.00 per each insertion.
- Reaches 245,824 readers.
- Fast reader service cycle.
- Short lead time for the placement of ads.

Call 516-293-3000 to reserve space. Ask for Arline Fishman. Limited number of pages available. Mail materials to: Computer Admart, RADIO-ELECTRONICS, 500-B Bi-County Blvd., Farmingdale, NY 11735.

TURBO CHARGE YOUR PC WITH THE ACCELERATOR 286

Replaces your PC, XT, or compatibles 8088 with an 80286 processor. It includes 8K of zero-wait-state cache memory, and your software can run up to 7 times faster. So why buy an AT? Upgrade your PC with the Accelerator. **\$275**

VIDEO SHARING DEVICE

\$59.95

Transmits color computer/VCR signal to any TV at home without cables. Simply plug it into com-puter's composite outlet or VCR's jacks. This is the least expensive way of upgrading your system to color without buying a color monitor. Minor assembly required.

PC Plus Corp. Monterey Park
 California 91754 710 E. Garvey Ave.
 (818)571-6991

CIRCLE 197 ON FREE INFORMATION CARD


COMPUTER DIGEST

VOL. 5 NO. 1 JAN. 1988

A NEW KIND OF MAGAZINE FOR ELECTRONICS PROFESSIONALS

MICROSOFT BOOKSHELF CD ROM Reference Library

Page 88

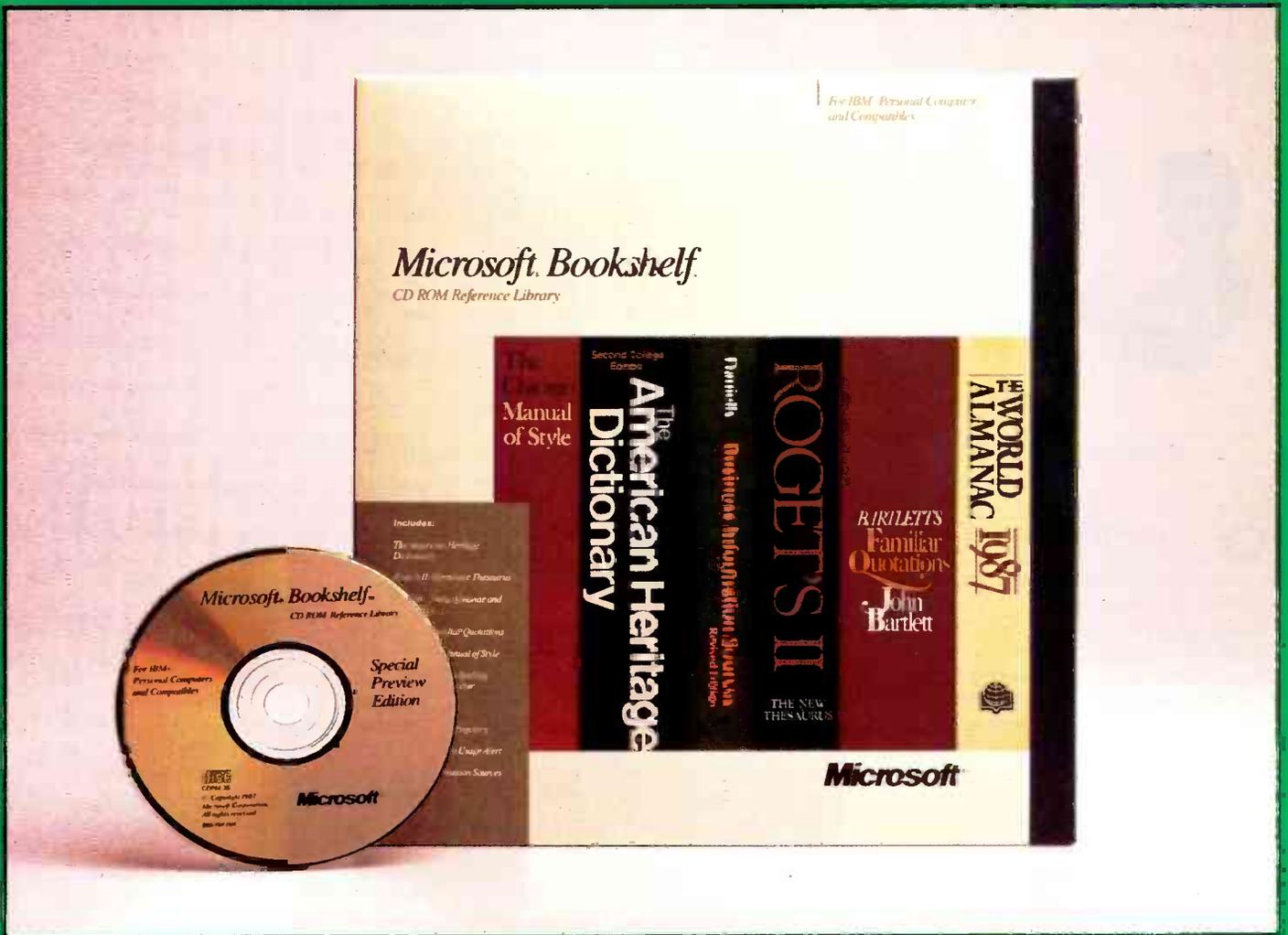

FLOPPY DISKS

Bits, bytes, and copy protection


Page 90

68000 COMPUTING

The CD Classroom continues

Page 96

EDITOR'S WORK- BENCH

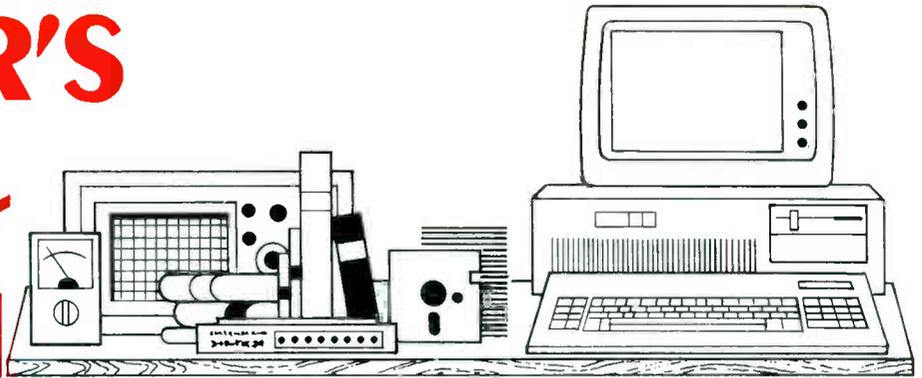

Microsoft Bookshelf

Optical storage will be at the core of the next evolution in computer technology, some say. Advantages include extremely high information density and very low production costs. To date, however, most commercial products based on optical technology (financial and other specialized databases) have had little mass appeal. The Electronic Encyclopedia published by Grolier on CD-ROM (Compact Disk read-only memory) was the first consumer-oriented optical product; it provides the entire database (text only) of the Grolier Encyclopedia. (See page 90 of the April 1987 issue for a review.)

Microsoft just released the second major CD-ROM product that is likely to have widespread appeal; it is called Bookshelf. Bookshelf consists not of a single database, like the Electronic Encyclopedia, but of ten reference works, including: *The American Heritage Dictionary*, *Roget's II Thesaurus*, *The World Almanac and Book of Facts*, *Bartlett's Familiar Quotations*, *The Chicago Manual of Style*, *The U.S. ZIP Code Directory*, a spelling checker, a usage checker, a set of form letters, and a categorized listing of sources of business information.

To run Bookshelf you need a CD-ROM drive, a PC, XT, AT, or clone, DOS 3.0 or higher, and a copy of the MS-DOS CD-

ROM extensions (software drivers for the CD-ROM drive, usually supplied by the manufacturer, and which are also available separately). Bookshelf itself costs \$295, and the drive will set you back about \$1000. In addition, a dual-floppy computer requires 640K of RAM to run Bookshelf; a hard-disk system can squeeze by with only 512K. The program will run on a dual-floppy system. We tested Bookshelf on a standard IBM PC XT with a 20-megabyte hard disk, a 500K RAM disk, and a 500K disk cache.

At those prices, obviously, Bookshelf will not compete with paperback reference works sold at dime stores, but that's not Bookshelf's intended market. The target, rather, is the serious writer—including the serious technical writer.

Setting up

The CD-ROM drive itself interfaces to your PC via a cable that connects to a plug-in expansion card. After installation, which includes modifying your CONFIG.SYS and AUTOEXEC.BAT files, the CD-ROM drive will become your next available drive. On an XT with a single floppy, a hard disk (C:), and a RAM disk (D:), the CD-ROM drive would appear as drive E.

After installing the hardware and system software, you log onto the CD-ROM drive (just as if it were a regular drive, except that you can't write to it), and run a Setup utility. That program copies files to your hard disk and installs the program according to the hardware and software you'll be using Bookshelf with.

Normally you run Bookshelf in a memory-resident mode so that you can call it up from within your word processor while you are writing. (You can also run Bookshelf as a transient application.) Bookshelf requires about 128K of memory (in memory-resident mode), and really works better with a RAM disk, which you'll probably want to locate in the EMS memory.

After booting and loading the program, you can call it up at any time by pressing a user-definable hot-key combination. Bookshelf will work with any word processor or other program that operates in text mode—not graphics mode. It works best, however, with most versions of Microsoft Word, Word Perfect version 4.2, Multimate Advantage version 1, IBM Display Write III, Volkswriter 3, Xy-Write III and III Plus, and PC Write version 2.71. It's more convenient to use a supported word processor because the thesaurus can replace words automatically, and the spelling checker can check an entire screen at a time. Other functions (the form letters, for example) that feed information into a document work fine, though.

Using it

Press your defined hot keys, and Bookshelf pops up. Figure 1 shows the ZIP Code reference display screen. The top line shows which word processor Bookshelf has recognized (it displays "Unknown" in an unsupported program); the second line presents a twelve-item menu bar which you can navigate using a mouse, the cursor-control keys, or by pressing the first letter of your choice. We found the latter method to be the most convenient.

After selecting the desired reference work, a menu appears, allowing various options for the chosen work. The dictionary's menu, for example, allows to look up a word, biographical information, or geographical information.

Next a dialog box appears, in which you enter additional information. Dialog boxes work differently according to which opus you're working with. The ZIP Code checker, for example, will pick an address off the screen and find the correct ZIP Code. Bookshelf will then feed the ZIP Code back into your word processor just as if you had typed it. Alter-

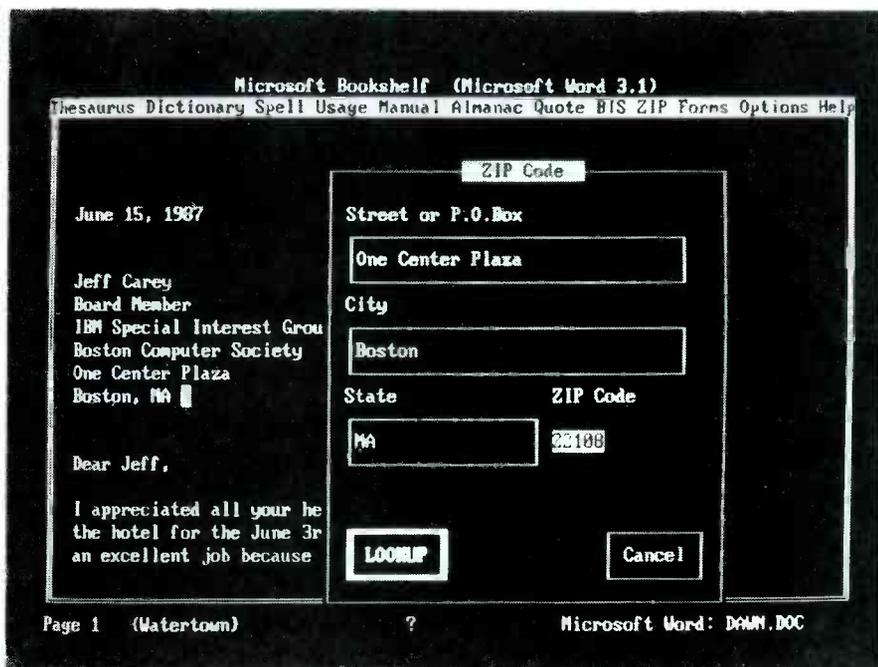


FIG. 1

natively, you can type an address in the dialog box, look up the ZIP Code, and feed the whole thing into your word processor.

The ability to look up ZIP Codes is useful, if unexciting. Bookshelf's real strengths are the dictionary, the thesaurus, the book of quotations, and the almanac. The dictionary is based on the full American Heritage dictionary; it includes complete definitions (not simple "synonyms"), word derivations, and biographical and geographical information. You can look up a word that Bookshelf reads from the screen or you can type one in from a dialog box. In addition, you can do cross-index searches—find all entries in which the word *computer* is used, for example. Unfortunately, you cannot paste definitions into your documents (presumably for copyright reasons). You can scroll through an alphabetized list of entry words only, without displaying definitions, and zoom in on one by pressing a key. In the expanded display, highlighting is used to indicate word entries, syllable breaks, derived forms, the definitions themselves, and derivation. Synonyms and points of usage are discussed at some entries, just as in the "real" (paper) version of the dictionary. For browsing, you can "open" the dictionary at the beginning of any letter—A for example.

Accessing the other works functions in a similar manner. However, locating information can be quirky, if not difficult. For example, I wanted to locate financial information in the almanac about the computer industry. After entering the words *computer* and *finance* in the dialog box, I was presented with a list of articles. I selected one, and then read it. I wanted

to return to the list of articles to choose another, but was unable to do so without re-entering the search words and waiting for Bookshelf to search its database. In general, depending on the type of search, you may end up doing a lot of thumb twiddling.

Conclusions


Bookshelf is a wonderful idea, but the implementation leaves something to be desired. In spite of the fact that it uses 128K of RAM and can use a RAM disk for temporary storage, it is slow. Search speed is slow, and display speed, once the information is found, is slow. In fact, text spills across the screen at a rate that is comparable to what a 1200-baud modem provides.

Bookshelf's strong point is the dictionary, which is truly a dictionary, unlike all other products for personal computers. The thesaurus and the quotations reference also work well. The almanac contains a great deal of information, but getting at it is a problem, as described in detail above.

As a professional editor and writer, I want to like Bookshelf, and I want the capabilities it can provide. But the program's slow performance, coupled with the high cost of the product and the hardware necessary to run it, cause me to question whether I couldn't get along without it. Admittedly, Bookshelf can do some things that would be impossible by hand—doing comprehensive searches, for example, or directly importing text into a document—but bread-and-butter searching and browsing can usually be done much more efficiently the old-fashioned way.

Microsoft is to be commended for

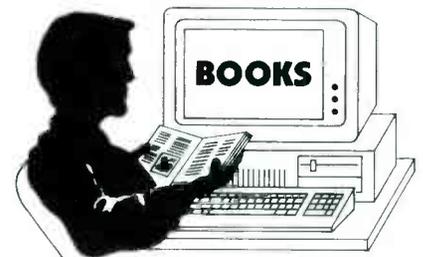bringing Bookshelf to market; eventually all personal computers will have comparable capabilities. Let's hope that the company sees fit to upgrade Bookshelf's performance to what it should be, and that CD-ROM drives fall in price to an affordable level. ♦♦♦



Borland-Osborne/McGraw-Hill Programming Series

Osborne/McGraw Hill books have for many years provided useful text and reference books for those involved in computers and electronics. Now the book-publishing company has teamed up with Borland International, publisher of many high-quality applications programs and programming languages, including Turbo Pascal, which single-handedly changed the programming language market when it was introduced several years ago. The two companies have launched a new line of books intended to support many Borland products, including the programming languages Turbo Pascal, Turbo C, and Turbo Prolog, and the applications programs Sprint and Reflex, a word processor and a database manager, respectively.

Advanced Turbo Pascal, by Herbert Schildt, for example, contains twelve chapters on advanced programming techniques in that language, including sorting and searching; queues, stacks, linked lists, and trees; dynamic memory allocation; assembly-language and DOS interfacing; etc. An introductory chapter reviews Pascal basics, and an appendix discusses converting programs from other languages. Schildt's style is quite readable, and his coverage appears thorough. The book contains many example programs, which Schildt will provide on disk for the healthy sum of \$24.95. ♦♦♦


Products Reviewed

- Microsoft Bookshelf, Microsoft Corporation, 16011 NE 36th Way, Box 97017, Redmond, WA 98073-9717, (206) 882-8080. **CIRCLE 000 ON FREE INFORMATION CARD**
- Osborne/McGraw-Hill, 2600 Tenth Street, Berkeley, CA 94710, (800) 227-0900, (800) 772-2531 (CA). **CIRCLE 000 ON FREE INFORMATION CARD**



FLOPPY-DISK DATA STORAGE

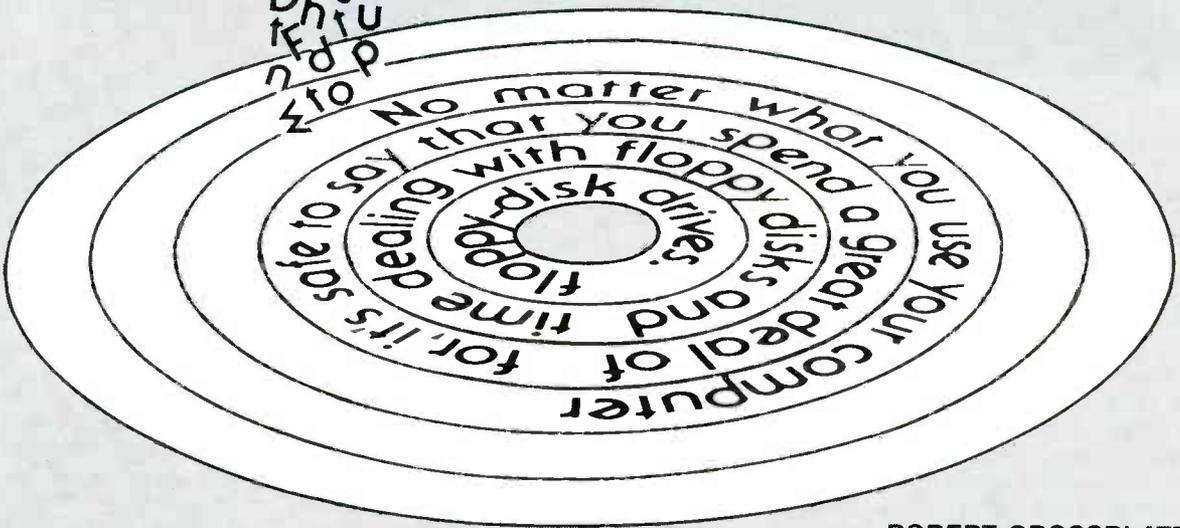Learn all about Apple and IBM disk formatting—including copy protection!



ROBERT GROSSBLATT

Part 2

This month we'll turn our attention more fully to copy protection, highlighting the schemes used to make Apple and IBM software secure.

Oddball formatting and nibble counting

The first two copy-protection schemes form the basis for most others. The basic idea behind oddball formatting is to format most of a disk in the usual manner, but to format one or more sectors in a unique manner. That way, when DOS first starts to read the disk, it assumes one format. When it runs into the odd sector, it thinks a data error has occurred. However, the copy-protected program itself knows where to expect that sector and how to deal with it.

Nibble counting is based on the fact that no two disk drives are exactly the same. In order for disks to be readable on various machines, DOS has a built-in "tolerance" factor that programmers can use to implement copy protection.

The major difference among drives is the speed at which the disk rotates. The standard is 300 rpm (200 milliseconds per revolution), but a drive only has to be within about 1% of that speed to be usable.

As we saw earlier, each sector on a disk has the room to store the requisite data. The remainder of the space is filled with gap bytes that separate one sector's data area from the next sector's ID area. The number of gap bytes written on a track is a direct function of the drive's speed and the rate at which the disk hardware spits out bits. But bit timing is in microseconds and drive timing is in milliseconds, so it's safe to say that the number of gap bytes depends exclusively on drive speed.

The gap bytes in a particular track, called the *signature track*, are counted, and the sum is stored elsewhere on the disk. Then, when you run the program (or boot the disk), the head is moved to the signature track, the bytes are counted and compared to the original number. If they're not the same, the software knows it's not running on the original disk, and that's what makes nibble counting tough to crack.

Track erase, directory move

The earliest forms of Apple copy protection were feeble by today's standards. For example, erasing one disk track would bring the normal copy program to a screeching halt. And if the erased track was near the

RADIO-ELECTRONICS

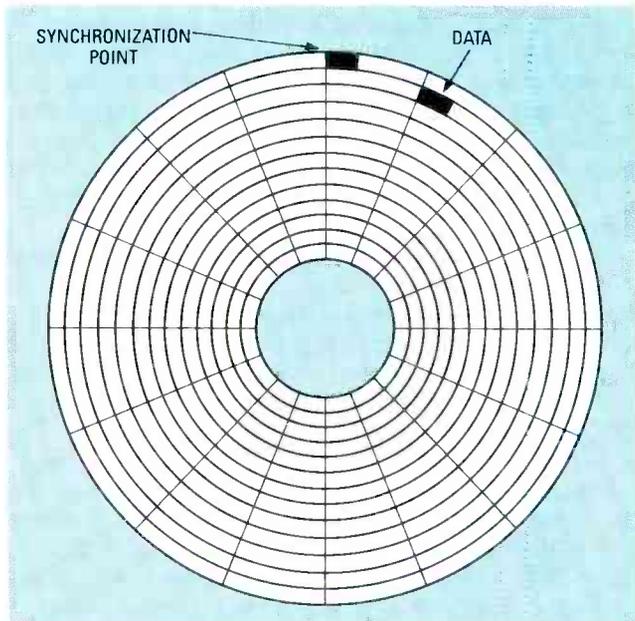


FIG. 5—TRACK SYNCHRONIZATION involves writing data at a particular location, stepping the read/write head, and writing additional data.

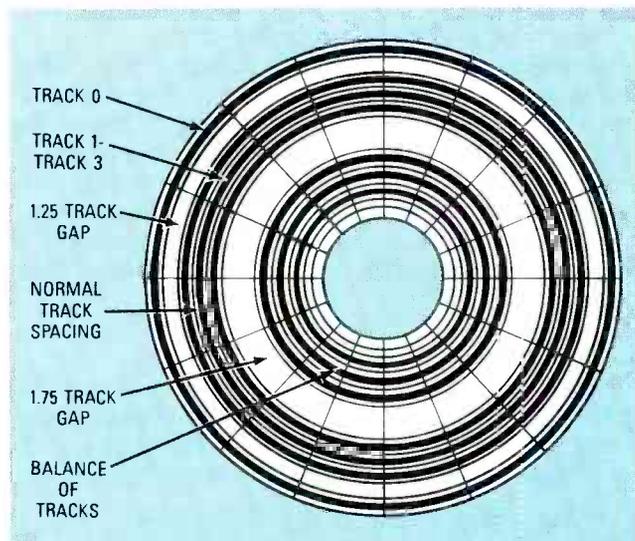


FIG. 6—NON-STANDARD TRACK WIDTH is achieved by stepping the read/write head in 1/4-track increments.

outside of the disk (track 3, for example), the rest of the disk would be protected.

Another early method was to move the catalog from track 11, where it was normally found. The files were also made unlistable by changing the standard load locations so you couldn't even look at the files. A reset would wipe out memory and reboot.

Those tricks, and a few others, were attempts to protect programs by altering DOS. They were effective for awhile because no one had taken DOS apart yet, so DOS parameter locations, sector formats, and file structure weren't common knowledge. After those things became known, however, the simple copy-protection schemes were dropped in favor of more-sophisticated ones.

The 36th track

When the copy-protection industry was in its infancy, someone discovered that, although DOS was designed

around 35-track hardware, most Apple drives could actually read 36 tracks. That was the first time the disk hardware itself was used as the basis of a copy-protection scheme. Publishers put part of their code on track 36 and checked to make sure it was there whenever the program was run. None of the standard copy programs knew anything about the extra track so the disk was uncopyable—until the method was found out and publicized. Even without the discovery, use of the 36th track was ineffective because not all drives could read that track. So, as soon as consumers started returning software, the method was dropped.

Track syncing

The next type of copy protection can be understood by looking at Fig. 5. When data is either read from or written to a disk, DOS is told to go to a specific track and then look at a particular sector; no special relationship is assumed between adjacent tracks. However, software publishers discovered that it was possible to keep very strict timing relationships when reading the disk. This meant that if you knew where you were on one track at the instant you told the head to step, you knew where you would be when you arrived at the next track.

Building a protection scheme around that fact involves writing a program that reads a track, steps the head when a particular data pattern is found, and then immediately writes some data to the new track. You now have a disk with known data patterns written in a particular order on adjacent tracks. If you change the write to a read and don't find the data pattern you originally wrote there, you know that it's not the original disk.

Playing With Apple DOS

The ways in which you can "customize" DOS are limited only by your imagination. After all, DOS is just another program. Here are a few suggestions on how you can change the internal workings of DOS to provide a measure of copy protection to your own disks.

Normally DOS reads your keyboard commands and tries to execute them. However, by patching in your own routine, you can cause DOS to do just about anything. Location \$9FED is a good patch point. In an unmodified DOS, you'll see the following code:

```
9FED      59 A4 A8      EOR      $A884,Y
```

That is the beginning of the code that parses the input line before going into the command table. Here are several ways to patch that code. First, by causing a jump to \$C600, any input line will cause the machine to reboot:

```
9FED      4C00 C6      JMP      $C600
```

This line will cause any input line to jump to BASIC:

```
9FED      4C 03 EO      JMP      $E003
```

This line will cause any input line to beep and go into the monitor:

```
9FED      4C 65 FF      JMP      $FF65
```

This line will cause any input line to beep and print "ERR":

```
9FED      4C 2D FF      JMP      $FF2D
```

DOS has both warm and cold boot routines, and it can tell which one is required by looking at the byte stored at location \$03F4. If you change the value in DOS, you'll force a cold boot whenever the reset switch is pressed. Normally DOS has the following code:

```
9E36      49 A5      EOR      #$A5
```

By changing the A5 to a 00, you'll be able to initialize a disk with a DOS that will reboot whenever reset is pressed.

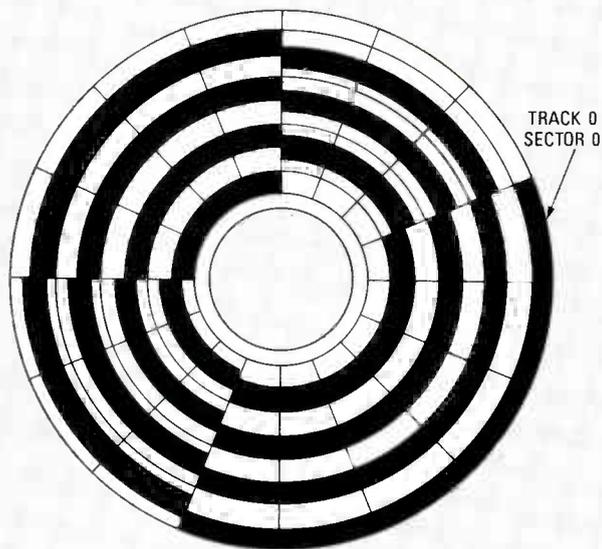


FIG. 7—A "SPIRAL" TRACK organization is achieved by offsetting alternate tracks or groups of tracks.

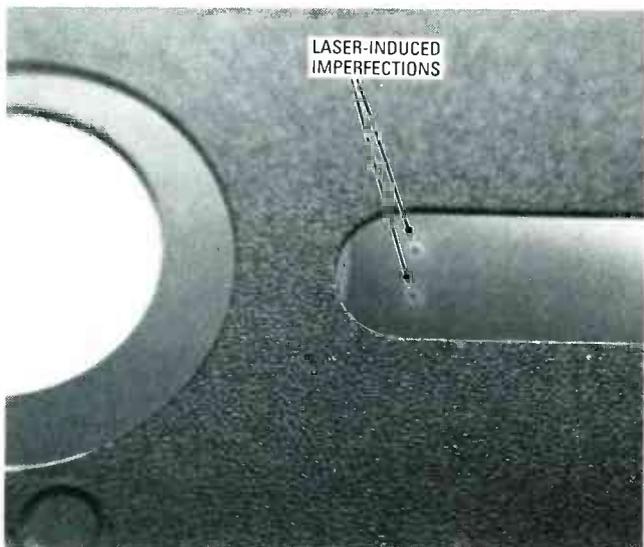


FIG. 8—A LASER-BURNED DISK can be backed up, reformatted, and the copies restored—and the copy-protection is still intact.

Using synchronized tracks became extremely popular. Publishers liked it because it was easy to implement and, at the time, none of the existing copy programs could get around it. Of course, that didn't last long. Most current copy programs can write synchronized copies, so that tracks on the copied disk are arranged in the same order as those on the original disk.

Quarter tracking

All of the copy-protection methods we've discussed so far are techniques that can be implemented from a regular DOS. Apple made their disk system very software intensive, so programmers have much control over the disk hardware. As more and more became known about DOS, programmers found new and sometimes bizarre ways to make their disks unreadable by normal methods.

Some unknown hero in the copy-protection business discovered that Apple DOS didn't actually move the

read/write head an entire track at a time, only a quarter of a track at a time. Being able to step between tracks seems useless because data must be at least one track apart for it to be read reliably by the computer. The problem is crosstalk—exactly the same sort of problem that crops up in audio and video tape. If the guard band is too small, or if the recorder's heads are out of alignment, the head can read from two tracks at the same time.

The secret lies in the fact that, although tracks must be separated by at least a whole track, they can also be separated by more than that. A disk using that method is shown in Fig. 6. Track zero is in the correct position, but there's a track and a quarter between it and track one. The next three tracks are one track apart, but then we have a gap that's one and three quarters of a track wide. The remainder of the tracks are separated by one whole track.

It doesn't take much to see that some of the data on the disk is going to be inaccessible to a normal DOS. It will be able to read track zero and the tracks from five to the end of the disk. But when DOS tries to read the odd-spaced tracks, the head won't be positioned over the center of the track, so the signal will be weak. Signal-to-noise problems guarantee that, although some of the data might be read correctly, a good part of it won't. The result is a disk unreadable by any DOS that doesn't know exactly how each track is positioned on the disk.

Writing quarter tracks on a disk requires careful attention to timing details. The stepping rate of the head must be carefully controlled, as does choosing the moment at which data can be read. Many disk drives, particularly older ones with slower stepping rates, have trouble reading a disk with quarter tracks. The problem is more pronounced with tracks that are written near the perimeter of the disk, because the disk turns with a slightly faster linear velocity there.

Spiral tracking

Next, the software industry developed the idea of spiral tracks, which solved the problem of wasted disk space, and made it even more difficult to make copies. Figure 7 is a representation of a disk with spiral tracks. You

LISTING 1

```

10 REM *****
15 REM * THIS PROGRAM WILL LET *
20 REM * YOU MOVE THE LOCATION *
25 REM * THAT DOS USES FOR THE *
30 REM * CATALOG TRACK. *
35 REM *****
40 :
50 OLDTRACK = PEEK (44033)
90 TEXT : HOME
100 PRINT "THE CATALOG IS NOW ON TRACK ";OLDTRACK
110 PRINT
120 INPUT "WHAT IS THE NEW CATALOG TRACK? ";YOURTRACK
125 VTAB 6: HTAB 1
130 IF YOURTRACK<3 OR YOURTRACK>35 THEN PRINT CHR$(7): GOTO 500
140 :
145 REM PATCH THE FILE MANAGER
150 POKE 44033,YOURTRACK
160 :
165 REM PATCH THE INIT ROUTINE
170 POKE 44703,YOURTRACK: POKE 44764,YOURTRACK
180 :
185 REM PATCH THE CATALOG ROUTINE
190 POKE 46012,YOURTRACK
200 :
210 PRINT "YOU CAN NOW INITIALIZE A DISK THAT HAS"
215 PRINT "FILES UNREADABLE BY A NORMAL DOS."
220 END
500 INVERSE : VTAB 24: HTAB 1
510 PRINT "THE NEW TRACK MUST BE BETWEEN 3 AND 35";: GOTO 125

```

LISTING 2

```

59E4      CF E7 59      DEC $59E7
59E7      CF              ???
59E8      EA              NOP
59E9      59 EF EA        EOR $FAFF,Y
59EC      59 AD 51        EOR $51AD,Y
59FF      C0 AD            CPY #$AD
59F1      54              ???
59F2      C0 AD            CPY #$AD
59F4      57              ???
59F5      C0 AD            CPY #$AD
59F7      52              ???
59F8      C0 20            CPY #$20
59FA      60              RTS
59FB      5B              ???
59FC      20 C5 5B        JSR $5BC5
59FF      20 4F 5B        JSR $5B4E
5A02      A9 04            LDA #$04
5A04      8D EC B7        STA $B7EC
5A07      A9 00            LDA #$00
5A09      8D EB B7        STA $B7EB
5A0C      A9 00            LDA #$00
5A0E      8D F0 B7        STA $B7F0
5A11      A9 60            LDA #$60
5A13      8D F1 B7        STA $B7F1
5A16      A9 40            LDA #$40
5A18      20 45 5A        JSR $5A45
5A1B      10 01            BPL $5A1E
5A1D      A9 20            LDA #$20
5A1F      91 5A            STA ($5A),Y
5A21      AD 50 C0        LDA $C050
5A24      A9 09            LDA #$09

```

• • •

can see that it meets the track-spacing requirement and that it makes maximum use of disk space. Trying to copy a disk like that can result in major brain damage. Not only do you have to know the track spacing, but you also must have the correct pattern.

There are two reasons why spiral tracks are a real problem for a copy program. The first is simply that it's hard to tell how many sectors have been placed on a particular track. The second more serious problem has to do with the nature of copy programs. We've already seen that there are so many ways to protect a disk that a good copy program can't make any assumptions about what it's going to find when it reads the disk. The more it expects to find, the less it will be able to deal with what's really there.

Let's suppose that you've just bought Acme Copy, the roughest, toughest, smartest, copy program in the world—it's so good it can even copy an unformatted disk—and you use it to make a copy of a spiral-tracked disk. You load the program and turn it loose. Even though

track zero is written upside down and backwards, Acme Copy copies it without a hitch. Let's also suppose that the rest of the disk is spiral tracked; only half of the sectors on each track contain real data. Acme Copy doesn't know anything about that—no assumptions, remember?

Acme Copy reads in a track, half of which is data and half of which is garbage—and that's where the problem comes in. There is no way for the program to distinguish garbage from copy-protected data. It reads the track's data, does some sort of analysis, writes out the copy, and steps to the next track. Of course the copy will be worthless. Even if Acme Copy goes through the disk quarter track by quarter track, the act of writing a quarter track will undoubtedly corrupt the previous quarter track. It's sad but true that the only way you can get it to work properly is to tell it what spiral pattern to follow as it goes through the disk.

IBM copy-protection

Most of the Apple protection methods we've looked at have their counterpart in the IBM world. Modifying DOS and messing around with sector information were done early on in PC history—and neither method lasted any longer there than in the Apple world. Most IBM copy programs can deal with those methods without even working up a sweat.

However, some of the more imaginative copy-protection methods found on the Apple simply couldn't be ported over to the IBM because of the basic difference in their disk systems. The PC's designers decided to let most of the disk system be handled by an LSI controller IC. That made it simpler to develop DOS, because the controller has built-in routines to handle disk primitives like moving the head, reading and writing data, formatting, and so on. The ability to do quarter tracking, for example, is impossible because the controller hardware can only step the read/write head in full-track increments. In fact, because of the limited repertoire of commands built into the floppy-disk controller IC, just about the only trick that appeared had to do with the index hole.

Contrary to popular belief, the IBM only uses the index hole when formatting a disk. Every time the head is stepped out to a new track, the PC waits for the index hole to appear and uses that point as the starting point for formatting the track. After a disk has been formatted, particular tracks and sectors are located using the same method as the Apple. The floppy controller reads in the sector address of its current position and then steps in or out to the track DOS wants it to read.

Some protection methods want the track-splice point (the place where start and end points meet) to be exactly at the index mark. As with any protection method, however, this one only baffled copy programs for awhile. After the method was uncovered, it wasn't long before most copy programs could handle it.

Undocumented op-codes

IBM's floppy controller is an NEC PD765, which is really a microprocessor that has been optimized to handle disk drives. Some programmers disassembled the microcode in the IC looking for features and abilities that didn't appear in the documentation.

Several undocumented features were found, the most popular of which was to mix FM (frequency modulation)

and MFM (modified frequency modulation) formatting on one track. None of the copy programs were able to handle that mixed formatting, because they didn't know how to make the PD765 do the trick. The result was a nearly unbeatable protection scheme.

However, there are two big problems with undocumented op-codes. The first is that the manufacturers who second-source the IC don't know about them. The second is that, because they aren't part of the 765's published vocabulary, there's no way to guarantee they'll still be there when new versions of the IC are released. And that's what spelled the death of mixed formatting on the IBM. The software ran well on computers that used the same run of 765's, but died on other machines. Needless to say, the scheme was dropped.

Other methods

The search is always on to discover new and wonderful ways to lock up disks. The older, software-only methods such as altering DOS or playing around with sector formatting and address bytes, are still used because they're inexpensive and easy to do. They're usually found on games and other low-priced software. Even though most copy programs know how to deal with them, some are still hard to beat, particularly nibble counting.

The publishers of more expensive software, however, have deep enough pockets to be able to afford more expensive protection schemes. There are two major high-end methods for protecting disks. Both are expensive because it takes more than just changing a few bytes to get them on a disk. The first involves what are called "weak bits," sectors written in such a way that they don't read the same way twice. All that's needed to activate weak-bit protection is to do two successive reads. If they're the same, the software knows it's running on a copy and can take appropriate action. Getting a sector like that on a disk involves the use of special duplicating equipment; it can't be done with a stock PD765.

Just as weak bits make the disk unique from a formatting point of view, laser holes make it unique from a physical point of view. The word *hole* is misleading because the disk isn't actually punctured, but burned, usually in two different places. The photograph in Fig. 8 shows what to look for if you suspect that the disk you're trying to copy has that kind of protection. The marks are usually located on the back side of the disk near the hub. It's easy for the software to check for the laser holes.

Laser-treated disks are probably the most expensive form of copy protection, but they have one big advantage for a publisher. Because the disk is physically unique, the publisher doesn't have to protect the files and can let you back them up on a regular disk. If you develop an error on the original disk, you can reformat it and copy the files from your backup. Remember that reformatting the disk has no effect on the laser holes. However, most copy programs can even get around laser-treated disks.

Because of the ease of overcoming most disk-based schemes, state-of-the-art copy protection these days is the hardware lock. It's a device that plugs into your serial or parallel port and remains totally transparent (in theory, at least) to the normal operation of the port. Software can check whether the device is present at various times during execution, and come to a screeching halt if it doesn't get the proper response.

References

Books (Apple): *Beneath Apple DOS*, Don Worth & Pieter Lechner, Quality Software, Computer Book Division, 21601 Marilla Street, Chatsworth, CA 91311, (818) 709-1721. *Beneath Apple ProDOS*, Don Worth & Pieter Lechner, Quality Software (address above).

Books (IBM): *The Programmer's Guide to the IBM PC*, Peter Norton, Microsoft Press, Dept. RC06, Box 97200, 10700 Northup Way, Bellevue, WA 98009. *Advanced MS-DOS*, Ray Duncan, Microsoft Press (address above).

Hardware (IBM only): *The Copy II PC Option Board*, Central Point Software, 9700 SW Capitol Highway, Suite 100, Portland, OR 97219, (503) 244-5782.

Software (Apple): *Locksmith 6.0*, Alpha Logic Business Systems, 4119 North Union Road, Woodstock IL, 60098, (815) 568-5166. *Copy II Plus*, Central Point Software, (address above). *Bag of Tricks 2*, Quality Software (address above). *Disk Repair Kit*, Penguin Software, 830 4th Avenue, P.O. Box 311, Geneva, IL 60134, (312) 232-1984.

Software (IBM): *Copy II PC*, Central Point Software (address above). *Master Key*, Sharpe Systems, Corp., 2320 E. Street, La Verne, CA 91750, (714) 596-0070. *CopyWrite*, Quaid Software Limited, 45 Charles Street East, Department 740, Third Floor, Toronto, Ontario M4Y 1S2, (416) 961-8243.

However, hardware locks are very expensive, so it's unlikely you'll see one protecting inexpensive software. Can a hardware lock be beaten? The answer is yes—sort of. The qualifier is there because, no matter what kind of protection scheme is employed, it only protects the disk, not the data. All the fancy tricks that have been used to lock up the software fall away when the program is loaded into the computer.

Your own copy protection

Several of the books mentioned in the References sidebar contain complete discussions and disassemblies of various versions of Apple DOS. By studying that information, you'll see that there are several ways to alter DOS and add simple copy protection to your own disks. DOS commands can be changed (or eliminated altogether), or your own code can be inserted in one of the unused areas of DOS. Then, when your program goes looking for it, if the code is there, the program will run normally. If it's not there—well, the choice is yours. You could be kind and just reboot the system, or you could be nasty and trash a couple of tracks.

If you're interested in playing with a modified disk organization, initialize a spare disk and run the program shown in Listing 1. It will create a diskette with the catalog located in a non-standard location.

To create a custom version of DOS, you can play with the ideas shown in the sidebar entitled *Playing With DOS*. However, just remember that those are fairly simple schemes, and they'll be no real obstacle to someone whose primary mission in life is to get a look at your code. The kinds of things you can do by messing around with DOS are the things a real "crack-ist" eats for lunch.

continued on page 102

BUILD THE PT-68K

Address decoders, RAM, and ROM.

PETER A. STARK, STARK SOFTWARE SYSTEMS CORPORATION



© 1987, Peter A. Stark

PART 4 In last month's installment, we described the 68000 microprocessor and got it running. This time we continue with the address decoders, RAM, and ROM. We'll assume that the jumpers we installed last time are still installed; don't remove those jumpers until you are told to do so. (One jumper connects pins 14 and 22 of IC47, to negate the 68000's \overline{BERR} line, and one connects pins 1 and 14 of IC66, to assert the 68000's \overline{DTACK} line.) In addition, the data bus should still be grounded via the two sets of Molex pins installed in the sockets for IC21 and IC27.

Step 8: Address decoding

Before building the address decoder, we need to develop the \overline{MAP} signal, which provides one input to the decoder. When the 68000 starts operating after power is applied or after a reset, it must know (a) where to place its stack, and (b) where to start executing instruction. It looks for those in the first eight bytes of memory, starting at address \$000000.

The problem is that in most 68000 computers address \$000000 is in RAM, and that RAM will contain random values after the computer is first turned on. So how and

where does the 68000 find the appropriate addresses? The usual solution is to set up the address decoder so that ROM, not RAM, occupies address \$000000 and beyond. The trick is that the ROM remains there just long enough for the 68000 to get its two addresses, after which the ROM is switched out of and the RAM is switched into the low-order addresses. A ROM of that type is often called a *phantom ROM* or a *shadow ROM* because it's seemingly there and then gone. The circuit in Fig. 1 implements the ROM-switching function.

IC90 is an eight-stage shift register. When power is first applied to the computer, and each time it is reset, all the flip-flops in IC90 are cleared by the \overline{RESET} signal. The output of the fourth stage (QD), which is jumpered through J25, then provides a low \overline{MAP} signal that tells the address decoder to put the ROM at address \$000000.

When the 68000 starts, it fetches the stack address and the program start address from ROM in four 16-bit reads; each read is accompanied by an address strobe (\overline{AS}). The positive (trailing) edge of each \overline{AS} then clocks IC90. Since both shift register inputs are tied high, each clock pulse shifts a high further into the register. After the first clock pulse, that high gets to QA; after the second pulse it gets to QB; and so on. After the fourth pulse it gets to QD and negates \overline{MAP} , which tells the address decoder to disconnect the ROM from address \$000000 and substitute RAM.

Now that we understand how the circuit actually works, let's build it and verify that it works. First install a socket for IC90 and a three-pin header block at J25. Insert the IC and place a shorting plug over position 1 of J25. (IC66 was installed in a previous step.) Turn on the power and verify that the \overline{MAP} signal on the center pin of J25 goes low while you short the reset pins (J23), and that it goes high about a second later, at the same time as the HALT LED goes off. (Unless you have a high-quality oscilloscope, it may be difficult to verify that exactly four \overline{AS} pulses go by before \overline{MAP} goes high, so you'll have to take it on faith that the circuit is functional.)

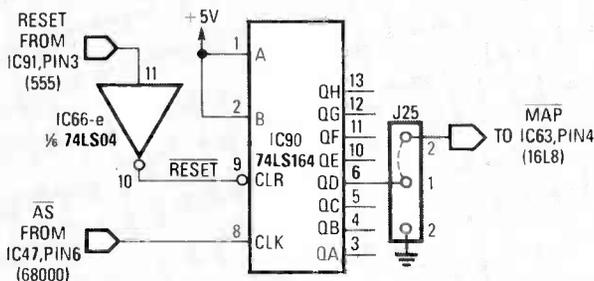


FIG. 1—THIS CIRCUIT GENERATES THE \overline{MAP} SIGNAL that forces the microprocessor to address ROM rather than RAM at power up and on subsequent resets.

JANUARY 1988

95

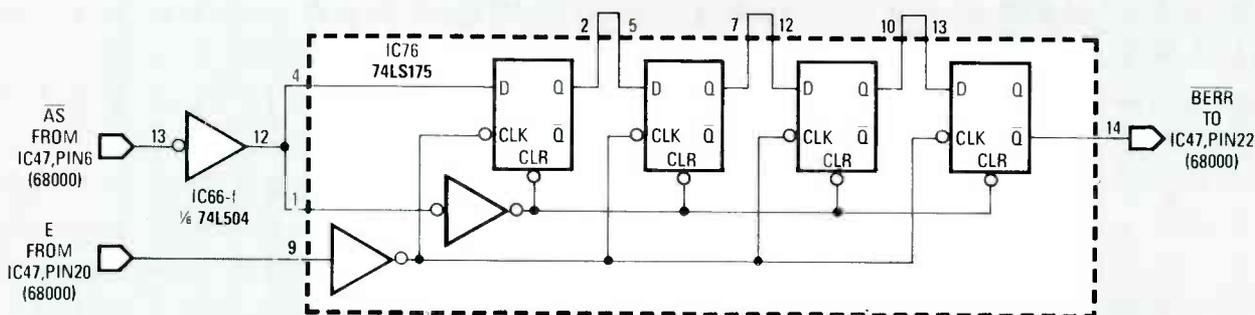


FIG. 2—A BUS ERROR (BERR) IS GENERATED if the address strobe (AS) continues through four E cycles without a data acknowledge (DTACK).

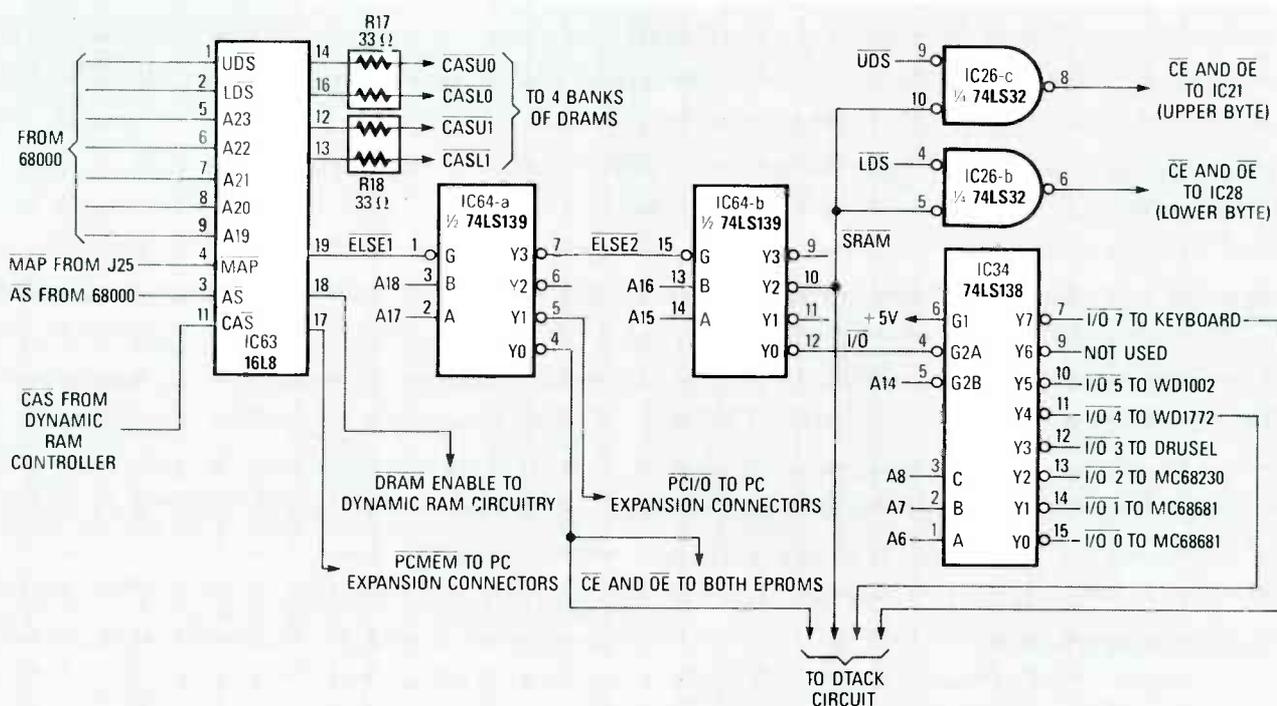


FIG. 3—ALL ADDRESS DECODING is accomplished by three IC's: each IC (or section thereof) further narrows the range of addresses decoded by its predecessor.

Step 9: The bus error circuit

Each time the 68000 wants to access memory or I/O, it sends out an address; \overline{LDS} , \overline{UDS} , or both; \overline{RW} ; and \overline{AS} . Then it sits back and waits for the memory or I/O to respond. If all goes well, the external circuit should return a low on \overline{DTACK} (data transfer acknowledge); if something goes wrong, it should return a low on \overline{BERR} (bus error).

When using slow memory or I/O, \overline{DTACK} can be used to slow down the 68000; the period of waiting is called a *wait state*. But suppose the 68000 tries—accidentally or otherwise—to access an address at which there is no memory or I/O. What happens then? Since there is nothing to generate \overline{DTACK} , the 68000 might go into a permanent wait state. That's where the bus-error circuit comes in. Its job is to detect the lack of \overline{DTACK} after some period of time, and then generate \overline{BERR} , which forces the 68000 into an error-recovery procedure.

When we first powered the 68000 up last time, we tied \overline{DTACK} low and \overline{BERR} high, which allowed the processor to run at maximum speed, and made it think that a bus error never occurred. Since we are still providing a fake \overline{DTACK} , the 68000 will go full-speed ahead, even though there is no memory in the system yet. However, we may as well install the \overline{BERR} circuit at this time.

The circuit shown in Fig. 2 looks complex, but actually it consists of just one new part: IC76, a 74LS175 quad D flip-flop. (IC66 was installed in a previous step.)

The four flip-flops are configured as a four-stage shift register that is driven by the 68000's E clock. That signal operates at one tenth the speed of μPCLK , or 800 kHz if the main clock is 8 MHz.

The input data comes from \overline{AS} , which is also connected to IC76's CLEAR pin. When the 68000 starts a memory or I/O access, it asserts \overline{AS} , which simultaneously negates IC76's

BUBBLES AND GATES

A given signal in a digital system can be either active high or active low; the signal's name often indicates which. For example, \overline{DTACK} is active low, and we know it as such because of the bar over the name. F_{CO} , on the other hand, is active high because it has no bar above it.

One way to mark a signal in a schematic diagram is with a bubble, which is simply a small circle at the end of a connecting line. Bubbles are a notational convention that, when used properly, can help prevent design errors. The basic idea is that active-high outputs can only go to active-high inputs; likewise with active-low signals. Many engineers and technicians tend to get careless with bubbles, so diagrams can't always be trusted. However, when properly used, bubbles can be very helpful. Look at Fig. 1 for a simple example; the circuit shown there is the Halt indicator discussed in an earlier installment.

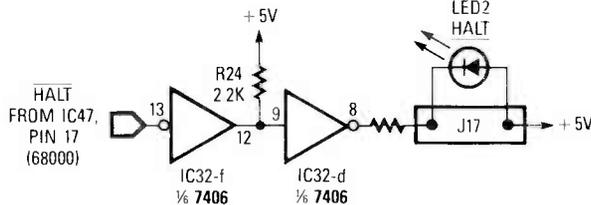


FIG. 1

The \overline{HALT} signal comes from pin 17 of the 68000 microprocessor; that signal goes low when the 68000 is halted. As stated above, an active-low output must go to an active-low input, so you'll notice a bubble on the input (pin 13) of IC32-f. The output of that inverter is active high, so it goes to an active-high input, IC32-d. The output of that inverter is active low, so we would expect that the LED would light when that output was low, and that is indeed the case.

It's important to understand that IC32d and IC32f are functionally identical—they're both open-collector inverters—even though their symbols are different.

The same principles can be applied to all the basic logic elements, as shown in Fig. 2. Each pair in that diagram is equivalent. For example, the gate on the left in Fig. 2-a is normally called an AND gate; described in words, its job is to "make the output high if input A is high and input B is high."

There is another way of describing its operation: If either input is low, then the output is low. So we could say "make the output low if A is low or B is low." That sounds like an OR gate that works with low-going signals—and that's what the gate on the right in Fig. 2-a shows.

CLR input and asserts its D input. Then, each time an E clock signal arrives, that high is shifted one stage to the right. If the \overline{AS} signal continues through four E cycles (about 4–5 microseconds), the last flip-flop will set, and \overline{BERR} will go low, informing the 68000 that too much time has passed since the memory or I/O access started. At that point a special interrupt occurs, and a software routine must decide what to do next.

Building the circuit is easy. First remove the jumper that was installed between pins 14 and 22 of IC47. (That jumper forced \overline{BERR} high.) Next install a socket for IC76, and then the IC (a 74LS175).

Testing is almost as easy. Using the LED probe, look at pins 4 and 9 of IC76. Because \overline{AS} and E are both square waves, and are on about 50% of the time, the LED should glow at about half brightness. Then look at pin 2, the Q output of the first flip-flop. \overline{AS} and E are not in any particular phase relationship, so the first flip-flop will trigger

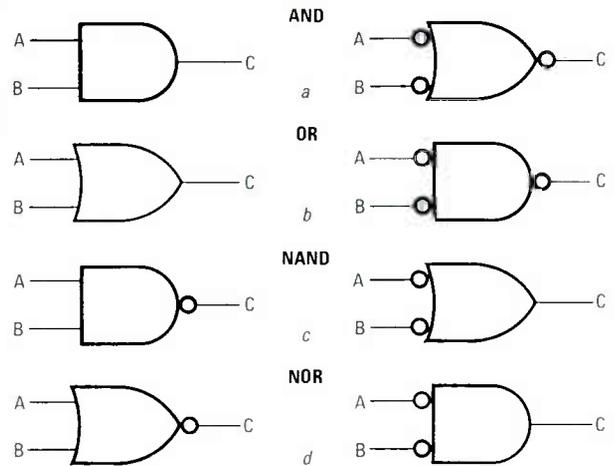


FIG. 2

You can convert from one form to the other by negating all terms on both sides of a logic equation. Highs become lows and vice versa, AND's become OR's and vice versa, and NAND's become NOR's and vice versa. So

$$A \text{ AND } B = C$$

becomes

$$\overline{A} \text{ OR } \overline{B} = \overline{C}$$

A designer might use either symbol for the same device, depending on what a particular circuit is supposed to do. Parts manuals, for example, usually describe gates in terms of the "positive logic" function—the symbols on the left in Fig. 2. The 7408, for example, may be described as a "quadruple two-input positive-AND gate." That means the 7408 has four two-input gates, each of which functions as a normal AND gate. However, the 7408 could just as well be called a "quadruple two-input negative-OR gate."

Similarly, Fig. 2-b shows a positive-logic OR gate on the left, and a negative-logic AND gate on the right. In reality, both functions could be provided by the same IC (a 7432).

A real-life example is the \overline{DTACK} generator shown in Fig. 5 of this installment. Note IC36—it's normally described as an eight-input NAND gate, but here it functions as an eight-input NOR gate.

All of that may sound strange, but as we go on, you'll see that the new symbols we've outlined here will help explain how the PT-68K computer works.

once every few \overline{AS} cycles, but it will never stay on for very long. Therefore, the flip-flop is mostly off, so the LED should be quite dim. The other flip-flops never get a chance to set, so the LED should remain dark when testing any of the other Q outputs. \overline{BERR} , of course, is high all the time, so the LED should be bright when testing pin 14.

Step 10: The address decoder

As described way back in the first part of this series, the address decoder continuously monitors the high order bits of the address bus and signals the RAM, the ROM, and the I/O interfaces whenever an address comes along that is intended for them. The PT-68K's address decoder consists of three IC's, as shown in Fig. 3.

The heart of the decoder is IC63, a 16L8 PLD (programmable logic device). A PLD is like a fast ROM in that it has a number of input and output lines. Each time a combination of ones and zeroes is presented to its input lines, the

PLD outputs a number that is stored in the corresponding location in its internal memory.

By the way, there are significant differences between a ROM and a PLD. The ROM is more complex than the PLD because it can store more information; but, being simpler, the PLD can run faster. In general, the ROM is meant to store numbers, and the PLD is meant to replace logic IC's. In our case, the PLD replaces almost a dozen gates and inverters, thereby saving both space and money.

The PLD functions as follows. It splits the sixteen-mega-byte address space of the computer into three areas:

- \$000000–\$0FFFFFF, system DRAM
- \$C00000–\$DFFFFFF, PC-compatible slots
- \$F80000–\$FFFFFF, everything else

Any other address simply isn't recognized by the address decoder. Now let's examine the details of how the circuit actually works.

1. If \overline{AS} is negated (high), the PLD does nothing; \overline{AS} must be low to ensure that a valid address exists.

2. If address lines A20–A23 are low, representing addresses \$000000 through \$0FFFFFF (i. e., the first megabyte of memory, where the system DRAM resides), pin 18 (\overline{DRAM}) is asserted. In addition, if \overline{CAS} is low, indicating that the DRAM refresh circuitry wants to access a column of DRAM, IC63 asserts one or two of the \overline{CAS} outputs (pins 12, 13, 14, and 16), which in turn activate a group of dynamic RAM IC's. \overline{UDS} and \overline{LDS} determine whether to assert one of the lower (\overline{CASL}) outputs, one of the upper (\overline{CASU}) outputs, or both, depending on whether an odd byte, an even byte, or a sixteen-bit word is to be accessed. Meanwhile, the A19 input of IC63 splits the DRAM megabyte into lower and upper 512K groups.

Incidentally, the four resistors, parts of 33-ohm resistor packs R17 and R18, slow the rise and fall times of those signals. Each \overline{CASL} and \overline{CASU} signal goes to eight DRAM IC's, and the fast rise and fall times cause sharp signal edges, which contribute to noise in the memory. The resistors reduce that noise and thereby improve reliability.

3. If the three high-order bits of the address bus are 110, representing all addresses beginning with a hex C (1100) or hex D (1101), \overline{PCMEM} is asserted. That signal goes to the six PC-compatible expansion connectors for accessing memory on plug-in cards.

4. If the five high-order address lines are high, representing all addresses between \$F80000 and \$FFFFFF, $\overline{ELSE1}$ is asserted; that signal implies that the chosen address contains something besides system RAM or memory in an expansion slot.

5. Operation is different when \overline{MAP} is low; then the DRAM is disabled and $\overline{ELSE1}$ signal is asserted instead. That maps the ROM instead of the RAM into address \$000000.

I/O decoding

When $\overline{ELSE1}$ is low, the address space from \$F80000–\$FFFFFF is divided into three groups by IC64-a, according to the states of A18 and A17. When the \overline{B} input of IC64 is asserted, one output is asserted according to the binary states of the A and B inputs. For example, the $\overline{V0}$ output is asserted when both inputs are low.

1. When A18 and A17 are 00, which occurs for addresses \$F80000–\$F9FFFF, IC64-a asserts the \overline{CE} and \overline{OE} signals for both EPROM's, thereby enabling them.

2. When A18 and A17 are 01, which occurs for address \$FA0000–\$FBFFFF, IC64-a asserts $\overline{PC1/0}$, which goes to the

WHAT'S IT ALL ABOUT?

The computer described in this series of articles is based on Motorola's 68000 microprocessor, which is also used in a number of personal computers (including the Macintosh, the Atari ST, the Commodore Amiga) engineering workstations, and laser printers. The computer, dubbed the PT-68K, will not run software designed for the IBM PC—at least not yet. But it will accept PC hardware, including keyboard, video display card, monitor, I/O ports, etc.

The PT-68K has a monitor program (HUMBUG) and a version of BASIC, both of which are contained in on-board EPROM. By adding a disk drive and the appropriate control circuitry, the computer will run the SK'DOS operating system, which includes an editor, an assembler, numerous utilities, and a 6809 emulator, which allows you to run much already written 6809 software. In addition, development of a full C compiler and an extended BASIC are nearly complete, and several firms have announced products including a full-screen editor, a disassembler, a communications program, and more. Up-to-date information on software and hardware is available from the SK'DOS BBS (914-241-3307). Technical support is also available there.

The PT-68K motherboard is the same size and shape as an IBM PC XT motherboard, so it may be mounted in an inexpensive clone cabinet. In addition, the PT-68K may be powered by an inexpensive PC clone power supply. Either a serial terminal, or a personal computer running a terminal emulator, or an IBM monochrome adapter card, monitor, and keyboard may be used to communicate with the PT-68K.

Presently we are looking into the possibility of designing or adapting a plug-in card that would contain an Intel microprocessor and would allow you to run PC software on your PT-68K. Right now, it looks very promising, and we'll keep you up to date on our progress.

six PC-compatible expansion connectors for accessing port-mapped I/O on plug-in cards.

3. When A18 and A17 are 10, which occurs for address \$FF0000–\$FDFFFF, IC64-a asserts its $\overline{V2}$ output, which is unconnected.

4. When A18 and A17 are 11, which occurs for address \$FE0000–\$FFFFFF, IC64-a asserts $\overline{ELSE2}$, which enables another decoder, IC64-b. So, as you can see, each IC in the address-decoding chain uses the output of its predecessor in the chain to narrow down the range of addresses it recognizes. In this case, IC64-b splits the \$FE0000–\$FFFFFF range into two smaller groups, depending on address lines A16 and A15.

1. If A16 and A15 are 00, which occurs for addresses \$FE0000–\$FE7FFF, IC64-b asserts $\overline{V0}$, which drives IC34.

2. If A16 and A15 are 10, which occurs for addresses \$FF0000–\$FF7FFF, IC64-b asserts \overline{SRAM} , which drives the static RAM and the clock/calendar via IC26-b and IC26-c. (The RAM circuit was shown in Fig. 3 in the December installment.) Note that \overline{UDS} and \overline{LDS} are combined with \overline{SRAM} to enable the upper byte (IC21), the lower byte (IC28), or both. For example, when both \overline{UDS} and \overline{SRAM} are asserted, the \overline{CE} and \overline{OE} pins of IC21 will be asserted, and the IC will be enabled.

ERROR CORRECTIONS

- The parts list presented in the October issue listed an incorrect part number for IC28: the correct number is 74S74.
- Several parts were inadvertently omitted from the parts list, including LED1–LED3, SPKR1, and 0.1 μ F bypass capacitors C69–C73.
- The parts-placement diagram (Fig. 3 in the November installment) was printed upside down, so references in the text will be rotated 180° from the true position. However, all locations on the board are labeled correctly.

3. The 01 and 11 states of A16 and A15 are not used.

That brings us to IC34, the last IC in the address-decoding chain. IC34's job is to decode addresses of the seven on-board system I/O devices: the two MC68681 DUART (dual UART) serial IC's, the MC68230 parallel port, a drive select latch that controls the floppy-disk drive, the WD1772 floppy-disk controller IC, an optional WD1002 hard-disk controller, and the PC-compatible keyboard. As stated above, IC34 is enabled by the $\overline{I/O}$ signal that is asserted for addresses \$FE0000–\$FE7FFF. In addition, IC34 requires a low (at its \overline{en} input) from A14, so it only responds to the 16K of addresses in the range from \$FE0000–\$FE3FFF. Then it decodes address lines A6–A8, asserting one of the $\overline{y0}$ – $\overline{y7}$ outputs. For example, when A8, A7, and A6 are 000, IC34 asserts the $\overline{y0}$ line, which enables the first DUART.

Now comes a difficult question: What is the range of addresses that the DUART responds to? Following the circuit from left to right, we see that, for $\overline{y0}$ to be low:

- A23 through A19 must be 11000
- A18 through A14 must be 00000
- A13 through A9 are unknown
- A8 through A6 must be 000
- A5 through A0 are unknown.

It's evident that the address decoder does not really look at all the bits of the address bus—there are eleven bits that are unaccounted for (or ten bits when we realize that A0 doesn't exist.) Let's ignore A0–A5 for the moment; A9–A13 are the problem.

Grouping those bits left to right by fours, they look like this:

1111 1110 00xx xxx0 00yy yyyy

Each of the five unknown bits corresponding to A9–A13 is labeled with an x; each of the six unknown bits corresponding to A0–A5 is labeled with a y. Each x and y bit could be either a zero or a one; first let's assume that all the x bits are zeroes:

1111 1110 0000 0000 00yy yyyy

Converting to hexadecimal, the first four digits are clearly \$F800. If the y bits are all zeroes, then the last two digits are \$00; if they are all ones, then the last two digits are \$3F. That tells us that the DUART is addressed from \$F80000–\$F8003F, a total of 64 locations.

But the x digits need not all be zeroes; they could just as well be 00001, which would make the complete address look like this:

1111 1110 0000 0010 00yy yyyy

The first four digits here are \$FE02; again assuming that the y digits can be anything from all zeroes to all ones, that gives us an address range of \$FE0200 through \$FE023F. In a similar manner, we see that the DUART responds to many addresses:

- \$FE0000–\$FE003F
- \$FE0200–\$FE023F
- \$FE0400–\$FE043F
- \$FE0600–\$FE063F
- \$FE0800–\$FE083F
- ... through ...
- \$FE3E00–\$FE3E3F

The latter addresses are decoded when the x bits are all ones.

The preceding is an example of *incomplete address decoding*; it arises because the address decoder does not decode all bits. In fact, the bits that can be either

Ordering Information

Complete details were given in part one (in the October issue). To summarize: The basic kit (PT1, \$200) contains all parts except power supply, case, and video terminal or personal computer to get a small system (ROM monitor, 2K RAM) up and running. The full basic system (PT68K, \$460) includes 512K of dynamic RAM, floppy-disk controller, parallel port, battery-backed clock/calendar, and three PC-compatible expansion slots. To order, or for more information, contact Peripheral Technology, 1480 Terrell Mill Road #870, Marietta, GA 30067, (404) 984-0742.

value are usually called *don't cares*. Incomplete address decoding results in using up more addresses than are actually needed, but it allows the circuitry to be simpler and less expensive. When programming an incompletely decoded device, we usually work with the base location—the 64 locations from \$FE0000–\$FE003F in this particular case.

The EPROM's are also incompletely decoded. As stated above, the EPROM is assigned addresses from \$F80000 through \$F9FFFF, a total of 128K bytes. Typically, however, a pair of 27128's would be used, and they provide a total of only 32K, so 96K of address space is wasted. What actually happens is that the 32K of EPROM appears in the 128K space four times. That is, the EPROM *appears* to occupy the entire 128K, but on closer examination we see that there are four copies of the same data in that space. The loss of that many addresses in an 8-bit computer with a total of 64K of addresses would be unthinkable; in a computer with 16 megabytes of addresses, the loss is insignificant.

The same situation occurs with the I/O. Although each I/O device may only require a few bytes of address space, each takes up 32 64-byte chunks of addresses, for a total of 2048 addresses.

Assemble and test the address decoder

Enough theory; it's time to build the address decoder. Install the following components: IC63 (with socket), R17 and R18 (solder directly to the board), IC64 (with socket), IC34 (with socket), and 0.1 μ F capacitors at C13, C67, C68, and C70. Place the J25 jumper in position 1, recheck all connections, and then apply power.

Although a thorough test of the address decoder would require sophisticated test equipment, we can perform a simple test with the aid of Fig. 4, which shows the waveforms output by the decoder circuit.

As you recall from last time, while our test circuit is wired up (i. e., the data bus is shorted to ground) the 68000 executes what it thinks are four million OR instructions, looping through the entire 16-megabyte memory space once every four seconds. Figure 4 shows what happens at several key points. During those four seconds the 68000 counts up through 16 megabytes of memory. The left edge of the figure corresponds to memory location \$000000, the right edge (just before the pulses) to location \$FFFFFF. The pulses at the extreme right end of the figure indicate the beginning of the next four-second cycle.

First let's look at the \overline{DRAM} signal. Since dynamic RAM occupies the first megabyte of addresses, the \overline{DRAM} signal

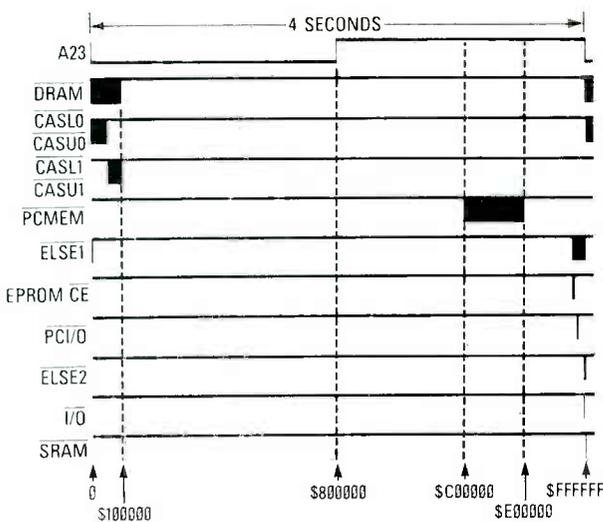


FIG. 4—VARIOUS OUTPUTS OF THE ADDRESS DECODER are shown here; these waveforms will be seen only with the test circuit (shorted data bus, etc.) installed.

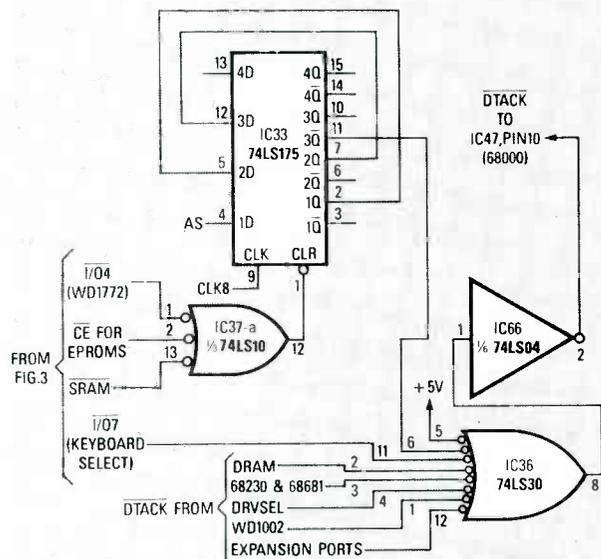


FIG. 5—THE DTACK GENERATOR is similar to the BERR circuit shown in Fig. 2. Here, however, the shift register (IC33) prevents the computer from locking up should a memory or I/O device not supply a data acknowledge.

goes low for the first 1/16th of the four-second cycle, or 1/4 second. The \overline{DRAM} signal does not remain low for the entire 1/4 second, however, and that's why it's shown as a solid block in Fig. 4. It doesn't stay low because, like all other signals in the address decoder, \overline{DRAM} is asserted only when the \overline{AS} is asserted. Because \overline{AS} rapidly cycles between high and low, so does \overline{DRAM} .

You can verify that with a good-quality scope; you should see a continuous high, with a short burst of pulses once every four seconds. Without a scope, you can connect your LED probe to \overline{DRAM} (at pin 18 of IC63). The LED should remain on continuously (because the signal is normally high), but once every four seconds, the LED will get slightly dimmer for about a quarter of a second.

Each of the other address-decoder outputs can be checked in the same way, except for the four \overline{CAS} outputs,

which will show a constant high because we have not yet supplied a \overline{CAS} input to IC63. Some of the other outputs will remain on for a longer period of time—such as \overline{PCMEM} , which will dim the LED for about 1/2 second—but most will be much shorter. The $\overline{I/O}$ and \overline{SRAM} outputs will be very difficult to see since they last only about ten milliseconds, just barely long enough to flicker the LED if you watch carefully. The outputs of IC34 are too short to be able to see on the LED, although a pulse-catching logic probe or oscilloscope will show a slight flicker once every four seconds.

Step 11: The data acknowledge circuit

Previously we generated an artificial \overline{DTACK} with a jumper; now it's time to install the real \overline{DTACK} circuit and see how it works.

Ideally, every device, whether memory or I/O, should generate its own \overline{DTACK} when it finishes an operation. The 68000 would then know that it was time to continue. That is practical in some circuits (DRAM and some I/O devices, for example), but in others a timer is required; the timer just waits for a period time and then generates \overline{DTACK} , assuming all is well. However, the PT-68K system uses both approaches.

Fig. 5 shows the \overline{DTACK} generator circuit. It has eleven inputs, of which two (\overline{AS} and $\overline{CLK8}$) are used for timing.

Four other inputs ($\overline{I/O4}$, $\overline{I/O7}$, the EPROM \overline{CE} signal, and \overline{SRAM}) come directly from the address decoder in Fig. 5. $\overline{I/O4}$ goes low whenever the address decoder enables the WD1772 floppy-disk controller; \overline{CE} goes low when either EPROM is selected; and \overline{SRAM} goes low when the static RAM is selected.

Whenever $\overline{I/O4}$, \overline{CE} , or \overline{SRAM} goes low, IC37-a provides a high to the \overline{CLR} input of IC33, a quad D flip-flop, which is configured like IC76 in Fig. 2. IC33 is clocked by $\overline{CLK8}$, the 8-MHz clock signal. The output of IC37-a is usually low, so its four flip-flops are usually in the reset state. Therefore, the $\overline{3Q}$ output is usually high.

Now suppose that the floppy-disk controller, the EPROM, or the static RAM is decoded. The output of IC37-a will go high, release IC33's \overline{CLR} signal, and allow it to start shifting. \overline{AS} is high at that point, and that high starts shifting through the flip-flops. After three $\overline{CLK8}$ pulses, $\overline{3Q}$ goes low, which sends the output of IC36 high, and the output of IC66-a low, thereby generating \overline{DTACK} . In other words, IC36 acts as a delay. Note that it is clocked by $\overline{CLK8}$, not $\overline{MPUCCLK}$. Even if you speed up the computer by using a faster $\overline{MPUCCLK}$, IC33's delay will not change.

Now let's look at IC36. When any of its inputs goes low, its output goes high. One input (pin 5) is not used, so it is tied high. Of the remaining inputs, one comes from IC33, as we saw above; one comes from the keyboard select line ($\overline{I/O7}$); and the other five come from other parts of the computer that we'll discuss (and build) in a later installment of this series.

For now, just understand that each of the other sections generates its own data-acknowledge signal, all of which are combined at IC36. In addition, the keyboard circuit operates very fast, so $\overline{I/O7}$, its select signal, immediately generates its own data-acknowledge signal.

To build the \overline{DTACK} circuit, first remove the jumper between pins 1 and 14 of IC66. Then install IC33 and IC36 (with sockets). IC37 and IC66 were installed previously; J25 should still be in position 1 from the previous step;

and the Molex pins should still be inserted in the EPROM sockets (IC21 and IC27). Now turn on the power and let's see what happens.

Nothing! Well, of course not. The problem is that the 68000 is still trying to execute four million OR instructions. It's still getting them from the Molex pins, but it's not getting \overline{DTACK} . Hence the \overline{BERR} circuit is timing out and halting everything. You probably noticed that the HALT LED goes on and never even flickers.

Now move the jumper at J25 from position 1 to position 2 and try again; you will see a slight flicker on the HALT LED about a second after you turn on the power (or force a reset by shorting J23), but it still goes on.

The Molex pins in IC21 and IC27 put all zeroes on the data bus, so the address that the 68000 picks up after a reset is also all zeroes. Therefore it starts to execute instructions at address \$000000.

With J25 in position 1, low memory is supposed to be dynamic RAM, but because there isn't any, IC36 gets no data acknowledge, so the 68000 quits with a bus error almost immediately after reset. With J25 in position 2, however, the EPROM is supposed to be mapped into low memory. There isn't any EPROM, of course, but the address decoder and the \overline{DTACK} generator don't know that; hence they generate \overline{DTACK} as if the EPROM were there. The 68000, therefore, executes the OR program until it passes the highest EPROM address, after which \overline{DTACK} disappears, and the system halts on a bus error.

Step 12: ROM and RAM

The circuitry for the EPROM and the static RAM was shown in Fig. 3 of the December installment. The 68000's data bus is 16 bits wide, but no one makes EPROM's or RAM's that have 16 data lines. The solution is to use two 8-bit-wide EPROM's and two 8-bit-wide static RAM's.

Three kinds of EPROM's can be used, but both EPROM's of a pair must be the same type. Two 27128's hold 32K bytes; two 27256's hold 64K bytes; and two 27512's holds 128K bytes. 27128's have enough capacity to hold our machine-language monitor (HUMBUG) and BASIC, but the prices on memory IC's are so unstable that kits may contain any of those, depending on current market conditions. Jumpers J19 and J20 are used to select the type of EPROM that is being used.

The static RAM's are pair of 6116's, which provide a total of 4K bytes of memory. But it is possible to replace one—or both—with a Mostek MK48T02, which has the same pinout as a 6116, but which also contains some RAM and two additional features: a clock/calendar (whose registers replace the top eight locations of the RAM), and a lithium battery that powers both the clock and the RAM when the computer is turned off. The battery is rated for at least 31,000 hours of operation, or slightly more than 3½ years. In actual use, it should last longer, because the battery powers the clock only when the computer is off. (Note that the MK48T02, if used, must be inserted into the IC28 socket, because the clock software in SK*DOS expects to find the IC in the lower byte.)

Integrated circuits IC20 and IC21 handle the upper eight bits of the data bus, and IC27 and IC28 handle the lower eight bits. That division may be confusing and hence needs explanation. When the 68000 stores a word (two bytes) from an internal register into memory, the left byte (also called the more significant byte, or the upper

byte) goes into memory first, and is always in an even-numbered location. The right byte (also called the least significant byte, or the lower byte) is stored in the next available memory location, an odd number. For example, the number \$1234 might be stored as \$12 in location \$3500 and \$34 in location \$3501. That arrangement is logical, but it is confusing for two reasons: (1) the upper byte is actually stored in the lower address, and (2) other microprocessors (particularly those in the Intel family) store words in the opposite order. \$1234 would be stored in sequential locations as \$34 followed by \$12.

Further complicating things is the fact that both EPROM's are controlled by the same \overline{CE} (chip enable) and \overline{OE} (output enable) signals, whereas there are separate enable signals for each of the static RAM's. Reading both EPROM's simultaneously does no harm; if the 68000 only wants one byte, it simply ignores the other half of the data bus. But writing to the static RAM requires two control lines to make sure that writing to one RAM does not inadvertently store unwanted data in the other.

Note also the difference between \overline{CE} and \overline{OE} —when RAM or EPROM is read, \overline{CE} enables the IC and starts the read process, but data does not appear on the bus until \overline{OE} is asserted. In many systems, \overline{CE} is used to put the entire chip into a low-power mode when it is not being accessed. In the PT-68K we control both lines together so the IC switches into low-power mode after every access.

Earlier we said that there is no A0 on the address bus; now let's see how the system gets by without it. Consider the static RAM, for example, which starts at \$FF0000. Memory locations are located in specific IC's as follows. All the even addresses are stored sequentially in IC21 (\$FF0000 is in location 0, \$FF0002 is in location 1, \$FF0004 is in location 2, etc.), and all the odd addresses are stored sequentially in IC28 (\$FF0001 is in location 0, \$FF0003 is in location 1, etc.).

The address lines are shifted by one bit because shifting a binary number to the right by one bit divides the number by two. For example, location \$FF0008 ends with the bits 1000; physically, that byte would be located in address 0100 (i.e., address 4) of IC21. Location \$FF0009, on the other hand, ends with the bits 1001; it would also be in location 0100, but in IC28. So the last bit of an address tells us which IC it is stored in.

Now that we understand how the EPROM and static RAM circuitry works, let's connect it. Remove the Molex pins from the IC21 and IC27 sockets, and install the following components: a socket for IC26 (74LS32), C12 and C66 (0.1 μ F), sockets for IC21 and IC28 (EPROM's), and three-pin header strips at J19 and J20.

Then install the EPROM marked *Upper* in IC20 and the EPROM marked *Lower* in IC27, and then the two 6116 static RAM's in IC21 and IC28. Before turning on the power, make sure that the jumpers are positioned correctly, according to the chart shown in Fig. 3 last time. Also, place jumper J18 in position 2 to address the EPROM at location \$000000. Now turn on the power.

If all is well, the HALT LED should go off after about a second. If it does, that's a pretty good sign that there are no serious problems, even though the computer is still not fully operational. If it doesn't, recheck all connections and parts installed since last time.

For more confidence, use the LED probe to check a few
continued on page 102

FLOPPY-DISK DATA STORAGE

continued from page 94

Breaking copy protection

Copy protection—both making it and breaking it—is big business. There are two fundamental ways to get around copy protection. The first is to buy a program that knows how to copy protected disks. If you're lucky, it will know how to make sense of the particular protection scheme(s) used on your disk and will be able to copy it with no muss and no fuss. But the price you pay for that kind of mindless copying is that, if the program can't copy the disk, there isn't a thing you can do except try some other copy program.

The second method is to use some disk tools to snoop through the disk and remove the copy protection yourself. As with most things, each method has advantages and disadvantages. The method you choose depends on how good your tools are, how well you can use them, how much you know about your computer, how much time you want to spend, and how badly you want to make the copy.

There's simply not space to go into the details of how to break copy protection; it's an art in itself. Basically, it involves spending endless hours at a totally unnatural act: staring at and trying to decipher page after page of undocumented object code. Unless you've actually done it, there just aren't any words to describe the amount of work involved.

One reason is that the code you'll be looking at probably was written to be confusing. The code in Listing 2 is a perfect example. Go through it and see whether you can

understand what's going on. It's real code from a popular Apple game. There are no tricks here, either. It's just that things aren't what they seem to be. The real meaning (and the real code) is hidden. If you figure it out, drop us a note. And if there's enough response, we'll take up the subject of copy breaking in another article.

If you want to learn about the in's and out's of copy protection, you'll have to get familiar with the normal workings of the standard DOS used by your computer. Read the books mentioned in the References sidebar, and follow their tutorials. Those books won't tell you how to break copy protection, but they'll give you the basic tools you need to do so.

If you just want to back up your copy-protected (IBM) software, try the Option Board from Central Point Software. It's the ultimate tool for dealing with disks on a bits-and-bytes level, and it also helps copy "un-copyable" software. All the screen dumps in this article were produced using the Option Board, which also reads disks formatted on just about any computer, including IBM, CP/M, and even the Apple! That's a major accomplishment—especially for a \$100 piece of hardware.

You'll also find a list of some good copy programs in the References sidebar; you should have some of them in your library even if you don't need to copy protected disks. Whenever you get a floppy-disk data error, chances are what has happened is that at least one sector was written incorrectly. All it takes is one bad bit in a header and the sector will be unreadable by DOS. If the damage is in the directory, you'll be unable to access any of the data and will be faced with the thankless job of trying to reconstruct your files. The point is that many programs capable of dealing with protected disks can deal with damaged disks as well. ♦♦♦

BUILD THE PT-68K

continued from page 101

signals. First, all data-bus lines should have pulses. Likewise, address lines A1–A18 should have lots of pulses, but A19–A23 should not dim the LED at all. If HUMBUG (the EPROM monitor) is running, it is accessing mostly EPROM locations \$F80000 and above, and static RAM locations \$FF0000 and above. Since the first five bits of both \$F8 and \$FF are 11111, the LED probe should indicate a high when it is connected to each line.

You can also test the outputs of the address decoder. You should note many pulses on pin 19 of IC63, which decodes all addresses above \$F80000. You should also see pulses on IC64, pin 4 (which selects the EPROM), pin 7 (which drives IC64-b), and pin 10 (which selects the static RAM.)

What you can't see on the LED (although you can on a good scope) are very brief pulses on the high-order address lines. The 68000 is trying to access error vectors (pointers to special software routines) because it senses a bus error due to the fact that no DUART (serial port) is installed. Likewise, you can see brief pulses on IC64, pin 5, as HUMBUG is desperately trying to access the expansion slots in the hope that there is a video board there to report the error on.

Step 13: Running at last!

Now we can finally get the computer to do something useful. Install IC10 (MC68681 DUART) and its socket, 10K resistors R9, R10, R12, R13, and IC3 (3.6864 oscillator) on the board. The pointed corner of the oscillator is pin 1. Last, connect a speaker to J18. The small speaker that comes with PC clone cabinets is best; any other inexpensive speaker will do. Just don't connect one of your stereo system's speakers!

Now turn on the power; about a second later, the HALT LED should go off, and another second later you should hear a beep-boop from the speaker. That's a signal from HUMBUG that it is running, and it's the first indication that there are no serious problems—even the slightest problem occurring would prevent HUMBUG from sounding that dual tone.

Now that a real program is running with no errors, the signals in the address decoder will be slightly different. HUMBUG is currently running a loop that continuously checks for the presence of a keyboard; that loop runs entirely in EPROM and calls the first DUART, so you will see pulses on the $\overline{\text{EPROM}}$ chip-select line, IC64-a, pin 4; the $\overline{\text{I/O}}$ line on IC64-b, pin 12; and the $\overline{\text{I/O}}$ line, IC34, pin 15. You will no longer see pulses on the $\overline{\text{SRAM}}$ chip select line.

Next time we will continue building the I/O section of the PT-68K so we can communicate with it. See you then. ♦♦♦

MARKET CENTER

FOR SALE

REPAIR your own TV...it's easy. Write RESEARCH, Rt. 3, Box 601BR, Colville, WA 99114.

PHOTOVOLTAIC battery chargers by Arco solar Cars, RVs, marine, etc. From \$49.50. Brochure. SUN POWER-TEXAS, P.O. Box 2788A, Freeport, TX 77541.

CLASSIFIED AD ORDER FORM

To run your own classified ad, put one word on each of the lines below and send this form along with your check to:

Radio-Electronics Classified Ads, 500-B Bi-County Boulevard, Farmingdale, NY 11735

PLEASE INDICATE in which category of classified advertising you wish your ad to appear. For special headings, there is a surcharge of \$23.00.

() Plans/Kits () Business Opportunities () For Sale
 () Education/Instruction () Wanted () Satellite Television
 ()

Special Category: \$23.00

PLEASE PRINT EACH WORD SEPARATELY, IN BLOCK LETTERS.

(No refunds or credits for typesetting errors can be made unless you clearly print or type your copy.) Rates indicated are for standard style classified ads only. See below for additional charges for special ads. **Minimum: 15 words.**

1	2	3	4	5
6	7	8	9	10
11	12	13	14	15 (\$42.75)
16 (\$45.60)	17 (\$48.45)	18 (\$51.30)	19 (\$54.15)	20 (\$57.00)
21 (\$59.85)	22 (\$62.70)	23 (\$65.55)	24 (\$68.40)	25 (\$71.25)
26 (\$74.10)	27 (\$76.95)	28 (\$79.80)	29 (\$82.65)	30 (\$85.50)
31 (\$88.35)	32 (\$91.10)	33 (\$94.05)	34 (\$96.90)	35 (\$99.75)

We accept MasterCard and Visa for payment of orders. If you wish to use your credit card to pay for your ad fill in the following additional information (Sorry, no telephone orders can be accepted.):

Card Number

Expiration Date

Please Print Name

Signature

IF YOU USE A BOX NUMBER YOU MUST INCLUDE YOUR PERMANENT ADDRESS AND PHONE NUMBER FOR OUR FILES. ADS SUBMITTED WITHOUT THIS INFORMATION WILL NOT BE ACCEPTED.

CLASSIFIED COMMERCIAL RATE: (for firms or individuals offering commercial products or services) \$2.85 per word prepaid (no charge for zip code)...**MINIMUM 15 WORDS.** 5% discount for same ad in 6 issues; 10% discount for same ad in 12 issues within one year if prepaid. **NON-COMMERCIAL RATE:** (for individuals who want to buy or sell a personal item) \$2.30 per word, prepaid...no minimum. **ONLY FIRST WORD AND NAME** set in bold caps at no extra charge. Additional bold face (not available as all caps) 50¢ per word additional. Entire ad in boldface, \$3.40 per word. **TINT SCREEN BEHIND ENTIRE AD: \$3.55 per word. TINT SCREEN BEHIND ENTIRE AD PLUS ALL BOLD FACE AD: \$4.15 per word. EXPANDED TYPE AD: \$4.30 per word prepaid.** Entire ad in boldface, \$5.15 per word. **TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD: \$5.40 per word. TINT SCREEN BEHIND ENTIRE EXPANDED TYPE AD PLUS ALL BOLD FACE AD: \$6.25 per word. DISPLAY ADS:** 1" x 2 1/4"—\$320.00; 2" x 2 1/4"—\$640.00; 3" x 2 1/4"—\$960.00. **General Information:** Frequency rates and prepayment discounts are available. **ALL COPY SUBJECT TO PUBLISHERS APPROVAL. ADVERTISEMENTS USING P.O. BOX ADDRESS WILL NOT BE ACCEPTED UNTIL ADVERTISER SUPPLIES PUBLISHER WITH PERMANENT ADDRESS AND PHONE NUMBER.** Copy to be in our hands on the 12th of the third month preceding the date of the issue. (i.e., Aug. issue copy must be received by May 12th). When normal closing date falls on Saturday, Sunday or Holiday, issue closes on preceding working day. Send for the classified brochure. Circle Number 49 on the Free Information Card.

RESTRICTED technical information: Electronic surveillance, schematics, locksmithing, covert sciences, hacking, etc. **Huge selection. Free brochure MENTOR-Z,** 135-53 No. Blvd., Flushing, NY 11354.

DESCRAMBLER catalog. All brands. Special combo Jerrold 400 and SB3 \$165. Descrambler kit \$39.00 (assembles in half hour). Send \$1.00. **MJ INDUSTRY,** Box 531, Bronx, NY 10461.

IS it true...Jeeps for \$44 through the government? Call for facts! 1 (312) 742-1142, ext. 4673.

TEST equipment, reconditioned. For sale. \$1.25 for catalog. **WALTER'S,** 2697 Nickel, San Pablo, CA 94806. (415) 724-0587.

TUBES, new, unused. Send self-addressed, stamped envelope for list. **FALA ELECTRONICS,** Box 1376-2, Milwaukee, WI 53201.

CB RADIO OWNERS!

We specialize in a wide variety of technical information, parts and services for CB radios. 10M-FM conversions, repairs, books, plans, kits, high-performance accessories. Our 11th year! Catalog \$2.

CBC INTERNATIONAL, P.O. BOX 31500RE, PHOENIX, AZ 85046

PHOTOFACT folders, under #1400 \$3.00. Others \$5.00. Postpaid. **LOEB,** 414 Chestnut Lane, East Meadow, NY 11554.

TI-99/4A software/hardware bargains. Hard to find items. Huge selection. Fast service. Free catalog. **DYNA,** Box 690, Hicksville, NY 11801.

FLASHLIGHT that needs no batteries measures 5' x 3' ideal for every situation money back guarantee \$10.—**SAMUELS ENTERPRIZES,** 724 East 231 Street, Bronx, NY 10466.

CABLE TV converters. "NEW" Zenith flash, Scientific Atlanta, Jerrold, Oak, Zenith, Hamlin. Many others. "New" video hopper "The Copy Killer." Visa, M/C & Amex 1 (800) 826-7623. **B&B Inc.,** 10517 Upton Circle, Bloomington, MN 55431.

CABLE TV equipment S.A., Jerrold, Zenith, Hamlin, Oak, Eagle filters remotes and more. Best prices C.O.D.'s accepted dealers needed. Ours work where others failed and we guarantee it! **TRANS-WORLD CABLE, Co.** (218) 543-6671.

TUBES 59¢. Year Guarantee. Free catalog. Tube tester \$8.95. **CORNELL,** 4215 University, San Diego, CA 92105.



VIDEO TAPE COPYGUARD

Eliminate the latest copyguard problems
units from \$59⁹⁵ to \$169⁹⁵

Deluxe Electronics (714) 998-6866
1432 Heim Way, Orange, Ca. 92665

CABLE-TV converters and descramblers. Low prices, quality merchandise, we ship C.O.D. Send \$2.00 for catalog. **CABLETRONICS UNLIMITED,** P.O. Box 266, South Weymouth, MA 02190, (617) 843-5191.

STAND-alone Eprom programmers \$225. Free info sheet. **SOLICON,** 8825 El Matador Dr., Gilroy, CA 95020.

SEMICONDUCTOR and transmitting tubes, quotation sent on request. **TSUTOM YOSHIHARA,** C1-105 Deguchicho-34, Suita, Osaka 564, Japan.

TUBES, name brands, new, 80% off list. **KIRBY,** 298 West Carmel Drive, Carmel, IN 46032.

TRANSISTORS-tubes: MRF421 \$24.00, MRF454 \$15.00, MRF455-MRF477 \$12.00, MRF492 \$16.95, SRF2072 \$13.50, 3800 \$18.95, 2SC2879 \$25.00, 6LF6-6LQ6-6JS6 \$10.95, 8950 \$15.95. New **Ranger AR3500** all mode 10 meter transceiver \$319. Quantity discounts! Best prices on hard-to-find parts, antennas, mics, power supplies, & equipment! Catalog \$1.00 (refundable), or free with order **RFPC**, Box 700, San Marcos, CA 92069. For information or same day shipment—call (619) 744-0728. Visa/MC/C.O.D.

SATELLITE & cable equipment. We have those hard to find units ready to go. Tired of junk that don't work properly, try our 10 day satisfaction guarantee & 90 day warranty (wholesale only) **HI TECH ELECTRONICS**, PO Box 42423, Detroit, MI 48242. (313) 722-9381.

LASERS, components and accessories. Free catalog, **M.J. NEAL COMPANY**, 6672 Mallard Court, Orient, OH 43146.

Cable Converters & Decoders

*Jerrold S.B. Add On.....	\$89.00	\$58.00
*Jerrold Tri-Bi Add On.....	\$98.00	\$78.00
Jerrold Starcom CSV.....	\$139.95	Call
MTS Converter + Remote.....	\$85.00	\$69.00
Jerrold 450 DRZ-3A.....	\$95.00	\$79.00
Parental Control MTS Plus.....	\$100.00	\$85.00
Hamlin MLD 1200-3.....	\$98.00	\$58.00
Scientific Atlanta Add On.....	\$140.00	\$99.00
M-35 B Combo With VariSync.....	\$99.00	\$69.00
Mini Code N-12 VariSync.....	\$99.00	\$58.00
442 VariSync (N-12 Substitute).....	\$89.00	\$58.00
Wireless Video Sender.....	\$45.00	Call
*S.B. TRI-BI Flashing Got You Down? Try original Jerrold Equipment it might just solve your problems. Call or write for Free Catalog. All products Guaranteed 90 days plus.		
M.D. Electronics 5078 So. 108th Suite 115 Omaha NE 68137 Phone (402) 554-0417		

SURVEILLANCE-counter, security. 202 products: alarms, bulletproof, detectors, to underwater, voice scramblers, wireless! Catalog \$2.00: **SPYPRO**, Dept. 048ER, POB 45521, Seattle, WA 98145-0521.

HACKING, crashing, pirating, and phreaking. Who's doing it, why they're doing it, and how they're doing it. Sample programs, phone numbers, and the tools of the trade. **Hacker's Handbook**, \$12.95. **Computer Underground**, \$14.95, \$1 postage to **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

CATV wholesaler and service center of new digital set top cable converters S.A., Jerrold, Panasonic, Pioneer, Sprucer, Hamlin and coax cable line-amps connectors tools. **REDCOAT ELECTRONICS**. (718) 459-5088.

TUBES: "Oldest," latest." Parts and schematics. **SASE** for list. **STEINMETZ**, 7519 Maplewood Ave., R.E. Hammond, IN 46324.

TELEPHONE tap listen to room and telephone conversations from any **PHONE LISTEN**, 603 Elgin, Musroger, OK 74401. (918) 683-9589.

COMMODORE CHIPS/REPAIRS C-64 repair \$39.95 complete. We sell chips at low cost (eg. 6526/6510-\$9.95 and many others). C-64 P.S. \$27.95. "Commodore Diagnostician," a complete chart for diagnosing faulty IC's \$6.95 + pp. Send for catalog. **VISA/MC. KASARA INC.**, 31 Murray Hill Drive, Spring Valley, NY 10977. (800) 642-7634 (800) 248-2983 (outside NY) or (914) 356-3131.

AIDS? Yes we have! Cable aids to help you. Zenith, Jerrold, Scientific Atlanta, Oak, Hamlins, much more. No Michigan sales! **HOTRONICS**, (313) 283 4299.

AMAZING space age metal. Hundreds of exciting uses. Send **SASE** and \$5.00 for sample and instructions. **BY DESIGN LABORATORIES**, 2754 Lexington Ave., Mansfield, OH 44904.

CABLE descrambler liquidation. Major makes and models available. Industry pricing! (Example: Hamlin Combo's, \$44 each...minimum 10 orders), **dealers only!** Call **WEST COAST ELECTRONICS**, (818) 989-0890.

CABLE TV equipment, specializing in Scientific Atlanta, Jerrold, Oak, Hamlin, and Zenith. Our units have worked where others have failed. **Call toll free 1 (800) 327-3407, or send \$3.00 for catalog to K.D. VIDEO, P.O. Box 29538, MLPS., MN 55429.**

TUBES (radio). New in original cartons. Also many used types. Parts, collectables. **LSASE** for list. **DIERS**, 4276-E3 North 50th Street, Milwaukee, WI 53216-1313.

PLANS AND KITS

HI-FI speaker systems, kits and speaker components from the world's finest manufacturers. For beginners and audiophiles. Free literature. **A&S SPEAKERS**, Box 7462, Denver, CO 80207. (303) 399-8609.

CRYSTAL radio sets, plans, kits, catalog \$1.00. **MIDCO**, 660 North Dixie Highway, Hollywood, FL 33020.

TUBES - 2000 TYPES DISCOUNT PRICES!

Early, hard-to-find, and modern tubes. Also transformers, capacitors and parts for tube equipment. **Send \$2.00 for 20 page wholesale catalog.**

ANTIQUE ELECTRONIC SUPPLY
688 W. First St. • Tempe, AZ 85281 • 602/894-9503

COMPUTER boards for process control. 8051, 8096, 68HC11, and 68008 microprocessors supported. Bare boards or assembled. **EPROM** resident software also available. **ALLEN SYSTEMS**, (614) 488-7122.

TEKTRONIX 545A 24MHz scope. \$125.00 lowest prices test equipment, parts, tubes. Free catalog. **EF ELECTRONICS**, Box 249, Aurora, IL 60507.

HARDWARE AND ELECTRONICS
International Inc.

<p>12" POLY WOOFER Clear polypropylene cone. 65 watts RMS, 11 oz magnet. Ferro fluid cooled 1 1/2" voice coil. Trim ring included. 25-2500 Hz. #290-100 \$15⁹⁵ \$13⁹⁵ (1-3) (4-UP)</p>	<p>8" POLY WOOFER Clear ribbed polypropylene cone. 60 watts RMS, 30 watts max power. 20 oz. magnet. 35-2500 Hz. 4-8 ohm compatible. #290-055 \$20⁹⁵ \$18⁹⁵ (1-3) (4-UP)</p>	<p>15" WOOFER 20 oz. magnet. 60 watts RMS, 90 watts max. 8 ohm impedance. 1 1/2" voice coil. 25-2000 Hz. #290-160 \$30⁹⁵ \$28⁴⁰ (1-3) (4-UP)</p>
<p>PIEZO TWEETER Mfg. #KSN1005A. 3 1/2" x 3 1/2". No crossover required. 50 watts maximum input power. #270-010 \$4⁹⁵ \$3⁹⁵ (1-79) (80-UP)</p>	<p>HORN TWEETER 3" wide dispersion horn tweeter. 1800-15,000 Hz response. 35 watts RMS, 50 watts max. 8 ohm impedance. #270-050 \$6⁵⁰ \$5⁹⁰ (1-9) (10-UP)</p>	<p>5 1/4" CUP MIDRANGE Tuned cup Paper cone, 1" voice coil. 9.3 oz. magnet. 50 watts RMS, 70 watts max. Response. 320-6000 Hz. 8 ohm impedance. #280-020 \$11⁵⁰ \$9⁹⁵ (1-9) (10-UP)</p>
<p>CROSSOVERS</p> <p>2-Way, 30 watt #260-190 \$3⁹⁵ 3-Way, 60 watt #260-200 \$7⁵⁰ 3-Way, 100 watt #260-210 \$12⁵⁰</p>	<p style="text-align: center; font-weight: bold; font-size: 1.2em;">FREE CATALOG</p> <p>Call or write today for your free catalog containing speakers, semi-conductors, CATV products, tools, hardware, TV-VCR parts, and more.</p>	

CALL TOLL FREE
1-800-255-3525

In Ohio: 1-800-322-3525
Local: (513) 222-0173

- 15 day money back guarantee. • \$10.00 minimum order. • COD orders accepted. • 24 hour shipping.
- Shipping charge = UPS chart rate (\$2.50 minimum charge). Hours 8:30 a.m. - 6 p.m. EST M-F.

ALL SALES SUBJECT TO THE TERMS OF OUR 90 DAY LIMITED WARRANTY. FREE COPY UPON REQUEST.

CALL FOR FREE CATALOG

TEXT TO SPEECH BOARD!

PC/XT COMPATIBLE. MAKE YOUR COMPUTER TALK!
A VERY POWERFUL AND AMAZING SPEECH CARD. USES THE NEW GENERAL INSTRUMENTS SPO256-AL2 SPEECH CHIP AND THE CTS256A-AL2 TEXT TO SPEECH CONVERTER.



THIS BOARD USES ONE SLOT ON THE MOTHERBOARD AND REQUIRES A COM SERIAL PORT. BOARD MAY ALSO BE USED IN A STAND ALONE ENVIRONMENT WITH ALMOST ANY COMPUTER THAT HAS A RS232 SERIAL PORT. FEATURES ON BOARD AUDIO AMP OR MAY BE USED WITH EXTERNAL AMPS. DEMONSTRATION SOFTWARE AND A LIBRARY BUILDING PROGRAM ARE INCLUDED ON A 5 1/4" INCH PC/XT DISKETTE. FULL DOCUMENTATION AND SCHEMATICS ARE ALSO INCLUDED.


NEW! PRICE CUT!

\$69⁹⁵
ASSEMBLED & TESTED

NEW! IC TESTER! \$149.00

SIMILAR TO BELOW EPROM PROGRAMMER. PLUGS IN TO YOUR PC OR XT. TESTS ALMOST ALL 14, 16, AND 20 PIN 74XX SERIES. INCLUDES STANDARD POWER, "S" AND "LS" DEVICES. ALSO TESTS CD4000 SERIES CMOS. SOFTWARE INCLUDED CAN EVEN DETERMINE PART NUMBERS OF MOST UNMARKED AND HOUSE NUMBERED DEVICES WITH SIMPLE MOD. THIS UNIT CAN ALSO TEST 6.4K AND 256K DRAMS! WITH MANUAL AND SOFTWARE: \$149. PERFECT FOR SCHOOLS.

PC/XT EPROM PROGRAMMER \$169

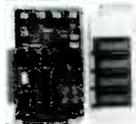

ASK ABOUT OUR NEW PAL PROGRAMMER!

• LATEST DESIGN • PROGRAMS UP TO 4 DEVICES AT ONE TIME • FEATURES EASY TO USE MENU DRIVEN SOFTWARE THAT RUNS UNDER PC OR MS-DOS. • USES AN INTELLIGENT PROGRAMMING ALGORITHM FOR SUPER FAST (8X) EPROM BURNING. • THIS PLUG-IN BOARD ATTACHES TO AN EXTERNAL MINI CHASSIS CONTAINING 4 TEXTOL Z.I.F. SOCKETS. • NO PERSONALITY MODULES REQUIRED • AUTOMATIC VPP SELECTION: 12.5V, 21V, OR 25V. • EPROM DATA CAN ALSO BE LOADED FROM OR SAVED TO A DISKETTE. • PROGRAMMING SOFTWARE SUPPORTS: 2716, 2732, 2732A, 2764, 2764A, 27128, 27128A, 27256, 27256A, 27512, AND 27512A. • ASSEMBLED AND TESTED, BURNED, IN WITH MANUAL. \$169 WITH SOFTWARE.

JUST RECEIVED. SAME AS ABOVE PROGRAMMER, BUT PROGRAMS 8 UNITS AT ONE TIME - \$299.

Digital Research Computers

P.O. BOX 381450 • DUNCANVILLE, TX 75138 • (214) 225-2309

TERMS: Add \$3.00 postage. We pay balance. Orders under \$15 add 75¢ handling. No C.O.D. We accept Visa and MasterCard. Texas Res. add 6-1/4% Tax. Foreign orders (except Canada) add 20% P & H. Orders over \$50 add 85¢ for insurance.

MACRO SCRUBBER ARTICLE PARTS

We stock the complete project for the Dec. 87 R.E. Article. Silk-screened PC board, case, adapter, all components, sockets and jumpers. Everything you need.

ONLY \$52.95 plus 3.50 S&H

Call Today: 1-617-339-1026
or send to: **THE HOBBY HELPER**
P.O. Box 308, Bridgewater, MA 02324
Visa, MC, COD's accepted

DECODING plans and theory booklets. Video tape copy protection, removes flashing and jitter. 30 pages, \$15.45. Jerrold DI and DIC decoder theory, 12 pages, \$6.95. Gated pulse decoding plus new universal single level suppression decoder, works on Hamlin, Jerrold, Sylvania, Eagle, 39 pages, \$15.00. Video scrambling techniques, the original secret manual, sinewave and Zenith SSAVI, 57 pages, \$14.95. Hidden signals on satellite TV, 178 pages, \$16.95. P.C. board and kits available. **ELEPHANT ELECTRONICS INC.**, P.O. Box 41865-J, Phoenix, AZ 85080. (602) 581-1793.

FREE catalog 99-cent kits—audio, video, TV, computer parts. **ALLKIT**, 434 W. 4th St., West Islip, NY 11795.

BUILD a Curvtracer for any scope. Plans, parts list, instructions. Send \$3.95. **SASE, MARTY'S ELECTRONICS**, 305 N. Grandview Blvd., Waukesha, WI 53188.


POWER supply pc board and plans for almost any 3-terminal regulator variable or fixed. Only \$10.00. **THIELE ENG.**, 801 Rinzetta, St. Louis, MO 63129.

VOICE disguisers! FM bugs! Telephone transmitters! Phone snoops! More! Catalog \$1.00 (Refundable). **XANDI ELECTRONICS**, Box 25647, Dept. 60W, Tempe, AZ 85282.

DETECTIVES, experimenters. Exciting new plans. Hard to find micro and restricted devices. Large catalog \$5.00, refundable on 1st order. **WILSON**, P.O. Box 5264, Augusta, GA 30906.

NOVELTY type electronics projects for the gadgeteer. Unusual, fascinating, and fun. Free information. **TAYLOR ELECTRONICS**, P.O. Box 1612, Destin, FL 32541.

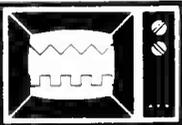BUILD this five-digit panel meter and square-wave generator including an ohms, capacitance and frequency meter. Detailed instructions \$2.50. **BAGNALL ELECTRONICS**, 179 May, Fairfield, CT 06430.



FINALLY!

An interesting and worthwhile project. This **EASY-TO-BUILD** circuit lets you use any regular TV set as a simple **OSCILLOSCOPE**. Build for less than \$10. **NO MODIFICATIONS TO TV!** Single or dual trace. Send for **FREE CATALOG** of other plans and kits.

DETAILED PLANS: \$4.95
TV-SCOPE
PENN RESEARCH, Box 3543
Williamsport, PA 17701

PROJECTION TV...Convert your TV to project 7 foot picture. Results comparable to \$2,500 projectors...Total cost less than \$30.00. Plans and 8" lens \$21.95...Illustrated information **Free**...**MACROCOMA-GE**, Washington Crossing, PA 18977. Creditcard orders 24hrs. (215) 736-3979.

TOP quality imported, domestic kits, surplus, discount electronics, computer components. **FREE** catalog. **TEKTRASONIX**, 1120 Avenue of the Americas, 1/11 suite 4038, New York, NY 10036.

NUTS & VOLTS

MAGAZINE

P.O. Box 1171-E
Placentia, CA 92670
714-632-7721

GIVE YOURSELF A BREAK — A PRICE BREAK!
NUTS & VOLTS WILL SAVE YOU MONEY
ON ELECTRONIC PARTS & EQUIPMENT
PLUS SHOW YOU WHERE TO FIND UNIQUE,
UNUSUAL AND HARD-TO-FIND ITEMS.

SUBSCRIBE TODAY!

Subscription Rates	
1st Class Mail	U.S. FUNDS REQUIRED
One Year	\$10.00
Two Years	\$18.00
Life	\$50.00
Air Mail	
One Year USA	\$18.00
CANADA/MEXICO	\$20.00
FOREIGN	\$24.50

A National Publication For The Buying And Selling Of Electronic Equipment

STRANGE stuff. Plans, kits, new items. Build satellite dish \$69.00. Descramblers. Bugging information adult toys. Informational photo package \$3.00 refundable. **DIRIJO CORPORATION**, Box 212, Lowell, NC 28098.

REMOTE control keychain! Complete with miniature RF transmitter and receiver. TTL outputs. \$19.95. Auto alarm plans included. **VISITEK INC.**, Box 5442, So. San Francisco, CA 94083-5442. (415) 872-0128.

THE decoder. National monthly technical newsletter covering Satellite/Cable descrambling systems. Includes: news, schematics, modifications, reviews, tips and more!!! \$18.00 per year. Sample \$2.00. **TELECODE**, Box 6426, Yuma, AZ 85364-08740.

VIDEOCIPHER, II manual 120+ pages/Oak "Orion" 120+ pages, either—\$27.45—both \$49.95. Plans, kits descrambling books. Catalog—\$2.00. **MICROTRONICS**, P.O. Box 6426, Yuma, AZ 85364-0840.

CABLE TV assortment #103 (February 1984 article) has printed circuit, TOKO coils (4), transistors, IC's, diodes with free power supply & "RF" connectors...Satellite TV assortment #301 (October 1986 article) Telease-Maast (see "After Dark" and more) has printed circuit, IC's, transistors, diodes...\$25.00/assortment five/\$112.50. Shipping \$2.00 **JIM RHODES, INC.**, P.O. Box 3421, Bristol, TN 37625.

MARK V ELECTRONICS INC.,

248 EAST MAIN STREET, SUITE 100,
ALHAMBRA, CA 91801
TELEX 3716914 MARK 5

1-800-423-3483
TOLL FREE

INFORMATION: 1-818-282-1196
MAIL ORDER: P.O. BOX 6610
ALHAMBRA, CA 91802

STATE OF ARTS HQ FET ST. PRE - AMP

* This Pre-amplifier employs 18 pairs of HIGH QUALITY N channel and P channel FET and 1/4 metal film resistor to form a state of arts full complementary symmetric mirror circuit.

* It uses "CR" RIAA EQ pre-amplifier to minimize TIM distortion and to obtain high fidelity.

* The power supply is based on by pass coupling DC stabilizer which uses class A design to obtain low internal impedance at high frequency and to greatly reduce transient distortion.

* Professional relay delay circuit prevents noise which may occur during power on and off.

* All FETs were tested and paired in the factory so no problem is likely to occur during building.

* It can be directly connected to any power MOSFET power amplifier. The best partner is TA-477 120W MOSFET power amplifier.

Kit/ASS. WITH TESTED METAL CABINET \$55/85 \$18

COLOR LIGHT CONTROLLER TY-238

As a result of the advanced technology, this unit can control various color spot lights or bulbs. The visual effect of which is most suitable in places like party, disco, electronic game centre and also in lighting for advertisements. Total output power is 3000W (1100W/Ch.) which can control 30 pieces of 100W or 600 pieces of 5W color light bulbs.

FEATURES:

1. "Music" mode: Audio signal is divided into high, middle and low frequency to drive 3 groups of lights; it has independent controller for sensitivity.
2. "Chasing" mode: Electronic circuit automatically controls 3 groups of color lights in sequential ON and OFF; also it has a speed controller and self-program "Chasing Mode" on the P.C. Board.

Kit \$65.00 Assembled with tested \$75.00

80W+80W PURE DC STEREO MAIN POWER AMPLIFIER

* It uses FET differential input to improve S/N ratio and input impedance.

* It is compatible with all kinds of preamplifier.

* It has a multipurpose protection system, including high tens. DC output protection circuit, high speed output short circuit, overload protection, and an automatic temperature control system. It can protect the loudspeakers and amplifier against damage.

Kit \$39.95

150MC Digital Frequency Counter



Frequency Range: 10Hz - 150MHz
Event Counter: 0 to 999999999 counts (8 Digit)
Input sensitivity: 1KHz range 10Hz - 10MHz 50mVrms
1MHz range 1MHz - 150MHz 40mVrms
Response time: 0.2 second
Hold Function: Hold the last input signal.
Power Supply: OCV6 Battery or OCV9 Adaptor.
Dimensions: 9 7/8" x 6 11/16" x 2 3/4"
Assembled with tested \$99.00

MULTIFUNCTIONAL LED D.P.M.

LARGE 3 1/2" DIGIT 0°C LED DISPLAY

MEASUREMENT RANGE:
D.C. VOLTAGE: 1mV - 1000V
A.C. VOLTAGE: 1mV - 1000V
DIGITAL THERMOMETER: 0°C - 100°C
D.C. CURRENT: 1µA - 2A
CAPACITOR METER: 1pF - 2µF Kit \$30.00
DIMENSIONS: 3 3/4" x 1 7/8" x 4 1/16" Assembled with tested \$36.00

120W MOSFET POWER AMPLIFIER


Kit \$61.28
Metal Cabinet/X-Former (Optional) \$26.00 \$19.88

TERMS: \$10.00 min order \$20.00 min charge card order. Check, money order or phone order accepted. We ship UPS Ground & Add 10% of total order (min \$2.50) for shipping, outside USA add 20% (min \$6.00) + Transit Insurance; add 5% of total (outside USA only) + CA residents add sales tax. All merchandise subject to prior sale. Price is a subject to change without notice. Any goods proved to be defective, MUST BE RETURNED IN ORIGINAL FORM WITH A COPY OF YOUR INVOICE WITHIN 30 DAYS FOR REPLACEMENT.

We've rated our goods with a Δ indicating the level of difficulty for kit assembly:

- Δ beginner level;
- $\Delta\Delta$ intermediate level;
- $\Delta\Delta\Delta$ advanced level;
- Δ^* indicates the product has already been assembled.

TALKING CLOCKS that really tell time!

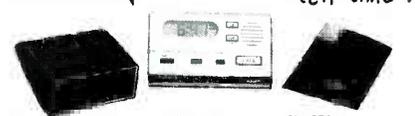

1. Talk: push button for voice announcement of time.
2. Read out: twelve hours system display for hour, minute, second (by color flash), AM & PM.
3. Display: three display modes of time, alarm time & date.
4. Alarm: on / off switch with thirty seconds voice alarm.
5. Snooze: reminder voice alarm of thirty seconds after 4 minutes of first vocal alarm.
6. Volume: two level of voice output.
7. Language available: English.

PARROT 8501 \$17.75
COCKATOO 8502 \$15.90 NOT A KIT!
MYNAH 8504 \$16.90

PROFESSIONAL COLOR LIGHT CONTROLLER SM-328

FEATURES:

1. FOUR GROUPS OF INDEPENDENT OUTPUT SYSTEM 1000W/CH MAX BOARD TYPE 3
2. PROFESSIONAL COLOR CONTROL SYSTEM (KEUR GROUPS OF INDEPENDENT INPUT SIGNAL ADJUSTMENT 4 FOUR CHASER 6 AUTOMATIC DIMMER CONTROL SYSTEM 4 FOUR OF SPECIAL CHASING PROGRAM 5 SPEED CONTROL OF MUSIC CHASING EFFECT 9 FORWARD BACKWARD PROGRAM AND disco and advertisements lighting. It consists of specialized for ballroom, CHASING effects, which employ professional color control system effects by using chaser selection. Therefore, it is capable of producing lighting effects by using chaser.
3. The first type is controlled by "music" signal. There are two kinds of lighting program: low A. and low B. frequency range. In order to adjust the brightness of four groups of lighting, each music signal will be separated into high, medium incorporated with an independent signal. Furthermore, each group of lighting is in effect of electrical circuits and this is the main part for creating a special lighting effect. It has four chasing programme.
4. Dimensions 14 5/16" x 8 15/16" x 3 3/16"

Assembled with tested \$150.00

OFFICE HOURS: (PACIFIC TIME)
MON.-FRI. 9:30 to 5:00 SAT. 10:00 to 5:00

Engineered In Quality

TENMA Test Equipment

#72-035 Tenma 30A Regulated Power Supply 2 YEAR LIMITED WARRANTY

This provides a very clean well regulated variable DC output that is well suited for high current applications.

Features: ■ Lighted cross needle meter: Displays voltage, current, and power simultaneously ■ Over current protection: Automatically shuts off current flow when maximum output is exceeded (31 amps) ■ Overload indicator: Illuminates when over current protection circuit is engaged ■ Multi-terminal output. Three sets of output terminals are provided for convenience. One set of high current output terminals (30 amp maximum) and two sets of low current output terminals (5 amp maximum) ■ Fan cooled for maximum heat dissipation

Specifications: ■ Output voltage: 1-15VDC variable ■ Output current: 30 amp one minute on, three minutes off; 24 amp continuous ■ Voltage fluctuation: Less than .5% at rated output ■ Ripple voltage: Less than 1mV at rated output **General:** ■ Power requirements: 110VAC, 60Hz ■ Dimensions: 7½" (W) x 6" (H) x 11¾" (D) ■ Weight: 22 lbs.



#72-420 Tenma Laboratory Power Supply 1 YEAR LIMITED WARRANTY

This is a lab quality DC power supply with adjustable current limiting.

Features: ■ Current limiter can be adjusted to any value between 0 and 3 amps ■ Output voltage adjustable between 0 and 18VDC ■ Separate voltage and current meters ■ Fine and coarse voltage adjustments for accurate voltage settings ■ Short circuit protection ■ Hi-Lo current scales ■ Can be used as a constant current or constant voltage source ■ Comes complete with leads and owners manual

Specifications: Constant voltage operation: ■ Line regulation: ± .01% ■ Load regulation: ± .2% ■ Ripple current: ± 3mA
Constant current operation: ■ Line regulation: ± .2% ■ Load regulation: ± .2% ■ Ripple current: ± 3mA **General:** ■ Power requirements: 110/220VAC 50/60Hz ■ Dimensions: 4¹³/₁₆" (W) x 6⁷/₈" (H) x 12" (D) ■ Weight: 7 lbs.



#72-280 Tenma 5 Amp Regulated Power Supply

Features: ■ Fuse protected with easily accessible fuse holder ■ Neon light power indicator ■ Heavy duty binding posts ■ Large heat sink for effective heat dissipation allows continuous use

Specifications: ■ Output: Regulated 13.8VDC ■ Input: 130VAC
■ Output current: 5 amp one minute on, 3 minutes off; 3.5 amp continuous



#72-290 Tenma 10 Amp Regulated Power Supply

Features: ■ Fuse protected with easily accessible fuse holder ■ Neon light power indicator ■ Heavy duty binding posts ■ Large heat sink for effective heat dissipation allows continuous use



Specifications: ■ Output: Regulated 13.8VDC ■ Input: 120VAC ■ Output current: 10 amp one minute on, 3 minutes off; 7 amp continuous


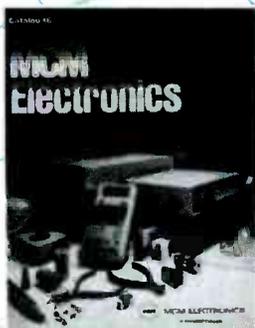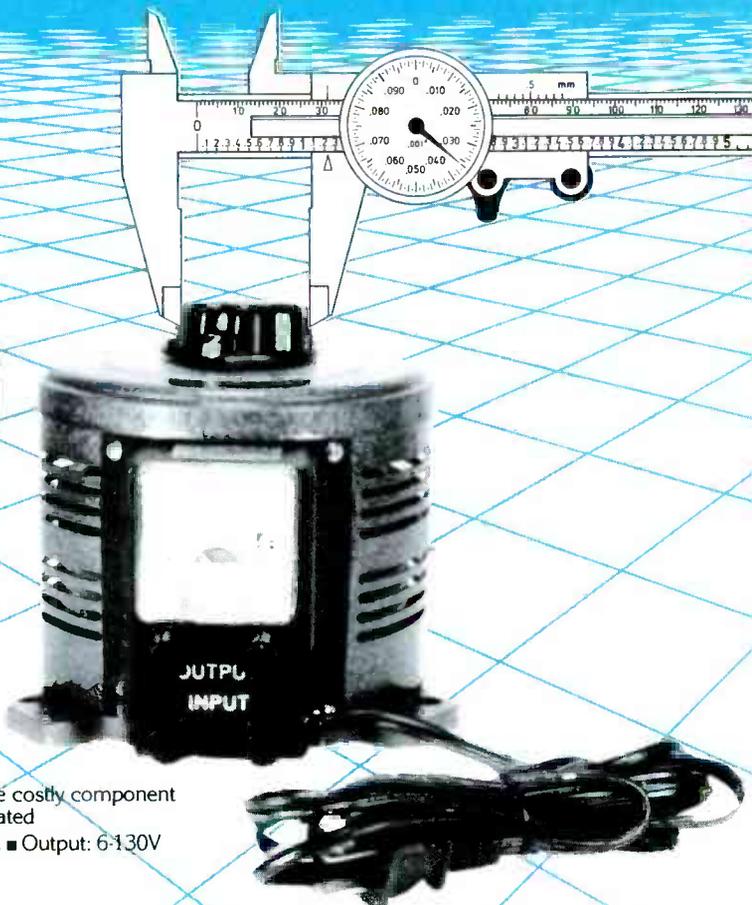
#72-110 Tenma 10 Amp Variable (Autotransformer)

Features: ■ Gives you ability to bring up line voltage slowly in order to monitor problems in a TV, stereo, or other electronic equipment ■ Built-in ammeter shows excessive current to check for shorts before they can cause costly component failure ■ Plug outlet on side ■ Non-isolated

Specifications: ■ Input: 120VAC, 60Hz ■ Output: 6-130V
■ Current: 10 amp, 1.3KVA



If you would like to know more about these Tenma products, ask for our free catalog...
Call TOLL-FREE 1-800-543-4330

In Ohio call 1-800-762-4315
In Alaska or Hawaii 1-800-858-1849



MCM ELECTRONICS
858 E. CONGRESS PARK DR.
CENTERVILLE, OH 45459
A PREMIER Company

©1988, MCM ELECTRONICS

SOURCE NO. RE-40

CIRCLE 87 ON FREE INFORMATION CARD

DESCRAMBLING. New secret manual. Build your own descramblers for **Cable and Subscription TV.** Instructions, schematics for SSAVI, gated sync, sinewave. (HBO, Cinemax, Showtime, etc.) \$8.95 \$1.00 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

TV stereo construction plans with free PCB. \$6.25 closeout. Similar to R-E March 1986 article. **DEL-PHONE**, Box 150, Elmont, NY 11003.

SATELLITE descrambling manual. Video Cypher II. Schematics, thorough explanation of digital audio encoding. EPROM code, DES, (HBO, Cinemax, Showtime.) \$10.95 + \$1.00 postage. **CABLETRONICS**, Box 30502R, Bethesda, MD 20814.

MINIATURE electronic devices, like James Bond's. Catalog \$2.00. **F & P ENTERPRISES**, Box 51272, Palo Alto, CA 94303-L.

EDUCATION & INSTRUCTION

F.C.C. Commercial General Radiotelephone license. Electronics home study. Fast, inexpensive! "Free" details. **COMMAND**, D-176, Box 2223, San Francisco, CA 94126.

SUPERFAST Morse Code supereasy. Subliminal cassette. \$10. Learn Morse Code in 1 hour. Amazing new supereasy technique. \$10. Both \$17. Moneyback guarantee. Free catalog: **SASE. BAHR**, 2549-E8 Temple, Palmbay, FL 32905.

SATELLITE TV

CABLE TV Secrets—the outlaw publication the cable companies tried to ban. HBO, Movie Channel, Showtime, descramblers, converters, etc. Supplier's list included \$8.95. **CABLE FACTS**, Box 711-R, Pataskala, OH 43062.

SATELLITE TV receiver kits! LNA's! Instructions! Schematics! Catalog \$1.00 (refundable): **XANDI ELECTRONICS**, Box 25647, Dept. 21AA, Tempe, AZ 85282.

DESCRAMBLERS movies, networks. \$149, video; \$399, complete. Catalog \$4.00. **SKYWATCH**, 238 Davenport Road, Toronto, Ontario, Canada, M5R-1J6.

CABLE/VCR technics hookups: VCR and cable wiring, VCR problems and special video devices. Manual \$8.50. **VOX, INC.**, P.O. Box 2191, Union, NJ 07083.

****SCRAMBLING NEWS**** PAY TV AND SATELLITE DESCRAMBLING

Schematics, theory, bypasses, 13 cable, 7 satellite. New SA turn-on, MLD-1200-3 \$14.95. Experiments With Videocipher, Cloning, musketeering. \$14.95. Cable TV Security design \$12.95. MDS/ MMD5 Handbook Microwave hacking \$9.95. Build Satellite Systems Under \$600 \$12.95. Any 3/527. Scrambling News. Monthly. Feature articles, product reviews, law history, patents. \$24.95/yr Sample \$5. Winter catalog \$1.

Shojiki Electronics Corp. 1327A Niagara St. Niagara Falls, NY 14303. COD's 716-284-2163

SCRAMBLE FACTS 718-343-0130

PHONE TODAY for 3 minutes of satellite TV industry news, technical tips, and new product information.

SATELLITE TV equipment. Buyers guide, discount prices. \$2.00 **N.E.C.S. INC.**, Box 22808-R4, Little Rock, AR 72221.

DESCRAMBLER. Build our low cost satellite TV video-only descrambler for all major movies and sports. Uses all Radio Shack parts. Order P.C. board and instructions by sending check, money order, or Visa for \$35.00 U.S. funds to: **VALLEY MICROWAVE ELECTRONICS**, Bear River, Nova Scotia, Canada. BOS-1B0. (902) 467-3577.

SUPER SAVINGS—SHOP G.E.I.


MULTI NI-CAD BATTERY CHARGER
Recharge 2 or 4 NI-CAD "AA Batt" or "AAA Batt"
10.00 each



COMMODORE 64 CARTRIDGES
• Num. Nabber • Star Post
• Financial Advis. • Frog Master
• Super Smash • Avenger • Radar
• Rat • Jupitire Landing • Magic
• Compos • Dragons Den • Simon
• Basic • Viduzzles • Star Ranger
• Gorf • Blue Print • ABC Voice
• Sales Demo
\$1.50 ea. (10 pc. min.)



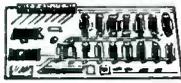STOPLOCK SECURITY BOARD
For IBM PC's & Compatibles
\$150 each




• Complete control of equipment access • Plugs into expansions lot • Prevents boot up without user code • No diskette software needed • Menu driven with single keystroke

POWER SUPPLY FOR THE COMMODORE AMIGA
+5VDC @ 8 Amps
+12VDC @ 1 Amp
-5VDC @ 1/4 Amp
\$39 ea.



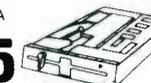MINI FLOPPY DISK DRIVE
by Shugart #SA465-3AA
1/2 height
Quad Density
5 1/4 Inch
\$65 Ea.



PATCH CORDS
5 ft. dual RCA color coded, stereo cords
99c Each



OPEN FRAME MONITORS
12" monitor 40-80 column display composite. Green screen 18 Mhz Bandwidth
\$20 Ea.



PERSONAL TELEPHONE MANAGER
Program & Adaptor
For IBM PC's & Compatibles
\$79 ea



• Create, store and print computerized telephone directories • Search for directory listings by first or last names, address, title or other variable • Place calls with one keystroke, receive electronic reminders for appointments and outgoing calls • Operate the program concurrently with other programs

Plug in WALL TRANSFORMER
Quantity Pricing Available
• 9.5 VDC @ 1 Amp \$3.00
• 19 VAC @ 300 MA \$1.50
• 25.4 VAC @ 1 Amp \$1.95
• 14 VDC @ 200 MA \$1.00



REGULATED LINEAR POWER SUPPLY
Computer Grade
+5VDC @ 8 Amps
+12VDC @ 6 Amps
-5VDC @ 0.5 Amps
Bench Style/Great for Hobblists
\$24 ea.



PASSIVE INFRARED MOTION DETECTOR
It can pick up any moving human body heat or moving vehicle with sensing range (40 x 60 ft.) and turn on the light.
\$60 Each



G.E.I.
GIANT ELECTRONICS INC.
19 Freeman St., Newark, New Jersey 07105
Toll Free: **800/645/9060**
201/344-8183 Fax # 201/344-3282

ANTIQUE RADIO

continued from page 85

"off-center voice coil" can occur. When the voice coil is uncentered it rubs against the speaker's magnet, producing a thin, tinny, distorted sound. Although the speakers used in modern radios make no provisions to recenter the voice coil, many of the speakers used in antique radios had some form of adjustment that allowed a voice coil to be recentered.

The voice-coil test is made with the set off and unplugged. Put the speaker on the workbench with its cone facing up. Lightly touch the cone at various places with the tips of your fingers. If you hear a mechanical scratching noise you know that the voice-coil is off-center because the scratching sound is caused by the voice coil rubbing against its magnet. If you have a steady hand and nerves of steel, you can try whatever steps are necessary to recenter the voice coil. But remember, if the cone is brittle just one "whoops!" can permanently damage the cone.

When we get together next time we will finish up with the voice coil before moving on. **R-E**

Multi-Channel Microwave T.V. Receivers
1.9-2.7 GHz Parabolic Dish 40+ dB Gain
LIFETIME WARRANTY
Complete System \$69.95 (Shipping Incl.)
Dealer Rates, Replacement Components & Expert Repairs Available
K & S ELECTRONICS Call now for same
P.O. BOX 34522 day shipping!
PHOENIX, AZ 85067 (602) 230-0640
VISA/MC/COD \$2 credit on phone orders!



DESCRAMBLER MODULE

COMPLETE cable-TV decoder in a mini-module. Latest technology upgrade for Jerrold SB-3 or Radio-Electronics Feb. 1984 project. Versatile, sophisticated, and low cost. For literature, **SOUTHTECH DISTRIBUTING**. (813) 222-3293.

WANTED

INVENTORS! AIM wants—ideas, inventions, new products, improvements on existing products. We present ideas to manufacturers. Confidentiality guaranteed. Call toll free 1-(800) 225-5800 for information kit.

INVENTIONS, ideas, new products wanted! Industry presentation/national exposition. Call free 1-(800) 288-IDEA. Canada, 1-(800) 528-6060. X831.

WANTED excess inventories of I.C.'s, disk drives, circuit boards, computers, etc. **WESTERN TECH.**, (818) 882-1355 (CA).

LASERS

LASERS 5mw Helium neon includes beam splitter, 3 front surface mirrors. \$185 **MWK INDUSTRIES**, 1724 W. Ball, Anaheim, CA 92804. (714) 956-8497.

BUSINESS OPPORTUNITIES

EARN thousands with your own part time electronics business. I do. Free proof, information. **INDUSTRY**, Box 531, Bronx, NY 10461.

HOME assembly. Assemble PC boards for video accessories. We supply materials. No experience needed \$7.50 per hour. Send self-addressed stamped envelope, to: **MICRON-ELECTRONICS**, Box 4716 Akron, OH 44310.

PROJECTION TV...Make \$\$\$'s assembling projectors...easy...results comparable to \$2,500 projectors...Total cost less than \$30.00...Plans, 8" lens and dealers information \$20.50...Illustrated information free...**MACROCOMA-GEX**, Washington Crossing, PA 18977. Creditcard orders 24hrs. (215) 736-2880.

MICRO-Electronic engineer to design and manufacture receiver. **JPH**, 4218 Bunker Hill, Bettendorf, IA 52722. (319) 355-2927.

EASY, lucrative. One man CRT rebuilding machinery. Free info: (815) 459-0666 **CRT**, 1909 Louise, Crystalake, IL 60014.

RECORD changer repairing is very profitable. Be an expert. Learn at home. Info-**R.C.T.C.**, P.O. Bx 1503, Leesburg, FL 32748.

BURGLAR alarms-booming business. Get started now information \$2.00. **DYNAMIC SECURITY**, P.O.B. 1456-TW, Grand Rapids, MI 49501.

ASSEMBLE TV commercial killers. Plans \$5.95 kit \$26.95. **EASTECH**, Box 3428, Charlotetown, PEI C1A 8C2 CAN.

BIG PROFITS **ELECTRONIC ASSEMBLY BUSINESS**

Start home, spare time. Investment knowledge or experience unnecessary. **BIG DEMAND** assembling electronic devices. Sales handled by professionals. Unusual business opportunity.

FREE: Complete illustrated literature
BARTA, RE-O Box 248
Walnut Creek, Calif. 94597

MECHANICALLY inclined individuals desiring ownership of small electronics manufacturing business—without investment. Write: **BUSINESS**, 92-R, Brighton 11th, Brooklyn, NY 11235.

SCIENTIFIC ATLANTA & SB-3

SCIENTIFIC Atlanta Models 8500—8550, remote included...\$240.00. **SB-3's**...\$74.00. **TRI-BI's**...\$95.00. **SBSA-3's**...\$99.00. **Zenith (Z-Tac)** descramblers...\$169.00. **N-12 (Vari-sync)**...\$89.00. **M-35 B (Vari-sync)**...\$99.00. **Panasonic** converters...\$95.00—\$99.00. Dealer discount on (5) units. Brochure available. Call...**N.A.S. INTERNATIONAL**. (213) 631-3552.

Cable TV Converters
Why Pay A High Monthly Fee?

Jerrold Products include "New Jerrold Tri-Mode," **SB-3**, Hamlin, Oak VN-12, M-35-B, Zenith, Magnavox, Scientific Atlanta, and more. (Quantity discounts) 60 day warranty. For fast service C.O.D. orders accepted. Send SASE (60 cents postage) or call for info (312) 658-5320. **Midwest Electronics, Inc.**, **HIGGINS ELECTRONICS**, 5143-R W. Diversey, Chicago, IL 60639. MC/Visa orders accepted. No Illinois orders accepted. Mon.-Fri.-9 A.M.-6 P.M.CST

PRINTED CIRCUIT BOARD LAYOUTS

GUARANTEED low pricing for single, double sided artwork layouts. (704) 464-1164; **PCBAL**. RT-3, Box 662-H, Conover, NC 28613.

A SINGER'S DREAM!



REMOVES VOCALS FROM RECORDS!

Now You can sing with the world's best bands! The **Thompson Vocal Eliminator** can remove most or virtually all of a lead vocal from a standard stereo record and leave most of the background untouched! Record with your voice or perform live with the backgrounds. Used in Professional Performance yet connects easily to a home component stereo system. Not an equalizer! We can prove it works over the phone. Write or call for a Free Brochure and Demo Record.

LT Sound, Dept. RL-7, 7980 LT Parkway Lithonia, GA 30058 (404) 482-4724
24 HOUR PHONE DEMO LINE: (404) 482-2485

INVENTORS

INVENTORS! Can you patent and profit from your idea? Call **AMERICAN INVENTORS CORPORATION** for free information. Over a decade of service. 1-(800) 338-5656. In Massachusetts or Canada call (413) 568-3753.

WRITE FOR
McGEE'S
SPEAKER & ELECTRONICS CATALOG

1001 BARGAINS IN SPEAKERS
toll free 1-800-346-2433 for ordering only.
1901 MCGEE STREET KANSAS CITY, MO. 64108

STATEMENT OF OWNERSHIP, MANAGEMENT AND CIRCULATION			
1. TITLE OF PUBLICATION		2. IN PUBLICATION NO.	3. DATE OF FILING
Radio-Electronics		0 0 3 3 7 8 6 2	10/8/87
4. FREQUENCY OF ISSUE		5A. NO. OF ISSUES PUBLISHED	5B. ANNUAL SUBSCRIPTION PRICE
Monthly		12	\$16.97
6. COMPLETE MAILING ADDRESS OF KNOWN OFFICE OF PUBLICATION (Street, R. T., County, State and Zip Code - Subsequent)			
500-B Bi-County Blvd. Farmingdale, NY 11735			
7. COMPLETE MAILING ADDRESS OF THE HEADQUARTERS OF GENERAL BUSINESS OFFICES OF THE PUBLISHER (No Post Office)			
500-B Bi-County Blvd. Farmingdale, NY 11735			
8. FULL NAMES AND COMPLETE MAILING ADDRESS OF PUBLISHER, EDITOR AND MANAGING EDITOR (Do not include home address)			
Publisher: Larry Steckler 500-B Bi-County Blvd. Farmingdale, NY 11735			
Editor: Arthur Kleinman 500-B Bi-County Blvd. Farmingdale, NY 11735			
Managing Editor: Brian Fenton 500-B Bi-County Blvd. Farmingdale, NY 11735			
9. OWNER (If owned by a corporation, its name and address must be stated and also immediately thereunder the names and addresses of stockholders owning or holding 1 percent or more of total amount of stock. If not owned by a corporation, the name and address of the individual owner must be given. If owned by a partnership or other unincorporated firm, its name and address, as well as that of each individual must be given. If the publication is published by a nonprofit organization, its name and address must be stated. Form must be completed.)			
FULL NAME		COMPLETE MAILING ADDRESS	
Cernsback Publications, Inc.		500-B Bi-County Blvd. Farmingdale, NY 11735	
Lawrence Steckler		500-B Bi-County Blvd. Farmingdale, NY 11735	
10. EXTENT AND NATURE OF CIRCULATION (See instructions on reverse side)			
A. TOTAL NO. COPIES (Net Press Run)		AVERAGE NO. COPIES EACH ISSUE DURING PRECEDING 12 MONTHS	ACTUAL NO. COPIES OF SINGLE ISSUE PUBLISHED NEAREST TO FILING DATE
B. PAID AND/OR REQUESTED CIRCULATION		82,085	74,542
1. Sales through dealers and carriers, street vendors and counter sales			
2. Mail Subscriptions (Third and fourth classes)		162,023	167,759
C. TOTAL PAID AND/OR REQUESTED CIRCULATION (Sum of 10B1 and 10B2)		244,362	242,301
D. FREE DISTRIBUTION BY MAIL, CARRIER OR OTHER MEANS (Samples, complimentary, and other free copies)		6,304	6,609
E. TOTAL DISTRIBUTION (Sum of C and D)		250,666	248,910
F. COPIES NOT DISTRIBUTED		10,280	1,769
1. Office use, left-overs, unsold copies, spoiled after printing			
2. Return from news agents		77,379	112,021
G. TOTAL (Sum of E, F, 1 and 2; should equal net press run shown in A)		338,324	362,700
11. I certify that the statements made by me above are correct and complete			
Signature and Title of Editor, Publisher, Business Manager or Owner		Date	
Larry Steckler - Publisher		10/8/87	

**At KELVIN...
Price, Service
& Quality for
over 42 years.**

**B & K · FLUKE · UNGAR
HITACHI · WELLER
BECKMAN · DREMEL
STANLEY · MAKITA
X-ACTO · KEPRO · XCELITE**



LISA HADAR
EXECUTIVE VP, CPA

METERS/OSCILLOSCOPES

B & K	2120	20Mhz Dual Trace	\$ 395*
Beckman	9020	20Mhz Dual Trace	425
Hitachi	V-209	20Mhz Dual Trace Portable	815
Hitachi	V-509	50Mhz Dual Trace Portable	1,225
Fluke	73	3 1/2" Digit DMM	73
Fluke	75	3 1/2" Digit DMM	95
Fluke	77	3 1/2" Digit DMM	130

*PLUS Shipping & Insurance. Prices subject to change without notice.

WE HAVE IT ALL...

• COMPONENTS • TOOLS • KITS • SECURITY • SEMI-CONDUCTORS • ELECTRICAL SUPPLIES • SOLDER EQUIPMENT • KELVIN KITS • TSM KITS • DRAFTING SUPPLIES

Volume Quotes, Industrial & School Bids Welcome.

ORDER TOLL FREE

FOR INQUIRES & N.Y.S.

1-800-645-9212

516-349-7620

**KELVIN
ELECTRONICS**

NEW ADDRESS:

7 Fairchild Avenue • Plainview, NY 11803 • FAX: 516-349-7830


VISA/MASTER CARD ACCEPTED

CIRCLE 199 ON FREE INFORMATION CARD

**SEND FOR
FREE
1987 CATALOG**
OUR NEW MAILING
ADDRESS IS:
P.O. BOX 567
VAN NUYS, CA 91408
800-826-5432

QUALITY PARTS * DISCOUNT PRICES * FAST SHIPPING!
ALL ELECTRONICS CORP.
ALL ELECTRONICS CORP.

BLACKLIGHT ASSEMBLY

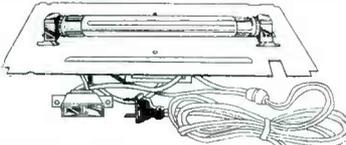

Complete, functioning assembly includes ballast, on-off switch, power cord, sockets and F4T5-BL blacklight. Mounted on a 7 1/8" X 3 1/8" metal plate. Use for special effects lighting or erasing EPROMS.

CAT# BLTA \$10.00 EACH

1mA METER


Modutec 0-1 mA signal strength meter with KLM logo. 1/4" X 1 3/4" X 7/8" deep.



CAT# MET-2 \$2.00 each

NI-CAD CHARGER/TESTER

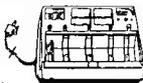DELUXE universal charger and tester for almost every size Ni-cad battery available.



CAT# UNCC-N \$15.00 each

RECHARGEABLE NI-CAD BATTERIES

- AAA SIZE 1.25V 180mAh \$2.25
- AA SIZE 1.25V 500mAh \$2.00
- AA with solder tabs \$2.20
- C SIZE 1.2V 1200mAh \$4.25
- SUB-C SIZE solder tab \$4.25
- D SIZE 1.2V 1200mAh \$4.25

COMPUTER GRADE CAPACITORS

- 1,400 MFD 200 VDC**
2" dia. X 3" high
CAT# CG-1420 \$2.00
- 7,500 MFD 200 VDC**
3" dia. X 4 3/4" h.
CAT# CG-75 \$4.00
- 22,000 MFD 25 VDC**
2" dia. X 4 3/4" h.
CAT# CG-22 \$2.50
- 72,000 MFD 15 VDC**
2" dia. X 4 3/8" h.
CAT# CG-130 \$3.50

TRANSISTORS

- 2N2222A**
3 for \$1.00
- PN2222A**
4 for \$1.00
- 2N2904**
3 for \$1.00
- 2N2905**
3 for \$1.00
- 2N3055**
\$1.00 each
- PN3569**
10 for \$1.00

WALL TRANSFORMER

11.5 Vdc
1.95 AMP.
Input:
120 Vac
SIZE: 3 3/4" X
2 7/8" X 2 5/8"
CAT# DCTX-11519
\$6.50 each



A/B SWITCH

JVC# PUS3593-2
High quality A/B switch.
Measures:
3 3/4" X 1 7/16" X 1".
75 OHMS IN/OUT
CAT# ABS-2 \$3.50 each



13.8 VDC REGULATED POWER SUPPLY

Solid state, fully regulated 13.8 Vdc power supplies. Both feature 100% solid state construction, fuse protection and LED power indicator. UL listed.



2 AMP CONSTANT, 4 AMP SURGE
CAT# DVP-412 \$22.50 each

3 AMP CONSTANT, 5 AMP SURGE
CAT# DVP-512 \$30.00 each

ELECTRET CONDENSER MIKE

Mouser# 25LMO44 Highly sensitive mini microphone. 6" wire leads. 0.39" dia. X 0.27" high. Omni directional. Operates on 2-10 Vdc @ less than 1 mA. 1K impedance. 50 to 8 K Hz range.
CAT# MKE-1 \$1.00 EACH

SLIM LINE FAN

TOYO# TF92115A New 115 Vac cooling fan. 3 5/8" square X 1" deep. Metal housing. 5 blade impeller.
CAT# SCPE-115 \$8.50 each
10 for \$75.00



2K 10 TURN

Multi-turn pot Spectrol# MOD 534-7161
CAT# MTP-10-2 \$5.00 each



VENTED PROJECT CASE

Bopla #B0 718L Vented top and bottom. Black plastic with removable end panels. 9" X 8 1/2" X 8"
CAT# MB-718 \$12.50 each



6-12 VDC MOTOR

Mabuchi # RS-550S Permanent magnet motor. 1 7/16" dia X 2 1/4" long 2,600 RPM @ 6 Vdc-200 mA 5,300 RPM @ 12 Vdc
CAT# DCM-7 \$3.00 each



LED'S

Standard Jumbo Diffused T 1-3/4 Size

- RED 10 for \$1.50
100 for \$13.00
CAT# LED-1 1000 for \$110.00
- GREEN 10 for \$2.00
100 for \$17.00
CAT# LED-2 1000 for \$150.00
- YELLOW 10 for \$2.00
100 for \$17.00
CAT# LED-3 1000 for \$150.00

FLASHING LED

w/ built in flashing circuit operates on 5 Volts...

- RED \$1.00 each
CAT# LED-4 10 for \$9.50
- GREEN \$1.00 each
CAT# LED-4G 10 for \$9.50

BI-POLAR LED

Lights RED one direction, GREEN the other. two leads.
CAT# LED-6 2 for \$1.70

LED HOLDERS

Two piece holder.
CAT# HLED 10 for 65c

CLIPLITE LED HOLDER

Makes L.E.D. look like a fancy indicator

- CLEAR CAT# HLDCL-C
- RED CAT# HLDCL-R
- GREEN CAT# HLDCL-G
- YELLOW CAT# HLDCL-Y
- 4 of one color \$1.00


48 KEY ASSEMBLY



NEW T.I. KEYBOARDS. Originally used on computers, these keyboards contain 48 S.P.S.T. mechanical switches. Terminates to 15 pin connector. Frame 4" X 9"
CAT# KP-48 \$3.50 each

PUSHBUTTON PHONE

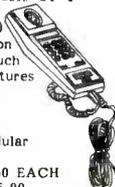Spectra-phone Model# OP-1 1 piece telephone with rotary (pulse) output. Operates on most rotary or touch tone systems. Features last minute redial and mute button. Includes coil cord with standard modular plug. IVORY.
CAT# PHN-1 \$8.50 EACH
2 FOR \$15.00



RELAYS

12 VDC-4PDT
P.C. mount
5 amp contacts
150 ohm coil
Size: 1 1/4" X
1 3/4" X 7/8"
CAT# 4PRLY-12PC \$3.50
10 for \$30.00



10AMP SOLID STATE

Control: 3-32 Vdc
Load: 10 AMPS, 120 Vac
Size: 2 1/2" X
3/4" X 7/8"
CAT# SSRLY-10A \$9.50
10 for \$85.00



25 AMP SOLID STATE

OPTO 22# 240D25 TTL compatible. INPUT: 3-32 VDC OUTPUT: 25 AMPS @ 240 VAC SIZE: 2 1/2" X 3/4" X 7/8"
CAT# SSRLY-2524 \$15.00 each



THIRD TAIL LIGHT

Sleek high-tech lamp assembly. Red lens is 2 3/4" X 5 1/2" mounted on a 4" high pedestal with up-down swivel adjustment. Has 12V replaceable bulb.
CAT# TLB \$3.95 each



SOUND EFFECTS BOARD


P.C board with 2 1/4" speaker, 2 LEDs, IC, battery snap, other components 2 3/8" X 3". When switch is pushed board beeps and leds light. Operates on a 9V battery (not included)
CAT# ST-3 \$1.25 each



XENON FLASH TUBE

3/4" long X 1/8" dia.
CAT# FLT-1 2 for \$1.00


VIC 20 MOTHERBOARD

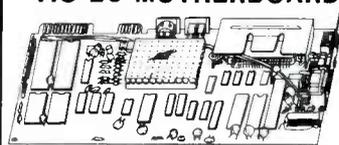

26 IC's including 6502A and 6560. 2 ea. 6522, 2 ea. 8128, 2 ea. 901486, 3 ea. 2114. Not guaranteed but great for replacement parts or experimentation.
CAT# VIC-20 \$15.00 each


SWITCHING POWER SUPPLY

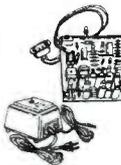Compact, well regulated switching power supply designed to power Texas Instruments computer equipment.
INPUT: 14-25 vac @ 1 amp
OUTPUT: +12 vdc @ 350 ma.
+5 vdc @ 1.2 amp
-5 vdc @ 200 ma.
SIZE: 4 3/4" square.
Includes 18 Vac @ 1 amp wall transformer designed to power this supply.
CAT# PS-TX \$5.00 / set
10 for \$45.00



LIGHT ACTIVATED MOTION SENSOR

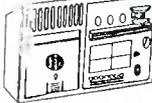This device contains a photo cell which senses sudden change in ambient light. Could be used as a door annunciator or modified to trigger other devices. 5 1/2" X 4" X 1". Operates on 6 Vdc. Requires 4 AA batteries (not included).
CAT# LSMD \$5.75 per unit



TRANSFORMERS

- 5.6 VOLT- 750ma**
CAT# TX-56 \$3.00
- 12 V.c.t.-1amp**
CAT# TX-121 \$4.00
- 12 V.c.t.-2amp**
CAT# TX-122 \$4.85
- 12 V.c.t.-4amp**
CAT# TX-124 \$7.00
- 18 VOLT-650ma**
CAT# TX-186 \$2.00
10 for \$18.00
- 24 V.c.t.-1amp**
CAT# TX-241 \$4.85
- 24 V.c.t.-2amp**
CAT# TX-242 \$6.75
- 24 V.c.t.-3amp**
CAT# TX-243 \$9.50
- 24 V.c.t.-4amp**
CAT# TX-244 \$11.00

SWITCHES

- MINIATURE TOGGLE SWITCHES**
rated 5 Amps
S.P.D.T. (ON-ON)
Non threaded brushing
P.C. mount.
CAT# MTS-40PC
75c each
10 for \$7.00
- S.P.D.T. (ON-ON)**
Solder lug terminals.
CAT# MTS-4
\$1.00 each
10 for \$9.00
- D.P.D.T. (ON-ON)**
Solder lug terminals.
CAT# MTS-8
\$2.00 each
10 for \$19.00

MINI PUSH BUTTON

S.P.S.T. momentary. Push to make 1/4" brushing. Red button.
CAT# MPB-1 35c each
10 for \$3.00

POLARITY SWITCH

Designed to control an external coaxial relay on a satellite t.v. system. Ideal for parts. Contains a 5 Vdc relay and many other parts on a P.C. board.
CAT# RPDS \$1.75 each 10 for \$15.00



STORES:
LOS ANGELES
905 S. VERMONT AVE.
LOS ANGELES, CA 90006
(213)380-8000
VAN NUYS
6228 SEPULVEDA BLVD.
VAN NUYS, CA 91411
(818)997-1806

MAIL ORDERS TO:
ALL ELECTRONICS
P.O. BOX 567
VAN NUYS, CA 91408
TELEX
TWX-5101010163
ALL ELECTRONICS
Foreign Customers
Send \$1.50 postage
for FREE Catalog!!

TOLL FREE
800-826-5432
INFO:(818)904-0524
FAX:(818)781-2653
QUANTITIES LIMITED
MINIMUM ORDERS \$10.00
CALIF. ADD SALES TAX
USA: \$3.00 SHIPPING
NO C.O.D.I
FOREIGN ORDERS:
INCLUDE SUFFICIENT
SHIPPING

SOUND AND VIDEO MODULATOR
T# UM1381-1. Designed for use with T.I. computers. Can be used with video cameras, games or other audio/video sources. Built in A/B switch enables user to switch from T.V. antenna without disconnection. Operates on channel 3 or 4. Requires 12 Vdc. Hook up diagram included.
CAT# AVMOD \$5.00 each

TELEPHONE COUPLING TRANSFORMER
STANCOR # TTCP-8
600 ohms c.t.
to 600 ohms c.t.
P.C. board mount.
3/4" X 5/8" X 3/4"
CAT# TCTXS
\$2.50 each

256K STATIC 150ns 32K x 8 \$12.95 256K DRAMS 150ns 256K x 1 \$2.95

STATIC RAMS

2112	256x4	(450ns)	2.99
2114	1024x4	(450ns)	.99
2114L-2	1024x4	(200ns)(Low Power)	1.49
TMM2016-100	2048x8	(100ns)	1.95
HM6116-4	2048x8	(200ns)(CMOS)	1.79
HM6116-3	2048x8	(150ns)(CMOS)	3.25
HM6116L-4	2048x8	(200ns)(CMOS)(LP)	1.85
HM6116L-3	2048x8	(150ns)(CMOS)(LP)	1.90
HM6116L-2	2048x8	(120ns)(CMOS)(LP)	2.45
HM6264LP-15	8192x8	(150ns)(CMOS)(LP)	3.95
HM6264LP-12	8192x8	(120ns)(CMOS)(LP)	4.49
HM43256LP-15	32768x8	(150ns)(CMOS)(LP)	12.95
HM43256LP-12	32768x8	(120ns)(CMOS)(LP)	14.95
HM43256LP-10	32768x8	(100ns)(CMOS)(LP)	19.95

DYNAMIC RAMS

4116-250	16384x1	(250ns)	.49
4116-200	16384x1	(200ns)	.89
4116-150	16384x1	(150ns)	.99
4116-120	16384x1	(120ns)	1.49
MK4332	32768x1	(200ns)	6.95
4164-150	65536x1	(150ns)	1.29
4164-120	65536x1	(120ns)	1.55
MCM6665	65536x1	(200ns)	1.95
TMS4164	65536x1	(150ns)	1.95
4164-REFRESH	65536x1	(150ns)(PIN 1 REFRESH)	2.95
TMS4416	16384x4	(150ns)	3.75
41128-150	131072x1	(150ns)	3.95
TMS4464-15	65536x4	(150ns)	4.95
41256-150	262144x1	(150ns)	2.95
41256-120	262144x1	(120ns)	3.95
41256-100	262144x1	(100ns)	4.95
HM51258-100	1048576x1	(100ns)(CMOS)	6.95
1 MB-120	1048576x1	(120ns)	19.95
1 MB-100	1048576x1	(100ns)	24.95

EPROMS

2708	1024x8	(450ns)	4.95
2716	2048x8	(450ns)(5V)	3.49
2716-1	2048x8	(350ns)(5V)	3.95
TMS2532	4096x8	(450ns)(5V)	5.95
2732	4096x8	(450ns)(5V)	3.95
2732A	4096x8	(250ns)(5V)(21V PGM)	3.95
2732A-2	4096x8	(200ns)(5V)(21V PGM)	4.25
27C64	8192x8	(250ns)(5V)(CMOS)	4.95
2764	8192x8	(450ns)(5V)	3.49
2764-250	8192x8	(250ns)(5V)	3.65
2764-200	8192x8	(200ns)(5V)	4.29
MCM68766	8192x8	(350ns)(5V)(24 PIN)	15.95
27128	16384x8	(250ns)(5V)	4.25
27C256	32768x8	(250ns)(5V)(CMOS)	7.95
27256	32768x8	(250ns)(5V)	5.95
27512	65536x8	(250ns)(5V)	11.95
27C512	65536x8	(250ns)(5V)(CMOS)	12.95

25V=Single 5 Volt Supply
21V PGM=Program at 21 Volts

★ ★ ★ ★ HIGH-TECH ★ ★ ★ ★ HM43256LP-15 \$12.95

- ★ 32K x 8 STATIC RAM
- ★ LOW POWER CONSUMPTION
- ★ HIGH SPEED — 100ns AVAILABLE
- ★ LOW STAND-BY CURRENT (2mA MAX.)
- ★ TTL COMPATIBLE INPUT AND OUTPUTS

★ ★ ★ ★ SPOTLIGHT ★ ★ ★ ★

CMOS

4001	.19	4049	.29
4011	.19	4050	.29
4012	.25	4051	.69
4013	.35	4052	.69
4015	.29	4053	.69
4016	.29	4060	.69
4017	.49	4066	.29
4018	.69	4069	.19
4020	.59	4070	.29
4021	.69	4081	.22
4023	.25	4093	.49
4024	.49	14411	9.95
4025	.25	14433	14.95
4027	.39	14497	6.95
4028	.65	4503	4.49
4040	.69	4511	.69
4042	.59	4518	.85
4044	.69	4528	.79
4046	.69	4538	.95
4047	.69	4702	12.95

HIGH SPEED CMOS

74HC00		74HCT00	
74HC00	.21	74HCT00	.25
74HC02	.21	74HCT02	.25
74HC04	.25	74HCT04	.27
74HC08	.25	74HCT08	.25
74HC14	.35	74HCT32	.27
74HC32	.35	74HCT74	.45
74HC74	.35	74HCT138	.55
74HC86	.45	74HCT151	.55
74HC138	.45	74HCT244	.89
74HC151	.59	74HCT245	.99
74HC154	1.09	74HCT273	.99
74HC157	.55	74HCT373	.99
74HC244	.85	74HCT374	.99
74HC245	.85	74HCT393	.99
74HC273	.69	74HCT401	1.19
74HC374	.69	74HCT404	.99
74HC374	.69	74HCT4060	1.49

TOLL FREE U.S. & CANADA (800) 538-5000

74LS00

74LS00	.16	74LS112	.29	74LS241	.69
74LS01	.17	74LS122	.45	74LS242	.69
74LS02	.17	74LS123	.49	74LS243	.69
74LS03	.18	74LS124	2.75	74LS244	.69
74LS04	.16	74LS125	.39	74LS245	.79
74LS05	.18	74LS126	.39	74LS251	2.39
74LS08	.18	74LS132	.39	74LS253	.49
74LS09	.18	74LS133	.49	74LS257	.39
74LS10	.16	74LS136	.39	74LS258	.49
74LS11	.22	74LS138	.39	74LS259	1.29
74LS12	.22	74LS139	.39	74LS260	.49
74LS13	.26	74LS145	.99	74LS266	.39
74LS14	.39	74LS147	.99	74LS273	.79
74LS15	.26	74LS148	.99	74LS279	.39
74LS20	.17	74LS151	.39	74LS280	1.98
74LS21	.22	74LS153	.39	74LS283	.59
74LS22	.22	74LS154	1.49	74LS290	.89
74LS27	.23	74LS155	.59	74LS293	.89
74LS28	.26	74LS156	.49	74LS299	1.49
74LS30	.17	74LS157	.35	74LS322	3.95
74LS32	.18	74LS158	.29	74LS323	2.49
74LS33	.29	74LS159	.29	74LS365	.39
74LS37	.26	74LS161	.39	74LS367	.39
74LS38	.26	74LS162	.49	74LS368	.39
74LS42	.39	74LS163	.39	74LS373	.79
74LS47	.75	74LS164	.49	74LS374	.79
74LS48	.85	74LS165	.65	74LS375	.95
74LS51	.17	74LS166	.95	74LS377	.79
74LS73	.29	74LS167	.39	74LS381	1.29
74LS74	.24	74LS173	.49	74LS393	.79
74LS75	.29	74LS174	.39	74LS541	1.49
74LS76	.29	74LS175	.39	74LS624	1.95
74LS83	.49	74LS191	.49	74LS640	.99
74LS85	.49	74LS192	.69	74LS645	.99
74LS86	.22	74LS193	.69	74LS670	.89
74LS90	.39	74LS194	.69	74LS682	3.20
74LS92	.49	74LS195	.69	74LS695	2.40
74LS93	.39	74LS196	.59	74LS783	22.95
74LS95	.49	74LS197	.59	25LS2521	2.80
74LS107	.34	74LS221	.59	26LS31	1.95
74LS109	.36	74LS240	.69	26LS32	1.95

7400

7400	.19
7402	.19
7404	.19
7406	.29
7407	.29
7408	.29
7410	.19
7411	.25
7414	.49
7416	.25
7417	.25
7420	.19
7430	.19
7432	.29
7438	.29
7442	.49
7445	.69
7447	.89
7473	.34
7474	.34
7475	.45
7476	.35
7483	.50
7485	.59
7486	.35
7489	2.15
7490	.39
7493	.35
74121	.29
74123	.49
74125	.45
74150	1.35
74151	.55
74153	.55
74154	1.49
74157	.55
74159	1.65
74161	.89
74165	.85
74166	1.00
74175	.89
74367	.65

LINEAR

LM567	.79
NE570	2.95
NE592	.98
LM723	.49
LM733	.98
LM734	.98
LM747	.69
MC1300	1.69
MC1350	1.19
LM1458	.35
LM1488	.49
LM1489	.49
LM1496	.85
ULN2003	.79
XR206	3.95
KR2211	2.95
LM2917	1.95
CA3046	.89
CA3146	1.29
MC3273	1.25
MC3470	1.95
MC3480	8.95
MC3487	2.95
LM3900	.49
LM3911	2.25
LM3919	.98
LM3914	1.89
MC4024	3.49
MC4044	3.95
RC136	1.25
RC4558	.69
LM13600	1.49
75107	1.49
75110	1.95
75150	1.95
75154	1.95
75188	1.25
75189	1.25
75195	.35
75452	1.49
75454	1.49
75477	1.29
H-TO-5 CAN, K-TO-3, T-TO-220	

8000

8031	3.95
8035	1.49
8039	1.95
8052AH BASIC	34.95
8080	2.49
8085	1.95
8086	6.49
8087 5MHz	99.00
8087-2 8MHz	159.95
8088	5.95
8088-2	7.95
8155	2.49
8741	2.99
8748	7.95
8749	12.95
8755	14.95
80286	79.95
80287 6MHz	179.95
80287-8 8MHz	249.95
80287-10 10MHz	309.95

6500

1.0 MHz	
6502	2.25
65C02 (CMOS)	7.95
6520	1.65
6522	2.95
6526	13.95
6532	5.95
6545	2.95
6551	2.95
2.0 MHz	
6502A	2.69
6502A	2.95
6522A	5.95
6532A	11.95
6545A	3.95
6551A	6.95
3.0 MHz	
6502B	4.25

Z-80

2.5 MHz	
Z80-CPU	1.25
4.0 MHz	
Z80A-CPU	1.29
Z80A-CTC	1.69
Z80A-DART	5.95
Z80A-DMA	5.95
Z80A-PIO	1.89
Z80A-SIO '0	5.95
Z80A-SIO '1	5.95
Z80A-SIO '2	5.95
6.0 MHz	
Z80B-CPU	2.75
Z80B-CTC	4.25
Z80B-PIO	4.25
Z80B-DART	6.95
Z80B-SIO '0	12.95
Z80B-SIO '2	12.95
Z8671 ZILOG	9.95

DISK CONTROLLERS

1771	4.95
1791	9.95
1792	9.95
1795	12.95
1797	12.95
1919	19.95
1939	19.95
2797	29.95
8272	4.39
UPD7665	4.39
MB8876	12.95
MB8877	12.95
1691	6.95
2143	6.95
9216	6.29

V 20 SERIES

V20* 5 MHz	8.95
V20* 8 MHz	10.95
V30 8 MHz	13.95

*Replaces 8088 to speed up your PC by 10 to 40%

CRYSTALS

32.768 KHz	.95
1.0 MHz	2.95
1.8432	2.95
2.0	1.95
2.4576	1.95
3.579545	1.95
4.0	1.95
5.0	1.95
5.0688	1.95
6.0	1.95
6.144	1.95
8.0	1.95
10.0	1.95
10.738635	1.95
12.0	1.95
14.31818	1.95
16.0	1.95
18.0	1.95
18.432	1.95
20.0	1.95
22.1184	1.95
24.0	1.95
32.0	1.95

UARTS

AY5-1013	3.95
AY3-1015	4.95

20 MEG HARD DISK DRIVE ON A CARD \$349!

CAPACITORS TANTALUM

1.0µf	15V	12	47µf	35V	.39
6.8	15V	42	1.0	50V	.45
10	15V	45	2.2	35V	.19
22	15V	99	4.7	35V	.39
22	35V	.15	10	35V	.69

DISC

10µf	50V	.05	680	50V	.05
22	50V	.05	.001µf	50V	.05
27	50V	.05	.0022	50V	.05
33	50V	.05	.005	50V	.05
47	50V	.05	.01	50V	.07
68	50V	.05	.02	50V	.07
100	50V	.05	.05	50V	.07
220	50V	.05	.1	12V	.10
560	50V	.05	.1	50V	.12

MONOLITHIC

.01µf	50V	.14	1µf	50V	.18
.047µf	50V	.15	47µf	50V	.25

ELECTROLYTIC

RADIAL		AXIAL			
1µf	25V	14	1µf	50V	.14
2.2	35V	11	10	50V	.16
4.7	50V	11	22	16V	.14
10	50V	11	47	50V	.19
47	35V	.13	100	35V	.19
100	16V	.15	220	25V	.25
220	35V	.20	470	50V	.29
470	25V	.30	1000	16V	.29
2200	16V	.70	2200	16V	.70
4700	25V	1.45	4700	16V	1.25

FRAME STYLE TRANSFORMERS

12.6 Volts AC	2 Amps (CT)	5.95
12.6 Volts AC	4 Amps (CT)	7.95
12.6 Volts AC	8 Amps (CT)	10.95
25.2 Volts AC	2 Amps (CT)	7.95

36 PIN CENTRONICS MALE

IDCEN36	RIBBON CABLE	3.95
CEN36	SOLDER CUP	1.85

FEMALE

IDCEN36/F	RIBBON CABLE	4.95
CEN36PC	RT. Angle PC Mount	1.85

EDGE CARD CONNECTORS

100 Pin Soldertail S-100	125	3.95
100 Pin Wirewrap S-100	125	4.95
62 Pin Soldertail IBM PC	100	1.95
50 Pin Soldertail APPLE	100	2.95
44 Pin Soldertail STD	156	1.95
44 Pin Wirewrap STD	156	4.95

VOLTAGE REGULATORS

TO-220 CASE		TO-3 CASE	
7805T	.49	7805K	1.59
7808T	.49	7812K	1.39
7812T	.49	7912K	1.49
7815T	.49		
7905T	.59		
7908T	.59		
7912T	.59	78L05	49
7915T	.59	79LJ5	.69
		79L12	1.49
LM323K	5 VOLTS, 3 AMPS, TO-3		4.79
LM338K	ADJUSTABLE, 5 AMPS, TO-3		6.95

RESISTOR NETWORKS

SIP	10 PIN	9 RESISTOR	.69
SIP	8 PIN	7 RESISTOR	.59
DIP	16 PIN	8 RESISTOR	1.09
DIP	16 PIN	15 RESISTOR	1.09
DIP	14 PIN	7 RESISTOR	.99
DIP	14 PIN	13 RESISTOR	.99

BYPASS CAPACITORS

.01 µf CERAMIC DISC	100/\$5.00
.01 µf MONOLITHIC	10C/\$10.00
.1 µf CERAMIC DISC	10C/\$6.50
.1 µf MONOLITHIC	10C/\$12.50

DISCRETE

1N751	.15
1N759	.15
1N4148 25/1.00	1.00
1N4004 10/1.00	1.00
1N5402	.25
KBPO2	.55
KBUBA	.95
MDA990-2	.35
N2222	.25
PN2222	1.0
2N2905	.50
2N2907	.25
2N3055	.79
2N3904	.10
4N26	.69
4N27	.69
4N28	.69
4N33	.89
4N37	1.19
MCT-2	.59
MCT-6	1.29
TIL-111	2.25
2N3906	.10
2N4011	.25
2N4402	.25
2N4403	.25
2N6045	1.75
TIP31	.49

IC SOCKETS

SOLDERTAIL	1-99	100+
8 PIN ST	1.11	.10
14 PIN ST	1.11	.09
16 PIN ST	1.12	.10
18 PIN ST	1.15	.13
20 PIN ST	1.18	.15
22 PIN ST	1.15	.12
24 PIN ST	1.20	.15
28 PIN ST	1.22	.16
40 PIN ST	1.30	.22
64 PIN ST	1.95	1.49

WIREWRAP	
8 PIN WW	.59
14 PIN WW	.69
16 PIN WW	.69
18 PIN WW	.99
20 PIN WW	1.09
22 PIN WW	1.39
24 PIN WW	1.49
28 PIN WW	1.69
40 PIN WW	1.99

ZERO INSERTION FORCE	
16 PIN ZIF	4.95
24 PIN ZIF	5.95
28 PIN ZIF	6.95
40 PIN ZIF	9.95

WISH SOLDERLESS BREADBOARDS

PART NUMBER	DIMENSIONS	DISTRIBUTION STRIP(S)	TIE POINTS	TERMINAL STRIP(S)	TIE POINTS	BINDING POSTS	PRICE
WBU-D	.38 x 6.50"	1	100	---	---	---	2.95
WBU-T	1.38 x 6.50"	---	---	1	630	---	6.95
WBU-204-3	3.94 x 8.45"	1	100	2	1260	2	17.95
WBU-204	5.13 x 8.45"	4	400	2	1260	3	24.95
WBU-206	6.88 x 9.06"	5	500	3	1890	4	29.95
WBU-208	8.25 x 9.45"	7	700	4	2520	4	39.95

EXTENDER CARDS FOR IBM

EXT-8088	\$29.95
EXT-80286	\$39.95



SHORTING BLOCKS

1" CENTERS	GOLD CONTACTS
5/\$1.00	

WHY THOUSANDS CHOOSE JDR

- ★ QUALITY MERCHANDISE
- ★ COMPETITIVE PRICES
- ★ MOST ORDERS SHIPPED IN 24 HOURS
- ★ FRIENDLY, KNOWLEDGEABLE STAFF
- ★ MONEY BACK GUARANTEE (ASK FOR DETAILS)
- ★ TOLL FREE TECHNICAL SUPPORT
- ★ EXCELLENT CUSTOMER SERVICE



EPROM ERASERS

SPECTRONICS CORPORATION				
Model	Timer	Chip Capacity	Intensity (µW/cm²)	Unit Cost
PE-140	NO	9	8,000	\$89
PE-140T	YES	9	8,000	\$139
PE-240T	YES	12	9,600	\$189

DATARASE \$34.95

- ERASES 2 EPROMS IN 10 MINUTES TIME
- VERY COMPACT—NO DRAWER
- THIN METAL SHUTTER PREVENTS UV LIGHT FROM ESCAPING

LIGHT EMITTING DIODES

LED DISPLAYS	
FND-357(359)	COM CATHODE 362" 1.25
FND-500(503)	COM CATHODE 5" 1.49
FND-507(510)	COM ANODE 5" 1.49
MAN-72	COM ANODE 3" .99
MAN-74	COM CATHODE 3" .99
TIL-313	COM CATHODE 3" .45
TIL-311	4x7 HEX W/ LOGIC 270" 10.95
DIFFUSED LEDS	
JUMBO RED	T1 1/4 .10
JUMBO GREEN	T1 1/4 .14
JUMBO YELLOW	T1 1/4 .14
MOUNTING HDW	T1 1/4 .10
MINI RED	T1 .10

RIBBON CABLE

CONTACTS	SINGLE COLOR		COLOR CODED	
	1'	10'	1'	10'
10	.18	1.60	.30	2.75
16	.28	2.50	.48	4.40
20	.36	3.20	.60	5.50
25	.45	4.00	.75	6.85
26	.46	4.10	.78	7.15
34	.55	5.40	1.07	9.35
40	.72	6.40	1.20	11.00
50	.89	7.50	1.50	13.25

WIREWRAP PROTOTYPE CARDS FR-4 EPOXY GLASS LAMINATE WITH GOLD-PLATED EDGE-CARD FINGERS

XT	
IBM-PR1	WITH +5V AND GROUND PLANE . . . \$27.95
IBM-PR2	AS ABOVE W/ DECODING LAYOUT . . . \$29.95

AT	
IBM-PRAT	LARGE +5V & GROUND PLANES . . . \$29.95
S-100	
P100-1	BARE - NO FOIL PADS . . . \$15.15
P100-2	HORIZONTAL BUS . . . \$21.80
P100-3	VERTICAL BUS . . . \$21.80
P100-4	SINGLE FOIL PADS PER HOLE . . . \$22.75

APPLE	
P500-1	BARE - NO FOIL PADS . . . \$15.15
P500-3	HORIZONTAL BUS . . . \$22.75
P500-4	SINGLE FOIL PADS PER HOLE . . . \$21.80
7060-45	FOR APPLE IIe AUX SLOT . . . \$30.00

PAGE WIRE WRAP WIRE PRECUT ASSORTMENT IN ASSORTED COLORS \$27.50

100ea: 5.5", 6.0", 6.5", 7.0"	
250ea: 2.5", 4.5", 5.0"	
500ea: 3.0", 3.5", 4.0"	
SPOOLS	
100 feet	\$4.30
250 feet	\$7.25
500 feet	\$13.25
1000 feet	\$21.95

Please specify color:
Blue, Black, Yellow or Red

SOCKET-WRAP I.D.™

- SLIPS OVER WIRE WRAP PINS
 - IDENTIFIES PIN NUMBERS ON WRAP SIDE OF BOARD
 - CAN WRITE ON THE PLASTIC, SUCH AS AN IC #
- | Pins | Part # | Pck. of | Price |
|------|-----------|---------|-------|
| 8 | IDWRAP 08 | 10 | 1.95 |
| 14 | IDWRAP 14 | 10 | 1.95 |
| 16 | IDWRAP 16 | 10 | 1.95 |
| 18 | IDWRAP 18 | 5 | 1.95 |
| 20 | IDWRAP 20 | 5 | 1.95 |
| 22 | IDWRAP 22 | 5 | 1.95 |
| 24 | IDWRAP 24 | 5 | 1.95 |
| 28 | IDWRAP 28 | 5 | 1.95 |
| 40 | IDWRAP 40 | 5 | 1.95 |
- PLEASE ORDER BY NUMBER OF PACKAGES (PCK. OF)

SWITCHES

SPDT	MINI-TOGGLE ON-ON	1.25
DPDT	MINI-TOGGLE ON-ON	1.50
DPDT	MINI-TOGGLE ON-OFF ON	1.75
SPST	MINI-PUSHBUTTON N/O	.39
SPST	MINI-PUSHBUTTON N/C	.39
BCD	OUTPUT 10 POS. 6 PIN DIP	1.95
DIP SWITCHES		
4 position	.85	7 position .95
5 position	.90	8 position .95
6 position	.90	10 position 1.29

"SNAPABLE" HEADERS

- CAN BE SNAPPED APART TO MAKE ANY SIZE HEADER, ALL WITH 1" CENTERS
- | | | |
|------|---------------------|------|
| 1x40 | STRAIGHT LEAD | .99 |
| 1x40 | RIGHT ANGLE LEAD | 1.49 |
| 2x40 | 2 STRAIGHT LEADS | 2.49 |
| 2x40 | 2 RIGHT ANGLE LEADS | 2.99 |

25 PIN D-SUB GENDER CHANGERS \$7.95

MUFFIN FANS	
3.15" Sq	\$14.95
3.63" Sq	\$14.95
3.18" Square	\$16.95
LINE CORDS	
2 conductor 39c	3 conductor 99c
3 conductor w/ female socket	\$1.49

IDC CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS					
		10	20	26	34	40	50
SOLDER HEADER	IDHxxS	.82	1.29	1.68	2.20	2.58	3.24
RIGHT ANGLE SOLDER HEADER	IDHxxSR	.85	1.35	1.76	2.31	2.72	3.39
WIREWRAP HEADER	IDHxxW	1.86	2.98	3.84	4.50	5.28	6.30
RIGHT ANGLE WIREWRAP HEADER	IDHxxWR	2.05	3.28	4.22	4.45	4.80	7.30
RIBBON HEADER SOCKET	IDSxx	.63	.89	.95	1.29	1.49	1.69
RIBBON HEADER	IDMxx	---	5.50	6.25	7.00	7.50	8.50
RIBBON EDGE CARD	IDExx	.85	1.25	1.35	1.75	2.05	2.45

FOR ORDERING INSTRUCTIONS, SEE D-SUBMINIATURE CONNECTORS, BELOW

D-SUBMINIATURE CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS						
		9	15	19	25	37	50	
SOLDER CUP	MALE	DBxxP	.45	.59	.69	.69	1.35	1.85
	FEMALE	DBxxS	.49	.69	.75	.75	1.39	2.29
RIGHT ANGLE PC SOLDER	MALE	DBxxPR	.49	.69	---	.79	2.27	---
	FEMALE	DBxxSR	.55	.75	---	.85	2.49	---
WIREWRAP	MALE	DBxxPWW	1.69	2.56	---	3.89	5.60	---
	FEMALE	DBxxSww	2.76	4.27	---	6.84	9.95	---
IDC RIBBON CABLE	MALE	IDBxxP	1.39	1.99	---	2.25	4.25	---
	FEMALE	IDBxxS	1.45	2.05	---	2.35	4.49	---
HOODS	METAL	MHOODxx	1.05	1.15	1.25	1.25	---	---
	GREY	HOODxx	.39	.39	---	.39	.69	.75

ORDERING INSTRUCTIONS: INSERT THE NUMBER OF CONTACTS IN THE POSITION MARKED "xx" OF THE "ORDER BY" PART NUMBER LISTED. EXAMPLE: A 15 PIN RIGHT ANGLE MALE PC SOLDER WOULD BE DB15PR.

MOUNTING HARDWARE 59C

DIP CONNECTORS

DESCRIPTION	ORDER BY	CONTACTS								
		8	14	16	18	20	22	24	28	40
TOOLED SOLDERTAIL IC SOCKETS	AUGATxxST	.62	.79	.89	1.09	1.29	1.39	1.49	1.69	2.49
TOOLED WIREWRAP IC SOCKETS	AUGATxxWW	1.30	1.80	2.10	2.40	2.50	2.90	3.15	3.70	5.40
COMPONENT CARRIES (DIP HEADERS)	ICCxx									

4164 150ns \$129

41256 150ns \$295

MONITOR STANDS

- MODEL MS-100 \$12.95**
 • TILTS & SWIVELS • STURDY PLASTIC CONSTRUCTION
- MODEL MS-200 \$39.95**
 • TILTS AND SWIVELS • BUILT-IN SURGE SUPPRESSOR
 • BUILT-IN POWER STATION INDEPENDENTLY CONTROLS UP TO 5 120 VOLT AC OUTLETS • UL APPROVED



NASHUA DISKETTES

- BOXES OF 10** 5 1/4" DS/DD SOFT SECTOR
- 5 1/4" DS/DD 360K \$9.95 **49¢ ea 39¢ ea**
- 5 1/4" DS/HD 9 2M \$24.95 BULK QTY 50 BULK QTY 250
- 3 1/2" DS/QD 720K \$16.95

5 1/4" DISKETTE STORAGE FILE \$8.95

- HOLDS 70 5 1/4" FLOPPIES
 • STURDY, ATTRACTIVE SMOKEED ACRYLIC CASE
 • COMPLETE WITH HINGED DIVIDERS
- VERSION FOR 3 1/2" FLOPPIES AVAILABLE \$9.95**



2 WAY SWITCH BOXES \$39.95

- CONNECT 2 PRINTERS TO 1 COMPUTER OR VICE VERSA
 • SERIAL & PARALLEL MODELS AVAILABLE
 • ALL LINES SWITCHED
 • GOLD PLATED CONNECTORS & QUALITY SWITCHES



6' INTERFACE CABLES

- MEETS FCC REQUIREMENTS 100% SHIELDED
- IBM COMPATIBLE PARALLEL PRINTER \$9.95
 CENTRONICS (MALE TO FEMALE) \$15.95
 CENTRONICS (MALE TO MALE) \$14.95
 IBM COMPATIBLE MODEM CABLE \$7.95
 RS232 SERIAL (MALE TO FEMALE) \$9.95
 RS232 SERIAL (MALE TO MALE) \$9.95
 COILED KEYBOARD EXTENDER \$7.95


JOYSTICK \$19.95

- SET X-Y AXIS FOR AUTO CENTER OR FREE MOVEMENT
 • FIRE BUTTON FOR USE WITH GAME SOFTWARE
 • INCLUDES ADAPTOR CABLE FOR IBM



SWITCHING POWER SUPPLIES

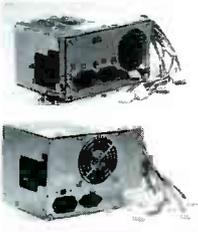- PS-135 \$59.95**
 • FOR IBM XT COMPATIBLE
 • UL APP. 135 WATTS
 • 5V 15A, 12V 4.2A
 • 5V 5A, 12V 5A
 • ONE YEAR WARRANTY
- PS-150 150W MODEL \$69.95**
- PS-200 \$89.95**
 • FOR IBM AT COMPATIBLE
 • 200 WATTS
 • 5V 22A, 12V 8A
 • 5V 5A, 12V 5A
 • ONE YEAR WARRANTY



MONITORS

SAMSUNG MONOCHROME

- IBM COMPATIBLE TTL INPUT
 • 12" NON-GLARE, LOW DISTORTION, AMBER SCREEN
 • RES: 720 x 350
 • SWIVEL BASE
 • 1 YEAR WARRANTY
- \$119.95**



MULTISYNC BY NEC \$549.95

- ORIGINAL CGA EGA/PGA COMPATIBLE MONITOR
 • AUTO FREQUENCY ADJUSTMENT
 • RESOLUTION AS HIGH AS 800 x 560

EGA BY CASPER \$399.95

- 15.75/21.85 KHz SCANNING FREQUENCIES
 • RES: 640 x 200/350 • 31mm DOT PITCH
 • 14" BLACK MATRIX SCREEN • 16 COLORS FROM 64

RGB BY CASPER \$279.95

- COLOR/GREEN/AMBER SWITCH • RES: 640 x 240
 • RGB/IBM COMPATIBLE • 14" NON-GLARE SCREEN
 • 39mm DOT PITCH • CABLE FOR IBM PC INCLUDED

MONOCHROME BY HYUNDAI \$69.95

- IBM COMPATIBLE TTL INPUT
 • 12" NON-GLARE AMBER SCREEN
 • ATTRACTIVE CASING WITH A TILT/SWIVEL BASE


TOLL FREE U.S. & CANADA (800) 538-5000

20MB HARD DISK ON A CARD



- SAVES SPACE AND REDUCES POWER CONSUMPTION
 • IDEAL FOR PCs WITH FULL HEIGHT FLOPPIES
 • LEAVES ROOM FOR A HALF LENGTH CARD IN ADJACENT SLOT
- \$349**

RITEMAN II PRINTER

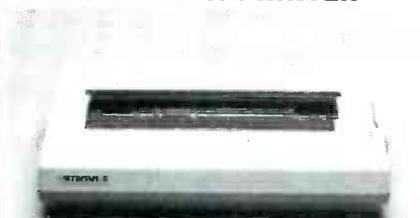

- 160 CPS DRAFT, 32 CPS NLQ MODE
 • SUPPORTS EPSON/IBM GRAPHICS
 • 9 x 9 DOT MATRIX
 • FRICTION AND PIN FEEDS
 • VARIABLE LINE SPACING & PITCH
- \$219.95**
- IBM COMPATIBLE PRINTER CABLE \$9.95
 REPLACEMENT RIBBON CARTRIDGE \$7.95

DISK DRIVES

5 1/4" SEAGATE HARD DISK DRIVES

- | | | | |
|---------|------------------|------------|-------|
| ST-225 | HALF HEIGHT 20MB | 65ms | \$259 |
| ST-238 | HALF HEIGHT 30MB | 65ms (RLL) | \$299 |
| ST-251 | HALF HEIGHT 40MB | 40ms | \$469 |
| ST-277 | HALF HEIGHT 60MB | 40ms (RLL) | \$649 |
| ST-4038 | FULL HEIGHT 30MB | 40ms | \$559 |
| ST-4096 | FULL HEIGHT 80MB | 28ms | \$895 |

1/2 HEIGHT FLOPPY DISK DRIVES

- | | | |
|------------------------------------|------|----------|
| 5 1/4" TEAC FD-55B DS/DD | 360K | \$109.95 |
| 5 1/4" TEAC FD-55F DS/QUAD | 720K | \$124.95 |
| 5 1/4" TEAC FD-55GFV DS/HD | 1.2M | \$154.95 |
| 5 1/4" MITSUBISHI DS/HD | 1.2M | \$119.95 |
| 5 1/4" DS/DD | 360K | \$69.95 |
| 3 1/2" MITSUBISHI DS/DD (AT OR XT) | | \$129.95 |

DISK DRIVE ACCESSORIES

- | | |
|----------------------------------|---------|
| TEAC SPECIFICATION MANUAL | \$5.00 |
| TEAC MAINTENANCE MANUAL | \$25.00 |
| 1/2 HT MOUNTING HARDWARE FOR IBM | \$2.95 |
| MOUNTING RAILS FOR IBM AT | \$4.95 |
| "Y" POWER CABLE FOR 5 1/4" FDDs | \$2.95 |
| 5 1/4" FDD POWER CONNECTORS | \$1.19 |

DRIVE ENCLOSURES WITH POWER SUPPLIES

- | | | |
|----------|--------------------------|----------|
| CAB-2SV5 | DUAL SLIMLINE FOR 5 1/4" | \$49.95 |
| CAB-1FH5 | FULL HEIGHT FOR 5 1/4" | \$69.95 |
| CAB-2SV8 | DUAL SLIMLINE FOR 8" | \$209.95 |
| CAB-2FH8 | DUAL FULL HEIGHT FOR 8" | \$219.95 |

EASYDATA MODEMS

All models feature auto-dial/answer/redial on busy, power up self test, touchtone or pulse dialing, built-in speaker, Hayes and Bell Systems 103 & 212A compatible, full or half duplex, PC Talk III Communications software with internal modems and more.



INTERNAL

- | | | |
|-----|---------------------|----------|
| 12H | 1200 BAUD 1/2 CARD | \$69.95 |
| 24B | 2400 BAUD FULL CARD | \$179.95 |


EXTERNAL

(NO SOFTWARE INCLUDED)


- | | | |
|-----|-----------|----------|
| 12D | 1200 BAUD | \$119.95 |
| 24D | 2400 BAUD | \$219.95 |

COMPUTER CASES

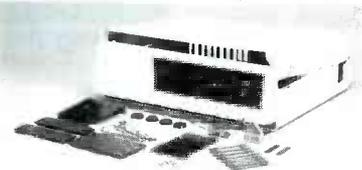Attractive, sturdy steel cases fit the popular sized motherboards and include speakers, faceplates, expansion slots and all necessary hardware.



- | | |
|--|----------|
| XT STYLE FLIP-TOP | \$34.95 |
| XT STYLE SLIDE-TOP | \$39.95 |
| AT STYLE SLIDE-TOP | \$89.95 |
| • FRONT PANEL KEYLOCK AND LED INDICATORS | |
| JR. AT STYLE FLIP-TOP | \$149.95 |
| • INCLUDES 180 WATT POWER SUPPLY | |
| • FRONT PANEL KEYLOCK AND LED INDICATORS | |

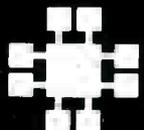

Visit our retail store located at 1256 S. Bascom Ave. in San Jose, (408) 947-8881

JDR Microdevices

110 Knowles Drive, Los Gatos, CA 95030

Toll Free 800-538-5000 • (408) 866-6200

FAX (408) 378-8927 • Telex 171-110

PLEASE USE YOUR CUSTOMER NUMBER WHEN ORDERING

TERMS: Minimum order \$10.00. For shipping and handling include \$2.50 for UPS Ground and \$3.50 for UPS Air. Orders over 1 lb. and foreign orders may require additional shipping charges—please contact our sales department for the amount. CA. residents must include applicable sales tax. All merchandise is warranted for 90 days unless otherwise stated. Prices are subject to change without notice. We are not responsible for typographical errors. We reserve the right to limit quantities and to substitute manufacturer. All merchandise subject to prior sale. A full copy of our terms is available upon request. Items pictured may only be representative.

COPYRIGHT 1987 JDR MICRODEVICES

THE JDR MICRODEVICES LOGO IS A REGISTERED TRADEMARK OF JDR MICRODEVICES. JDR INSTRUMENTS AND JDR MICRODEVICES ARE TRADEMARKS OF JDR MICRODEVICES. IBM IS A TRADEMARK OF INTERNATIONAL BUSINESS MACHINES CORPORATION. APPLE IS A TRADEMARK OF APPLE COMPUTER.

CIRCLE 183 ON FREE INFORMATION CARD

www.americanradiohistory.com

8087 5MHz \$9900

80287 6 MHz \$17995

INTERFACE CARDS

FROM MODULAR CIRCUIT TECHNOLOGY

MULTIFUNCTION CARDS

MCT-MF MULTIFUNCTION \$7995

ALL THE FEATURES OF 6 PACK- AT HALF THE PRICE
• 0-384K DYNAMIC RAM USING 4164s
• SERIAL, PARALLEL, GAME PORTS, CLOCK/CALENDAR

MCT-MGMIO MONOGRAPHS I/O \$11995

TOTAL SYSTEM CONTROL FROM A SINGLE SLOT
• 2 FLOPPY CONT, SERIAL, PARALLEL, GAME PORT, CLOCK/CAL
• RUN COLOR GRAPHICS SOFTWARE ON A MONOCHROME MONITOR

MCT-MIO MULTI I/O FLOPPY \$7995

A PERFECT COMPANION FOR OUR MOTHERBOARDS
• SERIAL, PARALLEL, GAME PORT, CLOCK/CALENDAR
• SUPPORTS UP TO 2 360K FLOPPIES, 720K WITH DOS 3.2

MCT-IO MULTI I/O CARD \$5995

USE WITH MCT-FH FOR A MINIMUM OF SLOTS USED
• SERIAL PORT, CLOCK/CALENDAR WITH A BATTERY BACK-UP
• PARALLEL PRINTER PORT ADDRESSABLE AS LPT1 OR LPT2

MCT-ATMF AT MULTIFUNCTION \$13995

ADDS UP TO 3 MEGABYTES OF RAM TO THE AT
• USER EXPANDABLE TO 1.5 MB OF MEMORY (ZERO K INSTALLED)
• INCLUDES SERIAL PORT AND PARALLEL PORT

MCT-ATIO AT MULTI I/O \$5995

USE WITH MCT-ATFH FOR A MINIMUM OF SLOTS USED
• SERIAL, PARALLEL AND GAME PORTS
• USES 16450 SERIAL SUPPORT CHIPS FOR HIGH SPEED OPERATION

MEMORY CARDS

MCT-RAM 576K RAM CARD \$5995

A CONTIGUOUS MEMORY SOLUTION IN A SHORT SLOT
• USER SELECTABLE CONFIGURATION AMOUNTS UP TO 576K USING 64K & 256K RAM CHIPS (ZERO K INSTALLED)

MCT-EMS EXPANDED MEMORY CARD \$12995

2 MB OF LOTUS/INTEL/MICROSOFT COMPATIBLE MEMORY FOR XT
• CONFORMS TO LOTUS/INTEL EMS • USER EXPANDABLE TO 2 MB
• EXPANDED/CONVENTIONAL MEMORY, RAMDISK AND SPOOLER

MCT-ATRAM AT 4 MB RAM CARD \$14995

A POWER USER'S DREAM 4 MB OF MEMORY FOR AT
• BACKFILL TO 640K, FLEXIBLE STARTING ADDRESS
• UP TO 2 MB ON CARD, 4 MB WITH OPTIONAL PIGGYBACK BOARD

MCT-ATEMS AT COMPATIBLE EMS \$13995

CAN BE USED FOR EXPANDED, EXTENDED OR CONVENTIONAL MEMORY
• CONFORMS TO LOTUS/INTEL EMS • USER EXPANDABLE TO 2 MB
• RAMDISK, PRINT SPOOLER AND LIM/EMS SOFTWARE INCLUDED

DRIVE CONTROLLERS

MCT-FDC FLOPPY DISK CONTROLLER \$2995

QUALITY DESIGN OFFERS 4 FLOPPY CONTROL IN A SINGLE SLOT
• INTERFACES UP TO 4 FDDs TO AN IBM PC OR COMPATIBLE
• SUPPORTS BOTH DS/DD AND DS/QD WITH DOS 3.2

MCT-HDC HARD DISK CONTROLLER \$7995

HD CONTROL FOR WHAT OTHERS CHARGE FOR FLOPPY CONTROL
• SUPPORTS 16 DRIVE SIZES INCLUDING 5, 10, 20, 30 & 40 MB
• DIVIDE 1 LARGE DRIVE INTO 2 SMALLER, LOGICAL DRIVES

MCT-FDC-1.2 1.2MB FLOPPY CONTROLLER \$6995

ADD VERSATILITY & CAPACITY TO YOUR XT
• SUPPORTS 2 DRIVES, BOTH MAY BE 360K OR 1.2 MEG
• ALLOWS DATA TO FLOW FREELY FROM XTs TO ATs

MCT-FH FLOPPY/HARD CONTROLLER \$13995

SYSTEM STARVED FOR SLOTS? SATISFY IT WITH THIS TIMELY DESIGN
• INTERFACES UP TO 2 FDDs & 2 HDDs, CABLING FOR 2 FDDs & 1 HDD
• SUPPORTS BOTH DS/DD & DS/QD WITH DOS 3.2

MCT-ATFH AT FLOPPY/HARD CONTROLLER \$14995

FLOPPY/HARD DISK CONTROL IN A TRUE AT DESIGN
• SUPPORTS UP TO 2 360K/720K/1.2MB FDDs
• AS WELL AS 2 HDDs USING STANDARD CONTROL TABLES

DISPLAY CARDS

MCT-EGA ENHANCED GRAPHICS ADAPTOR \$14995

100% IBM COMPATIBLE, PASSES IBM EGA DIAGNOSTICS
• 256K OF VIDEO RAM ALLOWS 640 x 350 IN 16 OF 64 COLORS
• COMPATIBLE WITH COLOR AND MONOCHROME ADAPTORS

MCT-CG COLOR GRAPHICS ADAPTOR \$4995

COMPATIBLE WITH IBM COLOR GRAPHICS STANDARDS
• SHORT SLOT SUPPORTS RGB, COLOR & COMPOSITE MONOCHROME
• 640/320 x 200 RESOLUTION, LIGHT PEN INTERFACE

MCT-MGP MONOCHROME GRAPHICS \$5995

TRUE HERCULES COMPATIBILITY, SUPPORTS LOTUS 123
• SOFTWARE DRIVER ALLOWS COLOR GRAPHICS PROGRAMS TO RUN ON A MONOCHROME MONITOR • PARALLEL PRINTER PORT

HALF HEIGHT HARD DISK DRIVES

40 MB \$469

Seagate model ST-251 5 1/4" half height FAST 40ms access time

60 MB \$649

Seagate model ST-277 5 1/4" half height FAST 40ms access time (RLL)

HALF HEIGHT HARD DISK SYSTEMS

20 MB \$289

30 MB \$329

Systems include Seagate 1/2 height hard drive, hard drive controller, cables and instructions. All drives are pre-tested and warranted for one year.

IBM COMPATIBLE MOTHERBOARDS

FROM MODULAR CIRCUIT TECHNOLOGY

MCT-TURBO TURBO 4.77/8 MHz \$10995

• 4.77 OR 8 MHz OPERATION WITH 8088-2 & OPTIONAL 8087-2 CO-PROCESSOR
• DYNAMICALLY ADJUSTS SPEED FOR MAXIMUM THROUGHPUT & RELIABILITY DURING DISK I/O
• CHOICE OF NORMAL/TURBO MODE OR SOFTWARE SELECT PROCESSOR SPEED

MCT-XTMB STANDARD MOTHERBOARD \$9795

MCT-ATMB 80286 6/8 MHz \$37995

• 8 SLOT (2 EIGHT BIT, 6 SIXTEEN BIT) AT MOTHERBOARD
• HARDWARE SELECTION OF 6 OR 8 MHz
• 1 WAIT STATE
• KEYLOCK SUPPORTED, RESET SWITCH, FRONT PANEL LED INDICATOR
• SOCKETS FOR 1 MB OF RAM AND 80287
• BATTERY BACKED CLOCK

MCT-BATMB MINI 80286 \$42995

• REPLACEMENT BOARD FOR XT STYLE CHASSIS
• OPERATE AT 6.10 MHz WITH UP TO 1MB ON-BOARD MEMORY (ZERO K INSTALLED)
• SOCKET FOR 80287 MATH CO-PROCESSOR
• BATTERY BACKED CLOCK
• 8 SLOTS: 2 EIGHT BIT, 6 SIXTEEN BIT
• USES CHIPS & TECHNOLOGY CHIP SET FOR RELIABILITY AND SMALL SIZE

IBM COMPATIBLE KEYBOARDS



MCT-5339 \$7995

• IBM ENHANCED STYLE LAYOUT
• SOFTWARE AUTOSENSE FOR XT OR AT COMPATIBLES
• LED INDICATORS
• AUTO REPEAT FEATURE
• SEPARATE CURSOR PAD

MCT-5060 \$5995

• IBM AT STYLE LAYOUT
• SOFTWARE AUTOSENSE FOR XT OR AT COMPATIBLES
• LED INDICATORS
• AUTO REPEAT FEATURE

MCT-5150 XT STYLE LAYOUT \$4995

MCT-5151 KB5151 EQUIV. \$6995

WHY BUY A SYSTEM FROM JDR?

- * BUILD IT YOURSELF AND SAVE
* QUALITY COMPONENTS AT COMPETITIVE PRICES
* TOLL FREE TECHNICAL SUPPORT IN THE U.S. AND CANADA
* MONEY BACK GUARANTEE (ASK FOR DETAILS)
* MORE THAN 10,000 SOLD!

I am very pleased with the computer system I purchased from you and all the outstanding support and courteous people on your staff. Your attitude & commitment to customer satisfaction is exceptional. YOUR ATTITUDE SHOULD BE INDUSTRY STANDARD.

Daryl Hammond

BUILD YOUR OWN 256K XT COMPATIBLE

- * MOTHERBOARD
* 256K OF MEMORY
* 135 WATT POWER SUPPLY
* FLIP-TOP CASE
* 5060 STYLE KEYBOARD
* 360K FLOPPY DRIVE
* DRIVE CONTROLLER
* MONOCHROME MONITOR
* GRAPHICS ADAPTOR

FOR ONLY \$49915

ANYONE CAN BUILD A SYSTEM IN ABOUT 2 HOURS USING A SCREWDRIVER AND OUR EASY-TO-FOLLOW INSTRUCTIONS!



DEVELOPMENT TOOLS

FROM MODULAR CIRCUIT TECHNOLOGY

MCT-EPROM PROGRAMMER \$12995

PROGRAMS 27xx & 27xxx EPROMS UP TO 27512
• SUPPORTS VARIOUS PROGRAMMING FORMATS AND VOLTAGES

• SPLIT OR COMBINE CONTENTS OF SEVERAL EPROMS OF DIFFERENT SIZES
• READ, WRITE, COPY, ERASE CHECK AND VERIFY
• SOFTWARE FOR HEX AND INTEL HEX FORMATS

MCT-EPROM-4 4 GANG PROGRAMMER \$18995

MCT-EPROM-10 10 GANG PROGRAMMER \$29995

MCT-PAL PAL PROGRAMMER \$26995

MCT-MP PROCESSOR PROG. \$19995



CALL FOR VOLUME QUOTES COPYRIGHT 1987 JDR MICRODEVICES

CIRCLE 184 ON FREE INFORMATION CARD

www.americanradiohistory.com

NEC V20 & V30 CHIPS

Replace the 8086 or 8088 in Your IBM-PC and Increase Its Speed by up to 40%!

Part No.	Price
UPD70108-5 (5MHz) V20 Chip....	\$ 8.75
UPD70108-8 (8MHz) V20 Chip....	\$10.75
UPD70108-10 (10MHz) V20 Chip....	\$29.95
UPD70116-8 (8MHz) V30 Chip....	\$13.75
UPD70116-10 (10MHz) V30 Chip....	\$29.95

7400

Part No.	1-9	10+	Part No.	1-9	10+
7400	29	19	7485	65	55
7402	29	19	7486	45	35
7404	29	19	7489	2.05	1.95
7405	35	25	7490	49	39
7406	39	29	7493	45	35
7407	39	29	74121	45	35
7408	35	25	74123	55	45
7410	29	19	74125	55	45
7414	49	39	74126	69	59
7416	39	29	74143	3.95	3.85
7417	29	19	74150	1.95	1.25
7420	35	25	74154	1.35	1.25
7430	35	25	74158	1.59	1.49
7432	39	29	74173	85	75
7438	39	29	74174	59	49
7442	55	45	74175	59	49
7445	69	59	74176	49	39
7446	89	79	74181	1.95	1.85
7447	89	79	74189	1.95	1.85
7448	2.05	1.95	74193	79	69
7472	89	79	74198	1.85	1.75
7473	39	29	74221	99	89
7474	29	19	74273	1.95	1.85
7475	49	39	74365	65	55
7476	45	35	74367	65	55

74LS

74LS00	29	19	74LS165	75	65
74LS02	29	19	74LS166	99	89
74LS04	35	25	74LS173	59	49
74LS05	35	25	74LS174	49	39
74LS06	1.09	99	74LS175	49	39
74LS07	1.09	99	74LS189	4.59	4.49
74LS08	29	19	74LS191	59	49
74LS10	29	19	74LS193	79	69
74LS14	49	39	74LS221	69	59
74LS27	35	25	74LS240	69	59
74LS30	29	19	74LS243	69	59
74LS32	35	25	74LS244	69	59
74LS42	49	39	74LS245	89	79
74LS47	99	89	74LS259	99	89
74LS73	39	29	74LS273	89	79
74LS74	35	25	74LS279	49	39
74LS75	39	29	74LS322	4.05	3.95
74LS76	55	45	74LS365	49	39
74LS85	59	49	74LS366	49	39
74LS86	35	25	74LS367	49	39
74LS90	49	39	74LS368	49	39
74LS93	49	39	74LS373	79	69
74LS123	59	49	74LS374	79	69
74LS125	49	39	74LS393	89	79
74LS138	49	39	74LS590	6.05	5.95
74LS139	49	39	74LS624	2.05	1.95
74LS154	1.09	99	74LS629	2.95	2.85
74LS157	45	35	74LS640	1.09	99
74LS158	45	35	74LS645	1.09	99
74LS163	59	49	74LS670	1.09	99
74LS164	59	49	74LS688	2.39	2.29

74S/PROMS

74S00	29	74S188*	1.49
74S04	29	74S189	1.69
74S10	35	74S196	2.49
74S18	29	74S240	1.49
74S32	35	74S244	1.49
74S74	45	74S253	79
74S85	1.79	74S287*	1.49
74S86	49	74S288*	1.49
74S124	2.75	74S373	1.49
74S174	79	74S374	1.49
74S175	79	74S472*	2.95

74F

74F00	29	74F139	69
74F04	29	74F157	69
74F08	29	74F193	2.95
74F10	29	74F240	99
74F32	39	74F244	99
74F74	39	74F253	99
74F86	39	74F373	99
74F138	59	74F374	99

CD - CMOS

CD4001	19	CD4076	59
CD4008	69	CD4081	25
CD4011	19	CD4082	25
CD4013	19	CD4093	35
CD4016	29	CD4094	89
CD4017	49	CD40103	2.49
CD4018	59	CD40107	79
CD4020	59	CD40109	49
CD4024	49	CD4510	69
CD4027	39	CD4511	69
CD4030	29	CD4520	79
CD4040	65	CD4522	79
CD4049	29	CD4528	79
CD4050	29	CD4541	79
CD4051	59	CD4543	89
CD4052	59	CD4553	4.95
CD4053	59	CD4556	7.99
CD4063	1.49	CD4559	9.95
CD4066	29	CD4566	2.49
CD4067	1.29	CD4583	89
CD4069	25	CD4584	89
CD4070	25	CD4585	89
CD4071	25	MC14411P	8.95
CD4072	25	MC14490P	4.49

MICROPROCESSOR COMPONENTS

MISCELLANEOUS CHIPS		6500/6800/68000 Cont.		8080 SERIES Cont.	
Part No.	Price	Part No.	Price	Part No.	Price
D765AC	4.95	6845	3.95	8228	2.95
VD9216	6.95	6850	1.95	8237-5	4.95
95H90	9.95	6852	1.95	8243	2.25
Z80, Z80A, Z80B SERIES		MC68000.8	11.95	8250A	6.49
Z80-CTC	1.25	MC68000.10	13.95	8250B (For IBM)	6.95
Z80-DART	4.95	MC8010L.10	49.95	8251A	1.89
Z80-PIO	1.79	MC68020RC12B	169.95	8253-5	1.95
Z80A	1.69	MC68881RC12A	149.95	8254	4.95
Z80A-CTC	1.79	8031	3.95	8255A.5	1.89
Z80A-DART	4.95	8031.1	3.95	8257-5	1.95
Z80A-PIO	1.69	8035	1.95	8259-5	2.25
Z80A-SIO	5.75	8073	9.95	8272	4.95
Z80B	3.49	8080A	2.95	8279-5	2.95
Z80B-CTC	3.95	8085A	2.49	8741	9.95
Z80B-PIO	4.29	8086	5.95	8742	29.95
		8086-2	6.95	8748 (25V)	7.95
		8087 (5MHz)	129.95	8748H (HMOS) (21V)	9.95
		8087-1 (10MHz)	229.95	8749	9.95
		8087-2 (8MHz)	169.95	8751	39.95
		8088	6.49	8755	14.95
		8088-2	8.95		
		8116	4.95		
		8155	2.49		
		8155-2	3.49		
		8156	3.95		
		8202	5.95		
		8203	9.95		
		8212	1.49		
		8224	2.25		

MICROPROCESSOR SALE!

Part No.	Price
8052AHBASIC CPU w/BASIC Interpreter.....	\$ 29.95
MC68000L8 32-Bit MPU (8-Bit Data Bus)....	\$ 19.95
MC68701 8-Bit EPROM Microcomputer....	\$ 14.95
MC68705P3S 8-Bit EPROM Microcomputer....	\$ 14.95
MC68705U3L 8-Bit EPROM Microcomputer....	\$ 10.95
80286-10 16-Bit Hi Performance MPU.....	\$ 99.95
80287-8 Math Co-processor (8MHz).....	\$299.95
80287-10 Math Co-processor (10MHz).....	\$329.95
80387-16 Math Co-processor (16MHz) ^{GRID ARRAY}	\$494.95

DYNAMIC RAMS

Part No.	Price
4116-15	16,384 x 1 (150ns)..... 89
4128-20	131,072 x 1 (200ns) (Piggyback)..... 3.25
4164-120	65,536 x 1 (120ns)..... 1.75
4164-150	65,536 x 1 (150ns)..... 1.25
4164-200	65,536 x 1 (200ns)..... 0.95
TMS4416-12	16,384 x 4 (120ns)..... 3.49
8118	16,384 x 1 (120ns)..... 4.49
41256-100	262,144 x 1 (100ns)..... 4.95
41256-120	262,144 x 1 (120ns)..... 3.95
41256-150	262,144 x 1 (150ns)..... 3.25
50484-15	65,536 x 4 (150ns) (4464)..... 6.49
511000P-10	1,048,576 x 1 (100ns) 1 Meg..... 34.95
514256P-10	262,144 x 4 (100ns) 1 Meg..... 29.95

STATIC RAMS

2016-12	2048 x 8 (120ns)..... 1.69
2018-45	2048 x 8 (45ns)..... 6.95
2102-2L	1024 x 1 (250ns) Low Power..... 1.95
2114N	1024 x 4 (450ns)..... 99
2114N-2L	1024 x 4 (200ns) Low Pwr..... 1.49
21C14	1024 x 4 (200ns) (CMOS)..... 2.49
2149	1024 x 4 (45ns)..... 2.49
5101	256 x 4 (450ns) CMOS..... 1.95
6116P-3	2048 x 8 (150ns) CMOS..... 1.89
6116LP-3	2048 x 8 (150ns) LP CMOS..... 1.95
6264LP-12	8192 x 8 (120ns) LP CMOS..... 4.25
6264P-15	8192 x 8 (150ns) CMOS..... 3.49
6264LP-15	8192 x 8 (150ns) LP CMOS..... 3.75
6514	1024 x 4 (350ns) CMOS..... 3.49
43256-15L	32,768 x 8 (150ns) Low Power..... 11.95

EPROMS

TMS2516	2048 x 8 (450ns) 25V..... 6.95
TMS2532	4096 x 8 (450ns) 25V..... 6.95
TMS2532A	4096 x 8 (450ns) 21V..... 9.95
TMS2564	8192 x 8 (450ns) 25V..... 5.95
TMS2716	2048 x 8 (450ns) 3 Voltage..... 6.95
2708	1024 x 8 (450ns)..... 6.95
2716	2048 x 8 (450ns) 25V..... 3.75
2716-1	2048 x 8 (350ns) 25V..... 4.25
27C16	2048 x 8 (450ns) 25V (CMOS)..... 5.49
2732	4096 x 8 (450ns) 25V..... 3.95
2732A-20	4096 x 8 (200ns) 21V..... 4.25
2732A-25	4096 x 8 (250ns) 21V..... 3.95
27C32	4096 x 8 (450ns) 25V (CMOS)..... 5.95
2764-20	8192 x 8 (200ns) 21V..... 4.25
2764-25	8192 x 8 (250ns) 21V..... 3.75
2764A-25	8192 x 8 (250ns) 12.5V..... 3.95
2764-45	8192 x 8 (450ns) 21V..... 4.95
27C64-15	8192 x 8 (150ns) 21V (CMOS)..... 6.49
27128-20	16,384 x 8 (200ns) 21V..... 6.95
27128-25	16,384 x 8 (250ns) 21V..... 5.95
27128A-25	16,384 x 8 (250ns) 12.5V..... 5.25
27C128-25	16,384 x 8 (250ns) 21V (CMOS)..... 6.95
27256-20	32,768 x 8 (200ns) 12.5V..... 6.95
27256-25	32,768 x 8 (250ns) 12.5V..... 5.95
27C256-25	32,768 x 8 (250ns) 12.5V (CMOS)..... 7.95
27512-20	65,536 x 8 (200ns) 12.5V..... 13.49
27512-25	65,536 x 8 (250ns) 12.5V..... 11.95
68764	8192 x 8 (450ns) 25V..... 13.95

EEPROMS

2816A	2048 x 8 (350ns) 5V Read/Write..... 5.95
2817A	2048 x 8 (350ns) 5V Read/Write..... 7.95
2865A	8192 x 8 (250ns) 5V Read/Write..... 9.95
52B13 (21V)	2048 x 8 (350ns) 5V Read/Write..... 1.49

*No specs. available
 **Note: 82S100PLA = U17 (C-64)

SATELLITE TV DESCRAMBLER CHIP

The MM5321 is a TV camera sync generator designed to supply the basic sync functions for either color or monochrome 525 line/60Hz interlaced and camera video recorder applications. COLOR BURST GATE & SYNC ALLOW STABLE COLOR OPERATION

MM5321N..... \$11.95

74HC HI-SPEED CMOS

Part No.	Price	Part No.	Price
74HC00	25	74HC175	69
74HC02	25	74HC221	1.19
74HC04	29	74HC240	99
74HC08	29	74HC244	99
74HC10	29	74HC245	99
74HC14	49	74HC253	5.95
74HC30	29	74HC259	99
74HC32	29	74HC273	99
74HC74	39	74HC373	99
74HC75	39	74HC374	99
74HC76	45	74HC595	1.29
74HC85	79	74HC688	5.95
74HC86	39	74HC683	8.95
74HC123	89	74HC4040	59
74HC125	49	74HC4049	59
74HC132	69	74HC4050	59
74HC138	49	74HC4060	59
74HC139	49	74HC4511	1.29
74HC184			

Worldwide • Since 1974

• QUALITY COMPONENTS • COMPETITIVE PRICING
• PROMPT DELIVERY

Mail Order Electronics - Worldwide
Jameco
ELECTRONICS

Jameco
ELECTRONICS

General Purpose NEW! Prototype PC Boards

- Wire Wrap
- Component Testing
- Point-to-Point Wiring
- 31/62 Connection



JE417 (Pictured)

- JE411 (6 1/2", No Pads, Gen. Purp.) \$12.95
- JE415 (6 1/2", No Pads, PC/XT) \$14.95
- JE417 (6 1/2", Plated w/Pads, PC/XT) \$19.95

Extender Boards Designed for Troubleshooting and Testing

JE419 (Pictured)

- JE419 (5 1/4" Extender, 22/44 Connector) . . . \$19.95
- JE421 (4 3/4" Extender, 31/62 Connector) . . . \$19.95

Accessories for Commodore VIC-20, C-64 & C-128

JE232CM (Pictured)

- *CM1 (300B Modem VIC-20, C-64) . . . \$19.95
- *JE232CM (RS232 Inter. VIC-20, C-64) . . \$39.95
- CPS10 (C-64 Power Supply) \$39.95
- CPS128 (C-128 Power Supply) \$59.95

ZUCKERBERG

TANDY 1000 Expansion Memory Half Card


Expand the memory of your Tandy 1000 (128K Version) to as much as 640K! Also includes DMA controller chip

- TE512 Includes 512K RAM \$119.95
- TANC Plug-in Clock option chip (only) . . . \$39.95

20Meg Hard Disk

- T20MB 20MB Hard Disk Drive Board for Tandy 1000 \$494.95
- SX20MB 20MB Hard Disk Drive Board for Tandy 1000SX \$499.95

DATA TRONICS 2400/1200/300 Modems

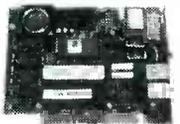

• Hayes command compatible • Bell 103/12A compatible • Auto-dial/auto-answer • FCC approved • 1-year warranty • The 1200H & 2400S include MaxiMile Communication Software • The 1200C & 2400E do not include software

- 1200H 1200/300 Baud Internal Modem . . . \$ 79.95
- 2400S 2400/1200/300 Internal Modem . . . \$174.95
- 1200C 1200/300 Baud External Modem . . . \$119.95
- 2400E 2400/1200/300 External Modem . . . \$219.95

NEW! Switching Power Supply

- +5V @ 5A, +12V @ 1A x 2
- Regulated, 110VAC/220VAC
- Switchable • 40 watt • Size: 8 1/2" L x 3" W x 2 3/4" H • Weight: 1.1 lbs. • Data included
- PSC07 \$14.95

INTRODUCING JAMECO'S NEW COMPUTER KITS!!

Jameco's IBM™ AT Compatible Kit! Mini-286 6/8/10/12 MHz Kit!

EGA Monitor
TE514 \$399.95
EGA Card
JE1055 \$149.95
(not included)



Part No.	Description	Price
JE1043	1.2M/360K Floppy Control	\$ 49.95
JE1015	XT/AT Style Keyboard	\$ 59.95
41256-120	512K RAM (18 Chips)	\$ 71.10
JE1012	Baby AT Flip-Top Case	\$ 69.95
JE1032	200W Power Supply	\$ 89.95
JE1022	5 1/4" High Density Disk Drive	\$109.95
JE1003	Baby AT Motherboard (Zero-K RAM-incl. Award BIOS ROM)	\$399.95



Regular List \$850.80
SAVE \$50.85!

JE1008 IBM™ AT Compatible Kit. \$799.95

Jameco's IBM PC/XT Compatible Kit

SAVE \$77.15

4164-150	128K RAM (18 Chips)	\$22.50
JE1040	Floppy Controller Card	\$29.95
JE1010	Flip-Top Case	\$34.95
JE1015	XT/AT Style Keyboard	\$59.95
JE1030	150 Watt Power Supply	\$69.95
JE1050	Mono/Graph. Crd. w/P/Port	\$59.95
JE1020	5 1/4" DSDD Disk Drive	\$89.95
GREEN	12" Mono. Green Monitor	\$99.95
JE1000	XT Motherboard (Zero-K RAM-incl. Award BIOS ROM)	\$89.95

**FREE! QUICKSOFT PC
WRITE WORD PROCESSING
SOFTWARE INCLUDED!**

Regular List \$557.10

JE1004 (IBM™ PC/XT Compatible Kit) \$479.95

Jameco's 4.77/8MHz Turbo IBM Compatible Kit

Same as JE1004 except comes with 640K RAM, JE1001 (Turbo) 4.77/8MHz motherboard, JE1071 multi I/O with controller and graphics, and AMBER monitor.

SAVE \$70.70 Regular List \$670.65

JE1005 (IBM™ PC/XT Turbo Compatible Kit) . . . \$599.95

IBM Compatible Motherboards

- 4.77/8MHz operation (Turbo only)
- 8087 Math Co-processor capability
- BIOS ROM included

JE1001 4.77/8MHz . . . \$129.95 \$104.95
JE1000 4.77MHz . . . \$109.95 \$ 89.95

Additional Add-Ons Available!

Color Graphics Card for PC/XT/AT



• Text: 40 or 80 x 25 • Graphics: 320 or 640 x 200 • Parallel Printer Port • Manual included
JE1052 \$49.95

EGA Card for PC/XT/AT



• Graphics: 720 x 348 • 16 out of 64 colors • Manual included
JE1055 \$149.95

I/O Cards for PC/XT/AT



• Printer Port
• RS232 Port
• Game Port
• Manual included
JE1060 (Pictured)

JE1060 I/O for XT . . . \$59.95
JE1065 I/O for AT . . . \$59.95

Multi I/O w/Controller & Graphics for PC/XT




• Printer port • RS232 port • Floppy controller • Graphics • Manual included

JE1071 \$119.95

Jameco
ELECTRONICS

Solderless Breadboard Sockets

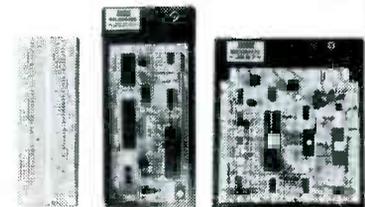

Part No.	Dim. L" x W"	Contact Points	Binding Posts	Price
JE20	6 1/2" x 3/4"	200	0	\$ 2.29
JE21	3 1/4" x 2 1/8"	400	0	\$ 4.49
JE22	6 1/2" x 1 3/8"	630	0	\$ 5.95
JE23	6 1/2" x 2 1/8"	830	0	\$ 7.49
JE24	6 1/2" x 3 1/8"	1,360	2	\$14.95
JE25	6 1/2" x 4 1/4"	1,660	3	\$22.95
JE26	6 7/8" x 5 3/4"	2,390	4	\$27.95
JE27	7 1/4" x 7 1/2"	3,220	4	\$37.95

Jameco
ELECTRONICS

Extended 80-Column Card for Apple IIe



• 80 Col./64K RAM • Doubles amount of data your Apple IIe can display as well as its memory capacity • Ideal for word processing • Complete with instructions

JE864 \$49.95

ADD12 (Disk Drive II, II+, IIe) \$99.95

Additional Apple Compatible Products Available

NEW!



**Seagate 20,
30 & 40MB
Half Height
Hard Disk
Drives**

ST225K (Pictured)

ST225	20 MB Drive only (PC/XT/AT)	\$269.95
ST225K	20 MB w/Controller (PC/XT)	\$319.95
ST238	30 MB Drive only (PC/XT/AT)	\$299.95
ST238K	30 MB w/Cont. (PC/XT/AT)	\$339.95
ST251	40 MB Drive only (PC/XT/AT)	\$469.95
ST251XT	40 MB w/Cont. Card (PC/XT)	\$549.95
ST251AT	40 MB w/Cont. Card (AT)	\$589.95



**Jameco PC/XT
& AT Compatible
Disk Drives**

JE1020 (360K Drive, PC/XT/AT) . . . \$ 89.95
JE1022 (1.2MB, AT Compatible) . . . \$109.95

DATA BOOKS

30003	National Linear Data Book (82)	\$19.95
30005	Logic Data Book - Vol. II (84)	\$19.95
30009	Intersil Data Book (87)	\$14.95
21398	CMOS Cookbook (86)	\$14.95
210830	Intel Memory Handbook (87)	\$17.95
230843	Intel Microsystem Hndbk. Set (87)	\$24.95

MUFFIN/SPRITE-STYLE FANS



TA450S \$11.95
Torin Industries (4.68" sq., 50 cfm)
SU2A1 \$11.95
EG&G Rotron (3.125" square, 34 cfm)

U.S. Funds Only
Shipping: Add 5% plus \$1.50 Insurance

\$20 Minimum Order

IBM is a registered trademark of International Business Machines

California Residents:
Add 6%, 6 1/2% or 7%
Sales Tax

FAX 415-592-2503

1/88



Mail Order Electronics - Worldwide
Jameco
ELECTRONICS



Data Sheets - 50¢ each
Prices Subject to Change

Send \$1.00 Postage for a
FREE 1988 CATALOG

Telex: 176043

©1987 Jameco Electronics

1355 SHOREWAY RD., BELMONT, CA 94002 • FOR ORDERS ONLY 415-592-8097 • ALL OTHER INQUIRIES 415-592-8121

CIRCLE 114 ON FREE INFORMATION CARD

www.americanradiohistory.com

CORPORATION

80-344-43

AK, Puerto Rico • 218-881-6674 Telex - 6287914 FAX - 218-881-3380 TWX - 910350882 DIGI KEY CORP

NATIONAL SEMICONDUCTOR • PANASONIC MACHINE • EWC, INC. • INTERSIL • AD EAC, INC. • J. W. MILLER • AAVDI ENGINEER • E. F. JOHNSON • ATLANTIC SEMICONDUCTOR

256K (262,144 x 1) DRAM 150NS \$5.70/1; \$39.95/9 Factory Firsts

DIODES • DIAMOND TOOL • UNGAR • ES • CW INDUSTRIES • AMDEK • G.E. UGAR • YAGEO • J. W. MILLER • LUXO • CHEMICALS • ARIES • PLESSEY

INTEGRATED CIRCUITS

Part No.	Description	Price
7400 TTL	74LS00	1.00
7401	74LS01	1.00
7402	74LS02	1.00
7403	74LS03	1.00
7404	74LS04	1.00
7405	74LS05	1.00
7406	74LS06	1.00
7407	74LS07	1.00
7408	74LS08	1.00
7409	74LS09	1.00
7410	74LS10	1.00
7411	74LS11	1.00
7412	74LS12	1.00
7500	74LS100	1.00

TT C. SOCKETS

Part No.	Description	Price
118	118	1.00
119	119	1.00
120	120	1.00
121	121	1.00
122	122	1.00
123	123	1.00
124	124	1.00
125	125	1.00
126	126	1.00
127	127	1.00
128	128	1.00
129	129	1.00
130	130	1.00
131	131	1.00
132	132	1.00
133	133	1.00
134	134	1.00
135	135	1.00
136	136	1.00
137	137	1.00
138	138	1.00
139	139	1.00
140	140	1.00
141	141	1.00
142	142	1.00
143	143	1.00
144	144	1.00
145	145	1.00
146	146	1.00
147	147	1.00
148	148	1.00
149	149	1.00
150	150	1.00

5% Carbon Film Resistors

Part No.	Description	Price
100	100	1.00
101	101	1.00
102	102	1.00
103	103	1.00
104	104	1.00
105	105	1.00
106	106	1.00
107	107	1.00
108	108	1.00
109	109	1.00
110	110	1.00
111	111	1.00
112	112	1.00
113	113	1.00
114	114	1.00
115	115	1.00
116	116	1.00
117	117	1.00
118	118	1.00
119	119	1.00
120	120	1.00

DISC CAPACITORS

Part No.	Description	Price
100	100	1.00
101	101	1.00
102	102	1.00
103	103	1.00
104	104	1.00
105	105	1.00
106	106	1.00
107	107	1.00
108	108	1.00
109	109	1.00
110	110	1.00
111	111	1.00
112	112	1.00
113	113	1.00
114	114	1.00
115	115	1.00
116	116	1.00
117	117	1.00
118	118	1.00
119	119	1.00
120	120	1.00

TANTALUM CAPACITORS

Part No.	Description	Price
100	100	1.00
101	101	1.00
102	102	1.00
103	103	1.00
104	104	1.00
105	105	1.00
106	106	1.00
107	107	1.00
108	108	1.00
109	109	1.00
110	110	1.00
111	111	1.00
112	112	1.00
113	113	1.00
114	114	1.00
115	115	1.00
116	116	1.00
117	117	1.00
118	118	1.00
119	119	1.00
120	120	1.00

7400 TTL

Part No.	Description	Price
7400	7400	1.00
7401	7401	1.00
7402	7402	1.00
7403	7403	1.00
7404	7404	1.00
7405	7405	1.00
7406	7406	1.00
7407	7407	1.00
7408	7408	1.00
7409	7409	1.00
7410	7410	1.00
7411	7411	1.00
7412	7412	1.00
7413	7413	1.00
7414	7414	1.00
7415	7415	1.00
7416	7416	1.00
7417	7417	1.00
7418	7418	1.00
7419	7419	1.00
7420	7420	1.00
7421	7421	1.00
7422	7422	1.00
7423	7423	1.00
7424	7424	1.00
7425	7425	1.00
7426	7426	1.00
7427	7427	1.00
7428	7428	1.00
7429	7429	1.00
7430	7430	1.00
7431	7431	1.00
7432	7432	1.00
7433	7433	1.00
7434	7434	1.00
7435	7435	1.00
7436	7436	1.00
7437	7437	1.00
7438	7438	1.00
7439	7439	1.00
7440	7440	1.00
7441	7441	1.00
7442	7442	1.00
7443	7443	1.00
7444	7444	1.00
7445	7445	1.00
7446	7446	1.00
7447	7447	1.00
7448	7448	1.00
7449	7449	1.00
7450	7450	1.00

WIRE WRAP DIP SOCKETS

Part No.	Description	Price
100	100	1.00
101	101	1.00
102	102	1.00
103	103	1.00
104	104	1.00
105	105	1.00
106	106	1.00
107	107	1.00
108	108	1.00
109	109	1.00
110	110	1.00
111	111	1.00
112	112	1.00
113	113	1.00
114	114	1.00
115	115	1.00
116	116	1.00
117	117	1.00
118	118	1.00
119	119	1.00
120	120	1.00

1% Metal Film Resistors

Part No.	Description	Price
100	100	1.00
101	101	1.00
102	102	1.00
103	103	1.00
104	104	1.00
105	105	1.00
106	106	1.00
107	107	1.00
108	108	1.00
109	109	1.00
110	110	1.00
111	111	1.00
112	112	1.00
113	113	1.00
114	114	1.00
115	115	1.00
116	116	1.00
117	117	1.00
118	118	1.00
119	119	1.00
120	120	1.00

PANASONIC LS SERIES

Part No.	Description	Price
100	100	1.00
101	101	1.00
102	102	1.00
103	103	1.00
104	104	1.00
105	105	1.00
106	106	1.00

Radio Shack Parts Place™

Start Your New Year Right—at Radio Shack

Rare Special-Purchase LEDs

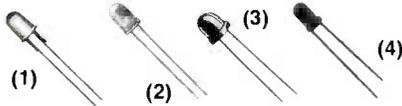


Fig.	Type	Cat. No.	Price
1	T-1 Super Bright Yellow	276-054	Pkg. 2/69
2	Micro-Size Yellow	276-055	Pkg. 2/59
3	T-1 Super Bright Green	276-056	Pkg. 4/89
4	Micro-Size Red	276-057	Pkg. 3/69

Color-Coded Test Cables



Insulated Clips at Both Ends

Set Of	Length	Clips	Cat. No.	Only
10	14"	Mini 'Gator	278-1156	3.99
4	30"	'Gator	278-001	3.49
6	40", Heavy Duty	Claw-Type	278-002	3.99
8	24", 4 Colors	Mini 'Gator	278-1157	3.99


Popular Transformers



Primarys 120 VAC, 60 Hz. CT = Center Tap. Transformers are UL listed AC.

Type	Volts	Current	Cat. No.	Each
Miniature	12.6	300 mA	273-1385	3.29
Miniature	12.6 CT	450 mA	273-1365	3.99
Miniature	25.2 CT	450 mA	273-1366	4.59
Standard	12.6 CT	1.2 A	273-1352	5.79

Special-Order Hotline

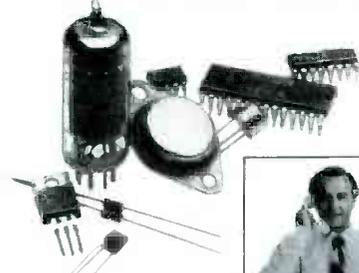

Over 200,000 Substitutions Available

Your Radio Shack store manager can phone in a special order for a wide variety of parts and accessories not in our regular catalog. These items include microprocessors and support chips, tubes, linear and digital ICs, diodes, transistors, phono cartridges and styli, popular TV modules, crystals and much more. No postage or handling charges, no minimum order! So, order today and we'll call you when your order arrives, in about a week.

Precision DC Voltmeter



- Measures 0 to 15 VDC
- Zero Adjust

Panel meter for monitoring the voltage of a car's electrical system or a custom-built power supply. Jeweled movement for accuracy to ± 5% of full scale. 2 3/4 x 2 1/4 x 1 1/4". Requires 1 7/8" round mounting hole. #270-1754 7.95

Predrilled PC Boards

Accept DIP ICs, Sockets, Headers

Grid Boards. Columns and rows are indexed to identify pin-outs. Solder-ringed holes.

Size	Cat. No.	Ea.
4 1/2 x 6 5/8"	276-147	3.49
2 3/4 x 3 3/4"	276-158	2.29
1 27/32 x 2 27/32"	276-149	.99



Computer Connections

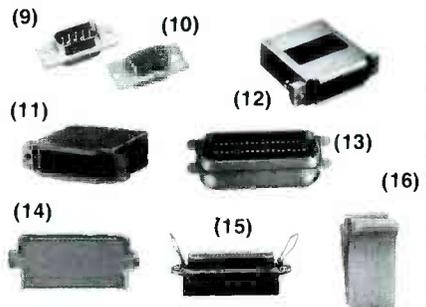


Fig.	Description	Position	Cat. No.	Each
(9)	Solder-Type "D" Submini, Male	9	276-1537	1.49
(10)	Solder-Type "D" Submini, Female	9	276-1538	2.49
(11)	Hood for 9-Position Connectors	—	276-1539	1.99
—	Solder-Type "D" Submini, Male	25	276-1547	1.99
—	Solder-Type "D" Submini, Female	25	276-1548	2.99
—	Hood for 25-Position Connectors	25	276-1549	1.99
(12)	Multipurpose Hood—25 Position	—	276-1520	1.79
(13)	Solder-Type Printer Connector, Male	36	276-1534	4.99
(14)	IDC Printer Connector, Male	36	276-1533	4.99
(15)	IDC Printer Connector, Female	36	276-1523	4.99
(16)	Printer Cable—Color Coded, 6 feet	36	278-774	4.69

Enclosure / PC-Board



- (5) Black Plastic With 2 x 3 1/8" Board. Accepts DIP ICs. With labels, feet, hardware. 3 7/16 x 2 5/16 x 1 3/16". #270-291 3.99
- (6) Gray Plastic With Predrilled PC Boards. Boards are IC-spaced (0.1" pitch) and etched. 2 1/8 x 3 5/16 x 1 3/8". #270-283 3.69
- 2 3/4 x 4 3/16 x 1 1/4". #270-284 4.69


Relays & Lighted Switch



- (7) SPDT 5 VDC, 90 mA, 55-Ohm Coil. Contacts: 1 amp, 125 VAC. #275-240 1.89
- 12 VDC, 38 mA, 320-Ohm Coil. #275-241 1.89
- (8) 120 VAC SPST Push On/Off Lighted Switch. 10 amps. Mounts in 7/16" hole. #275-671 3.49

Clamp-On Ammeter And AC Voltmeter


Includes Inductive Pickup/Multiplier

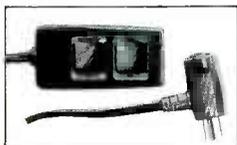

Measures up to 300 amperes AC without direct connection to circuit, and measures up to 600 volts AC with included test leads. Clamp jaws reach into tight places. Lock-switch freezes pointer for easy meter reading. #22-161 49.95




Special-Purchase Hot Values

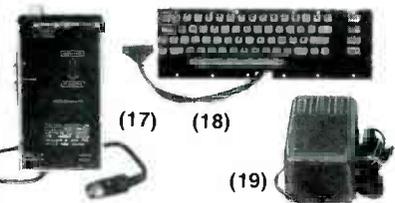

- (17) Sound/Color-Video TV RF Modulator. Prewired module with antenna/modulator switch. For 12 VDC. With data. #277-1015 4.95
- (18) Keyboard. Upgrade your membrane-type keyboard! Sixty three full-stroke keys, three function keys, 18-position connector. #277-1027 4.95
- (19) Plug-In 9 VDC Adapter. Provides 9 VDC at one amp, up to 13 VDC with a light load. UL listed AC. #277-1026 4.95

Dual-Tracking DC Supply

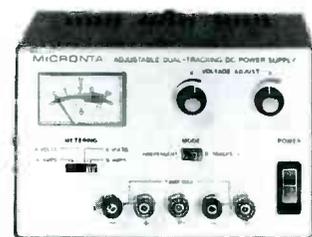

Delivers rock-steady DC that's easy to adjust to the exact voltages you need. Variable split 0-15 VDC or series up to 30 VDC. Offers choice of independent or slave operation; a single knob lets you adjust both voltages simultaneously, or use independent mode to adjust voltages separately. Switchable volt/amp meter for monitoring the voltage or current of either output. Fuse protected. UL listed AC. #22-121 69.95

Over 1000 items in stock: Binding Posts, Books, Breadboards, Buzzers, Capacitors, Chokes, Clips, Coax, Connectors, Fuses, Hardware, ICs, Jacks, Knobs, Lamps, Multimeters, PC Boards, Plugs, Rectifiers, Resistors, Switches, Tools, Transformers, Wire, Zeners, More!

Prices apply at participating Radio Shack stores and dealers

Radio Shack®
A DIVISION OF TANDY CORPORATION

AMAZING SCIENTIFIC & ELECTRONIC PRODUCTS

PLANS—Build Yourself—All Parts Available In Stock

- LC7—BURNING CUTTING CO₂ LASER \$ 20.00
- RUB4—PORTABLE LASER RAY PISTOL 20.00
- TCCT1—3 SEPARATE TESLA COIL
PLANS TO 1.5 MEV 20.00
- IOG1—ION RAY GUN 10.00
- GRA1—GRAVITY GENERATOR 10.00
- EML1—ELECTRO MAGNET COIL GUN/LAUNCHER 6.00

KITS

- MFT1K—FM VOICE TRANSMITTER 3 MI RANGE 49.50
- VWPM5K—TELEPHONE TRANSMITTER 3 MI RANGE 39.50
- BTC2K—250.00 VOLT 10-14" SPARK TESLA COIL 199.50
- LHC2K—SIMULATED MULTICOLOR LASER 39.50
- BL51K—100,000 WATT BLASTER DEFENSE DEVICE 69.50
- TTM1K—100,000 VOLT 20" EFFECTIVE
RANGE INTIMIDATOR 69.50
- PSP4K—TIME VARIANT SHOCK WAVE PISTOL 59.50
- PTG1K—SPECTACULAR PLASMA
TORNADO GENERATOR 149.50
- MYP1K SEE IN DARK KIT 199.50

ASSEMBLED

- PG70H—MULTICOLORLED VARIABLE
MODE PLASMA GLOBE "7" 199.50
- BTC10—50,000 VOLT—WORLD'S SMALLEST
TESLA COIL 44.50
- LGU40—1MW HeNe VISIBLE RED LASER GUN 199.50
- TAT20 AUTO TELEPHONE RECORDING DEVICE 24.50
- GPV10—SEE IN TOTAL DARKNESS IR VIEWER 349.50
- LUST10—SNOOPER PHONE INFINITY TRANSMITTER 169.50
- IPG70—INVISIBLE PAIN FIELD GENERATOR—
MULTI MODE 74.50

* CATALOG CONTAINING DESCRIPTIONS OF ABOVE PLUS HUNDREDS MORE AVAILABLE FOR \$1.00 OR INCLUDED FREE WITH ALL ABOVE ORDERS.

PLEASE INCLUDE \$3.00 PH ON ALL KITS AND PRODUCTS PLANS ARE POSTAGE PAID. SEND CHECK, MO. VISA, MC IN US FUNDS.

INFORMATION UNLIMITED
P.O. BOX 716 DEPT. RE, AMHERST, NH 03031

ADVERTISING INDEX

RADIO-ELECTRONICS does not assume any responsibility for errors that may appear in the index below.

Free Information Number	Page		Page	
81	A.I.S. Satellite	36	110 Omnitron	81
108	AMC Sales	81	197 PC Plus	86
107	All Electronics	110	— Pacific Cable	105
103	Allen W.B.	38	56 Parts Express	104
—	Amazing Devices	120	69 RAM	86
106	American Design Components	111	78 Radio Shack	119
—	Amway	86	179 Regency	5
84	Appliance Service	36	176, 178 Sencore	33, 23
180	Banner Technical Books	83	51 Silicon Valley Surplus	120
85	Blue Star Industries	37	92, 186 Tektronix	CV2, 79
109	C & S Sales	25	192 U.S. Cable/Movie Time	76
60	CIE	18	181 United Electronic Supply	74
194	Cabletronics	37	53 United Imports	85
193	Chenesko Products	37	185 WPT Publications	17
52	Circuit Cellar	37	— Wolfer Productions	86
—	Command Productions	85		
196	Compstar	86		
198	Consumertronics	17		
58	Cook's Institute	83		
191	Crystek	75		
—	DAK Industries	14, 15		
190	Daetron	83		
127	Deco Industries	36, 37		
82	Digi-Key	118		
—	Digital Research Computers	104		
—	Elec. Industry Association	7		
—	Electronic Technology Today	CV3		
—	Electronics Book Club	39		
120, 187	Elephant Electronics	37, 36		
100	Firestik II	85		
121	Fluke Mfg.	73		
—	Fordham Radio	CV4		
189	GEI	108		
—	Grantham College of Engineering	13		
—	Halix Institute	38		
86	Heath	26, 27		
188	ICS Computer Training	81		
—	ISCET	76		
67	Intek	37		
59	JDR Instruments	3		
113, 182	JDR Microdevices	112, 113		
183, 184	JDR Microdevices	114, 115		
114	Jameco	117, 116		
115	Jensen Tools	37		
—	Joseph Electronics	35		
199	Kelvin	109		
195	Laser's Edge	86		
87	MCM Electronics	107		
93	Mark V. Electronics	106		
—	McGraw Hill Book Club	28		
61	Microprocessors Unltd.	86		
—	NRI	8		
72	NuScope Associates	86		
80	OCTE Electronics	37		

Gernsback Publications, Inc.
500-B Bi-County Blvd.
Farmingdale, NY 11735
(516) 293-3000
President: Larry Steckler
Vice President: Cathy Steckler

For Advertising ONLY
516-293-3000

Larry Steckler
publisher
Arline Fishman
advertising director
Shelli Weinman
advertising associate
Lisa Strassman
credit manager
Christina Estrada
advertising assistant


SALES OFFICES

EAST/SOUTHEAST
Stanley Levitan
Eastern Sales Manager
Radio-Electronics
259-23 57th Avenue
Little Neck, NY 11362
718-428-6037, 516-293-3000

**MIDWEST/Texas/Arkansas/
Okla.**
Ralph Bergen
Midwest Sales Manager
Radio-Electronics
540 Frontage Road—Suite 339
Northfield, IL 60093
312-446-1444

**PACIFIC COAST/ Mountain
States**
Marvin Green
Pacific Sales Manager
Radio-Electronics
5430 Van Nuys Blvd. Suite 316
Van Nuys, CA 91401
1-818-986-2001

MOTION CONTROL SYSTEM

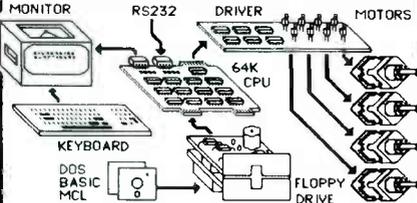

COMPUTER • MONITOR • KEYBOARD • FLOPPY
DISK DRIVE • MOTOR
CONTROLLER • FOUR
MOTORS • SOFTWARE
• A. C. POWER SUPPLY

\$199⁰⁰

■ GENERAL PURPOSE 64K SINGLE BOARD COMPUTER HAS 2 SERIAL PORTS & 1 CENTRONICS PORT ■ 800K OF DISK STORAGE—EXPANDABLE TO 3.2 MEG ■ AMBER MONITOR WITH 80 BY 24 LINES OF TEXT DISPLAY ■ HIGH-QUALITY KEYBOARD THAT HAS A SEPARATE NUMERICAL KEYPAD ■ LIGHTED CAPS LOCK AND ENTER KEYS ■ 10 FUNCTION KEYS ■ STEPPER MOTOR DRIVER KIT WITH 4 OF OUR "EASY STEPPER" MOTORS ■ CPM ■ DOS ■ MICROSOFT BASIC ■ PILOT LANGUAGE ■ MOTOR CONTROL PROGRAM WITH SOURCE LISTING ON DISK ■ ALL NECESSARY CABLES ■ JUST ABOUT EVERY THING YOUR ROBOT WILL NEED FOR "BUILT IN" SMARTS! ■ WE PROVIDE AN A. C. SUPPLY FOR BENCH TESTING. OUT PUT VOLTAGES ARE +12VDC @ 2.5 AMPS, -12VDC @ 5 AMPS, +5 VDC @ 5 AMPS, +24 VDC @ 1.5 AMPS ■ EXCEPT FOR THE STEPPER DRIVER KIT ALL BOARDS ARE ASSEMBLED AND TESTED JUST WIRE THEM TO THE POWER SUPPLY PLUG IN THE CABLES AND GO

HAVE A COMPUTER? THEN ORDER JUST THE MOTORS AND CONTROLLER
■ CENTRONICS INTERFACE ■ INCLUDES A.C. POWER SUPPLY AND SOFTWARE ■ SPECIFY MORROW = CPM/ENGINE = OR IBM BASIC

39⁰⁰


Call for a copy of 15 day trial agreement. Tax & freight extra. C.O.D. accepted just add \$1.90 Price may change Store Price may differ. While supplies last. No P.O.s, terms, or credit cards

Silicon Valley Surplus
415-261-4506
4401 OAKPORT OAKLAND CA. 94601
OPEN 10am-6pm
CLOSED SUN & MON
CALL OUR BBS 415-261-4513


CIRCLE 51 ON FREE INFORMATION CARD

Electronics Paperback Books

GREAT ELECTRONICS PAPERBACKS FROM ETT

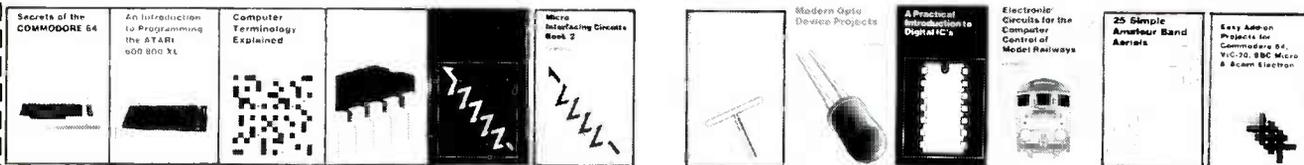

- BP125—25 SIMPLE AMATEUR BAND ANTENNAS.....\$5.00.** All are inexpensive to build, yet perform well. Diodes, beams, triangle and even a mini rhombic.
- BP128—20 PROGRAMS FOR THE ZX SPECTRUM AND 16K ZX82.....\$5.75.** Included with each program is a flow chart and a description of what happens. Notes for converting programs for use on other computers are also included.
- BP235—POWER SELECTOR GUIDE.....\$10.00.** Complete guide to semiconductor power devices. More than 1000 power handling devices are included. They are tabulated in alpha-numeric sequence, by technical specs. Includes power diodes, Thyristors, Triacs, Power Transistors and FETs.
- BP234—TRANSISTOR SELECTOR GUIDE.....\$10.00.** Companion volume to BP235. Book covers more than 1400 JEDEC, JIS, and brand-specific devices. Also contains listing by case type, and electronic parameters. Includes Darlington transistors, high-voltage devices, high-current devices, high power devices.
- BP99—MINI-MATRIX BOARD PROJECTS.....\$5.00.** Here are 20 useful circuits that can be built on a mini-matrix board that is just 24 holes by ten copper-foil strips.
- BP157—HOW TO WRITE ZX SPECTRUM AND SPECTRUM GAMES PROGRAMS.....\$5.95.** A crystal-clear step-by-step guide to writing your own graphics games programs.
- BP117—PRACTICAL ELECTRONIC BUILDING BLOCKS—Book 1.....\$5.75.** Oscillators, Timers, Noise Generators, Rectifiers, Comparators, Triggers and more.
- BP184—INTRO TO 68000 ASSEMBLY LANGUAGE.....\$6.50.** The 68000 is a great new breed of microprocessor. Programming in assembly language increases the running speed of your programs. Here's what you need to know.
- BP179—ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF ROBOTS \$5.00.** Data and circuits for interfacing the computer to the robot's motors and sensors.
- BP126—BASIC & PASCAL IN PARALLEL.....\$4.95.** Takes these two programming languages and develops programs in both languages simultaneously.
- 224—50 CMOS IC PROJECTS.....\$5.25.** Includes sections on multivibrators, amplifiers and oscillators, trigger devices, and special devices.
- 225—A PRACTICAL INTRODUCTION TO DIGITAL IC'S.....\$4.95.** Mainly concerned with TTL devices. Includes several simple projects plus a logic circuit test set and a digital counter timer.
- BP170—INTRODUCTION TO COMPUTER PERIPHERALS.....\$5.95.** Shows how to use a variety of co computer add-ons in as non-technical a way as possible.
- 227—BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS.....\$5.00.** How to tackle the practical side of electronics so you can successfully build electronic projects.
- BP169—HOW TO GET YOUR COMPUTER PROGRAMS RUNNING.....\$5.95.** Shows how to identify error in program and what to do about them.
- BP194—MODERN OPTO DEVICE PROJECTS.....\$6.25.** Crammed with great projects for the experimenter. Includes sections on Fiber optics, passive Infra-Red detectors, plus an assortment of miscellaneous projects.
- BP180—ELECTRONIC CIRCUITS FOR THE COMPUTER CONTROL OF MODEL RAILROADS.....\$6.25.** It's easy to interface home computers to model railroad control. The main problem is in interfacing the computer to the system.
- BP110—HOW TO GET YOUR ELECTRONIC PROJECTS WORKING.....\$5.00.** How to find and solve the common problems that can occur when building projects.
- BP33—ELECTRONIC CALCULATOR USERS HANDBOOK.....\$5.75.** Invaluable book for all calculator owners. Tells how to get the most out of your calculator.
- BP36—50 CIRCUITS USING GERMANIUM, SILICON & ZENER DIODES.....\$5.00.** A collection of useful circuits you'll want in your library.
- BP37—50 PROJECTS USING RELAYS, SCR'S & TRIACS.....\$5.00.** Build priority indicators, light modulators, warning devices, light dimmers and more.
- BP39—50 FET TRANSISTOR PROJECTS.....\$5.50.** RF amplifiers, test equipment, tuners, receivers, tone controls, etc.
- BP42—SIMPLE LED CIRCUITS.....\$5.00.** A large selection of simple applications for this simple electronic component.
- BP127—HOW TO DESIGN ELECTRONIC PROJECTS.....\$5.75.** Helps the reader to put projects together from standard circuit blocks with a minimum of trial and error.
- BP122—AUDIO AMPLIFIER CONSTRUCTION.....\$5.75.** Construction details for preamps and power amplifiers up through a 100-watt DC-coupled FED amplifier.
- BP92—CRYSTAL SET CONSTRUCTION.....\$5.00.** Everything you need to know about building crystal radio receivers.
- BP45—PROJECTS IN OPTOELECTRONICS.....\$5.00.** Includes infra-red detectors, transmitters, modulated light transmission and photographic applications.
- BP48—ELECTRONIC PROJECTS FOR BEGINNERS.....\$5.00.** A wide range of easily completed projects for the beginner. Includes some no-soldering projects.
- BP49—POPULAR ELECTRONIC PROJECTS.....\$5.50.** Radio, audio, household and test equipment projects are all included.
- BP51—ELECTRONIC MUSIC AND CREATIVE TAPE RECORDING.....\$5.50.** Shows how you can make electronic music at home with the simplest and most inexpensive equipment.
- BP56—ELECTRONIC SECURITY DEVICES.....\$5.00.** Includes both simple and more sophisticated burglar alarm circuits using light, infra-red, and ultrasonics.
- BP59—SECOND BOOK OF CMOS IC PROJECTS.....\$5.00.** More circuits showing CMOS applications. Most are of a fairly simple design.
- BP72—A MICROPROCESSOR PRIMER.....\$5.00.** We start by designing a small computer and show how we can overcome its shortcomings.
- BP74—ELECTRONIC MUSIC PROJECTS.....\$5.95.** Provides the experimenter with a variety of practical circuits including a Fuzz Box, Sustain Unit, Reverberation Unit, Tremelo Generator and more.
- BP91—AN INTRODUCTION TO RADIO DXING.....\$5.00.** How you can tune in on those amateur and commercial broadcasts from around the world in the comfort of your home.
- BP94—ELECTRONIC PROJECTS FOR CARS AND BOATS.....\$5.00.** Fifteen simple projects that you can use with your car or boat. All are designed to operate from 12-volt DC supplies.

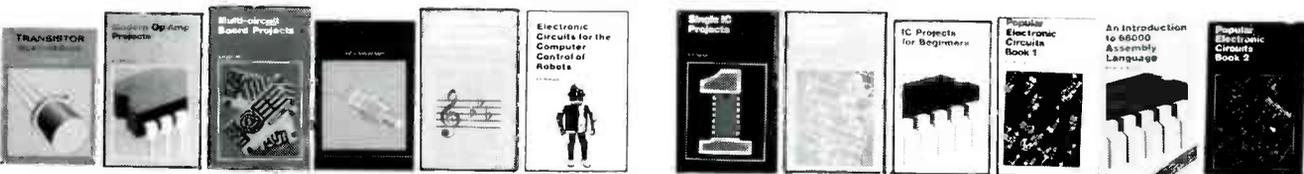

ELECTRONIC TECHNOLOGY TODAY INC.
P.O. Box 240, Massapequa Park, NY 11762-0240

Name _____
Address _____
City _____ State _____ Zip _____

SHIPPING CHARGES IN
USA & CANADA
\$0.01 to \$5.00 . . . \$1.00
\$5.01 to \$10.00 . . . \$1.75
\$10.01 to 20.00 . . . \$2.75
\$20.01 to 30.00 . . . \$3.75
\$30.01 to 40.00 . . . \$4.75
\$40.01 to 50.00 . . . \$5.75
\$50.01 and above . \$7.00

**SORRY No orders accepted
outside of USA & Canada**

Number of books ordered

Total price of merchandise \$ _____
Sales Tax (New York State Residents only) \$ _____
Shipping (see chart) \$ _____
All payments must be in U.S. funds
Total Enclosed . . . \$ _____

R1-88

SCOPE 3½ Digital Multimeters



Model DVM-638
\$8750

- Test leads included
- 11 function, 38 ranges
- Logic level detector
- Audible visual continuity
- Capacitance and conductance measurement

Model DVM-636
\$6750

- 8 function, 37 ranges
- Capacitance measurement

SCOPE 3½ Digit Capacitance Meter



Model DCM-602
\$5995

- Test leads included
- 8 ranges with full scale values to 2000 uF
- LSI circuit
- Crystal time base
- Frequency range 800 Hz to 8Hz

SCOPE Pocket Sized Audio Signal Generator



Model RC-555
\$5995

- Test leads & 9V battery included
- Low distortion sine-wave signal
- 46 step selected frequency
- x1 range 20 Hz to 1.5 KHz
- x100 range 2 KHz to 150 KHz

SCOPE 4½ Digit LCD Bench Digital Multimeter



Model DVM-6005
\$21995

- Test lead set 6, "D" size batteries included
- 0.4" high characters
- Conversion period: 500 milliseconds
- Automatic, negative polarity

Mini-Meters with Maxi-Specs

SCOPE 3½ Digit LCD with 8 Full Functions

Model DVM-632

\$4495
OUR PRICE

Measures only 5 3/8" x 2 13/16" x 1 1/4"

- Deluxe test leads included
- 0.5% accuracy
- Transistor gain test
- Audible continuity checking & diode test
- 10 Amp measurement

Zipped Carrying Case CC-30 **\$450**



SCOPE 3½ Digit LCD

Measures only 5" x 2 3/4" x 7/8"



Model DVM-630

\$2995

- OUR PRICE
- Test leads included
 - 0.5% accuracy
 - 6 functions, 19 ranges
 - Automatic zero adjust
 - Low battery indication

Zipped Carrying Case CC-30 **\$450**

ASK FOR FREE CATALOG.

Money orders, checks accepted. C.O.D.'s require 25% deposit.



Fordham

260 Motor Parkway, Hauppauge, NY 11788

Toll Free **800-645-9518**
In NY State **800-832-1446**

Service & Shipping Charge Schedule Continental U.S.A.

FOR ORDERS	ADD
\$25-\$100	\$4.50
\$101-\$250	\$6.00
\$251-500	\$8.00
\$501-750	\$10.50
\$751-1,000	\$12.50
\$1,001-1500	\$16.50
\$1,501-2000	\$20.00
\$2,001 and up	\$25.00